

KLIPSCH • BASS REPRODUCTION • VILLCHUR

OCTOBER 1957

Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor

How to Improve
Record Tracking

•

Understanding
Flyback Systems

•

Control Unit—
Preamplifier

•

The Cardmatic
Tube Tester


•

Audio Service
As a Business ▶

(See page 43)

35c


U.S. and Canada

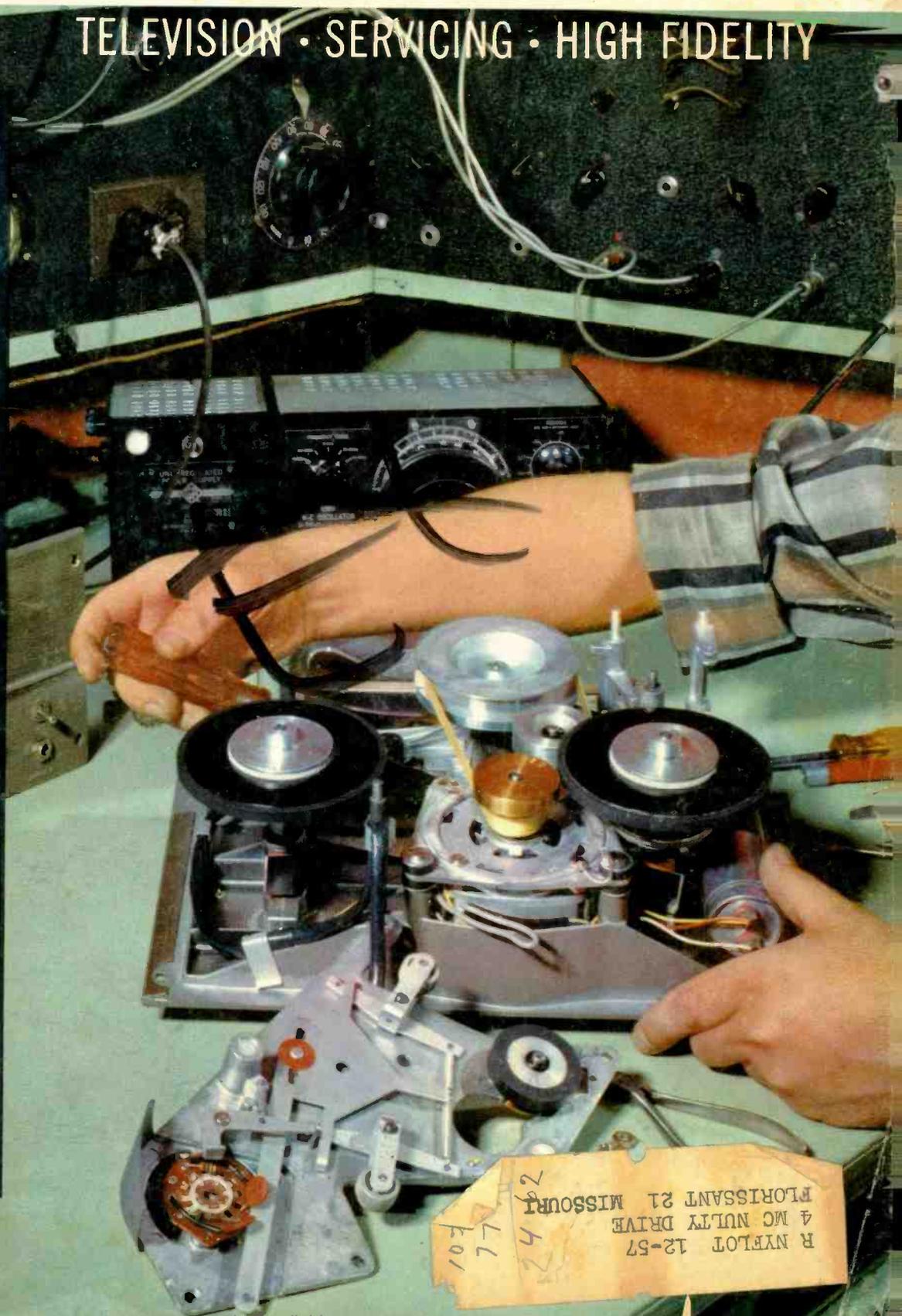

R NYELOT 12-57
4 MC NULTY DRIVE
FLORISSANT 21 MISSOURI
77
2462
K01

triple news

from triplett

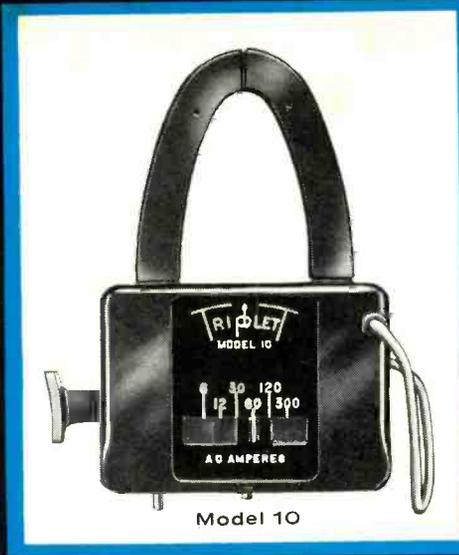

Here is a real value—much more value than in any other clamp-on ammeter. Remember, in Triplet Model 100 you get not only a clamp-on ammeter but a genuine Triplet complete Volt-Ohm-Milliammeter with which you can measure AC volts, DC volts, AC and DC current, and Ohms.

BURTON BROWNE ADVERTISING

1st news: Triplet Model 10 Clamp-On Adapter

Just plug into any Triplet Model 310 Miniature VOM it becomes an AC clamp-on ammeter to measure AC amperes without cutting or opening current carrying wires. The split transformer yoke opens at the touch of a lever to fit around a single conductor or bus-bar for direct readings of AC amperes from 6 to 300 in 6 steps. Model 10 \$14.50 net.

The Model 10 can be separated from the Model 310 as shown in the drawing at left by No. 311 lead attachment. This permits readings in difficult locations. No. 311 leads \$1.90 net.

2nd news: Triplet Model 101 Line Separator

Serves to plug in at outlet to divide 2 conductor cords for clamp-on measuring. Makes accurate, rapid-testing of radio and TV sets; phonographs, appliances, motors, etc. possible without opening or splitting double conductors. Also serves to increase ammeter sensitivity 10X and 20X, if desirable, for easier reading. Model 101 \$5.50 net.

3rd news: All four parts are available conveniently packaged in one handy, durable, high-quality carrying case. This complete package is known as Triplet Model 100 and is priced at \$61.90 net.

Model 100 consists of Model 310 VOM, Model 10 Clamp-On Adapter, Model 101 Line Separator, No. 311 leads and carrying case with provision for all parts.



Triplet Electrical
Instrument Company
Bluffton, Ohio

53 years of experience

In addition, to use with the Model 310, the Model 10 Adapter also can be used as a Clamp-On Ammeter with any Volt-Ohm-Milliammeter having a 3 AC volt scale at 5000 Ohms per volt such as Triplet Models 630, 630-A, 630-NA, 631, etc., by employing Triplet No. 611 leads, \$1.90 net.

Triplet Model 100 gives you the world's most flexible test equipment for all electrical and electronic applications.



631



630-NA



630



630-A



310



630-T



666-HH




625-NA



666-R

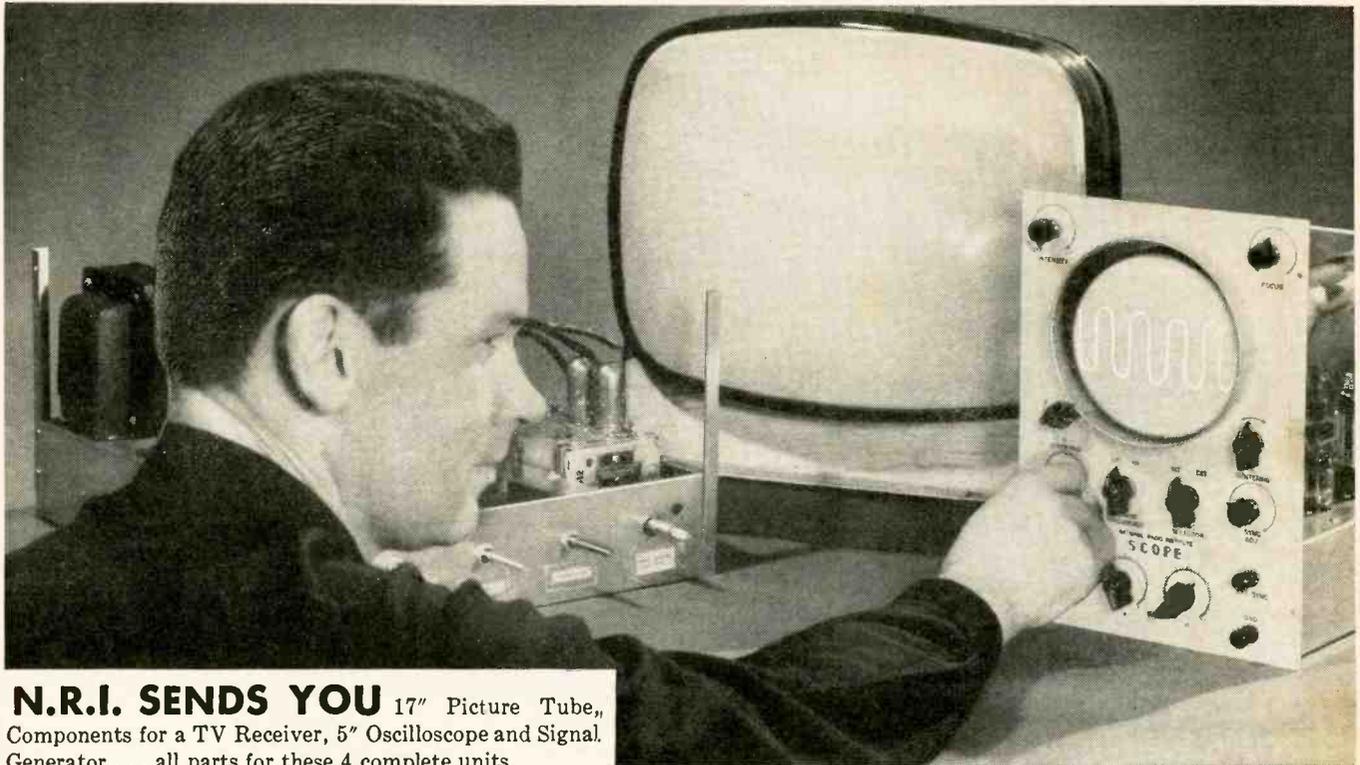Learn to be a PROFESSIONAL TV Technician AT HOME



N.R.I. SENDS YOU 17" Picture Tube, Components for a TV Receiver, 5" Oscilloscope and Signal Generator . . . all parts for these 4 complete units.

N.R.I. All-Practice Method Trains You in Spare Time to Fix TV Sets Quickly, Correctly, with Confidence

How many times have you day-dreamed of being your own boss? Or thought about what you could do if you were the man who made the decisions. The man who knows the answers—the well trained Technician—enjoys the prestige, gets the better jobs, higher pay.

It's time to stop dreaming. Here is the learn-by-practice training that shows you the way to be the boss, to earn top pay. Television Servicing needs well trained men.

Yes, if you have a basic knowledge of radio and electronics you can make *some* Television repairs *some* of the time. You can make some simply by trial and error. But sooner or later you will face Television Service problems you cannot solve. All the diagrams in the world won't help you then. And you can't get the training you need while customers wait.

NRI Is Oldest and Largest Home Study Radio-TV School

Forty years experience, and the record and reputation of NRI, back up this learn-by-doing Professional TV Servicing course. Instead of reading about TV problems, you build and conduct experiments on circuits in a TV receiver. Because you learn methods, "tricks of the trade" used and proved

by top TV Servicemen, you recognize and repair defects quickly and accurately. Learn to fix any set . . . any make, any model . . . with confidence. Earn a Diploma that certifies to your training.

Television is Forging Ahead with More Sets, More Color, Hi-Fi

TV Servicing has only started to grow in importance. New sets, portables, color TV, constant changes, improvements make this a genuine "gold rush" for the man who is trained and ready. Know . . . so you can get ahead. Learning how to build and use a professional-type 5" Oscilloscope is part

of the practice you get in this NRI All-Practice Training. Installing front-end channel selector strips, distinguishing between faulty blocking oscillator or a defect in the sync circuit, etc., are just a few of the important TV Servicing facts you learn through practice.

Not for beginners

Here is a course for men who know basic theory, either from Radio or TV Servicing experience or planned training, but realize the need for more knowledge to be able to forge ahead. Get details of this course now. Mail coupon today. Address: National Radio Institute, Dept. 7KFT, Washington 16, D.C.



Send for FREE BOOK →

NATIONAL RADIO INSTITUTE

Dept. 7KFT, Washington 16, D. C.

Please send FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name..... Age.....

Address.....

City..... Zone..... State.....

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

Radio-Electronics

Formerly RADIO CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION*

EDITORIAL

35 High-Fidelity Sound—Hugo Gernsback

AUDIO—HIGH FIDELITY

- 36 All-Transistor Tape-Head Preamp—Francis A. Gicca
- 38 Bass Reproduction in Loudspeakers—Edgar Villechur
- 40 Record Tracking—Norman H. Crowhurst
- 43 Audio Specialists—(Cover Feature)
- 44 Loudspeakers and Acoustic Fundamentals—Paul W. Klipsch
- 45 Hi-Fi Master Control Unit—Joseph Marshall
- 49 Design Calculations for R-C-Coupled Amplifiers—Herbert Ravenswood
- 146 New Records—Monitor

TECHNICAL REPORTS

52 Pictorial Report of New Developments

TEST INSTRUMENTS

- 53 Automation and the Tube Tester—Harold B. McKay
- 55 TV Bar Generator for Your Service Kit—Edwin Bohr
- 58 Impact Noise Meter Uses 3 Transistors—Nathaniel Rhita
- 59 Build This Amplifier-Rectifier Vtm for Audio Testing—L. B. Hedge
- 61 Regulating Bias and Polarizing Voltages—Ronald L. Ives

ELECTRONICS

- 62 Electronic Surveillance Kit (Part II)—Louis E. Garner, Jr.
- 64 A Photo-Sound Unit—Peter J. Vogelgesang
- 82 Two Channels? Easy—E. L. Safford, Jr.
- 84 Sensitive Relay Saves Standby Power—Rod Driver

RADIO

- 89 Multiplexing and You—Don Lewis
- 93 500-Million-Mc Transceiver—Harold Pallatz
- 95 Transistor Low-Voltage Supply—I. Queen

TELEVISION

- 100 Death Rides the Hot Chassis—Fred Shunaman
- 116 Practical Color Installation (Part II)—Robert G. Middleton
- 124 TV Service Clinic—Conducted by Robert G. Middleton
- 132 Flyback Systems—Jesse Dines
- 174 Books
- 168 Business and People
- 99 Corrections
- 16 Correspondence
- 139 New Devices
- 6 News Briefs
- 155 New Tubes and Semiconductors
- 158 Patents
- 164 Radio-Electronic Circuits
- 172 Technical Literature
- 152 Technicians' News
- 150 Technotes
- 161 Try This One
- 99 35 Years ago

ON THE COVER

(Story on page 43)

Tape-recorder repair in progress on a typical service bench at the Sigma Electric Co., New York City, specialists in repair of high-fidelity equipment.

Anso color original by Tom Carew

- Hugo Gernsback Editor and Publisher
- M. Harvey Gernsback Editorial Director
- Fred Shunaman Managing Editor
- Robert F. Scott W2PWG, Technical Editor
- Larry Steckler Assistant Editor
- I. Queen Editorial Associate
- Robert G. Middleton Television Consultant
- Elizabeth Stalcup Production Manager
- Cathy Cocozza Advertising Production
- Wm. Lyon McLaughlin Tech. Illustration Director
- Sol Ehrlich Art Director
- Fred Neinst Staff Artist
- Lee Robinson General Manager
- John J. Lamson Sales Manager
- G. Aliquo Circulation Manager
- Adam J. Smith Director, Newsstand Sales
- Robert Fallath Promotion Manager



Average Paid Circulation Over 195,000

Associate Member Institute of High Fidelity Mfrs., Inc.

RADIO-ELECTRONICS, October, 1957, Vol. XXVIII, No. 10. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1957 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U. S., U. S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$9.00 for three years; single copies 35c. Pan-American countries \$4.50 for one year; \$8.00 for two years; \$10.50 for three years. All other countries \$5.00 a year; \$9.00 for two years; \$12.00 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14th St., New York 11, N. Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive Editorial and Advertising Offices, 154 West 14th St., New York 11, N. Y. Telephone Algonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.
BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 177.
POSTMASTER: If undeliverable, send Form 3578 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N. Y.

*Trademark registered U. S. Pat. Offic.

RADIO-ELECTRONICS

Get into

TELEVISION RADIO-ELECTRONICS

Let National Schools of Los Angeles, a Practical Resident Technical School for over 50 years, train you at home by Shop-Method for unlimited opportunities in All phases of TV, Electronics, Radio.



LEARN ALL 8 PHASES OF THE INDUSTRY BY SHOP METHOD HOME TRAINING

1. Television . . . including Color TV
2. Radio . . . AM, FM
3. Industrial Electronics
4. Communications
5. Sound Recording & Hi-Fidelity
6. Automation
7. FCC License
8. Radar & Micro Waves

We give you parts to build a modern TV set . . . all tubes plus large screen Picture Tube . . . and a Superhet Receiver. You also receive a Professional Multitester

You get 19 Big Kits
... all this newest, practical equipment.

**GOOD JOBS . . . MORE MONEY
SECURITY . . . ALL CAN BE YOURS!**

You are needed in the great modern Television-Electronics industry. Trained technicians are in growing demand, at excellent pay, in sales and service, manufacturing, broadcasting, telecasting, communications, research, and many other important branches of the field. National Schools Master Shop-Method Training, with newly added lessons and equipment prepares you *in your spare time*, right in your own home, for these fascinating opportunities.

YOU EARN WHILE YOU LEARN

Many students pay for their entire training—with spare time earning. We'll show you how you can, too! You receive material that shows you how to earn extra money servicing TV and Radio receivers, appliances, and doing many other profitable jobs.

YOU GET EVERYTHING YOU NEED

Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects—consultation privilege with our qualified staff.

*Don't delay your future another day.
Send coupon for full information TODAY.*

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school—and part time job while you learn. Check box in coupon for full information.



Approved for GI Training

NATIONAL SCHOOLS
LOS ANGELES 37, CALIF.

CUT OUT ALONG THIS LINE

MAIL POSTAGE—FREE COUPON . . . NOW!

1. Fill out coupon in ink.
2. Cut along dotted line and fold coupon.
3. Staple, paste, glue, or tape ends together.
4. Mail today! No postage necessary.

FREE! Career Book in TV-Radio-Electronics, PLUS actual SAMPLE LESSON. No obligation; no salesman will call.



Name _____ Age _____
 Address _____
 City _____ Zone _____ State _____
 Check if interested ONLY in Resident Training in Los Angeles
 VETERANS: Give date of discharge _____

FOLD ALONG THIS LINE

Postage Will be Paid by Addressee


No Postage Stamp Necessary if Mailed in the United States

BUSINESS REPLY CARD
First Class Permit No. 3087, Sec. 34.9 P.L. & R., Los Angeles, Calif.

POSTAGE WILL BE PAID BY
NATIONAL SCHOOLS
 4000 South Figueroa Street
 Los Angeles 37, California

RG-107

IT'S **Blue Chip**
Quality

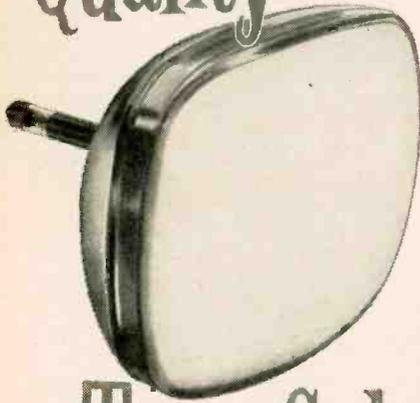


IT'S **Tung-Sol**
Quality



Tung-Sol receiving tubes for TV, radio and Hi-Fi replacement are exactly the same as those supplied to leading independent set makers. This one fine quality is your assurance of long, trouble-free service that keeps customers with you year after year. Tell your supplier you'd rather have Tung-Sol Tubes. TUNG-SOL ELECTRIC INC., Newark 4, N. J.

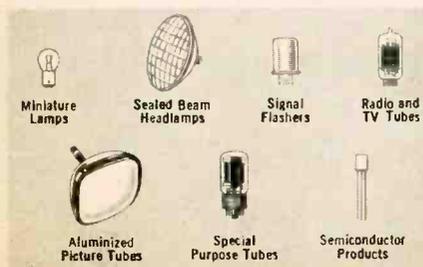TUNG-SOL
MAGIC MIRROR ALUMINIZED
PICTURE TUBES
RECEIVING TUBES



News Briefs



DR. IRVING LANGMUIR, one of America's great scientists, died Aug. 16, 1957. He was 76 years old. Dr. Langmuir was known best in the electronics field for his work on high-vacuum tubes and his invention of the mercury-vapor



pump, which made high vacuums possible. His specialty was, however, chemistry rather than electronics, and he taught chemistry at Stevens Institute of Technology until 1909, when he joined the staff of the General Electric research laboratory, where he remained until his retirement in 1950.


Early in his career at the laboratory, he developed the gas-filled lamp as an outgrowth of a "study of bad vacuums" on which he embarked, he said, because engineers were having trouble producing good vacuums. It was found that certain gases prolonged the life of the lamp rather than shortened it, and as a result it is said that he saved the American public nearly a billion dollars a year in electric-light bills.

His researches in oil films—which opened up the new field of two-dimensional or surface chemistry—made him the first American chemist to receive the Nobel Prize, which was awarded him in 1932. In later years his work—in connection with that of other G-E scientists—on artificial precipitation and cloud seeding may result in a measure of weather control which may ultimately prove more important than any of his other accomplishments.

Dr. Langmuir was a lifelong advocate of scientific investigation along the lines from which most knowledge could be gained, rather than with a particular application in view. He referred to this approach as the art of *serendipity*, which Webster defines as "the gift of finding valuable things not sought for," and stated of his work that "whatever has come in industrial applications has come incidentally from experiments followed for their interest alone."

Dr. Langmuir was a member of a large number of learned societies and received American and foreign awards and medals too numerous to list here. His wife, son Kenneth and daughter Barbara, all of Schenectady, N. Y., survive him.

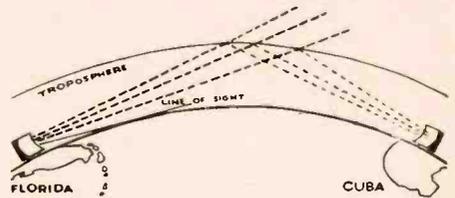OVER-THE-HORIZON communications link just completed between Florida and Cuba utilizes tropospheric scatter propagation for the 185-mile hop. The microwave beam (on the 692-880-mc band) is aimed slightly upward and portions of the signal scatter in the troposphere and are picked up by high-sensitivity receiving antennas. (See RADIO-ELECTRONICS, August, 1955, page



39, and September, 1956, page 37.) The Federal Telecommunications Laboratories' broad-band technique is used to provide a television path and 100 telephone channels. The Florida-Cuba link (both ends can send and receive) will be jointly operated by International Telephone & Telegraph and the American Telephone & Telegraph Co.

THREE-DIMENSIONAL COLOR TV system for remote servicing of reactors used in development of a nuclear aircraft propulsion system has been announced by General Electric. The closed-circuit system permits use of color-coded parts in reactor components and provides the degree of precise depth perception required for their correct positioning.

In use, the television camera is positioned inside the radioactive area. The camera is equipped with a dual optical system having a perspective similar to that of the observer's eyes. A rotating shutter in the special color TV camera alternately transmits the scene as viewed from the two points to the camera's tube. In the viewing console, light from the image formed on the cathode-ray tube passes through a drum composed of alternate segments of polarizing filters with axes of polarization at right angles to each other. This drum revolves in sync with the TV frame rate of the camera (90 per second) and polarizes alternate frames vertically and horizontally. Thus all left-eye pictures are polarized in one
(Continued on page 10)

This may be Your
PASSPORT
to a more
SECURE FUTURE

MAIL COUPON TODAY!

DeVry Technical Institute
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-10-N
Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed below.

Name _____ Age _____
Please Print

Street _____ Apt. _____

City _____ Zone _____ State _____

Check here if subject to military training.

DeVry Tech's Canadian Training Center is located
at 626 Roselawn Avenue, Toronto 12, Ontario
2025

Men 17-55...

Prepare at Home for an Interesting and Profitable Future in the Great Fields of

ELECTRONICS

as used in

GUIDED MISSILES, ETC.

There are big opportunities for men 17 to 55 in the exciting, profitable fields of Electronics. For more than 26 years we have been preparing men in their spare time at home without interfering with their jobs. During these years, to name a few, we have trained laborers, farmers, clerks, factory workers and salesmen . . . following the same basic method used in our Chicago and Toronto training laboratories. So regardless of your experience, why don't you write for FREE facts today? There is no obligation.

Live-Wire Employment Service

DeVry Tech's Placement Department is in contact with some of the best-known employers in the Electronics field. The service is free to all graduates—and DeVry Tech's record in helping to place men has been outstanding.

AN INDEX TO A BETTER JOB, A BRIGHTER FUTURE

- Communications • Radar
- Television • Micro-Waves
- Radio • Industrial Electronics
- Computers • Automation Electronics

NO ADVANCED EDUCATION OR PREVIOUS TECHNICAL EXPERIENCE NEEDED!

Draft Age?

We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.



FREE Booklet!

We'll give you a free copy of an interesting booklet, "Electronics and YOU." See for yourself how you may take advantage of the opportunities in this fast-growing field.



Accredited Member of National Home Study Council

"One of North America's Foremost Electronics Training Centers!"



DeVRY TECHNICAL INSTITUTE

Formerly DeFOREST'S TRAINING, INC.

**4141 BELMONT AVE.
CHICAGO 41, ILLINOIS**

Your Independent Service Advertising Program expands with your purchases of CBS tubes

One of a new series of full-page ads appearing in TV GUIDE



This family cook is your independent service-dealer. He's that busy neighbor who somehow finds time to be scoutmaster of his son's troop. He has his radio and TV service business in your town . . . and he knows he'll stay in business there only as long as he does superior work. In fact, when he works for you, he bets his family's bread and butter he'll do a better job . . . and he will.

for your radio and TV repairs, call the man who cares . . . your
INDEPENDENT SERVICE-DEALER

He actually bets his family's bread and butter he'll do a better job for you . . . his business success depends upon it.

He is a highly skilled technician, trained and equipped to service promptly *all makes* of radio and TV sets at a fair price. So next time your radio or TV needs repairs, call the man who cares. Call your *independent* service-dealer.



For the best in entertainment tune to CBS.

Look for this emblem . . .



Whenever your set needs a new tube, ask to have it replaced with a CBS tube. There are no better tubes made.

©CBS-HYTRON, Danvers, Mass.
A Division of Columbia Broadcasting System, Inc.

We know you like your Independent Service Program and want it expanded. We know it from a nation-wide survey . . . and from your increasing purchases of CBS tubes. May we remind you: each time you buy CBS tubes, you support your own independent service-dealer campaign. Keep it going . . . keep it growing . . . always specify CBS tubes.

SUPPORTING MATERIAL ALSO EXPANDS



- "The Independent Service Business and Your Future" booklet
- Independent Service decal
- 10 new postal cards
- 16 new advertising mats
- Radio and television scripts
- Consumer booklet "On the Care of a Television Set"

Ask your CBS Tube distributor for this tie-in material . . . or write for illustrated broadside PA-181.



CBS-HYTRON— Danvers, Massachusetts
A Division of
Columbia Broadcasting System, Inc.

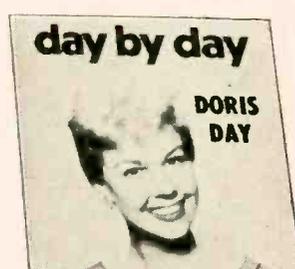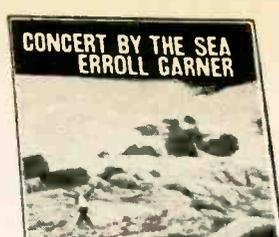FOR THE BEST IN ENTERTAINMENT TUNE TO CBS



CHOOSE ANY 3 OF THESE HIGH-FIDELITY COLUMBIA LP RECORDS

FREE

when you join the Columbia LP Record Club—and agree to purchase 4 selections during the coming 12 months

YES! You may have, FREE, ANY 3 of these best-selling 12" Columbia LP records. We make this unique offer to introduce you to the money-saving program of the Columbia LP Record Club . . . a program that selects for you each month the greatest works in every field of music—performed by the world's finest artists, brilliantly reproduced on Columbia LP records.

HOW THE CLUB OPERATES: To enjoy the Club's benefits—mail the coupon, indicating which one of the four Club Divisions best suits your musical taste: Classical; Jazz; Listening and Dancing; Broadway, Movies, Television and Musical Comedies.

Each month you will receive free the Club Magazine which describes the current selections in all four Divisions. You may accept or reject the monthly selection for your Division . . . or you may take records from other Club Divisions . . . thereby assuring you the widest possible choice of recorded entertainment. Or you may tell us to send you NO record in any month.

Your only obligation is to purchase four selections from the more than 100 that will be offered during the next 12 months. The records you want are mailed and billed to you at only \$3.98 (original cast Musical Shows somewhat higher), plus a small mailing charge.

FREE BONUS RECORDS GIVEN REGULARLY: The 3 records sent to you now represent an "advance" of the Club's bonus system—given to you at once. After you have fulfilled your membership obligation by purchasing four records, you will receive an additional free Bonus record of your choice for every two additional Club selections you accept. Bonus records are superb 12" Columbia LP records—the very best of the Columbia LP catalog—just like those shown here.

Indicate on the coupon which 3 records you want free, and the Division you prefer. Then mail the coupon at once. You must be delighted with membership or you may cancel it by returning the free records within 10 days.

COLUMBIA LP RECORD CLUB
Terre Haute, Indiana

FREE—ANY 3—VALUE UP TO \$12.94—MAIL ENTIRE COUPON NOW!

COLUMBIA LP RECORD CLUB,
Dept. 237, Terre Haute, Ind.

Please send me as my FREE gift the 3 records indicated here: (Select the records you want by circling 3 numbers in the list at the right)

. . . and enroll me in the following Division of the Club:

(check one box only)

- Classical Listening and Dancing
 Broadway, Movies, Television Jazz
 Musical Comedies

Each month you will send me the Columbia LP Record Club Magazine which describes the records offered in all four Club Divisions. I have the privilege of accepting the monthly selection in the Division checked above, or any other selection described, or none at all. My only obligation is to purchase four records in the next 12 months at the regular list price plus a small mailing charge. After accepting four records, I will receive a free Bonus record for every two additional records I purchase. If not delighted with membership, I may cancel within 10 days by returning all records.

Name (Please Print).....
Address.....
City..... Zone..... State.....

CANADA: Prices slightly higher. Address 11-13 Soho St., Toronto 2B 78

If you wish to have this membership credited to an established Columbia Records dealer, authorized to accept subscriptions, please fill in the dealer's name and address:

CIRCLE THE NUMBERS OF THE 3 RECORDS YOU WANT

- Beethoven: "Moonlight" Sonata; "Pathétique" Sonata; "Appassionata" Sonata. Rudolf Serkin, piano.
- The Voice. Frank Sinatra in 12 songs that first made him famous—*Lover, Fools Rush In*, etc.
- King of Swing: Vol. 1 Benny Goodman and Original Orch., Trio, Quartet. *Ridin' High, Moonglow*—9 more.
- My Fair Lady. Original Broadway Cast recording with Rex Harrison and Julie Andrews. The complete score including *The Rain in Spain, I Could Have Danced All Night*—14 more.
- The Great Melodies of Tchaikovsky. Philadelphia Orch., Ormandy, conductor. 8 memorable selections.
- Moonlight Becomes You. Here's mood music in Hi-Fi—Paul Weston and his Music from Hollywood, 12 songs.
- Ellington Uptown. Duke Ellington and Orchestra perform *Skin Deep, The Mooche, Perdido*—2 more.
- Levant Plays Gershwin. 3 works—*Rhapsody in Blue; Concerto in F; An American in Paris*.
- Day By Day. Doris Day sings 12 popular songs—including *The Song Is You, Autumn Leaves*, etc.
- Rimsky-Korsakov: *Scheherazade*. Philadelphia Orch., Ormandy conductor. A superb performance of this exotic score.
- Music of Jerome Kern. Andre Kostelanetz and his Orchestra play 20 Kern favorites.
- Concert by the Sea. Erroll Garner in an actual jazz performance at Carmel, Calif. *Teach Me Tonight, Where or When, I'll Remember April*—8 more.

Dealer's Name.....
Dealer's Address..... PA-1

© "Columbia" LP, ® Marcos Reg.

OCTOBER, 1957

direction and all right-eye pictures in the other.

An observer, wearing polarized glasses, sees the left optical path with his left eye and the right optical path with the right. The effective 45-frame-per-second rate gives him stereovision without an objectionable flicker.

The system is described as "currently not feasible for the American living-room" but is suited for adoption to other closed-circuit TV uses.

SIGNAL ENHANCEMENT, a technique which increases the effective power and range of radar in extremely large amounts, may give greatly increased protection against long-range guided missiles and bombers. Details are highly classified and all that has been released is that the discovery is a method of signal enhancement using frequency-modulation continuous-wave propagation. Announced by the United States Air Force and Columbia University, the new system does not increase the power used, but instead raises the strength of the reflected radar signal, compared to background noise received.

TWO NEW TV STATIONS began telecasting since our last issue:


- WPST-TV, Miami, Fla.....10
- KTVG, Ensign, Cimarron, Kans.....6
- KVVG, Tulare-Fresno, Calif., Channel 27, has dropped out.

WUTV, Charlotte, N. C., channel 36, changed to its new call letters from WQMC.

We now have 503 operating U. S. stations (413 vhf and 90 uhf), 25 of which are noncommercial (6 uhf).

THERMO-COMPRESSION, a new technique for attaching leads to semiconductors, uses heat and pressure to form a bond between various soft metals and clean, single-crystal semiconductor surfaces. The bond formed by this process is stronger than the lead itself. Developed by Bell Telephone Laboratories, two methods of forming such a bond are shown in the diagram. One uses a heated wedge to press the wire lead against the heated semiconductor with sufficient

(Continued on page 14)

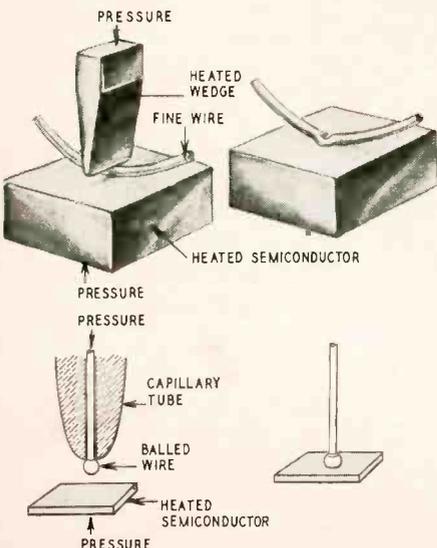

How to Pass

An FCC License can be

Get Your FCC License

We Guarantee
to train you until you receive
Your FCC License

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial FCC License with a radar endorsement. Completion of Section I only of the Master Course will prepare you for a Second Class Commercial FCC License. We guarantee to train and coach you, without any additional cost, until you receive the FCC License as indicated above. This guarantee is valid for the entire period of your enrollment agreement.

Cleveland Institute Training Results in success with commercial FCC examinations . . . easily . . . and quickly.

every month our trainees get jobs like these:



Boyd Daugherty:

"I recently secured a position as Test Engineer with Melpar, Inc. A substantial salary increase was involved. My Cleveland Institute training played a major role in qualifying me for this position."

Boyd Daugherty
105 Goodwin Ct., Apt. C
Falls Church, Va.

Top Grade Employers Like These Look

- Bendix Radio:** "We shall look forward to receiving completed applications from your students."
- Philco:** "We have employed a great number of well qualified electronics personnel who were graduates of Cleveland Institute."
- Westinghouse:** "We would appreciate your listing our current openings in your monthly Job Opportunities."

(Commercial)

FCC License Exams

your Guarantee of Success in Electronics

in a Minimum of Time

mail
coupon
NOW!

here's proof . . .

| Name and Address | License | Time |
|------------------------------------|---------|----------|
| Walter Eggers, Pacific Grove | 1st | 12 weeks |
| Paul Reichert, West Salem, Ohio | 2nd | 10 weeks |
| Harold Phipps, La Porte, Indiana | 1st | 28 weeks |
| John H. Johnson, Boise City, Okla. | 2nd | 12 weeks |
| James Faint, Johnstown, Pa. | 1st | 26 weeks |

Get Both FREE



James Glen:



When Jim enrolled, he was a temporary employee of the City of Tacoma, Washington. In the space of 14 months, he completed the Master Course and received his first class license. He is now installing and maintaining mobile and microwave equipment.

*James S. Glen, Jr.
2920 Knob Hill Road
Tacoma, Washington*

Accredited by National Home Study Council

Cleveland Institute of Radio Electronics

Desk RE-10, 4900 Euclid Ave., Cleveland 3, Ohio



Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name Age.....

Address

City Zone..... State.....

Special Tuition Rates to Members of Armed Forces Desk RE-10

To Cleveland Institute

Aerojet-General
American Airlines
American Telephone & Telegraph Co.
Bendix Radio
Braniff Airways
Burroughs Corp.
Capital Airlines
Continental
Air Lines, Inc.
Convair
General Electric
Glenn L. Martin Co.

Goodyear Atomic Corp.
IBM
International Telephone & Telegraph Co.
Mohawk Airlines
Motorola
North American Aviation, Inc.
Northwest Airlines
Philco
RCA
Ryan Aeronautical Co.
**Plus many others*

Sylvania TV Damper Tubes



...New design plus



New heater-cathode design helps Sylvania damper types pass this dynamic arc test with flying colors. Dynamic tests such as this have now been instituted by Sylvania on all important types in every

critical TV function. It's Sylvania's way of helping you overcome problems which often make the difference between profit and loss and a happy or unhappy customer.



new dynamic tests produce high E.L.A.*

Sylvania damper tubes scored an **Earned Life Average* of 99.54% in a recent test of types in the 6AX4GT family. This means greater service reliability for you with an absolute minimum of trouble resulting from arcing, heater-cathode shorts and heater burnouts. It's the result of a new heater-cathode design introduced by Sylvania to meet your service needs.

Earned Life Average is an established method for evaluating tube life performance; for the service industry it serves as an index of protection against call-backs. These tests

were performed in TV sets which simulated field service conditions where high line voltages are encountered.

109 Sylvania damper tubes performed for a total of 132,890 hours out of a possible 133,500 hours for an *Earned Life Average* of 99.54%.

To Sylvania this is satisfying evidence that the service industry has been provided with extra protection against the most common damper tube troubles. We think you'll agree too, that in the long run you'll profit more with Sylvania.



SYLVANIA

SYLVANIA ELECTRIC PRODUCTS INC.
1740 Broadway, New York 19, N. Y.
In Canada: Sylvania Electric (Canada) Ltd.
University Tower Bldg., Montreal

pressure to cause a slight deformation of the lead. Another useful connection is made by butting the balled (or headed) end of a wire against the heated semiconductor with a capillary tube. Temperatures of 200° to 300°C and pressures of 5,000 to 10,000 pounds per square inch are required by the process. These are not high enough to affect the electrical properties of the semiconductor material.

Calendar of Events

- Society of Motion Picture & Television Engineers Convention, Oct. 6-11, Hotel Statler, New York.
- National Electronics Conference, Oct. 7-9, Hotel Sherman, Chicago.
- Fall General Meeting of American Institute of Electrical Engineers, Oct. 7-11, Morrison Hotel, Chicago.
- New York High-Fidelity Show, Oct. 7-12, New York Trade Show Building, New York N. Y. (Annual Convention of the Audio Engineering Society will be held in conjunction with the show Oct. 9-12.) RADIO ELECTRONICS will exhibit in Room 526.)
- Canadian IRE Show, Oct. 16-18, Automotive Building, Exhibition Park, Toronto, Ont., Canada.
- New England High-Fidelity Music Show, Oct. 18-20, Hotel Touraine, Boston, Mass.
- High Fidelity Show, Oct. 18-20, McAllister Hotel, Miami, Fla.
- Ninth Regional NEDA Seminar, Oct. 20-22, Grossinger's Hotel, Grossinger, N. Y.
- Fourth Annual Computer Applications Symposium, Oct. 24-25, Hotel Sherman, Chicago.
- Fall Hi-Fi Festival, Oct. 26-27, Kansas Conservatory of Music, Kansas City, Mo.
- Technical Conference of IRE Professional Group on Electron Devices, Oct. 31-Nov. 1, Shoreham Hotel, Washington, D. C.
- High Fidelity Music Show, Nov. 1-3, Hotel Multnomah, Portland, Ore.
- International Congress and Exhibition of Measuring Instrumentation and Automation (Interkama 1957), Nov. 2-10, Düsseldorf, Germany.
- Puerto Rico Hi-Fi Show, Nov. 8-10 Normandie Hotel, San Juan, P. R.
- High-Fidelity Music Show, Nov. 8-10, New Washington Hotel, Seattle, Wash.
- Third Annual IRE Instrumentation Conference, Nov. 11-13, Biltmore Hotel, Atlanta, Ga.
- EIA (RETMA) Radio Fall Meeting, Nov. 11-13, King Edward Hotel, Toronto, Canada.
- New England Radio-Electronics Meeting, Nov. 15-16, Mechanics Hall, Boston, Mass.
- High-Fidelity Music Show, Nov. 22-24, Statler Hotel, St. Louis, Mo.

RADAR MAP, which provides a plane's pilot with his exact position and true flight path has been designed by the Hycon Manufacturing Co. Fully automatic, the instrument makes a photographic record of radar information on a slow-moving strip of film. The film is then sent through a 10-second developer and is moved across a translucent illuminated plate for the pilot's inspection.


TV RECEIVERS IN EUROPE totaled 8.3 million, according to estimates made early this year. England leads with 6.6 million receivers. Germany, with 681,839, is second and France is third with 420,000. Italy has 360,000, Belgium 144,000 and Holland 99,000. At the bottom of the list is Finland with 2,500 receivers. By comparison, the United States has 44.5 million.

SYMPOSIUM on Industrial Electronics is being held at the Morrison Hotel, Chicago, Ill., on Sept. 24 and 25. The main theme of the symposium is the characteristics, use and integration of transducers into complete systems to measure and control processes from start to finish. END

EXCITINGLY NEW COMPONENTS FROM H. H. SCOTT . . .

Get the facts! 11 brand new H. H. Scott components. NEW styling . . . NEW features . . . a completely NEW line for '58.

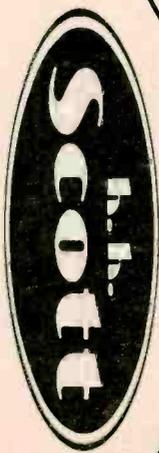Want all the facts on the most exciting hi fi line of the year? Then write for H. H. Scott's new free catalog. Get all the technical data on Scott's brand new Model 300 AM-FM tuner. Get technical specs on our completely redesigned 210F amplifier. Read all about the new features we've added to our famous '99' complete amplifier.



H. H. Scott, 111 Powdermill Road, Maynard, Massachusetts
 Export Dept.: Telesco International Corp.
 36 West 40th Street, New York City

Rush me your new catalog E-10 and complete technical specifications on H. H. Scott components for '58.


NAME

ADDRESS

CITY STATE

FREE!

ALLIED'S 1958 CATALOG

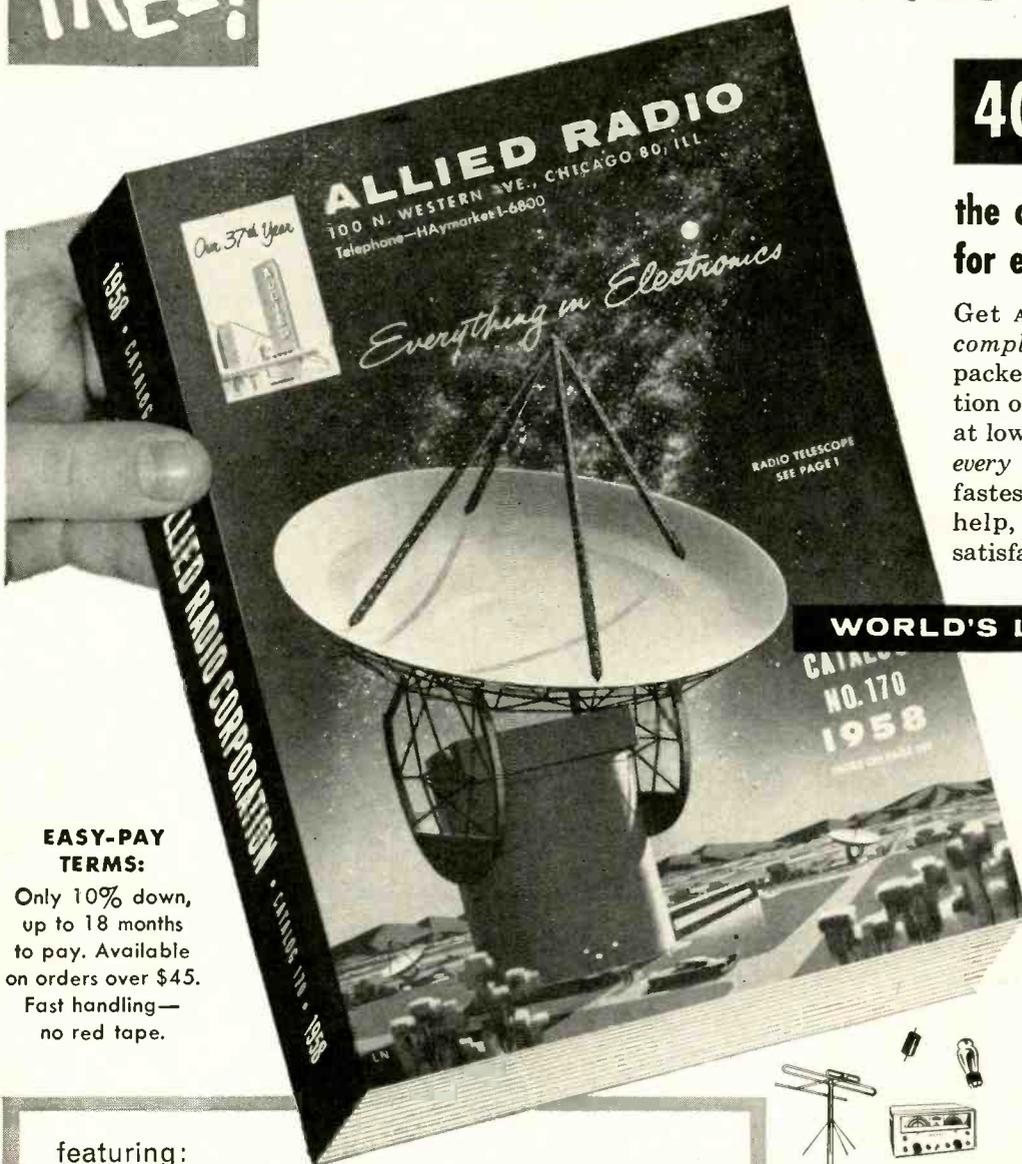

404 value-packed PAGES

the only **COMPLETE** catalog for everything in electronics

Get ALLIED'S 1958 Catalog—it's complete, up-to-date—404 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get every buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

WORLD'S LARGEST STOCKS

- Latest Hi-Fi Systems and Components
- Money-Saving, Build-Your-Own KNIGHT-KITS
- Recorders and Supplies
- Public Address Systems and Accessories
- TV Tubes, Antennas and Accessories
- Amateur Receivers, Transmitters, Station Gear
- Test & Lab Instruments
- Specialized Industrial Electronic Equipment
- Huge Listings of Parts, Tubes, Transistors, Tools, Books



EASY-PAY TERMS:

Only 10% down, up to 18 months to pay. Available on orders over \$45. Fast handling—no red tape.

featuring:

ALLIED'S money-saving knight-kits:

Finest electronic equipment in money-saving kit form. Over 50 quality kits available—Hi-Fi amplifier, tuner and speaker kits, Hobby kits, Test Instruments, Ham kits (see our KNIGHT-KIT values elsewhere in this publication). ALLIED KNIGHT-KITS are easiest to build and they SAVE YOU MORE.

EVERYTHING IN HI-FI

World's largest selection of quality Hi-Fi components and complete music systems—available for immediate shipment from stock. Save on exclusive ALLIED-Recommended complete systems. Own the best in Hi-Fi for less!



Our 37th Year

ALLIED RADIO

World's Largest Electronic Supply House

OCTOBER, 1957

send for the leading electronic supply guide **FREE!**

ALLIED RADIO CORP., Dept. 2-K7
100 N. Western Ave., Chicago 80, Ill.

Send FREE 404-Page 1958 ALLIED Catalog

Name _____

Address _____

City _____ Zone _____ State _____

It's
NEW

The **TRC**
triple-duty microphone



Actual size of new TRC microphone

for hand ...



it's versatile ...
lightweight ...
low cost, too!

Elgin's new TRC dynamic microphone offers faithful audio reproduction in the 80-8500 cps range, yet lists from \$11.50. It is designed for use with tape recorders ... yet has the versatility to perform ideally at meetings and assemblies, wherever p.a. systems are used. The TRC is less than five inches long, weighs only nine ounces, has a polished, chromeplated case. It is omnidirectional and picks up voices within a radius of ten feet under average conditions.

stand ...



The TRC is also available in crystal and ceramic types.

Get the facts on this new addition to Elgin's complete line of "American" microphones. Write today for specifications and complete descriptive literature.

or lavalier



ELECTRONICS DIVISION

ELGIN NATIONAL WATCH COMPANY
107 National Street, Elgin, Illinois



Correspondence



HOT WORDS ON BOOSTERS

By telling a Radiological Safety Conference a few months ago that boosters used on aging picture tubes might convert them into sources of X-rays, Dr. James B. Kelley, a research consultant for the New York State Commerce Department started a mild radiation scare. He was reported to have said that he had personally seen TV sets "which had their anode voltages raised from the usual 15,000 to as high as 30,000 or 35,000 volts." (See "Radiation Scare," RADIO-ELECTRONICS, August 1957, page 6.)

It seemed inconceivable that any such set could exist but, after all, the doctor is an expert in his own field at least and would not be expected to circulate irresponsible statements. So we wrote to active individuals in a number of TV and electronic service associations, asking if either they or any of their members had ever seen TV's in which the anode voltage had been boosted as described.

Dear Editor:

It is true that a booster increases the filament voltage. However it *lowers* the high voltage. It does it this way: As a picture tube gets older it pulls less current and the high voltage, which is unregulated in the average set, goes up. If you put a booster on a set or replace the tube, the set draws more current from the high-voltage supply, which in turn lowers the high voltage.

FORREST L. BAKER

Texas Electronics Association
San Antonio, Tex.


Dear Editor:

I am very puzzled by the comments of Dr. James B. Kelley who is cited as an "industrial consultant for the State Commerce Department" of New York. Either he is referring to some form of "booster" which I, in my 38 years experience in electronics, have never come in contact with or he is confused.

I have never seen one which raises the anode voltage. These devices generally operate on the principle of heating the cathode to a higher degree, thus allowing for more complete usage for the active cathode coating.

In my own service business we use boosters only as a last resort, to obtain the utmost in picture-tube life in hardship cases. We feel that the actual cost of a good picture tube per hour of use is so small as to make squeezing the last drop of highly unpredictable life hardly worth the effort. When a picture tube falls below proper operating level, it is time to buy a new one.

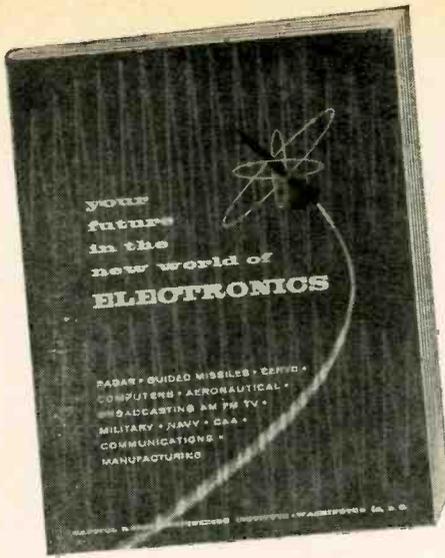May I suggest that Dr. Kelly either prove his point by an actual demonstration of a standard booster, using standard TV chassis, high-voltage meters and Geiger counters, or cease



The data that Launched
Thousands of Careers
is yours **FREE**

Tells how you can be successful
in **RADIO-TV-ELECTRONICS**

Send for Your Free Copy Today!

This is a brand new edition of the book which has launched thousands of men on good-paying careers in radio-tv-electronics.

It brings you completely up to date—answers important questions on newest career developments in electronics, including Radar, Guided Missiles, Servomechanisms, Computers, as well as Aeronautical Electronics, Broadcasting (AM, FM, TV), Military, Navy and CAA Electronics, Communications and Electronics Manufacturing.

This book, "Your Future in the New World of Electronics," also shows you how CREI Home Study leads the way to greater earnings in the booming electronics world.

However, CREI does not promise you a "snap." With an accredited technical school such as this you must study to convert your ambition into technical knowledge you can sell in the fabulous Electronics market.

Since its founding in 1927, CREI has provided thousands of professional electronics men with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics, at company expense, among them United Air Lines, Canadian Broadcasting Corporation, Trans-Canada Airlines, Douglas Aircraft Co., Glenn L. Martin Co., Columbia Broadcasting System, All-American Cables and Radio, Inc., Gates Radio Co., Canadair Ltd., Federal Electric Corp., and U. S. Information Agency. CREI courses are prepared by recognized experts, in a practical, easily understood manner. You get the benefit of time-tested study assignments under the personal supervision of a CREI staff instructor. This is accomplished on your own time, during hours selected by you, and controlled by your own will power. This com-

plete training is the reason that graduates find their CREI diplomas key-to-success in radio, TV and Electronics. CREI alumni hold top positions in America's leading firms. At your service is the CREI Placement Bureau, which finds positions for advanced students and graduates. Although CREI does not guarantee jobs, requests for personnel far exceed current supply. Now is the time of decision for you. Luck will not

propel you forward unless it finds you trained. Contacts won't budge you an inch unless you have the skill to back them up. The answer is: Technical Training . . . and willingness to learn. Together they will bring you increased earnings in this new Age of Electronics. Fill out the coupon below and mail it now. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—your future—is up to you!

ELECTRONIC TECHNICIANS

Growing Peninsula Co. has openings for 1st class electronic technicians to work directly with engineering in development of new products. Only those with CREI or equal training and 3 years minimum commercial experience will be considered. Top salaries to qualified applicants. Call Mr. McQueeney, DA. 4-4733 for appointment. **ALTO SCIENTIFIC Co., Inc.** 855 COMMERCIAL ST. PALO ALTO

CREI also offers Residence Training at some high technical level in Washington, D.C. Classes start at regular intervals. Qualified residence school graduates earn degree "Associate in Applied Science." Check coupon if you prefer residence study. **VETERANS:** If eligible for training under the new G.I. Bill of Rights, check the coupon for full information.

Industry Calls for CREI training By Name . . . SO SHOULD YOU!

Here you see an actual help wanted ad from the *San Francisco Examiner*, April 1, 1956, one of many which specify "CREI or equal" training. This shows that industry approves CREI training, even insists on it.

FILL OUT AND MAIL TODAY—BEFORE YOU FORGET IT!

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 1410-D, 3224 16th St., N.W., Washington 10, D.C.

ECPD Accredited Technical Institute Curricula - Founded 1927

Please send me your course outline and **FREE** Illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology

- CHECK FIELD OF GREATEST INTEREST
- Electronic Engineering Technology
 - Broadcast (AM, FM, TV) Engineering Technology
 - Aeronautical Electronic Engineering Technology
 - Television Engineering Technology

Name..... Age.....

Street

City..... Zone..... State.....

CHECK: Home Study Residence School Veteran

To help us answer your request intelligently, please give the following information:

EMPLOYED BY.....

TYPE OF PRESENT WORK.....

SCHOOL BACKGROUND.....

ELECTRONICS EXPERIENCE.....

IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED?



GI

PHONOMOTORS GUARD YOUR REPUTATION




MODEL D-10, 4-pole, shaded pole A.C. induction type for tape, wire, or disc recorders

Your reputation is secure when you follow the nation's leading O.E.M.'s and rely on GI for all your phonomotor needs. No other line can match GI's long record of dependable performance . . . and none can offer you the convenience of a complete selection of models from a single source. It pays to Rely on GI!

RELY on GI



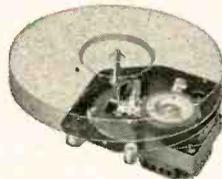MODEL BX
Battery powered, 3-speed motor
(45, 33 1/3, 16 2/3 R.P.M.)



MODEL DSS
3-speed, 4-pole motor




MODEL SS3-3 speed
SS4-4 speed
2-pole motor



MODEL DR
2-speed
4-pole motor



MODEL RM 4
Single speed
4-pole motor

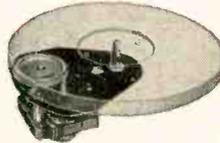

MODEL AX
Single speed
2-pole motor



THE GENERAL INDUSTRIES CO.

DEPT. GR • ELYRIA, OHIO

Look what **RADIO-ELECTRONICS** has
in store for you in the Months ahead!

- All-Transistor Tape Playback Preamplifier
- How to Use Tube Data
- Testing Audio Amplifiers
- Tricky Circuits in TV
- De Luxe Remote Baby Sitting System
- Common Fallacies in Color TV Servicing
- Tricks with Neon Lamps
- Tiny-Tran—A Real Pocket Radio
- A New Basic Audio Amplifier for the Constructor
- Substitution Resistance Boxes Make Servicing Easy
- Cheap TV Substitution Picture Tube

The NOVEMBER issue of RADIO-ELECTRONICS goes on sale October 24 at all better parts distributors and newsstands

SUBSCRIPTION RATES

One year \$4.00
RADIO-ELECTRONICS

Two years \$7.00

Three years \$9.00

154 West 14th Street, New York 11, N.Y.

CORRESPONDENCE (Continued)

to attempt to alarm our customers. We have enough problems as it is.

FRANK J. MOCH
*National Alliance of Television &
Electronic Service Associations
Chicago, Ill.*

Dear Editor:

While we were aware that using a TV filament booster causes no increase in anode voltage, a test was made by Warren Schei, our products director.

The results were "absolutely no increase in anode voltage."

To increase the normal 15,000 volts to 30,000 would necessitate a doubling of the horizontal output. This would almost immediately cause a voltage breakdown and shorting before the voltage could build up to that level. The commonly used rectifier tubes have maximum inverse voltages of from 16,000 to 21,000.

There is merit, however, to the dangers of X-ray radiation. The Minnesota Television Service Engineers, Inc., in cooperation with the University of Minnesota and Setchell-Carlson, Inc., are planning tests on radiation. The results should give us answers as to the amount of radiation and its dangers. If there were no dangers manufacturers would not need to include disclaimers in rectifier-tube cartons, on picture tubes or in service notes. If we must "live with it," what have we got? We hope to find out.

JOHN HEMAK
*American Institute of Television Service
Minneapolis, Minn.*

DR. KELLEY REPLIES

Dear Editor:

I am sorry that I was unable to answer your letter of July 1 sooner but I have been out of the country for some time and as a consequence have fallen behind on my mail.

With regard to the question you raise concerning a report of research done on television boosters I should like to correct what is apparently a misunderstanding on your part. At a Radiological Safety Conference held from June 12 to June 14 at Canisius College in Buffalo, N. Y., I delivered a paper entitled "Basic Physical Principles of Ionizing Radiation." I did not discuss television in that paper. However, in an interview with a reporter for the *New York Times* which I gave after I had delivered my paper I mentioned the fact that I had seen television receivers that had had their voltages boosted to levels which were approximately those at which soft X-rays might be given off.

Since the term booster has a technical significance in the television repair business, there was some confusion over my use of the word boost in a generic rather than technical sense. My opinions are based on sets which I have seen which had very high voltages and also on the fact that color television sets will have substantially higher voltages than black-and-white receivers. What I said was in the nature

(Continued on page 22)

Prepare for a Good Paying Job — Or Your Own Business

Learn **PRACTICAL RADIO-TV**
with **25 BIG KITS**

of equipment I send you while
you train with me . . . for valuable
shop bench experience . . .





17" to 24"
PICTURE TUBE

This is the new Sprayberry Training
Television receiver, built and tested
in sections for greatest instruction
value.

I now offer this fine modern oscil-
loscope to help you learn practical
television servicing.

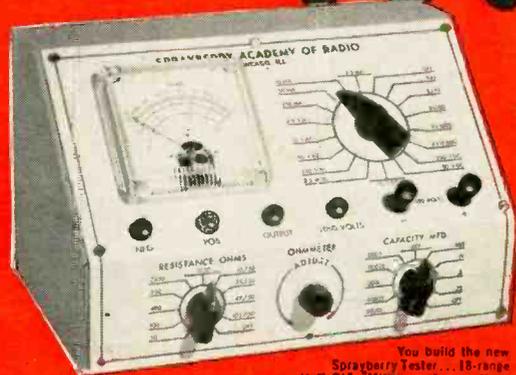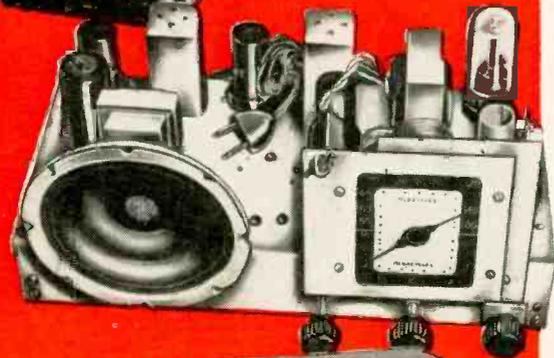You will build this powerful short
wave and broadcast superhet radio
receiver for valuable shop instruc-
tion practice.



You build the new
Sprayberry Tester . . . 18-range
V_{OH}-Ohm_Ω-Milliammeter readings
plus output meter and condenser
and resistor substitution selector.

Average cost per lesson
ONLY \$3.42
Including Kits and Equipment

"I Will Train You at Home in
RADIO-TELEVISION

On Liberal No Obligation Plan!"

**New Equipment! New Lessons! Enlarged
Course! The true facts are yours in my
big new catalog . . . YOURS FREE . . .**

JUST MAIL COUPON!

I can train and prepare you in as little as
10 months to step into the big opportunity
Radio-Television service field. Train *without*
signing a binding contract . . . without obli-
gating yourself to pay any regular monthly
amounts. You train entirely at home in spare
hours . . . you train as fast or as slowly as
you wish. You'll have your choice of **THREE SPRAYBERRY TRAINING
PLANS** . . . planned for both beginners as well as the more experienced
man. Get the true facts about the finest most modern Radio-Training avail-
able today . . . just mail the coupon for my big new 56 page fact-filled
catalog plus sample lesson—both **FREE**.



Frank L. Sprayberry
Educational Director

Train the Practical Way—with Actual Radio-Television Equipment

My students do better because I train both the mind and the hands. Sprayberry
Training is offered in 25 individual training units, each includes a practice giving
kit of parts and equipment . . . all yours to keep. You will gain priceless practical
experience building the specially engineered Sprayberry Television Training Re-
ceiver, Two-Band Radio Set, Signal Generator, Audio Tester and the new Spray-
berry 18 range Multi-Tester, plus other test units. You will have a complete set
of Radio-TV test equipment to start your own shop. My lessons are regularly
revised and every important new development is covered. My students are com-
pletely trained Radio-Television Service Technicians.

**NEWEST
DEVELOPMENTS**

Your training
covers U H F, Color
Television, F M,
Oscilloscope
Servicing, High
Fidelity Sound
and Transistors.

**See for Yourself . . . Make Your Own Decision
. . . Mail Coupon Today!**

The coupon below brings you my big new catalog plus
an actual sample Sprayberry Lesson. I invite you to read
the facts . . . to see that I actually illustrate every item
I include in my training. With the facts in your hands,
you will be able to decide. *No salesman will call on you.*
The coupon places you under no obligation. Mail it now,
today, and get ready for your place in Radio-Television.

SPRAYBERRY ACADEMY OF RADIO-TELEVISION

1512 Jarvis Avenue, Dept. 20-T, Chicago 26, Illinois

Mail This Coupon For Free Facts and Sample Lesson



SPRAYBERRY ACADEMY OF RADIO-TELEVISION

1512 Jarvis Ave., Dept. 20-T, Chicago 26, Ill.

Please rush all information on your **ALL-NEW** Radio-Te-
levision Training Plan. I understand this does not obligate me
and that *no salesman will call upon me.* Include New Cata-
log and Sample Lesson **FREE**.


Name _____ Age _____

Address _____

City _____ Zone _____ State _____


WHAT'S **NEW** FROM

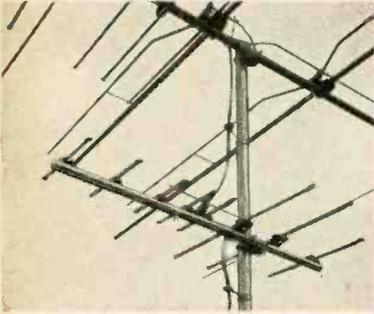Now...2 Ways to Add UHF to Your Fringe Area Color'ceptor



Here's something really new!

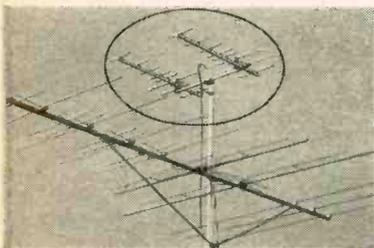A UHF antenna (Winegard Mod. GG-1) that connects in series with the same lead used for the VHF Color'ceptor. No couplers... no loss... no interaction. Perfect results every time! Can be oriented independently from CL-4 or CL-4X. Same general features as on GG-2 shown below. Completely gold anodized. Only \$7.95.



New UHF Colinear Yagis Model GG-2 mounted with CL-4X Color'ceptor

High gain UHF antenna has 4 col. driven elements, 10 directors, 6 reflectors. Pin point directivity. No minor lobes. Flat frequency response. Can be stacked up to 16 bays for up to 21 db gain. Completely gold anodized. Can be ordered factory peaked to favor your channels. Only \$14.95.

NEWS NOTE: Color'ceptor, the favorite fringe area antenna of professional installers everywhere, is now even better! —NEW TDM insulators. Low loss, unbreakable—NEW special alloy plus extra reinforcing used in reflectors. Four times more durable—NEW sunfast gold finish. Permanently anodized.

... NEW ... SUPER *twilight** FOR THE TWILIGHT* TV AREA

Biggest Advance Yet In Antenna Design!

Something new and wonderful has happened to antennas! Now you get the "whole ball of wax"... mast, lead-in, Antenna, mount... everything factory-assembled—factory-engineered into one simple, integral unit!

- NO loose parts to assemble
- NO wires to strip


Just take your Twilight out of the box... pop it open... put it up as easy as driving 3 nails... it's as simple as that!

Now you can make a complete installation (in most cases without even getting on the roof) in no more time than it takes to pull a TV chassis for repair! Twilight is so easy... it's a breeze to install.

Engineered for results... styled to sell... as new and modern as today!

SENSITIVITY COMPARISON CHART

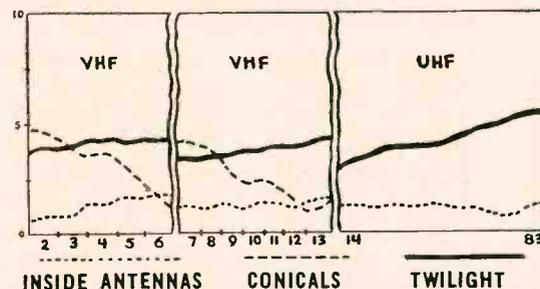
Note extremely linear frequency response of Twilight



LOOK AT THESE ALL NEW EXCLUSIVE ENGINEERING INNOVATIONS

- 1 **UNIVERSAL MOUNT*** goes up in minutes... super-sturdy... eliminates ugly guy wires, chimney brackets... fits all surfaces, flat, sloping and vertical.
- 2 **SPECIAL DRIVE FASTENERS** go in like nails, hold like screws... special gaskets seal roof automatically.
- 3 **SNAP-OUT MAST CLAMP**... automatic, self-aligning. No tools.
- 4 **SERIES-FED UHF** new intermixed design. No loss, no interaction, one lead-in. Can't become obsolete. And at no extra cost!
- 5 **ELECTRO-LENS HIGH GAIN DIRECTOR SYSTEM** for ultra linear frequency response and no ghost-catching minor lobes on any channel.
- 6 **DUAL "T" MATCHED DRIVEN ELEMENTS**... end-fire phased. Accurate 300 ohm impedance match.
- 7 **PERMANENT NON-CORROSIVE ANODIZED FINISH** in Sunfast Gold, Twilight Blue or Starbrite Silver... looks better, sells faster... makes all other antennas look as old-fashioned and out-of-date as they really are.

Horizontal Directivity Patterns

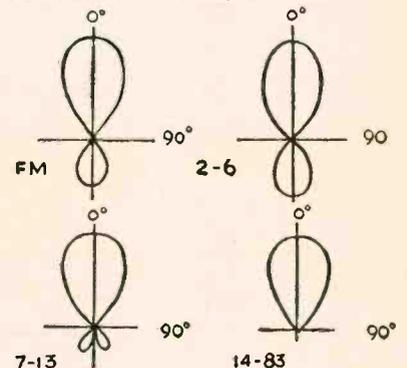

*Patent Pending

NEW PEEK-A-BOO PACKAGE

Makes beautiful display... lets customer see merchandise without opening carton... has complete sales story pitched to your customers on back of carton.




Winegard Co.

Winegard

COMPACT... POWERFUL!

THIS IS THE TWILIGHT AREA

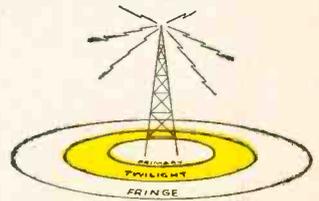

The "in-between" Twilight area (5 to 35 miles) presents reception problems all its own. Most set owners living within its boundaries have been enjoying neither the finest TV reception nor the poorest.

Because the Twilight area has many of the reception difficulties of both the fringe and primary areas, almost every type of antenna from rabbit ears to large arrays is used here. None of which were actually designed with the Twilight area's actual requirements in mind.

An extensive survey made by the Winegard Company in the Twilight areas of some of our larger cities brought to light these amazing facts:

- 42% of the TV owners were not really satisfied with their reception
- 72% of these dissatisfied TV viewers were using set-top antennas
- 53% didn't like antennas on top of their set
- 34% said set-top antennas were too difficult to adjust
- 49% thought outside antennas were too big and unsightly
- 34% thought outside antennas were too susceptible to corrosion-stained roofs... and were ruined by weather
- 49% of all set owners questioned were willing to spend up to \$30.00 for a TV antenna that would overcome all these objections. 7% would spend up to \$60.00

With the above information, Winegard engineers went to work to produce the first antenna designed specifically for the needs and wants of TV set owners in the Twilight area.

We call this new electronic masterpiece... appropriately enough... the Twilight!



**WINEGARD
TWILIGHT, MOD. TL-283**
All Channels 2-83 plus FM
Color or Black and White

All aluminum construction... can't stain roof. The Twilight* installation includes: antenna with mast, lead-in wire and set terminal clip attached; universal mounting base with special drive fasteners, roof-sealing gaskets and stand-off insulators. Antenna width: 87"—Height including mount 53". Net wt.: 4½ lbs., Shpg. wt.: 6 lbs. Can be mailed parcel post.

**NEW
Sunfast
Gold
Anodized**

You can buy Twilight two ways: complete installation, Mod. TL-283, list \$29.95; Twilight head only with standard mast clamp, Mod. 283, list \$19.95.

Note:


50 ft. heavy 80-mil
300 ohm lead-in wire
with set terminal clip.

**Absolutely
Nothing
Else
To Buy**


Twilight Mounts on ANY Surface—Sloping, Flat, Vertical




Side of roof

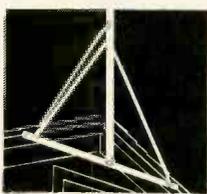

End of roof

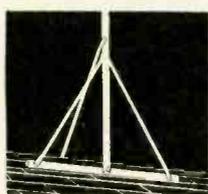

Peak of roof

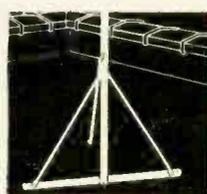

Flat or trailer

SELL THE LINE THAT HELPS YOU SELL!

As
Advised
in

LIFE

The Saturday Evening

POST

**Better Homes
& Gardens**

List price established nationally in Life magazine at \$29.95. Extra long discount structure so you can allow trade-ins or free installation if you wish... and still make your normal profit.

Mr. Dealer:
See Your
Winegard
Distributor
and


Mail Coupon
Today!

WINEGARD CO., Dept. RE-10
3000 Scotten Blvd., Burlington, Iowa

- Complete information on Twilight plus sales aids.
- Other Winegard Do-It-Yourself antennas and kits as low as \$14.95.
- Complete information on high powered Color'ceptor.

Dealer Firm Name.....
Address.....
City.....State.....

high fidelity FM reception

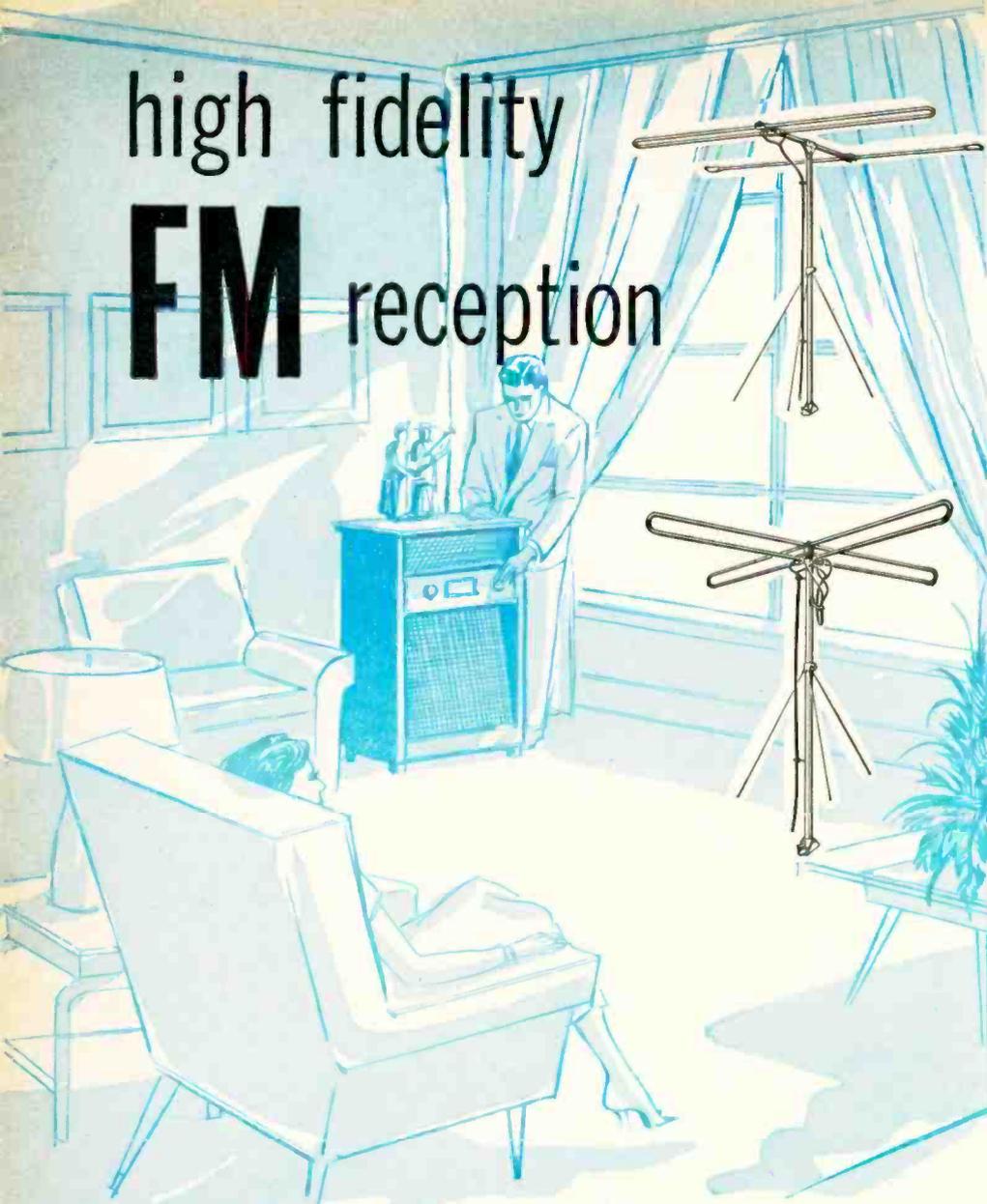

demands a fine antenna . . . *

. . . and the audiophile's best bet for clear, sparkling FM sound is an AMPHENOL broadband FM antenna. Available in two popular models, AMPHENOL FM antennas have been carefully engineered for specific reception problems. The 114-008 "Inline-type" folded dipole and reflector offers the unidirectional directivity pattern, high gain and mechanical rigidity that have made AMPHENOL's tv Inline antenna famous. The 114-010 "Turnstile" double folded dipole is intended for use in urban areas where there are many FM stations. Its circular directivity pattern assures efficient pick-up of such stations.

* *Do it yourself*

COMPLETE KITS \$16.25 each, list



AMPHENOL ELECTRONICS CORPORATION *chicago 50, illinois*

CORRESPONDENCE (Continued from p. 18)

of a warning telling people to be careful, particularly where children are concerned, that they do not put their faces too close to the receiving set (I recommended a distance of 6 feet from the set). It is my feeling that so little is known about both the short- and long-range effects of radiation that, when one is dealing with any instrument potentially dangerous in this area, extreme caution is always advisable. It is a caution I use with my own children and a caution a great many of my colleagues also use.

I had been referring to an increase in the anode voltage and not the serviceman's low-power "booster," which, incidentally, I have on my own TV.

I do not know how widely special glasses are used on commercial television receivers. I do know that one of the large manufacturers of the glass envelopes uses barium glass on the face of the viewing tube. This, however, is something that has been developed only in the last several years. I understand from this same manufacturer that a barium lead glass will be used on the color glass envelopes he manufactures. The reason he gave me in both instances was that, while most information to date would seem to indicate that the radiation of a television viewing tube is quite low, he would rather be sure than make a dangerous mistake. The plate glass which is usually in front of the tube is of the same composition as that found in ordinary windows.

JAMES B. KELLEY

*Consultant,
Technical Industrial Research*

BASEMENT TECHNICIAN

Dear Editor:

I am a part-time "basement technician." So this is how I see things!

For one thing, I do not have the necessary capital—or name—to open up a nice successful full-time service business. Maybe I should go to work for some service company. Well, I admit I might not get the pay I'm enjoying from my present full-time job. And with five kids it's hard to take a cut.

You full-timers have many good arguments and I'm with you on them. The part-timer is inclined to be cut-rate. I'm one who isn't! In my locality I believe a service call should be about \$5. They once were! Now it's \$3.50.

I put in some 16 months at a full-time radio school (plus a little Navy training). I put a lot of cabbage into test equipment, other than screwdrivers and emission tube testers, so catch me at cut-rating and I'll eat it all.

One thing I would like to know. How many of you full-time boys were once part-timers?

About licensing, I'm for it! No license, no servicing. However, I'd want the license awarded on the basis of *technical knowledge and ability.*

All I ask is a fair chance to show I'm not an incompetent. If you have a "dog," I'd like to try myself against it.

LARRY SCHWARTZ

Canton, Ohio

END

RADIO-ELECTRONICS

LEARN ELECTRONICS! EARN MORE MONEY!

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

LEARN BY MAIL OR IN RESIDENT CLASSES

Grantham School of Electronics *specializes* in preparing students to pass F.C.C. examinations. Correspondence training is conducted from Washington and Hollywood; resident DAY and EVENING classes are held in both cities. Either way, we train you quickly and well—NO previous training required. A beginner may qualify for his first class F.C.C. license in as little as 12 weeks.

THE GRANTHAM COMMUNICATIONS ELECTRONICS COURSE

offers you complete preparation for F.C.C. examinations required for a *first class F.C.C. license*. Even though it is planned primarily as preparation for F.C.C. examinations, it is *not* a "cram course" but prepares you by TEACHING you electronics.

HERE'S PROOF that Grantham Students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

| | License | Wks. |
|---|---------|------|
| Leo Bishop, 37 Calle Contenta, Flagstaff, Ariz. | 1st | 12 |
| Carl Deare, Jr., P.O. Box 467, Jeanerette, La. | 1st | 11 |
| Robert Umthun, 1918 Eye St., NW, Washington, D.C. | 1st | 21 |
| Tommy Lesley, 422 Wood St., Maysville, Ky. | 1st | 9 |
| Dan Breece, Station KOVE, Lander, Wyo. | 1st | 12 |
| Robert Todd, Station WWBG, Bowling Green, Ohio | 1st | 13 |
| Jackson York, 1029 N. Quincy St., Arlington, Va. | 1st | 15 |
| Paul Chuckray, 6874 Weber Rd., Affton, Mo. | 1st | 11 |

OUR GUARANTEE: If you should fail the F.C.C. exam after finishing our course, we guarantee to give you additional training at NO ADDITIONAL COST. Read details in our free booklet.

TWO COMPLETE SCHOOLS

To better serve our many students throughout the entire country, Grantham School of Electronics maintains two complete schools—one in Hollywood, California and one in Washington, D.C. Both schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.

Get your First Class Commercial F.C.C. License in 12 weeks by training at



GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD DIVISION


1505 N. Western Avenue, Hollywood 27, Calif. Phone: HO 2-1411

WASHINGTON DIVISION

821 - 19th Street, N.W., Washington 6, D.C. Phone: ST 3-3614

GET YOUR First Class Commercial F. C. C. LICENSE IN 12 WEEKS!

This
Booklet
FREE!

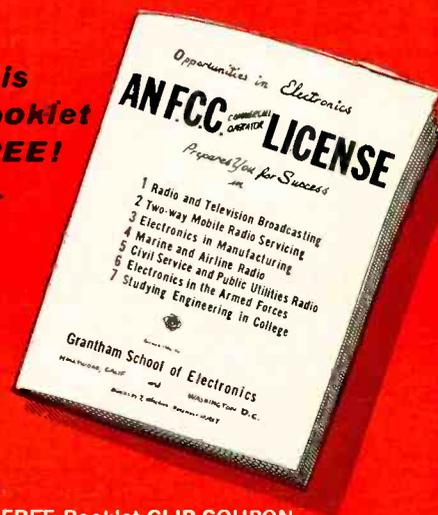

For FREE Booklet CLIP COUPON and mail in envelope or paste on postal card

MAIL TO SCHOOL NEAREST YOU

Grantham Schools, Desk 74-R

821 - 19th Street N.W. OR 1505 N. Western Ave.
Washington 6, D.C. Hollywood 27, Calif.

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____


Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes



AR-22

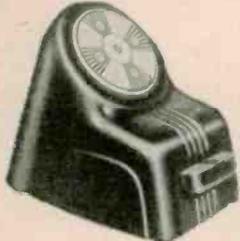


TR-2




TR-4

5-star feature...

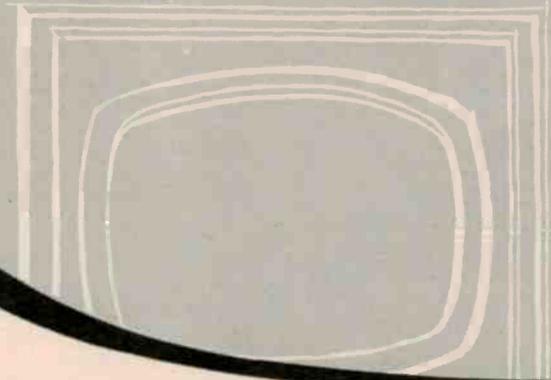
- ★ **1 the best color TV picture**
the growth of color TV means an even greater demand for CDR Rotors for pin-point accuracy of antenna direction.
- ★ **2 a better picture on more stations**
CDR Rotors add to the pleasure of TV viewing because they line up the antenna perfectly with the transmitted TV signal giving a BETTER picture . . . and making it possible to bring in MORE stations.



CDR ROTORS

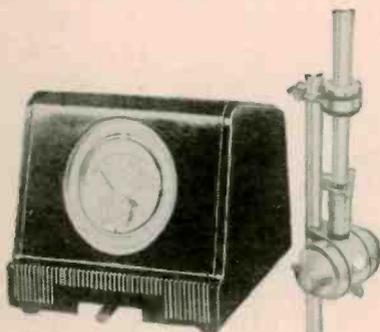


TR 11 and 12

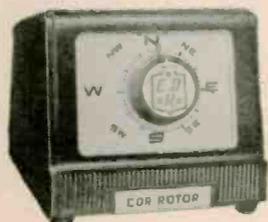

AR 1 and 2

- ★ **3 tested and proven dependable**
thousands and thousands of CDR Rotors have proven their dependability over years of unflinching performance in installations everywhere in the nation. Quality and engineering you know you can count on.
- ★ **4 pre-sold to your customers**
the greatest coverage and concentration of full minute spot announcements on leading TV stations is working for YOU . . . pre-selling your customers.
- ★ **5 the complete line**
a model for every need . . . for every application. CDR Rotors make it possible for you to give your customer exactly what is needed . . . the right CDR Rotor for the right job.

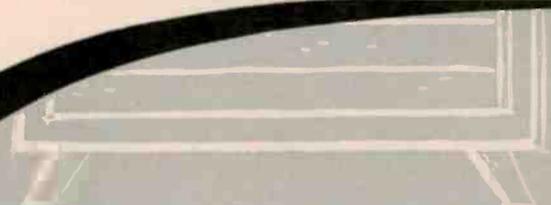

CORNELL-DUBILIER
SOUTH PLAINFIELD, N. J.



THE RADIART CORP.
CLEVELAND 13, OHIO

Electronics Boom Seen

Need For Television Technicians To Rise

Industry Warned About Shortage Of Trained Men

TV SALES SET NEW RECORD


Sylvania Head Expects Huge Electronic Gains

Transistor Radios Developed

RCA HEAD PREDICTS SALES BOOM FOR COLOR TV SETS

VETERANS - - NON-VETERANS

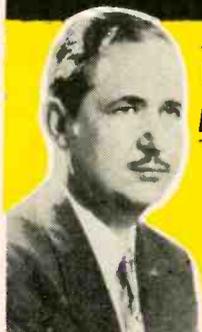Get Into The Field That's Making Headlines



All over the nation the Television-Radio-Electronics industry is making News — News that means opportunity for YOU. You can cash in on the headlines.

I WILL TRAIN YOU AT HOME FOR A TOP-PAY JOB IN TELEVISION

I will prepare you for a spot in America's fastest-growing industry. You can become a trained technician in your spare time without giving up your present job or social life. No experience needed.

LEARN BY DOING

Combination Voltmeter-Ammeter-Ohmmeter



C-W Telephone Transmitter

Super-Het Radio Receiver



Public Address System



AF-RF Signal Generator

As part of your training I give you the equipment you need to set up your own home laboratory and prepare for a top-pay job or set up your own business. You build and keep a TELEVISION RECEIVER designed and engineered to take any size picture tube up to 21-inch. (10-inch tube furnished. Slight extra cost for larger sizes.) . . . also a Super-Het Radio Receiver, AF-RF Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Transmitter, Public Address System, AC-DC Power Supply. Everything supplied, including all tubes.

STUDY NEWEST DEVELOPMENTS

My training covers all the latest developments in the fast-growing Television-Radio-Electronics industry. You learn about FM — RADAR — COLOR TV — TRANSISTORS — PRINTED CIRCUITS, etc.

CHOOSE FROM FOUR COMPLETE COURSES covering all phases of Radio, FM and TV

1. Radio, FM and Television Technician Course—no previous experience needed.
2. FM-TV Technician Course—previous training or experience in radio required.
3. TV Studio Technician Course—advanced course for trained men.
4. Color TV Technician Course—Includes latest color TV circuits.

EXTRA TRAINING IN NEW YORK CITY AT NO EXTRA COST!

After you finish your home study training in Course 1 or 2 you can have two weeks, 50 hours, of intensive Lab work on modern electronic equipment at our associate resident school, Pierce School of Radio & Television. THIS EXTRA TRAINING IS YOURS AT NO EXTRA COST WHATSOEVER!

FCC COACHING COURSE

Important for BETTER-PAY JOBS requiring FCC License! You get this training AT NO EXTRA COST! Top TV jobs go to FCC-licensed technicians.

VETERANS

My School fully approved to train Veterans under new Korean G. I. Bill. Don't lose your school benefits by waiting too long. Write discharge date on coupon.

Radio-Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y.

Licensed by the State of New York • Approved for Veteran Training

FREE HOW TO MAKE MONEY IN TV

FREE I'll send you my new 40-page book, "How to Make Money in Television-Radio-Electronics," a free sample lesson, and other literature showing how and where you can get a top-pay job in Television.

MAIL THIS COUPON TODAY!

Mr. Leonard C. Lane, President

RTTA

Dept. RE-10D, 52 East 19th Street, New York 3, N.Y.

Dear Mr. Lane: Send me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make TOP MONEY IN TELEVISION. I understand I am under no obligation.

(PLEASE PRINT PLAINLY)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

- Color TV Tech. Course
- Radio-FM-TV Technician Course
- FM-TV Technician Course
- TV Studio Technician Course

VETERANS!

Write discharge date

NO OBLIGATION!

**Removes all static and dust while record is played;
new moving coil microphones and transistor amplifier**

ESL DUST BUG


The problems of dust, lint, and static buildup on phonograph records and pickup styli have been solved by this ingenious new invention which cleans the record as it is being played. The plush pad is slightly moistened with special, harmless activating fluid supplied in a replaceable applicator. This helps to loosen groove dust and dirt, which is then collected by the pad. It also neutralizes the static charge present in all records. Every point on an LP record is cleaned by the wide pad approximately one hundred times during a single play.

ESL Dust Bug, complete with Dust Bug Fluid in applicator \$5.75

The automatic record cleaner



ESL MOVING COIL MICROPHONES

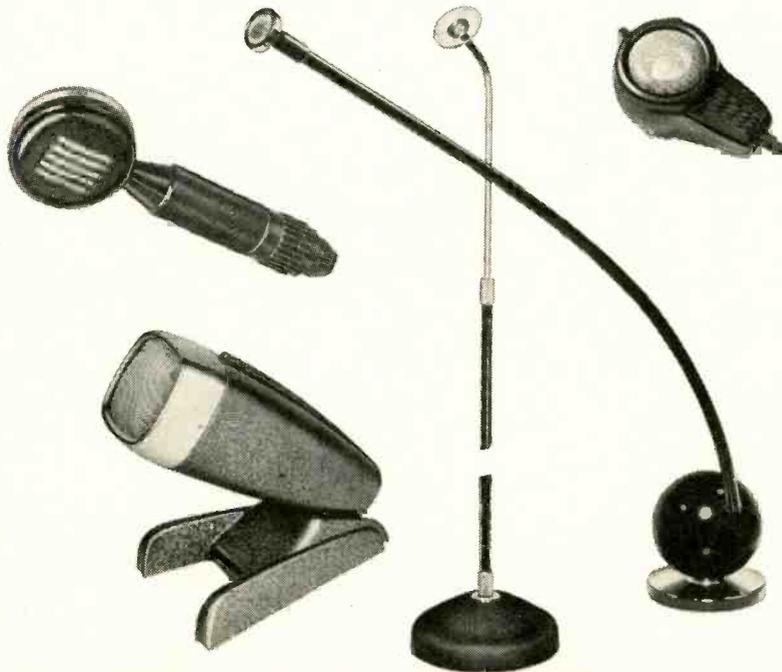

Highest fidelity at moderate cost

Electro-Sonic Laboratories is pleased to announce a complete new line of superb moving coil microphones, microphone transformers, and miniature earphones. For every application—broadcasting, professional recording, home recording, dictating machine, and public address—there is a low impedance ESL microphone specifically designed to provide the highest quality of performance at sensible cost.

A brochure describing the entire line of ESL moving coil microphones and accessories is available free upon request.

ESL TRANSISTOR AMPLIFIER

This hum-free, low-distortion amplifier can provide improved performance with moving coil microphones, for which it is a preamplifier, and with ESL electrodynamic cartridges, for which it is a pre-preamplifier. As its frequency response is flat and unequalized, it does not replace the conventional phono preamplifier. It permits use of greatly superior low-impedance microphones—such as the ESL—with medium-price tape recorders.

*Voltage gain: 20-30 db (1:10-1:20 voltage step-up) • Signal-to-noise ratio: minus 50 db
Frequency response: 20-20,000 cps \pm 1/2 db • IM distortion: 1/10 of 1% • Input impedance: 100 ohms • Output impedance: 2,000 ohms • Battery life: 1 year • Hum level: zero*

ESL-1 A, complete with battery \$16.50

Hum-free low impedance amplification



FOR LISTENING AT ITS BEST

Electro-Sonic Laboratories, Inc.


Dept. E • 35-54 Thirty-sixth St • Long Island City 6, N.Y.

*Additional information available
free upon request to ESL*

Learn TELEVISION-RADIO

Servicing or Communications
by Practicing at Home
in Spare Time

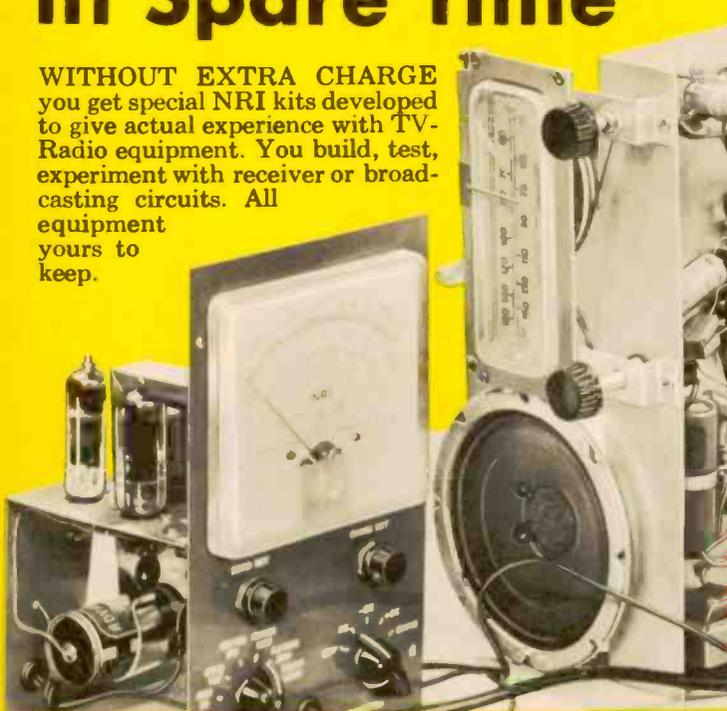WITHOUT EXTRA CHARGE you get special NRI kits developed to give actual experience with TV-Radio equipment. You build, test, experiment with receiver or broadcasting circuits. All equipment yours to keep.



NRI Has Trained Thousands for Successful Careers in TV-Radio

Have the High Pay, Prestige, Good Future of a Skilled TV-Radio Technician

People look up to and depend on the Technician, more than ever before. Offices, plants, homes everywhere are obliged to buy his knowledge and services. His opportunities are great and are increasing. Become a TV-Radio Technician. At home, and in your spare time, you can learn to do this interesting, satisfying work—qualify for important pay. To ambitious men everywhere here in the fast growing Television-Radio field is rich promise of fascinating jobs, satisfaction and prestige as well as increasing personal prosperity.

Increased Opportunities in Growing Field

A steady stream of new Electronic products is increasing the job and promotion opportunities for Television-Radio Technicians. Right now, a solid, proven field of opportunity for good pay is servicing the tens of millions of Television and Radio sets now in use. The hundreds of TV and Radio Stations on the air offer interesting jobs for Operators and Technicians.

More Money Soon—Make \$10 to \$15 a Week Extra Fixing Sets in Spare Time

NRI students find it easy and profitable to start fixing sets for friends and neighbors a few months after enrolling. Picking up \$10, \$15 and more a week gives substantial extra spending money. Many who start in spare time soon build full time TV-Radio sales and service businesses.

Act Now—See What NRI Can Do for You

NRI has devoted over 40 years to developing simplified practical training methods. You train at home. Get practical experience, learn-by-doing. Address: NATIONAL RADIO INSTITUTE, Washington 16, D. C.



Studio Engr., Station KATV
"I am now Studio Engineer at Television Station KATV. Before enrolling for the NRI Course, I was held back by limitation of a sixth grade education." BILLY SANCHEZ, Pine Bluff, Ark.

Has All the Work He Can Do
"Since finishing NRI Course I have repaired more than 2,000 TV and Radio sets a year. NRI training certainly proved to be a good foundation." H. R. GORDON, Milledgeville, Ga.

Has Good Part Time Business
"Quite early in my training I started servicing sets. Now have completely equipped shop. My NRI training is the backbone of my progress." E. A. BREDER, Tacoma, Wash.

The Tested Way To Better Pay See Other Side

CUT OUT AND MAIL CARD NOW

SAMPLE LESSON AND CATALOG BOTH FREE

NO STAMP NEEDED!
WE PAY POSTAGE

This card entitles you to Actual Lesson on Servicing, shows how you learn Television-Radio at home. You'll also receive 64-Page Catalog.

NATIONAL RADIO INSTITUTE, Dept. A Washington 16, D. C.

Please mail me the FREE sample lesson and 64-Page Catalog. (No Salesman will call.)

Name..... Age.....

Address.....

City..... Zone..... State.....

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL





**Technical "KNOW-HOW" Can Give You Interesting, Important Work
LEARN-BY-DOING with Kits NRI Sends at No Extra Charge**



YOU BUILD AC-DC Superhet Receiver

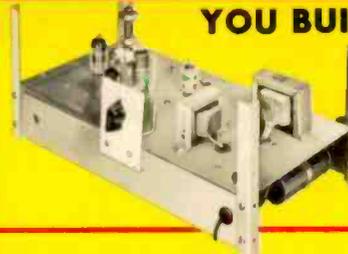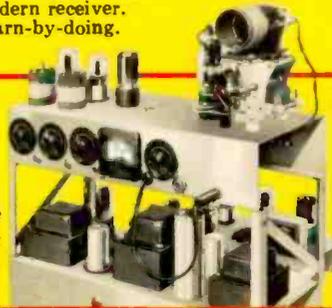NRI Servicing Course includes all needed parts. By introducing defects you get actual servicing experience practicing with this modern receiver. Learn-by-doing.



YOU BUILD Signal Generator

You build this Signal Generator. Learn how to compensate high frequency amplifiers, practice aligning typical I.F. amplifiers in receiver circuits. Make tests, conduct experiments.

YOU BUILD Broadcasting Transmitter

As part of NRI Communications Course you build this low power Transmitter, learn commercial broadcasting operators' methods, procedures. Train for your FCC Commercial Operator's License.

YOU BUILD Vacuum Tube Voltmeter

Use it to earn extra cash fixing neighbors' sets; bring to life theory you learn from NRI's easy-to-understand texts.



For Higher Pay, Better Jobs Be a Television-Radio Technician



Servicing Needs More Trained Men

Portable TV, Hi-Fi, Transistor Radios, Color TV are making new demands for trained Technicians. Good opportunities for spare time earnings or a business of your own.



J. E. Smith, Founder

Train at Home the NRI Way Famous for Over 40 Years

NRI is America's oldest and largest home study Television-Radio school. The more than 40 years' experience training men for success, the outstanding record and reputation of this school—benefits you in many ways. NRI methods are tested, proven. Successful graduates are everywhere, from coast to coast, in small towns and big cities. You train in your own home, keep your present job while learning. Many successful NRI men did not finish high school. Let us send you an actual lesson, judge for yourself how easy it is to learn.

Broadcasting Offers Satisfying Careers

4000 TV and Radio stations offer interesting positions. Govt. Radio, Aviation, Police, Two-Way Communications are growing fields. Trained Radio-TV Operators have a bright future.



No Experience Necessary—NRI Sends Many Kits for Practical Experience

You don't have to know anything about electricity or Radio to understand and succeed with NRI Courses. Clearly written, well-illustrated NRI lessons teach TV-Radio-Electronic principles. You get NRI kits for actual experience. All equipment is yours to keep. You learn-by-doing. Mailing the postage-free card may be one of the most important acts of your life. Do it now. Reasonable tuition. Low monthly payments available. Address: NATIONAL RADIO INSTITUTE, Washington 16, D. C.

NRI Graduates Do Important Work



Now Quality Control Chief
"Had no other training in Radio before enrolling, obtained job working on TV amplifiers before finishing course. Now Quality Control Chief." T. R. FAYALORO, Norwich, N. Y.

NRI Course Easy to Understand
"I opened my own shop before receiving my diploma. I have had to hire extra help. I am independent in my own business." D. P. CRESSEY, Stockton, Cal.

Works on Color-TV
"NRI changed my whole life. If I had not taken the course, probably would still be a fireman, struggling along. Now Control Supervisor at WRCA-TV." J. F. MELINE, New York, N. Y.

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D.C.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

Washington 16, D. C.

**SAMPLE LESSON
64-page CATALOG
both FREE**

**See Other Side
for more
information on
the Tested Way
to Better Pay**


how long would it take you to solve this service problem?

PHOTOFACT

helps you lick problems like this in just minutes for only *2½¢ per model!

SYMPTOM:

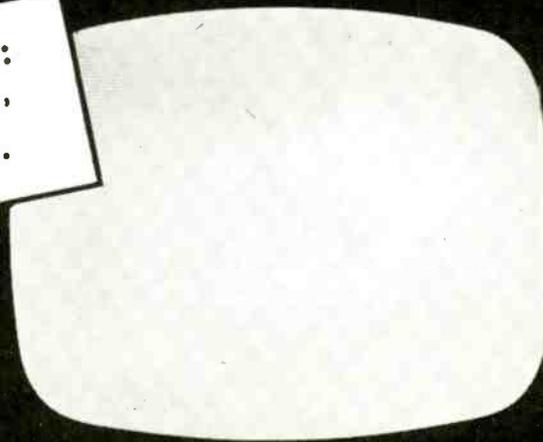Raster, No Sound,
No Picture,
and No Snow ...




Let's take a look at this problem: A condition such as this can exist only when there is no signal reaching the picture tube or the audio output stage. Using the Tuner Service data (found in every PHOTOFACT TV Folder), first isolate the trouble by connecting an amplitude-modulated signal to the mixer-grid test point "D." The appearance of one or more black bars on the face of the tube would indicate that the trouble is probably in the tuner. So look for the following possible causes:

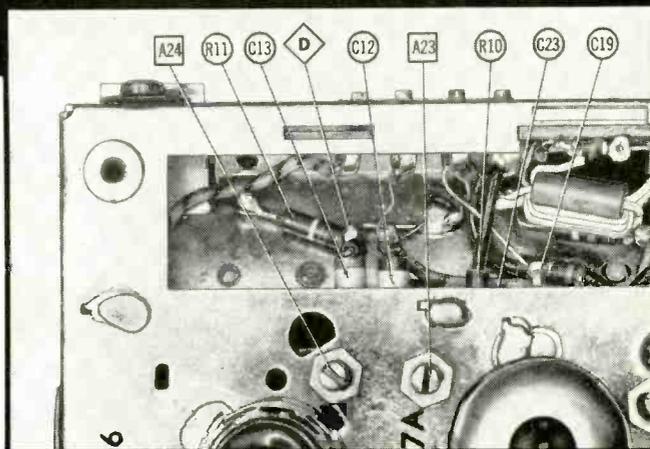1. Defective oscillator-mixer tube
2. Defective RF amplifier tube
3. Open plate-load resistor in the oscillator stage
4. Failure of the feedback capacitor in the oscillator stage
5. Open decoupling resistor
6. Dirty or faulty contacts
7. Cold solder joint

Using the applicable PHOTOFACT Folder you can troubleshoot and solve this problem in minutes. Here's how:

Check the oscillator-mixer and RF amplifier tubes. Tubes okay?—then: Check voltages on the tube pins (they're right on the schematic) for open oscillator plate-load



(Based on an actual case history taken from the Howard W. Sams book "TV Servicing Guide")

resistor, open RF decoupling resistor, faulty feedback capacitor, dirty switch contacts or cold solder joints.

Every PHOTOFACT Television Folder contains complete detailed information on Tuners, including separate Schematics, separate Keyed Chassis Photographs, Parts Lists, Alignment Points, Test Points, and Field Service Adjustments that will help you quickly locate the proper parts to replace and tell you how to do a touchup or thorough alignment job after making the necessary repairs. These features are a *plus* exclusive in PHOTOFACT.

Whatever your problem or favorite servicing procedure may be—you will always find all of the information you need at your fingertips in PHOTOFACT. For only *2½¢ per model, PHOTOFACT helps you solve your service problems in just minutes—helps you service more sets and earn more daily!

*Based on the average number of models covered in a single set of PHOTOFACT Folders.



MONEY BACK GUARANTEE!

Got a tough repair? Try this—at Howard W. Sams' own risk: see your Parts Distributor and buy the proper PHOTOFACT Folder Set covering the receiver. Then use it on the actual repair. If PHOTOFACT doesn't save you time, doesn't make the job easier and more profitable for you, Howard W. Sams wants you to return the complete Folder Set direct to him and he'll refund your purchase price promptly. GET THE PROOF FOR YOURSELF—TRY PHOTOFACT NOW!

FREE



FOR SERVICE TECHNICIANS ONLY

Fill out and mail coupon today for Free subscription to the Sams Photofact Index—your up-to-date guide to virtually any receiver model ever to come into your shop. Send coupon now.

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc.
2205 E. 46th St. Indianapolis 5, Ind.

Put me on your mailing list to receive the Sams Photofact Index and Supplements. My (letterhead) (business card) is attached.

I'm a Service Technician: full time; part time

My Distributor is: _____

Shop Name: _____

Attn: _____

Address: _____

City _____ Zone _____ State _____

Use
RAYTHEON
All-Set
TV & RADIO
TUBES

RAYTHEON

RAYTHEON

for all set replacement work!

You'll save yourself trouble if you standardize on Raytheon "All-Set" Tubes for replacement work.

Here's why:

Raytheon "All-Set" Tubes are designed to give perfect service in many makes and models of receivers because Raytheon sells Tubes to almost

every set manufacturer. To satisfy the many and varying needs of so many manufacturers, these tubes must combine top quality performance and dependability. This successful combination makes Raytheon "All-Set" Tubes tops for replacement.

Always use Raytheon "All-Set" Tubes to satisfy your "all-set" customers.

TV-Radio service is your business . . . serving you is ours



RAYTHEON MANUFACTURING COMPANY


Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these { Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes and Transistors, Nuclear Tubes, Microwave Tubes.



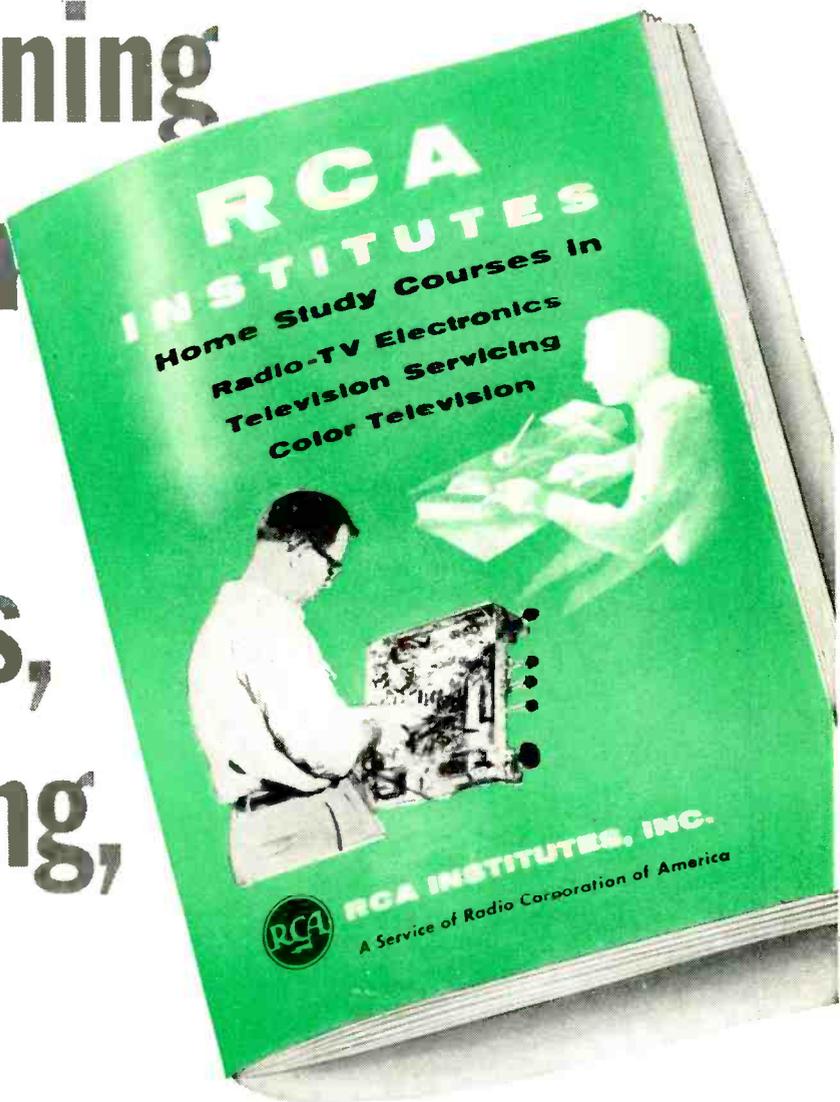RCA offers you the
 finest training
 at home in
 Radio-TV
 electronics,
 TV servicing,
 Color TV



SEND FOR THIS FREE BOOK NOW!

Pay-as-you-learn. You need pay for only one study group at a time. Practical work with very first lesson. All text material and equipment is yours to keep. Courses for the beginner and advanced student.



RCA INSTITUTES, INC.
 A SERVICE OF RADIO CORPORATION OF AMERICA
 350 WEST FOURTH STREET, NEW YORK 14, N. Y.

In Canada—RCA Victor Company, Ltd.,
 5001 Cote de Liesse Rd., Montreal 9, Que.

RCA Institutes, Inc., Home Study Dept. RE-107
 350 West Fourth Street, New York 14, N. Y.
 Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No Salesman will call.

Name.....
 Please Print

Address.....

City..... Zone..... State.....

KOREAN VETS! Enter discharge date.....

To save time, paste coupon on postcard



Shown at Bell Laboratories, Murray Hill, N.J., are, left to right, F. J. Herr, S. T. Brewer, L. R. Snoke, E. E. Zajac and F. W. Kinsman.

They're wiring the seas for sound

These five Bell Labs scientists and engineers may never "go down to the sea in ships." Yet, they're part of one of the most exciting sea adventures of modern times. Along with many other specialists, they are developing the deep-sea telephone cable systems of the future.

Here's how they join many phases of communications science and engineering—to bring people who are oceans apart within speaking distance.

F. J. Herr, M.S., Stevens Institute, is concerned with systems design and analysis. He studies the feasibility of new approaches and carries out analysis programs to select optimum parameters for a proposed system design.

S. T. Brewer, M.S. in E.E., Purdue, communications and electronics engineer, explores new designs for sea-bottom amplifiers needed to step up power of hundreds of simultaneous telephone conversations.

L. R. Snoke, B.S. in Forestry, Penn State, is the team biologist. He investigates the resistance of materials to chemical and microbiological attack in sea water. Materials are evaluated both in the laboratory and in the ocean.

E. E. Zajac, Ph.D. in Engineering Mechanics, Stanford, is a mathematician. He studies the kinematics of cable laying and recovery. Cable's dynamic characteristics, ship's motion, the mountains and valleys in the ocean bottom—all must be taken into account.

F. W. Kinsman, Ph.D. in Engineering, Cornell, solves the shipboard problems of storage, handling and "overboarding" of cable. New machinery for laying cable is being developed.

Deep-sea cables once were limited to transmitting telegraph signals. Bell Labs research gave the long underseas cable a voice. New research and development at the Labs will make this voice even more useful.



BELL TELEPHONE LABORATORIES

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT

NEW! 12-WATT Williamson-type HIGH FIDELITY INTEGRATED AMPLIFIER HF12




with Preamplifier, Equalizer & Control Section

KIT \$34⁹⁵ WIRED \$57⁹⁵

Compact, beautifully packaged & styled. Provides complete "front-end" facilities and true high fidelity performance. Direct tape head & magnetic phono inputs with NARTB (tape) & RIAA (phono) feedback equalizations. 6-tube circuit, dual triode for variable turnover bass & treble feedback-type tone controls. Output Power: 12 w cont., 25 w pk. IM Dist. (60 & 6000 cps @ 4:1): 1.5% @ 12 w; 0.55% @ 6 w; 0.3% @ 4 w. Freq. Resp.: 1 w: ±0.5 db 12 cps - 50 kc; 12 w: ±0.5 db 25 cps - 20 kc. Harmonic Dist.: 20 cps: 2% @ 4.2 w; 1/2% @ 2.5 w; 30 cps: 2% @ 11 w; 1/2% @ 6.3 w; 40 cps: 1% @ 12 w; 1/2% @ 9.3 w; 2000 cps: 1/2% @ 12 w; 10 kc: 1% @ 10 w; 1/2% @ 6 w. Transient Resp: excellent square wave reproduction (4 usec rise-time); negligible ringing, rapid settling on 10 kc square wave. Inverse Feedback: 20 db. Stability Margin: 12 db. Damping Factor: above 8, 20 cps - 15 kc. Speaker Connections: 4, 8, 16 ohms. Tone Control Range: @ 10 kc, ±13 db; @ 50 cps, ±16 db. Tubes: 2-ECC83/12AX7, 1-ECC82/12AU7, 2-EL84, 1-EZ81. Size: HWD: 3 3/8" x 12" x 8 1/4". 13 lbs. Mounts in or out of cabinet.

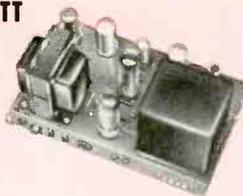NEW! 50-WATT Ultra-Linear HIGH FIDELITY POWER AMPLIFIER



HF50 KIT \$57⁹⁵ WIRED \$87⁹⁵

Like the HF60 shown below, the HF50 features virtually absolute stability, flawless transient response under either resistive or reactive (speaker) load, & no bounce or flutter under pulsed conditions. Extremely high quality output transformer with extensively interleaved windings, 4, 8, & 16 ohm speaker connections, grain-oriented steel, & fully potted in seamless steel case. Otherwise identical to HF60. Output Power: 50 w cont., 100 w pk. IM Distortion (60 & 6000 cps @ 4:1): below 1% at 50 w; 0.5% @ 45 w. Harmonic Dist.: below 0.5% between 20 cps & 20 kc within 1 db of rated power. Freq. Resp. at 1 w: ±0.5 db 6 cps - 60 kc; ±0.1 db 15 cps - 30 kc at any level from 1 mw to rated power; no peaking or raggedness outside audio range. All other specs identical to HF60 below. Matching cover Model E-2, \$4.50.



NEW! 50-WATT Ultra-Linear HIGH-FIDELITY

INTEGRATED POWER AMPLIFIER HF52 with Preamplifier, Equalizer & Control Section

Combines a power amplifier section essentially identical to the HF50 power amplifier with a preamp-equalizer control section similar to HF20 below. Provision for use with electronic crossover network & additional amplifier(s). See HF50 for response & distortion specs; HF60 for square wave response, rise-time, inverse feedback, stability margin, damping factor, speaker connections; HF20 for preamplifier, equalizer & control section description. Hum & noise 60 db below rated output on magnetic phono input (8 mv input for rated output), & 75 db below rated output on high level inputs (0.6 v input for rated output). Matching cover Model E-1, \$4.50.

7 NEW BEST BUYS by




NEW HIGH FIDELITY PREAMPLIFIER
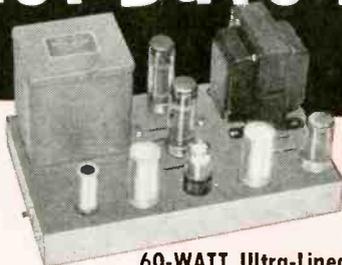
#HF61A KIT \$24⁹⁵, WIRED \$37⁹⁵

With Power Supply: #HF61 KIT \$29⁹⁵, WIRED \$44⁹⁵

Will not add distortion or detract from the wide-band or transient response of the finest power amplifiers at any control settings. High quality feedback circuitry throughout plus the most complete control & switching facilities. Heavy-gauge solid brushed brass panel, concentric controls, one-piece brown enamel steel cabinet for lasting attractive appearance. Feedback-type, sharp cut-off (12 db/octave) scratch & rumble filters. Low-distortion feedback equalization: 5 most common recording curves for LPs & 78s including RIAA. Low-distortion feedback tone controls: provide large boost or cut in bass or treble with mid-freqs & volume unaffected. Centralab printed-circuit Senior "Compentrol" loudness control with concentric level control. 4 hi-level switched inputs (tuner, tv, tape, aux.) & 3 low-level inputs (separate front panel low-level input selector permits concurrent use of changer & turntable). Proper pick-up loading & attenuation provided for all quality cartridges. Hum bal. control. DC superimposed on filament supply. 4 convenience outlets. Extremely flat wideband freq. resp.: ±1 db 8-100,000 cps; ±0.3 db 12-50,000 cps. Extremely sensitive. Negligible hum, noise, harmonic or IM distortion. Size: 4-7/8" x 12-5/16" x 4-7/8". 8 lbs.



60-WATT Ultra-Linear

HIGH FIDELITY POWER AMPLIFIER #HF60 with ACRO TO-330 OUTPUT TRANSFORMER KIT \$72⁹⁵ WIRED \$99⁹⁵

Superlative performance, obtained through finest components & circuitry. EF86 low-noise voltage amplifier direct-coupled to 6SN7GTB cathode coupled phase inverter driving a pair of Ultra-Linear connected push-pull EL34 output tubes operated with fixed bias. Rated power output: 60 w (130 w peak). IM Distortion (60 & 6000 cps @ 4:1): less than 1% at 60 w; less than 0.5% at 50 w. Harmonic Distortion: less than 0.5% at any freq. between 20 cps & 20 kc within 1 db of 60 w. Sinusoidal Freq. Resp.: at 1 w: 35 kc at any level from 1 mw to rated power; no peaking or raggedness outside audio range. Square Wave Resp.: excellent from 20 cps to 25 kc, 3 usec rise-time. Sensitivity: 0.55 v for 60 w. Damping Factor: 17. Inverse Feedback: 21 db. Stability Margin: 16 db. Hum: 90 db below rated output. ACRO TO-330 Output Transformer (fully potted). Speaker Taps: 4, 8, 16 ohms. GZ34 extra-rugged rectifier (indirectly-heated cathode eliminates high starting voltage on electrolytics & delays B+ until amplifier tubes warm up). Input level control. Panel mount fuse holder. Both bias and DC - balance adjustments. Std octal socket provided for pre-amplifier power take-off. Size: 7" x 14" x 8". 30 lbs. Matching cover Model E-2 \$4.50.



NEW

COMPLETE with Preamplifier, Equalizer & Control Section 20-WATT Ultra-Linear Williamson-Type HIGH FIDELITY AMPLIFIER #HF-20

KIT \$49⁹⁵ WIRED \$79⁹⁵

A low-cost, complete-facility amplifier of the highest quality that sets a new standard of performance at the price, kit or wired. Rated Power Output: 20 w (34 w peak). IM Distortion (60 & 6000 cps/4:1) at rated power: 1.3%. Max. Harmonic Distortion between 20 & 20,000 cps at 1 db under rated power: approx. 1%. Mid-band Harmonic Distortion at rated power: 0.3%. Power Response (20 w): ±0.5 db 20-20,000 cps; ±1.5 db 10-40,000 cps. Freq. Resp. (1/4 w): ±0.5 db 13-35,000 cps; ±1.5 db 7-50,000 cps. 5 feedback equalizations for LPs & 78s. Low-distortion feedback tone controls: large boosts or cuts in bass or treble with mid-freqs. & volume unaffected. Loudness control & separate level set control on front panel. Low Z output to tape recorder. 4 hi-level switched inputs: tuner, tv, tape, aux; 2 low-level inputs for proper loading with all cartridges. Hum bal. control. DC superimposed on filament supply. Extremely fine output transformer: interleaved windings, tight coupling, careful balancing, grain-oriented steel. 8 1/2" x 15" x 10". 24 lbs. Matching cover Model E-1, \$4.50.

NEW COMPLETE with FACTORY-BUILT CABINET - 2-WAY HI-FI SPEAKER SYSTEM #HF51 \$39⁹⁵

See the "BEST BUYS" NOW IN STOCK at your nearest distributor. Fill out coupon on other side for FREE CATALOG.

Prices 3% higher on West Coast.



Genuine 2-way book-shelf size speaker system. Jensen heavy duty 8" woofer (6.8 oz. magnet) & matching Jensen compression-driver exponential horn tweeter with level control. Smooth clean bass & crisp extended highs free of coloration or artificial brilliance. Factory-built tuned bass reflex birch hardwood cabinet (not a kit) constructed to high quality standards. Neutral acoustical grille cloth framed by a smooth-sanded solid birch molding. Freq. Resp. measured 2 ft. away on principal axis in anechoic chamber with 1 watt input - Woofer: ±4 db 80-1800 cps; Tweeter: ±2 db 2800-10,000 cps; Crossover Region: 1800-2800 cps, shift in level over this region depends on tweeter level control setting. Power-handling capacity: 25 watts. Size: 23"x11"x9". 25 lbs. Wiring Time: 15 min.


33-00 Northern Blvd., L.I.C. I, N.Y.



Turn page for other EICO ad.

the specs prove it . . .
 your BEST BUY is
EICO®

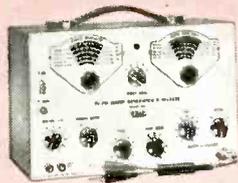for COLOR & Monochrome TV servicing
FREE CATALOG
 shows you HOW TO SAVE 50%
 on 50 models of top quality
 professional test equipment.
MAIL COUPON NOW!




NEW!
**TV-FM SWEEP
 GENERATOR &
 MARKER #368**
 KIT \$69⁹⁵ WIRED \$119⁹⁵

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional tuning accuracy: edge-lit hairlines eliminate parallax. Sweep Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, scope horiz., scope vertical. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

**NEW! RF
 SIGNAL GENERATOR
 #324**
 KIT \$26⁹⁵ WIRED \$39⁹⁵



150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble-shooting of TV, FM, AM sets; marker gen.: 400 cps audio testing; lab. work. 6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to ±1.5%; 6:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial. Plexiglass windows, edge-lit hairlines. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. amplifier: only 3.0 v needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

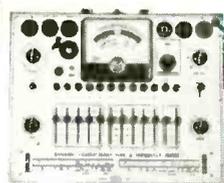

**NEW! DYNAMIC
 CONDUCTANCE
 TUBE & TRANSISTOR
 TESTER #666**
 KIT \$69⁹⁵ WIRED \$109⁹⁵

COMPLETE with steel cover and handle.
 SPEED, ease, unexcelled accuracy & thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Cp & peak emission. Simultaneous set of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: freepoint connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollechart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. CRA Adapter \$4.50



NEW!
**COLOR
 and Monochrome
 DC to 5 MC LAB & TV
 5" OSCILLOSCOPE
 #460**
 KIT \$79⁹⁵ WIRED \$129⁵⁰

• Features DC Amplifiers!

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull thru-out; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V&H positions; auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite graph screen; dimmer; filter; bezel fits std photo equip. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control.



**NEW! PEAK-to-PEAK
 VTVM #232 & UNI-
 PROBE (pat. pend.)**
 KIT \$29⁹⁵ WIRED \$49⁹⁵

Half-turn of probe tip selects DC or AC-Ohms.

Uni-Probe - exclusive with EICO - only 1 probe performs all functions!

Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4 1/2" meter, can't burn-out circuit. 7 non-skip ranges on every function. 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms. Uniform 3 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet.



**5" PUSH-PULL
 OSCILLOSCOPE
 #425**
 KIT \$44.95
 Wired \$79.95




**7" PUSH-PULL
 OSCILLOSCOPE
 #470**
 KIT \$79.95
 Wired \$129.50

**TUBE TESTER
 #625**
 KIT \$34.95
 Wired \$49.95

- tests 600 mil series string type tubes
- illuminated roll-chart

Pix Tube Test Adapter \$4.50

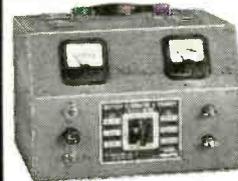

Sep. volt-meter & ammeter
 KIT \$29.95
 Wired \$38.95

**6V & 12V BATTERY ELIMINATOR &
 CHARGER #1050**



Sep. hi-gain RF & lo-gain audio inputs. Special noise locator. Calibrated wattmeter.
 KIT \$24.95
 Wired \$39.95

DELUXE MULTI-SIGNAL TRACER #147



**20,000 Ohms/Volt
 MULTIMETER #565**
 KIT 24.95
 Wired \$29.95

**1000 Ohms/Volt
 MULTIMETER
 #536**
 KIT \$12.90
 Wired \$14.90



Reads 0.5 ohms -500 megs, 10 mmdf-5000 mfd, power factor.

KIT \$19.95
 Wired \$29.95

**R-C BRIDGE & R-C-L COMPARATOR
 #950B**



| VTVM PROBES | KIT | Wired |
|----------------------|--------|--------|
| Peak-to-Peak | \$4.95 | \$6.95 |
| RF | \$3.75 | \$4.95 |
| High Voltage Probe-1 | | \$6.95 |
| High Voltage Probe-2 | | \$4.95 |

| SCOPE PROBES | KIT | Wired |
|--------------|--------|--------|
| Demodulator | \$3.75 | \$5.75 |
| Direct | \$2.75 | \$3.95 |
| Low Capacity | \$3.75 | \$5.75 |

EICO, 33-00 Northern Blvd., Long Island City 1, N. Y. C-10

Show me HOW TO SAVE 50% on Test Equipment and Hi-Fi. Send me FREE Catalog and name of neighborhood distributor.

Name.....
 Address.....
 City..... Zone..... State.....

TURN PAGE
 FOR MORE
 EICO VALUES



Send for
FREE CATALOG
 now

Prices 5% higher on West Coast.

33-00 Northern Blvd., Long Island City 1, N.Y.

HIGH-FIDELITY SOUND

... *A New Approach to Higher Fidelity* ...

THE basic principles of sound reproducers in use today for audio high-fidelity acoustics are comparatively ancient, as viewed by modern audio engineering. Only two fundamental principles are used in loudspeakers common today. The first is Dr. Alexander Graham Bell's electromagnetic telephone of 1876, now adapted into a loudspeaker. Bell's old vibrating 2-inch-diameter iron diaphragm has been expanded into a large vibrating cone (the latter is attached to a voice coil which floats in the magnetic field.) Roughly the same principle, however, remains. The second is Prof. Amos Emerson Dolbear's 1879 condenser (capacitance) telephone which worked on the "static" principle. It had two 2-inch iron or steel diaphragms separated about $\frac{1}{8}$ inch. One diaphragm was fixed, the other left free so it could vibrate. The transmitting line was connected to the two diaphragms. This astonishingly simple telephone worked exceedingly well. The same principle is used in our electrostatic loudspeakers today in a highly refined form.

As we all know, our modern loudspeaker reproducers—good as they are—leave much to be desired. They do not reproduce with complete fidelity—they only approximate in fact. The sound reproduction is a compromise. Indeed, if we wish the best reproduction possible with present-day means, we must use several reproducers simultaneously, one (or more) for the lower notes plus one (or more) for the higher register.

The main reason for this deficiency is that up to now we have no *inertialess* loudspeakers, with the possible exception of Siegfried Klein's *Ionophone*, which works on a combination of molecular motion and thermo effects. Unfortunately, it requires a very large horn, if it is to cover the full range.*

As we see it, we should dissociate ourselves from the fixed idea prevalent for over 80 years that we must move large masses of air in order to hear. Hence our present-day loudspeaker cones which we fashion to "grip" the surrounding atmosphere.

Have you ever placed your ear tightly to a solid wood telegraph or telephone pole and listened to the loud "singing" wires 40 feet above your head? This is sound conduction (often molecular) through a solid. Several decades ago, the same interesting phenomenon occurred when boys, living on the prairie, placed their ears against a rail on the ground to listen to an invisible oncoming (or receding) train many miles away. And the sound often was very loud, too. (Today's modern railroad signalling requires insulated joint bars between the rails. This cuts down long-distance sound reception.)

The writer made use of this principle when he patented the *Osophone*, in 1923, the first bone-conduction speaker, which near-deaf people held between their teeth. They could hear speech or music well, entirely through the osseous part of the cranium.

Another interesting example can be cited. Many years ago, we visited an experimenter friend of ours on Long Island. He was living in an old house supported in the cellar by several large round wooden beams, each about 8 inches in diameter. To the center post he had attached a large loudspeaker in such a manner that the speaker's armature was fixed solidly into the wooden pole. The loudspeaker itself was supported by the cement floor. The result: music and sound were propagated clearly through the entire house. The sound—and radio—could be switched off or on from any room on all floors.

These examples are given merely to illustrate how sound can be propagated in the absence of air. What we are trying to say is that the orthodox "grip" on the air by means of large vibrating "driver" surfaces is not necessarily a future requirement of high-fidelity loudspeakers.

At the same time, it is true that humans, immersed in ambient air, normally hear best when sound vibrations impinge via air columns of their ears onto their tympanums. But it makes no difference *how* the sound waves are propagated, or by what means, so long as the end result—high-fidelity sound reproduction—is perfect, or at least near perfect.

It would appear that inertialess molecular speakers would stand the best chance of succeeding in the end. The reasons seem obvious. Today's ideal audio reproducer is called upon to re-create faithfully tens of thousands of different sounds in every imaginable combination, with all sorts of overtones, resonances, timbres and intensities, in frequencies from 2 to 20,000 cycles. This seems an impossible task for a single vibrating or oscillating surface or set of surfaces. They cannot faithfully reproduce at the same time an entire orchestra with all its various instruments, plus a large singing chorus. At best we get an approximation, but a large percentage of *true* tones are lost.

An oscillating cone or surface swings to and fro. *It has inertia*. This requires time. During the long swing, on a low note, the cone must also vibrate at a higher rate to reproduce higher notes that may have to be reproduced simultaneously. They are thus out of phase, hence are not fully rendered. The molecular speaker on the other hand has no parts that move. It is inertialess, hence it cannot be out of phase.

This brings to mind a very early molecular type of inertialess telephone. Th. Du Moncel, in the magazine *Le Téléphone* (Paris, 1882) reported the invention as follows: "To convince himself whether the telephone effect of his instrument was based upon molecular or transverse vibrations, in the 1880's, Dr. Clément Ader, the French inventor, constructed a telephone without diaphragm or membrane; with it he could reproduce only articulated sounds, but not the human voice. Soon, however, by changing his central magnetic rod to various dimensions, he noticed that the intensity of the reproduction increased as the diameter of the magnetic rod was reduced. Finally, he used an iron wire only 1 millimeter in diameter. By rigidly fixing the wire in his instrument, reproduction of the voice and words became audible. The effect was even better when he fixed the iron wire rigidly at the top and weighted the free end with a large and heavy metal mass. The iron wire itself was surrounded along its middle by an induction coil which did not touch the iron wire."


Du Moncel explained the action as follows: "The molecular oscillations of the iron wire are principally effective along its longitudinal axis. They propagate themselves faster than normal (transverse) oscillations which are communicated to the inert metal mass; this action results in minute shocks which amplify the mechanical effect of the oscillations in the iron wire. The resulting total effect of the suspended metal mass then communicates itself along the iron wire to the upper fixed suspension of the wire, which is a solid block of copper. From here on, audio oscillations result which are now transmitted to the surrounding air by the instrument. There is of course no horn but instead a small wooden saucer-like surface."

It is to be hoped that future audio loudspeaker research will be in the molecular direction. It holds great hope for high fidelity.

—H.G.

*See also the editorial "Wanted—Inertialess Speakers," RADIO-ELECTRONICS, October, 1953.

All Transistor Tape-Head Preamp

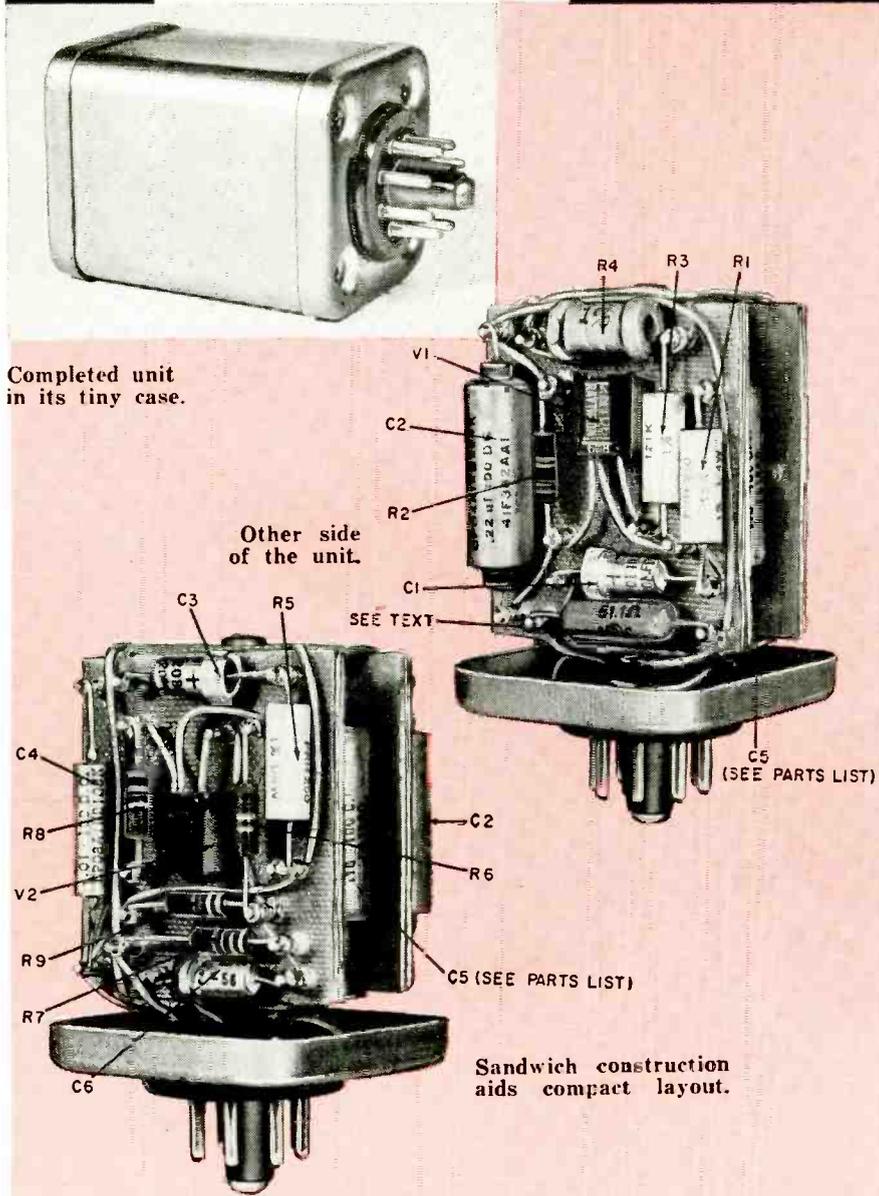

Completed unit in its tiny case.

Other side of the unit.

Sandwich construction aids compact layout.

Miniature two-stage preamp plugs into an octal socket

By FRANCIS A. GICCA *

AN ideal use for the transistor, in the audio field, is in a tape recorder preamp. Let's look at some requirements of a good tape preamp and we'll quickly see why a transistor unit can outperform its vacuum-tube cousin.

A tape head is a low-impedance device—usually about 500 ohms. For optimum performance it's important for a preamp to have a similar input impedance. High-frequency response of the head suffers seriously unless it is matched to a low-impedance preamp input.


Generally, it is not the mechanical gap width of the head that limits the high-frequency response, but the stray capacitance across the head's windings. For example, a typical tape head has a mechanical gap width of .0002 inch, a resistance of 500 ohms and a stray capacitance across the windings of 20 μ f. This head at 7½ ips has a mechanical gap cutoff frequency of 37,500

cycles ($f_{co} = \frac{7.5}{\text{gap-width}}$). With a preamp that has an input impedance of 1 megohm, the head's stray capacitance will cause the half-power point (3 db down) to be about 8,000 cycles. But, if our preamp has an input impedance of 500 ohms, the half-power point becomes about 16 mc. This allows the head's mechanical gap width to be the dominant high-frequency limitation.

For a vacuum-tube preamp to have an input impedance of 500 ohms we must use an input transformer. A good, wide-range input transformer is expensive. It easily picks up stray hum fields and we may lose high-frequency response in the transformer's secondary due to its stray capacitance. On the other hand, a grounded-emitter transistor stage has, by its very nature, a low input impedance.

Noise and hum are two other important problems. The NARTB tape-playback characteristic helps to minimize noise by calling for a 10-db gain reduction at 10,000 cycles. Vacuum tubes are noisiest at these higher frequencies—the thermal-noise region. A 10-db gain reduction at 10,000 cycles reduces the effect of this noise.

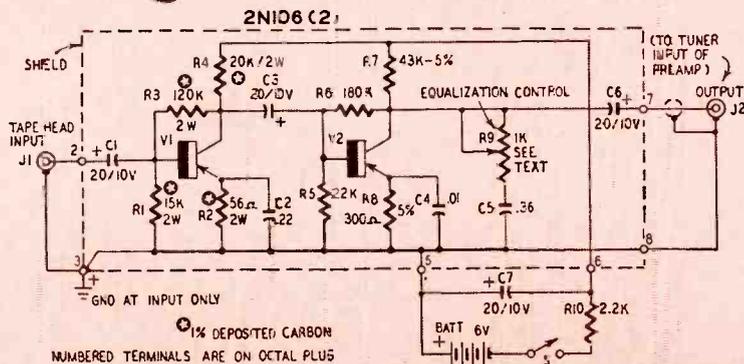Transistors have about the same noise problems as vacuum tubes. It is true that transistors generally have more noise at low frequencies than



- R1—15,000 ohms, 2 watts, deposited carbon
 - R2—56 ohms, 2 watts, deposited carbon
 - R3—120,000 ohms, 2 watts, deposited carbon
 - R4—20,000 ohms, 2 watts, deposited carbon
 - R5—22,000 ohms
 - R6—180,000 ohms
 - R7—43,000 ohms, 5%
 - R8—300 ohms, 5%
 - R9—pot, 1,000 ohms, linear taper, see text
 - R10—2,200 ohms
- All resistors ½ watt unless noted

- C1, 3, 6, 7—20 μ f, 10 volts, electrolytics
- C2—0.22 μ f, 100 volts
- C4—0.1 μ f, 100 volts
- C5—0.36 μ f, 100 volts; two 0.18- μ f in parallel or 0.25 μ f and 0.1 μ f in parallel
- J1, 2—RCA-type phono jacks
- S—spst, toggle
- V1, 2—2N106
- BATT, 6 volts
- Plug, octal
- Case, 1½ x 1½ x 2½ inches or larger

Fig. 1—Preamp circuit with a positive ground.

* Electronics development engineer, Raytheon Manufacturing Co.

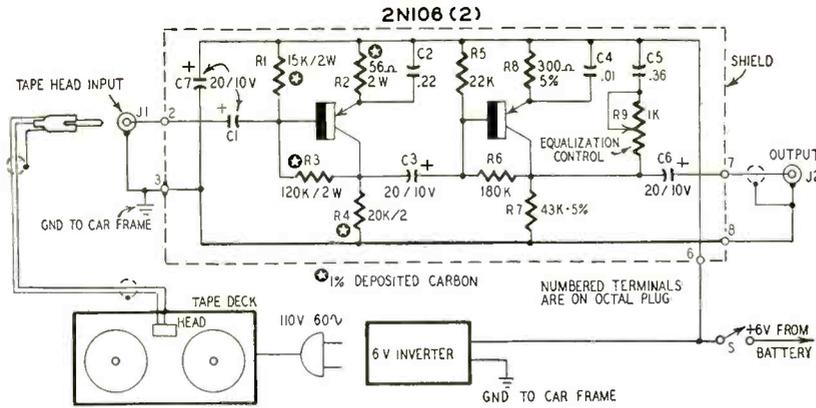


Fig. 2—Negative-ground circuit hooked to tape deck and inverter for auto use.

tubes, but the most noticeable noise also occurs at high frequencies. The Raytheon type 2N106 transistor is a new low-noise type developed especially for high-fidelity audio applications. When used with the NARTB tape-playback curve, it will have a signal-to-noise ratio of about 55 db, which is quite acceptable for a tape preamp.

Hum is much more of a problem, for the NARTB characteristic calls for 23 db of bass boost at 60 cycles. Unless a vacuum-tube preamp is very carefully wired or dc used for the heater, hum will be objectionable. The hum signal-to-noise ratio for a tube preamp can be as bad as 30 db. If we're willing to use a battery supply for a transistor preamp and shield the unit from stray hum fields, there will be no hum due to the preamp. This is extremely desirable—another victory for transistors.

Design features

A transistor preamp should be designed so that it can drive high-level inputs of audio control units, since most high-fidelity installations use such a control unit as the master control center for the system. Since the average tape head has about a 5-mv output at 1,000 cycles, preamp gain of 32 db at this frequency would provide 0.2 volt of signal to the control unit. This is adequate for all control units.

The NARTB tape characteristic calls for a maximum bass boost 26 db above the 1,000-cycle reference level, so our preamp must have a maximum gain of 58 db at extremely low frequencies to give an output of 0.2 volt. With careful design two 2N106 transistors supply this gain.

The grounded-emitter configuration was chosen as it has a low input impedance, high gain and is relatively stable. Bias current for the transistor base is obtained by using a resistive divider from the collector to ground. This type of biasing circuit also applies both dc and ac stabilizing negative feedback around the stage, helping to minimize transistor drift and individual variations. The use of emitter feedback in the form of a series emitter resistor also adds stability and allows us to adjust each stage for maximum flat frequency response by properly bypassing the emitter resistor.

To obtain the NARTB tape-playback

characteristic we use a simple R-C shaping circuit between V2's collector and ground. Since the NARTB curve follows the ideal 6-db-per-octave curve of an R-C network such an equalization circuit is simple and very effective for achieving the right response.

The circuit is shown in Fig. 1. Its overall simplicity is evident and its performance leaves nothing to be de-

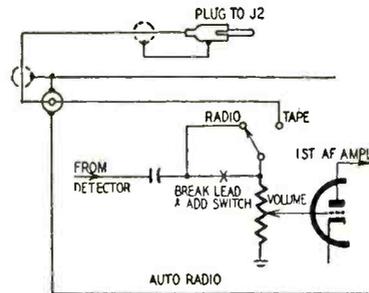


Fig. 3—Switching arrangement using car radio as tape recording amplifier.

sired. It follows the NARTB characteristic within 1 db from 20 to 20,000 cycles, has an overall signal-to-noise ratio of better than 55 db which includes no hum and provides the necessary 0.2 volt at 1,000 cycles to drive an audio control unit. No gain control is used since the audio control unit already has one.

An interesting application for this tape preamp is as part of a hi-fi tape player for your car. Since only 6 volts are required for the supply voltage, the car battery can power the preamp. Due to the unit's simplicity, it can be built into a tape deck. Then all you need do is power the tape deck's transport motor with an inverter and install a

switch in your car radio to connect the preamp to your radio's power amplifier.

The preamp will have to be modified slightly to operate with a negative ground. Fig. 2 shows this circuit. (For cars with a positive ground, the Fig. 1 circuit can be used.—Editor)

To modify your car radio for a tape player system, merely break the lead from your radio's volume control, and add a switch between this lead and the detector stage to allow you to switch from the radio to the preamp. This wiring change is shown in Fig. 3.

If your car has a 12-volt battery, insert a 15,000-ohm 2-watt resistor between the battery and the preamp power input and use a 12-volt inverter.

Construction details

There are many ways in which the transistor preamp can be built. I constructed my model using two phenolic boards with spacers glued between them. (Perforated bakelite boards can be used.—Editor) This allowed me to mount the entire preamp in a 1½ x 1½ x 2½-inch Mumetal case. This was a junkbox item. A small Bud Minibox is just as good. Input, output and power leads are brought into the preamp through an octal plug.

A conventional chassis will do just

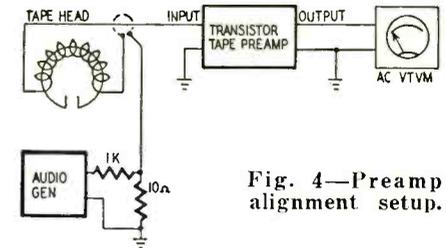


Fig. 4—Preamp alignment setup.

as well. The finished size is larger than the phenolic-sandwich type of construction, but a lot easier to build. It is wise to plan your layout so that the finished chassis will fit into a miniature case. The shielding from stray hum pickup, obtained by enclosing the preamp in a case is well worth the small cost.

To keep the input transistor noise low, use 1% deposited-carbon resistors for R1, R2, R3 and R4.

Be sure to use a single wire as a ground bus. Connect all grounds to this wire which should be connected to the chassis only at pin 3 of the octal plug. This eliminates hum from the

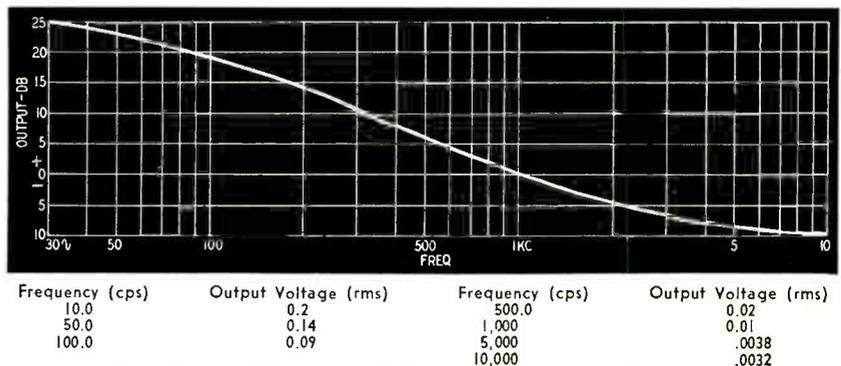


Fig. 5—NARTB curve followed for proper alignment.

AUDIO—HIGH FIDELITY

ground loops.

The EQUALIZATION CONTROL (R9) can be replaced by a nominal resistance. In the unit constructed an equalization control was not used. Instead, space was provided for a conventional resistor, and the proper value was soldered in to yield the standard NARTB tape curve.

If you use a resistor for R9, it must be chosen for the proper NARTB playback curve. To do this, insert a 10-ohm resistor in the ground lead from the playback head, as shown in Fig. 4. Connect an audio generator to this resistor through a 1,000-ohm resistor. Connect an ac vtvm to the preamp's output. The vtvm should have a flat response to at least 10,000 cycles. Set the audio generator to 1 kc and adjust its output control so that the vtvm reads .01 volt rms.

Temporarily, use a 1,000-ohm potentiometer for R9 and set the audio generator to the frequencies listed on the chart in Fig. 5. Adjust the potentiometer to obtain the output voltages listed. If the output at 100 cycles is greater than .09 volt rms, there is not enough resistance. If the output is less than .09, there is too much resistance. Continue adjusting the resistor until you get readings closest to those listed on the chart, or read on the curve. Each time you change R9, be sure to return the generator to 1 kc and readjust its output for a reading of .01 volt rms on the vtvm. When the proper setting is found, measure the pot and replace it with a 1% fixed resistor of equal value. The preamp now follows the NARTB characteristic.

If your audio control unit has tone controls, then it is a good idea to remove the equalization control to avoid interaction between tone and equalization controls. If the preamp is used as part of an automobile tape player, the equalization control is handy for adjusting tone to suit noise conditions.

To avoid ground loops between the head and the preamp use two-conductor shielded cable between them. Connect the hot lead from the head to one wire of the two-conductor cable, and the ground lead from the head to the other wire of the cable. The shield and ground lead should be soldered to the input's ground, but do not connect the shield to the recorder chassis.

The preamp's output impedance is fairly low and a relatively long lead can be used from the unit to an audio control unit or car radio. Up to 10 feet of shielded cable can be used without any loss of high-frequency response.

The 51-ohm resistor across the preamp input in the photos is a terminating resistor and is unnecessary. It was placed across the input to allow response runs with an audio oscillator.

Now all that's left is the listening. You have a tape preamplifier that is superior to vacuum-tube types in all respects. The preamp draws little current and the 6-volt battery lasts about a year under normal usage. END

Bass Reproduction in Loudspeakers

By EDGAR VILLCHUR*

*One view on the relationship between
cone excursion and bass reproduction*

THE Correspondence column of the May, 1957, issue of this magazine contained a letter from Paul W. Klipsch which I read with considerable interest. The issues raised are both important and fundamental and deserve treatment at some length. I subscribe entirely to the accuracy of the data quoted, but cannot agree with Mr. Klipsch's conclusions.

It has been known for a long time that a speaker cone must move increasingly greater distances as the frequency enters the bass regions. This relationship (among others) was pinned down in 1942 by Frank Massa in his classic book *Acoustic Design Charts*.

Chart No. 61 of Massa's book shows the relationship between the acoustic output of a vibrating diaphragm, in watts, to the distance of travel at various frequencies. Mr. Klipsch specifically points out in his letter, on the basis of the above, that the excursion required of a directly radiating 12-inch speaker cone, for 1 acoustic watt at 30 cycles, is 2.8 inches.

These figures are as accurate today as when they were published 15 years ago, but they must be interpreted with the same rigor that was used in their original formulation. They do *not* mean that a 12-inch loudspeaker cone has to vibrate over the impractical distance of almost 3 inches to reproduce 30-cycle energy at concert level in the home. If this were so, direct-radiator speakers would be incapable of reproducing the pedal line of a pipe organ or the explosive thud of a bass drum.

Bass power

The amount of bass power created by a speaker cone depends upon three things: (1) the cone travel, or excursion, relative to the frequency, (2) the size of the cone and (3) the solid angle in which the speaker is mounted. The significance of the first two factors is fairly obvious since the larger the cone, and the farther it moves, the more air will be pumped back and forth. The third factor is equally significant but the reasons for it being so are not as obvious.

Consider the hypothetical situation in which a loudspeaker system (including

*Acoustic Research, Inc., Cambridge, Mass.

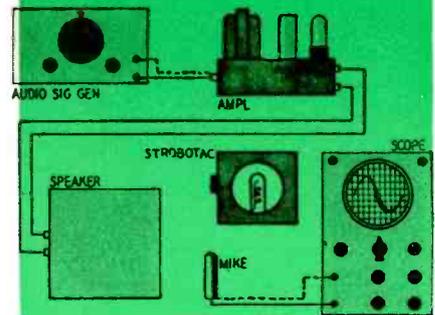


Fig. 1—Test setup for checking linearity of speaker sound output in relation to cone excursion.


enclosure) is suspended on a rope, in the center of the universe. There will be a tendency for energy at higher frequencies to be concentrated in the area directly ahead of the speaker, but bass frequencies will be radiated equally in all directions. Bass sound levels in front of the speaker are thus watered down relative to the treble by their better dispersion and are weaker in comparison.

Now let us place the speaker system behind an infinite baffle so that the speaker looks out on only half the universe. The treble portion of the signal will not be concentrated any more than it would be by the natural directive characteristics of the speaker but the bass, which was formerly radiated in all directions, is now restricted. The cone gets a better bite of the air that it engages at low frequencies and the area in front of the speaker receives a double concentration of bass.

Following the same analysis, halving the solid angle of radiation once more doubles the bass power again.

Translated into practical terms, this means that, when a speaker is mounted in a two-sided corner (such as at the junction of the floor and wall), the bass power radiated into the room, with given excursions, will be doubled compared to that produced by a speaker mounted in the center of a flat wall. If

Fig. 2—Waveform of speaker output using test setup shown in Fig. 1. Speaker mounted in 45° corner. Cone excursions are ½ inch. Input power is 39 watts to rated impedance.

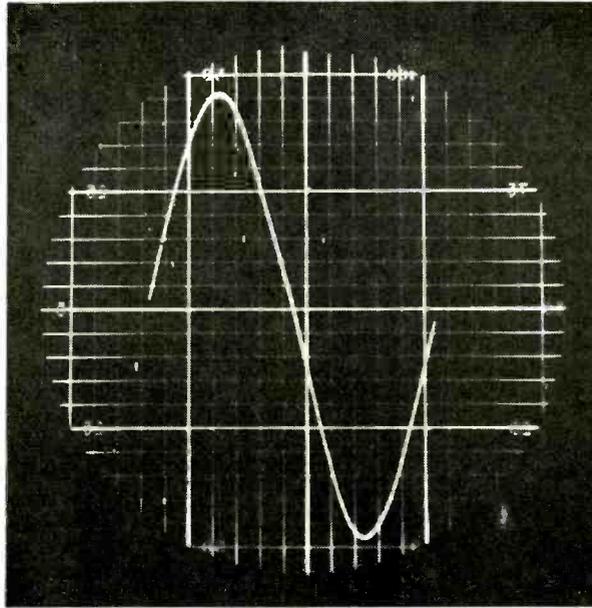

the speaker is mounted in a three-sided corner—the junction of two walls and the floor, for example—the bass power will be quadrupled.*

Massa is very explicit about the solid angle seen by his radiating diaphragm, as he must be for his data to be meaningful. The figures he gives us are for diaphragms radiating into 180° or, as he puts it, into semi-infinite space. His figures can thus only be applied to practical speakers in the mid-wall position. If we place our speaker in a corner on the floor, the same 2.8 inches of cone excursion will radiate an effective 4 watts of acoustic power at 30 cycles, rather than 1 watt.

The order of magnitude of acoustic power that we are discussing here is tremendous and, for a living room of even large size, literally ear-shattering. Massa's book also contains data on the number of acoustic watts required for musical reproduction at concert-hall level, in rooms of various sizes and reverberation periods (Chart No. 72). For a typical living room of, say 3,000 cubic feet, we would require about 0.4 acoustic watt total sound power.

Required cone excursion

It is highly unlikely that all of the sound would ever appear at 30 cycles. Assuming, however, that it did, we would require cone excursions of 0.8 inch peak to peak with the speaker mounted in a corner. If we used a more reasonable assumption, that no more than half of the total power would appear at 30 cycles, we find that ½-inch excursions will give us just a bit less than the 0.2 acoustic watt required.

The \$64,000 question then becomes: Is a direct-radiator 12-inch loudspeaker capable of linear ½-inch excursions? Or, to put it another way, can such a speaker radiate clean 30-cycle energy when its cone has to vibrate over a distance of ½ inch?

The answer must be given in terms

*Leo L. Beranek, "Acoustics," McGraw-Hill Book Co., 1954, page 320.

of practical demonstration rather than theory. At least one commercial direct-radiator speaker system is capable of such linear excursions and demonstrations of this capability have been made before professional groups—an AES meeting at the New York Trades Show Building in September, 1956, and an IRE meeting at MIT in May, 1957.

The test setup that was used is shown in Fig. 1. The speaker is fed by a high-powered amplifier, driven from a signal generator tuned to 30 cycles. The resulting sound output of the speaker is picked up by a microphone and the waveform is displayed on an oscilloscope screen so that deviations from the sine-wave pattern may be observed. A *Strobotac* light, tuned a few cycles off frequency, is played on the speaker cone, visually converting the vibrations to a slow, clearly observable breathing.

Viewing moving parts under a *Strobotac* light is a common industrial technique. The speaker cone, of course, is still vibrating at 30 cycles, but the apparent velocity of each repeated vibration is slowed down to the point where each motion can be seen and the distance easily gauged.

Fig. 2 is a photograph of the scope trace produced by the output of the microphone in front of the speaker. This waveform represents actual sound output from the speaker when the cone is undergoing ½-inch excursions at 30 cycles, the speaker in a 45° corner. The amount of electrical power that had to be used to produce this sound is not really relevant to the discussion here but it happened to be 39 watts to the rated speaker impedance.

An analysis of the sound power capabilities of a 12-inch direct-radiator speaker must be put into the context of the current loudspeaker state of the art for final evaluation. In comparing this power capability with that of a horn, for example, we will find that a

properly designed horn system can produce a much higher sound level at low distortion—and with far less amplifier power—than the direct-radiator, down to the former's cutoff frequency. If, however, we explore response below the horn cutoff frequency (which is indirectly a function of horn size), we will discover that the horn rapidly ceases to load the driver and that there is a sharp falloff of response. This falloff is increased by the fact that the usual horn driver—unlike the direct-radiator speaker mechanism—does not have to be and is not designed for very large excursions.

30-cycle performance

Mr. Klipsch, in speaking of performance at 30 cycles, chose a frequency region particularly favorable to the direct-radiator speaker system. I believe that the absolute 30-cycle power capability of a really good direct radiator, at low distortion levels, is greater than that of any commercial horn small enough to be used in the home. A ½ octave higher, however, the power capability of a good horn would swamp that of the direct radiator.

As for Mr. Klipsch's joshing about a "miniature 32-foot wavelength," I have always appreciated his keen and often biting humor. I am sure, however, that Mr. Klipsch does not mean to infer that a speaker system must have physical dimensions comparable to the wavelength of the low-frequency sound it is designed to produce. There is no direct relationship between wavelength and the size of a direct-radiator speaker structure since enclosure resonance is not employed as a design element and horn-mouth reflections do not have to be considered. In the acoustic suspension system there is no such relationship whatsoever, direct or indirect. Massa's data clearly show that our 0.2 watt of 30-cycle acoustic energy can be radiated from a diaphragm of any size (1 inch, let us say) provided that the diaphragm can move far enough in a linear manner.

There has been a running battle in hi-fi circles between self-styled "horn men" and "long-throw infinite-baffle men," each type of combatant serving with devotion. The truth is that both of the design approaches represented are valid and each presents advantages over the other in particular applications. The point made in this article is that, when the problem is clean reproduction of 30-cycle energy (admittedly not too great in importance compared to other problems), a linear direct-radiator speaker system always has the advantage over a reasonably sized horn. END




This article—as the author points out—presents one view on the subject of bass reproduction. Another view is presented on page 44 by no less doughty a champion than Paul Klipsch himself.

Record Tracking



Improper tracking can hurt the quality of a hi-fi system. Learn why it does and how to check for it

By NORMAN H. CROWHURST

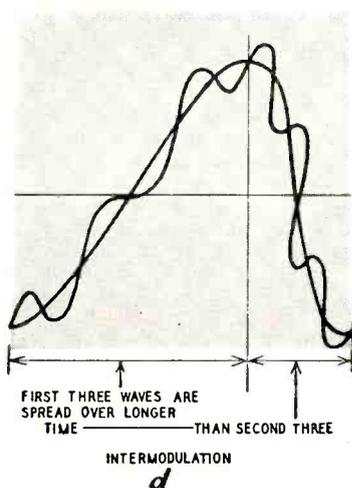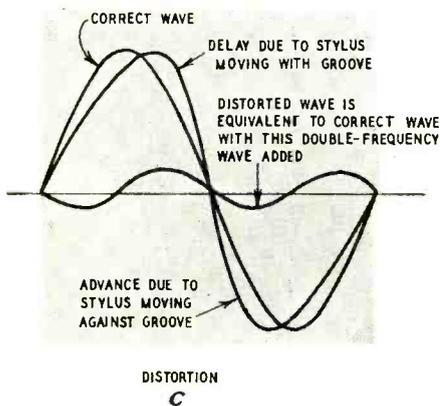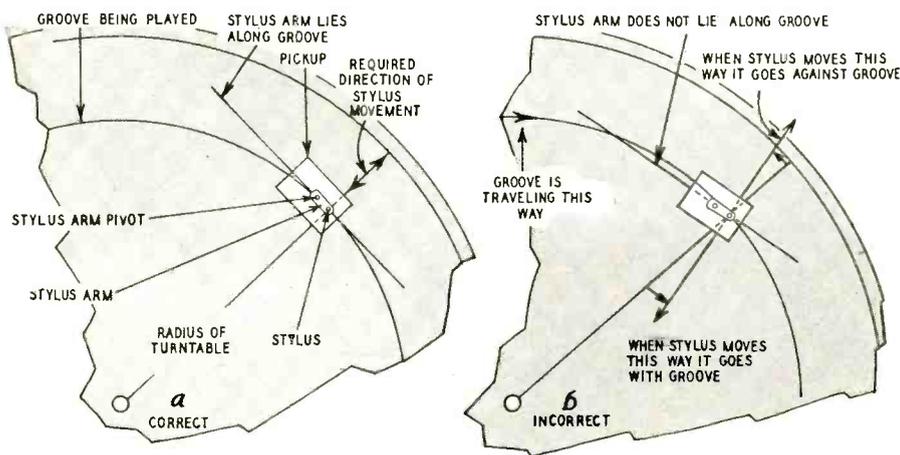

JUDGING from correspondence on the subject of mounting tone arms, there is some confusion about tracking—why records mistrack and how different constructions of tone arms and the method of mounting them obviate or minimize mistracking.

The record groove carries lateral vibrations that should move the stylus back and forth at right angles to the groove. As the groove is a very slight spiral and thus almost a perfect circle, with its center corresponding with the center of the disc, the stylus should move back and forth along a radius from the record's center.

All modern pickups carry the stylus on a stylus arm, pivoted so the arm moves over a relatively small arc. When the stylus arm is in line with the groove, the stylus moves at right angles to the groove. This relationship is illustrated in Fig. 1-a.

If the stylus arm gets out of line, the stylus movement is not at right angles to the direction of the groove. Then, as the modulation in the groove moves the stylus from side to side, it also moves it a little back and forth along the groove. At one point it will move with the disc and half a cycle later it will move against it (see Fig. 1-b).

This will distort sine-wave modulation in the groove so it has a slope as shown in Fig. 1-c. This is equivalent to adding a second-harmonic component to the groove modulation.

A small amount of second harmonic added to a sine wave is not very important. It is not audibly different from a pure sine wave. Because of the natural octave relationship, the ear identifies the two tones and cannot discriminate the second-harmonic component. The more important effect is due to what happens to other frequencies that may

Fig. 1—Correct and incorrect tracking and how it causes distortion.

be present with the same low-frequency sine wave.

Suppose the groove also contains a frequency six times as high as this low-frequency sine wave. This means there will be three waves going up the low-frequency wave and three waves coming down. The second harmonic, added by failure to track properly, results in frequency modulation of this higher frequency. The part of the low-frequency wave which is stretched out in time, due to the stylus tending to follow the groove round with the turntable, will take longer tracing its three cycles and thus momentarily produce a lower frequency than during the period when the stylus comes back again and momentarily makes the effective frequency higher (Fig. 1-d).

All the program, except the low-frequency tone which is causing it, gets frequency-modulated. This form of IM distortion produces a dithery effect in the reproduction, much like any other kind of IM distortion. This is why it is important that the stylus arm in the pickup should be in line with the groove, as nearly as possible, at all points across the record, so the stylus moves truly at right angles to the groove.

Producing good tracking

Now that we know what is wanted, let's examine different ways of doing it. The first thing to try is a straight arm with the pickup in line with the arm. This means the stylus moves at right angles to the end of the arm, as shown at Fig. 2. Variation of the mounting point will find different places across the groove at which the tracking is correct. At all other positions across the record (different radii of playing) the tracking will be incorrect.

By picking one radius and then moving the arm across the record, we can see which way the angle of stylus movement is in error. Note that the stylus arm or pickup head at a radius smaller than the correct one requires to be offset outward; while at a larger radius than the correct one it requires to be offset inward. The error is approximately proportional to the deviation from correct radius (Fig. 3).

The first step toward improving this situation uses an offset. The pickup is mounted at an angle to the end of the arm (and the mounting point for the arm has to be altered). If we put a considerable offset on, we can see why the right offset corrects matters very considerably.

Using too much offset, as shown in Fig. 4, there will again be only one radius of correct tracking for any particular mounting position of the arm. But this time, when the pickup is playing at a smaller radius the offset has to be more inward than that actually used. At a radius larger than the correct one the offset has to be more outward. We have reversed the situation that prevailed with the straight arm.

Somewhere in between these two extremes the offset will be much nearer to correct all the way across the record. This is what determines the correct offset, as shown by Fig. 5. This time we set the arm mounting to give perfect tracking at one radius near the middle of the playing area of the record. Then the deviation is very much smaller and also it is in the same direction, whether you go inside or outside the correct radius. Both ways the angle of offset should be a little bit more inward. But the deviation from correct has become extremely slight.

An even closer approximation to correct tracking can be achieved by slightly moving the mounting point for the arm, putting it a small fraction of an inch further from the turntable's center, the offset slightly incorrect at the center of the playing band. Now there will be two points across the record where the offset is correct and it will be incorrect at the inside, the center and the outside of the playing band. The direction of deviation will be the same at the inside and outside and in the opposite direction of the center of the playing area.

This reduces the maximum angle of tracking error to a very small amount—about 1° or less, depending upon the dimensions of the arm and the record. At this point it should be mentioned that it is immaterial, as far as tracking is concerned, whether the pickup is mounted at an angle, on a straight arm or in line with the end of a curved arm, provided the basic geometry is the same (Fig. 6).

When the arm is correctly mounted, distortion due to tracking error is extremely small; in fact it will be smaller than distortions due to other causes at present—that in the record due to recording equipment, in many instances, and also in the pickup due to nonlinearity of damping material and other factors. However, high-fidelity enthusiasts are perfectionists so they seek to eliminate all possible causes of distortion however small.

One method is to use a radial arm, which theoretically gives perfect tracking all the way. In this case the pickup is mounted on a slide rather than on a hinged arm (see Fig. 7). This needs a short pickup arm from the slide to the stylus point, which is not necessarily a serious disadvantage.

The difficult thing in this design is to get a sufficiently free sliding action because a good pickup should require no more than 1 gram vertical force on the stylus to keep it in the groove. It requires a very free sliding action to get the friction down to a very small fraction of a gram, which is necessary if we are to avoid displacement of the stylus due to friction.

The trapezoid arm

Another approach uses the double-hinge arm. The B-J is an example of this construction. This is based on the information shown in Figs. 3 and 5

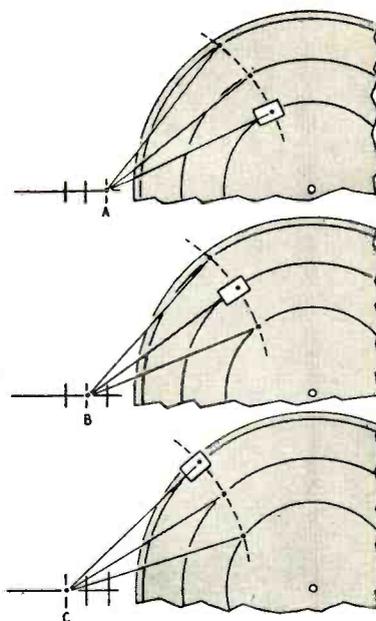


Fig. 2—An in-line arm can track correctly at only one point.

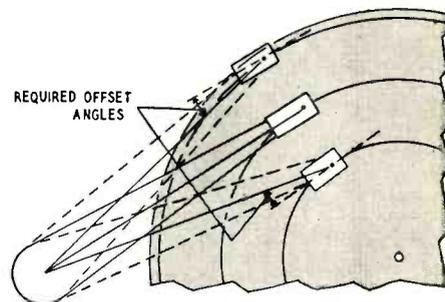


Fig. 3—Pickup mounted in line at intermediate groove needs offset to track correctly at inside of outside grooves.

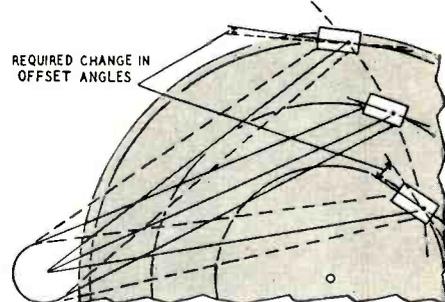


Fig. 4—Effect of too much offset.

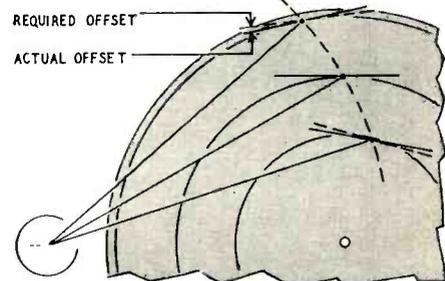


Fig. 5—Optimum offset reduces deviation to a minimum.

for the straight and offset arms. If we use, basically, a straight arm and then change the angle of offset as the pickup moves across the record, we can make a first-degree correction for track-

AUDIO—HIGH FIDELITY

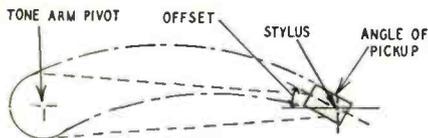


Fig. 6—It makes no difference if the arm is straight or curved, if the length from tone-arm pivot to stylus and the offset angle remain the same in each case.

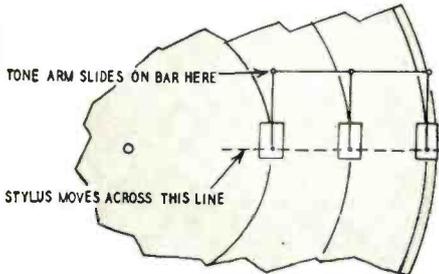


Fig. 7—The radial tone-arm slides on a bar and the stylus moves along the turntable's radius.

ing error. Using a double arm with a trapezoid action (a slightly offset parallelogram effect), the angle of offset changes due to the difference in the two short arms of the trapezium. This is shown in Fig. 8.

The link motion of the pickup arm changes the angle as the pickup moves across the record. Now, correct tracking is achieved at more points across the record and the deviation between the points of correct tracking is even smaller.

The first-degree step in this direction is based on a modification of the straight arm. This makes both of the long links of the movement equal. The number of correct points across the record is increased to three.

However, by making the two long links slightly different, which makes the arm more equivalent to an offset arm with correction for offset at different points across the record, the number of correct points can be increased to five. This means, of course, provided the arm is accurately mounted, the tracking is virtually correct all the way because the angle of deviation between five correct points must be extremely small.

The problem with this kind of arm is that, instead of having one tone-arm pivot, you have four. This leads to the possibility of four times as much friction in the movement. Also there is four times the possibility of play or slack, developing looseness in action. Extremely good pivots must be used, without any play whatever and with extreme freedom of movement to prevent introduction of any friction that may oppose the movement of the stylus across the record.

The principal reason the straightforward simple arm with an offset continues to be preferred is because it has only one pivot in a horizontal direction at the mounting point of the tone arm.

Using just the simple arm with an offset, the length of the arm deter-

mines the amount of deviation. Doubling the arm's length reduces the amount of deviation across the record by about 50%.

Conversely, using a smaller recorded area, as occurs on the 45-rpm record, a shorter arm can be used with a smaller deviation, provided the offset angle is correct for this particular range of radii. This was the reasoning behind the development of the original 45-rpm records: to produce a more compact unit with a shorter tone arm while still maintaining the same degree of accuracy in tracking available with the larger recordings and using a much longer tone arm. This is illustrated in Fig. 9.

The right offset

The correct offset for a tone arm (which is not usually adjustable so, if your tone arm is not correct, there is little you can do about it) is determined by the range of playing radii encountered in the record. The following table gives the average range of playing radii for different types of records, together with the design radius on which correct offset for this type should be based.

| Type of Record | Radii (inches) | | |
|-----------------|----------------|---------|--------|
| | Inside | Outside | Design |
| 45-rpm | 2.1 | 3.3 | 2.65 |
| 78-rpm, 10-inch | 1.75 | 4.75 | 3.07 |
| 78-rpm, 12-inch | 2 | 5.75 | 3.65 |
| 33-rpm, 10-inch | 2.5 | 4.75 | 3.55 |
| 33-rpm, 12-inch | 2.5 | 5.75 | 4 |

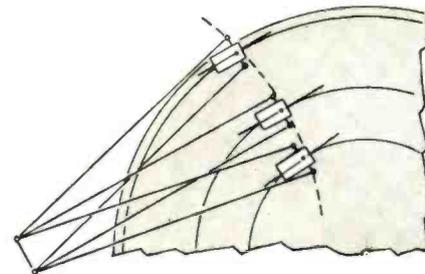


Fig. 8—Simplified construction shows action link-movement (trapezoid) arm.

The old 78-rpm records go down to a smaller inside radius than do the modern LP's. If we take the whole range of recordings including both LP's and 78's as a basis, we should come up with a slightly different answer for offset angle from that using only LP's. If you want to play 45's as well, this further complicates your choice. I prefer to use an offset and mounting position to suit 12-inch LP's and allow a little more tracking distortion at the inside of 78's and 45's. As the distortion on 78's usually starts out larger than on LP's, this seems to be the best balance of arrangement.

The offset should be such that the correct playing position, when only one correct playing position is selected, is a little inside of the mean radius of playing, as shown in Fig. 10. Then the tone-arm mount is moved a small fraction of an inch farther away from the turntable so as to have two correct

radii, near the inside and outside of the playing band.

How to set up

Finally we come to the question of how to set up the arm correctly to produce the best approximation to correct tracking across the record. In the case of a straight arm the best compromise is to have the tracking correct about one-third of the distance from the inside radius to the outside radius. This will then minimize the error at both inside and outside radius—both will be about equal.

For the offset arm there are a number of procedures. Most manufacturers specify either an overhang, by which is meant the distance between the stylus point and the turntable center when the arm is swung so as to cross the center of the turntable, shown as A in Fig. 11, or the spacing between the turntable center and the tonearm mounting point, shown as B in Fig. 11.

Gauges of different construction have also been described for measuring the overhang with a certain degree of precision. I have found another approach quite useful and use an ordinary transparent protractor. This method has the advantage of giving a much better visual idea of just what you are trying to do and not requiring a specially made tool.

It consists of laying the protractor

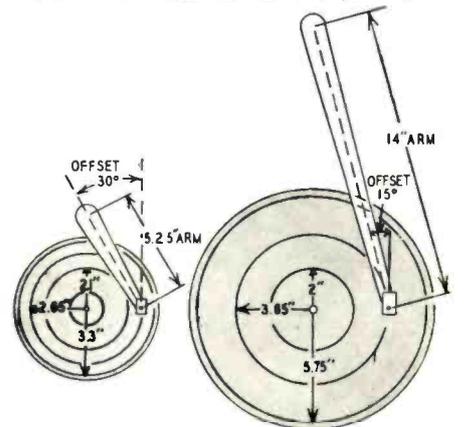


Fig. 9—A narrower band of recording makes a shorter tone arm possible without increasing tracking error.

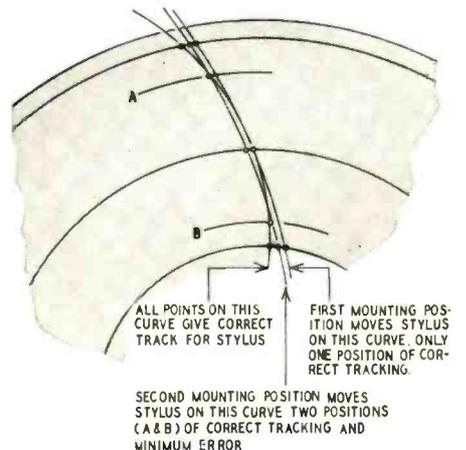


Fig. 10—Possible deviation from proper tracking with an offset arm.

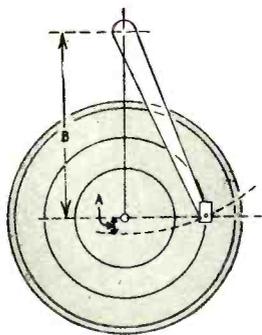


Fig. 11—Offset-arm mounting is specified in overhang (A) or distance from tone-arm mount to turntable center (B).

across the disc so the straight line between 0° and 180° lies along the radius of the record or turntable. Then the 90° line will be a tangent to the radius or should lie along the groove at this point. The stylus is rested upon the intersection or center point of the transparent protractor. If you now look along the 90° line between the pickup


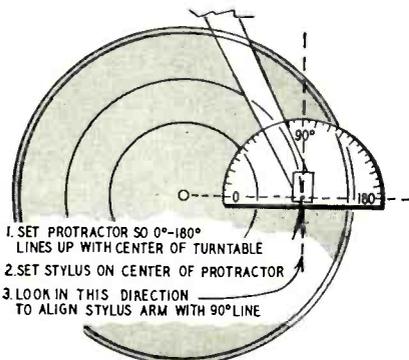


Fig. 12—Checking tracking visually.

arm and the protractor, you will be able to see whether the stylus arm of the pickup is in line with the 90° line on the protractor (see Fig. 12). If it is and the position you have chosen for the stylus point to rest represents the medium radius of playing, you are pretty close to the correct mounting point for the tone arm. If not, the tone arm, turntable and protractor can be moved to find a suitable mounting point.

Technically, when you get these two in line you should move the tone-arm mounting point from $1/16$ to $1/10$ inch farther away from the turntable's center. This will then get the correct position where there are two points of correct tracking and a minimum deviation across the record. Using this method, however, you will find it is extremely difficult to tell when you are exactly right, within $1/10$ inch, especially if you are using a tone arm with a length of 9 inches or more.

You can also use this method to check accuracy of tracking through the record from inside to outside and if you need to, choose a better compromise for the mounting position. It may also give you some idea of how academic are the claims that the offset arm does not achieve *perfect* tracking. The degree by which it misses is really so small as to be inconsequential compared to other causes of distortion. END

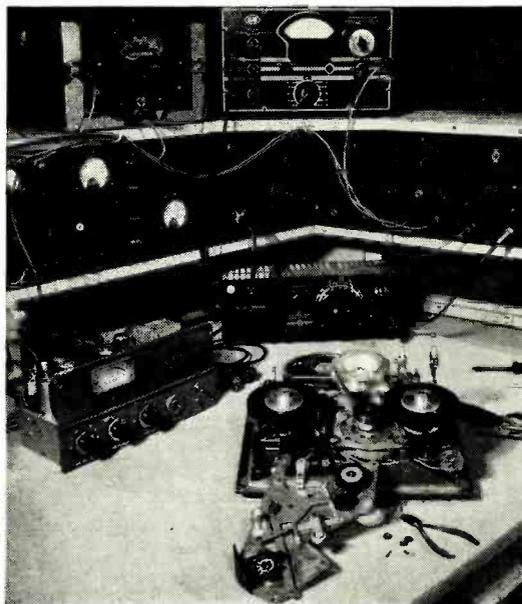

Another view of the service bench featured on our cover.

THE photograph on our front cover shows a corner service bench used by service technicians of the Sigma Electric Co., New York City, to do special audio service work. On the upper shelf is a D & R flutter meter and a Barker & Williamson distortion meter, necessities for checking quality high-fidelity record players, tape recorders, tuners and amplifiers.

On the lower shelf, at the left, part of a voltage-regulated power supply is seen. To its right, in the corner, is a Variac, into which the Ampex 601 undergoing servicing is plugged. The Ampex tape unit, already partially stripped down for inspection and repair, is in the foreground. The right side of the lower shelf is occupied by an audio amplifier, specially designed to accommodate a very wide variety of inputs and outputs so that any preamp, tuner or record changer can be thoroughly checked. At the extreme rear, on the bench, a General Radio oscillator, for determining frequency response of high-fidelity equipment, can be seen.

Sigma Electric is now completely an audio service company. All types of high-fidelity equipment are repaired.

Amplifiers, preamps, tuners, tape recorders and record changers, from an inexpensive home unit to precision broadcast equipment passes through their repair shop. An official service station for nine brands of tape recorders and an even larger number of tuners and amplifiers, Sigma employs 21 persons, including 5 doing clerical, counter and shipping work. The other 16 are technicians or assistants.

Although general service work, including radio and television, was once handled (see photo on page 37, RADIO-ELECTRONICS for June, 1954), at present the only deviation from high-fidelity audio units is the servicing of electronic-flash equipment. For this specialized work they hold franchises from four manufacturers of electronic-flash equipment.

The firm is owned by Arthur Peikes and Wilfred Goldstick, both of whom hold Bachelor of Science degrees from the University of Toronto Engineering School. Sigma Electric was started when these two men formed a partnership in 1949 to construct audio accessories on a contract basis and to service Brush tape recorders. END

RADIO-ELECTRONICS and GERNSBACH LIBRARY

will exhibit at the

HI-FI SHOW Oct. 7-12

New York Trade Show Building Room 526

Look for the **NOVEMBER** issue of RADIO-ELECTRONICS because:
Several months ago, RADIO-ELECTRONICS commissioned Norman H. Crowhurst to develop a new moderate-cost high-fidelity amplifier for our build-it-yourself readers.
Mr. Crowhurst has come up with an unusual design using a pair of EL84's in a twin-coupled output stage.
Next month we will publish full construction details on this new amplifier. Don't miss it!

Loudspeakers and acoustic fundamentals

By PAUL W. KLIPSCH*

MY letter in the May issue (reprinted here) has stirred a response from an unexpected quarter. It was far from my mind to offend one of the internationally respected pioneers — elder statesmen — in the audio art. I was pointing at some of the “new and marvelous inventions” which violate the principles of physics.

The response by Mr. H. A. Hartley (July, 1957) points out quite accurately that 1 acoustic watt in a living room would produce painful sound pressures. The response also accuses me of abandoning the scientific attitude and becoming dogmatic and inaccurate. I regret provoking this response because I have no desire to trap or provoke anybody into an inadvertent misstatement.

The facts behind my letter are:

As for the amount of motion to produce distortion, I refer to G. L. Beers and H. Belar “Frequency-Modulation Distortion in Loudspeakers,” *Proceedings of the IRE*, Volume 31, No. 4, pages 132-38, April, 1943. They showed that a cone performing an excursion of 1/8 inch (amplitude of 1/16 inch) produced 10% distortion by frequency modulation of a 5,000-cycle tone, expressing distortion as sideband amplitude. They mentioned that as low as 3% distortion causes perceptible change in quality. Probably listeners were less discerning in 1943 than now.

In good tape machines a total wow and flutter of 0.1% is just barely tolerable. Taking this to be true for the frequency-modulation distortion of a loudspeaker, then the cone must move less than 1/1,000 the velocity of sound or less than 34.4 centimeters per second. The amplitude of motion is expressed by the equation:

$$A = A_0 \sin \omega t$$

where A is the displacement at instant t, A₀ is the maximum displacement (in each direction) and ω is 2π times fre-

quency, the equation for velocity of movement is found by differentiating:

$$V = \frac{dA}{dt} = A_0 \omega \cos \omega t$$

The maximum velocity occurs when cos ωt = 1, or V = A₀ω.

Thus, at a frequency of 50 cycles per second, ω = 2π × 50 = 314, and we have

decided that V must not be more than 34.4 cm/sec. So the maximum permissible value of A₀ is

$$A_0 = \frac{V}{\omega} = \frac{34.4}{314} = 0.11 \text{ centimeter or } .043 \text{ inch maximum amplitude or } .086 \text{ inch maximum excursion.}$$

This “just tolerable” distortion excursion of .086 inch is a little larger than the .06 inch used in my original “fundamentals”; the difference is not an error, but a rather close agreement.

Experience indicates the factual significance of fluttering frequency shifts even as small as 0.1%. The higher the modulated frequency the greater the audible distortion, usually, up to about 6,000 cycles.

These facts pertain whether the cone is driven by a voice coil or a broom handle, is hung on a high-compliance suspension or low, or is high or low efficiency. Actually the “fault” would exist with a “perfect” speaker. *Modulation distortion is not a fault but a property of a vibrating surface or air boundary layer; it is minimized by reducing excursion.*

Far from abandoning the scientific attitude and becoming dogmatic and inaccurate, I would point to the vast supporting literature behind my statements, and the simple mathematics above. Kellogg used many speaker units to limit excursion to .06 inch in a year when intermodulation distortion had not yet been mentioned. (E. W. Kellogg, “Means for Radiating Large Amounts of Low-Frequency Sound,” *Journal Acoustic Society of America*, Volume 3, No. 1, Part 1, pages 94-110, July, 1931. Mr. Kellogg was co-inventor of the Rice-Kellogg speaker. See *Transcript AIEE*, 1925.) (The name Kellogg was unfortunately misspelled “Keller” in my original letter.)

This is not to deny that many speaker drive mechanisms can disdainfully handle 1/4 inch or larger excursion, with relatively low harmonic distortion. But

THE MAY LETTER

Dear Editor:

Much air must be moved to radiate appreciable power at low frequencies. The following table shows the excursion necessary to produce one acoustic watt output and the acoustic power output capability of a 10-inch piston (equivalent to a 12-inch speaker) executing an excursion of .06 inch (peak amplitude of .03 inch) which is regarded as about the maximum limit for tolerable distortion.¹

| Frequency | Excursion Needed To Radiate 1 Acoustic Watt | Power Radiated At .06-Inch Excursion Acoustic Watt |
|-----------|---|--|
| 60 | 0.7 | .0072 |
| 50 | 1.0 | .0036 |
| 40 | 1.5 | .0016 |
| 35 | 2.0 | .00085 |
| 30 | 2.8 | .00045 |

These figures are independent of box shape, suspension compliance or amplifier power supplied.

The facts of life in acoustics are simply that the undistorted output of a small cone at low frequencies would be too small to hear, regardless of the “response curve”.

In 1931 E. W. Kellogg proposed the use of 54 cones of 8-inch diameter to radiate 1 watt at 30 cycles, and the use of a corner horn. Structural designs have improved in the following 25 years but acoustical fundamentals have not changed.

There have been little speakers with big claims since the Edison phonograph of 1901, but nobody has devised a miniature 32-foot wavelength.


PAUL W. KLIPSCH

Klipsch & Associates
Hope, Ark.

¹Frank Massa, *Acoustic Design Charts*, Blakiston Co., Philadelphia.

*Klipsch & Associates, Hope, Ark.

Front panel of the completed unit.

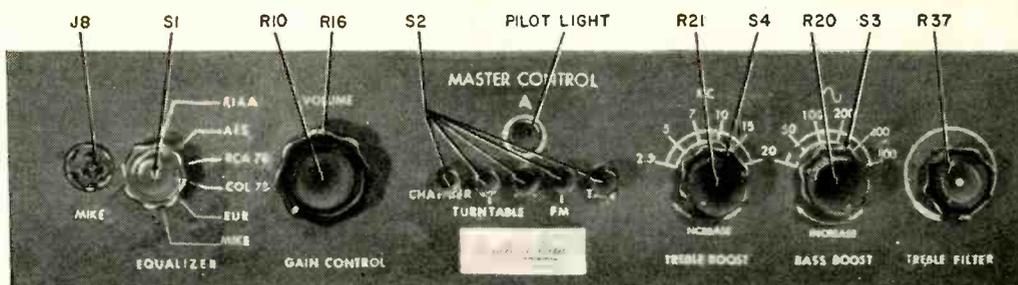

HI-FI MASTER CONTROL UNIT

*Easily built 6-tube circuit
is more versatile than most
commercial control units*

By JOSEPH MARSHALL

A SIX-TUBE control unit needs justifying. Even the crankiest hi-fi crank is likely to be taken aback by such extravagance, although several commercial units use five or six tubes. My justification is that it produces a versatility beyond that of commercial control units and approaches that of equipment used by broadcast stations and recording companies. The complete circuit is in Fig. 1.

The principal feature is the tone control circuit. Any two octaves from 20–20,000 cycles can be boosted 20 or 25 db with an insignificant increase in distortion. The bass and treble channels have six peaking points about an octave apart which are selected by switching.

This is highly useful to the record collector. Anyone who has tried playing ancient recordings on a modern hi-fi system knows that they usually sound pretty horrible. With this equalizer the

majority of them produce a satisfying sound.

Its versatility is also useful to the amateur recorder who makes off-the-air, off-the-record or live recordings.

A rolloff or high-frequency filter provides a way to minimize noise, beatnote interference, phase distortion in FM and similar distractions with little loss of musical quality.

The biggest problem of hi fi is to provide at a level tolerable in the home a tonal balance with some resemblance to that in the concert hall. Both people and rooms require different listening levels and the rooms themselves require compensation. No single loudness curve, slope, crossover or single combination of them can possibly suit anything but a fraction of the needs. This control unit will provide just about any conceivable tonal balance to take care of almost any acoustic condition, playback level

or any listener's personal taste.

Finally it provides a way for many hard-of-hearing persons to enjoy high fidelity. Loss of hearing involves, not only a loss in hearing acuity, but usually a serious modification of the hearing curve too. Most of the hard-of-hearing have holes in their hearing curves and unfortunately these holes do not always appear at the ends of the spectrum where they can be compensated by ordinary tone controls.

The tone control circuit of this unit fills any two such holes with 20–25 db of boost. The network is that used in most audiometers to measure and test hearing. Not everyone will find perfect compensation, but the control unit will do a good job for many.* Each individual can adjust the controls for the

*Note, however, that authorities have found that flat hearing aids are most acceptable to the hard-of-hearing.—Editor

Loudspeakers and Acoustic Fundamentals (Continued)

music is not just one single tone or frequency at a time; it is a terrifically complex mixture of high and low tones. Even if the bass speaker is crossed over to a tweeter or mid-range at 500 cycles, a mixture of 40 and 400 can produce unpleasant distortions when the diaphragm amplitude becomes large. Again, intermodulation is not a fault but a property of sound radiators performing large excursions.

The remedy to limit distortion is adequate radiating area and reduced excursion. As Kellogg proposed in 1931, a group of 8-inch cones can be used to produce large amounts of power.

Mr. Hartley states in his reply, "If we accept the Massa data . . . which I, for one do not . . ." The reference is to *Acoustic Design Charts*, Frank Massa, Blakiston, 1942. Granting that any particular piece of data in any publication might be in error, due perhaps to a misprint, I checked the particular data by computation from earlier and

more basic information and as far as I could tell the data were accurate. Incidentally, the basis for the information goes back to 1877 when a great British physicist derived the function of a piston vibrating in a hole in an infinite wall (Lord Rayleigh, *Theory of Sound*, MacMillan, 1877). The Massa data were not used without question, they were checked.

Mr. Hartley closed his remarks with an attack on the choice of driver units used in our speaker systems. No defense is needed here, for our bass driver is capable of nearly $\frac{3}{4}$ inch total excursion with very low harmonic distortion. And a $\frac{3}{4}$ -inch motion of a 15-inch speaker cone can really pump a lot of air. But this when used in a horn develops large pressures at almost invisible amplitudes, due to the way the acoustic matching of the horn provides an air load for the diaphragm. With these very small amplitudes, the doppler and amplitude distortions are extremely

low, compared with what the same driver would produce as a direct radiator.

For my part, I would question by what measure a speaker is required to pass a test of $\frac{1}{2}$ -inch excursion without cross-modulation and by what measure a speaker of any size can be claimed to be flat to 0 cycles or to be non-resonant in spite of being a mass suspended on a compliance.

Hermeneutics, the art of not being fooled, could well be applied to this new high-fidelity art wherein hard-well-established facts are disputed, wishful thinking is copy for ads and rave articles, and truth becomes a relative quantity. An especial premium should be placed on intellectual honesty, and the reader should school himself in hermeneutics and learn to distinguish fact from opinion and well-grounded opinion from mere wishing. I believe my own writings have been marked for the reader to distinguish between facts I present and my opinions. END

AUDIO—HIGH FIDELITY

tonal balance that sounds best and most natural to him. The only change is that of adding a phone jack at the output. Headphones can be used across the output of the cathode follower.

Specifications

A choice of five input sources is provided through pushbutton switches. The phono equalizer (Fig. 2-a) uses a cascode amplifier and provides a choice of five playback curves: two for LP discs (RIAA and AES) and three for 78 rpm (one with a 500-cycle crossover and a 6-db drop at 10,000 cycles, another with a 350-cycle crossover and a slightly greater drop and the third with a 250-cycle crossover and no treble slope). Specifications for additional equalizers are shown in Fig. 2-b.

The tone control circuit uses three parallel channels: the flat, bass and treble. Tone control networks are the Wien-bridge type and provide a broadly peaked curve. Each channel gives a choice of six peaking points about an octave apart. The extreme positions in each channel have the effect of changing the crossover and slope.

In normal use these positions may be used to increase the presence of some favored instrument. You can also improve the quality of old acoustic records. An output jack is provided for a recorder—this output is unaffected by the tone control.

Concentric controls are used for both volume (loudness) and gain (level). The volume control varies the gain of the flat channel. Relative boost of both

bass and treble channels will vary with the setting of this control. At maximum the bass and treble channels cannot produce more than 6 db of boost, while at minimum 20 or 25 db is possible. Therefore, the volume control provides an automatic increase or decrease of boost with volume level to take care of the Fletcher-Munson effect and is actually a loudness control.

The volume control adjustment is exactly opposite to that generally used. Usually the tonal balance is adjusted at maximum output levels. When the volume is reduced, the loudness control curve is supposed to provide compensation which produces a good balance at the desired level. This is the wrong way of getting the desired end and is not used in this unit. The control is

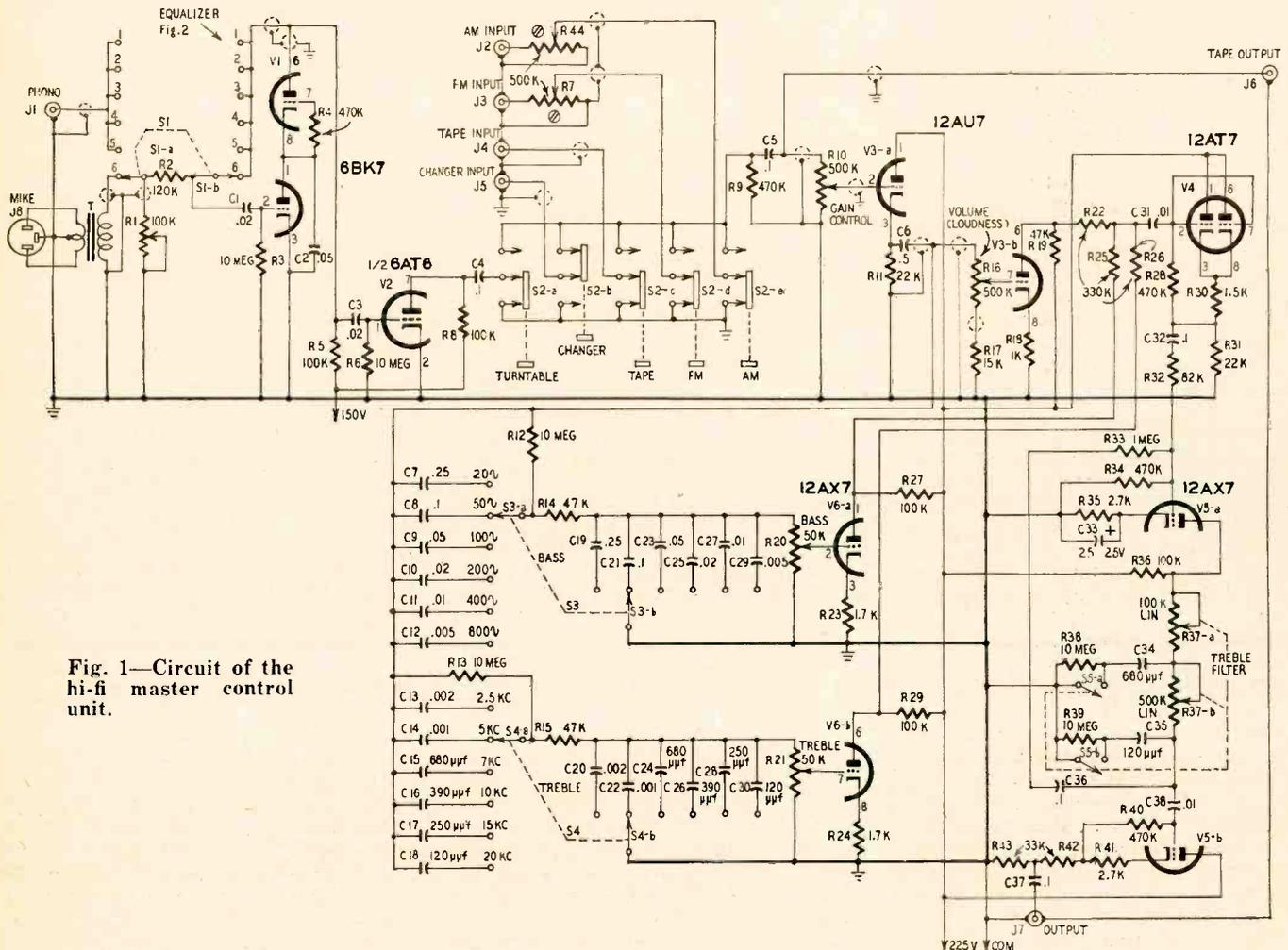


Fig. 1—Circuit of the hi-fi master control unit.

- R1—pot, 100,000 ohms, linear
- R2—120,000 ohms
- R3, 6, 12, 13, 38, 39—10 megohms
- R4, 9, 28, 34, 40—470,000 ohms
- R5, 8, 27, 29, 36—100,000 ohms
- R7, 44—pot, 500,000 ohms, audio screw-driver-adjust concentric (Centralab AB-60)
- R10, 16—pot, 5000,000 ohms (Centralab FI41+R2-42)
- R11, 31—22,000 ohms
- R14, 15, 19—47,000 ohms
- R17—15,000 ohms
- R18—1,000 ohms
- R20, 21—pot, 50,000 ohms, audio (Centralab B-32)
- R22, 25, 26—330,000 ohms
- R23, 24—1,700 ohms
- R30—1,500 ohms
- R32—82,000 ohms
- R33—1 megohm

- R35, 41—2,700 ohms
- R37—pot, 100,000—500,000 ohms, linear (Centralab FI-31+FI4, Solder shafts together and add KB-2 dpst)
- R42, 43—33,000 ohms
- All resistors 1/2 watt, see text for type
- C1, 3—0.02 μf, 200 volts
- C2—0.05 μf, 200 volts
- C4, 5, 32, 37—0.1 μf, 200 volts
- C6—0.5 μf, 200 volts
- C7, 19—0.25 μf disk
- C8, 21—0.1 μf disk
- C9, 23—0.5 μf disk
- C10, 25—0.2 μf disk
- C11, 27—0.1 μf disk
- C12, 29—0.05 μf disk
- C13, 20—0.02 μf disk
- C14, 22—0.01 μf ceramic
- C15, 24, 34—680 μf ceramic
- C16, 26—390 μf ceramic
- C17, 28—250 μf ceramic
- C18, 30, 35—120 μf ceramic
- C31, 38—0.1 μf, 400 volts
- C33—25 μf 25-volt electrolytic
- C36—0.1 μf, 400 volts
- C37—0.1 μf, 400 volts

- C18, 30, 35—120 μf ceramic
- C31, 38—0.1 μf, 400 volts
- C33—25 μf 25-volt electrolytic
- C36—0.1 μf, 400 volts
- J1—7—phono jacks
- J8—microphone jack
- S1, 3, 4—2-pole 6-position rotary
- S2—single-pole 5-position pushbutton or rotary
- S5—dpst Centralab type KB2 on R37
- T—hi-fi mike-to-grid transformer
- V1—6BK7
- V2—6AT6
- V3—12AU7
- V4—12AT7
- V5, 6—12AX7
- See-Zak Chassis: (see text) 2—R28; 2—R216; 1—PB16; 1—P616
- Vector No. 8NN-7A5-4 (see text) (2)
- Vector No. 10-3N-11A7-4
- Miscellaneous hardware

turned to minimum and GAIN CONTROL is set for a desired loudness of mid-frequencies. Now the bass and treble controls are adjusted for the desired balance. Then when volume is increased with the volume control, bass and treble boosts are reduced until at maximum volume you have just about a flat response. For broadcasting and similar uses the volume is regulated with the GAIN CONTROL, which has no effect on the compensation.

The unit has enough gain to provide at least 2 volts of output, either with 20-db boosts at any two points or flat.

The tone controls provide only boost and no means for attenuation. There is a treble filter with a 12-db-per-octave slope and a continuously adjustable crossover between 4,000 and 15,000 cycles.

The total IM distortion at a 2-volt output ranges between 0.3 and 0.7%. At lower levels it is insignificant.

A simple filter is included to attenuate transients due to warped or eccentric records, FM squelches, shortwave fading, beatnotes of stations on the same broadcast channel but whose frequencies differ by 1-20 cycles, etc. The filter does little good on rumble whose frequency is usually between 20-30 cycles. If you are troubled by rumble, considerable relief can be obtained by reducing the value of the output capacitors of the phono preamp and the following input capacitor to .05 or .03 μ f.


Power supply

An independent well filtered power supply with dc for the heaters is essential. Any attempt to feed this preamp from the power amplifier's power supply is almost certain to result in motor-boating or instability. The supply diagrammed (Fig. 3) uses two regulator tubes to supply 255 volts to the tone control stages and 150 volts to the phono channel. The .05- μ f capacitors in shunt with the regulators minimize hash. If the preamp shows any tendency to oscillate at mid or high frequencies, try removing this capacitor before making any other checks. Dc for the heaters is necessary to keep hum down. Even 1 or 2 μ v of hum applied to the first phono tube will produce an output of several hundred millivolts.


Building the unit

The construction uses See-Zak chassis components and Vector turret walls. The chassis comes in pieces like an Erector set. I used two 16-inch rails for the front and back, two 8-inch rails for sides, one 8-inch bottom plate and a 6-inch top plate. The rear rail is set in 6 inches from the front. Don't worry about fastening it to the side rails since the top and bottom plates will tie the whole works together. (These chassis are available at many radio parts distributors or can be obtained from U M & F Manufacturing Co., 10929 Vanowen St., N. Hollywood, Calif.)

The Vector turret walls are combina-

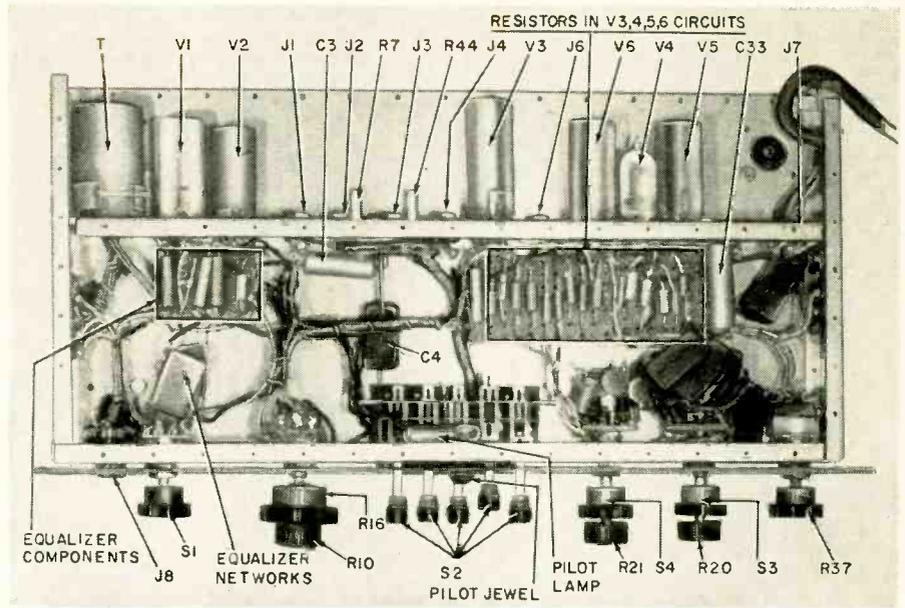

Internal layout as seen from the top.

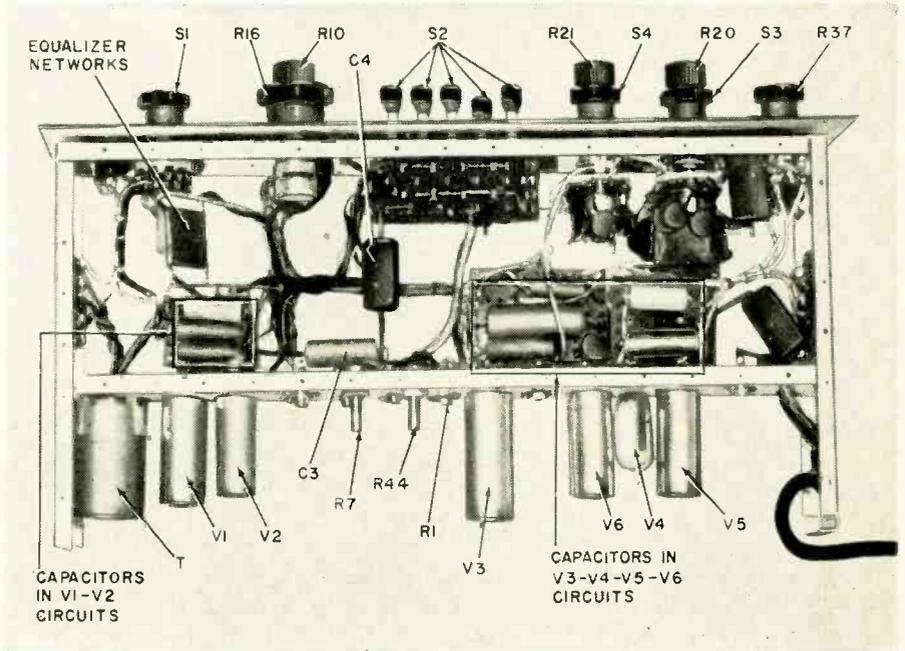

Bottom view of the control unit.

tions of terminal strips and tube sockets and are available in almost any combination. Here we use one two-tube wall for the equalizer, a three-tube wall with one socket removed and a two-tube wall for the rest of the stages. If you cannot obtain these, the more easily available Vector turret sockets may be used instead.

The turret walls are mounted on the rear rail along with the mike transformer, input and output plugs and level controls. Resistors are mounted on one side of the walls, capacitors (and a few resistors) on the other side. Connections from tube sockets to components are short. Connections between components are made on the wall. A common ground bus of heavy wire is run along the edge of the turret walls under the last series of holes.

Components which are grounded are mounted so that the tinned lead of the grounded end can be put through the hole, wrapped around the ground bus and soldered. The terminals at the bottom of the walls are used for voltage supply and any interconnections which may be required.

The controls are mounted on the front rail. A couple of these R21-S4 and R20-S3 are not commercially available: the combination of double-pole six-position rotary switch and a concentric potentiometer. If a standard 3-inch chassis is used, there will be room for independent switches and potentiometers. Replacing the push-button switch with a rotary unit will also give more room. Capacitors in the tone control channels are grouped at the switches.

AUDIO—HIGH FIDELITY

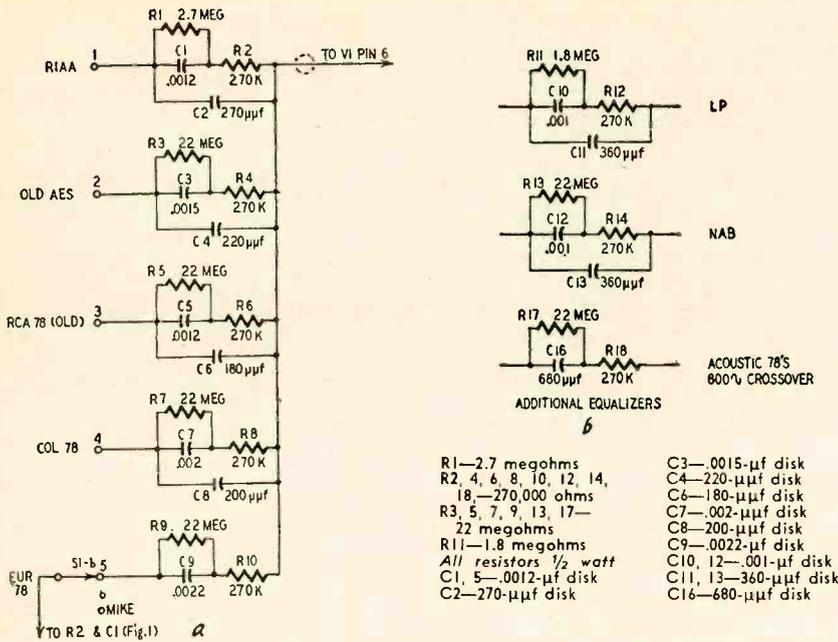


Fig. 2-a.—Equalization circuit for the control unit; b—additional equalization networks.

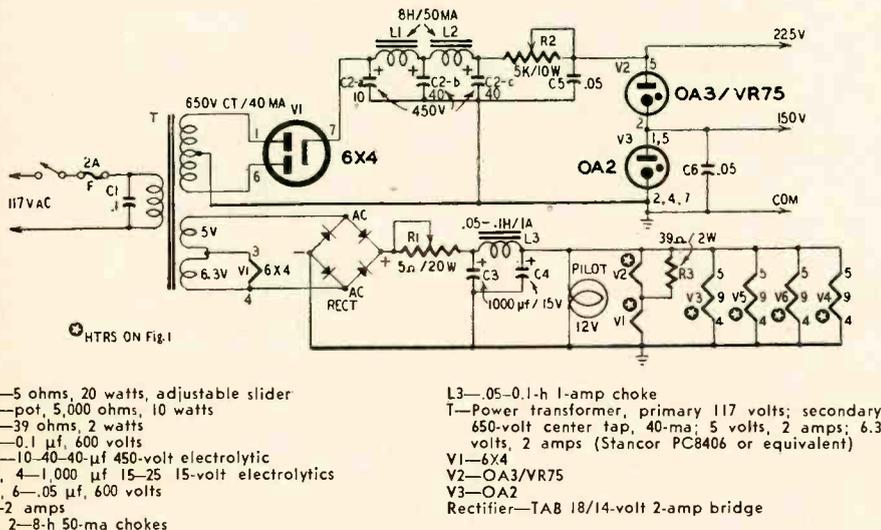


Fig. 3—Power supply for control unit. Note dc filament supply.

When the front and rear rails are wired as far as they can be, the side rails are attached to the front and the 6-inch plate is temporarily fastened with three or four screws. Now start interwiring. I used fine shielded and insulated phono input leads for the leads from the input jacks to various portions of the circuit. *This shielding is necessary.*

Except where a short direct connection was possible, I ran these interconnecting leads along the ground bus and then cabled the works with twine. Except for shielding the indicated leads, there is nothing critical about the wiring. Duplicate the layout as closely as possible for highest insurance, but if a similar but not exactly identical layout is used, no trouble should arise. I used deposited-carbon resistors in all stages preceding the rolloff stage, but believe that if deposited-carbon types are used only for the plate loads and wirewound resistors for cathode loads,

the others can well be good quality carbons.

Power supply construction

The power supply is separate. In my case it is mounted on the same chassis which supplies power to two amplifiers. There is nothing critical about it, especially if the two regulator tubes are used to establish voltages. The 12-volt ac can be obtained either from a 12-volt filament winding or 6.3- and 5-volt windings wired in series. (If you do not get about 12-volt ac, reverse one winding.) You can use the 5-volt winding for a rectifier with a separate cathode, or use a 6-volt rectifier with cathode (6W4 or 6X4) on the 6-volt winding (see Fig. 3).

Please note that there is a series parallel connection of the 6BK7, 6AT6 and 39-ohm resistor. This value is critical if you want a reasonable life from these tubes. Adjust the potentiometer in the heater supply to provide no

more than 12 volts. Remember, the voltage will rise if you remove a tube. The total heater drain of the dc string, wired as indicated, is 1.05 amps.

No other adjustment is necessary. I had no trouble with oscillation or motorboating. If any occurs, the chances are 9 to 1 you have one of the two feedback loops (one in the phone equalizer and the other in the cutoff filter) wired wrong, have accidentally used the wrong value resistor or capacitor or the regulator tubes are not operating properly.

You should have no trouble with hum if you shield the leads indicated and follow the layout. Excessive noise, especially hash and crackling, may be the result of a bad tube or of badly soldered joints which might rectify the hum field which exists in any house.

You are quite likely to have some trouble with microphonic tubes, especially the 12AU7. It can be replaced with the taller 12BH7 which seems to be free of microphonism. The newer 12AU7-A is even less microphonic.

If you want to use a high-impedance mike without the transformer, connect the mike input to the phono-equalizer switch the same way the transformer now is. Incidentally, the transformer of a Ferranti, Electro-Sonic, Fairchild, etc. pickup can be connected directly across the 100,000-ohm input load. Any load up to 100,000 ohms can be provided by varying the load potentiometer. Calibrate with an ohmmeter.

The panel is a piece of 1/16-inch aluminum 4 inches wide. Drill it at the same time you drill the front chassis rail by clamping the two together. It was sprayed with Spray-O-Namel in a dark gray glossy finish. Wrinkle, crackle and other finishes are also available in spray cans. (A paint spray that dries to a hammertone finish is available and can be used.—Editor) *Do your spraying outside.* The fine mist is likely to spread all over the house and cause domestic havoc. It's tough on the lungs, too. When dry, apply decals for the controls.

Because of the complications in the circuit and construction and in use, I recommend this unit only for special requirements. For most home listening the control unit for Golden Ears (March, 1954, RADIO-ELECTRONICS) will be fully satisfactory. But those who need and can use the versatility will find this control unit like nothing they ever used or heard before. **END**

In RADIO-ELECTRONICS
for November:

Hybrid and Transistor
Auto Radios

By Jack Darr

Twin-Coupled
Hi-Fi Amplifier

By Norman Crowhurst

Did you make any of these errors in your R-C-coupled amplifier design?

design calculations for R-C COUPLED AMPLIFIERS

By HERBERT RAVENSWOOD

HAVE you ever found a circuit that didn't perform according to the calculations for it? This too common occurrence is often dismissed as being an inherent discrepancy between theory and practice—the idea being that calculations cannot be that accurate or else the measurements may be wrong, so let's just make some adjustments and try to get it right experimentally.

This procedure takes time. Sometimes it completely fails to give us the desired results. It is much better to put theory and practice together and make them both work for us. It has been said that theory is the guide to practice and practice the ratification of theory. Applying this principle to our work on audio-coupling circuits can save considerable time in making calculations and experiments.

Let's start with a simple coupling arrangement (see Fig. 1). The tube may be a triode or pentode, with an ac resistance designated R_a . Plate current is fed from B plus through coupling resistor R_c and signal voltages are coupled to the grid resistor of the next stage (R_g) through capacitor C . We will leave complications, like the cathode-bias resistor, its decoupling and any plate decoupling, for the moment to get the simple circuit straight. Then we can take these factors one at a time.

Gain calculation

The first common mistake, even found in some textbooks, is in stage gain calculations. The accepted method is to take the quoted amplification factor of

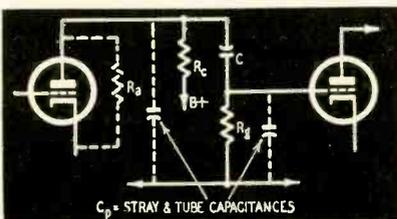


Fig. 1—Simple R-C-coupled stage; C_p is total of stray capacitances shown.

the tube (μ) and then use the formula:

$$A = \mu \frac{R_L}{R_L + R_a}$$

where R_L is the plate load resistance and R_a the tube ac resistance. When using R_L , don't forget to include the effect of the grid resistance of the following stage. The usual error consists of taking R_L to be just the plate coupling resistor, while the true value for calculating mid-band gain requires using the resistance of R_c and R_g in parallel.

Even this leaves us liable to some error because we are taking for the amplification factor of the tube a quoted value which may not be realized under the operating condition we are using. However, for a good approximate gain figure, take the amplification factor of the tube and use the above formula. Use a corrected value for R_L , taking into account the effect of R_g . This will give us results as close as it is possible to obtain without referring to a complete set of tube characteristics.

To see what the error could amount to, let's take values from a typical triode circuit. Let μ be 100 and R_a 77,000, R_c 220,000 and R_g 470,000 ohms. If we assume R_L is just R_c :

$$A = \mu \frac{R_L}{R_L + R_a}$$

$$A = 100 \times \frac{220,000}{220,000 + 77,000}$$

$$A = 74$$

If we use the correct value of R_L which consists of 220,000 and 470,000 ohms in parallel or 150,000 ohms:

$$A = \mu \frac{R_L}{R_L + R_a}$$

$$A = 100 \times \frac{150,000}{150,000 + 77,000}$$

$$A = 66$$

The difference, as you can see, is appreciable.

The corresponding formula usually used for pentode stages is $A = g_m R_L$.

Here we assume that g_m is a mutual conductance of 2 ma per volt (.002 mho or 2,000 μ mhos) and we use the same values of R_c and R_g , 220,000 and 470,000 ohms, respectively. The gain, making an incorrect assumption that R_L is 220,000 ohms, is:

$$A = g_m R_L$$

$$A = .002 \times 220,000$$

$$A = 440$$

On the other hand, using the correct value of 150,000 ohms for R_L , the gain is:

$$A = g_m R_L$$

$$A = .002 \times 150,000$$

$$A = 300$$

This is a difference of more than 3 db.

Calculating the gain of a stage tells us what it will contribute to overall amplifier gain and, if we make similar mistakes in several stages of an amplifier, we may end up 10 or 20 db short.

We also want to know the frequency response, first of individual stages and then for the whole amplifier. Where feedback is used, this is especially important because accurate prediction of the response for individual stages is necessary to determine whether the amplifier will be stable or why it gets into a region of instability.

Low-frequency response

First, let's take the low frequencies. A common but erroneous statement says: The low-frequency response is obtained by comparing the reactance of coupling capacitor C with the resistance of R_g . When the reactance is equal to the resistance, the frequency response is 3 db below maximum at the low-frequency end.

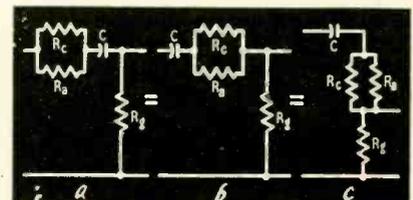


Fig. 2—Step-by-step deduction of how circuit elements contribute to low-frequency response.

AUDIO—HIGH FIDELITY

This statement fails to take into account the ac resistance of the tube and coupling resistor, both of which enter into the correct formula for predicting low-frequency response. Fig. 2 shows a step-by-step derivation of the correct low-frequency network.

We start by redrawing the circuit to take into account all the impedances. As series elements we have the parallel combination of R_a and R_c in series with C feeding grid resistor R_g . In considering response it makes no difference if we switch the positions of C and the parallel combination of R_c and R_a . Then, by redrawing this arrangement, so the resistors appear as a simple fixed potentiometer with coupling capacitor C feeding, it becomes evident that the correct frequency response is determined by comparing the reactance of C with the combined resistance of R_c in series with the parallel combination of R_a and R_e .

How will this adjustment affect our calculation? Let's take the same example as for the gain calculations and assume a .02- μ f coupling capacitor is used. With the triode arrangement the .02- μ f capacitor will have a reactance of 470,000 ohms at 17 cycles. To obtain the correct value we should add to 470,000 ohms the equivalent of 220,000 and 77,000 ohms in parallel, or 57,000 ohms. The capacitor will have a reactance of 527,000 ohms at 15 cycles. This is not too serious an error.

Now let's turn to the pentode. This time we will assume that a grid resistor of 220,000 ohms is used and that the pentode plate resistance R_a is 1 megohm. The parallel combination of 1 megohm and the plate coupling resistor's 220,000 ohms is 180,000 ohms. The usual statement which compares the capacitive reactance with the grid resistance would set the 3-db point at the frequency where the reactance of C is 220,000 ohms. This is 36 cycles. Using the correct value of 400,000 ohms obtained by adding 180,000 and 220,000 ohms, the 3-db point is 20 cycles, a large difference.

High-frequency response

Here, too, we find a number of common errors. The correct solution is found by taking all the circuit resistances effectively in parallel. This can be seen in Fig. 3 which shows the equivalent circuit for high-frequency loss. The accepted way of proving that this reduces to an equivalent of three resistors in parallel involves Thevenin's theorem. A little simple reasoning may be better.

Let's take the effect of C_p with each

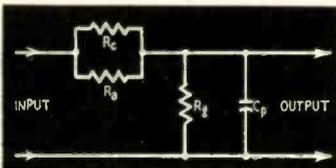


Fig. 3—Basic circuit for high-frequency response. All resistance shown must be taken into account.

part separately. If R_e is removed, the output voltage will differ from the input voltage due to the current C_p draws through the parallel combination of R_a and R_c . Now suppose that R_a and R_c are replaced with a high resistance approaching infinity to produce a constant current feed through C_p and R_g in parallel. Under this condition there will be a 3-db drop when the reactance of C_p is equal to the resistance R_g .

Now combine these two ideas to see the effect of C_p when R_a and R_c are effective as well as R_g . We see that first the output voltage is reduced due to the current C_p draws through the parallel combination of R_a and R_c . It is also reduced due to the current which C_p bypasses from R_g . But there is only one value of current in C_p . So the voltage drop must be due to the combined current that C_p draws from the equivalent parallel circuit of R_a , R_c and R_g .

Omission of R_a , R_c or R_g from this calculation will throw the result into error. In the example given, a combination of 77,000, 220,000 and 470,000 ohms works out to 52,000 ohms. The combination of 1 megohm with two 220,000-ohm resistors in parallel produces a total value of 100,000 ohms. The degree of error will depend upon which value gets overlooked.

The biggest error occurs in the case of the triode circuit if the ac resistance is overlooked. The equivalent value of 220,000 and 470,000 ohms in parallel is 150,000 ohms instead of 52,000 ohms. This represents a change in the turnover point of approximately 3 to 1.

The value of C_p is a little difficult to estimate. It is made up of the combination of the plate-to-ground capacitance of the previous tube, the effective grid-to-ground capacitance of the following tube (including any that may be due to Miller effect) and stray capacitance of the wiring. Under the last heading should be included stray capacitance due to the coupling capacitor itself. Often a large coupling capacitor will have as much stray capacitance to

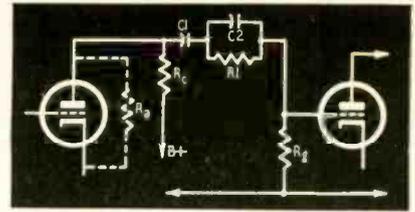


Fig. 4—Treble boost added to an interstage coupling.

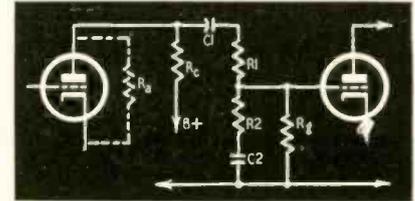



Fig. 5—Adding bass boost—practical circuit.

ground as all the rest of the circuit put together, and often gets overlooked. Metallized capacitors are particularly susceptible to producing a large stray ground capacitance.

Interstage equalizers


Before going on to consider the effect of decoupling components, we turn to interstage equalizers because each of the decoupling arrangements can be converted into the equivalent of an equalizer circuit. The same kind of error already mentioned with respect to simple coupling circuits can also occur in the calculation of response of compensating networks, particularly for treble or bass boost, using the arrangements shown in Figs. 4 and 5.

What often happens in calculating the response of these arrangements is that only the obvious components are taken into account. The plate resistance of the preceding stage is often forgotten in both circuits, and in the bass boost circuit a grid resistor is necessary to insure correct bias voltage on the following stage. This also can get left unconsidered sometimes. Using a step-by-step method of transposition to

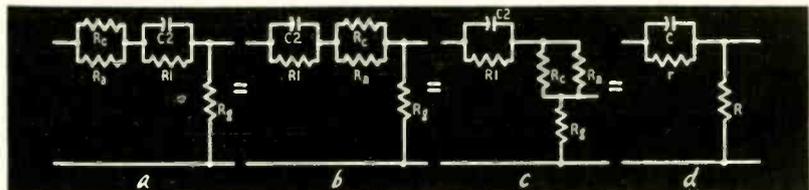

Inverted rolloff frequency given by $X_c = r$ $r = R_1$
Final rolloff frequency given by: $X_c = \frac{rR}{r+R}$ $R = R_g + \frac{R_a R_c}{R_a + R_c}$

Fig. 6—Reduction of circuit in Fig. 4 to its basic form.

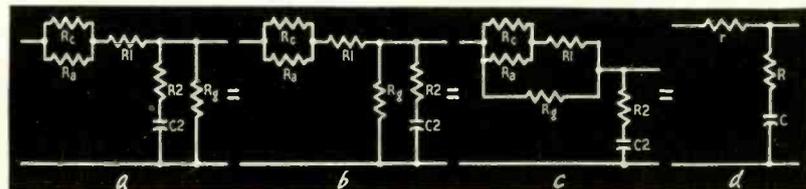

Inverted rolloff frequency given by: $X_c = R$ $r = \frac{R_c (R_1 + \frac{R_a R_c}{R_a + R_c})}{R_c + R_1 + \frac{R_a R_c}{R_a + R_c}}$
Final rolloff frequency given by: $X_c = \frac{rR}{r+R}$

Fig. 7—Reduction of actual circuit of Fig. 5 to its basic form.

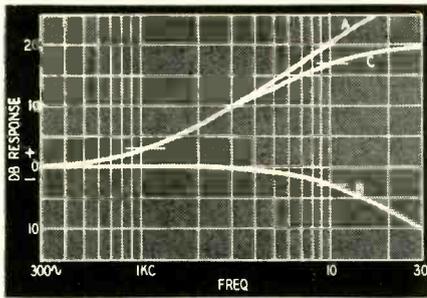


Fig. 8—Graphic construction for frequency response Fig. 6 circuit; curve A, inverted rolloff; curve B, direct rolloff; curve C, resultant response. Design frequencies shown by short horizontal lines cutting curves.


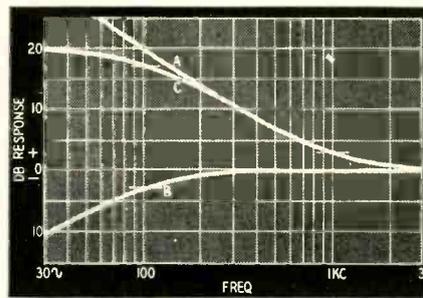


Fig. 9—Construction for frequency response of circuit in Fig. 7; curve A, inverted rolloff; curve B, direct rolloff; curve C, resultant response.

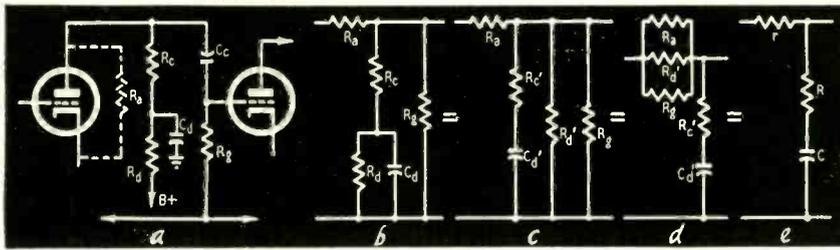

Conversions: $R_c^1 = R_c \left(1 + \frac{R_c}{R_d}\right)$ $C = C_d^1 = C \left(1 + \frac{R_c}{R_d}\right)$ $r = \frac{R_b R_g R_d^1}{R_b R_g + R_g R_d^1 + R_c R_d^1}$
 $R_d^1 = R_c + R_d$ $R = R_c^1$

Fig. 10—Practical plate decoupling circuit and stage-by-stage reduction to basic form. Note conversion between b and c of R_c , R_d and C_d , to a new configuration, using different values, R_c^1 , R_d^1 and C_d^1 , making simple conversion from c to d to e possible.

see how the equivalent boils down to the simple basic circuits, Figs. 6 and 7 show how the hidden circuit resistances are taken into account in each case.

In Fig. 6-a the basic equivalent circuit is developed from the practical treble boost circuit of Fig. 4. This is rearranged following the method of Fig. 2, to get an arrangement in which the resistances appear as a straight fixed potentiometer in combination with a simple frequency-discriminative circuit involving a single capacitor and two resistances shown at 6-d. The equivalent values and derivation for the symbolic quantities r and R are shown at the bottom of the figure.

What often happens in this circuit is that R is taken to be just the value of R_c , which is not correct. To this must be added the parallel combination of R_b and R_g to get the equivalent value of R .

When the correct circuit values have been ascertained the treble-boost response can be predicted by the method shown in George Fletcher Cooper's articles on this kind of circuit (RADIO-ELECTRONICS, December, 1950; February, 1951), combining an inverted rolloff (A) with a direct rolloff (B) which becomes more of a rollover (C) because it neutralizes the effect of the inverted rolloff. This is shown in Fig. 8.

Following a similar method of step-by-step deduction, the actual bass-boost circuit shown in Fig. 5 can be reduced to the equivalent shown in Fig. 7 and the values are derived by the method shown and given in formula form at the bottom of the figure. This circuit gives a bass-boost response (C) which

can be produced by combining an inverted rolloff (A) with a direct rolloff (B) in the manner shown in Fig. 9.

In this case the use of incorrect values results in taking r as just equal to R_1 , whereas in fact it is the complicated expression shown. The next common error is leaving out the parallel combination of R_b and R_g . Even when this is incorporated, sometimes grid resistor R_g is omitted.

An accurate prediction of the response requires that all these values be taken into account to find the effective value of the resistance r .

In this case omitting the resistors R_b and R_g from consideration will result in an effective value of r smaller than it should be. On the other hand, omission of R_g from consideration results in a value of r larger than it should be. Incomplete consideration in this case can result in an error either side of the correct value.

Decoupling circuits

The only kind of decoupling circuit that can be accurately predicted, without some reference to tube characteristics that are not usually available, is the plate decoupling. This prediction is illustrated in Fig. 10. Fig. 10-a is the actual circuit. The remaining figures show the derivation of the equivalent practical circuit. In this case a transformation effect is introduced to simplify the ultimate calculations.

C_d is tapped across a junction between R_c and R_d in Fig. 10-b. To get an equivalent that can be further reduced, the values of C_d , R_d and R_c are transformed from an equivalent Y

into an equivalent delta network. The conversion for this is shown at the bottom of Fig. 10. From this point the network may further be reduced to a simple equivalent which can be used for design purposes.

Cathode and screen decoupling produce an effect opposite to that of plate decoupling. This cannot readily be reduced to an equivalent circuit because it depends on certain tube characteristics. However, it is not very difficult to calculate on the basis of empirical information.

In the case of cathode decoupling, the height of step introduced will depend upon the amount of feedback which the cathode resistor produces. This can easily be checked by removing the capacitor and checking the change of gain that it produces at a mid-frequency. This is usually about 6 db.

When the reactance of the capacitor is equal to the bias resistance, the feedback effect will be 3 db less than when the capacitor is completely removed. This means that the 3-db point on the inverted rolloff in Fig. 11 occurs at the frequency where the reactance of the decoupling capacitor is equal to the bias resistance. If the step is 6 db high, representing a 2-to-1 ratio, the rolloff point will be at twice the frequency of the inverted rolloff point.

The same procedure can be used for deducing the response due to screen decoupling. The screen decoupling capacitor is removed and the change of gain at a mid-frequency is noticed. The inverted rolloff point will then occur at a frequency where the reactance of the decoupling capacitor is equal to the screen feed resistor. The direct rolloff point will be higher than this by a ratio equal to the change in gain.

Suppose the change in gain was 12 db and the screen decoupling consists

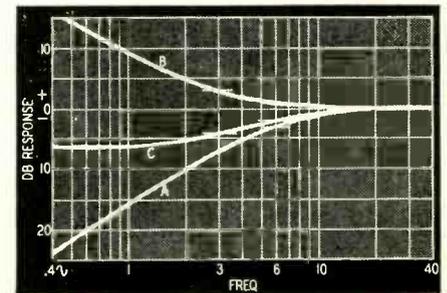


Fig. 11—Response curve of cathode decoupling, using 50 μf across 1,000-ohm resistor and assuming change of gain at mid-band when capacitor is removed to be 6 db. Rolloff points at 3 and 6 cycles are indicated.


of a 0.1- μf capacitor with a 150,000-ohm resistor. The reactance is equal to this resistance at 10 cycles so the inverted rolloff will be at 10 cycles and the direct rolloff at 40. At the mid-point of 20 cycles the response will be 6 db down due to this screen decoupling.

As you have seen, a slight error can cause a lot of difficulty. The next time you calculate gain, response or boost for an R-C amplifier use all the values. They can save you a lot of work. END


what's

new


?

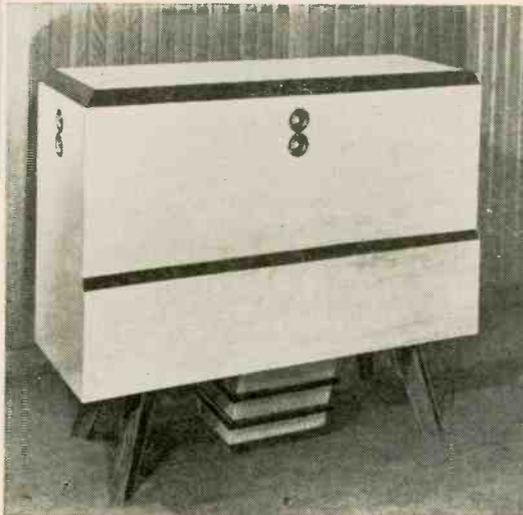

SPEAKERS MOUNTED OUTSIDE the cabinet is the startling feature of the Periphonic Speaker System, by General Electric Co., Ltd. of England. Sound is radiated through a small slot into the cabinet from the peripheries of two metal-cone loudspeakers mounted as shown in a V-shaped enclosure on the outside of the cabinet. The air coupling of these speakers, which move in opposite directions, reduces the distortion which occurs with a single unit, particularly at bass frequencies. The complete system, with the speakers mounted below the cabinet, reproduces the lower frequencies from 2,000 cycles down to 30 cycles. Six tweeters, two mounted on the front and both sides of the cabinet cover the frequency range above 2,000 cycles.

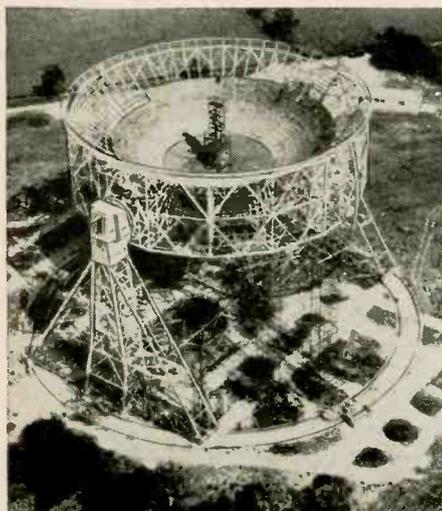


GIANT RADIO TELESCOPE, Jodrell Bank, Cheshire, England, is to be 10 times more powerful than any other in existence. Built for Manchester University for the exploration of the skies by radio astronomy, the lensless telescope is expected to be able to reach out into space to a distance of 1 billion light years. It has a directable reflector 218 feet in diameter, and the completed structure weighs 2,000 tons.

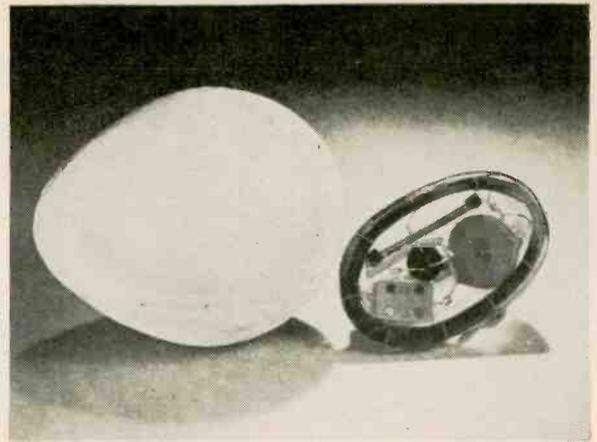

THERMOMETER THAT TRANSMITS its indications by radio was developed to measure the temperature inside a penguin egg. Biologists wanted to know how cold the penguin embryo gets and, since the penguin carries its egg with it when it moves from place to place, it would have to work by radio. Object of the study is to find out how living things survive cold—possible application to human life includes research for enzymes that will aid man to adapt to cold or even make it possible to lower human body temperature during operations, etc.

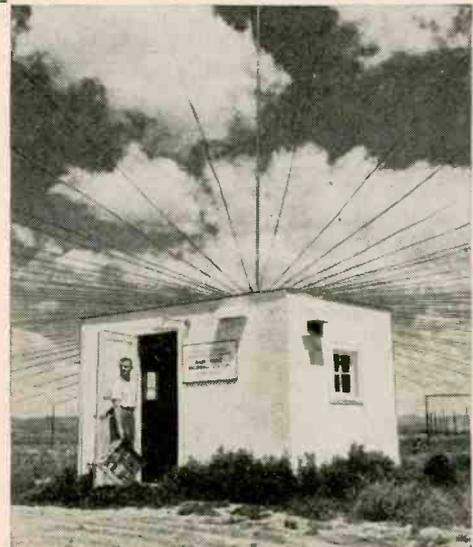The thermometer is inserted in an egg that has been emptied and filled with gelatin. A thermistor measures the temperature and a transistor is the heart of the transmitter. It is powered by three mercury cells that occupy less than $\frac{1}{2}$ cubic inch and run 125 hours. The transmitter shown next to the king penguin egg has an operating range of 80 feet and is accurate to within 0.2°F .



NOISE RECEPTION is the sole purpose of this radio station. Called the dog house by scientists at Boulder Laboratories of the National Bureau of Standards, it is one of a world-wide chain of observation stations that, during the International Geophysical Year, are recording static and radio noise largely generated by thunderstorms. The wires radiating out from the 21.75-foot vertical-whip antenna, near the center of the building, are part of an elevated radial system used to stabilize reception.

automation

The Hickok
Cardmatic,
model 123



Hickok Cardmatic requires no manual settings or roll chart

By HAROLD B. MCKAY

AUTOMATION has reached the tube-tester field in the form of an instrument which checks all important aspects of a vacuum tube under actual service conditions and literally does it in one-two-three fashion.

Operation One consists of plugging a tube into a socket and placing a card in a slot. This immediately tests the tube for shorts, leakage and grid emission. Pushing a button marked 2 tests the transconductance, and button 3 tests the tube for gas.

The new device is Hickok's Cardmatic Tube Testing Machine (models 123 and 123A) and its construction permits anyone who can read the words GOOD and REPLACE to test tubes with laboratory accuracy.

The outstanding mechanical feature of the tester is a multiple-contact sandwich switch. This consists of an assembly of plastic panels about the size of a postcard. The bottom part of the unit contains over 170 specially designed switch-contact units.

These units are made up of plungers resembling copper nails, which, when pushed downward through copper sleeves, enter and make contact with other sleeves below. (See Fig. 1.)

In operation, a card corresponding to the tube type to be tested is put in a slot in the sandwich and pushed until it touches a snap-action switch at the rear of the unit (Fig. 2). This triggers an electromagnet inside the instrument case, which pulls the sandwich assembly down on the copper switch plungers.

If there is a hole in the card over any given switch plunger, it will not be pushed through to the bottom sleeve and the switch remains open. In positions where the card is not punched, it bears down on the switch plunger and closes the circuit.

and the tube tester

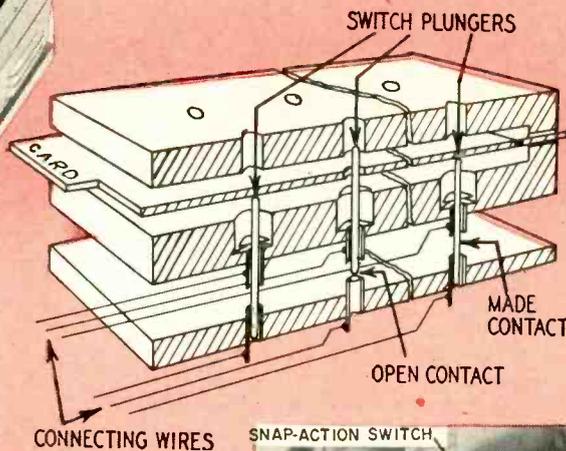


Fig. 1—The card switch, heart of the automatic tester.

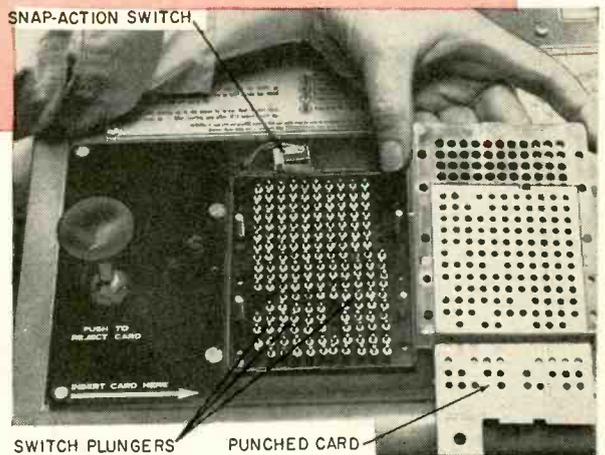


Fig. 2—Inside the switch housing. Each plunger is a separate switch.

A notch cut in the top of the card coincides with the plunger for the sensitive snap-action switch if the card is inserted upside down. This safeguard prevents the test from being made until the card is right side up.

When a test is completed, the card is released by pressing a large button which mechanically restores the sandwich assembly to normal, lifting it upward. This action releases the card so that it can be withdrawn. It also pulls upward on the switch plungers of all made contacts, causing them to withdraw from the bottom sleeve and again become open.

Short test

Once a card and tube have been placed in the machine, operation is almost completely automatic. The first operation, that of testing for inter-electrode shorts, is done at once, without even pushing a button.

A voltage divider places a voltage gradient across all electrodes in the tube. The gradient is such that five neon indicators which peer out from under a tiny hood remain dark if no shorts exist. If a resistance path is present between tube elements, it up-

sets the voltage distribution. The lamps flash for a high- or glow steadily for a low-resistance path in the tube.

Grid emission, a highly objectionable defect not revealed by some tube testers, shows up on the short test because of the way the dc neon lamp supply is polarized when connected to the tube.

Heater-cathode leakage is indicated by the first of three scales on the meter. A definite reject point is indicated (by the words GOOD and REPLACE) but this point may be as low as 10 microamperes for some tubes. The holes in the card determine the test placed on the tube.

An aim in the instrument's design is to overcome the principal objection that many radiomen have to all tube testers, that "the best test of any tube

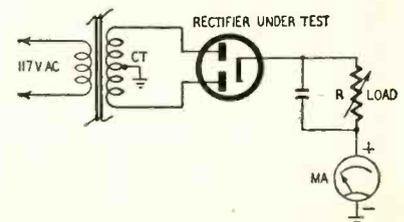


Fig. 3—Rectifier tubes deliver rated current to loads typical of circuits in which they would be used.

TEST INSTRUMENTS



Fig. 4—Potentiometer adjustments are used in calibrating the instrument.


is how it acts in the circuit for which it was designed."

Military standards

A 6X4 is usable with a 150- μ a leakage (at 100 volts) between heater and cathode, while an amplifier such as the 6AU6 cannot tolerate a leakage of over 10 μ a. TV damper diodes also are rejected if leakage exceeds this value. The reject points in all Cardmatic tests are determined by using standard military specifications as a guide.

In all cases, the tester automatically applies conditions which simulate those encountered in actual service. For instance, diodes may be classed as falling into at least six basic operational groups. These include full-wave high-voltage group (5U4); half-wave low-voltage group (35Z5); TV dampers (6W4); TV high-voltage diodes (1B3); high-perveance detectors (6AL5) and low-perveance diodes (6AV6).

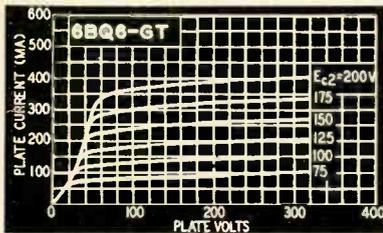Each of these groups is given tests common to the group as well as specific tests called for by the individual tube type. Thus, a 5U4 and a 6X4 will both



Graph of plate curves of a 6BQ6 TV deflection amplifier.

be tested in a circuit using a high-voltage center-tapped ac winding and a load resistance with filter capacitor. The 5U4 will be required to deliver its handbook rating of 200 mas and the 6X4, 70 ma or show as REPLACE (Fig. 3).

Television damper tubes such as the 6W4 must withstand high inverse voltages in service, therefore the Cardmatic applies a set of conditions which will test this feature. A low voltage applied to the plate of such a tube readily tests its emission characteristic, and this may be sufficient for some classes of service. For damper service, however, 1,200 inverse volts are applied because this is what the tube might be expected to withstand in actual service.

Sometimes, in testing diodes, gassy tubes may arc, causing the meter to slam beyond full-scale deflection. If this happens, a protective relay trips, turning the tester off before any harm can be done.

Actual laboratory tests with defective tubes have shown this machine balks and refuses to test gassy tubes.

Triodes

Pentodes and triodes may be operated in one of two basic modes—fixed bias and self-bias.

A fixed-bias test is a stringent one to apply if a tube is intended for self-bias operation. This is because self-bias provides a kind of self-regulating effect for the tube when in operation. Thus, a tube under self-bias conditions will show a mutual conductance rating closer to the published value, while fixed bias would indicate REPLACE long before the tube would fail otherwise.

The tester selects the correct mode before applying a mutual-conductance test to a tube. However, while mutual conductance is perhaps the most important measurement that can be made on most tubes, some tubes in certain applications require an additional test.

An example of this is television horizontal deflection amplifiers which must supply high current. Tubes of this type have plate-voltage current curves like those shown in the graph. These curves feature a knee where plate saturation is reached at about 60 volts, with a given screen voltage. In service this tube must sweep from near cutoff to full saturation at the knee of this curve. Therefore, the test applied to a tube like the 6BQ6-GT checks mutual conductance and makes an additional test for high emission at the knee of the curve.

Tubes which contain two units in one envelope, or extra elements such as the two control grids in the 6DT6, are tested with two or more cards—one for each tube functions.

The Cardmatic model 123A contains a couple of features not found on the 123. These include a cathode-activity or *Life Test* and a provision for testing regulator tubes.

Life test

The Life Test is an approximation, but it is one used with good results by

large tube users such as the telephone company. This feature is operated by a spring-loaded switch which decreases the heater voltage by 10%. If a tube has considerable reserve life left, the mutual conductance does not change appreciably. Tubes in which emission drops as much as 25% for a 10% heater-voltage reduction may be considered as being near the end of their useful life.

The Hickok automatic tube testers do not use a calibration for line voltage. Instead the critical electrode voltages applied to the tube are obtained from regulated power supplies, making line-voltage calibration unnecessary.

But perhaps the most outstanding feature of the new machines is the means by which they can be made to test themselves. Normally a tube tester must be regarded as a sort of a standard; tubes are accepted or rejected on the basis of a reading obtained on the meter of such a tester. Yet the tester itself can lose its calibration or otherwise get out of order, and the user may be none the wiser until he has thrown away a lot of good tubes.

The conventional tube tester is checked by specially calibrated tubes—tubes which have been tested by a laboratory. These tubes are retested on a tube checker of doubtful accuracy to see if the same readings are obtained as were produced in the laboratory.


None of this is necessary with the Cardmatic. Each instrument comes supplied with a set of special test cards. To use them, you have only to remove a small panel on the side of the instrument, which exposes a set of potentiometer shafts (see Fig. 4). Each card is placed in the slot assembly and the corresponding potentiometer adjusted to a specified reading on the meter scale. The card itself tells the amount of deflection which should be obtained on the meter.

These adjustments compensate for aging of the tubes inside the tester and they are not dependent upon the use of standard or pretested tubes.

One of the principal ideas which governed the design of the tester was the creation of a foolproof instrument which could be operated by the customer himself. This is in line with the thinking which is placing tube testers in supermarkets and drugstores.

The Cardmatic is expected to have a profound appeal to this class of customer. This could be especially true in radio shops which are meeting the supermarket competition by allowing customers to do their own tube testing.

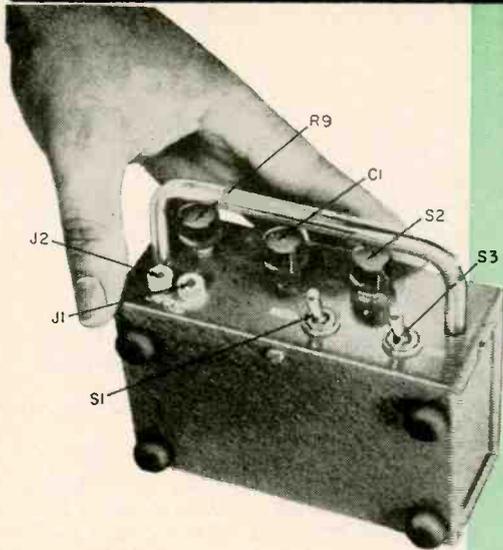However, beyond this obvious application, the automatic tube-testing machine has a strong appeal to industry because of its foolproof operation. If the machine is used in special industrial applications where tubes are operated in something other than their normal manner, special cards can be supplied, which will be punched out to supply a test for any type of tube operation required. END



By EDWIN BOHR

THIS television bar generator occupies no more toolbox room than a couple of 5U4's. It is just the thing for either home-service calls or bench work. There are no vacuum tubes—transistors are used throughout—and the unit is entirely self-contained.

No dangling and tangling power cord is needed. A single 4-volt mercury battery supplies enough power for about 2 years of operation in a shop with plenty of work to get out.

The circuit contains three oscillators and uses four transistors. One oscillator generates a carrier signal in the 30-mc range. Harmonics from this oscillator fall within the TV channels, producing good signals even in the high end of the vhf band.

This 30-mc oscillator uses a surface-barrier transistor made by Philco. These transistors cost more than conventional junction varieties. But, if you really need a bar generator in your service work, this additional cost will not be prohibitive. The generator, including battery, can be assembled for around \$32.

Other transistors used in the unit are two G-E type 2N107 and a G-E 2N135. The 2N107 transistors function in a multivibrator that generates the horizontal bar frequencies for modulating the carrier oscillator. This audio-frequency signal is also very handy for signal-injection checking of amplifiers and audio stages of radios and TV sets.

The vertical bar generator oscillates at 10 times the horizontal sweep frequency. This is well into the rf region and we found that an L-C tuned-circuit oscillator is necessary for adequate frequency stability. A miniature transistor type if transformer, with additional shunt tuning capacitance, serves this purpose.

Circuit details

Looking at the schematic (Fig. 1), you can see that the circuit is pretty simple and naturally divides itself into


TV

Four-transistor miniature unit generates horizontal and vertical bars; is easily built



GENERATOR

for your service kit

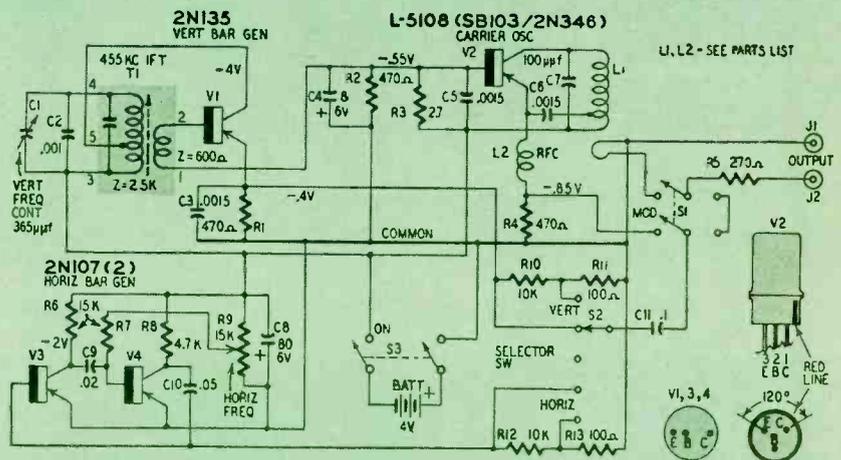

- R1, 2, 4—470 ohms
- R3—2,700 ohms
- R5—270 ohms
- R6, 7—15,000 ohms
- R8—4,700 ohms
- R9—pot, 15,000 ohms, miniature (Lafayette VC-35 or equivalent)
- R10, 12—10,000 ohms
- R11, 13—100 ohms
- All resistors 1/2 watt or less
- C1—365 μf, variable (Lafayette MS-274 or equivalent)
- C2—.001 μf, tubular ceramic
- C3, 5, 6—.0015 μf, disc ceramic
- C4—8 μf, 6 volts, miniature electrolytic
- C7—100 μf, disc ceramic
- C8—80 μf, 6 volts, miniature electrolytic
- C9—.02 μf, 75 volts, ceramic
- C10—.05 μf, 75 volts, ceramic
- C11—0.1 μf, 75 volts, ceramic
- J1, 2—tip jacks
- L1—5 turns from Barker & Williamson No. 3003 Mini-ductor
- L2—rf choke, approximately 30 turns No. 26 wire, 1/2-inch diameter
- S1—dpdt, toggle
- S2—1-pole 5-position rotary
- S3—dpst, toggle
- T1—transistor if transformer (Lafayette MS-268-A or equivalent) 455 kc; primary, 25,000 ohms; secondary, 600 ohms
- V1—2N135
- V2—L-5108 (SB103/2N346)
- V3, 4—2N107
- BATT—mercury, 4 volts (Mallory TR-233R or equivalent)
- Case—5/4 x 3/4 x 2/3 inches (ICA 3797 or equivalent)
- Perforated, insulated chassis board
- Handle
- Knobs
- Miscellaneous hardware

Fig. 1—Circuit of the miniature generator.



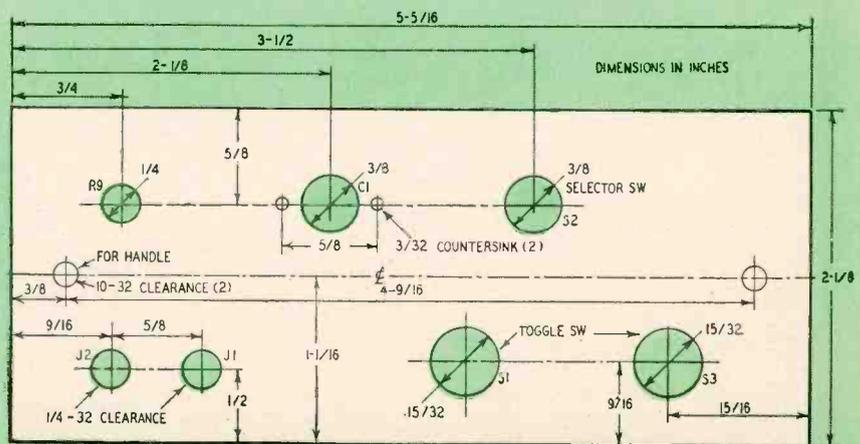


Fig. 2—This panel layout was found to be the best.

TEST INSTRUMENTS

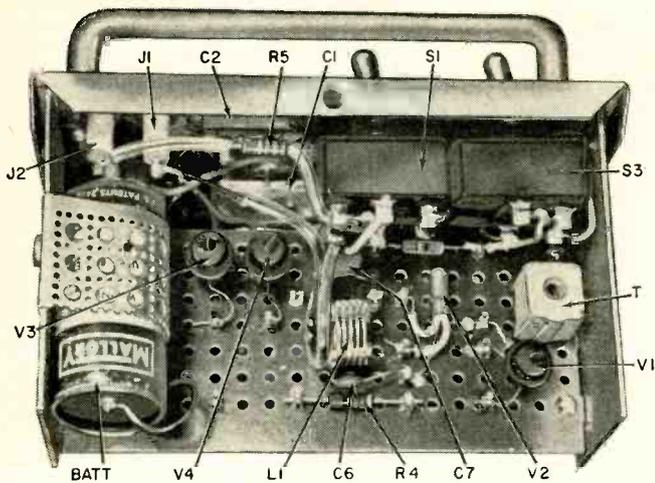

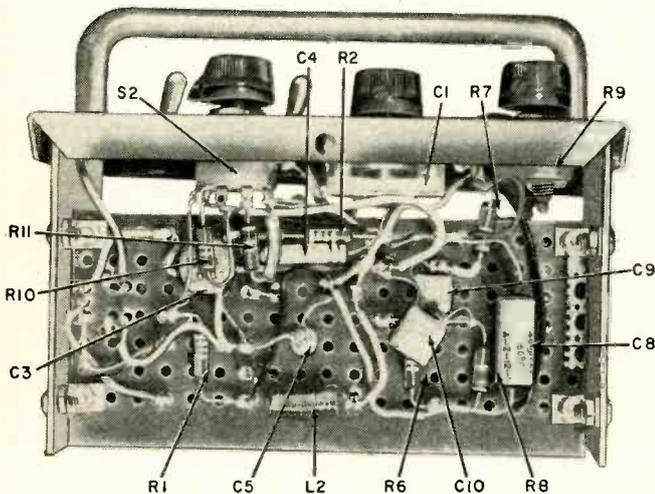Top of the chassis board. Transistor sockets are not used.



The other side of the chassis board. Most small parts are mounted here.

necting the generator to the TV set.

Switch S1, in one position, connects the output of S2 to V2's emitter for modulation and also connects the pick-up loop to the output jack J2. This position of S1 is marked MOD on the panel. The other position of this switch connects S2 directly to the output jack J2. The outputs of either the horizontal or vertical bar generators are then available for direct injection into video amplifiers.

In our model of this generator, S2 is an eight-position switch, but only four positions are electrically active. One dead position is necessary to turn off modulation. Only a five-position switch is needed. I used the extra terminals of the eight-position unit for tie points.

There are two switch positions for both of the modulating oscillators. One provides a signal attenuated by 100 for signal injection into high-gain amplifiers without overloading them. For modulating the carrier, S3 must be in the unattenuated positions.

Vertical bar generator

The vertical bar generator uses a 455-kc if transformer, shunted with both a fixed capacitance of .001 μ f and a variable tuning capacitor. These capacitances are in addition to the capacitance inside the transformer can. Capacitor C1 is variable. The one shown in the photographs is a two-gang superhet type. We used it *only* because it was on hand. This two-gang capacitor is a Lafayette MS-270 but, because of its lower cost, we recommend a single-gang MS-274 be used. They are very compact, solid-dielectric types.

The if transformer we used is a Lafayette MS-268-A. This type is desirable because it can be tuned from the top — in fact, from either end.

A vertical-bar modulating signal is taken from the emitter of V1. It might appear that C3 would bypass all this signal to ground. It does not. At the oscillator frequency, its reactance is roughly 700 ohms.

Two inexpensive G-E 2N107 transistors, operating in a multivibrator circuit, produce a horizontal-bar modulating frequency. Because of the non-linear operating conditions for this type of circuit and variations in low-cost transistors, the values of C9 and C10 *may* have to be varied somewhat. This is a job that must, of course, be left until the generator is completed.

If the frequency-varying control R9 does not have enough range to produce the number of desired bars, lower the values of these capacitors to increase the number of bars and vice versa.

Despite the low internal impedance of the mercury battery, a bypass electrolytic C8 is placed across the horizontal bar generator supply voltage. This prevents feedback through the collector supply.

Construction

The cabinet is a control and switch

three sections: carrier oscillator, vertical bar generator and horizontal bar generator. Of course, the carrier oscillator is the heart of this unit.

As you probably know, we must apply a bias to transistors to cause collector current to flow. Also, the bias circuit should be designed to maintain a constant collector current, despite temperature changes and varying transistor characteristics.

Resistors R2 and R3 connect across the battery supply and provide a constant bias voltage to both the L-5108 carrier oscillator transistor (V2) and the vertical bar 2N135 transistor (V1). This voltage is applied to the transistor base circuits. The emitter resistors of these transistors are chosen for the desired collector current.

Resistor R4 determines the nonoscillating current of V2. The assigned value of 470 ohms sets this current at about 1 ma. However, when the circuit begins to oscillate, rectification at the emitter-base junction changes this bias, automatically placing the operating point in the class-C region.

With V2 oscillating vigorously, the rectified signal may reach an average value of 0.3 volt. Notice the higher negative voltage of V2's emitter. Ordinarily, if this were an amplifier rather than an oscillator, the emitter potential would then be approximately 0.1 volt

lower than the value of the base voltage.


Choke L2 is a simple coil of wire designed to keep the 30-mc carrier out of R4 and the bar-generating circuits. The exact wire size and turns are not too important.

A feedback tap for the emitter is placed approximately three-quarter turn from the -4-volt end of coil L1. This, we found, produced the strongest carrier. If you wish to experiment with this tap position, turn off all modulation, connect a low-range voltmeter across R4 and place the tap for maximum voltage reading.


Although the oscillator is fixed-tuned, it could easily be made variable by replacing fixed capacitor C7 with a variable unit. Coil L1 is a five-turn section from a prewound type 3003 Miniductor. This coil has a diameter of $\frac{1}{2}$ inch and a pitch of 16 turns per inch. If you wish, you can wind your own coil from No. 20 wire. The exact wire size is noncritical, but the coil should be wound on a form and doped for rigidity.

Notice the oscillator coil is placed near the geometric center of the case (see photos). This reduces loading effects of the small steel cabinet.

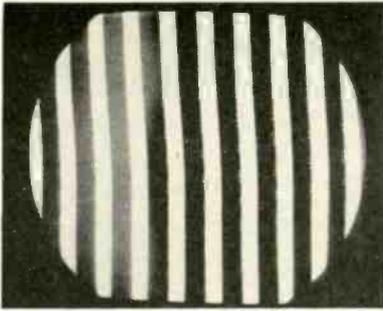A single loop of stiff wire, insulated with spaghetti, couples the oscillator carrier to the output jacks. A 270-ohm series resistor R5 is necessary to eliminate standing waves on the leads con-



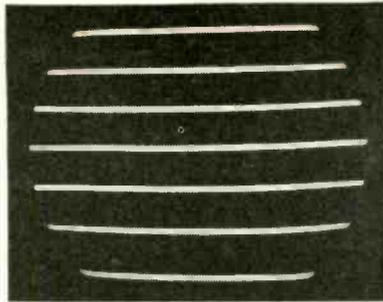Vertical bars produced by the all-transistor unit.



Horizontal bars generated by the portable instrument.

case, fabricated from steel with welded end plates.

This is a small case but there is enough room to mount all parts with a generous margin of space and accessibility. The completed electronic package is strong enough to drop from a service truck without major damage.

A front-panel layout (Fig. 2) shows where to place the controls and switches. This is an optimum arrangement—the result of several hours' planning—and I suggest very strongly that it should be followed exactly.

The insulating-board chassis is supported by two aluminum brackets. In my model, these brackets are held to the front panel by the same screws that secure the chrome handle. If you do not want to use a handle, use the handle holes for ordinary screws. A 6-32 screw fastens the brackets.

Four small right-angle brackets hold the insulating-board chassis to the aluminum brackets.

A strap of perforated aluminum, cut from a large sheet sold at the local hardware store, holds the mercury cell in place. One end of the strap hooks around the insulating-board chassis and the other end wraps over the aluminum bracket and is held there by a self-tapping screw.

We attached rubber feet to the case with aluminum rivets. These are also sold in hardware stores. The rivet is pushed into the rubber bumper and through a hole in the case. Then a short spacer (a sawed-off piece of volume-control shaft works very well) is pushed against the rivet head inside the bumper and rested against the work bench. Thenpeen the rivet inside the case, using a punch if necessary.

Wiring the generator

I suggest wiring the horizontal bar generator first. When it is complete, it can be checked by connecting its output to headphones or into the video amplifier of a TV set. An audio growl with a rather high pitch should be heard in the phones. Horizontal bars should be seen on the screen.

Now, assemble the carrier oscillator. If it is oscillating, the emitter voltage should be greater than the base voltage. If it does not oscillate, and the voltages check OK at the base and collector, add more capacitance to C7 or try changing the tap on L1. The L-5108 (V2) is a hot little transistor and I have never

had any trouble getting it to work, but I offer these suggestions as a safety measure.

Generous leads are left on all the transistors. This protects them from abusive soldering practices and breaking leads at the case.

Be sure of your wiring for the L-5108. If it is wired correctly, nothing should go wrong. But even a momentary wrong voltage can ruin its microscopic internal connecting leads.

With this much wired, you should be able to receive the carrier with horizontal bar modulation. If not, check your switches and wiring for possible errors.

Next, wire the vertical bar generator. This will produce vertical stripes on the TV screen, of course. If the generator works except for these bars, try reversing the leads numbered 1 and 2 on the if transformer or increase the value of C3. With variable capacitor

C1 in mid-position, adjust the if transformer slug, with an insulated screwdriver (nonmetallic), until the desired number of vertical lines are obtained.

As you can see in the photographs, leads were soldered to the mercury battery. It is easy to solder to a mercury cell if you scrape the surface and quickly tin it with a hot iron. Then tack a pretinned wire in place with the iron.


Here is one last construction note. If it is anticipated that high voltages may accidentally ever be applied to J1 and J2, I recommend that a .01- μ f capacitor, with a suitable voltage rating, be placed in series with resistor R5.

Using the unit

This is simple. Just flip S3 to the ON position, connect J1 and J2 to the set's antenna terminals and switch on the modulation. The number of bars and their sync are adjusted from the front panel. Receiver brightness and contrast are adjusted for the best pattern.

The tuned-circuit constants gave us a signal on channels 5, 8 and 13. For other channels, vary the value of C7.

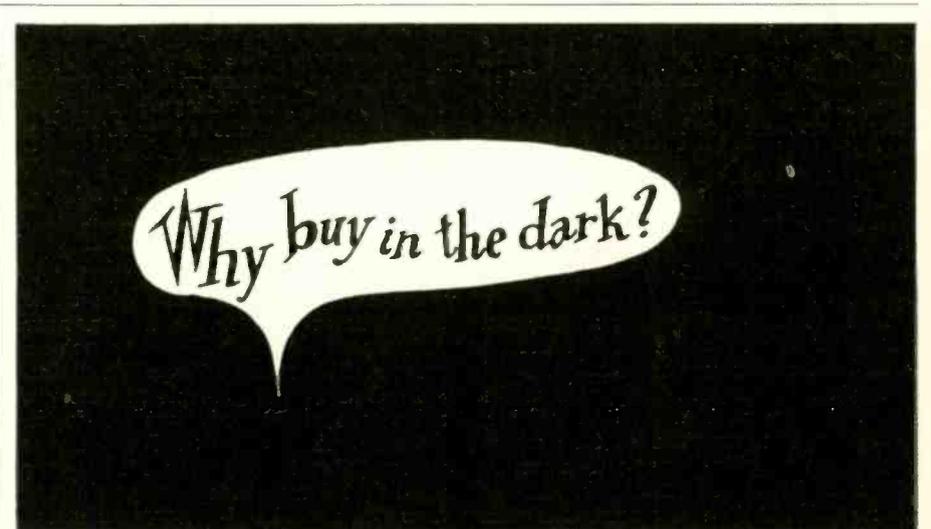This circuit shows that transistors are becoming more capable replacements for vacuum tubes, especially in high-frequency applications. In the not-too-distant future I hope to have a completely transistorized color bar and dot generator, both in the same size case. END



RADIO-ELECTRONICS believes that its readers have the right to know just what to expect when they buy tubes through mail order advertising. That's why since January 1956, we have been insisting that mail-order tube advertisers warrant that the tubes they are offering for sale are new and unused, not mechanical or electrical rejects, or not washed or rebranded. If they do not meet these requirements, or if they are in any way substandard, the advertiser must say so specifically in his ad.

IMPACT NOISE METER USES 3 TRANSISTORS

A transistorized instrument to measure impact noise without an oscilloscope

By NATHANIEL RHITA


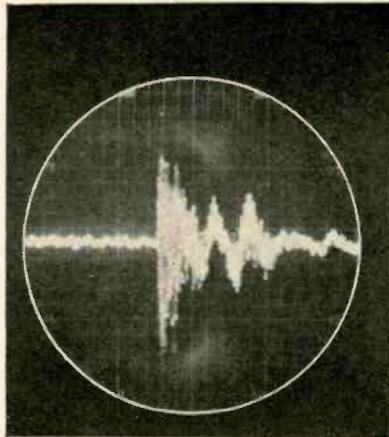


Fig. 1—Oscilloscope trace of a handclap. Horizontal scale 2 msec per division.

Fig. 2—Oscilloscope trace from a small drop hammer. Horizontal scale 10 msec per division.

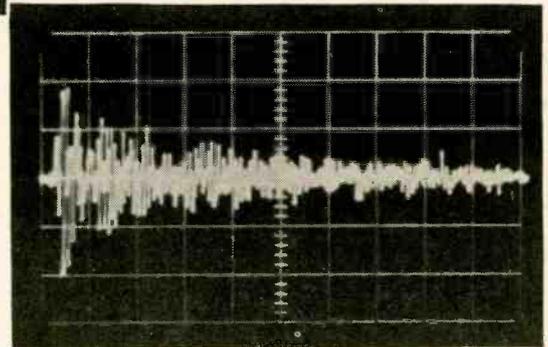

IMPACT noise—the sound of drop hammers, typewriters and gas engines—is important to industrial technicians who must study it to be able to control and reduce it. These sounds generate complicated wavetrains that vary greatly from one instant to the next. Fig. 1 is a typical handclap wave and Fig. 2 that of a small drop hammer. In each case the peak pressure is approximately 118 db (above .0002 microbar). An ordinary sound-level meter alone is of little use in measuring impact noise which varies so much in so little time. The oscilloscope method is effective but very complicated and expensive. General Radio Co. has an instrument (No. 1556-A) designed to measure impact noise.

This meter uses three transistors and one tube. It is intended for use with a noise-level meter or analyzer.

Fig. 3 is a simplified diagram of the new instrument. The first transistor, V1, is a phase inverter so that either positive or negative noise pulses can be measured by means of S1. V2 and V3 form a highly stable amplifier with negative feedback. Output can be switched into separate networks.

With S2 in the QUASI-PEAK position the network has a rise time less than 1

millisecond and a slow decay, about 0.6 second. Therefore, the capacitor can follow successive peaks quite closely. This position is useful for measuring recurring noises like the explosions of a gas engine.

In the PEAK position, the attack time is only 100 microseconds, practically instantaneous. The peak voltage is stored on a capacitor which has no discharge path. This voltage is stored for several seconds without appreciable loss so it may be measured by the voltmeter tube V4 at a later time.

The TIME AVERAGE network provides seven different time constants (not shown) so its capacitor charges for a short or long interval as desired. This voltage also remains on a capacitor for subsequent measurement. This network indicates the average level of a noise as measured over a definite period of time.

Peak and average levels of an impact noise are important, but so is the duration of the noise. Most impact noises (Figs. 1, 2) begin with an initial peak that decays indefinitely. The wave duration may be defined by the time taken for its peak to fall 8.7 db. This is called the time constant of the impact decay. The time constant is determined from the peak and average levels of the

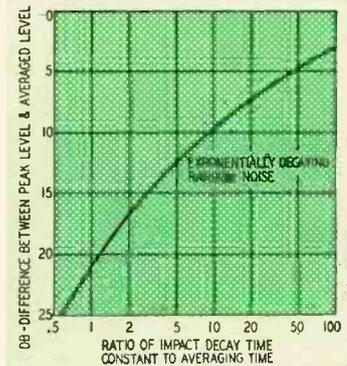


Fig. 4—Chart of relationship between the ratio of the peak-to-average value and the time constants of an impact (plus those of the circuit).

noise as well as the charging time (averaging time) of the capacitor network. These relationships are shown in Fig. 4.

As an example, let the impact meter be set to an averaging time of .01 second. A noise is now measured as having a peak of 115 db and an averaged level of 98 db. This gives a difference of 17 db. The chart shows that the time constant is twice the averaging time. Therefore, the impact decay time is $2 \times .01$, or .02 second. END

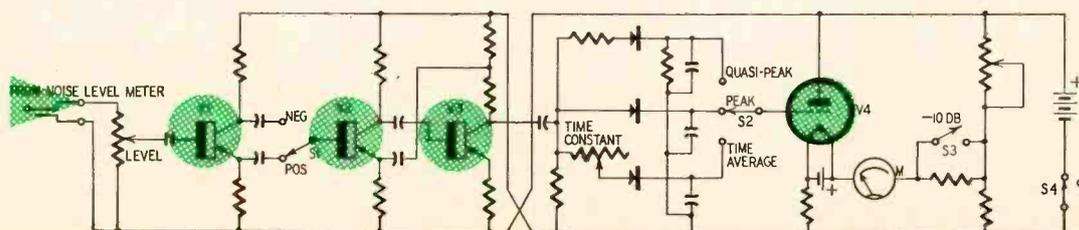



Fig. 3—Simplified circuit of the meter.

BUILD THIS...

Amplifier-Rectifier VTVM for Audio Testing

First of a series of articles on apparatus and techniques for testing hi-fi equipment

By L. B. HEDGE

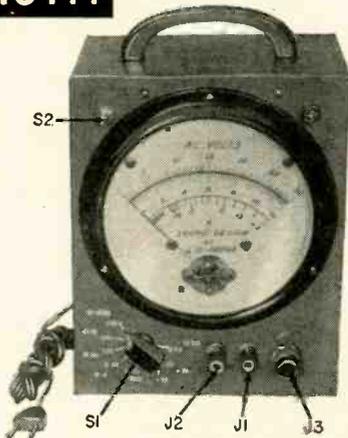

Finished meter in its portable case.

THE serious worker in the audio field—professional or amateur, engineer or hi-fi enthusiast—is constantly faced with the problem of testing the equipment on which he works. The simplest and ultimate test of sound equipment is the listening test which, in practice, is simple only in concept. Evaluation of sound by listening depends on subjective reactions of the listener. These reactions vary greatly between any two persons.

Practical tests of audio systems which permit evaluation of specific system performance characteristics and their correlation with pertinent characteristics of the system's components have been evolved. Amplifiers, which are basic units in all electronic sound systems, are evaluated by tests which determine: amplification (voltage and power gain); frequency response (amplitude distortion); harmonic and intermodulation distortion, and phase-shift characteristics.

Each of these characteristics can be determined by tests using a variety of instruments and accessories. An audio oscillator and a high-impedance ac voltmeter alternately connected across the input and the output of the amplifier under test, provide basic gain, frequency response and output power checks (see Fig. 1). An oscilloscope connected across the voltmeter simplifies detection of amplifier oscillation and permits identifying serious distortions (changes in waveform between input and output).


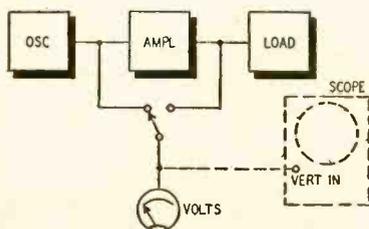


Fig. 1—Basic test setup for gain, frequency response and output power checks.

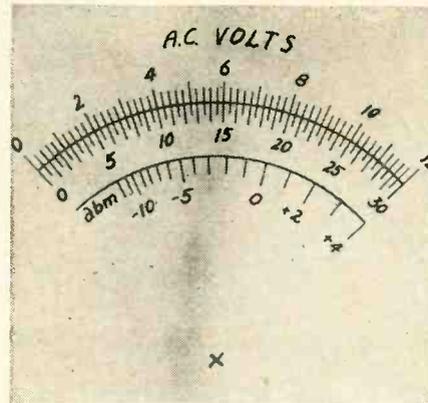

Scales for meter. Drawn for 90° movement.

Adding an electronic switch to the test setup makes visual comparison of input and output waveforms much easier. It also allows recognition of distortion of a much lower order than that identifiable with a scope alone. Phase-shift measurements can be made with a scope with or without an electronic switch, although the switch and scope method is generally more accurate and less involved (see Fig. 2).

Including a narrow-band filter (analyzer) in the setup—an instrument which suppresses any selected frequency in the audio range, while giving negligible attenuation to the higher harmonics of the selected frequency—permits measuring total harmonic distortion (Fig. 3). (See "Measuring Distortion" and "Distortion Totalizer" in the December, 1951, and August, 1954, issues, respectively.) Adding a mixing network (See "Build an IM Analyzer," December, 1953) to supply a mixture of a 60-cycle signal with the output of an audio oscillator to the amplifier input permits determining intermodulation distortion by measurements made with the scope and ana-

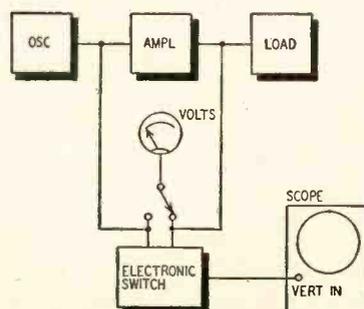


Fig. 2—Electronic switch and scope added to basic setup.

lyzer (Fig. 4).

Except for certain readings made directly from the scope in the intermodulation and phase-shift tests, all measurements are of voltage measurements. Because of this basic function of voltage measurements in testing procedures and because of voltage measurements are also necessary for adjusting oscillators and other af test equipment, the logical unit with which to start an af test setup is an audio voltmeter.

Why an A-R vtvm

Since audio tests require voltage measurements over a range from a few millivolts (inputs to preamps) to over 100 volts (output signal across the primary of a power output transformer), over a wide frequency range (30 to 15,000 cycles at least; 15 to 50,000 cycles for special tests and analysis), and with a minimum loading of the test circuit by the meter, an amplifier-rectifier (A-R) type vtvm is indicated for the job. Although the A-R type vtvm responds to the mean (average) voltage rather than the root-mean-square (effective) voltage for pure sine-wave inputs, the errors resulting from using meter readings for effective voltage values will be less than 4% for waves containing up to 10% in harmonics and much smaller for waves with smaller harmonic content. No more accurate instruments of high input impedance, wide frequency range and extended voltage range are available as simple and economical units. The A-R vtvm's accuracy is quite adequate for tests in which the decibel is the significant unit and basic scale for reference standards.

The meter is quite conventional in general concept and form. It differs from more conventional instruments of this type, however, in two significant features:

1. The indicating meter used is not

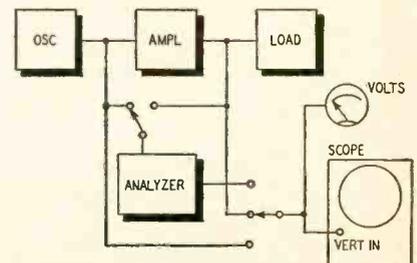


Fig. 3—Analyzer provides accurate harmonic-distortion measurements.

TEST INSTRUMENTS

a supersensitive unit—a 5-ma meter is used instead of the conventional 200- μ a meter.

2. The two voltage scales (each of which is used with successive multipliers of successive powers of 10) differ from each other by a factor of 2.5 (0.4) instead of the more conventional $\sqrt{10}$ ($\sqrt{0.10}$), with db intervals of 12 and 8 instead of 10 and 10.

The first of these differences makes possible the use of cheaper, more readily available and less delicate meter movements. To provide the additional current in the meter circuit, a "power" output stage is required, but the actual power requirements are sufficiently low that no essential complication results therefrom. The second feature permits the use of even values of precision resistors in the voltage range multiplier and considerably simplifies the meter scales, both in layout and for reading, since the same scale divisions are used on each range scale.


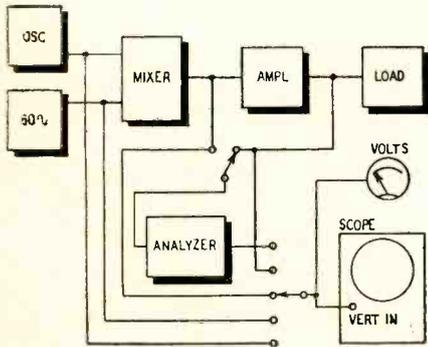


Fig. 4—Adding a 60-cycle source and mixer prepares for IM distortion tests.

Layout and construction of the meter system are critical in only a few aspects. Since the input stage of the amplifier is a high-gain stage with high input impedance and operating at a low input signal level, complete shielding of the unit is necessary to prevent inaccuracies due to stray signal pickup. The unit shown in the photos is built into a wooden frame with a light sheet-copper shield attached to the outside and with a metal front panel and perforated rear cover plate. If a metal cabinet is used, ventilation should be provided for the tubes and transformer. Heater supply wiring should be twisted to minimize hum pickup. The masonite subpanel is attached to the meter by the two meter terminals. The insulated panel reduces stray capacitances in the circuit wiring. These capacitances tend to reduce the high-frequency response of the amplifier and consequently of the meter itself.

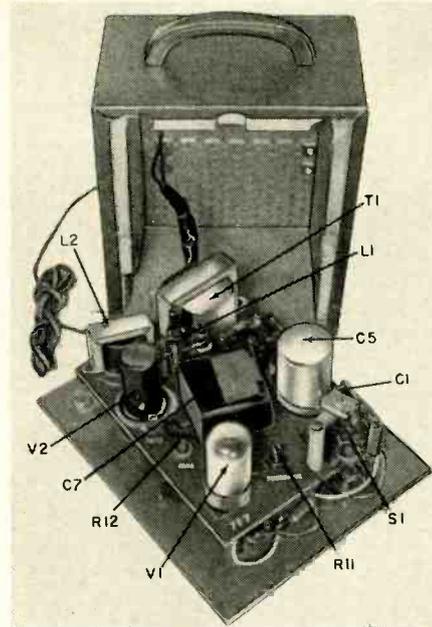Capacitors C1, C2 and C3 (See Fig. 5) provide high-frequency compensation for the range attenuator network. With these capacitors omitted, the meter unit provides readings that are accurate to within a fraction of a decibel from 15 to more than 20,000 cycles.



Inside the meter's case.

Including the compensating capacitors extends the accurate range beyond 50,000 cycles. If the extended frequency range is required, connections A and B should be left open on assembly and completed as part of the calibration procedure described later. The inductance L1 consists of two TV width controls in series and set at maximum inductance (16 mh each).

Meter scales

Layout of the meter scales is indicated at head of article. Voltage scales

can be drawn using the diagram as a template for 90° meter movement scales. Scales for meter movements other than 90° can be drawn with ruler, compass and protractor without difficulty. Scale markings for the dbm (0 = 0.7746 volts—0.001 watt at 600 ohms) are shown in the table in terms of the 0–1.2-volt scale.

On completion of the vtvm assembly, the cascade bias potentiometer (R12) should be set at approximately mid-position, and the feedback potentiometer R11 (calibration control) set at maxi-

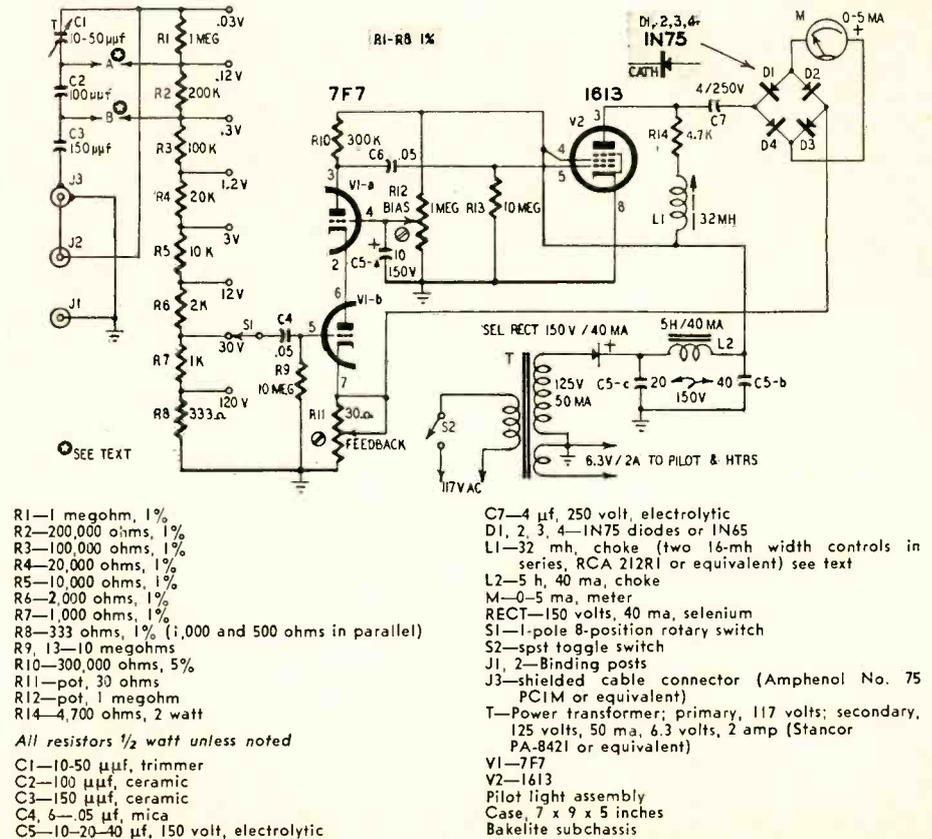


Fig. 5—Circuit of the A-R vtvm.

Regulating Bias and Polarizing Voltages

Use neon bulbs
as voltage regulators

By RONALD L. IVES

imum resistance. After a warmup period of a few minutes, the range switch should be set to the 0-12-volt range and a 6.3-volt 60-cycle signal connected across the meter input. This check signal can be provided by a temporary connection between the ungrounded heater supply and the ungrounded input terminal. With the 6.3-volt signal applied, R12 should be adjusted for

TABLE I—Dbm Voltages into 600-ohm load—1.2 Volt scale, and additive factors for other scales.


| Dbm | Volts | Voltage Range | Dbm |
|-----|-------|---------------|-----|
| -14 | .155 | 0- .03 | -32 |
| -13 | .173 | 0- .12 | -20 |
| -12 | .195 | 0- .30 | -12 |
| -11 | .218 | 0- 1.2 | 0 |
| -10 | .245 | 0- 3.0 | +8 |
| -9 | .275 | 0- 12.0 | +20 |
| -8 | .308 | 0- 30.0 | +28 |
| -7 | .346 | 0- 120 | +40 |
| -6 | .388 | | |
| -5 | .436 | | |
| -4 | .489 | | |
| -3 | .548 | | |
| -2 | .617 | | |
| -1 | .670 | | |
| 0 | .775 | | |
| +1 | .869 | | |
| +2 | .975 | | |
| +3 | 1.094 | | |
| +4 | 1.228 | | |

maximum meter reading. When the correct (maximum output) setting for R12 has been established, R11 is adjusted to give a meter reading corresponding to the input signal voltage. If a reference meter is available for checking this voltage, this adjustment will provide the required calibration for the meter. If a variable voltage source and reference meter are available, mid-range checks in each voltage range should be made and R11 adjusted to give the smallest average errors in all ranges (the errors should all be small if the multiplier resistors are accurate, but some deviation can be expected).

The compensator capacitor network can be adjusted with a signal of about 10,000 cycles and 0.1-volt amplitude. The signal should be sufficiently stable to maintain its voltage amplitude over an extended period during which the meter is disconnected from it. Check the voltage reading with the meter range switch set to the 0-0.12-volt range. Complete the connections A and B and adjust C1 to give the same reading that it gave on the same signal with A and B open. The compensation thus provided is adequate for the extended audio range of 15-50,000 cycles.

Tubes used in this unit (7F7 for V1 and 1613 for V2) were selected on the basis of performance and low-priced availability. The 7F7 can be replaced by a 6SL7 without changes in the circuit (a different socket is required, however). The 1613 can be replaced by a 6F6, a 6V6 or a 1621 with no changes at all, but calibration and other adjustments may require changes, due to differences in characteristics—the 6V6, for example, will require somewhat greater feedback due to its higher transconductance. END

REGULATION of bias and polarizing voltages used in many types of electronic equipment, test instrument power supplies, etc., is quite costly power-wise when standard regulator tubes are used. Each tube uses 1½ to 3 watts, which is radiated as heat. The regulator circuit uses and radiates as heat an additional wattage determined by the I²R loss in the dropping resistor. This power loss is particularly annoying because the current consumed by the bias or polarizing circuit is usually less than 1 ma, and in some instances is actually much less than 1 μa. Therefore the power needed to control the bias or polarizing voltage is several thousand times that used in the regulated circuit.

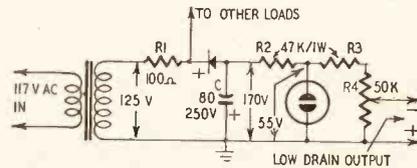

R1—100 ohms, 1 watt
R2, 3-47,000 ohms, 1 watt
R4—pot, 50,000 ohms
C—80-μf 250-volt electrolytic
NE-32 neon bulb
Half-wave power transformer, primary, 117 volts, secondary 125 volts, power rating to suit load current

Fig. 1—Neon-regulated bias rectifier circuit.

This power waste can be reduced by a factor of 5 or more in many low-voltage low-current regulated supplies by using neon bulbs as regulators. Experiments show that many neon bulbs, drawing from 1/25 to 1 watt, have a constant voltage drop of about 55 through a very wide range of current consumptions, and hence make ideal voltage regulators.

A typical bias rectifier circuit and regulator, using neon-bulb regulation, is shown in Fig. 1. Output voltage, at various ac inputs, is plotted in Fig. 2, output being set at 3 volts when line voltage was 117. Some shifting of the end points of the plateau of the curve

is possible by changing the value of the series resistor. The length of this plateau can be extended by using a higher-wattage neon bulb and shortened with a bulb of lower wattage. In general, the very small neon bulbs such as the NE-2 and NE-51 are not very satisfactory as regulators, but all resistorless neon bulbs of higher wattage seem to work very well. Bulbs with a symmetrical arrangement of the electrodes are completely nonpolar and work equally well on either socket connection. Bulbs with asymmetrical electrode arrangement tend to be polar and may work better if the connections are reversed.

When operated about midway between the "will-fire" current and the catalog rating, the life of standard neon bulbs is measured in tens of thousands of hours.


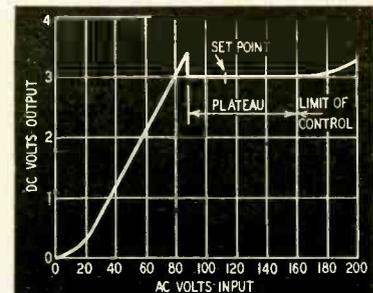


Fig. 2—Regulation characteristics of neon-regulated bias supply.

One limitation on the use of neon bulbs as regulators should be kept in mind—they do not work well as regulators in total darkness. This difficulty can be eliminated very effectively and cheaply by putting a drop of luminous paint on each bulb before installation in a dark location. If ambient light exceeding 0.1 foot-candle reaches the tube location, this precaution is not necessary. After an initial "triggering" by something less than 0.1 foot-candle, the bulbs perform satisfactorily as regulators until the ambient light level exceeds 1,000 foot-candles. END

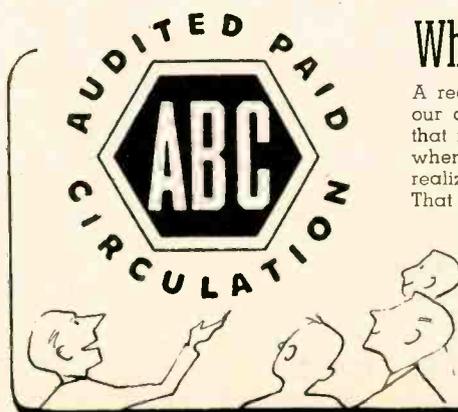

What does that mean?


A reader recently asked us what the ABC on our contents page meant. We quickly replied that it meant Audit Bureau of Circulations. But when we thought about it for a while, we realized that was not the complete answer. That insignia means RADIO-ELECTRONICS is a member of a nonprofit association established 43 years ago to insure dependable circulation statements and accurate details about the character of circulation. It is in effect a badge of honesty—a mark of character. RADIO-ELECTRONICS is proud to be a member of the group privileged to display it.




ELECTRONIC SURVEILLANCE KIT

Part II—More pickups and accessories to make your kit more versatile


By LOUIS E. GARNER, JR.

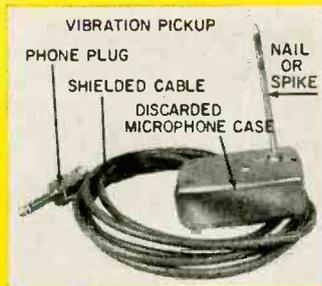

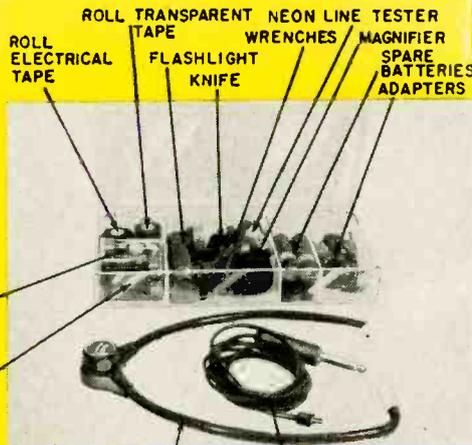
The vibration pickup. The spike is solidly fastened to the case.



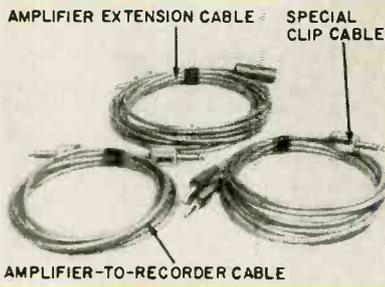TELEX HEADSET HEADSET-TO-AMPL CABLE
Spare-parts kit and Telex headset.



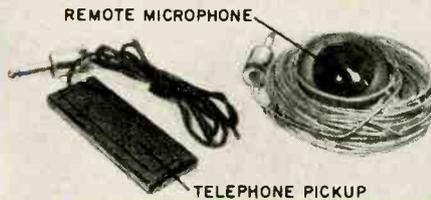Accessory cables include: amplifier to recorder, amplifier extension and special clip cable.



Telephone pickup and remote microphone. Thin cable for the microphone makes its concealment easy.



Tool kit. Small tools are wrapped in convenient plastic case.

LAST month we described the main components that make up an electronic surveillance kit. You now have the amplifier, an rf pickup and an induction pickup. To extend the versatility of your kit, a variety of other pickups, listening devices, cables, spare parts and tools are needed. These are the items described here.

Vibration pickup

Few of the accessories included in an electronic surveillance kit are as versatile as a vibration pickup. The unit is used for such tasks as locating a suspected time bomb; listening through doors, windows and partitions; detecting hidden machinery or even opening combination locks and safes. Basically, it is an electromechanical transducer, converting physical vibrations into audio-signals. (See diagram.)

The pickup consists of a standard crystal or ceramic phonograph cartridge mounted in a thick-walled metal case. The model shown in the photographs was assembled from a discarded microphone. The original, defective cartridge was removed and the phono cartridge installed. A hardened nail or metal spike is mounted in one side of the case so that it bears against the cartridge's outer case. A 3- or 4-foot shielded output cable is provided, with the braid connected to one cartridge terminal and the metal housing, and the center lead to the cartridge's other terminal.

In operation, the point of the spike is held against the source of vibrations—a package, safe, door or wall partition. The vibrations travel along the spike to the phono cartridge's case and are transferred to it. The case tends to vibrate *around* the element, which in turn resists this vibration by virtue of its own inertia. A twisting action results, producing an electrical signal in the cartridge element. The signal is fed to the amplifier.

The telephone pickup is one of the standard flat inductive pickup coils stocked by many local and mail-order radio parts distributors and intended for use with high-gain tape recorders. A plug to match the amplifier's IN jack is added to the output cable. In use, the telephone pickup is simply placed under the base or next to the receiver of the telephone with which it is to be used. This unit has more sensitivity than the induction pickup, but it is not satisfactory for line pickup.

Intended for use as a plant in a suspect's room or office, a remote microphone permits the operative to overhear personal and business conversation. It consists of a thin crystal microphone cartridge attached to a 30- to 50-foot length of shielded cable and a plug to match the amplifier input. Small-diameter shielded cable is essential to permit concealment under rugs, behind baseboards, along moldings or behind furnishings. The kit may be equipped with several remote microphones since they must often be expendable.

A standard headset is the output de-

vice most commonly used. It is a high-impedance magnetic or crystal earphone equipped with a plug to match the amplifier's output jack. Any standard headset is suitable, but it is best to choose a unit that is comfortable to wear, compact and lightweight. Sturdy construction is another must since the headset may, on occasion, receive rough treatment in transportation and handling.

Essentially a high-impedance magnetic or crystal hearing-aid type earphone equipped with a plug to match the amplifier's OUT jack, a special earphone is used for undercover work where the operator may be seen by other people.

In a typical situation, the amplifier will be concealed in an inside coat pocket and the special earphone mounted so the operator appears to be an ordinary hard-of-hearing individual wearing a hearing aid. Actually, the operative may have the vibration or rf pickup concealed in the palm of one hand, with the connecting cable inside his coat sleeve.

Cable requirements

An assortment of properly terminated shielded cables is essential if the kit is to have maximum utility. These cables may be from 4 to 6 feet long, with one end terminated in a plug to match the IN and OUT amplifier jacks. The other end of each cable is terminated in another connector.

While the exact number and variety of accessory cables needed are largely a matter of individual preference, the following types may be considered as basic to any well-designed general-purpose kit:

1. Recorder Cable—terminated in a connector to fit a standard tape or wire recorder. It is used to connect the amplifier to a recorder when it is necessary or desirable to obtain a permanent record of monitored conversations.
2. Extension Cable—terminated in a female cable jack like those on the amplifier. It is used to extend the "reach" of other accessories.
3. Special Clip Cable—terminated in alligator clips and short lengths of flexible wire, is an all-purpose cable. It is used for tapping lines or connecting a special pickup or output device to the amplifier.

Spare parts

In making up the electronic surveillance kit, it must be remembered that an agent or operative using the kit in the field may not have ready access to a stockroom. Everything needed to keep the kit in operating condition or to facilitate the installation of the various accessories must be included in the kit.


A spare-parts kit may be assembled in a small multicompartment plastic box and should include: a supply of light and dark wiring nails; small rolls of transparent and black Scotch tape; a small magnifying glass; spare A and B batteries; a small penlight or flashlight; an electrician's pocket knife; a neon line-voltage tester; a set of tubes for the

amplifier; and special-purpose adapters.

Where space permits and where the kit may be in the field for extended periods of time, a supply of hookup wire and shielded cable plus a small roll of rosin-core solder might be included with the spare parts.

Tool kit

Small hand tools are essential to the proper installation and use of many of the kit's components. An agent must be able to pry baseboards or moldings away from walls so he can hide microphone wires; reinstall moldings without leaving scratches or tell-tale marks; remove carpet and upholstery tacks to facilitate hiding a microphone or cable; cut small holes in walls or partitions for feeding a wire through or for use as a peephole; make minor repairs to the components in his kit and measure distances accurately in order to locate hidden wall compartments.

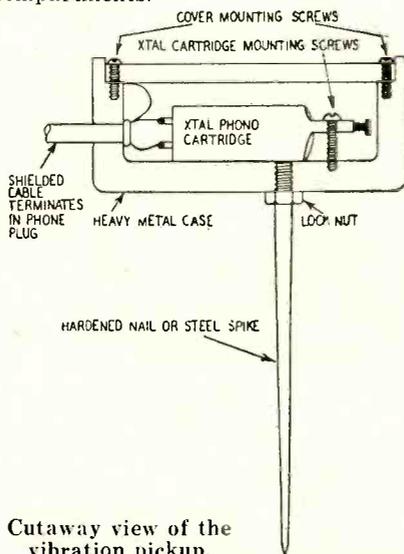

Cutaway view of the vibration pickup.

The following tools should be included as a minimum complement: small claw hammer; awl type drill saw; tape measure; small hacksaw; assortment of screwdrivers; a pair of long-nose pliers with a wire cutter or a separate diagonal cutter.

Optional tools, useful for some types of work but not absolutely essential, include a small soldering iron, a hand drill and assortment of bits, tweezers and a small set of wrenches.

Although not a functional part of the kit, the type of carrying case is extremely important. The case must be small, sturdy, lightweight and camouflage its contents.

A skate carrying case, with the various components held in place by small brackets and coil-spring straps, does a good job. A sturdy fiber case will serve as well; rubber, cloth or leather straps can be used to secure the components in position. Care should be taken in designing mounting brackets and straps—they must hold each item securely in position even when the kit is subjected to rough handling, and permit the ready removal and replacement of any component.

For camouflage purposes, many oper-

PARTS LIST (Vibration pickup)

Metal case (1)
Crystal or ceramic phono cartridge (1)
Hardened nail or steel spike (1)
Phone plug (1)
Shielded cable, 3 to 4 feet
Miscellaneous hardware

PARTS FOR OTHER ACCESSORIES

Phone pickup, Lafayette MS-16 (1)
Crystal cartridge, Argonne AR-56 (1)
Headphone, 2,000 ohm, magnetic, Telex 4626 (1)
Cord and phone plug, Telex 3280 (1)
High impedance earphone, Lafayette MS-276 (1)
Phone plugs (5)
Cable phone jack (1)
Shielded cable
Alligator clips (2)

SPARE PARTS KIT

Dark cable tacks (1 box)
Light cable tacks (1 box)
Transparent tape (1 roll)
Electrical tape (1 roll)
Flashlight (1)
Electrician's pocket knife (1)
Neon, line tester (1)
Magnifying glass (1)
Phone plug to coaxial cable adapter (1)
Spare B battery (1)
Spare A batteries (2)
Multicompartment plastic box (1)
Extra set of tubes CK512AX (2); CK525AX (1)

TOOL KIT

Screwdriver set, including flexible tape rule and long-nose pliers.
Small hammer
Drill saw
Carrying case—Aluminum skate box modified to hold electronic surveillance kit and accessories

atives prefer that the electronic surveillance kit be mounted in a small leather briefcase or a dispatch case. For maximum protection against accidental discovery, the entire kit might be concealed under a false bottom in an overnight bag or suitcase, or even hidden in concealed pockets in a large overcoat.

Space limitations prohibit a detailed discussion of all possible applications of the Surveillance Kit. In general, however, its function is to assist an agent in obtaining information and in detecting the use of technical espionage equipment such as planted radio transmitters.

The basic operational setup includes one of the pickup devices, the amplifier and an output device. For example, the rf pickup, amplifier and standard headset might be used for searching a room for a small hidden transmitter. In another instance, the vibration pickup, amplifier and standard headset might be used for opening a safe in a suspect's office or in listening for ticks in a package suspected of concealing a bomb.

Often, the recorder cable is used to connect the amplifier to a standard tape or wire recorder to make a permanent record. For example, the vibration pickup, amplifier, recorder cable and a recorder might be used to record a suspect's conversation through a wall or partition. In more favorable circumstances, the remote microphone (hidden in the suspect's room) could be used for the same purpose. The amplifier's gain, coupled with the normal gain of a good recorder, gives an amazing sensitivity.

While the use of many kit components may be obvious from their very nature, their value depends greatly on the skill of the individual agent. As he acquires experience in using the kit, he can develop tricks and special techniques of his own to obtain the most from each piece of equipment.

END

*Audio signal triggers camera
for fast action shots*

a PHOTO-SOUND unit

By PETER J. VOGELGESANG

FAST films and fast shutters are the tools of the modern action photographer; the technical achievements of the photographic industry have eliminated the problem of the long exposure. Remarkable action pictures are being made every day by photographers who use comparatively simple camera equipment and ordinary films. For example, a photographer at ring-side, using a press type camera and flash bulbs, can successfully stop the swiftest punch a fighter can throw. He can stop the punch, that is, if his own reflexes are quick enough to anticipate it and trip the shutter at the proper instant. A photographer could stop a baseball player in the middle of a home-run swing of the bat, too, if he were capable of deciding in a fraction of a second whether the batter was going to follow through. So, while the photographer has the equipment with which to take fast action pictures, he is still confronted with the problem of synchronizing that equipment with the action he wishes to photograph.

Because sound almost always accompanies action, it is an excellent synchronization medium. A camera shutter tripped by the crack of a bat is sure to photograph the batter at the peak of his swing. The same would be true of a golfer striking a golf ball or a football player kicking. Sports is by no means the only field in which a sound-synchronized camera can be used. Any photogenic, fast-action phenomenon that makes sound is a good subject. It might be cars colliding at a thrill show or the blasting of rock in a stone quarry. There is material for countless prize-winning photos everywhere, and a sound-triggered camera will guarantee good results every time.


The first step in building a sound-triggered camera is the construction of an electrically actuated shutter. Many press type cameras come equipped with solenoid-actuated shutters, and those persons fortunate enough to possess such cameras have much of the problem already solved. It is virtually impossible to describe the construction of a mechanism that would be adaptable to all types of cameras. Instead, a principle is described from which an

Panel view shows
the 4-inch speaker.

Rear view with triggering device.

actuating mechanism can be adapted to any particular make of camera.

The mechanism illustrated was constructed to fit a Rolleicord IV camera. The power required to trip the shutter is supplied by a 1-inch coil spring. The spring is stretched and the mechanism is cocked before each exposure. The shutter-triggering lever is held in the cocked position against the tension of the spring by the armature of a sensitive relay. A short pulse of electricity sent through the relay coil pulls the armature free of the triggering lever and releases it, thereby tripping the shutter and making the exposure. The action is almost instantaneous. The base of the mechanism is designed to be mounted by sandwiching it between the camera and tripod, eliminating the necessity of fastening anything to the camera. The device is very simple and can be adapted to almost any camera.

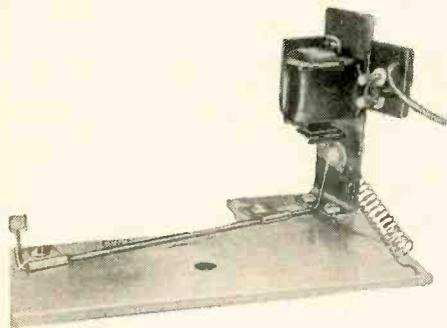


Closeup of camera-triggering device.

The electronic portion of the unit is equally simple. A 4-inch PM speaker is used as a microphone. The speaker feeds a two-stage audio amplifier through a voice-coil-to-grid transformer. The first tube of the amplifier is a pentode connected for maximum voltage gain; the second stage is triode-connected for lower output impedance. The sensitivity control is connected between the two stages.

The output of the amplifier is fed to the starter anode of an 0A4-G. This tube is normally nonconducting because the voltage from cathode to anode is insufficient to cause ionization. However, a comparatively low voltage applied to the starter anode will start ionization and cause the entire tube to conduct. The cathode of the 0A4 is returned to ground through the coil of the shutter-triggering device. Each time a sound hits the microphone, the amplified voltage fires the 0A4 which in turn trips the shutter of the camera.


Once the 0A4 is fired, it will continue to conduct until the plate voltage is removed. To eliminate the necessity of opening the plate circuit of the 0A4 after each exposure, the plate voltage is supplied to the tube through a 220,000-ohm resistor. This resistor charges the 10- μ f capacitor to the battery terminal voltage. However, when the 0A4 conducts, it discharges the 10- μ f capacitor in less than a second. The resistance of the plate resistor is such

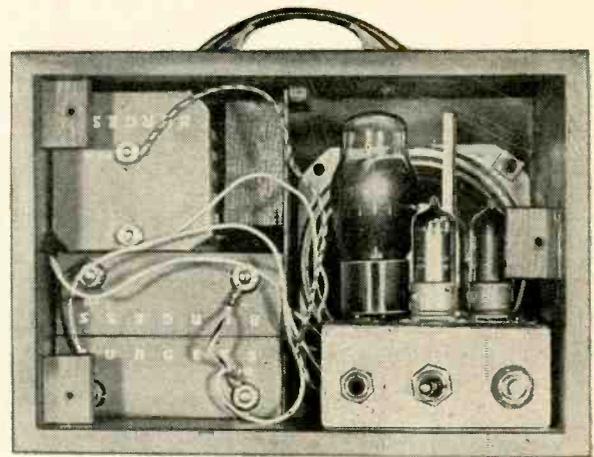Compact cabinet of photo-sound unit contains batteries and small chassis.



that it will not sustain tube conduction. The capacitor discharge current is more than sufficient to energize the coil of the triggering mechanism but, since the peak current of the 0A4 must be limited to 100 ma, the resistance of the coil on the triggering mechanism should not be less than 2,000 ohms.

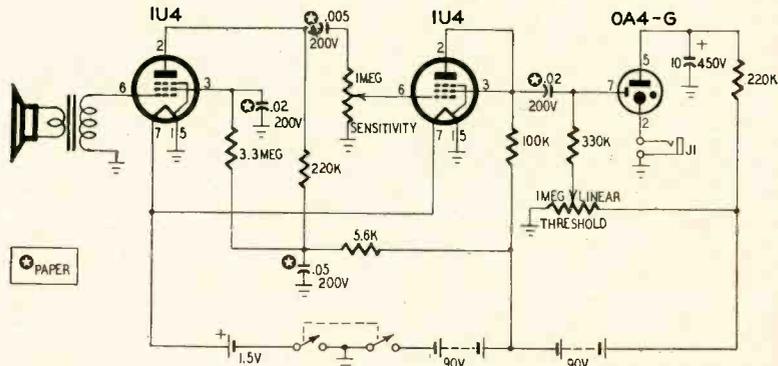is the case, a plate type relay may be installed in the cathode circuit of the tube and the normally open contacts used to energize the solenoid with the proper voltage. The contacts of the relay can be connected directly to the external receptacle of the flash gun unit.



Resistors: 1—5,600, 1—100,000, 2—220,000, 1—330,000 ohms; 1—3.3 megohms, 1/2 watt; 1—1-megohm pot, audio taper (sensitivity); 1—1-megohm pot, linear taper (threshold).

Miscellaneous: 1—.005, 2—.02, 1—.05 μ f, 200 volts, 1—10- μ f 450-volt electrolytic, capacitors; 1—1.5-volt A battery (Burgess 4FH or equivalent); 2—90-volt B batteries (Burgess N60 or equivalent); 1—phone jack; 1—dpst switch; 2—1U4's and sockets; 1—0A4-G and socket; 1—4-inch PM speaker; 1—transformer, voice coil to grid (Stancor A-4744 or equivalent); 1—chassis and cabinet; 1—triggering device.

Schematic diagram of photo-sound unit showing the external jack circuit.

The starter anode of the 0A4 must be operated with positive dc bias obtained from the threshold potentiometer. This potentiometer is adjusted just below the point where the 0A4 will fire without additional voltage from the amplifier.

Most commercial shutter solenoids have too low a resistance to be used in the cathode circuit of the 0A4. If such


The unit is constructed on a small sheet-metal chassis and installed in a wooden box with batteries. The sensitivity control, power switch and jack are accessible through an opening in the back of the box. The threshold control is left as an internal adjustment. The unit is extremely sensitive. A low whistle will trigger it at a distance of 15 or 20 feet. END

Everybody benefits
when everybody gives
the **UNITED** way



everybody's
doing it!

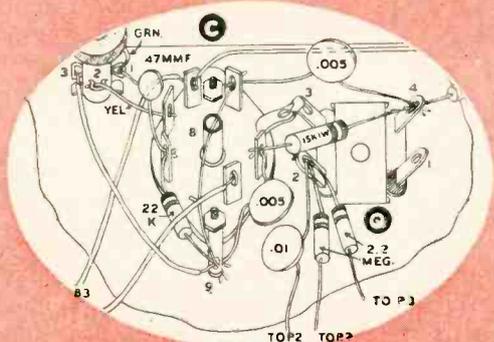Motion picture and TV personality, Jackie Coogan, looks on with unbelieving interest as his 14-year-old son, Anthony, prepares to assemble his latest Heathkit, a hi-fi FM tuner. The Coogans have found out about the fun and savings of building their own electronic equipment the Heathkit way . . . so why don't you?



You'll get plenty of these detailed pictorial diagrams in your Heathkit construction manual to show where each and every wire and part is to be placed. Everything you do is spelled out in pictures so you can't go wrong. That's what makes it such fun!

Heathkits[®]

By DAYSTROM

...fun to build
and a thrill to own!

and here's why...

1. You get higher quality at lower cost by dealing direct, and by doing your own assembly.
2. You receive personal, friendly, service (before and after sale) for complete satisfaction.
3. You benefit from the latest in engineering designs because of our concentration on kit-form equipment only.
4. You may depend on performance as advertised—backed by Heath's world-wide reputation for quality.
5. You can take a full year to pay with the HEATH EASY TIME PAYMENT PLAN.

- (✓) Connect a 22 KΩ resistor (red-red-orange) from socket C1 (NS) to ground lug C9 (NS). See Figure 8.
- (✓) Connect a .005 μfd disc capacitor from socket C4 (NS) to IF transformer Q4 (NS).
- () Bend socket lug C5 and IF transformer lug Q3 toward each other until they make contact and overlap slightly. Solder the connection securely. (1).
- () Install a .005 μfd capacitor from socket C5 (NS) to ground lug C9 (NS). Dress the capacitor close to chassis, under the capacitor previously installed.

Read the step . . . perform the operation . . . and check it off—it's just that simple. These plain-worded, easy-to-follow, steps are combined with pictorial diagrams to take you through every phase of assembly. Let our experience be your teacher!

TIME PAYMENTS . . .

The Heath Time Payment Plan was designed for your convenience. Now, you can order the kits of your choice, and pay for them in small monthly installments. Write for full details.

HEATHKIT EXTRA PERFORMANCE 70-WATT AMPLIFIER KIT

For really high performance, with plenty of reserve power, the W-6M is a natural. The full 70-watts output will seldom, if ever, be required. However, this reserve insures distortion-less sound on power peaks. The W-6M will loaf along at normal listening levels and yet is always ready to extend itself when program material demands it, without the least amount of strain. The output circuit employs 6550 tubes with a special-design Peerless output transformer for maximum stability at all power levels. A quick-change plug selects 4, 8 and 16 ohms or 70-volt output and the correct feedback resistance. A variable damping control is also provided for optimum performance with any speaker system. Extremely good power supply regulation is possible through the use of a heavy-duty transformer along with silicon-diode rectifiers, which are noted for their very long life, and yet are smaller than a house fuse. Frequency response at 1 watt is ± 1 db from 5 cps to 80 kc with controlled hf rolloff above 100 kc. At 70 watts output harmonic distortion is below 2%, 20 to 20,000 cps and IM distortion below 1%, 60 and 6,000 cps. Hum and noise 88 db below full output. In addition to high performance, its fine appearance makes it a pleasure to display in your living room. Proper layout of chassis insures ease of assembly by eliminating those cramped and difficult places to get at. Clear instructions—and top-quality components. Get started now and make this amplifier the heart of your hi-fi system. Shipped express only. Shpg. Wt. 50 lbs.

MODEL W-6: Consists of W-6M kit, plus WA-P2 preamplifier. Express only. Shpg. Wt. 59 lbs. \$129.70

MODEL W-6M

\$109⁹⁵

HEATHKIT HIGH FIDELITY FM TUNER KIT

This tuner can bring you a rich store of FM programming, your least expensive source of high fidelity material. It covers the complete FM band from 88 to 108 mc. Stabilized, temperature-compensated oscillator assures negligible drift after initial warmup. Features broadbanded circuits for full fidelity, and better than 10 uv sensitivity for 20 db of quieting, to pull in stations with clarity and full volume. Employs a high gain, cascode RF amplifier, and has AGC. A ratio detector provides high-efficiency demodulation without sacrificing hi-fi performance. IF and ratio transformers are prealigned, as is the front end tuning unit. Special alignment equipment is not necessary. Edge-lighted glass dial for easy tuning. Here is FM for your home at a price you can afford. Shpg. Wt. 8 lbs.

MODEL FM-3A

\$25⁹⁵

(with cabinet)

HEATHKIT BROADBAND AM TUNER KIT

This AM tuner was designed especially for high fidelity applications. It incorporates a special detector using crystal diodes, and the IF circuits feature broad band-width, to insure low signal distortion. Audio response is ± 1 db from 20 cps to 9 kc, with 5 db of preemphasis at 10 kc to compensate for station rolloff. Sensitivity and selectivity are excellent, and tuner covers complete broadcast band from

550 to 1600 kc. Quiet performance is assured by 6 db signal-to-noise ratio at 2.5 UV. Prealigned RF and IF coils eliminate the need for special alignment equipment. Incorporates AVC, two outputs, two antenna inputs, and built-in power supply. Edge-lighted glass slide-rule dial for easy tuning. Your "best buy" in an AM tuner. Shpg. Wt. 8 lbs.

MODEL BC-1A

\$25⁹⁵

(with cabinet)

HEATHKIT MASTER CONTROL PREAMPLIFIER KIT


Designed for use with any of the Williamson-type amplifiers, the WA-P2 has five switch-selected inputs, each having its own level control to eliminate blasting or fading while switching through the various inputs, plus a tape recorder output. A hum control allows setting for minimum hum level. Frequency response is within $\pm 1\frac{1}{2}$ db from 15 to 35,000 cps. Equalization provided for LP, RIAA, AES, and early 78's. Separate bass and treble controls. Low impedance cathode follower output circuit. All components were specially selected for their high quality. Includes many features which will eventually be desired. Shpg. Wt. 7 lbs.

MODEL WA-P2

\$19⁷⁵

(with cabinet)

*An amplifier
you will be
proud to own*

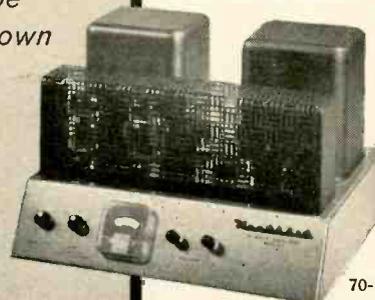

**70-WATT
AMPLIFIER**



AM-TUNER

FM-TUNER

*Selects and
controls sound
to your taste*



PREAMPLIFIER

HEATH COMPANY A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICH.**


OCTOBER, 1957

67




ADVANCED-DESIGN
25-WATT AMPLIFIER

*Top performance
in its
power class!*

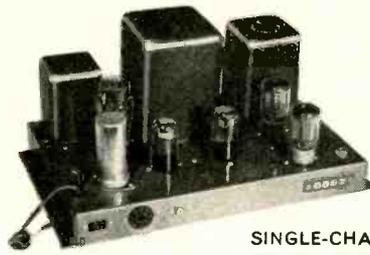

SINGLE-CHASSIS
20-WATT AMPLIFIER

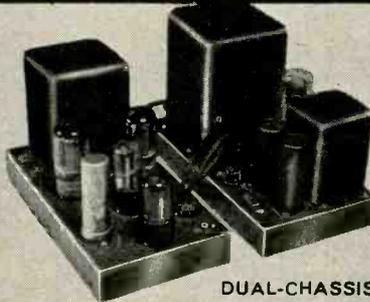*Hi-Fi equipment
for your listening
pleasure!*



DUAL-CHASSIS
20-WATT AMPLIFIER



GENERAL-PURPOSE
20-WATT AMPLIFIER

HEATHKIT ADVANCED-DESIGN 25-WATT HIGH FIDELITY AMPLIFIER KIT

Designed especially to satisfy critical audio requirements, the W-5M incorporates the extra features needed to complement the finest in program sources and speaker systems. Faithful sound reproduction is assured with a frequency response of ± 1 db from 5 to 160,000 cps at 1 watt, and harmonic distortion is less than 1% at 25 watts, with IM distortion less than 1% at 20 watts. Hum and noise are a full 99 db below rated output, assuring quiet, hum-free operation. Output taps are 4, 8 and 16 ohms. Exclusive Heathkit features include the "tweeter saver", and the "bas-bal" balancing circuit, requiring only a voltmeter for indication. Years of reliable service are guaranteed through the use of conservatively rated, high quality components. KT66 tubes and Peerless output transformer are typical. Shipped express only. Shpg. Wt. 31 lbs.

MODEL W-5: Consists of W-5M kit above plus model WA-P2 preamplifier. Express only. Shpg. Wt. 38 lbs. \$79.50

MODEL W-5M
\$59⁷⁵

HEATHKIT DUAL-CHASSIS 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model W3-AM is a Williamson-type amplifier built on two separate chassis. The power supply is on one chassis, and the amplifier stages are on the other chassis. Using two separate chassis provides additional flexibility in installation. Features include the famous acrosound model TO-300 "ultralinear" output transformer and 5881 tubes for broad frequency response, low distortion, and low hum level. The result is exceptionally fine overall tone quality. Frequency response is ± 1 db from 6 cps to 150 kc at 1 watt. Harmonic distortion is less than 1% and IM distortion is less than 1.3% at 20 watts. Hum and noise are 88 db below 20 watts. Designed to match the speaker system of your choice, with taps for 4, 8 or 16 ohms impedance. A very popular high fidelity unit employing top quality components throughout. Shipped express only. Shpg. Wt. 29 lbs.

MODEL W-3A: Consists of W-3AM kit above plus model WA-P2 preamplifier. Express only. Shpg. Wt. 37 lbs. \$69.50

MODEL W-3AM
\$49⁷⁵

HEATHKIT SINGLE-CHASSIS 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model W4-AM Williamson-type amplifier will amaze you with its outstanding performance. A true Williamson circuit, featuring extended frequency response, low distortion, and low hum levels, this amplifier can provide you with many hours of listening enjoyment with only a minimum investment compared to other units on the market. 5881 tubes and a special Chicago-standard output transformer are employed to give you full fidelity at minimum cost. Frequency response extending from 10 cps to 100 kc within ± 1 db at 1 watt assures you of full coverage of the audio range, and clean clear sound amplification takes place in circuits that hold harmonic distortion at 1.5% and IM distortion below 2.7% at full 20 watt output. Hum and noise are 95 db below full output. Taps on the output transformer are at 4, 8 or 16 ohms. Shipped express only. Shpg. Wt. 28 lbs.

MODEL W-4A: Consists of W-4AM kit above, plus model WA-P2 preamplifier. Express only. Shpg. Wt. 35 lbs. \$59.50.

MODEL W-4-AM
\$39⁷⁵

Heathkits...

BY DAYSTROM

*bring you the lasting satisfaction
of personal accomplishment*

HEATHKIT GENERAL-PURPOSE 20-WATT HIGH FIDELITY AMPLIFIER KIT

The model A-9C will provide you with high quality sound at low cost. Features a built-in preamplifier with four separate inputs, and individual volume, bass and treble controls. Frequency response covers 20 to 20,000 cps within ± 1 db. Total harmonic distortion is less than 1% at 3 db below rated output. Push-pull 6L6 tubes are used, with output transformer tapped at 4, 8, 16 and 500 ohms. A true hi-fi unit using high-quality components throughout, including heavy-duty "potted" transformers.

Shpg. Wt. 23 lbs.

MODEL A-9C
\$35⁵⁰

**HEATHKIT "BASIC RANGE"
HI-FI SPEAKER SYSTEM KIT**

The extremely popular Heathkit model SS-1 Speaker System provides amazing high fidelity performance for its size. Features two high-quality Jensen speakers, an 8" mid-range woofer and compression-type tweeter with flared horn. Covers from 50 to 12,000 CPS within ± 5 db, in a special-design ducted-port, bass reflex enclosure. Impedance is 16 ohms. Cabinet measures 11½" H x 23" W x 11¼" D. Constructed of veneer-surfaced plywood, ½" thick, suitable for light or dark finish. All wood parts are pre-cut and pre-drilled for easy, quick assembly. Shpg. Wt. 30 lbs.

MODEL SS-1
\$39⁹⁵

**HEATHKIT "RANGE EXTENDING"
HI-FI SPEAKER SYSTEM KIT**

Extends the range of the SS-1 to ± 5 db from 35 to 16,000 CPS. Uses 15" woofer and super-tweeter both by Jensen. Kit includes crossover circuit. Impedance is 16 ohms and power rating is 35 watts. Measures 29" H x 23" W x 17½" D. Constructed of veneer-surfaced plywood ¾" thick. Easy to build! Shpg. Wt. 80 lbs.

MODEL SS-1B
\$99⁹⁵

**HEATHKIT "LEGATO"
HIGH FIDELITY SPEAKER SYSTEM KIT**

The quality of the Legato, in terms of the engineering that went into the initial design, and in terms of the materials used in its construction, is matched in only the most expensive speaker systems available today. The listening experience it provides approaches the ultimate in esthetic satisfaction. Two 15" theater-type Altec Lansing speakers cover 25 to 500 CPS, and an Altec Lansing high-frequency driver with sectoral horn covers 500 to 20,000 CPS. A precise amount of phase shift in the crossover network brings the high frequency channel into phase with the low frequency channel to eliminate peaks or valleys at the crossover point, by equalizing the acoustical centers of the speakers. The enclosure is a modified infinite baffle type, especially designed for these speakers. Cabinet is constructed of veneer-surfaced plywood, ¾" thick, pre-cut and pre-drilled for easy assembly. Frequency response 25 to 20,000 CPS. Power rating, 50 watts program material. Impedance is 16 ohms. Cabinet dimensions 41" L x 22¼" D x 34" H.

Choice of two beautiful cabinets. Model HH-1-C in imported white birch for light finishes, and HH-1-CM in African mahogany for dark finishes. Shpg. Wt. 195 lbs.

MODEL HH-1-C
MODEL HH-1-CM
\$325⁰⁰
EACH

Heathkits...

By DAYSTROM

*let you save up to ½
or more on all types
of electronic equipment.*

HEATHKIT SINE-SQUARE GENERATOR


The new AG-10 provides high quality, sine and square waves over a wide range, for countless applications. Some of these are; radio and TV repair work, checking scope performance, as a variable trigger source for telemetering and pulse work, and checking audio, video and hi-fi amplifier response. Frequency response is ± 1.5 db from 20 CPS to 1 MC on both sine and square waves, with less than .25% sine wave distortion, 20 to 20,000 CPS. Sine wave output impedance 600 ohms, square wave output impedance 50 ohms, (except on 10v ranges). Square wave rise time less than .15 usec. Five-position band switch—continuously variable tuning—shielded oscillator circuit—separate step and variable output attenuators in ranges of 10, 1, and .1 volts for both sine and square wave, with extra range of .01 volt on sine wave. Both sine and square wave can be used at the same time without affecting either wave form. Power supply uses silicon-diode rectifiers. Shpg. Wt. 12 lbs.

MODEL AG-10
\$49⁹⁵

HEATHKIT AUDIO ANALYZER KIT

The AA-1 is actually three instruments in one compact package. It combines the functions of an AC VTVM, an audio wattmeter, and an intermodulation analyzer. Input and output terminals are combined, and high and low frequency oscillators are built in. VTVM ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts (RMS). Wattmeter ranges are .15 mw, 1.5 mw, 15 mw, 150 mw, 1.5 w, 15 w and 150 w. IM scales are 1%, 3%, 10%, 30% and 100%. Provides internal load resistors of 4, 8, 16 or 600 ohms. A tremendous dollar value. Shpg. Wt. 13 lbs.

MODEL AA-1
\$49⁹⁵

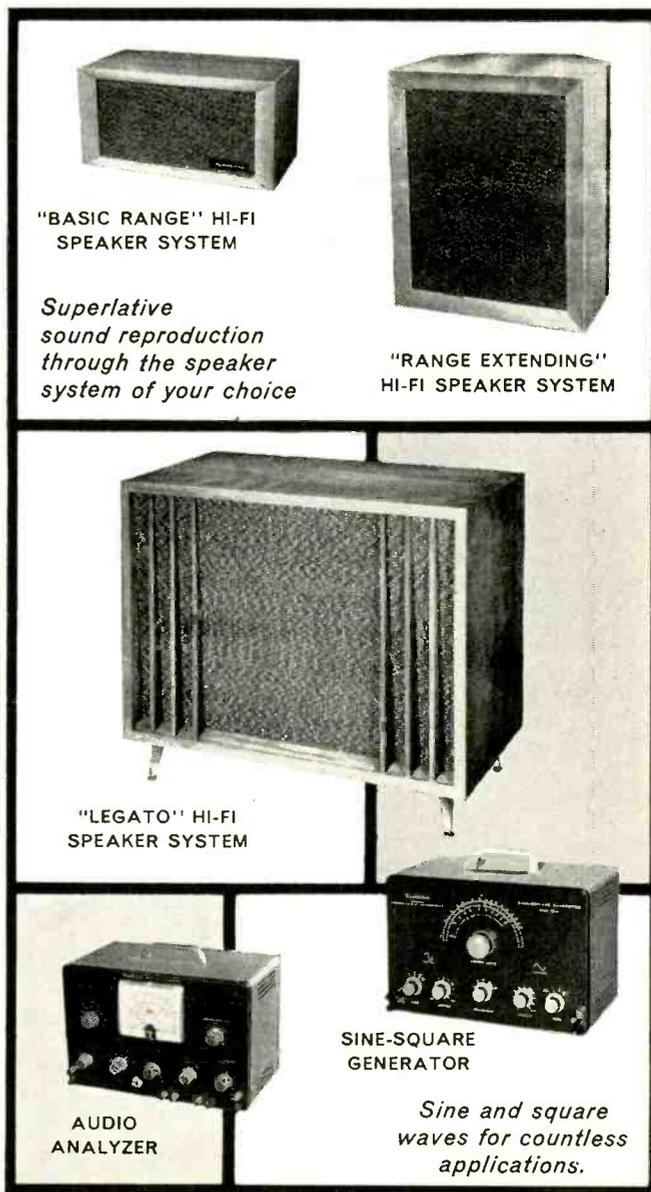

"BASIC RANGE" HI-FI
SPEAKER SYSTEM

*Superlative
sound reproduction
through the speaker
system of your choice*

"RANGE EXTENDING"
HI-FI SPEAKER SYSTEM

"LEGATO" HI-FI
SPEAKER SYSTEM

AUDIO
ANALYZER


SINE-SQUARE
GENERATOR

*Sine and square
waves for countless
applications.*



Audio equipment for your hi-fi testing

GENERAL PURPOSE" SCOPE

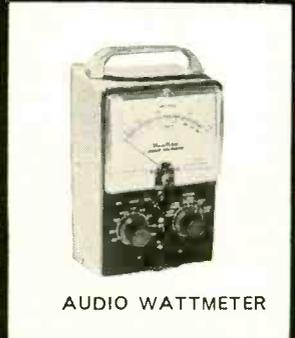


AUDIO WATTMETER



AUDIO GENERATOR



HARMONIC DISTORTION METER

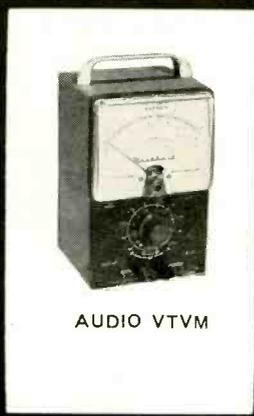

AUDIO VTVM

HEATHKIT "GENERAL PURPOSE" 5" OSCILLOSCOPE KIT

The model OM-2 Oscilloscope is especially popular with part-time service technicians, students, and high fidelity enthusiasts. It features good vertical frequency response ± 3 db from 4 cps to over 1.2 mc. A full five-inch crt, and sweep generator operation from 20 cps to over 150 kc. Stability is excellent and calibrated grid screen allows precise signal observation. Extra features include external or internal sweep and sync, 1-volt peak-to-peak calibrating reference, 3-position step-attenuated input, adjustable spot shape control, push-pull horizontal and vertical amplifiers, and modern etched-metal circuits. Easy to build and a pleasure to use. Ideal for use with other audio equipment for checking amplifiers. Shpg. Wt. 21 lbs.

MODEL OM-2

\$42⁵⁰

HEATHKIT AUDIO WATTMETER KIT

The AW-1 Audio Wattmeter can be used in any application where audio power output is to be measured. Non-inductive LOAD resistors are built in for 4, 8, 16 or 600 ohms impedance. Five power ranges cover 0.5 mw, 50 mw, 500 mw, 5 w, and 50 w full scale. Five switch-selected db ranges cover -10 db to +30 db. All indications are read directly on a large 4 1/2" 200 microampere meter. Frequency response is

± 1 db from 10 cps to 250 kc. Precision type multiplier resistors used for high accuracy, and crystal diode bridge for wide-range frequency response. This meter is used in many recording studios and broadcast stations as a monitor as well as servicing. A fine meter to help supply the answers to your audio operating or power output problems. Shpg. Wt. 6 lbs.

MODEL AW-1

\$29⁵⁰

HEATHKIT AUDIO SIGNAL GENERATOR KIT

The model AG-9A is "made to order" for high fidelity applications, and provides quick and accurate selection of low-distortion signals throughout the audio range. Three rotary switches select two significant figures and a multiplier to determine audio frequency. Incorporates step-type and a continuously variable output attenuator. Output indicated on large 4 1/2" panel meter, calibrated in volts and db. Attenuator system operates in 10 db steps, corresponding to meter calibration, in ranges of 0-.003, .01, .03, .1, .3, 1, 3 and 10 volts RMS. "Load" switch permits use of built-in 600-ohm load, or external load of different impedance. Output and frequency indicators accurate to within $\pm 5\%$. Distortion less than .1 of 1% between 20 and 20,000 cps. Total range is 10 cps to 100 kc. Shpg. Wt. 8 lbs.

MODEL AG-9A

\$34⁵⁰

HEATHKIT HARMONIC DISTORTION METER KIT

All sounds consist of dominant tones plus harmonics (over-tones). These harmonics enrich the quality and brightness of the music. However, additional harmonics which originate in the audio equipment, represent distortion. Used with an audio signal generator, the HD-1 will accurately measure this harmonic distortion at any or all frequencies between 20 and 20,000 cps. Distortion is read directly on the panel meter in ranges of 0-1, 3, 10, 30 and 100% full scale. Voltage ranges of 0-1, 3, 10 and 30 volts are provided for the initial reference settings. Signal-to-noise ratio measurements are also permitted through the use of a separate meter scale calibrated in db. High quality components insure years of outstanding performance. Full instructions are provided. Shpg. Wt. 13 lbs.

MODEL HD-1

\$49⁵⁰

Heathkits...

By DAYSTROM

are well known for their high quality and reliability.

HEATHKIT AUDIO VTVM KIT

This new and improved AC Vacuum Tube Voltmeter is designed especially for audio measurements and low-level AC measurements in power supply filters, etc. Employs an entirely new circuit featuring a cascode amplifier with cathode-follower isolation between the input and the amplifier, and between the output stage and the preceding stages. It emphasizes stability, broad frequency response, and sensitivity. Frequency response is essentially flat from 10 cps to 200 kc. Input impedance is 1 megohm at 1000 cps. AC (RMS) voltage ranges are 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts. Db ranges cover -52 db to +52 db. Features large 4 1/2" 200 microampere meter, with increased damping in meter circuit for stability in low frequency tests. 1% precision resistors employed for maximum accuracy. Stable, reliable performance in all applications. Shpg. Wt. 5 lbs.

MODEL AV-3

\$29⁹⁵

HEATHKIT COLOR BAR AND DOT GENERATOR

The CD-1 combines the two basic color service instruments, a Color Bar Generator and White Dot Generator in one versatile portable unit, which has crystal-controlled accuracy and stability (no external sync lead required). Produces white-dots, cross hatch, horizontal and vertical bars, 10 vertical color bars, and a new shading bar pattern for screen and background adjustments. Variable RF output on any channel from 2 to 6. Positive or negative video output, variable from 0 to 10 volts peak-to-peak. Crystal controlled sound carrier with off-on switch. Voltage regulated power supply using long-life silicon rectifiers. Gain knowledge of a new and profitable field by constructing this kit. Shpg. Wt. 12 lbs.

MODEL CD-1

\$59⁹⁵

HEATHKIT "EXTRA DUTY" 5" OSCILLOSCOPE KIT

This fine oscilloscope compares favorably to other scopes costing twice its price. It contains the extra performance so necessary for monochrome and color-TV servicing. Features push-pull horizontal and vertical output amplifiers, a 5UPI CRT, built in peak-to-peak calibration source, a fully compensated 3-position step-type input attenuator, retrace blanking, phasing control, and provision for Z-axis modulation. Vertical amplifier frequency response is within +1.5 and -5 db from 3 CPS to 5 MC. Response at 3.58 MC down only 2.2 db. Sensitivity is 0.025 volts RMS/inch at 1 kc. Sweep generator covers 20 CPS to 500 kc in five steps, five times the usual sweep obtained in other scopes through the use of the patented Heath sweep circuit. Etched-metal circuit boards reduce assembly time and minimize errors in assembly, and more importantly, permit a level of circuit stability never before achieved in an oscilloscope of this type. Shpg. Wt. 21 lbs.

MODEL O-11

\$69⁵⁰

Heathkits...

By DAYSTROM

are guaranteed to meet or exceed advertised specifications

HEATHKIT ELECTRONIC SWITCH KIT

A valuable accessory for any oscilloscope owner. It allows simultaneous oscilloscope observation of two signals by producing both signals, alternately, at its output. Four switching rates. Provides gain for input signals. Frequency response ± 1 db, 0 to 100 kc. A sync output is provided to control and stabilize scope sweep. Ideal for observing input and output of amplifiers simultaneously. Shpg. Wt. 8 lbs.

MODEL S-3

\$21⁹⁵

HEATHKIT TV ALIGNMENT GENERATOR KIT

This fine TV alignment generator offers stability and flexibility difficult to obtain even in instruments costing several times this low Heathkit price. It covers 3.6 mc to 220 mc in four bands. Sweep deviation is controllable from 0 to 42 mc. The all-electronic sweep circuit insures stability. Crystal marker and variable marker oscillators are built in. Crystal (included with kit) provides output at 4.5 mc and multiples thereof. Variable marker provides output from 19 to 60 mc on fundamentals and from 57 to 180 mc on harmonics. Effective two-way blanking to eliminate return trace. Phasing control. Kit is complete, including three output cables. Shpg. Wt. 16 lbs.

MODEL TS-4A

\$49⁵⁰

HEATHKIT VOLTAGE CALIBRATOR KIT

This unit is an excellent companion for your oscilloscope. Used as a source of calibrating voltage, it produces near-perfect square wave signals of known amplitude. Precision 1% attenuator resistors insure accurate output amplitude, and multivibrator circuit guarantees good sharp square waves. Output frequency is approximately 1000 CPS. Fixed outputs selected by panel switches are; .03, 0.1, 0.3, 1.0, 3.0, 10, 30 and 100 volts peak-to-peak. Allows measurement of unknown signal amplitude by comparing it to the known output of the VC-3 on oscilloscope. Shpg. Wt. 4 lbs.

MODEL VC-3

\$12⁵⁰

Functional styling with clean uncluttered look



COLOR BAR AND DOT GENERATOR



"EXTRA DUTY" SCOPE



TV ALIGNMENT GENERATOR



ELECTRONIC SWITCH



VOLTAGE CALIBRATOR

HEATHKIT TUBE CHECKER KIT

Eliminate guesswork, and save time in servicing or experimenting. The TC-2 tests tubes for shorted elements, open elements, filament continuity, and operating quality on the basis of total emission. It tests all tube types encountered in radio and TV service work. Sockets are provided for 4, 5, 6 and 7-pin, octal, and loctal tubes, 7 and 9 pin miniature tubes, 5 pin hytron miniatures, and pilot lamps. Tube condition indicated on 4½" meter with multi-color "good-bad" scale. Illuminated roll chart with all test data built in. Switch selection of 14 different filament voltages from .75 to 117 volts. Color-coded cable harness allows neat professional wiring and simplifies construction. Very easy to build, even for a beginner. Shpg. Wt. 12 lbs.

MODEL TC-2
\$29.50

HEATHKIT HANDITESTER KIT

The small size and rugged construction of this tester makes it perfect for any portable application. The combination function-range switch simplifies operations. Measures AC or DC voltage at 0-10, 30, 300, 1000 and 5000 volts. Direct current ranges are 0-10 ma and 0-100 ma. Ohmmeter ranges are 0-3000 (30 ohm center scale) and 0-300,000 (3000 ohm center scale). Very popular with home experimenters, electricians, and appliance repairmen. Slips easily into your tool box, glove compartment, coat pocket, or desk drawer. Shpg. Wt. 3 lbs.

MODEL M-1
\$14.50

HEATHKIT PICTURE TUBE CHECKER KIT

The CC-1 can be taken with you on service calls so that you can clearly demonstrate the quality of a customer's picture tube in his own home. Tubes can be tested without removing them from the receiver or cartons if desired. Checks cathode emission, beam current, shorted elements, and leakage between elements in electromagnetic picture tube types. Self-contained power supply, and large 4½" meter. CRT condition indicated on "good-bad" scale. Relative condition of tubes fluorescent coating is shown in "shadow-graph" test. Permanent test cable with CRT socket and anode connector. No tubes to burn out, designed to last a lifetime. Luggage-type portable case. Shpg. Wt. 10 lbs.

MODEL CC-1
\$22.50

HEATHKIT ETCHED-CIRCUIT VTVM KIT

This multi-purpose VTVM is the world's largest selling instrument of its type—and is especially popular in laboratories, service shops, home workshops and schools. It employs a large 4½" panel meter, precision 1% resistors, etched metal circuit board, and many other "extras" to insure top quality and top performance. It's easy to build, and you may rely on its accuracy and dependability. The V7-A will measure AC (RMS) and DC voltages in ranges of 0-1.5, 5, 15, 50, 150, 500 and 1500. It measures peak-to-peak AC voltage in ranges of 0-4, 14, 40, 140, 400, 1400 and 4000. Resistance ranges provide multiplying factors of X 1, X 10, X 100, X 1000, X 10k, X 100k, and X 1 megohm. Center-scale resistance readings are 10, 100, 1000, 10k, 100k, 1 megohm and 10 megohms. A db scale is also provided. The precision and quality of this VTVM cannot be duplicated at this price. Shpg. Wt. 7-lbs.

MODEL V7-A
\$24.50

Heathkits...

By DAYSTROM

*let you fill your exact needs
from a wide variety
of instruments*

HEATHKIT 20,000 OHMS/VOLT VOM KIT

This fine instrument provides a total of 25 meter ranges on its two-color scale. It employs a 50 ua 4½" meter, and features 1% precision multiplier resistors. Requires no external power. Ideal for portable applications. Sensitivity is 20,000 ohms-per-volt DC and 5000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5000 volts, AC and DC. Measures direct current in ranges of 0-150 ua, 15 ma, 150 ma, 500 ma and 15 a. Resistance multipliers are X 1, X 100 and X 10,000, with center-scale readings of 15, 1500 and 150,000 ohms. Covers -10 db to +65 db. Easy to build and fun to use. Attractive bakelite case with plastic carrying handle. Shpg. Wt. 6 lbs.

MODEL MM-1
\$29.50

TUBE CHECKER

High quality test gear you will be proud to own

ETCHED CIRCUIT VTVM

Priced low to fit your budget

HANDITESTER

PICTURE TUBE CHECKER

20,000 OHMS/VOLT VOM

HEATHKIT RF SIGNAL GENERATOR KIT

Even a beginner can build this prealigned signal generator, designed especially for use in service work. Produces RF signals from 160 kc to 110 mc on fundamentals in five bands. Covers 110 mc to 220 mc on calibrated harmonics. Low impedance RF output in excess of 100,000 microvolts, is controllable with a step-type and continuously variable attenuator. Selection of unmodulated RF, modulated RF, or audio at 400 CPS. Ideal for fast and easy alignment of radio receivers, and finds application in FM and TV work as well. Thousands of these units are in use in service shops all over the country. Easy to build and a real time saver, even for the part-time service technician or hobbyist. Shpg. Wt. 8 lbs.

MODEL SG-8

\$19⁵⁰

HEATHKIT LABORATORY RF GENERATOR KIT

Tackle all kinds of laboratory alignment jobs with confidence by employing the LG-1. It features voltage-regulated B+, double shielding of oscillator circuits, copper-plated chassis, variable modulation level, metered output, and many other "extras" for critical alignment work. Generates RF signals from 100 kc to 30 mc on fundamentals in five bands. Meter reads RF output in microvolts or modulation level in percentage. RF output available up to 100,000 microvolts, controlled by a fixed-step and a variable attenuator. Provision for external modulation where necessary. Buy and use this high-quality RF signal generator that may be depended upon for stability and accuracy. Shpg. Wt. 16 lbs.

MODEL LG-1

\$48⁹⁵

HEATHKIT DIRECT-READING CAPACITY METER KIT

Here's a fast, simple capacity meter. A capacitor to be checked is merely connected to the terminals, the proper range selected, and the value read directly on the large 4½" panel meter calibrated in mmf and mfd. Ranges are 0 to 100 mmf, 1,000 mmf, .01 mfd, .1 mfd full scale. Not affected by hand capacity. Shpg. Wt. 7 lbs.

MODEL CM-1

\$29⁵⁰

Heathkits...

By DAYSTROM


*are educational
as well as functional*

HEATHKIT "IN-CIRCUIT" CAPACI-TESTER KIT

With the CT-1 it is no longer necessary to disconnect one capacitor lead to check the part, you can check most capacitors for "open" or "short" right in the circuit. Fast and easy—to save your valuable time in the service shop or lab. Detects open capacitors from about 50 mmf up, so long as the capacitor is not shunted by excessively low resistance value. Will detect shorted capacitors up to 20 mfd (not shunted by less than 10 ohms). (Does not detect leakage.) Employs 60 cycles and 19 megacycle test frequencies. Electron beam "eye" tube used as indicator. Compact, easy-to-build, and inexpensive. Test leads included. Shpg. Wt. 5 lbs.

MODEL CT-1

\$7⁹⁵

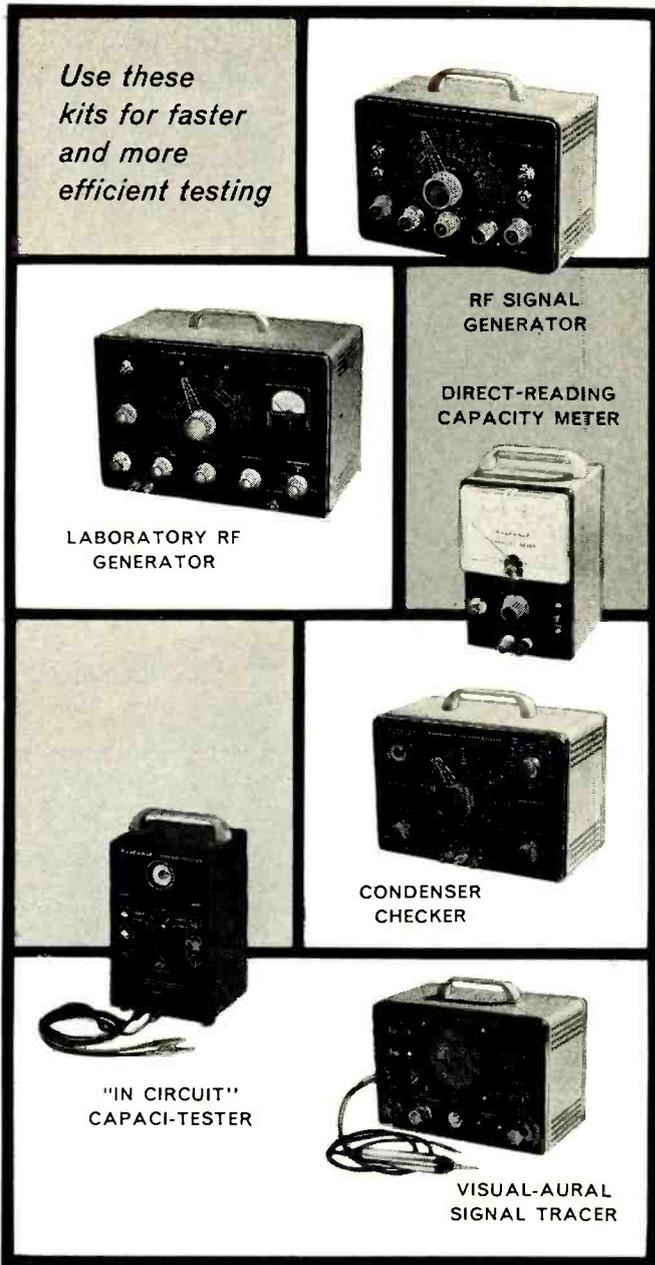

HEATHKIT CONDENSER CHECKER KIT

This handy instrument uses an electron beam "eye" tube as an indicator to measure capacity in ranges of .00001 to .005 mfd, .5 mfd, 50 mfd and 1000 mfd. Also measures resistance from 100 ohms to 5 megohms in two ranges. Checks paper, mica, ceramic and electrolytic capacitors. Selection of five polarizing voltages. Shpg. Wt. 7 lbs.

MODEL C-3

\$19⁵⁰

HEATHKIT VISUAL-AURAL SIGNAL TRACER KIT

Although designed originally for radio receiver work, the T-3 finds application in FM and TV servicing as well. Features high-gain channel with demodulator probe, and low-gain channel with audio probe. Traces signals in all sections of radio receivers and in many sections of FM and TV receivers. Built-in speaker and electron beam eye tube indicate relative gain, etc. Also features built-in noise locator circuit. Provision for patching speaker and/or output transformer to external set. Shpg. Wt. 9 lbs.

MODEL T-3

\$23⁵⁰

HEATHKIT IMPEDANCE BRIDGE KIT

The model IB-2A employs a Wheatstone Bridge, a Capacity Comparison Bridge, a Maxwell Bridge, and a Hay Bridge in one compact package. Measures resistance from 0.1 ohm to 10 megohms, capacitance from 100 mmf to 100 mfd, inductance from 0.1 mh to 100 h, dissipation factor (D) from 0.002 to 1, and storage factor (Q) from 0.1 to 1000. A 100-0-100 ua meter provides for null indications. The decade resistors employed are of 1% tolerance for maximum accuracy. Completely self-contained. Has built in power supply, 1000-cycle generator, and vacuum-tube detector. Special two-section CRL dial insures convenient operation. Instruction manual has entirely new schematic that clarifies circuit functions in various switch positions. A true laboratory instrument, that will provide you with many years of fine performance. Shpg. Wt. 12 lbs.

MODEL IB-2A
\$59.50

HEATHKIT "LOW RIPPLE" BATTERY ELIMINATOR KIT

This modern battery eliminator incorporates an extra low-ripple filter circuit so that it can be used to power all the newest transistor-type circuits requiring 0 to 12 volts DC,


and the new "hybrid" automobile radios using both transistors and vacuum tubes. Its DC output, at either 6 or 12 volts, contains less than .3% AC ripple. Separate output terminals are provided for low-ripple or normal filtering. Supplies up to 15 amps on 6 volt range or up to 7 amps on 12 volt range. Output is variable from 0 to 8 or 0 to 16 volts. Two meters constantly monitor output voltage and current. Will also double as a battery charger. Shpg. Wt. 23 lbs.

MODEL BE-5
\$39.95

HEATHKIT ISOLATION TRANSFORMER KIT

The model IT-1 is one of the handiest units for the service shop, home workshop or laboratory. Provides complete isolation from the power line. AC-DC sets may be plugged directly into the IT-1 without the chassis becoming "hot". Output voltage is variable from 90 volts to 130 volts allowing checks of equipment under adverse conditions such as low line voltage. Rated for 100 volt amperes continuously or 200 volt amperes intermittently. Panel meter monitors output voltage. Shpg. Wt. 9 lbs.

MODEL IT-1
\$16.50

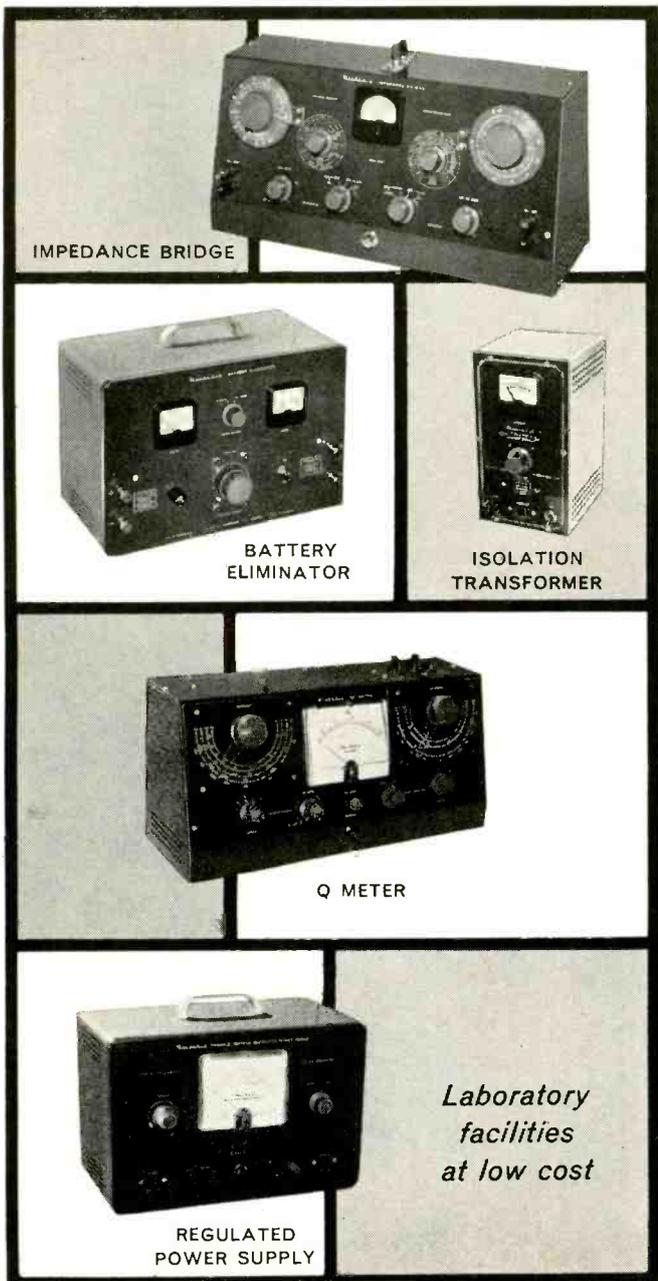

Heathkits...

By DAYSTROM

*are designed with high-quality,
name-brand components to
insure long service life*

HEATHKIT "Q" METER KIT

At this price the laboratory facilities of a Q Meter may be had by the average service technician or home experimenter. The Q Meter permits measurement of inductance from 1 microhenry to 10 millihenry, "Q" on a scale calibrated up to 250 full scale, with multipliers of 1 or 2, and capacitance from 40 mmf to 450 mmf \pm 3 mmf. Built in oscillator permits testing components from 150 kc to 18 mc. Large 4½" panel meter is featured. Very handy for checking peaking coils, chokes, etc. Use to determine values of unknown condensers, both variable and fixed, compile data for coil winding purposes, or measure RF resistance. Also checks distributed capacity and Q of coils. No special equipment is required for calibration. A special test coil is furnished, along with easy-to-follow instructions. Shpg. Wt. 14 lbs.

MODEL QM-1
\$44.50

HEATHKIT REGULATED POWER SUPPLY KIT

Here is a power supply that will provide DC plate voltage and AC filament voltage for all kinds of experimental circuits. The DC supply is regulated for stability, and yet the amount of DC output voltage available from the power supply can be controlled manually from 0 up to 500 volts. At 450 volts DC output, the power supply will provide up to 10 ma of current, and provide progressively higher current as the output voltage is lowered. Current rating is 130 ma at 200 volts output. In addition to furnishing B+ the power supply also provides 6.3 volts AC at up to 4 amperes for filaments. Both the B+ output and the filament output are isolated from ground. Ideal unit for use in laboratory, home workshop, ham shack, or service shop. A large 4½" meter on the front panel reads output voltage or output current, selectable with a panel switch. Shpg. Wt. 17 lbs.

MODEL PS-3
\$35.50



*Terrific values
in amateur
equipment!*



DX-20 TRANSMITTER



DX-35 TRANSMITTER



DX-100 TRANSMITTER

HEATHKIT DX-20 CW TRANSMITTER KIT

The Heathkit model DX-20 "straight-CW" transmitter features high efficiency at low cost. It uses a single 6DQ6A tube in the final amplifier stage for plate power input of 50 watts. A 6CL6 serves as crystal oscillator, with a 5U4GB rectifier. It is an ideal transmitter for the novice, as well as the advanced-class CW operator. Single-knob band switching is featured to cover 80, 40, 20, 15, 11 and 10 meters. Pi network output circuit matches various antenna impedances between 50 and 1000 ohms and reduces harmonic output. Top-quality parts are featured throughout, including "potted" transformers, etc., for long life. It has been given full "TVI" treatment. Access into the cabinet for crystal changing is provided by a removable metal pull-out plug on the left end of the cabinet. Very easy to build from the complete step-by-step instructions supplied, even if you have never built electronic equipment before. If you appreciate a good, clean signal on the CW bands, this is the transmitter for you! Shpg. Wt. 18 lbs.

MODEL DX-20
\$35⁹⁵

presents a most attractive appearance, and is designed for complete shielding to minimize TVI. Back panel control provides convenient switch selection of three different crystals, reached through access door at rear of cabinet. A most remarkable power package for the price. Complete step-by-step instructions with pictorial diagrams to assure your success in assembly. Shpg. Wt. 24 lbs.

MODEL DX-35
\$56⁹⁵

HEATHKIT DX-100 PHONE AND CW TRANSMITTER KIT

Listen to any ham band between 160 meters and 10 meters and note how many DX-100 transmitters you hear! The number of these fine rigs now on the air testifies to the enthusiasm with which it has been accepted by the amateur fraternity. No other transmitter in this power class combines high quality and real economy so effectively. The DX-100 features a built in VFO, modulator and power supplies, complete shielding to minimize TVI, and pi network output coupling to match impedances from approximately 50 to 600 ohms. Its RF output is in excess of 100 watts on phone and 120 watts on CW, for a clean strong signal on all the ham bands from 10 to 160 meters. Single-knob band switching and illuminated VFO dial and meter face add real operating convenience. RF output stage uses a pair of 6146 tubes in parallel, modulated by a pair of 1625's. High quality components are used throughout, such as "potted" transformers, silver-plated or solid coin silver switch terminals, aluminum heat-dissipating caps on the final tubes, copper plated chassis, etc. This transmitter was designed exclusively for easy step-by-step assembly. Shpg. Wt. 107 lbs.

MODEL DX-100
\$189⁵⁰

Heathkits...

BY DAYSTROM

*are designed by
licensed ham-engineers,
especially for you*

HEATHKIT DX-35 PHONE AND CW TRANSMITTER KIT

The DX-35 transmitter can be thought of as the "little brother" of the DX-100. It features both phone and CW operation on 80, 40, 20, 15, 11 and 10 meters. A single 6146 tube is used in the final amplifier stage to provide full 65 watt plate power input on CW, or controlled carrier modulation peaks up to 50 watts for phone operation. Modulator and power supplies are built right in and single knob band switching is combined with a pi network output circuit for complete operating convenience. The tight fitting cabinet

FUNCTIONAL DESIGN . . .

The transmitters described on this page were designed for the ham, by hams who know what features are desirable and needed. This assures you of the best possible performance and convenience, and adds much to your enjoyment in the ham shack.

HEATH COMPANY A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICH.**

OCTOBER, 1957


Automatically turns off transmitter and gives visual signal




"AUTOMATIC"
CONELRAD ALARM



GRID DIP METER

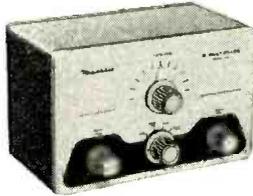

"Q" MULTIPLIER

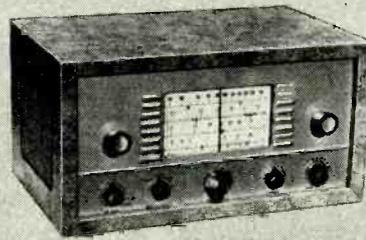

COMMUNICATIONS-TYPE
RECEIVER

*An ideal receiver
for the beginning
ham or short
wave listener*

HEATHKIT "AUTOMATIC" CONELRAD ALARM KIT

This conelrad alarm works with any radio receiver; AC-DC-transformer operated—or battery powered, so long as the receiver has AVC. Fully complies with FCC regulations for amateurs. When the monitored station goes off the air, the CA-1 automatically cuts the AC power to your transmitter, and lights a red indicator. A manual "reset" button reactivates the transmitter. Incorporates a heavy-duty six-ampere relay, a thyratron tube to activate the relay, and its own built-in power supply. A neon lamp shows that the alarm is working, by indicating the presence of B+ in the alarm circuit. Simple to install and connect. Your transmitter plugs into an AC receptacle on the CA-1, and a cable connects to the AVC circuit of a nearby receiver. A built-in sensitivity control allows adjustment to various AVC levels. Receiver volume control can be turned up or down, without affecting alarm operation. Build a Heathkit CA-1 in one evening and comply with FCC regulations now! Shpg. Wt. 4 lbs.

MODEL CA-1
\$13⁹⁵

HEATHKIT "Q" MULTIPLIER KIT

The Heathkit Q Multiplier functions with any AM receiver having an IF frequency between 450 and 460 KC, that is not "AC-DC" type. It derives its power from the receiver, and needs only 6.3 volts AC at 300 ma (or 12 VAC at 150 ma) and 150 to 250 volts DC at 2 ma. Simple to connect with cable and plugs supplied. Adds additional selectivity for separating signals, or will reject one signal and eliminate heterodyne. A tremendous help on crowded phone and CW bands. Effective Q of 4000 for sharp "peak" or "null". Tunes any signal within IF band pass without changing the main receiver tuning dial. A convenient tuning knob on the front panel with vernier reduction between the tuning knob and the tuning capacitor gives added flexibility in operation. Uses a 12AX7 tube, and special high-Q shielded coils. Instructions for connecting to the receiver and operation are provided in the construction manual. A worthwhile addition to any communications, or broadcast receiver. It may also be used with a receiver which already has a crystal filter to obtain two simultaneous functions, such as peaking the desired signal with the crystal filter and nulling an adjacent signal with the Q Multiplier. Shpg. Wt. 3 lbs.

MODEL QF-1
\$9⁹⁵

HEATHKIT GRID DIP METER KIT

A grid dip meter is basically an RF oscillator for determining the frequency of other oscillators, or of tuned circuits. Extremely useful in locating parasitics, neutralizing, identifying harmonics, coil winding, etc. Features continuous frequency coverage from 2 mc to 250 mc, with a complete set of prewound coils, and a 500 ua panel meter. Front panel has a sensitivity control for the meter, and a phone jack for listening to the "zero-beat." Will also double as an absorption-type wave meter. Shpg. Wt. 4 lbs.

Low Frequency Coil Kit: Two extra plug-in coils to extend frequency coverage down to 350 kc. Shpg. Wt. 1 lb. No. 341-A. \$3.00

MODEL GD-18
\$19⁹⁵

HEATHKIT ALL-BAND COMMUNICATIONS-TYPE RECEIVER KIT

This communications-receiver covers 550 kc to 30 mc in four bands, and provides good sensitivity, selectivity, and fine image rejection. Ham bands are clearly marked on an illuminated dial scale. Features a transformer-type power supply—electrical band spread—antenna trimmer—head-phone jack—automatic gain control and beat frequency oscillator. Accessory sockets are provided on the rear of the chassis for using the Heathkit model QF-1, Q Multiplier. Accessory socket is handy, also, for operating other devices that require plate and filament potentials. Will supply +250 VDC at 15 ma and 12.6 VAC at 300 ma. Ideal for the beginning ham or short wave listener. Shpg. Wt. 12 lbs.

Cabinet: Fabric covered cabinet with aluminum panel as shown. Part no. 91-15A. Shpg. Wt. 5 lbs. \$4.95.

MODEL AR-3
\$29⁹⁵

(Less cabinet)

Heathkits...

BY DAYSTROM

*are outstanding in performance
and dollar value*

RADIO-ELECTRONICS

HEATHKIT REFLECTED POWER METER KIT

The Heathkit reflected power meter, model AM-2, makes an excellent instrument for checking the match of the antenna transmission system, by measuring the forward and reflected power or standing wave ratio. The AM-2 is designed to handle a peak power of well over 1 kilowatt of energy and may be left in the antenna system feed line at all times. Band coverage is 160 meters through 2 meters. Input and output impedances for 50 or 75 ohm lines. No external power required for operation. Meter indicates percentage forward and reflected power, and standing wave ratio from 1:1 to 6:1. Another application for the AM-2 is matching impedances between exciters or R.F. sources and grounded grid amplifiers. Power losses between transmitter output and antenna tuner may be very easily computed by inserting the AM-2 in the line connecting the two. No insertion loss is introduced into the feeder system, due to the fact that the AM-2 is a portion of coaxial line in series with the feeder system and no internal connections are actually made to the line. Complete circuit description and operation instructions are provided in the manual. Cabinet size is 7-3/8" x 4-1/16" x 4-5/8". Can be conveniently located at operating position. Shpg. Wt. 3 lbs.

MODEL AM-2

\$15⁹⁵

HEATHKIT VARIABLE FREQUENCY OSCILLATOR KIT

Enjoy the convenience and flexibility of VFO operation by obtaining the Heathkit model VF-1 Variable Frequency Oscillator. Covers 160-80-40-20-15-11 and 10 meters with three basic oscillator frequencies. Better than 10 volt average RF output on fundamentals. Plenty of output to drive most modern transmitters. It features voltage regulation for frequency stability. Dial is illuminated for easy reading. Vernier reduction is used between the main tuning knob and the tuning condenser. Requires a power source of only 250 volts DC at 15 to 20 milliamperes and 6.3 volts AC at 0.45 amperes. Extra features include copper-plated chassis, ceramic coil forms, extensive shielding, etc. High quality parts throughout. VFO operation allows you to move out from under interference and select a portion of the band you want to use without having to be tied down to only two or three frequencies through use of crystals. "Zero in" on the other fellow's signal and return his CQ on his own frequency! Crystals are not cheap, and it takes quite a number of them to give anything even approaching comprehensive coverage of all bands. Why hesitate? The model VF-1 with its low price and high quality will add more operating enjoyment to your ham activities. Shpg. Wt. 7 lbs.

MODEL VF-1

\$19⁵⁰

Heathkits...

BY DAYSTROM

are the answer for your electronics hobby.

HEATHKIT BALUN COIL KIT

The Heathkit Balun Coil Kit model B-1 is a convenient transmitter accessory, which has the capability of matching unbalanced coax lines, used on most modern transmitters, to balance lines of either 75 or 300 ohms impedance. Design of the bifilar wound balun coils will enable transmitters with unbalanced output to operate into balanced transmission line, such as used with dipoles, folded dipoles, or any balanced antenna system. The balun coil set can be used with transmitters and receivers without adjustment over the frequency range of 80 through 10 meters, and will easily handle power inputs up to 250 watts. Cabinet size is 9" square by 5" deep and it may be located any distance from the transmitter or from the antenna. Completely enclosed for outdoor installation. Shpg. Wt. 4 lbs.

MODEL B-1


\$8⁹⁵

HEATHKIT 6 OR 12 VOLT VIBRATOR POWER SUPPLY KITS

These little power supply kits are ideal for all portable applications with 6 volt or 12 volt batteries, when you are operating electronic equipment away from power lines. By replacing the power supplies of receivers, small public address systems, or even miniature transmitters with these units, they can be used with conventional 6 or 12 volt batteries. Use in boats, automobiles, light aircraft, or any field application. Each unit provides 260 volts DC output at up to 60 milliamperes. More than one power supply of the same model may be connected in parallel for increased current capacity at the same output voltage. Everything is provided in the kit, including a vibrator transformer, a vibrator, 6X4 or 12X4 rectifier, and the necessary buffer capacitor, hash filter, and output filter capacitor. Shpg. Wt. 4 lbs.

6 VOLT
MODEL VP-1-6
12 VOLT
MODEL VP-1-12

\$7⁹⁵ Each

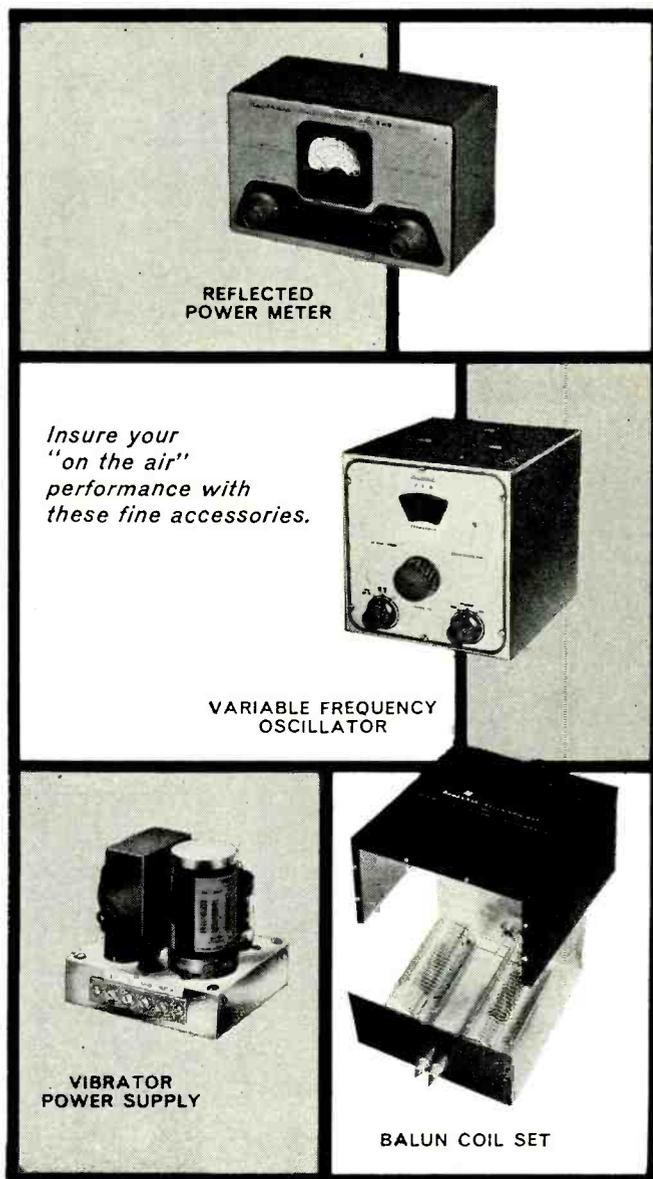

REFLECTED
POWER METER

*Insure your
"on the air"
performance with
these fine accessories.*

VARIABLE FREQUENCY
OSCILLATOR

VIBRATOR
POWER SUPPLY

BALUN COIL SET

HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.

OCTOBER, 1957

77

**HEATHKIT ELECTRONIC
IGNITION ANALYZER KIT**

Previous electronic experience is not necessary to build this fine ignition analyzer. The construction manual supplied has complete step-by-step instructions plus large pictorial diagrams showing the exact placement and value of each component. All parts are clearly marked so that they are easily identified. The IA-1 is an ideal tool for engine mechanics, tune-up men, and auto hobbyists, since it traces the dynamic action of voltage in an ignition system on a cathode-ray tube screen. The wave form produced is affected by the condition of the coil, condenser, points, plugs, and ignition wiring, so it can be analyzed, and used as a "sign-post" to ignition system performance. This analyzer will detect inequality of spark intensity, a poor spark plug, defective plug wiring, breaker-point bounce, an open condenser, and allow setting of dwell-time percentage for the points. An important feature of this instrument is its ability to check dynamic performance, with the engine in operation (400 to 5000 RPM). It will show the complete engine cycle, or only one complete cylinder. Can be used on all types of internal combustion engines where breaker-points are accessible. Use it on automobiles, boats, aircraft engines, etc. Shpg. Wt. 18 lbs.

MODEL IA-1
\$59⁹⁵

**HEATHKIT PROFESSIONAL
RADIATION COUNTER KIT**

This Heathkit professional-type radiation counter is simple to build successfully, even if you have never built a kit before. Complete step-by-step instructions are combined with giant-size pictorial diagrams for easy assembly. By "building it yourself" you can have a modern-design, professional radiation counter priced far below comparable units. Provides high sensitivity with ranges from 0-100, 600, 6000 and 60,000 counts-per-minute, and 0-.02, .1, 1 and 10 miliroentgens-per-hour. Employs 900-volt bismuth tube in beta/gamma sensitive probe. Probe and 8-foot expandable cable included in kit price, as is a radiation sample for calibration. Use it in medical laboratories, or as a prospecting tool, and for civil defense to detect radioactive fallout, or other unknown radiation levels. Features a selectable time constant. Meter calibrated in CPM or mR/hour in addition to "beep" or "click" from panel-mounted speaker. Prebuilt "packaged" high voltage power supply with reserve capacity above 900 volt level at which it is regulated. Merely changing regulator tube type would allow use of scintillation probe if desired. Employs five tubes (plus a transistor) to insure stable and reliable operation. Kit price includes batteries. Shpg. Wt. 8 lbs.

MODEL RC-1
\$79⁹⁵



IGNITION
ANALYZER



*Kit includes everything
you need for
construction — even
batteries!*

RADIATION COUNTER

Heathkits...


By DAYSTROM

*are supplied with comprehensive
instructions that eliminate costly
mistakes and save valuable time*

HEATHKIT ENLARGER TIMER KIT

The ET-1 is an easy-to-build electronic device to be used by amateur or professional photographers in timing enlarger operations. The calibrated dial on the timer covers 0 to 1 minute, calibrated in 5-second gradations. The continuously variable control allows setting of the "on" cycle of your enlarger, which is plugged into a receptacle on the front panel of the ET-1. A "safe light" can also be plugged in so that it is automatically turned "on" when the enlarger is turned "off." Handles up to 350 watts with built-in relay. All-electronic timing cycle insures maximum accuracy. Timer does not have to be reset after each cycle, merely flip lever switch to print, to repeat time cycle. A control is provided for initial calibration. Housed in a compact plastic case that will resist attack of photographic chemicals. A fine addition to any dark room. Shpg. Wt. 3 lbs.

MODEL ET-1
\$11⁵⁰

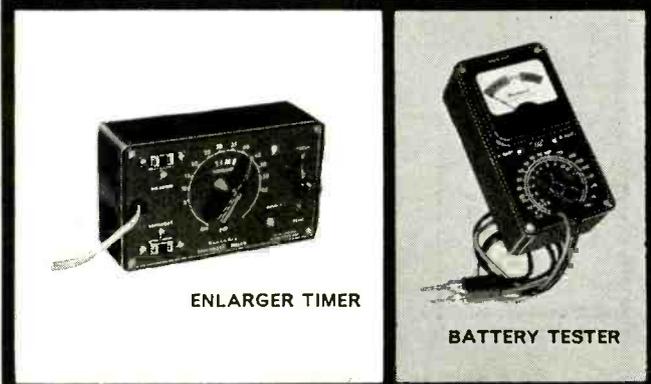


ENLARGER TIMER

BATTERY TESTER

HEATHKIT BATTERY TESTER KIT

The BT-1 is a special battery testing device that actually "loads" the battery under test (draws current from it) while it is being tested. Weak batteries often test "good" with an ordinary voltmeter but the built-in load resistance of the BT-1 automatically draws enough current from the battery to reveal its true condition. Simple to operate with "good-weak-replace" scale. Tests all kinds of dry cell batteries within ranges of 0-15 volts and 0-180 volts. Slide switch provides for either 10 ma or 100 ma load, depending on whether you're testing an A or B battery. Not only determines when battery is completely exhausted, but makes it possible to anticipate failure by noting weak condition. Ideal for testing dry cell hearing aid, flashlight, portable radio, and model airplane batteries. Test batteries in a way your customers can understand and stimulate battery sales. Shpg. Wt. 2 lbs.

MODEL BT-1
\$8⁵⁰

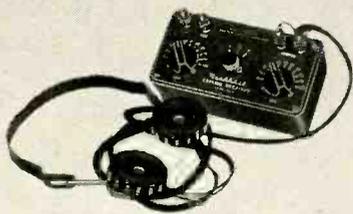


CRYSTAL RADIO



Now you can have radio
wherever you go —
with the portable
that plays anywhere!



BROADCAST BAND RADIO

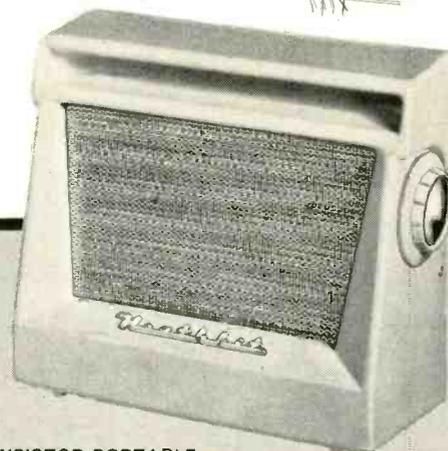

TRANSISTOR PORTABLE

HEATHKIT CRYSTAL RADIO KIT

The Heathkit model CR-1 crystal radio is similar to the "crystal sets" of the early radio days except that it has been improved by the use of sealed germanium diodes and efficient "high-Q" coils. The sealed diodes eliminate the critical "cats whisker" adjustment, and the ferrite coils are much more efficient for greater signal strength. Housed in a compact plastic box, the CR-1 uses two tuned circuits, each with a variable tuning capacitor, to select the local station. It covers the broadcast band from 540 to 1600 kc. Requires no external power whatsoever. This receiver could prove valuable to emergency reception of civil defense signals should there be a power failure. The low kit price even includes headphones. Complete step-by-step instructions and large pictorial diagrams are supplied for easy assembly. The instruction manual also provides the builder with the basic fundamentals of signal reception so that he understands how the crystal receiver functions. An interesting and valuable "do-it-yourself" project for all ages. Shpg. Wt. 3 lbs.

MODEL CR-1
\$7⁹⁵

result of these efforts. Six name-brand (Texas Instrument) transistors were selected for extra good sensitivity and selectivity. A 4" by 6" PM speaker with heavy magnet was chosen to insure fine tone quality. The power supply was designed to use six standard size "D" flashlight cells because they are readily available, inexpensive, and because they afford extremely long battery life (between 500 and 1000 hours). Costs you no more to operate from batteries than what you pay for operating a small table-model radio from the power line. An unbreakable molded plastic was selected for cabinet material because of its durability and striking beauty. Circuit is compact and efficient, yet components are not excessively crowded. Transformers are prealigned so it is ready for service as soon as construction is completed. Has built in rod-type antenna for reception in all locations. Cabinet dimensions are 9" L x 8" H x 3 3/4" D. Comes in holiday gray, with gold-anodized metal speaker grille. Compare this portable, feature by feature, to all others on the market, and you'll appreciate what a tremendous dollar value it represents! Shpg. Wt. 4 lbs.

MODEL XR-1

\$34⁹⁵

(Less batteries)
(With cabinet)

Heathkits...

By DAYSTROM

are easy and fun to build,
and they let you learn
by "doing-it-yourself"

HEATHKIT TRANSISTOR PORTABLE RADIO KIT

Heath engineers set out to develop a "universal" AM radio, suitable for use anywhere. Their objective was a portable that would be as much "at home" inside as it is outside, and would feature top quality components for high performance and long service life. The model XR-1 is the

HEATHKIT BROADCAST BAND RADIO KIT

This table-model broadcast radio is fun to build, and is a fine little receiver for your home. It covers the standard broadcast band from 550 to 1600 kc with good sensitivity and selectivity. The 5 1/2" PM speaker provides surprisingly good tone quality. High-gain IF transformers, miniature tubes, and a rod-type built in antenna, assure good reception in all locations. The power supply is transformer operated, as opposed to many of the economy "AC-DC" types. It's easy to build from the step-by-step instructions, and the construction manual includes information on operational theory, for educational purposes. Your success is assured by completely detailed information which also explains resistor and capacitor color codes, soldering techniques, use of tools, etc. A signal generator is recommended for final alignment. Shpg. Wt. 10 lbs.

MODEL BR-2

\$18⁹⁵

(Less cabinet)

Cabinet: Fabric covered cabinet with aluminum panel as shown. Shpg. Wt. 5 lbs. Part no. 91-9A. \$4.95.


HEATH COMPANY A Subsidiary of Daystrom, Inc. BENTON HARBOR 20, MICH.

OCTOBER, 1957

79

protects against possible explosion and fire from undetected fuel vapor

FUEL VAPOR DETECTOR

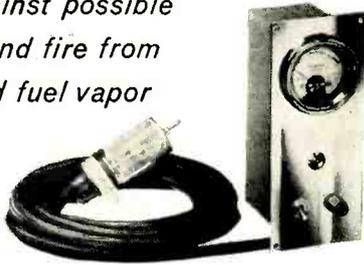



detects electrolysis currents which cause deterioration of underwater metal fittings on your boat

ELECTROLYSIS DETECTOR



indicates condition and charge of batteries for safe cruising

BATTERY CHARGE INDICATOR

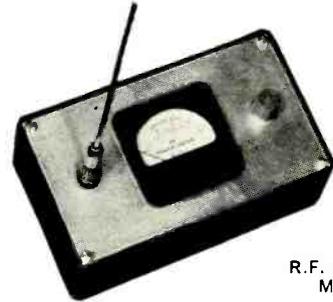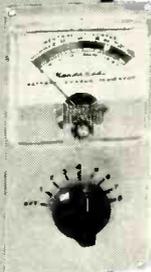

R.F. POWER METER

HEATHKIT FUEL VAPOR DETECTOR KIT

Protect your boat and its passengers against fire or explosion from undetected fuel vapor by building and using one of these fine units. The Heathkit Fuel Vapor Detector indicates the presence of fumes on a three-color "safe-dangerous" meter scale and immediately shows if it is safe to start the engine. A pilot light on the front panel shows when the detector is operating, and it can be left on continuously, or just used intermittently. A panel control enables initial calibration of the detector when installed. Features a hermetically-sealed meter with chrome bezel, and a chrome-plated brass panel. It is very simple to build and install, even by one not having previous experience. Models FD-1-6 (6 volts DC) and FD-1-12 (12 volts DC) operate from your boat batteries. The kit is complete in every detail, even to the inclusion of a spare detector unit. Shpg. Wt. 4 lbs.

6 volt
MODEL FD-1-6
12 volt
MODEL FD-1-12

\$35⁹⁵
EACH

cause gradual corrosion and deterioration of the propeller or other metal fittings below the water line. It is particularly helpful when installing electrical equipment of any kind, or to determine proper polarity when power is obtained from a shore supply. Easy-to-build, the model ED-1 consists of a hermetically-sealed, waterproof meter, special sensing plate, and sufficient wire to install, including the necessary hardware. Mounts on instrument panel where it can be easily seen. Requires no power for operation, and gives instant warning to guard your boat for a lifetime. Shpg. Wt. 2 lbs.

MODEL ED-1
\$9⁹⁵

HEATHKIT RF POWER METER KIT

The Heathkit RF Power Meter Kit is designed to sample the RF field in the vicinity of your transmitter, whether it be marine, mobile, or fixed. Output meter is merely placed in some location close to the transmitter, to pick up RF radiation from the antenna. Requires no batteries, electricity, nor direct connection to the transmitter. It provides you with a continuing indication of transmitter operation. You can easily detect if power is dropping off by comparing present meter readings with past ones. Operates with any transmitter having output frequencies between 100 kc and 250 mc, regardless of power. Sensitivity is 0.3 volts RMS full scale, and a special control on the panel allows for further adjustment of the sensitivity. Meter is a 200 ua unit, mounted on a chrome-plated brass panel. The entire PM-1 measures only 3 3/4" W x 6 1/4" L x 2" D. An easy way to put your mind at ease concerning transmitter operation. Shpg. Wt. 2 lbs.

MODEL PM-1
\$14⁹⁵

HEATHKIT BATTERY CHARGE INDICATOR KIT

The Heathkit model CI-1 Marine Battery Charge Indicator has been designed especially for the boat owner, although it has found use in service stations, power stations, and radio stations where banks of batteries are kept in reserve for emergency power. It is intended to replace the hydrometer method of checking storage batteries, and to eliminate the necessity for working with acid in small, below-decks enclosures. Now it is possible to check as few as one, or as many as eight storage batteries, merely by turning the switch and watching the meter. A glance at the meter tells you instantly whether your batteries are sufficiently charged for safe cruising. Dimensions are 2-7/8" W x 5-11/16" H x 2" D. Operates on either 6 or 12 volt systems using lead-acid batteries, regardless of size. Simple installation can be accomplished by the boat owner in fifteen minutes. Shpg. Wt. 3 lbs.

MODEL CI-1
\$16⁹⁵


HEATHKIT ELECTROLYSIS DETECTOR KIT

The Heathkit model ED-1 Electrolysis Detector indicates the extent of electrolysis currents between the boat's common ground and underwater fittings, except on boats having metal hulls. These currents, undetected, could

Heathkits...

BY DAYSTROM

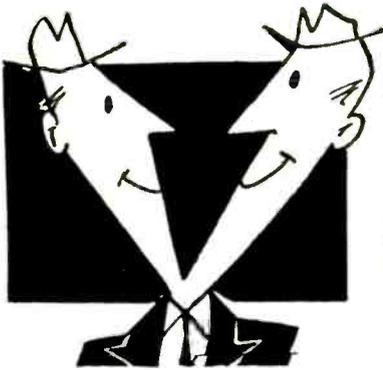now offer you completely modern marine equipment with outstanding design features



TWO CHANNELS?...EASY!

Modify your one-channel remote-control system for two-channel operation

By E. L. SAFFORD, Jr.

ONCE in a great while an idea comes along which is so simple and practical, that it becomes an outstanding contribution to the field of radio control. Such an idea is the brainchild of Lt. Col. William Sydnor, which allows anyone who has a single-channel receiver to make a simple addition and get two control channels.

If a standard single-channel receiver relay is connected to two time-delay secondary relays (Price 100-ohm type shunted by a 100- μ f 15-volt electrolytic capacitor) as illustrated in Fig. 1, two control channels are available when the proper code is transmitted. Note that if the receiver relay (Ry1) armature is caused to vibrate so that the time it is away from, say, contact X is less than the time it takes capacitor C1 to discharge through the windings of Ry2, that relay will be actuated and remain so as shown. The same reasoning applies to relay Ry3. This vibratory action of the armature then must be in the vicinity of 25 to 30 cycles. When this pulse rate is transmitted, control relays Ry2 and Ry3 are actuated and open the control circuits. Now, we must be able to close (de-energize) either relay as desired if the control circuit is to be operated at will.

If the pulse rate becomes a continuous carrier or tone, the receiver relay does not vibrate. It is energized and the armature makes contact with Y, staying there as long as the signal is transmitted. This causes Ry3 to remain energized, holding its control circuit open, but allows Ry2 to de-energize and close its circuit. The reverse is also true: if the signal is cut off, the receiver


relay armature remains on contact X, holding Ry2's circuit open and allowing Ry3 to close its control circuit. The code then consists of a fast pulse rate for no control, full signal for channel 1 and no signal for channel 2.

The coder

The coder is as simple as the decoder. It consists of a relay connected to form a buzzer. If the relay is similar to the one used in the receiver, the receiver relay will be able to follow its vibrations. The variable resistor and the capacitor across the relay allow some control of the vibrating frequency (see Fig. 2).

To use the unit, close switch S1, causing the armature to vibrate. Adjust resistor R and the receiver plate relay so that the receiver's control relays operate properly. To send signals to channel 1 or channel 2, either S2 or S3 is depressed.

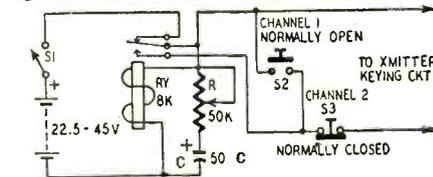Because of the high vibration frequency and the low delay time, it is possible to send pulses fast enough (using the pushbutton switches) to operate the compound type escapements



- R—pot, 50,000 ohms
- C—50 μ f, 50 volts, miniature electrolytic
- Ry—spdt, 8,000 ohms, plate circuit
- S1—spst, toggle
- S2—spst, normally open, pushbutton
- S3—spst, normally closed, pushbutton
- Battery, 22.5 to 45 volts

Fig. 2—Encoder unit circuit for two-channel operation with a one-channel remote-control circuit.

in either channel. This allows up to six functions of control and fail-safe neutrals.

Several types of pulser units are available. They are constructed with circular magnets. These units, when fed a pulse-width-pulse-spacing code, allow proportional control of, say, a plane rudder. See Chapter 2, *Radio-Control Handbook* (Gernsback Library). It seems quite feasible to modify such a unit to replace the two decoder relays, as shown in Fig. 3. Centering springs are required so that the magnet armature will spring away from the contact when pulsing is stopped and not result in a bounce which might cause a standard escapement to skip.

This method could be used to energize a steering motor for a boat or car.

A second idea which also seems feasible, if you are experiment-minded, would be to construct a unit to replace all three relays. Such a unit is shown in Fig. 4. If you build a solenoid with a winding equivalent to that of a 8,000-10,000-ohm relay and add a light compression spring within the hollow core so the magnetic plunger is pulled against it when the coil is energized, it is possible to cause the moving armature attached to the plunger to float between the two control contacts. A solenoid is suggested since the pull on the plunger is roughly proportional to the current flowing through the windings and the magnetic path is not broken by an air gap as in a relay type of unit.

With such a device, small and light, the receiver's relay stage could be modified so that the amount of current drawn through the tube would be proportional to a pulse-spacing-pulse-width variation. Pulses would be transmitted as before, but this time the width and spacing would be adjusted until the armature of the solenoid floated between the two contacts. Operation of the two channels would then be as previously described. The details are left to the builder's ingenuity, but remember, two channels are better than one. END

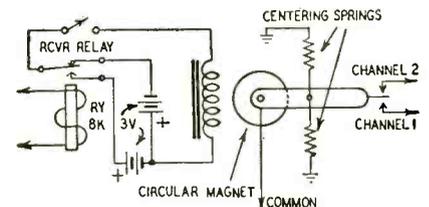


Fig. 3—Experimental circuit uses circular magnet pulser.


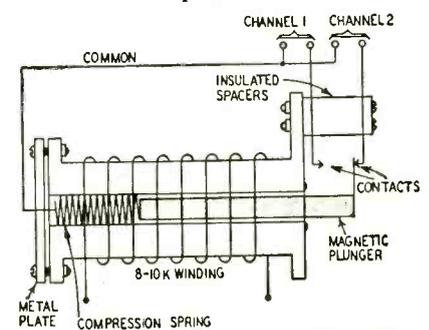


Fig. 4—Spring-loaded solenoid could replace all three relays in receiver circuit.

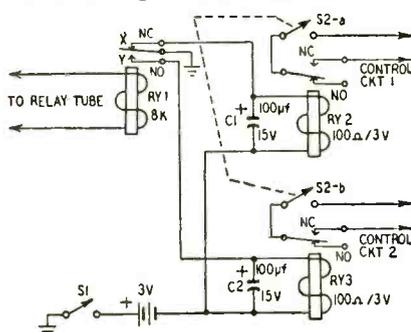

- C1, 2—100 μ f, 15 volts, miniature electrolytics
- Ry1—spdt, 8,000 ohms, plate circuit
- Ry2, 3—spdt, 100 ohms, 3 volts (Price type 1001)
- S1—spst, toggle
- S2—dpst, toggle
- Battery, 3 volts

Fig. 1—Circuit of decoder unit.



NO FINGERNAIL FUMBLING!

Exclusive

"T - GUARD"

STYLUS

only with the

PICKERING

Fluxvalve



PICKERING'S introduction of the *truly* miniature FLUXVALVE magnetic phonograph cartridge represents a new era in high fidelity cartridge design. This newest of PICKERING cartridges brings the music lover the most exciting and *safest* idea in a stylus assembly since PICKERING introduced the first lightweight high fidelity pickup more than a decade ago.


The "T-Guard" stylus assembly is a quick-change, easy to slip-in unit which eliminates precarious finger-nail fumbling. Its practical "T" shape provides a firm and comfortable grip for safe and easy stylus change.

The most flexible cartridge in the world . . . the FLUXVALVE is the *only* cartridge with the remarkable 1/2 mil stylus . . . exclusive *only* with PICKERING. The FLUXVALVE can be used with any one of *five* styli, to meet any requirement or application . . . to play any record, at any speed.

If you are planning to buy a new cartridge—the fact that PICKERING developed this revolutionary stylus is *important to you!* All of the research, development and planning that went into the "T-Guard" stylus is conclusive proof of the superlative engineering skill in every FLUXVALVE model you buy.



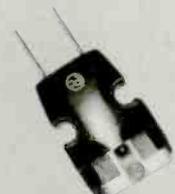FLUXVALVE TWIN SERIES 350 — A turn-over cartridge providing a rapid change of stylus point radius. Available in 12 models featuring many combinations of styli, prices start at a modest \$24.



FLUXVALVE SINGLE SERIES 370 — A miniature high quality cartridge for use in any type of auto-changer or manual player arm. Available in 5 models, prices start at a low \$17.85.

The FLUXVALVE features exclusive hum rejection circuit—requires no adjustment!

Model 194D UNIPOISE Pickup Arm—A new . . . lightweight . . . integrated arm and cartridge assembly containing the FLUXVALVE with exclusive "T-Guard" stylus. The complete assembly—tone arm and cartridge—is only a fraction of the weight of conventional tone arms. The high compliance of the "T-Guard" stylus, with the lightweight tone arm and single friction-free pivot bearing



assures distortionless tracking of microgroove and standard groove recordings. Available with the 1/2, 1 or 2.7 mil diamond stylus, prices from \$59.85.

"For those who can hear the difference" FINE QUALITY HIGH FIDELITY PRODUCTS BY



PICKERING & COMPANY, INC., Oceanside, N. Y.

Sensitive Relay Saves Standby Power

By ROD DRIVER

LIGHT, voice and radio are but a few examples of the signals that will operate this relay which stands by indefinitely, drawing practically no power.

A relay that operates on voltage changes and draws only a few μ a from the control element is not new, but it usually requires tubes that deteriorate and whose filaments draw power while the circuit is inactive. This circuit uses one cold-cathode tube that lasts almost indefinitely if operated within its ratings and the only power consumed when standing idle is that drawn by a 100,000-ohm potentiometer across the ac line.


The heart of the circuit is a Chatham 313C gas-filled, cold-cathode trigger tube. It has a cathode, anode and a starter anode, and operates like a positive-grid thyratron.

The main gap (anode to cathode) will not conduct current until the anode is about 185 volts positive. Then the tube voltage drops instantly to 75, the main-gap sustaining voltage, and the current depends only on the resistance in series between the tube and power supply.


The starter gap (starter anode to cathode) behaves like the main gap but, being closer spaced, has a firing voltage of 70 and a sustaining voltage of 60. Again there must be enough series resistance in the circuit to limit the current to a safe value.

The tube is useful for control purposes due to the fact that a current of a few microamperes in the starter gap slightly ionizes the gas in the tube and greatly reduces the voltage necessary to fire the main gap. Fig. 1 shows how the main-gap firing voltage depends on the starter-gap current. As in a thyratron, once the main gap has fired the starter has no more control over it. The only way to stop conduction is to reduce the anode voltage below the sustaining value.

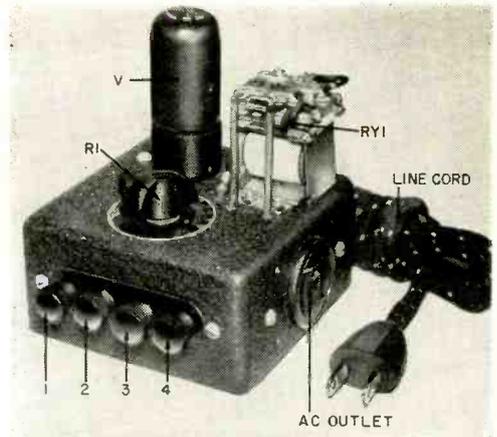Versatile circuit is triggered by many types of signals



Top—The sensitive standby relay.

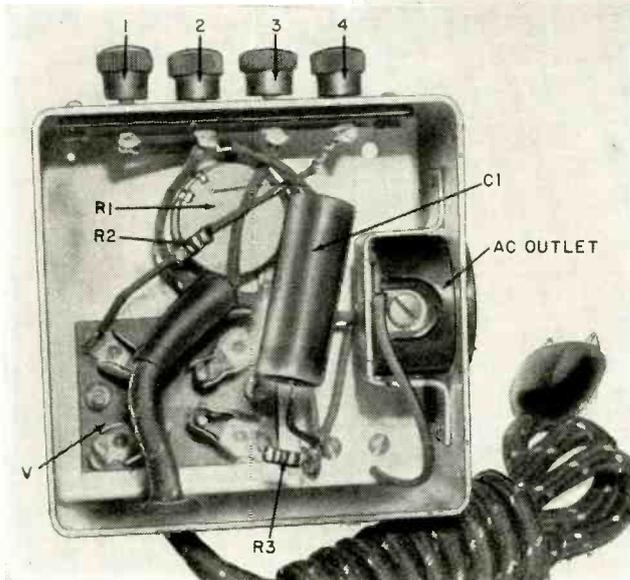

Left — Bottom view of relay chassis. Parts layout is not critical.


To use the tube as a relay, it is necessary to add the control voltage to a pedestal voltage high enough to give a total of 70 volts or more on the starter anode, while simultaneously applying voltage to the main gap. The load (relay) is in the main-gap series circuit. The problem is to get a high enough voltage from the control so that control signals will fire the tube but variations in the pedestal supply voltage will not.

The relay circuit

The relay circuit shown in the photos and in Fig 2-a needs no dc power

supply. The 313C tube operates satisfactorily on ac because it conducts very little current in the reverse direction.

The circuit used on 117 volts ac can operate only at instants when the anodes are positive. The sensitivity control is set so that the peak voltage from the cathode is less than 70, say 65 volts. Terminals 3 and 4 connect to the control and, if it is putting out 5 volts with terminal 4 positive, the starter gap will fire. The starter-gap current will then fire the main gap which conducts current until the voltage falls below the sustaining value.

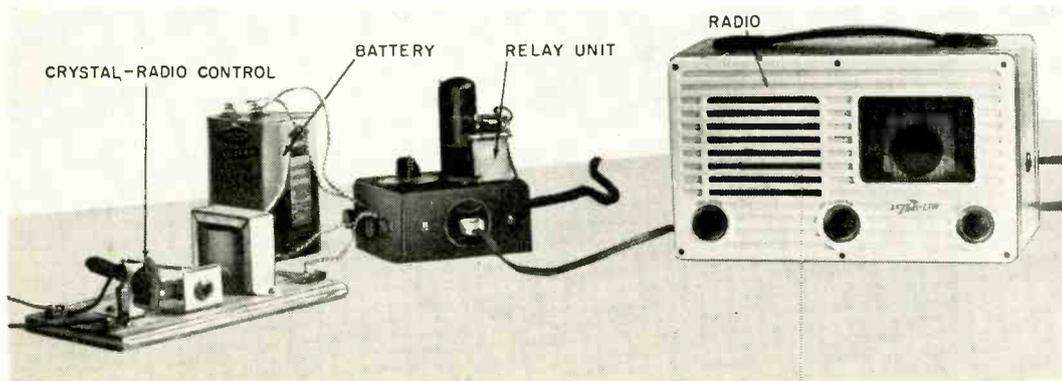

Left — Crystal set control connected to turn on a radio.

Right — Some controls that will operate the relay.

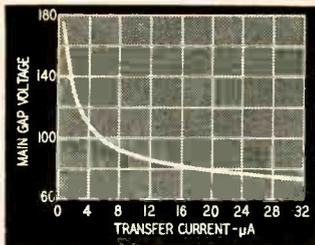


Fig. 1—Transfer characteristics of Chatham 313C cold-cathode tube.

For long tube life, the average cathode current should not exceed 10 ma and the peak cathode current should not exceed 30 ma. In 117-volt ac operation the peak cathode current restriction makes a 3,300-ohm limiting resistor in series with the relay necessary. Any of the following relays or others in between will then work:

| Coil resistance (ohms) | Actuating Current (ma) |
|------------------------|------------------------|
| 1,000 | 2.0 |
| 2,500 | 1.5 |
| 5,000 | 1.0 |

If you want it to lock on a single signal, the relay must have double-pole contacts capable of handling the desired current so that one set can serve in the locking circuit. For locking action, a battery large enough to close the relay is connected to terminals 1 and 2 of Fig. 2-a, with 2 positive.

The most likely source of such a relay is a surplus dealer. If you cannot get this relay—or if you have others on hand—use a single-pole plate circuit relay and connect it to a double-pole low-voltage relay as shown in Fig. 2-b for the locking effect. Often a relay rated at higher current will work with careful adjustment.

Test the completed relay circuit as follows: Short control terminals (3 and 4) together, leaving terminals 1 and 2 open. Then plug the relay circuit into the ac line and turn up the sensitivity control. The plate circuit relay should close positively as soon as the sensitivity control is turned up enough (about half rotation) so that it closes at all. If it starts to close at one setting and closes positively at a higher setting of the sensitivity control, you need a more sensitive relay.

Since the terminals are "hot" and the circuit components may be damaged by accidentally shorting other than the control terminals, unplug the relay when making any connections to it.

Photocell relay


A phototube connected to the relay circuit as shown in Fig 3-a will close the relay on increasing light intensity. Almost any gas or vacuum phototube (868, 929, 930, etc.) will work. The load resistor can be anywhere from 1 to 20 megohms. Higher resistances usually give a more sensitive circuit.

As the light increases, the increased phototube current gives a greater voltage drop across the load resistance and raises the starter anode voltage. The intensity level that fires the tube depends on the sensitivity control setting.

If you want decreasing values of light to operate a relay, connect the phototube as shown in Fig. 3-b. Note that the cathode of the phototube connects to the bottom line lead of Fig. 2-a. Add a terminal connected to this line if you intend to use the relay this way.

Sound-powered relay

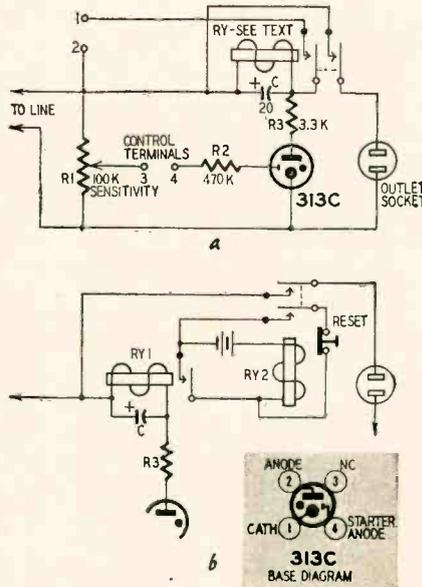A carbon microphone connected through a 6-volt battery and a high-



- R1—pot, 100,000 ohms, 2 watts
- R2—470,000 ohms, 1/2 watt
- R3—3,300 ohms, 1 watt
- C—20-μf 150-volt electrolytic
- RY1, 2—see text
- V—313C, Chatham cold cathode (State Labs Inc., 649 Broadway, New York, N. Y.)
- Tube socket—4 prongs
- Chassis 4 x 4 x 2 inches
- Terminal strip—4 lug
- Outlet socket—117 volts
- Line cord
- Miscellaneous hardware

Fig. 2-a—Standby relay circuit; 2-b—modification allows locking effect.

ratio transformer to the control terminals gives a sound-operated relay (Fig. 4). I used a Stancor A-4747 input transformer which has a 1 to 137 ratio.

To operate, adjust the sensitivity control to a point slightly below firing voltage, and turn on the microphone. This unit could serve as a sound-powered burglar alarm or for controlling displays by voice commands.

Radio-powered relay

A crystal set such as shown in Fig. 5, coupled to the control terminals through a high-impedance stepup transformer, will turn on the relay whenever the radio station tuned starts broadcasting. The idea for this application came from the Sylvania booklet *Electronic Shortcuts for Hobbyists*. A good outdoor antenna and a good ground will be essential in most cases.

The relay operates on the audio signals rather than on the carrier and the difficulty lies in getting a suitable transformer to step up the audio voltage. Ideally it would have an input impedance of 3,000 ohms or more and a ratio of 1 to 10 or more. The closest standard transformer I have found that will work is the Stancor A-4726 (discontinued) which has an input of 2,500 ohms and a ratio of 1 to 6.3. (This is not the transformer shown in the photograph.) Others that may be tried are the Chicago IN-16 and Triad A-42Z universal interstage transformers with 1-to-6-turns ratios.

Using the Stancor A-4726, the circuit


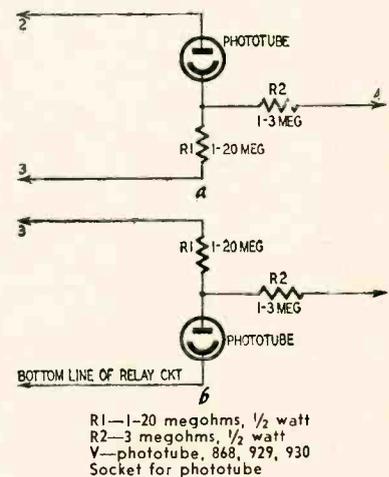


Fig. 3-a—Increase in light keys relay; 3-b—Relay triggered by decrease in light.

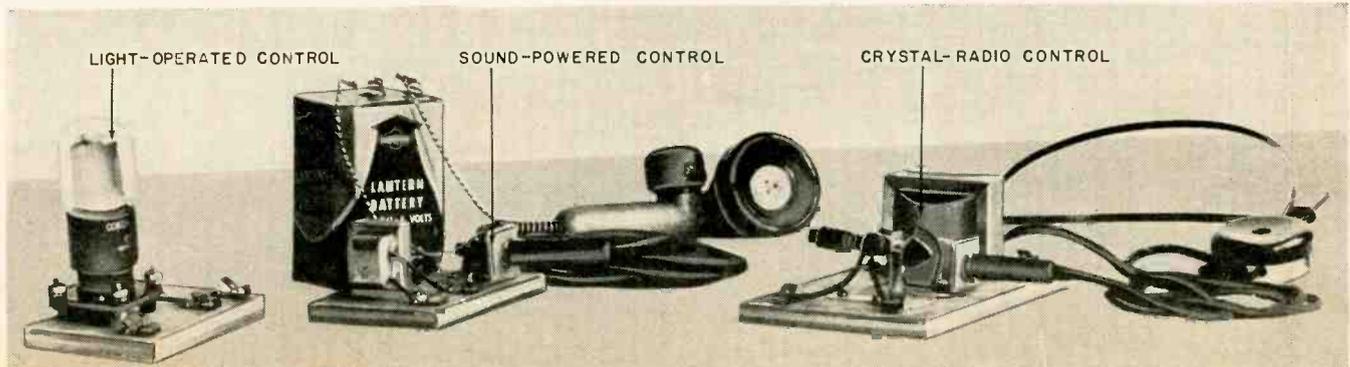

how to pick up the chips in the

Non Color-Blind **HELIX**

SELL



Yes Mr. Service Dealer

Your thousands of Colortenna orders and reorders prove it . . .

You like the idea of an integrated antenna line that assures you the right antenna answer for every reception problem . . .

You like the idea of the red helix which identifies the Colortenna to prospects as an outstanding performer in black and white and color . . .

NOW WITH BRILLIANT ALCOA SPEC.

You like the big prizes and trips you win in the fabulous Colortenna Sell-A-Bration . . .

You like the hard-hitting local advertising and promotion that pays off in Colortenna sales in your store . . .

You like the ready-made customer acceptance and confidence that Colortenna performance builds for you . . .

And in 1958

You'll love the spectacular new JFD Colortenna line that will send your antenna profits rocketing to new highs. Put its dynamic selling power to work for you by seeing your JFD distributor now.

CASH IN ON THE SELL-A-BRATION SWEEPSTAKES!

Over \$100,000.00 worth of prizes given so far to TV dealers and servicemen!

3 GRAND PRIZES TO SERVICE-DEALERS

with highest totals for season, September 1, 1957—March 31, 1958.

Winners to be announced May 19, 1958.

First Prize ALL-Expenses Paid Trip for Two to Paris

Second Prize ALL-Expenses Paid Trip for Two to Bermuda

Third Prize ALL-Expenses Paid Week-End for Two at the Waldorf-Astoria in New York

EVERY COLORTENNA COUNTS FOR FREE PRIZES!

Wallace 16 Pc. Tableware Set
Only 14 Power Helix—PX911S

12 Spalding GOLF Ball Set
Only 25 Star Helix—SX711



Chatham Orlon Blanket
Only 11 Wonder Helix—WX811S

Samsonite Ladies Case
Only 38 Wonder-Helix—WX811

Samsonite Men's "Quick-Tripper"
Only 40 Wonder-Helix—WX811

Aluminum Fishing Tackle Box
Only 11 Star Helix—SX711S

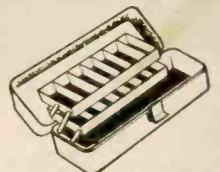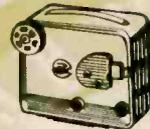PLUS HUNDREDS OF OTHER BRAND-NAME PRODUCTS



TV Antenna Market

TENNAS®

SUN-FAST GOLD ANODIZING!



WONDER-HELIX
 model type
 AX811 Gold Anodized
 WX811 Regular

POWER-HELIX
 model type
 AX911 Gold Anodized
 PX911 Regular

STAR-HELIX
 model type
 AX711 Gold Anodized
 SX711 Regular

SUPER-HELIX
 model type
 AX511 Gold Anodized
 RX511 Regular

JUNIOR-HELIX
 model type
 AX311 Gold Anodized
 JX311 Regular

GLEAMING GOLD ANODIZING GIVES YOU MORE TO SHOW!... MORE TO SELL!


New... new... new! *Gold* Colortennas with ALCOA Spec. fade-proof gold anodized finish that catches the eye and makes them buy.

NEW UNBREAKABLE "KRALASTIC" INSULATORS

You get the toughest, hardest, strongest insulators money can buy. Matchless electrical, physical and weathering properties for better performance all year, every year.

NEW RIGIDIZED REFLECTORS

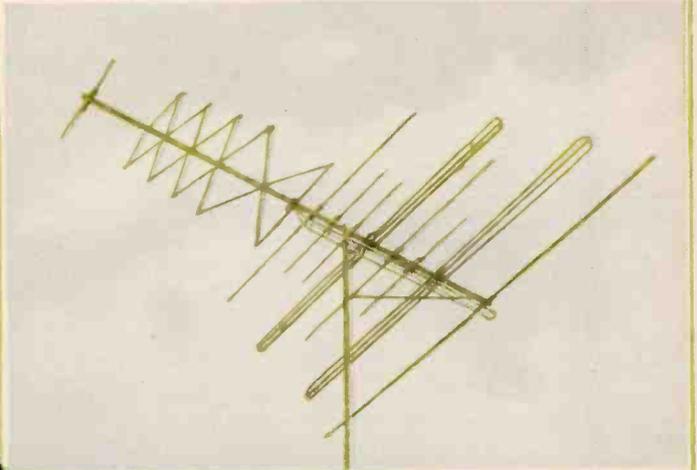Twice the strength—twice the rigidity. Every element over 30 inches long is now reinforced with 16 inch aluminum dowels in center. Never before so many dynamic selling features packed in one antenna.



THE FUSE IS LIT! *Get Set* FOR THE COLORTENNA BOOM *in 1958*

**IN PROFITS!
PERFORMANCE!
PREMIUMS!
PROMOTION!**



See your JFD distributor.

ELECTRONICS CORP.

Brooklyn 4, N. Y.

Pioneers in electronics since 1929

**New items
to save time,
make money**

**...literally hundreds of them,
in Centralab's
new Catalog 30**

Tells you what's new at your Centralab distributor. Keeps you up to date on the latest developments that make servicing of radio, TV, and electronic equipment faster and more profitable.

Shows hundreds of new, exciting items it pays you to know about — new values in Packaged Electronic Circuits — new volume controls — new ceramic capacitors — new switches — new transistor amplifiers.


Everything is arranged so that it's easy to find just what you're looking for.

Ask your Centralab distributor for your free copy. Or write us today.




Centralab A DIVISION OF GLOBE-UNION INC.
922J EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
G-958

ELECTRONICS

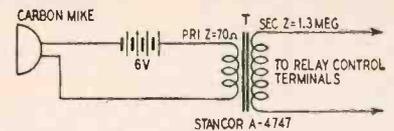

T—input transformer 370 ohms to 1.3 megohms (Stancor A-4747 or equivalent)
Carbon microphone
Battery—6 volts

Fig. 4—Sound-powered control for stand-by relay.

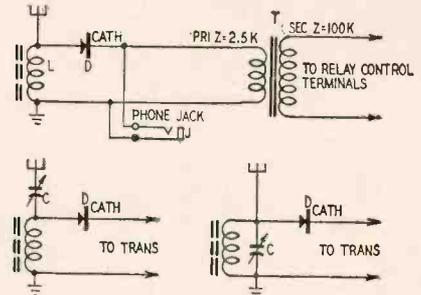

C—365- μ mf tuning capacitor
D—1N34 crystal diode
J—phone jack
L—ferrite-core antenna coil
T—input transformer (see text)

Fig. 5—Crystal-radio control circuits.

adjustment is critical. Tune the crystal set to a powerful station, using the headphones or, better yet, a high-resistance (20,000 ohms per volt) dc voltmeter, to get maximum output. If you use a voltmeter, disconnect the transformer while tuning as it shorts out the direct voltage. Series or parallel capacitance tuning (Fig. 5) may also help, depending on your antenna.

Finally adjust the sensitivity control so that the relay just closes on the loud audio signals and doesn't close at all when the station is detuned. After adjusting, unplug the headphones to get more output to the relay.

If left tuned to a particular station frequency, the relay circuit can turn on a receiver or sound an alarm when that station starts broadcasting.

Other applications

You can operate the relay circuit with many other controls—thermistors, capacitance circuits and wired wireless controls, for example. The only requirement is that they give voltage changes of at least 3 volts if dc or 4-volt peaks at not more than 5,000 cycles if ac. *Be sure that any control used is isolated from ground as the relay has an internal ground from the power line.*

The relay will work better on any low-output control if it is supplied from a dc source (top line Fig 2-a positive). Modify the main-gap limiting resistor (R_3 in Fig. 2-a) so the current is no more than 10 ma after the tube voltage drops to 75. The tube will then drive a less sensitive relay. If you use batteries for the power supply, the circuit becomes more dependable for small-signal triggering since line-voltage fluctuations are eliminated. Also, when using dc, no locking circuit and relay capacitor are necessary. Once energized, the relay will stay closed until the main-gap voltage is reduced. END



Bogen model RM-2, a crystal-controlled multiplex receiver.

THE FCC authorized multiplexing by FM broadcast stations two years ago, and since then several stations have gone into this field. It provides a way for a single FM station to transmit additional programs privately at the same time as regular public broadcasts. Multiplex transmissions cause no interference with the public or main FM channel. If you turn the dial of your FM receiver to a station that is multiplexing, you will hear the usual program on the public channel, with no trace of the multiplex transmission. However, if you are a subscriber with a multiplex receiver, you then would hear the special program being transmitted by the station's subchannel.

How it works

At the FM station, an FM subcarrier having a center frequency such as 41 kc is impressed pick-a-back on the main-carrier wave. This is accomplished in a special exciter unit of the FM transmitter by a slight shift in the phase of the frequency-modulated main carrier

When your editor first discussed this article with the author, Mr. Lewis feared that perhaps the subject was a bit premature and actually hesitated for some months. However, within days after the article was completed, a new FM station came on the air and disclosed it would transmit stereophonic programs by multiplex. Your editor's crystal ball was right on frequency. The station is WGHF at Brookfield, Conn., near the New York border. It is operated by W. G. H. Finch and A. J. Detzer, two retired Navy captains. Captain Finch pioneered FM and facsimile in New York City many years ago and now will pioneer stereo by multiplex. On the main-channel frequency of 95.1 mc, 20,000-watt power, they are broadcasting excellent high-fidelity programs. Of their two subchannels, one provides station income by carrying background music. The other will be combined with the main channel for stereocasting. WGHF has not yet released information on how listeners will be able to adapt their FM receivers to pick up the stereo channel. Inquiries may be addressed to WGHF at Brookfield, Conn.

*Multiplex Services Corp., New York, N.Y.

MULTIPLEXING and YOU

Multiplex systems allow simultaneous transmission of two or three programs on one FM channel

By DON LEWIS *

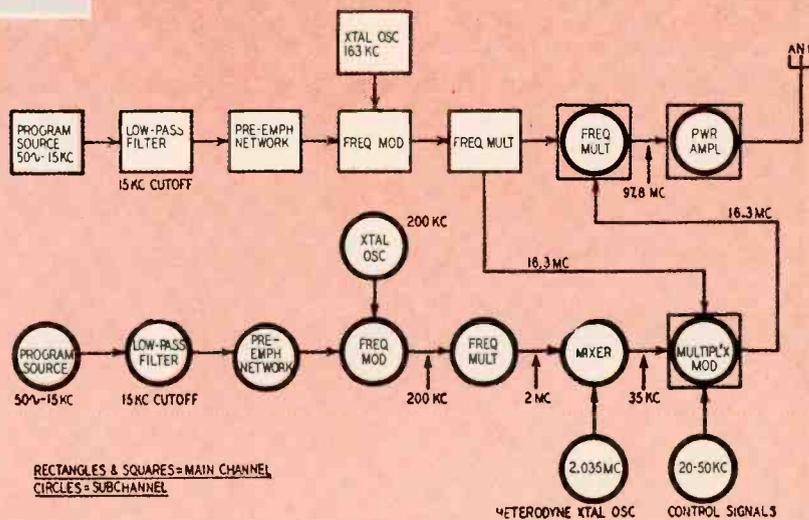


Fig. 1—Block diagram of a two-channel multiplex transmitter.

at a specific point in the frequency-multiplier chain of the transmitter (see Fig. 1). The subcarrier is impressed on the main carrier at a level such that the main carrier is frequency-modulated 10 to 20% by the subcarrier. The subcarrier, in turn, is frequency-modulated by the audio program signals associated with the multiplex service. The frequency deviation of the subcarrier usually is plus or minus 6 to 12 kc, depending on the type of system, transmission requirements and other factors. The frequency deviation of the main channel is reduced so that modulation is approximately 70% on program peaks, or about 3 db below the maximum modulation percentage permitted by FCC rules and regulations.

At the receiver, the main carrier is amplified and detected in the normal manner by a special FM receiver. This functions basically in the manner of conventional receivers but is designed throughout to provide maximum phase linearity.

A receiver with suitable performance characteristics is important. Any appreciable nonlinearity will increase the amount of intermodulation and introduce crosstalk in the subchannel from the main-channel signals.


In multiplex receivers now in commercial service (see Fig. 2), one or two stages of rf amplification are employed to give maximum sensitivity and increase quieting action. By a conven-

tional heterodyne method, using a crystal-controlled oscillator, the main FM carrier is beat downward to an intermediate frequency such as 10.7 mc. This if signal is usually passed through two or more if stages, each having good phase-linearity characteristics. The amplified rf carrier next goes through one or two limiter stages, also designed to minimize intermodulation due to nonlinearity. Then the FM signal is demodulated by a wideband discriminator with good linearity characteristics. From the main discriminator, the audio program signals, modulating the main carrier, may be passed through a standard de-emphasis network and audio amplifier to operate one speaker in a stereophonic system, for example. From the main discriminator, the multiplex subcarrier is fed through a bandpass filter which accepts subcarrier signals within a given subchannel frequency range and rejects signals of other frequencies. After the desired subcarrier has been filtered in this manner, it is amplified, limited and fed to an FM subcarrier demodulator whose function it is to convert the frequency variations in the subcarrier to audio program signals.

Following the demodulation process, audio-frequency signals from the subcarrier discriminator are applied to a low-pass filter which removes the residue of the subcarrier. Where hi-fi multiplex reception is required, the low-pass filter may be designed to cut off at a


The World's Most Extensive

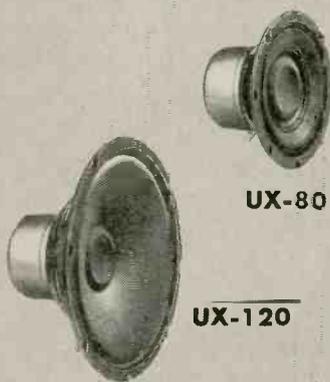Now you can select your Jensen loudspeaker



UX-80

UX-120

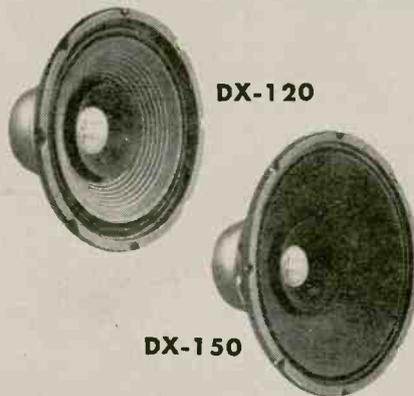

DX-120

DX-150



CX-225


CX-120

CX-150

CX-255

New Performance Levels in New Price Ranges

UNAX* SINGLE ELEMENT

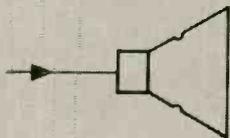


The new Jensen UX Series provides a new high in single-cone single voice coil loudspeakers at unusually low cost, actually outperforming comparable (and even more complex) units selling for much more. A listening test will convince you that this is a maximum value buy in hi-fi listening pleasure.

Of course, there are special design elements that enable us to give so much for so little. The cone is artfully dual acting, the center sector operating effectively for unusually extended highs, while the whole moves to reproduce the lows.

Withal, there is superb balance and cleanliness. And, if you choose, you can step up performance later with the inexpensive KTX-2 Step-Up Kit which substitutes a compression driver tweeter for the top.

UX-80. 3-in. Speaker. Net \$14.50
UX-120. 12-in. Speaker. Net \$19.50

DUAX* 2-ELEMENT SYSTEMS

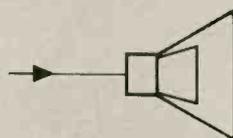


A step-up in the reproduction scale is the DX Series in which two carefully coordinated cones are driven by one voice coil. (Some call these "coaxials," but we reserve the name for still more elaborate systems and higher performance.)

The separate auxiliary radiator gives the designer a chance to attain a wider frequency range than with a single cone (albeit dual acting as in UX Series). The result is, with low cost, additional performance and added listening pleasure. We know of no similar speakers with equal sound, none with as high efficiency or as low distortion at anywhere near DX Series cost. Again you can step-up performance easily at anytime with KTX-2 Kit to substitute high-order compression driver tweeter operation at the high end.

DX-120. 12"; 1-lb. mag. Net \$25.50
DX-150. 15"; 1-lb. mag. Net \$35.50

COAXIAL 3-ELEMENT SYSTEMS

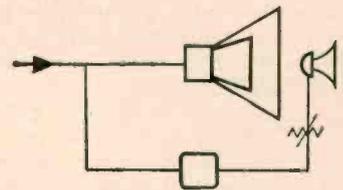

Still better than the "all paper" system with single voice coil is the use of a compression driver tweeter for the highs. The least expensive way to do this is to nestle a supertweeter coaxially inside the cone; it must cross over high in the frequency scale at 3500 to 4000 cycles. The third element is the diffusion radiator which shapes and disperses middle-high response. (Some call such speakers "Triaxial," though Jensen alone is entitled to use this registered name, applied by us to true 3-way speakers only.) Again, we guarantee more and better sound, cleaner hi-fi at lower cost, than all comparable speakers. And you can step up performance correctly and impressively with a real C.D. horn 600-4000 cps mid-channel (KTX-3 Kit) that leaves you with a real 3-way system.

12" Models. CX-120* \$49.50
CX-225 \$59.50
15" Models. CX-150* \$66.50
CX-255 \$76.50

*Denotes 1-lb. magnet; others 1 3/4 lbs.



SELECTING A HI-FI SPEAKER? YOU'LL WANT THESE HELPFUL, INFORMATIVE BOOKS

"How to Select a High Fidelity Loudspeaker." A comprehensive, authoritative manual covering all types of high fidelity loudspeakers and systems, their operating principles, performance and relative advantages. 24 pages, profusely illustrated. Write for Manual 1061. Price 25¢.

"Guide to Jensen High Fidelity Loudspeakers." Complete specifications and detailed descriptive information on all Jensen high fidelity loudspeakers and accessories. 24 pages. Send for Brochure 1021. Price 25¢.



High Fidelity Loudspeaker Line

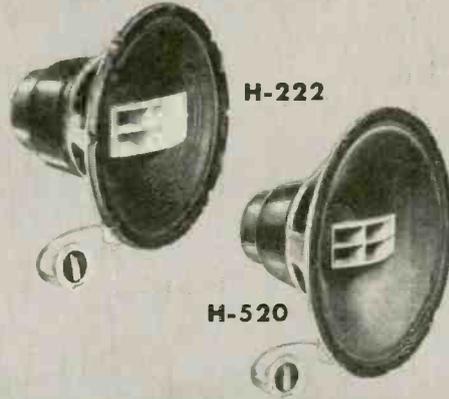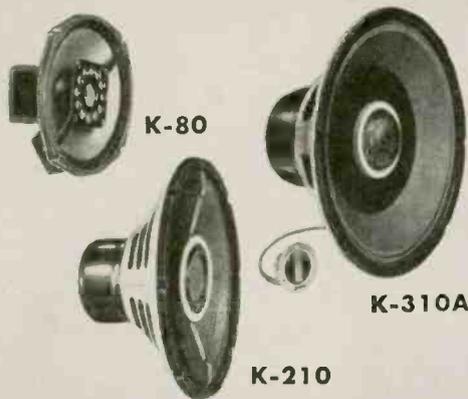from this new complete range of types and sizes.



...All with Traditional Jensen Quality

COAXIAL 2-WAY SYSTEMS

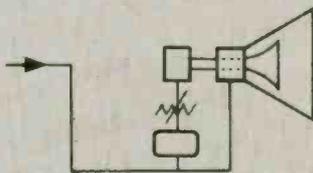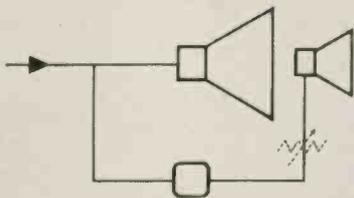

By using two completely independent (but carefully coordinated) speakers, each with its own magnetic system, voice coil and cone, the true two-way system spans the frequency range to obvious advantage in smoothness and extent, cleanness, low distortion and uniformity of angular dispersion.

Coaxial mounting makes them a convenient unitary package. Please note that we at Jensen use the term "coaxial" only in referring to a speaker with two completely independent systems.

Lowest in cost in the Jensen coaxial family is this fine group of speakers employing "cone" type direct radiator units for both tweeter and woofer. Available in 8, 12 and 15-inch models, they provide a maximum of value in true two-way system speakers.


K-80. Coaxial, 8-in. Net \$16.75
K-210. Coaxial, 12-in. Net \$27.50
K-310A. Coaxial, 15-in. Net \$39.75

The highest type of performance in the coaxial two-way loudspeaker is attained by the use of a compression-driver horn-loaded tweeter for the high end. When properly designed, there results an outstanding clarity, realism and instrumental separation not achieved by lesser designs. By adopting the expensive "thru bore" construction, the tweeter horn can be made long enough to operate at the lowest practicable crossover frequency, a very desirable feature for the very best sound.

In this manner, the very popular Jensen H-222 and H-520 give you the "tops" in fine coaxial performance. Crossover is at 2000 cycles. Though many will see no need to, you can step-up performance to full three-way with KTX-1 Range-Extender Supertweeter Kit.

H-222. Coaxial, 12-in. Net. \$62.50
H-520. Coaxial, 15-in. Net. \$79.50

TRIAxIAL* & TRIAX* 3-WAY SYSTEMS

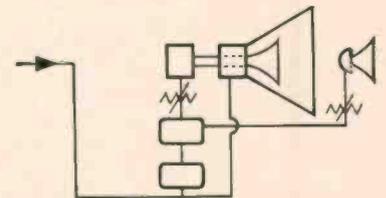

The true three-way speaker system divides the range in three parts with three electrically and acoustically distinct and independent elements, each designed to perform near-ideally in its portion of the range.

The famous G-610A TRIAXIAL was the first (and until our new G-600), the only speaker made in accordance with this concept! It employs a heavy woofer and two compression driver horn-loaded elements for m-f, and h-f channels. (The woofer cone acts as the final section of the m-f horn.) Its performance is so outstanding that it easily rates as the world's most wanted hi-fi speaker.

Now, for those who would like a G-610A, but are dissuaded by the price tag, Jensen announces the new lighter, less expensive G-600 TRIAX with similarly outstanding features and performance.

G-610A. Triaxial, 15". Net \$252.75
G-600. Triax, 15". Net \$129.50

Jensen MANUFACTURING COMPANY
 6601 South Laramie Ave., Chicago 38, Illinois

SEND FOR FREE DATA
 SHEET 165-B

RADIO

point slightly above 15,000 cycles. From the low-pass filter, the audio signals on the multiplex channel are amplified and appear at the loudspeaker.

Multiplex uses


Up to now, virtually all FM multiplexing by broadcast stations has been for supplying background music in restaurants, hotels, factories, offices and other commercial establishments. Reception by nonauthorized persons is not intended and, in fact, any commercial unauthorized reception is considered to be a violation of the basic protective provisions of Section 605 of the Communications Act, which assures privacy for users of radio or wire services.

Background music presently is the most profitable and obvious use for multiplex although this transmission method is not limited to that service alone. Like any other new medium, its potentials and applications will increase as the art matures and expands. This is where stereophonic broadcasting comes in.

Until now, stereophonic music has been broadcast by transmitting the stereo programs through two stations, usually the AM and FM outlets of the same broadcasting company. Two receivers are required, one AM and one FM. With multiplexing a single FM station can be used for both stereo channels by transmitting one stereo signal on the public channel and the other on a multiplex channel. The listener needs only one FM receiver with a multiplex adapter.

The quality of stereophonic programs by multiplex was demonstrated for the first time in 1950 by William S. Halstead of Multiplex Development Corp. and later by Major Armstrong, shortly before his death. Special programs by an instrumental trio were transmitted from the studio of FM broadcast station KE2XKH in downtown Manhattan, New York City. Reception tests were at the Reeves Sound Studios, in mid-Manhattan, for representatives of the broadcast industry, FCC, other Government agencies and the press. In these first transmissions, the presence effect of the artists was remarkable, with listeners being able to sense the relative location of the different instruments of the trio and the movement of a singer as she moved between microphones. Since these early tests, additional stereo transmissions have been conducted with two 15,000-cycle channels. These numerous tests showed that stereophonic transmission by multiplex is not only practical but offers a superior way of rendering this high-fidelity service.

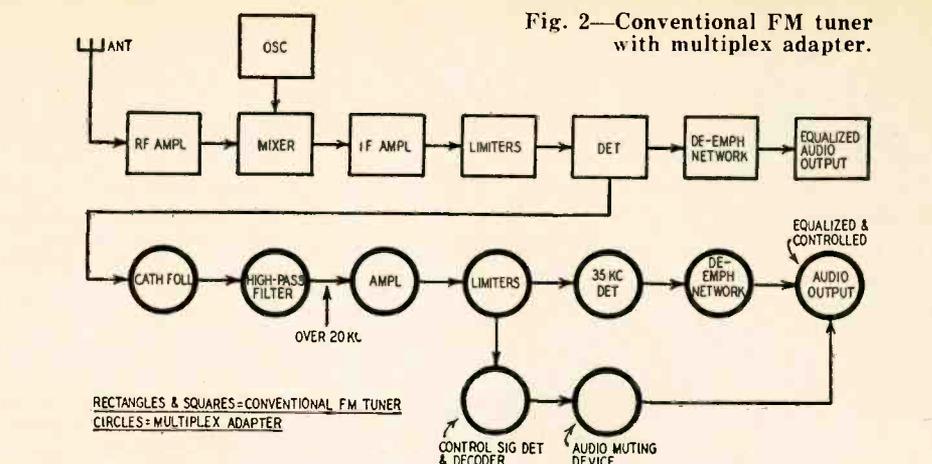Following these demonstrations, the FCC was petitioned to permit the use of multiplexing by FM broadcast stations. It required nearly 5 years for authorization, due to the question of the legality of adding a private point-to-point type of service to a public broadcast channel. This cuts squarely across the basic definition as to what constitutes a public broadcast service. (Simi-



larly, the present subscription TV controversy concerns using a public-service channel for a nonpublic function.)

Approval of the multiplex petition recognized that multiplexing would permit certain FM stations to continue for a time to render specialized program services by what is termed the "simplex" transmission method. These stations were profitably engaged in transmission of special background music on their public channels, with commercials and other nonmusic material being deleted automatically by ultrasonic control or beep signals.

Simplexing provided many FM stations with enough revenue to weather the economic storms of this broadcast medium. However, the FCC considered that music directed to subscribers was not a public service as called for by FCC rules and regulations. Multiplexing permits these stations to move their simplex operation from the main to a subchannel. They can then derive revenue from sponsored main-channel programs as well as draw income from subscribers to the subchannel service.

As presently visualized, the multiplex stereophonic receiver would be available in either of two forms—a specially designed receiver with built-in multiplex circuitry or a multiplex adapter which would attach to your present receiver. There would be separate volume controls and you could tune in the main channel of any station or flick a switch to bring in the subchannel. If stereophonic music is broadcast, both could be picked up simultaneously.

Existing FM receivers

Ordinary FM radios were not engineered for multiplex reception. However, most of these receivers can be upgraded by the addition of minor parts or circuit changes. An adapter then can be attached without serious crosstalk problems. Service technicians could do this. Suitable multiplex kits containing the necessary components and a schematic could be packaged and stocked by radio shops. A receiver with built-in multiplex will probably be in the price range of present good-quality FM receivers. A multiplex adapter for a home FM receiver will cost about the same as an inexpensive FM tuner.

Fig. 2—Conventional FM tuner with multiplex adapter.

Initially stereophonic broadcasts will be a repetition of the chicken-and-egg process experienced in the development of television and other forms of broadcasting. After all, receivers are not automatically sold before a station begins broadcasting. Like the birth and growth of television, a station must initiate this broadcasting to a ghost audience with demonstrations to interest the general public in buying receivers.

The growing number of excellent stereophonic tapes now on the market will be the basic material for programs. Many broadcasts now picked up live would also be broadcast stereophonically, thereby improving the quality of such transmissions. Stereophony would add a great deal to the realism and dramatic effect of plays and other shows.

In certain parts of the United States where there are relatively few radio stations, it is conceivable that multiplexing may be used primarily for providing a variety of programs rather than for stereophony. At present, for example, many daytime-only stations provide evening programs on their affiliated FM transmitter. In some areas, it is very difficult to provide static-free AM programming at any time of day or night. The listener's choice becomes severely limited. Since such places cannot support a great number of FM stations, it might be more practical for an FM station to perhaps provide sports programs, network programs and other nonmusical shows on the main channel and transmit music and news on a subchannel. This way, one station could have twice as many programs as at present, twice as much advertising income, twice as many listeners—and its technical operating expenses would still be about the same as before. Such an arrangement would not prevent providing stereophonic music.

Although there are other excellent uses for this development, which can all be in our future, the primary thought is that multiplex is with us now. Radio stations need only begin multiplexing a service such as stereophonic programs. The public has already given a welcome acceptance to stereophony, so there will undoubtedly be a similar response when it is initiated in this new multiplex entertainment medium. END

500-million-mc TRANSCIEVER

*This super-high-frequency
communications
system uses
cesium-vapor lamps*

By HAROLD PALLATZ




NO license of any kind is required for this two-way communications system. The waves transmitted by the cesium vapor lamps are only some 40 millionths of an inch long (about 500 million megacycles per second). These frequencies act more like light waves than radio waves and in fact are only slightly removed from the visible spectrum. The waves travel in straight lines and distance is limited only by the power of your equipment or the curvature of the earth, whichever comes first.

Circuit hookup is very simple and is actually easier than for regular transmitters (see diagram). All you need is an audio amplifier, dc power supply (18 volts at 3 amperes) and a cesium vapor lamp. The lamp is modulated by the audio amplifier output. For greater distance a parabolic reflector can be placed behind the lamp. The reflector concentrates the waves in a small highly directional beam and directs waves that would ordinarily be lost as stray radiation. For night work where no light should show at all, the faint pink glow of the lamp may be eliminated with an infra-red filter.

The receiver section consists of the same amplifier with a speaker replacing the lamp in the output and a phototube replacing the microphone at the input. A dpdt toggle switch changes from "transmit" to "receive" and the entire system may be used as a transceiver. (The components of my receiver are simply soldered to the photocell socket terminals and receiver and mike are alternately plugged into the amplifier.)

Voice transmission will be virtually

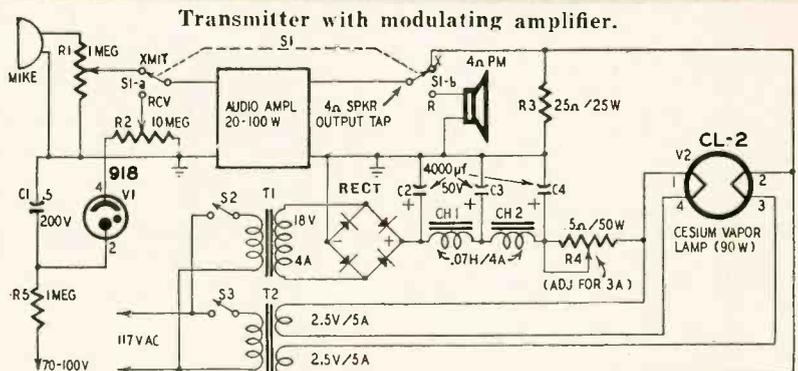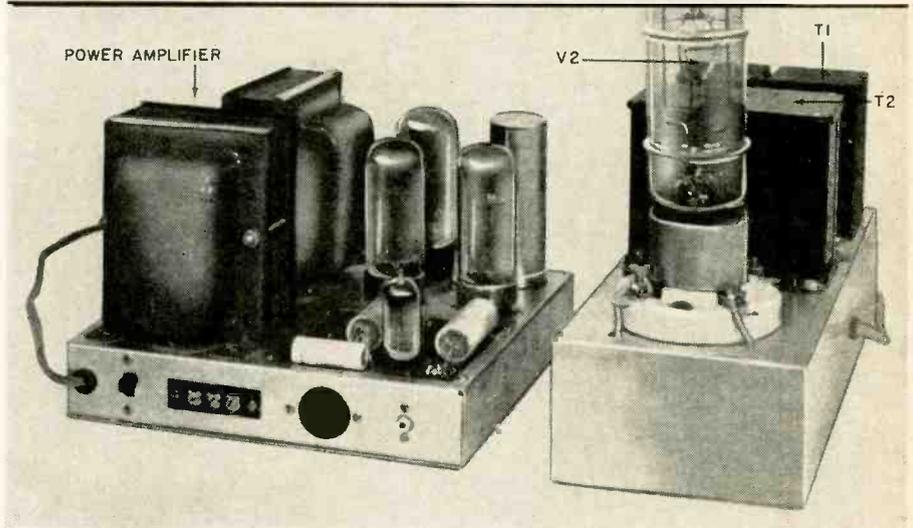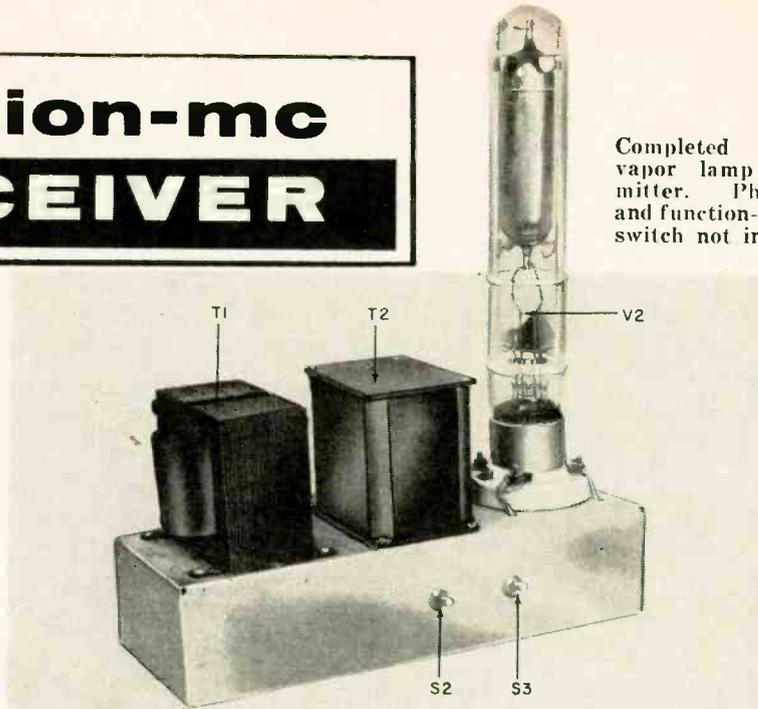Completed cesium-vapor lamp transmitter. Phototube and function-selector switch not installed.




- R1—pot, 1 megohm for crystal mike, matching value for magnetic mike
- R2—pot, 10 megohms
- R3—25 ohms, 25 watts
- R4—5 ohms, 50-100 watts
- R5—1 megohm, 1/2 watt
- C1—0.5 µf, 200 volts
- C2, 3, 4—4,000 µf, 50 volts; two 2,000-µf 50-volt capacitors in parallel
- *CH1, 2—.07 h, 4 amp
- S1—spdt toggle
- S2, 3—3-spt toggle
- *T1—rectifier transformer, 117-volt primary; 18-volt 4-amp secondary
- *T2—filament transformer, 117-volt primary;

- two 2.5-volt 5-amp secondaries
- V1—918 phototube
- *V2—cesium vapor lamp, 90 watts
- *RECT—28 volts, 4 amps, full-wave bridge, selenium
- Speaker—4-ohm voice coil
- Socket—jumbo 4-pin bayonet
- Amplifier—20-100-watt output. Must have 4-ohm output winding that can carry 3-amp dc
- Mike—crystal or magnetic
- *Infra-red filter—used only where no glow from vapor lamp is to show
- *These items obtainable from Barry Electronics Corp., 512 Broadway, New York 12, N.Y.

Circuit of the transceiver.

CHANGER OR TURNTABLE?

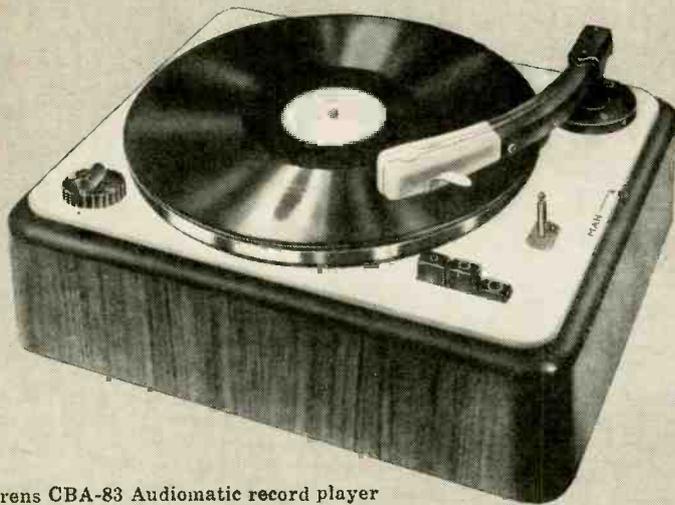

Thorens CBA-83 Audiomatic record player

You get the best features of both in the Thorens CBA-83

Not a changer, not a conventional turntable, but so easy to use you can play it in the dark!

Place your precious records, by hand as gently as you please, on the 12-inch turntable of the Thorens Audiomatic CBA-83. Press the button—there's one for 7, 10, or 12-inch records. That's all you do!

A precision mechanism takes over and lowers the stylus gently and silently into the lead groove. No cueing light required. No stooping to look for the stylus point. No sighting along a cueing mark. No danger of scraping over the first few grooves. You don't need a steady hand—your hand need never touch the tone-arm at all!

Easy playing is just one feature of the Thorens Audiomatic. Take the motor, for example. Like all Thorens units, the Audiomatic is powered by a famous Swiss-precision direct-drive motor to assure silent opera-

tion. Accurately machined, electronically-balanced fast-rotating parts hold wow, flutter to less than ½%.

Ask for the Thorens CBA-83 Audiomatic record player at your hi-fi dealer's today! Its performance will surprise you.

And don't forget to send for free booklet "Hi-Fi and Your Budget." Write Thorens Company, Dept. E10.7, New Hyde Park, N.Y. 7.8



CB-33 manual player (above) starts when tone arm is lifted, shuts off silently, automatically at end of record. Has same Swiss-precision motor as CBA-83. From changer to transcription turntable, there's a Thorens for every need.



ONE YEAR GUARANTEE. Now all Thorens units are covered by a 1-year guarantee—4 times as long as the usual 90-day electronic equipment guarantees! Ask your hi-fi dealer about this,

THORENS

SWISS MADE PRODUCTS
HI-FI COMPONENTS • LIGHTERS
SPRING-POWERED SHAVERS
MUSIC BOXES
NEW HYDE PARK, NEW YORK

RADIO

distortion-free as the lamp response is from dc to 10,000 cycles. Clarity will depend mainly upon your audio system. Static and other transmission noises in regular radio-wave transmitters will be almost nonexistent. About the only noise you are likely to run into is possible pickup from a street light or other bulb operating on ac. This is minimized by the directivity of the units. Normal daylight does not have a rapidly changing light level. About the only thing daylight will do is put a bias on the phototube (never point a phototube at the sun), which in some cases will require a readjustment of the input gain control. Daylight transmission may also require more shielding of the phototube, particularly on long-distance transmissions, to prevent the weaker signals from becoming completely masked out.

Dc power supply


It is very important to have a hum-free dc power supply, just as it is in a transmitter intended for speech. The diagram shows the circuit of a typical unit. A 18- or 24-volt aircraft battery (lead storage type) that will stand 3 amperes of constant drain can also be used.

This will give you hum-free results but has the inconvenience of requiring constant attention for recharging and refilling. Since cesium vapor lamps have a negative resistance characteristic, some means of limiting the maximum current must be used. For this we use a slide type wirewound resistor.

In use, the two filaments of the lamp are lit for about a minute (up to 15 minutes on breaking in a tube for the first time). *Do not turn on the B supply until the filaments have been on for a minimum of 30 seconds.* An arc is struck by tapping on the microphone (this causes a high-voltage peak across the lamp which ignites the arc). The slider is moved on the resistor until approximately 3 amperes are flowing through the lamp. The filaments can then be turned off and the plate current should be about the same. If you have difficulty in starting your lamp, you can tilt it slowly until it starts.


Since the penetration of infra-red waves is slightly different from light waves, you will still be able to communicate even under conditions of poor visibility due to fog. The size of the water-vapor molecule is the restricting agent. Water-vapor particles smaller than the wavelength of our transmitter are relatively transparent. Large vapor particles will in some cases completely stop the rays.

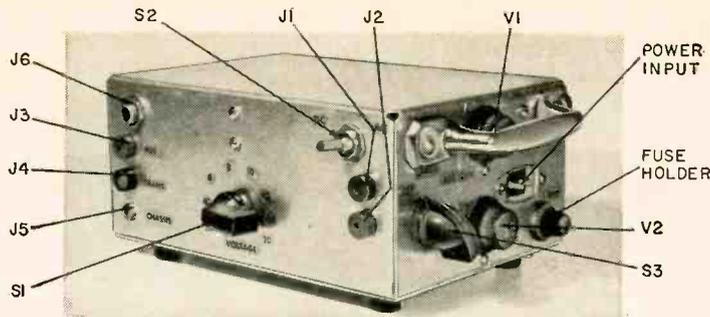For code enthusiasts, the microphone may be replaced with an oscillator and a telegraph key. Communication will be the same as with low-frequency radio waves but will have the advantages of simpler construction and no code speed requirements. When your code speed does pick up from these practice sessions it will be easier to obtain higher-grade licenses. **END**



The low-voltage supply. Transistors are mounted on front of case.

All parts fit easily into aluminum case.

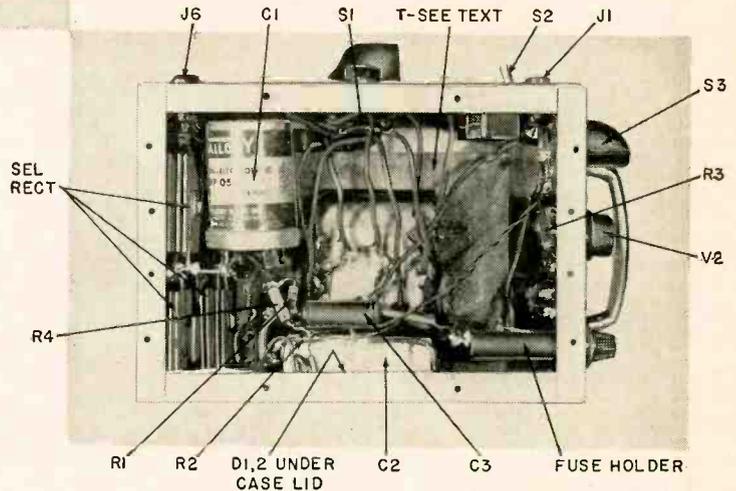

transistor LOW-VOLTAGE SUPPLY

Need ac, dc, pure dc or regulated dc? Then you want this transistorized device

By I. QUEEN
EDITORIAL ASSOCIATE

ALMOST every experimental laboratory, individual researcher or service shop needs some kind of low-voltage power supply. This power source provides three types of output: ac, regular dc and pure dc. The ac is suitable for filament supplies, motors and relays. Regular dc is for low-hum filament circuits, small dc motors and relays, battery charging, electroplating and wherever a 5% ripple can be tolerated. The pure dc source is actually a battery eliminator as its ripple is less than 0.1%. It is excellent for audio circuits using power transistors and can energize portable transistor radios. Pure dc is available either as *unregulated variable voltage* or as *regulated 12.6 volts*.

Except for the regulated output, the voltage is variable in small steps. The ac has a maximum of 19–20 volts at 3 amps, dc the same voltage at about 2 amps continuous. The *pure* dc delivers 14 volts maximum at 1 amp. If more is drawn the voltage drops. The load is always insulated from the line. Peak-to-peak ripple at full output is less than 10 mv. Note that this is the *peak-to-peak* value observed on a scope. The rms value is far below this, and is therefore well below 0.1%. The pure dc therefore closely approaches a battery supply.

None of the circuits is critical in any way. You don't have to use components identical to those described here and you don't need to include *all* the circuits. Perhaps you don't want or need the *regulated* feature or maybe you can do without a *variable* voltage. It's

easy to adapt this device to fit your own needs.

The ac circuit

A tapped transformer secondary provides the variable voltage output. Three center-tapped filament transformers, each 6.3 volts, are connected in series to provide a total of 19 volts (see Fig. 1). Each transformer should be rated at 3 amps. These transformers are common radio items.

To select voltage, a tap switch is needed. Grayhill type 5006 is excellent for the purpose since it has six terminals, is tiny and can handle up to 5 amps.

The transformer shown in the photos is an old model-train type which happened to be available. It was removed from its metal case (which was ready to fall apart) and the tapped leads connected to the Grayhill switch. It provides variable output up to 14 volts, in steps of 2 volts, plus a maximum terminal of 20 volts. It is, therefore, nearly equivalent to a series of three filament transformers. If you have such a transformer well and good, but

the filament units are electrically equivalent and much easier to mount in the box.

When switching ac voltage, it is preferable to rotate the switch to the desired value *before* connecting the load. The switch handles 5 amps continuously but is rated to *break* much less current.

For easy manipulation and good appearance you may wish to mark each voltage tap as I did. The ac output is led to insulated pin jacks on the front of the box. Green jacks were chosen to color-code the ac.

Regular dc circuit

When converting ac to dc at high current, we are faced with two problems: rectification and filtration. The first is solved by using low-voltage bridge rectifiers. The second problem is partly solved by a large capacitance (C1) across the output terminals. Good filtering is difficult without a choke coil capable of carrying high currents. Such coils are not regular radio components and do not even appear in radio catalogs, other than those issued by a few firms specializing in battery chargers, eliminators and other high-current supplies. For this reason we settled for 5% ripple.

The ac voltage (selected by the rotary switch) is fed to selenium rectifiers. The diagram shows a single bridge but actually three are used in parallel, to increase current capacity. Each bridge may be a Federal 1017 or Sarkes-Tarzian 604-B. Either can deliver 600 ma continuously. A total of at least 1.8 amps may be drawn continuously when three bridges are connected in parallel. For shorter periods,

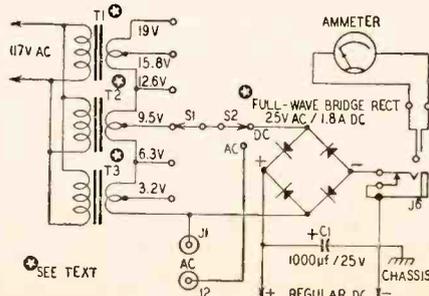


Fig. 1—Ac and regular dc circuit.

Model TD-55 — Terms:
\$6.95 after 10 day trial then
\$5.00 per month for 4 months.

OPERATING INSTRUCTIONS
FOR MODEL TD-55
TUBE TESTER



Model TV-12 — Terms:
\$22.50 after 10 day trial then
\$10.00 per month for 5 months.

Model TV-40
— Terms: \$3.85
after 10 day trial
then \$4.00 per
month for 3
months.



Model TW-11 — Terms:
\$11.50 after 10 day trial then
\$6.00 per month for 6 months.

SHIPPED ON APPROVAL NO MONEY WITH ORDER NO C.O.D.

Superior's New Model **TD-55** EMISSION TYPE **TUBE TESTER**

FOR

The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester.
The Professional Serviceman, who needs an extra Tube Tester for outside calls.
The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by:

1. Simplification of all switching and controls.
2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket. It is impossible to insert the tube in the wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system. The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin or even the "top-cap."

Checks for shorts and leakages between all elements. The Model TD-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. This is important, especially in the case of an element terminating at more than one pin. In such cases the element or internal connection often completes a circuit.

Elemental switches are numbered in strict accordance with R.M.A. specification. One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

Complete with carrying case.....

\$26⁹⁵
NET

Superior's New Model **TV-40** **PICTURE TUBE TESTER**

Not a Gadget—Not a Make-Shift Adapter, but a **Wired Picture Tube Tester** with a **Meter** for Measuring Degree of Emission—at Only **\$15.85**

Of course you can buy an adapter for about \$5—which theoretically will convert your standard tube tester into a picture-tube tester; or a neon type instrument which sells for a little more and is supposed to be "as good as" a metered instrument. Superior does not make nor do they recommend use of C.R.T. adapters or neon gadgets because a Cathode Ray Tube is a very complex device, and to properly test it, you need an instrument designed exclusively to test C. R. Tubes and nothing else.

Tests ALL magnetically deflected tubes . . . in the set . . . out of the set . . . in the carton!

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Test for open elements.

EASY TO USE: Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (ion trap need not be on tube). Throw switch up for quality test . . . read direct on Good-Bad scale. Throw switch down for all leakage tests.

Only.....

\$15⁸⁵
NET

Superior's New Model **TV-12** TRANS-CONDUCTANCE **TUBE TESTER**

TESTING TUBES

- Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.
- NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.
- SAFETY BUTTON—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.
- NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY. Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

Extra Feature

Model TV-12 Also Tests Transistors!

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.
Housed in hand-rubbed oak cabinet.....

\$72⁵⁰
NET

Superior's New Model **TW-11** STANDARD PROFESSIONAL **TUBE TESTER**


- Tests all tubes, including 4, 5, 6, 7, Octal, Lockin, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.
- Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.
- The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
- Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

NOISE TEST: Phone-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE: SEPARATE SCALE FOR LOW-CURRENT TUBES. Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types. Housed in hand-rubbed oak cabinet.....

\$47⁵⁰
NET

USE APPROVAL FORM ON NEXT PAGE ➔

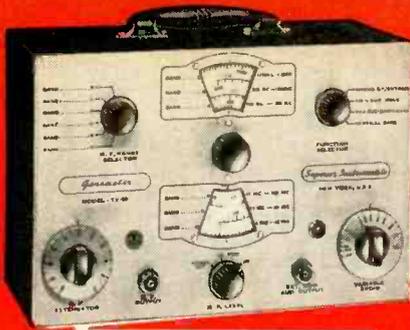

Model TV-50 — Terms:
\$11.50 after 10 day trial then
\$6.00 per month for 6 months.



Model 76—Terms: \$6.95
after 10 day trial then \$5.00
per month for 4 months.



Model 770-A — Terms:
\$3.85 after 10 day trial then
\$4.00 per month for 3 months.



Model 670-A — Terms:
\$7.40 after 10 day trial then
\$3.50 per month for 6 months.

TRY FOR 10 DAYS

before you buy! **then** if satisfactory pay in easy, interest free, monthly payments. See coupon below.

Superior's New Model TV-50 **GENOMETER**

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

R. F. SIGNAL GENERATOR: 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.

CROSS HATCH GENERATOR: Pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.

MARKER GENERATOR: The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.)

Complete with shielded leads.....

\$47⁵⁰
NET

Superior's New Model 670-A **SUPER-METER**

A Combination VOLT-OHM MILLIAMMETER PLUS
Capacity, Reactance, Inductance and Decibel
Measurements.

ADDED FEATURE: Built in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.

SPECIFICATIONS:

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
- RESISTANCE: 0 to 1,000/100,000 Ohms to 10 Megohms
- CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Good-Bad scale for checking quality of electrolytic condensers.)
- REACTANCE: 50 to 2,500 Ohms 2,500 Ohms to 2.5 Megohms
- INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
- DECIBELS: -6 to +18 +14 to +38 +34 to +58

Complete with test leads.....

\$28⁴⁰
NET

Superior's New Model **76**

- ✓ IT'S A CONDENSER BRIDGE
- ✓ IT'S A RESISTANCE BRIDGE
- ✓ IT'S A SIGNAL TRACER
- ✓ IT'S A TV ANTENNA TESTER

SPECIFICATIONS

✓CAPACITY BRIDGE SECTION 4 Ranges: .00001 Microfarad to .005 Microfarad; .001 Microfarad to .5 Microfarad; .1 Microfarad to 50 Microfarads; 20 Microfarads to 1000 Microfarads. Will also measure the power factor of all condensers from .1 to 1000 Microfarads.

✓RESISTANCE BRIDGE SECTION 2 Ranges: 100 ohms to 50,000 ohms; 10,000 ohms to 5 megohms.

✓SIGNAL TRACER SECTION With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc.

✓TV ANTENNA TESTER SECTION Loss of sync., snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? Locates a break in any TV antenna and measures the location of the break in feet from the set terminals.

Complete with R.F. and A.F. probes and test leads.....

\$26⁹⁵
NET

Superior's New Model 770-A **POCKET-SIZED VOLT-OHM MILLIAMMETER**

● USING THE NEW "FULL-VIEW" METER 71% MORE SCALE AREA—Occupies exactly the same space used by the older standard 2 1/2" Meters, yet provides 71% more scale area. As a result, all calibrations are printed in large easy-to-read type and for the first time it is now possible to obtain measurements instead of approximations.

● Compact—measures 3 1/8" x 5 7/8" x 2 1/4". ● Uses "Full View" 2% accurate, 850 Microampere D'Arsonval type meter. ● Housed in round-cornered, molded case. ● Beautiful black etched panel.

Specifications: 6 A.C. VOLTAGE RANGES: 0-15/30/150/300/1500/3000 Volts. 6 D.C. VOLTAGE RANGES: 0-7.5/15/75/150/750/1500 Volts. 2 RESISTANCE RANGES: 0-10,000 Ohms, 0-1 Megohm. 3 D.C. CURRENT RANGES: 0.15/150 Ma., 0-1.5 Amps. 3 DECIBEL RANGES: -6 db to +18 db, +14 db to +38 db, +34 db to +58 db.

Complete with test leads.....

\$15⁸⁵
NET

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-391, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance or interest charges added. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

Name

Address

City Zone State

All Prices net. F.O.B. N.Y.C.

- Model TW-11 Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.
- Model 76 Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00
monthly for 4 months.
- Model TD-55 Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00
monthly for 4 months.
- Model TV-50 Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.
- Model TV-40 Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00
monthly for 3 months.
- Model 670-A Total Price \$28.40
\$7.40 within 10 days. Balance \$3.50
monthly for 6 months.
- Model 770-A Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00
monthly for 3 months.
- Model TV-12 Total Price \$72.50
\$22.50 within 10 days. Balance \$10.00
monthly for 5 months.

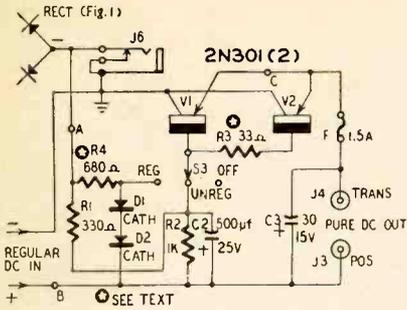


Fig. 2—Circuit for changing regular dc into pure dc.

up to 3 amps will not cause undue rectifier heating.

Each rectifier has four elements and its terminals are coded for easy identification. To parallel them, simply connect like terminals.

The regular dc output is connected to a pair of pin jacks. The positive one *must* be insulated and may be colored red. The negative terminal is not insulated. As shown in the diagram, the negative output of the bridge is tied to the chassis (through a phone jack). The jack (J6) is normally closed and permits inserting a meter in series with the dc power so that current may be monitored or checked. The meter will measure the total dc drawn from the unit.

No line switch has been used in this device but you can quickly shut off its output without removing the cord. If you are using the dc terminals, switch (S2) to ac. Conversely if you are using ac, switch (S2) to dc. A line switch may be installed in the line cord, of course.

The 5% ripple compares favorably with outputs of commercial dc power supplies used for battery charging, energizing solenoids, etc. It is even suitable for powering transistor radios and other transistor circuits where slight hum modulation is not serious.

Pure dc output

Generally we rely on some L-C combination to do a good filtering job. At low voltages, capacitance is no problem. For example, a 1,000- μ f 25-volt unit for C1 is small and cheap. Coils are another story. A coil to handle 1.5 amps or more is a special item. It would be bulky and expensive, for it must be wound with heavy wire.

You are probably aware that a transistor *saturates* when supplied with sufficiently high collector voltage at rather low base current. For example, increasing collector voltage from 6 to 8 (33%) may produce a rise in current from 0.5 to 0.52 amps (4%). If the bias is nearly pure dc, the output will also be pure dc, despite considerable ripple in the collector supply voltage.

Fig. 2 shows the circuit for obtaining pure dc from regular dc. For unregulated (and variable) voltages switch S3 is thrown to UNREG.

Two RCA 2N301 transistors are used to filter the output. The bases of V1 and V2 are fed through an R-C


network that easily eliminates much of the ripple (since current is low in this circuit). The load is connected in the emitter returns. Measurement shows approximately 800-mv peak-to-peak ripple between points A and B. Yet with full load, output ripple is less than 10 mv peak to peak, almost too small to detect on a sensitive scope.

It is unlikely that the transistors you use will be matched perfectly, so one will tend to do more than its share in handling the current. For this reason a resistor is needed in series with the base of the more efficient transistor. This resistor (R3) is shown as 33 ohms, but you may wish to experiment to find the correct value for your own transistors. To do so, plug a meter into J6 to measure total current. Also, temporarily cut the lead to one emitter (at C) and insert another ammeter here. This meter will

flange (collector connection) of each transistor thus returns to negative potential, and the metal case serves as a heat sink. On the inside of the box, a nine-pin miniature socket plugs onto the transistor pins. Use pin 5 for the base and pin 9 for the emitter of each transistor. For convenience, each socket may also be screwed down to the box from the inside. In this way you may remove either transistor at any time (for test or temporary use elsewhere) merely by removing the machine screws and unplugging the transistor. For convenience, each socket may also be screwed down to the box from the inside. In this way you may remove either transistor at any time (for test or temporary use elsewhere) merely by removing the machine screws and unplugging the transistor.

Using the power supply

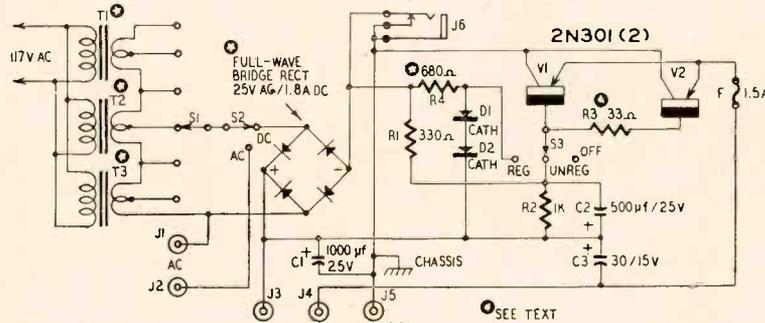When operated near maximum output, the transistors will become warm to the touch, but they should never be too hot to hold. Both should be at



- R1—330 ohms
- R2—1,000 ohms
- R3—33 ohms, see text
- R4—680 ohms, see text
- All resistors 1/2 watt unless noted
- C1—1,000 μ f, 25 volts, miniature electrolytic
- C2—500 μ f, 25 volts, miniature electrolytic
- C3—30 μ f, 15 volts, miniature electrolytic
- D1, 2—Regulator diodes (Texas Instruments 652C8)
- F—1.5 amps
- J1, 2, 3, 4—pin jacks, insulated
- J5—pin jack, uninsulated
- J6—phone jack, normally closed
- S1—single pole, 6 position, rotary (Grayhill 5006 or equivalent)
- S2—spdt, toggle
- S3—single-pole 3-position rotary
- T1, 2, 3—filament transformers: primary 117 volts; secondary, 6.3 volts, 3 amps
- V1, 2—2N301
- RECT—Bridge, 2 amps, 25 volts (Federal 1017 or equivalent) (3 25-volt 600-ma bridges in parallel)
- Fuse holder
- Sockets, 9 pins, miniature (2)
- Case, 3 x 5 x 7 inches
- Knobs
- Miscellaneous hardware

Fig. 3—Complete power supply circuit.

measure input to only one transistor, so it should indicate approximately half the total current shown by the other ammeter. R3 is placed in series with the base of the transistor supplying more than its share of power (V2 in this case). Choose R3 so that V1 and V2 divide the load equally. This should be done while nearly maximum current (for example, 1.5 amps) is drawn.

The bias filter network R1, R2, C2 is not critical. R1 affects output and ripple to some extent. If reduced in value, it provides greater output but tends to raise the ripple. R2 controls regulation and output. If its value is decreased, the output drops while regulation (output voltage vs. load current) improves slightly. The values for R1 and R2 shown in Fig. 2 were found to be optimum. A 1.5-amp fuse protects the transistors.

The photos show how the transistors mount directly to the case. The metal conducts heat from the transistors, keeping their temperature to a minimum. Each 2N301 is mounted with a pair of 6-32 machine screws. The

nearly the same temperature if they are sharing the load equally. At a flange temperature of 80°C, a 2N301 can dissipate up to 7.5 watts so it is ideal for the application described here.

Regulated dc

The unregulated supply provides nearly 18 watts of pure dc, and since the output is variable it can be adjusted for the load. Sometimes, however, a load fluctuates considerably, yet it is desired that the voltage remain nearly constant. A Class-B amplifier is such a load. When switched to REG, the circuit of Fig. 2 delivers a regulated voltage.

Two silicon reference diodes, Texas Instruments 652C8, are connected in series. These are rated at 6.3 volts each, so the total regulated voltage will be approximately 12.6. Actually, Texas Instrument diodes are available in steps of 0.1 volt so you can use any type that regulates close to 6 volts.

R4 controls current through the diodes and may need careful selection. With the load terminals open, maxi-

RADIO

mum diode current should not exceed 22 ma. On the other hand, a value of current that is too low will drop the available load current that can be regulated. When a load is connected, there will be a drop in diode current. This is because base current into the transistor opposes current flow through the diodes and R4. As the load current rises, the diode flow will fall until, at 6 ma or less, there is no regulating action.

A maximum regulating current of approximately 1.25 amps is available. No-load output will be approximately 12.5 volts. At 1.25 amps, the voltage will drop to slightly more than 11. For minimum ripple, the load should not exceed about 1 amp and the voltage will be 11.5.

The complete diagram of this power supply is shown in Fig. 3. To use it, first switch S2 to ac or dc as desired, then plug the load leads into the correct jacks. If regular voltage is to be used, connect to J3 and J5. For transistor filtered voltage, use J3 and J4.

The transistor switch S3 must be set as desired: regulated or unregulated. The OFF position is selected when the transistors are not being used, when the load requires ac or regular dc: END

CORRECTION

In the parts list for the TV sound tuner (June, 1957, page 46) the dimensions of the forms for L1 and L2 are erroneous. The forms (Cambridge Thermionic Corp. type LS3 or equivalent) are $\frac{3}{8}$ inch in diameter and $1\frac{1}{2}$ inches long. The number of turns and the winding lengths are correct as given in the parts list.

Thirty-Five Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder

| | |
|---------------------------------|------|
| Modern Electrics | 1908 |
| Wireless Association of America | 1908 |
| Electrical Experimenter | 1913 |
| Radio News | 1919 |
| Science & Invention | 1920 |
| Television | 1927 |
| Radio-Craft | 1929 |
| Short-Wave Craft | 1930 |
| Television News | 1931 |

Some larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

In October, 1923, Science and Invention (formerly Electrical Experimenter)

A Modern (Electronic) Charlatan, by A. B. Tripp.
 How Radio Aids Mine Rescue, by W. B. Arvin.
 Balloons to Support Antennae.
 Leviathan's Radio Transmitter.
 Radio Doll.
 Radio-Directed Torpedo of Tomorrow.
 Station WKAQ, Puerto Rico.
 Receiving the New Wave-Lengths, by Marius Logan.
 Radio for the Beginner (No. 20 Rheostats), by Armstrong Perry.
 Four Good Single Tube Hook-Ups, by Marius Logan.
 \$200.00 Single Tube Radio Contest.
 Special "Reflex" Amplifier, by R. B. Hall.
 The Radio Oracle.

OCTOBER, 1957

spectacular...new Tape System Components PENTRON

• STEREO • MONAURAL

Select the Tape units to meet your needs


Pentron combines professional features and custom styling with building-block flexibility. You buy what you want and add to your system when you desire—from the simplest monaural system to the all inclusive stereo systems.

PENTRON LEADERSHIP FEATURES

- Precision made and tested professional head assembly with Azmur-X spring loaded screw adjustment.
- Simple single rotary control.
- Four outputs plus two AC convenience outlets.
- Mounts VERTICALLY, horizontally, or at any angle.
- Speed change lever at front panel.
- Removable pole pieces in heads, as easy to change as a phono needle.
- Automatic self-energizing differential braking.

basic specifications TM series mechanisms

COMBINATION HEAD:
 Frequency response: 40-14,000 cps with proper equalization. Signal-to-Noise: 55 db with CA units; track width: .093"; gap width: $\frac{1}{4}$ mil; impedance of record section: 6000 ohms; inductance of erase section: 60 mh • **STACKED HEAD:** track width: .080"; gap width: .15 mil; impedance: 3500 ohms • **FLUTTER:** under 0.4% at $7\frac{1}{2}$ ps; under 1% at 3 $\frac{3}{4}$ ips. • **CAPSTAN DRIVE:** Idler driven • **MOTOR:** 4 pole induction type, individually balanced • **OUTPUTS:** 4 standard pin jack outputs to accept shielded phono plug • **CONVENIENCE OUTLETS:** two auxiliary AC outlets controlled by mechanism power switch. Supplied with removable mounting brackets with shock mounts.

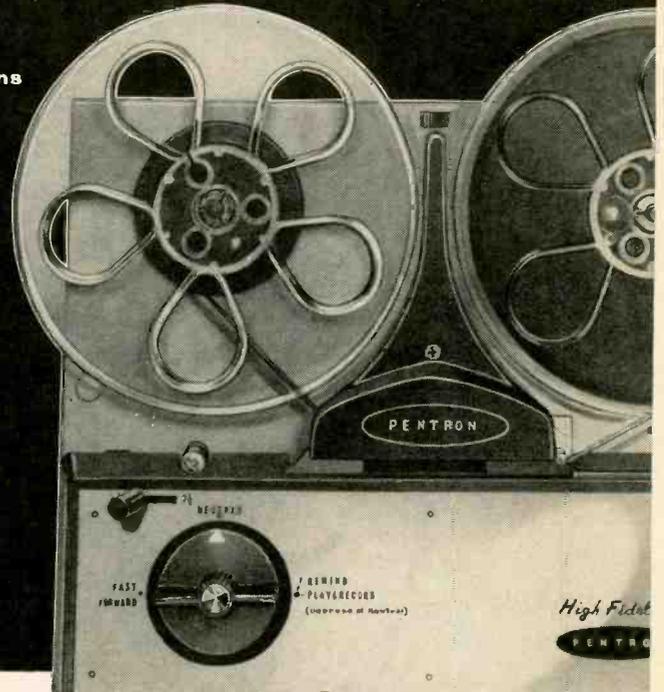

preamplifiers



CA-11

Tape Playback only. Response: 20-20,000 cps. Signal-to-Noise: 55 db



CA-13

Tape playback preamp and record amplifier. Response: 20-20,000 cps. Signal-to-Noise: 55 db



CA-15

Stereo dual channel playback. Response: 20-20,000 cps. Signal-to-Noise: 60 db

ALL CA UNITS HAVE SAME PHYSICAL DIMENSIONS AND REQUIRE SAME CUTOUT.

HEAR PENTAPE RECORDED TAPES—"GREATEST SOUND EVER FOUND"



779 S. Tripp Avenue
 Chicago 24, Illinois
 Canada: Atlas Radio Ltd. Toronto

Send brochure on tape components

Name _____

Address _____

City & State _____

DEATH

rides the HOT CHASSIS

Improperly grounded electrical equipment can kill . . .

By **FRED SHUNAMAN**
MANAGING EDITOR

PUBLIC attention has been focused sharply on the hazards of transformerless electronic equipment by the electrocution of a 6-year-old boy, Howard Erenstein Jr. of Skokie, Ill. He apparently brushed his bare leg or other part of his body against the metal stand of a 17-inch portable TV while reaching for a knife in the drawer of a sink cabinet.

The danger is not confined to TV receivers. On the same day a musician, Wm. Sennit of London, England, was killed by his own electric guitar. Nor is it rare. Within the last few months another small child—a 4-year-old boy—was killed while crawling under a TV set stand. Appearing in a local paper the event did not receive the burst that followed the accident in a Chicago suburb. Local papers continually carry stories of people being killed by wire antennas attached to ac-dc receivers, by receivers falling into bathtubs, etc. A compilation of the annual deaths caused by household electronic and electric equipment would produce what might truly be called a shocking total.

What's it all about?

What causes the danger and why is transformerless or portable equipment so often mentioned? Equipment with transformers, it is true, can become defective and cause accidents, but the danger is not as great.

In the home, electricity is usually brought in on two conductors, at about 117 volts. One of the two conductors is grounded close to the point the electric lines enter the house. This is in itself a safety measure, but has one drawback. The ungrounded or hot wire can form a circuit with any object connected to earth (Fig. 1). Your radiators, wash-

stands, sinks, furnaces, water and steam pipes and even such small objects as the switch plates on the walls can become—with the hot lead—part of an electric circuit.

Probably the world's most dangerous piece of electronic equipment is a small hot-chassis type ac-dc radio removed from its case. If the attachment plug is inserted in the wall receptacle in one direction, there is a difference of 117 volts between the chassis and any grounded object. If the plug is turned around, the chassis is at ground voltage and quite harmless (Fig. 2). But if the chassis is hot, any person who touches it and any grounded object at the same time is across the electric line. The part of the body in the circuit and the amount of moisture on the skin determine that person's chances of survival.

If the path is through vital organs—as from one hand to the other or (as in the Skokie case) from a leg through the body to the one hand—the result is likely to be fatal. Very dry skin may act as a partial insulator, but damp skin lowers resistance dangerously.

In transformerless TV and radio equipment, one side of the circuit is directly connected to one side of the electric line. In much of such equipment, the metal chassis on which the components are mounted is part of that circuit—in some others a single lead or bus—usually forming the negative-dc lead of the circuit as well—is connected directly to the ac line. This bus is often connected to the chassis through a small capacitor shunted by a large resistance, to increase operational stability. In

(Continued on page 109)

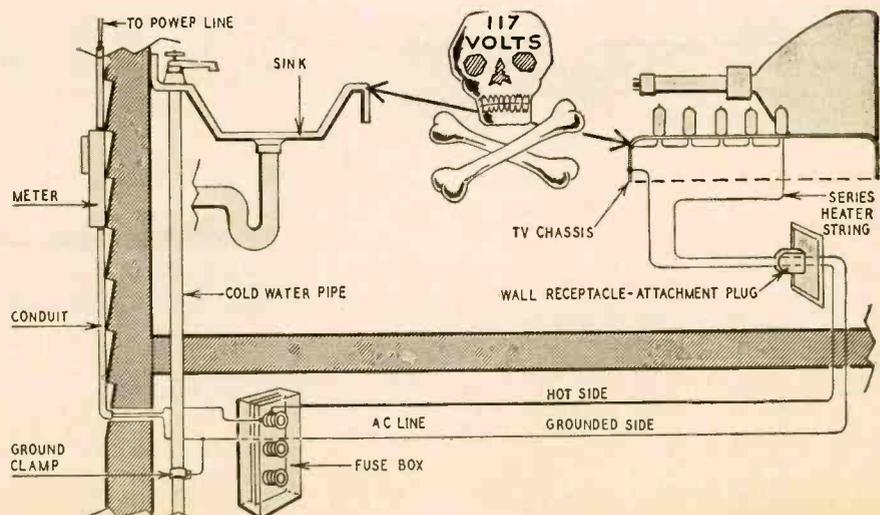


Fig. 1—The full line voltage is between the TV chassis and sink.

Build the Best— build ALLIED knight®-kits



the finest electronic equipment in money-saving kit form

LOWEST COST

ALLIED'S giant buying power passes biggest savings on to you—you do the easy assembly and your finished instrument equals the performance and appearance of equipment selling for several times the low KNIGHT-KIT cost. Your savings are BIG.

EASIEST TO BUILD

KNIGHT-KIT "Step-and-Check" instruction manuals with wall-sized picture diagrams are marvels of clarity—it's like having a good instructor at your side. No experience required—you can easily build any KNIGHT-KIT and get professional results.

LATEST DESIGN

Each ALLIED KNIGHT-KIT incorporates the very latest circuitry for top-quality performance. Tried and proved professional design and the use of premium quality parts throughout help insure your building success to bring you quality results.

COMPLETE KIT SELECTION:

- HI-FI
- HOBBY
- INSTRUMENT
- AMATEUR



MONEYBACK GUARANTEE. When properly assembled, KNIGHT-KITS fully meet published specifications or we refund your money in full.

EASY TERMS. If your KNIGHT-KIT order comes to \$45.00 or more, you can make your purchase on our attractive Easy Payment Plan.

High Fidelity Everyone Can Afford

- World's Finest Hi-Fi Kits
- Custom-Styled
- Easiest to Build Hi-Fi
- Money-Saving



knight-kit High Fidelity FM-AM Tuner Kit

Model Y-787

\$49.95

Only \$4.99 down

- Latest Time-Saving Printed Circuit Design
- Flywheel Tuning
- Automatic Frequency Control
- 2.5 μ v FM Sensitivity
- True High Fidelity Response
- Beautiful Custom-Styled "Space Saver" Case

The best-looking, best-performing FM-AM tuner kit your money can buy! Carefully designed for quick, easy construction—a tuner you'll enjoy assembling and be proud to own, both for its amazing musical performance and outstanding beauty. Covers the full AM broadcast band and 88 to 108 mc FM. On FM, sensitivity is a remarkable 2.5 microvolts for 20 db of quieting; hum and noise, -60 db; IF bandwidth, 200 kc at 50% down on curve; response, \pm 0.5 db, 20-20,000 cps. On AM, sensitivity is 3 microvolts for 10 db signal-to-noise ratio; IF bandwidth, 8 kc at 50% down on curve; response, 20-8000 cps. Outstanding features include: Inertia Flywheel Tuning for effortless, accurate tuning; Automatic Frequency Control (plus AFC disabling) to "lock-in" FM stations; printed circuit board (with most of the kit wiring already done for you) assures time-saving, error-free assembly; pre-aligned RF and IF coils; tuned RF stage on FM; drift-compensated oscillator; neon glow tuning pointer; cathode follower output; two output jacks—one for recorder, one for amplifier; rotatable built-in ferrite antenna for AM. Includes beautiful French-gray case with chrome-finished tapered feet, 4 x 13 x 8". Ideal for use with 18, 20 or 30 watt KNIGHT-KIT amplifiers. Ready for easy assembly. Shpg. wt., 12 lbs.

Model Y-787. FM-AM Tuner Kit. Net only..... **\$49.95**



knight-kit 18-Watt Complete Hi-Fi Amplifier Kit

Model Y-786

\$39.95

Only \$3.99 down

- The Last Word in Custom Hi-Fi Styling
- Full 18 Watts with Superb Hi-Fi Specifications
- 8 Inputs for Every Desired Signal Source
- Printed Circuit Switch and Printed Circuit Boards
- Full Equalization for All Record Types

Here is a custom-styled, easy-to-build complete Hi-Fi amplifier at a price that defies comparison. Delivers full 18 watts output with wide-range, flat frequency response for true hi-fi reproduction. Features 8 inputs for every possible signal source, including NARTB equalized tape head input. At full 18 watts output, distortion is only 0.5%; uses new RCA 6973 hi-fi output tubes. Frequency response is \pm 1 db, 20-30,000 cps; tape head and magnetic cartridge sensitivity, 5 microvolts for 18 watts output; hum and noise level better than 60 db below 18 watts. Output taps for 4, 8 or 16 ohm speakers. Controls: Input and Record Equalization; Bass Boost and Attenuate; Treble Boost and Attenuate; Volume. Simplest assembly is made possible through the use of an exclusive printed circuit switch and two printed circuit boards—most of the kit wiring is already done for you. With custom-styled French-gray "space-saver" case on tapered feet finished in chrome, 4 x 13 x 8". Complete with case, tubes, all parts, and step-by-step instructions, for easy, error-free assembly. Shpg. wt., 15 lbs.

Model Y-786. 18-Watt Hi-Fi Amplifier Kit. Net only..... **\$39.95**

EASY TERMS TO FIT YOUR BUDGET. ALLIED KNIGHT-KITS may be purchased under our Easy Payment Plan. Your order need total only \$45.00 or more—only 10% down, small monthly payments thereafter. No red tape—fast handling assured.

Our 37th Year



® Registered Trade-Mark of Allied Radio Corporation

ORDER FROM **ALLIED RADIO** 100 N. WESTERN AVE. • CHICAGO 80, ILL.

www.americanradiohistory.com

Now you can have Custom-Styled Hi-Fi in **ALLIED**



knight-kit 30-Watt Complete Hi-Fi Amplifier Kit

Model Y-762

\$76⁹⁵

- Full Equalization, $\pm \frac{1}{2}$ db of Recommended Accuracy
- Printed Circuit Switches • Printed Circuit Boards
- 8 Inputs For Every Possible Signal Source
- Full 30 Watts Output • Custom-Styled Beauty

Only \$7.69 down

Comparable to the best in Hi-Fi—at far less cost! Deluxe features include: Linear-deluxe Williamson-type circuit for flawless response; equalization for all records within $\frac{1}{2}$ db of recommended accuracy; 2 exclusive new printed circuit switches in preamp section (no complex wiring to do); 3 printed circuit boards for time-saving, error-free assembly; separate, continuously variable Level and Loudness controls; use of premium 12AY7 tube for low noise and hum; DC on all filaments of preamp tubes; exclusive A-AB-B speaker selector switch (use speakers of mixed impedances without mismatch). 8 inputs: Tape Head direct; G.E. and Pickering cartridges; Ceramic cartridge; Microphone; Auxiliary; Tape Preamp; Tuner (with separate Level Set control). Power amplifier response, $\pm \frac{1}{2}$ db, 15-100,000 cps at full 30 watt level; distortion—harmonic, 0.55% at 30 watts—IM, 0.74% at 20 watts. Separate Bass and Treble controls; rumble filter switch; variable damping. Output, 8 and 16 ohms. With smart French-gray cabinet, 4 x 15 x 15". Ready for easy, money-saving assembly. Shpg. wt., 32 lbs.

Model Y-762. 30-Watt Hi-Fi Amplifier Kit. Net only **\$76.95**

knight-kit High Fidelity FM Tuner Kit

Model Y-751

\$38⁹⁵

- Authentic High Fidelity FM Response
- Flywheel Tuning • Automatic Frequency Control
- Printed Circuit • Pre-Adjusted Coils and IF's
- 4 Microvolt Sensitivity Guaranteed

Only \$3.89 down

Here is top value in creative engineering, impressive hi-fi performance and distinctive design—a tuner you'll be proud to build and own. Covers the full FM band, 88 to 108 mc. Features Automatic Frequency Control (with disabling feature) to "lock-in" stations and prevent drift; Inertia Flywheel Tuning for velvet-smooth, accurate station selection; pre-adjusted RF coils; pre-aligned IF's; cascode broad-band RF amplifier; drift-compensated oscillator; neon bulb pointer. All critical wiring is already done for you in the form of a printed circuit board—assembly is simple. Sensitivity is 4 microvolts for 20 db of quieting across entire band; output, 2 volts at 1000 microvolts input; IF bandwidth, 200 kc; response, 20-20,000 cps. with only 0.6% distortion. Output jacks for amplifier and tape recorder; cathode follower output. Ideal for use with the KNIGHT-KIT amplifiers, or any amplifier with phono-tuner switch. Features custom-styled case in French-gray, with tapered chrome-finished feet, 4 x 13 x 8". Includes all parts, tubes and step-by-step instructions for easy assembly. Shpg. wt., 12 lbs.

Model Y-751. Hi-Fi FM Tuner Kit. Net only **\$38.95**

knight-kit Deluxe 3-Way Speaker System Kit

Model Y-937

\$89⁵⁰



Only \$8.95 down

- Pre-Finished "Quik-Craft" Corner Enclosure
- Klipsch Designed and Licensed
- Famous Knight 12" 3-Way Speaker
- Easy to Assemble—Top Hi-Fi Quality
- Choice of Enclosure Finishes

Deluxe quality high fidelity speaker system at a money-saving low price. Easy to assemble—all you need is a screwdriver. System includes KNIGHT "Quik-Craft" corner-type folded-horn enclosure kit, and the famous-value KNIGHT 3-Way 12-inch speaker. Just assemble the enclosure—no finishing required—all surfaces are finished in hand-rubbed Korina blonde, mahogany or walnut. The speaker is the new 3-way type: 12" woofer cone for bass (full $1\frac{3}{4}$ pound woofer magnet), conical radiator for mid-frequencies, built-in compression-type tweeter (with wired

level control and calibrated dial) for highest frequencies. Unexcelled enclosure efficiency and superb speaker performance combine to cover the whole spectrum of audible sound for true hi-fi response from 35 to 15,000 cps, ± 3 db. Kit includes 12" 3-Way speaker, prefinished enclosure panels, grille cloth, hardware and instructions. Specify Korina blonde, mahogany or walnut when ordering. Shpg. wt., 44 lbs.

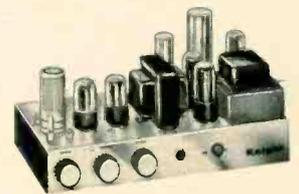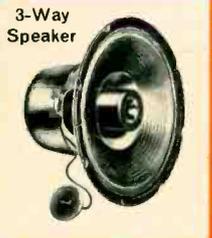Model Y-937. 3-Way Speaker System Kit. Net only **\$89.50**



knight-kit 10-Watt Hi-Fi Amplifier Kit

Y-753

\$23⁵⁰


Only \$2.35 down

Low-cost, authentic hi-fi amplifier. Response, ± 1 db, 30-20,000 cps. Input for crystal phono or tuner; chrome-plated chassis is punched for preamp kit below, to permit use of magnetic phono. Only 0.5 volt drives amplifier to full output. Separate bass and treble controls. Only 1% harmonic distortion. Matches 8-ohm speaker. 7 x 13 x 6". With all parts, tubes and instructions. Shpg. wt., 13 lbs.

Model Y-753. Net only **\$23.50**
 Y-235. Preamp Kit. **\$ 3.10**
 Y-757. Metal Cover. **\$ 3.95**

knight-kits

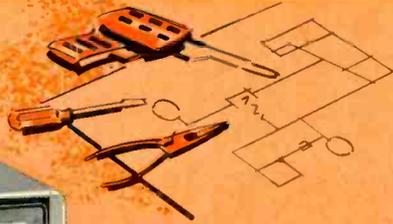THE VERY FINEST MUSICAL QUALITY—SO EASY TO BUILD
MONEY-SAVING HI-FI EVERYONE CAN AFFORD



So Easy To Build
Anyone can build
KNIGHT-KIT HI-FI.
No experience re-
quired to get top
results!



knight-kit High Fidelity Preamplifier Kit

Model Y-754

\$39.95

Only \$3.99 down

- Exclusive Printed Circuit Switches and Boards
- Equalization $\pm \frac{1}{2}$ db of Recommended Accuracy
- 8 Inputs Including Tape Head
- DC on All Tube Filaments
- Self-Powered
- Custom-Styled

Sensational Hi-Fi design at amazing low cost. Provides precise record equalization guaranteed within $\frac{1}{2}$ db of recommended accuracy!—more accurate than all but the most expensive factory-built preamps. Includes exclusive new KNIGHT-KIT printed circuit switches for easy, error-free assembly; 2 printed circuit boards eliminate all other wiring, except for power supply and control leads—so easy to build. Has built-in power supply; includes premium 12AY7 and ECC82 tubes. Frequency response, ± 0.5 db, 10-50,000 cps. Has 8 inputs: Tape Head; G.E. Phono; Pickering Phono; Ceramic; Microphone; Auxiliary; Tape Preamp; Tuner. Level adjustment for tuner input. Includes separate Bass and Treble controls; separate Level and Loudness controls; Rumble Filter switch; DC on all tube filaments; cathode follower output; 2 extra AC outlets. You get every advanced hi-fi feature in this easy-to-build preamplifier at the lowest possible cost. Includes beautiful custom-styled French-gray case, with tapered chrome-finished legs, 4 x 13 x 8". With all parts, tubes, step-by-step instructions; ready for easy assembly. Shpg. wt., 12 $\frac{1}{2}$ lbs.

Model Y-754. Hi-Fi Preamp Kit. Net only **\$39.95**

knight-kit 25-Watt Hi-Fi Basic Amplifier Kit

Model Y-755

\$44.50

Only \$4.45 down

- Hi-Fi Response, ± 0.5 db, 10 to 120,000 cps
- Only 0.15% Distortion at 30 Watts Output
- Printed Circuit Wiring Board • Chrome-Plated Chassis
- Williamson-Type Circuit with Over 25 Watts Output

Here's superb Hi-Fi performance at less than half the cost of a comparable commercially-assembled unit. Williamson-type linear-deluxe circuit delivers over 25 watts of virtually undistorted reproduction. Ideal for use with the KNIGHT-KIT preamp at left. Includes printed circuit board for simplified, error-free assembly. Remarkable hi-fi response, ± 0.5 db, 10-120,000 cps at 20 watts. Harmonic distortion, 0.15% at 30 watts; 1M, 0.4% at 20 watts. Hum level, 85 db below 25 watts output. Output impedances, 4, 8 and 16 ohms; output tubes, 2-5881. Includes balance control for precise matching of the output tubes; variable damping control for maximum performance with any speaker system—prevents low-frequency distortion from overdamping or underdamping. Very attractive black and chrome styling, 6 $\frac{1}{4}$ x 14 x 9". An outstanding engineering achievement in a basic hi-fi amplifier, delivering performance equal to the finest commercially assembled units. Includes all parts and tubes; with step-by-step instructions, ready for easy assembly. Shpg. wt., 25 lbs.

Model Y-755. 25-Watt Amplifier Kit. Net only **\$44.50**

Y-759. Metal Cover for above; black finish. 5 lbs. Net **\$4.25**



knight-kit 20-Watt Hi-Fi Amplifier Kit

Y-750

\$35.75

\$3.57 down

True hi-fi for less! Complete with full set of controls and built-in preamplifier. Response, ± 1 db, 20-20,000 cps; distortion 1% at 20 watts. Inputs for magnetic phono, microphone, crystal phono or recorder, and tuner. Compensation positions for 78 and LP records. Separate bass and treble controls. Output impedances, 4, 8, 16 and 500 ohms. Chrome-plated chassis. 7 x 13 x 8 $\frac{3}{4}$ ". Ready for easy assembly. Shpg. wt., 20 lbs.

Model Y-750. Net only. . . . **\$35.75**

Y-758. Metal Cover **\$4.15**

knight-kit 2-Way Hi-Fi Speaker System Kit

Model Y-789

\$49.95

Only \$4.99 down

- Easy to Assemble—Pre-Finished Enclosure
- High Fidelity Response, 45 to 14,000 cps
- 12" Woofer and Horn-Type Tweeter
- A Wonderful Money-Saving Speaker Value

BIG SAVINGS—assemble your own quality KNIGHT-KIT 2-way speaker system—it's quick and easy! The cabinet is *pre-finished* in full-grained, high luster blonde or mahogany—you just assemble 7 pieces, mount the speaker components and enjoy rich, thrilling hi-fi sound—at incomparably low cost. Special Jensen-engineered baffle features "ducted port" construction to bring out the full beauty of bass notes, perfectly matching the Jensen woofer and compression tweeter; genuine L-pad control is rear-mounted to permit adjustment of tweeter for best tonal balance. Impedance, 16 ohms. The assembled unit delivers a frequency response of 45 to 14,000 cps. Enclosure measures 26 x 19 x 14". Beautifully styled to blend in any room. Kit includes Jensen 12" woofer, Jensen compression-type tweeter, pre-finished wood parts (with grille cloth installed), acoustic material, glue, hardware and step-by-step instructions. Absolutely no furniture finishing required. *Specify blonde or mahogany finish when ordering.* Shpg. wt., 33 lbs.

Model Y-789. 2-Way Speaker System Kit.

Net only **\$49.95**




knights-kit HI-FI IS AVAILABLE ON EASY TERMS TO FIT YOUR BUDGET

Fascinating

ALLIED **knight-kits**

FOR EXPERIMENTERS AND HOBBYISTS

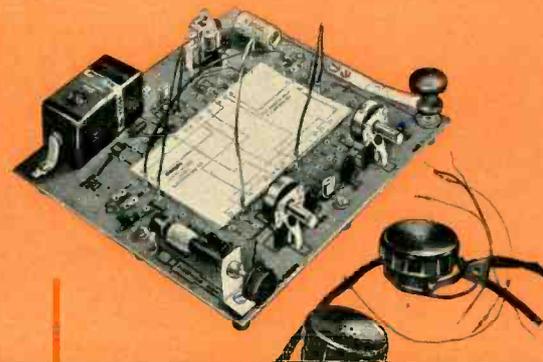

knight-kit 2-Transistor Pocket Radio Receiver Kit

Model Y-262 • Loud, Clear Local Reception
• Newest Printed Circuit Board
• Built-In Loop Antenna
• Complete Kit—Nothing Else To Buy

\$14.65

It's fun to build this pocket-size two-transistor radio—and you'll enjoy its crystal-clear local broadcast-band reception wherever you go! Fits in your pocket, or with its button-down flap, can be worn from your belt. Completely self-contained with built-in ferrite loopstick antenna—no external antenna needed. Extremely efficient reflex type 2-transistor circuit actually does the work of 3 transistors! Printed circuit board reduces building time to about one hour. Has air-dielectric variable capacitor for easy, accurate station tuning. Operates for months and months on long-life alkaline battery supplied. Sensitive miniature earpiece provides crystal-clear tone. Handsome tan carrying case, plastic-impregnated, is styled to resemble leather; only 4x3 $\frac{3}{4}$ x1 $\frac{3}{4}$ ". Kit includes all parts, transistors, earpiece, battery and case. Shpg. wt., 1 $\frac{1}{2}$ lbs.

Model Y-262. Net only \$14.65

knight-kit "Trans-Midge" Transistor Receiver Kit

Model Y-767 Tiny, cigarette-pack-size one-transistor radio kit—fascinating to build—so low-priced. This novel miniature receiver will provide endless listening

pleasure the moment assembly is completed. Covers the local AM broadcast band with exceptional sensitivity and selectivity. Special features include: Efficient, slug-tuned coil for excellent station separation; external knob for easy station tuning; low-drain transistor operating for months from single penlight cell supplied; hinged-back, red plastic case. Kit includes all parts, transistor, battery, compact case and easy-to-follow instructions for quick assembly. (External antenna and headphones required.) Shpg. wt., 8 oz.

Model Y-767. Net only \$2.45
J-149. 4000 Ohm Headphones. 1 lb. \$2.15
C-100. Antenna Kit. 1 $\frac{1}{2}$ lbs. \$1.03

knight-kit 10-Circuit Transistor Lab Kit

Model Y-299 Sensational experimenters' transistor kit—an electronic marvel! Perfect for experimenter, student or hobbyist. Assemble basic parts once,

then complete project after project (10 in all), by simply plugging leads into proper jacks on printed circuit board—no wiring changes needed. You learn how transistors operate by "plugging in" to make any one of the following circuits; AM radio for strong headphone reception; 2-stage audio amplifier; wireless broadcaster; code practice oscillator; electronic timer; electronic switch; electronic flasher; photoelectronic relay; voice-operated relay; capacity-operated relay. Includes all parts, 2 transistors, battery, headphones, circuit leads, relay, photocell, special guide cards for each project, explanation of each circuit. 3 lbs.


Model Y-299. Net only \$15.75

knight-kit 5-Transistor Superhet Personal Portable Radio Kit

Model Y-766 • Styled to Equal the Finest
• Push-Pull Audio Drives 3 $\frac{1}{2}$ " Speaker
• Printed Circuit for Easy Building
• 200 Hour Battery Playing Life

Beautiful, easy-to-build transistorized personal portable with every ultra-modern design feature: 5 Texas Instrument Co. transistors; latest printed circuit chassis for easy, error-free assembly; bigger-than-average 3 $\frac{1}{2}$ " speaker; class B push-pull audio output; built-in high-gain ferrite loopstick antenna; plus phone jack output for private listening. Provides sensitive reception of the AM broadcast band with exceptional tone quality. Ultra-smart high-impact ivory plastic case has handsome gold trim with ebony accents; includes pull-out handle; only 7 $\frac{1}{2}$ x3 $\frac{3}{8}$ x1 $\frac{3}{4}$ ". With all parts, transistors, 9 volt transistor radio battery, carrying case and instructions anyone can easily follow. Shpg. wt., 2 lbs.

Model Y-766. Net only \$29.95

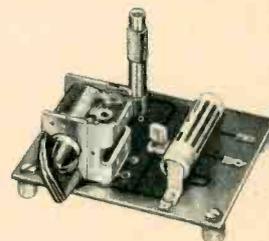

1-Transistor Radio Kit

\$3.95 Offers excellent AM local broadcast headphone reception. Printed circuit board for easy assembly. Operates from single penlight cell for months. Complete with all parts, transistor and penlight cell. (Antenna and headphones required.) Shpg. wt., 1 lb.

Model Y-765. Net only \$3.95



"10-In-One" Electronic Lab Kit

\$12.65 Famous experimenters' kit. Builds any of 10 fascinating projects, including broadcast receiver, wireless phono oscillator, code practice oscillator, signal tracer, relays, etc. Shpg. wt., 5 lbs.

Model Y-265. Net only \$12.65



"6-In-One" Electronic Lab Kit

\$8.45 A favorite with beginners. After basic wiring is completed, you make circuit changes without soldering. Builds any of six favorite projects, including radio, wireless broadcaster, etc. Shpg. wt., 3 lbs.

Model Y-770. Net only \$8.45



Crystal Set Hobby Kit

\$2.15 Entertaining, educational. Delivers clear headphone reception of local broadcast stations. With all parts, ready for easy assembly. (Antenna and headphones required.) Shpg. wt., 1 lb.

Model Y-261. Net only \$2.15



Wireless Broadcaster Kit

\$9.50 Play music or make announcements through your radio set—no connection to set required! Loads of fun—easy to build. Works up to 50 feet from set. Shpg. wt., 3 lbs.


Model Y-705. Net only \$9.50

ORDER FROM **ALLIED RADIO** 100 N. WESTERN AVE. • CHICAGO 80, ILL.

FUN TO BUILD . . . INSTRUCTIVE . . . LATEST CIRCUITS FOR TOP PERFORMANCE
WIDEST CHOICE OF QUALITY HOBBYIST KITS



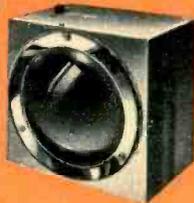Interruption of light beam triggers relay, which in turn sounds chime or bell, turns on lights, etc.



knight-kit Photoelectronic Relay Kit

Model Y-702 Advanced-design, ultra-sensitive photoelectronic relay—build it yourself and save! Dozens of uses: for automatic control of lights, door announcer, burglar alarm, counting devices, etc. Provides dependable operation up to 250 feet with white light, up to 125 feet with "unseen" light (red filter) from Light Source Kit listed below. Selectable operation, with "trip" for burglar alarm to provide continuous ringing of alarm; and "auto" if relay is to operate each time beam is broken (for chimes, counting devices, turning on lights at darkness). Has SPST relay operated from thyatron; 6.3 v. terminals provide power for accessories. For 105-120 v. 50-60 cy. AC use. 6 lbs.
Model Y-702. Relay Kit. Net only. **\$13.50**
Model Y-703. Light Source Kit. With bulb and red filter. Shpg. wt., 3½ lbs. Net. **\$6.75**

knight-kit "Ocean Hopper" All-Wave Radio Kit

Model Y-740 This top-performing regenerative receiver puts a world of listening pleasure at your finger-tips. Tuning range (using coils listed below) is virtually world-wide; covers 155 kc to 35 mc. including every type of radio transmission: AM broadcast, marine, aircraft, distress channels, direction-finding, Amateur, frequency standard, foreign broadcast, and police. With hand-spread tuning. For use with headphones or 3-4 ohm PM speaker. Kit is supplied with standard broadcast hand coil and all tubes and parts. (Less extra coils, headphones, speaker and cabinet.) Shpg. wt., 5 lbs.
Model Y-740. Net only. **\$11.95**
Y-746. Cabinet for above. 1½ lbs. Net **\$2.90**
 Extra coils available: Long Wave Coil (155-470 kc). Net 79c. Short Wave (1.65-4.1 mc; 2.9-7.3 mc; 7-17.5 mc and 15.5-35 mc). Each 65c.



knight-kit "Space-Spanner" Bandswitching World-Wide Radio Kit

Model Y-243 • Broadcast or Short Wave Reception
 • Sensitive Regenerative Circuit
 • Convenient Bandsread Tuning
 • Built-In Loudspeaker
\$15.95
 Imagine the thrill of hearing overseas broadcasts on a precision receiver you've built yourself—and then, at the flip of a switch, being able to tune to your favorite local broadcast station! Bandswitch selects exciting short wave, including foreign broadcasts, amateur calls, aircraft, police and marine radio on the 6.5 to 17 mc range, as well as standard 540-1700 kc broadcasts. Features highly sensitive regenerative circuit. Includes built-in 4" PM speaker and beam-power tube for strong volume and clear tone. Headphone connectors are available for private listening; switch cuts out speaker. Controls: Bandsread, Main Tuning, Antenna Trimmer, Bandswitch, Regeneration, Volume. 7x10x6". Easy to build from step-by-step instruction manual. For 110-120 v., 50-60 cy. AC or DC. (Less cabinet.) Shpg. wt., 5 lbs.
Model Y-243. Net only. **\$15.95**
Y-247. Cabinet for above. Shpg. wt. 2 lbs. Net. **\$2.90**




"Ranger II" Superhet Receiver Kit

\$17.25 Popular Broadcast band receiver built and enjoyed by thousands. Features built-in antenna, automatic volume control, ball-bearing tuning condenser, PM dynamic speaker. Handsome plastic cabinet. Easy to assemble. AC or DC operation. Shpg. wt., 8 lbs.
Model Y-735. Net only. **\$17.25**

knight-kit 2-Way Intercom System Kit

Model Y-295 • Low Cost—Easy to Assemble
 • High Gain—Clear Tone
 • Handsome Metal Cabinets
 • Includes 50-Foot Cable
\$14.75
 Easy to build at lowest cost—ideal for home, office, shop or school. Consists of Master unit and Remote unit. Remote unit may be left "open" for answering calls from a distance, for "baby sitting", etc. Remote also may be set for "private" operation—cannot be "listened-in" on, but it can be called and can originate calls. Master unit includes high-gain 2-stage amplifier, combination volume control and on-off switch, plus pilot light. Each unit has 4" PM dynamic speaker. System responds to even a whisper. Handsome Antique white cabinets, each 4¾x6½x4¾". With all parts, tubes and 50-ft. cable (up to 200-ft. may be added). For 110-120 v., AC or DC. 8 lbs.
Model Y-295. Master and one Remote. Net only. **\$14.75**
Y-296. Extra Remote Station Kit. 3 lbs. **\$3.75**

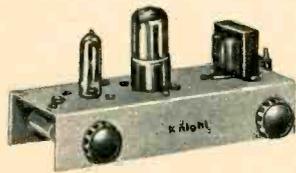

Phono Amplifier Kit

\$9.45 Build it yourself—and save! Ideal for use in a portable phonograph—just add record player and 3-4 ohm speaker. 1½ watts output. Inverse feedback circuit. Easy to assemble. Shpg. wt., 3 lbs.
Model Y-790. Net only. **\$9.45**



Electronic Photoflash Kit

\$28.50 Ideal for color or black and white photography. 1/700th-of-a-second flash; 50 watt/second output. Synchronizes with any camera with X or O shutter. (Less battery.) Shpg. wt., 4 lbs.
Model Y-244. Net only. **\$28.50**



Code Practice Oscillator Kit

\$3.95 Ideal for beginners learning the code. Transistorized circuit. Operates for months from single penlight cell supplied. Clear, crisp 500 cycle tone. Jacks for headphones; screw terminals for key. 1 lb.
Model Y-239. Net only. **\$3.95**



Phono Oscillator Kit

\$5.85 "Broadcasts" recorded music through any standard radio set up to 50 feet away. No direct connection to set required. Easy to build—fun to use. Shpg. wt., 2 lbs.
Model Y-760. Net only. **\$5.85**



knight-kit Low-Cost Tube Tester Kit

- Model Y-143
- With 16 Filament Voltages
 - 600 Latest Tube Types Listed
 - Easy-to-Read 4½" Meter
 - Tests Series-String TV Tubes

\$29.75

Expertly designed for complete, up-to-date coverage of tube types. Tests *series-string TV tubes*; tests 4, 5, 6 and 7 pin large, regular and miniature types, octals, loctals, 9-pin miniatures and pilot lamps. Tests for open, short, leakage, heater continuity and performance (by amount of cathode emission). Big 4½" square meter has clear "GOOD-?-REPLACE" scale. With line-voltage indicator and line-adjust control. Choice of 16 filament voltages from 0.63 to 117 volts to check virtually all receiving tubes; blank socket for future type tubes. Universal-type selector switches permit selection of any combination of pin connections. Single-unit, pre-assembled 10-lever function switch simplifies and speeds assembly. Up-to-date illuminated roll chart lists over 600 tube types. Counter model case, 5 x 14 x 10". Easy to build. 14 lbs.

- Model Y-143. Net only **\$29.75**
 Y-142. Portable Case model. 15 lbs. Net **\$34.75**
 Y-141. Picture Tube Adapter. 1 lb. Net **\$ 4.25**



knight-kit RF Signal Generator Kit

Model Y-145 Build this wide-range, extremely stable RF signal generator—save two-thirds the cost of a comparable wired instrument! Large, semi-circular dial is clearly calibrated; range is covered in 5 separate bands for close accuracy in setting individual frequencies. Ideal for aligning RF and IF stages in radio and TV sets and for troubleshooting audio equipment. Delivers output on fundamentals from 160 kc all the way out to 112 mc; useful harmonics to 224 mc. Has built-in 400-cycle sine-wave audio oscillator for modulating RF; audio is also available externally. Features high-stability Colpitts circuit. Convenient jack for external modulation. Maximum audio output 10 volts; RF output over 0.1 volt on all ranges. Step and continuous-type attenuator controls. Supplied with precision-wound coils that require no adjustment. 7 x 10 x 5". Shpg. wt., 11 lbs.

Model Y-145. Net only **\$19.75**



knight-kit 1000 Ohms/Volt VOM Kit

Model Y-128 Exceptional accuracy and versatility at amazing low cost. Ideal for service shop, lab or Amateur use. Large 4½", 400 microamp meter with separate scales for AC and DC voltage and current, decibels and resistance. Uses 1% precision resistors; has 3-position function switch and 12-position range switch. 38 ranges include: AC, DC and output volts, 0-1-5-10-50-500-5000 (1000 ohms/volt sensitivity); Resistance, 0-1000-100,000 ohms and 0-1 meg (center scale readings of 60, 150 and 1500 ohms); Current, AC or DC, 0-1-10-100 ma and 0-1 amp; Decibels, -20 to +69 in 6 ranges. Precision resistors are used as shunts and multipliers to assure exceptional accuracy of measurements. With all parts, battery, test leads and black bakelite case with convenient carrying handle, 6¾ x 5¼ x 3¾". A great value in an easy-to-build quality instrument. Shpg. wt., 2½ lbs.

Model Y-128. Net only **\$16.95**



knight-kit Vacuum Tube Voltmeter Kit

- Model Y-125
- 200 µa Movement, 4½" Meter
 - Includes AC, Peak-to-Peak
 - Balanced-Bridge, Push-Pull Circuit
 - 1% Film-Type Resistors

\$24.95

Top buy in an extremely stable, highly accurate VTVM. Easy to assemble—entire chassis is printed circuit board. Perfect for radio-TV service work, lab and Amateur use. Features low-leakage type switches; 1% film-type precision resistors; balanced-bridge, push-pull circuit (switch to any range without readjusting zero set); zero center scale and direct-reading db scale; polarity reversing switch. Ranges: Input Resistance, 11 megs; DC and AC rms, 0-1.5-5-15-50-150-500-1500; AC Peak-to-Peak, 0-4-14-40-140-1400-4000; Response, 30 cycles to 3 mc; Ohms, 0-1000-10K-100K and 0-1-10-100-1000 megs; db, -10 to +5. Includes all parts, tubes, battery, test leads and portable case, 7¾ x 5¼ x 4¾". Easy to assemble. Shpg. wt., 6 lbs.

- Model Y-125. Net only **\$24.95**
 Y-126. Hi Voltage Probe; extends DC to 50,000 v. **\$ 4.75**
 Y-127. Hi-Frequency Probe; extends AC to 250 mc. **\$ 3.45**



6V-12V Battery Eliminator Kit

\$32.95 High current rating; continuously variable filtered output; delivers 15 amps at 6 volts, 10 amps at 12 volts. May be used as battery charger. Two meters provide simultaneous current and voltage readings. Shpg. wt., 18 lbs.

Model Y-129. Net only **\$32.95**



Transistor Checker Kit

\$8.50 Checks gain ratio of all types of transistors; checks germanium and silicon diodes; checks for continuity and shorts. A valuable instrument at very low cost. Easy to assemble. Shpg. wt., 2½ lbs.

Model Y-149. Net only **\$8.50**



Flyback Checker Kit

\$19.50 Checks condition of all types of horizontal output transformers and deflection yokes, as well as TV linearity and width coils. 4½" meter; widest range in its field. Shpg. wt., 6 lbs.

Model Y-118. Net only **\$19.50**



Sweep Generator Kit

\$43.75 Extreme linearity on a par with costly lab instruments; fundamentals to 250 mc; output flat within 1 db; electronic blanking. Easy, money-saving assembly. Shpg. wt., 16 lbs.

Model Y-123. Net only **\$43.75**



Capacitor Checker Kit

\$12.50 Tests capacitors while in the circuit! Has widest range—20 mmf to 2000 mfd. Exclusive circuit for cancelling lead capacity. "Magic Eye" indicator. Save 60% over factory-wired units. 5 lbs.

Model Y-119. Net only **\$12.50**

**ADVANCED-DESIGN INSTRUMENTS FOR SERVICE, INDUSTRIAL AND RESEARCH USE
IN EASIEST-TO-BUILD, MONEY-SAVING KIT FORM**



knight-kit 20,000 Ohms/Volt VOM Kit

Model Y-140 Outstanding quality and performance at money-saving low price. Features 1% precision multipliers; 4 1/2" meter accurate within 2% of full scale deflection; 50 microamp sensitivity for 20,000 ohms/volt input resistance on DC; front panel "Zero adjust"; single switch to select function and range. 32 ranges: AC, DC and output volts, 0-2.5-10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg.; DC ma, 0-0.1-10-100; DC amps, 0-1-10; Decibels, -30 to +63 in six ranges. Moisture-resistant film-type resistors for extreme accuracy. Carefully engineered circuit design achieves high sensitivity and extremely versatile application. Kit includes all parts, battery, test leads and black bakelite case with highly legible white markings; size 6 3/4" x 5 1/4" x 3 3/4". Easy to assemble. Shpg. wt., 5 lbs.

Model Y-140. Net only \$29.50



knight-kit High-Gain Signal Tracer Kit

Model Y-135 A remarkable value in an easy-to-build instrument which permits visual and aural signal tracing of RF, IF, video and audio circuits. Has highest gain in its price class. Traces signal from antenna to speaker. Reproduces signal at plate or grid connection of any stage. Identifies and isolates "dead" stages. Features: usable gain of 91,000; "magic eye" with calibrated attenuators for signal presence indication and stage-by-stage gain measurements; built-in 4" PM speaker; combination 2-position probe, one for RF (6 mmf. input), the other for audio. Provides noise test; built-in watt-meter calibrated from 25 to 1000 watts; provision for external scope or VTVM. Binding posts provide output transformer and speaker substitution test, plus external 280 volts B+. With all parts, tubes and probe. 7x10x5". 12 lbs.

Model Y-135. Net only \$26.50



knight-kit 5" Wide-Band Oscilloscope Kit

- Model Y-144**
- 5 mc Width for Color TV
 - Horizontal Sweep to 600 kc
 - 25 mv/inch Sensitivity
 - Z-Axis Input
 - Printed Circuit Construction

\$6900
Only \$6.90 down

Equals or betters the performance of commercially wired scopes costing far more. Two printed circuit boards and laced wiring harness assure wiring accuracy and cut assembly time. Ideal for lab use, color TV servicing and high frequency applications. Wide sweep range—15 to 600,000 cps. Vertical response, ± 3 db, 5 cps to 5 mc; only 1 db down at 3.58 mc color burst. High vertical sensitivity of .025 rms v/inch. Input capacity, 20 mmf. Outstanding features: cathode follower inputs; 2nd anode provides 1400 volts high-intensity trace; push-pull amplifiers; positive and negative locking; frequency-compensated attenuator; Z-axis input; one volt P-P calibrating voltage; astigmatism control; retrace blanking circuit; DC positioning control. Includes CRT. 14 1/2" x 9 1/2" x 16". 40 lbs.

Model Y-144. Net only \$69.00
Y-148. Demodulator Probe. Net \$ 3.45
Y-147. Low Capacity Probe. 12 mmf. Net \$ 3.45



knight-kit 5" General-Purpose Scope Kit

- Model Y-146**
- Phantastron Linear Sweep
 - 25 mv/inch Sensitivity
 - Printed Circuit Board
 - Retrace Blanking Circuit

\$4200
Only \$4.20 down

Feature for feature the world's best oscilloscope kit value. A stand-out in its class with all these fine features: *Printed Circuit* wiring board and laced harness for quick, error-free assembly. *Phantastron Sweep Circuit* for high linearity of sweep from 15 to 150,000 cps. *25 Millivolts Per Inch Sensitivity*—3 times that of similarly priced scope kits. *Calibration Voltage*—1 volt peak-to-peak square wave, fully regulated. *Vertical Amplifier*—frequency response ± 3 db, 3 cps to 1.5 mc (± 6 db to 2.5 mc). Includes: Directly coupled positioning controls; retrace blanking circuit; frequency-compensated vertical input attenuator; positive and negative internal sync; high 2nd-anode voltage for high-intensity trace; input capacity, 45 mmf. Kit includes CRT. 9 1/2" x 13 3/4" x 17 3/4". 26 lbs.

Model Y-146. Net only \$42.00



Voltage Calibrator Kit

\$1275 Permits use of any scope as precision peak-to-peak AC voltmeter. Puts a true square-wave voltage on scope screen. Selects any voltage between .01 and 100 volts; feeds external signal direct to scope for instant comparison. Shpg. wt., 5 lbs.

Model Y-136. Net only \$12.75



Resistance Substitution Box

\$595 Easily determines resistor values required in a circuit. Makes available 36 standard 1-watt resistance values in 2 ranges between 15 ohms and 10 megohms, with 10% accuracy. Slide switch selects range; 18-position switch for value selection. Shpg. wt., 2 lbs.

Model Y-139. Net only \$ 5.95



Capacitance Substitution Box

\$595 Makes it easy to find capacitor values needed in a circuit. Provides 18 standard values from .0001 mfd to .22 mfd, ± 20%. All values are 600 volt, except .15 and .22, which are 400 volt. 18-position selector switch. Shpg. wt., 2 lbs.

Model Y-138. Net only \$ 5.95



Audio Generator Kit

\$3150 Excellent design; range, 20 cps to 1 mc; less than .25% distortion; 600 ohm output. Ideal for hi-fi testing; offers the flat response of a lab standard. Shpg. wt., 16 lbs.

Model Y-137. Net only \$31.50



R/C Tester Kit

\$1950 Measures capacitance and resistance. Balanced-bridge circuit; indicates power factor; tests capacitors at rated voltage. Large, easy-to-read dial and "magic eye." Shpg. wt., 10 lbs.

Model Y-124. Net only \$19.50

EASY TERMS AVAILABLE

Take advantage of the most liberal Easy Pay plan in electronics. On Knight-Kit orders totaling \$45 or more—just 10% down, small monthly payments thereafter. Low carrying charges—no "red tape."



knight-kits FOR THE RADIO AMATEUR

knight-kit All-Band Amateur Receiver Kit

Model Y-726
\$104⁵⁰

Only \$10.45 down

- Tunes 540 kc to 31 mc
- Built-In Q-Multiplier
- Constant Running HF Oscillator
- Worthy of the Advanced Ham Operator
- Printed Circuit Bandswitch
- Printed Circuit Board • 1.5 μ v Sensitivity

A sensational communications receiver value with all the selectivity, sensitivity and features of high-priced commercial units. Uses printed circuitry throughout, including the exclusive new KNIGHT-KIT printed circuit bandswitch, for remarkably easy assembly. Covers 540 kc to 31 mc in 4 ranges; calibrated, electrical bandspread on 80-10 meter Ham bands; slug-tuned Hi-Q coils; continuous, VR tube-regulated B+ applied to HF oscillator lets you switch from standby to receive with no drift; built-in Q-multiplier peaks desired signal or nulls interference; delayed AVC; provision for crystal calibrator (below). Sensitivity, 1.5 microvolts for 10 db signal-to-noise ratio. Selectivity: variable from 300 cps to 4.5 kc at 6 db down. Exalted BFO injection. Controls: Main tuning, bandspread, band selector, Q-multiplier selectivity, Q-multiplier tune, null-off-peak, BFO pitch, RF gain, AF gain, BFO-MVC-AVC-ANL, off-stby-rec-cal, antenna trimmer, and phone jack. Cold-rolled $\frac{1}{8}$ " steel chassis. Handsome metal cabinet, 10 x 10 x 16 $\frac{1}{2}$ ". (Less phones, 8-ohm loudspeaker and S-meter.) 23 lbs.

Model Y-726. Amateur Receiver Kit. Net. . . . \$104.50
 Y-727. S-Meter Kit for above. 1 lb. Net. . . . \$9.50

knight-kit 50-Watt CW Transmitter Kit



Model Y-255
\$38⁹⁵

Only \$3.89 down

- Ideal for the Novice
- Pi Antenna Coupler
- Bandswitching—80 to 10 Meters

There's exceptional value in this very popular bandswitching transmitter kit. Compact and versatile, it's the perfect low-power rig for the beginning novice as well as the seasoned veteran. Has bandswitching coverage of 80, 40, 20, 15 and 10 meters. Rated at 50 watts—actually operates at up to 60 watts on 80 and 40 meters. Oscillator is efficient 6AG7; final is reliable 807. Crisp, clean, cathode keying of oscillator and final. Built-in pi coupler permits use with random length antennas. Has highly effective TVI suppression. Other features not usually found in transmitter kits at this low price include: Ceramic-insulated final tank capacitor; pre-assembled switches; pre-wound parasitic chokes; ceramic coil forms; coax connector; crystal and VFO socket on front panel; power take-off jack for accessory equipment. Meter reads either plate or grid current of final. Takes crystal or VFO without circuit changes. Cabinet interior and chassis are copper-finished. Size, 8 $\frac{1}{2}$ x 10 $\frac{1}{2}$ x 8 $\frac{1}{4}$ ". With tubes and all parts for easy assembly. (Less crystal and key.) Shpg. wt., 19 lbs.

Model Y-255. 50-Watt Transmitter Kit. Net only. . . . \$38.95

knight-kit Self-Powered VFO Kit



Model Y-725
\$28⁵⁰

Only \$2.85 down

Complete with built-in power supply! Careful design and voltage regulation assure high stability. Excellent oscillator keying characteristics for fast break-in without clicks or chirps. Full TVI suppression. Has plenty of bandspread; separate calibrated scales for 80, 40, 20, 15, 11 and 10 meters; vernier drive mechanism. 2-chassis construction keeps heat from frequency determining circuits. Output cable plugs into crystal socket of transmitter. Output: 40v on 80, 20v on 40. With Spot-Off-Transmit switch for spot frequency tuning. Extra switch contacts for operating relays and other equipment. Attractive metal cabinet, 8 $\frac{3}{4}$ x 6 x 6". Ready for easy assembly. Shpg. wt., 8 lbs.

Model Y-725. VFO Kit. Net only. . . . \$28.50

knight-kit 100 Kc Crystal Calibrator Kit

Model Y-256
\$10⁵⁰

Crystal frequency standard at very low cost. Gives marker every 100 kc up to 32 mc. A "must" for marking band edges. Mounting flanges for installation in or back of receiver cabinet. Size only 1 $\frac{1}{2}$ x 1 $\frac{1}{2}$ x 3". Requires 6.3 v. at 0.15 amp and 150-300 v. DC at 3-6 ma. Trimmer for zero-beating with WWV; On-Off switch. Complete with tube, crystal, all parts and easy-to-follow instructions. Shpg. wt., 1 lb.

Model Y-256. 100 Kc Crystal Calibrator Kit. Net only. . . . \$10.50



knight-kit Amateur RF "Z" Bridge Kit



Model Y-253
\$5⁸⁵

Measures standing wave ratio (SWR) and impedance-of antenna systems; ideal for adjusting antenna systems for optimum results. Measures impedances from 20 to 400 ohms up to 100 mc; SWR to 150 mc. Any VOM may be used for null indicator. With coax input and output connectors. Meters both input and bridge voltage. Calibrated dial gives direct impedance reading; includes 1% precision resistor for precise calibration adjustment. With all parts and handy plasticized SWR chart (less meter). 2 $\frac{1}{2}$ x 3 x 4 $\frac{1}{2}$ ". Shpg. wt., 1 $\frac{1}{2}$ lbs.

Model Y-253. "Z" Bridge Kit. Net only. . . . \$5.85

ORDER BLANK

ALLIED RADIO

100 N. WESTERN AVE., CHICAGO 80, ILL.

ALLIED RADIO, Dept. PF, 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

| Quantity | Description | Model No. | Price |
|----------|-------------|-----------|-------|
| | | | |
| | | | |
| | | | |

\$..... enclosed. (For parcel post, include postage—express is shipped collect).

My Down Payment in the amount of \$..... is enclosed. Send Time Payment form.

Name.....

Address.....

City..... Zone..... State.....

ALL PRICES NET F. O. B. CHICAGO



Our 37th Year



FREE 1958
404-PAGE
ALLIED
CATALOG

See the 1958 ALLIED 404-Page Catalog for complete listings of more than 50 KNIGHT-KITS, covering Hi-Fi, Hobby, Test Instrument and Amateur Kits. The 1958 ALLIED Catalog is your complete Buying Guide to the world's largest stocks of everything in Electronics.

Send FREE 404-Page 1958 ALLIED Catalog.

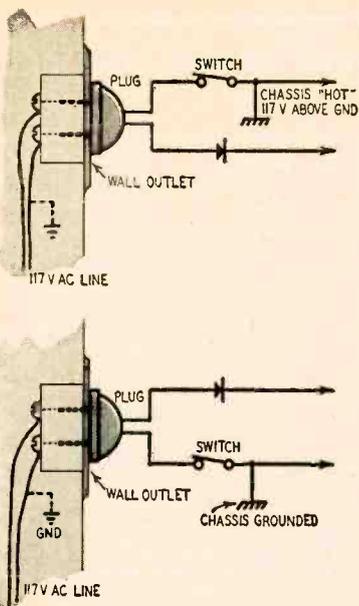


Fig. 2—With plug in one way, chassis is grounded; in other, 117 volts above ground.

(Continued from page 100)

most portable TV sets, the chassis is hot or directly connected to the line, and the metal cabinet is connected to the chassis through a capacitor-resistor network like that shown in Fig. 3. Without this network, large static charges might accumulate on the cabinet, giving anyone who touched it an unpleasant though not necessarily dangerous shock.

In a transformer set, the current from the electric line passes through the transformer's primary winding, which is carefully insulated from all other parts of the set, and through that winding only (see Fig. 4). The transformer insulation effectively isolates the secondary voltages from the line so the chassis ground is effectively separated from the line. The B-supply voltage in an ac set can be dangerous—particularly to persons with heart difficulties or with naturally damp skin—but is not so likely to be contacted accidentally because, to get a shock, one must contact two points of widely separated voltage in the receiver circuitry itself. An ac chassis is inherently "cold." Even ac equipment is not failure-proof. On rare occasions a capacitor breakdown may short one side of the line to the chassis or metal cabinet, making it hot. There are also some sets containing filament transformers or autotransformers that are not entirely isolated from the line, and so present all the hazards of transformerless equipment.

What to do about it

A number of ways to make electronic household equipment completely safe have been proposed. The Chicago authorities have suggested making a three-wire system (Fig. 5) mandatory for transformerless sets. It is standard practice for small hand-held tools and appliances, and window air conditioners. A third wire is attached to the

metal shell of the appliance and runs to a pin on a three-prong plug. It has been urged that the three-wire attachment lead presents a new hazard. Most householders do not hesitate to replace or splice line cords, even if they will not touch anything else electrical. With a three-wire cord, confusion and the possibility of wrong or dangerous connections might result. In spite of that, the three-wire line seems the surest approach to safety in home electronic and electrical equipment. The plan has one weakness. Practically no homes have the necessary three-wire receptacles and though a municipality could no doubt enforce a ruling that no equipment be sold unless fitted with three-wire plugs, it could not as easily compel homeowners to install the necessary three-prong receptacles.

This should not prevent the individual life-loving home owner from having receptacles installed for his own electric and electronic equipment. It is comparatively simple to run a three-wire line for the average TV set. The third (grounding) wire may be attached firmly under a screwhead on the cab-

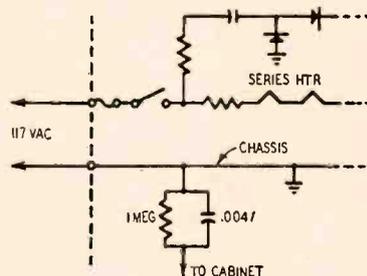


Fig. 3—A typical resistance-capacitance isolation network.

inet. The three-prong receptacle is not always so easy. The problem is to find a good earth to which it can be grounded. Most modern homes are wired with conduit, armored cable or a three-wire flexible cable with one conductor designed to act as the ground lead. In these cases installation is merely a matter of removing the two-conductor receptacle and replacing it with a three-conductor type. The third prong must be connected to the conduit, armor or ground lead, and tests made between it and a known good earth to make sure it is actually grounded.

Some cheaper homes have been wired with a two-conductor flexible cable which makes no provision for grounding, and some older houses may be wired in the ancient knob-and-tube style, with the wires widely separated and run on porcelain standoffs or through porcelain tubes. These systems do not normally have a ground lead and installing one is likely to be costly.

Even worse are the cases where houses or parts of houses are wired with ungrounded armored cable. This does happen and is the reason why all three-wire receptacles should be checked after installation to make sure the grounds are really grounded.

An apparently simpler proposal is to use two-prong polarized plugs. You may not be aware of it, but the chances are

10 to 1 that the receptacle on the wall nearest you is polarized—one slot is wider than the other. The wide slot is connected to the grounded wire of the electric system (or should be). Used with a polarized plug (one prong larger than the other) this would seem to mean that a TV or radio set could be so hooked up that the chassis would stay at ground potential. But one serious drawback stands in the way of this easy-looking solution.

The polarized plug would make a chassis safe if it were connected to the grounded side of the line at all times. Unfortunately, many pieces of equipment, including most small radio receivers and some TV sets, have the line switch between the set or chassis ground and the line. When the switch is opened, the connection to earth is broken and the whole set becomes hot (see Fig. 6-a). If the switch is on the other side of the line (Fig. 6-b) so that the hot lead is disconnected when the switch is turned off, the equipment remains connected to ground and is safe.

Another suggestion is that an isolation transformer be used. This would presumably make the set safe, but in an awkward and expensive way. The suggestion presumes that the sets are inherently unsafe, which is not the case. The weight and bulk of an isolation transformer destroy the portability of a portable TV and the cost of a large isolation transformer is high (\$15-\$20).

The technician's role

A more fruitful immediate solution is to insure that nothing in done to a TV set (or other piece of electronic equipment) that will make it dangerous. When the sets come from the factory, they are presumably safe. How do they become otherwise?

Two things can make a hitherto normal piece of equipment dangerous. One is internal breakdown, such as the shorting of a capacitor between a hot chassis and cabinet. The other is external damage or improper servicing. A cabinet can be dropped so that items that should be separated come into contact or the same result may be produced by careless servicing or inexpert tinkering by unqualified repairmen. The metal-cabinet sets, in general, have a hot chassis carefully separated from the cabinet by insulating washers or strips. A capacitor shunted by a high-ohmage resistor is usually installed be-

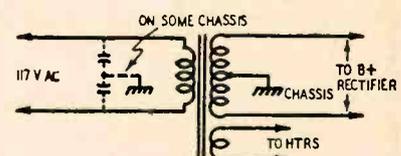


Fig. 4—Why a transformer set is safer.


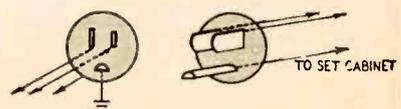



Fig. 5—The 3-prong plug has a grounded terminal.

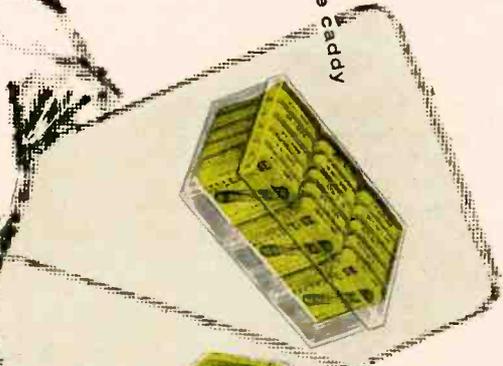


A fuse caddy for your tube Caddy



New LC fuse caddy—15 LC types

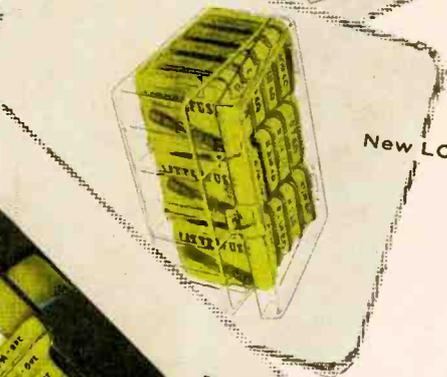

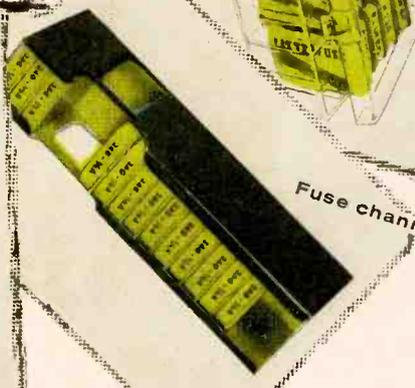Fuse channels—time saver for your fuse stock



Packaged Snap-on fuse holders for quick pigtail replacement

The right fuse—For your convenience and accuracy
Littelfuse is listed in All Howard Sam's Photofact folders and in Counttracts at your distributors.



BURTON BROWNE ADVERTISING

Draw to a Straight success with . . .

LITTELFUSE
DES PLAINES, ILLINOIS

TELEVISION

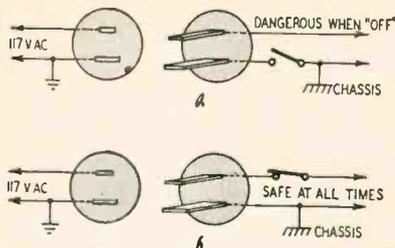


Fig. 6—Why a set can be safe turned on and dangerous turned off.

tween the negative terminal of the circuitry (normally the chassis) and the cabinet, to prevent static charges, as pointed out previously. The antenna leads may be entirely isolated from the rest of the circuitry, or may have a pair of capacitors or capacitors shunted by resistors. In the General Electric M3—presumably the chassis involved in the Skokie accident—the arrangement is as shown in Fig. 7. Shorting of any of the capacitors can cause a hot cabinet.

More serious is the possibility of mechanical contacts. Where the chassis is held to the cabinet with screws inserted through tapped nylon inserts, a long screw may make contact with hot metal. Shorts may actually be introduced by tampering with antenna isolating networks.

One manufacturer recognized the problems of metal cabinets as long ago as the introduction of the 8-inch personal portable. Instructions to the service technician for replacing the chassis in the cabinet include:

Make sure the insulating boards have been placed in their proper positions. The boards are provided to prevent any thin metal object, which may fall or be inserted through the louvres, from coming in contact with high-voltage circuits or from causing a short circuit to cabinet. [Italics ours.]

More recent instructions—on current 17-inch portables—say:


The three insulating boards—one between the lower chassis and the printed circuit, another fastened to the bottom of the cabinet back and the third the disc around the fine tuning shaft must be replaced if removed for any reason. . . . A final check should be made when servicing the receiver, to insure that no loose metal object is shorting between the receiver chassis and the cabinet. (RCA Service Data, 1957 No. T1)

No similar warnings (other than the usual hot-chassis notice) have been found in other service data so far in-

Cause of the Skokie electrocution was a short through insulation to the 135-volt B plus lead of the television chassis, a jury of experts reported after examining the set. The connection caused a combination of direct current and the 120-volt ac supply to appear between the outside cabinet and ground, the jury stated.

Probable cause of the short was stated: "The jury believes that during the factory assembly the 135-volt direct current bus was accidentally wedged between the mounting bracket and the vertical holding control.

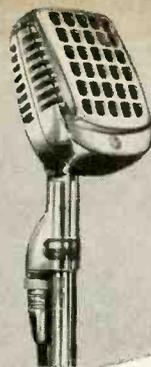The probability is very great that the deceased died of shock from simultaneously contacting the TV set and the grounded metal trim of the kitchen counter top."



UNI-DIRECTIONAL

"MONOPLEX"


MODEL 737A



SEMI-DIRECTIONAL

"SONODYNE"

MODEL 51

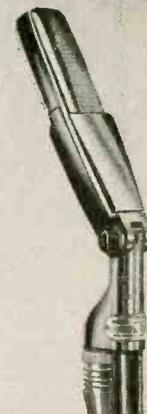

BI-DIRECTIONAL

"GRADIENT"

MODEL 315

You
have
your choice
of three

SHURE

moderately
priced
general-purpose
microphones

Where quality is essential, yet cost is a factor—
you can rely on these SHURE Microphones

FOR PUBLIC ADDRESS • HOME RECORDING •
COMMUNICATIONS • PAGING AND INTERCOM
SYSTEMS

MODEL 737A "MONOPLEX": Uni-directional, moisture-proofed crystal microphone—reduces feedback by 67%! Can be used under adverse conditions of background noise where conventional microphones would be practically useless. "Humi-seal" Crystal for trouble-free operation even in humid climates. High impedance unit with excellent response to 10,000 cps. Output -54.0 db.
LIST PRICE \$46.00

MODEL 51 "SONODYNE": Semi-directional, dynamic microphone. Switch for low, medium, or high impedance makes it three microphones in one! Ideal for recording and "close-talking" applications. Frequency response is 60-10,000 cps, Output -52.5 db. Unusually rugged microphone; can be used in any climate, indoors or outdoors.
LIST PRICE \$49.50

MODEL 315 "GRADIENT": Bi-directional high fidelity microphone with multi-impedance switch. Picks up sound equally from front and rear; is "dead" at sides. Ideal for interview broadcasting or group recording. Frequency response 50-12,000 cps. Provides exceptional voice and music reproduction. Particularly useful in installations where feedback is a problem. Output -57 db.
LIST PRICE \$85.00

All three units have rugged, die-cast metal cases and are finished in a rich satin chrome.


SHURE BROTHERS, INC.

Microphones ~ Electronic Components

212 HARTREY AVENUE • EVANSTON, ILLINOIS

"In Electronics Since 1925"

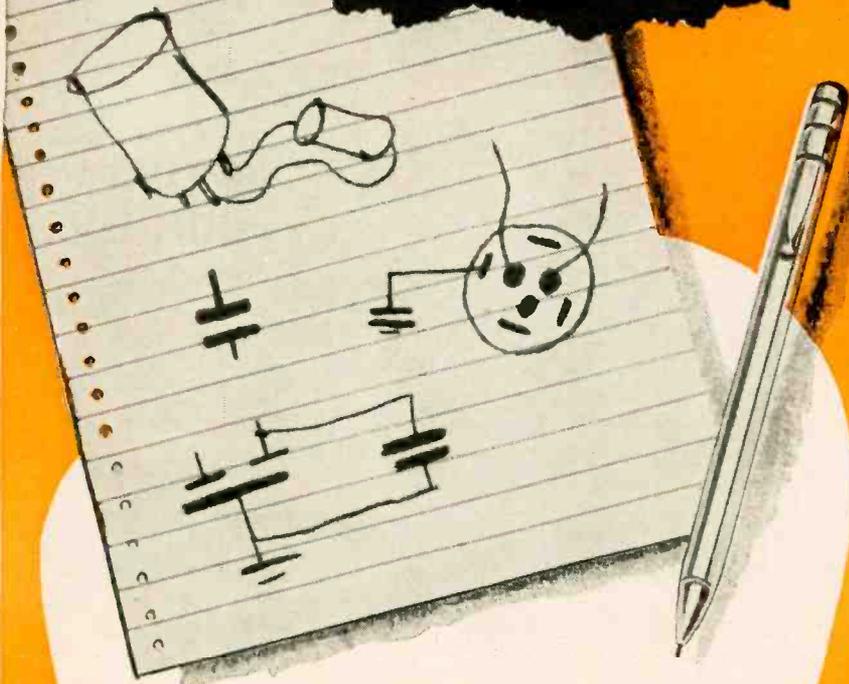P. R. MALLORY & CO. INC.
MALLORY
Clippings



*(A series of service hints
 gleaned from the notebooks
 of Mallory design and
 application engineers)*

Some replacement capacitors may be physically larger, or slightly more costly, than the original capacitors used in a piece of equipment. Still it may be preferable to use these replacement capacitors which are not "exact", rather than obsolete the equipment because "exact replacements" are not available.

For example, one or more sections of a multiple unit can be left unconnected, if not needed, without affecting or impairing the capacity or useful life of the remainder of the units.

A separate tubular capacitor can be paralleled with any section of a multiple capacitor to create a capacity section not available in stock multiple units. The lowest voltage rating of the paralleled sections must not be exceeded!

Regardless of the circuit—you can count on Mallory capacitors to do any service job—right. See your Mallory Distributor, today, and lay in a working replacement stock.

P. R. MALLORY & CO. INC.
MALLORY

P. R. MALLORY & CO. INC., INDIANAPOLIS 6, INDIANA

Capacitors • Controls • Vibrators • Resistors • Switches • Rectifiers
 Power Supplies • Filters • Mercury and Zinc-Carbon Batteries

TELEVISION

spected, but there is little doubt that most service manuals printed in the future will carry very definite warnings and information on proper precautions to be taken when servicing such sets.

Summary

It is possible and necessary to increase the TV and radio safety factor greatly by following a few simple precautions:

Make sure that the insulating medium provided by the manufacturer is not removed or damaged during servicing. If it is damaged, replace it.

After the set is installed in the cabinet, make a visual check, then finally a check from cabinet to a known ground with an ac voltmeter, with the plug in both positions in the receptacle and with the power switch in both on and off positions.

Make sure that isolating networks, especially in antenna circuits where they are more likely to be disturbed, are intact. The cabinet-ground test will check the capacitors in these networks.

The service technician or technical set owner may under some circumstances take further steps to insure safety:

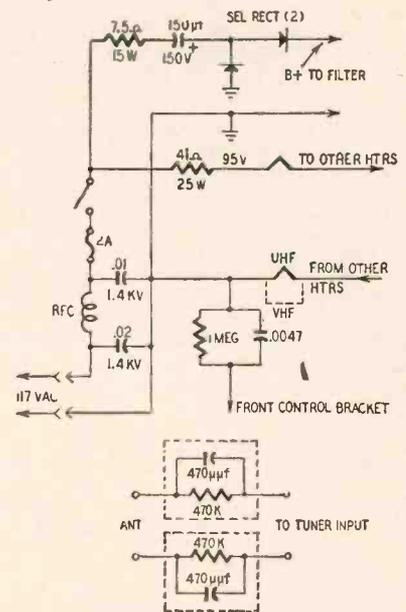


Fig. 7—Isolating networks in the General Electric M-3 chassis.

If the power switch is found to be in the hot side of the line, a two-prong polarized plug may be attached, making sure, of course, that the large prong is on the chassis side; if three-prong receptacles can be installed, a three-wire lead may be used to ground the cabinet.

Sets may be placed well away from grounded objects like radiators, bathtubs or pipes. They can also be situated well away from windows, where rain may drive in the back and temporarily short insulating boards.

Sets should be inspected immediately after any damage, such as may be caused by tipping over a portable TV stand.

Obviously, the usual procedures, such

TELEVISION

as checking for frayed line cords, should be observed and the fire hazard should not be ignored. Check for, and replace, oversized fuses and warn against installations in poorly ventilated places.

The technician may also perform another service of considerable psychological value. On completing work on a receiver, he can give the owner a statement that the equipment has been tested and found free from shock hazard. This may be typed out on the bill. At the present time, such a statement will carry considerable reassurance to the owner and may even be of value to the technician if an accident should occur some time after the equipment has been serviced. **END**

REFERENCES

Cyrus Glickstein, "Don't Be a Shock Absorber," *RADIO-ELECTRONICS*, March, 1957, page 46.
Guy Slaughter, "Murder by Radio," *RADIO-ELECTRONICS*, March, 1950, page 44.

A BRUSH WITH DEATH

The greatest occupational hazard in TV servicing is the ever-present danger of a picture-tube implosion. Although it doesn't happen too often, most technicians know the hair-raising sensation when the neck of a tube cracks or snaps off.

This may happen while a chassis is being carried and the protruding neck is carelessly bumped against a door frame or in some cases during the installation or removal of a tube from a tight-fitting yoke.

In any event, the technician is usually in a precarious position and for several seconds can do little more than hold his breath and hope . . . as he listens to the tell-tale hiss of rushing air.

On one occasion, a near-victim was driving in a coupe with a 21-inch chassis and tube on the seat beside him. The speaker was resting directly behind him, near the rear window. At a sudden traffic stop the speaker fell forward and struck the picture tube.

Of course it was all over in a split second and the driver remembers nothing more than the boom of the implosion and the awareness of flying glass. When I saw him emerge from his car a few minutes later, his head was dripping blood and he staggered dazedly.

The inside of car was a shambles with broken glass everywhere, no one piece much larger than a half-dollar. The material damage was extensive: one yoke, one flyback transformer, eight tubes, one speaker, several items on the car's instrument panel and two windows. The latter, one on each side, were apparently shattered by the impact of the flying pieces of the 1/2-inch faceplate.

The remarkable thing is that the driver wasn't seriously injured. Within this area of bombardment he escaped with only a few superficial cuts, one being on the chin, only a fraction of an inch from the throat.—*Charles G. Buscombe*

... another
MALLORY
service-engineered
product



MALLORY VIBRATORS

to meet every service requirement

1

FOR THE VERY BEST IN PERFORMANCE . . .

Mallory Gold Label Vibrators are the result of over 27 years of vibrator pioneering and leadership. Employing the exclusive Mallory buttonless contact design, they eliminate problems of sticking contacts . . . insure positive starting . . . provide far longer life . . . are unbelievably quiet. For utmost dependability, and to build your reputation for service, make Mallory Gold Label Vibrators your standard of quality.

Depend on Mallory
for vibrator dependability
—for any job



2


FOR ECONOMY JOBS . . .

The Mallory Highlander is a new line designed expressly for the jobs that must be done at a lower price. It delivers trouble-free service longer than any vibrator in its price class—second only to the Gold Label line. Ask your Distributor for the new Mallory Highlander—in the handy new 10-pack carton.


P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

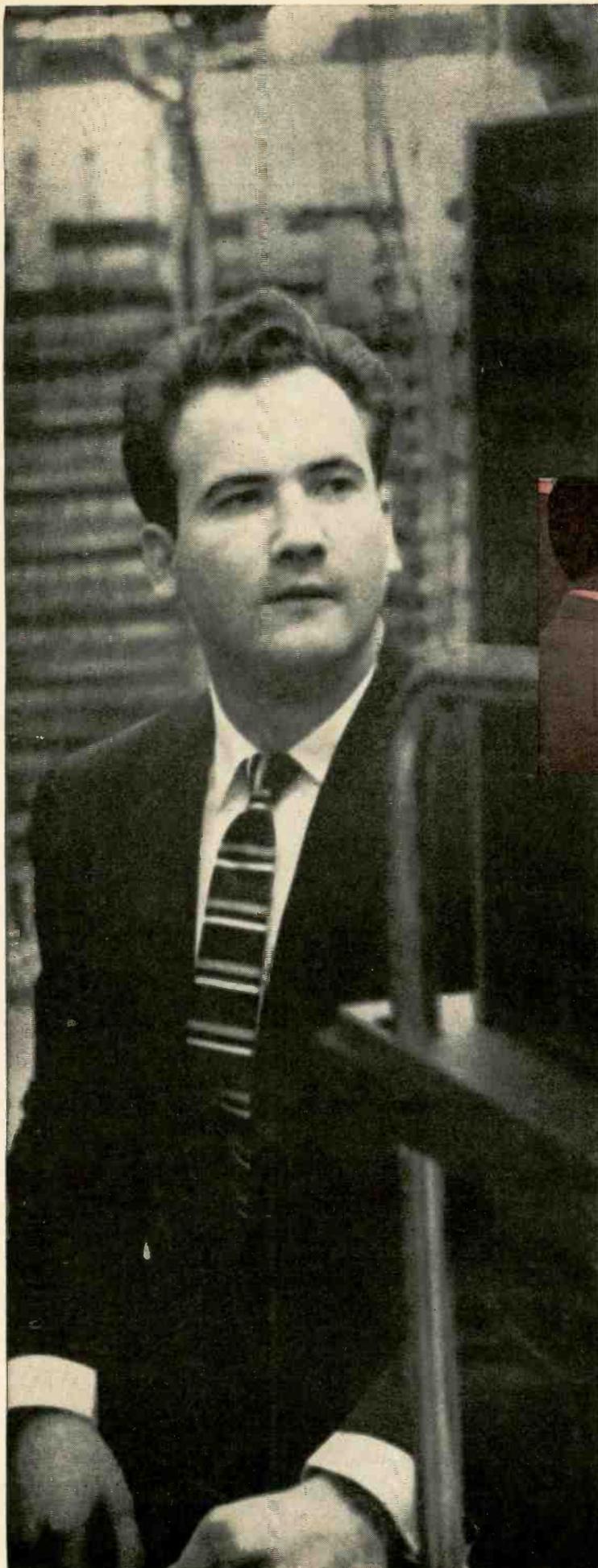- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters



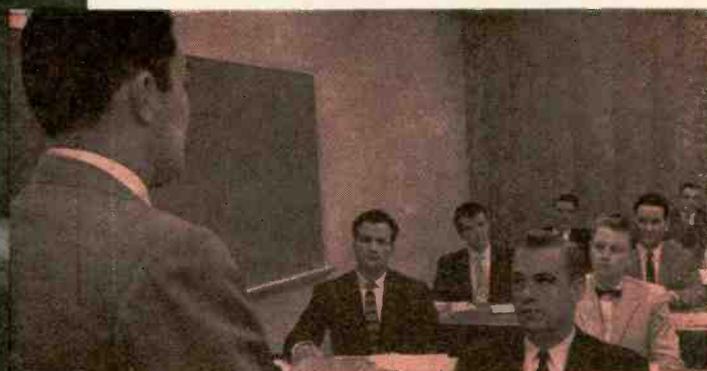How Far Can You Go in Electronics Without a Degree?



“Student” Fred Gunther in the IBM school

Fred Gunther has no degree. Yet, today, at IBM, Fred is a Technical Engineer working on America's biggest electronics project. His story is significant to every technician who feels that lack of formal training is blocking his road to the top.


Let's go back to 1950 and watch Fred Gunther, at 18, as he goes about the business of determining his life's work. Fred spent almost a year trying his hand at various jobs. None of these turned out to be the one that Fred wanted to devote his life to. So, still undecided about his career, Fred entered the Navy for a four-year hitch.

Fred learned something very valuable in the Service, as have many other men who eventually discover the electronics field. His aptitude tests revealed him as an excellent electronics prospect, and he received ten months' training in electronics fundamentals and radar. Upon his discharge in 1955, he was an Electronics Technician, First Class.

Something even more important to Fred's career occurred during his Service hitch. He began to hear such terms as “automation” . . . “data processing” . . . “electronic computer.” “Then, one evening, while glancing through the paper,” he recalls, “I spotted a story about *Project SAGE*.”

What is Project SAGE?

SAGE means Semi-Automatic Ground Environment. It is part of America's radar warning system—a chain of defense that will ultimately ring our country's entire perimeter. At the heart of this system are giant electronic computers, which digest data filtered in from Texas towers, picket ships, reconnaissance planes, ground observers. The computers analyze this information for action by the Strategic Air Command and other defense units. These computers are the largest in the world. Each contains perhaps a million parts—occupies an entire city block. They are built for the Project by IBM.

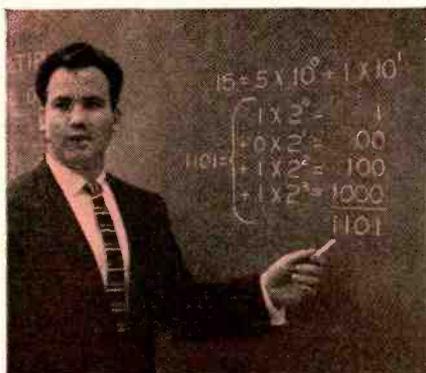

Answering instructor's questions

Fred joins IBM

SAGE fascinated Fred, for it embodies the most advanced electronic concepts in giant computer work. And, when he learned that IBM would train him at full salary, plus a living allowance, to become a Computer Units Field Engineer, he seized the opportunity. Fred started his new electronics career in the IBM school, with twenty other technicians. He attended classes 8 hours a day. Courses consisted of some 20 subjects—computer circuitry and units, maintenance techniques—everything he would need to become a full-fledged Computer Units Field Engineer.

Assigned to McGuire AFB

His training completed, Fred was assigned in May, 1956, to McGuire Field, where the first of the giant SAGE computers is located. Here he assisted in the cable installation for this vastly complicated electronic giant. He helped to set up the computer, interconnect its many sections, check it out and make it ready for operation. Fred spent five months

at McGuire Air Force Base, but his education was not yet completed.

Becoming a Computer Systems Engineer

"I like to think it was due to my interest and grade of work," Fred says, "but at any rate, last October I was invited to return to Kingston for further training—to become, in fact, a Computer Systems Engineer. Naturally, I was proud and pleased, for this training would give me a much greater range of understanding . . . make me more valuable to the company and myself . . . and give me a chance to assume actual engineering responsibility." Fred completed the



At the operating console of the computer

Computer Systems course. After several months of outstanding work in his new capacity, he received a *third* promotion—to Technical Engineer—in a field engineering liaison group.

What does the future hold?

What does the future hold for Fred Gunther, now that he has become a Technical Engineer? "It's hard to even set a goal in a field as rapidly moving as this," Fred says, "but with my IBM training back of me, the future sure looks good. I've advanced from Radar Technician to Computer Units Field Engineer to Computer Systems Engineer to Technical Engineer in two years—and received a valuable electronics education besides!"

How about YOU?

Since Fred Gunther joined IBM Military Products and the Project SAGE program, opportunities are more promising than ever. This long-range program is destined for increasing national importance, and IBM will invest thousands of dollars in the right men to insure its success.

If you have 2 years' technical schooling—or equivalent experience—IBM will train you for 20 weeks as a *Computer Units Field Engineer*.

This intensive training leads to positions of unusual responsibility. Thousands of IBM electronic engineers, graduates of this course, can vouch for its effectiveness.

After training, you will be assigned to an area of your choice within the United States. You receive *salary*, not wages, plus overtime pay. In addition, every channel of advancement in the entire company is open, and IBM is a leader in a field that is sky-rocketing in growth. And, of



Home to the family, Pemberton, N. J.

course, you receive the famous IBM company-paid benefits that set standards for industry.



WHY NOT WRITE—today—to:

Mr. N. H. Heyer, Room 3110
Military Products Division
IBM Corp., Kingston, N. Y.?

You'll receive a prompt reply. Personal interviews arranged in all areas of the United States if your résumé of experience and education indicates you have the qualifications.

IBM

**MILITARY
PRODUCTS**

- DATA PROCESSING
- ELECTRIC TYPEWRITERS
- MILITARY PRODUCTS
- SPECIAL ENGINEERING PRODUCTS
- SUPPLIES
- TIME EQUIPMENT

Practical COLOR ● Installation

Part II—Purity, degaussing and convergence are the key to Red and Fuzz discussion

By BOB MIDDLETON

NOW, before we get back to this degaussing routine," remarked Fuzzball, "which do you do first, purity or convergence?"

"From a practical standpoint, you should make up your mind right away which you are going to do," Red observed.

"So, how do I make up my mind?" asked Fuzzball helplessly.

"Maddening, isn't it?" Red grinned. "All you do is to start on the one that is out the farthest."

"That makes sense," Fuzz admitted, "but it gets confusing. One service manual I remember tells you to make good static convergence before and during purity adjustments — another tells you to make all the purity adjustments before going to the convergence controls."

Red stuck his tongue in his cheek. "If you listen to too many guys at the same time, you'll just make more business for the head-shrinker. In this racket you got to try to get the general idea of what it's all about."

"The way I understand it, then, is like this," Fuzzball mused, "if the convergence looks pretty decent but the purity is for the birds, I start to bring in the purity first. Then I touch up the convergence and ought to have it made."

"You're so right," agreed Red. "And of course, sometimes vice is versa. If the purity happens to look about right but convergence is cruddy, then you work on convergence to start with, and end with purity touchup, in case it seems like there is room for improvement."

"Likewise and furthermore," suggested Fuzz, "if they are both out quite a ways, you might have to work back and forth several times between them."

"Sometimes I feel like there is really some hope for you," Red remarked admiringly.

"OK, never mind the compliments,"

Fuzz muttered; "let's get back to degaussing."

Red inhaled a thoughtful swig of java. "Well," he said, "first you got to get a degaussing coil. Some of the screwdriver mechanics tell me you can use the ac field from a soldering gun — personally I wouldn't know anything about that."

"You got me fogged," protested Fuzz. "What's a degaussing coil?"

"Just a large air-core coil that you plug into the 117-volt ac line," Red explained. "They are stocked by some jobbers, or you can make your own."

"Could I make a degaussing coil?"

"Sure thing. Any country boy can do it. Just wind 300 or 400 turns of magnet wire—about No. 22 or 24—on a 12- or 18-inch circle and tape it up like a doughnut. Connect 8 or 10 feet of zip cord to the coil and you got it made."

"So how do I use it, in case the purity is bad on the picture tube?"

"That falls in the class of easy problems for easy boys," Red grinned.

"To listen to you," Fuzz protested sourly, "I would figure that I belong to the new generation of idiots."

"It's only one man's opinion," Red replied soothingly. "But seriously, the first thing you do is to remove the rim magnets from around the picture tube. In a Motorola set, you unsnap the magnets from their clips, and lay them aside while the tube is being degaussed. In an Admiral, you find the other type of rim-magnet arrangement—the rim magnets can be pulled back into iron cups or magnetic shunts. When the magnets are inside the shunts, there is no danger of demagnetizing them with the field of the degaussing coil."

"Suppose somebody forgets about the rim magnets?"

Red made a weak gesture. "As Confucius say, 'You have had it.' You will take so much magnetism out of the rim magnets that they won't do a job anymore."

"OK," agreed Fuzz, "I'll remember about the rim magnets. So how do I use the coil?"

"First try degaussing the tube from the front. Plug the coil into an outlet and hold it square in front of the screen for 20 or 30 seconds. Then back off slowly. When you are 6 or 8 feet away from the receiver, you can unplug the coil."

"Why this slow backing away before the coil is unplugged?" asked Fuzz with a puzzled look.

"Well, when you unplug the coil, there's going to be a spark at the contacts and a surge through the coil. It could leave the tube magnetized worse than when you started. You have to get far enough away that the surge won't affect the tube."

"Should the set be turned off?" asked Fuzz.

"Doesn't have to," replied Red, "although it could be called good practice. If you have the set on, you'll get a color pattern on the screen that's out of this world, in case you're the curious type."

"Then I recheck the purity?"

"Yep. Usually, the first treatment does it. In some cases, the tube or the tube shield or the chassis itself gets magnetized in a spot where the first treatment doesn't get it."

"What do I do when the ball bounces in that direction?"

"Well, then you have to get the degaussing coil down around the sides of the tube, and maybe under the chassis, too. But when you are working back on the tube, be sure to remove the beam magnets, lateral corrector magnet and purity magnets while you're using the coil. If you demagnetize them and have to come back to the shop for replacements, the boss will chew you out but good."

"I see where you got to use the coil with discretion," Fuzz admitted.

"You said a mouthful," Red agreed. "Just get careless once and lay the coil

TRANSMIT PICTURE and SOUND

AT ANY TIME—TO ANY TV SETS





Displays any pattern, picture, or message for TV servicing or for closed-circuit telecasting



Provides crystal-controlled, full color rainbow display for complete color TV testing



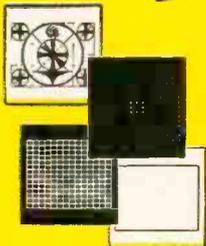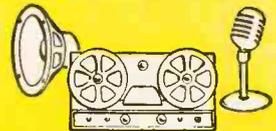Provides FM sound carrier. Has built-in audio tone generator plus input for tape, tuner, mike



3 Slide Transparencies and One Clear Acetate Supplied with Dyna-Scan Includes one Indian Head, one White Dot, and one White Line crosshatch pattern, plus one clear acetate for messages

B&K NEW MODEL 1050 **DYNA-SCAN** PORTABLE VIDEO and AUDIO GENERATOR

THE FLYING SPOT SCANNER produces a composite video and sync signal that operates any standard black & white or color TV receiver, at any VHF television frequency. Reproduces your own test pattern or picture on the TV screen with high definition, anytime, anywhere, from any slide transparency—or transmits messages typed or written on clear acetate. Can be used with one or more TV sets or fed into a master or community antenna system. Maximum resolution capability is well in excess of 450 lines at video.

BUILT-IN COLOR-SCAN provides crystal-controlled, full color rainbow display of orange, red, magenta, blue, cyan, green. Enables you to test color sync circuits—check range of hue control—align color demodulators, etc.

BUILT-IN AUDIO-SCAN provides FM sound transmission exactly like a TV station, 4.5 megacycles above video carrier, with modulation from any available audio source. Enables you to combine speech or music with the video display. Can be modulated with built-in 400 cycle tone generator for test signal or from external signal source such as microphone, tape recorder, FM - AM tuner, or from audio oscillator. Has built-in audio amplifier and volume control.

Facilitates servicing, installation or demonstration of black & white and color TV receivers. Provides closed-circuit TV system with both video and audio for commercial, industrial, and educational applications. Allows convenient stand-by and break-in, or distribution line check, for community antenna system operation.

Model 1050 DYNA-SCAN complete portable video and audio generator, with built-in Color-Scan and Audio-Scan. Includes 3 test pattern slide transparencies, one clear acetate and slide holder. Comes with 6 ft. r.f. cable. Size 16½ x 10¾ x 9½ in. Net, **\$259.95**

Model 1000 DYNA-SCAN picture and pattern video generator. Has all the features of the Model 1050 above, except without the Color-Scan and Audio-Scan sections. Net, **\$199.95**

Color-Scan or Audio-Scan or both can easily be added to the Model 1000 at any time.

Model C15 COLOR-SCAN for Model 1000. Net, \$19.95

Model S16 AUDIO-SCAN for Model 1000. Net, \$29.95

Available from most Electronic Parts Distributors on easy time-pay plan.



MODEL 1000



C15


S16

See your B&K Distributor, or write for Bulletin 1050-E

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois

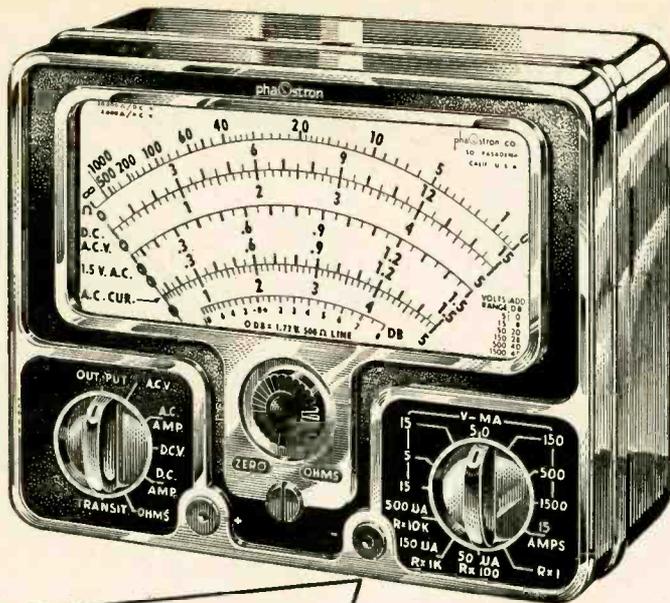Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont. Export: Empire Exporters, 439 Broadway, New York 13, N.Y.





555A VOM

YOU NEED THESE FEATURES:

Meter Movement Protection up to 500 times overload is provided by a rectifier network.

The 555A Measures: AC Current, DC Current, AC Voltage, DC Voltage, Output, Resistance

43 Unduplicated Ranges

Separate Range and Function Switches

Double Magnetic Shielding

3% DC, 4% AC Permanent Accuracy

Easy to Read, Four Color Scales 4 7/8" long

Metal Case with Die Cast Bezel 6 1/8" x 4 5/8" x 2 1/8"

Sensitivity: 20,000 Ohms/Volt DC, 2000 Ohms/Volt AC

NEW LOW PRICE

Not \$49.50, but priced lower than ever before. Complete with probes and batteries. (Replaces former model 555)

NOW ONLY

\$44⁹⁵

PHAOSTRON INSTRUMENT AND ELECTRONIC COMPANY

151 Pasadena Avenue, South Pasadena, California

TELEVISION

near a meter, and you're in hot water. That meter will read low and can't be used until it goes back to the factory for repair."

"How does a picture tube get magnetized, anyhow?" Fuzz asked.

"Lots of ways. Some guys forget and use magnetized tools around a color set. If you get screwdriver-happy, you'll have a degaussing job right away. Sometimes a guy forgets and lets a PM speaker get close to the picture tube. Some meters have an external field that causes trouble if the meter is rested on the tube or shield. Then, there are cases that you just can't tie down—the set has been running OK but the purity gradually gets out and can't be adjusted unless a degaussing job is done."

"I reckon I ain't too sharp, but I'm hep," Fubb remarked. "Then what comes after the purity adjustments?"

"Can't figure whether you're bragging or complaining," Red replied. "But we ain't quite through with this purity deal yet. In most cases, the green and blue fields will come in OK after you get good red purity. You will find cases though where you may have to compromise a little in purity adjustments for the three fields."

"How do you compromise?"

"Well, you work back and forth between the three fields and always favor the red as much as possible. The customer will be most critical of the flesh tones because the actors carry the action and their faces are the center of attention. That's why you should balance the purity in favor of the red field, when necessary."

Fuzz pulled a bottle of aspirins out of his pocket and handed it to Red. "Have two," he offered; "they're small."

"It isn't really that bad," Red replied. "There's headaches all right, at the start, but when you get enough practical experience this color setup is a breeze."

"What else should I know about the purity adjustments?" asked Fuzz.

"That's about it. As a final check, balance up the three screen controls for a neutral gray raster and see if there is any tinting anywhere on the screen. If you see any you will know that you slipped a little somewhere along the line. Sometimes, when the tinting is very minor at this point, you can make the final purity touchup on the gray raster without going back to the individual color fields."

"Then we get with the convergence," Fuzzball suggested.

"Well, this is where you come to the pièce de résistance, as you might say. For the first few days, you're going to figure that color TV is a comedy of errors, and wonder if you have all your buttons."

"I'm listening."

"OK. It's easy enough to get good convergence in the center of the screen by adjusting the three beam magnets and the lateral corrector. Getting convergence at the top and bottom and

Bull's-eye every time!

MODERN DESIGN

VERSATILE


DEPENDABLE

TIME SAVING

We hit the target again . . .
with this new, modern version of the
most wanted service-test instrument.

Pyramid introduces the CRA-2 Capacitor-Resistor Analyzer, a versatile, up-to-date, moderately priced test instrument. The CRA-2 is the perfect multi-purpose analyzer for the technician, serviceman and engineer, in industrial and military electronics, black and white, and color television, and all related fields.

The guesswork has been removed from circuit trouble shooting. When making leakage-current measurements, the values are read directly from the meter while the rated operating voltage is applied to the capacitor. A vacuum-tube ohmmeter circuit displays accurate insulation-resistance values on the meter for many types of capacitors. The extended range calibrated power factor control permits power factor measurements of electrolytic capacitors rated as low as 6 volts DC working and as high as 600 volts DC working. This special "QUICK CHECK" circuit performs rapid "IN CIRCUIT" test for short, open, intermittent high RF impedance and high power factor without removing or disconnecting the component from its operating circuit.

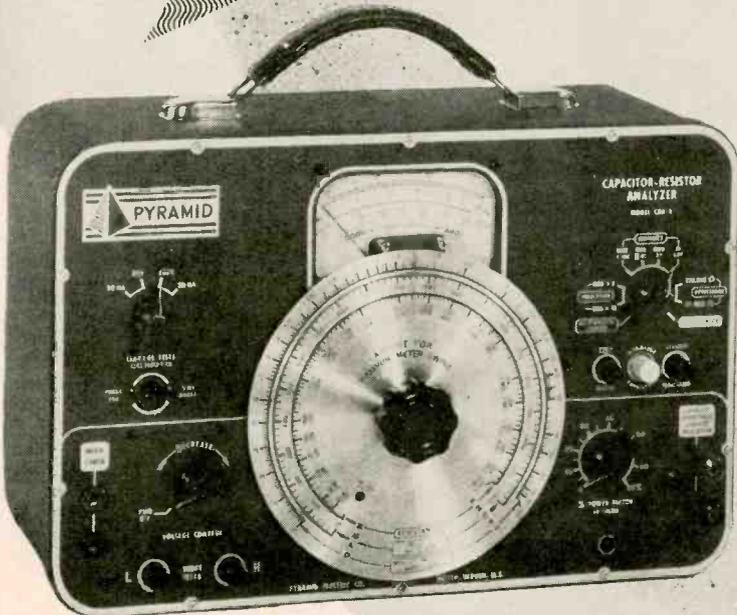

FEATURES

- ▶ "Quick Check" in circuit test for Open Circuits. Short Circuits. Intermittents. High RF Impedance. High Power Factor.
- ▶ Speedily and accurately checks: Capacitance. Power Factor. Resistance. Insulation-Resistance. Leakage Current.
- ▶ Precision meter for accurate readings of leakage current, applied voltage and insulation resistance.
- ▶ Combination Wien and Wheatstone bridge.
- ▶ Accurate vacuum-tube meter circuit.
- ▶ Parts of the highest quality are used. Wire and wiring meet military specifications.

Examine it today
Being introduced by leading Electronic Parts Distributors

PYRAMID ELECTRIC COMPANY

1445 Hudson Blvd., North Bergen, New Jersey



Using the degaussing coil on a color TV installation.

sides of the screen is a horse from a different garage—this is where the dynamic convergence controls come in.”

“So I turn on the white dot generator now.”

“Reet. And make blame sure that the generator is synced in at 15,750 cycles.”

“Why is that so important yet?” Fuzz asked.

“Simply because the horizontal phasing coils are turned to resonance with the horizontal sweep frequency, as I will explain. Obviously, if your white dot generator is locking in a hundred cycles or so off frequency, you will mistune the horizontal phasing coils—you can converge the picture tube but, when you tune in a black-and-white program, the tube will be out of convergence on the left- and right-hand sides and the customer will complain about rainbow fringing.”

“I see what you mean. Then I’ll go bats doing the dynamic convergence all over again.”

“That’s it,” Red agreed. “A guy could end up in a padded cell.”

“So how can I be sure the white dot generator isn’t a white elephant generator?”

“Well,” said Red, “there are several ways. Some generators have horizontal sync and some don’t. If the generator doesn’t have sync, you have got to supply sync from a black-and-white station transmission—the instruction book for a generator of this type explains how to do this.”

“But,” suggested Fuzz, “if the dot generator has its own sync, I have nothing to worry about.”

“Not if you use your head for something besides a hat rack,” agreed Red. “You will find that some generators provide a crystal-controlled sync oscillator and you have nothing to check out. Other dot generators use a vfo sync oscillator with a control on the

instrument panel for setting the sync frequency.”

“Is it a job to set the sync to the right frequency?” asked Fuzz.

“It’s easy enough,” Red replied, “if you watch the screen pattern while you’re adjusting the sync frequency. All sets have at least a trace of 60-cycle hum in the circuits and when the vertical sync is zero-beat with the power line, there is no writhing or movement in the dot pattern. But, if the vertical sync is not zero-beat with the power-line frequency, you’ll see more or less snaking in the pattern.”

“Clue me in here,” Fuzz protested. “We started talking about setting the horizontal sync frequency in the generator and now you talk about the vertical sync rate.”

“It’s simple enough,” Red explained. “The horizontal sync and vertical sync in this type of generator are locked together—if one is right, the other is correct too.”

“I got you now, Red. The station operates its own vertical sync in step with the power-line frequency, I heard somewhere.”

“You heard right,” he agreed.

“What size dots are best?” Fuzz asked next.

“Frankly, I can’t answer that one,” Red admitted. “So much depends upon the particular situation and personal preferences. On some of these color sets, you have to make some or all of the convergence adjustments from the rear, using a mirror in front on the screen.”

“That’s where large dots will come in handy,” Fuzz suggested.

“As a matter of fact, you may not be able to see small dots at all in a mirror, unless you darken the room like the inside of a cow. You better have a pretty good mirror, too.”

“Guess though, if I had a helper along

in a case like that, he could tell me how the pattern looks from in front,” Fuzz remarked.

“Only after you have both had plenty of experience,” Red shot back. “Otherwise you will find out quick that you are not talking each other’s language.”

“Small dots would give you a more accurate check on convergence, wouldn’t they?”

“They’d tend to,” Red agreed. “Don’t forget too, that it will be a cold day in July when you get a picture tube 100% converged. The trick is to know when to stop.”

“When would that be?” Fuzz asked.

“Well, as a general rule, if you can’t see any misconvergence when you are 5 feet back from the screen, you probably have convergence about as close as you are going to get it.”

“Suppose the customer complains, though, about not having 100% convergence?”

“We have an almost irresistible urge to shoot him right at the beginning,” Red advised him. “I generally put his name on the stink list, and tell him I’m all booked up the next time he calls.”

“Not to get off this fascinating subject of customer beefs,” Fuzz said, “but I been hearing a lot about white crosshatch for convergence. What’s the scoop?”

“Well, I like it for at least certain parts of the job,” Red replied. “However, I can get along very nicely with white dots only. Seems to be partly a matter of opinion, I would say.”

“I know that we have juggled with at least a dozen dynamic convergence controls,” Fuzz remarked. “Where do I start?”

“We covered the beam magnets and the lateral corrector for center-screen convergence,” Red replied, “and the main thing to keep in mind here is that these static convergence controls, as they are called, produce exactly the same motion of a color dot at any point over the entire screen.”

“Then the dynamic controls cause nonuniform dot motions,” Fuzz suggested.

“That’s what they do. The first rule is to keep the three color dots converged at all times in center screen while working the dynamic controls to bring in the dots around the edges of the screen.”

“I smell something here,” Fuzz announced. “Do you mean that the dynamic adjustments will interact with the static adjustments and throw the convergence out at center screen?”

“You are so right,” Red replied. “Convergence is a matter of continual back-and-forth adjustments. That’s one of the reasons why it eats up so much time.”

“Clue me in a little more on these dynamic controls.”


“Well, you have the dynamic group for vertical—usually six controls. Then you have the dynamic group for horizontal—again usually six controls. In some cases you may also have a couple of yoke balancers for final touchup.”

FINCO® announces

MODELS UNLIMITED!

NOW ... you can sell a TV Antenna designed for your area

| | | | |
|-------------------------|---------------------------|-----------------------------|--------------------------|
| | BUFFALO SPECIAL | SYRACUSE-ROCHESTER SPECIAL | DUO-DIRECTIONAL SPECIALS |
| | SAN DIEGO B-6 | CHICAGO SPECIALS | PITTSBURGH SPECIAL |
| LONGVIEW, TEXAS SPECIAL | VICKSBURG SPECIAL | FLORIDA, WEST COAST SPECIAL | GEOMATIC SPECIALS |
| | PATENTED FIDELITY PHASING | DETROIT-TOLEDO SPECIAL | MODEL B-8 |
| UHF-VHF SPECIALS | MODEL B-66 | | |
| MODEL B-7 | FRONT-TO-BACK SPECIALS | | |

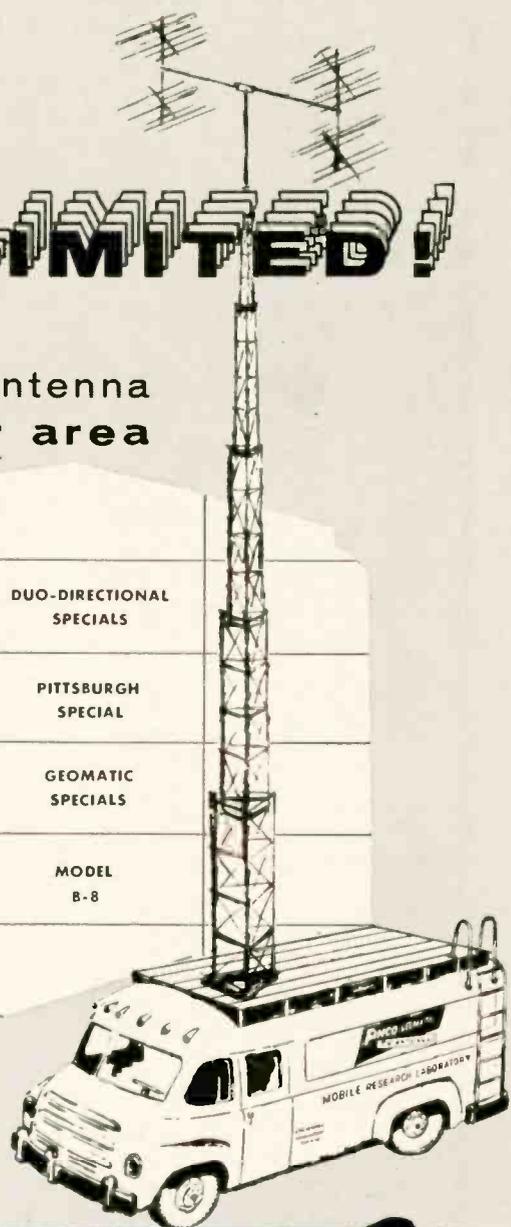

• IN SOLVING UNUSUAL, LOCALIZED RECEPTION PROBLEMS, FINCO has proved that the only positive way to develop the most efficient and economical TV Antenna is by actual MOBILE RESEARCH LABORATORY TESTS combined with Expert Topology and Channel Power Plotting.

If a distributor qualifies, Finco's research department assumes the task of studying the specific, local reception problems. If the problems can possibly be solved the result is an exclusive Red-Hot, High-Profit Hi-Performance Antenna For Your Area —

Hundreds of FINCO research projects are now in process or already completed, giving dealers and servicemen a big jump on their competition. The total cost to your Jobber IS HIS COOPERATION ... urge Your Jobber to write, wire or call FINCO TODAY!

FINCO®

is often imitated ...

the leader always is!



FINCO®


THE FINNEY COMPANY • 34 West Interstate Street • BEDFORD, OHIO • Telephone: BEDford 2-6161

Copyright 1957, The Finney Co.

Form No. 20-199

SNOWY PICTURE?

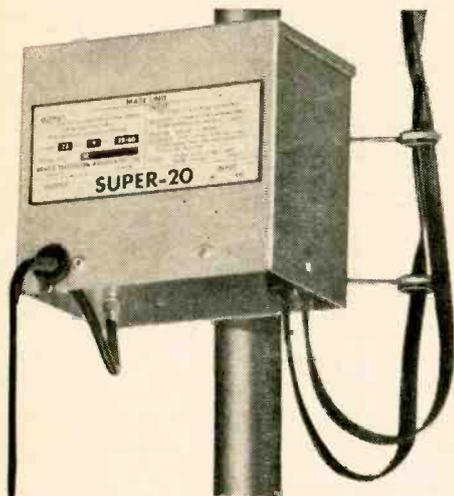
TRY THE **BENCO**
LOW NOISE
SUPER '20'
MAST-MOUNTED
BOOSTER



- Very Low Noise Cascade Circuit Brings Weak Snowy Pictures to Entertainment Level.
- Automatic ON-OFF from TV Receiver
- Easily mounted on Mast
- Supplied Complete with all Connectors (Solderless)
- 20 DB Gain
- Contains separate 3-tube Amplifiers for High and Low Bands (3 Dual Triodes).
- Amazing Low Price

\$45.00
Suggested
User Net

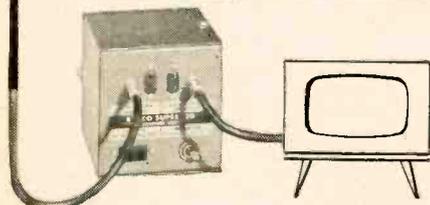BENCO research engineering has its eye on the future. We're proud of our large new plant and facilities where we are producing the finest VHF and UHF Pre-amps, Crystal Converters, Solderless Tap-offs and Line Amplifiers. Write for full information.



USE THIS HANDY COUPON

Benco Television Associates Ltd.,
27 Taber Road
REXDALE, Ontario, Canada

- Please send me complete details on the SUPER "20"
- Other Equipment for Hotels, Motels, Apartments and Community Systems

Name

Address

City..... State.....
Prov.....

TELEVISION

"Which do I start in with first?"

"It's customary to start vertical dynamic convergence first. You pick out a column of dots down the center of the screen and start making vertical dynamic adjustments to converge this column of dots—forget the others."

"Why do we work on just the center column of dots?"

"Simply because convergence at the left- and right-hand sides of the screen is affected much more by the horizontal controls, and you will go all around the mulberry bush if you pay any attention to them at this point in the procedure."

"I see," said Fuzz. "How about filling me in on the vertical controls?"

"Well, we have them grouped into red, green and blue controls. We have a tilt and an amplitude control for each color—total of six."

"They interact with each other?"

"Unfortunately, yes. You will seldom be able to make a final adjustment once and for all on any one of these controls," Red observed.

"Now, judging from the names, I guess the tilt controls will make the column of color dots slant one way or the other."

"You're partly right," Red agreed, "but you're partly wrong, too. The red and green tilt controls produce some slanting or tilting of the dot column, but the dot motions are complex and there is more than tilt in the movement. Moreover, the blue tilt control has no tilting action whatsoever—it changes only the relative spacing of the blue dots."

"This is intriguing," Fuzz commented. "Do you figure that color TV will ever get off the ground?"

"It is off the ground, buddy," Red replied somewhat sharply. "I can play the violin, too. You and I are up against the maintenance of color sets in the field right now."

"I ain't giving you any static, Red," Fuzz apologized; "I'm confused."

"Everybody gets confused in this racket until they get some practical experience. You remember the first black-and-white set you worked on."

"Amen," Fuzz grunted.

"Now to get back, the amplitude controls adjust the amount of parabolic current flowing through the convergence coils, and the tilt controls adjust the amount of sawtooth current in the coils."


"What does that mean in English?"

"Practically, what you do is to work back and forth on the amplitude and tilt controls to get the red and green dots in parallel columns, because they can then be brought into a straight single vertical column with the beam magnets."

"What about the blue dots?" asked Fuzz.

"We don't have to even look at them, if we don't want to, while we are lining up the red and green dots. In fact, some techs cut off the blue gun during this time."

"You mean that the blue dots will

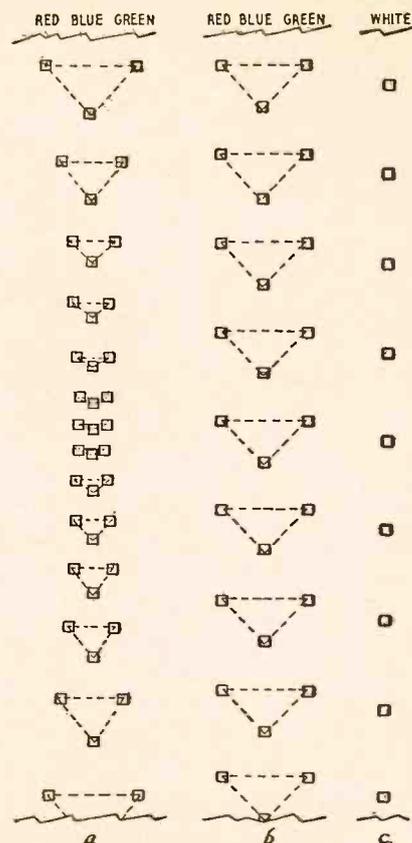

Vertical dynamic convergence of one line of dots: a—pattern when starting; b—red, blue and green dots lined up in parallel columns; c—convergence completed, only white dots can be seen.

come in OK once the red and blue dots are straightened up?"

"Right. The blue dots always line up straight in a vertical column because of the mounting of the convergence pole pieces. And since the green and red dots must line up straight in a vertical column when they are adjusted to be parallel, we don't have to worry about the blue dots to start with."

Fuzz scratched his head a moment. "So it looks like the final adjustment will be work with the blue vertical amplitude and tilt controls to bring them into convergence with the yellow dots."

"That's the general idea," Red agreed. "Remember, you have to touch up the beam magnet adjustments while you are doing this. You will also find that every time you make a considerable adjustment of the blue controls, you will probably have to go back and make a little touchup on the red and green controls."

"I'm kind of shook up," Fuzz announced, "but I'm still game. What next?"

"That pretty much ties down the vertical convergence until after the horizontal convergence has been made. Then you will probably have to retouch the vertical controls."

"Before we go ahead," Fuzz suggested, "I think we owe ourselves another coffee."

Red held up two fingers. "Garçon, draw two." TO BE CONTINUED

for the Right
'LYTIC replacement
... use an exact
SPRAGUE replacement



YOU GET EVERYTHING IN A SPRAGUE TVL! *Every* TVL for *every* voltage rating is made with the more expensive high-purity etched-foil anode construction using ultra-stable film formation techniques. Cathodes are etched to meet high ripple requirements. Sprague TVL's give maximum trouble-free service—NO HUM—as well as long shelf life. And they perform just as well in the cold North as they do in the sub-Tropics. Yet this premium quality costs you no more!

That's why Sprague Twist-Lok[®] electrolytic capacitors are the first choice of leading radio-TV set makers and independent service technicians alike. Insist on TVL's for more exact ratings . . . quality that meets original equipment specifications . . . and all the latest results of capacitor research. Write for catalog C-612.

don't be vague . . . insist on

SPRAGUE[®]

world's largest independent capacitor manufacturer


SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER CAPACITORS FOR YOU

Sprague Products Company • Distributors' Division of the Sprague Electric Company • North Adams, Massachusetts

TV Service CLINIC


conducted by

ROBERT G. MIDDLETON

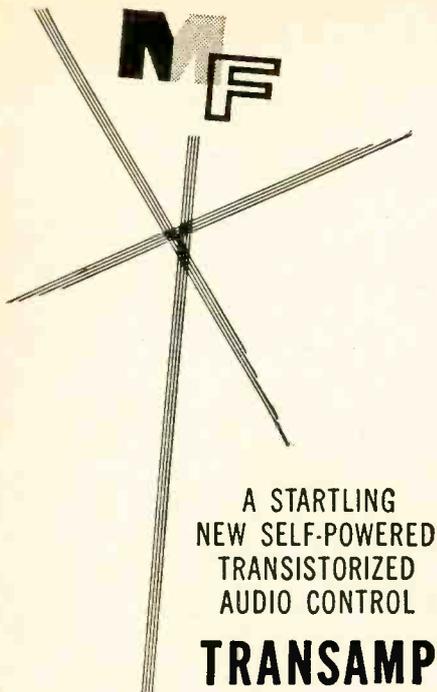

A STARTLING
NEW SELF-POWERED
TRANSISTORIZED
AUDIO CONTROL
TRANSAMP

MADISON FIELDING PRE-AMPLIFIER PR-45

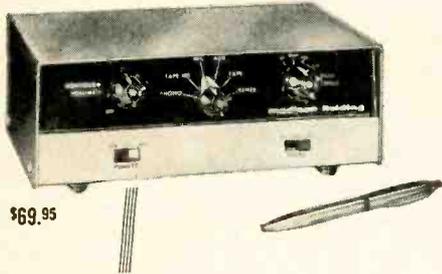

\$69.95

ALL-TRANSISTOR FRONT END

Completely eliminates HUM and MICROPHONICS.

MATCHED FUNCTION OUTPUT CONTROL

Selects either 1 or 3-volt output for best Signal-to-Noise Ratio when used with ANY BASIC AMPLIFIER regardless of rated output or sensitivity.

MINIATURIZED CHASSIS

Measures only 8" by 5 1/4" x 2 3/4" with completely separate power-supply.

CHECK THESE FEATURES

HUM — Non-Measurable.

NOISE — Non-Measurable in 1-volt position.

GAIN — 10 mv in phono for 3 volts at 1000 cps.
100 mv in tape and tuner positions for 3 volts output.
300 mv in Aux position for 3 volts output.

FREQUENCY RESPONSE — Plus or Minus 0.25 db, 20 tp 20,000 cycles.

FILTERING — Rumble and Noise Filters with 12/db octave slope. Rumble: 50 and 100 cycles; Noise: 4 and 8 kilocycles.

TONE CONTROLS — Variable crossover feedback type.

DISTORTION — For 1 volt output; in the order of 0.2%

LOW IMPEDANCE OUTPUT

EQUALIZATION — RIAA in phono, with settings for LP, AES, and EUR. NARTB 7 1/2" per second tape playback characteristics.

For complete catalog see your local dealer or write

MADISON FIELDING CORPORATION
Creators of Distinctive Audio Instruments

861 Madison Street, Brooklyn 21, New York

PICTURE analysis is one of the most useful tools in troubleshooting color TV receivers. Every distortion in picture reproduction has a reason behind it and, if you are on your toes, a lot of time which would otherwise be wasted in hit-and-miss approaches can be saved.

Here are some of the more basic elements of color picture analysis:

Horizontal rainbows

Each rainbow shows that the color subcarrier oscillator is 60 cycles off frequency. Thus, a picture with one horizontal rainbow shows that the color subcarrier oscillator is running 60 cycles above or below 3.58 mc.

A picture with two horizontal rainbows shows that the oscillator is running 120 cycles above or below 3.58 mc.

Let's consider the single horizontal rainbow. If the oscillator is exactly 60 cycles off frequency, the rainbow will stand still. But if the oscillator frequency is slightly less than 60 cycles, the rainbow drifts downward. On the other hand, if the oscillator frequency is slightly higher than 60 cycles, the rainbow drifts upward. Here's why:

When the oscillator is exactly 60 cycles off frequency, the oscillator returns to its starting phase at the beginning of each vertical scan. In other words, the rainbow repeats itself exactly at the beginning of each vertical scan—the rainbow stands still.

But when the oscillator frequency is slightly lower than 60 cycles, the rainbow is a bit incomplete at the end of the vertical scan and is completed only after a portion of the next scan has been completed—the rainbow thus drifts down the face of the picture tube.

If the oscillator frequency is slightly greater than 60 cycles, the rainbow develops faster, and more than completes itself in one vertical scan. For this reason, the rainbow drifts up the screen.

As the oscillator frequency goes up, the rainbow drifts up faster and faster until we cannot see it any more and the color seems to have dropped out of the picture—when red, green and blue flash past our eyes at a speed greater than

the persistence of vision, the colors blend into a gray.

When the oscillator frequency becomes still higher and approaches 120 cycles, we see two rainbows drifting down the screen. At exactly 120 cycles above 3.58 mc, the two rainbows stand still. A slight increase in oscillator frequency, and they start to drift upward.

Thus, by counting rainbows and observing their drift, we can quickly determine how many cycles the oscillator is off frequency, and whether it is higher or lower than burst frequency.

Match Gonset line

What is the best way to match 450-ohm Gonset line to 300-ohm ribbon? One manual says to split the Gonset line, tapering it down to the 300-ohm line over a span of 30 inches or more. This is difficult and slow.—R. L. B., Bluefield, W. Va.

This is a good question (and we like 'em!) because it brings out some of the practical considerations in impedance matching which are sometimes overlooked. In the first place, you are working with a SWR (standing-wave ratio) of 1.5 to 1, on the basis of nominal impedance ratings. This is splitting the old hair a bit thin, for the following reasons:

1. Some 300-ohm ribbon line does have a characteristic impedance very close to 300 ohms. But, on the other hand, some of the stuff measures much higher or much lower. If you want to be sure of what you are trying to match to what, better get a really good sweep generator and check the lines

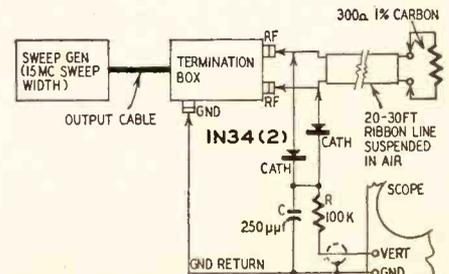


Fig. 1—Method of checking SWR. Ground return lead carries rf currents and must be kept very short.

New Transcription-Type Tone Arm Makes *Collaro* World's First True High Fidelity Changer



The Turntable That Changes Records

From Collaro, Ltd., world's largest manufacturer of record playing equipment—comes the most significant development in the field in years—the new transcription-type tone arm.

This arm, exclusive with Collaro, literally changes the conventional record changer into a brand new instrument—a TRANSCRIPTION CHANGER—with features of the finest professional equipment.

The arm is a one-piece, spring-damped, counter-balanced unit which will take any standard high fidelity cartridge. It is free of any audio spectrum resonances. It permits the last record to be played with the same low stylus pressure as the first. Between the top and bottom of a stack of records there is a difference of less than a gram in tracking pressure as compared with 4 to 8 grams on conventional changers. Vertical and horizontal friction are reduced to the lowest possible level. These qualities, found only in the Collaro Transcription Changer, insure better performance and longer life for records and styli.

In its superb performance, the new Collaro Continental, Model TC-540, meets the rigid requirements for high fidelity

equipment. Here, for the first time in a changer is professional quality at a record changer price. The Continental is \$46.50. Other Collaro changers are priced from \$37.50 up. (Prices slightly higher west of the Mississippi.)

In addition to the new tone arm, the Collaro Continental features include: 4 speeds, manual switch for turntable operation; wow and flutter specifications—0.25% RMS at 33 $\frac{1}{3}$ RPM—superior to any changer in the world; automatic intermix; automatic shut-off after last record; heavy duty 4-pole, shaded pole induction motor; heavy rim-weighted balanced turntable; muting switch and pop-click filter for elimination of extraneous noises; jam proof machinery; pre-wiring for easy installation; attractive two-tone color scheme to fit any decor; tropicalization to operate under adverse weather and humidity conditions; easy mounting on pre-cut board or base; custom testing at the factory for wow, flutter, stylus pressure and correct set down position.

FREE: Colorful new catalog describes complete Collaro line. Includes helpful guide on building record collection.

ROCKBAR
Corporation


WRITE TO
ROCKBAR CORPORATION

Dept. D-010

650 Halstead, Mamaroneck, N.Y.

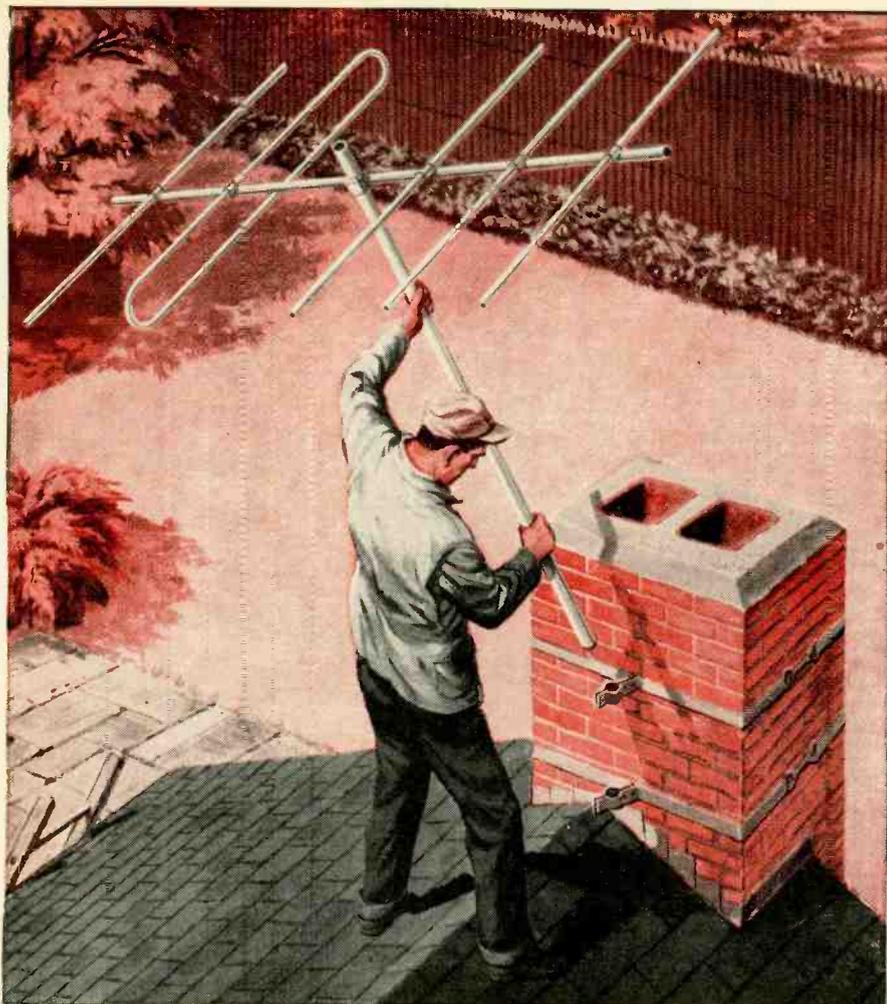Rockbar is the American sales agent for Collaro and other fine companies.





sturdy, steel **PERMA-TUBE** lasts three times longer than galvanized TV masting

Resistance to bending in Perma-Tube TV masts is greater than in galvanized masting. Perma-Tube's extra resistance to bending and damage by wind-force protects your reputation and improves TV reception.

Machine-fitted joints speed field assembly, insure close tolerance. *Perma-Tube joints are stronger than the tubing itself.*

Perma-Tube is corrosion-proof. It is treated with vinsynite—then coated with a metallic vinyl resin base both *inside and outside*. It successfully passes ASTM's 500-hour

minimum salt spray test—which guarantees longer life under corrosive conditions.

Five diameters of fitted joint Perma-Tube are available, ranging from 2½" OD to 1¼" OD. Telescoping masts can also be erected up to 50 feet high, using 10 foot lengths of high strength J&L 16-gage Perma-Tube.

For complete details on easy-to-sell Perma-Tube TV masting, write to the Jones & Laughlin Steel Corporation, Dept. 496, 3 Gateway Center, Pittsburgh 30, Pennsylvania.



Jones & Laughlin
STEEL ... a great name in steel

TELEVISION

with a series demodulator probe (see Fig. 1) against precision (1%) carbon resistors. You may possibly be surprised when you find out what you are trying to match to what.

2. Even if you find that you are really concerned with matching 300 ohms to 450 ohms, how about the SWR in the rest of the system? That is, if you sweep each terminated section of the system, do you find SWR's in the order of 1.2 to 1, or perhaps more like 3 to 1 or 5 to 1? It is only logical to make certain that we are not swallowing a camel, while gagging at a gnat. Fig. 2 shows the extremes of patterns encountered in SWR tests.

When the trace touches the zero-reference line, as in Fig. 2-b, the SWR is infinite. That is, any peak voltage divided by zero is infinite.

You will obtain this pattern when the end of the line is open or when it is dead shorted. However, the phase of the null shifts, of course, along the base line for a short, as compared with an open.

To measure SWR, we divide the maximum voltage (or current) by its minimum value, as shown in Fig. 3, taken from the AARL Handbook. When the minimum is zero, we have an infinite SWR.

When you are working on a very long section of line, the loss is appreciable. This can also be measured. Short the end of the line and then note the voltage by which the pattern *fails* to touch the zero-volt reference line. This amount is *double* the line loss.

On short lines, such as 20 or 30 feet, we can't even see the loss, and we forget about it. The pattern is given purely in terms of VSWR (voltage standing-wave ratio).

A dc scope is as useful as a zero-volt reference line from a scope because the resting position of the beam with no signal applied shows us the zero-signal level, which can be drawn on the screen with a wax pencil.

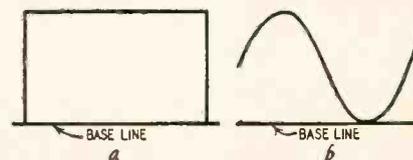


Fig. 2—*a*, Rectangular pattern shows perfect match of line to load; *b*, sine-wave pattern touching base line shows complete mismatch—dead short or wide open.


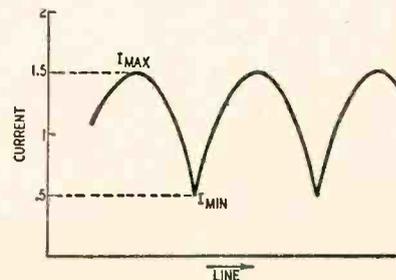



Fig. 3—Measuring SWR: I_{max} is 1.5 and I_{min} is 0.5, so SWR equals $I_{max}/I_{min} = 1.5/0.5 = 3$ to 1.

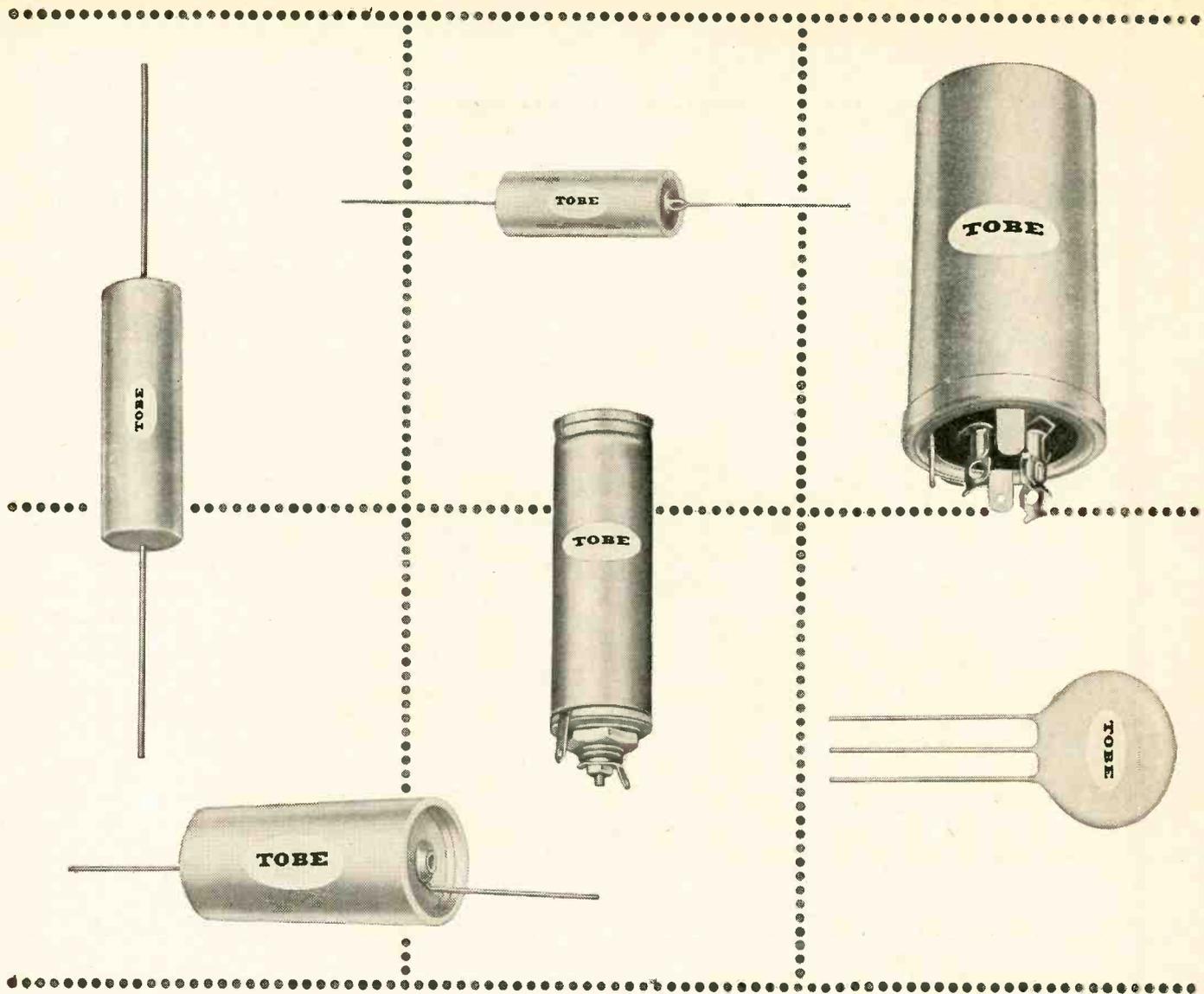

thousands of servicemen have happily discovered

TOBE QUALITY SERVICE CAPACITORS

have you?

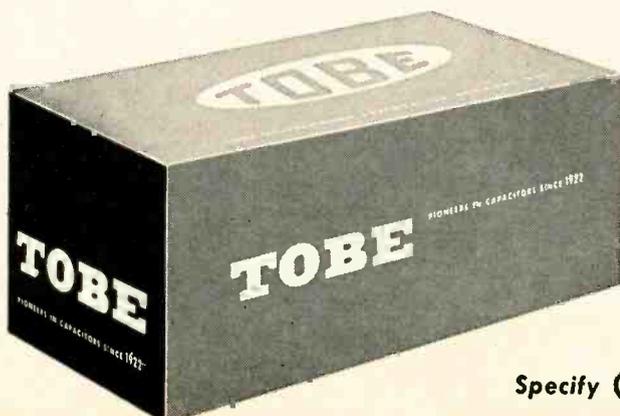

Specify **TOBE** Capacitors • Pioneers since 1922

COMPLETE RADIO-TV SERVICE TRAINING

at a price you can easily afford!



This famous Ghirardi Service Library

**TELLS YOU HOW—!
SHOWS YOU HOW!**

If broken into "lessons" and sent to you as a course, you'd regard these 2 great books as a bargain at \$100.00 or more! Instead, you get them both for only \$13.00 . . . with 3 months to pay! Almost 1500 pages and



over 800 how-to-do-it charts, diagrams and pictures show step-by-step how to handle every phase of troubleshooting and servicing.

Radio & TV TROUBLESHOOTING & REPAIR

A complete service training and "expertizing" course for only \$7.50

Here, in one giant, 822-page book is absolutely complete, fully modern training in professional service methods.

Radio & Television TROUBLESHOOTING AND REPAIR teaches you to handle ANY trouble in ANY TV, Radio, Communications Receiver or Record Playing Equipment. No meaningless theory. Instead, it gets right down to brass tacks in guiding you through service procedures . . . from locating troubles quickly to fixing them fast and right. Block diagrams, oscilloscope patterns, quick summaries of problems and other features speed your work . . . make every step doubly clear.

For beginners, it is an easily understood training course. For experienced servicemen, it is an ideal way to develop better troubleshooting techniques and shortcuts and to find quick answers to problems.

Here are some of the basic subjects: Component Troubles; Basic Troubleshooting Methods; Shortcuts, Tips and Ideas; Complete Guide to TV Service; Realignment Made Easy; Servicing FM, Communications Receivers & Special Equipment; Auto Radios; Loudspeakers; Tuner and Switching Mechanisms . . . and dozens more, 417 clear illustrations. Price only \$7.50. See MONEY-SAVING OFFER.

Handy troubleshooting charts save you loads of time!

Even experienced servicemen will find these a big boon! Time-saving, easily-understood Troubleshooting Charts include TV Trouble Symptoms and Their Causes; General Troubleshooting; Car Receivers; Radio Front Ends; IF and Detector Sections; AF Amplifier & Loudspeaker Sections; AM & FM Realignment; Record Changers; Component Troubleshooting . . . and others.

Radio & TV CIRCUITRY & OPERATION

Learn circuits . . . and watch service headaches vanish!

It's amazing how much easier and quicker you can repair radio and TV sets and even special electronic equipment when you know all about the circuits that are used. That's where this big 669-page book Radio & TV CIRCUITRY AND OPERATION is worth its weight in gold to servicemen who want to forge ahead.

You locate troubles in lots less time . . . because you know exactly what to look for and where. You make repairs better and faster . . . because you eliminate useless testing and guesswork. You qualify for good-pay jobs . . . because you have the circuit "know how" that really pays off.

Covers every circuit commonly used in modern equipment plus many puzzling circuit variations. Teaches you to understand their peculiarities and likely troublespots. Over 110 pages explain Television from scanning to signal to every detail of each of the sectional receiver circuits. Price \$6.75 . . . or see MONEY-SAVING OFFER in coupon.

Brings you the complete "know how" of: AM . . . FM . . . R-F Amplifiers & R-F . . . AM Superhets . . . AM Detector and AVC Systems . . . PB Tuning and AFC Systems . . . A-F Amplifiers . . . Speakers . . . Power Supplies . . . Television . . . Antenna Systems . . . Pickups & Record Players . . . Changers . . . Receiver Construction . . . and lots more.

PRACTICE 10 DAYS FREE!

Dept. RE-107, RINEHART AND COMPANY
232 Madison Ave., NEW YORK 16, N.Y.

Send books checked for 10-DAY FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing. (NOTE: Send cash with order and we pay postage. Same 10-day return privilege with money promptly refunded.)

MONEY SAVING COMBINATION

- Radio & TV Troubleshooting and Repair (\$7.50)
 Radio & TV Circuitry and operation (\$6.75)

Both books only \$13.00 . . . you save \$1.25. Payable at rate of \$4 (plus postage) after 10 days and \$3 a month thereafter until \$13.00 has been paid.

Name:

Address:

City, Zone, State:

OUTSIDE U.S.A.—\$8.00 for TROUBLESHOOTING AND REPAIR; \$7.25 for CIRCUITRY AND OPERATION; \$14.00 for both. Cash with order only. Money refunded if you return books in 10 days.

TELEVISION

The center frequency of test depends on the frequency you are interested in. It might be channel 2 or 13 or 75. The sweep width of the generator should be sufficient to throw a maximum and a minimum on the screen. Otherwise, the tuning dial of the sweep generator can be rocked a little back and forth, to run both onto the pattern.

If we find that this 1.5-to-1 mismatch is our camel, it is quite possible to bag the beast. The method of matching the 450-ohm line to the 300-ohm line depends upon the particular channel or channels to be accommodated.

In case several channels are to be received, the instruction to split the Gonset wire line and to graduate the spacing down to that of the 300-ohm ribbon is the most practical solution.

However, if only one channel is to be received, you can make up a quarter-wave matching section which is mechanically more convenient than a tapered line.

The impedance of the matching section should be 365 ohms, which can be obtained by using No. 12 wire spaced 1 inch between centers. The length of the matching section must be equal to a quarter wavelength of the picture carrier on the desired channel.

For general tests, I have found the RCA WR-59 sweep generator hard to beat. The output is acceptably flat, the output cable is terminated with a center-tapped load which greatly facilitates use of the double-ended demodulator probe, and there is enough output voltage on the high channels that you can really work with it.

SWR and impedance-matching tests are difficult or impossible with many sweep generators which are highly touted by their manufacturers. One of the hidden faults to be guarded against is the presence of spurious frequencies in the output which can vitiate the test. For example, if we are checking an rf tuner for match on channel 7, and the sweep generator has strong spurious outputs on channels 2 and 13, our test is little more than a farce.

Few technicians seem to realize how essential a really good sweep generator is for the accomplishment of any serious test work.

High B plus

I replaced the focus-coil circuit in an Olympic 766 with an equivalent resistor and PM focus control to correct a condition of too high voltage from the B-plus power supply. This did not have any effect on the voltage, which still remains about 70 volts too high. The resistor is a variable wirewound type and, no matter where the slider is set, the voltage remains the same.

Lifting the B-plus lines off the bleeder also has no effect on the B-plus voltage. Is the trouble in the power supply?—A. J. K., Milwaukee, Wis.

The fact that you can lift the B-plus lines off the bleeder with no effect on the supply voltage suggests that the bleeder is open. If the bleeder has con-

TELEVISION

tinuity and normal resistance, there must be some change (at least a little drop) in the voltage value when the bleeder draws current from the supply. I would suggest that you check the bleeder for an open circuit before proceeding further.

Long-range reception

My problem is I am trying to receive channels 9 and 11 at a distance of 105 miles from New York. Here in Philadelphia we have a powerful station on channel 10. I can receive 10 without any antenna at all. Hence, the chief problem is to keep channel 10 from interfering with the weak signals on 9 and 11. Should I use a double-stacked traveling wave or a 10-element Yagi cut to 9 and 11? Also, is a booster really helpful, or does it just boost the noise?—V. D., Philadelphia, Pa.

You may find that you will have difficulty in trying to receive channels 9 and 11 from New York with any type of antenna since you are receiving 10 without an antenna. Adjacent-channel traps may be insufficient in this case, and you may have to enclose the chassis in a screen box.

Any unbalance in the lead-in can also be very troublesome in a case like this, and you may find it advisable to use shielded 300-ohm ribbon lead. The outer braid of the lead-in is grounded to the screen box.

A double-stacked traveling-wave antenna would ordinarily be a good choice, although in this particular situation its high gain on channel 10 could work against you. The fact that 10 is not in line with 9 and 11 in your location does give you a certain advantage in the front-to-back ratio of the traveling-wave antenna. An experimental installation would be required to determine if the available rejection would be adequate.


A Yagi cut to 9 and 11 can be designed to have a deep dip through 10 and, if used with shielded ribbon lead and possibly a screened chassis, would seem to be the most conservative selection in your particular situation.

A booster will give you a definite advantage if it is installed at the antenna and if the booster itself has a low noise figure. The cascode type of booster is one of the types with low noise. Any booster installed at the receiver end of a long down lead will have to contend with the line noise, which may be appreciable. To make certain that you are getting the maximum signal-to-noise boost, it is advisable to make the installation at the antenna terminals.

Vertical nonlinearity

I have a Crosley model H-21COWH receiver that has a bright horizontal stripe moving up across the picture. It is almost 1/2 inch wide and other than this the entire picture is fine. I have replaced the vertical linearity control but this did not help. All capacitors and resistors have been checked

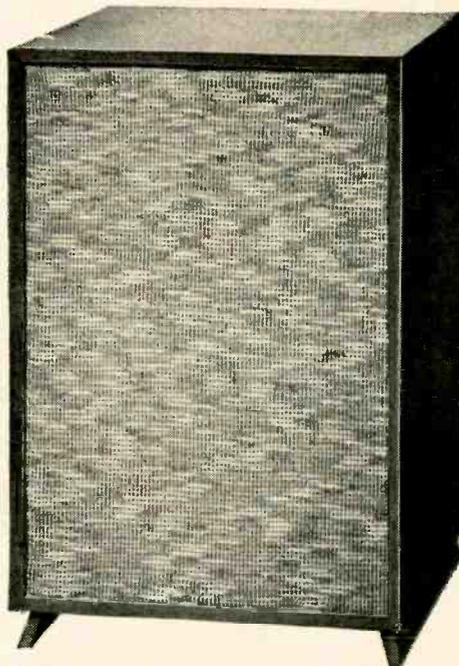NOW! A TRUE COAXIAL SPEAKER SYSTEM: ONLY \$79.50




The Sonotone "110" Loudspeaker System

Only system in this price range to give you all these big-cabinet features:



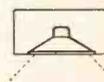True 2-speaker coaxial... 2 separate drivers... inductor-capacitor dividing network... full frequency range.



Speakers radiate *directly* for wide dispersion, true "presence"... cabinet can be placed *anywhere* in room.



"Rectilinear" vent enables startlingly vivid low-frequency performance equal to many larger-cabinet systems.



Hand-rubbed cabinet in choice of 3 fine finishes... ideal size for most homes (and for true 2-system stereo).

Interested? Wait till you *hear* it! Ask your dealer to demonstrate the "110." Send in the coupon below for full details!

Cabinet: 30" x 14" x 20"—Available in mahogany, blond or walnut hand-rubbed finish on birch. Shipped with CA-12 installed. Shipping weight: Approx. 50 lbs.

Price: **\$79.50**

Slightly higher in the West

Speaker: CA-12 12-inch coaxial
Power handling capacity 10 watts
Frequency range 40-14,000 cycles
Resonant frequency 50 cycles
Crossover frequency 2000 cycles
Impedance 50 ohms
Flux density 12,000 gauss

SONOTONE® CORPORATION

Electronic Applications Division
Dept. LE-107
Elmsford, N. Y.

Sirs: Please send me full details on the "110" loudspeaker system.

Name _____

Address _____

City _____ Zone _____ State _____

Excitingly new!


DX-16 Super Deluxe TV KIT

For the CUSTOM-BUILT CHASSIS that even a high school student can build.

The DX-16 SUPER DELUXE TV KIT is a worthy successor to the famous #630 TV KIT . . . a product in which we took a leading role. In designing and engineering this NEW KIT, we used the #630 as a standard of comparison for POWER, STABILITY and FRINGE AREA RECEPTION . . . resulting in a NEW TV CHASSIS equal in performance and with even greater versatility.

NEW IN DESIGN

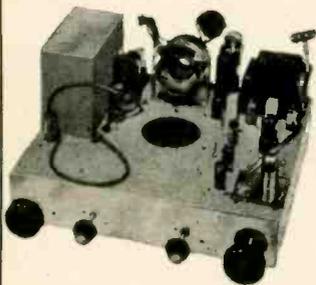Mounts Horizontally, Vertically or Sideways



Dimensions 17 1/2" W x 16" D
Shipping weight 52 lbs.

- ★ Produces a 16-Tube Chassis with 30-Tube performance.
- ★ Latest Intercarrier Circuitry and Multi-section Tubes.
- ★ Standard Cascode Tuner for Selectivity and Fine Definition.
- ★ 16KV—Operates 21" and other size 70° Picture Tubes.
- ★ 5 Microvolts Sensitivity (20V peak to peak at CRT grid).
- ★ Fast Action AGC for Drift Free, Steady and Clear Pictures.
- ★ 3 Hi-gain Video I.F. Stages for fine Contrast and Details.
- ★ AGC Level Control, for adjusting reception to signal area.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Latest circuits for Full Horizontal and Vertical Blanking.
- ★ Large 250ma Power Transformer for dependable service.
- ★ Large 12" Concert-tone Speaker.

COMPLETE KIT with LIFE-SIZE step-by-step Assembling Instructions (less tubes & CRT) **\$69.97**

COMPLETE WITH SET OF **WESTINGHOUSE TUBES** (less CRT) **\$79.97**


COMPLETE WITH SET OF **WESTINGHOUSE TUBES** and **WESTINGHOUSE 21YP4A Aluminized CRT** **\$99.97**

WESTINGHOUSE OR CBS PICTURE TUBES

BRAND NEW in Factory Sealed Cartons—With a Full Year Guarantee

| | | | |
|------------------------------------|---|---|---|
| 17" ^{70°} #17BP4A \$22.66 | 21" ^{70°} #21YP4A Aluminized \$32.21 | 24" ^{90°} #24CP4A Aluminized \$48.99 | 27" ^{90°} #27EP4A Aluminized \$74.31 |
| ^{90°} #17VP4A Aluminized | ^{70°} #21EP4B Aluminized | | |

BUILD YOUR OWN TV CABINET

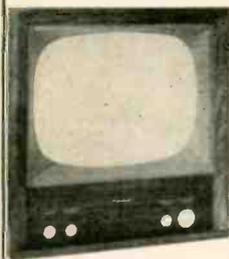


Comparable to the type that Top Mfrs. use on their high priced TV Sets. Prefabricated for you—is the FRONT PANEL as pictured with mask and safety glass (knob panel supplied undrilled) and TOP and SIDES cut to size, all in a satin finish in mahogany, walnut or blond. Nothing extra for any finish. Included is an amazing booklet of easy to follow step-by-step instructions. FRONT PANEL sold separately for TV Wall Mounting or for use in modernizing old TV Cabinets that used round or smaller CRT's.

| | |
|-----------------------------------|---------------------------------------|
| 21" TV CABINET | 24" or 27" TV CABINET |
| FRONT PANEL 25" W x 26" H \$17.45 | FRONT PANEL 28 1/2" W x 30" H \$22.97 |
| TOP and SIDES 7.50 | TOP and SIDES 9.50 |
| \$24.95 | \$32.47 |

UNIVERSAL Picture Tube MOUNTING BRACKETS

Fits All 1 1/2" to 2 1/2" Picture Tubes

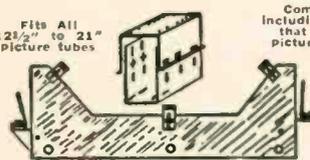

Complete including band that holds picture tube

\$6.97

TV CRYSTAL-CLEAR LUCITE MASKS

Framed in Rich Goldleaf Finish

| Tube Size | Overall Dimensions | Price |
|-----------------------------------|--------------------|---------|
| 17"—Rectangular 13 1/8" x 16 1/2" | | \$ 4.56 |
| 21"—Rectangular 16 1/8" x 21 1/4" | | 6.92 |
| 24"—Rectangular 20 1/4" x 25 1/4" | | 11.84 |
| 27"—Rectangular 20 1/4" x 26 1/4" | | 12.18 |

On 17" and 21" specify type number of CRT used

TV PLASTIC OPEN MASKS

Used in conjunction with safety glass

| | |
|-----------------------------------|--------|
| 17"—Rectangular 15 3/4" x 18 1/2" | \$1.49 |
| 21"—Rectangular 18" x 22 1/2" | 2.38 |
| 24"—Rectangular 21" x 26" | 4.93 |
| 27"—Rectangular 21" x 26" | 4.93 |

On 17" and 21" specify type number of CRT used

TV SAFETY GLASS in HANDY SIZES

| | |
|----------------------------|--------------------------------|
| 16" x 20" \$2.94 | 18" x 22 1/2" \$5.16 |
| 16" x 22" 3.97 | 21" x 26" 5.87 |

*Available in new tinted grey 50c extra

21" TV CONVERSION KIT

NOW . . . Anyone with even a limited knowledge of TV—can Convert any Size, any Make TV RECEIVER to operate 21" or any 70° Picture Tube.

COMPLETE SET OF ESSENTIAL PARTS includes matched set of Todd 70° COSINE DEFLECTION YOKE and TODD HV FLYBACK TRANSFORMER, FOCALIZER, 20KV FILTER, DRIVE TRIMMER, LINEARITY COIL, CONDENSERS, RESISTORS.

Your Price **\$13.97** List Price \$33.50
Incl. CONVERSION MANUAL with Step-by-Step Instructions & Diagrams

SIMILAR KIT for 24", 27" or any size 90° CRT. **\$15.98**

PULSE KEYED AGC KIT

Finest, most accurate and the easiest Kit to Install in any make TV RECEIVER including the No. 630. Improves performance and insures a steady picture on all channels.

COMPLETE SET OF PARTS **\$4.59**
Including 6AU6 tube & Instructions

STANDARD CASCODE TUNER

For better all around performance Complete with tubes and Brooks CASCODE MANUAL with step-by-step Instructions and all extra parts needed. **\$15.97**

#630 TECHMASTER

COMPLETE LINE AT SPECIAL PRICES
Video Theatre TV . . Hi-Fi Kits
Catalog mailed on request

TELEVISION

and none are bad. I also replaced the vertical output transformer but this gave no improvement in the linearity. Varying the linearity control changed the width of the horizontal line a little, but not nearly enough. The output of the vertical oscillator looks good on my oscilloscope and so it appears that the trouble is in the vertical output stage. But I am at a loss as to what the trouble might be.—T. F., Orlando, Fla.

The symptoms you describe point very strongly to 60-cycle interference in the vertical output stage. I assume that you have replaced the 12BH7 output tube and we can most likely eliminate heater-cathode leakage as the cause of the compressed lines or nonlinearity. The vertical movement of the bright horizontal line is due to the fact that your local power line is not synchronized with that of the transmitted sync pulses. This trouble is not unusual in this chassis, and in a synchronous area the horizontal bar will remain stationary.

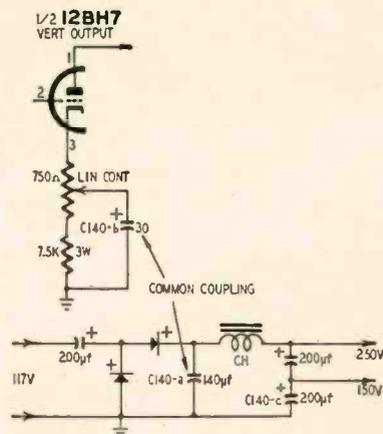


Fig. 4—Leakage between units of a multiple-section capacitor in half-wave doubler and video cathode bypass causes 60-cycle interference and one white bar.

The cause of the trouble is the common coupling between sections a and b of C140 (Fig. 4). Section a introduces a power supply component into the vertical sweep output circuit. This condition can be corrected simply by clipping the lead from C140-b and connecting a new 30- μ f capacitor rated at 150 volts. As long as you are making this change, if your area is subjected to appreciable variations in ac line voltage, use a larger capacitor of about 80 μ f. This will minimize changes in vertical linearity at the top of the picture caused by line-voltage fluctuations.

END

Next Month's
TV Clinic
•
That First
Color
Service Call
•



FOR RESTAURANTS, NIGHT CLUBS
Neat, trim, unobtrusive, the MLC is a superb little performer too. Delivers clean, sweet music and voice reinforcement that overcomes noise and dead spots.




SOUND AND AMUSEMENT TRUCKS
The versatile, dependable MLC efficiently handles all types of program material without harsh, annoying blare prohibited by many town ordinances.



PATIOS, SWIMMING POOLS, LAWNS
Here's weatherproof high fidelity that is also low in price. With the MLC, you can economically extend a music system outdoors and retain hi-fi quality.



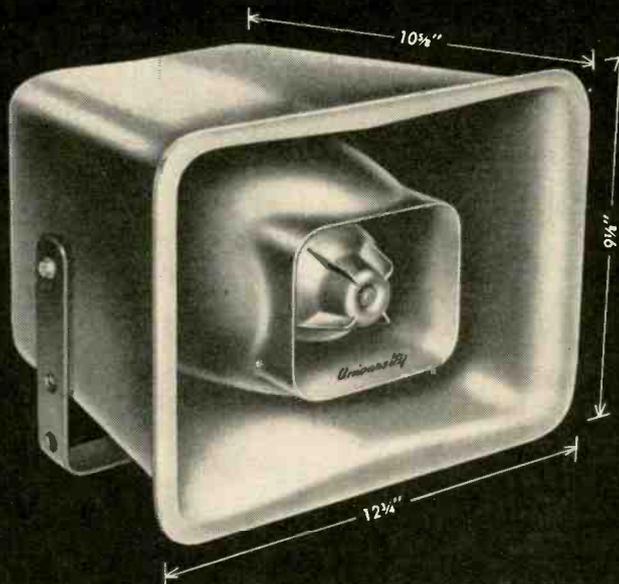TO ADD HI-FI TO P.A. SYSTEMS
In paging applications, the MLC penetrates high noise levels... its wide frequency range adds deep richness to music reproduction. Here's double duty, double value!



MODEL

NEW...UNIVERSITY DUAL-RANGE MLC

Weatherproof Super-Compact Speaker System for Voice and Music

Now...real high fidelity never before available in a rugged, small size, weatherproof speaker system. Unique wide-angle, dual folded horn design with separate low and high frequency drivers. Dependable, easy to install, low in cost, the MLC offers these outstanding features:

BETTER LOWS: Balanced "compression" folded horn, starting with 6" throat and energized by top quality woofer driver provides *more* lows than other designs.


BETTER HIGHS: Driver unit tweeter with wide angle horn transmits more highs with greater uniformity... high frequency response that you can hear!

BETTER EFFICIENCY: Dual range theater type system permits uncompromising design of the woofer and tweeter sections for greatest efficiency. Penetrates noise with remarkable fidelity and intelligibility.


LESS DISTORTION: *Separate* low and high frequency driver systems reduce intermodulation and acoustic phase distortion found in other systems which use two different horns on a single diaphragm.

MORE DEPENDABLE: Experienced mechanical engineering and careful electrical design meet the challenge of diversified application and environmental hazards. Rugged and conservatively rated—you can *rely* on the MLC.

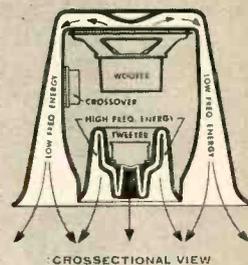SPECIFICATIONS: Power Capacity, 15 watts; Frequency Response, 150-15,000 cps; Impedance, 8 ohms; Dispersion, 120°; Sound Pressure Level, 117 db taken at 4 ft., 750-1250 cps with 1 cps sweep; Dimensions, Bell Mouth 12 3/4" W x 9 1/4" H, Overall Depth 10 3/4"; Shipping Weight, 10 lbs.; **\$54.50 List.**




FOR HEAVY DUTY APPLICATION...

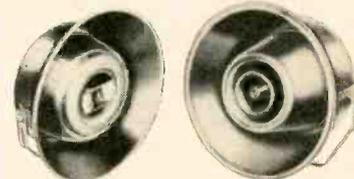

MODEL BLC employs same design principles as the MLC except for heavy duty 8" woofer with uniform response from 70 cps. exclusive "reciprocating flare" wide-angle tweeter and has 25 watt power capacity. Exceptionally shallow depth, only 9", ideal for close quarters. **\$86.00 List.**

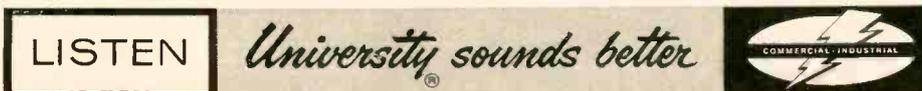MODEL WLC, largest of the series, has 30 watt power capacity, 12" super-efficient woofer with response from 50 cycles, heavy duty radial tweeter... and a decade of successful performance in concert halls, rinks, auditoriums, stadiums and outdoor theaters throughout the world. **\$250.00 List.**



UNIVERSITY LOUDSPEAKERS INC., 80 SOUTH KENSICO AVENUE, WHITE PLAINS, N.Y.

MODERN FLYBACK CIRCUITS

By JESSE DINES*

A better knowledge of how the three main types operate can simplify some of your service problems and eliminate others

THE several variations of high-voltage and horizontal deflection systems used in TV receivers include the rf, isolation-transformer, autotransformer and direct-drive arrangements. All of these (except the rf) perform the same basic functions—production of sawtooth sweep current for the horizontal yoke coils, boost voltage for the horizontal output and other stages, high voltage for the second anode of the picture tube, filament voltage for the high-voltage rectifier. Flyback systems may also be designed to provide any, or a combination, of the following: age pulses, afc pulses, horizontal blanking pulses, horizontal linearity control, picture width control, horizontal centering. All functions of the system occur simultaneously.

The rf supply (high-voltage system) was used extensively with 10- and 12-inch picture tubes prior to the advent of the 630 chassis. In this system an rf oscillator supplies energy to a separate transformer which produces the high voltage for the picture-tube second anode. The disadvantages of this system are the interference created (due to oscillator radiation) and the relatively great number of component parts. This led to its early extinction.

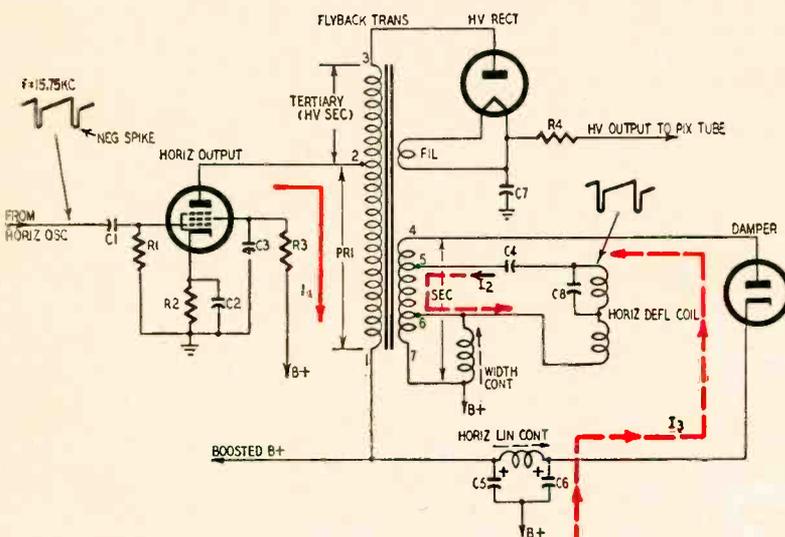


Fig. 1—Typical flyback circuit using isolation transformer.

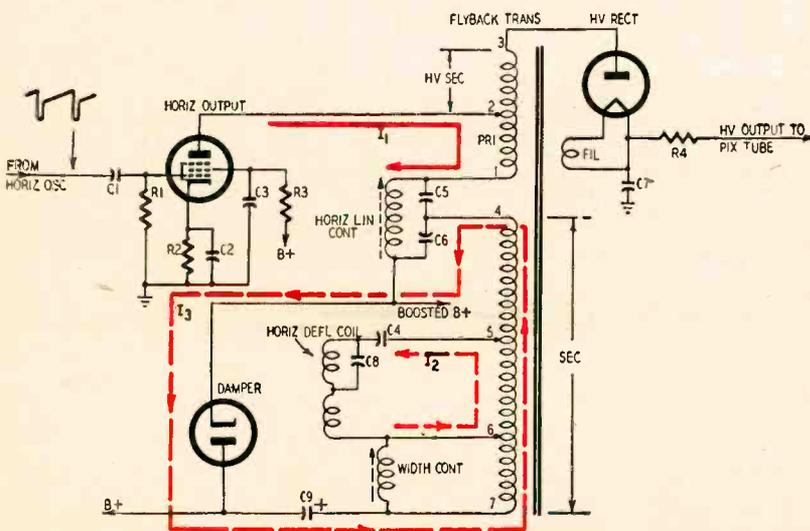


Fig. 2—Horizontal sweep circuit using an autotransformer.



Isolation type flyback

This circuit (Fig. 1) made its appearance with the 630 chassis and is still used in some of the very newest TV sets. The horizontal output tube supplies voltage pulses to the flyback transformer. The flyback transformer matches the relatively high impedance of the horizontal output tube with the low impedance of the horizontal yoke and provides additional windings and taps to connect other components such as the width coil. Pulses appearing across the 1-3 winding are rectified by the high-voltage rectifier tube which supplies a high dc voltage for the picture tube. The horizontal yoke provides sweep current for deflection. Spurious oscillations which occur in the yoke circuit are removed by the damper tube. The width and linearity coils control picture width and horizontal linearity, respectively.


*Author *Servicing TV Sweep Systems* (H. Sams).

ANODIZED


... it lasts forever

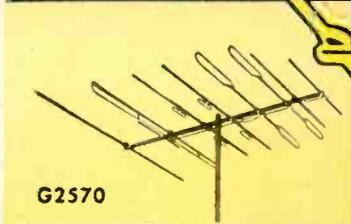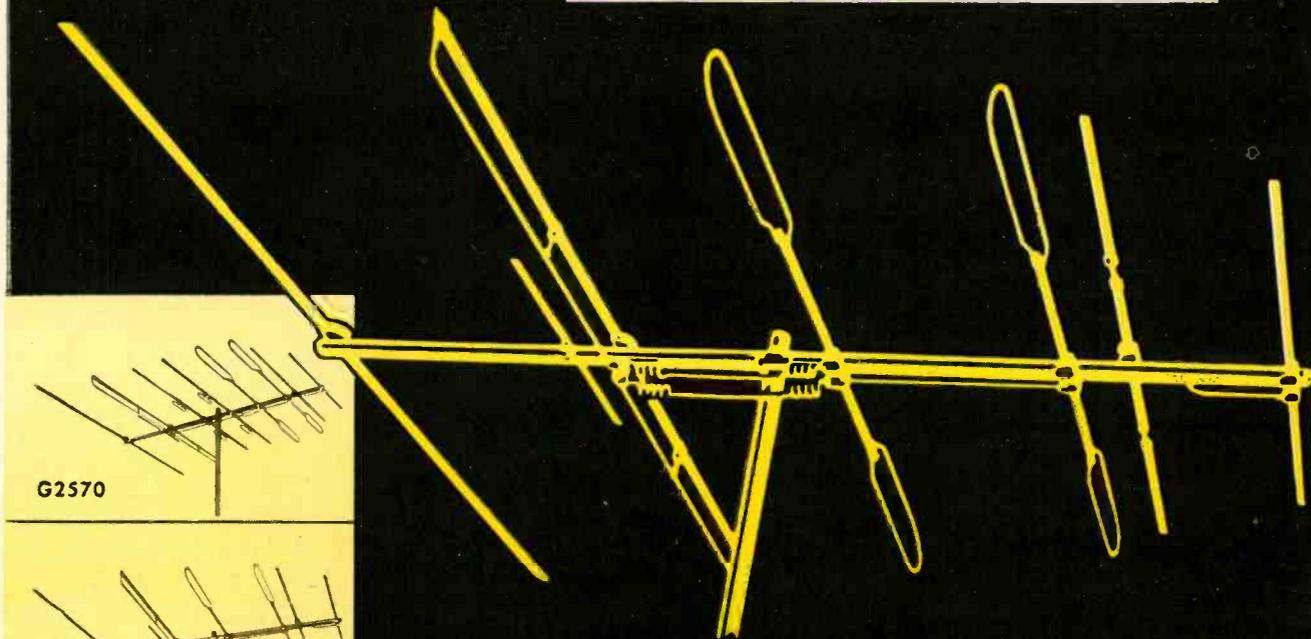


G2570

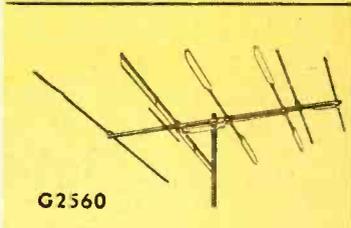

G2560

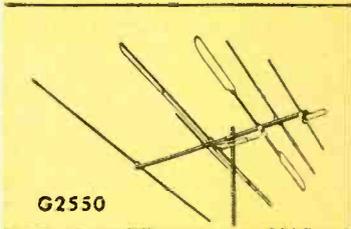

G2550

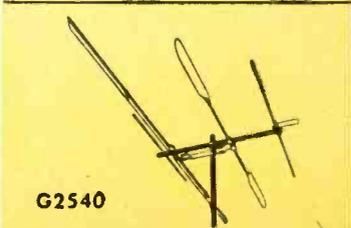

G2540

The new magnificent
GOLDEN
Topliner

Trade-mark

Completely anodized to lock out corrosive fumes and weather elements . . .

Designed to outperform any antenna, dollar-for-dollar, or size-for-size . . .

Designed to make your installation look better . . .

This is the new Taco Golden Topliner, the antenna you've been waiting for . . .

Install a Golden Topliner. You'll marvel at its performance.



TECHNICAL APPLIANCE CORPORATION
SHERBURNE, N. Y.

In Canada: Hackbusch Electronics, Ltd., Toronto 4, Ont.

TELEVISION

C1-R1 form the input coupling network and C2-R2 the cathode bias network for the horizontal output tube. C3-R3 are the screen grid coupling capacitor and dropping resistor, respectively. C4, C5 and C6 are the yoke dc blocking, resonant (with linearity coil) and boost capacitors, respectively. C7-R4 form the filter network for the rectifier tube.

During the latter two-thirds of the sweep portion of the input to the horizontal output tube, the tube conducts and current I_1 flows in the primary of the flyback transformer. The sawtooth yoke current I_2 develops due to transformer action. The negative spike of the input signal cuts off the horizontal output tube sharply and the entire flyback circuit, since it is not being loaded down now by the tube's conduction, breaks into oscillation at 70-90 kc. The first negative half-cycle of oscillation appears across the secondary and is transferred back to the 1-3 winding; it is rectified and used to obtain the high-voltage output of the system.

The next positive half-cycle of oscillation (as well as all other positive halves) appearing across the secondary causes the damper tube to conduct (I_3), charging boost capacitor C6 with the indicated polarity. In about one-third of the trace time C6 charges to the peak voltage appearing across the secondary. The damper cathode becomes positive enough, with respect to its plate, to cut the tube off. After one-third of the horizontal trace the horizontal output tube conducts and the cycle repeats.

The boost voltage which appears from pin 1 of the flyback to ground results from the charge across C6 and the B-plus voltage in series with it.

The linearity coil and C5 resonate at about 15,750 cycles. This alters the instantaneous plate voltage of the horizontal output tube which, in turn, affects the horizontal linearity of the picture. The width coil is a power-absorbing device. That is, its inductance (variable) changes its impedance and the current flowing through it. The greater the current flow through it, the less the current available for the flyback system the narrower the picture width; the converse is also true.

Autotransformer flyback


The basic circuit is shown in Fig. 2. In comparing this with the isolation type it is seen that both circuits are practically identical. (The same symbols and pin numbers are used for the corresponding component parts.) In fact, it would appear at first glance that the only difference is that the 4-7 secondary winding in Fig. 1 has simply been repositioned so that it lies directly below the primary winding. However, the basic difference is that in the autotransformer the B plus is applied to the damper tube plate instead of directly to the secondary winding. (This is necessary to permit I_3 flow through the damper tube, as shown.)

C9 is added in the circuit to permit the ac conduction of I_3 and to prevent dc from being applied directly to the 4-7 winding of the flyback. Boost capacitor C6 charges as shown. The boost voltage appears from the damper cathode to ground, which includes the charges across C6 and the B-plus supply (and C-9) added to each other.


Current I_1 flows from pin 7 to 4 of the flyback and in Fig. 1 (the isolation type circuit) it flows from 4 to 7, making the polarity across the winding opposite for both types of circuits. This does not

alter the operation of the flyback circuit, as was explained previously, but merely makes the waveforms and polarity of the autotransformer secondary winding 180° different from that of the isolation type.


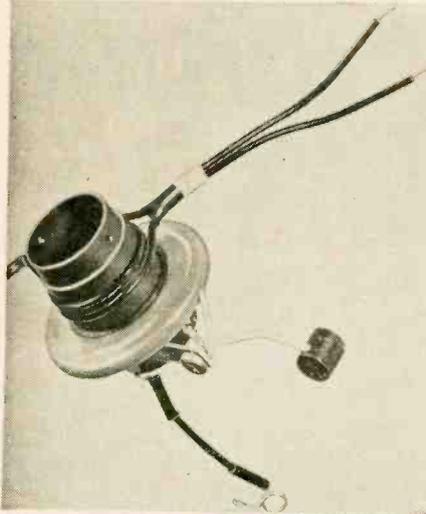
The advantage of the autotransformer sweep circuit over the isolation type is its greater operating efficiency, by virtue of the closer coupling between windings and the increased turns ratio between primary and secondary (for the same given number of transformer turns). For this reason, practically all



Air-core flyback transformer.

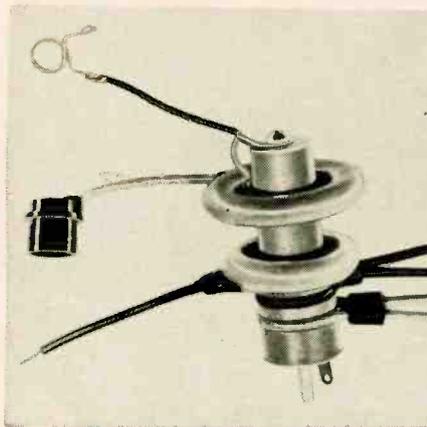

Ceramic-core flyback transformer

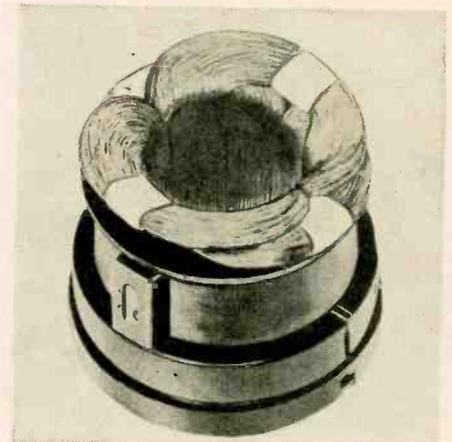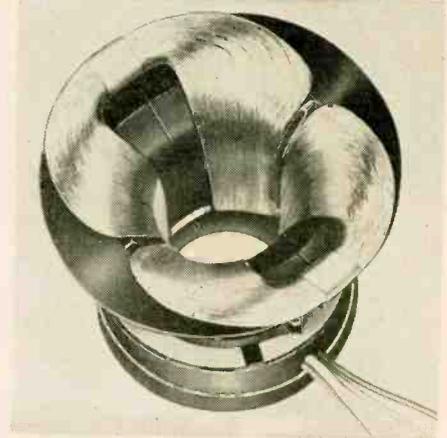

—Photos courtesy of Ram Electronics
Deflection yokes: above—90° type; below—70°. Note the considerable difference in the angle of flare.



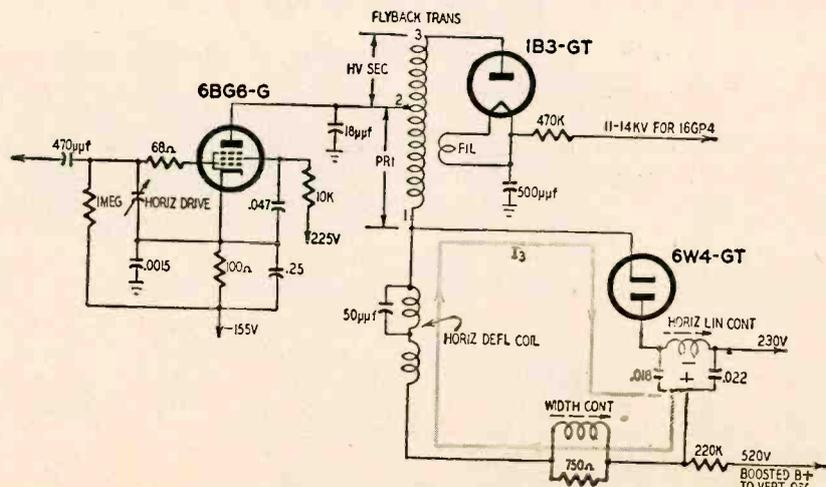


Fig. 3—Schematic diagram of the little-used direct-drive arrangement.

FULL **C** **O** **L** **O** **R** TV

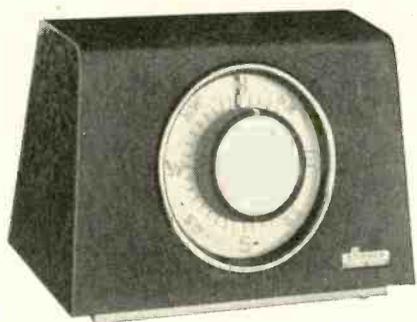

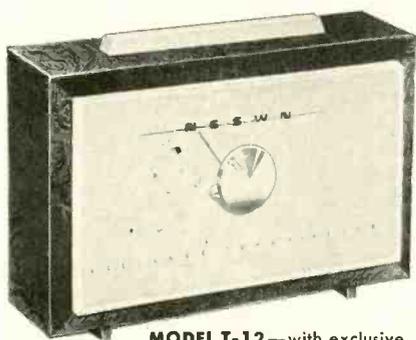MODEL U-98—first and finest fully automatic rotator. Eye-appealing decorator colors—Ivory, Forest Green and Standard Mahogany Grain. Retail \$44.25



MODEL T-12—with exclusive Tenna-Teller Pointer—highly accurate. Striking, modern design. Forest Green and Ivory or Standard Mahogany. Retail . . . \$34.25
Decorator Colors priced \$2.00 extra.

demands reliable



DON'T ASK VIEWERS TO PUT UP WITH A 'STAY-PUT' ANTENNA!

- TV authorities admit the higher sensitivity of color.*
- Viewers won't tolerate weak, washed out color!
- Maximum directivity with ALLIANCE TENNA-ROTOR is the best insurance for top antenna performance—for FULL COLOR!

Wherever you find Color TV, it will pay you to recommend Alliance!


- Every color TV buyer is a potential Tenna-Rotor sale . . . even in metropolitan areas. Because the "**fringe**" area for color is closer to the transmitter! Viewers who might tolerate black and white TV that's "so-so", will **not** put up with irritating, "ghosty" color. And independent interviews **at point of sale** show that color TV customers find it **easy** to say Yes to Alliance Tenna-Rotor!

**Many TV authorities agree that color is more sensitive than black and white. "Chromatic gradation" with color that's ghosty, is harder on the eyes than black and white. Many recommend properly installed outdoor antennas with rotators, to improve directivity of the antenna, to help overcome interference and reduce annoying effects caused by the higher sensitivity of color, and the normal characteristic of color to "drop out" quicker.*

Meet the Constant Changes in Television!

Alliance Tenna-Rotor makes any good outside antenna more directional. New stations, channel changes, new towers, more power, UHF-VHF . . . AND NOW COLOR! They all add up to Alliance Tenna-Rotor!

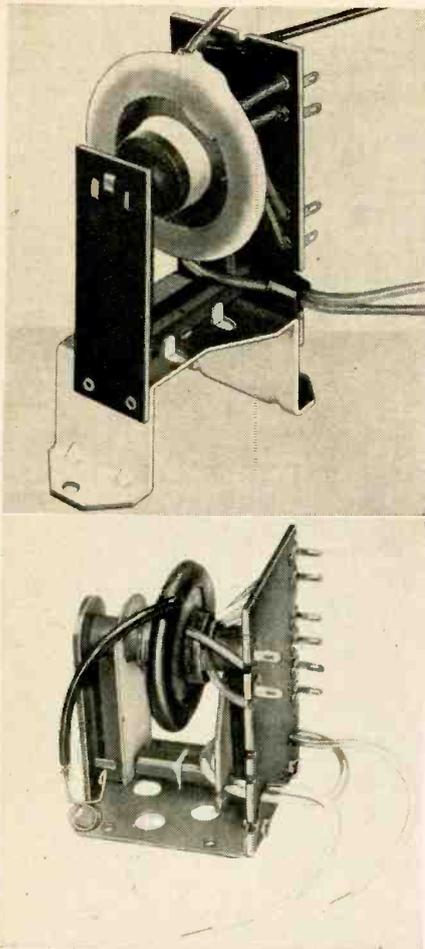**THE ALLIANCE
MANUFACTURING COMPANY, INC.**
(Division of Consolidated Electronics Industries Corp.)
ALLIANCE, OHIO
In Canada—ALLIANCE MOTORS, Schell Avenue, Toronto 10



Horizontal output transformers (fly-backs): above—90°; below 70°.

of the newer flyback circuits contain an autotransformer.

Direct-drive circuit

Several years ago, the direct-drive system was employed in the chassis of many set manufacturers. Although many TV sets contain such a circuit it is practically extinct in the newer sets because of its tendency to break down. This circuit was designed to produce

optimum efficiency while using a minimum number of component parts.

A typical direct-drive circuit, used in Emerson chassis 120124, is shown in Fig. 3. The most distinguishing feature of the circuit is that the flyback transformer has only three terminals and one tap point. The horizontal yoke winding, since it is in series with the 1-2-3 flyback winding, takes the place of an additional secondary winding. In other words, it is equivalent to the 4-5-6-7 secondary winding shown in Fig. 2, making the direct-drive circuit equivalent to an autotransformer type flyback circuit. In Fig. 3, the damper tube is effectively connected across the yoke and the width coil, in series with the yoke.

The conduction of the damper tube is indicated to show how the .022- μ f boost capacitor develops its 290-volt charge. The 520-volt boost, thus, is formed by the charge across the boost capacitor and the 230 volts of B plus.

The horizontal yoke inductance of this system is very high (30 mh) since it actually takes the place of the flyback transformer winding which normally also has a high inductance. The inductance value is the same as that of winding 1-2. Thus, winding 1-2 provides approximately 2.5 kv peak-to-peak across it, as well as the yoke. From terminal 2 of the flyback to ground, there is developed, therefore, 2×2.5 or 5 kv, voltage needed to develop 11-14 kv at the output of the high-voltage supply.

The flyback transformer used in this particular system is an air-core type. This is one of the first direct-drive fly-backs used. Later types employ a circular ceramic core, permitting its overall size to be reduced considerably. The air-core type requires many more winding turns from terminals 1 to 2 to obtain the necessary impedance and, therefore, its dc resistance is much greater than for ceramic-cores.

The direct-drive system is highly efficient. Its design is based upon its inherent distributed and stray capac-

itances. Thus, lead dress must not be disturbed when servicing such a circuit. The circuit is designed so that the retrace time (about 5-6 μ sec) is very low, thus helping to achieve its high efficiency.

The 90° flyback circuit

This designation refers to the deflection angle of the picture tube. The sweep components must be designed to work with such a picture tube. Originally, 90° tubes were 24 and 27 inches. However, some 10-, 17- and 21-inch tubes have been included recently.

There are no noticeable mechanical distinctions between 70° and 90° fly-backs whether they be isolation or autotransformer types. As a matter of fact, they may even be interchanged, provided they meet all other design requirements. Electrically, more winding turns are used for the 90° flyback to obtain a greater high-voltage output and thus its dc resistance is higher than those of the 70° flyback. However, there are exceptions to this rule.

The winding flare of the 90° yoke is much greater than that of the 70° unit. The greater flare is necessary to provide sufficient deflection to cover the entire picture-tube screen with good edge-to-edge focusing. Also, the horizontal inductance of the 90° yoke (over 20 mh) is much greater than that of the 70° type (usually less than 20 mh, except for direct-drive systems). Although the magnetic field of the 90° yoke is used to better advantage because of its flare, the field has less effect on the gun beam since the distance between field and beam is much greater. To compensate for this and, at the same time, to obtain more magnetic energy the yoke inductance is made greater. (The energy of an inductor is directly proportional to its inductance.)

The width and linearity coils used in the 90° system are the same as those used for 70°. However, the former more often uses horizontal output tubes such as the 6CD6 and 6CU6 and damper tubes such as the 6AX4 and 6AU5 to


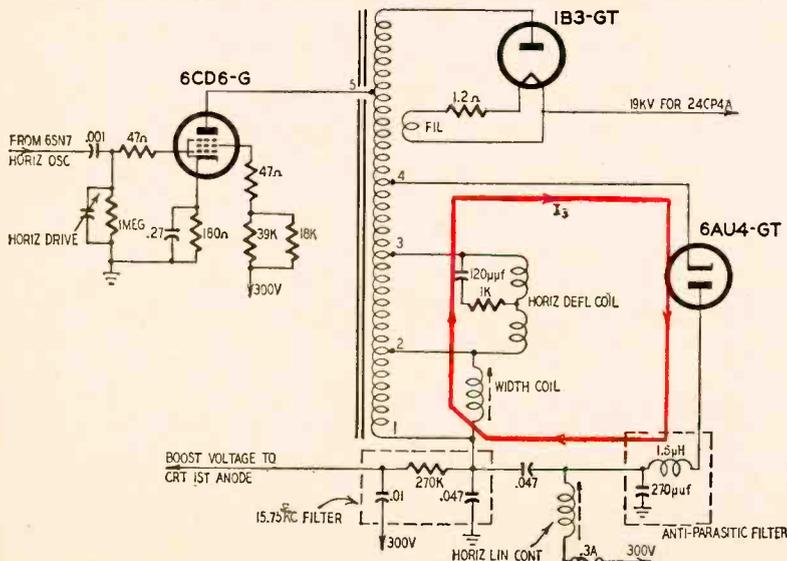


Fig. 4—Typical 90° deflection circuit used in the RCA chassis KCS89.

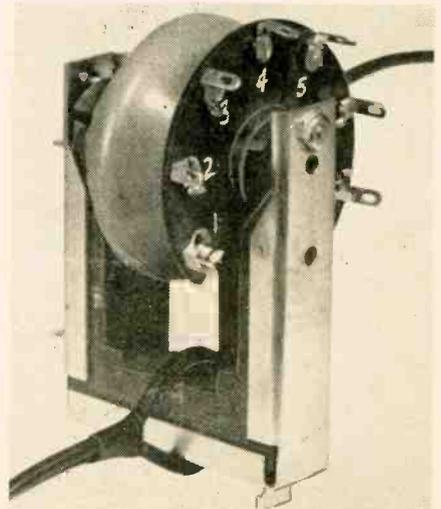


Merit model HVO-57 horizontal output and high-voltage transformer.

WIRE FOR EVERY ELECTRONIC PRODUCT




TV CAMERA CABLE

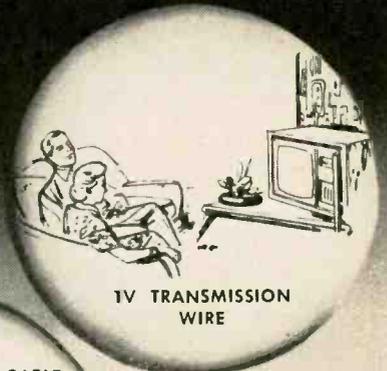


TV TRANSMISSION
WIRE



MAGNET WIRE—
HOOK-UP WIRE

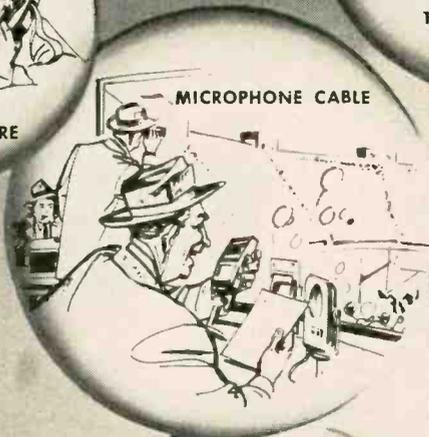


MICROPHONE CABLE

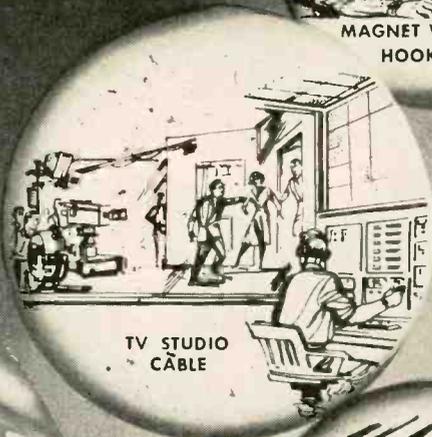

TV STUDIO
CABLE




BROADCAST
AUDIO CABLES

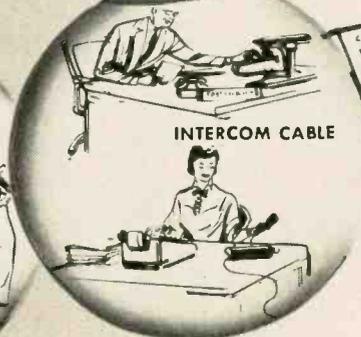

INTERCOM CABLE

SOUND SYSTEM CABLES

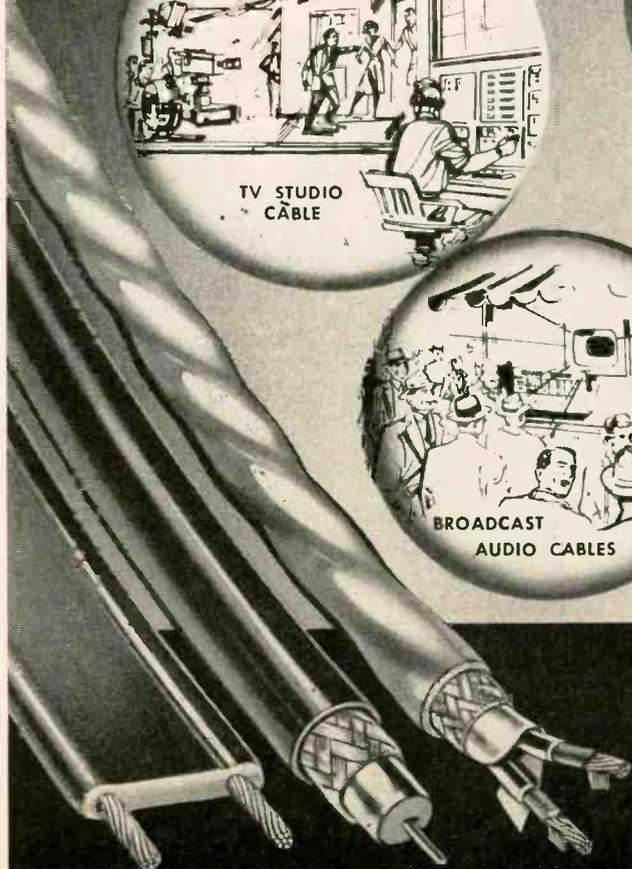


Belden

WIREMAKER FOR INDUSTRY
SINCE 1902

CHICAGO

3-E

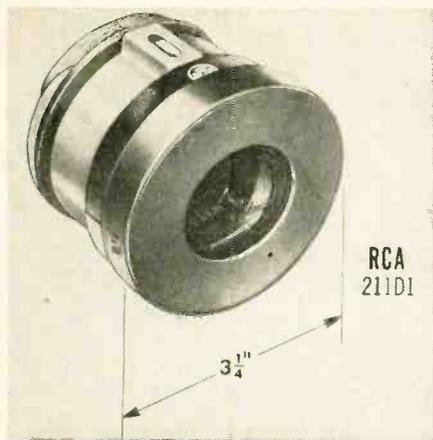

The RCA general-purpose model 211D1 70° cosine deflection yoke.

withstand the greater currents and peak voltages which prevail in this system.


In practically every case the 90° system uses an autotransformer flyback. A typical 90° circuit, used in the RCA chassis KCS89, is shown in Fig. 4. Unlike the 70° autotransformer circuit in Fig. 2, the flyback transformer is one continuous winding and the linearity coil is connected to the bottom of the flyback instead of in between a split winding. This does not alter the circuit operation (as was explained previously) since the linearity coil serves the same function — to vary the instantaneous plate voltage to the horizontal output tube plate. The advantage of the linearity coil arrangement in Fig. 4 is that it is not subjected to the high peak voltage which appears across the damper cathode, thus making it less susceptible to breakdown.

The damper current I_3 is indicated in Fig. 3. It charges the .047- μ f boost capacitor which is in its path. The boost voltage, therefore, appears from pin 1 to ground, which is the average charge across the boost capacitor (290 volts) plus the 300-volt B-plus supply. The boost voltage is fed to the C-R tube first anode to obtain proper focusing. The 15,750-cycle filter is, therefore, inserted between the boost voltage supply and the first anode to prevent 15,750 cycles from causing intensity modulation of the electron beam.

The linearity coil does not have a resonant capacitor (C5 in Fig. 2) since the stray distributed capacitances of the coil as well as the other capacitances in the circuit provide the needed capacitance. A 1.5- μ h choke and a 270- μ f capacitor, connected in the 6AU4 plate circuit, form an antiparasitic filter to prevent the higher harmonics developed in the flyback circuit from entering the 300-volt B-plus supply.

High-voltage circuits

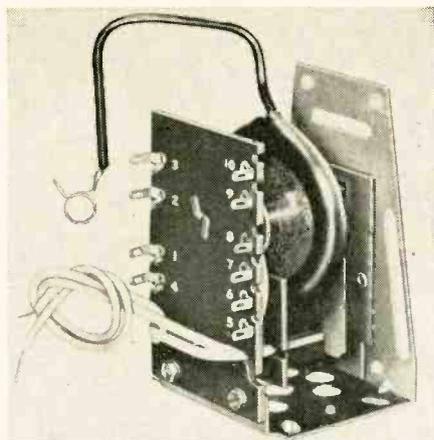
Many of the early TV sets used multiple high-voltage rectifier systems, doublers in particular. A few of the newer sets, such as Sylvania chassis 1-387, also use doublers. Tripler, quadrupler and even quintupler circuits are used in projection sets to obtain very



RCA's 232T1 universal 70° horizontal output transformer.

high voltages, in the order of 30 kv. However, since these are limited in their use, only the operation of the doubler circuit is discussed.


The basic doubler circuit is shown in Fig. 5. The operation of V1, R1, C1 and C2 is that of a single rectifier. When positive pulses appear at the plate of V1, it conducts (I_1), charging up C2 as shown. Between positive pulses C2 discharges (I_2) as indicated and charges C1. R1, in series with C1, prevents the latter from losing too much of its accumulated charge. After several cycles, C1 and C2 are charged to the full value of E. From point X to ground (between flyback transformer pulses) E exists, by virtue of the charge across C1. When the positive pulses from the flyback appear, another E voltage is superimposed on the already-existing one across C1, thus making the voltage from point, X to ground approximately

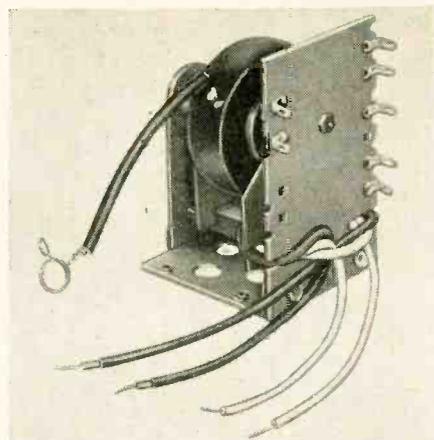


The RCA 228T1 70° horizontal output transformer, for voltages to 15 kv.

2E. The voltage has thus been doubled.

V2 and C3 operate in the following manner: The V2 filament is effectively connected to point X since the plate resistance of V2 is very small when it conducts during positive pulses. Therefore, C3 charges (I_3) as shown and after many pulses it is charged to the full 2E value. The charge of C3 discharges C1 (since it lies in the I_3 current path). However, C1 once again regains its E charge between positive pulses. Actually, the high-voltage output is about 2 V less than 2E, due to the inherent losses (such as loss in voltage by the drop across V1 and V2 during their conduction and the voltage drop across R1) in the circuit. END

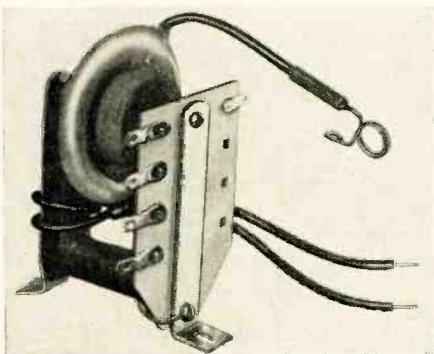

Stancor's A-8254 flyback transformer.

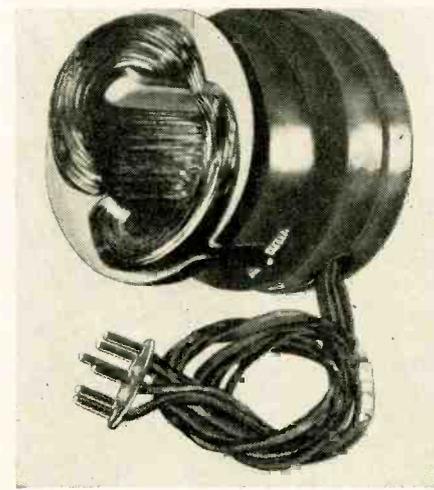

The Merit MDF-79 deflection yoke.


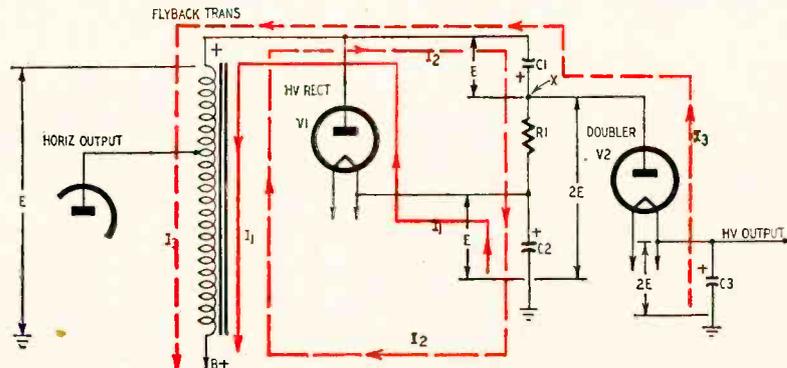


Fig. 5—A conventional voltage doubler.

new Devices

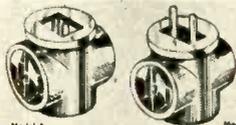


CHEATER CUBES. Type A (left) for RCA type interlock, B for Zenith. Plugs into inter-



lock cord on back of set and provides three-way power source.—R-Columbia Products Co., Inc., Highwood, Ill.

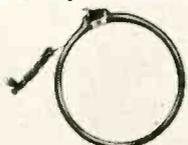COLOR SERVICING TOOLS. Degaussing coil No. 9317 demagnetizes magnetic fields set up in color picture tubes. Color




No. 9317 G-C DEGAUSSING COIL

No. 9299 G-C COLOR TV TOOL

TV tool No. 9299 adjusts concentric potentiometer and convergence controls.—General Cement Mfg. Co., 400 S. Wyman St., Rockford, Ill.

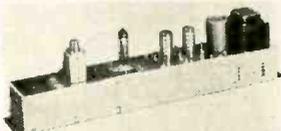CRYSTAL-CONTROLLED CONVERTER model CO-3. For conversion of channels from uhf to




vhf. Frequency stabilized by quartz crystal and regulated power supply.—Television Associates Ltd., 27 Taber Rd., Rexdale, Ontario, Canada.

TV ANTENNAS, Color King se-




ries. 13-element *Super Color King* (illustrated) and a 9-element *Color King*. Also 5 indoor antennas: *Top-Hatter No. 3710*, *Cinderella No. 3720*, *Hideaway No. 3870*, *Firefly No. 3860* and *Serenade No. 4150*.—Channel Master Corp., Ellenville, N. Y.

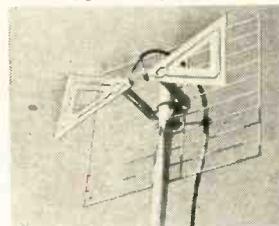UHF ANTENNA, model 3011. Bowtie type using air dielectric.




7-db gain over entire uhf spectrum.—Technical Appliance Corp., Sherburne, N. Y.

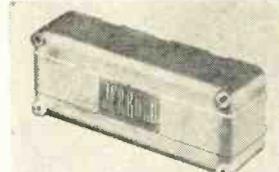MULTI-SET COUPLERS. 3 models include 2- and 4-set couplers



for strong-signal and fringe areas. Polystyrene cases.—Jerrold Electronics Corp., 23rd & Chestnut Sts., Philadelphia 3, Pa.

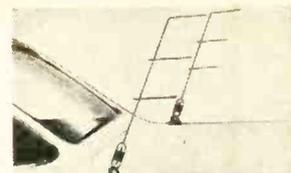AUTO-RADIO ANTENNAS, Fidelitytrend line. 6 models. *Moderne, model CEM* illustrated.




Available for cowl, rear deck and dual fender mounts.—Electrend Products Corp., State & Water Sts., St. Joseph, Mich.

ELECTROCARDIOGRAPH, model 300 Visette. Uses 3 tubes, 12 transistors and diodes and printed-circuit boards to reduce weight to only 18 pounds.



Printed-circuit boards are plug-in units.—Sanborn Co., 39 Osborn St., Waltham, Mass.

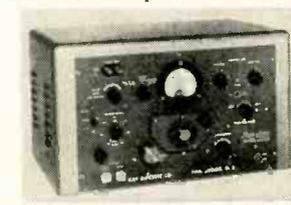MEGA-SWEEP model marker. Variable sweep width from 50



Abraham Marcus,
co-author of famous
best-seller
"Elements of Radio"
makes amazing
offer!



TRY MY TV and RADIO REPAIR COURSE FREE FOR 1 MONTH

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

Here it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-copy best-seller. Second, because these books get right to the point—tell you what to do in 1-2-3 fashion. For example, once you master the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls.

DON'T WAIT! you risk nothing when you send the coupon at right. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.

WHAT YOU GET IN THESE 3 GIANT VOLUMES

ELEMENTS OF TELEVISION SERVICING. Analyzes and illustrates more TV defects than any other book, and provides complete step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

RADIO PROJECTS. Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned-radio-frequency tuner—AC-DC superheterodyne receiver—etc.

RADIO SERVICING Theory and Practice. Here is everything you need to know about radio repair, replacement, and readjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers; Shortwave, portable, automobile receivers, etc. Explains how to use testing instruments such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.



MAIL THIS COUPON

Prentice-Hall, Inc., Dept. 5744-M1
Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$5.60. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. Or I will keep the course and send you two more payments of \$5.60 a month for two months.

Name

Address

City..... Zone..... State.....

TRIO®

Color Antennas *Specifically designed for color*



TRIO® **COLORITE**

recommended for both color and black and white reception in areas formerly using conical and conical-yagi installations

small and compact *for easier installation and improved outside appearance.*

flat frequency response *a necessity for good color reception*


U.S. PATENT No. 2,772,413
CANADIAN PATENT No. 541,670

magna **chrome** element system

The Magni-Chrome element system consists of an EXTENDED WING DIPOLE accurately coupled with a precision V'ed dipole. This combination is designed to magnify the chromatic characteristics of the incoming color signal to assure true, full-color reception. The folded dipole is V'ed at the exact

angle that gives greatest gain and band width when used in conjunction with the EXTENDED WING DIPOLE. Extremely flat frequency response across the entire VHF band is obtained together with improved gain.

for the ultimate in color reception

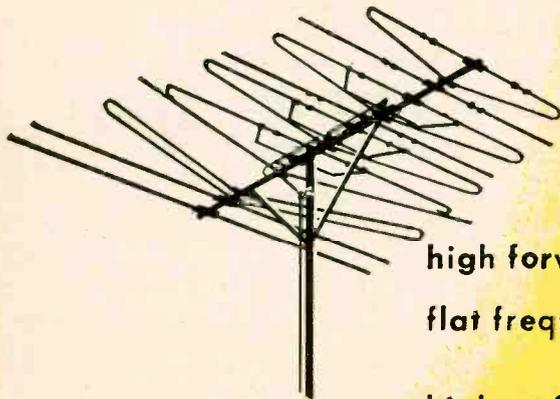

TRIO® **COLOR-ROYAL**

high forward gain *Sharper, Clearer Pictures High Signal-to-Noise Ratio*

flat frequency response *Improved Contrast on Black & White -
Perfect Reproduction of the Color Signal*

highest front-to-back ratio *For Freedom From Co-channel Interference*

tri-stop reflectors

Used in combination with the "Wing" and Collinear directors give exceptionally high front to back ratio while maintaining optimum gain on all channels.

THE LINE WITH PROTECTION




Export Sales Div., Scheel International Inc., 5909 N. Lincoln Ave., Chicago, U.S.A. Cable Address: HARSHEEL

COPYRIGHT 1957 TRIO MFG. CO.

NEW DEVICES (Continued)


ke—40 mc. Output waveform: less than 5% harmonic distortion at full output. Regular sawtooth sweep, approximately 20 volts. Internally coupled oscillators provide marker demonstration directly on sweep.—Kay Electric Co., 14 Maple Ave., Pine Brook, N. J.

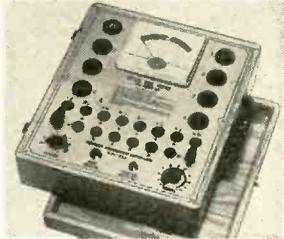TUBE TESTER, model 301. 2 controls to set. Checks for




shorts, leakage and quality. 4½-inch meter. Oak carrying case.—Electronic Measurements Corp., 625 Broadway, New York 12.

TUBE-TESTER ADAPTER, model VB-2, Vibra-Adapter. For checking 3- and 4-prong vibrators. Tube-tester set for 6AX4 or 6SN7 when checking 6-volt vibrators; 12AX4 or 12SN7

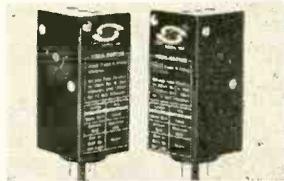

for 12-volt vibrators.—Service Instruments Corp., 171 Official Rd., Addison, Ill.

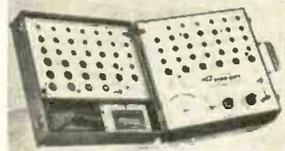TUBE AND TRANSISTOR TESTER. Model 630, Dyna-




Quick. Tests each section of multiple tubes for mutual conductance, shorts, grid emission, gas content and life. Instantaneous heater-continuity check. Pin straighteners mounted on panel. Checks leakage current and forward gain ratio of all types of junction, point contact and barrier transistors.—B & K Mfg. Co., 3731 No. Southport Ave., Chicago 13, Ill.

SCOPE PREAMP, model SPR-100. Increases selectivity by 40




db. Flat response from 10–25,000 cycles. Hum and noise output less than 5 mv.—Jerrold Electronics Corp., 23rd & Chestnut Sts., Philadelphia 3, Pa.

MOLDED TRANSFORMERS for

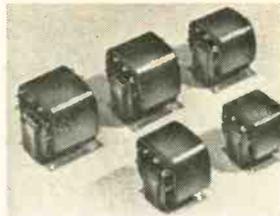

airborne applications. 10 sizes, 0.2–1.5 pounds. Available for standard or high-temperature use.—United Transformer Corp., 150 Varick St., New York 13, N. Y.

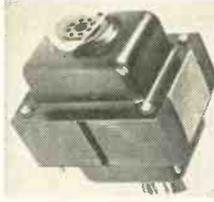
REPLACEMENT TRANSFORMERS. P-3049 (illustrated) exact



replacement for Motorola power transformer 25C737472. P-2865 replaces Philco 32-8512; P-2868 replaces Philco 32-8586; P-2683 replaces Philco 32-8575 and P-2871 replaces Philco 32-8635.—Merit Coil & Transformer Corp., 4427 No. Clark St., Chicago 40, Ill.


FILAMENT TRANSFORMERS. 6 new models: 21F13; 21F25; 21F28; 21F29; 21F30 and 21F31.—Thordarson-Meissner Mfg. Co., 7th & Belmont Ave., Mt. Carmel, Ill.

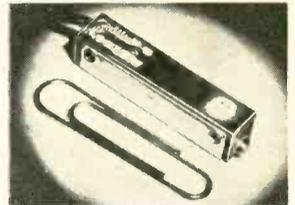PRECISION POTENTIOMETER, Padohm. Screwdriver-adjusted. 100–20,000 ohms. 10%



tolerance.—Clarostat Mfg. Co. Inc., Dover, N. H.

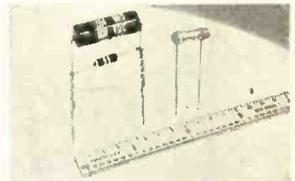TUBE-R-CAP. Resistor-capacitor unit takes up space of tubular capacitor alone. CC20: 500-volt capacitor 400 µf—.00215 µf; resistance tolerance 20% below 1 megohm. CC25: 500-volt 970 µf—.005 µf; resistance tolerance 20% below 1



megohm, 30% over 1 megohm.—Centralab, 900 E. Keefe Ave., Milwaukee 1, Wis.

CARBON RESISTORS, Hi-Stab. In molded, noninsulated, hermetically sealed, ceramic-encased types. Deposited carbon. High stability.—Erie Resistor Corp., 639 W. 12 St., Erie, Pa.

Get This Valuable Book

FREE



NOW!

7 BIG BOOKS IN ONE GREAT SET!

Just For Examining COYNE'S New Set

"Applied Practical Radio-Television"

on 7 DAY FREE TRIAL!

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press. Gives complete 11 x 22" Schematic Diagrams on leading models Radio and TV Sets. Easy-to-read, large 8½ x 11" pages, with full instructions on how to use the diagrams. A "must" in every repair kit. You get this book as a FREE Gift for asking to see Coyne's new 7-book set, "Applied Practical Radio-Television"!

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it covers COLOR TV, UHF and the latest on TRANSISTORS. All this plus Volume 6—NEW Coyne TECHNICAL DICTIONARY with over 4000 definitions of the latest terms, symbols and abbreviations in radio-TV, electronics and electricity.

EXTRA! 900-Page Television Cyclopeda Included

And then, for speedy on-the-job use, you get volume 7—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation, etc. In easy-to-find ABC order, cross-indexed. Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book ABSOLUTELY FREE!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
 500 S. Paulina St., Dept. A7-T1, Chicago 12, Ill.

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
 COYNE ELECTRICAL SCHOOL, Dept. A7-T1
 500 S. Paulina St., Chicago 12, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name..... Age.....


Address.....

City..... Zone..... State.....

Where Employed.....

Check here if you want library sent C.O.D. You pay postman \$22.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

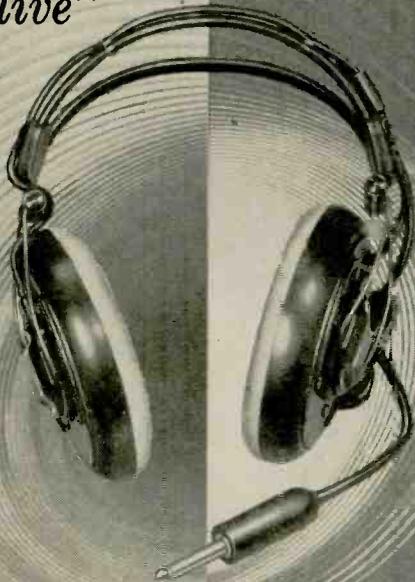suddenly
stereophonic
sound
comes
"alive"



the new binaural dynamic earspeakers
DIMENSI-FONES

For the first time, enjoy the full, exciting realism of binaural sound. New DIMENSI-FONES create the feeling of true stereophonic depth and direction. Each ear hears a separate sound channel... exactly as picked-up by each recording or broadcast microphone. Amazing frequency response reproduces the full orchestral scale within human hearing. Perfect for private hi-fi, AM-FM radio, TV, and short-wave listening. Used and recommended by leading performers and engineers. Equipped with comfortable ear cushions to eliminate all external noise. Monaural headset models also available. Sold at high fidelity and radio parts dealers.

FREE! Write for booklet "16 Ways to Hook-up DIMENSI-FONES" and information on Permoflux high fidelity speakers, systems, and components.

Permoflux PRODUCTS COMPANY

4101 San Fernando Road • Glendale 4, Calif. • CHapman 5-5111

NEW DEVICES (Continued)

DEPOSITED-CARBON RESISTORS. *Dalohm MC type.* Molded




plastic coating. 3 sizes: 1/2, 1 and 2 watts. — Dale Products Inc., Box 136, Columbus, Neb.

TURNTABLE, model 1/S-3. 4 speeds. Neon stroboscope. Magnetic speed adjustment. Rim




drive, capacitor type, 4-pole motor—Intersearch Inc., 7 Arcadia Place, Cincinnati 8, Ohio.

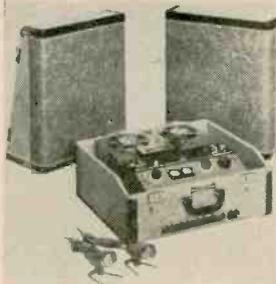STEREOPHONIC RECORDER, Stericorder. Records and plays back stereophonic sound. Hysteresis synchronous motor, 2 VU meters, cueing and editing




facilities and 2 self-contained independent channels of pre-amplification and power amplification.—Superscope Inc., Audio Electronics Div., 780 Gower St., Hollywood 38, Calif.

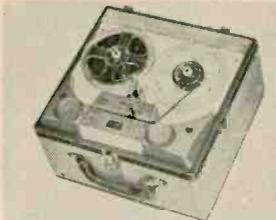TAPE RECORDER, model 1960. 2 speeds, 3 3/4 and 7 1/2 inches



per second. Dual-track recording. Fast forward and rewind. Weighs less than 15 pounds.—Telectrosonic Corp., 35-16 37th St., Long Island City, N.Y.

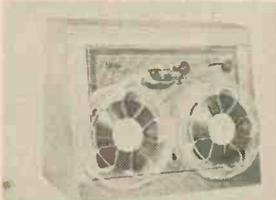CASES, Model 400 (illustrated) holds any Viking tape deck and



can be used vertically or horizontally. Model 401 for amplifier or preamp.—Viking of Minneapolis, 9600 Aldrich Ave. So., Minneapolis 20, Minn.

MAGNETIC TAPE. Scotch brand no. 131 *Low-Print.* Reduces print level by 8 db and increases high-frequency response.—Minnesota Mining &




Mfg. Co., Dept. A7-236, St. Paul, Minn.

PHONO CARTRIDGES, Climatite, model 120TS (illustrated): 3-volt output, 30-11,000 cycles. Model 118TS: 0.75-volt output, 30-13,000 cycles. Model 124TS: 3-volt output, 30-11,000 cycles. *Soundflo:* plug-in cartridge-needle combination. Model 89TB: 1.3-volt output, 30-15,000




cycles. Crystal mike model M-332: 30-15,000 cycles. Output level —57 db.—Astatic Corp., Conneaut, Ohio.

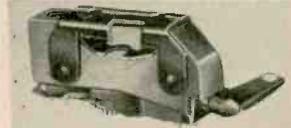PHONO CARTRIDGE, twin-lever ceramic. 30-15,000 cycles. Dual needles. 1-mil stylus for 33 1/3 and 45 rpm; 3-mil for 78



rpm.—Shure Brothers Inc., 222 Hartrey Ave., Evanston, Ill.

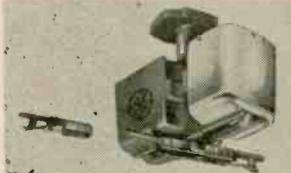PHONO CARTRIDGES, Series VR-II Magnetic variable reluctance. Frequency response:



20-20,000 cycles. Tracking pressure: 4 grams. Electrostatic shield. 7 models: 4 single-stylus and 3 dual-stylus types. Diamond or sapphire styli.—General Electric, Specialty Electronic Components Dept., W. Genesee St., Auburn, N. Y.


REMOTE-CONTROL UNIT, Duo-Master, for TV sets can also be used for monitoring tape recordings. Single-wire hookup. Provides remote tuning of picture, sound and station selec-



tion.—Tech-Master Corp., 75 Front St., Brooklyn, N.Y.

WIDE-ANGLE PROJECTOR, model CLH. Omnidirectional swivel mounting enables projector to be rotated 360°. Air column length 4 1/2 feet. Horn cutoff 120 cycles.—University

NEW DEVICES (Continued)

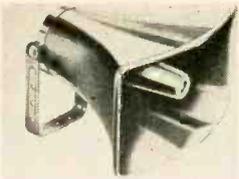


Loudspeakers, Inc., 80 S. Ken-sico Ave., White Plains, N.Y.

TRANSISTORIZED MICRO-PHONE, model 505T. Built-in transistor amplifier. No bat-teries, extra power supplies or



circuit changes needed. Transis-tor-powered by available current normally used by carbon mike unit.—Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Ill.

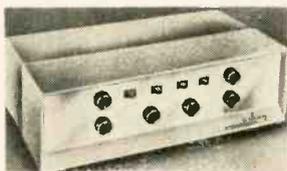BINAURAL PREAMP. Model SA-25. Kit or factory-wired. Dual-channel preamp drives its own 25-watt amplifier in con-junction with any present am-




plifier. Response 20-20,000 cycles. Equalization controls. 2-position low-cut and high-cut filter.—Arkay, 120 Cedar St., New York, N.Y.

PREAMPLIFIER. Includes dip-soldered printed-circuit board




with factory-mounted com-ponents. Dc filaments. Fre-quency response ± 0.5 db, 6-60,000 cycles. 6 inputs. Feedback type tone control. Dyna Co., 617 No. 41 St., Philadelphia 4, Pa.

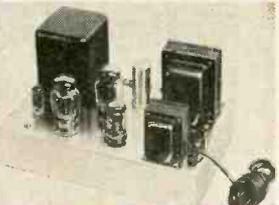HI-FI AMPLIFIER, model M-60. 60 watts, 7-70,000 cycles ± 1 db. IM distortion less than 1% at 60 watts. Harmonic dis-tortion less than 1% from 20-20,000 cycles. Sensitivity, 1.5



volts rms for full output.—MusiCraft, 48 E. Oak St., Chi-cago, Ill.

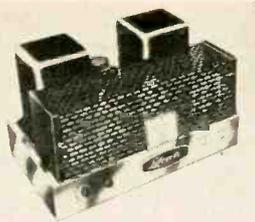70-WATT AMPLIFIER, kit (KT-400) or wired (LA-70).




20-20,000 cycles ± 1 db at full output. Uses 2 KT88's, 1 6AN8, 1 GZ34 and a selenium rectifier. Meter for bias and balance ad-justment.—Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N.Y.

HIGH-FIDELITY AMPLIFIER, Mark III. 60 watts, 16-24,000



cycles ± 0.1 db. KT88 for power output.—Dyna Co., 617 No. 41 St., Philadelphia 4, Pa.

BINAURAL FM-AM TUNER,

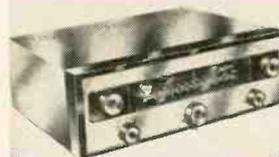

kit (KT-500) or wired (LT-50). Separate AM and FM sections. 20-20,000 cycles ± 0.5 db. Har-monic distortion less than 1% on FM, less than 1% on AM for 80% modulation.—Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N.Y.

HOOKUP WIRE. Conforms to MIL Spec 16878-B. Plain vinyl



or vinyl with nylon jacket. 16-26 gauge, 10 solid and 9 striped colors.—Belden Mfg. Co., 4647 Van Buren St., Chicago 80, Ill.


CLUTCH FACING KIT. Cor-rects slipping manual tuner on pushbutton-tuned auto radios. Contains cleaning swabs, sol-



vents and spare clutch facings.—Colman Tool & Machine Co., Amarillo, Tex.

DUAL CONTROLS. Concentric controls snap together to as-semble a custom dual-concen-

Just Out

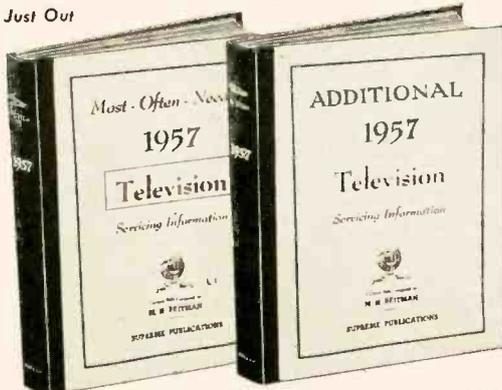

These two 1957 TV volumes cover practically all sets of all makes. The new ADDITIONAL 1957 TV manual includes material almost to the minute. Each giant manual has 192 pages of service data, changes, double-size circuits. Special price, each only \$3

New ADDITIONAL 1957 TV Volume
LARGE MANUAL COVERS NEWEST 1957 TV SETS
EARLIER TV VOLUMES STILL SOLD AT ONLY \$3

AMAZING BARGAIN

Supreme twin 1957 TV manuals are the scoop of the year. Cover all sets of all im-portant makes. New ADDITIONAL 1957 TV volume gives you the very latest material. Your price for this mammoth manual is only \$3. Supreme super values defy com-petition. Each prior-year manual (at only \$3) has a whole year of service material. Each volume covers different material, from 1948 to latest 1957 sets. Include circuits, wave-forms, alignment, voltage charts, service hints, changes, and double-spread diagrams.

ALL NEEDED TV DATA

Supreme TV manuals supply all needed service material on every TV set of every important manufacturer. Here is helpful, practical, factory-prepared data. It will really make TV servicing and adjustment easy for you. Join 157,000 servicemen who use, benefit, and save with SUPREME service manuals. In these volumes you get correct factory-checked circuits, alignment procedure, response curves, service hints, recommended changes, voltage charts, wave-forms, and easy-to-use giant-size diagrams. Here is your TV service material to help you do expert work double-quick; and priced at only \$3 per annual volume. Be ready to repair any model by carrying in your car all 12 TV volumes listed in cou-pon below. Or try one of the new 1957 TV manuals to see what an amazing bargain you get for only \$3. Send coupon for prompt shipment or ask your jobber.

Practically tell you how to make every repair. More pages, more diagrams, more service data per dol-lar of cost. Get the best for less. Get SUPREME.

TELEVISION SERVICING COURSE

Let this new course help you in TV servicing. Amazing bargain, complete, only \$3, full price for all lessons. Giant in size, mammoth in scope, topics just like a \$200.00 correspondence course. Lessons on picture faults, circuits, adjustments, short-cuts, UHF, alignment facts, hints, antenna problems, trouble-shooting, test equipment, picture analysis. Special, only \$3



Newest

RADIO DIAGRAMS

Here is your complete source of all needed RADIO diagrams and service data. Covers everything from the most recent 1957 radios to pre-war old-timers: home radios, auto sets, combinations, changers, FM, and portables. Super-sensational values. Only \$2 for most volumes. Every manual contains extra large schematic diagrams, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and helpful hints. Volumes are large in size, 8 1/2 x 11 inches, about 190 pages. See coupon at right for a complete list of these radio manuals.—



NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 1760 Balsam Rd., Highland Park, Ill.

- 1957 Radio Manual, \$2.50
- 1956 Radio Diagrams, \$2.50
- 1955 Radio Manual, only \$2
- 1954
- 1953
- 1952
- 1951
- 1950
- 1949
- 1948
- 1947
- 1946
- 1942
- 1941
- 1940
- 1939
- 1926-1938 Manual, \$2.50
- Radio & TV Master Index, 25c

These annual RADIO volumes specially priced at only \$2.50 each

THIS GROUP ONLY \$2 EACH

Rush today TV manuals checked below and Radio manuals at left. Satisfaction guaranteed.


- Additional 1957 TV, \$3.
- 1956 Television Manual, \$3
- Additional 1955 TV, \$3
- 1953 Television Manual, \$3.
- 1951 Television Manual, \$3
- 1949 TV Manual, \$3.
- New Television Servicing Course, complete... \$3.
- Early 1957 TV, \$3.
- Early 1955 TV, \$3.
- 1954 TV Manual, \$3.
- 1952 TV, \$3.
- 1950 TV, \$3.
- 1948 TV Manual, \$3.

I am enclosing \$..... Send postpaid.
 Send C.O.D. I am enclosing \$..... deposit.

Name:
Address:

Supreme Publications
Sold by All Leading Parts Jobbers


**LEEDS & NORTHRUP
MICROMAX
RECORDERS**

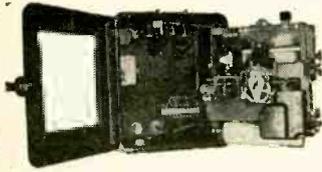

Strip type recorder used for controlling and recording wide variety of processes. Used originally for temp. range of 350-550° C. but may be changed for other applications. Operates on Wheatstone bridge principle using AC galvanometer movement. Original cost several times our low price. Returned from demilitarized equipment which in many cases was new. Sold as used but guaranteed, or money back if not satisfied. Ship. wt. approx. 165 lbs.

\$179.50 ea.

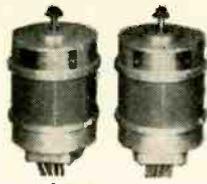**SYNCHROS,
SELLSYNS, AUTOSYNS!!!
At money-saving prices!!!
LARGE QUANTITY
20,000 in stock
110 v. 60 cycle Units**




| Navy Size & Type | Approx. Weight (lbs.) | Approx. Length (inches) | Approx. Diameter (inches) | Price Used |
|------------------|-----------------------|-------------------------|---------------------------|------------|
| 5F | 5 | 6.0-6.8 | 3.4-3.6 | \$5.00 |
| 5G | 5 | 6.0-6.8 | 3.4-3.6 | 5.00 |
| 5DG | 5 | 6.0-6.8 | 3.4-3.6 | 5.00 |
| SCT | 8 | 6.0-6.8 | 3.4-3.6 | 5.00 |
| 6G | 8 | 6.4-7.5 | 4.5 | 7.50 |
| 7D | 18 | 8.9-9.2 | 5.8 | 10.00 |
| 7DG | 18 | 8.9-9.2 | 5.8 | 10.00 |

110 V. 400 Cycle Units

| Size & Type | Approx. Weight (lbs.) | Approx. Length (inches) | Approx. Diameter (inches) | Price Used |
|-------------|-----------------------|-------------------------|---------------------------|------------|
| 5F | 5 | 6.0-6.8 | 3.4-3.6 | \$3.50 |
| 5G | 5 | 6.0-6.8 | 3.4-3.6 | 3.50 |
| 5C | 5 | 6.0-6.8 | 3.4-3.6 | 3.50 |


CT—Control Transformer; D—Differential Motor;
DG—Differential Generator; F—Motor (Follower);
G—Generator. Mfg. by Bendix, Ford Instrument Co. and General Electric. Specify. Bendix, Ford & GE in stock

**RC-58-B
FACSIMILE SET \$59.50 ea.**

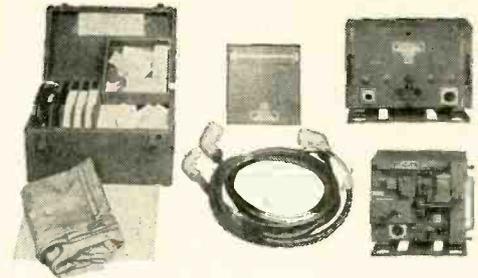

Brand new, complete, ready to operate by connecting to 12 V. DC source. Spare parts included with ample supply of ink and paper. Transmits and receives and prints, signatures and copy. Ideal for loan offices, banks or other businesses where signatures must be verified, etc. Use two sets together with 2 wires telephone line or radio carrier between. Cost Govt. approx. \$6000. Your price, in original packing, only \$59.50 ea. Ship. wt. approx. 300 lbs.

**M-1 SERVO
UNIT FOR
BEAM
ROTATION**

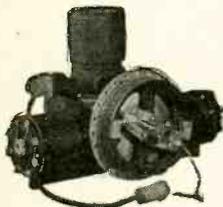

Unit has self-contained hydraulic pump actuated by 27 V. -11 Amp. 1/5 hp. motor which pumps oil into either side of hydraulic piston giving better than a 100 lbs. torque to cable drum. Unit is reversible by actuation of either of two self-contained solenoid hydraulic valves. Connect by cable around antenna beam for any desired rotation speed. Greater adaptability than any other surplus device on the market. Ship. wt. 37 lbs. Brand New—Only a few, order early.

Price.....\$7.95 ea.




**M-1 ODOGRAPH
Over \$5,000 Value
\$89.50**

See Nov. 1944 Electronics for Full Description

This is a survey instrument for automatically drawing a map of the terrain over which the jeep or other vehicle to which it is attached traverses. These instruments mfgd. currently by Monroe Calculating Machine Co. and sold in excess of \$5,000. Our surplus purchase allows passing on these machines at this value. Order early, only 200 in stock. Units have been rebuilt by Corp of Engineers. U.S. Army and guaranteed good condition. Ideal for prospectors, oil companies, power line and farm use. Nothing else needed for operation except vehicle. Many are using the compass unit for automatic pilots, on boats—many, many applications. A real machine. Ship. Wt. approx. 300 lbs. Our Price.....\$89.50 ea.

**Brand
New
12 V.
Dynamotor**

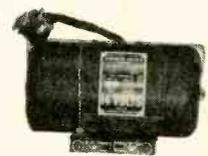

DM-40. Input: 12-14 V 3.4 A. Output: 172 V. -138 Ma. An ideal dynamotor to adapt to mobile uses on the new 12 V. cars. Don't pass up this buy even if your intended uses are not immediate. Size 6 3/4" L. x 3 1/2" dia. 4" lead with 6 pin Jones plug. Ship. wt. 7 1/2 lbs.....\$2.75

**We are not going out of business or losing our lease—
but compare this list of prices & items anywhere**

Due to lower prices on these items we cannot accept orders unless total amount is \$5.00 or more


- a. BC-604 Transmitter—10 tube 20-27.9 MC. F3 converts easily to 10 meter. For 12 or 24 V. DC use (no dynamotor supplied) complete with tubes. Size 18"x12"x10". Excellent condition. Shipping wt. 100 lbs. ea. Price \$6.95 ea.
- b. Metal locator—famous SCR 625 mine detector for finding treasure, pipes, and lost articles. Complete in carrying case ready to operate with batteries Case size 28 1/4"x16"x8 1/4". Ship. wt. 55 lb. Used. Price \$29.50 ea. Batteries \$4.25 per set.
- c. Receiver R-1/ARR-1—two stage RF range, 235 to 248 MC. Ideal for conversion to preselectors, ham 220 MC converter, etc. Complete with tubes in compact aluminum case 10"x3 1/2"x3". Insulation on input coil has been broken by Army for demilitarization. Easily repaired with cement or replacement. Shipping wt. 4 lb. New. \$1.25 ea.
- d. Coaxial relay—operates on 12 or 24 V. Ideal for your mobile transmitter receiver equipment. Ship. wt. 2 lb. New \$1.25 ea.
- e. TS 9 Hand set—telephone type with switch in handle. Ideal for your mobile equipment. \$2.95 ea.
- f. 30 Amp Battery charger—cost gov't \$300 ea. Mfg. by Ward-Leonard. Charging rates up to 30 amps on 12-30V battery combinations. Operates from 110 V DC. Size 20" wide x 20" high x 10" deep. Complete with metal spare parts box, spares, and cord. Ship. wt. 145 lb. In original wood box. New. Price \$10.00 ea.
- g. PE-237 Vibrator Power Supply—\$5.95. 6, 12, 24 V. Non-synchronous vibrator type. Input 6 V. 36 amp., 12 V. 17 amp., or 24 V. 9.5 amp. DC Output: 525 V. DC .095 amp. 1105 V. DC 4.2 Ma., 6.5 V. DC 2 amp., 6 V. DC 1/2 amp., 1.35 V. DC 450 Ma. Higher current drain may be obtained with no ill effect. This power supply has been successfully used for powering the BC 604 Xmtr. Steel brown crackle case. Size 20 1/2"x11"x10". Ship wt. 119 lbs. Excellent to new condition. Vibrator not included.
- h. J-47 Telegraph Key \$1.00 Brand new Signal Corps surplus key in original packing. Ship. wt. 2 lbs.
- i. 200 KC Crystal in DC-15A holder for ART-13 or calibration monitors. \$1.00 ea.
- j. Freq. crystals 100—\$4.95 Kit of 100 brand new crystals worth \$3.50 to \$12.50 ea. All mounted in various holders. Plenty of ham band frequencies in assortment. Ship. wt. 4 lb.
- k. Camp stove or portable sports heater—Evans blue flame heater originally used for keeping engines warm in Arctic climates, but ideal for camp cooking or heat for ice fishing, tents, etc. (Not recommended for confined or poorly ventilated bldgs.) Burns kerosene or gasoline. Size 10" dia. x 12" high with bail type carrying handle. Cost Gov't many times our low price. Shipped in original packing. Ship. wt. 47 lbs. \$4.75 ea.
- l. OVA-1 Test Signal Generator—\$17.50. This signal generator was used to provide a test signal of constant frequency for operation and alignment of IF amplifier stages in the CG-46 ACQ type receivers. The generator covers the range between 150-250 megacycles. Amplitude modulated square wave output is obtained at frequencies of .1, 1, 10, and 100 kc depending on the position of the freq. mod. pulse switch. A 15 Mc. signal is also provided by a second osc. stage. Power is supplied by internal 115 V. 60 cycle

- AC supply connected to source by cord provided. Brand new with instruction book. Ship. wt. 62 lbs. \$17.50.
 - m. 357 Marker Beacon Receivers—\$2.95. Contains sensitive relay and tubes, operates on 75 MC. Ideal for radio control.
 - n. T-26 Carbon Mike—\$1.95. Chest mounted switchboard type, leaves hands free for mobile work. Uses F-1 W. E. microphone element.
 - o. 115 V. 400 cycle Inverters \$4.95 ea. New. 24 V. DC input-115V 400 cycle output inverters for numerous ADF, radar, and other electronic items. Size 9"x6"x4 1/2". Ship. wt. 12 lbs.
 - p. 1-KW Plate Transformer—\$8.95. Brand new—Arma II V. Contains two 400 V. CT. 1.25 amp. windings which may be series or parallel connected. 110V. 60 cy. Pri. Size 9 1/2"x9"x8". Ship. wt. 100 lb.
 - q. Edison 37 1/2 AH 6 V. Batteries—\$17.50 ea. Iron-Nickel Alkaline type consisting of 5 type B2H cells.
 - r. AN/ART-4 Dual Target Transmitter—\$3.95 dual transmitter one on 55.5 mc, others on 56.75 MC built into a 6 ft. x 30 ft. plastic screen. Shipped in original box. Ship. wt. 75 lbs.
 - s. Torque Amplifier 110V AC—\$7.50. Works like the power steering on a car—light movement of input shaft is transmitted to output shaft in direct ratio with torque being added by 110 V. 1/40 H.P. motor which is part of unit. Size 12"x7 1/2"x5 1/2". Shipped in original box. Ship wt. 45 lbs.
 - t. 30 Amp. DC Ammeter—\$1.00. New—3" round panel type 0-30 Amps., DC, white face, black scale, Mfg. by Hoyt, Ship. Wt. 2 lbs. ea.
 - u. DM-42 Dynamotor—\$9.50—12-14V. DC Input-515 and 1030V. output @ 260 ma. continuous. Size 12 1/2"x7"x7". Ship. wt. 30 lbs.
 - v. 110V to 28V Transformer—\$5.00. 110V. 60 cycle pri. 28V. 8 amp. secondary transformer for building your 24 volt charger or DC supply. New. Ship. wt. 10 lbs.
 - w. BB-54-2V. 34AH Battery—\$1.95. New. Plastic case storage battery, size 5 3/8"x4"x3", Shipped dry charged. Ship. wt. 5 lbs.
 - x. Mallory AC Capacity selector—\$1.50. MSS-100 capacity selector for determining correct replacement motor starting capacitors. Fraction of jobbers price—New—Ship. wt. 3 lbs.
 - y. Golf Car Motor—\$4.50. Storage battery operated reversible motor—1 1/4 H.P.—12 to 24 V. DC. Speed to 6000 RPM. Measures 4 1/8" dia. x 9" long 3/8" spline shaft. NEW Ship. wt. 13 lbs.
 - z. 100 amp 6V. Leece-Neville Alternator and Rectifier for police car or other automobile or boat use where high charging currents are needed. Used but guaranteed. Ship. wt. approx. 100 lbs. \$45.00 ea.
- OIL CAPACITORS: All New**
- | | |
|----------------------------------|--------------|
| 2x1 mfd. 600V. Aerovox 24C16 | \$2.50/dozen |
| 4 mfd. 600V. Sprague 23C16 | 3.50/dozen |
| 3x2 mfd. 4000V. Tobe 30C16 | 7.50/dozen |
| 12 mfd. 15000V. GE Pyranol 35C16 | 2.50 each |
- Variable Condensers: All New**
- 100 mfmfd. midget variable Bud MC 1265 Reg. \$2.45 price—Special \$1.00 ea. \$7.50/dozen. Defiance Replacement type ganged, all 6 models \$2.75 for 6.

**ESSE RADIO CO. 42 WEST SOUTH ST.
INDIANAPOLIS 25, IND.**


REMIT SHIPPING CHARGE AND INSTRUCTIONS WITH ALL ORDERS. OTHERWISE ORDER WILL BE SHIPPED EXPRESS COLLECT. ALL ITEMS GUARANTEED TO YOUR SATISFACTION OR MONEY REFUNDED IF RETURNED PREPAID WITHIN 10 DAYS OF RECEIPT

NEW DEVICES (Continued)

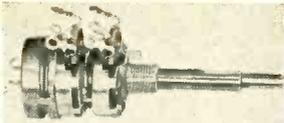


tric control. A variety of combinations.—P. R. Mallory & Co., Inc., 3029 E. Washington St., Indianapolis, Ind.

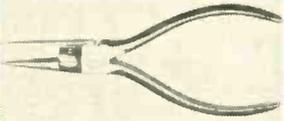LONG-NOSE PLIERS, no. 208-6-NC. For wiring by cut, hook



and crimp method. Replaceable cutting blade. Self-opening coil spring.—Mathias Klein & Sons, 7200 McCormick Rd., Chicago 45, Ill.

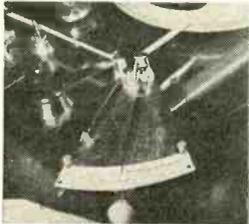TAPE TENSION GAUGE. Imported from West Germany,




this precision-built instrument measures the tension of tapes in tape recorders. All movable parts are mounted on ball-bearings.—American Elite Inc., 7 Park Ave., New York, N. Y.

VARIABLE INDUCTORS. Subminiatures, 1 1/4 x 34/64 by 34/64 inches. AF-87 (illus-




trated): 30-500 cycles, 400-cycle peak. AF-88: 50-1,000 cycles, 800-cycle peak.—Burnell & Co. Inc., 45 Warburton Ave., Yonkers 2, N. Y.

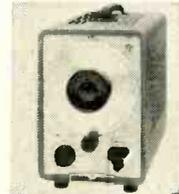AUDIO SWEEP OSCILLATOR, model 207A. 20-20,000 cycles.



±4% accuracy, including warm-up drift and component aging. Designed for motor drive.—Hewlett-Packard Co., 395 Page Mill Rd., Palo Alto, Calif.

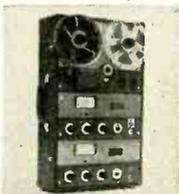
STEREOPHONIC RECORDER, model 601-2. 7 1/2 ips, 30-15,000



cycles. Separate record, playback, microphone and line input amplifiers.—Ampex Corp., 934 Charter St., Redwood City, Calif.


INDICATOR SWITCH, Pan-i-Lite. For low-voltage indicating and switching applications, 6, 12 and 28 volts. Blue, red, green, white or yellow. Mounts in 3/4-inch hole.—Alden Products Co., 117 N. Main St., Brockton 64, Mass.

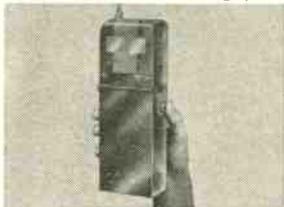RADIO-CONTROL UNITS, Model F-249 (illustrated): crystal-controlled, single-channel transmitter. 1-mile range, with




27,255 crystal and tube; F-208: matching receiver, 3 x 2 1/4 x 1 1/2 inches; F-327: motor-driven, electric servo mechanism, single-pulse operation, electronic return to neutral.—Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

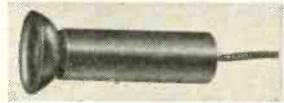TELEPHONE PICKUP COIL, model HP-61. Transcribes tele-




phone conversations with recorder or makes messages audible with amplifier. 3/8-inch diameter, 2 3/8 inches long. With 6-foot shielded cable terminated in standard phone plug.—Microtran Co. Inc., 145 E. Mineola Ave., Valley Stream, N. Y.

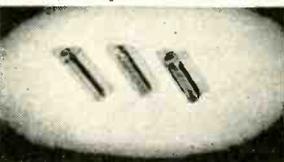ANTENNA-MATCHING COILS, for RCA TV sets. No. 1213 (center) replaces coils with



X-shaped cross section. Nos. 1214 (left) and 1230 (right) replace 2 hollow-core coil sizes.—Colman Tool & Machine Co., Amarillo, Tex.

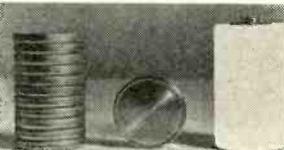NICKEL-CADMIUM BATTERY, rechargeable. For miniature and subminiature applications.



Available in 1.2-volt 0.25-ma-hour and 1.2-volt 0.5-ma-hour sizes.—Gulton Industries Inc., 212 Durham Ave., Metuchen, N. J.

POWER SUPPLY, model R-10. Dc output variable from 200-325 volts at 100 ma. Regulation better than .07% from zero to full load. Ripple less than 200 microvolts rms at 115 volts ac. Ac output, 6.3 volts, 3 amps. Ac input 105-125 volts, 60 cycles.—L. E. E., Inc., 625 New York Ave., N. W., Washington 1, D. C.

All specifications given on these pages are from manufacturers' data.

LEARN MORE! EARN MORE!
WITH H. G. CISIN'S TV SERVICE BOOKS

NEW 1957 TV TUBE LOCATOR—VOL. 2

Contains **TROUBLE INDICATING TUBE LOCATION GUIDES** for thousands of latest TV models including all most popular makes from Admiral to Zenith. Tells which tubes to replace to cure every trouble due to tube defects. Shows exact locations and gives types of all tubes.



directions for locating defective tubes causing each fault. 1954-1957 models.

TV TUBE LOCATOR—Vol. 1 contains over 3000 most popular TV models covering 1947 to 1953 sets.

These two books are a "must" for every TV service bench. A storehouse of TV tube servicing information.

VOL. 2—No. K2.....\$1.50 VOL. 1—No. K1.....\$1

ABC of COLOR TV



This easily understood new book takes the mystery out of Color TV.

Fully illustrated. Covers basic color principles, color transmission and reception, the color signal, color tubes. Helps you cash in on this profitable new field.

No. R1.....\$1

RAPID TV TROUBLE SHOOTING METHOD

New Edition

Novel TV servicing method enables a novice to diagnose TV troubles as rapidly as an expert. I.F., raster and sound troubles are listed and given code numbers. When combined they tell exact location of trouble.



No. T1.....\$1

TV CONSULTANT



The TV serviceman's silent partner. New rapid methods of pinpointing faults. Tells WHAT to do and HOW to do it. Includes UHF, COLOR and use of test instruments. **NO MATH, NO THEORY, NO FORMULAS.** Just practical servicing info covering all types of TV sets.

No. L1.....\$2


SHOOT TV & RADIO TROUBLE FAST

Quickest radio & TV trouble shooter locates radio & TV faults in record-breaking time, regardless of make or model. Section on printed circuits. Only book containing radio & TV trouble tracing in one vol.



No. T2.....\$1.50

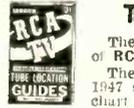RCA & ADMIRAL TROUBLE INDICATING TV TUBE LOCATION GUIDES



These two books contain the most complete compilation of RCA and ADMIRAL tube location guides ever published.

The RCA volume includes all TV models from the earliest 1947 sets to latest models, more than any 5 ordinary tube chart books.

The ADMIRAL book includes over 1500 Admiral TV models from the earliest sets to the newest 1956 models. Also contains a PICTURE GUIDE to TV tube troubles.

RCA GUIDE—No. A1.....\$1 ADMIRAL GUIDE—No. M1.....\$1

TV PIX GUIDE



Pictures show oft-recurring faulty TV conditions. Probable causes are explained and logical cures suggested. A second section clearly defines and explains technical TV terms. Over 70 illustrations. 1957 Edition

No. G1.....\$1

TV DOCTOR

Just the info. needed to start TV servicing. Includes: How to recognize and remedy TV troubles; How to replace defective tubes including Pix tube; Easy TV trouble checks; Color TV; Antenna know-how; How to combat interference, ghosts & Snow; UHF installation & servicing; How to read schematics and much other valuable TV info for beginners.



No. D5.....\$1

TV TUBE SUBSTITUTION GUIDE



Tube replacements for TV & radio sets. All fit same sockets and **NEED NO CHANGES IN WIRING.** Book also contains complete data on PICTURE TUBE replacements, many directly, others with only slight changes.

No. S1..Only 50c

TV TROUBLE TRACERS

Six vols. different **TROUBLE INDICATING TUBE LOCATION GUIDES** in each. Hundreds of popular TV models. Each vol. has over 70 illustr. 40 most common TV troubles illustrated.

Vol. 1 (No. TT1) Older sets
Vol. 2 (No. TT2) '52-'53 sets
Vol. 3 (No. TT3) '53-'54 sets
Vol. 4 (No. TT4) '54-'55 sets
Vol. 5 (No. TT5) '55-'56 sets
Vol. 6 (No. TT6) New PORTABLES & '57 RCA sets
Each Volume50c

FREE: \$2 WORTH OF BOOKS—FREE—with every purchase of entire CISIN TV LIBRARY of 17 valuable TV service books listed above. Regular Price \$15.50—yours for only \$13.50!

IF JOBBER IS OUT OF STOCK MAIL "NO RISK" TRIAL ORDER COUPON
5-day Money Back Guarantee

H. G. CISIN, Dept. E-43, AMAGANSETT, N.Y.

Enclosed find \$ _____ RUSH POSTPAID following books:

| | | | |
|------------------------------------|---------------------------------|------------------------------------|----------------------------------|
| <input type="checkbox"/> K2—\$1.50 | <input type="checkbox"/> A1—\$1 | <input type="checkbox"/> T2—\$1.50 | <input type="checkbox"/> TT2—50c |
| <input type="checkbox"/> K1—\$1 | <input type="checkbox"/> M1—\$1 | <input type="checkbox"/> T1—\$1 | <input type="checkbox"/> TT3—50c |
| <input type="checkbox"/> L1—\$2 | <input type="checkbox"/> G1—\$1 | <input type="checkbox"/> S1—50c | <input type="checkbox"/> TT4—50c |
| <input type="checkbox"/> D5—\$1 | <input type="checkbox"/> R1—\$1 | <input type="checkbox"/> TT1—50c | <input type="checkbox"/> TT6—50c |

Enclosed find \$13.50.
Send entire Cisin TV LIBRARY listed above.

Name.....
Address.....
City..... Zone..... State.....



Marion McPartland
makes her tape recordings on

irish
BRAND

ferro-sheen
recording tape.

That alone is not the reason
why you should use

irish
BRAND

ferro-sheen
recording tape.

Here's why you should use

irish
BRAND

ferro-sheen
recording tape:

It's the best-engineered tape in the world... gives you better highs... better lows... better sound all around! Saves your tape recorder, too — because the **irish** FERRO-SHEEN process results in smoother tape... tape that can't sand down your magnetic heads or shed oxide powder into your machine. Price? Same as ordinary tape!



Available wherever quality tape is sold.

ORRADIO Industries, Inc., Opelika, Alabama
Export: Morhan Exporting Corp., New York, N.Y.
Canada: Atlas Radio Corp., Ltd., Toronto, Ontario



MONITOR

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

Audio Follies
Bargain Sampler of Indecent Proportions

Cook L-XX

If Emory Cook set out to produce a hi-fi sampler to end all samplers, he may well have succeeded. Certainly no previous sampler comes close to offering so complete a sampling of a catalog or such a variety of sound.

There are 15 selections here from 15 Cook records, starting with very real trains, proceeding through steel bands, calliopes, carousels, a variety of unusual instruments such as the zither, cimbalon and pedal harpsichord, the more familiar organ (but in Cook's awesome realism), the orchestra and finally calypso and hot jazz. Many of these I have reviewed previously, but this recording may well be superior to the originals because it is pressed by the new Microfusion process.

The claimed superiority of this process seems to be realized. Surface noise is at a new low—though the material is not immune to electrostatic noise and, therefore, needs treatment for it. Cook claims, also, that the material is stiffer and, therefore, the high frequencies are not as likely to be wiped off. In any event the high highs are extremely sharp and the transient response very notable, indicating a wider and cleaner bandwidth. On all accounts, as a sampler of Cook's peculiar genius, hi-fi sounds and the new process, this is recommended without any reservations.

Fiesta in Hi-Fi
Hanson and Rochester Symphony
Mercury MG-50134

Here are four pleasant and colorful works by four contemporary American composers all based on familiar folk songs: McBride's *Mexican Rhapsody*, Nelson's *Savannah River Holiday*, Mitchell's *Kentucky Mountain Portraits* and Vardell's *Joe Clark Steps Out*. The music is both melodic and rich in orchestral color with a spectacular bass, tremendous drums and a variety of high highs. The recording is truly Olympian with tremendous crescendos—so tremendous that in spots even the best pickups may be overdriven if tracking and pressure are not optimum. Thus, it provides a very real challenge and test. But on those systems that can take it and dish it out, the effect will be sufficient to pop vest buttons with pride.

Hi-Fi Fiedler
Fiedler and Boston Pops
RCA Victor LM-2100

A very felicitous combination of music most people—even newcomers to music—will enjoy and brilliant sound that will nicely prove the value of high fidelity. The works are Rimsky-Korsakov's *Coq D'Or*, Rossini's *William Tell* and Tchaikovsky's *Marche Slave*. Between them they provide a little of everything from sharp high highs to thundering tympani. The balance is exemplary; though the recording is live, definition is excellent, and with the best pickups there will be no noticeable distortion. It will sound good on any hi-fi, but on the best it should pro-

vide a complete illusion of listening to a live concert in a seat 75 or 100 feet from the stage.

HONNEGER: Pacific 231
Rugby
and other works
Scherchen conducting Philharmonic Symphony of London
Westminster XWN-18486

Pacific 231 is the now famous musical impression of a locomotive which offers as fine fare for a first-rate (and test for poor-to-middlin') hi fi as there is on records. This version is particularly outstanding for the good double bass, very low drums, definition, clarity and the overall awesomeness of the performance. *Rugby* is a rather similar musical impression of a Rugby game. *Mouvement Symphonique* has been described as *Pacific 231* coming back. *Prelude to the Tempest* is even more awesome to my ear than 231 with its thunderous drums and buzzing strings. The other shorter works are of an earlier period. Here is a pretty good anthology of Honneger music and, for those who can tolerate it, excellent material for system testing—especially of definition and dynamic capability—as well as notably realistic samples of various instruments—particularly string basses and drum—and some remarkable tonal effects.

TCHAIKOVSKY: Nutcracker
(Excerpts)
Fiedler and Boston Pops
RCA Victor LM-2052

This version contains not only those most familiar excerpts usually performed as the *Nutcracker Suite*, but other less familiar portions of the original ballet. The music provides fine show-off and demonstration material particularly rich in the high percussives. The recording is outstanding with a brilliant liveness, realistic balance and very clean throughout.

KABALEVSKY: Comedians' Suite
Calus Breugnon Suite
Horlick conducting Paris Conservatory Orchestra
Schuechter conducting Philharmonia of London
MGM-E3506

The *Comedians' Galop* from *The Comedians* by this contemporary Russian composer has become a great pop favorite. Here is the full suite of excerpts from the original ballet. While the other sections are not as exciting as the *Galop*, they are all interesting in tone coloration and pleasant to listen to. The less familiar *Suite from Calus Breugnon*, an opera, possesses equal interest and even more spectacular sound material, particularly a fine bass, heavy drumming and big climaxes. The recording is one of MGM's very best with a fine balance, liveness and exceptionally clean.

The Deutschmeisters Take a Holiday
Deutschmeister Band conducted by Herrmann
Westminster WP-6044

There are bigger brass bands than the Deutschmeister and there are records of bands playing more demanding music, but no other band plays with such an authentically Viennese sentiment-

Now you can order precise KITS BY MAIL... from Your Local Parts Distributor!




Precise Engineered QUICK-TEST TUBE TESTER

Only 3 Knobs for GM, EM, Short and Gas Tests.

This is the finest fast-check tube tester and dollar-earning traveling companion for a Serviceman... or for use in the factory. You can plug in 5 tubes of the same type and check each one individually by rotating the Tube Bank switch. It actually checks 5 tubes in 20 seconds... or 4 seconds per tube. By rotating the function-switch, each triode of a dual triode is checked individually, each diode and the triode of a duo-diode-triode is separately tested and not lumped as in other testers... and a pentode is tested as a pentode—not a diode. Transistors, shorts, gas, life, mutual conductance and emission can be tested with this model. Includes a deeply etched panel, beautiful Moleskin covered wood carrying case and cover. Easy to carry.

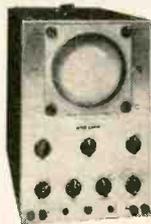Precise Model 116K Kit Form.....\$ 79.95
Precise Model 116W Factory Wired 139.95



Precise Engineered 5" SCOPE UP to 9 mc FLAT to 5 mc for color work

After you've built this 'scope, you'll be amazed at its versatility. No other 'scope below a \$100.00 can meet all of its specifications. Design features include push-pull vertical and horizontal... high sensitivity... 5CP1 tube with post acceleration... frequency compensated stepping attenuators for both vertical and horizontal... focus, intensity and astigmatism controls... and calibration output voltage. Vertical amps are flat through 5 mc ± 8 db through 9 mc. Sensitivity is 10 mv/cm. Horizontal amps within ± 6 db through 500 kc, have frequency compensated stepping attenuator input and cathode follower to assure linear horizontal trace. Hard vacuum sweep frequencies with sufficient expansion to see color bursts clearly, and a sensitivity approximately 40 mv/cm, made this instrument the exceptional buy of the year.

Precise Model 3151K Kit Form\$ 59.95
Precise Model 3151W Factory Wired 109.95

Precise Engineered POWER LAB For all your electrical needs!

For the first time in the industry, one instrument takes the place of more than 11 pieces of equipment... Here's what you get:

- A BATTERY ELIMINATOR for 6v and 12v radios
- A BATTERY CHARGER up to 24 volts
- A HIGH CURRENT LINE VOLTAGE VARIAC — up to 10 amperes
- AN AC LINE VOLTAGE METER
- AN AC LINE AMMETER
- AN AC LINE WATTMETER
- AN AC LINE ISOLATION TRANSFORMER — 100w or 300w
- A LOW VOLTAGE, HIGH CURRENT AC SUPPLY — 24v at 10 amperes
- A DC LINE VOLTAGE VARIABLE SUPPLY
- A DC HIGH CURRENT AMMETER
- AN AGC BIAS BOX



| Precise Model | | Isolation |
|---------------|--------------------|--------------|
| 711K | KIT FORM | \$49.95 100w |
| 711W | FACTORY WIRED | 64.95 100w |
| 713K | KIT FORM | 62.95 300w |
| 713W | FACTORY WIRED | 79.95 300w |

Mutual Conductance and Emission TUBE TESTER

Here is a tester that actually checks a tube for its applications, not whether it is just good or bad. On the Model 111, GM and Emission are checked separately. It is the first and only device that measures 600-mil tubes on a meter Sweeps from 0 through the normal testing range when making measurements, which gives an average evaluation for the tube over an extended range of operation. Connects test voltages to each tube element. Uses a single rotary switch to check each element against every other element for shorts, whether they're hot or cold. Measures tube bias directly on a meter. Features a no-backlash roll chart. Includes provisions for testing all prong types. Cathode-Ray tubes may also be checked with the use of an adaptor. An exceptional instrument for the shop, one that has won an impartial independent scientific survey hands down.

Precise Engineered



Precise Model 111K Kit Form\$ 79.95
Precise Model 111W Factory Wired.... 139.95

You benefit from faster delivery, lower price, postage savings, and the personal local service of your nearby parts distributor when you order by mail... if you are close enough, drop by and see the top quality parts included in each kit. Here are 8 of the many PRECISE distributors who are ready to serve you. Use the handy coupon below to order your PRECISE kit by mail.



GRAHAM ELECTRONICS SUPPLY, INC.
102 S. Pennsylvania St.
Indianapolis 4, Ind.

H. H. Thompson... Creative Engineering and quality components assure customer satisfaction with PRECISE equipment.

LEUCK RADIO SUPPLY
243 South 11th St.
Lincoln, Nebraska

L. H. Soderholm... We have found that the advanced engineering of PRECISE kits offers design features comparable with many laboratory instruments.



RADIO ELECTRIC SERVICE CO. OF PENNA., INC.
N. W. Corner 7th & Arch Sts.
Philadelphia 6, Penna.

Albert N. Kass, vp & gen. mgr... For quality and precision, we always recommend PRECISE in test equipment.



STANDARD PARTS
277 N. Franklin St.
Hempstead, N. Y.

William Hull... Refreshing original design built into every PRECISE kit.



THRIFTY ELECTRONIC SUPPLY CO.
3647 Burbank Blvd.
Van Nuys, California

Al Ex... PRECISE engineered kits give you more value for your money.



WHOLESALE RADIO PARTS, CO., INC.
308 West Redwood St.
Baltimore 1, Maryland

Manuel Freeland, vp... We have found that PRECISE's Nock for giving quality and value — economically — goes hand-in-hand with our pursuits.



WINTERADIO INCORPORATED
1468 West 25th St.
Cleveland 13, Ohio

Edward J. Gorycyo... PRECISE kits—a quality line that has no equal.



TEE VEE SUPPLY CO.
3211 Washington St.
Jamaica Plains, Mass.

Herbert Gamer... Everyone who buys a PRECISE kit is always satisfied.

Mr. Precise Distributor:
I would like to order the following Precise kits:

| 5" Scope | Powerlab | Tube Tester |
|-------------------------------------|-------------------------------------|-------------------------------------|
| Model | <input type="checkbox"/> Model 711K | <input type="checkbox"/> Model 111K |
| <input type="checkbox"/> 3151 Kit | <input type="checkbox"/> Model 711W | <input type="checkbox"/> Model 111W |
| <input type="checkbox"/> 3151 Wired | <input type="checkbox"/> Model 713K | <input type="checkbox"/> Model 116K |
| <input type="checkbox"/> Catalog | <input type="checkbox"/> Model 713W | <input type="checkbox"/> Model 116W |


Please send kits COD Bill my account
Remittance Enclosed, Ship Prepaid

Print Name Clearly

Street Address

City & State

Transistorized Power Supply

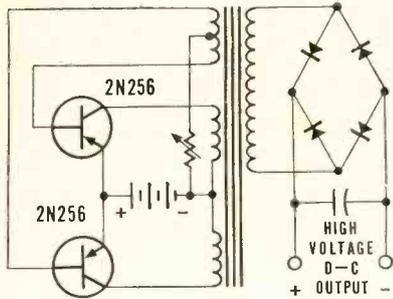

Go modern. Build this transistorized mobile power supply using popular CBS 2N256. Compact combined inverter, rectifier and filter operates from automobile battery. Delivers up to 50 watts d-c output . . . for example, 250 volts at 200 ma. Replaces troublesome vibrator pack or dynamotor. Has no moving parts and offers efficiencies up to 85%. Inverter output is square-wave . . . 0.1 mfd filters it. This easy-to-build supply is ideal for mobile . . . transmitter, receiver, sound system, etc.

CBS 2N255 (6-volt) and 2N256 (12-volt) power transistors are useful in many other economical amplifiers . . . fixed or mobile. Write for CBS Power Transistor Applications, PA-16, for complete details on 15 practical circuits, including this power supply. Or pick up Bulletin PA-16 along with your 2N255 and 2N256 transistors at your CBS Tube distributor's.



2N255...\$2.60 net

2N256...\$3.00 net

CBS-HYTRON

Semiconductor Operations, Lowell, Mass.
A Division of
Columbia Broadcasting System, Inc.

NEW RECORDS (Continued)

tality or sounds more like brass bands used to sound in that golden era of brass bands 50 and more years ago. Here they are again with eight engaging concert marches, waltzes, polka, etc. The drum is big and untrickily beats a big beat, the snares play the typically Teutonic cliches, the brasses have that real Continental plaintiveness. There are just enough instruments to give the music full color, but not so many that any choir is drowned out. The recording is extremely good and the definition especially is outstanding.

SURINACH: Second Symphony
TURINA: Rhapsodia Sinfonica
Winograd conducting Philharmonia of Hamburg
With Sandra Bianca, piano
MGM E-3510

Somehow or other the blend of modern and Spanish is far more palatable than straight modern. In any event, it produces in these works some interesting sound, well punctuated with percussion and accentuated by some big peaks. Surinach is more modern than Turina, yet sounds more Spanish in this particular work. Even those who ordinarily dislike modern music may find both these works engaging. The recording is one of the best of this orchestra and presents the music to very good advantage.

HOVANESS: Anahid
Alleluia and Fugue
Tower Music
Surinach conducting MGM Orchestra
MGM E-3504

I have previously reviewed several recordings of this very individual American composer. This one gives a pretty good review of his three periods: *Alleluia and Fugue* goes back to his more conventional early days, *Anahid* is from his Armenian period and *Tower Music* from his more recent neo-Archaic period. The three works are fairly representative though not the most remarkable of his unique style. There are plenty of unusual effects, including a bass solo and considerable percussion. I do not know why some of it was cut so high, however, with the result that in spots even solitary trumpets are ragged.

BRAHMS: Symphony No. 1
Munch and Boston Symphony
RCA Victor LM-2097

The first movement of this great symphony is almost a concerto for tympani, and a very fine showing they make in this recording. No comment is necessary about the music and everybody has his own preference as to its interpretation. The recording is clean, spacious and live enough to yield an appropriately romantic quality. Definition is good enough and the overall sound at a moderately loud level yields a fine presence. Not at all spectacular from a hi-fi point of view but an outstanding example of the way a fine hi-fi recording can enhance great music and yield an experience of it almost as good as a live performance.

LECLAIR: Concerto for Flute, Strings and Harpsichord
HAYDN: Concerto for Flute and Strings
PERGOLESI: Concerto for Flute Traverso
Camillo Wanaussek, Flute
Pro Musica Chamber Orchestra of Vienna
Vox PL-10-150

The flute is one of the most felicitous of all instruments on a fine hi-fi system and this recording provides three very fine examples of music written especially for it, beautifully and very cleanly recorded. Incidentally, if you live in an area where there are lots of birds, play this next spring when they are in their best voice and you'll attract a choir of flute-lovers and imitators.

SHUBERT: Death of Lazarus
Winograd conducting Philharmonia of Hamburg
With vocal soloists
MGM E-3526

This was intended to be the first act of a full-length opera, but only the first act was finished. It was not performed until very recently and




ASTRON EXACT REPLACEMENT CAPACITORS

A serviceman's reputation is his most important asset. And Astron is determined to help you protect yours . . . to do this we developed "Staminized" Capacitors, a special group of service-designed units that guarantee reliable, no-call-back performance under the severest conditions.

You can stake your reputation on this Astron quality and win everytime!

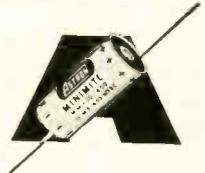
• **MINIMITE*** "SAFETY MARGIN"* Miniature Electrolytics. Very stable capacitance characteristics; low resistance contacts; crystal clear markings; specially sealed against moisture.



• **TYPE ES** "SAFETY MARGIN" Tubular Electrolytics. Plastic-wrapped, moisture-proof sections; conservatively rated; high quality foil specially etched; pre-tinned leads.



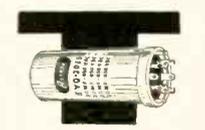
• **TWIST-PRONG** "SAFETY MARGIN" Electrolytics. Wide range of single/multiple-section types; reliable operation up to 85° C; clearly marked terminal code.



• **TYPE E** "SAFETY MARGIN" Screw-Base Electrolytics. Mount quickly, easily with supplied palnut; pre-stripped, pre-tinned leads; stable operation; special terminal design stops moisture damage.



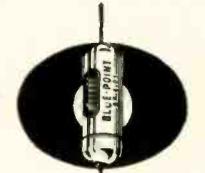• **BLUE POINT®** Paper Tubulars. Finest plastic-cased capacitor made; exclusive seals lock-out moisture, lock-in leads; tough heat-proof shell; clearly marked.



• **TYPE AP** - Ceramic-Cased Tubulars. Rugged, oil-impregnated, paper section construction; non-melting end seals hold leads firm; economical for all replacements.



FREE SERVICING AID

Astron offers a wide variety of materials to help you service better . . . send for your copy of handy, pocket-sized Replacement Catalog AC-4D . . . it will save you time!



NEW RECORDS (Continued)

won some acclaim not only for its intrinsic musical values but for its Wagnerian effects as well. This recording presents it complete and is the first performance on American records.

BACH, K.P.E.: *Concerto for Four Viols*

MASCHERA: *La Capriola*

GABRIELI: *Canzone*

TOMOSINI: *Suite for Violetta*

Ensemble Marius Casadesus

Westminster XWN-181-30

Four composers of the 16th, 17th and 18th centuries are represented here with chamber works performed on ancient string instruments by a group which has specialized in recreating this music as authentically as possible. Especially interesting to me was the way four viols in the Bach concerto's second movement manage to sound like an organ. Thanks to the fine recording, the contrast of the viols to our modern violins is well and flatteringly presented. You don't have to be a musical antiquarian to enjoy this music either.

VIVALDI: *Concerto for Two Trumpets in C*

Concerto for Two Trumpets in E Flat

Concerto for Oboe and Strings in D

Minor

Concerto for Oboe and Strings in F

Winterthur Symphony Orchestra

Concert Hall CHS-1242

Except in brass band music, the trumpet is seldom allowed to take the spotlight. Here a pair of them is given the opportunity to showoff both the capability of the instrument and the virtuosity of its players in very pleasant music and a very fine recording which presents the trumpets at their best and a very fine test of mid-range and tweeter coloration. Assuming the pickup tracking is good, the tone should be clean and sweet throughout, brassy but without stridency. The oboe is about a half octave higher in range and offers a contrast in tone. This one is unusually sweet and mellow.

COPLAND: *Piano Concerto 1926*

Leo Smit, piano; Radio Rome Sym-

phony conducted by the composer

BLOCK: *Four Episodes for Chamber*

Orchestra

Scherman conducting

Radio Zurich Symphony Orchestra

Concert Hall Society CHS-1238

This is an early Copland, seldom heard nowadays, in which he employed jazz idioms. It will be especially interesting because it is conducted by its composer and because it shows only traces of the style so characteristic of his later works. The Block *Episodes* are very interesting chamber music with an oriental flavor in spots—modern but most people would find the modernisms unobjectionable. The recording is excellent except that it is overcut in spots and will drive some pickups into distortion.

VERNON DUKE: *Souvenir de Monte Carlo*

ROBERT COBERT: *Mediterranean Suite*

Surinach conducting

MGM Chamber Orchestra

MGM E-3497

An opportunity to savor hitherto unperformed music. Duke is a Russian-born contemporary American composer who has scored Broadway shows and some popular songs, including *April in Paris*. He has also written serious music (at first under his patronimic Dukelsky) which shows very few traces of Broadway or pop music. *Souvenir de Monte Carlo* is a ballet composed about ten years ago but never produced. Cobert is a clearly promising young American composer who here receives the first performance of his works. Neither of these is at all hard to listen to. Both have some excellent percussion. The recording is excellent. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.



Simpson

announces

NEW

HANDISCOPE

model 466

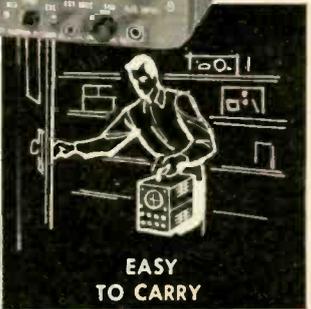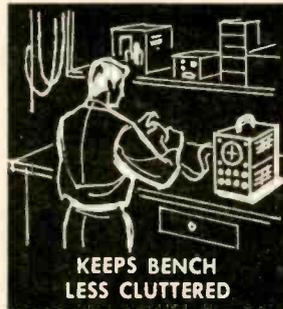

perfect for:

- Hi-Fi troubleshooting
- Industrial maintenance
- Production line tests
- Communications equipment checks
- AM & FM radio servicing
- Useful for black and white TV, too

MEASURES ONLY 8" x 12 1/4" x 16 1/2"—Use this rugged little instrument for the 101 jobs where a big specialized scope isn't needed. It brings you quality features such as a filter type graticule, universal-fit bezel, and 5" screen, yet is economically priced. And like other Simpson test equipment, Model 466 is built to give you years of hard service.

Frequency Response of Vertical Amplifier:
From 15 cycles/sec to 100 Kc/sec, flat within ± 1 db; 6 db down at 250 Kc/sec; useable to 1 Mc/sec.

Maximum Vertical Deflection Sensitivity:
30 Millivolts RMS/inch.

Frequency Response of Horizontal Amplifier:
From 15 cycles/sec to 20 Kc, flat within ± 1 db; 6 db down at 100 Kc/sec.

Maximum Horizontal Deflection Sensitivity: 0.7 volt RMS/inch.

Z-Axis Sensitivity (Voltage Required to Extinguish Beam): 20 volts RMS.

Calibrating Voltage (at 117.5 VAC power source): 1 volt P-P $\pm 10\%$.

Maximum Input Voltage: 400 volts peak.

Input Resistance: 0.1 Meg (at atten. x 1); 0.5 Meg (at atten. x 100).

Input Capacitance: 40 uuf (at atten. x 1); 35 uuf (at atten. x 100).

Sawtooth Sweep Range: 15 cycles/sec to 80 Kc/sec.

Power Consumption (at 117.5 volts AC): 50 watts.

Model 466 with Lead, Operator's Manual.....

\$144⁹⁵

See your Electronic Distributor, or write

SIMPSON ELECTRIC COMPANY

5200 W. Kinzie Street • Chicago 44, Illinois • Phone: EStbrook 9-1121

In Canada: Bach-Simpson Ltd., London, Ontario




WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

another



quality
engineered
product

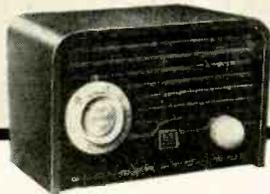


all channel UHF converter

Model 99 is your best buy in a UHF converter. Features include tuned input, precise impedance match, UL approval, one-knob tuning and drift-free performance. Largest selling UHF converter in the country at \$22.95 list ... In difficult reception areas use the BTU-2..... only \$39.95

another



quality
engineered
product

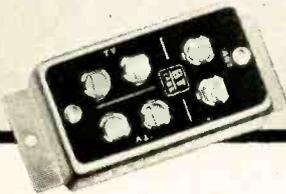

2-set coupler

Model TV-42 a 2-set coupler approved for color, UHF, VHF and FM. Matched resistive circuit with 12db interset isolation and flat response—0-900 megacycles. Another quality TV accessory engineered by B-T Labs..... \$2.95 list

Sold by electronic parts distributors
for further information
use coupon below

BLONDER-TONGUE LABS, INC. RE-10
9-25 Alling Street, Newark 2, N. J.
Please send me literature covering
 B-T TV Accessories
Name.....
Address.....
City..... Zone..... State.....


Technotes



CROSLLEY AT-10M

Complaint: excessive buzz, most pronounced on strong and medium signals. The set employs a gated beam tube as FM detector, limiter and first audio

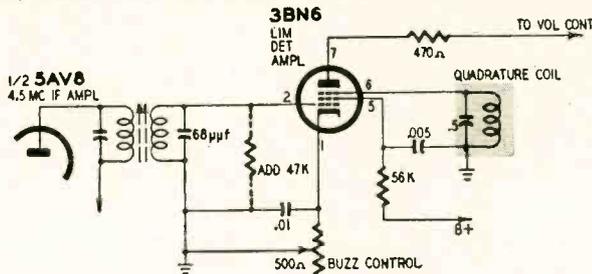As a cure, the secondary of the if transformer feeding the 3BN6 was shunted with a resistor as shown in the partial schematic. The highest value



amplifier. For minimum buzz the alignment of the preceding 4.5-mc if coils must be on the button. A high hiss developed whenever alignment was attempted, showing that the stage was oscillating at an ultrasonic rate.


that would permit alignment was 68,000 ohms. To insure a permanent cure, a 47,000-ohm resistor was installed with no noticeable loss of volume. (The added resistor acts as a damper to kill the oscillation.)—J. R. Vought

DUMMY TUBE

Not long ago, trying to find which tube had an open heater in a transformerless Motorola VT-71, I had an unusual experience. As a substitute for other tubes, I was using a 6AG5 which had a cathode-to-heater short and which had the cathode pins cut off. Soon I found the bad tube—a 6AU6 limiter. And, much to my surprise, the audio operated loud and clear! With a limiter

tube without cathode pins! Only when the audio control was fully advanced, could any audio disturbance—a 60-cycle hum—be heard. Evidently the cathode, shorted internally to the heater, was reaching ground through the heater string. And bias must have been correct because there was no noticeable distortion on normal audio levels! —B. W. Welz

RCA TRANSISTOR PORTABLE

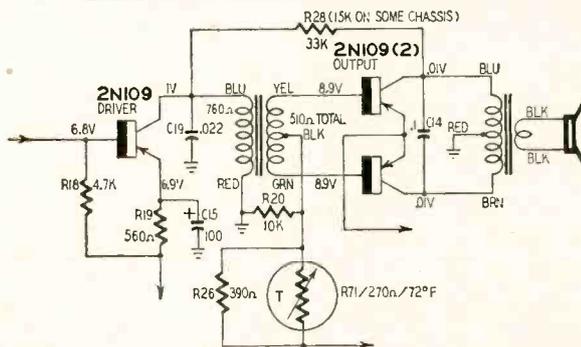

In model 7-BT-10K a 33,000-ohm resistor R28 has been added from the collector of the driver to the collector of one of the output transistors as shown in the diagram. This introduces negative feedback, improving audio response and cutting distortion.


Other components are changed in value as follows: R19, from 1,000 ohms to 560; R20, from 12,000 ohms to 10,000; C19, from .0047 μ f to .022. The affected components are shown in the partial schematic.—RCA Victor and Victrola Service Tips

FRONT-END FAULT

We were demonstrating a new color bar generator on an early Sylvania 15-inch receiver. The receiver gave good results on color TV programs. The generator looked very bad with incorrect hues for all bars except black and

white. No setting of the color phasing control served to produce correct hues. We then considered the possibility of the tuner having poor response on the channel for which the generator was set (channel 3). There was no possibil-

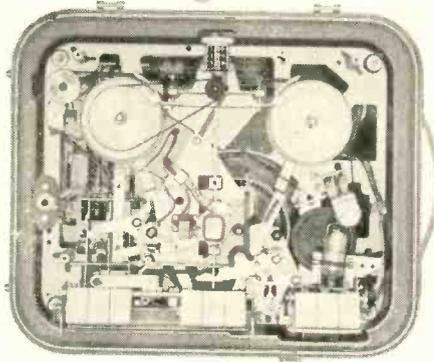**THIS IS THE WAY
A GREAT
TAPE
RECORDER
IS BUILT...**



the
new
imported

NORELCO®

'CONTINENTAL'

*world's
most advanced
all-in-one
portable*

**TAPE
RECORDER**

Engineered by Philips of the Netherlands, world pioneers in electronics
Precision-crafted by Dutch master technicians

Styled by the Continent's top designers
Three speeds (7½, 3¼ and 1½ ips) ...
twin tracks... pushbutton controlled
Special narrow-gap (0.0002 in.) head
for extended frequency response
Built-in wide-range Norelco speaker
Also plays through external hi-fi set

*For the name
and address
of your nearest
Norelco dealer,
write to*



Norelco NORTH AMERICAN PHILIPS CO., INC.
High Fidelity Products Division
230 DUFFY AVENUE, HICKSVILLE, L.I., N. Y.


TECHNOTES (Continued)

ity of switching channels, since the generator was fix-tuned. Another color receiver was not available for a cross check.

We did have a spare tuner and wired it into the receiver. This solved the problem, all colors came through properly both on a channel-5 program and on channel 3 with the generator. Another example of the fact that tuned-circuit response is considerably more important for color reception than for black-and-white.—Robert G. Middleton

COMPRESSION

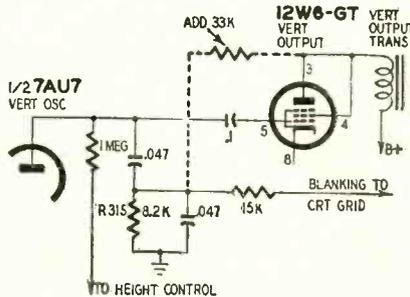A Tru-tone TV model 2D1530B showed compression of scanning lines at the top of the picture. Tube changes and linearity-control manipulation would not remove the bunching.



The condition was remedied by feedback to the vertical peaking resistor from the vertical output transformer. As the diagram shows, a 33,000-ohm resistor was connected from the hot side of the peaking resistor (R315) to the plate (pin 3) of the vertical output tube. Value of the resistor may have to be a little higher or lower for different sets of the same model.—Peter Miliano

ADMIRAL TUNERS

Poor performance in Admiral all-channel tuners may be due to improper lead dress. The lead between the uhf antenna terminals and the uhf tuner doubles as a quarter-wave trap at the mean frequency of the low vhf channels and a three-quarter-wave trap at the mean frequency of the high vhf channels. The lead must be dressed away from any metal, particularly the metal brackets of the rear kinescope mount. If the lead is found doubled up or looped it should be straightened out.—Warren J. Smith


END



"Plenty of B plus, but no B minus!"


**8 NEW
B-T
LABS
PRODUCTS**

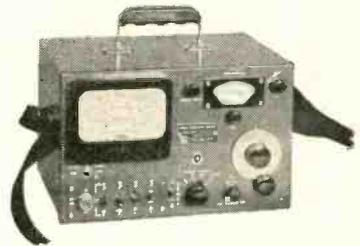... just a few of the many
new B-T precision
engineered products



FIELD STRENGTH METER Model FSM-1

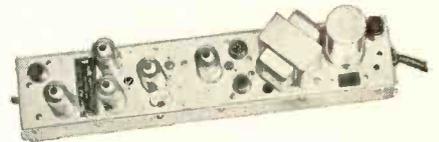A portable precision instrument for accurate measurement of RF signals. Continuous tuning from 54 mc to 216 mc covering VHF-TV, FM, mobile, aircraft, ham, industrial and CD. Use of B-T UHF converter extends range to entire UHF band. **\$310 net**



3 MASTERLINE CRYSTAL-CONTROLLED CONVERTERS

Model MVC: Hi-to-Lo channel VHF converter.
Model MLC: Lo-to-Lo channel VHF converter.
Model MUC: UHF to VHF converter.

Extremely stable, self-powered with two matched 75 ohm outputs. All channel VHF mixing network. Flat within ½ db over full 6 mc output. For color and black and white TV.

4 INDOOR TV SYSTEM TAPOFFS

Easy to install, matched low cost tapoffs
Model TO1-75: single isolated tapoff for recessed mounting. For RG-11/U or RG-59/U, with 75 ohm jack.
Model TO1-300: has 300 ohm terminals.

Model TO2-75: two 75 ohm outlets from RG-11/U or RG-59/U cable.
Model TO2-300: two 300 ohm isolated outlets from RG-11/U or RG-59/U cable.

sold by electronic parts distributors
for further information use coupon below

BLONDER-TONGUE LABS, INC.
9-25 Alling Street, Newark 2, N. J. Dept.

Please send me literature covering:

Field Strength Meter Masterline Converters
 Indoor TV System Tapoffs

Name.....

Address.....

City..... Zone..... State.....

NOW—
Get it from
your Parts
Jobber!

Admiral—
 rated by servicemen
 as the most foolproof
 and trouble-free of
 all changers!

Admiral—
 built into more
 phonos and combinations
 than any other
 changer in the world!

Admiral®


4-Speed Record Changer

Hi Fidelity



Beige and Coral
 with Golden trim
 (Base Optional)

- **PLAYS ALL FOUR SPEEDS—** 33 $\frac{1}{3}$, 45, and 78 plus "talking book" 16 $\frac{2}{3}$ r.p.m. Has neutral position. Changes 12 to 14 records; intermixes those of same speed. Automatic 2-way shut-off after last record. Returns tone arm to rest, stops turntable motor completely. NOTE: Can be wired to shut-off radio or amplifier chassis.
- **RUBBER TURNABLE MAT**
- **FEATHERWEIGHT TONE ARM—**new resonance-free design. Less than $\frac{1}{3}$ oz. pressure. Positive tracking . . . no "skip" or "jump" on loud passages.
- **DIAMOND LP STYLUS—**separate LP diamond and 78 r.p.m. sapphire needles for finest sound reproduction, long record life.
- **ATTACHED 40" SHIELDED AMPLIFIER CABLE—**eliminates pickup of unwanted noise. Cable has phono tip plug for quick easy connection into standard input phono-tip jack.

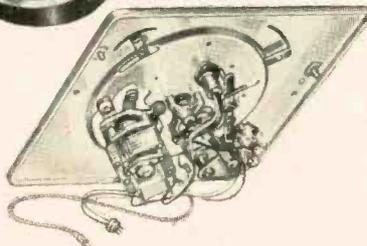

HEAVY DUTY MOTOR—powerful 4-pole constant speed shaded pole induction type motor. Operates without hum, rumble or "wows" (as little as 0.1590). Maintains even speed even if line voltage varies. Six foot line cord attached.



CERAMIC PICK-UP CARTRIDGE—twin lever hi-fi cartridge changes with flick of the finger from LP to 78 r.p.m. needle. Impervious to heat and humidity. High lateral compliance minimizes wear, eliminates hum and distortion. Smooth even response (± 3 db) over the full high-fidelity frequency range (30-15,000 c.p.s.).

Write for Illustrated Specification Sheet.

Admiral® / SPECIAL PRODUCTS DIVISION
 3800 West Cortland Street
 Chicago 47, Illinois



TEXAS ELECTRONIC FAIR

The Texas Electronics Association (TEA) held its fifth annual clinic and Fair on Aug. 2, 3 and 4, at the Texas Hotel in Fort Worth, Tex. Total attendance was more than 450, out of a total registered membership of over 500.

The opening night was highlighted by a banquet. After the invocation, the guests were addressed by Tommy Thompson, of the Fort Worth City Council, representing the Mayor; Bill Inman, president of TEA, and the Honorable Robert S. Calvert, Comptroller of the State of Texas. Keynote speaker of the evening was Hal F. Bersche, of RCA, who spoke on "The Future of Independent Service in Electronics."

The second day's features included addresses by John Bennett, general manager of Philco's factory-supervised service program, and J. A. Milling, president of Howard W. Sams, Inc. Mr. Bennett's talk dealt with "Etiquette for Servicemen" and Mr. Milling discussed "Selling Service."

After a coffee break the technicians heard talks by Cecil Lightfoot, of Texas Instruments Co. on "Transistors and Their Effect in the Service Industry" and on the "TV Orphan," by Irv Tjomsland (see RADIO-ELECTRONICS, July, page 103) of Triad Transformer Corp. Then the group was addressed by Robert K. Cannell, service manager of V-M Corp., on "Servicing Tape Recorders." After lunch John Thompson of G-E Distributor Sales Tube Division spoke on "Service Can Be Profitable." "Color Alignment and Convergence" was discussed by Verne Ray, editor of Howard Sams' *PF Reporter*.

Management seminars during this period covered "Independent vs Captive Service" by Dick Fenick of Tung-Sol Tube Co. and "Basic Needs of the Modern TV Shop" by E. W. Merriam, of Sylvania, followed by an open discussion period.

On the closing day the first address was by Ed Meagher of CBS-Hytron on "An Eye to the Future." Technical personnel heard talks by Al Coumont of Sprague on "Ceramic Capacitors and Their Application" and the day was ended with a panel discussion of various technical problems. James Palmer of TEA moderated the panel consisting of Bill Renner, Ed Meagher, Irv Tjomsland, Bob Hodges, Cecil Lightfoot, Gordon Gow, Al Coumont and Clint Walter.

During the talks several interesting facts were brought out, including the

successful effort by TEA and its members to kill a licensing bill brought up in the Texas Legislature during the past session, but whose principles were considered incorrect by TEA members.

The business sessions closed with talks on "Advertising and Promotional Aids" by Wm. J. Nagy of Philco; "Accident Reduction Made Effective" by Bill Leonard of the National Safety Council and "Developing a Store's Personality" by Al Robertson of Oklahoma City.

NEW GUILD FORMED

A state organization of independent radio-television service groups was created at a recent meeting held in Cambridge by delegates from six Massachusetts cities. The group is chartered as the Electronic Technicians Guild of Massachusetts (ETGM).

Elected president of the new group was Nicholas A. Averinos, Colonial Radio & Appliance Co., South Weymouth; vice president, Gilbert P. Clark, Centronics Co., Newton; secretary, Lawrence J. McEvoy, technician, West Newton; treasurer, Albert N. Giddis, TV service manager, Lowell; assistant to the president, Remo DiNicola, South Shore Television Services, Quincy.

LETTER TO THE FTC

The following letter was sent by the National Alliance of Television & Elec-

tronic Service Associations (NATESA) to the Federal Trade Commission: "Gentlemen:

"We note with growing concern the tremendous pressure being exerted upon your commission to authorize 'Pay-as-you-see TV.' It appears that those who are pushing the hardest are huge, interlocking combines which would profit immensely from authorization of captive broadcasting. It appears that exclusive rights to movies, sporting events, etc., are tied up by these people and that manufacturing facilities are also already within these combines.


"With such potential monopoly so evident in other phases touching upon 'Pay-as-you-see TV' and in view of the fact that should authorization be forthcoming, control of the operation of all sets would become vital to the operators, it becomes crystal clear that the monopoly would be extended to include service and maintenance of TV sets.

"The independent TV service people, of whom there are roughly 120,000, have pioneered and developed the service business at great cost and sacrifice. They are little, little businessmen and cannot easily afford the cost of defending their rights against huge corporations. Further, they have learned from many years of contact with set owners that by and large, the public is happy with TV broadcasting as now practiced, even though they may not be completely satisfied.

Bob Middleton

says:

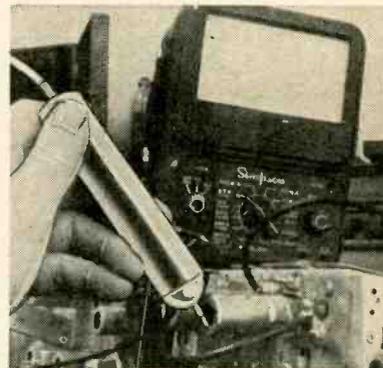"Here is a real Service Short Cut, SIGNAL TRACING WITH A VOLTMETER!"



For information, see your Jobber or write to:

Futuramic
Co.

915 S. Broadway


Park Ridge,

Illinois



You'll be delighted!

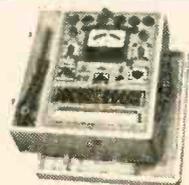
with EMC's New Test Equipment . . . in advance design and precision construction features found only in higher priced instruments. It pays to save more and service better with the complete EMC line.



NEW! EMC Model 206P
Dynamic Mutual
Conductance
Tube Tester

The lowest priced mutual conductance tube checker on market. Checks tubes for microhmo value and gas content. Completely flexible switching. Your best buy in a quality tube tester.


Hand Rubbed
Carrying Case \$83.50

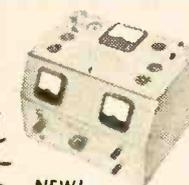

NEW! EMC Model 905-6A
Battery Eliminator,
Charger, and
Vibrator Checker

A MUST for auto radio service. Features continuously variable voltage output — In either 6 or 12 volt operation. Checks all 6 or 12 volt vibrators.

Wired \$67.90
In Kit Form \$44.90

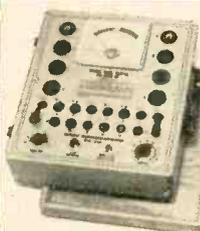

NEW! EMC Model 301
Speedi Tube Tester

Precision crafted for checking tubes in seconds. Only 2 settings to make. Checks for shorts, leakages, and quality. Over 375 tubes now listed, including 024 tube. New listings available. Uses line voltage regulation. Checks and rejuvenates picture tubes with Model PTA, Picture Tube Adaptor (only \$4.50).


Model 301P (illustrated), with 4 1/2" plastic front meter in oak carrying case, \$47.50; Kit, \$33.20.



NEW! EMC Model 108
Handi Tester

The only appliance and auto battery tester in its price class to use a D'Arsonval, instead of an iron vane type meter. You get exclusive advantages of maximum accuracy, maximum scale length, and minimum battery replacement cost . . . yet, pay no more than for competitive makes. Comes complete with test leads and instruction manual.

Wired \$15.95
In Kit Form \$12.95

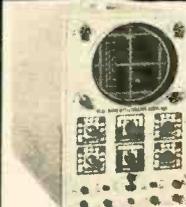

NEW! EMC Model 601
Wide Band Oscilloscope
For Color And Mono-
chrome TV

Exclusive features: full 5 mc band-width for color TV servicing — push-pull vertical amplifier, .02 volt per inch sensitivity — 5 U P 1 — 5" scope tube — 60 cycle phasing control — DC positioning controls eliminates overshooting and bounce — built-in peak to peak calibration reference — 2-step compensated attenuator input — multi-vibrator sweep, from 15 cycles to over 75 kilocycles. \$117.90, wired and tested.

Yes, I want to see for myself, send me ^{RE-10}
FREE — a detailed catalog of the COMPLETE
EMC LINE OF PRECISION TEST EQUIPMENT.

NAME _____

STREET _____

CITY _____ STATE _____

EMC ELECTRONIC
MEASUREMENTS
CORPORATION

625 Broadway, New York 12, N. Y.
Export Dept. — 370 Broadway, New York 13, N. Y.

for

LOWEST
hum...noise...
microphonics
in a high- μ dual triode . . .



the

Amperex®
ECC83 A PLUG-IN
REPLACEMENT FOR THE 12AX7

MICROPHONICS:

Negligible in amplifiers requiring an input voltage of at least 50 mv for an output of 5 watts. No special precautions against microphonics necessary even though the tube is mounted in the near vicinity of a loud-speaker with 5% acoustical efficiency.

HUM AND NOISE LEVEL:

Better than -60 db relative to 50 mv when the grid circuit impedance is no greater than 0.5 megohms (at 60 cps), the center tap of the heater is grounded and the cathode resistor is bypassed by a capacitor of at least 100 mfd.

OTHER Amperex TUBES FOR HIGH-FIDELITY AUDIO APPLICATIONS:

- EL84/6BQ5 9-pin power pentode; 17 W PP
- 6CA7/EL34 High-power pentode; 100 W PP
- EF86/6Z67 Low-noise high- μ pentode
- ECC81/12AT7 Low-noise medium- μ dual triode
- ECC82/12AU7 Low-noise low- μ dual triode
- ECC85/6AQ8 High- μ dual triode for FM tuners
- GZ34/SAR4 Cathode-type rectifier; 250 ma.
- EZ80/6V4 9-pin rectifier; cathode; 90 ma.
- EZ81/6CA4 9-pin rectifier; cathode; 150 ma.

At All Leading Electronic Parts Distributors

Amperex
ELECTRONIC CORP.
230 Duffy Ave., Hicksville, Long Island, N.Y.



TECHNICIANS' NEWS (Continued)

"Small service businesses are good for the American economy in both peace and war. With the rapid development of bigness in all phases of business, we believe service is the last frontier of free enterprise and that it must be preserved.

Sincerely,
Frank J. Moch
Executive Director"

ASSOCIATION MAGAZINE

The first issue of the SRTT IPET has appeared. It will be produced and distributed monthly as the official publication of the Society of Radio and Television Technicians, Inc. of California (SRTT). IPET means: for the Independent Professional Electronic Technician. The magazine is mailed free each month to members of SRTT and nonmember radio and TV dealers in the San Fernando Valley and the adjoining territory.

GUILD HITS DISTRIBS

Long Island, N. Y., electronic parts distributors were blasted for indiscriminate consumer sales by the Radio & Television Guild of Long Island (RTG). A report in the *Guild News*, the association's monthly journal, listed distributors accused by the guild of indiscriminate sales. Also listed were distributors who would not sell to a consumer under any circumstances.

This action was taken after persistent reports from members indicated that existing guild shopping policies required strengthening. Long Island service dealers have strongly objected to the number of parts jobbers selling to defense plant employees.

The *Guild News* noted that, if the more than 200,000 defense workers of the region make an average annual purchase of \$5 in parts from distributors, more than \$1,000,000 in retail sales would be routed from normal retail outlets.

RTA-PASADENA NEWS

Recent meetings of the Pasadena Radio Television Technicians Association (RTA) have seen a group of informative speakers, due to the efforts of Cecil Parker and Bill Yatty, program chairmen.

Bernard H. Linden, of the Los Angeles FCC office, presented a full discussion on interference problems with a description of the makeup and activities of the Cooperative Interference Committee, and the local FCC office.

At another meeting Miss Lillian Dionne, representing the Pasadena Office of the Social Security Administrations, covered all aspects of social security from both employer and employe viewpoints with special reference to the problems of service technicians and dealers.

Another interesting talk was given by W. W. Cotie of the Hickok Instrument Corp. Mr. Cotie discussed tube testers and answered questions concerning his firm's test instruments. END

STAN-BURN

CATHODE RAY TUBE SPECIALS

ONE YEAR GUARANTEE

| G.E. | Type | STAN BURN | G.E. | Type | STAN BURN |
|---------|---------|-----------|---------|----------------|-----------|
| \$15.80 | 10BP4 | \$10.00 | \$30.75 | 17CP4 | \$20.50 |
| 19.10 | 12LP4A | 13.95 | 33.90 | 17GP4 | 21.50 |
| 18.75 | 12QP4 | 10.50 | 24.75 | 17LP4 | 18.00 |
| 20.75 | 14CP4 | 13.75 | 15.00 | 17RP4 | 24.00 |
| 33.75 | 13DP4 | 14.50 | 28.35 | 20CP4A | 18.95 |
| 32.20 | 16AP4 | 15.25 | 32.10 | 20CP4B* | 21.95 |
| 23.50 | 16KP4* | 15.75 | 36.50 | 21AP4 | 25.00 |
| 27.20 | 16KP4A* | 18.75 | 29.75 | 21EP4A | 20.15 |
| 33.75 | 16GP4* | 18.75 | 37.00 | 21FP4 | 21.15 |
| 31.90 | 16LP4A | 15.25 | 29.75 | 21VP4 | 22.00 |
| 31.50 | 18WP4 | 15.25 | 100.00 | 24AP4 | 56.00 |
| 23.50 | 17BP4 | 15.75 | | (6 mos. guar.) | |
| 27.50 | 17BP4B* | 18.75 | 46.60 | 24CP4A* | 38.00 |
| | | | 48.20 | 24DP4A* | 39.00 |

*Aluminized—INQUIRE FOR ANY TUBE TYPE NOT LISTED. STAN-BURN CRT TUBES RCA LICENSED—MFD. BY LINCOLN. All orders of 6 or more STAN-BURN CRT are subject to additional 10% discount. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

WHY PAY MORE?

- HI-FI COMPONENTS • KITS
- RECORD PLAYERS • TAPE RECORDERS • TUNERS
- AMPLIFIERS • SPEAKERS • ELECTRONIC PARTS & TUBES • Etc.

Top brand nationally adv. merchandise in this and other Radio & TV mags. is yours at low, low cost. Send us your list. Give Mfr's name and Model No. of item. Write for '57 catalogs to Dept. RE-10 today.

WHILE THEY LAST!!

BRAND NEW IMPORTED TAPE RECORDERS

Clear, sharp music and speech reproduction. Dual track, 5 tube, 6" tape reel. AMAZING VALUE!
single speed (3 $\frac{3}{4}$).....\$64.95
dual speed (3 $\frac{3}{4}$ & 7 $\frac{1}{2}$)..... 74.95

FREE reel of tape with each recorder!

HI-FI DIAMOND NEEDLES—1 Yr. Guar.

SINGLE DIAMOND NEEDLES.....\$9.49 ea.
DIA/SAPP TANDEM.....\$11.49 ea.
(Dual Needles)
Shipped PPD. (Specify cartridge make)

RECORD CHANGERS

Collaro RC-456, 4 speed changer.....\$33.81
Garrard RC-88, 4 speed changer..... 53.41
Garrard RC-98, 4 speed changer..... 66.15

FREE wood mounting base, record wiping cloth and 45 RPM spindle with all orders for Collaro and Garrard changers, with this ad.

VM 4 speed HI-FI CHANGER—Model 1210 with Ronette or Astatic flip-over cartridge.....\$22.95

MONARCH Model UA8U 4 SPEED AUTO. INTERMIX CHANGER less crystal cartridge.....\$19.95

RONETTE (phono fluid) cartridge flip-over type \$2.98
SONOTONE cartridge, flip-over.....\$2.98

General Electric Hi-Fi Variable Reluctance cartridge. Replaces discontinued RPN050 type. Full range reproduction 20—20,000 cycles. Four gram tracking force for minimum record and stylus wear.
4G050—Dual Sapphire needles, 33-15, 78.....\$18.99
4G052—Diamond, Sapphire needles.....\$8.77

KITS!

We stock the following manufacturers complete line of kits—see reference pages.
EICO see pages 33-34 DYNA see pages 164-165
QUALITY see page 177 ARKAY see page 167
PRECISE see page 147 ELECTRO-VOICE
BOGEN Inside Back Cover
GROMMES CABINART
All domestic orders will be shipped prepaid. Send us your list. Order by Mfr. and Model No. of item.

\$20 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: Porcelain sockets, coils, speaker, transf. resis, cond. ONLY.....\$1.98 (plus 50c postage)

RECORDING TAPE

Excellent reproduction qualities.
1800 Ft. Mylar.....\$2.59
1200 Ft. Acetate.....\$1.59

FREE! 32-page illustrated booklet—"Speaking of Loudspeakers" by University Co. Packed with info on the history and mysteries of speakers. Write today to Dept. RE-10

YOU NAME IT—WE HAVE IT


Complete line of T.V. & Radio receiving tubes, coils, transf., controls, antennas & accessories—No Minimum Order—DEALER DISCOUNTS! Thousands of satisfied Hi-Fi enthusiasts and dealers will vouch that STAN-BURN GIVES THE BEST DEAL POSSIBLE!
Export inquiries and offers invited.
Terms: 20% with order. Balance C.O.D. All prices F.O.B. NEW YORK Warehouse.
Write for our latest price list and Hi-Fi Catalog RE-10. All Prices Subject to Change Without Notice

STAN-BURN RADIO and ELECTRONICS CO.
558 CONEY ISLAND AVE. • B'KLYN 18, N. Y.

A Box Is Not A Musical Instrument!


your present
speaker
in a

KARLSON TRANSDUCER

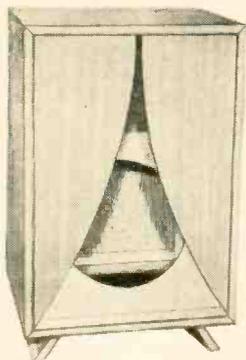

**CAN GIVE YOU
10x THE EFFICIENCY**

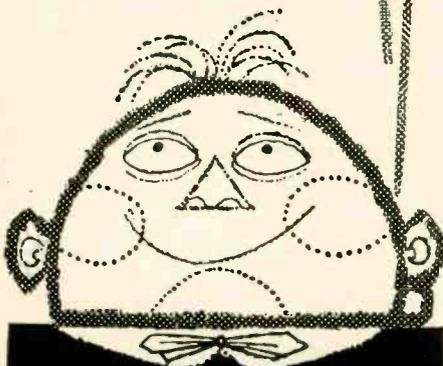- 2x the dispersion!
- 2 more octaves bass!
- Flatter response — Less distortion!
- Unexcelled transient response!



IN EASY-TO-ASSEMBLE

KITS

Hardwood exteriors - capable
of fine furniture finish -
from \$18.60 to \$57 net.

Also assembled models from \$26.70 to \$174.


See Your Dealer or Write:

KARLSON ASSOCIATES INC.

Send for your free catalog Dept. RE-8
1610 Neck Rd., Bklyn. 29, N.Y.




New Tubes & Semi- conductors

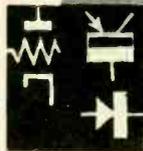

Among the month's releases are two transistors. One of these is accompanied by a diagram showing its use in a neon indicator circuit. A tube-based silicon rectifier, a multiunit seven-pin miniature and a stacked rectifier also appear.

2N398

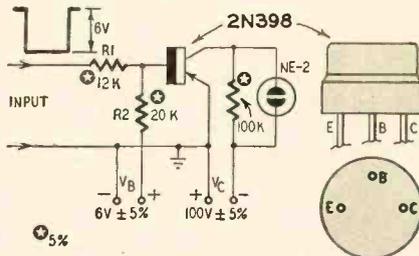A germanium alloy-junction transistor of the p-n-p type. Made by RCA and specifically designed for use in high-voltage, on-off control applications, particularly neon indicator, relay puller, incandescent-lamp driver and direct-indicating counter circuits of electronic computers.



A typical neon indicator circuit is shown in the diagram. An input of -6 volts lights the lamp by overcoming the transistor's cutoff bias and causing the 2N398 to conduct heavily (saturate), grounding the lamp through the low collector-to-emitter resistance. With 0-volt input, the 2N398 is cut off by the base bias circuit (V_B , R_2 , R_1) and acts like an open switch due to the high collector-to-emitter resistance.

Maximum ratings in switching service are:

| | |
|----------------------------------|------|
| V_{OB} | -105 |
| V_{CE} | -105 |
| I_E (ma) | 100 |
| V_{EB} | -50 |
| I_E (ma) | 100 |
| Dissipation at 25°C (mw) | 50 |
| at 55°C (mw) | 10 |
| Ambient temperature operating °C | 55 |

2N274

A drift transistor of germanium p-n-p type. Specifically designed for use as a rf amplifier in very compact military and commercial equipment and in entertainment type receivers operating at frequencies covering the AM broadcast band and up into the short-wave bands. An important design feature is the use of shielding to minimize interlead capacitance and coupling to adjacent circuit components. It is provided by a fourth lead situated between the collector and emitter leads and internally connected to the insulated metal envelope. The RCA 2N274 is

"LIVING SOUND" IS THE LUXURY

OF LISTENING TO REALISTIC REPRODUCTION

THROUGH Norelco® TWIN FULL RESPONSE SPEAKERS



Write today to Dept. D-10 for brochures and attractive prices of these unique speakers.

NORTH AMERICAN PHILIPS CO., INC. • 230 Duffy Ave., Hicksville, L. I., N. Y.

OXFORD HI-FIDELITY SPEAKERS

Optimum Range at Minimum Cost!

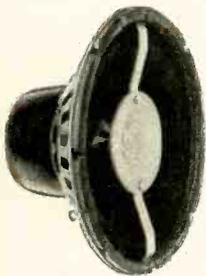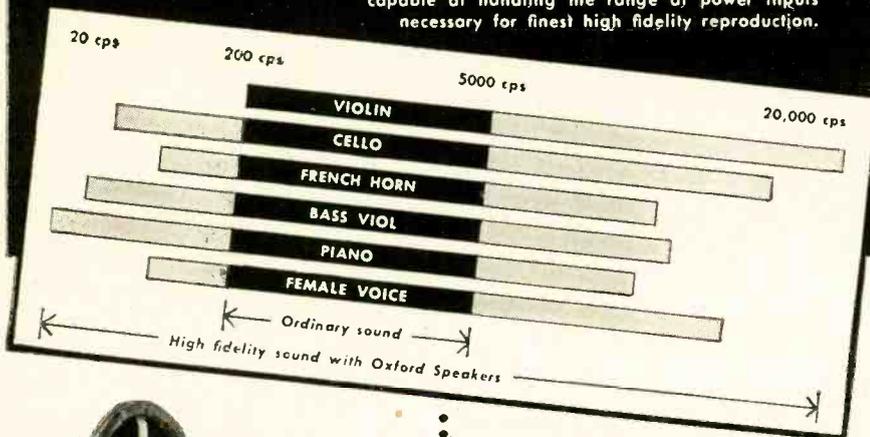Engineered for finest performance at minimum cost, OXFORD HI-FI SPEAKERS have a flat response throughout the audible range and are capable of handling the range of power inputs necessary for finest high fidelity reproduction.




COAXIAL SPEAKERS

- C12J408 12"
Frequency response:
40-15,000 cps.
- C15L608 15"
Frequency response:
30-15,000 cps.




EXTENDED RANGE SPEAKERS

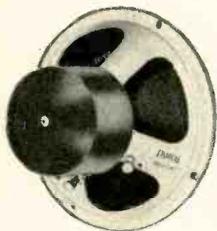- HF8JB 8"
- HF10JB 10"
- HF12JB 12"
- HF12LN 12"
- HF15LN 15"
- Frequency responses:
70-10,000 cps.



FULL RANGE SPEAKERS

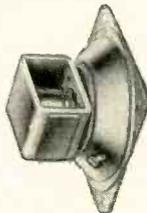- F8J408 8"
Frequency response:
50-13,000 cps.
- F12J408 12"
Frequency response:
50-12,000 cps.
- F12L608 12"
Frequency response:
40-10,000 cps.



TWEETERS

- T3C208 3"
Frequency response:
1,800 to 15,000 cps.
- T5C208 5"
Frequency response:
1,100 to 15,000 cps.

Finer HIGH FIDELITY SPEAKERS engineered for best reproduction ... designed to sell.

Illustrated literature is available

OXFORD Components, Inc.

Subsidiary of Oxford Electric Corp.

556 West Monroe Street • Chicago 6, Illinois

Export: Roburn Agencies, New York City In Canada: Atlas Radio Corp., Ltd., Toronto



LOWEST PRICES ANYWHERE
Picture Tubes—Transmitter Tubes—Radio & TV Parts
WRITE FOR STANLEY'S NEW FREE CATALOG
DUMONT and RCA inc.
BRAND NEW TV PICTURE TUBES
UNCONDITIONALLY GUARANTEED FOR ONE YEAR
No dud required


| | |
|----------------------|----------------------|
| 10" Tube.....\$10.95 | 17" Tube.....\$17.95 |
| 12" Tube.....\$12.95 | 19" Tube.....\$20.95 |
| 14" Tube.....\$14.95 | 20" Tube.....\$20.95 |
| 16" Tube.....\$16.95 | 21" Tube.....\$22.95 |

Add \$4.00 to above prices for atomized tubes
TERMS: 25% deposit on all COD's. Picture tubes F.O.B. Paterson, N. J. via Railway Express.

STANLEY ELECTRONICS CORP. 840 MAIN ST. PATERSON, N. J.

CONVERT TO COLOR TV
COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any-size black-and-white TV, direct view or projection, to receive compatible color TV. **COLORDAPTOR** is simply attached to TV set, does not affect normal operation and can be built from parts experimenters have on hand.
Complete specifications including theory of operation, complete simplified construction plans, schematic and sample color filters **\$1.95**
Essential parts kit containing all special parts—coils, delay line, crystal, color filters—
Up to 16" **\$19.95** 17" and larger—**\$20.95**
sets—
All other **COLORDAPTOR** parts, kits, motors, etc. available. Write for information and prices.
COLORDAPTOR, 3471 Ramona, Palo Alto, Calif.

NEW TUBES & SEMICONDUCTORS (Contd.)

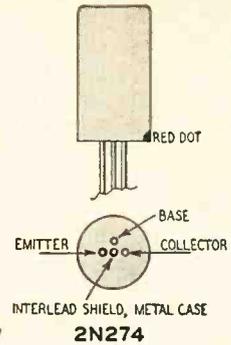


hermetically sealed and has flexible leads.

Maximum ratings for class-A rf amplifier service are:

| | |
|--|-------|
| V_{CB} | —35 |
| V_{EB} | —0.05 |
| I_C (ma) | —10 |
| I_E (ma) | 10 |
| Collector dissipation for ambient temperatures up to 71°C (mw) | 35 |

S6X4

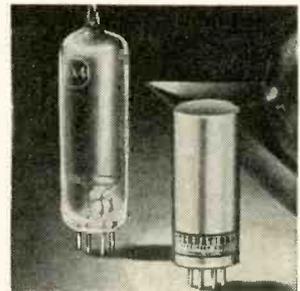
A tube-base-mounted silicon replacement for the 6X4. Directly interchangeable with the 6X4, it has a maximum dc output of 85 ma, an input voltage



of 400 rms and a maximum peak current of 225 ma. Maximum peak inverse voltage is 1250. Voltage drop at 70 ma is 6 volts. It is made by International Rectifier.

IDN5

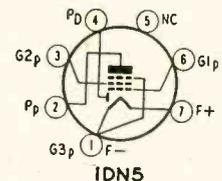This diode-remote-cutoff-pentode is a seven-pin miniature type with a 1.4-volt .05-amp coated filament. Designed for use in battery-operated portables, it performs the combined functions of AM detection and af amplification. It is manufactured by RCA.




Typical operation, pentode unit, as a class-A1 amplifier:

| | |
|-----------------------------|------|
| V_p | 67.5 |
| V_{g2} | 67.5 |
| V_{g1} | 0 |
| R_p (megohms) | 0.6 |
| g_m (μ mhos) | 630 |
| I_p (ma) | 2.1 |
| I_{g2} (ma) | 0.55 |
| Maximum rating, diode unit: | |
| I_p (ma) | 0.25 |

Rectifier stacks

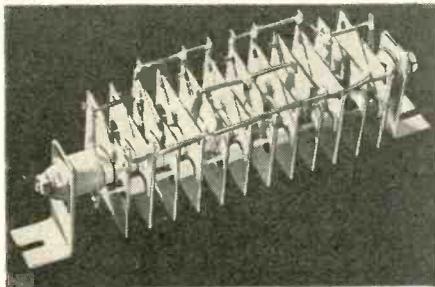
A new line of 170°C silicon rectifier stacks has been announced by G-E. More than 200 standard models, completely wired for various uses, are in-



cluded. A typical example is the 12-fin stack shown in the photo. This model is rated at 280 volts rms, input and 250 volts dc, output. Current rating at 25°C is 9 amps; at 170°C, 3 amps.

6BA8-A

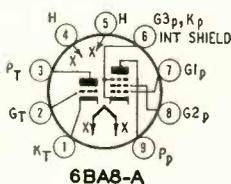A general-purpose multiunit tube of the nine-pin miniature type containing a medium-mu triode and sharp-cutoff pentode. The pentode unit is especially useful as a video amplifier tube. It



may also be used as a reactance or age amplifier tube. The triode unit can be used in low-frequency oscillator and phase-splitter circuits. Made by RCA, the 6BA8-A is designed with a 6.3-volt 600-ma heater having a controlled warmup time.

Its characteristics as a class-A1 amplifier are:

| | Triode Unit | Pentode Unit |
|------------------------------|-------------|--------------|
| V_p | 200 | 200 |
| V_{g2} | | 150 |
| V_{g1} | -8 | 0 |
| Cathode-bias resistor (ohms) | | 180 |
| μ | 18 | |
| R_p (k ohms) | 6.7 | 400 |
| g_m (μ mhos) | 2,700 | 9,000 |
| I_p (ma) | 8 | 13 |
| I_{g2} (ma) | | 3.5 |

Other types

A miniature twin-triode with separate cathodes has been released by Amperex. Type 7062 is designed as a plug-in replacement for the 5965.

A 6198-A Vidicon has been announced by RCA. It is a small camera tube intended primarily for industrial television applications.

A high-power high-vacuum diode has been introduced by IT&T. Designated the F-7030, it has a maximum peak inverse voltage rating of 25 kv.

Two uhf beam-power tubes with ceramic metal seals have been announced by RCA. They are the 6816 and 6884. END

YOU

NEED THIS...

FREE

GIANT ALL NEW 1958

BA CATALOG

A COMPLETE BUYING GUIDE FOR EVERYTHING IN

RADIO • TV

ELECTRONICS

BA 1958

ANNUAL CATALOG 581

SINCE 1927

172

KING-SIZED PAGES

EVERYTHING IN RADIO TV AND ELECTRONICS

100'S OF NEW ITEMS LISTED HERE FOR 1st TIME

21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

Guarantee

We guarantee everything in our Catalog to be of the quality and value represented... no compensation... to perform exactly to the illustration and description... to perform in the manner and give the service intended for such purposes.

RUSH COUPON TODAY!

INDEX PAGE 175 PHONE BANK

BURSTEIN-APPLEBEE

BURSTEIN-APPLEBEE CO. Dept. M,
1012-14 McGee St., Kansas City 6, Mo.

Send Free 1958 B-A Catalog No. 581.

NAME _____

ADDRESS _____

CITY _____ STATE _____

ENGINEERING

B. S. DEGREE IN 27 MONTHS

Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, playing field. Earn part of your expenses in Fort Wayne. G.I. approved. Enter Dec., March, June, Sept. Catalog.

INDIANA TECHNICAL COLLEGE

1710 E. Washington Blvd., Fort Wayne 2, Indiana

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

Electronics Chemical Aeronautical
 Civil Mechanical Electrical

B.S. DEGREE IN 36 MO. in: Math. Chem. Physics

Name _____

Address _____

2 WAY PORTABLE RADIO SET

Sends—Receives up to 10 miles as shown

or hundreds of miles with outside antenna! 80 and 40 meter amateur radio bands (novice) also Aircraft and overseas broadcasts (3 to 8 mc.) POWERED WITH SELF-CONTAINED PORTABLE RADIO BATTERIES. NO AC PLUG-INS NEEDED! Take it with you everywhere you go—Keep in contact with home friends. Has 5 watt crystal controlled transmitter—Sensitive Regenerative Receiver. Send receive switch. Wt. only 3 lbs. Size, only 6"x4"x4". TESTED—PROVEN—SIMPLIFIED—PRACTICAL—Full information given on quick easy to get license.


SEND ONLY \$3.00 (bill. ck. mo)

man \$11.95 COD postage on arrival and pay post- for postpaid delivery. Complete kit includes all parts, tube, coils, plastoid cabinet, easy instructions. (Set of batteries—\$2.95; crystal \$1.25). COMPLETELY WIRED AND TESTED POSTPAID \$19.95. A regular \$49.95 value—Order now before price goes up. GUARANTEED—AVAILABLE ONLY FROM: WESTERN RADIO Dept. BNR-10 KEARNEY, NEBR.

TeleMatic


CUSTOM HIGH FIDELITY KITS

AM/FM TUNER

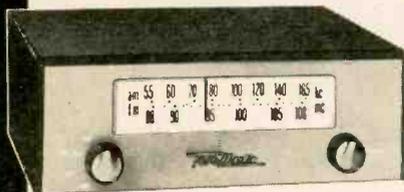

2 uv for 20 DB quieting, AFC plus Deafat, Full Frequency Response, 300 KC bandwidth.
 Model KC-400 Less Cage \$34.95 (FED. EX. TAX INC.)
 Wired and Tested 59.95


20-WATT INTEGRATED AMPLIFIER

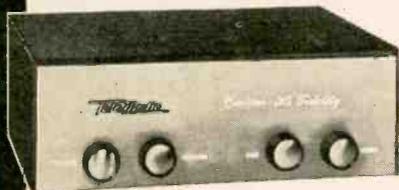

Power Response CONSTANT at 20 Watts, 1 ± DB Full Frequency Response, Infinite Equalization Bass Treble Controls; 3 Hi, 1 Low inputs.
 Model KC-401 Less Cage \$46.00
 Wired and Tested 64.95

Exclusive! STEREOPHONIC KITS

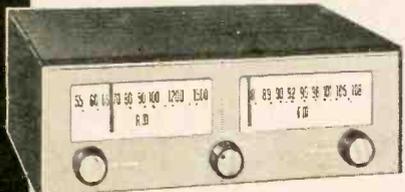AM/FM STEREOPHONIC TUNER WITH WIRED FM FRONT END



NEW DIMENSIONS IN SOUND—Each section used individually or together—0.9 uv for 20 DB quieting, 330 kc Bandwidth 3-gang variable AM tuning, 15 uv per meter loop sensitivity.
 Model KB-402 Less Cage \$69.95 (FED. EX. TAX INC.)
 Wired and Tested 99.50

40-WATT STEREOPHONIC AMPLIFIER



NEWEST DEVELOPMENT IN STEREOPHONIC SOUND FOR THREE DIMENSIONAL LIFE-LIKE REALISM! Twin 20-Watt Channels—Each with FULL PRE-AMP sections and Master Volume Control.
 Model KB-403 Less Cage \$ 82.50
 Wired and Tested 109.50

For full details, see your local dealer or write

TELEMATIC INDUSTRIES, INC.
 16 HOWARD AVENUE, BROOKLYN 21, N. Y.

Patents




CALIBRATION CIRCUIT FOR PEAK-READING VOLTMETER

Patent No. 2,765,442

Mason A. Logan, New Providence, N. J. (Assigned to Bell Telephone Labs, Inc., New York, N. Y.)

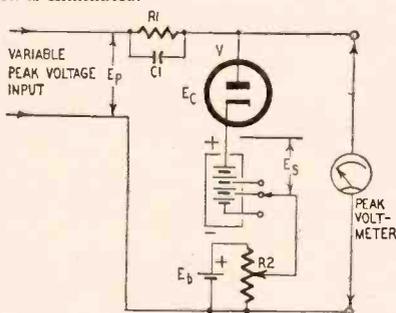This circuit is a convenient setup for calibrating a peak-reading voltmeter. The voltage source is one that has the same general waveform as that which the meter is to measure. Network R1-C1 (see diagram) has a time constant equal to that of the meter. Therefore, waveform distortion is eliminated.



To prepare the calibration circuit, E_b is first adjusted to cancel diode contact potential E_c .

Then E_s , the standard voltage, is set to the desired value. Now E_p is increased and, when its peak voltage is equal to E_s , the meter deflection will cease to rise. At this point V begins to conduct and shunts current out of the meter. If, as presumed, E_s is known so is the peak of E_p and the voltmeter may be calibrated.

Note that the voltage across the meter is lower than E_s (or the peak of E_p) due to the voltage-dividing effect of R_1, C_1 , so this network must be taken into account.

ALERTING DEVICE

Patent No. 2,744,194

Martin Auerbach, Flushing, N. Y.

This is an adapter for a broadcast radio that can be tuned to any nearby station. Radio and adapter are energized at all times, but during standby periods power consumption is very low. In case of an air raid or other emergency, the broadcast station transmits a predetermined steady tone which operates the adapter, switching the radio to full gain and sounding an alarm.

The adapter includes a pair of plugs for insertion into the rectifier and power tube sockets of the radio. These tubes (see diagram) V_1 and V_2 , are removed from the radio and plugged into corresponding sockets of the adapter. No soldering is necessary. The adapter also contains a line outlet for a warning light or audible alarm and an adjustment knob.

The heart of the adapter is a bimetallic strip which is heated by the alerting signal. This strip is spring-loaded so even slight bending causes it to trigger the multi-pole switch. This switch (S_1 to S_4) is shown in its standby position.

With S_1 as shown, series resistor R_1 reduces heater current to the radio. This saves power during standby when full radio amplification is not necessary. S_2 feeds the output of V_2 back to its grid through $L-C_1$. This degenerative network is tuned to the warning tone, so this is the only frequency that does not incur degeneration. It is the only frequency that is fully amplified during this time. The speaker is shorted by S_4 which connects CH and C_2 to pass the steady



COMPUTERS, ROBOTS AUTOMATION

Finally out! Plans for ALLSOLVER! Inexpensive computer can be built from standard parts. Instructions and worked-out problems. Over 30 pages for \$3.

200-page manual on robot construction and plans, only \$5.

RELAYS, up-to-date manual. Explains types, uses, how to use logic etc. Contains projects for building special types. \$2.75

SPECIAL — Course in Mathematical Logic, includes Boolean Algebra, Binary counting, games. Only \$12.50 as an introduction. This includes 350-page textbook and personal instruction.

Courses in computers for beginners, start at \$12.50. No experience over simple algebra required.

ELECTRONICS, over 1000 pages of text and material. Time payments. Investigate today. Includes Radio, Radar, Computers, Servosystems, Television, Test equipment and more.

For FREE information send to:

ELECTRONIC BRAIN ENTERPRISES, INC.
 1015 Atkin Ave., Salt Lake City 6, Utah

Name.....


Address.....

BETTER HI-FI BY



ELECTRONICS COMPONENTS-ACCESSORIES

AMPLIFIERS

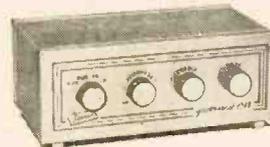

PRICED AS LOW AS \$39.50
"QUADNAURAL" SPEAKER SYSTEMS
 Trade Mark Registered


- RECORD COMPENSATORS
- RUMBLE FILTERS
- HI-PASS FILTERS
- LOW-PASS FILTERS
- SPEAKER SELECTORS
- TRI-SET COUPLERS
- MOLDED-ON CONNECTORS
- DUO-JACK ADAPTERS
- FILTER-TENNA

SOLD BY BETTER DISTRIBUTORS EVERYWHERE!

Send for Catalog Sheets on all Dynamic Products

"UNMISTAKABLY THE FINEST"

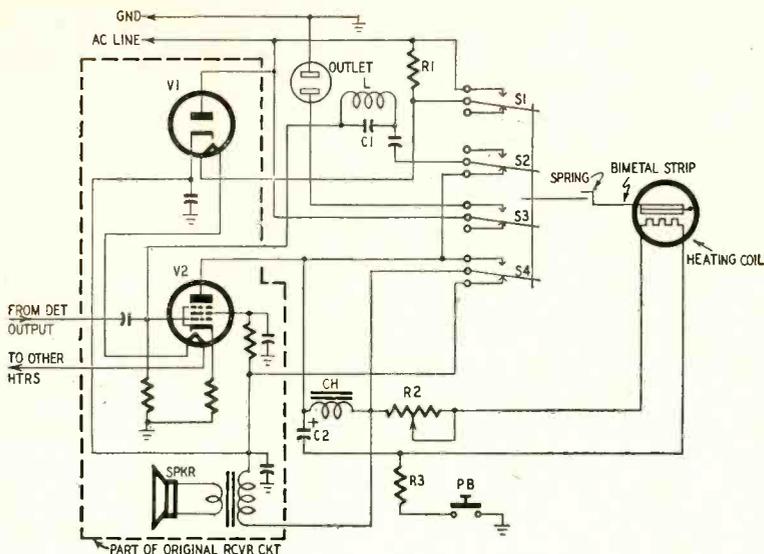Manufactured By
DYNAMIC ELECTRONICS-NEW YORK, INC.
 Forest Hills, Long Island, N. Y.



tone into the coil which heats the bimetal strip, triggering the alarm.

On receipt of an alert signal, S1 shorts R1, and the radio is set for full gain. S3 energizes the ac outlet to set off any desired visual or audible alarm. S4 shorts out CH and places the loud speaker across V2.

This adapter appears fool proof unless the

IONIC SPEAKER

Patent No. 2,793,324

Michael N. Halus, Palo Alto, and Stanley W. Holcomb, Mountain View, Calif. (May be used by the U. S. Government without payment of royalties.)


Corona is something to be avoided in TV sets, but here it is the basis of operation. The ionic speaker is an efficient device for converting audio currents into sound. It does this by generating an intense stream of ions (or corona) which

power should be interrupted. PB is provided to periodically check the circuit. When momentarily depressed, dc from the power tube flows into the heating coil and R3. If the alert device is operating properly, the bimetal strip should be triggered in about 30 seconds. R2 is used to adjust input to the heating coil. A knob on the front panel resets the device.

cause the air to expand and contract in accordance with the audio currents. Having no mechanical parts, the ionophone is efficient and without resonant frequencies.

This invention (see Fig. 1) is an improvement

Can you think faster than this Machine?

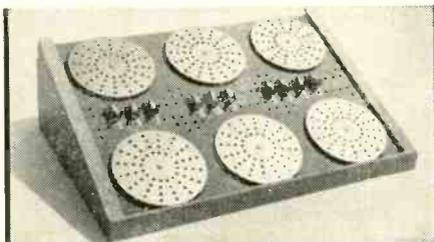

Control Panel of GENIAC set up to do a problem in check valve research.

Be careful before you answer. GENIAC the first electrical brain construction kit is equipped to play tic-tac-toe, cipher and encipher codes, convert from binary to decimal, reason (in syllogisms) as well as add, subtract, multiply and divide. Specific problems in a variety of fields—actuarial, policy claim settlement, physics, etc., can be set up and solved with the components. Connections are solderless and are completely explained with templates in the manual. This covers 33 circuits and shows how new ones can be designed.

You will find building and using GENIAC a wonderful experience; one kit user wrote us: "This kit has opened up a new world of thinking for me." You actually see how computing, problem solving, and game play (Tic-tac-toe, num. etc.) can be analyzed with Boolean Algebra and the algebraic solutions transformed directly into circuit diagrams. You create from over 400 specially designed and manufactured components a machine that solves problems faster than you can express them.

Schools and colleges, teachers of science or math, engineering, philosophy or psychology will find these excellent demonstrators of circuitry solutions in symbolic logic, theory of numbers, cybernetics, and automation.

Note: Teachers take advantage of our 10% discount to educational institutions and for group purchases. SEND for your GENIAC kit now. Only \$19.95 with over four hundred components and parts, fully illustrated manual and wiring diagrams. We guarantee that if you do not want to keep GENIAC after one week you can return it for full refund plus shipping costs.

MAIL THIS COUPON —
SCIENCE KITS, Dept. RE107A, Oliver Garfield Co.
126 Lexington Ave., N.Y. 16, N.Y.

Please send me:
1 GENIAC Electric Brain Construction KIT and Manual.
\$19.95 (East of Mississippi)
\$20.95 (Elsewhere in United States)
\$21.95 (Outside the United States)

Returnable in seven days for full refund if not satisfied.
I enclose \$..... in full payment.
My name and address are attached.

■ "High fidelity" might be defined as the precision reproduction of music by a system of specialist-built components. Among these components—amplifiers, radio tuners, record players—nowhere is precision workmanship more important than it is in the loud-speaker.

■ Consider the function of a loud-speaker. It must vibrate at exactly the same frequency as the electrical signal fed to it by the amplifier. This frequency may vary from 30 to as many as 15,000 times a second! Consider that now we are not dealing with electrons of negligible mass, neither are we working with a tiny phonograph stylus; in a loudspeaker we must control the actual physical movement of a considerable mass of metal and fiber. A moment's reflection will show that in this component precision workmanship is all important.

■ JBL Signature Speakers made by James B. Lansing Sound, Inc., are made with that degree of precision usually associated with scientific instruments or navigational chronometers. Perhaps they should not be called "loud-speakers" at all, but should be given the more technically correct appellation: precision transducers. No matter how difficult the manufacturing operation, if a refinement will result in better sound, it is built into JBL Signature Loudspeakers.

The place to see and hear JBL Signature units is in the component demonstration room of the authorized JBL Signature High Fidelity Sound Specialist in your community.

For his name and address, write to:
James B. Lansing Sound, Inc.
3249 Casitas Ave. • Los Angeles 39, Calif.



Only JBL Signature speakers are made with 4" voice coils... such as the 15" JBL D130—Extended Range unit.




Only the JBL Signature D123 is made with a frame so shallow that it may be mounted flush with wall surface.




Only JBL Signature High Frequency components are made with acoustical lenses for smooth treble distribution.



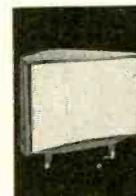The ring radiator in the 075 High Frequency unit is an exclusive JBL Signature development.



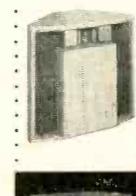Most handsome and versatile speaker enclosure made—the JBL Signature Harlan.



Universally acclaimed first choice for high fidelity—"Dream Set"—the JBL Signature Hartfield.



Most popular enclosure—the JBL Signature Model C34 back-loaded folded horn.



Speakers of the highest precision bear this trademark. "JBL" means James B. Lansing Sound, Inc.

Dave Rice's
OFFICIAL ORDER BOOK
for every TV-Radio service call



Triplicate forms serve as order form, invoice and office record with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10.

... and for customer's prices on every replacement part, Dave Rice's

OFFICIAL PRICING DIGEST

listing over 60,000 items. \$2.50

In stock at your distributor, or write

ELECTRONIC PUBLISHING CO. INC.
180 North Wacker Drive Chicago 6, Illinois



**THE REACH IS RIGHT AND TIGHT
with KRAEUTER LONG NOSE PLIERS**



#1781-7"

You can depend on reachability and cutting power with Kraeuter's #1781 Long Chain Nose Pliers. And your reach will be tight and sure for those hard-to-get-at jobs with the extra long milled jaws of these pliers.

Buy the right line—Sell the right line. It's the Kraeuter line for electronic and electrical work. Kraeuter tools are unreservedly guaranteed.

Send for catalog #25 illustrating complete Kraeuter line.

BUY THE FINEST
BUY KRAEUTER
BUY AMERICAN



AS MODERN AS TOMORROW

kraeuter & co., inc

FOR 100 YEARS THE FINEST IN HAND TOOLS 1860-1960 • NEWARK, N. J.

**DON'T REMOVE THAT
CRT TUBE!**

Snap it back to normal brilliance with new improved Kinecure. INSTANTLY and PERMANENTLY corrects 33 different CRT defects. Saves time, money, and irritation for both servicemen and customers. Thousands of TV servicemen now use new, improved Kinecure. Now time tested and job proven on over 50,000 sets. There is just nothing else like patented Kinecure. It looks different — operates different — works like a charm! Ask your Jobber. Or write for free full information.

CIRCUIT MANUFACTURING CO., INC.
923 Shadeland Ave., Drexel Hill, Pa.



PATENTS (Continued)

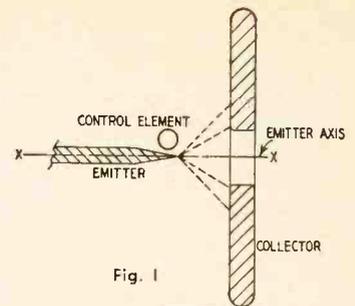


Fig. 1

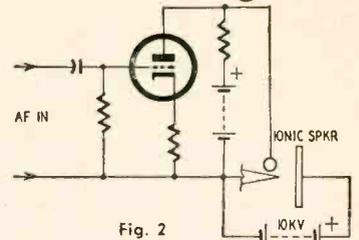


Fig. 2

over previous types. There are three elements: an emitter, a metallic rod with pointed end; collector, a circular metal ring with opening at its center; a control element wire (whose cross-section is shown as a small circle). A high voltage is impressed between emitter and collector to set up a corona discharge. The ion stream must not be too intense or an arc will occur.


Fig. 2 shows how to connect the ionic speaker to an audio output tube.

ANTI-SHOPLIFTER DEVICE

Patent No. 2,744,060

Thomas F. Thompson, Eugene, Ore. (Assigned to Richard B. Thompson, Dale Belford and Oliver D. Olson)

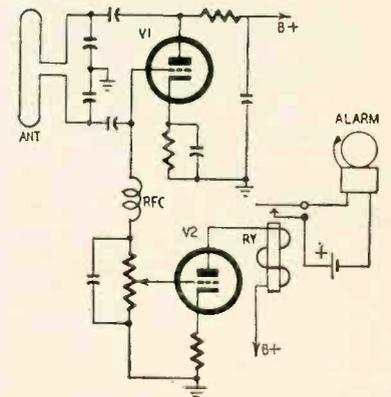This invention protects against theft of merchandise from department stores and similar shops. A tiny resonant circuit is concealed within the price tag of each article. If the article is stolen and carried through an rf field generated for the purpose, it affects an oscillating circuit which sets off an alarm.




The diagram shows a grid-dip oscillator (V1) which generates a field around its antenna. The latter may be a loop placed near the counter of the store cashier. Each shopper must pass through this field. If he or she is carrying stolen merchandise through the field, its resonant circuit reacts on the dip oscillator. There is a reduction of grid current to V1, lowering the bias on V2. The latter tube passes more current, energizing the relay and setting off an alarm.

The oscillator frequency may be as high as 5,000 mc. At such frequencies the resonant circuit may be a conductor about 1 inch long. END


RAINEX VS RADAR?

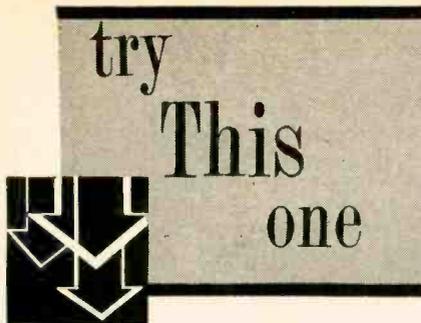Vatican City Latinists bemoan that Latin is continuously being pushed to the rear. They claim Latin is by no means dead and their scholars keep adding modern terms. Sample: *Radio-electricum instrumentum exploratorium* (radar).



TRANSISTOR RECTIFIER

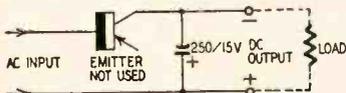Everyone knows that a junction transistor is made up of two rectifiers, but few have tried it for rectification purposes. Actually, the base-collector junction is very efficient when used as an ac rectifier.



The circuit is shown in the diagram. The transistor is any high-power p-n-p transistor, such as a 2N256 or 2N301. Load currents and voltages are shown below. In these tests the transistor junction was compared with that of a low-voltage (25-volt) selenium rectifier.

| Ac volts | Load (ohms) | Load Current (ma) Transistor | Load Current (ma) Selenium |
|----------|-------------|------------------------------|----------------------------|
| 12 | 12.5 | 600 | 500 |
| 10 | 8. | 600 | 520 |
| 6 | 8. | 350 | 280 |

If you find yourself without a high-current rectifier for a sudden experiment, try a transistor. Even a damaged unit may still be suitable as a rectifier. For example, it is quite possible that a dead short may occur between emitter and base, without affecting the other junction. Under this condition, it is still possible to use the collector-base junction.—I. Queen

CUT CONTROL SHAFTS

New subminiature controls used in transistor equipment have 1/8-inch-diameter shafts. These shafts can be cut to length in less than a second using an AMP type screw-cutting and terminal tool.

Insert the shaft into the 8-32 or 10-32 screw-cutting opening and squeeze. The shaft will cut off clean as a whistle without any burrs or distortion.—Edwin Bohr

PAINTING ETCHED PANELS

Repainting electronic equipment with control markings etched on the metal panel is quite a problem. Many shun this type of work because of the time spent in "picking" the recessed letterings, which are usually numerous. Here is a simplified method of repainting this type of panel with a minimum of effort and with simple and inexpensive equipment.

To start with, you will need a paint sprayer or a hand type insecticide sprayer with a good pump. This is imperative if you want a fine spray finish. You will also need a stiff brush, a few sticks of writing chalk, paint thinner

LOOK! \$10 WORTH OF RADIO PARTS WITH ANY \$10 ORDER FREE PLUS

SURPRISE BONUS GIFT INCLUDED WITH ANY SIZE ORDER!

ANY ORDER ENROLLS YOU IN OUR CREDIT-BONUS PLAN TO EARN FREE KITS . . . START TODAY

FREE! SEND NAME AND ADDRESS FOR OUR GIANT FALL BARGAIN FLYER!

FAMOUS KIT KING DOLLARBUYS! SOLD AND GUARANTEED ONLY BY LEKTRON

- 2 SUB-MINI I.F. TRANSFORMERS. 1 1/2" sq. double-ended tuned ferrite cores. 30 terms. Transistor printed circuit. \$1
- 2 TRANSISTOR TRANSFORMERS. UTC "bomber" type. Interstage, 1x8/4x3/4". Imp. ratios unknown. Color-coded leads. Reg. \$10.
- "Postage-stamp" CRYSTAL MIKE. 3/4" sq. Crisp, clear to 8,000 cps.
- SUB-MINI PNP TRANSISTOR. 1/2 pencil eraser size, used in "name" portables. W/spec sheets. \$1 \$5 value!
- 50 TUBULAR CONDENSERS—REG. \$12. .0002 to 1 mf.; to 2000 V. Oil. incl. Wt. 2 lbs.
- 40 MOLDED CONDENSERS—REG. \$8. Black beauties, porcelain, etc. Oil. too. To 1 mf.; to 100V. Wt. 1 lb.
- 8 TRANSISTOR SOCKETS—REG. \$3. Mica-filled; for sub-mini portables, too.
- 60 RESISTORS—REG. \$18. Inl. 1/2 to 2 W. 10 ohms to 10 megs. 30 values. Wt. 1/2 lb.
- 30 TUBE SOCKETS—REG. \$8. Transistor, printed circuit, 4-14 prong, mini & standard types. Some mica-filled. Wt. \$1 1 lb.
- 60 TRANSFORMERS, COILS—REG. \$15. 1F, RF, ant., slug-tuned coils, chokes. 25 types. Wt. \$1 3 lbs.
- 40 TRANSISTOR RESISTORS—REG. \$6. Only 1/4" long. 20 values: 15 ohms to 10 megs. Color-coded. \$1
- 3 LBS. HARDWARE—REG. \$8. Approx. 2000 pcs. Assorted screws, brackets etc.
- 50 OUTPUT TRANSFORMERS—REG. \$6.50. 30L4, 35L6, 6V6, 30B4 to 3-4 ohm v.c. \$1 Wt. 1 lb.
- 175-FT. HOOKUP WIRE—REG. \$3.75. In 28-ft. rolls. Ass'd. colors, stranding, insulation. \$1 #18 to #24 Wt. 2 lbs.
- 53 VALUE! Plastic handle, 3/10, 7/32 1/4, 5/16, 11/32, 3/8, 7/16, steel socket wrenches in plastic case. Wt. 1 lb.
- 15-PC. TWIST DRILL SET—REG. \$4. 1/16 thru 3/4" by 8/ths in graduated plastic holders.
- 60 TERMINAL STRIPS, POSTS. Wide variety solder lug, binding. Wt. 1 lb.
- SIX DIODES—REG. \$15. Ass'd. sizes. crystal & silicon.
- WORLD'S SMALLEST RADIO KIT—REG. \$3.50. 2 1/2x1 3/4x3/4". W/ permeability tuner, diode all parts, instruce. \$1
- 40 PRECISION RESISTORS—REG. \$18. Carbon film, Wilkors, etc. 1/2 & 1 W. asstd. Wt. 1/2 lb.
- 30 DISC CONDENSERS—REG. \$15. Transistor & printed circuit types.
- 100 RADIO PARTS—REG. VALUE OVER \$15! Surprise asstmt. \$1 Wt. 2 lbs.
- 50 PLUGS & RECEPTACLES. Audio, power, chassis, panel & spkr. types. Wt. 2 lbs.
- R/C CONTROL SCOOP! Chassis incl. 3000-ohm mini control rel. 115 to 60-3-1.5A fl. ximr., resistors, cond. pot., sock. ets. Wt. 2 lbs.
- 15 VOLUME CONTROLS—REG. \$10. Singles, duals to 1 meg. Wt. \$1 1 lb.
- 10 "POLY" BOXES—REG. \$2.50. Ass'd. sizes. Clear plastic, hinged, w/ snap locks.
- 40 ELECTROLYTICS—REG. \$14. Ass'd. can. Tubular types to 300 mf. Wt. 3 lbs.
- 125 RESISTORS—REG. \$15. 1/2 1 W. 40 values; 50 ohms to 10 meg. \$2.50.
- 60 MICA CONDENSERS—REG. \$5. 30 values: 1000V. Silver, 50¢ \$1 incl. Wt. 1 lb.
- 20 PRINTED CIRCUITS—REG. \$10. Ass'd. top makes, for transistor, radio, hobby circuits.
- 60 STANDARD KNOBS—REG. \$9. Bakelite & plastic, ass'd. colors. Set. asstmt. types, too. Wt. 2 lbs.
- 10 I.F. TRANSFORMERS—REG. \$15. Metal can, asstd. (reqs. for radio, TV, hobby uses. Wt. \$1 3 lbs.
- 30 POWER RESISTORS—REG. \$8. W.V. cand. ohm, sand-coated, vitreous. 13 values: 5 to 50 W. 35 to 11000 ohms. Wt. \$1 2 lbs.
- 30 POPULAR BULBS—REG. \$3. Ass'd. min. screw & bayonet to 8V. Wt. 1/2 lb.
- EMERSON TUNER—REG. \$5. Hi-Q, permeability-tuned ANT & OSC coils w/ padders on 2x1/4 plate; variable tuning \$1 mech. 500 to 1800 kc.
- 2 SUB-MINI SOLENOIDS—REG. \$5. 1x 5/8x3/8". Change elec. energy to mechanical. 12 VDC @ 200 ma. actuates \$1 plungers. Wt. 2 oz.
- 15 ROTARY SWITCHES—REG. \$10. Ceramic & bakelite; 1, 2, 3-gangs; \$1 std. shafts. Wt. 3 lbs.
- 100 CERAMIC CONDENSERS—REG. \$15. Ass'd. types, 30 values. \$1 color-coded. Discs, too.
- 5 FERRI LOOPSTICK CORES—REG. \$1. Ass'd. flat & tubular, 5 to 7" long. Wt. 1 1/2 lbs.
- 60 PORCELAINIZED RESISTORS—REG. \$12. Carbon film, precision-type. 25 values: 1/2 to 1 W. 50 ohms to 1 meg. Wt. \$1 1 lb.
- SURPRISE KITSCOOP! Reg. \$15 value! Wide asstmt. resistors, condensers, term. strips. Ap \$1 prox. \$50 pcs.
- 40 HI-Q CONDENSERS—REG. \$15. Metal can, asstd. tubular cased. Ass'd. pop. values. Reg. \$1 8¢.

▲ \$1 each ▲ \$1 each ▲ \$1 each ▲ \$1 each ▲

ROCK-BOTTOM BARGAINS!

- TRANSISTOR PORTABLE RADIO KIT with speaker**
No experience necessary! Famous make, with powerful Hi-Q ferrite antenna, diode det., 2 transistor ampl. stages, 4" spkr. 7 1/2 x 5 1/2" styrene case. For broadcast bands. Instructions, diagrams, pictorials. all parts. \$12.95
9V battery, 69¢ extra
- CRYSTAL PHONE**
High-impedance, hearing-aid type. Use as mike, too. \$1.39
- Sun-Powered Transistor Radio Kit BATTERY**—the only such kit usable day & night! NEVER WEARS OUT! No bulky ant. needed. All parts sub-mini transistor, 3 x 2 x 1 1/2" case, instructions. (Use with our Super-Powered Phone for best results.) Ship wt. 1 lb. \$5.98
- POCKET MULTI-TESTER**
\$13 value! 3 1/2 x 2 x 1 1/2" bakelite case. 1000 ohms/V. Zero adj. 0.15/150/1000 AC & DC V; 0/150 ma; 0/100,000 ohms. W/ test leads, in orig. pack. \$6.99
- SUPER-SENSITIVE RELAY**—Reg. \$15
100 to 500 micro-amps dr. 1/2 inch VDC SPDT con. Stakes nifty transistor amplified photo-electric relay (plans incl.). For models, TV commercial handsets. \$2.98
- 3-TUBE AC DC AMPLIFIER**
Reg. \$5. Fully wired; sep. vol., tone controls. Lowest price ever! TUBES. \$1.91 EXTRA. \$2.99
- MINIATURE TRANSISTOR TRANSFORMER**
Open frame; 20K to 1K ohms imp. Only 23/32 x 1 1/2" w/ color-coded leads. Finest steel. \$1.19
- "SLIM JIM" CRYSTAL MIKE**
\$14.85 value! 60 to 10,000 cps. Sleek, lightweight aluminum; 4 3/8 x 1 1/2" dia. ON-OFF sw. \$4.88
- 12" HI-FI PM SPEAKER**
50 to 10,000 cps, Ivy-Africa magnet; 2.2 ohm v.c. Wt. \$3.99 3 lbs.
- SUPER-POWERED PHONE**
Hearing-aid type; dynamic. 8,000 ohms. W/ cord & mini plug. Makes weak sigs loud, clear. \$3.33
- SUPER SOLAR BATTERY** REG. \$10
Generates greater energy than (famed B2M, 2 1/2 x 1 3/4 x 1 1/2" plug-in type; in handy case. \$2.88
- TRANSISTOR ADD-A-STATE**
Makes any crystal set into transistor radio, easily, quickly. All parts, instructions. \$1.99
- AMAZING "PILLOW" SPEAKER**
"Silent-sound" by bone conduction to inner ear. 2-4 ohm v.c. 100% personal listening! \$2.88 W/cord.
- 1/3 H.P. DELCO WORKSHOP MOTOR**
Reg. \$41.50; 1750 RPM; 1 1/2" dia. shaft, ball-bearing, 8' cord set. w/ switch. \$14.88 Wt. 23 lbs.

NO QUANTITY LIMIT ON BONUS OFFER FEATURED IN THIS AD. \$20 PURCHASE EARNS \$20 WORTH OF PARTS, TWO FREE \$1 KITS. ALL PURCHASES APPLY TOWARD BONUS!

HOW TO ORDER

Check items wanted. Return entire ad w/check or M.O. including sufficient postage; excess returned. C.O.D. orders, 25% down. Rated, net 30 days. Print name, address, amount money enclosed, in margin. (Canada postage; 45¢ 1st lb., 28¢ ea. addl. lb.)

EXPORT ORDERS INVITED! 131 EVERETT AVE. CHELSEA 50, MASS.

LEKTRON

TELEVISION TUNER SERVICE UHF & VHF

FOR THE EXACT TV TUNER REPLACEMENT USE A CASTLE REBUILT UNIT

EVERY REBUILT TUNER CARRIES FULL 90 DAYS WARRANTY

Aligned to Original Standards Under Laboratory Conditions Oscillator Tracking Assured by Crystal Standards on All Channels

SAME DAY SERVICE Exchange Tuner shipped same day defective unit received

\$9.95 Dealer Net ANY TUNER (VHF or UHF) Including All Worn Parts (except tubes, where needed)


(Any Tuner, for which a rebuilt unit is out of stock, over 8" & returned within 48 hours.)

Just forward defective Tuner prepaid. Complete with good tubes and all damaged parts; quote make and model.

1723 W. LUNT AVE., CHICAGO 26, ILL., U.S.A. Ambassador 2-7505

152 MAIN ST., TORONTO 13, ONT., CANADA OXford 4-5637

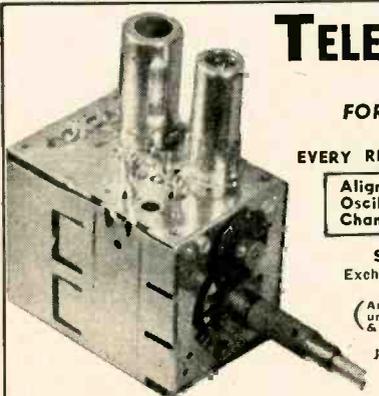Suppliers of rebuilt TV Tuners to leading manufacturers, technicians & service dealers, coast to coast. TERMS: C.O.D. f.o.b. CHICAGO or TORONTO



Castle TV Tuner Service

FOR TOP-O'-CHASSIS SERVICING

locates defective stage in
less than 5 minutes for average
TV receiver.



NEW FROM
Wintronix
MODEL 850
**INDUCED WAVEFORM
ANALYZER**
complete with
"Phantom Probe"
and attachments
**ONLY
\$169⁹⁵**

Localize troubles in TV, radios, amplifiers, etc., right from the top of the chassis . . . and without making a single direct connection to the circuit! The new Wintronix Model 850 does all this by the modern, easy-to-use Induced Waveform method. Helps you quickly spot those often overlooked tube and circuit defects that mean callbacks or extra troubleshooting.

Simply connect the output of the Model 850 to any scope, then slip the Phantom Detector Probe successively over each tube in the receiver under test. By viewing the waveform of the received signal (from broadcast station or generator) at each stage, you quickly localize troubles to the offending stage. Works equally well for RF, IF, video, sync, and audio circuits. A real time and trouble-saver for portable TV.

See and try the new Wintronix Induced Waveform Analyzer at your local Wintronix dealer or write for free literature.

**WINSTON
ELECTRONICS INC.,**
4312 Main St., Phila. 27, Pa.

TRY THIS ONE (Continued)

and of course quick-drying enamels of the desired shades.

In repainting etched panels, start with the etched letters. Give the inside of the letters a thin coat of the desired color using a stiff brush to apply the paint. Use jabbing strokes. Next, wipe off paint smears on the panel's surface with a rag wet with paint thinner. Do not use too much thinner or you will flood the etchings. Allow the paint to dry completely (this is absolutely necessary) before you tackle the whole panel surface. If quick-drying lacquer or enamel is used in the operation, the repainting can be completed the same day. Here's where the real problem comes in. How do you prevent paint from smearing the nice job you made on the etched lettering? Very simple!


Get out those sticks of blackboard chalk and, with the panel laid flat on a table, rub particles of chalk into the etched letters to fill the depressions completely. Wipe off excess chalk that gets on the panel's surface, being careful not to scratch out the chalk that is in the etchings. Now you are ready to spray.

Fill up the sprayer with the desired paint and spray it on the whole panel surface. Allow the paint to dry completely. When dry, restore the markings by picking them with a stiff brush. The thin paint coating breaks loose easily under the pressure of the stiff brush. The loosened particles of chalk may then be blown out of the depressions and clear, neat letters remain.
—Jesus N. Ongchua

NOVEL AUDIO SWITCHING

Many record players (both manual and automatic) have a switch that opens the line circuit at the end of the last record. By substituting an spdt switch for the normal spst line switch

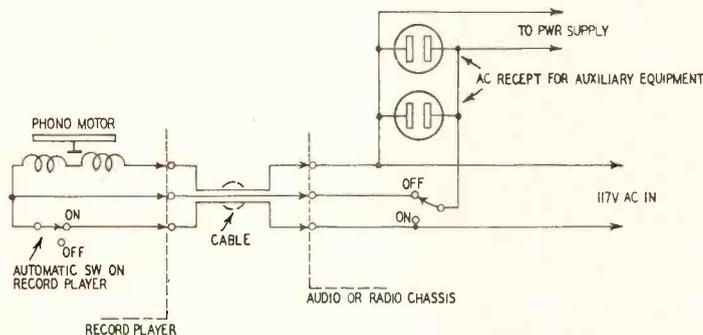amplifier or radio line switch is off, the equipment can be turned on by closing the switch on the record player. Throwing the radio or amplifier line switch to ON makes the equipment inde-




pendent of the switch on the record player. A three-conductor cable and polarized connectors are recommended for making connections between the record player and audio chassis.—John E. Meyer

The record player is controlled at all times by its on-off switch. When the

pendent of the switch on the record player. A three-conductor cable and polarized connectors are recommended for making connections between the record player and audio chassis.—John E. Meyer

SOLDERING VISE

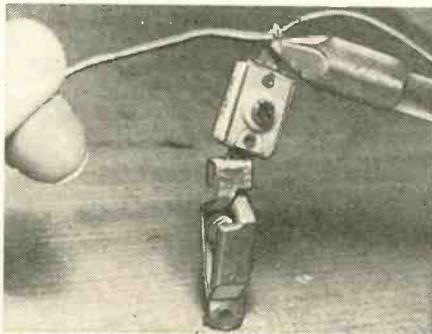

Ever wish you had a third hand to hold small parts when soldering? Make a small vise for the purpose from a test clip and a woodscrew. Clip off the wire supports at the rear of the clip, remove the screw and pinch the rear projection flat. Hacksaw the slot in the woodscrew 1/25 inch deeper, insert the back of the clip into the slot and solder it in place. Screw the vise into a pilot hole drilled in a convenient spot on the top of your workbench.—John A. Comstock

CRYSTAL-PICKUP TEST

Checking crystal phono and microphone cartridges is quick and simple when a bridge type capacitor analyzer is used.

Disconnect the leads from the cartridge and clip test leads to the terminals. Set the capacitor checker's range selector switch to the 10-5,000- μf range and balance the bridge with the tuning eye or other indicator just as you would when checking a capaci-

tor. Now, gently pluck the phono needle or thump the mike cartridge with a finger while watching the balance indicator on the tester.

If the crystal is good, the indicator flickers or deflects violently as the generated voltage and change in capacitance unbalance the bridge. On the other hand, little or no variation will be noticed if the crystal is defective.
—Paul Mitnaul

END

SCHOOL DIRECTORY

RADIO-TV ELECTRONICS



CREI graduates in big demand, ECPD-Accredited Technical Institute Curricula. New classes start monthly. Free placement service for grads. Resident school courses in Electronic Engineering Technology leading to "Associate in Applied Science" degree. Write for free Residence School catalog. Approved for veterans.

CAPITOL RADIO ENGINEERING INSTITUTE
Dept. RE, 3224 - 16th St., N. W., Washington 10, D. C.

ELECTRONICS ENGINEERING DEGREE IN 27 MONTHS



Prepare for unlimited opportunities in electronics:

B.S. degree in 27 months, mathematics, electrical engineering, TV, advanced radio theory and design. Modern labs. Low tuition, earn board. Also Aero., Chemical, Civil, Electrical, Mech., Engineering. B.S. degree in 36 mo. in Math., Chem., Physics. Also prep courses, G.I. appr., 20 bldgs., dorms, gym. Enter Dec., March, June, Sept. Keeping Pace With Progress.

INDIANA TECHNICAL COLLEGE
1510 E. Washington Blvd., Fort Wayne 2, Ind.

CODE SENDING RECEIVING SPEED



Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dept. 3-L, Box 928, Denver 1, Colo., U.S.A.

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

TOP-FLIGHT ELECTRONICS



Train for technical representative, field engineer, electronic specialist on missiles, computers, radar, automation, radio, color-TV. Basic and advanced theory and laboratory. Mathematics. Major firms select our graduates. Dormitories campus, 21 months' program. High school grad, or equivalent, G.I. approved. Start January, April, July, September. Write for illustrated catalog today.

VALPARAISO TECHNICAL INSTITUTE
Dept. C., Valparaiso, Indiana

college grads get ahead faster!

have higher incomes... advance more rapidly. Grasp your chance for a better life. Share rewards awaiting college-trained men. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter. Approved for Vets.

Bach. Sc. degree in 27 months

Complete Radio Eng. courses (TV, UHF, FM, Electronics). Also Mech., Civil, Elec., Chem., Aero., Eng. 36-months in Bus. Adm. (Gen. Bus., Acctg., Motor Transport Mgt.). Superior students faster. More professional class hours. Small classes. Enrollment limited to 150. Beautiful campus. Well-equipped labs. Prep courses. Enter Jan., Mar., June, Sept. Earnest, capable students (whose time and budget require accelerated courses and modest costs) are invited to write Jean McCarthy, Dir. Adm., for Catalog and "Your Career in Engineering and Commerce."



TRI-STATE COLLEGE

24107 College Ave., Angola, Indiana

ENGINEERS: Boost your gain!

Up your income with Announcing and Sales! The demand NOW is for combo-engineers-announcers. Write NOW for details of our residence or correspondence course in announcing.

NATIONAL ACADEMY OF BROADCASTING, INC.
3338 16th St. N.W. Dept. RE Washington, D.C.

ENGINEERING DEGREES

UNDER AND POSTGRADUATE



E.E.
Option Electronics

Earned through
HOME STUDY

Residence Classes Also Available

PACIFIC INTERNATIONAL UNIVERSITY

5719-M, Santa Monica Blvd., Hollywood 38, Calif.

NOW!

Step ahead faster

as an

INDUSTRIAL ELECTRONICS TECHNICIAN



Turn your experience into a big, new better-paying career!

Day by day industrial plants are adding more electronic devices for sorting, counting, checking almost any control job you can name. Cash in on industry's great need for men who can keep these devices in top working order. Make more money, feel more secure, doing work that is second nature to you. With what you already know about electronics you have a long head start in a field just beginning to boom. GET INTO IT RIGHT NOW with the help of

PRACTICAL INDUSTRIAL ELECTRONICS LIBRARY

No long sessions on math or theory! These 4 practical volumes show you how to keep the plant's electronic equipment working... how to locate and correct tube and circuit troubles... how to install, service, and maintain even brand new equipment without being stumped by new circuits!

4 volumes (1360 pp., 102 illus.).
Chute's Electronics in Industry

Miller's Maintenance Manual of Electronic Control

Markus & Zeluff's Handbook of Industrial Electronics Circuits

Henney & Fahnestock's Electron Tubes in Industry

FREE TRIAL—EASY TERMS

McGraw-Hill Book Co., Dept. RE-10,
321 W. 41st St., N.Y.C. 36

Send me the Practical Industrial Electronics Library for 10 days' examination on approval. In 10 days I will send \$2.50, then \$4.00 a month until \$22.50 is paid. (A saving of \$5.50 under the regular price of \$28.00.) Otherwise I will return books postpaid. (Print)

Name.....
Address.....
City.....Zone.....State.....
Company.....
Position.....RE-10

For price and terms outside U.S. write McGraw-Hill Int'l., N.Y.C.

Your choice of school is highly important to your career in



INDUSTRIAL ELECTRONICS



RADIO-TELEVISION



ELECTRONICS COMMUNICATIONS

Become an

ELECTRICAL ENGINEER

or an

ENGINEERING TECHNICIAN

at

MSOE in Milwaukee

Choose from courses in:

ELECTRICAL ENGINEERING
Bachelor of Science degree in 36 months—
Communications or Electrical Power.

ENGINEERING TECHNICIAN
Associate in Applied Science degree in 18 months—
Electronics Communications or Electrical Power.

MSOE—located in Milwaukee, one of America's largest industrial centers—is a national leader in electronics instruction—with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter—offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students. Excellent placement record. Previous educational, military, and practical experience is evaluated for advanced credit.



QUARTERS BEGIN SEPTEMBER, JANUARY, APRIL, JULY.

Choose wisely—your future may depend on it. Mail coupon today!

MILWAUKEE SCHOOL OF ENGINEERING

Dept. RE-1057, 1025 N. Milwaukee St. MS-57 Milwaukee, Wis.

Please send free illustrated career booklet (please print)

I'm interested in.....
Name.....Age.....
Address.....
City.....State.....
Are you eligible for veterans educational benefits?.....
Discharge date.....

MS-57

DYNAKIT

Amplifier Kits

A proven circuit of finest sound quality in a new deluxe 60 watt model and standard 50 watt model



MARK III 60 watts 79.95*
4, 8, 16 ohm outputs net

The new Mark III includes all the sensational attributes of the popular Mark II plus these outstanding deluxe features

- ★ 60 watts at less than 1% distortion. Instantaneous peak power of 140 watts. IM less than .05 at average listening levels.
- ★ Choke filtering and low noise circuitry reduce hum and noise to 96 db below 60 watts.
- ★ New rugged KT-88 tubes and other heavy duty parts used conservatively.

MARK II 50 watts 69.75*
8, 16 ohm outputs net

The Mark II is the best buy in high power high fidelity kits


- ★ Ease of assembly due to uniquely simple circuitry and printed circuit construction with factory-mounted parts.
- ★ Highest stability using patented stabilizing networks with minimum number of phase shifting stages. Suitable for all loud-speaker systems including electrostatic.
- ★ Dyna Biaset (patent pending) for simplified adjustment and complete freedom from effects of unbalanced components. No balancing adjustments required to meet published specifications.
- ★ Dynaco Super-Fidelity output transformer with patented para-coupled windings. This is the finest available transformer of its type for the most critical audio uses.

Available from leading Hi-Fi dealers everywhere

Descriptive brochure available on request.


DYNA COMPANY
617 N. 41st Street, Philadelphia, Pa.
Slightly higher in West

radio-electronic Circuits

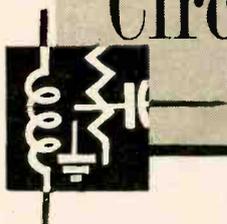


SIGNAL-POWERED SET

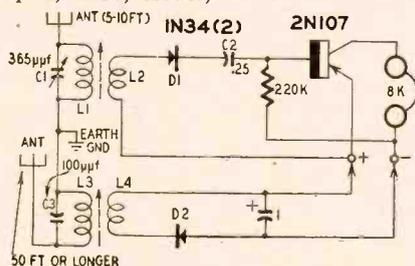For years we have dreamed of erecting an antenna and using the energy it picks up to operate electrical appliances. Now, in a limited application, this dream can come true. We can rectify and filter the carrier of a broadcasting station and use it as "battery" power to operate a transistor amplifier. (See "Free-Power Receivers" in the April, 1957, issue.)



The diagram shows the circuit of my signal-powered transistor receiver. In the set shown in the photo the "battery" circuit is separate and is connected to the receiver through a cable. A strong local signal is picked up by tuned circuit L3-C3 and coupled to D2 and rectified to provide "battery" voltage for the transistor amplifier. L3-C3 should be tuned to the frequency that provides the maximum voltage across the 1-μf filter capacitor. On strong signals the voltage will be between 0.4 and 0.8. If the strongest signal is below about 800 kc, increase the value of C3 to 200 or 300 μf.

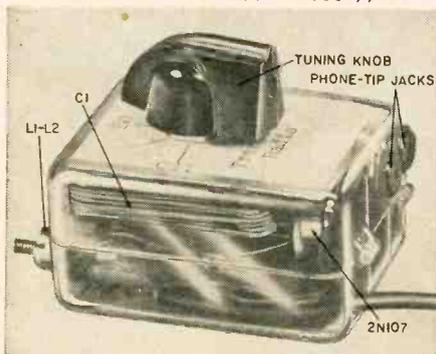


The receiver portion of the circuit consists of tuned circuit C1-L1, diode D1 and a 2N107 transistor as an audio amplifier. C1 may be one of the 365-μf midget tuning capacitors used in transistor circuits. C2 couples the detector to the 2N107 amplifier. The phones should have an impedance of at least 8,000 ohms to provide an acceptable match to the transistor. Coils L1 and L3 are ferrite-core

NEW
SPEAKER
MODELS
WITH A
FREQUENCY
RESPONSE
FOR EVERY
APPLICATION

MID RANGE
EXTENDED
TWEETER
WOOFER
COAXIAL



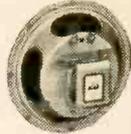High Frequency
Model GT5F
List Price \$8.75



Mid Range
Model GM8J
List Price \$13.80



Woofer
Model G15P
List Price \$42.65



Coaxial
Model G12J3
List Price \$39.75

FABULOUS IS THE ONLY WORD FOR THEM

Utah

FABULOUS "G" SERIES
SOUND REPRODUCERS

Are ideal for single or multiple installations, additions in Hi Fi systems or for bi-aural applications. Their fabulous features of superb range, response and overall perfection of performance—and unbelievable low price—makes Utah's new "G" series your best buy in Hi Fi. The incomparable, precision combination of molded, seamless cones permanently welded with indestructible adhesive to rugged 8 ohm. voice coils powered by oriented grain Alnico V magnets, assures you of full power handling capacities.

Write for complete fabulous "G" Catalog and technical folder.

See the FABULOUS "G" at your dealers today.

UTAH RADIO PRODUCTS CORP.

HUNTINGTON, INDIANA

Export Dept. Roche International, N. Y. C.

INVENTORS

Send for
PATENT INFORMATION
Book and
INVENTORS RECORD
without obligation

GUSTAVE MILLER
107-RE WARNER BUILDING
WASHINGTON 4, D. C.

REGISTERED PATENT
ATTORNEY

ASSOCIATE EXAMINER
U.S. PAT. OFF. 1922-1929

Patent Attorney & Advisor
U.S. Navy Dept. 1930-1947

PATENT LAWYER

**GARAGE DOOR
OPENER** Actuator
Mechanism \$24.50

EASY TO INSTALL. SAFE, RELIABLE
WRITE for interesting free information TODAY

P. E. HAWKINS CO.
631 PROSPECT DEPT. R-E KANSAS CITY 24, MO.


RADIO-ELECTRONICS

hi-LOW with ATLAS

high quality
low price



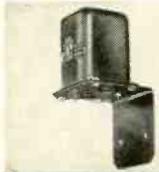PAGING & TALK-BACK SPEAKERS
6 sizes and types.
All impedances from 4 to 45 ohms.
From 5 to 15 watts.
From \$15.00 to \$24.00 NET.



WEATHERPROOF LINE MATCHING TRANSFORMERS
For constant impedance or constant voltage systems.
\$5.00 NET.




HIGH-POWERED PUBLIC ADDRESS SPEAKERS
Four sizes from 2 1/2' to 6' air column.
From \$10.00 to \$39.00 NET.



U-L APPROVED EXPLOSION-PROOF SPEAKERS
For hazardous applications.
Several sizes, all classes.
From \$66.00 to \$75.00 NET.



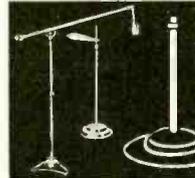SUPER-POWER DRIVER UNITS
For all purposes, powers, frequencies.
From \$15.00 to \$30.00 NET.



MIKE STANDS & ACCESSORIES
All sizes and types: boom stands, desk stands, adapters, fittings, etc.



NEW! SWITCHBOARD MIKE SUPPORT
Adjustable 12" goose neck. Use as desk support, for dispatcher office, dais, table, etc.
#SB-1 ... \$7.80 NET.



NEW! "CHESTY" NECK-SUPPORTED MIKE STAND

Quick, easy 3-way adjustment. Lightweight. Multiple uses.
#NS-1 ... \$3.00 NET.



NEW! MIKE FOOT SWITCH
Hand, foot or knee operation—shielded, grounded, noise-free, dependable, damage-proof.
#FS-1 ... \$7.20 NET.

SEND FOR COMPLETE FREE CATALOG



ATLAS SOUND CORP.

1443 39th St., Brooklyn 18, N. Y.

In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

RADIO-ELECTRONIC CIRCUITS (Continued)


antenna coils. L2 consists of 50 turns of fine wire wound close to the grounded end of L1, and L4 has approximately 75 turns of fine wire wound close to the grounded end of L3.

This set uses two antennas and a common ground. The antenna for the "battery" circuit should be at least 50 feet long and as high as practical. In many areas the other antenna need not be longer than 5-10 feet.—M. E. Quisenberry

DYNA BIASSET

A novel method of obtaining an accurate bias adjustment is incorporated in all new Dynakit amplifiers. Called *Biaset*, it insures top performance of the completed amplifier and eliminates the need of high-quality meters to make accurate bias settings.

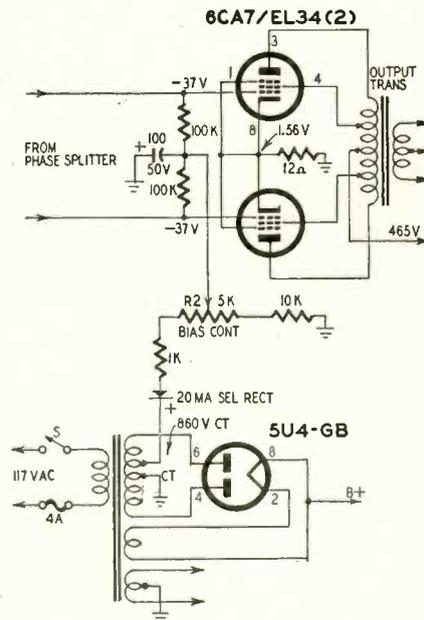The bias adjustment using the Biaset technique results in the same setting that would be obtained by adjusting the amplifier for minimum distortion.



The circuit is seen in the diagram. When bias is correctly set, the total cathode current of the 6CA7/EL-34's is 130 ma. This current, flowing through the precision 12-ohm resistor R1, produces a voltage drop of exactly 1.56 dc. As 1.56 volts is the voltage furnished by a D type flashlight cell, any fresh cell of this type acts as an accurate reference standard for bias adjustment.


The method of setting the bias is to measure the voltage output of a D type cell and note the meter reading. Then place the meter across R1. Plug in the rectifier and almost immediately there will be a current flow which will cause a meter deflection.

As the rectifier warms up, the reading rises. The bias control (R2) should then be adjusted until the meter reading is the same as that across the dry cell. There may be some drifting as the tubes heat, but this will stabilize in 15 to 30 minutes, after which no further adjustment is necessary.

Although the setting is semipermanent,

DYNAKIT PREAMPLIFIER

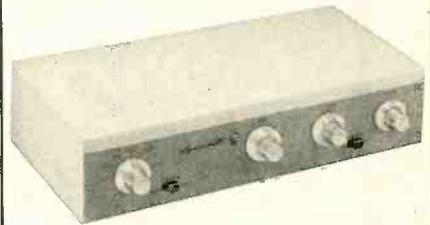An Outstanding Companion Kit to the World Famous Dynakit Amplifiers



This handsome new control unit gives crystal clear, noise-free reproduction from any modern program source. Its unique all feedback design by David Hafner sets a new standard of preamplifier performance. The design of the Dynakit preamplifier is a synthesis of outstanding features which produce smoother, more natural sound. Compare these features with any other units regardless of price.

★ Unequaled performance

Actually less than .1% distortion under all normal operating conditions. Response $\pm .5$ db 6 cps to over 60 kc. Distortion and response unaffected by settings of volume control. Superlative square wave performance, and complete damping on any pulse or transient test.

★ Easiest assembly

All critical parts supplied factory-mounted on XXXP printed circuit board. Eyeleted construction prevents damage to printed wiring. This type of construction cuts wiring time by 50% and eliminates errors of assembly. Open simplified layout offers complete accessibility to all parts.

★ Lowest noise

Integral dc heater supply plus low noise components and circuitry bring noise to less than 3 microvolt equivalent noise input on RIAA phono position. This is better than 70 db below level of 10 millivolt magnetic cartridge.

★ Finest parts

1% components in equalization circuits to insure accurate compensation of recording characteristics. Long life electrolytic capacitors and other premium grade components for long trouble-free service.

★ High Flexibility

Six inputs with option of extra phono, tape head, or mike input. Four AC outlets. Controls include tape AB monitor switch, loudness with disabling switch, full range feedback tone controls. Takes power from Dynakit, Heathkit, or any amplifier with octal power socket.

★ Outstanding appearance

Choice of bone white or charcoal brown decorator colors to blend with any decor. Finished in indestructible vinyl coating with solid brass es-cutechon.

★ Best Buy

Available from your Hi-Fi dealer at only \$34.95 net (slightly higher in the West), and yet the quality of performance and parts is unexcelled at any price.

Descriptive brochure available on request.

DYNA CO., 617 N. 41st St., Phila., Pa.


Pat. Pending

A New CONCEPT IN AMPLIFIER KIT

Construction

The ERIE AUDIO-AMPLIFIER KIT

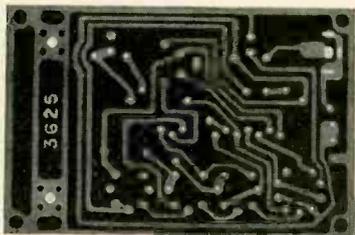featuring
"PAC" and an ERIE Embossed Wiring Board



MODEL
PAC-AMP-1

With these Plug-in Components:

- ERIE "PAC" (Pre-Assembled Components)
- ERIE EMBOSSED BOARD
- OUTPUT TRANSFORMER
- FILTER CAPACITOR
- VOLUME CONTROL and SWITCH
- TUBE SOCKETS
- CAPACITORS
- TONE CONTROL
- TUBES

SPECIFICATIONS FOR ERIE STANDARD AUDIO-AMPLIFIER

- Frequency Response: 30 cycles to 12,000 cycles +0, -3.5 db.
- Sensitivity: 0.56 volt RMS (input at 1 KC) for 4 watt output.
- Power Output: 4 watts • Input Impedance: 2 megohms.
- Output Impedance: 4 ohms • AC Power Consumption: 17 watts.
- Overall Dimensions: 6 7/8" L x 4 1/8" W x 3 7/8" H • Shipping Weight: 2 lbs.

See and hear it at
your local distributor
or Write for
nearest source.



COYNE
TRAINS YOU
IN SPARE TIME
AT HOME

COYNE QUALITY TRAINING AT LOWEST COST

TELEVISION

RADIO-COLOR TV

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes UHF and COLOR TV. Personal guidance by Coyne Staff. *Practical Job Guides* to help you EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. COSTS MUCH LESS—pay only for training—no costly "put together kits."

SEND COUPON FOR FREE BOOK

SEND COUPON BELOW for Free Book and full details including EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL.



B. W. COOKE, Jr., Pres. **COYNE** FOUNDED 1899
ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. Paulina, Dept. 77-HT4, Chicago 12, Illinois

COYNE ELECTRICAL SCHOOL
Television Home Training Div.
500 S. Paulina St., Chicago 12, Ill., Dept. 77-HT4

Send FREE BOOK and details of your Television Home Training offer.

Name _____
Address _____
City _____ State _____

NOW . . . Check Vibrators
In ANY Tube Checker

SENCORE "VIBRA-DAPTOR"

MODEL VB-2

Another Sencore Time-Saver

2 ADAPTORS IN 1

Checks Both Three and Four Prong Vibrators

- Merely plug into any tube checker. Set for 6AX4 (or 6SN7) for 6 Volt Vibrators and 12AX4 (or 12SN7) for 12 Volt Vibrators.
- Two lamps viewed through top of adaptor indicate whether or not Vibrator needs replacing.
- Rugged — Made of steel.
- Replaceable but unbreakable #51 indicating Lamps.
- Operates easily with Sencore LC2 Leakage Checker.
- Complete instructions screened on front.

At leading distributors everywhere

ONLY \$275
DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Handy "36"
- Vibra-Daptor

MANUFACTURED BY
SERVICE INSTRUMENTS CORP.
171 OFFICIAL RD. ADDISON, ILL.



RADIO-ELECTRONIC CIRCUITS (Continued)

ment, resetting the bias at times of tube replacement or similar repair or maintenance work will preserve peak performance and keep distortion at an absolute minimum.

SIMPLE AUDIO OSCILLATOR

This easily built audio test oscillator uses a minimum of parts, has enough output to test speakers and can be connected to high or low impedance circuits.

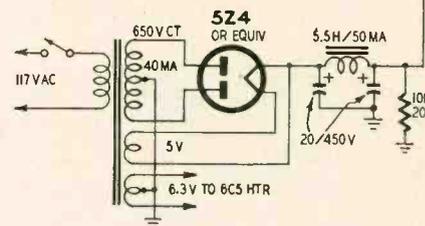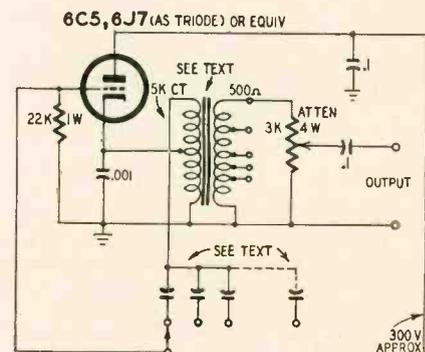The cathode of the oscillator tube connects to the center tap on the primary of an audio transformer and is bypassed to ground by a .001- μ f capacitor. The transformer has a 5,000-ohm center-tapped primary and 500-ohm secondary. I used a Stancor A-3800. The oscillator is capacitance-tuned by switching capacitors in the grid circuit. A 2- μ f paper unit produces oscil-



lations at around 20 cycles and a 500- μ f unit changes the frequency to around 20 kc. The frequency selector switch may be a 12- or 17-position rotary type such as the Mallory 32112J or 32117J, respectively. Use a soft-iron sheet-metal shield between the oscillator and power supply if both are on the same chassis.

This oscillator can be calibrated with the aid of a calibrated generator and an audio amplifier. Connect both outputs to the amplifier input and trim the tuning capacitors for zero beat. For example, if you want 400 cycles at a particular switch position and a .05- μ f capacitor produces a 450-cycle signal, bridge small capacitors across the large one until the frequency is correct.—
W. M. Finley, Jr. END

SHOCKING ERROR

On my first job
Didn't use good sense or
I'd never have touched
That high-voltage condenser!

—Phyllis Barlow

Hi-Fidelity AM-FM Radio



FAMOUS MAKE
RCA LICENSED
Reg. Price
\$139.50
For Radio
Alone
SALE PRICE
\$59.95

1958 Model Ready to Play

Here is a complete Hi-Fidelity FM-AM radio made by one of the top manufacturers. This set is ideal for custom installations. Built-in 14-Watt Hi-Fidelity push-pull amplifier. Separate bass and treble controls. Built-in AM and FM antennas, phone jack, output jack for tape recorder. Frequency Range 20-20,000 cycles \pm 2db. Output trans. tapped for 3-2, 8 and 16 ohms. This 11 tube set comes complete with crystal and magnetic phono inputs, including a 12" RCA extended range speaker. Size 12 1/2x7 1/2x7 1/2. Amplifier, Pre-amplifier, AM-FM tuner — ALL ON ONE CHASSIS. Schematic Diagram on Request.

Provides Endless Hours of Static-Free

and Drift-Free FM Listening Pleasure

11 Tubes: 6CH6, 12AT7, 6BA6, 6AL5, 12AX7, GAUG, 6SC7, 6BE6, 2-6V6, 5Y3, & IN34 Diode.

Come in for free demonstration

Or send for yours today

Send for our low price on the

Hi-Fi components you require

BRAND NEW—GUARANTEED

Prompt attention given to mail

orders. Send \$20 on C.O.D. orders

A \$5 dep. will reserve yours for XMAS

UNITE AUDIO CENTER, Dept. RE

30 North Van Brunt St., Englewood, N.J.

LO 8-1264—Next to Plaza Theatre



LMB "SAL-MET"

LMB Presents The New

FREE 1957 CATALOG covering the full precision engineered line of original box chassis as manufactured by LMB including new Miniature, new Jiffy, new T.P., new Utility Boxes. Eleven different types, 160 different shapes and sizes. A ready reference for engineers, experimenters or anyone using metal boxes. Send for your FREE CATALOG now! "SAL-MET" Non-corrosive Flux—solders copper to aluminum, aluminum to aluminum, any metal to any metal using conventional solder and regular soldering methods. Send for both LMB and "SAL-MET" Catalogs.

LMB, 1011 Venice Blvd., Los Angeles 15, Calif.

OPPORTUNITY ADLETS

Rates—50¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for December issue must reach us before October 15, 1957.

RADIO-ELECTRONICS,

154 West 14 St., New York 11, N. Y.

"FREE Cathode Ray Tube with 100 pounds surplus electronic parts and equipment \$9.95. AC cords with plugs 6 for \$1. Junco 4-Pin Transmuting Tube Sockets 4 for \$1. No C.O.D. ALPINE PRODUCTS, Dept. 10A, 2236 Hepburn, Dayton 6, Ohio."

HIGH-FIDELITY SPEAKERS REPAIRED. AM'RITE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean, special purpose receiving, TV types, magnetrons, klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. WALKER 5-7000.

20-50% DISCOUNTS on Hi-Fi, tape recorders, tape accessories, photographic equipment, individual quotations only. No catalogs. CONMAR CAMERA & HI-FI, 121-07 237th Street, Rosedale 22-R, N. Y.

WANTED: Electronics men to qualify for Engineering Degree equivalence by comprehensive examination. No courses. Excellent employment opportunities waiting. CRAWWELL INSTITUTE, RE-1, Adams, Mass.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model. DIAGRAM SERVICE, Box 672-RE, Hartford 1, Conn.

WANTED: SIGNAL GENERATORS TS-403, TS-497, TS-621, SC-3/U, TS-437, TS-510, TS-588, TS-608, etc.; TS-186 Frequency Meters, AN/APR-4 Tuning Units, other "APR" Receivers, ARC-3, other Surplus; also Hewlett-Packard and other laboratory quality equipment, Weston, etc. instruments; technical manuals; for quick cash or swap for Zenith Transistor Portables, etc. LIT-TELL, Fairhills Box 26, Dayton 9, Ohio.

LOOKING FOR CLEAN RESPONSE to 20 Cycles! Listen to the radically new "Racon Hi-C" foam suspension speaker. Write for free literature, RACON ELECTRIC CO., INC., 1261 Broadway, N.Y. 1, N.Y.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT Co., 128 Liberty Street, New York, N.Y.

NEW!

AN ARKAY EXCLUSIVE


STEREO HI-FI KITS AND PREWIRED



ST-11—a binaural tuner designed to provide the listener with stereo Hi-Fi of exceptional quality. Because each section contains own tuning condenser I.F. strip, detector and cathode follower outputs, monaural tuning of AM or FM is possible. Arkay "Miracle Ear" sensitivity on FM gives 4 mv. for 20 db. quieting; Bandwidth 200 KC, 8 db. down; freq. resp. \pm 5db. 20 to 20,000 cycles; Hum level—65 db.; AFC: adj. cathode follower output: 75 microsecond de-emphasis network.

Arkay "Miracle Ear" sensitivity on AM gives 3mv. for 20 db. quieting; Bandwidth — 8 KC; freq. resp. 20-8,000 cycles; adj. cathode follower output.

Kit \$47.95 Wired \$69.95

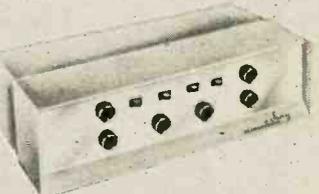

SP-6—Dual channel, preamp with cathode follower outputs. Can be used with tape deck, mag. phono, tuner, or aus. equipment. The construction of the SP-6 allows for use as a conventional pre-amp. Features include 6 position func. switch. Simultaneous volume control; Loudness control; Bass control \pm 16 db. @ 60 cps; Treble control \pm 16 db. @ 10,000 cycles; 3 position Hi-filter and Lo-filter; Freq. response \pm .5 db. 20 to 40,000 cps. Sensitivity—tape, 4 mv. for .5 volt output—phono, 6 mv. for .5 volt output—tuner and aux. .3 volt for .5 volt output; DC fil.: Built-in power supply.

Kit \$34.95 Wired \$47.95

MODEL SA-25—dual channel pre-amp drives a monaural 25 watt Linear Williamson amp. with your present amplifier for unsurpassable realism of Binaural sound.

Channel 1—25 watt amp; freq. resp. \pm 2-db. @ 20 watts, 20 to 20,000 cycles; sens. tape phono—4 mv. for 20 watts; tuner aux.—.3V for 25 watts; Loud. Control; Volume Control —controls dual channels; Bass Control and Treble Control 2 pos. "Lo-Cut" and "Hi-Cut" filters; Equal. switch for all labels plus NARTB tape head.

Channel 2—.5V output—same sens. as channel 1; same pre-amp. features. Just add your present Hi-Fi amp. to channel 2 and prepare yourself to enjoy the sound reproduction only ARKAY stereo can offer.

Kit \$59.95 Wired \$89.95

Get the new, big catalogue and specifications of the remarkable ARKAY radio, Hi-Fi and TV line
Now at your local dealer!

ARKAY 120 CEDAR STREET NEW YORK 6, N. Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 606 Sunrise Highway, Babylon, N.Y.

COMPLETE Television Sets \$11.95. JONES TV, 1115 Hambley, Pottstown, Pa.

LEARN WHILE ASLEEP! Details free. RESEARCH ASSOCIATION, Box 610-RE, Omaha, Nebraska.

RECORDERS, HI-FI, Tapes, Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

PROFESSIONAL Electronic Projects—Organs, Timers, Intercoms, Counters, etc. \$1 each. List Free. PARKS, Box 946 Redwood City, Calif.

LONG PLAYING RECORDS 20 to 50% Discount Brand-New Factory Fresh Unplayed—All Labels—Send 20¢ for catalogue to RECORD SALES, 1110 Winbern, Houston 4, Tex.

Patents, Copyrights. SANDERS, Registered Patent Attorney, 6430 Evans, Chicago 37, Ill.

DIAGRAMS! Repair Information! Radios—Amplifiers—recorders \$1, Televisions \$1.50. Give make, model, chassis. TV MERTIE, Box 101EA, Hicksville, N.Y.

FREE! COMIC AD CARD KIT

FREE CATALOG TOO!—shows our complete line of TV Service Reports, Call Books, Phone Message Books, Job Tickets, Service Pricing Guide, File Systems, Service Contracts, Parts Warranties, P.O. Forms, Statement Books, Label Books, Sketch Pads, Cash Books, etc. See them at your parts jobber. **WRITE NOW!**
Oelrich Publications 4308 Milwaukee Ave. Chicago 41, Illinois

TAPE RECORDERS

Tapes—Accessories
Nationally Advertised Brands
UNUSUAL VALUES
Send for Free Catalog
DRESSNER

69-02 RE; 174 St. Flushing 65, N.Y.

MERITAPE
Low Cost, High Quality Recording Tape—in boxes or cans.

NEW AUTOMATION PUNCHED CARD TV TUBE TESTER PROVED!

IN OVER 1 1/2 MILLION TUBE TESTS!



Smallest, lightest
tube tester ever made!



Model
DM456

Speed-test complete set of tubes in minutes with the new DynaMatic Tube Tester

- So simple to use—a customer can operate it!
- LIGHTEST and SMALLEST Gm tester available. Take it on ALL house calls.
- Perforated plastic cards set up socket pin connections and test voltages.
- Permits full-complement tube testing.
- DynaMatic is a dynamic mutual conductance tester—NOT an emission checker.
- Accurately measures mutual conductance in micromhos on 2 ranges. 0-6000, 0-18000.
- Also checks battery tubes



**IMMEDIATE
DELIVERY!**

136-10 31st Road, Flushing 54, N. Y.

Dealer Net

149⁹⁵

Prices slightly
higher west of
the Rockies

Business and People

Centralab Div. of Globe Union Inc., Milwaukee, Wis., designed and produced a 30-section, 3-pole, 6-position ceramic



switch for a West Coast aircraft manufacturer. The huge switch achieves 540 contact combinations.

General Electric Receiving Tube Dept., Owensboro, Ky., established a nation-wide public-service award program for TV service technicians. Eleven 1957 All-American Awards will be given to the service technicians in



various sections of the country who have performed outstanding community service. The trophy shown and a \$500 check for the winner's favorite charity or public service will be the prize for each winner.

Finney Co., Bedford, Ohio, developed a mobile research laboratory unit to



study unusual and difficult TV reception problems.

Vaco Products Co., Chicago, has

SERVICE MEN KNOW THERE IS JUST ONE

HUSH

Reg. U.S. Pat. Off.

Chemically engineered for tuners and switching mechanism



Hush comes in a 6 oz. pressure can with sufficient pressure to reach all contacts to wash-away that dirt, leaving clean and positive contacts, protected with a lasting lubricant film.

\$2.25 net

Hush also available in 2 oz., 8 oz. and 32 oz. containers.

See your distributor or write to

CHEMICAL ELECTRONIC ENGINEERING, INC. Matawan, New Jersey

EVER-QUIET

Reg. U.S. Pat. Off.

Since 1949 the Original Volume Control and Contact Restorer



EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning and contacts and leaving a safe protecting film. Harmless to metals, wire or carbon. Will not affect inductance, capacitance or resistance.

2 oz.

only **59c**
Net

(Also available in 32 oz. containers and 6 oz. pressure cans)

NO TV PROBLEM IS TOUGH--

WHEN YOU OWN THIS NEW GERNSBACK LIBRARY BOOK

Now solve the toughest TV problem faster with this new book—RAPID TV REPAIR—By G. Warren Heath. With this unique new book no problem will be too tough for you—no job too difficult. RAPID TV REPAIR lists alphabetically more than 500 problems. It gives you symptoms, causes and cures. It's cross-referenced where necessary and thoroughly illustrated with helpful photos, diagrams and schematics. Theory is kept to an absolute minimum. Easy-to-use troubleshooting charts help you put your finger on troubles in minutes. With this handy book you'll be able to cut troubleshooting time down—handle more jobs—and increase your income! Order your copy now.

These and Hundreds of Other Troubles Covered

- Arcing
- Barber pole effect
- Barkhausen oscillations
- Barrel effect on screen
- Bend in pix
- Bowtie pattern
- Cloudy pix
- Excessive brightness
- Excessive contrast
- Burn on screen
- Buzz
- Intermittent centering
- Hot chassis
- Distortion
- Double pix
- Negative pix
- Flashes in pix
- White lines in pix
- Squegging
- Horizontal ripple
- Loss of sync
- Intermittents
- Oscillator drift
- Slow flicker
- Horizontal foldover
- Geartooth effect.



NOW--GET THIS \$4.60 BOOK FOR ONLY \$3.35!

The deluxe hard-cover edition of RAPID TV REPAIR is nationally advertised for \$4.60—but if you join THE G/L TECHNICIAN'S BOOK CLUB now, you can get it for only \$3.35 post-paid—a discount of 27%!



THE G/L TECHNICIANS' BOOK CLUB was formed to help service technicians get the kind of books they need to get ahead without paying high prices! By mass printing and selective distribution, high printing and production costs were cut to the bone—and passed on to you as a healthy 27% discount.

No contracts—no written promises. You agree to accept a minimum of only four books of all those offered during your whole enrollment period. You may cancel anytime after that. Written by top authors, these books are beautifully bound in deluxe, durable hard covers, and expertly printed on high quality paper.

HOW THE CLUB WORKS

The book you select is sent to you ON APPROVAL—you examine it in your own home at our risk for 10 days—if you like it, send remittance—if not, simply return it in the same container in which you received it.

New books are published about every three months and sent to you on the same no-risk approval plan.

SEND NO MONEY—you keep only the books you want and pay only for the books you keep.

HOW TO ENROLL

Just fill in the coupon below. Select RAPID TV REPAIR—or any other book. **SEND NO MONEY NOW.** You'll receive the book you select promptly for a NO RISK 10-day inspection in your own home. If you like the book—keep it, and send us your remittance of \$3.35 (regular retail price \$4.60). If you don't want the book simply return it. New books will be published at regular three month intervals. Join now to be eligible for the exciting new books to be published soon.

These Books Already Published

Select RAPID TV REPAIR—or any one of these books.

JUST OFF THE PRESS

SERVICING COLOR TV—By Robert G. Middleton. Answers all your questions about chroma circuits, matrix testing, the flyback system, test equipment and much more. Troubleshooting charts help you find the toughest trouble quickly.

TV—IT'S A CINCH—By E. Aisberg. All about TV theory from studio to picture tube. Written in breezy conversational style illustrated with hundreds of specially-drawn humorous sketches.

SERVICING RECORD CHANGERS—By Harry Milnef. Make extra money servicing changers.

THE V.T.V.M. By Rhys Samuel. Get more out of this electronic workhorse.

SWEEP AND MARKER GENERATORS FOR TELEVISION AND RADIO. By Robert G. Middleton. A must for television servicing.

PROBES—By Bruno Zucconi and Martin Clifford. How to use probes for better servicing with today's complex test instruments.

THE OSCILLOSCOPE—By George Zwick. Are you getting full use of your 'scope? This book shows you how!

Books To Be Published Soon

- RAPID RADIO REPAIR
- SERVICING TAPE RECORDERS
- TV AND RADIO TUBE TROUBLES—By Sol Heller
- WORKING WITH THE 'SCOPE—By Alfred Haas

CASH-IN ON THIS MONEY-SAVING PLAN NOW!

Take advantage of this NO-RISK money saving plan now. Don't take a chance with the future. Make more money—assure success by getting the information you need to keep in step with this fast-moving industry.

—SEND IN THIS COUPON TODAY.—

GERNSBACK LIBRARY, INC., Dept. 107 C
154 West 14th St., New York 11, N.Y.

Enroll me in the G/L TECHNICIANS' BOOK CLUB. Begin my membership with the book checked below. Please check one only.

- RAPID TV REPAIR
- SERVICING RECORD CHANGERS
- SERVICING COLOR TV
- THE OSCILLOSCOPE
- TV—IT'S A CINCH
- THE V.T.V.M.
- SWEEP AND MARKER GENERATORS
- PROBES
- Send me more information on the G/L TECHNICIANS' BOOK CLUB

Name..... please print
Street.....
City..... Zone..... State.....

BUILD 16 RADIO CIRCUITS AT HOME \$22.95

with the New DELUXE 1958 Progressive Radio "Edu-Kit" only

COMPLETE HOME RADIO COURSE

NOW ALSO INCLUDES:

- TRANSMITTER
- SIGNAL TRACER
- SIGNAL INJECTOR
- CODE OSCILLATOR

- No Knowledge of Radio Necessary
- No Additional Parts or Tools Needed
- Excellent Background for TV



REG. U.S. PAT. OFF.

FREE TOOLS

NO NEED TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The 1958 "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. You will learn radio theory, construction and servicing. You will learn how to build radios, using regular schematics; how to solder and wire in a professional manner; how to service and troubleshoot radios. You will learn how to work with punched metal chassis as well as the new Printed Circuit chassis. You will learn the principles of RF and AF amplifiers and oscillator detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for TV. In brief, you will receive a basic education in Electronics and Radio, worth many times the small price you pay, only \$22.95 complete.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern principle of "Learn by Doing." You begin by building a simple radio. Gradually, in a progressive manner, and at your own rate, you construct more advanced multi-tube radio circuits, learn more advanced theory and techniques, and do work like a professional radio technician.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. The "Edu-Kit" is used by young and old, schools and clubs, by Armed Forces Personnel and Veterans Administration for training and rehabilitation. One of the most important aspects of the "Edu-Kit" is the Consultation Service which we provide. We welcome students to send us their problems, whether related to any of the material covered in the "Edu-Kit" course, or encountered in other experiences in the field of electronics.

COMPLETE RADIO COURSE—NOTHING EXTRA TO BUY

You will receive all parts and instructions necessary to build 16 different radio and electronic circuits, each guaranteed to operate. Our kits contain tubes, tube sockets, variable electrolytic mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, wire, solder, etc. In addition, you receive Printed Circuit Chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools—cutters, an alignment tool, professional electric soldering iron, and a self-powered, dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide, FCC Amateur License Training Book, and a Quiz Book. Operates on house current.

All parts, components, etc., of the "Edu-Kit" are 100% unconditionally guaranteed, brand new, carefully selected, tested and matched. Everything is yours to keep. The complete information of this practical home Radio and Electronics course is only \$22.95.

TROUBLE-SHOOTING LESSONS

You will learn to trouble-shoot and service radios, using the professional Signal Tracer, the unique Signal Injector, and the dynamic Radio and Electronics Tester. Our Consultation Service will help you with any technical problems.

J. Stasulis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for course, but I found your ad and sent for your kit."

FREE EXTRAS

- Set of Tools • Radio Book • Radio and Electronics Tester • Electric Soldering Iron • Pliers-Cutters • Alignment Tool • Tester Instruction Book • Hi-Fi Book • TV Book • Quiz Book • Membership in Radio-TV Club; Consultation Service • FCC Amateur License Training • Printed Circuitry • Certificate of Merit

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR & CONDENSER KITS WORTH \$7

- "Edu-Kit" Postpaid. Enclose full payment of \$22.95.
- "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Send me FREE additional information describing "Edu-Kit." Include FREE valuable Radio & TV Servicing Manuals. No obligation.

Name.....
Address.....

PROGRESSIVE "EDU-KITS" INC.

497 Union Ave., Dept. 133G, Brooklyn 11, N.Y.

**PROFITABLE
COLOR SERVICING
Starts Here!**



MODEL 250

\$12995
NET

Wintronix

"Jitter-Free"

**COLOR CONVERGENCE
DOT GENERATOR**

A MUST for color jobs... a real time-saver for black & white. Used by leading TV manufacturers. Incorporates complete standard sync chain with AFC for optimum white dots, cross hatch, vertical or horizontal bars. Enables fast, callback-free troubleshooting and adjustment of: *Dynamic Convergence • D-C Convergence • Beam Magnets • Dynamic Amplitude & Tilt • Deflection Coil Positioning • White Balance & "Y" Matrix • Focus • Linearity and Pix size • etc.* Ultra-stable, automatically-locked circuits guarantee "jitter-free" dot patterns regardless of pix tube size. Preset r-f output, variable 30 db.



MODEL 150

\$4995
NET

Wintronix

RAINBOW GENERATOR

New Wintronix "Linear Phase Sweep" Circuit produces vertical color bars of all possible hues representing 360 degrees of phase sweep. Simplifies home and shop alignment, adjustment or troubleshooting of any color TV. Detailed, well-illustrated instructions. The equal of color pattern generators costing many times more.

At Leading Parts Distributors Everywhere


**WINSTON
ELECTRONICS INC.**

4312 Main St., Phila. 27, Pa.



designed a counter display box as a self merchandiser for its interchangeable tool handles and blades.

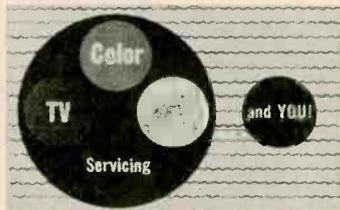Radio Television Training Association, New York, has established a



Color TV Correspondence Course for men with previous radio-TV training.

Charles M. Odorizzi, executive vice president—sales and services of RCA, was elected a member of the board of directors.



Sterling C. Spielman, director of electronic engineering for the Government and Industrial Div. of Philco Corp., Philadelphia, was appointed director of engineering for the division.



Albert Coumont (left) and Kenneth Price were named regional sales supervisors for Sprague Products Co., North Adams, Mass. Coumont was formerly



assistant to the president and is well known in the industry having served for four years as service coordinator for RETMA (now EIA). Price was previously Midwestern field engineer for Sprague Products and before that was on the engineering Staff of Radio Condenser Co.

Goodwin Mills, general manager of Knight Electronics Corp., Chicago, manufacturer of Knight Kits, was elected vice president of the company.



Bruce Fritz, sales manager of Lincoln Radio & Television Corp., Chicago, was elected vice president.



Jack W. Merritt (left), sales manager of the Photofact Div. of Howard W. Sams & Co., Indianapolis, was named sales manager of the new Electronic Distributor Div. Walton G. Wilson,



who joined the company in 1955, has been promoted to sales manager of the Industrial Service Div., succeeding Joe H. Morin, who recently became general sales manager.



Richard W. Griffiths was appointed director of sales for the Components Div. of Litton Industries following recent consolidation of the division and U. S. Engineering, a Litton subsidiary. Production, engineering, administration and sales functions are now centered in one Los Angeles location. He had been with Graybar Electric.

Alfred P. Petrusky, sales service manager of the Sylvania Radio Tube Div. in Williamsport, Pa., was promoted to manager of marketing, research—electronic products, with headquarters in New York.



Robert Black was appointed to the new position of Government contracts manager with Astron Corp., East Newark, N. J. He comes to the company from Servo Corp. of America.



George Mucher, Jr. joined the Distributor Sales Div. of Clarostat Manufacturing Co., Dover, N. H. He is the son of George Mucher, executive vice president—engineering activities.



Donald G. Haines, manager of the Chicago office of the Electronic Applications Div. of Sonotone Corp., was elected chairman of Chicago's IRE section.



BUSINESS AND PEOPLE (Continued)

Arthur M. Liebschutz joined RCA as administrator-planning and entertainment, Semiconductor Div., Somerville, N. J. He had been manager of sales in the Selenium Rectifier Div. of Federal Telephone & Radio Corp.



Richard Deutsch, sales engineer for Channel Master Corp., Ellenville, N. Y., was promoted to chief sales engineer.



Allen S. Johnson was appointed sales manager of Cletron Inc., a division of Cleveland Electronics, Cleveland, Ohio, for its line of loudspeakers, speaker kits, hi-fi enclosures and related equipment. He has been active in sales and management with Westinghouse, Colonial Radio, Thompson Products and Webcor.



Reginald G. Schuler joined Brush Electronics Co., Cleveland, Ohio, as general engineering manager. He comes to the company from Badger Meter Manufacturing Co.



Sprague Products Co., North Adams, Mass., recently received its fourth Friends of Service Management Award from NATESA at that group's confer-



ence in New Orleans. Sidney L. Chertok (left), sales promotion manager for Sprague, is shown accepting the award from Harrol O. Eales, NATESA West Central vice president. END




"Does it say how to get it back in the case?"

In Stock . . . at "the place to buy" hallicrafters

Only \$31⁴¹

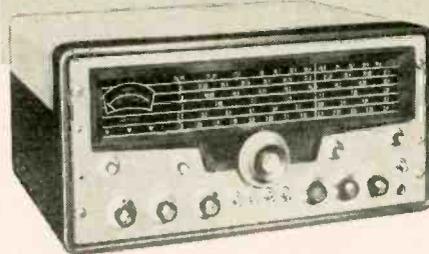PER MO. JUST 10% DOWN
NET PRICE: \$395.00



Top flight receiver in the field; seven ham bands, large slide rule dial; 1.8-2.4 mc., 3.2-4.1 mc., 7.0-7.3 mc., 14.0-14.4 mc., 21.0-21.5 mc., 26.95-27.35 mc. and 28.0-29.7 mc., plus special 10 mc. position for WWV. Covers most important MARS frequencies. Dual conversion receiver with exclusive upper/lower side band selection, T-notch filter, 50:1 tuning knob ratio with absolute re-setability, built-in precision 100 kc. marker crystal. Illuminated dual scale S-meter functions with AVC off. Five steps of selectivity from 500-5000 cycles and precision temp. compensation. 52 ohm antenna input. 14 tubes plus voltage regulator and rectifier. Size: 20x10¹/₂x16". Shp. wt. 74 lbs. R-46B Speaker, wt. 13¹/₂ lbs. — \$17.95

SX-101


at **WORLD RADIO**

"The World's Largest Distributor of Amateur Radio Equipment!"

- ✓ Top Trades!
- ✓ Prompt Shipment!
- ✓ Easy Terms!

FREE 1958 Catalog

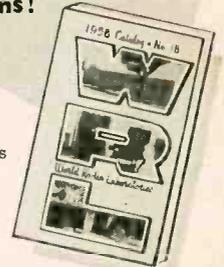200 pages, hundreds of illustrations, 15,000 top value items write for yours, today!




Please send me Free Catalog . . . and complete info on Hallicrafters SX-101.

NAME: _____
ADDRESS: _____
CITY & STATE: _____

GET MORE WORK OUT OF YOUR OSCILLOSCOPE!

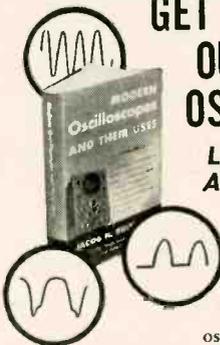Learn to service ANY radio or TV easier and faster!



Here, in an enlarged 2nd edition, is THE book that really shows you how to use oscilloscopes on every job! Clearly as A-B-C. MODERN OSCILLOSCOPES AND THEIR USES tells you exactly when, where and how. You learn to locate either AM or FM radio or television troubles in a jiffy. Even tough realignment jobs are made easy. No involved mathematics! Every detail is clearly explained—from making connections to adjusting circuit components and setting the oscilloscope controls. And you learn to analyze patterns fast and RIGHT!

'SCOPES IN COLOR TV!

Includes latest data on use of 'scopes in color TV, industrial electronics, teaching . . . even in atomic energy work. Over 400 pages and more than 400 clear pictures. Dozens of pattern photos make things doubly clear.

PRACTICE 10 DAYS FREE!


Dept. RE107, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N. Y.
Send new, 2nd edition of MODERN OSCILLOSCOPES AND THEIR USES for 10-day examination. If I like book, I will then send \$6.50 (plus postage) in full payment, or return book postpaid and owe you nothing.

Name _____
Address _____
City, Zone, State _____

OUTSIDE U.S.A.—Price \$7.00, cash with order only. Money back if you return book in 10 days.

GENIAC® KIT

Makes 34 Different Computing Machines

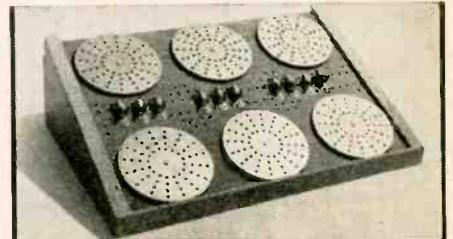

Control Panel of GENIAC set up to do a problem in check valve research. This world famous kit, over 10,000 sold to schools, colleges, business firms and electronically minded people like yourself, has proven itself as the best and only way to learn about computers with simple easy to read manuals and parts you can put together yourself.

No Soldering—you put the machines together and take them apart with solderless connections. Quick rewiring from wiring diagrams gives you an easy method of progressing from simple to complex with interesting illustrated manuals, and a 200-page book—Machines and the Mind—which discusses cybernetics, advanced computers, how the human mind functions as a computer. Every kit comes complete with over 400 parts, components, texts, manuals and accessories.

Some of the machines you construct—adding, subtracting, multiplying and dividing machines, code analyzing and decoding machines, syllogism solvers, binary to decimal converters, game playing machines (can you beat the machine at Tic-tac-toe and Nim) and among the dozen of others a machine that composes musical tunes. Send for your GENIAC® and have fun while you learn to build computers.

Return Guarantee—If you use the Geniac for 10 days and return it in good condition we will immediately refund your money.

The complete Geniac® Kit with tools, components, texts, parts for constructing 34 different calculating, reasoning, game playing and puzzle-solving machines.

only \$19.95 postpaid
(add 80c W. of Miss., \$2.00 Outside U.S.)
Send check or money order to

OLIVER GARFIELD CO., Inc. Dept. RE-107B
126 Lexington Avenue, New York 16, N.Y.

SAMS "BEST SELLER" BOOKS

FOR THE TECHNICIAN • STUDENT
EXPERIMENTER • HOBBYIST



USE THIS HANDY ORDER FORM

Pinpoint TV Troubles in 10 Minutes. Amazingly practical procedures for solving TV troubles. Includes over 50 time-saving check charts, dozens of diagrams and test Methods, circuit explanations, etc.—a real timesaver for TV repairs. 299 pages; 5½ x 8½"; fully illustrated. Only..... **\$3.95**

TV Servicing Guide. Quick reference guide for Technicians. Trouble symptoms are illustrated by picture tube screen photos and proper repair procedures are clearly described. Covers all sections of the TV circuit. 132 pages; 8½ x 11"; illust. Only..... **\$2.00**

Tape Recorders. Explains recorder theory, tape characteristics, how recorders work; covers motorboard mechanisms, drive motors, volume indicators, bias oscillators, amplifiers, magnetic heads, equalization circuits. 176 pages; 5½ x 8½"; illust. Only..... **\$2.75**

Transistor Circuit Handbook. The authoritative book on transistor types, construction, characteristics, applications, circuitry, techniques for wiring and testing. Covers every phase of the subject. 430 pages; 6 x 9"; illust. Only **\$4.95**

Hi-Fi Handbook. Invaluable data on Hi-Fi design, selection and installation, including fidelity, sound theory, analysis of all components (speakers, enclosures, amplifiers, tuners, etc.), systems design, proper selection and installation. 240 pages; 5½ x 8½"; illust. Only..... **\$3.00**

Servicing AGC Systems. Describes operation and circuit variations of AGC systems; explains applicable servicing techniques. Illustrated by actual case histories and photos of symptoms. 132 pages; 5½ x 8½"; illust. Only..... **\$1.75**

Learning Electricity Fundamentals. The complete, fascinating story of electricity: history, electron theory, static electricity, uses of switches and fuses, resistance, Ohm's Law, magnetism, electro-magnetism, transformers, generators and motors, circuits and controls, practical wiring, etc. 416 pages; 6 x 9"; illust. Only..... **\$5.95**

Transistors. A very practical, complete book on Transistors and their application in TV-Radio-Electronics. Explains theory, circuitry, installation, testing techniques and servicing. 100 pages; 5½ x 8½"; illust. Only..... **\$1.50**

Color Television. An outstanding training course for Technicians. Covers principles of the color TV system; color receiver circuits; installation and servicing of color receivers. Includes color blocks outlining use of color test equipment. 260 pages; 8½ x 11"; profusely illustrated. Only..... **\$6.95**

Electronic Metal Locators. Explains basic types and their operation; tells how to construct your own units; describes applications. Covers interesting uses in industry as well as in prospecting and mine location. 124 pages; 5½ x 8½"; illust. Only..... **\$2.50**

HOWARD W. SAMS & CO., INC.

Order from your Parts Jobber, or mail to
Howard W. Sams & Co., Dept. 2-K7
2201 E. 46th St., Indianapolis 5, Ind.

Send books checked above. My (check) (money order)
for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

(outside U.S.A. priced slightly higher)

technical Literature



TRANSFORMER GUIDE

Assembled with the technician in mind, *Catalog TV-57* describes a comprehensive line of replacement transformers and coils for TV applications. An alphabetical listing indicates the correct replacements for many TV sets.

Triad Transformer Corp., 4055 Redwood Ave., Venice, Calif.

ELECTRONIC ORGAN

A two-color 16-page illustrated booklet describes an electronic organ you can build and details the 24 kits that make up the completed organ.

Schober Organ Corp., 2218 Broadway, New York 24, N. Y.

REPLACEMENT GUIDE

This revised replacement guide for substitution of germanium for selenium rectifiers in TV sets lists all American-made sets built since 1953 in which seleniums can be replaced by germanium rectifiers.

General Electric, Semiconductor Products Dept., Electronics Park, Syracuse, N. Y.

GENERAL CATALOG

Green Sheet lists new and surplus test equipment, communications receivers and transmitters and parts.

Barry Electronics Corp., 512 Broadway, New York 12, N. Y.

DECIMAL EQUIVALENTS

A three-color wall chart of decimal equivalents with decimals running down the center of each column with 64ths to the right and 32nds and 16ths to the left. Guide lines connect each decimal with its equivalent fraction. 16 x 23 inches and 4 x 8½ inches.

John Hassall, Inc., P.O. Box 2242, Westbury, N. Y. Attn: Mr. Brewster.

CAPACITORS

Illustrated 24-page *Catalog 5701* offers a variety of ceramic, electrolytic, metallized paper and paper-oil replacement capacitors.

Tobe Deutschmann Corp., 2900 Columbia Ave., Indianapolis, Ind.

BAFFLES

A complete line of loudspeaker baffles and housings is described in an eight-page brochure, *No. P-100*. Included are wall, ceiling and portable models; hi-fi enclosures, accessories.

J. J. Powers Co., 1317 S. Fifth Ave., Maywood, Ill.

Rauland
Golden Series HI-FI

The "GOLDEN ENSEMBLE"...
Tuner, Preamp and Amplifier
in a single, compact, balanced
unit... complete Hi-Fi at
extremely low cost...

one of a complete line of
advanced design high fidelity
tuners, amplifiers and components...

hear these quality RAULAND units at
your Hi-Fi dealer or write for details...

RAULAND-BORG CORPORATION
3515 W. Addison St., Dept. A, Chicago 18, Ill.

BEWARE OF IMITATIONS

There Is Only One
Original, Dependable

NO-NOISE

Tuner-Tonic
with PERMA-FILM

Cleans, lubricates, restores all tuners, including wafers type. Won't change or affect capacities. Inductance or resistance. Won't harm insulations or precious metals, nor attack plastics. Eliminates all noise, oxidation and dirt indefinitely. For television, radio and FM.

Non-toxic, non-inflammatory, insures trouble-free performance.

6 oz. Aerosol Can. Net to servicemen.

\$3.25

Extra economical because a small amount does the job! And does it well!

Cleans, lubricates, protects... NOT A CARBON TET SOLUTION. Still available in the new 6 oz. spray can. Net to servicemen..... **\$2.25**

Volume Control and Contact Restorer with Perma-Film

2 oz. bottle. Net to servicemen.

\$1.00

Also available in 8 oz. bottles and quart cans.

At Your Nearest Distributor

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue Jersey City 4, N. J.

MEASURING TIME INTERVALS

Data File 112, *Time Interval Measurements and How to Make Them*, describes time-interval meters, the measurement of pulse width and elapsed time, and timing relay operations.

Beckman/Berkley Div. 2200 Wright Ave., Richmond, Calif.

EIA STANDARDS

Five new standards have been published: RS-189: *Encoded Color Bar Signals*, from Standards Proposal No. 524; RS-192: *Definitions and Dimensional Characteristics of Quartz Crystal units*, from Standards Proposal No. 528, a revision of TR-112-A; RS-193: *Designation System for Cathode-Ray Tubes*, from Standards Proposal No. 540, a revision of ET-111-A. RS-194: *Microwave Relay System Towers*, from Standards Proposal No. 537; RS-195: *Mechanical Characteristics for Microwave Relay System Antennas and Passive Reflectors*, from Standards Proposal No. 538.

EIA, Engineering Dept., 650 Salmon Tower, 11 W. 42nd St., New York 36, N. Y. RS-189, 30c; RS-192, 50c; RC-193, 25c; RS-194, 40c; RS-195, 50c.

NEW PRODUCTS

What's New With the Electron . . . 1957, is a listing of this manufacturer's new products for 1957. Klystrons, cer-

amic tetrodes, ceramic triodes and other special types are covered.

Eitel-McCullough, Inc., San Bruno, Calif.

BATTERY CONNECTORS

New 32-page catalog GB6 contains information on battery-power and heavy-duty connectors for industrial and allied applications.

Cannon Electric Co., 3208 Humbolt St., Los Angeles 31, Calif.

KNOBS AND DIALS

A versatile line of standard instrument and control knobs, dials and assemblies made from thermosetting plastic is featured in Catalog 106.

Kurz-Kasch Inc., Standard Parts Div., Dayton 1, Ohio.

PRECISION RESISTORS

Comprehensive data on construction, types, winding techniques, winding forms, impregnation, terminals and characteristics of wirewound precision resistors is presented in illustrated Bulletin D-1b.

International Resistance Co., 401 N. Broad St., Philadelphia 8, Pa. END

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

ONE DOLLAR buys

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.

SPECIAL THIS MONTH DEDUCT 10% ON ANY ORDER OF \$10 OR OVER

Plus a FREE SURPRISE PACKAGE

- 100 - ASSORTED 1/2 WATT RESISTORS.....\$1
- 70 - ASSORTED 1 WATT RESISTORS.....\$1
- 35 - ASSORTED 2 WATT RESISTORS.....\$1
- 100 - FUSES 1 AMP standard size 1 1/4" x 1/4".....\$1
- 5 - RCA 6' LINE CORDS 550Ω with plugs.....\$1
- 10 - 6 FT. ELECTRIC LINE CORDS with plugs.....\$1
- 5 - TV CHEATER CORDS with both plugs.....\$1
- 4 - 50' SPOOLS HOOK-UP WIRE 4 colors.....\$1
- 100' - TWIN LEAD-IN WIRE 300Ω heavy duty.....\$1
- 50' - FLAT 4-CONDUCT. WIRE, many purposes.....\$1
- 1 - 57 INDOOR TV ANTENNA hi-gain 3 section.....\$1
- 20 - ASST. TV KNOBS, ESCUTCHEONS, Etc.....\$1
- 15 - ASSORTED ROTARY SWITCHES \$15 worth.....\$1
- 100' - FINEST NYLON DIAL CORD best size.....\$1
- 200 - SELF TAPPING SCREWS #8 x 1 1/2".....\$1
- 50 - ASST. TUBULAR CONDENSERS 85°.....\$1
- 5 - ELECTROLYTIC COND. 100/50 - 50/25v.....\$1
- 35 - ASST. RADIO KNOBS screw and push-on.....\$1
- 100 - KNOB SPRINGS standard size 3/8" x 1/2".....\$1
- 100 - ASSORTED KNOB SET-SCREWS.....\$1
- 25 - ASSORTED CLOCK RADIO KNOBS.....\$1
- 400 - ASST. H'DWARE, screws, nuts, rivets, etc.....\$1
- 50 - ASST. SOCKETS octal and miniature.....\$1
- 50 - ASST. MICA CONDENSERS some hi 5%.....\$1
- 50 - ASST. CERAMIC CONDENSERS.....\$1
- 10 - ASST. VOLUME CONTROLS less switch.....\$1
- 5 - ASST. VOLUME CONTROLS with switch.....\$1
- 20 - ASST. PILOT LIGHTS #14, 46, 47, 51.....\$1
- 10 - PILOT LIGHT SKTS. bayonet type, wired.....\$1
- 50 - ASST. TERMINAL STRIPS 1, 2, 3, 4 lug.....\$1
- 10 - ASST. RADIO ELECTRO. CONDENSERS.....\$1
- 5 - ASST. TV ELECTROLYTIC CONDENSERS.....\$1
- 15 - ASST. TV COILS vnc, parking, white, etc.....\$1
- 25 - ASST. MICA TRIMMER CONDENSERS.....\$1
- 50 - TUBULAR CONDENSERS .02-100v.....\$1
- 50 - TUBULAR CONDENSERS .001-600v.....\$1
- 20 - TUBULAR CONDENSERS .017-600v.....\$1
- 50 - TUBULAR CONDENSERS 85° .01-400v.....\$1
- 3 - ELECTROLYTIC COND. 50/30 - 150v.....\$1
- 3 - ELECTROLYTIC COND. 40/10/10 - 450v.....\$1
- 3 - ELECTROLYTIC COND. 40/40 - 450v.....\$1
- 15 - TUBULAR CONDENSERS .015-1600v.....\$1
- 10 - HV TUBULAR CONDENSERS .006-1600v.....\$1
- 10 - HV TUBULAR CONDENSERS .03-2000v.....\$1
- 10 - HV TUBULAR CONDENSERS .003-3000v.....\$1
- 10 - HV TUBULAR CONDENSERS .001-6000v.....\$1
- 10 - HV TUBULAR CONDENSERS .005-6000v.....\$1
- 35 - MICA COND. 20 - 100 mmf & 15 - 250 mmf.....\$1
- 35 - MICA COND. 20 - 470 mmf & 15 - 1000 mmf.....\$1
- 35 - MICA COND. 20 - 880 mmf & 15 - 10K mmf.....\$1
- 35 - CERAMIC COND. 20-25 mmf. & 15-47 mmf.....\$1
- 35 - CERAMIC COND. 20-68 mmf & 15-1500 mmf.....\$1
- 35 - CERAMIC COND. 20-250 mmf and 15-680 mmf.....\$1
- 50 - 100Ω 1/2 WATT RESISTORS 5%.....\$1
- 75 - 680Ω 1/2 WATT RESISTORS 10%.....\$1
- 75 - 470KΩ 1/2 WATT RESISTORS 10%.....\$1
- 50 - 3.3Ω 1 WATT RESISTORS 10%.....\$1
- 50 - 15KΩ 1 WATT RESISTORS 10%.....\$1
- 50 - 470KΩ 1 WATT RESISTORS 10%.....\$1
- 25 - 2.2Ω 2 WATT RESISTORS 5%.....\$1
- 25 - 3.3Ω 2 WATT RESISTORS 5%.....\$1
- 25 - 100KΩ 2 WATT RESISTORS 10%.....\$1
- 10 - ASST. WIREWOUND RES. 5, 10, 20 watts.....\$1
- 3 - AUDIO OUTPUT TRANSFORMERS 50L6 type.....\$1
- 3 - AUDIO OUTPUT TRANS. 6X6 or 6V6 type.....\$1
- 3 - I.F. COIL TRANSFORMERS 450kc.....\$1
- 3 - I.F. COIL TRANSFORMERS 10.7 mc FM.....\$1
- 4 - OVAL LOOP ANTENNAS asst. hi-gain types.....\$1
- 3 - LOOPSTICK ANT. new ferrite, adjustable.....\$1
- 12 - RADIO OSCILLATOR COILS 450kc.....\$1
- 3 - 1/2 MEG VOLUME CONTROLS with switch.....\$1
- 1 - 5" PM SPEAKER alnico #5 magnet.....\$1
- 5 - SETS SPEAKER PLUGS, wired.....\$1
- 10 - SETS PHONO PLUGS and PIN JACKS.....\$1
- 2 - \$2.50 SAPHIRE NEEDLES 4000 playings.....\$1
- 5 - DIODE CRYSTALS 2-IN21 2-IN23 1-IN64.....\$1
- 1 - TV VERT. OUTPUT TRANS. 10 to 1 ratio.....\$1
- 5 - TV CRT. SOCKETS with 18" leads.....\$1
- 5 - HI-VOLT. ANODE LEADS with 18" leads.....\$1
- 1 - TV SYNCHROGUIDE TRANSFORMER #205R1.....\$1
- 1 - TV SYNCHROLOC TRANSFORMER #208T8.....\$1
- 1 - TV RATIO DETECTOR TRANS. 4.5mc.....\$1
- 1 - SET TV KNOBS standard type incl. decals.....\$1
- 1 - LB SPOOL ROSIN CORE SOLDER 40/60.....\$1
- 6 - SPIN TIGHT SOCKET SET 3/16" to 7/16".....\$1
- 3 - TV ALIGNMENT TOOLS 7", 12", 18".....\$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted, enclose with money order or check. You will receive a new copy of this ad for re-orders.

ON SMALL ORDERS—include stamps for postage, excess will be refunded. Larger orders shipped express collect.

BROOKS RADIO & TV CORP.

84 Vesey St., Dept. A, New York 7, N. Y.

Please send items checked

Name _____

Street _____ please print

City _____ State _____



MERIT DOES NOT carry water on both shoulders MERIT SELLS

its entire Production to Independent Electronic Parts Distributors for re-sale to Independent Service Dealers!

MERIT
MERIT COIL & TRANSFORMER CORP.
4427 N. CLARK ST., CHICAGO 40, ILLINOIS



"Notice how we've been using it more since we got the JENSEN NEEDLE?"

14th EDITION

RADIO Handbook

\$7.50 at your dealer in U.S.A. (plus any tax)

766 Pages of Practical, Down-to-Earth Radio Information!

OSCILLOSCOPES
POWER SUPPLIES
TEST EQUIPMENT
V.T. PRINCIPLES
SEMI-CONDUCTORS
V.T. AMPLIFIERS
FM TRANSMISSION
MOBILE EQUIPMENT

D-C & A-C CIRCUITS
TRANSMITTER DESIGN
TRANSMITTER KEYING
WORKSHOP PRACTICES
TRANSMITTER CONSTR.
R-F V.T. AMPLIFIERS
S.S.B. TRANSMISSION
AMPLITUDE MODULATION

RECEIVING EQUIPMENT
TV & BC INTERFERENCE
SPECIAL V.T. CIRCUITS
RECEIVER FUNDAMENTALS
ANTENNAS, H-F, V-H-F,
U-H-F & BEAMS
SPEECH & AM EQUIPMENT



BETTER TV RECEPTION

You can greatly improve performance and take the failure out of many unsuccessful fringe area installations through the use of this book. It has become a standard guide for the installation technician and a popular text for TV enthusiasts.

\$2.50 (paperbound)



RADIOTELEPHONE LICENSE MANUAL

PREPARES FOR LICENSE EXAMINATION

Contains 4 elements:

- I. Questions on basic law
- II. Basic operating practice
- III. Basic radiotelephone
- IV. Advanced radiotelephone

\$3.75 (paperbound)



BUY FROM YOUR FAVORITE DISTRIBUTOR

at above price or add 10% on direct mail orders to:

EDITORS and ENGINEERS, Ltd.

SUMMERLAND 3, CALIFORNIA

BOOKSTORES: ORDER FROM BAKER & TAYLOR CO., HILLSIDE, N.J.

TAPE RECORDERS

WHOLESALE PRICES

HI-FI COMPONENTS

NATIONAL BRANDS

WRITE FOR FREE CATALOGUE

CARSTON

215-7D E. 88 ST.
NEW YORK 28, N.Y.

Most Merchandise & Kits advertised in this Magazine

May be Purchased at

RADIO PARTS SALES INC.

5220 So. Vermont Ave.

Los Angeles 37, Calif.



IT'S NEW!
IT'S A BARGAIN!
IT'S "IN THE BAG"!

VACO® 5-PIECE ALL HOLLOW SHAFT Nut Driver Kit

No. K 505

Only \$3.68 NET

Convenient! Compact!

Here's a practical, quality built nut driver kit . . . economically priced, too! 5 popular sizes . . . 3/16", 1/4", 5/16", 11/32", 3/8" ideal for every service need . . . in one convenient plastic bag with button-down flap to keep drivers in place! Made to VACO professional quality standards throughout backed by our famous unconditional guarantee.

See Your Parts Distributor, Today!




Break-Proof Shock-Proof Comfortome Handle

All-Hollow Heavy Duty Shaft

Extra Hard Long Wearing Hex Head

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.
In Canada: ATLAS RADIO CORP., Toronto 10, Ontario

Books

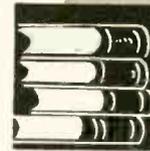

MARINE RADIO TELEPHONY, SC-34. Radio Technical Commission for Marine Services, c/o FCC, New Post Office Building, Room 6120, Washington 25, D. C. 5 1/2 x 8 1/2 inches, 48 pages. 60c (1-25 copies), 50c (over 25 copies).

Over 50,000 boats and ships carry radiotelephone equipment. Unfortunately many users do not understand how best to use radiotelephone to carry on their business, exchange vital information relating to navigation and management and, above all, for safety. This educational booklet describes proper use of the radiotelephone. It is prepared by the Radio Technical Commission for Marine Services (RTCM), an association of manufacturers, transportation groups and government agencies.

The handy guide lists calling, working and distress frequencies; summarizes radio rules and recommends procedure in case of emergency. To assure safe, as well as happy sailing, a copy should be aboard.—IQ

SERVICING COLOR TV, by Robert G. Middleton. Gernsback Library, 154 W. 14th St., New York, N. Y. 5 1/2 x 8 1/2 inches, 224 pages. Soft cover \$2.90, hard cover \$4.60.

With color television becoming more common, the service technician has been given a new and more difficult job. Color receivers are more complex and circuit action more critical than in monochrome sets. This book is written for the technician who is going to repair color receivers, rather than the man who wants to understand their fundamental principles of operation. It translates the theoretical approach, issued by the manufacturers, into an integrated, practical servicing technique that applies to all color sets.

Nine chapters cover all phases of color servicing. Numerous illustrations showing partial schematics, waveforms and screen patterns appear throughout. Some of the topics covered are: preliminary servicing, color sync servicing, servicing chroma demodulators, matrix testing, signal tracing and test equipment.—LS

ACOUSTICAL ENGINEERING, by Harry F. Olson. D. Van Nostrand Co., Inc., 257 Fourth Ave., New York 10, N. Y. 6 x 9 inches, 718 pages. \$13.50.

Modern acoustics has become a science of gigantic proportions. It is an essential part of radio, TV, recording, sound movies, ultrasonics and underwater detection and communications. This revised and enlarged edition

BOOKS (Continued)

brings the whole subject up-to-the-minute for technicians and engineers. The author explains his subject by frequent comparisons with electronics and mechanics. Analogies between the systems appear often.

The book covers basic principles of sound waves, radiators and vibrators. Detailed data and charts are provided for the various types of speakers, microphones and specialized transducers.

Calibration of microphones, testing of speakers, measurement of wow, absorption and noise are given detailed attention. Of course, there is an entire chapter on the nature of hearing. After all, it is the ear mechanism that decides what hi fi is and distinguishes between sounds.—IQ

TRANSISTOR CIRCUITS AND APPLICATIONS, edited by John M. Carroll. McGraw-Hill Book Co., 327 W. 41 St., New York 36, N. Y. 8½ x 11 inches, 283 pages, \$7.50.

More than 100 articles are reprinted in their entirety, from past issues of *Electronics* magazine. Theoretical and practical subjects are included. Transistor ratings and tables also appear.

Articles are grouped into sections: circuit design, amplifiers, oscillators, broadcast applications, communications computers, etc. Among the devices are a video amplifier, binary counter, pocket-size FM transmitter, hearing aids and hi-fi equipment. Besides germanium triodes, there are articles on tetrodes, silicon transistors and special high-frequency units. This is a convenient and comprehensive source of transistor information.

MOST-OFTEN-NEEDED 1957 RADIO DIAGRAMS AND SERVICING INFORMATION, compiled by M. N. Beitman. Supreme Publications, 1760 Balsam Rd., Highland Park, Ill. 8½ x 10¾ inches, 192 pages. \$2.50.


A compilation of original manufacturers' schematic diagrams and servicing data on the most popular late 1956 and early 1957 home and auto radios, phonographs and tube and transistor portables. Sets covered include several hundred models and chassis made by 33 manufacturers. END



"Well, he shouldn't give us too much competition."

OCTOBER, 1957

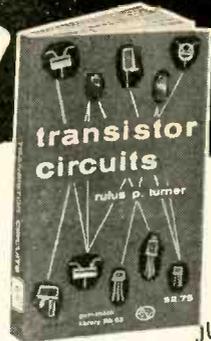Yours now—over 150 practical circuits using TRANSISTORS!



JUST OFF THE PRESS!

Rufus P. Turner, popular transistor authority and engineer, takes transistors out of the laboratory and puts them on the work bench. He has collected over 150 practical circuits for amplifiers, oscillators, power supplies, amateur equipment and other units. All were designed by experts—some by the author himself. All were tested in the author's laboratory—and *all of them work!* No watering down with transistor testing or theoretical explanation circuits! This book offers a treasure chest of building blocks which will save hours of tiresome designing. You can put these circuits to an infinite number of uses other than those originally suggested. No one who works with transistors at home or in the lab can afford to miss Turner's latest book. Order your copy now.

SOME OF THE HIGHLIGHTS

Audio Amplifiers • RF and IF Amplifiers • DC Amplifiers • Oscillators • Power Supplies • Radio Receivers • Triggers and Switches • Control Devices • Test Instruments • Amateur Devices • Miscellaneous Circuits including Geiger counter, phono oscillator, hearing aid, and intercom.

ORDER THESE COMPANION VOLUMES BY TURNER

Transistors—Theory & Practice—The practical man's "Bible" on transistors. Covers theory, characteristics, tests, plus a guide to commercial transistors. Written so the practical man can read, understand and learn how to work with transistors. No. 51—144 pages. \$2.00

Transistor Techniques—A handbook for the experimenter who wants to work with transistors! Gives scores of hints on how to use transistors in various types of equipment. Covers testing, performance, construction, care and measurements. A practical how-to-do-it book which keeps theory and math to a minimum. No. 61—96 pages. \$1.50

TRANSISTOR CIRCUITS—By Rufus P. Turner. 160 Pages. Gernsback Library Book No. 63. Paper cover. \$2.75

MAIL THIS COUPON TODAY

GERNSBACK LIBRARY, Inc., Dept. 10
154 West 14th St., New York 11, N.Y.

My remittance of \$..... is enclosed. Please send me the books checked below postpaid.

- No. 63 Transistor Circuits. \$2.75
 - No. 61 Transistor Techniques. \$1.50
 - No. 51 Transistors—Theory & Practice \$2.00
- Prices 10% higher in Canada.

NAME.....
please print

STREET.....

CITY.....STATE.....

LEARN

Television

RADIO-COLOR-TV

Electricity

ELECTRONICS

IN THE GREAT SHOPS OF **COYNE**

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Veterans and Non-Veterans—Get practical training in top opportunity fields. Prepare now for a better job and a real future. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students. *Training in Refrigeration and Electric Appliances can be included.*

FREE BOOK Clip coupon for Big Free Illustrated Book. No obligation and *No Salesman Will Call.* Act NOW.

B. W. Cooke, Jr., President

COYNE
ELECTRICAL SCHOOL

OPERATED NOT FOR PROFIT
Established 1899
500 S. Paulina, Chicago
Dept. 71-81H

B. W. COOKE, Jr., Pres.
COYNE Electrical School
500 S. Paulina St., Chicago 12, Ill. Dept. 71-81H

Send FREE BOOK and full details on:

- TELEVISION-RADIO
- ELECTRICITY-ELECTRONICS

NAME.....

ADDRESS.....

CITY.....STATE.....

SENCORE

Another Sencore Time-Saver

Handy "36"

R-C

Substitution Unit

"36"

Most Often Needed Components At YOUR Fingertips!

3 pole, 12 position switch individually selects one of the "36" components for direct substitution.

Contains:

- ★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
- ★ 12—½ watt 10% resistors from 10K ohms to 3.6 megohms
- ★ 10—600 volt capacitors from 100-mmf. to .5mf.
- ★ 1—10mf., 450V Electrolytic
- ★ 1—40mf., 450V Electrolytic

Completely isolated

ONLY \$1275 DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

AVAILABLE AT ALL PARTS DISTRIBUTORS!

SENCORE SERVICE

INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information.

BUY DIRECT FROM FACTORY

TRANSVISION

Oldest Name in Electronic Kits

SPLIT/KITS

PAY AS YOU WIRE
INVEST SLIGHTLY MORE—but—
BUILD THE BEST!

- A FEW DOLLARS GETS YOU STARTED: Each Kit is "split" into a few packages, or stages, which you buy one-by-one as you wire.
- EASIEST TO ASSEMBLE
- FREE educational aids
- Money-Back Guarantee

A COMPLETE LINE OF

- TV KITS
- INSTRUMENT KITS
- HI-FI KITS
- HI-FI Speaker Systems
- HI-FI CABINETS

A wide assortment to house any make Hi-Fi units. Exquisitely styled, beautifully finished. Cannot be equalled anywhere.

Write for Complete Catalog



NEW!
Transistorized
VTVM-VOM KIT
\$39.95 for Kit

Only \$10 gets you started. This covers the 1st stage. Balance in 2 stages; pay as you wire... Also, factory wired for \$79.

New TV KIT

Learn TV while building a DELUXE TV SET
Only \$15 gets you started. Balance in easy stages. Profit 3 ways: Learn by doing; save up to 50% on a DELUXE TV SET; prepare for COLOR TV.

FREE: A TV Course of Study with Kit. Prepared by a recognized educator, this course alone is worth many times the cost of the TV Kit.

TRANSVISION, INC.,
NEW ROCHELLE, N. Y.

TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. E

I'm enclosing \$_____ deposit. Send the following: _____

Send FREE copy of your latest Catalog.

Name _____

Address _____

City _____ State _____

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

| | |
|---|---------------|
| Admiral Corp..... | 152 |
| Alliance Manufacturing Co., Inc..... | 135 |
| Allied Radio Corp..... | 15, 101-108 |
| Amperex Electronics Corp..... | 154 |
| Amphenol Electronics Corp..... | 22 |
| Arky Inc..... | 167 |
| Astron Corp..... | 148 |
| Atlas Sound Corp..... | 165 |
| B & K Manufacturing Co..... | 117 |
| Barjay Co..... | 177 |
| Barry Electronics Corp..... | 176 |
| Belden Manufacturing Co..... | 137 |
| Bell Telephone Labs..... | 32 |
| Benco Television Associates Ltd..... | 122 |
| Blonder-Tongue Labs..... | 150-151 |
| Brooks Radio & Television Corp..... | 130, 173 |
| Brustein-Applebee Co..... | 157 |
| CBS-Hytron..... | 8, 148 |
| Capitol Radio Engineering Inst..... | 17, 180 |
| Carston Studios..... | 174 |
| Castle Television Service Ltd..... | 161 |
| Centralab Div. of Globe Union..... | 88 |
| Chemical Electronic Engineering Inc..... | 168 |
| Circuit Manufacturing Co., Inc..... | 160 |
| Cisin (H. G.)..... | 145 |
| Cleveland Institute of Radio Electronics..... | 10-11 |
| Coloradaptor..... | 156 |
| Columbia Record Club..... | 9 |
| Cornell-Dubilier Electric Corp..... | 24 |
| Coyne Electrical School..... | 141, 166, 175 |
| Deutschmann (Tobe) Corp..... | 127 |
| DeVry Technical Institute..... | 7 |
| Dressner..... | 167 |
| Dyna Co..... | 164-165 |
| Dynamic Electronics..... | 158 |
| Editors & Engineers..... | 174 |
| Electro-Sonic Labs..... | 26 |
| Electro-Voice, Inc. Inside Back Cover | |
| Electronic Brain Enterprises..... | 158 |
| Electronic Chemical Corp..... | 172 |
| Electronic Instrument Co. (EIO)..... | 33, 34 |
| Electronic Measurement Corp..... | 153 |
| Electronic Publishing Co..... | 159 |
| Elgin National Watch Co..... | 16 |
| Erie Resistor Corp..... | 166 |
| Esse Radio Co..... | 144 |
| Finney Co..... | 121 |
| Futuramic..... | 153 |
| Garfield (Oliver) Co..... | 159, 171 |
| General Industries Co..... | 18 |
| Gernsback Library, Inc..... | 169, 175 |
| Grantham School of Electronics..... | 23 |
| Hawkins, (P. E.) Co..... | 164 |
| Heath Co..... | 66-81 |
| IBM..... | 114-115 |
| Indiana Technical College..... | 157 |
| JFD Electronics..... | 86-87 |
| Jensen Industries..... | 173 |
| Jensen Manufacturing Co..... | 90-91 |
| Jones & Laughlin Steel Corp..... | 126 |
| Karlson Associates, Inc..... | 155 |
| Kraeuter & Co., Inc..... | 160 |
| Kuhn Electronic Products..... | 177 |
| LMB..... | 167 |
| Lafayette Radio..... | 178-179 |
| Lansing, (James B.) Sound, Inc..... | 159 |
| Lektron Specialities..... | 161 |
| Littlefuse, Inc..... | 110 |
| Madison Fielding..... | 124 |
| Mallory, (P. R.) & Co., Inc..... | 112-113 |
| McGraw-Hill Book Co., Inc..... | 163 |
| Merit Coil & Transformer Corp..... | 173 |
| Miller (Gustave)..... | 164 |
| Moss Electronics Distributing Co..... | 96-97 |
| National Radio Institute..... | 3, 27-28 |
| National Schools..... | 5 |
| North American Philips Co., Inc..... | 151, 155 |
| Oelrich Publications..... | 167 |
| Opportunity Adlets..... | 167 |

HQ for the 5 TOP QUALITY brands of

TUBES

AT SENSIBLE PRICES!

- Individually boxed • First quality only
- Brand New • 90-DAY RETMA guarantee
- No rebrands • No private brands • No rejects

WRITE FOR LATEST TUBE CATALOG FREE!

| | | | | | |
|----------------|--------|------------------|-------|----------------|-------|
| 0A2..... | .75 | 4PR60A..... | 30.03 | 956..... | .30 |
| 0A3 VR75..... | .88 | 4X500A..... | 45.00 | 957..... | .30 |
| 0B2..... | .70 | 5C22..... | 24.00 | 958A..... | .35 |
| 0B3 VR90..... | .80 | 6AK5W..... | 1.00 | 991..... | .20 |
| 0C3..... | .75 | 6C21/450TL..... | | CK1005..... | .30 |
| 0D3..... | .75 | | 13.50 | CK1007..... | .45 |
| 1B35..... | 3.35 | 6J4..... | 1.70 | 5517..... | 1.35 |
| 1B4..... | 2.00 | FG32..... | 4.25 | 5636..... | 2.75 |
| 1P25A..... | 20.00 | *35T0..... | 2.00 | 5642..... | 1.00 |
| 1P29..... | 1.60 | VC50/32V..... | 8.00 | 5646..... | 4.00 |
| 1P30..... | 1.25 | RK-65/5023..... | | 5651..... | 1.00 |
| 2E22..... | 1.90 | | 7.50 | 5654..... | 1.20 |
| 2E24..... | 2.25 | HY69..... | 2.10 | 5676..... | .65 |
| *2N155..... | 3.75 | RKR72 or 73..... | 1.00 | 5677WA..... | 4.50 |
| (CBS)..... | 3.25 | VXR-130..... | 1.00 | 5693..... | 4.50 |
| *2N255..... | 2.90 | GL299..... | 1.50 | 5703WA..... | 3.95 |
| (CBS)..... | 2.90 | 307A..... | .60 | 5719..... | 1.40 |
| 4-1000A..... | 95.00 | 3573..... | 14.00 | 5725..... | 1.50 |
| 28D7..... | .80 | 371B..... | .75 | 5726..... | .65 |
| 813..... | 8.75 | 403A..... | .90 | 5744..... | 1.00 |
| 830B..... | 1.50 | 403B..... | .90 | 5749..... | .95 |
| 892-R..... | 250.00 | 404A..... | 12.50 | 5763..... | 1.25 |
| 6004..... | 2.00 | 416B..... | 22.50 | 5814..... | 1.00 |
| 28P..... | 3.95 | 417A..... | 2.25 | 5819..... | 23.95 |
| CL-2..... | 10.00 | 474/5842..... | | 5840..... | 3.50 |
| 2C35..... | 2.00 | | 12.00 | 5841..... | .70 |
| 2C39A..... | 10.00 | KU-610..... | 3.50 | 5881..... | 2.80 |
| 2C40..... | 6.75 | GL673..... | 12.50 | 5910..... | .45 |
| 2C53..... | 9.75 | 703A..... | .95 | 5911..... | .50 |
| 2E24..... | 2.25 | 7177..... | .25 | 6111..... | 4.50 |
| 2K45..... | 35.00 | *K5722..... | 30.00 | 6112..... | 4.50 |
| 2K55..... | 15.00 | *750TL..... | | 6130/3C45..... | 4.75 |
| 3E20..... | 1.50 | 803..... | 1.50 | 6161..... | 45.00 |
| 3B24W..... | 4.25 | 805..... | 4.00 | 6201..... | 2.50 |
| 3B29..... | 4.75 | 807W/5933..... | 1.50 | 6539..... | 9.00 |
| 3BP1..... | 1.85 | 814..... | 2.50 | 8008..... | 3.25 |
| 3C23..... | 3.95 | | | 8020..... | 1.00 |
| 3C31..... | 1.00 | 836..... | 2.00 | 9001..... | .70 |
| 3C45..... | 6.75 | 838..... | 1.25 | 9002..... | 1.25 |
| 3J40..... | 25.00 | 838..... | 1.40 | 9004..... | .25 |
| 3K20000LK..... | | 866A..... | 1.20 | 9006..... | .25 |
| | | 872A..... | .90 | | |
| *4-65A..... | 15.00 | 872A (GE)..... | 2.75 | 9007..... | 1.25 |
| *4-125A..... | 30.25 | 918..... | 1.10 | 9008..... | .25 |
| *4-250A..... | 35.00 | 927..... | .95 | AND OTHERS | |
| *4-400A..... | 45.00 | 954..... | .10 | *(Surplus) | |
| 4B24/EL3C..... | 4.00 | 955..... | .30 | (transistor) | |

WE ARE FACTORY AUTHORIZED DISTRIBUTORS OF CBS-HYTRON, EIMAC, PENTA, etc.

INVISIBLE INFRA-RED CL-2 LAMP \$10.00

The device that makes license free transmission a reality! 2 way voice or MCW can be transmitted over concentrated invisible infra-red rays. Information on how to construct a 2-way transmission receive station available.

CL-2 LAMP, w/info (worth \$50)..... \$10.00

2-COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partitions prevent tube breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices.

| SIZE | PORT TUBE | PER 100 |
|----------------|----------------|---------|
| Miniature..... | 6AU6, etc..... | \$1.00 |
| GT..... | 6SN7, etc..... | 1.25 |
| Large G..... | 1A3, etc..... | 1.50 |
| Large G..... | 5U4G, etc..... | 2.00 |

WHITE GLOSSY BOXES Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

TUBE STACKERS

White glossy only. Ministacker holds 10 Mini. tube cartons; "GT" stacker holds 10 "GT" cartons.

| SIZE | PER EACH |
|------------------|----------|
| Ministacker..... | 1 1/2c |
| GT..... | .02 |

\$10.00 Per Case of 1000 FOB NYC.

All cartons & stackers f. o. b. NYC

NEW! CLOSED CIRCUIT TV. LOW PRICED! THE ELECTRON CAMERA

A brand new concept in low priced, portable closed circuit TV equipment. The unique camera is completely self contained with no excess cables running in all directions. No special TV monitor required. Any regular TV set will receive from the camera. Its range can be adjusted to any practical distance by choice of lens. Highly stable and light sensitive. No professional lighting required. Excellent for use by amateurs, service dealers, industry, department stores, penal institutions, medicine, churches, police, military, etc. All units are brand new, factory fresh, and covered by standard RETMA guarantee. Complete instructions provided. Order from this ad or write for free descriptive literature.

| | |
|--|----------|
| TV CAMERA KIT, model V-100 (with f/1.9 lens)..... | \$395.00 |
| Same as above but factory assembled and ready to go..... | 495.00 |
| TRIPOD for V-100 camera..... | 29.00 |
| 17" VIDEO MONITOR (all above FOB factory)..... | 299.00 |

WRITE FOR "BARRY'S GREEN SHEET" FREE!

TERMS: 25% deposit with order, balance C.O.D. All merchandise guaranteed, F.O.B. N.Y.C. Subject to price variation and stock depletion. MINIMUM ORDER \$10.00

BARRY ELECTRONICS CORP.

512 Broadway, Dept. RE, N.Y. 12, N.Y.
Phone: Walker 5-7000

| | | | |
|--|----------|--|---------------|
| ORRadio Industries, Inc..... | 146 | Stan-Burn Radio & Electronics..... | 154 |
| Oxford Components, Inc..... | 156 | Stanley Electronics Corp..... | 156 |
| Pentron Corp..... | 99 | Supreme Publications..... | 143 |
| Perrajflux Corp..... | 142 | Sylvania Electric Products, Inc..... | 12-13 |
| Phaotron Instrument & Electronics Co..... | 94 | Technical Appliance Corp..... | 133 |
| Pickering & Co., Inc..... | 83 | TeleMatic Industries Inc..... | 158 |
| Precise Development Corp..... | 147 | Teletest Inc..... | 168 |
| Prentice-Hall, Inc..... | 139 | Thorens Co..... | 118 |
| Progressive "Edu-Kits," Inc..... | 169 | Transvision, Inc..... | 176 |
| Pyramid Electric Co..... | 119 | Trio Manufacturing Co..... | 140 |
| Quality Electronics..... | 177 | Triplett Electrical Instrument Co. Inside Front Cover | |
| Radiart Corp..... | 24 | Tung-Sol Electric Co..... | 6 |
| RCA Electron Tube Division Back Cover | | United Audio Center..... | 167 |
| RCA Institutes..... | 31 | University Loudspeakers, Inc..... | 131 |
| Radio Parts Sales Co..... | 174 | Utah Radio Products Corp..... | 164 |
| Radio-Television Training Associates..... | 25 | Vaco Products Co..... | 174 |
| Rauland Borg. Corp..... | 172 | Western Radio..... | 157 |
| Raytheon Manufacturing Co..... | 30 | Winegard Co..... | 20-21 |
| Rek-O-Kut Co., Inc..... | 170 | Winston Electronics, Inc..... | 162, 170, 177 |
| Rinehart & Co., Inc..... | 128, 171 | World Radio Labs..... | 171 |
| Rockbar Corp..... | 125 | | |
| Sams, (Howard W.) & Co., Inc..... | 172 | | |
| Scott (Herman Homer)..... | 14 | | |
| Service Instruments Corp..... | 166, 175 | | |
| Shure Brothers, Inc..... | 111 | | |
| Simpson Electric Co..... | 149 | | |
| Sonotone Corp..... | 129 | | |
| Sprague Products Co..... | 123 | | |
| Sprayberry Academy of Radio..... | 19 | | |

SCHOOL DIRECTORY PAGE 163

Baltimore Technical Institute
Candler System Co.
Capitol Radio Engineering Institute
Indiana Technical College
Milwaukee School of Engineering
National Academy of Broadcasting, Inc.
Pacific International University
Tri-State College
Valparaiso Technical Institute

BRANCH ADVERTISING OFFICES: Chicago: 1413 Howard St. Tel. Rogers Park 4-800. Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire. Tel. DUmkirk 7-2328. San Francisco: Ralph W. Harker and Associates, 444 Market St., Tel. GARfield 1-2481.

FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4. Australia: McGil's Agency, Melbourne. France: Brentano's, Paris 2e. Belgium: Agence et Messageries de la Presse, Brussels. Holland: Trilectron, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency, Ltd., Johannesburg. Capetown, Durban. Natal: Universal Book Agency, Johannesburg. India: Broadway News Centre, Dadar, Bombay #14. Pakistan: Paradise Book Stall, Karachi 3.

BE QUALITY WISE... BUY QUAL-KITS!



HI-FI AMP. KIT
Complete 6 tube-10 watt amplifier Push-pull beam power output, built-in pre-amp. 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response 1/2 db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion. **\$28.50**

Every kit complete with 28 page fully illustrated instruction and assembly manual. Cover and legs optional. *Add 10 percent for new federal tax



HI-FI AM-FM TUNER KIT
Advanced 7 tube circuit plus Rectifier for full sensitivity and selectivity. Distortion less than 1%. Sensitivity is 5 uv for 30 db quieting on FM, 25 uv AM. Armstrong FM Circuit with limiter. Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control — no drift. Easy assembly. **\$28.95***

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

QUALITY-ELECTRONICS

319 Church St. Dept. RE10 New York 13, N. Y.

CRYSTAL CONTROLLED CONVERTERS

POLICE • FIRE • COMMERCIAL



- ✓ Precision—Stability
- ✓ Sensitivity
- ✓ Easy Installation

\$32.50

• A compact converter supplied with commercial tolerance crystals, self contained automatic noise limiter. Also models with squelch. Ideal for mobile or home use.

TUNERS

Enjoy FM Programs While You Drive.

- FM BROADCAST
- 30-50 MC
- 108-176 MC

from **\$22.50**

WRITE FOR LITERATURE



KUHN ELECTRONICS

20 GLENWOOD CINCINNATI 17, OHIO

TEST CONDENSERS IN THE SET!

Test Selenium Rectifiers!
CHECK CAPACITORS UNDER WORKING CONDITIONS!



NOT A KIT • SATISFACTION GUARANTEED OR RETURN WITHIN TEN DAYS FOR REFUND

CAPACITEST 2

with thousands already in use, is an improved, compact checker that does a giant job to save you time and money. It tests Selenium Rectifiers! It will check condensers at 150 volts, which is approximately the working voltage in a radio or TV set. Meters will not give this type of check since the applied voltage is 20 volts or less. Avoid call-backs by using CAPACITEST. Accurately, quickly shows open, shorted or intermittent capacitors and leaky electrolytics. Compact: 4"x4"x2"—lightweight for bench or tool kit.

CAPACITEST

Quickly, Accurately Checks:

- PAPER, CERAMIC, MICA CAPACITORS
- ELECTROLYTICS
- SELENIUM RECTIFIERS
- CONTINUITY
- AC/DC VOLTAGES
- FLASHBULBS

\$9.95

postpaid dir. net complete, ready to operate

FREE SET OF LEADS with each CAPACITEST 2 for limited time. Order direct from mfr. Send \$3 deposit with COD's. Save PP & COD fees. Send \$9.95 and we'll pay postage.

The Barjay Co. 145 West 40 Street New York 18, N. Y.

SPOT INTERMITTENTS FAST!



\$89.95 NET

NEW Wintronix INTERMITTENT ANALYZER

Makes any TV or Radio Super-Sensitive to Intermittents & Noisy Components...

NO WAITING



NO "COOKING"



NO "FREEZING"

Save valuable time and bench space when troubleshooting intermittents. Just connect output of Model 828 to Radio or TV receiver antenna terminals, and use exclusive "Electro-Wand" (for tubes) or "Electro-Probe" (for components) to quickly pinpoint intermittent or noisy tubes, capacitors, resistors, coils, transformers, defective connections, etc. No direct circuit connection needed.

Special Wintronix circuit immediately makes any receiver super-sensitive to intermittents. Lets you hear intermittents through built-in speaker. Reduces callbacks by detecting borderline components before they fail.

See the Wintronix Model 828 at your local parts distributor or write for free literature.

WINSTON ELECTRONICS INC.

4312 Main St., Phila. 27, Pa.

FREE!
LAFAYETTE
CATALOG

JUST
OFF
THE
PRESS!




**NEW 180 PAGE ELECTRONIC
CATALOG FEATURING
THE BEST BUYS IN THE BUSINESS**

The newest and largest assortment of Electronic, Radio and TV parts, Hi-Fi and Public Address Components and systems, Test Equipment, tubes, Transistor Kits and miniaturized components for transistor circuitry, Ham Equipment, Builders Kits, Tools, Books, Microscopes, Binoculars, Telescopes, Cameras, and Drafting Equipment.—**ALL AT LOWEST PRICES**—Catering to the economy minded dealer, serviceman, engineer, technician, experimenter and hobbyist. **CRAMMED FULL OF MONEY SAVING BUYS. SEND FOR YOUR FREE COPY TODAY.**


Lafayette

Introduces Hi-Fi Gems


... at prices everyone can afford

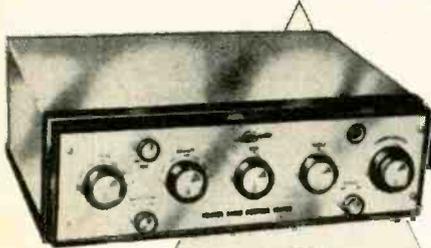


**KT-300
IN KIT
FORM
39.50**

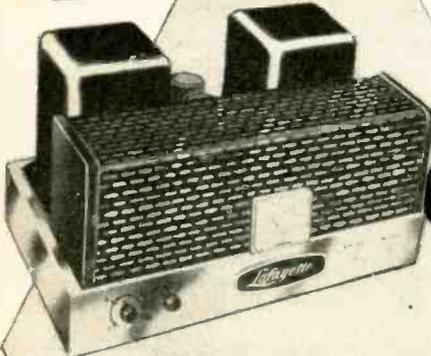

**KT-400
IN KIT
FORM
69.50**

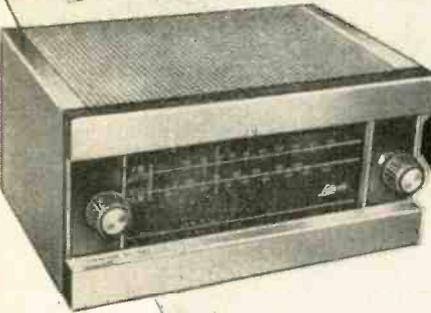

**KT-100
LESS CAGE
34.95**

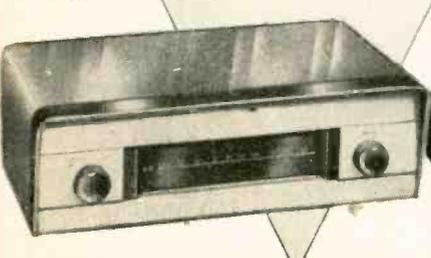

**LT-60
WIRED
FM TUNER
49.95**

**LAFAYETTE MASTER AUDIO CONTROL CENTER
with BINAURAL CHANNEL AND DUAL VOLUME CONTROL.
Years Ahead of Every Other Control Unit ... Ahead In Sound ... Ahead In Styling
Ahead In Design ... Ahead In Features ... Available In Kit and Wired Form**

This is not only the finest hi-fi preamp characterized by unmatched features, but it has been functionally designed to keep pace with the conversion of your present hi-fi system to binaural (stereophonic) sound. Incorporates an extra channel and dual volume control for binaural reproduction. Features include DC on all tube filaments, negative feedback in every stage, dual cathode follower output stages and latest printed circuit construction. Less than 0.09% 1M distortion and less than 0.07 harmonic distortion at 1V. Hum and noise level better than 80 db below 3V. Uniformly flat frequency response over entire audible spectrum. 7 inputs for every type of phono, tuner or tape. Tasteful styling, brilliantly executed. Size 12 1/4 x 9 1/2 x 3 3/4". Shpg. wt., 10 1/2 lbs.

KT-300—Lafayette Master Audio Control Kit Complete with cage and detailed assembly instructions. Net **39.50**
LT-30—Same as above completely wired and tested with cage and instruction manual. Net **59.50**

DELUXE 70 WATT BASIC AMPLIFIER

• Conservatively Rated At 70 Watts • Ultra-Stable • Variable Damping
• Metered Balance And Bias Adjust Controls • Available In Kit And Wired Form
Here's ultra-stability in a 70 watt basic power amplifier employing highest quality components conservatively rated to insure performance and long life. Features matched pair KT 88's and wide range linear output transformer, variable damping control, meter for bias and balance and chrome plated chassis. Frequency response 10-100,000 cps ± 1db. Hum and noise 90db below full output. 1M distortion less than 1 1/2% at 70 watts from 20 to 20,000 cps ± 1db. Output impedance 4,8 and 16 ohms. Handsome decorative cage perforated for proper ventilation. Size 14 1/2 x 10 x 7 3/8" including cage and knobs. Shpg. wt., 40 lbs.

KT-400—Lafayette 70 watt Deluxe Basic Amplifier Kit complete with cage and detailed assembly instructions. Net **69.50**
LA-70—Same as above completely wired and tested with cage and instruction manual. Net **94.50**

LAFAYETTE'S EXCLUSIVE FM-AM TUNER KIT

FM-AM Tuner with outstanding Specifications and astonishing Performance — All at a Budget Price — In easily assembled kit form.
Excellence of design and quality of components provide this compact hi-fi FM-AM tuner with superb characteristics normally found in most expensive tuners. Features Armstrong FM circuit with limiter and Foster — Seeley discriminator, grounded grid triode RF amplifier, AFC defeat circuit combined with front panel tuning control and simplified tuning with slide rule dial and counterweighted mechanism. Excellent sensitivity, selectivity and frequency response. Distortion less than 1% at rated output. Meets FCC requirements for radiation. Attractive etched copper-plated and lacquered finish. Simplified detailed Construction Manual with step-by-step assembly instructions. Size 9 3/8" W x 9 1/2" D (excluding knobs) x 5 1/4" H. Less metal cage. Shpg. wt., 9 lbs.

KT-100—FM-AM Tuner Kit, less Metal Cage Net **34.95**
ML-100—Metal Cage for above. Shpg. wt., 3 lbs. Net **5.00**

**NEW! Lafayette DELUXE HI-FI FM TUNER
COMPLETELY WIRED AND TESTED.**

• Armstrong Circuit with Dual Limiters • 9 Tubes Plus Selenium Rectifier
• Temperature Compensated and AFC • Custom Styled
Lafayette engineers bring to the discriminating music lovers who confine their broadcast listening to FM (the true hi-fi spectrum), a tuner giving the utmost possible value in performance and quality. Features Armstrong circuit with Foster-Seeley discriminator, 3-gang condenser with tuned RF stage, 4 IF stages (including dual limiters), AFC and AFC defeat, temperature compensated circuitry, and has 9 tubes plus selenium rectifier. Sensitivity 3.5 μv for 20-30db. Distortion less than 1%. Frequency response 20-20,000 cycles ± 0.5db. Cathode follower and high impedance outputs. Meets FCC requirements for radiation. Low modern lines, attractively finished in brushed gold-brass and maroon, for shelf or table top use. Completely self powered and wired, ready for operation. Size: 14" W x 7" D x 4 1/4" H. Complete with cover. Shpg. wt., 13 lbs.

LT-60—FM tuner Net **49.95**

*Lafayette
Radio*

DEPT JJ-1

165-08 LIBERTY AVE.
JAMAICA 33, N. Y.

NAME _____
ADDRESS _____
CITY _____ ZONE _____
STATE _____

**SEND
FREE
CATALOG
305**

CUT OUT AND MAIL TODAY!

HIGH FREQUENCY TWEETER WITH ACOUSTIC LENS



New!

**DIRECT IMPORTATION
MAKES THIS PRICE POSSIBLE!**

- FREQUENCY RESPONSE FROM 2000 CPS TO BEYOND AUDIBILITY
- LOUVERED ACOUSTIC LENS FOR UNIFORM SOUND DISPERSION
- HANDLES 25 WATTS OF POWER
- PRICED EXCEPTIONALLY LOW

14.95

New high frequency tweeter featuring a louvered acoustic lens for uniform sound dispersion and capable of handling up to 25 watts of distortion-free power. The directional tendency of high frequency notes is overcome by the natural wide dispersion angle of the short horn and the acoustic lens which disperses and radiates the high notes smoothly throughout the entire listening area. The lens is detachable for panel mounting, with a separate base for the tweeter furnished for external mounting where desired. Aluminum voice coil has 16 ohms impedance. Size: 4 1/4" long x 3" diameter, lens extends 2 1/2". Requires a crossover network, preferably one with a level control, such as the LN-2. With full instructions. Shpg. wt., 5 lbs.

HW-7 Net **14.95**

LAFAYETTE SENSATIONAL VALUES! IN COMPLETELY WIRED TEST EQUIPMENT at LESS than the PRICE of KITS!



LAFAYETTE SIGNAL GENERATOR

NEVER BEFORE HAS A COMPLETELY WIRED AND TESTED INSTRUMENT OF SUCH ACCURACY AND QUALITY BEEN OFFERED AT SUCH A PRICE!

- FREQUENCY 120 KC TO 260 MC
- 120 KC TO 130 MC ON FUNDAMENTALS
- LABORATORY ACCURACY AND QUALITY

A completely wired and tested instrument not to be confused with units sold in kit form at almost the same price, but with a quality and accuracy of instruments 3 to 4 times its price. Six overlapping ranges generate signals of 120KC - 320KC, 320KC-1000KC, 1MC-3.2MC-11MC, 11MC-38MC and 37MC-130MC all on fundamentals with calibrated harmonics from 120MC to 260MC. Selector switch gives instant choice of ranges. Switch gives choice of internal modulation of 400 CPS or use of any external source at other frequencies. For audio testing the 400 cycle signal can be used separately. Outputs are unmodulated RF, modulated RF and 400 CPS audio. RF output is in excess of 100,000 microvolts and jacks are provided for choice of either high or low RF output. Stability is insured by special circuit design. Has a fine adjustment RF control. AF output is protected by transparent plastic bezel. Common AF terminals for EXT-MOD input and INT-AF for audio tests eliminate need for special AF output connectors. Machine engraved panel lettering. Handsome gray metal case with carrying handle. Measures 6 1/2" x 10" x 4 1/2". Comes complete with pair of leads. AC line cord and plug. Operates on 105-125V 50-60 cycle AC. Shpg. wt., 8 lbs.

22.50

Outputs are unmodulated RF, modulated RF and 400 CPS audio. RF output is in excess of 100,000 microvolts and jacks are provided for choice of either high or low RF output. Stability is insured by special circuit design. Has a fine adjustment RF control. AF output is protected by transparent plastic bezel. Common AF terminals for EXT-MOD input and INT-AF for audio tests eliminate need for special AF output connectors. Machine engraved panel lettering. Handsome gray metal case with carrying handle. Measures 6 1/2" x 10" x 4 1/2". Comes complete with pair of leads. AC line cord and plug. Operates on 105-125V 50-60 cycle AC. Shpg. wt., 8 lbs.


LAFAYETTE LSG-10 SIGNAL GENERATOR

22.50

NEW POCKET AC-DC VOM MULTITESTER

2,000 ohm per volt Sensitivity on both DC and AC

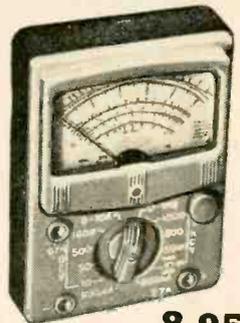- 160 ua 3" METER
- 1% PRECISION RESISTORS
- SILVER CONTACT SELECTOR SWITCH



FULL SCALE RANGES
 DC Volts: 0-10; 0-50; 0-500; 0-1000 Volts—AC
 Volts: 0-10; 0-50; 0-500; 0-1000 Volts—DC Current:
 500 ua and 500 ma—
 Resistance: 0-10K; 0-1 Meg—
 Decibels: -20 to +22;
 +20 to 36 db (0 db =
 0.775 V)—Capacity: 250
 mmd to .2 mfd—.005 mfd
 to 1 mfd—Output Ranges:
 0-10; 0-50; 0-500; 0-1000
 volts

8.95

Best Buy in America! A very accurate and sensitive VOM. This Multitester is a complete instrument (not a kit) with high quality and sensitive 160 microamp meter; 2000 ohm per volt on both AC and DC. Single selector switch, 1% precision resistors, 3" meter. Features extreme versatility, accuracy and ruggedness. In attractive extreme versatility, with metal bottom for ruggedness and shielding. front panel, city range requires 50 volt AC source. Second capacity range requires 10 volt AC source. Size 4 1/4" x 3 1/2" x 1 1/2". Complete with test leads and batteries. Shipping weight 4 lbs.
 RW-27A Complete 8.95

NEW!

LAFAYETTE CAPACITANCE-RESISTANCE TESTER WITH "IN-SET QUICK CHECK"

COMPLETELY WIRED AND TESTED



- TWO INSTRUMENTS IN ONE
- CHECKS ELECTROLYTIC, PAPER, MICA AND CERAMIC CONDENSERS
- 4 DIRECT READING CAPACITY SCALES FROM .00001 MFD TO 1000 MFD
- CHECK FOR OPEN SHORTS, LEAKAGE AND INTERMITTENTS
- 2 RESISTANCE RANGES FROM 100 TO 5 MEGOHM

34.50

Here is a "must" for servicemen and lab technicians. A completely self-contained AC operated capacitance and resistance bridge plus a quick check for in the set testing. Large 5 direct reading scale has 4 ranges of .00001-.005 MFD, .001-.5 MFD, 1-.50 MFD and 20-1000 MFD. Resistance ranges are 100-50,000 OHMS and 10,000 to 5 megohm. Quick check feature enables you to check capacitors for shorts, open or intermittent while in circuit—no need to remove them from the set till you're sure they need replacement. Leakage test switch gives you choice of 25, 150, 250, 350 or 450 volts for checking leakage under correct potential. Separate power factor control with continuous settings from 0 to 50%. Operation is simple and accurate, using a magic-eye tube as the null detector. Attractively finished steel case with etched panel and rounded corners, measures 14 1/2" L x 8 1/4" H x 5" D. Shpg. wt. 19 lbs.

MODEL LC-4

NET 34.50

HIGH SENSITIVITY 20,000 OHM PER VOLT DC 10,000 OHM PER VOLT AC MULTITESTER



LOOK AT THESE FULL SCALE RANGES!

- D.C. Volts: 0-6; 0-30; 0-120; 0-600; 0-1200; 0-6000 Volts—A.C. VOLTS: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts—RESISTANCE: 0-10K; 0-100K; 0-1 Meg; 0-10 Megohms—D.C. CURRENT: 0-60 Microamp; 0-6; 0-60; 0-600 Milliamps—DECIBEL: -20 to +27 db (0 db = 0.774V)—CAPACITY: .005-.01; .005-.15 mfd—INDUCTANCE: 20-2000 millihenry—OUTPUT RANGES: 0-6; 0-30; 0-120; 0-600; 0-1200 Volts

19.95

The new Lafayette high sensitivity Multitester is a complete instrument (not a kit). In addition to its unusual sensitivity of 20,000 OHMS PER VOLT ON D.C. AND 10,000 OHMS PER VOLT ON A.C., and the extraordinary number and scope of its ranges, it is packed with features that would make it cost at least twice as much if made in this country. Uses 1% precision resistors, silver contacts on selector switch, 35 ua 3" meter. Dependable, rugged and accurate. Even the test leads are heavy duty with high voltage insulation. Voltage source required for low capacity range is 120V A.C., for high range capacity and inductance scale is 6V A.C. Attractive plastic front with metal bottom. Size 6 1/4" x 4 1/4" x 2 1/2". Complete with batteries and leads. Shipping weight 4 1/2 lbs.
 RW-30A Singly, Each 19.95
 In lots of 8, Each 19.25

NEW!

LAFAYETTE CAPACITOR-RESISTANCE TESTER

COMPLETELY WIRED AND TESTED



21.50


- COMPLETELY WIRED AND TESTED
- CHECKS ALL TYPES OF CONDENSERS FOR CAPACITY, LEAKAGE, OPEN SHORTS OR INTERMITTENT CONDITION
- DIRECT READING SCALES FROM .00001 TO 1000 MFD AND 100 TO 5 MEGOHMS

A stable and accurate bridge type circuit measures capacitance in 4 ranges of .00001-.005 MFD, .001 to .5 MFD, .1 to 50 MFD and 20 to 1000 MFD. Two resistance ranges of 100-50,000 and 10,000 to 5 megohms. Check leakage under actual load with choice of 25, 150, 250, 350 or 450 volts available by selector switch. Power factor control from 0 to 50%. Checks for leakage, open, short, or intermittent operation. All readings taken directly off scales after setting magic eye to maximum. Completely self-contained power supply. Attractively finished steel case with rounded corners and etched panel. Operates from 110V AC. Size 9 1/2" L x 7 1/2" H x 5 1/4" D. Shpg. wt. 10 lbs.

MODEL LC-15

NET 21.50

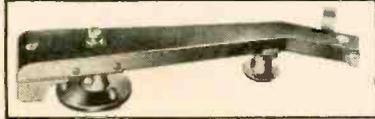VISCOUS DAMPED TRANSCRIPTION TONE ARMS NOW AT THE LOWEST PRICES ANYWHERE



12" VISCOUS DAMPED ARM 11.95

LICENSED UNDER CBS U. S. PATENT NO. 2676806

Here is the finest professional transcription tone arm with its "floating action" at the lowest price ever. Gives dependable stable operation with high compliance and perfect record tracking. Single point jewel bearing support and automatic fluid control. Adapters accommodate all popular cartridges and permit instant plug-in cartridge change. Gray hammettone finish. Shpg. wt., 2 1/2 lbs.

PK-90—12" Transcription Tone ArmNet 11.95



16" VISCOUS DAMPED TRANSCRIPTION TONE ARM

NOW ONLY 17.95 LICENSED UNDER CBS U. S. PATENT 2676806

A 16" viscous damped arm at an unbelievable low price. An exclusive sealed unit eliminates possibility of silicone leakage. Features single point pivot mounting, precision pickup arm adjustment controls, and plug-in adapters for all popular cartridges. Shpg. wt., 3 1/2 lbs. PK-170—16" Transcription Tone ArmNet 17.95



TRANSCRIPTION-TYPE MANUAL PLAYER

with TONE ARM and TWO PLUG-IN HEADS

- MAGNETIC BRAKE FOR FINE ADJUSTMENT OF EACH SPEED
- 4-POLE, HEAVY DUTY TRANSCRIPTION-TYPE MOTOR
- ACCOMMODATES ALL POPULAR CARTRIDGES
- STYLUS WEIGHT ADJUSTMENT SCREW ON TONE ARM

All the important features of professional transcription players have been incorporated in this precision turntable. Extremely smooth and quiet heavy duty 4-pole motor plays 78, 45 and 33 1/3 RPM records. Exclusive magnetic brake, controlled by knob on base plate, permits instantaneous fine adjustment of each speed. Stroboscope disc included checks speeds. Speed selector safety switch protects mechanism by making it necessary to pass through OFF position when switching from one speed to another. 10" weighted turntable has rubber traction mat.

Mounting plate has pickup rest and ON-OFF switch. Size 12-15/16" left to right. 10 7/8" front to rear. Requires 2 3/4" clearance below motor board and 3" above. With AC line cord, 2 plug-in heads, output cable, 45 RPM adapter. For 105-120V, 60 cycles AC. Shpg. wt., 12 lbs. (NOTE: For protection in shipping, tone arm is separate. Just fasten to mounting plate.)

- PK-160—Less cartridge and baseNet 25.95
- PK-162—Wood base for PK-160. Shpg. wt., 5 lbs.Net 3.95
- PK-163—Unfinished mounting board only. Shpg. wt., 1 lb.Net .95

LAFAYETTE RADIO 165-08 Liberty Ave. DEPT JJ-2 JAMAICA 33; N. Y. include postage with order.

It's New! Send for this

FREE

booklet today!

see

what the

rapidly

expanding

field of


ELECTRONICS

offers

you

- BETTER JOB
- BETTER PAY
- PROMOTION
- GREATER SECURITY
- GREATER CONFIDENCE
- BETTER LIVING FOR YOU AND YOUR FAMILY

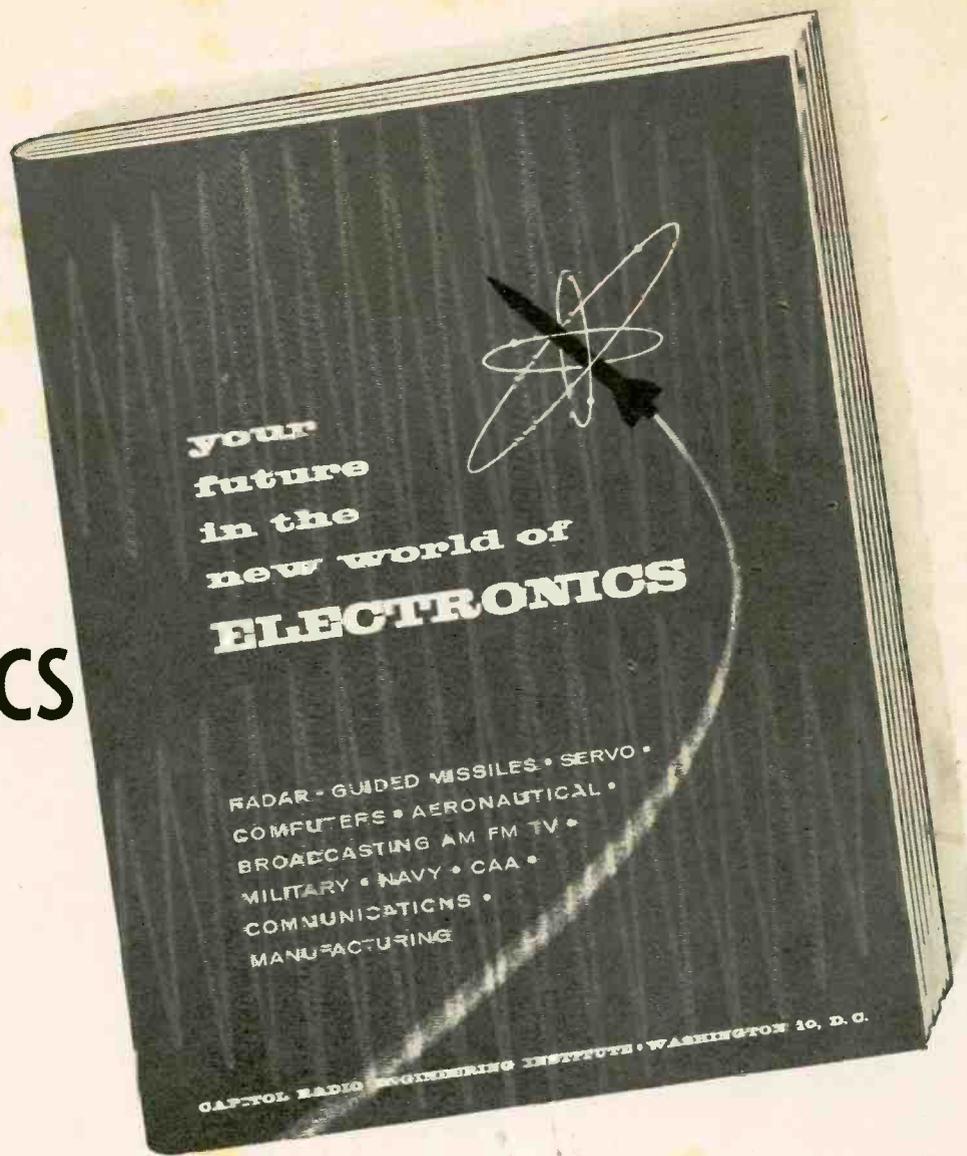All these benefits can be yours if you act now! Take that first big step this minute—No obligation whatsoever!



TAKE A MINUTE TO MAIL THIS COUPON FOR FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula—Founded 1927
Dept. 1410-W, 3224 16th St., N.W., Washington 10, D.C.

Please send me your course outline and FREE Illustrated Booklet "Your Future in the New World of Electronics" describing opportunities and CREI home study courses in Practical Electronic Engineering Technology.

- CHECK FIELD OF GREATEST INTEREST
- Electronic Engineering Technology
 - Broadcast (AM, FM, TV) Engineering Technology
 - Television Engineering Technology
 - Aeronautical Electronic Engineering Technology

Name..... Age.....

Street

City..... Zone..... State.....

CHECK: Home Study Residence School Korean Veteran

To help us answer your request intelligently, please give the following information:

EMPLOYED BY.....

TYPE OF PRESENT WORK.....


SCHOOL BACKGROUND.....

ELECTRONICS EXPERIENCE.....

IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED?

Electro-Voice® Variable-D Cardioid Microphones

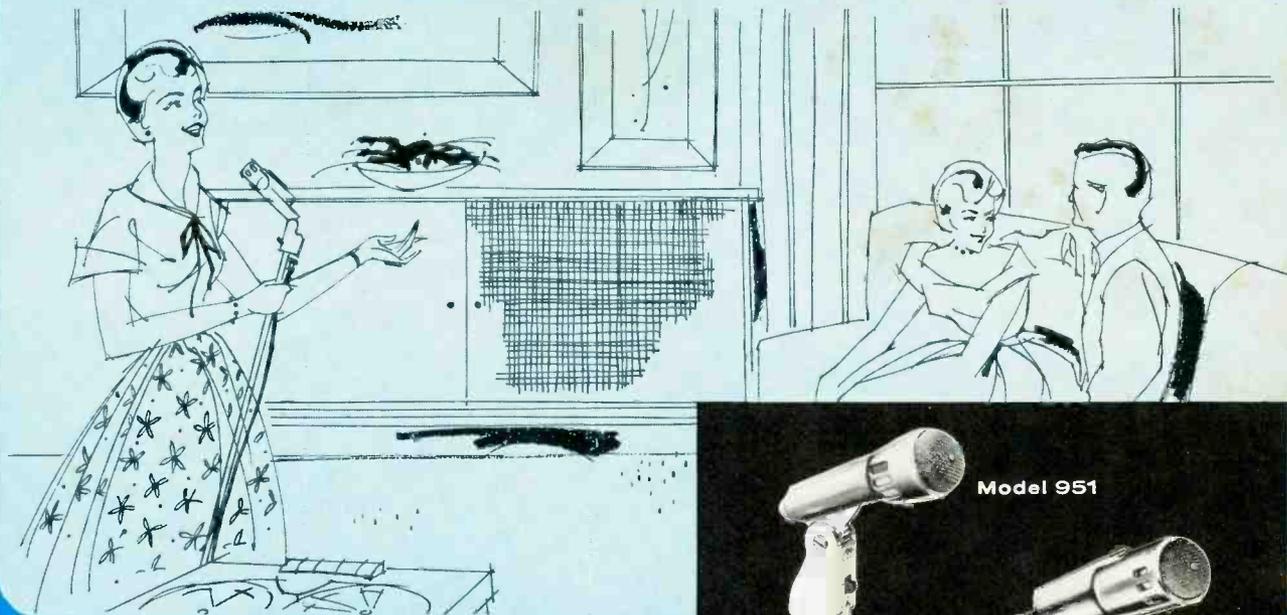Record the Quality You Want . . . and that's ALL!



You'll make professional-quality, high-fidelity tape recordings with an Electro-Voice microphone — the choice of broadcast and TV engineers!

The secret of success is the unique E-V Variable-D, which stops background sound you *don't* want, picks up the sounds you *do* want. Work close — you'll record no "boom." Pick up from a distance — the sound is clean and free from "roominess." The single moving element is E-V's exclusive, virtually indestructible Acoustalloy diaphragm.

NEW Model 951 Crystal Cardioid—Professional quality at a Modest Price

This newest addition to the E-V line uses the same Variable-D principle as E-V's broadcast cardioids to give you uniform directivity of pickup and high discrimination against unwanted sound. Response is 50 to 11,000 cps. Has chrome-finished pressure-cast case, On-Off switch. Just \$49.50, list, less stand.

Model 664 Cardioid Dynamic—Finest of its Kind!

Without a doubt, Model 664 is the world's best general-purpose cardioid! It's guaranteed to outperform all others. Unidirectional high fidelity Model 664 gives you highly directional sound selectivity, reduces pickup due to ambient noise up to 50%, has smooth, peak-free response at all frequencies from 40 to 15,000 cps. Convenient on-off switch, chrome finish. List, \$85, less stand.

Electro-Voice manufactures the most complete high-fidelity product family...speakers, speaker systems, speaker enclosures, amplifiers, preamps, tuners, phono cartridges, do-it-yourself enclosure kits and microphones. Available at leading high-fidelity distributors.


For the finest microphone, see your hi-fi dealer. For all the facts, write us for "The ABC's of Microphones," Booklet W-710




Model 951



Model 664

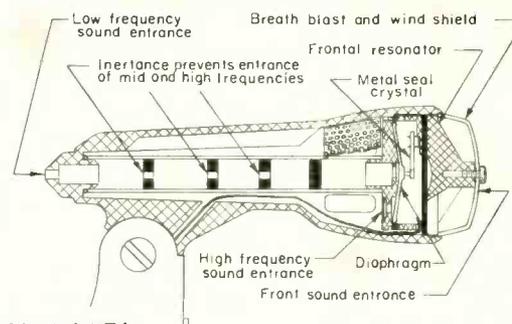


Model 951

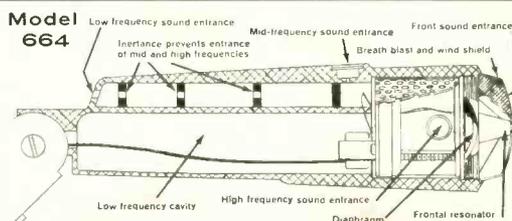

Model 664

Electro-Voice®

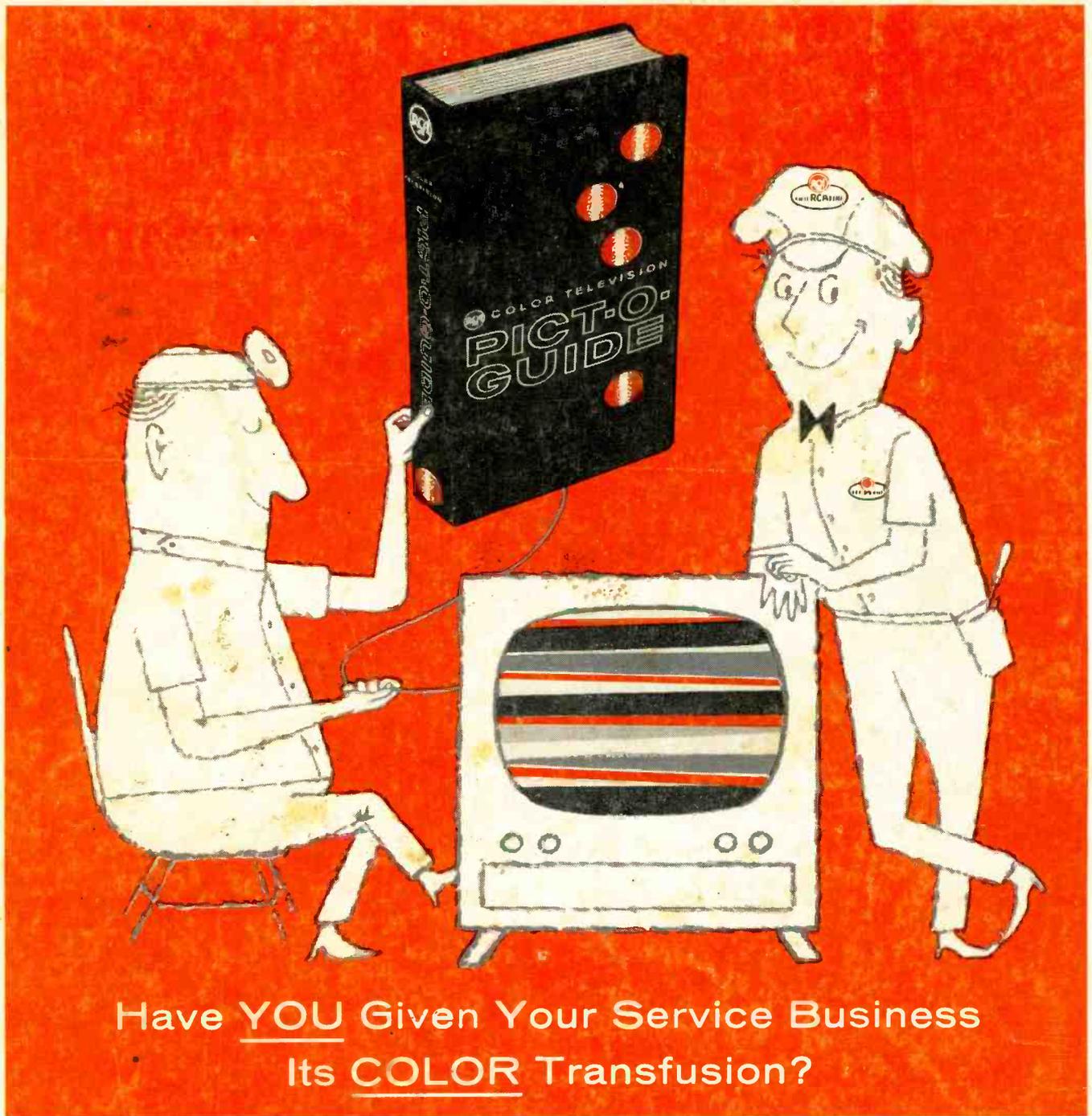ELECTRO-VOICE, INC. BUCHANAN, MICHIGAN
 Export: 13 East 40th Street, New York 16, U. S. A.
 Cables: ARLAB



Have YOU Given Your Service Business
Its COLOR Transfusion?

This TV service-dealer is "hep". He's getting ready now for healthy, wealthy business. "Doctor", of course, is his RCA Tube Distributor. And he'll give you your "booster shot", the new RCA PICT-O-GUIDE for COLOR-TV, with your order for RCA TUBES—free of extra charge!

Written by RCA's well-known TV-service authority John R. Meagher (who also wrote the famous RCA Pict-O-Guide series for black-and-white TV), this volume is profusely illustrated with full-color photos, packed with step-by-step alignment and trouble-shooting instructions, and loaded with labor- and time-saving short cuts for *profitable color-TV servicing*.

See for yourself what other service technicians have learned—*color-TV servicing has been simplified!* See your RCA TUBE DISTRIBUTOR with your order today!



**RCA COLOR-TV
PICT-O-GUIDE CONTAINS
SECTIONS ON:**

- Color Mixing • RCA Compatible Color TV System • Purity • Convergence • Gray-Scale Tracking
- Color Operating Controls • Antenna Considerations • RF-IF Bandpass Alignment • Color Test Equipment • Color-Bar Patterns
- Troubleshooting • Signal Tracing • Interference • "Green Stripe" Test Signals



RECEIVING TUBES

RADIO CORPORATION OF AMERICA
© Electron Tube Division Harrison, N. J.