

Radio-Electronics

DECEMBER



TELEVISION • SERVICING • HIGH FIDELITY

HUGO BERNBACK, Editor

Three Ignition-Operated
Tachometers

Ultrasensitive
3-Transistor Radio

Electronic Timer
Is Easy to Build

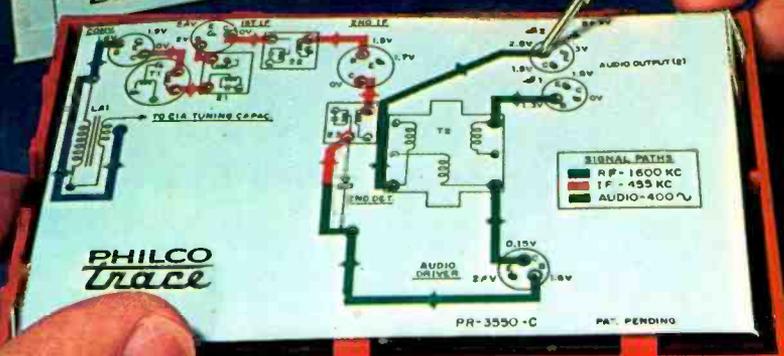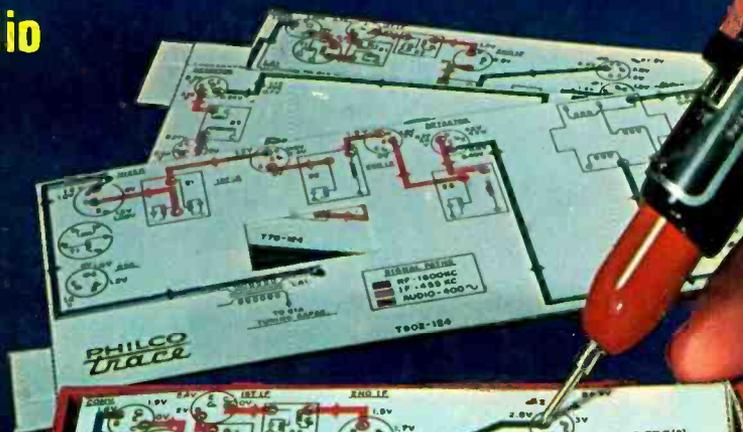

50c

CARL S TOWNSEND 12-63
11636 ROCKLAND
DETROIT 39 MICHIGAN

"Trace" Cards

Have 310 • Will Travel...

Light!

Burton Browne Advertising

- Hand size, but with the features of a full-size V-O-M.
- 20,000 ohms per volt DC; 5,000 AC.
- EXCLUSIVE SELECTOR SWITCH speeds circuit and range settings. The first miniature V-O-M with this exclusive feature for quick, fool-proof selection of all ranges.
- SELF-SHIELDED Bar-Ring Instrument; permits checking in Strong Magnetic Fields.
- Fitting interchangeable test prod tip into top of tester makes it the common probe, thereby freeing one hand.
- Unbreakable plastic meter window.
- BANANA-TYPE JACKS—positive connection and long life.



MODEL 100



Actual Size
\$34.50
Net
Carrying Case
\$3.20



The most comprehensive test set in the Triplet line is Model 100 V-O-M Clamp-On-Ammeter Kit, now available at distributors. The world's most versatile instrument—a complete accurate V-O-M plus a clamp-on-ammeter with which you can take measurements without stripping the wires. Handsome, triple-purpose carton holds and displays all the components: Model 310 miniaturized V-O-M, Model 10 Clamp-On-Ammeter, Model 101 Line Separator, No. 311 extension leads and a Leather Carrying-Case, which neatly accommodates all the components. Model 101 literally makes it possible to separate the two sides of the line when using Model 10. Extension leads permit use of Model 10 at a distance from the V-O-M. Complete Model 100 is only \$59.50.




For full information see your Triplet distributor
or write

TRIPLET ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO



PANEL METERS

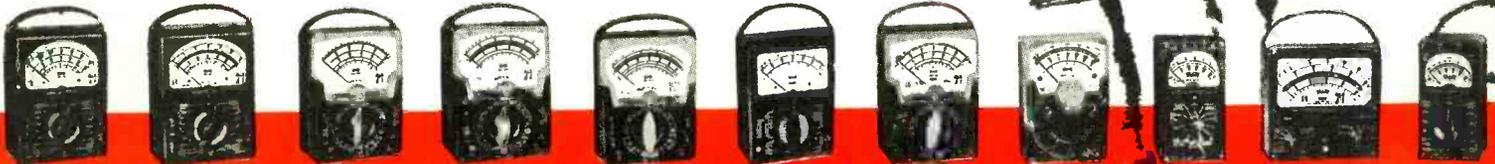AND A VOM FOR EVERY PURPOSE AND EVERY PURSE



630 630-A 630-PL 630-APL 630-NA 630-T 631 310 666-HH 625-NA 666-R

Why are more Service-Dealers Switching to **JFD HI-FI TV ANTENNAS?**



The Businessman in the Serviceman suit knows five million TV antennas are in need of replacement. For his installation, he relies on the superior performance and quality of JFD HI-FI Antennas to guarantee complete customer satisfaction—guard his reputation.

JFD

HI-FI HELIX HI-FI BANSHEE HI-FI FIREBALL



because

they know 5 million antennas need replacement—that JFD HI-FI TV antennas assure them a bigger share of this profitable market.

because

JFD all-out advertising sells for them in powerful national mass media—such as Look, TV Guide, Successful Farming, Farm Journal, Progressive Farmer.

because

JFD is the total antenna line with the right model, at the right price for every location—does the most for them in mile-shrinking performance and customer confidence.

because


JFD sales stimulators such as cloth patches, decals, mobiles, banners, displays and direct mail give them the complete package to sell new customers.

HOW MUCH INSTALLATION BUSINESS ARE YOU LOSING BY NOT SWITCHING TO JFD? THE TV ANTENNA LINE AMERICA KNOWS BEST!


HI-FI HELIX
Silver or Gold Anodized



HI-FI BANSHEE
Silver or Gold Anodized

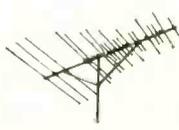

HI-FI FIREBALL
Silver or Gold Anodized

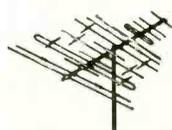

THE BRAND THAT PUTS YOU

JFD

IN COMMAND OF THE MARKET

JFD ELECTRONICS CORPORATION, Brooklyn 4, New York
JFD International, 15 Moore Street, New York, New York • JFD Canada, Ltd., 51 McCormack Street, Toronto, Ont., Canada

Radio-Electronics

DECEMBER, 1960

Formerly RADIO-CRAFT — Incorporating SHORT WAVE CRAFT — TELEVISION NEWS — RADIO & TELEVISION*

OVER FIFTY YEARS OF ELECTRONIC PUBLISHING

Hugo Gernsback
..... Editor and Publisher

M. Harvey Gernsback
..... Editorial Director

Fred Shunaman
..... Managing Editor

Robert F. Scott, W2PWG
..... Technical Editor

Larry Steckler
..... Associate Editor

I. Queen
..... Editorial Associate

Elizabeth Stalcup
..... Production Manager

Fernando Martinez
..... Art Director

Wm. Lyon McLaughlin
..... Tech. Illustration Director

Fred Neinast
..... Art Associate

Lee Robinson
..... Director, Advertising Sales

John J. Lamson
..... Eastern Sales Manager

G. Aliquo
..... Circulation Manager

Adam J. Smith
..... Director, Newsstand Sales

Robert Fallath
..... Promotion Manager

editorial

27 How Far Amplification—*Hugo Gernsback*

electronics

- 28 Integrating Timer, A Versatile Unit Easily Built—*John Potter Shields*
- 54 Build at Least One of These Ignition-Operated Tachometers—*Alex M. Schotz*
- 56 A Look at the Electronic Strain Gauge—*Arthur S. Kramer*
- 58 Electronic "Auxiliary Heart"
- 81 Electronics Classroom
- 99 Watch That Tube Replacement—*J. W. Essex*

television

- 30 Taming the Video If System—*Wayne Lemons*
- 51 Servicing TV Distribution Systems, Part II—*Jack Beever*
- 63 TV Service Clinic—*Conducted by Jack Darr*
- 88 TV Quiz—*Bob Eldridge*

audio-high fidelity

- 33 Puzzled About Output Transformers?—*Norman H. Crowhurst*
- 40 Preamp Input Circuit
- 45 Use R-E Printed-Circuit Board to Construct a Transistor Stereo Preamp—*Daniel Meyer*
- 53 Stereo PA at Newport—*Jack Allison*
- 82 New at the New York Hi-Fi Show

industrial electronics

- 35 Transitone Locates Hidden Wiring—*Harry D. Parker*
- 70 Be Careful With Ignitrons—*Allen H. Lytel*

what's new

- 44 Pictorial Reports of New Developments

test instruments

- 36 "Trace" Speeds Transistor Radio Servicing—*Larry Steckler*
- 59 Modern Picture-Tube Testers—*William Kelvin*
- 90 Capacitance Meter Makes a Worthwhile Project—*J. H. Sutton*

radio

- 39 Construct an Ultra-Sensitive 3-Transistor Radio—*Joseph Amorose and Edward Hoffmeister*
- 41 The Old-Timer Gives a Safety Lecture—*Jack Darr*
- 77 Make-It-Yourself Remo-Nemo for Remote Pickups—*Harold Reed*
- 86 Small Radio Uses an Original Transistor Amplifier—*Anthony P. Ciardi*

the departments

- | | | |
|----------------------------|----------------------------------|-------------------------|
| 130 ANNUAL INDEX for | 125 New Literature | 117 Noteworthy Circuits |
| Radio-Electronics for 1960 | 113 New Patents | 110 Technicians' News |
| 122 Business and People | 104 New Products | 115 Technotes |
| 18 Correspondence | 100 New Tubes and Semiconductors | 120 Try This One |
| 128 New Books | 6 News Briefs | 127 50 Years Ago |

Average Paid Circulation
Over 163,000



ON THE COVER

(Story on page 36)

Troubleshooting with Trace reveals no voltage at the audio output transistor base—a good lead toward spotting the trouble in this transistor radio.

Color original
by Philco

Radio-Electronics is indexed in
Applied Science & Technology Index
(Formerly *Industrial Arts Index*)

Radio-Electronics December, 1960, Vol. XXXI, No. 12. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class postage paid at Mt. Morris, Ill. Copyright 1960 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.

Subscription Rates: U.S., U.S. possessions and Canada, \$5.00 for one year; \$9.00 for two years; \$12.00 for three years. Pan-American countries \$6.00 for one year; \$11.00 for two years; \$15.00 for three years. All other countries \$6.50 a year; \$12.00 for two years; \$16.50 for three years.

Subscriptions: Address correspondence to Radio-Electronics, Subscriber Service, 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.

Gernsback Publications, Inc. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.

Advertising Representatives: Los Angeles: Harker-Husted-Coughlin, 400 South Alvarado St., Tel. DUmalkirk 7-2328. San Francisco: Harker-Husted-Coughlin, 444 Market St., Tel. GARfield 1-0151. Chicago: 8631 East Prairie Road, Skokie, Ill. Tel. OLRehard 5-3740.


Foreign Agents: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4.

Postmaster: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y. *Trademark registered U. S. Pat. Office.

BREAK THROUGH TO HIGHER PAY

in ELECTRONICS

TV-RADIO

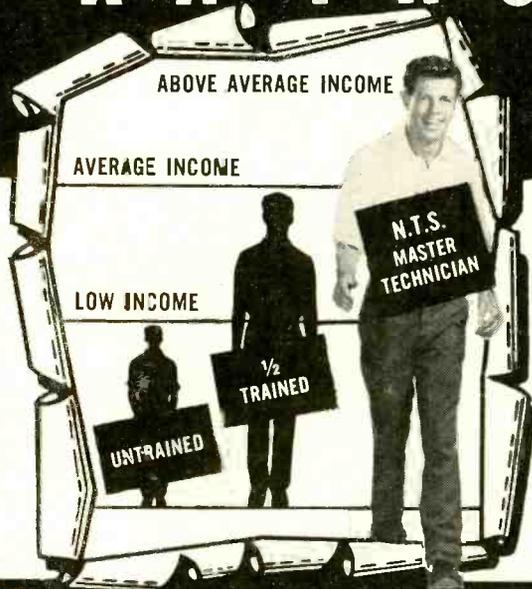

START NOW! Break through the Earning Barrier that stops half-trained men. N.T.S. "All-Phase" training prepares you — at home in spare time — for a high-paying CAREER in Electronics — TV — Radio as a MASTER TECHNICIAN. One Master Course at One Low Tuition trains you for unlimited opportunities in All Phases: Servicing, Communications, Preparation F.C.C. License, Broadcasting, Manufacturing, Automation, Radar and Micro-Waves, Missile and Rocket Projects.

A more rewarding job... a secure future... a richer, fuller life can be yours! As an N.T.S. MASTER TECHNICIAN you can go straight to the top in industry... or in your own profitable business.


You work on actual job projects



SUCCEED IN MANY HIGH-PAYING JOBS LIKE THESE...

- TV-Radio Sales, Service and Repair
- Profitable Business of Your Own
- Communications Technician — F.C.C. License
- Hi-Fi, Stereo & Sound Recording Specialist
- TV-Radio Broadcasting Operator
- Technician in Computers & Missiles
- Electronics Field Engineer
- Specialist in Microwaves & Servomechanisms
- Expert Trouble Shooter
- All-Phase Master Technician

19 BIG KITS YOURS TO KEEP

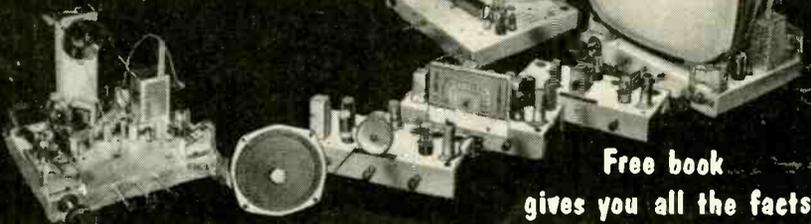

Free book gives you all the facts

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905
4000 SO. FIGUEROA ST., LOS ANGELES 37, CALIF., U.S.A.
Write Dept. RG-120



RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, start NOW in our big, modern Shops and Labs. Work with the latest Auto and Diesel engines — all types — fuel injection, automatic transmissions, all power equipment — most complete facilities offered by any school. Expert, friendly instructors. Graduate Employment Service. Help in finding home near school — and part time job while you learn.

WRITE FOR SPECIAL RESIDENT SCHOOL CATALOG AND INFORMATION



ACCREDITED MEMBER
... the only nationally recognized accrediting agency for private home study schools.

N.T.S. Shop-Tested HOME TRAINING is Better, More Complete, Lower Cost... and it is your key to the most fascinating, opportunity-filled industry today!

YOU LEARN QUICKLY AND EASILY THE N.T.S. SHOP-TESTED WAY

You get lessons, manuals, job projects, unlimited consultation, graduate advisory service.

You build a Short Wave-Long Wave Superhet Receiver, plus a large-screen TV set from the ground up, with parts we send you at no addi-

tional cost. You also get a Professional Multitester for your practical job projects.

EARN AS YOU LEARN... WE SHOW YOU HOW!

Many students pay for entire tuition — and earn much more — with spare time work they perform while training. You can do the same... we show you how.

SEND FOR INFORMATION NOW... TODAY! IT COSTS YOU NOTHING TO INVESTIGATE.

N.T.S. HOME TRAINING is

- Classroom Developed
- Lab-Studio Planned
- Shop-Tested
- Industry-Approved
- Specially Designed for Home Study



MAIL COUPON NOW for FREE BOOK and ACTUAL LESSON

NO OBLIGATION! NO SALESMAN WILL CALL

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

Mail Now To
National Technica Schools, Dept. RG-120
4000 S. Figueroa St., Los Angeles 37, Calif.

Please rush FREE Electronics-TV-Radio "Opportunity" Book and Actual Lesson. No Salesman will call.

Name _____ Age _____
Address _____
City _____ Zone _____ State _____


Check here if interested ONLY in Resident Training at Los Angeles.
VETERANS: Give date of discharge _____

News Briefs

New Compact Cyclotron Is Office-Desk Size

A 2,000,000-volt cyclotron no larger than an office desk was presented to Pomona (Calif.) College by trustee Frank Seaver as part of the college's 73rd Founder's Day ceremony. It was built by Hughes Aircraft Co. The cyclotron speeds up charged particles in a pillbox-shaped chamber. The particles travel in circular paths and get two accelerating "kicks" on each revolution.

Technically, a cyclotron is a vacuum chamber containing two semicircular hollow metal accelerating electrodes called dees (one shown in drawing). Particles of hydrogen gas in the chamber are ionized by a hot filament near the center (at end of two-wire line). Dees are charged alternately positive and negative by the rf oscillator in the cage at upper left, which feeds dees through a large coax or dee-stem. Ions move toward the dee that is negative at the instant and are given a circular motion by the powerful electromagnetic field generated by the coils of ½-inch busbar above and below the chamber (top coil shown). The voltage and frequency are so chosen that, as the particle leaves one dee and enters the other, it finds a repellent positive charge behind it and an attractive negative one ahead

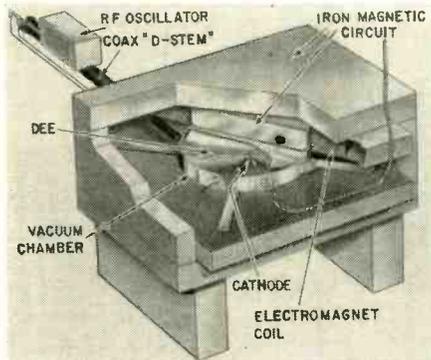

of it. Thus it travels in a spiral and keeps on gaining speed till it reaches the outside wall, where it escapes at atom-smashing velocity through an electronic gate into the target chamber.

This cyclotron can produce protons of 2,000,000 electron-volts or deuterons at 4 mev energy at currents up to 25 μ amp. The accelerating voltage is 17.5 kv at 13.8 mc, and the magnetic field 9 kilogauss. Power consumed is 11 kva at 220 volts.

Ball Lightning for Defense?

Electronic fireballs of highly concentrated charged particles (plasma) might be used to destroy missiles, physicists of the Armour Research Foundation believe. The balls would be kept active and be guided

by a concentration of radar beams. Data on the subject is being studied by the Air Force, the foundation stated.

The work is based on speculation by Peter Kapitsa, the leading Russian nuclear scientist, who theorizes that a natural lightning ball is a mass of highly ionized plasma fed continuously from outside resonance absorption of intense radio waves. He believes that artificial lightning balls can be created by a powerful source of sustained radio waves focused into a small volume of space. Natural lightning balls are most often from 10 to 20 cm in diameter, which would indicate wavelengths between 35 and 70 cm, Dr. Kapitsa stated.


Courier Satellite Is World's First Space Station

A genuine radio station in space went into action with the launching of the Courier satellite. Intended to act chiefly as a delayed relay station, storing information sent to it for later release, it can, of course, act as a simultaneous relay as well.

The satellite system was conceived by the Army Signal Research and Development Laboratory at Fort Monmouth, N. J., under direction of the Advanced Research Projects Agency of the Department of Defense in Washington, D. C. The satellite itself was designed and developed in Palo Alto, Calif., at the Western Development Laboratories of Philco Corp., in accordance with specifications by the directing agencies.

The Courier has two complete radio systems. One, operating at vhf, is intended for tracking and locating; the other, in the microwave region, for actual communication.

The vhf transmitter sends a 50-mw signal. When orbiting, the transmitter is on for 1 second, then off for 9. The receiver follows with a 1-second listening period. When the satellite's signal is picked up by a ground station, a command signal is sent and it goes into continuous action, sending telemetered data as to the condition of the satellite and electrical equipment. At the same time, it turns on the microwave equipment. In all, 35 items are telemetered, ranging from battery voltage and signal strengths to satellite temperature. The telemetry information is sent by a 1.5-watt transmitter. There are two of these, to assure greater reliability. There

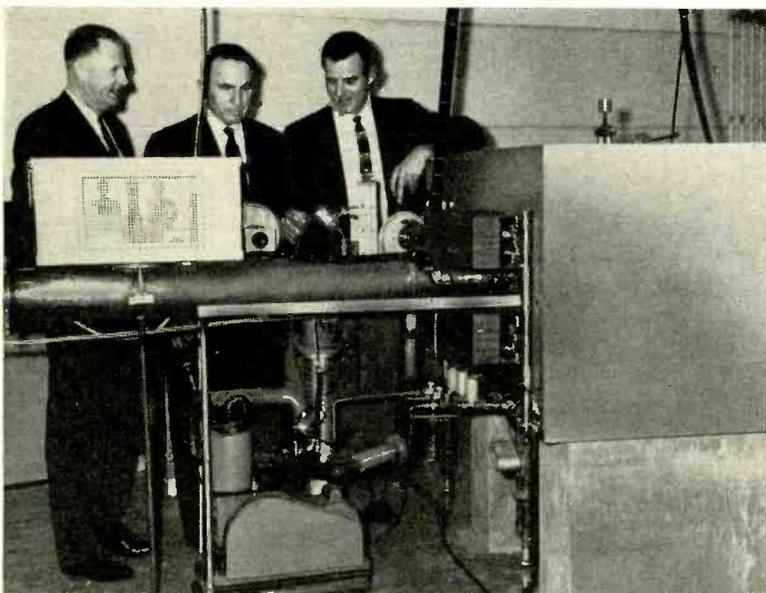

The cyclotron and auxiliary apparatus. The semi-circular chambers, or "dees", are in the huge iron-block electromagnet at right. The charged atom-smashing particles strike targets inserted at the right face of the block, not visible in the photograph. Viewers from left to right are—Dr. B. Wilson Lyon, president of Pomona College; Frank Seaver, college trustee who donated the machine, and Dr. Edward M. Fryer, acting chairman of the college's physics department.



NO ADVANCED EDUCATION NEEDED!

NO PREVIOUS TECHNICAL EXPERIENCE REQUIRED!

MEN 17-55

Prepare now to enter one of the many profitable branches of

ELECTRONICS

SEND FOR FREE FACTS!

The day the first Satellite spiraled into outer space will be known to thousands of men throughout the United States and Canada as "Opportunity Day" — because it brought to light the tremendous possibilities that the field of Electronics holds for the man who seeks a better job or a business of his own.

One of the great things about the giant field of Electronics is the fact that even a man who does not have an advanced education or previous technical experience can prepare for many profitable opportunities in his spare time at home . . . or, if he desires, he may attend our well-equipped CHICAGO or TORONTO laboratories.

If you seek a better job or a business of your own, why don't you fill in the coupon below for FREE facts?

Make "Satellite Day" your "Opportunity Day," too!

DRAFT AGE?

We have valuable information for every man of draft age; so if you are subject to military service be sure to check the coupon.

LIVE-WIRE EMPLOYMENT SERVICE

Through long-established contacts with well-known employers, DeVry Tech's Placement Department has helped many men toward better jobs in Communications, Guided Missile Control, Radar, Automation, Television, Instrumentation, etc. The service is free to graduates.

SEND for 2 FREE BOOKLETS

We'll give you a free copy of 2 interesting booklets, "Electronics in Space Travel" and "Pocket Guide to Real Earnings." See for yourself how you may take advantage of the opportunities in this fast-growing field.

Get into One of Today's Fastest Growing Fields!

IN YOUR SPARE TIME AT HOME OR IN OUR CHICAGO OR TORONTO LABORATORIES.

Look at these Job Opportunities!

- Radar • Guided Missile Control
- Television • Microwaves
- Communications • Radio
- Industrial Electronics • Computers
- Automation Electronics • Broadcasting

WILL NOT INTERFERE WITH PRESENT JOB!

EARN WHILE YOU LEARN!



DeVRY Technical Institute

CHICAGO • TORONTO

Accredited Member of National Home Study Council



"One of North America's Foremost Electronics Training Centers"

MAIL COUPON TODAY!

DeVRY TECHNICAL INSTITUTE
4141 Belmont Avenue, Chicago 41, Ill. Dept. RE-12Q

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunities (check one or more):

<input type="checkbox"/> Space & Missile Electronics	<input type="checkbox"/> Communications
<input type="checkbox"/> Television and Radio	<input type="checkbox"/> Computers
<input type="checkbox"/> Microwaves	<input type="checkbox"/> Broadcasting
<input type="checkbox"/> Radar	<input type="checkbox"/> Industrial Electronics
<input type="checkbox"/> Automation Electronics	<input type="checkbox"/> Special "Short Courses"

Name _____ Age _____

PLEASE PRINT

Address _____ Apt. _____

City _____ Zone _____ State _____

Check here if you face military service.
Canadian residents: Write DeVry Tech of Canada, Ltd.,
970 Lawrence Avenue West, Toronto 19, Ontario 2038

TUBES YOUR CUSTOMERS CAN TRUST


Give your customers tubes they can trust. Give them Sonotone miniaturized electronic tubes. Produced under the highest quality-control standards... rigorously tested to assure superior performance even under extreme conditions. In fact, Sonotone reliable tubes are being used right now in space and military vehicles. Over 150 different types available... for commercial, entertainment and military purposes.

Sonotone, for quality tubes you can rely on.

Sonotone PROB

Electronic Applications Division, Dept. T2-120
ELMSFORD, NEW YORK

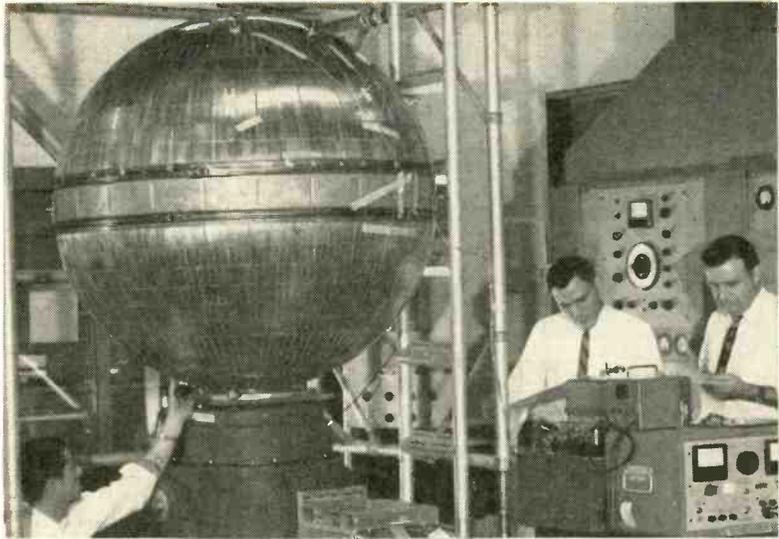Leading makers of rechargeable batteries, phono cartridges, speakers, microphones, tape heads and electronic tubes.
In Canada, contact Atlas Radio Corp., Ltd., Toronto



The satellite is checked for performance under simulated launching conditions.

are also two 50-mw "acquisition" transmitters.

The satellite has four 5-watt microwave transmitters. Two of them operate at a time, tuned to slightly different frequencies and connected to different antennas. Four receivers operate together. The signals received over the microwave link can be used to modulate the microwave transmitter, relaying the message to a second ground station, or can be stored. The satellite has five tape recorders to handle information from high-speed teletype machines or other sources. The information is transmitted backward on the rewind cycle of the tape, and is reversed again by being recorded and played back by a tape recorder at the ground station.

Power is supplied by the 19,000 solar cells that cover more than 70% of the total area of the sphere. The cells are hooked up in series-parallel to deliver 32 volts to a nickel-cadmium storage battery. Diodes between the batteries and the solar-cell network prevent reverse current. Diodes are also inserted between each 84-cell unit of the solar battery and the common bus, since cells on the dark side of the sphere can dissipate considerable leakage current.

BBB Cites Electronics Complaints

Third place in the national complaints-by-customers marathon went last year to the home electronic devices field, Kenneth B. Wilson of the National Better Business Bureau told the EIA service committee at its recent quarterly meeting. Leader of the pack was the home-improvement field, runner-up the major household appliance industry.

Service technicians will be pleased to hear that the larger number of consumer electronic complaints were directed at the manufacturer, and that many against the technician were based on customer misunderstanding of manufacturers' warranties.

Wilson offered the following suggestions to the manufacturers' service committee:

Ship only pretested products.

Educate the public to the nature and limits of warranties.

Limit ad claims to the product's field performance; step up replacement parts availability.

Keep the service industry better informed on products.

Recognize and correct "bugs" promptly.

New Maser Amplifies Light

A true amplifier of light was demonstrated by Bell Telephone Laboratories in early October. Unlike light intensifiers (sometimes called light amplifiers), the apparatus actually uses light to stimulate light, much in the manner of radio waves in a regenerative radio circuit.

A maser is a circuit in which radiation from atoms is stimulated. (Maser = Microwave Amplification by Stimulated Emission of Radiation.) In the optical maser, light is radiated as microwaves were in the earlier maser (RADIO-ELECTRONICS, June, 1955).

The optical maser depends upon the same principle as earlier ones, that atoms which absorb power from radiation are "excited" or raised to a higher energy level and then radiate energy if they drop back to their original level.


The optical maser is a rod of ruby, with chromium atoms introduced as controlled impurities. When excited by bright bluish light from a photo-flash tube (see illustration), these chromium atoms are excited to a higher energy level, decaying back to the original level in two steps. The first of these steps is very rapid; the second a more stable condition from which the atoms, when they drop back to their original level, fluoresce or emit a deep red light.

The light emitted by the first few atoms stimulates others to emit. The ends of the ruby rod are silvered to act as reflectors so that, when a ray

ALLIED value-packed 1961

444-PAGE ELECTRONICS CATALOG

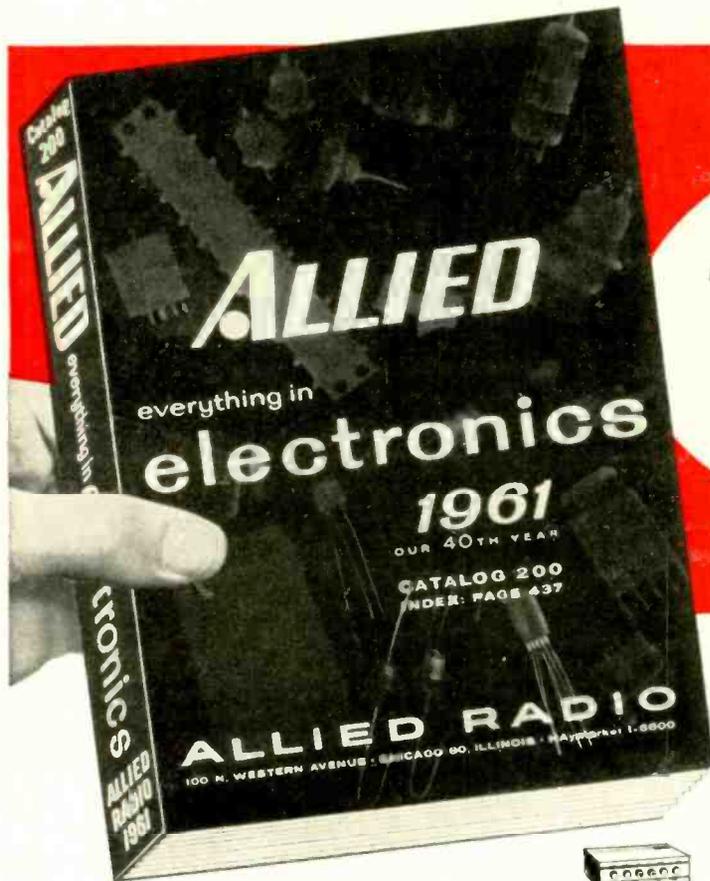including products available only from Allied



complete
up-to-date

free

send for it today!

SAVE MOST ON EVERYTHING IN ELECTRONICS

- Newest Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Recorders & Supplies
- Newest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters, and Station Gear
- Citizen's Band 2-Way Radio
- Test and Laboratory Instruments
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books



BUY ON EASIEST TERMS ONLY \$2 DOWN

Yes, only \$2 down on orders up to \$50; only \$5 down on orders up to \$200; only \$10 down over \$200. Up to 24 months to pay.

ALLIED Exclusives:

MONEY-SAVING KNIGHT-KITS®—truly the very best in build-your-own electronic equipment—designed to save you money, easiest to assemble—the only kits offered with Free Inspection Privilege. See the complete selection of Stereo hi-fi kits, Hobbyist kits, Test Instrument and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

KNIGHT® STEREO HI-FI—comparable to the best in quality and performance, yet priced far lower in cost. Select super-value KNIGHT components or complete systems and save most. Also see the largest selection of famous-name hi-fi components and money-saving ALLIED-recommended hi-fi systems.

ALLIED RADIO

our 40th year

**SATISFACTION GUARANTEED
OR YOUR MONEY BACK**

World's Largest Electronic Supply House

Get every buying advantage at ALLIED: lowest money-saving prices, fastest shipment, expert personal help, easiest-pay terms, satisfaction guaranteed or your money back.

free

the most complete
electronics catalog!



ALLIED RADIO, Dept. 2-M
100 N. Western Ave., Chicago 80, Ill.


Send FREE 1961 ALLIED Catalog:

Name _____

Address _____


City _____ Zone _____ State _____

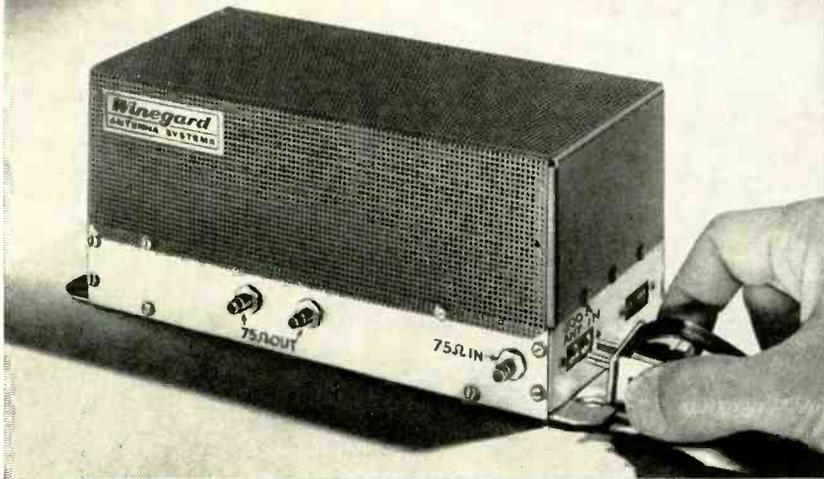*More Signal
Power with Winegard
TV Amplifiers and
Booster Couplers!*



New Precision Amplifier A-400 drives 1 to 30 TV sets. You get up to 26db gain on TV and FM bands with the Winegard A-400. Has four 6FY5 neutroelectrode tubes with extremely low noise characteristics. Dual 75 ohm outputs—300 ohm balanced input with no-strip disconnect plug and 75 ohm coaxial input. Unit completely fused. Finest amplifier in its class—\$79.95.

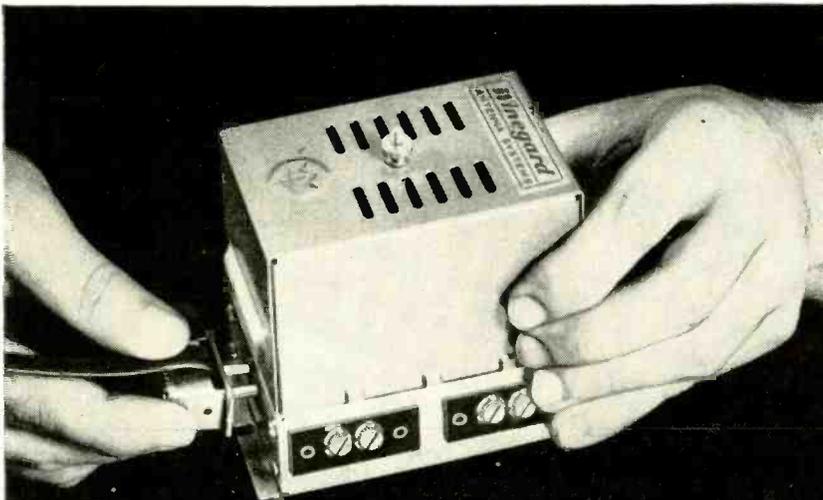Booster Coupler WBC4—operates 1 to 4 TV and FM sets. Delivers up to 12.5 db gain all channels on one set. Operates 2, 3 or 4 sets with up to 6 db gain for each set. Powerful 6DJ8 tube, shielded and protected. 4 sets of no-strip lead-in terminals—quick disconnect plug for antenna lead-in—\$27.50.



Write today for full information
on Winegard TV distribution systems
and famous Winegard TV antennas.




Winegard Co.

3013-12 Scotten Blvd. Burlington, Iowa

Antenna Systems

Everything from the
antenna to the set

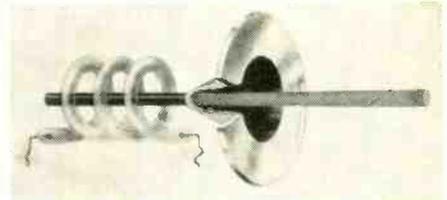

Heart of the light maser. In use, the instrument is sealed in a metal cylinder, of which the cone assembly here forms one end, to prevent light from escaping.

of light reaches one end, it is again sent down the rod, stimulating emission from other atoms. Thus an intense radiation is built up and continues as long as the outside source of "pumping" energy (the photoflash tube) continues to raise atoms to higher energy stages.

Obviously, the light which moves along the rod stimulates many other atoms to emit. Light from these atoms moves in the same direction as the stimulating light, so a very powerful beam is built up, becoming powerful enough to penetrate the thin silvering on the ends of the tube. This output can be used for signaling, in spectroscopy, or as a source of very narrow-frequency monochromatic light.

With the further development of the optical maser, it is expected that all the techniques of modulation and amplification used with lower frequencies can be applied to it. Thus the maser may extend the communications spectrum upward to an extent that will make our present ranges from the very low to the super-high frequencies an insignificant portion of the total spectrum.

Patents on the optical maser are held jointly by Professor Townes, inventor of the original maser, and A. L. Schawlow of Bell Laboratories.

Calendar of Events

- EIA Winter Conference, Nov. 29-Dec. 1, Fairmont Hotel, San Francisco, Calif.
- Third Annual Futronics Exposition, Nov. 30-Dec. 2, Roosevelt Raceway Exhibit Hall, Westbury, N. Y.
- Vehicular Communications Meeting, Dec. 1-2, Sheraton Hotel, Philadelphia, Pa.
- EIA Conference on Maintainability of Electronic Equipment, Dec. 5-7, Grenada Hotel, San Antonio, Tex.
- URSI-IRE Fall Meeting, Dec. 12-14, NBS Boulder Laboratories, Boulder, Colo.
- Eastern Joint Computer Conference, Dec. 13-15, New Yorker Hotel and Manhattan Center, N.Y.
- Symposium on Thermoelectric Energy Conversion, Jan. 8-12, Staller Hotel, Dallas, Tex.
- National Symposium on Reliability & Quality Control, Jan. 9-11, Bellevue-Stratford Hotel, Philadelphia, Pa.
- Symposium on Space Instrumentation, Jan. 16-17, Washington, D.C.
- ERA Southwest Chapter Distributor-Representative Manufacturer Conference, Jan. 29, McAllen, Tex.
- Cleveland Electronics Conference, Jan. 31-Feb. 2, Cleveland Engineering and Scientific Center, Cleveland, Ohio.

Stereo at 100 Cycles, Says AES

Two papers read at the recent Audio Engineering Society Convention in New York City indicate that frequencies down to 100 cycles have a part in the stereo effect. One, by

(Continued on page 14)

How Secure Is ... Your FUTURE?



Your readership of this magazine shows you have a real interest in electronics. Is electronics your career? Or do you plan to make electronics your career? If so, we can help you make it interesting and profitable.

If you have a high school diploma and previous electronics education or experience, a Cleveland Institute program can lead directly to a higher income and more interesting work.

Write today for free booklets pictured at the right. There is no obligation.



Send for these 3 free booklets Cleveland Institute of Electronics

DESK RE48A 4900 EUCLID AVE. CLEVELAND 3, OHIO

Please send me Free Career Information Material prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- | | |
|---------------------------------------------|---------------------------------------------|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?


Name..... Age..... Address.....

City..... Zone..... State.....

RE 48A

Cleveland Institute of Electronics

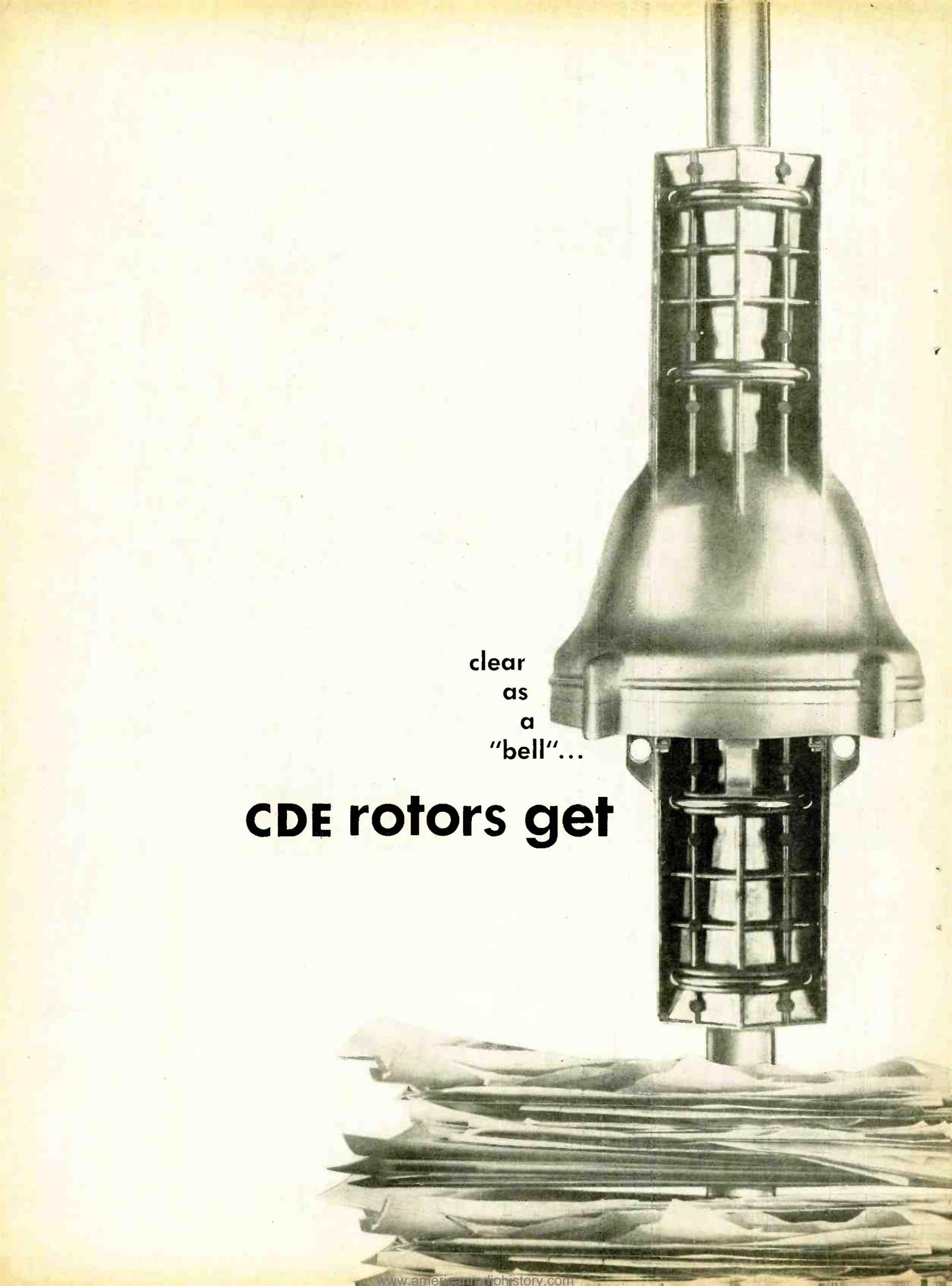DESK RE 48A 4900 EUCLID AVE. CLEVELAND 3, OHIO



clear
as
a
"bell"...

CDE rotors get

the biggest customer reception!

CDE TV antenna rotors are the big-ticket sales that build big customer acceptance for your reputation. Take the AR-22 for example: installed on roof or tower, this heavy-duty beauty weathers the winter like old St. Nick himself. The reason? A sealed, die-cast bell housing which encloses precision *planetary* drive gears instead of conventional worm gears. The AR-22 is also *automatic*. Just set the selector knob—and walk away. The AR-22 turns the antenna to the desired position, stops and locks itself in place—automatically! Examine this and other rugged CDE rotors . . . there are models for every budget . . . at your CDE Distributor. Or write today for catalog No 1630 to: Distributor Sales, Cornell-Dubilier, South Plainfield, New Jersey

**CORNELL-DUBILIER
ELECTRONICS DIVISION**
Federal Pacific Electric Company





BRIGHT NEW VIEW

for Multi-set TV-FM
Home Operation...



...and a
Bright Profit Outlook for YOU with


NEW JERROLD HSA-43

Amplified 3 SET COUPLER

Here's a new precision-perfected amplifier that provides 5 DB min. gain across all TV-FM channels on two outputs and no loss in the third output. Housed in a rugged, compact and handsome case. The HSA-43 features single tube operation (6DJ8), A.C. interlock and no-strip twin lead terminals. Its excellent isolation and match prevents set interaction and ghosting. IDEAL FOR FEEDING ONE FM AND TWO TV SETS FROM THE SAME ANTENNA.

\$29.95 list

TYPICAL APPLICATIONS

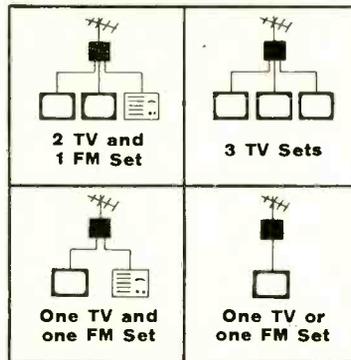

Write Jerrold today for full details on this new Profit Outlook!

JERROLD ELECTRONICS CORPORATION, Distributor Sales Division
Dept. IDS-103, Philadelphia 32, Pa.
Jerrold Electronics (Canada) Limited, Toronto
Export Representative: CBS International, New York 22, N.Y.

LEADER AND LARGEST MANUFACTURER OF TV DISTRIBUTION SYSTEM EQUIPMENT

(Continued from page 10)

F. K. Harvey and M. R. Schroeder of Bell Labs stated that all listeners found a 500-cycle cutoff different from full-range stereo, and that less than 20% found a good spatial resemblance to full-range stereo. The RCA paper stated that some directional information is carried by frequencies from 100 cycles to 10 kc.

Post Office Goes Electronic

Electronics plays an important part in the new all-automated post office in Providence, R. I., which was dedicated on Oct. 20.

Electronic devices switch trays of incoming mail from one conveyor to another as directed by coded elements attached to the trays. A cancelling-facing machine checks the position of the stamp on each letter, passes it through the cancellor so that it arrives in the proper position,



and stacks the letters, now properly positioned, for transmission to the semi-automatic sorting machines.

Here the letters pass at the rate of 50 a minute before human coders, who press keys to assign the letter to any one of 300 destinations. The coded signals are recorded in the magnetic memory of the sorting machine, and the letter is directed down the correct conveyors to the 300 destination boxes.

The system was designed and developed by Intellex Corp., a subsidiary of ITT.

Mechanical automation backs up electronics at a number of points to make the whole operation of receiving, unloading, sorting and re-dispatching the mail automatic.

The project is expected, not only to be a super-efficient post office, but a means for testing other new postal machines and for gaining knowledge that may be applied to the United States postal system as a whole.

Underground TV

A TV camera was used by the Washington Gas Light Co. to inspect the gas mains under the route of the Presidential inaugural parade, to guard against any leaks. The camera was pulled through the 24-inch mains to spot cracks. Workmen above watched the screen, noted the position of bad sectors, and plugged the leaks with sealing fluid. **END**

RADIO-ELECTRONICS

Do you WISH you were EMPLOYED in ELECTRONICS?

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radio telephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham course covers the required subject matter completely. Even though it is planned primarily to lead directly to a first class FCC license, it does this by **TEACHING** you electronics. Some of the subjects covered in detail are: Basic Electricity for Beginners, Basic Mathematics, Ohm's and Kirchhoff's Laws, Alternating Current, Frequency and Wavelength, Inductance, Capacitance, Impedance, Resonance, Vacuum Tubes, Transistors, Basic Principles of Amplification, Classes of Amplifiers, Oscillators, Power Supplies, AM Transmitters and Receivers, FM Transmitters and Receivers, Antennas and Transmission Lines, Measuring Instruments, FCC Rules and Regulations, and extensive theory and mathematical calculations associated with all the above subjects explained simply and in detail.

OUR GUARANTEE

If you should fail the F. C. C. exam after finishing our course, we guarantee to give additional training at **NO ADDITIONAL COST**. Read details in our free booklet.

Get
Your First Class Commercial


F.C.C. LICENSE QUICKLY!

Learn by Correspondence or in Resident Classes

Grantham training is offered by correspondence or in resident classes. Either way, we train you quickly and thoroughly---teach you a great deal of electronics and prepare you to pass the F. C. C. examination for a first class license. Get details now. Mail coupon below.

This booklet
FREE!

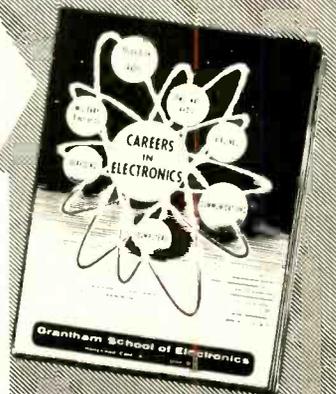This free booklet gives details of our training and explains what an F.C.C. license can do for your future. Send for your copy today.



To get ahead in electronics—first, you need the proper training; then, you need “proof” of your knowledge. Your first class commercial F. C. C. license is a “diploma” in communications electronics, awarded by the U. S. Government when you pass certain examinations. This diploma is recognized by employers. Grantham School of Electronics specializes in preparing you to **earn** this diploma.

Grantham training is offered in resident classes or by correspondence. Our **free** booklet gives complete details. If you are interested in preparing for your F. C. C. license, mail the coupon below to the School's **home office** at 1505 N. Western Ave., Hollywood 27, California—the address given in the coupon—and our free booklet will be mailed to you promptly. No charge—no obligation.

Grantham School of Electronics

HOLLYWOOD
CALIF.

SEATTLE
WASH.

KANSAS CITY
MO.

WASHINGTON
D. C.

RESIDENT CLASSES
HELD IN FOUR CITIES

If you are interested in attending day or evening classes mail the coupon for free information to our home office in Hollywood, Calif.



(Mail in envelope or paste on postal card)

To: **GRANTHAM SCHOOL OF ELECTRONICS**
1505 N. Western Ave., Hollywood, Calif.

Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study; Seattle classes

Hollywood classes, Kansas City classes, Washington classes

04-T

MAIL COUPON NOW—NO SALESMAN WILL CALL →

see the exciting **1961**

knight-kits[®]

A PRODUCT OF ALLIED RADIO


in this value-packed ***ALLIED*** catalog

free

**444 pages
most complete**

send for it!

use coupon
on next page

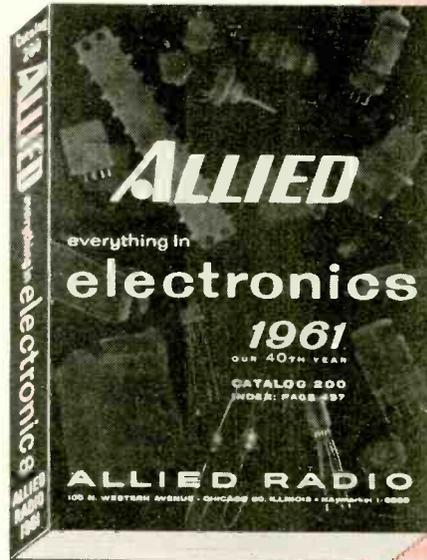

knight-kits—Best by Design

FUN TO BUILD Building it yourself is always satisfying fun—it's fun at its best when you build Knight-Kits—they're so beautifully engineered, so much easier, more pleasurable to work with...

YOU SAVE You save substantially because you buy direct from Allied at our money-saving big-volume-production prices—and because you do the easy building yourself...

YOU OWN THE BEST You'll be glad you built a Knight-Kit, because you'll own and enjoy with pride a true custom-built product, professionally engineered and styled—designed for superior performance...


EASIEST TO BUY **only \$2 down** on orders up to \$50; \$5 down up to \$200; \$10 down over \$200—up to twenty-four months to pay...

exclusive knight-kit MONEY BACK GUARANTEE

Every Knight-Kit is unconditionally guaranteed to meet our published specifications for performance or your purchase price is refunded in full.

**Buy Any Knight-Kit!
...Build and Use It!
It Must Perform
Exactly as Claimed!**

Your Satisfaction is Guaranteed

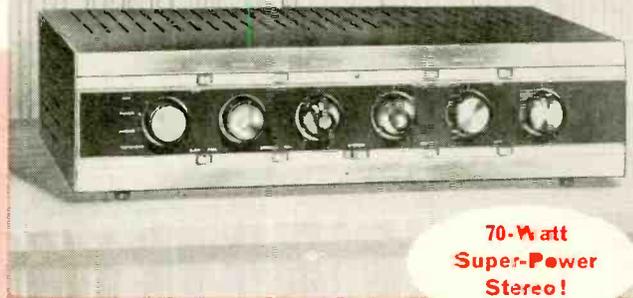


**70-Watt
Super-Power
Stereo!**

DELUXE 70-WATT STEREO AMPLIFIER

Super-power to drive any of today's speakers; the ultimate in control flexibility and functions. 83 YU 934 **\$119.95** only **\$5** down

see many more great **HI-FI KITS**

Stereo Preamp	18-Watt Amplifier
60-Watt Stereo Amplifier	12-Watt Amplifier
Stereo Control	FM Tuner
25-Watt Amplifier	Speaker Systems

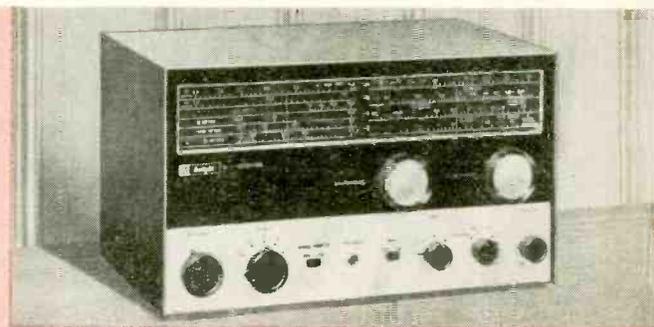

ALL-BAND SUPERHET RECEIVER

Covers 540 kc to 36 mc, plus 6 meters; general coverage tuning and calibrated Amateur bandspread tuning. 83 YU 935 **\$67.50** only **\$5** down

see many other **HOBBYIST KITS**

"Space Spanner"® Receiver	Transistor Radios
"Ocean Hopper" Radio	Intercom Systems
Radio-Intercom	Electronic Lab Kits
Clock-Radio	Photoelectronic System



BEST VTVM VALUE

High sensitivity general-purpose VTVM; 11 meg input resistance; balanced-bridge circuit; 4½" meter. 83 Y 125.... **\$25.75**

only **\$2** down



only **\$2** down

From original concept to final design, each Knight-Kit is produced by and comes directly to you from ALLIED


sold exclusively by
ALLIED

knight-kits: best in build-your-own electronic equipment

STEREO TAPE RECORD/PLAY PREAMP

Professional quality; permits tape monitoring, sound-on-sound and echo effect; use with any tape transport. 83 YX 929 (less case) **\$79.95**

only **\$5** down

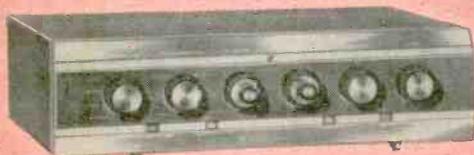

DELUXE 40-WATT STEREO AMPLIFIER

Full frequency center channel. Finest amplifier available anywhere in this price range. 83 YU 774 **\$76.95**

only **\$5** down



Only \$39.95 For Full 20 Watts Stereo!

SUPER-VALUE STEREO HI-FI AMPLIFIER

20-Watt Stereo Hi-Fi Amplifier, with special clutch-type dual-concentric level control; biggest bargain in Stereo hi-fi. 83 YX 927..... **\$39.95**

only **\$2** down

DELUXE FM-AM STEREO HI-FI TUNER

Dynamic Sideband Regulation, variable AFC, "Magic Eye" slide-tuning, multiplex add-in. 83 YU 731 **\$87.50**

only **\$5** down



SUPERHET CITIZENS BAND TRANSCEIVER

Dual-conversion receiver for highest sensitivity and selectivity; 2-channel crystal-controlled 5-watt transmitter. 83 YX 712-2..... **\$79.95**

only **\$5** down



only **\$2** down

\$39.95 For This Citizen's Band Transceiver

TOP VALUE CITIZENS BAND TRANSCEIVER

Lowest-priced complete Citizens Band Transceiver. Tunable 22-channel super-regenerative receiver; 5-watt transmitter. 83 Y 713-2..... **\$39.95**



FM-AM HI-FI TUNER BUY

Outstanding FM-AM Hi-Fi Tuner; with AFC and tuned RF stage on FM; includes multiplex jack. 83 YX 928.... **\$49.95**

only **\$2** down

SENSATIONAL 4-BAND "SPANMASTER" RECEIVER

For thrilling world-wide reception; exciting Short-wave and Broadcast; band-switching, 540 KC to 80 MC. With cabinet. 83 YX 258 **\$25.95**



only **\$2** down



32-WATT STEREO AMPLIFIER VALUE

Money-saving 32-Watt Stereo Hi-Fi Amplifier; high power at low cost; full frequency center channel. 83 YU 933..... **\$59.95**

only **\$5** down



only **\$2** down

"600" TUBE CHECKER

Checks over 700 types; illuminated roll-chart; obsolescence-proof design. 83 YX 143... **\$32.95**


RF SIGNAL GENERATOR

Output to 112 mc on fundamentals; 400-cycle modulation. 83 Y 145..... **\$19.75**

full selection of INSTRUMENT KITS

- 5" Oscilloscopes
- AC VTVM
- Tube Checkers
- Signal Tracer
- Audio Generator
- Sweep Generator
- Battery Eliminator
- Capacity Checker
- Transistor Checker
- R/C Tester,
- plus many others*

Knight-Kits are available in Canada

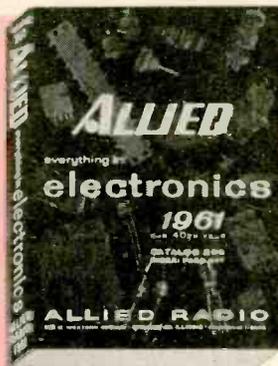

free

SEND FOR THE 444-PAGE 1961 ALLIED CATALOG

Write today for the world's biggest electronics catalog, featuring the complete KNIGHT-KIT line. See the big news in quality electronic kits—save on everything in Electronics. Send for your FREE copy.

send for it today!

ALLIED RADIO, Dept. 162-M

100 N. Western Ave., Chicago 80, Ill.

Send FREE 1961 ALLIED Catalog

Name _____


Address _____

City _____ Zone _____ State _____

RADIO

Pioneer in electronic kit development

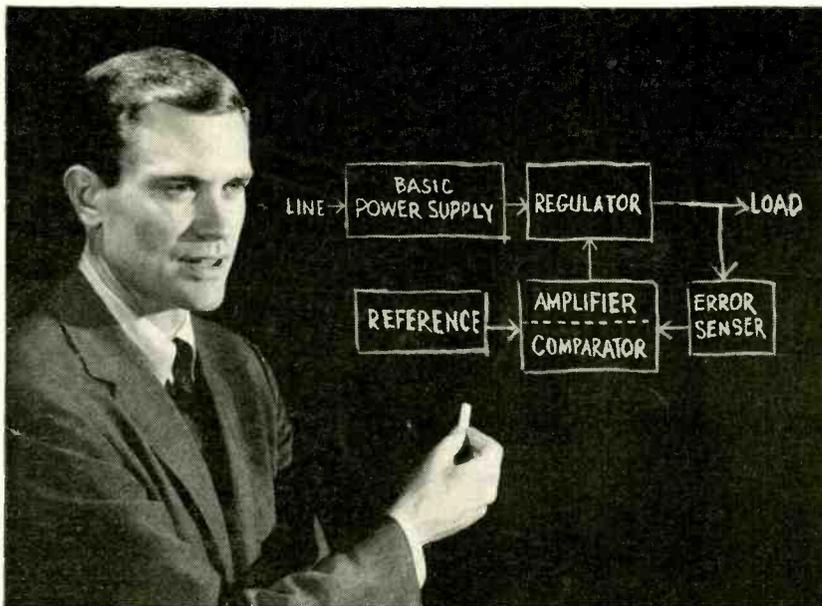Latest issue of
TUNG-SOL TIPS
tells you what you should know about
DC POWER SUPPLIES



PICTURED above is a block diagram of an electronically regulated power supply. It's the subject of the latest issue of Tung-Sol's monthly series for the industrial serviceman, *Tung-Sol Tips*. And it's must reading if you're going to deliver fast and efficient trouble shooting service to your customers.

You get a big, broad analysis of how each of these elements contribute to the overall performance of these power supplies. There's a thorough discussion of one of the most critical elements in the power supply, namely the regulator . . . with lucid illustrations and explanations of several common (and not so common) regulating devices in use today . . . PLUS a ready-to-use, problem-solving series regulator trouble shooting guide that will prove a big help to you in your work.

Then, to top things off: a lengthy description of how designers design regulated power supplies. Right in this issue, the author takes you through a step-by-step analysis of designing procedures. You actually design a power supply with him. He shows you how circuit elements are selected through graphical means. He explains why particular tubes are suited for the design. And finally, to cap it all, you get a complete circuit diagram of the finished design . . . a tried and tested regulated dc power supply that delivers a 250 volt output at 50 to 250 mA.

So, don't miss out on this really important issue. It's yours merely for the asking. Just drop in to see your Tung-Sol distributor. He'll be glad to place your name on the mailing list. Or else write directly to us and start getting your issues of *Tips* immediately. Tung-Sol Electric Inc., Newark 4, N. J.

 **TUNG-SOL®**

SALES OFFICES: ATLANTA, GA.; COLUMBUS, OHIO; CULVER CITY, CALIF.; DALLAS, TEXAS; DENVER, COLO.; DETROIT, MICH.; IRVINGTON, N. J.; MELROSE PARK, ILL.; NEWARK, N. J.; PHILADELPHIA, PA.; SEATTLE, WASH. CANADA: TORONTO, ONT.

Correspondence



HOW ABOUT A FUSE STORY

Dear Editor:

I would like to see an authoritative article about fuses printed in RADIO-ELECTRONICS.

As you know, fuses are rated both as to current and voltage. I became curious about the voltage angle and in an unorganized information sort of way learned that the voltage rating is on account of the explosion hazard.

The question came up because I wanted to fuse a 400-volt power supply. Due to unknowns in the picture, I developed a simple circuit breaker instead. But I was so surprised to learn of a fuse explosion hazard that I thought the whole subject might be explored by an article in RADIO-ELECTRONICS. JOSEPH H. SUTTON
 Kansas City 13, Mo.

[We have just such a story scheduled for the near future, and a shorter treatment on page 99 of this issue.—Editor]

IDENTIFY CALIBRATION SIGNALS

Dear Editor:

I enjoyed the article "Identify Your Calibration Signals" in the September, 1960, issue. I have often had to identify my own calibration signals on my communications receiver. However, I use a simpler identification system than the one proposed in the article.

When there is some doubt as to whether a signal is the calibration oscillator signal or a strong unmodulated carrier, just turn off the calibration oscillator. If the signal stops, it came from your oscillator; if not, it is not from your oscillator.

Obviously, my method is far inferior to the one you suggest. However, you must admit that my method is less expensive. JAMES F. VAN DETTA
 Schoharie, N. Y.

[We admit it is cheaper, but as you say—it isn't better.—Editor]

BUILDS PREAMP AFTER READING R-E

Dear Editor:

I have just completed building the preamp described in "Design Your Own Preamp," on page 61 of the May issue.

In my version I have changed the design for stereo, using four 7025 tubes—one section of each tube per channel. I used only RIAA equalization to reduce wiring problems and keep components to a minimum and because it is almost the only equalization needed today. Switching provides for stereo, stereo reverse, FM single channel, FM both channels, FM multiplex.

Learn RADIO, TELEVISION AND ELECTRONICS by Practicing at Home in Your Spare Time

At No Extra Cost you get specially developed Electronic Training Kits for practical experience. Shop and laboratory practice at home make learning easier, interesting, faster. You do not need a high school diploma or previous experience.

Increasing Demand for Trained Men

This is the Electronics age. Men with Electronic know-how are in demand. They enjoy high pay and growing opportunities for advancement. Satellites, Radar, Automation in Industry, Missiles, Rockets, Planes, Stereo, TV, Radio, Two



Way Communications for transportation are a few of the fantastic developments in the fast growing Electronics industry. If you are not completely satisfied with your work; if you are doubtful about your future, investigate Electronics.

High Pay, Prestige, Bright Future

What branch of Electronics interests you? Thousands of successful NRI graduates prove that NRI's learn-by-practice method is the way to success. You start in your chosen career 'way ahead of the man who only learns from books. You do not need to give up your job. You do not need to go away to school. You learn at home, get practical knowledge from training kits NRI provides.




Train With the Leader

NRI is the world's oldest and largest home study Electronics school. You benefit from the experience NRI has gained from training men for 45 years. NRI offers you proven courses of home study in Electronics; Principles, Practices and Maintenance—Radio Television Communications—Radio Television Servicing.

Start Soon to Earn More

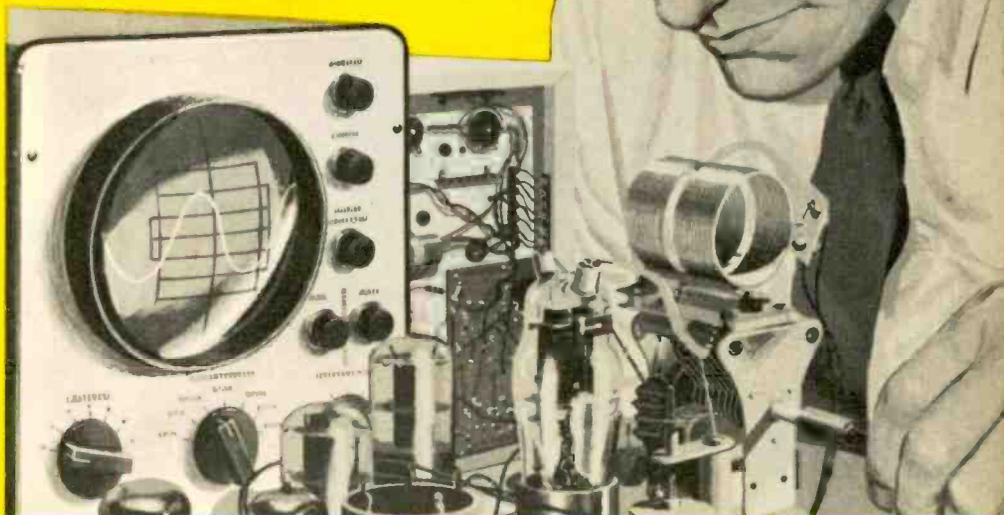Soon after enrolling NRI shows you how to apply your knowledge to earn extra money doing Electronics repairs or servicing Radio and Television sets for friends and neighbors. Take the first step toward success now. Find out what NRI offers you. Mail the postage-free card. No obligation. Cost of NRI training is low. Monthly payment plan available. NATIONAL RADIO INSTITUTE, Washington 16, D.C.



NRI Has Trained Thousands for Success



"I get over twice the salary I made before enrolling. NRI training gave me a thorough understanding." H. ATKINSON, Austin, Tex.



"I started with station CJIC, now in charge of sound effects for CBC. NRI opened doors to greater opportunity for me." F. TUDOR, Toronto, Ontario



"Averaged \$150 a month spare time before I graduated. Now have my own full time business and employ 2 men." F. W. COX, Hollywood, Cal.

NEW COURSE IN ELECTRONICS *TURN PAGE*

Cut Out and Mail—No Stamp Needed

64-PAGE CATALOG FREE

No Salesman will call. (Please PRINT) Z


Name _____ Age _____

Address _____

City _____ Zone _____ State _____

OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL
National Radio Institute
WASHINGTON 16, D. C.

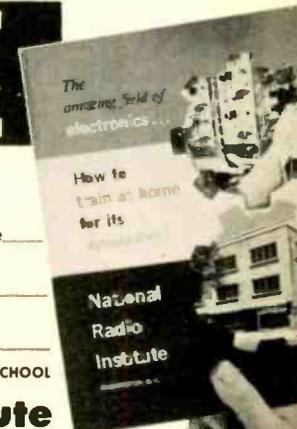ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL





JOB COUNSELORS ADVISE LEARN ELECTRONICS

NEW Home Study Course in **ELECTRONICS** Principles-Practices-Maintenance **NOW READY**

This is the Electronic Age. Electronic equipment is already being used to count and control flow of liquids, solids, gases. Electronics is employed to search for oil, make surveys, control traffic, machine complex parts and in atomic installations. Military uses of Electronics are great and expanding rapidly. In business, Automation with Electronics plays an important part, prepares payrolls, calculates engineering formulas.

Learn More to Earn More

Now, to meet the growing demand for trained Electronic Technicians NRI has developed a comprehensive, complete course in Electronics Principles, Practices, Maintenance. This training stresses fundamentals. It is a course specially prepared for beginners and for Technicians. You get both theory and practical experience in an interesting, exciting way.

Ten Special Training Kits Give Practical Experience

You get practical experience with Thyatron Tube circuits, Multivibrators, build a D'Arsonval type Vacuum Tube Voltmeter (Kit 2); work and experiment with pentode tubes, selenium resistors, oscillators, transistors, magnetic amplifiers; and get practical experience in telemetry circuits as used in earth satellites, digital and analog computers (Kit 9).

NRI—Oldest and Largest School

Wishing for success won't bring success. You must act. Get FREE 64-page Catalog from America's oldest and largest home study Electronic-Radio-Television school. It gives facts, opportunities in Industrial and Military Electronics careers, also shows what you learn, tells about NRI's other courses in Radio Television Servicing and Radio Television Communications. Monthly payments plan. Mail Postage Free Card for 64-page Catalog.
NATIONAL RADIO INSTITUTE, Washington 16, D.C.



PRACTICE WITH
17" TV RECEIVER

PRACTICE WITH
LOW POWER TRANSMITTER

PRACTICE WITH ULTRA
HIGH FREQUENCY OSCILLATOR

SPECIAL TRAINING KITS NO EXTRA COST

PRACTICE WITH
D'ARSONVAL TYPE VOLTMETER

PRACTICE WITH
AC-DC RECEIVER

← **SEE OTHER SIDE** →

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D.C.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

National Radio Institute

3939 Wisconsin Avenue

Washington 16, D.C.

POSTAGE FREE CARD
MAIL NOW

Listening tests show the preamp to be equal to if not better than commercial units. Please convey my thanks to Mr. Crowhurst for such a fine design.
W. R. WILLIAMS

Toronto, Canada

[We sent your letter to Mr. Crowhurst, who is favorably impressed. He suggests that, since his story was a design article only and as you have constructed a prototype, it might make a useful construction story. Do you feel like writing a story on it?—Editor]

MORE TRANSISTORS, PLEASE

Dear Editor:

Please print more data on transistors as they are introduced.

L. C. ERNST


Ann Arbor, Mich.

[We list the most interesting new transistors in our monthly New Tubes and Semiconductors column. You'll find it listed on the contents page.—Editor]

PREAMP POWER SUPPLY

Dear Editor:

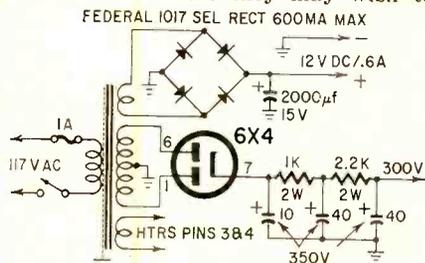Many readers may want to build the preamp discussed in "Design Your Own Preamp," on page 61 of the May, 1960, issue. As an assist they may wish to



use the power supply shown here. It centers around a Webster Electric transformer No. 212-19764-97-0, which puts out 300 volts B-plus and 12.5 volts from its heater winding.

C. L. KING

Plainfield, Ill.

[Thanks for the circuit. All interested preamp builders please note.—Editor]

DISPLEASED

Dear Editor:

Please list me along with other readers who were disappointed with the statements of your Mr. Middleton regarding "Eggy." I noticed with pleasure that he went on in his article to use equations and information which were certainly not the work of the uneducated.

Mr. Middleton's attempted ridicule of anyone possessing an uncommon amount of knowledge is, however, surpassed by Mr. Jack Darr's efforts in the TV Service Clinic in the September issue. What does he mean by "even a 'PhD' can do it himself"? Is he one? If he were, he would be aware of how to write and punctuate the letters standing for the degree. Later he mentions quitting a training course in disgust since he disagreed with a statement made by the instructor. Why wasn't he teaching the course?

Of all magazines in which to find people and knowledge in general held


(Continued on page 24)



New kind of KIT from H. H. Scott...

EASY-TO-BUILD 72 WATT
STEREO AMPLIFIER KIT
LOOKS AND PERFORMS
LIKE FACTORY-
BUILT UNITS!

\$149⁹⁵*

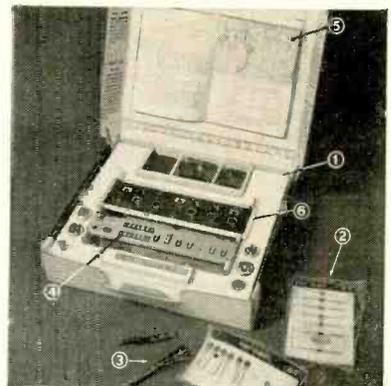

IMPORTANT FEATURES OF THE NEW H. H. SCOTT LK-72 COMPLETE AMPLIFIER

1. Unique Kit-Pak container opens to a convenient worktable. Folds up at night like a suitcase.
2. Part-Charts — All parts mounted in order of installation. No sifting through loose parts.
3. All wires pre-cut, pre-stripped to cut assembly time.
4. Mechanical parts all pre-mounted. Tube sockets and terminal strips riveted to chassis.
5. Easy-to-follow full color instruction book.
6. Special features include: Center Channel Level control; Scratch Filter; Tape Recorder Monitor; Separate Bass and Treble on each channel; DC operated heaters for lowest hum.

*Slightly higher west of the Rockies.

H. H. SCOTT

H. H. SCOTT INC., DEPT. RE12
111 POWDERMILL ROAD • MAYNARD, MASS.

Rush me complete details on your new LK-72 Complete Amplifier Kit, LT-10 FM Tuner Kit, and Custom Stereo Components for 1961.

Name.....
Address.....
City..... State.....

Export: Telesco International Corp.
36 W. 40th St., N. Y. C.


Here's the kit that makes you a professional. Beautifully designed, perfectly engineered, and so easy to wire that you can't go wrong. In just a few evenings you can build a professional 72 watt H. H. Scott stereo amplifier . . . one so good it challenges factory-assembled units in both looks and performance.

H. H. Scott engineers have developed exciting new techniques to ease kit-building problems. The Kit-Pak container unfolds to a self-contained worktable. All wires are pre-cut and pre-stripped. Parts are mounted on special cards in the order you use them. All mechanical parts are pre-riveted to the chassis.

Build a new H. H. Scott LK-72 for yourself. You'll have an amplifier that meets rugged IHFM specifications . . . one that delivers sufficient power to drive any speaker system . . . one that's professional in every sense of the word.

TECHNICAL SPECIFICATIONS: Full Power Output: 72 watts, 36 watts per channel • IHFM Power Band: extends down to 20cps • Total Harmonic Distortion: (1kc) under 0.4% of full power • Amplifier Hum Level: better than 70db below full power output • Tubes: 4 — 7591 output tubes, 2 — 7199, 4 — 12AX7, 1 — 5AR4 • Weight of Output Transformers: 12 pounds • Amplifier fully stable under all loads including capacitive • Dimensions in accessory case: 15½ w, 5¼ h, 13¼ d. Size and styling matches H. H. Scott tuners.

WHAT GOES ON HERE?

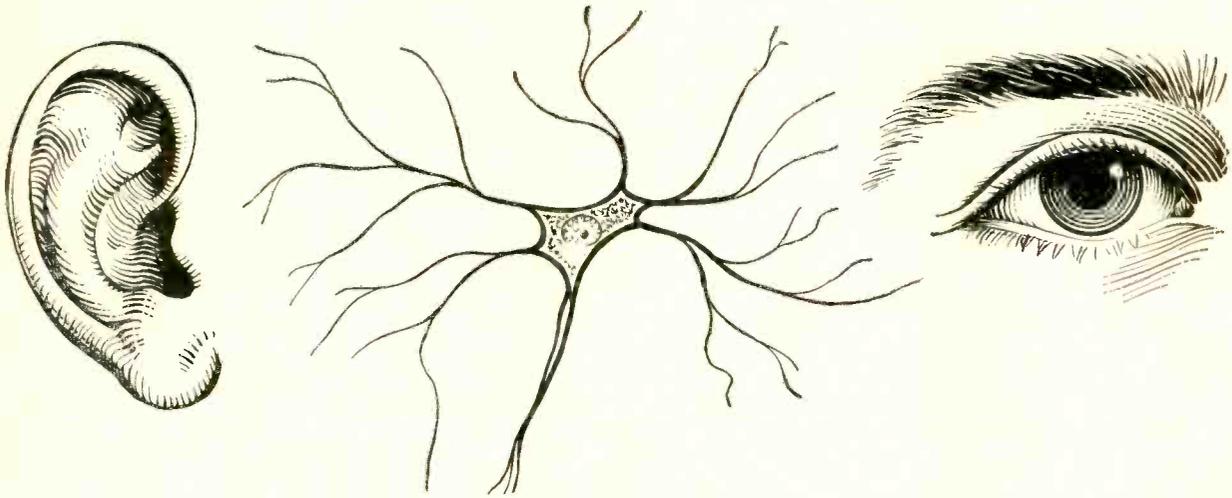

Bell Telephone Laboratories' new electronic "nerve cell" is a step toward finding out

One fascinating area of communications has long resisted exploration — what happens inside the nervous system when you see, or when you hear.

This area is of special interest to telephone science; knowledge of how the nervous system handles sound and picture signals can help determine what information is essential to perception. This in turn may lead to more efficient communication instruments and systems.

To probe the mystery of nerve activity, Bell Telephone Laboratories scientists have developed an electronic model of a living nerve cell or neuron. Consisting of transistors, resistors, capacitors and diodes, the "artificial neuron" exhibits many of the characteristics of a living neuron; for instance, "all-or-none" response and fatigue.


In one experiment at Bell Laboratories, a network of artificial neurons is subjected to a stimulus from light through a set of photocells. The network can distinguish specific patterns of light and dark, thus duplicating roughly some of the eye's basic reactions to light. Similar studies are underway to explore our hearing processes.

At present, too little is known about neural action to permit exact electronic duplication. But experiments with artificial neurons can provide suggestive clues, contributing to a stimulating interplay between electronics and neurophysiology which may help workers in both disciplines.

The human nervous system, including the brain, is the most efficient and versatile data processing system known; and data processing is an essential part of communications. The artificial neuron provides a new approach to investigating and understanding basic nerve network functions. It is a fresh example of how Bell Telephone Laboratories constantly explores new frontiers to improve America's communications system, now and in the years ahead.



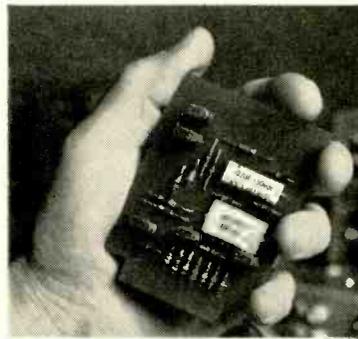Network of neurons is assembled by L. D. Harmon of Bell Laboratories, the initiator of this new research. Many kinds of assemblies are possible.



A single artificial neuron. It delivers electrical impulses when stimulated, like a living cell. Neurons are also being used for research into hearing.

BELL TELEPHONE LABORATORIES
WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT



AT LAST!

RADIO-TV and ELECTRONICS TRAINING ... AT A PRICE YOU CAN AFFORD!



***21 INCH**
Receiver Kit included

Yes, this great course costs far less than any training of its kind given by other major schools! Radio-Television Training School will train you for a good job in Television or Industrial Electronics — AT HOME IN YOUR SPARE TIME.

Think of it—a complete training program including over 120 lessons, Fourteen Big Radio-Television Kits, Complete Color-TV Instruction, Unlimited Consultation Service . . . ALL at a really big saving to you. How can we do this? Write to us today . . . and find out!

And what's more — you can (if you wish)

OPEN YOUR OWN RTS-APPROVED AND FINANCED RADIO-TV SERVICE SHOP

We Want Many More Shops This Year

This 38 year old training organization — called RTS, that's Radio-Television Training School — wants to establish a string of Radio-TV Repair Shops in principal cities throughout the U. S. So far, a great many such shops are NOW IN BUSINESS AND PROSPERING. We are helping and training ambitious men to become future owners and operators of these shops in all areas.


FOR UNSKILLED INEXPERIENCED MEN ONLY — WE TRAIN YOU OUR WAY!

We must insist that the men we sign up be trained in Radio-TV Repair, Merchandising and Sales by our training methods—because WE KNOW the requirements of the industry. Therefore, we will TRAIN YOU . . . we will show you how to earn EXTRA CASH, during the first month or two of your training period. YOU KEEP YOUR PRESENT JOB. TRAINING TAKES PLACE IN YOUR OWN HOME, IN YOUR SPARE TIME!

RTS
APPROVED SERVICE SHOP

COMPLETE COLOR TV INSTRUCTION INCLUDED

YOU BUILD THESE AND OTHER UNITS!

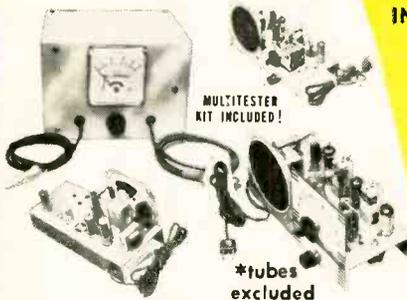


MULTITESTER KIT INCLUDED!

*tubes excluded

RADIO-TELEVISION TRAINING SCHOOL

815 E. ROSECRANS AVENUE
LOS ANGELES 59, CALIFORNIA

Est. 1922

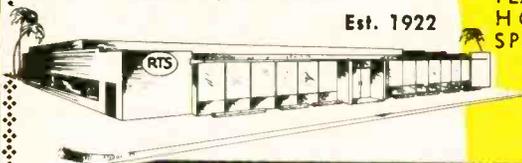

ACT NOW!


Get your free book on the **FAMOUS RTS BUSINESS PLAN** find out how you can open **A REPAIR SHOP OF YOUR OWN**

We supply and finance your equipment

When you are ready and qualified to operate one of our RTS-Approved TV Repair Shops WE WILL SUPPLY AND FINANCE EVERY BIT OF EQUIPMENT YOU NEED TO GET STARTED plus an inventory of parts and supplies. In other words we will stake you . . . AN OFFER NEVER MADE BEFORE BY ANY TRAINING ORGANIZATION. Under the RTS Business Plan you receive:

1. An electric sign for the shop front.
2. Complete laboratory of test equipment.
3. Letterheads, calling cards, repair tickets, etc.
4. Basic inventory of tubes, parts, supplies.
5. Complete advertising and promotional material.
6. Plans for shop arrangement.
7. Instructions on how to go into business.
8. Continuous consultation and help.
9. The right to use RTS Seal of Approval, and the RTS Credo.
10. The right to use the Famous Trade Mark.

ACCREDITED MEMBER

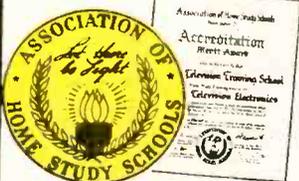

RTS' Membership in The Association of Home Study Schools is your assurance of Reliability, Integrity, and Quality of Training.

ALL THESE FREE!

BUSINESS PLAN

SAMPLE LESSON

GOOD JOBS - RADIO-TV ELECTRONICS

CUT OUT AND MAIL — TODAY!

RADIO-TELEVISION TRAINING SCHOOL

815 EAST ROSECRANS AVENUE Dept. RE120
LOS ANGELES 59, CALIFORNIA

SEND ME FREE — all of these big opportunity books — "Good Jobs in TV-Electronics," "A Repair Shop of Your Own" and "Sample Lesson." I am interested in:

- Radio-Television Industrial Electronics (Automation)

Name _____ Age _____

Address _____

City & State _____

302

Mail This Coupon Now—No Salesman Will Call

For Push-Pull AND Push-Push Switch Type Controls

it
all
adds
up
to
Centralab
ERL®



Look at the figures—78% of the TV, radio and hi-fi sets now being produced utilize push-pull or push-push controls! Only CENTRALAB gives you a complete line of replacements for them—35 push-pulls, plus the *only* push-push units available! To multiply your choice, these CENTRALAB switch-type controls are divided into 4 types—Adashaft, Universal Shaft, Fastatch or dual concentrics, and Twin types for stereo. Whatever kind you need, you can be sure your CENTRALAB distributor has it. For a complete accounting on these push-pull and push-push controls, ask your distributor for Bulletin 42-936 or write us for your free copy.

Centralab
ERL®

THE ELECTRONICS DIVISION OF GLOBE-UNION INC.
922M EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
CENTRALAB CANADA LIMITED—AJAX, ONTARIO

ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

(Continued from page 21)
up to ridicule, RADIO-ELECTRONICS with its excellent articles and scientifically brilliant editorials should be the last. As the editorial in this very issue (September) implies, this is the age of interstellar activities. It is not the era of Robert Fulton. H. L. COVER
Fredericksburg, Va.

MR. DARR'S REPLY

Dear Mr. Cover:

It seems to me that both Bob Middleton's article and my TV Clinic introduction did not present our point as clearly as they might have. What we were both trying to say, in different ways, was that TV technicians need *more* knowledge, certainly not less!

However, the point was, as both of us have said repeatedly, it is *not* necessary for a practicing TV technician to know how to *design* a TV set before he is able to service it. He must know the basic circuits, their commercial applications and the characteristics of all types of parts. But, as for the higher-level math needed in design work—it is not only unnecessary, but actually useless in service work.

The proficient service technician must have *both* a theoretical and a practical knowledge of TV circuitry! Either one alone is quite useless. I remember (another) college instructor, also with a PhD (plus a doctorate in math, too) and a complete knowledge of radio design theory, who was completely unable to locate an open filter capacitor in a little ac-de radio! I showed him how; I was at his home to get some help in math. He not only laughed, but told the incident in class the next day!

So it depends upon the instructor. I am still in complete disagreement with the attitude of the highly educated gentleman mentioned in the column—that all a TV technician needs to know is how to clip out and replace parts. First, he must have enough knowledge of circuitry to *find* them!

JACK DARR

BOOKS DISTRIBUTED

Dear Editor:

After going through the replies to my letter, which appeared in the June issue of RADIO-ELECTRONICS, I have distributed the books among those who wrote. I wish to thank you and your staff for your co-operation. It has been more than I ever expected and I appreciate it more than words can say.

NAME WITHHELD

[The kind donor was somewhat reluctant to describe her part in the distribution, so here is a brief summary.]

A total of 32 books was distributed among seven persons. The breakdown was made by the donor and took into consideration both the need of the recipient and the suitability of the subject matter of the books. Two persons receiving books were also presented 1-year subscriptions to RADIO-ELECTRONICS by the donor.

We have been delighted to cooperate on such a worthy project and are pleased to have been offered the opportunity.—Editor]

END

Over 2 MILLION EICO instruments in use throughout the world. Add 5% in the West.



IF YOU LOVE TO CREATE... BUILD **EICO** KITS

In **STEREO** and

Mono Hi-Fi...
the experts say
your Best Buy
is EICO



Stereo Amplifier-Preamplifier HF81†



Stereo Preamplifier HF85††



FM Tuner HFT90††
AM Tuner HFT94††
FM/AM Tuner HFT92†



100W Stereo Power Amplifier HF89
70W Stereo Power Amplifier HF87
28W Stereo Power Amplifier HF86



Stereo Integrated Amplifier AF4††



3-Way Speaker System HFS3
2-Way Bookshelf Speaker Systems
HFS5 and HFS4



NEW!
Stereo Automatic Changer/
Player 1007



- Exclusive advanced systematized engineering
- Latest and finest quality parts
- Exclusive "Beginner-Tested" easy step-by-step instructions
- Exclusive TRIPLE quality control
- Exclusive LIFETIME guarantee at nominal cost

IN STOCK — Compare, then take home any EICO equipment — right "off the shelf" — from 1500 neighborhood EICO dealers throughout the U. S. & Canada, most of whom offer budget terms.

HF81 Stereo Amplifier-Preamplifier selects, amplifies, controls any stereo source & feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Provides 28W monophonically. Ganged level controls, separate balance control, independent bass and treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers. "Excellent!" — SATURDAY REVIEW. "Outstanding... extremely versatile." — ELECTRONICS WORLD. Kit \$69.95. Wired \$109.95. Incl. cover.

HF85 Stereo Preamplifier: Complete master stereo preamplifier-control unit, self-powered. Distortion borders on unmeasurable. Level, bass & treble controls independent for each channel. Or ganged for both channels. Inputs for phono, tape head, mike, AM, FM, & FM-multiplex. One each auxiliary A & B input in each channel. "Extreme flexibility... a bargain." — HI-FI REVIEW. Kit \$39.95. Wired \$64.95. Incl. cover.

New HF89 100-Watt Stereo Power Amplifier: Dual 50W highest quality power amplifiers. 200W peak power output. Uses superlative grain-oriented steel output transformers for undistorted response across the entire audio range at full power, assuring utmost clarity on full orchestra & organ. 60 db channel separation. 1M distortion 0.5% at 100W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 100W. Kit \$99.50. Wired \$139.50.

HF87 70-Watt Stereo Power Amplifier. Dual 35W power amplifiers identical circuit-wise to the superb HF89, differing only in rating of the output transformers. 1M distortion 1% at 70W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 70W. Kit \$74.95. Wired \$114.95.

HF86 28-Watt Stereo Power Amp. Flawless reproduction at modest price. Kit \$43.95. Wired \$74.95.

FM Tuner HFT90: Prewired, prealigned, temperature-compensated "front end" is drift-free. Prewired exclusive precision eye-tronic® traveling tuning indicator. Sensitivity: 1.5 uv for 20 db quieting; 2.5 uv for 30 db quieting, full limiting from 25 uv. IF bandwidth 260 kc at 6 db points. Both cathode follower & FM-multiplex stereo outputs, prevent obsolescence. Very low distortion. "One of the best buys in high fidelity kits." — AUDIOCRRAFT. Kit \$39.95*. Wired \$65.95*. Cover \$3.95. *Less cover, F.E.T. incl.

AM Tuner HFT94: Matches HFT 90. Selects "hi-fi" wide (20-9000 cps @ -3 db) or weak-station narrow (20-5000 cps @ -3 db) bandpass. Tuned RF stage for high selectivity & sensitivity. Precision eye-tronic® tuning. "One of the best available." — HI-FI SYSTEMS. Kit \$39.95. Wired \$65.95. Incl. cover & F.E.T.

FM/AM Tuner HFT92 combines renowned EICO HFT90 FM Tuner with excellent AM tuning facilities. Kit \$59.95. Wired \$94.95. Incl. cover & F.E.T.

AF4 Economy Stereo Integrated Amplifier provides clean 4W per channel or 8W total output. Kit \$38.95. Wired \$64.95. Incl. cover & F.E.T.

HF12 Mono Integrated Amplifier (not illus.): Complete "front end" facilities & true hi-fi performance. 12W continuous, 25W peak. Kit \$34.95. Wired \$57.95. Incl. cover.

HFS3 3-Way Speaker System Semi-Kit complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, full-inch excursion 12" woofer (22 cps res.) 8" mid-range speaker with high internal damping cone for smooth response, 3 1/2" cone tweeter. 2 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest frequency & best transient response. 32-14,000 cps clean, useful response. 16 ohms impedance. HWD: 26 3/8" x 13 7/8" x 14 5/8". Unfinished birch. Kit \$72.50. Wired \$84.50. Walnut or mahogany. Kit \$87.50. Wired \$99.50.

HFS5 2-Way Speaker System Semi-Kit complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, 3/8" excursion, 8" woofer (45 cps. res.), & 3 1/2" cone tweeter, 1 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest freq. & best transient resp. 45-14,000 cps clean, useful resp. 16 ohms.

HWD: 24" x 12 1/2" x 10 1/2". Unfinished birch. Kit \$47.50. Wired \$56.50. Walnut or mahogany. Kit \$59.50. Wired \$69.50.

HFS1 Bookshelf Speaker System complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range. 8 ohms. HWD: 23" x 11" x 9". Kit \$39.95. Wired \$47.95

HFS2 Omni-Directional Speaker System (not illus.) HWD: 36" x 15 1/4" x 11 1/2". "Fine for stereo" — MODERN HI-FI. Completely factory-built. Mahogany or walnut \$139.95. Blond \$144.95.

New Stereo/Mono Automatic Changer/Player: Jam-proof 4-speed, all record sizes, automatic changer and auto/manual player. New extremely smooth, low distortion moisture-proof crystal cartridge designed integrally with tonearm to eliminate mid-range resonances. Constant 4 1/2 grams stylus force is optimum to prevent groove flutter distortion. No hum, turntable attractions, acoustic feedback, center-hole enlargement. Only 10 3/4" x 13". 1007S: 0.7 mil, 3 mil sapphire, \$49.75. Incl. F.E.T. and "Magnadaptor."

†Shown in optional Furniture Wood Cabinet WE71: Unfinished Birch, \$9.95; Walnut or Mahogany, \$13.95.

††Shown in optional Furniture Wood Cabinet WE70: Unfinished Birch, \$8.95; Walnut or Mahogany, \$12.50.

EICO, 33-00 N. Blvd., L.I.C. 1, N. Y. C-12


Show me how to SAVE 50% on easy-to-build top-quality Hi-Fi. Send FREE catalog, Stereo Hi-Fi Guide plus name of neighborhood EICO dealer.

Name _____

Address _____

City _____ Zone _____ State _____

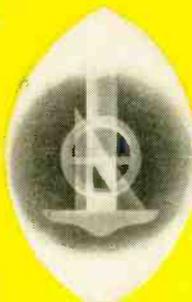
New! 36-page Guidebook to Stereo and Mono Hi-Fi... Send 25¢ to cover handling and postage.




DESIGNED

AS YOU WOULD DESIGN IF YOU WERE AN ELECTRONICS ENGINEER...

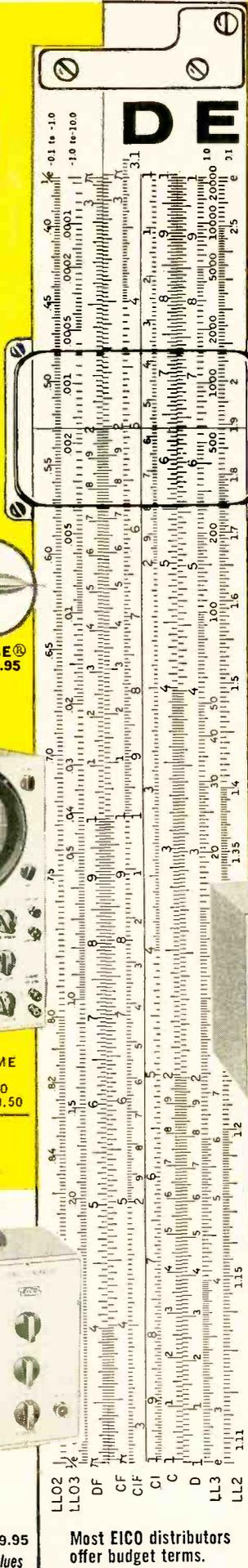Praised by the experts as Best Buys... **EICO**




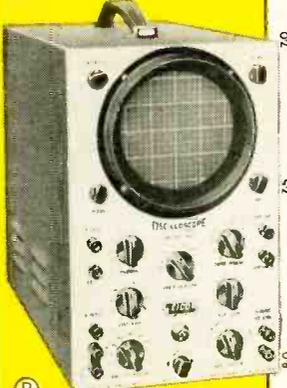A PEAK-TO-PEAK VTVM #232 & UNI-PROBE® KIT \$29.95 WIRED \$49.95
U. S. Pat. No. 2,790,051



B COLOR & MONOCHROME DC TO 5 MC LAB & TV 5" OSCILLOSCOPE #460 KIT \$79.95 WIRED \$129.50

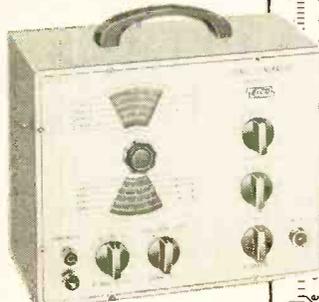
Also available:
5" Push-Pull Oscilloscope #425 Kit \$44.95 Wired \$79.95



C RF SIGNAL GENERATOR #324 KIT \$26.95 WIRED \$39.95
Turn Page For More EICO Values



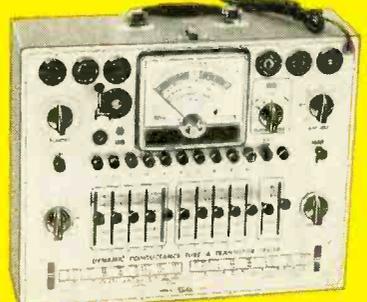D TV-FM SWEEP GENERATOR & MARKER #368 KIT \$69.95 WIRED \$119.95



E DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #666 KIT \$69.95 WIRED \$109.95
Complete with steel cover and handle

A By far the best professional VTVM value in electronics; nobody but EICO brings you such outstanding instrument performance for so low a price! Calibration without removing from cabinet. Measure directly p-p voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 volts with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 4 1/2" meter, can't burn-out circuit, 7 non-skip ranges on every function. Zero center. Features EICO's exclusive UNI-PROBE: your terrific time-saver, performs all functions: a half turn of probe-tip selects DC or AC-Ohms!

B An engineering achievement unmatched in the industry! EICO-designed for laboratory precision and EICO-priced for lowest cost. Features DC amplifiers. Flat from DC to 4.5 mc, usable to 10 mc. Vert. Sens.: 25 mv/in.; input Z 3 megs; direct-coupled & push-pull throughout. 4-step frequency-compensated attenuator up to 1000:1. Sweep: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps). Pre-set TV V & H positions. Auto sync limiter & amplifier Direct or C coupling; balanced or unbalanced inputs; edge-lit engraved lucite screen with dimmer control.

C More features and versatility, more range and accuracy than in generators costing three to four times as much. 150 kc to 435 mc with ONE generator in 6 fundamental bands and 1 harmonic band! ±1.5% frequency accuracy. Colpitts RF oscillator directly plate-modulated by K-follower for improved modulation. Variable

depth of internal modulation 0-50% by 400 cps Colpitts oscillator. Variable gain external modulation amplifier: only 3 volts needed for 30% mod. Turret-mounted, slug-tuned coils for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv, AF output to 10 v.

D Provides more ranges, greater ease and accuracy, and better performance than any competitive unit. Entirely electronic sweep circuit with accurately-biased inductor for excellent linearity. Extremely flat RF output. Exceptional tuning accuracy. Hum & leakage eliminated. 5 fundamental sweep ranges: 3-216 mc. Variable marker range: 2-75 mc in 3 fund. bands, 60-225 mc on harmonic band. 4.5 mc crystal marker osc., crystal supplied. Ext. marker provision. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Narrow range phasing control for accurate alignment.

E Speedy, simple operation, unexcelled sensitivity and accuracy; superb electrical and mechanical design. Tests all receiving tubes (picture tubes with adapter), n-p-n and p-n-p transistors. Composite indication of Gm, Gp & peak emission. Simultaneous selection of any one of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot.). Sensitive 200 ua meter. 10 six-position lever switches: freepoint connection of each tube pin, 10 push-buttons: rapid insert of any tube element in leakage test circuit. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. CRA Adapter \$4.50.



All Transistor Portable RA-6 Kit \$29.95 Wired \$49.95 less battery



Power & Bias Supply for Transistorized Eqt. #1020 Kit \$19.95 Wired \$27.95



DeLuxe Multi-Signal Tracer #147 Kit \$24.95 Wired \$39.95



Tube Tester #625 Kit \$34.95 Wired \$49.95 Pix Tube Test Adapter \$4.50



6 & 12V Battery Eliminator & Charger #1050 Kit \$29.95 Wired \$38.95 #1060 Kit \$38.95 Wired \$47.95



V-O-M #565 Kit \$24.95 Wired \$29.95 V-O-M #536 Kit \$12.90 Wired \$14.90



R-C Bridge & R-C-L Comparator #950B Kit \$19.95 Wired \$29.95

Most EICO distributors offer budget terms.

EICO 33-00 Northern Blvd., L. I. C. 1, N. Y. C-12
 Show me HOW TO SAVE 50% on Test Instruments
 Hi-Fi Ham Gear. Send me FREE Catalog, name of neighborhood dealer. Send free Short Course for Novice License.
 Name.....
 Address.....
 City..... Zone..... State.....

© 1960 EICO 33-00 N. Blvd., L. I. C. 1, N. Y. Add 5% in the West

HOW FAR AMPLIFICATION?

... *It Is Doubtful That Ultimate Amplification Is Possible Soon* ...

WHEN Marconi in 1901 sent his historic letter S across the ocean, a distance over 2,000 miles, from Poldhu (England) to St. John's (Newfoundland), he used what was then considered a terrific amount of power (20 kilowatts) to do so. The reason: modern electric amplification was unknown. Hence his primitive auto-coherer (detector), even with a high antenna, was just sufficient to intercept the faint signals over the single 'phone he used at that time.

True electronic amplification was not possible till the advent of de Forest's vacuum tube and the principles of regeneration, superregeneration and amplification using a number of tubes in cascade, each step amplifying the original signal enormously.

Today's radio amateur can easily communicate with his friend at the antipodes with a transmitter that uses but a few dry cells and has a power output of only a few watts. To achieve this, the signal is amplified hundreds of millions of times at the receiver; yet only a minimum number of vacuum tubes or transistors are used.

Spectacular as these results are, amplification at present has its limitations. Vacuum tubes cannot be added indefinitely in cascade because the tube noises are amplified too, and very soon a point is reached where the inherent noises of the receiver overpower the signal.

A similar condition exists in transistor receivers to a lesser degree. Nevertheless, with each additional transistor the noise ratio increases, soon preventing further magnification of the original signal.

As time goes on, the obvious remedy seems to lie in the greater and ever greater sensitivity of the detectors used, as well as radically new amplifiers. It all started with Hertz' detector, a wire with a brass ball on each end and formed into a loop. You saw the result in the form of a tiny spark. Then came the Branley metal-filings coherer, followed by the Marconi hysteresis-iron-wire-band detector, later the crystal detector, then the vacuum tube, a while later the transistor. More recently new low-noise amplifiers, the *parametric amplifier* and the maser, have appeared. These produce very much less noise than do tube amplifiers, and hence can be used to amplify signals that would formerly have been lost in receiver noise. This covers the comparatively short time of some 60 years.

There would seem to be little doubt that as time goes on more and more sensitive detectors will be invented. Amplifiers too will be vastly improved. It appears certain that the amplifiers of 60 years hence will give many thousands of times greater amplification than those we have today. This despite the fact that scientists will tell you that you cannot drive amplification beyond a certain mathematical limit. Their ideas stem from the fact that even if you succeed in eliminating all the extraneous and inherent noises, you will then amplify the colliding electrons themselves.

Very true. Nevertheless, remedies for such an eventuality will be found, probably in new applications of *cryo-electronics*, i.e., in hypercooled circuits, near absolute zero, coupled with atomic power that generates the necessary supply current. Incidentally, masers in use today already use cryo-electronics to reduce thermal noise to the minimum.

Why the race for superamplification? In military missile detection, in submarine detection, our present instrumentation is still, to put it bluntly, extremely crude. We have made only a start in this direction.

Further, we still struggle with atmospheric and ionospheric interference of radio waves; the quality of the signal is all too often not very good. This is particularly true in radio astronomy, where all signals must pierce our atmosphere. As we have mentioned before on this page, one remedy would consist of a lunar detecting center. Then the highly amplified, powerful signal could be sent to earth without difficulty.

Despite atmospheric and ionospheric difficulties, we have been able to receive radio signals over immense distances. In 1950, Professor Lovell and his associates at England's Jodrell Bank radio observatory succeeded in registering radio signals from the Great Nebula in Andromeda (M31) 2,000,000 light-years distant! The frequency, incidentally, was 1.9 meters (158 mc). A light-year is the distance covered by light traveling at 186,285 miles per second during one year, or almost 6,000,000,000,000 (6 trillion) miles. Radio astronomers really should call the unit a *radio-year*, since they use radio waves, not light waves.


If Marconi's original letter-S signal had not been absorbed completely by the ionosphere, it would be speeding out into space now almost 60 light-years—or 60 radio-years. Later, also more powerful, short-wave signals are 35 radio-years out in space, winging through space to be intercepted by other civilizations, should they exist in a neighboring world. But as our galaxy measures more than 100,000 radio-years across, it may be many thousands of years before our radio emissions reach a radio-civilized planet of some galactic sun. Hence we cannot hope for an early answer or other communications from some other intelligent world which has known electronics for eons.

Furthermore, there is always the possibility that weak, attenuated signals from other worlds have reached the earth for ages. But we have not intercepted them because of our crude detectors and insufficient amplification.

It is one thing to intercept signals from a star naturally powered with billions of horsepower. It is quite another proposition to detect signals with a moderate power of 1,000 or 10,000 kilowatts that would originate from a planet inhabited by intelligent beings. Such signals would arrive on earth so attenuated that we would certainly not be able to intercept them for a long time, due to the present crude state of our electronic art.

—H.G.



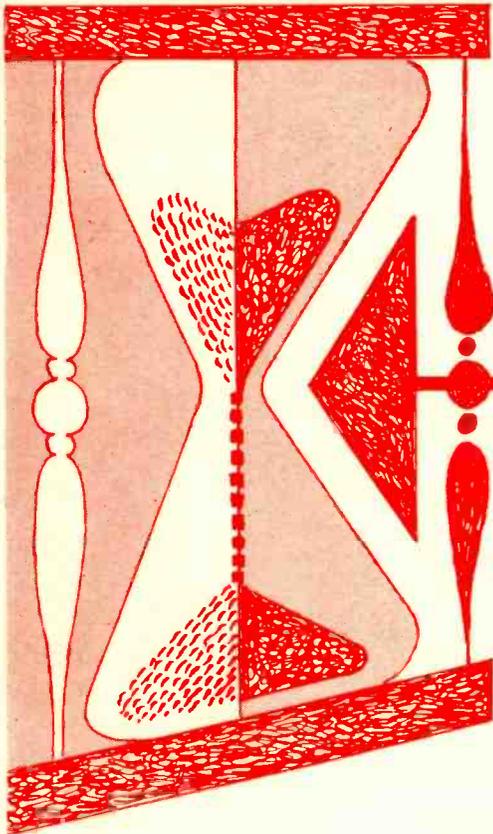

an integrating timer

It adds up light, temperature, pressure or humidity till the total keys a relay.

By JOHN POTTER SHIELDS

THIS electronic timer has been designed for use where the average timer is inadequate. It is battery-operated, freeing it from the power lines and, since no vacuum tubes are used, it is extremely rugged. Although the timer was originally developed as an electronic exposure timer, it can be used for practically any other timing operation including event timing, time delay and process control.


As mentioned above, this timer was originally designed to be used as an exposure timer. However, unlike the ordinary indicating exposure meter, this one "integrates" the total amount of light or other types of radiation received, and trips a relay when a predetermined amount has been received. By choosing the proper photoconductive cell, various types of radiation from infrared to X-rays will actuate the timer. One practical application is that of accurately controlling the exposure time of a photo enlarger. The tiny photocell is placed so it will receive the same amount of light from the enlarger as the unexposed print paper. Once the timer has been calibrated for the various kinds of papers to be used, it will automatically control the time of exposure, depending upon the density of the

negative used and the enlarger lens opening. Since the unit is portable, it can be even taken out to the beach to monitor how long you sunbathe!

The timer is easy to build. It requires no special components, and current consumption is slight, making it economical to operate. The timing interval is from several seconds to about an hour.

How it works

Fig. 1 is the unit's circuit. The neon lamp, calibration control R1, photoconductive photocell V1, and R2 are

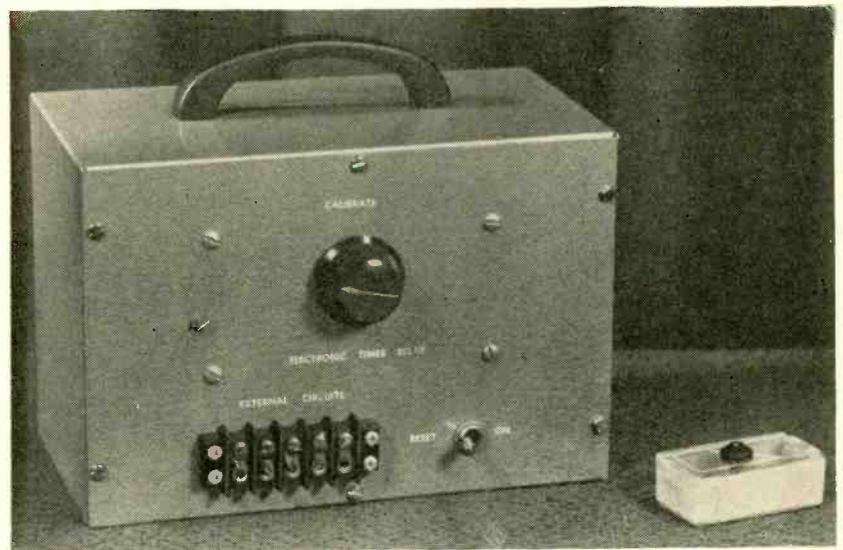

There are only two controls on the face of the instrument. Note the photocell at the right.

- R1—pot. 5 megohms, linear taper
- R2—1,000 ohms, 1/2 watt
- R3—470 ohms, 1/2 watt
- R4—100 ohms, 1/2 watt
- R5—15,000 ohms, 1/2 watt
- C1—40 μ f, 150 volts (tantalum or standard electrolytic, depending on space requirements)
- C2—0.5 μ f, 200 volts
- BATT 1, 2—67.5 volts (Burgess P45 or equivalent)
- RY—dpdt, 2,500-ohm coil (Potter & Brumfield type LM-11 or equivalent)
- S1—dpdt toggle
- V1—CL-2 or CL-3, Clairex photoconductive cell
- V2—2N332
- Terminal strip, barrier type, 3 or more terminals
- Neon lamp, NE-2
- Case and chassis to suit
- Miscellaneous hardware


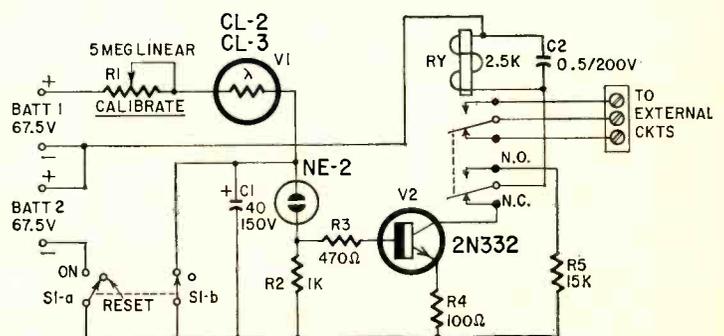


Fig. 1—Circuit of the timer.

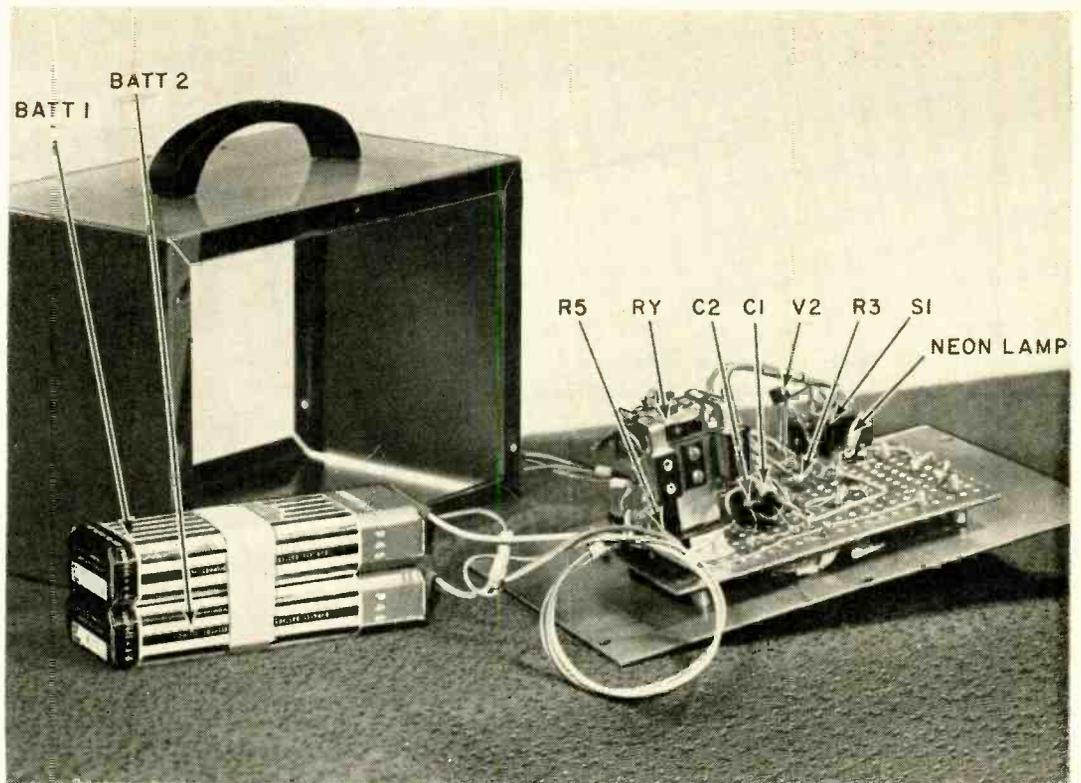

Since parts layout is not critical, this is only one possible way of assembling the unit.

connected in series across the two 67.5-volt batteries. Capacitor C1 and reset switch S1-a are connected across the neon lamp. When the power switch S1-b is closed, current from the two batteries flows through R1 and V1, charging C1. The charging rate for C1 depends upon the setting of R1 and the resistance of V1, which will vary from many megohms in total darkness to a few thousand ohms in bright sunlight. Thus, the capacitor's charging depends on the internal resistance of V1, which in turn depends on the amount of radiation (light or otherwise) striking it.

When C1 charges enough to fire the neon lamp (around 75 volts), a brief positive-going pulse is developed across resistor R2. The pulse is applied, through isolating resistor R3, to V2's base. The pulse momentarily biases the transistor's base positive with respect to the emitter, causing a corresponding pulse of collector current to flow through the relay coil, energizing the relay. A dpdt relay is used, and one set of contacts is connected so that, once energized, the relay stays locked in until the power switch, which is ganged with the reset switch, is opened. Re-

sistor R5 limits relay coil current when the relay armature is energized. If you want the relay to close only momentarily, wire it as shown in Fig. 2.

The timer circuit was assembled on a perforated phenolic-board chassis which is fitted into a metal cabinet. The photocell is mounted in a small metal box and connected to the main timer unit by a length of ordinary line cord. This is done so the photocell can be conveniently located in tight corners if necessary. A barrier type terminal strip is mounted on the front of the timer cabinet, and the photocell and second set of relay contacts are connected to it. The two batteries are held in place with simple sheet-metal straps. Decals dress up the units. Give them a coat of clear plastic spray after they are thoroughly dry. While a tantalum charging capacitor was used in the original model to save space, an ordinary tubular electrolytic will work just as well.

Calibration and operation

The timer must be calibrated before it is placed in operation. The simplest way to do so is to expose the photocell to the light source to be used and, with the unit operating, adjust the CALIBRATE control for the desired timing interval. This must be done with the photocell placed at its normal operating distance from the light source. If the cell is placed at a different distance from the light source, the timing interval will change because of the difference in light intensity.

If the timer is to be operated in applications involving extremely high illumination levels such as direct sunlight, place a filter over the photocell to get a reasonably long timing interval. If such a filter is not used, the photocell's resistance will be extremely

low, and unreasonably large values for charging capacitors will be required for reasonable timing intervals. If desired, a variable aperture can be used in place of a filter. Generally speaking, the filter or aperture should keep the cell's internal resistance somewhere between 1 and 5 megohms when it is exposed to the light source.

If desired, replace the photocell with a fixed resistor and use the unit as a conventional electronic timer. Then the calibration consists of just setting the timing control for the desired timing interval.

A thermistor can be substituted for the photocell if a change in timing with a change in temperature is desired. In fact, any variable-resistance transducer—pressure, humidity, sound—can be used with this timer.

As mentioned before, this circuit is not critical with respect to components and a number of substitutions are possible. If desired, two 45-volt batteries can be used in place of the 67.5-volt units shown. Also, a p-n-p transistor such as the 2N398 can be used in place of the 2N332. All that is required is that the battery and charging capacitor C1's polarity be reversed; no other circuit changes are necessary. A different relay can be used as long as its sensitivity is equal or better than that of the one specified. (It may be necessary to change the value of R5 slightly, if a different relay is used. This resistor should be chosen so the relay just stays pulled in when it is energized. Too low a value of resistance will cause excessive current flow through the relay coil and reduce battery life.) Parts layout is not critical, and almost any desired layout and housing can be used.

Well, that's the story. Why don't you build one of these little timers? You'll be surprised at its many uses. END


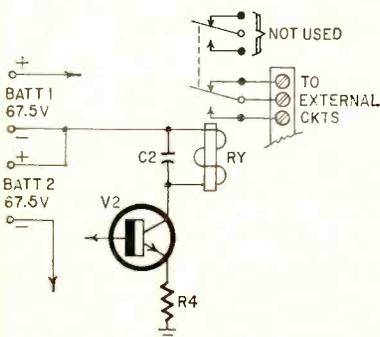


Fig. 2—Alternate circuit for momentary relay closing.

TAMING THE VIDEO IF SYSTEM

Speed up if troubleshooting with these tricks of the trade

By WAYNE LEMONS

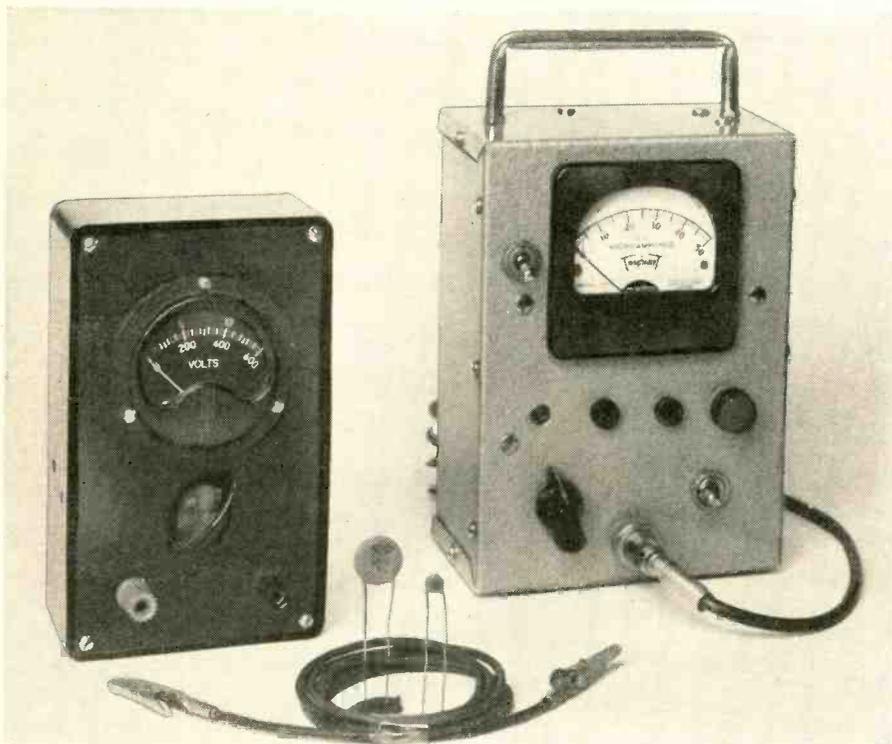

Bias box (left), dc vtm, clip leads and ceramic capacitors are all you need to tame the video if.

THE video if system can be exasperating when it doesn't function properly. It develops troubles that are hard to pin down to a particular stage or component. These problems are all the more difficult to solve because of the high-frequency signal paths involved.

These tricks of the trade that have been developed over the years will speed if troubleshooting procedure. They can help you turn a potential dog into an interesting challenge. They may be just what you need to cure that service headache "twice as fast!"

Test equipment

These tricks do not involve any expensive or complicated special test equipment. A jumper wire with an alligator clip on each end, a couple of ceramic capacitors, a vtm and a bias box are all you need. See photo above.

If you don't already own a bias box, a schematic is shown in Fig. 1. Its


design is quite flexible. About the only precaution necessary is that the output be isolated from the power line. A low-impedance output is necessary so that the bias box can take over the agc line by swamping out any other voltages developed on it. Use a low-resistance high-wattage pot for the VOLTAGE ADJ control. This will insure a low-impedance output, and any voltage on the agc line will not damage the control.

A meter across the bias box output is desirable. This will immediately indicate a shorted agc line. Almost any meter with reasonable accuracy is satisfactory.

Locating a dead stage

Sometimes it is pretty hard to track down the actual defective stage even though you know the if system is faulty.

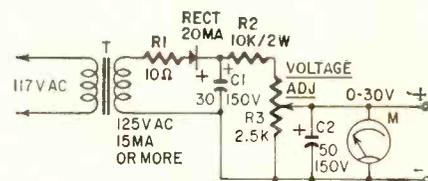Obviously, all voltages should be checked. Check plate and screen voltages and for low or high agc voltage



- R1—10 ohms, 1/2 watt
 - R2—10,000 ohms, 2 watts
 - R3—pot, 2,500 ohms, 4 watts, linear taper
 - C1—30 μ f, 150 volts electrolytic
 - C2—50 μ f, 150 volts electrolytic
 - M—voltmeter, 0 to 30 volts
 - T—primary, 117 volts; secondary, 125v ac, 15 ma or more
 - RECT—20 ma or more, selenium
- Case and binding posts

Fig. 1—Bias box schematic. Transformer may be salvaged from antenna booster.

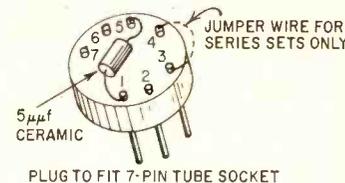


Fig. 2—Small ceramic capacitor mounted on plug completes stage jumper.

at the if tube grid. Make sure the tube is the correct type. An incorrect tube type is commonly overlooked, and can make you feel like a fool when you do stumble onto it.

If no obvious faults are uncovered, we may suspect that the stage is not really defective at all. However, there are so many possible troubles that we can sometimes miss even the more obvious. How often have you wished that you could just substitute a stage for a suspected one? In the video if it's easy! How? Remove the if tube. Take a 5- μ f ceramic capacitor and solder it from the grid to the plate terminal on the tube socket. These are always pin Nos. 1 and 5 for seven-pin tubes. Leave the tube out and turn the set back on. If the stage is defective, you will now get picture and sound because all parts in the stage have been bypassed (with the possible exception of the coupling transformers). You can jump these also with a capacitance link if necessary.

Stage jumper

Fig. 2 shows a stage jumper using a miniature seven-pin plug and a 5- μ f capacitor soldered from pin Nos. 1 to 5. This will let you find a defective stage without pulling the chassis. It may also be used to check an rf stage. For

series-heater sets, connect a jumper between pins 3 and 4. This will raise the voltage on the other heaters while you are testing, but the rise will be so slight as to be unimportant (for test purposes).

After finding the defective stage, you should have no trouble finding the defective part, using conventional methods.

Unfortunately, the stage jumper might be misleading if the set has age troubles. The reason is that the gain of the system is lowered so that, if it had been overloading, it might operate OK when the stage jumper is used. (Of course, the cause of the overload should be found rather than just returning the set to the customer with the stage jumper installed!) But seriously, if the customer is in an extremely strong signal area and the age in his set is inherently poor, the stage jumper might be the answer to a lot of problems.

Checking Tubes

Although checking tubes without a tube tester is not always the quickest way, it can be the most accurate.

You can become adept at checking emission and stage operation by just measuring the voltage drop across the cathode resistor. This voltage repre-

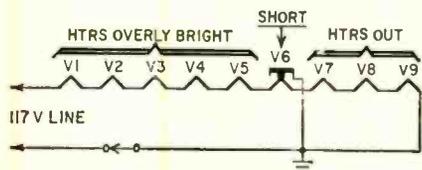


Fig. 3—Heater-cathode short in V6 extinguishes V7, 8 and 9, applies excessive heater voltage to other tubes in string.

sents all the tube currents (except heater) in the stage. Cathode voltage, therefore, can tell quite a story—if you will let it.

For example, let's suppose you have little or no cathode voltage. The trouble could be a defective tube or it could be that the age bias on the grid is excessive. To check tube emission, use a jumper wire between the grid and cathode. For most circuits, simply connect the grid to chassis. Usually the set contains two (or more) stages having identical cathode resistors, so you can compare one tube against another.

The big advantage of making the tube tests in this manner is that the tube is tested under actual operating (or nonoperating) conditions. No tube tester will exactly duplicate conditions found in a set. This method may also show up faults in the circuit such as an incorrect tube type, defective wiring, etc.

Heater-cathode shorts are easily isolated in parallel-heater sets. Clip the jumper wire from the cathode terminal of the tube socket to the chassis. If the hum bar in the picture disappears, you have isolated the defective tube. Sometimes this method will burn out the short in the tube and it will seem to operate normally. It is

usually best, though, to replace the tube.

Heater-cathode shorts in series-heater sets nearly always either burn themselves out or else bypass the heater circuit so that some tubes will light (usually too brightly) and others will not. Tubes that do remain lit may be damaged by excessive heater voltages. A simplified schematic (Fig. 3) shows how this happens.

Checking for gas or grid leakage is a little more difficult but can be done. Disconnect the leads from the grid and cathode terminals of the tube socket. This leaves the tube grid and cathode floating. Now, using a vtvm, measure the voltage on the floating grid terminal (Fig. 4). Any tube with a positive grid voltage, though small, must be replaced.

Note that all elements in the tube except the control grid (and suppressor grid and heater, which are not important in this test) are at a relatively high positive voltage. Any leakage to the grid is therefore indicated as a positive voltage.

Stacked stages

A few manufacturers have used stacked video if stages—two tubes in series across the power supply. Fig. 5 is a schematic of a stacked stage similar to that used in some Zenith models. They can be tricky to troubleshoot. For example, if you have little or no plate or screen voltage on V1—the trouble is almost sure to be in tube (or stage) 2! This could be caused by a defective tube or by an open 56,000-ohm resistor from the B-plus line.

Note that this resistor sets the bias for V2's grid. This positive bias on the grid of V2 causes it to conduct. V2's cathode is in series with tube V1 and goes positive. This voltage is used as the plate and screen supply for V1. This circuit is similar to that used in cascode rf amplifiers.

Touchup

Touchup of the if stages is often frowned on by the so-called professionals, especially the text-book set. You will find from actual experience though, that touchup can be the lesser of many evils. It should be used only when it is apparent that no other method will produce the desired results.

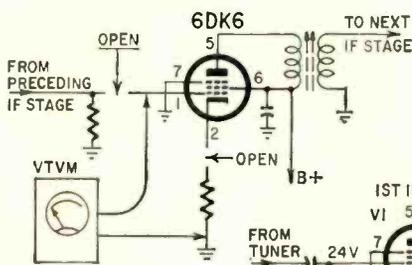


Fig. 4—If the grid is positive, the tube is defective.

For instance, we don't recommend it when using a built-in antenna or rabbit ears. Moving the antenna can upset the overall response of the set and make touchup useless. If, however, an outside antenna is used, a touchup may mean the difference between a passable and a really good picture and sound.

Don't go hog wild, but if you have a sound buzz that is obviously caused by too much sound gain in the video if (and you can't eliminate it with adjustments in the sound if or age system) moving one of the if slugs slightly may eliminate the buzz. Adjust for the best sound while watching the picture. You will usually find an adjustment that produces both good sound and picture. If a slight turn smears the picture, move the slug back and try turning it in the opposite direction.

Touchup can also improve picture detail. If the fine detail is hard to make out, a slight adjustment of one if slug may produce a crisp, clear picture (or you might need glasses).

Touchup may be required even after a sweep alignment of the video if. This need may be caused by either poor alignment equipment or improper technique. Next time try the touchup procedure *before* you align the set. You may get a world of improvement with just a "twist of the wrist!"

Re- and degeneration

Although regeneration and degeneration are exact opposites, they can be caused by the same component going bad. This depends entirely on stage design. An open bypass capacitor may cause a stage to oscillate (regeneration) or have low (even less than unity) gain (degeneration).

Regeneration symptoms take many forms but usually herringbone lines appear in the picture or (if severe) the picture may actually appear negative. Because regeneration can also affect many types of age circuits and cause them to produce excessive voltage, the screen may be blank (raster but no picture).

Measure the voltage across the detector load resistor (Fig. 6). If the if system is oscillating, the drop will be several volts even though no station is tuned in.

A good method for isolating the os-

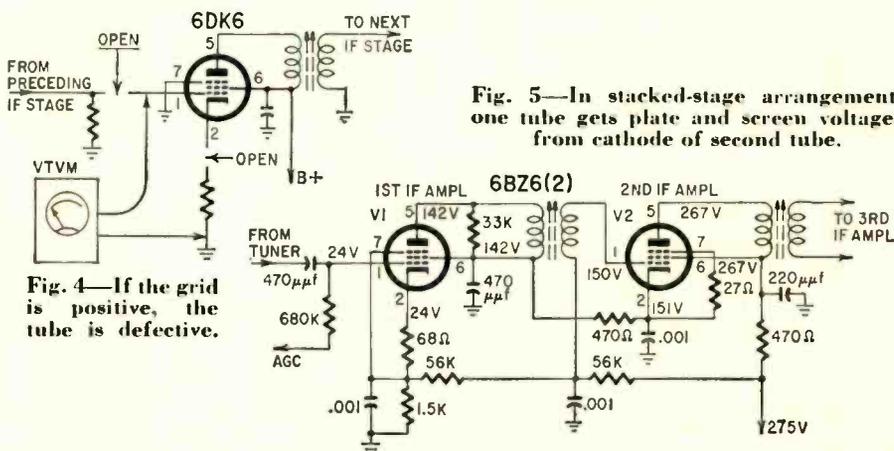


Fig. 5—In stacked-stage arrangement, one tube gets plate and screen voltages from cathode of second tube.

oscillating stage is: beginning with the first if, pull the tube while watching the voltage across the detector load resistor. If the voltage drops to near zero when the tube is pulled, then either the stage is oscillating or is part of an oscillating network. If there is no voltage change, move on to the second stage, etc.

Once you have found the defective stage, check for missing tube shields, defective grounds, incorrect tube type, open suppressor-grid connection or open bypass capacitors. The capacitor giving the most trouble is the screen and plate decoupling bypass. This capacitor, when open, can also cause degeneration and washed-out pictures.

Improper alignment may cause regeneration but this is rare unless the set has been tampered with. So look for all other possibilities first.

The stage jumper described at the beginning of this article is ideal for spotting a case of severe degeneration. It may also be helpful in spotting a regenerative stage (and determining if other troubles exist).

Agc problems

Of all the difficulties encountered in the if system, perhaps none is more dreaded than an agc problem.

Here's what we feel to be the best approach. First, use a bias box to *make sure that you really have an agc problem*. A symptom that points to the agc system may be caused by something else entirely. The bias box, when connected to the agc line, will restore the picture at some voltage adjustment—if the trouble is caused by improper agc action.

The bias box will determine whether the fault is in the agc system. Tracking down the actual defective part is seldom so easy. But, at least we now know where to look.

There are many types of agc circuits. It would be impossible to discuss them all in this article. Usually, as with most

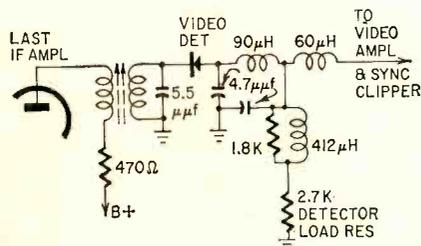


Fig. 6—Typical video-detector stage.

TV problems, trouble is caused by a component failure. In some cases though, perhaps only an adjustment is necessary.

Keyed agc circuits are usually more difficult to troubleshoot. A trick or two here is essential. First, if you find that you have little or no agc voltage, divide the circuit—find out in which direction the fault is.

Artificially "keying" the agc keyer tube is an easy way to divide the circuit. Use a jumper wire between the keyer tube grid and cathode. This will zero-bias the tube, and it will conduct, producing 15 to 50 volts negative on its

plate *unless* something is wrong in the keyer circuit. If you get little or no negative voltage, it is likely that you have a defective keyer tube or wiring or that you are not getting the keying pulses from the horizontal sweep circuit.

If the keyer seems to operate correctly, the fault obviously is in the keyer biasing circuit. The keyer's grid-bias voltage is usually developed across a video plate-load resistor, but is sometimes developed by the first sync stage. Any fault in the keyer biasing stage will upset the keyer bias. Fig. 7 shows a typical biasing arrangement for a keyer tube.

A defective video-detector diode is a frequent cause of agc problems even though it may detect the signal properly. The diode should also be suspected if the agc is slow to "take hold" when changing channels.

Another thing to look for in the agc circuit is an open or partially open agc bypass filter. This can cause what appears to be a sync problem. An open bypass will nearly always cause critical vertical hold and may cause the picture to bend or tear. If this is suspected, bypass the agc line with a 2-µf filter capacitor while watching for improvement in the picture or sound.

Shorted bypasses sometimes occur. Often they are not suspected because the voltage on the agc line is normally low. (This is a common fault in RCA KCS47 series. When you have an agc problem with one of these, be sure to check for a shorted bypass.)

Too much agc voltage will lower gain in the video if stages and the tuner. Quite often a set may appear normal on a strong local station, but be completely insensitive to weaker stations. A meter on the agc line may indicate several volts negative. The most common cause for this condition is an open bucking or delay resistor. This resistor ranges in value from 4.7 to 22 megohms and is tied from the B-plus line to the agc line. Often it is tied only to the tuner agc but occasionally it is also tied to the video if agc. When this resistor opens, it allows the negative voltage on the agc line to rise above its normal value (go more negative) with resulting lower gain. So whenever there is no snow on an inactive channel, it is wise to check the agc voltage with your VTVM.

Don't overlook the possibility that a hidden agc control may be incorrectly adjusted. When working on any set, it is always wise to have a schematic of the set for reference.

Intermittents

An intermittent if system, as with any intermittent, can be vexing. Probably no procedure will work every time. Whatever the procedure, however, we must always make sure the trouble is duplicatable. By this we mean that you should be able to produce the symptom by *causing* the defect in the suspected circuit.

For example, if you suspect that a printed circuit is open at a certain point, make sure it is—by cutting

across it (you're going to repair it anyway). When you deliberately open it this way, it should produce the symptom (that had previously been intermittent) on a steady basis. Only by making sure, in duplicating the fault, can you be really positive that you have corrected the intermittent.

Quite often you are tempted, when confronted with an intermittent printed circuit, simply to run a bead of solder over each conductor and heat each terminal, then hope for the best. This *may* do the trick, but you can't ever be

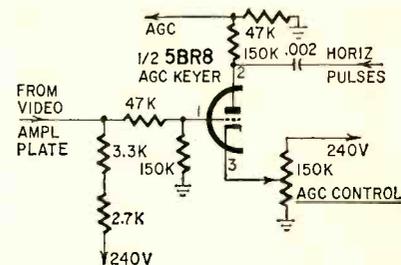


Fig. 7—Keyer tube in keyed agc circuit.

really sure and you get no sense of satisfaction from the job. There always is the nagging worry that something may have been overlooked.

One big source of intermittents is tube sockets. If they are the wafer type, they can be crimped from underneath (with the tube removed) so that a firmer connection is made to each pin. The molded type tube socket and the wafer type used with printed circuits usually cannot be repaired if they make poor connection to the tube pin—but something else can be done! Bend the tube pins out, then back in so they are slightly bowed (don't try this with an octal-based tube). This will insure a tight fit in the socket and just about eliminates any intermittent conditions from that source.

[Bending all the pins can be a bit tricky so this method works best when you know which pin is intermittent. Also, coating the intermittent pin with a light film of solder is a good expedient. In either case, be careful and don't crack the tube.—Editor]

The stage jumper described earlier is an excellent stage isolation device. It bypasses so many parts that it is practically foolproof. Slip it in the suspected stage in place of the tube. If the intermittent disappears, you have only to concentrate on that particular stage to find the trouble.

Summary


Finding needles in haystacks is difficult only when we must look through *all* the hay. If we could narrow down the location of the needle to a single cubic foot of hay in the haystack—finding it would be infinitely easier. So it is with TV troubleshooting. If we can confine our search for the defective part to a small portion of the TV receiver, we have the battle almost won. We hope this article may help to make it a little easier for you to pinpoint both defective stages and defective components in the if stages. **END**



about

OUTPUT

TRANSFORMERS

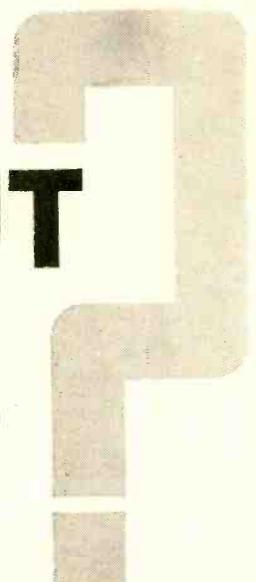

You can measure the turns ratio and power handling ability of that idle transformer and put it to use

By NORMAN H. CROWHURST

PEOPLE write to me for advice about output transformers. They want to know which one to get, or whether a certain transformer can be used in a particular way. They quote manufacturers' catalog numbers, or even send me sheets torn from catalogs. But my chances of answering these questions (with any authority) from catalog information stands only the slightest chance of being better than their own semi-educated guesses.

Then, of course, there's the case of the "unknown" transformer that's been lying on the shelf. Maybe it could be used for something, but how does one go about finding out its specifications? Or maybe the specification sheet reads 4,000 ohms center-tapped to 4, 8 and 16 ohms. Could this be used for an 8,000- (or 2,000-) ohm load?

First, it is practically impossible to tell from published specifications which is the better of two transformers *even for its own job*. What complicates matters here is the fact that no two manufacturers list the same data. Some list rated power, impedance and frequency response (even if it only says 20-20,000 cycles). Some state the permissible primary plate current, while others specify the permissible dc unbalance in the two halves of the primary. Some give dimensions, with or without a case, while others also include weight. From such diversified information how can any-

one compare products of different manufacturers?

If rated power is given, it probably does not state the lowest frequency at which this power can be handled. One can only presume, with no guarantee of being correct, that the lowest figure quoted under frequency response (if this is given) is applicable. The impedance figure says what it was designed for, but not necessarily for what mode of operation. A transformer that works well with triodes or triode-strapped pentodes may not do so well with pentodes, *or vice versa*. Taps may be provided for "universal" application, but can these be used for Ultra-Linear? Frequency response is given, measured in a "standard" test circuit that represents no practical output arrangement.

So the more you know about transformers, the more you realize the specifications usually printed don't really tell you anything, except that the unit is designed for a specific purpose or as a replacement for some other type. The best answer is take one and measure it. But what simple measurements can we make to find out a transformer's capabilities?

Transformer characteristics

The first thing to find out about an unknown transformer is its ratio. Apply line voltage to its primary—this should be less than the plate-to-plate voltage it normally handles, so should not saturate it. Then measure both the primary voltage and the secondary voltage, with a suitable voltmeter (Fig. 1). Don't bother about loading it. The ratio between the voltages gives the turns ratio of the transformer, as close as your voltmeter can measure it.

Suppose the line voltage reads 115

and the secondary voltage 4.6. The overall ratio is $\frac{115}{4.6} = 25:1$. While you're

at it, check that a center tap does divide the voltage equally. Don't rely, though, on its being exactly half—your voltmeter may not be that accurate. Rather check that the reading on each half is *the same*. Both halves may read 60 volts (or 55) although the total is 115. This is probably scale error on the meter. By the same token the actual ratio may be anywhere between, say, 22 to 1 and 27 to 1 for those readings. But loudspeaker impedances aren't so close that you need to be more critical.

Now you know the turns ratio is 25 to 1. The impedance ratio, or transformation, is this squared, or 625 to 1. It might be 10,000 to 16 ohms, 5,000 to 8 ohms, or something like that. Allowing for your voltmeter error, if the ratio is 22 to 1, the impedance ratio is 484 to 1. If it is 27 to 1, the impedance transforms 729 to 1. On this basis, an 8-ohm load would be transformed to something between 3,900 and 5,800 ohms—that's if it really is 8 ohms and if the transformer losses don't modify it slightly.

But now you know the ratio, what impedances was it *intended* for? That you may never know. More to the point is, what impedances can you *use* it for? One way to tackle this is to measure the winding resistances. *Then a simple approximate rule is to multiply the resistance of each winding by the expected power-handling capacity.*

Suppose you want to handle 20 watts and the primary resistance measures 300 ohms. The intended impedance is *probably around* 6,000 ohms. If the secondary resistance is 0.75 ohm, the same calculation would give its im-

Transformer Power-Handling Capacity (Transformer saturates at 31 volts)

Secondary Impedance (ohms)	Lowest frequency for listed output (cycles)			
	20	30	40	60 \curvearrowright
8	13.3	30	53	120 watts
12	8.9	20	36	80 watts
16	6.7	15	26.7	60 watts

Chart for hypothetical transformer.

pedance as $20 \times 0.75 = 15$ ohms. But 6,000 to 15 is *not* 625 to 1. Does this prove your voltmeter readings were off? More likely the use of convenient wire sizes does not allow equal losses in both windings. If 15 ohms is correct, then the primary should be $15 \times 625 = 9,375$ ohms. The ratio could have been intended for 7,500 to 12 ohms, splitting the difference. But this is only a rough guide.

The thing to recognize is that the resistance of the windings is your main loss, except at the low-frequency end. If each winding has a resistance 5% of its working impedance (or if your working impedance is 20 times the measured resistance of each winding), the transformer will work at 90% efficiency. If all winding resistances are then halved in proportion to their respective impedances, the efficiency rises to 95%.

Power measurements

To find the actual power-handling capacity, find out where the transformer saturates. To do this, you will need a 5,000-ohm 4-watt potentiometer as well as a scope. Connect as in Fig. 2. Now turn the pot up until the waveform goes distorted. Take a voltage reading at the point where it just departs from a sine wave. Add about 20%, and this is the voltage-handling capacity at 60 cycles.

Suppose you get 26 volts. Add 20%. This gives about 31 volts. If your secondary impedance is 16 ohms, the 60-cycle power rating is $\frac{E^2}{Z}$, or $\frac{31 \times 31}{16}$, or approximately 60 watts. If you use it for 8 ohms (in which case your efficiency will be lower), it will handle $\frac{31 \times 31}{8}$, or about 120 watts, at 60 cycles.

Presumably this is a high-fidelity transformer, in which case power is required to a frequency lower than 60 cycles. Just divide by the square of the ratio between the frequencies (for example, 60 cycles to 20 cycles or 3 to 1, square is 9). We have drawn up a little table (Page 33) for the rating of the imaginary transformer we just measured.

Now we can see the answer to the question about whether a transformer can be used for other impedances. Used for 10,000 ohms to 16 ohms, the winding resistances are about 5% each, primary and secondary, so the transformer is about 90% efficient and will handle 20 watts down to about 35 cycles (interpolating the lower line of the table). Used for 5,000 ohms to 8 ohms, the efficiency drops to 80%, but it will handle 20 watts down to about 25 cycles (interpolating second line).

Actually, using different impedances will also affect the high-frequency response. But to predict this you need to know more about how the transformer is wound—its winding sectionalizing—as well as the output circuit. However, we can lay down some ground rules.

Mode of operation

Starting with the impossible first:

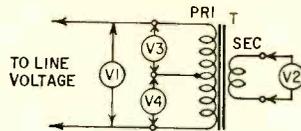


Fig. 1—Measure all the ac voltages indicated to determine the turns ratio.

pentodes in class B, or semi-class B (class AB), require very specially designed output transformers—don't try it with strangers! But pentodes in class A are a fairly safe bet with a simple inexpensive transformer, using little mixing. You can use feedback without too much likelihood of trouble. Such a transformer will show equal voltages on primary halves in the ratio test, but will *not* have equal resistance in each half.

With triodes, or triode-connected pentodes, you should look for a "better" transformer—one with more mixing or interleaving of the windings. One where the resistances of primary halves measure the same, as well as its ratio showing accurate center tap, is a good one to try.

If you want to try Ultra-Linear operation, my advice is to buy a transformer designed for it. But you can try a universal job, if you have one around. Use the outside ends for the plates. The square root of the nominal impedance ratio will give the percentage tapping for the screens. If the outside ends are nominally 14,000 ohms apart, the 4,000-ohm taps will be $\sqrt{\frac{4,000}{14,000}} = 0.535$, or 53.5%. That's the nearest you can come to 43%. Higher taps will represent higher percentages.

Another thing about these universal jobs: they are designed as a "replacement" item. Being a stop-gap measure, their performance is below the standard of items designed for a specific job. A really high-quality universal transformer can be made, but it is a laboratory item at a price that would put it out of the replacement market—or any commercial application.

Catalog specifications

So much for transformers you can take and measure. But many inquiries are concerned with possible alternatives to buy, and the only information available is that in the makers' catalogs.

If weight is quoted, this can give you some clue about low-frequency response, where the specification omits this information. A transformer with good low-frequency response and reasonable efficiency for its power rating will run between 2 and 3 watts per pound. So a 20-watt transformer will weigh between 6 and 10 pounds. These so-called "universal" jobs usually run 10 watts or more per pound, as do most kitchen radio outputs.

Nominal power is usually quoted, but since it does not say "... watts at ... cycles," the figure does not mean much. As the tabulation showed, a transformer that will give 20 watts at 30 cycles can handle 80 watts at 60 cycles. Specification of frequency response from 20 to 20,000 may or may

not mean it will handle its rated power down to 20 cycles.

Incidentally, the type of output circuit can affect this too. Some circuits can supply quite a hunk of saturation current in the output transformer before distortion shows up, others cannot.

A few definitions

When you look at a catalog, you read everything pertinent if you really want to make a critical choice. Knowing this, catalog writers put in all kinds of flowery descriptions—"scientifically designed," "using the latest engineering principles," "applying improved techniques," etc. The implication drawn by the tyro is that a manufacturer who does any of these things has a better product than one who does not.

Unfortunately, *some* who make these

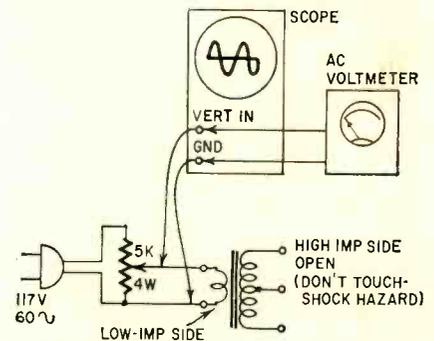


Fig. 2—An oscilloscope and ac voltmeter are used to determine the transformer's power handling capacity.

claims apparently follow these definitions:

Scientifically Designed: A process consisting of buying a competitor's sample of a new line, pulling it apart, and making a "Chinese copy."

Latest Engineering Principles: The engineer bought a new slide-rule, so no longer counts on his thumbs. He has learned to use scales A, B, C and D and may some day learn what all those other scales are.

Improved Techniques: If the competitor used black paint, we dip it in shellac. This *may* make it more durable, but does not affect its performance.

It should not be inferred that all manufacturers use such methods, but I have been surprised to find how many do! A few years ago I wanted some special filter transformers made. I had worked out the necessary data; all I needed was someone to wind them. But this was unorthodox—"we don't work that way," "our engineering department does all our design work."


However, after one company had made them to my data, the rapidity with which other companies produced Chinese copies was surprising. My experience tells me, when a representative (styled a "sales engineer") gives me a pitch about his company's superior engineering facilities, to take it with "a grain of salt." A company that's really progressive, in transformers as with other things, is one that's first with really new lines. And don't always believe advertising that says "another first!" Watch to see who really is first.

END

TRANSITONE LOCATES HIDDEN WIRING


Conduit imbedded in a concrete wall or buried underground can be traced easily with this simple instrument

By HARRY D. PARKER

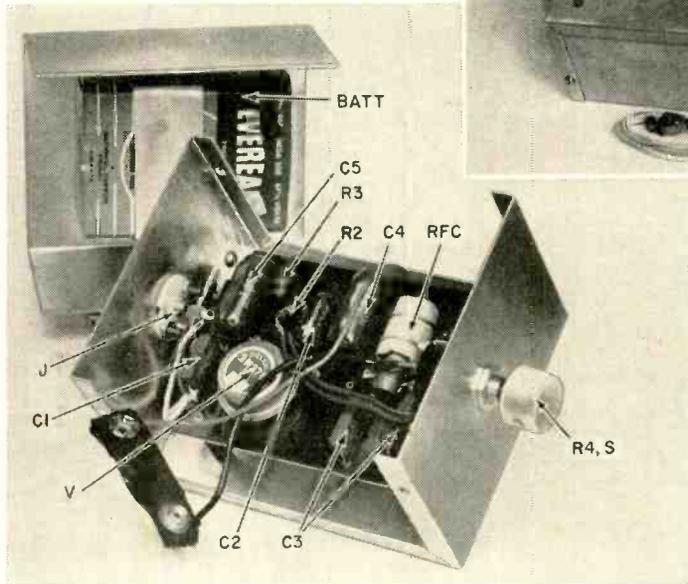

Finished unit forms neat package.

Parts arrangement inside aluminum case.

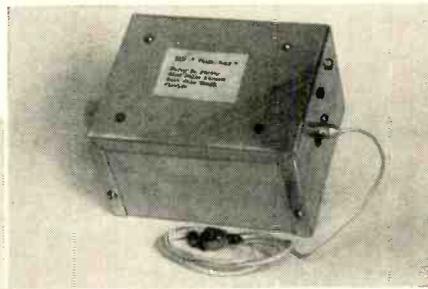

a 50-volt collector rating, so with proper biasing the voltage may be raised to any level as long as the collector-to-emitter voltage does not exceed 50 and the collector power rating is not exceeded. The low current drawn by the unit (about 4 ma) is so slight that the transistor does not need any heat sink.

All components are mounted on a 3 x 4-inch phenolic board, and wiring is straightforward.

A 3 x 4 x 5-inch case houses the unit. A phono plug and jack with a clip lead is used for the output connection. Brass spacers 1/2 inch long are used to mount the phenolic chassis to the cabinet. A metal strap holds the battery in place and a standard snap-on battery terminal connects the battery into the circuit.

Now use it

The unit is tuned with L's slug or with R3. Use the slug to center the frequency on a quiet spot in the AM band and fine-tune with the pot. Don't vary R3 too much as it affects the base bias and may make the circuit stop oscillating.

The receiver is only a means of detection and any home portable set may be used or you may make one just for this purpose.

The transmitter, when connected to a pipe line, does not radiate very far into the surrounding air, only a few feet at best. So, no matter how much power is used, you are not breaking FCC requirements. But don't let this fool you either as the signal may be picked up several blocks away on the pipe line. It has proved ideal in large motels when we wanted to know where existing wiring was so as not to cut into it when cutting through walls during a TV antenna installation. END

MANY times a service technician has to know where wiring conduit is located. This is especially true when installing electronic equipment (sound systems, intercoms, fire and burglar alarms, etc.) in hotels, apartments, warehouses, factories, etc. The little transistor Transitone will find the conduit for you.

The unit consists of a tone-modulated transmitter and any portable broadcast radio. Here in the South, as in many other places, building regulations state that wiring conduit and plumbing must be buried in the concrete walls and floors. So when future installations or repairs have to be made, it is convenient to know where the conduit is. Just clip the Transitone's antenna to the case of an outlet box or a water pipe and with a transistor radio tuned to the transmitter frequency you can trace the tubing through the building. Chalk lines on the walls or flooring to indicate the tubing's position. Many other uses are obvious; such as locating buried wiring in outdoor stadiums, from house to garage and so on.


Circuit description

The transmitter consists of a simple rf oscillator and is self-modulated by

the blocking action of C4 and R1 (see schematic). Varying C4's value changes the transmitted tone and the power output. R2 and R3 are base-bias resistors and C2 is the base rf bypass. Capacitor C3 is the feedback capacitor that starts and maintains oscillation. If it is too small, the circuit won't oscillate; if too large, you can't get the frequency high enough. Coil L and C1 act as a ringing circuit and determine the frequency. Changing either L or C1, or varying the value of R3 shifts the frequency. A small pot (R4) (about 25,000 ohms) may be used as a fine frequency control instead of L's adjustable core. Varying the supply voltage will also shift the frequency slightly. Capacitor C5 is an rf bypass across the power supply. The rf choke is a horizontal oscillator coil for a TV set and is part of the audio blocking network that includes C4 and R1.

A toggle or slide switch is inserted in one battery lead. If you use a control for R3, a switch could be included with it.

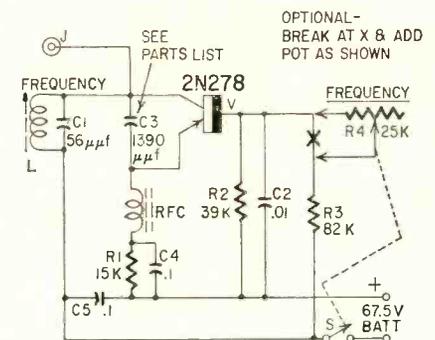Notice the battery voltage. It is 67.5 volts. This may confuse you as most transistors are operated at 6 or 12 volts. This unit will oscillate at a lower voltage but it will not be tone-modulated. The Delco 2N278 transistor has



Circuit of 1-transistor transmitter.

- R1—15,000 ohms
- R2—39,000 ohms
- R3—82,000 ohms
- R4—optional pot. 25,000 ohms with switch
- All resistors 1/2-watt 10%
- C1—56 μf mica
- C2—.01 μf, ceramic
- C3—1390 μf, .001 μf and 390 μf in parallel
- C4, 5—0.1 μf
- BATT—67.5 volts
- J—phono jack
- L—ferrite antenna for broadcast band
- RFC—horizontal oscillator coil, Thordarson HS-30 or equivalent
- S—spst on R4 or separate toggle
- V—2N278
- Case—3 x 4 x 5 inches
- Miscellaneous hardware

TRACE

Simplifies Servicing

Easy to use aid that speeds transistor radio servicing may open the door to a new era in printed-circuit service techniques

By **LARRY STECKLER**
ASSOCIATE EDITOR

TRANSISTOR Radio Automatic Circuit Evaluator (TRACE) is a group of five words that may spell out a new approach to servicing electronic devices that use printed circuits. In this first version, it is the work of a single manufacturer, and is adapted to transistor radios only. It could just as easily work for hi-fi amplifiers and preamps, TV sets or any other kind of electronic gear that incorporates printed circuits.

In its present form, TRACE consists of a folder containing nine plastic-coated cards—one for each transistor radio chassis in the 1960 Philco line. More will be issued as newer sets are made, and Philco is currently considering issuing TRACE boards for older sets.

A typical TRACE board is shown in Fig. 1. It is printed in four colors—black to indicate components and voltages; blue to show the rf signal path and rf generator setting; red for the if signal path and the proper generator setting, and green to indicate the audio path and generator setting.

Servicing is simply a matter of signal injection, a procedure familiar to all service technicians. Starting from the speaker, a signal generator is used to inject a signal into the receiver at the proper frequency. Then the technician works his way back through the receiver to the antenna. The trouble always lies between the last point where a signal is heard in the speaker and the first point at which it isn't. Naturally, the technician changes his generator

settings as he works through the various types of circuits in the radio.

Using TRACE

This is a standard troubleshooting procedure and can be followed with or without TRACE. But by using a TRACE panel, the technician knows just where to apply his signal generator and doesn't have to keep referring back and forth between set, schematic and printed circuit to determine which point is which. He refers to the schematic only after the trouble is localized and when he has to replace a component. Now let's see how this works. The TRACE board shown in Fig. 1 matches the circuit shown in Fig. 2. Both are for the Philco model T-901 code 124.

This is a nine-transistor set with a push-pull output stage.

So let's take a short walk over to Harry's Radio & TV Repair and see how he handles one of these sets. There's one on his bench—must have just come in. Harry's first step is to make some preliminary checks:

- ▶ Are the batteries good?
- ▶ Are the battery terminals corroded?
- ▶ Is the on-off switch OK?
- ▶ Does the tuning capacitor have any shorted plates?
- ▶ Is the printed-circuit board cracked?
- ▶ Is there an obvious open in the printed-circuit board?
- ▶ Is the antenna OK?
- ▶ Is the speaker working?



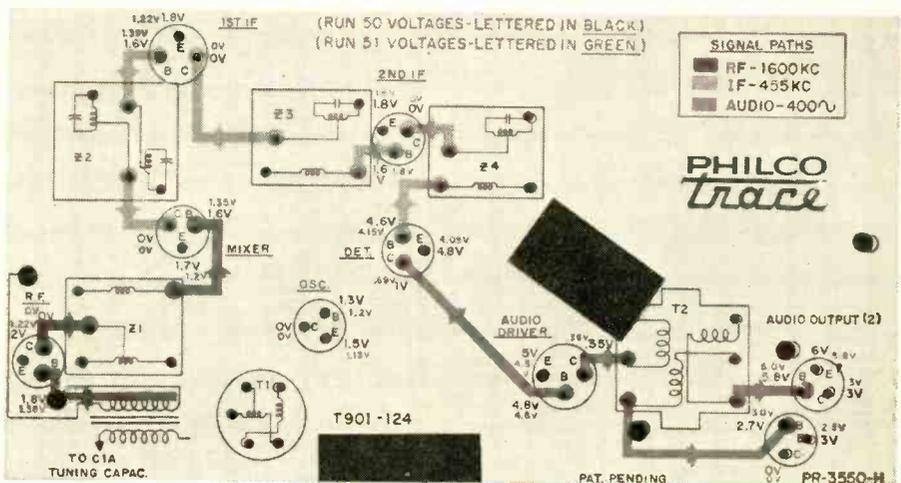


Fig. 1—Philco TRACE board for model T-901 code 124 transistor radio.

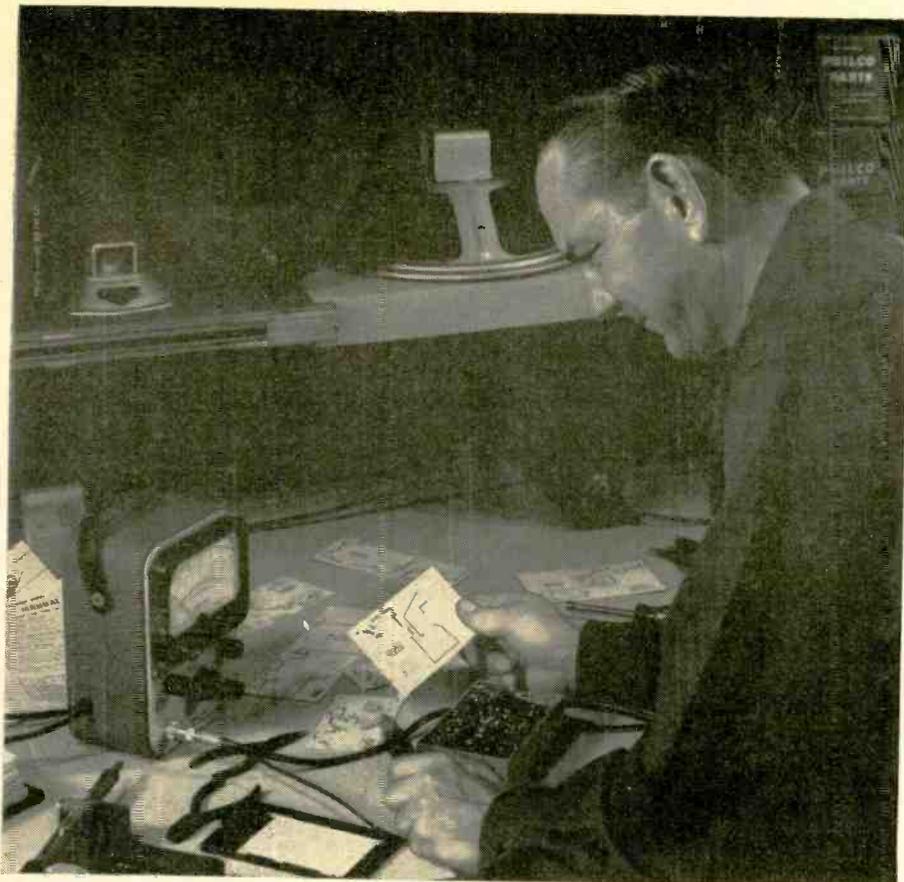

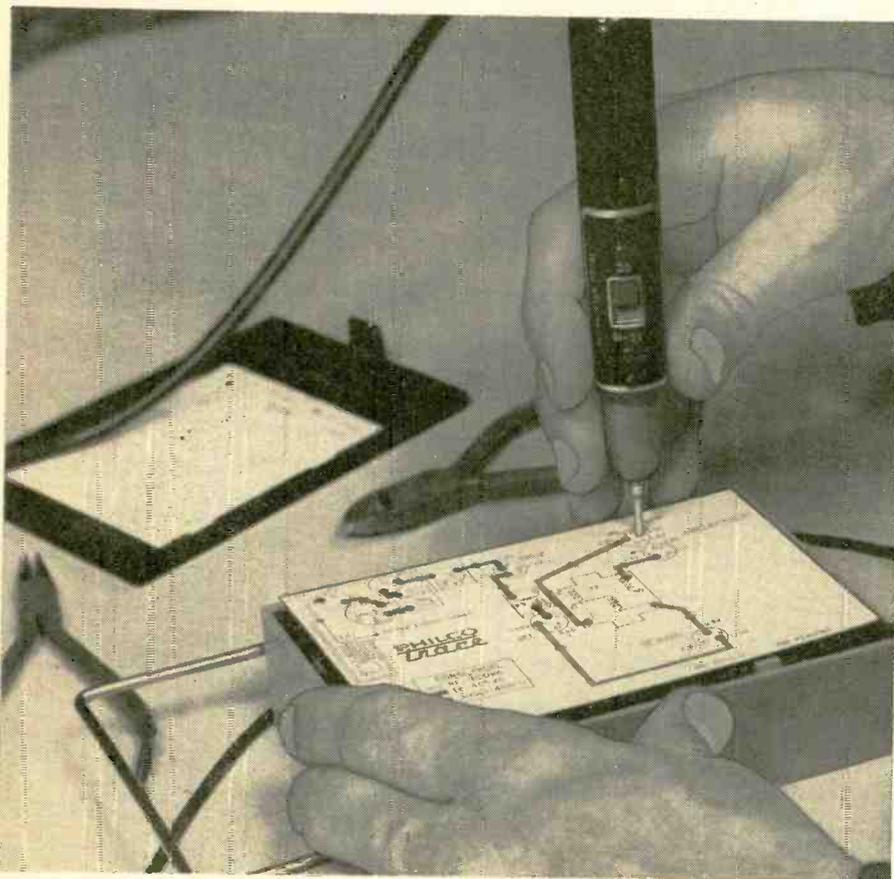The technician picks out the proper TRACE card for the receiver he is working on.



Vtm measurements pinpoint the defect in the radio.

- ▶ A lower than normal emitter voltage reveals a shorted transistor or a low resistance in the base circuit.
- ▶ If the base voltage reads high, it shows a shorted transistor or an open or high resistance in the base circuit.
- ▶ Lower than normal base voltage could mean an open transistor or a short or low resistance in the base circuit.
- ▶ Higher than normal voltage at the collector usually means a shorted transistor or an open or high resistance in the collector circuit.
- ▶ A lower than normal collector voltage means an open transistor.

There is one thing to remember when checking voltages in transistor circuits: A high or low voltage does *not* mean 10 or 20 volts higher or lower than normal. A difference of only a few tenths of a volt is considered high or low and can keep a transistor set from working. After all, we are dealing with voltages that measure only between 0 and 6, and in many circuits never get higher than 1 or 2 volts. A few tenths of a volt is an appreciable portion of these small voltages. This means the technician must have a voltmeter he can trust, one that is accurate and is capable of measuring small voltages. The rule that a technician must be able to rely on his instruments is doubly valid in transistor work.

General service hints

TRACE or not, the usual general service rules still apply. Distorted sound usually means a bad speaker or output transistors. Motorboating, when not caused by weak batteries, is usually due to an open B-plus filter. Low sensitivity is often the result of trouble in the antenna, rf or if stages. No reception at the high end of the broadcast band calls for a check of alignment and the converter transistor. No reception at the low end of the band can be caused by a defective converter transistor or low supply voltage.

Some service technicians take a short cut to signal injection servicing. They start off by applying an if signal to the input of the detector. If they get a good signal from the speaker, they know that the whole audio section is good. Next they go to the mixer and apply a signal at the mixer base. Again either the whole if checks good or the trouble lies between the mixer and the detector. But whether you use the short cut or follow the time-tested technique of running through the whole set from speaker to antenna, TRACE will speed repair time and make it possible for you to give your customer a reasonable repair bill. Every hour of your time is worth at least \$6, so if you save 15 minutes, you're ahead \$2.

Other manufacturers are sure to follow with their versions of the TRACE board. One is already out. G-E is turning out a similar device called Silent Partner, a single-color card encased in laminated plastic (Fig. 3). Each card comes in its own envelope that has the set's schematic printed on the back. Only one card is out to date, but more are sure to follow. END

ULTRA-SENSITIVE 3-Transistor RADIO

Standard-size components and a large loop antenna give sensitivity and selectivity far above average 3-transistor set


By **JOSEPH AMOROSE**
and **EDWARD HOFFMEISTER**

BACK in the early '50's, RADIO-ELECTRONICS printed an interesting original receiver circuit by Edwin Bohr. The set was a good performer; it had sensitivity, stability and other fine features. So intrigued were the authors by this circuit that they carried on experiments to simplify, sensitize and otherwise improve this novel hookup for several years. (Hoffmeister did the major part of the research.)

Primarily, the plan was to come up with a set that was unusually sensitive. It had to be selective, easy to make and tune, use few parts, be economical to operate and, last but not least, it had to be long-lived and troublefree. In striving for such an above-average receiver, we feel that we have achieved our aims.

The set shown is unusually sensitive. Selectivity is high enough to warrant vernier control. Although designed solely for headphone use, the rig will work a speaker on strong nearby stations. With a class-B audio stage added, this receiver has outperformed a well-known manufacturer's superhet rig. It got more stations, produced more volume. Tested in an all-metal car, housed in a metal garage, the receiver still brought in four of the local, louder stations, with "no strain, no pain." Since most Richmond stations are about 10 miles away and use only 5,000 watts input, receiver sensitivity must be considered very good. In the open, all eight locals could be tuned in with ease.

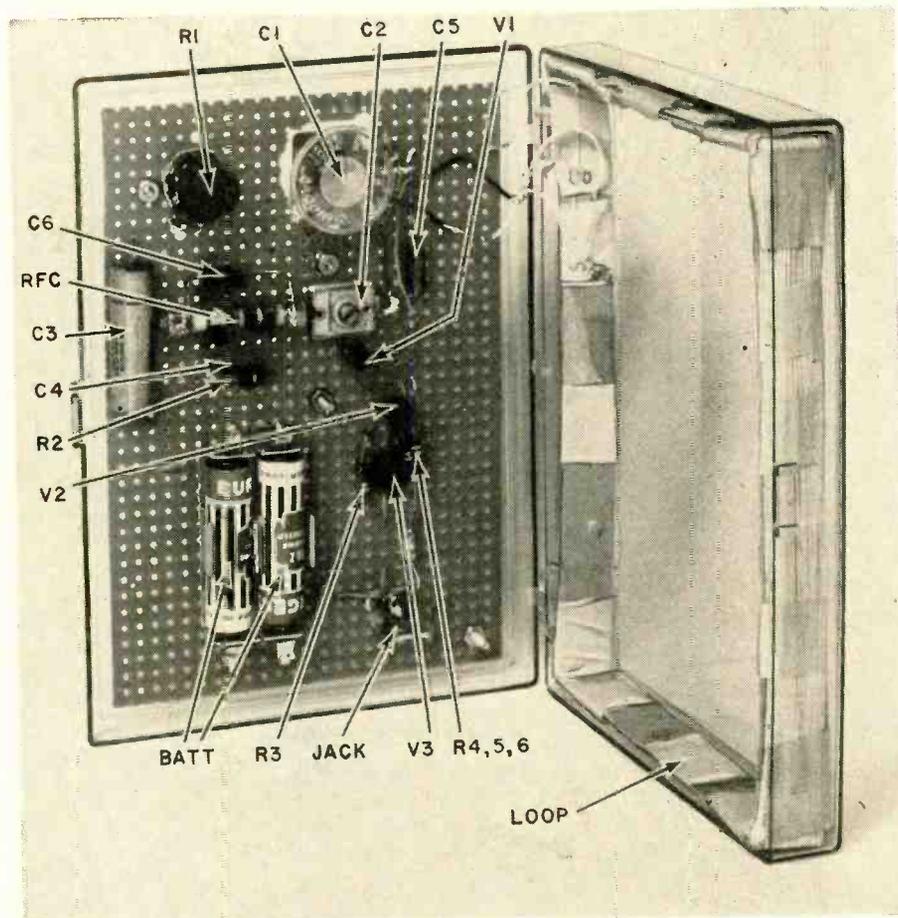In St. Louis (Hoffmeister's home town), all 11 stations between 550 and 1600 kc were received clearly. The dx log there was impressive too. Regeneration is smooth, sure and noncritical. The most sensitive spot is easy to find and hold. There is no annoying, sudden "spilling over" into oscillation.



Lid-mounting parts makes set more accessible and separates it from antenna.

Since utmost sensitivity was desired, no attempt was made at miniaturization; full-size parts were used. Yet they fit comfortably, without crowding, in a 5½ x 7½-inch cabinet—overcoat-pocket size. This set makes an ideal bedside companion for the hospital patient who wants more variety in his radio fare than hospitals' "single-shot" systems provide. It has proved a natural for patients lolling around on the sunporches too.

Construction

The schematic is self-explanatory and should be easy to follow. The loop antenna is a most important part of this set. Upon its proper impedance and the correct tuning of the associated circuits

depends the high performance of the whole receiver. In strong-signal areas, a tapped Ferris-loop coil works well, but with lessened sensitivity.

To wind the loop, make a 5½ x 7½-inch cardboard form. On it, wind 23 turns of No. 24 double-cotton-covered wire. Tap at the 8th turn. This lead goes to C2, the regenerative padder capacitor. *Wind the loop in solenoid fashion!* Jumble winding won't do; it requires more taps to cover the band. Pancake winding is OK if the proper inductance is approximated. Run the 23d turn to the stator of C1; the first turn goes to C1's rotor. (Reverse these two leads if hand-capacitance is noted. Also, try a .001-μf capacitor across the phone cords.)


BENCH



TESTED

Tested in Brooklyn, this receiver picked up 12 stations. At a point a little over 20 miles from New York City, 7 stations were received with good listening volume. The set is remarkably free from the distortion and noise heard in many of the smaller regenerative sets with "miniaturized" antenna systems.

Preamplifier Input Circuit

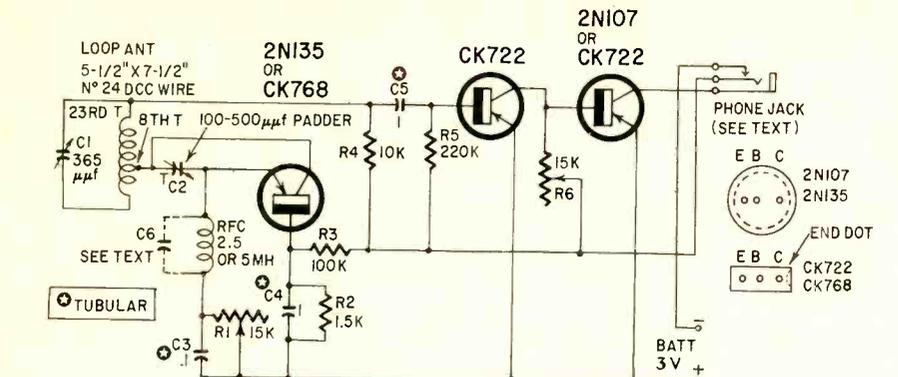

Schematic of the ultra-sensitive 3-transistor receiver.

- R1—15,000-ohm pot
- R2—1,500 ohms
- R3—100,000 ohms
- R4—10,000 ohms
- R5—220,000 ohms
- R6—15,000 ohms
- C1—365- μ f variable
- C2—100-500- μ f padder
- C3—0.1- μ f tubular
- C4, C5—1- μ f tubular
- C6—See text
- RFC—2.5 or 5 mh
- J—Phone jack, see text
- BATT—2 penlight cells
- Case, wire, mounting board, miscellaneous hardware

This set is built in reverse; that is, the loop goes in the deep part of the cabinet, the parts assembly (mounted on a perforated board) goes in the lid. One or two screws through the lid hold the parts board down. This permits removing the entire parts assembly from the cabinet for experiments or changes. It also keeps the antenna away from the components, thus avoiding detuning effects and loss of signal strength.

To eliminate problems caused by capacitor aging and reforming, no electrolytics are used. Tubulars take their place with no noted loss of performance. Long life and troublefree performance are thus assured. The 0.1- μ f capacitor C3 adds sensitivity. A 1- μ f at C4 and C5 substitute for the electrolytics. Recommended RFC is 2.5 mh, though we have used 5 mh with good results. As the rf choke is made bigger, sensitivity increases, but so does regeneration. [In the set constructed by the RADIO-ELECTRONICS staff, shown in the photo, a small capacitor (C6) was placed across the choke to control regeneration. C6 will vary widely with different sets, and in many cases must be omitted, but in this particular receiver the best value was 33 μ f.—Editors]

The set will work well with a 1.5-volt dry cell but 3 volts of battery is best. Six volts will give more volume and sensitivity, but with it come increased regeneration and need of more careful tuning. In strong signal areas, hearing-aid type earphones work well. But let's face it, the volume they give does not approach that of a full-size standard 2,000-ohm headphone.

The best volume is produced by 24,000-ohm headphones. The impedance match is better and sensitivity is optimum with this value. [In the receiver shown in the photograph an earphone was used, with some probable sacrifice in sensitivity. The phone jack was used to turn the radio on and off. This unit is sold as a "subminiature jack—may be used for both open and closed circuits," and is adjusted so that it closes the battery contact when the plug is inserted.—Editors]

In strong-signal areas, R6 can be replaced with a 15,000-25,000-ohm potentiometer for volume control.

A word about transistors. Both the 2N135 and the CK768 types work excellently. The higher the cutoff fre-

quency, the higher will be the set's sensitivity, the authors' tests showed. As old-timers know, transistors vary widely in performance, even among "identical" units. So try all the transistors you have on hand. Tune in a weak station—choose the best performer.

The set took about 4 hours to build. It can be made more compact, but the loop antenna should be at least 4 by 5 inches for good performance. Set values are not too critical, but keep leads short and direct. Do not overcrowd parts unduly. Use special transistor sockets (the authors don't believe in soldering their leads). Be sure to check and re-check wiring before trying out set. *That's a must!*

Aligning the set

Be sure the 8th turn goes to C2 and that the larger number of turns appears between C2 and the C1 stator. Then fully mesh C1's rotor until you get regeneration. Or, better still, tune in a local in the 550-kc region (if you have one), and adjust C1 and C2 until you can bring the station in clearly. Use as much C2 capacitance as you can. This is the low-frequency adjustment.

To adjust the high-frequency end, unmesh C1 rotor and tune in a local between 1500 and 1600 kc. If this station does not come in, adjust C2 slightly until it does. Now go back to the station in the 550-kc region. If it doesn't come in now, take one turn off the loop aerial at a time, at the stator end of the coil, until the station is received. When this is done, all stations between 550 and 1600 kc should come in easily. (Avoid ultra-small variable capacitors. Some of those tried wouldn't tune in the entire band.) That's about all there is to it. (All parts used in this set were obtained from Lafayette Radio, 165-08 Liberty Ave., Jamaica, N. Y.)

If you are a hobbyist weary of building miniature, museum-piece creations and you want a private listening receiver which will give you optimum performance with a minimum of effort and expense, this project will interest you. Here is a radio which will give you the "mostest" for the "leastest."

END

Modern hi-fi equipment must provide inputs for AM radios, FM radios, record players and tape recorders. These inputs are usually selected by a switch which is connected to the various sources by shielded cables that are anywhere between 2 and 5 feet long and have a capacitance of 50-150 μ f. But a 150- μ f cable capacitance introduces a loss of 3 db at 20 kc when the output resistance of the unit feeding the cable reaches 50,000 ohms. A higher output impedance would increase signal loss further and curtail the audio quality.

A way around this problem is to use a plate follower so cable capacitance can be countered by placing the input resistor at the source end of the cable as described in *Wireless World* (June, 1959). The circuit is shown below. The charts show how much capacitance is now needed at a particular input to produce a 3-db drop at 20 kc for different values of R2. Obviously, lower capacitances are nothing to worry about. Of course proper gain must be maintained for the input circuit, so choose resistor values wisely.

END

TABLE I
R2 = 2.2 MEGOHMS


R1 (K Ω)	Gain (db)	Capacitance (μ f) for -3db at 20 kc
47	31	750
100	26	690
220	19.5	650
470	13	630
1,000	6.5	610
2,200	0	600

TABLE II
R2 = 4.7 MEGOHMS


R1 (K Ω)	Gain (db)	Capacitance (μ f)
47	36	450
100	31.5	330
220	25.5	280
470	19.5	270
1,000	13.5	260
2,200	6.5	260
4,700	0	260
8,200	-5	260

TABLE III
R2 = 1 MEGOHM

R1 (K Ω)	Gain (db)	Capacitance (μ f)
47	25	1,300
100	19.5	1,150
220	12.5	1,100
470	6	1,100
1,000	0	1,100
2,200	-6	1,100

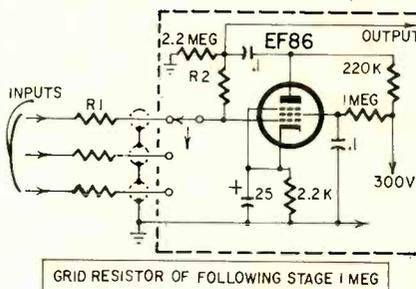

THE OLD TIMER GIVES A SAFETY LECTURE

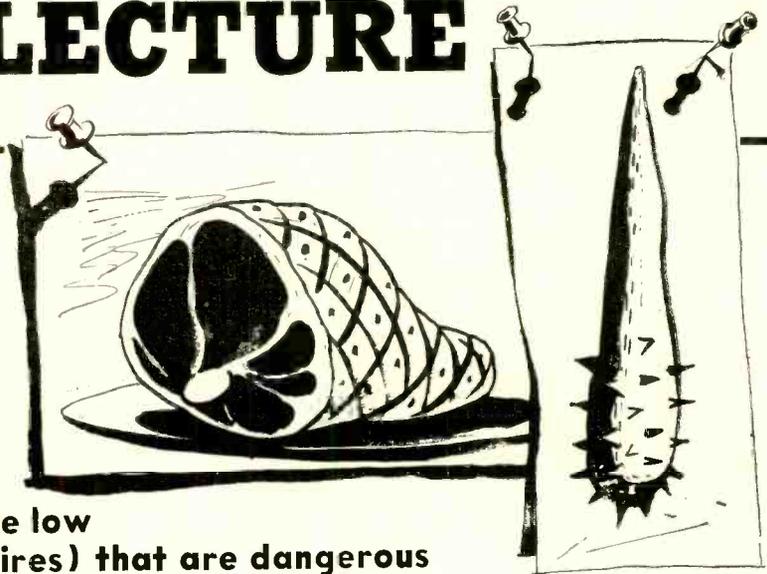

It's the little (?) things (like the low voltage in a TV and exposed wires) that are dangerous

By JACK DARR

THE Old-Timer came in the back door of the shop, whistling "Colonel Bogey" very softly. He smiled as he heard loud voices from the small back room he had donated for the Ham Club the Young Ham had organized. The smile turned into a full-sized grin as he saw the new sign the Young Ham had made a few days before. It was simply two colored pictures clipped from magazines: a luscious ham and a fearsome looking spiked club, pasted to a board.

The voices rose as he neared the door. "No, Eddie, look here now! You're not getting any rf out into the load because you haven't got enough coupling! See? This coil has got to go over a little more!"

"Well, it's lighting th' light, ain't it?" said the other voice.

"Yes, but not near enough," said the first speaker, the Young Ham. "A little ol' yellow glow like that ain't 50 watts, is it? You oughta get a bright white on that bulb!"

The Old-Timer glanced through the doorway at the two boys. They were bent over a piece of equipment at the far end of the bench. The smile froze on his face as he saw the tangle of wires trailing down the bench. Quietly, unheard in the continuing argument, he



He reached for the master switch . . .


reached for the master switch he had insisted they install after they had left the lights on all night a few times. He snapped it off, which brought a simultaneous roar from both boys. "Hey! What'd you do now?" They looked up and saw him leaning against the side of the door. The look on his face brought them both upright with apprehension written on their faces.

Fireman's friend

"All right," said the Old-Timer grimly, pointing to the mess of wires on the bench. "What'd I tell you about that?"

"That" consisted of: (a) approx-

imately 3 feet of slightly dilapidated line cord with a molded plug, connected to the ac outlet; (b) 6 feet of plastic-insulated bell wire connected to the other end of the line cord; followed by (c) 3 feet more of line cord terminating at the power transformer of the homemade power supply. All the connections were twisted (none too tightly) and all were completely innocent of tape or covering of any kind. From the output terminal board of the power supply, several similar leads went to the small transmitter the boys had been working on. These were also haywired (twisted to screws, twisted together, or simply twisted) and sans insulation or tape.

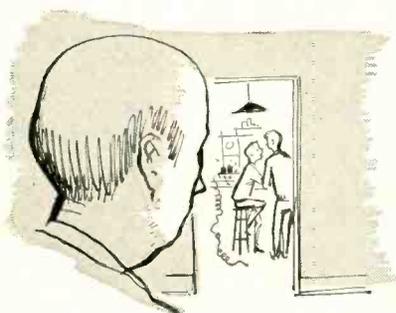

The Young Ham gulped and hung his head. The Old-Timer snorted and glared at him.

"Dang it all, now you know better'n that! I'll swear some people git up *bright* and early, looks like you just got up *early*! If I've told you once about them haywire hookups, I've told you a thousand times and this is the last one. From now on, use a little common sense around this stuff. I know I pay Dick a heck of a lot of money for fire insurance on this place, but I don't want none of it back. There's new line cord and stuff all over this place. Why didn't you use some of it?"

"Well, we were just trying it out," said the Young Ham sheepishly. "We didn't want to waste any new stuff on it until we knew whether it'd work."

"Look, Jughead," fumed the Old-Timer. "I don't care if it ain't for but 10 seconds. Don't *ever* let me catch you hookin' up a Fireman's Friend like that again! Why, a new plug and line cord wouldn't cost over 30 cents. My gosh, I'd rather *give* you th' stuff! Did I ever fuss at you guys about usin' stuff like that?"

"No," admitted the Young Ham, "but I've seen you usin' things like that in the shop. Hooking up record players an' things."

"Hah? Oh, you mean th' Fool-Killer? Come here just a dad-burned minute!" He chased them up the long hall ahead of him, into the service shop. He picked up a 5-foot piece of POSJ cord from a hook above the bench. One end was fitted with a bulky plug, the other terminated in two rubber-covered test clips. "Now, is this what you're talking about?"

"Yes," said the Young Ham, "and I've seen you use it a thousand times!"

"Well, Junior, there's a wee mite of difference," said the Old-Timer, shoving the plug under the boy's nose. "Look here. Do you notice anything unusual about that plug?"

"Yes," admitted the Young Ham, "it's a fusible plug."

"Well?" demanded the Old-Timer. "Doesn't that spell anything to you? There's a pair of nice little 2-amp fast-blow fuses in there, one on each side of the line. If I do get a short in anything, or let the clips touch accidentally, one of 'em pops out and everything's pretty safe—as far as the *fire hazard* is concerned. That ain't sayin' anything about th' shock hazard, though! You just gotta use a little *common sense* with it! Dang it, do you know how close Eddie's elbow was to one of them frazzly connections you had in there? About 2 inches! You were so busy arguin' about that transmitter you didn't even notice it. Those frazzlin' B-plus wires with about 500 volts on 'em weren't over a few inches away! Y'know, sometimes I wonder how you guys managed to get as old as you are."

"Aww, we were watching it," said the Young Ham.

"Junior!" said the Old-Timer, sternly. "You weren't watching *me*, and I stood there for a minute or so before I noticed what you were doing. Why, I

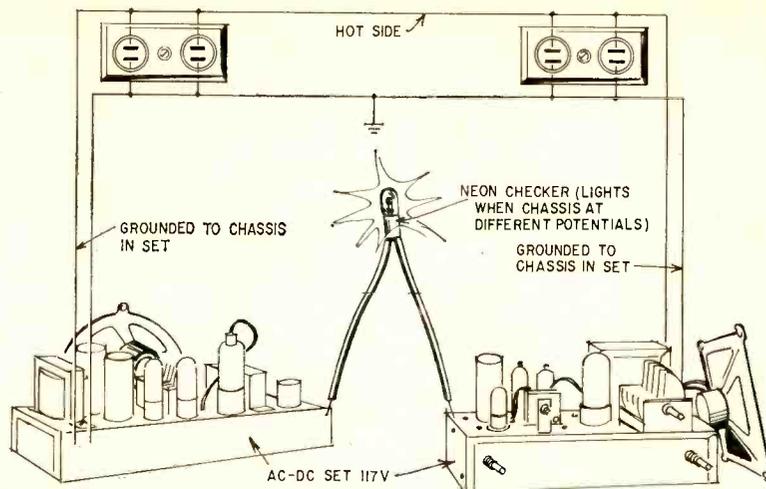


Fig. 1—A pair of ac-dc sets may have full line voltage between the chassis.

saw both of you darn near get electrocuted three or four times! I was so scared that I like to never found that switch. Now you listen to me, young sprouts. From this moment on, *every* time you hook up anything like that around here, you take the proper precautions, and that means making sure that all your connections are safe, well insulated and tight! *Then*, you can go ahead and argue till you're blue in th' face about your loading procedure and you'll be safe. But, if I *ever* find another haywire hookup like that one around here, out you go, the whole gang of you, while you're still alive. Get me?"

The boys looked at the fire flashing from the Old-Timer's eyes and decided that he really meant what he was saying, so they surrendered gracefully. "OK, we'll be good, from now on," said the Young Ham. Eddie nodded agreement.

"You'd better be," said the Old-Timer, with a return of his normal good humor. "I'll be danged if I want to take the trouble to break in any more young squirts around here, to say nothin' of all th' money I'd have to spend for flowers. No, young fellers, I know that you guys feel like you know quite a bit about electricity and things, but that's the *one* thing you never ought to do in th' electronics business: get cocksure! Y' know, you can always tell th' difference between an old-timer and a new hand just fresh out of radio school: ask 'em both the same question. Th' young dude right out of school will pop right back at you with a positive answer; the more experienced man will always say: 'Well, I don't know right now. Let's check it and see!' Time you get to the point where you realize you don't actually know nothin' about this bewildering business, then you're gettin' to be a pretty good radio man!"

"I sure am thirsty," piped up the Young Ham, nudging Eddie, who dutifully echoed, "Me, too."

"All right, you human sponges, come on," growled the Old-Timer in mock anger. "Let's go gitta cuppa cawfee. But if you think you're gonna take my mind off the lecture you're gonna get, you're mistaken! You've both earned a good chewin' and you're gonna get it!" He led the way out the back door, down

the alley and into the drugstore.

Ac-dc sets

"Speakin' of hot stuff, which you'd probably rather I wouldn't but I'm goin' to anyhow," said the Old-Timer, stirring briskly, "now you're gonna get the rest of that lecture you got comin'. Didn't I see you workin' on two ac-dc's at the same time on the radio end of th' bench?"

"Yes," replied the Young Ham. "One of 'em needed a filter capacitor and I was cooking the other one after I changed the rectifier, to see if there was any more trouble in it." He had a strange gleam in his eye, but the Old-Timer pursued the questioning, not noticing.

"Well and good," said the Old-Timer. "But I didn't tell you to work on *two* ac-dc's at the same time on the same end of the bench. Tell me, how's the ac line connected to an ac-dc set?"

"One side to the chassis?" asked the Young Ham innocently.

"Yep. Now, if you got two chassis with this kind of line connections, both of 'em out of th' box with the chassis exposed, what's the ac potential between them?"

"Zero," said the Young Ham quietly, sipping his coffee. The gleam brightened.

"Zero?" The Old-Timer's left eyebrow shot up, a trick he had practiced for many a year.

"Zero!" repeated the Young Ham firmly. "Nyaaa! You were going to catch me, weren't you? I actually remembered what you told me about that. So, I checked between the two chassis with the little neon checker (Fig. 1) and turned the plug around on one of 'em! Zero voltage! Also made sure both chassis were on the ground side of the line."

"Well, I'll be cow-kicked!" said the Old-Timer, shaking his head in amazement. "You got me, f'ar and squ'ar! I'll swear, I thought that had gone in one ear and right out the other in that non-resonant cavity you use for a head! My, my! I just can't git over it." He shook his head solemnly. "Congratulations, young feller. Just for that, I'll buy th' coffee!"

"You might not have known it, but you were going to anyhow." The Young Ham grinned. "I'm broke."

"This is unusual?" said the Old-Timer. "Well, sir, I'm glad you thought of that, though. It's sure a good habit when you're workin' around stuff like that. You know how I found out about it, don't you?"

"Yes, sir!" said the Young Ham. "And you got reminded of it just last week, when I had that portable sitting on my end of the bench, and you backed into it while you were moving that ac-dc TV set! Goodness, such language!"

"Well, I was mostly mad at myself," admitted the Old-Timer. "Us old fools ought to remember them things automatically, and we do, most of th' time, but we still git caught now and then. That's just th' reason I yowl at you guys so much about bein' careful with electricity. Workin' with it all th' time, you're gonna get a plenty of shocks accidentally, even with good habits. There's only one way to stay alive in this business, and that's to be careful, dern careful! And that's somethin' else you've got to do for yourself. There sure ain't nobody goin' to do it for you!"

"'Nother thing, while you're workin'

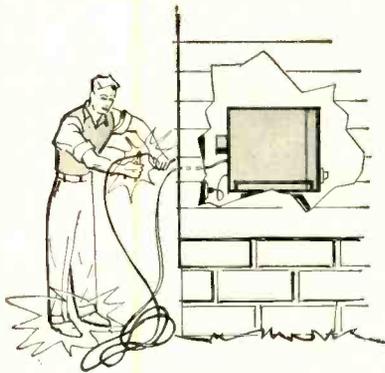


Fig. 2—Never touch an "outside antenna" lead of a radio or TV when standing on the ground unless the set's plug is out of the socket.

with a transmitter like you were a while ago. Don't ever let anybody else handle the key. You do it yourself! If you're the one makin' the adjustments, you do th' keyin'; it's a heck of a lot safer! I 'member once durin' th' War, while I was with the Air Force. Three or four of us was arguin' about a transmitter, just exactly like you were just now. All of a sudden one feller keyed the thing to illustrate a point he was tryin' to make. Only trouble, I happened to be leanin' on the final plate caps with my elbow!"

"What happened?" asked the Young Ham. "Did it hurt you much?"

"Well, not too much, but I'll tell you one thing. I was the only man that left the ground that day on that field without takeoff clearance from th' tower! I got darn near as much altitude as some of the kay-dets! Th' moral of that is: if someone is workin' on a piece of equipment, stay clear of it. If you're workin' on it, make *everybody else* stay clear and always look to see that everything's safe before you mash that button. Saves a lot of trouble!"

The Old-Timer paid for the coffee, as usual, and they trooped out the back door and across the alley to the shop.

Lighting his pipe, he perched on the end of the bench and continued the discussion.

"Y'know, there's lots of what you might call 'everyday' hazards that we run into that we don't really pay enough attention to. F'rinstance, even you know enough not to go outdoors, stand on the ground, and try to hang up an antenna wire that's already tied to an ac-dc radio in th' house (Fig. 2). You'd be surprised how many folks don't, though! Way I look at it, that oughta be part of our job; to kinda warn the customers about such hazards."

"Yeah," agreed the Young Ham, "I've heard you tell lots of 'em about that kind of stuff. I hope they paid attention to it."

"So do I, Junior," said the Old-Timer soberly. "If all th' techs would take a little time to warn their customers about some of the hazards, maybe we wouldn't be hearin' about so many people gettin' electrocuted by touchin' a TV set and stuff at the same time. While we're on th' subject, that's one thing I want you to promise me you'll always remember to do: never let a set git out of here in such a shape that it could hurt anybody. I'm pretty proud of you so far. You've been dern good about it. Keep it up."

"You mean like always putting the backs back on little ac-dc radios and checking the line cords for bare wires, and so on?" asked the Young Ham.

"That's it," said the Old-Timer. "And if the radios *should* have a metal cabinet, be dern sure that the chassis is isolated from that cabinet, like it ought to be. Remember the little set we found with the chassis shorted to the cabinet 'cause some kid had poked a metal bobby pin into it? And, most especially, watch out for these metal-cased portable TVs with the hot chassis. Pretty near all of 'em are provided with some kind of insulation between chassis and cabinet, but be awful careful to check those insulators. I've found several of 'em chewed out and shorted: found one set shorted to the case cause some sloppy-joe had dribbled a big hunk of solder down the chassis!"

"Yeah, I've found them myself," agreed the Young Ham.

"Tell you one more," said the Old-Timer, relighting his pipe. "You know the little isolating networks in the antenna connection? Couple of little capacitors in series? I found one only day 'fore yesterday, where some jerk had shorted those out! Don't know who did it, but they were shorted out beautifully. Tied a piece of wire across 'em! I do know what the result was: he managed to burn out the balun coil on th' tuner doin' it! It was one of those stinkers, too. I had the heck of a time gettin' it back in that tight place. Wish they'd put 'em on the outside!"

"That would make life too easy!" opined the Young Ham.

"I could stand a little of that," said the Old-Timer. "T'ain't too easy as it is. No kiddin', though, that's something *you* want to watch out for. You can git th' infernal waddin' knocked out of you

if you happen to get hold of the lead-in with one hand and touch the chassis with the other! Don't ask me how I found *that* one out, either. I remember once I was squattin' down behind a TV set and got between antenna and chassis: I bounced off, hit th' wall and bounced right back onto th' TV set again, which promptly bounced me right back to th' wall, and so on! I'll tell you, when I finally stopped bouncin', I felt like the oldest punching bag in Johannsen's gym!"

"I'd like to have seen that!" The Young Ham laughed. "I'll bet you were mad!"

"Yep," said the Old-Timer ruefully. "Like before, I was mad at myself for bein' so careless, and that's the worst kind! Seriously, though, you wanna watch out for that kind of stuff. I was readin' an article in a science magazine a while ago, and the doctor who wrote it told how much current it took to be fatal. Guess how much it was."

"Golly, I don't know. Quite a bit?"

"Nope," said the Old-Timer, soberly. "Eleven milliamperes! That ain't much, is it? A 50L6 draws a heck of a lot more'n that: so, always remember that figure! If you get caught by an electric current so that that amount of current flows through your heart, you're off the air for good. So, that's one of the reasons for this old sayin' about 'one hand in your pocket.' Although a shock any place is bad, I believe it's worse if you get it from 'hand to hand,' you might say, so that the current path is through your chest. You can git pretty bad shocked say from fingertip to elbow, and although it'll hurt like fury, it wouldn't be as bad as if it was from arm to arm."

"That's the reason I always wear thick rubber-soled shoes, and keep 'em dry whenever I'm foolin' around anything. Long as you ain't grounded, you ain't in near as much danger."


"I might give you another word on th' matter, too. You notice everybody seems to be pretty scared of the high voltage in a TV set, even lots of guys who should know better. Well, that stuff isn't near as dangerous as th' 300 volts or so in what we laughingly refer to as the 'low-voltage supply.' Actually, th' low-voltage'll kill you a lot quicker'n th' high voltage. Best way, of course, is to keep off of both of 'em!"

"Right," assented the Young Ham.

"Well, sir, I'll give you one last word, while I'm at it: you seen a darn good example of it this morning, right here. Regardless of how much you know about electricity, and how skillful you are, a well insulated and properly installed circuit won't bite you. So, the best thing for any of us to do is use the most useful remedy—good old common sense!"

END



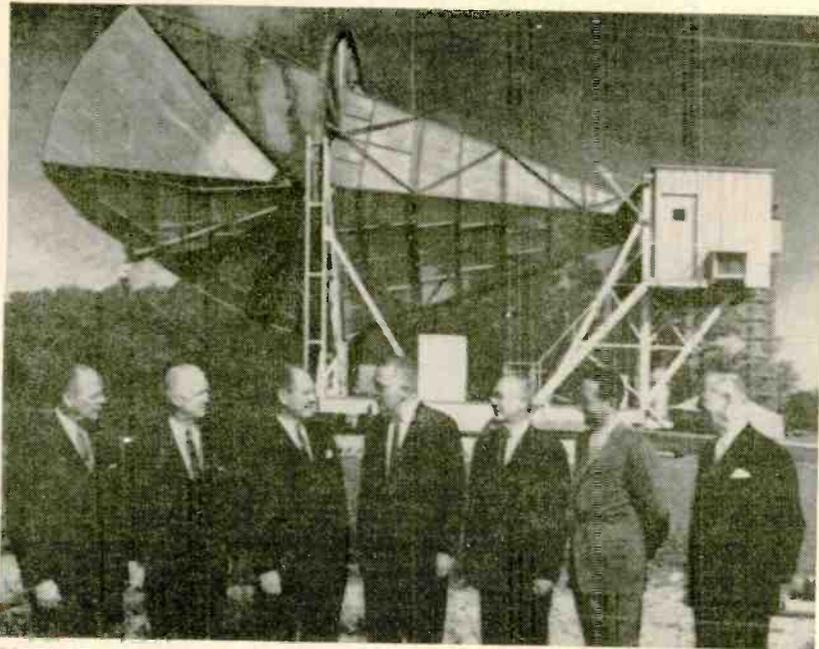

PICTURE BOUNCED OFF ECHO I satellite shows FCC members and NASA administrator. The photo, taken at Bell Telephone Labs in Holmdel, N. J., was transmitted by land line to the Naval Research Laboratory at Stump Neck, Md., and then bounced off the Echo I satellite back to Holmdel. The horn antenna in the background was used to receive the picture. People in the photo are (from left to right): FCC Commissioners John S. Cross and Rosel H. Hyde; Dr. T. Keith Glennan of NASA; Frederick W. Ford, FCC chairman; and Commissioners Robert T. Bartley, Robert E. Lee and T. A. M. Craven.


WHAT'S NEW

STEREO RECORD DEMONSTRATOR consists of a stereo amplifier, stereo headphones and a manual turntable and arm with a stereo cartridge. Made by Sargent-Raymont, Oakland, Calif., the unit is used to demonstrate stereo records in crowded noisy surroundings.




PORTABLE SCRAMBLER PHONE insures telephone privacy. Device fits over standard phone, uses 10 transistors to transform ordinary speech into incoherent gibberish. The gibberish is transmitted over the regular phone circuit and only a second scrambler unit will translate it back into normal speech. Developed by the Delcon Corp., Palo Alto, Calif., the units are coded at the factory with one of several basic codes and must be used in pairs—one at each end of the phone line.

ARTIFICIAL LARYNX includes a control that allows the user to vary the pitch of his voice, producing more natural inflection and emphasis. Earlier models gave a stiff mechanical quality to the voice. Transistorized unit developed by Bell Laboratories will be sold by American Telephone and Telegraph at manufacturer's cost on a first-come first-served basis. The larynx was described, with a schematic, in **RADIO-ELECTRONICS**, August, 1959, on page 10.

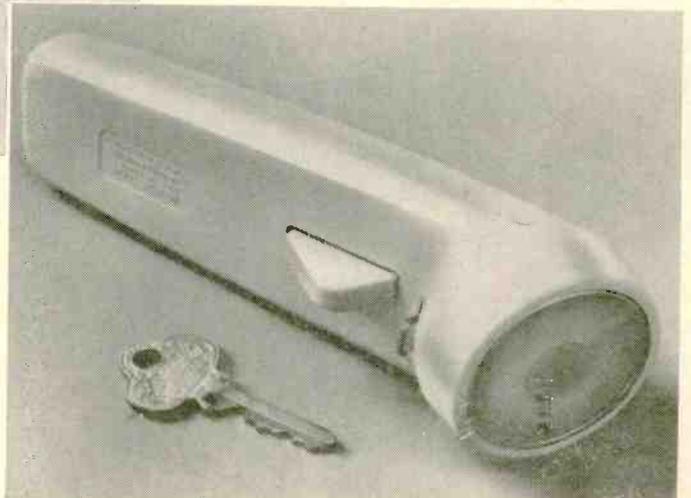

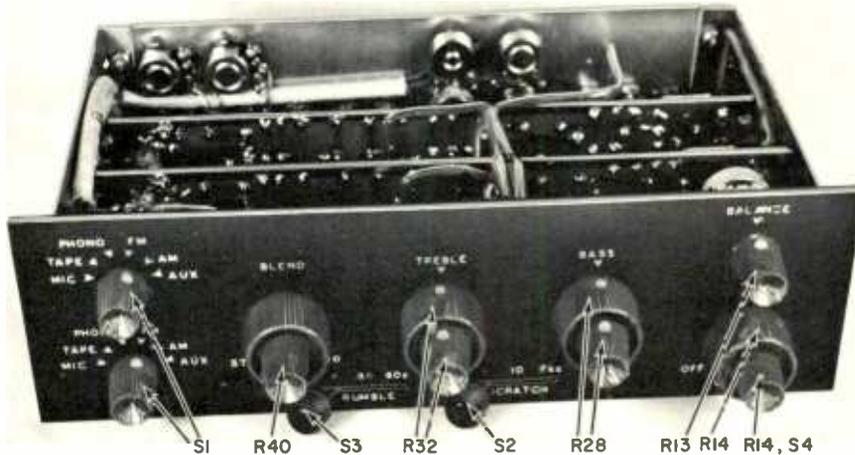ALL-TRANSISTOR STEREO PREAMP YOU CAN BUILD



Front-panel layout of the preamp.



Underchassis view of preamp. Angle brackets fasten the circuit boards to ends of chassis frame.

Two printed-circuit boards make this unit a comparatively easy construction project and low-cost transistors keep the price down

By DANIEL MEYER*

THIS all-transistor stereo preamp was designed to replace a monophonic preamp that has been in service for some 5 years. I decided to use a transistor preamp for stereo because of the advantages a transistor circuit could provide. Transistors are quieter than tubes in low-level stages if used properly. They are smaller and need less power, which means less heat, and heat can be a problem in a stereo installation. Their size makes possible a small, compact preamp. These factors, and the challenge of building something new and different, led to the construction of this preamp when I converted to stereo.

The controls and features included meet my needs. If you have different tastes in controls, simply change the circuit slightly to get what you want.

The input selectors (Fig. 1) are somewhat unusual—there is a separate switch for each channel. This in combination with the BLEND control makes a very flexible input switching arrangement. With the more usual arrangement—a selector and a mode switch—a separate position is needed on the selector switch for each possible combination of inputs. If you start adding up the possible combinations such as AM-FM, FM-FM, TV-AM, TV-FM, etc., and then consider that we could also have a reverse condition for each, the reason for the system becomes obvious. With this arrangement the only thing not possible is reversing the two channels when both are on the same input. While this is not usually necessary it could be easily done with a dpdt switch (Fig. 2).

In the PHONO position, each preamp is compensated to match the RIAA recording curve. No provision was made on the original unit to change this since the RIAA has been standard for

Once again RADIO-ELECTRONICS is pleased to announce that the printed-circuit boards used in this article can be purchased. The price is \$1.50 each, postpaid (get only one if you want a monaural all-transistor preamp). They are available from RADIO-ELECTRONICS, 154 W. 14 St., New York 11, N. Y., or direct from Electro-Technik Co., 19456 Meyers Road, Detroit 35, Mich.

*Research engineer, Southwest Research Institute, San Antonio, Tex.

electronically speaking—

START OFF THE NEW YEAR RIGHT

with articles like these

next month

SPECIAL REPORT: 1961 TV RECEIVER CIRCUITRY

A complete digest from Admiral to Zenith of all the new and interesting features in the new TV receivers. Veteran service technician Wayne Lemons, who wrote the memorable 1960 preview, does an even better job now. Required reading for all service technicians—recommended for everyone else.

ZENER DIODES SIMPLIFIED

This new electronic device has seldom been used to the limits of its capabilities—and mostly because many people do not realize just how versatile it is. This article gives you all the dope. You'll be amazed at the many unrealized applications the zener has.

10-METER WALKIE-TALKIE

Designed for the new amateur who has graduated from the Citizens Band! This portable transmitter-receiver has all the simplicity and easy-handling features of CB equipment but adds refinements like separate transmitter and receiver circuitry to upgrade effectiveness.

RADIO-ELECTRONICS PRINTED-CIRCUIT STEREO PREAMPLIFIER

Another **Radio-Electronics'** construction project you can build on ready-made circuit boards. This fully transistorized stereo preamp will bring out the best in the finest hi-fi amplifier and associated equipment. And that printed-circuit feature makes it so easy to build.

Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

Special Report: 1961 TV Receiver Circuitry

Easily Constructed 10-meter
Walkie-Talkie

Zener Diodes
Simplified



Radio-Electronics

JANUARY ISSUE

on sale DECEMBER 15th

50c at newsstands and parts distributors.

RESERVE YOUR COPY NOW!

YOU SAVE UP TO \$6.00 over the newsstand price on subscriptions.


3 years \$12

2 years \$9

1 year \$5

Radio-Electronics

154 West 14th St., New York 11, N. Y.

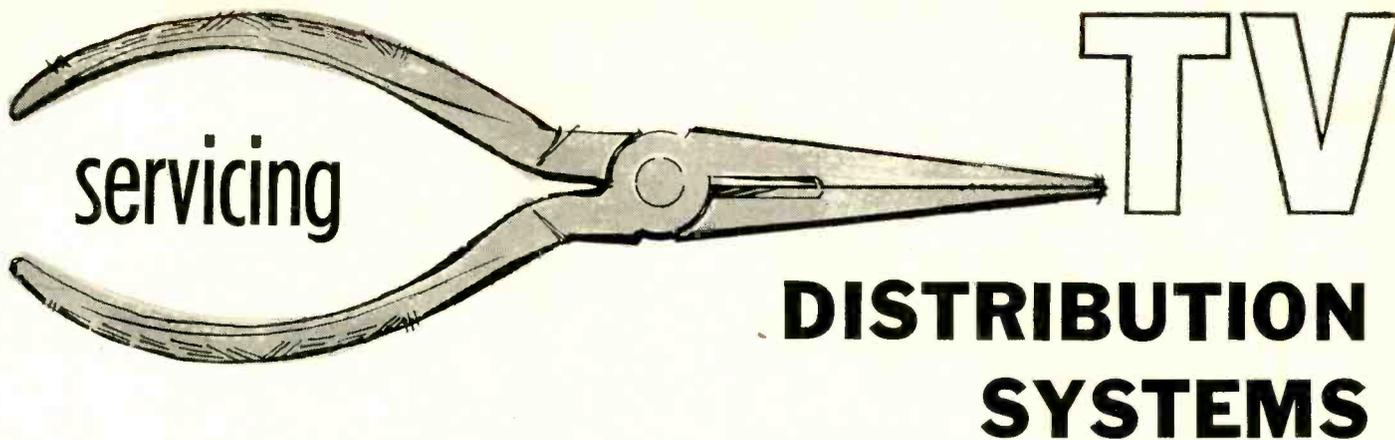

DISTRIBUTION SYSTEMS

Part II—System defects: How to troubleshoot and find their causes

By JACK BEEVER *

THE first part of this series discussed types of distribution systems and some of the requirements of each. Now let's get down to the defects that may show up in these systems and see what causes them.

When faced with a defective system, the first thing to do is *think!* Don't just start testing here and there. Get an idea of the general layout. If possible, get a plan of cable layout and the equipment specifications. You will need one additional service instrument, a direct-reading field-strength meter, preferably one that will read the video and audio TV carriers separately.

Remember first that the average TV set owner who is connected to a TV distribution system always calls the system servicing people before he calls his TV technician—he hopes that the trouble lies in the system since service would then cost him nothing. The system technician should check, perhaps by telephone, with other people in the building to see if their sets are also out. Check apartments on each side and above and below, unless you know the wiring pattern of the building. If other sets are out or functioning improperly, then the trouble must be tracked down in the system. Listed below are a series of symptoms, their causes and cures.

No pictures on any channel all over the building. Usually an amplifier or the power supply of a strip head end is out. Check for a bad tube, blown fuses etc. Don't forget to check the ac power lines. If these are OK, the output line may accidentally have been cut somewhere between the amplifier output and the first splitter in the system (if it were elsewhere, there would be pictures in part of the system). Structural failure of the antenna system may be the cause.

No pictures on one channel, others OK all over. In a strip type head end,

one amplifier or the associated antenna or preamplifier is out.

Snowy picture on one or more, but not all, channels at the ends (farthest points from the head end) of the system. In a strip head end, this usually means defective tubes in the amplifier of the channels involved. It may be a broken antenna connection or an antenna slewed on its mast (or corroded). The snow is an indication of too little signal to the TV receiver and signals are usually lowest at the system extremities.

In broad-band systems, this is usually caused by antenna difficulties, most often misorientation.

Snowy pictures on all sets, but head-end sets are getting high signal voltages. This is an indication that the amplifier is still operating, but is getting too low signals from the antennas. This results in a bad (low) signal-to-noise ratio at the amplifier input. When such a situation exists, no matter how much the signals are amplified (beyond this point) the pictures will still be snowy.

If the system has worked well in the past, the trouble is quite likely low antenna signals. In general, amplifiers should have signals of over 1,000 μv at their inputs. Preamplifiers should have a minimum of 150 to 200 μv for good crisp pictures.

All sets on the system show one or two horizontal black bars, with shaded edges, moving or stationary. This is hum modulation and can be caused by a heater-cathode short in a tube or by defective filter capacitors in an ampli-


fier. It will not be caused by anything past the amplifiers—ac on the system wiring will not cause it. If found on a strip type system, it will usually appear on only one channel if caused by a heater-cathode short. In the broad-band system, it may appear on all channels or just the channels of one band, depending on the circuitry of the particular amplifier. Usually, a dried-out or open filter capacitor puts the symptom on all channels.

A heavy, black vertical bar is seen moving across the screen, sweeping back and forth irregularly. This is "windshield-wiper" effect, properly called cross-modulation. In a strip type system, it means that a powerful signal is overdriving the amplifier or preamplifier of a weaker channel. The highest-power portions of this unwanted signal are the blanking pulses and are seen on the desired signal as an overlaid, unsynchronized pattern. The remedy is to trap out the undesired signal *before* it enters the amplifier—it cannot be taken out afterward.

In a broad-band system, the undesired signal is easy to identify. It will be the channel which *does not* have the symptom. This signal must be reduced. Bear in mind that broad-band amplifiers are actually double amplifiers. If channels 2, 4 and 8 are being used and 4 has the windshield-wiper pattern, channel 2 will be the offender. Channel 8 is in the high-band amplifier and could not normally overdrive the channel 4 in the low-band section.


In extremely severe cases, it is possible for a low-band section to be overdriven by a high-channel signal or vice versa, but it generally requires signals in excess of 100,000 μv .

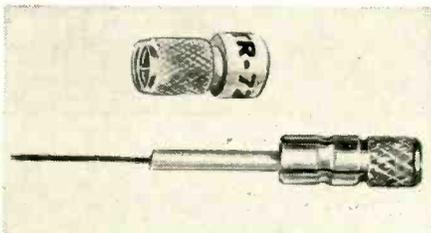A percentage, or all, of the sets on a system show vertical instability and are very touchy about vertical hold control setting. This is also a symptom of overdriving and is called sync clipping. When an amplifier is overloaded, it tends to clip off the high points of the signal. This reduces the sync pulse size. Many sets will then synchronize to the



Terminating resistors for 72-ohm lines. Jerrold

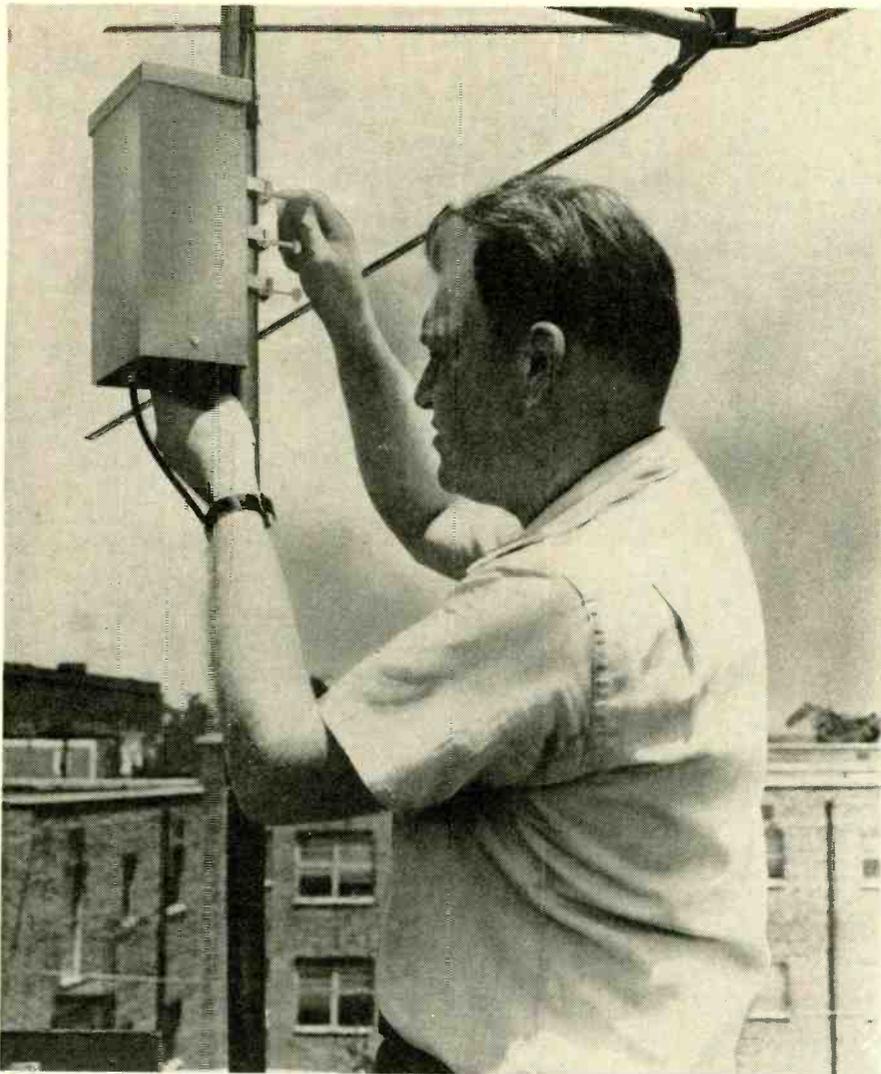*Applications engineer, Jerrold Electronics Corp.



Technician replacing mast-mounted preamplifier

Jerrold

shorted between that last strong picture and the first weak one. Remember that a break and a short are the same to a coaxial cable and that neither stops signals entirely. A considerable amount of energy will get past the interruption. The easiest technique is to open the suspected outlet and check with an ohmmeter for continuity through the terminating resistor. Readings of 80 to 120 ohms are normal; less than 75 indicates a short.

Pictures along a line are smeary. Some sets have weak signals on one channel, but other sets on either side of the outlet may have higher signals. Close examination of pictures near the head end will usually show a close trailing ghost. The symptom indicates a poor or bad termination. An open or shorted terminating resistor or a short or open near the end of the feeder cable can cause this. The ghost is due to reflection from the unterminated line end, which also produces standing waves on the line, resulting in alternately weak and strong signals.

Leading ghosts (to the left of the main image) are seen on the local channel(s). This is caused by direct pickup of the local signal. The set is getting one signal from the system (delayed by the amplifier and cable) and is picking up a second undelayed signal directly from the station. Therefore, we have two images on the screen.

The remedy is to change the ratio between the direct-pickup signal and the system signal in favor of the system signal. Since we cannot change the strength of the direct-pickup signal in the vicinity of the set, two courses are open to us. The first is to increase the level of the system signal. Increase the output of the head end as much as possible. If this is not sufficient, it may be helpful to install higher-powered amplifiers.

The second way is to reduce the amount of set pickup. Coaxial cable from the tap to the set (which may require changing the tap to one with a coaxial output) will reduce pickup considerably. Shielded ribbon type line may be installed between the set's antenna terminals and the tuner to re-

leading edge of the blanking pulse and lose interlace. They may show vertical jitter as they alternate between the weakened sync pulse and the leading edge of the blanking pulse. In a strip type head end, this will usually occur on one channel. The remedy is to reduce the signal level to the overdriven amplifier.


In the broad-band types, it may be necessary to "pad down" (attenuate) all signals or reorient the antenna to get satisfactory results.

Sync buzz in sound on all sets, and the audio carrier reads much lower than the video carrier. A defective antenna can sometimes cause this, but it usually is amplifier misalignment. Before doing anything else, check the signals from the antenna. If audio signals here are about even with the video signals or a little less (as is normal), the trouble lies in the amplifiers. Read the output levels of the preamplifier or amplifier to pin down where the trouble starts.


When found, change tubes from a known good set and reread the signals. If the trouble does not disappear, the amplifier is out of alignment. *Don't* grab an alignment tool. These amplifiers are much more difficult to align than a TV set, and the proper equip-

ment is needed. Unless you have the proper sweep oscillators, delay lines, attenuators and detectors, don't touch; return it to the manufacturer.

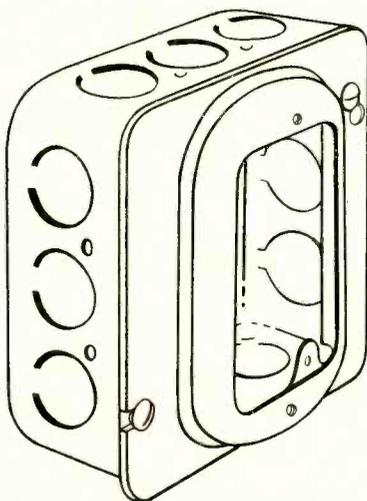Along a feeder line, sets have strong but slightly smeared pictures, up to a point on the line. Beyond this point, pictures are weaker and ghosty. This is an indication that the line is broken or



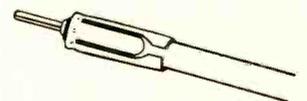Standard coaxial outlet used in many systems.



duce pickup on this section of exposed line.

If these remedies fail, a final but more expensive recourse is left. Convert the local channel to an unused, nonadjacent channel before inserting it into the system. Crystal-controlled converters are available for this purpose. As an example, suppose the channels in use are 3, 5 and 10, and there is too much direct pickup on channel 3. Channel 3 may be converted to channel 7, 8, 12 or 13. Channels 2, 4, 6, 9 and 11 cannot be used because they are adjacent to 3, 5 and 8. This could result in adjacent-channel interference (herringbone patterns).

Pictures flash or streak when trucks go by or elevators are operated. This trouble is usually just what it appears to be—a loose connection somewhere. Before pulling wires, however, check all tubes and antenna connections. Pound or shake the antenna mast while an assistant watches a TV set. Don't trust a signal-strength meter for this since the needle cannot move fast enough to indicate a loose connection. If these measures fail, jiggle all cable connections and check them for corrosion or oxidation. *Carefully check ground leads to the amplifier chassis—these can raise the devil due to ground currents.*

Keep in mind that the trouble is not necessarily in the system—the vibration of elevators or trucks going by may cause an arc in a loose power connection somewhere near the antenna. If this is the trouble, you have to locate it and inform the building superintendent. Usually, this effect will be more pronounced on distant channels and less noticeable or absent on the local station.

General notes

When an obscure trouble exists, a good procedure is to "strip down" the system. This is a process in which a television receiver is used to check all stages of the system. Start with the antenna leads (everything else disconnected), insert the preamplifiers, then the amplifiers, etc. The cable system is broken down into sections by removing all but one branch of the wiring from the splitters and terminating (connecting terminating resistors) to all unused "spigots" (coaxial connectors). Each leg can then be checked separately.

Finally, season all work with large doses of common sense. Good luck! END

Problems for Imports

Sales of imported TV and stereo sets are prevented in some parts of the US by lack of UL approval. Certain states and cities ban the sale of nonapproved devices.

A set is normally inspected at the factory (using the manufacturer's test equipment) when there is an Underwriters Laboratories branch nearby. Where Japanese imports are concerned (a UL branch has not yet been set up), the importer may have the sets inspected in this country as long as he makes any necessary design changes.

STEREO PA AT NEWPORT

By JACK ALLISON

ALTHOUGH the 1960 Newport Jazz Festival was wound up at the halfway point through no fault of its own, the first half of the show was covered as completely as possible by electronic means.

While the musicians performed on stage, behind the scene 30 engineers and technicians were busy at their jobs, making the coverage a 100% affair.

As the sound went into the six mikes on stage, it was being picked up on three-track and two-track Ampex equipment by Vanguard Records. Some of the material will be released by Vanguard; other tapes will be sold to the company that has a particular performer under contract, such as RCA Epic and Columbia. From Vanguard, a composite monaural signal was fed to the Voice of America facilities nearby.

A similar signal was simultaneously picked up on the audio track of the Videotape recorder Sports Network Inc. had brought along. SNI had three cameras covering the action. Their work is under contract to the US Information Agency and the tapes they have made are in demand by all the foreign TV networks. It seems that jazz is one of America's most easily assimilated exports.

A third mono signal was taken from the Vanguard truck by the CBS Radio Network. They had Mitch Miller narrate the programs on the spot and were able to broadcast a complete hour-long program, commercials and all, from


Newport over special lines the telephone company had installed.

Of particular interest was the PA system. Few critics failed to mention the excellent sound at the festival.

The three channels picked up by Vanguard were fed into two three-channel high-fidelity mixers so that, as you faced the preamp-mixers, the controls on each unit rode gain on left, center and right channels. Each preamp fed a 200-watt McIntosh commercial high-fidelity amplifier capable of over 500 watts peak. In turn, each amplifier was connected so that one half or side of the audience was covered by it.

If the left channel were fed directly to the left speakers, and the right the right, this would mean that those sitting near a speaker would get only half a channel of music, hardly a fair situation. To correct this, both halves of the signal were fed to all speakers, but on the left side the right signal was cut down 3 db and on the right side just the opposite was done. The center or solo signal was fed, slightly reduced, equally to both sides. Listeners at the sides near the front heard a complete signal. However, the vast majority near the center and back of the audience obtained the stereo illusion which made the music seem to come right from the stage, and the speakers themselves drew no attention.

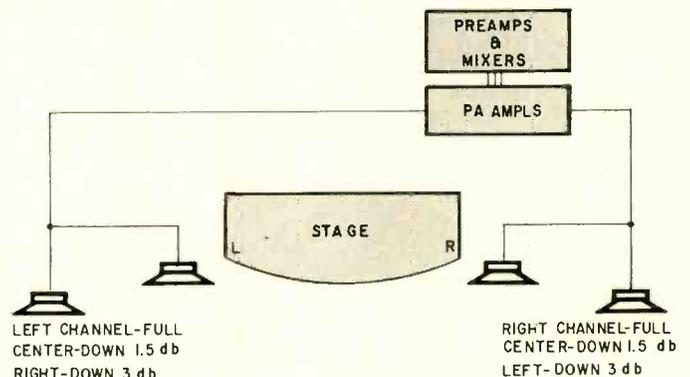The Newport Jazz Festival was a spectacular show, musically and electronically. END




AUDIENCE

How the speakers were fed to give the stereo illusion.

IGNITION-OPERATED TACHOMETERS

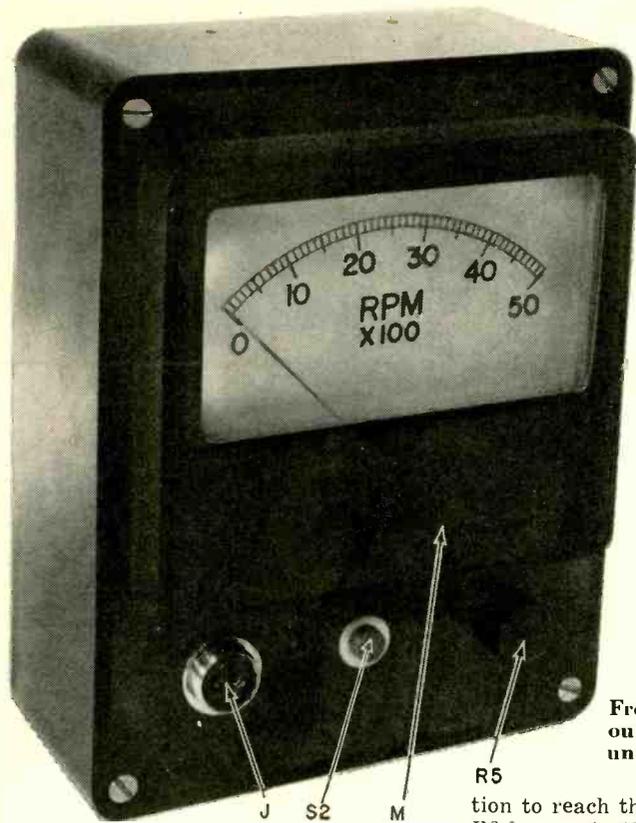Three types of tachometers that will measure engine rpm of almost every type of gasoline engine—lawn mower to automobile



Front panel layout of all three units is identical

By ALEX M. SCHOTZ*

THESE are many types of electronic tachometers, each designed for a specific purpose. Two of the three units described in this article can be used on either 2- or 4-cycle engines with battery or magneto ignition (on engines with up to eight cylinders). The third one is a battery ignition-operated tachometer only.

The spark plugs fire on every stroke in a 2-cycle engine, and on every other stroke in a 4-cycle engine. Therefore, each revolution, one pulse is produced at the primary of the ignition coil for each cylinder in a 2-cycle engine, and one pulse for every other revolution per cylinder in a 4-cycle engine. The pulse width varies with the dwell time of the ignition points and the engine speed.

The first instrument is a combination electronic-electromechanical tachometer (Fig. 1). Its input is connected between the hot side of the ignition breaker points and ground. When used with a battery-ignition engine, the input leads must match ignition polarity. The pulse received from the primary of the ignition-coil circuit is fed through a low-pass filter composed of R1, R2, C1 and C2 that is designed to eliminate counting extraneous and breaker-point-bounce pulses. The desired pulses, from the low-pass filter, are coupled through dc blocking capacitor C3 to the base of transistor V. Also connected to the base of V is D1's anode. The diode clamps the pulses, allowing only the negative por-

tion to reach the base of the transistor. R3 is a protective resistor for the diode. Transistor V operates as a switch and is turned on by the negative pulse, is off between pulses and allows current to flow through the relay coil with the pulses. D2 is placed across the relay coil to prevent negative peaks which might otherwise damage the transistor. The contact arm of the millisecond relay swings between the Zener-regulated voltage supply and the meter. When it is connected to the supply, capacitor C5 is charged. Resistor R7 limits charging current and later discharges the capacitor through the meter circuit. The average or dc value of these discharges is determined by the frequency of the discharges multiplied by the capacitance and voltage ($I = F \times C \times E$). If the capacitance is in microfarads, current will be in microamps.

To calibrate the instrument, apply the secondary voltage of a 6.3-volt filament transformer to the input. Then adjust potentiometer R5 so the meter indicates the proper rpm for the amount of pulses received at 60 pulses per second (see calibration chart, below.)

CALIBRATION CHART (ADJUST R5)	
PULSES PER REV	METER READS
1	3,600
2	1,800
3	1,200
4	900

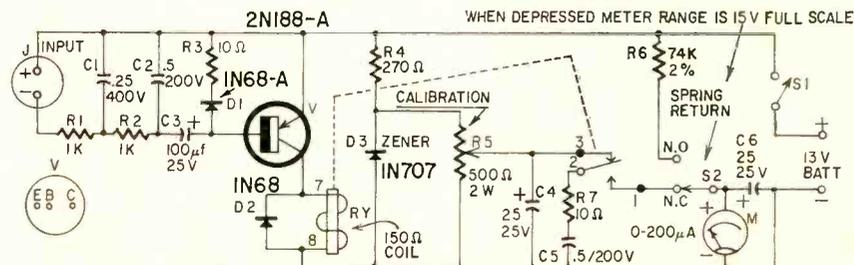


Fig. 1—Electromechanical tachometer for magneto- or battery-ignition engines.

In many magneto-operated ignitions there are separate coils for individual cylinders or pairs of cylinders. When the tachometer is operated, this must be considered when figuring the pulses received.

The condition of the instrument's battery is shown when S2 is depressed, the meter reading voltage. Current drain is less than 50 ma, and the instrument is accurate within 2%. The frequency limit is set by the type of millisecond relay, dwell time of the ignition points and engine rpm.


Electronic tachometer

The second instrument is an all-elec-


- R1, 2—1,000 ohms
- R3, 7—10 ohms
- R4—270 ohms
- R5—pot, 500 ohms, 2 watts, linear taper
- R6—74,000 ohms, 2% (73,200 and 806 ohms, 1%, in series)
- All resistors 1/2-watt 10% unless noted
- C1—0.25 μ f, 400 volts, paper
- C2, 5—0.5 μ f, 200 volts, paper
- C3—100 μ f, 25 volts, electrolytic
- C4, 6—25 μ f, 25 volts, electrolytic
- BATT—13 volts (2—6.5-volt mercury batteries in series) (Mallory TR-135R or equivalent)
- D1—1N68-A
- D2—1N68
- D3—1N707, Zener diode, 6.2—8 volts, 5 ma (Hughes or equivalent)
- J—2 contact input receptacle
- M—0-200 μ A, 4-inch rectangular (Simpson Model 29 or equivalent 1,000-ohm meter)
- RY—millisecond type, 6-volt 150-ohm coil (Stevens-Arnold type 173 or equivalent)
- S1—sps toggle
- S2—spsdt pushbutton, spring return
- V—2N188-A
- Case, bakelite, 6 3/4 x 5 1/4 x 2 1/4 inches
- Panel, bakelite, 6 1/2 x 5 inches
- M scellaneous hardware

WHEN DEPRESSED METER RANGE IS 15V FULL SCALE

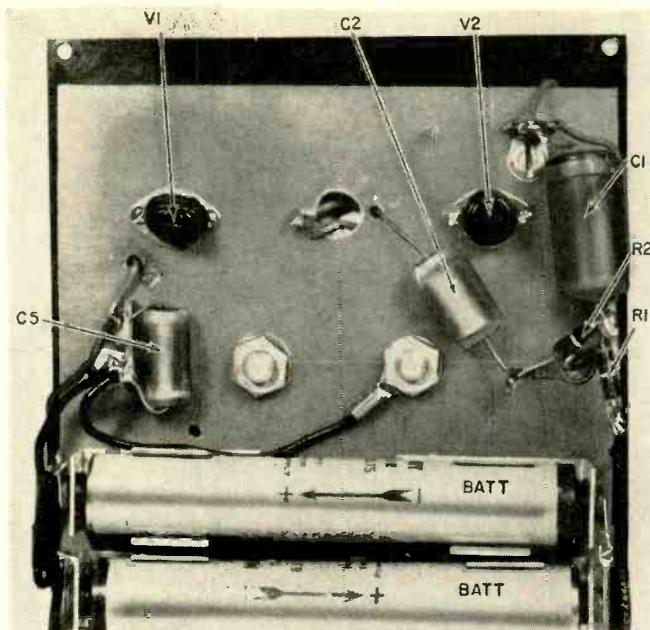*Outboard Marine Research Center, Milwaukee, Wis.



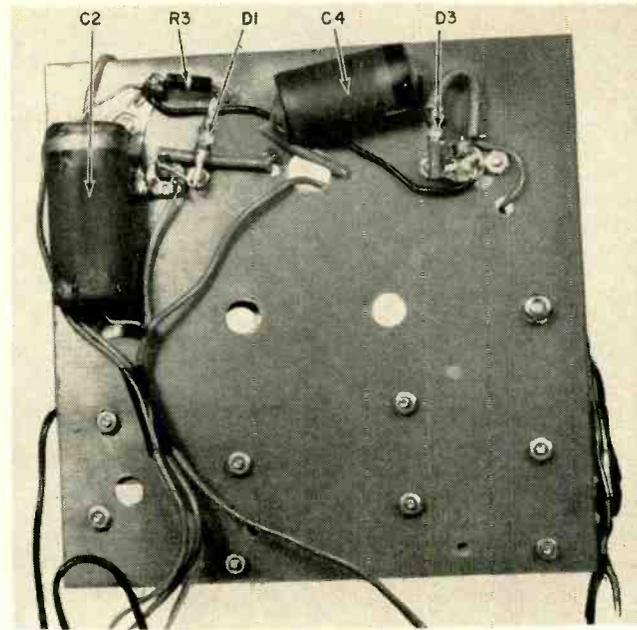Inside all-electronic unit of Fig. 2. Note transistors.



Rest of components are on this side of chassis board.

tronic tachometer that can be used on battery- or magneto-ignition engines (Fig. 2). The input circuit is the same as for the first one.

A negative pulse is fed to the base of transistor V1, making it conduct. Between pulses, V1 is cutoff. Through voltage dropping resistor R4, Zener diode D2 swings between its maximum rated voltage when V1 is conducting and zero volts when V1 is not conducting. The pulse coming from D2 has a definite amplitude and is fed to potentiometer R5, which acts as a pulse amplitude control. This pulse is then fed to C4, giving it a charge with every pulse.

C4 is part of a transistor pump circuit that was described in *Wireless*

- R1—2—1,000 ohms
- R3—10 ohms
- R4—270 ohms
- R5—pot, 500 ohms, 2 watts, linear taper
- R6—74,000 ohms, 2% (73,200 and 806 ohms, 1% in series)
- All resistors 1/2-watt 10% unless noted
- C1—0.25 μ f, 400 volts, paper
- C2—4—0.5 μ f, 200 volts, paper
- C3—100 μ f, 25 volts, electrolytic
- C5—25 μ f, 25 volts, electrolytic
- BATT—13 volts (2—6.5-volt mercury batteries in series) (Mallory TR-135R or equivalent)
- D1—1N68-A
- D2—1N707, Zener diode, 6.2—8 volts, 5 ma (Hughes or equivalent)
- D3—1N68
- J—2-contact input receptacle
- M—0-200 μ a, 4-inch rectangular (Simpson Model 29 or equivalent 1,000-ohm meter)
- S1—spst toggle
- S2—spst pushbutton, spring return
- V1—2N188-A
- V2—2N293
- Case, bakelite, 6 3/4 x 5 1/4 x 2 1/4 inches
- Panel, bakelite, 6 1/2 x 5 inches
- Miscellaneous hardware

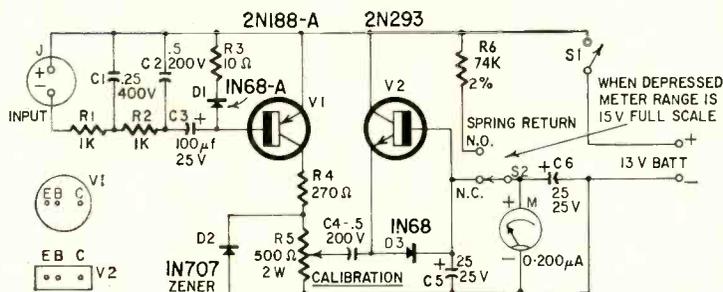


Fig. 2—All-electronic tachometer for magneto- or battery-ignition engines

World, March 1958 ("Unusual Transistor Circuits," page 107, by P. L. Burton and J. Willis). V2, D3 and C5 are all part of this circuit which discharges through the meter. The amount of current supplied to the meter from C4, the calibration, and the rest of the circuit are the same as Fig. 1. Again the instrument's accuracy is well within 2%, but it draws less than 30 ma from the power supply.

Battery-ignition unit

The third instrument is fundamentally electromechanical and can be used only with battery-ignition engines (Fig. 3). The input is in parallel with the breaker points with the proper polarity to ground. When checking a 12-volt system, leave S open. For 6 volts, close the switch. The 6-volt millisecond relay coil is energized every time the breaker points open and is de-energized when they close. When the relay is energized, C1 is charged through R4 from the Zener-diode regulated source. The charge on C is then applied to the meter circuit, as previously discussed. Calibration is also the same as in the other two tachometers described. Accuracy of this circuit is about 3%.

There are many possible variations of these tachometer circuits. The meter can be replaced by a resistor and a dc voltage proportional to the frequency which will appear across it can be used to activate any type of readout device

- R1—150 ohms, 1 watt, 10%
- R2—100 ohms, 1 watt, 10%
- R3—pot, 500 ohms, 2 watts, linear taper
- R4—10 ohms, 1/2 watt, 10%
- C—1 μ f, 200 volts, paper
- D—1N705, Zener diode, 4.3—5.4 volts, 5 ma (Hughes or equivalent)
- J—2-contact input receptacle
- M—0-200 μ a, 4-inch rectangular (Simpson Model 29 or equivalent)
- RY—millisecond type, 6-volt 150-ohm coil (Stevens-Arnold type 178 or equivalent)
- S—spst toggle
- Case, bakelite, 6 3/4 x 5 1/4 x 2 1/4 inches
- Panel, bakelite, 6 1/2 x 5 inches
- Miscellaneous hardware


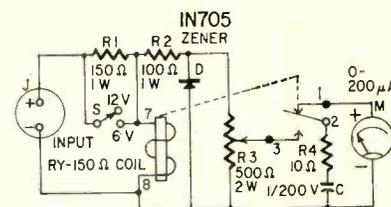


Fig. 3—Simple electromechanical unit checks battery-ignition engines.

or to control another circuit. Or you can use the electronic tachometer with a magnetic pickup setup to count the teeth in a gear or flywheel. The only requisite for a magnetic pickup is that the gear or flywheel be made of a magnetic material. The low-pass filter and clamping diode circuit can then be removed and the pulse fed through a capacitor directly to the base of V1. Bias the transistor so that center voltage appears at V1's collector. Then as the negative portion of the pulse is fed to V1's base from the magnetic pickup, the transistor will conduct and be cut off during the positive half of the pulse. The type and the placement of the pickup must provide sufficient voltage to make V1 conduct and cut off, or another stage of amplification will have to be added. Capacitor C4 should then be calculated for the frequency range of the pulses that will be received from the magnetic pickup at the gear's maximum speed so it provides sufficient current to the meter or indicating device.

END

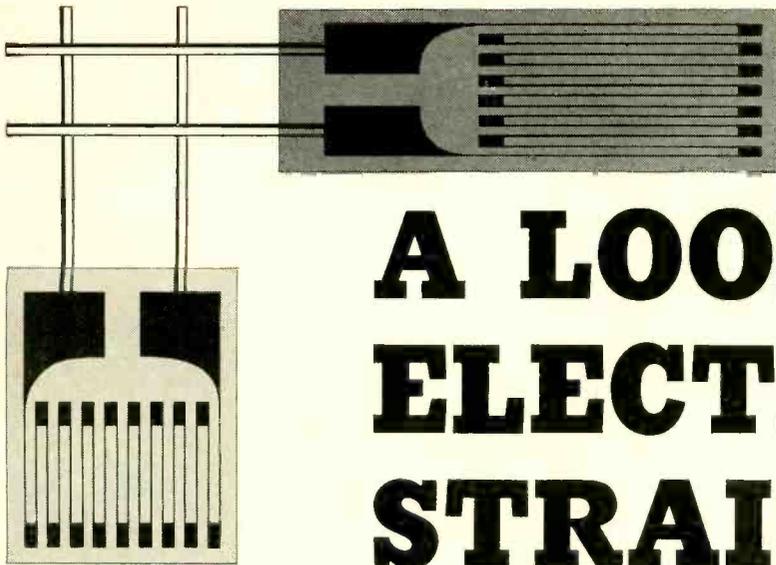

A LOOK at the ELECTRONIC STRAIN GAUGE

Strain gauges make it possible to measure the distortion of a steel beam or measure fluid pressure

By ARTHUR S. KRAMER

If you wonder why strain and stress measurements are important, take a look at some pictures or drawings of old-style rotating machinery. The reason why such massive heavy parts were used is simply that designers of those days had no convenient and accurate method to measure dynamic and static stresses. Cut-and-try methods were used, together with a multiplying "safety factor" of 4 or 5. The result was a large, heavy machine, costly in material and upkeep.

Contrast this picture with today's requirements for aircraft design, where maximum strength per pound of material is required. Other applications where strain measurements are of great importance are in concrete-highway and steel-bridge design. Several applications will be described and pictured further on in the article.

Early types

Before electronic strain gauges were invented, several ingenious mechanical and optical types were used. One used a pen to record strains on a moving chart. Another, for measuring stress conditions in concrete structures, was equipped with a writing stylus at the end of a long lever arm. A third mechanical type measured and recorded the stresses on a drum. All purely mechanical and optical types have one major disadvantage: they cannot be used in telemetering. This makes them of little use for flight testing of experimental aircraft, missiles and space vehicles.

One of the very first applications of the electronic strain gauge was in Los Angeles in 1931. A crude type was built and used in the Big Tujunga Arch dam

project. Basically, it consisted of a framework of two unglazed porcelain plates grooved to accommodate three coils of steel wire. Although it was fairly accurate, it was big clumsy and relatively insensitive.

Another early type was magnetic rather than electrical, and was arranged in an ac bridge circuit. The air gap of the strain-gauge head varied according to the strain in the tested specimen, and unbalanced the bridge.

The modern resistance-wire strain gauge (invented almost simultaneously by Simmons and Ruge in 1938) is a transducer which transforms a strain in a tested specimen into a change of electrical resistance. If the gauge is one of four resistors connected as a Wheatstone bridge, a strain will unbalance the bridge. This is the way in which most resistance-wire gauge circuits function. The essential parts of a simple system consist of the gauge cemented

to the specimen, three other resistors (possibly dummy gauges), an energy source such as a battery and an indicating meter.

Baldwin acquired the original inventions (wire-resistance strain gauge) by Simmons and Ruge and began to manufacture them as SR-4 (Simmons-Ruge) gauges. Early SR-4 gauges consisted of a simple grid of 1-mil wire looped back and forth and cemented to a sheet of thin paper. Short copper lead wires were provided. In use, the paper was cemented to the desired spot on the specimen and the gauge was oriented in the direction in which the strain was to be measured.

Modern types

Modern strain gauges are made in several forms. One of the most common is the bonded-wire type as shown in Fig. 1. A piece of fine resistance wire is looped back and forth and connected

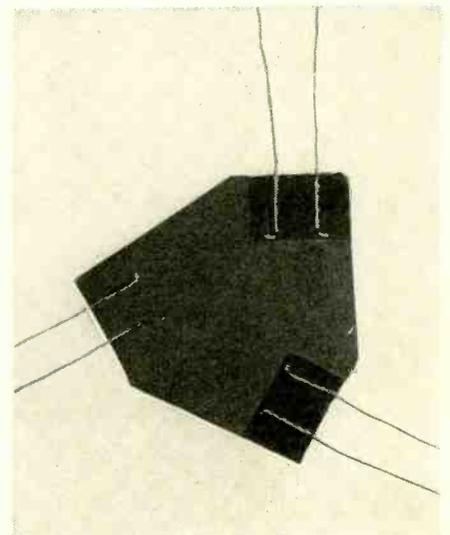
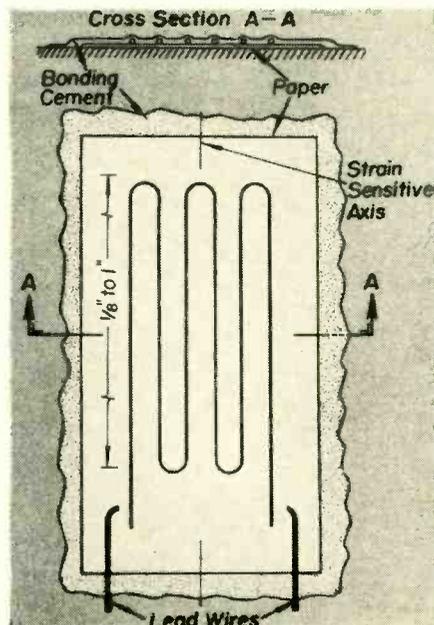


Fig. 2—Rosette gauge with three elements.

Fig. 1—Bonded-wire strain gauge.

by leads to the external measuring circuit. A cross-section shows how the wire is bonded to the paper with cement. When gauges of this type are made with Karma wire, (a special alloy usable up to 900°F) they are suitable for use in high-temperature applications.

A variation of this type is the multiple-grid or *rosette*. It consists of several gauges mounted with their major axes at various angles to one another and is used for measuring multidirectional strains at one point on the specimen (Fig. 2).

Consolidated Electrodynamics Corp. produces a chamber type of unbonded strain-gauge pressure pickup (Fig. 3). It is claimed that this transducer retains its accuracy at pressures up to 10,000 pounds per square inch. A spring type sensing element with four active arms is used. Pressure against the diaphragm displaces the sensing element, changing the resistance of the active arms and causing an output proportional to the applied pressure.

An important sort, with a growing list of applications, is the etched-foil gauge (Fig. 4). These are produced from an extremely thin foil sheet by photo-etching techniques and have no

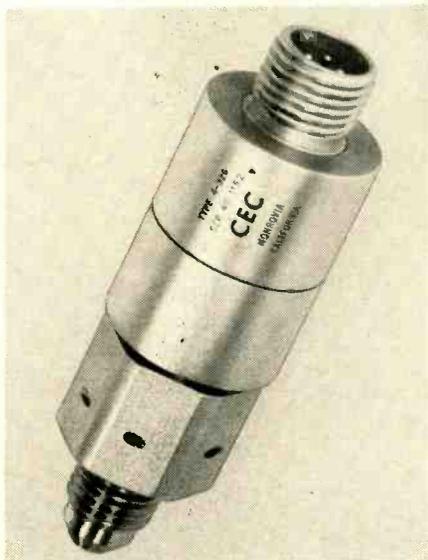


Fig. 3—Chamber type pressure pickup by Consolidated Electrodynamics Corp.

critical internal joints. They are rugged and stable and are easily fitted to sharply curved surfaces. It is possible to stack them in rosette form.

Polyphase Instrument Co. (Bridgeport, Pa.) has developed a "load-sensitive bolt." This permits direct measurement of the actual bolt load. The bolt is threaded right into the structure under test. Tension or compression is sensed by special resistance type strain gauges potted axially at the center of the screw (bolt or rod) (Fig. 5).

The vibrating-wire kind of strain gauges uses different principles. The resonant frequency of a taut steel wire varies with the tension. A wire is rigidly anchored in a frame which, in turn, is securely fastened to the specimen. In use, the wire is "plucked" by an electromagnet, which then picks up the vibrations as stress is applied to the

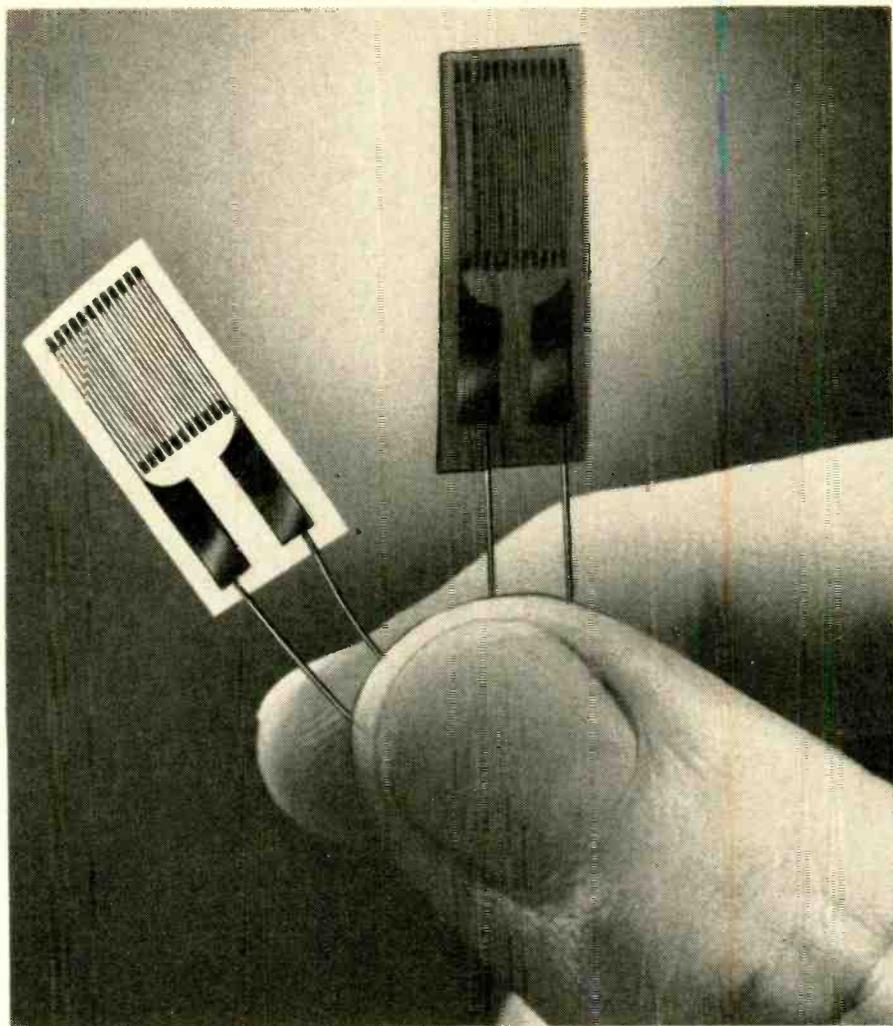


Fig. 4—Etched-foil gauges are more flexible than bonded-wire types.

specimen. The frequency is measured and, from previous calibration, the strain and stress are determined. This type is fairly common in England for measurements on concrete highways.

The Baldwin SR-4 fluid pressure cell illustrated in Fig. 6 consists of a pressure-sensitive metal tube to which bonded-wire strain gauges are attached. Changes in fluid pressure result in minute deformations of the tube with resultant changes in strain-gauge resistance. These changes will show on the external meter.

Stress and strain

In any discussion of strain gauges, *stress* and *strain* are frequently mentioned. Stress is the force exerted upon

an object or body which deforms it. Strain is the total change in any linear dimension of a body (because of external stress). *Unit strain* is the total change of any given dimension (of the stressed body) divided by the original (unstressed) dimension. Strain gauges usually measure unit strain in micro-inches per inch.

A 17th-century English physicist, Robert Hooke, formulated a law relating stress and strain. Simply stated, Hooke's law is "stress is proportional to strain." Algebraically, it is expressed as: $E = \beta/\lambda$ where β = stress, λ = strain and E = modulus of elasticity (Young's modulus).

Proper use of strain gauges makes determining the average stress intensity

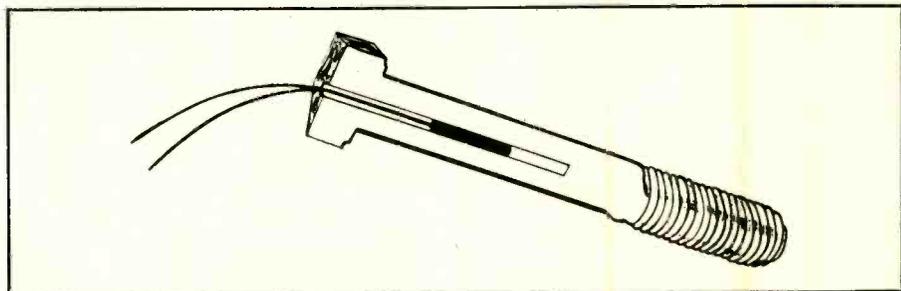


Fig. 5—Strain gauge imbedded in a bolt allows its stress to be measured.

ELECTRONIC

"AUXILIARY HEART"



Fig. 6—The Baldwin SR-4 fluid pressure cell.

at some point in a specimen quite easy. Just measure the strain at the point and multiply it by the modulus of elasticity. As an example, suppose a strain-gauge circuit indicates a strain of 2,000 microinches per inch ($2,000 \times 10^{-6}$ in/in). If the sample's modulus is 17.2×10^6 pounds per square inch (17.2×10^6 lb/in²), stress is $E = (17.2 \times 10^6 \text{ lb/in}^2) (2,000 \times 10^{-6} \text{ in/in}) = 34,400 \text{ lb/in}^2$. This is the way in which strain-gauge readings are used to determine stress at one point (or many) in a specimen.

Gauge factor

Strain-gauge factor (or simply gauge factor) is a very important quantity. This is the ratio of unit change of gauge resistance to unit strain. As a formula,

$$F = \frac{\Delta R/R}{\Delta L/L}$$

where R = original resistance of the gauge wire,

L = the original length of the gauge wire,

ΔR = the small change in resistance which takes place as the gauge is strained,


ΔL = the small change in length which takes place as the gauge is strained.

Various wire materials have different gauge factors. For nichrome, F is +2; for manganin, +0.47; for platinum, +4.8, and for nickel, -12.1. The gauge factor is equivalent to the sensitivity of the gauge. Other factors being equal, the material with the greatest gauge factor would usually be picked for a given application.

Strain gauges are used to weigh heavy loads, determine the strain on a gun barrel, measure torque, measure the thrust of a jet engine, etc. A future article will show some of these uses and discuss measuring circuits.

The author wishes to express his thanks to Mr. T. L. Gaffney of Baldwin-Lima-Hamilton Corp., Waltham, Mass., who contributed much useful technical information and the photos of Figs. 1, 2, 4 and 6.

END

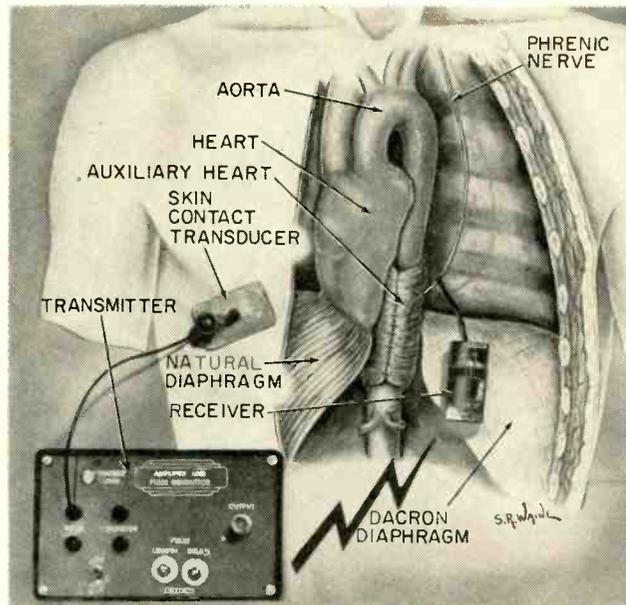

The artificial heart is a section of the diaphragm wrapped around the large artery. Its assistance to the real heart can be decisive in some cases.



Fig. 1—Block diagram of transmitter.

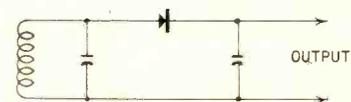


Fig. 2—Simplified schematic of receiver.

An electronically actuated heart "booster" can take over as much as 25% of the work of an impaired natural heart.

Developed by Dr. Adrian Kantrowitz, director of cardiovascular surgery, and Dr. William M. P. McKinnon, research fellow, at Maimonides Hospital in Brooklyn, N. Y., the electronic "second heart" has been used successfully in animals.

The rather crude diagrammatic representation shows how the electronic heart would be applied to human beings. The auxiliary heart actually is formed from a section of the diaphragm, which is replaced by the sheet of Dacron fabric. The diaphragm section retains its original blood supply and its connection with the phrenic nerve. The aux-

iliary heart is wrapped around the aorta (the large artery that carries blood to the body).

The skin-contact transducer picks up the natural heartbeat. It is translated into an rf pulse in the transmitter (Fig. 1). The pulses are transmitted to the Lucite-encased receiver (Fig. 2) embedded in the body. The receiver emits a faint electrical impulse which stimulates the phrenic nerve and causes the muscle to contract.

A relay system in the transmitter makes it possible to cause the auxiliary heart to beat alternately with the natural heart, if desired. Researchers currently are exploring methods to shield the receiver against random radio waves.

END

MODERN PICTURE-TUBE testers

This article will clear up some of the confusion surrounding the terms "open, reactivate and rejuvenate" as applied to TV picture tubes

By WILLIAM KELVIN

Chief engineer, Mercury Electronics Corp., Mineola, N.Y.

If you've been in the TV service business for a few years, you have probably run into at least one case where you were willing to bet a month's income that the picture tube was bad. All the symptoms were there (uncontrollable brightness, bad focus, barely discernible video, but good sync and plenty of high voltage). Later you were glad you didn't make the bet out loud because you would have lost it to a shorted video coupling capacitor! This has happened to plenty of competent men who did not use a good picture-tube tester. Even sadder is the case of those who confidently installed a new picture tube in the home, with the customer watching!

Today, the well-equipped service technician must be able to identify a bad cathode-ray tube every time. And, just as important as being able to convince the set owner that his "big tube" is bad, the technician must also convince himself.

A professional picture-tube tester must:

- Check heater continuity
- Check picture-tube output or "quality"
- Check life expectancy
- Reactivate low-emission cathodes
- Check for interelement shorts
- Repair interelement shorts
- Check for opens
- Reweld opens

No instrument can repair all bad tubes, but a good one can tell the service technician when a tube is repairable and when it is not. And it can guide him in using his judgment on those inevitable borderline cases.

Heater continuity

All popular CRT testers use a neon indicator for this test. Fig. 1 is a typical heater continuity circuit (in simplified form). The tube heater is put in series with a neon lamp, a current-limiting network and a 117-volt portion of the transformer secondary. Usually, if the heater shows no continuity, the picture tube must be replaced. Rewelding a CRT heater is not practical for reasons mentioned later.

Picture-tube quality

Since picture quality is directly related to cathode emission, emission measurement is known as a quality check. Practically all picture-tube testers use the emission-check principle that has been used for decades to test receiving tubes.

Fig. 2 shows a simplified circuit of the most widely used method for checking picture-tube cathode emission. In this circuit, the screen grid is tied to the control grid. Resistance R limits cathode current to a maximum of 5 ma. This is a heavier drain on the CRT than would be put on it by a TV set, but not enough to damage the emitting surface. Many engineers favor this design because the slight overload on the cathode shows up a weak-emitting condition at once. In this way, a BAD quality reading is obtained for tubes with nearly exhausted cathodes. Many of these nearly dead tubes still show a dull raster that gives a poor although usable picture. The BAD reading warns the technician that the tube will shortly be needing reactivation, if not replacement.

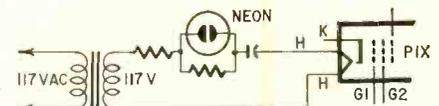


Fig. 1—Basic circuit used to check heater continuity.

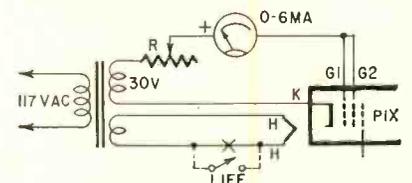


Fig. 2—Circuit used to measure cathode emission and life expectancy.

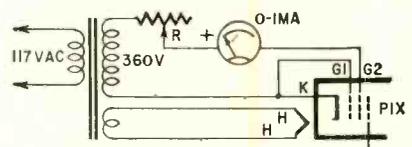


Fig. 3—An alternate emission test using the screen grid.

Another method of checking emission is shown in Fig. 3. This circuit is less common but is favored by some designers because the test voltage is applied between screen grid and cathode, thus more closely approximating beam current. Notice that over 10 times as much test voltage is required. The maximum cathode current drawn by this method is 1 ma.

As an addition to the emission test, a few picture-tube testers provide an extra—a means for measuring the CRT cutoff voltage. This adds to the cost of the instrument and is omitted by most designers because this characteristic of

a cathode-ray tube is actually of more interest to the tube manufacturer than to the service technician or set owner. It is a measure of the contrast ratio that the tube will show on its screen. Referring to Fig. 4, the CUTOFF control applies increasing negative bias to the picture-tube grid (or increasing positive bias to the cathode) as it is advanced. The less bias needed to cut off the cathode current, the greater is the tube's contrast ratio. Thus a high cut-off voltage would seem to indicate a

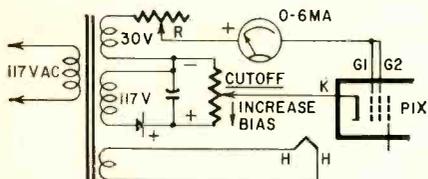


Fig. 4—Emission test circuit with cutoff voltage measurement feature.

bad tube because it means low contrast ratio. However, this does not necessarily follow because high-cut-off-voltage tubes can still show good contrast ratio if cathode emission is high.

Life expectancy

A means of checking the life expectancy of a CRT is found in all but the lowest-price instruments. As a service technician, you must have been asked by many customers: "How long do you think my picture tube will last?" With a life expectancy test, you can give a reliable answer.

All manufacturers who include such a test use a method like that illustrated in Fig. 2. The quality reading is noted and then the heater circuit is opened with the LIFE switch. The cathode cools causing emission to fall off. A "countdown" of the number of seconds it takes for the current to fall to zero measures the life expectancy of the tube, since it is directly related to the amount of emitting material on the cathode.

The question of gas content arises here, since gas in a CRT will shorten its life. The gas particles ionize within the

tube leading to the familiar negative-picture effect. A gassy tube must be replaced once this effect has become severe.

Cathode reactivation

The term "reactivation" is frequently misunderstood or misapplied. It is also called "rejuvenation". Both terms seem valid because it may be said that after *reactivating* an inactive cathode, the tube has been *rejuvenated*, since it performs like a youngster once more! The successful repair of shorted or open elements in a CRT is definitely a case of reactivation, since the tube was certainly out of action before the repair. For consistency, the word *reactivate* will be used here to denote any kind of an operation performed to cure an ailing picture tube.

The best known reactivator for weak emission is the common brightener. Professional tube testers always contain a built-in brightener, or booster, in addition to their other features. The circuit shown in Fig. 5 illustrates the most widely used method of boost re-

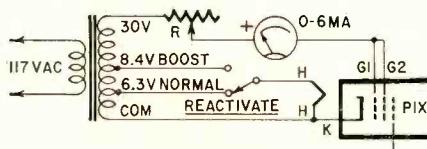


Fig. 5—Boost reactivation raises tube's heater voltage somewhat.

activation with an additional feature that the manufacturer calls "Watch It Reactivate." This consists of boosting the heater voltage while reading the emission. The service technician can see whether or not the picture tube responds to reactivation. When this is done in the home, the TV set owner also can see the results obtained with his tube.

As shown in the full schematic of Fig. 6, the latest picture-tube tester design has provision for picture tubes

with the new heater ratings of 2.35, 2.68 and 8.4 volts. Some designers call for a 1- to 2-minute period of overheating the cathode before measuring emission. One manufacturer provides a double boost, but most reactivators have a boost voltage approximately 30% above normal. This limit avoids any danger of heater burnout.

A more powerful method of emission reactivation is called "sweeping" the cathode or "shot" reactivation. The service technician will find this provided in all the medium- and higher-priced instruments. Basically, a high voltage is applied to the CRT signal grid (for a short period of time) and


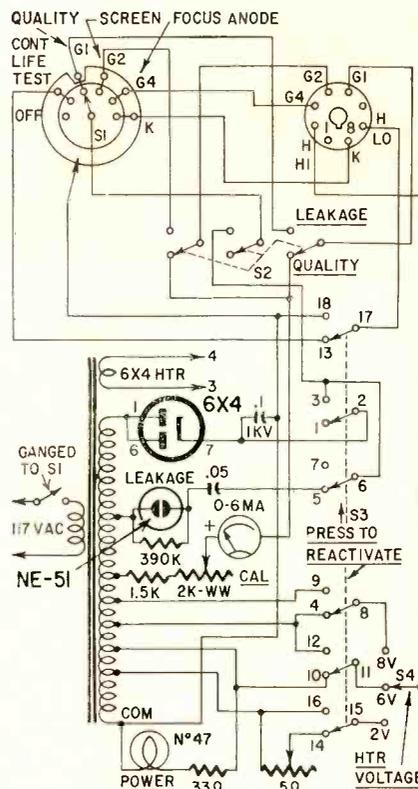



Fig. 6—Schematic of Mercury 800 CRT tester.

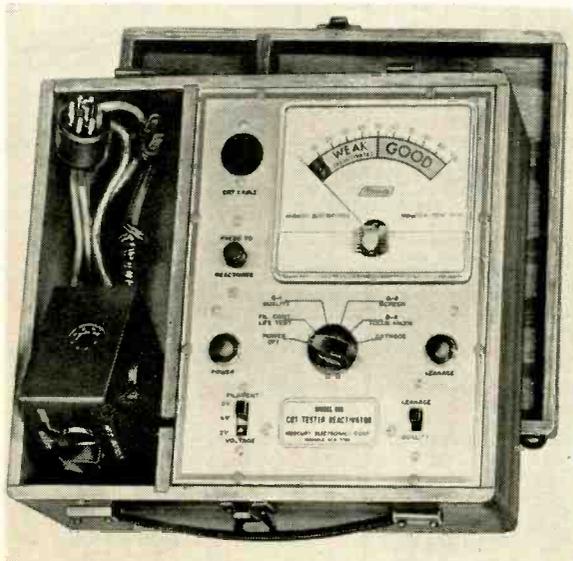

Mercury 800 CRT tester.



Superior Instruments model 83-A.

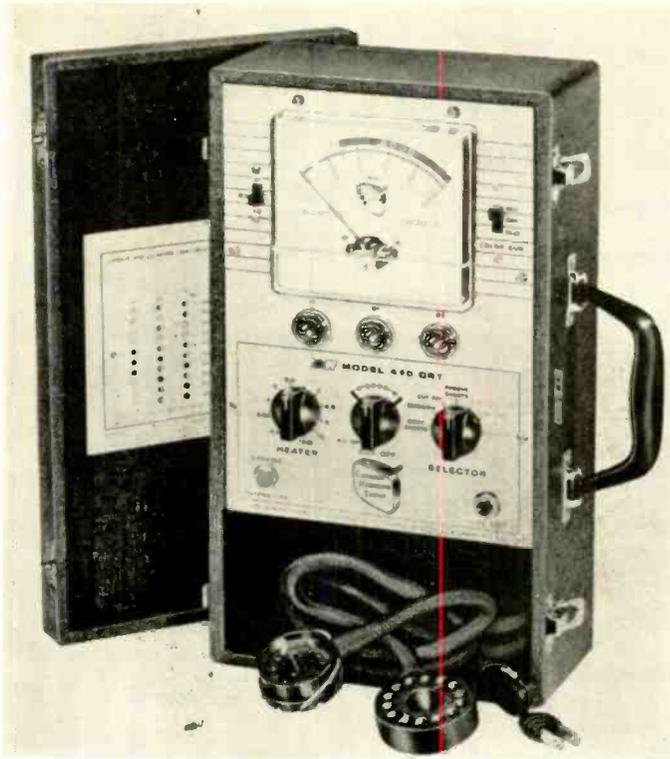

B & K 440 Cathode Rejuvenator Tester.



Anchor Products T-470 CRT tester.

draws a *momentary* emission current of very high density. This knocks contamination from the cathode surface and allows emission to return to normal.

The high voltage used for shot reactivation varies from 200 to 1,000. Fig. 7 shows a 1,000-volt shot reactivation circuit. Note that the applied voltage is

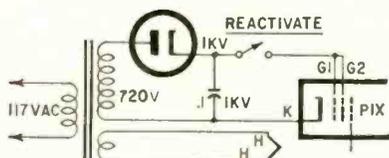


Fig. 7—Shot-reactivation circuit.

dc, which takes advantage of the power-supply characteristic to control the current flow and avoid damage to the picture tube.

Interelement shorts

Not all shorts in a picture tube are repairable. But a surprising number of picture tubes which seem hopelessly shorted and which show a poor raster (or no raster at all) can be completely cleared of shorts and restored to useful life.

Fig. 8 shows a type of short that can be repaired. It is caused by a bit of metallic dust getting between two elements in the CRT gun. Fig. 9 shows a short that usually cannot be repaired. This is a structural defect that

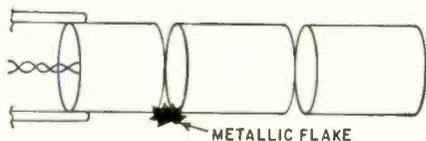


Fig. 8—A metallic flake can short two elements together.

might be a fault of manufacture or caused by excess heat of operation. Note that the CRT gun elements are warped and touching each other.

To check for a short, we need an indicating device and a means of isolating the shorted element. A neon lamp is invariably used as the indicating device. All popular CRT checkers use one of two methods to isolate the shorted element.

The first method—preferred by the majority of manufacturers — uses a switch. Each position is labeled with the name of the element to which it is connected. If the neon lamp lights when the switch is turned to any one position, one of the shorted elements is positively identified (Fig. 10). Switch section A contacts all but one element and connects them through the neon-indicator network to one side of a transformer winding. Section B of the switch con-

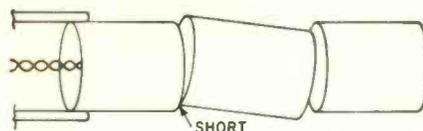


Fig. 9—A short caused by structural deformation.

nnects the isolated element to the other side of the transformer winding. Thus, a short between the isolated element and any of the other elements causes the neon lamp to glow.

The second method (Fig. 11) employs several indicator lamps. Here each element is isolated by a lamp except for the cathode. An advantage of this method is that no switch is necessary. To identify the shorted elements, however, it is necessary to interpret the various combinations in which the four lamps can glow.

Repairing interelement shorts

To repair a short, a momentary high current must be passed through the shorted path (in an action similar to shot reactivation as described above). The intense heat of the high current burns up the loose material lodged between the elements and thus clears the short. In the circuit of Fig. 12, a switch similar to that of Fig. 10 allows you to apply the repair voltage to any one element. This method can clear a cathode-to-heater short, a feature not provided by some instruments. Danger of heater burn-out is avoided by separating the heater- and repair-current paths.

Ac may also be used for repairs. One early manufacturer of CRT testers used a high-voltage rf supply called a Sparker. Repair circuits have proved to be a very popular feature and are found in nearly all instruments.

Open elements

Technicians often misunderstand the term "open element" in a picture tube. In particular, a cathode whose emitting surface has become dead is often referred to as an open cathode. It is not open unless there is an actual break in the wire leading from the base pin. Such breaks do occur and can sometimes be seen inside the tube neck (Fig. 13). However, whether the failure of the element to pass current is due to a lack of emitting material or due to a break, the treatment is the same and is covered in the various instruction manuals under the heading of Welding. A simple test for an open is to tap the neck of a CRT which shows no raster at any brightness level. If the screen lights up momentarily at each tap, an element (usually the cathode) is intermittently open and it is worth try-

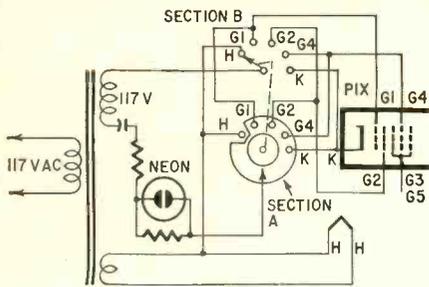


Fig. 10—Double-section switch allows identification of shorted elements.

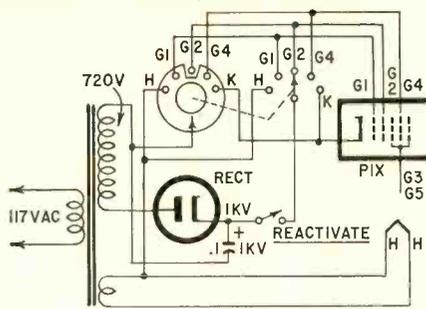


Fig. 12—A high-voltage pulse may be used to burn out certain shorts.

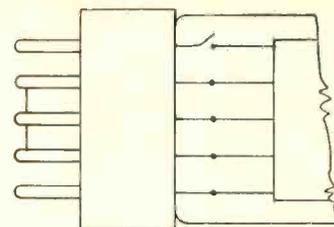


Fig. 13—A visible open in a CRT neck.

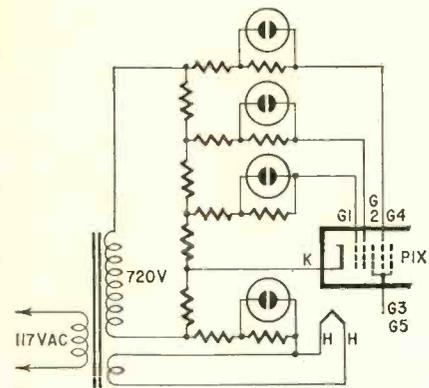


Fig. 11—A short check that requires no switch.

ing to reweld it. In Fig. 13 the break where the gun element will be welded to the base pin can be seen.

Rewelding opens

Spot welding in industry is bonding two metals by the heat of an electric current or arc passed between them. An open element in a CRT is welded in the same way. The welding technique is modified for picture tubes, to accommodate the relatively large gap presented by an open element. The CRT tester must force an arc to cross the gap. This requires high voltage. Even so, unless the ends of the element are very close or touching they cannot be welded.

Technicians who use reactivators with a welding feature tap on the CRT neck while applying the high voltage. The tapping jiggles the broken ends. When they brush against each other, the arc completes the weld. This can be done by the circuit that is used to repair shorts, shown in Fig. 12. For welding, the high voltage is applied continuously until an arc is struck, rather than momentarily as when repairing of an interelement short.

Rewelding CRT elements is completely successful in less than half the attempts. But those welds which hold enable the picture tube to perform as well as ever once more.

A note about open heaters: In general, you cannot successfully reweld them. The heater is a high-current element, passing 600 ma in most picture tubes, as compared with only 2 ma for the cathode. This heavy current will heat up and open any weld which has appreciable resistance. Also, the filament expands and shrinks when the TV set is turned on and off. This will open the weld unless it is perfect. Most technicians prefer to recommend CRT replacement when they diagnose an open heater.

Adapters

All manufacturers of CRT testers provide for testing the small-based

110° picture tubes, and most also accommodate color picture tubes. This is done by adding cables or by supplying adapter caps for use with the standard socket on the existing cable. In the model designed by the author, shown in one of the photographs, a Multi-Head solves this problem. The Multi-Head is seen in the compartment at the left side of the instrument case. It is a single cable terminating in a head that contains all four socket types in use today. A COLOR-GUN switch is also included in the head. Fig. 6 is a complete schematic of this instrument (which will check the newer 2- and 8.4-volt types).


A check with various cathode-ray manufacturers shows that no new bases are planned at present. However, adapters can be made for any new bases. The test procedure will not change because the emission characteristics of all picture tubes are very similar.

Today's technician must be armed with something more than a "brightener" in his caddy if he expects to win enough customer confidence to get his share of the picture-tube repair and replacement business. And brother, it's a big business! If you don't think so, just do some figuring. There are 60,000,000 sets in the country, average picture-tube life is 3 to 4 years and the retail price of replacement picture tubes averages over \$30 apiece. The annual gross is over a half-billion dollars and still growing! END

THREE DISHES

The two prettier ones are sitting in the center of a 40-foot parabolic antenna at ITT Labs, Nutley, N. J.

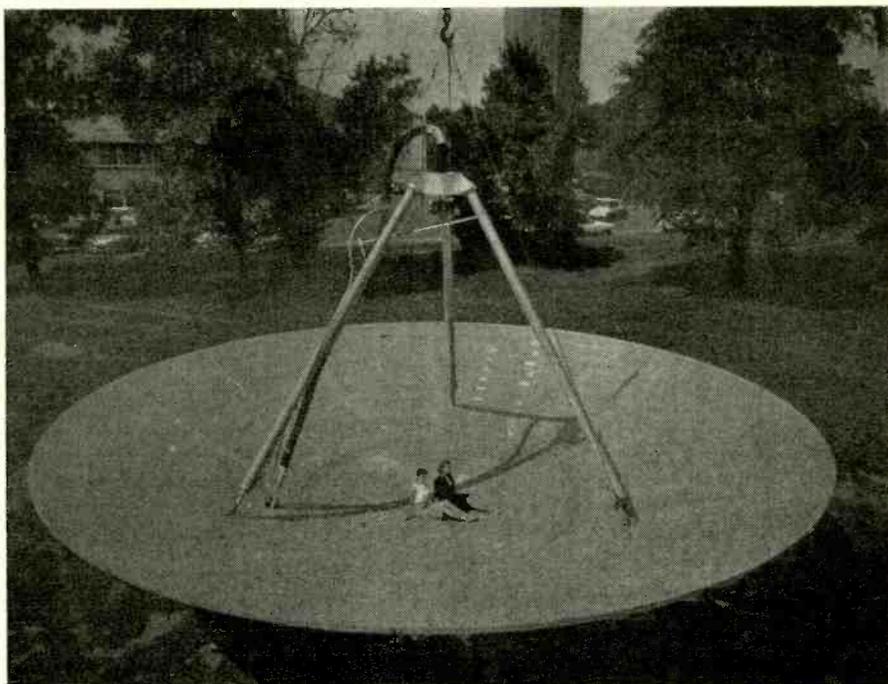The big one, when mounted, will enable scientists to pick up radio signals bounced off the moon or man-made satellites.



TV Service CLINIC

conducted by
JACK DARR

CONTRARY to the old saying, lightning does strike twice in the same place. (One of the reasons they used to give me for its not doing so was that the place struck actually wasn't there the second time!) Be that as it may, there is one place where lightning strikes much more than once—the tuner input coils of a TV set (Fig. 1).

These are usually pretty delicate. Fig. 2 shows a representative sample of the types found in modern tuners. They're wound of very fine wire and it doesn't take too much of a jolt from lightning to knock out one or both of the coils. This plays havoc with the picture, of course, because it upsets the impedance match between the tuner input and the lead-in.

The only purpose of these coils is to transform the 300-ohm balanced impedance of the lead-in to the 75-ohm unbalanced impedance of the tuner input, to be applied to the grid of the rf ampli-

Fig. 1—Typical balun coil used in tuner input.

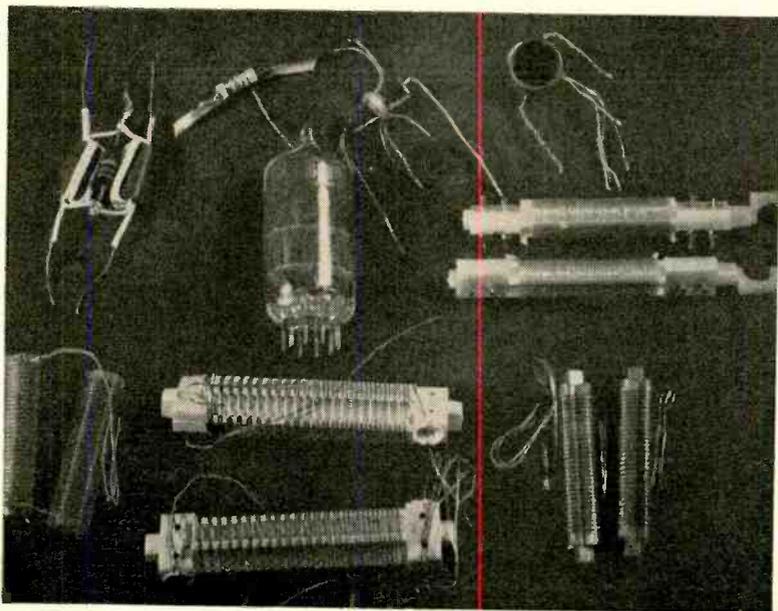
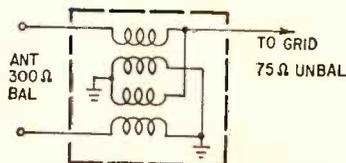


Fig. 2—Representative samples of tuner input coils.

DECEMBER, 1960


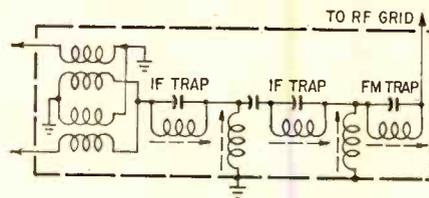


Fig. 3—Antenna matching unit used in better TV receivers.

Fig. 4—Lightning off power line can affect set. Lightning passes through line bypass capacitors to chassis, through chassis to grounded end of balun, from balun up lead-in to antenna, then down mast to ground. In hot-chassis receiver lightning goes directly to bottom of balun.

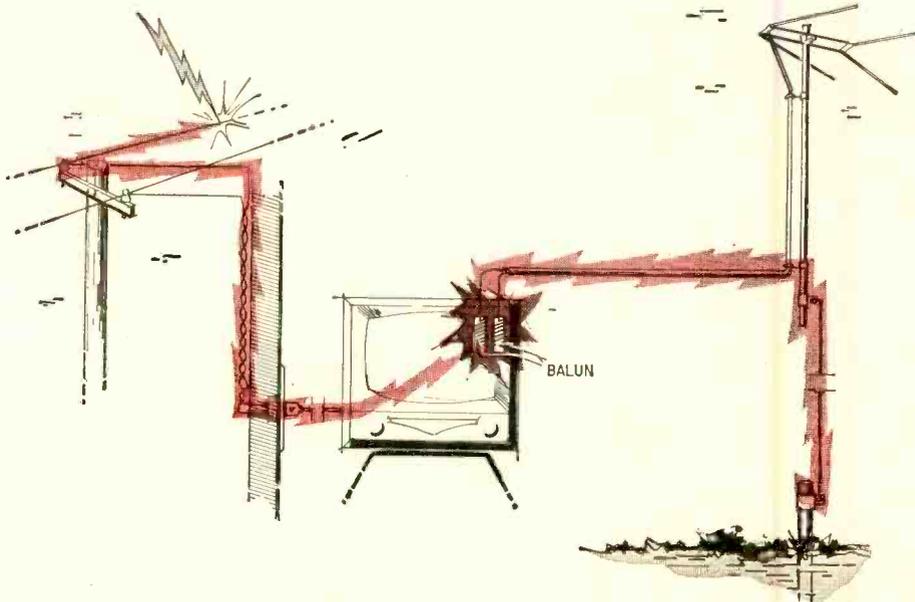

fier. For this reason, they're called balun coils—they work between BALanced and an UNbalanced load.

In addition to the baluns, many tuners incorporate if and FM traps in the tuner input (Fig. 3). These are usually a bit sturdier than the balun windings, but still fragile enough to be damaged on occasion. Capacitors used in the traps can be opened by a severe hit, while isolating R-C networks used between the set's antenna terminals and the tuner are often blown out in the most literal sense of the words!

It doesn't take a big direct hit to do a lot of damage here either. There are quite a few hits by lightning that we never know anything about. Lightning striking rural or city power wiring can blow tuner coils. This has been definitely proven in many cases! The path taken by the energy here is somewhat like that shown in Fig. 4. It's a long way around, but it gets there!

So if the complaint happens to be excessive snow, lack of contrast or an intermittent condition in picture or sound, check those balun coils in the tuner with an ohmmeter from the tuner input. The grid lead may have to be opened for a positive check, but it is usually easy. If they have taken a good hit, the evidence will be very clear! However, never rely on a visual check.

(Continued on p. 68)

nicians, marine enthusiasts, sports car owners and hobbyists. And many Heathkit products are now available in both wired and kit form!

Address _____

City _____ Zone _____ State _____

Dealer and export prices slightly higher.

(Continued from page 63)

We once pulled a coil which was apparently undamaged on the outside, only to find every turn blown open on the back side!

Standard replacements are available—Fig. 2 shows a typical service-shop stock. The coils shown will replace 95% of the input coils in modern tuners. It takes a long thin soldering iron, a very long-nosed pair of tweezers and infinite patience to replace some of them, but it has to be done!

Unsound sound

In a Packard-Bell 2111-2 TV, the picture is good but sound is fuzzy on channels 7, 9 and 11. Channels 4 and 5 are normal or nearly so. I've tested the tubes in the tuner and video if without results.—T. R. W., Seattle, Wash.

I believe I'd check the tubes in the sound if and the ratio detector by substitution before I did anything else. If this doesn't help, alignment of the audio section is a must.

You can align the sound if's by using a station signal, if you have a good strong one nearby. Connect the dc

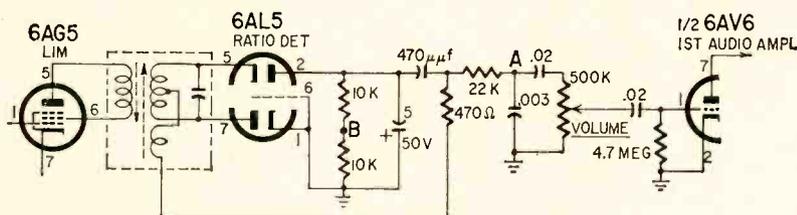


Fig. 5—Partial schematic of Packard-Bell 2111-2 audio section.

probe of a vtvm to the junction of the 22,000-ohm resistor and .02-µf capacitor between the 6AL5 and the 6AV6 first af amplifier (point A in Fig. 5). Now, tune in the best picture on the set, and set the vtvm for about a midscale reading; this should be only a few volts, and will be negative. Next, tune the sound if coil in the grid circuit of the 6AG5 for maximum. Now tune the primary of the ratio-detector transformer for maximum—you'll have to trace this one, but it's usually the bottom slug on the transformer. Tune all these for maximum reading.

Move the vtvm to the junction of the two 10,000-ohm resistors between pins 1 and 2 of the 6AL5 (point B). Adjust the secondary of the ratio-detector transformer for zero voltage at this point. You should have equal and opposite swings as the adjustment is varied about zero. In other words, if it swings 4 volts positive, it should swing 4 volts negative.

After this adjustment the sound should clear up if all parts are all right. If it is still fuzzy, replace the 5-µf electrolytic capacitor across the two 10,000-ohm resistors as this is a frequent cause of this kind of trouble. In fact, it might be a good idea to try this first, before you do the alignment. Might save a lot of time!

Metal to glass

My distributor says that I can replace the 21MP4 (metal-coned) picture tube in a Silvertone 25WG-3075 with a

glass tube, using a conversion kit. What electrical modifications would have to be made in the chassis and what type of tube would be the best replacement?—G. McK., Menasha, Wis.

Your distributor is right. Because of the ever-present shock hazard of the metal-coned tubes, it is a good idea to replace them with glass equivalents (when they need replacing). Using the conversion kit, it is not difficult to mount a glass tube in place of the metal tube.

The 21YP4-A is electrically interchangeable with the 21MP4 and no modifications are required. The only difference lies in the fact that the glass tube is about 3/4 inch longer than the metal one. This may require that the yoke bracket be set back slightly and you may have to cut a small hole in the "cup" on the back (if the original tube was too close).

Horizontal roll

A Motorola TS-425 TV came into the shop for horizontal rolling. Replacing several capacitors and a resistor eliminated the rolling. It now has a

phasing ghost about a third of the way across the screen from the left side. It also has a slight jitter. I've tested all components, replaced the dual diode in the afc and all other components in the horizontal circuits. All tubes have been replaced, including the damper and high-voltage rectifier.—W. H. R., Brad-dock, Pa.

Like yourself, I would have replaced that afc diode first! This cures most of these complaints. Since it didn't, there may be something else wrong in that circuit.

The first thing to do here is run a very careful alignment of the horizontal oscillator. In this series, the horizontal hold control should have a normal range of about 30°. If it doesn't, it needs adjustment.

Ground the horizontal afc, from pin 4 of the test receptacle on the chassis (Fig. 6). Connect a 0.1-µf capacitor between 2 and 5 on this socket to short out the ringing coil. Now adjust the horizontal hold control until the picture

stands still or as near to still as you can get it—it will drift from side to side. Now leaving the controls where they are, take the capacitor jumper off the ringing coil and adjust the slug for a locked-in picture. After the picture locks in, keep on turning the slug until it falls out again. Now, turn it back and leave it halfway between the two points.

If this process does not stop the trouble, try changing those diodes again just for luck! Incidentally, these diodes are the type connected with both diodes "looking the same way" (Fig. 6). Be sure that you have the right type, and also be sure that the polarity is right! Reversing the diode could cause trouble!

No magnet

A set brought in the other day had been converted to use a 21CQP4 tube. It has a single ion-trap magnet on the neck. I cannot get the picture bright enough and it is out of position, too. Neck shadows are always bad. Do you think the magnet is not strong enough, or what?—E. J. B., Hatfield, Ark.

Someone may be playing a prank on you. The 21CQP4 tube does not use an ion-trap magnet at all! This is a straight-gun type of tube, with electrostatic focusing. The surprising thing is that you got any picture on the screen with an ion-trap magnet of any strength at all on the neck. It looks as if the beam bender must be fairly weak.

Take the ion-trap magnet off and be sure that the picture-positioning magnets (the two thin metal rings with tabs) have been installed on the back cover of the yoke. Since this was a conversion job, whoever did it may not have installed them. They are necessary to get the picture placed properly on the screen with this type of tube.

Horizontal sync trouble

I am having trouble in the horizontal sync circuit of a G-E 21T14 TV. I originally had a shorted capacitor in the screen circuit of the horizontal output tube. I replaced it and the resistor, and brought the picture back in. When I put the chassis back in the cabinet and had everything connected and adjusted, I could not get the horizontal sync to lock in as it should. A large vertical black streak on the right side of the screen pulls to the left. When it moves, the picture tears up. I can just barely touch the horizontal hold. It stays locked in for 1 to 5 minutes, then tears again.—J. T. D., Babson Park, Fla.

The "large black streak" you see on

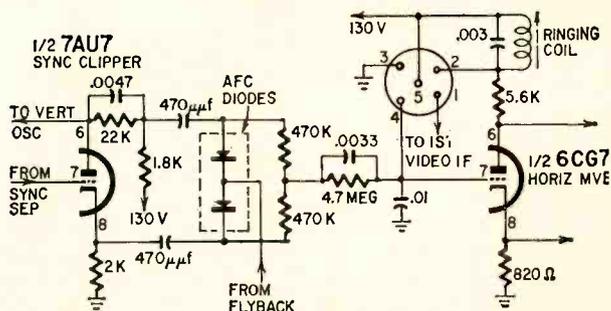


Fig. 6—Part of the horizontal sync and sweep circuits of a Motorola TS-425.

TV Service CLINIC

conducted by
JACK DARR

CONTRARY to the old saying, lightning does strike twice in the same place. (One of the reasons they used to give me for its not doing so was that the place struck actually wasn't there the second time!) Be that as it may, there is one place where lightning strikes much more than once—the tuner input coils of a TV set (Fig. 1).

These are usually pretty delicate. Fig. 2 shows a representative sample of the types found in modern tuners. They're wound of very fine wire and it doesn't take too much of a jolt from lightning to knock out one or both of the coils. This plays havoc with the picture, of course, because it upsets the impedance match between the tuner input and the lead-in.

The only purpose of these coils is to transform the 300-ohm balanced impedance of the lead-in to the 75-ohm unbalanced impedance of the tuner input, to be applied to the grid of the rf ampli-

Fig. 1—Typical balun coil used in tuner input.

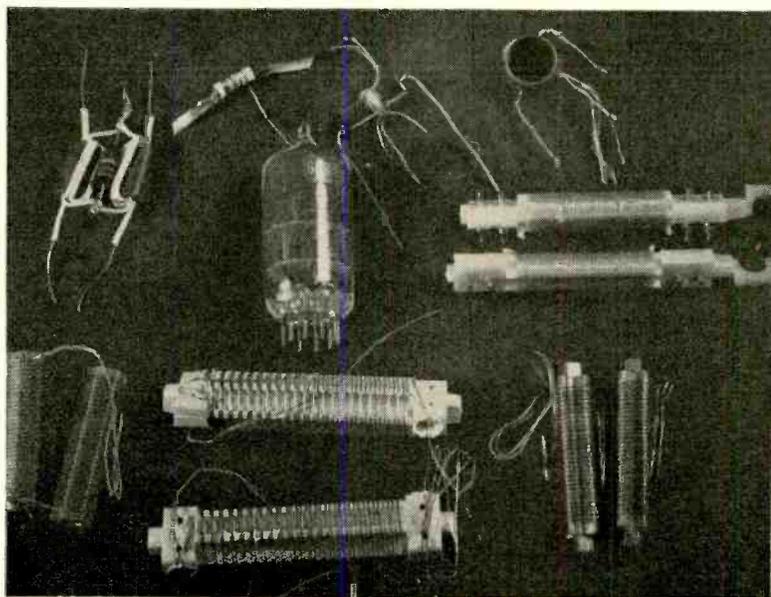
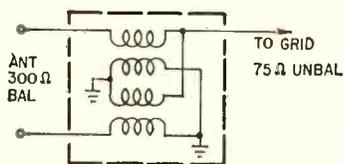


Fig. 2—Representative samples of tuner input coils.


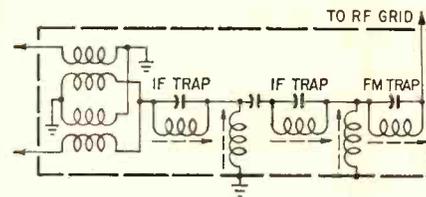


Fig. 3—Antenna matching unit used in better TV receivers.

Fig. 4—Lightning off power line can affect set. Lightning passes through line bypass capacitors to chassis, through chassis to grounded end of balun, from balun up lead-in to antenna, then down mast to ground. In hot-chassis receiver lightning goes directly to bottom of balun.

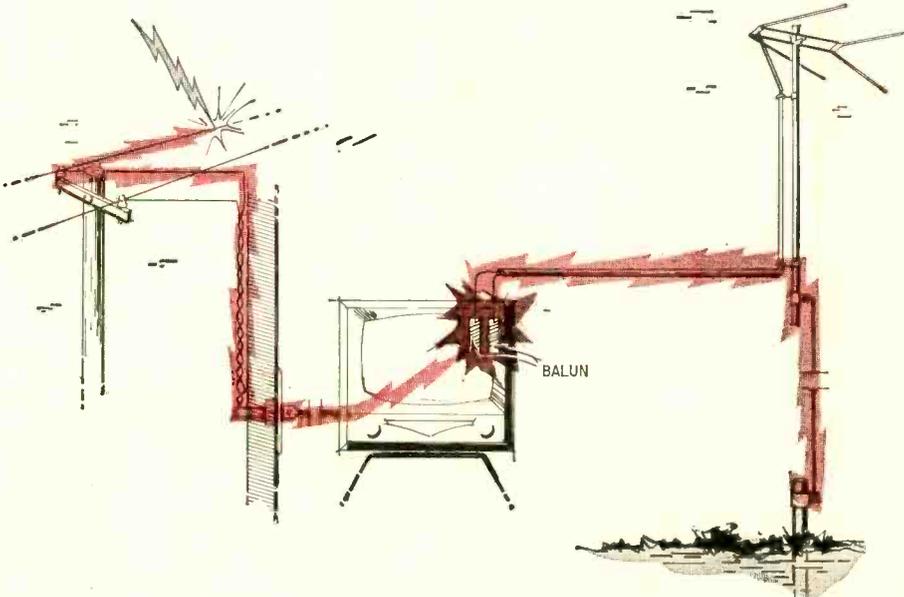

fier. For this reason, they're called balun coils—they work between BALanced and an UNbalanced load.

In addition to the baluns, many tuners incorporate if and FM traps in the tuner input (Fig. 3). These are usually a bit sturdier than the balun windings, but still fragile enough to be damaged on occasion. Capacitors used in the traps can be opened by a severe hit, while isolating R-C networks used between the set's antenna terminals and the tuner are often blown out in the most literal sense of the words!

It doesn't take a big direct hit to do a lot of damage here either. There are quite a few hits by lightning that we never know anything about. Lightning striking rural or city power wiring can blow tuner coils. This has been definitely proven in many cases! The path taken by the energy here is somewhat like that shown in Fig. 4. It's a long way around, but it gets there!

So if the complaint happens to be excessive snow, lack of contrast or an intermittent condition in picture or sound, check those balun coils in the tuner with an ohmmeter from the tuner input. The grid lead may have to be opened for a positive check, but it is usually easy. If they have taken a good hit, the evidence will be very clear! However, never rely on a visual check.

(Continued on p. 68)

for the ultimate in Christmas giving...



for the ultimate in electronic
design

**THIS YEAR
GIVE A
HEATHGIFT**

HEATHKIT® by DAYSTROM

**NOW ONLY
HEATHKIT®
Brings You
ALL 3!**

1.
HEATHKIT
for the do-it-yourself
hobbyist

2.
HEATHKIT
factory-wired &
tested units ready for
immediate use &
enjoyment

3.
HEATHKIT
Science Series ...
entertaining,
instructive
explorations into
science & electronics
for youngsters

"DELUXE" AM/FM STEREO TUNER

Exciting new styling and advance-design features rocket this Heathkit to the top of the Christmas value list. Featured in this outstanding tuner are: complete AM, FM, Stereo reception, plus multiplex adapter output; individual flywheel tuning; individual tuning meters on each band; FM automatic frequency control (AFC) and AM bandwidth switch. 24 lbs.

Model AJ-30 (kit) \$9.75 dn. **\$97.50**
 Model AJW-30 (wired) . . \$15.30 dn. **\$152.95**



HI-FI RATED 50-WATT STEREO AMPLIFIER

In the inimitable style of the Heathkit AJ-30 Tuner above, this complete stereo amplifier offers you the ultimate in stereo conveniences. Jam-packed with extra features, including: mixed-channel center speaker output; "function selector" for any mode of mono or stereo operation; "stereo reverse"; "balance" and "separation" controls; ganged volume controls; and separate concentric bass and treble tone controls. 30 lbs.

Model AA-100 (kit) \$8.50 dn. **\$84.95**
 Model AAW-100 (wired) . . \$14.50 dn. **\$144.95**



ACOUSTIC SUSPENSION SPEAKER SYSTEM KIT

Its "bookshelf" size belying its gigantic capabilities, this amazing unit outperforms speakers 4-times its size. A 10" acoustic suspension woofer and two "dispersed-array" cone tweeters deliver high-fidelity tone with fantastic brilliance over the entire range of 30-15,000 cps. \pm 5 db. Preamsembled cabinet in choice of finishes or unfinished woods. Measures 24" L x 11 $\frac{1}{2}$ " D x 13 $\frac{1}{2}$ " H. 28 lbs.


Model AS-10M or W (mag. or wal.) . . \$6.50 dn. **\$64.95**
 Model AS-10U (unfinished) . . \$6.00 dn. **\$59.95**


STEREO EQUIPMENT ENCLOSURE ENSEMBLE

Now, just in time for Christmas, Heathkit introduces new factory-assembled, ready-to-use equipment and speaker cabinets designed to house complete monophonic or stereophonic systems. The cabinets, resplendently styled in a timeless and universally compatible motif, are available in rich hand-rubbed walnut or mahogany finishes . . . or unfinished if desired. $\frac{3}{4}$ " stock is used for all exterior panels and supports; solids for edgings, furniture grade veneers for front and side panels and shelves. Versatile in accommodations, the center cabinet has room for all components of a complete stereo or mono hi-fi system except speakers. The changer compartment will accept any Heathkit record changer or most tape recorders. The storage compartment holds records and tapes or using an accessory slide-out drawer may be used for a tape recorder. Two shelf compartments accept tuners and amplifiers. The power amplifier compartment will hold any Heathkit stereo power amplifier, a pair of UA-2 mono amplifiers or any single mono amplifier. The handsome speaker-wing cabinets in two models for 12" and 15" speakers are designed to blend into the flowing lines of the center cabinet and are perfectly acceptable as single console speaker enclosures. Adapter rings are provided for using other size speakers, while a special port is provided for installation of a horn-type tweeter.

Complete ensemble as low as **\$133.50**. Send for details in FREE HEATHKIT CATALOG.

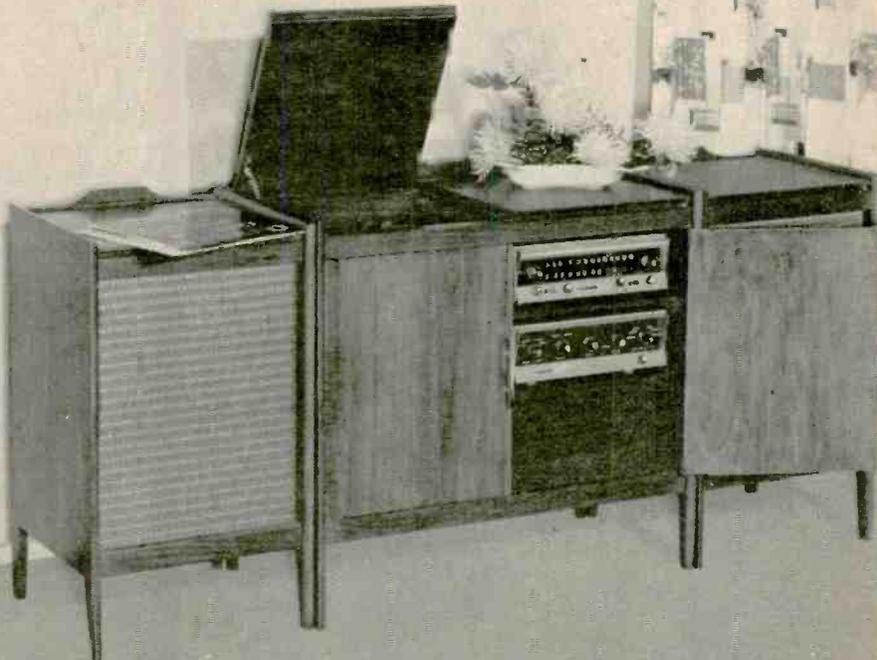*completely assembled
 . . . quality construction
 . . . contemporary styling . . . low cost*



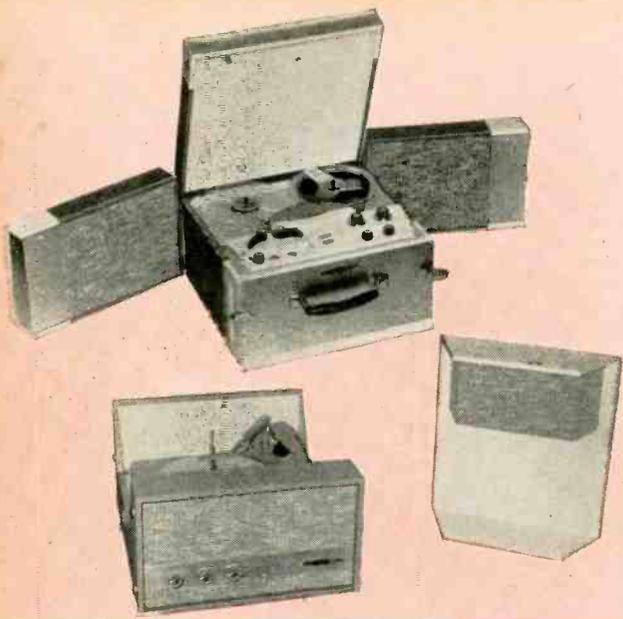

HEATHKIT®... for finer

PORTABLE 4-TRACK STEREO TAPE RECORDER KIT

What better gift than this? ... a compact portable tape recorder just waiting to record the caroling, frolicking family joys of the holiday season! You'll thrill to the natural stereophonic sound of this new unit that also serves as a hi-fi, power center for your tuner and record player. Tape deck and cabinet are preassembled.

Model AD-40... \$18.00 dn., \$16.00 mo. **\$179.95**

STEREO/MONO PORTABLE STEREO PHONO KIT

Thrill to your favorite Christmas recordings in life-like stereo! This GD-10 offers you complete stereo and mono operation *plus* portable convenience. Handsome aqua and white two-tone vinyl clad cabinet and four-speed automatic changer come preassembled—you build only the amplifier in just a few enjoyable hours. Changer has turnover diamond and sapphire stereo cartridge. Complete tone controls. Measures 15½" W x 18" D x 8¾" H. 28 lbs.

Model GD-10... \$7.00 dn., \$7.00 mo. **\$69.95**



HIGH FIDELITY AM TUNER KIT

Here is the AM counterpart of the best selling Heathkit FM-4 tuner bringing you high fidelity AM reception plus many extras. Switch selection of broad or narrow band width, flywheel tuning, edge-lighted slide-rule dial, built-in antenna, self-powered. Styled to match Heathkit FM-4.

Model AJ-20... **\$29.95**




AUTOMATIC RECORD CHANGER KIT

Jam-proof mechanism ... quick-change cartridge holder ... "muting" switch ... and "size-selector" for intermixing 7", 10" and 12" records of the same speed! Holds up to 10 records, for hours of delightful stereo or mono listening enjoyment.

Model AD-50... **\$49.95 to \$54.95** depending on cartridge.

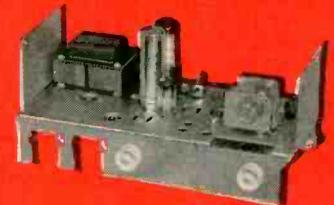Other models from **\$22.95**. Send for FREE Heathkit catalog today!



EDUCATIONAL KIT

Perfect gift for all ages ... a basic course in radio that teaches radio theory in a way you can understand. Actual experiments are performed with radio parts supplied leading in successive steps from the construction of a simple crystal radio to a genuine regenerative radio receiver. Designed as a continuation of the popular EK-1 Educational Kit—but equally valuable as a starting point in radio electronics.

Model EK-2A... 8 lbs. **\$19.95**



HAND-HELD CITIZENS BAND TRANSCEIVER

The perfect HEATHGIFT for everyone on your shopping list! No license required ... anyone can use this 2-way radio! Operates up to a mile between units ... more with regular Citizens Band stations. It's ideal for hunting, fishing, boating ... most anywhere you need 2-way communications. Features 4-transistor circuit; fixed-tuned, super-regenerative receiver and crystal-controlled transmitter. 3 lbs.

Model GW-30 (kit) ... **\$32.95** (64.95 a pair)

Model GWW-30 (wired) ... **\$50.95** (99.95 a pair)

DELUXE 2-WAY CITIZENS BAND TRANSCEIVER

This Christmas, give the best that money can buy in a Citizens Band Transceiver. The efficient superheterodyne receiver has an automatic "noise limiter" and adjustable "squelch" control, single channel "crystal" or continuous tuning. The transmitter has press-to-talk microphone and can be switched to any of the three crystal-controlled channels. Choose the "under-dash" DC mobile model or "fixed" station AC unit. 11 lbs.

Model GW-10 (kit) ... \$6.30 dn., \$6.00 mo. **\$62.95**

Model GWW-10 (wired) ... \$10.00 dn., \$9.00 mo. **\$99.95**

(specify 117 v AC or 6 or 12 v DC model)

gifts of lasting value!

"SPACE-SAVER" 3" DC OSCILLOSCOPE KIT

Almost, but not quite tiny enough for a Christmas stocking, this compact scope saves valuable work-bench space, while providing versatile features to fill a multitude of applications in medical, industrial and general service fields. Ideal as a "read-out" for computers; for wave-form observations; and for voltage, frequency and phase shift measurements. Identical vertical and horizontal DC coupled amplifier, transformer operated power supply—and many more outstanding features.

Model IO-10...14 lbs...\$8.00 dn., \$8.00 mo.....**\$79.95**

LABORATORY 5" OSCILLOSCOPE KIT

A real time-saver in audio and TV service work, where the same sweep frequencies are used over and over; the IO-30 offers two extra, switch-selected, pre-set sweep frequencies. Kit is supplied with capacitors appropriate for TV service giving preset frequencies of 30 cycles and 7875 cycles; by changing capacitor values, any two desired preset frequencies within the sweep frequency range can be made available.

Model IO-30...22 lbs...\$7.70 dn., \$7.00 mo.....**\$76.95**

2 new scopes...

just in time for Christmas!



Model IO-10

Model IO-30



PHONE AND CW TRANSMITTER KIT

Brand-new in every respect, the DX-60 combines smart styling, top-flight performance and low Heathkit cost to offer the "Amateur rig" value of the season. Ideal for General class Amateurs, the Transmitter may also be run at reduced power for novice operation. Covers 80 through 10 meters. Power input; 90-watts peak, carrier controlled phone or CW. 27 lbs.

Model DX-60...\$8.30 dn.....**\$82.95**



2, 6 & 10 METER TRANSCEIVER KITS

Make a hit with the "Hams" on your gift list by giving one of these outstanding transceivers. All are identically styled to the popular Heathkit CB-1 Citizens Band Transceiver, feature variable-tuned superregenerative receivers; 5-watt input crystal-controlled transmitters. All are supplied with mike, power cables and AC power supply.

Model HW-30... (2 meters).....**\$49.95**

Model HW-29... (6 meters) or

HW-19 (10 meter).....**\$39.95 ea.**



DELUXE VACUUM TUBE VOLTMETER KIT

Hobbyist and professional alike will prize this useful gift. This brand-new Heathkit features big, easy-to-read 6" meter with multi-color scales; high-visibility switches; greater accuracy; longer meter scales; special low voltage AC scales; broader frequency response; thumb-wheel controls and easy-access adjustments.

Model IM-10... 7 lbs.....**\$32.95**



SEND FOR
YOUR FREE
HEATHKIT®
CATALOG



You'll find the perfect gift for family or friends among the over 200 Heathkit items for hi-fi fans, amateur radio operators, students, technicians, marine enthusiasts, sports car owners and hobbyists. And many Heathkit products are now available in both wired and kit form!

ORDER DIRECT BY MAIL OR SEE YOUR HEATHKIT DEALER



ORDERING INSTRUCTIONS

Fill out the order blank below. Include charges for parcel post according to weights shown. Express orders shipped delivery charges collect. All prices F.O.B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice.

HEATH COMPANY,
Benton Harbor 20, Michigan

Please send the following HEATHKITS:

ITEM	MODEL NO.	PRICE

Ship via () Parcel Post () Express () COD () Best Way

() SEND MY FREE COPY OF YOUR COMPLETE CATALOG

Name _____

Address _____

City _____ Zone _____ State _____

Dealer and export prices slightly higher.

(Continued from page 63)

We once pulled a coil which was apparently undamaged on the outside, only to find every turn blown open on the back side!

Standard replacements are available—Fig. 2 shows a typical service-shop stock. The coils shown will replace 95% of the input coils in modern tuners. It takes a long thin soldering iron, a very long-nosed pair of tweezers and infinite patience to replace some of them, but it has to be done!

Unsound sound

In a Packard-Bell 2111-2 TV, the picture is good but sound is fuzzy on channels 7, 9 and 11. Channels 4 and 5 are normal or nearly so. I've tested the tubes in the tuner and video if without results.—T. R. W., Seattle, Wash.

I believe I'd check the tubes in the sound if and the ratio detector by substitution before I did anything else. If this doesn't help, alignment of the audio section is a must.

You can align the sound if's by using a station signal, if you have a good strong one nearby. Connect the dc

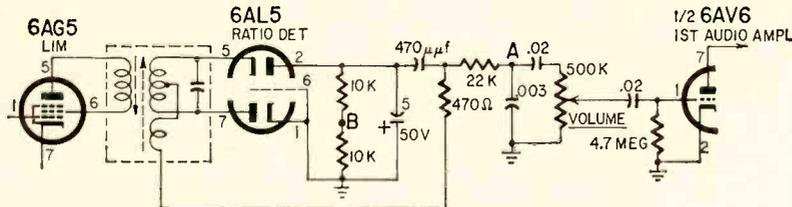


Fig. 5—Partial schematic of Packard-Bell 2111-2 audio section.

probe of a vtvm to the junction of the 22,000-ohm resistor and .02-µf capacitor between the 6AL5 and the 6AV6 first af amplifier (point A in Fig. 5). Now, tune in the best picture on the set, and set the vtvm for about a midscale reading; this should be only a few volts, and will be negative. Next, tune the sound if coil in the grid circuit of the 6AG5 for maximum. Now tune the primary of the ratio-detector transformer for maximum—you'll have to trace this one, but it's usually the bottom slug on the transformer. Tune all these for maximum reading.

Move the vtvm to the junction of the two 10,000-ohm resistors between pins 1 and 2 of the 6AL5 (point B). Adjust the secondary of the ratio-detector transformer for zero voltage at this point. You should have equal and opposite swings as the adjustment is varied about zero. In other words, if it swings 4 volts positive, it should swing 4 volts negative.

After this adjustment the sound should clear up if all parts are all right. If it is still fuzzy, replace the 5-µf electrolytic capacitor across the two 10,000-ohm resistors as this is a frequent cause of this kind of trouble. In fact, it might be a good idea to try this first, before you do the alignment. Might save a lot of time!

Metal to glass

My distributor says that I can replace the 21MP4 (metal-coned) picture tube in a Silvertone 25WG-3075 with a

glass tube, using a conversion kit. What electrical modifications would have to be made in the chassis and what type of tube would be the best replacement?—G. McK., Menasha, Wis.

Your distributor is right. Because of the ever-present shock hazard of the metal-coned tubes, it is a good idea to replace them with glass equivalents (when they need replacing). Using the conversion kit, it is not difficult to mount a glass tube in place of the metal type.

The 21YP4-A is electrically interchangeable with the 21MP4 and no modifications are required. The only difference lies in the fact that the glass tube is about 3/4 inch longer than the metal one. This may require that the yoke bracket be set back slightly and you may have to cut a small hole in the "cup" on the back (if the original tube was too close).

Horizontal roll

A Motorola TS-425 TV came into the shop for horizontal rolling. Replacing several capacitors and a resistor eliminated the rolling. It now has a

phasing ghost about a third of the way across the screen from the left side. It also has a slight jitter. I've tested all components, replaced the dual diode in the afc and all other components in the horizontal circuits. All tubes have been replaced, including the damper and high-voltage rectifier.—W. H. R., Brad-dock, Pa.

Like yourself, I would have replaced that afc diode first! This cures most of these complaints. Since it didn't, there may be something else wrong in that circuit.

The first thing to do here is run a very careful alignment of the horizontal oscillator. In this series, the horizontal hold control should have a normal range of about 30°. If it doesn't, it needs adjustment.

Ground the horizontal afc, from pin 4 of the test receptacle on the chassis (Fig. 6). Connect a 0.1-µf capacitor between 2 and 5 on this socket to short out the ringing coil. Now adjust the horizontal hold control until the picture

stands still or as near to still as you can get it—it will drift from side to side. Now leaving the controls where they are, take the capacitor jumper off the ringing coil and adjust the slug for a locked-in picture. After the picture locks in, keep on turning the slug until it falls out again. Now, turn it back and leave it halfway between the two points.

If this process does not stop the trouble, try changing those diodes again just for luck! Incidentally, these diodes are the type connected with both diodes "looking the same way" (Fig. 6). Be sure that you have the right type, and also be sure that the polarity is right! Reversing the diode could cause trouble!

No magnet

A set brought in the other day had been converted to use a 21CQP4 tube. It has a single ion-trap magnet on the neck. I cannot get the picture bright enough and it is out of position, too. Neck shadows are always had. Do you think the magnet is not strong enough, or what?—E. J. B., Hatfield, Ark.

Someone may be playing a prank on you. The 21CQP4 tube does not use an ion-trap magnet at all! This is a straight-gun type of tube, with electrostatic focusing. The surprising thing is that you got any picture on the screen with an ion-trap magnet of any strength at all on the neck. It looks as if the beam bender must be fairly weak.

Take the ion-trap magnet off and be sure that the picture-positioning magnets (the two thin metal rings with tabs) have been installed on the back cover of the yoke. Since this was a conversion job, whoever did it may not have installed them. They are necessary to get the picture placed properly on the screen with this type of tube.

Horizontal sync trouble

I am having trouble in the horizontal sync circuit of a G-E 21T14 TV. I originally had a shorted capacitor in the screen circuit of the horizontal output tube. I replaced it and the resistor, and brought the picture back in. When I put the chassis back in the cabinet and had everything connected and adjusted, I could not get the horizontal sync to lock in as it should. A large vertical black streak on the right side of the screen pulls to the left. When it moves, the picture tears up. I can just barely touch the horizontal hold. It stays locked in for 1 to 5 minutes, then tears again. —J. T. D., Babson Park, Fla.

The "large black streak" you see on

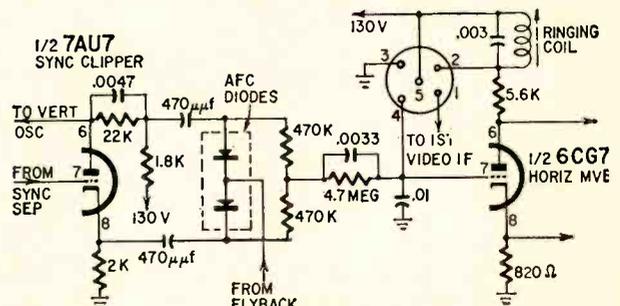


Fig. 6—Part of the horizontal sync and sweep circuits of a Motorola TS-425.

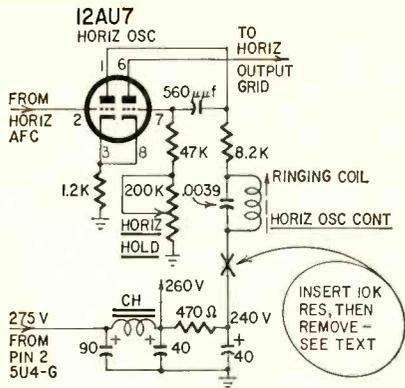


Fig. 7—470-ohm resistor in power supply may be a sleeper, a component that failed when a capacitor in the horizontal oscillator went.

the screen is obviously the horizontal blanking bar between frames. It is pulling in on you because of some trouble in the horizontal afc circuit or possibly in the oscillator itself.

This is not an uncommon trouble, but it can be annoying. I'd change the 12AT7 horizontal phase detector tube first, if you haven't already done so, then the 12AU7 horizontal oscillator. And don't get them mixed up, as this can lead to some strange and wonderful results! I know!

Next, run a complete realignment on the horizontal oscillator. Short out the ringing coil, set the hold control for a stationary picture, then open the short on the coil and adjust the slug for the most stationary picture. You'll have to add about 10,000 ohms temporarily between the ringing coil and B-plus to get the oscillator to work, as the original resistor here has a value of only 8,200 ohms.

There is one more good possibility. Check the operating voltages on the oscillator stage. When that capacitor went out, it may have burned up the 470-ohm resistor in the power supply, between the 240- and 260-volt lines. It is connected from the output of the filter choke to the 40-µf electrolytic (Fig. 7).

There is a modification on this series too. If the set has the 220,000-ohm resistor shunted across the horizontal hold control, cut it out. This will increase the horizontal hold range quite a bit.

Slow agc

I am presently working on a Capehart model 3011M TV. It does fine, except that the agc is too slow. I have to readjust it every time channels are changed. Can I change this to keyed agc?—M. J. B., Southington, Conn.

Check the 10-µf filter on the agc amplifier plate, also all resistors and capacitors in the agc network. Also check the diode clamp which is a part of the 6AV6 af amplifier. Leakage here can cause trouble.

You might reduce the time constant somewhat by using smaller agc bypasses. It would be a pretty rough job to attempt to install keyed agc in this set!

END

NOW!
one Britener
for ALL
series string
heaters



MODEL C412 VU-BRITE
110° Button Base—Series
ALL Filament Voltages
\$1.75 net

MODEL C403 VU-BRITE
Duodecal Base—Series
ALL Filament Voltages
\$1.12 net

MODEL C411 VU-BRITE
110° Button Base—Parallel
ALL Filament Voltages
\$1.49 net

MODEL C311 UNIVERSAL
110° Button Base—6.3 Volts
Series or Parallel
\$2.98 net

all available from your
Perma-Power Distributor

Perma-Power COMPANY

3106 NORTH ELSTON AVENUE • CHICAGO 18, ILLINOIS

ANOTHER
Mercury
SERVICE AID

The versatile **MULTI-PROBE** Patent Pending
DOES THE WORK OF 4 PROBES!

Can be used
with your
VTVM,
SCOPE or
SIGNAL
TRACER

Save the
cost of
4 separate
probes!

A quarter turn of the head
selects either DC,
AC/Ohms, Lo-Cap
or RF probe
positions

DC Probe

AC/Ohms Probe

RF Probe

Lo-Cap Probe

Model MP-1 \$975
MULTI-PROBE Net

Now for the first time — exclusive with MERCURY — a MULTI-PROBE that does all the work of 4 different probes. Functions: DC position . . . matches VTVM input impedance • AC/Ohms position . . . for all low frequency, low impedance, voltages and wave forms • RF position . . . a demodulator for checking RF voltages, wave forms and signals and TV/radio RF and IF stages • Lo-Capacity position . . . a must for high impedance, TV sync and radio circuits where regular probes overload the circuit.

See your electronics parts distributor

MERCURY ELECTRONICS CORP.,

77 SEARING AVENUE, MINEOLA, NEW YORK
West Coast Office: 4306 W. Victory Blvd., Burbank, Calif.

BE CAREFUL WITH IGNITRONS

By ALLAN H. LYTEL

Although they look and are rugged, ignitrons are not immune to abuse. Take care of them, and they'll work for you!

IGNITRONS are powerful gas-filled rectifiers whose cathodes are pools of mercury. They come in a variety of sizes (see photo) and can carry up to tens of thousands of amperes in various industrial applications. The ignitron is no ordinary mercury-vapor rectifier. Its secret is in the little third electrode, the ignitor, from which the tube gets its name. By applying a positive voltage to this third element, an arc which ionizes the mercury can be struck. The mercury ions aid the flow of electron current from the cathode (a pool of liquid mercury) to the anode, as long as the output current remains above a threshold level.

Since the ignitor can be pulsed to start the arc at any part of the positive alternation, the tube can supply current for a full half-cycle or only a very small portion of a cycle, as desired. It becomes an efficient current regulator as well as rectifier. In fact, in some applications, the rectifying action is ignored. Two tubes are used back to back, so that output current flows on both halves of the cycle. The combination can then be used to supply any desired amount of current, from almost zero to the maximum available in the circuit.


When the direction of current changes, the arc goes out and remains

out through the nonconducting half of the cycle. Thus the possibility of arc-back is cut down as compared with tubes that are filled with ionized gas throughout the cycle.

Fig. 1 shows the construction of a typical ignitron. Note that it has an additional anode. The reason is that if the current to the main anode drops too low, the arc goes out. With the auxiliary anode, a small current flows until the anode goes negative keeping the arc alive.

Because ignitrons are powerful, rugged tubes that can handle up to tens of thousands of amperes, there is sometimes a tendency to treat them as if they could not be damaged. They can be ruined by abuse or improper operation, and reasonable care in using them will pay off in long life and reliable performance.

A typical use is in welding control (Fig. 2). Here we see the back-to-back action, giving output on both halves of the cycle. The ignitor excitation is usually taken from the anode voltage in resistance welding equipment. A rectifier (here, a thyatron) is connected between the anode and the ignitor to prevent reverse ignitor current. Where a thyatron is used the grid of this thyatron is used to determine the welding cycle (the portion of the

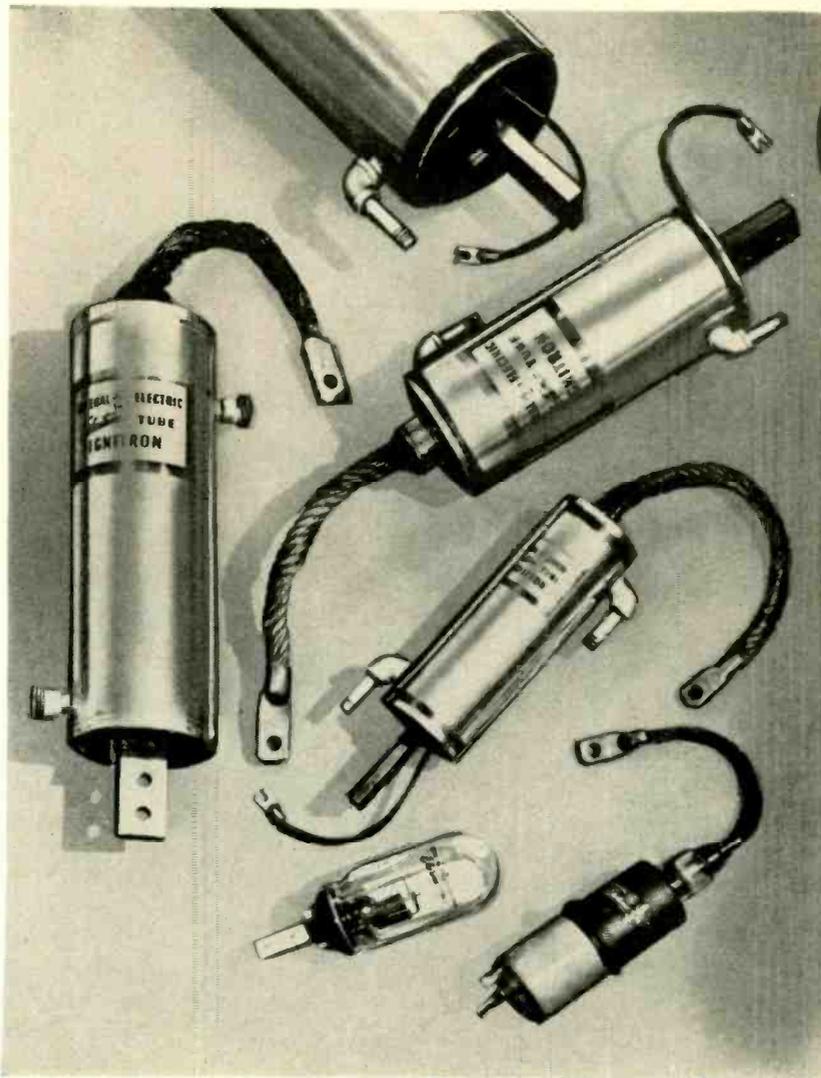

Ignitrons come in all sizes

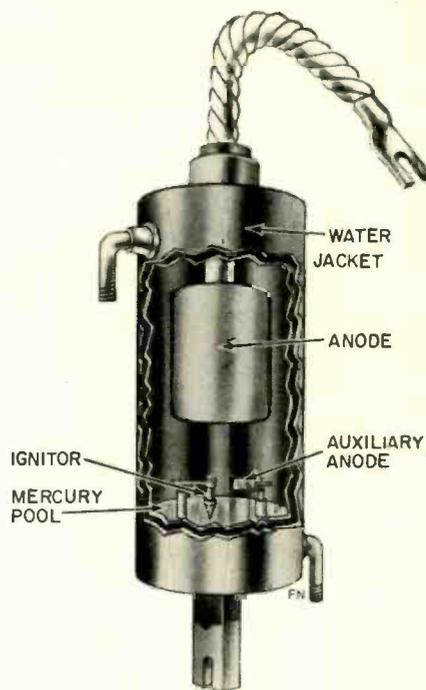


Fig. 1—An ignitron, showing all parts. Some types add other features, such as de-ionizing grids and splash baffles.

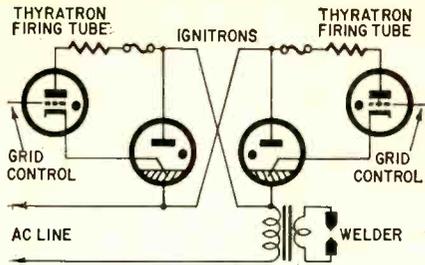


Fig. 2—Typical welder-control circuit. In this hookup, the ignitrons supply controlled ac rather than dc.

positive alternation during which the tube connects). In some installations, a relay in the rectifier circuit will determine the firing point in the welding cycle. A fuse and a resistor are used to limit the ignitor current to its maximum rated value.

Industrial rectifiers (as in Fig. 3) have the ignitor circuit separated from the anode circuit. One part of a three-phase rectifier is shown.

Storage precautions

Ignitrons require care in storage. Their stainless-steel construction protects them from physical damage during normal handling and storing. But it is necessary to take precautions to prevent the mercury in the tube from being deposited on the anode or glass seal. Any mercury droplets deposited on the glass seal or the anode can cause arc-backs which can damage the tube. For this reason ignitrons should be stored in the vertical position as shown in Fig. 4. By accident a tube may be placed on its side, causing the mercury to run from its normal position. If this happens, shake it from side to side to bring any drops of mercury to the bottom. Several tubes, depending on specific needs, may be kept on "replacement standby" to prevent operational delays. This is done by keeping their tops slightly above room temperature with a heat source such as a 100-watt lamp in a reflective enclosure (Fig. 5). Only the top of the tube is heated, removing any deposited mercury from the seal or anode.

Installation precautions

Protect the tubes from vibration and

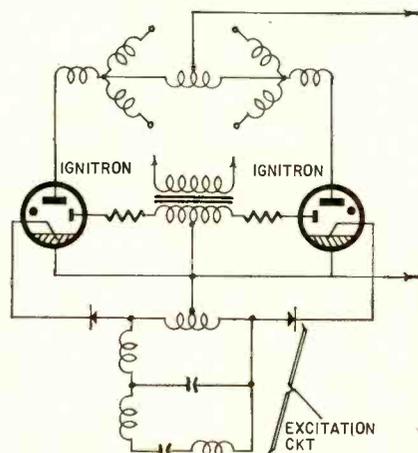


Fig. 3—Industrial rectification circuit, with auxiliary anodes and separate excitation circuit for ignitor firing.

for the Experimenter
for the Boat Owner
for the Hi-Fi Enthusiast
for the Ham
for the Retailer

PRECISION adds 6 new products

to the

PACO

kit line!



1
NEW

PACO MODEL T-61C AND MODEL T-61F SELF-SERVICE TUBE CHECKER KITS

For the enterprising retailer who wants to increase his store traffic with this extra service. 2 models: Counter (T-61C illus.) and Floor (T-61F). 24 tube sockets, 3 simple selectors. Complete instruction data cards make tube-checking a "snap".

Model T-61C (Kit) Net Price: \$ 99.95
Model T-61CW (Wired) Net Price: \$134.95
Model T-61F (Kit) Net Price: \$124.95
Model T-61FW (Wired) Net Price: \$164.95



2
NEW

PACO MODEL B-12 REGULATED POWER SUPPLY KIT

Two instruments in one! A reliable source of variable regulated DC plate voltage from 0-400 volts at 150 ma, plus bias and AC filament voltages...with an exclusive 12.6 volt AC supply! Maximum stability. Lab-quality PACE double-jewelled D'Arsonval meters.

Model B-12 (Kit) Net Price: \$69.95
Model B-12W (Wired) Net Price: \$99.95



3
NEW

PACO TK-6 TOOL KIT

For the kit-builder or experienced electronic technician, this complete set of precision-built English and American-made tools can handle any assembly job, large or small.

Includes: diagonal cutters; long-nosed pliers; 40-watt soldering iron; two screwdrivers; a pair of wire-strippers, plus see-through carrying case.

Model TK-6 Net Price: \$9.95



4
NEW

PACO MODEL G-15 GRID DIP METER KIT

Truly, a hand-held electronic "jack-of-all-trades" — VFO; Absorption Wavemeter; Signal Source; field strength indicator, plus an exclusive visual/aural "on-the-air" Modulation Indicator. A "must" for the ham or electronic technician who wants maximum quality at the lowest possible cost.

Model G-15 (Kit) Net Price: \$31.95
Model G-15W (Wired) Net Price: \$49.95



5
NEW

PACO MODEL L-1 HIGH FIDELITY SPEAKER SYSTEM SEMI-KIT

A 'bookshelf' speaker system whose sound output and small size will astound you! So efficient, it assures perfect results even with low-powered amplifiers. Response, 50-14,000 cps. Only 15 1/4" x 9 1/4" x 8 1/2". 12 lbs. Assembly-time—1 hour!

Model L-1U (Semi-kit) in unfinished walnut Net Price: \$24.95



6
NEW

PACO DF-90 TRANSISTORIZED DEPTH FINDER KIT

An absolute necessity for protection against shoals, and for finding that elusive school of fish! Range, 0 to 120 feet. Large, illuminated dial for easy readings. Operates on self-contained batteries or from ship's power source. Completely fungus and moisture-proof.

DW-90 (Kit) Net Price: \$ 84.50
DF-90W (Wired) Net Price: \$135.50

PACO "Instruments in Kit Form" are produced under the auspices of **PRECISION APPARATUS COMPANY, INC.**, world-famous manufacturer of industrial and laboratory electronic test instruments for over a quarter of a century. Write for new complete PACO Catalog, just off the press.



SEE THESE KITS AT ALL LEADING ELECTRONIC PARTS DISTRIBUTORS
PACO ELECTRONICS CO., INC.

70-71 84th Street, Glendale 27, L. I., N. Y.
Kit Division of
PRECISION APPARATUS CO., INC.,
a subsidiary of Pacotronics Inc.

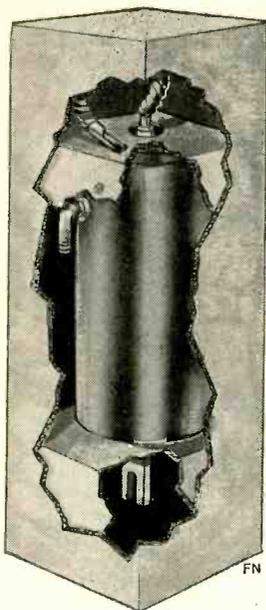


Fig. 4—How an ignitron is shipped.

shock. Although they are metal, they require care and protection against mercury splashes onto the anode or tube walls. Voltage surges should be kept off the tube as much as possible, since voltage surges may cause arcing within the tube.

Keep terminals clean and securely fastened to the mounting brackets.

Shield tubes from nearby high-frequency fields, which sometimes initiate arcs within the tube. Also, shield them from magnetic fields, which may cause the arc to form on the tube side walls. The tubes are usually sufficiently shielded by the metal panel enclosures. However, high-frequency lines and conductors carrying large currents should still be kept away from the panels.

When replacing a faulty ignitron tube in the panel be sure to check the rectifiers in the ignitor circuit. They may have caused the original failure by applying negative voltages to the ignitor.

Cooling the ignitron

Specific design-temperature limits and the heavy current flow make temperature control important. Temperature is controlled by the amount of water flowing through the water jacket. Measuring the water temperature at the outlet indicates the actual ignitron temperature. These tubes will often overheat if the water is turned off when the anode power is removed. To avoid this, the water flow should be maintained for the time indicated by the manufacturer. (It may run up to an hour for some ignitrons.)

Cooling-water temperatures and flow

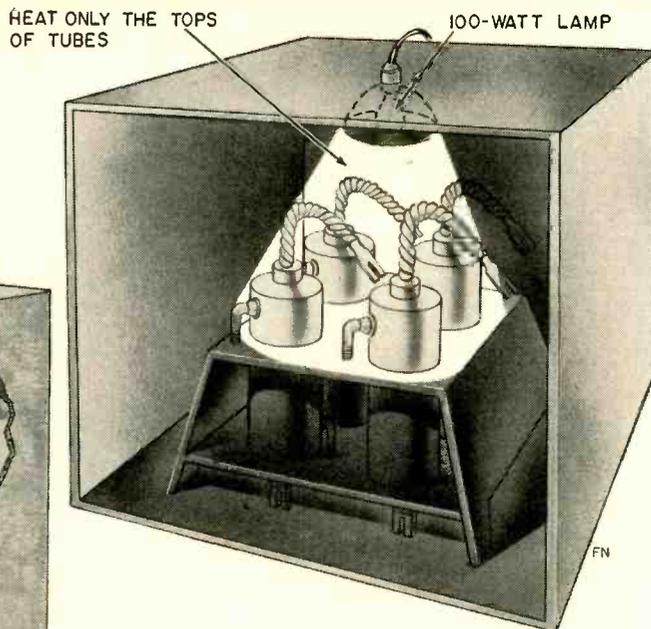


Fig. 5—Taking care of standby tubes.

rates are always specified by the manufacturer. Both minimum and maximum inlet temperatures are usually given. For normal service conditions, a better working minimum is a point approximately midway between the rated minimum and maximum values. If an ignitron is operated for long periods near the rated minimum temperature, certain load conditions can cause high-voltage surges in the tube. These surges will in turn cause breakdowns in the associated equipment unless it is adequately protected. Outlet water temperature depends upon the peak inverse voltage, which is the voltage in the nonconducting direction.

Servicing

Ignitron failures or improper and sporadic tube operation can usually be traced to one of three basic conditions:

- ▶ Inadequate flow of cooling water
- ▶ Failure of the rectifiers which block ignitor current flow
- ▶ Operating the tubes outside of their published ratings

These cause other conditions that lead to tube failure or irregular operation, as shown in the chart.

Ignitor wetting is a special problem in these tubes. In proper or normal operation the mercury in an ignitron is uncontaminated. The mercury does not wet the ignitor. The ignitor is composed of a number of crystals touching the mercury but not wetted by it. When a voltage is impressed between the ignitor and the mercury, a cathode spot occurs at the juncture between the crystal and the mercury due to high voltage gradients. As long as this cathode spot forms on the mercury, the ignitor is unchanged and should last for years.

If the mercury becomes impure it attaches itself to the ignitor. Under this condition, the crystal-to-mercury junctures become short-circuited. This results in sporadic tube operation or com-

plete failure of the ignitor to initiate the arc.

Inadequate water flow will cause tube overheating. As stated, the water flow should be continued after the tube anode power is removed. This cools the tube before shutdown. Excessive tube temperatures will result from improper cooling (see chart). This can result in holes burned through the tube walls or in ignitron wetting.

If the water jacket becomes clogged, it will have to be cleaned. This is a critical process, in which powerful acids are used. A person qualified to work with acids, preferably a chemist, should handle this job. Follow manufacturer's directions exactly. An excellent set of instructions can be found in General Electric's handbook, *Instructions for Handling, Servicing, Installing G-E Ignitrons*. This booklet is the source material for most of the information in this article, as well as the illustrations, and can be obtained from the Electronic Components Div., Power Tube Dept., General Electric Co., Schenectady, N.Y.

Tube ratings are given by the manufacturer and are the basis for operating the tube properly. Ratings are maximum and are not to be exceeded if proper tube operation is expected.

Blocking rectifiers are important. Their failure can destroy the ignitor and the tube. Note in the chart that the rectifier failure can cause lack of firing control or even complete breakdown.

Testing the ignitron

Fig. 6 shows the method of testing for ignitor wetting. First remove the ignitron from the socket after all power has been disconnected from the equipment. Support the tube vertically on a table and connect an ohmmeter between ignitor and cathode. The cathode connec-

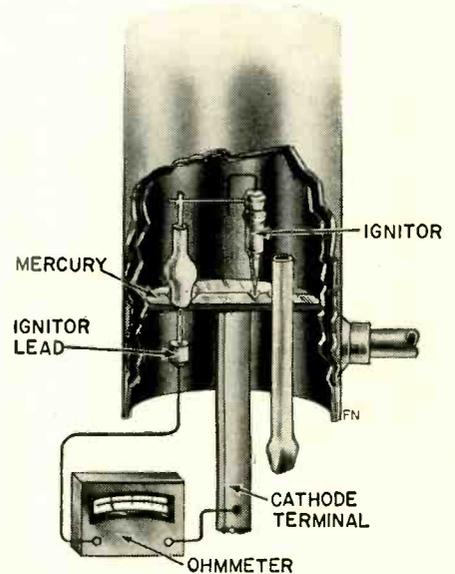


Fig. 6—Checking for ignitor wetting.

tion can be made to any portion of the tube jacket or to the cathode terminal. Tilt the tube slowly back and forth to change the depth of immersion of the ignitor in the mercury.

The ignitor resistance varies approximately uniformly on a good tube until



Replace improper equipment with the only
microphone
designed specifically **THE TURNER 350C**
for citizen's band

This reasonably priced, mobile-type ceramic microphone is the perfect replacement for the many improper, tape recorder-type microphones now being used on CB equipment. Has DPST switch wired for relay operation with easily reversible terminals to allow modifications (if necessary); wiring diagram enclosed with each microphone; hanger button and standard dash bracket for mobile rig mounting; and an 11" retracted (five foot extended), plastic-jacketed, coiled cord. Response: 80-7,000 cps. Output: -54 db. List price: \$16.80 complete. See your Turner Distributor, listed below, he has the 350C in stock.

THE TURNER MICROPHONE COMPANY
934 17th St. N.E.
Cedar Rapids, Iowa

ARKANSAS

Little Rock: Southern Radio Supply
Texarkana: Lavender Radio & T.V. Sup.

CALIFORNIA

Downey: Net Electronics
Hemet: Gil Severns
Hollywood: Pacific Radio Exchange
Los Angeles: Radio Product Sales
The Sound Foyer

Oakland: Elmar Electronics
Sacramento: Selectronics
San Francisco: Market Radio Sound Dept.

DISTRICT OF COLUMBIA

Washington: Electronic Wholesalers

FLORIDA

Miami: East Coast Radio & TV
Tampa: Kinkade Radio Supply

GEORGIA

Atlanta: Specialty Distributing

ILLINOIS

Chicago: Nationwide Radio
Irving Joseph, Inc.
La Salle: Klaus Radio & Electric
La Salle Electronics

Peoria: Klaus Radio & Electric

INDIANA

Anderson: Seybert's Radio Sup.
Bloomington: Stansifer Radio Co.
Evansville: Hutch and Son, Inc.
Ohio Valley Sound

Fort Wayne: Pembleton Laboratories
Indianapolis: Brown Distributing Co.
Graham Electronic Sup.
Van Sickle Radio Supply

Kokomo: George's Electronic Sup.
Michigan City: Tri-State Electrical Sup.
Portland: Buck's Hi-Fi
Richmond: Fox Electronics Company
Terre Haute: Midwest Supply Company

IOWA

Cedar Rapids: Iowa Radio Supply

Des Moines: Bob & Jacks, Incorporated
Radio Trade Supply Co.

KANSAS

Topeka: Acme Radio Supply

KENTUCKY

Lexington: Radio Equipment Co.
Louisville: Arcby Electronics
P. I. Burks Company
Peerless Electronic Equipment Co.

LOUISIANA

Baton Rouge: Davis Electronics Sup.
New Iberia: Brooks Electronics

MASSACHUSETTS

Boston: A. W. Mayer Company
O'Donnell Electronic Supply
Radio Shack Corp.

Lawrence: Alco Electronics

MICHIGAN

Ann Arbor: Purchase Radio Supply
Detroit: High Fidelity Workshop
Lansing: Offenhauer Company

MINNESOTA

Minneapolis: Lew Bonn
National Electronics Co.
Harry Starks, Inc.
Schaak Electronics

MISSOURI

St. Louis: Radonics

NEW JERSEY

Berlin: Midstate Radio Supply
Jersey City: Nidisco-Jersey City
Mountainside: Federated Purchaser

NEW YORK

Albany: Greylock Electronics Supply
Buffalo: Radio Equipment Corp.
Farmingdale, L.I.: Gem Electronics
Forest Hills: Beam Electronics
Hicksville: Gem Electronics
Kingston: Greylock Electronics
Long Island City: Spera Electronics
Mt. Vernon: Davis Electronics

New York: Harvey Radio Company
Acme Electronics

Poughkeepsie: Greylock Electronics
Rochester: Rochester Radio Supply

NORTH CAROLINA

Greensboro: Johannesen Electric Company
Raleigh: Southeastern Radio Supply Co.
Winston-Salem: Womack Company

OHIO

Cleveland: Pioneer Electronic Sup.
Columbus: Whitehead Radio Company
Mansfield: Wholesaling, Inc.
Toledo: Lifetime Electronics

OKLAHOMA

Oklahoma City: Johnson Wholesale

OREGON

Portland: United Radio Supply

PENNSYLVANIA

Homestead: M. Leff Radio Parts
Lancaster: George D. Barbey Co.
Lebanon: George D. Barbey Co.
Philadelphia: Radio Electric Service Co.
Pottstown: George D. Barbey Co.
Reading: George D. Barbey Co.
Wilkes-Barre: General Radio & Electronics
York: Radio Electric Service Co.

RHODE ISLAND

Providence: Del Padre Supply Co.

SOUTH CAROLINA

Columbia: Dixie Radio Supply Company

SOUTH DAKOTA

Watertown: Burghardt Radio Supply

TEXAS

Houston: Sound Equipment Inc.

VIRGINIA

Arlington: Rucker Electronic Products
Falls Church: The Television Workshop
Richmond: Banner Electronics, Inc.

WISCONSIN

Chippewa Falls: Bushland Radio Spec.
Eau Claire: Bushland Radio Spec.

THE TURNER MICROPHONE COMPANY

934 17th St. N.E., Cedar Rapids, Iowa

Please send me further information on The Turner 350C citizen's band microphone.

NAME _____

STREET OR RFD _____

CITY _____


ZONE _____

STATE _____

Send this coupon to the nearest Turner distributor listed above or write The Turner Microphone Company for the name of a distributor in your area.

THE TURNER MICROPHONE COMPANY

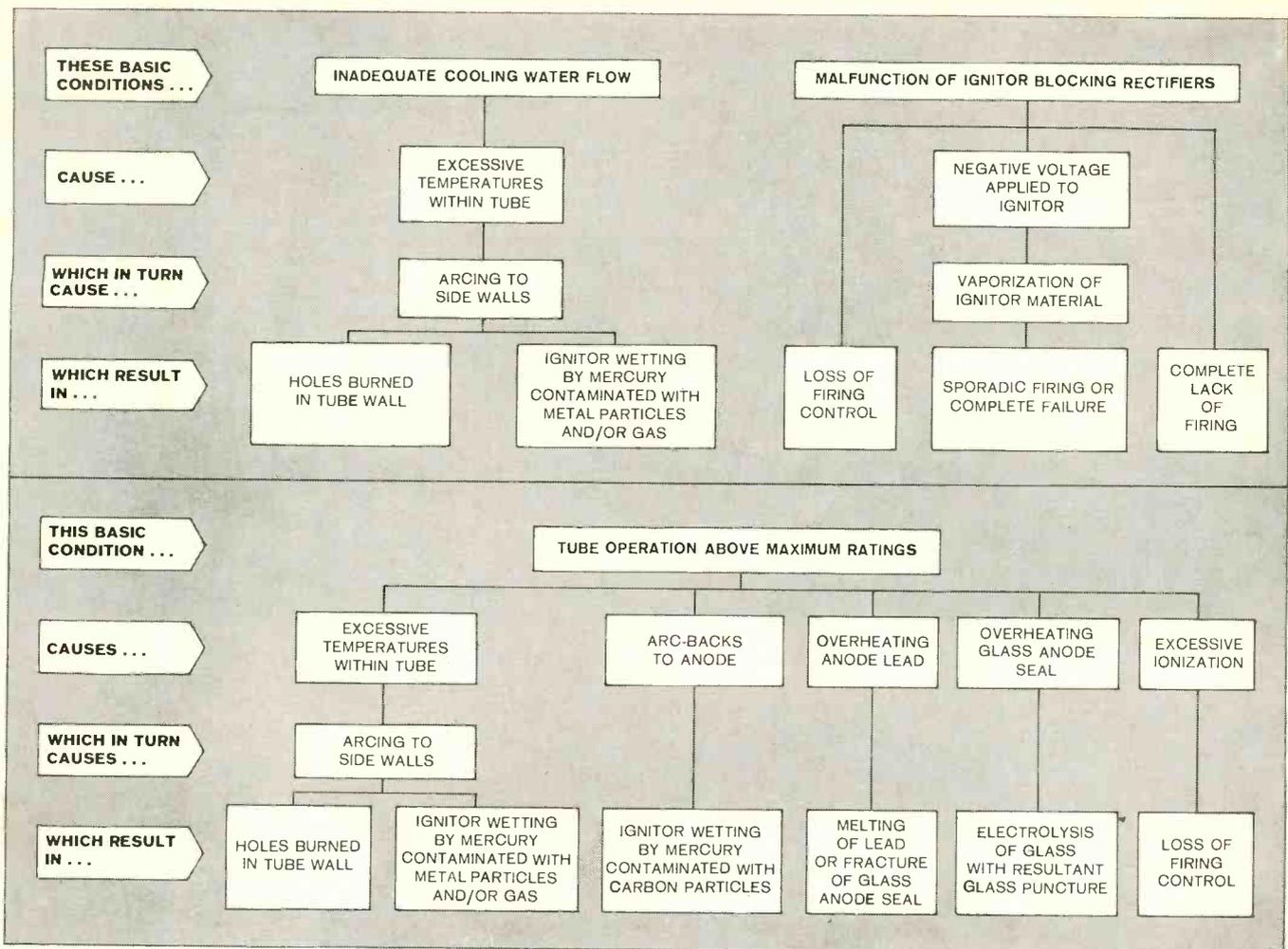934 17th St. N.E. . . . Cedar Rapids, Iowa



Causes and Symptoms of Ignitron Troubles

either the ignitor is completely out of the mercury or the mercury completely covers the lead. If the resistance remains constant through a considerable arc as the tube is tilted, a portion of the ignitor is wetted.

The technician would be well advised to test several tubes, including new ones, to gain experience and ability to detect ignitor wetting.

If the tests show that the ignitor is

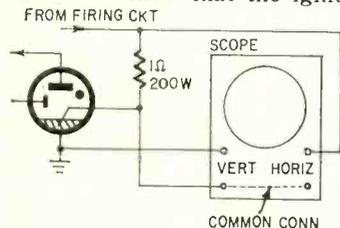


Fig. 7—How equipment is connected for checking ignitor firing characteristics.

wet, the tube may still operate satisfactorily for a time, however, but sporadic operation or complete tube failure will result eventually.

Wet ignitors indicate that the tubes have been operated at too high temperatures. Determine and correct the cause.

Ignitor characteristics can be determined with an oscilloscope as shown in Fig. 7. Connect a 1-ohm resistor with a power rating of 200 watts (noninductive) in series with the ignitor lead as indicated. One vertical (V) input is tied to ground; the other vertical lead is to

the ignitor. This same point is connected to one of the horizontal (H) inputs. Voltage across the 1-ohm load is fed to the other horizontal input.

A straight line at an angle with the horizontal appears on the scope. The angle depends upon the dynamic resistance of the particular ignitor being measured and on the relative gain of the vertical and horizontal amplifiers.

Since there is considerable variation in the voltage and current values from cycle to cycle, watch for the maximum values displayed over about 1 minute and record these maximum deflections. The data should be taken under both light-load and full-load conditions.

After taking a number of readings,

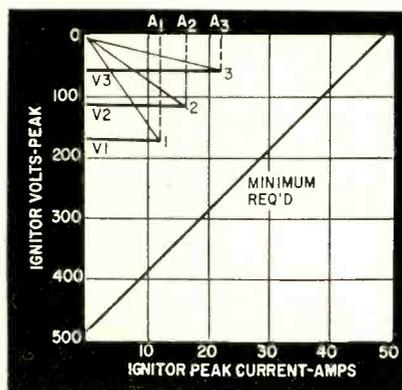


Fig. 8—Ignitor firing characteristics are plotted on a sheet like this one.

the peak voltage and current can be established. If the resistor is exactly 1 ohm, the voltage across it is equal to the current. V1 is maximum voltage; A3 is maximum current. The points 1 (V1, A1) and 3 (V3, A3) are both plotted on the ignitor volt-ampere requirement sheet. All points plotted for a good ignitor, at both low and high loads within the tube rating, will lie to the left of (and above) the line marked **minimum** required in Fig. 8. If the ignitor passes this test and the test for mercury wetting of ignitors, it may be considered satisfactory. The minimum required ignitor characteristics are given by the manufacturer for each tube.

To test for gas, leave the tube out of service for a week. Hook it up with cathode and anode in series with the secondary of an oil-burner or other transformer with about a 12-kv output. Insert two 50,000-ohm, 100-watt resistors in circuit to limit current, and put a 2-watt neon lamp across one of them. Use a variable autotransformer between primary and line and advance the control till the lamp lights steadily. Then check the time till the lamp goes out (clean-up time). If this is less than 30 seconds, the tube is probably good. If a little more, it can be used for continuous, but not intermittent service. If the clean-up time is several minutes, the tube is unusable, and should be returned to the manufacturer if still within warranty. END

**Courses in Radio and
Electronic Fundamentals –
TV Servicing – Color TV –
Electronics for
Automation –
Transistors**



SEND FOR THIS **FREE**
64 PAGE BOOK TODAY!

Check Home Study!

RCA Institutes Home Study School offers a complete program of integrated courses for beginners and advanced students . . . all designed to prepare you for a rewarding career in the rapidly expanding world of electronics. Practical work with your very first lesson. And you get top recognition as an RCA Institutes graduate!

CANADIANS — take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to:
RCA Victor Company, Ltd., 5581
Royalmount Ave., Montreal 9, Que.

SEE OTHER SIDE

CUT OUT AND MAIL THIS POSTAGE-FREE CARD TODAY!

RCA INSTITUTES, INC., DEPT. RE-DO

350 W. Fourth St. • New York 14, N. Y.

Please rush me your FREE illustrated 64-page book describing your electronic training programs. No obligation. No salesman will call.

Home Study Book

Resident School Book

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Korean Vets: Enter Discharge Date _____

HOME STUDY SCHOOL

RESIDENT SCHOOL



RCA TRAINING CAN BE THE SMARTEST INVESTMENT YOU EVER MAKE

With RCA Institutes Home Study training you set your own pace in keeping with your own ability, finances and time. You get prime quality equipment as a regular part of the course . . . and you never have to take apart one piece to build another. Perhaps most important, RCA's liberal Pay-As-You-Learn Plan is the most economical home study method *because you pay only for lessons as you order them . . . one study group at a time!* If you drop out at *any* time, for *any* reason, you do not owe RCA one penny! No other obligations! No monthly installment payments! Licensed by New York State Education Department.

START YOUR CAREER IN ELECTRONICS NOW AT RCA INSTITUTES in Los Angeles-New York City

CHOOSE FROM THIS LIST . . .

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad, with Algebra, Physics or Science	Day 2 1/4 yrs. Eve. 6 3/4 yrs.
B	TV and General Electronics (V-7)	2 yrs. High School, with Algebra, Physics or Science	Day 1 1/2 yrs. Eve. 4 1/2 yrs.
C	Radio & TV Servicing (V-3)	2 yrs. High School	Day 9 mos. Eve. 2 1/4 yrs.
D	Transistors*	V-3 or equivalent	Eve. 3 mos.
E	Electronic Drafting (V-9)*	2 yrs. High School, with Algebra, Physics or Science	Eve. 3 yrs.
F	Color TV	V-3 or equivalent	Day 3 mos. Eve. 3 mos.
G	Audio-Hi Fidelity*	V-3 or equivalent	Eve. 3 mos.
H	Video Tape*	V-3 or equivalent	Eve. 3 mos.
I	Technical Writing (V-10)	V-3 or equivalent	Eve. 3-18 mos.
J	Radio Telegraph Operating (V-5)*	2 yrs. High School, with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs.
K	Radio Code (V-4)*	8th Grade	Eve. as desired
L	Preparatory Math & Physics (P-0)	1 yr. High School	Day 3 mos.
M	Preparatory Mathematics (P-0A)	1 yr. High School	Eve. 3 mos.

*Courses to be added to Los Angeles Curriculum

SEE OTHER SIDE

First Class
U. S. Postage
PAID
Permit No. 10662
New York, N. Y.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in U. S.

Postage will be paid by—

RCA INSTITUTES, INC., DEPT. RE-DO

350 West Fourth Street

New York 14, N. Y.



RCA Institutes is one of the largest technical institutes in the United States devoted exclusively to electronics. Co-educational Day and Evening classes. Free Placement Service. Applications now being accepted.



SEND FOR THIS FREE ILLUSTRATED BOOK TODAY. Fill in the other side of the postage-free card and check Resident School.

RCA INSTITUTES, INC. A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N.Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

the

REMO NEMO

THE purpose of the Remo-Nemo is to provide for remote control of remote (or nemo) pickups of program material for radio broadcasting. The device, of course, is not limited to just this application.

I have observed in numerous instances, that radio-station plans for remote pickups of local events and entertainment are discarded when the cost of engineering personnel overtime and transportation are estimated, in addition to telephone-line charges. This is especially true when the intended pickup would be a daily feature and particularly so if the station is operating under the terms of a union contract.

The Remo-Nemo is intended primarily for single-channel program use although, with proper input impedance matching, additional microphones could be used. There would, of course, be no individual control over each microphone. However, the majority of the average radio station's local remote pickups are the type that can be handled satisfactorily with a single microphone. It is always preferable to assign a radio technician to the type of program pickup requiring elaborate engineering setups.

Radio broadcasting stations have resorted to different means in an attempt to overcome this situation. Standard remote equipment has been

By HAROLD REED

installed at the remote points and set in advance, making it necessary for an announcer to throw only one switch to feed a program to the station control room. In some cases, when the announcements are made at the studios, the individual or one of a group of those comprising the program may place the equipment in operation.

The disadvantages in the above methods are many. In the first place, most union contracts would prohibit this procedure: all station equipment must be operated by a technician of the station. Expensive remote apparatus is tied up at each pickup point, regardless of the simplicity of the program. This costly equipment is also subject to thievery and vandalism. It requires either 117-volt ac power or a supply consisting of an expensive group of batteries.

The Remo-Nemo can be built into a small metal box. It can be self-powered with self-contained, inexpensive batter-

Designed for handling remote pickups from the studio, this little unit has many applications in various types of distant monitoring or control

ies, and with no external controls to be manipulated at the remote point. The unit can be installed in some location not easily accessible to the public. Only two external connections are required: microphone input and output to the telephone company program line. These connections may be made inside the box so they cannot be tampered with. The box can be locked if desired.

Very little maintenance is required to keep this device in operation and the cost of each unit is such that a station may keep several available for

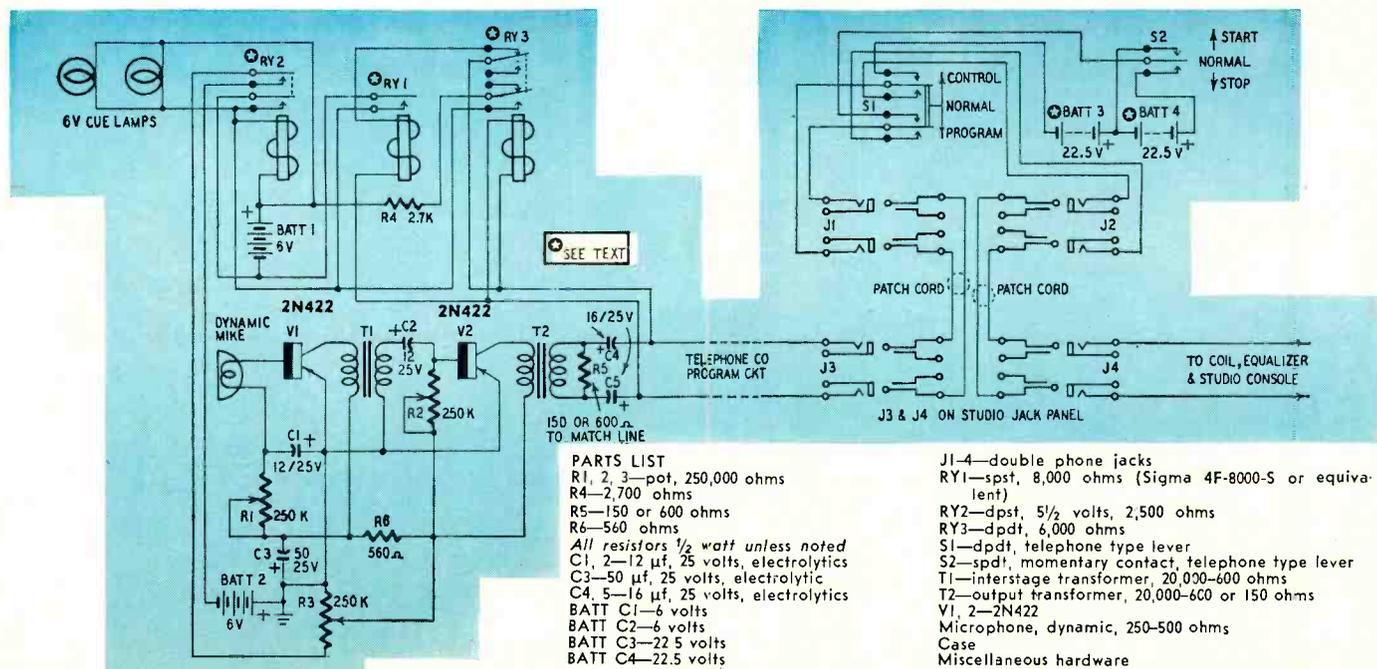


Fig. 1—Circuit of remote pickup and studio control unit.

field work. In fact, in some instances, the cost in overtime paid for several remote pickups may very well be as great as the cost of one of these units.

Circuit design


The Remo-Nemo is designed around the 2N422, a p-n-p junction transistor. The 2N422 should provide a power gain of 30 db per stage. The diagram shows the circuit of a two-stage common-emitter amplifier. A dynamic microphone of 250-500-ohm impedance is connected directly to the input, between base and emitter. Microphones of other impedances may be used with a proper impedance-matching transformer. The secondary of transformer T2 (Fig. 1) is connected to the program line. This output winding may be 150 or 600 ohms as required.

Variable controls R1, R2 and R3 are adjusted to obtain the greatest possible gain, with acceptable values of noise and distortion levels. These variable controls used in the experimental model may be replaced with fixed resistances after optimum values have been determined. The best values for these resistances in tests made with the other components as used in the experimental model were: R1—100,000 ohms, R2—250,000 ohms and R3—200,000 ohms. Because of the common battery supply a filter composed of R6 and C3 is necessary to prevent the amplifier from breaking into oscillation.


The CK722 can be used, and were in fact the original complement of the equipment. With these, the battery voltage (BATT 2) is 15. Different CK722 transistors were tried. With these, gains of between 25 and 31 db per stage were possible. In the two-stage amplifier (see diag.), an overall gain of 55 db was realized with acceptable values of noise and distortion levels. These measurements were made with a collector voltage of -9, collector current of 2 ma, and base current 50 μ a. The input fed to the first stage for these tests was a 400-cycle signal from a General Radio Co. audio oscillator, attenuated to a level of -65 db. Noise level in the amplifier, below the signal input level, was -40 db. In the experimental unit these tests were made without special care in shielding and grounding and I believe that lower noise levels may be obtained.

An oscilloscope connected at the amplifier's output gave evidence of a good sine wave under the above conditions of operation. Attempts to obtain greater gain, by increasing or decreasing the operating values of the circuit, resulted in flattening the sine-wave peaks. A scope also indicates objectionable distortion when the level of the 400-cycle audio input signal is increased. Frequency response is shown by the graph of Fig. 2.

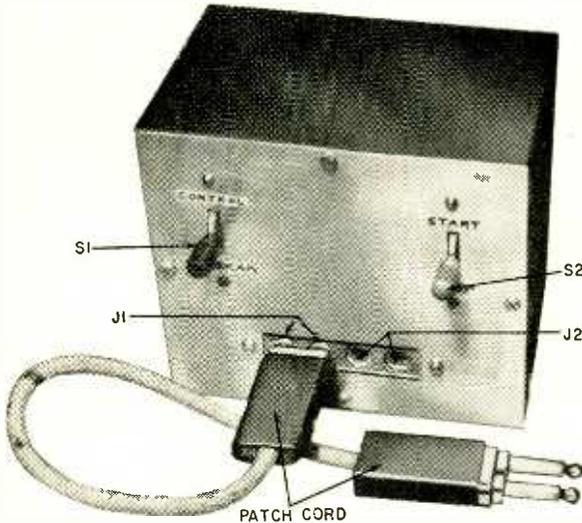
An amplifier used for this purpose should be capable of providing approximately 0-db level to the program line. A two- or three-stage amplifier may be required, depending upon the output of the microphone used. The photographs show two separate stages. For



Completed control unit for the studio.

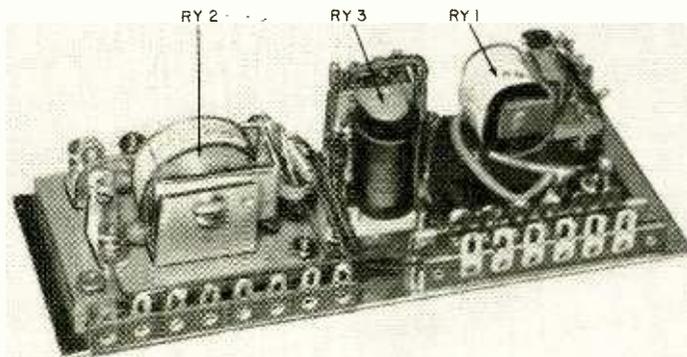

Relay strip controls remote operation.

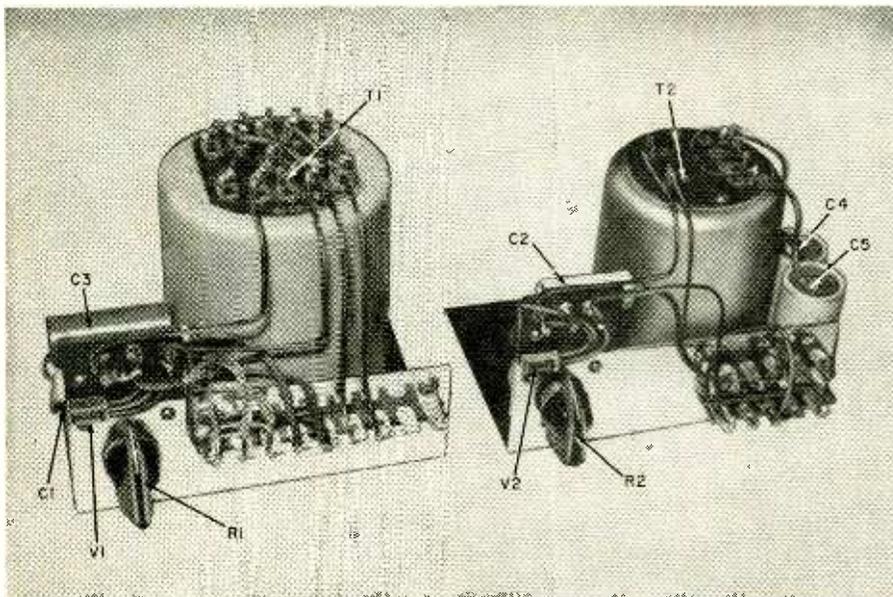

Two-stage transistor amplifier uses broadcast line bridging coils.

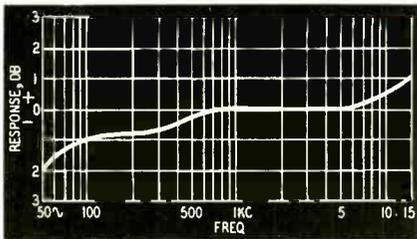


Fig. 2—Response curve of amplifier.

experimental reasons each stage was constructed individually so it could be tested separately and so that additional stages could be added to the first stage as required. As you can see, no attempt was made at miniaturization. Components on hand were used and the transistors are dwarfed to the extreme by the relatively large size of the transformers which are the usual high-quality bridging to 600-ohm coils normally used in radio broadcasting station service. The equipment can be miniaturized by employing minute transformers, such as the UTC A-25, the UTC Ouncer O-9 or the Microtran Co.'s transistor transformers designed for audio-frequency transistor circuitry. In this manner the remote unit would be reduced to a very small package.

The Remo-Nemo requires only one telephone-line pair which is used for program transmission, control circuit and cue line. This line is the standard, unequalized type circuit supplied by the phone company. Most radio broadcasting stations use this type of line, providing their own equalization.

Three inexpensive relays are used in the control-cue system. During program time the line must be free of battery potentials and appreciable loading by apparatus not associated with program transmission. Two of the three relays are continuously across the line but, because of their high coil resistance with respect to the low impedance of the line, they have a negligible effect on the program circuit. Fig. 1 also gives the wiring diagram of the relays and a photograph shows the relay strip. Only RY2 is in operation for the full time that the program is in progress. The relays in this experimental model were those that happened to be on hand. Other relay combinations operating at other voltages may, of course, be utilized.

Using the unit

When it is time for the program to begin, the operator at the studio control point throws S1 (Fig. 1) to CONTROL. S2 is momentarily placed in the START position. S1 is then pushed to PROGRAM.

When the operator places S2 in the START position, the low dc potential of BATT 3 is placed across the line and operates RY1 at the remote point (see Fig. 1). When RY1 closes, voltage from BATT 1 is applied to RY2. When RY2 closes, it completes the circuit between BATT 1 and the coil of RY2, holding the relay closed after S2 is released and RY1 opens. RY2 also closes the circuit of the battery supply to the


Now Completely SELF-CONTAINED

For Testing & Rejuvenating

BLACK AND WHITE and **COLOR** including **110° TUBES**

NEW CRT 440



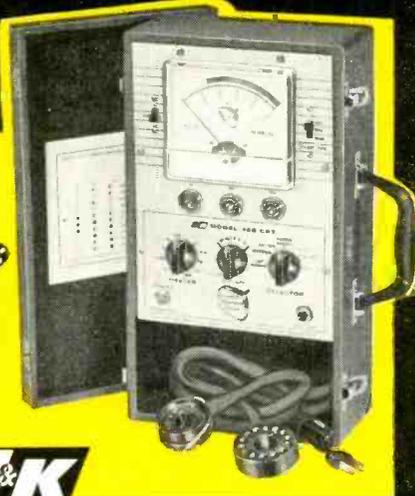

TESTS AND REJUVENATES

all black & white and color picture tubes at correct filament voltage from 1 to 12 V.

TESTS AND REJUVENATES

110° tubes with 2.34, 2.68, 6.3 and 8.4 volt filaments.

TESTS AND REJUVENATES

color picture tubes. Checks each color gun separately same as black & white tubes.

*Used by Thousands of Professional Servicemen
 MAKES NEW PICTURE TUBE SALES EASIER*

Gives you more value than ever—all-in-one. Quickly checks and corrects most TV picture tube troubles in a few minutes right in the home without removing tube from set. Gives new useful life to weak or inoperative tubes. Checks leakage. Restores emission and brightness. Repairs inter-element shorts and open circuits. Life test checks gas content and predicts remaining useful life of picture tube. Completely self-contained in leatherette-covered carrying case. Net, \$74⁹⁵

ACCESSORIES for USE ONLY with FORMER B&K Models 400 and 350 CRT



Model C40 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates TV color picture tubes and 6.3 volt 1 0° picture tubes. Net, \$9.95


Model CR48 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95



See your B&K Distributor
 or Send now for Bulletin AP16-E

B & K MANUFACTURING CO.

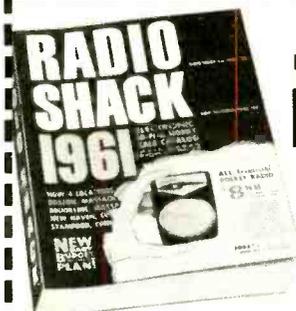1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
 Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
 Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.



JUST CLIP THIS AD
 Fill in your name and address. Receive giant new

FREE RADIO SHACK
 Electronics CATALOG
 plus every new issue for full year

See America's finest values in Hi-Fi, Stereo, Ham Radio, Kits and Parts! Over 100,000 electronic marvels for today's enjoyment, exciting gifts, all-year pleasure. Low as \$2 down, pay balance after Christmas.




See values like this!
 Transistor Pocket Radio only \$8.88



Mail this ad to
RADIO SHACK, Dept. 60M10 • 730 Commonwealth Ave., Boston 17, Mass.

YES! Without obligation mail free catalogs for full year.

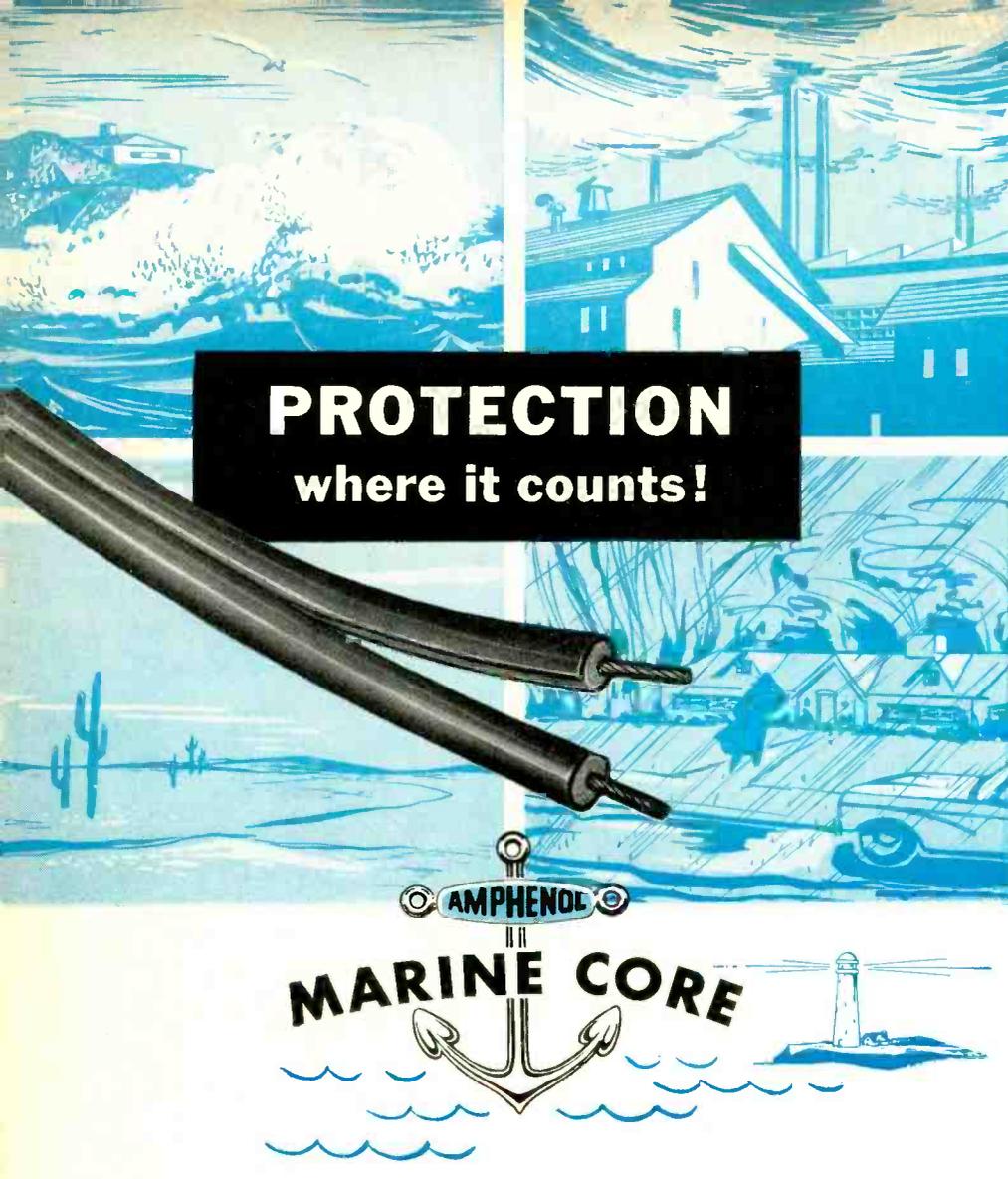Name _____ Address _____
 City _____ Zone _____ State _____



**PROTECTION
where it counts!**



AMPHENOL
MARINE CORE

TWIN LEAD

Are you in a problem area? AMPHENOL's new Marine Core Twin Lead is winning new friends daily by solving reception problems all over America!

In salt-laden air along the coasts, in ultra fringe areas, in cities with heavy industrial contamination and in locations with heavy precipitation, Marine Core gives protection where it counts, consistently bringing in good pictures.

If you have reception problems try Marine Core—find out for yourself how really good it is!

Marine Core is available in 50, 75, 100 and 500 foot coils and in 1000 foot reels. Order by part number 214-103 from your Authorized AMPHENOL Distributor.



AMPHENOL

DISTRIBUTOR DIVISION
BROADVIEW, ILLINOIS

Amphenol-Borg Electronics Corporation

www.americanradiohistory.com

transistor amplifier and lights the "on the air" cue. Two lamps are connected in parallel to guard against failure.

At the end of the program S1 is thrown to CONTROL and S2 is momentarily placed in the STOP position. This places BATT 3 and 4 in series across the line. This higher voltage closes RY3 which places a resistance across the coil of RY2, causing it to open, thus removing BATT 1, opening of BATT 2 supply and extinguishing the cue lights. RY1 will not operate on this higher voltage as its coil is in series with a pair of contacts on RY3 which open when the higher potential is applied.

The starting and stopping control potentials of BATT 3 and BATT 4 must not be applied while the line is patched to the input of the control room program console. This is prevented by S1, which makes it impossible to apply dc control voltages while the line is terminated to the input to the line coil or console.

BATT 3 and 4 may be single batteries with the correct voltage taps. This reduces the number of batteries required for the complete system to two. A single 45-volt B-battery was used for BATT 3 and 4, using the 22.5-volt tap as BATT 3. RY1, with a coil of 8,000-ohm resistance, operated on the 22.5 volts, while relay RY3, with a coil of 6,000 ohms, pulled in when the 45 volts were applied across the line. The required battery control voltage will vary according to the coil resistance of the relays and the relay adjustments as well as the resistance of the telephone company's program line, which is dependent on its length. Using higher battery voltages and variable controls average potentials suitable for all encountered local line lengths may be arrived at.

The low-resistance winding of the transistor amplifier output transformer is isolated from the program line, as far as dc control voltage is concerned, by two 16- μ f capacitors. I found that these capacitors had negligible effect on the frequency characteristics of the line. In fact, frequency measurements made with and without the capacitors in the circuit gave the same results throughout the range from 50 to 10,000 cycles with the exception of a 1-db drop at 50 cycles with the capacitors in the line.

The control equipment at the studio may be mounted in a small box, including input and output jacks, or arranged on a standard relay rack panel. The installation should be made near the jack panel on which the remote lines are terminated so that patching may be effected between any line, the control equipment and the program console input. A photograph shows this control unit for the studio control room.


As the device is simple and straightforward, working with low dc voltages and low current drain and using no tubes to contribute to failure, it should operate for long periods of time with little maintenance. END




1



2

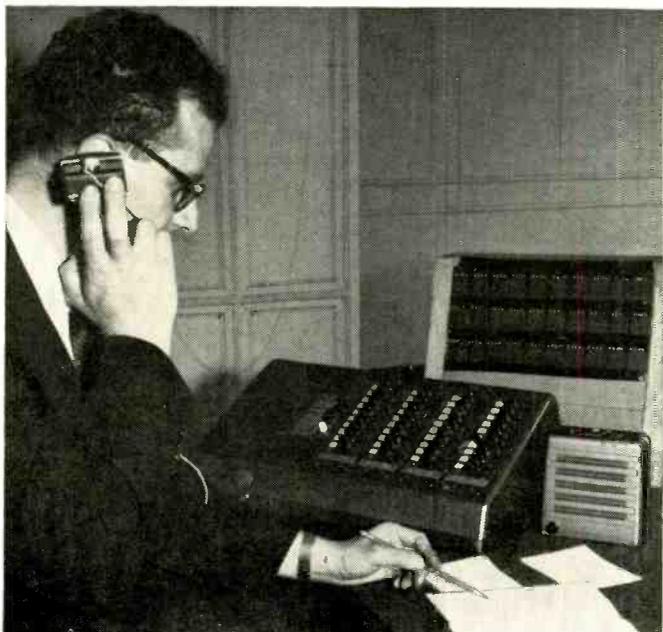

3

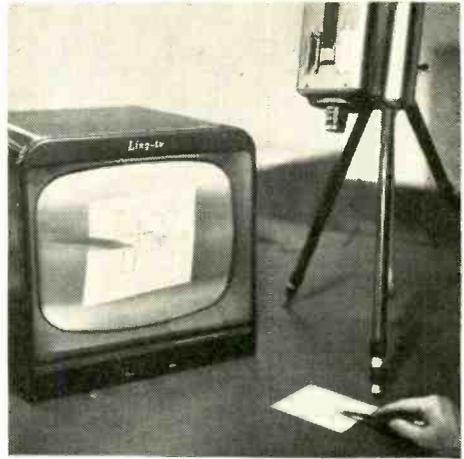

4

ELECTRONIC classroom

AN electronic teaching and testing laboratory using teaching machines and designed to take the guesswork out of teaching has been developed and installed by the New York Institute of Technology. It uses a combination of electronic intercommunication, closed-circuit TV, record players, tape recorders and telemetry devices to supplement and supplant standard teaching aids.

In the class, each student receives the lesson to be learned in small steps. Necessary diagrams are on preprinted cards. The student also has a programmed workbook and a special stylus for answering examination questions. The earpiece and miniaturized transmitter he uses are his private property. This portion of the course can also be recorded as shown in Photo 1 or be on tape, TV film, etc.

After going over the lesson material the student is tested for an understanding of the content and then for application of the theory and problem solution. He indicates his test answers with an answer stylus that simultaneously perforates a permanent examination record card; surrounds the perforated mark with a color indicating the correctness of his choice; registers his score on an indicator at the teacher's desk; and lights a lamp on his own desk to indicate right or wrong. If the student has picked the wrong answer he is directed to alternate data in a reference workbook or is connected to an equivalent source of data.

A student having trouble can contact the instructor through an intercommunication system (Photo 2). Also, the instructor can speak to a student if his telemetered data shows such a step to be necessary. The telemetry indicator appears at the far right in Photo 3 and records the number of correct answers for each student. When asking a question the student uses a mike that has a miniature acoustic chamber which eliminates the need for booths and insures privacy. The mike doubles as a receiver when the instructor speaks to the student.

The instructor can answer a student's question by referring to the diagram the student is using or by using other material transmitted to the student from a TV camera at the instructor's desk (see Photo 4). The teacher can also call on a central TV studio to televise a TV film or other visual material or for an answer from another teacher.

The student follows this instruction on a TV monitor at his desk. If desirable, the instructor can switch a number of students into the circuit to hold a joint discussion.

By following a carefully programmed set of directions the student continues the steps he has taken in the electronics classroom to allow optimum conditions for efficient learning.

END

NEW at the NEW YORK Hi-Fi SHOW

The recent High Fidelity Music Show saw new developments in tuners, phonographs and pickups, amplifiers and speakers.



The upside-down record player operating. Empire's Gale Guterman is varying the stylus angle by a very simple means.

THE most spectacular sight at the High Fidelity Music Show held in New York City early in September was a record player operating upside down in one of the demonstration rooms. The Empire arm, which was doing the playing, operates on a principle used by few other arms. It is balanced perfectly, then pressure is applied with a spring to obtain the correct tracking force.

The Empire record player on which it was used is a three-speed type *without speed-changing mechanism*. It is belt-driven. The motor, mounted at one corner of the case, swings on a hinge so that a spring maintains belt tension. The shaft, like that of many record changers, is stepped at the end (Fig. 1). To change speed, one simply removes the protective case from the motor and moves the belt up or down to the step that gives the correct speed. Thus speed is changed *manually*, not mechanically.

The three stepped shaft sections are crowned slightly, and a knurled adjustment screw that cants the motor a little causes the belt to ride up or down a small amount. This slows the turntable down or speeds it up as the belt moves

to a point of greater or smaller shaft diameter, giving a very fine speed correction.

Another record player—exhibited by Rek-O-Kut—had an automatic shutoff guaranteed not to affect tracking. ESL (Electrosonic Laboratories) also showed a new improvement in pickup arms—an elliptical ring under the arm support that made it possible to adjust exactly the amount of overhang.

A German company, Korting, demonstrated a tape recorder with *reverbation*. Two small heads picked up the signal after the tape had come from the recording head and re-recorded it along with the original signal before

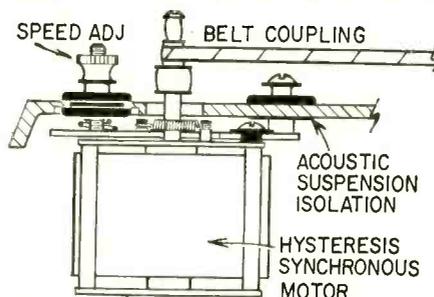


Fig. 1—Mechanism of new Empire record player.

the tape reached the playback head. An echo effect similar to the most extreme heard on some popular vocal records was easily achieved.

Last year's speaker favorites still led the field. The notable feature this year was the rise in electrostatic speakers. The Quad speaker from England received considerable attention, as did the new KLH speaker, designed by Arthur Janszen. This giant (nearly 6 feet high and 2 feet wide) is, like the Quad, a pure electrostatic all-frequency job, using from 30 to 75 watts per speaker. They are normally sold in pairs, for stereo systems, at a price of \$1,030 per pair.

Another electrostatic, sold by Cosmos Industries, resembles vaguely a pair of wings mounted about 6 inches in front of the cabinet that holds the bass speaker. The woofer operates from the



The Marantz 9A, showing bias meter.


low end of the spectrum to 600 cycles, and the electrostatic units take over from there to beyond audibility.

A growing tendency toward bias indicators was noted. Used for some time on the Marantz they appeared on two others this year. Bogen showed an amplifier that was in effect a whole music distribution system. Two input selector switches are used instead of the usual one. Thus each channel of the stereo amplifier can be used for a separate unit—channel 1 could be tuned to TV sound and channel 2 to FM for example. A set of illuminated indicators shows exactly what is being piped into each channel at all times. Four switches on the output control local and remote speakers, so that a stereo program may be reproduced on local or remote, or both, or two separate programs can be played on the desired speakers. Thus it is possible to feed FM to a speaker in an upstairs room and at the same time play 45's for a playroom in the basement. Speaker switching is shown in Fig. 2.

The increasing strength of FM was shown by a number of FM kits. One of these was by H. H. Scott, a newcomer in the kit field. Another, the Dynatuner, was offered by Dynaco and is that company's first kit outside the audio amplifier field.

Another new component was the reverb unit, now popular in packaged audio. These were offered by Fisher and Sherwood.

The contest between live players and recorded music—often a feature of audio demonstrations—appeared at this show, this time with a slightly new motive. The Fine Arts Quartet (Everest Records and Concertape artists) played alternately and simultaneously with a pair of Dynakit amplifiers and AR-3 speakers. In the words of the sponsors—Acoustic Research and Dynaco—this was done, not to show again that recording can be indistinguishable from a live program, but to “demonstrate that stereo high fidelity can be a transparent medium for re-creating a musical program rather than a means for creating a ‘new’ sound.” Some special efforts were necessary to prove the point—for example, studio reverb was eliminated by recording outdoors, as seen in one of the photos. END

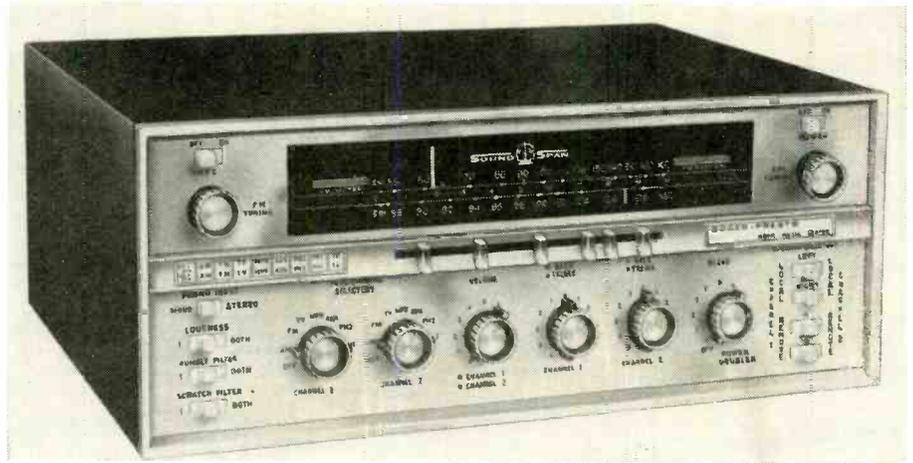

The Bogen RP-40. Unit consists of AM-FM stereo tuner, stereo preamp and dual power amplifiers. The amplifier system is also available without the tuner.

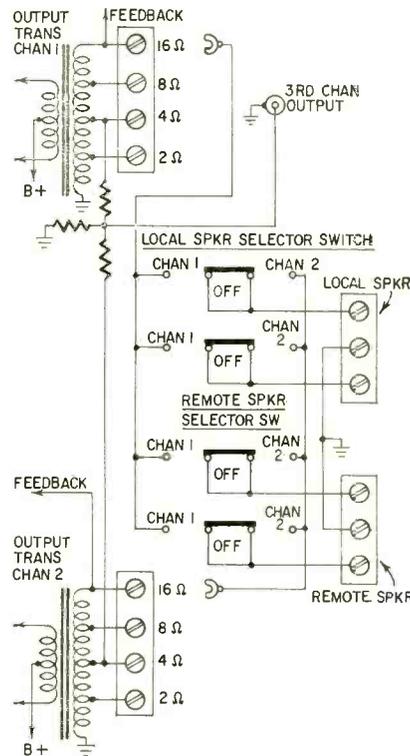


Fig. 2—Output circuitry of Bogen RP-40 home music center.

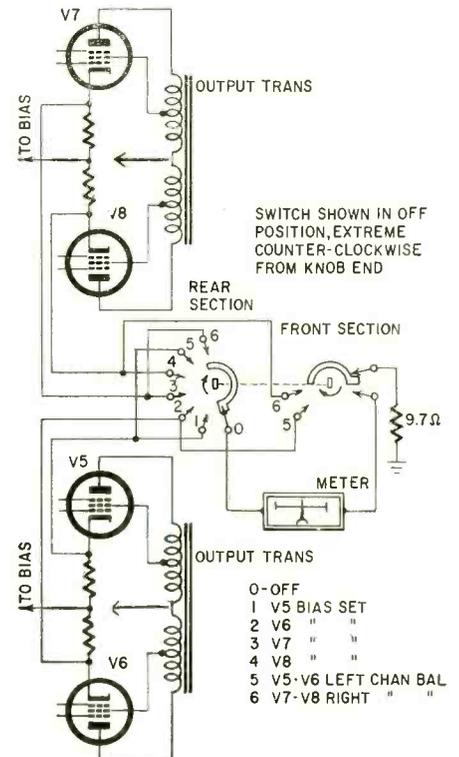


Fig. 3—Bias and balance metering in Acersound 120. In first 4 positions, meter is connected between each cathode and ground in turn. In positions 5 and 6 it is between the cathodes in each pair and shows balance by zero indication.



Recording sessions for the Dynaco-Acoustic Research project were held outdoors to reduce reverberations to zero.



The Fine Arts Quartet playing in cooperation with their own recording, as reproduced through the speakers in the rear.



SUPERIOR'S NEW MODEL TW-11

STANDARD PROFESSIONAL

TUBE TESTER

★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminars, Proximity tube types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE

SEPARATE SCALE FOR LOW-CURRENT TUBES: Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

Model TW-11—Tube Tester
Total Price\$47.50
Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a handsome portable saddle-stitched Texon Case. Only\$47⁵⁰



SUPERIOR'S NEW MODEL 83

C. R. T. TESTER

TESTS AND REJUVENATES ALL PICTURE TUBES

ALL BLACK AND WHITE TUBES

From 50 degree to 110 degree types
—from 8" to 30" types.

ALL COLOR TUBES

Test ALL picture tubes—in the carton—out of the carton—in the set!

● Model 83 is not simply a rehased black and white C.R.T. Tester with a color adapter added. Model 83 employs a new improved circuit designed specifically to test the older type black and white tubes, the newer type black and white tubes and all color picture tubes.

● Model 83 provides separate filament operating voltages for the older 6.3 types and the newer 8.4 types.

● Model 83 employs a 4" air-damped meter with quality and calibrated scales.

● Model 83 properly tests the red, green and blue sections of color tubes individually—for each section of a color tube contains its own filament, plate, grid and cathode.

● Model 83 will detect tubes which are apparently good but require rejuvenation. Such tubes will provide a picture seemingly good but lacking in proper definition, contrast and focus. To test for such malfunction, you simply press the rej. switch of Model 83. If the tube is weakening, the meter reading will indicate the condition.

● Rejuvenation of picture tubes is not simply a matter of applying a high voltage to the filament. Such voltages improperly applied can strip the cathode of the oxide coating essential for proper emission. The Model 83 applies a selective low voltage uniformly to assure increased life with no danger of cathode damage.

Model 83—C.R.T. Tube Tester
Total Price\$38.50
Terms: \$8.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

Model 83 comes housed in handsome portable Saddle Stitched Texon case—complete with sockets for all black and white tubes and all color tubes. Only\$38⁵⁰

TRANSISTOR RADIO TESTER and DYNAMIC TRANSISTOR TESTER

THE MODEL 88 . . . A NEW COMBINATION



Model 88 — Transistor Radio Tester and Dynamic Transistor Tester. Total Price . . . \$38.50
— Terms: \$8.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

The Model 88 is perhaps as important a development as was the invention of the transistor itself, for during the past 5 years, millions of transistor radios and other transistor operated devices have been imported and produced in this country with no adequate provision for servicing this ever increasing output.

The Model 88 was designed specifically to test all transistors, transistor radios, transistor recorders, and other transistor devices under dynamic conditions.

AS A TRANSISTOR TESTER

The Model 88 will test all transistors including NPN and PNP, silicon, germanium and the new gallium arsenide types, without referring to characteristic data sheets. The time-saving advantage of this technique is self evident. A further benefit of this service is that it will enable you to test new transistors as they are released! The Model 88 will measure the two most important transistor characteristics needed for transistor servicing, leakage and gain (beta).

AS A TRANSISTOR RADIO TESTER

The Model 88 provides a new simplified rapid procedure — a technique developed specifically for transistor radios and other transistor devices.

An R.F. Signal source, modulated by an audio tone is injected into the transistor receiver from the antenna, through the R.F. stage, past the mixer into the I.F. Amplifier and detector stages and on to the audio amplifier. This injected signal is then followed and traced through the receiver by means of a built-in High Gain Transistorized Signal Tracer until the cause of trouble whether it be a transistor, some other component or even a break in the printed circuit is located and pin-pointed.

The Model 88 provides a new simplified rapid procedure — a technique developed specifically for transistor radios and other transistor devices. An R.F. Signal source, modulated by an audio tone is injected into the transistor receiver from the antenna, through the R.F. stage, past the mixer into the I.F. Amplifier and detector stages and on to the audio amplifier. This injected signal is then followed and traced through the receiver by means of a built-in High Gain Transistorized Signal Tracer until the cause of trouble whether it be a transistor, some other component or even a break in the printed circuit is located and pin-pointed.

Model 88 comes housed in a handsome portable case. Complete with a set of Clip-On Cables for Transistor Testing, an R.F. Diode Probe for R.F. and I.F. tracing; an Audio Probe for Amplifier Tracing and a Signal Injector Cable. Complete—nothing else to buy! Only.....

\$38⁵⁰

EXAMINE BEFORE YOU BUY!
USE APPROVAL FORM ON NEXT PAGE



Model TV-50A—Genometer. Total price—\$47.50—Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary!

GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV
R. F. SIGNAL GENERATOR: The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.
VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peak wave audio signal.
BAR GENERATOR: The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.
MARKER GENERATOR: The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency).

THE MODEL TV-50A comes absolutely complete with shielded leads and operating instructions.

\$47⁵⁰
NET

CROSS HATCH GENERATOR: The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV) Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

SUPERIOR'S
NEW MODEL 77



Model 77—VACUUM TUBE VOLTMETER
 ... Total Price \$42.50—Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary!

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V.T.V.M. made by any other manufacturer at any price

- ✓ Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only \$42.50.
- ✓ Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- ✓ Model 77 uses new improved SICO printed circuitry.
- ✓ Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.
- ✓ AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.
- ✓ AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.
- ✓ AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.
- ✓ Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench—use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only.....
- ✓ Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibility of damage or value changes of delicate components.
- ✓ Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- ✓ Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

SPECIFICATIONS

• DC VOLTS—0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance. • AC VOLTS (RMS)—0 to 3/15/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak)—0 to 8/40/200/400/800/2,000 volts. • ELECTRONIC OHMMETER—0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms • DECIBELS—10 db to +18 db, +10 db to +38 db +30 db to +58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • ZERO CENTER METER—For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

\$42⁵⁰
NET

SHIPPED ON APPROVAL

NO MONEY WITH ORDER — NO C. O. D.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-834 3849 Tenth Ave., New York 34, N.Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligations.

- Model TW-11 . . . Total Price \$47.50 \$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 83 . . . Total Price \$38.50 \$8.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model 88 . . . Total Price \$38.50 \$8.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model TV-50A . . . Total Price \$47.50 \$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 77 . . . Total Price \$42.50 \$12.50 within 10 days. Balance \$6.00 monthly for 5 months.

Name.....

Address.....

City.....Zone.....State.....

All prices net, F.O.B., N. Y. C.
 Export Division: Rocke International Corp.
 13 East 40th Street, New York 16, N. Y.

SMALL RADIO USES AN ORIGINAL TRANSISTOR AMPLIFIER

By ANTHONY P. CIARDI

THIS transistor circuit will not be found in any transistor handbook but, for simplicity, results, and unexplored possibilities, it is hard to beat. It closely follows direct-coupling techniques used with vacuum tubes.

Designed for headphone use and powered by a 1.5-volt penlight cell, it is the utmost in economy and its volume is excellent for such a small array of parts and low battery voltage. While I did not attempt to miniaturize the unit, the few parts can be assembled into a very compact amplifier.

As I have been a direct-coupling enthusiast for many years, using tube amplifiers, I was determined to try my luck with transistors. However, I soon discovered that transistors do not follow tube techniques, except in a general way.


As the first step in building an experimental transistor radio receiver, using a direct-coupled amplifier, I reviewed present direct-coupling techniques and discovered that all existing circuits had their own particular shortcomings. There were multiple battery arrangements, use of complementary transistors, use of similar transistors in low-gain circuits. But, none had the simplicity, gain and exact configuration I desired and finally developed. My goal was a single-battery power supply at a low voltage, and two common-emitter stages to deliver the greatest voltage and power gain.

Fig. 1 shows the circuit I started with. It was attractive because large input signals could be handled before peak clipping set in and it has a voltage gain of 50 with a 1.5-volt battery. Values for R_b and R_L are selected to suit individual transistors, but in the final circuit a single potentiometer takes their place. This permits the use of any low-power transistor and gives the best compromise between voltage gain, noise and minimum distortion.

To my circuit of Fig. 1, I added another stage, just like the first, which is powered by the same battery. The final version (see Fig. 2) was the result.


The two fixed resistors R_b and R_L in Fig. 1 are replaced by a 500,000-ohm potentiometer (R, Fig. 2) which in effect becomes a split resistor. Approximately half of R is used to supply V1's base bias and the other half for V1's output load. The variable feature sets the values required for the proper operating points of the transistor. Potentiometer R must be large enough so the operating position of its arm will fall toward a center setting, giving a large-enough range to provide adequate biasing plus output load resistance.

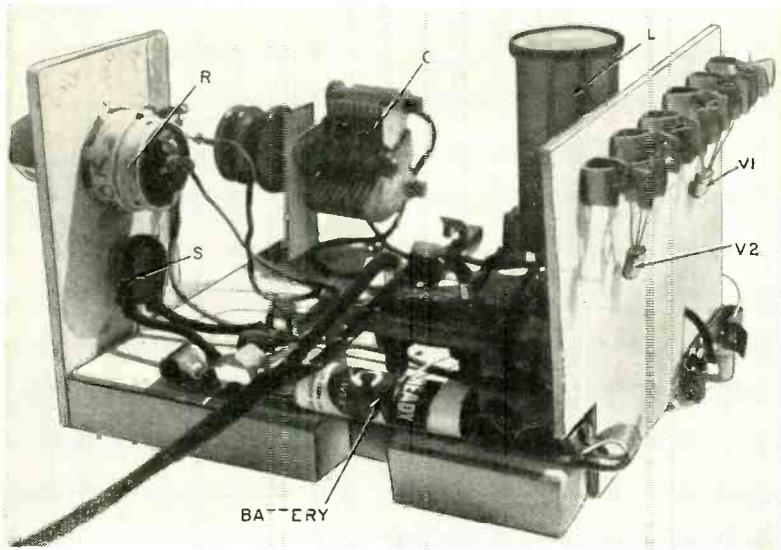The R_L section of R is the output load resistance for V1 and the R_b section is the base-biasing portion. For V2 the R_L section of V1 acts as the base-biasing resistor while the output load is a pair of headphones, output



One view of transistor unit. Note that transistors are fastened to FahstocK clips for easy mounting.

Top view of completed receiver.

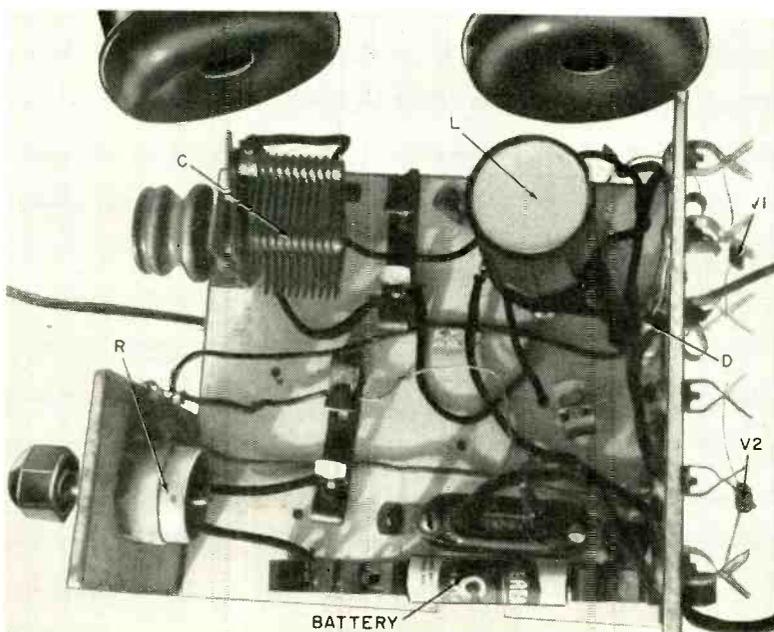

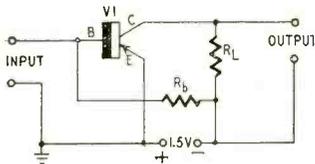


Fig. 1—This single-stage circuit was the starting point.


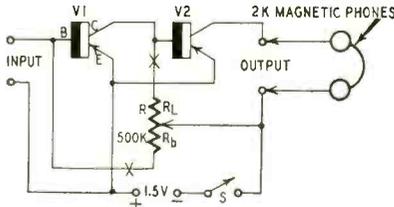


Fig. 2—Another stage, V2, has been added, and resistors R_L and R_b have been replaced by potentiometer R.

transformer or other suitable device. Thus the R_L portion of R is common to both transistors and is both the output-load resistor of one and at the same time the base-biasing resistor of the other. This follows vacuum-tube procedure as the interstage coupling resistor is common to both output and input circuits.

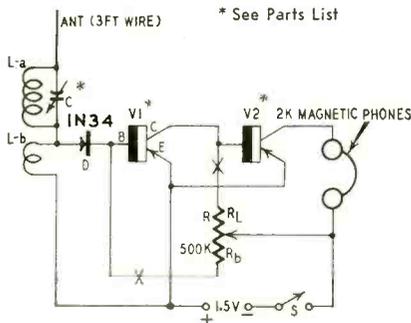A crystal diode detector, variable capacitor, antenna coil and antenna were attached to the amplifier's input



R—pot, 500,000 ohms, linear
 C—variable capacitor, 100 or 140 μf
 D—IN34 or equivalent
 L—broadcast coil set, tuned to 190-550 meters (ICA 1473 or equivalent)
 S—sps
 V1, V2—any inexpensive p-n-p audio transistors, CK722, 2N107, 2N238
 Headphones
 Battery, 1.5-volt penlight cell
 Chassis
 Knobs
 Miscellaneous hardware


Fig. 3—The detector circuit has been added and a simple headphone radio is the result.

as in Fig. 3, to make a simple but usable radio receiver. I use a short antenna—a longer one will be better in weak-signal areas. Of course, the output from a phono cartridge, crystal microphone or other high-impedance high-output source can be fed to the amplifier's input.

Just one word of caution: 1,000-ohm $\frac{1}{2}$ -watt resistors should be inserted at points X of Figs. 2 and 3 to prevent the transistors from being damaged by excess current.

I am pleased with my results and the layout of my breadboard setup is shown in the photos. I'm sure you'll like it too. END

Lowest Priced Tube Tester with the HICKOK Gm Circuit

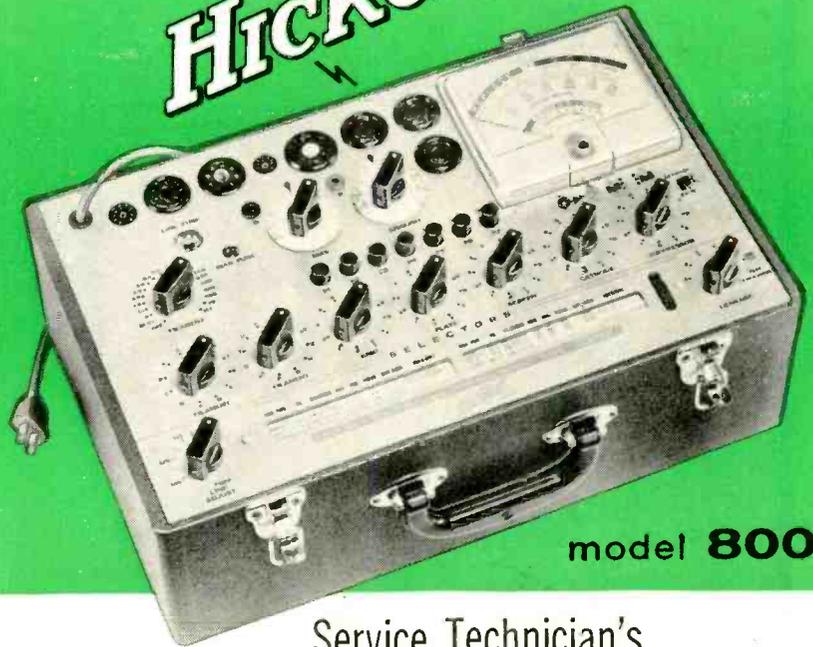

model 800

Service Technician's Portable Tube Tester, Transistor and Diode Checker

- Built-in roll chart contains test data on latest tubes, including NUOVISTORS
- Inter-element leakage and shorts read directly on the meter
- New filament continuity test speeds checking series-string tubes
- Cathode reserve measurement provided
- Only HICKOK offers roll chart subscription service

See Your Distributor, Ask for a Demonstration!
\$169.50 net

The Hickok Electrical Instrument Co.

10531 DUPONT AVENUE • CLEVELAND 8, OHIO

Over 3000 Sold in 3 Months! Not One Returned To Date!

JUMBO PAKS!

RADIO-TV PARTS BY THE POUND 500-1000 pcs. per pound

16 TONS of mfr's Over-runs

COMPLETE SATISFACTION—MONEY BACK GUARANTEE

- ONE POUND Precision ResistorsWorth \$100, NOW
- ONE POUND Disc CondensersWorth \$50, NOW
- ONE POUND Ceramic CondensersWorth \$85, NOW
- ONE POUND Discs & CeramicsWorth \$75, NOW
- ONE POUND Discs, Ceramics, Precisions.....Worth \$70, NOW

\$3⁰⁰ per pound

BUY 4 PAKS for \$11.00

clip out & mail

FREE GIANT BARGAIN CATALOG WRITE FOR YOURS!

HOW TO ORDER: Include check or M.O. with sufficient postage; excess returned. C.O.D. orders, 25% down; rated, net 30 days. INCLUDE POSTAL ZONE in address.

LEKTRON

131 Everett Ave. CHELSEA 50, MASS.

T V QUIZ

By **BOB ELDRIDGE**

HERE are a few practical questions to test your powers of deduction. Each of the faults described has occurred in actual operation, and enough information is given to let you make an accurate diagnosis.

Voltage measurements have been taken with a vtvm.

For cases 1 through 4 refer to Fig. 1, which shows the sync phase inverter, phase detector and horizontal oscillator stages of an orthodox TV set.

Case 1

There is no raster. Pulling the 6AL5 causes the raster to appear, but the 6AL5 checks OK. A scope check at pin 7 of the 6AL5 shows high amplitude spikes at this point instead of the normal sawtooth waveform. *What is the fault?*

Case 2

There is no raster. If the 6AL5 is pulled, there is still no raster. A voltage check on the 6SN7-GT reveals the following:

Pin Volts	
1	— 100
2	— 100
3	— 25
4	— 4
5	— 150
6	— 25

These voltages are the same whether the 6AL5 is in or not. The 6SN7-GT checks normal. *What is it?*

Case 3

There is no raster. If the 6AL5 is pulled, there is still no raster. A voltage check on the 6SN7-GT reveals the following:

Pin Volts	
1	— 0
2	— 240
3	— 11
4	— 150
5	— 70
6	— 11

The voltages are the same whether the 6AL5 is in or not. The 6SN7-GT checks OK. *What is it?*

Case 4

There is no raster. A measurement at the grid of the 6BQ6-GT shows -25 volts, but a scope check at the same point shows the frequency of oscillation to be about 5,000 cycles. The 6AL5 is pulled and left out—no change. The ringing coil is shorted with a jumper wire—no change. The 6SN7-GT checks OK. Voltages at the 6SN7-GT socket are all normal. Capacitors C61 and C64 are checked and found OK. If R90 (15,000 ohms) is shorted out, the raster appears, with a white overdrive line on it. *What is it?*

(For the next three cases, refer to Fig. 2.)

Case 5

There is no raster. High voltage at

the second-anode cavity of the picture tube is normal. The following voltages are measured at the picture-tube socket, with the picture tube connected.

Pin Volts

2	— 0
10	— 450
11	— 100, brightness control at "min"
	90, brightness control at "max"

The socket is removed from the picture tube and each voltage checks the same as before. It is noted that the voltage on pin 11 varies with movement of the contrast control. *What is it?*

Case 6

Age action is too much delayed. Tuner and if strip have zero bias even with a medium strong signal. It is noticed that, although the alignment has been checked and found normal, there is poor resolution of fine detail in the picture. A check of voltages on the 6CS6 shows:

Pin Volts

1	— 110 (normal is 130)
2/7	— 145 (normal)
6	— 300 (normal)

Resistor R28 (180,000 ohms is checked and found OK. *What is it?*

Case 7

There is a dim raster at "max" position of brightness control. At all other positions the screen is black. High voltage at the second-anode cavity of the picture tube is normal. The following voltages are measured at the picture tube socket connector:

Pin Volts

2	— 0
10	— 450
11	— 130, brightness control at "min"
	40, brightness control at "max"

The connector socket is removed from the picture tube, and the voltage on pin 11 is now found to be:

Pin 11	— 130 volts at "min" of brightness control
	0 volts at "max" of brightness control

The picture tube is checked and found to be normal. *What is it?* **END**

(Answers are on the opposite page. The honor system applies!)

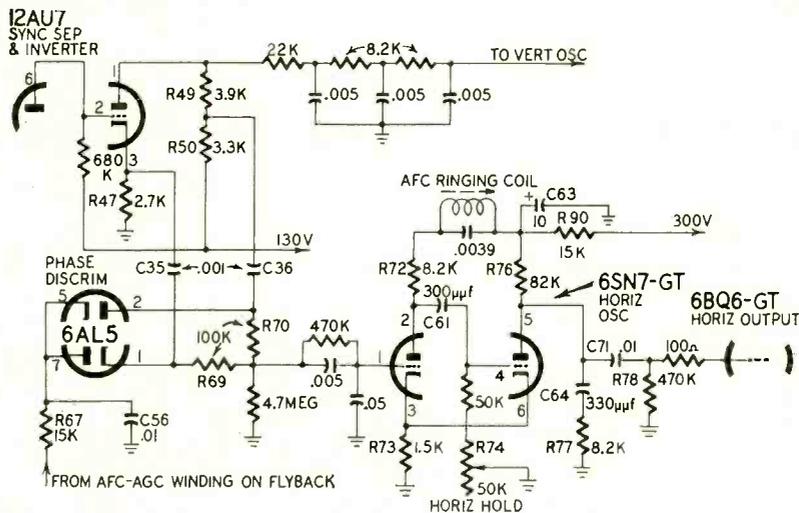


Fig. 1—This partial circuit, showing a TV receiver's sync phase inverter, phase detector and horizontal oscillator stages is used for cases 1, 2, 3 and 4.

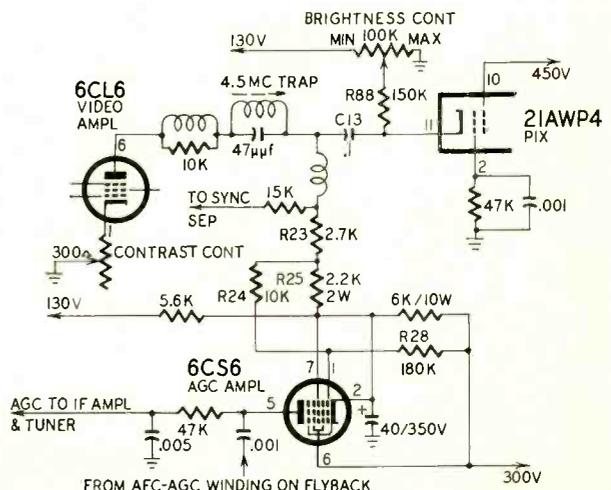


Fig. 2—For cases 5, 6 and 7, use this diagram of the age, video output and C-R tube circuits.

to it and study!
 practice, very tired, or need to get down
 more than 60 you can hold your head high.
 kicks, not for job ratings! But if you scored
 Well, how did you fare? This quiz was for
 input resistance of the vtm.
 age drop across R88 because of the high
 tube disconnected, there is very little volt-
 the voltages at the socket with the picture
 when beam current flows. When checking
 matically biasing the picture tube back
 acts as a self-bias cathode resistor, auto-
 R88, a 150,000-ohm resistor, is high. This

Case 7
 resistance is too high.
 quency response suffers if the plate load

is less likely, and you have overlooked the
 clue about the picture detail. High-fre-
 quency response suffers if the plate load
 R25, a 2,200-ohm resistor, is high. The
 voltage drop across this resistor establishes
 the bias between grid and cathode of the
 6CS6, and this sets the keying level.

Case 6
 through the video amplifier tube. Score 10
 sistance, due to changes in conduction
 across the video amplifier plate load re-
 sistance, due to changes in conduction
 caused by a change in potential drop
 occurs with contrast control variation is
 tube cathode. The change in voltage which
 a permanent positive bias on the picture-

Case 5
 a low-impedance path to ground. Score 20
 cuts. Shorting out R90 (15,000 ohms) con-
 the impedance of the oscillator plate cir-
 C63, a 10- μ t electrolytic, is open, raising

Case 4
 age appearing on the grid.
 is the only possible cause of positive volt-
 age appearing on the grid.

Case 3
 Leakage or short in C61, a 300- μ t capac-
 itor. The tube having been eliminated, this
 is very likely.

Case 2
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 1
 C56, a .01- μ t capacitor, is open. This ca-
 pactor normally forms a sawtooth. In its
 absence, the uninhibited spikes coming from
 the flyback cause heavy conduction in the
 phase detector. The resulting high dc bias
 produced on the oscillator's control grid
 pushes the oscillator way off frequency.
 Note the fault only appears when the
 6AL5 is plugged in.

Case 5
 Score 5
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 4
 age appearing on the grid.
 is the only possible cause of positive volt-
 age appearing on the grid.

Case 3
 Leakage or short in C61, a 300- μ t capac-
 itor. The tube having been eliminated, this
 is very likely.

Case 2
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 1
 C56, a .01- μ t capacitor, is open. This ca-
 pactor normally forms a sawtooth. In its
 absence, the uninhibited spikes coming from
 the flyback cause heavy conduction in the
 phase detector. The resulting high dc bias
 produced on the oscillator's control grid
 pushes the oscillator way off frequency.
 Note the fault only appears when the
 6AL5 is plugged in.

Case 5
 Score 5
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 4
 age appearing on the grid.
 is the only possible cause of positive volt-
 age appearing on the grid.

Case 3
 Leakage or short in C61, a 300- μ t capac-
 itor. The tube having been eliminated, this
 is very likely.

Case 2
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 1
 C56, a .01- μ t capacitor, is open. This ca-
 pactor normally forms a sawtooth. In its
 absence, the uninhibited spikes coming from
 the flyback cause heavy conduction in the
 phase detector. The resulting high dc bias
 produced on the oscillator's control grid
 pushes the oscillator way off frequency.
 Note the fault only appears when the
 6AL5 is plugged in.

Case 5
 Score 5
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 4
 age appearing on the grid.
 is the only possible cause of positive volt-
 age appearing on the grid.

Case 3
 Leakage or short in C61, a 300- μ t capac-
 itor. The tube having been eliminated, this
 is very likely.


Case 2
 R47 in the cathode of the phase inverter.
 Have been from the voltage developed across
 as high as 100 because the leakage would
 on the grid of the 6SN7-GT could not be
 tor. If C35 was the culprit, positive voltage
 Leakage or short in C36, a 100- μ t capaci-

Case 1
 C56, a .01- μ t capacitor, is open. This ca-
 pactor normally forms a sawtooth. In its
 absence, the uninhibited spikes coming from
 the flyback cause heavy conduction in the
 phase detector. The resulting high dc bias
 produced on the oscillator's control grid
 pushes the oscillator way off frequency.
 Note the fault only appears when the
 6AL5 is plugged in.

OXFORD the Leader

OXFORD SPEAKERS

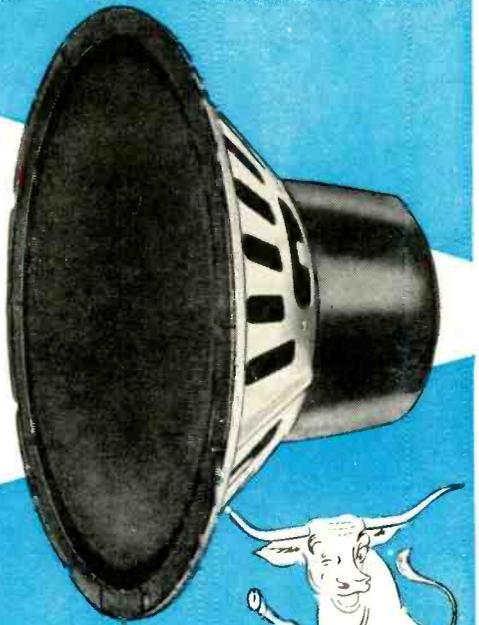
- ... Preferred for
 Original Equipment
- ... Proven for
 Replacement



GET IN THE MAJOR LEAGUES!

Oxford is the major supplier of speakers to original equipment manufacturers throughout the world. Our replacement speakers, too, meet the most exacting design requirements. We have a complete line for any application ... from 2 1/2" to 15". Order Oxford ... you'll be glad you did!

Our catalog is available upon request.

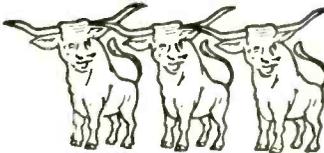

OXFORD Components,

A Division of Oxford Electric Corp.

556 West Monroe St., Chicago 6, Illinois

Oxford Speakers are available from recognized electronic parts distributors.



LOOK
 no further . . . if you're searching for hi-fi savings. Write us your requirements now.
 Key Electronics Company
 120-A Liberty St., N.Y. 6, N.Y.
 Cloverdale 8-4288

FREE! CATALOG OF HI-FI, RADIO, TV PARTS & ACCESSORIES - yours for the asking!

Vidaire ELECTRONICS MFG. CORP.
 365 BABYLON TPKE. - ROOSEVELT, N. Y.

ELECTRONICS

Engineering-Technicians

Bachelor of Science Degree, 30 Months


Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans DAY AND EVENING CLASSES

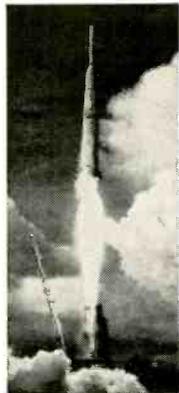Write for Catalog and Registration Application. New Term Starting Soon.



U.S. Air Force Photo

Missile headed for outer space. Courtesy of Space Technology Laboratories, Inc.

HEALD'S ENGINEERING COLLEGE

Established 1863

Van Ness at Post, RE
 San Francisco, Calif.

Your Name


Address

City

State

CAPACITANCE

METER

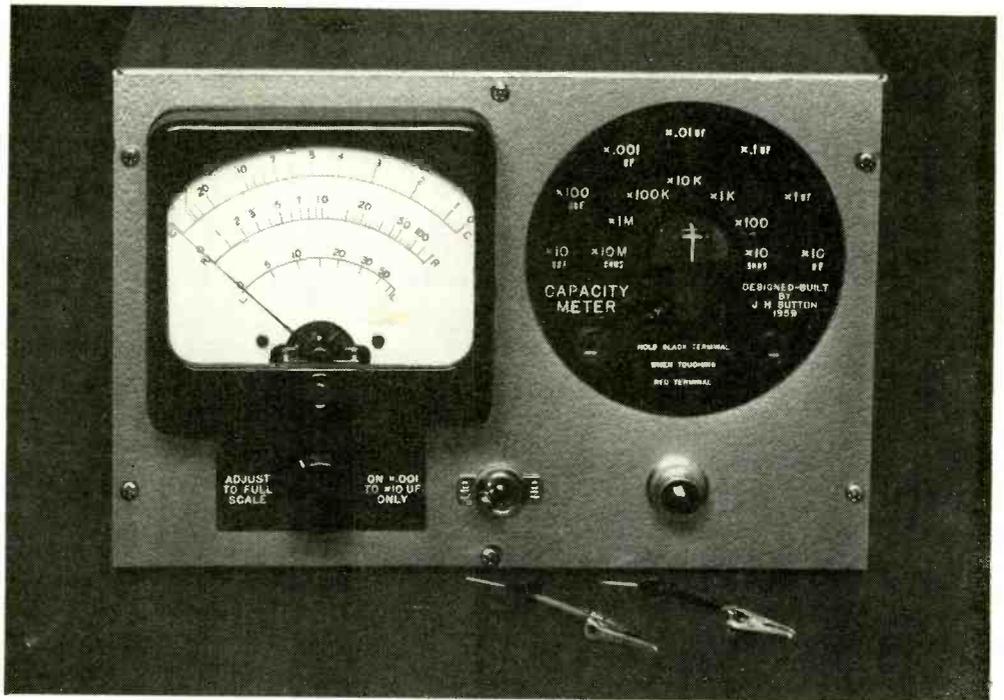

Front view of meter. Plugs and clips connect component to be measured to meter.

This one-tube unit measures capacitance, resistance and inductance

By J. H. SUTTON

THIS capacitance meter covers the unusually wide range of $1 \mu\text{f}$ to $500 \mu\text{f}$. Accuracy for nonelectrolytics is as good as that obtained on a high-grade impedance bridge (electrolytics may be measured approximately). Hand-capacitance does not affect readings, and there is no shock hazard (the maximum test voltage is only 6.3 ac). Warmup time is rapid, less than a minute.

The basic circuit is very simple (Fig. 1-a). But to measure the voltage across the capacitor accurately, the voltmeter must have practically infinite impedance. Hence we add an ordinary cathode-follower stage (Fig. 1-b) whose input impedance is almost open-circuit.

In this circuit, the voltmeter could be a good ac vtvm. A voltmeter with a lower input impedance will distort the cathode follower output. But good ac vtvm's are scarce. Most show large errors on low ac ranges. Because of this, we replace the voltmeter in Fig. 1-b with a good linear amplifier and then read this amplified output on a vtvm, vom or, as in my pictured instrument, on a 1-ma meter. The complete schematic is shown in Fig. 2.

Construction

Construction layout is noncritical, ex-

The instrument measures capacitance from $1 \mu\text{f}$ to $50 \mu\text{f}$. Can operate with a low-priced 1-ma meter.

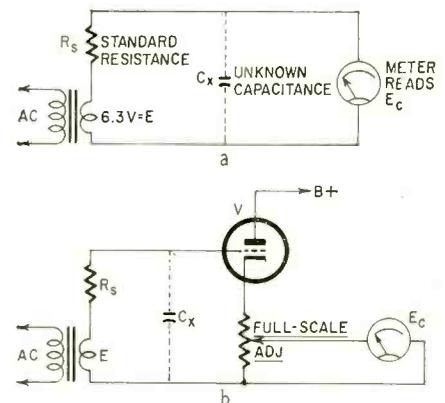


Fig. 1-a—Basic measuring circuit; b—with vacuum-tube amplifier added to reduce loading.


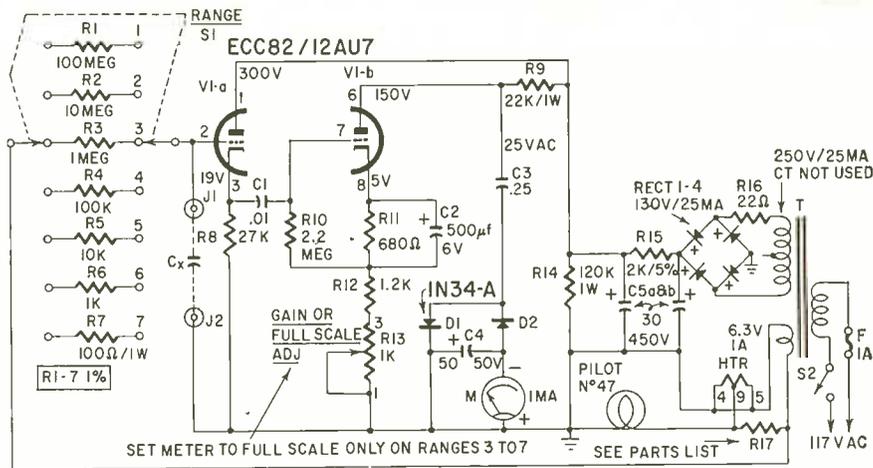


Fig. 2—Schematic of meter.

- R1—100 megohms, 1%, see text
- R2—10 megohms, 1%, see text
- R3—1 megohm, 1%
- R4—100,000 ohms, 1%
- R5—10,000 ohms, 1%
- R6—1,000 ohms, 1%
- R7—100 ohms, 1 watt, 1%
- R8—27,000 ohms
- R9—22,000 ohms, 1 watt
- R10—2.2 megohms
- R11—680 ohms
- R12—1,200 ohms
- R13—pot, 1,000 ohms, linear taper
- R14—120,000 ohms, 1 watt
- R15—2,000 ohms, 5%
- R16—22 ohms
- R17—adjust for 6.3 volts across 12AU7
- all resistors 1/2 watt, 10% unless noted
- C1—0.01 μ f, 600 volts, disc ceramic
- C2—500 μ f, 6 volts, electrolytic
- C3—0.25 μ f, 400 volts
- C4—50 μ f, 50 volts, electrolytic
- C5—30, 30 μ f, 450 volts, electrolytic
- J1, 2—sockets for 1/8-inch plug, 1 red, 1 black, (Amphenol 78-1M or equivalent)
- V1—12AU7
- RECT 1, 2, 3, 4—selenium rectifiers, 130 volts, 25 ma or higher
- D1, 2—1N34
- S1—2-pole, 7 position rotary, Steatite insulation (Centralab PA 2004 or equivalent)
- S2—spst toggle
- M—1-ma meter, see text for scale
- T—power transformer, 250 volts, 25 ma, (ct not used); 6.3 volts, 1 ampere (Stancor PS8416 or equivalent)
- F—1-ampere fuse and holder
- Pilot lamp, No. 47 and socket
- Cabinet, 9 x 6 x 5 inches, aluminum
- Chassis, aluminum
- Miscellaneous hardware: knobs, tube socket, line cord, rubber feet, terminal strips, etc.

RANGE	MULTIPLIER	
	CAPACITANCE	RESISTANCE
1	X 10 μ f	X 10 MEG
2	X 100 μ f	X 1 MEG
3	X .001 μ f	X 100K
4	X .01 μ f	X 10K
5	X .1 μ f	X 1K
6	X 1 μ f	X 100 Ω
7	X 10 μ f	X 10 Ω

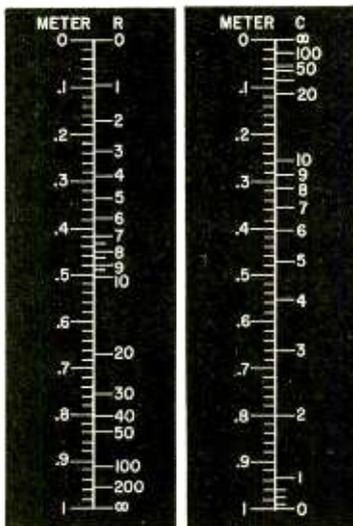

Meter reading	$R_s = 1,000$ ohms		$R_s = 10$ ohms	
	Capacitance in μ f	Meter reading	Resistance in ohms	Meter reading
1.000	0.0	1.000	infinite	
0.998	0.2	0.952	200	
0.989	0.4	0.938	150	
0.975	0.6	0.909	100	
0.958	0.8	0.900	90	
		0.889	80	
		0.875	70	
0.935	1.0	0.857	60	
0.911	1.2	0.833	50	
0.884	1.4	0.818	45	
0.856	1.6			
0.828	1.8			
		0.800	40	
0.799	2.0	0.778	35	
0.770	2.2	0.750	30	
0.742	2.4	0.737	28	
0.714	2.6	0.722	26	
0.688	2.8	0.706	24	
		0.688	22	
		0.667	20	
0.662	3.0			
0.638	3.2			
0.615	3.4	0.655	19	
0.593	3.6	0.643	18	
0.572	3.8	0.630	17	
		0.615	16	
		0.600	15	
0.553	4.0	0.593	14	
0.534	4.2	0.583	13	
0.516	4.4	0.575	13	
0.500	4.6	0.565	12	
0.484	4.8	0.524	11	
		0.500	10	
0.469	5.0			
0.454	5.2	0.487	9.5	
0.441	5.4	0.474	9.0	
0.428	5.6	0.455	8.5	
0.416	5.8	0.446*	8.0*	
		0.412	7.0	
0.404	6.0	0.375	6.0	
0.378	6.5	0.333	5.0	
0.354	7.0	0.286	4.0	
0.333	7.5	0.231	3.0	
0.315	8.0	0.167	2.0	
0.298	8.5	0.091	1.0	
0.283	9.0	0.000	0.0	
0.269	9.5			
		0.256	10	
		0.216	12	
		0.186	14	
		0.164	16	
		0.146	18	
0.132	20			
0.088	30			
0.066	40			
0.053	50			
0.027	100			
0.000	infinite			

Fig. 3-a—Meter-current and capacitance scales ($R_s = 1,000$ ohms); b—meter-current and resistance scales ($R_s = 10$ ohms).

cept that input grid leads should be short to obtain low distributed capacitance. The switch should be steatite, double-deck for ease of resistor mounting. The test jacks are high-dielectric Amphenol sockets 78-1M. Residual capacitance of the instrument is only 15 μ f, about half that normal to a commercial product.

Your vtvm or vom, provided it has nearly linear response, will make a quite satisfactory indicating meter for this device. Using the scale in Fig. 3, voltage readings can be quickly translated into capacitance. Also, ac resistance can be similarly translated. Or, if your ohms scale mid-point is 10, ac resistance can be read directly.

The meter scale of my instrument is home-made and hand-drawn. But this requires some experience plus either a linear calibrating meter or a precision potentiometer. A similar dial can be purchased through your dealer from the Triplett Electrical Instrument Co. (Bluffton, Ohio) for a very few dollars plus cost of the meter. Supply Table I data to them interpreted in ma.

A 1-ma meter is used for two reasons. First, the accuracy of meter readings tends to increase as the meter current increases (i.e. as the sensitivity decreases). Second, a current as heavy as possible through the rectifiers improves their response linearity. My meter actually has a 40- μ a movement with sensitivity reduced to 400 μ a by heavy springs. It is then shunted with a 10% carbon resistor so that full-scale deflection requires about 1 ma. If a vtvm or vom is used as the indicating meter, shunt the terminals and possibly increase series capacitance (C3) until roughly 1 ma is required for full-scale deflection.


Capacitance ranges

The ranges of the instrument are:

Range	Scale Multiplier	Measures Capacitance	Scale Multiplier	Measures Resistance
1	X 10 μ f	0-500 μ f	X 10 megohms	see text
2	X 100 μ f	0-5,000 μ f	X 1 megohm	0-200 megohms
3	X .001 μ f	0-0.05 μ f	X 100,000 ohms	0-20 megohms
4	X .01 μ f	0-0.5 μ f	X 10,000 ohms	0-2 megohms
5	X .1 μ f	0-5 μ f	X 1,000 ohms	0-200,000 ohms
6	X 1 μ f	0-50 μ f	X 100 ohms	0-20,000 ohms
7	X 10 μ f	0-500 μ f	X 10 ohms	0-2,000 ohms

For the Man Who Wants an Advanced Home-Study Program in Electronic Engineering Technology or Nuclear Engineering Technology...

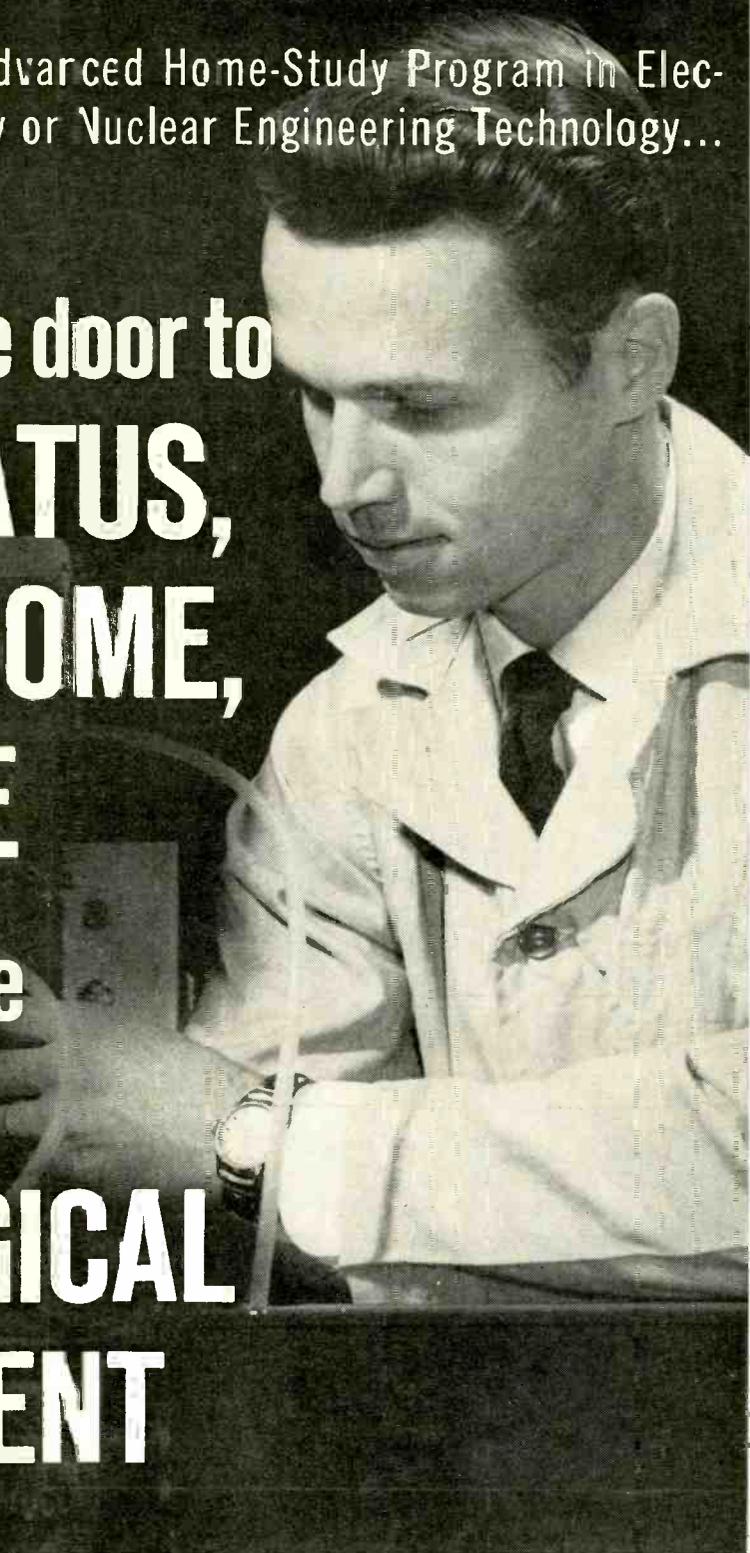CREI opens the door to
HIGHER STATUS,
BETTER INCOME,
and a **SECURE**
FUTURE in the
forefront of
TECHNOLOGICAL
ADVANCEMENT



The world of science is the world of the future. There is no career more stimulating, challenging, or rewarding than that of working with topflight scientists and engineers to develop deep space probes and orbital satellite systems . . . package nuclear power reactors to provide economical, long-lasting power anywhere in the world . . . electronics and radioisotopes for use in medicine, agriculture and industry . . . missile systems for the Armed Forces . . . computers and data processing systems which

will become accepted necessities by finance, industry and government . . . to develop a thousand and one concepts that will make our world a better and safer place for all. You can have a career—or speed up your present career—in one or more of these areas if you are eligible to enroll in a CREI home-study program . . . a program recognized everywhere as excellent insurance for a secure future, high professional stature, and better income.

CREI's Extension Division now offers you college-level programs combining the technological content of advanced residence courses with convenience and economy of home study.

The quality of a CREI education may be gauged by the fact that the demand for CREI graduates and students at the CREI Placement Bureau has far exceeded the supply for several years. Many leading companies and Government agencies send representatives to CREI every year to hire graduates and students for their technical staff. The CREI educational programs were developed in conjunction with leading industrial concerns and government agencies directly interested in the nation's scientific and technological future.

There are now more than 20,000 CREI students in all the 50 states and most countries of the free world. You, too, can follow your CREI program while you remain in your present job. You study at home, when and as you choose . . . and you avoid the time and expense of commuting to a residence school. Within two to four years, depending upon the courses you select and the time you have to apply, you can complete a CREI program in engineering technology. The courses are written in easy-to-understand format, and your personal progress is carefully guided by CREI's competent faculty.

CREI programs bring you the latest technical advances and breakthroughs.

Recent advances and new techniques have placed great importance on how modern and up-to-date the individual's education is. Recognizing this, CREI maintains a large staff of engineers, educators and scientists who occupy prominent positions in government and industry. These men continuously revise the CREI courses and incorporate all new technical information. CREI courses are the most modern you will find . . . anywhere.

The CREI program is designed to meet your present and future employment needs and to increase your professional status and earning power.

CREI students frequently gain promotions and increases in pay long *before* they complete the program. As a graduate you will find that you gain stature and respect among your professional colleagues and supervisors, and

NEW 56-Page Catalog Gives Important Facts About Electronics, Nucleonics . . . and CREI. Send Post-Paid Card Attached For Your Free Copy.

Just published to include new courses being offered by CREI, this informative catalogue discusses the electronic and nuclear industries and answers searching questions about future manpower requirements and career opportunities. The catalogue describes all the courses, the alternative programs . . . it introduces the faculty who will be carefully guiding your progress . . . and it points

that you enjoy a personal satisfaction that comes from working and communicating intelligently with your associates. CREI graduates are important members of the engineering team. Your employer will recognize the assets of your up-to-date education . . . to your personal advantage.

Officials of private industry and government approve CREI for their own personnel.

The National Broadcasting Company . . . Radio Corporation of America . . . Pan American Airways . . . The Martin Company . . . Canadair Limited . . . Canadian Marconi . . . the Voice of America . . . the British Air Force, Navy and Army . . . and some 50 other electronic and nuclear organizations actually *pay all or a substantial part of the tuition* for employees taking a CREI home-study program. Right now, there are 5,240 U. S. Navy personnel enrolled in the CREI extension program.

Official accreditation and recognition.

Founded in 1927, CREI is one of the oldest technical institutes in America. CREI co-founded the National Council of Technical Schools, and was one of the first three institutes whose curricula was accredited by the Engineer's Council for Professional Development. The U. S. Office of Education lists CREI as an "institution of higher learning."

CREI conducts a residence school

in Washington, D. C., for those who wish to attend classes. The regular program of 27 months leads to an AAS degree. No previous technical experience or training is necessary for the residence school.

Qualifications for enrollment.

You qualify for CREI enrollment if you have a high school diploma or equivalent, and if you have had basic technical training or practical experience. Send for free catalogue for details. Tuition is reasonable, and veterans can take advantage of the G.I. Bill.

out how the courses are especially laid out for home study. *The catalogue is yours without cost or obligation, and it is of vital importance to every man desiring to further himself in the expanding world of science and technology. Mail this card today for your copy of "Your future in Electronics and Nuclear Engineering Technology."*


ECPD ACCREDITED TECHNICAL INSTITUTE CURRICULA • FOUNDED 1927

The Capitol Radio Engineering Institute




Home Office:
3224 16TH STREET, N.W.,
WASHINGTON 10, D.C., U.S.A.,
Dept. 1412G

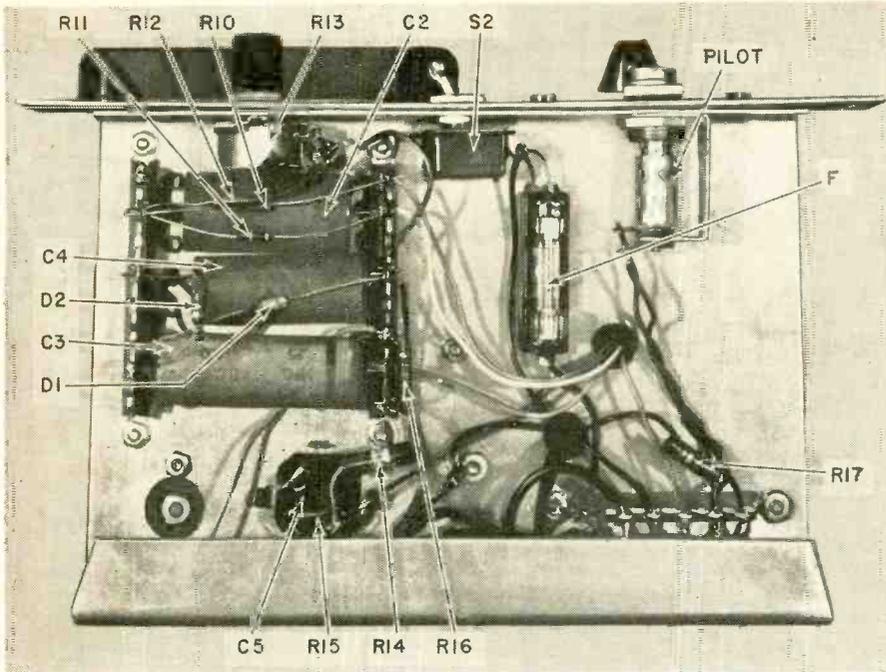England:
CREI LONDON, GRANVILLE HOUSE,
132-135 SLOANE STREET, LONDON,
S.W. 1, ENGLAND



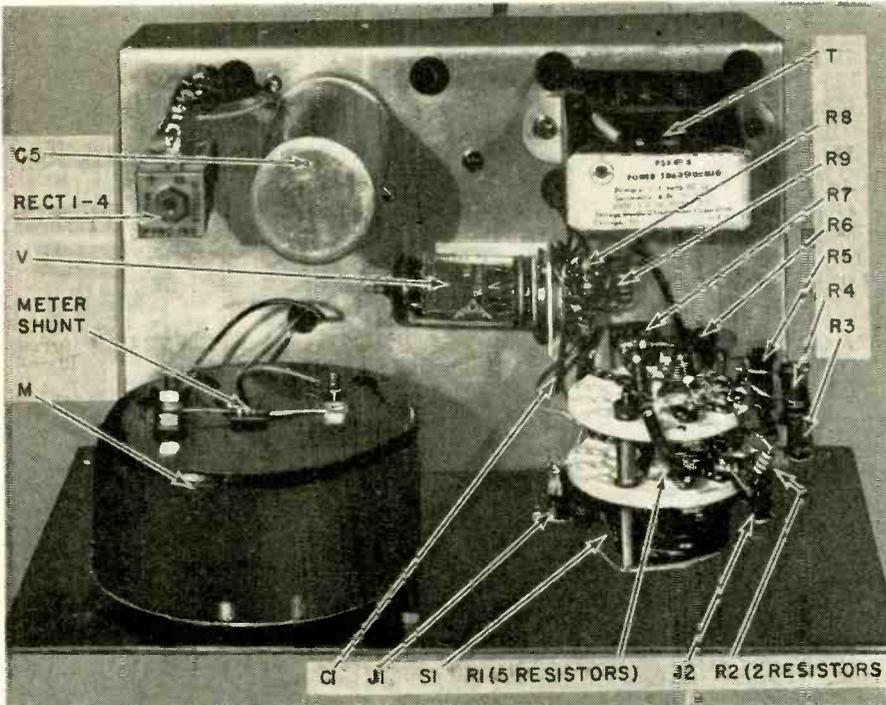Underchassis view. Terminal strips allow neater, easier wiring.



Top view of chassis. Rectifiers are mounted in a stack.

terminal is touched, to prevent needle slamming (from stray ac input). Since inherent capacitance is noted on only the first two ranges, the full-scale adjustment (by R13) should be made on any of the other ranges. This adjustment will hold for all ranges. Normal line-voltage variations affect this setting to only a minor extent.

Electrolytics

Ranges 5 to 7 can be used to measure electrolytic capacitance, provided the effect of power factor is noted. The master will see the power-factor resistance (say R_c) simply as a decrease of capacitive reactance, so that the indi-

cated electrolytic capacitance will be greater than the true capacitance (X_c). However, this discrepancy diminishes progressively to the left of mid-scale. For example, a 17- μf electrolytic with 40% power factor is indicated 17 μf on the $\times 1 \mu\text{f}$ range, and 24 μf on the $\times 10 \mu\text{f}$ range. Again, an 8- μf capacitor with a 5% power factor measures 8 μf on the $\times 1 \mu\text{f}$ range, and 10 μf on the $\times 10 \mu\text{f}$ range.

The power factor of nonelectrolytics is normally neglected but would be similarly indicated. For example, to an .012- μf mica, power factors of 5%, 10% and 15% were added successively. These additions went unnoticed on the

$\times .001 \mu\text{f}$ range; but on the $\times .01 \mu\text{f}$ range, the readings became .013, .014, and .015.

The formula giving capacitance in terms of relative voltage is presented in an appendix. The calculation result is shown in Table I and Fig. 3. The table of resistance value (also in terms of relative voltage) is suitable for calibrating the meter scale.

Inductance

The dial of my meter shows an inductance scale. The inductance-scale multiplier is not engraved on the range selector because I am uncertain of its accuracy. Inductance is related to capacitance, on the meter scale, by an extremely simple formula:

$$\text{Inductance (in henries)} = \frac{7}{\text{capacitance reading (in } \mu\text{f)}}$$

The 7 is an approximation, the full value being 7.036, derived as follows: The relative voltage across a pure inductive reactance X_L will be the same as across a pure capacitive reactance. Hence on the meter $X_L = X_C$. Then by substitution:

$$2\pi fL \text{ (henries)} = \frac{1}{2\pi fC \text{ (farads)}}$$

which simplifies to the above formula when $f = 60$ cycles. Thus, inductance to 1 henry would be measured on range 7 and up to 1,000 henries on range 4. This would limit measurements to large iron-cored inductors, such as audio and power supply chokes.

Concerning choke ratings, the Stancor (Chicago Standard Transformer Corp.) catalog states the following:

"Inductance varies with the amount of dc flowing thru the coil... Filter chokes are rated at 10 volts, 60 cycles, with maximum dc in winding... Audio chokes are rated at 2 volts, 200 cycles, with maximum dc in winding. Tolerance of minus 15% to plus 50% is maintained on all ratings."

In view of this wide rating tolerance, perhaps the following capacitance meter measurements, on four chokes I have, are not too bad:

Type and rating	Range 4	Range 5	Range 6
power, 10 h, 300 ohms	—	7.5 h	5.9 h
power, 10 h, 300 ohms	—	16 h	9 h
power, 2 h, 150 ohms	—	2.35 h	2.25 h
audio, 25 h, 660 ohms	24 h	35 h	—

One might assume, as for electrolytics, that the lowest-range reading is to be accepted; but here the second choke is a notable exception, unless its rating is in error. Measuring this choke's value by the voltmeter-ammeter method, with 10 volts ac but no dc in the winding, indicated that the rating might indeed be in error (measured 22 h, "high" readings being the rule by this method).

Available literature does not detail manufacturers' methods of rating chokes. The resonance method often cited in the literature (RADIO-ELECTRONICS, June, 1956, page 112) is more than likely incorrect.

Other measurement methods

As far as I have read (see bibliography), the various types of capacitance-measuring devices are never compared in the literature. In fact, most texts are blissfully unaware of accurate methods other than by bridge. Yet this comparative information is

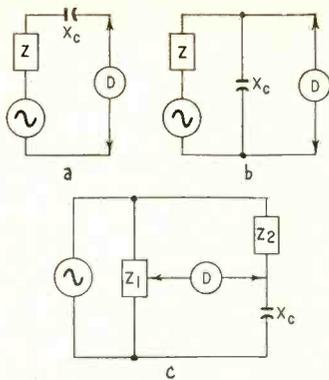


Fig. 4—Basic measuring circuits using: a—detector in series; b—detector in parallel, and c—bridge.

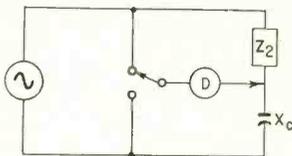


Fig. 5—Special bridge circuit using a spdt switch.

helpful to the technician, so that he may select the method best suited to his use.

Only three capacitance-measurement methods appear possible, depending on the position of the detector (meter, electron-ray tube, etc.) in the circuit (Fig. 4). They are: series detection, parallel detection and bridge detection. Additional configurations do not appear possible, except for interchange or elaboration of the elements.

In a special case of the bridge (Fig. 5) Z_1 becomes an infinite-impedance (an open switch) and D, instead of being a null detector, is a meter to equalize the voltages across Z_2 , X_c . If D is a negligible load, we can say that Z_2 (usually a variable resistor) equals X_c .

All three are represented in construction articles published by RADIO-ELECTRONICS since January, 1955 (as far back as my files go). Table II lists pertinent data on these and on the Heathkit CM-1 (series detector) and the Knight-kit capacitor checker (bridge).

In the series-detector design, the oscillator voltage must be high if the frequency is low (if the voltage is not high, the range is limited). Calibration procedure is always empirical because the detector impedance is effectively a part of Z. By "empirical" I mean, to quote construction articles, "pick up a couple of dozen good fixed capacitors" and "mark the meter reading with the capacitor's value." The Heathkit CM-1 is supplied with four precision capacitors and, because circuit response is linear, readings should be accurate.

In the parallel-detection system, the oscillator voltage can be low without sacrificing measurement range. The oscillator and detector impedance must be included in Z.

The null-detection bridge can be made the most accurate of all measurement methods. Moreover, only this type can measure the power factor apart from the capacitance. There are, however, disadvantages. At mid- to high-range



SMALLER THAN A PORTABLE TYPEWRITER YET OUTPERFORMS TESTERS COSTING HUNDREDS OF DOLLARS!

Fast, accurate, never lets you down

ONLY **59⁵⁰**

The MIGHTY MITE by SENCORE

The TC109 Tube Checker is a real money maker for the serviceman and a trusty companion for engineers, maintenance men and experimenters. Even students and hobbyists can afford the Mighty Mite for their own use or to service an occasional Radio or TV set. This small complete tester is a tremendous performer that spots bad tubes missed by costly mutual conductance testers.

New unique "stethoscope" approach tests for grid emission and leakage as high as 100 megohms, yet checks cathode current at operating levels. Special short test checks for shorts between all elements. The MIGHTY MITE will test every radio and TV tube that you encounter (over 1300!) plus picture tubes, foreign, five star and auto radio tubes (without damage). As easy to set up as a "speedy tester" from easy to follow tube booklet. New tube charts free of charge. Simple operating instructions are screened on the front panel.

Check these plus Sencore features • Meter glows in dark for easy reading behind TV set • Stainless steel mirror in cover for TV adjustment • Rugged, all steel carrying case and easy grip handle • Smallest complete tester made • Inner chassis can be easily transferred to tube caddy, bench or counter. • Only 9" x 8" x 2½". • Wt. 8 lbs.

See your Distributor... if he cannot help you, Pat will



PAT RUPE, Customer Service

SENCORE, ADDISON 3, ILLINOIS

Dear Pat: Will you please...

- Send me _____ Mighty Mite
 Check or M.O. enclosed (PP Prepaid.) Send C.O.D.

Distributor's Name (if any) _____

Your Name _____

Street _____


City _____ Zone _____ State _____

ALL UNITS FULLY GUARANTEED OR MONEY BACK WITHIN 10 DAYS

RECORDS SOUND BEST
with

DYNACO STEREO DYNES

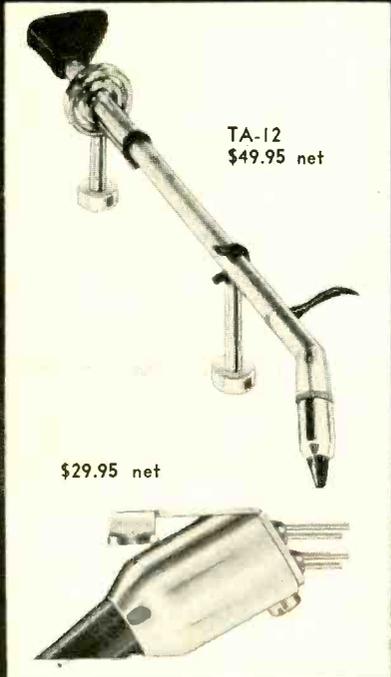Choose either the Stereodyne II (mounts in all standard arms) or the slim, trim TA-12 arm-cartridge combination for the most natural sound from both stereo and mono recordings.



TA-12
\$49.95 net

\$29.95 net

DESIGNED TO THE HIGHEST
DYNACO STANDARDS

- ★ unequalled performance
- ★ outstanding engineering
- ★ unsurpassed value

Rigorous laboratory testing of every unit assures that your cartridge will exceed every specification.

- Smoothest response: ± 2 db from 30 cps to 15 KC. With standard Westrex 1A test disc.
- True stereo: More than 22 db channel separation effectively maintained throughout the audio spectrum, with accurate balance and proper phase relationship.
- Superior tracking: highest compliance, low mass, plus exclusive symmetrical push-pull design for minimum record wear and lowest distortion.
- Complete freedom from hum.

Hear and compare it at your favorite dealer's showroom.

Write for complete specifications

DYNACO, INC.

3912 Powelton Ave. • Phila. 4, Pa.
CABLE ADDRESS: DYNACO, PHILA.

TABLE II—Previously Published Data on Capacitance Meters

Reference	Oscillator Frequency	Volts	Measurement range	Detector	Calibration Procedure
Series detection					
Sept. '58, p. 109	60	125	1,000 $\mu\mu\text{f}$ to 10 μf	1-ma meter	empirical
Apr. '59, p. 39	60	270 max.	250 $\mu\mu\text{f}$ to 10 μf	ac vom	"
Aug. '59, p. 88	60	6.3	250 $\mu\mu\text{f}$ to 0.5 μf	dc vtvm	"
Heath CM-1	—	low	1 $\mu\mu\text{f}$ to 0.1 μf	50- μa meter	"
Parallel detection					
March '57, p. 95	1 mc	0.13	12 $\mu\mu\text{f}$ to 300 $\mu\mu\text{f}$	50- μa meter	component
the present article	60	6.3	1 $\mu\mu\text{f}$ to 500 μf	1-ma meter	"
Bridge detection					
March '55, p. 106	audio	low	not stated	headphones	component
July '55, p. 40	1,000	—	not stated	"	"
Feb. '57, p. 60	audio	low	10 $\mu\mu\text{f}$ to 1 μf	"	"
Aug. '58, p. 80	60	200	10 $\mu\mu\text{f}$ to 1 μf	vtvm	"
Knight-checker	60	60	10 $\mu\mu\text{f}$ to 1,000 μf	electron-ray tube	"

audio frequencies, measuring components must be shielded or accuracy will suffer. Also, the detector is practically limited to headphones, a disadvantage in noisy surroundings. At 60 cycles, components can be unshielded. A visual detector is practically universal, although there are complaints that the electron-ray tube is not completely satisfactory (RADIO-ELECTRONICS, January, 1956, page 180). To cover a wide measurement range, the oscillator voltage must be relatively high. Sometimes this voltage is higher than should be impressed on low-voltage low-capacitance electrolytics. For example, if the oscillator voltage is 60 in series with the usual 2- μf standard, then 10 volts of raw ac will be impressed on a 10- μf electrolytic. This may damage a 25- or 50-volt bypass capacitor, and almost certainly will damage 6- to 15-volt transistor types.

Because of the above, I decided to construct a parallel-detection instrument. For speed of measurement, a definite meter reading is preferred to hunting for a null indication. **END**

Bibliography

- Kinnard, *Applied Electrical Measurements*, Wiley, N.Y., 1956, Part I, Section 4.
 Frank, *Electrical Measurement Analyses*, McGraw-Hill, N.Y., 1959, Chapter 8.
 Smith & Wiedenbeck, *Electrical Measurements*, McGraw-Hill, N.Y., 1959.
 Golding, *Electrical Measurements & Measuring Instruments*, Pitman, London, 1955, Chapter 6.

- Termin & Petit, *Electronic Measurements*, McGraw-Hill, N.Y., 1952, Chapter 3.
 Banner, *Electronic Measuring Instruments*, Chapman & Hall, London, 1958, Chapter 7.
 Buckingham & Price, *Principles of Electrical Measurements*, English University Press, London, 1955, Chapters 5, 8.
 American Radio Relay League, *Radio Amateur's Handbook*, West Hartford, Conn., 1959 edition, page 525.
 Henney, *Radio Engineering Handbook*, McGraw-Hill, N.Y., 1959, Chapters 4, 14.
 Termin, *Radio Engineers Handbook*, McGraw-Hill, N.Y., 1943, Sections 2, 13.
 Orr, *Radio Handbook*, Editors & Engineers, Ltd., Summerland, Calif., 1956 edition, pp 684-9.
 Scroggie, *Radio Laboratory Handbook*, Wireless World, London, 1954, Chapter 9.

Appendix: Capacitance Calculation

Input current (I) flows through the standard resistance (R_s) and through the unknown capacitive reactance (X_c) in series, so:

$$(R_s^2 + X_c^2)^{1/2} I = E \text{ (input voltage)}$$

In R_s we include the ac resistance of the input transformer which, in practice, is negligible compared to the minimum measuring resistance used, 100 ohms. The detector measures the voltage E_c across X_c , so the relation of E_c to E is:

$$\frac{X_c I}{(R_s^2 + X_c^2)^{1/2} I} = \frac{E_c}{E}$$

Solving for E_c and converting X_c to C_x :

$$\frac{E_c}{E} = \frac{X_c}{(R_s^2 + X_c^2)^{1/2}} = \frac{1}{(4\pi^2 f^2 R_s^2 C_x^2 + 1)^{1/2}} = E_c$$

From this we calculate E_c by assigning scale values to C_x : power of 10 values to R_s and to E, a nominal full-scale meter value, say 1. E_c will then be given in terms of a 0-to-1 meter scale. So if a 0-to-10 scale is used, multiply the tabular values by 10. For a 0-to-12 scale, multiply the values by 12, etc. Table I was calculated using a five-place logarithm table. The resistance formula and data are derived in a similar fashion.




"Of course, technically, I'll have to charge you for a house call."

WATCH THAT FUSE REPLACEMENT

The fuse that fits isn't always the right one!

By JAMES W. ESSEX

THE mushrooming growth of electrical apparatus has helped the lowly fuse rival the vacuum tube in abundance and variety. There are sizes and shapes to fit any application—from circuits requiring slow-blow types for electric motors to vibrationproof fuses (see diagram) for aircraft and mobile equipment. All come in a wide variety of amperage ratings from the 1/500-amp 8AG fuse designed to protect sensitive instruments to the 9AG with its 50-amp rating for Diesel trucks. All serve the needs of industry (and the home). What would our costly circuits be worth (even home TV's) if a malfunction of one part could destroy many others? Fortunately, with the aid of the fuse, we can buy protection for a few pennies.

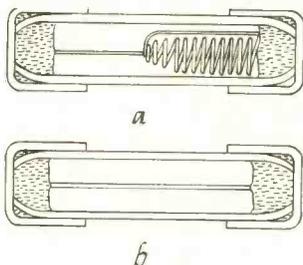

An anti-vibration fuse (a) and a standard type (b).

But there are limitations. Failing to note a few important facts about fuses can negate their usefulness and practically eliminate their money-saving potential. The electric windshield wipers on a friend's car failed one winter day. He tried to get things going again by inserting another fuse. He didn't bother to observe the markings on the one he took out. The one he put in was chosen merely because "it fitted." It blew. Angry, he wrapped cigarette foil around it and tried again. That fixed it. Everything was fine until a severe snowstorm caused the wipers to bind momentarily. He had no protection. The electric motor burned out. Cost—\$4.75 plus labor. Choosing the correct fuse in the first

place would have been less costly. Moral: do not choose a fuse replacement by size alone.

In our plant, we make fire engines, and fuses play an important part in the intricate lighting network of a truck. Where time is sometimes short, choosing the wrong fuse can be a serious mistake. Our wiring networks feed flashing lights, signal warning lights, compartment lights for night operation, and panel lights.

Three of the fuses (to give only one example) are the same physical size but have amperage ratings of 5, 20 and 30. Think what could happen if a 5-amp fuse were inserted in a 30-amp circuit or vice versa because someone chose a fuse by size alone. In one case, the circuit would not stand up. In the other, there would be no protection.

Auto manufacturers have made every effort to guard against over- or under-fusing by adopting a system in which fuse lengths correspond to amperage ratings. The shorter the fuse, the lower the amperage-carrying capacity. The longer the fuse, the greater the current capacity. But they have been victims of progress, just as the changing designs in automobiles keep new cars old. According to Mr. A. M. Kalata of Littelfuse Inc. of Des Plaines, Ill., it is an inheritance of the past which progress has outdated. He says, "When the fuse industry first went into the manufacturing of fuses, they were primarily for the automotive trade. The Society of Automotive Engineers started a particular new line with the thought in mind that each amperage would have a different physical length. But the line got too big. Consequently, they reverted to the commercial standard field or nomenclature, as we know it." To name a few, there are 1AG, 3AG, 4AG, etc. The old SFE line (which is still the prefix for the automotive fuses) is still with us. For example, you'll still find SFE 20 and SFE 14 fuses widely used in autos to protect car radios. Others, like the SFE 6 and SFE 9, are used for headlight circuits.

How do the newer fuses—1AG, 3AG, etc.—differ from the old? First, the SFE line maintains the standard that fuse length corresponds to amperage. The new fuses, like the 1AG and 3AG, have a standard length for each type regardless of amperage. Thus, you can get a 3AG fuse which is 1 1/4 inches long in any amperage from 5 to 30, while only the 20-amp SFE has the same length. If you want a 30-amp fuse in the SFE series, length would jump to 1 7/16 inches.

The variety of fuses in the one-length type continue on into the 4AG, 5AG and on through 9AG types. Each group has its own particular use. Each group has a particular length.

When replacing a fuse, note the nomenclature stamped on the barrel and put in a similar one. Don't use a fuse just because it fits. For a rough guide in choosing fuses for original equipment follow these steps:

Determine the physical dimensions of the fuse to be used. Then choose a fuse that has the current-carrying capacity the circuit calls for. If you are working with a circuit in which momentary surges occur but you don't want to sacrifice protection by going higher in fusing, choose a slow-blow fuse, which has a high time lag. It can withstand heavy surges yet blow quickly on shorts.

I've often seen technicians confused by the voltage ratings marked on some fuses—32 volts or 250 volts, for example. This simply means that the 32-volt fuse can be used in any circuit up to 32 volts. Or a 250-volt fuse can be used in any circuit up to 250 volts. If your application calls for 32 volts and the fuse you get is marked with the proper amperage, but 250 volts, it will work satisfactorily, but it may cost a little more. END

Current Rating (amperes)		Length (inches)
3AG	SFE	SFE*
—	4	5/8
5	—	—
—	6	3/4
7 1/2	—	—
—	9	7/8
10	—	—
—	14	1 1/8
15	—	—
20	20	1 1/4
25	—	—
30	30	1 7/16

*All 3AG fuses are 1/4 inch in diameter and 1 1/4 inches long

A listing of two series of 32-volt fuses. Note that the 3AG types are all 1/4 inch in diameter and 1 1/4 inches long. The length of SFE automotive fuses changes in relation to current rating, making it impossible to put too large a fuse in a circuit.


Neatest Tool Trick In Years!

It's

VACO's®

"PIGGY-BACK" SCREW DRIVER OFFER

Look What You Get!

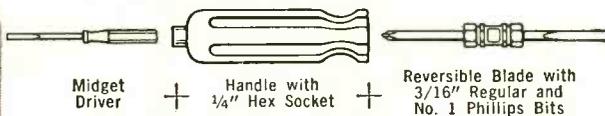

Only \$1.28 complete (Dealer Net)

A regular Vaco instrument-type screw driver is included FREE in this deal with the purchase of a quality VACO DU-11 Reversible with dual purpose regular and Phillips bits and 1/4" hex socket on dome of handle.



Midget Driver FREE!

The midget driver handle, as illustrated, fits "piggy-back" into the hex socket of the DU-11 handle dome. This gives extra length and precision control when working in hard-to-get-at places.

Look for this display or ask your Parts Distributor for the VACO DU-11 "Piggy-Back" offer.

VACO PRODUCTS COMPANY

317 East Ontario Street, Chicago 11, Illinois

Mercury offers you **MORE TUBE TESTER** for your money!

CHECKS ALL RADIO AND TV TUBES FOR:

- ✓ Cathode emission
- ✓ Shorts and leakage
- ✓ Grid leakage
- ✓ Gas content

Housed in sturdy gray-hammertone steel case with retractable handle

Model 103 TUBE TESTER **\$4775** Net



Although low in price the Model 103 has a range of operation that will outperform more expensive tube testers.

Here's how easy it is to test all tubes completely, accurately — IN JUST SECONDS!

- 1 SET 3 CONTROLS
- 2 INSERT TUBE
- 3 PRESS QUALITY BUTTON

- Tests picture tubes with a specially designed built-in CRT socket
- Positively cannot become obsolete... circuitry is engineered to accommodate all new tube types
- New tube charts furnished periodically to registered owners

See your electronics parts distributor

MERCURY ELECTRONICS CORP., 77 SEARING AVENUE, MINEOLA, NEW YORK


West Coast Office: 4306 W. Victory Blvd., Burbank, Calif.

NEW TUBES and SEMI-CONDUCTORS

A VERY DIVERSE group of products were released this month. There are 12.5-mc amplifier transistors, Zener diodes, 150-watt power transistors, and a set of tubes for ac-dc radios.

2N776, -777, -778

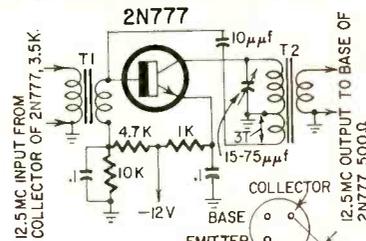A family of silicon surface-alloy diffused-base transistors for 12.5-mc amplifier applications. The transistors feature a typical power gain of 25 db at 12.5 mc. Each transistor has a different beta range, making it possible to use these transistors in both narrow and wide-band video amplifiers.



T1 - PRI = 20T, N°28 ENAM WIRE CLOSE-WOUND ON 1/4" OD COIL FORM (CAMBION LS6 FORM WITH RED CORE)
SEC = 8T, N°28 ENAM WIRE CLOSE-WOUND OVER PRI
T2 - PRI = 23T (OTHERWISE SAME AS T1 PRI)
SEC (SAME AS T1 SEC)

Maximum ratings of these Philco transistors are:

V _{CB0}	20
V _{CE0}	15
V _{EB0}	2
I _c (ma)	100
P _{total} (mw)	150


Beta gain characteristics are:

2N776	6-18
2N777	11-36
2N778	28-90

The diagram shows a typical single-stage 12.5 mc amplifier using the 2N777.

2N174, 2N1100, 2N1358

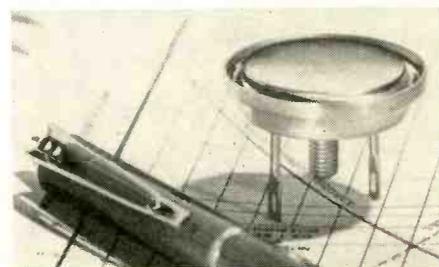Three "doorknob" transistors that have a 150-watt power rating. All are intended for power applications where



RADIO-ELECTRONICS

GOING "BROKE" ON FILAMENT "BREAKS"?



**NEW SYLVANIA 1G3/1B3 HAS
"BUILT-IN "PROFIT PROTECTION."**

IT'S HARD to make a dollar in this TV service business. And callbacks on tubes make it even tougher. That's why Sylvania concentrates on making tubes that perform better and last longer.

Take the new Sylvania 1G3/1B3, for example. The improved filament has increased life span and operates at reduced temperature. Plate is extra-big. Volume of space between it and the filament is enlarged. (That adds to "cooler" filament operation without lowering emission capabilities, and cuts probability of plate-to-filament arc-over.) Glass envelope has extraordinarily high electrical resistivity. This reduces electrolysis and the development of gas and leakage.

Further, every new Sylvania 1G3/1B3 is tested for emission, for arcing and electrical stability at maximum ratings, and arc-over-proofed at higher-than-rated plate voltages to give extra assurance of long tube life.


So, give yourself a break. Replace defective 1G3/1B3 high-voltage rectifier tubes with the new long-life SYLVANIA 1G3/1B3. Available from your distributor . . . now! Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.



SYLVANIA

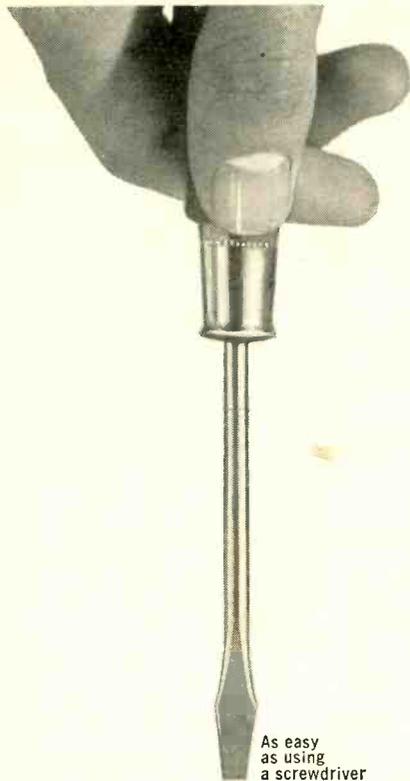Subsidiary of **GENERAL TELEPHONE & ELECTRONICS**





As easy
as using
a screwdriver

EVERY ROOM A TV OR FM ENTERTAINMENT CENTER NEW BLONDER-TONGUE TV/FM HOME SYSTEM KIT

It's so easy to enjoy brilliant TV or FM performance on up to four sets. Good reception starts with a remarkable new indoor antenna  Installs easily in attic or other convenient indoor areas. In primary signal areas, eliminates the need for an outdoor antenna, yet provides the reception capabilities of an outdoor antenna. The TV signal is distributed by a quality engineered 4-set coupler  providing exact match, low loss, inter-set isolation. And, you get sparkling TV or FM performance here. Only \$9.95 list



engineered and manufactured by

BLONDER-TONGUE LABORATORIES, INC., 9 ALLING STREET, NEWARK 2, N. J.

Canadian Div.: Benco Television Assoc., Ltd., Toronto, Ont. Export: Morhan Export Corp., New York 13, N. Y.
home TV accessories • UHF converters • master TV systems • industrial TV systems • FM-AM radios


a beta gain of 25-50 at a 5-amp collector current are needed.

Maximum ratings of these Motorola transistors are:

	2N174	-1100	-1358
V_{CB}	80	100	80
V_{EBO}	60	80	60
I_E (amps)	15	15	15
I_B (amps)	4	4	4

Squarer square corners

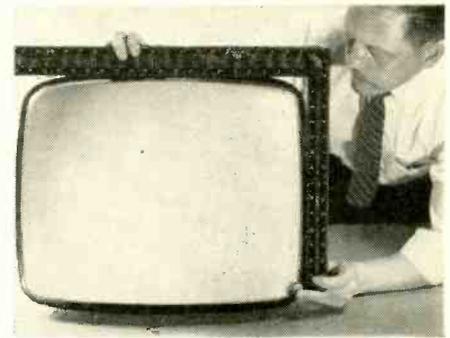Nearly square corners on new 19- and 23-inch picture tubes have expanded the useful viewing area to more than 95% of the area needed to display all picture information transmitted. Although the tubes are almost identical




in height and width to typical 17- and 21-inch versions, they have 11% more screen area (17 square inches) than conventional 17-inch tubes and 8% more area (20 square inches) than 21-inch tubes. A look at the 23-inch Westinghouse 23FP4 shows just how square the corners are getting.

18FX6, 18FW6, 18FY6, 34GD5, 36AM3-A


Here are five tubes that can make up the tube complement of an ac-dc AM radio. All are 7-pin miniatures and all have 100-ma heaters. A complete AM radio using these tubes would have a power consumption of about 20 watts.

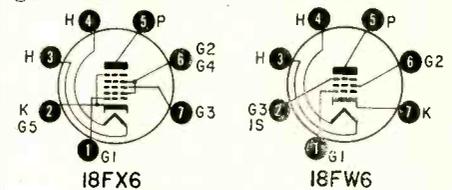The 18FX6 is a pentagrid converter intended for use with grid 3 as signal input electrode; and cathode, grid 1 and grid 2 uses as a triode oscillator.




The 18FW6, a remote-cutoff pentode for use as an rf or if amplifier tube, has a 4,400- μ mho transconductance at 11-ma plate current.

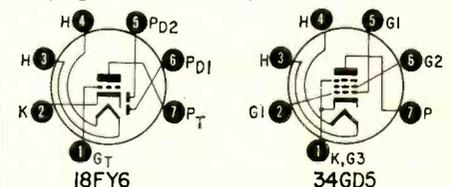The 18FY6 is a twin-diode, high-mu triode intended for use as an AM detector, age and af voltage amplifier.



The 34GD5 is a beam power tube designed for the output stages of small ac-dc radios with 110-volts on the plate, it can deliver 1.4 watts of audio.


The 36AM3 is a half-wave rectifier.

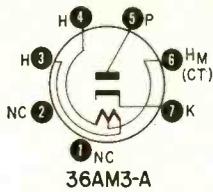

Together, these 5 tubes become an AM ac-dc radio team.

IN3016 through IN3051

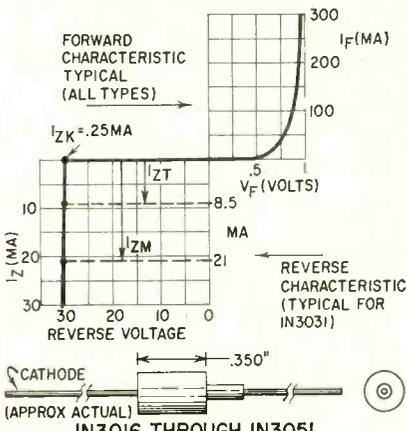A series of Zener diodes rated at 1 watt range from a 6.8- to a 12-volt unit. Silicon, diffused-junction types with sharp zener knee; 5%, 10% or 20% tolerances, as desired.




Ratings of some of these Motorola units are:

	Zener Voltage	Max dc Zener Current (ma)
IN3016	6.8	100
IN3020	10	65
IN3024	15	42
IN3028	22	29
IN3032	33	20
IN3036	47	13
IN3040	68	9
IN3044	100	6
IN3048	150	3.7
IN3051	200	3

1/4 M2.4AZ through 1/4 M6.8AZ

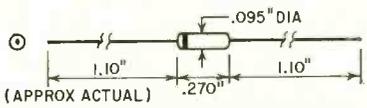A series of 1/4-watt Zener diodes for use as constant-voltage references for 2.4- through 6.8-volt applications. The units in 5%, 10% or 20% tolerances. The cathode end is indicated by a color band. When the diode is operated in the Zener region, the cathode end will be positive with respect to the anode end.



1/4 M2.4AZ THROUGH 1/4 M6.8AZ

Electrical characteristics of these Motorola units are:

Type	Zener Voltage	Max Zener Imped (ohms)	Current (ma)
1/4 M2.4AZ	2.4	60	70
1/4 M2.7AZ	2.7	60	65
1/4 M3.0AZ	3.0	55	60
1/4 M3.3AZ	3.3	55	55
1/4 M3.6AZ	3.6	50	52
1/4 M3.9AZ	3.9	50	49
1/4 M4.3AZ	4.3	45	46
1/4 M4.7AZ	4.7	35	42
1/4 M5.1AZ	5.1	25	39
1/4 M5.6AZ	5.6	20	36
1/4 M6.2AZ	6.2	15	33
1/4 M6.8AZ	6.8	10	30

FREE

GIANT 1961 204 PAGE CATALOG

SAVE UP TO 50% ON B-A SELECTED KITS

TOP VALUES IN POWER AND HAND TOOLS

HI-FI AND STEREO SYSTEMS & COMPONENTS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

100'S OF NEW ITEMS LISTED HERE FOR 1st TIME

BURSTEIN-APPLEBEE CO. Dept. RE
1012-14 McGee St., Kansas City 6, Mo.

Send Free 1961 B-A Catalog No. 611

RUSH COUPON TODAY!

NAME _____

ADDRESS _____

CITY _____ STATE _____

Unbelievable **LOW PRICES!**
NOT KITS . . . But Factory Wired and Guaranteed
HIGH QUALITY INSTRUMENTS

New! Model 999 Radio & TV SIGNAL GENERATOR

Provides highly stable signal. Generates R. F. frequencies from 150 Kilocycles to 50 Megacycles. (150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics). R.F. is obtainable separately or modulated by the Audio Frequency. Measures 7 3/4" x 7 3/4" x 5". Weight 8 Lbs.

Complete—only \$14.95

New! TC-75 Univ. Combination TEST SPEAKER & SIGNAL TRACER

Plus resistor tester
Plus condenser tester
Plus output indicator
Plus speaker substitution. Plus resistor substitutor
Plus substitute 100 V D.C. power supply
Plus field substitutor. Plus condenser substitutor
Plus voice coil substitutor
Plus signal tracer
Plus universal output transformer
Plus experimental one stage audio amplifier
Measures 7" x 11" x 5". Weight, 8 Lbs.

Complete—only \$19.95

Order directly from **METROPOLITAN ELECTRONICS** • 106 Fifth Ave., New York 11, N.Y.



It's smart to get the BEST and keep the rest of your PROFITS! . . . with EMC TEST EQUIPMENT . . . the finest quality line of precision instruments at the lowest possible prices.

new PRODUCTS




COMPONENT SUBSTITUTER, model 500. Substitutes 20 values of resistors from 33 ohms to 10 megohms, 10 values of capacitors from .0001 to 0.5 μf , 10 values of electrolytics from 4 to 330

prods. 6 x 4 inches.—Audiotex Mfg. Co., Div. of Textron Electronics, Inc., 400 S. Wyman St., Rockford, Ill.

LABORATORY SCOPE, model 600. Wide-band or high-sensitivity operation. Regulated power supply. Sweep-frequency pulse output on panel terminal. Wide-band vertical amplifier, flat within 1 db from less than 20 cycles to 4.9 mc. 2-range vertical sensitivity from 20 mv/inch. Uniform horizontal amplifier response within 2 db from less than




Model 102 Volometer
Features a $3\frac{1}{2}$ " 2% accurate—800 microamperes D'Arsonval-type plastic front meter with 3 AC current ranges, and the same zero adjustment for both resistance ranges. Specifications . . . AC Voltage—5 Ranges: 0 to 12-120-600-1200-3000 volts. DC Voltage—5 Ranges: 0 to 6-60-300-600-3000 volts. AC Current—3 Ranges: 0 to 30-150-600 ma. DC Current—4 Ranges: 0 to 6-30-130 ma. 0 to 1.2 amps. Two Resistance Ranges: 0 to 1000 ohms, 0 to 1 megohms. Model 102, Wt. 1 lb. 5 oz. Size: $3\frac{1}{4}$ " x $6\frac{1}{4}$ " x 2". \$14.90. Kit, \$12.50.

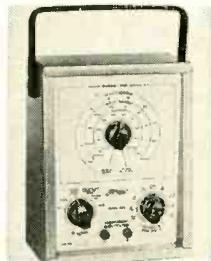

Model 204 Tube-Battery-Ohm Capacity Tester

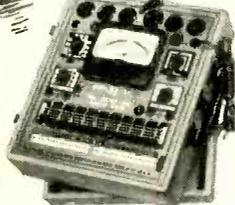Emission tube tester. Completely flexible switching arrangement. Checks batteries under rated load on "reject-good" scale. Checks condenser leakage to 1 meg. Checks resistance up to 4 megs. Checks capacity from .01 to 1 mfd. Model 204P, illustrated, \$55.90. Model CRA, Cathode ray tube adaptor, \$4.50.




μf , power rectifiers up to 55 ma, crystal diodes. Continuously variable power resistance up to 5,000 ohms, and bias voltages up to 15 volts either polarity. Hammertone-finish steel case, carrying handle folds back to tilt instrument when in use. — Mercury Instruments Corp., 77 Searing Ave., Mineola, N. Y.


GRID-CIRCUIT TESTER, GCT-9, for all TV tube types. 6AF6 eye indicator. Checks grid emission, leakage, cathode continuity and interelement shorts.

20 cycles to 200 kc. Linear sawtooth sweep, 10 cycles to 100 kc. Input calibration voltage 10 volts peak to peak. Camera studs for mounting standard 5-inch scope camera. Accessory probes available. 15 x $9\frac{1}{2}$ x 13 inches.—Jackson Electrical Instrument Co., 124 McDonough St., Dayton, Ohio.

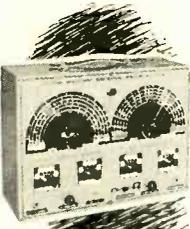
TEST PANEL, models 610-500, 610-550, 610-650. To add to manufacturer's 500, 550 and 650 tube testers for use on all new, future and foreign tube types.



Model 700 RF-AF Crystal Marker TV Bar-Generator
Complete coverage from 18 cycles to 108 megacycles on fundamentals. Bar generator for TV adjustment, with a variable number of bars available for horizontal or vertical alignment. Square wave generator to 20 kilocycles. Wien Bridge AF oscillator with sine wave output from 18 cycles to 300 kilocycles. Crystal marker and amplitude control. Individually tuned coils. Constant RF output impedance. Stepped RF attenuator. Variable percentage of modulation. Model 700 . . . \$55.90

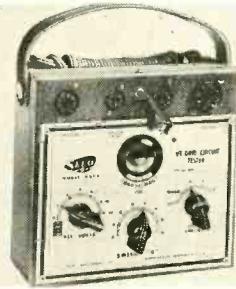

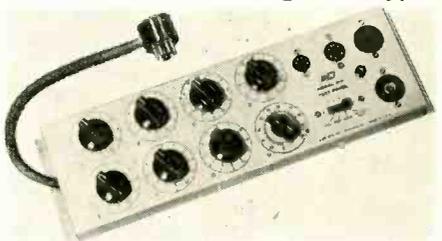Metal case with exposed panel (GCT-9S) or portable carrying case (GCT-9W). $6\frac{1}{2}$ x $6\frac{1}{2}$ x $2\frac{1}{2}$ inches.—Seco Electronics, Inc., 5015 Penn Ave. S., Minneapolis, Minn.




Completely wired.—B&K Manufacturing Co., 1801 W. Belle Plaine, Chicago 13, Ill.


RESISTOR-CAPACITOR TESTER, model 311 Lab-type bridge circuit. 4 capacitance ranges from 10 μf to 1,500 μf . 4 resistance ranges from 1 ohm to

Model 205 Tube Tester

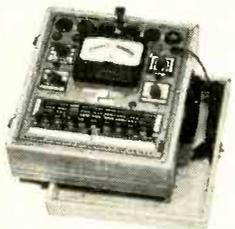
Uses standard emission test. Tests all tubes including Noval and subminiatures. Completely flexible switching arrangement. Checks for shorts, leakages and opens. Model 205P, Hand rubbed oak carrying case, \$47.50 (illustrated). Kit, \$36.20. Model CRA, Cathode ray tube adaptor, \$4.50.



Model 104 Volometer
Features a $4\frac{1}{2}$ " 50 microampere meter, with 3 AC current ranges and 3 resistance ranges to 20 megohms. Specifications . . . DC Voltage: 5 ranges (20,000 ohms per volt); 0 to 6-60-300-600-3000 volts. AC Voltage: 5 ranges (1,000 ohms per volt); 0 to 6-60-300-600-3000 volts. DC Current—3 Ranges: 0 to 6-60-600 ma. AC Current—3 Ranges: 0 to 30-300 ma. 0 to 3 amps. 3 Resistance Ranges: 0 to 20k, 0 to 200k, 0 to 20 megs. 5 DB Ranges—4 to +67 DB. Model 104, with carrying strap. Wt. 2 lbs. 5 oz. Size: $5\frac{1}{4}$ " x $6\frac{3}{4}$ " x $2\frac{1}{4}$ ". \$26.95. Kit, \$19.95. Model HVT, 30,000 volt probe for Model 104, \$7.95.

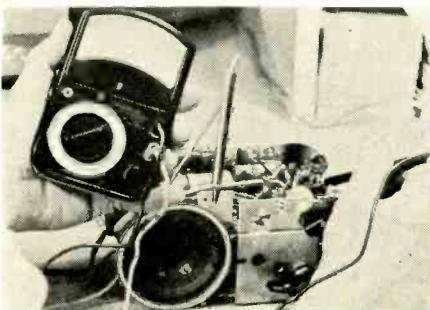

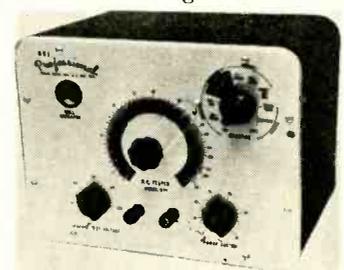POCKET METER. Serves as ohmmeter, decibel meter, dc micro- or milliammeter, and dc and ac rms voltmeter. Also reads inductance, capacitance and relative signal output. Pair of test




Yes, tell me more, send me FREE a detailed catalog of the Complete EMC Line. Dept. RE-126

NAME _____
STREET _____
CITY _____ STATE _____

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Ex. Dept., Pan-Mar Corp., 1270 B'way, New York 1, N. Y.

150 megohms. Fully variable dc voltage up to 450. 1% precision resistors. 5% capacitors. 6E5 null indicator tube. Kit or assembled.—National Radio Institute, 3939 Wisconsin Ave., Washington 16, D. C. Request *Circular SD151*.

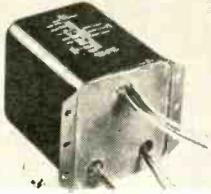OUTPUT TRANSFORMERS, 65-watt high-fidelity, *BO-15* (shown). Use with 6550, EL34 or KT88's for 40- or 60-watt hi-fi amplifier with tertiary feedback construction. Total harmonic distortion less than ± 1 db 20 to 10,000




cycles; 1 db 20 to 20,000 cycles power response. Request *Bulletin CT-47*. *VO-110*, *VO-111* and *VO-112*: Isolation types with turns ratios of 16:1, 18:1 and 8:1. 18,000-, 20,000- and 7,000-ohm primary impedance. *OV-113*: autoformer type with turns ratio of 15:1 and 13,000-ohm primary impedance. Request *Bulletin 571*.—Chicago Standard Transformer Corp., 3501 Addison, Chicago 18, Ill.

AXIAL LEAD RESISTORS. 3-, 5-, 7-, 10-, 15- and 20-watt. Resistance range from 0.24 to 6,200 ohms. Standard tolerances of $\pm 5\%$ and $\pm 10\%$.




Fireproof. Heavy-duty precision crimp termination.—International Resistance Co., 401 N. Broad St., Philadelphia 8, Pa.

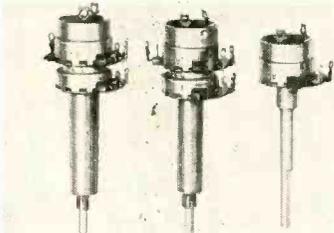AUTO-RADIO-CONTROL REPLACEMENTS. *A/U-1* and *A/U-2* for



Automatic Universal radios used in 31 lines of foreign autos; *A/U-3* for 1957, 1958 and 1959 Fords.—Centralab Div. of Globe-Union, Inc., 900 E. Keefe Ave., Milwaukee 1, Wis.

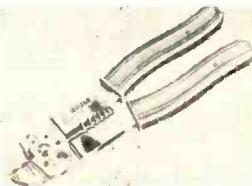CRIMPING TOOL, *CT-3050*. Crimps terminals in wire ranges 22 through 10.



Cuts and strips wire. Shears bolts and screws.—Waldom Electronics, Inc., 4625 W. 53rd St., Chicago 32, Ill.

ATR TUBE PROTECTOR. Use with



This Christmas...
ask for
Weller®
TOOLS

They'll do a complete job
on radio and hi-fi building

FOR STRONG, NOISE-FREE CONNECTIONS...

Dual Heat Soldering Gun Kit

Features the tool that's indispensable in electronic soldering and the favorite of service technicians... the new Weller Dual Heat Gun. Heat and spotlight come on instantly, and 2 trigger positions give 2 soldering temperatures. Switches instantly to low 90-watt or high 125-watt heat as your job requires. High efficiency, long life tip gets into tight spots. Cleaning brush, soldering aid, solder included.



MODEL
8200K
\$795

FOR FINISHING CABINETS, SPEAKER MOUNTS

Weller Power Sander




Sands wood smooth in a jiffy with big 25 sq. in. sanding area and 14,400 strokes a minute. Assorted sandpaper, polishing cloth included.

MODEL 700
\$1348

Available at Electronic Parts Distributors **WELLER ELECTRIC CORP., EASTON, PA.**

ORDER YOUR ENCLOSURE KITS FROM HOMEWOOD

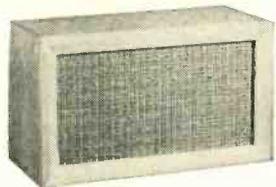
Bring out the best in your speakers... save dollars in assembly and finishing costs... get the fun of "doing-it-yourself"!



ONLY **\$11.95**

MODEL 6

Factory assembled, ready for finishing. Makes your 8" speaker sound like a million! Made of 1/2" hardwood ply, beautifully grained and smoothly sanded. 10" h. x 16" w. x 9" d. 9 lbs. Order two for matched stereo performance.

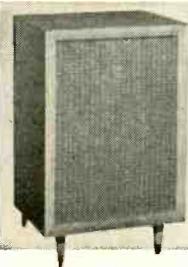

MODEL 1

4 1/2 cubic feet of baffle space assures you crispest, cleanest bass response from any 12" speaker system. Full-grained white birch ply, with pre-attached bracing cleats for easy assembly. Kit includes everything you need for assembly. 29" h. x 20" w. x 12 1/2" d. (5" legs), 25 lbs. \$18.95

MODEL 2

Clear-grained on four sides for bookshelf or floor use. Acoustically accurate for 12" systems, with adapter board for 8" speakers. Sturdy, 3/4" ply eliminates unwanted resonances, improves bass response. 14" h. x 21" w. x 11 3/4" d. 20 lbs.

In Birch, \$14.50
In Walnut, \$19.95

MODEL 13. Finishing kit; includes generous quantities of everything you need to do a professional, long-lasting finishing job, plus brush, sandpaper and easy-to-follow instructions. Specify: Mahogany, Walnut, Blonde, Oak, Fruitwood, Maple, Cherry, Ebony, Natural. \$3.88

Ten-day money-back guarantee. All items shipped freight collect. Please send check or M.O. (No COD's)

HOMWOOD INDUSTRIES, Inc.

26A Court Street, Brooklyn 1, N.Y.

Please send me:

- () Model 6 () Model 1 () Model 2 (Birch) (Walnut)
() Model 13
() Homewood catalog

I enclose remittance in the amount of \$ _____


Name _____

Address _____

City _____ Zone _____ State _____

Something every **TAPE RECORDER OWNER** would like for Christmas

SWITCHCRAFT®
"Mini-Mix"

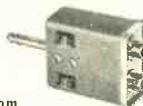

from **\$7.95**

MIXES 2 SOUND SOURCES



(1) Voice with record or radio. (2) 2 Mics in different places. (3) Instrument with background music. No technical knowledge necessary.

Built-in volume control for each sound source. Ask for free reference guide No. 236 to select proper "Mini-Mix."

4 CHANNEL MIXERS

Add to the enjoyment and versatility of Recorders. User can blend or fade out signals for professional type recordings.

Monophonic type permits mixing up to 4 sound sources from TV, Radio, Phonograph or Microphones to one input of Recorder. Stereo type provides for Stereo music accompaniment to narration of home movies, etc.



See your Hi-Fi specialist or write for name of dealer nearest you.

SWITCHCRAFT® 5579 N. Elston Ave.
Chicago 30, Illinois

CITIZEN BAND KIT SALE

We're closing out our large stock of Citizen Band Transceiver Kits. These were nationally advertised at \$39.95. All Kits complete with cabinet, tubes, parts, crystal, FCC form, Instructions, less mike. All sales final.

110 VOLT TRANSCEIVER KITS.....\$19.95

12 VOLT TRANSCEIVER KITS.....\$22.95

6 VOLT TRANSCEIVER KITS.....\$22.95

FAMOUS MAKE CITIZEN BAND

XMTG CRYSTALS.....\$1.99

3 ELEMENT CB BEAM ANTENNA.....\$11.99


Send for our Citizen Band Sale Flyer. Loads of Values! Sorry, no C.O.D.'s. Incl. Postage. Shpg. Weight —15 lbs.

GROVE ELECTRONICS, Dept. RE.
4078 Milwaukee Ave. Chicago 41, Illinois

Please mention **RADIO-ELECTRONICS** when answering advertisements


any equipment having 100 to 300-watt input. Golden - brown hammerloid - finished metal case.—American Television & Radio Co., St. Paul 1, Minn.

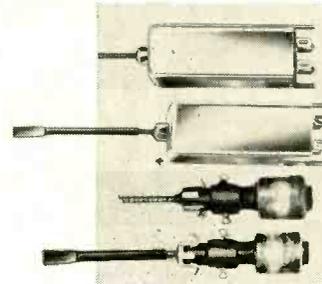REPAIR SHAFTS for repair without coil replacement. Coils with broken




studs on top in photo, repaired studs below. 6 sizes.—Superex Electronics Corp., 4 Radford Pl., Yonkers, N. Y.

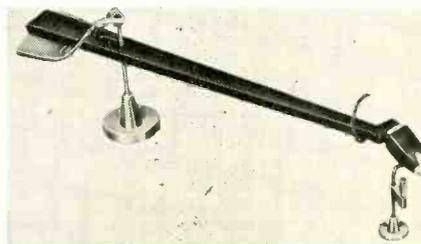TONE ARM, Unipoise model 198 with integrated Stereo Fluxvalve cartridge. Flat response within 2 db 20 to 15,000 cycles. 15-mv output per channel. 35-db



channel separation. 2 to 5 grams tracking force. Mounts on 15 1/2 x 15 1/2-inch motorboard. 6 oz.—Pickering & Co., Inc., Sunnyside Blvd., Plainview, N. Y.

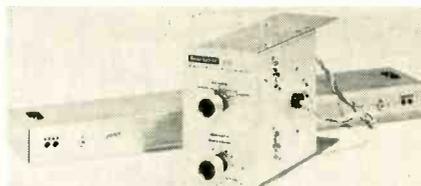REVERBERATION COMPONENT, Reverbatron. Combination reverberation and echo unit. Compatible with basic



amplifiers. Electronics portion selects function and percentage intensity. Mechanical portion uses 2 delay lines of discrete pitch driven by 2 ferrite rotors controlled by electronic part.—Sargent-Rayment Co., 4926 E. 12th St., Oakland 1, Calif.

PROJECTOR, cone type, DC-5. 5-inch-diameter cone speaker. Low-frequency response to 120 cycles. Bracket



swivels horizontally or vertically. Adapter strap for electrical fitting or direct wall or ceiling mounting. 7-inch bell diameter; 14-inch overall length.—Atlas Sound Corp., 1449 39th St. Brooklyn 18, N. Y.

EXTENSION SPEAKER SYSTEM, wall mounting, PT-2. 3 inches deep. 6 x 9-inch inverted woofer, 3 x 5 inch tweeter, bass relief port. 8-watt power handling. 8-ohm impedance. Use as second speaker in monaural or stereo sys-




FREE Catalog Of The **WORLD'S** FINEST **GOV'T** SURPLUS **ELECTRONIC BARGAINS**

AUTOMATIC CONTROL UNIT

• Industrial • Electronic Autotune • Railroadings
115 V 60 cycle 1/100 HP capacitor type motor with automatic gear and ratchet assy. to pre-set motor stops at any 10 positions within 360 degrees. Unit geared to 2 deck 12 position ceramic wafer switch that terminates into a plug-in socket. Local control panel has channel position selector, light dimmer control, & switch for local or remote operation. Part of RDZ-1 Trans. Autotune Assy. Collins #596A-1. Size: 9 x 4 x 6". Stock No. RE-23491— **\$14.95**
Price: NEW



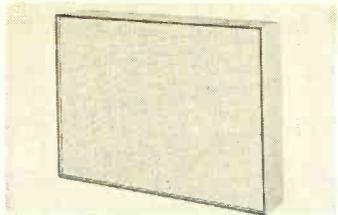FAIR RADIO SALES
2133 ELIDA RD. • P.O. Box 1105 • LIMA, OHIO




tem. Blonde or mahogany.—Utah Radio & Electronic Corp., 1124 E. Franklin St., Huntington, Ind.

SPEAKER ENCLOSURE, model 8. Accommodates 12-inch speaker, adapter for 8-inch. Factory-installed acoustic damping material. Unfinished birch



veneer, full-face grille cloth, 5-inch flared legs. 18 x 29½ x 17 inches.—Homewood Industries, 26 Court St., Brooklyn 1, N. Y.

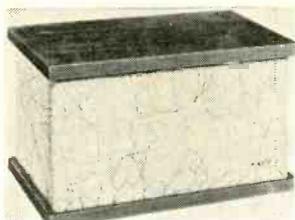BOOKSHELF LOUDSPEAKER, L-1. Mounts vertically or horizontally. 50 to



14,000 cycles. Speaker impedance 4-8 ohms. Handles 16 watts. Unfinished walnut ready to oil. 15¼ x 9¼ x 8½ inches.—Paco, 70-31 84th St., Glendale 27, N. Y.

TURNTABLE AND ARM, Troubadour. 3-speed mono-stereo. Satin gold



or chrome finish. Matching walnut base.—Dyna-Empire, Inc., 1075 Stewart Ave., Garden City, N. Y.

TAPE TRANSPORT, Collaro Studio. 3-speed. 3-motor. 1½, 3¾ and 7½ ips. ¼-track stereo-monoaural recording and




reproduction. Up to 7-inch reels.—Rock-

yes

STANCOR[®]

has a complete line of
RF-IF COILS

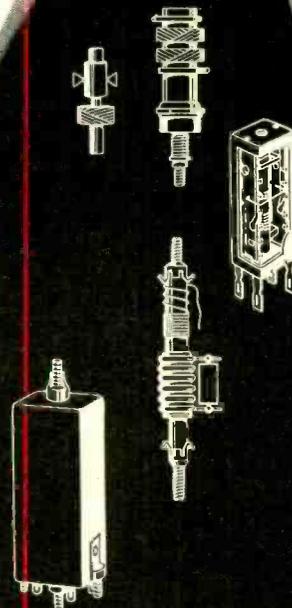The Stancor name is a synonym for quality and dependability. Just as you rely on Stancor for the best in exact replacement flybacks and yokes, so you can expect the highest standard of performance from Stancor coils. Your parts distributor has them in stock.



CHICAGO STANDARD TRANSFORMER CORPORATION

3501 ADDISON STREET

CHICAGO 18, ILLINOIS

**ANOTHER
Mercury
SERVICE AID**

CONVERT YOUR TUBE TESTER INTO A HIGHLY EFFICIENT PICTURE TUBE TESTER . . .



No other CRT Adapter does as much as the MULTI-HEAD!

- ✓ TEST **ALL** BLACK AND WHITE PICTURE TUBES
- ✓ TEST **ALL** COLOR PICTURE TUBES

The MULTI-HEAD incorporates:

- 12-pin socket—for all standard base black and white tubes
- 8-pin socket—for all 110 degree narrow-neck RCA type tubes
- 7-pin socket—for all 110 degree narrow-neck Philco and Sylvania type tubes
- 14-pin socket—for all color TV tubes in use today
- Color gun switch—for checking the red, green and blue color guns separately

See your electronics parts distributor

Model MH-1 MULTI-HEAD **\$12.45** Net

MERCURY ELECTRONICS CORP.

77 SEARING AVENUE, MINEOLA, NEW YORK
West Coast Office: 4306 W. Victory Blvd., Burbank, Calif.

**COYNE offers
LOW COST
TELEVISION**

Training in
Spare Time **AT HOME**

The future is **YOURS** in
**TELEVISION—RADIO
COLOR TV!**

A fabulous field—good pay—fascinating work—a prosperous future! Good jobs, or independence in your own business!



Coyne brings you **MODERN—QUALITY** Television Home Training; training designed to meet Coyne standards. Includes **RADIO, UHF and COLOR TV.** No previous experience needed. Practical Job Guides to show you how to do actual servicing jobs—make money early in course. You pay only for your training, no costly "put together kits."

Send coupon or write to address below for **FREE Book**

and full details including easy Payment Plan. No obligation, no salesman will call.



B. W. Cooke, Jr., President

Coyne—the Institution behind this training... the largest, oldest, best equipped residential school of its kind now in its new home pictured here... Founded 1899.

**COYNE
ELECTRICAL SCHOOL**


1501 W. Congress Pkwy., Chicago, Dept. 90-H5
Chartered as an Educational Institution
Not For Profit

COYNE Television, Home Training Division
Dept. 90-H5—New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.
Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name _____
Address _____
City _____ State _____
(It is understood no salesman will call)


bar Corp., 650 Halstead Ave., Mamaronck, N. Y.

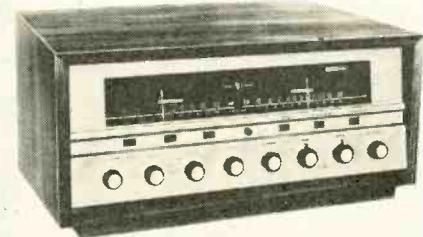STEREO AM-FM RECEIVER, Festival II, model TA 260. 18 to 40,000 cycles. 60-watt stereo amplifier (120-watt peaks). Separate AM and FM sections. Dual preamp. 2 magnetic inputs. Headphone receptacle. Third-channel amplifier output. Brushed gold and charcoal




brown.—Harman-Kardon, Inc., Ames Court, Plainview, N. Y.

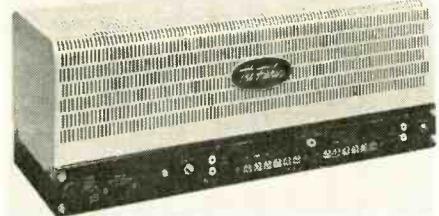STEREO AMPLIFIER, SA-300-B. 45 watts music power per channel. 35 watts per channel rms. Connections for 4-, 8- and 16-ohm speakers. Terminals for adding resistor to match speaker's recommended damping factor. Center channel



output jack for connection of third amplifier and speaker to unit. Two input jacks for each channel, with uniform frequency and controlled frequency response when using electrostatic speakers. Brushed-brass, slotted cage 16 5/8 x 7 1/4 x 6 3/8 inches. 32 lbs.—Fisher Radio Corp., 21-21 44th Dr., Long Island City 1, N. Y.

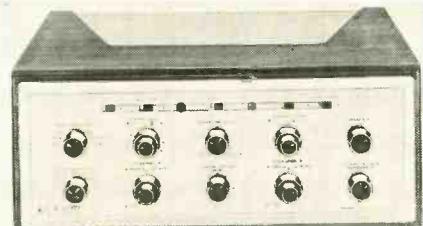STEREO AMPLIFIER model 272. 88 watts output. Binaural rumble suppressor. Center channel, phone and acoustic




level controls. 14-lb output transformers with EL34 output tubes. 47 lbs total weight.—H. H. Scott, Inc., Dept. P, 111 Powdermill Road, Maynard, Mass.

STEREO TUNER KIT, AJ-30. 3 printed-circuit boards. Wired, pre-aligned 3-tube tuned cascode FM tuning unit. Pre-aligned if transformers and coils. Balanced 300-ohm FM antenna input and built-in AM rod antenna. Bal-



anced push-pull germanium diode detector. Delayed, amplified avc. Lug-gage-tan vinyl covering over all-steel cabinet with polished anodized aluminum trim.—Heath Co., Benton Harbor, Mich.

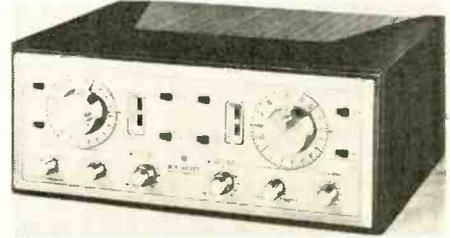STEREO TUNER/AMPLIFIER COMBINATION, 399. 2 preamplifiers




and 2 20-watt power amplifiers, AM and FM tuners on one copper-bonded aluminum chassis.—H. H. Scott, Inc., Dept. P, 111 Powdermill Rd., Maynard, Mass.

FM TUNER KIT, KT-650. Low-noise front end with triode mixer plus double-tuned dual limiters and wide-band Foster-Seeley discriminator. Sensitivity 2 μ v for 30-db quieting. Plate-follower outputs for use up to 50 feet from amplifier. $\pm 1/2$ -db from 15 to 35,000 cycles with standard 75-sec de-emphasis network. Variable afc control. Electronic bar tuning indicator tube. Front-panel



tuner level control. 14 x 5 1/2 x 11 inches.—Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

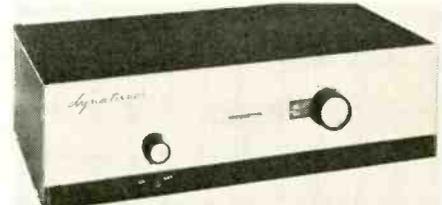FM TUNER KIT, Dynatuner. Etched-circuit design. Sensitivity 4 μ v. Broad-



band, bridge-balanced discriminator. Less than 0.25% IM distortion. Planetary drive system for tuning capacitor.—Dynaco, Inc., 3912 Powelton Ave., Philadelphia 4, Pa.

CHASSIS PUNCH SET makes 6 sizes of holes—1/8, 1/4, 3/8, 1/2 and 5/8 inch.



Drill 1/4-inch pilot hole, insert pilot rod, assemble punch, hit it with hammer and get smooth hole that needs no filing.—Punches, Box 415, Toledo 1, Ohio. END

All specifications are from manufacturers' data.

the only one of its kind!



NOW . . . THE *First* ANALYZER DESIGNED EXCLUSIVELY FOR TESTING TRANSISTOR CIRCUIT CAPACITORS!

SPRAGUE MODEL TCA-1 TRANSFARAD*

THERE'S NOTHING LIKE IT ON THE MARKET ANYWHERE . . . AT ANY PRICE!

Here, for the first time, is a precision-made instrument which is specifically designed to *safely* test low-voltage aluminum and tantalum electrolytic capacitors, film and paper capacitors, and ceramic capacitors. *No laboratory or shop working with transistor circuit capacitors can afford to be without one!*

CAPACITANCE BRIDGE: $1\mu\text{f}$ to $2,000\mu\text{f}$ in five overlapping ranges, with laboratory accuracy.

INSULATION RESISTANCE: 50 megohms to 20,000 megohms. Only 25v d-c is applied, permitting measurements on low-voltage ceramic, paper, mica, and film capacitors. For ceramics rated below 25 volts, IR may be calculated from leakage current measurements at exact rated voltage.

POWER FACTOR: Measured by Wien Bridge from 0 to 50%.

LEAKAGE CURRENT: $0.6\mu\text{a}$ to $600\mu\text{a}$ in 7 ranges. Measured directly on meter at exact rated d-c voltage of capacitor. No guessing on eye-width or counting lamp blinks!

A-C BRIDGE VOLTAGE: Only 0.5v is applied to the bridge. The voltage across the capacitor is less than this applied voltage, the amplitude depending upon capacitance being measured. No danger of overheating and ruining even a 1-volt electrolytic or a 3-volt ceramic.

POLARIZING VOLTAGE: Continuously adjustable, 0 to 150v.

STABILITY: Dual regulation of the power supply assures short-time reliability, while specially processed etched circuits and complete encapsulation of the critical meter amplifier insure long-time stability.

MAGIC-EYE TUBE: Simplifies bridge balancing for capacitance and power factor measurements.

HIGH GAIN AMPLIFIER: Sensitivity control for magic-eye null detector permits accurate measurements of small capacitances.

CAPACITANCE DIAL: Latest design jet black dial with brilliant white calibrations for quick, accurate readings from any position.

BINDING POSTS: Shielded for protection against pick-up of strays, assuring greater accuracy during low-capacitance measurements. 5-way connection feature for use with all types of test leads.

SAFETY DEVICES: Automatic discharge of capacitor after testing. Three-wire line cord grounds instrument case.

OPERATING PROCEDURES: Easy-to-follow operating procedures clearly shown on pull-out slide at base of instrument. Always handy for ready reference.

MODERN CASE: Handsome grey Hammerloid finish on heavy-gage steel. Measures 8 $\frac{1}{2}$ " high, 14 $\frac{1}{2}$ " wide, 9 $\frac{1}{2}$ " deep. Weighs only 21 pounds.

See the remarkable new TCA-1 TRANSFARAD at your Sprague distributor or write for descriptive folder M-792a to Sprague Products Company, 81 Marshall Street, North Adams, Massachusetts.

ONLY
\$197.50
NET

*Trademark

SPRAGUE®

world's largest capacitor manufacturer

"A Complete Library of PHOTOFACT is a 'must'..

The customer appreciates knowing that all facts about his receiver are available to me, and I appreciate not having to guess or wonder about component values and circuitry throughout the set... Yes, PHOTOFACT users are informed about each and every receiver...and the public has knowledge of this through PEET publicity..."

—Robert L. Gaither
Gaither Radio and TV
Parker, Ariz.



**Service Technicians! YOU EARN MORE...
YOU RATE with the public when you own
the PHOTOFACT® service data library!**

You enjoy maximum earnings as the owner of a complete PHOTOFACT Service Data Library! It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily—EARN MORE, DAY IN AND DAY OUT...*

What's more—as the owner of a complete PHOTOFACT Library, you know your customers' sets *best*. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you.

HOW TO STAY AHEAD...

Yes, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly. (They're eligible for the benefits of membership in PEET, too—see below!)

ONLY \$10 DOWN puts the complete PHOTOFACT Library in your shop—and you have up to 30 months to pay. See your Sams Distributor today, or write to Howard W. Sams

TECHNICIANS'

NEWS

N. Y. PICTURE-TUBE LAW

A new state law that went into effect Oct. 1, 1960, makes the service technician responsible for picture tubes being correctly marked to show whether a tube is new, rebuilt or what. Sale of an unmarked or falsely marked tube and carton is a violation of the law.

The new law requires:

Only tubes using all new parts and new glass can be represented directly or indirectly as new.

The picture tube and its carton must be labeled to show the true quality or condition of the tube.

The marking on the tube may be removed only by the purchaser after the tube has been purchased.

TV technicians must furnish a written statement to the customer stating the true quality or condition of the tube furnished to the customer, even though the tube is marked as required by law.

ANTI-LICENSING SUIT

A group of 12 service dealers and four employees of service dealers have filed a suit against the new Kansas City, Mo., TV servicing licensing law. They claim that the new ordinance is unconstitutional.

Those who brought the suit to court say that law deprives service dealers of their liberty and property without due process of law and denies them equal protection of the law. They go on to point out that the ordinance does not require a license for persons who service other appliances and consumer products. The complaint also charges that the licensing board, which is made up with a majority of service dealers, has the power to prevent potential competitors from getting a license, thus keeping them from becoming competitors.

MEETING OF MINDS

Mauro E. Schifino, president of the National Distributors Association, and Frank J. Moch, executive director of the National Alliance of Television & Electronic Service Associations, met in Chicago for an informal discussion. They exchanged views on common problems and expect the exchange "to go a long way toward contributing to the welfare and achieving the mutual objectives of all segments of the industry."

Also at the meeting were Col. Gail S. Carter, executive vice president of NEDA; Lewis G. Groebe of Sherwood and Groebe as legal council, and S. I. Neiman of the Electronics Information Bureau as public relations consultant. Schifino and Moch said, "We con-

NOW IS THE TIME TO JOIN



THE POWERFUL NEW PROGRAM FOR QUALIFIED TECHNICIANS

If you now own a PHOTOFACT Library or plan to own one, you can apply for membership in "PEET." It's the first industry program really designed to build powerful public acceptance for the Service Technician who qualifies. Builds enviable prestige and business for its members. Benefits cost you absolutely nothing if you qualify. Ask your Sams Distributor for the "PEET" details, or mail coupon today.

HOWARD W. SAMS & CO., INC.

1726 E. 38th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program.
- Send full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm interested in a Standing Order Subscription.
 - I'm a Service Technician full-time; part-time

My distributor is _____

Shop Name _____

Attn: _____

Address _____

City _____ Zone _____ State _____

cluded that the most effective and direct method of arriving at a clear understanding of each other's problems was to hold this informal talk, following which we could make concrete suggestions to all interested sections of the industry which may enlarge the scope of such talks and formalize them into larger and more comprehensive meetings." They added that a plan for such meetings will be presented to the industry after each has had an opportunity to report to his respective organization.

TECHNICAL TRAINING SESSIONS

Again this year, Westinghouse is holding technical training sessions for television service technicians, on their 1961 line of TV receivers. Sessions will be conducted by distributor specialists trained by the Television-Radio div. service department.

These sessions are open to all service technicians, and they are advised to get in touch with their nearest Westinghouse distributor to get full information on meetings to be held in their area.

At the end of the session, each technician will be given a *Service Training Manual* and a *1961 Pocket Master*—a compact reference source that includes schematics and service data for TV, hi-fi and radio.

PROFITS IN INDUSTRIAL SERVICE

An important sidelight of the annual convention of the National Alliance of Television & Electronic Service Associations is the way in which industrial electronic service was pushed.

Robert B. Sampson of RCA's Tube Div. told TV service technicians to get out of their radio-TV straight-jacket and make more money, implying that it is time that the TV technician branch out into the industrial field where there is distinct shortage of qualified men.

BOOST FOR LICENSING

Currently, the North Carolina Federation of Electronic Associations is licensing qualified members. To aid this program, the North Carolina Department of Instruction has agreed to help the federation. Classes will be conducted under the supervision of the local school system and will be open only to those who are employed as full-time service technicians. The classes are intended to give the service technician the opportunity to qualify himself for the federation license.

THOUGHTS FOR SET DISTRIBUTORS

Why not set up a "will call" department for those professional people who value their time and want to restore your brand of set for the owners as quickly as possible at the lowest cost? Why penalize them by wasting their time while your parts men handle the service and the public who don't know what they really want?

Why don't you realize you have far more to gain than lose by getting out of

retail service? You have no legitimate excuse to be in that field, and you are, in many cases, in unfair competition with your dealers and the sincere professional service people.

Why not set up a sensible "warranty part" exchange setup, that does not eventually in most cases cost the purchaser of your brand far more than the value of the parts?

Why not give a special discount to those in the trade who order parts by proper part number to expedite handling?—(From *The Word* published for TESA—Chicago.)

WANT SERVICE LICENSE BILL

Harrisburg, Pa., was the scene of a meeting by the Federation of Radio-Television Service Associations, called to complete plans for promoting the electronics service license bill which comes before the 1961 Pennsylvania legislature.

All factions of the service industry were invited to attend and discuss the issues of captive and factory service, do-it-yourself tube testers, bait and unethical advertising, and wholesale-retail sales by parts distributors.

CORRESPONDENCE COURSE

Electronic technicians who are interested in getting an FCC communications license will be interested in a new home-study course being offered by Raytheon. It consists of 24 lessons intended to give the technician enough technical background to enable him to pass FCC examinations for communications licenses. After obtaining such a license, the technician can service Citizens and commercial radio transmitters.

Those applying for the course will be given a preliminary test to determine whether they have the background to enable them to complete the course.

IMPORTS CUTTING INCOME

Low cost of electronic imports has cut into the technician's income, according to David Krantz, active for many years in service associations. Mr. Krantz said, "the most damaging blow to the growth of independent service" has been the tremendous number of imported radios on the market and their prices. A major portion of a recent meeting of the Television Service Association of Delaware Valley was spent in trying to work out a solution.

Many technicians are complaining that customers are abandoning defective radios in service shops or letting them "rot" at home and replacing them with a newer model, since repairs based on American replacement parts and American wage scales would be impractical. The customer has been taught to look for price as the major selling point, not quality.

Mr. Krantz went on to say: "What we fear more than anything else, however, is that American manufacturers are going to have to produce more and more cheap radio and TV sets to compete effectively."

"If this condition arises, the entire independent service industry may be-

NEW IMPORTANT SAMS BOOKS

ALL ABOUT TV FRONT ENDS

Servicing TV Tuners

by Jess E. Dines



Here, at last, is the much-needed, complete and authoritative book on TV Tuners! This single book incorporates everything you need to know to be an expert at servicing the difficult TV front-end. Covers tuner circuitry right down to the smallest detail; describes the mechanical and electrical

characteristics of practically every type of tuner made. Complete sections are devoted to fundamentals, construction, replacement, repair, alignment and servicing. It's the kind of time-saving, truly helpful book every service technician should have at his bench. **\$4.95**
272 pages; 5½ x 8½". Only

HOW TO GET HIGHER QUALITY HI-FI

All About Crossover Networks



by Howard M. Tremaine

The author of "The Audio Cyclopaedia" tells you in this new book (the only one on the subject) how to get the highest possible reproducing quality from a hi-fi system. Explains in detail the theory and design of crossover networks, shows you how to determine their frequencies and actually tells how to build as well as test crossover networks. Handy charts and tables make it easy to compute component values. This book is your best source of valuable information on this little-understood but highly important subject. Valuable for the hi-fi serviceman, audiophile and hobbyist. **\$7.50**
80 pages; 5½ x 8½". Only

JUST OUT—NEW VOLUME 11!

Auto Radio Manual



Keeps you right up-to-date on auto radio repairs. Contains complete PHOTOFACT® coverage on 47 popular auto radio models produced in 1959 and 1960, including these makes: Allstate, American Motors, ATR, Automatic, Buick, Ford, International, Mercury, Mopar, Motorola, Oldsmobile, Pontiac, Riverside, and Stromberg-Carlson. Includes alignment information, comprehensive schematics, parts lists and every bit of useful data you need to help you service auto radios faster and more profitably. 160 pages; 8½ x 11". Only **\$2.95**

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. M-20 1720 E. 38th St., Indianapolis 6, Ind.

Send me the following books:

- "Servicing TV Tuners" (STD-1)
 "All About Crossover Networks" (CNT-1)
 "Auto Radio Manual" Vol. 11 (AR-11)

\$.....enclosed. Send Free Book List

Name.....

Address.....

City..... Zone..... State.....

(Outside U.S.A. priced slightly higher)

RCA KITS

FOR VALUE, QUALITY AND PERFORMANCE!



RCA WV-38A (K) VOLT-OHM-MILLIAMETER

only **\$29.95*** (includes batteries, probe and cable with slip-on alligator clip, ground lead and clip, assembly and operating instructions) (available factory-wired and calibrated—only \$43.95*)

Exclusive features make this RCA VOM kit the buy of a lifetime! Extra 1-volt and 0.25 volt (250 mv) ranges for wider usage in transistor servicing—new handle clip accommodates probes and test leads for extra carrying convenience. Assembles in a breeze!

FEATURING: ohms-divider network fuse-protected • easier-to-read scales • extra-large 5/4 inch meter • polarity reversal switch • excellent frequency response • full-wave bridge rectifier • low circuit loading • standard dbm ranges.

SPECIFICATIONS: Input Resistance—20,000 ohms per volt on DC; 5,000 ohms per volt on AC • Accuracy—± 3% DC, ± 5% AC (full scale) • Regular Scales—2.5, 10, 50, 250, 1000, 5000 volts, AC and DC; 50 μ a 1, 10, 100, 500 ma, 10 amps (DC) • Extra Scales—250 mv. and 1 volt (dc) • Frequency Response—AC-flat from 10 cycles to 50 Kc (usable response at 500 Kc) • Ohms—3 ranges: Rx1—(0-2,000 ohms); Rx100 (0-200,000 ohms); Rx10,000 (0-20,000,000 ohms) • Dimensions—W. 5 1/4", H. 6 7/8", D. 3 1/8"


RCA WO-33A (K) 3-INCH OSCILLOSCOPE

only **\$79.95*** (complete with Low-Cap, Direct Input Probe and Cable) (also available factory-wired and calibrated—only \$129.95*)

The first 'scope kit with "get-up-and-go!" Use it for practically everything—video servicing, audio and ultrasonic equipment, low level audio servicing of pickups, mikes, pre-amps, radios and amplifiers, troubleshooting ham radio, hi-fi equipment, etc.—and you can take it with you, on the job, anywhere!

FEATURING: voltage-calibrated frequency-compensated, 3 to 1 step attenuator • scaled graph screen and calibrating voltage source for direct reading of peak-to-peak voltages • "plus-minus" internal sync... holds sync up to 4.5 Mc • shielded input cable with low capacitance probe included • weighs only 14 pounds • includes built in bracket to hold power cord and cables.

SPECIFICATIONS: Vertical Amplifier (Narrow Band Position)—Sensitivity, 3 rms mv/inch; Bandwidth, within -3 db, 20 cps to 150 Kc • Vertical Amplifier (Wide Band Position)—Sensitivity, 100 rms mv/inch; Bandwidth, within -3db, 5.5 cps to 5.5 Mc • Vertical Input Impedance—At Low-Cap cable input... 10 megohms, 10 μ f (approx.); At Direct-cable input... 1 megohm, 90 μ f (approx.) • Sweep Circuit—Sawtooth Range, 15 cps to 75 Kc; Sync, external, \pm internal; Line Sweep, 160° adjustable phase.

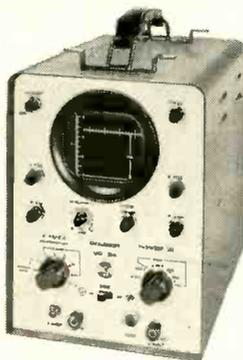

RCA WV-77E (K) VOLT-OHM-MYST®

only **\$29.95*** (also available factory-wired and calibrated only \$43.95*)

Think of it—an RCA VoltOhmMyst Kit at this low, low price! You get famous RCA accuracy and dependability, plus the easiest to assemble kit you've ever seen!

FEATURING: ohms-divider network protected by fuse • ultra-slim probes and flexible leads • sleeve attachment on handle stores probes, leads, power cord • separate 1 1/2 volts rms and 4 volts peak-to-peak scales for accuracy on low ac measurements • front-panel lettering acid-etched.

SPECIFICATIONS: Measures: DC Volts—0.02 volt to 1500 volts in 7 overlapping ranges; AC Volts (RMS)—0.1 volt to 1500 volts in 7 overlapping ranges; AC Volts (peak-to-peak)—0.2 volt to 4000 volts in 7 overlapping ranges; Resistance—from 0.2 ohm to 1000 megohms in 7 overlapping ranges. Zero-center indication for discriminator alignment • Accuracy—± 3% of full scale on dc ranges; ± 5% of full scale on ac ranges • Frequency Response—flat within ± 5%, from 40 cycles to 5 Mc on the 1.5, 5, and 15-volt rms ranges and the 4, 14, and 40-volt peak-to-peak ranges • DC Input Resistance—standard 11 megohms (1 megohm resistor in probe).

*User Price (Optional)



See them all at your local RCA Test Equipment Distributor!
RADIO CORPORATION OF AMERICA
ELECTRON TUBE DIVISION HARRISON, N.J.

come something of the past. We see thoughts in this direction in the way more and more manufacturers are sounding out independent shops to do factory work."

Mr. Krantz said that much of the imported equipment, including radios, television and tape recorders, is tinier than ours and requires more work, time and finer tools. "Coupled with the high cost of American labor, it becomes economically unsound for customers to have the sets repaired. It's cheaper to replace them."

AGAINST CAPTIVE SERVICE

Sell yourself and your service! Refuse to be new-set salesmen! Advise your customers to have their old sets repaired and not to purchase new ones! These are the recommendations the Television Service Association of Delaware Valley is making in its monthly publication, as a part of its fight against captive service.

The association goes on to point out that is only through the combined efforts of all independent service dealers that captive service can be stopped.

LICENSING FOR LOUISIANA

State Bill HB761 now enables all electronic technicians, including those in rural areas and towns under 20,000, to become eligible to operate under the Louisiana TV license law. Until now, only technicians in towns with a population of more than 20,000 were affected.

The bill was apparently supported by almost all groups. This is how it went in the State Legislature:

House committee—passed unanimously

House floor vote—61 to 25

Senate committee—passed unanimously

Senate floor vote—35 to 1

SERVICE GROUP ISSUES LICENSES

To identify qualified service technicians and dealers, the Federation of Radio & Television Associations of Pennsylvania is issuing its own licenses to qualified shops and technicians. The licenses are framed certificates that bear the association's seal and are intended to identify to the public those technicians and shops that are both reputable and qualified to do TV service work. END




new PATENTS

TRANSISTORIZED IGNITION SYSTEM

Patent No. 2,941,119

Gerald M. Ford, Kokomo, Ind. (Assigned to General Motors Corp., Detroit)

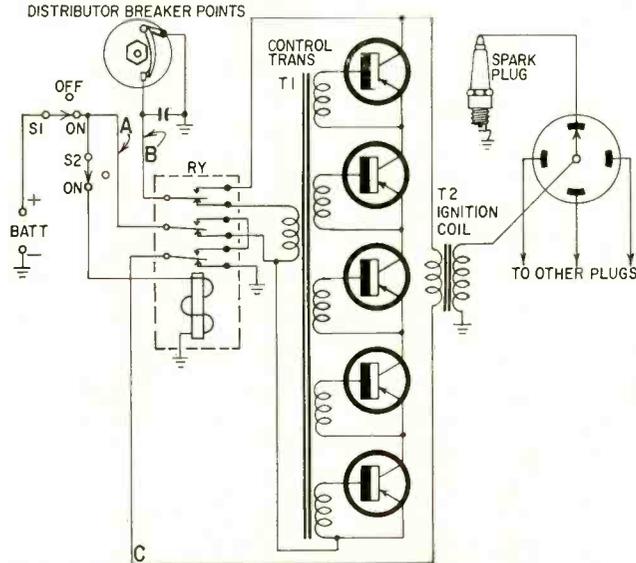This ignition system permits higher stepup electrodes by breaking the current in a low-voltage circuit and minimizes burning of spark-plug



Television RADIO-ELECTRONICS Electricity ELECTRONICS IN NEW SHOP-LABS OF COYNE

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Get practical training in New Shop-Labs of Coyne. Prepare for a better job and a successful future in a top opportunity field. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students.

FREE BOOK Clip coupon or write to address below for Free Illustrated Book, "Guide to Careers"—Describes all training offered. No obligation and *No Salesman Will Call*. Act NOW.


B. W. Cooke, Jr., President
COYNE CHARTERED NOT FOR PROFIT
ELECTRICAL SCHOOL Established 1899
1501 W. Congress Pkwy., Chicago, Dept. 90-5C

COYNE Electrical School
1501 W Congress Pkwy., Chicago 7, Ill.
Dept. 90-5C

Send FREE book "Guide to Careers" and details of all training you offer. However, I am especially interested in:

ELECTRICITY TELEVISION BOTH FIELDS

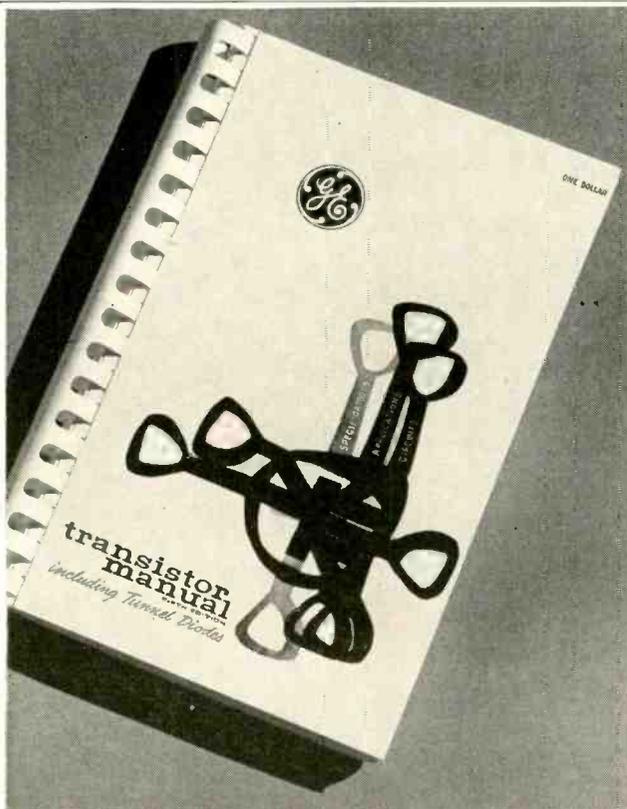NAME.....
ADDRESS.....
CITY.....STATE.....



LEARN TUNNEL DIODE THEORY:

General Electric Transistor Manual

New Fifth Edition of an Industry Classic

These days you hear a lot about the amazing tunnel diode—100 times faster than the fastest transistor. But do you know its basic theory of operation . . . how it performs a feat considered impossible in terms of classical physics?

You will after you've studied the new Fifth Edition of General Electric's famous Transistor Manual— one book that's indispensable for a working knowledge of the transistor field. New material in its 320 fact-filled pages includes tunnel diode switching circuits and amplifiers . . . hi-fi and radio circuits . . . feedback and servo amplifiers . . . silicon controlled rectifiers . . . and complete specs and JEDEC listings.

Get your copy today from your G-E Semiconductor Distributor or by mailing one dollar with the coupon below.

General Electric Company, Semiconductor Products Dept.,
Section S60120, Electronics Park, Syracuse, N. Y.

Rush me the enlarged new 5th Edition of the General Electric Transistor Manual. I enclose \$1.00. (No stamps, please.)

Name.....

Address.....

City.....Zone.....State.....

GENERAL  ELECTRIC

NEW FROM Arkay

Manufacturers of the world famous line of Golden '60 electronic kits

Versatile MULTITESTER KIT

for laboratory, service shop and amateur use




4 1/2" meter (400 microamps movement). Separate scales for AC voltage and current, DC voltage and current, decibels and resistance. Bakelite case. Construction manual, batteries available.

Model M-4 \$13.50

NEW 23" 110° TV TUNER KIT

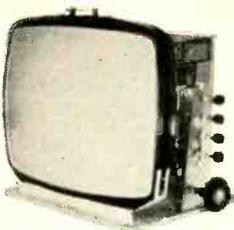WITH STAGE-BY-STAGE ASSEMBLY AND CHECK SYSTEM



Unique ARKAY tuner kit permits checking of each stage as it is finished. Modern slim-line chassis. Five separate controls plus fine tuning ring on channel selector. Clean design, superb performance.

Model 14T23 \$79.95 less C.R.T.

5 tube radio DYNAMIC DEMONSTRATOR

mounted on easy-to-read schematic board



A complete radio education in one project. Consists of a 5 tube super-het radio mounted on a large demonstration board. Clearly illustrates circuitry and the functions of the components.

Model DD5 \$39.95

10 project EXPERIMENTERS KIT



10 PROJECTS ONLY \$13.95

Educational, practical. Build a radio receiver, phono-microphone amplifier, broadcast station, signal tracer, electronic timer, five other projects. Teaches functions of circuitry while you have fun building. With detailed 12 pg. instruction manual.

all prices 5% higher west of the Mississippi

For complete catalogue of ARKAY KITS write today to:

arkay HIGH FIDELITY ELECTRONIC KITS
88-06 Van Wyck Expressway, Richmond Hill 18, N.Y.

S1 is the battery switch. S2 is turned ON for transistorized ignition and OFF for conventional operation. With S2 on, relay RY is energized to attract (downward) its three-gang armature. Current flows through line A, primary of control transformer T1, line B, distributor and ground. The distributor cam makes and breaks the current to induce a high voltage in the secondary of T1. At some critical moment, this biases all transistors to conduction. When the voltage collapses, the transistors are blocked again.

During conduction, the current can be traced through line A, the transistors, primary of ignition transformer T2, line C and ground. A high voltage appears at the spark plug due to induction.


With S2 off, the system becomes a conventional one. RY releases its armature. The only current path is now through line A, line C, primary of T2, distributor and ground.

MICROWAVE OSCILLATOR

Patent No. 2,944,167

Herbert F. Mataré, West End, N. J. (Assigned to Sylvania Electric Prod., Inc., Wilmington, Del.)

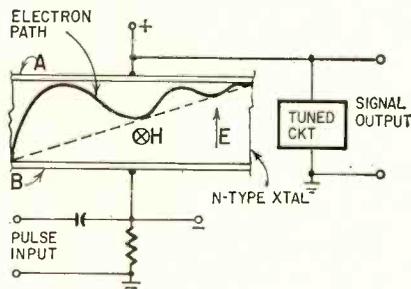This oscillator performs at frequencies as high as 24,000 mc. It consists of an N-type crystal at a very low temperature. An electric field E—developed between plates A and B secured to the crystal—and magnetic field H are applied at right angles. See the diagram, E is upward, H is into plane of paper.



A pulse injects electrons into the semiconductor. These tend to move toward the positive E terminal, as well as to move in clockwise circles around H. A typical electron will miss the

upper plate because of its curved path. E slows it down and finally reverses its direction. Again the electron accelerates and travels clockwise.

The electron gives up energy during acceleration, absorbs energy during deceleration. This energy is transferred to a resonant circuit or cavity tuned to the proper frequency. If a cavity is used, it must be insulated to avoid shorting E. Mica spacers may be used to separate the E terminals from the cavity walls.


SERIES TRANSISTOR AMPLIFIER

Patent No. 2,943,267

Dominick Randise, Ozone Park, N. Y. (Assigned to Sperry Rand Corp., Great Neck, N. Y.)

Transistors connected in series can handle output voltages too high for a single transistor. Thus, if each can carry 10 volts safely, then a series of three can handle a maximum of 30 volts.

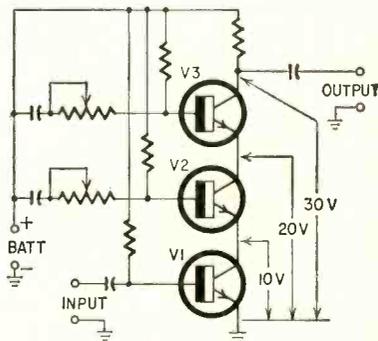V1 is shown as a common-emitter stage. The



others are common-base. Load current flows through them all in series. Knowing the beta of a transistor and its collector flow, its base current and dropping resistor may be calculated.

The input signal should be sufficient to drive V1 to maximum output, in this case 10 volts. V2 should have a gain such that 10 volts between emitter and ground produces 20 volts between collector and ground. A base R-C network controls the gain of this stage. V3 also has a gain-controlling network. END

Ask By Name For GENUINE "NO NOISE" PRODUCTS



NO-NOISE VOLUME CONTROL AND CONTACT RESTORER

- Cleans • Lubricates
- Protects • For Pin-Point Applications
- Not a Carbon Tet Solution

2 oz. Bottle \$1.00
6 oz. Spray Can \$2.25

Net to Servicemen

NO-NOISE TUNER-TONIC with PERMA-FILM

- Cleans, lubricates, restores all tuners, including wafers type.
- Non-toxic, non-inflammable.
- For TV, radio and FM use.
- Economical—a little does a lot.



6 oz. Aerosol Can \$3.25

Net to Servicemen



FREE 5" PLASTIC EXTENDER

- Push Button Assembly
- For Pin-Point Applications
- Does Not Cause Shorts

ELECTRONIC CHEMICAL CORP.

813 Communipaw Avenue Jersey City 4, N. J.

P.S. Be Sure To Ask For NO-NOISE RUBBER COAT 6 oz. Spray Can \$3.25

Purchasing A HI-FI SYSTEM?

TIME PAYMENTS AVAILABLE

Up to 2 years to pay!

Send Us Your List Of Components For A Package Quotation

WE WON'T BE UNDERSOLD!


All merchandise is brand new factory fresh & guaranteed.

Free Hi-Fi Catalog

AIREX RADIO CORPORATION


64-RE Cortlandt St., N.Y. 7, CO 7-2137

Jim Lansing*
Altec Lansing
Electrovoice
Jensen
Hartley • Viking
University
Acoustic Research
Janszen
Wharfedale
USL Citizen Band
Gonset • Hallcrafters
Texas Crystals
Concertone
Bell • G.E.
Weathers
Harman-Kardon
Eico • Pilot
Acrosound
Quad Ampl & Spkrs*
Dual Changer
Bogen • Leak
Dynakit • Fisher
H. H. Scott
Thorens* Sherwood*
Pentron • Roberts
Ampex • DeWald
Sony • Tandberg*
Challenger
Wollensak
Garrard
Miracord
Glaser-Steers
Rek-O-Kut
Components
Norelco
Fairchild
Pickering • Gray
Audio Tape
Magnecord*
Artizan Cabinets
Rockford Cabinets
*Fair Traded

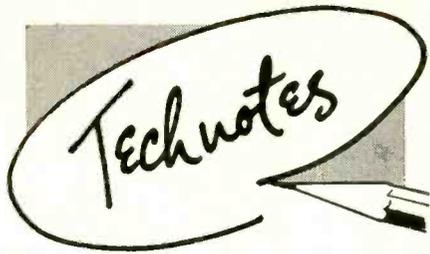

WESTINGHOUSE MODEL H736T17

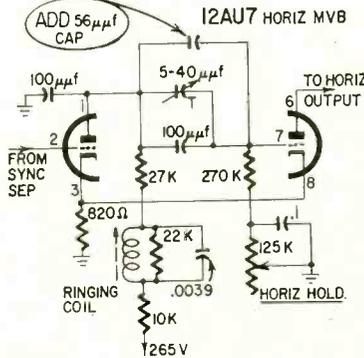The complaint was poor horizontal stability varying with the different channels.



We tried adjusting the trimmer capacitor in the multi-vibrator. Sync improved as it was tightened but we were not able to get enough capacitance variation. So we changed the total capacitance by shunting the trimmer with a 56-µµf ceramic disc capacitor. Then we readjusted the trimmer for best sync on all stations.—*Jack Roberts*

CAR RADIO TROUBLE

Recently I encountered a number of auto radios with power supply trouble only during humid weather. Inspec-

For An
Important
Message
Concerning
Your Career
In Electronics
See Page 75

BECOME A RADIO TECHNICIAN for only \$26.95 BUILD 20 RADIO

CIRCUITS AT HOME

with the New Progressive
RADIO "EDU-KIT"®

Reg. U.S.
Pat. Off.

All Guaranteed to Work!

PRACTICAL only
HOME RADIO COURSE **\$26.95**

NOW INCLUDES

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR



TRAINING ELECTRONICS
TECHNICIANS SINCE 1946

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE
- QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING
- RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS
- ALIGNMENT TOOL • WRENCH SET • CERTIFICATE OF MERIT
- VALUABLE DISCOUNT CARD

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$26.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplifier circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hookup wire, solder, selenium rectifiers, volume controls, switches, knobs, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

UNCONDITIONAL MONEY-BACK GUARANTEE

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc., for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00

- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name.....
Address.....

Progressive "EDU-KITS" Inc. 1186 Broadway, Dept. 171G
Hewlett, N. Y.

BUY PYRAMID! GET MORE!




Only Pyramid offers you so much! Only Pyramid gives you highest quality capacitors plus so many "all new" extras.

THE VU-PAK

An entirely new way to package capacitors . . . clear plastic tubes, plainly labeled and packed with the highest quality electrolytic twist-mount capacitors. Each re-usable Vu-Pak comes with a blank label, ideal for storing small parts and tools on your bench or in your tool kit.

EXTRA OFFER!

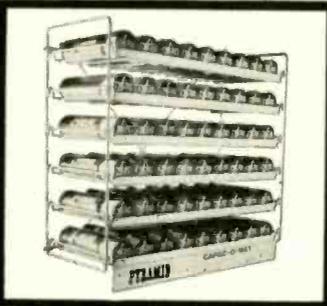Save 50 Vu-Pak labels and get the fabulous new Pyramid storage rack the Capac-o-mat, at tremendous savings from your authorized Pyramid distributor. The Capac-o-mat fits right on your shelf, is dust-free and holds 54 Vu-Paks.



JEWEL BOX


Handsome tan plastic, high impact cabinet with 9 drawers, contains 45 assorted Mylar* paper Gold Dip capacitors, type 151. Practical . . . convenient . . . for storage in your shop, or home. Actual value of the Jewel Box with 45 Gold Dip capacitors—\$19.50, dealer net only \$9.25.



Gold Dip capacitors are also available in Clear-Vu paks . . . 5 to a package. Find them on Pyramid's new Whitl-o-mat on your favorite parts distributor counter.

"GOLD STANDARD" 111 KIT

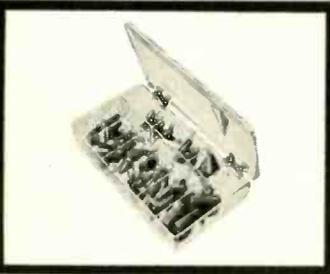Clear lucite hinged box containing 75 Pyramid's popular assorted Gold Standard Mylar* capacitors. You'll find so many uses for the Gold Standard 111 Kit. Actual value is \$26.00, dealer net only \$13.00.



515 LYTIK-KIT

Hinged cover, clear lucite box with 15 assorted miniature low voltage electrolytic capacitors for transistorized circuit replacements, type MLV. This Kit is a constant companion to any busy serviceman. Actual value, \$20.60, dealer net only \$10.30.



PYRAMID ELECTRIC COMPANY

DISTRIBUTOR DIVISION: UNION CITY, NEW JERSEY


Factories: Gastonia, North Carolina • Darlington, South Carolina
In Canada: Wm. Cohen, Limited, 8900 Tanguay Street, Montreal
Export: Morhan Exporting Co., 485 Broadway, New York 13, N. Y.

tion revealed arcing at the base of the vibrator socket, caused by accumulations of dirt and grime. To correct the difficulty and prevent callbacks, I cleaned the bottom of the vibrator socket and sprayed on a coat of anti-corona dope.
—John A. Comstock

ZENITH MODEL 2229

Trouble: Unstable sync, waveforms near normal.

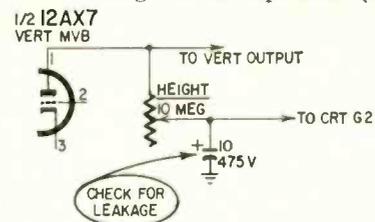Check the boost-voltage filter capacitor (10- μ f 475-volt



unit off the arm of the height control). May be leaky, feeding pulse into sync circuit, cancelling sync at vertical oscillator.—William Porter

SAVE YOKE COILS

Sometimes the inside of a yoke or even a focus coil sticks to the neck of the picture tube. This would never happen, if a coating of light grease were applied to the inside of the coils. The grease forms a film between the coil and the neck of the picture tube and keeps it from sticking.—A. von Zook

RCA T100

Complaint: Buzz in sound when picture control is set for best picture. When age control is set for no buzz, sound is too weak.

Cure: Adjust age for normal picture or turn it all the way up. Then adjust the bottom slug in the sound discriminator transformer for minimum or no buzz. Age control can then be operated at any setting without buzz in sound. Align entire sound section for maximum output.—Harry C. Keller


END

To Learn Some
Vital Facts
About Your
Career
In Electronics
See Page 76

NOTEWORTHY CIRCUITS

NOVEL BCI TRAP

I live about a half block from KFSG, operating on 1150 kc. BCI is so severe that I can't use my radio. A few days ago, I salvaged a two-section permeability tuner from a discarded trf set and connected the coils as interference traps in the cathode returns of the rf amplifier and mixer of an old Hoffman receiver (see diagram). When the tuner's circuits, L1-C1 and L2-C2, were adjusted to 1150 kc, I received several

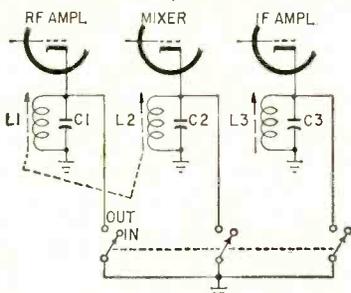

stations without interference. I plan to connect a similar trap (L3-C3) in the if circuit and tune it to the interference if caused by stations on channels adjacent to the one being tuned in. This circuit will have to be retuned for each station received, so I'll probably try an old bfo transformer.—*Nate Silverman*

[If cathode bias is used on any of the stages being trapped, connect the trap (L1-C1, etc.) between the cathode and the bias network.—*Editor*]

RE: NIGHT SWITCH FOR HI-FI


The article "Night Switch for Hi-Fi" in the May, 1959, issue reminded me of a simple modification that I made in my phonograph which featured a SIESTA switch—the ac input to the amplifier was controlled by the automatic shutoff switch on the changer. I don't like this feature as originally installed because by the time that you can get a new stack of records on the changer, the amplifier's tubes are cold. When you start the changer, the arm drops on the record before the tubes have a chance to warm up and you are cheated out of the first few seconds of play.

The diagram (Fig. 1) shows the hookup. When the dpdt switch is in the SIESTA position, one side of the amplifier's power line is completed through the shutoff switch on the changer. After the last record, the switch opens and cuts off the changer and amplifier. The next day, just throw the switch to NORMAL to turn on the amplifier.

NOW IN KIT FORM FOR THE FIRST TIME!

RCA Senior VoltOhmyst® WV-98B (K)

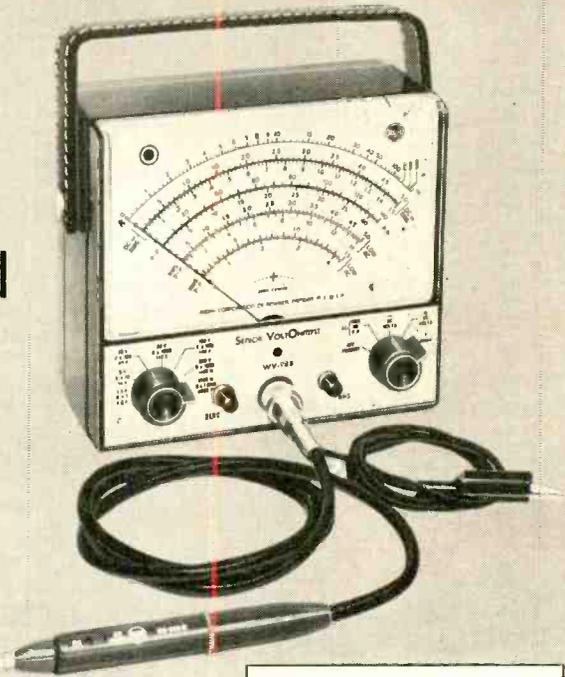with
completely
assembled and
soldered
etched-circuit
board!



SPECIFICATIONS

DC Voltmeter: Ranges—0 to 1.5, 5, 15, 50, 150, 500, 1500 volts
Accuracy— $\pm 3\%$ of full scale
Input Resistance—11 megohms (1 megohm in probe tip)
Sensitivity—7.3 megohms-per-volt on 1.5-volt range
Zero—Center-scale adjustment for discriminator alignment

AC Voltmeter: Ranges—RMS—0 to 1.5, 5, 15, 50, 150, 500, 1500 volts
Peak-to-Peak—0 to 4, 14, 42, 140, 420, 1400, 4200 volts
Accuracy— $\pm 3\%$ of full scale

Ohmmeter: Ranges—0 to 1000 megohms (7 overlapping ranges)
Center-Scale Values—10, 100, 1000, 10,000 ohms; 0.1, 1, 10 megohms

Here's the VTVM deluxe—the famous RCA Senior VoltOhmyst preferred by professionals—brought to you now in easy-to-assemble kit form! All components and leads on the etched-circuit board come to you completely mounted and soldered! The input probe and cable, with built-in DC/AC-Ohms switch, comes completely assembled and wired! Assembly time is cut in half! The etched-circuit board, itself, is 50% thicker to provide extra strength!

The Senior VoltOhmyst measures peak-to-peak voltages of complex wave forms for use in video, sync or deflection circuits—rms values of sine waves—voltages—and resistance. Meter is electronically protected against burnout. Applications for the WV-98B (K) include measurements at audio and radio-broadcast frequencies.

CHECK THESE DELUXE FEATURES

- ✓ Large, easy-to-read meter with expanded scales—6½ inches wide, 26 square inches!
- ✓ 3% accuracy full-scale on both ac and dc measurements.
- ✓ 200-microampere meter movement, with less than 1% tracking error.
- ✓ Precision multiplier resistors with accuracy of 1%.
- ✓ Sturdy single-unit streamlined probe with built-in DC/AC-OHMS switch.
- ✓ Rugged die-cast aluminum case.
- ✓ Rugged construction specially designed for rapid, easy assembly.
- ✓ Leather carrying handle.

For further information, check with your Authorized RCA Electronic Instruments Distributor, or write: Commercial Engineering, RCA Electron Tube Division, Harrison, New Jersey.

all for only
\$62.50*

Complete with pre-assembled WG-299D probe and cable, alligator clip and ground cable. Plus easy-to-follow step-by-step instructions for assembly and operation.

*User price optional



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA

SERVICE MASTER...

**EVERY TOOL YOU NEED
99% OF THE TIME**



complete 23-piece kit for radio, TV,
and electronic service calls

2 HANDLES:
shockproof plastic.
Regular 4" length
... 2" Stubby. Inter-
changeable. Patented
spring holds snap-in
tools firmly in place.

9 NUTDRIVERS:
High Nickel chrome
finish, 3/16" to 1/2"

**3 STUBBY
NUTDRIVERS:**
1/4", 3/8", 1/2"

EXTENSION BLADE:
Adds 7". Fits
both handles.

3 SCREWDRIVERS:
Two slotted ...
3/16", 3/32"
= 1 Phillips

2 REAMERS:
1/8-3/8", 1/4-1/2"

**ADJUSTABLE
WRENCH:**
6" thin pattern,
1" opening

LONG NOSE PLIER:
"Cushion Grip",
2 1/4" nose

DIAGONAL PLIER:
"Cushion Grip",
hand-honed
cutting edges

ROLL UP KIT:
Durable, plastic-
coated canvas.
Compact, easy-
to-carry.

Ask your distributor to show you kit 99 SM

XCELITE

XCELITE, INC. • ORCHARD PARK, N.Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

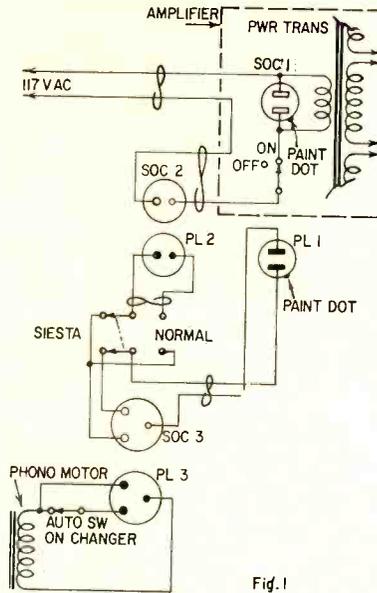


Fig. 1

SOC 1 is an ac receptacle mounted on the back skirt of the amplifier chassis. It and its mating plug PL 1 should be polarized types or must be polarized with dabs of paint. Connectors SOC 2 and PL 2 disconnect the amplifier from the switching circuit. Use a

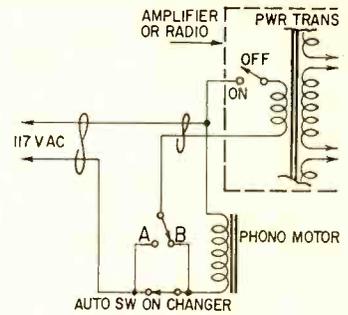


Fig. 2


shorting plug in SOC 2 to restore the amplifier to normal use or when servicing. Connectors SOC 3 and PL 3 are for disconnecting the changer for servicing.—C. L. Van Liew

The Night Switch in the May issue is a good circuit but it may be difficult for a layman to wire without a technician's help. My circuit (Fig. 2) is simpler and does not require a relay or neon lamp. With the switch in position A, the changer's shutoff switch is bypassed and the amplifier or radio is turned on and off with its own switch. Position B shunts the radio or amplifier's ac input across the phono motor so it is switched off after the last record has played.—M. H. Gurbaxani

ONE-TRANSISTOR SUPERHETERODYNE

This circuit was put together just to see if it would work. Selectivity was good, but the set wasn't any better on sensitivity than a well designed one-

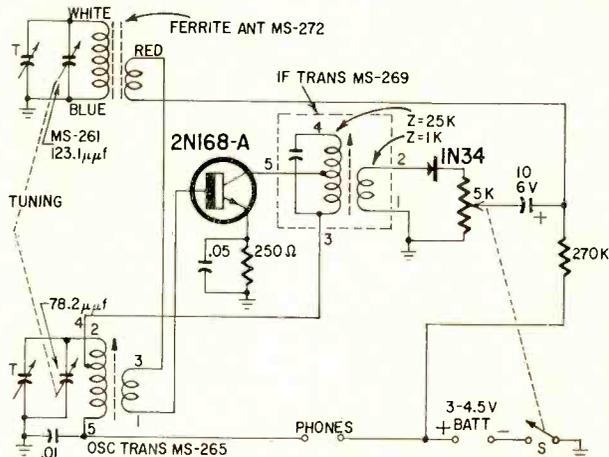bringing this wire out and rewinding the secondary to make two separate windings. Of course, if you can get a ferrite-core antenna that already has



transistor circuit, but it was a superhet and as simple as one could be.

The ferrite-core loop antenna is modified by unwinding the secondary and breaking the connection where it joins the ground end of the primary,


separate primary and secondary windings, you save yourself a job.

The set overloads on two locals, but a resistor from ground end of loop to the chassis, 10,000 to 40,000 ohms, may help.—W. G. Eslick

AM DETECTOR IMPROVEMENT

By changing the connection of the volume control in Leonard E. Geisler's article "Rejuvenation for the AM Detector" (October, 1959), the circuit can be improved. The way it is now arranged, the volume control is floating. If it is connected as shown here, it will act in a much more positive fashion.

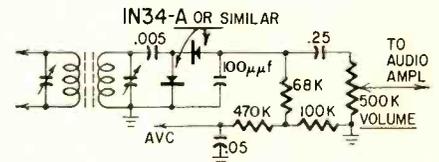
Also note the changed capacitor and resistor values. They will help give improved AVC action in small superheterodyne sets.



Using this detector, you can change the 12SQ7 to a 12SN7 and get an extra if or af stage. If you don't like the 12SN7, try a 12SC7 or a 12AX7.—Leslie A. Moss
END

DX-16 Super Deluxe TV KIT

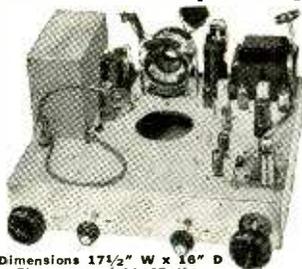70° or 90° — operating all 17", 21", 24" and 27" PICTURE TUBES



Dimensions 17 1/2" W x 16" D
Shipping weight 40 lbs.


- ★ Produces a 16-Tube Chassis with 30-Tube performance.
- ★ Latest Intercarrier Circuitry and Multi-section Tubes.
- ★ Standard Neutrode Tuner for Selectivity & Fine Definition.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Large 250ma Power Transformer for dependable service.
- ★ 12" Speaker or Twin-cone 6" x 9" Speaker.

Includes LIFE-SIZE step-by-step Building Instructions
Most Up-To-Date and Practical Course in Television

COMPLETE KIT
with SET OF WESTINGHOUSE TUBES \$93.49

4-6CB6, 6U8, 6T8, 6C4, 12BH7, 6SN7, 6B06, 6W4, 6K6, 1X2B, 5U4, 6BN3, 6GC8, incl. in the Tuner (less CRT)

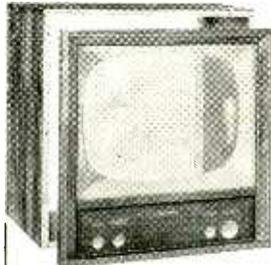Also sold on EASY-PAYMENT-PLAN Buy LIFE-SIZE Instructions—\$2.49—and buy Parts as you build.



23" TV Cabinet Kit . . \$28.47 24" or 27" TV Cabinet Kit . . \$38.47 24" or 27" Front Panel Assembly . . \$24.97

BUILD YOUR OWN CABINET FOR ANY TV CHASSIS

Comparable to the type that Top Mfrs. use on high priced TV sets.

CABINET KIT with 90% of the job done, includes—
FRONT SECTION in Solid Mahogany, Walnut or Blond Korina. TOP, SIDES, BACK, MASK, SAFETY GLASS, ETC.
And EASY-TO-FOLLOW ASSEMBLY INSTRUCTIONS

Front, Top and Sides supplied in a beautiful Piano Finish • Knob panel undrilled • For matching Mask specify type or number of CRT used. Same price—Mahogany, Walnut or Blond. (Shipping weight 36 lbs.)

21" CABINET KIT 26"H. 25"W. 22"D **\$26.97**

TECH-MASTER for 1961 ★ "GOLD MEDAL" #2430-B

LATEST #630 CIRCUITRY WORLD'S MOST POWERFUL TV CHASSIS
COMPLETE ready to play — including Tubes, 12" Speaker, Knobs, Etc. (less CRT)
90° TV Chassis \$175.85 110° TV Chassis \$182.60 Brochure on request

TUBULAR CONDENSERS—85°C TOP QUALITY—Equally as good for Radio or TV work
.0047-400v, .01-400v, .02-400v, .047-400v, .001-600v, .0047-600v, .01-600v, .02-600v, .03-600v 5¢ ea.
.1-400v, .25-400v, .47-400v, .047-600v, .1-600v, .25-600v, .001-1000v, .0047-1000v, .01-1000v, 8¢ ea.
.039-1000v, .047-1000v, .1-1000v, .007-1600v, .03-1600v, .05-1600v, .005-3000v, .001-6000v, 14¢ ea.

ELECTROLYTIC CONDENSERS—85°C 1-50v, 1-150v, 2-350v, 25-50v, 8-150v 19¢ ea.
20/20-150v, 50/30-150v, 40-150v, 10-450v, 20-450v, 30-450v, 40-450v, 60-450v, 80-450v,34¢ ea.

CARBON RESISTORS—Regular factory stock in Stackpole, Speer, etc.
1/2 WATT 10% 10, 39, 47, 100, 120, 150, 270, 330, 390, 470, 560, 680, 820, 1k, 1800Ω 2¢ ea.
1/2 WATT 10% 2700, 3300, 3900, 4700, 5600, 6800, 8200, 10k, 15k, 18k, 22k, 27k, 33kΩ 2¢ ea.
1/2 WATT 10% 39k, 47k, 50k, 56k, 68k, 82k, 100k, 120k, 150k, 180k, 200k, 220k, 270k, 330kΩ 2¢ ea.
1/2 WATT 10% 390k, 470k, 560k, 680k, 820k, 1, 1.2, 1.5, 2.2, 6.8, 10, 15 MEGΩ 2¢ ea.
1 WATT 10% 3.3, 10, 39, 100, 120, 150, 330, 470, 560, 680, 820, 1k, 1800, 2700, 4700Ω 3¢ ea.
1 WATT 10% 6800, 10k, 15k, 18k, 22k, 27k, 33k, 39k, 47k, 68k, 82k, 100k, 150k, 470k, 680kΩ 3¢ ea.
2 WATT 10% 18, 22, 82, 100, 180, 2200, 3900, 4700, 6800, 8200, 18k, 22k, 100k, 470kΩ 4¢ ea.

WIREWOUND RESISTORS 5-5w, 16-10w, 20-10w, 47-5w, 100-5w, 140-5w, 220-5w. 9¢ ea.
280-10w, 390-5w, 470-5w, 500-10w, 680-10w, 820-5w, 1K-5w, 1K-10w, 1500-5w, 2K-10w. 9¢ ea.
2500-5w, 3K-10w, 4700-5w, 5K-10w, 6K-10w, 7K-10w, 8200-5w, 10K-5w, 15K-5w, 22.5K-12w. 9¢ ea.

CERAMIC CONDENSERS 1, 2, 3, 5, 6, 10, 22, 25, 47, 50, 51, 56, 82, 100, 120, 150 mmf 3¢ ea.
CERAMIC CONDENSERS 220, 250, 270, 330, 470, 1k, 1200, 1500, 2k, 5k, 6800, 10k mmf 3¢ ea.

MICA CONDENSERS 5, 25, 50, 60, 68, 75, 100, 120, 150, 220, 270, 330, 470, 510 mmf 3¢ ea.
MICA CONDENSERS 560, 680, 820, 1k, 1500, 2k, 2500, 3300, 4700, 6k, 6800, 8k, 10k mmf 3¢ ea.

- 1-5" PM SPEAKER alnico #5 magnet \$1
- 1-4" PM SPEAKER alnico #5 magnet \$1
- 1-3" PM SPEAKER alnico #5 magnet \$1
- 1-3 1/2" TWEETER SPEAKER for HI-FI \$1
- 4-AUDIO OUTPUT TRANS. 50L6 type \$1
- 3-AUDIO OUTPUT TRANS. 6K6 or 6V6 type \$1
- 3-I.F. COIL TRANSFORMERS 456 kc \$1
- 3-I.F. COIL TRANSFORMERS 10.7 mc. FM \$1
- 3-I.F. COIL TRANSFORMERS 262 kc (auto) \$1
- 40-ASST. PRECISION RESISTORS best sizes \$1
- 5-SELENIUM RECTIFIERS 65ma list \$1.50 ea. \$1
- 4-SELENIUM RECTIFIERS 75ma \$1
- 3-SELENIUM RECTIFIERS 150 ma \$1
- 3-SELENIUM RECTIFIERS 250ma \$1
- 2-SELENIUM RECTIFIERS 300ma \$1
- 2-SELENIUM RECTIFIERS 450ma 1-65 ma. \$1
- 10-TV CARTWHEEL CONDENSERS 10kv \$1
- 3-TV CARTWHEEL CONDENSERS 20kv \$1
- 2-TV CARTWHEEL CONDENSERS 30kv \$1
- 1-TV RATIO DETECTOR COIL 4.3mc \$1
- 1-TV RATIO DETECTOR COIL 10.7mc \$1
- 1-TV SOUND I.F. COIL 4.3mc \$1
- 3-HV RECTIFIER SOCKETS 1B3 m'nted \$1
- 3-HV RECTIFIER SOCKETS 1X2 m'nted \$1

10-TUBES #1U4..\$1

- 2-SILICON RECTIFIERS 500ma \$1
- 1-SILICON RECTIFIER 750ma \$1
- 1-LB. SPOOL ROSIN CORE SOLDER \$1
- 4-50' SPOOLS HOOK-UP WIRE 4 colors \$1
- 10-6' ELECTRIC LINE CORDS with plugs \$1
- 5-TV CHEATER CORDS with both plugs \$1
- 5-TV CRT. SOCKETS with 18" leads \$1
- 5-HI-VOLT. ANODE LEADS with 18" leads \$1
- 50-STRIPS ASST. SPAGHETTI best sizes \$1
- 100-ASST. RUBBER GROMMETS best sizes \$1
- 100-TWIN LEAD-IN WIRE 300Ω heavy duty \$1
- 50-FLAT 4-CONDUCT. WIRE many purposes \$1
- 25-INSULATED SHIELDED WIRE \$1
- 32-TEST PROD WIRE deluxe (red or black) \$1
- 1-S7 INDOOR TV ANTENNA-gain 3 section \$1
- 20-ASST. TV KNOBS, ESCUTCHEONS, Etc. \$1
- 1-RCA 70T FLYBACK TRANS. #75240 \$1
- 1-TV VERT. OUTPUT TRANS. 10 to 1 ratio \$1
- 15-ASST. TV COILS sync. peaking, width, etc. \$1
- 15-ASST. STANDARD TUNER VHF STRIPS \$1
- 6-ASST. STANDARD TUNER UHF STRIPS. \$1

"ONE DOLLAR" Buys

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.
DEDUCT 10% ON ANY ORDER OF \$10 OR OVER (ON DOLLAR BUYS)

Plus a FREE SURPRISE PACKAGE

- 100-ASST. 1/2 WATT RESISTORS some 5% . . . \$1
- 70-ASSORTED 1 WATT RESISTORS \$1
- 35-ASSORTED 2 WATT RESISTORS \$1
- 50-ASST. TUBULAR CONDENSERS \$1
- 50-ASSORTED FUSES popular sizes \$1
- 75-220K 1/2 WATT RESISTORS 10% \$1
- 75-470K 1/2 WATT RESISTORS 10% \$1
- 5-DIODE CRYSTALS 2-IN21 2-IN22 1-IN64 \$1
- 3-DIODE CRYSTALS 1-IN60 1-IN64 1-IN6W \$1
- 4-DIODE CRYSTALS 1N34A \$1
- 100-ASST. CERAMIC CONDENSERS \$1
- 10-ASST. WIREW'ND RES. 5, 10, 20 watt . . . \$1
- 100-MICA CONDENSERS 1000mmf-500v . . . \$1
- 10-HV TUBULAR CONDENSERS .005-6000v . . \$1
- 35-ASST. DISC CERAMICS best numbers . . . \$1
- 50-ASST. MICA CONDENSERS some in 5% . . \$1
- 6-ASST. SLIDE SWITCHES spst, dpdt, etc. . . \$1
- 4-BAKELITE KNIFE SWITCHES dpdt \$1
- 3-ASST. TOGGLE SWITCHES spst, dpdt, etc. \$1
- 15-ASST. ROTARY SWITCHES \$8.15 worth . . \$1
- 100-FINEST NYLON DIAL CORD best size . . . \$1
- 200-SELF TAPPING SCREWS #8 x 1/2" \$1
- 35-ASST. RADIO KNOBS screw and push-on . \$1
- 100-ASSORTED KNOB SET-SCREWS \$1
- 25-ASSORTED CLOCK RADIO KNOBS \$1
- 600-ASST. H'DWARE screws, nuts, rivets, etc. \$1
- 35-ASST. SOCKETS metal, novel and miniature \$1
- 25-ASST. PRINTED CIRCUIT SOCKETS \$1
- 10-ASST. VOLUME CONTROLS less switch . . \$1
- 5-ASST. VOLUME CONTROLS with switch . . \$1
- 20-ASST. PILOT LIGHTS popular types . . . \$1
- 10-PILOT LIGHT SKTS. bayonet type, wired. \$1
- 50-ASST. TERMINAL STRIPS 1, 2, 3, 4 lug. \$1
- 10-ASST. RADIO ELECTRO. CONDENSERS \$1
- 5-ASST. TV ELECTROLYTIC CONDENSERS. \$1
- 25-ASST. MICA TRIMMER CONDENSERS. \$1
- 15-TUBULAR CONDENSERS .47-400v \$1
- 15-TUBULAR CONDENSERS .25-600v \$1
- 6-TV ION TRAPS standard for all CRT's . . \$1
- 15-TUBULAR CONDENSERS .047-600v . . . \$1
- 2-ELECTROLYTIC COND. 40/40-450v \$1
- 3-ELECTROLYTIC COND. 50/30-150v \$1
- 25-ASST. PEAKING COILS popular types . . \$1
- 1-ELECTRIC PHONO MOTOR 78rpm 110v. . . \$1
- 10-WIREWOUND RESISTORS 20 ohm-4W . . . \$1
- 300-ASST. 1/2W RESISTORS short leads . . \$1
- 4-TV CENTERING RINGS \$1
- 35-DISC. CERAMIC CONDENSERS 5000mmf \$1
- 25-ASST. RADIO DIAL POINTERS \$1
- 8-ASST. LUCITE CASES handy for parts . . . \$1
- 100-MICA CONDENSERS 820 mmf-500v . . . \$1
- 3-ASST. SIZES RADIO CHASSIS PANS. . . . \$1
- 3-VARIABLE CONDENSERS super 420/162mfd \$1
- 4-OVAL LOOP ANTENNAS ass't hi-gain types \$1
- 3-LOOPSTICK ANT. new ferrite adjustable . . \$1
- 3-1/2 MEG VOLUME CONTROLS with switch \$1
- 5-50K VOLUME CONTROLS less switch . . . \$1
- 5-ASST. 4 WATT WIREWOUND CONTROLS \$1
- 5-1/2 MEG VOLUME CONTROLS less switch \$1
- 5-1 or 2 MEG VOLUME CONTROLS 1/switch \$1
- 100-VOLUME CONTROL HEX NUTS \$1
- 10-SURE GRIP ALLIGATOR CLIPS \$1
- 1-GOLD GRILLE CLOTH 14"x14" or 12"x18" . . \$1
- 5-SETS SPEAKER PLUGS wired \$1
- 10-SETS PHONO PLUGS and PIN JACKS. \$1
- 2-\$2.50 SAPPHIRE NEEDLES 4000 playings \$1
- 35-MICA COND. 20-50 mmf & 15-68 mmf . . \$1
- 35-MICA COND. 20-100 mmf & 15-270 mmf . . \$1
- 35-MICA COND. 20-470 mmf & 15-680 mmf . . \$1
- 35-MICA COND. 20-820 mmf & 15-1000 mmf . . \$1
- 35-MICA COND. 20-2200 mmf & 15-2400 mmf . . \$1
- 35-MICA COND. 20-6800 mmf & 15-10000 mmf . \$1
- 35-CERAMIC COND. 20-5 mmf & 15-10 mmf . . \$1
- 35-CERAMIC COND. 20-25 mmf & 15-47 mmf . . \$1
- 35-CERAMIC COND. 20-56 mmf & 15-82 mmf . . \$1
- 35-CERAMIC COND. 20-100 mmf & 15-150 mmf . \$1
- 35-CERAMIC COND. 20-270 mmf & 15-470 mmf . \$1
- 35-CERAMIC COND. 20-1000 mmf & 15-1500 mmf \$1
- 35-CERAMIC COND. 20-200 mmf & 15-5000 mmf \$1
- 4-KENRAD TUBES #6SH7 \$1
- 2-TOP NAME #6S07 TUBES. \$1
- 2-TOP BRAND TUBES #35W4. \$1

TOP NAME TUBES 024, 1B3, 1X2B, 5U4, 6AC7, 6AX4, 6CB6, 6J6, 6K6, 6U8, 6V6, 6SN7, 6X8, 12AU7, 12AX7, 50L6 Each \$1

3-TV ALIGNMENT TOOLS assortment #1. . . . \$1
3-TV ALIGNMENT TOOLS assortment #2. . . . \$1
3-TV ALIGNMENT TOOLS assortment #3. . . . \$1
3-TV ALIGNMENT TOOLS assortment #4. . . . \$1
3-TV ALIGNMENT TOOLS assortment #5. . . . \$1

EACH ALIGNMENT TOOL is different and valued at over \$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N. Y. TELEPHONE Corfland 7-2359

NOW DELIVERING

the "Big 3"

Citizens Band 2-Way Radios

from

GLOBE ELECTRONICS

The CB-200 Broadcaster Deluxe has been designed for the consumer who desires more versatility and greater selectivity. Five channels — four crystal controlled for both transmitting and receiving. Fifth position allows tunable channel selection for receiving.



the Broadcaster Deluxe

Dual conversion and newly designed squeelch circuit eliminates adjacent channel interference and silences normal receiver noise.

Unit is only 4x12x10", with 3x5" oval speaker. Tri-centric tuning dial simplifies control. Microphone has retractable coil cord and removable plug. Pi Network. \$189.95 each, list.

the Citizens Broadcaster

The CB-100 Broadcaster is smartly styled, and weighs only 13 pounds. It measures 3½x10½x13", with a range of 6 to 10 miles. Three channels with lighted color buttons indicate which channel is in use. Can be used in car, boat, office or home. FCC Form 505 included with each unit for station license. Complete with crystals for one channel and push-to-talk microphone. \$129.95 ea. list.

the Pocketphone

This transistorized 2-way radio is only 1½x2¾x6¼" — actually fits in your pocket. Weighs just 13½ oz. No license required unit to unit. Range is from ½-1 mile. Completely portable with "Power-Pak" rechargeable battery lasting a year or more. Microphone and speaker built in. May be used with other Globe Units for additional range. \$125.00 each, list.

RE

GLOBE ELECTRONICS
A Division of Textron Electronics, Inc.
Council Bluffs, Iowa

PLEASE SEND:

BROCHURE ON THE ENTIRE CITIZENS BAND LINE

COMPLETE DEALER INFORMATION

NAME: _____

FIRM: _____

ADDRESS: _____

CITY & STATE: _____



TUBE CARRIER


Plastic flower boxes are available in various sizes, and may be used as light-weight durable carriers for shop equipment. Tubes which are kept on hand



for use as trial tests may be handily stored and transported to and from the test bench in such a box. The box in the photo is about 28½ inches long and 6½ inches wide at the top and about 6 inches deep.—H. Leeper

EXTRA HEAT SINK FOR POWER TRANSISTORS

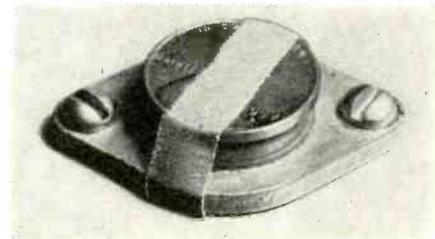
The popular types of power transistors have metal cases and are intended



to be bolted to a metal chassis or other sheet of metal, which acts as a heat sink to absorb some of the transistor heat. However, there is no provision for drawing off heat from the top of the transistor. I figured it would be a good idea to tape a copper coin or iron washer to the top of the transistor as a secondary heat sink. Thus the transistor is provided with heat sinks on the top and bottom at the same time to insure cooler operation. — Art Trauffer

TRANSISTOR SOCKET MOUNT

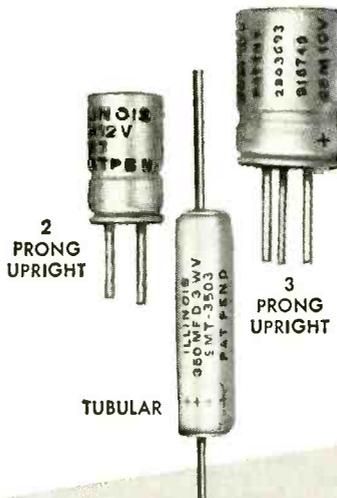A mount for transistor sockets will simplify many experimental transistor circuit layouts. Such a unit can be made from a CTC or similar terminal board. Drill a hole in the center of the board. Put the socket in the hole and cement



NOW!
In stock at your distributor


SMT

SUB-MINIATURES

For all transistorized electronics


Unsurpassed where size is essential in countless replacement applications. Available in full range of capacities and voltages . . . SMT, SMTU (up-right), upright common positive, upright common negative and non-polarized.

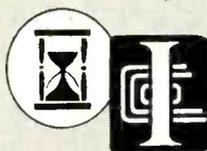Order from your distributor now. Our new SMT catalog is available upon request.



ILLINOIS

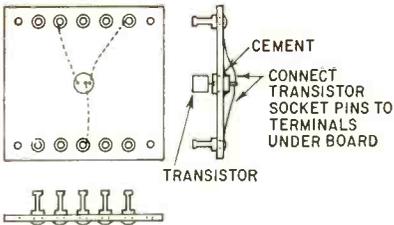CONDENSER COMPANY
1616 North Throop
Chicago 22, Illinois
Phone EV 4-1300



it in place. Then connect the socket pins to the board terminals. The extra board terminals make convenient tie points for associated components.—*Sherwood M. Kidder*

VOM IN A SHAVING BAG


Whenever a service technician is called to repair a set in the customer's home, his reputation is hanging in the balance. The appearance of his test equipment can leave either a good or bad impression on the customer, depending on shape it's in. Obviously a



vtm or vom with a cracked meter face or a badly scratched case isn't going to leave as good an impression as one having a new appearance. To keep your vom or vtm looking new, store it in a travel type shaving bag. You'll find there's generally plenty of space in the bag for test leads and that you don't actually have to remove the meter from the bag to use it. The convenient handle makes it easy to carry too.—*Charles A. Cunningham*

KEEP JUMPERS UNTANGLED

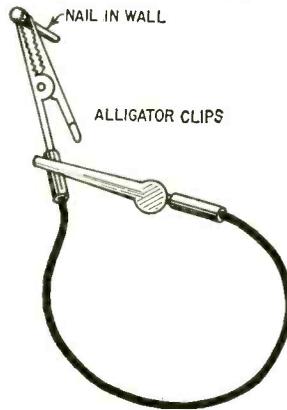Almost every service technician uses jumpers, and they are usually all tangled up when not in use. An easy way to keep this from happening is to



hook one clip on the other before hanging up the jumper. Now any number of jumpers can be hung on the same nail with little chance of entanglement.—*Joseph Amorose* END

AT ELECTRONIC PARTS JOBBERS



2 FOR 1 DC POWER SUPPLY

1... operates ALL auto radios
—transistor, hybrid, tube—

2... operates miniature radios
—transistor portables—

... also operates experimental transistor circuits, relays, use it for electroplating, laboratory work.

- Transistor protection.
- EPL patented cooling.

2 OUTPUT RANGES

VOLTS	CURRENT	RIPPLE
0-16	5 amps.	0.5%
0-20	75 ma.	0.15%

Compare and you'll buy Model PS-2 \$4995

Also—Kit Model KPS-2... \$43.50

Send for FREE literature, name of your jobber!

Electro Products Laboratories
4501-R Ravenswood, Chicago 40, Ill.

Name _____

Address _____

City _____

Zone _____ State _____

0766

TV-RADIO Servicemen or Beginners...

Send for *Coyne's*
7-Volume Job-Training Set
on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

Answers ALL Servicing Problems QUICKLY...
Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick". No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$4 in 7 days and \$4 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."
—Guy Bliss, New York

"Swell set for either the serviceman or the beginner. Every service bench should have one."
—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!



Like Having An Electronics Expert Right At Your Side!

VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.

VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS! 403 pages; fully illustrated.

VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.

VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them. 368 pages; illustrated.

VOL. 5—EVERYTHING ON TV TROUBLESHOOTING! Covers all types of sets. 437 pages; illustrations, diagrams.

VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.

VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

ALL 7 BOOKS HAVE BRIGHT, MODERN, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division

COYNE ELECTRICAL SCHOOL

1455 W. Congress Parkway, Dept. CO-T1, Chicago 7, Illinois

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per your offer. Include "Patterns & Diagrams" book FREE!

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Check here if you want Set sent C.O.D. Coyne pays shipping charges. 7-Day Money-Back Guarantee.

Coyne ELECTRICAL SCHOOL

1455 W. Congress Parkway
Dept. CO-T1, Chicago 7, Illinois

DYNACO


MAKER OF THE WORLD'S FINEST
HIGH FIDELITY COMPONENTS

*proudly presents
the all new*

dynatuner

*superb companion
to your*

DYNAKITS

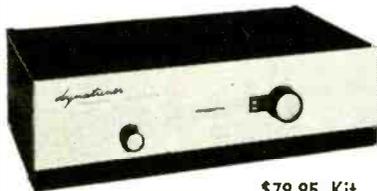

\$79.95 Kit
\$119.95 Wired

EASIEST TO ASSEMBLE

Dyna's traditional streamlined circuits and etched circuit boards enable complete construction and alignment in 6 hours.

SIMPLEST TO ALIGN

You achieve minimum distortion and maximum sensitivity—yourself—without any instruments.

UNPARALLELED PERFORMANCE

Highest effective sensitivity plus lowest distortion plus superior quieting plus precise, drift-free tuning.

Hear and compare it at your favorite dealer's showroom.

Write for complete specifications

DYNACO, INC.

3912 Powelton Ave. • Phila. 4, Pa.
CABLE ADDRESS: DYNACO, PHILA.


BUSINESS and PEOPLE

Electronic Instrument Co., Long Island City, N. Y., outlined plans for a stepped-up winter advertising and public relations campaign for its Eico hi-fi kits and equipment at a sales representative meeting at its plant. Eico



president, Harry R. Ashley (right); executive vice president, Phil Portnoy (standing left), are shown explaining the new panel designed for Eico stereo tuners and amplifiers to the company's sales representatives.

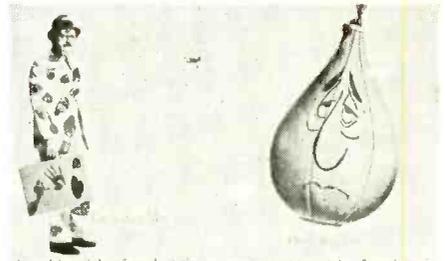Rek-O-Kut Co., Corona, N. Y., and its subsidiary, Audax Div., are using a series of off-beat posters displayed on



relax with a night of good music on high fidelity components by
REK-O-KUT

relax with a night of good music on high fidelity components by
REK-O-KUT AUDAX

Long Island RR stations to promote sales of its hi-fi components. The campaign ties in with local dealers by imprinting their names in local trading areas.

Pyramid Electric Co., Darlington, S. C., designed a new Whirl-O-Mat capacitor dispenser for its parts distributors. The company is also packaging its mylar-paper Gold-Dip capacitors in a plastic jewel box which may be reused for small parts storage.



COMPUTER CUSTOMER SERVICE ENGINEERS

(WASHINGTON AREA)

Attractive assignments now available for senior engineers who have had at least 3 years' experience in installation and maintenance of large scale data processing systems.

Comprehensive training program provided at company expense prior to assignment in Washington, D.C., area.

FOR INTERVIEW CONTACT

Mr. John Felos, Professional Emp. Manager

PHILCO/COMPUTER DIVISION, Willow Grove, Pa.

PHILCO



Famous for Quality the World Over

Jensen Industries, Forest Park, Ill., is in full swing on a Give a Diamond for Christmas promotion featuring its



diamond needle in a gift package in an effort to stimulate Christmas sales.

Sencore, Addison, Ill., is continuing its series of coast-to-coast service technicians' clinics. Ed Flaxman, Sencore vice president—(fourth from left, front



row), and representative Mark Markman (seventh from left), are shown leading the discussion at Mobile TV Service Lab, Compton, Calif.

Fidelitone, Inc., Chicago, Ill., has launched a nation-wide advertising



campaign on its Pyramid diamond needles in trade and consumer magazines.

R. F. Meinicke was appointed vice president—sales of Amphelol Distributor Div., Amphelol-Borg Electronics Corp., Broadview, Ill. He joined the company in 1949 and was sales manager of the division immediately prior to his promotion.



Robert G. Lynch is now equipment sales manager for Sylvania Electronic Tubes Div., New York, N. Y. He was manager of industrial equipment sales.




Lloyd R. Day was promoted to the newly created position of manager of new business development, ICA Electron Tube Div., Harrison, N. J. He was planning manager.



LEARN ALL ABOUT TRANSISTORS and other SEMICONDUCTORS!

WITH THESE 6 BOOKS ONLY \$15.95

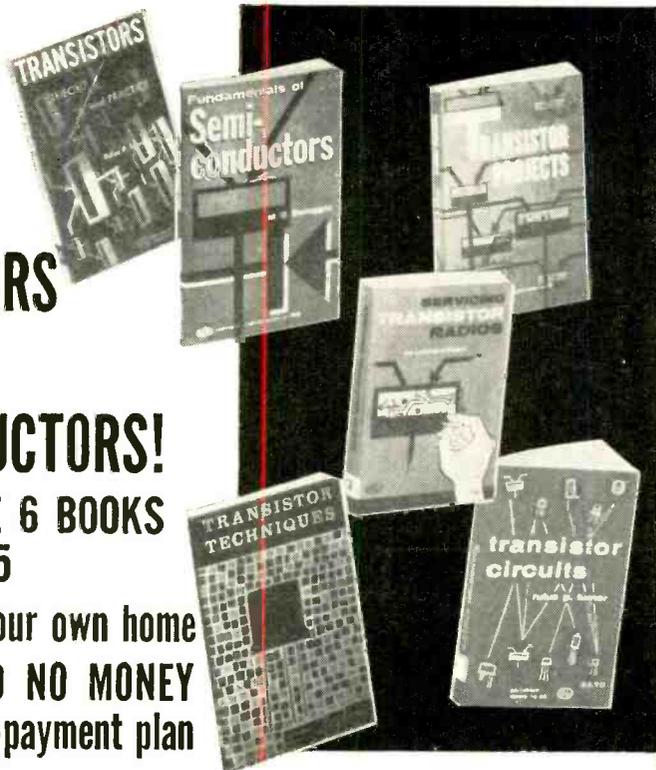FREE TRIAL in your own home
SEND NO MONEY
easy-payment plan



Semiconductors are the key to the future in electronics. Here's an easy way to learn all about them now. Six complete Gernsback paper-bound books that cover everything from basic theory to practical bench techniques and circuit design. Insure your future in an electronics career or hobby. Get these books this easy-payment way and master semiconductors now.

FUNDAMENTALS OF SEMICONDUCTORS

By M. G. Scroggie, BSEE

This outstanding British authority gives you a clear, authoritative and complete study of the whole field of semiconductors. In this truly superior book, he covers the whole range of semiconductor devices—transistors, rectifiers, photoelectric devices—everything. Tells you how they are used and what their future's likely to be. Virtually a complete course on semiconductor fundamentals. No. 92 160 pages. \$2.95

TRANSISTOR PROJECTS

The best of the how-to-do-it's selected from Radio-Electronics Magazine. Top writer-authorities like Rufus P. Turner, I. Queen, Edwin Bohr and Leonard D'Airo give you step-by-step information on how to use transistors in building radios, instruments and accessories. Clears away many misconceptions. Lets you in on plenty of inside hints. No. 89 160 pages. \$2.90

SERVICING TRANSISTOR RADIOS

By Leonard D'Airo.

How to make money servicing these new members of the electronics family. An expert technician tells you how to solve the many specialized problems you'll meet. Shows you the pitfalls to avoid, the techniques to master. Many helpful troubleshooting charts included plus a chapter

on transistor characteristics, interchangeability charts and substitution data. No. 76 224 pages. \$2.90

TRANSISTORS—THEORY AND PRACTICE (2nd edition)

By Rufus P. Turner.

THE book on transistors. This popular authority crams more into this book than any other book in its price range (and many priced much higher). Discusses why transistors work, what you can do with them, measurements, tests, equivalent circuits, care. Completely revised. Much new material added. No. 75 160 pages. \$2.95

TRANSISTOR TECHNIQUES

How to work with transistors. What to avoid. How to test them, measure them, take care of them. Not much math or theory but loaded with all sorts of practical hints—including some construction projects for test instruments, amplifiers, geiger counters, etc. No. 61 96 pages. \$1.50

TRANSISTOR CIRCUITS

By Rufus P. Turner.

A workbook for the experimenter. Gives you over 150 tested transistor circuits for all types of electronic equipment to work with, fool with, have fun with. They all work. No. 63 160 pages. \$2.75

SEND NO MONEY—Examine books in your own home FREE. Just fill in the coupon and we'll send you the complete set (six books) for a free 7-day examination in your own home. If you like them keep them and send us your first payment of \$2.95. Then pay only \$2.60 each month for five months thereafter until the total price of \$15.95 plus postage is paid. If you don't like the books, just send them back within 7 days of receipt.

FREE TRIAL COUPON

GERNSBACK LIBRARY, Inc.—Dept. 120
154 West 14th Street
New York 11, N. Y.

Send me the 6 G/L Transistor books for 7-day FREE trial. If satisfied I will send you \$2.95 down payment and \$2.60 per month for five months until the total of \$15.95 plus postage is paid. If not satisfied I agree to return them in 7 days.

Print name _____

Street _____

City _____ Zone _____ State _____

SAVE POSTAGE COST Enclose remittance of \$15.95 with order and we pay postage. Same return privilege.

BRAND NEW UNITED'S FIRST QUALITY TUBES DISCOUNTS up to 80% OFF

GUARANTEED ONE FULL YEAR! NOT USED! NO PULLS! WHY PAY MORE?

Qty.	Tube #	Price	Qty.	Tube #	Price	Qty.	Tube #	Price	Qty.	Tube #	Price	Qty.	Tube #	Price	Qty.	Tube #	Price
002A	75	3CV5	70	6AC7	75	6B8	69	6U8	77	12CU6/	1.00	17L6	57				
1A5	80	3D6	59	6AH4	82	6BX7	1.02	6V6	65	GA	1.00	18A5	50				
1A7	84	3DT6	49	6AH6	98	6BY6	56	6W4	60	12BR7	70	18FV6	49				
1AX2	70	3Q4	68	6AK5	3/1.00	6BZ6	54	6W6	68	12BV7	80	18FX6	52				
1B3	73	3Q5	89	6AL5	46	6BZ7	96	6X4	38	12BV7	73	18FY6	40				
1C5	1.02	3S4	60	6AL7	1.35	6BZ8	1.05	6X5	58	12BZ7	74	19AU4	80				
1G3	73	3VA	57	6AM8	77	6C4	42	6X8	75	12C5	55	19B6	1.39				
1G4	60	4AU6	54	6AN8	84	6C5	53	7AD7	80	12CU5	55	19T8	78				
1H5	75	4AU6	54	6AQ5	49	6C6	59	7A7	70	12CV5	55	21X6	1.40				
1J3	72	4BC5	55	6AQ6	60	6CD6CA	1.40	7AU7	60	12CR6	53	25A4	71				
1K3	72	4BC8	95	6AR5	54	6CF6	63	7EY6	75	12CT8	90	25B6	1.00				
1L4	60	4BN6	75	6AS5	59	6C7	64	8A18	82	12CX6	53	25C6	1.20				
1L4A	99	4B7	97	6AS6	2.25	6C8	76	8AW8	92	12DB5	68	25C6/	1.20				
1L6	99	4BS8	97	6AS8	85	6CM7	65	8BQ5	59	12DE8	74	25C6/	1.20				
1L8	99	4B8	70	6AT6	42	6C7	64	8C7	63	12DL8	84	25C6/	1.20				
1L8A	99	4B26	57	6AU4	81	6C8	83	8CM7	67	12DQ6	1.00	25C6/	1.20				
1LD5	99	4B27	95	6AU5	1.05	6CR6	50	8CN7	65	12DS7	78	25C6/	1.20				
1LE3	99	4CB6	57	6AU6	49	6CS6	56	8CB8	90	12E6	53	25C6/	1.20				
1L85	99	4CS6	60	6AU7	60	6CS7	70	8EB8	93	12E6	55	25C6/	1.20				
1LH4	99	4CV5	70	6AU8	86	6CS8	57	9CL8	75	12E6	53	25C6/	1.20				
1LN5	99	4D6	61	6AV6	59	6C9	80	8CB8	90	12E6	53	25C6/	1.20				
1NS	90	4DT6	54	6AV6	39	6CY5	70	11CY7	74	12E6	52	25C6/	1.20				
1SA6	1.10	5AM8	78	6AW8	88	6CY7	70	12AB5	54	12E6	52	25C6/	1.20				
1R5	61	5AR6	85	6AX4	65	6DE5	57	12AC5	48	12E6	52	25C6/	1.20				
1S4	75	5A8	51	6AX5	75	6DK6	59	12AD6	56	12E6	52	25C6/	1.20				
1S5	50	5AT8	79	6BA6	48	6DN6	1.40	12AE6	42	12FA6	49	25C6/	1.20				
1T4	57	5AV8	1.00	6BA7	92	6DT	1.00	12AF7	72	12FM6	44	25C6/	1.20				
1U4	56	5Y5	45	6B6GA	1.50	6DQ6	1.65	12AF6	48	12G6	75	25C6/	1.20				
1U5	49	5BK7	81	6BC5	54	6DS5	65	12AJ6	45	12FX8	85	25C6/	1.20				
1V2	99	5BQ7	96	6BC7	93	6DT6	52	12AL5	44	12GC6	1.05	25C6/	1.20				
1X2	75	5C8	75	6BD6	50	6EB8	90	12AL8	78	12H5	64	25C6/	1.20				
2A4	95	5CC8	75	6BD6	50	6EB8	90	12AQ5	51	12L6	61	25C6/	1.20				
2B3	1.00	5EAB	79	6BE6	54	6EU8	78	12AT6	42	12S7	85	25C6/	1.20				
2BN4	63	5EUB	79	6BF5	88	6EWA	78	12AT7	75	12S7	75	25C6/	1.20				
2CV5	70	5J6	67	6BF6	43	6FE	85	12AU6	49	12SF5	75	25C6/	1.20				
3A3	84	5T8	80	6B6CA	1.40	6HG	55	12AU7	59	12S7	75	25C6/	1.20				
3A4	55	5U8	59	6B6GA	1.50	6J5C	35	12AV6	70	12SQ7	85	25C6/	1.20				
3AF4	1.02	5U8	80	6BH6	64	6J5CT	50	12AV7	74	12SL7	88	25C6/	1.20				
3AL5	43	5V4	82	6BH8	86	6J6	66	12AW6	75	12SN7	66	25C6/	1.20				
3AU6	50	5V6	55	6BJ6	65	6J7	85	12AX4	65	12SN7	66	25C6/	1.20				
3AV6	40	5W4	95	6BK5	85	6K6	58	12AX7	62	12U7	61	25C6/	1.20				
3B2	1.50	5X4	78	6BK7	84	6L5	1.10	12AY7	1.44	12V6	52	25C6/	1.20				
3BA6	50	5X6	77	6BL7	95	6S4	54	12AZ6	62	12W6	52	25C6/	1.20				
3BC5	53	5Y5	45	6B6A	56	6SA7	75	12B4	62	12X4	37	25C6/	1.20				
3BE6	51	5Y7	77	6BN6	73	6SC7	75	12BA6	49	14H7	80	25C6/	1.20				
3BN4	63	6A4	1.10	6BQ5	59	6SF5	75	12BA6	49	14N7	80	25C6/	1.20				
3BN6	75	6A7	1.15	6BQ6	56	6SH7	75	12BD6	49	14P6	66	25C6/	1.20				
3B8	70	6AB4	45	6B8	1.00	6SJ7	75	12BE6	52	17BQ6	66	25C6/	1.20				
3BY6	54	6AC7	85	6C6/	1.00	6SK7	3/1.00	12BF6	43	CTB	1.00	25C6/	1.20				
3BZ6	54	6AF3	72	6CA	1.00	6SL7	75	12BH7	72	17CU6/	66	25C6/	1.20				
3CB6	53	6AF4	96	6BQ7	94	6SN7	64	12BL6	55	17CS7	57	25C6/	1.20				
3CF6	59	6AF4A	96	6BR8	77	6SQ7	72	12BQ6	1.00	17DQ6	1.00	25C6/	1.20				
3CS6	51	6AC5	44	6B8	93	6T8	84	CTB	1.00	17E5	50	25C6/	1.20				

ALL-PURPOSE ALUMINUM DIODES—25c EA. WIRE LEADS. 500 mil. silicon rectifiers 59c ea. 10 for \$3.50.
 SEND FOR COMPLETE PARTS CATALOG WITHOUT COST USE THIS AD AS ORDER BLANK

UNITED RADIO CO. BOX 1000 B NEWARK, N. J.

TERMS: remit full price plus postage with order. No COD. Mail to Dept. RE. Excess postage will be refunded. Subject to Prior Sale \$5 MINIMUM ORDER

TAPE RECORDERS

HI-FI COMPONENTS SLEEP LEARN KITS

MERITAPE Low cost, high quality recording tape, in boxes or cans.

UNUSUAL VALUES FREE 1961 CATALOG

DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.

OUT OF SPACE?

You bet we'd be... if we were to tell you all about AUDION'S 'Out of this World Hi Fi Values'.


Write for free Catalog

audion 25-E Oxford Road Massapequa, New York

new "LEADER" test instrument

LAG-55 AUDIO GENERATOR SINE SQUARE

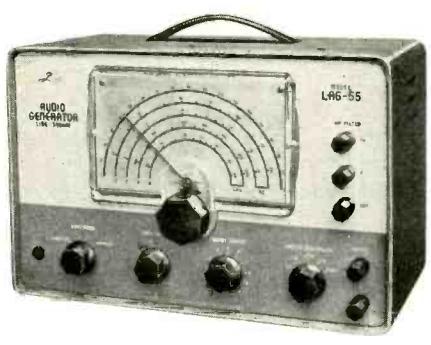A multi-purpose generator for measurements on audio equipment—amplifiers, speakers, networks. Three waveforms: sine, square and complex for all types of measurements including response, distortion, transient and I-M distortion checks. Full range is from 20 to 200,000 cps, output 5 volts with minimum amplitude variation throughout whole range.



The LEADER test instruments are being used in the more than 36 countries, attesting their excellence in design, performance and usefulness.

OHMATSU ELECTRIC CO. LTD.

850 TSUASHIMA-CHO KOHOKU-KU YOKOHAMA, JAPAN

David Hughes, former director of marketing of Hickok Electrical Instrument Co., Cleveland, was named vice president and general manager of the Meter and Controls Div. which will have the responsibility for the development and sales of meters and controls to the original equipment market. Frank H. Sawonik, former vice president, government sales, is now vice president and sales manager of the Industrial Instrument and Government Div. Both divisions were newly set up by the company. P. H. Neville, president of Leece-Neville Co., was appointed a director of Hickok.



Jacob H. Ruiter, Jr., joined the Weston Instruments Div. of Daystrom, Inc., Murray Hill, N. J., as manager of sales promotion. He comes from Allen B. DuMont Laboratories where he had been technical advertising manager and public relations manager.




L. H. Niemann was promoted to director of government relations for CBS Electronics with headquarters in Washington, D. C. He was previously semiconductor sales manager.



Joseph W. Yuhas is now manager of the Distributor Div. of Pyramid Electric Co., Darlington, S. C. He joined the company in February of this year from Astron Corp.



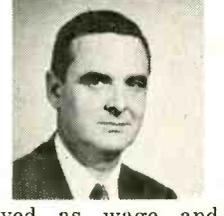Harry P. Hancock, Jr., (left) was promoted to industrial relations manager of the Raytheon receiving tube plant in Quincy, Mass. Prior to the



promotion, he served as wage and salary administrator for the Industrial Components Div. Arthur W. Randall joined Raytheon as Chicago district manager for the Distributor Products Div. He came to Raytheon from General Electric where he was a district representative for housewares and radio receivers.

Julian King Sprague, president and director of Sprague Electric Co. and a director of Sprague Products Co., died of a heart attack at his ranch in Presidio, Tex., at the age of 57. END

new LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

ELECTRONICS CATALOG No. 71, for industry, defense and broadcast. Mail order and direct sales. 448 illustrated pages.—Newark Electronics Corp., 223 W. Madison St., Chicago 6, Ill.

ACOUSTICAL CABINETY Bulletin R-16 describes and illustrates equipment, speaker and record cabinets in console and chairside types for separate or combined use in high-fidelity stereo and mono music systems.—Rockford Special Furniture Co., 1803 W. Belle Plaine, Chicago 13, Ill.

PLANNING A STEREO HI-FI SYSTEM is studied in *Tech-Specs*. With an eye on the audiophile's space problems, the pocket-size booklet coordinates hi-fi components to the enclosure or cabinet and facilitates balanced selection with a special planning chart and complete technical specifications of manufacturer's cartridges.—Dept. PR6, Pickering and Co., Inc., Sunnyside Blvd., Plainview, N. Y.

AUDIO TAPE RECORDER DIRECTORY 60-61 supplies such quick facts as model, price, frequency response and other technical data for magnetic tape recorders, audio accessories, tape and related items, manufacturers and their complete addresses. 27 pages profusely illustrated in black-and-white and color.—Audio Devices, Inc., 444 Madison Ave., New York 22, N. Y. 10¢ mailing charge.


YOKE AND FLYBACK BULLETIN, No. YFX, available to service technicians for simplification of replacement problems. Index cross-references manufacturer's equivalents for other brands of replacement yokes and flyback transformers.—Chicago Standard Transformer Corp., 3501 W. Addison St., Chicago 18, Ill.

SEMICONDUCTOR PRODUCTS BROCHURE charts germanium power, audio, switching, silicon and germanium mesa transistors, silicon rectifiers and Zener diodes, and key specifications such as breakdown voltage, current capacity, operating temperatures and power dissipation of manufacturer's industrial and military semiconductor line.—Tech-

TV TUNERS OVERHAULED

ONE PRICE . . . \$9.95 VHF tuner
UHF tuner
UV Combination*

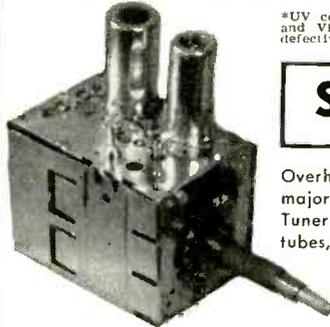YES, low overhaul rate of \$9.95 covers ALL makes and models.



*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners with coil or gear drives must be dismantled and the defective unit only sent for overhaul.

SAME DAY SERVICE

ON POPULAR TYPES—48 HOURS ALL OTHERS

Overhaul charge includes labor and minor parts; tubes and major parts are extra at net prices. Written 90 days warranty. Tuner to be overhauled should be shipped complete; include tubes, shield cover and any damaged parts. Quote model and state complaint. Pack well and insure.

WRITE FOR SPECIAL QUANTITY RATES

Castle TV Tuner Service, Inc.

5710 N. WESTERN CHICAGO 45, ILL. U.S.A. 136 MAIN ST. TORONTO 13 CANADA

Castle pioneered the first complete TV tuner service almost a decade ago; remember Castle will service ALL makes and our many years of experience in this field assures you of the best service available today.

ENGINEERING SCIENCE MATH DEGREE IN 27 or 36 MOS.

Accelerated year-round program prepares for early employment in fields of Science and Engineering. Regular 4-year program for B.S. Degree completed in 36 months. special engineering degree program in 27. Classes start January, March, June, July, September. Quality education. Graduates employed from coast to coast. Government approved for veteran training. Students from 50 states, 40 countries, 20 buildings; dorms, gym, Campus. Save time and money. Earn board while studying. Write for catalog and complete information. 1712 E. Washington Boulevard, Fort Wayne 2, Indiana

INDIANA TECHNICAL COLLEGE

UHF, TV and LAB EQUIPMENT

RCA UHF Sweep-Marker Generator Model WR 40A	\$219.50
rack mount	89.50
RCA UHF Sweep-Marker Generator Model 40A	79.95
RCA UHF Sweep Generator Model WR 41A	99.50
RCA Video Sweep Generator Model WA 21A	49.95
rack mount	79.95
RCA TV Sweep Generator Model WR 59B	39.50
RCA TV RF Sweep Generator Model WR 94A	39.50
New London Instrument Co. Noise Source, Model 175A	39.95
D&R Flutter Meter Model FL-3B	49.95
Ferris Microvoltage Model 24A	34.95
Dumont 5" Oscilloscope Model 208B	34.95
Sylvania Polymeter Type 134Z	24.95

Send M.O. or check with order. Write for complete list.

R W ELECTRONICS

2430 S. MICHIGAN AVE. DEPT. RE
Chicago 16, Ill. Phone: CALumet 5-1281

How to make more money with your OSCILLOSCOPE

Noted electronics authority Albert C. W. Saunders tells you how in his fascinating new book **WORKING WITH THE OSCILLOSCOPE**. 26 illustrated projects, 200 diagrams, show you exactly how to use "electronics' most useful instrument" in electronics, radio, TV, transistors, vacuum tubes, other work.

The author, director of a famous electronics school, has worked with oscilloscopes 40 years. In clear, simple language he tells you how the 'scope works, the many jobs it will do, how to use it to make extra money, just as if he were sitting with you at your bench.

Send for your copy of **WORKING WITH THE OSCILLOSCOPE**

today at the special limited-time price of only \$3 postpaid. Satisfaction guaranteed or money refunded.

CUT OUT AND MAIL TO

Electronic Technical Publishing Co., Dept. RE, P.O. Box 306, Astor Sta., Boston, Mass.

Please rush A. C. W. Saunders' "Working with the Oscilloscope" to me. I enclose \$_____ for _____ copies at \$3 each.

Name _____

Street _____

City & Zone _____ State _____

TIME TO CLEAN UP YOUR SYSTEM . . .



Norelco® T-7 LOUDSPEAKERS

with voice coil magnets of Ticonal-7 steel (30% more efficient* than Alnico V)

* . . . 30% more efficient response to the full signal range of your amplifier . . . WHETHER ITS RATED OUTPUT is 10 WATTS or a HUNDRED . . . at any listening level from a whisper to a shout!

Guild-crafted by Philips of the Netherlands to give you

THE CLEANEST SOUND AROUND

Ask for a demonstration wherever good sound is sold or write to:

**NORTH
AMERICAN
PHILIPS
CO., INC.**

High Fidelity Products Division,
230 Duffy Avenue,
Hicksville, L. I., N. Y.

ATTENTION SERVICE TECHNICIANS ASSOCIATIONS, CLUB MEMBERS, STUDENT GROUPS. SPECIAL SUBSCRIPTION RATES TO RADIO-ELECTRONICS ARE AVAILABLE TO ASSOCIATIONS, CLUBS, SCHOOLS, EMPLOYEE GROUPS, ETC. FOR INFORMATION WRITE G. ALIQUO.

Radio-Electronics Subscriber Service, 154 West 14th St., New York 11, N. Y.

nical Information Center, Motorola Semiconductor Products, Inc., 5005 E. McDowell Rd., Phoenix, Ariz.

SILICON RECTIFIER SHORT FORM CATALOG quotes from technical bulletins for various models of silicon rectifiers. Diagrams, charts and graphs give absolute maximum ratings (60 cycles) and operating characteristics. Interesting USA map on back of book highlights area sales reps.—Standard Rectifier Corp., 620 E. Dyer Rd., Santa Ana, Calif.

STEREO monthly report in manufacturer's *Newsletter* describes new products, projects under development and available literature on the subjects.—Harman-Kardon, Inc., Plainview, N. Y.

STEREO "BALANCE KIT," *Do It Yourself*, demonstrates scientific principle of balance in all planes. Center of mass of piece of cardboard can be located for balance identical to that of a transcription arm and its pivot at center of its mass.—Audio Empire, 1075 Stewart Ave., Garden City, N. Y.

WIRES AND CABLES in a variety of of types, including transmission and open line wire, rotor, coaxial and inter-communication cables, plastic molded products, accessories and tools are graphically illustrated in *Catalog b-22*.—Saxton Products, Inc., 4320 Park Ave., Bronx 57, N. Y.

SOUND SYSTEMS FOR SCHOOLS itemizes and illustrates communication facilities available as production items or for integration into custom adapted program.—DuKane Corp., St. Charles, Ill.

POWER SUPPLIES for utility, industrial, military and electronics applications are explained in *Bulletin GED-4184*. Discusses new line of 30 standard units with 25% fewer components and with protective circuit. Photos and charts outline specifications.—General Electric Co., Schenectady 5, N. Y.

CONTROL COMPONENTS GUIDE includes military telemetering pressure and displacement position transducers, high accuracy and voltage pressure transmitters among manufacturer's products. Complete specifications and illustrations.—International Resistance Co., 401 N. Broad St., Philadelphia 8, Pa.

1960 SHORT FORM CATALOG contains representative items from manufacturer's line of oscilloscopes, oscillators, generators, voltmeters, milliameters, electronic counters, measuring and monitoring equipment and wideband amplifiers. Also lists sales reps and instrument repair stations for North America and overseas on back page.—Hewlett-Packard Co., 1501 Page Mill Rd., Palo Alto, Calif.

RELAYS, sensitive, power, antenna, micro-miniature, hermetically sealed, telephone and multi-pole sensitive types, and their complete electrical operating characteristics, diagrams and prices, in *Catalog No. 60-8*.—Kurman Electric Co., 191 Newel St., Brooklyn 22, N. Y.

CIRCUIT BREAKER CATALOG gives

Now . . . Build
**35 ELECTRONIC
PROJECTS** with
these amazing kits!

- No knowledge of electronics necessary
- No soldering . . . easy pegboard mounting . . . parts can be used and reused
- Only a screwdriver needed

Model LAB-18
Net \$11.95

ELECTRONIC LAB

Model LAB-35
Net \$17.95

18 ELECTRONIC EXPERIMENTS FOR EVERYONE!

Get started on an interesting hobby or successful electronics career building and experimenting with SOLAR ENERGY—SPACE COMMUNICATIONS—RADIOS—TRANSISTORS—OSCILLATORS. It's fun and easy to do. Kit comes complete with all parts and simple picture instructions perfect for even a beginner!

Get Your Electronics Lab Kit Today!
. . . Give One as a Gift!

At your local radio parts supplier, or write



35 PROJECTS FOR THE ELECTRONIC ENTHUSIAST!

Contains all parts and simple illustrated instructions to build projects as PHOTO ELECTRIC RELAYS—SOLAR POWERED RADIOS—RAIN ALARM—INTERCOM—VOICE OPERATED RELAY—TV COMMERCIAL KILLER—CAPACITY RELAY—BURGLAR ALARM—FIRE ALARM—FLASHER—WIRELESS CODE TRANSMITTER—TIMER and many more. Biggest money's worth you've ever seen!



6 Radford
Place,
Yonkers,
New York

brief description, technical data and additional design requirement information on manufacturer's products in addition to ample photos and schematics. —Wood Electric Co., Inc., 244 Broad St., Lynn, Mass.

1961 CATALOG presents latest miniature-transformer information, diagrams and detailed specifications. Includes also special transformers manufactured per customer needs; electronic, electrical, aircraft and missile application transformers meeting MIL-T-27A and other military requirements. —Microtran Co., Inc., 145 E. Mineola Ave., Valley Stream, N. Y. **END**

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In December, 1910, Modern Electrics

- Wireless On Airships, by A. C. Marlowe.
- A Selenium Alarm.
- A Universal Wireless Testing Set, by William Dubilier.
- How to Find the Required Capacity of Transmitting Condensers, by I. H. Glickman.
- Rotary Spark Gap.
- Construction of a Sensitive Wireless Detector, by William H. Taber.
- New Military Quenched Spark Set, by Oliver A. DeCelle.
- How to Make An Oscillation Transformer, by Ralph Weddel.
- Construction of a Rotary Spark Gap, by Hallam Anderson.
- A Circular Potentiometer, by Fannon Beauchamp.
- Unique Potentiometer, by R. E. Baker.
- Wireless Institute, by A. C. Austin, Jr.

STATEMENT REQUIRED BY THE ACT OF AUGUST 24, 1912, AS AMENDED BY THE ACTS OF MARCH 3, 1933, JULY 2, 1946 AND JUNE 11, 1960 (74 STAT. 208) SHOWING THE OWNERSHIP, MANAGEMENT, AND CIRCULATION OF RADIO-ELECTRONICS, published monthly at Mount Morris, Ill., for Oct. 1, 1960.

1. The names and addresses of the publisher, editor, managing editor, and business managers are: Publisher, Hugo Gernsback, 154 W. 14 St., New York 11, N. Y.; Editor, Hugo Gernsback, 154 W. 14 St., New York 11, N. Y.; Managing Editor, Fred Shumanan, 154 W. 14 St., New York 11, N. Y.; Business manager (none).

2. The owner is: (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual member, must be given.) Gernsback Publications, Inc., 154 W. 14 St., New York 11, N. Y.; Hugo Gernsback, 154 W. 14 St., New York 11, N. Y.; M. Harvey Gernsback, 154 W. 14 St., New York 11, N. Y.


3. The known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages, or other securities are: (If there are none, so state.) None.

4. Paragraphs 2 and 3 include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting; also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and transactions underlying each stockholder and security holder who do not appear upon the books of the company as trustees, hold stock and security in a capacity other than that of a bona fide owner.

5. The average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the 12 months preceding the date shown above was: (This information is required by the act of June 11, 1960 to be included in all statements regardless of frequency of issue.) 165,401.

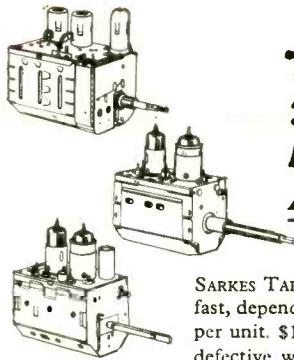H. Gernsback, Publisher
Sworn to and subscribed before me this 14th day of October, 1960.

Joane Dodge, Notary Public (SEAL.)
(My commission expires March 30, 1962.)



TUNERS REPAIRED \$8.50

24-Hour Service 6-Month Warranty

Repair Charge includes ALL Replacement Parts

SARKES TARZIAN, INC., pioneer in the Tuner Manufacturing business, offers fast, dependable, factory repair service on all makes and models. Cost—\$8.50 per unit. \$15 for UV combinations. Now offering 6-month warranty against defective workmanship and parts failure due to normal usage. Tuners repaired on approved, open accounts. Replacements available at low cost on tuners beyond practical repair.

Tarzian-made tuners easily identified by this stamping. When inquiring about service or replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency, chassis identification. And, allow a little more time for service on these tuners. Use this address for fast, factory repair service:

SERVICE MANAGER • TUNER DIVISION DEPT. C



SARKES TARZIAN INC

east hillside drive
bloomington, indiana
edison 2-7251

Mfrs. of Tuners, Semiconductors, Air Trimmers, FM Radios, Audio Tape, and Broadcast Equipment

RENT stereo tapes

- OVER 1500 DIFFERENT ALBUMS
- POSTPAID TO AND FROM YOUR HOME

SEND FOR FREE BROCHURE | stereo-parti 
811-BA Centinola Avenue, Inglewood 3, California

HOLIDAY SPECIALS!!!

Auto Transformer In: 230 V. @ 60 CPS. Out: 80 to 125 V. by means of 9 taps 5 Volts apart. 2.25 KVA. 1600 volt insulation. New, in orig. box. \$15.00.

BRAND NEW FACTORY STOCK. WESTINGHOUSE RUNNING TIME METER. 120 V. @ 60 CPS. Up to 99,999.9 running hours. 3" square. Brand new. Latest production. 3 1/2" deep behind panel, including terminals. 1 lb. Jobber boxed. \$20.02 each. 2 to 4 @ \$19.24 each.

50 Amp Transformer. Pri: 115 VAC @ 60 CPS. Sec: 24 VAC @ 50 Amps. (CT on Sec. @ 12 V. Open frame construction. \$29.00.

High Current Choke (to match above xfmr). .001 H. 50 Amps. \$24.00.

Acme Luminous Tube & 'Scope Xfmr Pri: 115 V. 60 CPS. Sec: 2000 V. @ 18 Ma. \$2.50.

Teletype Paper. Perfection 3 copy—8 1/2" Wide. Standard Yellow color. \$1.00 Roll.

Modulation Transformer. 850 Watts Audio. Made by Chi. Xfmr. Pri: 10,000 Ohms. Sec: 3750 and 7500 Ohms. Brand new. Orig. wood box. 63 lbs. \$44.00.

Modulation Xfmr. 2500 Watts max. audio. Pri impedance: 12 K Ohms. Sec. Imp: 7500/5000 Ohms. New in orig. Kenyon wood box. \$75.00.

G.E. Selenium Rectifier 1450 V. @ 100 Ma. 1/2 Wave. Pair will deliver approx. 1400 V. @ 200 Ma. in full wave circuit. 75¢.

Famous W2EWL SSB Miniature Transformer. New in orig. cartons. 95¢ each. (3 for \$2.50. 10 for \$7.50).

2 Hy. 130 Ma. FTR Miniature Choke. Herm. std. 2 3/4" x 1 1/2" x 1". 40¢.

1/2 & 2 Meter Xfmr. Using 6360 final. Only 3 1/2 lbs. \$15.00.

Wonderful Gift . . . Beautiful framed raised relief maps of the World or USA. In color! Decorative, accurate, educational. 28 1/2" x 18 1/2" \$9.95. 26" x 41" \$24.95. 42" x 63" \$49.95.

Write for New Winter catalog. Check full of specials on TUBES, EQUIPMENT, COMPONENTS. Full of values & savings to industry Servicemen & Experimenters.

Barry Electronics Wishes You All
Sincere Holiday Greetings . . .

BARRY ELECTRONICS CORP.
512R Broadway, New York City 12, N.Y.
Walker 5-7000

PACKAGE HI FI or SINGLE COMPONENTS

You'll find our prices low and service fast.

Write for our quotation
CENTER INDUSTRIAL ELECTRONICS, Inc.
74-R Cortlandt Street, New York 7, N.Y.

all new edition

up-to-date component prices

PLUS the quick easy way to figure service charges

EQUALS



Dave Rice's


OFFICIAL PRICING DIGEST

VOL. 4, NO. 1



Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

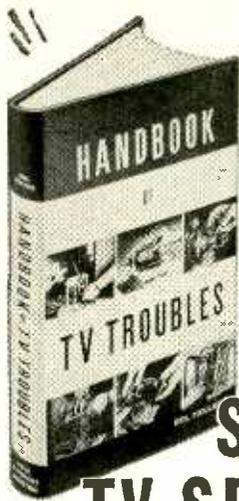ELECTRONIC PUBLISHING COMPANY, INC.
180 N. WACKER DRIVE, CHICAGO 6, ILL.



new Master Guide to TIME- SAVING TV SERVICE

A modern manual for fast, "symptomatic" TV trouble analysis and servicing



**TAKES THE
GUESSWORK
OUT OF
TV REPAIR!**

Covers all causes of practically every television receiver trouble including:

- BRIGHTNESS TROUBLES
- CONTRAST TROUBLES
- PICTURE DISTORTION
- UNSATIS-

**FACTORY PICTURE
DETAIL**

- LINE OR BARS IN PICTURE
- SYNCHRONIZATION TROUBLES
- MISSING PICTURE
- SIZE AND CENTERING TROUBLES
- SOUND TROUBLES
- TELEVISION INTERFERENCE, ETC.

From beginning to end, this big manual is designed for daily use at the bench as a complete easily understood guide to practically any job on any TV receiver. It isn't a "study" book!

Just turn to the Index. Look up the trouble symptoms exhibited by the TV you're working on. The HANDBOOK OF TV TROUBLES then tells you exactly what and where to check. Outlines time-saving short cuts. Explains puzzling details. Eliminates guesswork and useless testing. More than 150 test pattern, wave form and circuit illustrations help explain things so clearly you can hardly fail to understand.

LOOK! LISTEN!

... then Follow This
Easy Guide!

Almost regardless of set make or model, this remarkable new 302-page Handbook helps you track down TV troubles from the symptoms they produce in the set itself—screen intermittently dark; "blooming"; abnormal contrast in spots; "snow"; poor detail; sync troubles; sound troubles—and all the many others. Then it explains how to make needed adjustments or replacements.

Printed in large type. Has sturdy, varnished covers for "on the job" use. The TV TROUBLE INDEX helps you find what you want in a jiffy. Throughout, it's the ideal guide for beginners and experienced servicemen alike! Try it for 10 days AT OUR RISK. You be the judge!

PRACTICE 10 DAYS FREE!

Dept. RE-120, Holt, Rinehart and Winston, Inc.
Technical Div., 383 Madison Ave.,
New York 17, N.Y.

Send new 302-page HANDBOOK OF TV TROUBLES for 10-day FREE trial. If I decide to keep book, I will then send you \$7.50 in full payment. If not, I will return book postpaid and owe you nothing.

SAVE! Send \$7.50 with order and we pay the postage. Same 10-day return privilege with money promptly refunded.

Name.....

Address.....

City, Zone, State.....

OUTSIDE U.S.A. — Price \$8.00 cash only.
10-day return privilege with money refunded.

new BOOKS

CLASS "D" CITIZENS BAND RADIO CALL BOOK, supplement to Vol. 2, No. 1, 1960. International Crystal Mfg. Co., Inc., 18 N. Lee, Oklahoma City, Okla. 9 x 11 in. 230 pp. \$3.95.

The great increase in licensees in this band has made it necessary to publish this supplement. These new calls were issued between Jan. 1 and July 1. Actually 40,000 new calls are listed here, about twice the total issued before Jan. 1. All 24 districts are represented.

101 MORE WAYS TO USE YOUR SCOPE IN TV, by Robert G. Middleton. Howard W. Sams & Co. Inc., 1720 E. 38 St., Indianapolis 6, Ind. 5½ x 8½ in. 160 pp. \$2.50.

This book discusses 101 ways to test equipment, rf and if amplifiers, video amplifiers, agc, sync separators and sweep circuits with a scope. For each test the equipment needed, connections required, test procedures and an analysis of the result of the test are given. In this way, the technician and experimenter can become more proficient in the use of his oscilloscope.—LS

MOTOROLA POWER TRANSISTOR HANDBOOK (1st edition). Motorola Semiconductor Products, 5005 E. McDowell, Phoenix, Ariz. 5½ x 8½ in. 205 pp. \$2.

This manual features theory, design and application. Beginning with the basic principles and characteristics of semiconductors, it explains their ratings, thermal effects, breakdown and other parameters. Diagrams, nomograms, schematics and equations show how to design amplifiers, switches, ignition systems and other circuits for which power transistors are useful. Among special applications discussed are electronic filters, regulators, inverters and TV deflection. A handy reference for engineers and technicians.—IQ

ELECTRONICS FOR THE BEGINNER, by J. A. Stanley. Howard W. Sams & Co. Inc., 1720 E. 38 St., Indianapolis 6, Ind., 5½ x 8¾ in. 192 pp. \$3.95.

This book plus a little assistance may start a 12-year-old on a career in electronics. Hand it to someone older, and you've given him a new hobby. For young or old, this little book is packed with information—starting with a brief introduction, a few hints on soldering and a number of interesting construction projects ranging from a 1-hour radio through home broadcasters and a stereo amplifier. All units are built with transistors and use low-voltage batteries, making them safe same even for the youngest youngster.—LS

INSTALLING HI-FI SYSTEMS, by Jeff Markell and Jay Stanton. Gernsback Library, Inc., 154 W. 14 St., New York 11, N.Y. 5½ x 8½ in. 224 pp. \$3.20.

There are so many "angles" to hi-fi

CITIZENS BAND EQUIPMENT

Check Power Output, Standing

Waves Cescro Transcheck. Gives meter indication of power output, VSWR. Ideal for transmitter tuning. Specify auto splice or PL-259 type coax connector. **\$20.95** Postpaid

Eliminate Generator Whine

Cescro Generator Filter. Eliminates generator whine in mobile installations. Tunable for maximum attenuation. Most effective generator noise filter made. Also available for other frequencies.

Cescro Duopole Base Antenna

Rugged, tuned CB antenna with 1 to 1 VSWR. High gain, non-directional. All elements at DC ground potential for maximum lightning protection. Also available for other frequencies.

Send check or M.O. Ohio residents add 3% Sales Tax.



Postpaid **\$3.00**

\$29.95
Shipped Express Collect

THE STOTTS-FRIEDMAN CO. Dept. R
108 North Jefferson Street, Dayton 2, Ohio

OPPORTUNITY ADLETS

Rates—50¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for Feb. issue must reach us before December 10, 1960.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

BEFORE YOU BUY RECEIVING TUBES OR ELECTRONIC COMPONENTS, send NOW for your Giant Free ZALYTRON Catalog No. 103—featuring nationally known Zalytron First Quality TV-Radio Tubes, plus all types of Components, Kits, Amplifiers, Transceivers, etc. All priced to Save you Plenty—Why Pay More? ZALYTRON TUBE CORP., 220 W. 42nd St., N. Y. C.

LEARN WHILE ASLEEP. Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. SLEEP-LEARNING ASSOCIATION, Box 24-RD, Olympia, Wash.

NEW CONCEPT OF LEARNING SELF-HYPNOSIS! Now on tape or record! Free Literature. McKINLEY-SMITH CO., Dept. T5, Box 3038, San Bernardino, Calif.

FIRE ALARMS FOR HOMES AND SHOPS. \$9.25 ppd., additional heat detector \$1.25 each; special quotation to jobbers and distributors. KAMCO-ELECTROCHEM CO., 2712 N. Magnolia, Chicago 14, Ill.

DON'T BUY HI-FI COMPONENTS. Kits, Tape, Tape Recorders until you get our low, low return mail quotes. "We Guarantee Not To Be Undersold." Wholesale Catalog Free. HI-FIDELITY CENTER, 1797RC First Avenue, New York 28, N.Y.

COMPONENTS, Recorders, Tapes, FREE Wholesale Catalogue. CAIRSTON, 215-T East 88th St., New York 28, N.Y.

DISCOUNTS UP TO 50% on HI-FI amplifiers, tuners, speakers, tape recorders, individual quotations only, no catalogs. CLASSIFIED HI-FI EXCHANGE, 2375 East 65th Street, Brooklyn 34, N.Y.

HI-FI DOCTOR will solve your hi-fi problems on the spot. Acoustic, Audio, Radio Engineer, Stereo Designing. Professional visits, day evening, New York area. WILLIAM BOHN, Plaza 7-8569, weekdays.

AMPEX, Concertone, Crown, Magnecord, Presto, Norelco, Bogen, Tandberg, Sherwood, Rek-O-Kut, Scott, Shure, Dynakit, others. . . . Trades. BOYNTON STUDIO, Dept. RE, 10 Pennsylvania Ave., Tuckahoe, N.Y.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean radio and TV receiving, transmitting, special-purpose, Magnetrons, Klystrons, broadcast types, etc. Want military & commercial lab/test and communications equipment such as G.R., I.L.P., AN/UIPM prefix. Also want commercial receivers and transmitters. For a fair deal write BARRY, 512 Broadway, New York 12, N. Y. WALKER 5-7000.

QUALITY PRINTING. Economically priced. Speedy service. Free samples on request. JOHN H. TAYLOR, R. D. 2, Box 215, West Middlesex, Pa.

NEW, TRANSISTORIZED SIGNAL GENERATOR, 150 KC. to 120 MC. on fundamentals. Battery operated. Internal 400 cycle, any external audio modulation. Socket for Citizens Band Crystals. Send for free information. PEL ELECTRONICS, Box 555, Ridgewood, N. J.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. New and used instruments bought, sold, exchanged. HAZELTON INSTRUMENT CO., 128 Liberty Street, New York, N.Y.

ATTENTION—LEARN THE MORSE CODE IN MINUTES BY A PROVEN METHOD. Copyright 1960, send \$2.00 to: EASY METHOD MORSE SYSTEM, Box 86, Perrysburg, Ohio.

DIAGRAMS FOR REPAIRING RADIOS, television \$2. Give make and Model, DIAGRAM SERVICE, Box 672 RE, Hartford 1, Conn.

RADIO-ELECTRONICS

that it does not seem possible to cover them all clearly in a single volume. Yet these two professionals have done just that. They discuss the planning and techniques of monaural and stereo components, systems, interconnections, acoustics, noise problems, etc. The esthetic viewpoint is well represented. The reader learns the elements of design, color, styling, size and shape. Photos and diagrams illustrate the text.

The book is written for the hi-fi fan as well as the professional installer. Cabinet construction, finish and repair are described. One chapter is devoted to legal considerations including the basic facts of business life, codes, liabilities, etc.

Before you undertake building into, drilling or wiring a wall, you should consult the final chapter. It discusses and illustrates the masonry construction, wood frames and steelwork that make up walls, windows and doors.

MASERS, by Gordon Troup. John Wiley & Sons, Inc., 440 Fourth Ave., New York 16, N.Y. 4 x 6 1/2 in. 168 pp. \$2.75.

The maser has but a few outstanding features compared with other types of amplifiers and oscillators. However, low noise and precision frequency make it unbeatable for applications such as long-range radar, radio astronomy, microwave spectroscopy and time measurement.

The author approaches his subject by way of quantum mechanics and thermodynamics. He discusses excitation methods and derives equations pertaining to

gain, bandwidth and noise. He reviews experimental results obtained by scientists and indicates the work still to be done.—IQ

MAGNETIC AMPLIFIERS, by Paul Mali. John F. Rider Publisher, Inc., 116 W. 14th St., New York 11, N.Y. 5 1/2 x 8 1/2 in. 101 pp. \$2.45.

This book discusses basic principles of magnetic circuits as well as magnetic amplifiers. Clearly written and containing many illustrations, it explains the various types of devices and shows how they are used to control, switch, compute and memorize. A good first book on the subject for technicians and students. END



"They all broke down at the same time"

TV PICTURE TUBES AT LOWEST PRICES

ALL ALUMINIZED GLASS TYPES

Tube Type	Price With Old Tube	Tube Type	Price With Old Tube	Tube Type	Price With Old Tube
10EP4	7.95	17BJP4	11.50	21CEP4	21.00
121P4	8.95	17CP4	11.50	21CXp4	15.75
14AJP4	14.00	17CK/CA 8Z	17.00	21DEP4	21.00
14ATP4	14.00	BRP4	17.00	21DFP4	21.00
14E/CP4	10.00	17DLP4	17.00	21DLP4	21.00
14HP4	11.00	17H/RP4	12.50	21DP4	21.00
14QP4	11.00	17L/VP4	12.50	21EP4	14.25
14RP4	11.00	17OP4	11.50	21FP4	14.50
14W/ZP4	11.00	20C/DP4	13.50	21WP4	16.00
14XP4	11.60	20H/MP4	14.50	21XP4	16.50
16DP4	12.00	21AC/BS	15.75	21YP4	16.00
16K/VP4	9.95	AMP4	15.75	21ZP4	15.50
16LP4	12.50	21AL/ATP4	16.75	24C/VP4	23.50
16TP4	9.95	21AU/AVP4	16.75	24AEP4	24.50
16WP4	12.00	21AWP4	15.75	24HP4	25.50
17AT/AVP4	12.50	21BTP4	15.75	27EP4	39.95
17BP4	9.95	21CBP4	16.75	27FP4	39.95
				27SP4	40.95

METAL TYPES

12UP4	12.00	16GP4	14.50	19AP4	16.00
13AP4	13.50	17CP4	17.00	19TP4	19.75
16EP4	14.00	17GP4	17.60	21WP4	20.75
		17TP4	17.60		

TEST TUBES

8XP4	16.07	8YP4	16.07
------	-------	------	-------

Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.

ALL PRICES FOB CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25¢ deposit required on C.O.D. shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express. Shipped only to Continental U.S. and Canada.

WRITE FOR COMPLETE LIST

—PICTURE TUBE OUTLET—
2922 MILWAUKEE AVE., CHICAGO 16, ILLINOIS
Dickens 3-2648

LEARN TO DRAW; READ BLUEPRINTS, SCHEMATICS, WIRING DIAGRAMS; and to render any Mechanical, Electronic, Architectural & Art Drawing or Painting

SELF STUDY COURSES & Drafting Room Essentials available in simplified form: Plan 1: Send \$2.25 for any one of the above desired "Individual" chapter. Plan 2: Send \$9.00 for the "Special Metal Chapters" of our book entitled, "Encyclopedia of Drawing & Design" (for Home Study or School Text).

Publisher: (Author's experience: Chief Draftsman, Art Director. Engineer. LOUIS D. PRIOR, INC., 23-09 169th Street, Whitestone 57, New York, N. Y.

HI-FI RECORDING TAPE

Splice Free (except 2400')
15 day money-back guarantee

1200' 7"	Acetate	3.29	12-	12-	24-
1800' 7"	acetate	1.79	1.59	1.17	\$1.09
1800' 7"	mylar	2.09	1.99		1.85
2400' 7"	mylar	3.29	2.99		2.75
2400' 7"	tensitized mylar	4.25	3.95		3.75

Can Be Assorted, Add 15¢ Postage Per Reel.
10¢ For 24+ Lot Orders.

HI-FI COMPONENTS TAPE RECORDERS available from wide variety of stock and shipped within 24 hours. Write for free wholesale catalogue. "WE WILL NOT BE UNDERSOLD." Write us and see why.

CARSTON 125-RO East 88 St. New York, 28, N. Y.

The January issue of Radio-Electronics will be on sale Dec. 15. Order your copy from your dealer now.

MAKE MONEY IN SPARE TIME Learn at Home to Fix ELECTRIC APPLIANCES

Tester Furnished—No Extra Charge. Fix toasters, irons, fans, other electric appliances for friends and neighbors. Make money in spare time or build your own full time business. SAVE cash by repairing your own appliances. Enjoy the security of a skill to fall back on during slack periods, seasonal layoffs, when you retire. NRI will train you at home. MAIL COUPON NOW. Sample Lesson and Catalog FREE.

National Radio Institute, Dept. FNO, Wash. 16, D. C.
Please send me Electrical Appliance sample lesson and catalog FREE (No Salesman Will Call).

Name.....Age.....
Address.....
City.....Zone.....State.....

Olson

FREE!

Olson Radio Catalogs FOR ONE YEAR

★ 8 Different Issues
★ All Bargain Packed

FREE One Year Subscription to OLSON RADIO'S Fantastic Bargain Packed Catalog—Unheard of LOW, LOW WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

Another OLSON Bargain!

RADIO-INTERCOM

- Radio with Remote Speaker
- It's a Two-Way Intercom

No. RA-341 **\$15.93**
3 for \$45.00
Lots of 12, Ea. \$14.00

5-tube superheterodyne radio in handsome ivory case with built-in PM speaker, 50 feet of cable and remote speaker. 4-position function switch selects operation as radio, radio with remote speaker, and talk or listen in intercom position. Radio tunes standard (AM) broadcast band (530 to 1600 KC). Tiny 2 1/2" remote speaker is mounted in a matching ivory cabinet (only 2 1/2"x3"x1 1/2") and has a jack for easy connection to the radio-intercom. When used as an intercom, it is so sensitive, it picks up the ticking of a clock on the other side of the room. Master station size: 5 1/2"x3 1/2"x4 1/2". For 117 volts A.C. or D.C.

MAIL COUPON TODAY

Fill in coupon below for your FREE one year subscription to Olson's Bargain Packed Catalog. To order Radio Intercom, simply check quantity desired and send remittance along with coupon. (Include enough for postage or parcel post shipment. Send \$2.00 deposit for C.O.D. orders.)

FREE Olson Catalogs for One Year
 Radio-Intercom RA-341 Ea. \$15.93
 Lots of 12, Ea. \$14.00
 3 for \$45.00

NAME.....
ADDRESS.....
CITY.....ZONE.....STATE.....

OLSON RADIO CORPORATION
714 S. Forge St., Akron 8, Ohio

1960 ANNUAL INDEX

Vol. XXXI, January-December, 1960

RADIO-ELECTRONICS

A

About Those Color TV Controls (Middleton)	Jun	80
Air Ionizers (McKay)	Jul	32
Alarms—See Electronic(s); Alarms		
Amplifier Test-Load Box (Smith)	Nov	98
Another Forgotten Inventor [Wilkerson] (Leslie)	Jun	47
Antennas—See Radio, Television		
Audio		
Attenuator-Padder for Low-Level Testing (Reed)*	May	46
Comparator (Pugh)	Jul	39
Generator for Industrial Service Jobs (Kernin)*	Mar	60
Wattmeter from Vtvm (Casey)	Aug	31
Corres	Oct	26

AUDIO—HIGH FIDELITY

AM Broadcasting Station, Hi-Fi	Feb	43
AMPLIFIERS—See also Audio, Stereo		
Bias Circuit, Class-B (NC)	Jan	139
Cathode-Follower (NC)	Jul	111
Combination Does 3 Jobs (Dalley)*	Sep	36
Hum Reduction	Mar	46
Low-Cost, Starved-Current (Lederer)*	Aug	36
New at New York Show	Dec	83
Postage-Stamp (Bohr)*	May	59
Power, for Ac-Dc Sets (Dewar)	May	60
6DZ7 (Voss)*	Nov	40
Transistor (NC)	Sep	120
Twin-Coupled		
High Power for (Crowhurst)*	Oct	34
Updating R-E (Crowhurst)*	Jun	30
Video-Audio	Mar	49
Cabinets, Retouch, Repair, Refinish (Markell)		
Part I	Mar	109
Part II	Apr	60
Circuits, New Developments (Scott)	Mar	47
Cityrama, Multilingual Tourist Bus	Mar	46
Feedback Tone Control (NC)	Jul	111
FM—See FM		
Headphones for TV (Rasmussen) (NC)	Jan 56;	Feb 148
Intercom, Automatic Doorbell (Kampf)*	Sep	34
Intercoms and Boat Hailers Improved by Transistors (Scott)	Aug	34
Intermodulation Indicator (Pat)	Aug	100
Kits, Turntable and Pickup-Arm (Graham)	Mar	44
Labs Help Teach Languages, Electronic (Johnson)	Jun	33
Lows Are Directional Too	Mar	49
Megaphones, Two (NC)	Feb 148;	Oct 112
Microphone		
Electro-Voice 644 Sound Spot (WN)	Feb	61
Hidden (Pat)	Jul	109
Mixing and Matching to Audio Inputs	Jul	88
New at New York Show	Dec	82
Night Switch (Bemis)*	May 64;	(NC) Dec 117
Organ, Electronic (WN)	Jun	63
Oscillator, Tunnel-Diode (Grossman and Friedman)*	Sep	40
Output Wait, What Is (Graham)	Jan	60
Output Transformers, Puzzled About? (Crowhurst)	Dec	33
PA Systems		
Feedback in, Stop (Schroeder)	Feb	40
Improving (Sands)	Nov	71
Phase Inverter, High-Gain	Mar	48
Pickup Arm, Vacuum Cleaner Built in (WN)	Sep	59
Pickup Arms, Turntables from Kits (Graham)	Mar	44
Preamp Input Circuit	Dec	40
Preamps, Design Your Own (Crowhurst)		
Part I—Losser, Feedback Equalizer Circuits	Jan	53
Part II—Tone Controls	Feb	47
Part III—2-Stage Feedback Tone Control	Mar	54
Part IV—Volume and Loudness Controls	Apr	87
Part V—Putting the Pieces Together	May	61
Corres	Dec	21
Records and Record Changers		
Record of Future? (Corres)	May	26
Record and Tape Reviews (Santon)	Jan 61;	Feb 50;
Jan 57	Mar	57
Jan 57	Jan	57
Stroboscope Flasher (Taylor)	May	35
Upside Down	Dec	82
Reflex Stage (Pat)	May	130
Reverberation, and Now	Aug	43
Reverberation, Tape Recorder with Rumble Filter (Zenith)	Dec	82
Jul	Jul	95
Service—See Servicing, Audio		
Show Stirs Controversy	Sep	33
Sound at Cocktail Party	Oct	78
Speaker(s)		
Burnout, Zener Diodes Prevent (Ives)	Aug	42
Core, New Speaker Has No	Apr	94
Electrostatic, New	Dec	82
Flattest? (NB)	Sep	6
Lighthouse, Loudspeaking (WN)	Feb	61
More Bass from Smaller (Crowhurst)		
Part I—Miniaturizing Speakers and Enclosures; Principles	Jul	81
Part II—5 More Ways of Getting More Bass	Aug	37
Corres	Oct	26
Response Curves, How Valid (Augsburger)	Mar	50

KEY TO SYMBOLS AND ABBREVIATIONS

* Construction Articles	
† Section of Full-length article	
Cl	Television Clinic
Corr	Correction
Corres	Correspondence
NB	News Briefs
NC	Noteworthy Circuits
Pat	New Patents
Tech	Techniques
TTO	Try This One
WN	What's New

Regular departments not itemized are Business and People, New Books, New Literature, New Products, Technicians' News.

Single Transistor Operates 8-Inch, for Radio (Grace)*	Oct	52
Wall of Sound	Aug	33
Woofers and Tweeters, No More? (NB)	Feb	6
Stereo		
At 100 Cycles (NB)	Dec	10
Amplifiers		
RCA's 2-Way (Scott)	Feb	44
Simple (NC)	Nov	19
Video-Audio	Mar	49
Committee Out (NB)	Apr	6
Design (WN)	Mar	43
Ear Not Fooled	May	58
FM-AM (RCA TPM-13)†	Jul	95
FM Distortion Eliminator†	Mar	47
Magnavox	May	72
Motorola†	May	70
PA at Newport (Allison)	Dec	53
Packages, New Features (Scott)	May	68
Pickups, New (Hirsch)		
Part I—Ceramics	Sep	30
Part II—Grado Master, Neumann DST, Dynaco A-12, G-E VR-22, London-Scott 1000	Oct	48
Part III—ESL C99 Micro/Flex, Empire 88, Pickering 380, Shure M212/M216, Stereotwin 210/D, Fairchild SM-1	Nov	52
Preamp, Transistor (Meyer)*	Dec	45
Record Demonstrator† (WN)	Dec	44
Simplified (Pat)	Apr	112
Speaker, Third, Add Easy Way (Burstein)	Oct	45
Standards Soon (NB)	Nov	12
System, Test to Single Out Best	Sep	58
Tape and Tape Recorders		
4-Track, Matchbox-Size (Johnson)*	Jul	76
Corr	Sep	116
1 7/8 ips†	May	58
Three-Channel†	May	70
Underwater (NB)	Oct	12
Zenith	May	68
Swedish System Combines Amplifier, Speakers (WN)	Jul	45
Tape and Tape Recorders		
Bulk Eraser (McKay)	Apr	98
Micro-Inch, Not Micron (Corres)	Feb	22
Reverberation†	Dec	82
Special Effects (Larson)	Aug	40
Strobe for (McCormick)	May	40
"Talkie" Outfit for Slide Projectors (Costigan)*	Jun	36
Thermoplastic Recording (NB)	Mar	6
Tips, Four (Stillwell and Comstock)	Sep	39
Word Puzzle (Comstock)	Feb	43
Wow (Tech)	Sep	114
TV Audio into Hi-Fi Systems, Feed (Leonard)	Mar	56
Transformers, Using (Ravenswood)	Apr	100
Transistors in Audio (Part II—Distortion in Amplifiers) (Ravenswood)	Jan	62
Tuner, Wide-Band (Pat)	Jun	106
Turntables and Pickup Arms from Kits (Graham)	Mar	44
Wired Broadcasts in Italy	Jan	59
Automobile		
Radio—See Radio, Auto		
Solar-Powered (WN)	Jun	63
Voltage Regulator, All-Transistor (Meyer)*	Feb	107
Corres	Apr	22
Automatic		
Ac Vtvm (Marshall)	Aug	26
Doorbell Intercom (Kampf)*	Sep	34
Recycling Timer (Fannon)*	Jul	36
TV Brightness Control, New (Maxwell)	Sep	91

Balancing for Better Motors, Electronic (Essex)	Feb	58
Be Careful with Ignitrons (Lytle)	Dec	70
Benchmark Can Be Tricky (Middleton)	Apr	52
Better Photos with Transistor Slave Flash (Merkler)*	Oct	39
Better Power Pentodes	Jun	37
Better Yet, Use Spiral (Jaski) (Corres)	Jan	26
Boat Hailers and Intercoms Improved by Transistors (Scott)	Aug	34
BOOKS, NEW	Jan 152; Feb 154; Mar 146; Apr 134; May 136; Jun 128; Jul 120; Aug 119; Sep 134; Oct 130; Nov 130; Dec 128	
Boost Bridge Accuracy with Null Amplifier (Frantz)*	Aug	32

Brightness Control, New Automatic TV (Maxwell)	Sep	91
Build This Transistor Auto Radio (Martin)*	Mar	40
Building Own Citizens Radio (Sands)*	Jan	110
BUSINESS AND PEOPLE	Jan 149; Feb 150; Mar 140; Apr 129; May 131; Jun 123; Jul 116; Aug 115; Sep 125; Oct 125; Nov 121; Dec 122	

C


Cabinet Repair, Rapid (Bohr)	Feb	118
Cabinet, Retouch, Repair, Refinish (Markell)		
Part I	Mar	109
Part II	Apr	60
Cable Checker, Handy (Smith)	Mar	71
Calibration Signals, Identify (Ives)*	Sep	56
Capacitance Relay, Transistor (Turner)	Oct	54
Capacitance Meter (Sutton)*	Dec	90
Capacitor Test Box Finds Intermittents (Fred)	Jul	44
Car—See Automobile; Radio, Auto		
CB Transceiver Circuitry (Scott)	Sep	52
Challenge to Americans (Thach)	Apr	32
Characteristic Impedance, What's With? (Middleton)	Mar	74
Corres	Jun 18; Jul 22; Sep 21; Dec 21	
Citizens Band—See Radio, Citizens Band		
Cityrama, Multilingual Tourist Bus	Mar	46
Clamp Type Ac Microammeter	Feb	39
Classroom, Electronics in (Prensky)	Mar	76
Code Oscillator, Economy (Martin)	Feb	128
Combination Amplifier Does 3 Jobs (Dalley)*	Sep	36
Conelrad Alert Monitor (Reed)*	Jan	108
Crystal Oscillator, Multipurpose Transistor (Merkler)*	Jan	82
Corres	May	28

D

Decade Amplifier, Measure Millivolts with (Henry)*	Sep	94
Design Your Own Preamp (Crowhurst)		
Part I—Loss, Feedback Equalizer Circuits	Jan	53
Part II—Tone Controls	Feb	47
Part III—2-Stage Feedback Control	Mar	54
Part IV—Volume and Loudness Controls	Apr	67
Part V—Putting Together	May	61
Corres	Dec	21
Direction Finder, Poor Man's (Craig)	May	94
Divide and Multiply with Wheatstone Bridge (Frantz)*	Jun	48
Doorbell Intercom, Automatic (Kempf)*	Sep	34
Double Value from Your Vtvm (Guertin)	Apr	73
Dress Up That Meter (Henry)*	Jun	94
Duo-junction (Queen)*	Oct	51

E

Economical Highway FM (Borzner)*	Nov	56
EDITORIALS (by Hugo Gernsback unless otherwise stated)		
Around the World in 80 Seconds (M. Harvey Gernsback)	Jul	25
Automation in Electronics	Jan	31
Brain an Electronic Computer (Stafford-Clark)	Mar	33
Future Space Traffic	Nov	33
How Far Amplification	Dec	27
Instructive Electronic Devices	Oct	53
Interstellar Communication	Sep	29
Inventions Wanted	May	31
Microelectronics	Feb	33
Corres	Jul	18
Microtelevision	Aug	25
Millions of Electronic Facts (Corres)	Feb	22
Recording the Invisible	Jun	29
Superception	Apr	31
Corres	Jul	18
Electromyography (Post)	Nov	34
Electron-Ray Tube, Versatile (Shields)*	Mar	64
ELECTRONIC(S)		
Air Ionizers (McKay)	Jul	32
Alarms		
Clock Radios (Maxwell)	Feb	115
Flare Flashes Warning Signals (Kaufman)*	Mar	72
Headlight Tattletale (Young)	Apr	41
Lifeguard (WN)	Mar	43
Power-Line (Pat)	May	130
Proximity Relay (D'Airol)*	Sep	48
Sleep (NC)	May	124
Amplifier(s)		
Direct-Coupled (Pat)	Nov	100
Fluid	Aug	56
Laser, Light Amplifier (NB)	Sep	10
Magnetic (Pat)	Jul	109
Microwave, Most Sensitive (NB)	Jun	6
Pulse, Diode (Pat)	Feb	137
Arc, 5,000,000-Amp	Sep	45
Corr	Nov	118
Automation in Post Office (NB)	Dec	14
Balancing for Better Motors (Essex)	Feb	58
Ball Lightning for Defense (NB)	Dec	6
Battery (ies)		
Nickel-Cadmium, How Live? (Rhita)	Oct	38
Rechargeable (WN)	Apr	62
Reserve Power for Survival (Prensky)	Jul	96
Silver-Mercury for Portable TV (NB)	Apr	6
Blinker, Light (NC)	Mar	137
Corr	Jun	110
Boating and (NB)	Mar	6
Boats, Small, Electronics Goes to Sea in (Garden)	Jul	29

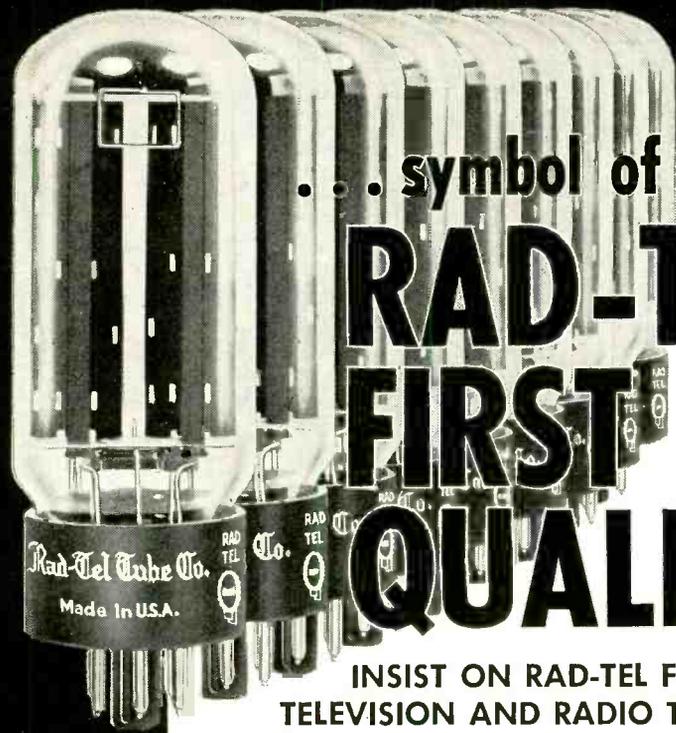

... symbol of
RAD-TEL
FIRST
QUALITY

INSIST ON RAD-TEL FOR EVERY TELEVISION AND RADIO TUBE NEED

TRANSISTORS

at fabulous discounts

RF MIXER and IF **49¢** ea.

AF DRIVER and OUTPUT **39¢** ea.

AUTO TYPE **80¢** ea.
 POWER OUTPUT

HIGH POWER **\$1.40** ea.
15 AMP Collector Current

Up to 75% OFF on BRAND NEW TUBES

GUARANTEED ONE FULL YEAR!

You Can Rely On Rad-Tel's Speedy One Day Service!

Not Used — Not Pulled Out Of Old Sets • Each Tube Individually and Attractively Boxed!

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	024M	.79	—	3DT6	.50	—	6AB4	.46	—	6E08	.79	—	12A4	.60	—	12EG6	.54
—	1AX2	.62	—	3Q5	.80	—	6AC7	.96	—	6E88	.79	—	12AB5	.55	—	12E26	.53
—	1B3GT	.79	—	3S4	.61	—	6AF3	.73	—	6H6GT	.58	—	12AC6	.49	—	12F5	.66
—	1DN5	.55	—	3V4	.58	—	6AF4	.97	—	6BN4	.57	—	12AD6	.57	—	12F8	.66
—	1G3	.73	—	4BC5	.56	—	6AG5	.65	—	6BN6	.74	—	12AE6	.43	—	12FM6	.45
—	1J3	.73	—	4BC8	.96	—	6AH6	.99	—	6BQ5	.65	—	12AF3	.73	—	12BQ6	1.06
—	1K3	.73	—	4BN6	.75	—	6AK5	.95	—	6BQ6GT	1.05	—	12AF6	.49	—	12BY7	.74
—	1L6	1.05	—	4BQ7	.96	—	6AL5	.47	—	6BQ7	.95	—	12A16	.46	—	12BZ7	.75
—	1LN5	.59	—	4BS8	.98	—	6AM8	.78	—	6BR8	.78	—	12A15	.45	—	12C5	.56
—	1R5	.62	—	4BU8	.71	—	6AN4	.95	—	6BU8	.70	—	12A18	.95	—	12CA5	.59
—	1S5	.51	—	4BZ6	.58	—	6AN8	.85	—	6BY6	.54	—	12A25	.52	—	12CN5	.56
—	1T4	.58	—	4BZ7	.96	—	6AQ5	.50	—	6BZ6	.54	—	12A26	.43	—	12CR6	.54
—	1U4	.57	—	4CS6	.61	—	6AR5	.55	—	6BZ7	.97	—	12A27	.76	—	12CU5	.58
—	1U5	.50	—	4DE6	.62	—	6AS5	.60	—	6C4	.43	—	12A28	.76	—	12CW6	.69
—	1X2B	.82	—	4OK6	.60	—	6AT6	.43	—	6CB6	.54	—	12A29	.57	—	12CX6	.54
—	2AF4	.96	—	4OT6	.55	—	6AT8	.79	—	6CD6	1.42	—	12A30	.57	—	12DB5	.69
—	3AL5	.42	—	5AM8	.79	—	6AU4	.82	—	6CF6	.64	—	12A31	.41	—	12DE8	.75
—	3AU6	.51	—	5AN8	.86	—	6AU6	.50	—	6CG7	.60	—	12A32	.75	—	12DL8	.85
—	3AV6	.41	—	5AT8	.80	—	6AU7	.61	—	6CG8	.77	—	12A33	.67	—	12DM7	.67
—	3BA6	.51	—	5BK7A	.82	—	6AU8	.87	—	6CM7	.66	—	12A34	.63	—	12DQ6	1.04
—	3BC5	.54	—	5BQ7	.97	—	6AV6	.40	—	6CN7	.65	—	12A35	.86	—	12L6	.58
—	3BE6	.52	—	5BR8	.79	—	6AW8	.89	—	6CR6	.51	—	12A36	.63	—	12M6	.70
—	3BN6	.76	—	5CG8	.76	—	6AX4	.65	—	6CS6	.57	—	12A37	.50	—	12N6	.83
—	3BU8	.78	—	5CL8	.76	—	6AX7	.64	—	6CU5	.58	—	12A38	.67	—	12O6	.61
—	3BY6	.55	—	5E8	.80	—	6BA6	.49	—	6CUG	1.08	—	12A39	.67	—	12P6	.61
—	3BZ6	.55	—	5E8	.80	—	6BC5	.54	—	6CY5	.70	—	12A40	.67	—	12Q6	.61
—	3CB6	.54	—	5J6	.68	—	6BC7	.94	—	6CY7	.71	—	12A41	.67	—	12R6	.61
—	3CF6	.60	—	5T8	.81	—	6BC8	.97	—	6DA4	.68	—	12A42	.67	—	12S6	.61
—	3CS6	.52	—	5U4	.60	—	6BD6	.58	—	6DB5	.69	—	12A43	.67	—	12T6	.61
—	3CY5	.71	—	5U8	.81	—	6BE6	.55	—	6DE6	.58	—	12A44	.67	—	12U6	.61
—	3DK6	.60	—	5V6	.56	—	6BF6	.44	—	6DG6	.59	—	12A45	.67	—	12V6	.61
—			—	5X8	.78	—	6BG6	1.66	—	6DQ6	1.10	—	12A46	.67	—	12W6	.70
—			—	5Y3	.46	—	6BH6	.65	—	6DT5	.66	—	12A47	.67	—	12X6	.70
—			—			—	6BH8	.87	—	6DT6	.53	—	12A48	.67	—	12Y6	.70
—			—			—			—			—	12A49	.67	—	12Z6	.70
—			—			—			—			—	12A50	.67	—		

SEND FOR FREE TROUBLE SHOOTER GUIDE AND NEW TUBE & PARTS CATALOG.

NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY.

RAD-TEL TUBE CO.

55 Chambers St
 Newark 5, N. J.

TERMS: 25% deposit must accompany all orders — balance C. O. D.
 \$1 HANDLING CHARGE FOR ORDERS UNDER \$5. Subject to prior sale.
 Please add postage. No C. O. D.'s outside continental U. S. A.

RE-T260

ELECTRONICS (Cont'd)

Camera Takes Movies	Jul	33
Carrier Current, Squelched (Pat)	Apr	110
Challenge to Americans (Thach)	Apr	32
Classroom	Dec	81
Classroom, Electronics in (Prensky)	Mar	76
Comparator, Diode (Pat)	Jul	109
Computer(s)		
Adder (Pat)	Nov	99
Automatic Industrial (NB)	Mar	16
Memory Drum, Miniature (WN)	Nov	63
Party Line Next? (NB)	Oct	16
Rally-Pal (Allison)*	Nov	46
Talks Back (NB)	Mar	6
Ultrafast (NB)	Apr	12
Control(s)		
Model-Train	Feb	114
Level of Molten Glass (Barlowe)	Mar	52
Cooling Electric Blanket (Pat)	Oct	118
Cyclotron, Desk-Size (NB)	Dec	6
Diffraction Pattern (WN)	Aug	73
Diodes—See Semiconductors; specific subject		
Elevators Direct Passengers (NB)	Oct	10
Facsimile Mail (NB)	Jan	18
Fishing, Electronics Goes (Milanowski)	Jan 36; (NB)	Mar 40
Flash, Better Photos with Transistor Slave (Merkler)*	Oct	39
Flash-Unit Control (NC)	Aug	98
Flasher (Pat)	Jul	109
Fuel Cell†	May	57
Goes Down to Sea (in Small Boats) (Garden)	Jul	29
Handwriting, Machine Reads (NB)	Jan	14
Highlights of 1959 (NB)	Jan	6
Ignition System (Pat)	Jan 143; (Pat)	Dec 113
Impedance, What's with Characteristic? (Middleton)	Mar	74
Corres	Jun 18; Jul 22; Sep 21;	Dec 21
Indicator, Miniature	Sep	49
Industrial—See Industrial Electronics		
Infrared Guides Missiles (Spencer)	Jan	96
Corres	May	22
Inventor, Another Forgotten [Wilkerson]? (Leslie)	Jun	47
Ion Engine (NB)	Mar	16
Jets and (NB)	Feb	6
Lamp, Smallest Incandescent (WN)	Apr	62
Language(s)		
Labs for Schools (NB)	Oct	16
Labs Help Teach (Johnson)	Jun	33
Machines Translate (NB)	Jul	8
Latching Circuit Uses Standard Relay (NC)	Mar	136
Light Amplifier—Laser (NB)	Sep	10
Luna Part of Signal System	Apr	45
Magnetohydrodynamic Generation of Power (NB)	Jan 8; †May	57
Maser Amplifies Light (NB)	Dec	8
Medicine		
Alertness Indicator (Pat)	Sep	118
Body Parts (NB)	Feb 18; Oct	10
Cardiac Pacemaker (WN)	Jun	62
Electromyography (Post)	Nov	34
Heart, Auxiliary	Dec	58
Heart, Electronics Can Save (Post)	May	54
Heartbeat Timer (NB)	Jan	18
Human Body Broadcaster?†	May	58
Knee Noise Signals Arthritis (NB)	Nov	14
Larynx, Artificial (WN)	Dec	44
Meeting (NB)	Nov	6
Mouse Transmits Own Temperature (Griffith)*	Feb	101
Probe (NB)	Feb	6
Radio Beam Injurious (NB)	Jul	6
Radio Waves and Life (Jaski)	Sep	43
Corres	Nov	30
Stereo for Unborn (NB)	May	6
Telemetered Humans (NB)	Nov	6
Telemetered Teeth (NB)	Apr	18
TV Fluoroscope	Sep	42
Metal Detector, Underwater (Richardson)*	Jul	30
Corres	Sep 21; Oct	21
Metals, Electrons Weld (NB)	Nov	20
Metals, Saltwater Cuts (NB)	Jan	6
Microminiature Circuits (NB)	Feb	10
Micromodules, Today and Tomorrow (McQuay)	Feb	96
Microwave Link to Alaska (NB)	Jan	8
Miniaturization to Molecular Level (NB)	Jan	14
Missile(s)		
Control and Guidance (Hobbs)	Aug	60
Infrared Guides (Spencer)	Jan	76
Corres	May	22
Measurements (Pat)	Nov	99
Tracking, Accurate (NB)	Sep	6
Motion Study, Ultrasonic (Pat)	Sep	119
Movie Camera and Projector Records Sound on 8-mm Film (WN)	Apr	62
NEWS (Redgrave)	May	48
Nuclear-Blast Detector (NB)	Jun	6
Oscillator, Stable (Pat)	Sep	119
Microwave (Pat)	Dec	114
PNP-NPN Transistor (Merkler)*	Nov	91
Ovens, No More!	Aug	49
Paris Meet (Garcin)	Jun	46
Phone Scrambler, Portable (WN)	Dec	44
Photos, Aerial, Rapid (NB)	Apr	8
Power		
Booster (WN)	Aug	73
Four New Sources	May	57
Thermionic Converter	†May 57; (NB) Nov	6
Thermoelectric Generator	†May 57; (WN) Jun	62
Prefixes, New (NB)	Apr	6
Printed Circuits, Inductors for (WN)	Nov	63
Pulse Integrator, Transistor (NC)	Nov	119
Radar—See Radar		
Radiation Detector (Pat)	Nov	100

ELECTRONICS (Cont'd)

Radiation Detector, New Semiconductor (Shuman)	Apr	42
Radio Stars, Locating (NB)	Jun	6
Radio Telescope, Largest (WN)	Mar	43
Rectifier: Stack, Simplified (NC)	Aug	99
Relay(s)		
Capacitance, Transistor (Turner)	Oct	54
Latching Circuit Uses Standard (NC)	Mar	136
Proximity (D'Airo)*	Sep	48
Touch-Plate (NC)	Jun	107
Using 24-28-Volt Dc (Oberto)	May	35
Resistance Calculator, Parallel/Series (Salva)*	Aug	72
Resistor, Adjustable Fixed	Apr	37
Satellite(s)—See also Electronic(s), Space Communications via (NB) Mar 6; May 6; Oct 6	Mar 6; May 6; Oct 6	
Courier First Space Station (NB)	Mar	6
Fifty Asked for (NB)	Sep	12
Navigation, in Orbit (NB)	Jun	12
Picture Bounced Off Echo I (WN)	Dec	44
Pioneer V, Remote Control of (NB)	Jul	6
Reflecting Ring to Orbit Earth? (NB)	Oct	10
Telemetry System (WN)	Apr	62
Three Dishes	Dec	62
TIROS in Sky (Steckler)	Jun	86
Weather Eye (WN)	Aug	73
Semiconductors—See Semiconductors		
SOFAR Underwater Distance Record (NB)	Oct	12
Solar		
Cells, How to Make (Chapin)	Mar	39
Dish Powers Radio Network (WN)	Sep	59
Powered Auto (WN)	Jun	63
Powered Oscillator (NC)	Mar	136
Space		
Antenna, Low-Noise (WN)	Jun	63
Humans Telemetered (NB)	Nov	6
Ionized Band Encircles Earth (Warshaw)	Jun	38
Luna Part of Signal System	Apr	45
Magnetic Cloud (NB)	Jun	6
Magnetometer at Work in Outer Space (Mansir)	Apr	38
Messages, Trying to Intercept (NB)	May	18
Mobot Mark I (WN)	Feb	61
Saturn, Signals from (NB)	Nov	20
Sun, Signal Reflected from (NB)	Apr	10
Sunspot Peak Past (NB)	Apr	12
USSR Timetable (NB)	Feb	14
Stroboscope, Battery-Operated (NC)	Jul	110
Supply, Voltage-Limited (NC)	Oct	113
Switch, FluxLink (NB)	May	6
Telemeter, Ignition Operated (Schotz)*	Dec	54
Telephone Cable, Long (NB)	Apr	6
Telephone Service Expanded (NB)	Oct	16
Thermometer, Acoustic (NB)	Sep	12
Thermostat (Pat)	Aug	100
Thermostat, Transistor (Pat)	Sep	119
Timer, Automatic Recycling (Fannon)*	Jul	36
Darkroom (NC)	Apr	127
Corr	Jun	106
Integrating (Shields)*	Dec	28
Transformer (Woods)*	Jun	98
Transformers, Smallest (WN)	Sep	59
Ultrasonics Measures Liquid Flow†	May	58
Voltage Regulator for Car, All-Transistor (Meyers)*	Feb	107
Corres	Apr	22
V-R Pulse Circuit (Pat)	Nov	99
Waveguide, Transoceanic (NB)	Mar	6
Weather Station, Unmanned (WN)	Jul	45
Wheatstone Bridge, Divide and Multiply with (Frantz)*	Jun	48
Equipment Can Be Easy to Service	Sep	46
Experimenter's Dual Electroscop (Moen)*	Jun	99
F		
Feed TV Audio into Hi-Fi Systems (Leonard)	Mar	56
Feedback in PA Systems, Stop (Schroeder)	Feb	40
Field-Check Color CRT's (Egan)	Jun	96
50 Years Ago	Jan 107; Feb 149; Mar 132; Apr 138; May 111; Jun 93; Jul 113; Aug 111; Sep 124; Oct 124; Nov 120; Dec 116	
Fix Radios Faster (and Make More Money) (Darr)	Nov	43
Fix That Multimeter (Bohr)	Jan	74
Flare, Electronic, Flashes Warning Signals (Kaufman)*	Mar	72
FM		
-AM		
Detector Switching (Blonder-Tongue R-98)†	Jul	94
Portable, All-Transistor	Jun	52
Portables, Transistor, Are Here (Scott)	Apr	43
Stereo System, Tests to Single Out Best	Sep	58
Tuning Indicator (RCA TPM-13)†	Jul	95
Auto Radio(s)		
Interference, Eliminate (Steckler)	Jan	124
Marketed (Motorola) (NB)	Feb	18
Transistor-Powered	Aug	52
Converter for TV, Simple (Vanderwall)*	Nov	80
Crystal Oscillator for (Pat)	Aug	100
Detector, Self-Tuned (Pat)	May	129
Distortion Eliminator†	Mar	47
DX in 1959 (Cooper)	Jan 49; Feb	83
Finally Makes It (Lachenbruch)	Nov	39
Front End, Miniature, for Receivers (Lucas)	Mar	38
Highway, Economical (Borzner)*	Nov	56
Increasing (NB)	Jan 6; Oct	12
Medical Net (NB)	Apr	6
Multiplex in England	Jul	74
Sensitivity Switches	Mar	39
Station Given Away (NB)	Feb	6
Tuner, Wide-Band (Pat)	Jun	106
Flash, Better Photos with Transistor Slave (Merkler)*	Oct	39
Foldover, Halos and Cure (Algarra)	Aug	78
Four-Track Stereo, Matchbox-Size (Johnson)*	Jul	76
Corr	Sep	116

G

Gibbons Substituter (Davis)	Jul	61	
Grid-Current Limiting Resistors (Darling)	Aug	59	
Guided-Grid, TV Tuner with (Lucas)	Jan	43	
H			
Hand-Sized Grid-Dip Meter (Queen)*	May	42	
Headlight Tattletale (Young)	Apr	41	
Headphones for TV (Rasmussen)	Jan 56; (NC)	Feb 148	
Heart, Electronics Can Save (Post)	May	54	
High Power for Twin-Coupled Amplifier (Crowhurst)	Oct	34	
Highlights of 1959 (NB)	Jan	6	
Hints from Transithusiast's Workshop, More (Klein)	Jan	98	
How to Fix Radios Faster (and Make More Money) (Darr)	Nov	43	
How Much Rf? (Chapel)	Jul	97	
How Valid Are Speaker Response Curves? (Augsburger)	Mar	50	
I			
Identify Calibration Signals (Ives)*	Sep	56	
Corres	Dec	18	
Ignition Operated Tachometers (Schotz)*	Dec	54	
Ignitrons, Be Careful with (Lytel)	Dec	70	
Impedance, What's with Characteristic? (Middleton)	Mar	74	
Corres	Jun 18; Jul 22; Sep 21;	Dec 21	
Improving PA Systems (Sands)	Nov	71	
Improving TV Receiver (Feingold)	May	86	
Indicator, Miniature	Sep	49	
INDUSTRIAL ELECTRONICS			
Audio Generator for Industrial Service Jobs (Kernin)*	Mar	60	
Automatic Control (NB)	Mar	16	
Diagrams, Understanding (Jaski)	Jun	64	
Electronic Balancing for Better Motors (Essex)	Feb	58	
Fishing, Electronics Goes (Milanowski)	Jan 36; (NB)	Mar 10	
Grid-Current Limiting Resistors (Darling)	Aug	59	
Ignitrons, Be Careful with (Lytel)	Dec	70	
Industry Controls, Warns, Indicates, Counts Photoelectrically (Lytel)	Jun	70	
Infrared in Industry (Kemp)	Aug	57	
Injec-Check, Industrial Test Unit (Kernin)*	Oct	88	
Leak Detectors, How They Work	Mar	59	
Machines That Read (Gronich and Briefel)	Sep	64	
Magnetron, Industrial Power Generator (Jaski)	Oct	68	
Molten Glass, Electronics Controls Level (Barlowe)	Mar	58	
Motors, Electronic Balancing for (Essex)	Feb	58	
Oscillographs in Action (Thomas)	Jul	49	
Photoelectric Control Made Easy (Winklepleck)*	Mar	62	
Photoelectric Register Controls (Lytel)	Part I	Jan 38; Part II	Feb 54
Strain Gauge, Look at (Kramer)	Dec	56	
Power Supply, Regulated Low-Voltage (Murphy)*	Aug	53	
Relays, Preventive Maintenance Keeps Them Working (Conant)	Apr	71	
Safety Interlock (Ives)	May	39	
Semiconductors for Controls (Jaski)	Jul	46	
Servicing (See also Servicing) (Corres)	Feb 22, 26; Mar	18	
Servomechanisms, How They Work (Safford)	Jul	53	
Signal-Trace Industrial Circuits (Kernin)*	Sep	72	
Solder Removal Made Easy (McGuinness)	Jun	68	
Corres	Nov	29	
Static Controls (Jaski)	Apr	63	
Corres	Sep	21	
Mere (Jaski)	May	36	
Strain Gauge—Look at (Kramer)	Dec	56	
Subcarrier Techniques in Telemetry (Bukstein)	Nov	49	
Television			
ITV Camera, Setting Up (Noll)	Jan	32	
ITV Lens and Lighting System (Noll)	Feb	51	
Tech to Military Technician (Kaufman)	Jan	42	
Tech Repairs Weld Timer (Darling)	May	32	
Transient Capacitor—What Is It? (Darling)	Nov	79	
Transitone Locates Hidden Wiring (Parker)*	Dec	35	
Ultrasonics, Introduction (Jaski)	Aug	54	
Ungrounded Equipment Can Be Fatal Using 24-28-Volt Relays (Oberto)	Sep	75	
Weld Timer, TV Tech Repairs (Darling)	May	35	
Whaling by Electrolocation	Jan	42	
Industry Controls, Warns, Indicates, Counts Photoelectrically (Lytel)	Jun	70	
Infrared in Industry (Kemp)	Aug	57	
Infrared Guides Missiles (Spencer)	Jan	96	
Corres	Nov	22	
Injec-Check, Industrial Test Unit (Kernin)*	Oct	88	
Integrating Timer (Shields)*	Dec	28	
Intercom, Automatic Doorbell (Kampf)*	Sep	34	
Intercom Booster Aids TV Director (Hahhr)*	Jun	76	
Intercoms and Boat Hailers Improved by Transistors (Scott)	Aug	34	
Interference—Causes, Remedies and Location (Frantz)	Jul	98	
Corres	Oct	21	
Intermittents, Licking (Greenlee)	Mar	95	
International Electronic Meet at Paris (Garcin)	Jun	46	
Ionized Band Encircles Earth (Warshaw)	Jun	38	
IRE, New at 1960 Convention (NB) May 6; May	58		
ITV Lens and Lighting Systems (Noll)	Feb	51	
K			
Kits, Turntables and Pickup Arms (Graham)	Mar	44	

SCHOOL DIRECTORY

ENGINEERING EDUCATION for the Space Age

NORTHROP INSTITUTE of Technology is a privately endowed, nonprofit college of engineering offering **TWO-YEAR** accredited technical institute curricula and complete Bachelor of Science degree programs. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation.

NORTHROP INSTITUTE OF TECHNOLOGY
1181 West Arbor Vitae Street, Inglewood 1, California

engineering degree in 27 months

Grasp your chance for a better life. Rapid advancement. Better income. **BACHELOR OF SCIENCE DEGREE IN 27 MONTHS** in Elect. (Electronics or Power major), Mech., Civil, Aero., Chem., Engineering. **IN 36 MONTHS** in Business Administration (General Business, Acctg., Motor Transport Mgt. majors). Small classes. More professional class hours. Well-equipped labs. Campus. Dorms. Modest costs. Year-round operation. Founded 1884. Enter Jan., Mar., July, Sept. Write J. G. McCarthy, Director of Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE 24120 College Ave.
Angola, Indiana

SCIENCE ENGINEERING

BACHELOR'S DEGREE IN 27 OR 36 MONTHS
Accelerated year-round program: Aero., Chem., Civil, Elec., Mech., Metal.; Math., Chem., Physics. Modest rate. Earn board. New classes start Jan., Mar., June, July, Sept. Catalog. 15120 E. Washington Blvd., Fort Wayne 2, Ind.

INDIANA TECHNICAL COLLEGE

LEARN RADAR MICROWAVES
COMPUTERS—TRANSMITTERS
CODE • TV • RADIO
Phila. Wireless Technical Inst.
1533 Pine St., Philadelphia 2, Pa.
A Non-Profit Corp.
Founded in 1908
Write for free Catalog to Dept. RE-12
Classes now forming

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 29 mos. B.S. in electronic engineering obtainable. ECED accredited. G.I. approved. Graduates in all branches of electronics with major companies. Start February, September. Dorms, campus. High School graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Indiana



Learn Transistor Electronics At Home!

■ Prepare now for a profitable career in this growing field. Learn theory, construction and applications of all types of transistors with this proven home-study course from the Philco Technological Center.

FOR FREE INFORMATION PLEASE WRITE TO:

PHILCO
TECHNOLOGICAL CENTER

"C" and Ontario Sts., Philadelphia 34, Pa.

AT LAST! A home study course covering all phases of electric and electronic organ servicing. An extensive course covering every make of organ—repair, regulating, and troubleshooting.

A NEW COURSE

Electronic ORGAN SERVICING

Your Opportunity To Get Into A New, Rapidly Expanding Field At The Start. Don't Miss It!!

WRITE NOW FOR FREE BOOKLET

NILES BRYANT SCHOOL
Dept. E., 3731 Stockton Blvd.
Sacramento 29, California

NHSC Approved • The Pioneer School
Established 1898

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

FREE! ELECTRONICS CAREER KIT

If you're interested in breaking into a good-paying job in Radio-TV-Electronics, I.C.S. will send you absolutely free a famous Career Kit with 3 famous booklets that have helped thousands of others—just like yourself—on the road to real success. Includes:

- 1 "HOW TO SUCCEED" Career Guide — 36-page gold mine of career tips and information.
- 2 "JOB CATALOG" of opportunities in your field of interest.
- 3 "SAMPLE LESSON" (math) to demonstrate the famous I.C.S. method.

Send today for your free I.C.S. Career Kit with these 3 famous booklets. There's no obligation. This may be the big break you've been waiting for. Mark and mail the coupon today.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 37683L Scranton 15, Penna.

Please send free Career Kit with 3 famous booklets

General Electronics Radio-TV Serv'g Practical Electrician
 Industrial Electronics Sound Equip. Serv'g Profess'l Eng. (Elec.)
 Radio-TV Eng'r'g Electrical Eng'r'g Electrical Drafting
 Electronic Servicing Electrical Sh. Other _____

Name _____ Age _____

Address _____

City _____ State _____

FREE CAREER BOOKLET



to guide you to a successful future in

ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

MISSILES • RADAR • RESEARCH
ELECTRICAL POWER • ROCKETRY
AUTOMATION • AVIONICS
SALES • DEVELOPMENT

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

MILWAUKEE SCHOOL OF ENGINEERING

MAIL COUPON TODAY!

MILWAUKEE SCHOOL OF ENGINEERING
Dept. RE-1260, 1025 N. Milwaukee St.
Milwaukee, Wisconsin MS-113

Please send FREE "Your Career" booklet
I'm interested in Electronics Radio-TV
 Computers Electrical Engineering
 Mechanical Engineering
(PLEASE PRINT)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I'm eligible for veterans education benefits.

Discharge date _____

L		NOTEWORTHY CIRCUITS (Cont'd)		R	
Languages, Electronics Labs Help Teach (Johnson)	Jun 33	Sleep Alarm	May 124	RADAR	
Leak Detectors, How They Work	Mar 59	Supply, Voltage-Limited	Oct 113	Equipment Can Be Easy to Service	Sep 46
Legal Pitfalls (Parker)	Nov 24	Television		Largest (NB)	Jan 14
Lightning, TV Antennas Invite	Oct 92	Headphones	Feb 148	MADRE (NB)	Mar 12
Limiting Resistors, Grid-Current (Darling)	Aug 59	Hum-Cancelling Circuit	Feb 148	Mapping (NB)	Jul 12
LITERATURE, NEW	Jan 146; Feb 152; Mar 144; Apr 132; May 129; Jun 126; Jul 118; Aug 117; Sep 128; Oct 117; Nov 127; Dec 125	Width Stabilization	Jan 139	Missile Tracking (WN)	Mar 43
"Little Handful" Citizens-Band Transceiver (Queen)*	Aug 50	Test Instruments		New for	Nov 55
Look at Electronic Strain Gauge (Kramer)	Dec 56	Alpha Tester, Transistor	Jun 109	Principles of Modern (McQuay)	
Low-Cost, Starved-Current Amplifier (Lederer)*	Aug 36	Beta Tester, Transistor	Aug 98	Part I—AM and FM	Jun 42
Lows Are Directional Too	Mar 49	Probe, Battery-Current	Apr 128	Part II—Pulse Doppler	Jul 34
		Stereoscope, Battery-Operated	Jul 110	Range Increased (NB)	Jun 10
		Substitution Box, Improved	Aug 99	River Navigation (NB)	Mar 12
		Timer, Darkroom	Apr 127	Radiation Detector, New Semiconductor (Shunaman)	Apr 42
		Touch-Plate Relay	Jun 106		
		Transistor Class-B Circuits, Four	Jun 107	RADIO	
		Transistors, Power, Mounting	Jun 107	Alarms, Electronic, in Clock Radios (Maxwell)	Feb 115
		Novel "Talkie" Outfit for Slide Projectors (Costigan)*	May 122	Amateur(s)	
		NPN-PNP Transistor Oscillator (Merkler)*	Jun 36	Break-in, Faster (NC)	Mar 137
			Nov 91	Corres	Nov 26
				Cleveland Ham Wins Edison Award (NB)	Apr 6
				Honored (NB)	Nov 6
				License Rise (NB)	Jun 12
				Moon Bounce (NB)	Oct 6
				Satellite Bounce (NB)	May 6
				Antenna, Spiral Conical	Apr 49
				Auto	
				FM (Motorola) (NB)	Feb 18
				Eliminate Interference (Steckler)	Jan 124
				Transistor-Powered	Aug 52
				Hybrid (Motorola 406)†	Jul 95
				Transistor, Build This (Martin)*	Mar 40
				Corr	May 130
				Varicaps Tuned	May 58
				Arc for Hallicrafters S-94 (NC)	Nov 120
				Battery-less (Pat)	Feb 136
				Cabinet Repair, Rapid (Bohr)	Feb 118
				Cabinets, Repair, Retouch, Refinish (Markell)	
				Part I	Mar 109
				Part II	Apr 60
				Calibration Signals, Identify (Ives)*	Sep 56
				Corres	Dec 18
				Circuitry, New Developments in (Maxwell)	Jul 94
				Citizens Band	
				Apelco AR-9†	Sep 52
				Arc for Hallicrafters S-94 (NC)	Nov 120
				Break-in, Faster (NC)	Mar 137
				Corres	Nov 26
				Building Your Own (Sands)	Jan 110
				Canadian? (Corres)	Jun 22
				Citizens Hamming up Status of FCC Warns Against Rag-Chewing	Jun 51
				Field-Strength Meter, Transistor (Greenlee)*	Jan 126
				Radio Control with Oomph (Thomas)*	Oct 76
				Remote-Control Transmitter (NC)	Oct 52
				Radson†	Nov 120
				Transceiver Circuitry (Scott)	Sep 30
				Transceiver, "Little Handful" (Queen)*	Sep 52
				Two-Way Radios for (Scott) (Corr)	Aug 50
				Vocaline EP-27†	Jan 91
				Weather Radio?	Sep 55
				Clocks, Electronic Alarms in (Maxwell)	Jul 47
				Code, Learns at 5	Feb 115
				Code Oscillator, Economy (Martin)	Jan 121
				Conelrad Alert Monitor (Reed)*	Feb 128
				Control with Oomph (Thomas)*	Jan 108
				Control Transmitter, Portable (Queen)*	Oct 82
				Direction Finder, Poor Man's (Craig)	Sep 50
				Distance Record (NB)	May 94
				Fix (Pat)	Jun 6
				FM—See also FM	Jun 105
				Front End, Miniature (Lucas)	Mar 38
				Sensitivity Switches	Mar 39
				Frequency Standard (NB)	Jun 6
				Interference	
				BCI Trap, Novel (NC)	Dec 117
				Causes, Remedies and Location (Frantz)	Jul 98
				Corres	Oct 21
				Short-wavers Cooperate (NB)	Nov 6
				Inventors of [Edison] (Leslie)	Apr 48
				Luna Part of Signal System	Apr 45
				Marine—Radio-Telephones for Small Boats (Robberson)	Mar 34
				MARS Schedule (NB)	Jan 6; Feb 6; Mar 12; Apr 18; May 18
				Mobile, Installing, Hints (Hendrick)	Mar 22
				(Corres)	Mar 22
				No More Ovens!	Aug 49
				Paperthin (Fiction) (Fips)	Apr 46
				Oscillator, Tunnel-Diode (Grossman and Friedman)*	Sep 40
				Paging System, Bell (NB)	Nov 10
				Portable(s)	
				FM-AM Here (Scott)	Apr 43
				FM-AM All-Transistor	Jun 52
				Matchbox (Martin)*	Jun 58
				Pocket, 7-Transistor (Wittlinger)*	Mar 18
				(Corres)	
				Shirt-Pocket Reflex for Local Listening (Mason)*	Jul 92
				Super-Eight (Klein)*	Aug 44
				Corr	Sep 116
				Transitube Pocket (Davidson)* (Corr)	May 130
				World Series Special (Stanley)*	Sep 57
				Preselector, No-Band-Switching (Abbatecola)*	Feb 116
				Receiver, Souping Up That Old (Jaski)*	May 106
				Remo-Nemo (Reed)*	Dec 77
				Remote-Control Transmitter (NC)	Nov 120
				Rf	
				How Much? (Chapel)	Jul 97
				Stage Boosts Sensitivity (Foldi)	Jun 60
				Transmitter, Automatic Tuning (Pat)	Jan 142
				(Continued on page 138)	

FREE!

LAFAYETTE'S 1961 CATALOG

324 GIANT SIZED PAGES


The Complete Catalog Featuring
"The Best Buys In The Business"

- Stereophonic Hi-Fi Equipment
- Public Address Systems
- Tape Recorders
- Radio and TV Tubes and Parts
- Citizen Band Equipment
- Amateur Equipment
- Industrial Supplies

Send for Lafayette's FREE Catalog—the most complete, up-to-the-minute electronic supply catalog crammed full of everything in electronics at our customary down-to-earth money-saving prices.

CONTAINS HUNDREDS OF EXCLUSIVE LAFAYETTE ITEMS NOT AVAILABLE IN ANY OTHER CATALOG OR FROM ANY OTHER SOURCE—SEND FOR YOUR COPY NOW!

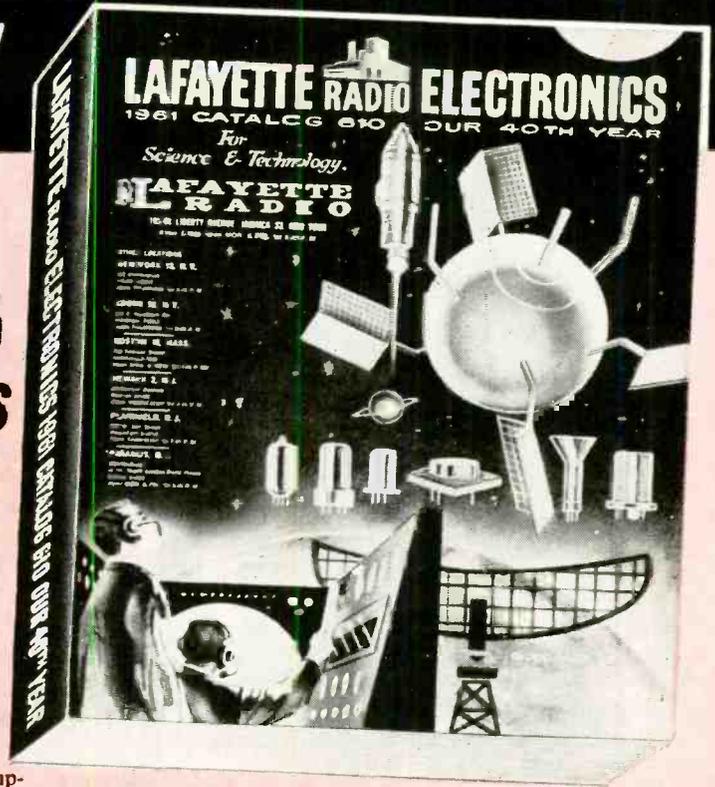A "must" for the economy-minded hi-fi enthusiast, experimenter, hobbyist, engineer, technician, student, serviceman and dealer.



Our 40th Year

EASY PAY PLAN—the simplest, and quickest way to get what you want when you want it. As little as \$2 down . . . up to 24 months to pay.



Communications Receiver
KT-200, Kit HE-10, Wired,
64.50 79.95



RK-400 2-Speed
Portable Tape Recorder
49.50



RW-60 20,000 Ohms Per
Volt Multitester
13.50

TE-15 Tube Checker
19.95



TM-14
Radio Field Indicator
7.95



HE-800WX
Citizen Band Mobile Antenna
6.95

LAFAYETTE RADIO

Mail the coupon today for your
FREE copy of Lafayette Radio's
1961 catalog.



Lafayette Radio Electronics Corp.

Dept. J-6, P.O. Box 190
Jamaica 31, N. Y.

Send me the FREE Lafayette 324 page
1961 catalog 610

Name.....

Address.....

City..... Zone..... State.....

RADIO (Cont'd from p. 134)

Single-Sideband Transmitter Adjustments (Noll)	Aug	47
Small, Uses Original Transistor Amplifier (Giardi)*	Dec	86
Snitcher, More on (NC)	Oct	113
Souping Up That Old Receiver (Thomas)*	May	106
Speaker, 8-Inch, Single Transistor Operates (Grace)*	Oct	52
Squelch Without Tubes (Shaum)*	Jun	50
Stars, Locating (NB)	Jun	6
Stereo AM SSB Broadcasting, Foreign (NB)	Mar	16
Stereo System, Tests to Single Out Best Telescope, Largest (WN)	Sep	58
Time Standard, New	Mar	43
Transistorized—Transistor(ized), Radios Troubleshooting with FCC	Jul	55
Ultra-Sensitive, 3-Transistor (Amorose and Hoffmeister)*	Sep	51
Underground (NB)	Dec	39
Voice of Africa? (NB)	Oct	6
Voice of America's New Transmitter (NB)	Nov	6
Wave Duct (NB)	Mar	10
Waves and Life (Jaski)	Apr	6
Corres	Sep	43
Radiotelephones, Small-Boat (Robberson)	Nov	30
Rally-Pal Computer (Allison)*	Mar	34
Rapid Cabinet Repair (Bohr)	Nov	46
Record Changers, Servicing Faster (Sheneman)	Feb	118
Regulated Low-Voltage Power Supply (Murphy)*	Jan	57
Remo-Nemo (Reed)	Aug	53
Reserve Power for Survival (Prensky)	Dec	77
Resistance Calculator, Parallel/Series (Salva)*	Jul	96
Retouch, Repair, Refinish Cabinets (Markell)	Aug	72
Part I	Mar	109
Part II	Apr	60
Reverberation, And Now	Aug	43
Rf Stage Boosts Sensitivity (Foldi)	Jun	60
Roundword Puzzle (Nahrwald)	Jul	31

6DZ7 Amplifier (Voss)*	Nov	40
6E5 for Transistor Circuits (Turner)*	Nov	98
Safety Interlock, Industrial (Ives)	May	39

SEMICONDUCTORS—See also Transistor(s); Transistor(ized)

Diode(s)	Nov	99
Adder (Pat)	Jan	142
Amplifier (Pat)	Feb	137
Amplifier, Pulse (Pat)	Jul	109
Comparator (Pat)	Apr	12
High-Frequency (NB)	Mar	128
Recovery Time, Reducing (Pat)	Oct	51
Duo-junction (Queen)*	Aug	100
Gate (Pat)	Jul	46
Industrial Controls (Jaski)	Jul	46
New—See also New Tubes and Semiconductors		
Departures in Tubes and (Steckler)	Aug	68
Material (NB)	Feb	21
Radiation Detector New (Shunaman)	Apr	42
Something New in (Crawford and Milligan)	Jan	105
Corres	Apr	22
Tunnel Diode(s)	Nov	42
Noise Generator (Queen)*	Sep	40
Oscillator (Grossman and Friedman)*	Oct	58
Really Works (Queen)*	Jul	26
Story (Walters and Clays)	Aug	42
Zener Diodes Prevent Speaker Burnout (Ives)	Aug	42

SERVICING—See also specific subject; Technofes; Test Instruments; Try This One

Adapter, Phone-Tip (TTO)	Jul	115
Air-Conditioner Fan Motors (Tech)	May	115
Audio		
Distortion (Soundmirror BK 414) (Tech)	Feb	133
Hum (RCA 6RF9) (Tech)	Jun	119
Plug Adapter (TTO)	Apr	107
Record Changers, Servicing Faster (Sheneman)	Jan	57
Recorder, Noisy (Soundmirror 414) (Tech)	Jan	141
Speaker Transformers, Mounting (TTO)	Sep	123
Tape Recorder Kink	Mar	56
Tape Recorder Wow (Tech)	Sep	114
Tape Splicer, Cleaning (TTO)	Mar	133
Turntable, New Flocking (TTO)	Oct	120
Cabinet(s)		
Repair, Rapid (Bohr)	Feb	118
Retouch, Repair, Refinish (Markell)		
Part I	Mar	109
Part II	Apr	60
Clippings, Saving (Corres)	Jan 26;	May 26
Electrolytics, Discharging	Feb	129
Hole Shrinking (TTO)	Aug	114
Industrial Electronics—See also Industrial Electronics		
Corres	Feb 22, 26;	Mar 18
Ignitrons, Be Careful with (Lytel)	Dec	70
Injec-Check (Kernin)*	Oct	88
Signal-Trace Industrial Circuits (Kernin)*	Sep	72
Intermittents, Capacitor Test Box Finds (Fred)	Jul	44
Intermittents, Foil Foils (TTO)	Feb	145
Legal Pitfalls (Parker)	Nov	84
Meter Scales, Brighten (TTO)	Jul	114
Military Technician, TV Tech to (Kaufman)	Jan	42
Parts Substitution in Dogs (TTO)	Sep	114
Power Supply, Transistor, for Service Bench (Pugh)*	Aug	29

SERVICING, Radio (Cont'd)

Printed-Circuit Grounds (Tech)	Nov	110
Projectors, Parts for Natco (Corres)	Oct	21
Radio		
Audio Output (Tech)	Jan	140
Auto		
Coil Slugs, Freeing If (Tech)	May	115
Generator Noise (Tech)	Aug	109
Power Supply (Tech)	Dec	115
Sound		
Distorted (Ford 74BF) (Tech)	Oct	111
Out (Philco P5703) (Tech)	Nov	111
Sep 115; (Tech)	Nov	111
Squeals (Motorola 78MF) (Tech)	Nov	111
Weak (Ford 74BF) (Tech)	Aug	110
Stations Off Frequency (Ford 74BF) (Tech)	Jun	120
Transistor, Heat Damage (Ford 74BF, 75BF) (Tech)	May	116
Battery, Check Shorted (Tech)	Apr	116
Earpiece Repair (TTO)	May	114
Fix Radios Faster (and Make More Money) (Darr)	Nov	43
FM-AM, Lightning-Struck (Zenith 7T04) (Tech)	Aug	110
Fringe Reception, Boost (TTO)	Mar	133
Goodwill Kink (TTO)	Oct	124
Grid-Cap Leads, Mark (Tech)	May	117
If Transformer, Leaky (Tech)	Feb	133
Interference		
Causes, Remedies, Location (Frantz)	Jul	98
Corres	Oct	21
Man-Made, Variable Filter Eliminates (NC)	Sep	120
Loopslick Tracking (Tech)	Jul	113
Rf, How Much? (Chapel)	Jul	97
Safety Lecture, Old-Timer Gives (Darr)	Dec	41
Selenium Rectifiers, Replacing (TTO)	Mar	133
Tough Dog; (Fred)	Feb	125
Trace Speeds Servicing of Transistor (Steckler)	Dec	36
Tracking (G-E 646 Portable) (Tech)	Jan	141
Tricky Radios, Those (Craig)	May	100
Warmup Time, Eliminate (TTO)	Jun	122
Relay, Cure Sticky (TTO)	Aug	114
Relay Sensitivity, Improve (TTO)	Feb	145
Solder		
Removal Made Easy (McGuinness)	Jun	68
Corres	Nov	29
Spaghetti Insulates (TTO)	Apr	108
Soldering		
Aid (TTO)	Sep	124
Cast Iron (TTO)	Jun	122
Corres	Jun	26
Heat Sink, Handy (TTO)	Aug	114
Transistor Life Saver (TTO)	Oct	122
Soldering Iron		
Cleaner (TTO)	Oct	120
Holder (TTO)	Jul	115
Maintenance (TTO)	Jul	114
New Departure in	Jun	69
Rest (TTO)	Feb	145
Tips, Custom (TTO)	Nov	125
Streamlining I-Man Shop (Miller)	May	88
Television		
Agc Slow (Capehart 301M) (CI)	Dec	69
Agc Trouble (Admiral 21Z1) (CI)	Aug	80
Agc-Width Coil (Stromberg-Carlson TC-19) (CI)	Oct	68
Alignment (Mattison 630) (CI)	Mar	118
Antenna(s)		
Community (CI)	Jan	50
Distribution Systems (Beever)		
Part I	Nov	60
Part II	Dec	51
Improvement (CI)	Apr	58
Lead-in Cable (CI)	Feb	77
Lightning (CI)	Dec	63
Antennas Invite	Oct	92
Arrester Tent (TTO)	Jul	115
Stacking (CI)	Jul	59
Unusual Job (TTO)	Aug	113
Anti-ringing Capacitor (CI)	Feb	82
Barkhausen Oscillation (G-E 14P1209) (Tech)	Jan	141
Benchwork Can Be Tricky (Middleton)	Apr	52
Bending Pix (CBS U3T616) (Tech)	May	115
Bounce in Pix (Sylvania 225MU) (CI)	May	84
Buzz and Hum (CI) Aug 80; (RCA T100) (Tech)	Aug	80
Business Primers, Two	Dec	116
Channels Shifted (Bendix TS 17DU) (CI)	Oct	44
Check Tube (CI)	Jul	59
Christmas-Tree Effect (Philco 51T 2130) (CI)	Apr	59
Color		
Black-and-White Temperature Adjustments (RCA 700, 800 Series) (Tech)	Feb	80
Chroma Demodulators (Middleton)	Mar	143
Controls, About Those (Middleton)	Feb	62
CRT's, Field-Check (Egan)	Jun	80
Demodulators (CI)	Jun	96
Fringing (Silvertone 7140-A) (Tech)	Apr	57
Hum Bars (Motorola TS 902) (CI)	Oct	110
Set or Station Causing Trouble? (Darr)	May	82
Side Convergence (RCA CTC7A) (CI)	Aug	90
Signal Voltages in Chroma Matrix (Middleton)	Aug	83
Sync Out on Purpose (Tech)	May	74
Compressed Pix (CBS 1021-2) (Tech)	May	116
Control Assembly, Dual (TTO)	Apr	115
Controls Charred (RCA 21T74 17U) (CI)	Jul	114
Convergence (CI)	Jun	90
	Oct	60

SERVICING, TV Conversion (Cont'd)

Conversion(s)		
16GP4 for 16ZP4 (Philco 51-T-1604) (CI)	Apr	59
to 16- or 17-Inch (Dumont RA-103) (CI)	Apr	58
16- to 21-Inch (Sentinel 1U416,416) (CI)	Feb	82
to 17- or 21-Inch (Arvin 3160) (CI)	Feb	82
Gassy Replacements (CI)	Jul	60
Inadvisable (RCA KCS-82D) (CI)	Nov	64
Metal to Glass (CI)	Nov	66;
(Silvertone 25WG-3075) (CI)	Dec	68;
(Stewart-Warner 21T9210) (CI)	Sep	79
Corona on Agc Line	Aug	109;
Corona Cures (Tech)	Sep	81
CRT Coating (TTO)	Sep	112
DcRestorer (Capehart 1C213) (CI)	Jan	51
Detail Lacking in Pix (RCA 21T207) (CI)	Aug	80
Detectors, First and Second (CI)	Feb	80
Dim Pix (Capehart 324) (CI)	Apr	57
Distortion, Scope Detects (CI)	Nov	64
Dogs, We Learned from (Centerville)	Jun	71
Electrostatic-Focus CRT's (Tech)	May	117
Fine Tuning (Admiral 12YP3D) (CI)	Sep	78
Flyback Hot (Silvertone 132.045-5) (CI)	Aug	82
Focus Adjustments, Easing	Feb	88
Focus Off (Dumont RA-164) (CI)	Sep	80
Foldover, Halos and Cure (Algarra)	Aug	78
Height Insufficient (Crosley G17TOMH) (CI)	Jan	52
Herringbone Pattern (Tech)	Sep	115
High Voltage		
Boost (Transvision A41) (CI)	Oct	66
Doubler Trouble (Sylvania 512-1) (CI)	Jun	90
None (Admiral 21B1) (CI) Jun 88;		
(Emerson 163-D) (Tech) Jan 141;		
(Hallicrafters 730) (CI)	Jan	52
Holes, Compound Fills (TTO)	Aug	114
Horizontal		
Foldover (Tech) Jan 141; (Capehart 3C312M) (CI)	Apr	58
Hold Critical (Admiral 18XP4BZ) (CI) May 83; (G-E 14T017) (CI) Jul 60; (Philco 9H25U) (Tech)	Jul	112
Instability (CI) Jun 88; (Westinghouse H736T17) (Tech)	Dec	115
Jitter, Stop (Shaw)	Aug	84
Oscillator		
Bad (Capehart 14F215) (CI)	Aug	83
Critical (CBS 1621) (CI)	Mar	118
Troubleshoot (Jacques)	Apr	55
Output Stages (Jacques)	Jul	56
Roll (Motorola TS-425) (CI)	Dec	68
Sync (G-E 21T14) (CI)	Dec	68
Hum (Crosley 11-459MU) (CI)	Nov	65
Buzz and (CI)	Aug	80
Pickup (Bendix T-19) (Tech)	May	115
Identifying (DeForest 20A-05A) (CI)	Sep	78
If Oscillation, Spotting (Smith)	Feb	74
Interference		
Causes, Remedied, Location (Frantz)	Jul	98
FM (Tech)	Sep	114
Snivet (Tech)	Nov	110
Intermittents, Don't Use Heat Lamp (TTO)	Jan	144
Intermittents, Licking (Greenlee)	Mar	95
Knobs, Plastic (TTO)	Oct	112
Marginal Defects (CI)	Jun	88
Mask-Removal Tool (TTO)	Apr	108
Minus Rf (Dille)	Feb	88
Motorola's New Transistor	Sep	82
New Complaint (Spracklen)	Nov	93
One-Man Shop, Streamlining (Miller)	May	88
Oscillation, Transient (RCA KCS-68C) (CI)	Feb	79
Oscillator Troubles (CI)	Oct	61
Output and Vertical Oscillator Stages, Troubleshooting (Jacques)	Oct	40
Overload (Westinghouse H21T104) (Tech)	Feb	133
Peaking Coils, Watch (Shaw)	Aug	95
Piecrust Pix (Magnavox) (Tech)	Nov	111
Pulling (Raytheon C-21A) (CI)	Nov	70
and Tearing (Philco 51 T 2130) (CI) at Top (Capehart CX33) (CI)	Feb	80
Jan 51		
Raster		
Dim (CBS) (CI) May 85; (Sentinel 1U-1101-T) (CI)	Jan	52
Hole in (Crosley G21TOWH) (CI)	Mar	117
Lost (Coronado 15TV4) (Tech) Oct 111; (G-E 21T7) (CI) Sep 81; (Zenith 12Z11) (Tech)	Apr	116
Small, No Pix or Sound (G-E Portable MM) (Tech)	Jan	143
Reception, Poor (CI)	Apr	57
Rectifier Bad? (Emerson 1184) (CI)	Oct	61
Remote Uncontrol (Zenith 16Z21Q) (CI)	Nov	65
Resistors		
Burning (Packard-Bell 2301) (CI) Feb 79;		
(Philco 7640) (CI)	Sep	79
Charred (RCA 21T7417U) (CI)	Jun	90
Retrace Eliminator (CI)	Jan	52
Ringin (Sylvania I-523) (CI)	Nov	70
Roll (Philco F4628) (CI)	Jan	51
Scope		
Troubleshooting with (CI)	Sep	78
Waveforms, Voltage and Current (CI)	Feb	78
Corr	May	130
Wide-Band (CI)	Feb	77
Zero-Reference Levels (CI)	Mar	116
Shock-Absorbing Ride (TTO)	Jul	115

SERVICING TV (Cont'd)

Shrinking Pix (Setchell-Carlson 551) (CI)	Sep	78
Silver Lining in Pix (Admiral 122DX121) (Tech)	Aug	109
Smear Pix (Admiral 14YP3) (CI)	Mar	116
Sound		
Noisy and Intermittent (Tech)	Jun	119
Slow and Intermittent (Philco E-2006-11 Portable) (CI)	Oct	66
Takeoff (Schloemer)	Jan	45
Unsound (Packard Bell 2111-Z) (CI)	Dec	68
Streaks and Flashes (Tech)	Oct	110
Sweep Circuits, Troubleshooting (Sykes)	Jul	37
Sync (Stewart-Warner 21T9300A) (Tech)	Feb	133
Buzz (AMC) (CI) Jan 52; (Hyde Park 172) (CI)	Mar	118
Drifting (Trav-Ler 729-17A Portable) (CI)	Nov	70
Loss (Sparton 21322) (Tech)	Jan	140
Unstable (Magnavox CT257) (Tech) (Zenith 2229) (Tech)	Jul	112;
Transistor, Motorola's New	Dec	116
Traps Out of Tune (Freed-Eisemann 1916) (CI)	Sep	82
Tube(s)		
—Changing Tough Ones (Darr)	Oct	84
Check, Remember	Jul	58
Pix		
Breakdown (Muntz 17B6) (CI)	Jan	42
Cathode Open (Tech)	Mar	143
Cleaning Aid (TTO)	Sep	123
Shields, Replace (Tech)	May	117
Short Life (Motorola 21T25CH) (CI)	Jun	89
Tuner		
Inoperable (Bendix T20) (Tech)	Jul	112
Noisy (Philco UG3052-BL) (Tech)	Oct	110
Trouble (RCA 7T1033) (CI)	Apr	58
Vertical		
Circuits, Compensating Capacitors for (Tech)	Jun	119
Compression (Sylvania 1-544-1) (Tech)	Nov	110
Foldover (G-E 17P1330) (Tech)	Jun	119
Hold Critical (CBS 22C07M) (CI)	May	84
Instability (CI) Jun 88; (RCA KCS-124) (CI)	May	85
Jitter (Motorola 17P3-1) (Tech)	Apr	118
Line (RCA 800 Portable) (Tech)	May	117;
(RCA KCS-68) (CI)	Aug	83
Linearity Poor (Zenith Super K) (CI)	Jun	88
Oscillator and Output Stages, Troubleshooting (Jacques)	Oct	40
Raster Collapsed (CBS-Columbia U3T602) (Tech)	Aug	111
Roll (RCA KCS-92) (CI)	Oct	61
Roll and Poor Sync (G-E 17T14) (CI)	Apr	59
Sync Trouble (Philco TV-300) (CI)	Apr	58
Voltages Missing (Stromberg-Carlson TC-19) (CI)	Jun	90
Video If Systems, Taming (Lemons)	Dec	30
Width		
Coil Burnout (Sentinel 416) (CI)	Jul	59
Excessive (G-E 17P1329) (Tech)	Oct	111
Insufficient (G-E 14P1210) (Tech)	Mar	142
Yoke(s) (CI)	Mar	114
Coils, Save (Tech)	Dec	116
Flashover (RCA 2T60) (CI)	Sep	78
Magnets Not Used (CI)	Dec	68
Test Instruments		
Marker Generator Trouble (CI)	Aug	82
Meter Case Nonmagnetic (TTO)	Aug	113
Sine Waves, Using (Tech)	Nov	110
Vtm Readings Low (EICO 221, 221K) (Tech)	Jun	120
Test Lead Extensions (TTO)	Jun	122
Weld Timer, TV Tech Repairs (Darling)	May	32
Wiring, Transistone Locates Hidden (Parker)*	Dec	55
Servomechanisms, How They Work (Safford)	Jul	53
Set or Station Causing Color TV Troubles? (Darr)	Aug	90
Setting Up ITV Camera (Noll)	Jan	32
Shirt-Pocket Reflex for Local Listening (Mason)*	Jul	92
Shoot with All-Transistor Photoflash (Ahrns)*	Apr	36
Signal-Trace Industrial Circuits (Kernin)*	Sep	72
Signal Voltages in Chroma Matrix (Middleton)	May	74
Single-Control Multimeter (Stratmoen)*	Feb	34
Single-Pulse Generator (Thomas)*	Apr	79
Single-Sideband Transmitter Adjustments (Noll)	Aug	47
Single Transistor Operates 8-Inch Speaker (Grace)	Oct	52
Small-Boat Radiotelephones (Robberson)	Mar	34
Solar Cells, How to Make (Chapin)	Mar	89
Solder Removal Made Easy (McGuinness)	Jun	68
Corres	Nov	29
Souping Up That Old Receiver (Thomas)*	May	106
Speaker Response Curves, How Valid (Augsburger)	Mar	50
Special Effects with Tape Recorder (Larson)	Aug	40
Spotting Video If Oscillation (Smith)	Feb	74
Squelch Without Tubes (Shaum)*	Jun	50
Static Controls in Industry (Jaski)	Apr	63
Corres	Sep	22
More (Jaski)	May	36
Stereo—See Audio—High Fidelity, Stereo; Radio		
Stop Feedback in PA Systems (Schroeder)	Feb	40
Stop Horizontal Jitter (Shaw)	Aug	84
Strain Gauge, Look at (Kramer)	Dec	56
Streamlining One-Man Shop (Miller)	May	88

Strobe for Tape (McCormick)*	May	40
Stroboscope Flasher (Taylor)	Jun	35
Subcarrier Techniques in Telemetry (Bukstein)	Nov	49
Super-Eight, Build (Klein)*	Aug	44
Corr	Sep	116
Sweep Generator, Simple, Uses Varicap (Barron)*	Nov	58
T		
Tachometers, Ignition-Operated (Schotz)*	Dec	54
"Talkie" Outfit for Slide Projectors, Novel (Costigan)*	Jun	36
Taming Video If Systems (Lemons)	Dec	30
Tape—See Audio—High Fidelity, Tape		
Tape Recorder Word Puzzle (Comstock)	Feb	43
TECHNICIANS' NEWS Jan 130; Feb 130; Apr 124; May 118; Jun 102; Jul 106; Aug 106; Sep 110; Oct 114; Nov 112; Dec 110		
TECHNOTES—See also Servicing; Try This One		
Air-Conditioner Fan Motor	May	115
Audio		
Distortion (Soundmirror BK414)	Feb	133
Hum (RCA 6RF9)	Jun	119
Phono Inoperative (Sylvania 4312)	Sep	114
Recording Noisy (Soundmirror 414)	Jan	141
Tape Recorder Wow	Sep	114
Printed-Circuit Grounds	Nov	110
Radio		
Audio Output (RCA 7-BT-9J)	Jan	140
Auto		
Generator		
Noise	Aug	109
Hint	Mar	142
Power Supply	Dec	115
Sound		
Distorted (Ford 74BF)	Oct	111
Out (Philco P5703)	Sep 115; Nov	111
Squeals (Motorola 78Mf)	Nov	111
Weak (Ford 74BF)	Aug	110
Stations Off Frequency (Ford 74BF)	Jun	120
Transistor, Heat Damage (Ford 74BF, 75BF)	May	116
Battery, Check Shorted	Apr	116
FM-AM, Lightning-Struck (Zenith 7T04)	Aug	110
Grid-Cap Leads, Mark	May	117
If Transformer, Leaky	Feb	133
Loopstick Tracking	Jul	113
Tracking (G-E 646 Portable)	Jan	141
Sine Waves, Using	Nov	110
Television		
Barkhausen Oscillation (G-E 14P1209)	Jan	141
Capacitors, Compensating	Jun	119
Color		
Black-and-White Temperature Adjustments (RCA 700, 800 Series)	Mar	143
Fringing (Silvertone 7140 A)	Oct	110
Sync Out on Purpose	May	116
Compressed Pix (CBS 1021-2)	Apr	116
Corona Cures	Aug 109; Sep	115
Electrostatic-Focus CRT's	May	117
FM Interference	Sep	115
High-Voltage Lacking (Emerson 163-D)	Jan	141
Horizontal Foldover	Jan	141
Horizontal Hold Critical (Philco 9H25U)	Jul	112
Hum Pickup (Bendix T-19)	May	115
Overload (Westinghouse H21T104)	Feb	133
Picture Bends (CBS U3T616)	May	115
Piecrust Pix (Magnavox 105)	Nov	111
Pix-Tube Cathode Open	Mar	143
Raster Lost (Coronado 15TV4) (Zenith 16Z21)	Oct 111; Apr	116
Raster Small, No Sound, No Pix (G-E Portable MM)	Jan	140
Silver Lining on Pix (Admiral 122DX121)	Aug	109
Shivet Interference	Nov	110
Sound Buzzy and Weak (RCA T100)	Dec	116
Sound Noisy and Intermittent (Zenith 23H22)	Jun	119
Streaks and Flashes in Pix	Oct	110
Critical (Stewart-Warner 21T9300A)	Feb	133
Loss (Sparton 21322)	Jan	140
Unstable (Magnavox CT257)	Jul	112;
(Westinghouse H736T17)	Dec	115;
(Zenith 2229)	Dec	116
Tube Shields, Replace	May	117
Tuner Inoperable (Bendix T20)	Jul	112
Tuner Noisy (Philco UG3052-BL)	Oct	110
Vertical		
Blanking Poor (G-E 17P1330)	Sep	114
Compression (Sylvania 1-544-1)	Nov	110
Foldover (G-E 17P1330)	Jun	119
Jitter (Motorola 17P3-1)	Apr	118
Line, Jagged (RCA 800 Portables)	May	117
Raster Collapse (CBS-Columbia U3T602)	Aug	111
Width Excessive (G-E 17P1329)	Oct	111
Width Insufficient (G-E 14P1210)	Mar	142
Yoke Coils, Save	Dec	116
Test Instruments		
Square Waves, Using	Mar	142
Vtm Readings Low (EICO 221, 221K)	Jun	120
Teleducated Techs (Melton)	Apr	50
Telemetry, Subcarrier Techniques in (Bukstein)	Nov	49
TELEVISION		
Antenna(s)		
Community (CI)	Jan	50
Distribution Systems, Servicing (Beever) Part I	Nov 60; Part II	Dec 51
Invite Lightning to Strike	Oct	92
Yagi, Build-It-Yourself (CI)	Nov	65
Audience Survey System (Pat)	Mar	128
Audio		
Feed into Hi-Fi Systems (Leonard)	Mar	56

TELEVISION, Audio (Cont'd)		
FM Converter, Simple (Vonderwall)*	Nov	80
Headphones br (Rasmussen)	Jan	56
Hum-Cancelling Circuit (NC)	Feb	148
Video Amplifier	Mar	49
Booster Operators Cooperate (NB)	Nov	12
Brightness Control, New Automatic (Maxwell)	Sep	91
Cabinet(s)		
Repair, Rapid (Bohr)	Feb	118
Retouch, Repair, Refinish (Markel) Part I	Mar 109; Part II	Apr 60
Cameras, ITV		
Lens and Lighting Systems (Noll)	Feb	51
Setting Up (Noll)	Jan	32
Channel Allocation (NB)	Apr	8
Closed-Circuit, Elevator, for Safety (NB) Color	Nov	14
Beam-Registration Circuit (Pat)	Feb	136
Controls, About Those (Middleton)	Jun	80
Japan, 2-Color (NB)	Sep	12
Set or Station Causing Trouble? (Darr)	Aug	90
Signal Voltages in Chroma Matrix (Middleton)	May	74
Upswing (NB)	Jun	14
Design Trends, 1960 (Lemons)	Jan	46
Dx in 1959 (Cooper)	Jan 49; Feb	83
Dx, Photographing (Simkin) Corr	Jan	91
Education		
Classroom, Electronic	Dec	31
Demonstrator (WN)	Nov	63
Stratovision (NB)	Mar	10
Teleducated Technicians (Melton)	Apr	50
Fluoroscope	Sep	42
Improving the Receiver (Feingold)	May	86
Intercom Booster Aids TV Director (Haahr)*	Jun	76
Interference—Cause, Remedies and Location (Frantz)	Jul	98
Corres	Oct	21
Intermittents, Licking (Greenlee)	Mar	95
Japanese, Coming (NB)	Nov	14
Key TV for Rating Shows (WN)	Sep	59
Minus RI (Dilley)	Feb	88
Number up to 94,000,000 (NB)	Nov	20
Portable, New Products for? (NB)	Apr	6
Production Up (NB)	Apr	8
Quiz (Eldridge)	Dec	88
Remote Viewer (Pat)	May	129
Sawtooth Sticklers (Balin)	Nov	90
Sky Spy, Automatic (Pat)	Aug	100
South African (NB)	Apr	6
Station List Jan 14; Mar 12; Apr 10;	May	16
Tech to Military Technician (Kaufman)	Jan	42
Tech Repairs Weld Timer (Darling)	May	32
Toll Trial (NB)	Apr	18
Tower, Tallest (WN)	Feb	61
Transistor(ized) (NB)	Feb	6
19-Inch (Motorola) (NB)	Jul	12
Japanese (NB)	Apr	8
Motorola's New, Servicing	Sep	82
Tubes—See Tubes		
Tuner with Guided Grid (Lucas)	Jan	43
Tuner, Wide-Band (Pat)	Jun	106
Uhf Tests (NB)	Sep	6
Underground (NB)	Dec	14
Video Width Stabilization (NC)	Jan	139
Video Tape with Time Delay (NB)	Mar	10
Visible Sound, British Deaf Want	Nov	81
Weather Eye (WN)	Aug	73
TEST INSTRUMENTS—See also Servicing; Try This One		
Adapters (Simpson) (Scott)	Jul	40
Audio		
Attenuator-Padder for Low-Level Testing (Reed)*	May	46
Comparator (Pugh)	Jul	39
Generator for Industrial Service Jobs (Kernin)*	Mar	60
Millivoltmeter, Square-Law (Turner)	Jan	91
Signal Tracer for Industrial Circuits (Kernin)*	Sep	72
Wattmeter Out of Vtm (Casey) Corres	Aug	31
Oct 26		
Bridge Accuracy, Boost with Null Amplifier (Frantz)*	Aug	32
Cable Checker, Handy (Smith)	Mar	71
Capacitance Meter (Sutton)*	Dec	90
Capacitor Test Box Finds Intermittents (Fred)	Jul	44
Chroma Tracer	May	45
CRT's Field-Check (Egan)	June	96
Decade Amplifier, Measure Millivolts with (Henry)*	Sep	94
Dry-Cell Tester	Apr	82
Electron-Ray Tube, Versatile (Shields)*	Mar	64
Electrolytics, Practical Tester for (Conant)*	Oct	46
Electroscope, Experimenter's Dual (Moen)*	Jun	99
Field-Strength Meter, Transistor, for Citizens Band (Greenlee)*	Oct	76
Frequency Meter, Direct-Reading (Pat)	Jun	105
Generator, Single-Pulse (Thomas)*	Apr	79
Grid-Dip Meter, Hand-Sized (Queen)*	May	42
Injec-Check, Industrial Test Unit (Kernin)*	Oct	88
Meter		
Dress Up That (Henry)*	Jun	94
Faces, Brighten	Jun	101
Scales, Expand (NC)	Jun	109
Microammeter, Clamp Type Ac	Feb	39
Mini-capacitance Test Set (Stone)*	Mar	66
Mini-tracer Speeds Radio Repairs (Stone)*	May	44
Multimeter, Fix That (Bohr)	Jan	74
Multimeter, Single-Control (Stratmoen)*	Feb	34
Noise Generator, Tunnel-Diode (Queen)*	Nov	42

"TAB" Tubes Tested, Inspected, Boxed

Six Months Guarantee! No Rejects!
New & Used Gov't & Mfgs. Surplus!

Orders \$10 or more, Receiving types only ppd, 48 states

0A2	.80	6B36	.69	12AT6	.59	18S1	1.00
0B2	.65	6BK7	.74	12AX7	.79	17Z6	1.10
0C3	.69	6BL7	1.25	12AU6	.69	4-65A	16.00
0D3	.35	6BN6	.98	12AU7	.69	2D21	2/81
0Z4	.59	6CQ6	.74	12BY7	.79	3D23	3/85
1A7	.89	6BZ7	1.25	12BA6	.65	717A	5/81
1B3	.78	6C4	.43	12BA7	.69	4-125	29.00
1R5	.78	6CS	.69	12BD6	.59	4-250	35.00
1S4	.78	6CD6	.80	12BE6	.59	4-227	7.00
1T4	.78	6CD6	1.49	12BF6	.59	4PR60	29.50

Send \$5 for Catalog!

1U4	3/81	6H6	3/81	12BM7	.69	4X150C	\$15
1U5	.73	6J5	.74	12BY7	.79	4X500	35.00
1X2A	.68	6J6	.48	12BZ7	.99	4X500	38.00
3Q4	.68	6K6	.59	12C06	1.45	5BP1	4.98
3Q5	.89	6K7	.74	12SA7	.94	5BP4	4.98
3S4	.68	6L6	1.19	12SG7	.89	35T	4.00
3V4	.83	6SA	.59	12SM7	.89	39	10/81
5R4	.98	6S8	.99	12SQ7	.75	316A	5/81
5U4	.59	6SA7	.89	12SK7	.64	389A	3/81
5V4	.80	6SB7	1.19	12SQ7	.84	4166	16.00

Wanted Surplus Electronics from schools & U

5Y3	.59	6SC7	.89	19B6	2.15	450T	42.00
6A4	.79	6SC7	.79	13R8	1.39	809	3.00
6AC7	.70	6M7	.69	25BQ6	1.39	809	3.00
6AG7	.89	6S7	.69	25L6	.69	811	4.40
6AM6	.99	6K7	.79	28W4	.75	812	2.00
6AK5	.69	6SL7	.89	25Z5	.63	813	9.00
6AL5	2/81	6SN7	2/81	25Z6	.75	814	3.45
6AG5	.69	6K7	.79	EL34	3.49	815	2.75
6A57	3.00	6SR7	.79	EL37	2.49	826	.59
6AT6	.49	6T8	.98	35L6	.69	829B	8.00

Wanted 30;TL Tubes & ALL TYPES!!!

NEW POWER CONVERTER
12VDC to 500VDC up to 200ma 100 Watts. Tap at 250VDC Type C1250E \$35. Hi efficiency, low ripple, low current - Sillicon rectifiers; Toroidal HiFi Mag-metal tape wound transformer, fused & short circuit proof, small in size! Quiet! Light weight! C1250EE built, ready to go. Conservatively Rated. Delco Transistors Heavy Copper-Heatsink. 12VDC to 250VDC up to 150MA Type C1255A \$30.



TRANSISTORS & ACCESSORIES

2N141	\$3.	2N442	\$4.50.	2N277	\$4.	2N278	\$5.
2N155	\$1.39.	2N178	\$1.80.	2N177	\$1.	2N178	\$5.
\$1.75.	2N242	\$1.80.	2N255	\$1.20.	2N270	\$9.95.	
2N274	\$1.25.	2N408	\$8.80.	2N544	\$1.20.	2N578	\$1.80.
2N579	\$2.20.	2N581	\$1.25.	2N582	\$2.10.	2N174	\$8.50.
2N443	\$5.20.						

DIAMOND BASE MICA MOUNTING KIT \$.30
DELCO ROUND BASE MICA MOUNTING KIT \$.30
DELCO POWER HEAT SINK WITH FINS. 1.00

"TAB" KITS! "TAB" THE BEST KITS! "TAB"
All Kits Contain Most Popular Values & Sizes

Kit 2 Eng. Parallel Rules	Kit 5 Sub-Min Tubes
Kit 35 Precision Resistors	Kit 75 Mica Condensers
Kit 75 Resistors 1/2, 1/2W	Kit 100 Ceramic Condens.
Kit 12 Electrolytic Cond's	Kit 10 Diodes
Kit 500 Lug & Eyelets	Kit 5 FT243 Xtal Holders
Kit 10 Bathub Oil Cond's	Kit 8 Sillicon Diodes
Kit 5 lbs. Surprise Pckg.	Kit 4 Ass'd Rectifiers
Kit 10 Xmttr Mica Cond'sr.	Kit 2 PNP Transistors
Kit Circular Silde Rule	Kit 4x50 FT Hookup Wire
Kit 4 Photo Suntab Cells	Kit High Gain XTL Mike

BUY 10 KITS—GET ONE FREE! EACH KIT 99¢

"VACDAC" SILICON TUBE REPLACEMENTS
WITH BUILT IN RF SURGE & SERIES BALANCING PROTECTION

TYPE	VRMS/PIV	AMPS	PRICE
ST866	5000/10400	0.3	\$20.00
ST816	5000/7000	0.3	\$16.00
ST514	1900/2800	0.5	\$15.00
ST514	1120/1600	0.6	\$ 8.00



ART13 AC POWER SUPPLY—"TABPAK" DELIVERS
1250VDC, 500VDC & 28VDC AT 10 AMPS. ALL FILTERED. USES SILICON H'SEALD DIODES. "TABPAK" PS/ART13.....\$125

NEW BATTERY CHARGER BC6-12V FOR 6V OR 12 VOLT BATTERIES. TRICKLE & FULL CHARGE up to 4 AMP



Charges 6 & 12 volt batteries. Built BC6-12V \$10.00

★ NEW "TEKSEL" SELENIUM RECTIFIERS
FULL WAVE BRIDGE RECTIFIERS. ONE YEAR OTD!

AMP.	18VAC	36VAC	72VAC	144VAC
CONT.	14VDC	28VDC	56VDC	118VDC

1AMP	\$ 1.30	\$ 2.00	\$ 4.90	\$ 6.50
2AMP	2.15	3.00	6.25	12.30
3AMP	2.90	4.00	8.60	16.75
6AMP	4.15	8.00	18.75	36.15
10AMP	6.10	12.15	26.10	51.70

Write for Complete Rectifier Catalog

NEW SILICON 750MA* DIODES TOP HATS
GENERAL PURPOSE SPECIAL 39¢ 400 PIV at 250 MA 25 FOR \$8

rms/ply 35/50 19c	rms/ply 70/100 29c	rms/ply 140/200 34c	rms/ply 210/300 43c
rms/ply 280/400 50c	rms/ply 350/500 89c	rms/ply 420/600 89c	rms/ply 490/700 95c
rms/ply 560/800 \$1.05	rms/ply 630/900 \$1.70	rms/ply 700/1000 \$1.70	rms/ply 770/1100 \$2

* CAPACITOR INPUT DERATE 20%!
(\$5 or more we pay postage 48 states)

"TAB" TERMS: Money Back Guarantee! 5th year. \$2 m. order F.O.B. N.Y.C. Add shpg charges or for C.O.D. 25% Dep. Prices shown subject to change.
111-GX LIBERTY ST., N. Y. 6, N. Y.
Send 25¢ PHONE: RECTOR 2-6245. for Catalog

ADVERTISING INDEX


Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Alex Radio Corp.	114	National Radio Institute	19-20, 129
Allied Radio Corp.	9, 16, 17	National Technical Schools	5
Amphenol-Borg Electronics Corp.	80	North American Phillips Co., Inc. (Norelco)	126
Arkay International Inc.	114		
Astatic Corp.	3rd Cover	Ohmatsu Electric Co. Ltd.	124
Audio Unlimited Inc.	140	Olson Radio Corp.	129
Audion	124	Opportunity Adlets	128
		Oxford Components, Inc.	89
B & K Manufacturing Co.	79		
Barry Electronics Corp.	127	PACO Electronics Co., Inc.	61
Bell Telephone Labs.	22	Penna-Power Company	79
Blender-Tonine Labs.	102	Phileo (Techrep Div.)	122
Bonafide Radio	140	Picture Tube Outlet	129
Brooks Radio & TV Corp.	119	Rouls D. Prior, Inc.	125
Burstein-Applebee Co.	103	Progressive "Edu-Kits" Inc.	116
		Pyanid Electric Co.	116
Capitol Radio Engineering Institute	92, 95, 94, 95	R. W. Electronics	125
Carston Studios	129	RCA (Tube Div.)	Back Cover
Castle TV Tuner Service Inc.	125	RCA (Test Equipment Div.)	112, 117
Central Industrial Electronics Inc.	127	RCA Institutes	75-76, 115, 116
Centralab Div. of Globe Union	21	Rad-Tel Tube Co.	131
Chicago Standard Transformer Corp.	107	Radio Shack Corp.	79
Cleveland Institute of Electronics	11	Radio TV Training School	23
Colordapter	140	Rinehart & Co.	128
Cornell-Dubilier Electric Corp.	12, 13		
Coyne Electrical School	108, 113, 121	Sams & Co., Inc. (Howard W.)	110, 111
		Scott, Inc. (H. I.)	21
DeVry Technical Institute	7	Service Instruments Corp. (Sencore)	8
Dressner	124	Sonotone Corp.	97
Dynaac Inc.	98, 122	Sprague Products Co.	109
		Stereo-Part	127
Electro Products Labs.	121	Stotts-Friedman Co.	128
Electronic Chemical Corp.	114	Superec Electronics	126
Electronic Instrument Co. (EICO)	25, 26	Switchcraft, Inc.	106
Electronic Measurement Corp.	104	Sylvania Electric Products Inc.	101
Electronic Publishing Co., Inc.	127		
Electronic Technical Publishing Co.	125	T A B	140
		Sarkes Tarzian, Inc.	127
Fair Radio Sales	106	Triplet Electrical Instrument Co.	2nd Cover
		Tung-Sol Electric Co.	18
General Electric Co. (SemiCond. Div.)	113	The Turner Microphone Company	73
Gensback Library, Inc.	123	United Radio Company	124
Globe Electronics (Div. of Textron Electronic Inc.)	120		
Grantham School of Electronics	15	Vaco Products Company	100
Grove Electronic Supply Co.	106	Vidair Electronics Mfg. Corp.	89
		Weller Electric Corp.	105
Harman-Kardon	142	Winegard Company	10
Health Engineering College	89	Xcelite, Inc.	118
Health Company	64-67		
Hekok Electrical Instrument Co.	87		
Holt, Linehart & Winston Inc.	128		
Homewood Industries	106		
Hudson Specialties Co.	140		
Illinois Condenser Co.	120		
Indiana Technical College	125		
JFD Electronics Corp.	3		
Jerrold Electronics Co.	14		
Key Electronics Co.	89		
Lafayette Radio Electronics Corp.	125-137		
Lektron Inc.	87		
Mercury Electronics	69, 100, 107		
Metropolitan Electronics	102		
Moss Electronic Inc.	84-85		

SCHOOL DIRECTORY PAGE 133

Baltimore Technical Institute	
Niles Bryant School	
Indiana Technical College	
International Correspondence School	
Milwaukee School of Engineering	
Northrop Institute of Technology	
Phila. Wireless Technical Institute	
Phileo Technological Center	
Tri-State College	
Valparaiso Technical Institute	

CONVERT TO COLOR TV

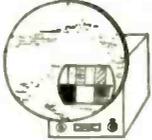

COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any size B & W TV to receive compatible color TV.
COLODAPTOR—Easily attached to any TV set, does not affect normal operation, often built from parts experimenters have on hand. BRILLIANT COLOR!

Complete booklet—gives theory of operation, all construction details, schematic, and sample color filters.
Essential Parts Kit—All Special Parts—Coils, Delay Line, Crystal, Color Filters
Up to 16" **\$19.95** 17" and Larger **\$20.95**
Other Kits, Wired Chassis, Motors Available
1728 Santa Cruz, Menlo Park, Calif.

HI-FI & STEREO COMPONENTS

Send us your list for a **SPECIAL PACKAGE DEAL QUOTE**
No sale too small. Trade-ins accepted. BONAFIDE offers biggest discounts on all standard brands. Expert advice and full guarantee are assured at
BONAFIDE ELECTRONICS
Dept. RE12, 89 1/2 Cortland St., N.Y. 7, N.Y.
WE WILL NOT BE UNDERSOLD

A NOTE TO THE HI-FI BUYER

AIR MAIL us your requirements for an **IMMEDIATE LOWEST PRICE QUOTATION** Components, Tapes and Recorders
SHIPPED PROMPTLY AT LOWEST PRICES
WRITE TODAY FOR FREE CATALOG
AUDIO UNLIMITED 714-R Lexington Ave. New York 22, N. Y.

SUPER MAGNET SUPER SAVING!

Buy this Little Giant magnet, most powerful made, a sensational bargain! The low price of \$1.95 is less than 50% of what you'd pay for this magnet. Experimenters, hobbyists will find hundreds of uses for this powerful 6 oz. Africa permanent magnet. LIFTS 5 lbs. EASILY. Limited quantity. Order several today. Measures 1 3/4 x 1 1/2 x 1/2
Item No. 86 **\$1.50**
Special Bargain (Shp. Chgs. 10c)



250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions.
ITEM NO. 123 **\$2.95** (Shp. Chgs. 10c)



AMAZING BLACK LIGHT

250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertainment, unusual lighting effects.
Shp. wt. 2 lbs. ITEM NO. 87 **\$2.95** (P. P. & Mdlg. Chgs. 35c)



HUDSON SPECIALTIES CO., 160 W. 14th St. Dept. RE-1260, New York 7, N.Y.

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)
87 33 86 123

Name _____ Please Print Clearly
Address _____
City _____ Zone _____ State _____



WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Shp. wt. 14 lbs.
ITEM NO. 33 **\$4.50** NOW ONLY (P.P. & Mdlg. Chgs. \$1.25)

TEST INSTRUMENTS (Cont'd)

Null Amplifier, Boost Bridge Accuracy with (Frantz)*	Aug	32
Ohmmeters Can Be Accurate (Conant) Oscillator	Jan	84
Multipurpose Transistor Crystal (Merkler)*	Jan	82
Universal 2-Terminal (Lederer)*	Mar	63
Panel Meter Uses Printed-Circuit Coils (WN)	Jul	45
Picture-Tube Testers, Modern (Kelvin)	Dec	59
Power Supply, Portable (Queen)*	Feb	37
Power Tester, Make (Winklepleck)	Sep	102
Probe, Battery-Current (NC)	Apr	128
Resistance-Box Modification (TTO)	Jan	144
Scope		
Deflection Correction (Pat)	Oct	117
Troubleshooting with (CI)	Sep	78
Voltage and Current Waveforms (CI) Corr	May	130
Wide-Band (CI)	Feb	77
Signal-Trace Industrial Circuits (Kernin)*	Sep	72
Sound-Intensity Indicator (Shippee)	Jan	90
Spiral, Better Yet Use (Jaski) (Corres)	Jan	26
Square Waves, Using (Tech)	Mar	142
Strobe for Tape (McCormick)*	May	40
Stroboscope, Battery-Operated (NC)	Jul	100
Stroboscope Flasher (Taylor)	Jun	35
Substituter, Gibbons (Davis)	Jul	61
Substitution Box, Improved (NC)	Aug	99
Sweep Circuits, Troubleshooting (Sykes)	Jul	37
Sweep Generator, Simple, Uses Varicap (Barron)*	Nov	58
Tachometer, Ignition-Operated (Schotz)*	Dec	54
Test-Load Box, Amplifier (Smith)	Nov	98
Trace Speeds Transistor Radio Servicing (Steckler)	Dec	36
Transformer, Electronic (Woods)*	Jun	98
Transistor(s) Checker	Apr	83
Alpha Tester (NC)	Jun	109
Beta Tester (NC)	Aug	98
Substitution Box (D'Airo)*	Feb	38
Voltage Indicator, Neon Lamps Make (Greenlee)*	Sep	98
Voltmeter, Transfer Standard Calibrates (Lederer)*	Jun	100
Vtvm		
Ac, Automatic (Marshall)	Aug	26
Double Value from (Guertin)	Apr	73
Readings, Equalize (Sutton)	May	41
Wire Stripping with Foot Pedal (Hughes)	Sep	92
Third Speaker, Add Easy Way (Burststein)	Oct	45
Timer, Automatic Recycling (Fannon)*	Jul	36
TIROS in Sky (Steckler)	Jun	86
Tough Dog! (Fred)	Feb	125
Trace Speeds Transistor Radio Servicing (Steckler)	Dec	36
Transfer Standard Calibrates Voltmeter (Lederer)*	Jun	100
Corres	Sep	22
Transformer, Winding Transistor-Power-Supply (Winklepleck)	Oct	55
Transformers, Using Audio (Ravenswood)	Apr	100
Transient Capacitor—What Is It? (Darling)	Nov	79
Transitone Locates Hidden Wiring (Parker)*	Dec	35


TRANSISTOR(ized) (Cont'd)

Printed-Circuit Board (WN)	Jun	63
Pulse Integrator (NC)	Nov	119
Radiation Detector (Pat)	Nov	100
Radio(s)		
Auto		
Build This (Martin)*	Mar	40
Corr	May	130
FM	Aug	52
Heat Damage (Tech)	May	116
FM-AM Portable	Jun	52
FM-AM Portables Are Here (Scott)	Apr	43
Loopstick Tracking (Tech)	Jul	113
Matchbox (Martin)*	Jun	58
Corres	Jul	20
Remo-Nemo (Reed)*	Dec	77
Remote-Control Transmitter (NC)	Nov	120
Reserve Power for Survival (Prensky)	Jul	96
7-Transistor, Pocket (Wittlinger)*	Mar	18
Corres		
Shirt-pocket Reflex for Local Listening (Mason)*	Jul	92
Speaker, 8-Inch (Grace)*	Oct	52
Super-Eight (Klein)*	Aug	44
Corr	Sep	116
Superheterodyne, 1-Transistor (NC)	Dec	118
Trace Speeds Servicing (Steckler)	Dec	36
Transceiver, "Little Handful" for Citizens Band (Queen)*	Aug	50
Transitube Pocket (Davidson)* (Corr)	May	130
Ultra-Sensitive, 3-Transistor (Amorose and Hoffmeister)*	Dec	39
Uses Original Transistor Amplifier (Ciardi)*	Dec	86
World Series Special (Stanley)*	Sep	57
Reflex Stage (Pat)	May	130
Relay, Capacitance (Turner)	Oct	54
Relay, Touch-Plate (NC)	Jun	107
Stroboscope, Battery-Operated (NC)	Jul	110
Tape Recorder, 4-Track, Matchbox-Size (Johnson)*	Jul	76
Corr	Sep	116
Television (Emerson) (NB)	Feb	6
19-Inch (Motorola) (NB)	Jul	12
Japanese (NB)	Apr	8
Servicing Motorola's New Thermostat (Pat)	Sep	82
Transmitter, Remote-Control (NC)	Sep	119
Voltage Regulator for Car (Meyer)*	Nov	120
Corres	Feb	107
Apr	22	
Tricky Radios, Those (Darr)	May	100
Troubleshooting Sweep Circuits (Sykes)	Jul	37
Troubleshooting Vertical Oscillator and Output Stages (Jacques)	Oct	40
Technotes		
Adapter, Phone-Tip	Jul	115
Audio		
Plug Adapter	Apr	107
Speaker Transformers, Mounting	Sep	123
Tape Splicer, Cleaning	Mar	133
Turntable, New Flocking for	Oct	120
Ballpoint-Pen Uses Bushings from	Feb	146
Insulating Sleeve from	Feb	147
Oil Dropper	Feb	146
Batteries, Vials Hold	Feb	147
Battery Reminder	Nov	124
Battery Replacement	May	112
Cable Connectors	Sep	121
Can Opener Is Service Tool	Jun	121
Caps, Corkscrew for Tightening	Nov	124
Chemicals, Tape Protects	May	113
Clips, Double, Are Useful	Sep	122
Connectors, Solderless	May	113
Drop-Cloth Pockets	May	113
Experimenter's Hint	Nov	126
File, Plastic Rubber Cleans	Nov	126
Fuse Holder for Spares	Jul	115
Hole Shrinking	Aug	114
Intermittents, Foil Foils	Feb	145
Jumpers, Keep Untangled	Dec	121
Line-Cord Fraying, Reduce	Nov	125
Line-Cord Plug	Jun	121
Liquid-Metal Service Aid	Jan	145
Loop Oil	Oct	120
Metal, Drilling Thin	Jan	145
Meter Case, Nonmagnetic	Aug	113
Meter Scales, Brighten	Jul	114
Mirror Holder	Jun	122
Panel Markings, Renew	Apr	108
Panels, Attractive	Nov	126
Parts Bin, Handy	Mar 134; Nov	124
Corres	Jun	26
Parts Substitution in Dogs	Sep	124
Probe Guards, See-Through	Jun	121
Punch Care	Apr	107
Punch Sharpening	May	113
Radio		
Earpiece Repair	May	114
Fringe Reception, Boost	Mar	133
Goodwill Kink	Oct	124
Selenium Rectifiers, Replacing	Mar	133
Warmup Time, Eliminate	Jun	122
Relay, Cure Sticky	Aug	114
Relay Sensitivity, Improve	Feb	145
Resistance-Box Modifications	Jan	144
Screws, Turning Tough	Jan	145
Screws, Tighten Self-Tapping	Nov	126
Shock Absorbers	May	114
Socket Mount	Dec	120
Socket, Testing at Top	Oct	120
Solder Dispenser	Mar	135
Solder, Spaghetti Insulates	Apr	107
Soldering		
Aid	Sep	124
Cast Iron	Jun	122
Heat Sink, Handy	Aug	114
Transistor Life Saver	Oct	122

TRY THIS ONE (Cont'd)

Soldering Iron			
Cleaner	Mar 135;	Oct	120
Corres		Jun	26
Holder		Jul	115
Maintenance		Jul	114
Pencil-Iron Rest		Feb	145
Tips, Custom		Nov	125
Tips, Spare		Jun	122
Technotes, Keep Tabs on		Mar	134
Television			
Antenna(s)			
Gimmick Reduces Nuisance Calls	May	113	
Lightning Arrester, Tent for	Jul	115	
Unusual Job	Aug	113	
Control Assembly, Dual	Jul	114	
CRT Cleaning Aid	Sep	123	
CRT Coating	Aug	112	
Fuses, Keep Handy	Mar	134	
Heat Lamp, Don't Use	Jan	144	
Holes, Compound Fills	Aug	114	
Knobs, Plastic	Oct	122	
Mask-Removal Tool	Apr	108	
Shock-Absorbing Ride	Jul	115	
Test-Lead Extensions	Sep	122	
Tool Holder	Nov	125	
Tools, Color-Code	Jan	145	
Transistor Heat Sink	Dec	120	
Transistor Sockets, Power	Jun	121	
Trouble Light, Stay-Put	Jul	115	
Tube Empties, Carbons Mark	Feb	147	
Tube Holder	Feb 146;	Dec	120
Vom in Shaving Bag	Dec	121	
Wire			
Liquid Metal Anchors	Sep	123	
Stripper	Jun	122	
Stripping Short Harnessed	Feb	146	
Wrench, Double-Duty Allen	May	114	
Tube-Changing, Tough Ones (Darr)	Oct	84	
TUBE(S)			
CRT's, Field-Check (Egan)	Jun	96	
Cure Discovered!	Mar	113	
Most Powerful (WN)	Jan	63	
New, and Semiconductors	Jan 127; Feb	142;	
Mar 130; Apr 113; May 109; Jun 116; Jul	102;		
Aug 96; Sep 104; Oct 96; Nov 115; Dec	100		
New Departures in Semiconductors and			
(Steckler)	Aug	68	
Polyoptic Sealing	Jul	52	
Pix			
Aluminized Low-Voltage	Aug	69	
Reflection-Free	Aug	68	
Solid-State Emitter (NB)	Apr	6	
Square-Necked (WN)	Jul	45	
19-Inch Square (NB)	Feb	21	
Power Pentode, Better	Jun	37	
Recording, Dual-Gun TV (NB)	Jul	6	
Three in One Envelope (NB)	Sep	6	
Tunnel-Diode			
Noise Generator (Queen)*	Nov	42	
Oscillator (Grossman and Friedman)*	Sep	40	
Really Works (Queen)*	Oct	58	
Story (Walters and Claeys)	Jul	26	
Turntables and Pickup Arms from Kits			
(Graham)	Mar	44	
Twin-Coupled Amplifier			
High Power for (Crowhurst)*	Oct	34	
Updating R-E (Crowhurst)*	Jun	30	
Two-Way Radio for Citizens Band (Scott)	Jan	91	
U			
Ultra-Sensitive 3-Transistor Radio (Amorose and Hoffmeister)*	Dec	39	
Ultrasonic Motion Study, System for (Pat)	Sep	119	
Ultrasonics, Introduction (Jaski)	Aug	54	
Understanding Industrial Diagrams (Jaski)	Jun	54	
Underwater Metal Detector (Richardson)	Jul	30	
Corres	Sep 21;	Oct	21
Ungrounded Equipment Can Be Fatal	Sep	75	
Universal 2-Terminal Oscillator (Lederer)*	Mar	63	
Updating R-E Twin-Coupled Amplifier (Crowhurst)*	Jun	30	
Using 24-28-Volt Dc Relays (Oberio)	May	35	
V			
Varicap Sweep Generator, Simple (Barron)*	Nov	58	
Versatile Electron-Ray Tube (Shields)*	Mar	64	
Voltage Indicator, Neon Lamps Make (Greenlee)*	Sep	98	
Voltage Regulator, All-Transistor, for Car (Meyer)*	Feb 107;	Apr	22
Corres	Apr	73	
Vtvm, Double Value from (Guertin)			
W			
We Learned from Dogs! (Centerville)	Jun	91	
We Troubleshoot Horizontal Oscillator (Jacques)	Apr	55	
Weld Timer, TV Tech Repairs (Darling)	May	32	
What's with Characteristic Impedance (Middleton)	Mar	74	
Corres	Jun 18; Jul 22;	Oct	21
Wheatstone Bridge, Divide and Multiply with (Frantz)*	Jun	48	
Winding Transistor-Power-Supply Transformers (Winklepleck)	Oct	55	
World Series Special (Stanley)*	Sep	57	
Z			
Zener Diodes Prevent Speaker Burnout (Ives)	Aug	12	

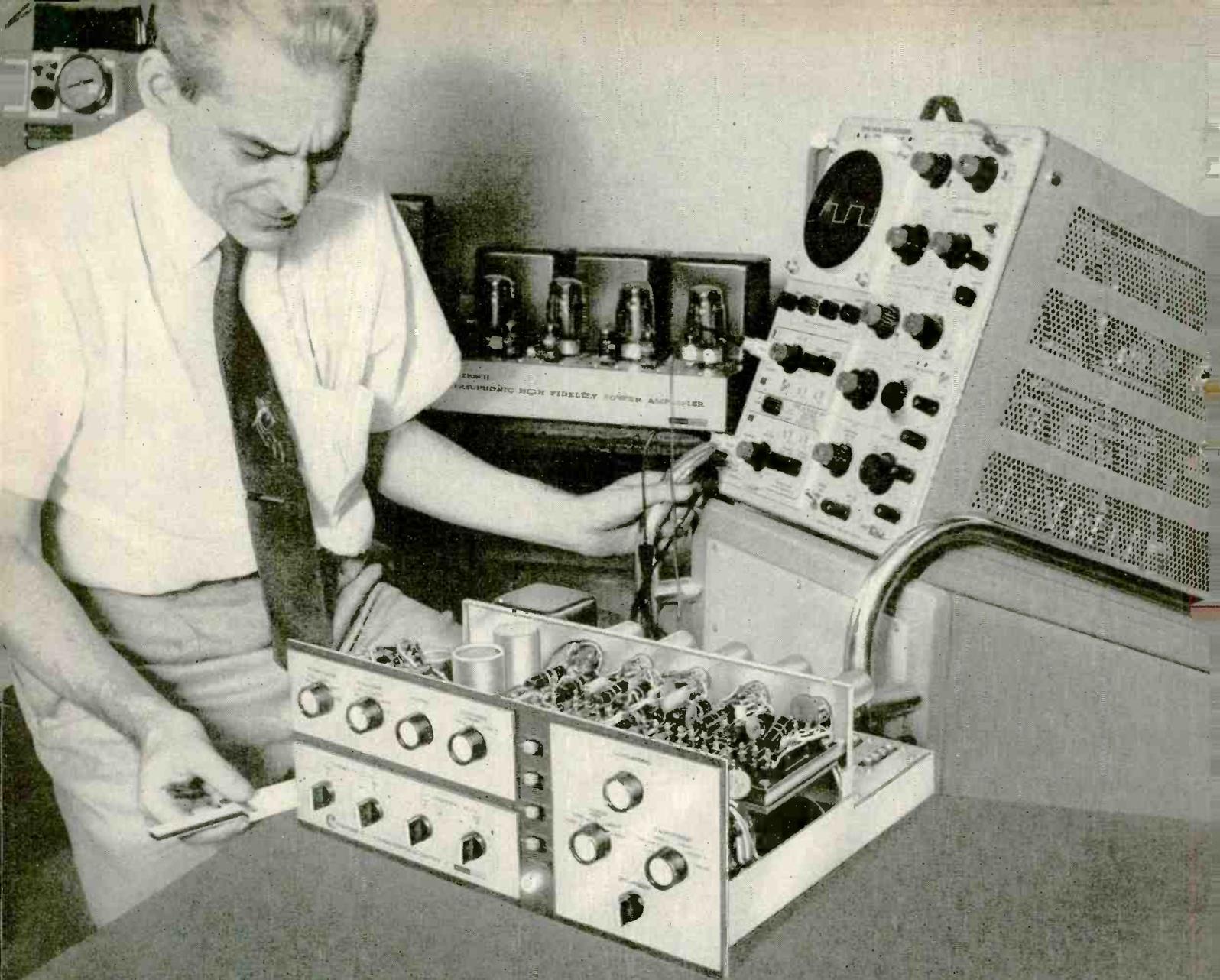[This ANNUAL INDEX is another service to readers. "One-side copy," it is planned to be cut out for convenience in use. Key to symbols on page 130.]



AT NORMAL LISTENING LEVELS THE ONLY MEASURABLE DISTORTION COMES FROM THE TEST EQUIPMENT!

Measuring intermodulation, harmonic or phase distortion on the new Citation Kits can be a unique experience for any engineer. He will find that *at normal listening levels the only measurable distortion comes from the test equipment.*

But let's put the numbers away. The real distinction of Citation is not in its specifications — remarkable as they are. It is, rather, in its performance — which goes well beyond the point of numbers. *Citation actually sounds recognizably best.* The "Citation Sound" has created so profound an impression, that the words have become part of the language of high fidelity.

In AUDIO MAGAZINE, editor C. G. McProud, wrote: *"When we heard the Citations, our immediate reaction was that one listened through the amplifier system clear back to the original performance, and that the finer nuances of tone shading stood out clearly and distinctly for the first time."*

The basic quality of the "Citation Sound" was summed up by the Hirsch-Houck Labs in HIGH FIDELITY: *"The more one listens... the more pleasing its sound becomes."* Another glowing tribute to Citation and its talented engineering group, headed by Stew Hegeman (shown above), came from Herbert Reid who said in HI-FI STEREO REVIEW: *"Over and above the details of design and performance, we felt that the Citation group bore eloquent witness to the one vital aspect of audio that for so many of us has elevated high fidelity from a casual hobby to a lifelong interest: the earnest attempt to reach an ideal — not for the sake of technical showmanship — but for the sake of music and our demanding love of it."*

THE CITATION I, Stereophonic Preamplifier Control Center... \$159.95; Factory-Wired... \$249.95; Walnut Enclosure, WC-1... \$29.95.

THE CITATION II, 120 Watt Stereophonic Power Amplifier... \$159.95; Factory-Wired... \$229.95; Charcoal Brown Enclosure, AC-2... \$7.95. All prices slightly higher in the West.

For a complete report on these remarkable instruments, write Dept. RE-12 Citation Kit Division, Harman-Kardon, Plainview, N. Y.

Build the Very Best **CITATION KITS** by **harman kardon**

ASTATIC 77

DYNAMIC CARDIOID MICROPHONE

with the industry's most positive anti-feedback characteristics



Something to Sing about

LIST PRICES
Model 77 (Illustrated)
Chrome Finish, \$82.50;
Gold Finish, \$92.50.
Model 77L (Head only),
Chrome Finish, \$72.50;
Gold Finish, \$82.50.
Model G-77 (Complete with G-Stand),
Chrome Finish, \$97.45.

When you're looking for the ultimate in cardioid microphones, consider these advanced features of Astatic's Model 77 and see if you don't agree that no other manufacturer has SO MUCH TO SING ABOUT—the most positive anti-feedback characteristics ever achieved, -18 db; exclusive Mylar diaphragm that is pop-proof and blast-proof, retains like-new flex properties for more years; an exclusive sintered bronze method of acoustic phase shifting that creates the industry's top directional characteristics; -52 db output and exceptionally flat response through 30 to 15,000 cps.


Do one thing for your own satisfaction. On your next installation, make a direct comparison of the Astatic 77 with any other cardioid. We'll guarantee—when anyone mentions the word "cardioid" again, you'll sing the praises of this incomparable Astatic instrument.

THE **Astatic** CORPORATION, CONNEAUT, OHIO
IN CANADA: CANADIAN ASTATIC LIMITED, TORONTO, ONTARIO
EXPORT SALES: ROBURN AGENCIES INC. 431 GREENWICH ST., N. Y. 13, N. Y., U.S.A.

FROM What You HEAR

GO BY BRAND
—GO BUY ASTATIC

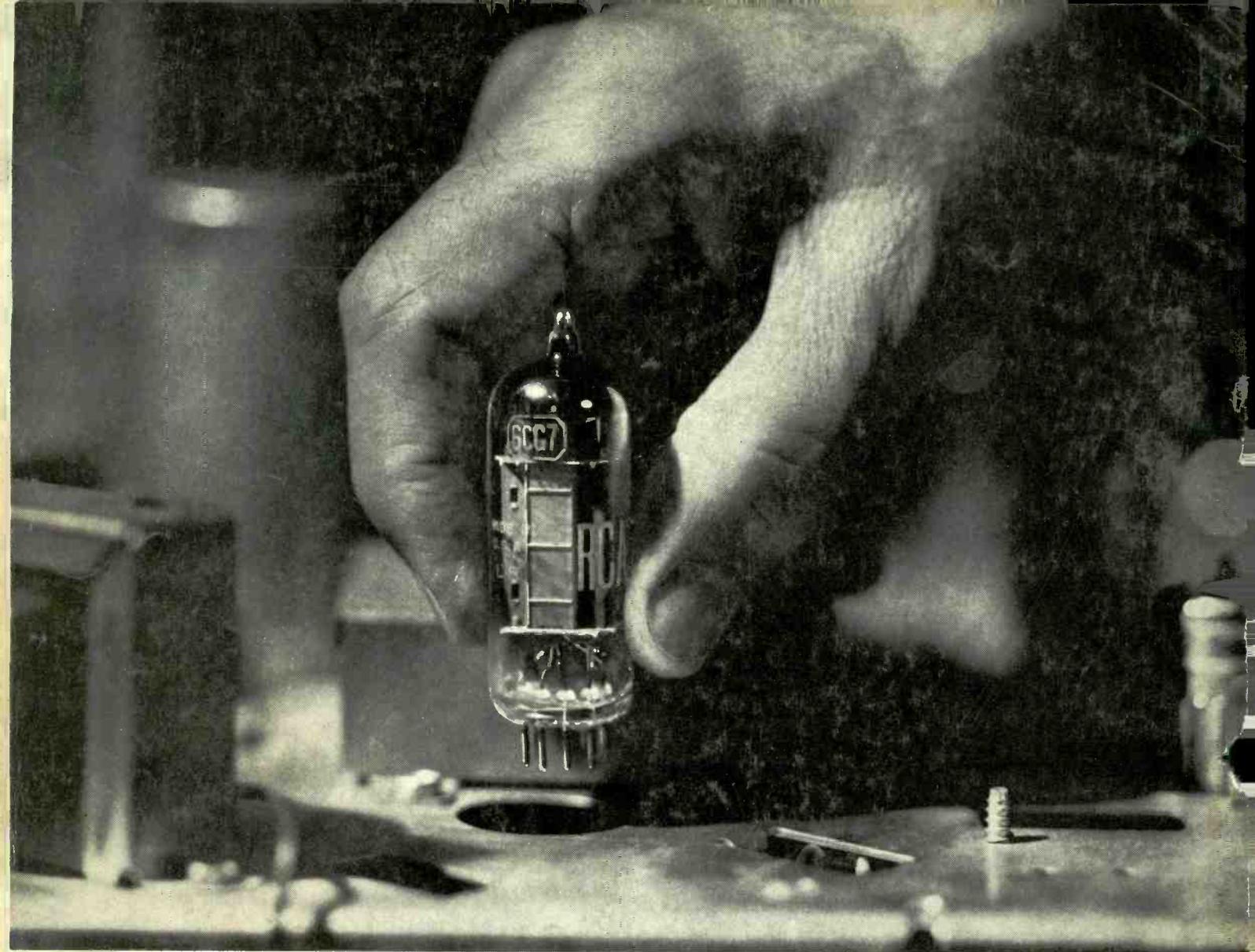SINGING SOUNDS BETTER WHEN THERE'S AN ASTATIC MICROPHONE ABOUT



WHEN YOU REPLACE A TUBE . . .

You have a lot at stake each time you replace a receiving tube in a customer's set. Your professional reputation, your customer's confidence, your day's profits—even future business—all depend on the quality of that replacement tube.

It is RCA's constant aim to provide receiving tubes you can install with confidence. To this end, RCA carefully controls every step of the tube making process from initial design to final test.

QUALITY BY DESIGN—Some of the foremost tube experts in the industry collaborate on each new RCA tube design. Engineers, chemists, physicists, metallurgists, production specialists, field representatives, all contribute their own skills and knowledge before a new RCA tube design ever leaves the drafting board.

IMPROVED QUALITY FROM NEW AND IMPROVED MATERIALS—All parts and materials in RCA tubes are either *produced* or *processed* by RCA under strictest quality control. Moreover, RCA scientists search constantly for new and better materials which will still further improve performance of RCA tubes. Many tube types you install today benefit from new cathode and plate materials developed in RCA labs.

QUALITY IN MANUFACTURING—Because tube construction is just as important as design and materials, RCA maintains a system of supervisory microscopic inspection at key points on every production line to detect any flaw in assembly. And to minimize the chance of human error, RCA has automated certain critical steps in tube production.

QUALITY BY TESTING AND CONTROL—Before shipment, *every single RCA receiving tube* is factory-tested for every significant characteristic. *A tube that fails one single test is rejected and destroyed. So there is no such thing as a "second" when you buy RCA.* In addition, thorough aging of tubes and rating-lab tests assure strict adherence to performance specifications.

This is why **YOU CAN REPLACE WITH CONFIDENCE** with RCA tubes . . . and why RCA tubes give you an extra advantage on every service job. Electron Tube Division, Harrison, N. J.



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA