

JANUARY

# Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

**Electronics Cools / Build an Electronic Micrometer**  
**Simple Reverberator / What's New in 1962 TV's**

GO GERNSBACK, Editor-in-chief



**Biggest Electron Microscope  
Is Tool for Tube Improvement**

See page 4

50c

OW 06 5  
NOLLY  
-6



# NEW CALLBACK-PROTECTION WELDED INTO EVERY SILVER SCREEN 85 TV PICTURE TUBE

Sylvania technique  
eliminates tube failures  
caused by open heater or  
cathode lead welds.  
Protects your profits.

Sylvania . . . the leader in picture tube improvements . . . now gives you another built-in plus — “Controlled Atmospheric Welding”! Engineering investigations revealed that in the welding of picture tube gun parts something more than automatic controls, skilled operators and careful inspection was needed. The uncontrolled factor was the degree of oxidation occurring at the time of welding. The answer — control the atmosphere surrounding the weld at the instant it is made!

Now . . . through “Controlled Atmospheric Welding” Sylvania Silver Screen 85 TV picture tubes give you maximum assurance against callbacks. Common field problems of intermittent, poor, or open connections due to oxidized welds have been eliminated. Every year hundreds of thousands of TV picture tubes are replaced with Silver Screen 85. No wonder. It's more profitable in the long run.

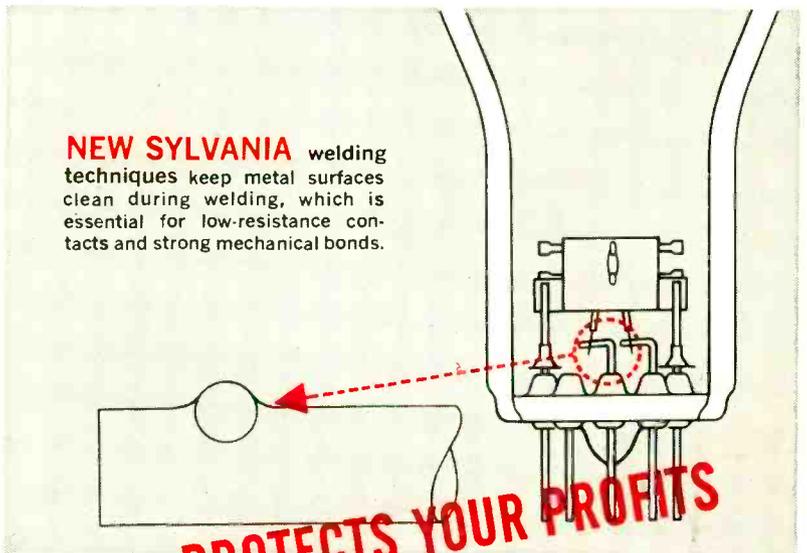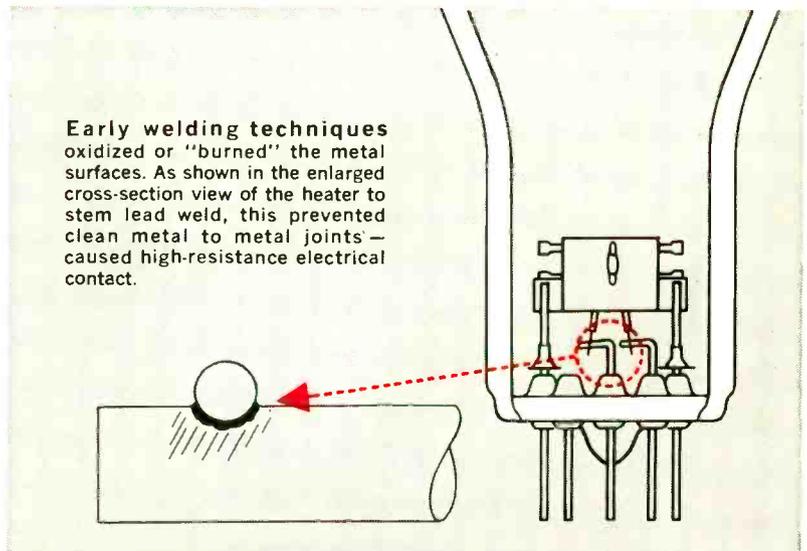Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, New York.



**PROTECTS YOUR PROFITS**

# SYLVANIA

SUBSIDIARY OF

**GENERAL TELEPHONE & ELECTRONICS**



# SUPERB NEW SCOTT MULTIPLEX TUNER KIT




## Now you can build a Multiplex Tuner that meets rigid factory standards

Now have the fun of building a genuine H. H. Scott Wide-Band FM Stereo Tuner in just a few hours . . . and save money, too. Revolutionary Scott-developed kit building techniques assure you of performance equaling Scott factory units.


The new LT-110 Scottkit features a pre-wired and tested multiplex section plus the famous silver-plated factory built and aligned front end. Sensitivity of this magnificent new tuner is 2.2  $\mu$ v. IHFM. There are special provisions for flawless tape recording right "off-the-air."

Scott Wide-Band multiplex tuners are the standard of the industry. They have been chosen by leading FM stations from Boston to San Francisco. If you want to build a truly professional component choose a Scottkit. All H. H. Scott kits are backed by over 15 years experience in the design and production of superb components. Important features include front panel tape recorder output and precision illuminated tuning meter. All critical parts heavily silver plated. Unique Ez-a-Line system assures factory performance without expensive test equipment. Dimensions: 15½ W x 5¼ H x 13 D in accessory case.

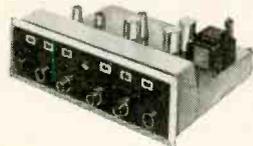
## New Scott Amplifier Kits to match the LT-110



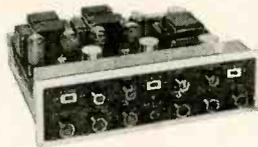
**LC-21 Preamp Kit**  
Performance so outstanding this kit is used for laboratory purposes. Hum level —80 db, distortion less than 0.1%, frequency response 8 to 50,000 cps. **\$99.95\***  
Matching LK-150 130 Watt Power Amplifier **\$169.95\***



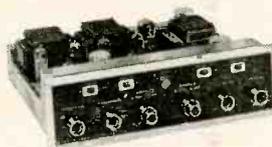**LK-72 80 Watt Stereo Amplifier Kit** —  
Plenty of power for any hi-fi system. Complete tape recording and monitoring facilities. Oversized transformers weigh 12 pounds! Performance equal to the best pre-amp/power amp systems. **\$159.95\***



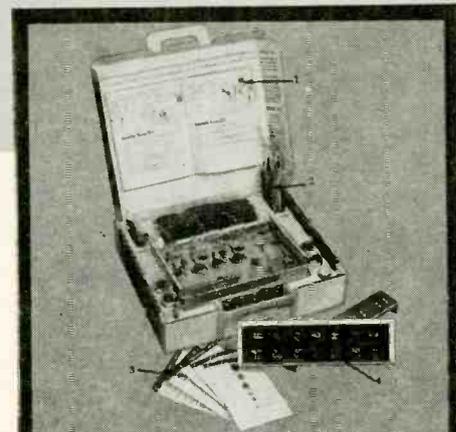**LK-48 48 Watt Stereo Amplifier Kit** —  
12 front panel controls. Gives full power down to 20 cps. Husky output transformers. All aluminum chassis and DC operated preamps. Scott quality at a best-buy price. **\$119.95\***



### These Exclusive Scottkit Features Make Kit Building Foolproof and Fun

1. All assembly diagrams show parts in exact size and in full color, eliminating mistakes.
2. All wires cut to exact length and pre-stripped assuring correct lead placement and dress.
3. Exclusive Part-Charts with parts mounted in order of assembly, eliminating confusion and mistakes. No loose bag of parts.
4. Handsome appearance makes Scottkits completely professional in looks as well as in performance.

**H. H. SCOTT**

H. H. SCOTT, INC., Dept. 570-01, 111 Powdermill Road, Maynard, Mass.

Send me your new Scottkit catalog and complete information on FM Stereo.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Export: Morhan Exporting Corp., 453 Broadway, NYC. Canada: Atlas Radio Corp., 50 Wingold Ave., Toronto.

\*Case extra. Slightly higher west of Rockies

RADIO-ELECTRONICS published monthly at Mt. Morris, Ill., by Gernsback Publications Inc. Second-class postage paid at Mt. Morris, Ill. Copyright © 1962, by Gernsback Publications Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions. SUBSCRIPTION RATES: US and possessions, Canada: \$5 for 1, \$9 for 2, \$12 for 3 years. Pan-America countries: \$6 for 1, \$11 for 2, \$15 for 3 years. Other countries: \$6.50 for 1, \$12 for 2, \$16.50 for 3 years.

# Radio-Electronics

Formerly RADIO CRAFT — Incorporating SHORT WAVE CRAFT — TELEVISION NEWS — RADIO & TELEVISION\*

JANUARY 1962  
VOL. XXXIII No. 1

## editorial

Hugo Gernsback 25 Future of Service Industry

## television

- Larry Steckler 37 Tube Layouts In TV Sets, Admiral 1960-61  
*Handy fold-up booklet for your tube caddy.*
- Wayne Lemons 50 TV Designs '62  
*Special 8-page report—What's new for '62*

## industrial electronics

- Lawrence H. Ott 26 Electronic Cooling and Heating  
*Another way to use semiconductors*
- Tom Jaski 46 Installing, Testing and Maintaining Relays  
*The practical aspects of handling relay equipment*
- Ed Bukstein 68 Industrial Electronics Dictionary  
*From photoelectric pyrometer to proportional control*

## audio-high fidelity

- George Manning Lewis 30 Build a Simple Reverberator  
*Find out about reverb for yourself*
- Warren Roy 39 Modern Audio Expansion  
*Fuller sound from your hi-fi*
- E. Aisberg and Fred Shunaman 63 Flat Voice Coils Make Flatter Speakers
- Chester S. Lawrence 78 Phase Checker Speeds Hi-Fi Installation

## test instruments

- John A. Dewar 62 Simple Unit Tests Intermittent Capacitors  
*Useful instrument is easy to build*
- Alvin Mason 66 Antenna Meter for Citizens Band  
*Home-built—checks SWR, output power, field strength*
- Wayne Lemons 74 Test Equipment Report  
*Lafayette KT-174 vtvm kit*
- R. E. Baird and J. A. Brady 79 For a Cooler Scope

## electronics

- Dave Stone 34 An Electronic Micrometer  
*Home-made instrument measures thickness accurately*
- Aurelius Sandor 42 Seeing Is Believing in Cathode Research (Cover Story)  
45 What Is Your EQ?  
*December solutions on page 86*
- H. Schreiber 79 Photomagnetic Toy Is True Servomechanism  
84 Automatic Secretary Nearer

## what's new

- 49 Pictorial Reports of New Developments

## radio

- 29 Instant-On Circuit for Ac-Dc Receivers
- D. Gifford 40 End Auto Radio Interference  
*Freedom from ignition noise up to 1,000 mc*
- Dude Lynn 83 CB Antenna

## the departments

- |  |                                |                         |                  |
|--|--------------------------------|-------------------------|------------------|
| 18 Correspondence                      | 112 New Patents                | 6 News Briefs           | 106 Technotes    |
| 116 New Books                          | 87 New Products                | 100 Noteworthy Circuits | 114 Try This One |
| 96 New Literature and Business Getters | 108 New Tubes & Semiconductors | 82 Shortwave Forecast   | 115 50 Years Ago |
|  |                                | 98 Technicians' News    |                  |

## Over 50 Years of Electronic Publishing

EDITOR-IN-CHIEF AND PUBLISHER  
*Hugo Gernsback*

EDITOR

*M. Harvey Gernsback*

MANAGING EDITOR  
*Fred Shunaman*

TECHNICAL EDITOR  
*Robert F. Scott, W2PWG*

ASSOCIATE EDITOR  
*Larry Steckler*

EDITORIAL ASSOCIATE  
*I. Queen*

SERVICE EDITOR  
*Jack Darr*

ART DIRECTOR  
*Harry Schlack*

TECH. ILLUSTRATION DIRECTOR  
*Wm. Lyon McLaughlin*

ART ASSOCIATE  
*Fred Neinast*

PRODUCTION MANAGER  
*Elizabeth Stalcup*

DIRECTOR, ADVERTISING SALES  
*Lee Robinson*

EASTERN SALES MANAGER  
*John J. Lamson*

CIRCULATION MANAGER  
*G. Aliquo*

DIRECTOR, NEWSSTAND SALES  
*Joseph L. Bund*

PROMOTION MANAGER  
*Robert Fallath*



Average Paid Circulation  
Over 155,000

## —on the cover—

Story on page 42

**Dr. Sandor studies cathode action with the help of the world's biggest microscope.**

Color original by Larry Ankerman, Bayside Laboratories, General Telephone & Electronics Laboratories, Inc.

## Gernsback Publications, Inc.

EXECUTIVE, EDITORIAL, ADVERTISING OFFICES

154 W. 14 St., New York 11, N.Y.  
Telephone AL 5-7755

CHAIRMAN OF THE BOARD  
*Hugo Gernsback*

PRESIDENT  
*M. Harvey Gernsback*

SECRETARY  
*G. Aliquo*



Radio-Electronics is indexed in  
*Applied Science & Technology Index*  
(Formerly Industrial Arts Index)

\*Trademark registered U. S. Pat. Office

# GET YOUR ELECTRONICS-TV-RADIO HOME TRAINING FROM N.T.S. RESIDENT SCHOOL

## BREAK THROUGH TO HIGHER PAY, GREATER JOB SECURITY

START NOW! Break through the Earning Barrier that stops "half-trained" men. N.T.S. "All-Phase" Training prepares you . . . at home in spare time . . . for a high-paying CAREER as a MASTER TECHNICIAN in Electronics — TV — Radio. One Master Course at One Low Tuition trains you for unlimited opportunities in All Phases: Servicing, Communications, Preparation for F.C.C. License, Broadcasting, Manufacturing, Automation, Radar and Micro-Waves, Missile and Rocket Projects.

A MORE REWARDING JOB . . . a secure future . . . a richer, fuller life can be yours! As an N.T.S.

MASTER TECHNICIAN you can go straight to the top in industry . . . or open your own profitable business.

Over 1 City Block of Modern School Facilities, Laboratories and Shops Housing Over 1,000 Students.

50,000 Graduates — all over the World — since 1905

BETTER . . . MORE COMPLETE . . . LOWER COST . . . WITH NATIONAL SCHOOLS' SHOP-METHOD HOME TRAINING!

BETTER . . . Training that is proved and tested in N.T.S. Resident School shops and laboratories, by a School that is the OLDEST and LARGEST of its kind in the world.

MORE COMPLETE . . . You learn ALL PHASES OF Television — Radio — Electronics.


LOWER COST . . . Other schools make several courses out of the material in our ONE MASTER COURSE . . . and you pay more for less training than you get in our course at ONE LOW TUITION!

**NATIONAL TECHNICAL SCHOOLS**  
WORLD-WIDE TRAINING SINCE 1905

THE SCHOOL BEHIND YOUR HOME-STUDY TRAINING



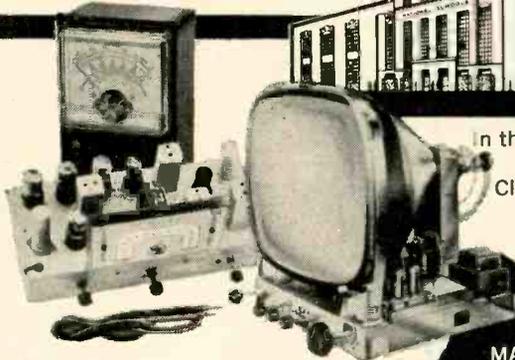In these modern School Headquarters your Home Training is: Classroom-Developed, Lab-Studio Planned, Shop-Tested, Industry-Approved, Home Study-Designed.



TRAIN AT HOME IN YOUR SPARE TIME . . . AT YOUR OWN PACE!

## 19 BIG KITS YOURS TO KEEP

- Friendly Instruction and Guidance
- Graduate Advisory Service
- Unlimited Consultation
- Diploma Recognized by Industry
- EVERYTHING YOU NEED FOR SUCCESS

## N.T.S. IS NOT JUST A MAILING ADDRESS ON A COUPON

N.T.S. is a real school . . . a world famous training center since 1905. Thousands of men from all over the world come to train in our shops, labs, studios and classrooms.

You learn quickly and easily the N.T.S. Shop-Tested way. You get lessons, manuals, job projects, personal consultation from instructors as you progress. You build a Short-Wave, Long-Wave Superhet Receiver plus a large screen TV set from the ground up with parts we send you at no additional cost. You also get a Professional Multimeter for your practical job projects. The Multimeter will become one of your most valuable instruments in spare time work while training, and afterwards, too. Many students pay for their entire tuition with spare time work. You can, too . . . we show you how.

SEND FOR INFORMATION NOW . . . TODAY!  
IT COSTS YOU NOTHING TO INVESTIGATE

After you graduate you can open your own TV-Radio repair business or go into high paying jobs like these: Communications Technicians, Hi-Fi, Stereo and Sound Recording Specialists, TV-Radio Broadcasting Technician, Technician in Computers & Missiles, Electronics Field Technician, Specialist in Micro-Waves and Servomechanisms, Expert Trouble Shooter, All-Phase Master Technician, TV-Radio Sales, Service and Repair.

RESIDENT TRAINING AT LOS ANGELES  
If you wish to take your Electronics-TV-Radio training in our famous Resident School in Los Angeles — the oldest and largest school of its kind in the world — write for special Resident School catalog and information, or check special box in coupon.



ACCREDITED MEMBER

**NATIONAL TECHNICAL SCHOOLS**

WORLD-WIDE TRAINING SINCE 1905  
4000 SO. FIGUEROA ST., LOS ANGELES 37, CALIF., U. S. A.

MAIL COUPON NOW FOR FREE BOOK & ACTUAL LESSON

No obligation.  
No salesman will call.



**NATIONAL TECHNICAL SCHOOLS**  
WORLD-WIDE TRAINING SINCE 1905

Mail Now To  
National Technical Schools, Dept. RG-12  
4000 S. Figueroa St., Los Angeles 37, Calif.  
Please rush FREE Electronics-TV-Radio "Opportunity" Book and Actual Lesson.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check here if interested ONLY in Resident Training at Los Angeles.  
VETERANS: Give date of discharge \_\_\_\_\_

# News Briefs

## Electronic Highlights of 1961

Satellite summary as of Nov. 1 shows that the US has launched 55 satellites and still has 31 in orbit around the earth and two in a solar orbit. Twelve of these are still transmitting. The Soviet Union has launched a total of 16 satellites. Thirteen are still in orbit around the earth and two are in a solar orbit. All are crammed with various types of electronic gear ranging from ordinary radio transmitters, receivers and repeaters to TV cameras, solar cells, radiation detectors and propagation measuring instruments.

Back on earth there has been a surge in transistorized CB transceivers. Pocket units with a range of up to 1 mile fall within the FCC low-power rules and can be used without an FCC license. FM multiplexing has put

stereo broadcasts into thousands of homes across the US. Only a handful of stations are now broadcasting, but their number is expected to multiply rapidly.

Some new apartment houses and homes have closed-circuit TV for seeing who is at the front door.

Transistor use is ever growing, threatening tubes. Latest word is that two manufacturers are closing down tube operations, will produce only transistors in the future.

Color TV took an upswing with color manufacturers getting out of the red for the first time. Field is also getting competitive with introduction of Zenith color receiver. A Japanese import using an RCA color picture tube also appeared.

with instruments. In FAA tests of many types of electronic devices, only FM receivers were found to be a potential cause of trouble. (August, page 6.)

### JANUARY

**Electric Anesthetic.** A 700-cycle signal applied to patient's temples renders him unconscious in less than a minute. When current is removed, patient awakens. There are no known aftereffects. Complete system costs only \$150. (March, page 6.)

**TV Classroom in the Sky.** Educational TV programs are broadcast over a six-state area from two planes packed with TV transmitting gear. They fly at an altitude of 23,000 feet. (March, page 12.)

**Magnetic Waveguides Around Earth.** Scientists have discovered "ducts" in space around the earth that bend radar beams, channelling them in a circular path. They come back to earth thousands of miles from the transmitter site. The ducts follow lines of the earth's magnetic field. (April, page 8.)

### FEBRUARY

**Entertainment Wall.** Deluxe apartments in Chicago come equipped with a living-room wall filled with AM and FM radio, stereo hi-fi and 4 1/2 x 6-foot projection TV. The rental fee will also be deluxe. (April, page 18.)

**Hi-Speed X-Rays.** Pulsed X-ray system cuts exposure time to as little as 1 microsecond. Pulse system delivers a 20-megawatt electron beam focused on X-ray tube target. (April, page 18.)

**5-Gigacycle Transistor.** Even uhf is not safe from transistors. MADT prototype with 14-db gain at 1,000 mc has been made to oscillate at 5 gigacycles (5,000 mc). (May, page 14.)

### MARCH

**Dark Heater Tube.** Operates at 20% cooler temperature than equivalent types with standard heater. New type is expected to reduce effects of ac leakage and hum and cut down on heater-cathode shorts. (May, page 6.)

**Circuit Size Cut 90%.** New manufacturing techniques combining deposited film and sputtering processes produce a microminiature circuit that looks like an ordinary transistor (except for the number of leads). Unit actually contains 4 transistors and 2 resistors. (June, page 6.)

**Uhf Ultrasonics.** New piezoelectric semiconductor operates at frequencies up to and beyond 10,000 mc. Made of a gallium arsenide semiconductor base with an extremely thin metal film deposited on it. (June, page 8.)

### APRIL

**Wireless Power.** Amplifon tube which can deliver more than 1,000 kw of rf power at microwave frequencies may lead to transmission of electric power by radio. Antenna systems for minimum loss and economics of generating power for transmission are still problems. (June, page 12.)

### MAY

**Living Batteries.** New source of electric power is a fuel cell that uses living bacteria. Such cells are said to offer the possibility of greater power conversion rates than existing types. Also, living batteries do not depend on high temperatures or pressures needed by existing types. (August, page 6.)

**FM Portables Banned from Planes.** Radiation from these receivers was proved to interfere

### JUNE

**FM Stereo on the Air.** Following final FCC ruling authorizing FM stereo transmission, Zenith and G-E put FM stereo broadcasts on the air. By end of the year about 15 stations were broadcasting. All use FCC-approved system which combines methods developed by G-E and Zenith. (June, page 6.)

**Ephi to Track Tornadoes.** Special three-antenna receiving system picks up static disturbances from storm centers. Triangulation pinpoints location, enables observers to track storm with extreme accuracy. (July, page 6.)

### JULY

**New Color CRT.** From England comes word of a new kind of color TV picture tube—a 4-inch cylinder surrounded by a lens arrangement that rotates at about 1,000 rpm. Image produced by the experimental arrangement is projected on a mirror for viewing. (October, page 6.)

**Solid-State IFT.** Ceramic coupling unit replaces if transformers in transistor radios and could reduce price of these receivers. The device has three leads and consists of two discs of a modified zirconate compound. (September, page 8.)

### AUGUST

**Electronics and Miss Universe.** They were one and the same this year as German electronic engineer Marlene Schmidt was crowned Miss Universe in Florida. Some called her electronics' answer to Marilyn Monroe. (September, page 6.)

**Medical Electronics Convention.** Devices from radio pills for telemetering data from the stomach to computers capable of analyzing and identifying 800 diseases were shown. Vladimir B. Zworykin presided at the conference. (October, page 13.)

### SEPTEMBER

**Diamond Semiconductors.** These are made in the laboratory from a mixture of graphite and catalyst to which impurities such as boron, beryllium or aluminum are added to give the crystal semiconductor properties. To date only p-type crystals have been made. Experiments are continuing to develop n-type materials. (November, page 6.)

**Ion-Engine Space Drive.** Operating engine has been tested in vacuum chamber. It uses a cesium propellant diffused through a hot tungsten element and then through a system of electrodes which accelerates the ions to a very high exhaust velocity. Device cannot be used in an atmosphere, but should make excellent space drive. (December, page 6.)

### OCTOBER

**Communications Belt Around Earth.** Highly controversial experiment placed 350 million tiny copper hairs into orbit 2,100 miles above earth. They are expected to form a temporary belt which can be used to reflect radio signals for long range communications. If successful, larger-scale experiments may be attempted. (December, page 10.)

## Pay TV in Arrears?

The experimental pay-TV system in Toronto's suburb Etibicoke was stated to be losing \$11,000 a week after nearly 2 years of operation. The statement was made by director Norman Robertson of Famous Players Canadian, as he resigned a directorship he had held 20 years. He accused Paramount Pictures of "milking" its subsidiary Famous Players Canadian while baring the public with "laudatory press releases about what is happening in Etibicoke."

A Paramount spokesman in New York, repudiating Robertson's claims, pointed out that the experiment was never designed to make money. Also, losses amounted to \$3,500 a week not the \$11,000 charged.

## Satellites for Home TV's?

Nuclear power could be used aboard television satellites to provide enough power to broadcast direct to home-style TV receivers over a large part of the earth, according to a recent study by RCA. Presently planned satellites are designed to beam low-power signals to highly sensitive relay stations on earth, where they could be stepped up to higher power and would be rebroadcast from local TV stations. Under the proposed plan, a transmitter on a satellite could broadcast direct to all home receivers in an area as large as Europe or the United States.

The reactor powering the TV transmitters would also be used to drive an electric propulsion system that would help get the satellite into space and bring it a 22,300-mile-high orbit. At that altitude it would revolve around the earth once daily and could, therefore, be made to remain over one spot. The antenna would of course be kept directed at the earth. Such a satellite, said Dr. Korman of RCA's Advanced Military Systems Office, could be developed for less than \$100 million, which he  
(Continued on page 10)

**Advertising Representatives:** Los Angeles: Harker-Husted-Coughlin, 408 1/2 South Alvarado St., Tel. DUnlirk 7-2328. San Francisco: Harker-Husted-Coughlin, 444 Market St., Tel. Garfield 1-0151. Atlanta: J. Sidney Crane & Associates, 22 Eighth St. N.E., Tel. TRinity 2-6720. Florida: Lu Neff Associates, 15 Castle Harbor Isle, Fort Lauderdale, Fla. United Kingdom: Publishing & Distributing Co., Ltd., Mitre House, 177 Regent St., London, W. 1, England.  
**Foreign Agents:** Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4.  
**Subscription Service** Address form 3579 and correspondence to Radio-Electronics, Subscriber Service, 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.

# Now! Work Over 300 PRACTICAL PROJECTS with these PARTS AT HOME!

## to help You learn ELECTRONICS RADIO - TELEVISION - RADAR

NOW . . . at home in your spare time you can get the very kind of training and subsequent Employment Service you need to get started toward real earnings in one of today's brightest opportunity fields—TELEVISION-RADIO-ELECTRONICS. Now that Electronics is entering so many new fields, here is a chance of a lifetime to prepare to cash in on its remarkable growth.

DeVry Tech's amazingly practical home method enables you to set up your own HOME LABORATORY. You spend minimum time to get maximum knowledge from over 300 practical projects, using the same type of basic equipment used in our modern Chicago and Toronto Training Centers!

### DeVry Tech Provides EVERYTHING YOU NEED . . .

—to help you master TV-ELECTRONICS. In addition to the home laboratory and easy-to-read lessons, you even use HOME MOVIES—an exclusive DeVry Tech series. You watch hidden actions . . . see electrons on the march. Movies help you to learn faster . . . easier . . . better.



### EARN WHILE YOU LEARN

DeVry Tech's practical training helps you toward spare time income servicing Radio and Television sets.

### LABORATORY TRAINING

Full time day and evening training programs in our modern Chicago and Toronto Laboratories are also available. MAIL COUPON TODAY for facts.



**EFFECTIVE EMPLOYMENT SERVICE**  
Get the same Employment Service that has helped so many DeVry Tech graduates get started in this fast-growing field.

"One of North America's Foremost Electronics Training Centers"




Accredited Member of National Home Study Council



Electronics in SPACE TRAVEL

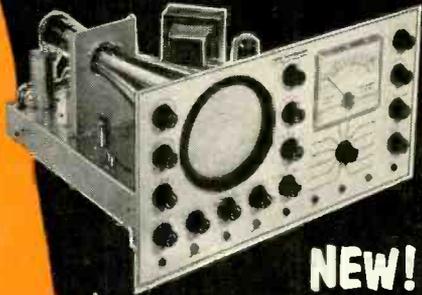**✓ CHECK These Exciting JOB Opportunities:**

- TV-Radio Broadcast Technician
- Color TV Specialist
- Radar Operator • Airline Radio Man
- Missile Electronic Technician
- Laboratory Technician
- Computer Specialist
- Your Own Sales & Service Shop
- ... PLUS MANY OTHERS



**NEW!  
ALL NEW!**

Shown above is the valuable new combination oscilloscope and voltmeter which DeVry Tech men build during their training.



Build and keep this BIG DeVry Engineered TV set—easily converted to U.H.F. (DeVry offers another home training, but without the TV set.)

### MAIL COUPON TODAY!

DeVRY TECHNICAL INSTITUTE  
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-15

Please give me your FREE booklet, "Electronics in Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.

Name \_\_\_\_\_ Age \_\_\_\_\_  
PLEASE PRINT  
Street \_\_\_\_\_ Apt. \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

2045 Canadian residents address: DeVry Tech of Canada, Ltd.  
970 Lawrence Avenue West, Toronto, Ontario

**DeVRY TECHNICAL INSTITUTE**  
CHICAGO 41, ILLINOIS

## ★ TRIPLE TREAT SPECIAL



**YOU GET  
ALL THIS WITH**

## NEW TARZIAN STEREO TAPE OFFER

ONE FULL HOUR  
OF PRE-RECORDED  
4-TRACK STEREO  
MUSICAL ENTERTAINMENT

### Silk Satin and Strings


Jalousie  
Laura  
Falling in Love  
From This Moment On  
Holiday for Strings  
Sleepy Lagoon  
It's All Right With Me  
Stella by Starlight  
Out of My Dreams  
El Choclo  
Blues in The Night  
Jazz Pizzicato

### Gigi

Title Song  
Waltz at Maxim's  
Thank Heaven for Little Girls  
The Parisians  
I Remember It Well  
The Night They Invented Champagne  
Reprise: Gigi
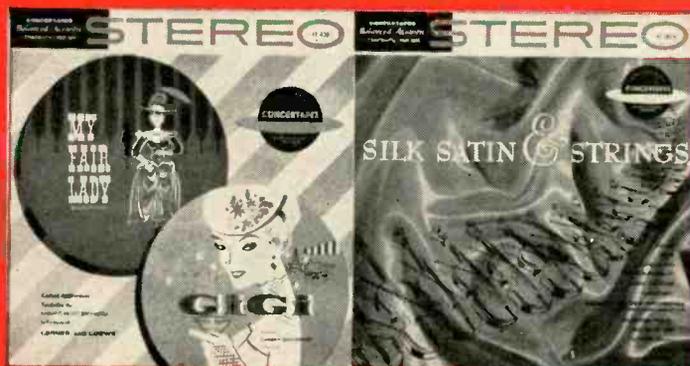
### My Fair Lady

On the Street Where You Live  
I've Grown Accustomed to Her Face  
With a Little Bit of Luck  
I Could Have Danced All Night  
The Rain in Spain  
Wouldn't It Be Lovely  
Show Me



★ Original Broadway arrangements of 13 top tunes from both "Gigi" and "My Fair Lady," re-creating the sparkle of opening night for thirty entertaining minutes

★ PLUS "Silk Satin and Strings," a half-hour of all-time favorites including "Blues in the Night," "Holiday for Strings," and ten more memorable melodies...two current catalog albums (Concertapes No. 4T-4001, \$7.95, and No. 4T-3006, \$6.95) combined on one hour-long Tarzian Tape to give you a \$14.90 value

★ PLUS a full 7-inch reel of blank Tarzian Tape, factory-sealed in protective plastic and quality-guaranteed.

**This entire "Triple Treat" package is now available at leading tape dealers for only the price of two reels of blank Tarzian Tape and \$1.49.**

Here is music for pleasurable listening, imaginatively interpreted by Caesar Giovannini and the Radiant Velvet Orchestra in true stereo sound. It covers the entire range of popular music at its best...from the romantic "Falling in Love With Love" to the toe-tapping tempo of "The Night They Invented Champagne." This is current catalog music, available now at a price far below the retail cost—and combined on one professional-quality Tarzian Tape to provide a full hour of musical entertainment.

As you listen, your ears will detect a wide frequency response and dynamic range; a smoothness and clarity of sound unusual even in high-fidelity stereo tapes. That's when you should unwrap the blank reel of Tarzian Tape. Use this tape to record a special FM program, or several favorite records. We'll bet that the playback will reveal the same depth and realism that you enjoyed on the studio-produced tape.

Hard to believe? That's exactly why we are making this special offer. More surely than anything we can say, *your* ears can prove to you that Tarzian Tape does indeed make possible a new fidelity in sound reproduction, in your home as in the professional studio.

Try it. Visit your favorite tape dealer today and get your "Triple Treat" package from Tarzian.



### SARKES TARZIAN, INC.

World's Leading Manufacturers of TV and FM Tuners • Closed Circuit TV Systems • Broadcast Equipment • Air Trimmers • FM Radios • Magnetic Recording Tape • Semiconductor Devices

**MAGNETIC TAPE DIVISION • BLOOMINGTON, INDIANA**

Export: Ad Aurpema, Inc., N.Y. • In Canada, Cross Canada Electronics, Waterloo, Ont.

# exclusive in PHOTOFACT

the world's finest electronic service data

## famous Howard W. Sams ALIGNMENT SYSTEM and PARTS GUIDE!

speedy shortcuts to simplify servicing...to eliminate guesswork...  
to save you valuable hours each day for greater profits...

### Time-Saving ALIGNMENT SYSTEM

#### OVERALL VIDEO IF RESPONSE CHECK

Connect the negative lead of a 6 volt bias supply to point  $\diamond$ . Posi  
Connect Vert. Amp. of scope thru 47K to point  $\diamond$ . Low side to c

SWEEP GENERATOR FREQUENCY	MARKER GENERATOR FREQUENCY	ADJUST	REMARKS
45.0MC (10MC Swp.)	42.5MC 45.75MC	A5 and Mixer Plate Coil	Adjust for maximum gain and response similar to Fig. 1 w shown.
"	42.5MC 45.0MC 45.75MC	A1, A2, A3	Check for response similar t necessary, retouch A1, A2, proper response.

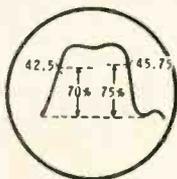


FIG. 1


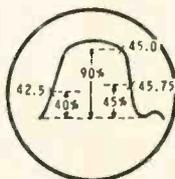


FIG. 2

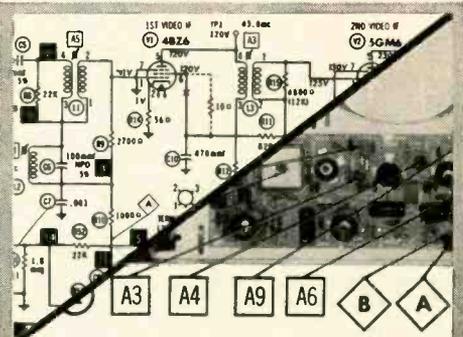

**1.** Complete ALIGNMENT INSTRUCTIONS are presented in an easy-to-follow, standardized form. All procedures have actually been performed and verified in the PHOTOFACT analysis lab. Tells you what to adjust, how to connect equipment, and how to perform the alignment.

**2.** Detailed response curves show you where alignment markers should appear for proper frequency response. Response curves are developed from actual scope measurements made during lab processing. For convenient use, actual frequencies and markers are shown on response curve.

**3.** Test equipment connections (test-points) and adjustment sequences given in the Alignment instructions are clearly coded to the famous Sams Standard Notation Schematic and photos for quick, easy identification.

### Tell-All PARTS GUIDE



#### TRANSFORMERS (SWEEP CI

ITEM No.	USE	REPLACEMENT DATA			
		OLYMPIC PART No.	Merit PART No.	Stancor PART No.	Thor PART No.
T3	Vert. Output Yoke Horiz. 18.4MH (92% Vert. 40MH Rear Cover and Centering Device Horiz. Output	TN-25791-3 CL-3600-7	MDF-92 L	DY-16A L	Y-16
T4		TR-3599-5	HVO-131 *	HO-315 *	FLY

1. Use original rear cover and centering device, yoke damping network if  
2. Drill new mounting holes. 3. Filament require two

\* HORIZONTAL OUTPUT TRANSFORMER CON

ORIGINAL TERMINAL CONNECTIONS	Merit Replacement Connections	Stancor Replacement Connections	Thorston Replacement Connections
0	0	0	4

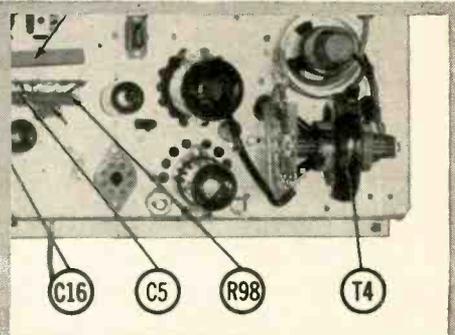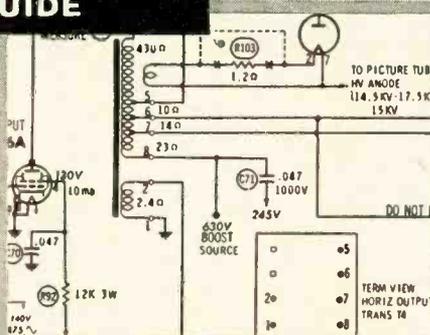

**1.** A complete PARTS GUIDE is available for each model. Parts List item numbers tie in with schematic and photos. Original set manufacturer's part numbers are shown, as well as a choice of replacement part numbers. Parts connection data is given to eliminate guesswork.

**2.** The Standard Notation Schematic identifies components and values, shows terminal numbers and layouts, color codes, and resistance of coil windings—all invaluable helps in localizing trouble quickly.

**3.** All items on Parts List are keyed to and clearly identified on chassis photos and Standard Notation Schematic for easy cross-reference.

The exclusive time-saving Alignment System and tell-all Parts Guide are just two of dozens of great features in PHOTOFACT for fastest, easiest, most profitable servicing.  
See your Sams Distributor for full details on an Easy Buy Library or Standing Order subscription!

**FREE!**

#### BONUS 20-LESSON COURSE

Beginning This Month in PHOTOFACT!

#### SECOND-CLASS RADIOTELEPHONE LICENSE COURSE

Take advantage of this special bonus offer Course! Will help you pass the exam for an FCC License, so you can upgrade your career in electronics and become an expert in communications. Course begins this month (in Photofact Set No. 561) as a bonus to PHOTOFACT subscribers. Be sure your Sams Distributor has your Photofact Standing Order subscription!

**SUBSCRIBE TODAY!**



#### HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc., Dept. 6-A2  
1720 E. 38th St., Indianapolis 6, Ind.

Please enter my subscription to Photofact.

My Distributor is: \_\_\_\_\_

Send FREE Photofact Cumulative Index


Send Details on:  Easy Buy Plan  "Peet" Program

Shop Name \_\_\_\_\_

Attn.: \_\_\_\_\_

Address \_\_\_\_\_

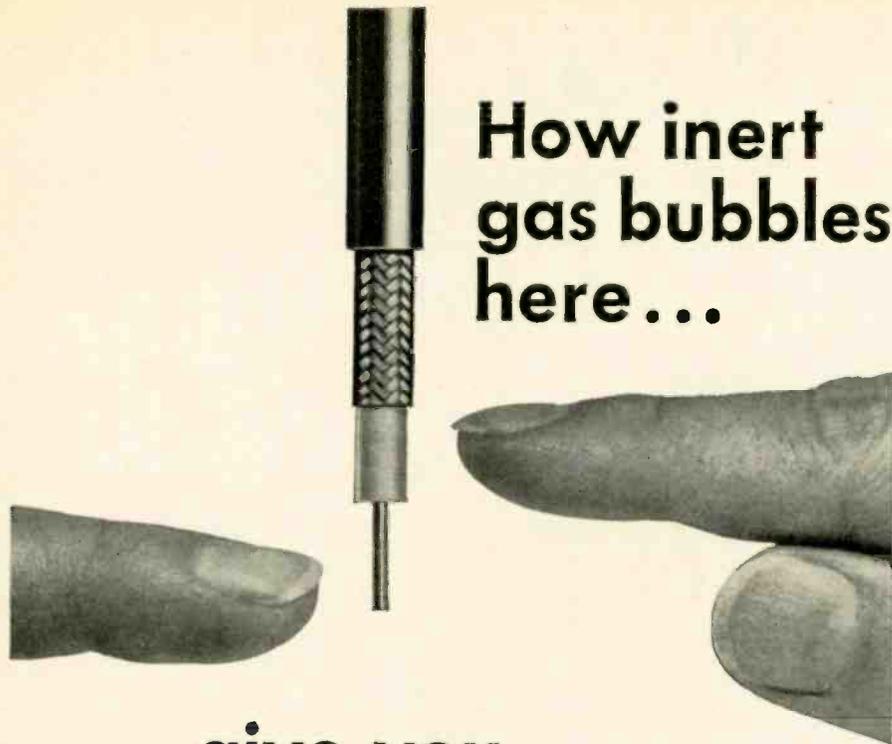City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



## How inert gas bubbles here...

# ...give you up to 35% greater signal strength here

When you use Amphenol Polyfoam® coaxial cable, you consistently increase signal strength up to 35% over ordinarily used RG-/U cable. The secret? It's in the new Polyfoam dielectric material—a cellular polyethylene that uses inert gas as the expanding agent to form tiny, completely enclosed cells in the polyethylene. It gives you a dielectric constant of 1.50 as compared with 2.26 for solid polyethylene—for lower attenuation and minimum capacitance.

That's not all! With Polyfoam cable, you still utilize minimum diameters. Matter of fact, Polyfoam cable actually weighs less than standard RG cables.

You're ahead all these ways—and at surprisingly low additional cost—when you use genuine Amphenol Polyfoam for your coaxial cable requirements. See your authorized Amphenol Distributor. If you don't know who he is, write to Amphenol Distributor Division, 2875 S. 25th Avenue, Broadview, Illinois, or call COLUMBUS 1-2020.

**AMPHENOL** Distributor Division / Amphenol-Borg Electronics Corporation

(Continued from page 6)  
called "a modest sum when compared with the multibillion dollar space program now under way."

### New Flat Picture Tube?

According to a report in *TV Digest*, the Navy is expected to issue—some time early next spring—a progress report on a flat nonvacuum-tube electroluminescent panel that can achieve better definition and brightness than a television picture tube. The new display panel, it is stated, could be adapted to picture-on-the-wall TV.

The new display device is being developed for the Navy by Lear, Inc. It is intended for use as an aircraft readout display that can be mounted on the windshield of the plane. The most important weakness uncovered so far, from the standpoint of the TV viewer, is that the new picture-on-the-wall "tube" alone would cost far more than the price of a complete present-day TV receiver.

### IRE-AIEE to Unite?

The Boards of Directors of both the Institute of Radio Engineers and the American Institute of Electrical Engineers have voted unanimously to consider consolidation. The action took the form of resolutions stating in effect that the directors of both societies "have deemed it advisable to move actively toward consolidation of the activities of both organizations" and to appoint members of a joint committee to study the problems involved and report back. The committee consists of four members of each group.

The united society would be the largest engineering group in the world. IRE now has 91,000 members, including 17,000 students. Membership of AIEE is 66,000, including 11,000 students. There is some overlapping; 6,000 engineers are members of both societies.

Sentiment in both societies was pretty well summed up by Patrick E. Haggerty, president-elect of IRE, who said, "There are not two kinds of electrons; why should there be two societies to deal with that very same electron?"

### Scientists Learn Why Worm Turns

The earth's magnetic field dictates the way the proverbial worm turns, according to Dr. Frank A. Brown of Northwestern University. He made this report at a conference on high magnetic fields sponsored by the Air Force office of scientific research at MIT.

In experiments with the flat-worm *Dugesia*, the worms were oriented in the earth's magnetic field and a barrier to their motion set up. In the winter months, Dr. Brown observed, the worms turned to the right in the fortnight of the full moon and to the left in the fortnight of the new moon. In the spring they turned in the opposite direction—to

(Continued on page 16)

# 365 Days From Now Your Future In Electronics Can Be Assured

*Join the Men Who Have Moved UP Through Cleveland Institute's Accredited Training Program*

What You Already Know About Electronics . . . Radio . . . Television PLUS additional knowledge in modern electronic applications . . . advanced theory . . . slide rule math—will qualify you for the thousands of unfilled jobs open to advanced technicians and engineering assistants.



Men who are trained in electronics are the men who can qualify successfully for a First-class FCC License (Commercial) with a radar endorsement; and men who hold this license are in demand for better jobs TODAY . . . and will be in demand TOMORROW.


*Carl E. Smith, E.E.  
Chairman of the Board,  
Cleveland Institute*

Respond to Your Natural Desire to Learn More About . . .

- Basic Math • Color TV • Industrial Electronics • Radio Telemetry • A.C. Circuit Analysis • Radar • Advanced Measuring Techniques • Instrumentation • Pulse Circuitry • Automation • Computers • Semiconductors

. . . all covered in the Master Course in Electronics.

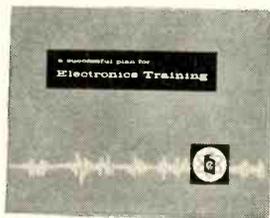Resolve Now to Improve Your Future in the Next 12 Months. Start Today by Sending for our free booklet . . .



"A Successful Plan for Electronics Training". See for Yourself How Cleveland Institute prepares you to successfully pass the FCC Commercial Examination and assures you of a more profitable future in electronics.



### Yours To Keep—Free!

This Handy Pocket Guide. Conversion factors, formulas, tables and color codes at your fingertips. Yours without obligation, simply for responding NOW to this opportunity to improve your future.

## Cleveland Institute of Electronics



1776 E. 17th St., Desk RE-61 B, Cleveland 14, Ohio

Accredited by the Accrediting Commission of the National Home Study Council (An Accrediting Commission Approved by the U. S. Office of Education.)



Your Passport to a Brighter Future . . . Your FCC Commercial License . . . or your money back.

Completion of the Master Course will prepare you for a First-Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination for this license after successfully completing the Master Course, you will receive a full refund of all tuition payments. This guarantee is valid for the entire duration of your enrollment agreement.

I want to know more about your electronics home study training program. Please send me your free booklet described above plus your handy pocket Electronics Data Guide. I understand there is no obligation. I have had training or experience in electronics as indicated.

### Mail Coupon To

Cleveland Institute of Electronics  
1776 E. 17th St., Desk RE-61 B, Cleveland 14, Ohio

- |   |   |
|---|---|
| <input type="checkbox"/> Military           | <input type="checkbox"/> Amateur Radio      |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Broadcasting       |
| <input type="checkbox"/> Manufacturing      | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Communications     | <input type="checkbox"/> Other              |

I'm now working in \_\_\_\_\_

I want to know about the following area of electronics \_\_\_\_\_

(please print)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# AUTHENTIC! COMPLETE! MODERN!



## DOWN-TO-EARTH TRAINING

THAT HELPS YOU REPAIR ANY TV OR RADIO SET EVER MADE!



Let these two famous training books teach you to handle all types of AM, FM and TV service jobs by approved *professional* methods—and watch your efficiency and earnings soar! Almost 1500 pages and over 800 clear pictures and diagrams explain EVERY troubleshooting and repair operation as clearly as A-B-C. No needless mathematics. No involved theory. You get straight-from-the-shoulder training of the type that teaches you to do the best work in the shortest time!

**SAVE \$2.00!**

Make your service library complete! Get both these famous Ghirardi books at a saving of \$2.00 under the regular price. See MONEY-SAVING COMBINATION OFFER in coupon.

### 1 Complete Training in MODERN CIRCUITS

You can repair ANY radio, TV or other electronic equipment lots easier, faster and better when you're fully familiar with its circuits and know just why and how each one works . . . and that's exactly the kind of specialized training you get in Ghirardi's 669-page Radio & TV CIRCUITRY AND OPERATION training guide. It gives a

complete understanding of basic modern circuits, then shows what troubles to look for and how to eliminate needless testing and guesswork in servicing them. Throughout, it gives you the above average training that takes the headaches out of troubleshooting and fits you for the best-paid servicing jobs. 417 clear illustrations. Price \$9.00 separately.

### 2 Complete guide to PROFESSIONAL SERVICE METHODS

Radio & TV TROUBLESHOOTING AND REPAIR is a complete 822-page guide to *professional* service methods . . . the kind that help you handle jobs faster, more profitably. For beginners, this giant book with its 417 clear illustrations is an easily understood course in locating troubles fast and fixing them *right*. For experienced servicemen, it is an ideal way to develop

better methods and shortcuts; or to find fast answers to problems. You learn troubleshooting of all types from "static" tests to dynamic signal tracing methods. Step-by-step charts demonstrate exactly what to look for. A big television section is a down-to-earth guide to all TV service procedures. Price \$10.00 separately.

## LEARN ELECTRIC MOTOR REPAIR!



Handle ANY job from minor repairs to complete rewinding

It pays to train for something different! ELECTRIC MOTOR REPAIR is a complete guide that helps you cash in on this growing field. Shows how to handle all repair

jobs (including complete rewinding) on practically ANY AC or DC motor or generator in common use — from fractional horsepower to giant industrial motors. Special duo-spiral binding brings text and related how-to-

do-it diagrams side by side so that you learn fast, easily and right. It's the ideal book whether you want to train for a good-pay motor repair job or simply want to fix motors as a sideline or hobby! 560 pages; over 900 pictures. Price \$9.25.

## SHORT CUTS TO TV REPAIRS!



Eliminate needless testing!

Just turn the dial of the pocket-size PIX-O-FIX TROUBLE FINDER GUIDE! When the picture in the PIX-O-FIX window matches the image on the TV screen—presto!—you've got your clue. PIX-O-FIX shows the likely causes of the trouble—indicates the receiver section involved—then gives clear repair instructions. Two PIX-O-FIX units Nos. 1 and 2 cover 48 different TV troubles. Together, they're a comprehensive guide to quick "picture analysis" servicing of any TV. Price only \$3.95 for the two.

## CASH IN ON APPLIANCE REPAIRS!




**ONLY \$6.75 FOR THE COMPLETE TRAINING**

Save on repair bills! Earn in spare time!

When you consider the prices charged for electrical appliance repairs these days you'll quickly recognize the tremendous money-making opportunities open to trained men in this literally tremendous field!

At only a small fraction of prices charged for mail-order training courses, this 370-page, low cost book teaches you step-by-step how to repair practically any home electrical appliance. Troubleshooting charts help you locate faults quickly. Book even explains how to make your own inexpensive test tools and trains you in modern appliance refinishing methods. Includes specific service details on: Std. & automatic washers; ironers; toasters; ranges; cleaners; mixers; hotplates; razors; clocks; motors; water heaters; bottle warmers; waffle irons, and many more. Price \$6.75.
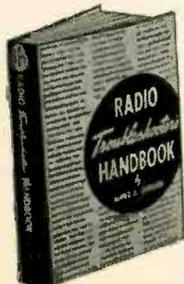
## FIX OLD RADIOS FAST! Without Useless Testing!



Only guide of its kind still in print

Just look up the how-to-do-it data on that old radio!

Four times out of 5, this giant, 3½-pound, 744-page Ghirardi RADIO TROUBLESHOOTER'S HANDBOOK tells what is likely to be causing the trouble . . . shows how to fix it. No useless testing. Covers every model made by 202 mfrs. from 1925 to 1942. The only guide of its kind still in

print. Cuts service time in half! Includes common trouble symptoms and their remedies for over 4,800 models of old home, auto radios and record changers. Airline, Apex, Arvin, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G-E, Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Spartan, Stromberg and dozens more. Price \$10.00.

## DIGITAL COUNTERS & COMPUTERS

A good working knowledge of electronic computers may not be as complicated as you think—and this new 248-page book proves it! Written for technicians, students and experimenters it explains computer theory, design, application and output interpretation in readily understandable terms. Includes details on number systems; binary counters; readout indicators and special counter tubes; decade counters; storage devices; logic circuits; computer applications; digital-to-analog and analog-to-digital conversion and many others. By explaining basic circuit configurations, DIGITAL COUNTERS AND COMPUTERS by E. Bukstein quickly breaks down computer "mysteries" and starts you on a clear understanding of one of the "hottest" subjects in Electronics today. Fully illustrated. Price \$8.75.



# SPECIALIZED TRAINING GUIDES!


*Complete, Easy-to-Understand!*

Each of these famous books is the equivalent of a complete training course in its subject—written for fast, easy understanding—and priced far less than you might ordinarily expect to pay for such remarkably complete

and authentic training. Hundreds of thousands of copies have been sold for home study purposes—because they are so clearly written and so remarkably complete.

## PRACTICAL TV SERVICING

JUST OUT!

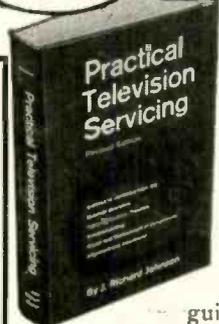

Most complete, genuinely helpful television training in 10 years!

Written by a man who has actually done the work himself and knows how to make things clear, this big, fully revised book is an up-to-the-minute


guide to modern television servicing. Saves experienced men loads of time! Is a complete training course for beginners!

### The "Cream" of Modern Service Methods —Clearly Explained

First, PRACTICAL TELEVISION SERVICING by J. R. Johnson acquaints you with receiver layouts, sections and construction. A big *troubleshooting section* teaches you to pinpoint troubles in a minimum of time. *Case histories* on specific service calls demonstrate service procedures as clearly as A-B-C. Over 40 pages describe *critical alignment procedures* including connecting and adjusting instruments. *Common faults* in TV circuits are explained section by section. A chapter on *color television* principles brings you up to date in this field.

448 pages and over 325 illustrations help you handle any job by approved professional methods—helps you say "goodbye" to guesswork on even the toughest jobs! Price \$7.95.

## Guide to ELECTRONIC TEST PROCEDURES!

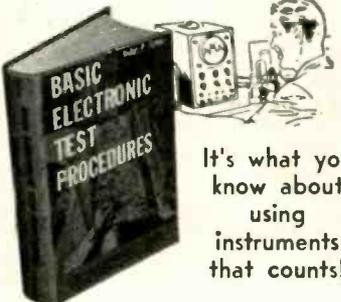


It's what you know about using instruments that counts!

Rufus P. Turner's 316-page BASIC ELECTRONIC TEST PROCEDURES manual with more than 190 illustrations, pattern photos and procedure diagrams teaches you to test any circuit, equipment or component in a fraction of the usual time. It is a complete course in professional testing techniques! For instance, you learn to check for distortion by the 'scope, rejection filter, harmonic distortion meter, wave analyzer or oscillator methods. You learn to measure resistance with a current meter, a voltmeter, voltmeter, ohmmeter, or via the bridge method—and so on.

Includes Current checks; measuring Power, Capacitance, Resistance, AF, RF Phase, Distortion & Modulation; testing Tubes and Semiconductors; testing Amplifiers; checking Sensitivity, RF Gain, Fidelity, AVC Voltage, etc. Even includes industrial electronic test procedures. Price \$8.50.
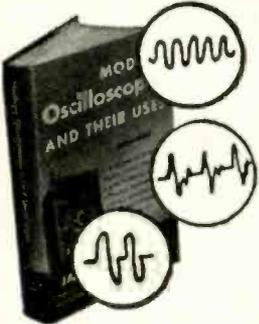
## Here's What You Need to Know About 'SCOPES!




'Scope experts get the big pay jobs!

Men who really know how to use oscilloscopes locate troubles faster, repair them more accurately—and this famous manual teaches you the methods they use. In short, MODERN OSCILLOSCOPES AND THEIR USES get right down to earth in bringing you the complete "know how" of using the handiest, most versatile instrument of them all!

Particular attention is paid to

realignment procedures. Every detail of testing is explained from connecting the 'scope and setting its controls to adjusting components in the chassis being tested. Illustrated instructions teach you to analyze patterns. Even includes data on quantitative measurements (as used in color TV servicing) and use of 'scopes in industrial electronics and atomic work. 370 illustrations. Price \$8.75.
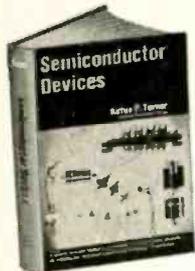
## NEW! Practical guide to SEMICONDUCTORS



- Diodes • Transistors
- Thermistors
- Varistors
- Rectifiers
- Photo cells, etc.

### PLUS

use, test and measurement data

This down-to-earth, 278-page book gives you a good working knowledge of all commonly used semiconductors. It answers your questions. It makes semiconductor construction, circuit applications and use understandable without a lot of highly technical training. In short, Rufus P. Turner's SEMICONDUCTOR DEVICES has been specifically written for technicians, servicemen and experimenters who now find these tiny devices so important in their work. Standard and special types are explained. Over 250 illustrations demonstrate semiconductor circuitry, operational and construction features. Semiconductor test and measurement methods are described in detail. Price \$7.50. Use coupon.

**USE COUPON FOR 10 DAY FREE TRIAL**

Dept. RE-12, Technical Division,  
HOLT, RINEHART & WINSTON, Inc.,  
383 Madison Ave., New York 17, N.Y.

No. 623900

Send books checked for 10 DAY FREE EXAMINATION at prices indicated plus postage. SAVE! Send cash with order and we pay postage. Same 10 day return privilege with money promptly refunded.

#### MONEY-SAVING SERVICE TRAINING COMBINATION

Radio & TV Circuitry & Operation; and Radio & TV Troubleshooting & Repair, only \$17 for both books. (Regular price \$19 separately—you save \$2.00) #709006.

#### Check here to order Individual Books

- |   |        |  |      |
|---|--------|--|------|
| <input type="checkbox"/> Radio & TV Circuitry and Operation (#708214).....    | 5 9.00 | <input type="checkbox"/> Digital Counters & Computers (#708131).....     | 8.75 |
| <input type="checkbox"/> Radio & TV Troubleshooting and Repair (#708578)..... | 10.00  | <input type="checkbox"/> PIX-O-FIX Trouble Finder Guides (#708412)       | 3.95 |
| <input type="checkbox"/> Electrical Appliance Service Manual (#708172)        | 6.75   | <input type="checkbox"/> Basic Electronic Test Procedures (#708933)..... | 8.50 |
| <input type="checkbox"/> Radio Troubleshooters' Handbook (#708297)            | 10.00  | <input type="checkbox"/> Modern Oscilloscopes & Their Uses (#708818)     | 8.75 |
| <input type="checkbox"/> Electric Motor Repair (#708735).....                 | 9.25   | <input type="checkbox"/> Semiconductor Devices (#709003).....            | 7.50 |
|   |        | <input type="checkbox"/> Practical Television Servicing (#705657).....   | 7.95 |

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

(OUTSIDE USA — Add 50¢ to each book. Cash with order, but money refunded if books are returned in 10 days.)

(Above offers expire Oct. 15, 1962)

Two outstanding products by the HIDDEN

500\*

who plan for your future:



**DIFILM<sup>®</sup> BLACK BEAUTY<sup>®</sup> CAPACITORS**  
molded tubular



**DIFILM<sup>®</sup> ORANGE DROP<sup>®</sup> CAPACITORS**  
dipped tubular

**TWO GREAT TUBULARS . . . TAKE YOUR CHOICE!**

(± 10% Capacitance Tolerance is standard at no extra cost)

- Sprague Difilm Capacitors can't be beat! Dual-dielectric construction combines the best features of both Mylar<sup>®</sup> polyester film and special capacitor tissue. And for additional reliability, Difilm capacitors are impregnated with Sprague's HCX<sup>®</sup>, a solid impregnant which produces a rock-hard capacitor section—there's no wax to drip, no oil to leak!
- **BLACK BEAUTY Molded Tubulars** are actually low-cost versions of the famous Sprague high-reliability capacitors used in modern military missiles. They're engineered to withstand 105°C (221°F) temperatures . . . even in the most humid climates! And their tough, molded phenolic cases can't be damaged in handling or soldering.
- **ORANGE DROP Dipped Tubulars** are the perfect replacement for radial-lead capacitors now used by leading manufacturers of TV sets. Leads are crimped for neat mounting on printed wiring boards. Extremely small in size, they'll fit anywhere, work anywhere. And they're double-dipped in epoxy resin for extra protection against moisture.

\* The "Hidden 500" are Sprague's 500 experienced researchers who staff the largest research organization in the electronic component industry and who back up the efforts of some 7,000 Sprague employees working in 14 manufacturing operations—four at North Adams, Mass.; Bennington and Barre, Vt.; Concord and Nashua, N. H.; Lansing, N. C.; Grafton, Wis.; Visalia, Calif.; two at Ponce, Puerto Rico; and Milan, Italy.



WORLD'S LARGEST CAPACITOR MANUFACTURER

# The Same School That Originated The RTS BUSINESS PLAN

**NOW**  
Proudly  
Presents...

## A SPECIAL COMPACT COURSE COVERING ALL THREE PHASES OF **ELECTRONICS**

The Entire Course Is Made  
Up Of The Following:


- 35 LESSONS COVERING BASIC AND INTERMEDIATE ELECTRONICS
- 9 EQUIPMENT KITS COMPLETE WITH TUBES AND BATTERIES
- SOLDERING IRON
- 25 LESSONS COVERING THESE ADVANCED ELECTRONIC SUBJECTS:

Thyratron Tubes • Semiconductors •  
Electronic Symbols and Drawings •  
Voltage Regulators • Electronic  
Timers • Control Systems • X-Rays •  
Photoelectric Devices • Dielectric  
Heating • Geiger Counters • Pulse  
Circuitry • Clippers and Limiters •  
Multivibrators • Electronic Counters •  
Radar • Magnetic Amplifiers • Analog  
Computers • DC Amplifiers • Digital  
Computers • Storage Systems • Input  
and Output Devices • Servomechanisms •  
Telemetering

- 60 EXAMINATIONS
- UNLIMITED CONSULTATION SERVICE
- KIT MANUALS
- DIPLOMA UPON GRADUATION

AND MUCH MORE...

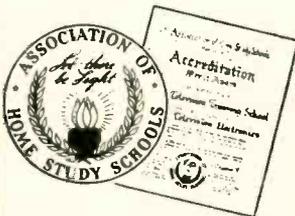RTS' Membership in  
The Association of  
Home Study Schools  
is your assurance of  
Reliability, Integrity and  
Quality of Training.



RTS ELECTRONICS DIVISION  
815 E. ROSECRANS AVENUE  
LOS ANGELES 59, CALIFORNIA

Est. 1922



L 2018

**BASIC • INTERMEDIATE • ADVANCED  
DESIGNED FOR THE BUSY MAN OF TODAY**

This is MODERN training for the MODERN man. You'll find no "horse and buggy" methods here. Every page of this streamlined course is devoted to important Electronics principles and practical projects. You'll be amazed how fast you grasp Electronics the RTS way. RTS has combined modern THEORY and PRACTICE to make this the finest training program of its kind available!

**SATISFIES NOVICE, TECHNICIAN OR HOBBYIST**

Whether you're new to Electronics or an old "pro," chances are you'll find this to be the ideal course for you. The novice will appreciate the completeness of the training. It starts with the most basic considerations, covering each important point thoroughly, yet concisely. The technician will enjoy the practical review of fundamentals and profit from the 25 advanced subjects covered.

**RTS GIVES YOU "TOP MILEAGE" FOR YOUR TRAINING DOLLAR**

The price quoted below buys EVERYTHING — there are no extras to pay for. RTS has gone "all out" to give you the best training value in America. Why pay hundreds of dollars for training such as we offer when it's available for this LOW PRICE? If you can find a better training bargain... BUY IT!

**CAN BE COMPLETED IN MONTHS INSTEAD OF YEARS**

Some students will complete this course with "Jet-Like" speed but we allow up to two years if your circumstances require it. You study at your own rate. You are ENCOURAGED but not pushed. You'll find the lessons professionally written but easy to understand. LET US SEND YOU ONE OF THESE LESSONS ALONG WITH YOUR CAREER BOOKLET SO YOU CAN SEE FOR YOURSELF. NO OBLIGATION!

COMPLETE  
COST...  
INCLUDES ALL KITS,  
TUBES, BATTERIES, ETC.  
**\$125.00\***

\* TERMS ALSO AVAILABLE  
AS LITTLE AS

\$500 DOWN \$500 PER MONTH

**SAVE TIME — SEND  
\$5.00 WITH COUPON**

YOUR FIRST LESSONS AND  
KIT WILL BE RUSHED TO YOU  
THE SAME DAY THEY ARE RECEIVED!

**Rush  
Coupon**

**NO  
SALESMAN  
WILL  
CALL!**

**DON'T LOSE OUT — FIND OUT!**

RTS ELECTRONICS DIVISION, Dept. RE-12

815 E. ROSECRANS AVENUE LOS ANGELES 59, CALIFORNIA

Rush me full information by return mail. (Please Print)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**ENROLL ME NOW**  **SEND MORE FACTS**

# COLOR CODED NUTDRIVER SETS

no fumbling...  
you reach for  
the right one  
every time!



No. 17  
HANDY  
BENCH STAND

- 7 Most-used sizes —  $\frac{3}{16}$ " thru  $\frac{3}{8}$ "
- High carbon steel, polished and plated
- Precision fit case-hardened sockets
- Shockproof plastic handles (UL)
- Large, readable size indexes



No. 127  
SPACE-SAVING  
WALL RACK (Lockable)

OTHER SETS, TOO: hollow-shaft or mixed  
PLUS A FULL RANGE OF SEPARATE NUTDRIVERS:  
3/32" thru 3/4" — Regular, Stubby, Extra-long,  
Midget (Pocket clip)  
available through leading electronic distributors

XCELITE, INC. — ORCHARD PARK, N. Y.  
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

## XCELITE

### HAND TOOLS

Quality screwdrivers, nutdrivers, pliers,  
wrenches, service kits, and special purpose tools.

(Continued from page 10)

the right in the 2 weeks of the new moon and to the left during the full-moon period. In summer they faced to the right on new and full moons and to the left at each quarter. "The kinds of magnetic response described for Dugesia appear not to be specific for this worm but simply to represent a general property of living things," Dr. Brown, who has experimented with other worms, snails and the one-celled paramecium, reported.

Considerable skepticism was expressed when Dr. Brown made his report. The skeptics were, however, challenged by Dr. Otto Schmidt, chairman of the session at which the paper was presented: "Either explain it or explain it away."

#### Calendar of Events

IRE, AIEE, ASQC and EIA Symposium on Reliability and Quality Control, Jan. 9-11, Statler Hilton Hotel, Washington, D. C.

ERA Annual Convention, Jan. 23-27, Hollywood Beach Hotel, Fla.

IRE Winter Convention on Military Electronics, Feb. 7-9, Ambassador Hotel, Los Angeles, Calif.

Pacific Electronic Trade Show, Feb. 9-11, Shrine Exposition Hall, Los Angeles, Calif.

IRE, AIEE International Solid State Circuits Conference, Feb. 14-16, Sheraton Hotel and University of Pennsylvania, Philadelphia, Pa.

International Exhibition of Electronic Components, Feb. 16-20, Parc des Expositions, Paris, France.

#### Peter Jensen Passes

The co-inventor of our present electrodynamic loudspeaker and originator of the line of Jensen speakers died Oct. 25, 1961, aged 75.

Jensen was one of the earliest of the electronic pioneers and is one



of the contenders for the title of inventor of wireless telephony. Working with Valdemar Poulsen (inventor of magnetic recording and the Poulsen arc), he transmitted voice over the Poulsen wireless equipment in the early 1900's. Staying up every night to play phonograph records for radio operators on ships at sea, he became unquestionably the world's first disc jockey.

He came to the United States in 1909 to install wireless equipment for Poulsen Laboratories. Remaining to become an American citizen, he worked with another engineer, Edwin L. Pridham to develop what became the Magnavox dynamic speaker. Later he went to Chicago and began to make speakers under the Jensen name.

When World War II broke out, Jensen resigned from his own company and took a low-salaried post with the War Production Board, obtaining sound equipment for the Armed Forces. After the war he founded Jensen Industries and began manufacturing phonograph needles.

His native Denmark recognized his contributions to electronics by making him a knight and hanging a plaque at his birth place.

Jensen Industries, now making phonograph cartridges and accessories as well as needles, is being carried on by his son Karl.

#### How Much Dc Restoration?

How far should dc restoration go in modern TV receivers is a question that has been bothering a standards committee of the Electronic Industries Association, reports *Television Digest*. Dc restoration—maintaining the background level—once universal in TV receivers, has been almost universally omitted during the past several years. While it is almost necessary to give true blacks and whites, TV viewers have grown accustomed to a picture in various shades of gray. Now several manufacturers have restored it, and others plan to do so in new lines (see page 50 for more on this). The viewer now often finds that his new "high-fidelity" set gives him more trouble—the brightness and contrast controls may have to be readjusted when moving from one station to another.

The black-level committee is studying a possible recommendation for the stabilization of the dc levels. Present findings are that from 30% to 50% of the dc level can be restored without causing too many tuning complications for the user, but that 50% to 70% (full black level) would give a superior picture.

#### First PA System Found

A loudspeaker setup roughly 2,000 years old has been found in the ruins of a Roman theater at Nora in Sardinia. The system consisted of a number of earthenware "acoustic vases," the best descriptive terms that could be applied to them by the technical writers of the time. The so-called "vases" were each about 5 feet long and open at both ends. They were tapered slightly and had a maximum circumference of 3½ feet. A number of them were placed horizontally in niches cut in the low wall that formed the front of the raised stage. Thus they acted as megaphones, amplifying the voices of the actors and directing them toward the audience.

These "vases" had been mentioned by an early writer on acoustics, but none had ever before been discovered. Apparently the wealthier theaters used bronze, which was not able to stand the ravages of time as well as the low-cost jobs employed by the little theater in Sardinia. END

# F.C.C. COMMERCIAL OPERATOR F.C.C. LICENSE

## Training... for Jobs in Electronics

### F. C. C. LICENSE — THE KEY TO BETTER JOBS

An F. C. C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

### WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by this license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate certain radiotelephone equipment but not commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of commercial radiotelephone equipment including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available. Many companies which employ industrial electronics technicians require this license.

### GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS** F. C. C. license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F. C. C. license.

### CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way, you are trained quickly and well. Write, or mail the coupon below, to any division of Grantham School of Electronics. Our free booklet will be sent to you immediately.

### HERE'S PROOF...

that Grantham students prepare for F. C. C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
James C. Bailey, 217 Behrends Ave., Juneau, Alaska.....	1st	12
Edward R. Barber, 907 S. Winnifred, Tacoma, Wash.....	1st	20
M. A. Dill, Jr., 20 Cherry St., Gardiner, Maine.....	1st	12
Bernhard G. Fokken, Route 2, Canby, Minn.....	1st	12
Kenneth F. Foltz, Broad St., Middletown, Md.....	1st	12
James C. Greer, Mound City, Kansas.....	1st	12
Thomas J. Hoof, 216 S. Franklin St., Allentown, Pa.....	1st	22
Clyde C. Morse, 7505 Sharronlee Dr., Mentor, Ohio.....	1st	12
Louis W. Pavak, 838 Page St., Berkeley 10, Calif.....	1st	16
Wayne Winsauer, 2009 B St., Bellingham, Wash.....	1st	12

### FOUR SCHOOLS TO SERVE YOU

To better serve our many students throughout the entire country, Grantham School of Electronics maintains four Divisions—located in Hollywood, California; Kansas City, Mo.; Seattle, Wash.; and Washington, D.C. Grantham offers rapid courses in F. C. C. license preparation, either by home study or in resident classes.

Get your First Class Commercial F. C. C. License in 12 weeks by training at

# Grantham School OF ELECTRONICS

HOLLYWOOD  
CALIF.

1505 N. Western Ave.  
Hollywood 27, Calif.  
(Phone: HO 7-7727)

SEATTLE  
WASH.

408 Marion Street  
Seattle 4, Wash.  
(Phone: MA 2-7227)

KANSAS CITY  
MO.

3123 Gillham Road  
Kansas City 9, Mo.  
(Phone: JE 1-6320)

WASHINGTON  
D. C.

821-19th Street, N. W.  
Washington 6, D. C.  
(Phone: ST 3-3614)

for **FREE** Booklet **CLIP COUPON** and mail  
in envelope or paste on postal card.



To: **GRANTHAM SCHOOL OF ELECTRONICS**

1505 N. Western • 408 Marion • 3123 Gillham Rd. • 821-19th, NW  
Hollywood • Seattle • Kansas City • Washington

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

I am interested in:  Home Study,  Resident Classes 24-A

MAIL COUPON NOW

# VERY BIG ON RESPONSE

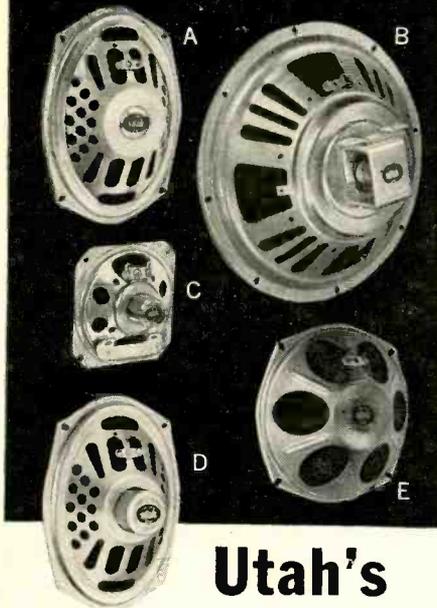

## Utah's famous micro-gap replacement SPEAKERS

Better response — better sound reproduction than original equipment! Better customer response, too, when you install Utah Micro-Gap replacement speakers. Single-packed in custom-fitted cartons. Illustrated above:

**A** SP69NF 6x9" Oval Inverted Auto Speaker **B** SP12J 12" Round Speaker **C** SP4A 4" Square Outdoor Speaker **D** SP69G 6x9" Oval Auto Speaker **E** SP8NF 7½" Inverted Pin Cushion Speaker.

Write for illustrated literature



## Correspondence



### LET ME CORRECT MYSELF

Dear Editor:

In my "Don't be Afraid of Color TV" article in the November 1961 issue I made a howler! You do *not* run the contrast control all the way down on the older color TV sets! If you do, you won't have a picture.

This statement *does* apply to the later RCA models such as the CTC9, CTC10 and CTC11, and the Admiral 25A6, 25B6, but not to the older CTC4 and similar chassis. JACK DARR

### MOUNTAINS OUT OF MOLEHILLS

Dear Editor:

I am surprised that Mr. Crowhurst, in his article "Does FM Stereo Follow Its On Theory?" in the October 1961 issue can make such a complicated thing out of the relatively simple Zenith time-switching approach to stereo multiplex. He spends a whole column explaining what a poor approximation a sine wave is for a square wave, a fact which has no relation to the theory in question. He fails to comment on the very strong resemblance between Fig. 1, in which a square wave jumps between the left and right signals, and Fig. 4, in which a sine wave jumps between the left and right signals. Yet this close resemblance is the key to the Zenith system. If you take a waveform such as Fig. 1 (which can be considered the output of a time-switching device) and filter out all the harmonics of 38 kc above the first, the resulting waveform will be almost identical to Fig. 4 (his Fig. 4 represents the signal desired for transmission). Adding a small amount of L + R to the resulting waveform to compensate for the fact that the first-harmonic component of a square wave has a greater peak-to-peak amplitude than the square wave itself (giving an apparent increase in L - R subcarrier) makes the conversion from Fig. 1 to Fig. 4 mathematically perfect. This is the complete mathematical explanation of the Zenith system, and a very similar discussion can explain receiver operation using a time-switching function. I do not find this approach at all hard to understand or visualize.

Ann Arbor, Mich. JAMES A. SPROWL

### THE AUTHOR REPLIES

Dear Editor:

After reading Mr. Sprowl's letter twice, I am still not certain whether he understands the confusion that the mathematical explanation to which he refers has caused. What he says is quite

correct, as anyone who has learned Fourier analysis knows. But on the basis of this, I have found several engineers, working on adapter design, actually putting in  $2/\pi$  compensation, then finding separation lacking and putting in further compensation which was essentially compensating for the fact that the  $2/\pi$  correction wasn't needed in the first place.

If the adapter circuit uses square-wave type switching—as some do—it also needs  $2/\pi$  compensation, as at the transmitter when this method of modulation is used. But the use at the adapter is *not because it was used at the transmitter*. With the specified form of transmitted signal, each method is independent of the other. If the adapter circuit does not use square-wave switching, or equivalent, it doesn't need  $2/\pi$  compensation.


If Mr. Sprowl understands this, I agree with him it is not difficult. But as several engineers apparently did not understand this, I concluded it must be difficult to some and needed explaining. From experience, I have found that people who protest something I explained rather carefully was not that difficult, later come to me and tell me they have discovered the difficulty and that my explanation was quite right. It may be Mr. Sprowl has still not seen the difficulty. NORMAN H. CROWHURST  
Audio Design Service  
Bayside, N.Y.

### IGNITION-SYSTEM NOTE

Dear Editor:

It might be easier to build an electronic ignition system for your car (April 1961, page 90) by using a phase inverter transistor before the power transistor to reduce the contact point current, and use the distributors that are now in use, one that grounds the contact. The basic circuit is shown here (Fig. 1), but check with Bosch Co. of Germany as they have had an ignition system using transistors for quite a while.

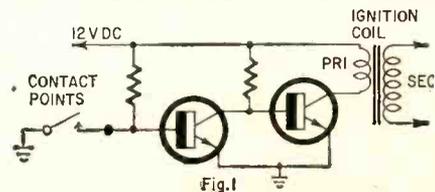Another possible circuit that would be compatible with present distributors is shown in Fig. 2. It requires a bias voltage other than the battery in the car but could be added to a car without





## Special Training Equipment Included

Pick the field of your choice—and train at home with the leader—NRI. In addition to Industrial Electronics and FCC License training explained at the right, NRI offers comprehensive courses in Radio-TV Servicing and Radio-TV Communications. Except for the FCC course, all NRI courses include—at no extra cost—special training equipment for actual practice at home, building circuits and working experiments. Makes theory you learn come to life in an interesting, easy-to-grasp manner.


## Multiplexing, FM Stereo Broadcasting Included

NRI training keeps up with the times. New, additional profit opportunities exist for the Technician who understands the latest technical advances. Course material now covers FM Stereo Broadcasting, tells you about Multiplexing equipment, other recent developments.

## Learn More to Earn More

Act now. The catalog NRI sends you gives more facts about the field of your choice, shows equipment you get and keep. No obligation. Cost of NRI training is low. Monthly payments. 60-Day Trial Plan. Mail postage-free card today. **NATIONAL RADIO INSTITUTE, Washington 16, D.C.**

Send for  
64-Page  
CATALOG  
FREE

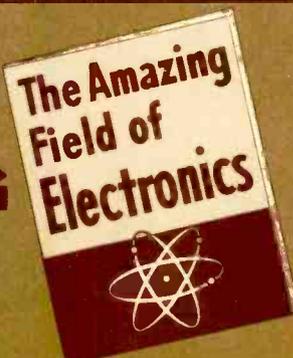

# NRI—Oldest and Largest Radio Television School Now Offers NEW HOME STUDY TRAINING IN INDUSTRIAL ELECTRONICS & MILITARY

This is the age of Electronics. Rapidly expanding uses for Electronic Equipment in industry, business, the military demands more trained men. Prepare now for a career as an Electronic Technician to assure advancement or to profit from your hobby. NRI now offers a complete course in **ELECTRONICS—Principles, Practices, Maintenance.** Computers, telemetry, automation, avionics are changing our world, yet all employ the same basic principles . . . and that is what this NRI course stresses with illustrated lessons and special training equipment. Mail card below.



## NEW HOME STUDY TRAINING FOR YOUR FCC LICENSE



An FCC Commercial License combined with NRI time-tested training can be the keys to a better future for you with higher pay, interesting work, more rapid advancement as the rewards. Prepare at home *quickly* for your FCC examinations through

NRI's new, low-cost, special training. Like other NRI-trained men, you can be monitoring TV shows, radio broadcasts, operating shipboard and aviation radio, or holding down other important jobs. Get full details—mail the card below.

**FOR MORE INFORMATION-TURN PAGE**

## Cut Out and Mail—No Stamp Needed



**NATIONAL RADIO INSTITUTE  
WASHINGTON 16, D.C.**

Send me your Electronic, Radio-TV catalog without cost or obligation. I am interested in the course checked below: (No representative will call. Please PRINT.)

- INDUSTRIAL ELECTRONICS     COMMUNICATIONS  
 FCC LICENSE                       SERVICING                      **WX**


Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

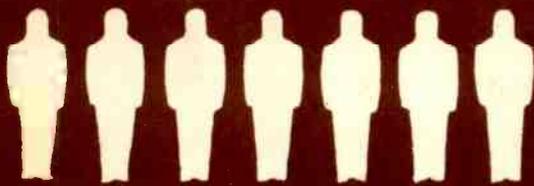**ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL**

**ELECTRONICS NEEDS  
4 TO 7  
QUALIFIED TECHNICIANS**



**FOR EVERY ENGINEER**



**Choose from 4 Courses**

- 1 INDUSTRIAL ELECTRONICS**  
Learn Principles, Practices, Maintenance of Electronic equipment used today by business, industry, military, government. Covers computers, servos, telemetry, multiplexing, many other subjects.
- 2 FCC LICENSE**  
Every communications station must have one or more FCC-licensed operators. New NRI course is designed to prepare you for your First Class FCC exams. You learn quickly, training at home in your spare time.
- 3 COMMUNICATIONS**  
Training for men who want to operate and maintain radio and TV stations; police, marine, aviation, mobile radio, etc. Includes FM Stereo broadcasting. Course also prepares you for your FCC license exam.
- 4 SERVICING**  
Learn to service and maintain AM-FM Radios, TV sets, Stereo Hi-Fi, PA systems, etc. A profitable, interesting field for a spare-time or full-time business of your own.

**SEE OTHER SIDE**

**Join The Thousands  
Who Trained For  
Advancement With NRI**

Thousands of NRI graduates throughout the U. S. and Canada are proof that it is practical to train at home. NRI graduates are in every kind of Electronics work: inspectors, maintenance men, lab technicians, testers, broadcasting and mobile communications operators, Radio-TV service technicians, or in essential military and government posts. Catalog tells more about what NRI graduates do and earn. Mail postage free card.



"THE FINEST JOB I EVER HAD" is what Thomas Bilak, Jr., Cayuga, N. Y., says of his position with The G. E. Advanced Electronic Center at Cornell University. He writes, "Thanks to NRI, I have a job which I enjoy and which also pays well."



**BUILDING ELECTRONIC CIRCUITS** on specially-designed plug-in type chassis, is the work of Robert H. Laurens, Hammonton, N. J. He is an Electronic Technician working on the "Univac" computer. Laurens says, "My NRI training helped me to pass the test to obtain this position."



"I OWE MY SUCCESS TO NRI" says Cecil E. Wallace, Dallas, Texas. He holds a First Class FCC Radio-telephone License and works as a Recording Engineer with KRLD-TV.



**MARINE RADIO OPERATOR** is the job of E. P. Searcy, Jr., of New Orleans, La. He works for Alcoa Steamship Company, has also worked as a TV transmitter engineer. He says, "I can recommend NRI training very highly."



**FROM FACTORY LABORER TO HIS OWN BUSINESS** that rang up sales of \$158,000 in one year. That's the success William F. Kline of Cincinnati, Ohio, has had since taking NRI training. "The course got me started on the road," he says.

FIRST CLASS  
PERMIT  
NO. 20-R  
(Sec. 34.9, P.L.&R.)  
Washington, D.C.

**BUSINESS REPLY MAIL**  
NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY




**National Radio Institute**  
3939 Wisconsin Avenue  
Washington 16, D.C.

**NRI IS OLDEST—LARGEST  
SCHOOL OF ITS KIND**

Training men to succeed by home study has been the National Radio Institute's only business for over 45 years. NRI is America's oldest and largest Electronics home-study school. Don't delay. Cut out and mail POSTAGE-FREE CARD.



**MAIL POSTAGE-FREE CARD**

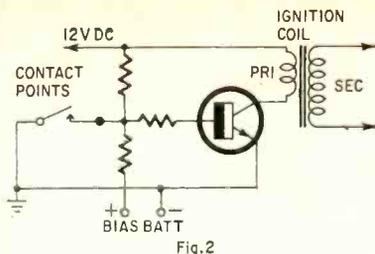

changing the distributor.

Seine, France ROBERT G. CASEY

[A complete ignition system—transistorized and electronic—is in the September 1961 issue, page 38.—Editor]

### AC LINE ANTENNAS

Dear Editor:

We've just moved to a 50-apartment building. Rabbit ears for our TV give us a fair picture, with lots of snow. What is your opinion of the TV antennas that plug into the light socket?

Santa Monica, Calif. THEODORE STERN

[These things are not only useless, but some of them can be dangerous. I would not recommend them under any circumstances. They are simply sucker bait, like the static eliminators they used to sell when I was a boy.—Jack Darr, Service Editor]

### WHY?

Dear Editor:

After reading "RFI: Invisible Killer" in the Sept. 30, 1961 issue of the *Saturday Evening Post*, I have a question to ask which has been bothering me for years.

No doubt radio-frequency interference is a problem. I'm particularly familiar with ignition static. For years I've been listening to trucks, buses and cars ruin short-wave reception because they were not equipped with ignition-noise suppressors.

Since many types of radio service are vital, why doesn't the FCC or the Government make it illegal to operate motor vehicles without suppressors?

After all, suppressors are cheap and easy to install. Doesn't anyone want to at least try to eliminate ignition static? Surely someone beside me is annoyed by unsuppressed ignition noise in radio and TV.

One simple law could make it mandatory that vehicle manufacturers install suppressors. This would help, wouldn't it? It's done in England.

Chicago, Ill. KEN GREENBERG  
[Amen!—Editor]

### MORE X-BREVIATIONS

Dear Editor:

I noted with some interest Nate Silverman's letter in the September 1961 issue, dealing with X = Trans. I have always used a similar system with the following abbreviations:

- Xtr = Transistor
- Xfmr = Transformer
- Xmtr = Transmitter
- Xducer = Transducer

Wantagh, N.Y. C. H. PEARSALL, JR.  
(Many thanks. Anyone else got a few to add to the list?—Editor) END

# The Professional Series TRANSVISION TV CHASSIS

## For Hi-Fi or Custom Installations

Designed for the perfectionist seeking maximum performance!

### Available in 19", 23", and 27" Sizes

Also available in KIT form which anyone can assemble.

Designed for all types of Custom Installation, Walls, Bookcases, Cabinets, etc. Complete line of accessories facilitate custom installation.

## 2 IMPORTANT TYPES

**FOR HI-FI SYSTEM:** Less Audio System, incorporates a Cathode Follower Circuit for operation into a Hi-Fi Audio System.

**WITH ITS OWN HI-FI AUDIO:** Includes its own Hi-Fi 10 Watt Push-Pull Audio Amplifier and Dual Hi-Fi Speaker system with 6" x 9" speaker, 6.8 oz. magnet, 3" tweeter, condenser crossover, extended range tone control.

**OPTIONAL ACCESSORIES:** Front panels for horizontal or vertical mounting of chassis (\$15.). For ease of servicing, front panel, tube, and chassis can be unitized with a "Rigidizing" assembly for sliding out from front. Slides included with "Rigidizing" assembly (\$10.).

### TECHNICAL FEATURES:

Ultra-linear sweep circuits • D-C restoration • Newest Standard Coil Guided Grid Turret Tuner with automatic fine tuning, provisions for UHF • Special low noise tubes • 5 microvolt sensitivity • 4 megacycle picture bandwidth • Heavy-duty dual 5U4G transformer type power supply • Ruggedized construction, hand-wired for trouble-free long life • True FM sound circuits.

All Parts are premium quality. RCA, Sylvania tubes, Allen-Bradley resistors, Cornell-Dubilier condensers. ALL PARTS Guaranteed for FULL YEAR!

### PRICES: CHASSIS or KITS

Item Size	Description	Chassis	Kit
(Prices include Pic. Tube)			
1 19"	No audio, for use with HI-FI System	\$263.00	\$178.00
2 19"	With HI-FI Audio incorporated	293.00	194.00
3 23"	No audio, for use with HI-FI System	268.00	183.00
4 23"	With HI-FI Audio incorporated	298.00	199.00
5 27"	No audio, for use with HI-FI System	328.00	243.00
6 27"	With HI-FI Audio incorporated	358.00	259.00


Picture tubes are the new bonded tubes. The protective glass is fused to the tube face improving picture contrast, reducing reflections, and eliminating dust between glass and tube. All Chassis are completely factory-wired, carefully tested and rigidly inspected. This is the Chassis selected by thousands of school systems and U.S. governmental agencies when premium type performance is required.

Dealer Inquiries Invited.


TRANSVISION Electronics, Inc., New Rochelle, N. Y. Dept. RE-C

Please send more information on  TV Wired Chassis  TV Kit. Enclosed is  \$25 deposit. Please send Item No. \_\_\_\_\_ (Chassis or Kit), balance C.O.D. Enclosed is \$\_\_\_\_\_ payment in full for Item No. \_\_\_\_\_. I understand that freight is prepaid when payment is made in full.

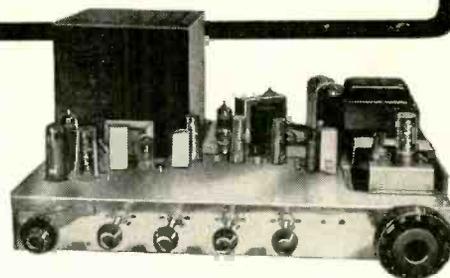
Name \_\_\_\_\_ Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



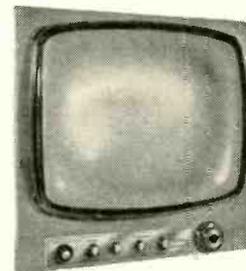
Top view of "Professional" Chassis with controls in horizontal position.




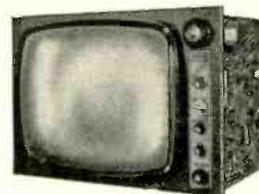Chassis can be mounted "Horizontally" or "Vertically"



Beautiful Cabinets available.

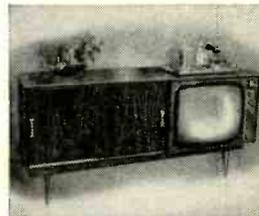

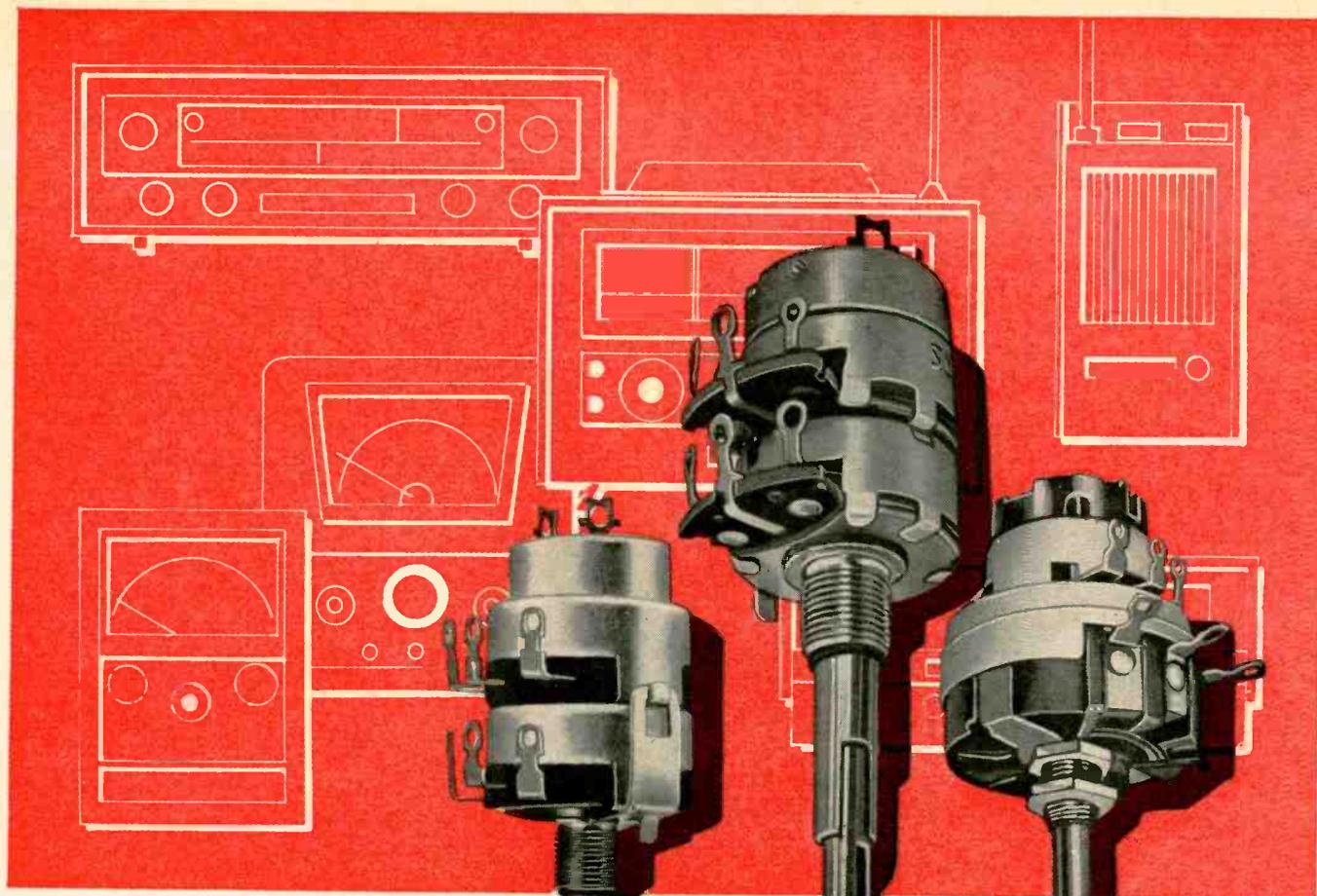

**wherever control is needed . .**

★  
*Dual and single carbon controls*

★  
*Dual and single wire-wound controls*

★  
*RTV exact-duplicate dual concentrics*

★  
*Uni-Tite field-assembled dual concentrics*

★  
*Switches*

★  
*Sound system controls*

**...USE  
CLAROSTAT  
REPLACEMENTS**

Television, radio, auto radio, citizens' band, amateur equipment, hi-fi, multiplexers, stereo, marine equipment...and just about every place electronic control is required you'll find the right control at your Clarostat distributor.


Clarostat specializes in controls for replacement purposes. These controls are designed to fit right, work right in every single case. They save you time, money and headaches. Always ask for CLAROSTAT controls in the green box and back your skills and knowledge with the very finest performances available.

ASK YOUR DISTRIBUTOR FOR CLAROSTAT CATALOG...

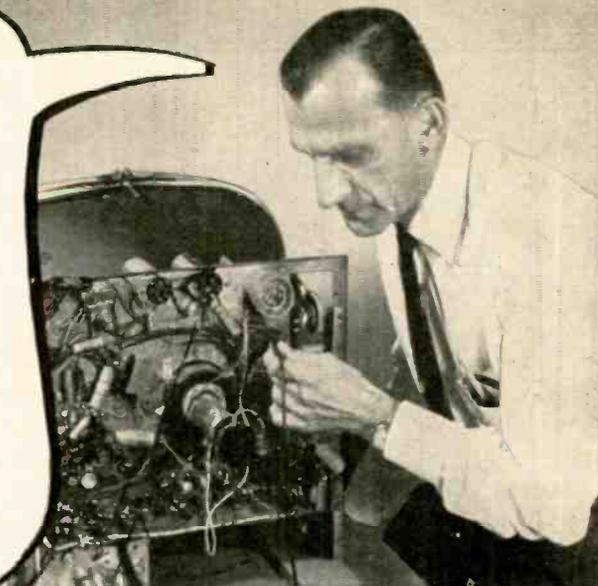**CLAROSTAT**

CLAROSTAT MFG. CO., INC. DOVER, NEW HAMPSHIRE

I chose **COYNE TELEVISION**  
**RADIO-COLOR TV**  
 home training because  
 Coyne has been training  
 men for good jobs OR  
 their **OWN BUSINESS** for  
**NEARLY 60 YEARS**



Giant opportunity field! Join the thousands Coyne Home Training is preparing for a successful future in TV—open the door to better pay jobs, or your own business! COYNE—a leading residential, practical school—oldest of its kind—established 1899—is the institution behind this training.

Here is **MODERN—QUALITY TELEVISION** Home Training designed to meet the rigid standards that have made Coyne famous. You get personal supervision of Coyne Staff who know TV and know how to teach. **Learn quickly and easily in spare time.** No previous experience or advanced education necessary.

I chose **COYNE** because  
 their new method costs less  
 than half what most others do!



**SEND COUPON FOR FREE BOOK**

Send coupon below for all-new fully-illustrated book and full details including **EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL**



Modern, up-to-the-minute. Easy to follow, step-by-step instructions—fully illustrated with 2150 photos and diagrams. **UHF and COLOR-TV included.** So practical you can quickly earn extra money in TV-Radio Sales and Service. Not only Coyne Quality training, but costs *half* what you'd expect to pay because you pay only for training—no costly extras. Free life-time employment service.

B. W. Cooke, Jr.  
 President

**COYNE** Founded 1899  
**ELECTRICAL SCHOOL**

CHARTERED AS AN EDUCATIONAL INSTITUTION NOT FOR PROFIT  
 1501 W. Congress Parkway, Dept. 12-H5, Chicago 7, Illinois

**COYNE TELEVISION HOME TRAINING DIVISION**

1501 W. Congress Parkway Chicago 7, Ill.  
 Dept. 12-H5


Send **FREE** Book and details of your Television - Radio - Color TV Home Training offer.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

# FM MULTIPLEX STEREO

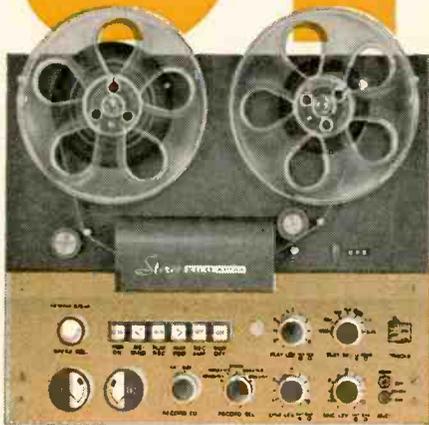

**TRANSISTORIZED  
4-TRACK STEREO TAPE DECK RP100**  
Completely assembled, wired and tested.  
\$399.95  
Semi-kit includes a completely assembled and tested transport, electronics in kit form.  
\$299.95  
Luggage-type Carrying Case—\$29.95  
Standard 19-inch Rack Mount—\$9.95

A top quality stereo tape recorder permits you to build a stereo tape library of your favorite music at low cost. As your musical interests change, you may record the new music that interests you at no additional cost.  
Perfected 4-track stereo/mono recording, 4 & 2 track playback. True high fidelity transistor electronics, individual for record & playback, plus separate record & playback heads permitting off-the-tape monitor. 2 recording level meters, mixing, mic & level controls, switched sound-on-sound recording. Electro-dynamically braked supply & take-up reel motors; hysteresis synchronous capstan motor. Individual solenoids for pinch-roller & tape lifters. All-electric, interlocked push-button transport control & interlocked safety "record" pushbutton. Precision tape guidance & sweep loading — no pressure pads. No slurring or tape bounce problems. Digital turns counter. Vertical or horizontal mounting. Modular plug-in construction. An original, exclusive EICO product designed & manufactured in U.S.A. (patents pending).



**FM-AM STEREO TUNER ST96**  
Kit \$89.95    Wired \$129.95  
Includes Metal Cover and FET



**70-WATT INTEGRATED STEREO AMPLIFIER ST70**  
Kit \$94.95    Includes Metal Cover    Wired \$149.95  
**40-WATT INTEGRATED STEREO AMPLIFIER ST40**  
Kit \$79.95    Includes Metal Cover    Wired \$129.95

**ST96:** FM and AM stereo tuners on one compact chassis. Easy-to-assemble: prewired, pre-aligned RF and IF stages for AM and FM. Exclusive precision prewired EYETRONIC® tuning on both AM and FM.

**FM TUNER:** Switched AFC (Automatic Frequency Control). Sensitivity: 1.5uv for 20db quieting. Frequency Response: 20-15,000 cps  $\pm 1$ db. Multiplex-ready: Regular and MX outputs built in.

**AM TUNER:** Switched "wide" and "narrow" bandpass. High Q filter eliminates 10 kc whistle. Sensitivity: 3uv for 1.0V output at 20db S/N ratio. Frequency Response: 20-9,000 cps ("wide"), 20-4,500 cps ("narrow").

**BOTH AMPLIFIERS:** Complete stereo centers plus two excellent power amplifiers. Accept, control, and amplify signals from any stereo or mono source.

**ST70:** Cathode-coupled phase inverter circuitry preceded by a direct-coupled voltage amplifier. Harmonic Distortion: less than 1% from 25-20,000 cps within 1 db of 70 watts. Frequency Response:  $\pm 1/2$ db 10-50,000 cps.

**ST40:** Highly stable Williamson-type power amplifiers. Harmonic Distortion: less than 1% from 40-20,000 cps within 1 db of 40 watts. Frequency Response:  $\pm 1/2$  db 12-25,000 cps.



**NEW FM MULTIPLEX  
AUTODAPTOR MX99**  
Kit \$39.95  
Wired \$64.95  
An original EICO  
contribution to  
the art of FM  
Multiplex reception.

(Patent Pending)

Designed for all EICO FM equipment (HFT90, HFT92, ST96) and any other component quality, wide-band FM tuners having multiplex outputs, the new MX99 incorporates the best features of both matrixing and sampling techniques. It is free of phase-distorting filters and provides the required, or better-than-required, suppression of all spurious signals including SCA (67kc) background music carrier, re-inserted 38kc sub-carrier, 19kc pilot carrier and all harmonics thereof. This is very important for high quality tape recording, where spurious signals can beat against the tape recorder bias oscillator and result in audible spurious tones in a recording. This adaptor will synchronize with any usable output from the FM tuner and will demodulate without significant distortion tuner outputs as high as 7 volts peak-to-peak (2.5 volts RMS).

The MX99 is self-powered, provides entirely automatic stereo/mono operation and includes low impedance cathode follower outputs to permit long lines. An indicator lamp turns on when the station selected is broadcasting multiplex stereo. A separation of 35db between channels is typical across the entire audio spectrum. An over-all gain of unity is provided from input to output on both stereo and mono.

C-1

EICO, 3300 N. Blvd., L.I.C. 1, N. Y.  
 Send free 32-page catalog & dealer's name  
 Send new 36-page Guidebook to HI-FI for which I enclose 25¢ for postage & handling.

Name .....

Address .....

City ..... Zone .... State.....

Over 2 MILLION EICO instruments in use.  
Most EICO Dealers offer budget terms.  
Add 5% in West.



© 1962 Electronic Instrument Co., Inc.  
3300 N. Blvd., L.I.C. 1, N.Y.



Listen to the EICO Hour, WABC-FM, N.Y. 95.5 MC, Mon.-Fri., 7:15-8 P.M.

Export Dept., Roburn Agencies Inc., 431 Greenwich St., New York 13

# FUTURE OF SERVICE INDUSTRY

. . . *Service Technicians' Future Seems Assured* . . .

**D**URING the past few years, electronic breakthroughs have occurred that could not have been imagined a decade ago. Beginning with the transistor revolution around 1950, in quick succession there evolved a miniaturization of most components, making possible the module type of set whereby a whole radio (minus its speaker) could be shrunk to less than 1 cubic inch.

A little later came molecu- larization that reduced transistors and their chief components to such a microscopic size that you could no longer see the total assembly with the naked eye. When molecular electronics is mass-produced—which will be soon—it is safe to assume that, since there are neither mechanically fashioned nor soldered connections between individual components, and since the total array of the components is so minute, it will theoretically last for generations. Neither air nor moisture will be able to get at the various parts. Because the mass and volume—hence weight—of such an array of components are so microscopic, even the most severe shocks should not damage it, unless violently crushed.

When such sophisticated electronic assemblies are then used in conjunction with printed circuits, as they surely will be, it would seem that radio and TV sets thus fashioned would last "forever" and never need servicing.

This reasoning, if we can believe the not-too-occasional letters from readers, has turned many radio-electronic technicians into prophets of doom who can no longer see any future in their business. "If," they say, "all new and upcoming sets are manufactured so perfectly that they no longer fail, what's the sense of staying in the servicing business?" Well, we answer, this reasoning is wrong.

To begin with, let us assume that the new super-receivers were to come off the assembly lines tomorrow. Then let us take inventory and this is what we find:

There are now in existence in the US alone

**186,300,000 home and personal radios**

**41,000,000 auto radios**

**34,500,000 radio-phonographs**

**55,700,000 television sets, not including closed-circuit TV.**

On a conservative basis, these 317,500,000 receivers will probably require 20 years or more of servicing before they have "worn out" or become hopelessly antiquated. Admittedly, the "average" life of a radio or other electronic device is much shorter. But, if you look around, you will see numbers of good radios 15 to 20 years old, and converted 1948 or 1949 TV sets that show no signs of an early demise. We should also not lose sight of the important fact that even today a considerable percentage of *these* tube sets never fail, if we except an occasional tube replacement. As we are writing this, on top of our desk there sits an 11-year-old, four-tube, plastic, molded-case, ac-dc radio. It is used daily, chiefly to get the news. Occasionally it runs for hours.

Believe it or not, in 11 years it has *never* failed. No tube has ever been replaced. The only failure was purely mechanical: the friction tuner knob came loose and had to be tightened! We bring this up only because, if *every* set in the land had to be serviced regularly, there would not be enough servicing technicians to do the work and it would take months before every set owner could have his set serviced.

Now let us consider the new molecular sets that may soon make their appearance in vast quantities.

All the components, such as transistor, capacitors, resistors, etc., with the exception of the speaker, tuning device and volume control, will probably be mounted on a socket with pins, just as we do now with our tubes. There may be several such *component clusters* and there may be a dozen or more contact pins to a cluster. Thus, a complete amplifier stage with all its components will be in a single cluster.

Should anything go wrong, the cluster can be removed just as you remove a tube today. The service technician probably will have a new type of troubleshooting instrument which will inform him speedily *which* cluster failed and why. He will replace it with a new one, discarding the old. If this system is economically unfeasible, the cluster leads would then be soldered or mechanically fastened to the printed circuits. Service technicians would then have to unfasten such a cluster, if defective, and replace it with a new one.

TV sets, always more complex than any radio, will also require more servicing because their greater complexity, even in the future, will make for more failures. This will be true even when all TV's will be completely transistorized.

We can even foresee when future TV sets will be powered atomically. Atomic energy will furnish the necessary high-voltage supply, probably quite independent of the house current. In this manner *all* radios and TV's will be truly portable.

While future sets—radios, TV's and other wholly unimagined, communication, education and entertainment units may theoretically become so perfect that they may never require servicing, practically we doubt that this will ever come about.


There will always be intermittents, mechanical failures in various connections, tuning devices, loud-speakers, volume controls and others, particularly devices where continuous mobility or motion is necessary.

We are convinced that the prophets of doom who see the servicing industry going to pot have misread the future completely. In our complex civilization that requires objects of many parts, be they clocks, cars, elevators, telephones, air conditioners or TV's—a goodly percentage of them must be serviced occasionally, no matter how careful their construction. Even such well constructed objects as humans with a long history of millions of years behind them must also be serviced occasionally by those well trained technicians, the medical doctors. Serviced they always will be, far into the most distant future we can foresee.

—H.G.

# electronic cooling & heating

New uses for an old principle

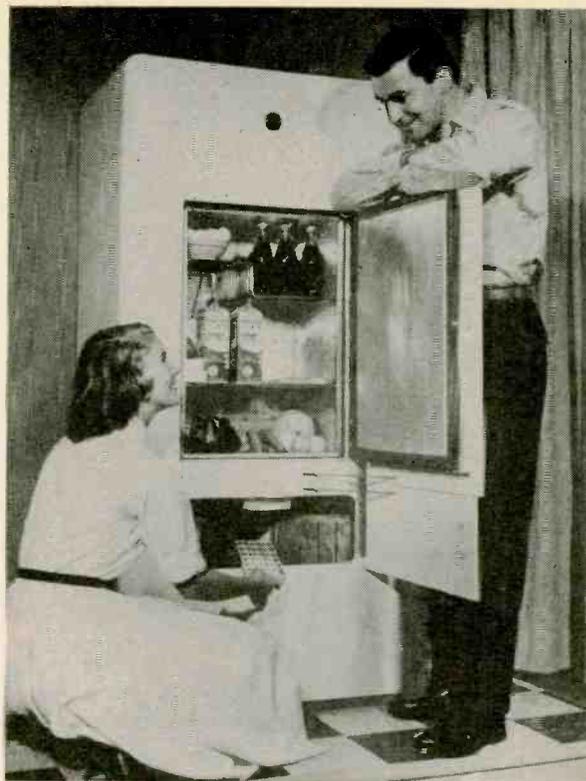

Thermoelectricity keeps this experimental RCA refrigerator cold.

By LAWRENCE H. OTT, Ph.D.\*

DEVELOPMENTS IN THERMOELECTRICITY are making electronic headlines and are being carefully watched by specialists in many fields. Two factors are responsible for the recent upsurge of interest in this 140-year-old discovery—the growing list of applications for thermoelectric devices, and the increasing indications that we are on the brink of startling advances in this field.

Interest in thermoelectricity is following two main lines. First there are developments in the generation of elec-

trical power. Second there is great activity in thermoelectric refrigerating systems or heat pumps.

Space satellites have created a need for special power sources. Some of the new devices being studied include thermoelectric generators, fuel cells, solar cells and thermionic converters. Main interest has been in thermoelectric generators because of their simplicity and versatility. The commercial power industry is also seeking new ways to increase power-plant efficiency and reduce their size and complexity.

In refrigeration, thermoelectricity promises important advantages over mechanical systems. These include elim-

ination of moving parts, less noise, simpler control and adaptability to small-scale cooling applications.

## Thermoelectric effects

The simplest thermoelectric effect is conductor heating by current flow, or Joule heating. However, this is an irreversible process and is not ordinarily included under the heading of thermoelectricity.

The two most important thermoelectric effects are the Seebeck effect, in which a potential difference is generated when the junction between dissimilar conductors is heated, and the Peltier effect which covers the absorption

\*Senior staff engineer, Aerospace Group, Hughes Aircraft Co.

or generation of heat when a current flows across the junction between two different conductors.

Thermoelectricity is more than a century old. Thomas Johann Seebeck in 1821 was experimenting in Berlin with a bar of antimony that had a coil of brass wire wound around it and attached to its ends to form a loop. He noted that, when a junction of the bar and wire was heated, a nearby magnetic needle was affected. Two years before this event Oersted had discovered the magnetic effect of a current, and Seebeck believed that he had discovered a magnetic effect caused by heat. The idea of a current flowing in the conductors did not at first occur to him. Four years later when Ohm discovered his famous law, he used the Seebeck effect to produce small voltages.

Fourteen years afterward, Jean Charles Peltier, a French physicist, noticed that when a current flowed in a circuit of two dissimilar metals, one junction between the two was heated while the other was cooled. To us the Seebeck and Peltier effects are complementary but, at the time of their discovery, they were imperfectly understood, and it was not until 1857 that Lord Kelvin, then William Thomson, showed the exact relationship between the two and postulated a third small thermoelectric effect, now called the Thomson effect, caused by the thermal gradient in conductors.

The Seebeck and Peltier thermoelectric effects are small when ordinary metals are used, and for over a hundred years the principal uses were for thermocouples and thermopiles for temperature-measuring and heat-detecting devices. Thermoelectricity could not compete with other electrical power-producing methods such as batteries and generators as the power conversion efficiencies for thermoelectrics were generally below 1%.

The recent advances in knowledge of solid-state physics, particularly in the field of semiconductors, have brought about an upsurge of interest in thermoelectricity. All conducting materials have measurable Seebeck and Peltier effects, but certain semiconductor materials exhibit markedly greater effects than ordinary materials. They also have the proper values of electrical resistance and thermal conductivity necessary to give good performance in thermoelectric heat-transfer and power-generation applications. Both n- and p-type semiconductor materials are useful. The first can be thought of as having a surplus of free electron carriers, while the second type has a deficiency. In p-type materials the current carriers are positive carriers or "holes". In both types, the density of current carriers is very much less than in ordinary metal conductors.

### Seebeck and Peltier effects

To get a working concept of the Seebeck effect, visualize the current carriers in metallic conductors as if they were a liquid, and in semiconductors as if they were a gas. When one end of

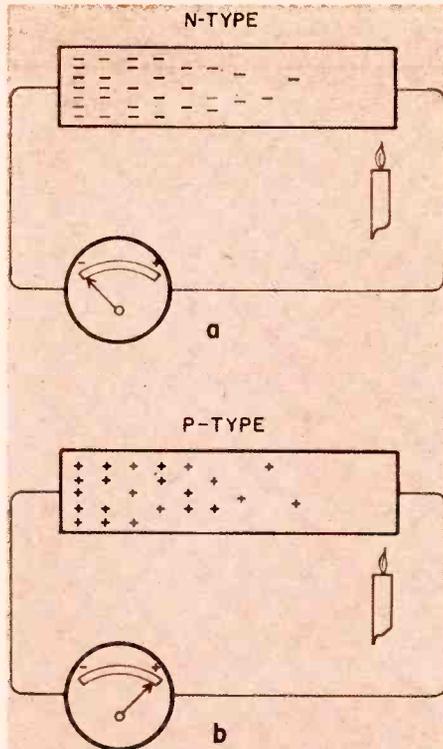


Fig. 1—Seebeck effect. Movement of electrons in semiconductor material caused by heating. a—N-type semiconductor. b—P-type semiconductor.

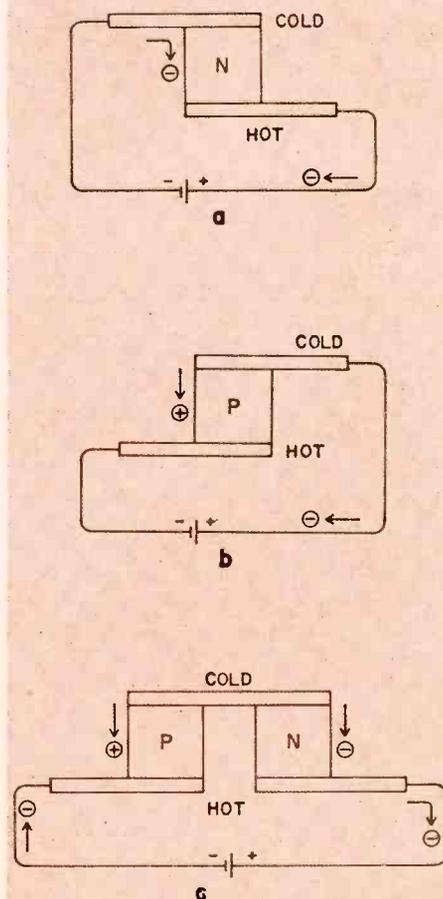



Fig. 2—Peltier effect. An applied voltage forces electrons to flow through semiconductor material, absorbing heat at one terminal and emitting heat at the other.

a piece of n-type semiconductor is heated, the conduction electrons at this end, visualized as a gas, increase in pressure and are driven to the cold end. In this way the cold end of n-type has a greater density of conduction electrons and will show a negative potential with respect to the hot end (Fig. 1-a). In a similar way, when one end of p-type semiconductor is heated, the "hole" conductors, also visualized as a gas, increase in pressure and are forced to the cold end (Fig. 1-b). The latter then has a greater density of "hole" conductors and a positive potential with respect to the hot end. Forming a thermocouple with n-type material for one leg and p-type for the other is then an obvious way to combine them for maximum thermoelectric voltage effect.

The Peltier effect can be understood in a similar way by visualizing the current carriers operating in a gas-liquid transformation. Now consider a piece of n-type semiconductor with a metal strip attached to each end. If we apply a dc voltage, electrons are forced to flow from the negative pole of the battery around the circuit. The electrons in the external metal conductor are visualized as a liquid and, when they pass across the junction of the semiconductor, they leave the energy levels of a liquid and enter the vapor state of a gas. This "evaporation" process absorbs heat and a cold junction results (Fig. 2-a).

At the other terminal the electrons are forced by the potential from the gaseous state in the semiconductor into the liquid state in the metal. This corresponds to a "condensation" change of state, and heat is emitted and the junction becomes hot. With p-type materials the carrier flow from metal to semiconductor is a cooling transition, and the flow from semiconductor to metal is heating. With the same direction of current flow, the heating-cooling effects at the junctions are opposite to those of n-type material (Fig. 2-b). Combining an n-type leg and a p-type leg in a circuit couple will create a hot junction and a cold junction for maximum effect (Fig. 2-c). If heat can be continuously dissipated from the hot side of the couple, that is, to a heat sink, a temperature difference can be maintained between the two junctions. In other words, we have an electrical heat pump. The temperature difference between the opposite ends depends upon the heat load to the cold side and the efficiency of the heat sink. In practice, many couples are connected in series electrically with their heat pumping capacities in parallel.

One of the popular misconceptions about Peltier coolers or heat pumps is that, with the passage of a current through the semiconductor materials connected in couples, heat is somehow annihilated at one junction. It is important to recognize that while a quantity of heat may be "pumped" from an object while maintaining the object below the effective environment—that is, heat is made to flow "uphill"—to do this electrical power must be expended. The amount of power may range from a

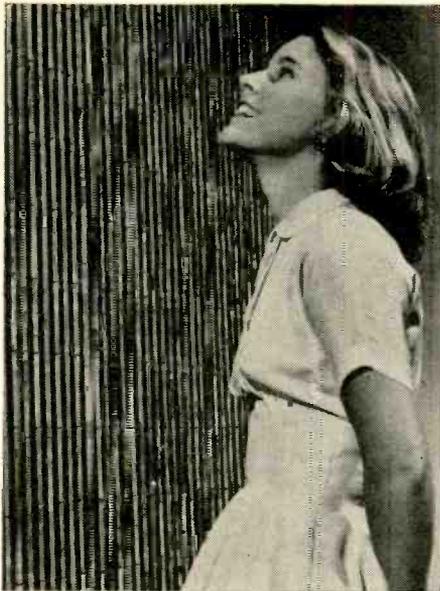

Wall of thermoelectric elements makes a room air conditioner.



Experimental diode cooler for spot-cooling tests on electronic components.

fraction to several times the quantity of heat pumped. Thus, while Peltier devices lower the temperature of the cooled object, they require the expenditure of energy. Therefore the heat to be disposed of is larger than the heat removed from the object.

However, operating the Peltier unit in the heating cycle (that is, with current reversed), the device is more efficient than resistive heating since, in addition to the  $I^2R$  heating, there is added the heat pumped from the cold side. Thus, as a heat pump in the heating mode, it may supply up to several times more output heat than an equivalent, purely resistive, heating element.

The total amount of heat pumped is directly proportional to the cross-section area of the semiconductor material perpendicular to the direction of

heat flow. Since total cross-sectional area is the important factor, it makes no difference whether the material is in many small pellets or a few large pellets. For each size of pellet there is, however, an optimum cooling current. The only geometrical influence on heat-pump performance is the ratio of length to area of cross-section. Thus for a given  $L/A$ , the smaller the element the more heat can be pumped per unit area for the same change in temperature and current.

### Good thermoelectric semiconductors

A research group at Baso, Inc. in 1948 found that lead telluride, suitably doped with an impurity, was an efficient thermoelectric material. In 1955, a detailed study of bismuth telluride, a material first suggested by Goldsmid, led to the development of associated alloys used for practical thermoelectric devices.

The ideal thermoelement would possess a high Seebeck coefficient together with infinite electrical conductivity and zero thermal conductivity. The three properties are combined in a single design parameter for the material, named the figure of merit,  $Z$ , which is related to the Seebeck coefficient,  $S$ ; to the electrical resistivity,  $\rho$ , and to thermal conductivity,  $k$ , by the equation  $Z = S^2/\rho k$ . These three properties are not independent of each other, but depend upon the number of mobile electron and hole carriers. The Seebeck voltage and the electrical resistivity are inversely proportional to the number of mobile carriers, while the thermal conductivity is approximately a linear function of the carrier density.

There is a never-ending search for better thermoelectric materials. To get optimum efficiency or maximum power output, it is necessary to find the correct mobile carrier density. Typical carrier densities for a good conductor such as copper, and a good insulator, such as quartz, are  $10^{23}$  and  $10^9$  carriers per cubic centimeter, respectively. The range for semiconductors lies between  $10^{14}$  and  $10^{20}$  carriers per cubic centimeter. A value of  $10^{18}$  carriers per cubic centimeter has been found best for lead telluride, bismuth telluride and germanium telluride.

The figure of merit, the important material parameter mentioned above, is a function of temperature. Generally, it reaches a maximum value at some particular temperature and then drops off rapidly. At higher temperatures no potential difference is generated by the semiconductor material. This fact has led to extended research in materials.

The maximum efficiency of a thermoelectric device is governed by the same Carnot limitation as a reversible heat engine. That is, the greater the difference in temperature between the hot and cold ends, the higher the conversion efficiency. Present-day devices are inefficient energy converters averaging about 6%. A modern industrial power plant with turbine generator can operate with a thermodynamic cycle efficiency of 45% and an electrical gener-

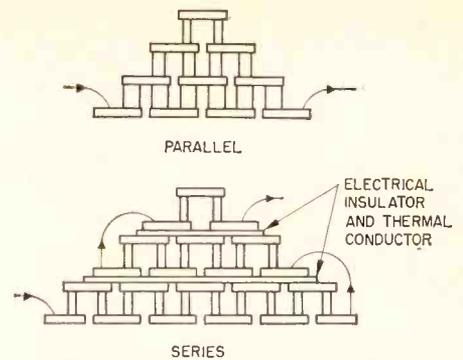


Fig. 3—Two common configurations of three-stage coolers. In such arrangements the cold junction of the first set of the thermocouples serves as the heat sink for the second, etc.

ator efficiency of 95%. This results in an overall thermal efficiency of 42%.

The forecast for thermoelectric generators in the next 25 years is that thermal efficiencies may reach approximately 30%. While this is lower than that achieved by the turbine-generator power plant, thermoelectricity may find its place in some areas.

### Practical devices

In spite of lower efficiency, thermoelectric power generators have much to offer for certain applications. The Atomic Energy Commission has sponsored a program to develop several nuclear-fueled generators for SNAP (Systems for Nuclear Auxiliary Power). One of the first products of this program, the SNAP-III radionuclide battery was demonstrated in January 1959. The unit weighed about 5 pounds and had an output of five watts to a matched load. The heat source consisted of a small amount of radioactive Polonium 210, and a temperature differential of about  $600^\circ\text{F}$  is maintained between hot and cold junctions. During the half-life of this material, the generator is calculated to deliver a total of over 9,000 watt-hours of power, or the equivalent of more than 100 pounds of the best chemical storage batteries.

A larger unit, SNAP I-A, weighing 175 pounds, has an output of 128 watts at 28 volts. This generator has 277 thermoelectronic couples imbedded in a shell enclosing a nuclear fuel package of Cerium 144. The unit is smaller than a solar-cell system and operates continuously. Provision is made to maintain the electrical output constant as the nuclear fuel decays.

The Navy is interested in thermoelectric power generators for ship and submarine use. Kerosene is the fuel source for a 5-kw generator being built that has many combinations of voltage and current outputs ranging from 500 amperes at 10 volts to 42 amperes at 120 volts. Lack of operational noise, compactness and the possibility of using nuclear fuel make thermoelectric generators advantageous for submarines.

An interesting commercial development in small thermoelectric generators is a portable unit to provide emergency power for operating a transistor radio receiver. This unit consumes 1 pint of kerosene or fuel oil in 24 hours, develops

0.75 volt and delivers 0.5 watt of power to a matched load. A built-in transistor converter changes the 0.75-volt output to the 3 to 9 volts required to operate most transistor radios.


In the field of heat pumping and refrigeration there are plans to employ thermoelectric devices for small refrigerators for home, auto, boat, plane, and camping and water coolers.

One manufacturer has designs for several sizes of refrigerators with from 1 to 4 cubic feet of capacity. The smallest size is designed for a 25-watt thermal load and uses 30 bismuth telluride thermocouples 2/10 inch in diameter and 1/4 inch long. The operating current is 20 amperes at 2.5 volts. The 4-cubic-foot model is designed for a 65-watt thermal load, uses 80 of the same thermocouples. The boxes are insulated with plastic foam 1 inch thick and will maintain an inside box temperature of 40°F or lower when operating in an outside ambient of 90°F.

Another manufacturer is producing small thermoelectric refrigerators for installation in all the new rooms of a Chicago hotel to provide guests with self-service ice cubes.

In medical research there have been applications for controlled cooling of particular areas of the body, for example, spot cooling of parts of the brain. These studies are leading to increased knowledge of human physiology. Such a thermoelectric cooler has been designed at Hughes Aircraft Co. and used at UCLA's Medical Research Center for experimental brain research.

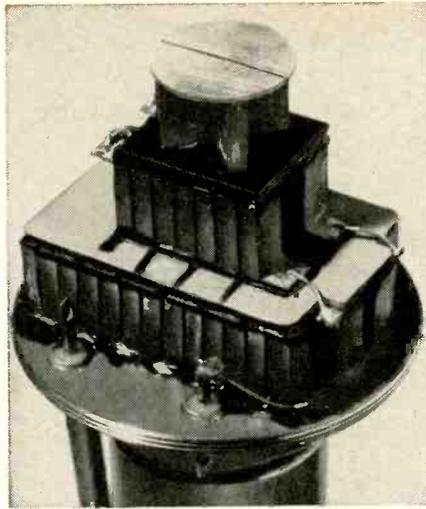Thermoelectric cooling is being used to air-condition an experimental space suit to keep an astronaut comfortable at a temperature of 80°F in environments



Hughes

**Infrared detector is cooled by three-stage cascaded thermoelectric device. Operating on 2 amperes at 2 volts, the unit drops temperature from 25°C to -77°C.**

up to 135°F. A thermoelectric cooler-heater unit fits into the back of the suit with the battery power source in the front.

The electronics field offers countless uses for general and spot cooling of component parts. Spot cooling is usually by direct conductive connection between the part and the Peltier cooler. Power diodes, transistors, ferrite cores, infrared cells, photocathode and photomultiplier tubes, fluorescent light sources, etc. are all temperature-sensitive components. Most solid-state devices are limited to a specific maximum temperature of operation, above which their characteristics deteriorate and reliability diminishes. So keeping tem-

peratures down becomes important.

Infrared detector cells, important for guiding some types of missiles, have increased sensitivity and lower noise output level when operated at temperatures below that of dry ice. Obviously, it is not convenient to maintain a supply of dry ice or liquefied refrigerant in each missile. Thermoelectric coolers have been successfully developed for this important application. Such devices begin to operate the instant current is turned on. A unit operating at 2 amperes and 2 volts achieves a temperature drop from 25°C to -77°C, enough to cool an infrared detector down to its optimum operating temperature. The Hughes cooler is a three-stage cascaded device using cell loading of about 125 mw.

In the cascaded arrangement of thermocouple elements, the cold junction of the first set serves as the heat sink for the second set, and the cold junction of the latter cools the hot junction of the third set, and so on (Fig. 3). In this way a greater temperature difference can be built up between the heat sink and the final cold junction. Unfortunately, due to the temperature variation of certain material parameters, not much is gained by employing more than three stages.

Such is the current state of thermoelectric technology. The great promise of thermoelectricity is that, with some further advances which seem within our grasp, it will perform a wide variety of tasks important to man's welfare more efficiently, more simply and more conveniently than existing devices. As our knowledge of solid state phenomena increases, its future appears to be well-nigh limitless. END

## "Instant-on" Circuit for ac-dc receivers

SOME NEW WESTINGHOUSE RADIO AND portable TV's incorporate an ingenious circuit which keeps the series-string tube heaters running at about quarter power even when the set is turned off. The result is that, when the set is turned on, it plays instantly with no warmup delay. At the same time, the tube heaters are spared the jolting current surge which hits them when an ordinary receiver is turned on.

The Westinghouse circuit requires an additional silicon rectifier and a dpst line switch to replace the original spst. The circuit can be added to an existing ac-dc radio with little difficulty.


Best results are obtained in sets which use a semiconductor to rectify the high voltage. Receivers with vacuum-tube rectifiers may not play instantly when turned on. However, they will play within a few seconds.

Two circuits are shown. Fig. 1 is for use in sets where the on-off switch is connected between the chassis and one side of the line. Fig. 1-a shows the original, 1-b the modified circuit. Fig. 2 is for those sets where the chassis connects directly to one side of the line with the line switch inserted in the


other leg, Fig. 2-a is the original, 2-b the modified circuit. Note that the additional silicon rectifier is bridged across the main line switch and is shorted out when the switch is in the ON position. In the OFF position, the B-supply is disconnected by the other section of the switch and the filament string is supplied with a reduced dc potential instead of its normal 117 volts ac. The silicon rectifier delivers approximately 55 volts dc. This voltage across the entire heater string results in a drain about a fourth the normal filament wattage but is enough to start the set playing as soon as the B-supply voltage is applied by turning on the switch.

Assuming that the heater string draws 150 ma, the added current drain from running the heaters at quarter power when the set is off should not add more than 75¢ to \$1.50 to the annual electric bill, depending on electricity rates. However, tube life should be extended greatly by continuous heater operation, so the end result may be an actual dollar saving.

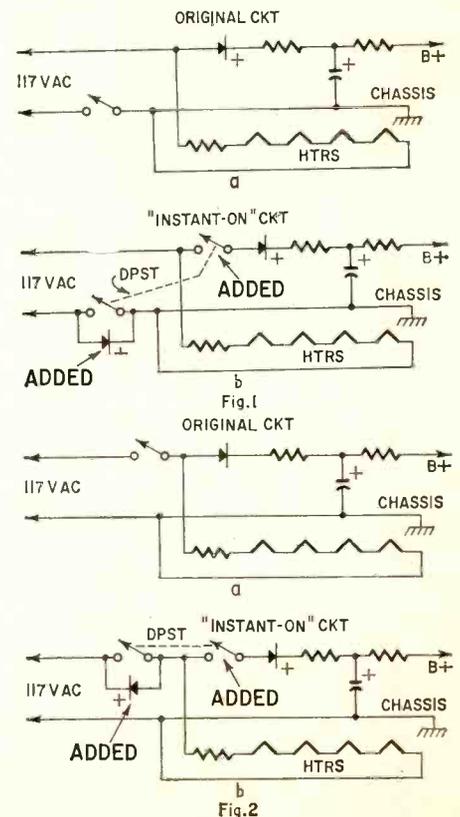The added silicon rectifier can be one of the universal 130-volt rms, 250-500-ma types. END



# BUILD

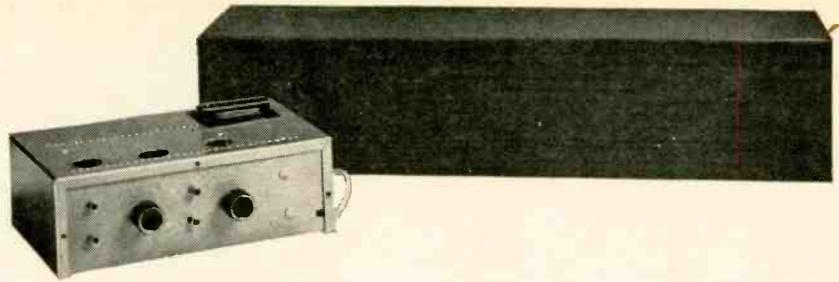

## A SIMPLE REVERB UNIT

An interesting project for the audio experimenter

By **GEORGE MANNING LEWIS**

THIS ARTICLE PRESENTS A PRACTICAL REVERBERATOR unit designed to be inserted into the builder's high-fidelity system. It can be built by the average hi-fi enthusiast or kit builder in a few hours. The materials can often be salvaged from other electronic equipment. If purchased new, the cost should not be over \$20 or \$25.

Introduced only about 2 years ago, several electronic devices on the market supply various amounts of reverberation when inserted into the circuitry of a monaural or stereophonic home music system.

There has been some controversy as to the value of reverberation. Some dismiss it as a worthless fad. To me, however, reverb is no mere novelty or sales gimmick, but a major advance in home music reproduction.

Little material intended to enable the electronics hobbyist or kit builder to construct a practical reverberator has been published, and some of what has been printed has come from far out in left field. The unit presented here is the product of a period of research and experiment during which several methods and devices—and several electronic circuits—were explored. It is not perfect, but it is a practical, easily constructed device that will give highly gratifying results with either stereo or monaural recorded material.

To keep the story simple, we are discussing primarily a monaural unit. It can be modified for use in a stereo circuit. The constructor can make the monaural unit first, leaving space on the chassis, and later add the other tube and wiring to make it a stereo instrument.

But, because of the nature of stereo and the acoustics of the average living room, many listeners find that adding reverb to only the right channel of a stereo system is adequate.

### How reverberation works

Much of the tonal richness and vibrancy of a well designed (acoustically) concert hall is the result of a mixture of sounds simultaneously reaching the ear. Some of these sounds have traveled directly—in a straight line—

to the listener's ear. Other portions of the same sounds have first been reflected from the ceiling, walls and even the people in the audience. This causes them to reach the listener's ear a fraction of a second later than the sound that traveled directly from the stage to the auditor.

But that is not all. Reflecting the sounds modifies their tonal quality. It alters the character of the sound—its quality, volume, duration, pitch and timbre—by altering the complex resultant of the concomitant sound vibrations. To produce reverberation electronically, it is necessary to take a portion of the audio signal from the audio signal path at some point before the power amplifier stages and to delay it for 20 or more milliseconds (about 40 or 50 milliseconds is optimum for the average living-room application—unless one likes echoes, the time delay must be less than 1.8 seconds). During this process its tonal character is modified. Then it is reintroduced into the audio signal path, being mixed with the undelayed (primary) audio signal (Fig. 1).

The problem of designing a practical reverberator unit then resolves itself into two parts: achieving the time delay and approximating the normal concert hall's ability to modify the total character of the sounds being bounced off the walls and ceiling. This may be done with a mechanical device such as a length of spring wire, through which the sound must travel before being reintroduced into the audio signal path.

Thus the reverberator unit consists of two parts: an electronic unit which is essentially a lo-fi amplifier and transducer, that builds the amplitude up and converts it to auditory sound which may be mechanically delayed; and a mechan-

ical delay device (that also performs the character modification function) with its pickup and mixer circuitry.

### Building the reverberator

The unit presented here for hobbyist construction (Fig. 2), takes a portion of the audio signal from a voltage-divider network and directs it through a triode-pentode tube (a 6BM8/ECL82) for amplification, following which the reverb signal is directed through an ordinary 1,000-ohm headphone) to which a small wire loop has been soldered in the exact center of the phone diaphragm, which converts the reverb signal to audible sound. (To distinguish between the two signal portions we now have, let us speak of this portion of the signal which has been diverted from the audio signal path as the reverb signal; the other signal as the audio signal.)

The sound is directed, by the loop soldered to the diaphragm, into a length of coiled spring wire, the other end of which is attached to a crystal cartridge which reconverts the audible reverb signal into an electronic signal. This in turn is mixed—in a 6EU7 mixer tube—with the audio signal, after which it is fed to the main power amplifier.

The use of a mixer tube as a means of introducing the reverb signal into the audio signal path is necessary to prevent feedback of the reverb signal to the voltage divider and thence to the grid of the 6BM8. That would, if allowed, create a ring-around-the-roses condition of oscillation. The choice of a 6EU7 was dictated by several considerations: It is an extremely quiet tube. Its pin connections make wiring into the circuitry of the reverb unit easy. Being a tube specifically designed for hi-fi audio application, its fidelity is


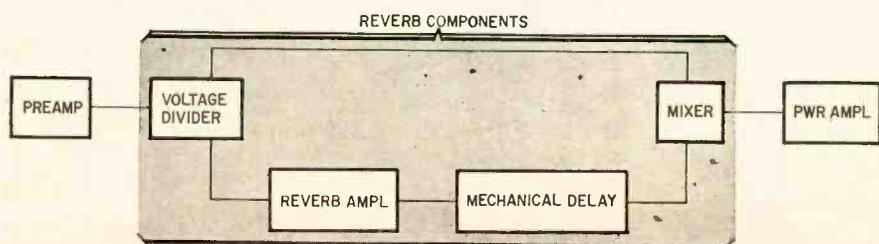
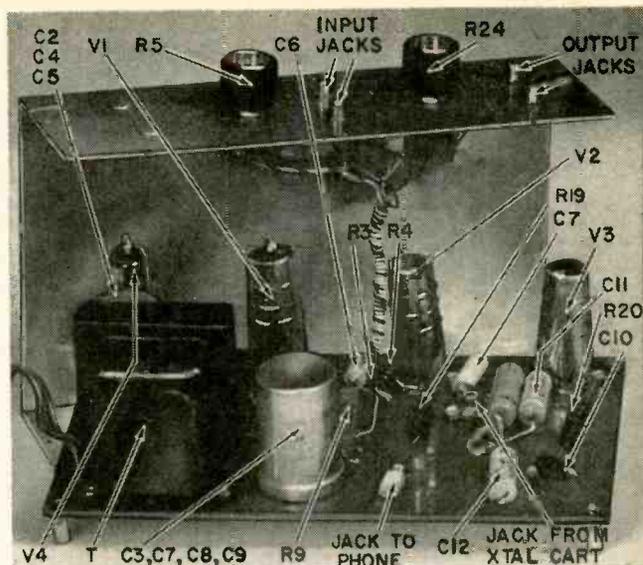


Fig. 1—How reverb unit fits into a monaural hi-fi system.

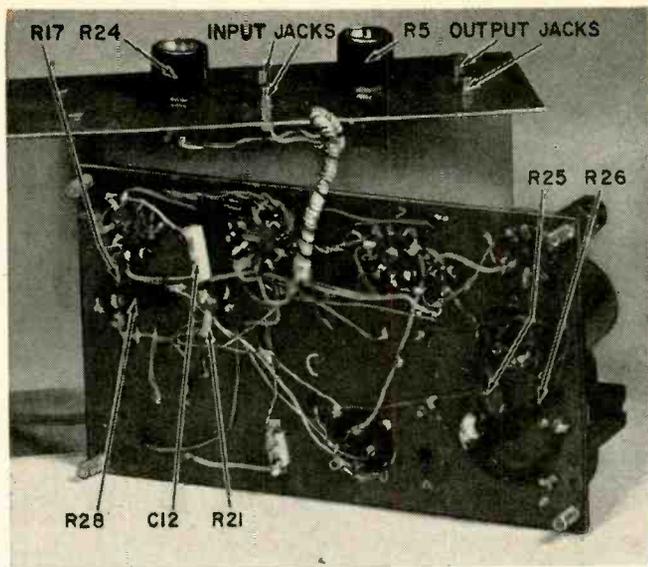

Top and bottom views of the reverb unit chassis.

extremely high and reliable. Its two triode sections are matched for identical performance.

Wired as shown in the schematic (Fig. 2), it has an overall gain of about 12, approximately equivalent to the loss of audio signal at the voltage divider. Thus this additional stage in the pre-amplifier part of a hi-fi rig scarcely increases the overall preamplifier signal gain, and the use of the 6EU7 as mixer makes no perceptible difference in the tonal quality or fidelity of the audio signal passing through it.

Although the 6BM8/ECL82 is not (in this country) a popular audio tube, experiments indicated that it is eminently suitable for this particular application. The triode section used as a driver, resistance-coupled to the pentode section, used as an output pentode, can produce about 4 watts of audio power, more than sufficient to energize the 1,000-ohm phone that drives the spring.

Parts placement is not too critical, but you must use every precaution against introducing hum or noise into the audio signal path. Shield the grid leads (Fig. 2), and ground to the chassis at one point only (to prevent so-called ground loops). Usual commercial

(10%) tolerances in component values are acceptable. The B-plus should be liberally filtered.

The electronic portion of the unit can be constructed on a 5 x 7 x 2-inch chassis. Because I have a bookcase hi-fi rig, with components in full view, my reverb unit (see photo) was constructed on a 5 x 7 x 3/16-inch laminated paper phenolic board, so that it could be encased in a 6 x 8 x 4-inch Bud utility box.

The choice of a 6X4 for the rectifier was purely arbitrary. Any other full-wave rectifier tube or selenium rectifier bridge could be used satisfactorily. A half-wave rectifier tube or selenium stack would probably introduce hum into the audio signal.

### The mechanical delay

The purpose of this section is to delay the reverb signal for 20 or more milliseconds, before feeding it back into the audio signal path, and to approximate the tone character modification of concert-hall reverberation.


The actual length of the delay (as well as the amount of reverberation) is determined by several factors, including personal preference and size and acoustics of the room in which it is to

be used. Hence some experiments will be needed when the unit is completed, and controls for adjustment must be provided in the design.

This is done by enclosing the unit in a plywood box (Fig. 3). The spring is attached on one end to the phone (to which a small wire loop has been soldered at the exact center of the diaphragm). The other end of the spring terminates with an eyebolt that passes through a 1/4-inch rubber grommet inserted into a hole in the plywood end of the box. A wing nut is used on either eyebolt. Thus the tension of the spring may be adjusted as desired, or as experimental listening indicates. The phone is fastened with a similar grommet to the other end of the box, as the photo indicates.

The spring itself is a variable and, since no readily available springs are made to exact standards (of "springiness", sound-vibration transmitting ability, etc.), some experimenting will be needed. The one I found satisfactory was wound of No. 30 steel wire on a 3/16-inch diameter form and was purchased from a local hardware store (Belknap, general-purpose spring, S-3016-30). When purchased it was tightly

Fig. 2—Schematic of the simple reverbulator for a one-channel system.

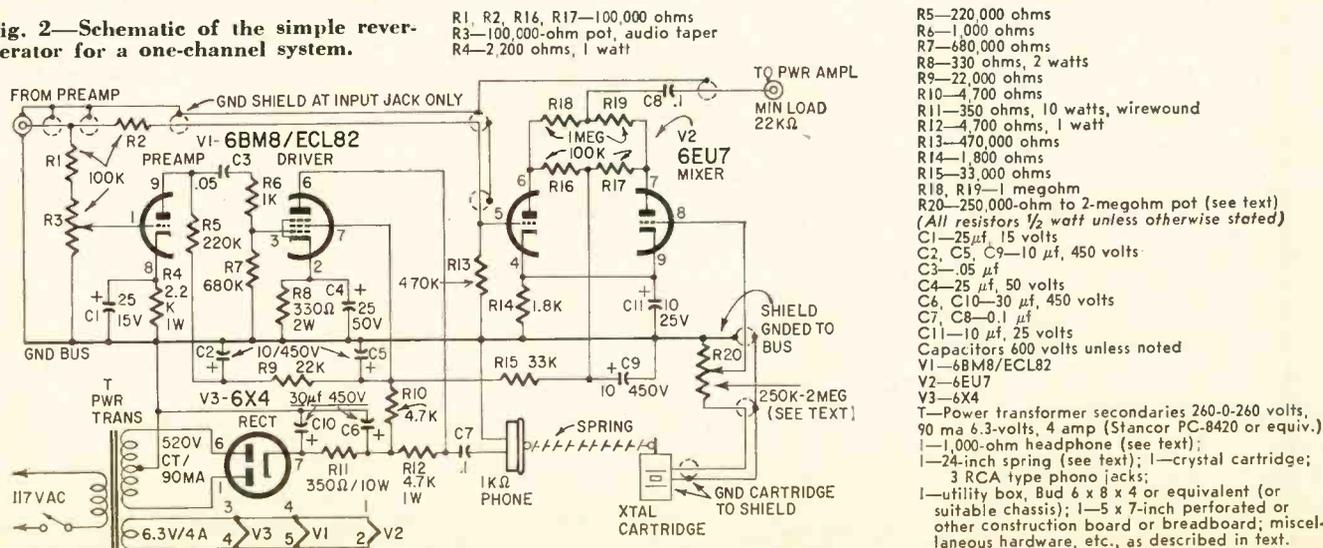

wound, one coil turn touching the other, with an overall length of 24 inches. The spring was held tightly in a vise and stretched until the turns were slightly separated one from the other. Later, in refining the operation of the unit, I found it advantageous to spread the first two inches (from the phone) of the spring so that the coils were about 1/16 inch apart. This seemed to decrease the sensitiveness of the unit to room and floor vibrations.

The phone should be mounted at one end of the box near the bottom while the other end of the spring passes through the grommet near the top of the other end so that the spring is suspended at about a 20° angle from the horizontal. This is necessary, as are the damper block and the shock-mounting of the cartridge support, to prevent the spring from responding to every footstep or vibration in the room.

So constructed (Fig. 3), ordinary walking and passing outside traffic will not noticeably affect the vibrations of the spring or the operation of the unit. It can be placed at almost any convenient place for operation, except on top of a speaker cabinet.

In my experimental work several types of cartridges were used to pick up the vibrations of the spring and convert them again into an electrical signal. In actual operation it was difficult to distinguish between one of the cheaper hi-fi crystal cartridges and a common crystal cartridge such as those used in one-tube portable record players. The more sensitive cartridge, however, seemed more prone to respond to extraneous noises which affected the spring. Because of this, and since fidelity is not of primary


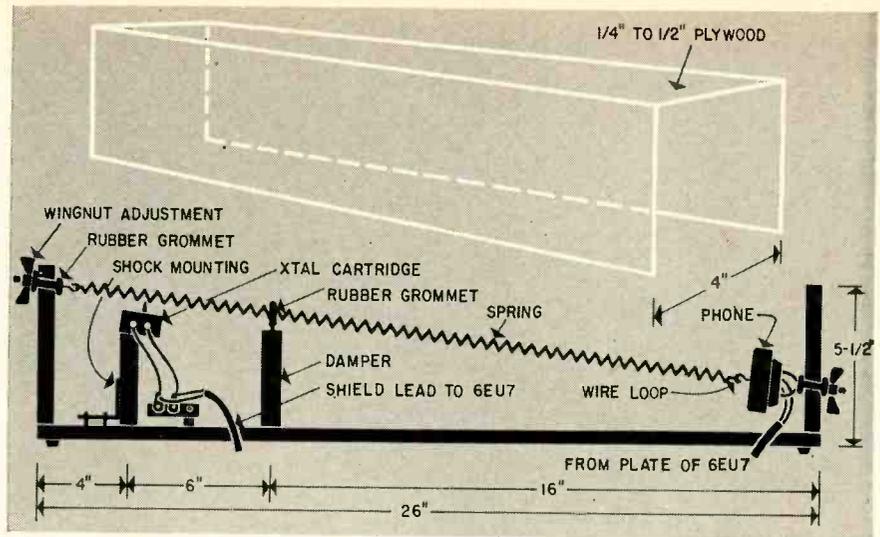


Fig. 3—Time-delay unit—construction detail.

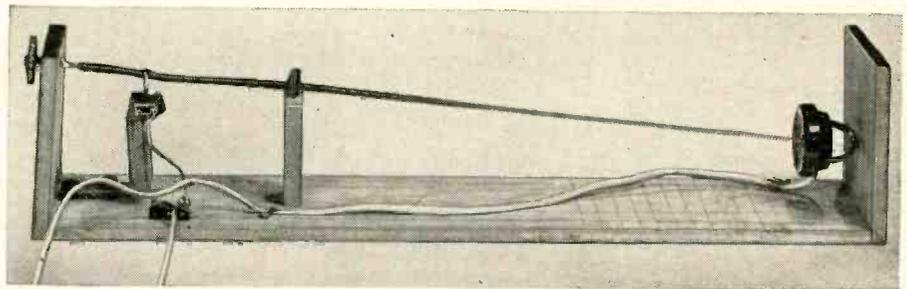

The completed unit on its wood frame.

concern here, I use in my unit an As-tatic model L-12U. It has a response from 50 to 5,000 cycles, and produces a voltage output of slightly more than

1/2 volt rms at a 1,000-cycle note input at room listening level—more than enough to feed the mixer grid and produce a desirable amount of reverberation.

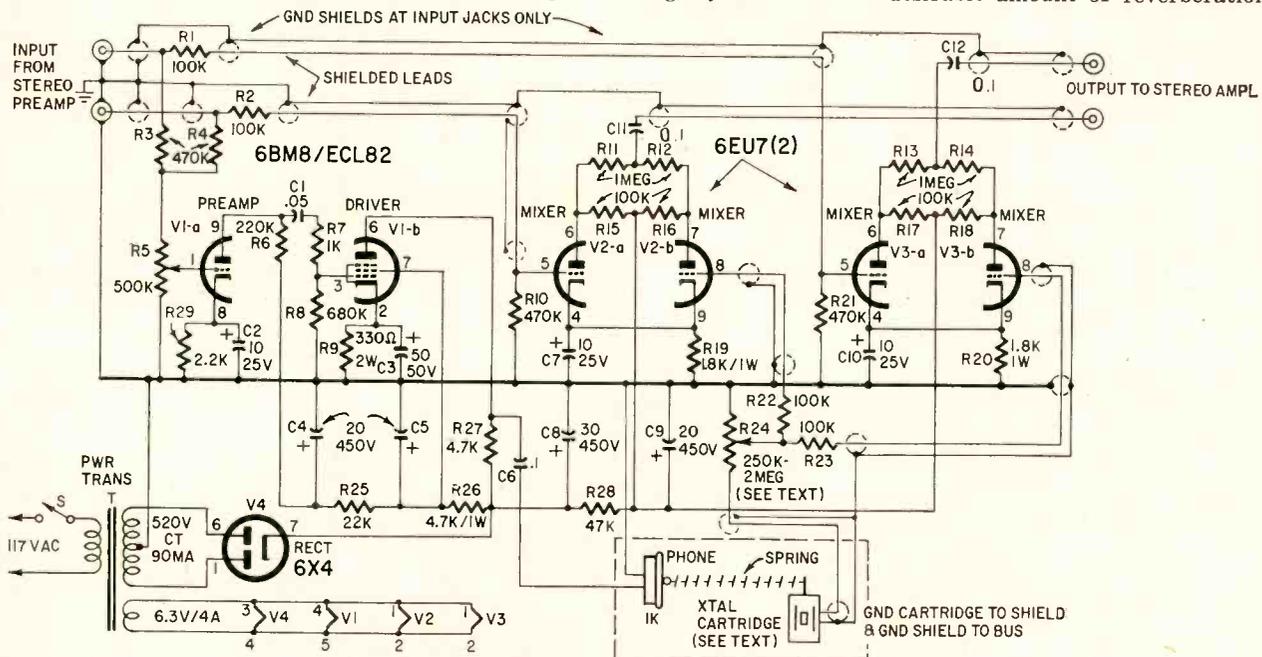


Fig. 4—A simple stereo reverberator unit.

- R1, R2, R15, R16, R17, R18, R22, R23—100,000 ohms
- R3, R4—470,000 ohms
- R5—500,000-ohm pot, audio taper
- R6—220,000 ohms
- R7—1,000 ohms
- R8—680,000 ohms
- R9—330 ohms, 2 watts
- R10, R21—470,000 ohms
- R11, R12, R13, R14—1 megohm
- R19, R20—1,800 ohms, 1 watt
- R24—250,000 ohms to 2-megohm pot (see text)
- R25—22,000 ohms
- R26—4,700 ohms, 1 watt
- R27—4,700 ohms
- R28—47,000 ohms
- R29—2,200 ohms, 1 watt

- (All resistors 1/2 watt unless otherwise stated)
- C1—.05  $\mu$ f
- C2—10  $\mu$ f, 25 volts
- C3—50  $\mu$ f, 50 volts
- C4, C5, C9—20  $\mu$ f, 450 volts
- C6, C11, C12—0.1  $\mu$ f
- C7, C10—10  $\mu$ f, 25 volts
- C8—30  $\mu$ f, 450 volts

Capacitors 600 volts unless noted.

- V1—6BM8/ECL82
- V2, V3—6EU7
- V4—6X4
- T1—Power transformer; primary, 117 volts secondary, 260-0-260 volts, 90 ma (Stancor PC-8420 or equivalent)
- I—24-inch coil spring, 3/16-inch inside coil diameter, No. 30 steel wire (see text)
- 1,000-ohm headphone, crystal cartridge, chassis, paneling, hardware, etc.
- 4—RCA type phono jacks



How the spring is attached to a ceramic cartridge. Damper block is also shown.

A cartridge like the Astatic model L-12U may be attached to the spring with a short piece of No. 18 solid hookup wire, soldered to the spring. Stiffen it somewhat by coating it thinly with solder, then insert it into the needle socket and secure it with the thumbscrew at the front of the cartridge. However, when using one of the high-fidelity crystal or ceramic cartridges, the spring may be affixed to the cartridge with an old discarded stylus of the spade variety (one that has a little spade or Y at one end by which it is intended to be mounted in the cartridge). This stylus can then be soldered to the spring in such a manner as to permit the stylus "Y" to fit snugly over the damper block in the cartridge (see the photo above). Be careful that the Y fits snugly over the damper block—a loose fit will affect the operation of the unit.

Mount the crystal cartridge on a block, about 4 inches from the inside of the end of the box, at right angles to the spring (so the needle will move laterally in line with the spring) and at a plane angle corresponding to the angle of the spring (in relation to the horizontal). The block should be shock-mounted. This can be done by attaching it to the base of the box with a metal 2-inch angle iron, mounted to the base of the box through two rubber grommets. The value of the reverberation control (R20 and R24 in mono and stereo versions, respectively) is selected for optimum load on the cartridge. The nominal value is around 1 megohm.

A damper block is optional, depending upon where the unit will be placed in operation. If it is subjected to much external vibration, it is well to insert the damper. It is made from a wooden block

(size is unimportant) on which there is a small rubber grommet through which the spring will pass. It should be so positioned that it has a stabilizing effect but exerts no perceptible tension upon the spring, and should be located about two-thirds to three-fourths the distance up the spring from the headphone. Some experiment may be needed before it is affixed to the base of the box permanently. Since my unit was designed for a bookcase installation, the damper was found necessary and was positioned 9 inches from the headphone. It works very satisfactorily there.


The box containing the delay part of the reverb unit (the headphone, spring and pickup cartridge) should also be mounted on rubber feet, and may be finished, painted or veneered, or left unfinished as desired. It may be constructed entirely of ½-inch plywood, or the top may be constructed of either ½-

or ¾-inch plywood, as convenient.

As stated earlier, the unit may be modified for stereo. For the purist, the correct approach would be to construct two identical units, each with its own spring, and insert one in each channel. The method shown in Fig. 4 has the advantage that the period of reverberation will be the same on each channel, and is recommended.

In Fig. 4 a portion of the stereo input signal is tapped off through R3 and R4 and mixed on the grid of V1-a. The mixed stereo output of the delay line is fed to the grids of V2-b and V3-b. After amplification, it is combined with the undelayed stereo signals in the resistive matrix networks in the plate circuits of V2 and V3. Now, the output of each channel has mixed with it a delayed or reverberated sum signal whose amplitude is set by the reverberation control. **END**

## handy drill holder

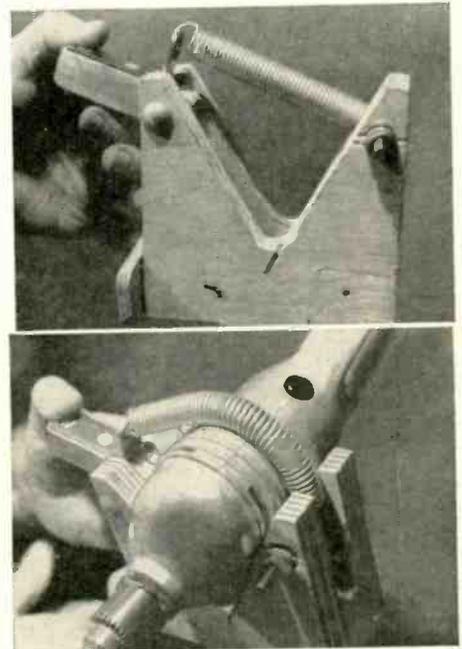

The ¼-inch utility electric drill often serves as a vise-held grinder and sander. This extremely versatile tool makes light work of grinding chores and would probably be used more often if it were possible to hold it securely in the small vises usually found in many shops. To make this possible, a drill-holder accessory is needed since the jaws of most vises are not deep or wide enough to hold the drill.

Such a holder, with a quick-change feature can be readily made with a few pieces of scrap plywood. Saw a deep V in two blocks of ¾-inch plywood. The blocks should be a little wider than your drill and perhaps a foot long. Below the bottom of the V, separate the two blocks with a smaller one; then nail all three together. Now saw out the bottom half of the block to make a rough Y. To hold the electric drill, fasten a fairly heavy coil spring to one side of the V with a bolt. Hook the

other end of the spring into a small angle bracket which, in turn, is fastened to another small block of plywood. This block, which serves as a clamp-tightening trigger, is pivoted on the other side of the V. This completes the holder except for a small turn block at the base of the V to hold the trigger when the drill is centered in the V. The holder eliminates the need for a vise to hold the drill since it can be clamped or screwed directly to the work bench. It is readily portable and can be used on a job away from the shop by clamping it to any convenient upright.

Another advantage is that the drill can be clamped securely in the holder in a matter of seconds and removed just as quickly. It holds a heavy drill securely and will not damage the drill housing in any way. The device, of course, can be clamped in any vise, however small. If desired, it can be sanded and painted. —Glen F. Stillwell

# BUILD



## ELECTRONIC MICROMETER

By DAVE STONE

The electronic micrometer determines wire gauge sizes from No. 10 to No. 40; measures chassis, panel or metal stock thickness from 1 mil (.001 inch) to about 250 mils (0.250 inch); measures the diameters of resistor or capacitor leads to obtain hole drilling size for printed-circuit boards, and measures rod, dowel and machine-screw diameters.

It can also be used for unusual measurements like determining the thickness of paper or mica dielectric in capacitors, the thickness of a coat of paint on a panel or the thickness of paper insulation, to name a few.

This electronic counterpart of the standard machinist's micrometer is assembled from readily available parts and only ordinary hand tools are needed. Its overall accuracy depends upon the size of the meter and how carefully it is calibrated. A large meter with many scale divisions allows closer calibration and greater accuracy. The 2½-inch meter in the unit shown in the photographs is adequate for most electronic applications.

### Operating principles

The electronic micrometer operates upon well known transformer principles. An iron-core filament transformer has a core made up of E- and I-laminations. The layer-wound winding is placed over the center E-lamination arm (Fig. 1).

The I-laminations complete the magnetic flux path after the winding is assembled. If they are removed, the induced secondary current drops considerably because the magnetic flux path is open. If the I-laminations are deliberately moved in or out, secondary current will increase or decrease in proportion to the spacing between the I-laminations and the E-lamination core.

The thickness of the material to be measured determines the spacing between the two lamination stacks. The resulting secondary current is rectified by a germanium diode and fed to the indicating meter. The usual stack of I-

laminations is replaced by a solid iron block of equal size. A bracket and metal rod (Fig. 2) support the block and permit it to be moved toward or away from the E-lamination stack.


An extension arm fastened to the metal rod holds a flat, ground-down bolt head. This is used as a measuring surface. An identical ground-down bolt is fastened to the chassis directly below the extension arm's measuring surface. These measuring surfaces correspond to the two flat surfaces of a machinist's micrometer. The material to be measured is placed between the flat surfaces. The combination extension arm and I-block is then lowered to contact the material and the meter indicates the thickness.

### Mechanical construction

The core of the filament transformer used in this unit consists of alternately arranged E- and I-laminations. It must be taken apart to rearrange the E-laminations in one direction, and to remove and discard the I-laminations. Cut off the small metal fingers that hold the

core in the U-shaped mounting strap and slide the core assembly out. Removing the laminations will be slightly difficult at first as they are tightly stacked and often varnish-impregnated. [Most medium-grade transformers are put together with two or three E-laminations in one direction, capped with an equal number of I-laminations, the same number in the other direction, and so on. A good way to remove the laminations is to knock out the center group of I-laminations with a screwdriver or small piece of strap iron or steel and a mallet or hammer. Then put the transformer on a vise with the jaws slightly open so that the center E-laminations are over the gap, and drive the E-laminations out with the strap-iron delaminating tool and hammer. Tap carefully and not too hard, and be sure the laminations are going out straight.—*Editor*] Tap the core frequently to loosen the varnish and try not to bend the laminations. The rest of the job becomes considerably easier once the first few laminations are removed.

After the laminations are pulled

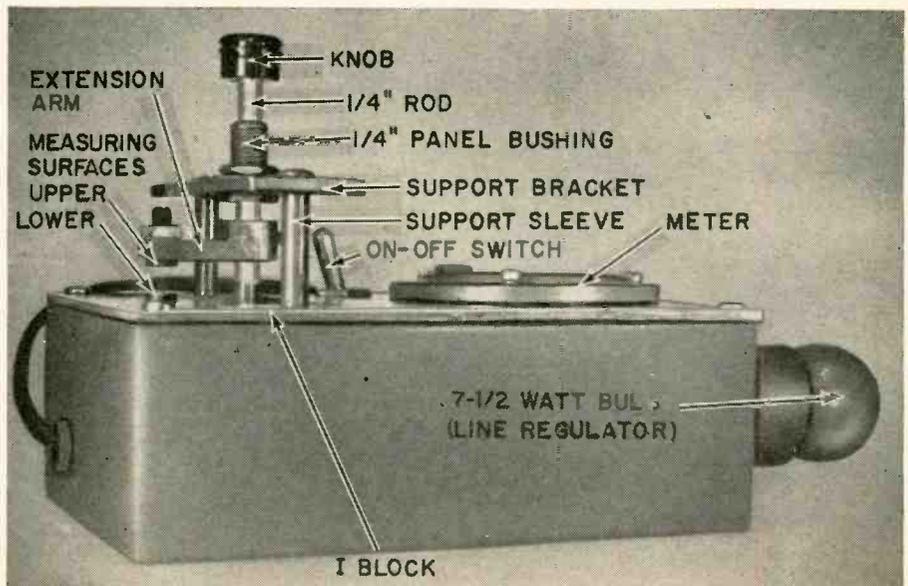

Side view shows details of the mechanical portion.

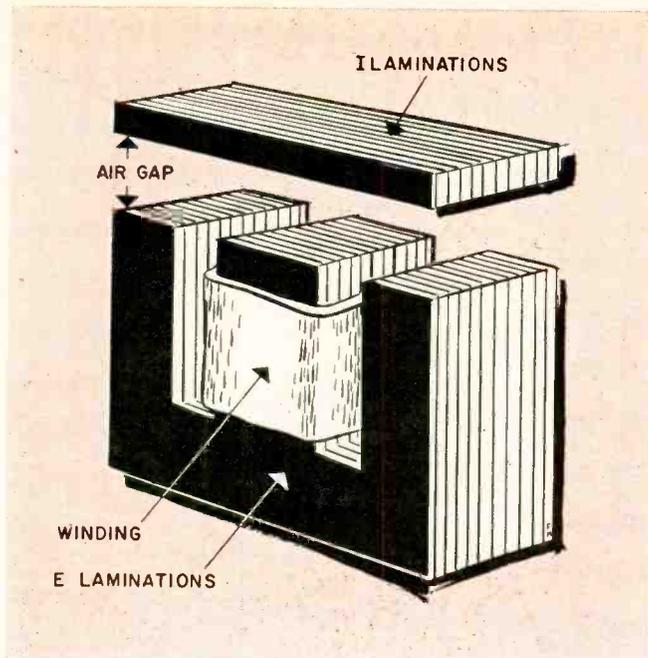


Fig. 1—Transformer core assembly.

apart, reassemble the E-laminations all in one direction. Put the stack back into the mounting strap without the I-laminations. Tap the face of the E-stack to drive it as far as possible into the mounting strap, and to make sure all the laminations are lined up to provide a flat surface. Drill a small hole through the strap and lamination stack on both sides and fasten tightly with a nut and bolt (Fig. 2).

Cut a 1-1/6 x 2-5/16-inch rectangular hole in the chassis and drill the mounting holes to mount the transformer temporarily directly beneath the opening. The I-block will pass through the opening and into the space left above the E-stack face. It should fit snugly, without binding, and lay flat on the core's face. Measure the exact center of the I-block and drill and tap for a 1/4-20 thread.

Drill a 3/8-inch hole in the exact center of the support bracket and mount the panel bushing. Cut three or four 1/4-20 threads on one end of a 2 1/2 inch long, 1/4-inch diameter brass or aluminum rod. Thread it into the I-block and tighten. File away any excess rod material that projects past the lower face of the block.

Fasten the extension arm firmly to the rod, fasten the threaded sleeves to the support bracket, insert the rod in the panel bushing and assemble it all to the chassis. The transformer's mounting bolts go through the chassis into the bottom end of the threaded sleeves to support the entire assembly rigidly.

Place the winding back on the middle E-core arm and install the lower measuring-surface bolt on the chassis directly below the extension-arm measuring surface before final assembly.

### Electronic construction

The 5-volt transformer winding is connected to the 117-volt ac line through

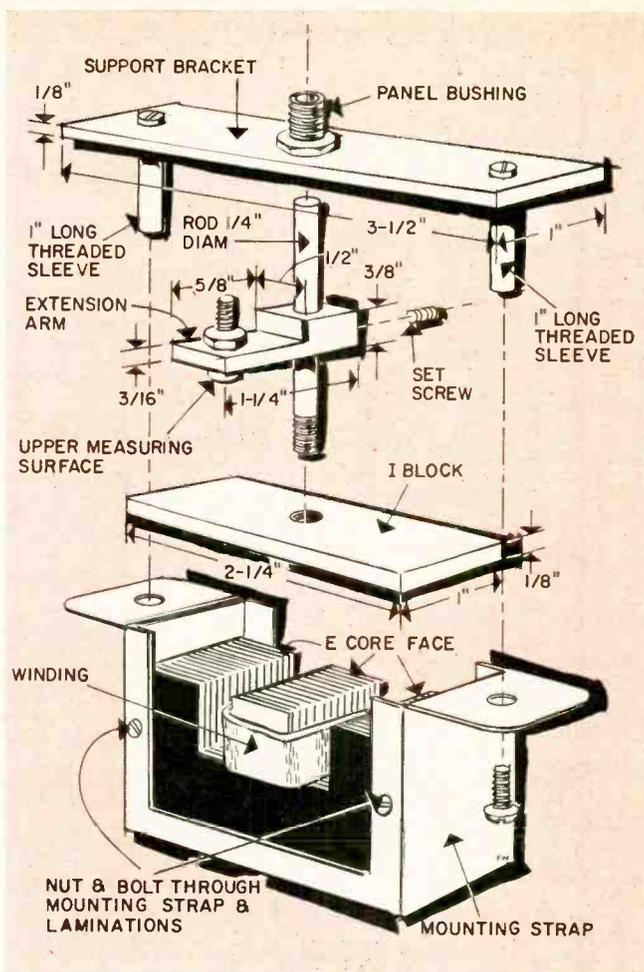


Fig. 2—Mechanical assembly of the micrometer.

a 7 1/2-watt 120-volt lamp bulb (Fig. 3). The lamp operates as a dropping and ballast resistor to regulate the line voltage input. Output from the transformer's 117-volt winding is rectified by a 1N69A diode and fed to a 1-ma meter. A variable shunt, potentiometer R2, is placed across the meter for calibration.

There is nothing critical about the layout of the electronic circuitry. Any standard diode may be used for the rectifier and the unit will work well with any standard 1-ma meter. Drill a hole in the case for access to the screwdriver adjustment of the calibrating potentiometer.

### Calibration and use

Loosen the setscrew on the extension arm and slide the I-block into the transformer mounting strap so that it fits

flush against the E-core face. Plug the unit into the 117-volt line and watch the meter. If the electronic micrometer has been wired correctly, the reading will be almost full scale. Adjust for full-scale deflection with R2 to obtain the zero thickness setting.

Position the upper measuring surface on top of the lower measuring surface and set for a snug contact between the two. Make sure the I-block is resting flat against the E-core face and the measuring surfaces contact each other without strain. Tighten the extension-arm setscrew and the unit is ready for calibration.

An inexpensive feeler gauge from the local auto supply store is used to calibrate the electronic micrometer. It starts with a 2-mil (.002-inch) gauge and goes up to about 250 mils with various combinations of the gauging strips.


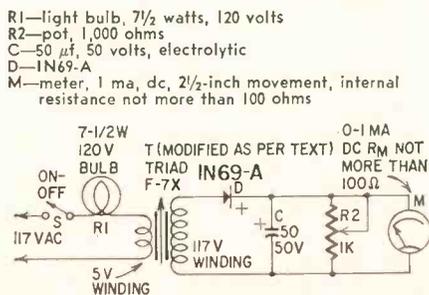


Fig. 3—Simple electronic circuit depends on a variable transformer.

- R1—light bulb, 7 1/2 watts, 120 volts
- R2—pot, 1,000 ohms
- C—50  $\mu$ f, 50 volts, electrolytic
- D—1N69-A
- M—meter, 1 ma, dc, 2 1/2-inch movement, internal resistance not more than 100 ohms

- S—spst, toggle switch
- T—filament transformer: primary, 117 volts; secondary, 5 volts (Triad F-7X)
- I—block, mild steel or iron, 1/8 inch thick, 2 1/4 x 1 inch
- Support bracket, aluminum or brass, 1/8 inch thick, 3 1/2 x 1 inch
- Extension arm, aluminum or brass block, 1/2 inch square, 1 1/4 inches long, cut down as shown
- Rod, aluminum or brass, 1/4 inch diameter, 3 inches long
- Threaded sleeves, standard hardware item, 1 inch long, tapped for 6-32 screws (2)
- Panel bushing, 1/4 inch, standard hardware item
- Measuring surfaces, hex-head bolts with heads ground down to flat surface (2)
- Case to suit
- Miscellaneous hardware

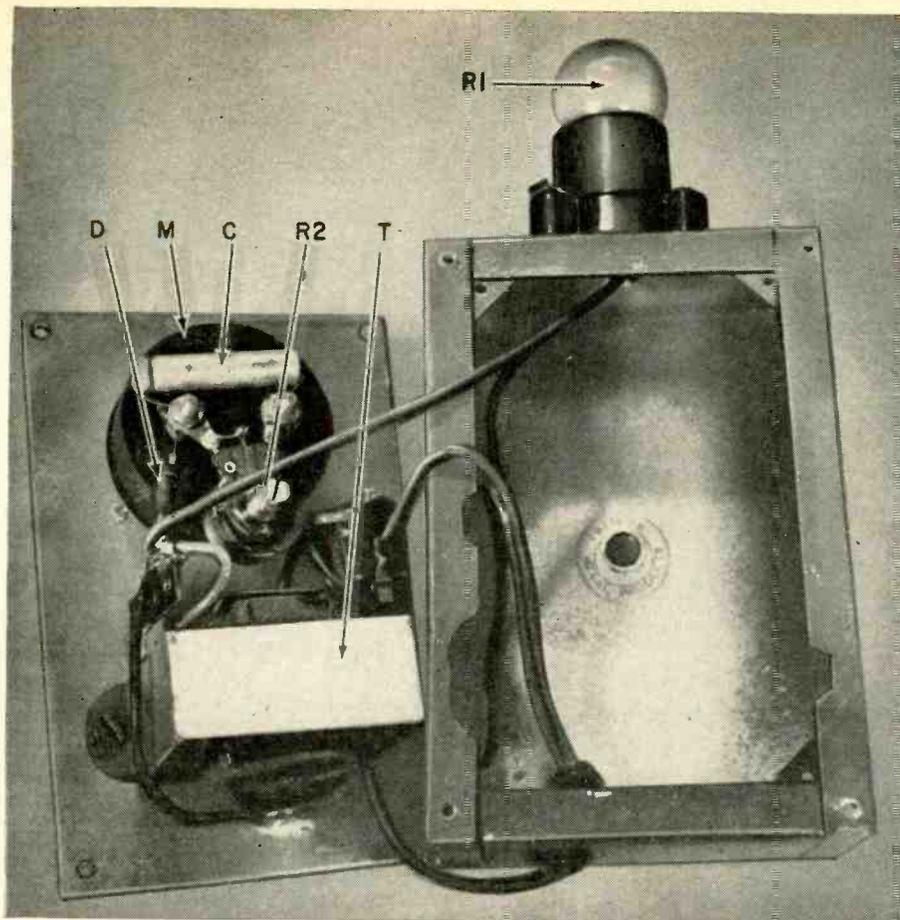

Parts layout inside the instrument.

Obtain a piece of flat aluminum foil from the kitchen to calibrate the 1-mil setting. Most flat varieties of aluminum foil are 1 mil thick.

Raise the rod, place the foil on the lower measuring surface, lower the rod to contact the foil with the upper measuring surface with slight pressure and record the reading. Repeat with the 2-mil feeler gauge and so on, for as many thicknesses desired to obtain a meter reading thickness chart.

Note that, above 60 mils or so, the meter readings decrease slowly for relatively large increases in thicknesses. This is no disadvantage for general measurements, but if greater accuracy is desired, use a larger meter with more divisions.

It is easy to use the electronic micrometer for measuring an unknown thickness or diameter. Place the material (metal stock, wire, plastic, paper, etc.) on the lower measuring surface and lower the rod until the upper measuring surface bears down upon the material. Rock the material slightly to insure that it is perfectly flat between the two surfaces, and read the meter. Refer the meter reading to the chart to obtain the material's thickness or diameter.

To measure the thickness of a coat of paint on a panel, first measure the bare panel's thickness and jot the reading down, then apply the paint. When dry, measure the thickness again and obtain the paint thickness from the difference between the first and second readings.

The calibration should be checked occasionally if the line voltage is known

to vary considerably, by lowering the I-block to the E-core face. You should read zero thickness—full-scale deflection. Normally, it will not be necessary to readjust the calibrating potentiometer for long periods of time, for the regulating lamp does a good job.

The electronic micrometer is very useful for rapid measurement of many pieces of material and the meter is much easier to read than the barrel of a machinist's micrometer. It is easy to assemble, fun to construct and the end result is a useful measuring instrument. END

***Because of the complete report on 1962 TV in this issue we have been forced to leave out the Service Clinic this month. It will be with us again in the February issue and with a bigger-than-usual installment***



## attention technicians



With this issue RADIO-ELECTRONICS is starting a special feature aimed to help speed your service work. The page to the right is actually an 8-page booklet of tube basings for the 1960 and 1961 Admiral TV receivers. A new booklet will appear each month. Each one will cover a different make of TV receiver. When clipped together you will have a complete guide to tube layouts that will easily fit into your tube caddy.


To put your booklet together, cut out the page. Fold the top down and back, keeping the cover facing you. Then fold from left to right on the line marked *fold here*, keeping the cover facing you. Staple the booklet along the left hand edge. Now run a sharp knife or razor blade along the closed top and you're finished. You now have a useful piece of service information, exclusive with RADIO-ELECTRONICS.

If you have any comments on this booklet or suggestions for other subjects that might be covered in the same format, send them to Booklet Editor, Radio-Electronics, 154 West 14 Street, New York 11, N.Y.





- 3
- |                                       |                               |           |
|---------------------------------------|-------------------------------|-----------|
| V501-5U4GB                            | V401-6B8U                     | V202-6A5S |
| V406-1G3GT                            | V305-23AHP4                   | V201-6DT6 |
| V405-6DQ6A or<br>6AX4GTA/GTB          | V304-6AW8A<br>(Crystal Diode) | or 6CG8A  |
| V404-6DQ6A                            | V303-1N87A                    | V102-6CG8 |
| V403-6CG7                             | CR301-1N87 or                 | V702 or   |
| V402-6DE7                             | V302-6BZ6                     | in 20K7B  |
| CR401-93B5-6<br>(Dual Selenium Diode) | V301-6BZ6                     | V101-6CY5 |
|                                       |                               | in 20K7   |
|                                       |                               | V701-6FH5 |

CHASSIS 20K7, B

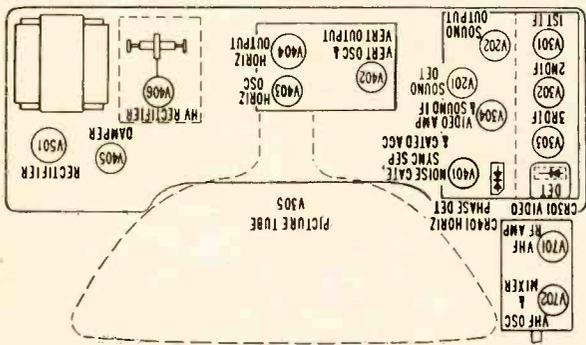

- 6
- |                                       |                               |           |
|---------------------------------------|-------------------------------|-----------|
| V501-5U4GB                            | V401-6B8U                     | V202-6A5S |
| V406-1G3GT                            | V305-23AHP4                   | V201-6DT6 |
| V405-6DQ6A or<br>6AX4GTA/GTB          | V304-6AW8A<br>(Crystal Diode) | or 6CG8A  |
| V404-6DQ6A                            | V303-1N87A                    | V102-6CG8 |
| V403-6CG7                             | CR301-1N87 or                 | V702 or   |
| V402-6DE7                             | V302-6BZ6                     | in 20K7B  |
| CR401-93B5-6<br>(Dual Selenium Diode) | V301-6BZ6                     | V101-6CY5 |
|                                       |                               | in 20K7   |
|                                       |                               | V701-6FH5 |


CHASSIS 18B7, B

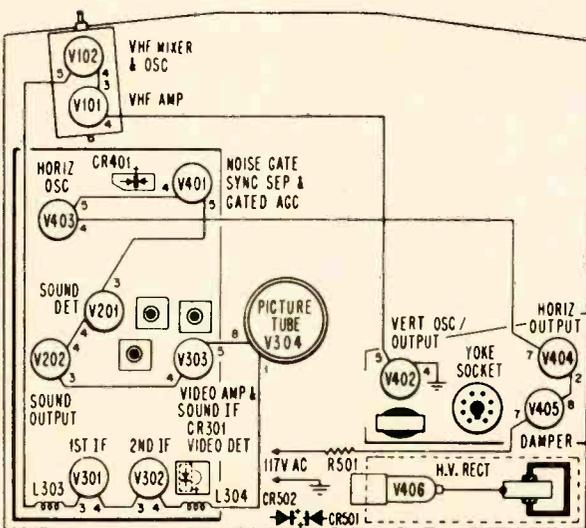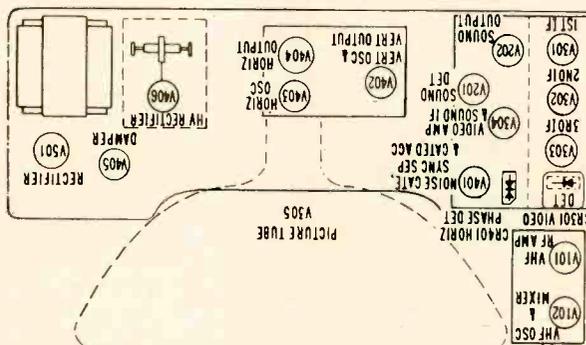

CHASSIS 15G1B

- |            |             |                        |
|------------|-------------|------------------------|
| V101-2CY5  | V303-6AW8A  | V405-12AX4GTA/B        |
| V102-5CG8  | V304-19XP4  | V406-1G3GT or<br>1K3GT |
| V201-3DT6  | V401-3B8U   | CR301-1N87 or<br>1N87A |
| V202-12CU5 | V402-10DE7  | CR401-93B5-6           |
| V301-3BZ6  | V403-6CG7   | CR501-93B12-1          |
| V302-3DK6  | V404-12DQ6A | CR502-93B12-1          |

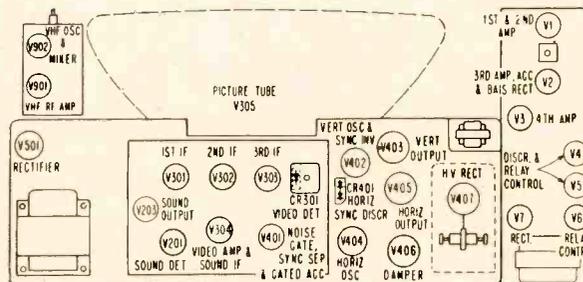Series string wiring is shown including pin numbers.



CHASSIS 20M6

- |           |                        |                       |
|-----------|------------------------|-----------------------|
| V1-12AX7  | V303-6CB6              | V403-6EM5             |
| V2-6AV6   | CR301-1N87 or<br>1N87A | V404-6CG7             |
| V3-6AU6   | V405-6DQ6A             | V406-6AU4GTA          |
| V4-6B8    | (Crystal Diode)        | V407-1G3GT            |
| V5-6B8    | V304-6AW8A             | V501-5U4GB            |
| V6-6CG7   | V305-23CP4,            | V901-6ER5             |
| V7-6X4    | 23GP4 or<br>23HP4      | V902-6CG8<br>or 6CG8A |
| V201-6DT6 | V401-6B8U              |                       |
| V2-6A5S   | CR401-93B5-4           |                       |
| V301-6BZ6 | V402-6CG7              |                       |

# MODERN AUDIO EXPANSION

By WARREN ROY

NO HI-FI SYSTEM CAN PRODUCE BETTER sound than that on the record being played. And a record must fall short of containing the full dynamic range of a concert orchestra—by many db. It just isn't possible to cut such a range on any practical stereo record. But the record manufacturer must still get all the music on the record, and does so by compressing the high-amplitude sections so they fit within the existing restrictions.

In an attempt to restore the full audio range, the hi-fi owner has resorted to several devices, labeled expanders, to restore the normal range of the orchestra. The earliest ones used ordinary light bulbs, connected across the amplifier output. On loud passages, more current passes through the bulb and its filament heats up. As it heats, its resistance increases and the volume of the passage being played rises.

But light bulbs are comparatively bulky and difficult to handle. Also, they do not have the particular resistance-voltage characteristics that make a good expander. However, some audiophiles are still using this basic type of expansion circuit.

Now there is a new device available to do this job. It carries the name Componder, is made by Fairchild, and is designed to work with modern stereo hi-fi systems. Unlike the simple light-bulb arrangements, it does two jobs—expansion and compression. The light bulbs have been replaced with much more modern devices too—cadmium sulfide photocells. These units, actually semiconductor devices, have a resistance characteristic that changes in direct



The Fairchild Componder.

## Adds 6 db to the dynamic range of your records

proportion to the amount of light applied to them, and are designed specifically for this particular use.

There are four neon lamps on the Componder's front panel. They are connected to the outputs of the stereo amplifier, two for each channel. The intensity of the lights, therefore, is in direct proportion to the amplifier output. These lights are placed so they illuminate the cadmium sulfide resistors. As the lamps increase in brightness, the resistance of the cadmium sulfide units goes down.

Volume expansion occurs because the variable resistance cadmium sulfide resistors are part of a signal voltage divider. The divider is placed in series with the signal by connecting the Componder either between the cartridge and preamp input (Fig. 1) or between the preamp output and the amplifier input (Fig. 2). For compression they are placed across the input circuit.

The four lamps serve another purpose too. They let the user see just what the Componder is doing. Watch them with the Componder switched out of the circuit while a particular passage is played. Then switch the unit into the circuit and play the same passage again. The action will be obvious.

The lights are also handy for setting the dynamic sensing control that selects the point at which expansion or compression begins. You'll find that your eyes are much more sensitive to slight changes in light level than your ears are to minor changes in audio level. Because of this the lights show you just when the Componder begins to do its stuff and you can set it to the exact point desired.

As mentioned earlier, there are two lights for each channel. One lamp of each pair is marked HI and the other LO. During normal music passages only the LO light will flicker. As volume increases and the Componder goes into action, the HI light will flicker too.

It is usually more convenient to use the Componder between the preamp and amplifier. It then affects whatever music source you are using. It will be especially welcome for AM radio. Of course, if you are using an integrated amplifier you will have to connect the Componder between the cartridge and preamp.

When normal program material is being played, the Componder drops the unexpanded amplitude by 6 db. This is compensated for by turning up the amplifier level control to restore the normal listening level. Now when a loud passage comes through, the added voltage across the resistors causes them to decrease in value, thereby boosting the loud passage by as much as 6 db, depending upon the original level of the passage.

There is even a little boost on quiet passages, but it is so slight that increase cannot be heard by the average person. The user sets the exact point at which the boost begins by adjusting two front-panel DYNAMIC SENSING controls—one for each stereo channel.

When used as a compressor, the Componder works in reverse. Now it knocks all the peaks off the music so it comes through at a constant level. This is especially useful for music systems in restaurants or business locations, or wherever only background-type music is desired. END

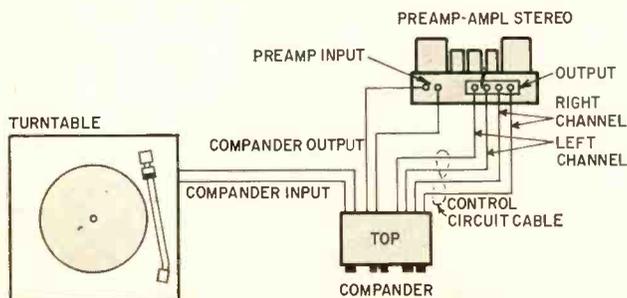


Fig. 1—Block diagram shows how Componder is connected between the phono cartridge and the preamp input.


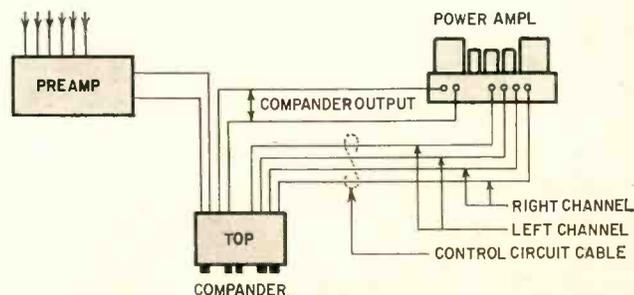


Fig. 2—If you have a separate preamp and amplifier you can connect the Componder between them.

# END AUTO RADIO INTERFERENCE

INSTALLATION ON HIGH-TENSION COIL

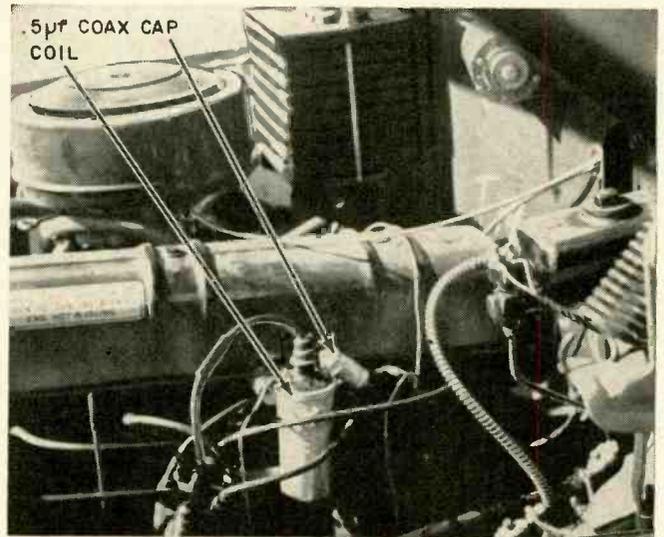

Typical noise-stopping coax capacitor installation on high-tension coil.

*Protect mobile radio receivers against interference at all frequencies from below the broadcast band to 1,000 mc*

By D. GIFFORD

THE MAIN SOURCES OF AUTOMOTIVE RADIO interference are the generator, the voltage regulator and the ignition system. The heater fan motor, electric windshield wiper motor and gas gauge also cause trouble at times.

The degree of suppression required depends on the frequency or band of frequencies covered by the radio installation and the intensity of the interference. The suppression described here is effective from below the broadcast band through to 1,000 mc. It is especially useful for Citizens-band installations.

Before applying suppression techniques to any unit of the vehicle, it must be properly adjusted and in normal operating condition. Otherwise your efforts may be in vain and the suppression could conceivably aggravate any abnormal condition of the unit.

Radio interference from the generator can be stopped with a 0.5 µf coaxial capacitor (Sprague 48P18 is ideal).

It is readily mounted on the end of the generator. Clean the area thoroughly (removing the paint) from the spot where the capacitor is to be mounted to get a good rf bond between the capacitor case and the generator housing. Remove the lead attached to the armature terminal of the generator and connect it to the output side of the coaxial capacitor (the side farthest from the generator armature terminal). Connect the other end of the capacitor to the armature terminal with a short direct lead. Should a capacitor already be connected to the armature terminal, it is probably a pigtail type. Remove it completely.

This suppression is so effective that interference from the voltage regulator that was hidden by the generator interference can be heard.


Regulator interference may occur at engine idle speed or at the point where the relay begins to chatter. If your car has an ammeter, you can spot this point by watching the quivering motion of the ammeter needle.

The point at which this interference occurs depends on several things—the condition of the battery, the idle rpm of the engine, and the generator output. Mount a 0.5-µf (Sprague 48P18) coaxial capacitor under one of the regulator mounting screws. Remove the lead from the battery terminal of the voltage regulator and connect it to the end of the capacitor farthest from the regulator. Connect the other end of the capacitor to the battery terminal

of the voltage regulator with a short direct lead.


If you have a "hot" receiver installation and still have some regulator interference at 9 to 14 mc and at the second harmonic of these frequencies, install a small mica capacitor from the field terminal of the regulator to the regulator case. The capacitance of this mica capacitor depends on the frequency or frequencies affected and is determined experimentally. If there is a pigtail type capacitor already on the regulator, remove it.

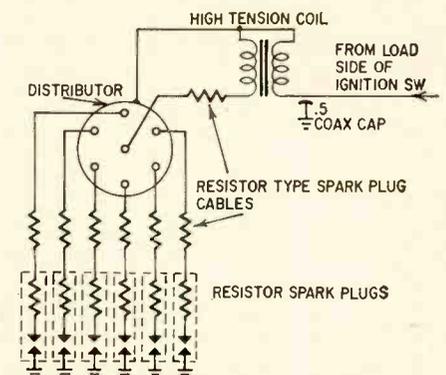Automotive manufacturers do not recommend connecting capacitors to the field circuits of the regulator or the generator. However, in my more than



Resistor spark plugs, resistance spark-plug cables and a 0.5-µf coax capacitor at the high-tension coil will stop ignition noise.

## ON GENERATOR ARMATURE

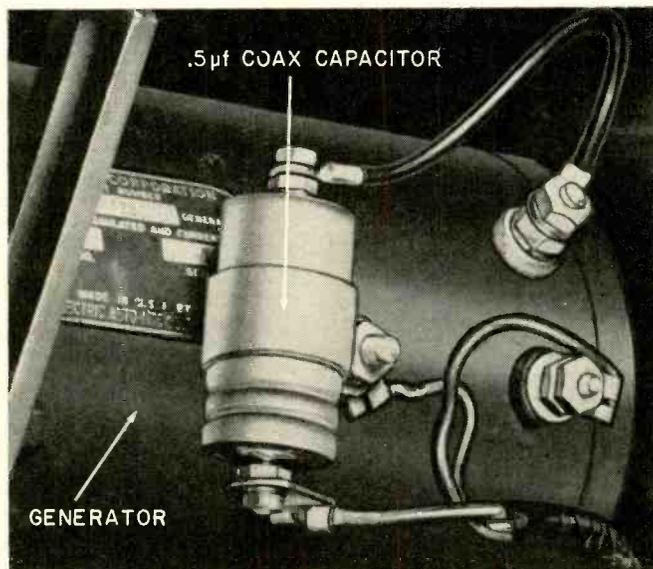

Coax capacitor connected at generator armature quiets that noise maker.

## ON VOLTAGE REGULATOR



Motorola photos

To silence the voltage regulator, you'll need some more coax capacitors.

24 years' experience with interference suppression, I have yet to learn of a case where these capacitors have caused trouble or have been detrimental in any way to the operation of the regulator or the generator.

Ignition interference is another nuisance that must be dealt with. Unlike regulator or generator interference, it varies from car to car of the same make and model as well as from make to make. V8 engines are among the worst offenders. The place to start is at the spark plugs. If they are the standard type, replace them with resistor type plugs. Check the gap. It should be smaller than for standard plugs. I set the gap about .010 inch less than for standard plugs. Measure the resistance of the resistor plugs—they should be 10,000 ohms; some run as low as 6,000 ohms.

Replace the spark-plug cables, includ-

ing the high-tension cable, with resistor type cable (4,000 ohms per foot). This may reduce your gas mileage slightly and prevent you from taking off like a rocket, but, if the engine is properly timed and tuned, it will present no great hardship and ignition interference will be greatly reduced if not eliminated. A 0.5- $\mu$ f coaxial capacitor (Sprague 48P18) on the high-tension coil battery terminal will help considerably at some frequencies.

If ignition interference is still objectionable, check the distributor rotor. If it has an aluminum contact bar, replace it with one that has a copper contact bar. This will reduce interference 10 db or more. The copper contact rotor will last much longer, too, as it will not burn or corrode as readily as the aluminum type. It also gives a cleaner spark.

Shielding the distributor cap will reduce the interference another 10 or 12 db at some frequencies, depending on make and model of the car. A simple and economical way of doing this is to cement aluminum foil around the body of the cap, being sure to bring the foil down over the rim of the cap so it contacts the distributor housing when in place. Wrap a layer of plastic electrician's tape over the foil to protect it. Commercial shielding harnesses such as Hallett (Hallett Manufacturing Co., 5910 Bowcraft St., Los Angeles 16, Calif.) are available, but I am sure the suppression outlined in this article is adequate for most if not all radio installations.


One of the things we are apt to lose sight of in dealing with interference from an automobile is that a car is essentially a broadcast station—the engine and electrical system being the oscillator and the car body the antenna.

The hand-brake cable system of the 1959 and 1960 Studebaker Lark is a lovely rhombic at 48 or 49 mc. Use ½-inch copper braid and bond the brake cable on the right side of the car to the muffler tailpipe, then to the floor of the car body.

Most car bodies are poorly bonded, rf-wise, to the car frame. Use ½-inch copper braids to bond the body to the frame at strategic points—hood, trunk lid, etc.

At some frequencies it is better not to tie the antenna transmission-line shield to the car body or frame (remember, it is the interference radiator) as this only forms a loop and may cause more interference to be fed into the receiving equipment. This also applies to bonding the receiver chassis to the car body. If the equipment operates from the car battery, it is often better to run the power leads directly to the battery than to risk forming loops by depending on the receiver chassis and the car body to be thoroughly and directly connected to the battery. It may be good enough electrically but we are dealing with rf.

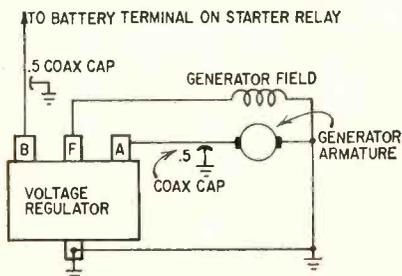Fundamentally, interference suppression simply creates a low-impedance path to ground for the rf at the source of the interference, ground being the electrical return of the source. END



Coax capacitors at the voltage regulator and generator stop interference caused by these units. B, F, & A are battery, field and armature terminals.

# SEEING IS BELIEVING

## IN CATHODE RESEARCH

*Largest electron-emission microscope replaces abstract theory with visible reality in search for better tube cathodes*

**COVER STORY**

**By Dr. AURELIUS SANDOR\***

IN THE EARLY DAYS OF THE ELECTRON-optical science (in the beginning of the '30's) I once respectfully called my professor, the famous H. Geiger of Geiger counter fame, to watch a demonstration of an oxide cathode in my laboratory. He came, and I pulled down the window shades with deep reverence. Out of the black nothingness the brilliant landscape of the "moon" appeared on the rather small phosphor screen of the cathode-ray tube, like a materializing ghost with craters, mares and criss-cross channels, brightly scintillating in their versatile texture.

But the dynamic changes of the electron emission pattern suggested more than just the topography of the moon, and the show took an even more dramatic turn when—induced by an increase in cathode-heater voltage—the craters gradually covered themselves with a dense veil and all sharp detail merged into a heavy, bright fog. The relaxed voice of the otherwise nervous professor, colored with a shade of sentimentality, was heard out of the dark: "Oh, my, Oh, my! Is this really possible?"

There was no doubt that Professor Geiger knew in all its implications the theory that was hiding behind those mirages, but he could not suppress the sincere voice of his relieved conscience, since somewhere, in a small corner of his great mind, he had not been so unconditionally sure of the reality behind that theory.

To me, as a young engineer-physicist, this was quite an experience and I still remember it with great respect everytime a new pattern of

similar astronomical quality appears on our new emission microscope screen, a pattern greatly emphasized by its present large size.

### Electron optics

The gadget used in the early demonstration was an early "electron emission microscope," a brother of the better known transmission electron microscope, but because of its different physics unfortunately inherently limited in resolving power. The principles of electron optics are abstract, but happily light optics offers analogies that help us to explain them. Both electron optics and the optics that uses

fields have to substitute for glass lenses; we find apertured anodes and in certain designs also magnetic coils.

The emission microscope developed in our General Telephone & Electronics Laboratories in Bayside, N. Y., represents a novel approach, conceived to conform with modern research requirements. Complicated electric fields develop in the electron gun, that also accommodates the exchangeable cathode to be viewed (Fig. 1). A first and a larger second magnetic coil (lenses) surrounding the tube neck represent the actual optical elements; this objective lens and this projection lens throw a true and magnified electronic image



The pattern on the tube face can be photographed together with other instruments showing the time, pertinent voltages and other information, for a permanent record.

glass lenses are based on the propagation of elementary masses which are related to electromagnetic waves. In light optics, one speaks of "photon masses" of wave character; in electron optics of "electron masses" also endowed with wave properties. The main difference between the two is that electrons are electrically charged and photons are not. So in electron optics specially shaped electric and magnetic

of the  $\frac{1}{8}$ -inch diameter cathode onto the full 21-inch phosphor screen. The phosphor radiates visible light from the points of impact, varying in shade according to the striking electron density.

Electron beams form images in the same way as light rays do. The focal length of electron-optically shaped fields can also be changed simply by changing the field strength value of the

\*General Telephone & Electronics Laboratories Inc., Bayside 60, N. Y.

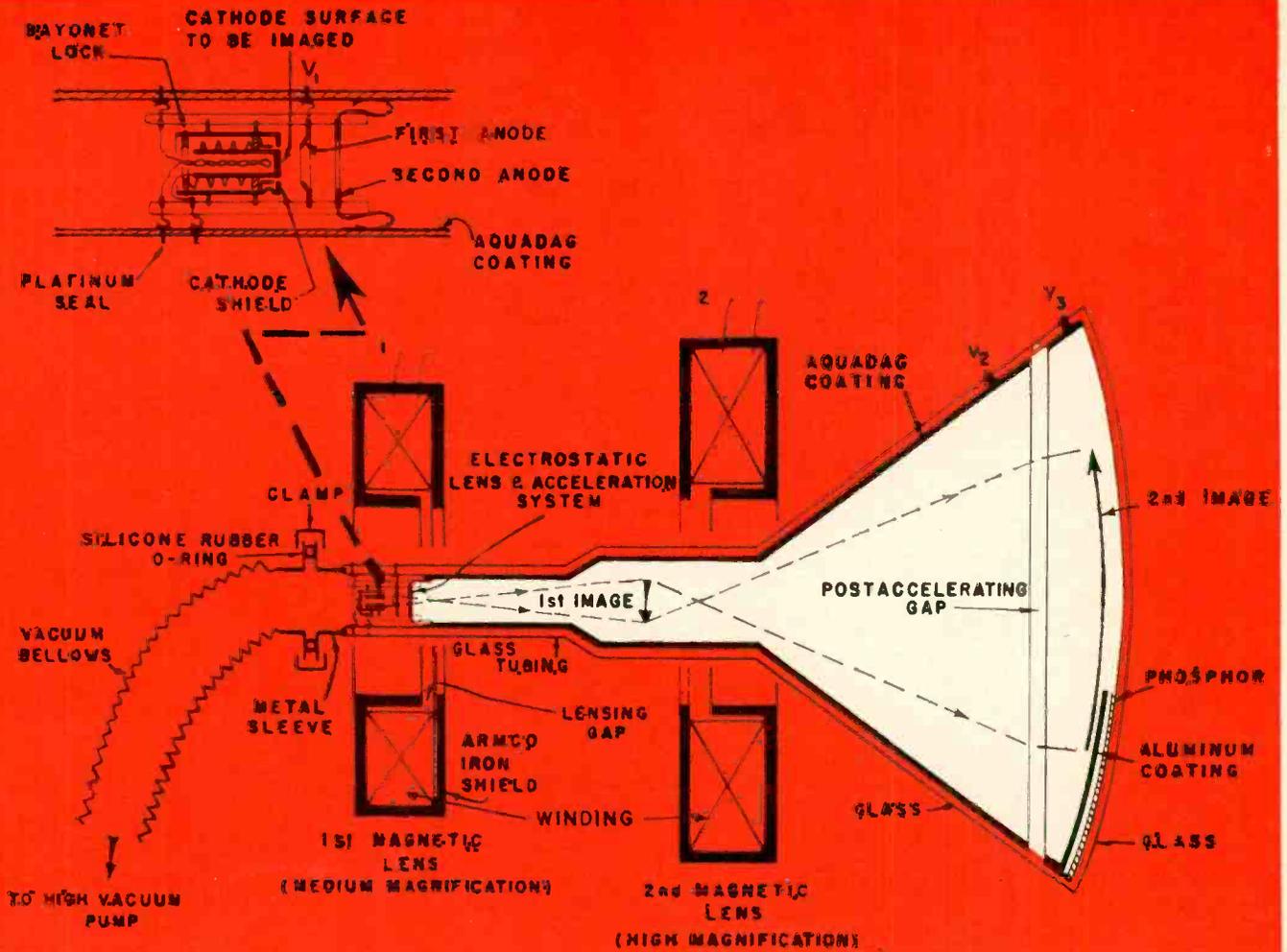


Fig. 1—Schematic of the emission microscope tube.



Fig. 2—The magnified images of cathode crystals are very sharp.



Fig. 3—The effect of decreasing emission with increasing temperature.

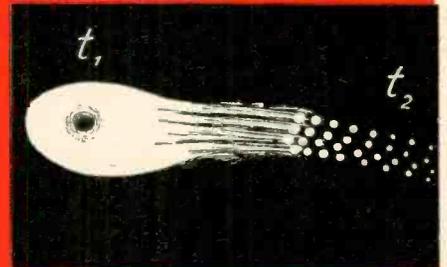


Fig. 4—Vaporization of a portion of the cathode surface.



Fig. 5—First stage in emission from tungsten dispenser cathode.

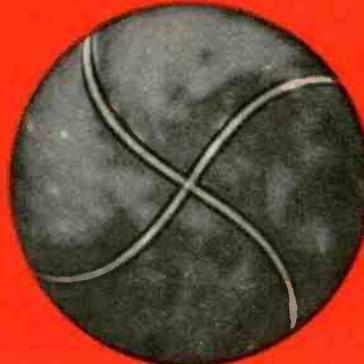


Fig. 6—More uniform diffusion of barium comes to cathode surface.



Fig. 7—The completely activated cathode.

"lenses" (potentials, currents). Correction of lens defects is of paramount importance, but corrections in electron optics are far more difficult than in light optics. Hence the resolving power of 200 milli-microns obtained on the screen with this design and amounting to only 80 milli-microns on a photographic plate in a vacuum is a result not to be sneezed at, particularly when we consider the extreme picture size. Photographers among our readers will appreciate this. Magnifications on the screen may be varied from 7 to 300 times, followed, if so required, by post-magnification with optical equipment.

The microscope tube shown in the schematic is a demountable type connected by flexible vacuum bellows to the high-vacuum pump. More sensitive cathodes are investigated in tubes that can be baked out thoroughly during evacuation before sealoff, to prevent any chemical change on the cathode from occurring by reaction with gaseous residuals.

An automatic time drive located in the box on the instrument panel (see photo) adjusts the cathode heating cycles; it takes hours to complete a series of investigations. Time-lapse cinematography is also used to record and analyze sequences of cathode development, until the desired electron activity is obtained, as can be judged from the screen pattern.


The film strip also photographs the major experimental data, such as date, time, frame number, pressure in the tube and the cathode temperature (which is derived from amplified signals of an infrared sensor positioned outside the glass envelope, opposite the glowing cathode).

If the pressure in the microscope tube rises accidentally above a permissible value, visual and acoustic alarms go off and all electric power connections are automatically cut. This is good practice, since the 15 kilovolts that are applied could destroy delicate systems in case of electrical gas discharges, and possibly initiate an implosion of dangerous dimensions.
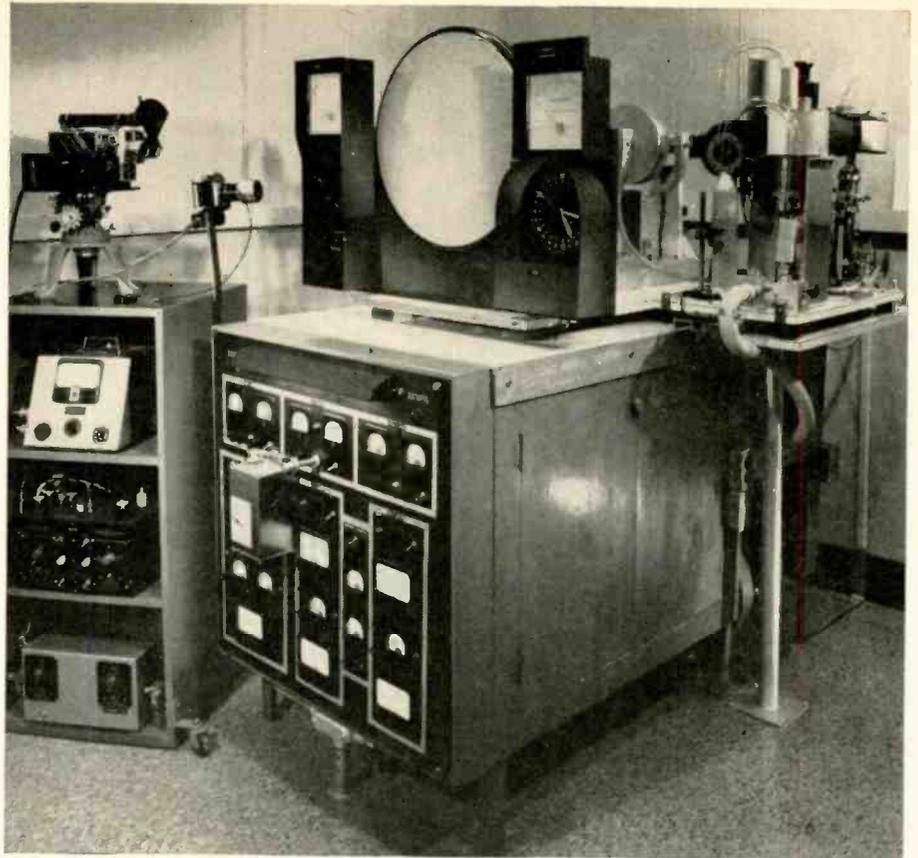
#### Research on cathodes

An electron tube is only as good as its cathode; its life starts and ends with the electron source. The importance of this tube component justifies the elaborate research in this field that started half a century ago with the alkaline earth oxide cathode introduced by Wehnelt.

For some time, progress on thermionic emitters was slow because of the atomic complexity of the physics involved. Although in the '30's electron optics had put one foot in the door by making electron radiation directly visible on phosphor screens, the subject was not followed up to its full extent—researchers did not realize they had a potential tool for exploring the physics and technology of heated cathodes. In those days—and even recently—they were aiming at too high magnification of too small cathode areas. Therefore, acquainted with the non-



The complete electron microscope in the Bayside laboratory.

optical cold field-emission microscope that could reproduce the image of a point only, they underestimated the early electron-optical microscope and ascribed limitations to it that did not really exist.

In the General Telephone & Electronics Laboratories the line was successfully picked up again. We worked on the philosophy that only the observation of simultaneous local events over a large cathode surface could produce meaningful conclusions that would be of value in promoting technical progress. This led to the design of the large electron microscope on the cover.

Analyzing the brightness content (related to emission intensity) and the geometry of the half-tone pattern on the luminous screen enables the cathode physicist to draw realistic conclusions about the emission mechanism. In the past, projected—and therefore speculative—conclusions were drawn about details of the active cathode surface. Diode type current measurement was the tool employed; the actual elements of emission could not be pinned down as can easily be done by direct visual observation.

At first glance, it seems surprising that a cathode, which, as you can see in any electron tube, glows perfectly evenly, does not necessarily emit electrons with comparable uniformity. But the electron pattern usually reveals extensive patchiness of varying intensities, from strongly emitting areas down to dark and dead spots on the screen. The bright spots are said

to have a lower "work function." This term expresses in terms of electric charges and potentials, the force at the cathode surface that resists ejection of thermally energized electrons. The electron emission is subject to spectacular intensity variations because of the widely varying local surface properties of the cathode material, which in turn results in local work-function changes. Small differences in work-function values produce high contrasts in brightness, since a physical law, very sensitive to the work-function term, establishes the strength of the emission current.

#### What is being done

As shown on the cover, a 21-inch screen displays such emission patterns. The author, who in the picture is directing a photosensitive probe onto one crystal plane of a multi-crystal emitter surface, conducts studies under a contract with the Cambridge Research Laboratories of the US Air Force (Office of Aerospace Research, Bedford, Mass.) on thin-film-coated nickel cathodes. Nickel, basically having a high work function, would not lend itself to emission experiments in the rather low temperature range of from 700 to 1,100°C, so an artificial activation process has to be adopted. A thin barium film about 1,000 atomic layers thick is chemically precipitated from an organic barium solution. It is then thermally evaporated down to only a few atomic layers, until the crystal structure of the nickel gradually comes into

prominence on the phosphor screen. The thin barium coating lowers the work function of the bare nickel surface.

As Fig. 2 reveals, very sharp grain structures become visible. Brightness is uniform within their boundaries, indicating the consistency of uniform work-function properties within each individual crystal face. It is due to the differences in the packing density of nickel atoms in different crystal planes that the work function varies.

Very interesting new phenomena were discovered with this potential tool in modern cathode research. Among other effects, the so-called "emission reversal" was brought into prominence. It consists of the appearance of higher emission currents at lower temperatures. This seems to contradict the law of emission. The bright crystal face near the picture center in Fig. 2 exhibits this phenomenon in a convincing manner. It was taken at 890°C, while in the picture of the same cathode at 935°C (Fig. 3), the brightness on the same crystal face is much lower.

With the help of the large-screen microscope we were able to discover that effects like this were a direct result of barium droplet formations that cover certain faces like a mesh-work and alter the straightforward concepts of uniform layer coverage.

Almost as exciting as a good love story to young people is visualizing evaporation to the physicist. It is simply fascinating to watch on the large screen how barium pools, forming on nickel with their typical "black eye" as depicted in Fig. 4, go into a most spectacular vaporization act when heated to 1,100°C. They elongate and develop a fuzzy tail structure just like a comet. The tail breaks up into round globules that constantly sweep in the direction of the higher temperature region,  $t_2$ , gradually reducing in volume till they reach atomic size and disappear. The emission microscope cannot, of course, follow the entire process down to the atomic scale, but limits the observability to its own resolving power. The smallest visible barium globule is 200 millimicrons in diameter.

Other important investigations now become feasible, such as those determining the migration paths of active materials on hot surfaces and in studying the mechanism of structural transformations to the point where the substances are completely dissipated in vacuum.

Another successful application of this new instrument is for demonstrating the emission mechanism of the modern impregnated tungsten matrix cathodes. These, also known as impregnated dispenser cathodes, can draw high currents for thousands of hours. The inventors of this important type of cathode knew its operational characteristics for some time, by empirical measurements. However, their knowledge was confined to critical points only, without knowing the actual physical phenomena connected with them.

Again, the large screen of this

instrument dissipated the fog that surrounded the physical secrets of this type of cathode. What made this emitter tick suddenly became clear. An initial state of pseudo-emission is shown in Fig. 5. Residuals of the impregnant left on the surface after fabrication took the place of true dispenser action of active barium. This state is succeeded by a profuse diffusion of liquid barium through the pores of the sintered tungsten pellet, as visualized in Fig. 6.

Finally, at 1,230°C, a complete surface flooding indicates the end of the desired activation, as seen in Fig. 7. (The windmill-like figure was etched into the cathode to aid microscope centering.) Emission patchiness is a very undesirable feature since, not only does the tube characteristic change, but load

conditions on the surface become non-uniform and noisiness in signal amplification increases.

These different stages of activation are a function of temperature, leading to chemical conversions in the impregnant. They start at 400°C and are followed by secondary conversions. After that, operation at 1,140°C guarantees during the tube life an adequate continuous replenishment of active barium out of the pores by surface migration along the tungsten.

These few examples may show that this new design concept in emission microscopy is in a position to expand the stagnant field of cathode research. It also lends itself to investigations on cold electron and ion emitters and may also play an important role in metallurgical research. END

## WHAT'S YOUR EQ?


It's stumper time again. Here are three little beauties that will give you a run for the money. They may look simple, but double-check your answers before you say you've solved them. For those that get stuck, or think that it just can't be done, see the answers next month. If you've got an interesting or unusual answer send it to us. We are getting so many letters we can't answer individual ones, but we'll print the more interesting solutions (the ones the original authors never thought of). Also, we're in the market for puzzlers and will pay \$10 and up for each one accepted. Write to EQ Editor, Radio-Electronics, 154 West 14 St., New York, N. Y.

### Zenith 17 B20

The picture looked like the photo. This is the best that could be done. The horizontal hold would get the picture up this far; then it would flip rapidly over to the same thing, leaning the other way! This picture would be quite stable like this, holding very well. It would not come up and lock in at all.

Horizontal afc? A check of the tube showed it OK. Horizontal oscillator, afc and horizontal control tubes, OK. All parts in afc circuit good. All dc voltages OK.

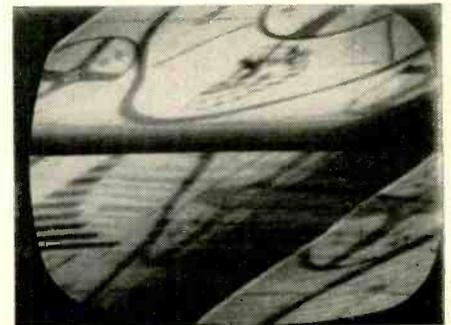Is this trouble in the horizontal afc/oscillator circuit or not? — Jack Darr



HINT: Check pulses on plates of afc.


### High-Output Black Box

This Black Box has four terminals. It contains a number of resistors and capacitors so connected that, for a specified frequency or band of frequencies, the output voltage exceeds the in-

put voltage. The box contains nothing but resistors and capacitors and the necessary wire to connect them. How do you figure this is possible? — Richard L. Koelker
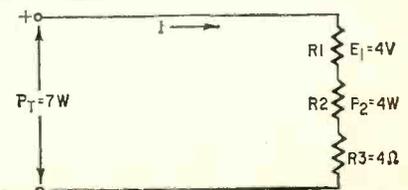
### A Puzzle In Fours

Find the values of R1 and R2 from the information given on the schematic. — Don J. Ponce, Jr.



By TOM JASKI

# RELAYS

## INSTALLING, TESTING AND MAINTAINING THEM

With special attention to modernization and modification jobs

MODIFICATION AND MODERNIZATION OF industrial plants often calls for installing relays or relay control systems in connection with existing equipment. This type of installation calls for more careful thought than even the selection and installation of relays in new plants. The new relay is often part of an important control system. Thus the reliability of the whole plant is controlled by the relay's reliability.

Many factors must be considered when installing relays. The main ones are: the most advantageous location; environmental conditions, such as dust, fumes, vibration and high temperatures; accessibility for service; the space needed and the availability of wiring runs, ducts or conduits. In each individual case, all sorts of other considerations may also enter into any decisions on just how and where to install a relay.

The best location for a relay depends on what you want to do with it. Most often it is best placed near the controlled device, avoiding heavy wiring runs.

When selecting the best place for a relay, accessibility is an important consideration. A relay is an electromechanical device, with moving parts. It is subject to wear. Thus it must be placed where it can be serviced adequately.

It is often possible to add new relays to existing enclosures or panels. If not, special enclosures may be needed. If they are installed on a 117-volt (or higher) circuit, fuses may be required by the local electrical code. Heavy fuses, designed to protect against short circuits or heavy overloads, make for greatest reliability.

In most cases it should be possible to disconnect the relay from the control circuit so that it can be serviced without having to work on "hot" wires. This is especially important when the relay is controlled by an automatic device. It might close the circuit at an inappropriate moment—say while the technician

is holding the disconnected wires!

Relays should be about the last thing installed on a job, since they are more easily damaged than most devices. Such operations as drilling or sawing on metal frameworks are especially bad, since the filings might lodge in relay contact openings. If such work must be done on a relay panel, the relays already on it must be protected with a covering.

In addition to vibrations from the environment, relays have a certain self-vibration each time the armature closes. Use lockwashers on all mounting bolts! In many less expensive relays the terminal leads are taped directly to the winding. Use a terminal

block for such relays, to avoid strain on the terminals.

Basically all such considerations are a matter of common sense and good mechanics' practice. A relay is usually one of the most important links in the control chain, and as such deserves the most considerate workmanship possible. Quality in installation will reflect in reliability of the control.

### Testing relays

What is there about relays that can, and needs to, be tested? Some tests can be made quickly and simply, some require sophisticated equipment. But none are very difficult. How much testing will be done depends on the application, how much is known about the relay and how critical the operation is. Certainly before installing the relay—even one fresh from the factory—it makes sense to give it a quick test for operation. This requires only a simple setup with the right voltage for the relay coil.

Second, it is very simple to test the contacts for closure. Connect the low-ohms scale of your meter across the contacts to be closed, and check if they do indeed close with the correct voltage on the coil.

Other tests on relays might include coil continuity, impedance and resistance, contact resistance, contact heating with rated current, armature chatter (which might result from excessive spring tension), contact bounce (which can result in arcing), hum in ac relays and, at a more sophisticated level, the relay's operating speed.

In industry some of these things are often taken for granted. The relay was carefully selected for its characteristics, it is reasoned, so why then should we test? This is true enough in most cases. But sometimes relays are used from spare parts or surplus stock, and then it may become necessary to know more about the relay than the manufacturer publishes.

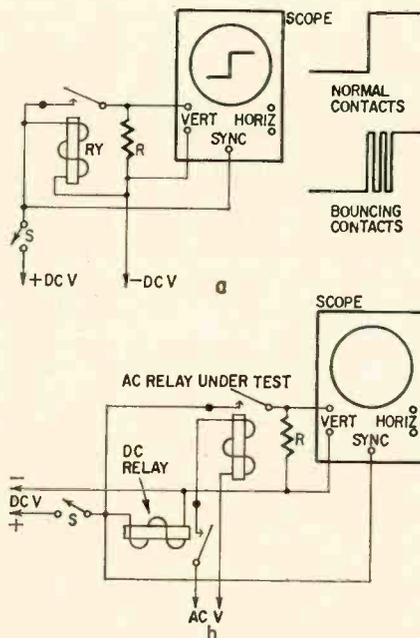


Fig. 1-a—Setup for checking dc relays. b—With ac relays another relay is needed to provide sync before tested relay closes.

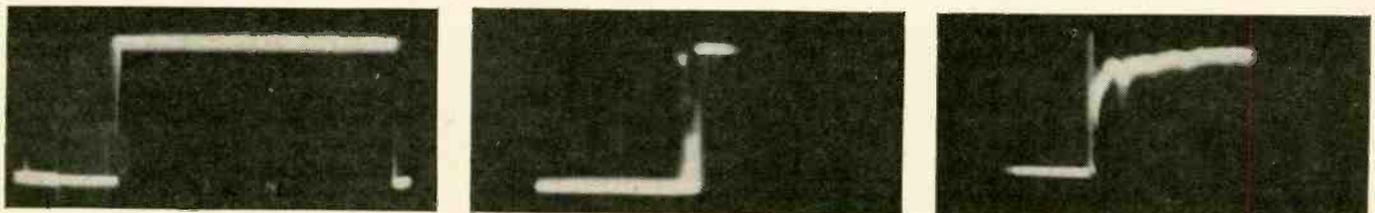



Fig. 2 (left)—How perfect contact closing looks on scope. (center)—Contact shows slight bounce. (right)—This contact is arcing.

The resistance or impedance of a coil is best measured with a Wheatstone or general-purpose bridge. The ac relay coil impedance is measured with the armature *not* attracted. This gives the lesser impedance, and the more important figure, for the greatest amount of energy must be supplied to the relay in the open position. It also gives a rough indication of the in-rush current for the ac relay, which must be considered when selecting fuses.


Armature chatter can be caused by excessive spring or contact pressure, when this does not allow the armature to be completely attracted against the core. A chattering armature can materially increase the relay holding current, thus overheating the coil in an ac relay. In a dc relay it leads to noise and premature wear of the armature hinge.

Hum in ac relays is hard to avoid entirely. There are two sources of hum, the laminations of the core and armature, and the air gap between armature and core. The former is a matter of good relay construction and not easily corrected on a relay in place. The latter may be the result of excessive return-spring tension or contact pressure. These can be adjusted on most relays. Particles of dirt or dust between armature and core can also increase hum. Another cause for hum can be under-voltage on the coil.

Fig. 1 shows how to test a relay for bouncing contacts. With a triggered scope and dc vertical amplifier, the circuit is as shown. R reduces stray ac pickup in the scope; can be from 100,000 to 150,000 ohms. With an ac scope and sync only (rather than triggered

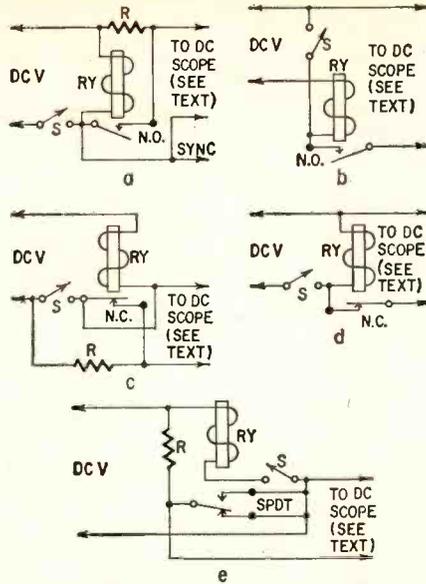

**Fig. 3—Circuits for measuring relay operating time, using dc scope calibrated sweep opening.** a—Closing time, N.O. contacts. b—Opening time, N.O. contacts. c—Closing time, N.C. contacts. d—Opening time, N.C. contacts. e—Transfer time, spdt contact.

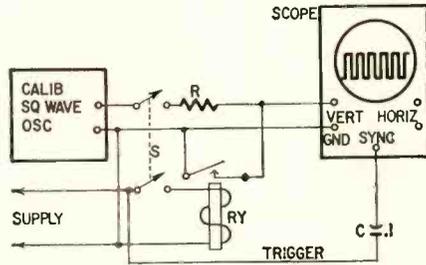

**Fig. 4—How operating time is measured with an ac scope and square wave generator.**


They all work in much the same way. As an example, in Fig. 3-a, as soon as the switch is closed, deflection starts and, when the relay contact closes, it shorts the vertical amplifier and deflection stops. The other circuits in Fig. 3 work the same way for different contact configurations. If the scope sweep is not calibrated, an electronic switch can be used to provide a timing trace along with the deflection by the relay. The switch amplifier must also be a dc amplifier. R in each case must be small enough to make a definite change in the voltage to the scope, big enough to avoid loading the power supply.

Fig. 4 shows how to go about this with an ac scope. Instead of a dc deflection, a calibrated square wave is fed to the relay contact and scope vertical amplifier, but a double-pole switch must be used. Operating time is then counted by the number of excursions of the beam (Fig. 5). All other arrangements in Fig. 3 can be modified in this way to operate with an ac scope; triggered sweep is still an advantage which insures the picture will be in the middle of the screen and not broken up.


Sometimes the relay contact resistance is critical. Particularly in automotive, railroad and aircraft applications, where voltages may be low and currents high, a contact resistance of even 1 ohm may make a significant difference. In that case tests with an ohmmeter may not be conclusive, and a special bridge may have to be used. If you have a meter with a high current range and known internal resistance, it will also work. The relay contact is connected in parallel with the meter. After the meter has been adjusted to



**Straightening bent contact springs.**

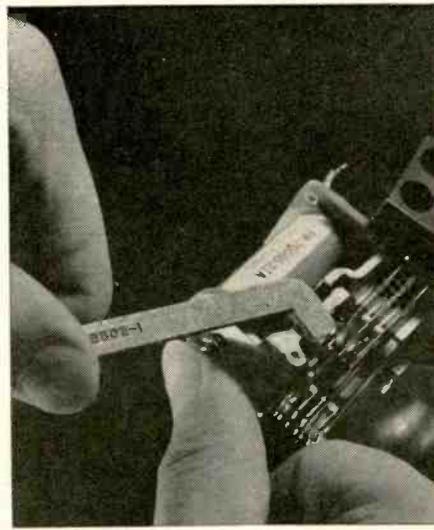

**Bending an armature arm.**

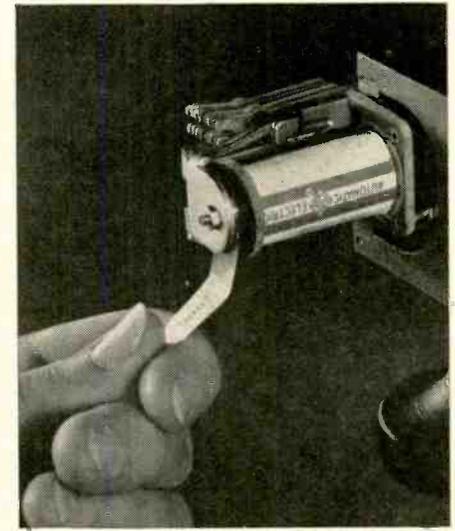

**Bent gauge is used to measure stroke of armature.**

sweep), the switch must be replaced with a periodic contact made by a motor-driven switch or the relay pulse generator described earlier in the series. Bouncing contacts will show as multiple vertical deflections where only a single vertical line would show for properly closing contacts (Fig. 2).

Fig. 3 shows various ways to measure operating time with a dc scope.



**Fig. 5—Square wave measurement with 20-cycle square wave. Relay timing is shown to be 0.6 second.**

deflect full scale, the relay is energized. The contact resistance can then be calculated approximately from the reduction in deflection on the meter scale and the meter internal resistance.

Many other tests of relays are made in production. These are not usually considered necessary by users in industry. Relay factories give their product life tests in which relays are operated

until they fail or decay to some minimum standard. Heat runs are made to determine coil behavior after long hours of continuous operation at high temperatures. Relays designed for high-altitude operations must meet the problems of reduced atmospheric pressure, which may cause arc-over. These relays are tested in special altitude chambers. In general, the few basic tests described here will provide any information you may need about relays in industrial situations.

### Servicing relays

Relays are easy to service and require a minimum of service compared to most electromechanical machinery. Contacts are the most likely source of trouble if they carry rated current and interrupt an inductive load. Although it may not be serious, some arcing is likely to take place. This will lead eventually to burning, pitting and coating of the contacts. The simplest and best way to clean relay contacts is to cut a thin strip of the finest sandpaper available, and drag it once or twice through the contact opening while holding the contacts closed; then turn over the sandpaper and repeat for the other contact. Too, you can do a good job with an approved burnishing tool. *Never* use emery cloth on relay contacts. Emery contains conducting particles, which may lodge in the contact springs, and then the job becomes really tough. *Never* use crocus cloth on relay contacts. Crocus cloth is made from aluminum oxide, an insulator, and you may just coat the contacts with it and worsen the problem.

Cleanliness is one of the first rules in relay service. When soot and grease can deposit on the insulating material between contacts, sooner or later they may arc over. An arc may slightly carbonize the surface of the insulating material. This will require replacing the insulation, a job requiring removing the relay at least, and its complete replacement at worst.

Another good rule to follow in relay service is: *leave well enough alone*. If relays are clean, properly operating and not arcing excessively, don't fool with them!

Salt and saline atmospheres are tough on relays. The problem is not as serious with ac relays, but dc relays soon show a tendency toward electrolysis. It is almost impossible to keep a relay dry enough to prevent electrolysis. When I took care of hundreds of relays out at sea, I would make it a practice to paint all nonmoving parts of relays with Glyptal or other available insulating varnish each trip. Usually this resulted in minimum labor on relays for months afterwards. Coil terminals should be especially well protected.

Special contacts, such as tungsten, require a hard file (such as you find in ignition kits) for dressing. But on the other hand, tungsten contacts seldom require dressing. Silver contacts may turn black. This does not reduce their

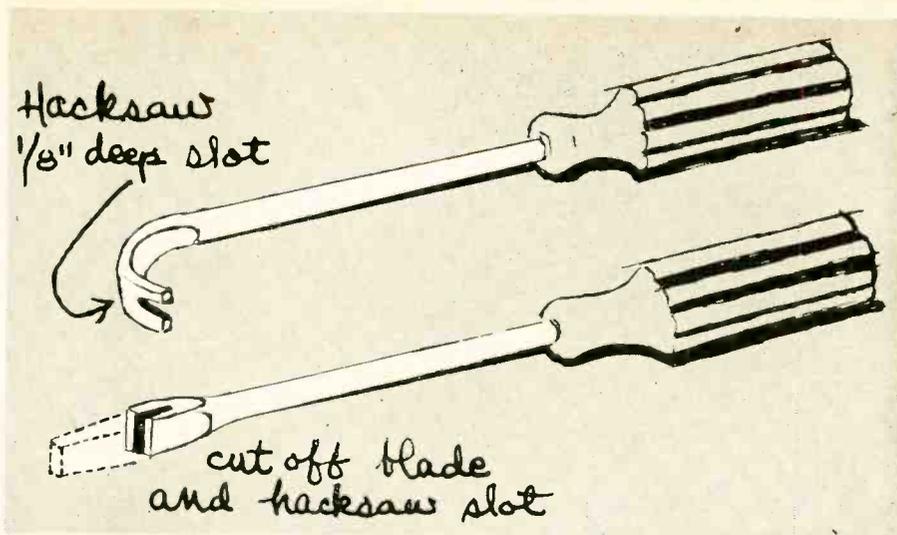


Fig. 6—Instruments for relay adjustment.

contact value, and there is no point in trying to keep silver contacts bright and shiny. You'll soon find it a hopeless task anyway.

Contact adjusting tools can be made simply from modified screwdrivers. The cheap, ten-cent-store variety is best since they are usually made of relatively soft steel and will give you the least trouble with a hacksaw. Fig. 6 shows how to make such tools. Use them sparingly. A bent contact that happens to be straightened out!


Contact pressure can be measured with small commercial gram-gages, but contact pressure is rarely critical, so long as it is not unusually far off. When contacts on a relay open and close at the same time, you can be fairly sure that the contact pressure is very nearly equal, unless one of the springs is badly distorted making its contact pressure different.

When ac relays hum badly, try cleaning between armature and core. I used to use a small strip of canvas and drag


it through the opening while holding the armature down. This usually gets most of the dirt, which lodges in the rough weave of the canvas. *Never* oil relays unless the manufacturer calls for it. I have never come across a relay that needed oiling, but who knows, there may be some somewhere. Oil can raise havoc with the contacts, and in moving joints it just invites dirt to clog.

Here are some of the rules for getting along with relays. In this series we have tried to give you some practical ideas about relays, their application, selection, testing and maintenance, and perhaps you've met some relays you never saw before. Admittedly only a small part has been told of what *could* be told about relays, much of it from practical experience living with them. One cannot but wonder if Henry foresaw, more than a hundred years ago, that his simple electromechanical invention would some day be the most prolific control device in industry everywhere. END

All photos courtesy Automatic Electric

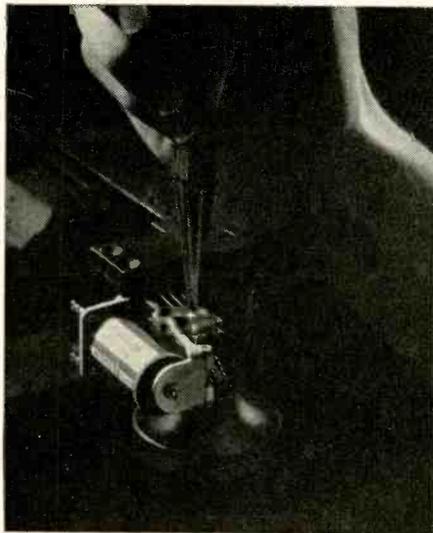


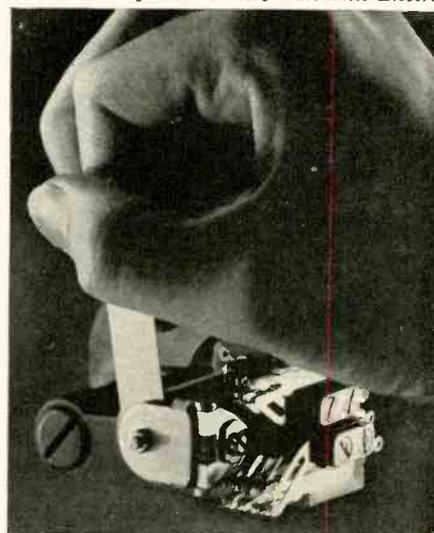Long-nose pliers is used to adjust spring tension.



Measuring the "residual" spacing between armature and coil core.

# What's New


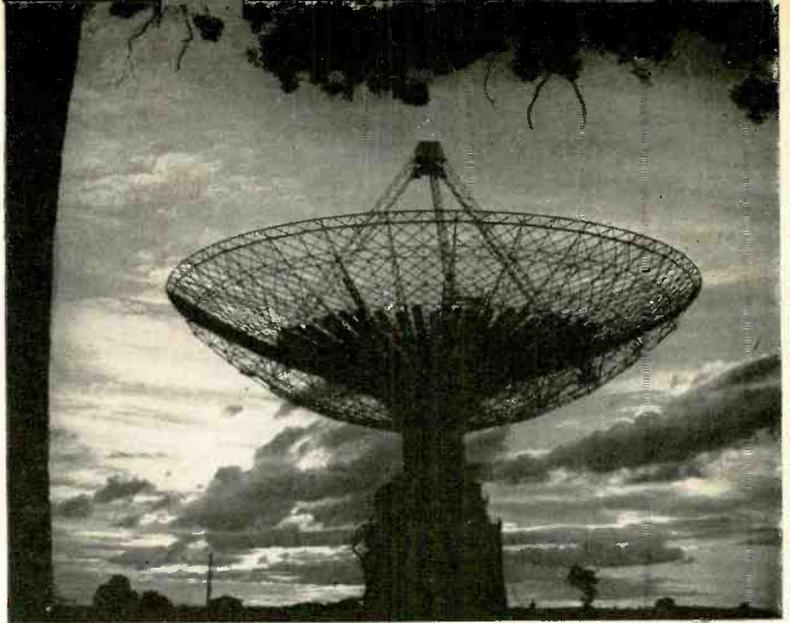


**LISTENING TO THE STARS** is the job of this 210-foot radio telescope, the world's second largest. It is located in Australia about 200 miles from Sydney and is intended mainly for radio study of the Milky Way and other galaxies. Though smaller than the 250-foot antenna at Jodrell Bank its greater accuracy is said to make it superior to any other instrument for detecting radio waves. The photo is from the Radiophysics Division, (Australian) Commonwealth Scientific and Industrial Research Organization.



**LUNAR ROVERS** Dumbo and Porkie are experimental moon exploring devices made by RCA's Astro Electronics Division. Dumbo is the large unit standing on the table. Porkie is being held by Judith Wrona. They were developed as part of a program to create locomotion techniques for getting around on the moon where wheels may not be as useful as their flat pad feet.

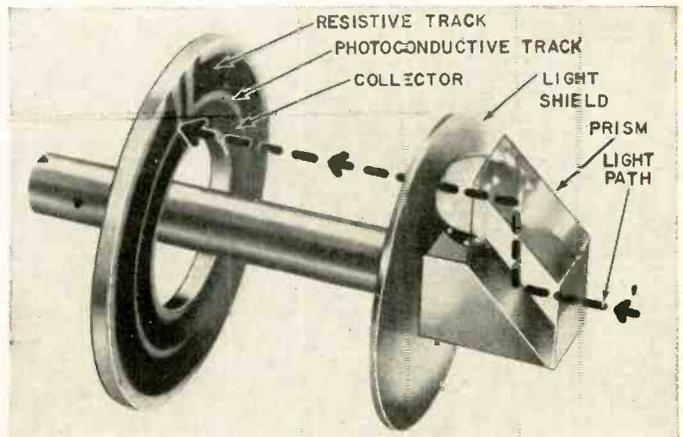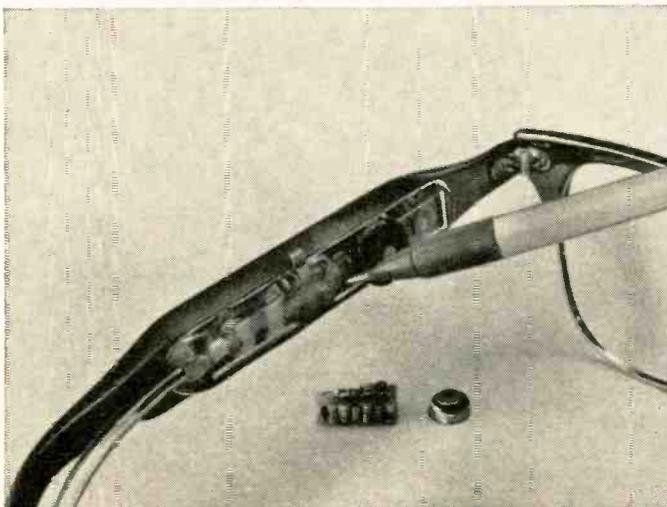**SUBMINIATURE HEARING-AID AMPLIFIER**—the entire section shown in the clear plastic case—snaps in and out of specially made eyeglass frames. Made by Dictograph Products, the device can be used with a variety of frames, unlike previous versions which were built into the frames. Its gain is 33 db.



**ELECTRO-OPTICAL POTENTIOMETER** features an entirely new operating principle. A light beam passes through a prism mounted on the potentiometer shaft and on to a photoconductive track. The point the light hits is determined by the shaft setting. High conduction at this point completes a circuit between collector and resistive track. Advantages of the Duncan Electronics pot are frictionless pickup, long life, and no contact noise.

# TV DESIGN '62

We're lifting the curtain on the new features of 1962  
television receivers

## By WAYNE LEMONS

YES, NEARLY ALL MANUFACTURERS HAVE made some changes for 1962, but you may not be able to recognize some of those changes without a score card. So let's take a fast pan across and then a look at each maker's offering individually.

First off, nearly all tuners use a neutralized triode rf amplifier. A new frame-grid triode, the 6GK5, is the most popular. Mixers are still all triode-tetrodes or triode-pentodes but some new tube types have been added. In the if sections we find many portables have only two stages but, to help compensate, higher-gain tubes are used. In other circuits you probably expected several of the much heralded 12-pin Compac-trons. They are found in only one set—no, not G-E—in Admiral. The one used is a triple triode combination noise inverter, sync clipper and keyed age.

Advertising emphasis, in many cases, is placed on "blacker blacks and whiter whites and a full gray scale in between." Basically, they're ballyhooing a circuit always found in designs around 1950 but which has fallen into neglect in the last several years. It was known as dc restoration or, as some call it, dc reinsertion.

The simplest form of dc restoration is just not to lose it in the first place. This is done by designing the video circuits to retain the dc component by direct coupling from the detector to the video amplifier to the picture tube. This is how it is done where we find it this year, in all except some Packard-Bell sets. Since they use two stages of video amplification, they prefer diode restoration—in this case a diode-connected triode, part of the 6EA8 second video amplifier.


Why have dc restoration anyhow? In simple terms, its purpose is to keep background brightness constant regardless of the video content of the picture. Without it, the background tends to vary in proportion to the average amount of video. For example, when there is a lot of white in the picture, the whole screen goes whiter just as if you had turned up the brightness control. This means dark backgrounds will be too gray. A dc restorer counteracts this by automatically increasing the picture tube bias.

Philco and Packard-Bell have switches on some models to demonstrate this action to the customer.

Dumont, Magnavox and RCA have models with automatic brightness/contrast controls. These circuits use a light-dependent resistor (LDR) whose resistance decreases when room light is increased. You may remember that Hoffman, who no longer builds TV's, used a similar circuit last year.

Westinghouse probably has the most startling innovation, the "instant on" circuit. There is no waiting period; as

Motorola and Packard-Bell have a customer control for varying the video response to compensate for customer preference. These tend to eliminate the snow effect in fringe areas by bypassing some of the high frequencies. Some foreign sets do this slightly in reverse. They have a two-position switch: one side accentuates the high frequencies (crispens) while the opposite position provides normal response. The clever

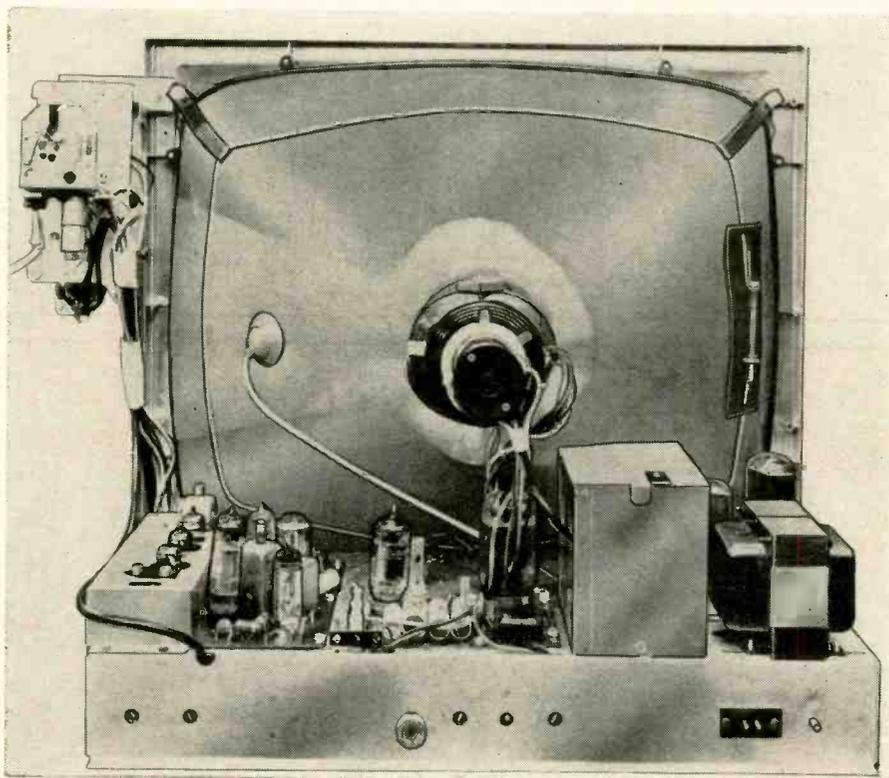

Admiral's 1962 chassis.

soon as you pull the switch you have picture and sound. Westinghouse's "silent sound" is another of its innovations. This is a transistor transmitter that rebroadcasts TV sound to a nearby AM radio.

Philco uses a varistor in some sets to regulate the high voltage automatically. This tends to prevent blooming when a high average value of white information is being transmitted.

Motorola is still marketing the 19-inch transistorized portable TV it introduced last year. It has some competition from Sony (Japan), who has introduced an 8-inch transistor portable.

part is the labeling. The crisp position is labeled FILM and the other LIVE. Since films (old movies at least) lose something in the transition, the crisp position sharpens up the outlines.

More home-entertainment units are being made this year. They feature TV, AM-FM, FM stereo and stereo phonos with stereo amplifiers of up to 100 watts of music power.

Nearly every manufacturer has wireless remotes of varying complexity, as has been the case for a couple of years now—but this year there seem to be more remote equipped portables than before.

Zenith plunged into color with both



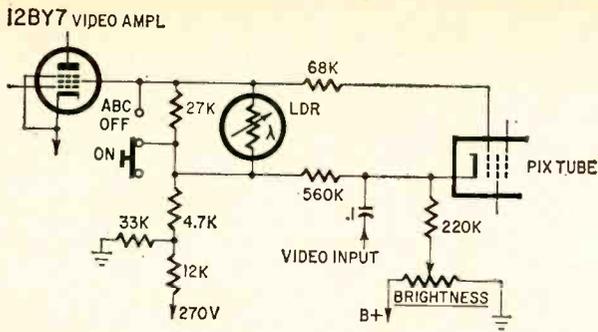


Fig. 2—DuMont's automatic brightness/contrast circuit using a light-dependent resistor.

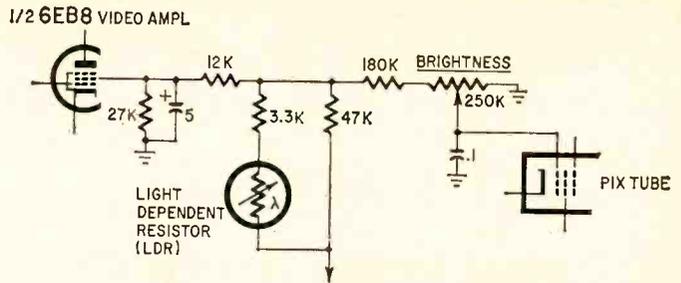


Fig. 3—Automatic brightness/contrast circuit in the Magnavox 35 and 36 series.

transformer-powered and have three if's.

All models have individual vhf channel slug adjustments that can be reached from the front of the set.

Admiral color sets are the same as the RCA CTC11 circuitwise.

### ATR

According to Mr. Goffstein, general manager of ATR Electronics, this company does not believe in "planned obsolescence" but rather endeavors to improve its existing model to be as foolproof as possible.

The set has a cascode Standard Coil tuner, four video if's, two sound if's, ratio detector and push-pull audio output. Two 5U4's are used in a transformer power supply. The horizontal oscillator is a Synchroguide and feeds a 6CD6 horizontal output and 6V3 damper. Twenty-six tubes in all are used in their deluxe chassis.

### DuMont

The new 800 series DuMonts are similar to last year's transformer-powered 600 and 700 series except for a few improvements. An audio output jack has been added that works independently of the volume control. It is useful for tape recording or using an external amplifier. An automatic circuit breaker with a reset button on the rear apron of the chassis has been inserted in the power transformer primary. New frame-grid rf and if amplifiers are used.

An automatic brightness/contrast circuit is included in some models (Fig. 2). Note that a light-dependent resistor (LDR) is connected across the 27,000-ohm resistor in the screen circuit of the video amplifier. As room light increases (in daylight or when lamps are turned on), the resistance of the LDR decreases. This places more voltage on the video amplifier screen, which increases the contrast. At the same time voltage on the picture tube grid is increased through the 68,000-ohm resistor and brightness is increased too.

### General Electric


The MV chassis is very similar to last year's M6 with these exceptions: A 6DT6 gated-beam sound detector is used instead of a ratio detector. The shielded cable from the tuner has been covered with insulated tubing. A 41.25-mc trap has been added inside a larger

first if can and a 47.25-mc trap has been added inside the second if.

Tuners are similar except for the triode rf amplifier replacing last year's tetrode.

The horizontal afc diodes are silicon instead of selenium and, shortly after start of production, a 3A3 replaced the 1J3 as the high-voltage rectifier. The additional heater voltage was obtained by winding three turns around the fly-back core and using a dropping resistor.

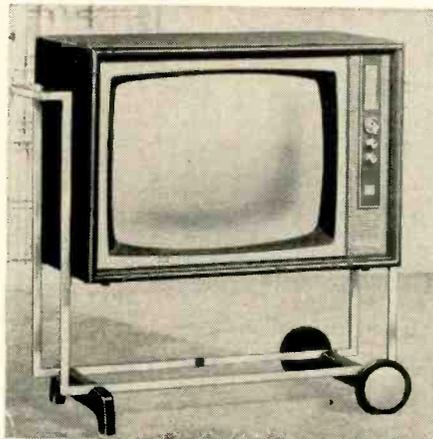G-E's color set (chassis CW) uses an RCA CTC11 chassis.



Intenna teacart used by Packard-Bell. The frame of the cart is a dipole antenna for the TV set.

### Magnavox

New Magnavox receivers are transformer-powered and use silicon rectifiers in a voltage-doubler circuit. A circuit breaker is used in the primary of the transformer.

The automatic brightness/contrast circuit shown in Fig. 3 is similar to the DuMont circuit. It is in the 35 and 36 series -02, -03, -04, -05.

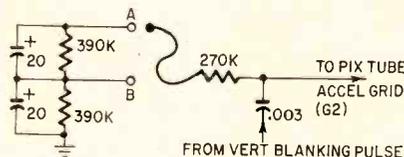


Fig. 4—Tap for CRT accelerator grid voltage may have to be changed to get proper automatic brightness action in the Magnavox 35 series. Connect it to either point A or B—which gives the best results.

It may be necessary to change the accelerator-grid (G2) voltage, especially if the picture tube is changed, to get the proper automatic brightness action. Do this by selecting either tap A or B, shown in Fig. 4, to give optimum results.

New Magnavox sets have 23-, 24- and 27-inch picture tubes.

### Motorola

All new Motorola table and console models use a new horizontal oscillator and control circuit. They also have a "picture optimizer" for customer control of video response.

The oscillator and control circuit (Fig. 5) is different in that no reactance tube is used. The sine-wave oscillator is controlled directly by the output of the phase detector.

The oscillator is a modified Colpitts. Note the cathode feedback taken between .0033- $\mu$ f C507 and .007- $\mu$ f C508, across the horizontal oscillator coil. The "plate" for the oscillator is the screen. It is bypassed to ground through B-plus by 0.1- $\mu$ f C509. This isolates the oscillator from the wave-shaping network, C510 and R511, in the plate circuit.

Motorola, in its circuit analysis of the control circuit, speaks of a sawtooth superimposed on a sine wave by the time constant of C506 and R506, and that the correction voltage varies the size of the sawtooth to provide control. We think it can best be understood from a service standpoint by simply saying that a positive control voltage speeds up the oscillator and a negative voltage slows it down.

### Picture Optimizer

The optimizer control is connected in series with a fixed 1,500-ohm detector load resistor (Fig. 6). This results in a variable detector load resistor. Electrically, it varies the Q of the third if. Increasing the load resistance increases the Q by lowering the loading. This results in a loss of high-frequency response and reduces snow while increasing gain for fringe-area reception. Decreasing the Q gives a sharper, crisper picture for areas of higher signal strength.

### Olympic

New Olympic 100 series are hand-wired, transformer-powered circuits with only two if's. The second if, however, is a new high-gain frame-grid tube. The 200 and 500 series are also

TRADE THE POSTAGE-PAID  
REPLY CARD BELOW  
FOR THESE TWO

# FREE BOOKS!

Get Your FREE COPY of this 64 Page Catalog

...telling you all about the amazing opportunities in the exploding field of electronics. Learn about the profit opportunities in the field of Radio-TV Electronics and **APPLIANCE SERVICING**. Get the facts about Central Technical Institute's NEW, down-to-earth **PRACTICAL ELECTRONICS** Home Study Course... brand new **INSTANT KITS** that can be used in starting your own business or that can be sold at a profit to friends, neighbors and customers!

Get Your FREE COPY of this 31 Page FCC Prep Book


...telling you all you need to know to pass the 3rd class FCC Radiotelephone examination. FCC 3rd class license qualifies you to operate radiotelephone transmitting stations used by airlines, police, railroads, emergency services, etc.

**EARN EXTRA MONEY SOON  
IN YOUR SPARE TIME!** Train at home  
for a Career in Radio-TV Electronics and  
Profitable **APPLIANCE SERVICING!**

### NO EXPERIENCE NEEDED!

Enroll in Central Technical Institute's New Home Study Course—**PRACTICAL ELECTRONICS**. Central will show you how to make money soon—servicing AM-FM radios, TV sets, small appliances... building and installing electronic equipment in homes, factories and business offices. The future is bright for trained technicians and servicemen. Get started today toward a prosperous business of your own or a better job... with Central's **PRACTICAL ELECTRONICS** Home Study Course. Join the thousands of Central students and graduates who are making extra money in their spare time—have their own business—or a good job with a future.

SEE OTHER SIDE!

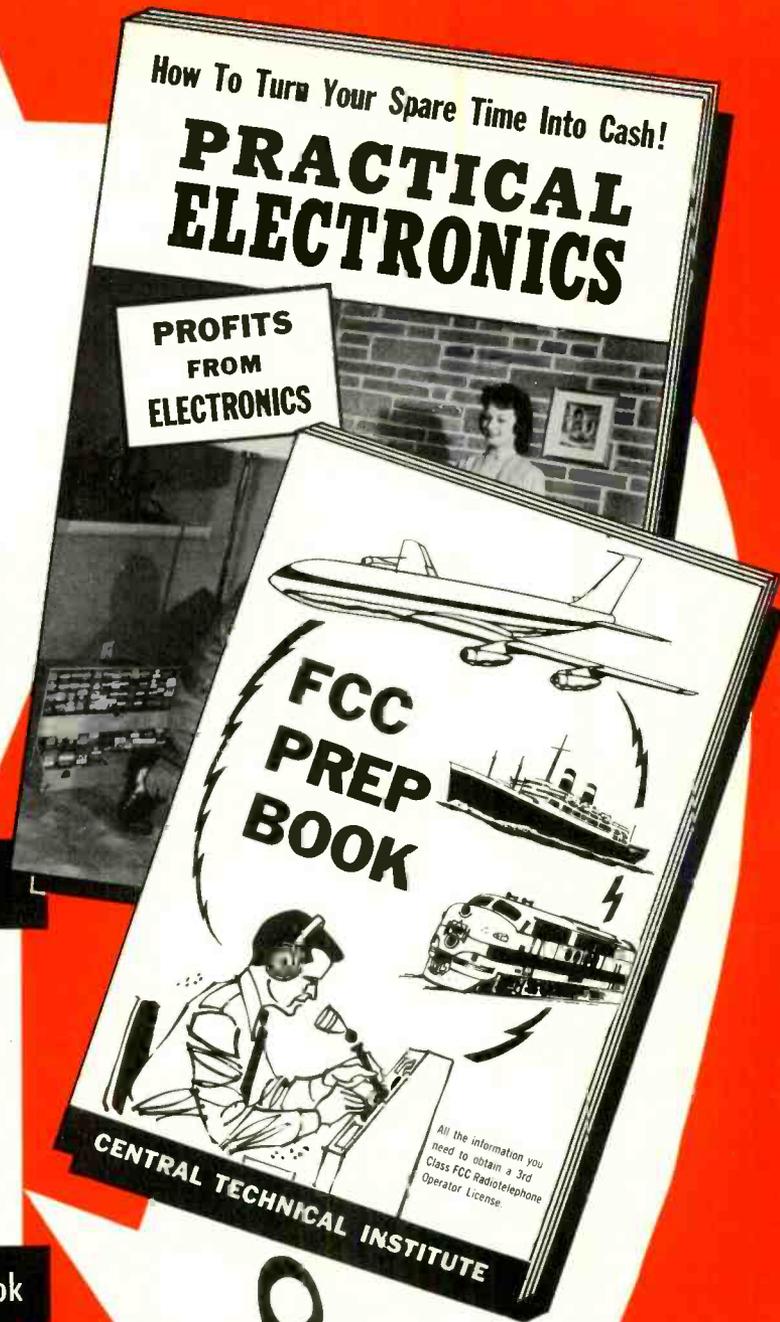

Clip and Mail This Postage-Free Card Today!  
**GET 2 FREE BOOKS!**

Please send me my FREE copies of  
**PRACTICAL ELECTRONICS** and **FCC PREP BOOK**

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**CENTRAL TECHNICAL INSTITUTE**

Accredited Member National Home Study Council  
Over 50,000 Successful Graduates since 1931!





**NEW**



# CENTRAL'S INSTANT KITS<sup>®</sup>

**Help you to START MAKING MONEY...SOON!**

**CHOOSE THE  
INSTANT KITS  
THAT APPEAL  
TO YOU!**

- Transistorized Electronic and Appliance Tester
- Code Oscillator
- CB Converter
- RF Signal Generator
- Photoelectric Switch
- 4 Transistor Portable Radio
- Oscilloscope

**They're MODERN • PRACTICAL • COMPLETE • MEET COMMERCIAL STANDARDS**

**Study Practical Electronics with Central Technical Institute—Select the equipment you wish to build—start making money servicing and repairing radio-TV sets and appliances**

**NO EXPERIENCE NEEDED!** You don't need a high school diploma or previous knowledge of electronics to get started, with Central's **PRACTICAL ELECTRONICS COURSE**. Quick, low-cost home training for young and old. New, illustrated lessons make learning easy. You learn by doing—building modern, complete, useful equipment furnished by Central. You earn *extra money* in your spare time doing work that is profitable and enjoyable. Keep your present job—set your own pace—add to your income—find out how much fun electronics can be!


**OVER 50,000 SUCCESSFUL GRADUATES**

"I wouldn't be in my present position if it weren't for my Central Technical Institute training. Naturally, I recommend the school very highly. Damon Alarm has ten employees, and four service vehicles." CLARENCE S. DAMON, President, DAMON ALARM CORP., K. C., Mo.



"I am in business for myself, operating a part-time Radio & TV Service Shop in my home. My gross part-time earnings average \$100 per month." Grad CARROLL B. SCARBOROUGH, Belton, Mo.

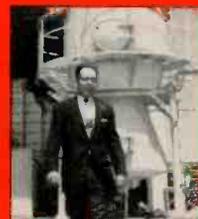"The field of electronics is exciting. There are opportunities galore. I received training at Central Technical Institute and I recommend the school without qualification." FRANK LEENKNECHT, CONVAIR ASTRONAUTICS DIVISION, GENERAL DYNAMICS CORP.



**RESIDENT TRAINING**—Central also offers a full-time ECPD-Accredited Technical Institute program at its resident school in Kansas City, Mo., for qualified high school graduates. Details in **FREE** catalog.

FIRST CLASS  
Permit No. 3021  
Kansas City, Mo.

BUSINESS REPLY MAIL

**NO POSTAGE STAMP NECESSARY**

IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY—

**CENTRAL TECHNICAL INSTITUTE**

1644 Wyandotte Street  
Kansas City 8, Missouri


Dept. RE 12 B

**ACT NOW! RECEIVE 2 FREE BOOKS!**

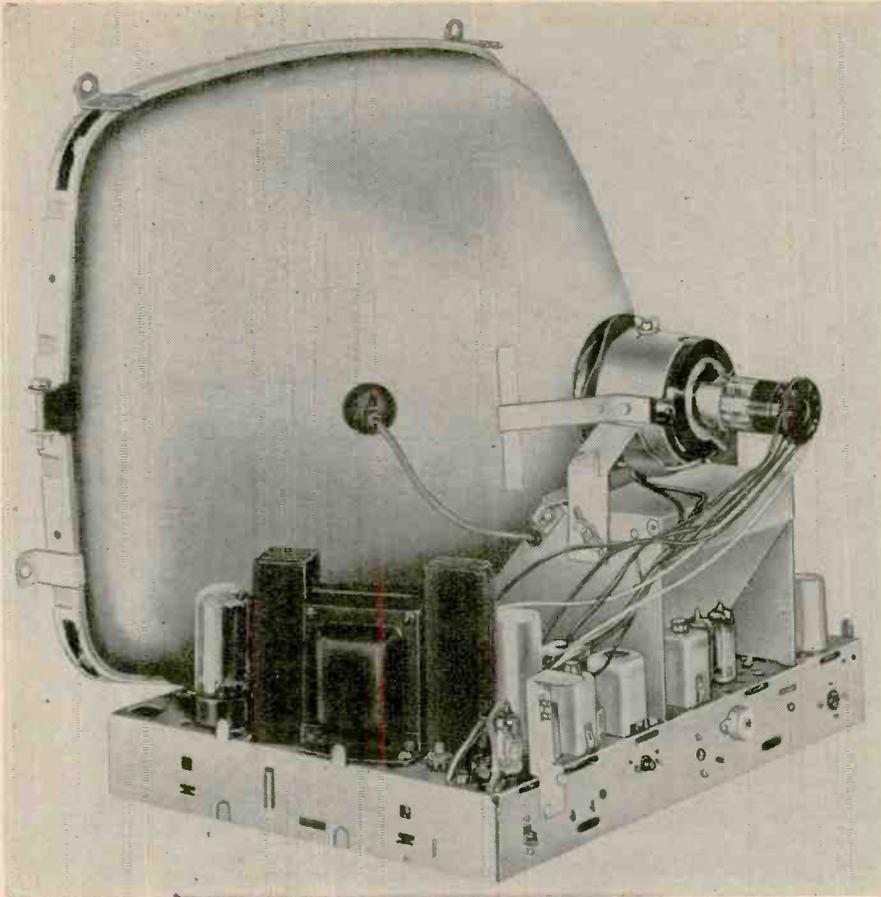
**FILL OUT REVERSE SIDE AND MAIL TODAY!**








Zenith's 16H28 chassis—new for '62.

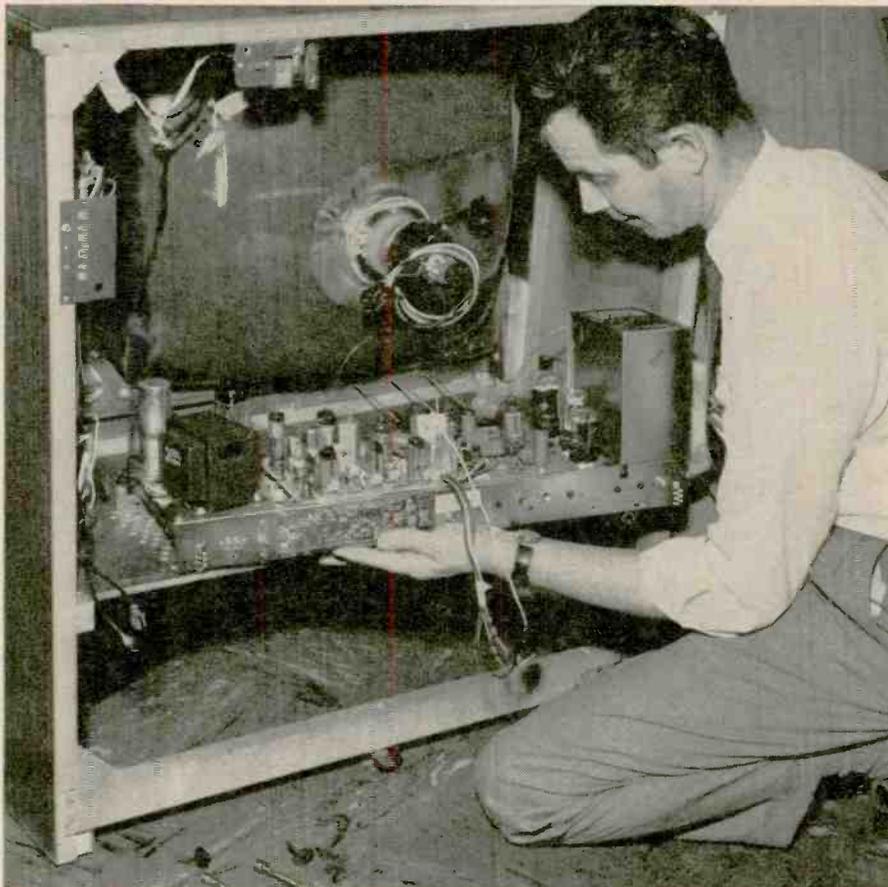

TV technician demonstrates accessibility of Sylvania GT-555 chassis.

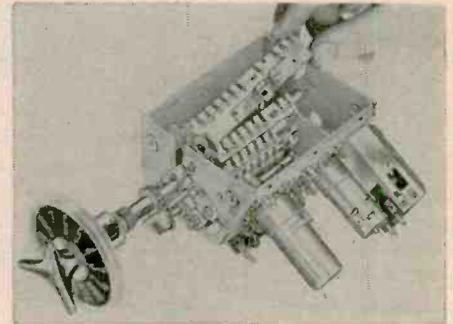With the LDR switched in, the dc component from the video amplifier plate is coupled through the switch to the CRT cathode. Since the LDR decreases in resistance, the CRT cathode will go less positive and brightness will



New tuner used by Zenith has provision for adding up to 4 uhf channel strips.

increase with an increase in room light.

With the LDR switched out, dc for the picture tube cathode is taken through R149 (56,000 ohms) and R148 (270,000 ohms) and R241 (150,000 ohms). The LDR is shorted by the other side of the switch.

A winding on the width coil supplies a horizontal blanking pulse to the picture tube grid. Vertical blanking is also applied to this grid.

#### RCA color

The principal change in the CTC11 RCA color set is the picture tube. The new 21FBP22 tube has up to 50% more brightness. All three phosphors are more evenly matched so that the red gun does not have to be driven harder. This eliminates the red border around bright, white objects. All three phosphors have about the same decay time. In the old tube, the blue phosphor decayed more rapidly (dimmed faster after being hit by the electron beam) than either red or green. This caused a yellow blur following fast movement in the picture.

Other changes are a new tuner using the 6CW4 nuvistor triode, and a circuit breaker replacing a fuse in the B-plus circuit.

Set up procedure is essentially the same as last year.

#### Setchell-Carlson


Setchell-Carlson has three chassis, all transformer-powered—the C-117 portable (also C-219 with AM radio), the 362 and the "unitized" 159.

The 159 is the same as last year except for a new tuner using a frame-grid triode (6GK5) rf amplifier. The same chassis is used with 23-, 24- and 27-inch picture tubes.

The 362 chassis has three video if stages (as do the others) and two video amplifier stages.

The power supply is the same in both the portable C-117 and the 363 chassis. It is a little unusual (Fig. 12) in that 115 volts B-plus is taken off at the lower end of the power transformer

(Continued on page 60)


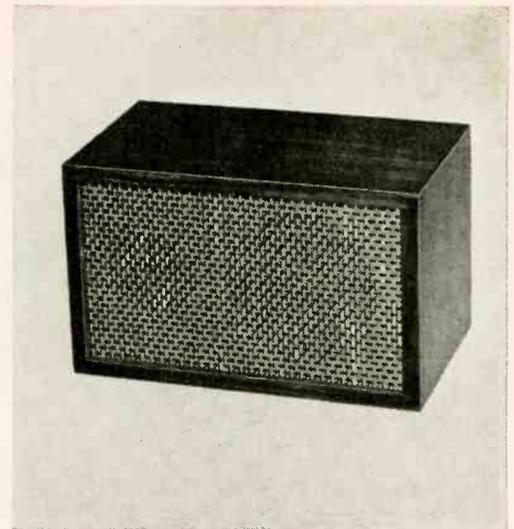


**FM STEREO AT LOW COST**

A "value packed" combination for exciting stereo FM entertainment! Tuner has pre-assembled, prealigned FM tuning unit for fast, easy assembly. Features flywheel tuning, automatic frequency control, handsome modern styling. Stereo converter has self-contained power supply, cathode follower outputs for A & B channels. 12 lbs.  
**Kit AJ-31S** (includes AJ-31 tuner and converter)...no money down, \$7 mo....  
 Saves \$2.50.....only **\$69.95**

**SPACE-SAVING AS-81 SERIES  
 MINIATURE HI-FI SPEAKER SYSTEM KITS**

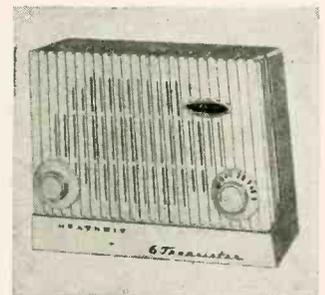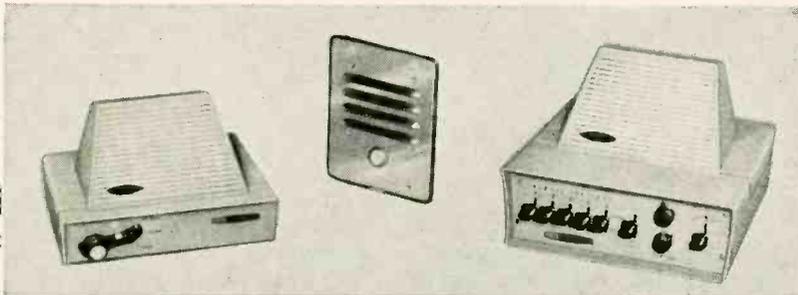Measures only 10 3/4" x 6 1/2" x 6 3/8". 70-14,000 cps response. 6" woofer, 3" tweeter. 8 ohm imp. 6 watt power rating. Factory assembled cabinet. 10lbs.  
**Kit AS-81**... Unfinished..... **\$17.50**  
 ... Mahogany or Walnut..... **\$19.95**



**SAVE TIME & STEPS WITH A HEATHKIT INTERCOM SYSTEM**

Complete indoor & outdoor communications facilities in easy to build kit form. All-transistor master handles up to five indoor or outdoor remotes. Powerful 1 watt output and specially designed frequency response assure crisp, clear communications. Costs only 5c a month to operate!  
**Kit GD-121 Master Station** . . . 5 lbs. . . . no money down, \$5 mo. . . . . **\$29.95**  
**Kit GD-131 Indoor Remote** . . . 3 lbs. . . . . **\$8.95**  
**Kit GD-141 Outdoor Remote** . . . 2 lbs. . . . . **\$5.95**

**"CORDLESS" AM RADIO**

Battery powered. 4" x 6" PM speaker; transistor circuit; ivory & green. 3 lbs.  
**Kit GR-131 Radio**  
 (less battery)..... **\$19.95**  
**GRA-131-1: Battery pack**  
 2 lbs..... **\$1.10**

**HEATHKIT® offers MORE—more new**

Whatever your interest, there's a Heathkit for you. Over 250 kits—each priced to save you money. Guaranteed to be easy to build and to provide years of enjoyment and superior performance.

*Why take chances in kit buying—  
 Heathkit's broad guarantee  
 assures satisfaction every time.*

Compare this guarantee with any competitive electronic kit manufacturer. See why Heathkit gives you more. Our pride in our quality, in our reputation and goodwill, in our painstakingly engineered "check-by-step" instructions is reflected in the unconditional guarantee that you, regardless of technical knowledge or experience, can build any Heathkit.


**MONEY BACK GUARANTEE**  
 The Heath Company unconditionally guarantees that you can build any Heathkit product and that it will perform in accordance with our published specifications, by simply following and completing our check-by-step instructions, or your purchase price will be cheerfully refunded.



**WORLD-WIDE REACH!  
SHORT WAVE RECEIVER**

Covers 550 kc to 30 mc in four bands. Illuminated 7" slide-rule dial & meter. Versatile controls for top reception. "Velvet touch" tuning. Easy circuit board assembly. Beige & aqua color. 9 lbs.

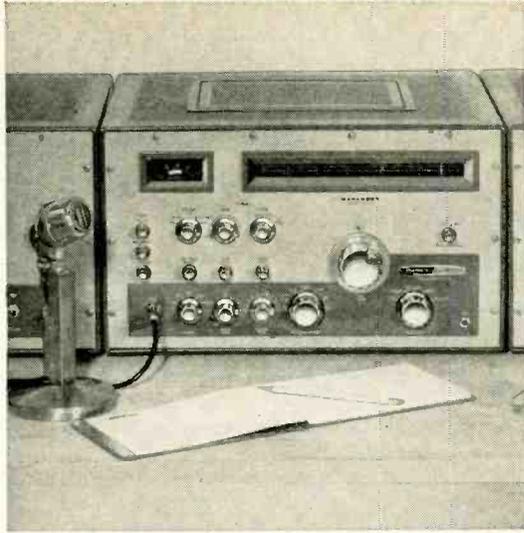Kit GR-91... no money down, \$5 mo. .... **\$39.95**



**NEW! FIRST COMPLETE FILTER-TYPE  
SSB TRANSMITTER IN KIT FORM!**

Another Heathkit first! Every desired SSB feature at half price. Send for full specifications and compare for yourself! Operates 80 through 10 meters with out-of-band coverage for MARS operation. 180 watts PEP—SSB & CW, 75 watts AM. Parallel 6146's in final. All power supplies built-in. Unique simplified alignment procedure!

Kit HX-10 SSB TRANSMITTER... 92 lbs... no money down, as low as \$22 mo. **\$334.95**



**NEW CITIZEN'S BAND TRANSCEIVERS**

New high-efficiency transmitter. 3-crystal controlled transmitting channels; single crystal or variable receiver tuning. Adjustable squelch, automatic noise limiter. Press-to-talk mic. Signal meter. 13 lbs.

Kit GW-11... specify AC or DC... no money down, \$7 mo. .... ea. **\$69.95**



**POCKET SIZE  
"WALKIE TALKIE"**

4-transistor; crystal-controlled. Range 1 mile. Easy circuit board assembly. 2 lbs.

Kit GW-31 ea. **\$24.95**



**RESISTANCE & CAPACITOR DECADES**

Provide precision resistor values from 1 ohm to 999,999 ohms in one ohm steps, at 1/2 of 1% accuracy... capacitor values from 100 mmfd to 0.111 mfd in 100 mmf steps.

Kit IN-11... 6 decade resistance kit... 4 lbs... no money down, \$5 mo. .... **\$24.95**

Kit IN-21... 3 decade capacitor kit... 3 lbs. .... **\$17.95**

**kits, better guarantee, easier terms**

*Don't wait to buy the kit you need!  
Heathkit's easy terms let you  
enjoy it while you pay!*

No need for cash. Beginners, enthusiastic amateurs and dedicated professionals will find kits to meet their needs... and pocketbooks. Here is tremendous quality at the lowest possible cost PLUS new relaxed credit terms. You can purchase any kit from \$25 to \$600 with no down payment and take up to 18 months to pay. What's more, when you purchase the kit of your choice, you purchase with confidence, with the sure knowledge that it will outperform any competitively priced product. Enjoy it today... pay for it tomorrow. Remember, no money down and up to 18 months to pay. With a Heathkit every dollar invested gives double enjoyment, double value!

**HEATH COMPANY**  
Benton Harbor 20, Michigan



Yes, send me my free 1962 Heathkit catalog

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Order direct by mail or see your Heathkit dealer.

Ship  Parcel Post  Express  C.O.D.  Best Way

Ordering instructions: Fill out the order blank. Include charges for parcel post according to weights shown. Express orders shipped delivery charges collect. All prices F. O. B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice. Dealer and export prices slightly higher.

ITEM	MODEL NO.	PRICE

**Free Catalog!**



Send in today for your free 100-page catalog. Over 250 kits (more than 40 are new) in this most complete catalog of kits. Every piece is top quality... save up to 50%. Get a catalog now and receive 1962 Heathkit supplements.

*This Christmas Give a Heathgift... from the World's Shopping Center for Electronic Kits*



a power-transformer chassis with 5U4 rectifier and B-plus circuit-breaker in their table and console models. They have retained their series-string portable.

The transformer chassis is easily accessible for service. Yoke and tuner plugs make it simple to remove the chassis if service underneath is necessary.

Their remote control receiver has been updated to provide more functions. It now uses two tubes (12AX7, 12AT7) instead of the one (6AW8) used previously. The frequency of operation is the same, about 8 kc, as compared to other remotes which usually operate around 40 kc.

An unusual width-control circuit is used in all models. It has both screen-voltage adjustment and screen degeneration (Fig. 16). As the WIDTH control arm is moved toward B plus, the voltage on the screen decreases. At the same time, the .047- $\mu$ f screen bypass is placed in series with more resistance. This reduces the amount of screen bypassing; degeneration results and the horizontal amplifier has less gain. The main advantage, apparently, of this circuit is that the width control need not be a high-wattage pot.

### Westinghouse

The new Westinghouse table and console sets are transformer-powered with a fused primary. The portable is similar to last year except that some chassis have an Instant-On feature. Fig. 17 shows how this circuit works. Note that the upper section of the dpst switch opens the ac line to the silicon-rectifier power supply but the lower section going to the heaters is bypassed by a diode. This keeps the tubes lit dimly (and drawing about 32 watts) so that the picture and sound come on instantly when the off-on switch is pulled on.

Westinghouse believes that tube life will be extended in these sets because there is no sudden surge of current. The heat generated also helps to eliminate dampness that causes component failure in some areas of the country.

### Silent Sound

This is another unusual feature of this year's Westinghouse line. Silent Sound is a transistor transmitter that rebroadcasts the TV sound from the TV to any nearby AM radio (Fig. 18). This permits easy remote control of TV volume. You can turn down the volume on the TV set and listen only through your radio. A radio with an earphone plug can be used for private listening so as not to disturb other members of the family.

The circuit is extremely simple. A p-n-p transistor is used both as an rf oscillator and modulator. Sound coupled from ahead of the volume control is fed into the base circuit. Feedback from the oscillator is supplied through .01- $\mu$ f C5. C6 sets the frequency to a quiet spot on the radio dial. Power for the circuit is obtained from the cathode circuit of the audio output tube. *Caution: This*

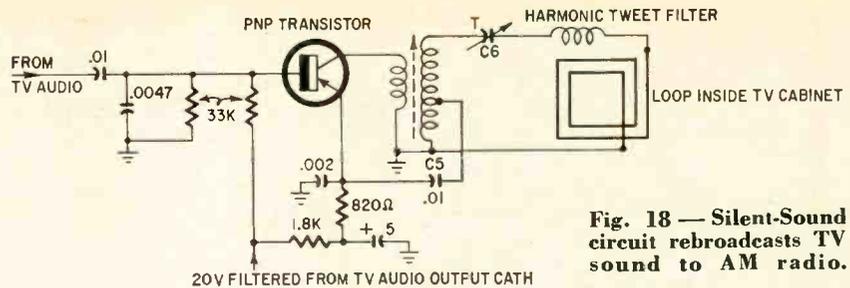


Fig. 18 — Silent-Sound circuit rebroadcasts TV sound to AM radio.

*circuit meets FCC specifications for radiation and should not be modified in an attempt to get more range.*

### Zenith

There hasn't been too much change in the Zenith line. Some new tube types will be noticed, including frame-grid if's in some chassis. A new turret tuner has been introduced this year and is used in most black-and-white sets and in the color chassis. It should be easy to service.

Like last year, the chassis are all hand-wired and transformer-powered. The 3DG4 introduced in one model last year is standard in all '62 models.

The 16H28 deluxe chassis has a couple of interesting features. A PEAK PICTURE control, similar to Motorola's PICTURE OPTIMIZER described earlier, is located on the rear apron of the chassis. It may be set from a slight smear to an exaggerated ringing condition. The other feature is an adjacent channel in-out switch. Picture response is a little better with the switch out and it should be left here unless the customer runs into adjacent-channel sound interference (Fig. 19).



Philco's varistor is located just inside the high-voltage cage.



Philco's 6FD7 vertical output tube has standard 9-pin base and dissipates more heat by using a larger than normal glass envelope and heavier construction.

### Zenith Color

This is the first new color set in several moons that hasn't been built by RCA. The Zenith set is hand-wired and uses an entirely new color detection circuit. The picture tube is an RCA (though labeled Zenith), and convergence and tracking adjustments are very similar to RCA. [A complete story on the Zenith color receiver will appear shortly, probably next month.—Editor]

The picture is positioned with strings. These strings go down inside the yoke assembly to turn magnetic rings much like those used on black-and-white sets. One set of strings moves the raster sideways, the other set moves it up or down.

The set has 29 tubes in all, including three frame-grid if's and two 3DG4 low-voltage rectifiers. **END**


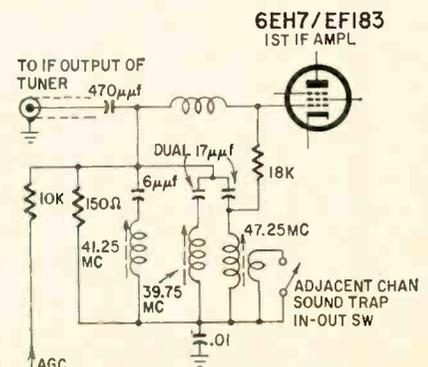
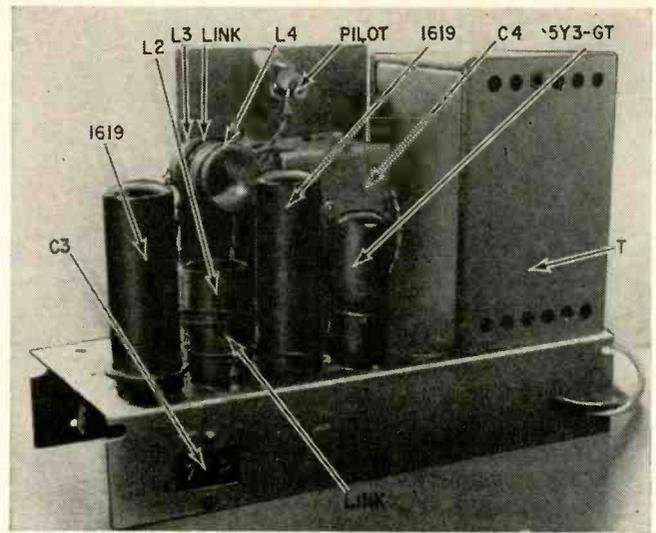


Fig. 19—Zenith 16H28 chassis has a switch to disable adjacent channel sound trap when set owner has no interference.

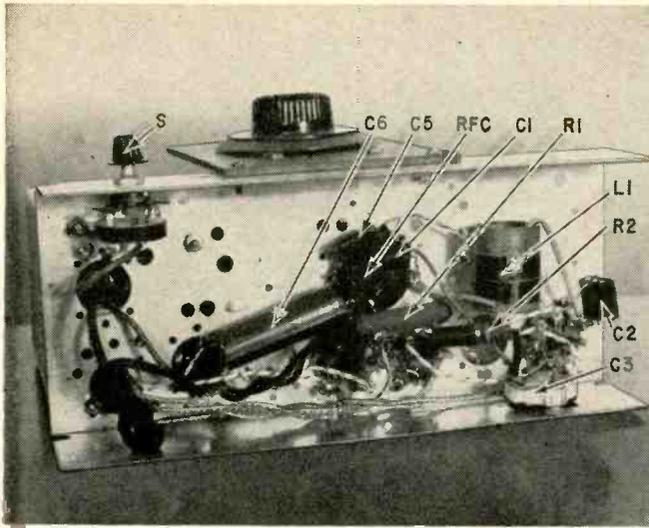

Top and bottom views of the intermittent checker.

# SIMPLE UNIT TESTS INTERMITTENT CAPACITORS

By JOHN A. DEWAR

Intermittent electronic equipment is one of the technician's worst headaches. Paper capacitors with loose internal connections are a common cause of this trouble. No other trouble is as hard to locate. Frequently the part fails to "intermit" when its leads are pulled or moved. "Cooking" the set is time-consuming and often ineffective. Replacing all capacitors is expensive and inconclusive. This intermittent-capacitor tester is, to me, the logical answer. The tester is basically an rf power oscillator, producing about 10 watts at around 5 mc. The capacitor to be tested is connected in series with C4 across L3. C4 is tuned to resonance with the oscillator which

causes a large rf current to pass through the capacitor under test. Resonance is indicated by maximum brilliance of the pilot light across L4.

Most of the parts of the unit can be found around the shop. Surplus 1619 tubes were used because they are quick-heating. Tubes like 6L6's or 807's can be substituted by using a power transformer with a 6.3-volt winding. Power transformer T is from an obsolete radio. C4 is a two-gang tuning capacitor with the two sections used in series. The rotor is ungrounded. C3 is a dual 30-100- $\mu$ f trimmer from an old if transformer. The parts list covers the other components.


The only filtering required is the 10- $\mu$ f

electrolytic shown. C3 is adjusted for maximum output. An rf ammeter in series with a .01 capacitor on test will read a little over 1 amp. A 7-watt 117-volt lamp should light up brightly.

The tester produces enough rf to give a good sting, so it is better to shut the power off when making connections. If slow-heating tubes are used, insert a switch from the high-voltage center tap to ground. This keeps the heaters hot for instant use.

Coil and wire sizes are not critical. Since the tester is not in frequent use and therefore not a permanent bench fixture, it need not be dressed up in a fancy panel and cabinet. Layout and lead dress are not critical. Construction time and cost are small.

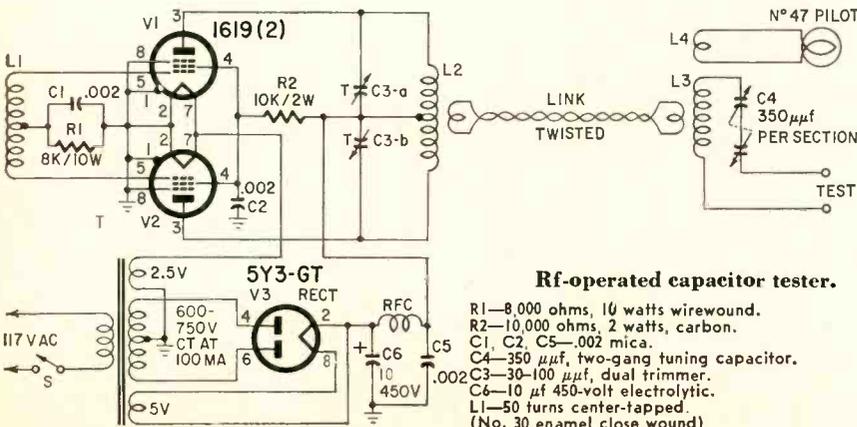It is advisable to leave the capacitor under test for several minutes. If it has a loose internal soldered connection between the foil and pig tail, it will arc, heat up and open, causing the pilot light to go out. If the capacitor is shunted by a fairly high resistance it need not be disconnected to make the test. END



Rf-operated capacitor tester.

- R1—8,000 ohms, 10 watts wirewound.
- R2—10,000 ohms, 2 watts, carbon.
- C1, C2, C5—.002 mica.
- C4—350  $\mu$ f, two-gang tuning capacitor.
- C3—30-100  $\mu$ f, dual trimmer.
- C6—10  $\mu$ f 450-volt electrolytic.
- L1—50 turns center-tapped.
- (No. 30 enamel close wound)

- L2—50 turns, center-tapped.
- L3—20 turns.
- L4 and link coupling coils—2 turns of insulated hook-up wire
- (No. 22 enamel wire close wound on 1/4-inch forms)
- RFC—45 turns No. 22 enamel on 1/4-inch form.
- T Power transformer, 2.5 volts 4 amps; 5 volts, 2 amps; 600-750 volts center-tapped, 100 ma.
- Pilot lamp—6-8 volts 150 ma (No. 47).
- V1, V2—1619 (see text)
- V3—5Y3-GT

The Orthophase speaker, as it appeared at the Parts Show in Paris.

*Winding the voice coil on a flat sheet makes these speakers as thin as electrostatics*

By E. AISBERG and FRED SHUNAMAN

ONE OF THE SURPRISES OF THE PARTS Show in Paris last spring was an entirely new speaker. Based on a novel concept that makes possible a dynamic speaker as flat as an electrostatic, it drew the crowds away from the classic dynamics and the rare electrostatic. It was called the Orthophase and its performance was remarkable.

It is based on the same principle as the ribbon mike. A light ribbon of conductive alloy laid out in the grid design shown in the photograph is attached to an extremely light but rigid sheet of polystyrene foam. The polystyrene is channeled out so that the ribbon rests on raised portions (Fig. 1). Each section of the ribbon is placed in the field of a powerful magnet. When low-frequency current is passed through the ribbon, the entire sheet vibrates, and the amplitude of the oscillations can reach nearly  $\frac{1}{4}$  inch.



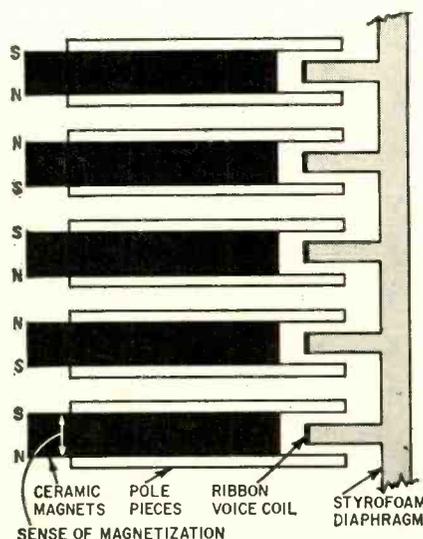


Fig. 1—Cross-section of the Orthophase

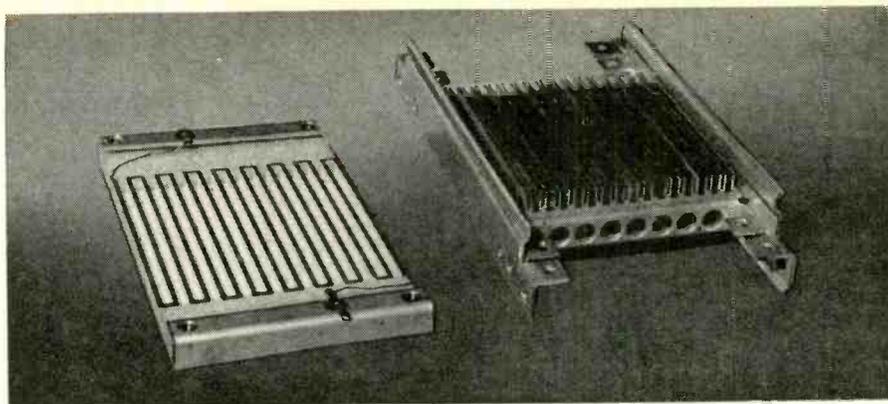
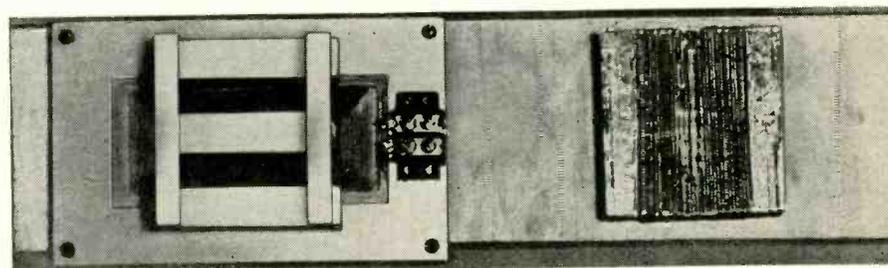
## FLAT VOICE COILS MAKE FLATTER SPEAKERS



Mid-range and high-frequency speakers of the Bogen-Rich system, as they appeared in a recent demonstration model.

The diaphragm thus formed measures 4 x 5 inches. It carries 17 straight sections of the ribbon. Its response characteristic is linear within  $\pm 2$  decibels from 1,000 to 25,000 cycles. The aperture angle at 15,000 cycles is  $30^\circ$  at 6 db down, the power is from 3 to 10 watts, the impedance 0.35 ohm.

Normally, an assembly of several Orthophase cells is used, placed side by side on a cylindrical surface to assure the best spatial distribution of the highs. One advantage to note—no baffle is needed.

A slightly different kind of flat speaker has been announced by Bogen & Rich, of Yonkers, N. Y. It also has a distributed flat voice coil. This one is made of aluminum wire cemented to a thin diaphragm of treated paper. Magnets, as seen in Fig. 2, are placed on each side of the diaphragm, with their like poles facing it. The result is a flat magnetic field over practically the whole face of the moving element. This speaker is designed to cover the range from about 1 to 6 kc. (The complete Bogen-Rich speaker system uses a unique type of cone speaker for the bass range. An 8-inch driver is coupled pneumatically to a larger piston or diaphragm of polystyrene foam.)

Another approach must be used for the region above 6 kc. At about (Continued on page 66)

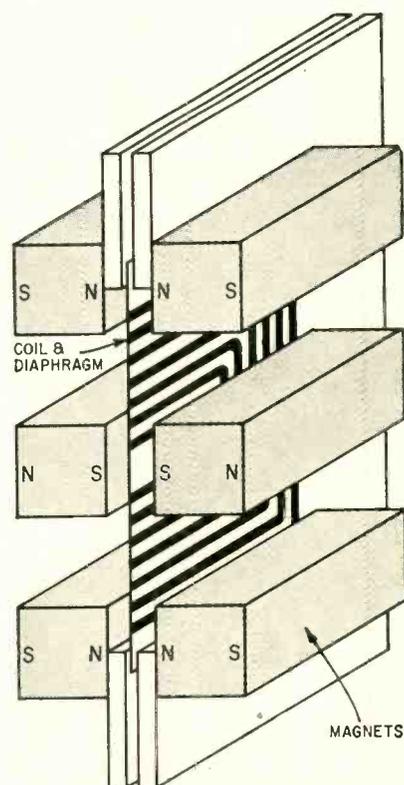


Fig. 2—The new Bogen-Rich mid-range speaker. Note that magnetic arrangement creates flat magnetic field.

# ACTUAL PHOTOS OF TV PICTURES RECEIVED UP TO 248 MILES AWAY

## PULLED IN BY A *Winegard* SUPER POWERTRON TV ANTENNA

We can't guarantee that everyone will get results like this but long distance reception performance is not unusual for the world's most powerful TV antenna.



### Why the Winegard Super Powertron is the Most Effective Antenna Ever Designed—

-  **IT CAPTURES MORE SIGNAL** than any other all-channel antenna ever made. Patented design, electro-lens director system, dual "TAPERED T" driven elements, 30 precision-tuned elements in all.
-  **IT'S THE ONLY TRUE ELECTRONIC ANTENNA.** Only the Winegard Powertron is built with the amplifier as part of the driven element—not an "add-on" attachment.
-  **IT ELIMINATES ALL SIGNAL LOSS** that normally occurs between the driven element and the amplifier due to transmission and coupling mis-match.
-  **IT BOOSTS WEAK SIGNALS UP OUT OF THE SNOW** far better than any other antenna or antenna-amplifier combination made.



ONLY POWERTRON HAS BOTH 300 OHM TWIN LEAD AND 75 OHM COAX TERMINALS ON BUILT-IN AMPLIFIER.



ONLY POWERTRON GIVES YOU YOUR CHOICE OF TRANSISTORS OR TUBES (TUBE MODELS 300 OHM ONLY).



ONLY POWERTRON HAS RANGE AND POLARITY CONTROL SWITCH TO PREVENT OVERDRIVING ON STRONG CHANNELS.




ONLY POWERTRON HAS AC PLUG-IN OUTLET FOR TV SET BUILT INTO THE POWER SUPPLY.



**POWERTRON POWER SUPPLY IS ALL AC—SAFE, SHOCKPROOF.** Transistorized Model has rectifier and filter in power supply—not in amplifier, where servicing is difficult. No nuisance batteries. Costs 27c to operate for a full year.
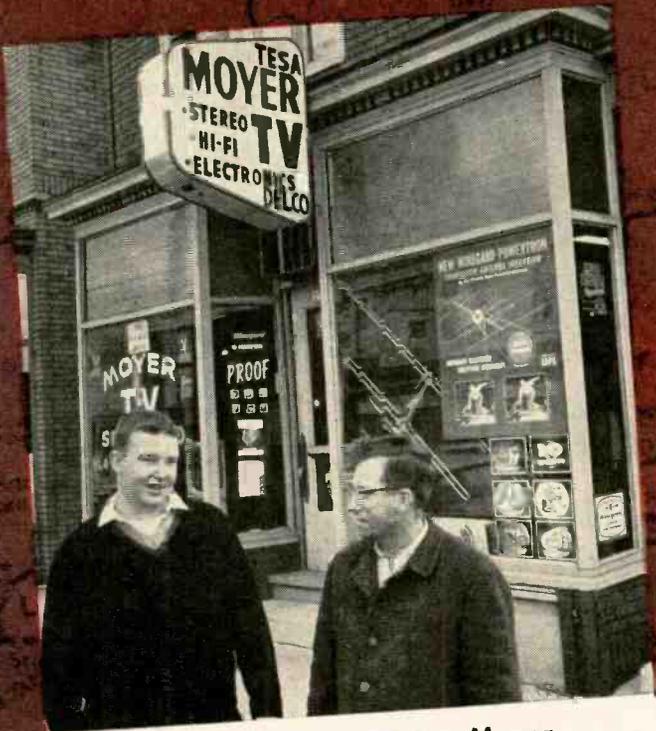
# Read what Charles J. Milton of Moyer TV, Milwaukee, has to say about the Winegard Super Powertron...



Charles Milton and Jim Moyer  
In front of Moyer TV

Of course, everyone can't get reception results like Charles Milton has experienced. Each area has its own unique reception characteristics and problems. But one thing we can promise, the Powertron will deliver more clean pictures on your TV screen than any antenna you can own.



## MOYER TV & RADIO SERVICE

3111 W. NORTH AVE.

2913 W. NORTH AVE.

TESA-MILW.

MILWAUKEE 8, WIS.

Hilltop 4-0740

Winegard Company  
3000 Kirkwood  
Burlington, Iowa

Gentlemen:

I would like to thank the Winegard Company for building the Super Powertron SP-44X.

With this antenna, reception at the local station level is perfect in both black and white and color. At medium range, the Powertron outperforms all others. Channel nine from Chicago, about 90 air miles, comes in clear and regularly. This is the Cubs baseball station and the one Milwaukeeans are willing to pay big money to get.

When the "Big Winegard", as it is affectionately called around the shop, is on long range it probes the unknown alone. All other antennas have fallen far behind. I have picked up eleven stations over 100 air miles away. The farthest of these is WWJ, Channel Four, Detroit, an unbelievable 251 miles. I have included a few pictures that I took off the TV with a Rolliflex F 3.5 at one second using Verichrome Pan.

We use the pictures in a window display and I use a set of pictures to explain the advantages of a Winegard to prospective customers. Believe me the pictures work -- and so does the "Big Winegard."

Sincerely,

*Charles J. Milton*

**POWERTRON IS 100%  
CORROSION-PROOFED**  
ANTENNA IS GOLD ANODIZED,  
ALL HARDWARE IRRIDIZED,  
AMPLIFIER HOUSING OF HIGH  
IMPACT POLYSTYRENE.

## PHOTOGRAPH YOUR OWN TV STATION PICTURES AND SEND THEM IN!

If you own a Powertron, chances are you too are experiencing unusual results. Why not photograph the stations you receive and send them in to us. We are always interested in hearing from Winegard antenna dealers and owners. We will be glad to enlarge your camera shots so that you can make your own window or store display like Moyer TV has done. The photos make

great sales persuaders to prospects and can be used in many ways to sell more Powertrons.

If you have never tried a Winegard Electronic Powertron, give it a test and be agreeably surprised. Don't take our word for it—let your eyes and ears and field strength meter tell the story. For full details and spec sheets, ask your distributor or write.



# Winegard

**ANTENNA SYSTEMS**

Winegard Co., 3013-1A Kirkwood St., Burlington, Iowa



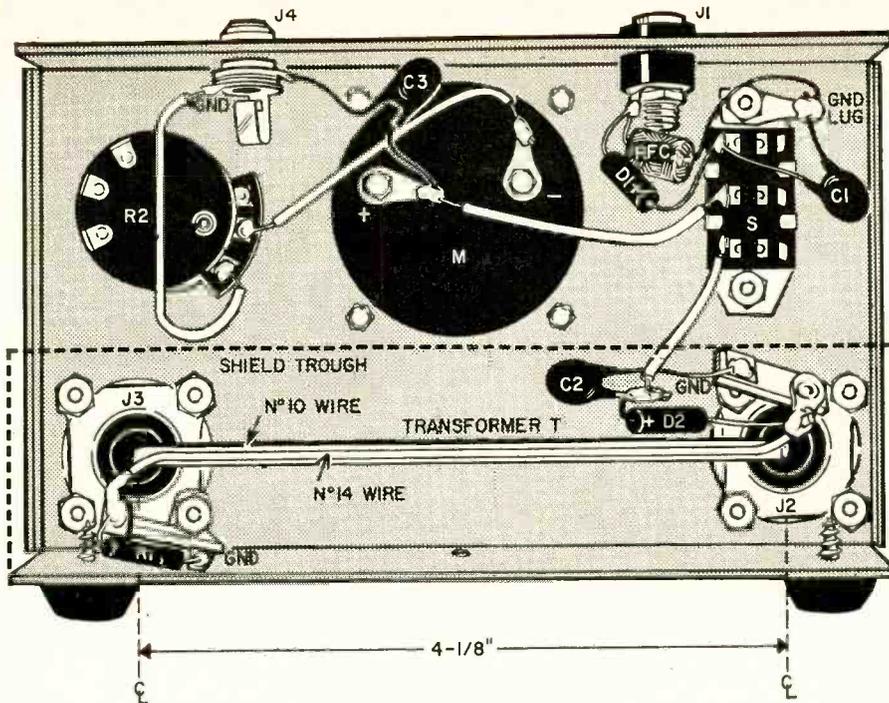


Fig. 2—Pictorial diagram shows you just where the parts go.

potentiometer becomes R2 in the new meter. J1, D1, RFC, C1, M, C3, R2, J4 and the telescopic antenna are all contained in the TM-14. The extra parts needed are T, J2, J3, D2, R1, C2 and S.


After the antenna multimeter is completed and checked out, connect a 1-foot length of RG-58-U coax cable with PL-259 connectors on each end to the transmitter and J3. Connect the antenna to J2. Rotate METER SET control R2 counterclockwise as far as it will go. Press the transmitter button and adjust R2 until the meter reads near center scale. Now transmitter adjustments can be made. The transmitter's final tank circuit is our first concern. The manufacturer's schematic will tell you whether this adjustment is a coil or a variable capacitor. Watch the meter carefully as you slowly tune up. Any increase in

transmitter output will increase the meter reading. The amount of increase depends upon how well the transmitter is matched to the antenna. In any case, adjust for maximum meter reading.

After final power adjustments have been made, check the antenna to determine how well it performs with the power fed into it. Do this by reversing the antenna and transmitter leads. Connect the transmitter to J2 and the antenna to J3. Leave R2 set at the position used when making transmitter adjustments. Now press the transmitter button and note the new meter reading. It is a relative indication of the standing-wave ratio (SWR) in your antenna.

A good antenna will read a tenth or less of the original reading. A fair antenna will read around one-fourth while a poor one will read one-half and up.

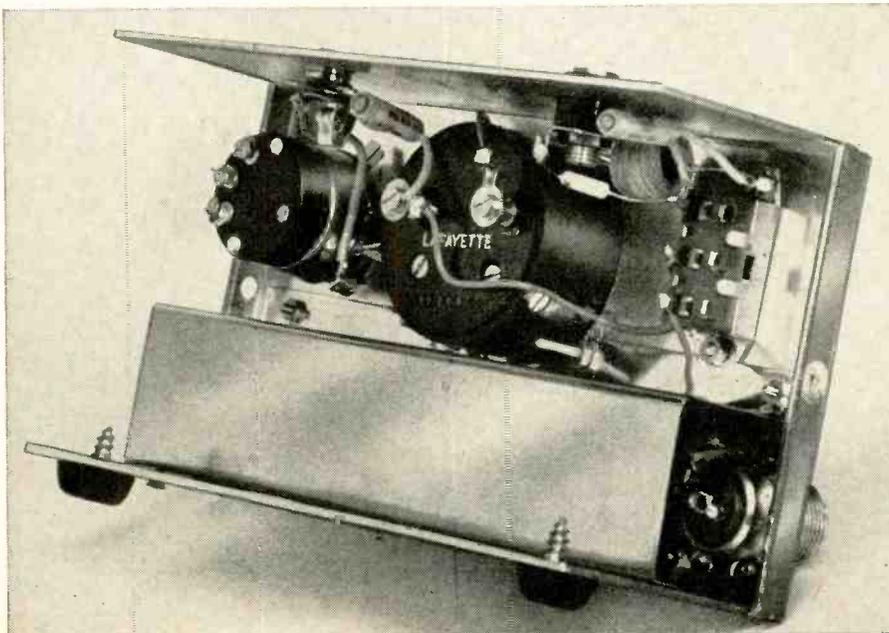Inside the chassis. Note the sheet-metal shield—it covers the two-wire transformer.



This can be calibrated more accurately by checking the unit on a known good antenna. Always remove the antenna multimeter from the transmission line after all tests have been completed.

When testing more than one transmitter (of different makes) on the same antenna, you may find that one unit has a much higher output than another. This does not mean that one transmitter is good and the other is bad. It simply indicates that some units are more efficient than others and that many transceivers are not made to operate at a full 5 watts input power. Many transmitters with 5 watts input power will have about 2 to 2½ watts output while others with the same input will put out 3 or more watts.

#### How it works

As a field-strength indicator, signals are picked up by the telescopic antenna and rectified by a detector circuit consisting of RFC, D1 and C1. From here they are fed via S to the meter and controlled by R2. The signal applied to the meter also feeds through C3 to J4. A high-impedance crystal earphone connected here is ideal for monitoring.

To read power output, the signal from the transmitter is fed into J3 and out into the antenna through J2. The current passing through the transformer primary induces a small current in the secondary. It is detected by D2.

The detected signal is also fed through switch S to the meter. Sensitivity is determined by the setting of R2. For SWR indication, reverse the input and output connections (jacks J2 and J3).

The standing-wave ratio meter circuit in the antenna multimeter uses the basic directional coupler for its operation. The circuit between J2 and J3 represents the primary of a transformer. The line closely coupled to the primary represents the secondary. The primary and secondary are coupled *electrostatically and magnetically*.

Current flowing in one direction in the primary produces currents in the secondary that are the result of electrostatic and electromagnetic coupling. Current flow due to magnetic coupling is dependent on the direction of current in the primary. Current flow in the secondary due to electrostatic coupling is in the form of a charge that travels in both directions from the point of coupling.

Thus, secondary current due to electrostatic coupling adds to the current developed through inductive coupling when measured at one end of the secondary and opposes it when measured at the other end.

This is a simplified form of the Moni-match SWR and power indicator. (QST, October, 1956).

Voltages induced in the secondary are rectified and measured on the meter. The setup is designed so the meter reads only when the rf signal is fed into the INPUT end of the coupler. Rf (reflected or otherwise) coming from the output end will not cause a reading on the meter.

END

PHOTOS

PHOTOS

RADIO-ELECTRONICS can use good photographs of service benches, service shops, high-fidelity audio layouts, and any other interesting and original radio-electronic devices.

We will pay \$10 each for good professional photos or equivalent, suitable for reproduction.

Full information on subject photographed will increase the acceptability.

The Editor,

**Radio-Electronics**

154 West 14th St., New York 11, N. Y.

# INDUSTRIAL ELECTRONIC DICTIONARY

From photoelectric pyrometer to  
proportional control

By ED BUKSTEIN

**Photoelectric pyrometer:** A temperature measuring instrument. The pyrometer is used industrially for measuring the temperature of heated or molten metal in a furnace. The heated metal emits infrared radiation in proportion to its temperature. The higher the temperature, the more infrared emission. If the metal is heated enough, it will emit visible red as well as infrared. At this point it has become red hot. At still higher temperatures the metal will emit radiation throughout the visible spectrum and is now white hot.

The circuit diagram of a photoelectric pyrometer is shown in Fig. 21. The phototube is positioned outside an opening in the furnace so it is illuminated by the infrared (and visible) radiation

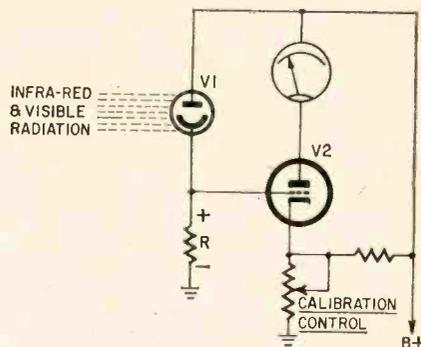


Fig. 21—Photoelectric pyrometer measures temperature of heated metal by monitoring infrared radiation.

from the heated metal. The resulting phototube current produces a voltage drop across resistor R which, in turn, increases V2's plate current. The plate milliammeter is calibrated to read directly in degrees of temperature. A relay may be connected in V2's plate circuit to turn off the furnace when the temperature has reached the required value. This modification permits control as well as measurement of temperature.

**Photoelectric register control:** Photoelectric device used to control the position of a strip of paper, cloth, metal, etc. with respect to the machine through

## If you can't afford a Fisher tuner... build one!

**Introducing the newest Fisher StrataKit: the KM-60 FM-Stereo-Multiplex Wide-Band Tuner.** Fisher FM tuners have always been reasonably priced considering their unsurpassed sensitivity and matchless overall design—but, even so, not everyone can afford them. If economics have thus far deterred you from buying the very finest, the new Fisher KM-60 StrataKit solves all your problems in exchange for a few evenings of entertaining and instructive work. It incorporates Fisher FM engineering at its most advanced, including built-in Multiplex and sophisticated wide-band circuitry—yet it costs almost one-third less than the nearest equivalent Fisher-built tuner.

This spectacular saving involves absolutely no risk, even if you are 'all thumbs.' The StrataKit method of kit construction has eliminated the difference between the expert technician and a totally unskilled person as far as the end result is concerned. You assemble your StrataKit by easy, error-proof stages (strata), each stage corresponding to a particular page in the Instruction Manual and to a separate transparent packet of parts. Major components come already mounted on the chassis, and wires are pre-cut for every stage—which means every page!

In the KM-60 StrataKit, the front-end and Multiplex circuits come pre-aligned. The other circuits are



aligned by you after assembly. That is accomplished by means of the tuner's laboratory-type d'Arsonval signal-strength meter, which can be switched into each circuit without soldering.

**This is the world's most sensitive FM tuner kit,** requiring only 0.6 microvolts for 20 db quieting! (IHF standard sensitivity is 1.8 microvolts.) Capture ratio is an unprecedented 2.5 db; signal-to-noise ratio 70 db. The famous Fisher 'Golden Cascade' RF stage, plus four IF stages and two limiters, must take most of the credit for this spectacular performance and for the superb rejection of all spurious signals. Distortion in the audio circuits is virtually non-measurable.

An outstanding feature of the Multiplex section is the exclusive Stereo Beam, the Fisher invention

that shows at a glance whether or not an FM station is broadcasting in stereo. It is in operation at all times and is completely independent of the tuning meter. Stereo reception can be improved under unfavorable conditions by means of the special, switchable sub-carrier noise filter, which does not affect the audible frequency range.

Everything considered, the KM-60 is very close to the finest FM tuner that money can buy and by far the finest you can build. Price \$169.50.\*

The Fisher KX-200 80-watt stereo control amplifier StrataKit, \$169.50.\*

\*Walnut or Mahogany cabinet, \$24.95. Metal cabinet \$15.95. Prices slightly higher in the Far West.


### USE THIS COUPON FOR FURTHER INFORMATION

Fisher Radio Corporation  
21-51 44th Drive,  
Long Island City 1, N. Y.

Please send me without charge the complete Fisher StrataKit catalogue.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

RE113

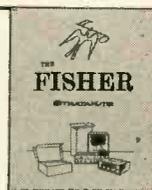

which the strip is passing. One form of register control, for example, is used to wind the strip of material onto a reel. The phototube and its light source are so positioned that the edge of the strip overlaps and blocks half of the light beam. Any sideward motion of the strip either increases or decreases the illumination of the phototube. The phototube output is amplified and controls a motor that adjusts the lateral position of the reel. Sideward motion of the strip of material is matched by an equivalent sideward motion of the reel, and the strip winds evenly with each layer positioned exactly over the layer beneath it.

**Photomultiplier tube:** A type of phototube characterized by extreme sensitivity. A small amount of light reaching the cathode can produce a considerable amount of plate current. As shown in Fig. 22, the photomultiplier contains a number of intermediate electrodes


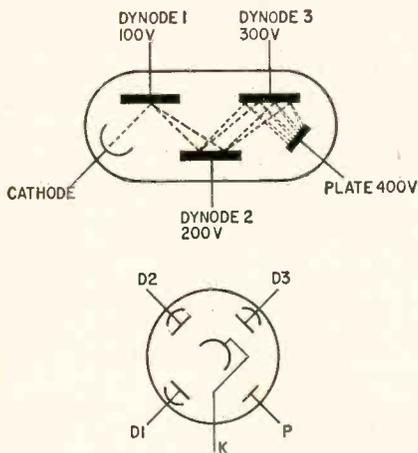
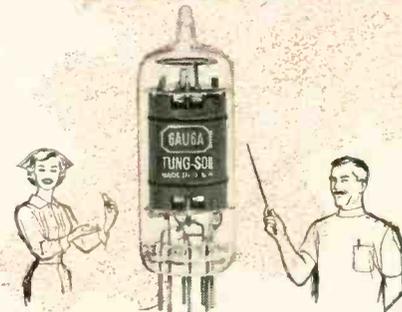


Fig. 22—The photomultiplier tube uses secondary emission to deliver high current gain.

(dynodes) between cathode and plate. Each dynode is operated at a higher positive potential than the preceding one, typically about 100 volts higher. As a result, electrons emitted from the cathode are attracted in succession from one dynode to the next. Furthermore, each dynode emits several secondary electrons for each primary electron it receives. Each electron from the cathode releases several secondary electrons from the first dynode. Each of these electrons releases several secondary electrons from the second dynode, etc. Thousands or even millions of electrons eventually reach the plate for each electron emitted from the cathode. This current gain accounts for the high sensitivity of the tube. For simplicity, only three dynodes are shown in Fig. 22, but 10 to 14 are often used in practice. Current gain typically is in the range of 200,000 to 2,000,000.

**Photo-relay circuit:** On-off type of control actuated by either an increase or a decrease of illumination. In the forward-acting photo-relay shown in Fig. 21, an increase of illumination causes the relay to energize. As illumination increases, the phototube draws  
(Continued on page 74)

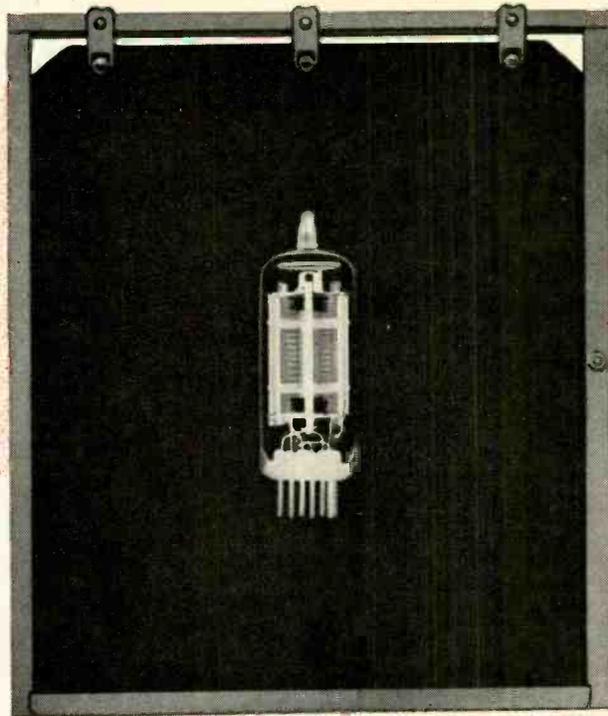

## ABSENCE OF "GRID EMISSION" AND GAS DEMONSTRATES GOOD HEALTH OF TUNG-SOL IF AMPLIFIER TUBES

Radio and TV doctors know that IF amplifier tubes must be physically sound in order to enjoy a healthy long life. Because they operate in a high impedance circuit, internal cleanliness is vital to avoid gas distress. Grid emission, which displays identical symptoms, likewise must be carefully avoided. Tung-Sol's exacting engineering standards and rigid quality control in every step of manufacture assure vigorous long life. Tung-Sol IF amplifier tubes are made in a humidity-controlled, dust-free atmosphere. The operator's hands never touch

the cathode coating. Gas evacuation and metal heating are done with critical precision by means of the most advanced equipment. As a result, Tung-Sol IF amplifier tubes possess unusual stamina and help you to maintain enviable standards in your service business.

### GOOD MEDICINE FOR PROFITS

One of the most highly recommended medicines for profits in radio and TV service business is the prescribing of tubes that are reliable. Cuts radio and TV set hospital visits. You can rely on Tung-Sol tubes.

#### HERE ARE SOME OF THE MORE POPULAR TUNG-SOL IF AMPLIFIERS:

1U4; 6AG5; 3AU6; 4AU6; 6AU6A; 12AU6; 3BA6; 4BA6; 6BA6; 12BA6; 3BC5; 4BC5; 6BC5; 6BH6; 6BJ6; 3CB6; 4CB6; 6CB6; 3BZ6; 4BZ6; 6BZ6; 12BZ6; 3DK6; 4DK6; 6DK6; 12AC6; 12BL6; 12AF6; 12EK6; 12EZ6; 18GD6A; 18FW6A



the first name to ask for when ordering

**TUNG-SOL**  
IF AMPLIFIER TUBES

TUNG-SOL ELECTRIC INC., NEWARK 4, N.J.


Free

ALLIED

444-PAGE ELECTRONICS CATALOG

WORLD'S BIGGEST • MOST COMPLETE

best buys for 1962

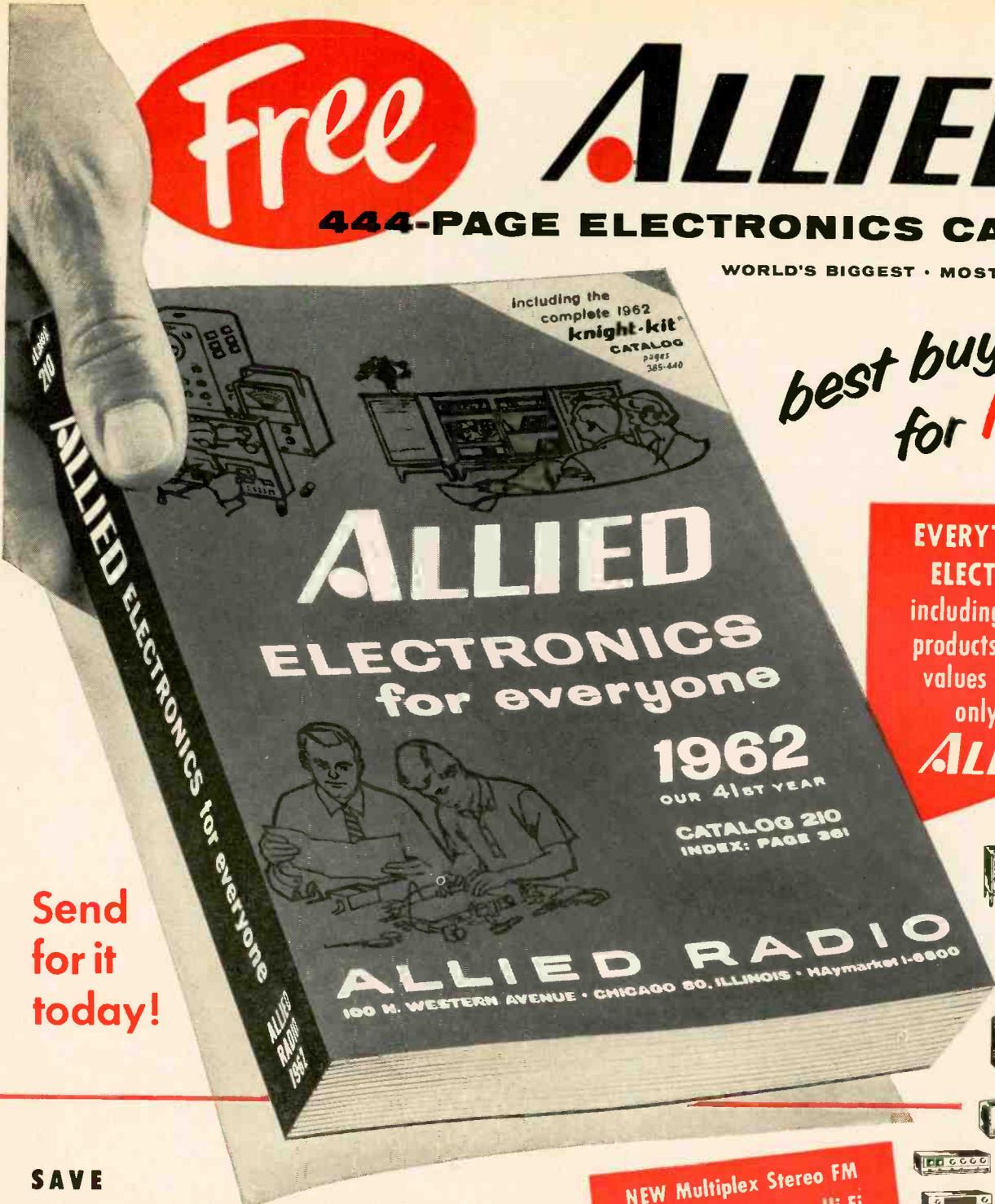

Send for it today!

EVERYTHING IN ELECTRONICS including exclusive products & special values available only from **ALLIED**



SAVE MOST ON EVERYTHING IN ELECTRONICS

- New Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- New Multiplex Stereo FM • All-Transistor Stereo Hi-Fi
- Money-Saving Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Tape Recorders, Tape, and Supplies
- Citizens Band 2-Way Radios • Short-Wave Receivers
- Amateur Receivers, Transmitters, and Station Gear
- Latest Public Address Systems, Paging and Intercom Equipment
- TV Tubes, Antennas, Accessories • Batteries, Wire and Cable
- Test and Laboratory Instruments • Tools, Hardware
- Huge Listings of Parts, Tubes, Transistors, Technical Books

NEW Multiplex Stereo FM All-Transistor Stereo Hi-Fi

new

NO MONEY DOWN on Allied's new Credit Fund Plan

Now—enjoy 50% more buying power—up to 24 months to pay—see our 1962 Catalog for simple details.

exclusive money-saving KNIGHT® products

SAVE MOST on famous KNIGHT Stereo Hi-Fi—comparable to the best in quality, styling and performance, yet priced far lower. Select super-value KNIGHT components or complete systems (including latest Multiplex Stereo and All-Transistor hi-fi) and save most. KNIGHT products are acclaimed by all those who recognize integrity in design and manufacture and who appreciate value.

SEND FOR 444-PAGE CATALOG TODAY!

Satisfaction Guaranteed or Your Money Back

ALLIED

RADIO-ELECTRONICS

**BIG PLUS!**

in your 1962  
**ALLIED**  
CATALOG

includes complete catalog featuring over 90 exciting

**knight-kits**<sup>®</sup> **k**  
A PRODUCT OF ALLIED RADIO

**NEW for '62 and simply great!**  
available only from **ALLIED**

including the  
complete 1962  
**knight-kit**  
CATALOG  
pages  
385-440



All-In-One FM-AM Tuner-Amplifier Kit with latest built-in MULTIPLEX Stereo FM, less case.....\$129.95



MULTI Adapter Kit for stereo reception



Self-Powered Stereo FM Kit.....\$19.95



Deluxe Stereo FM-AM Tuner Kit with latest built-in MULTIPLEX Stereo FM.....\$99.95

ALL-TRANSISTOR 50-Watt Stereo Amplifier Kit, less case.....\$79.95

**new**  
HOBBYIST KITS




ALL-TRANSISTOR Wireless Intercom System Kit (2 units).....\$45.90



TRANSISTORIZED Electronic Tachometer Kit.....\$24.95



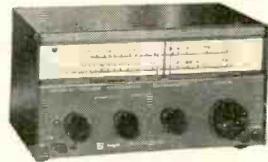Amazing 100-In-1 Electronic Science Lab Kit.....\$29.95



ALL-TRANSISTOR 2-Band AM-Shortwave DX'er Radio Receiver Kit.....\$19.95

**new**



Phone and CW 60-Watt Ham Transmitter Kit.....\$49.95



Mutual Conductance Tube Tester Kit.....\$99.50

**Knight-Kits offer the most satisfying build-your-own experience in the world!**

**5 BIG REASONS WHY:**


- **Convenience Designed**—makes you a kit-building expert—even the very first time!
- **Wonderful to Build**—you'll marvel at the sheer ease of assembly with the exclusive "show-how" manual guiding you like a good instructor.
- **You Own the Best**—you'll enjoy with pride a true custom-built product, professional in its engineering and performance.
- **You Save So Much**—because you buy direct from Allied at our money-saving volume prices—and because you do the easy assembly yourself.
- **Easiest to Buy**—NO MONEY DOWN on Allied's new Credit Fund Plan—easiest terms ever!

**MONEY BACK GUARANTEE:** Buy any Knight-Kit. Build it! Use it! You must be satisfied or you get your money back!

see more than 90 KNIGHT-KITS

- 21 HIGH-FIDELITY KITS
- 25 HOBBYIST KITS
- 31 INSTRUMENT KITS
- 14 AMATEUR & CITIZENS BAND KITS

KNIGHT-KITS are also available in Canada

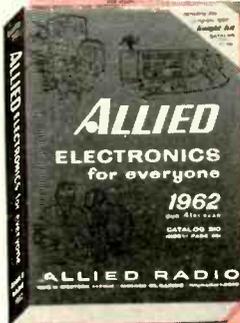

- World's Largest Stocks • Lowest Money-Saving Prices
- Fastest Shipment • Expert Help • Easiest-Pay Terms
- Satisfaction Guaranteed or Your Money Back

send for the world's biggest electronics catalog!

**Free**

ALLIED RADIO, Dept. 200-A2  
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1962 ALLIED 444-page Catalog

Name \_\_\_\_\_  
PLEASE PRINT

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**Send for it today!**

**RADIO** World's Largest Electronic Supply House

JANUARY, 1962



# Astonishing\*

## Cabinart SPEAKER SYSTEMS


outperform high-rated, higher priced systems

**FREE 10 DAY TRIAL OFFER** You Must Be Satisfied Or Your Money Back

### Check These. Cabinart Stand-Out Features

- ✓ Maximum possible speaker response
- ✓ Expertly engineered and matched
- ✓ Newer low resonance
- ✓ Smoother mid-range
- ✓ Less off-color tone

Acoustic dampening material inside

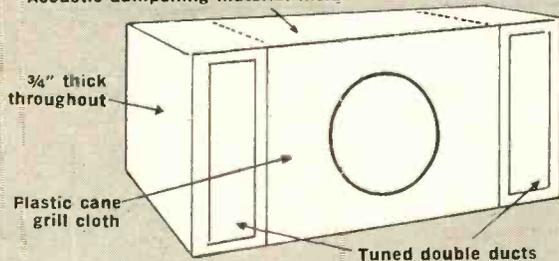

\*E. T. Canby says, "The Cabinart speaker system . . . is really an astonishing piece of equipment at its price which is an unbelievable \$15 — speaker and enclosure, complete and integrated . . . with an 8" speaker inside of quite extraordinary quality. I am really impressed by the sound and by the simple ingenuity of the entire construction." *In Audio, November, 1961.*

Reprint of Mr. Canby's complete review of Cabinart speaker systems is available on request.


Pioneers in hi fi quality since 1948.



Cabinart Is One Of America's Largest Manufacturers of Speaker Systems and Enclosures
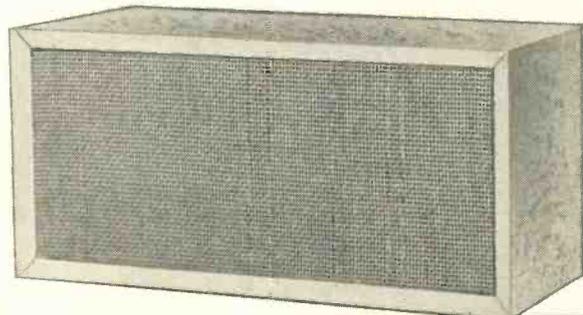
## SPECTACULAR INTRODUCTORY OFFER

Buy direct from Cabinart and **SAVE the difference!**



### mark I 8" model

11" high x 9½" deep x 23" long  
Shipping Weight: 27 lbs.

Genuine Walnut Veneer,  
Oiled Finish \$25.00

Extended range speaker response  
45 to 13,000 cps. 8 Ohm imp.

**\$15<sup>00</sup>**  
Unfinished

Prices F.O.B. Factory

### mark II 12" model

14" high x 11½" deep x 23¾" long  
Shipping Weight: 37 lbs.

Genuine Walnut Veneer,  
Oiled Finish \$36.00

12" coaxial incl. 3" Alnico V PM  
tweeter. 8 Ohm imp. Speaker response  
40 to 15,000 cps.

**\$22<sup>50</sup>**  
Unfinished

Cabinart Acoustical Eng. Corp.  
41 Geyer St., Haledon, N. J.

Please ship the following to be used in my home for 10 full days. I understand unit (s) may be returned and my money refunded within that time unless fully satisfied.

- ..... Mark I Unfinished \$15.00 each
- ..... Mark II Unfinished \$22.50 each
- ..... Mark I Oiled Walnut \$25.00 each
- ..... Mark II Oiled Walnut \$36.00 each

(Please make check or money order payable to Cabinart Acoustical.)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_



# FREE!

## LAFAYETTE

### 340 PAGE 1962 ELECTRONICS CATALOG

*"America's Hi-Fi & Electronics Shopping Center"*

Yours free for the asking — the biggest, best and most comprehensive catalog in the 41-year history of Lafayette Radio. Audiophile, Experimenter, Hobbyist, Technician, Engineer, Student, Serviceman, Dealer — you'll find what you want in this latest Lafayette catalog.



CATALOG # 620

**LARGEST STOCK SELECTION.** Stereophonic Hi-Fi equipment, Citizens Band, Ham and Amateur equipment, Radio & TV parts, Optics, Industrial Supplies, and much more, including all the favorite name brands.

**LAFAYETTE EXCLUSIVES.** Featured are the famous Lafayette Kits . . . dollar for dollar the best value for your money today. You'll also see hundreds of Lafayette specials . . . available only from Lafayette. And, as always, **SATISFACTION GUARANTEED OR MONEY REFUNDED.**

**LOWEST PRICES.** You'll save money too with Lafayette's low, low prices. The lowest prices are always in the Lafayette catalog.

**24-HOUR SERVICE.** Quick, courteous service is your guarantee at Lafayette. Most orders are fully processed within 24 hours after receipt in the mail Order Division.

**NEW EASY-PAY PLAN.**  
Now, **NO MONEY DOWN . . .**  
up to 24 months to pay.



COMPLETELY WIRED.  
FULL SIZE TUBE TESTER  
TE-15..... 19.95



10,000  
OHMS-PER-VOLT  
MULTITESTER  
TE-10..... 9.95



NEW! KORDEX™  
TRANSISTORIZED  
SEMI-KIT TAPE RECORDER  
RT-201..... 17.95

SUPERHETERODYNE  
COMMUNICATIONS RECEIVER  
KT-200, Kit..... 64.50  
HE-10, Wired..... 79.95



NEW!  
FM MULTIPLEX  
ADAPTER  
LT-200..... 39.50



CITIZENS  
BAND  
MOBILE ANTENNA WHIP  
HE-800WX..... 6.95

## LAFAYETTE'S

NEW MAIL ORDER HEADQUARTERS  
111 JERICHO TURNPIKE  
(2 Blocks West of South Oyster Bay Rd.)  
SYOSSET, LONG ISLAND, NEW YORK



LAFAYETTE RADIO, DEPT. JA-2  
P.O. BOX 10, SYOSSET, L. I., N. Y.

- Rush my FREE Lafayette 1962 Catalog 620  
 Please send me # \_\_\_\_\_, shipping charges collect.

I am enclosing \$ \_\_\_\_\_.



340 PAGES

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# PHASE CHECKER SPEEDS HI-FI INSTALLATION

By CHESTER S. LAWRENCE

HOW MUCH TIME DID YOU SPEND PHASING the speakers on that last high-fidelity installation? Ten minutes, twenty, half an hour? And was it right when you got it "checked"? Well, you don't have to go through that again, RCA tells us. You can set them up in 5 minutes and be sure you're right the first time if you use a phase checker.

This test instrument (WG-360A) consists of two little boxes and a length of coax cable. One box (unit A) contains a 4-inch 50-ohm speaker and a phono plug for the inter-connecting cable. The other (unit B) is a bit more complex. It houses a similar speaker and phono jack. In addition, there is a dpdt slide switch, audio transformer, crystal diode and three-lug terminal strip for connecting a vom, vtvm or scope.

The unit works very simply. But let's take a closer look and make sure we understand what it does. We'll assume that we have plugged in the interconnecting cable and placed both units, side by side, in front of the same speaker of the hi-fi system. What we have done is to connect the voice coil of each unit and the primary of the audio transformer in unit B in series. (The circuit is shown in Fig. 1.) Flipping the slide switch from one position to the other reverses the polarity of one voice coil in relation to each other.

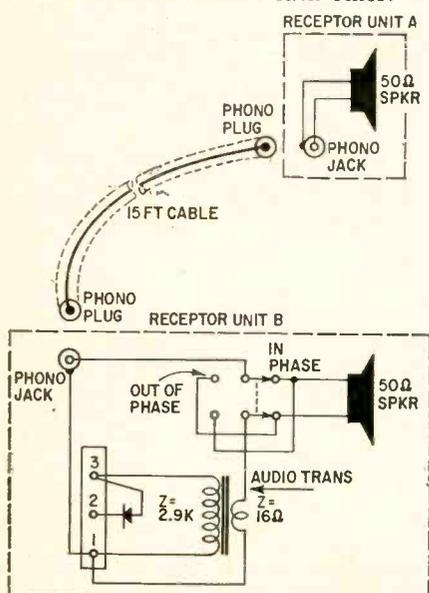


Fig. 1—Circuit of phase checker. Two units are connected with coax cable.

Now we connect the vtvm, vom or scope to the proper terminals on the rear of unit B (Fig. 2).

The audio waves from the speaker cause a similar motion in the phase-checker receptor units. When both are being driven from the same source, as is being done here, their voice coils move in phase with each other.

This movement produces a small ac output voltage across the voice coil. Naturally, this voltage varies according to the material being fed to the speaker. Assume that at some particular instant the voltage across the receptor unit voice coils is 0.1 volt.

Now we glance over at the meter we have connected to the terminal strip on unit B. If the switch on this unit is set to its in-phase position, the two voice coils are connected into a series-adding circuit, and the voltages appearing across the two voice coils are added, giving a total of 0.2 volt at the transformer primary. To insure an accurate reading, put your vom on its 0.25- or 1-volt range and turn up the gain control of the amplifier until you get a mid-scale reading on the meter.

If we now set the switch to its out-of-phase setting, the voice coils are out of phase and cancel each other. In practice, variations between the speakers cause the voltages produced in each voice coil to differ. Therefore, there isn't complete cancellation. However,


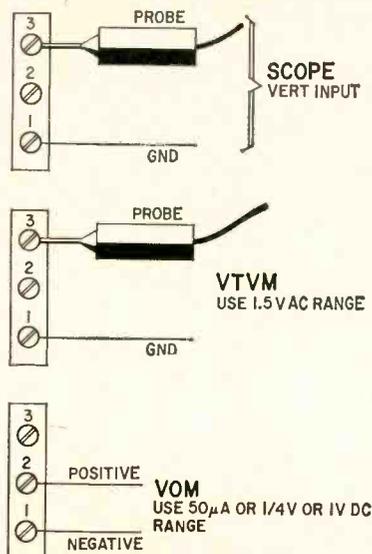


Fig. 2—How to connect meter probes when working with the unit.

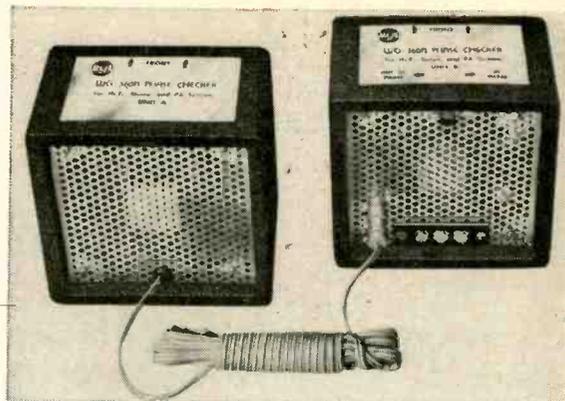

the drop will be easily noticeable. On actual program material the meter reading will fluctuate but, even so, you will have no trouble judging the larger signal.

Well, we're finished with the theory. Now let's see how the phase checker works on an actual installation. We place one receptor unit in front of the bass speaker for the right channel and the other receptor unit in front of the bass speaker for the left channel.

Next we hook our vom or other indicator to the proper terminals on the back of unit B, connect a monaural program source to the preamp input and set the balance control for equal output from the right- and left-channel speaker systems.

If the speaker systems are in phase, you will read the highest voltage when the switch is in the in-phase position. If you find you are getting the highest reading when the switch is in the out-of-phase position, the leads connecting to one system must be reversed.


An audio generator makes using this unit a joy, especially on installations where the speakers may not be absolutely identical. Set a signal generator for approximately 120 cycles and connect it to the amplifier input. Insert a shorted plug into the jack on unit B. Place the unit in front of one of the speakers and adjust the amplifier volume to a voltage reading of, say, 0.2 volt. Then place the unit in front of the other speaker and adjust the volume for an equal reading. You may have to go back and forth several times, adjusting both volume and balance controls before you get this straight. Once the volume is equal, check for proper phasing as before.

To check the phase of a woofer against a mid-range unit, hook up the audio generator again. This time set it to provide a sine-wave signal near the supposed crossover frequency. Using unit B as above, adjust the output frequency until each speaker is producing the same voltage. Then check for phasing as before. The phase checker works on frequencies below 4,000 cycles only. Don't try it to phase a tweeter or a super-tweeter.

The procedure sounds more complex than it really is. Once you try it you will find it takes less time to complete the procedure than to read this article.

END

# For a Cooler Scope

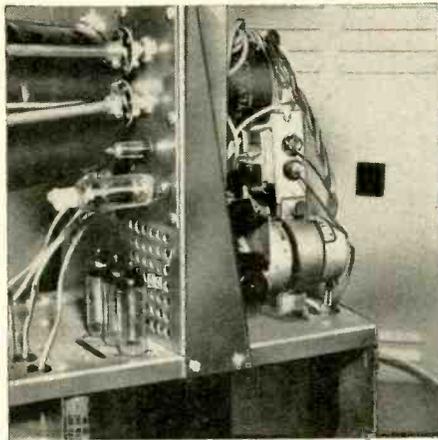

We won't say that when the Heath Co. built the OP-1 they built something as good as an \$800 or \$1,000 Tektronix scope. But they have come within shooting range. At Oregon Tech we do have seven or eight Tektronix scopes, but hardly enough for every student. We find the OP-1 often serves just as well.


The casual user probably does not use a scope more than an hour at a time. In our case, a scope may easily be run for half a day. Under these conditions the OP-1 gets pretty hot.

Having some surplus blowers on hand, we decided to incorporate a cooling system in our OP-1's. The photo shows the details of the installation. There is enough room on the rear of the chassis to mount the blower. Adding a neatly cut hole in the cabinet housing opposite the fan exhaust and drilling a number of holes in the upright rear panel allows hot air to be pulled out from the front of the scope. The scopes run cool all day. —R. E. Baird and J. A. Brady
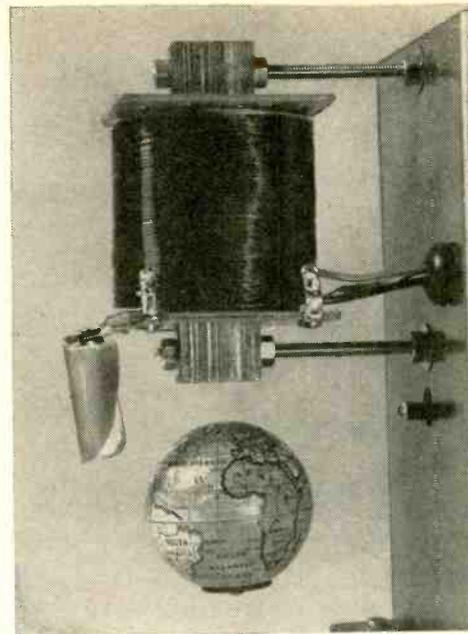
## Bacteria Batteries Improving

A new "bio battery" using bacteria to help generate electricity is reaching the stage where the Navy is planning to run ocean tests on it, according to recent reports. Batteries of this type have been constructed (See "Bugs in New Batteries," RADIO-ELECTRONICS, August 1961, page 6), but so far only insignificant amounts of power have been generated. The new battery, being developed by Magna Products, a subsidiary of Thompson-Ramo-Woodridge, can generate enough power to operate radio beacons, signal lights and similar equipment.

With the help of bacteria or enzymes, it might become possible to produce electricity from a wide variety of fuels or oxidants, such as vegetation or raw sewage. Batteries for ocean use would find a plentiful supply of fuel in the ocean water itself, which could also serve as the electrolyte for the battery.



World remains suspended in space, with North magnetic pole upward.

# PHOTOMAGNETIC TOY IS TRUE SERVOMECHANISM

By H. SCHREIBER

IT IS DIFFICULT TO EXPLAIN TO A LAYMAN in a few words just what a servomechanism is. But if, instead of depending on words, we demonstrate with a functioning piece of apparatus, we get the idea across quicker. If we want the education thus acquired to remain indelibly in the spectator's memory, the best thing to do is to choose a really spectacular application for an example. (We also arouse in the layman a certain respectful admiration for the possibilities of electronics.)

The apparatus we put together to carry out these general ideas is based on a very simple principle (Fig. 1). We decided to suspend—without any visible means of support—a little sphere of sheet metal (in this case, a tiny terrestrial globe that formed part of a pencil sharpener of the type found in 5-and-10-cent stores). This was done very simply by using an electromagnet

in which the exciting current was proportional to the light falling on a photocell. This cell is so aligned with a small light bulb that the globe cuts the light beam as it is drawn toward the magnet. The light on the photocell—and at the same instant the current through the magnet—diminishes as the globe approaches the iron core that attracts it. The force of attraction drops to the point where the globe finds a position of equilibrium, where it will remain indefinitely, even though spectators attempt to jar or blow it out of place. It is even possible to spin the globe. Since friction of the air and eddy currents are the only braking effects, it rotates for a long time.

As can be seen in the photo, the North pole of the globe points upward. This is done by taking out the pencil sharpener (which was at the South pole) and replacing it with two discs of bakelite kept in place with a screw. By adjusting the position of the screw carefully, it is possible to keep the North magnetic pole (situated in northern Canada) pointing upward, a detail that never fails to surprise the curious.

### How it's done

The diagram of our little demonstration apparatus is shown in Fig. 2. It is equipped entirely with semiconductors, but of course could be made with vacuum tubes or even other amplifying elements.

The power supply consists of two silicon diodes. A 1,000- $\mu$ f capacitor acts

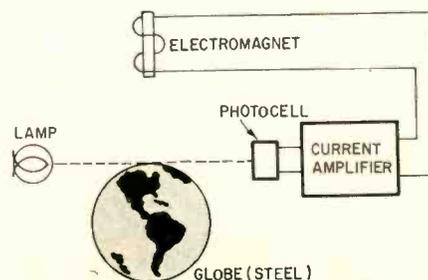


Fig. 1—As globe is attracted by electromagnet, it begins to block light beam, reducing magnetizing current.

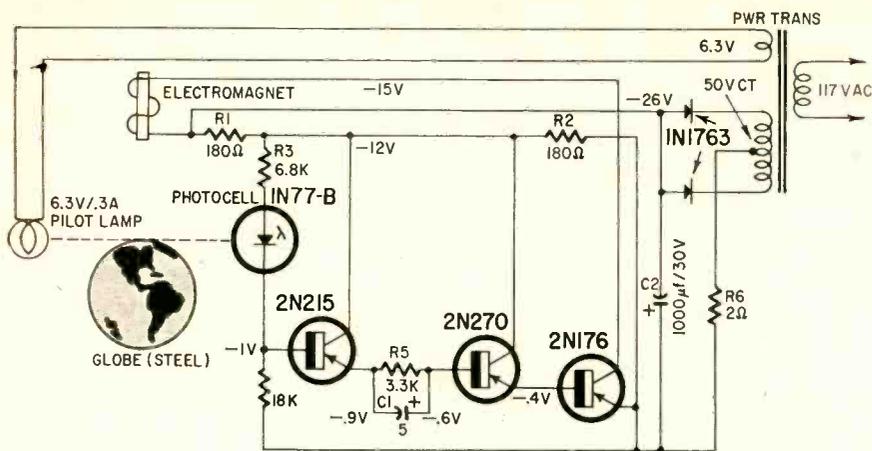


Fig. 2—Schematic. The photodiode is followed by a dc amplifier that controls the magnet. Original semiconductors were French. Diagram shows closest U.S. types.

as a filter. Resistor R6 protects the diodes in case of sudden surges. R1 and R2 are a voltage divider to drop the voltage for the photodiode and the two first amplifier transistors. Part of the dark current of the photodiode flows through R4; its value is chosen to bias the base of V1 till the current in the electromagnet winding is about 50 ma when no light shines on the photodiode. To obtain a lower resting current, simply reduce the value of R4. This, of course, will reduce the amplifier gain and make a stronger light necessary.

The electromagnet winding is in the collector circuit of power transistor V3, which is preceded by two stages of amplification working in a common-collector circuit. The only peculiarity of this preamplifier is the circuit made up of R5 and C1. It is intended to compensate for the thermic time constant of the transistors.

Fig. 3 illustrates the effect of this not-too-well-known characteristic of the transistor. When a voltage ( $V_b$ ) is applied to the base, the collector current ( $I_c$ ) rises at first very rapidly to point A. The rise time depends only on the internal capacitances of the transistor and the reactance of the load. It is so short that it is not significant in comparison with the inertia of our little tin globe. This is not the phenomenon we observe during the following 20 or 25 milliseconds; the increase in collector current is due then to heating of the junction by the power dissipated. At point B, the heat of the junction has become stabilized; the further very slight increase is explained by warming of the case (or radiator) of the transistor. The thermic time constant of the junction is—for practically all transistors—in the order of 8 milliseconds.

To compensate for this, it is necessary only to insert an R-C circuit of the same time constant. That of the correction used here is actually 16 milliseconds, for it must compensate for the effect of the two transistors. If this compensation is not used and the emitter of the first transistor is connected directly to the base of the second, the system becomes unstable. After being put in place, the globe

starts to oscillate with increasing amplitude and immediately leaves the magnet's field of attraction.

The core of the magnet has a cross-section of  $\frac{1}{2}$  by  $1\frac{3}{16}$  inch (14 x 20 mm). Its length is  $3\frac{3}{8}$  inch (85 mm). The winding is No. 26 AWG close-wound approximately  $\frac{1}{2}$  inch deep. (The dc resistance of the winding is about 35 ohms.)

The voltages measured at various points on the equipment, with the globe in place, are marked on the diagram (Fig. 2). The graph of Fig. 4 shows the current in the electromagnet in terms of the attractive force, the distance between the globe and magnet core being 1 cm. Under the conditions shown, the equilibrium becomes precarious at about 26 grams (1 ounce


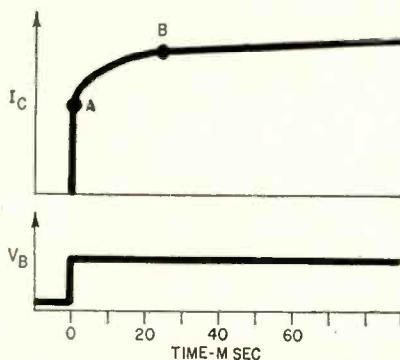


Fig. 3—To compensate for the junction's thermic time constant, series resistance R5 brings point B to the level where point A would have been without correction.

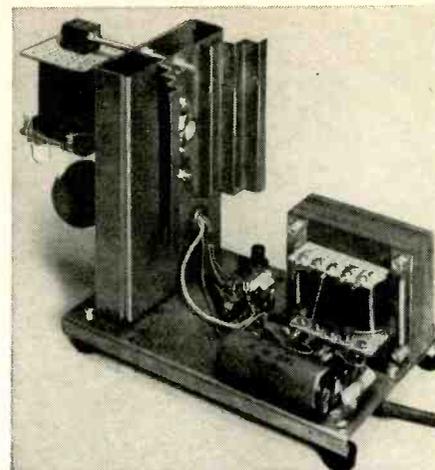

Rear view shows the servomechanism details.

roughly). The slightest current of air will release it from the attractive force of the magnet. Presumably the equipment could be made to work with greater weights by reducing the distance or increasing the power of the amplifier.

#### Applications

This apparatus was constructed with no other aim than to make a demonstration piece. That, of course, does not mean that there may not be practical applications of the principle on which it is based. A somewhat similar setup has been used as a frictionless bearing in an electric watt-hour meter. And maybe sometime you will want to paint a small metallic object on all its faces in such a fashion that no one can tell which of the faces it was placed on to dry!

END

The apparatus described was developed at the Superior Institute of Electronics, Paris.

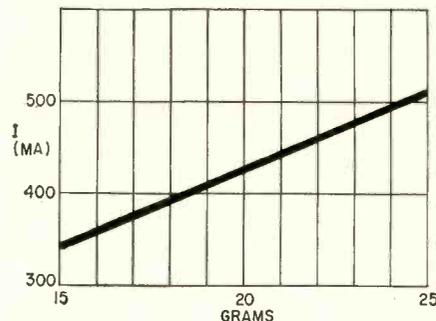


Fig. 4—Current in the electromagnet vs weight attracted, at a distance of 1 cm.

You'll never see this headline in Radio-Electronics

(almost) **NEW TUBES CHEAP**

no fine print, no flim-flam, no hidden-ball tricks permitted in Radio-Electronics mail-order tube advertising. Since January 1956, we have insisted that all mail-order tube advertisers state the exact condition of the tubes they are selling. This has cost us advertising — but it protects you against fraud.

# Wake Up



A new day is dawning in electronics. Transistors are here to stay... they are now being used everywhere; in radio, television, Hi-Fi, intercoms, and in nearly all new electronic equipment...

Why put off transistor circuit servicing any longer... there's gold in them thar hills. But you must be equipped to do the job fast and efficiently. Here are the tools that you will need.



## NEW SENCORE TRANSI-MASTER

This Tester will analyze the entire circuit in minutes and test transistors in-circuit or out of circuit. Here is how you can pin point troubles step by step.

First, check the batteries with the 0 to 12 voltmeter. If the batteries are O.K., check the current drain with the 0 to 50 milliamp meter. A special probe is provided so that you do not need to break the circuit. Excessive current indicates a short; low current indicates an open stage or cracked board. All PF schematics indicate average current.


If trouble is not located by now, isolate the trouble to a specific stage by touching the output of the harmonic generator to the base of each transistor and note spot where sound from speaker (or scope where no speaker is used) stops or becomes weak. The generator becomes a sine wave generator for audio stages to help find distortion.

If trouble points to a transistor, check it in a jiffy with the exclusive in-circuit power oscillator check provided by the TR110. A special probe is also provided for this.

If the transistor checks bad in-circuit, remove it and give it an out of circuit check with the oscillator check or the more accurate DC check.

The DC check is provided for comparison reasons, experimental or engineering work and to match transistors in audio output stages. Beta (current gain) is read direct or on a good-bad scale for service work.

DEALER NET. ONLY **\$4950**

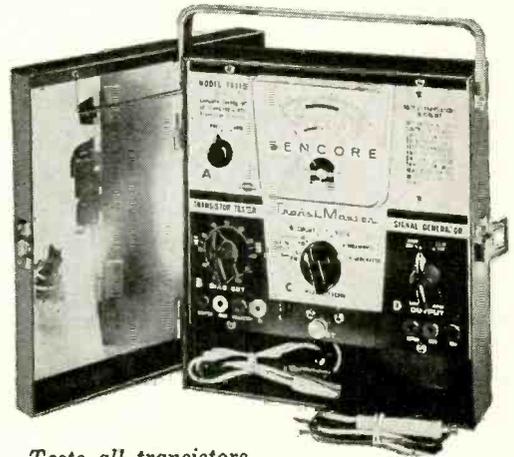

Tests all transistors in-circuit or out-of-circuit

### Model TR110

It's a COMPLETE TRANSISTOR TESTER

- SIGNAL TRACER • VOLTMETER
- BATTERY TESTER • MILLIAMMETER



## NEW SENCORE TRANSISTOR AND DIODE CHECKER

Here is a low cost tester that has become America's favorite. The TR115 provides the same DC out of circuit checks as the TR110; leakage and current gain. Beta (circuit gain) can also be read direct or as good or bad. Opens or shorts in the transistor are spotted in a minute. The TR115 checks them all from power transistors to the small hearing aid type. Japanese equivalents are listed also. This famous tester is used by such companies as Sears Roebuck, Bell Telephone and Commonwealth Edison. New circuits enable you to make service checks without set-up charts even though charts are provided for critical checks.




Model TR115  
Dealer Net  
**\$1995**


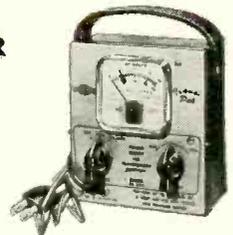
## SENCORE BATTERY ELIMINATOR AND TROUBLE SHOOTER

For replacing batteries during repair.

Many servicemen say that they wouldn't service transistor circuits without this power supply. The tried and proven PS103 is a sure fire answer. It can be used to charge the nickel cadmium batteries as well. Dial the desired output from 0 to 24 volts DC and read on meter. Low ripple insures no hum or feedback. Total current drawn can also be read on the PS103 by merely flicking the function switch to milliamps. The PS103 is the only supply that will operate radios with tapped battery supplies such as Philco, Sylvania and Motorola. No other supply has a third lead.



Model PS103  
Dealer Net  
**\$1995**

Now in stock at  
your Authorized  
Sencore Distributor



**SENCORE**  
ADDISON, ILLINOIS



**FREE**

**11 OLSON STORES PLUS MAIL ORDER**

Olson Stores In:

**FREE**

**AKRON, OHIO**  
69 W. State Street

**FREE**

**ATLANTA, GA.**  
485 Peachtree St.

**FREE**

**BUFFALO, N.Y.**  
711 Main Street

**FREE**

**CHICAGO, ILL.**  
4101 N. Milwaukee Ave.

**FREE**

**CHICAGO, ILL.**  
123 N. Western Ave.

**FREE**

**CLEVELAND, OHIO**  
2020 Euclid Ave.

**FREE**

**CLEVELAND, OHIO**  
6813 Pearl Road

**FREE**

**COLUMBUS, OHIO**  
142 N. High Street

**FREE**

**MILWAUKEE, WISC.**  
423 W. Michigan

**PITTSBURGH, PENN.**  
5918 Penn Avenue

Fill in coupon for a FREE One Year Subscription to OLSON'S Fantastic Bargain Packed Catalog—Unheard of LOW, LOW WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

MAIL TO: ■■■■■



**OLSON ELECTRONICS**  
728 S. Forge Street  
Akron 8, Ohio

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

# SHORT-WAVE FORECAST

Dec. 15—Jan. 15

By **STANLEY LEINWOLL†**

TYPICAL WINTER RADIO PROPAGATION CONDITIONS WILL CONTINUE THROUGHOUT the forecast period. During the daylight hours, maximum usable frequencies will remain at relatively high values, dropping off sharply after sunset.

In the Northern Hemisphere, atmospheric noise levels are at their lowest during the winter months. As a result, signal-noise ratios are high.

Although openings on the 21-mc band are expected to be fairly frequent, the 15- and 17-mc bands are expected to continue the best for long-distance reception during daylight hours.

During the evening and night hours, the 6- and 7-mc bands will be good from most parts of the world, with openings in the 4-mc broadcast band during periods when static levels are lower than usual.

Sunspot activity has now dropped to the point where dx reception on 26 mc will be the exception rather than the rule. With sunspot numbers continuing to decrease steadily, it is unlikely that there will be any 26-mc reception via the regular F-layers of the ionosphere for a number of years once the present winter period has passed.

The tables show the optimum broadcast band, in megacycles, for propagation of programs between the locations shown during the time periods indicated.

To use the tables, the listener selects the one most suitable for his location, reads down the left side to the region he wishes to hear, then follows the line to the right until he is under the appropriate time. (Time is given at the top of each table in 2-hour intervals from midnight to 10 pm, in your local standard time.) The figure thus obtained is the short-wave band (in megacycles) nearest to the optimum working frequency.

For example, a listener in New York City would use the Eastern USA table. He would be most likely to hear broadcasts from West Europe in the 11-mc band at 4 pm, EST.

## EASTERN US to:

	Mid	2	4	6	8	10	Noon	2	4	6	8	10
West Europe	6	6	6	9*	21	21	21	15	11	9	6	6
East Europe	6	6*	6*	7*	21	21	15	11	7	6	6	6
Northern Latin America	11	9	9	11	15	17	15	17	17	15	11	11
Southern Latin America	11	11	9	11	15	15	15*	17	17	15	11	11
Near East	7	7	6*	9*	21	21	15	11	9	9	7	7
North Africa	7	7	7	9*	21	21	17	15	11	11	9	9
South & Central Africa	9	7	7*	15	21	21	21	15	15	11	11	9
Far East	9	9	9	7	9	7*	9*	7*	7*	15	15	11
Australia & New Zealand	9	9	9	7	11	11	15	15	15	17	15	11

## CENTRAL US to:

West Europe	6	7*	7*	9*	21	21	15	11	9*	6	6	6
East Europe	7	7	7*	9*	17	11	9*	9*	9	9	7	7
Northern Latin America	11	9	7	15	17	17	15	17	17	15	11	11
Southern Latin America	11	9	7	15	15	17*	17*	17	17	15	11	11
Near East	9	7*	7*	9*	17	15	11	9	9	9	7	7
North Africa	7	7	7*	7*	17	17	15	11	9	9	7	7
South & Central Africa	9	9	7*	15	21	21	21	17	15	11	11	9
Far East	7*	7*	7	7	9	9	7*	9*	21	21	11	9
Australia & New Zealand	11	11	9	7	11	11	15*	15	17	17	15	11

## WESTERN US to:

West Europe	6*	7	7*	9*	21	17	15	7	7	6	6	6*
East Europe	7	7	7*	7*	15	15	15	9	9	7	7	7
Northern Latin America	9	9	9	9	15	15	15	17	17	15	11	11
Southern Latin America	11	9	9	11	15	15*	17	17	17	15	11	11
North Africa	7	7	7	11	21	17	15	9	9	9	7	7
South & Central Africa	9	9	7*	11	21	21	21	15	15	11	11	11
Far East	7	7	7	7	7	7	9	17	21	17	11	9
South Asia	7	7	7	7	9	15	11	11*	15	15	15	9
Australia & New Zealand	11	11	7	7	11	11	15	15	21	21	17	15

†Radio-frequency and propagation manager, RADIO FREE EUROPE.

\*Reception may be very poor or impossible on this path at this hour.






INDIVIDUAL  
WIDE-VIEW  
SCALE FOR  
EACH RANGE  
GIVES

# Quick, Direct, Error-Free Readings *without Multiplying!*


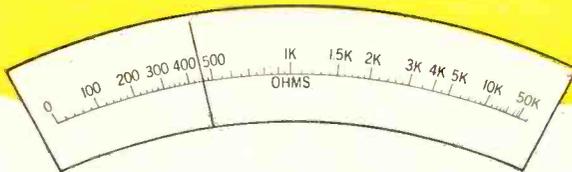
## New VTVM DYNAMATIC 375 Automatic Vacuum-Tube Voltmeter

- Individual Full-Size Scale for Each Range
- Range Switch Automatically Sets Correct Scale
- Only One Scale Visible at Any One Time
- All Scales Are Direct Reading
- No Multiplying . . . No False Readings
- Includes DC Current Ranges, too



Here's another exciting first by B&K. With direct-reading single scales, this professional *automatic* VTVM makes it easier, faster than ever to read the exact answer accurately on the correct scale . . . *without reading difficulty, calculation, or chance of error.* Greatly simplifies true reading of peak-to-peak voltages of complex wave forms in video, sync and deflection circuits, pulse circuits, radar systems, etc.

All scales are direct reading. Every scale is the same full size, and only one scale is visible at any one time. *Once you set the range switch properly, it is impossible to read the wrong scale.*

The DYNAMATIC 375 utilizes a single DC-AC ohms probe, anti-parallax mirror, and other desired features . . . to make accurate measurements with utmost convenience and reliability in laboratory, factory production, or service shop.

*Includes sturdy swivel stand which permits tilting "375" to any desired viewing angle, swings up as convenient carry-handle.*

<b>Ranges: DC Volts</b>	0 - 1.5, 5, 15, 50, 150, 500, 1500
<b>AC Volts (rms)</b>	0 - 1.5, 5, 15, 50, 150, 500, 1500
<b>AC Volts (peak-to-peak)</b>	0 - 1.5, 5, 15, 50, 150, 500, 1500
<b>DC Current</b>	0 - 5 ma, 50 ma, 500 ma
<b>Ohms</b>	0 - 500 ohms, 5 k, 50 k, 500 k, 5 meg, 50 meg, 1000 meg

**Input Resistance:** 11 megohms on all DC ranges

**Accuracy:**  $\pm 3\%$  full scale AC and DC

**Meter Movement:** Sensitive 100 microampere

**Precision Multiplier Resistors** with  $\pm 1\%$  accuracy

**Anti-Parallax Mirrored Scale** for precise readings

**Easy-to-See Iridescent Knife-Edge Pointer**

**Single DC-AC Ohms Probe** (supplied)


**Includes 1½ volt Battery.** Operates on 117 volts 50-60 cycle AC

**Sturdy, handsome metal case** with convenient combination swivel stand and handle. **Size:** 10¾" x 6¾" x 4" deep. **Net wt:** 8 lbs.

Model 375

Net, \$89<sup>95</sup>

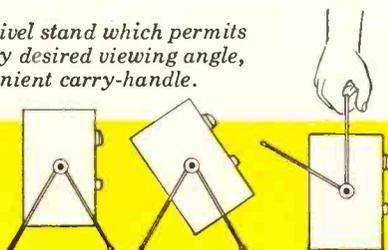See Your B&K  
Distributor  
or Write for  
Catalog AP18E




**B&K MANUFACTURING CO.**  
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.


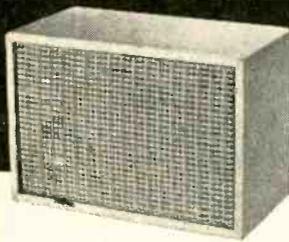
# the HiFi STEREO COMPACT EXTENSION SPEAKER

THIS AMAZING SPEAKER WILL BRING THE FINEST SOUND YOU HAVE IN YOUR HOME TO ANY ROOM YOU DESIRE.



Here is a speaker system ideal for the home, office or even industrial applications where clear undistorted sound is required.

By simple connections to your present sound source, such as Hi Fi and stereo components, consoles, TV, radio and public address or intercom systems, the "compact" will produce crystal clear sound with almost no distortion, even at high volume levels. Dimensions of cabinet 5" x 7" x 10".

**\$695**  
UNFINISHED

### 100% MONEY BACK GUARANTEE

If you do not feel this is the finest dollar value you have ever received in the high fidelity industry

NEWPORT MANUFACTURING CORP. RE  
1823 E. 40th St., Cleveland 3, Ohio

Please send \_\_\_\_\_ Compact Systems

Name \_\_\_\_\_

Address \_\_\_\_\_

Enclosed find  Money Order  Check


Please add 75¢ per unit to cover shipping and handling.

## What's Your EQ December Solutions
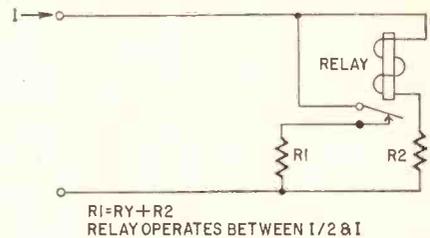
### What's the Sync

The technician first thought that the trouble must be due to an open cathode but, since there was obviously grid rectification and the cathode would have to be in circuit to produce it, he discarded this idea.


The trouble was finally found to be an open 2.2-meg grid resistor. This made the tube block since there was no grid return. Measuring with the vtvm provided an 11-megohm resistance to ground and the tube operated almost normally, but of course it blocked again when the vtvm was moved to measure the plate voltage!



In theirs, there is a resistor, R1, in parallel with a relay and a second resistor, R2. R2 and the relay coil together have exactly the same resistance as R1. Normally closed contacts of the relay connect the circuit through R1, and the relay is supposed to operate anywhere between 1/2 and 1. With one dry cell applied, the current divides between the two paths. With two dry cells, 2I starts to flow. This immediately actuates the relay, opening the circuit to R1. R2 and the relay now pass the same amount of current as one cell put through the two parallel channels.

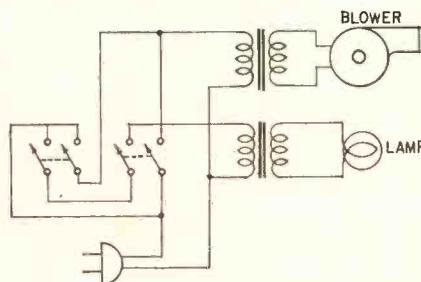
### Correct Switching

The circuit below is so arranged that no matter which switch is thrown first, the blower will be turned on first and off last, thus assuring air cooling at any time the lamp is burning.


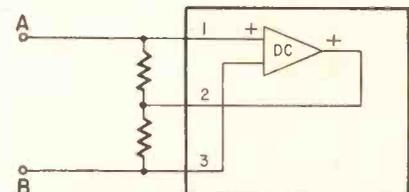
### Infinite Black Box

Terminals 1 and 3 are the input to a dc amplifier with a voltage gain of 1 and no phase inversion. The output of the amplifier is between terminals 2 and 3. Thus for any input between terminals 1 and 3, the same voltage



will appear at terminal 2. Both ends of R1 are then at the same voltage, no current can flow in the resistor and the input resistance is infinite. This is a good example of feedback increasing the input impedance of a voltage amplifier.

### Black Box No. 5 (September)

Two ingenious solutions to Black Box No. 3 (September, 1961) have been submitted. If you remember, the puzzle was a black box with two terminals. First one dry cell was connected to it, then two dry cells. In each case, the current was the same. What was in the black box was actually a nice, solid short circuit. Therefore the current depended only on the internal resistance of the cells, which of course increased in proportion to the voltage (number of cells in series), keeping the current the same.

Reader Ray R. Stark suggests that the external cells might have been 2-volt storage cells, and that two dry cells could be contained in the black box. Then whether one wet cell at 2 volts was applied, or two wet cells at 4 volts, the difference in both cases would have been 1 volt, and the current the same, though in reverse direction.

Readers W. Kaune and J. Molberg of Seattle have another solution.



"You have a wastebasket?"

# NEW PRODUCTS

**TEST SOCKET ADAPTERS, model 1449** (illus.), model 1447, 9- and 7-pin types respectively, simplify testing of tube pins for voltages or resistance by eliminating need for removing tube shields. Test tabs of sockets clear tops of captive or telescoping tube shields. Inter-element distrib-




uted capacitance about 1.5  $\mu\text{f}$ ; voltage breakdown elements exceed 1800 volts ac-dc. Insulation resistance more than  $5 \times 10^5$  megohms.—Pomona Electronics, Inc., 1500 E. 9th St., Pomona, Calif.

**AC VTVM, model 1M-21**, offers frequency response 10 cycles to 500 kc  $\pm 1\text{db}$ , 10-megohm input impedance. Cathode-follower stage on all ranges provides high input impedance; 2-stage amplifier with about 19-db negative feedback for high output stability and linearity. Voltage division by precision components more than doubles frequency range of Heathkit model AV-3.



VU type ballistic damping for monitoring audio signals in tape recording and like applications. Covers .01 to 300 volts rms full scale in 10 ranges. Db scale calibrated from -50 to +50 db. 10 db steps.—Heath Co., Benton Harbor, Mich.

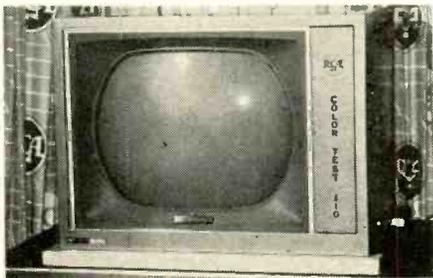**COLOR TEST JIG, model 11A1015**. Eliminates need to pull CRT and deflection assembly and then reconverge set after returning chassis to customer. Kit includes metal cabinet, deflection and convergence assemblies, hardware and all components for installing 21CYP22-A tri-color kinescope. 5 special extension cables available for




servicing RCA CTC-4, -5, -7, -9, -10, and -11 color receiver chassis.—RCA Parts & Accessories, P.O. Box 654, Camden, N. J.

**CR ANALYZER, model TE-25**, measures capacitance and resistance in 4 ranges, 1  $\mu\text{f}$  to 5,000  $\mu\text{f}$  and 0.5 ohms to 500 megohms; power factor of electrolytics from 0-55%. Dc voltage continuously variable to 600 volts, two ranges on meter 0-6, 0-60 ma. Ratio scales measure impedance and turns ratio of power and audio transformers in 2 ranges. Accuracy within 5%




over entire range. Tube complement: 1-6R4; 1-6E5. Power requirements 117 volts 50/60 cycles alternating current.—Lafayette Radio Electronics Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

**CRT REJUVENATOR TESTER, model TE-19**. Portable unit permits rapid check of black-and-white and color picture tubes, including 110° types, without removal. Fast shorts test with neon-lamp indicator. Determines CRT quality by emission test, rejuvenates all cathode-ray tubes. 4 1/2-in. meter for direct reading. Filament voltage selector switch, 6.3 and 12.6 volts. Repairs interelement shorts and open circuits;

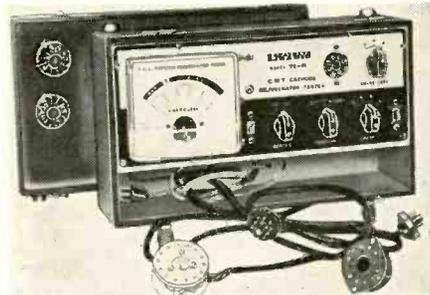

measures leakage. Two extra tube socket adapters for 110° deflection tubes. 105-120 volts, 60 cycles —Lafayette Radio Electronics Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

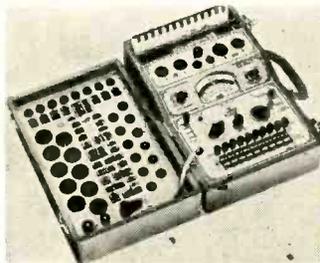**TUBE TESTER, model 107A**, tests 9-pin Novars, 12-pin Compactrons, new 10-pin tubes,




novistors, all standard domestic and foreign types. Mutual conductance test on prewired chassis, cathode-emission test using free-point selector system, and grid-circuit test for up to 11 simultaneous checks for leakage, shorts and grid  
(Continued on page 92)

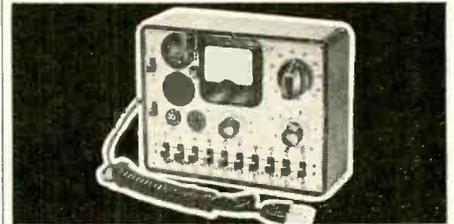
# Win with EMC




By far the **BEST VALUE** obtainable in either wired or kit form . . . compare and you'll agree "THE BEST BUY IS EMC."



**EMC Model — 211 Tube Tester** — The smallest, lowest priced, domestic made tube tester on the market. It is completely flexible and obsolescent proof. It checks each section of multi-purpose tubes separately, checks all octal, loctal, 9 prong and miniature tubes for shorts, leakages, opens, intermittents as well as for quality. Quality is indicated directly on a two color meter dial using the standard emission test. Comes complete with instructions and tube charts in ring bound manual. Size 6 3/4" x 5 1/4" x 2 1/4" deep. Shipping weight: 3 lbs. Wired ..... \$22.90 Kit ..... \$14.90  
CRT Picture Tube Adapter ..... \$ 4.50

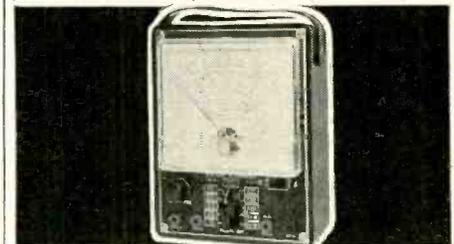

**EMC Model 109 — Voltmeter** — Features 20,000 OHMS volts DC sensitivity and 10,000 OHMS per volt AC sensitivity. Uses a 4 1/2, 40 microampere meter, with 3 AC current ranges, and 3 resistance ranges to 20 megohms. 5 DC and AC voltage ranges to 3000 volts and 3 DC current ranges; also 5 DB range.  
**Model 109 — With carrying strap, Weight 2 lbs. 5 oz.;**  
Size: 5 1/4" x 6 3/4" x 2 7/8" ..... \$26.95  
**Model 109K — Kit Form** ..... 19.25  
**Model HVT — 30,000 Volt Probe for Model 109** 7.95

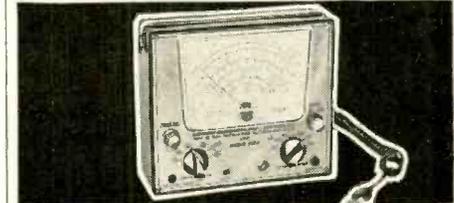

**EMC Model 107A — Peak to Peak Vacuum Tube Volt-Ohm Capacity Meter** — 6" meter cannot burn out — entirely electronic. Measures peak to peak AC voltages to 2800 volts in 6 ranges. Measures capacity in 6 ranges from 50 mmfd to 5000 mfd. Measures resistance in 6 ranges from .2 ohm to 1000 megs. Measures DC volts to 1000 volts in 6 ranges. Input resistance to 16.5 megs. Wired ..... \$51.40 Kit ..... \$36.50

Yes, tell me more, send me **FREE** a detailed catalog of the Complete EMC Line. Dept. RE-162  
NAME .....  
STREET .....  
CITY ..... STATE.....

**EMC** Electronic Measurements Corp.  
625 B'way, New York 12, N. Y.  
Ex. Dept., Pan-Mar Corp., 1270 B'way, New York 1, N. Y.

# A PROPHECY

For men and women with a sincere desire to succeed



“In the years that have passed since my days on the faculty of RCA Institutes, I have become even more firmly convinced that the individual who continues his education . . . particularly his technical education . . . is the individual who profits both as a thinking man and as a working man. Science and industry will reward you for your talents and energy. Out of your efforts may come inventions, new products, processes and services. There is everything good yet to be accomplished in our lives and in our work. What man has done, man can do better.”

*David Sarnoff*

Chairman of the Board,  
Radio Corporation of America

## *RCA Institutes Offers the Finest of Home Study and Resident Training for Your Career in the Rapidly Expanding World of Electronics*

RCA Institutes, founded in 1909, is one of the largest technical institutes in the United States devoted exclusively to electronics. A service of Radio Corporation of America, RCA Institutes offers unparalleled facilities for technical instruction . . . tailored to *your* needs. The very name “RCA”

means dependability, integrity, and scientific advance.

RCA Institutes Home Study School, licensed by the New York State Department of Education, offers a complete program of integrated courses for beginners and advanced students rang-

ing from electronic fundamentals to automation. All courses are designed to prepare you for a rewarding career in the rapidly expanding world of electronics. *The caliber of the training you receive is the finest!* And you get top recognition as an RCA Institutes graduate!

# HOME STUDY COURSES in

*Electronic Fundamentals • TV Servicing  
Color TV • Electronics for  
Automation • Transistors*

**Voluntary Tuition Plan.** The important thing to remember about RCA Institutes Training is the convenient, *no-obligation payment plan*. This plan affords you the most economical possible method of home study training because you pay for each study group only when you order it. If you interrupt your course *at any time, for any reason*, you owe nothing more. You *never* have to pay for the whole course if you don't complete it. No other obligations. No monthly installment payments!



**RCA Instruction is Personal.** With RCA Home Study training you set *your own pace* in keeping with *your own ability*, finances, and time. The Institutes allows you ample time to complete the course. Your lesson assignments are individually graded by

technically trained personnel, and helpful comments are added where required. You get theory, experiment, and service practice beginning with the very first lesson. All lessons are profusely illustrated. You get a *complete training package* throughout the entire course.

**You Get Prime Quality Equipment.** All kits furnished with the course are complete in every respect, and the equipment is top grade. You keep all the equipment furnished to you for actual use on the job... *and you never have to take apart one piece to build another!*

\* \* \*

## RESIDENT SCHOOLS in

*Los Angeles and  
New York City train  
you for any field of  
Electronics you may  
choose!*


**No Previous Technical Training Required For Admission.** RCA Institutes Resident Schools in Los Angeles and New York City offer training that will prepare you to work in re-

warding positions on research and production projects in fields such as automation, communications, technical writing, television, computers, and other industrial and advanced electronics applications. Even if you did not complete high school, RCA will prepare you for such training with courses specially designed to provide the basic math and physics required for a career in electronics.

**Free Placement Service.** RCA Institutes graduates are now employed in important jobs at military installations such as Cape Canaveral, with important companies such as IBM, Bell Telephone Labs, General Electric, RCA, and in radio and TV stations all over the country. Many other graduates have opened their own businesses. A recent New York Resident School class had 92.06% of the graduates who used the Free Placement Service accepted by important electronics companies... *and had their jobs waiting for them on the day they graduated!*



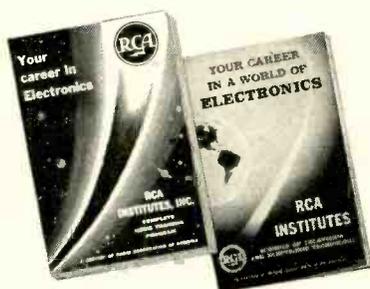**Coeducational Day and Evening Courses.** Day and Evening Courses are available at Resident Schools in New York City and Los Angeles. You can prepare for your career in electronics while continuing your normal full-time or part-time employment. Regular classes start four times each year.



**SEND POSTCARD FOR FREE ILLUSTRATED BOOK TODAY! SPECIFY HOME STUDY OR RESIDENT SCHOOL**

RCA INSTITUTES, INC. A SERVICE OF RADIO CORPORATION OF AMERICA, 350 W. 4th St., New York 14, N. Y., 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics

# LEARN and PROFIT from Gernsback Books

**TRANSISTORS** No. 94  
96 pages \$1.95



A handy work-book for the technician, experimenter or technical student. Tells how to test transistors and how to build the equipment you need to do the job—plus some interesting all-transistor equipment. They've all been bench-tested! A selection of the best from RADIO-ELECTRONICS magazine.

**RADIO CONTROL MANUAL** No. 91

By E. L. Safford, Jr.  
192 pages, \$3.20



How to build the ultimate R/C system. Starts with the most basic system and, by adding and modifying components, advances to a multi-channel system. There's a wealth of practical, do-it-yourself data here for both beginner and veteran.

**INTRODUCTION TO HI-FI** No. 88.

By Clement Brown  
192 pages, \$3.20



Gernsback Library acquired exclusive rights to publish this British book in America. A thorough study of a familiar subject from a refreshingly different point of view. Gives you a foundation on basics then digs into practical descriptions of pickups, preamps, amplifiers, speakers, acoustics, changers, hi-fi in the future. Gernsback Library edition available only in U.S.A.

SEE YOUR DISTRIBUTOR OR ORDER DIRECT  
In Canada: Len Finkler, 1794 Ave. Rd., Toronto 12, Ont.  
Export: Feffer & Simons, 31 Union Square, N. Y. 3

Gernsback Library, Inc. Dept. 12-A  
154 West 14th St.  
New York 11, N. Y.

Gentlemen please send me postpaid, the books indicated below. My remittance is enclosed.

94     91     88


NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_


(Continued from page 87)  
emission.—Seco Electronics Inc., 5015 Penn Ave. So., Minneapolis 19, Minn.

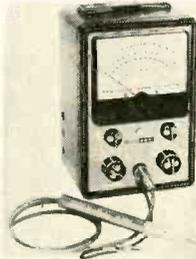VTVM, model 222. Direct-reading of ac-dc voltages to 1,500 and resistances 0.2 ohms to 1,000 megohms in 5 ranges. Calibration without removal from cabinet. Electronic overload protection plus fuse, 1% ceramic resistors and zero-center scale. Input impedance 11 megohms dc, 1 megohm ac. Voltage ranges: 0-3, 15, 75, 300



and 1500, ac/dc. Response 30 cycles to 3 mc; frequencies to 250 mc readable with Eico PRF probe. Resistance measurements 0.2 to 1,000 ohms, with 1.5-volt battery supplied. Wired or kit.—EICO Electronic Instrument Co., Inc., 33-00 Northern Blvd., L. I. C. 1, N. Y.

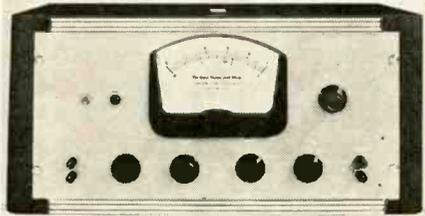FLUTTER METER, model 590-A-1. Visual indication of wow and flutter on tape recorders and playback equipment, including discs of all speeds as well as 16- and 35-mm sound film mechanisms. Built-in preamp and high-impedance input attenuator accepts voltages from 1 mv to 300 volts. Flutter and wow measured through high and low-pass filters. Built-in 3,000-cycle



oscillator. Three-range filter analyzes flutter and wow components. Frequency discriminator demodulates flutter signals, read on calibrated meter. Extraneous transients do not effect stability. Scales for flutter and wow: 0.3%, 1.0% and 3.0%; significant readings down to 0.01%. Measures variations in amplitude any rate from 0 to 40 cycles.—Amplifier Corp. of America, Instrument Div., 398 Broadway, New York 13, N. Y.

TWO-MANUAL THEATER-STYLED ORGAN, the York. Full 61-note manuals, 25-note concave-radiating pedal board and horseshoe stopboard with 40 multi-colored stop tablets. Dual expression pedals, separate vibrato on each




manual and independent oscillators for each note. Accessories: Band Box and Orchestra Bells. Finished or in kit form.—Artisan Organs, 4949 York Blvd., Los Angeles 42, Calif.

SPINET ORGAN KIT. 88 keys, 13 pedals; weighs less than 100 lb. Printed circuits permit easy assembly. Each component separate. Also




available Concert and Console models.—Scholer Organ Corp., 43 W. 61st St., New York, N. Y.

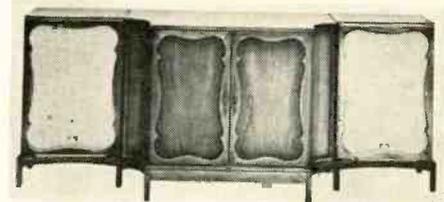COMPONENT CABINETS. Select-A-Style doors for easy removal and replacement. (Illustrated) Credenza component cabinet and two Medallion XII 12-inch 3-way speaker systems.



Italian Provincial, French Provincial, Swedish Modern and Colonial styles in various wood finishes.—University Loudspeakers, Inc., 80 So. Kensico Ave., White Plains, N. Y.

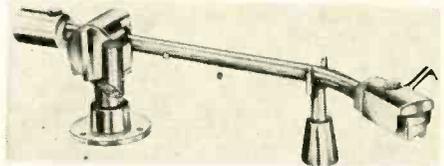PLAYBACK ARM, model 980. Dyna Lift mechanism lifts arm at end of record. Calibrated knob dials any stylus force from 0-8 grams, accuracy  $\pm 0.1$  gram. Cartridge bracket mount for adjustment of cartridge position in shell. Ground



loops eliminated by 5-wire circuit; separate fifth wire common ground for arm and turntable. Maximum compliance due to ball bearing suspensions, low fundamental resonance, low inertia and plug-in installation.—Dyna Empire, Inc., 1075 Stewart Ave., Garden City, N. Y.

MICROPHONE DESK STAND, model DS-10, accommodates any mike with standard  $\frac{5}{8}$ -27 NPSM thread. May be used with SSP10 and SA10 stand adapters. Knurled lock nut insures stable mounting.—University Loudspeakers, Inc., 80 So. Kensico Ave., White Plains, N. Y.

MICROPHONE, model C47D, combines noise cancelling and unidirectional properties for



maximum discrimination against distant and off-axis noise.—Euphonic Acoustics Corp., Box 2746, Rio Piedras, Puerto Rico.

PORTABLE TAPE RECORDER, model TC-1. All-electric self-contained Transitape uses 4 transistors, 1 diode. 1 $\frac{1}{2}$  and 3 $\frac{3}{4}$  ips. Fast forward rewind; separate erase head. Full-size playback speaker, wide-range response mike, safety interlock, separate volume control and battery and recording level indicators. Input 100,000 ohms; output 3.2 ohms; wow about 0.5% at 3 $\frac{3}{4}$  ips; overall gain 55 db.—Pentron Electronics Corp., 777 So. Tripp Ave., Chicago 24, Ill.

AUDIO/PA AMPLIFIER, McMartin model LT-80. All-transistor 8-watt continuous-duty unit for background music and PA. Peak power 20




watts, feedback circuit eliminates transistor damage if speaker load removed. No input transformer needed for telephone line input. Plug-in 600-ohm transformer optional.—Continental Mfg. Inc., 1612 California St., Omaha, Neb.

PA SPEAKER, model HP-75, for high-power applications to 75 watts. Bell diameter 9 in, total length 8 $\frac{1}{2}$  in. Model SHP-75, slightly


RADIO-ELECTRONICS

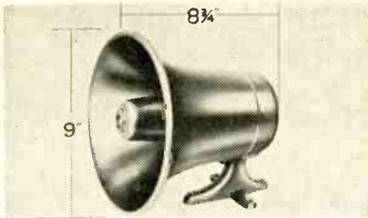smaller. All wiring connections made within cast-aluminum mounting bracket, with solderless con-



nectors provided.—Atlas Sound Corp., 1449 39th St., Brooklyn, N. Y.

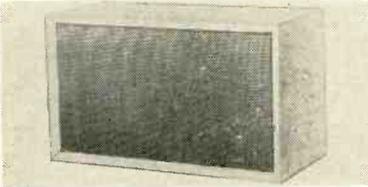**SPEAKER SYSTEMS AND CABINETS, Mark I** for medium- and low-level reproduction. Houses 8-inch speaker, 1-inch voice coil, 8 ohms impedance. Cabinet 11 x 9 1/2 x 23 in. Response 45 to 13,000 cycles. **Mark II** has 12-in. coaxial



speaker with 6.3 oz. Alnico V magnet, 1-inch voice coil, one-piece cone, 3-inch Alnico V PM tweeter. Power rating 12 watts, impedance 8 ohms. Cabinet 14 x 11 1/2 x 23 3/4 in. Response 50 to 15,000 cycles.—Cabinart Acoustical Engineering Corp., Haledon, N. J.

**SLIM-LINE SPEAKER KIT, model KS-1**, 5 1/4 in deep. 10-in woofer, 5-in mid-range, 3-in super-tweeter. Crossovers at 1,400 and 5,000




cycles; impedance 8 ohms. Also available as finished unit.—Fisher Radio Corp., 21-21 44th Drive, Long Island City, N. Y.

**SENSIPHONES, model ST-M**. Separate woofer and tweeter element in each phone. Adjustable crossover networks. High-compliance cone in woofer element for low-frequency ranges;




piezoelectric ceramic tweeter for high frequencies. Crossover control box has built-in resistor network to prevent blowout. Range 20 to 20,000 cycles.—Superex Electronics Corp., 4-6 Radford Place, Yonkers, N. Y.

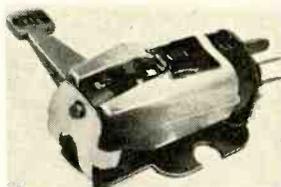**CERAMIC PHONO CARTRIDGE**. Turret action to eliminate twisting lead wires and de-



couple unused needle. U-line cartridge replaces all ceramic stereo and most monaural cartridges.—Euphonics Corp., Rio Piedras, Puerto Rico.

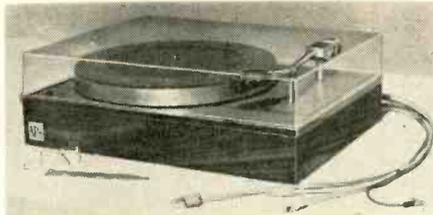**TURNTABLE-ARM COMBINATION**, 33-1/3-rpm. Arm, Walnut base, dust cover, cables, overhang adjustment device and needle force gauge. Belt drive from two synchronous motors, 3.5-lb. aluminum platter, shock mount-



ings from top plate. Tone arm floats down to record if dropped, damping mechanism disengaged when needle touches record.—Acoustic Research, Inc., 24 Thorndike St., Cambridge 41, Mass.

**AUDIO COMPRESSION AMPLIFIER** **Power Gainer** increases effective range of 2-way radio, amplifies low-level sounds to level equal to




low-frequency voice sounds. For base station or mobile applications.—Elenco Electronic Engineering Co., Wabash, Ind.

**TUNER KIT, model KF-90**. Built-in multiplex circuit and wide-band FM circuitry. Multiplex section reproduces full dynamic range of stereo FM without loss of response. Front-panel dimension control for varying channel separation. Dynamic sideband regulation reduces FM distortion from overmodulation or weak signals. AM




section offers sharp or broad tuning, 10-kc whistle filter and built-in loopstick antenna. Printed circuitry; rf and if transformers sweep-aligned.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

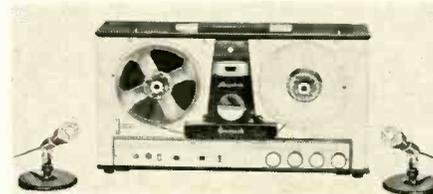**4-TRACK STEREO RECORDER, model 420**, for simultaneous recording and listening. Response 50-15,000 cycles 7 1/2 ips, 50-10,000 cycles 3 3/4 ips. Signal-to-noise ratio better than 48 db, wow and flutter less than 0.25% rms, bias oscillator frequency 65 kc. Built-in 5 1/2 x 7 1/2-in



speakers with 3/16-oz magnet and 1-in voice coils. Matching Gemark speaker pair S-204, two 6 x 9-in dualcone speakers with 1-in voice coils, 10-oz magnets and 8-foot cables, for extended speaker separation.—General Magnetics and Electronics, Inc., 134-09 36th Road, Flushing 54, N. Y.

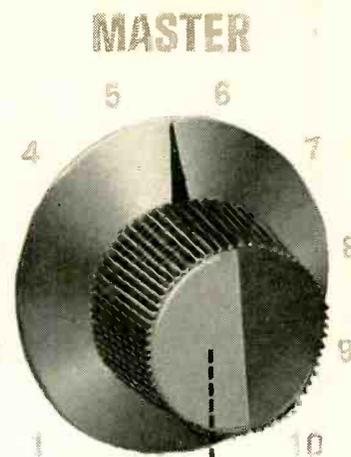**STEREO AMPLIFIER, model S-5000 II**, 80-watt amp/preamp unit. Presence-rise switch to increase level around 2,800 cycles by 5 db. Hum and noise ratio 60 db below 80 watts on phono channel, 1.2-mv phono sensitivity. 4 low and 8 high-level inputs; 12-db/octave scratch and rumble filter on all inputs. Friction-locked dual bass and treble controls for separate or ganged



**YOU WON'T FIND**

**THIS CONTROL**

**ON ANY OTHER P.A.**

**AMPLIFIER IN**

**THIS PRICE CLASS**



That's a fact. But all Harman-Kardon COMMANDER Series public address amplifiers incorporate a master volume control. These unique, popular-priced units include features generally found on much costlier "deluxe" equipment. For instance: Outputs for tape recorder, booster amplifiers and both 25 and 70 volt speaker lines; input for magnetic cartridge; DC on filaments of hi-gain stages; locking covers, etc. PLUS COMMANDER exclusives such as: multiple inputs for greater installation flexibility and optional single-control mixing of two program sources for convenience and ease of operation. Discover why sound men are switching to COMMANDER for all their needs. Write today, Commercial Sound Division, Harman-Kardon, Plainview, L.I., N.Y.

Send free detailed catalogs: Desk 1-F

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_

**harman kardon**

adjustment of channel settings.—Sherwood Electronic Laboratories, Inc., 4300 N. California Ave., Chicago 18, Ill.

**STEREO TEST RECORD** provides rapid frequency-response and channel-separation tests on automatic curve tracer, or manually with spot-frequency bands. Evaluates tone arm resonance, compliance, wavelength loss and stylus wear.—CBS Laboratories, High Ridge Road, Stamford, Conn.

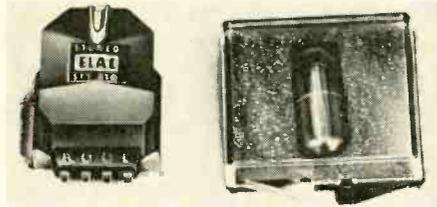**STEREO CARTRIDGE, Stereotwin STS-200.** Moving magnet. Channel separation 25 db 1,000 to 10,000 cycles. Output 10 mv at 5 cm/sec.



Mounted diamond 0.7-mil stylus plus extra diamond stylus.—Benjamin Electronic Sound Corp., 97-03 43rd Ave., Corona 68, N. Y.

**FM STEREO ADAPTER KIT, Unit GRA 21-1,** to accompany Heathkit GR-21 FM table radio or any FM radio. Self-contained and self-powered, has 6 X 9 in speaker and audio circuitry for matched response. Choice of FM stereo or monophonic reproduction, using speakers in radio and adapter or radio speakers alone. Master volume control for both channels. Tone controls on adapter and radio function inde-




pendently. Full-wave power supply uses silicon rectifiers and power transformer.—Heath Co., Benton Harbor, Mich.

**STEREO MULTIPLEX ADAPTER, model KN-MX.** For any FM or FM-AM tuner having multiplex output jack. External control for quick



separation adjustment. Self-powered, plugs in between tuner and stereo amplifier of stereo system. All connecting cables supplied.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

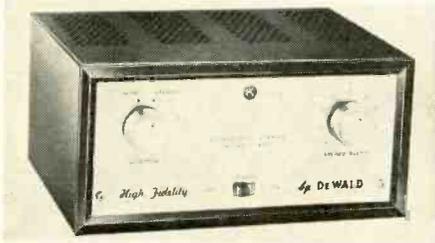**MULTIPLEX ADAPTER, model P-400** (illus). For most tuners with multiplex jack. 2 dual-purpose tubes, 1 power rectifier, 2 high-frequency diodes. AM-FM stereo multiplex tuner,




model R-1103, with built-in multiplex: 10 tubes 3 diode detectors and rectifier.—De Wald Radio, Div. United Scientific Labs, 35-15 37th Ave., Long Island City 1, N. Y.

**FM MULTIPLEX TUNER, model TM-214.** Three-tube multiplex circuit with factory-set balance and separation controls. Sensitivity 2.2  $\mu$ v IHFM standard, 1.3  $\mu$ v for 20 db of quieting; distortion less than 0.5% at 100% modulation, signal-to-noise ratio: 70 db, monaural; 50 db, stereo. 2 tape and 2 audio outputs, 11 tubes plus rectifier and matched germanium diode detectors.



—Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.

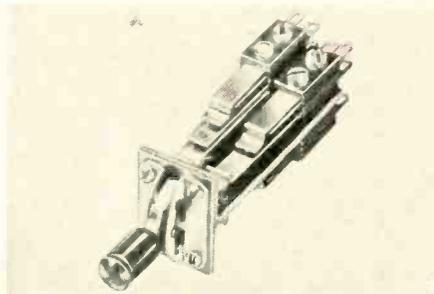**TELEPHONE TYPE LEVER SWITCH** prevents accidental switching. Lever-Lock lightweight construction. Index bracket locks actuator for switching position and doubles as




escutcheon plate. 3 amps, 300 watts max., ac noninductive load.—Switchcraft, Inc., 5555 N. Elston Ave., Chicago, Ill.

**CB MICROPHONE, model 350C.** 11-inch retracted (5 feet extended) *Koiled Kord*. Hanger button and standard dash bracket permit mobile



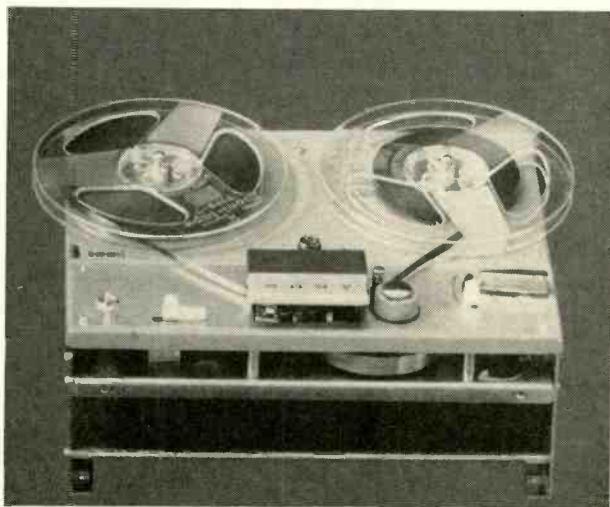rig mounting. Response 80 to 7,000 cycles, output -54db.—Turner Microphone Co., 901 17th St. N.E., Cedar Rapids, Iowa.



# NEW SONY STEREO TAPE DECK

Now, for less than the cost of a good record changer, you can add a versatile new dimension to your hi fi system. ■ The Sony 262-D tape deck has a 4 track stereo erase head and 4 track stereo record/playback head. Heads are wired to six output and input facilities for connection of external electronics to play and record four track stereo. This is the same quality mechanism used in the most expensive Sony Superscope tape recorders.

**\$89<sup>50</sup>**



**NOW AVAILABLE!**

Complete your 262-D stereo system: the long-awaited Sony SRA-2 stereo recording amplifier provides instant connection to the Sony 262-D stereo tape deck for complete 4-track stereophonic and monophonic recording. Two V.U. meters, track selector switch, record safety interlock, microphone and radio inputs. No modifications necessary.

**\$89<sup>50</sup>**

For literature or nearest dealer, write: Superscope, Inc. Dept. T, Sun Valley, California.

**SUPERSCOPE**

The Tapeway to Stereo


All Sony Stereorecorders are Multiplex ready!

**CB TRANSCEIVER, model 740.** Portable. Nickel-cadmium rechargeable battery and charger. Superhet receiver: 7 transistors and 1 diode; crystal-controlled local oscillator. Sensitivity 1 to 2  $\mu$ v for 10-db signal-to-noise ratio. Transmitter: 2 transistors; 100 mw input; modula-




tion to 100%. 41-in telescoping antenna. 2 1/4-in PM response-corrected speaker/microphone.—**Electronic Instrument Co., Inc., (EICO)** 33-00 Northern Blvd., Long Island City, N. Y.

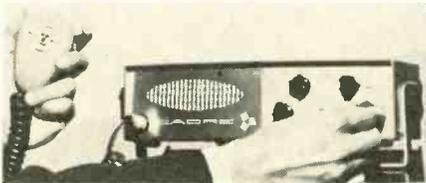**5-WATT CB TRANSCEIVER, model 500.** Completely transistorized, for autos, trucks, aircraft and boats. Squelch and automatic noise limiter permits clear reception above engine



noise. Range of 10-15 miles overland, 20 miles over water. Operates in 27-mc range with 5 receiving and 5 transmitting channels. Tunes all 23 CB channels. Modulation capability 100%, frequency stability .005%.—**Cadre Industries Corp., Endicott, N. Y.**

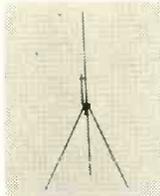**CB ANTENNA.** Ground-plane design with adjustable gamma-match feed system. All seam-



less aluminum, stainless-steel fasteners.—**Hi-Par Products Co., 347 Lunenburg St., Fitchburg, Mass.**

**RADIOTELEPHONE, Cruisephone 25.** 25-watt unit for outboards and other small craft. Over-head, chart table or bulkhead mountings;



reversible control panel. 5 channels, rf gain control and antenna booster control.—**RCA, 30 Rockefeller Plaza, New York 20, N. Y.**

**TRANSISTORIZED OSCILLATOR, Transi-Call** accessory for sound-powered phones alerts



party being called. 1000-cycle tone changes if other end open. 9-volt transistor battery, one transistor.—**Blan. The Radio Man, 64 Dey St., New York, N. Y.**

**CODOME,** Morse-code learning device with accompanying manual, for potential amateur ra-



## Centralab L&T PAD ATTENUATORS

offer these advantages  
in any  
sound installation

### SMALL SIZE...

less than 1 3/16" deep from mounting surface, these units fit into any standard junction or switch box with room to spare... diameter is only 1 3/32".

### HIGH WATTAGE...

conservatively rated at 20 watts audio, 5 watts D.C. yet they are no larger than units rated at 2 watts D.C. One size takes care of all your 2, 3, 4, and 5 watt requirements. Centralab's exclusive "thermo-pass" insulation combines fast heat transfer with a high dielectric constant to achieve this high rating.

### ANTI-BACKLASH CONSTRUCTION...

the "play" frequently found in dual controls is eliminated. The wiper contacts move in unison, assuring that there will be no alteration in frequency response due to variations in wiper position on the resistance tracks.

B-6124

**Centralab**

THE ELECTRONICS DIVISION OF GLOBE-UNION INC.  
9221 EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN  
In Canada: Centralab Canada Ltd., P.O. Box 400, Ajax, Ontario

**ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS**

# NEW SAMS BOOKS



## Transistor Circuit Manual

Allan Lytel presents hundreds of typical transistor circuits, illustrating virtually every type of application. Of great value to technicians, engineers and experimenters—makes design and operation understandable. Schematics and parts values are shown for each circuit; accompanying text describes function and characteristics. Applications include: Switching Circuits; Counters; Flip-Flops; Power Control; Tuners; Indicators; Photoelectrics; Controls; Converters & Inverters; Audio Amplifiers; RF & IF Circuits; Oscillators; Power Supplies & Regulators; Radio & TV Circuits; FM and Special Circuits. 224 pages; 5½ x 8½". Only... \$4.95

## 101 More Ways to Use Your VOM—VTVM

Sequel to Bob Middleton's earlier volume—shows all-new uses for VOM and VTVM units. Includes schematics and equipment hookup for checking and troubleshooting door openers, all types of appliances, fluorescent lamps, time controls, electric motors, audio and hi-fi circuits, power supplies, transmitters, tuned circuits, crystal circuits, transistor and photo-tube circuits, delta transformers, fuel gauges, burglar alarms, etc. Tells how to use units as S-meter, cavity-wave meter, tachometer, field-strength meter. 128 pages; 5½ x 8½". Only... \$2.50



## General Class Amateur License Handbook

Howard Pyle, W70E, provides a complete new guide, including typical questions and answers, to prepare the novice or aspirant for the Technician, Conditional, or General class amateur radio exam. Covers license requirements; learning the code; the written exam; transmitter circuits; basic electronics theory; FCC regs.; general operating practices. 128 pages; 5½ x 8½". Only... \$2.50

## ABC's of Electronic Organs

Explains theory, development, features and operation of electronic organs, electronic circuitry used, how to select an organ, maintenance and troubleshooting. Most informative for owners and potential owners of organs, as well as for technicians and students. 96 pages; 5½ x 8½". Only... \$1.95

## Commercial Sound Installer's Handbook

Leo G. Sands describes the installation, operation, and maintenance of the various types of sound and intercom equipment used in factories, schools, stadiums, vehicles and other commercial fields. Fully describes and illustrates amplifiers, input devices, speakers, distribution, control circuits, portable and mobile equipment, installation and maintenance. A valuable book for technicians and sound specialists. 288 pages; 5½ x 8½". Only... \$4.95

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. A-22 1720 E. 38th St., Indianapolis 6, Ind.

Send me the following books:

- Transistor Circuit Manual (TCM-1)
- 101 More Ways to Use Your VOM-VTVM (TEM-8)
- General Class Amateur License Hand. (ALP-1)
- ABC's of Electronic Organs (ECO-1)
- Commercial Sound Install. Hand. (ISS-2)


\$.....enclosed.  Send Free Book List

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

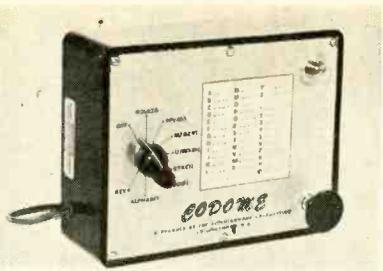IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7 (outside U.S.A. priced slightly higher)



dio operators or Novice licensees. 36 characters in groups of 6, with switch to select groups. Characters in each group transmitted repeatedly at random. Built-in key for practice in manual sending, flashing light accompanies audible transmission.—Accentrone Corp., 117 Crestmont Terrace, Collingswood, N. J.

**RADAR SENTRY.** Audible warning of radar-controlled speed zones within ½-mile range. Dual-band circuit continuously and simultaneously monitors two special frequencies in S- and



X-microwave bands, on which radar traffic controls operate. Printed wiring, 8 transistors and two 1,000-hour mercury cells, self-testing batteries.—Radartron, Inc., 232 Zimmerman St., N. Tonawanda, N. Y.

**DECADE RESISTOR/DIVIDER, model 1601,** for use with bridges and in determining resistance values in development circuits. 4 voltage-divider posts permit use as general-purpose wide-range divider, and allow setup for practical voltage ratios from .0001 to 1.0. Input resistance as divider 11 to over 110,000 ohms. 5 decades total 0–11,110 ohms. steps of 1 ohm. Tolerance ±0.5% in resistance elements (1-watt negligible inductance).—Precision Apparatus Co., Inc., 70-31 84th St., Glendale 27, N. Y.


**RESISTANCE SUBSTITUTION BOX, model 1702,** for rapid direct substitution of 36 resistance values by use of two rotary switches. Re-



sistance values 15 ohms to 10 megohms; wattage dissipation of all resistors 1 watt ±10% tolerance.—Precision Apparatus Co., Inc., 70-31 84th St., Glendale 27, N. Y.


**CABLE ASSEMBLY, model 10BF10.** Molded straight 3-conductor phone plugs at both ends of 36-inch shielded cable, built-in cable clamps.—Switchcraft, 5555 N. Elston Ave., Chicago 30, Ill.

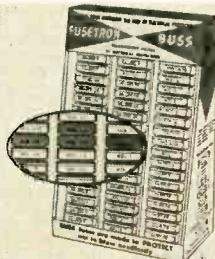**ELECTRONIC FUSE ASSORTMENT** in metal stand for easy reference service technicians. Individual shelves hold 5-in metal boxes;




tabs indicate size and type. Large style contains 255 fuses in 30 sizes; small, 130 fuses in 26 sizes.—McGraw-Edison Co., Bussman Mfg. Div., University at Jefferson, St. Louis 7, Mo.

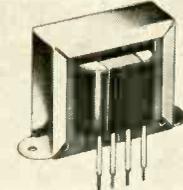**VERTICAL OUTPUT TRANSFORMER, part No. VO-114.** 6:1 turns ratio, primary impedance 5,000 ohms at 30 dc ma. Dc resistance 250 ohms primary, 6 ohms secondary. For direct replace-




ment in Airline, Coronado, Emerson, Sonora, Sylvania, Trav-ler and Truetone sets.—Stancor Electronics, Inc., 3501 W. Addison St., Chicago 18.

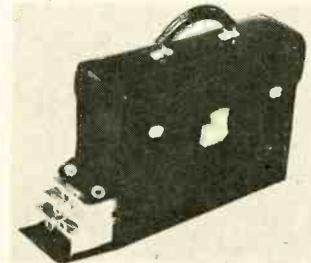**SERVICE TOOL KIT** holds large tools, meters, etc. Three sliding metal trays with compartments for small parts. Available with out-



side pocket for manuals.—K. Leather Products, Inc., 427-429 Broadway, New York 13, N. Y.

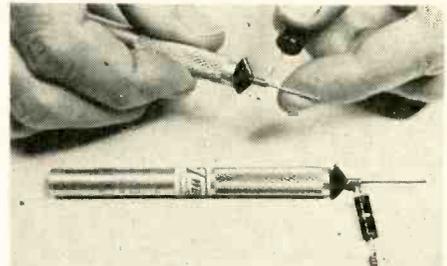**TWIRL-CON TOOL,** in three sizes. For printed-circuit work, modification of surplus equipment, repair of leads broken off close to



transformer winding, lengthening pigtailed, etc. Also makes pin plugs, fuse lead buttons and solderless connections.—Twirl-Con Tools, 101 N.E. St. Edna, Texas. END

All specifications are from manufacturers' data

## NEW BUSINESS GETTERS

## NEW LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

**TRANSISTOR DATA SHEETS** are explained in a 7-page booklet *How to Get More Value out of a Transistor Data Sheet.* Graphs, charts and explanatory material aid the design engineer in achieving reliability and low cost.—Motorola Semiconductor Products, Inc., 5005 E. McDowell Rd., Phoenix 8, Ariz.


**SILICON DIODES AND RECTIFIERS** are presented in 10-page *Bulletin 514.* Semiconductors include diffused-junction silicon diodes in general-purpose, high-conductance, computer switching and standard types, as well as diffused-

junction silicon rectifiers in glass, co-axial and epoxy package.—**Electron Research Inc.**, Div. Erie Resistor Corp., 530 W. 12th St., Erie, Pa.

**EXTENSION SPEAKER COUNTER DISPLAY** for two 4-inch extension speakers.—**Philco Corp.**, Philadelphia, Pa.



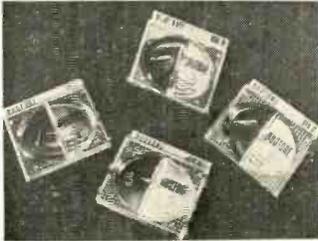**BUBBLE PACKAGE** for point-of-purchase needle display.—**Duotone Co.**, Keyport, N.J.



**ELECTRICAL TAPES** are illustrated in an 8-page full-color catalog, giving information and specs on Plymouth and Slipknot lines. New products include vinyl electrical tape for all-temperature use, rubber insulating tape and splicing compound.—**Plymouth Rubber Co., Inc.**, Tape Div., Canton, Mass.

**INSTRUCTION SHEET**, Form No. TK-303, a 6-page booklet, details the installation of a 21CYP22A color picture tube in the RCA model 11A1015 color test jig—a cabinet and deflection and convergence assembly kit for mounting a

color kinescope on the service bench.—**RCA Parts and Accessories**, PO Box 654, Camden, N. J.

**SPRAY PAINTS** and protective coatings are pictured and described in a 12-page catalog. New products include electronic contact cleaner-lubricant; matte finish spray for photos; varnish for oil paintings; pressure-sensitive spray adhesive and blue fluorescent spray paint.—**Krylon, Inc.**, Norristown, Pa.

**FOUR-TRACK STEREO** described in nontechnical terms in illustrated booklet. Scotch brand tapes and accessories also listed.—**Minnesota Mining & Manufacturing Co.**, Dept. Y1-522, 900 Bush Ave., St. Paul 6, Minn.

**REPLACEMENT COMPONENTS** are shown in 32-page *Catalog SE 501*. Included are ac capacitors, auto radio, ceramic, electrolytic, mica, Mylar, oil-paper and paper tubular types, as well as filters, hardware, instruments and capacitor kits. Pocket-size booklet *AFH-461* is devoted to twist-prong electrolytic capacitors only.—**Aerovox**, 740 Belleville, New Bedford, Mass.

**OFFICE AND INDUSTRIAL EQUIPMENT** is offered in a 31-page manual. Steel products include office desks, filing cabinets, extension ladders, tool storage carts and refuse disposal units. Also listed are wireless intercoms, telephone amplifiers, secretarial chairs and many other items.—**Precision Equipment Co.**, 8 Precision Bldg., 4403A Ravenswood Ave., Chicago 40, Ill.

**SERVICING DATA** described in a 4-page leaflet includes radio and television diagrams, service manuals, and other information useful to the technician.—**Supreme Publications**, 1760 Balsam Road, Highland Park, Ill.

**DC POWER APPARATUS** shown in detailed list. Complete specs given on power supplies, variable transformers, isolation rectifier transformers, full-wave bridge rectifiers, volt and amp meters and other products.—**Technical Apparatus Builders**, 109 Liberty St., New York 6, N. Y.

**HI-FI KITS** are explained in a question-and-answer brochure. Blend control, cabinet installation of preamps and tuners, kit packaging and extension of frequency ranges are among sub-

jects discussed.—**Harman-Kardon, Inc.**, Ames Court, Plainview, N. Y.

**COLOR CODES** for transformers on 8½ x 11-inch wall chart include those for power audio, output and if transformers, as well as connection codings for loudspeaker leads and plugs.—**Stancor Electronics, Inc.**, 3501 Addison St., Chicago 18, Ill.

**RELAY CATALOG** provides illustrations, specs and other information on industrial and commercial relays. Included are general-purpose, plate circuit, industrial control, telephone, printed-circuit, sensitive, digital-counter, antenna, power and plug-in types.—**Hillburn Electronics Corp.**, Mr. E. Fieldsteel, 55 Greenpoint Ave., Brooklyn 22, N. Y.

**RIGID COAXIAL TRANSMISSION LINE** *Catalog 200* gives description and specs on lines of varying dimensions, with copper or aluminum outer conductors. Also listed are supporting hardware, dehydration and pressurization equipment, required electrical and mechanical specs of rigid line, and attenuation and power rating data.—**Taco**, Sherburne, N. Y.

**BATTERY ENGINEERING SUPPLEMENT** outlines alkaline-manganese-zinc battery system throughout the range of battery types. Also included is specification and suggested list-price table.—**Union Carbide Consumer Products Co.**, 270 Park Ave., New York 17, N.Y. **END**

## ENGINEERING

Learn more . . . earn more. **B. S. DEGREE IN 27 MONTHS** in Engineering. **IN 36 MONTHS** in Business Administration. Small classes. *Low costs.* Enter Mar., June, Sept. Jan. Write **J. G. McCarthy** for *Catalog and Your Career Book.*

**TRI-STATE COLLEGE**  
2412A College Avenue • Angola, Indiana

# FOR SHARPEST, CLEAREST VOICE TRANSMISSION WITH ANY CITIZENS BAND TRANSCEIVERS, SPECIFY

## THE TURNER 350C

Even the best citizens band equipment is no better than the microphone it uses. That's why more Turner 350C microphones are used as original equipment in CB than any other. That's why it will pay you to specify the Turner 350C when you buy CB equipment or replace your microphone.

■ The 350C is furnished with an 11" retracted (five foot extended) coiled cord. Hanger button and standard dash bracket are included for mobile rig mounting. Response: 80 to 7000 cps. Output: -54 db. Net price: \$10.08

■ See Turner microphones at your electronic parts distributor or write for complete information and the name of your nearest Turner distributor.



### TURNER 254C FOR BASE STATION

Desk. type ceramic mike operates by a touch bar off-on switch and lever lock on-off switch. Response: 80-7000 cps. Output: -54 db. Net price: \$14.10.

THE **TURNER** MICROPHONE COMPANY

933 17th Street NE,  
Cedar Rapids, Iowa

**NEW! rust-proof,  
corrosion-proof, salt-water-proof**

# Heller-ply<sup>®</sup> STAPLES

**CUT COSTS IN HALF**

Perfected in one of America's best-known industrial laboratories . . . service proved under severest outdoor conditions. New *Heller-ply* staples are guaranteed against rust, chemical atmospheres or salt-water corrosion.

Made of steel base for strength, heavily electroplated with copper for lifetime protection, *Heller-ply* staples easily withstand severest conditions which, up to now, have required staples made of stainless steel or other expensive rust-proof metals.

And, new *Heller-ply* staples bring an important break-through in price. Cost only 1/2 as much as other rust-corrosion-salt-water-proof staples. Available in all standard industrial sizes, cost little more than standard staples.

Write today for complete information. Request Bulletin HPS.




A-5871A

For use in Heller tackers.

® Trade-mark registered
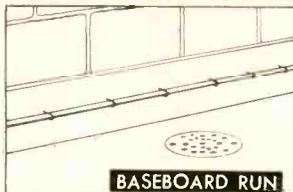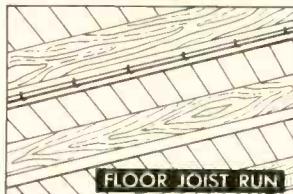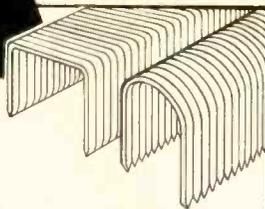
## HELLER ROBERTS Instruments Corporation

6115 Carnegie • Cleveland 3, Ohio • Dept. P • Telephone EN 1-6161



TECHNICIANS'

# NEWS

## HIGH COURT BACKS LICENSING

*Lansing, Mich.*—The State Supreme Court unanimously upheld Detroit's ordinance requiring the licensing of television service technicians. It was noted that the ordinance did not attempt to fix prices.

The ordinance was brought to court by William Murphy, a TV service dealer, who contended that having four of his competitors on the board was a threat of discrimination against him.

The court decided that the law is a valid exercise of police power and named other regulating groups which have members representing the controlled business.

## WORD FROM WISCONSIN

*Sheboygan County*—There was a lot of activity at a regular meeting of TESA—Sheboygan at the Grand Hotel. John Bruder and Fred Leonard reported on the NATESA convention. Members turned in lists of their shelf stock. These lists will be compiled into a master list, copies of which will be given to all members. Then one member will be able to draw on the stock of another for rare parts.

*Milwaukee*—Once again Covic's Amerwood Hall was the meeting place for TESA—Milwaukee. After the minutes of the previous meeting were read, Mr. and Mrs. Don Miller, representing Cardinal TV, were introduced. They attended to get an idea of the association's activities as they are considering joining.

## "FREE SERVICE" IN COURT

*St. Louis, Mo.*—The Post-Dispatch reported that Charles R. Thurber, trade practice consultant for the Better Business Bureau, told the Missouri Public Service Commission that television repairmen making "free" home service calls hold an advantage over other repairmen because television owners feel obligated to purchase parts from them.

Thurber's testimony came as hearings resumed before the commission on the petition of Videon Television Service, 379 No. Big Bend Blvd., University City, to force Southwestern Bell Telephone Co. to allow Videon to use the phrase "you pay nothing" if no tubes need changing, in the company's advertisement in the yellow pages of the telephone company directory.

The television industry, Thurber said, agreed voluntarily in 1954 to eliminate "free service" advertising. The telephone company allowed use of the "free service" phrase in the Videon company's advertisement in the 1960 di-

**MOBILE  
CITIZENS  
BAND**



## Heliwhip<sup>®</sup> Antennas

Exclusive "Static Sheath"<sup>™</sup> Helps You Hear Weak Signals over Greater Distances!

Mark HELIWHIP<sup>®</sup> Plastic Covered Fibre Glass Antennas noticeably improve mobile Citizens Band communications! Outperform long whips or base loaded antennas! Mark Mobile's exclusive "Static Sheath"<sup>™</sup> plastic covering reduces precipitation static—improves signal/noise ratio up to 20 db. High radiation efficiency with near-perfect 50 ohm match at resonant frequency. Broadband over all C/B channels with very low VSWR. Length only 4 feet overall—mount on trunk or cowl like broadcast antenna. Get out farther—improve your reception . . . switch to a HELIWHIP!<sup>®</sup>

\*HELIWHIP is a registered trademark  
U.S. Patent 2,966,679 \*U.S. Process Patent 2,938,210

Write for technical data or visit your nearest CB equipment supplier

**MARK MOBILE, Inc.**  
Dept. RE-1, 5441 WEST FARGO AVE.  
SKOKIE, ILLINOIS

Detect police radar traps  
before they detect you

Plans \$1.00 Kits (with assembled antenna) \$19.95  
wired units \$29.95 extra antennas \$4.50 each

## RADAR KING<sup>®</sup>

Both S- and K-band operation. S-band antenna shipped unless otherwise specified. Kits and wired units supplied with dual input for simultaneous operation of S- and K-band.

WARDELL SMITH

65 Glenwood Rd., Upper Montclair, N. J. est. 1924  
pat. pending



## BEAT?

Troubled with cold solder joints?

World's Finest  
ERSIN *Multicore*  
FIVE-CORE SOLDER



Sold only by Radio Parts Distributors.

rectory, but refused use of it in the 1961 directory.

[Credit is certainly due the Better Business Bureau of St. Louis and to the responsible service companies in the St. Louis area who adhere to good business practices in advertising and operation. The poor public image and bad publicity heaped upon servicemen in general is the result of opportunists who utterly disregard their responsibility to the industry they represent. It is interesting to note that, of the 300 or more service companies in the St. Louis area, Videon is the only company who feels they should be an exception to responsible practices, and KTVI, channel 2, is the only one of the television broadcasting stations that prefers to reject what other advertising media adhere to. — Editor's note — TESA—St. Louis News]

### SERVICE TECHS AT HI-FI SHOW

Philadelphia, Pa.—Visitors at the Greater Delaware Valley High Fidelity Music Show were treated to a special display run by members of the Television Service Association of Delaware Valley, Philadelphia, and TSA of Delaware County. They saw a view of their heart beats on an oscilloscope and heard them played back on a tape recording which they were given as a souvenir. Also, they were tested for their audio range.

### STIRRINGS IN THE WEST

Ventura, Calif.—There's a new service group in this area, the Electronic Service Dealers Association of Ventura County. They have already set up a cooperative advertising plan that includes advertising mediums in Oxnard and Ventura. Meetings are held the second Wednesday of each month.

Officers are: Rog Wimer, president; Ray Johnson, vice president; Fred Sueyres, secretary, and Rod Wignall, treasurer.

Redondo, Calif.—A talk on FM multiplexing and transistor servicing was given by Don Paulin, field engineer for Dumont-Emerson, before a combined meeting of the South Bay and San Antonio and Los Cerritos chapters of RTA.

Covina, Calif.—Service engineers from Sencore conducted a discussion and demonstration of Sencore service instruments before the membership of the San Gabriel chapter of the California State Electronics Association.

### CENTRALIZED SERVICE

Atlantic City, N. J.—Members of the Tri-State Council of TV service associations discussed centralized service at the annual Telerama convention here. Under the system, a cooperative central service shop would be established to handle all shop repair work. Dealers now operating their own shops would join together to establish the centralized shop.

In-the-house repair work would be done by individual service technicians who would maintain business phones.

All shop work would be done at the central shop and billed to the individual technician. This plan would cut shop overhead drastically, while all technicians would retain their own customers and share in the profits of the centralized shop.

### ELECTION RETURNS

New York, N.Y.—The Associated Radio Television Servicemen of New York held their annual election at the Central Plaza Annex. Max Liebowitz was re-elected president. First vice president is Herb Schneider; second vice president, Frank Vella; treasurer, O. Capitelli; corresponding secretary, Mark Schwartz and sergeant at arms, Richard Tice.

### A TECHNICIAN'S DAY


"Have you got this part for my lawn mower? What's the matter, this is a radio shop, isn't it?"

"My Space Command isn't working right, and you had better come and fix it right away. I am getting the same picture on channel 7 and channel 11." (Later she called back to say—"I am getting the same picture on my portable too on 7 and 11.")

"Just have your man stop by when he is in the neighborhood with one of those little things in a box that make the picture better."—TSA Service News, Seattle, Wash.
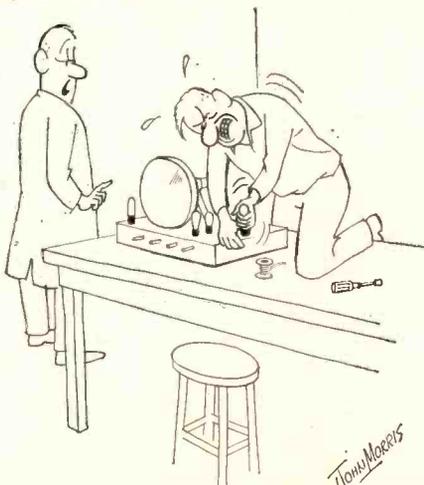
### FORUM BACKS LICENSING

New York, N.Y.—Licensing TV technicians to eliminate unscrupulous self-styled repairmen was the topic of a public forum at the Hotel Diplomat. Members of the Empire State Federation of Electronic Television Associations discussed complaints and practices brought up by individuals from their communities. The group considers licensing to be one of the most desirable methods of eliminating such activities. Licenses would be issued to competent, qualified, ethical technicians and would eliminate self-styled repairmen who cannot meet the requirements of TV experience and know-how. The public was urged to write their State Senators and Assemblymen, asking them to support the licensing bill when introduced again this year. END




"Sorry, I forgot to tell you the tubes in that set screw in."
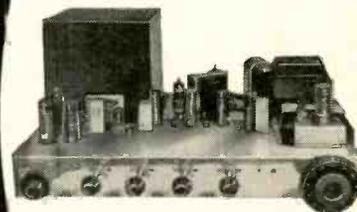
## BUILD THE FINEST Professional Quality CUSTOMIZED TV KIT

On Easy "Pay As You Wire" Terms Only \$15 for the Starting Package!

The "PROFESSIONAL" Series—designed for the perfectionist seeking the finest in TV performance. Easy to assemble. No technical knowledge required. An ideal "Learning" Kit with a Complete Course of Study is available.




Also available:

WIRED CHASSIS

for custom installations with a choice

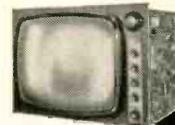of vertical or horizontal controls and the newest 19", 23" or 27" Picture Tube.



Beautiful Cabinets — designed to enhance sound quality and blend with modern decor. For TV or combination TV and Hi-Fi.

### A few of the Professional Quality Features:

Choice of push-pull 10-watt audio or output to your Hi-Fi system... D.C. restoration... Ultra-linear sweep circuits... Standard Coil Guided Grid Turret Tuner... Super-sensitivity for fringe areas... Complete line of Accessories for Custom Installations.

CHOICE OF 19", 23" or 27" CRT. Prices range from \$119 to \$199.

U.S. Armed Services and over 4000 schools and colleges have selected Transvision Receivers for educational television.

### Interested in Electronics?

Learn the basic principles of electronics from the Course available with the Kit.

ASSEMBLY MANUAL—\$2.00

See how easy it is to assemble the Transvision Kit. Cost of Manual refunded on purchase of Kit.

**TRANSVISION** New Rochelle, N.Y. NE 6-6000

START NOW — MAIL THIS COUPON —

TRANSVISION Electronics, Inc., New Rochelle, N.Y. Dept. RE

Send FREE 8-page Catalog...  I enclose \$2 for Assembly Manual, refundable on purchase of Kit.

I enclose \$15 for Starting Pkg. on pay-as-you-wire plan. (Complete Kits range from \$119 to \$199.)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**"TAB" XMAS! BARGAINS • TUBES**

Six Months Guarantee! No Rejects!  
NEW & Used Gov't & Mfgs. Surplus!

Orders \$10 or more, Receiving type only ppd, 48 states

0A2	.80	6B7	.69	12AT6	.59	18B1	1.00
0B2	.85	6B7	.69	12AT7	.74	317Z	1.10
0C3	.89	6B7	1.25	12AU6	.69	4-6SA	16.00
0D3	.58	6B7	.98	12AU7	.69	2021	2/81
0Z4	.59	6B6	1.19	12AX7	.71	313	3.85
1A7	.89	6B7	1.25	12BA6	.65	717A	3/81
1B3	.78	6C4	.43	12B7	.99	4-125	29.00
1R5	.78	6C5	.80	12BD6	.59	4-250	35.00
1S4	.78	6CB6	.80	12BE6	.59	4-27	7.00
1T4	.78	6CD6	1.40	12BF6	.59	4PR60	29.50

Send 25¢ for Catalog

1U4	3/81	8H6	3/81	12CN7	.99	4X150G	\$15
1U5	.73	6J5	.52	12BY7	.98	4X250	35.00
1X2A	1.09	6J6	.48	12BZ7	.99	4X500	38.00
3Q4	.68	6K6	.50	12CU6	1.45	5BP1	12.00
3Q5	.89	6KF	1.05	12SA7	.84	5BP4	7.20
3S4	.88	6L6	1.19	12SQ7	.89	35T	4.00
3V4	.83	6S4	.59	12SH7	.89	100T	7.00
5U4	.99	6SA7	.69	12SJ7	.75	319A	2/81
5V4	.89	6SB7	1.19	12SK7	.94	388A	3/81
				12SQ7	.84	416B	4.00

Wanted Surplus Electronics from schools, U.S.

5Y3	.59	6SC7	.89	19R6	2.15	410T	42.00
6A4	.59	6SC7	.79	19T8	1.16	807	1.00
6AC7	.70	6SH7	.69	25BQ6	1.39	866A	1.89
6AG7	.89	6SJ7	.69	25L6	.69	811	4.40
6AN6	.69	6SK7	.72	25W4	.77	812	3.00
6AR5	.69	6SL7	.89	25Z5	.63	813	9.00
6AL5	2/81	6SN7	2/81	32B6	.74	314	3.45
6AQ5	.63	6SQ7	.74	EL34	3.49	815	2.75
6AS7	3.00	6SR7	.79	EL37	2.49	826	2.00
6AT6	.49	6T8	.49	31L6	.69	829B	8.00

Wanted \$11, \$12, \$13 and \$01 TL tubes

6AU4	1.10	6UB	.98	35W4	.49	832A	7.00
6AU5	1.19	6V6GT	.70	35Y4	.69	872A	3.50
6AU6	.69	6W4	.69	50A5	.69	5146	4.00
6AX4	.79	6W6	.69	50A5	.69	5146	4.00
6BA6	.59	6X4	2/81	50B5	.69	5879	.98
6BA7	1.00	6X5	.69	50C5	.69	5881	2.70
6BD6	.69	6Y6	.97	50L6	.69	5850	3.90
6BE6	.59	7H7	.89	KT66	3.29	5654	1.00
6BG6	1.59	12AL5	.59	75L	.46	5894	12.00
6BN6	.72	12AQ5	.75	80	.59	7193	10/81

TUBES WANTED! WE BUY! SELL & TRADE!

**"TAB" FOR TRANSISTORS & DIODES!!!!**  
Factory Tested & Guaranteed!  
Full Length Leads  
U.S.A. Mfg.

PNP HI Power 15 Amp  
2N441, 2N277 \$1.12 for \$10  
2N442, 2N278 \$3.40 for \$24.43, 2N174 \$4 @ 10 for \$23, 20 for \$70  
3 Amp, 2N155, 2N156, 2N255, 2N256, 2N307, 2N554, TO3GP .49 @ 5 for \$2; 100 for \$25  
PNP 2N123, 2N107, CK722 5 for \$1; NPN 2N292, 2N3, 2N107, CK722 5 for \$1; PNP 2N223 c30 @ 12 for \$9, 100 for \$65  
PNP 2N670/300MW c50 @ 10 for \$4, 50 for \$18; PNP 2N671/1 Watt c75 @ 10 for \$6, 50 for \$25  
Round or Diamond Base Mica Mtd Kit c30 @ Power Heat Sink Fins 80 \$3.39  
Kit Glass Diodes equiv. 1N34A, 46, 48, 51, 60, 64, 87, 105, 109, 147, 267, 268, 295, 12 for \$1, 100 for \$6, 1000 for \$50



"VARIAD" Type Variable Transformer  
"SUPERIOR" Powerstat Type 10  
165 Watt 0 to 132V Special \$6 each, 2 for \$10

**"TAB", SILICON 750MA\* DIODES**  
NEWEST TYPE! LOW LEAKAGE  
D.C. or Batty. Derate 20%

rms/plv	70/100	rms/plv	140/200	rms/plv	210/300		
35/50	.98	70/100	.98	140/200	.98		
rms/plv	280/400	rms/plv	350/500	rms/plv	420/600	rms/plv	490/700
.38	.50	.63	.77				
rms/plv	560/800	rms/plv	630/900	rms/plv	700/1000	rms/plv	770/1100
.83	.98	1.08	1.35				

Low Priced T300 Silicon Diodes  
Rated 400piv/280rms@300Ma@100°C  
.25 each; 30 for \$7; 100 for \$22; 500 for \$100  
Diode order \$10 shipped Post free  
GTD! Octal Silicon-SU4G-Tube Replacement  
1120Rms 1600Piv \$4 @ 2 for \$6; 4 for \$10

**SILICON POWER DIODE STUDS\***  
Operation Up to 125°C Case Temp.

D.C. Amps	50Piv	100Piv	150Piv	200Piv
2	35Rms	70Rms	105Rms	140Rms
6	.25	.35	.45	.55
12	.60	.85	1.00	1.25
35	.70	1.00	1.25	1.50
6	.85	1.20	1.50	1.70
12	1.80	2.15	2.50	2.90
35	3.75	4.50	4.95	5.70
70	4.00	5.70	6.90	8.40
240				

\*Derate 20% for Battery or Capacitive Load or D.C. Blocking! \*Stud mounted on Heat-sink.

TWO 866A's and FILAMENT \$6  
XFMR 10 Kv Insitd SPECIAL!

**NEW BATTERY CHARGER BC612X**  
For 6 or 12 Volt Batteries  
Trickle & Full Charge up to 10 amps  
Charges 6 & 12 volt batteries.  
BUILT ready to use BC612X @ \$14.00  
BC612B up to 2 amps.....\$7.45




**TRANSISTOR POWER CONVERTER**  
12VDC to 500VDC up to 200MA  
100 Watts Tap at 250VDC  
Type C1225E \$30



12VDC to 250VDC up to 150MA  
Type C1225E \$30

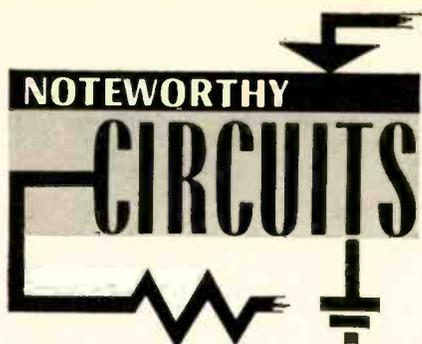**"TAB"** TERMS: Money Back Guarantee!  
Our 18th year, 52 min. order  
F.O.B. N.Y.C. Add shipping charges  
or for C.O.D. 25% Dep. Prices  
shown subject to change.  
111-GA Liberty St., N.Y. 6, N.Y.  
Send 25¢ for Catalog  
PHONE: RECTOR 2-6243




**ONE-TRANSISTOR RECEIVER**

Simple transistor circuits interest neophytes and advanced experimenters alike. Here is the circuit of a high-performance regenerative receiver that appeared in *Wireless World* (London, England).

generation is controlled by adjusting the emitter resistance, thus varying the collector current.

C1 is in series with C2 across the coil so the low-frequency end of the tuning range will be limited when using a nonadjustable antenna coil. You can get full tuning coverage by using an antenna coil with an adjustable ferrite core.

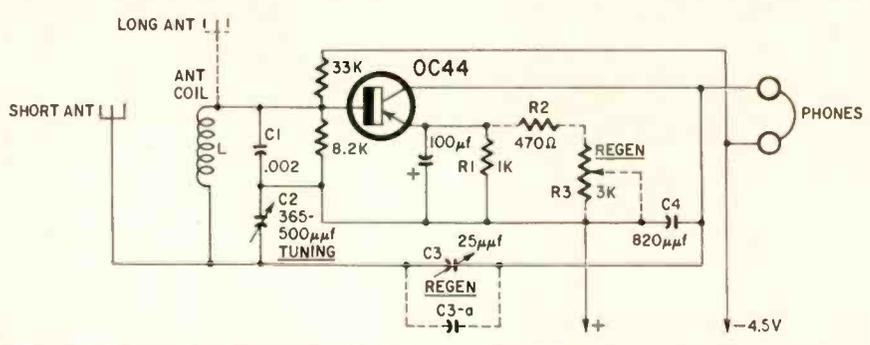The more common regenerative sets require either a tapped tuning coil or one with a tiekler winding. This circuit, based on the Colpitts oscillator, uses a




capacitive voltage divider (C1 and C2) to provide the tapping point across the coil. Regeneration is controlled by feedback capacitor C3. Capacitive regeneration controls are generally quieter and they have a tendency to cause detuning. Some detuning occurs in this set. This is because C4 and regeneration control C3 are in series across tuning capacitor C2. You can eliminate detuning by replacing C3 with a fixed value (C3-a) and replacing emitter resistor R1 with R2 and pot (R3) in series. Now, re-

The set works well with a short whip antenna connected to the "hot" (collector) end of the coil. A long antenna improves reception. Connect it to the low (base) end of the coil as shown in dashed lines or to the hot end through a capacitor of around 20 µf.

The set will cover the 140-425-kc band simply by substituting a suitable coil. For short-wave reception, use an OC170 or equivalent high-frequency transistor and reduce the values of C1 and C2 and experiment with their ratio to obtain smooth regeneration control.

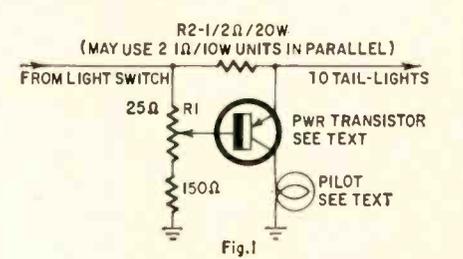**MORE TAIL-LIGHT MONITORS**

I noted the tail-light monitor circuit on page 108 of the April issue and decided to send you mine. This circuit (Fig. 1) uses less than half as many parts and no harness wiring. The circuit is adapted for 6- and 12-volt cars with either negative or positive ground by using the proper pilot light and transistor. With this circuit, the light comes on when either tail light goes out. (It does not indicate which light is out but, at least, it tells you that one is not working.)



The transistor is an audio power output type like those used in auto radios. A p-n-p type is used in a car with negative ground and a n-p-n type with positive grounds. Use either a 6- or 12-volt pilot lamp with a current rating not exceeding that of the transistor.

then back off until it just goes out. No further adjustment should be needed. The unit can be built into a small metal box and clipped under the dashboard. The voltage drop across R2 is too small to reduce light output noticeably. I suggest mounting R2 outside the box for cooling.—R. B. Clifton

To adjust, turn on the headlights and vary R1 until the pilot lamp comes on,

Many drivers frequently overlook the colored dashboard lights used for turn,

# SEE!

what **Radio-Electronics** has on tap for you **NEXT MONTH**

## CLOSED CIRCUIT TV

More and more TV closed circuit systems are being installed in schools, industrial plants, hotels, hospitals, public institutions. Here's a new frontier for installation and repair technicians. This thought-generating feature describes it for you.

## EASILY CONSTRUCTED AUDIO GENERATOR

Has only four transistors, yet it produces sine waves from 15 to 150,000 cycles. Obviously ideal for checking hi-fi equipment. You'll be able to think of many other uses for it too.

## TRANSISTOR POWER SUPPLY FOR YOUR SHOP

Build this hard-working 5-transistor supply. It will give you regulated voltage from 0.5 to 28 volts, and supply 2 amperes regulated up to 15 volts, 3 amperes from 15 to 28.

## RECORDING SOUNDS IN NATURE


Bird watchers go electronic! Dr. Peter Paul Kellogg, Professor of Ornithology and Biological Acoustics in the Department of Conservation and assistant director of the Laboratory of Ornithology at Cornell University describes some of the fascinating techniques used to record bird songs and other natural sounds. Something different for audio men.

Plus many other stimulating features and a dozen regular departments.



**FEBRUARY ISSUE  
ON SALE JANUARY 23**

JANUARY, 1962

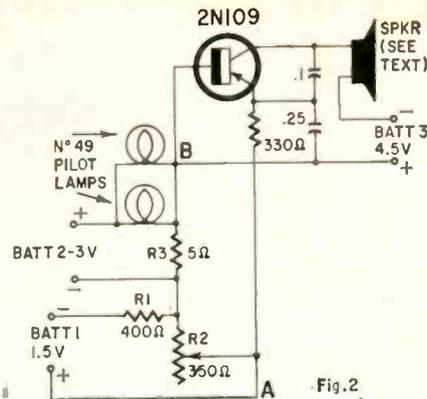

high-beam, ignition and oil-pressure indicators. I decided that a tail-light monitor should provide an audible signal to demand immediate attention. I haven't developed a practical circuit for my car, but the diagram (Fig. 2) shows an experimental circuit that works.

In this model I used a 3-volt battery (BATT 2) to represent the car's battery and two No. 49 (2.0-volt 60-ma) lamps as the tail lights. A 5-ohm resistor (R3) is in series with the battery and the lamps. The drop across this resistor is 0.5 volt. R1, R2 and BATT 1 are connected as shown and R2 is adjusted for zero volts (or milliamperes) between points A and B. If either lamp fails, the voltage between A and B rises to 0.25. It rises to 0.5 volt if both burn out. This small voltage triggers the transistor oscillator.

The oscillator is similar to that described by Charles Dewey in the June 1959 issue. For the speaker and oscillator tank, I used the driver element from an old (antique) horn type radio speaker. Because of the type of construction, the older elements provide higher output than the modern type.—Robert E. Flanagan

[Experimenters interested in the audible tail-light monitor might be able to simplify the circuit by using the car's battery for BATT 2 and BATT 3. An inexpensive audio power transistor and a small speaker and output transformer may be used in the oscillator circuit. The voltage of BATT 1 and the values of R1 and R2 can be determined experimentally. Send us details on any practical circuit that you develop from this.—Editor] **END**



We won't be able to get to that till New Year's eve.

**BECOME A RADIO TECHNICIAN  
FOR ONLY \$26.95**

**BUILD 20 RADIO  
CIRCUITS AT HOME**

with the New **PROGRESSIVE RADIO "EDU-KIT"®** only \$26.95

**ALL Guaranteed to Work!**

**A Complete Home Radio Course**

- 12 Receivers
- 3 Transmitters
- Signal Tracer
- Signal Injector
- Code Oscillator
- Sq. Wave Generator
- Amplifier

- No Knowledge of Radio Necessary
- No Additional Parts or Tools Needed
- Excellent Background for TV

**FREE** Set of Tools, Pliers-Cutters, Tester, Soldering Iron, Alignment Tool, Wrench Set.

**WHAT THE "EDU-KIT" OFFERS YOU**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. You will learn radio theory, construction and servicing. You will learn how to build radios, using regular schematics; how to solder and wire in a professional manner; how to service and trouble-shoot radios. You will learn how to work with punched metal chassis as well as the new Printed Circuit chassis. You will learn the principles of RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will build 20 Receivers, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator, Amplifier and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for TV. In brief, you will receive a basic education in Electronics and Radio, worth many times the small price you pay, only \$26.95 complete.

**PROGRESSIVE TEACHING METHOD**

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics trainings. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." You begin by building a simple radio. Gradually, in a progressive manner, and at your own rate, you construct more advanced multi-tube radio circuits, learn more advanced theory and techniques, and do work like a professional radio technician. These circuits operate on your regular AC or DC house current.

**THE KIT FOR EVERYONE**

You do not need the slightest background in radio or science. The "Edu-Kit" is used by young and old, schools and clubs, by Armed Forces Personnel and Veterans Administration for training and rehabilitation. One of the most important aspects of the "Edu-Kit" is the Consultation Service which we provide. We welcome students to send us their problems, whether related to any of the material covered in the "Edu-Kit" course, or encountered in other experiences in the field of electronics.

**THE "EDU-KIT" IS COMPLETE**

You will receive all parts and instructions necessary to build 20 different radio and electronic circuits, each guaranteed to operate. Our kits contain tubes, tube sockets, variable electrolytic, mica, ceramic and paper dielectric condensers, resistors, test strips, coils, hardware, tubing, punched metal chassis, instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls, switches, etc. In addition, you receive Printed Circuit materials, including Printed Circuit Chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, including: Pliers-Cutters, an alignment tool, professional electric soldering iron, Wrench set, and self-powered, dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide, FCC Amateur License Training Book, and a Quiz Book. All parts, components, etc., of the "Edu-Kit" are 100% unconditionally guaranteed, brand new, carefully selected, tested and matched. Everything is yours to keep. The complete price of this practical home Radio and Electronics course is only \$26.95.

**TROUBLE-SHOOTING LESSONS**

You will learn to trouble-shoot and service radios, using the professional Signal Tracer, the unique Signal Injector and the dynamic Radio and Electronics Tester. Our Consultation Service will help you with any technical problems.

**FREE EXTRAS**

- Set of Tools • Radio Book • Radio and Electronics Tester • Electric Soldering Iron • Pliers-Cutters • Alignment Tool • Tester Instruction Book • Hi-Fi Book • TV Book • Quiz Book • Membership in Radio-TV Club • Consultation Service • FCC Amateur License Training • Printed Circuitry • Certificate of Merit • Valuable Discount Card • Wrench Set

**UNCONDITIONAL MONEY-BACK GUARANTEE**


**ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00**

- "Edu-Kit" Postpaid. Enclosed full payment of \$26.95.
- "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name \_\_\_\_\_  
Address \_\_\_\_\_

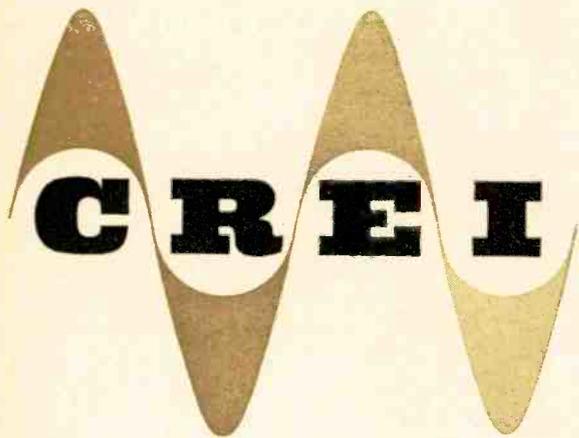**PROGRESSIVE "EDU-KITS" INC.**


1186 Broadway, Dept. 192G, Hewlett, N. Y.



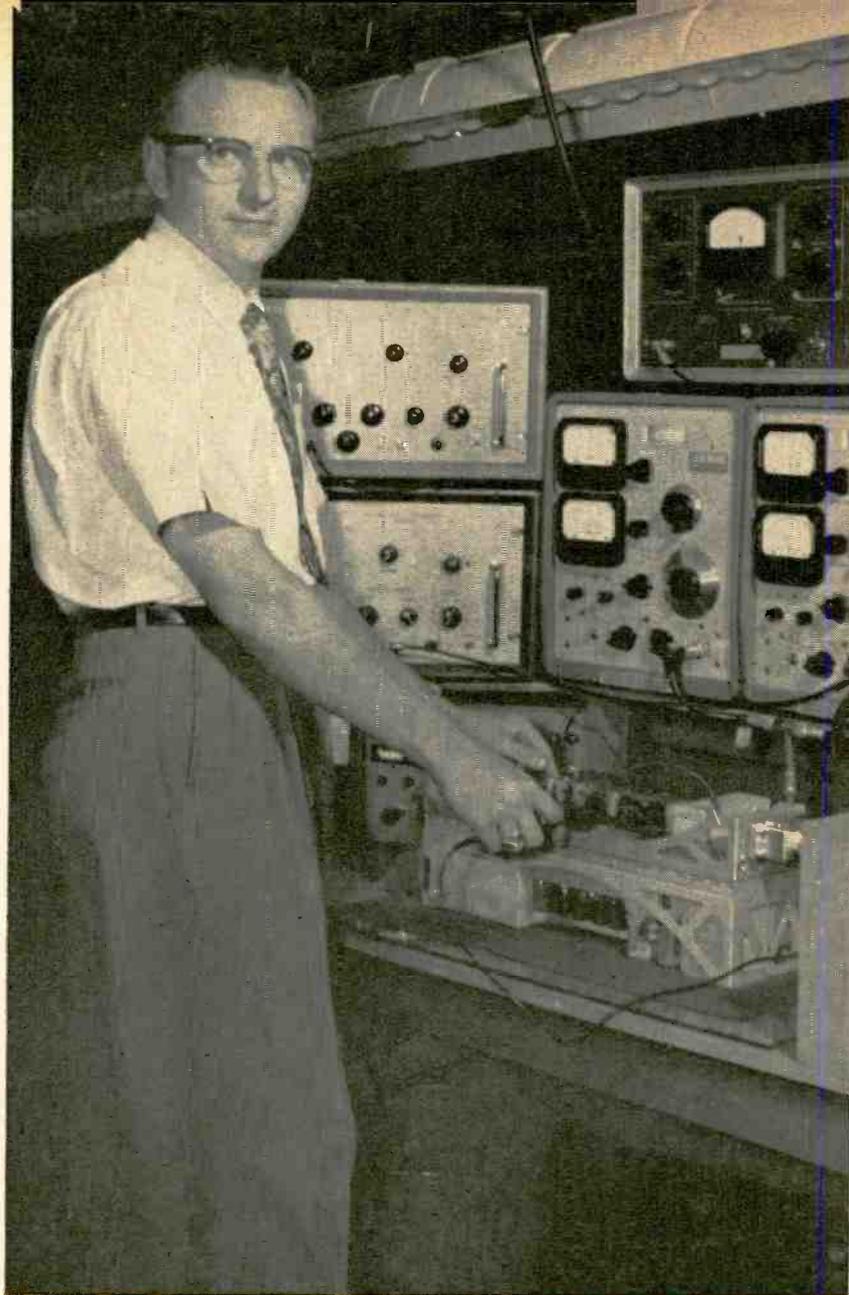**"a CREI home study program helped me feel at home with electronics engineers."**

"Since I took a CREI Home Study Program in Electronic Engineering Technology, my pay has increased a great deal and my responsibilities tripled. At present I am Supervisor, Electronic Test Dept. Your course has given me the background to feel at home with Electronics Engineers on the job."

*Richard S. Conway*  
Supervisor, Electronic Test Dept.  
Wilcox Electric Co.  
Kansas City, Missouri



**ELECTRONICS KNOWLEDGE YOU CAN USE.** *CREI Home Study preparation gives R. S. Conway the technical background to deal with Engineers as Supervisor, Electronic Test Dept., Wilcox Electric Co.*

**INDUSTRY-RECOGNIZED CREI HOME STUDY PROGRAMS PREPARE YOU FOR INCREASED RESPONSIBILITIES AND HIGHER-PAYING POSITIONS IN THE EXPANDING ELECTRONICS FIELD.**

**THERE IS A CREI PROGRAM TO MEET YOUR NEEDS.** Today thousands of advanced electronics personnel—engineering technicians, engineers, administrators, executives—attribute their present high salaries and positions to their CREI home study of Electronic Engineering Technology. Wherever you go—wherever thorough knowledge of electronic engineering technology is a prime requisite—CREI Home Study students and alumni are welcomed.

**TOP SCIENTISTS CONTRIBUTE TO COURSES.** More than 20,500 CREI students are presently working in almost every phase of electronics in all 50 states and most countries in the free world. They study courses to which a number of today's leading engineers and scientists have contributed. They are guided and assisted by CREI's staff of experienced instructors. How long it takes to complete a CREI Home Study Program depends on on-the-job experience, the amount of time devoted to study and the program selected.


**DEMAND FOR CREI-PREPARED MEN IS GREAT.** It far exceeds the supply and has for many years. Specifically designed to prepare you for responsible positions in electronics, CREI texts include the



**EMPLOYERS GIVE YOU SPECIAL CONSIDERATION** for advancement with CREI Home Study preparation. Quality Control Manager Ray V. Smith of Wilcox Electric Co. explains this to CREI alumnus Conway.



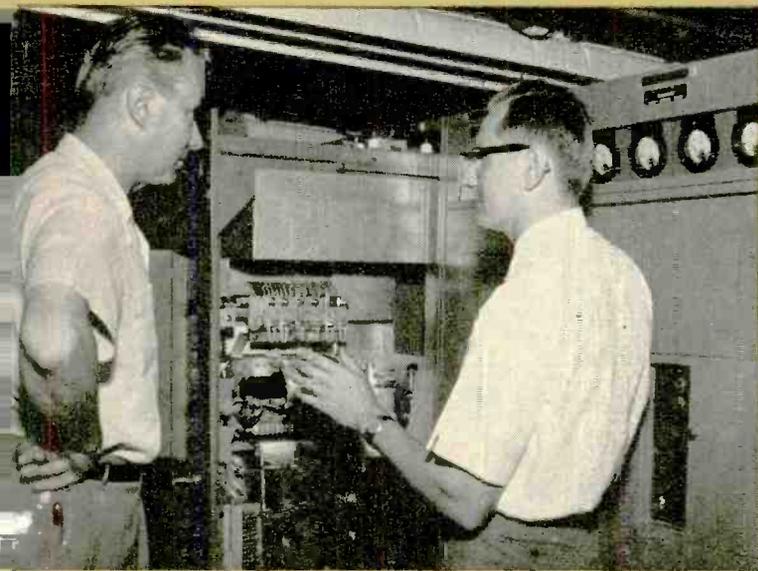**PREPARE FOR A SECURE FUTURE** in electronics with a CREI Home Study Program. Richard Conway is shown relaxing in his yard with his children. CREI helped further his career, increase his income.



**INCREASE YOUR PROFESSIONAL STANDING.** A CREI Home Study Program helps you gain new authority and respect. Examining a complex installation with Conway is R. M. Soldanel, a technician at Wilcox Electric Co. who is currently studying a CREI Program at home.



**YOUR WHOLE FAMILY SHARES YOUR SUCCESS.** Living is better for everyone when you get promotions and advancements through CREI Home Study. Above, Mrs. Conway and their two children, Cynthia and David, share Richard Conway's success.

latest advancements in electronics. We invite you to check the thoroughness and completeness of CREI Home Study Programs in the catalog provided on request. They include:

- INTRODUCTION TO ELECTRONIC ENGINEERING TECHNOLOGY • ELECTRONIC ENGINEERING TECHNOLOGY • SPECIALIZED COMMUNICATIONS ENGINEERING TECHNOLOGY • SPECIALIZED AERONAUTICAL AND NAVIGATIONAL ENGINEERING TECHNOLOGY • SPECIALIZED TELEVISION ENGINEERING TECHNOLOGY • SPECIALIZED SERVOMECHANISMS AND COMPUTER ENGINEERING TECHNOLOGY • SPECIALIZED ENGINEERING MATHEMATICS • AUTOMATION AND INDUSTRIAL ELECTRONIC ENGINEERING TECHNOLOGY • NUCLEAR ENGINEERING TECHNOLOGY

**RATES HIGH WITH INDUSTRY.** The high calibre of CREI Home Study Programs is attested to by America's biggest corporations, where CREI students and alumni attain positions ranging from engineering technicians to engineers to top officials. Such companies are National Broadcasting Company, Pan American Airways, Federal Electric Corporation, The Martin Company, Northwest Telephone Company, Mackay Radio, Florida Power and Light, and many others. These companies not only recognize the educational qualifications of CREI men, but often pay all or part of the tuition.


**ELECTRONICS HOME STUDY SPECIALISTS.** CREI Home Study Programs are the product of 35 years of experience; CREI itself was among the first to have its curricula accredited by the Engi-

neers' Council for Professional Development. Each program is developed with the same painstaking skill and care that CREI put into its World War II electronics courses for the Army Signal Corps, its special radio courses for the Navy, and its post-war group training programs for leading aviation and electronics companies. For those who can attend in person, CREI maintains a Residence School in Washington, D. C., also offering ECPD accredited Technical Institute curricula.

**REQUIREMENTS FOR ENROLLMENT.** Pre-requisite is a high school education or equivalent plus electronics training and/or practical electronics experience. (Electronics experience and/or training not necessary for Residence School.) If you qualify, send for the latest CREI catalog at no cost. Veterans may apply under the G.I. Bill. If you're doubtful about your qualifications, let us check them for you. Use the coupon inserted between these pages or—if coupon has been removed—send qualifications to:



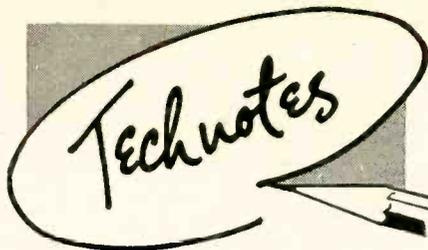**The Capitol Radio Engineering Institute**  
 ECPD Accredited Technical Institute Curricula • Founded 1937  
 Dept 1401-E 3224 Sixteenth St., N.W.  
 Washington 10, D.C.



### SIGNAL TRACING


Although arcing and breakdown of defective components should show up in the stage in which they are occurring, sometimes such a defect in an rf stage will not affect the signal until it has gone through the second detector. One such instance was when the 10.7-mc input if transformer of an AM-FM receiver went bad. The insulating material between the primary and secondary had broken down and tiny sparks were intermittently jumping, causing loud random noises from the speaker. Tracing the signal showed that the first place the noise became apparent was in the first audio tube although the sparks were jumping two stages ahead of the audio section. In this case, the defective transformer was located by visually sighting the tiny blue sparks.—*Alfred L. Hollinden*

### WESTINGHOUSE V-2373

The trouble was no raster, sound OK. There was 15 kv on the high-voltage lead to the pix tube but a weak thin spark indicated low current. The outside man had replaced a gassy 1X2-B. On the bench all tubes checked OK.

After a while, the fault became obvious. The 1X2-B had been replaced with a 1AX2. Unfortunately, filament ratings of these two tubes are different (1X2-B—1.25 volts, 200 ma; 1AX2—1.4 volts, 650 ma).

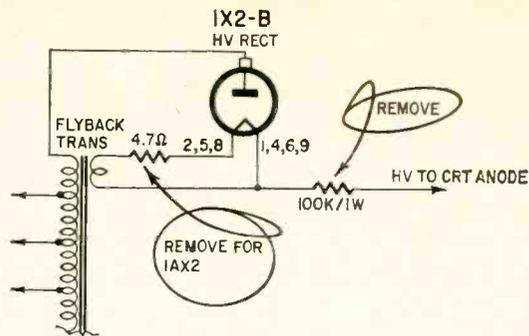To substitute the 1AX2 for a 1X2-B, the current limiting resistor must be removed (4.7 ohms in series with



the filament). At the same time, you might remove the 100,000-ohm 1-watt resistor in the high-voltage lead.—*Nate Silverman*

### RCA 21CT7865

The set came in with a buzz that the volume control had no effect on. There were no bad components in the audio or sync circuits, and it looked like this job was going to be a doozy. While tapping a couple of tubes and twiddling my thumbs, I happened to move a couple of leads around. The buzz varied with the movement. Isolating the lead causing the trouble showed that the yellow lead which carries the flyback pulse from the horizontal output transformer to the plate of the age amplifier was at fault. Changing the lead dress removed the buzz. I found that running the lead around the outside of the chassis opening for the PW200B board was best. If the lead is run across the board, you get buzz.—*Chester C. Lawrence*

### MAGNAVOX CHASSIS 29 SERIES

A common complaint with this receiver is decreased horizontal size. When this happens and normal servicing does not reveal any faults, check the 6DQ6's cathode resistor (horizontal output). If off value, replace it with a

**NEW MODEL 107A DELUXE "TRI-TESTER"**

ONLY \$1495.00 NET

TESTS ALL TUBES

Here's the finest, fastest tester at a popular price. Tests 9-pin NOVARS, 12-pin COMPACTRONS, new 10-pin tubes, NUVISTORS and all previous standard types. Triple test offers every important check you need to make money servicing—*Dynamic Mutual Conductance Test* on pre-wired chassis, *Cathode Emission Test* by free point selector system, and patented *Grid Circuit Test* with up to 11 simultaneous checks for leaks, shorts and grid emission. In handsome carrying case with handy chart for tube set-up data. Meets specifications for Federal Stock Classification: Tube Tester Type 107—FSN—6625-713-9075.

See your distributor for complete information.

**SECO ELECTRONICS, INC.**  
5039 Penn Ave. So., Minneapolis 19, Minn.

Please send FREE  107A operating instructions and schematic  "How To Test Tubes" chart  Seco full line folder.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

**ORGAN BUILDERS MANUAL**

Assemble a Beautiful *Artisan* ORGAN

### "20th Century Successor to the Pipe Organ"

Build an exciting Artisan organ, with either one, two or three manuals. Meets American Guild of Organists specifications.

This 160 page manual gives a wealth of information on this thrilling hobby, plus complete specifications, prices and parts lists. World's largest selection of organ parts and kits. "Horse-shoe" or conventional console.

Housewives, doctors, teen-agers, do-it-yourself fans by the hundreds are now enjoying this creative and rewarding hobby.

Step-by-step instructions are so simple anyone can follow them. If you can handle a soldering iron, you can build your own full size electronic organ and save hundreds of dollars.

**SEND \$2.00 with coupon TODAY!**

Please send me the Organ Builders Manual Enclosed \$2.00

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_  
State \_\_\_\_\_

*Artisan* Organ Division,  
Dorsett Electronics, Inc.  
4949R York Blvd. • Los Angeles 42, Calif.

**CONVERT TO COLOR TV**

**COLORDAPTOR**—A simple 10-tube circuit and rotating color wheel converts any size B & W TV to receive compatible color.

**COLORDAPTOR**— Easily attached to any TV set, does not affect normal operation, often built from parts experimenters have on hand. **BRILLIANT COLOR!**

Complete booklet—gives theory of operation, all construction details, schematic, and sample color filters. **\$195**

Essential Parts Kit— Includes all special parts—coils, delay line, crystal, color filters. Add \$1.00 for sets over 16". **\$19.95**

**COLORDAPTOR** 1798 Santa Cruz, Menlo Park, Calif.

**TV PICTURE TUBES** All Aluminized Glass Types **BUY DIRECT AND SAVE**

• 12LP4—\$8.95 • 17BP4—\$9.95 • 21AL/ATP4—\$16.75  
• 24DP4—\$24.50 • 27EP4—\$39.95

ALL TYPES AVAILABLE All Prices with old tube F.O.B. Chicago

These tubes are made from reprocessed glass. All materials including electron gun are brand new.

**PICTURE TUBE OUTLET** FREE... Write for complete Picture Tube list  
2922 MILWAUKEE • Chicago 18

**HI-FI RECORDING TAPE**

Splice Free (except 2400') Freq. Resp.; 20, 20,000 cps. 15 day money-back guarantee


1200' 7" Acetate	\$1.29	\$1.17	99¢
1800' 7" Acetate	1.79	1.59	1.45
1800' 7" Mylar	1.99	1.95	1.85
2400' 7" Mylar	2.69	2.59	2.49
2400' 7" Tensitized mylar	2.99	2.95	2.90

Can Be Assorted. Add 15¢ Postage Per Reel 10¢ for 24+ Lot Orders

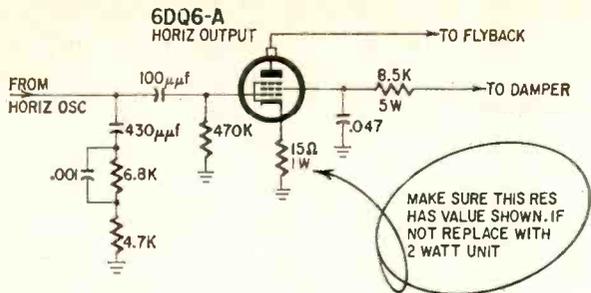**HI-FI COMPONENTS, TAPE RECORDERS**

At wholesale prices shipped within 24-48 hours. We'll airmail low quotes on your packaged HI-FI inquiries. Send for free wholesale catalogue.

**CARSTON** 125-RD East 88 St. New York 28, N. Y.



15-ohm 2-watt carbon unit. In early runs of this chassis, this resistor had a tendency to heat and change in value.—*M. L. Leonard*

### TAPE RECORDER TROUBLE

A tape recorder was brought into the shop several days ago with the complaint that it was picking up signals from a local FM station. The trouble was apparently due to the tuning effect caused by inductance and capacitance in the grid circuit of the first stage, for a 10,000-ohm resistor in series with the grid cured the trouble.—*John A. Comstock*

### HEATHKIT FM-3A TUNER

If distortion and insensitivity on weak signals are noted, the cause is very likely in the 6AL5 detector tube. This is especially true if the no-signal background hiss cannot be heard. The tube may test good, as the trouble is excessive contact potential, which will not show up in most tests. The remedy is a new tube.—*Charles Erwin Cohn*

### RCA 8-BT-10K


*Complaint:* Audio distortion.

*Cause:* Resistor R13 went up in value from its nominal rating of 3,600 ohms. It is in the bias circuit for the output transistors and as it goes up in value, the bias goes up too. As the output transistors are in a class-B circuit, a small increase in bias can make distortion noticeable. When re-
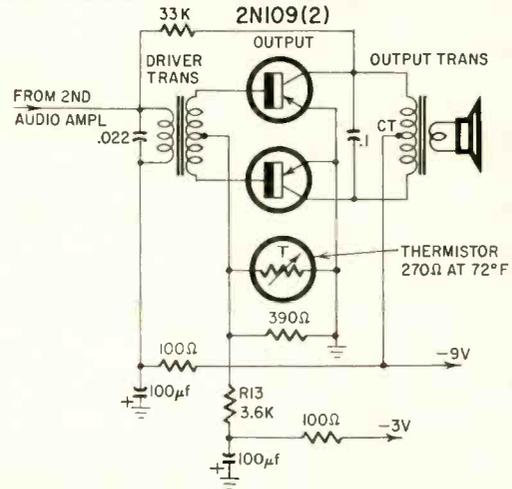
## WE BUY TECHNOTES

RADIO-ELECTRONICS wants Industrial Technotes. These should cover equipment (including closed-circuit television) actually used in industrial work, or technotes on counters, controls and other apparatus whose users are largely industrial. Unillustrated Technotes pay \$5; circuit diagrams raise the price to \$9 and acceptable photos are worth \$7 each. Send your technotes from industry to Technotes Editor, RADIO-ELECTRONICS, 154 W. 14th St., New York 11, N. Y.

placing this resistor do not use a unit that measures less than 3,300 ohms, or no-signal current will become very large. However, even a slight increase above 3,600 ohms will cause noticeable distortion.—*C. S. Lawrence* END



## TV-RADIO Servicemen or Beginners...

Send for *Coyne's*  
7-Volume Job-Training Set  
on 7-Day **FREE TRIAL!**



The First  
Practical  
TV-RADIO-  
ELECTRONICS  
Shop  
Library!

Answers **ALL** Servicing Problems **QUICKLY** . . .  
Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick". No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

**SEND NO MONEY!** Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

**"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"**

"Learned more from your first two volumes than from 5 years work."  
—Guy Bliss, New York  
"Swell set for either the serviceman or the beginner. Every service bench should have one."  
—Melvin Masbruch, Iowa.

**FREE DIAGRAM BOOK!**

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" **ABSOLUTELY FREE** just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!



Like Having An Electronics Expert Right At Your Side!

**VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES!** 300 pages of practical explanations; hundreds of illustrations.  
**VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS!** 403 pages; fully illustrated.  
**VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS!** 336 pages; hundreds of illustrations, circuit diagrams.  
**VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS!** How they work, how to use them. 368 pages; illustrated.

**VOL. 5—EVERYTHING ON TV TROUBLESHOOTING!** Covers all types of sets. 437 pages; illustrations, diagrams.  
**VOL. 6—TV CYCLOPEDIA!** Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.  
**VOL. 7—TRANSISTOR CIRCUIT HANDBOOK!** Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

ALL 7 BOOKS HAVE BRIGHT, MODERN, VINYL CLOTH WASHABLE COVERS

**FREE BOOK—FREE TRIAL COUPON!**

Educational Book Publishing Division  
**COYNE ELECTRICAL SCHOOL**

1455 W. Congress Parkway, Dept. 12R2, Chicago 7, Illinois

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per your offer. Include "Patterns & Diagrams" book FREE!

Name ..... Age .....

Address .....

City ..... Zone ..... State .....

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

**Coyne**

**ELECTRICAL SCHOOL**  
1455 W. Congress Parkway  
Dept. 12R2, Chicago 7, Illinois

# LIFE'S "LITTLE" PROBLEMS

ARE EASILY  
SOLVED  
WITH

## LITTLE SPACE

QUAM has a full line of shallow speakers, covering all popular applications.

## LITTLE TIME

QUAM speakers mount quickly and easily in the most difficult installations because of QUAM's unusual mounting bracket.

## LITTLE MONEY

QUAM speakers cost no more—and frequently cost less—than other speakers of the same size and magnet weight.

# QUAM

*Adjust-a-Cone*

# SPEAKERS


*ask for QUAM, the quality line for all your speaker needs*

Quam speakers are listed in Photofact Folders, Counterfacts, File-O-Matic, and Radio's Master.

A FREE copy of the latest QUAM catalog, listing over 100 replacement speakers, is available from your distributor, or from the Quam-Nichols Company.
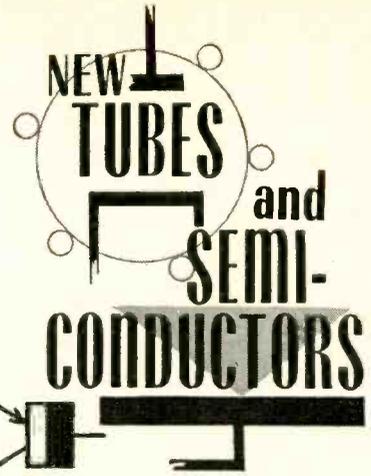
## QUAM-NICHOLS COMPANY


234 East Marquette Road Chicago 37, Illinois



SEMICONDUCTORS ARE IN CONTROL AGAIN, with only one group of Novar tubes to keep them from sweeping the column this month. We start with some MADT transistors for TV if strips, look at a couple of silicon power rectifiers and go on through a backward diode, micro-miniature switching diode, switching transistor, power rectifiers and Novar damper tubes.
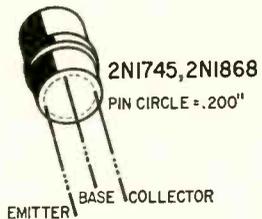
### 2N1745, 2N1868

Both units are p-n-p germanium micro-alloy diffused-base transistors (MADT) designed for vhf applications. The 2N1745 is intended for use as a 45-mc if amplifier in TV receivers (particularly in the first two stages) and the 2N1868 is a good final if amplifier. Both



can be used in general vhf applications to 200 mc where low-noise operation is not a major requirement.

Absolute maximum ratings for these Philco transistors are:


V <sub>CB</sub>	20
V <sub>CE</sub>	20
V <sub>EB</sub>	0.5
I <sub>C</sub> (ma)	50
P <sub>total</sub> (mw)	60

Electrical characteristics are:


h <sub>FE</sub> (V <sub>CE</sub> =-10, I <sub>C</sub> =2 ma) (typical)	33
PG (typical power gain) (db)	25
3-db bandwidth (typical mc)	2.4
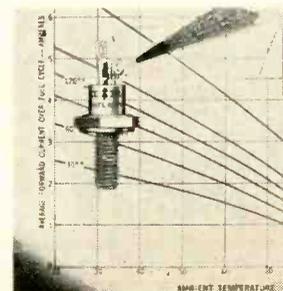
### Silicon-controlled rectifiers

Two new series of International Rectifier 3- and 5-ampere silicon-controlled rectifiers provide highly efficient


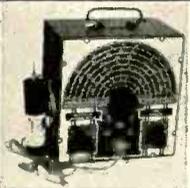
## Unbelievable LOW PRICES! NOT KITS . . . But Factory Wired and Guaranteed HIGH QUALITY INSTRUMENTS



### New! Model 999 Radio & TV SIGNAL GENERATOR

Provides highly stable signal. Generates R. F. frequencies from 150 Kilocycles to 50 Megacycles. (150 Kc. to 12.5 Mc. on Fundamentals and from 11 Mc. to 50 Mc. on Harmonics). R.F. is obtainable separately or modulated by the Audio Frequency.

Measures 7 3/4" x 7 3/4" x 5". Weight 8 Lbs.

Complete—only \$14.95



### New! TC-75 Univ. Combination TEST SPEAKER & SIGNAL TRACER

Plus resistor tester  
Plus condenser tester  
Plus output indicator

Plus speaker substitution. Plus resistor substitutor.  
Plus substitute 100 V D.C. power supply  
Plus field substitutor. Plus condenser substitutor  
Plus voice coil substitutor  
Plus signal tracer  
Plus universal output transformer  
Plus experimental one stage audio amplifier  
Plus Measures 7" x 11" x 5". Weight, 8 lbs.

Complete—only \$19.95


Order directly from METROPOLITAN ELECTRONICS • 106 Fifth Ave., New York 11, N.Y.

switching for computers, servomechanisms, static inverters and temperature, lighting and welding controls. The 3-ampere units, types 3RC5A to 3RC-40A, have a prv range from 25 to 400 and are electrically, but not mechanically equivalent, to the 2N1600 to 2N-1604.

The 5-ampere series, types 5RC2A to 5RC40A, have a prv from 25 to 400 and are electrically, but not mechanically equal to the 2N1770 to 2N1777. All permit rapid firing with minimum current (2.5 ma).

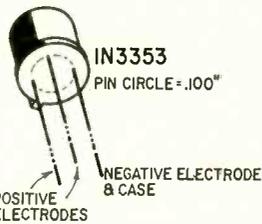**IN3353**

A germanium backward diode intended for use as a low-voltage unilateral coupling element for tunnel diode switching circuits and other low-level switching and uhf applications. The forward voltage at 1 ma is less than 100 mv. Two parallel positive electrode leads reduce lead inductance.



Maximum ratings for the Philco 1N3353 are:

Forward current (ma) 10

Reverse current (ma) 3

Electrical characteristics are:


$I_p$  (max peak-point current,  $\mu$ a) 100

$V_R$  (typical reverse voltage when  $I = 1$  ma) 510 mv

$V_F$  (typical forward voltage when  $I = 1$  ma) 80 mv

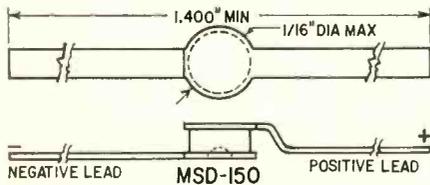**MSD-150**

A microminiature very high-speed silicon switching diode for computer circuits and general-purpose applications. It incorporates an oxide passivated planar structure built in a high resistivity epitaxial layer grown on a low resistivity silicon substrate. This makes possible a diode having high conductance, fast recovery time, low leakage and low capacitance combined with improved uniformity and reliability.



Minimum conductance is 50 ma at 1 volt and recovery time is less than 2 nano-seconds.

Maximum ratings of the G-E MSD-150 are:

$V_R$  (reverse voltage) 50

$I_{rect}$  (average rectified current, ma) 75

$P_{total}$  (mw) 250

**2N512, -A, -B**

A series of p-n-p alloy-junction germanium high-power transistors for high-power conversion, high-current switching and audio amplifier output stages.

Maximum ratings for these Texas

**NOW! FAIRCHILD PRESENTS THE NEW  
COMPANDER®  
FOR THE RECREATION OF ORIGINAL PERFORMANCE DYNAMICS**

A new, exciting and completely different development from Fairchild... a product so unusual that we believe every serious audiophile will want to know about the Compander. Briefly, the Compander is an automatic dynamic sensing device that overcomes the controls placed upon both disc and tape recordings and thereby restores the full dynamic range of the original performance. By freeing program material from the usual recording restraints the Compander brings you a giant step closer to the original performance. Accomplished without distortion, the Compander is easily integrated into any monaural or stereo quality component system. The Compander is priced at \$75.00. Write for our fully detailed bulletin.

FAIRCHILD RECORDING EQUIPMENT CORP., 10-40 45th AVE., LONG ISLAND CITY, N.Y.

**34¢ EACH**  
**\$32 Per 100 TUBES**

**ELECTRONIC MARKET**  
1 YEAR GUARANTEED  
RADIO-TV TUBES

All tubes not necessarily new, but may be electrically perfect factor 2000 at used 1000 clearly marked. ELECTRONIC MARKET will replace FREE any tube that becomes defective in use within 1 year from date of purchase. All tubes individually boxed and marked. Partial listing only. Thousands more tubes in stock.

104	354	6804	6A6	6X4	6X5	6X6	6X8	6X9	6X10	6X1048	6X10
-----	-----	------	-----	-----	-----	-----	-----	-----	------	------	------	------	-------	-------	-------	-------	--------	--------	--------	--------	------

# DX-16 Super Deluxe TV KIT

70° or 90° — operating all 17", 21", 24" and 27" PICTURE TUBES




Dimensions 17 1/2" W x 16" D  
Shipping weight 40 lb.

- ★ Produces a 16-Tube Chassis with 30-Tube performance.
- ★ Latest Intercarrier Circuitry and Multi-section Tubes.
- ★ Standard Neurotune Tuner for Selectivity & Fine Definition.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Large 250ma Power Transformer for dependable service.
- ★ 12" Speaker or Twin-cone 6" x 9" Speaker.

Includes **LIFE-SIZE** step-by-step Building Instructions  
Most Up-To-Date and Practical Course in Television

**COMPLETE KIT**  
with SET of WESTINGHOUSE TUBES \$93.49  
4-6CB6, 6U8, 6T8, 6C4, 12BH7, 6SN7, 6B06, 6W4, 6K6,  
1X2B, 5U4, 6BN4, 6QC8, incl. in the Tuner (less CRT)

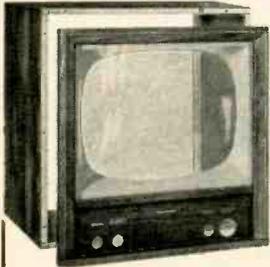Also sold on **EASY-PAYMENT-PLAN** Buy LIFE-SIZE Instructions—\$2.49—and buy Parts as you build.



23" TV CABINET KIT... \$28.47

## BUILD YOUR OWN CABINET FOR TV CHASSIS

Comparable to the type that Top Mfrs. use on high priced TV sets.

**CABINET KIT** with 90% of the job done, includes—  
**FRONT SECTION** in Solid Mahogany, Walnut or Blond Korina. **TOP, SIDES, BACK, MASK, SAFETY GLASS, ETC.**  
And **EASY-TO-FOLLOW ASSEMBLY INSTRUCTIONS**

Front, Top and Sides supplied in a beautiful Piano Finish • Knob panel undrilled • For matching Mask specify type or number of CRT used. Same price—Mahogany, Walnut or Blond. (Shipping weight 36 lbs.)

**21" CABINET KIT** 26"H, 25"W, 22"D \$26.97

21" or 23" FRONT SECTION \$19.45 24" or 27" FRONT SECTION \$24.97  
for flush to wall mounting....

**TUBULAR CONDENSERS—85°C TOP QUALITY—Equally as good for Radio or TV work**  
.0047-400v, .01-400v, .02-400v, .047-400v, .001-600v, .0047-600v, .01-600v, .02-600v, .03-600v 5¢ ea.  
.1-400v, .25-400v, .47-400v, .047-600v, .1-600v, .25-600v, .001-1000v, .0047-1000v, .01-1000v, 8¢ ea.  
.039-1000v, .047-1000v, .1-1000v, .007-1600v, .03-1600v, .05-1600v, .005-3000v, .001-6000v, 14¢ ea.

PACKAGE DEAL #1—52 TUBULAR CONDENSERS (2 of each) .. \$3.00

**ELECTROLYTIC CONDENSERS—85°C** 1-50v, 1-150v, 2-450v, 25-50v, 8-150v 16¢ ea.  
20/20-150v, 50/30-150v, 40-150v, 10-450v, 20-450v, 30-450v, 40-450v, 60-450v, 80-400v.....34¢ ea.

PACKAGE DEAL #2—14 ELECTROLYTIC CONDENSERS (1 of each) .. \$3.00

**CARBON RESISTORS—Regular factory stock in Stackpole, Speer, IRC, etc.**  
1/2 WATT 10% 10, 20, 39, 47, 68, 100, 120, 150, 270, 330, 390, 470, 560, 680, 820, 1k Ω...3¢ ea.  
1/2 WATT 10% 1800, 2200, 2700, 3300, 3900, 4700, 5600, 6800, 8200, 10k, 15k, 18k, 22k Ω...3¢ ea.  
1/2 WATT 10% 33k, 39k, 47k, 56k, 68k, 82k, 100k, 120k, 150k, 180k, 220k, 270k, 330k Ω...3¢ ea.  
1/2 WATT 10% 390k, 470k, 560k, 680k, 820k, Ω 1, 1.2, 1.5, 2.2, 4.7, 6.8, 10, 15 MEG Ω...3¢ ea.  
1 WATT 10% 3.3, 10, 39, 82, 100, 120, 150, 270, 330, 390, 470, 560, 680, 820, 1k, 1800 Ω...4¢ ea.  
1 WATT 10% 2700, 3300, 3900, 4700, 5600, 6800, 8200, 10k, 15k, 18k, 22k, 27k, 33k, 39k Ω...4¢ ea.  
1 WATT 10% 47k, 68k, 82k, 100k, 150k, 220k, 470k, 560k, 680k Ω 1, 2.2, 2.7 meg Ω...4¢ ea.  
2 WATT 10% 18, 22, 39, 47, 68, 82, 100, 120, 150, 180, 270, 330, 390, 470, 560, 680 Ω...5¢ ea.  
2 WATT 10% 820, 1k, 1500, 1800, 2200, 2700, 3300, 3900, 4700, 6800, 8200, 10k, 15k, 18k Ω...5¢ ea.  
2 WATT 10% 22k, 27k, 33k, 39k, 47k, 68k, 100k, 150k, 220k, 270k, 330k, 470k Ω 1, 10 meg Ω 5¢ ea.

PACKAGE DEAL #3—198 CARBON RESISTORS (1/2w—2 ea.) (1 & 2w—1 ea.) .. \$6.00

**WIREWOUND RESISTORS** 5-10w, 7-10w, 10-10w, 15-10w, 20-10w, 28-10w, 36-10w...9¢ ea.  
40-10w, 50-10w, 56-10w, 60-10w, 70-10w, 85-10w, 100-10w, 150-10w, 180-10w, 200-10w.....9¢ ea.  
250-10w, 350-5w, 470-10w, 560-10w, 650-10w, 680-10w, 820-5w, 1k-10w, 1500-5w, 2k-10w....9¢ ea.  
2500-10w, 3k-10w, 5k-10w, 6k-10w, 7k-10w, 8k-10w, 9k-10w, 10k-10w, 15k-10w, 20k-10w.....9¢ ea.

PACKAGE DEAL #4—37 WIREWOUND RESISTORS (1 of each) .. \$3.00

**CERAMIC CONDENSERS** 1, 2, 3, 5, 6, 10, 20, 22, 25, 30, 33, 47, 50, 56, 68, 75 mmf...3¢ ea.  
82, 100, 150, 220, 250, 270, 330, 470, 1k, 1200, 1500, 2k, 3300, 3900, 5k, 6800, 5k.....3¢ ea.

PACKAGE DEAL #5—66 CERAMIC CONDENSERS (2 of each) .. \$1.50

**MICA CONDENSERS** 5, 22, 25, 50, 60, 65, 68, 75, 80, 100, 120, 150, 220, 270, 330 mmf...3¢ ea.  
350, 470, 510, 560, 680, 820, 1k, 1500, 2k, 2500, 3300, 3900, 4700, 6k, 6800, 8k, 10k mmf.....3¢ ea.

PACKAGE DEAL #6—64 MICA CONDENSERS (2 of each) .. \$1.50

\* To order any PACKAGE DEAL, simply mention Package Number

- |  |   |  |  |  |   |  |   |  |   |  |   |   |  |  |  |  |   |   |   |  |  |   |
|--|---|--|--|--|---|--|---|--|---|--|---|---|--|--|--|--|---|---|---|--|--|---|
| <input type="checkbox"/> 15-ASST. ROTARY SWITCHES \$15 worth | <input type="checkbox"/> #18 brown or Ivory | <input type="checkbox"/> 8-ASST. LIGHT CASES handy for parts | <input type="checkbox"/> 10-6' ELECTRIC LINE CORDS w/plugs | <input type="checkbox"/> 5-TV CHEATER CORDS w/both plugs | <input type="checkbox"/> #15-"JACKPOT" TELEVISION PARTS | <input type="checkbox"/> 1-310 INDOOR TV ANT. hi-gain 3 sec. | <input type="checkbox"/> 100'-TWIN LEAD-INS WIRE 3000'heav.duty | <input type="checkbox"/> 50'-FLAT 4-COND. WIRE many purposes | <input type="checkbox"/> 15-ASST. STANDARD TUNER VHF STRIPS | <input type="checkbox"/> 6-ASST. UHFSTAND-ARD TUNER STRIPS | <input type="checkbox"/> 5-SETS SPEAKER PLUGS wired | <input type="checkbox"/> 3-AUDIO OUTPUT TRANS. 6K6 or 6V6 | <input type="checkbox"/> 2-AUDIO OUTPUT TRANS. 6K6 push-pull | <input type="checkbox"/> 3-AUDIO OUTPUT TRANS. 3Q4,3Q5,3B4 | <input type="checkbox"/> 10-CHOKE TRANS. 75Ω, 1 hy, 100 ma | <input type="checkbox"/> 4-50'SPOOLS HOOK-UP WIRE 4 colors | <input type="checkbox"/> 1-5" PM SPEAKER alnico #5 magnet | <input type="checkbox"/> 1-4" PM SPEAKER alnico #5 magnet | <input type="checkbox"/> 1-3" PM SPEAKER alnico #5 magnet | <input type="checkbox"/> 1-31/2" TWEETER SPEAKER for Hi-Fi | <input type="checkbox"/> 3-AUDIO OUTPUT TRANS. 50L8 type | <input type="checkbox"/> 2-AUDIO OUTPUT TRANS 50L8 pushpull |
|--|---|--|--|--|---|--|---|--|---|--|---|---|--|--|--|--|---|---|---|--|--|---|

# "ONE DOLLAR" Buys

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.

**DEDUCT 10% ON ANY ORDER OF \$10 OR OVER**

(ON DOLLAR BUYS)

Plus a **FREE SURPRISE PACKAGE**

- |   |  |  |  |  |  |   |  |  |  |  |  |   |   |  |  |  |  |   |   |   |   |  |   |   |   |   |  |  |   |   |  |  |   |   |  |   |  |  |   |  |   |   |   |  |   |  |   |   |   |  |   |  |  |  |   |  |  |  |  |  |   |  |   |  |   |  |   |  |  |  |   |  |  |  |  |   |  |  |   |  |  |   |  |   |   |   |  |  |  |  |  |   |   |   |   |   |   |   |
|---|--|--|--|--|--|---|--|--|--|--|--|---|---|--|--|--|--|---|---|---|---|--|---|---|---|---|--|--|---|---|--|--|---|---|--|---|--|--|---|--|---|---|---|--|---|--|---|---|---|--|---|--|--|--|---|--|--|--|--|--|---|--|---|--|---|--|---|--|--|--|---|--|--|--|--|---|--|--|---|--|--|---|--|---|---|---|--|--|--|--|--|---|---|---|---|---|---|---|
| <input type="checkbox"/> 100-ASST. 1/2 WATT RESISTORS some 5% | <input type="checkbox"/> 70-ASST. 1 WATT RESISTORS some 5% | <input type="checkbox"/> 35-ASST. 2 WATT RESISTORS some 5% | <input type="checkbox"/> 40-ASST. PRECISION RESISTORS 1% | <input type="checkbox"/> 35-CERAMIC 20MMF COND. 2 percenters | <input type="checkbox"/> 35-CERAMIC 30MMF COND. 2 percenters | <input type="checkbox"/> 300-ASST. 1/2 WATT RESISTORS short leads | <input type="checkbox"/> 50-ASST. MOLDED COND. short leads | <input type="checkbox"/> 100-RUBBER FEET for cabinets best sizes | <input type="checkbox"/> 4-OVAL LOOP AN-TENNAS ass't hi-gain | <input type="checkbox"/> 3-LOOPSTICK ANT. latest type adjustable | <input type="checkbox"/> 3-I.F. COIL TRANS-FORMERS 262kc(auto) | <input type="checkbox"/> 3-VARIABLE COND. super 420/162 mfd | <input type="checkbox"/> 3-ASST. SIZES RADIO CHASSIS PANS | <input type="checkbox"/> 20-ASST. PILOT LIGHTS popular types | <input type="checkbox"/> 3-1/2 MEG. VOLUME CONTROLS w/switch | <input type="checkbox"/> 5-1/2 MEG VOLUME CONTROLS less switch | <input type="checkbox"/> 5-ASST. 4 WATT WIREW'D CONTROLS | <input type="checkbox"/> 10-ASST. VOLUME CONTROLS less switch | <input type="checkbox"/> 5-ASST. VOLUME CONTROLS w/switch | <input type="checkbox"/> 200'-BUSS WIRE handiest size #20 | <input type="checkbox"/> 250-ASST. SOLDER-ING LUGS best sizes | <input type="checkbox"/> 10-SURE GRIP 2" ALLIGATOR CLIPS | <input type="checkbox"/> 1-GOLD GRILLE CLOTH 14x14or12x18 | <input type="checkbox"/> 10-SETS PHONO PLUGS and PINJACKS | <input type="checkbox"/> 3-I.F. COIL TRANS-FORMERS 456 kc | <input type="checkbox"/> 2-I.F. COIL TRANS. G.E. #RTL143, 458kc | <input type="checkbox"/> 3-I.F. COIL TRANS-FORMERS 10.7mc FM | <input type="checkbox"/> 50-ASST. TERMINAL STRIPS 1, 2, 3, 4 lug | <input type="checkbox"/> 35-ASST. RADIO KNOBS, screw, push-on | <input type="checkbox"/> 100-ASSORTED KNOB SET-SCREWS | <input type="checkbox"/> 25-ASSTED RADIO DIAL POINTERS | <input type="checkbox"/> 25-ASSTED CLOCK RADIO KNOBS | <input type="checkbox"/> 35-ASST. SOCKETS 7 pin, 8 pin, 9 pin | <input type="checkbox"/> 25-ASST. PRINTED CIRCUIT SOCKETS | <input type="checkbox"/> 100'-FINEST NYLON DIAL CORD best size | <input type="checkbox"/> 25-ASST. PEAKING COILS popular types | <input type="checkbox"/> 2-RCA SYNCHRO. GUIDE COILS #20SR1 | <input type="checkbox"/> 2-RATIO DETECTOR COILS 4.5 mc | <input type="checkbox"/> 2-RATIO DETECTOR COILS 10.7 mc | <input type="checkbox"/> 2-TV SOUND I.F. COILS 4.5mc | <input type="checkbox"/> 35-CERAMIC COND. 20-1000, 15-1500mmf | <input type="checkbox"/> 35-CERAMIC COND. 20-2000, 15-5000mmf | <input type="checkbox"/> 4-RCA 1U4 TUBES also serves as a 1T4 | <input type="checkbox"/> 3-SYLVANIA 35W4 TUBES | <input type="checkbox"/> TOP BRAND TUBES—1B3, 1X2B, 0Z4, 5U4, 6SN7, 6CB6, 6U8, 6V6, 6K6, 6X8, 6AX4, 6AC7, 12AT7, 12AU7 Each | <input type="checkbox"/> 25'-INSULATED SHIELDED WIRE | <input type="checkbox"/> 20-ASST. TV KNOBS, ESCUTCHEONS, etc. | <input type="checkbox"/> 15-ASST. TV COILS sync, peaking, width | <input type="checkbox"/> 5-TV CRT. SOCKETS with 18' leads | <input type="checkbox"/> 10-ASST. RADIO & TV TUBES | <input type="checkbox"/> 10-SYLVANIA 1AB5 TUBES | <input type="checkbox"/> 1-LB SPOOL ROSINS CORE SOLDER 40/60 | <input type="checkbox"/> 50'-HI-VOLTAGE WIRE top quality | <input type="checkbox"/> 5-HI-VOLT. ANODE LEADS with 20' leads | <input type="checkbox"/> 32'TEST PROD. WIRE deluxe (red or black) | <input type="checkbox"/> 600-ASST. HDWARE screws, nuts, riv., etc. | <input type="checkbox"/> 200-SELF TAPPING SCREWS #8 x 1/2" | <input type="checkbox"/> 50-ASSORTED FUSES popular sizes | <input type="checkbox"/> 50-ASST. TUBULAR CONDENSERS | <input type="checkbox"/> 50-STRIPS ASS'TED SAGNETTI best sizes | <input type="checkbox"/> 100-ASST. RUBBER GROMMETS best sizes | <input type="checkbox"/> 15-TUBULAR CONDENSERS .047-600V | <input type="checkbox"/> 20-TUBULAR CONDENSERS .01-600V | <input type="checkbox"/> 15-TUBULAR CONDENSERS .1-600V | <input type="checkbox"/> 15-TUBULAR CONDENSERS .25-600V | <input type="checkbox"/> 3-ELECTROLYTIC COND. 50/30-150v | <input type="checkbox"/> 2-ELECTROLYTIC COND. 80/80/20-150v | <input type="checkbox"/> 10-ASST. RADIO ELECTROLYTIC COND. | <input type="checkbox"/> 5-ASST. TV ELECTROLYTIC COND. | <input type="checkbox"/> 2-ELECTROLYTIC COND. 40/40-450v | <input type="checkbox"/> 4-ELECTROLYTIC COND. 80-400v | <input type="checkbox"/> 3-ELECTROLYTIC COND. 16/16-450v | <input type="checkbox"/> 2-ELECTROLYTIC COND. 50/50-150v | <input type="checkbox"/> 50-ASST. CERAMIC COND. some in 5% | <input type="checkbox"/> 50-100KΩ 1/2 WATT RESISTORS 10% | <input type="checkbox"/> 50-220K 1/2 WATT RESISTORS 10% | <input type="checkbox"/> 50-470KΩ 1/2 WATT RESISTORS 10% | <input type="checkbox"/> 50-ASST. MICA CONDENSERS some in 5% | <input type="checkbox"/> 20-ASST. WIREW'D RES. 5, 10, 20 watt | <input type="checkbox"/> 35-ASST. DISC CEF-RAMICS best numbers | <input type="checkbox"/> 35-DISC CERAMICS 5000 mmf | <input type="checkbox"/> 25-ASSORTED MICA TRIMMER COND. | <input type="checkbox"/> 5-DIODE CRYSTALS 2-1N24 & 1-1N84 1-1N82 | <input type="checkbox"/> 4-DIODE CRYSTALS 1-1N34 1-1N80 1-1N84 1-1N69 | <input type="checkbox"/> 3-SELENIUM RECT. 2-65ma & 1-75ma | <input type="checkbox"/> 2-SELENIUM RECT. 1-100ma & 1-250ma | <input type="checkbox"/> 2-SELENIUM RECT. 1-75ma & 1-350ma | <input type="checkbox"/> 2-SELENIUM RECT. 1-65ma & 1-450ma | <input type="checkbox"/> 2-SOUND DISCRIMI-NATOR COILS 10.7mc | <input type="checkbox"/> 1-70' FLYBACK TRANS. incl schematic | <input type="checkbox"/> 1-90' FLYBACK TRANS. incl schematic | <input type="checkbox"/> 1-SILICON RECTIF-IER 750 ma 500v | <input type="checkbox"/> 2-SILICON RECTIFI-ERS 500 ma | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #1 | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #2 | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #3 | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #4 | <input type="checkbox"/> 3-TV ALIGNMENT TOOLS assortment #5 |
|---|--|--|--|--|--|---|--|--|--|--|--|---|---|--|--|--|--|---|---|---|---|--|---|---|---|---|--|--|---|---|--|--|---|---|--|---|--|--|---|--|---|---|---|--|---|--|---|---|---|--|---|--|--|--|---|--|--|--|--|--|---|--|---|--|---|--|---|--|--|--|---|--|--|--|--|---|--|--|---|--|--|---|--|---|---|---|--|--|--|--|--|---|---|---|---|---|---|---|


HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.

ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.


**BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.** TELEPHONE COrtland 7-2359

Instruments transistors are:

$I_c$ (amps)	25
$I_b$ (amps)	5
$P_{total}$ (watts)	150

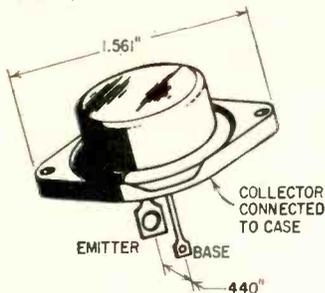

RECOMMENDED COLLECTOR CONNECTION

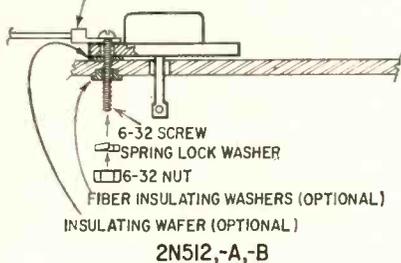


Electrical characteristics are:

	2N512, -A		-B
$BV_{CBO}$ ( $I_C=5$ ma, $I_E=0$ )	40	60	80
$BV_{CEO}$ ( $I_C=500$ ma, $I_E=0$ )	30	40	45
$h_{FE}$ ( $V_{CE}=2$ , $I_C=15$ A)	20	20	20

All ratings in this section are minimum figures.
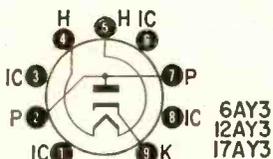
### 6AY3, 12AY3, 17AY3

A series of half-wave vacuum rectifiers designed for use as damper diodes in horizontal deflection circuits of black-and-white TV receivers. All are in the 9-pin Novar envelope. Except for heater ratings, electrical characteristics are the same for all three. The 6AY3 has a 6.3-volt 1.2-amp heater; the 12AY3 is rated at 12.6 volts 600 ma, and the 17AY3 at 16.8 volts 450 ma.



The 12AY3 and 17AY3 have an 11-second controlled warmup for use in series-string heater circuits.

Maximum ratings for these RCA tubes in damper service are:

$PIV_p$	5,000
$I_p$ (peak amps)	1.1
(dc ma)	175
$P_p$ (watts)	6.5

END




"Say, maybe it is me!"

# BOOST YOUR BRITENER SALES

with these

## SIX MAGIC WORDS

from **Perma-Power**

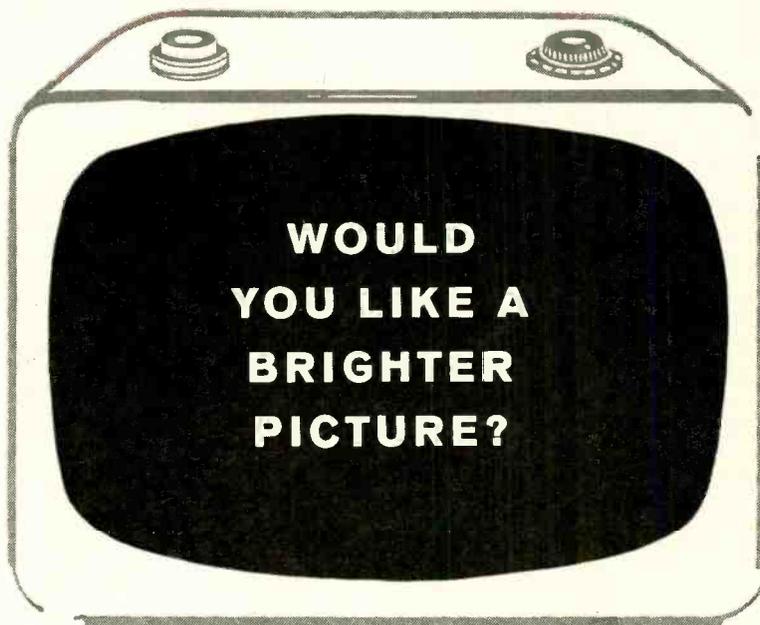

That's a question with only one possible answer—YES. Every customer wants a better, brighter picture... but doesn't realize how easy it is to get one.

When you say you'll brighten the picture—When you quote the low cost—you've sold the customer.

**Don't sell Briteners—sell Brighter Pictures!**

On every service call, remember to use Perma-Power's 6 Magic Words—Would You Like A Brighter Picture? You'll sell a 12-pack of Briteners almost as fast as you can say Perma-Power!

**Perma-Power** COMPANY—3106 N. Elston Ave.—Chicago 18

**OUT OF SPACE?**

You bet we'd be... if we were to tell you all about AUDION's 'Out of this World Hi Fi Values'.

Write for free Catalog

**audion**  
25-E Oxford Road  
Massapequa, New York

**TAPE RECORDERS**

**HI-FI COMPONENTS SLEEP LEARN KITS**

Unusual Values Free 1962 Catalog

**DRESSNER,**  
1523RE Jericho Tpke. New Hyde Park, N.Y.

**MERITAPE**  
Low cost, high quality recording tape, in boxes or cans.

**ENGINEERING DEGREE IN SCIENCE MATH** 27 or 36 MOS.

B.S. degree—36 mos. • B.E. degree—27 mos.

Accelerated year-round program prepares for early employment in fields of Science and Engineering. Regular 4-year program for B.S. Degree completed in 36 months, special engineering degree program in 27. Classes start January, March, June, July, September. Quality education. Graduates employed from coast to coast. Government approved for veteran training. Students from 50 states, 40 countries. 20 buildings; dorms, gym. Campus. Save time and money. Earn board. Write for catalog, 1712 E. Washington Boulevard, Fort Wayne 2, Indiana

**INDIANA TECHNICAL COLLEGE**

new books for  
the technician  
experimenter  
hobbyist  
who likes to **GET**  
**THINGS DONE**

**HINTS & KINKS FOR RADIO,  
TV & AUDIO**  
Edited by Martin Clifford  
Gernsback Library Book No. 103  
128 pages \$2.35



A unique and helpful selection of tips on how to use all sorts of gadgets and gimmicks like paper clips, drinking straws, grommets, corkscrews, tape and dozens of other everyday items as helps and timesavers in your servicing or experimenting be it TV, Radio, Audio—or just plain electronic tinkering. Editor Clifford selected the best from thousands of hints and kinks sent in to Radio-Electronics magazine by ingenious readers. This book is really priceless. Any one of these 280 suggestions may be worth hundreds of dollars to you in time and effort saved or in work more easily done.

**JUST A FEW OF THE COLLECTION OF 280  
HINTS & KINKS**

Test prods. • Test lead storage • Fuse puller • Sticky yokes • Reduce nuisance calls • Toothpaste-tube knob • Boost fringe reception • Servicing aids • Transistor lifesaver • Kit-building kink • Audio test rig • Soldering tip • Gun carries own sander • Novelty blinker • Spaghetti for miniature circuits • Tube tapper and wire pusher • Wing nut driver • Plus 263 more practical shortcuts, timesavers and bench helpers.

**RADIO-CONTROL HANDBOOK**  
By Howard G. McEntee  
Revised and greatly  
enlarged edition  
Gernsback Library Book No. 93  
304 pages \$4.95



Enough R/C material to fill two books. The book bulges with practical information with emphasis on how to do it, not why it happens. The original edition sold out completely after eight printings. This big second edition is completely updated—obsolescent material has been dropped, new developments added. Offers scores of new ideas, circuits and construction details on receivers, transmitters, servos, pulsers, escapements, controls, relays plus inside tips on installation, adjustments, testing and building of complete systems.

**ORDER TODAY FROM YOUR DISTRIBUTOR**  
or use this coupon  
Gernsback Library, Inc. 12  
154 West 14th St.  
New York 11, N. Y.  
Please send me the books indicated postpaid  
My remittance of \$\_\_\_\_\_ is enclosed  
\_\_\_\_\_ please list books selected by number  
NAME \_\_\_\_\_  
STREET \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

**new  
PATENTS**

**CONTROL SYSTEM**

Patent No. 2,967,278

James F. Sullivan and Vincent J. Lique, Danbury, Conn. (Assigned to Intl. Instruments, Inc., New Haven, Conn.)

Transistor circuitry plus a special meter are used to close an external circuit when current falls below a minimum limit. The circuit is opened when the current exceeds a maximum. Unlike present instruments, the pointer of this meter does not have to be attracted to and held by a magnet.

In Fig. 1, V1 is a 65-kc Colpitts oscillator. L1, L2 (generating coils) are each wound with 600 turns of No. 40 wire. They act as a tank. L3, L4 (pickup coils) each have 5,000 turns of No. 45 wire.

V2, V3 receive negative bias through R2, R3,

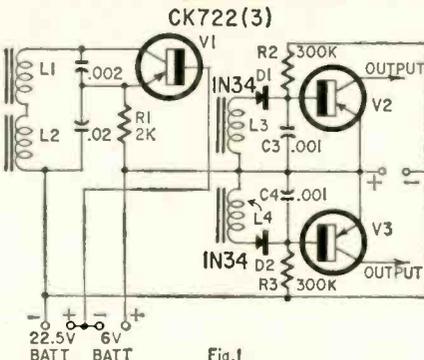


Fig. 1

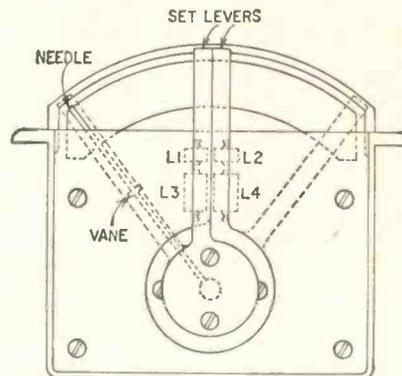


Fig. 2

respectively. If the 65-kc signal is picked up by L3 (or L4), it is rectified by the diode (D1 or D2), resulting in positive bias on C3 (or C4). Normally the positive bias is greater, so V2 and V3 are blocked.

The meter (Fig. 2) has 2 adjustable levers which may be set to the lower and upper limits of current. One generating coil and one pickup coil are mounted on each lever. The pointer of the meter carries a magnetic vane. As the pointer deflects (beneath a lever) its vane passes between a pair of coils, shielding one from the other. The 65-kc signal disappears from the pickup coil and the corresponding transistor conducts.

The outputs (not shown) of V2 and V3 are used to energize relays for opening and closing an external circuit.

to  
SERVICE  
CHARGES  
and  
RECORD  
KEEPING

**the  
business-like  
approach**

For customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national. Dave Rice's OFFICIAL PRICING DIGEST, listing over 63,000 items. \$2.50.

▲ AVAILABLE FROM YOUR DISTRIBUTOR ▼

If you want to operate on a professional level, Dave Rice's OFFICIAL ORDER BOOKS give you triplicate forms for order, invoice, and office records ... spaces for tubes, parts, serial numbers, labor and tax charges, signatures, etc. 75c per book, \$6.50 for dust-proof box of 10. *Dave Rice's*

**ELECTRONIC PUBLISHING COMPANY, INC.**  
133 N. Jefferson St. • Chicago 6, Ill.



**YOU  
SAVE  
MONEY!**

**RUSH US YOUR  
LIST OF HI-FI  
COMPONENTS  
FOR A SPECIAL  
QUOTATION**

**WRITE FOR FREE  
AUDIO DISCOUNT  
CATALOG A-15**

*New low prices on  
amplifiers, tuners, tape  
recorders, speakers, etc.*

**KEY** ELECTRONICS CO.  
120 LIBERTY ST.  
NEW YORK 6, N.Y.

## STEREO CARTRIDGE

Patent No. 2,944,118

Robert B. Gray, Erie, Pa. (Assigned to Erie Resistor Corp., Erie, Pa.)

This pickup is made of piezo-electric material. It is in the form of a bar with four arms. The junction of each pair is coated with metallic electrodes. The bar is polarized permanently by heat treatment which makes it sensitive to bending along axes X1, X2 (Fig. 1).

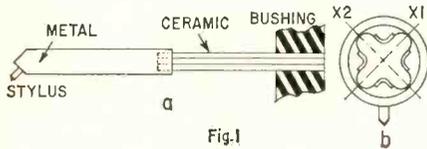


Fig. 1

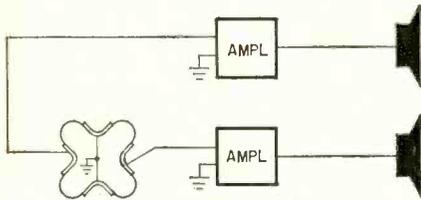


Fig. 2


The upper and lower electrodes are grounded (Fig. 2) and output is obtained from the other electrodes. Each stereo channel of a record exerts a force on the stylus which creates a strain along the two axes. Output from the side electrodes feeds separate amplifiers and speakers. Crosstalk between channels is less than 20 db.

## OSCILLATOR STARTER

Patent No. 2,970,279

Edward P. Donnelly, Jr., Seattle, Wash. (Assigned to USA as represented by Secretary of Navy)

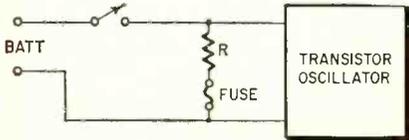Most transistor experimenters have noticed that it takes greater forward bias to start an oscillator than to keep it running. As an example, the inventor cites a sonobuoy transistor oscillator energized by a sea-water battery. The battery



voltage rises gradually when immersed, and under this condition the oscillator may not start at all.

In the diagram a shunt circuit (fuse and R) is placed across the oscillator power terminals. The battery voltage rises gradually, but in time there is enough power to blow the fuse. At this instant, a surge of current flows into the oscillator, assuring its operation.


## CLASS-B AMPLIFIER

Patent No. 2,955,257

James E. Lindsay, Moorestown, N.J. (Assigned to RCA)


A class-B driver feeds a class-B output stage. Complementary type transistors are used in each stage.

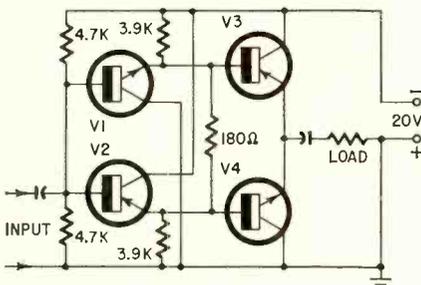With positive input, V1 conducts and V2 blocks. The drop across V1's collector drives the base of V3 positive and blocks it. With flow through V2's emitter resistor cut off, V4's base goes positive and the transistor conducts. Simi-



lar reasoning shows that V2, V3 conduct and V1, V4 block when the input is negative.

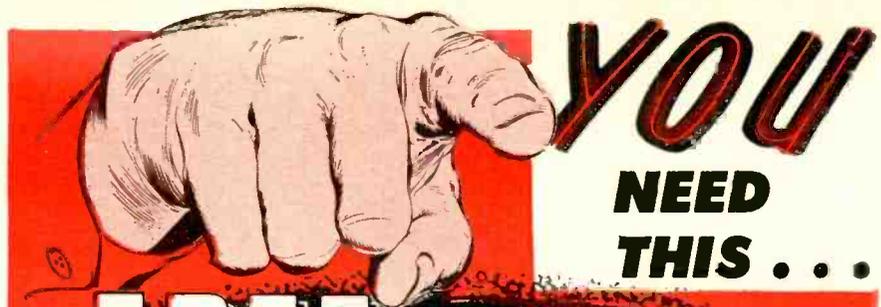One end of the load (or loud-speaker) connects the emitters of V3, V4. The other end goes to their collectors (battery impedance is zero for ac). Thus, during one half-wave of signal, the load is fed in one direction by V4. During the other half-wave, it is fed in the opposite direction by V3. END



**YOU  
NEED  
THIS...**

**FREE GIANT  
ALL NEW 1962  
BA CATALOG**



SAVE UP TO  
50% ON B-A  
SELECTED  
KITS

TOP VALUES  
IN POWER  
AND HAND  
TOOLS

HI-FI AND  
STEREO  
SYSTEMS &  
COMPONENTS

30 PAGES  
OF BARGAINS  
NOT IN ANY  
OTHER CATALOG

BURSTEIN-APPLEBEE CO. Dept. RE,  
1012-14 McGee St., Kansas City 6, Mo.

Rush me New 1962 B-A Catalog No. 621

**RUSH COUPON  
TODAY!**

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_

## TV Tuner Problems?

Simply send us your defective tuner complete: include tubes, shield cover and any damaged parts with model number and complaint.

Send for details and FREE Mailing Kit

**CASTLE TV TUNER SERVICE, INC.**

5710 NORTH WESTERN AVENUE, CHICAGO 45, ILLINOIS  
623 PALISADE AVENUE, CLIFFSIDE PARK, NEW JERSEY  
IN CANADA: 136 MAIN STREET, TORONTO 13, ONTARIO


Castle Overhaul

ALL MAKES  
ONE PRICE.

90 Day  
Warranty **995**

every standard electronic part you'll ever need is pictured and described in the 1962 RADIO ELECTRONIC MASTER

**JUST OUT!**  
**'62 EDITION**

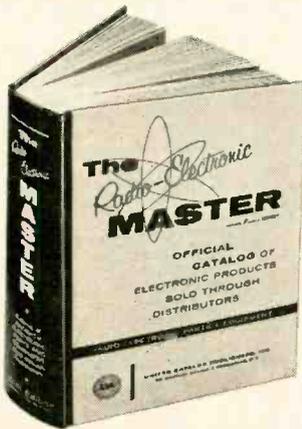

**1600 PAGES**

world's largest electronic catalog

It's new — covers all the latest radio-tv-audio electronic products for servicing, experimenting, design, industrial and military applications.

It's the world's biggest electronics purchasing guide! 1600 pages, more than 175,000 items — with descriptions, specs, illustrations and prices.

It's easy to use! organized in 32 product sections for rapid references; fully indexed to save you time. At parts distributors, \$3.95 (\$4.95 in Canada).

**THE RADIO-ELECTRONIC MASTER**  
60 Madison Ave., Hempstead, N.Y.



**INSULATE SPLICES FAST**

I always keep a length of Alphex shrinkable tubing on the bench. It has many uses. Best one is to insulate splices. Slip a length of tubing over one of the wires to be spliced. Then make



the splice just as you always do. Now center the tubing over the splice and heat it with your soldering iron. The heat will cause the tubing to shrink, making a neat tight insulated joint.—*Larry Steckler*

**SERVICE TOOL**

Braze or weld the stump of an Allen wrench to the shank of an old screwdriver to make a handy tool for reach-



ing Allen setscrews in cramped locations. A set of these, in varied sizes, makes a time-saving accessory.—*Harry J. Miller*

**SAVE DRILL BITS**

Breakage of 1/4-inch drill bits in hole saws ran high while drilling light metal chassis. When the bit went through the metal, it was difficult to keep it from breaking. We stopped this expensive annoyance by using the 1/4-inch bit only to drill the center hole. Then it is removed and a piece of 1/4-inch steel rod is substituted in the center of the saw.

Tapering the end slightly, drill holes with the hole saw.—*S. Clark*

**CHECKING SWITCHES**

One of my friends was recently drafted, and I bought his collection of radio-TV "junk" which, among other things, included 183 miscellaneous rotary and pushbutton switches. Some are

**PROOF OF SUPERIORITY  
NO OTHER MICROPHONE  
CAN MATCH!**

**LEADING NEWSWEEKLY  
MAGAZINES PICTURE E-V  
MORE OFTEN THAN THE NEXT  
FOUR BRANDS COMBINED!**

Write now for catalog of microphones preferred by top radio, TV, newsreel and sound engineers!

**Electro-Voice** ELECTRO-VOICE, INC.  
Commercial Products  
Div., Dept. 121E  
Buchanan, Michigan

those who Serve Best  
Use  
**QUIETROLE**



6 oz. SPRAY PACK CAN  
(with FREE Extender Tube)

2, 4, 8 oz. Bottles  
(with dropper)

Product of  
**QUIETROLE**  
COMPANY

Spartanburg, South Carolina

in Canada: CROSS CANADA ELECTRONICS  
12 Laurel Street, Waterloo, Ontario

There's never any doubt with QUIETROLE... it always says "Sh, Sh" to noisy controls and switches on TV, radio and electronics instruments. Now, Quietrole is even easier to use... has FREE EXTENDER TUBE that hits those hard to reach places right on the button. It's Quality Quietrole that makes those once pesty repairs easier than ever. See how Quietrole can ease the jangled nerves of even your hardest to please customers. Quietrole, helps the serviceman serve better than ever.




from junked ac-dc-battery radios; others are surplus.

I got tired of connecting ohmmeter leads to a pair of switch contacts, then looking up at the ohmmeter, to see if I got a reading. So, I simply hooked up the 6.3-volt winding from a power transformer to an ancient car radio vibrator and merely listened for the noisy vibrator to learn whether or not there was continuity between the switch contacts to which battery clips are connected. Also, as his vibrator takes more current than an ohmmeter, a bad switch contact is easily detected—vibrator vibrates very weakly and erratically.—*Nate Silverman*
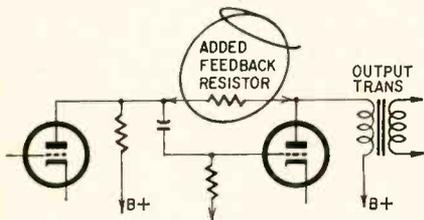
### FEEDBACK FOR AUDIO CIRCUITS

The tone quality of small radios and phonographs can be considerably improved by adding inverse feedback. Hum is also reduced and the frequency range extended.

A simple method of adding inverse feedback is to connect a 470,000- to 750,000-ohm resistor from the plate of the power output stage to the plate of the preceding amplifier (see diagram). A



higher value of resistance results in less feedback and a lower value produces more. A ½-watt rating is satisfactory for the resistor.

If you have a push-pull output stage, two identical resistors are used. The correct connection is the one which results in a loss of volume.

The difference in quality is noticeable and the slight cost and small effort worth while. There is a small loss of volume but most audio stages have plenty of gain.—*Herbert Greenberg*

END

### 50 Years Ago

In Gernsback Publications

#### HUGO GERNSBACK, Founder

Modern Electrics.....	1908
Wireless Association of America.....	1908
Electrical Experimenter.....	1913
Radio News.....	1919
Science & Invention.....	1920
Practical Electrics.....	1921
Television.....	1927
Radio-Craft.....	1929
Short-Wave Craft.....	1930
Television News.....	1931


Some larger libraries still have copies of Modern Electrics on file for interested readers.

In January, 1912, Modern Electrics

The Marconi Multiple Tuner.  
Tuned Waves, by F. M. Doolittle.  
Image Transmission.  
Wireless Telegraphy and Aeroplanes.  
Enclosed Combination Detector,  
by Stanley E. Hyde.  
Telephotography, by E. Dickey.

# ELECTRONICS

## Engineering-Technicians

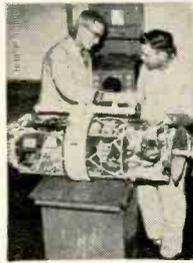

Heald's Microwave and Radar Laboratory Equipment.

Bachelor of Science Degree, 30 Months

Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Approved for Veterans  
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.  
New Term Starting Soon.

## HEALD'S ENGINEERING COLLEGE

Established 1863

Van Ness at Post, RE  
San Francisco, Calif.

Your Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_



Save 30% on 4-track  
Stereo Music on Tape!  
Empty 3 in. plastic reels 7¢ ea.

BARGAIN PRICES!

SEND FOR OUR FREE

Tape Recorder/Blank/Pre-recorded Tape Catalog

SAXITONE TAPE SALES

(Div. of Commissioned Electronics Co., Inc.)

1776 Columbia Road Washington, D.C.

Components • Recorders • Tapes  
SHIPPED PROMPTLY at WHOLESALE PRICES

Packaged Hi-Fi

Low Quotes

Air Mailed

Free 110-page  
Stereo Catalog

AUDIO UNLIMITED

190-R Lexington Ave.  
New York 16, N.Y.

## CONVERT TO COLOR TV



**COLORDAPTOR**—A simple 10-tube circuit and rotating color wheel converts any size B & W TV to receive compatible color.

**COLORDAPTOR** — Easily attached to any TV set, does not affect normal operation, often built from parts experimenters have on hand, BRILLIANT COLOR!

Complete booklet—gives theory of operation, all construction details, schematic, and sample color filters. \$195

Essential Parts Kit—Includes all special parts—coils, delay line, crystal, color filters. Add \$1.00 for sets over 16". \$19.95

COLORDAPTOR

1798 Santa Cruz,  
Menlo Park, Calif.

## Now... Tomorrow and for years to come!

### Sonar CITIZENS BAND RADIO

- 8 Channels, crystal controlled transmitter and receiver
- Tunable receiver for 22 channels
- Transmitter 100% Class B modulated
- Adjustable squelch
- Automatic noise limiter
- R. F. Power indicator
- 1 Year guarantee
- Easy to install. Ideal for home, boat, car or business. Weighs only 9 lbs. . . 4¾ x 9½ x 11¼
- FCC Type accepted\*

\*in preference to only certification

with 1 pair of  
crystals, microphone  
and power cables

**\$179.50**



Sonar  
RADIO CORPORATION

3050 West 21st Street • Brooklyn 24, N. Y.

Please send me complete information  
on Model "E" CB Radio.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_



# ELECTRIC APPLIANCES

**PAYS \$3 TO \$5 AN HOUR**  
**Spare Time, Full Time • Learn at Home**

**FREE BOOK** offered below shows how **YOU** can now have a good-paying business of your own, right in your home. No experience needed, just simple tools. Learn to repair Electric Appliances. Pays \$3-\$5 an hour!

**400 MILLION** Appliances are in American homes right now. **76 Million MORE** bought each year. People need them fixed, good times or bad. **YOU** make good money doing it. In your basement, garage, even on your kitchen table.

**Quick Way To Get Started**  
For less than 20¢ a day our easy, pictured instruction—backed by 45 years of success in home training—prepares you for top earnings in this booming field. Earl Reid of Thompson, Ohio says: "Made \$510 in one month spare time. NRI course is priceless." At no extra charge you even get all parts for your own Appliance Tester, too. Finds trouble-spots, speeds and checks your work.

Get your **FREE** Book and **FREE** Sample Lesson! Mail coupon below, letter or postcard, *now*.

### FREE BOOK • FREE LESSON

**NATIONAL RADIO INSTITUTE**, Appliance Division  
Dept. FA2, Washington 16, D. C.

Send **Free** Book, **Free** Appliance Repair Course Lesson. Am interested in:

Spare Time Earnings  My Own Business  
 Better Job

Name .....

Address .....

City ..... Zone ..... State .....

Accredited Member—National Home Study Council.

Ask By Name For

## GENUINE



your assurance of brand name quality

**NO-NOISE Volume Control and CONTACT RESTORER**

- Cleans • Lubricates • Protects
- Not a Carbon Tef. solution
- 2 oz. Bottle \$1.00
- 6 oz. Spray Can \$2.25

Net to Servicemen



**NO-NOISE TUNER-TONIC with PERMA-FILM**

- Cleans, lubricates, restores all tuners, including water type.
- Non-toxic, non-inflammable.
- For TV, radio and FM use.
- Economical—a little does a lot.
- 8 oz. Aerosol Can \$3.25

Net to Servicemen



**FREE** with each can of **ELECTRONIC CHEMICAL** products—**5" PLASTIC EXTENDER**

- Push Button Assembly
- For Pin Point Applications
- Does Not Cause Shorts

**Electronic Chemical new formula EC-44**  
Lubricates, conditions, cleans all electrical contacts. Economical... a little does a lot!

6 oz. spray can **\$3.50**  
Net to Servicemen.



**ELECTRONIC CHEMICAL CORP.**  
813 Communipaw Avenue Jersey City 4, N. J.

# HIGH-GRADE "HAM" EQUIPMENT FROM LOW-COST SURPLUS ITEMS



Volume III

— **Surplus Radio Conversion Manual** contains all data needed for putting surplus equipment to practical use.

### Contents, Volume III

**VOLUME III** — APN-1; ARC-5; ART-13; BC-191, 312, 342, 348, 375, 442, 453, 455, 456 to 459, 603, 624, 696, 1066, 1253; CBY-52000 series; COL-43065; CRC-7; DM-34D; DY-8 or DY-2A/ARR-2; FT-241A; LM; MBF; MD-7/ARC-5; RM-52, 53; R-9/APN-4; R-28/ARC-5; RT-19/ARC-4; RT-159; SCR-274N series; SCR-508, 522, 528, 538; T-15 to T-23/ARC-5; URC-4; WE-701-A. Schematics only: APA-10; APT-2; APT-5; ARR-2; ASB-5; BC-659, 1335A; CPR-46ACJ.

**\$3.00 per volume**

\*Order from your favorite electronic parts distributor.

If he cannot supply, send us his name and your remittance, and we will supply; foreign, add 10%.

### EDITORS and ENGINEERS, Ltd.

Summerland 5, California



Dealers: Electronic distributors, order from us. Bookstores, libraries, newsdealers order from Baker & Taylor, Hillside, N. J. Export (exc. Canada), order from H. M. Snyder Co., 440 Park Ave. So., N.Y. 16.



## CITIZEN BAND CLASS "D" CRYSTALS

3rd Overtone: Hermetically Sealed .005% tolerance—Meet FCC requirements. 1/2" pin spacing—.050 pin diameters. (.093 pins available, add 15¢) **\$2.95 EACH**  
ALL 22 FREQUENCIES IN STOCK!

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles):

26.965	26.975	26.985	27.005	27.015
27.025	27.035	27.055	27.065	27.075
27.085	27.105	27.115	27.125	27.135
27.155	27.165	27.175	27.185	27.205
27.215	27.225			

Matched crystal sets for all CB units \$5.90 per set. Specify equipment make and model numbers.

### RADIO CONTROL CRYSTALS in HCB/U HOLDERS—SIX FREQUENCIES

In stock for immediate delivery (frequencies listed in megacycles): tolerance .005%. 1/2" pin spacing—.050 pin diameter. (.093 pins available, add 15¢ per crystal.) Specify frequency.  
**26.995, 27.045, 27.075, 27.145, \$2.95 EACH**  
**27.195, 27.255** (add 5¢ per crystal for postage and handling)

**ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS**  
See big red display... if he doesn't stock them, send us his name and order direct from factory.

Send for **FREE CRYSTAL CATALOG #961 WITH OSCILLATOR CIRCUITS**

Now! Engineering samples and small quantities for prototypes now made either at Chicago or at Ft. Myers plant. 24 hour service!  
**CHICAGO PHONE Gladstone 3-3555**

All orders shipped 1st Class Mail. Rush order to:  
**TEXAS CRYSTALS**  
Dept. R-12, 1000 Crystal Drive, Fort Myers, Fla.  
For fastest possible service, Phone WE 6-2100



# new BOOKS

**STATIC RELAYS FOR ELECTRONIC CIRCUITS.** Edited by Richard F. Blake. Reinhold Publishing Corp., 430 Park Ave., New York, N.Y. 6 x 9 in., 198 pp. \$7

The design and application of solid-state, magnetic amplifier, and other nonmechanical relays.

**HOW TO LOCATE AND ELIMINATE RADIO AND TV INTERFERENCE (2nd Edition),** by Fred D. Rowe. John F. Rider Publisher, Inc., 116 W. 14th St., New York 11, N.Y. 5 1/2 x 8 1/2 in. 160 pp. \$2.90.

This practical book describes methods and equipment for reducing radiation from power lines and appliances.

**LINEAR GRAPHS AND ELECTRICAL NETWORKS,** by Sundaram Seshu and Myril B. Reed. Addison-Wesley Publishing Co., Inc., Reading, Mass. 6 x 9 in. 315 pp. \$9.75.

An introduction to a graphical, mathematical method for solving networks, including applications to digital computers, switching, logic. For advanced students.

**TEACH-R-MATIC STUDY COURSE NO. TV-1,** by H. G. Cisin. Harry G. Cisin, Amagansett, N.Y. 8 1/2 x 11 in. plus rotating circular disc chart 11 1/2-in. diameter. 11 pp. \$4.90.

New approach to teaching radio servicing uses "reinforced response" techniques. Numbered answers to multiple-choice questions in book are selected by turning disc chart, which indicates accuracy of answer.

**TRANSISTOR CIRCUIT ANALYSIS,** by Maurice V. Joyce and Kenneth K. Clarke. Addison-Wesley Publishing Co. Inc., Reading, Mass. 6 x 9 in. 461 pp. \$10.75.

Mathematical analysis of amplifiers, switches, oscillators and multi-vibrators, for designers and advanced engineering students.

**A PICTORIAL ALBUM OF WIRELESS AND RADIO 1905-1928,** by Harold S. Greenwood. H. S. Greenwood, 2341 Ivyland, Arcadia, Calif. 5 1/2 x 8 1/2 in. 219 pp. \$3.

A collection of photographs and reproductions of advertisements of components, radio sets, tubes and kits, from the first detectors (coherers) and early variable condensers to the first television kit. There is some explanatory text and a number of reproductions of old ads and magazine pages.

**INDUSTRIAL ELECTRONICS MADE EASY,** by Tom Jaski. Gernsback Library, 154 W. 14th St., New York 11, N.Y. 5 1/2 x 8 1/2 in. 288 pp. \$3.95.

A complete introduction covering generators, counters and computers, controls, recorders, transducers and service instruments and practices. **END**

## 'PHONES OR INSERTS WANTED

1BAs, 1BA7S, DLR5, or any sound powered Earphones wanted Urgently. Either pairs, single, or inserts. Any quantity.

Please state price and quantity.

### CONCORD ELECTRONICS

210 Church Road

Tel: HOVE 35296

Hove, Sussex, England

# SCHOOL DIRECTORY

## college degree in 27 months

Higher income . . . advancement. Major corporations regularly interview seniors. **B.S. DEGREE IN 27 MONTHS** in Engineering. **IN 36 MONTHS** in Business Administration. Small classes. Well-equipped labs. *Low costs.* Enter Mar., June, Sept., Jan. Write **J. G. McCarthy** for Catalog and Career Book.

**TRI-STATE COLLEGE**  
2412 College Avenue • Angola, Indiana

**LEARN**  
LEARN  
LEARN

LEARN  
RADAR MICROWAVES  
COMPUTERS—TRANSMITTERS  
CODE • TV • RADIO

Phila. Wireless Technical Inst.  
1533 Pine St., Philadelphia 2, Pa.  
A Non-Profit Corp.  
Founded in 1908  
Write for Free Catalog to Dept. RE-1  
Classes now forming

**ENGINEERING EDUCATION**  
for the Space Age

**NORTHROP INSTITUTE** of Technology is a privately endowed, nonprofit college of engineering offering a complete Bachelor of Science Degree Program and **TWO-YEAR** accredited technical institute curricula. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation.

**NORTHROP INSTITUTE OF TECHNOLOGY**  
1181 West Arbor Vitae Street, Inglewood 1, California

**B. S. DEGREE IN 36 MONTHS**  
INDUSTRY & GOVERNMENT NEED  
50,000 NEW ENGINEERS A YEAR!

Accelerated year-round program puts you in the job-market a whole year early! Also B.E. degree in 27 mos. Aero., Chemical, Civil, Electrical, Mechanical, Electronics; Math, Chemistry, Physics. Quality instruction; widely recognized. Graduates employed from coast to coast. Self-help program. Modest rate. Start Jan., Mar., June, July, Sept. Catalog: 1512 E. Washington Blvd., Ft. Wayne 2, Ind.

**INDIANA TECHNICAL COLLEGE**

**LEARN**  
ELECTRONIC  
ORGAN SERVICING

This new, high paying profession can now be learned easily in your spare time.

- ★ Complete Training—All Makes and Models
- ★ Scientific Teaching Aids Make Learning Easy
- ★ No Prior Knowledge of Electronics Necessary

**GET FULL DETAILS ON THIS AMAZING COURSE**  
**WRITE FOR FREE BOOKLET**

**NILES BRYANT SCHOOL**  
Dept. L, 3731 Stockton Blvd.  
Sacramento 20, California

**LEARN**  
TRANSISTOR, COMPUTER OR  
RADAR ELECTRONICS  
**AT HOME!**

Prepare now for a profitable career in one of these growing fields. Learn theory and practical application of all makes and types with proven home study courses from the Philco Technological Center.

For **FREE** information write:  
**PHILCO**  
TECHNOLOGICAL CENTER  
P.O. Box 4730, Dept. R-2, Philadelphia 34, Pa.

**HIGH SCHOOL**

You can still finish High School—at home, in your spare time. No interference with job or social life. Win more pay, better job, new respect. Take only the subjects you need. Personalized guidance. Diploma to graduates. I.C.S. will send you 3 valuable books **FREE** to help you get started: (1) "How to Succeed," (2) High School subjects, (3) sample lesson. Write: **INTERNATIONAL CORRESPONDENCE SCHOOLS**  
DEPT. 39087K, SCRANTON 15, PA.

**ENGINEERING DEGREES**  
E.E.  
Option Electronics, Mechanical,  
Also in Liberal Arts  
earned by  
**HOME STUDY**  
Resident Classes Also Available If Desired  
Specify course preferred  
**PACIFIC INTERNATIONAL COLLEGE OF ARTS & SCIENCES**  
Primarily a correspondence school  
Chartered 1935

**PACIFIC INTERNATIONAL**  
C. A. S.

5719-M Santa Monica Blvd. Hollywood 38, Calif.

**ETI** Engineering Technician  
A.S. Degree—2 Years  
Electronics Engineer  
B.S. Degree—4 Years

Write for Folder  
**ELECTRONIC TECHNICAL INSTITUTE**  
970 West Manchester Ave., Inglewood, Calif.  
SAN DIEGO—COSTA MESA


**GET INTO**  
**ELECTRONICS**

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 28 mos. B.S. in electronic engineering obtainable. ECPD accredited, G.I. approved. Graduates in all branches of electronics with major companies. Start February, September. Dorms, campus. High School graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. C Valparaiso, Indiana



**FREE CAREER BOOKLET**

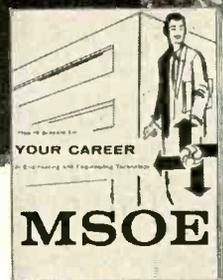

to guide you to a successful future in  
**ELECTRONICS**  
**RADIO-TV**  
**COMPUTERS**  
**ELECTRICAL**  
**ENGINEERING**

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • RADAR • RESEARCH**  
**ELECTRICAL POWER • ROCKETRY**  
**AUTOMATION • AVIONICS**  
**SALES • DEVELOPMENT**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

**MILWAUKEE SCHOOL OF ENGINEERING**

**MAIL COUPON TODAY!**

**MILWAUKEE SCHOOL OF ENGINEERING**  
Dept. RE-162, 1025 N. Milwaukee St. MS-113  
Milwaukee, Wisconsin

Please send **FREE** "Your Career" booklet  
I'm interested in  Electronics  Radio-TV  
 Computers  Electrical Engineering  
 Mechanical Engineering  
(PLEASE PRINT)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

I'm eligible for veterans education benefits.

Discharge date \_\_\_\_\_

**R-E****Classified****ADS**

**Rates—50¢ per word (including name, address and initials. Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for March issue must reach us before Dec. 11, 1961. RADIO-ELECTRONICS, 154 West 14 St., New York 11, N. Y.**

**FOR SALE****Electronics**

**HOFFMAN** silicon solar cells, type 120C. Minimum output current 23 ma, minimum power 9 mw at 10,000 foot-candle sunlight with 400-mv load. Size .788x.394x.025". Temperature range -65° to 175°C. Cells unmounted without leads. Reg net \$2.40, ONLY 3 for \$1.25; 6 for \$2.25. Unused, postpaid. Satisfaction guaranteed! Rush check or MO. No COD. **CLARK ELECTRONICS**, 190 W. Santa Clara, San Jose 13, Calif.

**PRINTED CIRCUITS**. Free catalog lists hundreds of circuits. **CLOUD "9" ENGINEERING**, Brookdale, Calif.

**SHORT CIRCUITS** pinpointed within 5 feet or your \$4.50 back. Own a patented pocket-size Dynamic Short Locator. **DYNAMICO**, 11370 SW 60th Terr., Miami 43, Fla.

**REWIND** electric motors yourself. Send \$1.00 today; receive rewinding data for 300 single-phase motors, plus wholesale parts catalog, plus big bargain circular, by return mail. **MODERN**, Box 8715, Kansas City 14, Mo.

**TRANSISTOR IGNITION**—save gas, tune-ups. Points, plugs last 50,000-100,000 miles. Improved cold starting, high-speed performance. Complete negative-ground 12v system, \$29.50. Special coil, \$9.50. **PALMER ELECTRONICS**, Carlisle, Mass.

**RADIO TOWER**, 205' in 20' sections. All guy wires, Revere beacon, obstruction lights, model 1615 Revere, steel, painted CAB regulations. Like new. Manufactured by Modern Electronics Company. Original cost \$4,250.00. Our price \$1,500.00 FOB Vicksburg, Miss. **W. J. RUNYON & SON INC.**, 3312 Oak St., Vicksburg, Miss.

**SCHEMATICS**, repair information. Television \$1.50. Radio 75¢. Send make and model. **SCHEMATICS UNLIMITED**, Box 65, Flushing 64, N.Y.

**SCHEMATIC DIAGRAMS**, exact replacement parts orders: Japanese transistor or tube radios, recorders, transceivers, electronics equipment. Give model and manufacturer, \$1.00. **TECHSERVICES**, CPO 849, Tokyo, Japan.

**TV, RADIO** tubes and parts wholesale. Brand New. List free. **R T M CO.**, 508 Cliford, Flint 3, Mich.

**4MF/600V** oils, 19¢. Many receiving tubes, 19¢. Motor brushes, 3¢. **MAX ABRAMSON**, 3238 Eliot Blvd., Oceanside, N.Y.

**DOOR OPERATOR**, \$59.95. Automatic chain drive. Not a kit—highest quality. Free Literature. **DEMSCO**, Sebring 25, Ohio.

**SEND FOR FLYERS** listing transmitters, receivers, teletype converters, tubes, components. **SPERA ELECTRONICS**, 37-10 33 St., Long Island City 1, N.Y.

**SUPERSENSITIVE** directional microphone picks up a whisper at great distances. Used by investigators to record faint, distant sounds without being detected. Easily constructed for about \$7. Step-by-step plans, \$1.95. **DEE CO.**, Box 7263-A, Houston 8, Tex.

**TELEVISION TUBES** 60% off. Brand-new, no factory rejects. First line. Prepaid. **PARKWAY ELECTRONICS**, Vestal, N.Y.

**APPLIANCE LAMP**, range, vacuum parts wholesale. Catalog 25¢. **SECO**, 112 So. 20th St., Birmingham 3, Ala.

**PROFESSIONAL ELECTRONIC PROJECTS**—Organs, Timers, Computers, etc.—\$1 each. List free. **PARKS**, Box 1665, Lake City, Seattle 55, Wash.

**BEFORE YOU BUY** Receiving Tubes or Hi-Fi Components send now for your giant FREE Zalytron current catalog—featuring nationally known Zalytron First Quality TV-Radio Tubes, Hi-Fi Stereo Systems, Kits, Parts, etc. All priced to Save You Plenty—Why Pay More? **ZALYTRON TUBE CORP.**, 220 W. 42nd St., N.Y.C.

**CONVERT ANY TELEVISION** to sensitive big-screen oscilloscope. Only minor changes necessary. Plans \$1.95. **RELCO**, Box 10563-D, Houston 8, Tex.

**SAVE DOLLARS** on Radio, TV Tubes. Brand new. Parts at less than manufacturer's cost. 100% Guaranteed. No rebrands or pulls! **UNITED RADIO**, Box 1000-R, Newark, N.J.

**PRECISION RESISTORS**, carbon-deposit. Guaranteed 1% accuracy. Millions in stock. ½-watt, 8¢. 1-watt, 12¢. 2-watt, 15¢. Leading manufacturers. **ROCK DISTRIBUTING CO.**, 902 Corwin Rd., Rochester 10, N.Y.

**RADIOS**, taperecorders, transceivers, tele-amplifiers. Everything Japanese. **UNITA**, 545 Fifth Ave., New York 17, N.Y.

**ELECTRONIC SURPLUS CATALOG**, 5,000 items. Send 10¢. **BILL SLEP CO.**, Drawer 178R, Ellenton, Fla.

**DIAGRAMS FOR REPAIRING RADIOS**, \$1; television \$2. Give make and model. **DIAGRAM SERVICE**, Box 672 RE, Hartford 1, Conn.

**TV DIAGRAMS**, \$1.00. State make and model. **DENVER DIAGRAM SERVICE**, 527 E. Exposition, Denver, Colo.

**Audio—Hi-fi**

**ORGAN BUILDERS**—Hammond generator, 92-note, guaranteed. **DAVE BRENER**, 224 Century, Playa Del Rey, Calif.

**NEW GRILLE CLOTH**, 10¢ sq. ft. Send self-addressed envelope for free samples. **NAEFTY PLASTICS INC.**, 4909 Midmoor Rd., Madison 4, Wis.

**COMPONENTS**, Recorders, Tapes. FREE Wholesale Catalogue. **CARSTON**, 125-T East 88th St., New York 28, N.Y.

**DON'T BUY HI-FI COMPONENTS**, Kits, Tape, Tape Recorders until you get our low, low return mail quotes. "We Guarantee Not To Be Undersold." Wholesale Catalog Free. Easy Time Payments Plan, 10% down—up to 24 months to pay. **HIFIDELITY CENTER**, 220 RC E 23 St., New York 10, N.Y.

**TAPE** recorders, Hi-Fi components, Sleep-learning equipment, Tapes, Unusual values. Free catalog. **DRESSNER**, 1523R Jericho Turnpike, New Hyde Park, N.Y.

**POPULAR** Piano and Organ lessons on tape, \$6.00, either tape. Write for particulars. **BOB MILLER TAPES**, Box 132-R, Cranford, N.J.

**HI-FI AMPLIFIERS**, tuners, speakers, Walkie Talkies, radios, telescopes, microscopes, cameras. LOW Prices. Free Catalog. **GM PHOTOELECTRONICS**, 623 Gay, Knoxville, Tenn.

**PROMPT DELIVERY**. Lower prices. Amplifiers, Tape Recorders, Tuners, etc. No catalogs. Individual Quotes. Compare. **L. M. BROWN SALES CORP.** Dept. R, 239 E. 24th St., New York 10, N.Y.

**SAVE 30%**. Stereophonic music on tape. Request tape, recorder Catalog R-1. **SAXITONE TAPE SALES**, 1776 Columbia Rd, Washington 9, D.C.

**RENT STEREO TAPES**—over 2,000 different—all major labels—free catalog. **STEREO-PARTI**, 811-RE, Centinela Ave., Inglewood 3, Calif.

**SALE ITEMS**. Component quotes. Bulk tapes. **BAYLA CO.**, Box 131-RE, Wantagh, N.Y.

**General**

**"EXPERIMENTERS' ELECTRONICS"** magazine. Tubes, transistors, crystal sets—25¢; 12 issues \$2.50. **LABORATORIES**, 1131-B Valota, Redwood City, Calif.

**100 FOREIGN STAMPS** only 10¢ with approvals. **RORRY STAMPS**, 7521 Mason, Dept. 112, Canoga Park, Calif.

**BUY/RENT COMEDY, PARTY RECORDS**. Sampler and catalogs, \$1.00. **DRC**, Dept. RE-1, 11024 Magnolia Blvd., No. Hollywood, Calif.

**100 DIFFERENT** United States commemorative stamps. ½¢ to 10¢ face, used \$1.00; mint, \$4.95. **IRWIN**, Box 12D, Brooklyn 29, N.Y.

**BUSINESS AIDS**

**500 PRINTED GUMMED** Name and Address Labels, \$1.00. No COD's. Print clearly. **ADDISON MAIL ORDER**, RE-5, 1840 Addison, Chicago 13.

**NIPPO** Check Protectors, \$9.95. Warranted! Free Trial Offer! **ALBRIGHT**, Tipton 1, Ind.

100 8½x11 LETTERHEADS, \$2.25 post-paid. McDONALD, 545 No. Oakland, Pasadena 4, Calif.

FREE SAMPLES, Business Cards. Low prices. CRAFTS, Box 7146, Nashville, Tenn.

## WANTED

WANTED: BC-348's, laboratory equipment, manuals, klystrons. Cash, swap. **ENGINEERING ASSOCIATES**, 434 Patterson Rd., Dayton 19, Ohio.

WANTED—MISCELLANEOUS Quicksilver Platinum, Gold, Silver. Ores analyzed. **MERCURY TERMINAL**, Norwood, Mass.

WANTED COINS. Buying list, \$1.00. **BARNEY NORVILLE**, Bells, Tenn.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean radio and TV receiving, transmitting, special purpose, Magnetrons, Klystrons, broadcast types, etc. Want military & commercial lab/test and communications equipment such as G.R., H.P., AN/UPM prefix. Also want commercial receivers and transmitters. For a fair deal write **BARRY**, 512 Broadway, New York 12, N. Y. WALKER 5-7000.

## EDUCATION/INSTRUCTION

GIANT ARMS. Dr. Young's D.C. Revolutionary discovery. \$2.00 Satisfaction or refund. **GAUCHO**, Box 9309-X5, Chicago 90.

SLEEP LEARNING. Startling method 92% effective. Brochure free. **ASR FOUNDATION**, Box 21RE, Henry Clay Station, Lexington, Ky.

LEARN WHILE ASLEEP, Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. **SLEEP-LEARNING ASSOCIATION**, Box 24-RD, Olympia, Wash.

NEW CONCEPT OF LEARNING SELF-HYPNOSIS! Now on tape or record! Free Literature. **McKINLEY-SMITH CO.**, Dept. T5, Box 3038, San Bernardino, Calif.

## SERVICES

PATENT drawings of your inventions made by our experts from your sketches. **PATENT SERVICE ASSOCIATES**, Haverhill, N.H.

TV TUNERS—rebuilt or exchanged, \$9.95 complete—all types—fast, guaranteed service. Send tuner with all parts to: **L. A. TUNER EXCHANGE**, 4611 W. Jefferson Blvd., Los Angeles 16, Calif.

TRANSISTORIZED products dealers catalog, \$1. **INTERMARKET**, CPO 1717, Tokyo, Japan.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. New and used instruments bought, sold, exchanged. **HAZELTON INSTRUMENT CO.**, 128 Liberty St., New York, N.Y.

HOW and where to obtain capital. Write **RELIABLE SERVICE**, Box 214-RE, Rome City, Ind.

## MISCELLANEOUS

BARBELLS, exercise equipment. Courses. Catalog 10¢. **GOOD BARBELL CO.**, Siloam Springs, Ark.

WHOLESALE OPPORTUNITY. Buy nationally advertised merchandise below wholesale. Free Catalog. **JOSEPH ROBERTS**, 1813 S. Federal, Los Angeles 25, Calif.

INDEPENDENT THINKERS—investigate Humanism! Write **AMERICAN HUMANIST ASSOCIATION**, Dept. RE, Yellow Springs, Ohio.

FREE Freethought book list and sample rationalist magazine "The Liberal." **FRIENDSHIP LIBERAL LEAGUE INC.**, Thomas Paine Center, 5233 N. 5th St., Box R-E, Philadelphia 20, Pa.

INVENTIONS WANTED for immediate promotion! Patented, unpatented. Out-right cash; royalties; **CASCO**, Dept. 3, Mills Bldg., Washington 6, D.C.

PRINTING PRESSES, type, supplies. List 4¢. **TURNBAUGH SERVICE**, Mechanicsburg, Pa.

## ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Allied Radio	70-73
Amphenol-Borg Electronics Corp.	10
Audio Unlimited Inc.	115
Audion	111
B&K Manufacturing Co.	85
British Industries Corp.—Multicore	98
Brooks Radio & TV Corp.	110
Burstein-Applebee Co.	113
Cabinart Acoustical Engineering Corp.	75
Capitol Radio Engineering Institute	102-105
Carston	106
Castle TV Tuner Service	113
Central Technical Institute	53-54
Centralab Div. of Globe-Union	95
Clarostat Manufacturing Co. Inc.	22
CLASSIFIED ADS	118-119
Cleveland Institute of Electronics	11
Colordaptor	106, 115
Concord Electronics	116
Coyne Electrical School	23, 107
DeVry Technical Institute	7
Dorsett Electronics Inc.	106
Dressner	111
Editors & Engineers	116
Electro-Voice Inc.	114
Electronic Chemical Corp.	116
Electronic Instrument Co. (EICO)	24
Electronic Market	109
Electronic Measurements Co. (EMC)	87
Electronic Publishing Co. Inc.	112
Fairchild Recording Equipment Corp.	109
Fisher Radio Corp.	68

Gernsback Library Inc.	92, 112
Grantham School of Electronics	17
Greylock Electronics	83
Harman-Kardon Inc.	93
Heald's Engineering College	115
Heath Co.	58-59
Heller Roberts Instrument Co.	98
Holt, Rinehart & Winston Inc.	12-13
Indiana Technical College	111
Key Electronics Co.	112
Lafayette Radio	77
Mark Mobile Inc.	98
Metropolitan Electronics	108
National Radio Institutes	19-20, 116
National Technical Schools	5
Newport Manufacturing Co.	86
Olson Electronics	82
Perma-Power Co.	111
Picture Tube Outlet	106
Progressive Edu-Kits Inc.	101
Quam-Nichols Co.	108
Quietrole Co.	114
RCA Electron Tube Div.	Back Cover
RCA Institutes	88-91
Rad-Tel Tube Co.	120
Radio-Electronic Master	114
Radio-TV Training School	15
Rohn Manufacturing Co.	83

Sams (Howard W.) & Co. Inc.	9, 96
Saxitone Tape Sales	115
Scientific Development Corp., Minivac Sales Div.	109
Scott (H. H.) Inc.	3
Seco Electronics Co.	106
Sencore	81
Smith (Wardell)	98
Sonar Radio Corp.	115
Sprague	14
Superscope Inc.	94
Sylvania Electric Products Inc.	Inside Front Cover
TAB	100
Tarzian (Sarkes) Inc., Magnetic Tape Div.	8
Texas Crystals	116
Transvision	21, 99
Tri-State College	97
Tung-Sol Electric Inc.	69
Turner Co.	97
University Loudspeakers Inc.	Inside Back Cover
Utah Electronics Corp.	18
Winegard Co.	64-65
Xcelite Inc.	16

## SCHOOL DIRECTORY PAGE 117

Niles Bryant School
Electronic Technical Institute
Indiana Technical College
International Correspondence School
Milwaukee School of Engineering
Northrop Institute of Technology
Pacific International College of Arts & Sciences
Phila. Wireless Technical Institute
Philco Technological Center
Tri-State College
Valparaiso Technical Institute
Printed in USA


# COSTS YOU LESS...

## RAD-TEL'S Quality Brand New Tubes

### up to 75% OFF

### ONE-DAY SERVICE

### 1 YEAR GUARANTEE

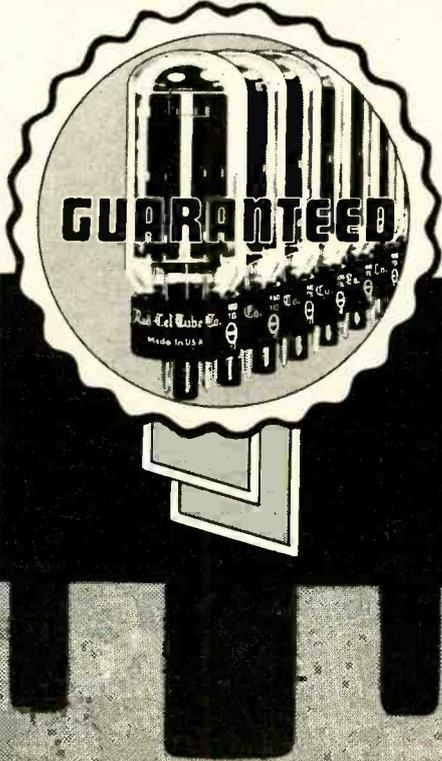

SEND FOR FREE TROUBLE SHOOTING GUIDE AND NEW TUBE & PARTS CATALOG

TERMS: 25% deposit must accompany all orders, balance C.O.D. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. Prices subject to change. No C.O.D.'s outside continental U.S.A.



# RAD-TEL TUBE CO.

DEPT RE162 55 CHAMBERS STREET, NEWARK 5, NEW JERSEY

EACH TUBE INDIVIDUALLY & ATTRACTIVELY BOXED & BRANDED RAD-TEL

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
	0Z4	.79		6AT8	.79		6GN8*	.94		12CU5	.58
	1AX2	.62		6AU4	.82		6H6	.58		12CU6	1.06
	1B3	.79		6AU6	.52		6J5GT	.51		12CX6	.54
	1DN5	.55		6AU7	.61		6J6	.67		12D4*	.69
	1G3*	.79		6AU8	.87		6K6	.63		12DB5	.69
	1J3*	.79		6AV6	.41		6L6	1.06		12DE8	.75
	1K3*	.79		6AW8	.90		6N7	.98		12DL8	.85
	1R5	.62		6AX4	.66		6S4	.51		12DQ6	1.04
	1S4	.59		6AX5	.74		6SA7GT	.76		12DS7	.79
	1S5	.51		6AX7	.64		6SG7GT	.41		12DT5*	.76
	1T4	.58		6AX8*	.92		6SH7GT	.49		12DT7*	.79
	1U4	.57		6BA6	.50		6SJ7	.88		12DT8*	.79
	1U5	.50		6BA8	.88		6SK7GT	.74		12DU7	1.01
	1X2B	.82		6BC5	.61		6SL7GT	.80		12DW8*	.89
	2AF4	.96		6BC7	.94		6SN7GT	.65		12DZ6	.56
	2BN4	.64		6BC8	.97		6SQ7	.73		12ED5	.69
	2EN5*	.45		6BD5	1.25		6T4	.99		12EG6	.54
	3AL5	.42		6BE6	.55		6T8	.85		12EK6	.56
	3AU6	.51		6BF5	.90		6U8	.83		12EL6	.50
	3AV6	.41		6BF6	.44		6VG6T	.54		12EM6	.79
	3BA6	.51		6BG6	1.66		6W4	.60		12EN6	.78
	3BC5	.54		6BH6	.65		6W6	.71		12EZ6	.53
	3BE6	.52		6BH8	.87		6X4	.39		12F8	.66
	3BN6	.76		6BJ6	.62		6X5GT	.53		12FA6	.79
	3BU8	.78		6BJ7	.79		6X8	.80		12FM6	.43
	3BY6	.55		6BK7	.85		7A8	.68		12FR8	.91
	3BZ6	.55		6BL7	1.00		7AU7	.61		12FX8	.85
	3CB6	.54		6BN4	.57		7B6	.69		12GC6	1.06
	3CS6	.52		6BN6	.74		7EY8*	.73		12J8	.84
	3DG4*	.85		6BQ6	1.05		7F8	.90		12K5	.65
	3DK6*	.60		6BQ7	1.00		7N7	.90		12L6	.58
	3DT6	.50		6BS8	.90		7S7	1.01		12SA7	.92
	3Q4	.63		6BU8	.70		7Y4	.69		12SF7	.69
	3Q5	.80		6BX7	1.02		8AU8	.83		12SH7	.49
	3S4	.61		6BY5	1.15		8AW8	.93		12SJ7	.67
	3V4	.58		6BY6	.54		8BQ5	.60		12SK7	.74
	4BQ7	1.01		6BY8	.66		8CG7	.62		12SL7	.80
	4BZ7	.96		6BZ6	.55		8CM7	.68		12SN7	.67
	4BZ8	1.10		6BZ7	1.01		8CN7	.97		12SQ7	.78
	4CS6	.61		6BZ8	1.09		8CS7	.74		12U7	.62
	4DT6	.55		6C4	.43		8CX8	.93		12V6	.53
	5AM8	.79		6CB6	.55		8EB8	.94		12W6	.69
	5AN8	.86		6CD6	1.42		8SN7	.66		12X4	.38
	5AQ5	.52		6CE5*	.57		9CL8	.79		17AX4	.67
	5AS8*	.86		6CF6	.64		11CY7	.75		17BQ6	1.09
	5AT8	.80		6CG7	.61		12A4	.60		17DQ6	1.06
	5AV8	1.01		6CG8	.77		12AB5	.55		17W6	.70
	5BC8	.79		6CK4*	.70		12AC6	.49		18FW6*	.49
	5BE8	.83		6CL8	.79		12AD6	.57		18FX6*	.53
	5BK7	.82		6CM6	.64		12AE7	.43		18FY6*	.50
	5BQ7	.97		6CM7	.66		12AE7	.94		19AU4	.83
	5BR8	.79		6CM8*	.90		12AF3	.73		19BG6	1.39
	5BT8*	.83		6CN7	.65		12AF6	.49		19C8	1.14
	5CG8	.76		6CQ8	.84		12AJ6	.46		19T8	.80
	5CL8	.76		6CR6	.51		12AL5	.45		21EX6	1.49
	5CM8*	.90		6CS6	.57		12AL8	.95		25AV5	.83
	5CQ8	.84		6CS7	.69		12AQ5	.60		25AX4	.70
	5CZ5*	.72		6CU5	.58		12AT6	.43		25BK5	.91
	5EA8	.80		6CU6	1.08		12AT7	.76		25BQ6	1.11
	5EU8	.80		6CY5*	.70		12AU6	.51		25C5	.53
	5J6	.68		6CY7	.71		12AU7	.60		25CA5	.59
	5T8	.81		6DA4*	.68		12AV6	.41		25CD6	1.44
	5U4	.60		6DB5	.69		12AV7	.75		25CU6	1.11
	5U8	.81		6DB6	.51		12AX4	.67		25DN6	1.42
	5V3	.90		6DE6	.58		12AX7	.63		25EH5	.55
	5V6	.56		6DG6	.59		12AY7	1.44		25L6	.57
	5X8	.78		6DK6	.59		12AZ7	.86		25W4	.68
	5Y3	.46		6DN6	1.55		12B4	.63		32ET5	.55
	6AB4	.46		6DQ6	1.10		12BA7	.84		32L7	.90
	6AC7	.96		6DT6	.53		12BD6	.50		35B5	.60
	6AF3	.73		6DT8*	.79		12BE6	.53		35C5	.51
	6AF4	.97		6EA8	.79		12BF6	.44		35L6	.57
	6AG5	.68		6EB5*	.72		12BH7	.77		35W4	.42
	6AH4	.81		6EB8	.94		12BK5	1.00		35Z5	.60
	6AH6	.99		6EM5*	.76		12BL6	.56		36AM3*	.36
	6AK5	.95		6EM7	.82		12BQ6	1.06		50B5	.60
	6AL5	.47		6EU8	.79		12BR7	.74		50C5	.53
	6AM8	.78		6EW6	.57		12BV7	.78		50EH5	.55
	6AQ5	.53		6EY6*	.75		12BY7	.77		50L6	.61
	6AR5	.55		6F5GT	.39		12BZ7	.75		70L7	.97
	6AS5	.60		6FE8	.75		12C5	.56		70Z5	.69
	6AS6	.80		6GH8	.80		12CN5	.56		807	.70
	6AT6	.43		6GK6*	.79		12CR6	.54		117Z3	.61

Popular New Tube Types Offered by Rad-Tel\*  
NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY



# play ball!

Heard better at Comiskey Park with University 4A4 P. A. loudspeakers\*

And why was University chosen to be the voice of the Chicago White Sox explosive scoreboard? For the same reasons that have made University Loudspeakers the choice of more P. A. users than any other brand in the world: proven dependability, greater value, superior performance.

University 4A4 Superpower Projectors are excellent examples of University quality. During World War II, the military needed an extremely compact, lightweight, high power unit capable of penetrating the terrific noise levels found under combat conditions. The first 4A4 fulfilled exacting military specifications—to perfection. As a result of University's ever-expanding R & D program, today's 100-watt Model 4A4—and its big brother, the B-12P—are actually far superior. You will find them at leading sports stadiums, race tracks, airports . . . in church towers for the transmission of chimes and organ music . . . and in many civil defense installations. They are simple to install, fool-proof in operation, and immune to weather conditions of every kind. Perhaps they could be the answer to your P. A. needs?

But whether you need superpower projectors, top quality drivers, trumpets, paging or weather-proof high fidelity speakers . . . portable super-hailers, explosion-proof or underwater speakers—check University *first*. Most P. A. users do.

Write today for complete 4A4 specifications and P. A. catalog.  
Desk S-11, University Loudspeakers, Inc., White Plains, N. Y.

\*Integrated in a Dukane Sound System, installed by Rich Sound Engineers, Chicago, Illinois.



A Division of Ling-Temco-Vought, Inc.



## “BUSINESS END” of a NOVAR tube

You're looking at the base of one of RCA's remarkable new novar tubes...the first in a new family of tubes that will mean better business for you through reduced call backs.

This new base—with 9 widely-spaced, heavy-gauge pins—characterizes novar, RCA's line of large all-glass integral base tubes designed to do the work of conventional tubes with molded bases. Because novars *outperform* these con-



ventional types, they are being selected for use in more and more radio and TV receivers as well as hi-fi equipment. From present indications, novar should become the standard of the industry.

Look for novar, RCA's latest contribution to electron tube design. Your Authorized RCA Electron Tube Distributor now has RCA-7868 novar and will soon have many other types to support your servicing business.

RCA ELECTRON TUBE DIVISION, HARRISON, N.J.



The Most Trusted Name in Electronics