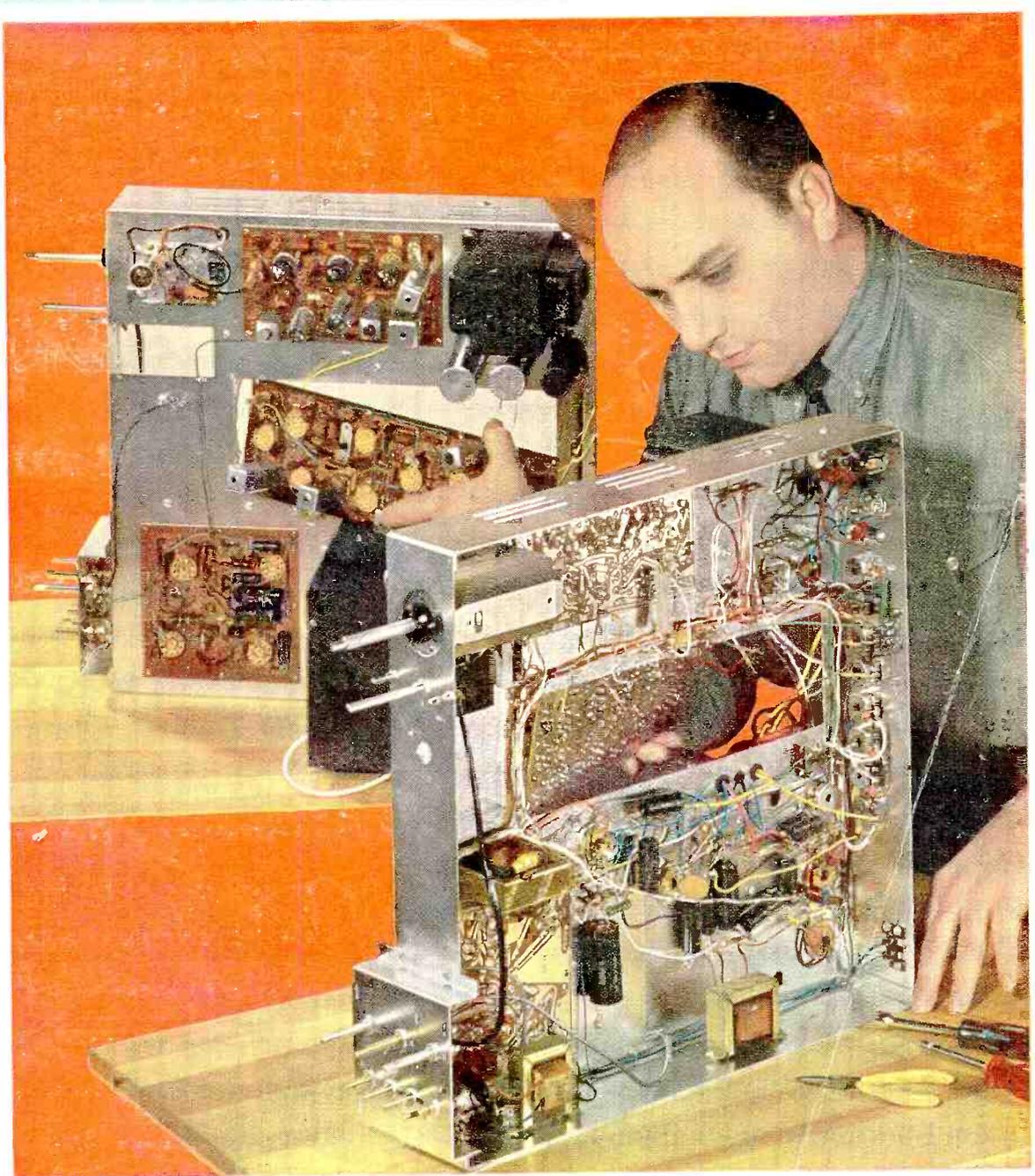


Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

GERNSBACK PUBLICATION

BUILD yourself a Little Dictator
REPAIR those Antenna Rotators
DESIGN your Speaker Enclosure



Good results from Kit-built Color TV
See page 40

200,000 OHMS PER VOLT


NEW AND THE FIRST

\$99.50
SUGGESTED
U.S.A. USE ONLY



Model 630-NS
VOLT-OHM-MICROAMMETER

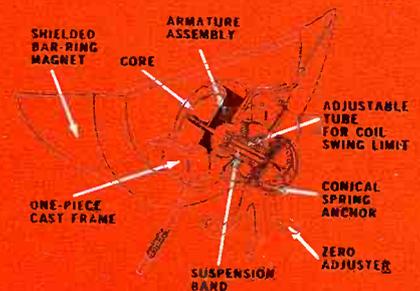TRIPLET SUSPENSION MOVEMENT
no pivots . . . no jewels
no hair springs . . . thus NO FRICTION.



FACTS MAKE FEATURES

- 1** 200,000 OHMS PER VOLT D.C. for greater accuracy on high resistance circuits. 20,000 OHMS PER VOLT A.C.
- 2** 5 μ A SUSPENSION METER MOVEMENT. No pivots, bearings, hair-springs, or rolling friction. Extremely RUGGED. Greater sensitivity and repeatability.
- 3** 62 Ranges, usable with frequencies through 100 Kc. Temperature compensated. 1 1/2% D.C. ACCURACY, 3% A.C.

Low voltage ranges and high input impedance make the 630-NS especially useful in transistor circuit measurement and testing. Input impedance, at 55 volts D.C. and above, is *higher than most vacuum tube voltmeters.*


The unit is designed to withstand overloads and offers greater reading accuracy. Reads from 0.1 μ A on 5 μ A range. Special resistors are rigidly mounted and directly connected to the switch to form a simplified unit. Carrying cases with stands are priced from \$9.90.

TRIPLET ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO

62 RANGES

D.C. VOLTS	0-0.6-3-12-60-300-1200 at 100,000 Ohms/Volt. 0-0.3-1.5-6-30-150-600 at 200,000 Ohms/Volt. 0-0.150 at 60 μ A
A.C. VOLTS	0-3-12-60-300-1200 at 10,000 Ohms/Volt. 0-1.5-6-30-150-600 at 20,000 Ohms/Volt.
DB	-20 to 77 in 10 ranges.
D.C. MICRO-AMPERES	0-5 at 300 MV. 0-60-600 at 150 MV. 0-120 at 300 MV.
D.C. MILLI-AMPERES	0-6-60-600 at 150 MV. 0-1.2-12-120-1200 at 300 MV.
D.C. AMPERES	0-6 at 150 MV. 0-12 at 300 MV.
OHMS	0-1K-10K-100K (4.4-44-440 at center scale)
MEGOHMS	0-1-10-100 (4400-44,000-440,000 Ohms center scale)

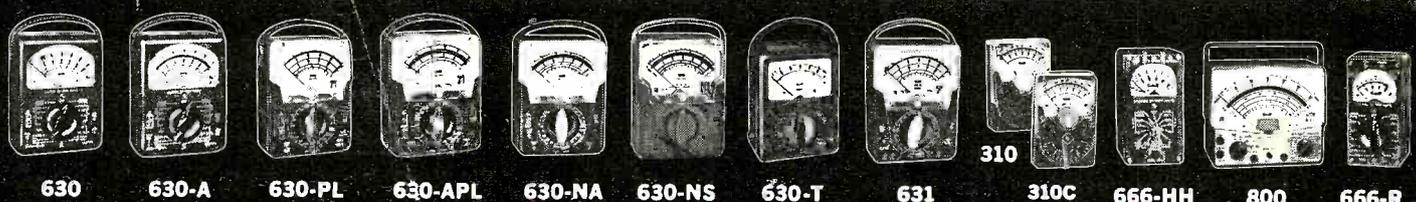OUTPUT: Condenser in series with A.C. Volt ranges.



THE WORLD'S MOST COMPLETE LINE OF V-O-M'S. AVAILABLE FROM YOUR TRIPLET DISTRIBUTOR'S STOCK

SEND NOW!

RCA INSTITUTES, INC. DEPT. RE-84

350 West 4th St., New York, N. Y. 10014

Rush me by return mail your FREE illustrated 64-page book on electronics careers through Home Training! No obligation to me! No salesman will call!

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Classroom Training available in New York City. Coeducational classes start four times a year. Check here for FREE Resident School Catalog

CANADIANS — Take advantage of these same RCA Institutes courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.

RCA will show you how to start a profitable career in Electronics at home!

Faster, Easier Way to Begin

If you are considering a future in electronics, now is the time to start! A great new teaching aid—"AUTOTEXT", developed by RCA and introduced by RCA Institutes, will help you master the fundamentals of electronics almost automatically. "AUTOTEXT" is a system of programmed instruction, a method of learning, proved with thousands of students. Even people who have had trouble with conventional home training methods in the past are finding it easier and more fun to begin their training this new way.

Complete Selection of Courses

RCA Institutes offers you a really wide selection of Home Training Courses for every phase of electronics. You can actually pick the field of your choice from a great

variety of courses such as:

- Electronics Fundamentals • TV Servicing • Color TV • Communications • Computer Programming • Drafting • Automation • Transistors • Industrial Electronics.

Liberal Tuition Plan

RCA Institutes Tuition Plan affords you the most economical possible method of home study training. You pay for lessons only as you order them. No monthly payments! No installments necessary! No long term contracts! If you should wish to interrupt your training for any reason, you can do so and not owe one cent!

Top Quality Equipment

All equipment furnished to you in RCA Institutes Home Training Courses is top quality. All kits and the equipment you build are yours to keep and use on the job! You never have to take apart one piece to build another!

Graduates Prove Results

RCA Institutes Graduates not only enjoy the prestige associated with the internationally famous name of RCA, but some have gone on to open their own businesses; have important positions in business, industry and government.

**START BUILDING A
BETTER FUTURE TODAY!
SEND COUPON RIGHT AWAY!**

RCA INSTITUTES, INC.

DEPT. RE-84

A Service of Radio Corporation of America
350 West 4th Street, New York, N. Y. 10014



**The Most Trusted
Name in Electronics**

Radio-Electronics

AUGUST 1964 VOL. XXXV NO. 8

Over 55 Years of Electronic Publishing

EDITORIAL

- 25 Medical ElectronicsHugo Gernsback

AUDIO-HIGH FIDELITY-STEREO

- 30 The Little DictatorWilliam D. Rexroad
A few parts make dictating machine out of tape recorder
- 32 Adapter For Mike ConnectorsArt Trauffer
- 44 Design Your Own Speaker EnclosureGeorge L. Augspurger
A how-to story for people without fancy test equipment
- 64 Equipment Report: Sonotone Mark IV Model 9TAHC and Bogen RT1000
Ceramic Cartridge and Transistor AM-FM-Stereo Receiver

ELECTRONICS

- 29 The 1960's—Superconductivity's Decade?Eric Leslie
Amazing magnet may foretell trend, as did transistor in 40's, maser in 50's
- 33 Watch Those Shifty ResistorsCarl L. Henry
Special "resistors" protect relays and transistors, measure light and heat
- 49 Tunnel Diode RegulatorI. Queen
- 50 Servicing SpeedlightsWayne Lemons
How commercial photoflash units work and how to fix them
- 55 Quick and Dirty Heat SinkRoy E. Pafenberg

GENERAL

- 16 Our Standard Abbreviations
- 37 What's New
Pictorial reports of new developments
- 39 Making Estimates Worries Many Servicemen
- 47 What's Your EQ?
- 62 Service Clinic
Flat-top Audio
- 88 Ten To The ManyJerry L. Ogdin
Help for people who figure

RADIO

- 28 Booster Triples Radio OutputHarry E. Stockman
- 38 Transistors and Voltage MeasurementsDavid R. Anderson
Troubleshooting with a voltmeter
- 53 Fixing Auto AntennasDavid Held
Anybody who's got a car with a radio in it can use this information

TELEVISION

- 26 How To Repair RotatorsHomer L. Davidson
First of two articles. Don't climb up on the roof till you have to

COVER STORY 40 Field Day For Kit Builders: Do-It-Yourself Color TV
Heath Color set comes with 124-page manual, degaussing coil and built-in dot-generator

- 48 More On Multiplex Video

TEST INSTRUMENTS

- 42 Pick-Off Box & Wattmeter For CBLyman E. Greenlee
Build one in a couple of hours to help you in CB service
- 56 Zener-Stabilized DC AmplifierAlex M. Schotz
Good preamp for dc scopes. Construction project
- 68 Equipment Report: Eico 430 and Texas Crystals TC-3
3-inch general-purpose scope and crystal alignment generator

THE DEPARTMENTS

12 Correspondence
90 New Books
79 New Literature
89 New Patents

76 New Products
71 New Semiconductors
6 News Briefs
84 Noteworthy Circuits

82 Technicians' News
73 Technotes
86 Try This One
90 50 Years Ago




Member,
Institute of High Fidelity
Radio-Electronics
is indexed in
Applied Science
& Technology Index
(Formerly
Industrial Arts Index).


HUGO GERNSBACK, editor-in-chief and publisher. M. HARVEY GERNSBACK, editor. Fred Shunaman, managing editor. Robert F. Scott, W2PWG, technical editor. Peter E. Sutheim, associate editor. Jack Darr, service editor. I. Queen, editorial associate. John J. Lamson, eastern sales manager. Wm. Lyon McLaughlin, technical illustration director.

GERNSBACK PUBLICATIONS, INC., 154 W. 14 St., N.Y. 10011. AL 5-7755. Board Chairman Hugo Gernsback, President M. Harvey Gernsback, Secy. G. Aliquo, Treas. Charles A. Raible

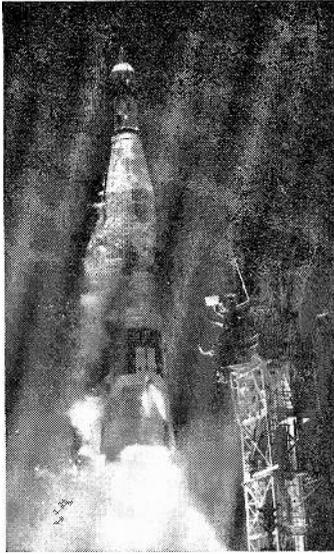A NEW WORLD OF OPPORTUNITY AWAITS YOU WITH N.T.S. ALL-PHASE HOME TRAINING IN ELECTRONICS



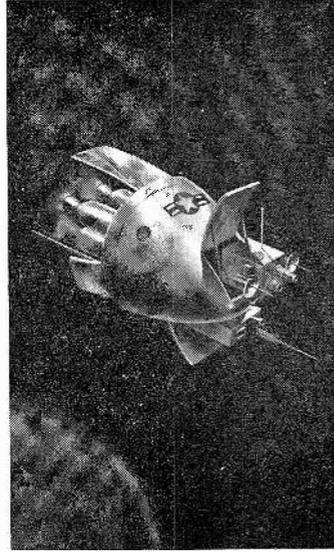
You can install and maintain electronic circuitry in missiles and rockets . . . specialize in micro-waves, radar and sonar.



You can succeed in TV-Radio Communications . . . prepare for F.C.C. License, service advanced satellites for industry and defense.



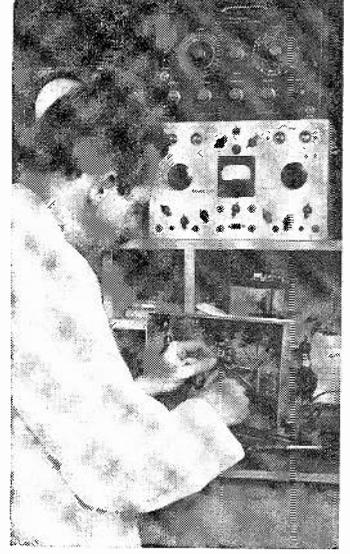You can service and repair the electronic "brains" of industry — computers, data processing, and other automation equipment.



You can become a highly-paid TV-Radio Technician, an electronics field engineer, or succeed in your own sales & service business.

The N.T.S. Master Course enables you to do more, earn more in ELECTRONICS • TELEVISION • RADIO Yet N.T.S. Training costs no more than other courses far less complete

There's a good reason why N.T.S. Master-Training opens a wide new world of opportunity for you in Electronics, Television, Radio.

Everything you learn, from start to finish, can be applied *directly* to all phases of the Electronics Industry.

As a result, the N.T.S.-Trained Technician can move ahead faster, in any direction — from TV-Servicing to Radio Communications to Space-Missile Electronics and Automation for industry and defense. You can go wherever pay is highest and opportunity unlimited.

Electronic circuitry, for example, is one of science's miracles that is basic to the entire field of Electronics. It is used in satellites, computers and space capsules as well as in today's television sets and high fidelity equipment. N.T.S. shows you how to service and repair electronic circuitry for all electronic applications.

You work on many practical job projects. You build a short-wave, long-wave superhet receiver, plus a large-screen television set from the ground up. N.T.S. training kits contain all the parts you need . . . at no extra cost. (See box at right.) You also receive a professional Multitester to use during training and on the job.

ONE LOW TUITION. You need training related to all phases of Electronics. Industry demands it. Only N.T.S. provides it . . . in ONE Master Course at ONE low tuition.

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your Electronics-TV-Radio training in our famous Resident School in Los Angeles — the oldest and largest school of its kind in the world — write for special Resident School catalog and information, or check coupon.



YOU ENROLL BY MAIL AND SAVE MONEY. No salesmen means *lower costs for us, lower tuition for you.*

START NOW. A whole new world of opportunity awaits the man with Electronic Home-Training from National Technical Schools — a recognized leader in technical training for 58 years.



19 BIG KITS
YOURS TO KEEP



**MAIL COUPON NOW FOR FREE
BOOK AND ACTUAL LESSON!**

NO OBLIGATION.
NO SALESMAN WILL CALL.

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

National Technical Schools, Dept. RG-84
4000 South Figueroa Street, Los Angeles, California 90037

Please Rush FREE Electronics-TV-Radio "Opportunity"
Book and Actual Lesson. No Salesman Will Call.

Name _____ Age _____


Address _____

City _____ Zone _____ State _____

Check if interested ONLY in Resident Training at L.A.

High school home study courses also offered. Check for free catalog.

NEWS BRIEFS

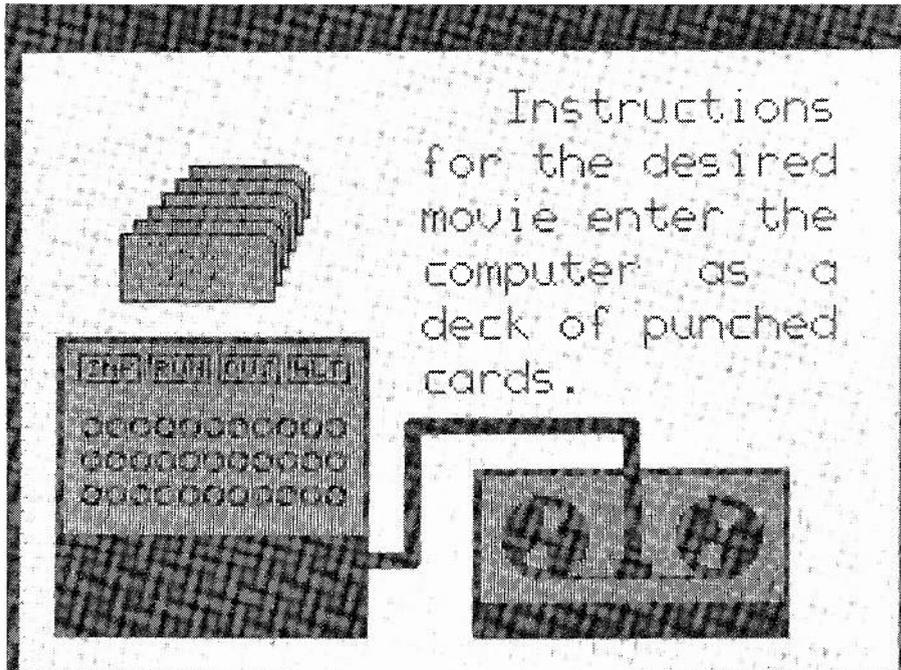

One frame of the animated film showing how cards are supplied to the computer, how the computer puts an output on the magnetic tape.

NOW—COMPUTER MAKES MOVIES

Simple animated films can now be made quickly and cheaply with a computer by a special programming language, according to a report from Bell Telephone Laboratories.

The "movie language" was developed by Kenneth C. Knowlton of the Laboratories. It includes instructions for drawing pictures consisting of straight lines, arcs, complicated curves, letters, simple geometric shapes and shaded areas.

To make movies by the computer, each frame is divided into 184 rows of 250 square dots, which may be black, white or various shades of gray in between. The special computer language (called BEFLIX, for "Bell Flicks") directs the computer to develop arrays and patterns, to enlarge, shift or copy from one area onto another, and perform other operations.

The instructions are fed to the computer, an IBM 7094, on IBM cards. It makes a tape which is fed to a Stromberg-Carlson 4020 microfilm recorder. This contains a cathode-ray tube similar to a television tube, and a film camera. Each of the lines is displayed on the tube as it would be on a TV tube. The intensity at any point depends on the instructions sent from the computer by

magnetic tape.

Delegates at the Joint Computer Conference held recently in Washington, D.C., saw a 17-minute movie in which the computer itself demonstrated the technique for producing animated movies.

The new technique, Dr. Knowlton says, can already be made at a cost that compares favorably with animation by traditional methods. Still experimental, all its possible applications cannot be foreseen, but it should be particularly valuable for educational films.

METAL BASED TRANSISTOR EXTENDS FREQUENCY RANGE

A new type of silicon transistor, described by Richard R. Garnache of Sprague Electric Co., is expected to increase the useful frequency range by a factor of 10. Mr. Garnache said the device has a theoretical upper frequency limit of 20,000 mc, but is not likely to exceed 10,000 mc in its present state of development.


The metal-base transistor consists of two layers of single-crystal silicon separated by a layer of metal no more than 100 angstroms thick. It is an invention of Donovan V. Geppert of Stanford Research Institute, and is licensed exclusively to Sprague Electric.

NEW VIDEO RECORDER OPERATES AT LOW SPEED

A new home video recorder has been announced by Stewart Hegeman, audio designer and engineer, and Robert Morrow, Baltimore designer and consultant. The new machine operates at 30 inches per second, as compared with the 120 inches per second of Fairchild and Telcan recorders previously announced in this magazine.

Hegeman states that the new *Par-Vision* recorder will use standard 7-inch tape reels with 1/4-inch wide audio tape. Recording is in two tracks, one for video and one for sound. The bandwidth is 2 megacycles.

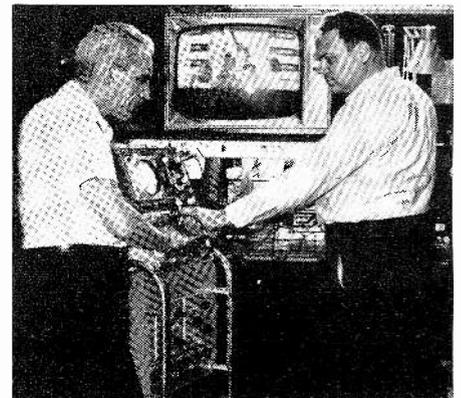Two engineers, after viewing a demonstration, felt the new machine had not advanced to the point of devel-



Stewart Hegeman (left) and Robert Morrow, making adjustments on the new recorder (in background, below the TV receiver).



opment of the Fairchild recorder. According to Hegeman, problems are about 85% licked and "We can see the end of the road without any major obstacles."

Another home video recording device is expected in the early fall, when the IIT (Illinois Institute of Technology) Research Institute plans to demonstrate a low-cost recorder.


ION-POWERED CRAFT COULD FLY AT 300,000 FEET

A model ion-powered craft which can lift itself off the ground and rise to a height of 20 feet in the laboratory has been demonstrated by Maj. Alexander P. de Seversky, aircraft designer and inventor. The invention was publicized

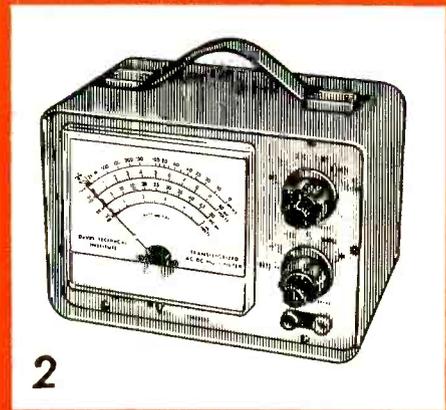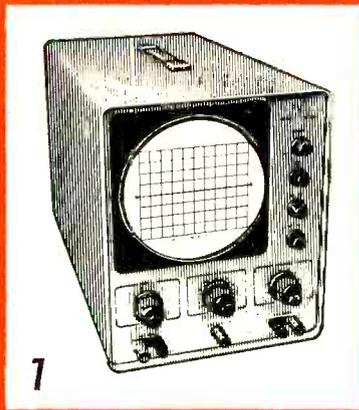5 in. Oscilloscope 1
 Transistorized Meter 2
 Modern Lessons 3



AT SEA
 ON LAND
 In the Air!

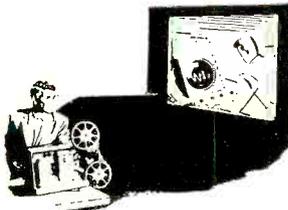

**TRAINING
 FILM**

You also get the loan of a motion picture projector and 16 reels of film to help you learn quickly, remember more.

Job Opportunities continue to increase for the Electronics Technician

Electronics is a multi-billion dollar industry, growing rapidly, calling for well-trained technicians, offering many good-paying opportunities. DeVry prepares you at home — or in its well-equipped training centers — for Radio, Television, Communications, Missiles, Computers, Radar, Control Systems, etc.

DeVry sends the type of materials you need for learning electronics at home. You build and keep (1) a modern 5-inch oscilloscope and (2) a portable transistorized meter. Use these on the job or to make money as you learn. You work 300 construction and test procedures with our exclusive "Electro-Lab". Modern lessons (No. 3 above) with their handy foldout diagrams help to speed your progress.

Let us put our more than 30 years of "know-how" behind you today to help you prepare for a lot of brighter, more prosperous tomorrows. Send coupon for 2 FREE booklets today.

Accredited Member of National Home Study Council

FREE!
 Send For 2
 Booklets Today!

**EMPLOYMENT
 SERVICE**

All DeVry graduates can receive the help of our highly effective employment service without additional cost.



DeVRY TECHNICAL INSTITUTE
 4141 Belmont Ave., Chicago, Ill. 60641 Dept. RE-8-U

Please give me your two free booklets, "Pocket Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Electronic Control |

Name _____ Age _____

Address _____ Apt. _____

City _____ Zone _____ State _____

Check here if you are under 16 years of age
 Canadian residents: Write DeVry Tech of Canada, Ltd.
 970 Lawrence Avenue West, Toronto 19, Ontario

2093


DeVry Technical Institute

Chicago • Toronto
 4141 Belmont Avenue
 Chicago, Illinois 60641

HERE'S ONE WAY TO
COOL A HOT AMPLIFIER



but
here is a
BETTER WAY

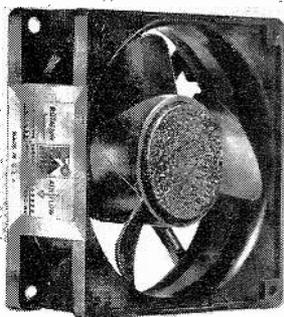

Only
\$14.85

the **ROTRON**


Whisper Fan
KIT

Beat the heat that wrecks the set by installing a Rotron Whisper Fan Kit. Breathing 60 cubic feet of cool air over, under and around every heat-generating component, the Whisper Fan improves performance by minimizing drift due to temperature change within the enclosure. Requires only 7 watts, just pennies a week to operate. Measuring only 4 1/8" square and 1 1/2" deep, it can be set in a corner or mounted on the rear panel in minutes. Comes complete with mounting hardware, plug and cord for electrical connections and installation instructions.



Write for details
or see your local dealer.

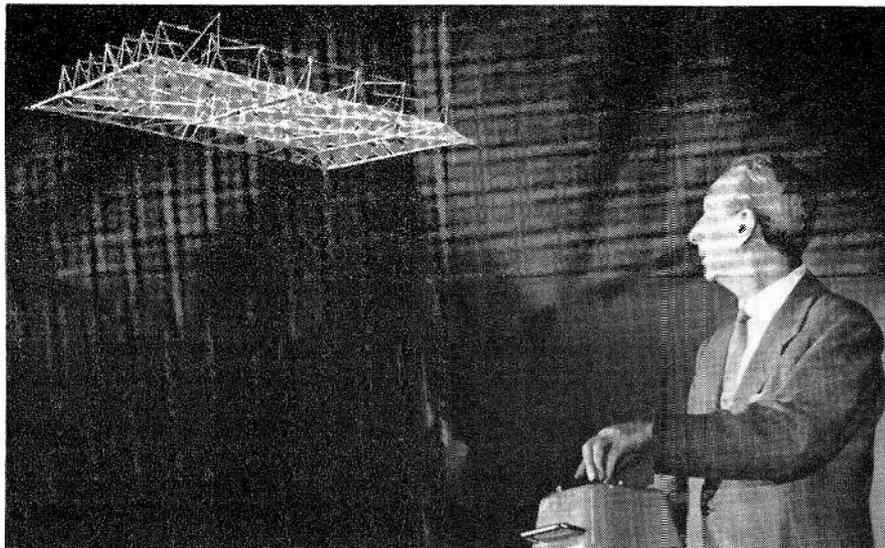ROTRON mfg. co., inc.
WOODSTOCK, NEW YORK
ORiole 9-2401



Major de Seversky maneuvering his Ionocraft in the laboratory.

immediately following issuance of the patent (No. 3,130,945).

The *Ionocraft*, as de Seversky calls it, keeps itself up by the "ionic wind" given off by a plane of emitting electrodes in the form of a mesh of hollow, lightweight rods or crossed wires. Below this plane is another similar one, charged to collect the ions emitted from the mesh above. Air molecules set in motion by the movement of the charged ions supply the lifting force. According to Major de Seversky, the test in an environmental chamber indicates that the lifting force is sufficient to give the *Ionocraft* a ceiling of approximately 300,000 feet (60 miles) above sea level.

A main application of the *Ionocraft* would be as an antenna. Two such antennas sustained approximately 65 miles high at strategic points in the United States would permit direct TV and radio transmission between New York and Los Angeles. The *Ionocraft* can be used also as an intercontinental ballistic missile interceptor, according to its inventor, who gives a large number of other possible applications.

**INVENTOR OF NEUTRODYNE
DIES AT 77**

Dr. Louis Alan Hazeltine, inventor of the neutrodyne radio receiver, retired consulting engineer, and former chairman of the physics department at Stevens Institute of Technology (New Jersey), died at his home in Maplewood, N.J., on May 24th.



Professor Hazeltine was famous chiefly for his invention in 1923 of the neutrodyne circuit, a means of preventing oscillation in the tuned-radio-frequency receivers of the period. The effect of tube capacitance was balanced out by small capacitors (*neutrodons*), and the radio-frequency transformers were placed at an angle (55-60 de-

CALENDAR OF EVENTS

National Alliance of Television & Electronic Service Associations (NATESA) Convention, Aug. 13-16; Chicago, Ill.

1964 Western Electronic Show and Convention (WESCON), Aug. 25-28; Los Angeles Sports Arena and Hollywood Park, Los Angeles, Calif.

International Convention on Military Electronics (MIL-E-CON 8), Sept. 14-16; Shoreham Hotel, Washington, D. C.

1964 Conference on Radio Meteorology, Sept. 14-18; National Bureau of Standards Boulder Laboratories, Boulder, Colo.


Advertising Representatives:

EAST John J. Lamson Eastern Sales Manager Radio-Electronics 154 West 14th Street New York, N.Y. 10011 (212) ALgonquin 5-7755	MIDWEST P. H. Dempers Co. 740 North Rush Street Chicago, Illinois 60611 (312) Michigan 2-4245
SOUTHEAST Neff Associates 15 Castle Harbor Isle Fort Lauderdale, Fla. (305) LOgan 6-5656	J. Sidney Crane, Assoc. 22 Eight St., N.E. Atlanta 9, Ga. (404) TRinity 2-6720
WEST COAST/SOUTHWEST Husted-Coughlin, Inc. 1830 W. 8th Street Los Angeles 57, Calif. (213) 389-3132	Huston-Coughlin, Inc. 444 Market Street San Francisco 11, Calif. (415) GARfield 1-0151

UNITED KINGDOM

Publishing & Distributing Co., Ltd., Mitre House,
177 Regent St., London W.1, England.

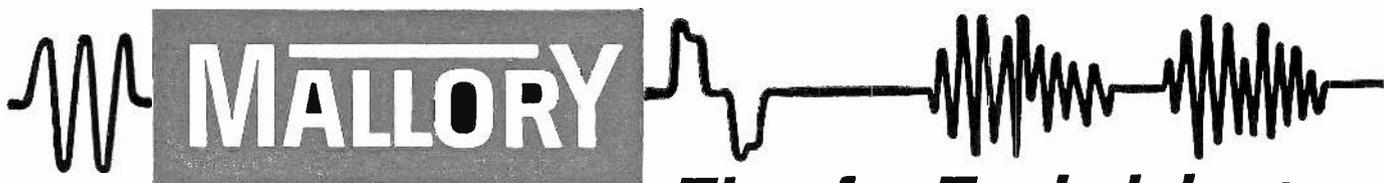Subscription Service: Address form 3579 and correspondence to Radio-Electronics, Subscriber Service, 154 West 14th Street, New York, N. Y. 10011. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.




MALLORY

Tips for Technicians

Mallory Distributor Products Company
A division of P. R. Mallory & Co. Inc.
Indianapolis, Indiana 46206

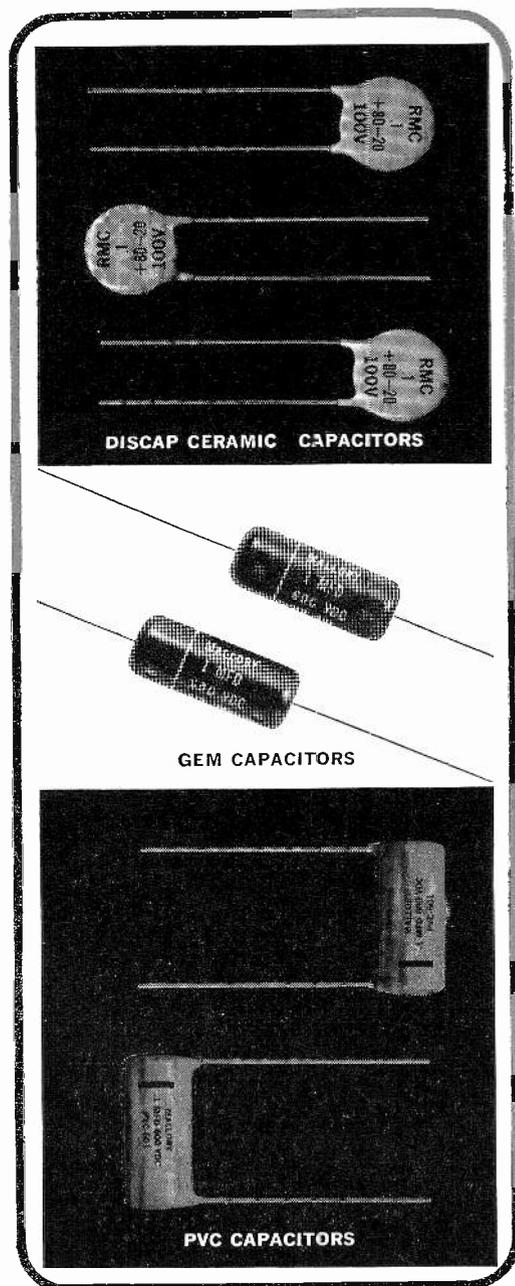How to break the capacitor replacement habit



Ever hear of "original capacitor-itis?" It's a habit that has been plaguing service technicians for decades. Here's what it means. If you need to install a new capacitor, you automatically get one *exactly* like the one that was in the circuit. The original capacitor, in theory, is the best one for the job.

But... it ain't necessarily so. And breaking the habit can often save you money.

When you need to replace a mica capacitor, for instance... consider ceramics. They'll often do a better job, for less cost (and we mean up to $\frac{1}{2}$ as much) than mica capacitors in most circuits. Ceramic capacitors often give you an extra safety factor in voltage rating, too; except for a few miniature and special types, their standard rating is 1000 volts DC. Some up to 30 KV. You can almost always replace mica with ceramic. But... you seldom can replace ceramic with mica, because ceramics are often selected by original equipment designers for temperature compensating functions.

Don't forget to think of ceramics, too, when you need to replace a molded tubular capacitor. They cost about the same or even less, value for value. If you've got 'em, you can use 'em.

Here are two tips that may save you time and money.


First... when you're replacing a capacitor, all you need 9 times out of 10 is the same microfarads and voltage rating. Not a round one. Or a square one.

Second... when you need capacitors, see your Mallory Distributor. He carries not only a complete line of Mallory Discap[®] ceramic capacitors... the finest in the industry... but also Mallory GEM[®] and PVC[®] Mylar* tubulars. Plus Mallory electrolytics, batteries, volume controls, switches, semi-conductors. All of them at famous Mallory quality, at sensible Mallory prices.


*Registered Du Pont Trademark

for peanuts, we'll build any of the 115 products shown in this catalog...

1964

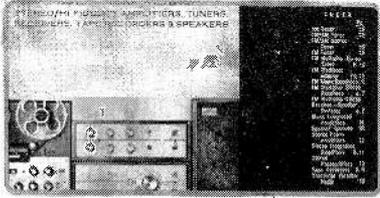

EICO kits and factory wired

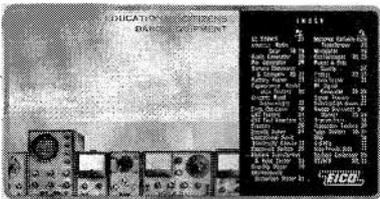

but, why miss all the fun?

Kit building is lots of fun. Besides it enables you to enjoy the best equipment available at a substantial savings. The new 1964 EICO catalog opens the door to kit building enjoyment. Browse through it and you'll find superb values in high fidelity and mono components like the new Classic stereo FM MX receivers, amplifiers and tuners 4-track stereo tape decks test instruments for bench, tube caddy & ham shack economically-priced speaker systems new CB radio kit and ham gear.

For free 1964 catalog, use coupon:

C-8



Electronic Instrument Co., Inc.
131-01 39th Avenue, Flushing, N.Y. 11352
Please send new 32-page 1964 catalog.

Name _____

Address _____

City _____

Zone _____ State _____

Roburn Agencies, 431 Greenwich St., N.Y. 13, N.Y.

grees from the vertical) to prevent inductive interaction.

Professor Hazeltine sold his patent—for \$1 million, according to reports—to a group who organized as the Hazeltine Corp. to license manufacturers under the Hazeltine patent.

In 1944 Professor Hazeltine retired from the faculty of the Stevens Institute and became a consultant to the Hazeltine Corp. He was also a director of the corporation, retiring 3 years ago.

Hazeltine was a Fellow of the Institute of Radio Engineers and president of the institute in 1936. He was also a Fellow of the American Institute of Electrical Engineers, and a member of the American Physical Society.

HUGO GERNSBACK AWARD


Herbert Paul Maruska, a student in the School of Engineering & Science of New York University, has received the 1964 Hugo Gernsback Scholarship Award, a \$1,000 grant presented yearly to a student chosen by the university's College of Engineering faculty.



Mr. Maruska was born in Dallas, Tex., in 1944. His parents moved to New York shortly thereafter, and he received his education in New York public schools and the Bronx High School of Science, becoming interested in electronics while attending high school. He is a member of engineering honor society Tau Beta Pi, and of the electrical engineering honor society Eta Kappa Nu. During last summer's vacation, he worked on medical electronics at the New York University Medical Center in Bellevue Hospital. He expects to work there again this summer. Mr. Maruska will graduate in 1965.

LASERS REACH ULTRAVIOLET

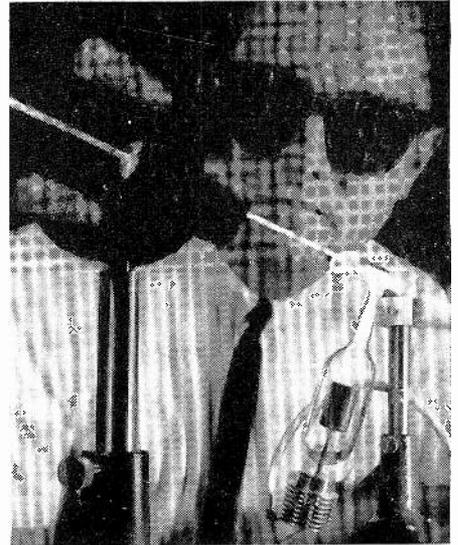Two recent reports from Hughes Aircraft Co. announce laser action at more than 60 new wavelengths, including the ultraviolet. One announcement speaks of a new class of gas ion lasers, using four gaseous elements: argon, krypton, xenon and neon, to achieve



Latest laser (glass tube at right) emits blue, green, violet, red and yellow beams, spanning entire visible portion of spectrum.

laser action.

The ion lasers cover a wide range of frequencies, a majority of the newly discovered color lines being in the blue-green portion of the spectrum.

Another report states that a Hughes Aircraft laser team has raised the efficiency of frequency doubling to obtain higher power than has previously been reported.

Between 25% and 30% conversion efficiency from ruby radiation to 3,471 angstroms (in the ultraviolet) was recently reported by Drs. Myer Geller and Walter Sooy. This represents a 10-megawatt output pulse at the ultraviolet frequency. The same group obtained between 15% and 20% efficiency in doubling infrared light at 1.06 microns to obtain 5,300-angstrom green radiation.

BRIEF BRIEFS

The Bell System has asked the Government to approve rates for its see-as-you-talk system between public locations in three cities: New York, Chicago and Washington. Proposed rates would be \$16 from Washington to New York, \$21 from Washington to Chicago, \$27 from Chicago to New York. Customers will be required to make advance arrangements.

New color TV tube introduced by Sylvania is said to get more than 40% higher brightness by using a new phosphor containing the rare-earth element europium.

New slumber-inducing device marketed by Majima Co., Tokyo, Japan, produces a "sleeping tone" which tranquilizes its users by emitting raindrop-like continuous sound. "Hearing the tone in bed falls you into deep sleep in a several minutes," says the maker. END


What Job Do You Want In Electronics?

Whatever it is, Cleveland Institute can help you get it!

Yes, whatever your goal is in Electronics, there's a Cleveland Institute program to help you reach it *quickly* and *economically*. Here's how: Each CIE program concentrates on electronics theory as applied to the solution of practical, everyday problems. Result . . . as a Cleveland Institute student you will not only learn electronics but *develop the ability to*

use it! This ability makes you eligible for any of the thousands of challenging, high-paying jobs in Electronics. Before you turn this page, select a program to suit your career objective. Then, mark your selection on the coupon below and mail it to us *today*. We will send you the complete details . . . without obligation . . . if you will act **NOW!**

Electronics Technology

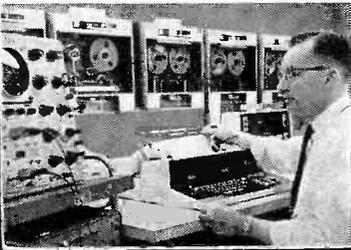


A comprehensive program covering Automator, Communications, Computers, Industrial Controls, Television, Transistors, and preparation for a 1st Class FCC License.

First Class FCC License




If you want a 1st Class FCC ticket quickly, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.

Industrial Electronics & Automation

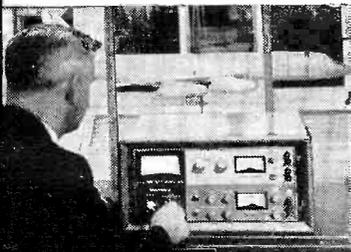


This exciting program includes many important subjects as Computers, Electronic Heating and Welding, Industrial Controls, Servomechanisms, and Solid State Devices.

Electronic Communications

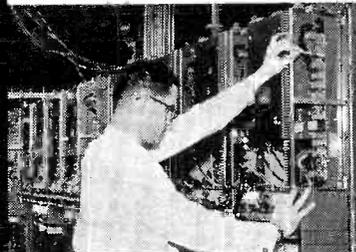

Mobile Radio, Microwave, and 2nd Class FCC preparation are just a few of the topics covered in this "compact" program . . . Carrier Telephony too, if you so desire.

Broadcast Engineering

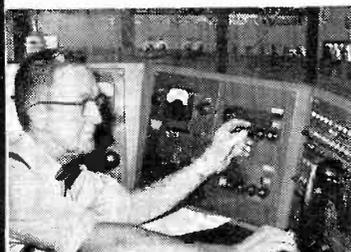

Here's an excellent studio engineering program which will get you a 1st Class FCC License and teach you all about Program Transmission and Broadcast Transmitters.

Mail Coupon TODAY For FREE Catalog


Cleveland Institute of Electronics

1776 E. 17th St., Dept. RE-94
Cleveland, Ohio 44114

Please send FREE Career Information prepared to help me get ahead in Electronics, without further obligation.

CHECK AREA OF MOST INTEREST—

- | | |
|---|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> First Class FCC License |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> Advanced Engineering |

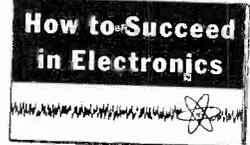

Your present occupation _____

Name _____ (please print) Age _____

Address _____

City _____ State _____ Zip _____

Approved for Veteran's Training under Korean GI Bill. RE-94

Cleveland Institute of Electronics

1776 E. 17th St., Dept. RE-94
Cleveland, Ohio 44114



Accredited Member

WHY risk your reputation with "just-as-good" capacitors?

When you pay little or no attention to quality in tubular replacement capacitors, you leave yourself wide open for criticism of your work . . . you risk your reputation . . . you stand to lose customers. It just doesn't pay to take a chance on capacitors with unknown or debatable performance records when it's so easy to get guaranteed *dependable* tubulars from your Sprague distributor!


There's no "maybe" with these 2 great SPRAGUE DIFILM® TUBULARS!

The ultimate in tubular capacitor construction. Dual dielectric . . . polyester film and special capacitor tissue . . . combines the best features of both. Impregnated with HCX®, an exclusive Sprague synthetic hydrocarbon material which fills every void in the paper, every pinhole in the plastic film *before it solidifies*, resulting in a rock-hard capacitor section . . . there's no oil to leak, no wax to drip. Designed for 105°C (220°F) operation *without voltage derating*.



DIFILM® BLACK BEAUTY® Molded Tubular Capacitors

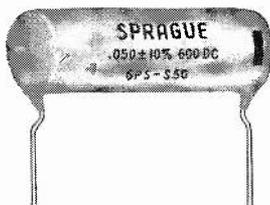The world's most humidity-resistant molded capacitors. Tough, protective outer case of non-flammable molded phenolic . . . cannot be damaged in handling or installation. Black Beauty Capacitors will withstand the hottest temperatures to be found in any TV or radio set, even in the most humid climates.




DIFILM® ORANGE DROP® Dipped Tubular Capacitors

A "must" for applications where only radial-lead capacitors will fit . . . the perfect replacement for dipped capacitors now used in many leading TV sets. Double-dipped in rugged epoxy resin for positive protection against extreme heat and humidity. No other dipped tubular capacitor can match Sprague Orange Drops!

For complete listings, get your copy of Catalog C-616 from your Sprague distributor, or write to Sprague Products Company, 81 Marshall Street, North Adams, Massachusetts.

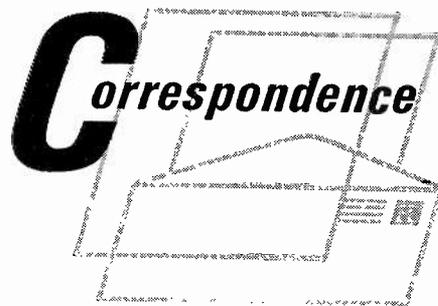WORLD'S LARGEST MANUFACTURER OF CAPACITORS



DITTO: WE NEED THAT NATIONAL FACTS CENTER

Dear Editor:

I agree 100% with your editorial, "Needed: A National Facts Center" in the May 1964 issue of RADIO-ELECTRONICS. Our facts should be gathered in a central place as the Library of Congress gathers books. The facts center should use the latest in information retrieval equipment to speed the gathering of those facts.

The computer in the center would be a little different from the regular scientific or business installation. Its principal function would be rapid recovery of information with little or no computing. This would mean lower cost because of simpler construction. It should be possible to store much of the information on photographic film rather than magnetic tape or cards. Film is, I understand, less expensive than tape or cards; also, the information is more permanent.

The data could be stored on the film by optical reduction, as in microfilm, or it could be changed to a binary code and stored that way. Computer retrieval would probably be easier with the binary code while manual retrieval would be easier with microfilm. The film could be stored in rolls, or on cards as film "chips". The type of storage would probably depend on the type of information. An information retrieval computer using all kinds of storage including photographic film is urgently needed to aid in the recovery of facts that might otherwise be lost.

Also urgently needed is Director John C. Green's "information scientist". His function would be, not only to collect and store the vast amounts of material coming off the printing presses, but to condense it with as little redundancy as possible. Today, we have not only tremendous amounts of new infor-

Stop kidding yourself about your future in electronics

You've been working long enough to know the truth. Education is what separates the men from the boys in electronics—and you're not going anywhere without more of it. The going gets tougher every day for the man without a sound technical education. And electronics changes so rapidly that even a good education isn't worth much unless it's kept up-to-date. Can't go back to school? You don't have to. CREI offers you industry-recognized home study education in every major area of electronics—even the new field of Space Electronics. Rusty on fundamentals? Don't worry—you're eligible if you work in electronics and have a high school education. Our FREE book gives the details. Tear out the coupon or write:

CREI, Dept. 1408-B, 3224 Sixteenth St., N.W.
Washington 10, D. C.



THE CAPITOL RADIO ENGINEERING INSTITUTE

FOUNDED 1927. ACCREDITED MEMBER OF THE NATIONAL HOME STUDY COUNCIL.
Dept. 1408-B, 3224 Sixteenth St., N.W., Washington 10, D. C.

Please send me FREE book describing CREI Programs in Electronics and Nuclear Engineering Technology. I am employed in electronics and have a high school education.

Name _____ Age _____

Address _____

City _____ Zone _____ State _____


Employed by _____

Type of Present Work _____

Check: Home Study Residence School G. I. Bill

T-21

tear out coupon—send for free book today

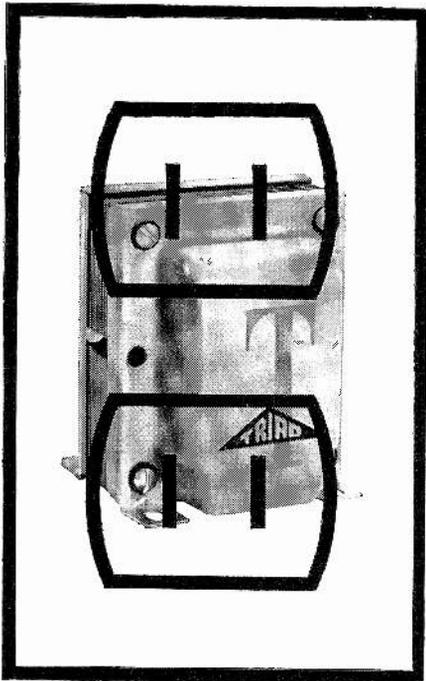

PLUG INTO HOUSE VOLTAGE ANYWHERE!

In auto, boat or plane, Triad's rugged DC-to-AC transistor power supply transformers make it possible for you to plug in a variety of handy household devices—television sets, radios, shavers, record players, dictating machines and heating pads. Two which operate with 12-volt inputs, for example, are the TY-75A which puts out 115 watts at 60 cps and the TY-76A which delivers 60 watts at 60 cps. With a little imagination and either of these units, you can quickly make mobile life far more pleasant and comfortable. Triad also makes a complete line of DC-to-DC transistor power transformers for use with 6, 12 and 28-volt battery-driven sources.

For Engineering Bulletin TY-63 and full details, including basic data, circuit diagrams, specifications and application notes, write to 305 North Briant Street, Huntington, Indiana.

TRIAD DISTRIBUTOR DIVISION
A DIVISION OF LITTON INDUSTRIES

mation, but much of it duplicated and expressed in too many words! Consider, for example, all the material that has been published on audio amplifier design. For someone designing a new audio amplifier to gather it all would take far more time than designing the amplifier. If the information had been previously collected and condensed, getting the data would be much simpler and faster. The reader can doubtless think of many other examples.

The "information scientist" is needed more and more all the time. If we do not conquer our facts, they may conquer us.

DAVID W. JOHNSTON
Washington, D. C.

A VOTE FOR HIGH-GRADE TEST-INSTRUMENT PROJECTS

Dear Editor:

The article "A Lab-Quality Audio Generator," by Jon Idestam-Almquist, is excellent (May 1964 issue). This is the kind of test instrument I have been looking for, for a long time now in a magazine. I believe many like myself prefer "better than available kits" test instruments. May I suggest that you keep on publishing more articles along this line. To follow up this audio generator, I suggest a good squarer (square-wave shaper), in conjunction with this generator.

A tube or transistor version of a good radio-frequency generator will be very much welcomed—one with crystal-controlled frequencies available.

More power to RADIO-ELECTRONICS!
BENJAMIN RESELLA

PRAISES PROJECTOR SERIES

Dear Editor:

The series "Servicing Sound Movie Projectors" (October 1963 through January 1964) was most welcome. Your service editor, Jack Darr, has done an excellent job on this series, as well as on many others. I would appreciate having future series on equipment not usually handled by the radio-TV technician.

I would like to make a few comments on Mr. Darr's statement about captive service policies (January 1964, page 44). In the last few years I have had several sound projectors in for service and have run into just that problem. Many companies refuse to sell parts to independent servicers. Yet sometimes they fail to provide good service themselves; thus independent shops can usu-

ally get all the projector work they can handle.

The best source I have found for special parts is LaVezzi Machine Works, 4635 W. Lake St., Chicago, Ill. It is the largest manufacturer of film sprockets and other parts for manufacturers. Catalogs are furnished on request, and items can be ordered on company letterhead or purchase order.

It would appear that the best answer to captive service is an independent organization with outstanding technical ability that can give the equipment user service quality unequalled by even the manufacturer.

Continue to bring us specialized service articles. I would also like to see more construction articles on laboratory-type test equipment.

D. K. HISKEY
Yorba Linda, Calif.

OPPOSES SCOUT SIGNALING REQUIREMENTS CHANGE

Dear Editor:

The proposed Revised Requirements for Boy Scouts of America, which become effective in September 1965, change the signaling requirement for a First-Class Scout. Instead of learning the International Morse code, he would be permitted to fulfill the requirements by learning semaphore. As a veteran Scouter, a Quarter Century Club radio amateur and a professional in communications for more than 25 years, I feel sure that this change will not benefit Scouting, national defense, the communications field, the Scout's pleasure or his community during an emergency.

In a small open launch off the coast of New England on a subfreezing, windy winter day, my companions and I found, as we wanted to get going again after a stop, that we had fouled the screws of the inboard engine with the anchor line. Efforts to free the line failed. We drifted and tossed close to threatening rocks. About then, someone sighted an approaching ship—possibly our only chance of being rescued.

I took a legal-size sheet of white paper and held it taut in the wind with two hands. I turned it flat-side-to and then edge-to the ship, alternately, trying to signal, like a blinker light, "SOS PROPOULED" in Morse code. I kept on as the ship approached, passed a few miles away and continued on its course.

Just as it was about to go out of sight, it changed course into a large cir-



The move into electronics is your decision. GRANTHAM SCHOOL OF ELECTRONICS makes your move easier...

Beginning at the beginning, Grantham training progresses in a logical, step-by-step manner up through the complex theory of the Missile Age—and all of the math you will need is taught as an integral part of our lessons. Because we present these all-important basic principles with maximum penetration, *you will learn to think and reason electronics* rather than relying on half-understood concepts and rote-memory.

The Grantham program is made up of three consecutive steps, and each completed step increases your value as an electronics man. The following is a "thumb-nail sketch" of the Grantham 3-step program for electronics advancement:

- Course I leads to attainment of your First Class F.C.C. License and may be completed in the classroom or through home study.
- Course II gives you practical experience on a great variety of "live" electronic equipment in the Grantham Student Laboratory.
- Course III offers Advanced Electronics Training (including microwave and radar) and prepares you to advance to senior-technician status.

Get complete details in our free 44-page booklet. Mail coupon, or telephone the school nearest you; phone numbers and addresses are listed below.

Prepare for Employment and/or Advancement in Electronics
by training with

GRANTHAM SCHOOL OF ELECTRONICS

Los Angeles Division
1505 N. Western Ave., Los Angeles, Calif. 90027

Phone:
HO 7-7727

Seattle Division
408 Marion Street, Seattle, Wash. 98104

Phone:
MA 2-7227

Kansas City Division
3123 Gillham Road, Kansas City, Mo. 64109

Phone:
JE 1-6320

Washington Division
821 — 19th Street, N.W., Washington, D.C. 20006

Phone:
ST 3-3614

AUGUST, 1964

[Mail in envelope or paste on postal card]


National Headquarters Office 44-M
Grantham School of Electronics
 1505 N. Western Ave., Hollywood 27, Calif.

Gentlemen:

Please send me your FREE 44-page booklet,
"CAREERS IN ELECTRONICS."

Name _____ Age _____
(PLEASE PRINT)

Address _____

City _____

State _____

I AM INTERESTED IN: HOME STUDY RESIDENT CLASSES

cle, coming close enough to us so we could hear its power megaphone. They said they had read our message, but, because of the rocks, would not get closer to us as long as we were afloat. However, they had radioed for assistance and would watch over us until help came.

Eventually we were towed back to port, grateful that someone able to read code had been aboard that ship.

Partly because of that experience, I am opposed to reinstating semaphore as a signaling option. It would not have worked in a case like the one just reported. I learned it as a Scout about 30 years ago and have had virtually no opportunity to use it. But there are many opportunities to use Morse code. There are more than a quarter million radio amateurs in the US, and many more overseas. There are about 600,000 registered First-Class Scouts, many ex-Scouts, communications men and others able to copy code in some degree. Radio amateurs are well known for their aid in time of disaster, and Scouts have been one of the principal sources for radio amateurs.

Ships usually use Morse blinker rather than semaphore for visual contact. Morse is certainly no harder to learn than semaphore, and is much more versatile: it needs only a single flag, blinker or audible signal.

Though semaphore might possibly be left as an option in the Signaling Merit Badge requirements, it should certainly not be an optional alternate to Morse code in the First-Class requirements.

I solicit your aid in preventing this change. Express your opposition to the National Council, Boy Scouts of America, New Brunswick, N. J.

WALTER TUCKER, K4BRI

Springfield, Va.

TRANSISTOR-PORTABLE POWER SUPPLY FILLS A NEED

Dear Editor:

A word of praise for the transistor radio power supply designed by Wayne Lemons ("Bench Supply for Transistor Radios," May 1964, page 38). This instrument certainly fills a definite need. It performs perfectly, and fits neatly under a shelf just above my workbench.

I consider Mr. Lemons one of your ablest contributors.

GLEN H. BRYANT

Hoisington, Kan.

END

OUR STANDARD ABBREVIATIONS

RADIO-ELECTRONICS has always tried to maintain a consistent style in the abbreviations used in text and artwork (diagrams and photo "call-outs"). New abbreviations are developed as new terms are added to our electronic vocabulary. We are printing this revised list of abbreviations to bring our old readers up to date and to help readers who have not been with us long enough to recognize the forms consistently used in our magazine.

The abbreviations are indexed by symbol with Greek letters treated like English phonetic equivalents. Many of those listed are always spelled out in the text and are abbreviated in our art work. Terms used only in artwork—and those capitalized in text—appear in capitals. Abbreviations in lower-case letters are so used in text and are capitalized in art work. Periods are used in abbreviations only where the abbreviation might be confused for a word. For example, *rf* and *i.f.* are our abbreviations for radio frequency and intermediate frequency, respectively.

ABBREVIATION	ELECTRONIC TERM
A	ampere(s)
ac	alternating current
acc	automatic chroma control
ADJ	adjacent, adjustment
af	audio frequency
afc	automatic frequency control
AFT	audio-frequency transformer
agc	automatic gain control
AM	amplitude modulation
amp	ampere(s)
AMPL	amplifier
ANT	antenna
apc	automatic phase control
AITEN	attenuator
AUTOTRANS	autotransformer
avc	automatic volume control
AWG	American wire gage
b or base	base (of transistors)
BAL MOD	balanced modulator
BALUN	balanced-to-unbalanced transformer
BATT	battery
BCI	broadcast interference
bfo	beat frequency oscillator
BO	Barkhausen oscillation
BTO	blocking-tube oscillator
c	collector (of transistors)
C, CAP	capacitor (capacitance)
CALIB	calibrate
cath (K on tube diagrams)	cathode
CATH FOLL	cathode follower
CENT	centering
CH	choke
CHAN	channel
CHG	charge
CKT	circuit

(continued on page 22)

RAVE REVIEW ON SONY 600



Radio-Electronics Magazine June, 1964 says:

"This recorder has some very good specifications and, although its price is above the 'cheap' range, one does not readily believe such excellent specs for a 4-track machine until they prove out. This machine fulfilled its promise. With it, you can tape your stereo discs and play them back without being able to detect any difference, which is saying something. The physical design of this unit is good, for either permanent installation or the most complete portability.

"The footage indicator is a footage indicator, not merely a place spotter, and it keeps its count with all normal tape movements. Independent control of left and right channels, so one can be operated in record, while the other is in playback, enable the unit to be used for an endless variety of 'special' effects.

"Playback and record functions are completely separate, so that a recorded program can be monitored immediately. Microphone and auxiliary inputs can be mixed for combination and re-record effects. First stage amplification uses transistors, while the main amplification uses tubes—a good marriage in this particular design.

"The mikes are very good, compared with most of the 'inexpensive' types used with home recorders. Extremely good realism is possible for home recordings. I had my family 'act natural' in front of the two-mike combination and the playback was unbelievably real.


"The Sony 600 will naturally take a little playing around to find out how to do various 'extra' things you may want. But when you get to know it, you'll find it a very versatile instrument. It's a recorder with which familiarity brings confidence."

Norman H. Crowhurst

For further information, or complete copy of the above test report, write Superscope, Inc. "600 Test Report G, Sun Valley, Calif.



The commanding presence of Sony sound

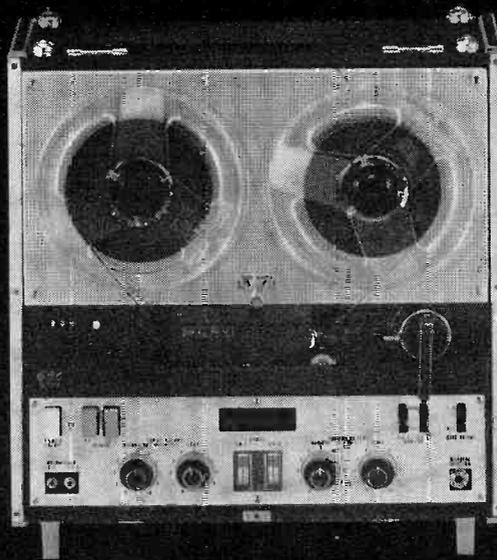

Now enter the world of the professional. With the **Sony Sterecorder 600**, a superbly engineered instrument with 3-head design, you are master of the most exacting stereophonic tape recording techniques.

Professional in every detail, from its modular circuitry to its 3-head design, this superb 4-track stereophonic and monophonic recording and playback unit provides such versatile features as: ■ vertical and horizontal operating positions ■ sound on sound ■ tape and source monitor switch ■ full 7" reel capacity ■ microphone and line mixing ■ magnetic phono and FM stereo inputs ■ 2 V.U. meters ■ hysteresis-synchronous drive motors ■ dynamically balanced capstan flywheel ■ automatic shut off ■ pause control and digital tape counter—all indispensable to the discriminating recording enthusiast. Less than \$450,* complete with carrying case and two Sony F-87 cardioid dynamic microphones.

SONY SUPERSCOPE The Tapeway to Stereo [■]Multiplex Ready!
* Yes, less than \$450!

Sony tape recorders, the most complete line of quality recording equipment in the world, start at less than \$79.50. For literature or name of nearest dealer, write Superscope, Inc., Dept. 58, Sun Valley, Calif. In New York, visit the Sony Salon, 585 Fifth Avenue.

You get more for your money from NRI- than from any other home-study Electronics, Radio-TV school

Compare if you like. You'll find—as have so many thousands of others—that NRI training can't be beat. From the delivery of your first lessons in the remarkable, new Achievement Kit we send you, to "bite size", easily-read texts and carefully designed training equipment . . . NRI gives you more value than any other home-study

school. Shown below is a dramatic, pictorial example of training materials included in just one NRI Course. *Everything* you see pictured below is included in low-cost NRI training. Other major NRI courses are equally complete. Text for text, kit for kit, dollar for dollar—your best home-study buy is NRI.




GET A FASTER START WITH NRI'S NEW EXCLUSIVE ACHIEVEMENT KIT

The day we receive your enrollment application we mail out your Achievement Kit. It contains everything you need to make an easy, fast start in the Electronics training of your choice. This attractive, new starter kit is an outstanding, logical way to introduce you to home-study as NRI teaches it . . . an unparalleled example of the value of NRI training . . . training that is backed up by a dedicated staff and the personal attention you should expect of a home-study school. It is your first of a number of special training aids carefully developed by the NRI laboratories to make your adventure into Electronics absorbing, meaningful. What's in the Achievement Kit? Your first group of lesson texts; a rich vinyl desk folder to hold your study material; the industry's most complete Radio-TV Electronics Dictionary; valuable reference texts; lesson answer sheets; pre-addressed envelopes; pencils; pen; engineer's ruler—even postage. No other school has anything like the NRI Achievement Kit.


LEARNING BECOMES AN ABSORBING ADVENTURE WITH NRI TRAINING KITS

Electronics comes alive with NRI training kits. What better way to learn than by doing it? That's why NRI pioneered and perfected the "home lab" technique of learning at home in your spare time. You get your hands on actual parts and use them to build, experiment, explore, discover. NRI invites comparison with training equipment offered by any other school. Begin NOW this exciting program of practical learning. It's the best way to understand the skills of the finest technicians—and make their techniques your own. Whatever your reason for wanting to increase your knowledge of Electronics . . . whatever your field of interest . . . whatever your education . . . there's an NRI instruction plan to fit your needs, at low tuition rates to fit your budget. Get all the facts about NRI training plans, NRI training equipment. Fill in and mail the attached postage-free card today. No salesman will call. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.

OUR 50th YEAR OF LEADERSHIP

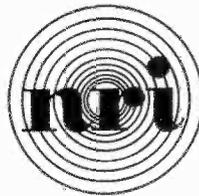

IN ELECTRONICS TRAINING

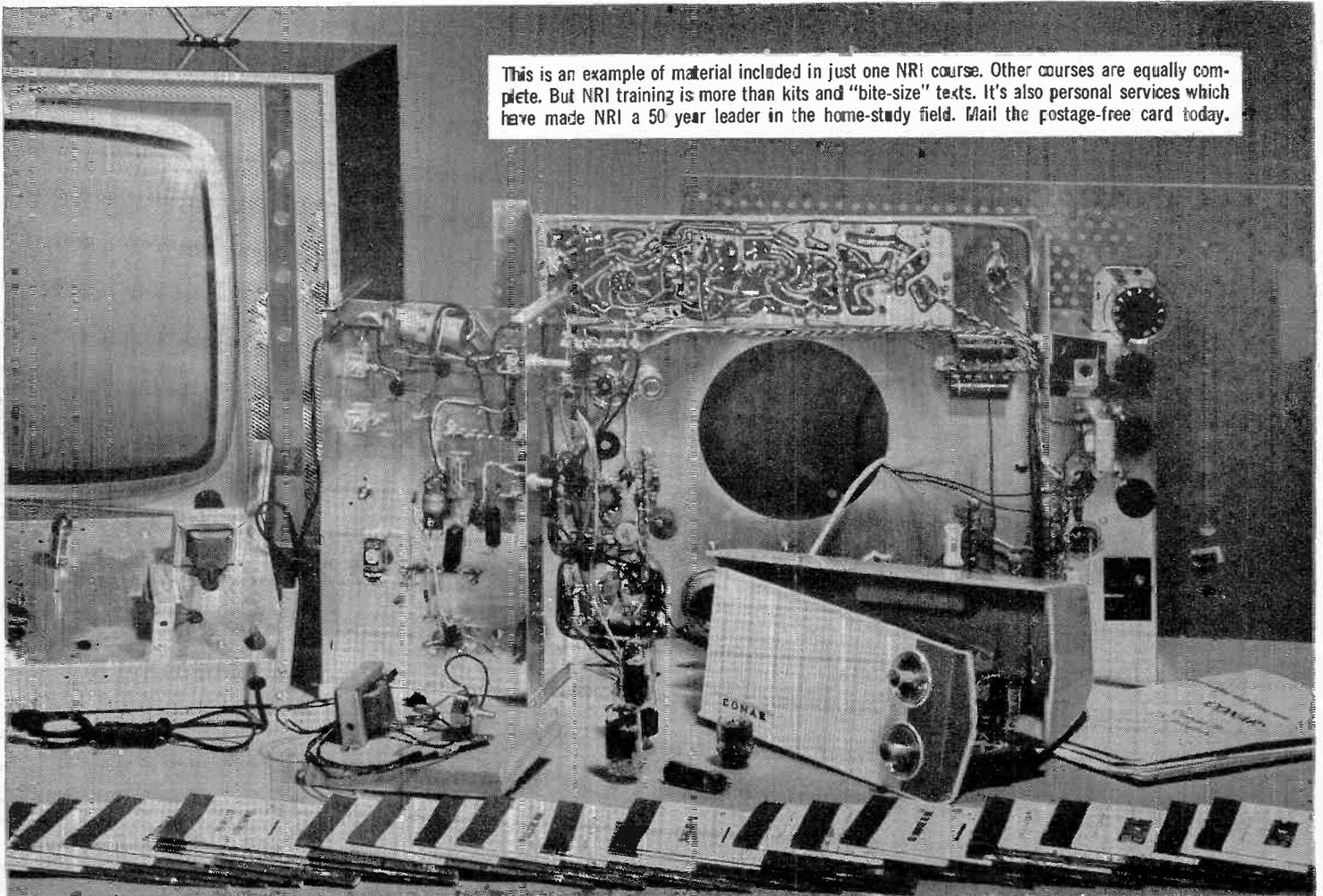

This is an example of material included in just one NRI course. Other courses are equally complete. But NRI training is more than kits and "bite-size" texts. It's also personal services which have made NRI a 50 year leader in the home-study field. Mail the postage-free card today.

(continued from page 16)

ABBREVIATION ELECTRONIC TERM

CKT BRKR circuit breaker
 coax coaxial
 COM common
 COND conductor
 CONN connection
 CONT control
 CONV convergence, converter
 counter emf counter electromotive force
 C-R cathode-ray (tube, etc.)
 CRO cathode-ray oscilloscope
 CRT cathode-ray tube
 CT center tap
 CW continuous wave
 D diode
 db decibel
 dc direct current
 dcc double cotton covered (wire)
 DC REST direct current restorer
 DEFL deflection
 DEMOD demodulator
 DET detector
 df direction finder
 DIELEC dielectric
 DIFF differentiator
 DISCH discharge
 DISCRIM discriminator
 dpdt double pole double throw
 dpst double pole single throw
 dsc double silk covered (wire)
 DYN dynamic
 dx distance
 e emitter (of transistors)
 E potential
 E (sometimes V in transistor diagrams) voltage
 ECO electron coupled oscillator
 ELEC electric; electrolytic
 ELECT electrode
 emf electromotive force
 ENAM enameled (wire)
 EQUIV equivalent
 ERASE HD erase head
 ERP effective radiated power
 EXT external or extension
 F (f as suffix) farad(s)
 f, FREQ frequency
 FIL (F in tube diagrams) filament
 FM frequency modulation
 FOLL follower (-ing)
 G (in tube diagrams) grid
 GCA ground controlled approach
 GDO grid dip oscillator
 GEN generator
 GND ground
 h henry (ies)
 HD head
 hf high frequency
 HORIZ horizontal
 HTR (H) heater
 I current
 IC internal connection (on tubes)
 i.f. intermediate frequency
 IFT intermediate frequency transformer
 ILS instrument landing system
 IM intermodulation
 INT integrator
 INV inverter
 ips inches per second
 K thousand
 K cathode (on tubes)
 kc kilocycle
 kw kilowatt
 λ (lambda) wavelength
 L inductor (inductance)
 L coil
 lf low frequency
 LIM limiter
 LIN linearity
 μ (mu) micro- (one-millionth)
 μ f microfarads
 μ h microhenry(ies)
 μ μ f see pf
 μ sec microseconds
 M meter
 M million
 ma milliampere(s)
 max maximum
 mc megacycle(s)
 meg megohm
 mh millihenry(ies)
 mike microphone
 MIN minimum

MOD modulation (modulator)
 MPX multiplex
 MULT multiplier
 MVB multivibrator
 NBFM narrow-band FM
 NC neutralizing capacitor
 N.C. normally closed (switch or relay)
 NE neon
 NEG negative
 NET network
 N.O. normally open (switch or relay)
 n-p-n negative-positive-negative (transistors)
 OSC oscillator
 P plate
 PA public address
 PC photocell
 PERM permanent
 pf picofarad ($\mu\mu$ f)
 phone(s) telephone, headphones
 PHOTO MULT photomultiplier
 pix picture (TV)
 PL pilot lamp
 PM permanent magnet (speaker)
 PM phase modulation
 p-n-p positive-negative-positive (transistors)
 POS positive
 POT potentiometer
 PP peak-to-peak
 PPI plan-position indicator (radar)
 pps pulses per second
 preamp preamplifier
 prf pulse repetition frequency
 PRI primary
 PT phototube
 Q reactance-resistance ratio
 Q transistor
 QUAD quadrature
 R resistance (resistor)
 RCDG recording
 RCDR recorder
 RECT rectifier
 REG regulator
 regen regeneration
 rf radio frequency
 RFC radio-frequency choke
 RFT radio-frequency transformer
 rms root mean square
 RY relay
 S switch
 scc single cotton covered (wire)
 SCR silicon controlled rectifier
 SEC second
 SEL (RECT) selenium (rectifier)
 SEP separator
 SG screen grid
 SIG signal
 SLD solenoid
 spdt single pole double throw (switch, etc.)
 SPKR speaker
 spst single pole single throw (switch, etc.)
 SSB single sideband
 ssc single silk covered (wire)
 SW shortwave, switch
 SWR standing wave ratio
 sync synchronization
 T transformer, trimmer
 TELEG telegraph
 TERM terminal
 tptg tuned plate tuned grid
 TRANS transformer
 trf tuned radio frequency
 TVI television interference
 uhf ultra-high frequency
 v volt(s)
 V tube
 va volt-ampere
 vac, vdc volts ac, dc
 VAR variable
 VC voice coil
 VERT vertical
 VFO variable frequency oscillator
 vhf very high frequency
 VIB vibrator
 VOL volume
 VOM volt-ohmmeter
 VR voltage regulator (tube)
 vtvm vacuum-tube voltmeter
 VU volume unit(s)
 W watt(s)
 X reactance
 xtal crystal
 Z impedance

—END—



DYMO

IDENTIFICATION SYSTEM

THE ELECTRONICS INDUSTRY IDENTIFIES ITSELF WITH DYMO! □ DYMO's M-55 TAPEWRITER makes raised-letter labels on-the-spot. Just dial letters, numbers, or symbols—and squeeze the handle. Letters come out crisp white on a colored background of self-sticking vinyl. Complete with round and square corner cutters, accessory wheels for technical symbols and vertical labels. With one tool, a complete system of identification. Always use DYMO tape!

\$29⁹⁵ Suggested Price



FREE: Tape samples and full details. Write to: DYMO INDUSTRIES, INC., P. O. Box 1030, Berkeley, Calif. Dept. RE-8-55. Prices slightly higher in Canada.

**need
reliable
service
data?**



Free SEND TODAY FOR THE LATEST INDEX TO PHOTOFAC!

your handy guide to the world's finest electronic service data

covers over 58,000 listings of:

- TV Receivers
- Home & Auto Radios
- Phonos & Hi-Fi
- Tape Recorders
- CB Radios
- Record Changers

Send today for this valuable 72-page guide covering virtually every model of home-entertainment electronic equipment produced since 1946! Helps you locate the proper PHOTOFAC Folder to quickly solve any service problem in any model. PHOTOFAC provides *everything* you need in complete, uniform style for quick, effective repairs: Famous Standard Notation Schematics packed with the service details you need; Full Photo Coverage of all chassis views; Complete Replacement Parts Lists; Tube Placement Diagrams; Alignment Instructions; CircuiTrace® for printed boards; Disassembly Instructions; Dial Cord Diagrams; Changer and Recorder "Exploded Views"—plus dozens of other great features. Send coupon for your FREE copy of the latest PHOTOFAC Index to the service data you need!

Take the Right Step to Time-Saving, Profit-building Servicing... See your Sams Distributor for details on an Easy-Buy PHOTOFAC Library and Standing Order Subscription.

NOW! INDEX INCLUDES MODELS COVERED IN THE PHOTOFAC SPECIALIZED SERIES MANUALS...

Lists all models now covered in the PHOTOFAC Specialized Series: Transistor Radios, Auto Radios, CB Radios, and Tape Recorders—absolutely complete!



**HOWARD W. SAMS & CO., Dept. REF-8
4300 W. 62nd St., Indianapolis, Indiana 46206**

- Send FREE Photofact Index
- Send full information on Easy-Buy Plan and Standing Order Subscription

My Distributor is _____

Shop Name _____

Attn.: _____

Address _____

City _____ Zone _____ State _____

INTERNATIONAL'S **NEW** EXECUTIVE 750-H CITIZENS BAND TRANSCEIVER . . . FOR PEOPLE WHO EXPECT THE **VERY BEST***




The International **Executive 750-H** introduces a transceiver that is quickly adaptable to all types of mobile or base installations.

The remote console, which is normally installed under the auto dash, has a new companion speaker console. It may be combined with the remote unit or mounted separately. The speaker makes a perfect base when the remote console is used on a desk. Provision has also been made for adding an S/meter.**

What's more, the Executive 750-H is loaded with extra performance features; such as, 23-crystal controlled channels, illuminated channel selector dial, a new speech clipper, increased selectivity, new connections for easy cabling.

The Executive 750-H is complete with crystals, mounting rack for the remote console, trunk mounting rack for the set, push-to-talk microphone, power cable kit, plus all necessary connecting cables. Operates on 6 vdc, 12 vdc, or 115 vac.

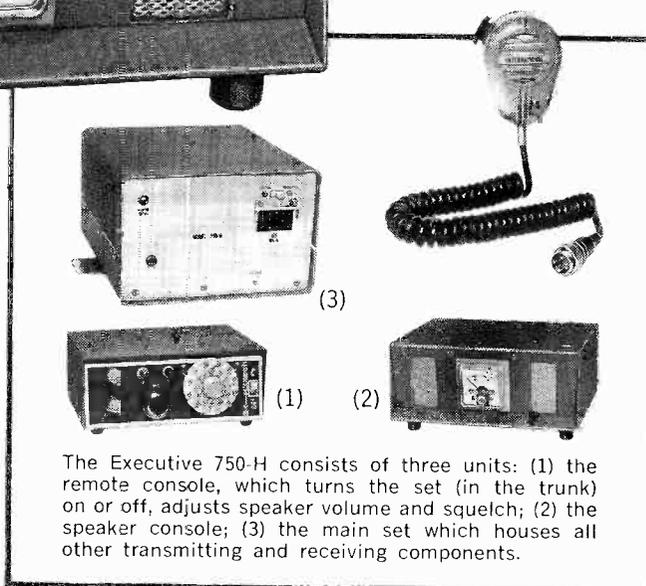Your International dealer has a liberal trade-in plan. **Step up to an Executive 750-H today!**



The Executive 750-H consists of three units: (1) the remote console, which turns the set (in the trunk) on or off, adjusts speaker volume and squelch; (2) the speaker console; (3) the main set which houses all other transmitting and receiving components.

*Performance—Construction—Design—Components
**S/meter available as an accessory item.

WRITE TODAY FOR OUR 1964 CATALOG.



18 NORTH LEE • OKLAHOMA CITY, OKLA.

RADIO-ELECTRONICS

MEDICAL ELECTRONICS

... An Immense Field Beckons the Researcher ...

THE FOLLOWING partial reprint is taken from our *July 1950 editorial*. Most of it is probably as true today as it was then. What prompted the reprint can be found in our last month's editorial, "Electronics' Future."

It is particularly addressed to the more than 67,000 professional engineers, technical and production workers who have been laid off recently because of Government cut-backs and cost-cutting programs. Many or all of these workers, mostly electronic technicians, anxious to make new connections, could not do worse than re-establish themselves in a vast new field: medical electronics. Many laboratories, large hospitals and other institutions always have openings for trained electronic men anxious to explore this new technology field. It can be very lucrative for the right men.

There is perhaps no field today which requires bio-electronic applications more urgently than medicine. Medicine is as yet not an exact science, but rather an art. The medical man still falls back upon most of his five senses when he makes a diagnosis. His trained eyes see many tell-tale signs; his ear evaluates heart, chest and lung sounds; his nose can often recognize certain diseases, such as measles, scarlet fever and others that have characteristic odors. Old-time practitioners touched the backs of their patients' hands with the tip of their tongue—the salinity, the acidity, etc., of the skin frequently was a good index of certain diseases.

Methods such as these seem crude and archaic in the electronic age. Yet the human body is a most complex machine, with most of its machinery hidden and inaccessible. Its electric organs are delicate and deep-seated. Its chemical plants are distributed widely throughout the body and are often difficult to contact. The body's heating and cooling plants are still not understood too well. The blood circulatory system—while better explored—still holds many unsolved problems.

Thousands of medical books covering every part and function of the human body cannot begin to more than suggest the extent of its complexities. This is particularly true of the vast field of diagnosis.

Electronically the human body can be compared to a sealed up radio or television receiver, with only a few exposed connections. The service technician parallels the physician who now is called upon to locate the hidden defect. But neither service technician nor the physician today has a universal "analyzer" that can locate all faults or troubles throughout a radio or TV set, or the vast and complex domain of the "sealed-unit" human machine.

There no longer remains any valid reason why electronic science should not give the medical practitioner a biological—electronic analyzer that could in time diagnose any disease, any dysfunction. The oscilloscope, the amplifier, the millivoltmeter and microammeter, the sensitive thermocouple and dozens of other electronic instruments can all be combined into a portable *bio-analyzer* in the future.

Even now, medical science uses thermionic amplifica-

tion plus a graphic galvanometer for recording heart impulses, brain waves and uterine contractions. The photoelectric cell has already been made an indispensable part of biochemical technique: the colorimeter is calibrated to read grams of haemoglobin per hundred cubic centimeters of blood directly, or milligrams of nitrogen . . . or creatine or uric acid. Heart sounds are accurately analyzed on a tape; murmurs are measured to a hundredth of a second. It is only a question of time until these present uses and others added are all integrated into one unit.

Once such an instrument has been evolved and perfected and the practicing physician has learned how to master its complexities, medicine will have a valuable tool to combat disease effectively. There will then no longer be any guesswork in diagnosis.

The doctor then can make his blood tests, his blood count on the spot—without puncturing the patient's skin—and without the necessity of going to a technician who specializes in such work. He will take his cardiogram on the spot. He will know the *exact* status of an appendix and will know if it is to be excised or if it can be treated. Puzzling rises of temperature of a patient can be tracked down fast—hidden abscesses for instance can be located by local temperature variations. Usually the site of an internal abscess has a higher temperature index than other parts of the body. Hundreds of similar examples could be cited to prove that bio-electronic diagnosis is possible and that undoubtedly it will be commonplace in the not too distant future.

Much research will have to be done in the meanwhile to make it an accomplished fact. Electronic and medical research teams will have to pool their joint talents and knowledge in collaboration with instrument technicians to evolve a medically acceptable bio-analyzer. Finally doctors will have to be trained to use the instrument and to evaluate all its ramifications. Admittedly this will take time, effort and money but it *will* be done.

What About the Immediate Future?

For many years, editorially and otherwise, the present writer has been talking about a replacement for (or a new or better addition to) our present X-rays. Good as they are, X-rays are at best only *shadowgraphs*. They give only vague outlines of our major organs. Today, the heart, the lungs, the kidneys, the adrenals, the liver, the internal sexual organs, the appendix and others must always be interpreted by qualified technicians. Disease does not always show. Incipient cancer rarely shows up clearly.

In the Christmas 1953 issue of the writer's *Forecast* magazine, he said:

"In the future, the medical technician will *actually* see all your interior organs and will watch them work.

"This will be done by a device placed directly against your body. It will be a light source, several times as powerful as the sun—but it will be *cold light*. The light source will be

Continued on page 74

PART ONE:

Two kinds of rotators and how they work, and where to look for trouble in them

HOW TO REPAIR ROTATORS

By HOMER L. DAVIDSON

MANY RADIO-TV SERVICE TECHNICIANS JUST WON'T REPAIR or install antennas or rotators. They quote many reasons, but I suspect the main one is that it is just too much work. Here's an illustration from a distributor salesman who calls on us every Friday afternoon.

He had just called on another shop. Its owner was standing looking out his window and worrying about business. He hadn't had one service call all morning. His bench man was sitting and hoping for 5 o'clock to come so he could go home. The shop owner was wishing that he had chosen another trade. At that moment the telephone rang and the helper answered it. A customer wanted his rotator fixed; his antenna was stuck in the wrong direction for the channel he

wanted to watch. The helper said, "We don't do any antenna or rotator work," and hung up the phone. He sat down again on his stool to do nothing. The salesman asked the service man why he didn't do antenna and rotator work. The answer was short and simple: No money and a lot of hard work.

Yet I know for a fact that the antenna repair business is good. Money can be made in it. And the help is kept busy, keeping that overhead down. Only a few things mark up to forty to fifty percent. Antenna and rotator work do if labor is properly charged for.

This article deals strictly with rotator repair. Insurance people are requiring that antennas and rotators be repaired if possible. If not, they can be replaced with new ones. Insur-

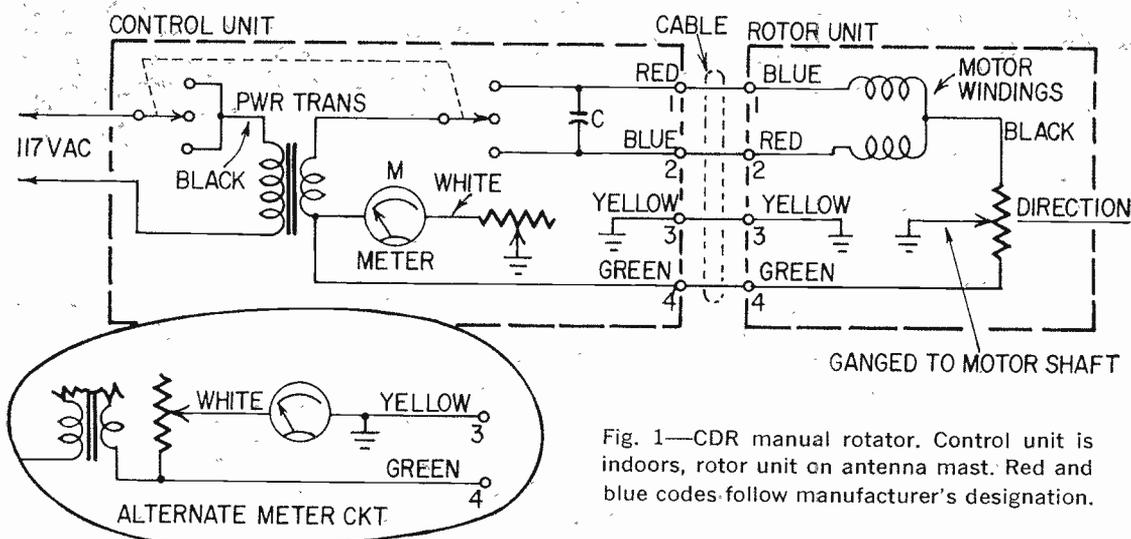


Fig. 1—CDR manual rotator. Control unit is indoors, rotor unit on antenna mast. Red and blue codes follow manufacturer's designation.

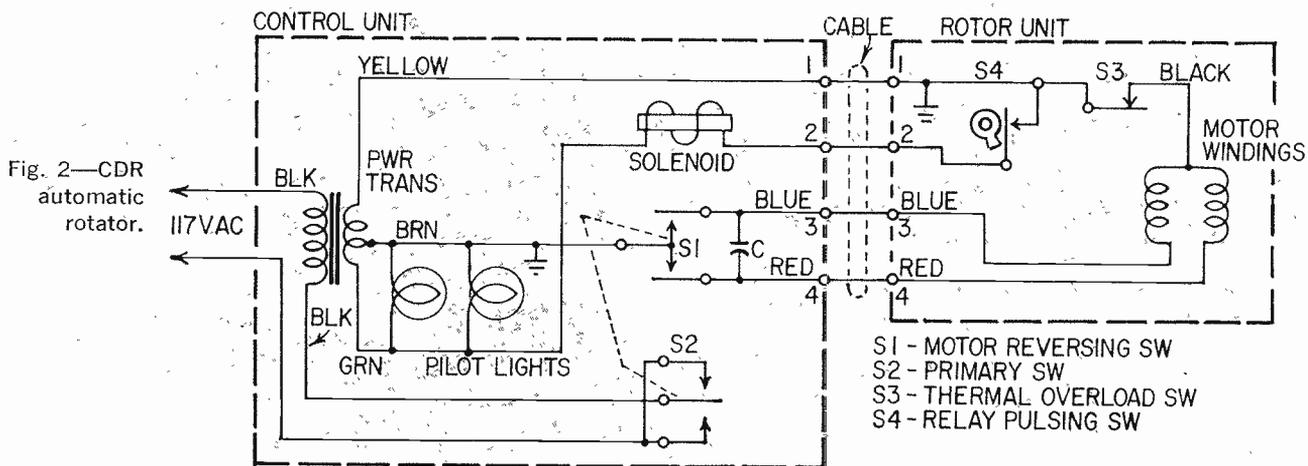


Fig. 2—CDR automatic rotator.

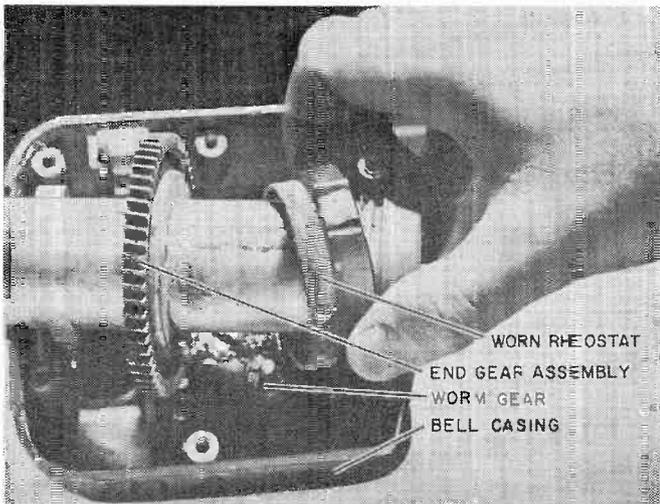


Fig. 3—Worn direction-sensing rheostat being removed.

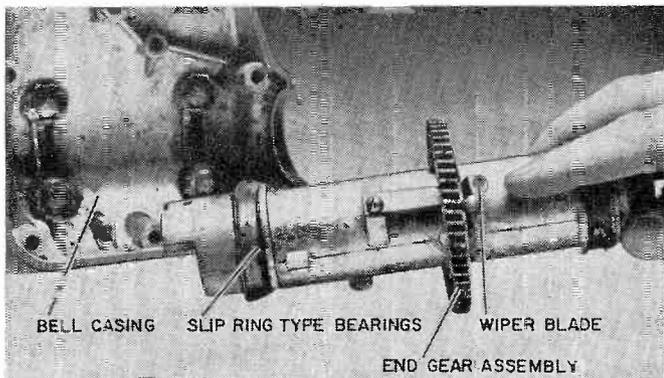


Fig. 4—Rheostat wiper blade is electrically common to case and frame.

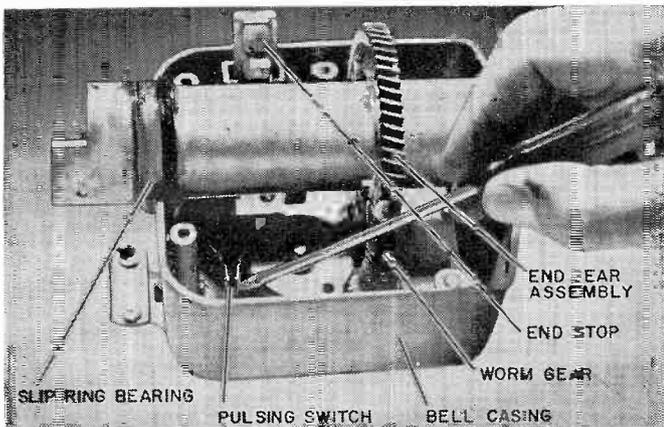


Fig. 5—Screwdriver here points to pulsing switch in automatic unit. Contacts are open.

ance work is sure money, if properly handled.

A rotator installation actually consists of three units: the rotator control box, rotator motor, and interconnecting rotator wire. Trouble in any of the three will keep the rotator from turning.

Fig. 1 is a schematic diagram of a manual rotator. The ac line voltage feeds to one side of a ganged switch. In most rotators this switch is held down by the operator. Press down on the right-hand side, and the rotator turns clockwise. Press down on the left side, and the rotator turns counter-clockwise. The switch transfers the supply to one side or other of the motor winding, reversing the field and direction of rotation.

A potentiometer in the motor assembly turns with the motor and acts as a direction sensor. Wire 4 is a return wire to the meter direction indicator and is in series with a small rheostat which is used to align the meter with the corresponding direction of the motor unit. The rheostat and wiping blade are shown in Figs. 3 and 4.

Fig. 2 is a diagram of an automatic rotator. This kind stops automatically at a preset point on a dial. The operator turns the direction knob to the direction he wants. The rotator turns to that direction and stops. A pulsing solenoid relay, pulsing switch and direction knob are basically the only differences between a manual and an automatic rotator.

The direction indicator knob which operates S1 is turned to the desired direction. S4 is a pulsing switch and is turned by the small rotator motor. (This switch is pointed out in Fig. 5.) When S1's and S2's contacts are closed, voltage is applied to the stepping or pulsing solenoid in the control unit. The solenoid clicks or pulses until the desired direction is reached and switch S2 opens. This removes the 117 volts ac on the primary side of the power transformer. The relay stops pulsing and the unit shuts off. If the direction indicator knob is turned in the opposite direction, the motor reverses and again pulses until the desired direction is reached. Fig. 6 shows the pulsing relay.

A rotator can be checked easily by substitution and continuity testers. An ohmmeter or light bulb and battery will check the continuity of the wiring and rotator. If the control box appears to be bad, substituting a new one will clear up the situation. Check the continuity and try substitution *before*

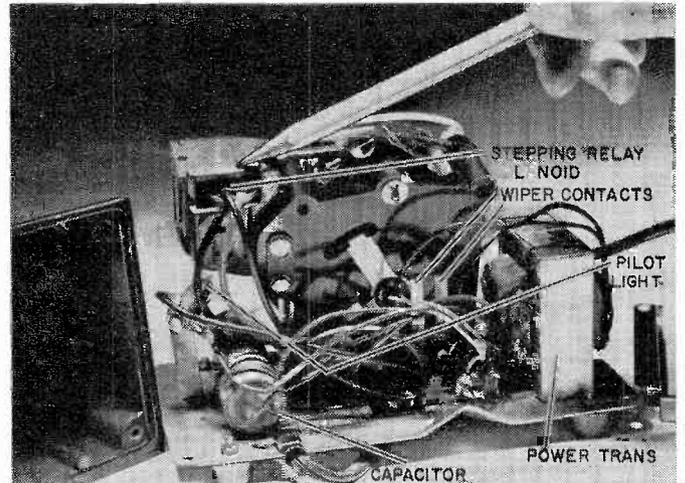


Fig. 6—Pencil shows stepping relay solenoid.

Fig. 7—Inside nonautomatic rotator control box.


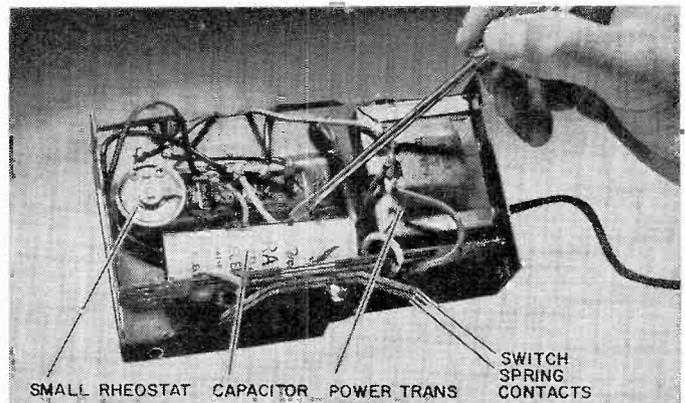


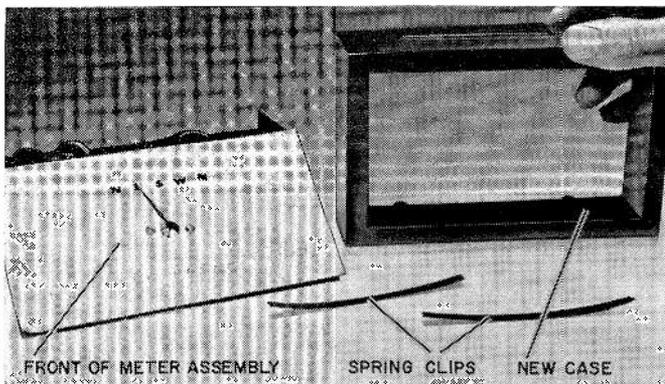

Fig. 8—Back of meter assembly (manual type).

Fig. 9—Manual unit comes apart easily. Curved strips in foreground are spring clips that hold meter to case.



you climb up on the roof. If the rotator motor is bad, it must be dismantled from the antenna mast and repaired or replaced.

The rotator itself consists of a motor and control box. Let's take an Alliance T12 control box and examine possible troubles. Most likely are a defective capacitor, burned-out transformer, open meter and a cracked control box. Fig. 7 shows the starting capacitor, power transformer and small rheostat. In Fig. 8 the back of the meter assembly is illustrated. A broken meter case is being replaced in Fig. 9.

Four bolts in the back can be removed to let the control unit slip out of its case. Check continuity of the meter and rheostat. Measure the transformer secondary voltage. It should be between 25 and 35 with the meter connected. Parts are available at most local distributors who sell rotators.

As an example, let's take a case where the meter will not read but the rotator turns. The meter is definitely bad and must be replaced. First unsolder the red, black and brown wires from their components. Pull back the two spring clamps at the back of the meter and remove the meter. Replace the meter assembly, spring the clips back into place and resolder the three color-coded wires. That's all.

Rotator repair is quite simple; there are only a few parts to replace. Instructions are usually included with replacement components by the manufacturers.

Next month we'll discuss troubleshooting, repairing and replacing defective rotator motors, and say some words about wind damage insurance for rotator assemblies.

TO BE CONTINUED

Booster Triples Radio Output

By HARRY E. STOCKMAN*


YOU CAN BUILD THIS SIMPLE GADGET IN an hour, and then sit back and marvel at the improved performance of your little transistor portable. This antenna is a parasitic device: it uses no tubes, transistors or batteries, and is not connected in any way to the radio.

Construction is shown in the drawing below. Though only one turn is shown, you will need about 13. Use No. 24 enamel or double-cotton-covered magnet wire. The loop is held upright by two $\frac{3}{8}$ -inch wooden dowels mounted in a vertical "V". The 350-pf variable is connected across the loop. Its value is not critical (a 365-pf variable can be used just as well).

To use the antenna, place your transistor portable so that its built-in ferrite-rod antenna is coaxial with (that is, "pokes through") the parasitic antenna. Turn on the radio and tune in a station (a weak or moderately weak one will show the greatest improvement).

Now tune the parasitic antenna's capacitor until you hear an increase in volume. It should be very noticeable.

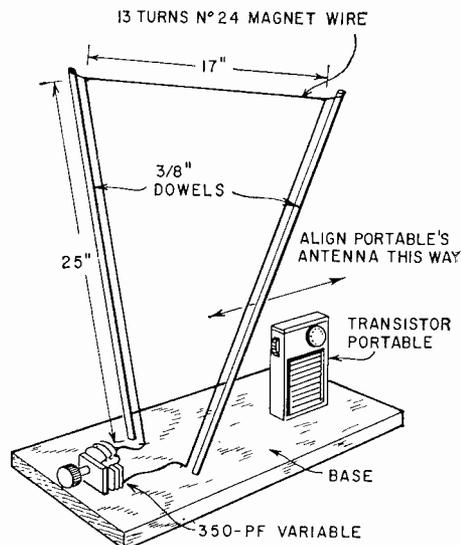For skeptics, some explanation is in order. In ordinary ferrite-rod anten-



nas, the length-to-diameter ratio is important to sensitivity. Because of space limits, this ratio is often well below what it should be, and a small set often doesn't perform as well as it might. Sometimes, too, low-Q ferrites are used. The parasitic antenna's function is not very different from that of any parasitic element on, say, a Yagi antenna. It helps intercept the signal, and its energy is coupled into the ferrite antenna by a kind of transformer action.

Measurements show that the audio voltage output from a particular station increases about three times when the parasitic antenna is used, though the exact improvement depends on the design of the transistor portable. Smaller antennas will work, too. One half the size of the one shown will still improve reception noticeably. A bigger one, on the other hand, gives even better results.

You can expect quite a bit of selectivity from this arrangement, to the point where sideband cutting produces distortion and loss of highs. In that case, detune the parasitic antenna slightly.

Directivity of this system is quite a bit better than that of a ferrite-rod antenna alone. If you mount this assembly on a rotating table, you have a dandy direction finder!

END

*Professor of electrical engineering, Lowell Technological Institute, Lowell, Mass.

The 1960's— Superconductivity's Decade?


By ERIC LESLIE

AS THE 1940's WERE MARKED BY THE transistor; the 50's by discovery of the maser-laser, so may progress in the 1960's be linked with the phenomenon of superconductivity. Already it is suggested that it may be instrumental in "achieving an exotic generation of high-performance computers, microwave radar and communications equipment, magnets, scientific instruments, high-current storage batteries, magnetohydrodynamic power supplies, and propulsion systems for outer space." The fact is that superconductivity is still so new in application that, like the laser in the 1950's, its possible applications are still largely unknown.

Unlike the laser and the transistor, which were absolutely new when brought to public attention, the principles of superconductivity have been known for many years. In 1911, Kammerlingh Onnes, experimenting with the production of extreme cold, discovered that certain metals lost all their resistance when lowered to the temperature of liquid helium (4° K approximately).

Not much use was made of this phenomenon for many years, for the simple reason that the magnetic field set up by any great amount of current through the superconductor would cause the superconductivity to disappear immediately. In recent years new superconductive materials, "hard superconductors", have been found that will work at higher temperatures and higher currents.

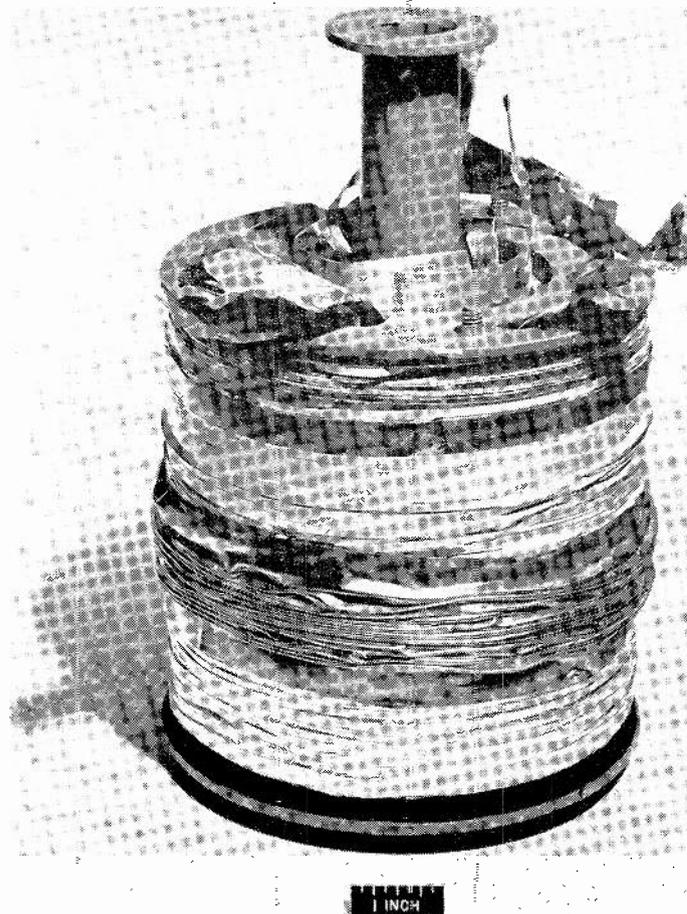A niobium-tin mixture has the greatest ability in this direction, but until recently was so brittle that it could not be made into usable conductors. A number of processes have been devel-



When this superconducting magnet "went normal" (out of superconductivity), fantastic power of magnet plated heat-absorbing copper sheet around center of magnet winding. Magnet still worked after that! Light-colored flat ribbon above and below accordion-pleated copper is niobium-tin alloy winding, which becomes superconducting at low temperatures. Wrinkled flat strips at top of winding form are connecting leads.


oped for using the niobium-tin compound. Possibly the most successful is that of Dr. J. J. Hanak, of RCA Laboratories, who evaporates niobium stannide on a stainless-steel ribbon.

A magnet made of ribbon produced by this process was demonstrated at the David Sarnoff Research Laboratories recently. A field of 107 kilogauss makes it one of the strongest magnets of the world; yet it is only about 6 inches in diameter and uses a fantastically small fraction of the power required by other magnets of similar type.

At the same demonstration, RCA showed a microwave amplifier that uses superconductivity to work in the gigacycle frequency range, a superconductive computer memory and a high-speed electronic switching system usable in computers.

All these devices, of course, depend on operating at extremely low temperatures. Other companies are developing the necessary "refrigerators" which will make it possible to handle such *cryogenic* devices efficiently and economically. END

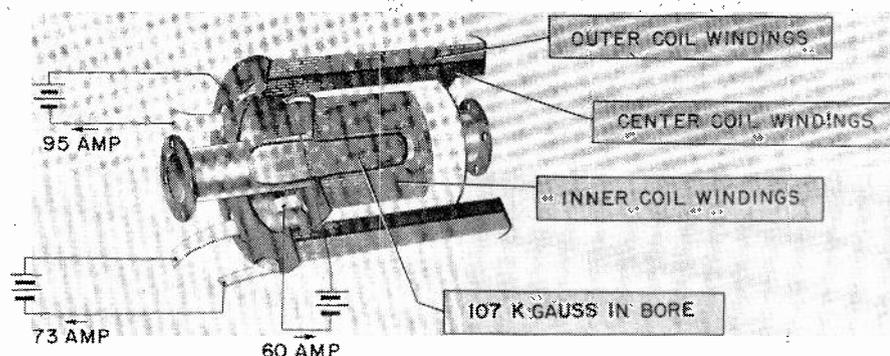
Detail of RCA's mighty supermagnet shown in the photo.



SPECIFICATIONS OF THE RCA 107-KILOGAUSS MAGNET

Weight	26 pounds
Total length Nb ₃ Sn	4,450 meters
Total turns	15,370
Magnetic field in 1 in. bore	107 kilogauss
Magnetic field in 3.4 in. bore	56 kilogauss
Stored energy	20,500 joules
Inductance	6.8 henrys
Magnetic pressure	7,000 psi

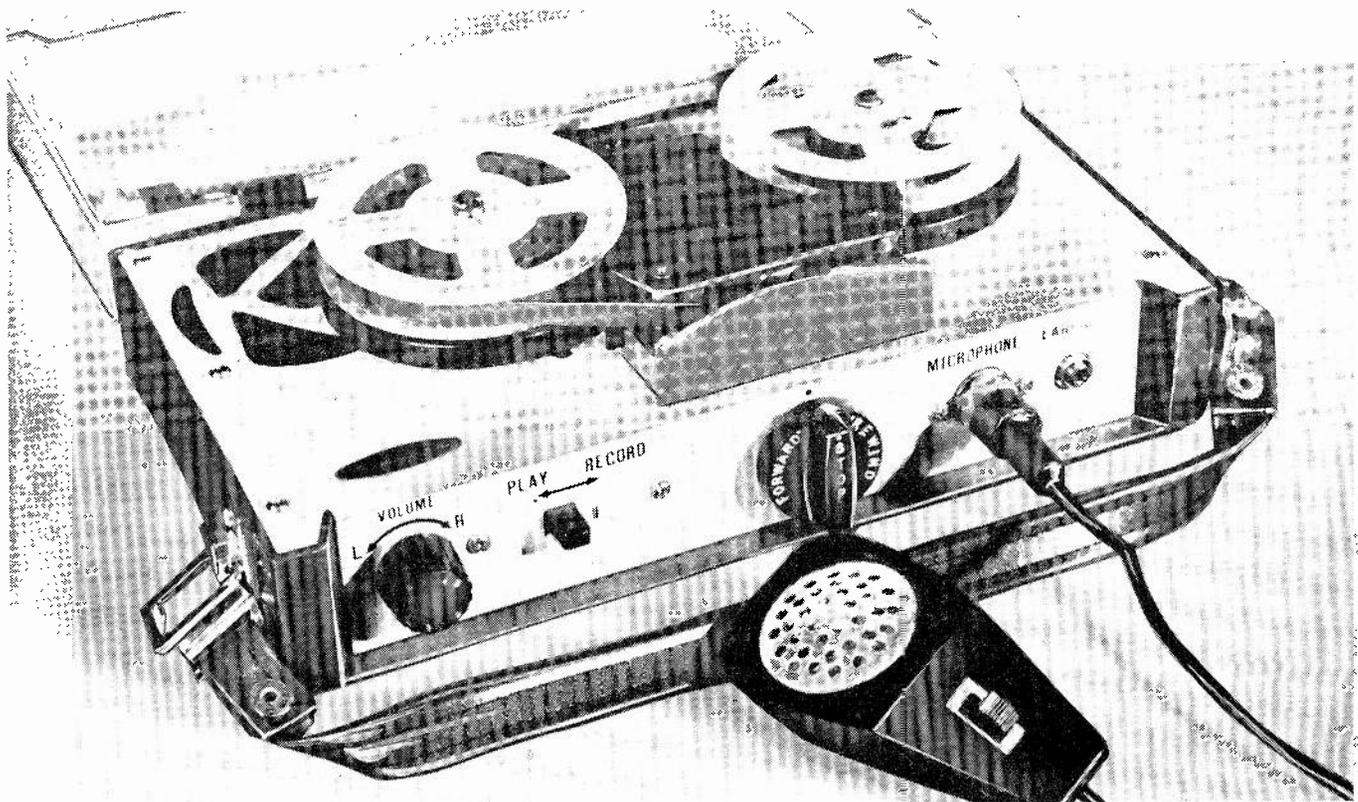HOME-MADE FOOT SWITCH AND PUSH-TO-TALK MIKE TURN LOW-PRICE PORTABLE TAPE RECORDER INTO GOOD DICTATING MACHINE



Daniel R. Schmitz

THE LITTLE DICTATOR

By WILLIAM D. REXROAD

THOSE WHO HAVE HAD AN OPPORTUNITY to use dictating machines have found them tremendous time-savers. Unfortunately, their high cost prevents them from being used more widely by businessmen to write letters, by students for dictating papers and by many others whose valuable time could be saved by speaking into a microphone instead of writing. An inexpensive Japanese tape recorder can be made into a good dictating machine for less than \$25. The

modified recorder has all the features of a much more expensive commercial counterpart.

Just what is a dictating machine? Basically, a recording device—a tape, wire or disc recorder. More than that, it must include a hand-held microphone with a push-to-talk switch, and some provision for transcribing the information from the recorder to paper. That usually consists of an earphone for the secretary, and a foot switch so that the recorder may be stopped and started conveniently while it is being played. The unit should be small and battery-powered so that it may be carried easily on trips or business calls, and used without plugging it into an ac outlet.

Several brands of Japanese-made tape recorders on the market today are small, lightweight, battery-powered, and, most important, inexpensive (\$15 to \$20). Such a recorder is a natural as the foundation of a cheap but versatile dictating machine. Your electronic junkbox will probably supply most of the parts necessary for the modification, which consists of rewiring the motor circuit to provide remote on-off control, adding a switch to the microphone and construct-

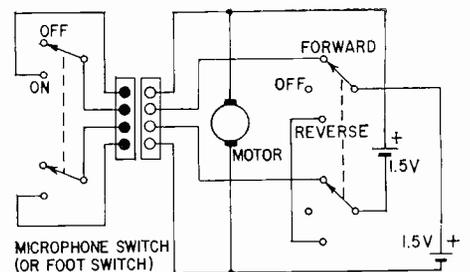


Fig. 2—Remote switch (foot pedal or on mike) starts and stops recorder conveniently.

ing a foot switch. If you have to buy the parts, they will add less than \$5 to the cost of the unit.

Where to begin

Fig. 1 is a diagram of the motor circuit in a typical Japanese tape recorder. In the FORWARD position of the function switch, the two 1.5-volt cells are in parallel to drive the motor, and a 9-volt battery is connected to the electronic circuitry. In the OFF position, none of the batteries are connected. In the REVERSE position, the 1.5-volt cells are connected in series to rewind the tape at a higher speed, and the 9-volt battery is disconnected from the electronics.

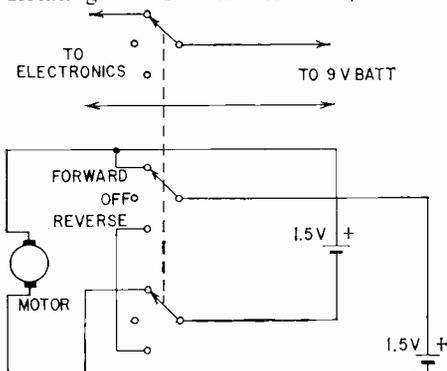


Fig. 1—Typical motor and power switching circuit of miniature portable recorders. Two 1.5-volt cells are paralleled for forward drive, in series for faster rewind.

The motor circuit must be modified to control the motor remotely only when the switch is in the FORWARD position. The remote on-off switch should be completely out of circuit in the STOP (or OFF) and REWIND positions. Fig. 2 shows how the motor circuit is rewired to provide these features. The leads to the FORWARD contacts of the switch are

motor control wires to four others. I used pins 6 and 7 for the microphone leads, and pins 1 through 4 for the motor control wires. This completes the modification of the recorder.

Two methods of remotely controlling the recorder are required: a switch on the microphone for dictating and a foot switch for when the tape is being

tube socket. To keep the wires from breaking off the plug, and to provide a means of gripping it, it was encapsulated in epoxy resin. I made a mold which consisted simply of concentric holes drilled in a block of plastic (Fig. 4). I filled the mold with epoxy resin (the type used in automobile repair kits will do nicely) and allowed it to cure.

A microphone with an on-off switch may be obtained in several ways: you can buy a commercial unit, or tape a switch to the microphone provided with the recorder. I bought an inexpensive crystal microphone cartridge and slide switch and molded them into an integral

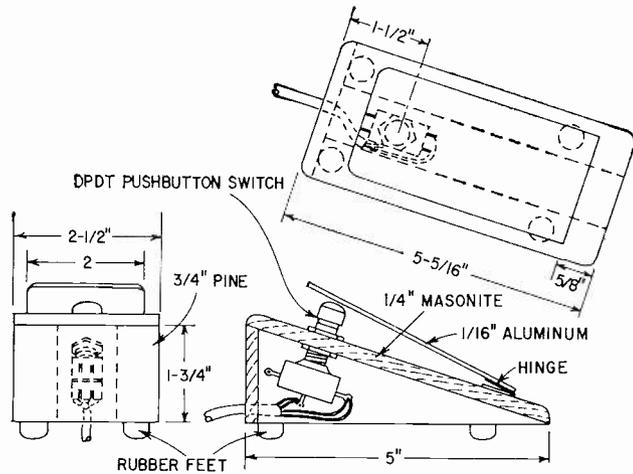


Fig. 3—Dimensions and details of the foot-pedal switch. It can be modified to suit any similar switch and whatever parts you have on hand.

broken and brought to a connector mounted on the recorder. A dpst switch in series with these leads provides remote on-off control when the function switch is in FORWARD, and does not affect the control circuit in OFF or REWIND.

Any small connector with at least six pins can be used to terminate the motor control wires. I used an ordinary seven-pin miniature tube socket installed in the hole formerly occupied by the microphone jack. The original hole is just the size for the screw of a 5/8-inch chassis punch. If you don't have such a punch, you can file or drill out the hole to 5/8-inch diameter. Regardless of the kind of connector you use and the size hole you make—or how you make it—protect the parts in the recorder from metal chips and filings.

After installing the connector, solder the leads from the original microphone jack to two of the pins, and the

transcribed. In both cases, a two-pole single-throw (dpst) switch is used.

The foot switch construction is shown in Fig. 3. A momentary-contact pushbutton switch is mounted in a housing so that it can be operated conveniently by the foot control. The housing is constructed of scrap pieces of pine and 1/4-inch Masonite. A small piece of sheet aluminum, which acts as a foot pedal, is attached to the housing with a small hinge, as shown in the illustration. Rubber feet prevent the foot switch from slipping.

The cable from the foot switch should be at least 5 feet long. It consists of four wires, no smaller than No. 26, enclosed in a piece of sleeving, which improves the appearance of the cable. The free end terminates in a plug which mates it with the connector on the recording unit. I used a seven-pin Cinch-Jones plug which mates with a seven-pin

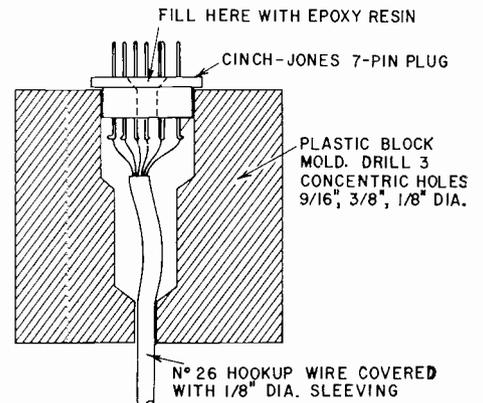


Fig. 4—Author's mold for plug "handle". Wide sleeve from phone jacks like Mallory 75 or 76 can also be adapted.

microphone unit. Fig. 5 shows the details of the unit I made. The mold was constructed by soldering pieces of thin sheet copper together. The dpst slide switch and mike cartridge were mounted in it, the cable attached, and the mold was filled with epoxy resin and allowed to cure. The opposite end of the cable was terminated with a plug identical to that used on the foot switch.


If it seems like too much trouble to mold plugs and microphone housings, a different type of connector on the recorder will do every bit as well. For instance, a six-terminal Jones connector (type S306AB and two mating plugs (Jones P306CCT) will solve the cable problem adequately. You can mount the slide switch on the microphone in other ways, too.


Using the Little Dictator

To use the dictating machine, simply plug in the microphone unit, turn the

The Little Dictator set up for transcribing a recorded tape. Earpiece facilitates transcription in noisy locations.

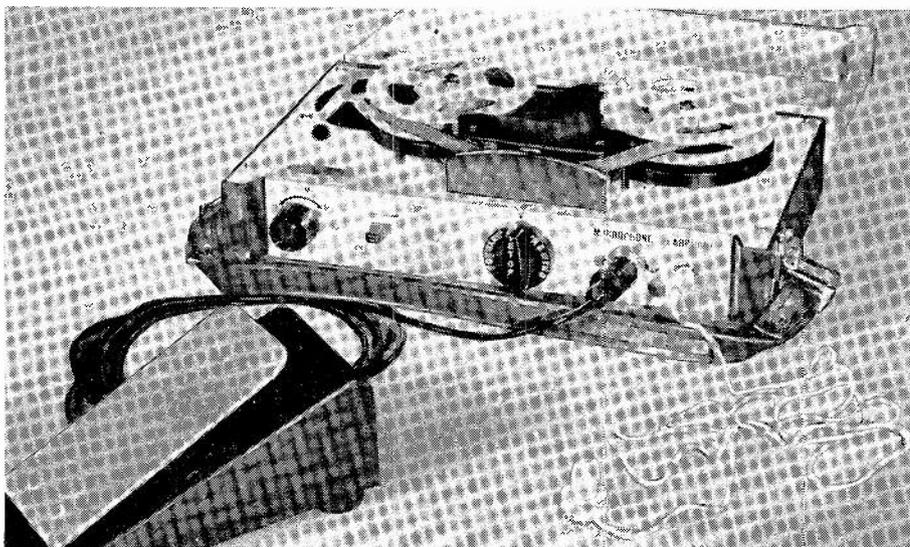function switch of the recorder to FORWARD and the PLAY-RECORD switch to RECORD. Turn the mike switch ON to dictate, OFF when not talking. One precaution: if you wish to back up and review what you have said, be sure the PLAY-RECORD switch is in the PLAY position before rewinding the tape. If you don't do this, all that you have recorded will



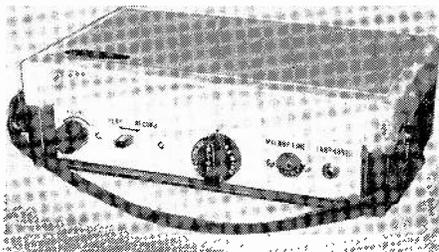

Converted recorder is no bigger than original machine; foot switch doesn't have to go along, since transcription will be done at home or office. Machine carries easily in briefcase or suitcase.

be erased.

When transcribing, the typist disconnects the microphone and connects the foot switch. The foot switch is then depressed and released alternately, allowing the information on tape to be transcribed a few words at a time until the entire tape has been reproduced. No unusual talents other than the ability to type are required of the person doing the transcribing. It is convenient for the transcriber to use the ear plug rather than to listen to the tape via the speaker; surrounding noises are less distracting.

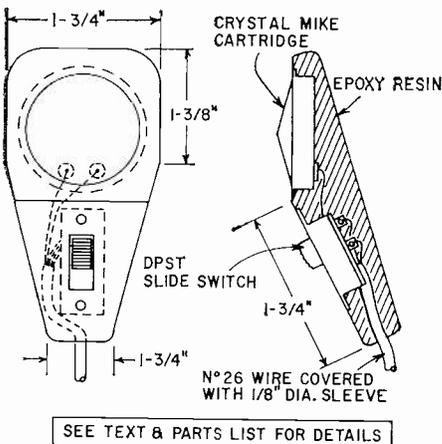



Fig. 5—Microphone unit is inexpensive crystal mike element with dpst switch, molded (or otherwise fastened) together. Depending on input impedance of recorder's amplifier, crystal mike cartridge may have to be wired with single-conductor flexible shielded cable.

- Tape recorder
 1 dpst pushbutton switch
 1 dpst slide switch
 1 crystal microphone cartridge (Burstein-Applebee 17B265 or equivalent)
 Connectors (see text)
 Mountings and hardware (see text)


Because tape speeds are not closely controlled on these little machines, you must usually play a tape on the same machine you recorded it on. Sometimes you can play a tape on another machine of the same make and model.

Once you overcome a natural shyness toward writing letters or reports by microphone rather than with a pencil or pen, the dictating machine becomes a valuable time-saver, and you will find yourself using it everywhere! END

Adapter For Mike Connectors

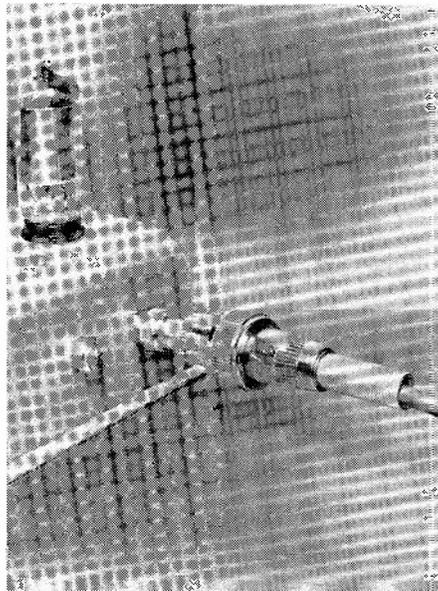


The diagram illustrates the simple construction of the adapter very clearly. Remove the setscrews and pull out the cord-protecting springs in both connectors. Saw a piece about 1/4 inch long off the end of the large connector, then file down the barrel of the miniature connector so it is a snug fit inside the large connector. A short length of hookup wire, running lengthwise inside the adapter, connects the center eyelets of both connectors. Now sweat-solder the barrels of both connectors together so they can't slip or turn.

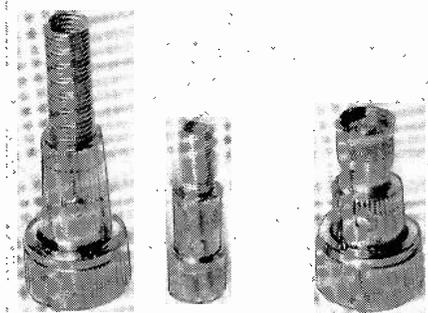

For many years, the well known Amphenol type mike connectors have been standard equipment on mike cables and audio amplifiers. Nowadays the miniature mike connectors promise to become just as popular for all kinds of transistor and miniature electronic apparatus. With both sizes of mike connectors in use, experimenters, audiophiles, service technicians and research labs need an adapter that will quickly and easily join the standard and miniature mike connectors.

To make such an adapter, you will need one Amphenol 75-MC1F mike connector or equivalent, one Switchcraft 5501F Mini-Con miniature mike connector and a short length of insulated hookup wire.

The adapter is is easy to use. Take the case of a mike cable with an Amphenol 75-MC1F or equivalent standard female connector and an amplifier with a miniature mike connector. Simply screw the small end of the adapter onto the panel connector. To couple the female connectors, unscrew the coupling ring from the connector on the cable and slide it back out of the way. Screw the cable connector onto the large end of the adapter to complete the hook-up. —Art Trauffer

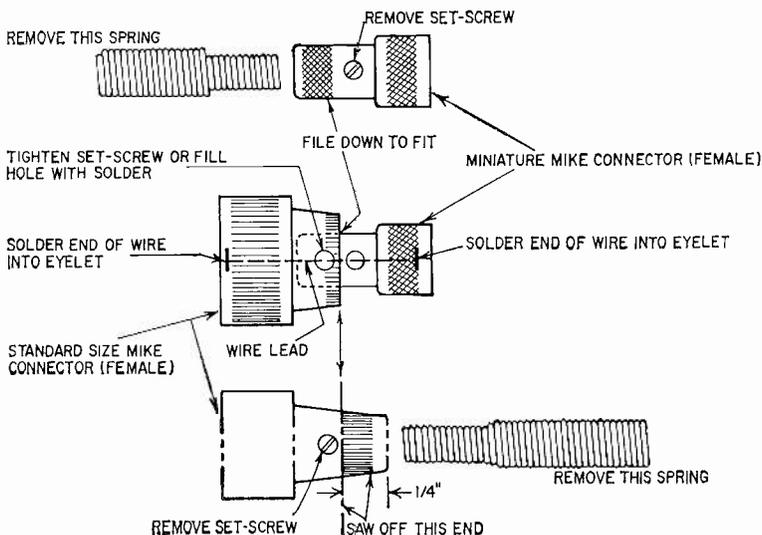


By **CARL HENRY**

THOSE STAR ACTORS LIKE THE TRANSISTOR and crystal diode usually hog the spotlight among the semiconductors. But several less publicized semiconductor devices are important in electronics today. Perhaps the oldest in common use is the thermistor, developed in its present form by Bell Telephone Labs in the early 1940s. Thermistors, made by sintering a ceramic material with a metallic oxide, can have a resistance variation with temperature of over ten million to one.

Why are thermistors important? Most items used in electronics have a positive temperature coefficient (their resistance increases with temperature). Since thermistors have a *negative* coefficient, they are widely used to compensate for the effects of temperature changes in circuitry. The photographs illustrate several types of thermistors. The wafers, discs and washers are usable to about 300°F., while the bead types can be used to above 600°.

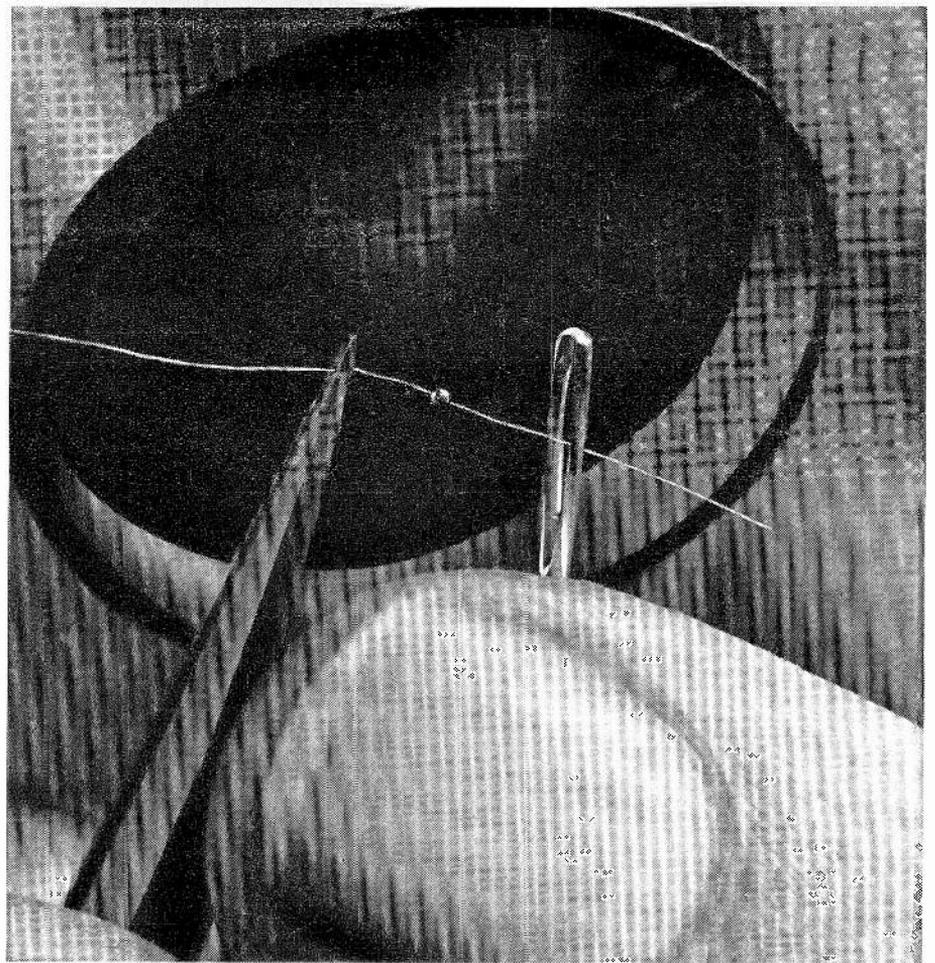Thermistors can be used in two ways. First, they can be placed in an ohmmeter circuit. The temperature of the thermistor's surroundings will determine its resistance. Fig. 1-a shows this




Gulton Industries

Tiny bead thermistor is .01 inch in diameter.

Watch Those Shifty Resistors!

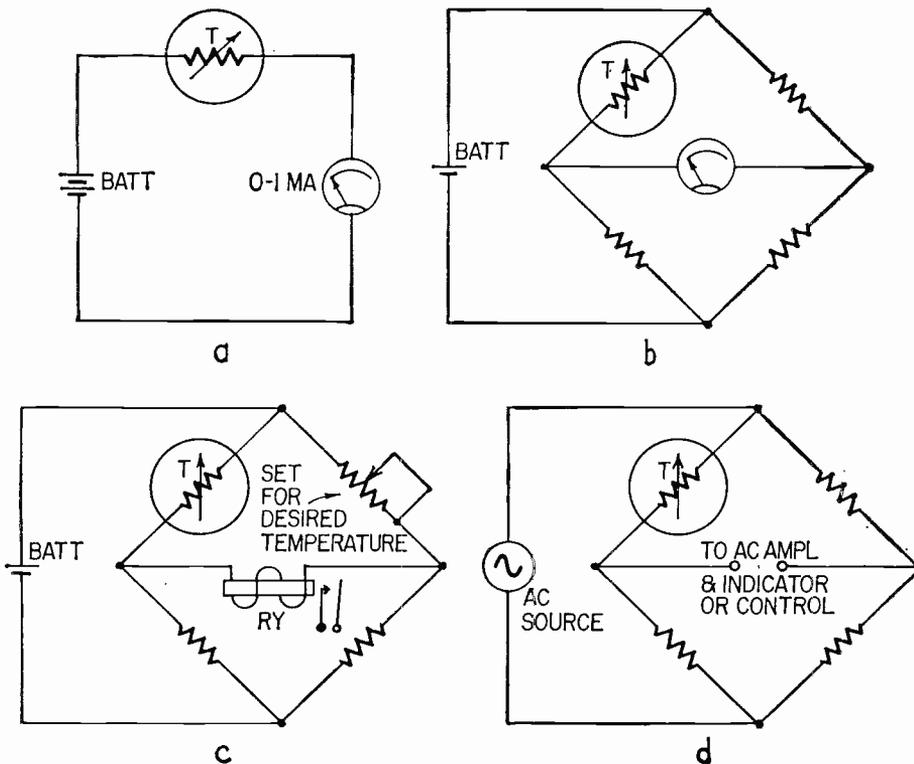Most resistors hold their values over a wide range of circumstances. But some are designed to change resistance



type of circuit, which can be used to measure temperature. In a more sophisticated version (Fig. 1-b), a bridge is used to indicate temperature more accurately. Figs. 1-c and 1-d illustrate applications of these circuits. Fig. 1-c is a crude control circuit to keep the temperature of an electric heater within a certain range. More accurate than a thermostat type of control, it is not as accurate as the circuit in 1-d, which will keep a chemical solution at a precise temperature.

In the second type of circuit, the thermistor is allowed to draw enough current to raise its internal temperature to 200° or 300°F. It is then placed in contact with the variable to be controlled

Fig. 1—Thermistor applications. In Fig. 1-a, direct temperature measurement; 1-b shows a bridge circuit with increased sensitivity. In (c), a control circuit for heaters, fans, etc. Thermistor is mounted near heating or cooling element. Fig. 1-d shows a potentially very sensitive temperature-change detector.

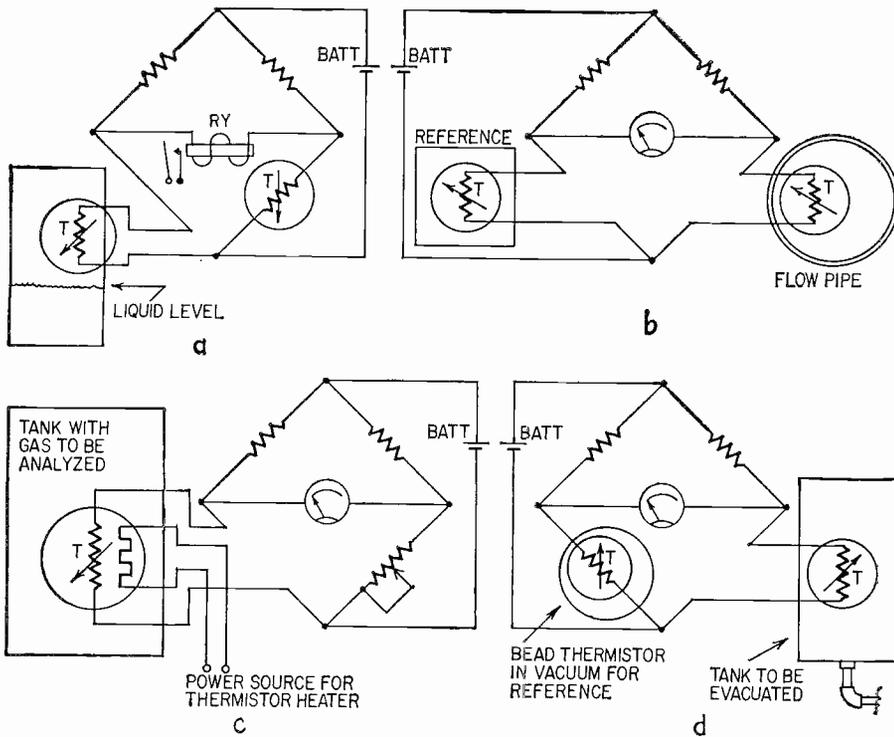


Fig. 2-a—Liquid-level control with thermistor. Relay controls tank valve. (b)—Thermistor flow meter. Reference is mounted in brass block. System detects flow rates as low as .001 ml/minute. (c)—gas analysis by registering change in specific heat of gas. (d)—Measuring vacuum; rate of heating and cooling will be different for the two thermistors until surrounding gas densities (degrees of vacuum) are equal.

or measured. In this manner it is possible to measure the liquid level in a tank, as in Fig. 2-a. The thermistor is placed at the point in the tank where the level is to be maintained. Since its internal temperature is high, its resistance is low. If the liquid in the tank rises, covering and

cooling the thermistor, the resistance will increase. This increase can turn off a relay or move an indicator. We can analyze the content of a gas, measure the flow of a liquid or a gas, and measure the degree of a vacuum, even down to 50 microns, in the same way. Fig. 2 illustrates the methods schematically.

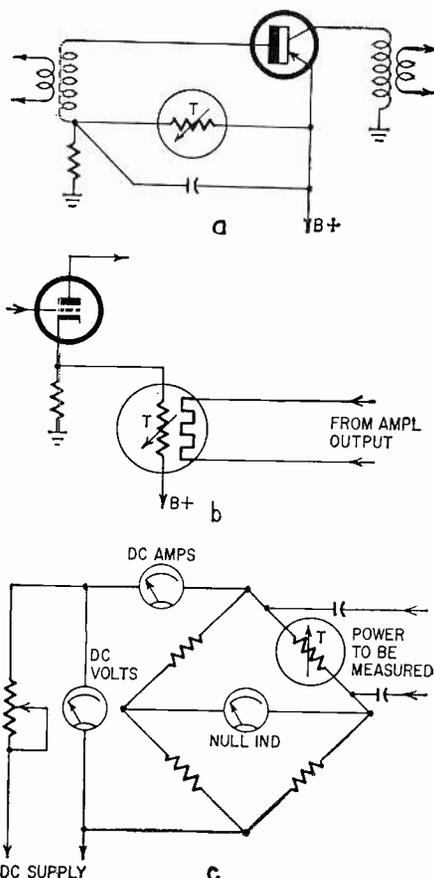


Fig. 3—Electronic applications for thermistors. In Fig. 3-a, thermistor "holds down" transistor stage with changes in temperature. As temperature rises, transistor tends to conduct more heavily, but thermistor, whose resistance drops with increasing temperature, tends to shunt away more and more bias, maintaining transistor's conduction at lower value. In (b), heating effect of audio amplifier output through thermistor controls bias on voltage amplifier, holding output approximately constant (volume compression). Expansion is also possible. In (c), thermistor bridge measures even high-frequency rf with noncritical dc instruments. Dc is applied, lowering thermistor's resistance enough to balance bridge (normally unbalanced). Applied ac unbalances bridge; dc power is then reduced to rebalance it. Difference in dc power (as read on meters) is equal to applied ac power.

The thermistor can also be used to give time delays of up to several minutes. For instance, a thermistor in series with a relay will not allow the relay to draw enough current to close until the thermistor has heated enough for its resistance to drop. The delay can be controlled by choosing thermistors of different characteristics.

Surge suppression is also possible with the proper thermistor. Also, several bulbs can be operated in series and when one bulb burns out, the others can continue at normal brightness. Merely put the proper thermistor across each bulb. When the bulb filament opens, the thermistor heats, its resistance drops and the circuit functions normally again.

Some bead thermistors have an external heater attached. By placing such a thermistor in the grid circuit of a vacuum tube, the gain of the tube may be varied

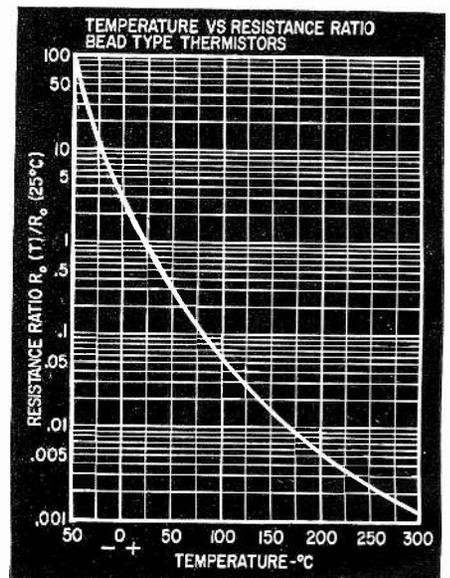


Fig. 4—Temperature/resistance characteristic of typical bead thermistor.

remotely simply by controlling the current in the external heater. The control carries only dc and is not critical; it can be located miles away without affecting the amplifier.

How is it used?

Fig. 3 shows several typical electronic applications. In 3-a, the thermistor is used to temperature-compensate a type of electronic circuit that is especially important in dc amplifiers and in oscillators. Transistors, in particular power transistors, change operating characteristics with changes in ambient temperature. Thermistors can be used to bias such circuits. With careful design, the same operating point can be maintained through a wide variation of ambient temperatures.

Fig. 3-b illustrates a method of stabilizing the output of an amplifier with a thermistor. Its resistance can be made to vary with the output in such a way as


to increase the bias or reduce the feedback if the output increases. Either a bead thermistor or an external-heater type is suitable. The major advantage of this kind of control is the wide range of frequency and amplitude it covers.

Since the thermistor decreases in resistance with heat, which in turn depends on the current through it, it can be used as a voltage regulator. Connect the same as a Zener diode or gas regulator—in parallel with the load. As voltage increases, the thermistor's resistance decreases and the current through it increases, restoring the original voltage. The main difference between this circuit and a conventional regulator is the time lag in the resistance change.

This is true of all the circuits mentioned so far. The resistance change of a thermistor is caused by a heating effect, which of course takes time. This may be unimportant in dc control and audio circuits, but severely limits the use of thermistors as control elements as the frequency increases. In general, the smaller the thermistor, the faster the response time.

Thermistors can be used in some circuits at higher frequencies, however. Fig. 3-c shows one such circuit. Here it is being used to measure power. The frequency can be anything from low ac to microwaves. This is because we are measuring the *heating effect* of the power, and not the power itself. We can compare the heating effect of this power with the heating effect of dc, or as in 3-c we can use dc to rebalance the bridge that the high-frequency power has unbalanced.

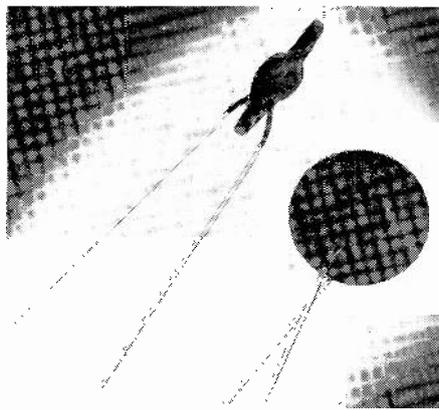Using thermistors at audio frequencies makes possible the simplest volume compressor-expander circuit. By oper-




Disc wafer thermistors.

ating the thermistor on the negative-temperature-coefficient section of its characteristic curve (Fig. 4), it acts as a limiter. If the circuit is properly designed, there will be no waveform distortion.

Varistors

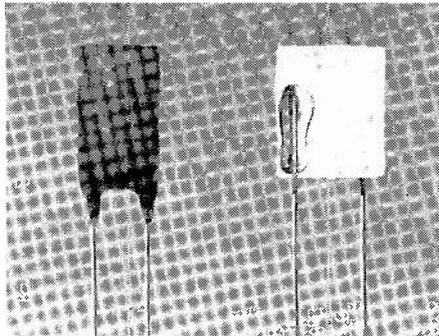Running thermistors a close second in importance is a component used in telephone circuits for years and years, but only now becoming widely used in electronics: the *varistor*, a resistor whose value varies with voltage. Fig. 5 illustrates two typical telephone type varistors. As the voltage across one increases,



Rectangular wafer thermistors.

its resistance decreases. Fig. 5 also shows a typical varistor application, an intercom speaker circuit sometimes known as a "talkback" speaker. It is desirable in this type of circuit not to attenuate the low-level signal from the speaker to the amplifier. However, the high-level signal from the amplifier to the speaker must be controlled, especially if the speaker is used in an office.

This paradox is resolved by using a varistor. When the transmission is from the speaker to the input of the amplifier, the voltage is very low, and the varistor acts as a high resistance. This effectively removes the T-pad from the circuit. When the transmission is from the output of the amplifier to the speaker, the voltage is high, the resistance of the varistor is low, and the T-pad controls the volume of the speaker.

From this you can see that the varistor will function as an audio limiter. It operates much faster than a thermistor and, with the proper circuit design, the output is undistorted.

A second type of varistor is shown in Fig. 6. Commercially this is known as a contact protector. Fig. 6 also shows a typical circuit, with the varistors protecting the contacts on a relay. The theory is that the high voltage generated at the relay contacts causes the varistors to conduct and prevent arcing. Normally the voltage across the contacts is not great enough to cause the varistor to conduct. You can visualize this better if you think of the varistor as two silicon rectifiers back to back. Ordinarily they will not conduct, because the voltage across them is too low. When a high voltage is generated by the relay contacts, the inverse voltage of the diodes is exceeded, and they short out the spark.

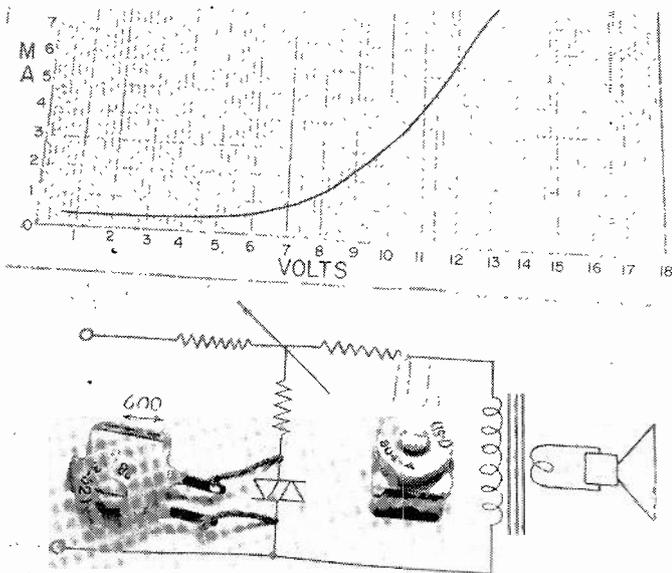


Fig. 5—Two Western Electric telephone type varistors, one of them "connected" to a diagram showing a typical application (see text). Above, general voltage characteristic of varistors.


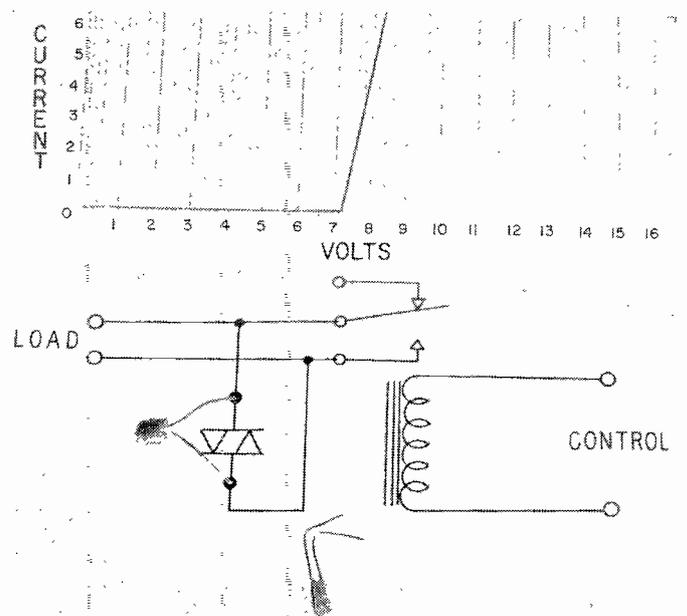


Fig. 6—Varistor as contact protector, with circuit and characteristic curve.

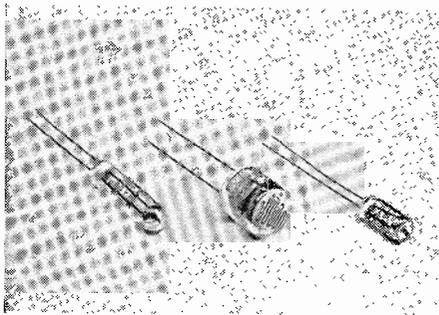

Clairex Corp.

Three typical photoconductive cells.

Photoconductive cells

The last of our "shifty" resistors is the photoconductive cell—a resistor that varies with light.

Two types of cells are in production now, cadmium sulfide and cadmium selenide. The selenide cell is faster-operating, peaks in the near infrared (690 millimicrons) and has a greater light-to-dark resistance ratio. The sulfide cell peaks near the same point as the human eye (520 $m\mu$) and has a better temperature characteristic. Two other types, the cadmium telluride cell, which peaks

plur applications. The photoconductive cell is exactly what the name implies, a resistor that shifts or decreases in value with light level. Fig. 7-a shows a simple circuit to measure light. A similar circuit is being used in several new photographic exposure meters on the market. A battery, the photocell and a meter are connected in series. As the light level increases, the resistance of the cell decreases, and the meter indicates more current. This type of circuit can be made so sensitive that you have to carry a flashlight to read the meter!

Lunar cells?

Fig. 7-b shows an extremely sensitive relay control circuit. With the transistor to amplify the already high sensitivity of the photocell, it is possible to operate the relay on moonlight. The photocell supplies a biasing current to the transistor. With an increase in light, the biasing current increases to the point where the collector current operates the relay.

Fig. 7-c shows the simple circuit needed to use these photocells for photometry. Such a circuit is accurate and sensitive enough to measure the blood pressure change of animals or humans by light transmitted through the finger or ear lobe. It may make the conventional sphygmomanometer obsolete.

Fig. 8 illustrates a typical conductive cell characteristic.

At this writing there are no accepted standards on photoconductors, but with increasing use this will undoubtedly be corrected. END

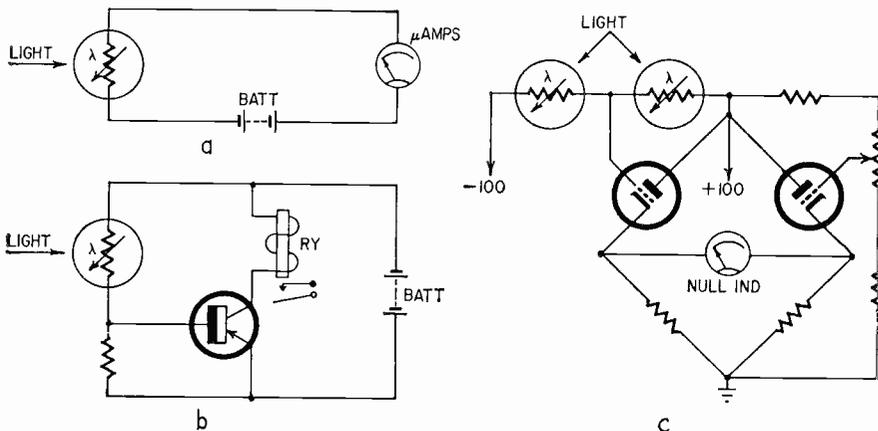


Fig. 7-a—Direct measurement of light—circuit used in many photographic exposure meters. (b) Greater sensitivity is possible with stage of amplification; cell controls transistor's bias. (c)—A comparison photometer, to compare brightness or luminosity of two objects or sources.

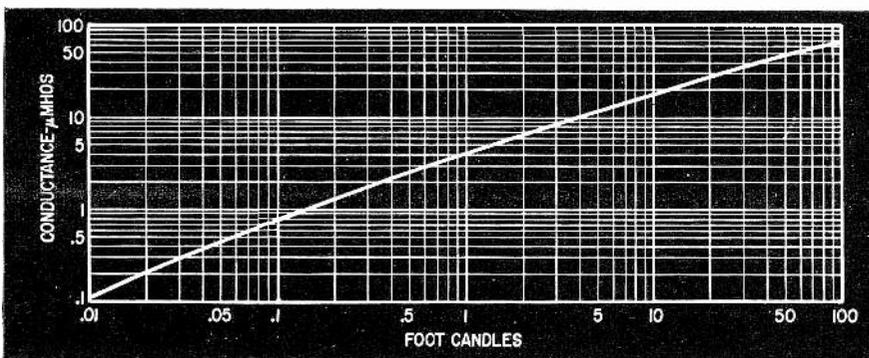


Fig. 8—Typical photoconductive cell characteristic.

Thyrite resistors

A rather sophisticated type of varistor is the *thyrite* resistor. It is constructed of silicon carbide, sintered in a ceramic material. Thyrite is a kind of super varistor. Its resistance changes over a range in the order of 100,000 to 1 for voltage changes of 1,000 to 1. A typical use for this "shifty" resistor would be in a pulsed sounding or echo circuit. In some of these circuits a pulse of 1,000 volts is transmitted to a transducer. The echo receiver must be connected to the transducer. A thyrite resistor across the receiver input prevents the transmitted pulse from damaging the sensitive receiver.

around 800 $m\mu$, and the zinc sulfide cell, which peaks at about 400 $m\mu$, will extend the use of the cell into the ultraviolet.

Both the cadmium sulfide and cadmium selenide are about 1,000 times more sensitive than the older selenium photovoltaic cells. It is also claimed that the photoconductive cell is 1,000,000 times more sensitive than the photoemissive cell (phototube). Photoelectric exposure meters for photographers, auto headlight dimmers (doing away with the complicated photomultiplier circuits) and anemometers are but a few of the applications of these cells.

Fig. 7 illustrates some of the sim-

Computer Solves Problem With 13,542 Variables

A record is claimed by Simeon E. Gordon, mathematician at IIT Communications Systems, Inc., Paramus, N. J., for the solution of a problem that consisted of finding the shortest message route to be followed through a network of 62 switching points.


The difficulty was that the messages had to be routed over the network without interference. The problem, Gordon explained, was similar to determining the shortest route a motorist could follow over a road network to avoid traffic delays at 62 intersections.

The problem, which involved 2,002 mathematical equations, as well as more than 13,000 variables, required approximately 6½ hours on the computer, and involved a technique known to computer mathematicians as linear programming.

It took Gordon more than a year of spare-time work to develop the program which made it possible for the computer to solve the record problem. It is the first time, Gordon believes, that a computer has been utilized to solve a problem of more than 1,023 equations.

WHAT'S NEW

MAGNETIC-FIELD-FREE ROOM was built to test space-bound instruments. Earth's magnetic field and other stray fields played havoc in adjusting delicate instruments for work in outer space. Marshall Laboratories, Torrance, Calif., manufactures the enclosures from Allegheny Ludlum's Mumetal and Moly Permalloy alloys, both high-permeability metals. The "fluxroom" must be heat-treated for maximum effectiveness only after assembly, since alloys are strain-sensitive and lose their properties under mechanical stress. Room is approximately 8 feet each way, and mounted on turntable so it can rotate 360°.

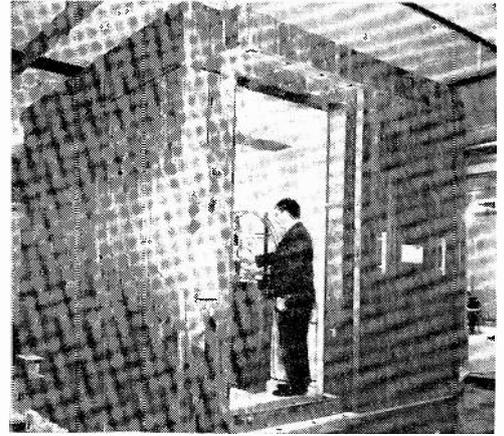

EDUCATIONAL TALKING TYPEWRITER teaches 3- to 8-year-olds to read and type. Dubbed "SLATE" (Stimulated Learning by Automated Typewriter Environment), Westinghouse-developed system lets child hear what he types. In "letter mode", pupil strikes key, sees letter printed and immediately hears it spoken. This teaches letter and punctuation-mark recognition. In "word mode", all keys are inactive except those that spell out words chosen by teacher. Machine responds to those only when pressed in correct sequence to spell word. Letters are pronounced one by one, then whole word is spoken. "Sentence mode" requires correct spelling of entire sentence. Unit can be programmed to work in any language.


INFRARED-AIMED LASER RADAR tracks and ranges noncooperative airborne targets with terrific accuracy, according to Electro-Optics Group of Sperry Rand Corp. System consists of passive infrared tracker, laser transmitter and photomultiplier receiver. It can put laser beam on target to within .01°. Transmitter is pulsed ruby laser with 375-kw peak output; tracker is indium antimonide photodiode cooled in liquid nitrogen. System, hailed as 10 times as accurate as microwave trackers, permits narrower, more intense laser beams for higher signal-to-noise ratios.



A LAMP? YES. A LOUDSPEAKER? YES. Decorative lampshade is 360° cylindrical electrostatic speaker for frequencies above about 400 cycles. Bass is reproduced by front-loaded cone type electrodynamic speaker in base. Acoustica Associates, Inc., manufacturer, quotes total frequency range as better than 40 to 25,000 cycles. Lampshade is translucent; less than 1/4 inch thick. System connects to ac wall outlet and to any hi-fi amplifier.

TRANSISTORS & VOLTAGE MEASUREMENTS

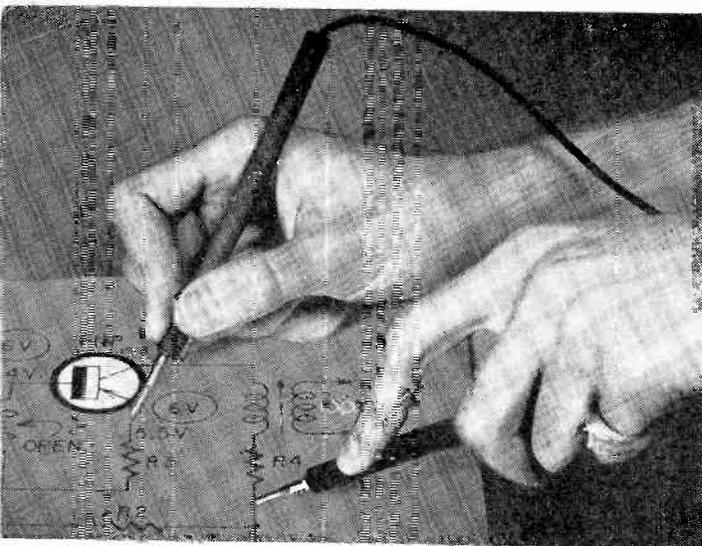Wrong voltages are good clues to transistor and circuit defects. Not the same as tubes, though By DAVID R. ANDERSON



HOW DOES AN OPEN BASE RESISTOR affect collector voltage? Can you tell what's open in a transistor circuit by what's happened to the element voltages?

When you work with tubes, you know that, if the plate voltage is the same as the supply voltage, the cathode resistor is almost certainly open. Why not learn the same diagnostics for transistors?

Look at Fig. 1, a basic n-p-n transistor circuit. Here, the collector voltage will always be the most positive, while the emitter voltage will be the most negative. The base will be biased so that it is slightly positive with respect to the emitter, and negative with respect to the collector.

The same relationship will hold true for the p-n-p transistor except that the polarity of the voltages will be reversed.

One battery supply

For simplicity, two batteries are shown in Fig. 1. Most practical circuits use an arrangement like that in Fig. 2 to obtain the operating voltages from a single battery.

In this arrangement, the collector is connected to one end of the battery and the emitter to the other end. The base is forward-biased with respect to the emitter by tapping off a part of the

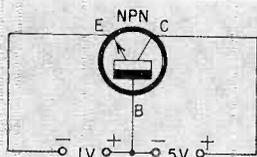


Fig. 1—Voltage relationships in an n-p-n transistor. With p-n-p types, polarity is just reversed.

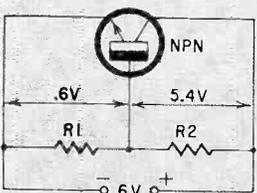


Fig. 2—Most practical circuits use single battery for all biasing.

battery voltage via R1 and R2. Polarity depends on whether an n-p-n or p-n-p transistor is being used.

Most technicians find it easiest to measure voltages from ground to the various transistor elements. This is quite acceptable. However, when a power supply like the one in Fig. 2 is used, either end of the battery may be grounded.

Fig. 3-a shows an n-p-n transistor circuit with the negative side of the battery grounded. Fig. 3-b shows the same circuit with the positive side grounded. The voltages measured at the various elements differ not only in value, but also in polarity, depending on which end of the battery is grounded.

For instance, the collector voltage in Fig. 3-a measures +5.5 from ground. The collector voltage in Fig. 3-b measures -0.5 from ground. So be sure to note which end of the battery is grounded before you begin measuring.

Open base circuit

Fig. 4-a shows the effect an open base circuit has on the operating voltages of an n-p-n transistor. The un-circled values show the normal operating voltages, while the circled values show the voltages measured from ground with the defect.

The collector voltage has increased. This happens because, with the base circuit open, the base-to-emitter bias disappears and the collector circuit stops conducting. When the collector is not conducting, no current flows through R4 and there is no voltage drop across it. As a result, the collector voltage rises to the battery voltage.

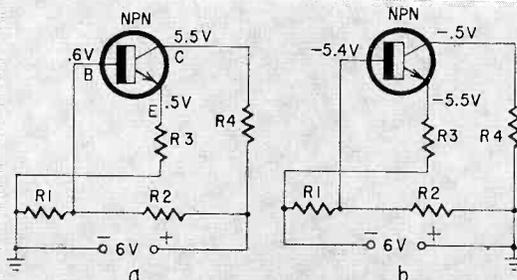


Fig. 3—Watch first to see which end of the battery is up! Magnitude and polarity of readings depend on where ground is.

Since the collector has stopped conducting, there is no appreciable current flow through R3 and no voltage drop across it, either. Thus, the emitter voltage falls to zero.

The base voltage becomes zero because it is no longer connected to its operating voltage.

In the p-n-p circuit of Fig. 4-b, an open base resistor has quite a different effect on the operating voltages. The collector voltage has dropped to zero, and the base and emitter voltages have risen to the full battery voltage.

This is because the battery polarity has been reversed, compared to the n-p-n circuit of Fig. 4-a, to supply the proper operating voltages for a p-n-p transistor. As a result, when you measure between collector and ground, you are reading the drop across R4. With the base circuit open, there is no drop across this resistor because there is no collector current, and you measure zero voltage.

When you put the probes from ground to emitter, the battery voltage,

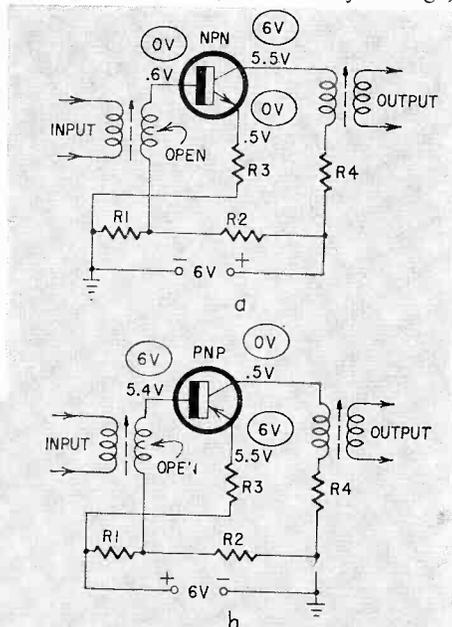


Fig. 4—Open base circuit with (a) n-p-n transistor; (b) p-n-p. Circled voltages are "defective". Voltages here are just examples; exact values depend on battery, transistor type and operation.

Making Estimates Worries Many Servicicers

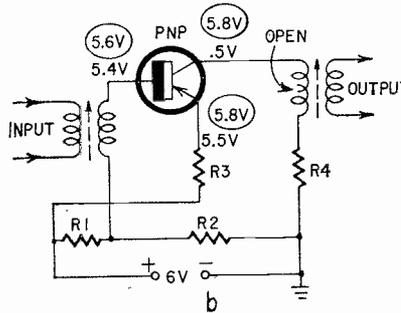
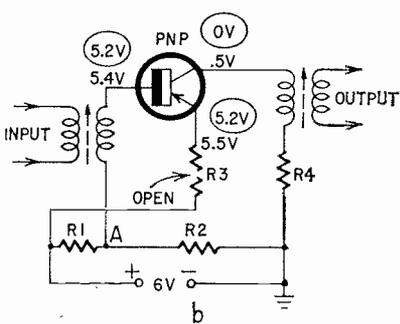
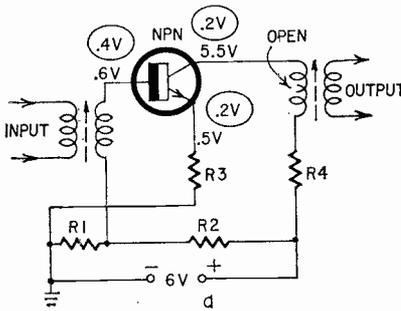
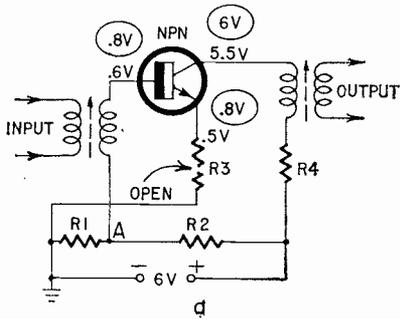


Fig. 5—Open emitter in (a) n-p-n circuit; (b) p-n-p.

less the drop across R3, is being measured. But since the collector circuit has stopped conducting, there is no drop across R3. As a result, you find the full battery voltage at the emitter.

The base circuit is open and no longer connected to its operating voltage, yet it measures the same voltage as the emitter voltage. This happens because a transistor has a low internal resistance between base and emitter, so the base rises to the emitter voltage.

Open emitter circuit

Fig. 5-a shows the effect of an open emitter circuit. The collector stops conducting and there is no current in the collector circuit. This results in no voltage drop across R4. With no drop across R4, the full battery voltage appears at the collector.

The open emitter circuit also stops the slight current flow in the base-emitter circuit. When this current flow is stopped, the voltage at point A rises slightly, causing the base voltage to rise also (go more positive).

The open emitter, because of the low internal resistance of the transistor, then assumes the base voltage.

In Fig. 5-b a p-n-p transistor with

Fig. 6—Open collector circuit with (a) n-p-n transistor; (b) p-n-p.

an open emitter circuit is shown. Here, the collector voltage is zero because there is no current flow in the collector circuit, and no voltage drop across R4.

The base voltage in this case has *dropped* slightly. As with the n-p-n transistor, a slight base-to-emitter current flows through R1. When the emitter-base circuit is open, this current flow stops and the voltage at point A drops slightly (goes less positive). This causes the base voltage to drop. The open emitter then assumes the base voltage.

Open collector circuit

Fig. 6 shows the effect an open collector circuit will have on the normal operating voltages of a transistor. In both the n-p-n and the p-n-p circuits, the emitter and collector voltages have become equal. The base voltage has changed very little.

Since the collector circuit is open, no current flows through it and the collector voltage rises or drops to the same voltage as the emitter.

Because of the large change in the collector voltage, and only a small change in emitter and base voltages, the defect is clearly in the collector circuit.

END

WHAT HAPPENS TO VOLTAGES WHEN ELEMENTS ARE OPEN

transistor type	open emitter		open base		open collector	
n-p-n	emitter	↑	emitter	0	emitter	↓
	base	↑	base	0	base	↓
	collector	↑	collector	↑	collector	↓
p-n-p	emitter	↓	emitter	↑	emitter	↑
	base	↓	base	↑	base	↑
	collector	0	collector	0	collector	↑

↑ = higher-than-normal voltage ↓ = lower-than-normal voltage 0 = zero voltage
 "Higher-than-normal" means voltage has risen toward potential of ungrounded battery terminal; "Lower-than-normal", voltage has fallen toward 0 (potential of grounded battery terminal with respect to ground).

"I ONLY WANT YOU TO LOOK AT MY SET and tell me what it will cost to fix it. I think it's just a tube."

So begins a thoughtful article in the Seattle TSA *Service News*. "If you give the customer an off-hand guesstimate," continues the article, "too often you find that the customer thinks you have given him a firm bid for a complete overhaul with an unlimited guarantee."

On the other hand, writes the author, if you take the time to pull the set apart, troubleshoot it and ultimately come up with some genuine but not obvious troubles, the customer may very well take his work elsewhere, and tell you that it's outrageous to charge him "just to look at it."

One suggested way out is that the customer isn't really interested, often, in knowing *exactly* what the charge will be. More likely, he wants to know whether it is going to \$10 or \$50 or \$100, so he can budget the coming weeks accordingly.

Tell the customer that you're more interested in getting the set fixed *right* than in giving him an exact figure in advance, one you'll feel bound to meet even at the sacrifice of some necessary work to the set.

If the set isn't worth repairing, in your opinion, tell the customer so. If you realize it needs a new picture tube, tell him. Remember, too, that recent sets usually develop just one trouble at a time. Older sets are likely to give way in several spots, and to have some weak or about-to-break-down parts as well.

If the customer wants a rockbottom price just to get the set going, make him understand that you will not guarantee it. The author advises staying away from that kind of repair altogether.


The writer, with a deliciously nervy sense of humor, has decided to fight back. A customer came in with a set, requesting the technician to "just look at it." The technician did—just that. Just looked at it.

"Or take the customer with the little \$9.95 squawker box. He wants an estimate because he doesn't want to spend very much. Try smiling and saying, 'Well, now, these seldom run over \$40 for a good repair.' You will certainly get his attention."

END



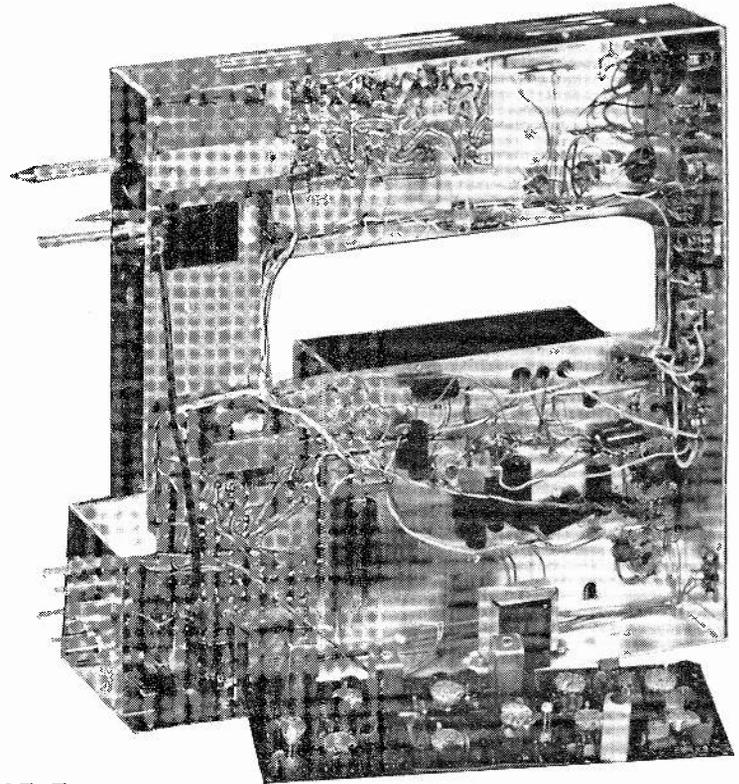OUR EDITORIAL REVIEWER FINDS THIS SET A TERRIFIC IMPROVEMENT OVER OLDER ONES. FUN TO BUILD AND EASY TO ADJUST, TOO.



Field-Day For Kit Builders:

DO-IT-YOURSELF COLOR TV

HAVING BEEN THE OWNER OF ONE OF the first 21-inch color TV sets since 1956, I was curious when Heath announced their color TV kit. I decided that putting one together would make an interesting story, particularly since I had a basis of comparison in the 1956 receiver.


Assembly was no more difficult than any other kit—just more of it. The instruction book is a story in itself—all 16 ounces of it. Not content with giving step-by-step assembly, adjustment, operating and service instructions, Heath included 16 pages on the fundamentals of TV theory—both black-and-white and

color. And there are eight pages of full-color photos of the picture-tube screen showing correct and incorrect color purity, convergence and color adjustments, as well as various defects, to aid in troubleshooting.

A considerable part of the kit is supplied preassembled. The front end and the video i.f. strip are factory-wired and aligned, with tubes already installed. The horizontal output stage and associated high-voltage rectifiers are prewired and assembled in a cage; the dynamic convergence control board is also furnished preassembled.

The builder must assemble two printed board assemblies: the sound-sync board and the color circuit board (the most complex). Then he must mount all circuit boards, miscellaneous transformers, chokes, controls and other parts on the chassis and interconnect them. A preformed and precut cable assembly is furnished which takes care of a large part of the interconnecting of circuit boards. I had a moment's difficulty figuring out which end of the cable assembly went where. But careful study of one of the many pictorials solved the problem.

Fig. 1—Unusual audio circuit in Heath GR-53 has two independent outputs. One is medium-impedance cathode follower for feeding hi-fi system; other output supplies up to 2 watts to 8-ohm speaker at low distortion. Note loudness compensation on volume control. Control does not affect hi-fi output—it works only on speaker portion. Treble-cut tone control circuit is omitted from this figure.

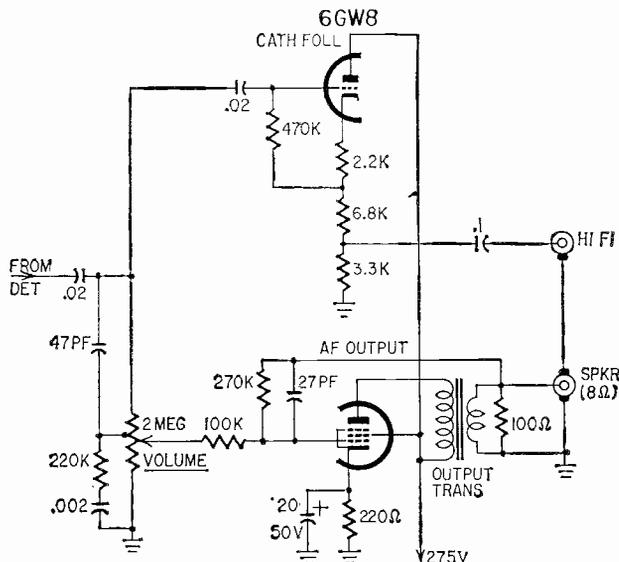

The step-by-step instructions were most complete and precise. Finally, after 34 hours (the instruction book says it can be done in 25 hours, but I took my time) I had all wiring completed, the chassis and picture tube degaussed. (A degaussing coil is furnished—it gets its power from the 6.3-volt heater winding on the power transformer.) I made the few precautionary checks suggested in the manual and turned the set on expectantly.

No sound, no raster! Then I noticed that the horizontal output tube's plate was cherry-red. No drive on the grid! A voltage check showed no B-plus on the horizontal oscillator tube. Tracing back from the rectifier to the horizontal oscillator, I found the trouble: the B-plus lead to the sound sync board

was loose. A cold-soldered joint (sob)! After re-soldering, I turned on the set again. This time picture and sound came forth. I was ready for the adjustments for color purity and convergence.

The purity adjustments proved to be quite simple. The next step was *static* convergence (at the center of the raster). This, too, was not a very difficult operation. Heath thoughtfully built into the set its own dot generator! A slide switch on the color circuit board puts it into operation. In addition, two clip leads soldered to the chassis make it a cinch to blank out one of the color beams to check convergence of any two guns.

After completing the static convergence I paused to admire my handiwork. I was startled to note that al-


though I hadn't started the *dynamic* convergence adjustments, convergence across the whole face of the tube was far better than our 8-year-old factory-built color set had ever been capable of, even after several hours of static and dynamic convergence adjustments!

Next, I tackled dynamic convergence. This was more involved, but again the instructions were so simple that the job was not too difficult. The final result was excellent convergence except at the extreme edges of the picture. At normal viewing distance even this slight misconvergence disappears and there is no evidence of color fringing (an annoying feature of the 1956 set). Purity and convergence adjustments took 3 hours and 20 minutes. (A repeat performance several weeks later took only about an hour because of familiarity with the adjustments.)


Expectantly, I tuned in a color program. No color! Acting on a hunch (and experience with the old color set) I replaced the 3.58-mc color oscillator tube (a 6GH8). That did it. The color came in. Next I touched up the color sync adjustment, following the service instructions in the book. (It can be done without instruments.) This done, color syne was stable as a rock, whether the receiver was just turned on or after several hours of operation.

Heath says that if width is insufficient (I didn't have this trouble), usually if line voltage is low, adding a 130-pf 6-kv ceramic capacitor across the horizontal yoke will give an inch more width. The capacitor can be mounted above or below the chassis.

Fig. 2—Circuit of built-in dot generator for convergence adjustments is described in detail in article. It can be switched in at any time once set is in operation.

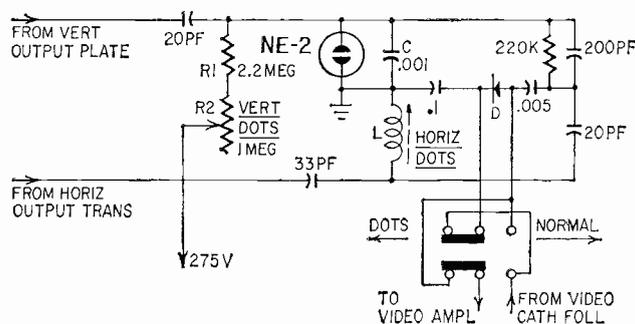

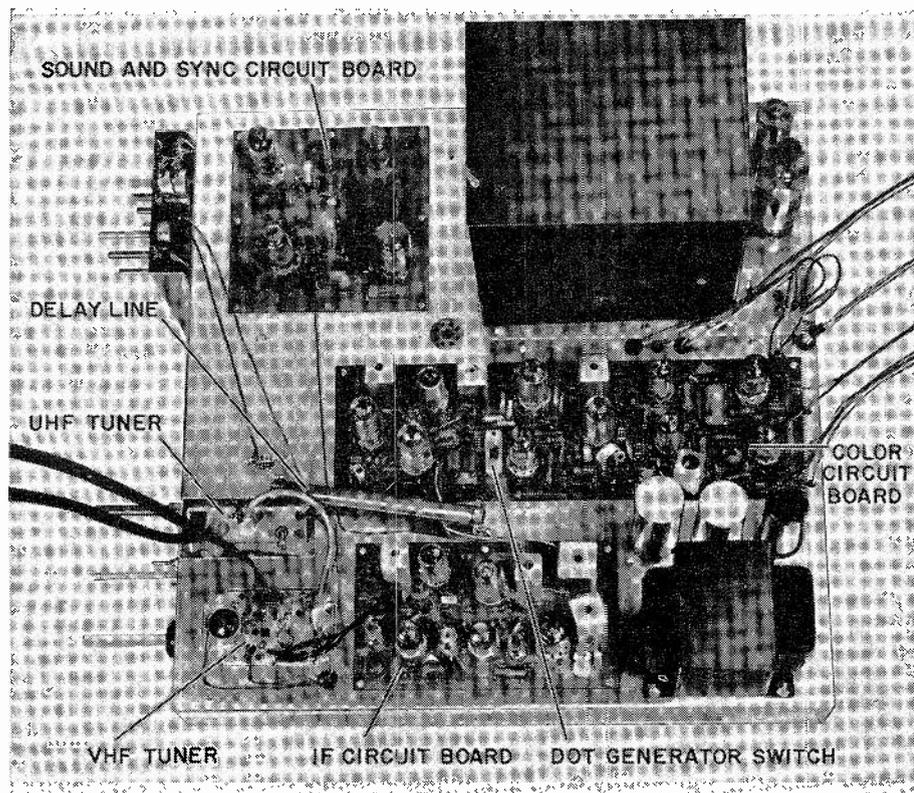Completed Heath color TV chassis ready for connection to 21FJP22 picture tube and installation in cabinet or custom mounting.



The circuit

The set uses RCA's high-voltage and sweep-convergence circuits as well as their color demodulator. Other circuits are Heath-designed but similar to those in the de luxe models of other set manufacturers. The vhf front end uses a turret tuner with a neutralized triode (nuvistor) rf stage. (Sets made after April 30 include an all-transistor uhf tuner as well.) The video i.f. amplifier has 3 stages. Video detector is a 1N295. A separate 1N295 serves as sync and sound detector followed by a combined sound i.f. and sync amplifier. A second sound i.f. feeds a locked-oscillator FM detector.

The audio system (Fig. 1) has two separate outputs. The first uses the triode half of a 6GW8 as a cathode follower. The output of this stage goes to a phono jack on the rear of the chassis for connection to your high-fidelity system. Output level is 2 volts maximum with less than 1% harmonic distortion and ± 1 db response from 50 to 15,000 cycles. Output impedance is 3,000 ohms.

The pentode half of the 6GW8 is used as a conventional sound output stage. About 10 db of negative feedback from plate to grid reduces distortion and flattens frequency response. The stage supplies 2 watts into 8 ohms at less than 3% harmonic distortion. Response is ± 2 db from 50 to 15,000 cycles. Using the oval speaker supplied with the console cabinet sound is vastly better than in most console TV's. With an external hi-fi system sound is limited only by the quality of the broadcast or the hi-fi system.


An extra stage of color amplification is provided. This stage has an a/c voltage applied to it (derived from the color burst) for automatic color control.

Color dot generator

The built-in dot generator circuit is shown in Fig. 2. R1 and R2 together, C and the NE-2 form a relaxation oscillator. R2, the VERTICAL DOTS control, varies the voltage applied to C as a way of controlling frequency. Oscillations are synced to a multiple of the vertical sweep frequency and applied to diode D. Coil L, the HORIZONTAL DOTS coil, is tuned to a multiple of the 15,750-cycle horizontal retrace frequency. It generates a chain of pulses when the retrace pulse shock-excites it. The pulses are mixed with the relaxation oscillator pulses and applied to D, which is biased so that only pulse tips are passed to the grid of the video amplifier. The VERTICAL DOTS control varies the number of *horizontal rows* of dots displayed on the picture tube. Changing the inductance of the HORIZONTAL DOTS coil L varies the number of *vertical columns* of dots. The dot generator output is fed to the grid of the video amplifier through a dpdt slide switch.

After using the set for several weeks, I can report that color and black-and-white reception is excellent, and tuning for color is noncritical. Convergence and color balance do not drift—in marked contrast to the 8-year old color set. Color TV has come a long way in those 8 years. The only remaining problem is the variable quality of the transmission from some stations. But then, we've had that trouble with black-and-white TV (and with radio, too) all these years!

END

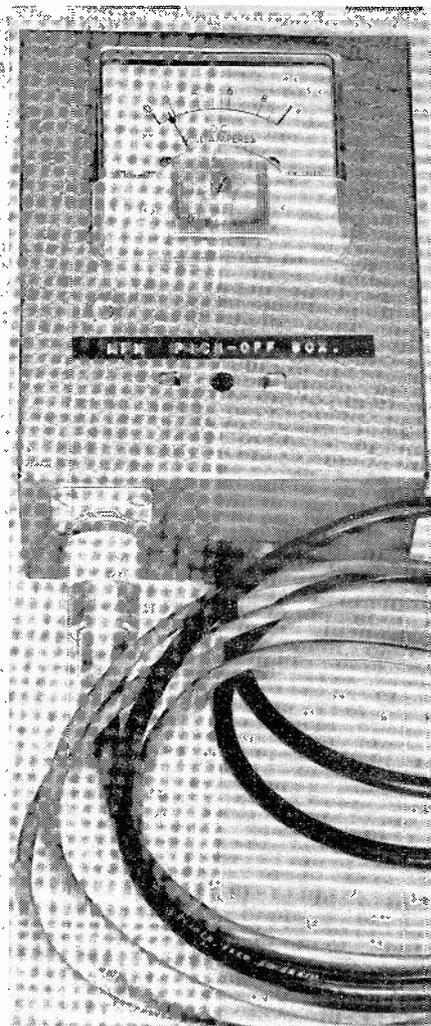

PICK-OFF BOX & WATTMETER FOR CB

Make transceiver power and frequency checks without creating interference

BY LYMAN E. GREENLEE

Servicing CB transceivers is now important business. But to make the frequency and power checks the FCC requires, you need specialized equipment. As channels become more and more crowded, you must limit on-the-air checks to an absolute minimum. Throwing a carrier on the air for frequency or power measurements is extremely annoying to all stations in the vicinity. The Pick-Off Box was designed to let you pick off a signal for frequency measurement or receiver checking without putting a carrier on the air. The cost of the Pick-Off Box and Wattmeter is so little in time and materials that no one who services any CB equipment can afford to be without it.

It was designed primarily to feed a signal to a frequency meter such as the Lampkin MFM (Micrometer Frequency Meter). About 3.5 watts rf input is required for a full-scale meter reading, and the Pick-Off provides just the right amount of output to beat with the MFM for an accurate frequency check.

If an accurate rf wattmeter is handy, you can set the 0-1 milliammeter for 3.5 watts rf full scale by adjusting the 5,000-ohm pot, R3. Otherwise, simply set R3 at half scale (2,500 ohms). The meter indication is useful for checking transmitter tuning and crystal activity as you make frequency measurements for the various channels, regardless of whether it is accurately calibrated in rf watts.

Radiation is so low that interference with other CB equipment on the same channel is negligible.

The block diagram (Fig. 1) shows the setup for making frequency measurements. The transceiver under test is coupled to the box through a short length of coaxial cable terminated with a standard Amphenol connector. For the pickoff for the MFM, a length of shielded microphone cable is terminated in a phone tip at one end and an Amphenol connector at the other.

Besides the MFM and Pick-Off Box, you will need an all-wave receiver that will tune to WWV. The antenna may be coupled direct to the MFM, using a small capacitor (C_x) of around 10 pf. C_x should be chosen to give a clear zero beat with the micrometer frequency meter without overloading the receiver's avc system.

After the equipment has warmed up thoroughly, set the MFM trimmer to zero-beat with WWV, and return the all-wave receiver to standby. Key the CB transceiver, note the power output

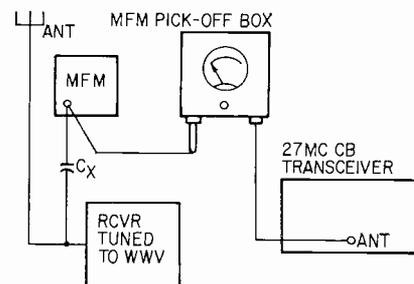


Fig. 1—Setup for measuring frequency with Lampkin MFM and Pick-Off Box.

and tune each channel to zero-beat with the MFM, noting the dial reading for each crystal. Calculate deviation from the chart supplied with the MFM for each channel. A weak crystal will show up immediately because the rf output read on the meter will be noticeably lower than on other channels.

Using a transmitter for receiver alignment is easy with the Pick-Off Box. Couple the transceiver being aligned through the box to another transceiver. The Pick-Off will provide an attenuated signal to the receiver, which can then be aligned to exactly the frequency of the transmitter. This type of alignment is important with fixed-tuned units. Each channel can be adjusted precisely to the frequency of the transmitter it is to receive, rather than to that of a test oscillator or frequency meter, which might be off-frequency compared to the transmitter. This alignment will insure maximum signal transfer between two units.

After one receiver is aligned for all channels for which crystals are available, reverse the procedure and align the other receiver by using the transmitter (of the transceiver already aligned) as a signal source. One of the biggest headaches with fixed-tuned transceivers is that they must be precisely tuned, and good reception is impossible if either the

transmitter or receiver is off frequency.

Obviously, it's better to tune the receiver exactly to the transmitter frequency than to set it precisely on the correct channel frequency, since the transmitter crystal may be either plus or minus as much as .005% and still be within FCC tolerances. If we had a transmitter operating at plus .005% and we happened to tune the receiver to minus .005%, the total error would be .01% between the two units, and reception would be very poor if the receiver had a crystal filter. It always pays to

check frequencies carefully if there is a complaint of poor, garbled, mushy reception between two fixed-tuned units. Most fixed-tuned receivers can be adjusted on each channel. If there is no such adjustment, change crystals in the receiver to match the transmitter frequency. Receiver crystals are often made to much broader tolerances than transmitting crystals, and it is usually possible to get the right one by careful selection.

Construction notes

Fig. 2 shows the wiring diagram of the Wattmeter and Pick-Off. R1 is used to make the Shurite meter read 1 ma full scale (the one I used read high). A more expensive 0-1 ma meter could be used, but this one is cheap, rugged and accurate enough. Check the meter by connecting it in series with an accurate 0-1 ma meter, a flashlight cell and 2,000-ohm rheostat. Choose a value for R1 that makes both meters read the same. R2 and R3 serve as limiting and calibrating resistors so that the meter will read about 3.5 watts rf with R3 set at half scale or 2,500 ohms. R3 may be set at its halfway position or adjusted to give a full-scale meter reading with 3.5 watts rf input if an accurate rf wattmeter is available for comparison.

The rf signal from the CB transceiver is fed through a length of RG-58A/U cable to the load resistor, made up of R4, R5 and R6 in series. Total resistance of this combination will be 56 to 57 ohms. A small portion of the signal is picked off through C1 from the top end of R6 while diode D rectifies part of the remainder and feeds it through the filter, L, C2, C3 and C4.

Construction should pose no problems. Everything fits neatly into the aluminum box, with room to spare. Layout is not critical, but keep all leads short, return rf grounds to a common point, and follow as closely as possible the parts arrangement shown in the photo of the interior of the instrument. There will be some radiation from the box, but not enough to cause objectionable interference. Ordinary microphone cable is adequate for the pickoff lead to the frequency meter. Strip the shield back about 3/4 inch from the phone tip used to connect to the MFM antenna jack. Cable length is not critical. END

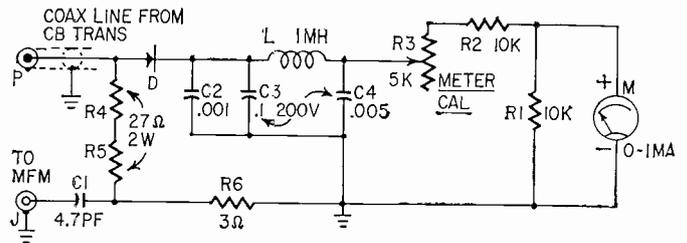


Fig. 2—Circuit of the Pick-Off Box.



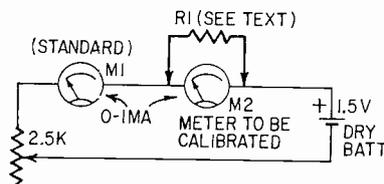


Fig. 3—Meter calibrating circuit.

Wiring the Pick-Off Box is a quick job.

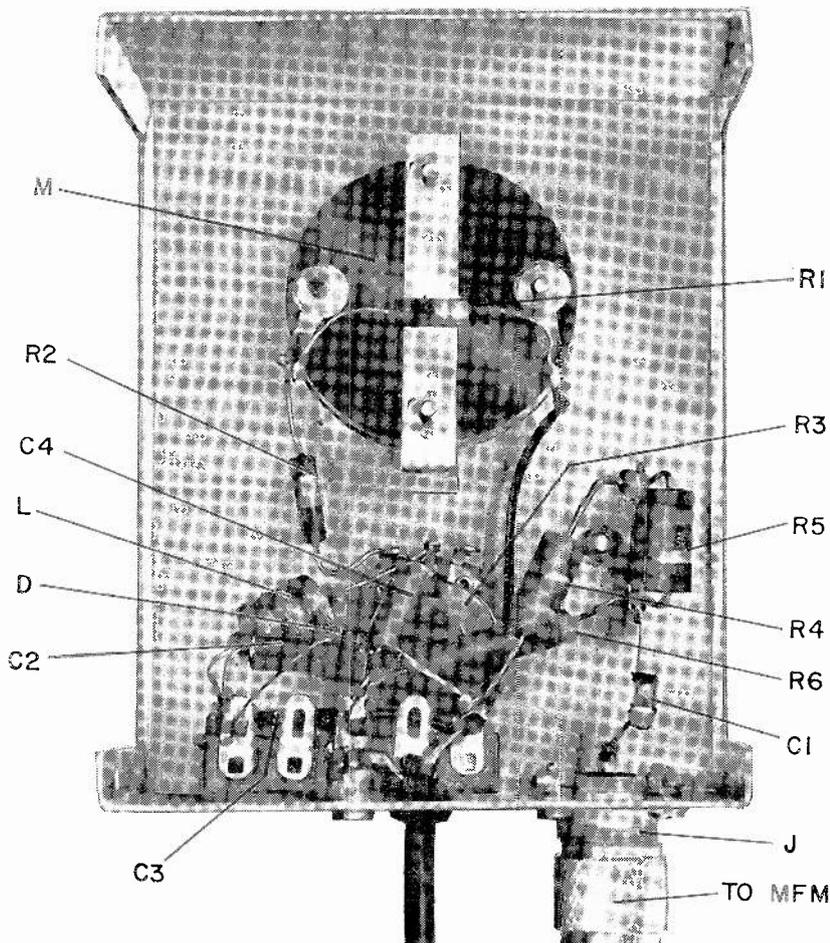

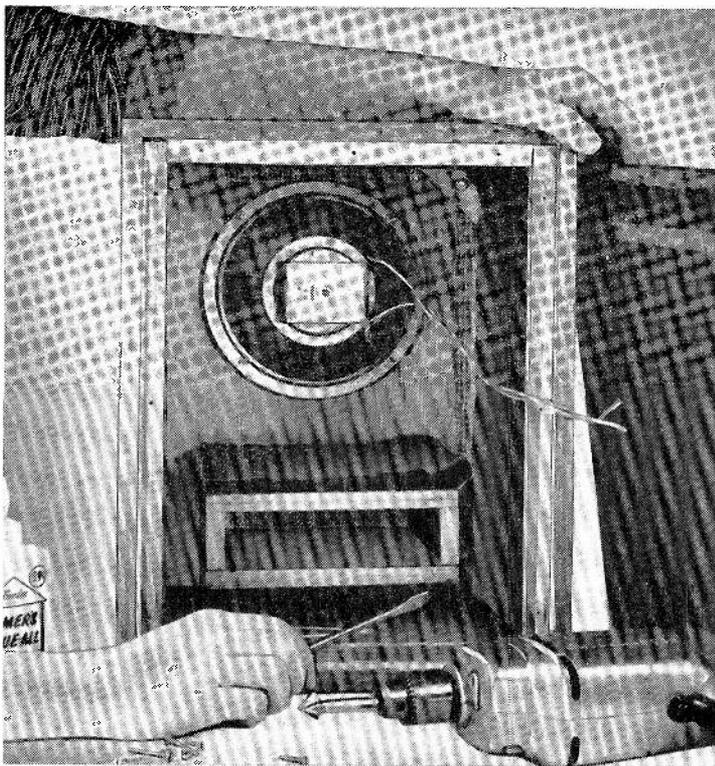

DESIGN YOUR OWN SPEAKER ENCLOSURE


YOU HAVE A HALFWAY DECENT SPEAKER and want to build an enclosure for the basement playroom. So far as audio test equipment goes, you have an ordinary vom and that's about it. What do you do?

Naturally, if the speaker is made by a well known manufacturer, you will write direct to the company for its recommendations. If it is an obscure imported model, or if you don't know who made it, you can still go ahead.

Find out what you can

What is the speaker diameter? Speaker diameter refers to overall frame size, not actual radiating area of the cone. If it is an oval speaker, assume it equivalent to the standard size which falls somewhere between the maximum and minimum diameters.

Fig. 1—Port area vs enclosure volume for the three kinds of speakers described in the text.

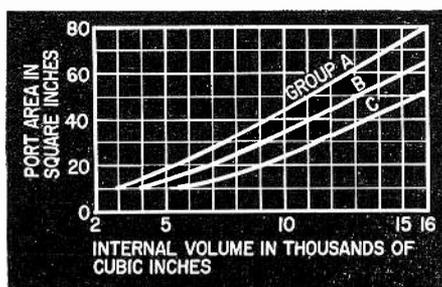

By **GEORGE L. AUGSPURGER**

FOLLOW THESE RULES AND YOU'RE
SURE TO GET THE BEST
FROM ANY HI-FI SPEAKER.

Second, determine the impedance. If it is not marked, measure the dc resistance with an ohmmeter and then double it for a rule-of-thumb impedance rating. There is very little chance that the figure will happen to be exactly 4, 8 or 16 ohms, but choose the one that comes closest as the nominal impedance of the speaker.

To make a reasonable estimate of what size enclosure will work best with a given speaker, we must place it in one of three groups:

(a) *Light cone/stiff suspension.* If the cone seems to be pretty thin and doesn't move easily when you touch it, the speaker probably belongs in this group. The great majority of PA speakers and auto speakers do.

(b) *Light cone/floppy suspension.* A good number of the bargain high-fidelity speakers, especially the imported units, have cones that move very easily. The outer edge of the cone may be treated with some kind of sticky substance to make it more flexible. If you

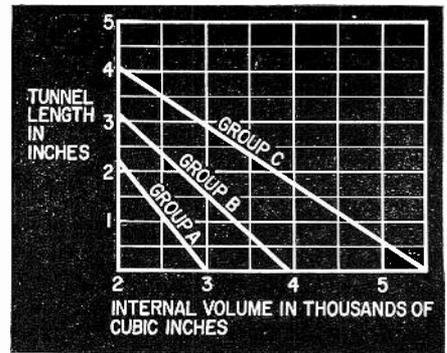


FIG. 2—Tunnel (duct) length for small enclosures with 10-square-inch port opening. Lengths on chart are measured from back of baffleboard. Thus, with a $\frac{3}{4}$ -inch front panel (baffle), actual duct length is $\frac{3}{4}$ inch longer than figure given. This has been allowed for in making chart. (Length shown does not include baffle thickness.)

hold the speaker up to a light, you may see that the outer edge of the cone is much thinner than the rest.

(c) *Heavy cone.* If the cone seems to be considerably thicker than a sheet of ordinary writing paper—more like a blotter, for example—and it is fairly soft, then the speaker is probably designed as a woofer.

In any case, hook the speaker up and listen to it before you start work. Without an enclosure, bass will be pretty weak, but you can get an idea of the mid-range and treble response. If highs are crisp and clean, there is no point in adding a tweeter unless you are willing to pay for a good unit. On the other hand, if the speaker sounds "mellow" and somewhat muffled, it won't be much good for anything but background music unless you add a tweeter. In this instance, a less expensive cone tweeter may be satisfactory.

Enclosure volume and dimensions

The internal volume of the finished box is important. The table next to Fig. 5 at the bottom of page 46 gives the minimum volume needed if you expect to extend bass response to the limits of the speaker itself. If you want to make a smaller cabinet and are willing to sacrifice some bass efficiency, it also tells you the minimum volume that can be expected to give pleasing sound.

Although some engineers have certain proportions they like to use in designing enclosures, there is no one magic formula for superior results. The main idea is to keep the cabinet interior from setting up strong resonances at certain frequencies. *To be safe, no dimension should be more than three times any other dimension.*

At this point you run into the struggle between acoustics and decor. An enclosure with only 2 cubic feet of internal volume is still a sizable object, and you may find that it *must* be squashed into an awkward shape to get

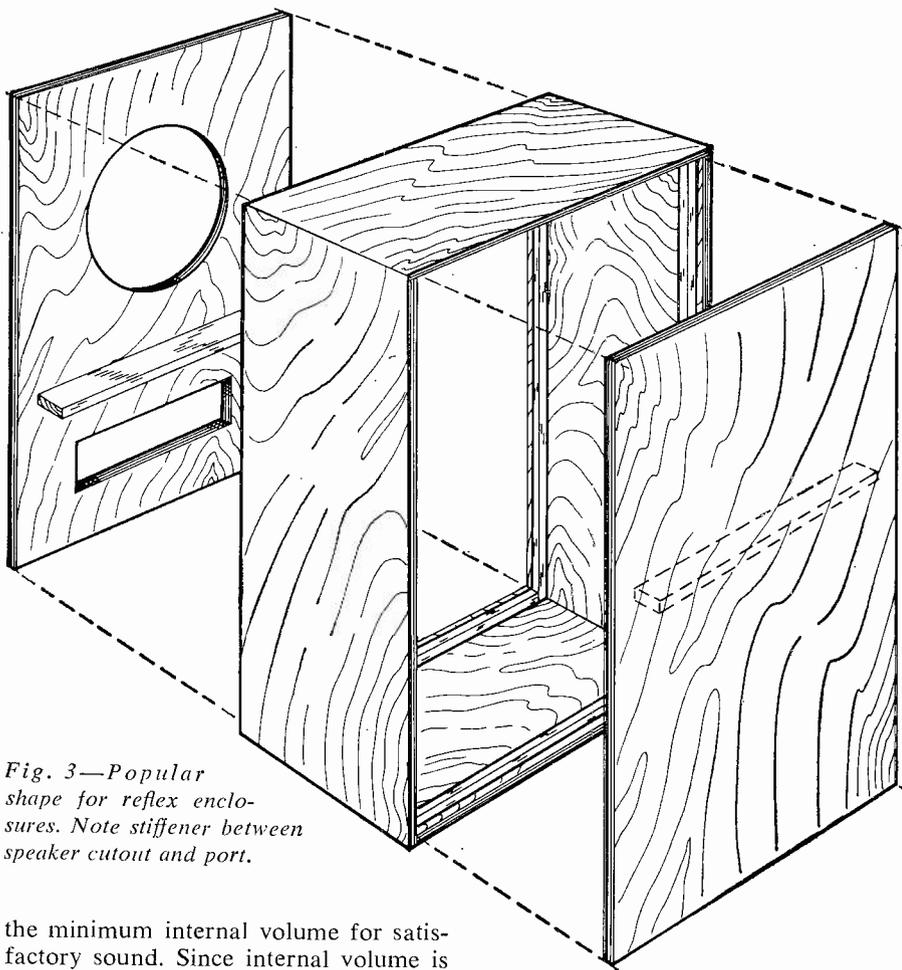


Fig. 3—Popular shape for reflex enclosures. Note stiffener between speaker cutout and port.

the minimum internal volume for satisfactory sound. Since internal volume is more important than proportions, go ahead anyway. A little farther on, we will take up these "problem cases" and show what can be done to make them perform almost as well as the more usual configurations.

You will have to juggle dimensions until you arrive at a set of figures to fit into the available space, yet allow adequate internal volume to work with the speaker you plan to install. Then lay out the baffleboard. A cutout must be provided for the speaker, for the tweeter (if you use one) and for the port.

Port size

"Aha!" you say. "But suppose I don't want to build a ported enclosure?"

Well, if you want to follow my suggestions, you have no choice. I've probably played with as many wild enclosure designs as any other audio nut, and I am convinced that for safe, predictable results from a variety of speakers, the ported enclosure is the best bet.

"All right," you reply, "but then I will need to know the cone resonance

This Lafayette "Mini-Duct" enclosure, used with a Lafayette SK-98 8-inch speaker, puts out some fine sound. Simple duct structure on floor of cabinet can be modified to suit various speaker resonant frequencies. Radiotron Designers Handbook (Fourth Edition, 1952) gives much valuable data, formulas, charts, etc., to assist you in designing or modifying an enclosure.

of the speaker, and the radiating area of the cone, and the formula for critical damping, and how to tune the port, and all that."

No, you will not. The term "reflex" has purposely been avoided since it implies a certain type of ported enclosure. But a lot of the bugaboos about "boom boxes" and tuning the system with clicks and bongs are pure mythology. So long as you observe the precautions sprinkled through this discussion, the completed project will work almost as well as if


you had all sorts of professional test gear. Not quite as well, perhaps, but your chances are at least as good as if you spend a lot of time playing test recordings and blowing smoke into the port.

Refer to the three curves in Fig. 1. Find the recommended port size for the speaker you wish to use and the cabinet volume selected from the table. The shape and position of the port are not particularly important but, again, its dimensions should not exceed the 3-to-1 ratio. If the idea appeals to you, you may even make a "distributed port" by drilling a number of holes in the front panel so that their combined area adds up to the suggested value. The individual holes should be at least $\frac{3}{4}$ inch in diameter if the arrangement is to operate the same as a single large port opening.

If you are building a small bookshelf enclosure, the port area may become so small that it will not radiate sound effectively. The minimum area of a port is about 10 square inches. Rather than make the opening any smaller, we must add a tube or tunnel to the port to tune the enclosure properly. Fig. 2 suggests the best tunnel length. It is possible to use tunnels with larger ports, but this involves additional complications. For a nice, simple predictable design, the large ducted port offers no real advantage, so we will just ignore it.

Baffleboard layout

Except for the problem cases to be mentioned later, the speaker will perform the same no matter where it is located on the front panel. It is a good idea to have the source of sound somewhere near ear level, so the speaker should be near the top of the panel if the cabinet is going to be set on the floor. If you plan to use a tweeter, this gets priority, and the main speaker is then

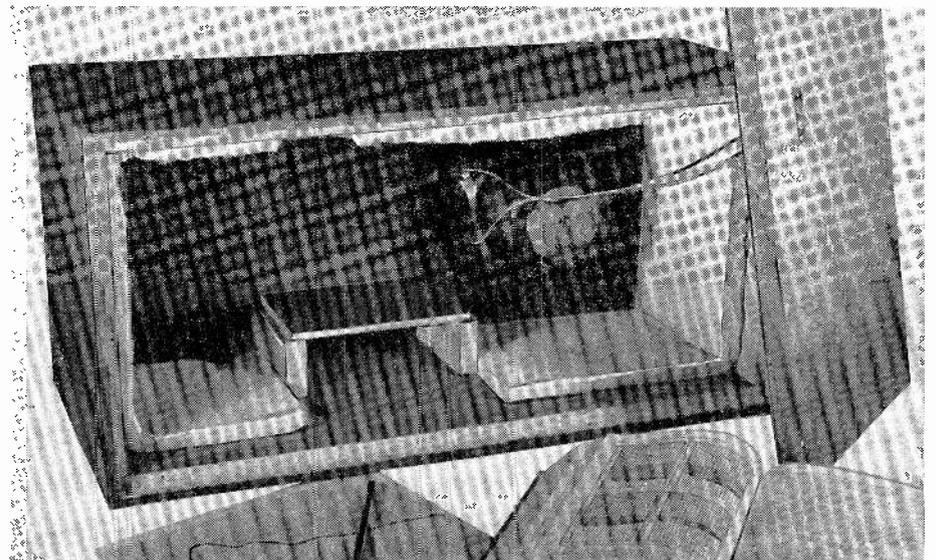

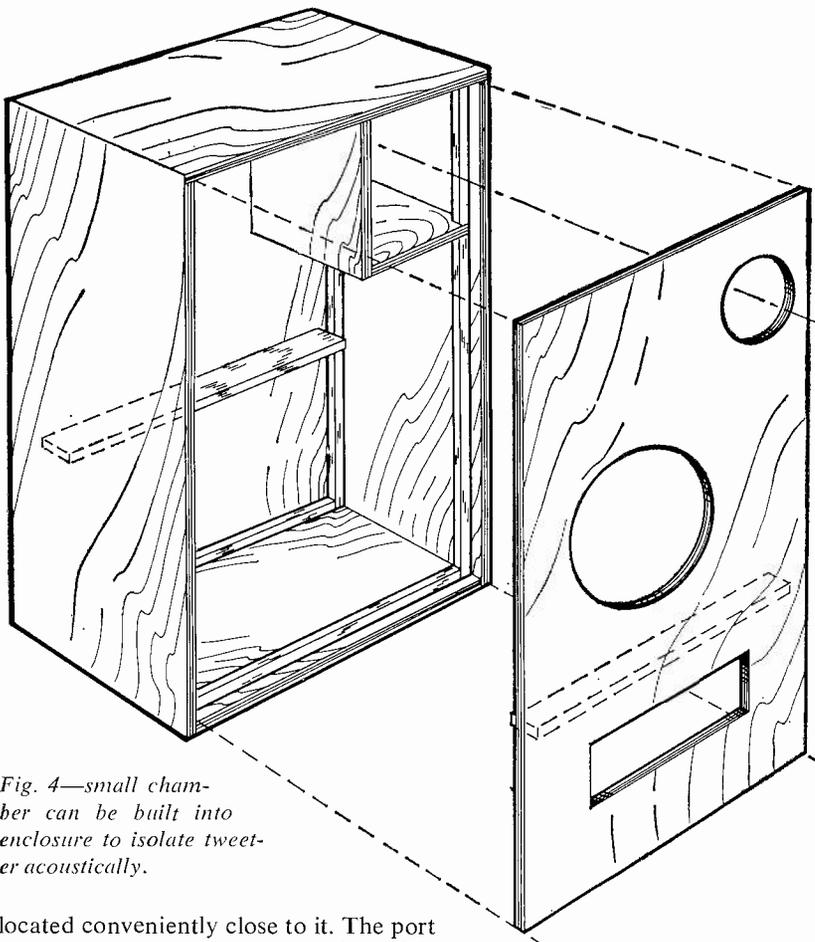


Fig. 4—small chamber can be built into enclosure to isolate tweeter acoustically.


located conveniently close to it. The port is generally near the bottom, but if it has to go somewhere else, don't worry about it.

Fig. 3 shows a popular configuration, established when the reflex enclosure came into general use. Symmetrical and easy to lay out, it works well. Note the stiffener across the baffleboard between speaker cutout and port. This braces the panel and at the same time gives a little acoustic isolation between the edge of the speaker cone and the port. If you can incorporate such a

stiffener into your design, it is a good idea. Whether it is there or not, the port and the speaker should be no closer than 2 inches, and no more than 6 inches apart, approximately.

A brief warning about the tweeter: You cannot take an ordinary 4-inch speaker and mount it in the same chamber with the main speaker. The two cones will be pneumatically short-circuited. Many small units designed specifically as tweeters are completely sealed, and in this case there is no problem. But if the one you choose is not, it must be installed in a separate little chamber within the main enclosure, as in Fig. 4. It should be completely lined with absorptive material, and the volume occupied by this little isolation chamber must be subtracted from the

Fig. 5—Layer of absorptive material across back of speaker sometimes controls "boom".

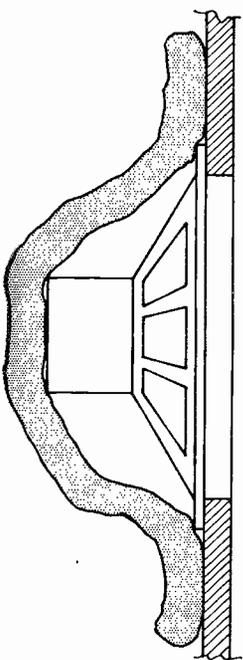

MINIMUM ENCLOSURE VOLUME (IN CUBIC INCHES)				
Speaker group	Speaker diameter (inches)			
	8	10	12	15
A Light and Stiff	4,300	6,000	8,200	10,100
	2,100	2,900	4,000	5,200
B Light and Floppy	4,100	5,700	7,600	9,500
	2,100	2,700	3,600	4,800
C Heavy	4,000	5,200	6,900	8,600
	2,100	2,600	3,300	4,300

Upper figure in each entry is minimum internal volume for optimum bass; lower figure is minimum for acceptable overall performance.

total cabinet volume when working out the port size.

Bracing

A good loudspeaker enclosure *must* be as rigid as possible. Enclosures with thin unbraced panels may sound quite distinctive, perhaps even pleasing. But, unless you are a gifted craftsman, willing to spend as much time on a speaker cabinet as you would in building a violin, it is much better to make sure that the enclosure does not add distinctive coloration to reproduced sound.

You can sometimes get by with little internal bracing if you use thick panels. But to be on the safe side, a brace should be added to any surface larger than 18 inches square. The easiest way to brace a panel is to glue and screw a piece of 1 x 3 on edge across the narrow dimension of the panel. The enclosure in Fig. 3, for example, has braces across the front and back panels. Since the cabinet is assumed to be less than 18 inches deep, no bracing is required on the remaining four surfaces.

As a final test, check the panels for rigidity when the enclosure is finished. Pound on them with the heel of your hand. If there is a strong "kettle-drum" sound, better add another interior brace or two. The more solid the enclosure, the firmer and crisper the bass response will be.

Padding

The only thing padding does is to absorb mid-range sound that would otherwise bounce around inside the enclosure and finally be reflected out through the port opening or the speaker cone itself.

The padding material should be at least $\frac{3}{4}$ inch thick, reasonably soft and fluffy. Several products available from most hi-fi dealers are specially formulated and packaged for this purpose. Scraps of ordinary felt rug padding are often used and work very well.

Padding does not have to be neat, it does not have to be fastened tightly to the interior surfaces, it does not have to cover any specific areas. Generally, the less padding used, the more "live" the sound. An accepted rule is to pad about half the interior surface area and arrange to have an unpadded wall always face a padded wall. For example, a good starting point is to pad the back, bottom and one side of the enclosure. Padding can be loosely tacked to the enclosure walls with upholstery nails, staples or large carpet tacks. Insulated wiring staples are easy to use and do a good job.

Whatever you do, don't put a layer of padding across the port opening. Some sophisticated variations of the ported cabinet do use that kind of resistive loading across part of the opening, but they are designed for use with specific speak-

ers. From time to time, articles suggest that two or three layers of old cheese-cloth across the port will damp out the "reflex boom". The only trouble with this idea is that it doesn't work, as can be demonstrated quite readily by blocking the port altogether. If the system boomed in the first place, chances are that the boom is still there when it is changed to a completely closed cabinet.

When such boominess does occur, it may be because of room acoustics, a cabinet too small or not sufficiently rigid, or a speaker which has a poor coupling coefficient. In some cases, the boom can be controlled by tacking a layer of padding across the back of the loudspeaker (Fig. 5).

Installing speakers

Remember that you will have to make one panel of the enclosure demountable for installing speaker components. Usually the back panel is removable, but if the enclosure is to be permanently hung or built-in, then the front panel is a more practical choice. The demountable panel should be held in place by screws spaced every 4 or 5 inches around the perimeter and screwed into wood strips glued in place on the top, bottom and sides of the interior.

Although small speakers can be held in place with wood screws, machine

screws make a neater job and simplify removing and reinstalling the speaker if this should ever be necessary. Machine screws can be used with matching nuts and washers, or screwed into T-nuts inserted from the opposite side of the panel. T-nuts can be purchased from most large hardware stores.

Connecting wires can be brought out through small holes in the back, or you can use screw terminals or a phone jack. A little extra time and thought here can save a lot of inconvenience when you hook up the system. Do *not* use ordinary ac connectors. If you do, sooner or later someone will plug the speaker into a wall outlet.

Grille cloth

I have purposely avoided any suggestions of styling or furniture finishing because that would require a treatise in itself. If you want to do a complete construction and finishing job, see Jeff Markell's book *Designing and Building Hi-Fi Furniture*, Gernsback Library. A simple and attractive grille can be made by constructing a frame which comes flush with the edges of the cabinet, and stretching grille fabric over it. The frame can be held in place by decorative screws, dowel pins or friction catches.


As to the grille fabric, there are a number of colors and patterns available

in synthetic materials made for this specific purpose. Most hi-fi dealers carry them. If you want something really distinctive, look for fabrics in the yard-goods department or the drapery counter of a department store. Choose a fairly hard (as opposed to fluffy), open-weave material (easy to blow through). Heavy upholstery fabrics or thick soft materials will absorb most of the high frequencies and make the system sound muffled.

The wooden panel behind the grille cloth should be painted a dull flat black so that it will not be visible. Fabric should be spaced $\frac{1}{8}$ inch or so away from the panel to help keep the cutouts from showing through. If the material is so open that it is easy to see through, back it with a second layer of black sheer rayon or silk to make the grille opaque.

Performance

Remember that room acoustics will affect the performance of the system almost as much as the speakers themselves. Don't place the speakers so that there are large pieces of furniture in the path of the sound. If you have two systems hooked up to a stereo source, place the cabinets so that a listener sees an angle of about 40° between the two sound sources. Don't be afraid to experiment with speaker placement for optimum results. END

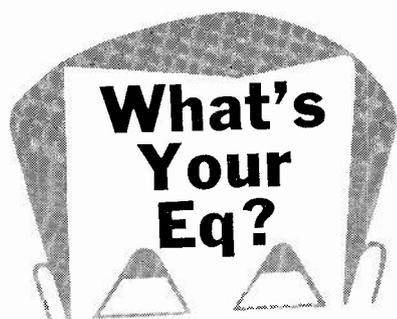


Conducted by
E. D. CLARK

Two puzzlers for the students, theoretician and practical man. Simple? Double-check your answers before you say you've solved them. If you have an interesting or unusual puzzle (with an answer) send it to us. We will pay \$10 for each one accepted. We're especially interested in service stinkers or engineering stumpers on actual electronic equipment. We get so many letters we can't answer individual ones, but we'll print the more interesting solutions—ones the original authors never thought of.
Write EQ Editor, Radio-Electronics, 154 West 14th Street, New York, N. Y. 10011
Answers to this month's puzzles are on page 60.

Autotransformer

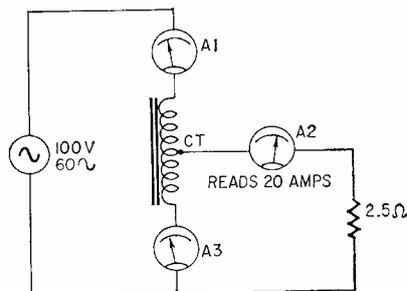
Can you determine the reading on ammeter A1 and ammeter A3?—*Kendall Collins*



Case of the Lost Energy

Here's a capacitor problem to test your ability in analyzing "simple" circuits:

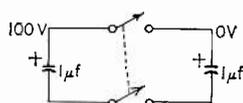
Two one-mike capacitors, and a switch connecting them. The left capacitor has been charged up to 100 volts; the right one is unchanged. The switch is then closed.



Since we have not changed the total amount of charge, and since the theory book tells us that:

Charge = Farads \times Volts ($Q = CE$)
the left capacitor will lose half of its

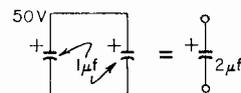charge to the right one. The voltage will now be 50, since the capacitance has doubled. The circuit now consists of a 2- μ f capacitor charged to a potential of 50 volts.



So far, so good. Now once again, we refer to our theory book and find the formula for the energy stored in a capacitor:

$$\text{Energy} = \frac{1}{2} \times \text{Farads} \times \text{Volts}^2$$

Let's try some numbers:

Originally,

$$\text{Energy} = \frac{1}{2} \times 1 \mu\text{f} \times 100^2 + \frac{1}{2}$$

$$\times 1 \mu\text{f} \times 0^2 \\ = 2,500 \mu\text{Joules} \\ = .005 \text{ Joule}$$

Finally,

$$\text{Energy} = \frac{1}{2} \times 2 \mu\text{f} \times 50^2 \\ = 2,500 \mu\text{Joule} \\ = .0025 \text{ Joule!}$$

We lost half the energy when we threw the switch! But a capacitor can only store energy, not dissipate it. Also, our theory book is a firm believer in conservation of energy.

Now then, simply, the problem: *Where did the energy go?*

(Assume that the switch is perfect.)
—*Donald E. Lancaster*

MORE ON MULTIPLEX VIDEO

THE EDITORIAL "MULTIPLEX VIDEO" IN the March issue aroused considerable interest. One of the comments on it was simply a copy of Patent No. 3,079,462, issued to W. Rosenthal for a "Television Receiver with Picture Selector Device."

The patent, which was filed July 21, 1958, and issued February 26, 1963, showed a rather conventional-looking television set (see figure) with a box containing eight additional panels mounted on top of it, and what is obvi-


ously a control device on the end of a cable. The two parallel rows in the box above the set are small pilot cathode-ray picture tubes, with medium-persistence screens.

Pressing a button on the control starts a rotating switch which selects each channel's signal for a period of, say, $\frac{1}{8}$ second. These signals are applied to the grids of video tubes in turn through a distributor. With a $\frac{1}{8}$ -second period for each tube, the tube would be scanned four times, and would receive

an impression that would persist while the remaining screens were being scanned. Thus, four channels could be scanned in $\frac{1}{2}$ second. If eight were scanned, the total period might be 1 second.

Circuitry is provided to transfer the picture on any one pilot screen to the main screen. This is one way of realizing the multiple video receiver described by Hugo Gernsback in the March editorial.

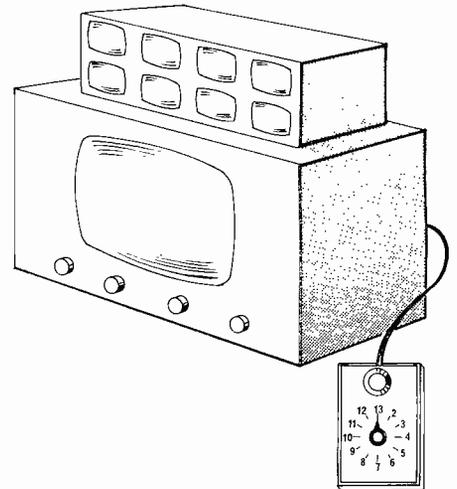Two of the references cited by the Patent Office are "The Radio-Controlled Television Plane," *Television News*, March-April 1931, and "Multiple Television, a Forecast," *Radio News*, pp. 528-529, December 1928. Both of these references are to early articles by Gernsback.



The set described in Pat. 3,079,462.

The radio-controlled television plane (shown in the illustration opposite) was actually reprinted by *Television News* from Gernsback's publication, the *Experimenter* of November 1924, and was indeed a concept of multiple television equipment (probably the first such concept).

The plane would be unmanned and controlled completely with television cameras (called "electric eyes" in the article) pointing north, south, east,

Set shown on the cover of Gernsback's *Radio News*, December 1928. The top screen is probably the first representation ever of a TV program in color.

Television Plane

Member of American Physical Society

west, up and down. The signals from the unmanned plane would be transmitted to a ground station, where the control operator looking at the six screens would be able to observe the action around the plane and control it accordingly.

Thus, if the plane were equipped with guns, the control operator could maneuver it, as a fighter, to down an enemy plane, or, if supplied with bombs, to knock out a ground installation. With the six screens before his eyes at the same instant, the control operator would be able to see more than an aviator actually sitting in the cockpit.


The second reference cited in the patent refers to an article printed in December 1928, after a few experimental television receivers had come into use. The reason for a multiple receiver was the same one given in the March 1964 "Multiple Video" editorial—the desirability of being able to see "what's doing" on several channels at a time.

The position of the screens on the multiple television receivers in the 1928 article is considerably different from that suggested in the 1964 editorial. The reason is that television in 1928 depended on a large rotating disc, perforated with a spiral of holes. Gernsback suggested that, instead of one spiral, the disc could have three sets: the large screen at the top would be scanned through one set of holes, and the two smaller ones at the base by two other sets, all at the same time. (This would be simultaneous, rather than sequential, television, as described in the more recent patent.)

Interestingly enough, the top screen in the set of the cover of *Radio News*, December 1928 (which was printed in four colors, is shown displaying its picture in full color. The smaller screens (labeled 2 and 3 on the cover) are in black-and-white.

Thus the wild dreams of the past come a little nearer to reality each time they are projected. The television plane of 1924 was described at a time when nothing existed that could really be described as television. The experiments of Francis Jenkins had succeeded in transmitting silhouettes, but there was no gradation of tone between black and white, and seldom were attempts at motion shown.

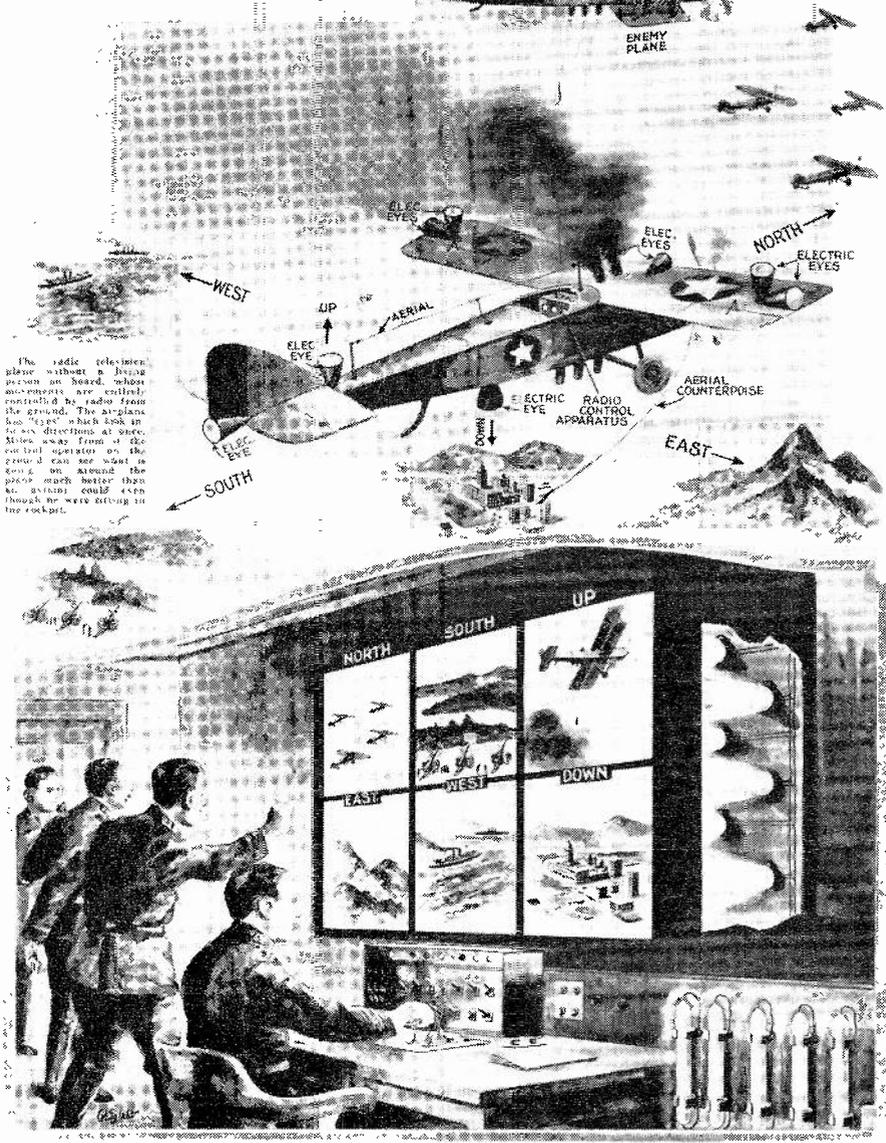In 1928, TV sets of a type were in existence—the means for making a true television picture were known. In 1964, as Patent No. 3,079,462 and the "Multiple Video" editorial show, all the means for producing a true multiple television device are at hand. If a designer had a strong enough desire for such a TV receiver, he could have one in the time it would take to put it together. **END**



The original multiple-screen television concept.


TUNNEL DIODE REGULATOR

HERE IS AN UNUSUAL APPLICATION FOR a tunnel diode. It regulates a dc supply and prevents the output from rising above a preset level, as disclosed in patent No. 3,108,218, assigned to International Business Machines Corp. Normally biased for positive resistance, the diode is stable. If the applied voltage rises for any reason, the bias is advanced to the region of negative resistance, and the diode oscillates.

During each positive alternation across the inductor, Q1 conducts. Its current flows through R1, C1, which smooth the pulses and deliver a forward bias to Q2 which also conducts.

A much larger current passes through Q2 than through Q1. In flow-

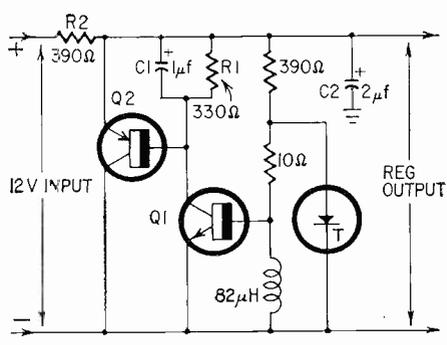ing through R2, it drops the voltage to normal and compensates for the undesirable increase.



C2 filters the regulated output. Suggested component values are for a 5-ma diode having a 5:1 peak-to-valley current ratio.—I. Queen



SERVICING SPEEDLIGHTS

Their circuits have much in common; there's little to go wrong!

By **WAYNE LEMONS**

ELECTRONIC PHOTOFLASH UNITS HAVE been used by professional photographers for years, but when these units need service, nobody seems to want the job—sometimes not even the factory. Yet almost any electronic technician is equipped to whip photoflash equipment back into shape and make himself a piece of change in the bargain.

Nearly all speed lights (or strobe lights, as they are sometimes called) work on identical principles. A gas-filled flash tube has high voltage across it, but that alone does not fire the tube

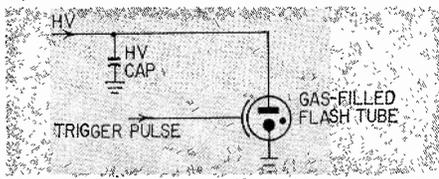


Fig. 1—How a speedlight is fired. High voltage remains across tube at all times, but tube does not fire until triggered by pulse.

until the tube is triggered with a voltage pulse. Fig. 1 shows the basic idea. The trigger pulse is fed to a small wire or clamp fastened around the outside of

the flash tube. The trigger pulse momentarily ionizes the gas inside, just as rf ionizes the gas inside a small neon bulb held close to a strong rf source.

When the gas is triggered, the current from the high-voltage capacitor is discharged through the flash tube and a short, brilliant flash is produced. The light energy output is calculated by photographers in *watt-seconds*. The number of watt-seconds is determined by the capacitance of the high-voltage capacitor and by the amount of voltage used to charge it. The formula is $\frac{1}{2}CV^2$, where C is capacitance in microfarads and V is voltage in kilovolts. For example, if the high-voltage capacitor is 20 μf and the voltage across it is 2 kv (2,000 volts) we would have $\frac{1}{2}(20 \times 2^2)$ or $\frac{1}{2}(20 \times 4) = 40$ watt-seconds.

The size of the high-voltage capacitor determines the speed of the flash; smaller capacitors give shorter flashes. A 15- μf capacitor at 2,000 volts has a flash duration of only 1/10,000 second. The speed change is not linear with capacitance; it takes almost 4 times as much capacitance to increase the time to 1/5,000 second.

The trigger circuitry

Nearly all studio speedlights are triggered by a scheme like that of Fig. 2. A pulse on the primary of the trigger transformer is stepped up in the secondary to a high enough voltage for triggering. A camera could be connected across the trigger button switch but the current in the primary circuit could easily damage the camera contacts. Some other arrangement is necessary. This is usually done with a thyatron trigger tube, occasionally with a relay, and in a few late models with a power transistor. Fig. 3 shows how a thyatron is connected as a trigger tube.

Studio speedlight is mounted like photoflood. Power pack is behind reflector, not separate as in most units. Its circuit is in Fig. 4.

The 0.5- μf capacitor (C2) in the trigger transformer primary is charged through the 100,000-ohm resistor. The charge is slow so that there is little output from the secondary. The thyatron is kept cut off by returning the grid resistor to -50 volts.

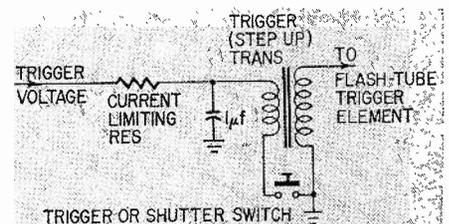


Fig. 2—Most common triggering method uses transformer to step up pulse. Closing switch sends "kick" through transformer and sets off tube.

When the points in the camera shutter close, the voltage on the grid goes to zero because of the charging current in C1. This drives the tube into conduction, ionizing the gas inside it, so that it has a very low resistance. C2 discharges through the trigger transformer primary and the thyatron and triggers the gas in the flash tube.

R1 discharges C1 so that it will be ready to drive the grid negative on the next shot. Even if the camera contacts remain together, the flash tube will not flash again until the contacts are opened and C1 is allowed to discharge.

Complete circuits

Fig. 4 is a complete circuit of a popular speed light of a few years ago. It uses a "cold-cathode" 0A4-G thyatron—no heater. This tube needs a large positive voltage on the starter anode before it will fire. When the camera shutter contacts close, the voltage on the starter anode goes more positive and triggers the tube. R1 is used to adjust the tube for the most sensitive trigger point without the danger of self-firing.

The one big problem with these units is the 0A4-G tube. It is erratic

unless specially aged. Just any tube picked off the shelf will not work. The factory supplies these special tubes but you can often age your own if you have a tube tester that will check thyratrons. Put the tube in the tester and fire it a number of times until it stabilizes. It will usually work OK after this treatment. A .25- μ f capacitor across R2 will often help stop erratic firing also.

Fig. 5 is a former relay-triggered circuit that was modified for electronic triggering because the owner wanted to fire the unit with a phototube. If a photographer uses more than one speedlight, he need fire only one from his camera. The light from it will fire his other lights if they have phototube connections.


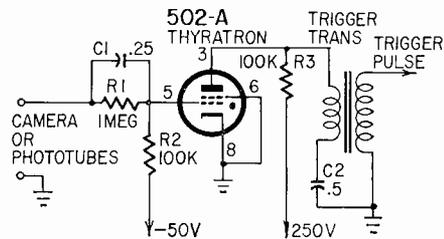


Fig. 3—Thyatron trigger “amplifier” saves camera sync contacts from heavy surge currents.

The original relay connections and the new circuitry are shown in Fig. 5. Starred parts (*) were added. Since the voltages on the bleeder were negative, the plate of the 502-A thyatron is grounded. A 47,000-ohm resistor (R) was added in series with the bleeder to make the voltage on the grid more negative than on the cathode so that the tube is kept cut off until triggered by the camera.

The circuit in Fig. 6 has some interesting features particularly important to the service technician. A safety switch shorts out the high-voltage capacitor when the lid is removed. This is important. A speedlight can kill you! It uses a brute-force power supply with a tremendous current potential. Never stick your hands in a speedlight circuit without making sure the capacitors are “dead.” You can discharge them with a screwdriver or a piece of wire but, if the capacitor is fully charged, there will be a loud report that can make you a nervous wreck. I prefer to discharge the capacitors through a 10,000-ohm, 10-watt resistor for a few seconds and then short them out. This is less grating on the nervous system, and must be easier on the capacitors.

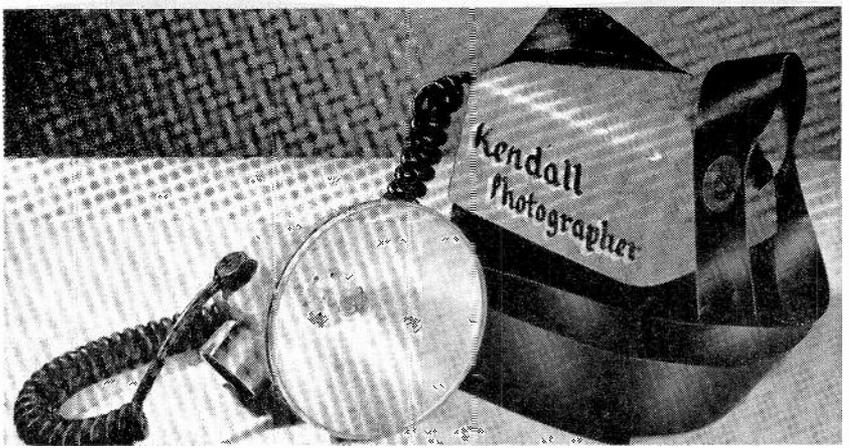If the flashtube can be made to fire just as the unit is turned off, this will discharge the capacitors and lessen the danger of probing around inside. The “Photogenic” unit in Fig. 6 has an extra set of contacts on the off-on switch that does just that. Notice that it does so by grounding the plate of the trigger tube. This means that even if the



Portable electronic flash. Power pack hangs on shoulder strap; flash tube and reflector assembly fits on camera.

trigger tube goes bad in service, the capacitors will still be discharged.

Another interesting feature of this unit is the flash indicator bulb. At first thought, it might seem foolish—you should certainly be able to tell whether there is a flash from the flash tube or not. This would be true if you were using only one unit but a professional photographer may fire several at the same time and he can't be sure that they have all fired. One misfire might ruin the effect he wants.

The flash indicator bulb lights bright after the unit flashes and slowly dims down and goes out when the unit is ready to fire again. It does this because it is wired in the primary circuit of the

plate transformer. When the flash tube fires, the 80- μ f high-voltage capacitor is short-circuited and discharged. The 2X2 rectifier starts drawing high current to recharge it. This high current is drawn from the primary and through the bulb. As the capacitor charges up, the current reduces and the flash indicator bulb dims and goes out.

A HIGH-LOW switch is also used on this unit to increase or decrease the watt-second rating. In the HIGH position the voltage is increased and the capacitor has more charge in it.

Some earlier models of the unit had the heater winding for the 502-A on T1. When the HIGH-LOW switch was on LOW, the heater voltage on the tube was



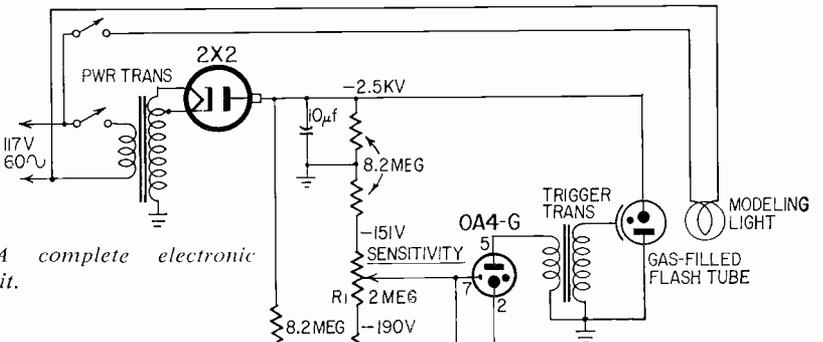


Fig. 4—A complete electronic flash circuit.

Fig. 5—Once triggered through a relay, this unit was adapted to use a thyatron so it could be set off with a photocell.

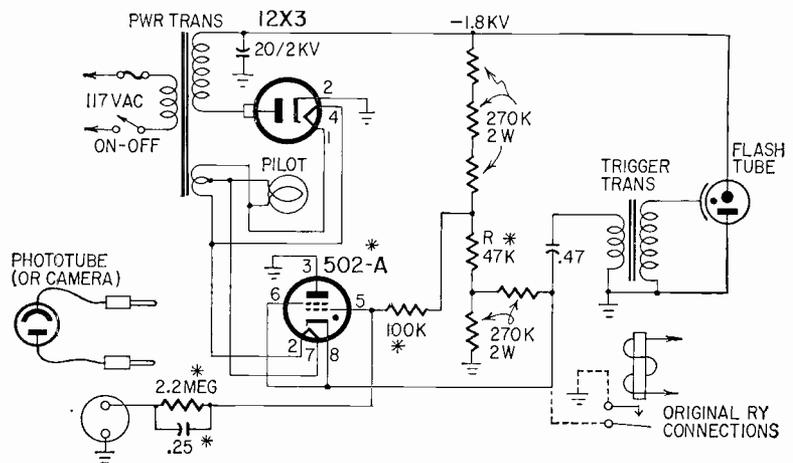

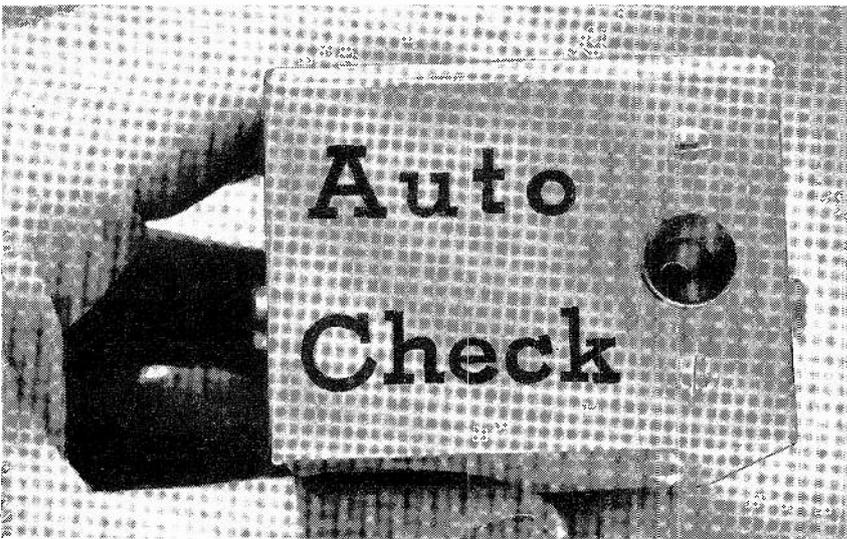

Auto Check

Fixing Auto Antennas

Knowing these tricks
can bring you customers

By DAVID HELD

Author's car radio antenna checker, built into a small two-piece aluminum box.

A TWO-TONED FORD STOPPED IN FRONT OF THE SHOP AND A well-dressed man opened the front door. "I have a car radio that quit about 10 miles outside of town. Could you look at it?"

This is the type of call we get several times a day; we're located at the edge of town on a busy highway. Auto and truck radio repair is good business, if you are prepared and equipped to do it. Of course it means climbing in and out of cars, standing on your head at times, letting dirt fall into your eyes and being smeared with oil and grease . . . so why go into it?

Several reasons. When you have a customer you've sold a TV set to, or one whose set you're servicing, you are giving him complete electronic service by fixing his car radio. That at times will help you keep him as a customer. Also, look at the customer's side of the picture. The car radio you repaired for him will lead him to call you again when his TV goes out or his kitchen radio quits.

Radio and TV business can be built up by doing car radio repair. Of course you may never again see the tourist who stops at your shop, but you have picked up a buck from outside your own community. *Don't nick him as he goes through!* Why? Down the road some 60 miles a gas station at a highway intersection recommends truck drivers to stop at your place for truck radio service. How come? Another truck driver's radio went out once and you fixed it. He told the filling station operator. Word of good service gets around.

Another reason why auto radio service is profitable is that it keeps enough work handy so your men will be busy at all times. Good service technicians are hard to find.


The auto antenna

The car radio antenna has only a few working parts, but it is vital. Without it, the radio won't work at all. A *top-cowl* antenna has four basic parts: the antenna rod, an insulator, tightening nuts and a lead-in cable. Each part must do its job, or bad reception results. These are the troubles you're likely to find:


1. Bad lead-in
2. Broken antenna mast
3. Loose connections
4. Dirty contacts
5. Shorts
6. Water leakage

When the lead-in goes bad, two things happen: There's a lot of rushing noise at maximum volume, and weak sound even on local stations. Check lead-in continuity with an


A Neat, Tight Splice in 5 Easy Steps

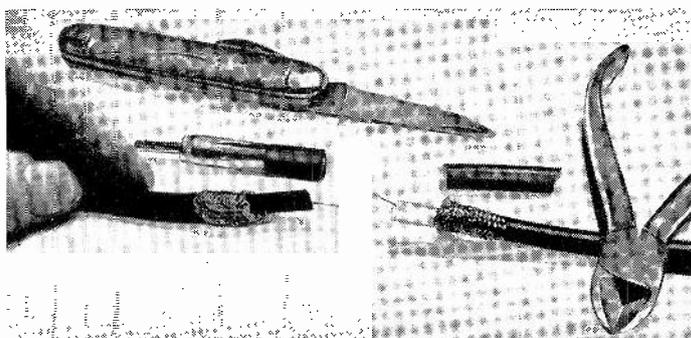

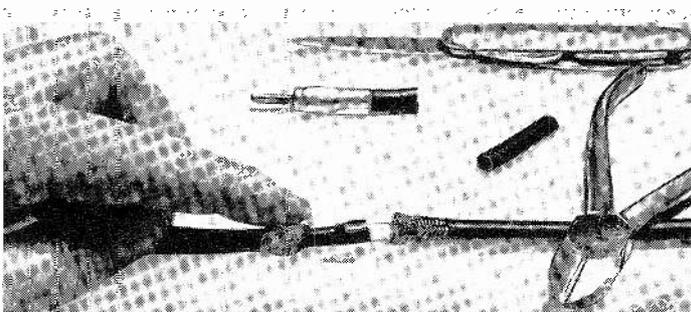
1. **Starting the splice.** Cut plug end off old cable, strip 1¼ inches of insulation off extension cable. Push braid back.



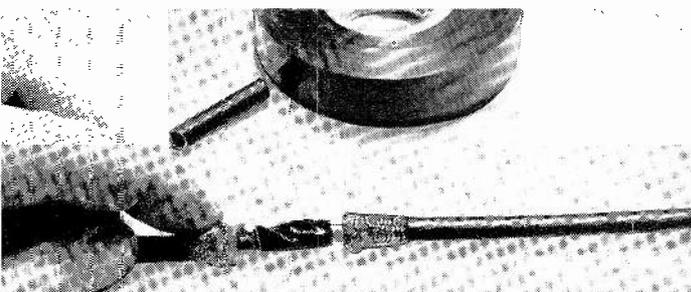
2. **Solder inner conductors together.** While joint is still hot, force soft plastic inner insulation over it.



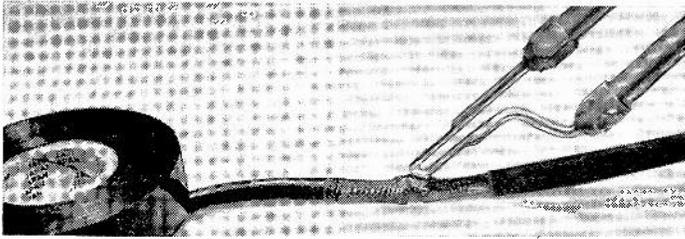3. **Wrap joint snugly with plastic tape.** Warming tape and splice slightly helps make a tight wrap.




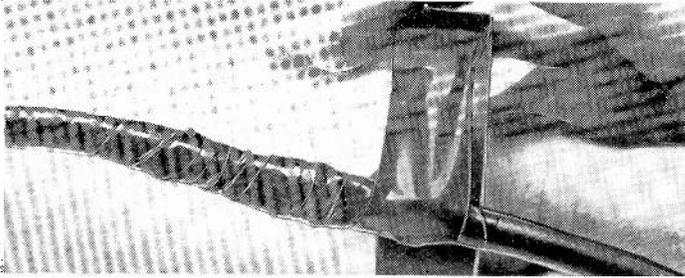4. Push metal braid ends together over joint and solder. Do not heat splice any longer than necessary.




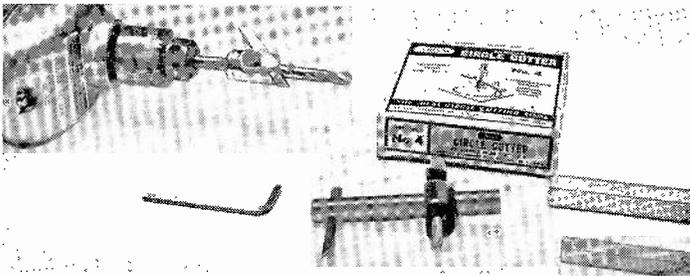5. Wrap completed splice tightly with plastic tape. Begin and end wrap at least an inch beyond point where original cable insulation was cut.


ohmmeter, or with a homemade gadget constructed as in the diagram below and the head photo on the first page. If the lead-in cable is open, it is probably open at the male plug that fits into the radio. Clip off the plug and tug on the insulated wire. If it is intact, make a continuity check. If continuity is good, replace the plug with a new one. Often the insulated wire is broken at the end where the antenna rod plugs into it. Replace the whole antenna in that case, since it is hard to match lead-ins to the many kinds of auto antennas.



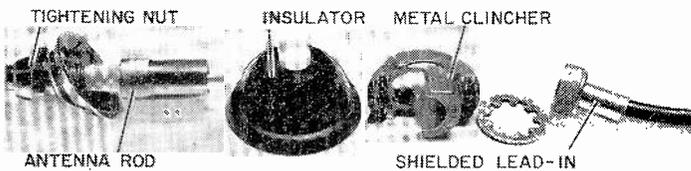Hole-drilling tools. Left, electric drill with small circle cutter in chuck. Device at right is larger circle ("flybar") cutter, also designed to be chucked in electric drill. Be sure to make sharp, small dimple with center punch at point where you want hole to prevent drill from "walking" away.



Parts of auto antenna mounting assembly.

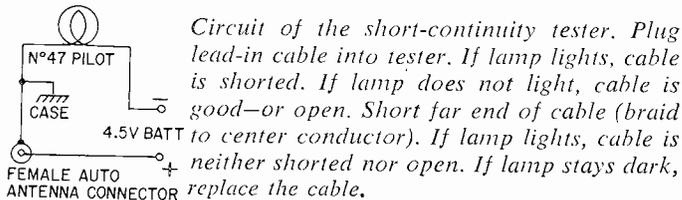

When you install an auto radio that has been pulled from another car, the existing lead-in is often not long enough. Lead-in extensions are made for this purpose, and you should always keep a variety in stock. They come in assorted lengths. If you happen to be caught without one, the photos show how to make a good extension splice.

Broken masts

If you're not sure that the car antenna is bad, plug a new antenna into the radio's antenna socket and hold it outside the automobile. Stations should come in all over the dial now if the old antenna was defective.

When the antenna mast itself is broken off, replace the whole antenna. These masts are often broken by mischievous kids, or sometimes by driving into the garage with the antenna extended. In many instances, the antenna can be replaced at no charge through the owner's insurance.

Antennas often loosen from the effects of wind and rough roads. A loose antenna assembly causes intermittent or noisy reception when the car is moving. Wiggle the antenna, with the car radio on, and this will show up at once.

When the antenna assembly becomes loose, motor noise will get into the radio reception. To determine what motor noise is being picked up by the auto antenna, unplug the antenna from the car radio. Start the motor and turn up the volume, listening for motor noise. (A little distributor noise is normal.) Plug the antenna back into the radio. If motor noise is now very loud and plain, the antenna system is picking it up. A bad lead-in, an ungrounded coax shield or a bad connection between shield bond and metal cowl can be at fault. Clean the spot where the antenna ground bites into the metal cowl of the automobile.

Mounting the antenna

When you install a new car radio antenna, watch out for several things. Be sure there is clearance for the antenna mounting assembly, and that the antenna rod will clear the car hood when it is raised. (I once saw a top-cowl antenna newly installed on a truck. When the hood was raised, the antenna mast was snapped off completely.)

There are several tools on the market designed to drill antenna mounting holes. Many commercial antennas built specially for a certain make or model car come with a template for mounting the car antenna. Be sure the antenna stands up straight and does not block the driver's view.

To be sure that the antenna is snug and tight, wiggle the rod as you tighten it. Use a wrench to tighten the chrome nut; pliers will mar the surface. A dropcloth thrown over the car fender will protect the finish from tool and belt-buckle scars. Squirt plastic cement around the hole where the cable goes through the firewall. This keeps moisture, dirt and dust out of the car.

Select (or urge your customer to select) a good antenna, moderately priced. Cheap antennas will not stand up and are very difficult to mount.

Many new cars have rear-fender antennas installed and in some cases twin fender mounts. A few technicalities are involved in repairing or installing such antennas.

Their lead-ins are long and are actually part of the radio's tuned input circuit. A front-cowl antenna can be tuned easily to the radio circuit with the antenna trimmer—set the dial above 1400 kc on a weak station and adjust the trimmer for loudest volume. But with a back-fender antenna, the lead-in is longer, resulting in increased capacitance that cannot be compensated by the antenna trimmer. Simply connect a 100-pf capacitor in series with the antenna and lead-in. Most antenna manufacturers include one in rear-fender antenna kits.

Rear-fender antennas also loosen in their mounts, and trouble often develops at the T or Y section. The inside shielded wire is easily broken at that junction. If you are in

a critical reception area, it is a good idea to use only one antenna hooked up to the radio. Use the other antenna only as a matched dummy, for looks. In some cases this may still not get enough signal to the car radio, so install a top cowl antenna on the front and leave the two rear fender-mounts for looks. It is always wise to readjust the trimmer on every auto radio as it (or a new antenna) is installed.

It is hard to match rear-fender twin antennas to the radio, because of their long cables. A "booster" helps, but to do a good job, I would rather install a universal top-cowl antenna.

Power antennas


Some of the more expensive autos have motor-driven antennas. These are operated by a dc motor or by vacuum from the engine. When you remove an antenna of the vacuum-operated kind, mark the hose connections so that they will go back onto the correct nozzles. Sometimes mud hangs on the dc motor connections and pulls them off, making the antenna inoperative. The telescoping sections become worn and begin to "flap," making reception intermittent.

One of the biggest trouble spots in a power or "disappearing" fender antenna is the point where the lead-in enters the antenna assembly. This male plug rubs against the antenna rod and doesn't make a good connection, or the connection becomes dirty. On deep-well antennas, moisture gets in, causing noisy and weak reception. An ohmmeter will show this up. Be sure that this kind of antenna is bonded well at the top and bottom straps on the antenna assembly.

In some cases, motors in the electric-powered antennas burn out, and sometimes, surprisingly, this is the fault of weak or rundown batteries. The nylon strip that raises and lowers the telescoping antenna tends to stiffen, requiring more power to move it. A weak battery will make the motor run more slowly than normal, and the user's normal reaction is to hold the switch until the antenna is where he wants it. As a result, the motor overheats and sometimes burns out.

Parts for these antennas can be picked up at automobile parts houses or ordered through them.

Many antenna gadgets are on the market — boosters, replacement antenna staffs, false antennas. There are several types of antenna boosters, one for which you cut the mast in two and install with self-contained screws. Some other types plug between antenna and lead-in. These were designed for dual rear mounts to improve long-distance reception. Some dual types claim to double the volume of regular antennas, but even with boosters they do not match the gain of front-cowl mounts. END

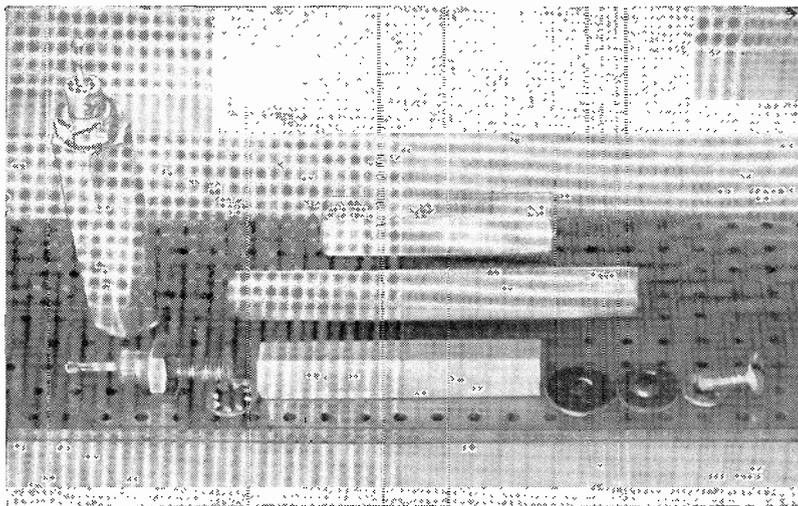

Quick and Dirty Heat Sink

By ROY E. PAFENBERG

MOUNTING TRANSISTORS AND SILICON rectifiers on aluminum or brass posts provides a neat, workmanlike method of installation and, at the same time, gives a bonus in the form of a remarkably effective heat sink.

The term "heat sink" is relatively new in the common vocabulary of electronics. Despite this, those who work with the various semiconductor devices must have a working knowledge of the subject. Semiconductors are physically small and all of them have a maximum operating temperature that may not be safely exceeded. Therefore, the power-handling capability of a transistor or diode is limited by the heat that can be radiated by the device and its heat sink.

The Sarkes Tarzian *Silicon Rectifier Handbook* states, as a rule of thumb, that each square inch of heat sink surface will radiate 8 mw of power per °C above the ambient temperature. The radiating capability of a heat sink may then be roughly approximated by:

$$P_m = \text{Area (sq. in.)} \times .008 \times T_r$$


where P_m is the maximum power radiated; T_r , the difference between the maximum operating temperature of the device and the ambient temperature in °C.

Aluminum or brass mounting posts offer several real advantages, particularly when an insulating chassis is used and the diode or transistor is operated somewhat short of the maximum rating, which might require a more elaborate heat sink. For example, calculation will show that the effective vertical surface area of a 1/2-inch diameter round post 2 inches high is 3.14 square inches. Applying the formula shows that for a maximum allowable temperature rise of

50°C, this post will radiate roughly 1.25 watts of power.

This method may be extended to supporting posts of any size and configuration. The silicon rectifiers shown in the photo mount by 10-32 threaded studs. The posts should be drilled and tapped to suit the device being mounted. A machine screw and lockwasher will secure the post to an insulated chassis. For a metal chassis, use conventional extruded insulating washers without regard for their thermal characteristics.

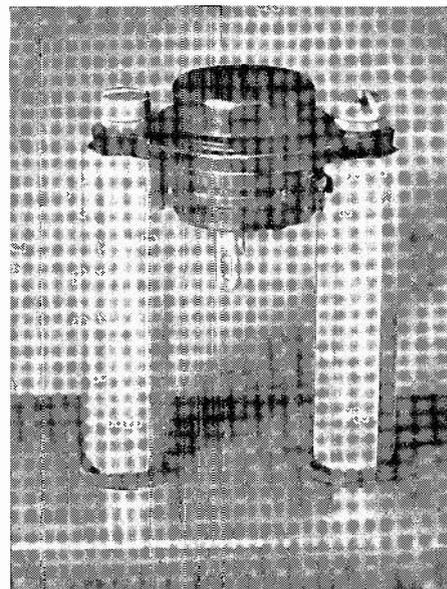While these calculations of heat-sink efficiency are perhaps oversimplified, they do produce useful approximation. The mounting methods certainly do not meet all semiconductor device mounting requirements, but they do provide a simple, low-cost answer to many difficult installation problems. END





Zener-Stabilized DC Amplifier

Zener diodes and a power transistor clamp operating voltages in this stable general-purpose dc amplifier

INDUSTRY AND RESEARCH HAVE MANY practical uses for a stable, low-drift dc amplifier: extending the range of a dc scope, reading dc millivolts direct from a bridge circuit, or as a thermocouple.

With Zener diodes, there is now an excellent way to stabilize operating voltage and current, so important for dc amplifiers. By regulating the B-plus, bias and heater supplies, I built a fairly drift-free dc amplifier (Fig. 1). These are its specifications:

1. Input impedance high, 2.5 meg-ohms.
2. Output impedance low, 500 ohms.
3. Voltage gain minimum 50, actually over 60.
4. Direct readout for static measurements. Meter used with this amplifier indicates ± 5 volts full-scale output, with an input of 20 mv per volt output when the amplifier's gain is set at 50. Meter can be switched off for dynamic operation.

By ALEX M. SCHOTZ*

5. Calibrated voltage source. It can be used to check or adjust gain. The 100-mv source is brought out to terminal post in rear.
 6. Good regulation. Power-line voltage can fluctuate from 90 to 135 without change in operation or calibration.
 7. Frequency response flat from 0 cycles (dc) to 30 kc; down 5 db at 100 kc.
 8. Output voltage before clipping approximately ± 12 .
 9. Signal-to-noise ratio at 10 vrms output better than 70 db down.
 10. Common ground input and output (galvanic ground). Polarity reverses from input to output, but can swing equally in either direction.
- Construction is simple. The heater-




A RADIO-ELECTRONICS Editor who tested Mr. Schotz's amplifier reported that it "does exactly what the author says it will. After 10-15-minute warmup, unit does not drift more than 1 or 2 divisions on the meter, apparently because of fine-voltage variations. (Each division is 10 μ .) Frequency response flat over entire audio range. When switched in and out between audio generator and scope, no apparent change in waveform. Maximum output voltage ranged between 10 and 12. Beyond that point, amplifier started to clip."

regulating power transistor is mounted on a piece of aluminum 3 x 3 x $\frac{1}{8}$ inch, painted black (except under the transistor) and "floated" above the chassis (electrically) on Lucite. Most of the small parts are placed on a terminal strip $5\frac{1}{2}$ x $1\frac{5}{8}$ x $\frac{1}{8}$ inches (Fig. 2). Take normal precautions in wiring the input; the input impedance is high.

The circuit works this way: signal voltage, either dc or ac, is applied to the input terminal and reaches the control grid of the 6AN8 pentode section via the

*Outboard Marine Research Center, Milwaukee, Wis.

New 1964 Heathkit® All-Channel Color TV

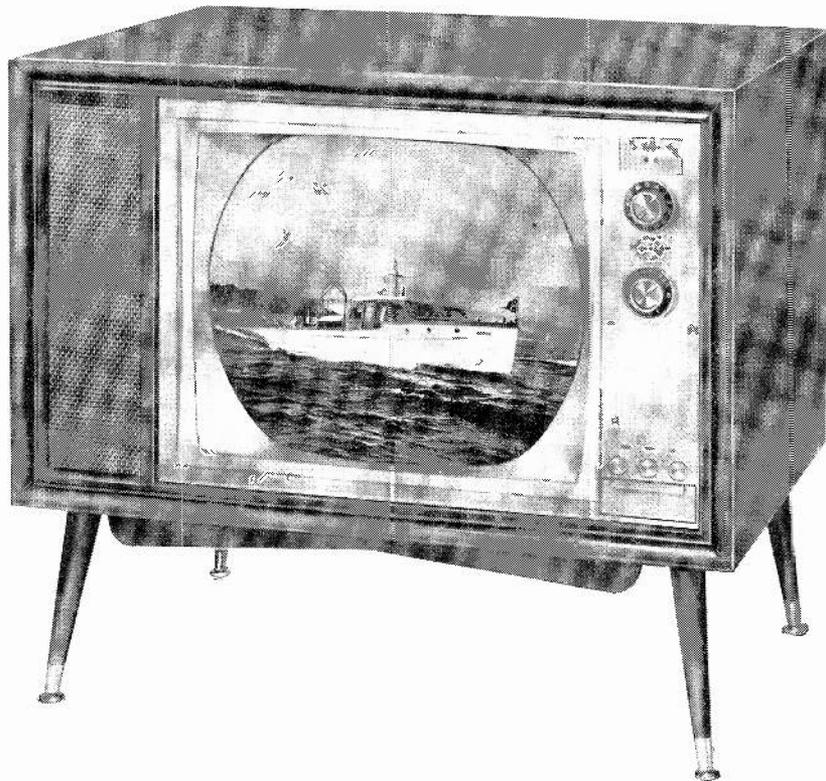

GR-53A
\$399⁰⁰

(Includes chassis, all tubes, VHF & UHF tuners, mask, mounting kit, & special speaker) cabinet optional \$49.00

Everyone Agrees It Outperforms Any Other, Is Easy To Build, & Saves Up To \$400!

Here's What The Experts Say! Popular Electronics, May issue: "The GR-53A is not a skimpy receiver in which corners have been cut to keep costs down and still provide color TV. Instead, the GR-53A (on a comparison shopping basis) has the same color and sound fidelity, flexibility, and ease of handling as those manufactured receivers which sell for over \$600."

Radio-TV Experimenter, June issue: "The repair cost savings during the Heath Color TV set's life compared to commercial units may be more than \$200."

Popular Mechanics, February issue: "Mounted, prealigned critical circuits enable beginners to assemble. Picture quality is top-notch."

Science & Mechanics, April issue: "Built-in servicing circuits such as a dot generator are valuable aids in getting the set operating for the first time & eliminating expensive service calls & bills when realignment or part replacement is needed later on."

Anyone Can Build It! No special skills or knowledge required . . . all critical assemblies are factory-built & tested . . . simple check-by-step instructions take you from parts to picture in just 25 hours! Here's what one Heathkit Color TV owner, Mr. Thomas R. McMahan of Cincinnati, Ohio says about the GR-53A manual: "I would consider the manual to be equal to a lifetime of warranties with an ordinary television."

Exclusive Built-In Service Center Eliminates Maintenance Costs! You adjust and maintain the GR-53A yourself with the degaus-

sing coil, service switch, and built-in dot generator! No more costly TV service calls! No other set has these self-servicing features!

No Expensive Service Contract! Since you maintain the set, there's no need for a costly service contract. Heath warrants the picture tube for 1 year, all other parts for 90 days!

Keep Your Present TV As A "Second" Set! Many manufacturers require your present set as a trade-in to qualify for their advertised price. With Heath, no trade-in is required! . . . your present set becomes a handy "second" set for use in den, children's room, bedroom, etc.!

Quality & Performance Comparable To Sets Costing \$600 & More! Mr. J. I. Newton of Chapel Hill, N. C. is even more enthusiastic about the performance of his Heathkit Color TV: "My friends tell me the color is better than they have seen on sets costing \$895, and I must say that I agree."

Compare These Additional Features: • 26-tube, 8-diode circuit • Deluxe Standard-Kollsman VHF tuner with push-to-tune fine tuning for individual channels, 2 thru 13 • New transistor UHF tuner for channels 14 thru 83 • High definition 70° 21" color tube with anti-glare bonded safety glass • 24,000 volt regulated picture power • Automatic color control & gated AGC for peak performance • 3-stage high gain video I.F. • Line thermistor for longer tube life • Thermal circuit breaker for component protection.

Cabinet Or Custom Installation! After assembly, just slip the complete unit into the handsome GRA-53-6 walnut-finished hard-board cabinet! Or, if you prefer, mount it in a wall or custom cabinet.

Enjoy Complete TV Reception Now! . . . by ordering the new 1964 Heathkit 21" High Fidelity Color TV!

Kit GR-53A, chassis, tubes, mask, VHF and UHF tuners, mounting kit, speaker, 121 lbs. \$399.00

GRA-53-6, walnut-finished cabinet 53 lbs. \$49.00

FREE 1964 HEATHKIT CATALOG
See these and over 250 other exciting Heathkits available in easy-to-build kit form. Save 50% or more by doing the easy assembly yourself! Send for your free catalog today!

HEATHKIT
by Components

HEATH COMPANY Dept. 20-8-1
Benton Harbor, Michigan 49023

Enclosed is \$ _____, plus freight. Please send model(s) _____.


Please send my Free 1964 Heathkit Catalog.

Name _____

Address _____
(Please Print)

City _____ State _____ Zip _____

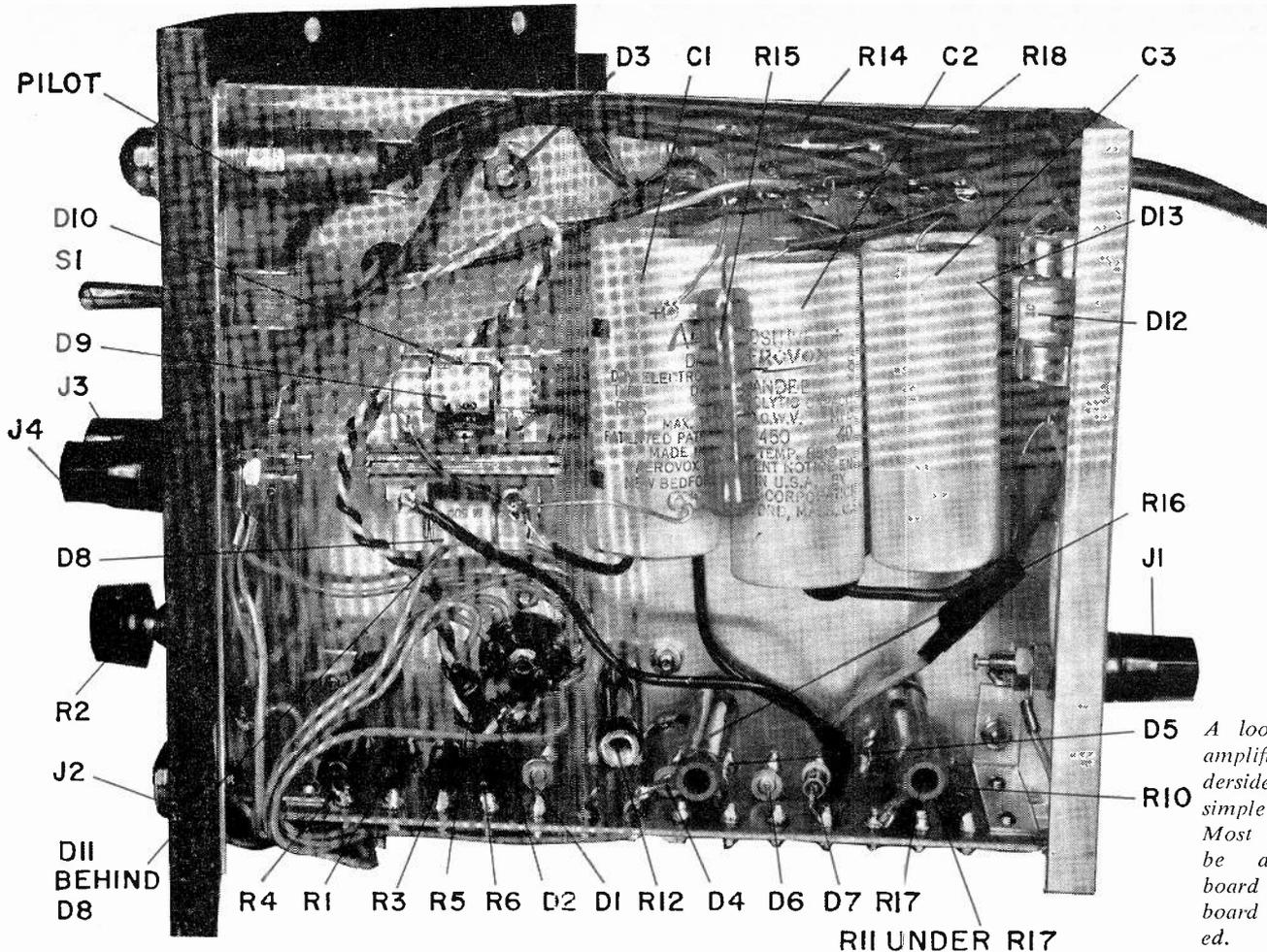Prices & specifications subject to change without notice. CL-185



A look at the amplifier's underside shows simple wiring. Most of it can be done on board before board is mounted.

- C1—500 μ f, 25 volts, electrolytic
- C2, C3—40 μ f, 450 volts, electrolytic
- D1—10-v Zener diode, 3/4 watt (International Rectifier 1N1512)
- D2, D4, D5, D6, D7—27-v Zener diodes, 3/4-watt (International Rectifier 1N1517)
- D3—5.6-v Zener diode, 3 1/2-watt (International Rectifier 1N1590)
- D8, D9, D10, D11—500-ma silicon rectifier (Sarkes Tarzian M500 or equivalent)
- D12, D13—150-ma silicon rectifier (Sarkes Tarzian M150 or equivalent)
- J1, J3, J4—5-way binding posts
- J2—coaxial microphone connector
- M—500-0-500- μ a meter (Simpson 27, or equivalent)

- Q—2N278 (Motorola)
- R1, R9—100 ohms, 1/2 watt, 1%
- R2—pot, 2.5 megohms, linear
- R3—10,000 ohms, 1/2 watt, 1%
- R4, R8—47 ohms, 1/2 watt, 1%
- R5—150,000 ohms, 1/2 watt, 1%
- R6—330 ohms, 1 watt
- R7—pot, 50 ohms, linear
- R10—2.2 megohms, 1/2 watt, 1%
- R11—15,000 ohms, 1 watt
- R12—5,000 ohms, 10 watts
- R13—10,000 ohms, 1 watt
- R14—75 ohms, 2 watts (or two 150-ohm 1-watt resistors in parallel)
- R15—5 ohms, 10 watts

- R16, R17—10,000 ohms, 10 watts
- R18—10 ohms, 10 watts
- All 1% resistors low-noise types
- S1, S2—sps toggle switches
- T1—power transformer, 135 v, 50 ma; 6.3 v, 1.5 a (Triad R-30X or equivalent)
- T2—filament transformer, 12.6 v ct, 1.5 a (Triad F-25X or equivalent)
- V1—6AN8
- Chassis, 7 x 7 x 2 inches (Bud AC-405 or equivalent)
- Cabinet to suit
- Pilot-lamp assembly and Na. 47 bulb
- Heat sink
- Miscellaneous hardware

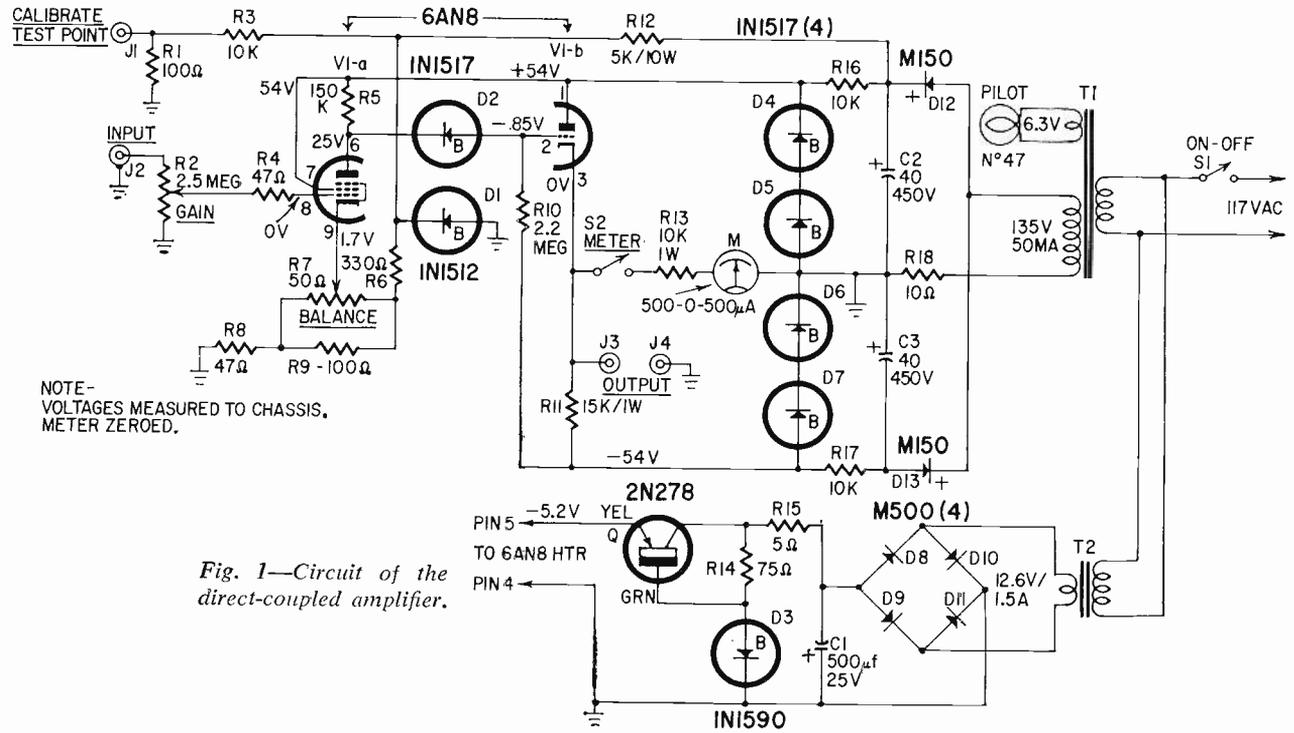


Fig. 1—Circuit of the direct-coupled amplifier.

1958...the RCA Radio-Phone Series

1959...the RCA Mark VII


1963...the RCA Mark VIII

and now 1964...

THE NEW RCA MARK NINE

the latest and greatest RCA CB radio of them all

Look at some of the new features...

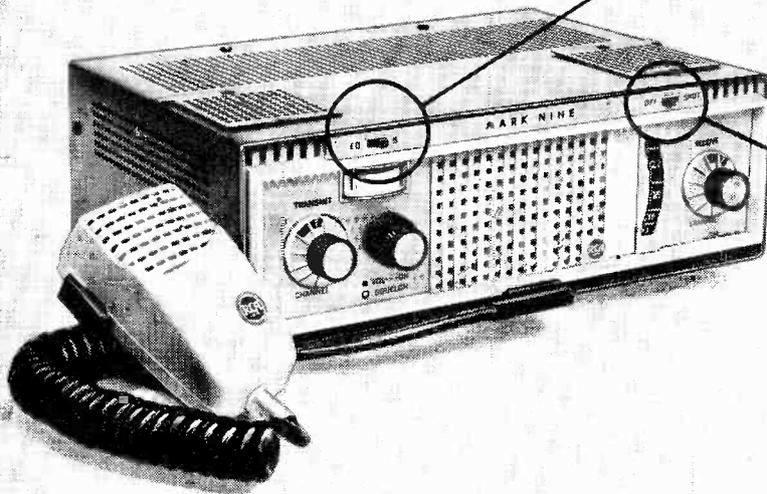

NEW! Combination "S" Meter and Relative RF Output Meter

"S" Meter indicates the relative strength of incoming signal in "S" units. RF Output Meter (EO) indicates relative strength of the signal being transmitted.

NEW! Spotting Switch

Permits precise manual tuning of receiver without use of receiver crystals. Receiver can be tuned (or "spotted") quickly to any incoming channel. This means, when you buy crystals for extra channels, you can (if you wish) omit the RECEIVE crystals and buy only TRANSMIT crystals.

NEW! External Speaker Jack

Lets you connect an external speaker to the set, so incoming calls can be heard in remote locations.

RCA, a pioneer in the development of citizens' band radio, has been providing quality equipment since the inception of the Class D Citizens' Radio Service in 1958. Now, these years of experience culminate in the great new RCA Mark Nine.

- 9 fixed crystal-controlled TRANSMIT/RECEIVE channels, separately controlled
- All-channel continuously tunable receiver
- Illuminated meter and working channel indicator
- Push-to-talk ceramic mike with coiled cord

ONLY **\$134.75** *

AC UNIT

*Optional User Price



The Most Trusted Name in Electronics

Get all the Facts Before You Buy.
Mail Coupon Today. Paste on 4¢ Post-Card


RCA ELECTRONIC COMPONENTS AND DEVICES
Commercial Engineering Dept. H 39 R
415 South Fifth Street, Harrison, N. J.

Please send more information on the RCA Mark
Nine CB Radiophone

Name _____

Address _____

City _____ Zone _____ State _____

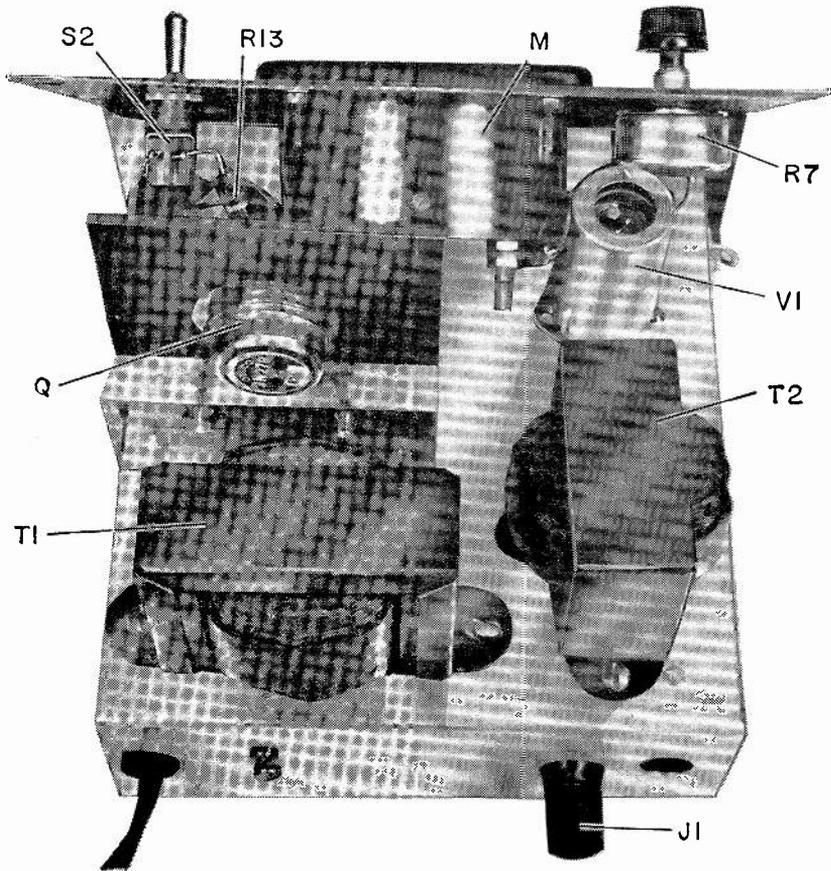

Heater-regulating transistor is mounted on sheet aluminum heat sink, insulated from chassis with clear plastic block.

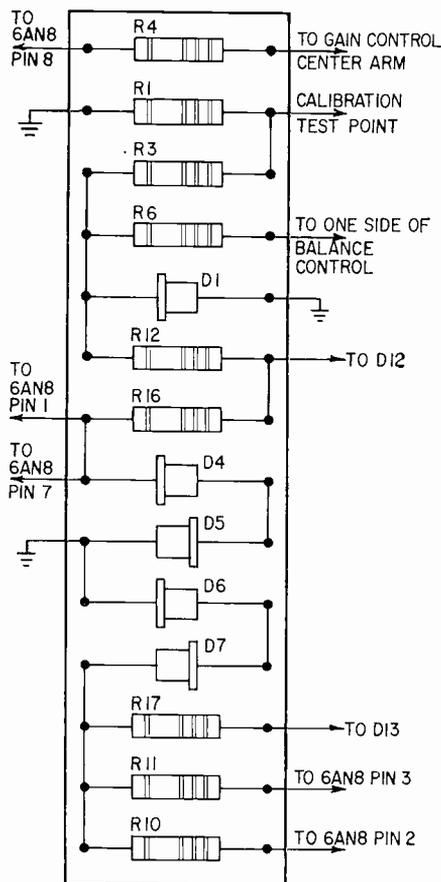


Fig. 2—Terminal board carries most of the wiring. It's optional.

attenuation control. This signal voltage is then amplified and the output from the pentode plate coupled through a Zener diode to the grid of the 6AN8 triode section. Using the Zener diode (D2) and the negative supply, puts the output of the cathode-follower 6AN8 triode section at the proper level. When the circuit is properly balanced, this permits the signal voltage to swing in either direction from ground (zero reference). With the 6AN8 triode operated as a cathode follower, the output impedance is low.


To balance this amplifier, let it warm up 10 minutes and turn the gain control fully counterclockwise. Switch the meter on, and adjust the balance control so that it shows a null (zero-center).

For dynamic output (when the signal varies) the meter should be switched off and the output applied to an appropriate readout device, like a scope or counter.

The meter can indicate potential directly from a static potential source. You can measure voltage by comparing the output from the calibrated voltage source to that of the measured point.

By presetting the gain with the calibrated voltage, the amplifier can be used as a decade amplifier, or as a millivoltmeter with a high input impedance for static potentials. END

Answers to

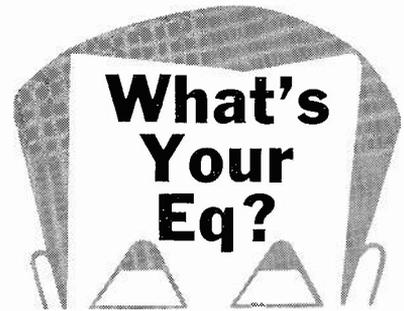

This month's puzzles are on page 47

Autotransformer


Ammeters A1 and A3 each read 10 amperes. The primary and secondary currents in an autotransformer are 180° out of phase (in phase opposition). They tend to cancel in the part of the primary winding which includes the secondary winding.

Taking into consideration a winding ratio of 2 to 1, and a secondary current of 20 amperes, the apparent primary current (and hence the apparent reading on A1 and A3) would be 10 amperes. Since the primary and secondary are 180° out of phase, the total primary current is the algebraic sum of the two, or 10 amperes.

Note: Core and winding losses are disregarded.

Case of the lost energy

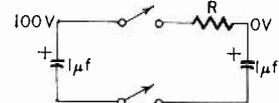This is really not as simple a problem as it looks. Suppose our problem circuit looked like this instead.




Now, for a time after closing the switch, current will flow through the resistor until the capacitor charges have become equal. Here in this resistor is a good place to get rid of energy, turning it into heat. Since we must conserve energy, the heat energy produced by the resistor evidently *must* be equal to the energy lost by the capacitors. Now what if we change R to a different value? If R gets bigger, the current flows for a longer time, but is weaker. If R gets smaller, the current flows for a shorter time, but is stronger. The energy dissipated in the resistor is *independent* of the value of the resistance and exactly equal to the difference between the initial and final values of capacitor energy.

Because of this, if we have *any* resistance in the circuit at all, we have explained where the energy went. In any practical problem, the small circuit lead

resistance would heat up and dissipate this energy. Since most energy values normally found in capacitor circuits are generally very small, this heating effect is not very noticeable. As an example, a 25-watt light bulb in 1 second dissipates or expends 25 joules of energy, or 10,000 times as much energy as that left in our capacitor problem!

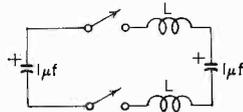This explains any practical problem. But what if there were absolutely no resistance in the circuit at all? Then there would be another way out of the problem. Near absolute zero (-460°F), we may have zero circuit resistance. But *always*, no matter what the temperature, we *must* have *some* lead inductance. Let's draw this into the circuit.



But this is a resonant circuit! It will oscillate. If it oscillates, it will radiate radio-frequency energy. And, the energy it radiates will be exactly equal to the difference between the initial and final energy in the circuit.

Any reasonable value of lead resistance will damp this circuit and it will not oscillate, so the resistance "wins" if it has half a chance.

Doodles in May

The scope trace in the May 1964 issue can also be produced by quickly moving the HORIZONTAL POSITION knob when the same frequency is put into both horizontal and vertical inputs, out of phase so as to produce a circular Lissajous figure. By noting whether the cusps are up or down, you can figure out whether the spot is moving clockwise or counterclockwise. Thus you can tell which input, horizontal or vertical, is leading and which is lagging. I have generated this pattern for the purpose many times.—Paul Penfield, Jr.


TV Sound On FM Tuner

In many parts of the country, people who have an FM section in their radios do not use it because there are no local FM stations. But it may be desirable to readjust the FM section to pick up the sound from television channel 6, if it is in use locally. There are TV programs which are interesting to listen to, such as special events and newscasts or weather reports. Blind persons particularly may wish to receive TV sound only.

The oscillator of an FM receiver may be readjusted to receive the TV sound (87.75 mc) at the low end of the dial and still pick up FM stations (you may lose a few at the high end of the band). Of course, the dial numbers will no longer be correct but for such limited use this is not objectionable.—Hugh Linebeck

SAVE VALUABLE SERVICING TIME with the Model 1400 IN-CIRCUIT CAPACITOR TESTER

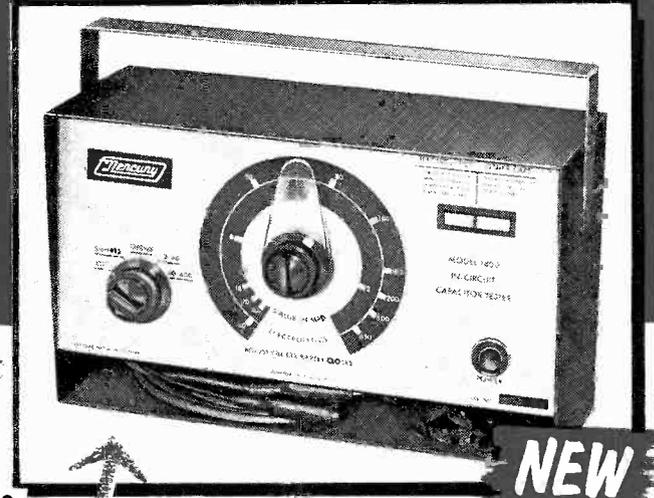eliminates the time consuming method of unsoldering and resoldering when checking capacitors



NEW

EXCLUSIVE!
Special low test voltage of 2.9 volts provided to prevent damage to the new low voltage electrolytics used in transistorized equipment

\$29⁵⁰ Net

Slightly higher in the West

FEATURES

- New, modern rectangular tuning-eye indicator...extremely sensitive and accurate
- Large, easy-to-read dial for precision readings
- Line isolated power supply... no shock or short-circuited hazards
- Special storage compartment stores coaxial cable and line cord
- Handsome two-tone metal housing
- Fully guaranteed by standard EIA factory warranty

The new Model 1400 IN-CIRCUIT CAPACITOR TESTER cuts capacitor testing time by at least 75% and enables you to service more TV sets in less time. It operates with amazing ease. You just connect the test leads across the capacitor **in-circuit** you wish to test... set the range switch and the Model 1400 automatically indicates shorted or open capacitors. It will also check electrolytics, by-pass, coupling, blocking and filter capacitors, all without **disconnecting them from the circuit!** The valuable money-making time you save with the Model 1400 will pay for it over and over again.

SPECIFICATIONS

SHORTS TEST

Detects shorted capacitors of all types **in-circuit** with shunt resistance as low as 6 ohms.

OPEN TEST

Detects open capacitors for all values **in-circuit** down to 7 mmfd., with shunt resistance as low as 150 ohms.

VALUE TEST

Indicates value of electrolytics **in-circuit** from 2 mfd. to 450 mfd.

Available at your local parts distributor

Mercury ELECTRONICS CORPORATION

manufacturers of quality electronic products

111 Roosevelt Avenue, Mineola, New York

IN CANADA: R. C. Kahnert Sales Ltd., 359 Enford Rd., Richmond Hill, Ontario

NOW! Buy or Sell with A NON-COMMERCIAL CLASSIFIED AD

- RADIO-ELECTRONICS is accepting classified ads from individuals at a new Non-Commercial Rate of 30¢ per word. (Our commercial rate remains at 55¢ per word.)
- This new non-commercial rate will enable you to buy or sell personal items or equipment at little cost.
- See the classified section for details and order form.

by Jack Darr
Service Editor

S Service clinic

A FLAT-TOP ISN'T TOO BAD AS A TEEN-age hair style, but it can play the dickens with an audio amplifier! One often unsuspected trouble, especially in fairly high-powered audio amplifiers, is clipping of the tops of the signal. This gives an unusual-sounding distortion, hard to describe but readily apparent when you listen to it. (This is the kind usually described by the customer as "It sounds Blaaaaah!") Seems to take place mostly on high-level sound. And it's quite possible for an amplifier to clip on lows and not on highs, or vice versa.

Quick check: look for it with a scope. Fig. 1 shows a sine-wave (single-tone) signal going through an amplifier with no clipping, and Fig. 2 shows the same signal with clipping. (The distortion here is actually caused by the odd-ball harmonics generated by the square-wave shape that the sine-wave signal gets made into.) This waveform was taken from the output plate, but you can check at any grid or plate all the way from the input.

Note that Fig. 2 shows both tops and bottoms of the waves clipped. This usually means that the trouble is taking place before the phase inverter or in the phase-inverter itself. Trouble in either one of the output tubes mostly shows up as clipping of either top or bottom alone. (Unless the clipping is due to simple overloads, but you can check that by reducing the input signal level.)

Common causes: drift in bias resistors, plate load resistors, screen-grid resistors, etc.; gassy tubes or tubes with grid emission in high-gain pre-amps. The most common cause, coupling capacitors with just a wee bit of leakage.

This often shows up in guitar amplifiers. Get someone to hit a chord on the guitar. This gives you several frequencies at the same time, and most of 'em are pretty pure sine waves. (I know that a lot of guitar players sound anything but pure, but that's the way they'll look on a scope!) At any rate,

set the amplifier gain as high as possible so that you can see the tops and bottoms of the waves. You may see, as I did on the last one, quite a few pretty good waves, and a few in the background with very distinct "flat-top" haircuts! This is a sure sign of distortion.

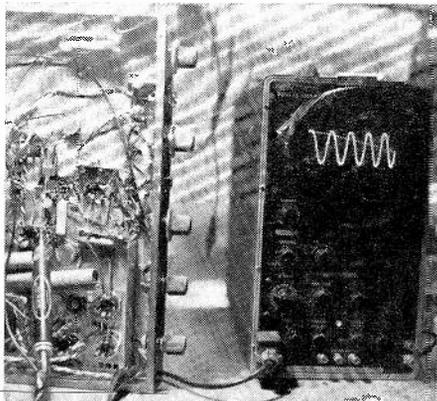


Fig. 1—Clean sine waves near amplifier's maximum output mean that it's working pretty well.

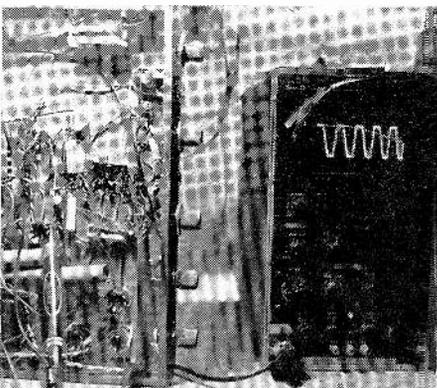


Fig. 2—Flat-topping like this is audible as harsh, gritty sound. If it isn't due just to overdriving the amplifier, look for shifted resistor values or leaky coupling capacitors.

A scope is about the only instrument that will definitely show up this kind of distortion. You won't get very much difference in the grid voltage readings, even with a vtvm, and the

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

leakage will be so small that you could even pass the capacitors on a test, but if it shows up flat-topping, I'd change the coupling capacitors on general principles.

Of course, with a guitar amplifier, sometimes the player tries to get more and more volume by cranking up the gain further. Since the amplifier can put out only its rated power, this kind of overdriving can cause distortion that isn't the amplifier's fault.

Incidentally, if you don't happen to have a tame guitar player around, you might try playing a guitar record through the amplifier. Probably better get one of the "classical" types or something like Chet Atkins, rather than some of the "surfing" type music. (That is, if you're looking for distortion, don't start out with it!)

Buzz in sound—good picture

I can't get picture and sound together on an RCA KCS-49A. Detune the fine tuner to one side of the best picture, and the sound is good. If I set up for the best picture, the sound develops a loud buzz. Could this trouble be in the tuner?—J. B., Brooklyn, N. Y.

Possible, but unlikely. The most likely cause of this trouble is misalignment, of either the sound i.f. or video i.f., or both. This kind of trouble is quite common in the fringe areas, but not too often encountered in strong-signal areas, unless it is due to age troubles.

I'd recommend setting the tuner up on a strong signal for the best picture, then trying a "twiddling" adjustment on the sound, especially the discriminator transformer. See if you can clear up the buzz. While "random experimental adjustments" often lead to trouble in i.f. stages, in this case it's worth a try. If this doesn't cure it, you're going to have to run a complete realignment of the whole set anyhow!

Check all parts and tubes in the sound i.f.'s, especially the electrolytic capacitors, and the matching of the resistors across the discriminator output,

etc. Check the 6AL5 tube for equal emission on both sides.

The video i.f.'s are a stagger-tuned 20-mc strip in this set. If you have a "droop" in the curve near the sound end, it can cause this kind of trouble. Run a single-signal alignment of the whole strip, then sweep it, to see if the curve is the proper shape.

You can check age action in this set by overriding the bias while watching the screen and setting the tuner. If this clears up the buzz, check out the agc circuit, especially the bypass capacitors in and around the tuner agc.

Vertical blanking for KCS-72

I can't find a place to get a vertical retrace blanking pulse on an RCA KCS-72 chassis. I need a negative pulse. Can I get this from the grid of the 6K6?—H. P., Minneapolis, Minn.

In this circuit, which uses an auto-transformer, you can get negative-going pulses from the grid circuit of the vertical output tube.

Feed them through a differentiating circuit consisting of something like a .002- μ f capacitor and an 8,200-ohm resistor in series. You'll need a spike of voltage, not a saw-tooth pulse. Try different part values for different circuits. If the retrace lines get worse when you connect the pulse, you've got the wrong polarity. Either reverse the polarity of the pulse or feed it to the other element of the CRT. Incidentally, blanking can be applied to the signal element, since the pulse should have no effect during picture-signal time, only during retrace time, when the beam should be blanked anyhow.

Momentary vertical roll

One of my customers complains bitterly because his TV sets rolls up a frame or two when there is a change in pictures, as when the station switches from program to commercial or from local to network programs. I've checked the set, and can't find anything wrong with it. The vertical hold is good.—A. P., Los Angeles, Calif.

This "flipping" on changes of program material isn't uncommon at all. Many sets do it, and it can be pretty difficult to stop entirely. When a TV station changes from local to network program material, there is necessarily a change in sync: from locally generated sync to network sync. Even from local live to film camera, there is a change. Each camera may have its own sync generator. So, if there is a difference of a fraction of a frame in phase between the two pictures, there will be at the very best a slight jump. If the sync catches the vertical oscillator halfway between frames, then the picture will roll up, usually.

Some of this may be due to the way the customer is operating the set. If he has a habit of setting the vertical hold so that the picture is just barely locked in, in either direction, any disturbance can cause a momentary loss of sync. Also, check the picture proportions: if the picture is overscanned vertically, stretched, it will lose a great deal of its holding ability. Set it up for about $\frac{1}{2}$ inch overscan at top and bottom, and the hold will be at maximum.

Tell the customer to set his vertical hold control near the center of its range. This will give him maximum stability, and the worst that should happen on picture changes will be a slight jump, as the new sync takes over.

You might also check the tiny vertical integrators used in this set. They are special "res-cap" combinations, and one of them could be leaking. This chassis should have very good "snap" in the vertical circuits; if it doesn't find out why.

Vertical troubles

When a Radio Craftsmen RC200 TV is turned on, the picture almost fills the screen, except for 3 inches from the bottom. After the tubes warm up thoroughly, the picture is only about 5 inches high, perfectly centered on the tube. It's in sync, showing only lack of height. Filters all good, tubes test good. Any suggestions?—D. B., Midland, Mich.

Lots of 'em! Most of this trouble is due to weak tubes. Always test them by replacement; a tube-tester reading is sometimes misleading, especially in vertical output stages.

Check operating voltages on both oscillator and output stages. I believe you're going to find a defective resistor somewhere in the oscillator stage, because you say the picture is linear, though small. The worst offender in these cases is the oscillator plate load or dropping resistor, which is sometimes the same. If the oscillator plate is fed from B-plus boost, there may be an extra dropping resistor in there, around 150,000 or 270,000 ohms. Check it for drift in value under load.

Metal-glass CRT conversion

Can I use a glass 21ZP4-B picture tube in an RCA 21T207 TV set to replace a metal 21AP4? Will the glass tube fit in the sponge-rubber mount on the front, or will I have to modify it?—C. H., San Antonio, Tex.

First question, yes. The 21ZP4-B is an exact replacement for the metal tube electrically. The -ZP4 is just a fraction of an inch longer overall.

As to the rubber mount, a lot of RCA's used a sort of plastic "socket"

affair on the front (mask) which could be converted to hold the face of a glass tube by just cutting out some parts with a good sharp pocket-knife. These were the cabinet-mounted tubes, and the straps that held the original tube can be used to hold the new one. Best way: place the cabinet face down on an old quilt, etc. Carefully set new tube down on the plastic mask. Note where cutouts need to be made, then trim the mask until the new tube drops down against it to make the front look neat. Install the straps, tighten well and the job is done.

Scott TV

I am enclosing a copy of the operating instructions for a TV set I just got in. It's a "Scott", and I can't find a schematic for the thing anywhere. Can you help me?—J. T., Brooklyn, N. Y.

Not too much, I'm afraid. However, even though I couldn't find any information at all on this brand name, I did notice one clue. On the back of the sheet you sent were the tiny letters "WG & C Series N71." This means that the set was originally built by the Wells-Gardner Co. for whoever sold it under the name of "Scott".

You can probably get the data from Wells-Gardner. Their address is Wells-Gardner Co., 2701 N. Kildare Ave., Chicago 39, Ill. Send to the service department.

If this doesn't work, try the "similarity method" we use so often. Get a schematic of another set made by Wells-Gardner using the same tubes, and you'll probably find it checks out pretty closely with the one you have.

Change Inputuner to newer type?


Is it possible to change the Inputuner on a DuMont RA-103 TV set to one of the newer types?—R. N., Brooklyn, N. Y.

Your worst trouble here will be size; the original Inputuner was pretty small. However, Standard Coil now has a line of very small tuners, and one of them should be small enough to fit this chassis. Get the new Standard Coil catalogue and check the dimensions. (Be sure you pick a 20-mc type!)

Electrically, there is only one possible change. The DuMont has the first video i.f. coil on the chassis instead of inside the tuner. Try connecting the tuner output directly to the video i.f. grid, disconnecting the original first i.f. coil. If that doesn't work, short out the coil in the tuner and reconnect the original. Give the whole video i.f. a thorough sweep alignment, and you should wind up with a very nice job. END

CASTLE

NEW
EASTERN
LOCATION

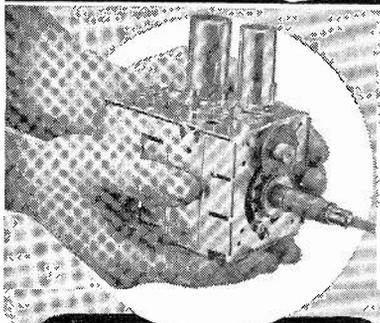

ALL MAKES
ALL LABOR
AND PARTS
(EXCEPT TUBES)*
ONE PRICE

9.95

ONE LOW PRICE INCLUDES ALL UHF
VHF AND UV COMBINATION* TUNERS

Fast Service . . . Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

90 Day Warranty
Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

CASTLE TV TUNER SERVICE, INC.

5715 N. Western Avenue, Chicago 45, Ill.

New Eastern Location

41-96 Vernon Blvd., Long Island City 1, N.Y.

In Canada: 136 Main St., Toronto 13, Ont.

*Major Parts are additional in Canada

AUDIO EQUIPMENT REPORT

Sonotone Mark IV Ceramic Cartridge

AN IMPORTANT AREA OF AUDIO PROGRESS which has not received the recognition it deserves is the recent improvement of ceramic phono cartridges. Virtually since the beginning of the hi-fi era in the late 1940's, magnetic cartridges dominated the field. Crystal and ceramic models were used mostly where low cost was more important than high fidelity. This concept has been challenged lately by a few quality ceramics offering, at a modest price, performance comparable to that of many magnetic cartridges. A case in point is Sonotone's Velocitone Mark IV stereo cartridge, model 9TAHC.



SPECIFICATIONS

(All specifications are the manufacturer's)

Frequency response: within 2 db of RIAA characteristic from 20 to 17,000 cycles. Deliberate rolloff to 20,000 cycles

Separation: 30 db

Stylus mass: 3 mg

Compliance: 15×10^{-6} cm/dyne in all directions

Tracking force: 1.5 to 3 grams for professional arms; 3 to 4 grams for changers

Output voltage: 7 mv/channel with equalizers; 0.2 v/channel without equalizers

Recommended load: 47,000 to 100,000 ohms with equalizers; 1 to 5 megohms without equalizers

Weight: 3.2 grams

Unlike most current high-fidelity cartridges, 9TAHC is a turnover design with dual-tip stylus. One side has a 0.7-mil diamond for microgroove discs, the other a 3-mil sapphire for 78's. Serious collectors who still like to spin their vintage records once in a while will find this a great convenience. The 78-rpm styli for magnetic cartridges are hard to come by, and often a cartridge change is necessary between LP's and 78's.

Taking the Velocitone from its box, you notice that no stylus guard is provided. It isn't necessary. The so-called Sono-Flex anchorage of the stylus shank in butyl rubber is so compliant that it is virtually impossible to damage the stylus. No matter how it is bent, it snaps right back into proper alignment. If the tone arm is accidentally dropped or scraped across a disc, the elasticity of the stylus mount protects the record and prevents chipping the diamond. This design makes the cartridge resist rough handling and eliminates the need for additional protective devices in the tone arm.

The high compliance of 15×10^{-6} cm/dyne in all directions accounts for the light tracking of the Velocitone Mark IV. When mounted for testing in a high-

quality tone arm (Grado), the cartridge tracked most music at 1 gram stylus pressure. It had no trouble in even the heaviest orchestral passages at inner record diameters at 1.5 grams pressure—a feat that only top-rank magnetics will equal. In automatic record changers the recommended tracking force is 3-4 grams.

Specified frequency response is 20-17,000 cycles ± 2 db with a deliberate rolloff to 20,000 cycles. When plugged directly into a high-impedance amplifier input (1-5 megohms), the cartridge automatically equalizes the RIAA recording curve. For amplifiers that have no separate input for ceramic or crystal cartridges, two plug-in equalizers are provided, one for each channel. With these equalizers on the input cables, the cartridge can be hooked up to any magnetic phono input without mismatch.

(Bear in mind, though, that old 78's were not recorded with the RIAA curve. When the cartridge is used to reproduce such discs, the bass must be reduced and the treble increased with the amplifier tone controls.)

Listening tests revealed that the character of individual instruments and of the human voice comes through quite free of artificial coloration. Despite the length of the stylus cantilever, its total moving mass is only 3 milligrams, which probably accounts for the absence of resonance peaks within the audible range. Percussive transients sound clean and snappy, without a trace of blur, and 30-db separation keeps stereo directionality clearly defined.

In A-B comparisons it seemed that the Velocitone did not quite equal the transparency of sound of the most advanced magnetic designs in heavy orchestrations. This difference was detectable only on an extremely fine speaker system. Surface noise was quiet and unobtrusive—further indication of peak-free response. Thanks to the high compliance, needle talk was very low.

Being nonmagnetic, the Velocitone cartridge is immune to hum. In hum-plagued sound systems, replacing a magnetic cartridge with a Velocitone might be advisable as a quick way to cure the trouble. And low-fi phonographs will be spectacularly improved if the Velocitone is substituted for stiff-jointed cartridges. The output of 0.20 volt per channel is sufficient without preamplification. With equalizers for magnetic inputs, the output is reduced to 7 mv so as not to overload the preamps. The cartridge can thus be used with virtually any phono amplifier.

If any criticism can be leveled against this Sonotone design, it is that the terminal pins are too close together,

NEW! Winegard BOOSTER COUPLER

A Dramatic Improvement
on an Old Favorite



MODEL
BC-208
Runs 1-4 TV or FM Sets
Replaces Model WBC4-X


ONLY
\$29.95
LIST

Winegard engineers have used two of the new 6HA5 ampliframes shielded triode tubes and new circuitry to create the all new Winegard Booster coupler that dramatically increases signal power & cuts noise to a minimum. This increased power means 8 DB gain to each of 4 outputs, reducing snow, picture smear and interaction between sets.

FM gets a boost in this new circuit as well, because it covers the entire FM Band 88-108MC. The new BC-208 Booster Coupler is another forward-looking product from Winegard . . . providing better color, black and white and FM reception. Ask your distributor or write today for spec. sheets.

Winegard Co. ANTENNA
SYSTEMS
3013-H Kirkwood • Burlington, Iowa

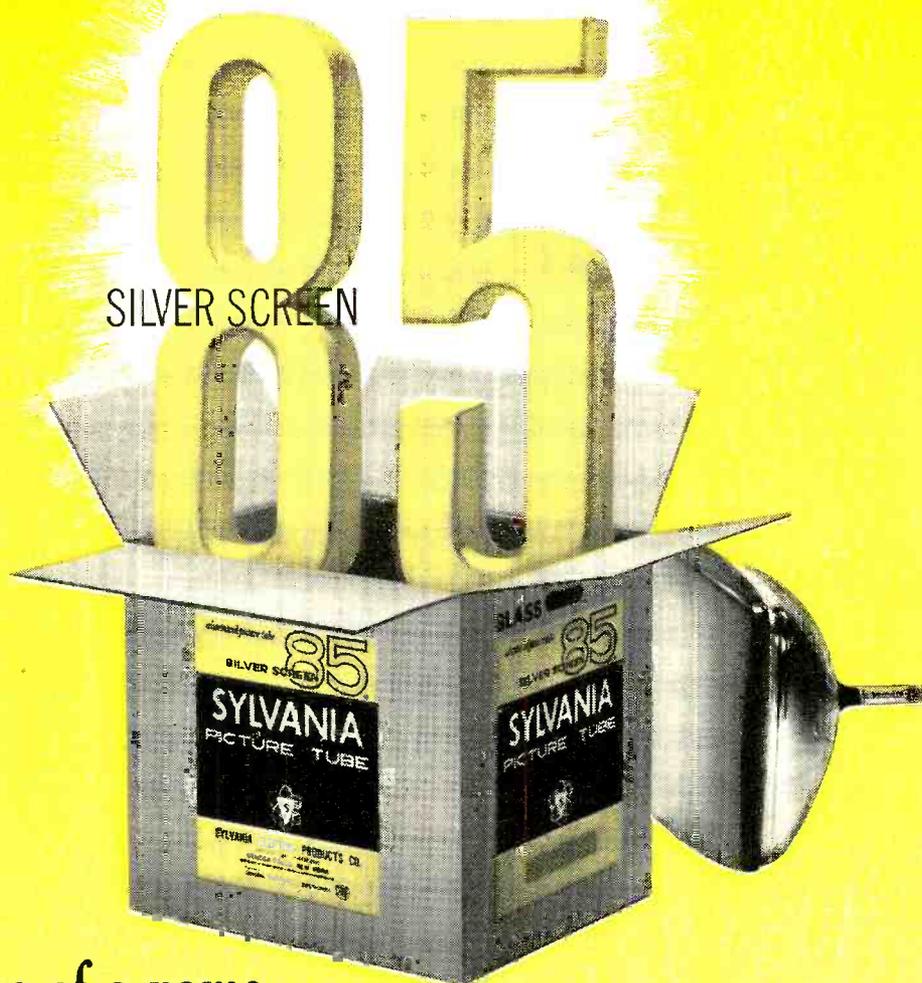you get **PRODUCT PLUS** from your Sylvania Distributor



The value of a name Dealers have long found that SILVER SCREEN® 85 picture tubes move off the shelves fast. Why? One big reason is the tube's precision-engineered features. Another is that through the years these same features have created the guaranteed acceptance of a *name*—SILVER SCREEN 85. ■ In picture tubes no brand name approaches the assured recognition of SILVER SCREEN 35 tubes. To your customers, the name means built-in quality and long life dependability. To you, SILVER SCREEN 85 picture tubes mean sales, profits, fewer callbacks, better satisfied customers. ■ Sylvania values that acceptance and safeguards it by applying every new research and development technique for product improvement. That's why the newest SILVER SCREEN 85 picture tubes have longer life and greater product uniformity. ■ Stay with the *quality* name in TV picture tubes—SILVER SCREEN 85. See your Sylvania Distributor.

SILVER SCREEN 85 picture tubes are made only from new parts and materials except for the envelopes which, prior to reuse, are inspected and tested to the same standards as new envelopes.


SYLVANIA
SUBSIDIARY OF
GENERAL TELEPHONE & ELECTRONICS **GTE**

NEW CAPABILITIES IN: ELECTRONIC TUBES • SEMICONDUCTORS • MICROWAVE DEVICES • SPECIAL COMPONENTS • DISPLAY DEVICES

TUNER REPAIRS

Includes ALL parts (except tubes)...
ALL labor on ALL makes for complete overhaul.

\$9.50

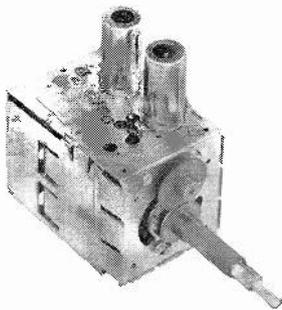

FAST, 24-HOUR SERVICE
with **FULL YEAR WARRANTY**

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, maintains two completely-equipped Service Centers, offering fast, dependable tuner repair service. Tarzian-made tuners received one day will be repaired and shipped out the next. More time may be required on other makes. Every channel checked and realigned per manufacturer's specs. Tarzian offers full, 12-month guarantee against defective workmanship and parts failure due to normal usage. Cost, including all labor and parts (except tubes), is only \$9.50 and \$15 for UV combinations. No additional costs. No hidden charges. You pay shipping. Replacements at low cost are available on tuners beyond practical repair.

Always send TV make, chassis and Model number with faulty tuner. Check with your local distributor for Sarkes Tarzian replacement tuners, parts, or repair service. Or, use the address nearest you for fast factory repair service.

S **SARKES TARZIAN, INC.**
TUNER SERVICE DIVISION

Dept. 200
537 South Walnut St.,
Bloomington, Indiana
Tel: 332-6055


Dept. 200
10654 Magnolia Blvd.,
North Hollywood, Calif.
Tel: 769-2720

making it difficult to keep the pin jacks from touching each other.

The price of the Velocitone Mark IV with diamond tip for microgroove and a sapphire for 78's is \$20.25 (model 9TAF-SDHCV). An alternate model with two diamond microgroove tips to provide double LP stylus life sells for \$24.25 (model 9TAF-D77HCV). On both models the styli are instantly replaceable.—*Hans Fantel*.

Bogen RT1000 Transistor AM-FM Stereo Receiver

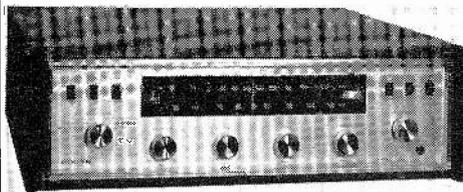THE BOGEN RT1000 IS AN IMPRESSIVE INSTRUMENT. Sounds fine, too. The only things to tip you off that it's all-transistor are the almost instant start (no warmup) and the hiss (back to that in a moment).



SPECIFICATIONS

(All specifications are the manufacturer's)
Power output: 50 watts per channel, 100 watts combined (IHF music waveform rating)
Frequency response: 15-45,000 cycles \pm 1 db
Distortion: 0.6% at rated output
Hum: -60 db
FM sensitivity: 2.5 μ V IHF
AM loop sensitivity: 75 μ V per meter for 20 db quieting
FM stereo separation: 35 db at 1,000 cycles
Monitoring output: Stereo headphones
Antenna: FM, built-in line with external connection for balanced 300-ohm feed or 75-ohm coax cable. AM, ferrite loop. External connection for outdoor antenna
Audio sensitivity: Mag. phono 3.5 mv, Tape head 2 mv, aux 0.25 v
Controls: 6-position program selector, loudness, balance, tuning, separate bass and treble, volume, low filter, high filter, tape monitor, mode, phase, afc, power, reverse, output
Output impedances: 8/16 ohms
Outputs: Speakers, tape, third-channel, headphones
Inputs: Mag phono, tape head, aux, tape monitor
Multiplex: Time-division type with "stereo-minder" indicator and tape recording filter
Semiconductor complement: 43. 22 diodes
Accessories: Walnut cabinet—model WE10 (\$29.95 extra)
Dimensions: 16-3/16 in. wide x 4-5/8 in. high x 15-13/16 in. deep, including knobs
Price: \$549.95

The RT1000 has a line-cord FM antenna built into it, and I was curious to see how it worked. Pretty well, for strong-signal locations (just what you'd expect, really). The only other qualification is that such an antenna seems more prone than even a simple dipole to multipath reception and consequent distortion in stereo. I was surprised at first, until I realized that such an antenna includes a tremendous length of wire: the set's cord itself, then who-knows-how-many feet of power wiring in the walls, and so on. And the direction of the wiring is anything but constant. But the receiver's performance with its own antenna was good enough on almost all stations in metropolitan New York to be completely satisfying.

The audio quality is crisp and up to the best modern standards. It's difficult to find anything new to say about it; it's

not really distinguished in any particular way. That's probably the highest compliment one can pay an audio instrument.

Again—a qualification. The hiss I mentioned at the beginning of the report is common to many all-transistor amplifiers and receivers. In this one, it is present even at zero volume, like a faint surf noise. It is more prominent with the volume (loudness) control turned up, but of course it is often masked by program material. Not always, though. At moderate volume settings, during soft musical passages in a quiet room, it is definitely noticeable. More so with earphones.

An unusual feature of the Bogen RT1000 is the way some circuit functions are switched. Pulling the loudness control knob out turns the control into a straight, uncompensated volume control. Pulling out the treble control knob switches in a treble filter (with a sharp pop!). Pulling the bass control puts in a low-cut filter. And (I think this is an especially nice touch) pulling the balance control reverses the channels! This approach increases control flexibility without making the panel look like something out of a spaceship.

If any one thing could be singled out to distinguish the RT1000, it would be that control flexibility. The receiver has about every control and switch feature that could possibly be useful, including afc defeat, channel phase, tape monitor, speaker on-off, in addition to the pull-knob ones! Exception: no stereo noise filter. Front-panel headphone jack, though, which is good for a gold star in my book.

The RT1000 can receive AM, too. Why, I don't know. After spending half an hour or so listening to FM and FM stereo, I switched to AM and was greeted by a mixture of fluorescent-light hash and motor noise, salted with a few dozen treble-less stations. About half of them could be received painlessly with perfect clarity on FM. The RT1000 has no whistle filter.

On the back of the chassis are loud (visual) warnings not to short the speaker terminals. Good idea, for a shorted output is the easiest way to do-in a transistor amplifier in milliseconds. The manufacturer meets the user halfway by spacing the terminal screws an inch apart, making it practically impossible to get a stray wire strand snuck out from under one screw to touch the other. In case someone manages nevertheless, there are fuses.

The back of the chassis also bears a "third-channel" output jack, for connecting a center-channel speaker or mono extension (remote) speakers.


The manual with the receiver is concise but comprehensive, rounding out the favorable overall impression I had of the RT1000.—*Peter E. Sutheim*

ALL NEW

better than ever!

Genuine

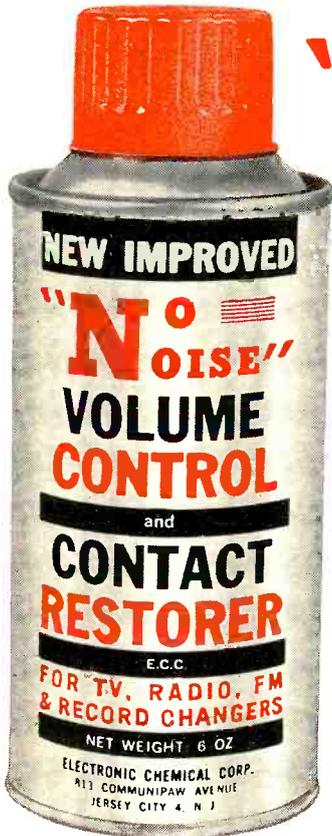"NO NOISE" VOLUME CONTROL and CONTACT RESTORER



▶ **WON'T AFFECT PLASTICS**

▶ **NON-TOXIC** ▶ **NON-FLAMMABLE** ▶ **NO CARBON TET**

CLEANS, LUBRICATES, RESTORES AND PROTECTS

FOR TV, Radio, FM . . . Volume Controls, Band Switches, Relays, Push-Button Assemblies, Electrical Contacts. Does NOT HARM precious metals . . . does not change capacities. DOES PREVENT gumming, eliminates binding on automatic record changes. ECONOMIC — A little Does A Lot!

\$2.25

AVAILABLE ONLY IN 6-OZ. SPRAY CANS

net to servicemen

IN STRICT CONFORMITY WITH ALL FEDERAL, STATE AND MUNICIPAL LAWS & REGULATIONS

Backed by 15 years of solid experience, the original "No Noise" products retain leadership in the field with an all-new, better-than-ever product! Imitated by many, equalled by no other product for **OUTSTANDING QUALITY.**

Experienced servicemen the land over insist on the genuine "No Noise" products . . . Never misled by cheap imitations, ineffective and sometimes dangerous by-products.

ALL NO-NOISE AEROSOL PRODUCTS ▶ **WON'T AFFECT PLASTICS**

▶ **NON-FLAMMABLE** ▶ **NON-TOXIC** ▶ **NO CARBON TET**

"NO NOISE"



Tuner-Tonic with Perma-Film

WON'T AFFECT PLASTICS

- Economical — a little does a lot.
- Cleans, lubricates, restores all tuners — including wafer type.
- Non-toxic, non-inflammable.
- Use for TV, radio and FM.

6 OZ. SPRAY CAN **\$3.25**
net to servicemen

New 1964 Jobber Plan!
Ask Your Rep. For Details

NO PRICE INCREASE!

Only With
"NO-NOISE" Aerosol Products
free

5" PLASTIC EXTENDER
with Push Button Assembly

Fastens easily and securely for the finest pin-point applications. Invaluable on all kinds of jobs. Positively won't cause shorts.

ALL PRODUCTS SOLD WITH MONEY-BACK GUARANTEE

ALL FREIGHT PREPAID

Buy EC-44 FOR ALL ELECTRICAL CONTACTS
new formula



EC-44

\$3.50

- net to servicemen
6 OZ. SPRAY CAN
economical
a little does a lot
- **LUBRICATES**
 - **CONDITIONS**
 - **CLEANS**
- All Electrical Contacts

ELECTRONIC CHEMICAL CORP. 813 Communipaw Ave. Jersey City 4, N. J.

NEW SAMS BOOKS

Introduction to Microelectronics & Integrated Circuits

by *Allan Lytel*. Provides a clear explanation of this increasingly significant development. Tells you what microelectronics is, how these astonishingly small integrated circuits are designed, how they work, and how and where they are used. Includes special glossary of terms to help you understand and work with miniature components and circuits. Chapters include: What is Integrated Electronics; Integrated Circuit Design; Printed Circuits; Micromodules; Microcomponents; Linear Circuits; Digital Circuits. 160 pages; 5½ x 8½". **\$295**
Order **ICL-1**, only.

Science Projects in Electricity/Electronics

by *Edward M. Noll*. Like the two preceding volumes in this series, this new book presents useful construction projects which help the experimenter to learn basic principles as he builds. Each individual project, when completed, is a useful piece of equipment. Detailed drawings, numerous photographs, and complete parts lists make construction easy. Projects include: Audio Power Amplifier; Crystal-controlled RF Oscillator; RF Amplifier; FM Tuner and Antenna System and others. A valuable and instructive book for hobbyists, students, and do-it-yourselfers. 128 pages; 5½ x 8½". **\$295**
Order **SPN-1**, only.

Tape Recorders—How They Work—New 2nd Edition

This popular book for tape recorder owners and repair technicians has been fully revised and completely updated. Explains the principles of magnetic recording; covers mechanisms and components; describes the various types of tape recorders; gives test procedures. Comprehensive and easy-to-read. Includes numerous illustrations and charts. A valuable reference book for everyone interested in tape recording. 224 pages; 5½ x 8½". **\$395**
Order **TRW-2**, only.

Electronic Gadgets for Your Car

by *Len Buckwalter*. This practical projects book includes complete instructions for building numerous electronic gadgets for automobile use. Projects include a tachometer, a transistorized battery checker and charger, a handbrake protector, and other practical automotive electronic devices. Do-it-yourselfers and auto mechanic hobbyists will find this a fascinating book. All projects are easy to construct; parts used are readily available. 128 pages; 5½ x 8½". **\$295**
Order **CAR-1**, only.

Microwave Test & Measurement Techniques

by *Allan Lytel*. The first comprehensive book on microwave tests and measurements. Clearly written for easy understanding by technicians, engineers, and students. Of special value to technicians interested in entering the microwave field. Fully describes microwaves; covers the various applications; explains how to test and measure microwave power, impedance, attenuation, frequency, noise, etc. Includes special chapters on radar equipment and microwave tubes. 224 pages; 5½ x 8½"; hard-bound. **\$695**
Order **MIL-1**, only.

Closed-Circuit Television Handbook

by *Leon A. Wortman*. Now—an authoritative guide to closed-circuit TV systems and applications. Absolutely the most comprehensive book on the subject. Provides a complete explanation of closed-circuit TV, the equipment used, applications in every conceivable field. Covers microwave relays, circuits, and service. Easily understandable for the interested nontechnical reader; invaluable for technical personnel involved in planning, installing, operating and maintaining CCTV. Fully illustrated and indexed. 288 pages; 5½ x 8½"; hardbound. **\$695**
Order **CLC-1**, only.

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. RE-8, 4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:

- ICL-1 TRW-2 MIL-1
 SPN-1 CAR-1 CLC-1

\$_____ enclosed. Send FREE Booklist

Name _____


Address _____

City _____ Zone _____ State _____

My Distributor is _____

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

test equipment reports

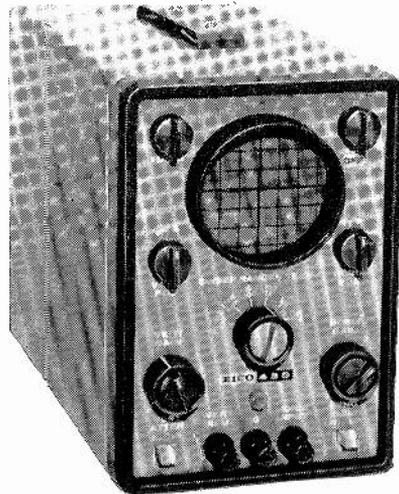

Eico 430 general-purpose oscilloscope

THIS 3-INCH SCOPE IS TRULY PORTABLE. It weighs but 11 pounds and takes about as much room as 24 issues of RADIO-ELECTRONICS (8½ inches high, 5¾ inches wide and 11¼ inches deep). The front panel is smaller than that of some vtvm's.

To make this size possible, front-panel controls have been reduced to a minimum for the simplest possible operation and less confusion. It's very difficult to grab the wrong knob when you're in a hurry. Automatic sync eliminates the sync-gain control.

There is a MuMetal shield around the neck of the 3-inch flat-faced CRT. This reduces the effects of external magnetic fields—the scope's power transformer and others nearby as well as things like motors and fluorescent light ballasts.

The 1,500-volt power supply gives a sharp, bright trace with no "blooming". Intensity and focus controls are on

the front panel. Astigmatism adjustments can be made without removing the cabinet.

The intensity modulation input has an impedance of 2 megohms shunted by 25 pf.

The preamplifiers and sweep oscillator are powered from a voltage-regulated point on the power supply bleeder. The sweep amplifier tubes use 400 volts B-plus, unregulated.

The vertical amplifier is flat from 2 cycles to 500 kc and down 6 db at 1 mc. The sweep sensitivity is 25 mv per centimeter. Input impedance is 1 megohm shunted by 30 pf, through a switchable 100:1 coarse attenuator into a cathode follower. Putting the "fine" gain control at the cathode-follower output increases the high-frequency response.


Vertical centering will let any part of the trace be centered on the CRT even when the vertical gain is set high enough to make the trace more than three times the CRT diameter. Such an expanded trace give details equivalent to the trace on a 9-inch CRT.

Expanded traces on the horizontal sweep are only twice the diameter of the CRT face. The horizontal amplifier is flat from 2 cycles to 350 kc with a sensitivity of 250 mv per centimeter.

The sweep selector has four overlapping ranges of sawtooth sweep from 10 cycles to 100 kc as well as 60-cycle sine-wave sweep. The four sawtooth sweep ranges have full retrace blanking with a choice of internal or external synchronization. The external sweep input is also selected by the sweep range switch.

The frequency response of the vertical amplifier is sufficient for most hi-fi, radio and black-and-white TV work. It can be used with a sweep generator for i.f. alignment. Video-signal and sync-pulse waveform observations will not be distorted by what may seem to be too low a high-frequency limit (500 kc). The color-burst frequency (3.85 mc) will not

Fig. 1—Compactron type 6D10 triple-triode is used in Eico 430 as sawtooth sweep generator, blanking pulse generator and automatic sync.

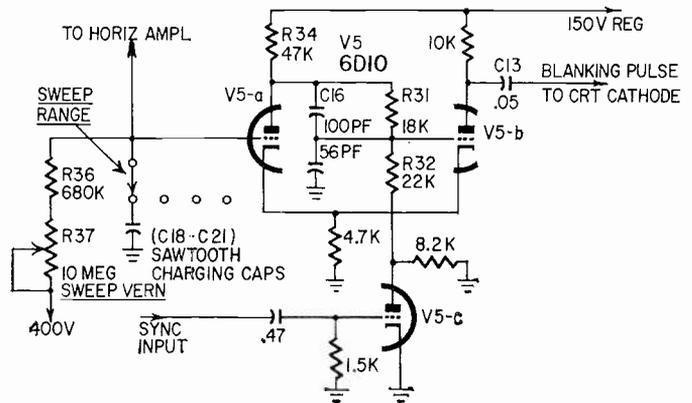


FREE

MAIL
CARD
TODAY

WORLD'S LARGEST ELECTRONICS CATALOG

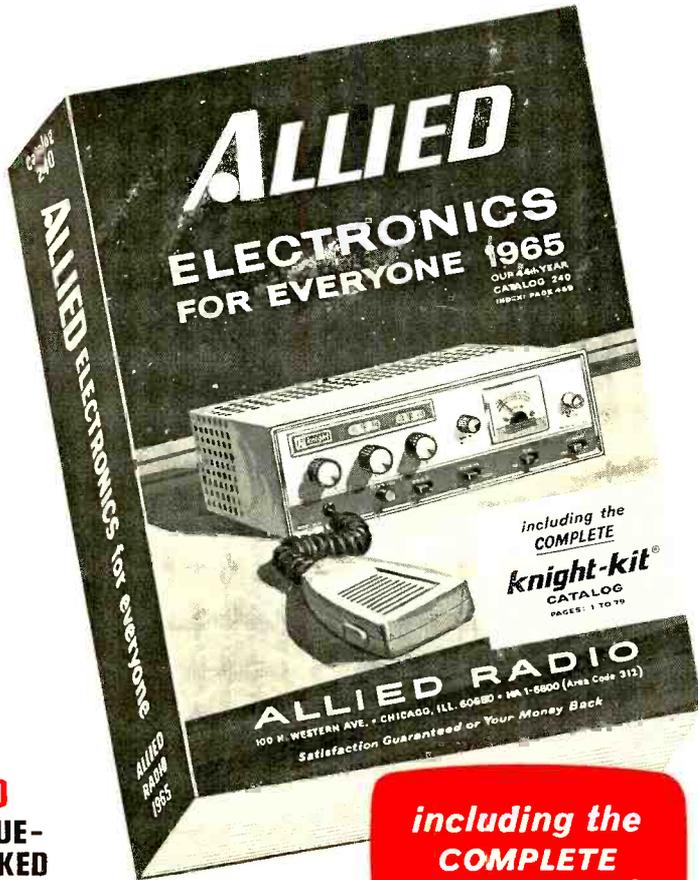WITH THE BIGGEST SAVINGS IN ALLIED'S HISTORY



490
VALUE-
PACKED
PAGES

including the
COMPLETE
knight-kit[®]
CATALOG

send today for your money-saving

ALLIED 1965 CATALOG

BIGGEST SELECTION • BIGGEST SAVINGS ON:

PLUS

**SPECIAL PRODUCTS
AND EXCLUSIVE
VALUES AVAILABLE
ONLY FROM**

ALLIED

EXTRA! BARGAIN PARTS SECTION!

satisfaction guaranteed or your money back

EASY TERMS: Use the Convenient Allied Credit Fund Plan

**SEE
OTHER
SIDE**

For your FREE 1965 ALLIED Catalog, fill in card, detach and mail now. (Please give other card to an interested friend.)

**SEND
CARD
TODAY**

MAIL
NOW

Name _____
PLEASE PRINT


Address _____

City _____ Zone _____

State _____

2-H

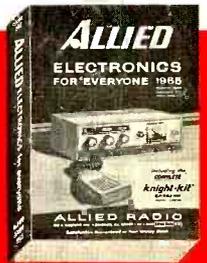SEND CARD TODAY
for your
FREE
ALLIED
1965 CATALOG



LOWEST PRICES ANYWHERE!

Name _____
PLEASE PRINT


Address _____

City _____ Zone _____

State _____

2-H

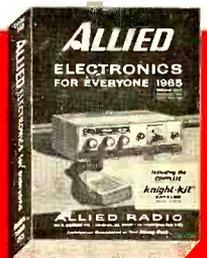SEND CARD TODAY
for your
FREE
ALLIED
1965 CATALOG




SAVE AS NEVER BEFORE!

FREE

send for your money-saving

ALLIED 490-PAGE

1965 ELECTRONICS CATALOG

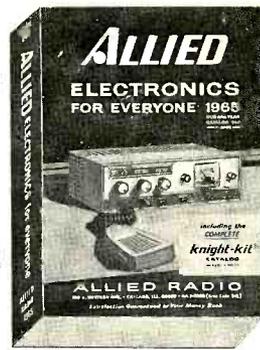

MAIL NOW

WORLD'S LARGEST • BIGGEST SELECTION
WITH THE BIGGEST SAVINGS IN ALLIED'S HISTORY!

1965 *knight-kits*[®]—save more than ever



NEW
Electronic Exposure Meter—ultra-sensitive, professional performance




NEW
Electronic Auto Analyzer for troubleshooting ignition systems

NEW
KG-834 Solid-State 54-Watt Stereo Hi-Fi Amplifier—at amazing low cost



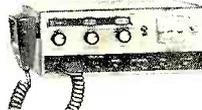NEW
King-size 6" VTVM—tops in accuracy at the lowest price



NEW
C-560 Deluxe CB Transceiver with transistorized power supply

See many other outstanding do-it-yourself kits: Hi-Fi, Hobby, Citizens Band, Amateur, Intercom, Test Instrument—wonderfully easy to build—savings up to 50%.

NEW STEREO HI-FI—most for your money



NEW
Knight KN-330 Stereo Hi-Fi Receiver—top performance at a new low price




NEW
Knight KN-990A Deluxe Hi-Fi Record Changer at tremendous savings



NEW
Knight KN-2350 Speaker System—acoustic suspension type at lowest cost

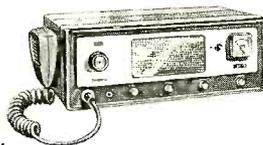CITIZENS BAND TRANSCEIVERS—top values in CB



NEW
Knight KN-2565 23 Channel CB Transceiver—a deluxe performer at big savings



NEW
Knight KN-2580 8-Channel CB Transceiver, with transistorized power supply

PLUS: Tape Recorders and Tape • Phonographs & Accessories • FM-AM and AM Radios • Ham Station Equipment • Test and Lab Instruments • Automotive Electronics Equipment • PA Systems and Intercoms • Top Values in Power Tools, Soldering Guns, Hardware • Biggest Selection of TV Tubes, Antennas, Parts, Tubes, Transistors, Books... everything in Electronics for everyone.

FREE

SEND CARD TODAY FOR YOUR 1965 ALLIED CATALOG, and give one card to an interested friend.

satisfaction guaranteed or your money back

EASY TERMS: Use the convenient Allied Credit Fund Plan to make your purchases.

ALLIED RADIO

100 N. Western Ave., Chicago, Illinois 60680

TO:

ALLIED RADIO

P. O. Box 4398

CHICAGO, ILLINOIS 60680

PLACE
STAMP
HERE

TO:

ALLIED RADIO

P. O. Box 4398

CHICAGO, ILLINOIS 60680

MAIL NOW

PLACE
STAMP
HERE

be visible—it is too far out of the amplifier bandpass.

Jacks and a switch make it easy to connect directly to the vertical deflection plates for making percentage-modulation tests on AM transmitters.

For technicians who have never used a scope with automatic sync, this unit will be a surprise and a treat. The juggling of the horizontal sweep vernier and sync-gain controls to get a stationary trace has been eliminated. All waveforms snap right in as long as the horizontal sweep isn't set too far off frequency.

This pleasure is made possible by a circuit using the 6D10 triple triode (Fig. 1). The three triodes provide the sawtooth sweep, retrace blanking and automatic sweep synchronization. Switches have been eliminated to simplify the circuitry.

The sawtooth charging capacitors are in the grid of V5-a. Whichever is selected charges through the 10-meg sweep vernier control (R37) and R36 across the 400-volt source.

When the grid of V5-a becomes positive with respect to the cathode, the capacitor discharges through the tube which, at this instant, might just as well be a diode—with the grid acting as an anode (plate). This discharge (the retrace) and the slow-charge waveform are fed to the horizontal amplifier.

The current flow during this discharge causes a voltage drop across R30—cutting off both V5-a and -b. With V5-a cut off, the voltage at the plate of V5-a rises and makes the grid of V5-b more positive (through R31 and C16). The current flow through R30 and V5-b keeps V5-a cut off and allows the sawtooth charging capacitor to charge.


When the voltage on the grid becomes more positive than its cathode, the capacitor discharges—starting the sweep cycle over again.

When both V5-a and -b are cut off, the voltage at the plate of V5-b rises sharply. The pulse drives the cathode of the CRT more positive (through C13) in relation to the CRT grid and the electron beam is cut off—the tube is “blanked” during the retrace.

The sync-control triode (V5-c) also controls the bias on V5-b. When V5-c is driven into conduction by a positive synchronization pulse on its grid, the voltage drops across R34 and R31 increase. This makes the grid of V5-b less positive. With the grid of V5-b less positive, the flow through the tube drops and V5-a can conduct sooner. When the capacitor discharges through V5-a, the sweep oscillator cycle starts. V5-c controls the point at which the retrace starts.

The Eico model 430 is priced at \$65.95 as a kit, and at \$99.95 wired.—*Elmer C. Carlson*

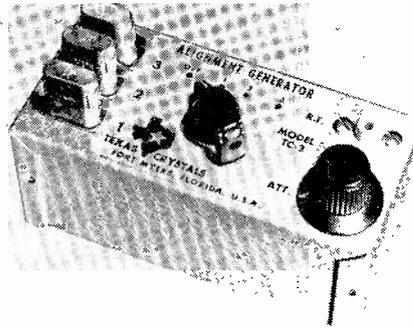Texas Crystals Alignment Generator Model TC-3



TEST SIGNALS ARE VERY HANDY BUT they must be accurate. The crystal oscillator is the easiest way of getting accuracy. Texas Crystals' TC-3 test oscillator can provide any three selected frequencies between 200 kc and 3 mc, with crystal accuracy. Many harmonics are also usable, as with any crystal oscillator like this.

Literally small enough to be held in the palm of your hand—and transistorized, of course—the TC-3 uses a standard 9-volt battery. Three small standard crystals are plugged into the row of sockets on the left end, and a combination on-off switch and crystal selector is in the center. A 250,000-ohm pot is used as an attenuator, and rf output varies from 100 mv at the high end of the range, around 3 mc, to 500 mv at the low end. Rf output is taken from a standard phono type coaxial jack; a 50-pf blocking capacitor in series with this cable is recommended, just in case you happen to hit a high-voltage point in the circuit under test!

This unit may be ordered with any three crystals in its range. Each is calibrated at the factory, and the actual frequency is entered on the instruction sheet. I chose a 1-mc crystal, which was given as 1,000.004 kc (well within the .002% tolerance claimed by the maker). Beating the 10th harmonic of this against WWV on 10 mc, I could hear an audio beat note which was very close to 40 cycles, without making a precision measurement. This accuracy is ample for all service shop usage, and the stability is excellent. I left it hooked up for about 15 minutes on zero-beat with WWV, and the drift wasn't perceptible to the “naked ear.”

An instrument like this could be very handy in the shop, especially for remote use: auto radio, two-way radio and such. We aligned a car radio, in the car, as a test, on 260 kc, checked the low i.f. of a two-way FM receiver at 455 kc, in the car, with the greatest of ease. CB radio work could be made easy by choosing the special 2708-kc “Frequency Spotter” crystal offered; crystals for


New Semiconductors and Tubes

Now: 10-pin miniatures

Four new standard-size miniature tubes with 10-pin (“decad”) bases have been announced by Amperex. The tubes originated in Holland with the Philips Co.'s Electron Tube Div.

The four tubes are the 6X9, 6U9, 6W9 and 6V9.

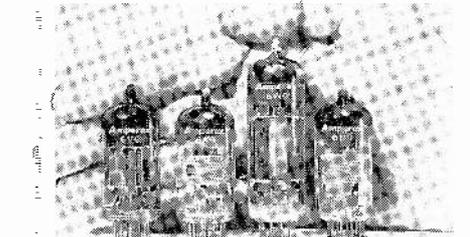Why the 10-pin bottoms? The extra connection is used to get greater flexibility of internal element design and



connection. For example, in the 6X9/ECF200, a triode-pentode, the pentode's suppressor is connected, together with an internal inter-section shield, to a separate base pin, and not to the cathode as in earlier designs. Thus it and the shield can be grounded, to give less interaction between sections. The same structure applies to the 6U9/ECF201.


The EFL200 (6W9) is a double pentode. The “F” (voltage-amplifier) section can be used as a sound-i.f. amplifier.—*(continued on page 72)*

any CB channel (on the appropriate harmonic, of course) could also be used, as could the i.f. crystals. The signal is not modulated, but you can get indication of output from the set in several ways: in FM receivers by using the built-in grid-current metering system, in CB sets with a vtvm on the avc line, etc.

Battery life should be good, if you remember to turn the oscillator off each time you're through with it! By the way, this would be a dandy instrument for setting up antenna trimmers on CB rigs, after installing them in the car. You can put a small radiator on a phono plug, hook it to the TC-3 and then set the thing on the fender, so that it radiates a weak signal into the antenna. This will allow peaking the trimmer very precisely, since the signal strength can be adjusted by moving the oscillator farther away or nearer.

Price of the Texas Crystals TC-3 is \$29.95 complete with three crystals.—*Jack Darr*

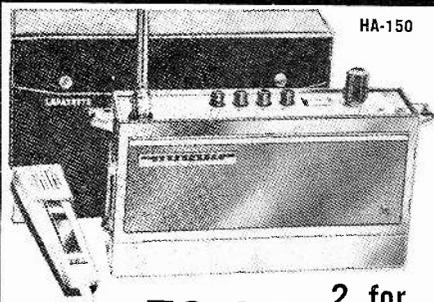NEW! LAFAYETTE 1-WATT 2-CHANNEL SUPER CB "WALKIE TALKIE"



79.95 2 for **154.95**

- Lightweight, compact . . . Self-contained with Leather Case and Shoulder Strap
- External Push-to-Talk Dynamic Microphone
- Powerful 13-Transistor 5-Diode Circuit
- Modulation/Battery Strength Meter
- Push-Button Operation
- Powered by Flashlight Batteries or External 12 VDC Supply
- Complete with 2-Pair Transmit/Receiver Crystals Imported

Free! Lafayette's 1964 Catalog No. 640

422 Giant-Size Pages Everything in Electronics, Hi-Fi, C.B., Test Equipment, Amateur Gear, TV and Radio Parts, and much more.





LAFAYETTE Radio ELECTRONICS
Dept. JH-4 P.O. Box 10,
Syosset, L.I., N.Y. 11791

- Rush me FREE Walkie-Talkie \$. Enclosed Shipping Charges Collect
- HA-150L Walkie-Talkie \$. Enclosed Shipping Charges Collect

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

fier, agc amplifier or sync separator. The "L" (power) section is designed as a video output stage, and can provide 100 volts of composite video signal with a plate load of 2,000 ohms.

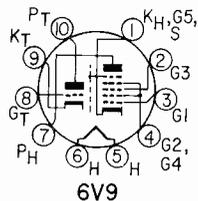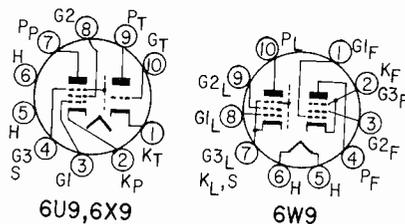The remaining tube, the ECH200/6V9, is a triode-heptode for use as sync amplifier and sync separator. Both sections are completely independent (except for the heater) and shielded from



each other—a result of using the 10-pin base.

The 10-pin base has the same pin-circle diameter as the familiar 9-pin (noval) miniature. Room for the extra pin comes from reducing the spacing between pins. According to a Philips bulletin, increase in interelectrode capacitance as a result of the closer spacing is negligible.

Ultimate objective of the new design is to make possible more compact TV sets by combining functions that till now had to be handled by separate tubes.

"Fast Fax" tube data file

A unique card file of condensed characteristics of the latest receiving tube types has been introduced by Raytheon Co.'s Industrial Components Division. The file is designed for ready reference by technicians, service dealers and tube distributors.

Tube data and basing diagram are on the same side of the card, so that all pertinent information can be seen without turning the card over. Tabbed index separator cards make it easy to locate tube cards. The set comes complete with



100 most-popular tube types and all new ones registered with the EIA in 1962, 1963 and the early part of 1964. It will be kept current with supplementary cards mailed automatically to subscribers. The first supplement, due in

September, will include all new types used in 1965 radio and TV sets.

Each card slides onto binder rods in the file holder without tools or dismantling. Cards can be removed, but will not come out accidentally.

Also included is an inventory control form on the back of each card, and an interchangeability guide. Suggested list price for the file, with one-year supplement service, is \$3.95. It is being offered through franchised Raytheon distributors.

Triac

A special silicon power semiconductor—a gate-controlled ac switch with three leads—has been announced by General Electric. It works more or less like two silicon controlled rectifiers connected in parallel back to back.

This characteristic permits it to conduct and control full-wave ac rather than pulsating dc as a single SCR does.


The Triac requires less than 3 volts at less than 50 ma to trigger it into conduction. The gating (or triggering) signal may be dc, ac or short pulses of either polarity.

G-E expects the Triac's widest application in explosion-proof static contactors for on-off switching of motors and lighting; motor starters and controllers; temperature regulators; welding controls, etc.

The device is packaged in conventional stud-mount or press-fit housings. A photo of it appeared on page 43 of the April 1964 RADIO-ELECTRONICS.

22-throw diode coax switch

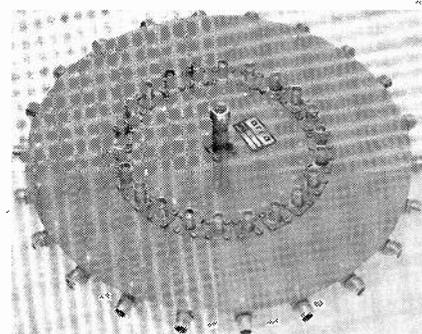An all-solid-state diode coaxial switch with 22 positions has been announced by ARRA (Antenna and Radome Research Associates). The units are usable up to 2 gc, have a maximum insertion loss of 3.5 db and a minimum



isolation of 30 db, and can handle up to 1 watt. Switching time is 100 nsec.

The switches are used for multi-channel antenna receiver switching applications, antenna lobing, and beam shaping in phased and steerable antenna arrays. Similar units, with insertion losses of only about 1 db, are available for the 100- to 1,000-mc range.

The price depends on the customer's requirements, but be sure you really need one before you order. The price will range from \$900 to \$1,500. END

IT ONLY COSTS
1/100 OF 1¢ MORE*
PER SOLDER JOINT
TO KNOW YOU
ARE USING THE
WORLD'S FINEST
CORED SOLDER



ERSIN
Multicore
FIVE-CORE SOLDER
Sold only by Radio Parts Distributors

*Based on cost comparison in current catalogs.
MULTICORE SALES CORP, PORT WASHINGTON, N.Y.

TECHNOTES


INTERMITTENT IN BROWN MODEL 152 ELECTRONIC INDUSTRIAL RECORDER

When you troubleshoot one of these recorders for intermittent, erratic operation (after you determine that the electronic amplifier and the measuring circuit components are not at fault), check the wiring harness located at the top left side of the instrument case. Loosen the chassis latch and swing the chassis out of the case. The harness, a laced cable, has a flexing point between the moving chassis and the clamp on the case. The wires in the harness eventually break because of this flexing, causing a hard-to-find intermittent. The harness must be replaced.—*F. G. Lewis*

POOR FOCUS IN HEATH 0-8 SCOPE

The user of this oscilloscope found he couldn't focus the trace until the focus pot was all the way against one end stop. Brightness control was satisfactory.

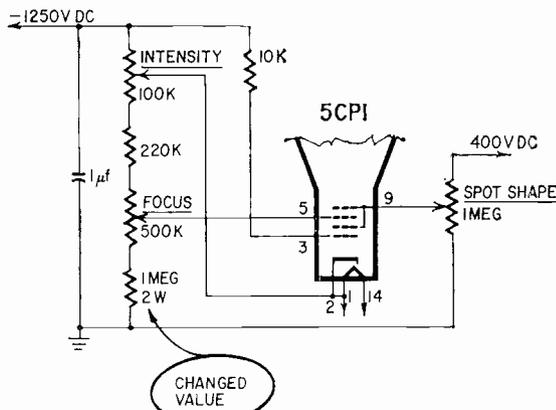The trouble was traced to the 1-megohm resistor at the



bottom of the string (see schematic). Its value had risen to over 2 megohms, throwing the range of voltage adjustment beyond the value needed by the CRT. A new resistor restored proper focus control.—*Donald R. Hicke*

REMEDY FOR INSUFFICIENT WIDTH

In sets with insufficient width (and no width control), after everything is known to be working correctly, try increasing the value of the horizontal output-tube screen resistor by 50% to 60%.

This reduces high voltage. To restore it to its former level, you will usually have to decrease the capacitor in the damper circuit by about 25% to 30%. Use a ceramic rated at 6 kv.

The changes can increase width by 2 inches or sometimes more.—*E. L. Deschambault*

INSUFFICIENT HEIGHT IN MOTOROLA TS-581, -584

A loss of vertical size in these chassis may be the result of an increase in the resistance of the 3.3-megohm resistor in series with the vertical size control. Sometimes the resistor may open up completely, killing the vertical sweep altogether.

This resistor is part of the vertical size and noise-gate control assembly and so can't be replaced separately. But

BECOME A RADIO TECHNICIAN for only \$26.95

BUILD 20 RADIO

CIRCUITS AT HOME

with the New Progressive RADIO "EDU-KIT"®

Reg. U.S. Pat. Off.

All Guaranteed to Work!

PRACTICAL

only

HOME RADIO COURSE

\$26.95



NOW INCLUDES

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

TRAINING ELECTRONICS TECHNICIANS SINCE 1946

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

FREE EXTRAS

- SET OF TOOLS ● RADIO & ELECTRONICS TESTER ● ELECTRIC SOLDERING IRON ● TESTER INSTRUCTION MANUAL ● MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE ● HI-FI GUIDE ● QUIZZES ● TV BOOK ● FCC AMATEUR LICENSE TRAINING ● RADIO BOOK ● PRINTED CIRCUITRY ● PLIERS-CUTTERS ● ALIGNMENT TOOL ● WRENCH SET ● CERTIFICATE OF MERIT ● VALUABLE DISCOUNT CARD

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$26.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory and practice testing, troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are 20 Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplifier circuits. These are not unprofessional "bread board" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory, troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced. In Hi-Fi and TV. Your education will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, Hook-up wire, solder, selenium rectifiers, volume control knobs, etc. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statais, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

UNCONDITIONAL MONEY-BACK GUARANTEE

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc., for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

ORDER FROM AD - RECEIVE FREE BONUS RADIO & TV PARTS JACKPOT WORTH \$15

- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name.....
Address.....

Progressive "EDU-KITS" Inc.

1186 Broadway, Dept. 225G
Hewlett, N. Y.

(ATT: S. GOODMAN, M.S. in ED., PRES.)

Continued from page 25

so strong that it will transilluminate the thickest part of the body. Thus the physician by accurate focusing can actually see in *three dimensions* your heart as it beats, *probably in full color*. He can also see the heart's interior and watch the working of the heart valves. He will watch the actual working of many of your glands, either with his own eyes, *by photography, or by motion pictures*.

"When that time comes, *and it is coming*, we will at long last know what makes us really tick."

This was written long before the laser was invented. Now we have a most powerful new tool, which the present writer believes will in the not too distant future be used to transilluminate the body. Using ordinary X-ray techniques but substituting a laser or related means, it should be possible to use a super-power beam or ray of coherent laser light that is sufficiently powerful to pierce any part of the human body. Then by focusing it accurately on any organ it can be transilluminated—probably in color—in its entirety. The new technique simply depends on the correct amount of applied power and intensity to achieve penetration of an opaque—or, let us say, a semi-translucent—subject, the body. The intensity of *pulsed* laser light is stupendous, many thousands of times greater than even sunlight.

Will the patient not be burned? No, not with the correct filters and, more important, the correct time exposure of the body. Future exposures—similar to present-day X-rays—will be done in very small fractions of a second. —H.G.

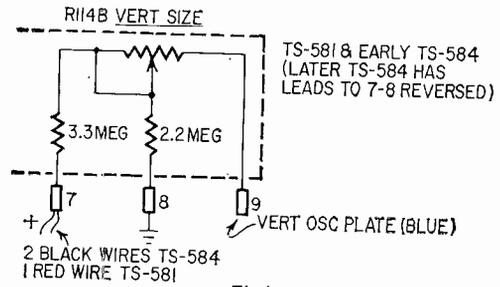


Fig.1

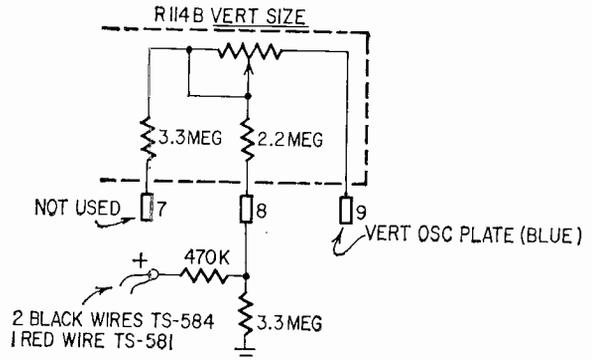


Fig.2

you can avoid having to replace the entire package by rewiring the circuit slightly. This will also prevent recurrence of the trouble. Fig. 1 shows the original circuit, and Fig. 2 the rewired version. You will have to ground the *horizontal* module at any convenient point.—*Motorola Tech-Review*

PULL-TYPE SPEAKER SWITCHES ON GERMAN RECORDERS


The Grundig TK40 and TK42, and the Uher SR 111 use pull type speaker cutouts. Lifting the volume knob disconnects the internal speaker when the recorder is used to drive other systems.

If you have to remove the volume knob, leave plenty of clearance between the knob and the surface below when you replace it. Putting the knob too far down on the shaft may make it impossible to turn on the internal speaker.

When you return one of these machines to the customer, make sure the switch is in the ON position. Nontechnical people who have never used the switch may not be able to operate the machine and will bring it back to you.—*S. P. Dow*

BATTERY POLARITY WARNING REDUCES SERVICE CALLS

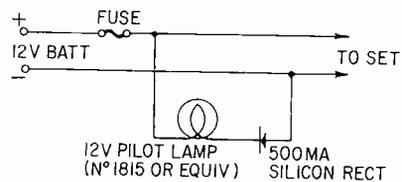In my area (Vancouver Island, British Columbia) there are many remote logging camps where people rely heavily on portable radiotelephones. Since these are mainly nontechni-



cal people, reversed battery connections often mean a long airplane trip to a service technician. In transistor or hybrid equipment, wrong polarity can ruin a set.

To combat this, I include the circuit shown here in all installations. If connections are reversed, the bulb lights, warning the operator before he turns the set on.—*A. A. Lamont*

FAULTY TUNER CAUSES INTERMITTENT PICTURE

In Motorola TS-539's, the three wafer strips in the tuner *plug in* to the tuner, and the plugs and electrical connections on each wafer are *bradded* instead of soldered.

COMPUTER TECHNICIANS

Immediate Stateside & Overseas Openings

Must have a minimum of 2 years' experience in the maintenance of military or commercial computers or data processing systems.

Excellent benefits including stock savings plan.

Qualified candidates please send complete resume to Mr. Don Kirkland, Dept. 806.

PHILCO TECHREP DIV.

A Subsidiary of Ford Motor Company

P.O. Box 4730

Philadelphia, Pa. 19134

An Equal Opportunity Employer

Coming Next Month in Radio-Electronics

ADD A MECHANICAL FILTER

Would you like to tune out stations on 1460 and 1470 kc and tune in a European on 1466? That's what our reviewer did when testing this little device. Using a Collins magnetostriction filter, and a single transistor, this unit plugs into an i.f. tube socket, is a great help in separating crowded stations on the broadcast band or short waves. Next month—how you can do it.

FLEXIBLE HOME INTERCOM

A system that permits any station to call and speak to any other, without going through a "master" station; to address all other stations simultaneously, or to switch to a "music mode" and listen to background music. In addition any station can switch so it cannot be called, and no station can be monitored arbitrarily by another. Only one amplifier (transistor-type) is used for the whole system.

MAKE MONEY WITH ELECTRONICS AFLOAT

The vast number of pleasure boats and the increasing amount of electronic gear they carry means there is a lot of work around for the service technician who goes after it. Marine equipment is simple and straightforward (at least compared to TV!) but the work calls for its own approaches and techniques.


RELIABLE TRANSISTOR IGNITION SYSTEM

A three-transistor circuit that makes it possible to construct a transistor ignition system without buying a special coil. Also makes Zener diodes unnecessary. Our checker reports "Acceleration and engine smoothness seemed improved, especially on long upgrades. Gas economy up. . ."

You'll find these and many other articles, features and regular departments in next month's RADIO-ELECTRONICS.

SEPT. ISSUE (on sale Aug. 18)

EIGHT INSTRUMENTS IN ONE

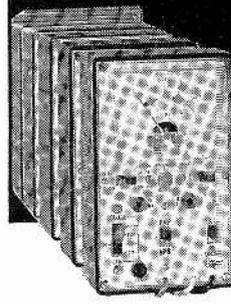

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212

Factory Wired & Tested — \$18.50
Easy-to-Assemble Kit — \$13.50

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me **FREE** catalog of the complete value-packed EMC line, and name of local distributor.

NAME _____ RE-8

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York 12, New York
Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

After a short time, the brads loosen or oxidize, and the result is intermittent or very poor reception. Each wafer section must be removed very carefully and all pins and brad connections soldered with a small gun or soldering pencil. To remove the wafer strips, the tuner must first be removed and the following steps completed:

- (1) Remove the seven mounting screws holding the tuner to chassis.
- (2) Drop the front end of tuner downward so that it protrudes toward the bottom of chassis.
- (3) On automatic-tuning models (motor on rear of tuner), remove the motor mounting screws and remove motor from tuner.
- (4) Remove the screw holding the automatic channel-selector disc to the rear of the tuner shaft. Remove the disc.
- (5) Remove the tuner cover plate to get at the wafer sections.
- (6) Remove Phillips screw holding the tuning shaft to detent mechanism.
- (7) Remove shaft by pulling straight out from the front of the tuner.

Each wafer can be removed by pulling it firmly but carefully out from the bottom of the tuner. After soldering each brad connection, replace the wafer carefully and see that each wafer pin is properly in place. Use a minimum of solder around pins.—*John B. Ledbetter*

BURNED VERTICAL OUTPUT RESISTOR IN PACKARD-BELL 99 CHASSIS

Whenever one of these sets loses boost voltage, the vertical output tube's plate dropping resistor burns up. The reason is that the vertical oscillator's plate supply is from the boost, while the vertical output stage draws its current from B-plus. When boost disappears, the oscillator stops, removing drive from the output stage grid. The output stage's plate current soars, burning the resistor.—*Joseph K. Nicholson* END

World's Fastest Selling FM Wireless Microphone



IMP II

Transmits voice or signal with power and fidelity to any standard FM tuner or radio. Perfect for use where mike cords are inconvenient. For broadcasting, remote tape recording, communicating or hundreds of other applications in schools, churches, theatres, plants, stores, homes and sporting activities, indoors or out. Tunable: 88-108 mc band.

IMP II-221 Transmitter only... **39.95**
IMP II/M-222 Complete with built-in pin-head microphone **49.95**



See Distributor or write Dept. R-8

Made in U.S.A.

kinematix, inc.

2040 West Washington Boulevard
Chicago, Ill. 60612 Area 312 • 666-0066

send for NEW FREE
CRYSTAL CATALOG
with NEW TRANSISTOR
OSCILLATOR CIRCUITS



3 PLANTS TO SERVE YOU BETTER
**HERMETICALLY SEALED
PRECISION GROUND
CUSTOM-MADE
NON-OVEN CRYSTALS**

Gold or silver plated, spring mounted, vacuum sealed or inert gas, high freq. stability, 10 milliwatt max. current cap. Meet mil. specs.

1000KC to 1600KC (Fund. Freq.) Prices on Request
1601KC to 2000KC (Fund. Freq.) \$5.00 ea.
2001KC to 2500KC (Fund. Freq.) 4.00 ea.
2501KC to 5000KC (Fund. Freq.) 3.50 ea.
5001KC to 7000KC (Fund. Freq.) 3.90 ea.
7001KC to 10,000KC (Fund. Freq.) 3.25 ea.
10,001KC to 15,000KC (Fund. Freq.) 3.75 ea.
15MC to 20MC (Fund. Freq.) 5.00 ea.

OVERTONE CRYSTALS

15MC to 30MC Third Overtone \$3.85 ea.
30MC to 40MC Third Overtone 4.10 ea.
40MC to 65MC Third or Fifth Overtone 4.50 ea.
65MC to 100MC Fifth Overtone 6.00 ea.

DRAKE 2-B Receiver Crystals \$4.00
(All Channels—Order by Freq.)

OVEN-TYPE CRYSTALS

For Motorola, GE, Gonset, Bendix, etc.

Add \$2.00 per crystal to above prices

SUB-MINIATURE PRICES slightly higher

ORDER FROM CLOSER PLANT
TEXAS CRYSTALS

DEPT. RE
1000 Crystal Drive
FORT MYERS, FLORIDA
Phone 813 WE 6-2109
TWX 813-334-2830


AND

4117 W. Jefferson Blvd.
LOS ANGELES, CALIF.
Phone 213-731-2258
TWX 213-737-1315

Division of




new Products

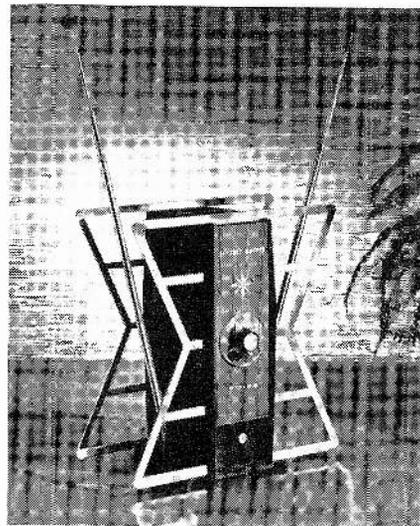

INDOOR ANTENNA


VU-82, model 4000, for uhf/vhf/FM. 2 antennas in one, each with own transmission line. Uhf diplexer circuit gives uni-directional pattern, can be automatically reversed 180° by switching, lets both uhf dipoles operate simultaneously, with twice gain of single antenna. Electronic tuner matches antenna's 300-ohm impedance to set and adjusts length of vhf elements to wavelength of channel. 96-in. elements joined to 10-in. walnut-grained column.—Channel Master Corp., Ellenville, N. Y.

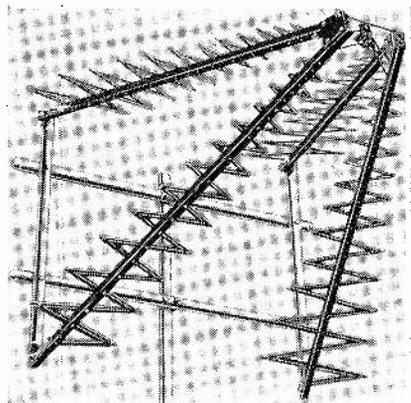

LOG-PERIODIC TV ANTENNA FOR UHF


LPV-ZU20: Zig-a-Log beam widths no less than 20° for easy orientation, uniform gain and impedance across wide bandwidth. Maximum usable gain for weak signal areas and minimal side lobes for ghost rejection. Input impedance matches 300-ohm transmission line. Vswr less than 1.8:1 across uhf channels. E- and H-

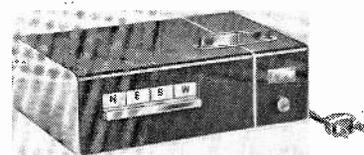plane beam widths have 1:2 ratio. Gain 16.5 ± ½ db over half-wavelength dipole. Aluminum elements, stainless steel take-offs.—JFD Electronics Corp., 15th Ave. at 62nd St., Brooklyn 19, N. Y.




ANTENNA ROTOR SYSTEM

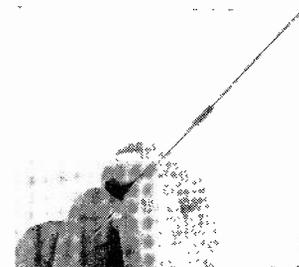TR-2C, features new control box with heavy-duty CD rotator. Finger-touch control. By depressing lever to left or right, antenna is rotated and position monitored by series of compass lights. Black leatherette and brushed aluminum. 6 x 4 x 2 in.—Cornell-Dubilier Electronics Div., 50 Paris St., Newark 1, N. J.





CORDWOOD-SIZE CERAMIC CAPACITOR

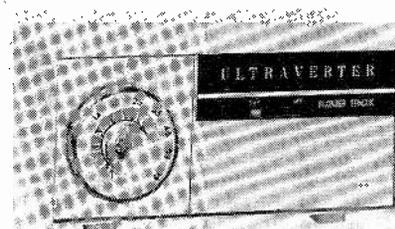MC-70. Ratings from 10 to 20,000 picofarads. For automatic insertion in printed circuits. 0.260-in. maximum length by 0.100-in. maximum diameter, with axial leads at least 1½ in. long.—Aerovox Corp., Distributor Div., New Bedford, Mass.




TUNNEL-DIODE CONVERTER FOR UHF

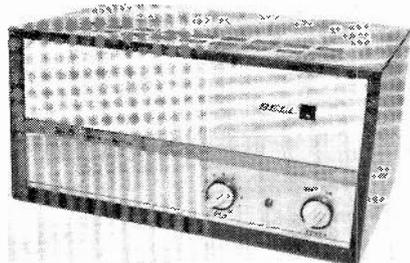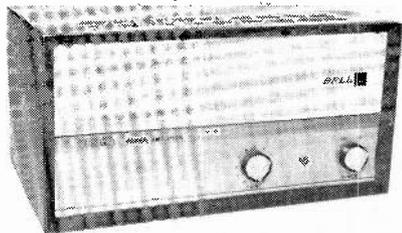Model BTD-44 Ultraverter cordless unit, uses single flashlight battery as power supply. Converts all uhf channels to vhf channel 5 or 6.—Blonder-Tongue Labs, Inc., 9 Alling St., Newark, N. J. 07102




BOOSTER AMPLIFIERS

35BA and 75BA, 35 and 75 watts, respectively, for additional power as slaves to main PA system. Used with Bell BE-M4 microphone mixer to form complete PA system. Signal-to-noise ratio over 75 db, frequency response 30 to 15,000 cycles. Plug-in relay for remote control of ac power or standby operation. Styled like BE series; bridging input standard but converts to 600 ohms balanced line with plug-in transformer input.—TRW Columbus Div., Thompson Ramo Wooldridge, Inc., 6325 Huntley Rd., Columbus 24, Ohio.

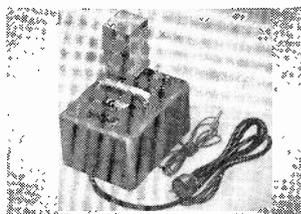

HAZARD SENSOR

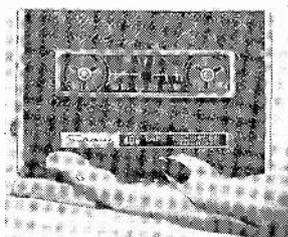
Has circuit breaker and fast-acting fault detector for 50/60 cycle ac. Protects equipment operators and others from electrical shock, instantaneously shuts down equipment when faults develop, detects danger from hot lines and opens source before shock hazard develops. Can be set on ac or pulsating dc.—Shock-Proof Electronics, Inc., 1601 Girard Trust Bldg., Philadelphia, Pa. 19102



ELECTRONIC NOTEBOOK


Transistorized, records up to 30 minutes on 1 tape. Picks up ordinary conversation

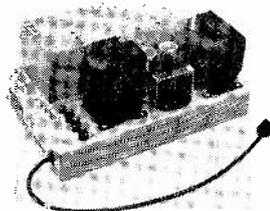25 ft away. Rewinds in less than 3 minutes. Built-in speaker. 1½ lb, 2 x 3½ x 5 in. Powered by standard 1.5-volt penlight batteries. Remote-control microphone, earphone, 4 batteries, tape, extra reel, leather carrying case, shoulder strap. Telephone pickup for recording phone conversations available.—Hahn Co., Dept. R-E, 3408 Motor Ave., Los Angeles, Calif. 90034




TV/FM DISTRIBUTION AMPLIFIER

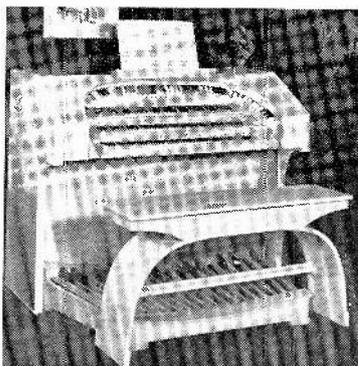Model LIID-404R. Feeds low and high vhf TV and full FM signals into as many as four distribution lines with output level of 50 db above 1 mv at channel 13. Fed from directional coupler or from end of distribution line; serves as either bridging or distribution line extender. Feeds 1½ miles of distribution lines.—Entron, Inc., 2141 Industrial Parkway, Silver Spring, Md.



ORGAN KIT


Cinema, smallest Artisan theater organ—30 in. deep, 46 in. high. Meets AGO specs with 3 full 61-note manuals, concave 32-note claviers. Intermanual couplers, twin expression pedals, independent vibratos, independent oscillators for each key, built-in music light and preset combination pistons. Stop list of authentic theater voices. Chimes, orchestra bells, vibra harp and band box optional. Variety of finishes.—Artisan Organs, 2476 N. Lake Ave., Altadena, Calif.

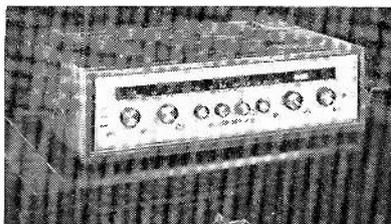

TUNER/AMPLIFIER

S-8000IV. 80 watts. Powered center speaker channel for center or third-channel speaker system or extending mono

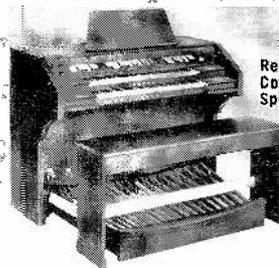ASSEMBLE YOUR OWN ALL-TRANSISTOR *Schober* ELECTRONIC ORGAN



3 NEW MODELS
Recital \$1500
Consolette II \$850
Spinet \$550

This is the all-new, all-transistor Schober

Recital Model... the most versatile electronic organ available today. Its 32 voices (plus amazing "Library of Stops"), 6 couplers and 5 pitch registers delight professional musicians... make learning easy for beginners. Comparable to ready-built organs selling from \$5000 to \$6000.

The pride and satisfaction of building one of these most pipe-like of electronic organs can now be yours... starting for as low as \$550. The Schober Spinnet, only 39¼ inches wide, fits into the smallest living room. The new, all-transistor Schober Consolette II is the aristocrat of "home-size" organs... with two full 61-note manuals, 17 pedals, 22 stops and coupler, 3 pitch registers and authentic theatre voicing.

AND YOU SAVE 50% OR MORE BECAUSE YOU'RE BUYING DIRECTLY FROM THE MANUFACTURER AND PAYING ONLY FOR THE PARTS, NOT COSTLY LABOR.

It's easy to assemble a Schober Organ. No special skills or experience needed. No technical or musical knowledge either. Everything you need is furnished, including the know-how. You supply only simple hand tools and the time.

You can buy the organ section by section... so you needn't spend the whole amount at once.

You can begin playing in an hour, even if you've never played before—with the ingenious Pointer System, available from Schober.

Thousands of men and women—teenagers, too—have already assembled Schober Organs. We're proud to say that many who could afford to buy any organ have chosen Schober because they preferred it musically.

Send for our free Schober Booklet, describing in detail the exciting Schober Organs and optional accessories; it includes a free 7-inch "sampler" record so you can hear before you buy.

THE Schober Organ CORPORATION

43 West 61st Street, New York, N.Y. 10023

Also available in Canada, Australia, Hong Kong, Mexico, Puerto Rico, and the United Kingdom

THE SCHOBER ORGAN CORP., Dept. RE-32
43 West 61st Street, New York, N.Y. 10023

Please send me FREE Schober Booklet and free 7-inch "sampler" record.


Enclosed find \$2.00 for 10-inch quality LP record of Schober Organ music. (\$2.00 refunded with purchase of first kit.)

Name _____

Address _____

City _____ State _____ Zip No. _____

ELECTRONICS

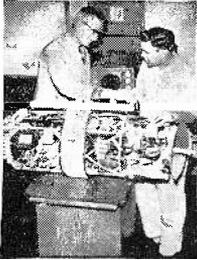

Engineering-Technicians

Bachelor of Science Degree, 30 Months
Save Two Years' Time

The Nation's increased demand for Engineers,

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
 - Electrical Engineering (B.S. Degree)
 - Mechanical Engineering (B.S. Degree)
 - Civil Engineering (B.S. Degree)
 - Architecture (B.S. Degree) (36 Months)

Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.

Approved for Veterans

DAY AND EVENING CLASSES

Write for Catalog and Registration Application. New Term Starting Soon.

Your Name

Address

City

State

HEALD'S

ENGINEERING COLLEGE

Est. 1863—101 Years
Van Ness at Post, RE
San Francisco, Calif.

moving?

When you move, send us your OLD address (as it appears on your latest copy of Radio-Electronics) as well as your NEW address. If possible, send us the actual address label which is pasted on the front cover. Include your ZIP code if you know it.

CORNELL TUBES

1 YR. GUARANTEED

Tubes are new or used and so marked
Mutual Conductance Lab tested. Individually
boxed, Branded and Code dated.

33¢ PER TUBE

100 TUBES OR MORE:
30¢ PER TUBE

OZ4	6AG5	6BD6	6CM7	6H6	6SC7	6SR7	12AD6	12SQ7
1B3	6AK5	6BG6	6CZ5	6J5	6SH7	6U7	12AE6	25L6
1H5	6AL5	6BH6	6D6	6J6	6SJ7	6U8	12AF6	25Z6
1J3	6AN8	6BJ6	6DA4	6K6		6V6	12AT7	35W4
1L4	6AQ5	6BL7				6W4	12AU7	35Z3
1T4	6AS5	6BN4				6W6	12AX7	35Z5
1U4	6AT6	6BN6				6X4	12BA6	50L6
1X2	6AT8	6BQ6				6X5	12BD6	24
3CB6	6AU4	6BZ6				7A7	12BE6	27
5U4	6AU5	6C4				7A8	12BF6	41
5V4	6AU6	6C6				7B6	12BH7	45
5Y3	6AV6	6CB6				7B7	12BL6	47
6A6	6AW8	6CD6	6DE6	6K7	6SK7	7B8	12BY7	75
6A8	6AX4	6CF6	6DQ6	6Q7	6SL7	7C5	12C5	77
6AB4	6BA6	6CG7	6EM5	6S4	6SN7	7N7	12CA5	78
6AC7	6BC5	6CG8	6F6	6SA7	6SQ7	7Y4	12SN7	84

If Not Shipped
in 24 hrs.
**YOUR
ORDER
FREE!**

NO SUBSTITUTIONS WITHOUT YOUR PERMISSION

Special!
With every \$10 Order

25¢ per tube

(No Limit) from this list.

6AG5 6SN7
6AQ5 6J6 6V6
6AU6 6K6 6W4

21" PICTURE TUBES
\$1395 1 Yr. Guar.
Aluminized
Pay Dud Deposit
COD or Send Dud
with Order

- ASK ABOUT OUR
- Tube Checkers
 - Tube Substitution Guides
 - Electronic Solder
 - T.V. Courses
 - Radio Courses
 - Tube Cartons
 - Electronic Cleaner
 - Diodes/Rectifiers


Other tubes and CRT's at low prices - send for free list.

TERMS: Add 3c per tube shipping. Orders under \$5.00 add 3c per tube shipping plus 50c handling. Canadian orders add approximate postage. Send 25% deposit on C.O.D. orders. No C.O.D. orders under \$5.00 or to Canada. No 24 hr. free offer on personal check orders.
5-DAY MONEY BACK OFFER!

CORNELL ELECTRONICS CO.


Dept. RE 8 4217 University Ave., San Diego, Calif. 92105

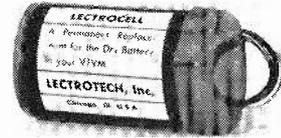speakers in other rooms. Front-panel stereo headphone jack and speaker disabling switch. 1.8 μ v (IHF) FM sensitivity. 2.4-db capture effect. FM inter-channel hush. FM distortion 1/2% at 100% modulation. 8-inch tuning dial with frequency markings every 200 kc.—Sherwood Electronic Laboratories, Inc., 4300 N. California Ave., Chicago, Ill. 60618




MINIATURIZED POWER SUPPLY

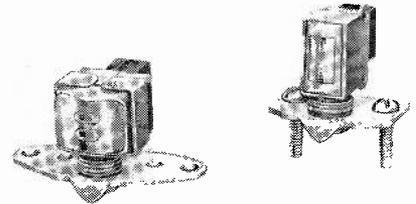Lectrocell replaces dry battery in vtvm ohmmeter circuit. Same size and shape as 1 1/2-volt battery it replaces.—Lectrotech, Inc., 1737 W. Devon Ave., Chicago, Ill. 60626



REPLACEMENT TAPE HEADS

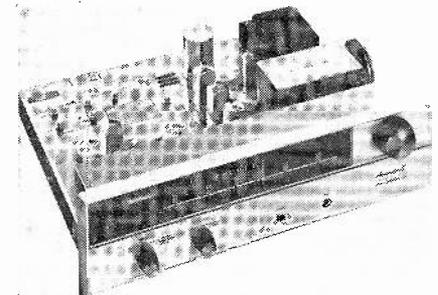(for Sony tape decks and recorders). Laminated professional type, match Sony models 101, 262-D and 262-SL. Packed in kit with mounting hardware, replacement pressure-pad material and instructions.—Nortronics, 1801 Nicollet Ave., Minneapolis, Minn. 55403



TRANSISTOR FM STEREO TUNER

Model 312. Silent automatic stereo switching not affected by momentary changes in signal strength; usable sensitivity (IHF) 2.2 μ v (minimum); signal-to-noise ratio 65 db, distortion under 0.8%; drift less than 0.02%. Frequency response (stereo) ± 1 db, 30-15,000 cycles. Capture ratio 4 db; selectivity 35 db; cross-modulation rejection 80 db. AM suppression 55 db; accuracy of calibration 0.5%; separation 35 db; 4 all-silicon i.f.'s. 15% x 5 1/2 x 1 3/4 in.—H. H. Scott, Inc., Dept. P, 111 Powdernill Rd., Maynard, Mass. END

All specifications from manufacturers' data.

booklets
New Literature
catalogs charts

CRYSTALS AND EQUIPMENT CATALOG. 24 pages, 2 colors, photos, charts and curves. Lists commercial crystals, crystal ovens, amateur and CB crystals, accessories, oscillators, frequency-alignment equipment, transistor subassemblies, transmitters/oscillators, converters and 3 pages of technical data for 1964.—**International Crystal Mfg. Co. Inc.**, 18 No. Lee, Oklahoma City, Okla.

RELAY CATALOG. 20 pages, 2 colors, describes line of standard industrial relays. Photos and charts, sectioned into high-performance, power, special, general and telephone types. Lists coil voltages, resistances, time values, contact ratings, terminations, dimensions for each relay.—**Potter & Brumfield, Div. of American Machine & Foundry Co.**, Princeton, Ind.

TRANSISTORS AND DIODES WALL CHART, CH-10-50M. 19 x 25 in., 2 colors. Lists 40 basic semiconductor replacements for EIA types, private-manufacturer and foreign types.—**L. Rivman, Semitronics Corp.**, 265 Canal St., New York, N.Y. 10013

GLOSSARY of 99 tape recording terms, 4 pages of well-spelled-out definitions of some of most common terms.—**3M Co.**, 2501 Hudson Road, St. Paul 19, Minn.

PERMANENT MAGNETS. *Bulletin 21* describes bars, multiple bars, rods, U-shapes, cylinders, arched and channel horseshoes and rings. Photos, charts, and dimensional drawings. 12 pages, 2 colors.—**Indiana General Corp., Magnet Div.**, Valparaiso, Ind.

SEMICONDUCTORS. 8-page brochure containing 8 typical circuits for n-p-n germanium alloy transistors, including characteristic curves in industrial and entertainment applications.—**Sylvania Electric Products Inc.**, SM-3929, 1100 Main St., Buffalo, N.Y. 14209

STEREO COMPONENTS CATALOG CL-643. 16 pages, describes full line of tuners, amplifiers, receivers, tape decks, tape recorders with specs and photos.—**Bell Sound, TRW Columbus Div.**, 6325 Huntley Road, Columbus, Ohio

SERVICE COMPONENTS CATALOG for 1964. 20 pages, photos, graphs and diagrams of line of wirewound and carbon potentiometers, fixed value or adjustable wirewound resistors, switches.—**Distributor Div., Clarostat Mfg. Co. Inc.**, Dover, N.H.

INSTITUTE PAMPHLET, "Opportunities in Electronics For You." 28-page booklet with photos suggest areas open to electronics technicians.—**Cleveland Institute of Electronics**, 1776 E. 17 St., Cleveland, Ohio

CATALOG of Teflon terminals including standoffs, feedthroughs, "cloverleaf" receptacles, bushings, test-point jacks, taper pin receptacles, probes and plugs, transistor units. Cross-indexed 40 pages with dimensional drawings, photos, specs.—**Sealectro Corp.**, 225 Hoyt St., Mamaroneck, N.Y.

ELAPSED-TIME INDICATORS, miniaturized series 95C and others described in 8-page booklet with photos, diagrams and specs.—**Elgin National Watch Co., Communications Div.**, Industrial Group, 366 Bluff City Blvd., Elgin, Ill. 60120

OPTOELECTRONIC CONTROL DEVICES folder describes 19 models of 4-terminal units operating via controlled light falling on photoresistive element. Photos, diagrams, chart.—**Richard Finger, Raytheon Co., Industrial Components Div.**, 55 Chapel St., Newton, Mass. 02158

STEREO EQUIPMENT—small folder describes *Allegra* series of stereo amplifiers, tuners and receivers. Photos and specs.—**Grommes, Div. of Precision Electronics Inc.**, 9101 King St., Franklin Park, Ill.

DC POWER SUPPLY DESIGNS. *Form 1039*, electrical data sheets to build 36 miniature power supplies including transformers, rectifiers and fil-

ters. Dc voltages from 10 to 80, power rating from 280 mw to 24 watts.—**J. S. Conklin, Magnetic Circuit Elements Inc.**, 3720 Park Place, Montrose, Calif.

COAXIAL CABLE Catalog CC-5, 16 pages, describes construction and characteristics of 58 coaxial cables made with polyethylene and Teflon insulation. Photos and charts.—**Alpha Wire Corp., U.S. Wire & Cable Div.**, 180 Varick St., New York, N.Y. 10014

CAPSULE THERMISTOR Course No. 6, "Thermistor Probe Assembly Design" discusses housing configurations for a thermistor probe assembly in a given application. Single loose-leaf page.—**Sales Engineering Dept., Fenwal Electronics Inc.**, 63 Fountain St., Framingham, Mass.

RECTIFIER LEAFLET. 4 pages outlining line of copper oxide instrument rectifiers with color code, specs, dimensions and internal circuits.—**Conant Labs**, Box 3997, Bethany Sta., Lincoln 5, Neb.

BRUSHLESS GENERATORS Bulletin GET-3137. 16 pages punched for ring binder describe 3 components of set—brushless generator, brushless exciter and SCR voltage regulator—no brushes, slip rings or commutators. Characteristics, photos, charts and circuit diagrams of SCR voltage regulator. For use where continuous or stand-by power required; can be direct-connected to gas or steam turbines or diesel engines.—**General Electric Co.**, Attn: Gregory Ellis, Schenectady 5, N.Y.

SWEEP and SIGNAL GENERATORS Catalog No. 64-A. 36 3-color pages contain general treatment of sweep generator operation, sweep measurement techniques. Specs, diagrams, oscilloscope patterns on 30 models. Describes accessories such as turret and toggle switch attenuators, coaxial switches, detectors, oscillators, cable sets. Section on crystal, harmonic, single-frequency, variable and sideband markers.—**Telonic Industries, Inc.**, 60 N. First Ave., Beech Grove, Ind.

HEAT-SHRINKABLE TUBING. Leaflet, in full color with photos and sample, describes Formtite tubing for insulating terminals and pigtailed, jacketing wires to form cables, providing identify-

ALL NEW
SENCORE
component
substitutor



MODEL RC121

All your favorite Sencore Substitution Time-Savers in One Compact Unit

A complete range of carbon resistors, wire wound power resistors, capacitors, electrolytics, and universal selenium and silicon rectifiers.

Imagine, all of these hard to locate parts at your finger tips for all the spot substitution. Say goodbye to messy, crumpled parts, unnecessary unsoldering and soldering of components for testing purposes only. Save valuable servicing time and be sure, by substituting.

NEW . . . each section operates independently with a value close enough for every substitution need. Components in each section are isolated from chassis and from the other sections. For example, a complete power supply can be constructed using the RC121 Components only.

NEW . . . dual electrolytics provided. A new circuit enables you to substitute up to 25 single electrolytic values or 9 duals. Exclusive surge protector provides protection on both singles and duals for both you and the circuit.

You save space and money. Equivalent Sencore substitution-pieces purchased individually (H36, PR111, RS106, ES102) cost you \$54.00

RC121 (all hand wired, all American made) only **3995**
RC121K (Kit) **2795**

Now in stock at your Sencore Distributor. See him today!

SENCORE
ADDISON 2, ILLINOIS

Make This Your Luckiest Day!



Join the Gernsback Electronics Book Club today, and get this outstanding practical two-volume work

only **99c**

A \$9.90 Value... Originally a \$25 Training Course!

You agree to buy only four additional books during the next 12 months at low Club prices.

How to Fix Transistor Radios and Printed Circuits! by Leonard C. Lane was originally prepared as a complete course in servicing transistor radios. This two volume version treats every aspect of transistors, much of it new, original, unavailable anywhere else in book form. Hundreds of illustrations aid understanding. Completely covers semiconductor fundamentals, how transistors work, transistor types, amplifiers, RF and IF stages, printed circuits, specific servicing methods and techniques, and many, many more subjects.

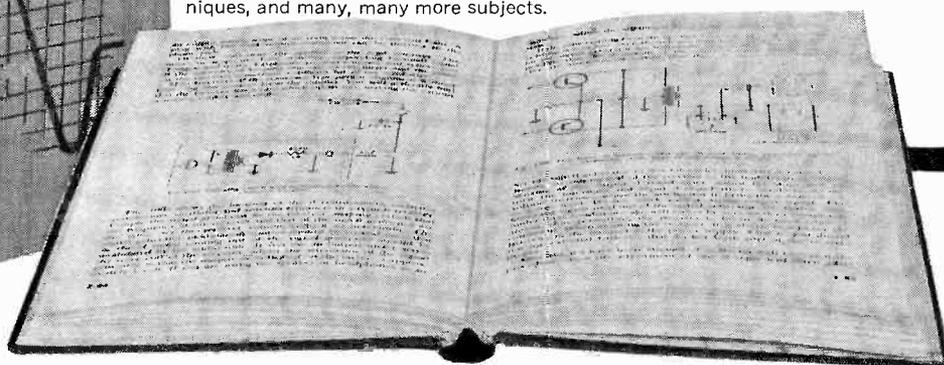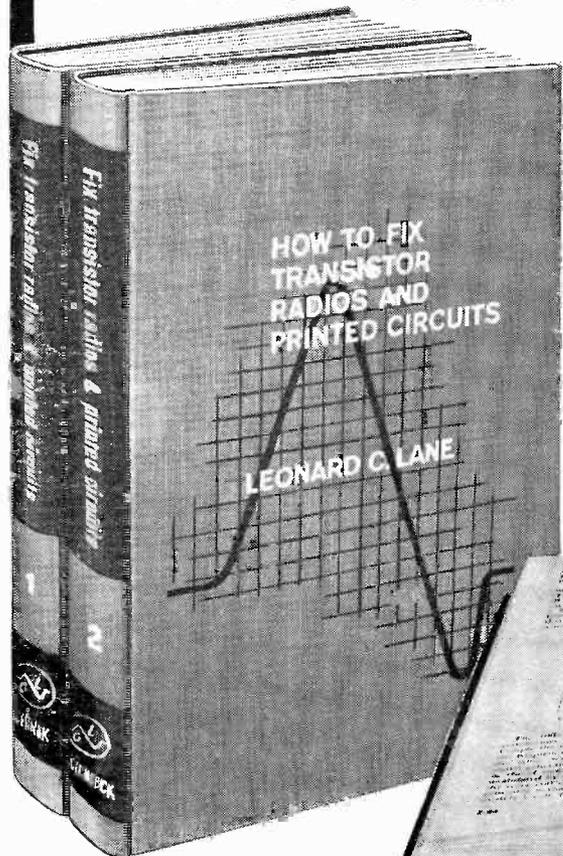

Here is a fabulous offer to introduce you to Gernsback Library's famous Electronics Book Club, specifically designed to help you increase your knowledge and earning power.

WHY YOU SHOULD JOIN

Whatever your interest in electronics — radio and TV servicing, audio and hi-fi, industrial or defense electronics, electronics as a hobby — you'll find that the Electronics Book Club will help you get the job you want, keep it, improve it, or make your leisure hours more enjoyable. By broadening your knowledge and skills, you'll build your earning power and electronics enjoyment as well.

WHAT KIND OF BOOKS ARE OFFERED?

From Gernsback Library and other leading publishers come the country's most respected books in the field of electronics. All are deluxe, hard-covered, attractive looking books of permanent value — books you'll want to own and keep in your personal, professional library.

HOW THE CLUB WORKS

Every two months, the Electronics Book Club will send you, ON APPROVAL, a significant new book on an important phase of elec-

tronics. Examine the book for up to 10 days. If you like it, keep it and send your check for the low club discount price — up to 27% off regular prices! If you are not completely satisfied, simply send it back and you owe nothing. You risk no money.

HOW TO JOIN

Simply fill out and mail the handy coupon today. You will be sent your two-volume set of "How to Fix Transistor Radios and Printed Circuits", worth \$9.90. We will bill you 99c (plus a few cents postage). If you are not satisfied with the books, send them back within 10 days and membership is cancelled. Remember, your only obligation is to buy four additional books from the many offered during the next 12 months. The selections listed are typical of those you'll be able to buy at the special reduced club member's price.

TYPICAL CLUB SELECTIONS:

Television Simplified by Milton S. Kiver
Most complete book on TV written. Every stage and part of receiver carefully explained. 637 pages of updated data. Graphs, diagrams, giant charts.
Regularly \$9.95 **Club price \$7.95**

Basic Transistor Course by Paul R. Kenian
Teaches you transistor fundamentals clearly, simply. Discusses transistors all the way from elementary circuits to radio receivers.
Regularly \$5.75 **Club price \$4.50**

Horizontal Sweep Servicing Handbook by Jack Darr
Fast, simple methods of locating and repairing troubles in the sweep system. Lots of practical shortcuts, developed and proved on the bench.
Regularly \$5.75 **Club price \$4.50**

Basic Radio Course (revised and enlarged) by John T. Frye
The original sold out through eight printings! This lighthearted course in practical servicing techniques is now completely revised and updated.
Regularly \$5.75 **Club price \$4.85**

Basic TV Course by George Kravitz
Up-to-the-minute television—even covers transistorized portables! Presents technical detail in easy-to-follow writing style. A must book.
Regularly \$5.75 **Club price \$4.85**

Basic Industrial Electronics Course by Alfred Haas
A practical, simplified approach to industrial electronics — the branch where earnings are nearly limitless; opportunities always open to skilled technicians.
Regularly \$5.95 **Club price \$4.70**

Basic Electronic Test Procedures by Rufus P. Turner
Solves test and measurement problems in every phase of electronics—from radio to rockets. Practical course and reference for student, teacher, and technician.
Regularly \$8.50 **Club price \$5.95**

Practical Television Servicing by Richard Johnson
Explains everything necessary for rapid location and remedy of receiver troubles. Theory included only when it makes servicing easier, faster, more profitable.
Regularly \$7.95 **Club price \$6.75**

GERNSBACK LIBRARY, INC.

154 West 14th Street, New York, N. Y. 10011

84A


Please send me the two-volume set HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS for only 99c (plus a few cents postage) and enroll me as a member of the Electronics Book Club. I understand that I need accept only as few as four Electronics Book Club selections during the next 12 months, and I may cancel my membership any time after that.

Name _____

Address _____

City _____ State _____ Zip _____ Code _____

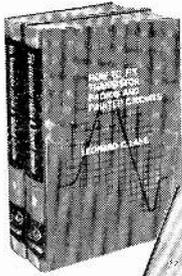We pay postage if you send your remittance with this coupon. You have the same return privilege. Remittance enclosed.



ADDITIONAL SELECTIONS FROM ELECTRONICS BOOK CLUB

Transistor Reference Book

Contains the most complete and up-to-date listing of semiconductor types available, with comprehensive specifications on each type.

Regularly \$6.00 Club price \$4.50

Semiconductor Devices

by Rufus P. Turner

Explains the theory of semiconductor devices in simple language and shows numerous applications. Profusely illustrated with hundreds of drawings and photographs.

Regularly \$6.00 Club price \$4.80

Electrical Appliance Service Manual

by William Gabbert

Expand your business! You can earn more with this complete guide for fast, easy repair of home electrical appliances. Fully illustrated, easy-to-follow charts.

Regularly \$6.75 Club price \$5.75

Radio Servicing Made Easy

(2 vols.) by Leonard C. Lane

Get the latest servicing information on new radio types. Full instructions on how to fix FM, M, AM-FM communications receivers, marine radios, transistors.

Regularly \$9.95 Club price \$7.75

The Oscilloscope

by George Zwick

A complete, practical, easy-to-understand guide to one of the most useful of all servicing instruments. Tells how to get more out of the scope in AM, FM and TV servicing—how to handle tough jobs faster!

Regularly \$5.20 Club price \$3.95

Elements of Electron Physics

by Norman H. Crowhurst

Explains in simple understandable language the how and why of electronics. Covers electron theory, semiconductors, tubes, circuits.

Regularly \$5.65 Club price \$4.45

How to Build Tiny Electronic Circuits

by Morris Moses

Explains "miniaturized" electronics for the hobbyist, experimenter and service technician.

Regularly \$5.85 Club price \$4.95

New Shortcuts to TV Servicing

(2 vols.) by Leonard C. Lane

A practical servicing speed-up course. No theory or math, but heavy on test and repair techniques that save time and make money.

Regularly \$9.90 Club price \$6.50

Basic Math Course for Electronics

by Henry Jacobowitz

Learn electronic mathematics and be miles ahead of your competitors. Use the math you learn in every electronics problem in and out of the shop.

Regularly \$6.45 Club price \$5.15

Industrial Electronics Made Easy

by Tom Jaski

Shows you opportunities in industrial electronics—and gives you the know-how to take advantage of them.

Regularly \$5.95 Club price \$4.35

MAIL COUPON TODAY!

ing markers, shockproofing tool handles and leak-proofing hydraulic fittings and plumbing.—**Surprenant Mfg. Co.**, Div. of ITT, Clinton, Mass.

PRECISION TOOLS CATALOG, 16 pages, punched for ring binders. Photos. Data covers burnishers, cleaning spray, cutters, files, tools kits, microscopes, mirrors, pliers, screwdrivers, tweezers, vises and other precision electronic tools for servicing equipment and relays.—**Jonard Industries Corp.**, 3733 Riverdale Ave., Bronx, N.Y. 10463

FUSES AND FUSE HOLDERS. *Forms SFB, US, HL-163* (latter two are supplements), punched for ring binders; 24 pages, 3 colors, with drawings, dimensions, weights, blowing-time charts, resistance, voltage ratings, vibration characteristics of Buss fuses, Fusestrons, and fuseholders.—**McGraw-Edison Co.**, Bussman Mfg. Div., St. Louis, Mo. 63107

MILITARY SPECS WALL CHART, 2-color, 20 x 26 in. All current military specs in detail for all fixed capacitors.—**Federal Pacific Electric Co.**, Cornell-Dubilier Electronics Div., 50 Paris St., Newark 1, N.J.

RESISTORS DATA SHEET, *CE-2.12*. Single looseleaf sheet with specs, characteristics and derating curve on 4 types of C-style tin oxide film resistors; design tolerances.—**Corning Electronic Components**, Corning Glass Works, Raleigh, N.C.

CAPACITOR CATALOG AND PRICE LIST, Miniature Alumalytic Capacitors (General Electric Type 76F), from 3 to 150 volts. Characteristics and dimensions, ratings, catalog numbers, curves, specs and separate price sheet. 9 pages, line of 109 capacitors.—**Semiconductor Specialists, Inc.**, 5700 W. North Ave., Chicago, Ill. 60639

BULLETIN GEA-7850. 6-page, 3-color folder with photos, specs and diagram describes the TE-17-A Educational Television Operating Center, a system of audio and video components for origination of broadcast or in-school TV programs.—**General Electric Co.**, Visual Communication Products, 212 W. Division St., Syracuse, N.Y.

TRANSISTORIZED LEARNING LABS, 12-page brochure (*GEA-7550*) gives details and illustrations on teacher's control console, tape decks and recorders, amplifiers, student booths, headphones and microphones.—**General Electric Co.**, Visual Communication Products, 212 W. Division St., Syracuse, N.Y.

WALL CHART of "quick-disconnect" devices, 8 x 11 in., 2-color, has 14 actual samples mounted on it in categories such as snap plugs, push-on terminals, adapters, insulated snap plug and tab receptacles, etc. *Form DD-3*.—**Waldom Electronics, Inc.**, 4625 W. 53rd St., Chicago 32, Ill.

VARACTORS CHART for harmonic generator applications, 6 pages, 3 colors, indicates appropriate varactor for doubler, tripler and quadrupler circuits for given input frequency range and power level.—**Sylvania**, Semiconductor Div., 100 Sylvan Rd., Woburn, Mass.

ULTRAMINIATURE CAPACITORS, *Bulletin NPJ-131*, single looseleaf page, gives photo, specs and stock listing of TTC-type electrolytic capacitors, so small that markings are limited to voltage and capacitance.—**Aerovox Corp.**, Distributor Div., New Bedford, Mass.

PHASE CALCULATION NOMOGRAPH covers frequency range from 200 to 10,000 mc, makes quick conversion from wavelength to distance along a slotted line in centimeters. Useful in Smith Chart calculations in conjunction with slotted-line measurements.—**General Radio Co.**, West Concord, Mass.

CATALOG SHEET. Single loose-leaf addition to Ferroxcube catalog listing 17 Ferroxcubes with short descriptions, photos, and prices.—**Ferroxcube Corp. of America**, Saugerties, N.Y. END


Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears.

UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.


Outperforms Finest Vacuum Tube Units

NEW SCOTT 312 SOLID STATE FM TUNER


... yet it's only \$259.95!

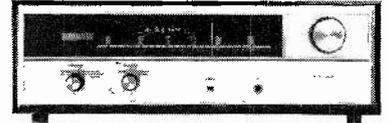

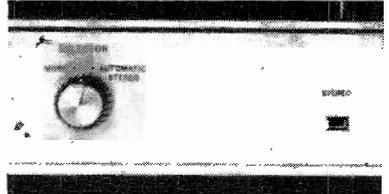Scott announces a top-performing solid-state FM stereo tuner at a modest price... a no-compromise tuner that exceeds the performance of conventional tube units... it's factory-guaranteed for 2 full years. Not just a redesigned unit, the Scott 312 incorporates an entirely new approach to tuner circuit design:



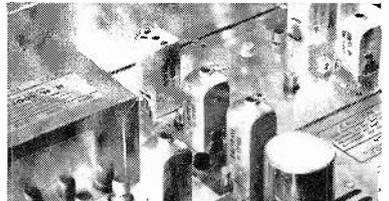Exclusive "Comparatron" provides foolproof silent automatic stereo switching. Momentary changes in signal strength will not cause stereo to switch in and out as do ordinary automatic devices.



"Flat-Line Limiting" circuits assure quiet, noise-free FM reception, impervious to outside electrical interference. There's actually less than 1 db difference in tuner output whether you listen to a strong local station or a weak distant one.



H. H. SCOTT, INC. Dept. 570-08
111 Powdermill Road, Maynard, Mass.

Please rush me complete information and specifications on the new Scott 312 FM solid-state tuner, plus Scott's full-color 24-page Guide to Custom Stereo for 1964.


Name _____

Address _____

City _____

State _____ Zip _____

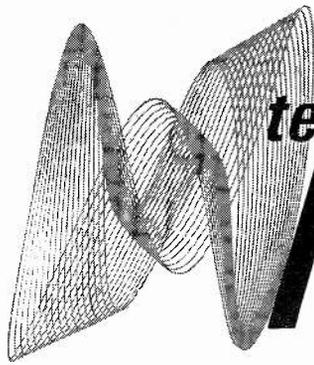Export: H. H. Scott International, 111 Powdermill Road, Maynard, Mass. Cable: HIFI Canada: Atlas Radio Corp., 50 Wingold Avenue, Toronto



technicians' News

THE BOUNCING CHECK GATHERS NO CASH

An article by Bill Dufer, Jr., in the May *NATESA Scope* brought together several noteworthy hints on handling the bad-check problem. The suggestions were more preventive than curative, but that's as it should be. Better not to accept a bad check in the first place than to try and make it good later.

One radio-TV technician, the article says, has installed in his shop a bulletin board on which he tacks up local "wanted" posters—photos and descriptions of "paperhangers" thought to be working in the vicinity. The board also bears up-to-date newspaper clippings of sentences meted out to check passers who have tried to bamboozle local merchants.

This same technician also has posters on his wall: "Please check your current checking account balance before

tendering us a check." Such posters, the author points out, do not offend customers whose intentions are honorable. If they irritate those customers whose intentions *aren't* honorable—well, who wants them, anyway?

Another shop insists that every customer who wants to pay by check show a checkbook and a deposit slip not more than a week old, unless the owner knows him personally. Every patron who tenders a check for "services rendered" receives a "conditional receipt"—a service invoice with the words "If this invoice has been paid by check, it will not be considered as having been paid until check clears *our* bank."

If the customer gets cash change, the amount is noted on the invoice, and the customer must sign it. The shop will not pay out more than \$10 in cash to anyone not personally known to them.

FTC FILES AGAINST DELAWARE VALLEY ASSOCIATION

Two former executives and present directors of the Television Service Association of Delaware Valley have been ordered by the Federal Trade Commission to appear at a hearing in Washington on July 20.

The FTC notified them that they would have to answer complaints against the local organization, and respond to a cease and desist order regarding the following charges:

That the TSADV was inciting servicers to boycott parts distributors who continue selling to the public or to non-servicing dealers; and that TSADV was intimidating distributors' organizations and advocating a policy of blacklisting distributors who didn't stop open selling.

Named specifically in the complaint were Herman Shore, former president and current member of the group's board of directors, and Raymond Fink, former recording secretary and now a director.

MILITARY MOONLIGHTER ORDERED TO HALT

Some members of the King County (Washington) Television Service Association noticed a TV service ad that gave a local military base (Fort Lawson) telephone exchange and featured evening service. TSA called the commanding officer of the post to ask about the Army's regulations covering use of military facilities for a commercial en-

HOTTEST

DEAL EVER OFFERED!

RCA

#CTC-11 COLOR TV CHASSIS \$86

We scooped the market—Wired complete (less Tubes & CRT) need minor finishing touches or parts, incl. Schematic

Including full Set of Tubes (less CRT) . . . \$99

FREE—1 DOLLAR BUY WITH EVERY 10 ORDERED—PLUS FREE GIFT

- UNIVERSAL 5" PM SPEAKER \$1
Alnico 5 magnet, quality tone . . .
- UNIVERSAL 4" PM SPEAKER \$1
Alnico 5 magnet, quality tone . . .
- ELECTROSTATIC 3" TWEETER \$1
SPEAKER for FM, HI-FI, etc. . .
- 2 — UNIVERSAL 2 1/4" PM \$1
SPEAKERS for Radios, Intercorn,
as multiple Speakers, etc.
- 3 — SPEAKER CABINETS for \$1
2 1/4" to 3" speaker, all purpose
- 3 — AUDIO OUTPUT TRANS- \$1
FORMERS 50L6 type
- 3 — AUDIO OUTPUT TRANS- \$1
FORMERS 6X6, 6V8
- 3 — AUDIO OUTPUT TRANS- \$1
FORMERS 3V4, 3Q4, 354
- 15 — RADIO OSCILLATOR \$1
COILS standard 456kc
- 3 — I.F. COIL TRANSFORM- \$1
ERS 456kc, most popular type
- 3 — I.F. COIL TRANSFORM- \$1
ERS 262kc, for auto radios . . .
- 3 — I.F. COIL TRANSFORM- \$1
ERS 10.7mc for FM
- 3-1/2 MEG VOLUME CON- \$1
TROLS with switch, 3" shaft . .
- 5 — ASST. 4 WATT WIRE- \$1
WOUND CONTROLS
- 10 — ASSORTED VOLUME \$1
CONTROLS less switch
- 5—ASSORTED VOLUME CON- \$1
TROLS with switch
- 5—I.F. COIL TRANSFORMERS \$1
sub-min for Transistor Radios .
- 5 — AUDIO OUTPUT TRANS- \$1
FORM sub-min for Trans Radios
- 5—PNP TRANSISTORS \$1
general purpose, TO-5 case . .
- 5—NPN TRANSISTORS \$1
general purpose, TO-5 case . .
- 10—DIODE CRYSTALS 1N34 \$1
- 10—ASST. DIODE CRYSTALS \$1
5—1N60 and 5—1N64
- 2—SILICON RECTIFIERS \$1
750ma, 400 PIV
- 25 — SYLVANIA HEAT SINKS \$1
for Transistors, etc.
- 70 — ASSORTED 1 WATT \$1
RESISTORS some in 5%
- 35 — ASSORTED 2 WATT \$1
RESISTORS some in 5%
- 50—PRECISION RESISTORS \$1
asst. list price \$50 less 98%
- 20 — ASSTED WIREWOUND \$1
RESISTORS, 5, 10, 20 watt . .
- 6 — ASST. SELENIUM RECTI- \$1
FIERS 65ma, 100ma, 300ma, etc.
- 2—LOOPSTICK ANTENNAS \$1
hi-gain, ferrite, adjustable . . .
- 10—TOGGLE SWITCHES SPST \$1
deluxe U.L. approved, 101 uses
- 5 — ASSORTED TRANSFORM- \$1
ERS Radio, TV and Industrial . .

- CHAPT ZU DI MITZIA "JACK- \$1
POT" double your money back
if not completely satisfied
- 10—6' ELECTRIC LINE CORDS \$1
with plug standard brands . . .
- 4 — 50' SPOOLS HOOK-UP \$1
WIRE 4 different colors
- 50' — INSULATED SHIELDED \$1
WIRE #20 braided metal jacket
- 32"—TEST PROD WIRE \$1
deluxe quality, red or black . .
- 50'—HI-VOLTAGE WIRE \$1
for TV, special circuits, etc. . .
- 200'—BUSS WIRE #20 tinned \$1
for hookups, special circuits, etc.
- 10 SETS — DELUXE PLUGS & \$1
JACKS asst. for many purposes
- 3—CONNECTORS #PL-259 \$1
- 3—CONNECTORS #50-239 \$1
- 3—3" RECORDER TAPES \$1
quality acetate, 150 feet
- 1—SQ. YARD GRILLE CLOTH \$1
most popular brown & gold design
- 8—ASST. LUCITE CASES \$1
hinged cover, handy for parts . .
- 30—BALL POINT PENS \$1
retractable, assorted colors . . .
- "EASY CUT" FIBERSCREEN \$1
FILTER 15"x24" cuts to size for
any Air Conditioner, perfect fit
- 4—TRANS. RADIO BATTERIES \$1
9 volt, same as Eveready #216

MARKET SCOOP COLUMN

- 1000' SPOOL HOOK-UP WIRE \$1
#22, solid, black, \$6.50 value
- 1000—ASST. HARDWARE KIT \$1
screws, nuts, washers, rivets, etc.
- 1000—ASSORTED RIVETS \$1
most useful selected sizes
- 1000—ASSORTED WASHERS \$1
most useful selected sizes
- 100'—STANDARD ZIP CORD \$1
2 conductor #18 white or brown
- 100'—MINIATURE ZIP CORD \$1
2 conductor, serves 101 uses . .
- 100—ASST. RADIO KNOBS \$1
all selected popular types
- 100—RADIO & TV SOCKETS \$1
all type 7 pin, 8 pin, 9 pin, etc.
- 100—ASST. TERMINAL STRIPS \$1
all types, 1-lug to 6-lug
- 100—ASST. CERAMIC CON- \$1
DENSERS some in 5%
- 100—CERAMIC CONDENSERS \$1
Erie 50mmf-500v, 5%
- 100 — ASSORTED 1/2 WATT \$1
RESISTORS some in 5%
- 100 — ASST 1/4 WATT RESIST- \$1
ORS choice ohmmages, some 5%
- STARLITE TRANSISTOR RADIO \$1
has Cabinet, Speaker & many
Parts—sold as-is & pot-luck . .
- 100—MIXED DEAL "JACK- \$1
POT" Condensers, Resistors,
Surprises

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y. TELEPHONE
COrtlandt 7-2359

terprise in competition with civilian businesses outside the base.

The post commander agreed that the free telephone, free rent and other tax-free benefits were a definitely unfair means of competition to outside establishments that couldn't have such advantages.

After investigation, the CO called TSA to assure them that the specific operation had been closed down, and that the post's daily bulletin would warn all personnel on the base that such operations are prohibited.

SEMICONDUCTORS INVADE AUTOMOBILE FIELD

The automobile industry spent more than \$15 million for semiconductor devices in 1963. According to D. I. Van Blois, graduate student at Michigan State University, the expenditure for 1965 will be about \$20 million, and in 1970 possibly \$65 million.

The most important use of semiconductors in automobiles, Van Blois said, was in car radios, which in 1963 represented \$8.2 million. Next significant use is in car alternators. At about 6 diodes per car, \$7.7 million was spent in 1963.

The transistorized voltage regulator is another important semiconductor adjunct, though cost is keeping down its wide-scale use. Transistor ignition is also, of course, one of the most rapidly growing consumers of semiconductors. Now available as an optional item on Pontiac and Chevrolet cars and Ford

trucks, its use is expected to spread rapidly.

Other uses of semiconductors are in temperature control systems ("Comfort Controls") automatic headlight dimmers, auto horns, fuel pumps and synchronized clocks.

SWEDEN TV VIEWERS UNHAPPY WITH TV DO SOMETHING ABOUT IT

A novel form of TV entertainment has been proposed by about 400 discontented television viewers of Smedjebacken, Sweden. According to a recent Reuters report, Ulf Jansson, a caretaker, stated, "We are tired of television and of staring stupidly at the screen. Now we aim to get together and have some fun instead. We will hold a dance here on Saturday and after the dance we will make a bonfire of 400 television sets."

INFRARED RADIATION NEW SERVICE TECHNIQUE?

Infrared radiation from electronic components can be used to identify short-life parts and predict the reliability of circuits. This statement was made by A. Feduccia of Rome Air Development Center, Griffis Air Force Base, New York, to the International convention of the IEEE.

An infrared camera is used to make thermal photographs (thermographs), showing the temperature distribution over desired areas. Cold areas are darker. As components become warmer, they

appear as lighter and lighter grays. Thus a thermograph of the underside of a chassis, printed-circuit board or single component can show immediately whether any areas of the components are hotter than normal, as indicated by comparison with a thermograph of known-good equipment.

TRANSISTOR ANTENNAS INVADE BRITAIN

An electronics engineer in Devon, England, claims to have invented a cigarette-pack-size transistor-and-battery device that makes outdoor TV antennas unnecessary and at the same time improves reception.

The unit, reminiscent of our recent endeavors in "antennaless antennas", is apparently some sort of booster, since it is described as plugging between set and indoor antenna. It sells for approximately \$12.

A British reporter who attended a demonstration of the new device told of "a brilliantly sharp picture and no interference."

David Sarnoff, chairman of RCA, predicts 3-D wall TV by the end of the century. He also said: "Ultimately, individuals equipped with miniature TV transmitter-receivers will communicate with one another via radio, switchboard and satellite, using personal channels, similar to today's telephone number."

END

IMMEDIATE DELIVERY... SCIENTIFIC LIGHT PACKING for safe delivery at minimum cost. **HANDY WAY TO ORDER**—Pencil mark items & enclose with check or money order, add extra for shipping, excess refunded with advantage to customer. Tearsheet will be returned with order, as your packing slip.

- 1-LB SPOOL ROSIN-CORE SOLDER 40/60 top quality .. \$1
- 250-ASST. WOOD SCREWS finest popular selection .. \$1
- 250 - ASST. SELF TAPPING SCREWS #6, #8, etc. \$1
- 150-ASST. 6/32 SCREWS and 150 6/32 HEX NUTS ... \$1
- 150-ASST. 8/32 SCREWS and 150-8/32 HEX NUTS .. \$1
- 150-6/32 HEX NUTS and 150-8/32 HEX NUTS .. \$1
- 100 - ASST RUBBER & FELT FEET FOR CABINETS best sizes \$1
- 10 - ASSORTED SLIDE SWITCHES SPST, DPDT, etc. \$1
- 4-TOGGLE SWITCHES SPST, SPDT, DPST, DPDT ... \$1
- 15-ASST. ROTARY SWITCHES all popular types \$20 value .. \$1
- 50-ASSORTED #3AG FUSES Popular assorted ampere ratings \$1
- 20 - STANDARD FUSE HOLDERS for 3AG fuses, easy mount \$1
- 250-ASST. SOLDERING LUGS best types and sizes .. \$1
- 50 - STRIPS ASSORTED SPAGHETTI handy sizes .. \$1
- 100 - ASSORTED RUBBER GROMMETS best sizes .. \$1
- 10 - SURE-GRIP ALLIGATOR CLIPS 2" plated .. \$1
- 10 - SETS PHONO PLUGS & PIN JACKS RCA type ... \$1

TV BARGAIN COLUMN


- \$15.00 TELEVISION PARTS "JACKPOT" best buy ever .. \$1
- 4 - TV ALIGNMENT TOOLS most useful assortment .. \$1
- \$12 TV FLYBACK TRANS 90° for all type TV's incl schematic \$1
- 90° TV DEFLECTION YOKE wired network, schematic diag. \$1
- 70° FLYBACK TRANSFORMER universal incl schematic diagram \$1
- 70° TV DEFLECTION YOKE wired network, incl schematic .. \$1
- 3-TV VERT OUTPUT TRANS universal 10:1 ratio for all TV's \$1
- 4-DUMONT VERT OSC TRANS incl schematic for many TV uses \$1
- 20-ASSORTED TV COILS I.F. video, sound, ratio, etc. .. \$1
- 40-ASSORTED TV KNOBS all standard types, \$40 value .. \$1
- REGO INDOOR TV ANTENNA hi-gain, 4 section, tiltproof .. \$1
- 100' - TWIN TV LEAD-IN WIRE 300 ohm, heavy duty .. \$1
- 5-TV CHEATER CORDS with both plugs .. \$1
- 20 - ASSORTED GRID CAPS for 1R3, 1X2, 6BG6, 6BQ3, etc. \$1
- 50-ASSORTED TV PEAKING COILS all popular types .. \$1
- 4-TV TAPER CABINET LEGS deluxe 10" walnut 4/18 screw \$2
- G.E. TV POWER TRANS 250-ma, 360/360v, 6.3-9A, 5v-3A .. \$4

- \$15.00 RADIO PARTS "JACKPOT" handy assortment .. \$1
- 50-RCA LUCITE RADIO KNOBS popular type w. indicator pointer .. \$1
- 3-ASST. SIZES RADIO CHASSIS PANS drilled & plated .. \$1
- 3-VARIABLE CONDENSERS asst. popular super-het types .. \$1
- 50-ASSORTED PRINTED CIRCUIT SOCKETS best types .. \$1
- 20 - INSTRUMENT POINTER KNOBS selected popular types \$1
- 100' - FINEST NYLON DIAL CORD best size, .028 gauge .. \$1
- 20-ASST. PILOT LIGHTS #44, 48, 47, 51, etc. \$1
- 20 - PILOT LIGHT SOCKETS bayonet type, wired .. \$1
- 3 - ELECTROLYTIC CONDENSERS 50/30-150v .. \$1
- 3 - ELECTROLYTIC CONDENSERS 40/40mf-400 volts .. \$1
- 10 - ASST. RADIO ELECTROLYTIC CONDENSERS .. \$1
- 3 - ELECTRO CONDENSERS 10/10/10-450 volts .. \$1
- 50 - ASST. TUBULAR CONDENSERS .001 to .47 to 600v \$1
- 20-GOODALL TUBULAR CONDENSERS .047-600v .. \$1
- 20-BENDIX BUFFER CONDENSERS .007-2000v \$15 value .. \$1
- 50-ASSORTED MILAR CONDENSERS .001 to .47 .. \$1
- 20 - EXTERNAL ANTENNA HANKS 15' for FM, other radios \$1

MARKET SCOOP COLUMN

- \$17.50 WEBSTER DIAMOND CARTRIDGE #SC2-D Stereo .. \$1
- RONNETTE DUAL SAPPHIRE CARTRIDGE flipover type ... \$1
- DIAM. NEEDLES Ronette BF40, Sonotone 2TS, Monarch, Vaco ea. \$1
- 3 SAPPHIRE STYLUS NEEDLES for all type pickups .. \$1
- 3-\$2.50 SAPPHIRE NEEDLES guaranteed 5000 playings .. \$1
- 50-G.E. FLASHLIGHT BULBS #PR-9, 2.7 volts .. \$1
- 4-IBM COMPUTER SECTIONS loaded with valuable parts ... \$1
- 8 - TV ELECTROLYTIC COND good range popular types .. \$1
- 3-G. E. COMPUTER SECTIONS loaded with valuable parts .. \$1
- 4-MAGNETIC SWITCHES Minneapolis Honeywell, latest type .. \$1
- 2-STANDARD ELECTROLYTIC CONDENSERS 40/40-450v .. \$1
- 3-STANDARD ELEC CON. DENS 20/20-450v serves as 40-450v .. \$1
- 10-ITT SELENIUM RECTIFIERS 65ma-14v brand new fact. stock \$1
- 8-ITT SELENIUM RECTIFIERS 100ma-14v brand new fact. stock \$1
- RCA TUBES-JOBBER BOXED 1A6, 1AD3, 1AH4, 1S4, 1T5, 3BE6, 3H8, 3HY6, 45Z3, 6J7, 6S7, 6ST7, 6U7, 6U7, 12BK6 .. \$1
- any amount of each or assorted your choice ... \$1

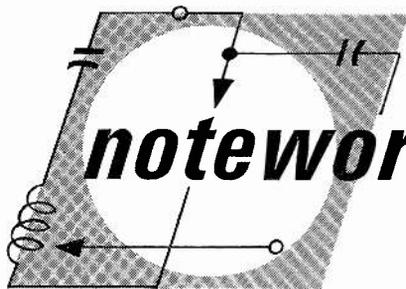BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N. Y. TELEPHONE COrtlandt 7-2359




noteworthy Circuits

BRAIN-WAVE AMPLIFIER

This simple-appearing amplifier uses a 2N2714 in its input circuit to handle much lower voltages than do ordinary transistors. The 2N2714 is an epitaxially grown passivated unit designed

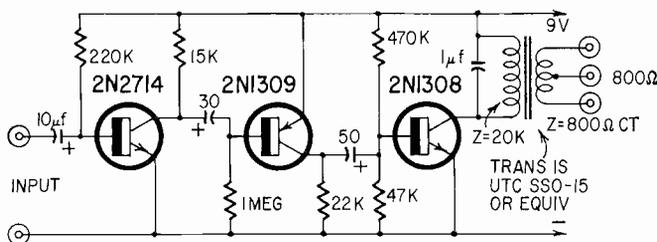nals from 0.5 to 30 cycles. Remove the 1- μ f capacitor across the transformer and the bandwidth rises to 20 kc. Input can be as low as 5 microvolts at 10 cycles and must not exceed 1 millivolt.



for high-gain, low-noise applications. With selected transistors, the amplifier's gain can be as high as 500,000.

The amplifier was designed for brain-wave potentials and handles sig-

Operated within its range, the amplifier makes a fine scope preamp. A step attenuator can be used to increase the range.—Tom Jaski

MORE ON THE SIGNAL INJECTOR

A number of readers constructed the 1-kc phase-shift oscillator described in "Build a Signal Injector Into Your VTVM" (RADIO-ELECTRONICS, April

The 25,000-ohm output potentiometer has been replaced by a transformer with a 100-ohm output impedance. (I used an Argonne AR-150 input transformer with the primary connected

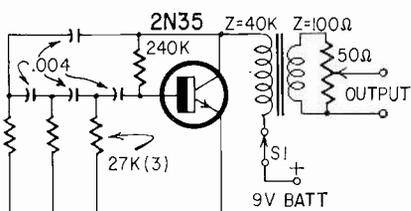


Fig. 1

1963) and have requested information on adapting it for other applications. Some want to use it as a troubleshooting accessory with battery power and a low-impedance output for feeding low-impedance mike inputs. Fig. 1 shows the circuit modified to comply with these requests.

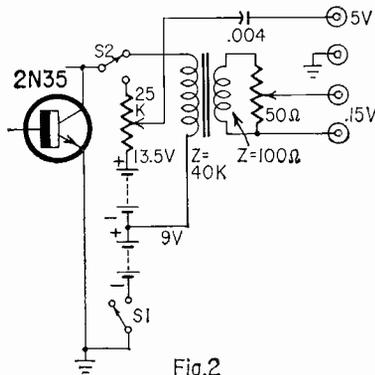


Fig. 2

as the secondary.) The original circuit received its power from the vtm. The version in Fig. 1 uses a 9-volt battery


such as the RCA VS-300A. The maximum output level is 0.15 volt. After 8 hours of continuous operation, the output drops not more than .03 volt.

Some constructors wanted both high- and low-impedance outputs so they would have the high output (up to 5 volts) for feeding directly into power amplifiers. Fig. 2 shows how the output circuit can be modified. S2 selects the desired output.

Several readers report constructing the oscillator in a 1 5/8 x 2 1/8 x 3 1/4-inch aluminum utility box and carrying it in their tool box for testing and troubleshooting.—Harold Reed

ADD A 2-KV RANGE TO EICO VTVM

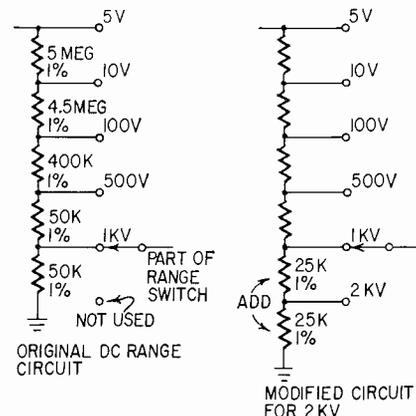The versatility of Eico model 214 and 221 vacuum-tube voltmeters can be increased by doubling the upper voltage range of 1,000 volts dc. The 2,000-volt range permits troubleshooting higher-voltage devices such as oscilloscopes and medium-power transmitters. Since these generally employ voltages rang-



ing between 1,000 and 2,000, you can't check them ordinarily without a high-voltage probe—with its inherent excess range multiplication.

Many Eico vtvm's employ a range-selector switch with an unused position beyond 1,000 volts. A simple circuit change utilizing this extra switch position permits adding a 2,000-volt range without difficulty. The original voltage-divider resistor to ground in the meter on the 1,000-volt range position is 50,000 ohms, 1%. To add a 2,000-volt range, substitute two 25,000-ohm 1% resistors for the 50,000-ohm unit. The diagrams show the original and modified circuits. The photo shows the modified range switch. If the lugs on the other sections of the range switch for this position are not wired connect them to the lugs corresponding to the 1,000-volt position. To prevent breakdown of the probe resistor, two series-wired 7.5-megohm 1/2-watt 5% (or better) carbon-composition resistors should be substituted for the original 15-megohm 1/2-watt 5% resistor. As an additional safety precaution, a more effectively insulated probe may well be used.

To use the vtvm on this new range, all readings made on the 1,000-

fix ELECTRIC APPLIANCES \$3 TO \$5 AN HOUR

FREE BOOK tells about profitable spare-time or full-time business that pays \$3-\$5 hour — right at home! 400 MILLION Appliances now in use. People need them fixed. YOU make good money doing it. Our complete, easy course trains you for top earnings. At no extra charge you get time-saving Appliance Tester. Get FREE Book. FREE Sample Lesson! Mail coupon now.

NATIONAL RADIO INSTITUTE, Appliance Div.
Dept. 503-084, Washington 16, D. C.
Send Free Book, Free Appliance Repair Course Lesson.
Name.....
Address.....
City.....Zone.....State.....

FREE BOOK


FREE LESSON

FREE Catalog

OF THE WORLD'S FINEST ELECTRONIC GOV'T SURPLUS BARGAINS

HUNDREDS OF TOP QUALITY ITEMS — Receivers, Transmitters, Microphones, Inverters, Power Supplies, Meters, Phones, Antennas, Indicators, Filters, Transformers, Amplifiers, Headsets, Converters, Control Boxes, Dynamotors, Test Equipment, Motors, Blowers, Cable, Keys, Chokes, Handsets, Switches, etc., etc. Send for Free Catalog—Dept. RE.

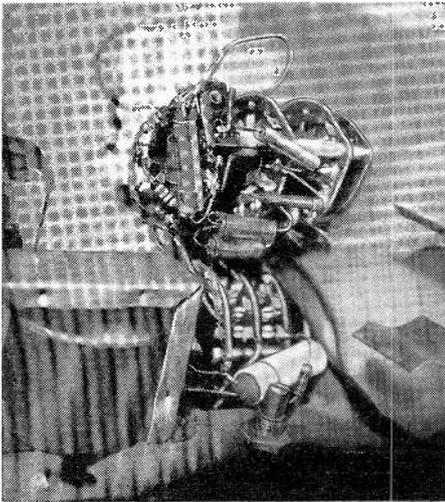FAIR RADIO SALES
2133 ELIDA RD. • Box 1105 • LIMA, OHIO




(0-10) volt scale are multiplied by 2.
—Harold J. Weber

[Eico engineers report that this is a worth-while modification but stress the fact that the switch insulation may break down. Keep the switch wafer clean and free of flux, dust and other foreign matter that may cause arcing or high-resistance shorts. They warn that this modification is limited to the dc voltage range. Attempting to measure over 1,000 volts ac is likely to damage the ac rectifier.—Editor]

VERTICAL DEFLECTION CIRCUIT

The 1964 Philco chassis have a number of interesting features. Among them are the unusual vertical size compensation circuit and a vertical size control that replaces the height control in earlier circuits. The vertical deflection circuit in the 14G20 chassis is shown in the diagram. Minor circuit variations are used in other recent chassis.

The varistor is a sort of automatic size control. It prevents any changes in the brightness setting or CRT operating level from affecting the overall height of the picture. During the retrace interval, high positive peaks are developed in the output transformer and across the .022- μ f capacitor and varistor in series. The varistor's resistance drops and the pulse is absorbed in charging the capacitor. During the normal sweep, the varistor's resistance returns to normal. The capacitor discharges through R24, R16, the VERT SIZE control and R53, and develops a negative voltage across this network. This biases the output stage.

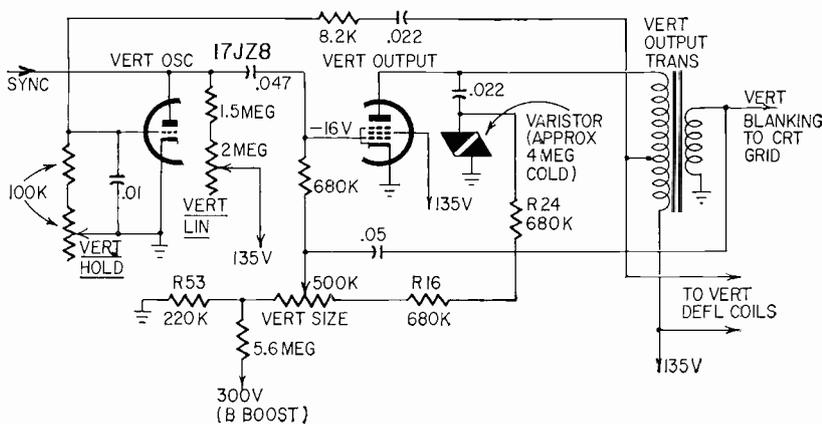

for the critical recordist...
ANOTHER "FIRST" FROM UNIVERSITY



THE 8000

It's shock-mounted! It's a dynamic!
It's a cardioid! And it's only \$29.95
(It's also guaranteed for 5 years!)

Today...from the laboratories of University...an advanced technology has produced a great new microphone for the critical home recordist. It represents a clean and dramatic break with tradition—with outmoded notions. Considering its moderate price, you would expect it to be an ordinary crystal, carbon—or at the most, dynamic omni-directional. It isn't. The 8000 is a cardioid dynamic typical of the finest professional recording microphones. With its superb directional characteristics, it virtually eliminates background noise. You can work close or far—you will achieve a degree of clarity and definition you never thought possible before. Response: 70-13,000 cps. Sensitivity: -156 db (EIA). Output Level: -59 db/1mw/10 dynes/cm². Includes 15 ft. cable with choice of high or low impedance at the Cannon plug and receptacle! Includes desk stand adaptor. Only \$29.95.

For complete specifications, write Desk RE-8, LTV/University, 9500 West Reno, Oklahoma City, Oklahoma,


LTV
UNIVERSITY

A DIVISION OF LING-TEMCO-VOUGHT, INC.

U-49R

Since the negative voltage is proportional to the amplitude of the vertical deflection voltage, it varies the bias in the direction that holds height constant.


The VERT SIZE control is unusual in that it affects the top and bottom of the picture. (Most height controls affect only the top of the picture.) The B-boost voltage (300 volts) is fed to the bias network for the output stage. When the BRIGHTNESS control is advanced, the beam current increases, the high voltage drops and the picture tends to expand. However, as the high voltage drops, the boost voltage decreases in proportion. The voltage across the size control becomes more negative. The bias increases and the deflection voltage is reduced to hold picture size constant.—H. Maxwell

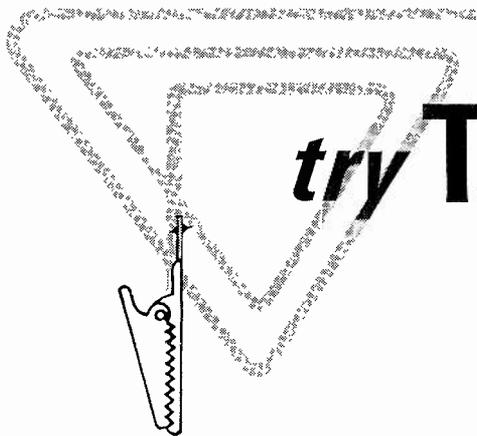

try This one

NEON PILOT IS READY LIGHT

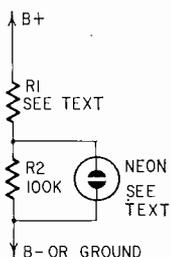By connecting a small neon lamp (like one of the NE-2 or NE-51 series) as shown in the diagram below, you can make a pilot light that indicates when




B-plus is up to full operating value. To set up the circuit, connect the

lamp across R2, 100,000 ohms, and use a 1-megohm pot as R1, set to maximum resistance. Reduce the pot's resistance until the lamp just fires. Measure the resistance and use the next lower 10% 1/2-watt fixed resistor. — *Irwin Math, WA2NDM*

TWO-FACED TAPE HOLDS TURNS

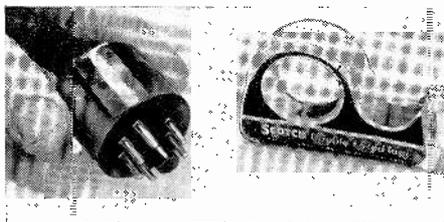
If you wind your own coils on smooth plastic or Bakelite forms, take a couple of strips of double-faced plastic



tape and place them on opposite sides of the coil form, lengthwise. The sticky, low-loss tape will hold each strand of wire securely in place so that the coil can be wound easily and spaced accurately. — *John A. Comstock*

RESISTORS "SPLIT" TRANSFORMERS WINDING

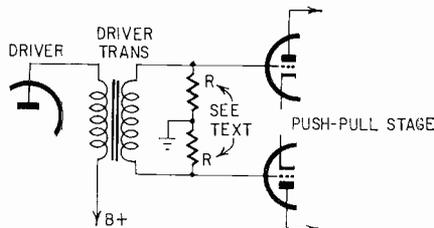Occasionally you may need to drive a push-pull stage, yet not have a split or center-tapped transformer, or room for a




phase inverter. Use a single-plate-to-single-grid transformer with a pair of closely matched resistors R connected as shown here. Values from 47,000 to 470,000 ohms are usually satisfactory. — *Irwin Math*

[This method is not generally good for class-AB₂ or -B amplifiers, which must have low grid impedances. — *Editor*]

CLOTHESPIN WIRE STANDOFFS

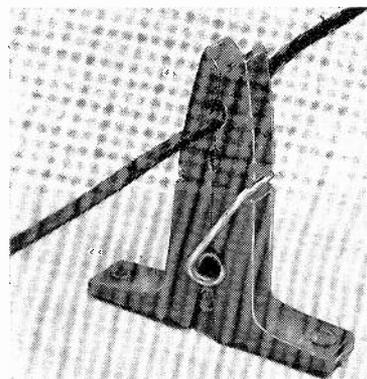
Need some standoff insulators for a radio or TV lead-in?



You can make ordinary plastic clothespins into low-loss standoffs for round or ribbon wire. Simply saw off the legs of each pin and cement them back in place at an angle to form feet. Don't try to heat and bend the legs, for they will probably break. Most any good plastic cement may be used. Mount the insulators with small nails driven through the holes in the feet. — *John A. Comstock*

INTENSITY MODULATING HEATH IO-10

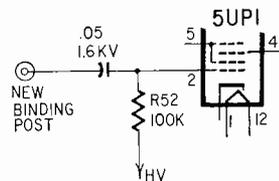To add intensity modulation to the Heath IO-10 dc oscilloscope, all that is needed is one high voltage capacitor,



connected to pin 2 of the CRT socket, and one new binding post. There is plenty of space for the post on the rear panel of the scope. — *Tom Jaski*

STORING SPARE PLUGS

In areas where you meet several kinds of power receptacles, compatibility is a problem. Sometimes adapters are available; sometimes not—the only choice is to change the plug. The problem here

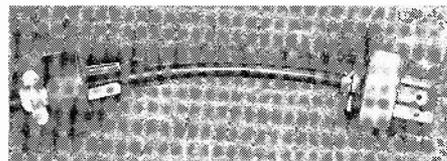



Photo by Morgan S. Gassman, Jr.

is that the unused plug is likely to get lost.

I saw a Western Union maintenance shop solve the problem as shown in the photo. The unused connector is slid back on the cord and fastened with the cable clamp. The required fitting is installed as usual. The unused plug can't possibly be lost, and is available right away when it's needed. — *Roy E. Pafenberg*

HIGH SCHOOL "GRADS"

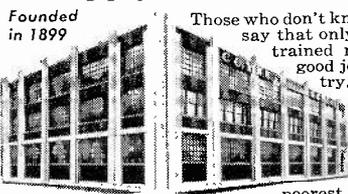You don't need college to have a fascinating job, a bright future, big pay and advancement.



Founded in 1899 Those who don't know the facts say that only the college trained men get the good jobs in industry. Wrong! But it is true that the average high-school graduate gets only the poorest kind of job—unless he has additional training in a specialized field.

For these men the biggest and fastest growing field open today is Electronics—all branches. Jobs are looking for men. You can train in as short a time as 35 weeks in the Electronic Labs of Coyne in Chicago, the Electronics Center of the Country. Most of your tuition can be paid after you graduate.

Like the great universities, Coyne School is an educational institution not for profit. A Coyne diploma gives you high standing with employers. Coyne graduates hold top jobs in Electronics all over the world.

See how little it costs to get the training you need. Don't put it off. Make your own decision. Send us your name, address now—this coupon or a postcard will do. No salesman will bother you at your home. All information is FREE.



Coyne Electronics Institute, Chicago 60607, Dept. C4-N

Coyne Electronics Institute, Dept. C4-N
1501 W. Congress Pkwy., Chicago, Ill. 60607

Please send Free Book "Your Opportunities in Electronics." I am under no obligation—no salesman will call at my home.


Name..... Phone.....

Address..... Age.....

City..... Zone..... State.....

TRANSISTOR TEST LEADS

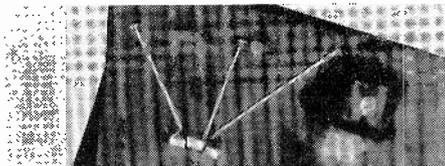Many times it is impossible to remove a transistor completely for insertion in a transistor tester, and many testers have no provision for connecting test leads. The easiest way to make the proper connection is to insert ordinary straight pins into the transistor socket of the tester. (Bend them away from



each other to avoid shorts.) Then use ordinary test leads or clip leads, with alligator clips at both ends, to complete the connection between tester and transistor.

If you have to do in-circuit testing frequently, it is a good idea to make a plug to fit the tester. One can be made easily by opening a dead transistor's case and soldering to the leads on the inside. Cut all leads on the outside to 1/2 inch and straighten them out. The other ends of the three leads soldered to your new plug should be fitted with alligator clips. Label the clips C, E and B.—*Ronald S. Newbower*

COMPRESSED AIR AIDS PRINTED CIRCUIT REPAIR

Any radio or television technician who has worked in a shop where compressed air was available is well aware of the contribution this facility makes to volume, high quality service. A well lighted cleaning booth with forced ventilation and a medium-pressure air hose will make light work of even the dirtiest chassis.

Those who have toiled over removing multiple-lead components from a printed-board circuit will be happy to learn that a blast of compressed air is just as effective in removing excess molten solder. Use a small iron for just as long a time as necessary to melt the solder. The instant the iron is removed, direct a blast of compressed air at the connection. The solder will lift off, leaving a clean tinned board. Direct the air blast to avoid splattering components, such as variable capacitors, that are easily damaged. There is much less mess than would be expected since the solder is cooled and solidified by the air the instant it is lifted from the connection.


This method is equally effective in removing the excess solder from those difficult sweated-solder jobs.—*Roy E. Pafenberg.* END

IODINE EATS RUST

A few drops of iodine on the rust that binds a bolt or screw will quickly loosen the most rust-seized component. The iodine dissolves the rust in a hurry.—*Harry J. Miller*

AUGUST, 1964

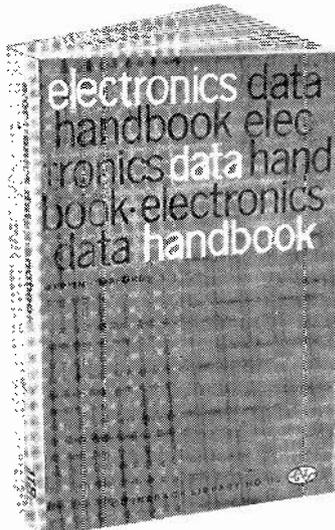ANNOUNCING A NEW GERNSBACK BOOK CONTAINING THE MOST USED, MOST NEEDED FORMULAS AND DATA IN ELECTRONICS



ELECTRONICS DATA HANDBOOK

By MARTIN CLIFFORD

160 PAGES
G/L No. 118

\$2.95 PAPERBACK
\$4.60 Clothbound

- For technicians, engineers, students, hobbyists, hams, experimenters ■ Arranged in logical, orderly fashion for quick easy reference ■ A basic book for your library

If you had only one book in your professional library, this would have to be it. This single volume answers such everyday questions as these: What formula do I need for this problem? Is there an easier formula? Where can I find the data I need? What substitutions can I make in formulas? What sequence of formulas must I use if I need to work with several of them? This one book gives you all the answers, grouped under appropriate headings. You'll wonder how you ever got along without it. Send for your copy today.

PARTIAL LIST OF CONTENTS

D. C. Resistors in series. Resistors in parallel. Resistors in series-parallel. Conversion of units. Resistance of a copper line. Length of a desired resistance. Calculating wire gauge. Resistance vs. temperature. Forms of Ohm's law. Power. Voltage drops. Bleeders. Bias resistors. Batteries in series. Batteries in parallel. Batteries in series-parallel. Kirchhoff's laws. The voltage law. The current law.

A. C. Wave length. Period. Frequency. Instantaneous current. Instantaneous voltage. Pulsating direct current. Alternating and direct currents combined. Capacitors in series. Capacitors in parallel. Capacitors in series-parallel. Amount of electricity stored in a capacitor. Capacitive reactance. Voltage distribution across capacitors in networks. Inductors. Inductors in series. Inductors in parallel. Mutual inductance. Coupled inductance. Inductors in series, aiding. Inductors in series, opposing. Inductors in parallel, aiding. Inductors in parallel, opposing. Q factor. Coefficient of coupling. Inductive reactance. Impedance. Phase angle. Ohm's law for alternating current. Power factor. True power. Apparent power. Resonance. Numerical magnitude of impedance . . . single resistor, resistors in series, single inductor, inductors in series, single capacitor, capacitors in series, resistance and inductance in series, resistance and capacitance in series, inductance and capacitance in series, resistance, inductance and capacitance in series, resistors in parallel, inductors in parallel, capacitors in parallel, inductance and resistance in parallel, capacitance and resistance in parallel, inductance and capacitance in parallel, inductance, resistance and capacitance in parallel, inductance and series resistance in parallel with capacitance, and capacitance and series resistance in parallel with inductance and series resistance.

VACUUM TUBES Thermionic emission. Amplification factor. Dynamic plate resistance. Mutual conductance (transconductance). Gain of an amplifier stage. Voltage output. Determining tube constants. Triode power output. Pentode power output. Maximum power output. Maximum undistorted power output. Plate efficiency. Approximate load resistance. Triode and pentode power sensitivity. Detector efficiency. Negative feedback. Miller effect. Rectifier ripple. Filter formulas. Regulation.

TRANSISTORS Emitter resistance. Base resistance. Collector resistance. Current gain. Voltage gain. Power gain. Collector capacitance. Cutoff frequency. Input impedance. Output impedance. Alpha. Beta. Negative resistance. Power dissipation. Power output.

ANTENNAS and TRANSMISSION LINES: Length of a Hertz antenna. Physical length vs. electrical length. Formula for "end" effect. Resonant frequency. Physical height in wavelengths. Antenna current. Antenna power. Characteristic impedance. Transmission line current. Transmission line peak voltage. Transmission line losses. Attenuation. Frequency. Field strength. Capacitance of a vertical antenna.

MEASUREMENTS: D. C. resistance of a milliammeter. Ohms-volt rating of a voltmeter. Ammeter shunts. Multi-range shunts. Voltage multipliers. Wheatstone bridge. Slide-wire bridge. Kelvin bridge. Series and shunt ohmmeters. Measuring resistance with a voltmeter. Measuring inductance with voltmeter and ammeter. Measuring capacitance. Capacitance-resistance bridge. Wien bridge.

TABLES and MISCELLANEOUS DATA Copper wire table. Specific resistance and temperature coefficients. Table of common logarithms. Natural sines and cosines. Natural tangents and cotangents. Table of vector conversions. Conversion factors. Constants. Mathematical symbols. Resistor color code. Capacitor color codes. Dielectric constants. Transformer color codes. I.F. transformer color codes.

- Buy now from your electronics parts distributor or mail in coupon
- Money-back guarantee within 10 days if not completely satisfied
- Books purchased for professional purposes are tax deductible

GERNSBACK LIBRARY, Inc.

154 West 14th Street, New York, N. Y. 10011

Enclosed is \$_____ Please send

_____ copy(ies) of Electronics Data Handbook @ \$2.95 (paperback)

_____ copy(ies) of Electronics Data Handbook @ \$4.60 (clothbound)

Name _____

Street _____

City _____ State _____ Zip Code _____

84

10 ⁶	1,000,000
10 ⁵	100,000
10 ⁴	10,000
10 ³	1,000
10 ²	100
10 ¹	10
10 ⁰	1
10 ⁻¹	0.1
10 ⁻²	.01
10 ⁻³	.001
10 ⁻⁴	.0001
10 ⁻⁵	.00001
10 ⁻⁶	.000001

10 to the many

Table I—Some Powers of 10

EVER HAD ONE OF THOSE EQUATIONS that turned out like Fig. 1? Well, read on, brother, you've company!

Most technicians shy away from mathematics because of the assumed complexity, but plenty of mathematicians wouldn't open a transistor radio for fear of getting shocked.

I propose to show you how you can reduce those formulas with many numbers to mere shadows of their former selves. Take another look at that formula in Fig. 1. It's only the calculation of

Table II—Some Examples

34,865 cycles	3.4865 × 10 ⁴ cycles
3,600 pf	3.6 × 10 ⁻⁹ farad
1,000 cycles	10 ³ cycles
1 megohm	10 ⁶ ohms
17.5 mc	1.75 × 10 ⁷ cycles
.00045 volt	4.5 × 10 ⁻⁴ volt
.0018 microamp	1.8 × 10 ⁻⁹ ampere

a coil and capacitor to resonate at 10 mc. Complex?

Now look at Fig. 2. Believe it or not, it's the same formula.

The power of ten

Ten is a funny kind of number, because we happen to have based our number system on it. 10 times 10 is 100, 10 times 10 times 10 is 1,000. In other words, every time we multiply by 10, we add a zero to the right side of the number. Odd, isn't it? Instead of writing 10 times 10 times 10 ad nauseam, let's indicate how many times 10 is multiplied by itself with a *superscript*. A superscript is a number placed to the upper right of any other number. Thus, 10 multiplied by itself 5 times (which equals 100,000) is 10⁵. Note that this is different from 10 multiplied by 5 (which equals 50). This system gives us multiples of 10 from 1 (10⁰ equals 1) to as high as you'd like to carry it.

To get numbers between 0 and 1, we can divide 10 by itself as many times

$$L = \frac{1}{4\pi^2 CF^2} = \frac{1}{4 \times 10000000000000 \times .0000000005 \times \pi^2} = .00000557$$

Fig. 1—In this disarmingly simple formula, L is inductance in henries, C capacitance in farads, and F frequency in cycles per second. All you have to do is lose count of the zeros, and then where are you?

as necessary. We show numbers between 0 and 1 with a *negative* superscript, one with a minus sign. Therefore, .01 or 1/100 (1 divided by 10 times 10) is the same as 10⁻².

The purpose of using the powers of 10 is to indicate large or small numbers conveniently. For example, 1 mc is 1,000,000 cycles. From Table I, 1,000,000 is equal to 10⁶ cycles.

Table I is only a guide, not a crutch. To find the power of 10 without using the table, count all the digits in the number, and subtract one. For our example, 1,000,000 has seven digits. Subtracting one leaves six. Therefore, 1,000,000 is equal to 10⁶.

For decimals, count all the digits to the right of the decimal point, but do *not* subtract. For another example, assume a 1-pf capacitor. 1 pf is equal to .000000000001 farad. Counting all the digits, we find there are 12. Because the number is a decimal, the superscript will be negative. Therefore, 1 pf is equal to 10⁻¹² farad.

REMEMBER, use *negative* superscripts for decimals, and *positive* superscripts for numbers 1 or larger.

What happens when you're working with some value that isn't evenly divisible by 10? Well, just multiply. If we were solving our frequency example for 5 mc, we could say that 5 mc equals 5 times 1 mc. Now solve for the power of 10 for 1 mc. The answer is written

$$5 \text{ mc} = 5 \times 10^6 \text{ cycles}$$

Using the system outlined above the answer will always be some number between 1 and 10, times some power of 10. Some examples are shown in Table II.

Let's summarize so far:

- The superscript is positive for numbers 1 or over.
- The superscript is negative for numbers less than 1.
- The superscript may be found for numbers from 0 to 1 by counting the number of digits to the right of the decimal point.
- The superscript for numbers 1

By JERRY L. OGDIN

or more may be found by counting the number of digits to the left of the decimal point, and subtracting one.

Rules for use

Now that we have our new tool, how do we use it? The rules are shown in Table III. This gets easier all the time!

Referring to Fig. 1, we know the frequency is 10 mc, but this must be squared for use in the formula (1 × 10⁷ × 1 × 10⁷ = 1 × 10¹⁴). Because any number multiplied by 1 is the same number, we can dispense with writing the 1. Therefore, (10 mc)² is equal to 10¹⁴ cycles. The 50-pf capacitor is 5 × 10⁻¹¹ farad. When these figures are put into the proper slots in the formula, we can multiply by 10's again, and 10¹⁴ × 10⁻¹¹ = 10³. After performing the rest of the regular division, we have .00557 over 10³.

By the rules in Table III, the number under the line may be moved to the top of the line by changing the sign of

Table III—The Rules

Rule one: If two powers of 10 are multiplied together, just add the superscripts.

Examples: 10¹⁰ × 10⁴ = 10¹⁴
 10⁶ × 10⁻³ = 10³
 10⁻² × 10⁻⁴ = 10⁻⁶

Rule two: If a power of 10 is on the "wrong side of the dividing line," we can move it, but we must change the sign of the superscript.

Examples: $\frac{3}{10^3} = 3 \times 10^{-3}$
 $4 \times 10^{-2} = \frac{4}{10^2}$


the superscript. Applying powers of 10 again, the answer is 5.57 × 10⁻⁶ henry, which is 5.57 microhenries.

By proper use of the powers of 10, the accuracy of your math will be increased, because you won't have to wrestle with cumbersome long numbers.

Good luck when you get a number like 10⁴³⁶². END

$$L = \frac{1}{4\pi^2 CF^2} = \frac{1}{4 \times 5 \times 10^{14} \times 10^{-11} \times \pi^2} = \frac{.00557}{10^3}$$

Fig. 2—Same formula, same numbers, expressed a different way. More convenient, because manipulation of powers of 10 uses just simple addition and subtraction. Takes less space, too. Likelihood of errors is drastically reduced.

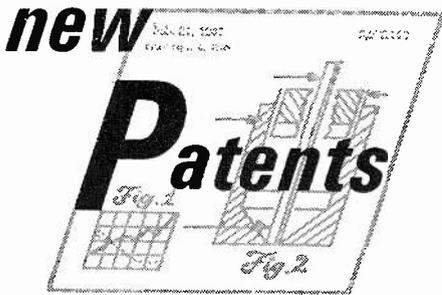


SEISMOMETER

PATENT No. 3,118,126

Fred A. Brock, Kenneth E. Burg, and Markwick K. Smith, Dallas, Tex. (Assigned to Texas Instruments, Inc.)

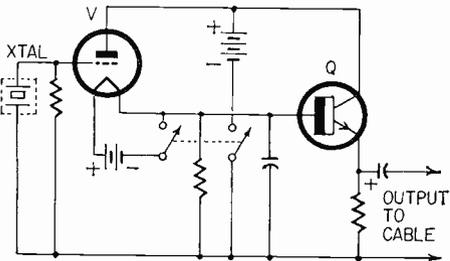Conditions below the earth's surface can be explored with pressure or shock waves. Reflections detected by a seismometer indicate the composition and density of the earth's layers. This seismometer, designed for underwater placement, contains a piezoelectric crystal, a tube, a transistor



and batteries. It matches the high-impedance crystal and a low-impedance transmission line output. The tube, connected as a cathode follower, has an input impedance of several megohms. Its relatively low output impedance feeds the transistor, an emitter follower, which has an output impedance of only a few hundred ohms.


V and Q are inside a compartment hemetically sealed against seepage. The crystal is constructed as a hollow cylinder, sensitive to pressure waves. A cable connects the instrument to a recording station on land.

AUTO BATTERY CHARGER

PATENT No. 3,117,269

Louis Pensak, Princeton, N.J. (Assigned to Radio Corp. of America)

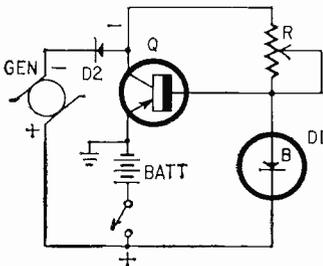The battery is charged from rectified output of a generator. D1 (a Zener diode) and R form a voltage divider for the base of Q. Assume the switch is closed. If the battery voltage is low (discharged), D1 operates below Zener value and



does not conduct. The base return is to the negative terminal. Therefore Q conducts heavily, and passes charging current into the battery.

As the battery voltage rises, a higher voltage appears across D1. When the Zener value is reached, D1 conducts and provides a path between base and the positive terminal. If R is properly set, Q is blocked and overcharging is prevented.

D2 is a conventional diode that merely protects the transistor from bearing the entire back voltage if the generator should fail when the battery is fully charged. It can be omitted if the transistor's breakdown rating is high enough. END

SCHOOL DIRECTORY

MATHEMATICS

ELECTRONICS

These courses are the result of many years of study and thought by the President of IHSI, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics and electrical and electronic engineering.

You will have to see the lessons to appreciate them! YOU SIGN NO CONTRACTS—you pay ONLY for the Lessons you order.

Write today for your outline of courses. You have nothing to lose, and everything to gain! The INDIANA Home Study Institute Eastern Division 64 Hemenway Road Framingham, Mass.

EARN Electronics Engineering DEGREE

You can earn an A.S.E.E. degree at home. College level HOME STUDY courses taught so you can understand them. Continue your education, earn more in the highly paid electronics industry. Missiles, computers, transistors, automation, complete electronics. Over 27,000 graduates now employed. Resident school available at our Chicago campus—Founded 1934. Send for free catalog.

American Institute of Engineering & Technology 1139 West Fullerton Parkway, Chicago 14, Ill.

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology and Electronic Technology curricula both available. Assoc. degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept., Feb. Dorms, campus. High school graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE Department C, Valparaiso, Indiana



ETI Engineering Technician A.S. Degree—2 Years Electronics Engineer B.S. Degree Evening Courses Available

ELECTRONIC TECHNICAL INSTITUTE 970 W. Manchester Ave., Inglewood, Calif. 4863 El Cajon Blvd., San Diego, Calif.

B. S. Degree in 36 months

Small professionally-oriented college. Four-quarter year permits completion of B.S. Degree in three years. Summer attendance optional. *Engineering:* Electrical (electronics or power option), Mechanical, Civil, Chemical, Aeronautical. *Business Administration:* General Business, Accounting, Motor Transportation Administration. One-year Drafting-Design Certificate program. Outstanding placement of graduates. Founded 1884. Rich heritage. Excellent faculty. Small classes, 200-acre campus. Well equipped labs. New library. Residence halls. Modest costs. Enter Sept., Jan., March, June. For Catalog and View Book, write J. G. McCarthy, Director of Admissions.

TRI-STATE COLLEGE 2484 College Avenue • Angola, Indiana

LEARN TECHNICAL WRITING

Personal attention by the Professional Technical Writers at CCS can prepare you for an exciting career, through home study. Electronically oriented Technical Writers earn \$10,000 per year . . . plus.

We offer you a free lesson without obligation

CENTURY CORRESPONDENCE SCHOOLS 1186 Fay Ave., Dept. L, Largo, Fla.

FOR AN ELECTRONICS CAREER
Write For Free Catalog RE
WEEKLY TUITION

MICROWAVE TECHNIQUES — TV INDUSTRIAL ELECTRONICS COMPUTERS—RADIO TRANS-MITTERS—RADAR—TRANSISTORS

PHILADELPHIA WIRELESS TECHNICAL INSTITUTE
1533 Pine Street Philadelphia 2, Pa.
Founded in 1908 • A Non-Profit Corp.

SCIENCE/ENGINEERING

Educationally-strong college courses in the fastest growing professional fields of Physics, Mathematics, Engineering (Nuclear, Electronic, Electrical); including Engineering Technology (Nuclear, Electronic). Optional four-quarter, all-year schedule permits completion of regular 4-year B.S. degree courses in three years; and, A.S. degree courses in two years. Electronic Engineering includes computer and space communication systems; and, laser/infrared engineering. Fall Quarter enrollments limited. Write now to Director of Admissions, for Catalog E-10.

NORTHRIDGE COLLEGE of SCIENCE & ENGINEERING

Northridge, California 91325


Learn Electronics for your SPACE-AGE EDUCATION at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech, in sunny Southern California.

COLLEGE OF ENGINEERING. Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

A & P SCHOOL. Practical experience on real aircraft. One-year course prepares you for F.A.A. A&P certificate. WRITE TODAY FOR CATALOG.

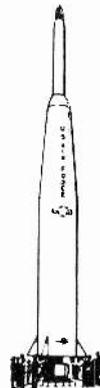NORTHROP INSTITUTE OF TECHNOLOGY 1199 W. Arbor Vitae, Inglewood, Calif.



when it's time to think of college you should read this **FREE CAREER BOOKLET** about electronics at **MISOE**

MILWAUKEE MS-220 SCHOOL OF ENGINEERING
Dept. RE-864, 1025 N. Milwaukee Street
Milwaukee, Wisconsin 53201
Tell me about an engineering career through residence study in:
 Electrical fields Mechanical fields
Name.....Age.....
Address.....
City, State.....

MILWAUKEE MS-220 SCHOOL OF ENGINEERING
Dept. RE-864, 1025 N. Milwaukee Street
Milwaukee, Wisconsin 53201
Tell me about an engineering career through residence study in:
 Electrical fields Mechanical fields
Name.....Age.....
Address.....
City, State.....

new Books

ORGAN BUILDERS MANUAL, by Robert L. Eby. Artisan Organs, 2476 N. Lake Ave., Altadena, Calif. 8 1/2 x 11 in., 250 pp. Paper, \$5

Based on the author's Artisan organ, the book contains much information valuable to organ builders in general.

BASIC ELECTRONICS, (2nd edition), by Royce G. Kloeffler, Maurice W. Horrell and Lee E. Hargrave, Jr. John Wiley & Sons, 605 Third Ave., New York 16, N. Y. 5 3/4 x 9 in., 643 pp. Cloth, \$11.

An intermediate level text that covers transistors, tubes and circuits. Math is held to a minimum.

HANDBOOK OF TRANSISTOR CIRCUITS, by Allan Lytel. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5 1/2 x 8 1/2 in., 224 pp. Paper, \$4.95.

A compilation of industrial and experimental circuits using SCR's, Zener diodes, tunnel diodes and other semiconductors. Each is accompanied by parts list and descriptive writeup.

RELIABLE ELECTRICAL CONNECTIONS (Vol. 1). Space Publications, Inc., Times Bldg., 221 Holmes Ave., Huntsville, Ala. 5 1/2 x 7 3/4 in., 68 pp. Paper, \$2.


Covers handling of wires and components, soldering, protecting connections, lacing, problems of printed circuitry. With appendix and index.

CITIZENS BAND RADIO HANDBOOK, by David E. Hicks. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5 1/2 x 8 1/2 in., 192 pp. Paper, \$2.95.

Information for the kit-builder, technician and operator. Covers typical equipment and latest regulations. Many schematics.

MASERS AND LASERS, How They Work, What They Do, by M. Brotherton. McGraw-Hill Book Co., 330 W. 42 St., New York, N.Y. 10036. 5 1/2 x 8 1/4 in., 207 pp. Cloth, \$8.50

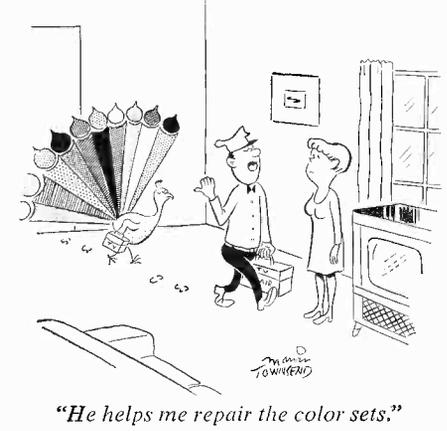The first six chapters are devoted to an introduction and explanation of the principles underlying maser action. Two chapters on the microwave maser follow, then eight on the laser. Elementary. END



"He helps me repair the color sets."

RADIO-ELECTRONICS

BRAND NEW UNITED'S FIRST QUALITY TUBES DISCOUNTS up to 80% OFF GUARANTEED ONE FULL YEAR! NOT USED! NO PULLS! WHY PAY MORE?

Tube	Price	Tube	Price	Tube	Price	Tube	Price	Tube	Price	Tube	Price	Tube	Price	Tube	Price
0A2	.80	3D24	.79	6A05	.52	6C08	.90	6G06	.92	7HG8	1.67	12D4	.67	17H3	.95
0A3	.90	3GK6	.97	6A06	.69	6C08R	.58	6G08	.92	7J7	1.50	12D8S	1.05	17J28	1.98
0A4G	1.35	3HS8	1.29	6A07	1.55	6C08S	.58	6G08S	.92	7L7	1.45	12DL8	.85	18A5	1.54
0B2	.80	3Q4	.79	6A08	1.20	6C08T	.67	6G25	.94	7N7	1.25	12DQ6	1.02	18FW6	.47
0B3	1.20	3S4	.73	6A08S	.84	6C08U	1.75	6HFS	2.99	7Q7	1.50	12DQ7	1.33	18FX6	.51
0C3	.75	3V4	.61	6A08R	2.19	6C08V	1.45	6HG8	1.65	7R7	1.15	12D7S	.82	18FY6	.48
0D3	.80	4AU6	.95	6A11	1.64	6C08W	1.75	6HJ8	1.25	7S7	1.60	12DT5	.74	19AU4	.85
0G3	2.75	4AV6	1.15	6A15	1.64	6C08X	1.52	6HJ8R	1.25	7T7	1.45	12DT7	.77	19B6	1.55
0Y4	1.20	4B6S	.85	6A15S	1.00	6C08Y	1.52	6HJ8S	1.25	7W7	1.45	12DT8	.76	19E8A	.77
0Z4	.77	4BC5	.95	6A15T	2.79	6C08Z	.88	6J4	2.95	7X7	1.25	12D9W	1.20	19H8V	1.44
1A3	.70	4B8	1.61	6A19	1.20	6C09	1.75	6J4WA	3.60	7Y7	1.95	12D9S	1.77	19W8S	1.20
1R5	.75	4BL9	.90	6A19S	1.87	6C09S	1.40	6J6	.98	7Z4	.95	12D9W8	.87	19T8	.83
1AG	.70	4BNC	1.35	6A21	1.87	6C09T	1.40	6J6E	3.25	8A8	.93	12DZ6	.60	21EX6	1.47
1A7	1.05	4BQ7	.99	6A27	.47	6C09U	1.75	6J6E8	1.50	8A8W	.96	12E6	.99	21G6	1.92
1A7A	1.30	4BQ8	1.35	6A27S	.81	6C09V	1.75	6J8	.95	8A8WR	.96	12E6R	.38	25AK4	.66
1A74	1.75	4B8U	1.29	6A28	.83	6C09W	2.50	6J8T	1.65	8C07	.63	12E6S	.60	25AX4	.68
1AX2	.60	4BZ6	.95	6A28S	1.75	6D10	1.56	6J8T8	1.40	8C07S	.63	12E6T	.60	25BK5	1.35
1R3	.75	4C06	.95	6A28T	.88	6D10S	1.56	6K8	1.45	8C07T	.63	12E6U	.60	25C8A	.51
1CS	.70	4C06S	.95	6A28U	.85	6D10T	1.56	6K8S	1.45	8C07U	.63	12E6V	.60	25C8B	.51
1DN5	.53	4C06T	.59	6A28V	.39	6D10U	1.56	6K8T	1.45	8C07V	.63	12E6W	.60	25C8C	.51
1Q3	.70	4C06U	.59	6A28W	.39	6D10V	1.56	6K8T8	1.45	8C07W	.63	12E6X	.60	25C8D	.51
1Q4	.69	4D06	1.19	6A28X	.57	6D10W	1.56	6K8T8S	1.45	8C07X	.63	12E6Y	.60	25C8E	.51
1G6	.80	4DK6	.60	6A28Y	1.49	6D10X	1.56	6K8T8T	1.45	8C07Y	.63	12E6Z	.60	25C8F	.51
1H4S	.69	4DT6	.55	6A28Z	.92	6D10Y	1.56	6K8T8U	1.45	8C07Z	.63	12E6A	.60	25C8G	.51
1H5	1.00	4E7	.60	6A29	.92	6D10Z	1.56	6K8T8V	1.45	8C07A	.63	12E6B	.60	25C8H	.51
1H6	.70	4EM6	.70	6A29S	.64	6D10A	1.56	6K8T8W	1.45	8C07B	.63	12E6C	.60	25C8I	.51
1J3	.75	4E7S	1.19	6A29T	.73	6D10B	1.56	6K8T8X	1.45	8C07C	.63	12E6D	.60	25C8J	.51
1J5	.95	4GK5	.94	6A29U	.95	6D10C	1.56	6K8T8Y	1.45	8C07D	.63	12E6E	.60	25C8K	.51
1J6	.95	4GM6	.59	6A29V	.95	6D10D	1.56	6K8T8Z	1.45	8C07E	.63	12E6F	.60	25C8L	.51
1K3S	.75	4G6	1.49	6A29W	1.30	6D10E	1.56	6K8T8A	1.45	8C07F	.63	12E6G	.60	25C8M	.51
1L4	.64	4G6S	1.49	6A29X	1.30	6D10F	1.56	6K8T8B	1.45	8C07G	.63	12E6H	.60	25C8N	.51
1L4A	1.30	4HM6	.92	6A29Y	1.30	6D10G	1.56	6K8T8C	1.45	8C07H	.63	12E6I	.60	25C8O	.51
1L4S	1.30	4H6	.92	6A29Z	1.30	6D10H	1.56	6K8T8D	1.45	8C07I	.63	12E6J	.60	25C8P	.51
1L6A	1.45	4HT6	.99	6A29A	1.15	6D10I	1.56	6K8T8E	1.45	8C07J	.63	12E6K	.60	25C8Q	.51
1L8A	1.80	5AM8	.77	6A29B	.48	6D10J	1.56	6K8T8F	1.45	8C07K	.63	12E6L	.60	25C8R	.51
1L8S	1.25	5AM8S	.77	6A29C	.48	6D10K	1.56	6K8T8G	1.45	8C07L	.63	12E6M	.60	25C8S	.51
1L6C	1.80	5A0S	.82	6A29D	.48	6D10L	1.56	6K8T8H	1.45	8C07M	.63	12E6N	.60	25C8T	.51
1L6S	1.95	5A0S8	.82	6A29E	.48	6D10M	1.56	6K8T8J	1.45	8C07N	.63	12E6O	.60	25C8U	.51
1L8D	1.95	5A0S8S	1.90	6A29F	2.00	6D10N	1.56	6K8T8K	1.45	8C07O	.63	12E6P	.60	25C8V	.51
1L8F	1.95	5B7	1.10	6A29G	2.00	6D10O	1.56	6K8T8L	1.45	8C07P	.63	12E6Q	.60	25C8W	.51
1L8S	1.95	5B7S	1.10	6A29H	2.25	6D10P	1.56	6K8T8M	1.45	8C07Q	.63	12E6R	.60	25C8X	.51
1L8A	1.25	5B7T	.84	6A29I	1.25	6D10Q	1.56	6K8T8N	1.45	8C07R	.63	12E6S	.60	25C8Y	.51
1L8S	1.25	5B7T8	.84	6A29J	1.25	6D10R	1.56	6K8T8P	1.45	8C07S	.63	12E6T	.60	25C8Z	.51
1N5	1.20	5B8	.99	6A29K	1.25	6D10S	1.56	6K8T8Q	1.45	8C07T	.63	12E6U	.60	25C8A	.51
1Q5	.95	5B8S	1.29	6A29L	1.25	6D10T	1.56	6K8T8R	1.45	8C07U	.63	12E6V	.60	25C8B	.51
1R3	.75	5C8	.79	6A29M	.88	6D10U	1.56	6K8T8S	1.45	8C07V	.63	12E6W	.60	25C8C	.51
1R3S	.75	5C8S	.79	6A29N	.88	6D10V	1.56	6K8T8T	1.45	8C07W	.63	12E6X	.60	25C8D	.51
1S4	1.15	5C08	.82	6A29O	1.66	6D10W	1.56	6K8T8U	1.45	8C07X	.63	12E6Y	.60	25C8E	.51
1T4	.70	5D4	.84	6A29P	1.60	6D10X	1.56	6K8T8V	1.45	8C07Y	.63	12E6Z	.60	25C8F	.51
1T5	.80	5E8	.79	6A29Q	1.60	6D10Y	1.56	6K8T8W	1.45	8C07Z	.63	12E6A	.60	25C8G	.51
1U5	.63	5G6	.99	6A29R	1.60	6D10Z	1.56	6K8T8X	1.45	8C07A	.63	12E6B	.60	25C8H	.51
1V	1.05	5G6S	.99	6A29S	1.60	6D10A	1.56	6K8T8Y	1.45	8C07B	.63	12E6C	.60	25C8I	.51
1V2	.80	5HC7	1.49	6A29T	1.45	6D10B	1.56	6K8T8Z	1.45	8C07C	.63	12E6D	.60	25C8J	.51
1X2B	.80	5H6	.84	6A29U	1.45	6D10C	1.56	6K8T8A	1.45	8C07D	.63	12E6E	.60	25C8K	.51
2A3	1.15	5T8	.84	6A29V	1.45	6D10D	1.56	6K8T8B	1.45	8C07E	.63	12E6F	.60	25C8L	.51
2A3S	1.15	5T8S	.84	6A29W	1.45	6D10E	1.56	6K8T8C	1.45	8C07F	.63	12E6G	.60	25C8M	.51
2A6	1.10	5U8	.84	6A29X	1.45	6D10F	1.56	6K8T8D	1.45	8C07G	.63	12E6H	.60	25C8N	.51
2A7	1.50	5V3	1.59	6A29Y	1.45	6D10G	1.56	6K8T8E	1.45	8C07H	.63	12E6I	.60	25C8O	.51
2A7A	1.50	5V3S	1.59	6A29Z	1.45	6D10H	1.56	6K8T8F	1.45	8C07I	.63	12E6J	.60	25C8P	.51
2A74	.93	5V6	.55	6A29A	1.45	6D10I	1.56	6K8T8G	1.45	8C07J	.63	12E6K	.60	25C8Q	.51
2A74A	.93	5V6S	.55	6A29B	1.45	6D10J	1.56	6K8T8H	1.45	8C07K	.63	12E6L	.60	25C8R	.51
2A74S	.93	5V6S	.55	6A29C	1.45	6D10K	1.56	6K8T8J	1.45	8C07L	.63	12E6M	.60	25C8S	.51
2A82	1.25	5W4	.95	6A29D	1.45	6D10L	1.56	6K8T8K	1.45	8C07M	.63	12E6N	.60	25C8T	.51
2A82S	1.25	5W4S	.95	6A29E	1.45	6D10M	1.56	6K8T8L	1.45	8C07N	.63	12E6O	.60	25C8U	.51
2B3	.98	5X8	.90	6A29F	1.45	6D10N	1.56	6K8T8M	1.45	8C07O	.63	12E6P	.60	25C8V	.51
2B7	.70	5Y4	.90	6A29G	1.45	6D10O	1.56	6K8T8N	1.45	8C07P	.63	12E6Q	.60	25C8W	.51
2B7S	.70	5Y4S	.90	6A29H	1.45	6D10P	1.56	6K8T8P	1.45	8C07Q	.63	12E6R	.60	25C8X	.51
2B84	.95	5Z3	.45	6A29I	1.45	6D10Q	1.56	6K8T8Q	1.45	8C07R	.63	12E6S	.60	25C8Y	.51
2C5	.95	5Y4	1.10	6A29J	1.45	6D10R	1.56	6K8T8R	1.45	8C07S	.63	12E6T	.60	25C8Z	.51
2D21	.70	5Z3	.45	6A29K	1.45	6D10S	1.56	6K8T8S	1.45	8C07T	.63	12E6U	.60	25C8A	.51
2X2	.60	5Z4	1.40	6A29L	1.45	6D10T	1.56	6K8T8T	1.45	8C07U	.63	12E6V	.60	25C8B	.51
2X2A	1.30	6A3	2.50	6A29M	1.45	6D10U	1.56	6K8T8U	1.45	8C07V	.63	12E6W	.60	25C8C	.51
3A2	1.55	6A4	.80	6A29N	1.45	6D10V	1.56	6K8T8V	1.45	8C07W	.63	12E6X	.60	25C8D	.51
3A3	.74	6A6	1.00	6A29O	1.45	6D10W	1.56	6K8T8W	1.45	8C07X	.63	12E6Y	.60	25C8E	.51
3A4	1.10	6A7	2.25	6A29P	1.45	6D10X	1.56	6K8T8X	1.45	8C07Y	.63	12E6Z	.60	25C8F	.51
3A5	1.10	6A8	1.00	6A29Q	1.										

CLASSIFIED ADVERTISING ORDER FORM

Please refer to heading at top of classified section for complete data concerning terms, frequency discounts, closing dates, word count, etc.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .30 Non-Commercial Rate } = \$ _____
 { @ .55 Commercial Rate } = \$ _____

Total Enclosed \$ _____

Insert _____ time(s) Payment must accompany order unless placed through accredited advertising agency. 84

Starting with _____ issue


NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SIGNATURE _____

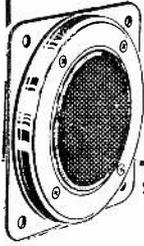MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011



HI-FI SPECIAL! ELECTROSTATIC TWEETER

MADE BY FAMOUS LORENZ—I.T.T.—FOR GRUNDIG—NEVER BEFORE OFFERED FOR SALE

BUY 2 FOR STEREO—4" SQ.

IT'S A NATURAL FOR THE HI-FI ENTHUSIASTS (Illustration resembles tweeters in stock)

\$1.49

EACH Includes Hookup **2 for 2.50**

SUBMINIATURE

1.95

3-TRANSISTOR

AMPLIFIER

- Only 3"x2"x3/4"
- Printed Circuit
- Wired
- W/Transistors

TESTED TRANSISTRON SCRs

PRV	AMP	AMP	5.5	2.5
50	1.00	1.25	1.50	1.50
100	1.50	1.75	2.00	2.00
150	1.75	2.00	2.25	2.25
200	2.00	2.25	2.50	2.50
250	2.25	2.50	2.75	2.75
300	2.50	2.75	3.00	3.00
350	2.75	3.00	3.25	3.25
400	3.00	3.25	3.50	3.50
450	3.25	3.50	3.75	3.75
500	3.50	3.75	4.00	4.00

DOUBLE BONUS
\$25

FREE WORTH OF
 • Transistors
 • Rectifiers
 • Condensers
 • Diodes
 • Knobs
 • Coils, etc.

PLUS FREE
CHOOSE ANY \$1 ITEM FREE

GET BOTH GIFTS FREE WITH EVERY \$10 ORDER

TESTED 10 WATT

ZENERS

\$1.49 EA.



<input type="checkbox"/>	42V
<input type="checkbox"/>	45V
<input type="checkbox"/>	50V
<input type="checkbox"/>	60V
<input type="checkbox"/>	70V
<input type="checkbox"/>	80V
<input type="checkbox"/>	90V
<input type="checkbox"/>	100V
<input type="checkbox"/>	110V
<input type="checkbox"/>	124V

WRITE FOR OTHER VOLTAGES

CD'ERS ATTENTION
 30 MC TRANSISTORS

TO-5 case, with built-in shield, 10 FOR \$1 like 2N247, untested

FACTORY TESTED SEMI-KON-DUCTORS

- 1-85W 2N1212 NPN SILICON, TO10 \$1
- 6 2N404 TYPE TRANSISTORS, rf, if, TO5 case... \$1
- 6 2N112 TYPE IF, OSC TRANSISTORS, TO22 Untested \$1
- 1 2N706 500MW, 300MC NPN PLANAR, TO18 \$1
- 3 TEXAS 20W TRANS'RS, 2N1038, heatsink, TO5 \$1
- 1 TRANSISTRON 85-W SILICON npn mesa, 2N424 \$1
- 4 G.E. 2N43 OUTPUT TRANSISTORS, TO5 case... \$1
- 3 2N1264 UHF TRANSISTORS, 300 MC TO 5 case... \$1
- 10 PNP SWITCHING TRANSISTORS, TO 5 case... \$1
- 1 2N964 EPITAXIAL MESA, 500 MC, PNP, TO-18 \$1
- TEXAS 20-WATT, TO5, heat sink stud, 2N1042 \$1
- 6 750 MA 400V EPOXY DIODES \$1
- 6 ZENER DIODES, upright styles, assorted \$1
- 3 2N243 750 MW NPN SILICON transistors, TO22 \$1
- 1 85W SILICON PWR TRANSR, npn, like 2N1212 \$1
- 2 TRANSISTRON 1N429 ZENER REFERENCES \$1
- 1 SILICON PLANARS: 2N497, 2N498, each \$1
- 4 SUBMINIATURE 2N131 TRANSISTORS, rf-if, pnp... \$1
- 4 CK721 TRANSISTORS in new aluminum case, pnp... \$1
- 10 NPN SWITCHING transistors, 2N440 equals \$1
- 2 CBS 35W PWR TRANSISTORS, 2N1434, pnp, stud... \$1
- 10 FAMOUS CK722 TRANSISTORS, pnp \$1
- 15 PNP TRANSISTORS, asst types and cases \$1

10¢ FOR OUR "SUMMER" BARGAIN CATALOG ON:
 Semiconductors Poly Paks Parts

- 15 CBS GERMANIUM DIODES, 1N34 equals \$1
- 15 NPN TRANSISTORS, asst types and cases \$1
- 2-2N341 NPN SILICON TRANSISTORS, 1 watt \$1
- 3 CBS 20-WATT TRANSISTORS, pnp, stud, 2N1320 \$1
- 1 3N35 TETRODE 150mc transistor, silicon \$1
- 5 SUN BATTERIES TO 1 1/2" sizes, lite sensitive \$1
- 3 2N255 PWR TRANSISTORS, or equal, TO3 case \$1
- 25 SEMI-KON-DUCTORS: transistors, diodes, rect. \$1
- 3 ONE WATT ZENERS, 6V, gold, axial \$1
- 5 GENERAL ELECTRIC 2N107 PNP transistors \$1
- 1 HOFFMAN SATELITE SILICON SUN CELL, 3/8x1" \$1
- 4 GENERAL ELECTRIC 2N170 RF NPN transistors \$1
- 15 UPRIGHT SILICON DIODES, worth \$40 \$1
- 2 'MESA' 4-WATT TRANSISTORS, npn, silicon, TO5 \$1
- 6 TRANSISTOR RADIO SET, osc-if-driver, p-p \$1
- 2-25-AMP SILICON STUD RECTIFIERS \$1
- 1-2N705 MESA 300 mc, 300 mw, pnp, TO18 \$1
- 20 WATT NPN SILICON MESA 2N1648 transistors \$1
- 2-500 MC PNP MESA TRANSISTORS: TO18 case \$1
- 6 TOP HAT RECTIFIERS, 750 mil, 400 volts \$1
- 1-SILICON NPN "PLANAR" 2N718, TO18 case \$1

POLY PAKS
 TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25%
 P.O. BOX 942R
 SO. LYNNFIELD, MASS.
 "PAK-KING" OF THE WORLD

WORLD'S MOST POPULAR \$1 PARTS PAKS

- 3 SUBMINIATURE MIKE TRANSFORMERS \$1
- 3 MOLDED COND., black beauty, mylar, vit-Q \$1
- 10 PHONO PLUG-N-JACK SETS, tuners-asm. \$1
- 3 SUBBOUNCER TR'STOR tr'sformer, input, output \$1
- 10 ELECTROLYTICS, FP & tubulars, to 500 mf. \$1
- 30 "TEXAS" PRECISION RESISTORS to 20W, 1% \$1
- 60 CERAMIC CONDENSERS, discs, npo's to .05mf \$1
- 4 TRANSISTOR TRANSFORMERS, asst, worth \$25 \$1
- 40 WORLD'S SMALLEST RESIST., 5% too, 1/10W \$1
- 40 SUBMINIATURE COND., to .05mf, ceram too \$1
- 3 'TINY' V. CONTROLS, 2/sw, 2K, .5 meg, 1 meg \$1
- 4 TRANSISTOR TRANSFORMERS, asst, worth \$25 \$1
- 1-INFRA-RED PHOTO DETECTOR TRANSDUCER \$1
- 1-INFRA-RED PARABOLIC REFLECTOR & FILTER \$1
- 30 PRECISION RESISTORS, 1/2, 1, 2W, 1% \$1
- 50 ONE WATTERS, resistors, asst values, 5% too \$1
- 60 TUBULAR CONDENSERS, to .5mf to 1KV \$1
- 40 DISC CONDENSERS, 27mfmf to .05mf to 1KV \$1
- 60 TUBE SOCKETS, receptacles, auto, plugs, etc. \$1
- 10 PANEL SWITCHES, rotary-micro-slide-power \$1
- 30 POWER RESISTORS, to 50W, to 24 Kohms \$1
- 50 MICA CAPACITORS, to .01mf, silvers too \$1
- 10 VOLUME CONTROLS to 1 meg, switch too \$1
- 50 RADIO & TV KNOBS, asst. colors, styles \$1
- 10 TRANSISTOR ELECTROLYTICS, 10 to 100mf. \$1
- \$25 RADIO-TV SURPRISE, wide variety \$1
- 50 COILS & CHOKES, rf-if, osc-peaking-etc. \$1
- 35 ALLEN BRADLEY & IRC TWO WATTERS \$1
- 100 ASST. HALF WATT RESISTORS, 5% too \$1
- 60 HI-Q RESISTORS, 1/2, 1, 2W to 1 meg, 5% too \$1
- 10 TANTALUM ELECTROLYTICS, worth \$15 \$1

150 WATT TRANSISTOR — \$1

TEXAS INSTR.—PNP—TO3—SWITCHING
SALE! SALE! SALE!
25 25 TRANSISTORS: audio switching, rf untested
 25 TOP HAT RECTIFIERS 750 mil untested
 25 EPOXY RECTIFIERS axial lead, 750 mil untested
 25 GERMANIUM DIODES 1N34, 1N48 untested...
\$1 per pak

SILICON POWER DIODE STUDS

Amps	Volts	Sale	Amps	Volts	Sale	Amps	Volts	Sale
6	50	1.25	200	1.60	50	200	2.95	
6	100	2.25	200	1.75	100	25	1.50	
6	200	3.75	200	1.95	100	50	1.80	
6	400	5.95	200	2.00	100	100	2.25	
6	600	8.95	200	1.25	250	25	1.50	
6	800	8.95	35	50	1.05	100	150	2.75
6	1000	9.95	35	100	1.25	250	25	1.50
12	50	1.10	150	1.50	250	50	4.95	
12	100	6.95	35	200	1.75	250	100	5.90
12	200	8.8	35	300	2.95	250	150	6.75
12	300	1.19	35	300	2.95	250	200	8.25
12	400	1.37	50	25	1.50	250	300	12.50
25	50	.99	50	50	1.95	250	400	19.95

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corp.	69-70
Arco Electronics, Inc. (Elmenco Div.)	Third Cover
Brooks Radio & TV Corp.	82-83, 91
Capitol Radio Engineering Institute, The	13
Castle TV Tuner Service, Inc.	64
CLASSIFIED	93
Cleveland Institute of Electronics	11
Cornell Electronics Co.	78
Coyne Electronics Institute	86
DeVry Technical Institute	7
Dymo Industries, Inc.	22
EICO Electronic Instrument Co., Inc.	10
Electronic Chemical Corp.	67
Electronic Measurements Corp. (EMC)	75
Fair Radio Sales	84
Gernsback Library, Inc.	80-81, 87
Grantham School of Electronics	15
Heald's Engineering College	78
Heath Co.	57
International Crystal Manufacturing Co., Inc.	24
Kinematrix, Inc.	76
Lafayette Radio Electronics Corp.	72
LTV/University (Div. of Ling-Temco-Vought, Inc.)	85
Mallory & Co., Inc., P. R.	9
MARKET CENTER	91
Mercury Electronics Corp.	61
Multicore Sales Corp.	72
National Radio Institute	18-21, 84
National Technical Schools	5
Philco-Techrep Division (Subsidiary of Ford Motor Co.)	74
Polypaks	92
Progressive "Edu-Kits", Inc.	73
Rad-Tel Tube Co.	94
RCA Citizens Band	59
RCA Electronic Components & Devices	Fourth Cover
RCA Institutes	3
Rotron Manufacturing Corp.	8
Sams & Co., Inc., Howard W.	23, 68
Sarkes Tarzian, Inc. (Tuner Service Div.)	66
Schober Organ Corp., The	77
SCHOOL DIRECTORY	89
Scott, Inc., H. H.	81
Senore	79
Sprague Products Co.	12
Superscope, Inc.	16-17
Sylvania (Subsidiary of General Telephone & Electronics)	65
Tarzian, Inc., Sarkes (Tuner Service Div.)	66
Texas Crystals (Div. of Whitehall Electronics Corp.)	76
Triad Distributor Div. (Div. of Litton Industries)	14
Triplet Electrical Instrument Co., The	Second Cover
United Radio Co.	90
University, LTV (Div. of Ling-Temco-Vought, Inc.)	85
Winegard Co.	64
MARKET CENTER	91
Brooks Radio & TV Corp.	
Editors and Engineers, Ltd.	
Edmund Scientific Co.	
Oelrich Publications	
Relco	
Stereo-Parti	
Tab	
Transistors Unlimited Co.	
Valley TV Tuner Service	
Warren Electronic Components	
SCHOOL DIRECTORY	89
American Institute of Engineering & Technology	
Century Correspondence Schools	
Electronic Technical Institute	
Indiana Home Study Institute, The (Eastern Div.)	
Milwaukee School of Engineering	
Northridge College of Science & Engineering	
Northrop Institute of Technology	
Philadelphia Wireless Technical Institute	
Tri-State College	
Valparaiso Technical Institute	

Classified Ads

COMMERCIAL RATE (for firms or individuals offering commercial products or services): 55¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for October issue must reach us before August 14th.

WORD COUNT: Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8x10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

Audio—Hi-Fi

SAVE 30-60% Stereo music on tape. Free bargain, catalog / blank tape / recorders / Norelco speakers. **SAXITONE**, 1776 Columbia Road, Washington D.C.

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. **CARSTON**, 125-R East 88, N.Y.C. 10028.

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. **STEREO-PARTI**, 1616 Terrace Way, Santa Rosa, Calif.

PHONOGRAPH NEEDLE discount sale. Write for Free brochure. **MOORE'S**, 19 Goldsboro, Easton, Md.

HI FI, Ham Equipment, Discount Catalog. **MENDOTA CAMERA SHOP**, Mendota, Minn.

TAPE recorders, Hi-Fi components, Sleep-learning equipment, Tapes, Unusual values. Free catalog. **DRESSNER**, 1523 Jericho Turnpike, New Hyde Park 5, N.Y.

WINDSOR TAPE CLUB members HEAR BEFORE THEY BUY. Free "samplers" of new releases. Save on tape purchases—all major labels. Free Brochure—**WINDSOR TAPE CLUB**, Dept. A, Windsor, Calif.

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. **HI FIDELITY CENTER**, 1797 (R) 1st Ave., New York, N. Y. 10028.

EDUCATION/ INSTRUCTION

SLEEP LEARNING. Hypnotism! Tapes, records, books, equipment. Details, strange catalog FREE. **RESEARCH ASSOCIATION**, Box 24-RD, Olympia, Wash.

HIGHLY—effective home study review for FCC commercial phone exams. Free literature! **COOK'S SCHOOL OF ELECTRONICS**, Craigmont, Idaho 83523.

FCC LICENSE in 6 weeks. First Class Radio Telephone. Results Guaranteed. **ELKINS RADIO SCHOOL**, 2603E Inwood, Dallas, Tex.

PHOTOGRAPHY FOR PLEASURE or profit. Learn at home. Practical basic training. Long established school. Free book. **AMERICAN SCHOOL OF PHOTOGRAPHY**, 835 Diversey Parkway, Dept. 187C, Chicago, Ill. 60614.

BUSINESS AIDS

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books, invoices, job tickets, phone message books, statements and file systems. **OELRICH PUBLICATIONS**, 6556 W. Higgins, Chicago, Ill. 60656.

1,000 Business Cards, "Raised Letters" \$3.75 postpaid. Samples. **ROUTH**, RE8, 2633 Randleman, Greensboro, N.C. 27406.

Electronics

RADIO & TV TUBES 33¢. Free List. **CORNELL**, 4217-E University, San Diego, Calif. 92105.

BEFORE You Buy Receiving Tubes, Test Equipment, Hi-Fi Components, Kits, Parts, etc. . . send for your Giant Free Zalytron Current Catalog, featuring all STANDARD BRAND TUBES all Brand New Premium Individually Boxed, One Year Guarantee—all at BIGGEST DISCOUNTS in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. WHY PAY MORE? **ZALYTRON TUBE CORP.**, 469R Jericho Turnpike, Mineola, N. Y.

TRANSISTORIZED Treasure Detectors Find buried gold, silver, coins. \$19.95 up. Kits available. Free catalog. **RELCO-A25**, Box 10563, Houston 18, Texas.

PRINTED CIRCUIT BOARDS. Hams, Experimenters. Catalog 10¢. **P/M ELECTRONICS**, Box 6288, Seattle, Wash. 98188.

TRANSISTOR TELEVISION TRANSLATORS. Re broadcast 25 miles, meets F.C.C. specifications. Battery powered. **KEITH ANDERSON COMPANY**, Piedmont, So. Dak.

7" TV TEST TUBE—\$6.99. Tubes 6146—\$2.95: 6211 (12AU7 equiv.) 39¢, 3 for \$1. Germanium diodes, tested, equiv. 1N34, 1N60 etc., 30 for \$1. Tophat silicon rectifiers, 750MA—1000 PIV 75¢. Transistors, tubes, resistors, condensers, etc., bargain priced. Free catalog. **ARCTURUS ELECTRONICS**, Dept. RE, 502-22nd St., Union City, N. J. 07087.

DIAGRAMS FOR REPAIRING RADIOS \$1.00. Television \$2.50. Give make, model. **DIAGRAM SERVICE**, Box 1151 RE, Manchester, Conn.

IGNITION! Transistor, Coil, Ballast \$7.50. Free Parts List. **TRANSFIRE**, Carlisle 20, Mass.

TRANS-NITION Electronic Ignition parts kit, Negative ground \$20. Coil, Manual SPECIAL \$8.50 Manual \$2. **ANDERSON ENGINEERING**, Wrentham, Mass.

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2. **RELCO**, Box 10563, Houston 18, Tex.

TRANSISTORS, SCR's, diodes, nickel-cadmium batteries, meters, crystals, components. Quality guaranteed. Send 10¢ for catalog. **ELECTRONIC COMPONENTS CO.** P.O. Box 2902B, Baton Rouge, La. 70821.

TV CAMERAS, transmitters, converters, etc. Lowest Factory prices. Catalog 10¢. **VANGUARD**, 190-48-99th Ave., Hollis, N.Y. 11423.

SEMICONDUCTORS, miniature electronic components, surplus bargains—free catalog. **ELECTRONIC CONTROL DESIGN COMPANY**—P.O. Box 1432A, Plainfield, N.J. 07061.

GOVERNMENT SURPLUS JEEPS—\$62.50, Voltmeters—\$1.05, Transmitters—\$6.18, Oscilloscopes, Walkie-Talkies, Multimeters. Typical Surplus Prices. Exciting Details Free. Write: **ENTERPRISES**, Box 402-F19, Jamaica 30, N.Y.

METER PROTECTOR, will protect the meter of your multi-tester permanently from accidental overloads due to the selector switch set on wrong position for voltage encountered, protector does not wear out, will not affect the accuracy of multi-tester, with this protector it

will become impossible to bend the pointer, or burn out the meter, you need this protection as you need the volt ohm meter itself, install yourself in few minutes, satisfaction guaranteed or money refunded, \$3.95 PP. **JAMES ELECTRONICS**, 8 W. Main Street, Du Quoin, Ill. 62832.

JAPANESE MERCHANDISE from Radio to Camera. Any inquiries answered. Catalog, and information \$1.00. **TOMIO UENO**, No. 538 Shibamatacho Katushikaku, Tokyo, Japan.

F.M. TUNERS. Single tube units 88-108 mcs. Brand new less tube. Die cast unit-pulley/string drive as used by Admiral-RCA in recent models. Output 10.7 mcs I.F. can be used for series or parallel heaters. 130 volts. B plus. Excellent for general replacement or construction. With instructions. Price only \$5.00 post paid. NO COD. **SELVEY ELECTRONICS**, 2409 Main Street, Evanston, Ill.

BRAND NEW 8YP4 Test Tube—\$17.95. "A must for every serviceman". (RADIO-ELECTRONICS, January, 1964 issue, Page 32.) Send check or money order for immediate delivery to: **SAMSON KINESCOPE**, Inc. 250 No. Goodman Street, Rochester, N.Y. 14607.

PROFESSIONAL ELECTRONICS PROJECTS—Organs, Timers, Computers, etc.—\$1 up. Catalog free. **PARKS**, Box 1665, Seattle, Wash. 98125.

FREE ELECTRONICS CATALOG. Tremendous bargains. **ELECTROLABS**, Department C-226G, Hewlett, N.Y. 11557.

General

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. **OELRICH PUBLICATIONS**, 6556 W. Higgins, Chicago, Ill. 60656.

Canadians

CANADIANS Have you seen ELECTRON, Canada's own Service and Hobby magazine? Subscription \$3.50. **ELECTRON**, Box 796, Montreal, Canada.

WANTED

QUICK CASH... for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! **BARRY**, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000.

PHOTOGRAPHS and TRANSPARENCIES wanted — to \$500.00 each. Valuable information — Free. Write **PICTURE**, Box 74607, Hollywood, 90004.

G-R, H-P, L&N, etc. Special tubes, manuals, military electronics. **ENGINEERING ASSOCIATES**, 434 Patterson Road, Dayton 19, Ohio.

SERVICES

TRANSISTORIZED products dealers catalog, \$1. **INTERMARKET**, CPO 1717, Tokyo, Japan.

SPEAKER RECONING. Satisfaction Guaranteed. **C & M RECONO CO.**, 18 E. Trenton Ave., Morrisville, Pa.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. **HAZELTON INSTRUMENT CO.**, 128 Liberty St., New York, N.Y.

INVENTORS. We will develop, help sell your idea or invention, patented or unpatented. Our national manufacturer clients are urgently seeking new items for outright cash sale or royalties. Financial assistance available. 10 years proven performance. For free information, write Dept. 53, **WALL STREET INVENTION BROKERAGE**, 79 Wall Street, New York, N. Y. 10005.

TV TUNERS Rebuilt and Aligned per manufacturer specification. Only \$9.50. Any Make UHF or VHF. We ship COD Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. **JW ELECTRONICS**, Box D, Bloomington, Ind.

METERS—MULTIMETERS REPAIRED and calibrated. **BIGELOW ELECTRONICS**, Box 71-B, Bluffton, Ohio.

MISCELLANEOUS

HIGH WEEKLY EARNINGS! Address-mail letters featuring real merchandise. Get \$10 with every order—keep \$8 profit. Supplies furnished. Free particulars. **MODERN MERCHANDISING**, Box 357, Oceanside, N.Y.

RAD-TEL'S
AMAZING OFFER...
YOUR CHOICE

IB3-IG3-IK3-IJ3

FREE!

HURRY OFFER EXPIRES
OCTOBER 31, 1964

RAD-TEL'S QUALITY
BRAND NEW TUBES

ONE YEAR GUARANTEE

Rad-Tel will replace any tube that does not give efficient performance for 1 year from date of purchase.

ONE TUBE FREE
IB3-IG3-IK3-IJ3

with the purchase of every 10 Rad-Tel Quality
BRAND NEW TUBES

up to **75% OFF***
Manufacturers Suggested List Price
500 TYPES IN STOCK



EACH TUBE INDIVIDUALLY & ATTRACTIVELY
BOXED & BRANDED RAD-TEL

RAD-TEL TUBE CO. NOT AFFILIATED WITH ANY
OTHER MAIL ORDER TUBE COMPANY

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	0Z4	.79	—	5AQ5	.54	—	6AX5	.74	—	6DA4	.68	—	6S7GT	.94	—	12AL8	.95
—	1AX2	.62	—	5AT8	.83	—	6BA6	.50	—	6DE6	.61	—	6T4	.99	—	12AQ5	.60
—	1B3	.79	—	5BK7	.86	—	6BC5	.61	—	6DG6	.62	—	6T8	.85	—	12AT6	.50
—	1DN5	.55	—	5BQ7	1.01	—	6BC8	1.04	—	6DJ8	1.21	—	6U8	.83	—	12AT7	.76
—	1G3	.79	—	5BR8	.83	—	6BE6	.55	—	6DK6	.59	—	6V6GT	.54	—	12AU6	.51
—	1J3	.79	—	5CG8	.81	—	6BF5	.90	—	6DN6	1.55	—	6W4	.61	—	12AU7	.61
—	1K3	.79	—	5CL8	.76	—	6BF6	.44	—	6DQ6	1.10	—	6W6	.71	—	12AV6	.41
—	1R5	.77	—	5CQ8	.84	—	6BG6	1.70	—	6DT5	.81	—	6X4	.41	—	12AV7	.82
—	1S5	.75	—	5EA8	.80	—	6BH8	.98	—	6DT6	.53	—	6X8	.80	—	12AX4	.67
—	1T4	.72	—	5EU8	.80	—	6BJ6	.65	—	6DT8	.94	—	7A8	.68	—	12AX7	.63
—	1U5	.65	—	5J6	.72	—	6BJ7	.79	—	6EA8	.79	—	7AU7	.65	—	12AY7	1.44
—	1X2B	.82	—	5T8	.86	—	6BK7	.85	—	6EB5	.73	—	7EY6	.75	—	12AZ7	.86
—	2AF4	.96	—	5U4	.60	—	6BL7	1.09	—	6EB8	.94	—	7Y4	.69	—	12B4	.68
—	3AL5	.46	—	5U8	.84	—	6BN6	.74	—	6EM5	.77	—	8AU8	.90	—	12BD6	.50
—	3AU6	.54	—	5V6	.56	—	6BQ6	1.12	—	6EM7	.82	—	8AW8	.93	—	12BE6	.53
—	3AV6	.42	—	5X8	.82	—	6BQ7	1.00	—	6EUB	.79	—	8BQ5	.60	—	12BF6	.60
—	3BC5	.63	—	5Y3	.46	—	6BU8	.70	—	6EV5	.75	—	8CG7	.63	—	12BH7	.77
—	3BN6	.75	—	6AB4	.46	—	6BX7	1.11	—	6EW6	.57	—	8CM7	.70	—	12BK5	1.00
—	3BU8	.78	—	6AC7	.96	—	6BZ6	.55	—	6EY6	.75	—	8CN7	.97	—	12BL6	.56
—	3BY6	.58	—	6AF4	1.01	—	6BZ7	1.03	—	6FG7	.69	—	8CS7	.74	—	12BQ6	1.16
—	3BZ6	.56	—	6AG5	.70	—	6C4	.45	—	6FV8	.79	—	8EB8	.94	—	12BR7	.74
—	3CB6	.56	—	6AH4	.81	—	6CB6	.55	—	6GH8	.80	—	8F7	.56	—	12BV7	.76
—	3CS6	.58	—	6AH6	1.10	—	6CD6	1.51	—	6GK5	.61	—	9CL8	.75	—	12BY7	.77
—	3DG4	.85	—	6AK5	.95	—	6CG7	.61	—	6GK6	.79	—	11CY7	.75	—	12BZ7	.86
—	3DK6	.60	—	6AL5	.47	—	6CG8	.80	—	6GN8	.94	—	12A4	.60	—	12CN5	.56
—	3DT6	.54	—	6AM8	.78	—	6CL8	.79	—	6H6	.58	—	12AB5	.60	—	12CR6	.67
—	3GK5	.99	—	6AQ5	.53	—	6CM7	.69	—	6J5GT	.51	—	12AC6	.55	—	12CU5	.58
—	3Q4	.63	—	6AS5	.60	—	6CN7	.70	—	6J6	.71	—	12AD6	.57	—	12CV6	1.06
—	3S4	.75	—	6AT6	.45	—	6CQ8	.92	—	6K6	.63	—	12AE6	.50	—	12CX6	.54
—	3V4	.63	—	6AT8	.86	—	6CR6	.60	—	6S4	.52	—	12AE7	.94	—	12D4	.69
—	4BQ7	1.01	—	6AU4	.85	—	6CS6	.57	—	6SA7GT	.99	—	12AF3	.73	—	12DE8	.83
—	4CS6	.61	—	6AU6	.52	—	6CS7	.69	—	6SH7	1.02	—	12AF6	.67	—	12DL8	.88
—	4DT6	.55	—	6AU8	.87	—	6CU5	.58	—	6SJ7	.88	—	12AJ6	.62	—	12DQ6	1.04
—	4GM6	.60	—	6AV6	.41	—	6CU6	1.08	—	6SK7GT	.95	—	12AL5	.47	—	12DS7	.84
—	5AM8	.79	—	6AW8	.90	—	6CY5	.70	—	6SL7GT	.84	—			—		
—	5AN8	.90	—	6AX4	.66	—	6CY7	.71	—	6SN7	.65	—			—		

OUR
16th
YEAR

ORDER TYPES NOT LISTED

 **CHEATER CORD** Easy to work on set while panel is off.
 6 ft., No. 154 **29¢ ea.** Lots of 3—**25¢ ea.**

TUBE SUBSTITUTION BOOK

- Over 11,000 direct tube substitutes
- Only all-inclusive directory of electron tube equivalents:
 - For USA electron tubes
 - Substitutes for foreign tubes
 - Picture tubes, newer models
 - Picture tubes, older models
 - transistor replacements
 - Army-Navy, V.T. substitutes

\$1.25 No. 193

RAD-TEL TUBE CO. TV, RADIO AND HI-FI
 DEPT. RE 55 CHAMBERS STREET, NEWARK, NEW JERSEY 07105

TERMS: 25% deposit must accompany all orders, balance C.O.D. Orders under \$5 add \$1 handling charge plus postage. Orders over \$5, plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. No C.O.D.'s outside continental U.S.A.

FREE! Send For New Tube & Parts Catalog
 Send For Trouble Shooting Guide

Fast, Dependable service — Selling direct by mail for over 16 years

RAD-TEL Tube Co. Total Tubes \$ _____
 Dept. RE Total Part(s) \$ _____
 55 Chambers Street Postage \$ _____
 Newark, New Jersey 07105 Grand Total \$ _____

ENCLOSED IS \$ _____ Please rush order.


SEND: _____ TUBE SUBSTITUTION BOOK, No. 193 @ 1.25 EACH
 _____ Cheater Cord 29c ea. Lots of 3 - 25c ea. #154

Orders under \$5.00 - Add \$1.00 handling charge - plus postage.

FREE! Send FREE Tube and Parts Catalog
 Send FREE Trouble Shooting Guide

NAME _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____

Quality is no gamble!

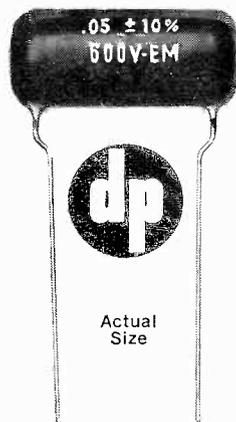

when you specify **ELMENCO** dipped Mylar* paper

Every time you make a call... service a circuit... change a component — you bet on the parts used. Make sure the odds are in your favor with miniaturized Elmenco Dipped Mylar-Paper (DP) capacitors. Over 100 million are in use now, because Elmenco DP capacitors give missile quality at commercial cost. Whether for radio-TV repairs, or critical industrial circuitry, reliable, dependable, rugged Elmenco capacitors eliminate profit-killing callbacks and customer complaints. Elmenco DP capacitors operate at 125°C without derating, are completely moisture proof, and are up to 50% smaller than comparable types. You can substitute values in a capacitor, but never virtues. Ask for Elmenco, and be sure you get it. Elmenco DP capacitors are available from stock only at authorized ARCO distributors throughout the U.S.A.

*Reg. Du Pont Trademark




ARCO
electronics inc.

ARCO'S RESERVE WAREHOUSES

You can get your Elmenco (DP) capacitors in any quantity within 24 hours from coast to coast. They're stocked in depth at Arco's reserve warehouses serving authorized Arco distributors throughout the nation. Call your Arco distributor today!

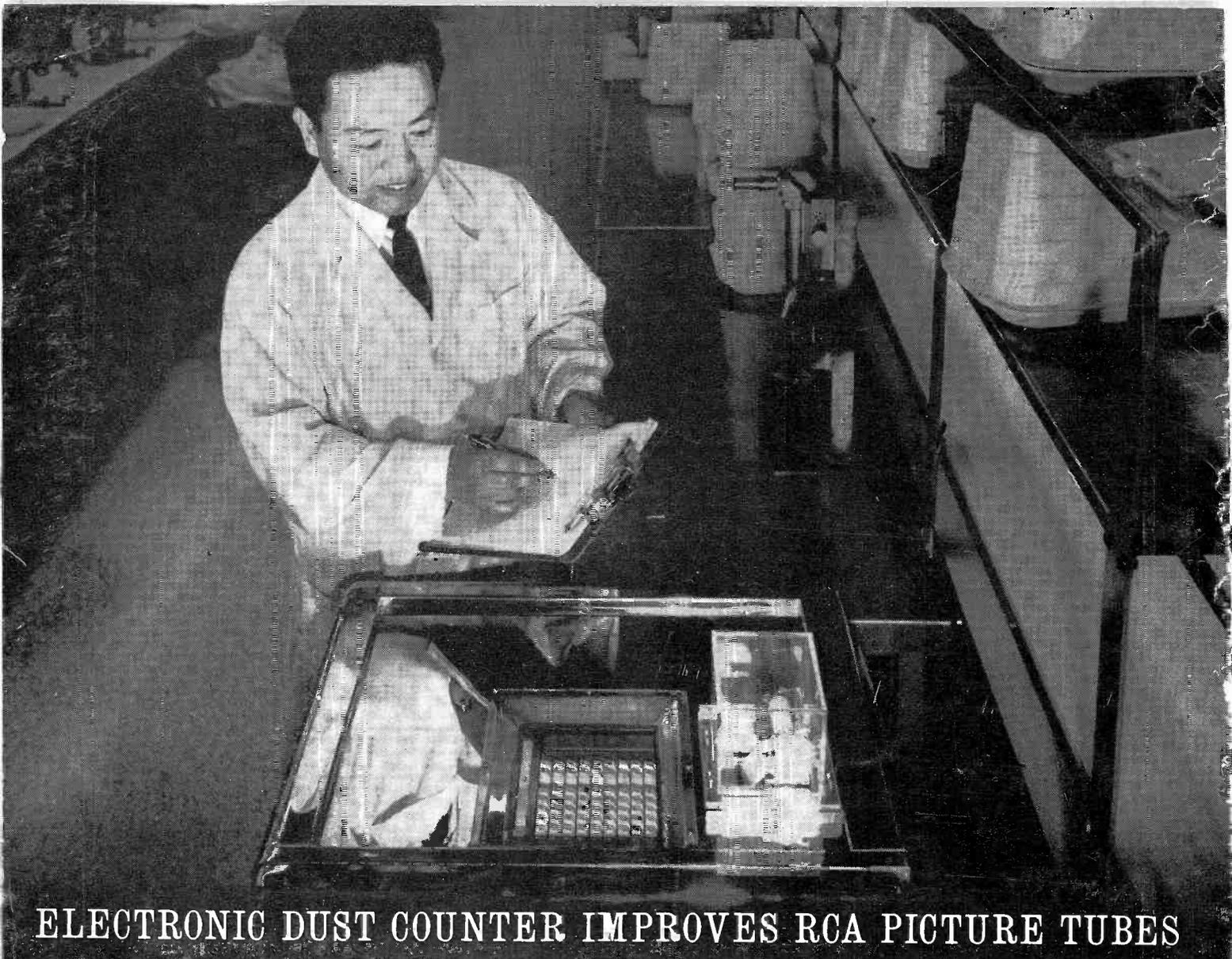Community Drive, Great Neck, N.Y. ☐ 516 HU 7-0500
Branches: Dallas 7 ☐ Los Angeles 35



ELECTRONIC DUST COUNTER IMPROVES RCA PICTURE TUBES

Strict environmental control extends electron gun life and performance

Even the smallest particle of dust can affect the life and precision performance of an electron gun in a television picture tube. In order to assure ultra-clean conditions for assembling guns that go into Silverama® Picture Tubes, RCA designed and built a space-age white room in its Marion, Indiana, plant.

Air in the white room is controlled by an electrostatic precipitator-type air conditioner. Higher than normal air pressure is maintained in the white room so no outside air can enter. At the entrance, "sticky floor mats" remove dust from workers' shoes. Workers wear lint-free Dacron smocks, lint-free nylon gloves, and rubber finger cots.

Yet, in addition to these precautions, RCA continually monitors

the white room's dust count by means of the digital-dust counter shown in the photo above. The unit is so sensitive it counts all dust particles from 0.32 micron (a micron is about one 39-millionth of an inch) to 8 microns. Only when the "dust count" is below an acceptable level can electron guns be processed.

These exceptionally strict environmental controls are another reason why you can be sure of customer satisfaction when you install an RCA Silverama Picture Tube.

Silverama is made with an all-new electron gun, finest parts and materials, and a glass envelope that has been thoroughly cleaned and inspected prior to re-use.



Electron gun mounts are washed by ultra-sonic vibration in extra-pure water to remove microscopic particles.



Electron guns, after drying, are kept in covered racks as further assurance against dust contamination.

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics