

BUILD — Stereo headphone control center

RUGO GERNSBACK, Editor-in-chief

60c ■ NOV. 1967

Radio-Electronics

TELEVISION · SERVICING · HIGH FIDELITY

GERNSBACK
PUBLICATION

Service Hints On New Color TV Sets

Stepping Relays Unlimited


Build Dummy Load and RF Meter

Make Your Own Printed Circuits

**SPECIAL REPORT
TV SET
X-Ray Radiation**

A1068 645028WGN0032E0A5L
A R WAGNER
32 N EAST ST
YORK PA 17403

**BUILD
TREASURE FINDER**
(See page 32)

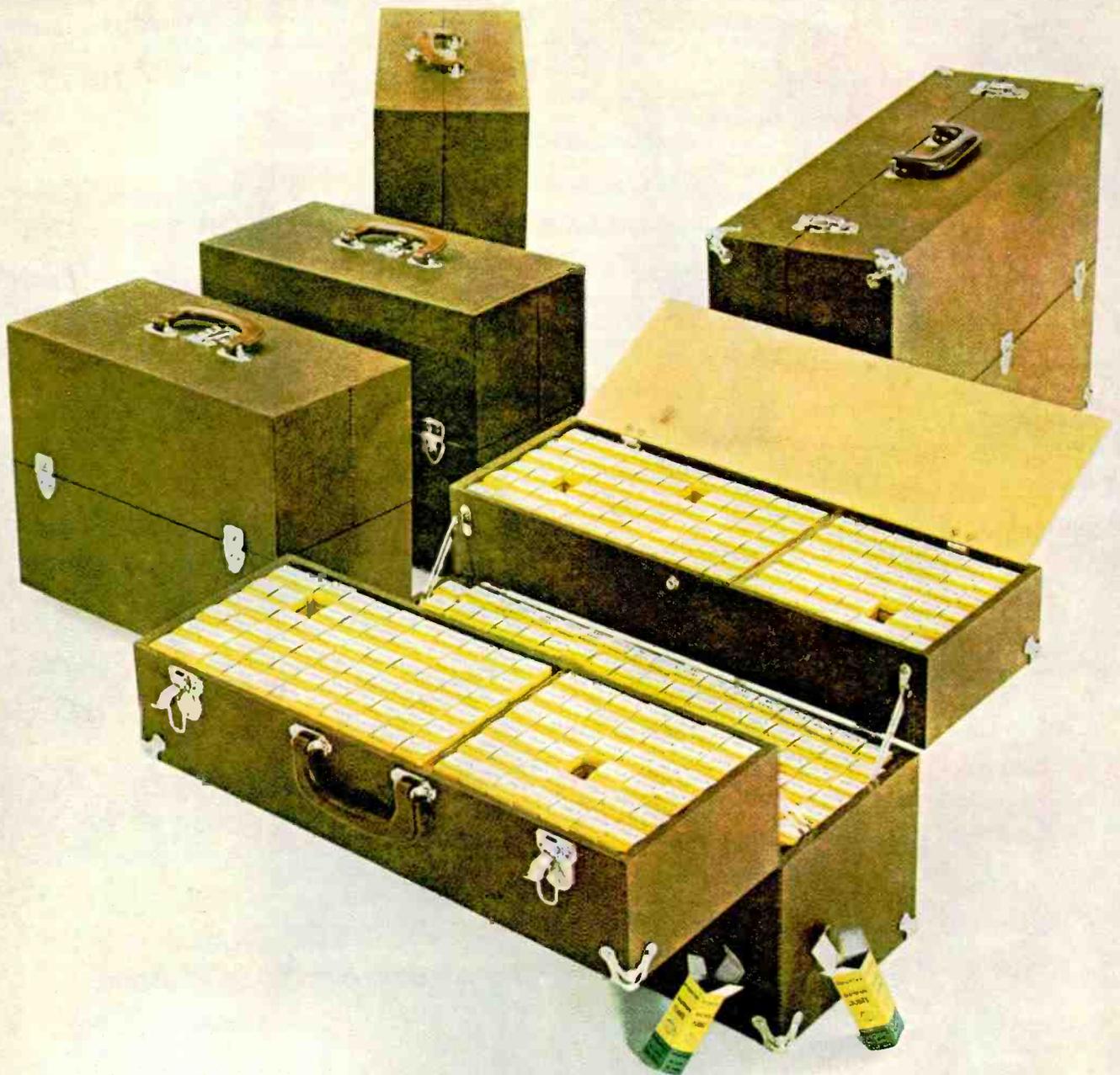


**One out of every five
professional servicemen
has switched to Amperex
TV replacement tubes**

It takes a lot of quality to change the buying habits of 20% of the most knowledgeable technicians in the business. These servicemen are following the pattern set by the leading TV manufacturers, who are designing more and more of their quality lines around tubes originated by Amperex. The Amperex line of popular types is expanding all the time. Look for the green and yellow cartons at your distributor's or write: Amperex Electronic Corp., Hicksville, L.I., N.Y. 11802.

Amperex

TOMORROW'S THINKING IN TODAY'S PRODUCTS



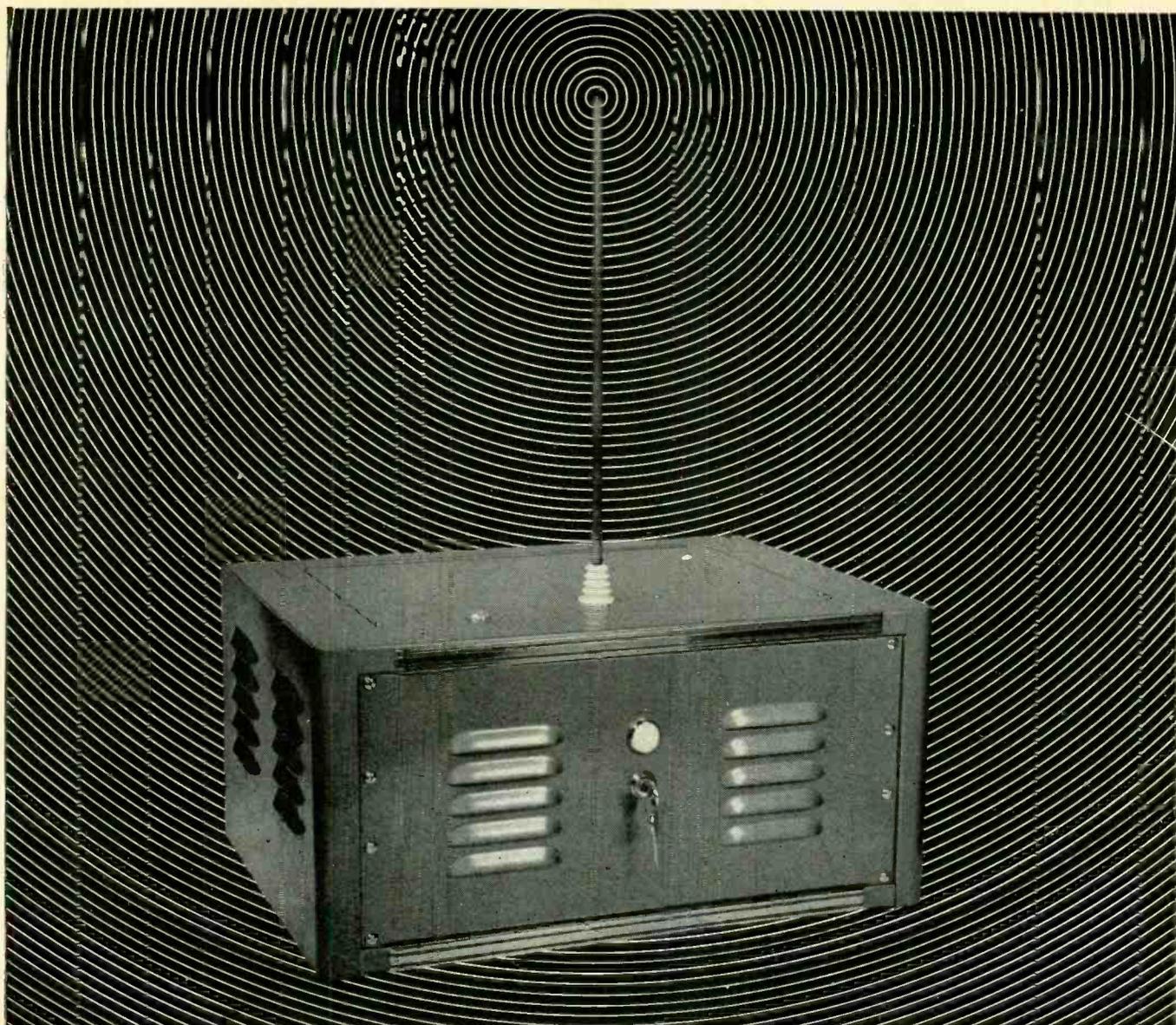

You are now in Radar Sentry Alarm's r.f. microwave field. Don't move a muscle!

This security system is so sensitive, it can be adjusted to detect the motion of your arm turning this page.

And if this Portable Model Unit were within 35 feet of you and you moved... people up to a half-mile away could hear the siren. Plus with optional equipment, it can detect fire... turn on lights... even notify police.

What does a burglar alarm have to do with you?

Just this: Radar Sentry is no ordinary alarm. It is the most modern and effective security system available. And it's also electronic.

That's why we need you. We need Dealers with technical knowledge. For the most successful Dealers for Radar Sentry Alarm are men who know electronics. This is a product that sells itself when demonstrated properly.

It's been proven time after time. In fact, many of the more than one thousand readers of electronics magazines who became Dealers in the past year — sold a system on their *first* demonstration.

And that's why we need men with technical knowledge and experience.

Men like you.

How about it?

Do you want to start a business of your own... or expand your present business with a product that in 8 years has become the world-wide leader in its field?

Do you want to earn up to \$5,000 a year in your spare time?

Do you want to earn \$20,000 and more full time?

We'll show you how.

O.K., now you can move.

Fill out the coupon and get complete Dealer/Distributor information... free.

Mail to: RADAR DEVICES MANUFACTURING CORP.
22003 Harper Ave., St. Clair Shores, Michigan 48080

RE-11



Please tell me how I can have a business of my own distributing Radar Sentry Alarm Systems. I understand there is no obligation.

Name _____

Address _____

City _____ State & Code _____

1

Grantham School of Electronics 11-67-RE
1505 N. Western Ave., Hollywood, Calif. 90027

Please send me free literature describing the Grantham course in Electronics Engineering Technology.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

Success in Electronics Comes as Naturally as 1-2-3 through Education

There they are — three big steps — three deliberate steps which lead directly to success in electronics. Your future is shaped by the moves *you* make — by the steps *you* take. Begin now with Step #1.

STEP #1 is a simple request for full information on the Grantham Associate Degree Program in Electronics. You take this step by filling out and mailing the coupon.

STEP #2 is earning your FCC first class radiotelephone LICENSE and radar endorsement. You complete this step in the first two semesters of the Grantham educational program (by correspondence or in residence).

STEP #3 is earning your ASEE DEGREE. This degree is conferred when you have earned credit for all five semesters of the Grantham curriculum.

Semesters 1 and 2, as mentioned above, are offered by correspondence or in residence.

Semester 3 is offered in residence, or students who have extensive *practical* experience in electronics may receive credit for this semester — credit based on that experience.

Semester 4 is offered by correspondence or in residence.

Semester 5 is offered in residence.

2



Accreditation, and G.I. Bill Approval

Grantham School of Electronics is *accredited* by the Accrediting Commission of the National Home Study Council, and is *approved* for both correspondence and resident training under the G.I. Bill. Just mail the coupon, or write or telephone us for full information without obligation.



Grantham School of Electronics

1505 N. Western Ave. 818 18th Street, N.W.
Hollywood, Calif. 90027 or Washington, D.C. 20006

Telephone:
(213) 469-7878

Telephone:
(202) 298-7460

RADIO-ELECTRONICS

3

Grantham School of Electronics

has conferred on

John Doe

the degree of

Associate in Science in Electronics Engineering

with all the rights and privileges thereunto appertaining. In witness thereof this diploma duly signed has been issued by the School Administration upon recommendation of the faculty at the School on this

first day of October, 1965.



D.J. Grantham
President
E. L. Witten
Acting Dean

Radio-Electronics

November 1967 VOL. XXXVIII No. 11
Over 55 Years of Electronics Publishing

4 Hugo Gernsback, 1884-1967 Fred Shunaman

SPECIAL REPORT

54 What You Should Know About X-Ray Radiation in TV Sets David Lachenbruch
No. You won't get fried

CONSTRUCTION PROJECTS

- 32 Build a Treasure Finder Charles D. Rakes
Sensitive, inexpensive metal locator
- 35 Build Stereo Headphone Control Center Peter E. Sutheim
It's the greatest... with bass boost too
- 42 Wooing the Tweeter J. T. McCormick
How low can you get with a small speaker?
- 50 Build Dummy Load and RF Meter E. F. Rice and Andrew J. Mueller
Nothing like putting 30 resistors in parallel

SERVICING

- 24 In the Shop... With Jack Jack Darr
Service Clinic
- 37 Servicing Hints on New Color-TV Sets Matthew Mandl
Things you should know to be a color-TV pro
- 52 Service Table-Model AM/FM Radios Homer Davidson
Some bread-and-butter procedures
- 72 Equipment Report: Sencore MU-140 Tube Tester

HAM BANDS


16 Incentive Licensing and Distinctive Call Signs
Right from the horse's mouth

GENERAL ELECTRONICS

- 39 Rotary Stepping Switches Tom Jaski
A primer - Part I
- 43 Electronics in the Modern Auto Fred W. Holder
More driving pleasure ahead
- 61 Shrink on the Insulation Julian N. Jablin
A little heat goes a long way
- 62 How to Make Printed Circuit Boards R. T. Montan's
Simple. Just follow the schematic

THE DEPARTMENTS


- | | |
|---|--------------------------|
| 6 Correspondence | 22 News Briefs |
| 77 New Audio Equipment | 96 Noteworthy Circuits |
| 82 New Literature | 86 Technotes |
| 80 New Products | 97 Try This One |
| 92 New Semiconductors and Microcircuits | 74 Reader's Service Page |
| 78 New Test Equipment | |

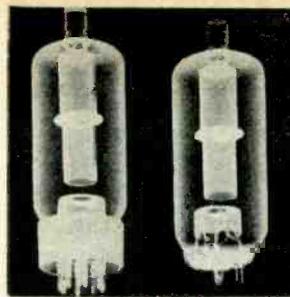


p 54—X-RAY RADIATION



p 35—HEADPHONE CENTER

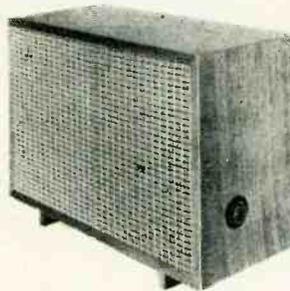

p 42—MINI WOOFER

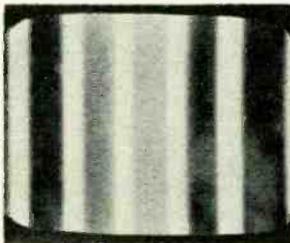

p 37—SERVICE COLOR TV



p 43—AUTO ELECTRONICS

RADIO - ELECTRONICS, NOVEMBER 1967, Volume XXXVIII, No. 11, Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302

Editorial, Advertising, and Executive offices: 154 West 14th Street, New York, N. Y. 10011. Circulation Office, Boulder, Colo. 80302.


Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U. S. and possessions, Canada, \$5. Pan-American countries, \$6. Other countries, \$6.50. Single copies: 60c. © 1967, by Gernsback Publications, Inc. All rights reserved.

POSTMASTERS: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.

COVER FEATURE



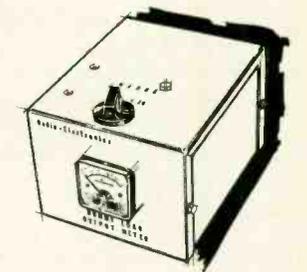p 32—Practical instrument "uncovers" all types of metals.



p 50—LOAD & METER



Member,
Institute of High Fidelity.
Radio-Electronics is indexed in
Applied Science & Technology
Index (formerly Industrial
Arts Index)



Fabian Buchtrach

Hugo Gernsback 1884-1967

Hugo Gernsback, founder and editor-in-chief of RADIO-ELECTRONICS, died August 19, 1967. He was 83.

ON AUG. 16, 1892, an 8-year-old boy studied intently an electric doorbell he had just been given for a birthday present. It was not the mechanical equipment in the wooden case nor the fast-moving clapper that held his attention. What he was watching was the tiny spark between the contacts as the armature made and broke the circuit. The career of Hugo Gernsback started at that moment—his life from that day was spent in learning more about things electric.

Learning more about electricity in the famous Technikum at Bingen on the Rhine, the young Gernsback conceived and developed a greatly improved dry battery. He decided to take it to the land of opportunity—America.

Little doubt that the battery was an improvement—the idea was used years later in large heavy-duty B-batteries. But it had one weakness: it cost nearly twice as much to manufacture as the batteries it was designed to replace. So Hugo had to give up the idea of making a fortune from his invention, and took a job as an engineer with a storage battery manufacturer, Emil Grossman.

Bringing the original thinking that had developed the layer-constructed battery to bear, and remembering the economic angles this time, Gernsback shortly developed a cheaper, lighter and stronger battery case than any on the market. But here a typical Gernsback characteristic—one invaluable to him in his future success—got in the way.

The Gernsback urge to brush aside trivial detail and get to the main objective was, he found, a real handicap in practical engineering. Not carefully tested for corrosion resistance, the new batteries started to leak, and were returned in droves by the dealers. Hugo decided that the plodding detail of an engineer's life was not for him, and formed the Electro Importing Co. to bring equipment from Europe and sell it to experimenters.

Within a year he was selling a radio set to the public. Advertised in the *Scientific American* early in 1906, it was "only" a spark set. But it included both a transmitter and receiver, was portable, had a range of one mile, and sold for \$7.50, complete with send and catch wires (which we would prosaically call receiving and transmitting antennas). Further, it operated (somewhere in the uhf band) without the trouble of tuning.

A catalog was published for mail-order customers. It contained numbers of instructive articles on new and unfamiliar equipment. Gernsback decided to put out a regular magazine to carry the instructive material. In April, 1908, *Modern Electrics* was born. Note the name—nobody would have dared to publish a radio magazine in 1908! But the first article in the first issue was titled "Wireless Telegraphy" and the magazine reported all the latest wireless news faithfully, and printed articles on theory and practical construction.

(continued on page 58)

RADIO-ELECTRONICS

Getting a hernia and not getting paid for it?

Switch to Elmenco dipped Mylar®-paper capacitors and you won't have to worry about call-backs, lost profits, broken reputations or broken anything else.

The only ordinary thing about them is their price. You get capacitors that meet the requirements of high-reliability computer and missile systems. You get capacitors that hold their rating at 125°C continuous operation. Yet you get them at TV set prices.

Elmenco dipped Mylar-paper capacitors come in just about any value you need from .001 mfd to 1.0 mfd. And just about any TV rated voltage you need, too, from 100V through 1600V.

Ask your Authorized Arco Distributor to put them on your next order. Without fail.

Tell him you're counting on his support.

(While you're at it, ask about other Elmenco types: padders and trimmers; high voltage dipped micas.)

Arco Electronics

A Division of Loral Corporation
Community Drive, Great Neck, N.Y./
Arlington, Texas / Elk Grove Village,
Illinois / Pasadena, Menlo Park, California.

© DU PONT TRADEMARK.





MORE WORD FROM OUTER SPACE

ROBERT C. RAMSEY
Chief Engineer, BC, TV
and Recording Equipment

Because of the attention being concentrated on the Gemini space program, further information on the microphones used in the capsule may be of interest to many audio engineers.

Electro-Voice has been intimately involved in the design and construction of the second generation of microphones used in the helmets worn by the astronauts during this program. Design criteria have been quite rigid, although interestingly, the requirements are not wholly dissimilar from those in any critical communications installation.

The environment must be considered as intermittently noisy—with a Titan II booster, noise level in the capsule reaches about 127 db at liftoff. A noise-cancelling element is employed inside the helmet to deal with this problem. This noise cancellation feature also reduces pickup of reverberant sound within the helmet, to significantly improve speech intelligibility.

Two microphones are used to safeguard against failure. This redundancy principle is common in space projects—for instance, each microphone is connected to a separate and independent transmitter.

The microphones are almost invisible in new photos of the astronauts. The shape is designed to put the unit out of the user's line of sight. A small tube leads from the dynamic element mounted near the astronaut's cheek, with the sound pickup port at the tip near his lips. The noise-cancelling port is on the back of this curved tube. Plastics molding of this tube was a feat in itself, with double, precision curved cores whose length and shape required removal by hand after molding.

The entire assembly was tested under extremes of vibration, acceleration, temperature and altitude variations. Much of this testing was in the nature of environmental "overload" tests, where the unit was tested to destruction to find the limits of its capabilities. In addition all materials were exposed to a 100% oxygen atmosphere to assure that no noxious odors were produced.

Among other design characteristics, these microphones had to perform properly at ambient pressures of only 5 psi, and be unaffected by rapid changes in pressure. They also had to be insensitive to high hum fields caused by the high density of adjacent electrical equipment. Special hum-bucking coils solved this interference problem. Response of the microphones had to be peak-free and sufficiently wide range to allow exact tailoring of the transmitter output for optimum signal-to-noise ratio and maximum intelligibility.

Preliminary testing indicates that the microphones developed by Electro-Voice will add to the efficiency of the Gemini program by providing a high order of communications effectiveness without intruding on the efficiency of the astronauts as they perform their flight and scientific duties.

For technical data on any E-V product, write:
ELECTRO-VOICE, INC., Dept. 1173E
613 Cecil St., Buchanan, Michigan 49107

Electro-Voice
SETTING NEW STANDARDS IN SOUND

Correspondence

BRICKBATS AND BOUQUETS

Yes, I have let my subscription lapse and until you make some changes I won't be sorry. I have never written to an editor before and was not going to do so now, but I guess that is the only way things can be corrected. First, I thought it should be a good article on Chet Atkins. Well, I quit on that one about 1/2 way through. I didn't know that it was a technical article on how short he smoked his cigars. Second, I really think it is stupid that everything in a technical magazine be written in conversation form. Say what you have to say and then shut up. Third, the biggest laugh came on your computer article, three pages of nothing and the most (only) technical thing was how it would work out the parallel resistor formula.

DALE R. BALMER
Ames, Iowa


... I like your magazine or I wouldn't bother writing. How about using the space taken up by "Coming Next Month" for something *this month*.

F. BUTTERFIELD
Brooklawn, N. J.

THE PLOT THICKENS

I am building the "Transistor Characteristic Plotter" (September, 1967). I'm having trouble visualizing the construction of the reed switch and the placement of some of the parts. Can you publish any additional diagrams or photos?

O. H. MAXWELL
Central Islip, N. Y.

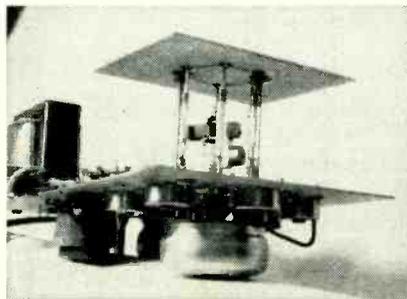

O. H., this photo should help. The reed switches are spaced 60° apart around
continued on page 12

Radio-Electronics

154 WEST 14TH STREET
NEW YORK, N. Y. 10011

HUGO GERNSBACK (1884-1967)

editor-in-chief and founder

M. HARVEY GERNSBACK, Publisher

ROBERT CORNELL, editor

Robert F. Scott, W2PWG, senior editor

Thomas R. Haskett, managing editor

Jack Darr, service editor

Peter E. Sutheim, audio editor

I. Queen, editorial associate

Matthew Mandl, contributing editor

Linda Albers, assistant to editor

Wm. Lyon McLaughlin,

technical illustration director

Bruce Ward, production manager

Adelaide Cassity, production assistant

G. Aliquo, circulation manager

Cover by Harry Schlack

RADIO-ELECTRONICS is published by
Gernsback Publications, Inc.

President: M. Harvey Gernsback

Vice President-Secretary: G. Aliquo

ADVERTISING REPRESENTATIVES

EAST

John J. Lamson,

RADIO-ELECTRONICS, 154 West 14th Street,
New York, N. Y. 10011, 212-255-7755

MIDWEST/N.&S. Car., Ga., Tenn.

Robert Pattis, the Bill Pattis Co., 4761 West
Touhy Ave., Lincolnwood, Ill. 60646,
312-679-1100

W. COAST/Texas/Arkansas/Oklahoma

J. E. Publishers Representative Co., 8380
Melrose Ave., Los Angeles, Calif. 90069,
213-653-5841; 420 Market St., San Francisco,
Calif. 94111, 415-981-4527

UNITED KINGDOM

Publishing & Distributing Co., Ltd., Mitre
House, 177 Regent St., London W.1, England

SUBSCRIPTION SERVICE: Send all subscription correspondence and orders to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302. For change of address, allow six weeks, furnishing both the old and new addresses and if possible enclosing label from a recent issue.

MOVING? Or writing about subscription? Be sure to fill out form below.

For FASTEST service on address change, missing copies, etc., attach old mailing label in first space below. Otherwise please print clearly your address as we now have it.

OLD ADDRESS (Attach old label if available)

Name

Address

City State

Zip Code

NEW ADDRESS


Name

Address

City State

Zip Code

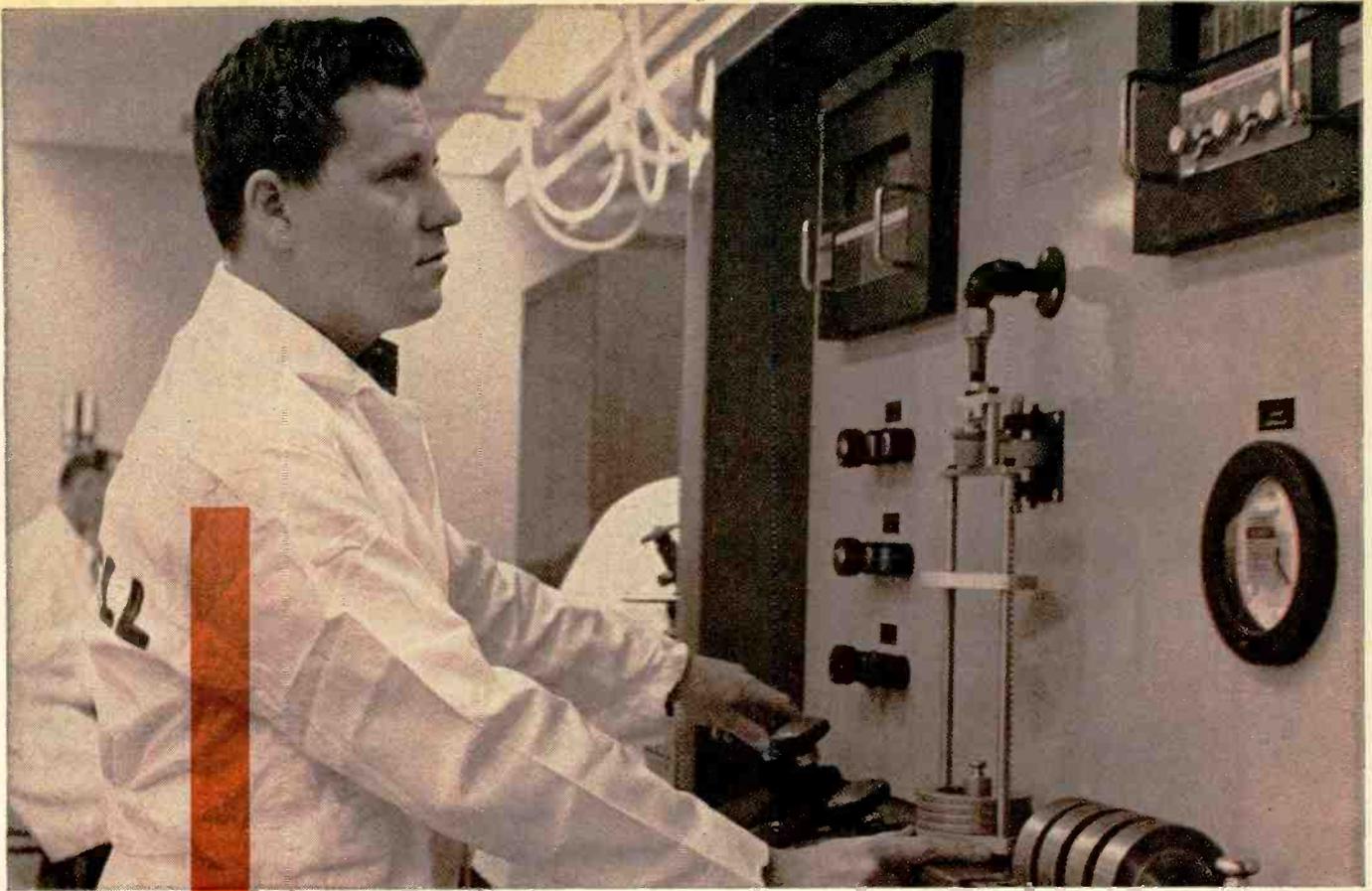Mail to: RADIO-ELECTRONICS
Subscription Dept. Boulder, Colo. 80302



DeVry Not Only Trained Me... But Helped Me Get a Good Job in Electronics

"One of the luckiest days of my life was when I sent for DeVry Tech's informative booklets on Electronics. It was my start toward a wonderful future," says William L. Hudson, originally from Pennsylvania.

"I attended DeVry's Resident School. Upon graduation, without added cost, their Employment Service helped me get a job. Like other graduates of their Resident School and Home Study programs, I am entitled to career-long placement service whenever I need it. That's a wonderful feeling!" concluded Hudson, who is shown above at his job as a laboratory electronics technician for a prominent manufacturer in the space program.

If you are between 17 and 45 years of age, send the coupon now for free details. See how DeVry

may prepare you at home in your spare time — or in day or evening classes at one of its three resident schools in Chicago, Phoenix or Canada. If you enroll in resident school, we help you find a part-time job to defray some of your expenses, if you wish.

Start to make the big switch now toward a bright, profitable future. The first step is to fill in and mail the coupon below.

Approved for Veterans

A SUBSIDIARY OF  **BELL & HOWELL**

Send for Full Facts!

Get two FREE booklets with facts on how a DeVry educational program may prepare you to enter the big field of electronics.



ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL

DEVRY INSTITUTE OF TECHNOLOGY
4141 BELMONT AVENUE, CHICAGO, ILLINOIS 60641

DeVRY INSTITUTE of TECHNOLOGY

4141 Belmont Avenue, Chicago, Ill. 60641, Dept. RE-11-X

Please give me your two free booklets, "Pocket Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Electronic Control |

Name _____ Age _____

Address _____ Apt. _____

City _____ State or Province _____ Zone or Zip Code _____

Check here if you are under 16 years of age.

2107 HOME STUDY AND RESIDENT SCHOOL PROGRAMS
AVAILABLE IN CANADA. SEND FOR DETAILS.

**Discover the ease
and excitement of NRI's**

3 DIMENSIONAL METHOD

of ELECTRONICS TV-RADIO TRAINING

10 HOME-STUDY PLANS TO CHOOSE FROM


Ask men whose judgment you respect about NRI's three dimensional method of home-study training. Ask about the new, remarkable NRI Achievement Kit. Ask about NRI custom-designed training equipment, programmed for the training of your choice to make Electronics come alive in an exciting, absorbing, practical way. Ask about NRI "bite-size" texts, as direct and easy to read as 50 years of teaching experience can make them. Achievement Kit . . . training equipment . . . bite-size texts . . . the three dimensions of home-study training; the essentials you must have to make

learning easier, more interesting, more meaningful. You get them all from NRI.

Whatever your interest . . . whatever your need . . . whatever your education . . . pick the field of your choice from NRI's 10 instruction plans and mail the postage free card today for your free NRI catalog. Discover just how easy and exciting the NRI 3-DIMENSIONAL METHOD of training at home can be. Do it today. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D.C. 20016.

**BEGIN NOW AN ABSORBING
ADVENTURE—LEARN ELECTRONICS
THE EASY NRI WAY—MAIL CARD TODAY**

OVER 50 YEARS OF LEADERSHIP

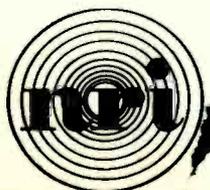


IN ELECTRONICS TRAINING

RADIO-ELECTRONICS

1 Start Fast with NRI's New Remarkable Achievement Kit

The day you enroll with NRI this new starter kit is on its way to you. Everything you need to make a significant start in the Electronics field of your choice is delivered to your door. It's an outstanding way of introducing you to NRI training methods . . . an unparalleled "first dimension" that opens the way to new discoveries, new knowledge, new opportunity. The Achievement Kit is worth many times the small payment required to start your training. No other school has anything like it. Find out more about the NRI Achievement Kit. Mail the postage-free card today.

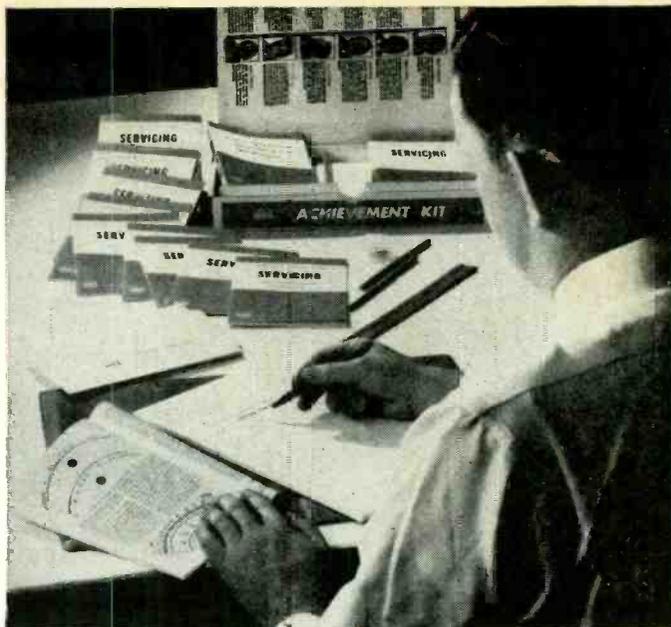

2 NRI "Bite-Size" Lesson Texts Program Your Training


Certainly, lesson texts are a necessary part of any training program . . . but only a part. NRI's "bite-size" texts are simple, direct, well illustrated, and carefully programmed to relate things you read about to training equipment you build. Here is the "second dimension" in NRI's training method. Here are the fundamental laws of electronics, the theory, the training of your choice, presented in a manner you'll appreciate. And in addition to lesson texts, NRI courses include valuable Reference Texts related to the subjects you study, the field of most interest to you.



3 Custom-Designed Training Kits Make Learning Come Alive

Electronics becomes a clear and understandable force under *your* control as you build, experiment, explore, discover. Here is the "third dimension" . . . the practical demonstration of things you read about in NRI texts. NRI pioneered and perfected the use of training kits to aid in learning at home. NRI invites comparison with equipment offered by any other school, at any price. Prove to yourself what 750,000 NRI students could tell you . . . that you get more for your money from NRI than from any other home-study Radio-TV, Electronics school. Mail postage free card for your NRI catalog. (No salesman will call.)

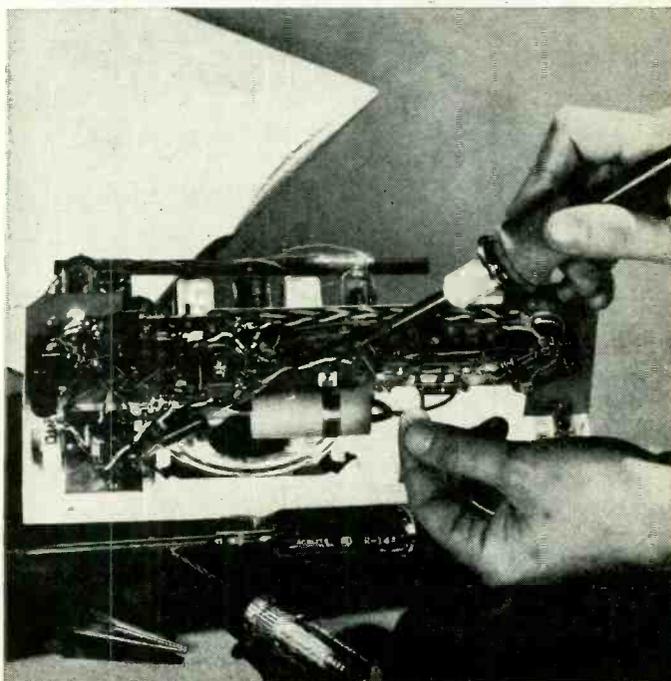AVAILABLE UNDER NEW GI BILL — If you served since January 31, 1955, or are in service, check GI line in postage-free card.



Introducing Winegard's

color★line 82

the finest
TV antenna
lead wire yet!

coaxial
cable
pack



**NOT JUST VHF!
NOT JUST UHF!**

But the first and only 1-piece, molded 82-channel coax system—complete with its own VHF-UHF band separator!

... actually lets you convert any antenna into the lowest loss coaxial system available, without special transformers, connectors and tools.

Look at the features you get only with Color-line 82

- 1 All-band 82-channel transformer** (VHF-UHF-FM) permanently molded onto cable—no connector needed—completely weatherproof! Includes soft drawn copper antenna leads permanently molded into transformer case.
- 2 Sensational new ultra-low-loss, foam-filled coax cable** specially designed and factory sweep-tested for channels 2 to 83. Temperature tested to -55°C . Tough, yet flexible vinyl jacket is easy to work with and won't deteriorate in any weather. Color-line 82 is completely shielded to shut out interference.
- 3 No loss VHF-UHF Band Separator** attaches to set and separates VHF and UHF signals coming from antenna to set. Can be used with 82-channel set or with straight VHF set.

That's what you get **only** with Winegard's Color-line 82—the only 1-piece, molded 82-channel coax system with its own band separator. Available in 50 foot hanks (CL-50), 75 foot hanks (CL-75) and 100 foot hanks (CL-100), each complete with plastic tape. Ready to hear more? Call your Winegard distributor or write for complete information today.



Winegard
ANTENNA SYSTEMS

WINEGARD COMPANY • 3000 KIRKWOOD STREET • BURLINGTON, IOWA 52601

© Copyright 1967, Winegard Company, Burlington, Iowa

Circle 14 on reader's service card



**NOTHING ELSE
TO BUY!**

- Completely self-contained
- Ready-to-install

CORRESPONDENCE continued

a circle just beyond the physical reach of the rotating magnet, but within reach of its magnetic field. The magnet is offset so that only one end effects the reed switches. The counterbalance just below the magnet compensates for the offset condition.

READERS' PRAYERS

I would like to see more construction projects. I would especially like to see a metal detector project of the receiver-transmitter type in which the receiver and transmitter loops are located in a common search head.

DRUCE BLACKWELL
Long Beach, Calif.

... More TV service and technotes to help me cure tough TV jobs. Also, more information about small electronic gadgets.

PETER LEGON
Malden, Mass.

... I would like to see articles on repairing guitar amplifiers and other gadgets.

C. WARREN CORBETT
Chicago, Ill.

... An article on stereo headphones and amplifiers for them.

STUART SJALUND
Haileybury, Ont.

... A lighting-control system using TRIAC's that has six channels, each of 15 amp capacity, with absolutely smooth and linear controls for each channel, plus a master to dim all six proportionally, for stage lighting purposes.

CLARK A. FERGUSON
Kitt Music Co.
Edgewater, Md.

... technical and construction articles.

A. F. BUCK
Vancouver, B. C.

... A master index which covers issues of several years in one little booklet, so that one can use your magazine as a reference book without having to search through every issue to find an article.

WOLFGANG STIER
Radio & TV Service
Orillia, Ont.

Amen.

STEREO FM IN CANADA

May I draw your attention to the Stereo Station Directory (August 1967) in which you listed CKWS as being stereo in the Kingston, Ontario


NEW!
MASTER COURSE
IN COLOR TV...

WITH NTS COLOR KITS

Big 25" Color TV kits included in new Master Color TV Home Study program. Learn Color TV; keep the new 25" color TV receiver you build with exciting kits we send you. 10 million homes in this country will have color TV by the end of 1967. This industry needs technicians as never before, and NTS-trained men can move quickly into the big money.


COLOR TV SERVICING BRINGS HIGH PROFITS

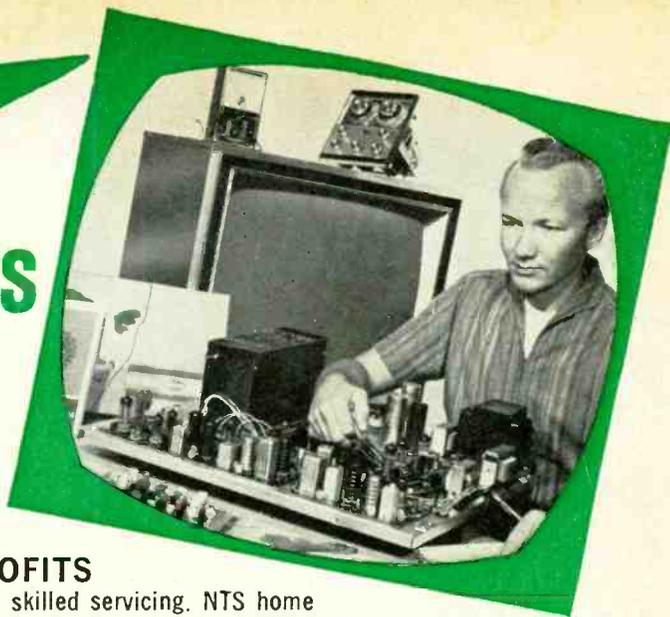New color sets need careful installation, precision tuning and skilled servicing. NTS home training can put you in this profit picture—prepare you for big pay, security, or start a business of your own.



LIFT OFF...TO
A "SPACE AGE"
CAREER IN
ELECTRONICS

This is the "space age". It offers new opportunities in communications, industrial electronics, computer technology, and many others. Automation has increased the need for skilled electronics technicians in thousands of manufacturing plants. Only the well trained man makes it big. Industry wants and demands this kind of man... the NTS man. Pick your field. Let an NTS Project Method Program help you toward a well-paid career in Electronics wherever you travel.

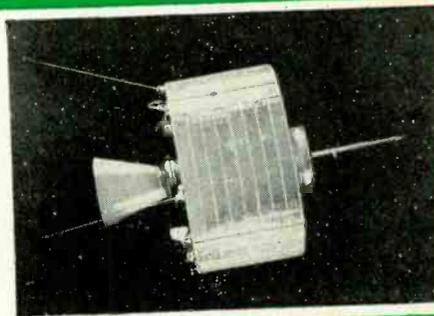

NEW CAREER KIT... FAST, EASY START TO NTS HOME TRAINING

The exclusive Project Method Career Kit helps you move quickly into your training program. Earn while you learn as you progress with your shop-tested Project Method lessons and kits.

Send for the New illustrated NTS Color Catalog. It shows the equipment and kits you work with and keep. Describes in detail the advantages of NTS Project Method Home Training. Tells you everything you need to know about starting your career in electronics.



HIGH SCHOOL AT HOME
 National offers accredited high school programs. Take only subjects you need. Study at your own pace. Everything included at one low tuition. Check special High-School box in coupon for full information & FREE catalog.

CLASSROOM TRAINING AT LOS ANGELES
 You can take Classroom Training at Los Angeles in Sunny Southern California. NTS occupies a city block with over a million dollars in facilities devoted exclusively to technical training.

MAIL REPLY CARD OR COUPON FOR NEW, FREE COLOR CATALOG AND SAMPLE LESSON.



NATIONAL TECHNICAL SCHOOLS

World Wide Training Since 1905
 4000 S. Figueroa St., Los Angeles, Calif. 90037
 You enroll by mail

We have no salesmen: This means lower tuition for you.
 Accredited Member National Home Study Council
 Member: National Association of Trade & Technical Schools

NATIONAL TECHNICAL SCHOOLS

4000 S. Figueroa St., Los Angeles, California 90037

APPROVED FOR VETERANS



Please rush Free Color Catalog and Sample Lesson, plus detailed information on field checked below. No obligation.

Dept. 206-117

- MASTER COURSE IN COLOR TV SERVICING
- COLOR TV SERVICING
- MASTER COURSE IN TV & RADIO SERVICING
- PRACTICAL TV & RADIO SERVICING
- MASTER COURSE IN ELECTRONIC COMMUNICATIONS
- FCC LICENSE COURSE
- INDUSTRIAL & COMPUTER ELECTRONICS
- STEREO, HI FI & SOUND SYSTEMS
- BASIC ELECTRONICS HIGH SCHOOL AT HOME


Name _____ Age _____

Address _____

City _____ State _____ Zip _____

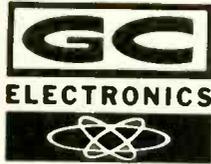- Check if interested in Veteran Training under new G.I. Bill.
- Check if interested ONLY in Classroom Training at Los Angeles.





has
everything in

audio & hi-fi accessories

Cash in on the booming home entertainment market with the GC-Audiotex line of fast-moving accessory items for the tape recorder, hi-fi and stereo fields.

You'll match every need and desire with a complete line of tape splicers, reel holders, pressure pads, spare reels, test tapes, tape Care Kits, and the new "Musi-Kleen" cartridge head cleaner for tape recorder buffs; record Care Kits, cleaning cloths and brushes, static eliminators, and record cleaners for the Hi-Fi record enthusiast.

The complete Audiotex line of microphones, connecting cables, plugs, jacks, and adaptors add depth and versatility to the line . . . build added sales and profits. All are quality products, attractively packaged to sell on sight, and priced to suit every budget.

Insist on GC-Audiotex . . . and you get the finest!

Write for your Giant **FREE** GC Catalog today . . . over 12,000 items including TV Hardware, Phono Drives, Chemicals, Alignment Tools, Audio, Hi-Fi, Stereo & Tape Recorder Accessories, Nuts & Bolts, Plugs & Jacks, Service Aids, and Resistive Devices.

*only GC gives you
everything in electronics.*

.....for almost 40 years!

GC ELECTRONICS COMPANY

400 South Wyman Street
Rockford, Illinois 61101
A DIVISION OF HYDROMETALS, INC.



Musi-Kleen—Tape Cartridge
Head Cleaner
Cat. No. 30-620



Deluxe Tape Splicer
Cat. No. 30-106



Auto Tape Player
Care Kit
Cat. No. 30-636



Stylus Microscope
Cat. No. 30-218



Merchandising Deal
Tape Recorder Accessories
Cat. No. 49-093



Merchandising Deal
Phono Accessories
Cat. No. 49-092



area. To my knowledge this is not the case.

However, CKLC-FM (98.3 MHz) has just completed its stereo installation and has been broadcasting in stereo on a limited time basis since July 17, 1967.

ALBERT AUGLEGER
CKLC Radio
Kingston, Ont.

STEREO ADAPTER

Where can I get a printed circuit board for the project, "A Modern FM Stereo Adapter" (August, 1967)?

GEORGE EDWARDS
Teaneck, N.J.

A drilled printed circuit board for this project (MD116) is available from Transitek Co., P.O. Box 205, Des Moines, Wash., 98016, for \$4.15, post-paid.

TECHNICIAN SHORTAGE

There is a nationwide shortage of suitably trained technicians to service consumer-type electronic equipment. Isn't it about time that our educational system did something more constructive to encourage and train more young men for an electronics career, particularly those who for one reason or another are unable to go beyond a high-school education? Educators and industrialists have, in the past, combined their talents and money to provide trained specialists to man factories and offices; why not do something for individuals who seek to be independent and to be in business for themselves?

BILL GENDLER
Laurelton, N.Y.

Bill, the Electronic Industries Association (EIA) is working on it.

A DOG'S BEST FRIEND


Last fall, you had asked my permission to run a small article in RADIO-ELECTRONICS about a Flashing Neon Collar Lite that I had rigged up for my old dog. I gave you my permission, of course. Since then I have made a few improvements on the collar. The producers of the Lassie TV program in Hollywood, after reading the story, presented me with a beautiful plaque called the "Lassie Gold Award". It is a coveted award in the animal world. It was first given to a soldier on Guadalcanal in World War II for saving the life of a dog.

S. A. SIBLEY
Hockessin, Del.

Congratulations, S. A.



R-E

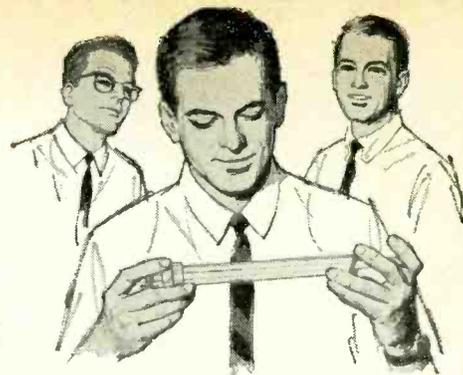Be the man who's always
first to say: "I've got
the answer right here!"



START USING THIS REMARKABLE

ELECTRONICS SLIDE RULE

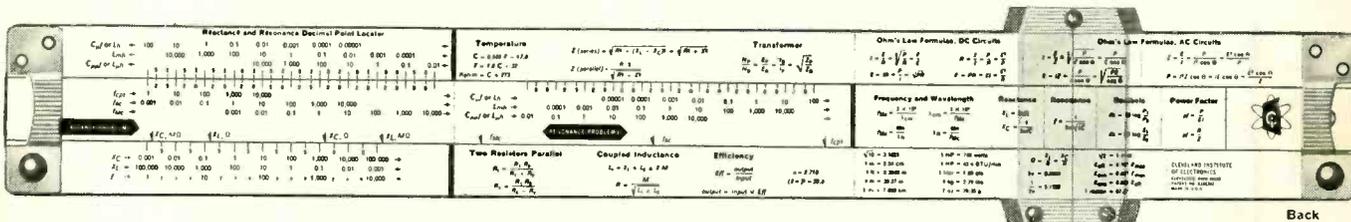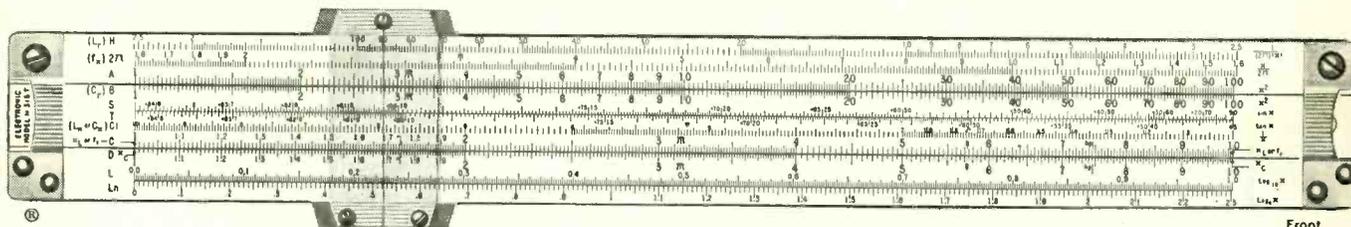

SOME DAY EVERYONE in electronics may have a slide rule like this. Till then, the man who uses one will seem like a wizard as he solves reactance and resonance problems in 12 to 20 seconds—without pencil and paper.

This is a professional slide rule in every detail, a full 10" long, made exclusively for Cleveland Institute of Electronics, to our rigid specifications, by Pickett, Inc. It can be used for conventional computation as well as special electronics calculations. All-metal construction assures smooth operation regardless of climate.

Handsome top-grain leather carrying case has heavy-duty plastic liner to protect slide rule; removable belt loop for convenient carrying. "Quick-flip" cover makes it easy to get rule in and out of case.

You also get four full-length **AUTO-PROGRAMMED™ Lessons**, which teach you how to use the special electronics scales on the slide rule. These lessons have been carefully designed to meet the same high educational standards as the electronics career courses for which our school is famous. Even if you've never used a slide rule before, you'll soon whiz through the toughest problems with this CIE rule.

Deliberately underpriced. Many men in electronics have told us that this unique slide rule, leather case, and 4-lesson course easily add up to a \$50 value. But we have deliberately underpriced it at less than \$25. Why? Our reason is simple: we are looking for men in electronics who are ambitious to improve their skills...who know that this will require more training. If we can attract you with the low price of our slide rule and course—and impress you with its quality—you are more

likely to consider CIE when you decide you could use more electronics training.


Send for free booklet. See for yourself why this amazing slide rule and course have made such a big hit with busy electronics men everywhere. No obligation, of course—just an opportunity to get in on the best offer ever made to people in electronics. Just mail coupon, or write Cleveland Institute of Electronics, Dept. RE-146, 1776 East 17th St., Cleveland, Ohio 44114.

CIE Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

MAIL THIS COUPON FOR **FREE BOOKLET**

Cleveland Institute of Electronics
1776 East 17th Street Cleveland, Ohio 44114

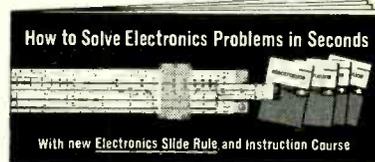Please send me without charge or obligation your booklet describing CIE Electronics Slide Rule and Instruction Course. **ALSO FREE** if I act at once: a handy pocket-size Electronics Data Guide.



Name _____ (please print)
Address _____
City _____ State _____ Zip _____



Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934

RE-146

Circle 17 on reader's service card



finger-
tip avail-
ability

AEROVOX HAS EVERY EXACT REPLACEMENT TWIST PRONG AFH ELECTROLYTIC

Why fool with "jerry-rigged" electrolytics when there's an Aerovox exact replacement to give you the right rating and the right size? Aerovox actually stocks all twist prong AFH electrolytics—this means off-the-shelf availability... not "we'll build it for you if you order it" delivery.

Available in singles, doubles, triples and quads, these popular types are now manufactured in new values for filter bypass applications in color TV as well as radio, black and white TV and amplifier equipment. Many values are now being used for industrial applications.

Aerovox AFH Twist Prong Electrolytics feature ruggedized prongs and mounting terminals, high purity aluminum foil construction, improved moisture resistant seal and 85°C operation. Here is the quality you need to protect your professional reputation.

Go to your Aerovox Distributor for a perfect electrolytic fit—he will deliver exactly what you want in less time than it takes to tell. Ask him for the new Aerovox Servicemen's Catalog #SE-567 or ask us. We'll be happy to send one your way.



**AEROVOX
CORPORATION**

DISTRIBUTOR SALES, NEW BEDFORD, MASS.

Technical Leadership—Manufacturing Excellence

Circle 18 on reader's service card

NEW FCC RULES FOR HAMS—

Incentive Licensing and Distinctive Call Signs

ON APRIL 1, 1965, THE FCC RELEASED a Notice of Proposed Rule Making to amend its rules to provide for incentive licensing and distinctive call signs in the Amateur Radio Service. In addition to those filed by organized amateur groups, more than 1700 formal comments—representing the views of about 4000 licensees—were received in response to the notice. Each comment was considered by the Commission. Almost without exception, the comments were set forth in an intelligent and thoughtful manner and, as a result, they were considered very helpful by the FCC.

The proposals in the proceeding were extensive and provided for higher classes of licenses with reserved frequency-operating privileges as an incentive to the general "upgrading" of licensees, the revision of the privileges and term of the Novice Class license, the modification of a basis of eligibility for the Conditional Class license, and distinctive station call signs. The primary purpose was to consider the establishment of an incentive licensing program.

A program of this nature was endorsed in two out of every three comments. Essentially, the favorable com-

ments concurred in the Commission's view that, in order to justify the continued allocation to the Amateur Radio Service of a substantial portion of the spectrum in the face of incessant and important demands by other radio services, there must be a continuing movement toward the goals set forth in Section 97.1 of the Rules.

The most frequently presented argument against incentive licensing was not based upon disagreement with the Commission's view but, instead, was based upon the contention that an incentive licensing program would have no long-range effect. It was felt that licensees who trained and educated themselves to obtain the higher classes of licenses would merely fall back to their present level of competence after achieving the higher status.

Early Proposals

The FCC proposed two higher classes of licenses for the incentive licensing program which would include the present Amateur Extra Class license and a new license to be designated the Amateur First Class license.

continued on page 56

What's Required to Get an Amateur License

CLASS	ELEMENT I Code speed words/minute	ELEMENT II Basic law and theory	ELEMENT III General theory and practice	ELEMENT IV(A) Intermediate theory and practice	ELEMENT IV(B) Advanced theory and practice
Novice	5	—			
Technician	5		—		
General	13		—		
Advanced	13		—	—	
Extra	20		—	—	—



This important job (and its big salary) is reserved for a qualified electronics technician. It can be you!

It's a fact. There are *thousands* of jobs like this available *right now* for skilled electronics technicians. What's more, these men are going to be in even *greater* demand in the years ahead. But how about you? Where do you fit into the picture? Your opportunity will never be greater . . . so act *now* to take advantage of it. The first step? Learn electronic fundamentals . . . develop a practical understanding of transistors, troubleshooting techniques, pulse circuitry, micro-electronics, computers and many other exciting new developments. Prepare yourself now for a job with a bright future . . . unlimited

opportunity . . . lasting security . . . and a steadily-increasing salary.

Over 23,000 ambitious men are using Cleveland Institute Electronics Training Programs as a stepping stone to the good jobs in electronics. Why not join them? You will learn at home, in your spare time, and tuition is remarkably low. Read the important information on the facing page. Then fill out the postage-free reply card and drop it in the mail today. Without obligation we'll send you all the details. But act now . . . and get *your* high-paying job just that much sooner.

Circle 20 on reader's service card

How You Can Succeed In Electronics

. . . Select Your Future From Five Career Programs

The "right" course for your career

Cleveland Institute offers not one, but five different and up-to-date Electronics Home Study Programs. Look them over. Pick the one that is "right" for you. Then mark your selection on the reply card and send it to us. In a few days you will have complete details . . . without obligation.

1. Electronics Technology

A comprehensive program covering Automation, Communications, Computers, Industrial Controls, Television, Transistors, and preparation for a 1st Class FCC License.



2. First Class FCC License

If you want a 1st Class FCC ticket *quickly*, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.




3. Broadcast Engineering

Here's an excellent studio engineering program which will get you a 1st Class FCC License and teach you all about Program Transmission and Broadcast Transmitters.



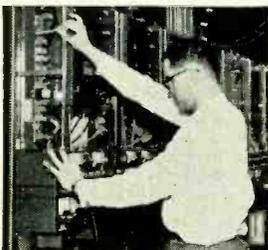4. Electronic Communications

Mobile Radio, Microwave, and 2nd Class FCC preparation are just a few of the topics covered in this "compact" program . . . Carrier Telephony too, if you so desire.



5. Industrial Electronics & Automation

This exciting program includes many important subjects such as Computers, Electronic Heating and Welding, Industrial Controls, Servomechanisms, and Solid State Devices.



An FCC License . . . or your money back!

In addition to providing you with comprehensive training in the area indicated, programs 1, 2, 3, and 4 will prepare you for a Commercial FCC License. In fact, we're so certain of their effectiveness, we make this *exclusive* offer:

The training programs described will prepare you for the FCC License specified. Should you fail to pass the FCC examination after completing the course, we will refund *all* tuition payments. You get an FCC License . . . or your money back!

CIE's **AUTO-PROGRAMMED**™ lessons help you learn faster and easier

Cleveland Institute uses the new programmed learning approach. Our **AUTO-PROGRAMMED**™ lessons present facts and concepts in small, easy-to-understand bits . . . reinforce them with clear explanations and examples. Students learn more thoroughly and faster through this modern, simplified method. You, too, will absorb . . . retain . . . advance *at your own pace*.

Lifetime job placement service for every CIE graduate . . . at no extra cost

Once enrolled with CIE, you will get a bi-monthly listing of the many high-paying interesting jobs available with top companies throughout the country. Many Cleveland Institute students and graduates hold such jobs with leading companies like these: American Airlines, American Telephone and Telegraph, General Electric, General Telephone and Electronics, IBM, Motorola, North American Aviation, New York Central Railroad, Raytheon, RCA and Westinghouse.

CIE lessons are always up-to-date

Only CIE offers new, up-to-the-minute lessons in all of these subjects: Logical Troubleshooting, Laser Theory and Application, Microminiaturization, Single Sideband Techniques, Pulse Theory and Application, Boolean Algebra.



Full accreditation . . . your assurance of competence and integrity

Cleveland Institute of Electronics is accredited by the Accrediting Commission of the National Home Study Council. You can be assured of competent electronics training by a staff of skilled electronics instructors.

ENROLL UNDER NEW G.I. BILL. All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on reply card for G.I. Bill Information.

CIE **Cleveland Institute of Electronics**
1776 E. 17th St., Dept. RE-41, Cleveland, Ohio 44114

NEWS BRIEFS

BIGGEST MICROSCOPE

An electron microscope has more magnification power than an optical one. But image size depends on voltage, which tends to limit resolving power.

Installation was recently completed on the most powerful electron microscope in the US—a 1-million-volt instrument. It's used by United States Steel for research studies on the nature of steel.

The microscope—built by RCA—uses a 1-million-volt accelerator (built by E. Haeffely Ltd.) which stands 17 feet high and weighs 15 tons.

ELECTRONIC CURE FOR COLOR BLINDNESS

A Japanese biologist—Prof. Koichi Honkawa—discovered some time

ago that electrical stimulation of the head can improve visual sensitivity to color. He found that frequencies of 77 and 42.5 Hz, when applied to the temples through a headphone-like device, stimulate sensitivity to the three primary colors—red, green and blue.

A corrective device called the *Sunvister* has been recently developed by Hayakawa Electric Co. which embodies Honkawa's principle. It corrects color blindness in 3 to 6 months of 20-minute daily sessions. *Sunvister* is transistorized and battery-operated.

IC VOLTAGE REGULATOR

So small it is mounted on the generator in some 1968 Pontiac autos, this voltage regulator uses integrated circuits. It was developed by Delco Radio Division and has no moving parts.



The system has no external wiring. It uses electronic sensors which remain unaffected by moisture or vibration.

ZIP-CODE MONITOR


Soon post-office mail sorters may simply read aloud the ZIP code from a letter as they drop it into a new device. The device—being developed by RCA for the US Post Office Department—can recognize spoken numbers. It promises to speed mail sorting.

Called the Numeric Speech Translating System, the machine recognizes spoken digits and activates a mechanical sorter. Device uses solid-state operational amplifiers and logic circuits to discern speech patterns associated with numbers.

FM RECEIVER BOOM

More FM radios are being sold now than ever before; nearly 40% of US radios can receive FM broadcasts. By contrast, in 1961 FM radios accounted for only about 10% of the total US market.

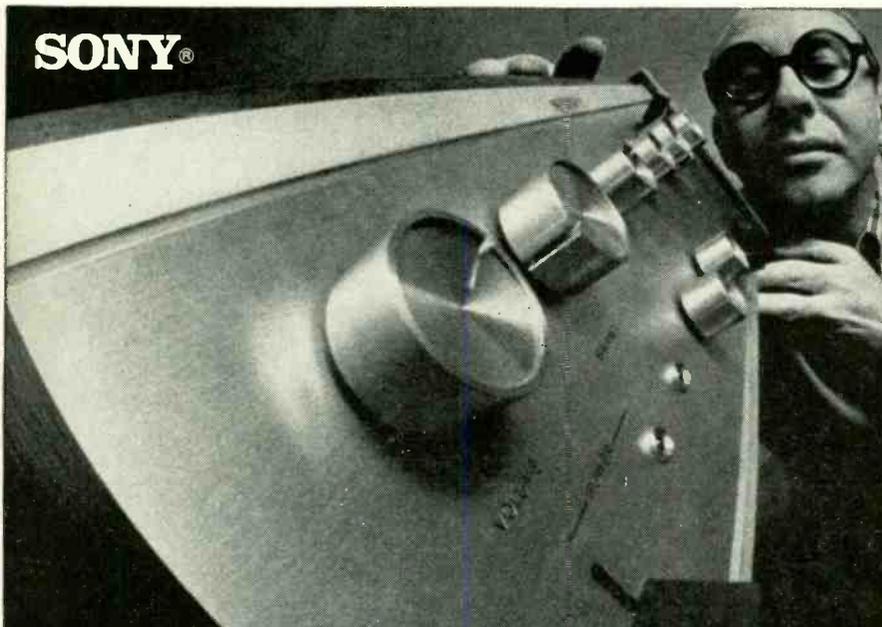According to the Electronic Industries Association, about 9/10 of all radio-phonograph combinations sold have FM capability. Approximately 1/3 of table models and portable radios are FM-equipped. Even clock radios have FM—nearly 1/4 of all units sold are so equipped. **R-E**



Building our own transistors has its advantages... Listen.


The new TA-1080 employs 30 Sony silicon transistors, some built specially for this integrated stereo amplifier.

The TA-1080, modestly-powered heir to the highly-regarded Sony TA-1120, delivers 90 watts IHF power to 8 ohms, both channels operating. Distortion is virtually non-existent at all power levels—less than 0.1% at 1/2 watt and 0.15 at rated output. Overall

frequency response is flat from 30 to 100,000 Hz (+0 db/-2 db). Damping factor and signal-to-noise ratio are excellent. The control facilities are everything you'd expect from the most deluxe units.

The TA-1080, \$299.50 (suggested list). Hear it at your high fidelity dealer. Sony Corp. of America, Dept. H., 47-47 Van Dam St., L.I.C., N.Y. 11101.

Circle 21 on reader's service card

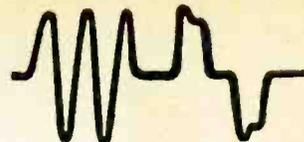

Which miniature electrolytics for transistorized AM-FM radios?

COMPARATIVE SIZES
OF CAPACITORS ALL RATED
10 MFD., @ 25 WVDC
(shown actual size)



TT aluminum electrolytic



MTA aluminum electrolytic




TAS solid tantalum



TAP wet slug tantalum



TLS wet slug tantalum

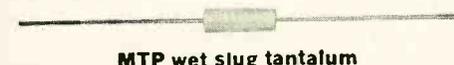

MTP wet slug tantalum

The new portable AM-FM radios are so compact you wonder how they get all those components into that little box. You wonder even more when you have to replace some of the parts.

Electrolytic capacitors, for example. The original electrolytic usually turns out to be a tiny thing jammed in among a dozen other midsize gadgets. Getting it out is a trick in itself. Getting a suitable replacement is even tougher! And unfortunately, you're apt to need replacements, because many of these tiny capacitors just aren't much good. They don't meet the quality specs of good domestic capacitor makers. But high quality domestic capacitors are often just a bit too big to fit in the space available.

What's the answer? Search the town for another "little-bitty" original capacitor? Tell your customer you can't finish the job?

Don't give up. We have a few suggestions.

First, try a Mallory TT aluminum electrolytic. This is a real quality capacitor, rated 85°C, and it's pretty doggone small. Or a Mallory MTA, a revolutionary molded case aluminum electrolytic with excellent quality at low price.

If neither of these will fit, try a Mallory tantalum capacitor. The TAS solid tantalum is about the same size as the TT, but it's rated 125°C. Need still smaller size? Take a look at the Mallory "wet slug" tantalum types TAP and TLS—and the super-miniature MTP, which gives you the most microfarads in the smallest size of anything on the market. The pictures at the left show you comparative sizes, all for a 10 mfd, 25 WVDC rating.

Sure, you'll pay a little more for the tantalum capacitor. But not as much as you might think. The TAP only costs 42c more than the TT, in the rating shown. And you get the utmost in reliability.

We certainly don't expect you to use a tantalum capacitor to replace every aluminum electrolytic. But they come in mighty handy sometimes. And you can get them when you need them from your Mallory Distributor. Ask him for our latest catalog, or write to Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

DON'T FORGET TO ASK 'EM — *What else needs fixing?* —

Circle 23 on reader's service card

A plug from...


The World's Largest Manufacturer
of Molded-On Cables and Connectors

BARKER

MOLDED-ON® PLUGS AND CONNECTORS



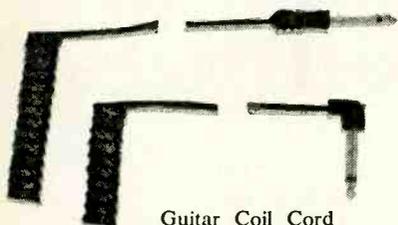Stereo Headset
Extension Coil Cord
"Molded-On" Stereo head
set extension coil cord.
Three conductor phone plug one
end of 15' (extended) coil cable. The other
end, a 3 conductor phone jack. Re-
tracted length 3'.



Guitar Coil Cord
Molded-On guitar coil cord. En-
gineered to connect guitar to amplifier.
Molded-On right angle, completely
shielded phone plug, one end of 20'
(extended) black jacket, shielded coil
cable. The other end a straight
Molded-On phone plug. Retracted
length is 3'. Part No. 20' RSP-RE.

The greatest name in "Molded-On" plugs and connectors is **Barker**—manufacturers of connecting cables for every audio, hi-fi and stereo need.

Barker plugs are solid plastic units, molded directly onto the wire ends to provide unflinching performance and unexcelled appearance. **Barker** has the most manufacturing experience... the most engineering experience.

If you are a manufacturer of—amplifiers, tuners, record changers, microphones, speaker accessories, stereo head sets or musical instruments—let **Barker** be your source of supply. Let us quote you! Distributors and dealers: write for our latest catalog. All our products made on our U.S.A. premises. Circle Reader's Service # for our latest catalog. For speedier service, write us direct.

BARKER PRODUCTS CO.

344 Central St., Saugus, Mass. 01906
Telephone: 617-233-6676

Subsidiary of
Component Manufacturing Service, Inc.

Circle 24 on reader's service card

In the Shop . . . With Jack

By JACK DARR

The screen won't light; what to do? Check the high voltage? Not necessarily, and especially not in a color TV set. Because of the dc coupling used in practically all color TV video amplifier circuits up till now, any fault in the video amplifiers will cause the screen to go dark. This can happen as far back as the first video amplifier or even the video detector!

Here's what happens: The video-amplifier circuit actually sets the bias on the color CRT (see the simplified diagram). The video (Y) signal is fed to the cathodes of the color picture tube, through a complicated network of resistors and coils. The plate voltage of the last video amplifier is fed through the KINE BIAS control and the BLUE and GREEN DRIVE controls.

What happens if there is something wrong in the video amplifier circuits that affects the current drain? You're right; it upsets the bias on the color CRT. If the dc voltage goes up (more positive) on the cathode of any tube, it is exactly the same as applying a negative voltage to the grid: the tube is cut off and the screen goes dark, and the set owner goes to the telephone!

Any of several things can cause this. For instance, in the popular RCA circuits, such as the CTC12 shown in the diagram, the 12BY7 video output tube shows +295 volts on the plate; this comes from the +390-volt line through the resistance network shown. Let's see what could happen.

The 12BY7 tube goes dead. No plate current drawn, so no voltage


This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

drop across load resistors—up goes the plate voltage (cathode voltage of the CRT) and out goes the raster. The 100-ohm resistor in the 12BY7 screen circuit opens: no screen voltage, down goes the plate current, up goes the voltage and here we are again. The 220-ohm resistor in the 12BY7 cathode circuit opens. Now the plate circuit is broken, and no plate current can flow—see above!

If you find a color-TV set with a black screen, make all the easy checks first: the CRT heater by visual inspection, HV, horizontal output and damper tubes, fuse and so on. Then start checking some bias voltages. (By the way, shoving one of the little neon HV testers up to the plate lead of the horizontal output tube, or near the flyback, is a very good short-cut check for the presence of HV. If you get a good bright glow, the chances are the HV circuits are okay.)

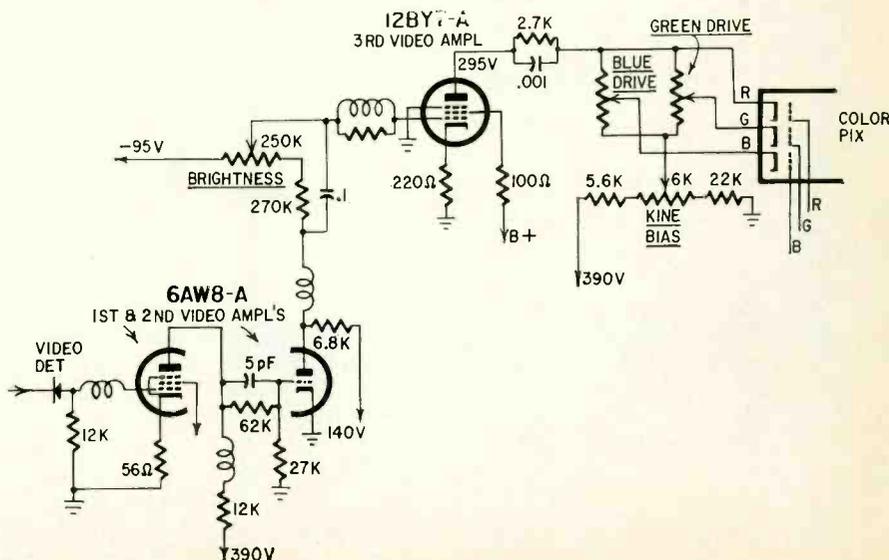Don't stop too soon, either; this
continued on page 26



1968

A Howard W. Sams PUBLICATION

Photofact[®] Annual Index

MASTER INDEX TO THE AUTHORITATIVE SERVICE DATA FOR THE ELECTRONICS INDUSTRY

COMPLETE PHOTOFACT COVERAGE

COVERS PHOTOFACT SETS 1 THROUGH 840 (All PHOTOFACT FOLDER releases from April 1, 1946 to January, 1968. All PHOTOFACT Specialized Series volumes released through Jan. 1968.)

IMPORTANT: Use this Master Annual Index with the latest current Supplement for complete up-to-date model coverage. Supplements are issued in February, May and September of each year.

See Complete Table of Contents on Page 1

Free Photofact[®] Annual Index

for your use throughout 1968



send today for your instant handy guide to the world's finest electronic service data!

COVERS OVER 75,000 LISTINGS:

Send today for this valuable 136-page guide covering virtually every model of home-entertainment electronic equipment produced since 1946! Helps you locate the proper PHOTOFACT Folder to quickly solve any service problem in any model. PHOTOFACT provides everything you need in complete, uniform style for quick, effective repairs: Famous Standard Notation Schematics packed with the service details you need; Full Photo Coverage of all chassis views; Complete Replacement Parts Lists; Tube Placement Diagrams; Alignment Instructions; CircuiTrace[®] for printed boards; Disassembly Instructions; Dial Cord Diagrams; Changer and Recorder "Exploded Views"—plus dozens of other great features. Send coupon for your FREE copy of the latest PHOTOFACT Index to the service data you need!

- Color and Black & White TV Receivers
- Home and Auto Radio Receivers
- Phonographs and High-Fidelity Sets
- CB Radios • Tape Recorders • Record Changers

YOUR COMPLETE REFERENCE TO PHOTOFACT COVERAGE FOR FASTEST REPAIR OF VIRTUALLY ANY MODEL!

Send for the Photofact Annual Index—your "master" reference throughout 1968. Once you are on our mailing list you will automatically receive Index Supplements to keep you up-to-the-minute on Photofact coverage of the latest equipment as it is released.



JOIN THE PHOTOFACT-OF-THE-MONTH CLUB:



NOW! Only \$10 per month brings you 20% MORE Photofact coverage to keep you current—saves you over \$60 per year!

- Get 6 new Photofact Sets each month
- Covers at least 50 new chassis
- At least 6 Color TV Folders monthly

NEW BONUS: MINIMUM OF 10 "ADVANCE" TV SCHEMATICS (MOSTLY COLOR) WITH EACH MONTH'S ISSUE—PLUS GREAT FILE CABINET DEAL WITH TRIAL 6-MONTH SUBSCRIPTION TO P.O.M. (PHOTOFACT-OF-THE-MONTH CLUB).

JOIN P.O.M.

For details, see your Sams Distributor, or send coupon

HOWARD W. SAMS & CO., Dept. REF-11
4300 W. 62nd St., Indianapolis, Indiana 46206



- Send FREE 1968 Photofact Annual Index and place my name on your mailing list to receive the Supplements
- Send Photofact-of-the-Month Club details

My Distributor is _____

Shop Name _____

Attn.: _____

Address _____

City _____ State _____ Zip _____

Circle 25 on reader's service card

WHY bother with makeshift twist-prong capacitor replacements?

When you substitute capacitor sizes and ratings, you leave yourself wide open for criticism of your work . . . you risk your reputation . . . you stand to lose customers. It just doesn't pay to use makeshifts when it's so easy to get the exact replacement from your Sprague distributor!

Get the right SIZE,
right RATING every time
with improved



SPRAGUE TWIST-LOK® CAPACITORS!

2,365 different capacitors to choose from!

The industry's most complete selection of twist-prong capacitors, bar none. Greater reliability, too. Exclusive Sprague cover design provides a leak-proof seal which permits capacitors to withstand higher ripple currents.

GET YOUR COPY of Sprague's comprehensive Electrolytic Capacitor Replacement Manual K-109 from your Sprague Distributor, or write Sprague Products Co., 81 Marshall Street, North Adams, Mass.



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

Circle 26 on reader's service card

In the Shop . . . With Jack


(continued from page 24)

kind of trouble could go as far back as the video detector, as you can see from the partial schematic. Check *all* voltages, and for goodness' sake don't forget to check the grid bias on these tubes—it is very important. A big negative voltage, leaking from somewhere, can cut off one of the video amplifier tubes; you get the same symptoms that you'd find if the plate resistor opened, etc. A change of only a volt or two back down the line can make a big difference, so don't overlook anything!

Tape recording from PA output

I ran into a problem in a church sound system. They want to record (on tape) from the PA system. I tried feeding the tape recorder from the PA output, and got hum and garble. Is this due to an impedance mismatch? It should be; I was using the high-impedance input. Can I rig up a low-impedance input on the tape recorder?—C.F., Wilbur, Ore.

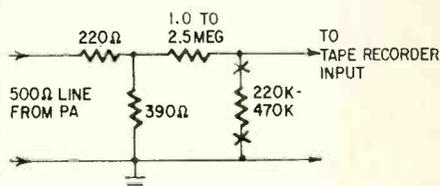The impedances are badly mismatched, but this isn't the main problem. You're feeding a very-high-level signal—several volts at least—into an input that is designed to work from only a few millivolts. Consequently, you're simply beating that poor little input tube to its knees from the overload!



I ran into exactly the same problem (in a church job, too) and solved it simply by adding a matching pad. The pad actually isn't primarily for matching, but mainly for knocking down that voltage. Use good-size series resistors and fairly small shunt resistors, and you'll find that you can get good recordings in this way.

Set up the pad (see the diagram) so that you can get good recording volume with the tape-recorder record gain control set at about half-open. Then watch the recording indicator (eye tube or meter) for your level. The pad resistors do not seem to be too critical. If you can't get enough reduction with a single section, add another section. The input values shown will make a pretty good match to a 500-ohm line; for a 70.7-volt line, raise the values just a little. **R-E**



Are you eligible for the Bright Guy Awards?

It's easy to get them—and to get all the business they'll bring you. New customers. More sales. More money.

The Bright Guy Awards is the big program Sylvania's running this year to boost your sales.


Your Sylvania distributor can put your name and address in TV Guide ads in your area. The ads call you "the brightest serviceman in town"—and tell people in your town why they should call you.



You'll get into the Yellow Pages, too, under the heading

"TV Service and Repairs."

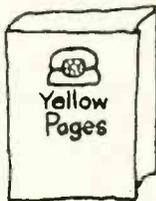
Once again this year you'll be eligible for over one hundred valuable, interesting



SMB-Bright Guy gifts, just for buying the Sylvania TV replacement parts you normally buy anyway.

And you'll get window displays proclaiming you "the brightest"—the TV serviceman everyone's reading about.

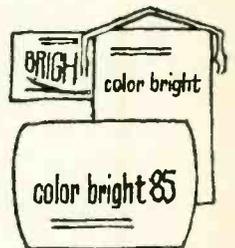You're eligible for the Bright Guy Awards just by buying Sylvania's famous *color bright 85*[®] picture tube. And our other picture tubes, and our receiving tubes. So see your Sylvania distributor.




Sylvania Electronic Tube Division, Electronic Components Group, Seneca Falls, New York 13148.

SYLVANIA

A SUBSIDIARY OF
GENERAL TELEPHONE & ELECTRONICS


Circle 27 on reader's service card

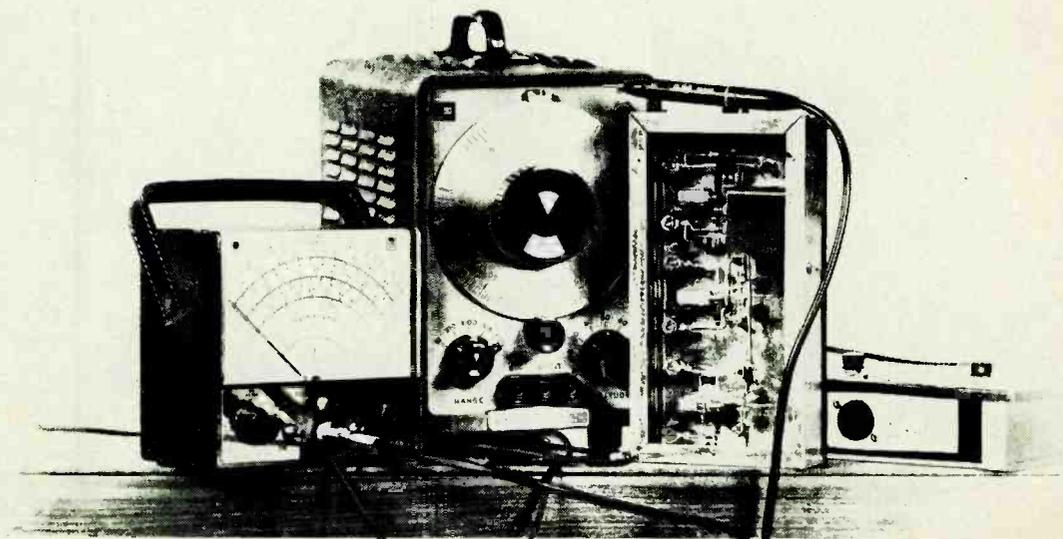SOMEONE SHOULD DEVELOP AN EASY WAY TO LEARN ELECTRONICS AT HOME



RCA INSTITUTES DID!

Here is a whole new approach to learning electronics at home! RCA Institutes, one of the nations' largest schools devoted to electronics, has developed a faster, easier way for you to gain the skills and the knowledge you need for the career of your choice. Here for the first time, is a student-proved, scientifically designed way to learn. If you have had any doubts in the past about home training in electronics —if you have hesitated because you thought you might not be able to keep up—or that electronics was too complicated to learn—here is your answer! Read how RCA Institutes has revolutionized its entire home training ideas!

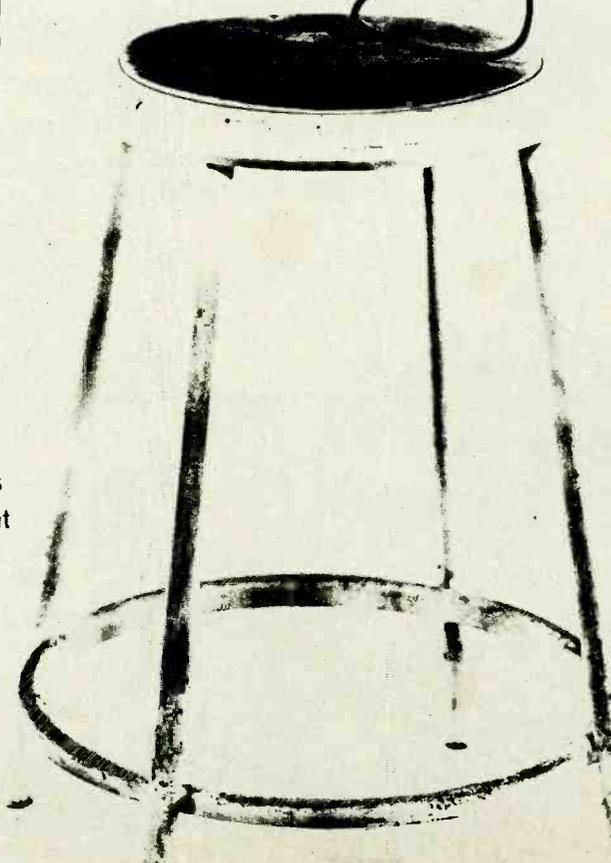

NEW CAREER PROGRAMS BEGIN WITH "AUTOTEXT" INSTRUCTION METHOD!

Start to learn the field of your choice immediately!

No previous training or experience in electronics needed!

With this new revolutionized method of home training you pick the career of your choice—and RCA Institutes trains you for it. RCA's Career Programs assure you that everything you learn will help you go directly to the field that you have chosen! No wasted time learning things you'll never use on the job! The Career Program you choose is especially designed to get you into that career in the fastest, easiest possible way!

And each Career Program starts with the amazing "AUTOTEXT" Programmed Instruction Method—the new, faster way to learn that's almost automatic! "AUTOTEXT" helps even those who have had trouble with conventional home training methods in the past. This is the "Space Age" way to learn everything you need to know with the least amount of time and effort.

CHOOSE A CAREER PROGRAM NOW

Your next stop may be the job of your choice. Each one of these RCA Institutes Career Programs is a complete unit. It contains the know-how you need to step into a profitable career. Here are the names of the programs and the kinds of jobs they train you for. Which one is for you?

Television Servicing. Prepares you for a career as a TV Technician/Serviceman; Master Antenna Systems Technician; TV Laboratory Technician; Educational TV Technician.

FCC License Preparation. For those who want to become TV Station Engineers, Communications Laboratory Technicians, or Field Engineers.

Automation Electronics. Gets you ready to be an Automation Electronics Technician; Manufacturer's Representative; Industrial Electronics Technician.

Automatic Controls. Prepares you to be an Automatic Controls Electronics Technician; Industrial Laboratory Technician; Maintenance Technician; Field Engineer.

Digital Techniques. For a career as a Digital Techniques Electronics Technician; Industrial Electronics Technician; Industrial Laboratory Technician.

Telecommunications. For a job as TV Station Engineer, Mobile Communications Technician, Marine Radio Technician.

Industrial Electronics. For jobs as Industrial Electronics Technicians; Field Engineers; Maintenance Technicians; Industrial Laboratory Technicians.

Nuclear Instrumentation. For those who want careers as Nuclear Instrumentation Electronics Technicians; Industrial Laboratory Technicians; Industrial Electronics Technicians.

Solid State Electronics. Become a specialist in the Semiconductor Field.

Electronics Drafting. Junior Draftsman, Junior Technical Illustrator; Parts Inspector; Design Draftsman Trainee Chartist.

SEPARATE COURSES

In addition, in order to meet specific needs, RCA Institutes offers a wide variety of separate courses which may be taken independently of the Career Programs, on all subjects from Electronics Fundamentals to Computer Programming. Complete information will be sent with your other materials.

LIBERAL TUITION PLAN

RCA offers you a unique Liberal Tuition Plan—your most economical way to learn. You pay for lessons only as you order them. No long term contracts. If you wish to stop your training for any reason, you may do so and not owe one cent until you resume the course.

VALUABLE EQUIPMENT

You receive valuable equipment to keep and use on the job—and you never have to take apart one piece to build another. **New—Programmed Electronics Breadboard.** You now will receive a scientifically, programmed electronic bread-

board with your study material. This breadboard provides limitless experimentation with basic electrical and electronic circuits involving vacuum tubes and transistors and includes the construction of a working signal generator and superheterodyne AM Receiver.

Bonus From RCA—Multimeter and Oscilloscope Kits. At no additional cost, you will receive with every RCA Institutes Career Program the instruments and kit material you need to build a multimeter and oscilloscope. The inclusion of both these kits is an RCA extra.

CLASSROOM TRAINING ALSO AVAILABLE

RCA Institutes maintains one of the largest schools of its kind in New York City where classroom and laboratory training is available in day or evening sessions. You may be admitted without any previous technical training; preparatory courses are available if you haven't completed high school. Coeducational classes start four times a year.

JOB PLACEMENT SERVICE, TOO!

Companies like IBM, Bell Telephone Labs, GE, RCA, Xerox, Honeywell, Grumman, Westinghouse, and major Radio and TV Networks have regularly employed graduates through RCA Institutes' own placement service.

SEND ATTACHED POSTAGE PAID CARD FOR COMPLETE INFORMATION, NO OBLIGATION. NO SALESMAN WILL CALL.

**ALL RCA INSTITUTES COURSES
AVAILABLE UNDER NEW GI BILL.**

Accredited Member
National Home Study Council



The Most Trusted Name in Electronics

RCA INSTITUTES, Inc., Dept. RE-N7

A Service of Radio Corporation of America
350 West 4th St., New York, N.Y. 10014

BUILD

A Treasure Finder

Unique, inexpensive metal locator "picks up" all metals

By CHARLES D. RAKES



FINDING BURIED TREASURE can be fun. This construction project can lead you to lost coins on the beach, keys dropped in a snowdrift, water pipes, electrical wiring and just about any type of metal object. It will detect the presence of coins and other small objects 4 to 8 inches from the search loop, and larger objects at a range of several feet.

Two popular types of metal locators are the beat-frequency and transmitter-receiver models. This one is different. It is a tuned-loop oscillator and a crystal filter acting in combination to provide sensing and indicating signals. It is simple, stable and sensitive and is easy to build and operate.

Theory of operation

As shown in Fig. 1, transistor Q1, search loop L1 and associated components form a Colpitts oscillator circuit. The frequency of operation is determined by C1, C2, C3, C4 and the inductance of the loop. Oscillator output is loose-coupled from the collector

of Q1 to the base of Q2, through C5 and R4. Operating as an emitter follower amplifier, Q2 has a voltage gain of less than one. From the emitter of Q2, the signal is fed through potentiometer R8 to Q3 through the 1-MHz crystal, XTAL 1.

If the oscillator is operating within the narrow passband of XTAL 1, the rf signal will pass through the crystal (in the series-resonant mode of operation). The rf is then rectified by D2 and the base-emitter junction of Q3. The resulting dc is amplified by Q3 and indicated on milliammeter M1.

Now let's see how the circuit operates as a sensitive metal locator. Assume that no metal is near the search loop and the power is on. Adjust the oscillator to the low-frequency end of the crystal bandpass and set R8 for a meter reading of about 0.2 mA.

If you bring the search loop close to a metal object, eddy currents will be induced. These currents decrease the loop inductance, changing the oscillator frequency. The crystal filter "looks"

at this slightly higher frequency with a lower impedance; passes a greater amount of rf energy to the base of Q3. The result is an increase in the meter reading.

If the oscillator had been adjusted to the high-frequency end of the crystal bandpass curve, the meter reading will drop when the loop nears metal. More about this later.

Construction

I built the crystal-filter metal locator in a deep drawn aluminum box measuring 5" x 3" x 2". All parts are mounted on the cover (Fig. 2). An aluminum utility box could be used but the mechanical stability of the deep-drawn box is preferable. Most components are mounted and wired on a section of perforated board 2½" x 3¾" with push-in terminals. For best results your parts layout should follow Fig. 3 as closely as possible. Trimmer capacitor C4 is mounted facing one end of the case, as you can see in Fig. 2.

I used a removable hole plug to allow fine adjustment after the device was assembled.

Since the metal locator will be carried around, the wiring should be well fixed in place. The mechanical assembly must be rigid and free of mechanical vibrations. If not, you will be inviting instability and random operation.

Mount the perforated board on the front panel with two metal spacers 1¼" long (Fig. 2). The front panel is held in position by a 10-32 x 2¼" machine screw. For a handle, you can use a 3-foot piece of ⅜" aluminum electrical conduit. The box is attached to the handle with a bracket made from ⅛" x ⅜" aluminum stock.

Search loop

Form the ⅜" copper tubing into a 10½"-diameter circle with a gap of about 1 inch between ends. Push approximately 36" of 6-wire cable through the circle of tubing. Let the cable extend out each end about 1 inch, and cut off the remaining wire. Then strip the plastic cover from the ends of the cable, exposing the 6 wires at each end of the tubing, then connect, solder and tape the connections to form a single 6-turn coil, as shown in Fig. 4. Ground only one end of the copper shield to the ground end of the loop—that is, the end of the loop connected to the shield of the coaxial cable.

The search loop is sandwiched between two 1½" discs of ¼" plywood (or similar nonmetallic material—see Fig. 6). I used a wing nut to mount the sandwich on the handle, so the loop angle is adjustable. A length of coaxial cable runs through the handle, from the control box to the search loop. The cable connects to the loop through J1 and P1.

Calibration

With the wiring completed, the loop connected and the battery in place, you can tune up the circuit. Position the search loop so that it isn't located near any metal objects, turn the power on and set potentiometer R8 about ⅛th turn clockwise from the end. Adjust the TUNE capacitor C1 so the plates are approximately half-meshed; then remove the hole plug and slowly adjust trimmer capacitor C4 until the meter swings up scale and pegs itself. Try to leave the trimmer set so there is a meter indication of greater than half scale. Replace the hole plug and adjust the TUNE capacitor for a meter reading of about 0.2 mA.

With the meter still indicating 0.2 mA, slowly bring the loop near a metal object. If the meter reading increases

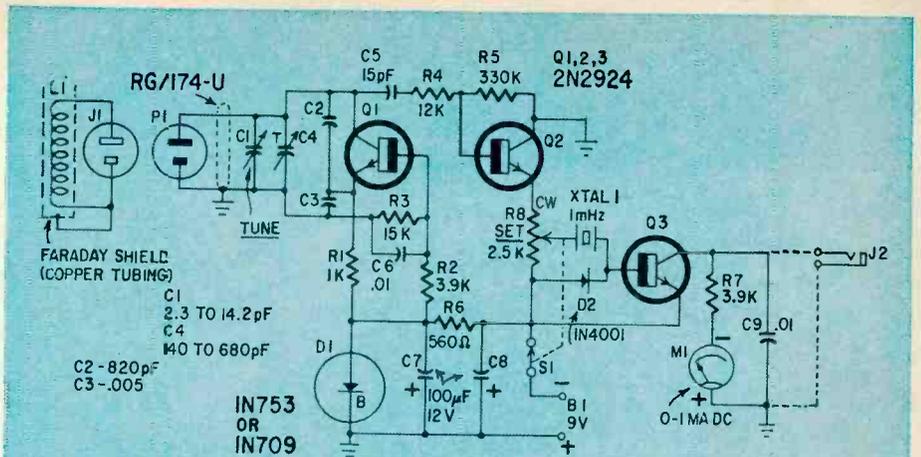


Fig. 1—Frequency of oscillator Q1 varies as search coil nears buried metal. The resulting variation in the rectified output of crystal filter shows on the meter.

Parts List for Metal Locator

- | | |
|--|---|
| B1—9-volt transistor battery, (NEDA 1604) | R5—330,000-ohm resistor |
| C1—2.3-pF to 14.2-pF miniature variable capacitor, (E. F. Johnson 160-107, or equivalent) | R6—560-ohm resistor |
| C2—820-pF silver mica capacitor (or better grade of disc ceramic) | R8—2500-ohm potentiometer with switch S1 |
| C3—0.005-µF disc ceramic capacitor | All resistors ½-watt unless otherwise noted |
| C4—140-pF to 680-pF trimmer capacitor, (Elmenco 468 or similar) | S1—S.p.s.t. switch (part of R8) |
| C5—15-pF silver mica capacitor | xtal 1—1000 kHz crystal |
| C6, C9—0.01-µF disc ceramic capacitor, (Elmenco 468 or similar) | 1—34" length of ⅜"-diameter copper tubing |
| C7, C8—100-µF, 12-volt electrolytic capacitor | 1—36" length of 6-conductor cable |
| D1—6-volt Zener diode, (1N753, 1N709, or equivalent) | 1—41" length of ⅜" aluminum conduit or material |
| D2—Silicon diode (1N4001, 1N4002, 1N4003, etc.) | 2—11¼" diameter loop covers made out of plywood, Masonite or similar material |
| J1, P1—Two-conductor polarized connectors, one male and matching female, (Cinch-Jones or equivalent) | 1—Unit mounting bracket (see text) |
| L1—Search loop, (see text) | 2—Aluminum "L" brackets for loop and handle assembly |
| M1—0-1 mA dc milliammeter, (Micronta miniature panel meter or equivalent) | 2—1½" metal spacer, circuit board support |
| Q1, Q2, Q3—Silicon transistors, (2N2924 or equivalent) | 1—2½" x 3⅜" section of perforated phenolic board |
| R1—1000-ohm resistor | 25—Push-in terminals |
| R2, R7—3900-ohm resistor | 1—6 foot section of RG-174/U (Belden 8216 coaxial cable or similar) |
| R3—15,000-ohm resistor | 1—3" x 5" x 2" Deep-drawn aluminum box, with a matching tight-fitting outside cover. |
| R4—12,000-ohm resistor | Misc. Knobs, screws, hookup wire, solder, plastic bicycle handle grip, battery holder and snap-on terminals, etc. |

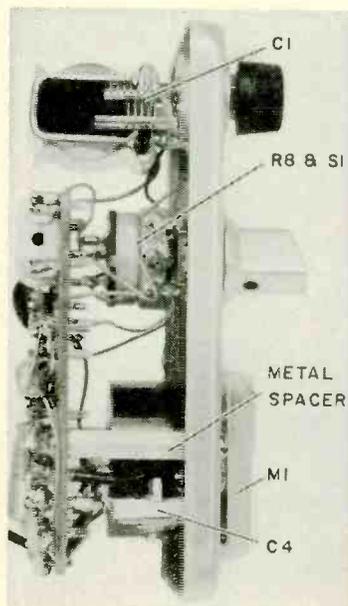


Fig. 2—Use spacers to hold perforated board on to panel.

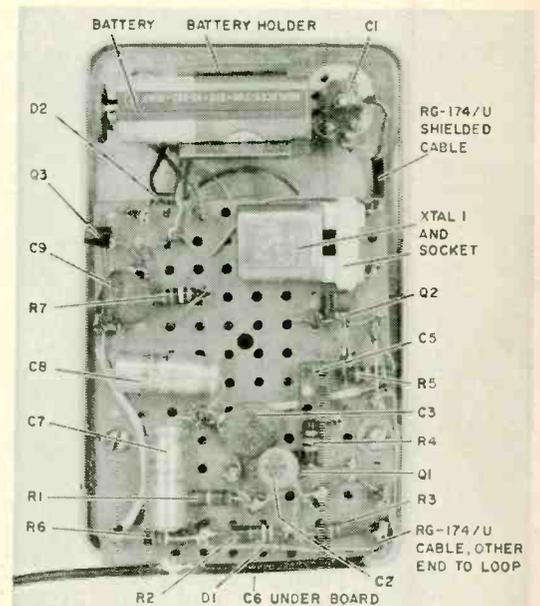


Fig. 3—Secure all components in place and follow this layout for reliable operation and stability.

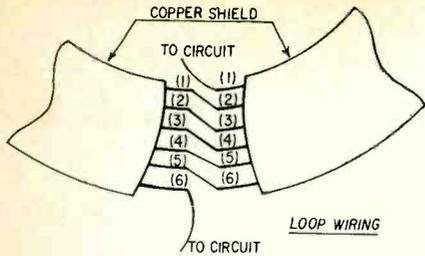


Fig. 4—Construction of the search loop is simplified by using 6-conductor intercom cable. Push it through the copper shield and connect the ends as shown.

To reduce this effect, operate the search loop approximately 4 to 6 inches above the ground.

After a bit of practice, you'll find the most sensitive operation occurs when SET potentiometer R8 is turned almost completely counterclockwise, and the TUNE capacitor C1 is set for a low scale indication.

For locating large objects near the

as shown in Fig. 1. Any small speaker will do, if it has an 8- or 4-ohm voice coil.

The squealer loads the meter circuit slightly and reduces sensitivity somewhat. While this is no disadvantage for many jobs, you may want to unplug the squealer and go by the meter reading alone when you need all the sensitivity you can get. **R-E**



Fig. 5—A meter and only two controls is an indication of the locator's simplicity and ease of operation. The jack at lower left is for the audible monitor.

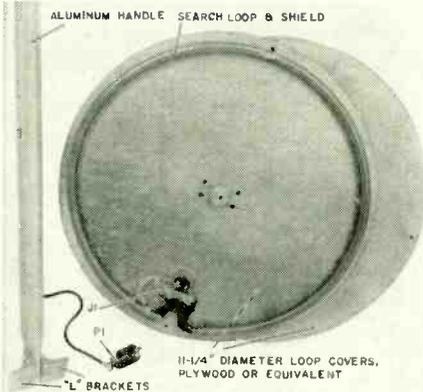


Fig. 6—Search loop is protected by plywood discs. P1 on end of coax cable connects loop (through J1) to oscillator in box on other end of handle.

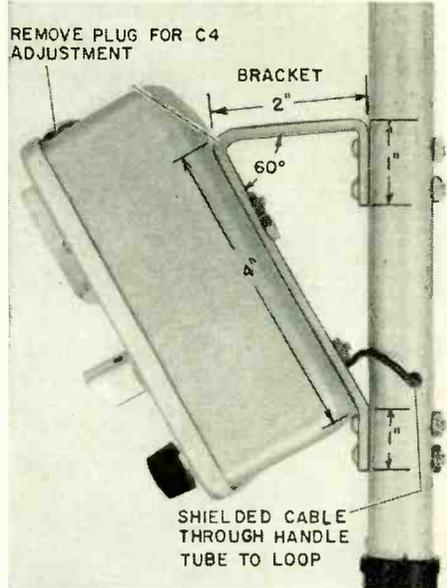


Fig. 7—Mount the oscillator box on the handle with a bracket constructed as shown from $\frac{1}{8}$ " x $\frac{3}{8}$ " aluminum stock. The angle is necessary so the meter can be easily read when operating the metal locator. Coax is threaded through handle.

sharply, the locator is adjusted to its most sensitive mode of operation. The oscillator is then working at the low-frequency end of the sharp crystal-filter curve. If the meter indication drops when the loop approaches a metal object, the oscillator is operating on the high-frequency end of the filter curve; it won't be quite as sensitive in this mode of operation.

Operation

Take the metal locator outdoors and set it up for the most sensitive mode of operation. Make these adjustments with the loop pointed away from the ground and any metal object. As the loop is lowered toward the ground the meter reading will drop slightly. This is caused by ground effect—the loop is coupling to the earth.

surface of the ground, you may want to adjust the circuit for less sensitive operation. Turn SET control R8 completely clockwise and adjust TUNE capacitor C1 for a full-scale reading. Bring the loop close to a metal object—the meter reading should drop. If it does, the device is ready for large-object searching.

Sound monitor

While the basic circuit shown in Fig. 1 permits the most sensitivity, an audible indicator is sometimes useful. If you want to add what I call a Piggy-Back Squealer, build the circuit of Fig. 8. I used a $2\frac{3}{4}$ x 2" x $1\frac{5}{8}$ " metal box, and mounted it with a battery clip on the handle, below the meter box. You'll have to add jack J2 to the original circuit, connecting it in parallel with C9,

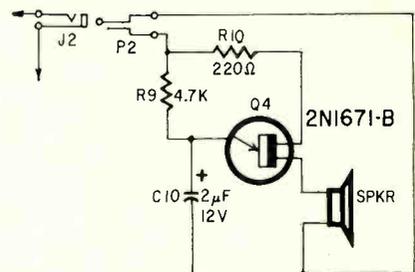


Fig. 8—A unijunction audio oscillator is the heart of the audible indicator.

Parts List for Optional Piggy-Back Squealer

- C10—2- μ F, 12-volt electrolytic capacitor
- J2, P2—Miniature two-conductor phone jack and mating plug
- Q4—2N1671B or almost any audio unijunction transistor
- R9—4700-ohm, $\frac{1}{2}$ -watt resistor
- R10—220-ohm, $\frac{1}{2}$ -watt resistor
- SPKR—miniature speaker with 8-ohm voice coil
- Misc.
- Case, wire, hardware, etc.



BUILD

Stereo Headphone Control Center



Patch your headphones to your amplifier and adjust blend, balance, bass boost and volume for better listening

By **PETER E. SUTHEIM**

STEREO HEADPHONES are great—they provide the ultimate in separation and you aren't distracted by room noise. Only trouble is they usually don't match your amplifier output. This stereo headphone control center takes care of the matching; moreover, it gives you full control of volume, bass, blend and balance. And you don't have to disconnect it to use the speakers.

The control center can be used with any stereo headset and any stereo amplifier—unless you have a very unusual headset or an amplifier.

Controls

For controls, it has a three-position selector switch: You can choose speakers only, phones only, or both at the same time. (The third choice may seem a bit strange, but it is much appreciated where one listener is hard of hearing. He can wear the phones and enjoy the music at a suitable volume level. The others can listen at a comfortable volume through the speakers.) The switch is of the shorting (make-before-break) type to reduce switching clicks.

There is, of course, a volume control for the phones, ganged so that both channels are controlled simultaneously. A balance control compensates for uneven tracking between the two sections of the volume control, and for individual differences in hearing sensitivity between the listener's ears.

The blend control corrects for the sometimes excessive stereo separation

in headphone listening. At its extreme counterclockwise position, the blend-control resistance is switched out of the circuit, allowing full separation. At the other extreme, the two channels are connected together, producing mono sound.

The bass control provides up to approximately 6 dB of boost at 40 Hz (referred to 1 kHz) to compensate for headsets whose air seal against the sides of the head is not good.

Connections

Leaving aside the convenience this box provides—which may or may not interest you—it might seem that there's a simpler way of connecting phones to an amplifier. The most obvious would be simply to connect the phones across the speaker terminals with a switch in series to turn the speakers on or off. This works, but has a couple of very serious disadvantages. First, earphones require only between

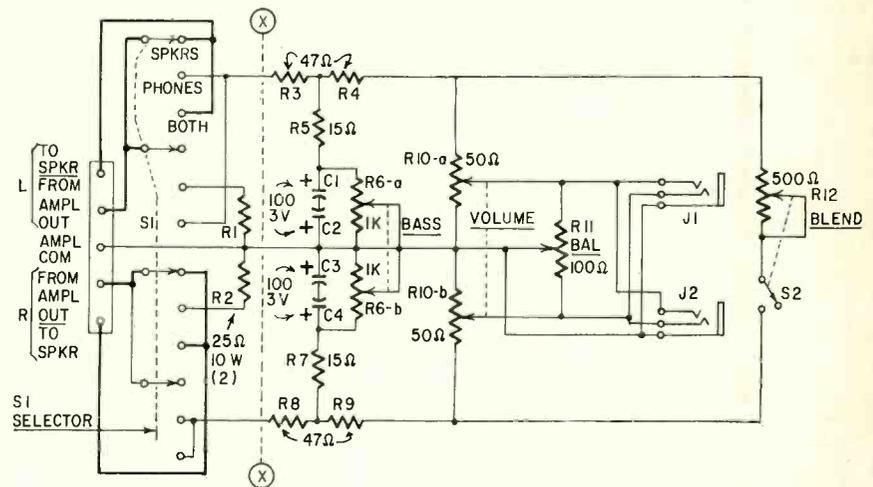


Fig. 1—Unique switching arrangement makes it possible to switch in speaker or phones only, or both. Amplifier is loaded, either by the speakers or R1 and R2.

PARTS LIST

C1, C2, C3, C4—100- μ F, 3-volt electrolytic capacitor
 J1, J2—Three-contact phone jack
 R1, R2—25-ohm, 10-watt wirewound resistor
 R3, R4, R8, R9—47-ohm, $\frac{1}{2}$ -watt resistor
 R5, R7—15-ohm, $\frac{1}{2}$ -watt resistor
 R6—Dual 1000-ohm potentiometer, log taper (Centralab, F5-1000 & R5-1000)

R10—Dual 50-ohm wirewound potentiometer
 R11—100-ohm wirewound potentiometer
 R12—500-ohm potentiometer (with S2)
 S1—4-pole, 3-position shorting-type (make-before-break) rotary switch
 S2—S.p.s.t. switch (on R12)
 Misc.—Plastic case with aluminum panel (Lafayette 99 H 6272 or similar); barrier-type terminal strip (5 terminals)

10 and 100 milliwatts for quite loud volume levels. This is in the neighborhood of one-thousandth of the power output capability of typical amplifiers.

Not only is the full amplifier power unnecessary for phones, but it can destroy them in a fraction of a second by burning out the voice coils or rupturing the diaphragms. As a result, the volume control on the amplifier can be only just barely cracked open. There has to be some way of cutting the power fed to the phones.

Furthermore, the high sensitivity of the phones results in a good bit of noise along with the music. The normal amplifier hiss and hum, usually inaudible a few inches from a speaker system, become definitely audible in high-sensitivity headphones pressed close to your ears.

The usual way of solving both problems is simple and quite satisfactory: Stick a resistance in series with each "hot" earphone wire. The value most commonly used is around 300 ohms. It cuts down the power to the phones and, of course, cuts back the noise at the same time. It also reduces the damping factor to nearly zero. But, this seems to have little audible effect on phones, which have very small, low-mass cones or diaphragms with little inertia. They are usually pretty well damped by internal absorbents and by close coupling to the ear chamber.

But a load in the vicinity of 300 ohms is almost an open circuit as far

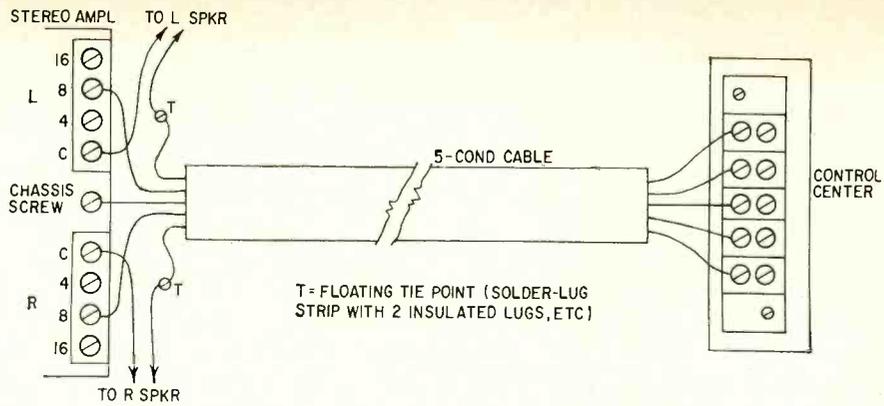


Fig. 2—To avoid undesirable power loss in the speaker wiring, don't use a cable longer than approximately 25 feet. Use impedance taps to match your speakers.

as the amplifier output is concerned. It becomes necessary then to provide a dummy load for the amplifier when the speakers are switched out. The value of the dummy load is not critical. It isn't necessary, or even desirable, to match the dummy to the amplifier output.

A considerable upward mismatch (for instance, 8-ohm output loaded by 25-ohm resistor) means much less power wasted in the dummy load as heat, since the amplifier will not usually develop nearly as much power into a 25-ohm load as it will into an 8-ohm load. This headphone box switches in a pair of 25-ohm 10-watt resistors (one for each channel) in the PHONES position of the selector only.


It might be worth while to digress for a moment to explain this matter of

protecting amplifiers with a dummy load. In general, the dummy is most important with tube amplifiers, principally because the high inductance of an unloaded output transformer can develop peak voltages during loud signals or instability high enough to break down transformer insulation or cause arcs in tubes or tube sockets. Almost any value of load resistance less than 5 or 10 times the nominal output impedance of the amplifier will load the transformer enough to prevent this type of trouble.

In transistor amplifiers, shorts across the output, rather than opens, most often cause trouble. However, it can do no harm to load the output of even a transistor amplifier in the same way. Dummy-loading may even save the output transistors if the amplifier happens to be unstable with no load. Occasionally a defective or poorly designed amplifier will oscillate with no load and damage its output transistors.

Construction

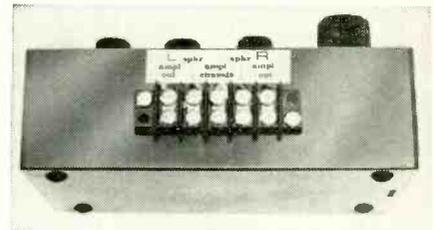
Few things could be simpler or less critical to wire than this switchbox.



Shorted output circuits in a solid-state amplifier can be destructive—use a barrier type terminal strip. Note: speaker and amplifier output terminals are shown in reversed order—follow the schematic.

The low impedances and relatively high signal levels make it unnecessary to observe any precautions about wire length, shielding, routing, and so forth. Be sure, though, to use wire no thinner

continued on page 73

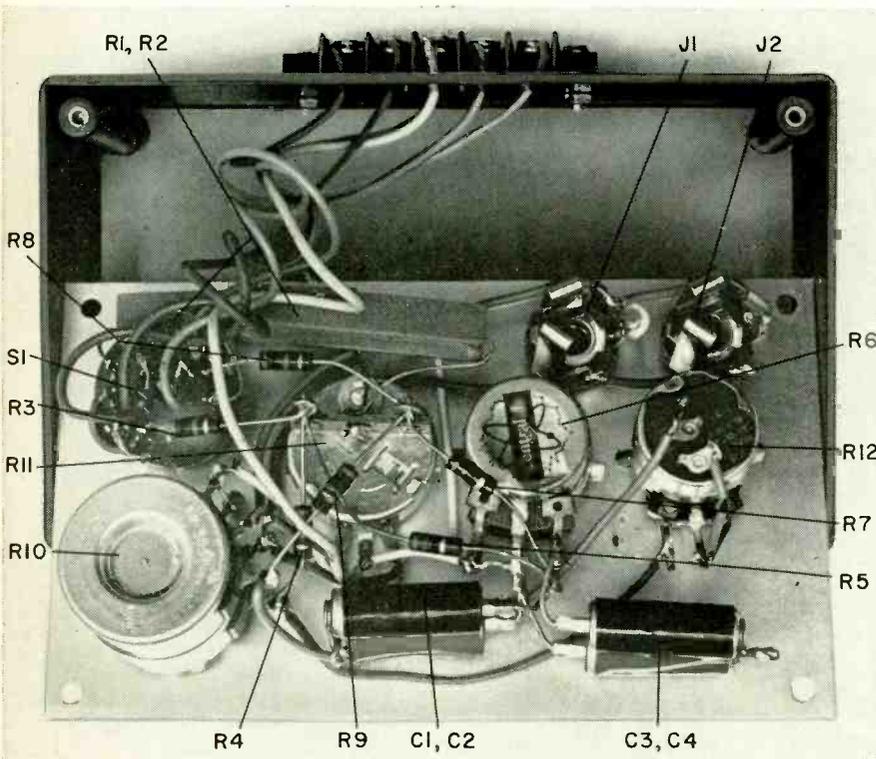

The limiting factor in parts mounting is size of the controls on the front panel. Wire position is not important; the circuit is all low impedance and high level.

SERVICING HINTS ON NEW COLOR-TV SETS

Latest techniques speed troubleshooting

By MATTHEW MANDL

TODAY'S COLOR RECEIVERS are highly superior to older models—greater signal sensitivity, more picture brilliancy, a better black-and-white picture, truer colors and improved tuners. These newer sets are also much easier to set up, and maintenance is simpler.

The innovations of just a few years ago have become regular features in most sets, including automatic degaussing, up-front convergence, simplified setup procedures, and wide-angle picture tubes. There are more solid-state components, integrated circuits, simplified customer controls and tuning indicators.

With the rare-earth phosphors, you no longer have to tolerate light gray for white, or dark gray for black, on the screen. The rectangular color tube is just about standard, showing more of the transmitted picture.

TV programming is almost all in color, and people want color sets today more than ever. This means more color business for all technicians.

In color servicing, some new techniques are called for and many old procedures should be modified to do an A-1 job. There is no question that color servicing takes longer and costs more than black-and-white. The new features, however, provide a number of short cuts which enable the service technician to do a better, faster job.

Automatic degaussing

This feature is now standard on all new color sets, thus reducing callbacks. Formerly, if a vacuum cleaner was used near the receiver, or if the set was moved, color impurities showed up on the screen and a service call was necessary. Now the automatic degausser takes care of erasing the picked-up magnetism.

This doesn't mean you can throw away your degaussing coil. You'll still need it for servicing old receivers or when an automatic degaussing system goes bad.

Basically, the system consists of coils (in either a series or parallel arrangement) mounted on a metal flange around the picture tube. A typi-

cal circuit is shown in Fig. 1, where a voltage-dependent resistor (VDR or varistor) is used with a thermistor. When the power is turned on, thermistor R2 has a high resistance and current flows through the lower-resistance coils and varistor R1. The resistance of R1 decreases as the voltage across it increases. The magnetic field set up around the coils demagnetizes the metallic components of the tube.

Some current flows through the high resistance of the thermistor to the low-voltage power-supply circuits. As the power supply draws more current, the thermistor heats and its resistance decreases, permitting even greater current flow through it. As less current flows through the varistor, its resistance increases, thus helping to route all current to the power supply and none through the degaussing coils. (In some systems a thermal switch is used instead of the varistor.)

If one of the degaussing coils or the varistor opens, your degaussing job during a service call will be temporary and callbacks will be necessary. If the thermistor opens, it will cut off the low-voltage supply and kill reception.

Quick check for an open condition: turn the set on and get a black-and-white picture; then use your degaussing coil to magnetize screen areas deliberately. This can be done by placing the degaussing coil against the tube face *while energized*, then releasing the degaussing switch while the coil is *still at the tube face*. The collapsing field resulting when current is shut off produces a dc component which magne-

tizes. (This is why the normal procedure is to keep the coil energized and back away about 6 feet before shutting it off.) Colored areas will appear on the screen and should be quite evident on a b-w picture (or raster).

Now turn the set off and wait 5 minutes or so for the thermistor to cool. Turn the set on and see if the color areas are still visible. If they are, the degaussing circuit is defective or sluggish. (There's insufficient current through the coils or they're intermittent.) If a coil replacement is necessary, make sure you position the new one the same as the old one (so it will be effective over the same area). Use exact replacements for the varistor and thermistor to assure proper resistance values during their hot and cold states.

Other VDR uses

Voltage-dependent resistors are found in several circuits of the new color sets. RCA uses one in many of their late color receivers to stabilize vertical scanning. Have you ever set the raster height just above and below the picture-tube mask, only to find later that the picture seems to have shrunk? Often line-voltage variations cause this. Increased voltage stretches the raster; decreased voltage shrinks it. A VDR takes care of this problem in the circuit of Fig. 2.

The grid bias for the vertical output tube is determined by the setting of the HEIGHT control. For normal operation, the cathode is 50/60 volts

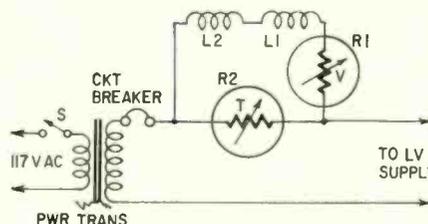


Fig. 1—The usual automatic-degaussing circuit used in a modern color-TV set.

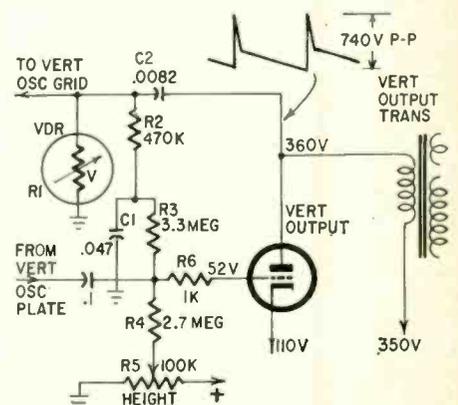


Fig. 2—RCA color chassis (right) uses a VDR to stabilize vertical scanning.

more positive than the grid. The grid bias is developed by a B+ voltage divider consisting of R1, R2, R3 and R4 fed from the arm of HEIGHT control R5. Picture height is stabilized against changes in ac line and B+ voltages by the action of the voltage-dependent resistor (R1).

During each scanning period, the high-amplitude positive-going retrace pulse charges C2 with a negative potential on the plate connected to the VDR. The time constant of C2's charging path is very short, while its discharge time constant is long. Thus, C2 maintains its charge for a period longer than the vertical sweep interval. This negative charge determines the effective value of R1.

If the amplitude of the retrace pulse increases, the higher charge on C2 causes the VDR's resistance to drop. This brings the tube's grid closer to ground, effectively increasing the bias and reducing the gain to restore the amplitude of the vertical output pulse to normal.

Conversely, if the sweep amplitude drops, due to a weak tube or low line or B+ voltage, the VDR's resistance increases. This makes the grid more positive, so the tube's plate current increases and compensates for the loss in height which would otherwise occur.

RCA also uses a VDR to stabilize the focus voltage. As with the vertical circuit, a self-stabilizing function prevails as long as the VDR is not defective. Zenith, Philco, Silvertone and others also use a VDR in their horizontal and high-voltage systems for regulation.

Reducing no-charge callbacks

If you have to go back to a customer's home to replace a defective tube you've installed just a few weeks ago, don't blame the tube manufacturer. Maybe you overlooked some basic facts of life in troubleshooting modern color sets.

Not only is tube replacement what you do the most of, the horizontal and high-voltage systems are often highest on the list of offenders. The reason, of course, is the complexity of these stages, particularly in modern color receivers. There are horizontal-sweep, high-voltage, boost, shunt-regulator, focus-rectifier and damper functions. Add pincushion correction and you have an imposing array of electronic units which can go bad!

It's one thing when troubles develop of their own accord, and quite another when you unconsciously cause them by your service procedure. Then you're in for "no-charge" callbacks.

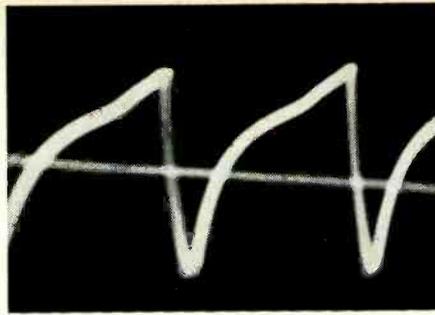


Fig. 3—Horizontal-output grid waveform dip shows nonlinearity due to improper bias. A result can be short tube life.

With the higher voltages used in the new color sets, you must *not* replace a defective horizontal-output tube unless you are sure the horizontal-oscillator section is operating properly. Otherwise, the new output tube may last only a few months, weeks, or even a few hours!

Examine horizontal output circuits and you'll find—in almost all cases—the cathode of the horizontal output tube at ground. The specified dc grid voltage, however, may range from a low of -40 to as high as -70 . Since the cathode is grounded, the bias is obviously obtained from the horizontal oscillator system.

In normal operation, the horizontal output tube has a plate dissipation around 15 watts. Decrease negative bias at the grid and plate dissipation shoots up rapidly: it may even exceed 100 watts! If the drive signal is excessively low, the increased plate dissipation may cause the circuit breaker to open or the fuse to blow.

When grid drive is only slightly low, however, plate current may not be high enough to trip the breaker. In this case, the increased plate dissipation overloads the tube and materially shortens its life, causing callbacks.

Some technicians replace both the

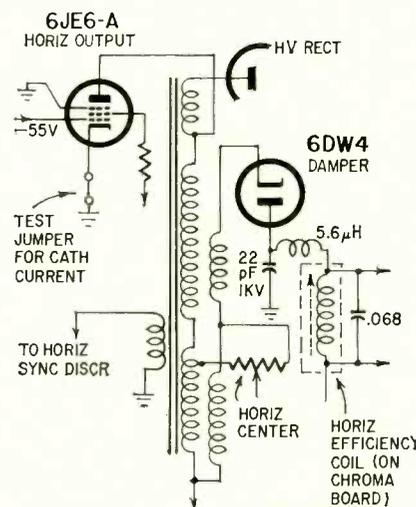


Fig. 4—Silvertone 7190 series chassis.

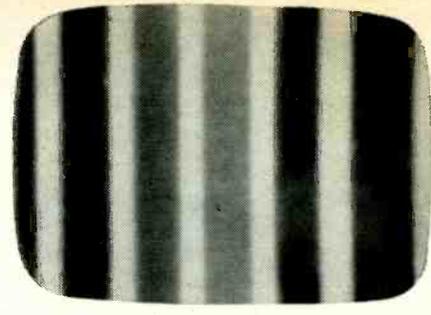


Fig. 5—Result of misadjusted or defective blue-shaping coil. Note thickening of the bars on right. They should be linear.

horizontal oscillator and the output tube when they find only the output tube bad. Even if you do this, measure the dc grid voltage and be sure it's correct. Also, look at the grid waveform with a scope and compare it with what the service notes show. The waveform of Fig. 3 for instance, indicates sweep distortion because there is a dip near the top of each sawtooth, which affects linearity on the right of the screen.

Efficiency-coil adjustment

If misadjusted, this coil can shorten the life of a horizontal-output tube by increasing its plate dissipation. Thus, a chassis that goes rapidly through flybacks calls for a readjustment of the efficiency coil if the horizontal oscillator system checks out all right. For proper adjustments it is necessary to read cathode current in the output tube, and many color receivers have a removable jumper or link for opening this circuit, as shown in Fig. 4.

You'll usually find the efficiency coil on the chroma board. Adjust the core slug for a dip in cathode current, as read on a milliammeter in the cathode circuit. After you've reached the lowest current point, gradually adjust the slug and raise current by approximately 10 mA (or the value specified by the manufacturer). Never permit the minimum cathode current to exceed the level specified by the set manufacturer. Then set the brightness control at minimum and adjust high voltage to 25 kV (or as specified in the service notes). Make sure your vtvm and high-voltage probe are accurately calibrated.

Blue shaping coil

Despite its name, this is *not* a convergence coil. If this coil is improperly set it will not only damage the output tube, but will cause horizontal nonlinearity. A vertical bar pattern indicates this trouble by a thickening of the right-hand bars, as shown in Fig. 5.

(continued on page 91)

Rotary Stepping Switches — They're Everywhere

Part 1—How they work and what you should know about them

By TOM JASKI

EVERY TIME YOU DIAL A TELEPHONE, YOU activate nearly a dozen electromechanical devices whose functions you probably have never figured out clearly. The voltage pulses produced by an interrupter switch, in the telephone base, travel through the phone line to the nearest central office. At this office, the call is routed by the actions of a series of rotary stepping switches.* These switches perform jobs that would take many relays, and they do these jobs faster and occupy less space than relays do.

Wired a certain way, steppers can perform the same operations over and over again. They provide complete isolation between controlling and controlled circuits. These desirable characteristics are two of the reasons telephone systems still use steppers. Other uses: remote control of radio and TV transmitters; counting items on a factory production line; selecting circuits for monitoring gas pressure, liquid volume, heat and cold, and similar measurements in factories and warehouses.


Abundantly available in surplus for some years now, rotary stepping switches were used as *line finders* in early automatic telephone exchanges. In association with Strowger switches† (two-motion, 100-point switches) they have, since 1918, carried literally billions of signals.

Cams


Apart from the Strowger switch, there are four basic types of rotary stepping switches (or rotary stepping relays, as they are sometimes called). First, there is the pawl-driven relay, with cams which open and close contacts. The top photo shows one example. Each set of contacts is completely separate from the others. Regular relay-type contacts and springs are used in any assortment that is normally used on re-

*A few newer central offices use crossbar or solid-state message routing. Most US telephone systems, however, still use stepping switches.

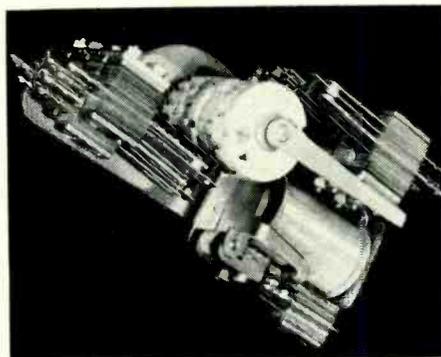
† Strowger switches are not discussed here.



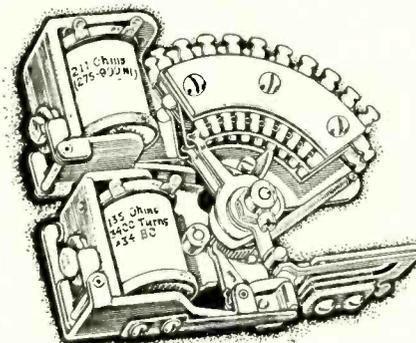A cam-operated relay with 36 separate steps per cam and 3 banks of switches.



The minor switch has a motor and a release magnet, and a maximum of 10 steps.

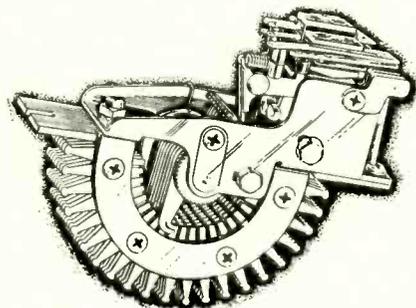

This 22-point rotary switch has 6 contact levels and a set of interrupter springs.

lays. Cams are available with up to 36 intervals. For each revolution of the shaft, the contacts can be opened or closed as much as 36 times.

In addition to *working* contacts, some rotaries use *off-normal* and *self-interrupter* contacts. *Off-normal* contacts are actually a form of reset. They are operated by a separate cam, only *once* per revolution, and only when the switch has been stepped away from a rest or "home" position.

Self-interrupter contacts are made for the heavy duty of interrupting the motor-magnet current without excessive arcing. They are operated by the armature directly, in the off position. Thus, if the current is supplied to the magnet through the interrupter, the coil will energize, open the contact, de-energize, close the contact, and so on. The rate of self-interrupted operation is limited by the mechanical inertia of the moving parts, and is often further decreased by external circuitry.

The working contacts on this stepper are limited to three stacks, and the relay is not particularly suited to such operations as selection. It is designed for sequential operation where only a few contacts are needed.

The driving mechanism for this relay, as for other stepping switches, can be either *direct* (the motor magnet operates the pawl directly) or *indirect* (the magnet charges a spring which operates the pawl when the coil de-energizes). The indirect drive is more reliable, for each stroke is exactly the same as the one before—even if the coil current varies, and provided the relay operates at all.

Single wipers

The second type of stepping switch (center illustration) has been used for some time in telephone work. It's called a *minor* switch, because it is often used with a Strowger, or *major*, switch. The one shown is directly driven. Its shaft is driven by a pawl and ratchet, which are driven in turn by the motor-magnet armature. The shaft carries fingers which wipe across 10 contacts in each layer or *bank*. A minor switch may carry as many as 6 banks of contacts.

In this type of switch, the dog that holds the ratchet is not fixed, but is at-

ROTARY STEPPING SWITCHES


tached to another arm. This arm can be operated by a second magnet, the *release* magnet. When energized, the release magnet causes the dog to be lifted from the ratchet, and a return spring pulls the contact wipers back to "home" position. Note the off-normal contacts operated by the roller cam on the shaft. A self-interrupter, if used, would be operated by the motor-magnet armature directly.

Double wipers


The third and older type of rotary switch (bottom picture page 39) has a double set of wipers. By continuous rotation, one wiper from a set always touches at least one contact. There's no return mechanism; to get to the starting position, the switch must be stepped *forward* to "home." As in previous examples, off-normal contacts and a self-interrupter can be used here. The switch can accommodate up to 6 banks of 22 contacts. Wipers can be so connected and adjusted that 2 banks can be scanned sequentially. Thus the switch can have 44 contacts in 3 levels.

A modern version of this kind of rotary switch is the Automatic Electric type 45 (see photo). This is an indirectly driven switch with 25 contacts per bank; a maximum of 10 banks per switch can be used. The contact banks are removable so that as few as are needed can be used. In addition, the wipers can be arranged so that instead of 10 levels of 25 contacts there are 5 levels of 50 contacts.

Photo at right shows two compact rotary stepping switches, the Automatic Electric types 40 and 80. These are also indirectly driven. The contacts are mounted in a 120° arc, and each set of wipers has three parts. Continuous scanning of 10, 20, or 30 contacts is thus possible. The type 40 has a maximum of 6 levels, and the type 80 has 10. These switches are very compact, the 40 requiring hardly more space than an

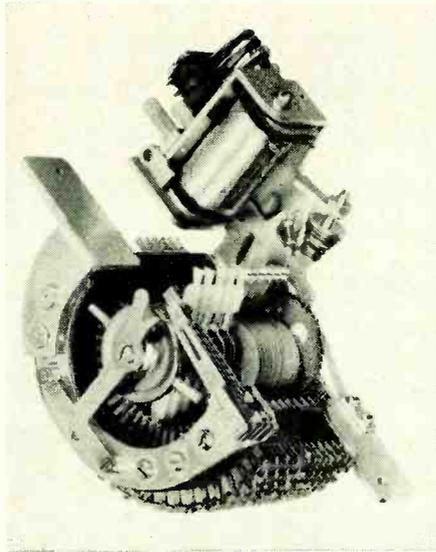

The Automatic Electric type 45 switch.

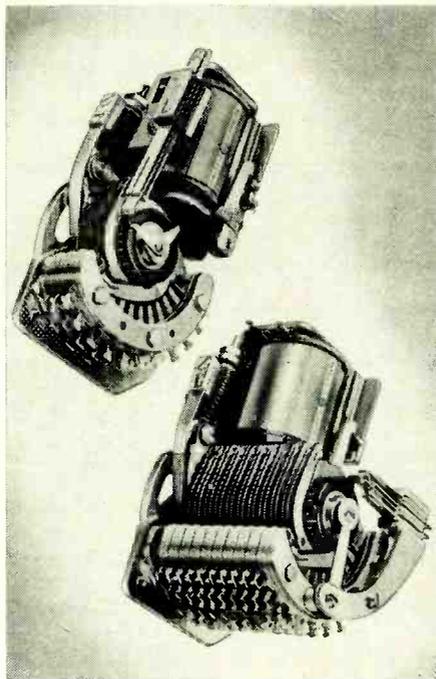

Compact steppers with 11 contacts each.


ordinary telephone relay. Various types of contacts are available—shorting, nonshorting, gold-plated, etc. So are different coil voltages. Note again the off-normal contacts and also the arm on the coil armature. This arm can be used to operate interrupter contacts.

A different type of construction is used in the Ledex rotary solenoid (see photo): the contacts are mounted on conventional rotary-switch wafers. The switch operates as follows: The armature has a collar with three sloped ball races; the housing has three corresponding ball races. The armature collar rides on these balls, and a spring rotates the armature so each ball rests in the shallowest part of its race; this is with the coil not energized and with the armature as far out of the coil as possible. When the coil is energized, the armature is pulled into the coil. This causes the armature to rotate against the spring. Rotation is 30° for each step. An index mechanism prevents the shaft from returning with the armature. On the original Ledex switches, standard switch wafers were used, and these are the kind found in surplus stores. Later models (see photo below) use relay contacts for greater reliability and heavy-duty switching.


Switch diagrams and circuits

When considering control diagrams for rotary switches, it does not matter which type of switch is used (excepting the minor switch) so long as there are sufficient contacts. Otherwise, switches differ mainly in the amount of current required for operation and in the current their contacts will carry.

Fig. 1 contains both telephone and industrial symbols for the steppers, relays and associated components in the control diagrams that follow. Industrial symbols are used for simplicity, but telephone-type symbols are also shown to permit comparing these diagrams with those of manufacturers. For those

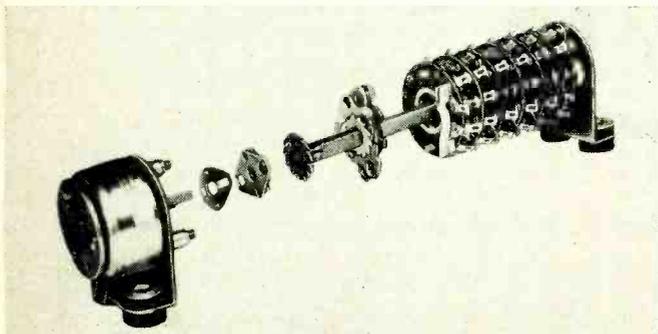


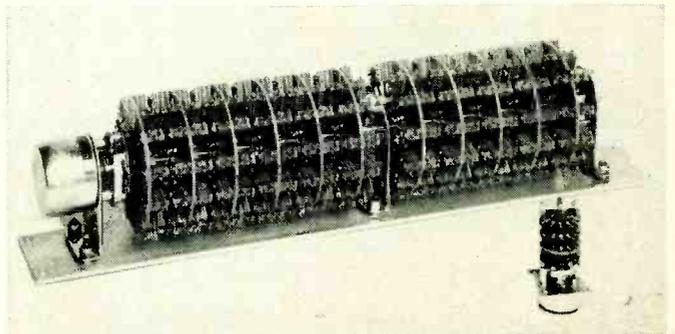Conventional switch wafers are used in this rotary stepper.



Ledex rotary switch uses relay contacts for heavy duty.

WOOFING THE TWEETER

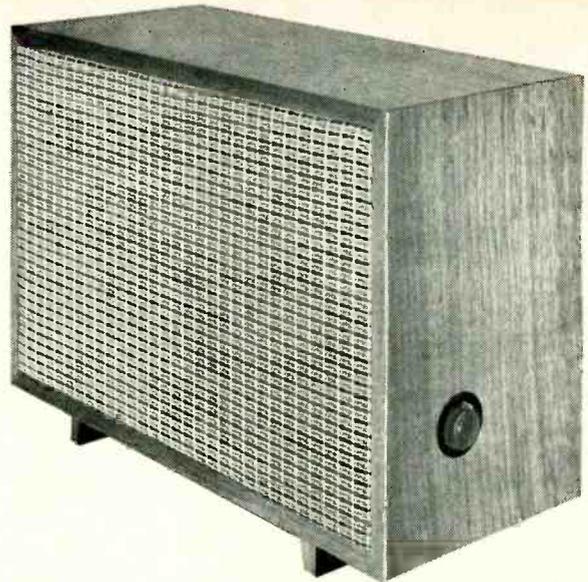

How to get more bass out of small speakers

By JIM McCORMICK

SMALL SPEAKERS ARE INCONSISTENT. They are efficient or inefficient, depending on frequency. Low-frequency response is limited and their response is often closer to a tweeter than a woofer. I decided to make one inefficient and bring up its lows for better performance. It was a 4-inch extension speaker in a tiny cabinet. The cabinet was stuffed in an effort to kill (or at least badly cripple) resonance. The efficiency of the cone, which tapered upward with frequency, was slapped back down by an electronic taper in reverse.

Plugged into a cheap radio set, the little loafer turned out to be a honey. Out came the deep natural sounds of the gut bucket, the tuba, and Senator Dirksen. And even when volume was reduced to a barely audible level, the lows were still there.

How often do you listen to the hi-fi rig? How much more time than that do you spend listening to small speakers horribly enclosed in table-model radio and TV sets? With nary a tone control to mitigate your misery? To give your ears a break, install a closed-circuit jack at the rear of each of these sets so you can plug in this inexpensive (but properly enclosed) extension speaker.

Before you choose the speaker, consider the volume you will require. Maximum volume in a low-cost speaker, before the onset of distortion, is determined roughly by cone size. For strictly personal listening, choose any size from an 8-ohm earphone up; for family listening, 5 to 8 inches.

Fig. 1 shows the woofing treatment. C1 and C2 are 300- μ F electrolytics, back to back. Diodes D1 and D2 pump up a dc potential to keep the dielectric formed. The resulting 150 μ F is used to shunt the speaker. At 50 Hz, where the cone's air coupling is poor indeed, the capacitive reactance is about 21 ohms, a not-too-severe shunt across an 8-ohm

voice coil. The efficiency of the cone's coupling rises rapidly with increasing frequency, but so does the severity of the capacitive shunt: 10.5 ohms at 100 Hz, 2.1 at 500 Hz, 0.21 ohms at 5,000, etc.

Obviously, the highest frequencies are about to be chopped off completely—or nearly so—which is the reason for R. Pure resistance is tone-deaf. R is a window through which all frequencies can reach the voice coil. If the window is opened wide enough to admit voice sibilants, you may be sure it is also open to all frequencies up to and beyond the lim-

it of audibility. In practice, R is adjusted to suit the nature of the amplifier and of the input material.

Magnet and capacitors join forces to damp the voice coil at middle and upper frequencies, just as the secondary of the output transformer and the magnet do at the lowest frequencies. This damping helps to keep the speaker from adding color of its own to the input material. You will appreciate this characteristic in the clarity of speaking and singing voices.

The woodworker who builds his own enclosure can write his own ticket. He can, for instance, enclose two 4-ohm speakers and connect them in series for the 8-ohm total. He will get better dispersion of directional highs because of the double source. Or he could use an 8-incher and four tiny tweeters. The tweeters (used because of cone and voice-coil inertia) need handle only the highest frequencies.

You cats who don't dig all this low-level stuff and want to enclose a large speaker—or a multiple array of small ones to get window-rattling volume—may as well forget the "woofing" business. You have enough cone area to get good bass output anyway.

If you happen to lack shop facilities, and are willing to pay for relief from ear torture, you can get help from your neighborhood service tech. He will find a way to install a closed-circuit jack in your miserable-sounding radio or TV set. (Resourceful, these men.) He will also order the extension speaker you choose. Give him this story and, when the speaker arrives, he will install the "woofing" parts and wiring.

The speaker pictured had a 20-ohm pot for a volume control. This was removed and a 3-ohm pad mounted in its place. A new knob with setscrew replaced the push-on knob. The capacitors are

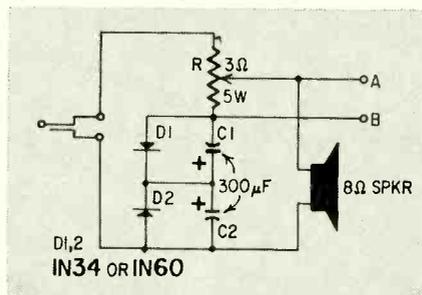


Fig. 1. Circuit rolls off the highs, but enclosure smoothens out the bass response.

Parts List	
C1, C2	300- μ F, 6-volt electrolytic capacitor (Sprague TE-1106, or similar)
D1, D2	Germanium diode (1N34, 1N60, or what have you?)
R	3-ohm, 5-watt potentiometer (Malloy VW3, or similar)
Misc.	One 8-ohm, fully enclosed speaker; plug and cord; closed-circuit jack; slab of 1-inch foam rubber; knob, etc.


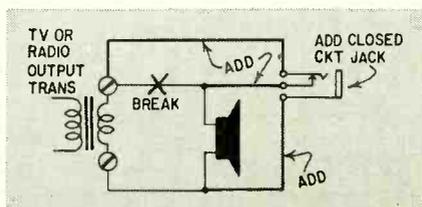


Fig. 2. Closed-circuit jack connected as shown lets you plug in another speaker.

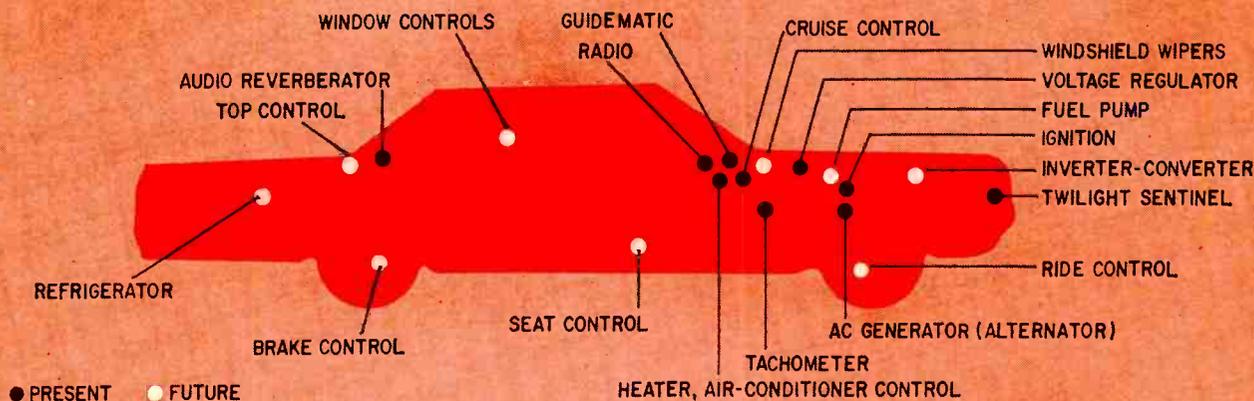

ELECTRONICS IN THE MODERN AUTO

Each year cars become more electronic. Now they're using silicon controlled rectifiers, Zener diodes and integrated circuits. From ignition to voltage regulation, more tasks are being done by semiconductors
By FRED W. HOLDER

DURING THE YEARS BETWEEN 1940 and 1960, the annual output of American auto manufacturers increased 3 million units with only minor changes in the basic automotive electrical system. Since 1960 production has risen another 3 million units. But now change is the rule rather than the exception.

The electrical system in a modern American car incorporates a broad range of electronic circuits. Most of these make extensive use of one or more semiconductor devices. Transistors, silicon controlled rectifiers (SCR's), integrated circuits (IC's) and other solid-state components give more snap to ignition systems, better-regulated alternator outputs, auto-dimming headlights and hi-fi stereo on the highway. Today's auto mechanic must be part electronic technician to repair electrical systems effectively. Table I lists several additions available either as standard equipment or as factory options on new cars.

Ready availability of low-cost semiconductors spurs accelerated application of electronic circuits to automobiles. Table II gives you some idea just how many semiconductors presently are used in GM cars; for instance, the total of all types listed ranges from 119 to 129 individual solid-state components in available options.

According to one industry report, United States automakers spent nearly \$20 million on semiconductors in 1963; by 1975 they will purchase about \$55 million annually. The same report suggests that automobile manufacturers may replace computer manufacturers as the leading consumers of semiconductor devices. With the average price of automotive semiconductors about 25 cents, it's easy to see what widespread impact car-borne electronic circuitry will have on the continued good health of semiconductor manufacturers.

The semiconductor diode, with its small size and high current-carrying capability, has helped alternators replace generators. The transistor gave us a hotter ignition system and a better voltage regulator, to say nothing of more compact radios and stereo tape decks. Now, with lower prices for SCR's and IC's even greater things are in store.

Alternators	Transistorized Burglar Alarms
Solid-state Voltage Regulators	Warning Devices (Overspeed, Lights Out, etc.)
Transistor Ignition Systems	Speed Controls
Capacitance-discharge Ignition Systems	Automatic Climate Controls
Photoelectric Headlight Controls	Transistorized Radio Receivers and Transmitters
Lights-off Delay Circuits	Transistorized Stereo Tape Systems

TABLE I. Automotive Electronic Features

Voltage regulators

In 1963, American Motors installed the first solid-state voltage regulator in its cars. This regulator was built by Motorola. Currently, American Motors, the Pontiac Division of GM, and Kaiser Jeep are the only manufacturers furnishing solid-state regulators as standard equipment. The prime advantage of this new breed of regulators is their nonmechanical switching of the alternator's field-current

Item	Rectifiers	Low-Power Diode	Zener Diode	Thyristor	Transistors			Thermistor
					Low Power	Medium Power	High Power	
Alternator	6							
Voltage Regulator			1			1	1	1
Guidematic		1			4-6			
Twilight Sentinel		2			2			
Electrocruise		1				1		
Comfortron		1			1	1		3
C-D Ignition		8	1	1	4	1		
AM Car Radio		3			5-7		1	
AM/FM Car Radio		8	1		10-12		1	
AM/FM/Stereo Car Radio		12	2		20-24		2	
Delco Stereo Tape Player		2			8		2	

TABLE II. Quantities and Types of Semiconductors Used in GM Automobiles



GM's Guide-Matic solid-state headlight dimmer (right) replaces vacuum-tube unit.

supply. The solid-state regulator functions as an electronically controlled, solid-state switch.

A simplified version of the Motorola voltage-regulator circuit used on 1967 Rambler American cars is shown in Fig. 1. When voltage at the alternator output terminal rises higher than 14.4, Zener diode D1 conducts to supply current to the base of Q1. Transistor Q1 turns on and reverse-biases Q2, which turns off the current supplied to the alternator field winding. When alternator output falls below 14.4 volts, the Zener diode stops conduction, Q1 turns off, and Q2 allows current to flow once again through the alternator field coil. This switching action of transistor Q2 occurs many times a second. Because the switching rate is high, no variation can be detected in the alternator output.

Thermistor R4 is a temperature-compensating resistor, the resistance of which varies with temperature to control the operating point of the Zener diode. This compensation produces a higher system voltage in cold weather, when needed, and a lower system voltage in warm weather.

In 1968, an integrated circuit similar to that shown in Fig. 2 will likely be used on most Ford and Chrysler models. This IC version will be similar to an earlier transistor regulator, except that a Darlington-type output will be used instead of the more conventional cascaded circuit. The current-carrying capacity of the circuit should be high enough to meet the expected increasing electrical load in autos for the next 5 years.

In the circuit shown, R5 and C1 set the basic operating frequency, allowing the system to be pulse-width-modulated for continuous control.

Ford and Chrysler probably will use a modified TO-3 package in their regulator. The unit most likely will be mounted directly to the alternator in the form of a block measuring 1.8" x 1.8" x 0.4". This arrangement, with the block bolted flat against a machined surface on the alternator housing, will permit the housing to serve as a heat sink.

Delco-Remy, a subsidiary corporation of GM, is making a similar IC voltage regulator for heavy-duty trucks, coaches and off-road equipment. The Delco regulator is expected to appear on the 1968 models of GMC trucks. A 5-year design life is planned for these first automotive IC

devices. By 1973, auto electrical systems are scheduled for conversion to 24 volts, and a new generation of regulators having greatly increased capacity will replace the first IC regulators.

Ignition systems

The next element of the auto to benefit from modern electronics technology will be the ignition system. Ford already has developed two static systems, using discrete germanium components. One of these, a contact-actuated transistor system, has been offered as an option since 1963. The other, a variable-coupling contactless system, may be offered on 1968 models. GM has had a contactless transistor system available as an option since 1964.

Roughly 150 to 200 different commercial transistor ignition systems are on the market at present. In all of them, a high current is furnished—through one or more power transistors—to the primary of the ignition coil during the time the contact points are closed. When the points open, the transistors turn off. A high voltage results from the rapidly collapsing magnetic field around the coil. A diode arrangement of one type or another is used to protect the transistors against damage from high inverse-voltage spikes.

Except for the method of triggering the transistors, contactless systems function in the same manner. In contactless systems, one of two methods generates the triggering pulse needed to turn off the power transistors: (1) in-

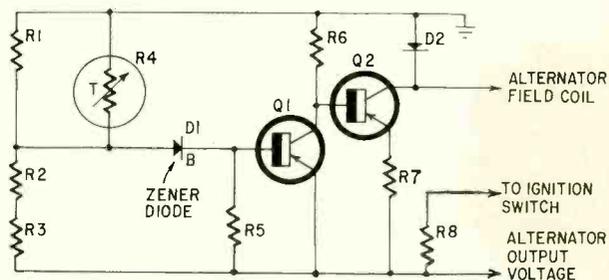


Fig. 1—Solid-state voltage regulator used by Rambler.

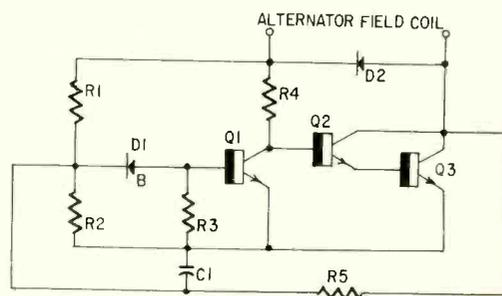


Fig. 2—IC voltage regulator for Ford and Chrysler.

interrupting or disturbing a magnetic field and (2) photoelectric methods.

Prices of these transistor ignition systems range between \$30 and \$100 or more. This places them beyond the point where they'd be economically feasible for standard use by the automotive industry. Consequently, transistor ignition systems have never progressed beyond option status. A breakthrough in pricing SCR's announced by a major supplier, however, will permit automakers to use these highly reliable switches. This suggests that some ignition

systems in 1968 or 1969 autos may use a form of capacitance-discharge (C-D) system similar to that available as a factory option on the 1967 Pontiac and Oldsmobile.

The Delco-Remy C-D ignition unit receives its timing impulse from a magnetic velocity pickup mounted inside the distributor. The pulse obtained has a consistent shape and duration and is well suited for triggering the voltage converter and thyristor. The power-supply circuit develops 300 volts dc to charge a storage capacitor.

During normal operation, the power-supply circuit functions as a one-shot converter circuit, pulsed "on" by the timing circuit and "off" by transformer saturation. During cranking, however, the circuit operates in the free-running mode to supply a full 300 volts dc to charge the capacitor, even when battery voltage falls as low as 4 volts.

This change in mode insures a full 30 kV at the spark-plugs over the entire operating range of speed and supply voltage. The switching circuit stores the 300-volt charge in the capacitor until a timing signal triggers the circuit, which then discharges the capacitor through the ignition coil. In this circuit, peak voltage is reached in 35 μ sec rather than the 125 μ sec required in the standard system; spark duration is reduced from 1200 to 200 μ sec.

Headlamp Controls

Several are commercially available. For example, the Guide Lamp Division of GM manufactures two electronic controls for automobile headlamps: the Guide-Matic electronic headlamp beam control and the Twilight Sentinel automatic light switch.

The Guide-Matic, an automatic dimmer, is completely self-contained in a satin-finish sensor small enough to be

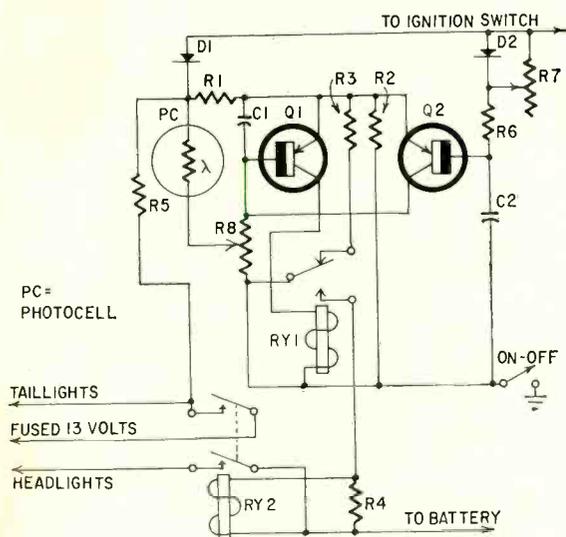


Fig. 3—Headlights are turned on automatically in near darkness by the Twilight Sentinel made by GMC Guide Lamp.

held easily in one hand (see photo). All components are hermetically sealed into the sensor, which is usually mounted on the cowl in front of the windshield. A second version mounts behind the front grille of the Cadillac. The new sensor replaces the Guide's previous headlight beam control, a much larger unit.

The Twilight Sentinel, an automatic "lights-on" switch, provides automatic turn on as well as a time-delayed turn off for automobile headlamps and taillights (see Fig. 3). When the light level on the photocell is reduced to 15

foot-candles (or any other preset value), photoresistance increases to drive transistor Q1 into conduction, energizing sensitive relay RY1. The normally open contacts of RY1 close, energizing the coil of power relay RY2. Full battery voltage is supplied to the headlights and taillights through the armature of RY2.

The positive charge on C2 reverse-biases the base of Q2, holding Q2 cut off. When the ignition switch is turned off, the ignition-switch terminal is at ground potential because of the various components in the car that are connected between this point and ground. The car lights remain on because the circuit receives operation voltage through resistor R5 from the taillight circuit. Capacitor C2 then discharges through resistor R6 and rheostat R7.

The turn-off time delay is a function of the time constant of this RC circuit. When the base of Q2 approaches ground potential, Q2 conducts to supply a current flow through sensitivity control R8. The base voltage of Q1 will then increase enough to turn off Q1 and release the sensitive relay, which turns off the car's lights and removes all voltage from the system. A back-up lamp option is also available with this circuit.

Automatic environment controls

In 1964, Cadillac introduced their Comfort Control system. This was the first automatic heater and air-conditioner system mass-produced for use in an automobile. In 1967, Ford Motor Company purchased a large number of the newly developed Bendix temperature-control system, called the Autonic control.

The Cadillac system uses a combination of electronic and vacuum controls to maintain the air temperature inside

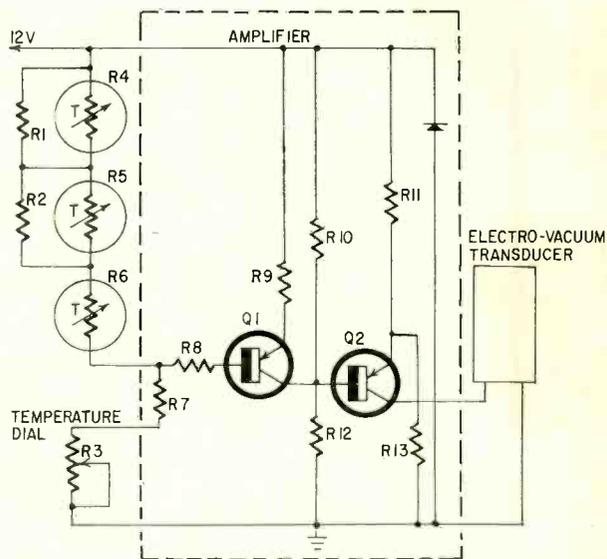


Fig. 4—Both temperature and air circulation in car are controlled by this Comfort Control circuit used by Cadillac.


at a preset level. Except during extremely hot or cold outside temperatures, both heater and air conditioner are used to hold the air temperature within the car at the desired level. A thermistor sensing network and amplifier circuit (see Fig. 4) controls an electrovacuum transducer. The transducer, in turn, controls a vacuum-operated servo motor. The servo actuates whatever components are needed to condition the air and also controls the blower motor to increase or decrease air flow as necessary.

continued on page 87

sell resist-
on, ener-
Batt-
ights
pf

**“Get more
education
or
get out of
electronics
...that’s my advice.”**



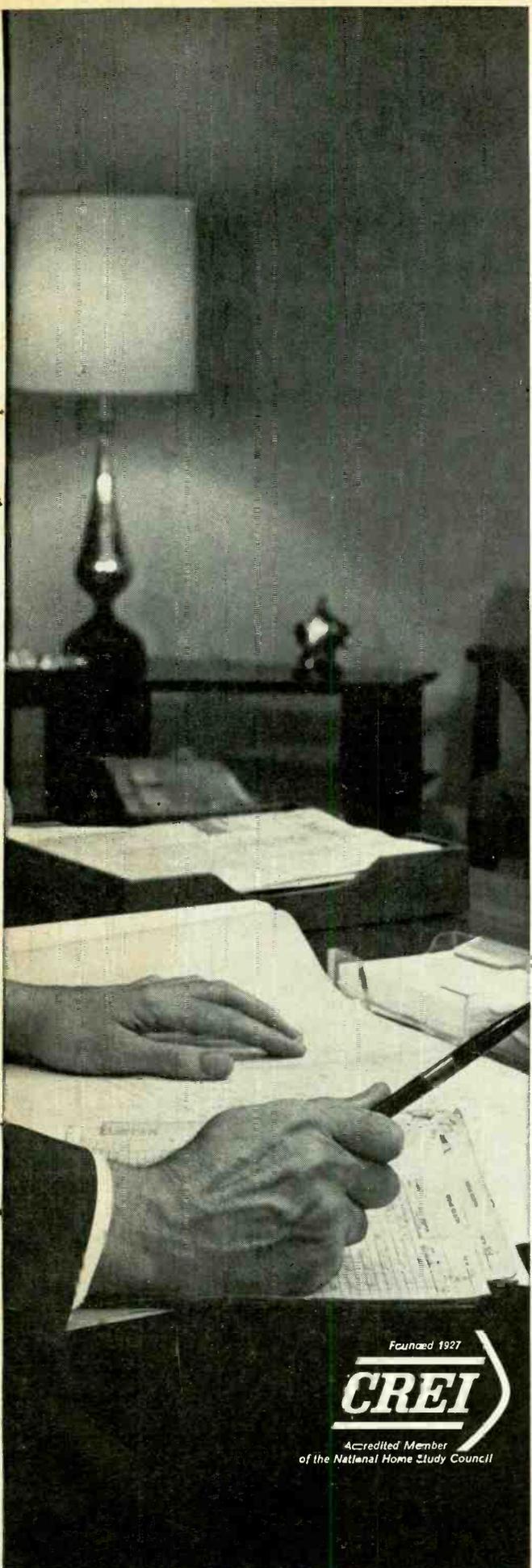

Founded 1927
CREI
 Accredited Member
 of the National Home Study Council

Ask any man who really knows the electronics industry.

Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff.

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Air-mail postpaid card for your copy. If card is detached, use coupon below or write: CREI, Dept. 1411-E, 3224 Sixteenth Street, N.W., Washington, D.C. 20010.



The Capitol Radio Engineering Institute
 A Division of McGraw-Hill, Inc.
 Dept. 1411-E, 3224 Sixteenth Street, N.W.
 Washington, D.C. 20010

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

EMPLOYED BY _____

TYPE OF PRESENT WORK _____ G.I. BILL

I am interested in Electronic Engineering Technology
 Space Electronics Nuclear Engineering Technology
 Industrial Electronics for Automation
 Computer Systems Technology

APPROVED FOR TRAINING UNDER NEW G.I. BILL

BUILD DUMMY LOAD AND RF METER

Check your transmitter without cluttering the airways

By E. F. RICE and ANDREW MUELLER*

TUNING OR TESTING a transmitter is much easier when you use a dummy load. Here is a device that serves as a dummy and a power-output meter for rigs up to 100 watts. Most CB and commercial-band two-way FM transmitters are designed to work into a 52-ohm antenna. This dummy load is a 50-ohm noninductive resistor, made up of 30 carbon resistors, each 1,500 ohms, 2 watts. They are connected in parallel and will dissipate 60 watts continuously or 100 watts intermittently.

Fig. 1 and the photo show how the resistors are mounted by soldering them in holes. Drill the holes in a pair of metal discs 2½ inches in diameter cut from No. 18 copper of the type used for flashing on roofs. Before assembling, tin the flange on the coax connector and also the area around the ⅝-inch hole in the copper disc so that the two pieces can be easily sweated together with a heavy soldering iron. After this is done the resistors can be soldered in place. Be careful not to overheat the disc or the resistors. Use heat-sink pliers on resistor leads.

The parts are mounted in a 6 x 5 x 4-inch aluminum box with the range switch on top. The power-output meter and the coax connector are opposite each other on the 5 x 4-inch ends. The photo shows parts location; wiring is not critical.

How it works

The schematic (Fig. 2) shows the 30 2-watt resistors as a single resistor, R1, across the input terminals. Voltage divider R2 and R3, across R1, lets a small part of the applied rf voltage get to D1, where it is rectified and filtered. The resulting dc is proportional to the input-signal power and is applied to the meter through the range switch and multipliers R4 and R5. R6 and R7 are calibration pots for the 10-watt and 100-watt ranges, re-



spectively. C2 bypasses the meter for rf and gives extra filtering.

Calibration

First disassemble the meter so that you can add the additional scale shown in the photo. The original 50- μ A scale is still on the meter face in the picture to help you determine the relative positions of the new marks. Notice that the new scale is not linear; power increases as the *square* of the current. The new marks can be made lightly with a pencil and the job completed with a lettering pen and India

ink. Practice on scrap paper first.

The ideal way to calibrate this instrument is by comparing its readings against those of a highly accurate rf wattmeter. If you haven't access to such a device, however, here's a reasonably accurate method: You will need the use of a transmitter with a 50-ohm output, a service-type vtvm, and an rf detector probe. The probe must be the type furnished by the vtvm manufacturer for that specific instrument. Representative models are the EICO 232 or 221, Hickok 470A, RCA WV-77E or WV-98C, Simpson 312, and Triplett 850.

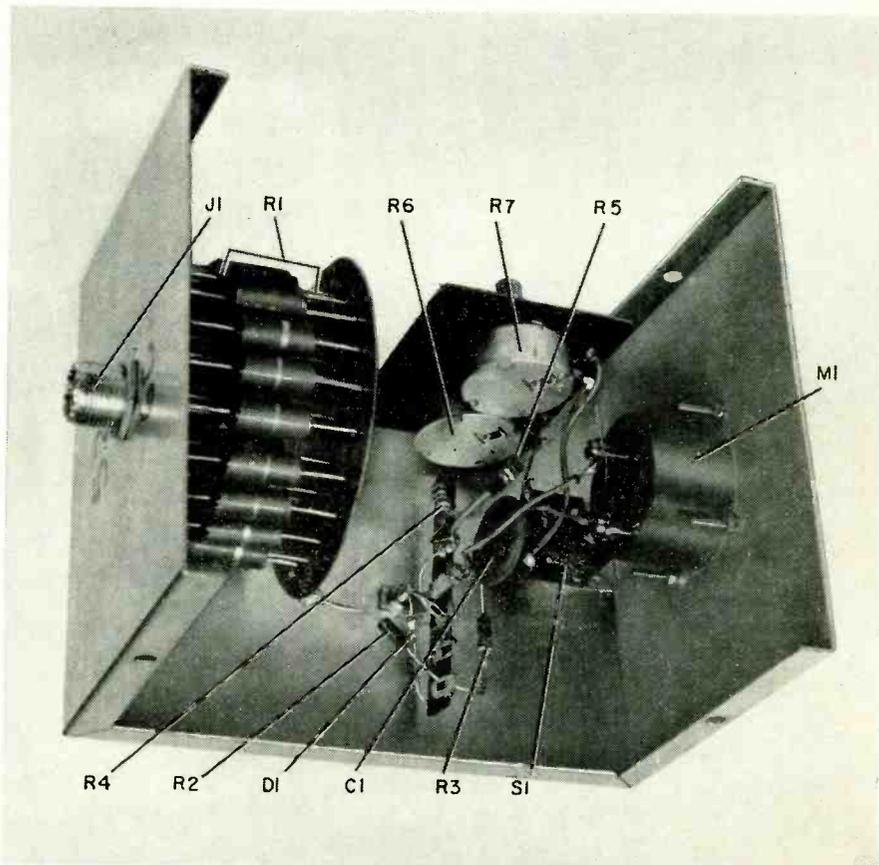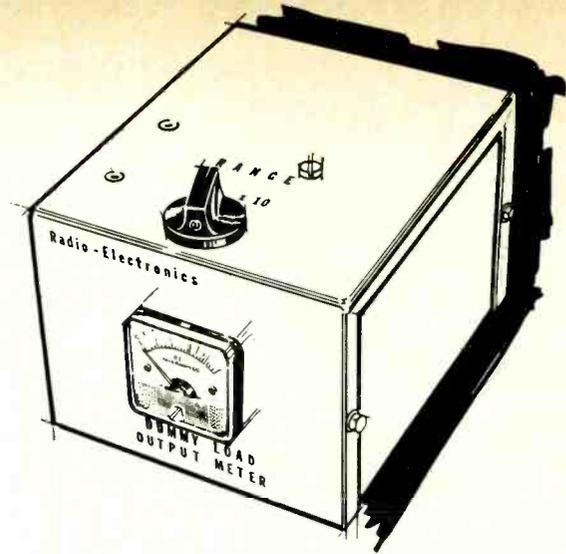

Use point-to-point wiring but keep leads short if you want flat frequency response.

*Chief service technician, Tel-Air Communications Co.

Couple the transmitter output to the dummy load. Don't modulate the rig. Then use the rf probe and vtvm to measure rf voltage. Since the maximum voltage rating of a probe can be anywhere from 20 to 40 volts rms (check manufacturer's specifications) you may want to measure rf across R3. Because it's part of a voltage divider, R3 will show only 1/10 the voltage across R2 and R3 (or R1).

Since the vtvm reads voltage, you will have to compute power. By Ohm's law,

$$P = \frac{E^2}{R}$$

and since $R = 50$,

$$P = \frac{E^2}{50} = .02E^2$$

Refer to the table and you'll see the voltage readings (these are rms volts, remember) you want for various wattages. On the dummy load, set the range switch to X1. Adjust the transmitter for either 22.4 volts across R1, or 2.24 volts across R3, depending on where your rf probe is. This will mean you have 10 watts in the dummy. Now adjust R6 (on the dummy) until the meter reads full scale. From now on leave R6 alone. Readjust the transmitter and follow the table, marking the meter dial (as shown in the photo) at each point.

Since the detector probe may be nonlinear below 1 volt, you may want to put the probe across R1 when you get down around 10 or 12 volts. You will then be reading the full 10 or 12 volts.

Next set the range switch to X10. Adjust the transmitter for some arbitrary wattage—say 5 or 10 watts—as measured by the vtvm and converted with the table. Then adjust R7 on the dummy until the meter reads exactly that value of watts. The rest of the points on the scale will then fall in line.

Using the output meter

The dummy load can be constructed to match other impedances. For example, if the transmitter is designed to feed a 300-ohm line, a suitable

Table of Voltage and Power

Volts (R1)	Watts	Volts (R3)
22.4	10	2.24
21.2	9	2.12
20.0	8	2.00
18.7	7	1.87
17.3	6	1.73
15.8	5	1.58
14.2	4	1.42
12.3	3	1.23
10.0	2	1.00
7.1	1	0.71
5.0	0.5	0.50
2.2	0.1	0.22

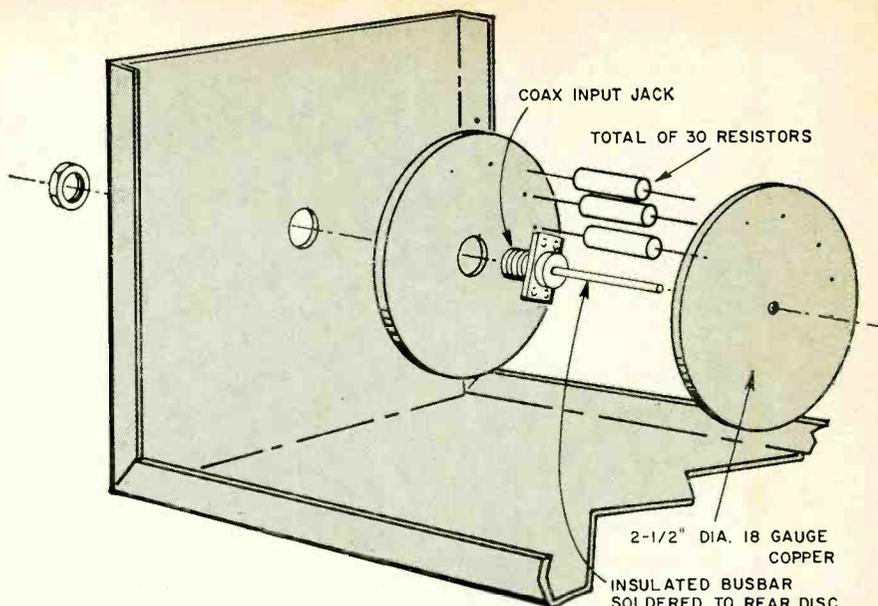


Fig. 1—Two copper discs form the terminals for the 30 resistors used in parallel as the dummy load. Be sure not to overheat them while soldering them in place.

PARTS LIST

C1—.05 μ F, 600 volts, disc ceramic
 C2—.005 μ F, 1,000 volts, disc ceramic
 R1—parallel combination of 30 resistors, each 1,500 ohms, 2 watts, 10%, carbon
 R2—8,200 ohms, 1/2 watt, 5%, carbon
 R3—910 ohms, 1/2 watt, 5%, carbon
 R4—39K, 1/2 watt, 5%, carbon

R5—180K, 1/2 watt, 5%, carbon
 R6, R7—wirewound pots, 100K, 5 watts (Centralab WN series or equivalent)
 D—IN914 silicon diode
 J1—coax receptacle (Amphenol 83-1R) or equivalent)
 M—0-50- μ A meter
 S—sptd rotary switch
 Chassis—6 x 5 x 4-inch aluminum box (Bud Minibox CU 3007A or equivalent)

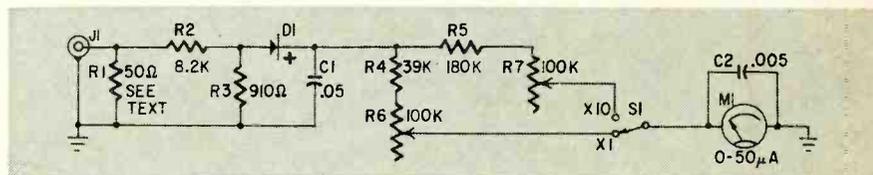


Fig. 2—The circuit contains the bare minimum to do the job efficiently.

dummy can be made by paralleling 33 resistors, each 10K, 2 watts.

When using the output meter remember that proper adjustment of the transmitter loading into the dummy does not assure proper operation when the rig is connected to the actual antenna. There is always some inductive or capacitive reactance at the transmitter terminals which must be tuned out by the coupling controls when the transmitter is finally tuned-up to the antenna. To make sure that an antenna and transmission line are working properly, check the standing-wave ratio before you connect the transmitter to the antenna.

For base stations, swr should be less than 1.5:1. You'll find that 2:1 is about right for roof-top mobile antennas. Transmitter tuneups on the air must be done by a person holding a First- or Second-Class commercial radiotelephone license. This applies to any adjustment which affects power, modulation or frequency.

The output meter is useful for ad-

justing the transmitter as a part of routine maintenance. Also, it can be used to determine the transmitter's ability to deliver its rated carrier power. This is particularly important to CB'ers. You can also use the dummy antenna when checking frequency and deviation in FM transmitters.

R-E



As you calibrate the meter with a known rf signal, mark the meter face by hand.

SERVICE

Table-Model AM/FM Radios

A brief rundown of troubles
and solutions in AM/FM radios

By HOMER L. DAVIDSON

In spite of the general trend toward FM-stereo tuners and expensive consoles incorporating complex FM circuitry, table-model sets are still used a lot. Several straightforward servicing hints can help any technician to speed his handling of these receivers. We'll cover a few of them here.

We can start by checking the AM/FM block diagram shown in Fig. 1. A 300-ohm lead-in ties the FM antenna to the first stage. This rf amplifier may consist of a single tube or a dual triode serving as both rf and converter stages. Generally, a dual-triode tube serves as a local oscillator, rf and mixer stage of the AM section.

Mixer output is coupled to the first i.f.-amplifier section. Two or three i.f. stages are used to increase selectivity and sensitivity. A limiter often follows the last i.f. amplifier stage in the older type of FM receivers. Newer receivers employ a ratio detector that does its own limiting and detecting. In this type of circuit, an unbalanced ratio detector develops the audio signal. The audio section may contain one or two tubes or a single dual-purpose tube.

The i.f.-amplifier section is common to both AM and FM reception. Each stage uses a pair of i.f. transformers—one for AM, the other for FM. The AM transformer is really a pair of mutually coupled, parallel-resonant tuned circuits, each consisting of a coil and a capacitor.

These circuits have a high impedance to signals around 455 kHz, but a low impedance at the FM i.f. of 10.7 MHz. Hence, in the AM mode the 455-kHz i.f. signal develops a voltage drop across each side of the transformer and the signal is therefore passed on to the next stage. In the FM mode, on the other hand, the impedance of the AM circuits is so low there is no volt-

age drop and the 10.7-MHz signal isn't passed on by the transformer.

The opposite action occurs in the FM transformer. Thus the AM and FM i.f. transformers don't interfere with each other.

FM converter

An AM/FM tube-type radio generally uses a dual triode, one section as an FM rf amplifier and the other as the FM mixer/oscillator-type converter. Plate voltages on the converter are typically 90 to 100. Grid voltage will vary from -5 to -3 . Remember, a vtvm should always be used in checking oscillator voltages.

A resistance change in the grid circuit of the oscillator will cause the tube to function weakly or not at all. A shorted grid resistor will stop oscilla-

tions entirely, and only a pronounced hissing noise will be heard. When you get a loud FM hiss but no station signal, suspect the FM-converter section.

If the value of grid resistance increases substantially, the receiver will produce a loud hiss, local FM stations will come through only weakly and, of course, selectivity will suffer. Oscillator voltage will increase to about twice the original value.

This was the story on a Zenith model Y733 FM radio that came into the shop a short time ago. The 10,000-ohm grid resistor had increased in value, resulting in poor selectivity and a loud hiss. Even a strong local FM station was weak. With the outside antenna connected, a station 40 miles away could barely be heard.

If the 50-pF capacitor (Fig. 2) opens, the receiver will not pass a signal. A loud FM hiss will be heard. Grid voltage becomes zero, but the plate voltage will not change.

This was the condition we discov-



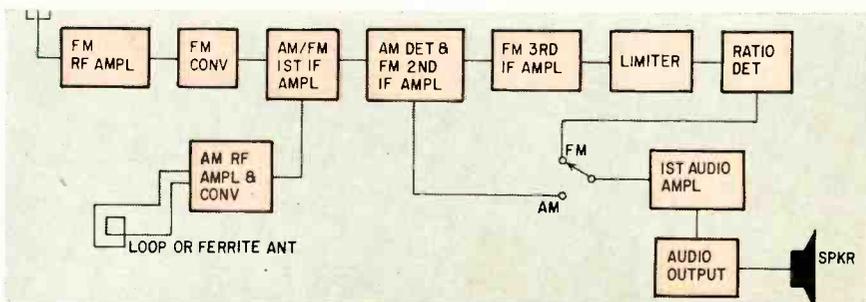



Fig. 1—Typical AM/FM set uses multifunction stages and some common sections.

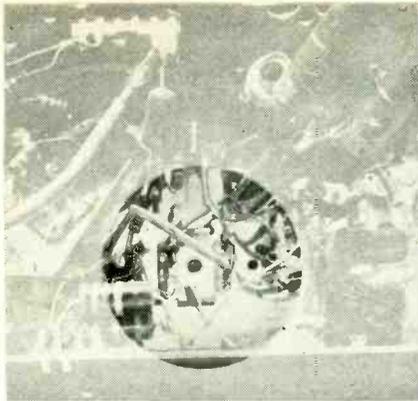

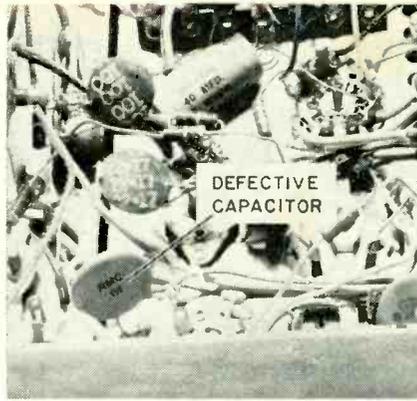When you replace an i.f. transformer, keep track of leads with masking tape.



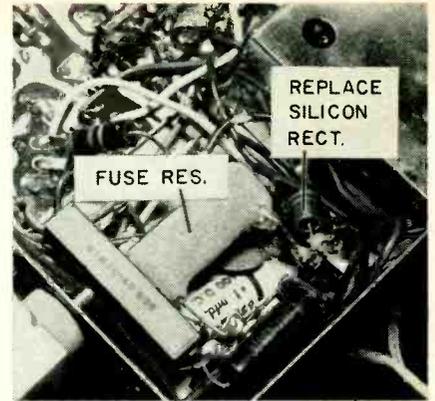B+ here was only 22 volts; that 0.01 μ F bypass capacitor had a partial short.



Be sure to replace the fusible resistor whenever you replace a silicon rectifier.

ered in a Zenith model C730 chassis. The oscillator circuit is similar to Fig. 2. Also, if the small bypass capacitor (not shown) connected from the plate of the oscillator to ground opens, there will be nothing but a loud hiss. Replace the capacitor with a ceramic type of 5% tolerance, or a silver-mica.

It's a simple matter to test several FM converter tubes and use the most active one as a replacement. Be sure it's not microphonic and that all pins are straight and clean.

I.f. limiter and discriminator stages

There generally are three i.f. stages in the typical inexpensive FM receiver. Some receivers also have a limiter amplifier following the third i.f. stage. Many ac/dc FM receivers use half of one tube as the ratio-detector stage and the other section as the first audio-amplifier stage.

The AM signal does not come through the limiter stage or the third FM i.f. section. It is tapped off at the output of the second AM/FM i.f. amplifier, detected and switched into the grid of the first audio stage. Voltages on the ratio-detector diodes are quite low; check with a vtvm.

An increase in resistance of either diode resistor will distort the signal and reduce its strength. If the bypass capacitor on the limiter's screen grid opens, the signal is really low. Hardly any FM hiss is audible and what audio there is will be distorted. Interference from automobile ignition systems also will be severe. Plate voltage on the limiter stage is low: 30 to 60 volts dc.

An FM i.f. transformer does not seem to go bad often. In the same chassis, however, the AM i.f. transformers sometimes short. Tap the can or wiggle the transformer lugs while listening to AM. Measure grid voltage of the following stage; it should be negative. If you find a positive voltage, the transformer is shorted. Sometimes when you've got negative grid voltage, pull the tube—if the transformer is shorted, the voltage will go positive.

You can also find a bad i.f. transformer during alignment. If one of the cans tunes broadly, replace it.

The AM detector has usually been a tube, but more and more today you'll find a solid-state diode. Sometimes the second FM i.f.-amplifier tube is biased and used as an infinite-impedance detector, as well as an FM amplifier. The rest of the receiver is generally conventional.

Alignment

All you need are a vtvm and an rf signal generator. Rotate the oscillator capacitor or permeability-tuning section to the open position. Apply a signal from the generator to the mixer grid at a frequency of 10.7 MHz. Tie the vtvm to the receiver at point A in Fig. 3. Keep generator output low—you should read around 1 volt on the vtvm. Adjust the slugs in the i.f. transformers for maximum readings.

For rf alignment leave the tuning capacitor at 108 MHz and tune the generator to the same frequency. Next adjust the oscillator trimmer capacitor, mixer and antenna or rf trimmer for maximum readings on the vtvm. Then close the tuning capacitor and set the generator to 88 MHz. Adjust the antenna, rf and oscillator coils for maximum indication. Repeat the rf alignment once.

Be sure all pilot lights are working. If one bulb seems to have a dark glass, replace it, for it won't last long and may mean a callback. Clean that dial glass. Brush the dirt and dust out of the cabinet corners. Polish that plastic cabinet; use soap and water. It is surprising how a few such details will add to the appearance of a service job.

R-E


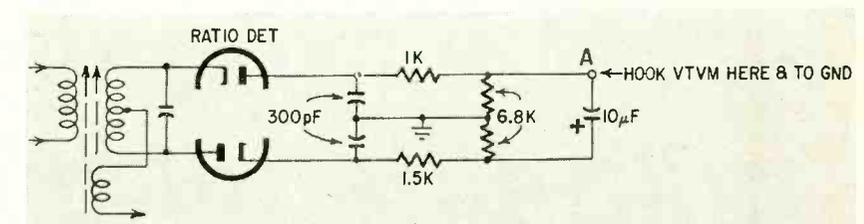


Fig. 2 (left)—In this circuit, the 50-pF grid capacitor opened, blocking oscillator signal.

Fig. 3 (above)—The FM ratio detector may be a tube or pair of solid-state diodes. For alignment, connect vtvm from the negative side of capacitor to ground.

SPECIAL FEATURE

By DAVID LACHENBRUCH

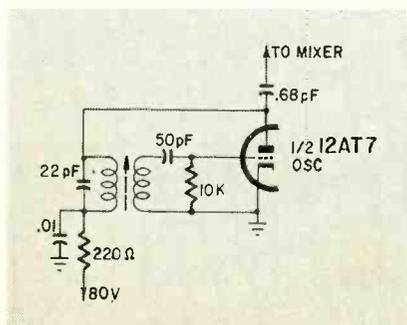

DO X-RAY EMISSIONS from color television sets pose a potential hazard to the public or to service technicians?

This question was widely publicized in recent months—but in the public press, at least, the answer seems to have gotten lost. The entire color-TV X-ray issue was brought to public attention as the result of a design error by a major manufacturer and the subsequent field modification of about 90,000 large-screen receivers. The General Electric incident touched off intensive TV testing activities by the Department of Health, Education and Welfare, by state and regional health authorities and by television manufacturers.

It resulted in the introduction of several bills in Congress for federally enforced standards and testing of high-voltage electronic devices. Hearings were held on the subject by two House subcommittees and one Senate committee, and it appears that one such bill will be passed in the next session of Congress.

The incident also prompted a wave of official concern for the safety of viewers and service technicians from possible X-ray overexposure.

Both the G-E problem and the X-ray scare in general are surprising in view of two well-established facts: (1) From the very birth of the TV industry, manufacturers have been especially vigilant on the subject of X-rays. (2) At the voltages employed in color television receivers, X-radiation can easily be stopped with very simple shielding.

A tiny leak

The G-E trouble—one of those things that “just could not happen”—resulted from a change in chassis design for the 1967 models, which went into production in spring 1966. The shunt regulator tube was sunk into a well in the chassis. After a large number of these receivers were in the field,

WHAT YOU SHOULD

High-voltage tubes in a color

G-E discovered in routine retests that excessive amounts of X-radiation were leaking downward in a fingernail-size arc through the tube socket. The size of the leak was so small that it had previously escaped detection.

Since G-E's 1967 KC chassis lacked external shielding below the shunt regulator tube (although the leakage in many models was stopped by the cabinet), the company instituted a crash program to develop a family of direct-replacement tubes which incorporated an extra measure of internal shielding, for modification of these sets in the field. A widespread effort resulted in location and modification of almost all of the questionable receivers through simple tube replacement.

The vast majority of the original G-E shunt regulator tubes (designed for the KC chassis) on dealers' and distributors' shelves were also taken off the market and replaced by the new heavily shielded types. However, there are still a few around, on shelves and in tube caddies. For each one returned, to a General Electric distributor—*regardless of the make of the tube*—G-E pays a bounty of \$5, plus a free exchange of a direct-replacement substitute.

Needless to say, no one should have any of the questionable tubes in his possession, and a search for any of these obsolete tube types may be both emotionally and financially rewarding:

<i>Obsolete type</i>	<i>Replacement</i>
6EA4	6EH4
6EF4	6EJ4
6LC6	6LH6

What about color-TV sets in general? Are there X-radiation dangers, hazards or pitfalls? Here a background review may be helpful.

The National Council on Radiation Protection and Measurements (NCRP), a government-chartered independent nonprofit organization, has recommended that X-radiation levels for TV sets not exceed 0.5 milliroentgen per hour (mR/hr) at a distance of 5 centimeters (about 2 inches) from the set's surface. This figure was not established for the protection of individuals (who can take exposures many times greater without ill effect) but for protection of the “population” at large, to help keep general background radiation levels down.

Any X-ray exposure from sets meeting this standard represents a very small percentage of the natural “background” radiation that is part of our everyday environment—in effect, it is negligible. The NCRP figure is considered, by NCRP and by radiation scientists, to be very conservative. In fact, it is one-fifth the amount of radiation permitted from TV sets by Underwriters' Laboratories until September, 1967, when UL changed its standard to conform with NCRP recommendations.

Following the G-E disclosures, American television set manufacturers, under the aegis of the Electronic Industries Association, conducted exhaustive X-radiation tests of more than 500 color TV receivers, covering chassis types representing approximately 95% of all color sets in use.

The results showed that, under normal operating conditions, not one set radiated above the 0.5-mR/hr standard. In fact, the vast majority measured considerably less—many of them below the capabilities of the measuring equip-

KNOW ABOUT X-RAY RADIATION IN TV SETS

receiver can produce soft X-rays, but you can easily protect yourself

ment used. Tests of Japanese receivers sold in the United States showed similar results.

X-rays are produced whenever a beam of electrons strikes some material at a relatively high velocity, as in a vacuum tube. Accelerating voltages of at least 10 or 15 kV are required before any significant quantity of X-rays is emitted. Because of the absorption of X-rays by glass tube envelopes, there is normally no significant escape of radiation from tubes unless voltages are in the range of 20 kV or higher. Thus, in a color television receiver, there are two or three potential sources of X-rays—the picture tube, the high-voltage power supply and the shunt regulator tube (if one is used).

Radiations produced at these voltages are known as “soft” X-rays—the type which does not significantly penetrate body tissue. The amount of exposure to X-rays depends on the amount of voltage, duration of exposure and distance from the source of the X-rays. The use of heavily leaded glass envelopes on picture tubes, and shielding around the other two high-voltage tubes, keeps X-rays well below the permissible figure in most normally operating color sets.

Clean bill

In all inquiries and tests to date, color receivers (except the G-E sets in question) have received a clean bill of health under “normal operating conditions.” This brings up two questions of utmost significance to the technician: (1) What are “abnormal” operating conditions and how can they be avoided? (2) Even if there is no danger to viewers, how can the technician be assured that he is not receiving excessive X-ray exposure?

Fortunately, the answers to both questions involve only common-sense precautions and the following of normal servicing instructions—instructions which should be heeded anyway to avoid shock and implosion danger and repeated set failure.

Specifically as to the second question: There are no concrete data to show that the technician—even the worst, most careless technician—can receive dangerous exposure. But, by the same token, there is no proof that he can't.

Since relatively little is still known about the cumulative effects of soft X-rays, the technician has an important responsibility to his customer (and himself) regarding those “abnormally operating” sets. These are receivers operating at above the high voltage specified by the manufacturer or without proper shielding. Many color sets with a recommended voltage of 25 or 26 kV can be operated as high as 33 kV (although they may fail prematurely).


At the level of voltages used in color sets, X-ray emission increases roughly in proportion to the square of the voltage increase. Though manufacturers' tests showed that many sets operating at too-high voltages quickly developed circuit failures (and those which continued operating emitted only moderately excessive radiation), don't tempt fate.

The rules to be followed in home or shop repair, for safety of both viewer and technician, are listed in most service manuals. Those which can keep X-ray exposure below the safe minimum deserve special emphasis:

1. Be sure that all service personnel are familiar with

the subject of radiation. This can be covered by having them read this article.

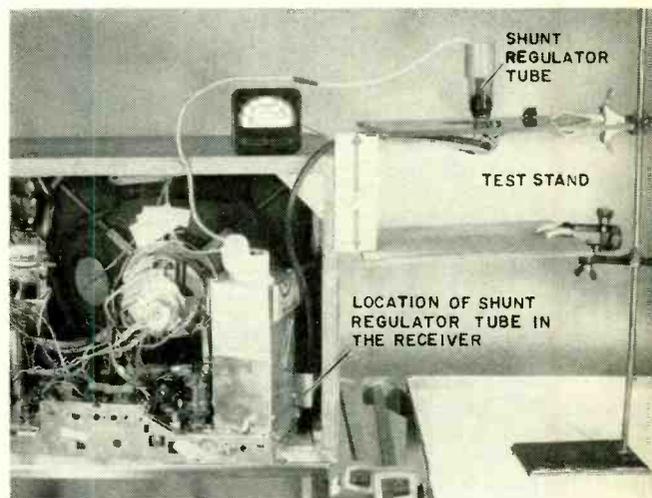2. To avoid possible exposure to radiation and shock hazard, never apply power to the receiver unless the high-voltage compartment is completely assembled with the door closed and all other original factory-installed shields are in place. These shields include any additional shielding on the outside of the high-voltage compartment, shields surrounding the high-voltage rectifier tube or the shield inside the plastic tube cap. If a shield is missing from an incoming set, replace it at once as a standard servicing procedure.



Courtesy National Center for Radiological Health

Experimental setup used to survey radiation from shunt regulator tubes. A G-E KC chassis was used as the power supply. Location of socket on chassis made radiation measurements almost impossible so an adapter and test jig were used. The tube was mounted 7 inches above a sheet of Royal Blue X-ray film.

3. High voltage must never be adjusted to exceed the factory-specified amount with the brightness and contrast adjusted to minimum (no illumination on the screen). Refer to the manufacturer's service manuals for specific instructions. If the high-voltage check indicates a malfunction or improper adjustment, correct this fault before any other service procedure—such as picture-tube setup, yoke adjustment or troubleshooting—is performed. It's important to use an accurate and reliable high-voltage meter. Meters should be calibrated at regular intervals.

4. Whenever tube replacement is necessary, replace regulator tube, picture tube and high-voltage rectifier tube only with the types specified for the specific receiver. Refer to the tube-location label attached to the inside of the receiver, or the service manual, since the tube being replaced may be an incorrect type previously installed by someone else.

5. In troubleshooting procedures, never apply a line voltage exceeding the manufacturer's specifications. Many technicians use a variable stepup transformer to let a set
(continued on page 88)

INCENTIVE LICENSING

continued from page 16

Eligibility for the Amateur First Class license was proposed to be limited to an Advanced, General or Conditional Class licensee who has held such license for at least one year. The examination for the new Amateur First Class license was to comprise a 16-word-per-minute code test and a written examination of a difficulty level between the present General and Amateur Extra Class license examinations. It was also proposed that the present Advanced Class license would no longer be renewed as such and that present holders of this license would be issued the General Class license upon renewal.

The proposal for creation of a new higher class of license to be known as the Amateur First Class license was very favorably received. The purpose of this license was to provide an intermediate advanced license as a "stepping stone" to the highest license attainable, the Amateur Extra Class license. A large number of comments recommended that the Advanced Class licensees be granted "grandfather" privileges to the new higher class license. The Commission agreed with these arguments and believes that the Advanced Class licensees, who qualified by examination for the incentive privileges in effect prior to 1952 and have operating experience of at least 15 years, presumably have qualities which was the purpose of the proceeding to foster. Accordingly, the recommendation for "grandfather" rights to the new license was adopted and will apply to present holders of the Advanced Class license.

Final Proposals

The Commission concluded that, effective November 22, 1967, the present Advanced Class license shall be retained as the new higher class of license instead of creating the Amateur First Class license. Present holders of the Advanced Class license will be renewed as such with all the privileges and status belonging to the new Advanced Class license. The Advanced Class license shall be available to any eligible applicant who successfully passes the examination requirements. These will include a code test of 13 words per minute and a written examination comprising elements 3 and 4(A) as set forth in Section 97.21 of the Commission's Rules, as amended. Since the code test for this license is being reduced to 13 words per minute, code test credit as well as credit for other elements, in accordance with

Unabridged Amendment of Part 97, FCC Rules

1. Section 97.7 is amended to read as follows:

§ 97.7. Privileges of operator licenses.

(a) **Amateur Extra Class and Advanced Class.** All authorized amateur privileges including exclusive frequency operating authority in accordance with the following table, effective on the dates shown:

Frequencies	Class of license authorized	Effective Date
3500-3525 kc/s 3800-3825 kc/s 7000-7025 kc/s 14000-14025 kc/s 21000-21025 kc/s 21250-21275 kc/s	Amateur Extra only	November 22, 1968
3500-3550 kc/s 7000-7050 kc/s 14000-14050 kc/s 21000-21050 kc/s	Amateur Extra only	November 22, 1969
3825-3850 kc/s 7200-7225 kc/s 14200-14235 kc/s 21275-21300 kc/s 50-50.1 Mc/s	Amateur Extra and Advanced	November 22, 1968
3825-3900 kc/s 7200-7250 kc/s 14200-14275 kc/s 21275-21350 kc/s 50-50.25 Mc/s	Amateur Extra and Advanced	November 22, 1969

(b) **General Class and Conditional Class.** All authorized amateur privileges except those exclusive frequency operating privileges which are reserved to the Advanced Class and/or the Amateur Extra Class.

(c) **Technician Class.** All authorized amateur privileges on the frequencies 50.25-54 Mc/s and 145-147 Mc/s and in the amateur frequency bands above 220 Mc/s.

Note: Technician Class licensees may additionally operate on the frequencies 50-50.1 Mc/s until November 22, 1968, and 50.1 to 50.25 Mc/s until November 22, 1969.

(d) **Novice Class.** Those amateur privileges designated and limited as follows:

(1) The d.c. plate power input to the vacuum tube or tubes supplying power to the antenna shall not exceed 75 watts, and the transmitter shall be crystal controlled.

(2) Operation on the frequency bands 3700-3750 kc/s, 7150-7200 kc/s, 21.10 to 21.25 Mc/s, and 145-147 Mc/s is authorized for radiotelegraphy using only type A-1 emission.

Note: Novice Class licensees may additionally operate until November 22, 1968, on 145-147 Mc/s for radiotelephony using types of emission as set forth in § 97.61.

2. Section 97.9 (b) is amended to read as follows:

§ 97.9 Eligibility for new operator license.

(b) **Advanced Class.** Any citizen or national of the United States.

3. Section 97.21 is amended to read as follows:

§ 97.21 Examination elements.

Examinations for amateur operator privileges will comprise one or more of the following examination elements:

- Element 1(A): Beginner's code test at five (5) words per minute;
- Element 1(B): General code test at thirteen (13) words per minute;
- Element 1(C): Expert's code test at twenty (20) words per minute;
- Element 2: Basic law comprising rules and regulations essential to

beginners' operation, including sufficient elementary radio theory for the understanding of those rules;

(e) Element 3: General amateur practice and regulations involving radio operation and apparatus and provisions of treaties, statutes, and rules affecting amateur stations and operators;

(f) Element 4(A): Intermediate amateur practice involving intermediate level radio theory and operation as applicable to modern amateur techniques, including, but not limited to, radiotelephony and radiotelegraphy;

(g) Element 4(B): Advanced amateur practice involving advanced radio theory and operation as applicable to modern amateur techniques, including, but not limited to, radiotelephony, radiotelegraphy, and transmissions of energy for measurements and observations applied to propagation, for the radio control of remote objects and for similar experimental purposes.

4. Section 97.23 is amended to read as follows:

§ 97.23 Examination requirements.

Applicants for original licenses will be required to pass the following examination elements:

- (a) Amateur Extra Class: Elements 1(C), 3, 4(A), and 4(B);
- (b) Advanced Class: Elements 1(B), 3, and 4(A);
- (c) General Class and Conditional Class: Elements 1(B) and 3;
- (d) Technician Class: Elements 1(A) and 3;
- (e) Novice Class: Elements 1(A) and 2.

text of unabridged amendment continued on page 83

Section 97.25 of FCC Rules, will be given to those applicants for the Advanced Class license who hold the General Class license.

The Commission noted the renewed interest in the Amateur Extra Class license since the inception of the proceeding (the number of holders of this license increased over 25% in little more than one year) and concluded that the continued issuance of the Amateur Extra Class license as part of the incentive licensing program was appropriate and warranted.


As the incentive for the upgrading of licenses, the Commission proposed the reservation of frequency segments in the 2-, 6-, 15-, 20-, 40- and 80-meter bands for the exclusive use of the higher-class licenses.


The FCC intends careful review and if it is determined that there is insufficient occupancy of any part of the reserved frequency segments then the effective date of the schedule will be postponed in whole or in part.

The Commission also adopted proposals that new holders of the Novice Class license shall be given a two-year nonrenewable license term in lieu of the present one year nonrenewable term, and that, effective one year after adoption of these rule changes, telephony privileges for the Novice Class licensees in the frequency segment 145-147 MHz shall be deleted.


One aspect of the proposed distinctive call-sign schedule related to the assignment of call signs with a single-letter prefix and a double-letter suffix (e.g., W2AB, K1AA). These call signs are popularly referred to as "two-letter" call signs and are cherished as the mark of an "old timer." At the present time the FCC has about 8000 of these call signs available for assignment.

To reflect both longevity and/or attainment in amateur licensing, the available two-letter call signs will continue to be assigned to previous holders and will also be assigned to holders of the Amateur Extra Class license who submit proof of having held an amateur radio station license issued by the United States Government 25 years or more prior to the date of application therefor. Present holders of two-letter call signs can continue to hold them even if they do not meet this requirement. The \$20.00 special call-sign request fee will apply to these requests. Applicants will not be permitted to select specific two-letter call signs. However, a former holder of a specific two-letter call sign may regain such call sign if it is available in accordance with Section 97.51(a)(1) and (2) of the Rules. Finally, new holders will be limited to one such assignment. **R-E**

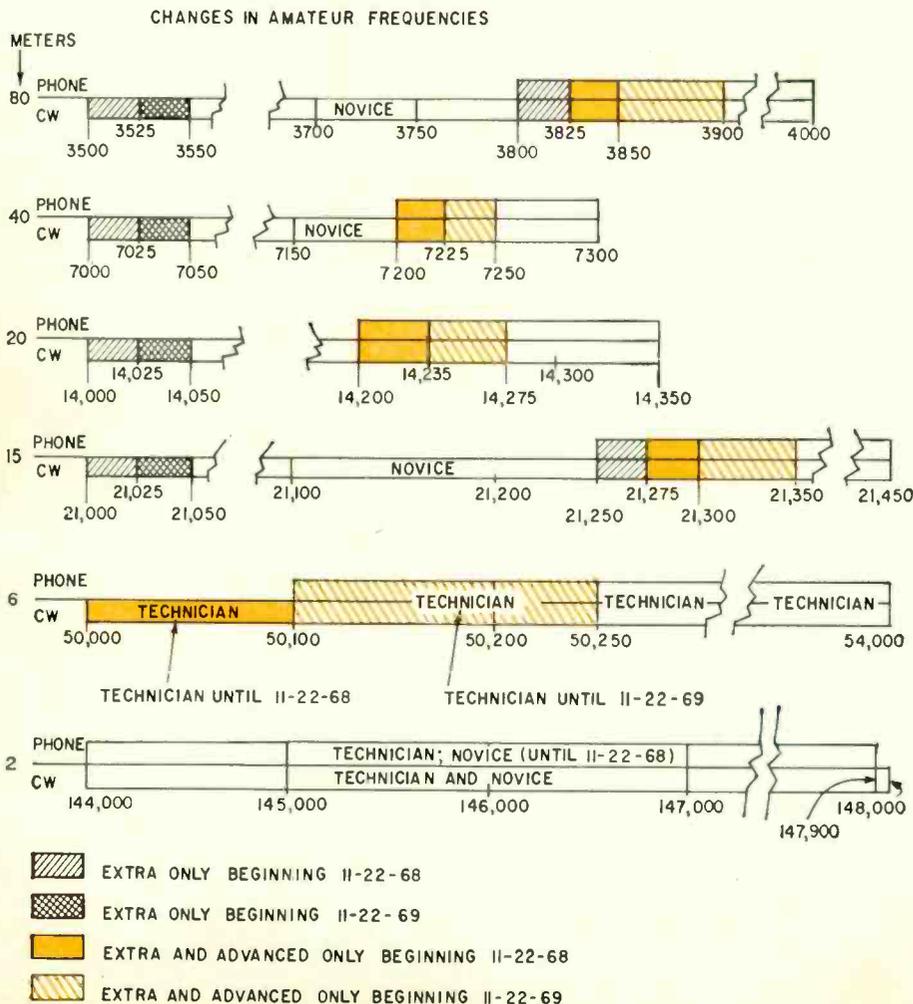

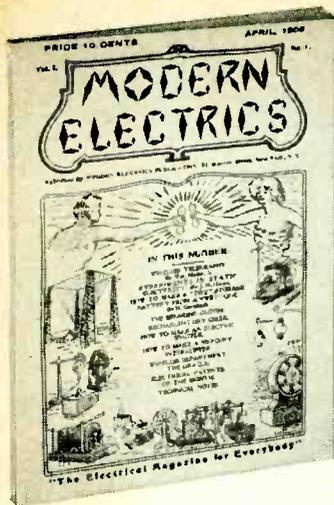

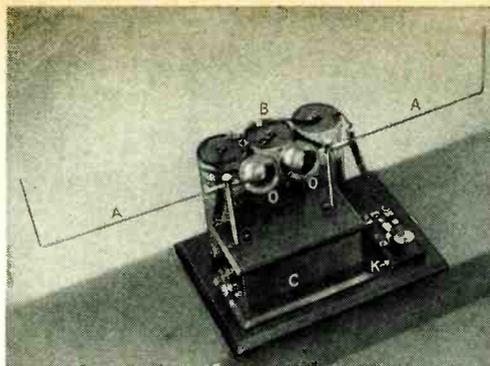The world's pioneer radio magazine, published by Gernsback as adjunct to his E.I. Co. catalog.



The Telimco radiotelegraph set—the first radio sold to the public. The transmitter is on the left and the receiver is on the right. Maximum range was about one mile.

Hugo Gernsback 1884-1967

(continued from page 4)

Gernsback as publisher

Though Electro Importing Co. continued (and was succeeded in the '20's by RASCO—the Radio Specialty Co.), Gernsback's main efforts in the future were to be in publishing. *Modern Electrics* was sold in 1912. After a number of combinations with other magazines, it (and the others) became today's *Popular Science*.

Gernsback immediately started a larger magazine, the *Electrical Experimenter*, which changed its name to *Science and Invention* in 1920. In 1919 he started the country's first "purely radio magazine," *Radio Amateur News*. It became *Radio News* in 1920 and is still in existence. (The name was changed to *Electronics World* in 1959, after a period as *Radio and Television News*.)

In 1926 he founded, with *Amazing Stories*, not only a new magazine, but a whole new genre. Science fiction had appeared regularly in all the Gernsback magazines (quite a bit of it written by Gernsback himself) and a little was published in other magazines, together with weird stories and fantastic fiction. But this was the first attempt at a magazine entirely devoted to true scientific fiction. Its success stimulated dozens of others into being. All, however, look back to Gernsback as the First Cause, and he is unanimously acclaimed the Father of modern Science Fiction.

In the winter of 1928-29 his publishing company ran into financial difficulties and the publications passed into other hands. Almost immediately Gernsback started RADIO-ELECTRONICS as *Radio-Craft* (the name was changed in 1948). He also started a number of other magazines, including *Television News*, which ran about a year in the early '30's, and *Short-Wave Craft* (later *Short Wave & Television and Radio & Television*), which was combined with *Radio-Craft* in 1941. In 1933, he introduced *Sexology*, the most successful of a number of biomedical publications he published at different times. Together with its Spanish-language version, *Luz*, it continues as a highly successful magazine.

Altogether, Gernsback published more than 50 magazines in the technical, experimental, biomedical, aviation and other fields (even one called *Motor Camper and Tourist*—in 1924!—and another called *Technocracy*). The number of books he published cannot be estimated accurately, but runs into the hundreds.

Gernsback as writer-prophet

The young Gernsback had to write much of the material in his earlier magazines, and was a regular contributor to the last years of his life. His first book, *The Wireless Telephone*, 1908, a combination of progress report and hopeful prediction, was an attempt to speed the development of the art.

In 1911 he wrote his most important work, *Ralph 124C 41+*, a science-fiction novel in which he predicted fairly accurately the progress of science and invention for the next half century and more. His other important full-length book, *Radio for All*, was a simple theory and how-to-do-it book for beginners. It was written in 1922.

Gernsback's imagination and scientific method led him to predict an almost unbelievable number of electronic advances that—seemingly absurd when suggested—became facts during his lifetime. *Ralph 124C 41+*, serialized in *Modern Electrics* in 1911, described radar (with an illustration) so clearly that it can be used as a textbook to explain radar today. (The imaginary equipment was used to locate a space vessel, incidentally.)


In the same book Gernsback mentioned two-way television, germicidal rays, tape recorders (with ¼-inch tape!), night baseball, artificial silk and wool, stainless steel, magnesium as a structural material, and fluorescent lighting.

Many of his predictions were made in his annual Christmas booklets, which were called *Forecast* since 1951. Some predictions have already been realized, like the Celestial TV (and airplane shelterway) of *Forecast 1952*, issued at Christmas 1951. Others, such as electronic weather control, are still in the future.

Another class of predictions—which might almost be called demands—appeared very early. The article "Television and the Telephot" appeared in *Modern Electrics* December 1909. In it, Gernsback unquestionably introduced the word "television" into the English language, insisted that wireless picture transmission must come, and suggested ways in which it could be realized.

As early as 1924 he described a radio-controlled military television plane that would transmit six pictures, covering all directions, to a viewing station on the ground. In 1928, he pioneered actual television broadcasting, transmitting tiny pictures from his broadcast station WRNY in New York City on a regular schedule. The 1.5-square-inch pictures were not considered entertainment quality even at that time, but the transmissions were picked up faithfully by 2,000-odd experimenters.

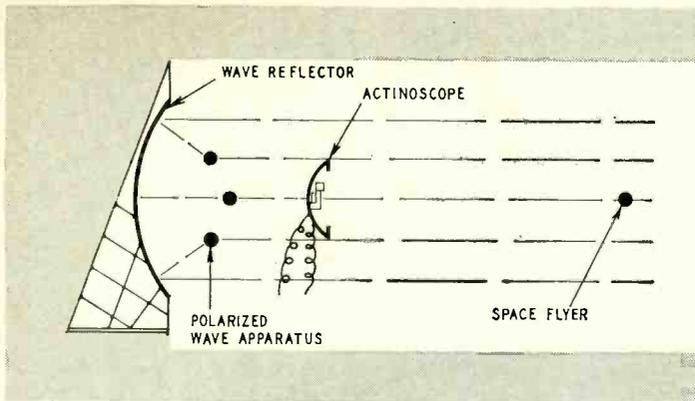Education by television—"Tel-Education"—was one of Gernsback's favorite subjects, and he advocated it in a number of articles and at least five editorials, beginning in 1951. He circulated some of his editorials on the subject to large numbers of educators, legislators and others.



First drawing of radar equipment appeared in *Modern Electronics*, December 1911, as illustration in the popular "Ralph 124C 41+."

In *Forecast 1955*, he proposed the Tele-Doctor, a device combining a television set with instrumentation for pulse, respiration, blood pressure and other needed data, which could be controlled by a doctor in a central office. The device would be rented by the patient, presumably from the local drugstore, and plugged into the telephone line. The doctor, with his control instrument, could then get all the information that could be obtained in a home visit, in a fraction of the time. (In 1967 a New York headline read "Heart Pattern by Phone Has Saved Many Here.")

One of his last demands was for a National Facts Center—a Washington-based computer and data-processing central, closely allied with the Patent Office. It would record, correlate and store all scientific knowledge. Such a center could save billions of dollars by preventing duplicated, useless research and by keeping researchers abreast of the exact state of any art.


Gernsback's influence

Gernsback's predictions and his demands on the future undoubtedly affected inventors, researchers and legislators—his correspondence bears witness to that. But his involvement was often much closer—he never hesitated to propagandize, lobby or even point with alarm when necessary.

As early as 1909 he founded the Wireless Association of America, to advance the interests of all interested in or connected with the radio art. In 1912, when legislators sought to eliminate the radio amateur, Gernsback sprang to his defense, pointed out his value to the country and to the art, and listed in an editorial what he believed the privileges and limitations of the amateur should be. The amateur section of the Wireless Act of 1912 is practically a paraphrase of that article.

In 1919 the very existence of amateur radio was threatened. Gernsback's article—with its famous "Verboten" cartoon by Paul—blasting the notorious Alexander Act is credited with being an important if not the decisive factor in the defeat of that bill. Later, he formed the first organization of radio repairmen—the Official Radio Service Men's Association (ORSMA). Gernsback editorialized continuously on service technicians' problems.

But his direct contributions, as early equipment supplier and later as publisher, had an even greater effect. By making it possible for the experimenter to buy otherwise unobtainable equipment in small quantities and at reasonable cost he drew thousands into the field who would never have become interested in scientific pursuits. (A prominent Australian engineer on a exchange visit to Canada came to New York a few years ago to see and photograph the man who had started him on his career. But first he made a

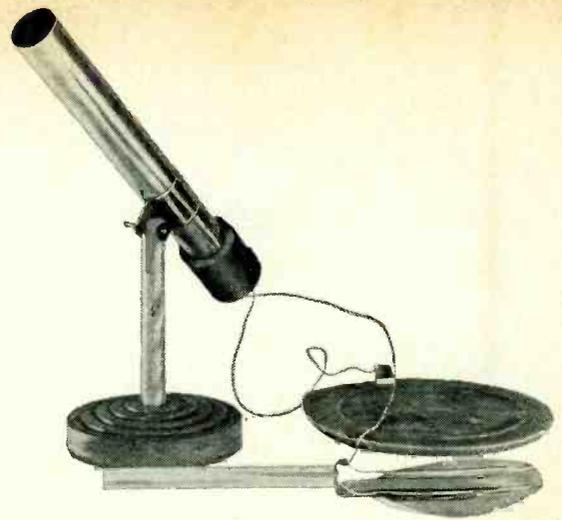

Electret and tester. The tester at left—one of Gernsback's latest inventions—is easy to use.

pilgrimage to 233 Fulton St., home of the Electro Importing Co.) In later years, the interest of many more thousands has been directed toward scientific and technical objectives by Gernsback magazines, with their continuous orientation toward the future and their never-ceasing flow of information presented so that the reader without an engineering education can understand and enjoy it, as easily as the more educated reader.

Gernsback as inventor

Gernsback obtained more than 80 patents during his lifetime. He made little attempt to commercialize most of them. An exception was the compression-type "condenser" (the principle of the present trimmer capacitor). It was used as the "book condenser" in the Crosley Trirdyn radio, and he licensed Crosley and a few others. A few other patents were obtained to protect some of the 60-odd devices he developed for the Electro Importing Co. His bone-conduction hearing aid, patented in 1928, was re-invented some years later and manufactured without interference from Gernsback. ("I never intended to market it," he said. "Why should I bother someone else?")

Not only did he develop many inventions but he suggested many more. Sometimes—as in signaling the planets—he went into exact details. Some of these turned out to be overcautious—it was not necessary, for instance, to erect sending and receiving stations on opposite sides of the earth to receive radio reflections from planets. In other cases, he suggested several possible approaches, without going into detail.

In other cases he promoted and pushed the work of other inventors directly. His interests in electrets, at a time when the average physicist did not even recognize the word, led him not only to print articles on the subject, but to persuade people into actually constructing them. Thus Edward Padgett first heard of electrets in the office of RADIO-ELECTRONICS and accepted the suggestion that he try to make some. He described his experiments in a series of articles in the magazine. The electret (a wax disc with a permanent positive charge on one face and a negative charge on the other) was publicized at the RADIO-ELECTRONICS booth at the next IRE show. Later, another old author, Victor Laughter, told readers how to make electrets as big as pie plates.

Gernsback the man

The feeling he invoked among those he inspired into electronic careers is difficult to describe. In many cases he produced disciples rather than readers—a prophet indeed with honor in his own group. The head of one large re-



This picture, from *The Experimenter*, in 1924, was first description of military TV. Radio-controlled plane with six cameras sent pictures back to headquarters for six-panel display.

search organization is impelled to testify, whenever the name is mentioned, that it was Hugo Gernsback who caused him to develop the interests that led him to his present position.

Gernsback, in turn, had a fantastic loyalty to old friends—and he counted his old readers in that group. When the name *Radio-Craft* was becoming obsolescent he asked his staff for a new name. It should contain the word “television” and be reasonably short. Not satisfied with the suggestions received, he sent them, together with a few of his own and a few extras to make weight, to 500 of his steadier subscribers. The result was an upset: more than 50% of the lists—with a choice of 13 names—came back with a vote for one of the weight-makers, RADIO-ELECTRONICS. Gernsback accepted the mandate of his loyal readers and used a title that did not include the magic word of the period.

His personal loyalties were equally strong. While Lee de Forest was under pressure from powerful interests, Gernsback never wavered in backing his claims to having developed a new instrumentality in the Audion (not merely “a Fleming valve with a grid in it”). He again supported him during the struggle over the discovery of regeneration, in spite of the fact that de Forest’s opponent was the largest advertiser in the electronics field. (In 1924 the Supreme Court acknowledged de Forest as the inventor of the regenerative circuit.)

He was also one of the last friends of the great (but in his last years, ignored) Nikola Tesla, and it was through his intervention that Tesla obtained from Westinghouse the pension—or consulting retainer—that maintained him the last years of his life.

Gernsback and the world

For some years a recognized figure as a great radio salesman and successful publisher, his “window into the future” irritated those whose viewpoint was more limited (Doesn’t he realize the difficulties in the way of. . . ?). His insistence, for instance, that pictures not only could be sent by wireless, but that the engineering fraternity should buckle down and devise means for doing so, did not ingratiate him with a group trained to concentrate on the problems in the way of accomplishing an objective.

With his financial near-collapse in 1928, his critics became more outspoken. Respectable scientists and industrialists often dismissed him as a harebrained crackpot. Only as his impractical ideas became prosaic facts did many of the solid citizenry of the electronics world begin to take notice of him again. And his economic advances in the 1940’s had a profound influence on the same group. Nothing succeeds like success, and it was again a successful publisher talking.

When the scientists at Massachusetts Institute of Technology first announced the successful reflection of signals from Venus in 1958, the paper opened with the statement that it was “first proposed by Gernsback in 1927” (“Can We Radio the Planets?” *Radio News*, February, 1927).

He received recognition and awards from many other sources, and was published in most of the wide-circulation magazines. A four-page spectacular in *Life*, July 26, 1963, was illustrated by his farthest-out (into space) concepts. *Ralph 124C 41+*, which first appeared in book form in 1925, came out in a second edition in 1950; was made a paperback by Crest Books in 1958, and appeared in a Russian edition (Moscow, 1964).

Gernsback drew his power from two things: a child-like and unquenchable curiosity and a strong urge to communicate. At all times he welcomed the new—however improbable—and on occasion was criticized for printing wild ideas. For example, he did not hesitate to publish the theories of Professor Ehrenhaft, who insisted there was such a thing as magnetic current. With Ehrenhaft’s death his theories disappeared (till a few months ago, at least). But Gernsback refused to learn from experience, and in 1950 printed an even wilder account of electronic spaceships that would maneuver with cathodic power. This was by another German professor named Oberth. (One can’t lose all the time, and within three years that wild idea was being discussed by scientific societies, and seemed hardly wild at all after the successful orbiting of Sputnik.)

No single magazine article can hope to cover adequately the life of Hugo Gernsback. He was too many things—was called the Father of Science Fiction, the Father of Radio Amateurism, the Fairy Godfather of the IRE (He retorted, “I accept the ‘godfather’ but ‘fairy’, no!”). For many years he was the mentor of the experimenter and constructor, and later of the radio service technician. (This magazine, incidentally, introduced the term “technician” instead of “serviceman.”)

Gernsback the humorist

Far from sharing the too-common view that a technical article or magazine must be deadly dull to be serious, Gernsback injected humor into his magazines from the beginning. (For a time, he even published a humor magazine, as well as a series of “Scientific Comics.”)

Modern Electrics carried a page entitled “The Martian Screech” in many issues. Supposedly edited by Fips the office boy, an immigrant from Mars, it described many electronic wonders of that planet, plus Fips’ own inventions. These included transmission of matter (such as ham sandwiches) and contrapolar current, a remarkable form of electricity carried on linen thread (insulated, of course, by wrapping it with bare copper wire). A coil of this contra-conductor, connected across a storage battery, would cool rapidly beyond the freezing point, instead of heating.

Years later, Fips reported his breakthroughs in the April issues of RADIO-ELECTRONICS. The *Westingmouse* was the most famous. A *vest-pocket* radio (in 1933!) it contained seven APR-1 tubes and was unbelievably small (hardly twice as large as a present-day transistor set). Reactions from a large electric company—that had received numerous orders from readers who were ready to believe the unbelievable—were so positive that Fips emerged again only in 1944, with a Radium Radio, so powerful it needed a throttle instead of a volume control. Every year thereafter he described new and revolutionary inventions, such as a crystal amplifier, office noise neutralizer, electronic brain servicing, and 3-D TV receiver. (The first three wild ideas are now in use, incidentally, and it is rumored that researchers are working hard on 3-dimensional TV.)

R-E

Shrink on the Insulation

Use modern, easy way to cover wire, splices, terminals, components, etc.

By JULIAN N. JABLIN, W9IWI

WOULDNT IT BE NICE

if you could point your finger at a hot spot and *presto!* it would be insulated.

Think of a wire splice in a TV high-voltage circuit, a resistor in a tight corner, or a connection to be weatherproofed—each neatly wrapped in a tight sleeve of tough material assuring permanent protection. If you could do this, gone would be the nuisance of applying bulky wrappings of tape in inaccessible spots. Also, you wouldn't worry about the possibility that the insulation could eventually dry out and come apart, or lose its ability to insulate.

Such magic is not yet part of the electronics scene. What is available now is a new tubular insulating material that you can slip over a soldered connection or a component and shrink to a tight grip. The results are fast, neat, and professional looking.

The material which makes this possible is plastic *shrinkable* tubing. It is made in a variety of diameters and, when heated, shrinks to a portion of its original size. You may have seen such tubing in commercial and military equipment, where it has been used for several years. Now it's available in consumer quantities at electronics distributors. Once you have tried it, you will find yourself devising new ways of employing the tubing to make your work easier and better. Probably you will substitute it in most cases where you might have used tape or spaghetti.

An example is the small power supply in Fig. 1. I put everything—transformer, silicon rectifiers, filter components, VR tube—in a 4" x 5" x 6" box. On the cover plate I mounted the pilot light and ac switch. Even with slack wiring, it would have been difficult to tape the connections to prevent shorts. So, I slipped short lengths of shrinkable tubing on the wires. Then, after soldering the splices, I slid the tubing down over the exposed joints and heated the tubing with my soldering gun. The insulation then shrank on. I prewired the VR tube (see Fig. 2) and, since it was mounted on short spacers above the surface of the metal box, I insulated all the lugs.

How it works

What makes the tubing shrink? In the manufacturing process, it is irradiated or otherwise treated and expands. When heat is applied, it shrinks to its original diameter and remains stable at this size. The usual shrinkage ratio is 2:1—that is, the tubing will shrink to 50% of the diameter it is when you buy it. Thus, when slipped over a wire or com-

ponent which is slightly smaller than its unheated size, the tubing will grip tightly after you have heated it. There is some slight shrinkage lengthwise, but for all practical purposes you can ignore this if you cut the tubing a bit longer than the part to be insulated.

Manufacturers produce shrinkable tubing in various diameters, made of several plastics which have different characteristics. Some are highly flexible after heating, some less so: some will withstand higher ambient temperatures than others: some have a meltable inner wall for better encapsulation of components. For the most part, the technician or experimenter can use any type that is available. All will do what you want—provide a tough, high-dielectric, stable sleeve over a part that is to be protected.

Shrinkable tubing is produced by several manufacturers. *Alphlex*, made by Alpha Wire, is packaged in a boxed assortment of sizes, types and colors, as well as in packages of 4' or 6" lengths in individual diameters. Other makers are Belden Manufacturing Co. and Birnbach Radio Co. Any electronics parts distributor or mail-order house listing these manufacturers' products can supply shrinkable tubing.

Heat and color code

To heat the tubing, I have used my soldering gun, a match, and my wife's oven, depending on the job. The insulating sleeves on the pliers in Fig. 3 were processed in an oven at 350°F for a few minutes. Because of the large difference in diameter from the middle to the end of the

continued on page 84

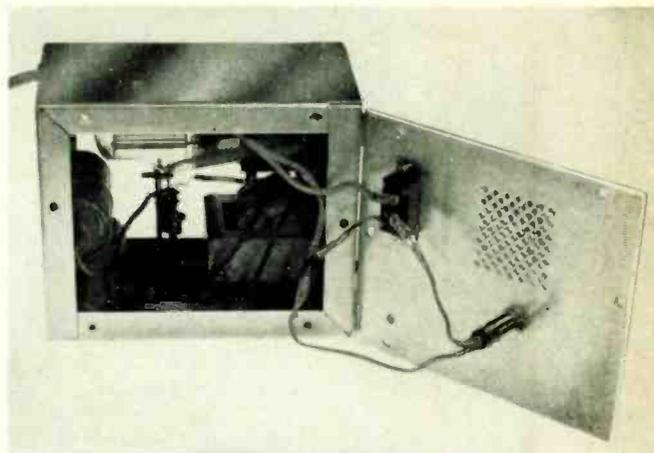


Fig. 1—(Top) Shrinkable tubing insulates splices in this compact power supply.


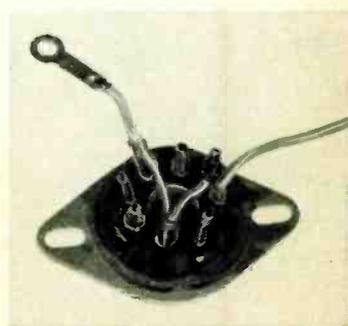


Fig. 2—(Right) VR tube socket in power supply is prewired before mounting. All lugs are covered with heat shrinkable tubing.

HOW TO MAKE PRINTED

Plan Layout Etch and Test

By R. T. MONTAN'E

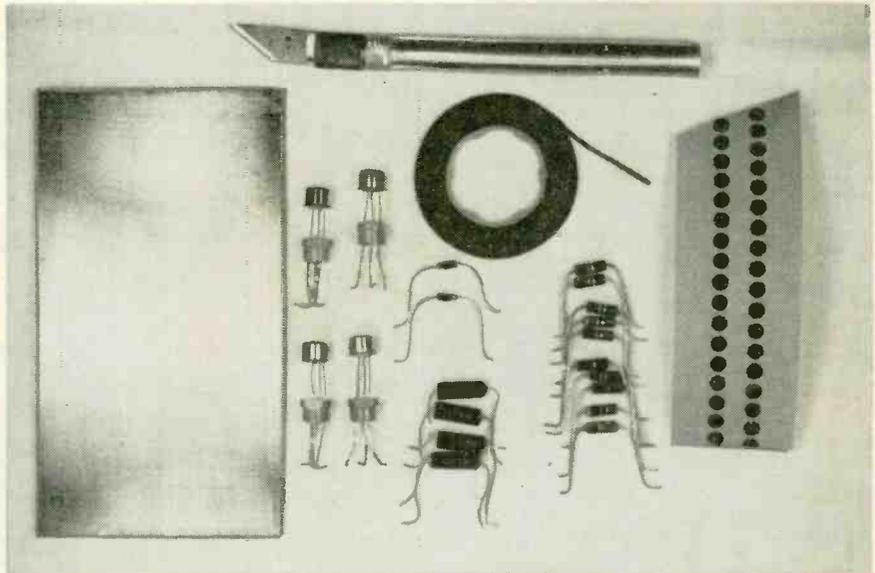

Before. Materials and components used to construct the amplifier are shown here. Resist-tape (center) and dots (right) mask the metal from the etchant in the acid bath.

Planning the layout of a printed-circuit board so it resembles the actual schematic diagram is the key to this simple circuit-evaluation technique. Interconnecting wiring is laid out by placing etch-resist materials on the copper side of a blank board. The prepared board is then etched. All components are soldered directly to the copper circuit that survives the etching process, and the breadboard is ready to be tested. The complete job, from layout to testing for a typical solid-state amplifier, takes about 2 hours.


All materials required to process the PC board can be obtained from almost any large electronic parts distributor. Complete kits of materials are available, or each item shown on the material list can be purchased separately. A kit usually has enough material to process two boards.

Select a board of adequate size, either by estimation or by laying out all necessary components in a rough approximation of the finished circuit. The four-stage amplifier, used here to illustrate the process, is constructed on a 3½ x 5-inch board.


After you've cut the board to the proper size, clean the copper-plated side with steel wool. It has to be absolutely free from dirt and oxidation, so avoid finger marks.

Following usual procedures for schematic layout, place the components on the board—input to the left, output to the right. Form the B+ and


Mask, Etch and Clean

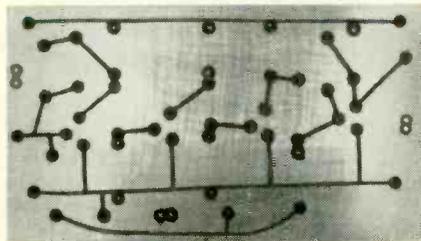

First, apply resist tape to the board.

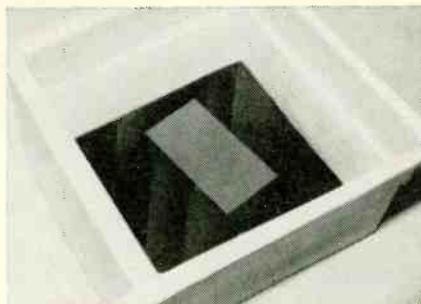

Then, put board in etchant, copper down.

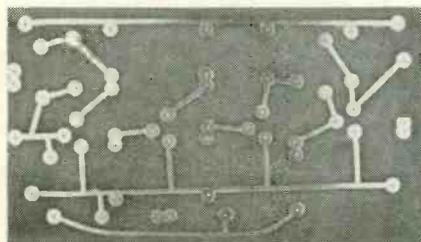

Finally, remove resist and wash.

ground buses using resist tape. Next, separate each transistor-socket lead and locate resist dots to provide connections for base, emitter and collector.

You can make things easier for yourself by not drilling holes in the board. Bend component leads at right angles and you'll be able to solder them directly to the copper lines.

Of course, it makes no difference in layout whether you drill holes or not. Follow the plans given here, laying out the circuit paths.

You can make your layout task easier if the schematic is drawn with as few crossed lines as possible. When a crossing must be made, a component (resistor or capacitor) usually can be used as the bridge.


Coupling and bypass capacitors should be mounted edgewise on the board to economize space. Collector resistors are mounted close to the collector supply line—the line is plus in this case for npn transistors.

At this point in preparing the board, your layout should be thoroughly checked for mistakes. The next step is to etch away the excess copper; once it's gone, mistakes are difficult.

A plastic pan, large enough to accommodate a 12 x 12-inch board, is required to contain the etching liquid (ferric chloride). The etchant is poured into the pan carefully; it leaves permanent stains on clothing. The liquid should be about ¼ inch deep.

All bubbles are removed from the

CIRCUIT BOARDS

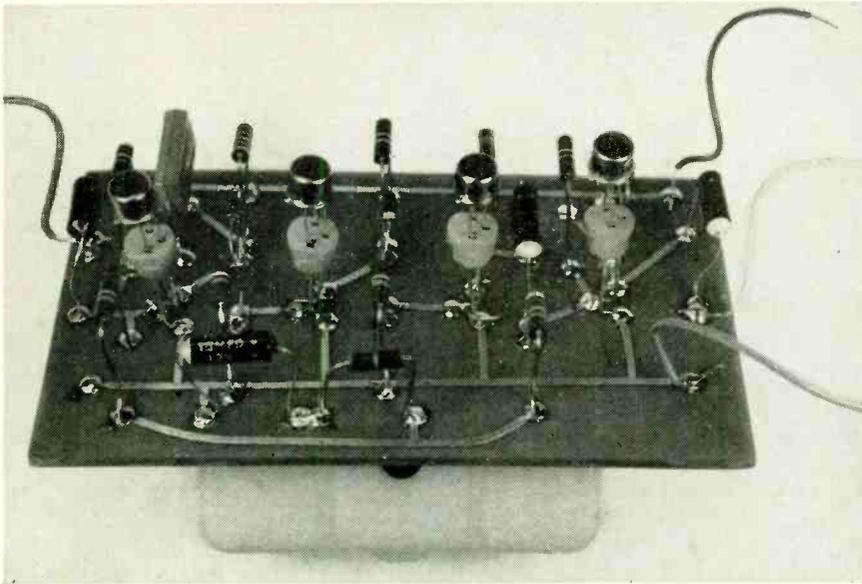

After. To avoid drilling you can connect the components on the wiring side of the board.

surface of the bath before the printed board, copper side down, is placed in the etchant. Remove the board after 1 minute and check to see if air bubbles have formed. Rub a little etching fluid over any area where bubbles appear, then place the board back into the pan for an additional 20 minutes. Check occasionally to be sure the board is

floating. Be careful not to overetch the board, or the copper underneath the resist tape may dissolve.


When all exposed copper has been dissolved, remove the board from the etchant. Rinse it thoroughly in cold, running water. At the same time, remove the resist tape and the resist dots. Clean the copper circuit paths and the board itself with household steel wool. To remove all traces of the etchant, rinse the board in running water for 10 minutes. Finally, dry the board for 30 minutes. Remove any unwanted copper burrs or snags with a sharp tool or knife.

From this point on, all you have to do is mount the components to the board. **R-E**

Materials List

Tape resist circles, 3/16" (Brady TC-187-062 or similar)
Tape resist strips, 1/16" (Brady CSR-062 or similar)
Copper-clad XXXP board
Liquid resist (Kepro R-2 or similar)

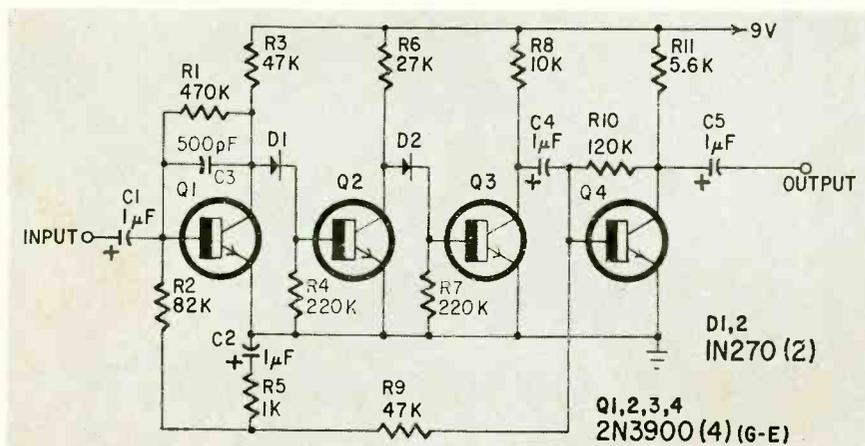Etching solution
Misc. Plastic pan to contain etching bath
Knife, solder, wire
Note: Materials are made in a variety of sizes, quantities and prices, are available at many distributors.



Notice the similarity of the layout of the schematic with the layout of the PC board.


Rx
avoid
headaches

use Sony Tape

If you've been using any of the so-called bargain tapes, chances are you should have your heads examined. The odds are good that the heads are excessively worn and you're not getting the most out of your recorder. If you want to keep "factory-fresh" sound to your recorder—and avoid future "headaches" and keep it that way—Here's the prescription—buy Sony Professional-quality Recording Tape. Sony Tape is permanently lubricated by the exclusive Lubri-Cushion process. Sony's extra-heavy Oxi-Coating won't shed or sliver and is applied so evenly that recordings made on Sony Tape are not subject to sound dropouts. Sony Tape captures and reproduces the strength and delicacy of every sound—over and over again. There's a bonus, too, with every 5" and 7" reel of Sony Tape—a pair of Sony-exclusive "Easy Threader" tabs to make tape threading the easiest ever. And Sony reels are a sturdier, heavier gauge plastic for protection against possible warping. It's just what the "Doctor" ordered and yours for just pennies more than "bargain" tape.

SONY **SUPERSCOPE**
SUN VALLEY, CALIFORNIA • 91352
Circle 29 on reader's service card

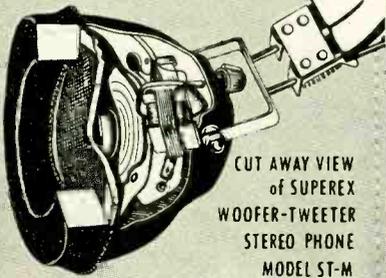pretty
clever...
those
fellows at
Superex



CUT AWAY VIEW
of SUPEREX
WOOFER-TWEETER
STEREO PHONE
MODEL ST-M

First they put a woofer/tweeter in their stereo headphones to provide a full range of response without distortion. They also added a complete crossover network right in the earpiece . . . for an authentically fine speaker system in miniature. Just what the true stereo buff ordered!


Then they extended their line in depth for the Hi-Fi enthusiast and for Education, Broadcast, Aviation, Marine and Communications use.

Now, they've developed a great new model, the ST-PRO-B . . . just about the last word in a professional quality headphone.

Pretty clever, those fellows at Superex. All they do is give you the edge in quality, value and forward-looking audio engineering. Ask your dealer for a demonstration.

Write for complete catalog.

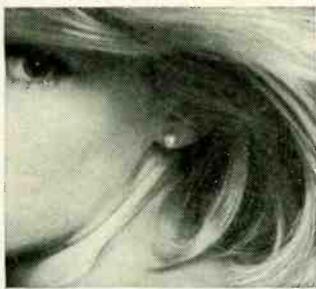SUPEREX ELECTRONICS
1 Radford Place, Yonkers, N.Y.



Circle 30 on reader's service card

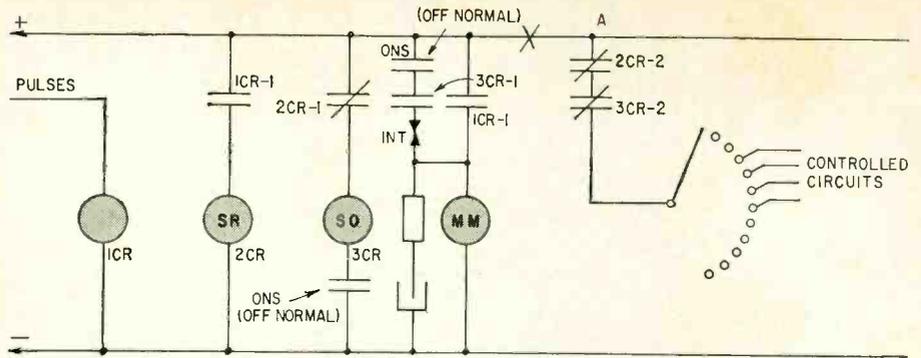


Fig. 4—This circuit makes switch step forward to "home" at end of its sequence.

ROTARY STEPPING SWITCHES

continued from page 41

lected contact is connected to a battery (the B + line), starting a controlling pulse, and slow-operate relay 3CR is energized. After another delay this relay stops the controlling pulse by opening normally closed contact 3CR-1 in the wiper circuit. Second, 3CR closes contact 3CR-2 which energizes the release magnet on the stepping switch.

Note the use of off-normal contacts (ONS). Relay 3CR cannot energize until the switch is away from "home." Notice too that neither relay 3CR nor the release magnet can energize until 2CR has released. Since 3CR is slow operating (meaning also slow release), and the wiper is connected through normally closed contact 3CR-1,

the switch wiper remains disconnected until after the switch has returned home. What has happened? Incoming pulses have selected a circuit, a control pulse has been delivered, and the switch has been returned home. Duration of the control pulse depends on 3CR. The pulse lasts as long as it takes this relay to open contact 3CR-1 in the wiper circuit.

Fig. 4, a similar circuit, outlines the circuit for a rotary switch without a release magnet. In this case 3CR also closes a circuit to the interrupter, allowing the switch to step forward to "home" by itself, which will happen in about 1/3 second. 3CR must remain closed that long. The off-normal con-

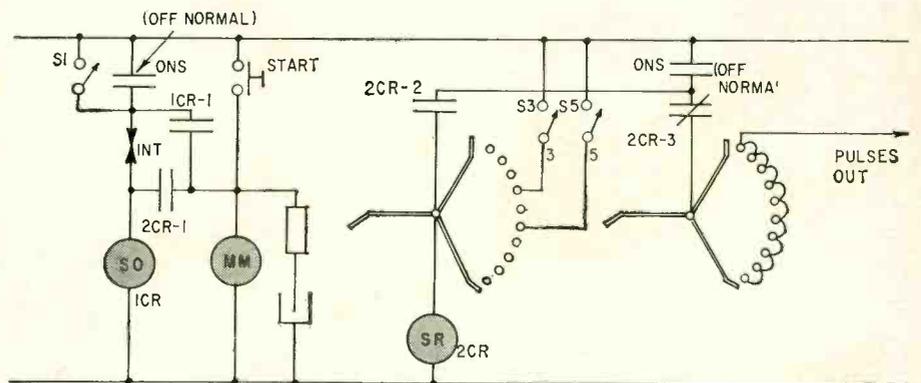


Fig. 5—When S3 closes, 3 pulses are transmitted and switch then steps "home."

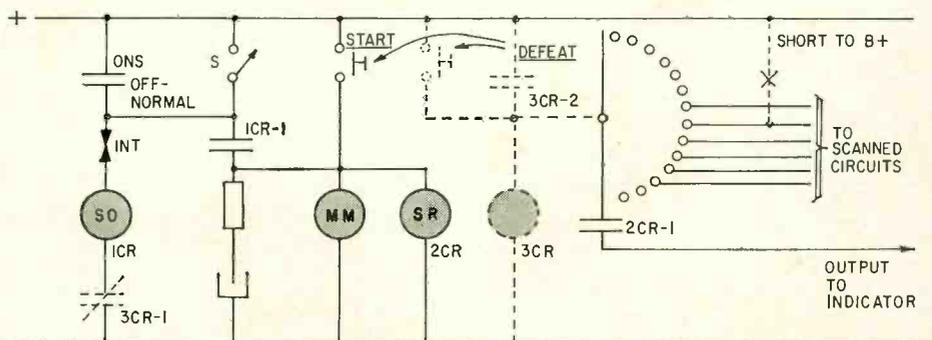


Fig. 6—When activated, this circuit will scan all the switch contacts, then stop.

facts will stop the switch. In using rotary switches in the self-stepping mode, it's best never to rely on a relay to stop a switch. The interrupter contacts are much faster than any relay, unless they are *slowed down* by a relay.

Such is the case in the circuit of Fig. 5 (although even so, the off-normal springs are relied upon to stop the switch). This is a pulse-sending circuit. Switches S3 and S5 are two of a set of nine. (The others aren't shown for simplicity's sake. Note also that usually no more than one or two switchbanks are shown, even though the switch may have several more.)

With S1 open, and S5 closed, the following actions occur: Push the START button. The rotary switch takes one step and gets off normal. This condition closes a path to interrupter I, which energizes slow-operating relay 1CR. After a pause, 1CR energizes the motor magnet for yet another step, and so on. Each time the rotary switch steps, a pulse is sent out over the second bank of contacts. When the switch gets to step 5, five pulses have been sent out. Now relay 2CR is energized through the first switch level. This cuts off the pulse line for outgoing pulses. It also connects the motor magnet directly to the interrupter, and the switch steps rapidly forward to home. Since 2CR is a slow-release relay, all these actions can happen while 2CR is closed. In home position the off-normal springs cut off the magnet and the switch stops.

If switch S1 is closed and S2 through S10 are left open, the sender will continue to send out pulses so long as S1 is left closed. The pulse rate depends on 1CR, and can be chosen as slow as 2 operations per second. Normally it will allow 10 pulses per second.

Automatic scanning

The same principle of slow stepping is used in the circuit of Fig. 6, a device that will scan all switch contacts, for example, to detect a voltage or a ground. A relay can be included in the output circuit to stop this switch when such an event occurs. This option is shown in dotted lines. Otherwise the circuit will scan once and stop, or, with switch S closed, will scan continuously.

In all rotary stepping-switch circuits it is imperative that careful attention be given to timing. In designing a stepping-switch relay circuit, a table showing the sequence of events can be very helpful. This will be covered in the next installment, along with information on how to make such a table, and how to select 1 out of 100 points using only 2 rotary switches and a few relays.



To be continued

Get Top **PERFORMANCE** from your Car! **Buy The Best!**



DELTA'S Remarkable, Proven MARK TEN CAPACITIVE DISCHARGE IGNITION SYSTEM

ONLY
\$4495
ppd.

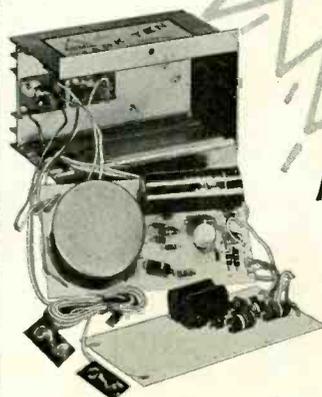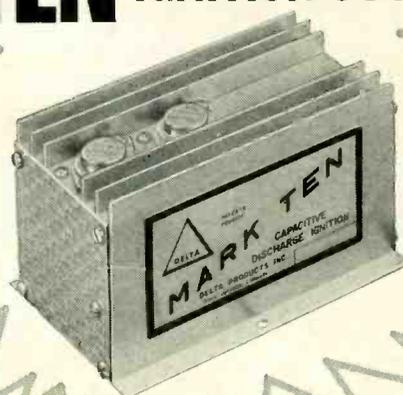

Available in Easy-to-Build

DELTAKIT® ONLY
ASSEMBLE IT YOURSELF! **\$2995**
ppd.

You've read about the Mark Ten in Radio Electronics, Electronics World, Mechanix Illustrated, Electronics, Popular Mechanics and other leading publications! Now discover what dramatic improvement in performance with capacitive discharge ignition is yours for your car, truck, jeep, boat—any vehicle! Delta's remarkable electronic achievement—on the market since 1963 and so unique that a patent has been granted—saves on gas, promotes better acceleration, gives your car that zip you've always wanted. Even Detroit has finally come around. Delta's Mark Ten, the original, the proven winner from Sebring to Suburbia, has set new records of ignition benefits attested to by thousands of satisfied purchasers. No re-wiring necessary. Works on literally any type of gasoline engine. Satisfaction guaranteed.

Order from coupon below, specifying car make, voltage and polarity. Like to build your own? Order a Deltakit® and save!

COMPARE THESE PROVEN BENEFITS!...

- ▲ DRAMATIC INCREASE IN ACCELERATION
- ▲ LONGER POINT AND PLUG LIFE
- ▲ IMPROVED GASOLINE MILEAGE
- ▲ MORE COMPLETE COMBUSTION
- ▲ SMOOTHER PERFORMANCE

Order Your Mark Ten Today! Shipped Postpaid at Once.



DELTA PRODUCTS, INC.

P.O. BOX 1147 RE — GRAND JUNCTION, COLORADO 81501

Enclosed is \$ _____ Ship prepaid. Ship C.O.D.
 Mark Tens (Assembled) @ \$44.95 Mark Tens (Deltakit®) @ \$29.95
(12 volt positive or negative ground only)

Specify 6 Volt: Negative Ground only.
 12 Volt: Specify Positive Ground Negative Ground

Car Year _____ Make _____

Name _____

Address _____

City/State _____ Zip _____

Instant Gift-Solving Guide From Heath...

Now There Are 3 Heathkit Color TV's To Choose From

Introducing The NEW Deluxe Heathkit "227" Color TV

Exclusive Heathkit Self-Servicing Features. Like the famous Heathkit "295" and "180" color TV's, the new Heathkit "227" features a built-in dot generator plus full color photos and simple instructions so you can set-up, converge and maintain the best color pictures at all times. Add to this the detailed trouble-shooting charts in the manual, and you put an end to costly TV service calls for periodic picture convergence and minor repairs. No other brand of color TV has this money-saving self-servicing feature.

Advanced Performance Features. Boasts new RCA Perma-Chrome picture tube with 227 sq. in. rectangular viewing area for 40% brighter pictures . . . 24,000 v. regulated picture power and improved "rare earth" phosphors for more brilliant, livelier colors . . . new improved low voltage power supply with boosted B+ for best operation . . . automatic de-gaussing combined with exclusive Heath Magna-Shield that "cleans" the picture every-time you turn the set on from a "cold" start, and keeps colors pure and clean regardless of set movement or placement . . . automatic color control and gated automatic gain control to reduce color fade and insure steady, flutter-free pictures even under adverse conditions . . . preassembled & aligned 3-stage IF . . . preassembled & aligned 2-speed transistor UHF tuner and deluxe VHF turret tuner with "memory" fine tuning . . . 300 & 75 ohm VHF antenna inputs . . . two hi-fi sound outputs . . . 4" x 6" 8 ohm speaker . . . one-piece mask & control panel for simple installation in a wall, your custom cabinet or either optional Heath factory-assembled cabinets. Build in 25 hours.

- Kit GR-227**, (everything except cabinet) . . . \$42 dn., as low as \$25 mo. **\$419.95**
GRA-227-1, Walnut cabinet. . . no money dn., \$6 mo. **\$59.95**
GRA-227-2, Mediterranean Oak cabinet (shown above), . . . no money dn., \$10 mo. **\$94.50**



Kit GR-227
\$419⁹⁵
 (less cabinet)
 \$25 mo.

Kit GRA-27
\$19⁹⁵



New Remote Control For Heathkit Color TV

Now change channels and turn your Heathkit color TV off and on from the comfort of your armchair with this new remote control kit. Use with Heathkit GR-227, GR-295 and GR-180 color TV's. Includes 20' cable.



Kit GR-295
\$479⁹⁵
 (less cabinet)
 \$42 mo.

Deluxe Heathkit "295" Color TV

Has same high performance features and built-in servicing facilities as new GR-227, except for 295 sq. in. viewing area (industry's largest picture) . . . 25,000 volt picture power . . . universal main control panel for versatile in-wall installation . . . and 6" x 9" speaker.

- Kit GR-295**, (everything except cabinet), 131 lbs. . . . \$48 dn., \$42 mo. **\$479.95**
GRA-295-1, Walnut cabinet (shown above), 35 lbs. . . . no money dn., \$7 mo. **\$62.95**
 Other cabinets from \$94.50



Kit GR-180
\$349⁹⁵
 (less cabinet & cart)
 \$30 mo.


Deluxe Heathkit "180" Color TV

Same high performance features and exclusive self-servicing facilities as new GR-227 (above) except for 180 sq. in. viewing area.

- Kit GR-180**, (everything except cabinet), 102 lbs. . . . \$35 dn., \$30 mo. **\$349.95**
GRA-180-5, table model cabinet & mobile cart (shown above), 57 lbs. . . . no money dn., \$5 mo. **\$39.95**
 Other cabinets from \$24.95

Deluxe 12" Transistor Portable B&W TV - First Kit With Integrated Circuit

Unusually sensitive performance. Plays anywhere . . . runs on household 117 v. AC, any 12 v. battery, or optional rechargeable battery pack (\$39.95); receives all channels; new integrated sound circuit replaces 39 components; preassembled, prealigned tuners; high gain IF strip; Gated AGC for steady, jitter-free pictures; front-panel mounted speaker; assembles in only 10 hours. Rugged high impact plastic cabinet measures a compact 11 1/2" H x 15 3/4" W x 9 3/8" D. 27 lbs.

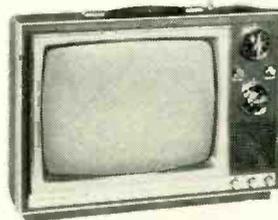

Kit GR-104
\$119⁹⁵
 \$11 mo.

Kit GR-104, 27 lbs. . . . no money dn., \$11 mo. **\$119.95**

No Money Down On \$25 to \$300 Orders — Write For Credit Form

Circle 33 on reader's service card

Turn Page For 18 More Solutions

Enjoy The Sounds Of Christmas With A Heathkit® Stereo System




Kit AR-17
\$72⁹⁵
 (less cabinet)
 \$8 mo.

NEW! Lowest Cost Solid-State Stereo Receiver

Features wide 18-60,000 Hz response @ ±1 db at full 5 watts RMS power per channel . . . 14 watts music power . . . inputs for phono and auxiliary . . . automatic stereo indicator . . . outputs for 4 thru 16 ohm speakers . . . adjustable phase for best stereo . . . flywheel tuning . . . and compact 9 3/4" D. x 2 7/8" H. x 11 1/4" W. size, 12 lbs. Optional factory assembled cabinets (walnut \$7.95, beige metal \$3.50).

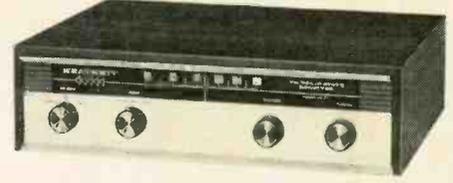Kit AR-17, (less cab.) 12 lbs. . . no money dn., \$8 mo. **\$72.95**



Kit AR-27
\$49⁹⁵
 (less cabinet)
 \$5 mo.

NEW! Low Cost Solid-State FM Mono Receiver

Features cool, solid-state circuit . . . 7 watts music, 5 watts RMS power . . . 18 to 60,000 Hz response @ ±1 db . . . inputs for phono and auxiliary . . . outputs for 4 thru 16 ohm speakers . . . flywheel tuning . . . front panel controls . . . preassembled & aligned FM front-end . . . and 9 3/4" D. x 2 7/8" H. x 11 1/4" W. bookshelf size, 9 lbs. Optional Heath factory assembled cabinets (walnut veneer \$7.95, beige metal \$3.50).

Kit AR-27, (less cab.) 9 lbs. . . no money dn., \$5 mo. . . **\$49.95**



Kit AR-15
\$329⁹⁵
 (less cabinet)
 \$28 mo.
 Assembled ARW-15
\$499⁵⁰
 (less cabinet)
 \$43 mo.

World's Most Advanced Stereo Receiver . . . Choose Kit Or Factory Assembled

Acclaimed by owners & audio experts for its advanced features like integrated circuits and crystal filters in the IF amplifier section; ultra-sensitive FET FM tuner; 150 watts dynamic music power; complete AM, FM and FM stereo listening; positive circuit protection; all-silicon transistors; "black magic" panel lighting; stereo only switch; adjustable phase control for best stereo and many more. 34 lbs. Optional wrap-around walnut cabinet \$19.95.

Kit AR-15 (less cab.), 34 lbs. . . \$33 dn., \$28 mo. . . . **\$329.95**

Assembled ARW-15, (less cab.), 34 lbs. . . \$50 dn., \$43 mo. . . . **\$499.50**

NEW! Heathkit Stereo Headphone Control Box



Kit AC-17
\$7⁹⁵

Now enjoy the convenience of switching from speaker to private headphone listening without leaving the comfort of your favorite chair. Connects to any headphone regardless of power, and has standard jacks to accommodate two sets of any impedance, 3 or 4 connector, stereo or mono headset. Tandem volume and balance controls. About the size of a pack of cigarettes. Includes 20' cable.

Kit AC-17, 3 lbs. . . . **\$7.95**

NEW! Exclusive Heath Hi-Fi Furniture . . . Fully Assembled And Finished

Contemporary Walnut Stereo/Hi-Fi Cabinet Ensemble Complements Modern Furnishings

Masterfully crafted of fine veneers and solids with walnut finish. Statuary Bronze handles. Equipment cabinet features adjustable shelves to accommodate all makes of hi-fi components, record storage or tape recorder compartment, turntable compartment. Speaker cabinet features special Tubular-Duct Reflex design for matching 8" or 12" speakers, plus slot for a horn tweeter.

Model AE-37, equipment cabinet. . .
 no money dn., \$12 mo. . . . **\$125.00**
 Model AEA-37-1, speaker cabinet. . .
 no money dn., \$6 mo. . . . each **\$59.50**

Early American Stereo/Hi-Fi Cabinet Ensemble

Early American richness with modern component layout. Constructed of specially-selected solids and veneers finished in popular Salem-Maple, Statuary Bronze handles. Equipment cabinet has adjustable shelves to accommodate any make hi-fi component, record storage or tape recorder compartment, turntable compartment. Speaker cabinet can be matched to any 8" or 12" speaker . . . has slot for horn tweeter.


Model AE-47, equipment cabinet. . .
 no money dn., \$13 mo. . . . **\$135.00**
 Model AEA-47-1, speaker cabinet. . .
 no money dn., \$7 mo. . . . each **\$64.50**

Mediterranean Pecan Stereo/Hi-Fi Cabinet Ensemble


Beautifully constructed of fine furniture solids and veneers with Pecan finish. Statuary Bronze handles. Equipment cabinet has adjustable shelves to house any make hi-fi component, record storage or tape recorder compartment, turntable compartment. Speaker cabinet can be matched to any 8" or 12" speaker . . . has slot for horn tweeter.

Model AE-57, equipment cabinet. . .
 no money dn., \$14 mo. . . . **\$150.00**
 Model AEA-57-1, speaker cabinet. . .
 no money dn., \$8 mo. . . . each **\$74.50**

Complete Ensemble
\$244⁰⁰

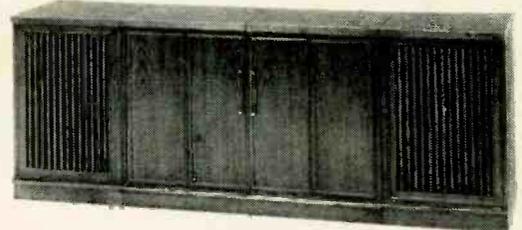

Complete Ensemble
\$264⁰⁰

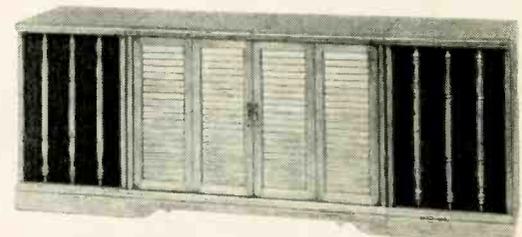


Complete Ensemble
\$299⁰⁰



Enjoy Widest Kit Selection, Easy Credit,

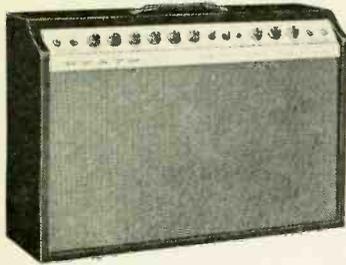"Starmaker" Dual-Channel Solid-State Guitar Amplifier



Features 25 watts EIA, 60 watts peak power; two channels, each with two inputs; handles lead guitar, singer's mike; tremolo & reverb; two 12" speakers; line bypass reversing switch for hum reduction; foot switches; black vinyl-covered wood cabinet with aluminum front panel & chrome knobs. 52 lbs.

Kit TA-16 **\$134⁹⁵** Assembled TAW-16 **\$199⁹⁵**
 \$13 mo. \$19 mo.

NEW! Single-Channel Solid-State Guitar Amplifier



Compare To Amps Costing \$175 & More! Boasts 20 watts EIA, 40 watts peak power; tremolo & reverb; two inputs for lead guitars, singer's mike; 12" speaker; line bypass reversing switch to reduce hum; foot switches; transformer power supply; black vinyl-covered wood cabinet with aluminum front panel & chrome knobs. 35 lbs.

Kit TA-27 **\$89⁹⁵** Assembled TAW-27 **\$134⁹⁵**
 \$9 mo. \$13 mo.

NEW! Deluxe Solid-State Combo Amplifier & Speaker System... Choose Kit Or Factory Assembled

Kit TA-17 Amplifier

\$175⁰⁰

\$17 mo.
(Wired TAW-17, \$275)

Kit TA-17-1 Speaker System


\$120⁰⁰

\$11 mo.
(Wired TAW-17-1, \$150)

Kit TAS-17-2 Special Combination Offer!
2 Speaker Systems & Amplifier
Save \$20

\$395⁰⁰

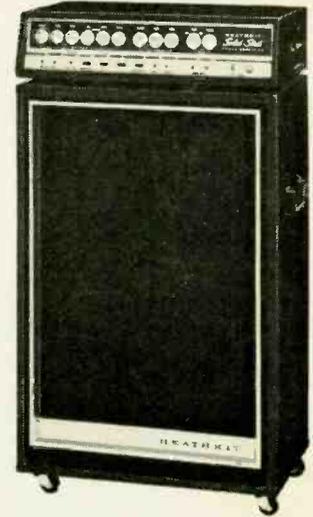\$40 dn.
\$34 mo.
(Wired TAW-17-2, \$545)



All the "big sound" features every combo wants... tremolo, built-in "fuzz", brightness, reverb, separate bass and treble boost and more. Delivers a shattering 120 watts EIA music power (240 watts peak power) through two TA-17-1 speakers... or 90 watts through one TA-17-1 speaker. Features 3 independent input channels, each with two inputs. Handles lead or bass guitars, combo organ, accordion, singer's mike, or even a record changer. All front panel controls keep you in full command of all the action.

Speaker system features two 12" woofers, special horn driver and matching black vinyl-covered wood cabinet with casters & handles for easy mobility.

NEW! Heathkit Jr.® Guitar Amplifier



Ideal For Youngsters! Build in an evening. All solid-state. 9 watts music power. 8" speaker. Single channel, two inputs. Variable tremolo. Volume & tone controls. Red vinyl-covered wood cabinet with striped grille cloth and carrying handle. 12 lbs.

Kit JK-37 **\$29⁹⁵**
\$5 mo.


NEW! Heathkit Jr.® Portable Phonograph



All solid-state. Plays all 4 speeds, all record sizes. Crystal cartridge with sapphire stylus for all types of records; 4" speaker; built-in 45 rpm adaptor; prebuilt turntable & hard-board cabinet. 117 v. AC, 60 Hz operation. 11 lbs.

Kit JK-17 **\$19⁹⁵**

Heathkit Jr.® Electronic Workshop "19"

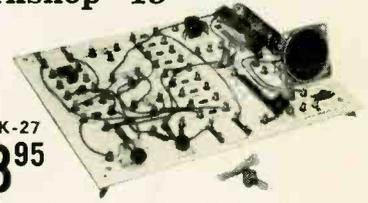

Kit JK-27 **\$13⁹⁵**

Ideal gift for any youngster who wants to learn electronics. Contains principles of operation & instructions for building 19 electronic projects... PA system, transistor radio, burglar alarm, etc. Spring-type connectors. Safe, flashlight battery operation. 4 lbs.

NEW! Professional 10-Band Shortwave Listener's Receiver

Kit SB-310 **\$249⁰⁰**
\$23 mo.



(SB-600 8 Ohm, 6" x 9" Speaker, \$18.95)

Covers 6 shortwave bands (49, 41, 31, 25, 19 & 16 meters)... 80, 40 & 20 meter ham bands... 11 meter CB. Includes 5 kHz crystal filter for AM, SSB and CW listening. Features selectivity that slices stations down to last kHz... no more guessing station identities; 11-tube circuit; crystal-controlled front-end for same rate tuning on all bands; prebuilt & aligned LMO; tuning dial to knob ratio 4 to 1; and many more deluxe SWL features. 2-tone green metal cabinet included. Optional crystal filters for optimum CW & SSB available. 20 lbs.

Deluxe 23-Channel CB Transceiver

Now FCC Type Accepted! All solid-state circuit. Full 5-watts. All crystal-controlled transmit & receive channels. Built-in speaker; "S" meter; squelch control; and other deluxe features. 12 v. neg. gnd. operation. AC power supply & crystal pack optional. 8 lbs.



Assembled GWW-14A **\$124⁹⁵**
\$12 mo.

NEW! Amateur Novice CW Transceiver



Kit HW-16 **\$99⁵⁰** \$10 mo.

Get on-the-air at lowest cost. CW operation on first 250 kHz of 80, 40 & 15 meter bands. 75 watt CW input, up to 90 watts for general class. "Break-in" CW operation. Crystal control transmit with VFO receiver tuning. Metal cabinet, easy to build. 25 lbs.

Circle 33 on reader's service card

Direct-To-You Delivery From Heath

Save Up To \$500 On This Heathkit® / Thomas "Paramount" Transistor Theatre Organ



Kit TO-67
\$995⁰⁰

(including bench)
Write for
credit details

All Genuine Thomas Factory-Fabricated Parts. Features 15 manual, 4 pedal voices; instant-play Color-Glo; all solid-state circuit; 200 watts peak power; two separate speaker systems . . . 2-speed rotating Leslie plus main system with two 12" speakers; two 44-note keyboards; professional horseshoe console with stop tablets; 28 notes of chimes; 13-note bass pedals; selective repeat & attack percussion; reverb; stereo headset outlet; assembled walnut finish hardwood cabinet and bench; and more. 265 lbs. 7", 33-1/3 rpm demonstration record 50c.

America's Lowest Cost Solid-State Organ

Save Up to \$205! Features instant-play Color-Glo; 10 organ voices; 13-note bass pedals; repeat percussion; two 37-note keyboards; 75 watt peak power; vibrato; matching preassembled walnut cabinet & bench; 5-year warranty on plug-in tone generators. 172 lbs. 7", 33-1/3 rpm demonstration record 50c.



Kit GD-325B
\$394⁹⁰

\$40 dn., \$34 mo.

NEW! Heathkit® / Thomas Organ Accessories

Exclusive Band Box Percussion


Automatically or manually adds 10 percussion voices to any Heathkit/Thomas organ. Build & install in 12 hours.

Kit TOA-67-1, no money dn., \$14 mo. **\$145.00**

Exclusive Playmate Rhythm Maker


Adds 15 fascinating rhythms to any Heathkit/Thomas Organ. Requires Band Box percussion (above) for operation.

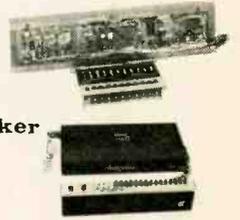Kit TOA-67-5, no money dn., \$18 mo. **\$189.90**



NEW! FM Stereo Generator

Kit IG-37
\$79⁹⁵
\$8 mo.

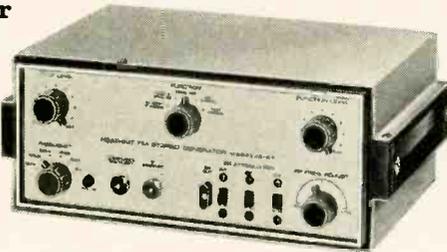

For RF, IF and FM stereo alignment. Switch selection of 400 Hz, 1000 Hz, 5000 Hz, 19 kHz and 65 kHz or 67 kHz SCA signals. Crystal controlled 19 kHz pilot signal adjustable from 0 to 10%. 100 MHz sweep signal (adjustable ±2 MHz). Phase test capability. 12 lbs.

NEW! Variable Regulated High Voltage Power Supply


Kit IP-17
\$59⁹⁵
\$6 mo.
Assembled IPW-17
\$89⁹⁵
\$9 mo.



Features 6 v. and 12 v. AC filament voltages; also furnishes B+ from 0 to 400 volts DC, bias from 0 to -100 volts DC; separate panel meters monitor B+ output voltage & current; voltmeter switched to read C- volts; output terminals isolated for safety; high voltage and bias may be switched "off" with filaments still "on" for maximum testing efficiency and safety. 17 lbs.

NEW! Deluxe Solid-State Volt-Ohm-Meter

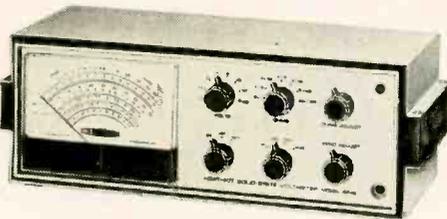Kit IM-16
\$44⁹⁵
\$5 mo.
Assembled IMW-16
\$64⁹⁵
\$7 mo.




Battery plus built-in AC power. 8 DC and 8 AC volt ranges, 0.5 v. to 1500 v. full scale; 7 ohmmeter ranges x1 (10 ohms center scale), x10, x100, x1k, x10k, x100k and x1 megohm; 11 megohm input resistance on DC & AC ranges; 6" 100 uA meter; single test probe. 10 lbs.

Solid-State High Impedance Volt-Ohm Milliammeter

Kit IM-25
\$80⁰⁰
\$8 mo.
Assembled IMW-25
\$115⁰⁰
\$11 mo.



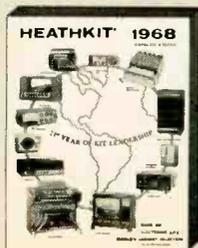Features 9 AC & 9 DC volt ranges from 150 mv to 1500 v. full scale; 7 resistance ranges, 10 ohms center scale with multipliers x1, x10, x100, x1k, x10k, x100k, x1 meg; 11 current ranges from 15 uA to 1.5 A; 11 megohm input resistance on DC, 10 megohm on AC; 6" 200 uA meter; Built-in battery or 120/240 v. AC, 50-60 Hz. 10 lbs.



NEW
FREE 1968
CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-11
Benton Harbor, Michigan 49022
In Canada, Daystrom Ltd.



Enclosed is \$ _____, including shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog.

Please send Credit Application.

Name _____

Address _____

City _____

State _____

Zip _____

Prices & specifications subject to change without notice.

CL--309

Weller®

...the soldering tools professionals depend on



The original Dual Heat Soldering Guns

Preferred by technicians for their fast heating copper tips, exclusive trigger-controlled dual heat, and high soldering efficiency. Available in 3 watt-age sizes, each with spotlight.

100/140-watt Model 8200, 145/210-watt Model D-440, and 240/325-watt Model D-550. Also in complete kits:

- **Model 8200PK** includes 100/140 watt gun, extra tips, tip-changing wrench, flux brush, soldering aid and solder
- **Model D-550PK** heavy-duty 240/325 watt gun kit with soldering, cutting and smoothing tips, wrench and solder

Dependable MARKSMAN Irons in a size for every job




Ideal for deep chassis work and continuous-duty soldering, Marksman irons outperform others of comparable size and weight. All five feature long-reach stainless steel barrels and replaceable tips.

- 25-watt, 1¾-oz. Model SP-23 with 1/8" tip (In kit with extra tips, soldering aid, solder—Model SP-23K)
- 40-watt, 2-oz. Model SP-40 with 1/4" tip
- 80-watt, 4-oz. Model SP-80 with 3/8" tip
- 120-watt, 10-oz. Model SP-120 with 1/2" tip
- 175-watt, 16-oz. Model SP-175 with 5/8" tip

NOW a BATTERY OPERATED IRON for field servicing

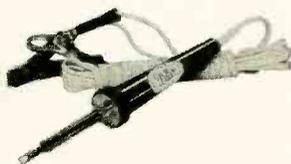Use this lightweight service tool for automotive wiring, model planes, or mobile communications. Works from any 12 volt battery or 12-14 volt AC/DC supply. Supplied complete with long-life patented "Temperature Sensing" tip, 12-ft. power cord and terminal clips. Model TCP-12—12 volt; Model TCP-24—24-28 volts.




Complete Weller Line includes replacement tips and solder at your Electronic Parts Distributor

WELLER ELECTRIC CORPORATION, Easton, Pa.

WORLD LEADER IN SOLDERING TECHNOLOGY

Circle 34 on reader's service card

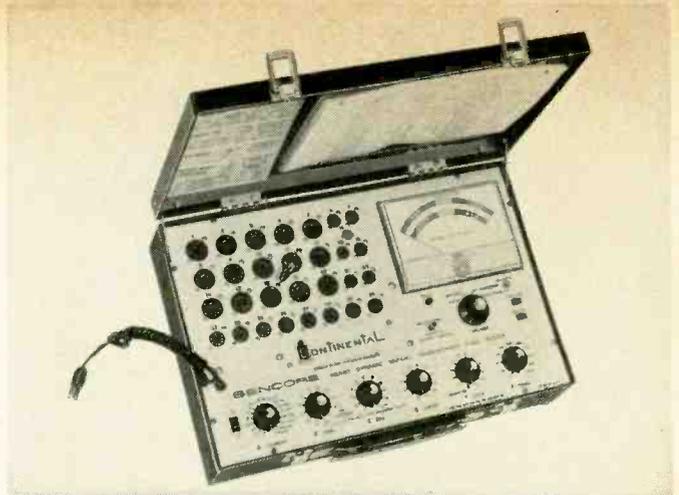

EQUIPMENT REPORT

Sencore MU-140 Tube Tester

Circle 35 on reader's service card

MORE THAN 3000 TUBE TYPES, including industrial and receiving, can be checked on the MU-140 Continental mutual-conductance tube tester. Compactrons, nuvistors and the new 10-pin decal types as well as the more conventional tubes can be checked for emission, mutual conductance, shorts, leakage and grid emission.

If you should find a tube that isn't listed, look up a similar type and use the settings indicated.

Should a new tube type require a new test position, the MU-140 has spare openings for four additional tube sockets. These openings are on the panel and are covered with a plate. Sencore will supply detailed hookup instructions for wiring in new sockets when they are needed.

The cathode-emission test is fast; only three controls have to be set—heater voltage, control-grid and load selector. A novel circuit is used here. Older emission testers tied all the elements except the cathode together and then metered the cathode current. The MU-140 measures control-grid current—most current flows from cathode to grid.

Tests for shorts are made with a low voltage, to prevent damage to closely spaced elements, such as in nuvistors and frame-grid tube types. Each element in the tube is checked against all the others for shorts. A special position for heater-cathode shorts is used.

For mutual-conductance tests, a special ABC (Automatic Bias Control) circuit automatically sets up bias and plate current and eliminates the need for adjustable controls. Only the main load is variable.

Mutual-conductance measurements require an ac signal. The test signal is a 5000-Hz square wave generated by a transistor multivibrator circuit. Its output voltage is regulated by the setting of the F SIGNAL control.

The meter circuit is protected by a diode and is calibrated to read "100" on the scale when the tube lives up to its rated G_m . The customary "BAD-?-GOOD" scale is used, as well as a numerical scale marked from zero to 120.

Grid emission or leakage is monitored by the meter. The dividing line between "GOOD" and "?" on the meter indicates approximately 200 megohms of grid leakage. The line between "BAD" and "?" is about 100 megohms. This is a sensitive test; grid current as small as 0.5 μA shows.

This grid test can catch the 6AL5 with "grid" emission. Yes, I know—this is contamination of the mount in the tube, but it'll shake you up the first time you run across it! Any diode which shows "grid" emission will affect the operation of sensitive detector circuits.

All in all, the MU-140 is a well-built instrument. —Wm. Darragh

Price: \$179.50


R-E

Stereo Headphone Control

continued from page 36

than No. 22 for the leads that will carry the full speaker current (heavy lines drawn on the schematic).

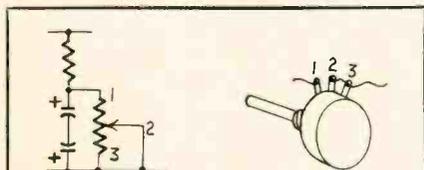The photos show all the details for wiring the control center. The solder-lug strip mounting is soldered to the back of the balance control.



The Stereo Headphone Control Center works as described. It is important to try to obtain log-taper (audio taper) controls for R6, otherwise the change from flat response to full boost occurs all in the first few degrees of rotation from the counter-clockwise stop.

Be sure to wire the control exactly as shown. If you don't, the taper is in effect reversed and the rate of change will be even more extreme than with a linear-taper control.

If the electrolytic capacitors have uninsulated metal cases, as the ones in this model did, insulate them with tape to prevent their touching the panel. The panel must be electrically common to the common side of the circuit unless you want to provide insulating bushings for the phone jacks.

Modifications

Of course you can provide only one jack if you wish, or three or more. Volume will diminish as you parallel more sets of phones. If you like, you can provide a separate volume control for each headset. You can, in fact, duplicate the portion of the circuit after the switching (to the right of the dashed line X-X on the schematic) so that each headset has full, separate control facilities.

If you like your headphone music extremely loud, you may have to forgo the bass-boost circuit (R5, R6 and R7 and C1, C2, C3 and C4). To provide 6 dB of bass boost, the circuit must introduce 6 dB of loss everywhere else in the spectrum, except at the low frequencies. In a passive equalizer, there is no way around this fact of life. So if you need loudness, disconnect or omit the bass boost circuit.

Connecting the thing

Fig. 2 shows how the control center is to be connected to an amplifier. Note that the common terminal on the control center goes to the amplifier chassis, not to either of the speaker

terminals often labeled "common" or "C". The reason is that in many amplifiers the so-called "common" terminals are *not* common to each other or to the chassis, and cannot be connected together without disrupting some circuit function.

This connection is for headphone operation only. The normal connection to the speakers is in no way affected by the addition of the box if you follow the scheme given here. The speakers can be turned off or on by the selector switch in the control center, but this is done by interrupting the *high* (4-, 8-

or 16-ohm) side of the wiring, not by disturbing the connection to the amplifier's low side.

Flat, five-conductor antenna-rotator cable is handy for making the connections between control center and amplifier because it can be slipped under a rug or run alongside of base-board molding.

The wire should be No. 22 or heavier. Avoid running more than about 50 feet to prevent a sizable portion of your expensive amplifier power to be dissipated in the wiring. **R-E**



JEWELRY for your best gal— STUNNING PINS

from
Perma-Power

you get them **FREE** with either
of these **BRITENER PACKS**

Whether it's a special occasion or an unexpected surprise—the gals *all* love to receive jewelry. Give your best gal one of these unusual Gold-Fashioned pins (they'd cost as much as \$4.95 in an exclusive shop). Watch her face brighten up!

Brightening up is a Perma-Power specialty, although it's usually directed at faded picture tubes. Vu-Brite and Tu-Brite boost picture tube brightness, and boost your popularity with your customer. Always keep both kinds on hand!



The pin is free (many unusual designs)—when you buy 12 Vu-Brites, Series or Parallel, at the special \$9.95 price.



You also get one of these "Gold-Fashioned" beauties with a pack of 4 Tu-Brites. If the base is right, the boost is right. Only \$8.95.

NEW! 110° Button Base Vu-Brite/Jewelry Pack . . . \$8.95

6 model C-411 Parallel or 5 model C-412 Series

SEE YOUR DISTRIBUTOR NOW FOR BOTH THESE SPECIALS.

PERMA-POWER COMPANY

5740 North Tripp Avenue, Chicago, Ill. 60646
Phone (312) 539-7171

RADIO-ELECTRONICS READER'S SERVICE

Here's how you can get manufacturers' literature fast:

1. Tear out the post card on the facing page. Clearly print or type your name and address.

Include zip code! Manufacturers will not guarantee to fill your requests unless your zip code is on the reader service card!

2. Circle the number on the card that corresponds to the number appearing at the bottom of the **New Products, New Literature or Equipment Report** in which you are interested.

For literature on products advertised in this issue, circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested. Use the convenient index below to locate quickly a particular advertisement.

3. Mail the card to us (no postage required in U.S.A.)

Advertisements in this issue offering free literature (see the advertisements for products being advertised):

AEROVOX CORPORATION (Distributor Div.) (Pg. 16)	Circle 18
ALLIED RADIO CORP. (Pg. 85)	Circle 117
AMPEREX ELECTRONIC CORP. (Second Cover)	Circle 7
ARCO ELECTRONICS (A division of Loral Corporation) (Pg. 5)	Circle 10
ARROW FASTENER CO., INC. (Pg. 82)	Circle 113
ARTISAN ORGANS (Pg. 82)	Circle 110
B & K (Division of Dynascan Corporation) (Pg. 83)	Circle 115
BARKER PRODUCTS CO. (Audio Division of Component Manufacturing Service, Inc.) (Pg. 24)	Circle 24
BROOKS RADIO & TV CORP. (Pg. 92-93)	Circle 124
BURSTEIN-APPLEBEE (Pg. 87)	Circle 119
CASTLE TV TUNER SERVICE, INC. (Pg. 95)	Circle 128
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 15)	Circle 17
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 18-21)	Circle 20
CORNELL ELECTRONICS CO. (Pg. 100)	Circle 145
DATAK CORPORATION, THE (Pg. 82)	Circle 111
DELTA PRODUCTS, INC. (Pg. 67)	Circle 32
EDMUND SCIENTIFIC CO. (Pg. 101)	Circle 146
EICO ELECTRONIC INSTRUMENT CO., INC. (Third Cover)	Circle 149
FINNEY CO. (Pg. 79)	Circle 107
GC ELECTRONICS CO. (Pg. 14)	Circle 16
GOODHEART CO., INC., R. E. (Pg. 93)	Circle 125
HEALD ENGINEERING COLLEGE (Pg. 95)	Circle 129
HEATH COMPANY (Pg. 68-71)	Circle 33

WE WANT TO KNOW MORE ABOUT YOU! HELP US COMPLETE OUR READER PROFILE

At the bottom of the Reader's Service Card you'll find numbers from 1 through 6. Read the following statements and then circle the number (or numbers) on the Reader's Service Card corresponding to the statement (or statements) that best describes you.


1. I do no electronic servicing (except of my own equipment).
2. Electronic servicing is my full-time occupation. I service color TV receivers.
3. Electronic servicing is my full-time occupation. I do not service color TV receivers.
4. Electronic servicing is my full-time occupation. I service industrial electronic equipment.
5. I do part-time electronic servicing. I service color TV receivers.
6. I do part-time electronic servicing. I do not service color TV receivers.

INTERNATIONAL CRYSTAL MFG. CO., INC. (Pg. 102)	Circle 148
LAFAYETTE RADIO ELECTRONICS (Pg. 89-90)	Circle 121
MALLORY DISTRIBUTOR PRODUCTS COMPANY (Div. of P. R. Mallory & Co., Inc.) (Pg. 23)	Circle 23
MIKE QUINN ELECTRONICS (Pg. 98)	Circle 141
MUSIC ASSOCIATED (Pg. 92)	Circle 123
OLSON ELECTRONICS, INC. (Pg. 96)	Circle 130
PERMA-POWER COMPANY (Pg. 73)	Circle 35
PERMOFLUX CORP. (Pg. 95)	Circle 127
POLY PAKS (Pg. 101)	Circle 147
QUIETROLE CO. (Pg. 82)	Circle 112
RADAR DEVICES (Pg. 1)	Circle 8
READING IMPROVEMENT PROGRAM (Pg. 97)	Circle 132
RYE INDUSTRIES, INC. (Pg. 86, 87)	Circle 118
S & A ELECTRONICS INC. (Pg. 91)	Circle 122
SAMS & CO., HOWARD W. (Pg. 25)	Circle 25
SAMS & CO., INC., HOWARD W. (Pg. 65-66)	Circle 31
SAMS & CO., INC., HOWARD W. (Pg. 78)	Circle 106
SENCORE (Pg. 81)	Circle 109
SENCORE (Pg. 88)	Circle 120
SOLID STATE SALES (Pg. 99)	Circle 143
SONY CORP. OF AMERICA (Pg. 22)	Circle 21
SONY/SUPERSCOPE (Pg. 63)	Circle 29
SPRAGUE PRODUCTS COMPANY (Pg. 26)	Circle 26
SUPEREX ELECTRONICS (Pg. 64)	Circle 30
SURPLUS CENTER (Pg. 96)	Circle 131
SYLVANIA (Subsidiary of General Telephone & Electronics) (Pg. 27)	Circle 27
TAB BOOKS (Pg. 94)	Circle 126
TURNER MICROPHONE COMPANY, THE (Pg. 80)	Circle 108
UNITED RADIO CO. (Pg. 99)	Circle 142
WARREN ELECTRONIC COMPONENTS (Pg. 100)	Circle 144
WELLER ELECTRIC CO. (Pg. 72)	Circle 34
WINEGARD CO. (Pg. 12)	Circle 14

NEW AUDIO EQUIPMENT

More information on new audio equipment is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader's Service Card facing page 74 and circle the numbers of the new products on which you would like information. Detach and mail the postage-paid card.

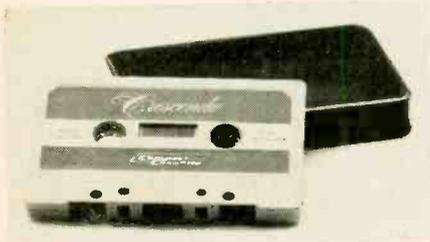COMPACT TAPE CASSETTES. The C-120 120-min. playing time. Packaged either individually in plastic, shatterproof containers, in card-stock mailing



cartons, or bulk-packed in poly bags. Full-range response at slow cassette playback speeds. Cassette dropout specifications available.—Certron Corp.

Circle 46 on reader's service card


STEREO RECEIVER, No. 99-0185WX. Solid-state, single chassis pre-amplifier and amplifier, 62.5 watts/channel, response 22-20,000 Hz \pm 1 dB @ 1 watt, power response 25-35,000 Hz, sensi-



tivity 80 mV. Direct-coupled output matches 4, 8, or 16 ohms. Front and rear panel tape outputs, tuner inputs, low- and high-frequency filters. Enclosed in simulated walnut grained metal case.—Lafayette Radio Electronics

Circle 47 on reader's service card

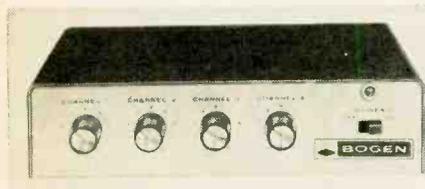MIXER-AMPLIFIER, MX6A-T. Ac powered, all-silicon, solid-state, can be used to add four more microphones or other signals to an existing system. Up to 3 MX6A-T units can be paralleled to provide 12 individual inputs, with the 3 mix-




ers mounted "piggy-back". Inputs handle either high- or low-impedance microphones or electric guitars with individual volume controls. Two of the four channels will accept tuner or crystal cartridge signals. Output can drive any packaged am-

plifier through its auxiliary input. It will also do this with 5-volt or more sensitivity. Operates hundreds of feet from the amplifier without rewiring. Uses standard phone jacks for high-impedance microphones and guitars; screw terminals for low-impedance microphones; phono jacks for output to auxiliary input of public address amplifier or tape recorder. \$74.85—Bogen Communications, Div., Lear Siegler, Inc.

Circle 48 on reader's service card

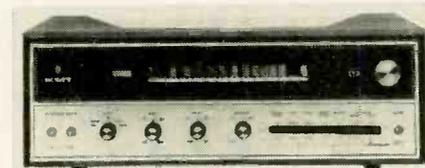STEREO RECEIVERS, FM 344C, AM/FM 384, both solid-state stereo with integrated circuit i.f. strip and FET front end, 1.9 μ V sensitivity, 90 dB cross modulation rejection, 2.2 dB capture ratio, 46 dB adjacent-channel selectivity, and 36



dB stereo separation. Both feature automatic stereo switching, interstation muting, tape monitoring facilities, dual speaker switches, noise filter, and push-button switches. 344C is \$399.95 and 384 is \$439.95.—H. H. Scott, Inc.

Circle 49 on reader's service card

STEREO RECEIVER, CR-3000. Transistorized, six bands with 30 watts IHF output. Frequency bands: 185-400 kHz, 550-1600 kHz, 2-4 MHz, 5.9-10.2 MHz, 11.4-18.2 MHz and 88-108 MHz (for FM/FM stereo. Features electrical bandspread and adjustable bfo. Accessory



jacks include phono inputs, tape deck inputs, and connections for auxiliary stereo equipment. 35 transistors, 22 diodes and 4 thermistors. Housed in vinyl-covered steel cabinet with chrome and black trim. Complete system—CR-3000 receiver and RSP-1 loudspeakers, \$389.85. CR-3000 alone, \$269.95.—Hallicrafters Co.

Circle 50 on reader's service card

STEREO RECEIVER, Model 18, delivers 40 watts continuous rms watts per channel with less than 0.2% distortion. Four-ohm acoustic suspension to 16-ohm


electrostatic type speakers can be used. Oscilloscope tuning indicator, non-amplifier front end eliminates overloading, "Gyro-Touch" tuning knob is actually a



large, heavy flywheel turned so that its edge protrudes through the panel. \$595.00. Accessory walnut cabinet, Model B18-0, \$39.50—Marantz Co., Inc.

Circle 51 on reader's service card

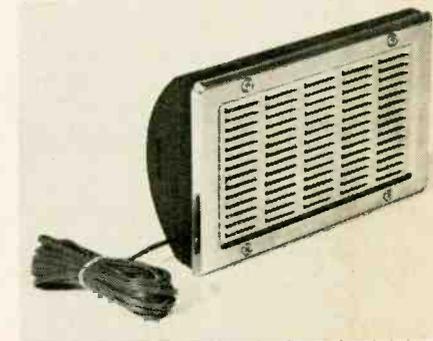
AUXILIARY SPEAKER, Model AX46B3-1. Ideal for use in cars, cabs, trucks, locker rooms, or in-plant paging stations. Solidly built with polished chrome grill designed to protect against



sharp instruments. Voice coil is $\frac{3}{4}$ " for handling up to 6 watts. Speaker rating, 8 ohms. Includes twin leads and mounting bracket.—Oxford Transducer Co.

Circle 52 on reader's service card

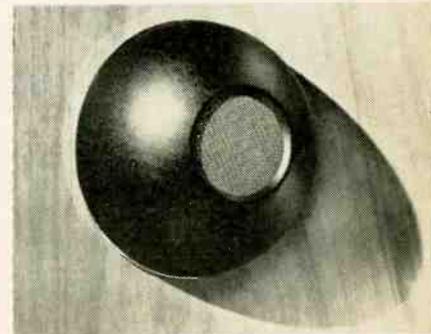SPEAKER, PVS-800. Cleaner, less distorted sound is achieved with the use of a patented lens-type opening. Com-




pletely weatherproof . . . can be used indoors or outdoors.—Oaktron Industries, Inc.

R-E

Circle 53 on reader's service card

Know Your Sweep Generators

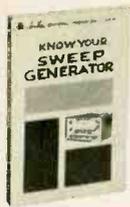

by Robert G. Middleton. This detailed reference book explains the basic principles of sweep alignment, methods of f-m test-signal generation, and the proper operation of beat-frequency generators and associated instruments. Describes practical troubleshooting methods for generators. Explains generator kit construction and how to avoid common errors; how to check the flatness of generator output, how to measure sweep width, and how to calibrate the completed instrument. A useful "refresher" book for old-timers, and a valuable basic reference for the beginner. Makes an excellent text for technical institute and junior college use. 176 pages; 5 1/2 x 8 1/2". Order 20593, only \$325

ABC's of Radio & TV Broadcasting

by Earl J. Waters. A fascinating explanation of what goes on at the transmitting end in radio and television broadcasting. Describes how the radio and television signals are formed, built up, and transmitted, and in the process, provides a basic understanding of transmitter principles and operation. Here is a full explanation of how radio energy is developed and radiated from an antenna, how it is made stronger, and how it carries an audio and video signal. Also details the use of accessory systems, such as power supplies, antennas, and remote transmission equipment. A readily understandable book. 128 pages; 5 1/2 x 8 1/2". Order 20575, only \$225

new Sams books

FET Circuits

by Rufus P. Turner. Since field-effect transistors (FET) are now commercially available at lower prices, interest in their use is growing. While this book begins with the principles of FET operation and describes their construction, it stresses the application of FET's in practical circuits. Describes oscillator and amplifier circuits and shows examples for use in receivers, transmitters, and accessory equipment. Also covers types of test instruments where circuitry can use FET's to advantage. All circuits described have been tested to verify their effective performance; a number of these may help generate ideas for designers and experimenters. Appendices include biasing diagrams of the FET's covered in the book, and a list of manufacturers. 160 pages; 5 1/2 x 8 1/2". Order 20585, only \$325

Citizens Band Radio Handbook (3rd Ed.)

by David E. Hicks. This latest edition of an extremely popular book, is the comprehensive, authoritative work on all aspects of CB. It is a complete guide for anyone who uses CB equipment, for the service technician who installs and maintains CB gear, and for anyone planning a CB purchase. Describes some of the latest equipment (including solid-state) and accessories to help you select the proper gear for a specific application. Explains how to obtain a license and required operating procedures. Also describes transmitter and receiver circuitry; antennas; installations, both fixed and mobile; adjustments, maintenance, and servicing procedures. Appendices include complete Part 95 of the FCC Rules and Regulations, radio districts of the U.S., and a glossary. 192 pages; 5 1/2 x 8 1/2". Order 20569, only \$425

Fundamentals of Digital Magnetic-Tape Units

by UNIVAC Division of Sperry Rand Corp. Provides a thorough background for understanding magnetic-tape units which are coming into wide use for information storage. Presents the basics concerning magnetism and magnetic fields and shows their application in magnetic tape recording. Describes in detail recording heads and tape-handling mechanisms. Explains the circuits required for writing and reading magnetic tape. Shows the latest recording techniques applicable to the most recent digital recording processes. Includes many illustrations. Review questions are included at the end of each chapter. An invaluable book for computer operators, programmers, and maintenance and servicing personnel. 96 pages; 5 1/2 x 8 1/2". Order 20580, only \$225

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.
4300 WEST 62nd ST. • INDIANAPOLIS, INDIANA 46268

Circle 106 on reader's service card

NEW TEST EQUIPMENT

More information on new test equipment is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader's Service Card facing page 74 and circle the numbers of the new products on which you would like information. Detach and mail the postage-paid card.

HEAVY-DUTY SOLID-STATE POWER SUPPLIES, PSR-500 Series.

Feature silicon rectifiers, SCR regulation, 500-watt outputs, line or load regulation less than 1% (no load to full load), ripple less than 1% at maximum rated current,




10-turn voltage control. Primary fuse and output circuit breaker prevent overloads. 3 models available: 2-32 Vdc, 0-15 amps; 2-55 Vdc, 0-10 amps; and 2-125 Vdc, 0-5 amps. 1 year warranty. \$375 to \$395 price range.—Electro Products Laboratories, Inc.

Circle 54 on reader's service card

GOOD/BAD TRANSISTOR ANALYZER, model TT-250.

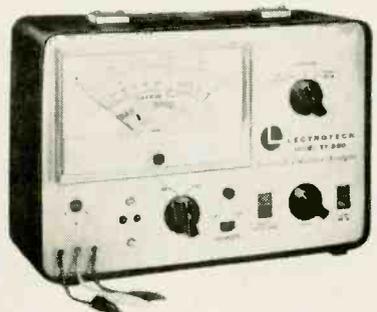Checks transistors in or out of circuit. No numerical readings to decipher, but Good/Bad readings. Leads don't have to be unsoldered to test. Measures out-of-circuit Beta or




gain on 2 scales: 0-250 and 0-500. Also measures leakage. All testing is non-destructive to transistors. Pnp or npn are determined without set-up book. Features 6" meter in a steel case. \$87.50—Lectrotech, Inc.

Circle 55 on reader's service card

CURRENT TEST ADAPTERS,

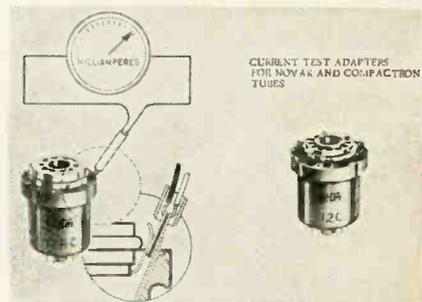Model T9RC and T12C measure any pin position of Novar and Compactron tubes. Probes are gripped by the Test Tabs. Current is read at the meter to which the leads are connected. \$3.65 and \$3.85 ea.




P-2 Probes .79 ea.—Vector Electronic Co., Inc.

Circle 56 on reader's service card

PORTABLE TRANSISTOR ANALYZER, model 260.

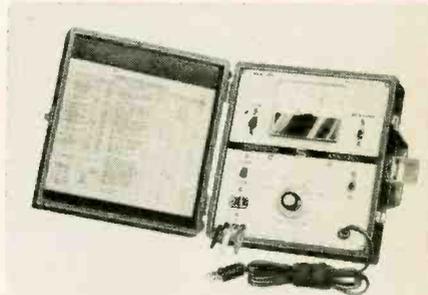Analyzes power and signal transistors without set-up or removing transistor from circuit. Electrically inserts transistor into oscillator circuit for go-no-go check. Enables fast identifica-




tion of npn and pnp transistors and lead connections. Out-of-circuit dc analysis; Beta test for direct meter reading of dc gain; I_{ceo} and I_{cbo} tests read collector-to-emitter and collector-to-base leakage. \$69.50—Seco Electronics Corp.

Circle 57 on reader's service card

REGULATED POWER SUPPLY,

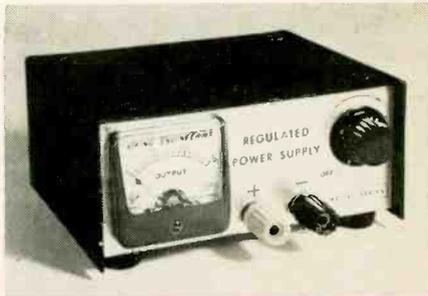model PZ-131. Variable outputs from 0.5 to 25 volts at currents to 200 mA, load regulation more than 100 mV, line regulation of +30 mV and ac ripple and



noise less than 2 mV at full load. Features isolated "floating" output and protection against short circuit. \$34.95—Viking Engineering of Minneapolis R-E

Circle 58 on reader's service card

NEW

FINCO®

COLOR SPECTRUM™ ANTENNAS

are "signal customized"
for better color reception...



"the ANTENNA that captures the RAINBOW"

FINCO has developed the Color Spectrum Series of antennas — "Signal Customized" — to exactly fit the requirements of any given area.

There is a model scientifically designed and engineered for your area.

Check this chart for the FINCO "Signal Customized" Antenna best suited for your area.

STRENGTH OF UHF SIGNAL AT RECEIVING ANTENNA LOCATION ▼	Strength of VHF Signal at Receiving Antenna Location				
	NO VHF ▼	VHF SIGNAL STRONG ▼	VHF SIGNAL MODERATE ▼	VHF SIGNAL WEAK ▼	VHF SIGNAL VERY WEAK ▼
NO UHF →		 CS-V3 \$10.95	 CS-V5 \$17.50 CS-V7 \$24.95	 CS-V10 \$35.95	 CS-V15 \$48.50 CS-V18 \$56.50
UHF SIGNAL STRONG →	 CS-U1 \$9.95	 CS-A1 \$18.95	 CS-B1 \$29.95	 CS-C1 \$43.95	 CS-C1 \$43.95
UHF SIGNAL WEAK →	 CS-U2 \$14.95	 CS-A2 \$22.95	 CS-B3 \$49.95	 CS-C3 \$59.95	 CS-D3 \$69.95
UHF SIGNAL VERY WEAK →	 CS-U3 \$21.95	 CS-A3 \$30.95	 CS-B3 \$49.95	 CS-C3 \$59.95	 CS-D3 \$69.95



NOTE: In addition to the regular 300 ohm models (above), each model is available in a 75 ohm coaxial cable downlead where this type of installation is preferable. These models, designated "XCS", each come complete with a compact behind-the-set 75 ohm to 300 ohm balun-splitter to match the antenna system to the proper set terminals.

THE FINNEY COMPANY

34 West Interstate Street • Dept. RE • Bedford, Ohio 44146

Circle 107 on reader's service card

*For home recording,
stereo taping,
public address work...*




**Eliminate
background
noise, feedback,
with the
TURNER 500
Cardioid.** Model 500 List Price \$84.00

The Turner Microphone Company—Cedar Rapids, Iowa

Circle 108 on reader's service card

NEW PRODUCTS

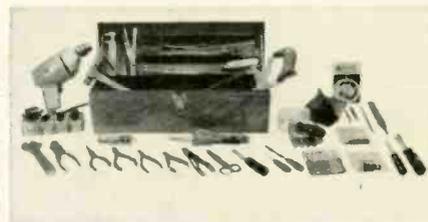TOOL KIT, JTK-5. 75-piece kit for electronic technicians. Includes hacksaw, electric drill, socket punches, screwdriv-



ers, nutdrivers, wrenches, pliers, cutters and soldering iron. Comes with 6" x 6" x 19" steel toolbox with tray. Catalog available.—Jensen Tools


Circle 59 on reader's service card

23-CHANNEL CB TRANSCEIVER. The Courier 23 features 23 crystal-controlled channels, dual conversion, transistor power supply, illuminated S/rf me-



ter and channel selector. PA system, auxiliary speaker jack, single-knob tuning, modulation indicator. \$169—Courier Communications, Inc.


Circle 60 on reader's service card

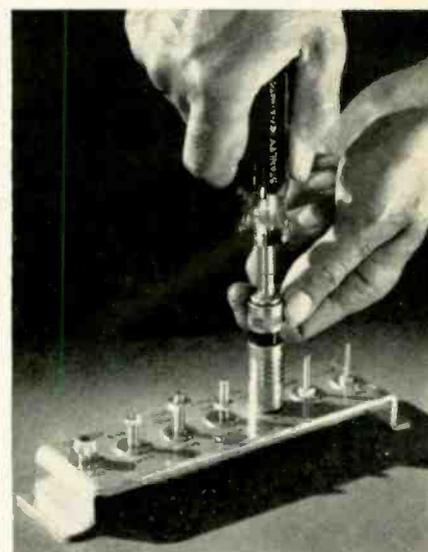

NUTDRIVER, Hex-a-Matic. Six-fingered collet chuck adjusts automatically to 15 standard sizes of nuts and screws.—The Stanley Works

Circle 61 on reader's service card

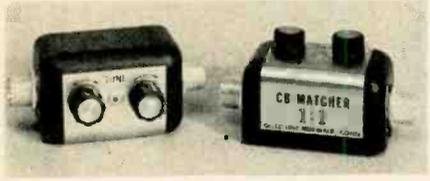
ANTENNA-MATCHING NETWORK, the *CB MATCHER*. This antenna matching network achieves a VSWR of



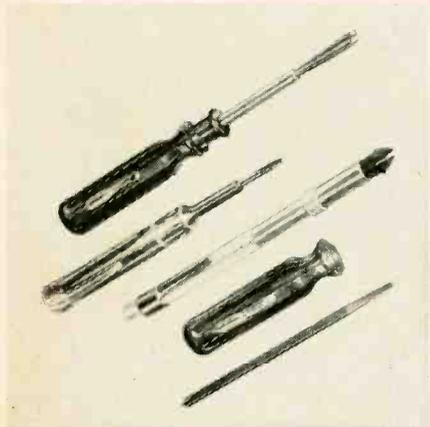1.1:1, which eliminates power losses of up to 30%. The *Matcher* measures 1 3/4" x 2 1/4" x 3 3/4" and is finished in black and gold.—**Gold Line Connector, Inc.**

Circle 62 on reader's service card


MINI TOOLS, The *K-23*, 1/8" x 3" *Screw Launcher* holds, starts, and drives small screws. Double-bladed bit grips screw by sliding gripping sleeve forward. The *TK-500 Circuit Tester Screw Driver* tests 100- to 500-volt circuits. Handle lights up if circuit is live. The *DU-1* is a



reversible screw driver with 1/8" sq. blade for regular screws on one end, and No. 1 Phillips bit on other. No. *K-14*, 5" *Phillips Screw Launcher* starts and removes all cross-slot screws. Each of these four "mini" tools have pocket clips.—**VACO Products Co.**

Circle 63 on reader's service card

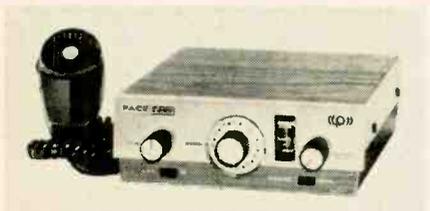CITIZENS BAND RADIOTELEPHONE, *Pace 2300*. Solid-state 23-channel transceiver has silicon output transistor with four watts output, double-conversion superheterodyne receiver featuring *Pace* noise limiting circuitry, 22 silicon



transistors. Walnut grain cabinet, public-address jack, front-panel control, two external-speaker jacks, sensitivity control are standard equipment. Lifetime guaranteed circuit board. Parts have a year replacement warranty. \$219.95—**Pace Communications Corp.**

Circle 64 on reader's service card

LIFE INSURANCE

ISSUED BY MAIL • KEEP IT FOR LIFE

MAIL THIS AD

NO OBLIGATION
APPLICATION MAILED TO YOU
\$5000 ENTRY AGES 21 to 70 • \$2000 ENTRY AGES 21 to 80
Whole Life Policy pays world-wide for death from any cause, any time, except during first policy year for either suicide or death from undisclosed pre-existing health conditions. Mail your name, address, zip code, year of birth and ad to Great Lakes Insurance Co., Elgin, Ill. 60120 Dept. LD125J6

SUPERCONDUCTIVE MAGNET. Industry's first commercial 125 kilogauss superconductive magnet delivered to Rutgers University by RCA. Smaller than a 1-gallon can, it contains more than 4 miles of "zero resistance" windings.

TOOL KITS

FOR ELECTRONIC TECHNICIANS

Industrial kit JTK-2C above (44 pieces) only \$39.95 (delivered). Write for new tool catalog.

JENSEN TOOLS and ALLOYS
3630 E. Indian School Road, Phoenix, Arizona 85018



USERS CAN'T BE WRONG!

Technicians everywhere rely on famous Sencore Mighty Mites. Here's why.

- Grid Leakage Test with ultra-high sensitivity of 100 megohms
- Emission Test at full rated cathode current
- Shorts Test picks out interelement shorts of 180K ohms or less
- Mighty Mite accurately checks over 3,000 tubes, including foreign.



NEW MIGHTY MITE V

TC142


Now, Sencore's new Mighty Mite V gives you the same reliability and accuracy, plus new features that make the "V" the most up-to-date tester of all.

- NEW—Magnoval socket so you check many more tubes.
- NEW—Horizontal in-line switch layout saves setup time.
- NEW—Rugged vinyl-clad steel case stays new longer.
- NEW—Brushed chrome panel; detachable cover.

The new TC142 is truly Sencore's mightiest Mighty Mite and it's still only

\$74.50

IN STOCK AT YOUR DISTRIBUTOR NOW.

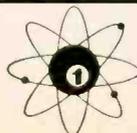

SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 109 on reader's service card

Yes, you can



YOU
CAN
BUILD

AN ARTISAN TRANSISTORIZED ORGAN
WITH KITS AND SUB-ASSEMBLIES

Save \$2000 or more

Easy enough to be fun. Difficult enough to be challenging.

Relax with one of the world's most rewarding hobbies . . . build a full-size, concert quality transistorized organ. The Artisan Kit Organ has the same rich pipe-like tones, the same features, as the famous Artisan Custom Organ. There's not one bit of difference in tonal beauty, console style, high quality.

10 styles for home, church, school




Write for brochure

Dept. RE
1372 East Walnut Street
Pasadena, Calif. 91106

Circle 110 on reader's service card

Because you've got to SEE it to BELIEVE it
..... we will send you a FREE sample!

instant lettering

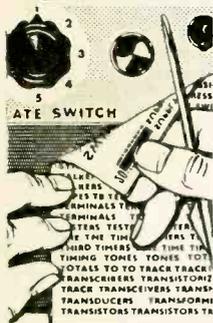

DATAMARK

— the easy new way to label your projects!

Just rub over the pre-printed words or symbols with a ballpoint pen and they transfer to any surface! Looks like finest printing! Label control panels, meter dials, letter on anything!

LOOK FOR **instant lettering**

DATAMARK SETS only \$1.25 each
— at leading electronic distributors

DATAMARK SETS AVAILABLE FOR:

- Amateur Radio, CB
- Audio, Hi-Fi, TV
- Experimenter Home Intercom
- Industrial Test Equipment
- Switch & Dial Markings
- Alphabets & Numerals in

1/8", 1/4" and 1/2"

— each set has black, white, and gold

SEND FOR FREE SAMPLE RE-117

THE DATAK CORPORATION
85 HIGHLAND AVENUE • PASSAIC, N. J. 07055

Circle 111 on reader's service card

NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here are free for the asking with a Reader's Service number. Turn to the Reader's Service Card facing page 74 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

RELAYS AND SWITCHES. 26-page booklet covers relays, switches, push-button control stations and reversing drum controls. Presents complete electrical and mechanical specifications and features. A replacement pocket-size guide for potential type motor-start relays with over 1400 listings is also included.—**Relay and Control Corp.**

Circle 65 on reader's service card

SEMICONDUCTOR PLASTIC RECTIFIERS. 12-page booklet gives important electrical and mechanical characteristics of new low-priced, plastic-encapsulated rectifiers. Contains characteristic curves and dimensional diagrams for 9 rectifier types, rated from 1.5 to 40 amps, for both lead- and stud-mounted devices. An interchangeability chart relates the rectifiers, both mechanically and electrically, to established industry types. Price lists included.—**Westinghouse Semiconductor Div.**

Circle 66 on reader's service card

ANTENNA ROTOR SYSTEM. 4-page brochure describes AR-10B antenna rotor system, including an adapter for large antenna arrays, and a TA-6 thrust bearing for installation of antenna arrays more than 5 ft. above the rotor unit. Correct chimney, eave or wall, roof-guyed, and tripod mounted antenna rotor systems are illustrated.—**Cornell-Dubilier Electronics**

Circle 67 on reader's service card

1968 ELECTRONICS CATALOG, No. 680, 512 pages. Lists latest electronics components and new IC's. Includes stereo hi-fi, Citizens band 2-way radio, tape recorders, ham gear, test equipment, radios, TV sets and accessories, cameras, optics, marine equipment, auto accessories, tools, books, etc.—**Lafayette Radio Electronics**

Circle 68 on reader's service card

ELECTRONIC COMPONENTS. 72-page, fall 1967 catalog lists components of all major manufacturers and features such items as: accelerometers, counters, meters, motors, precision potentiometers, servo motors, test equipment and timers. Complete sections are devoted to relays, pressure transducers and gyros. Contains photos, drawings, and diagrams.—**American Relays, Electronics Div.**


Circle 69 on reader's service card

DC VOLTAGE REGULATOR MODULES. Application note provides detailed descriptive information about technical specs, parameters and series/shunt circuit applications. Engineering Data Sheets are provided for each type of unit.—**Bendix Semiconductor Div.**

Circle 70 on reader's service card

INSTANT LETTERING. 1967 catalog describes over 2,000 dry-transfer alphabet sheets and marking sets for electronics, architectural drawings, equipment, art work and general office use. Includes an organic chemical symbol set, a logic diagram set, 14 new preprinted title sets, *Letratone* shading tints and heat resistant letters for drafting.—**The Datak Corp.**

Circle 71 on reader's service card

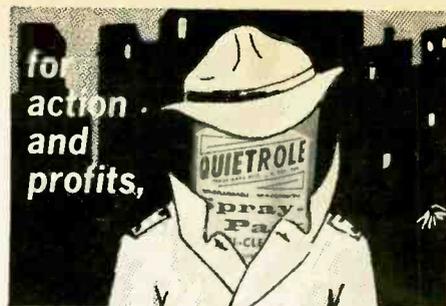

for action and profits,
check the "Silencer" . . .
QUIETROLE



Check QUIETROLE . . . the "Silencer" for noisy radio, TV, (black and white, color too) and instrument controls, that protects your reputation, guards your profits.

QUIETROLE, the quality lubricant-cleanser for over 20 years, is harmless to plastics and metals, is non-conductive, non-corrosive, non-flammable . . . with zero effect on capacity and resistance.

For best results, specify QUIETROLE . . . Mark II for tuners Spray Pack for controls and switches Silitron for general use Available in Aerosol Can or Dropper Bottle



manufactured by

QUIETROLE COMPANY
Spartanburg, South Carolina

Circle 112 on reader's service card




**EFFICIENT!
SAFE!
FAST!**

AUTOMATIC

STAPLE GUNS

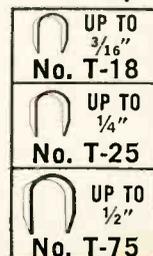For Fastening Any
Inside or Outside
Wire Up to 1/2" in Diameter



- Telephone wire
 - Intercom wire
 - Bell wire
 - Thermostat wire
 - Radiant heating wire
 - Hi-Fi, Radio & TV wires
- Tapered striking edge gets into close corners!

Available in:
Brown, Ivory, Beige,
Monel, Bronze, Natural

ARROW FASTENER COMPANY, INC.

SADDLE BROOK, N. J. 07663

Circle 113 on reader's service card

Unabridged Amendment of Part 97, FCC Rules

(continued from page 57)

5. Section 97.25 (c) is amended to read as follows:

§ 97.25 Examination credit.

(c) An applicant for the Amateur Extra Class operator license will be given credit for examination elements 1(C), 4(A), and 4(B), if he so requests and submits evidence of having held a valid amateur radio station or operator license issued by any agency of the United States Government during or prior to April 1917, and qualifies for or currently holds a valid amateur operator license of the General or Advanced Class.

6. Section 97.29 (a) is amended to read as follows:

§ 97.29 Manner of conducting examinations.

(a) The examination for Amateur Extra, Advanced, and General Classes of amateur operator licenses will be conducted by an authorized Commission employee or representative at locations and at times specified by the Commission.

7. Section 97.31 (b) is amended to read as follows:

§ 97.31 Grading of examinations.

(b) Seventy-four percent (74%) is the passing grade for written examinations. For the purpose of grading, each element required in qualifying for a particular license will be considered as a separate examination. All written examinations will be graded only by Commission personnel.

8. Section 97.33 is amended to read as follows:

§ 97.33 Eligibility for re-examination.

An applicant who fails examination for an amateur operator license may not take another examination for the same or a higher class amateur operator license within 30 days, except that this limitation shall not apply to an examination for an Advanced or General Class license following an examination conducted by a volunteer examiner for a Novice, Technician, or Conditional Class license.

9. Section 97.51 (a) (5) is amended to read as follows:

§ 97.51 Assignment of call signs.

(a) * * *

(5) One unassigned two-letter call sign (a call sign having two letters following the numeral) may be assigned to a previous holder of a two-letter call sign the prefix of which consisted of not more than a single letter. Additionally, a two-letter call sign may be assigned to an Amateur Extra Class licensee who first held an amateur radio station license issued by the United States Government 25 years or more prior to the receipt date of an application for such assignment. Applicants for two-letter call signs are not permitted to select a specific assignment except in accordance with subparagraphs (1) and (2) of this paragraph.

10. Section 97.59 (a) and (b) are amended to read as follows:


§ 97.59 License term.

(a) Amateur operator licenses are normally valid for a period of 5 years from the date of issuance of a new or renewed license, except the Novice Class which is normally valid for a period of 2 years from the date of issuance.

(b) The license for an amateur station is normally valid for a period of 5 years from the date of issuance of a new or renewed license except that an amateur station license issued to the holder of a Novice Class amateur operator license is normally valid for a period of 2 years from the date of issuance.

Audio-Color

Lets you see your music

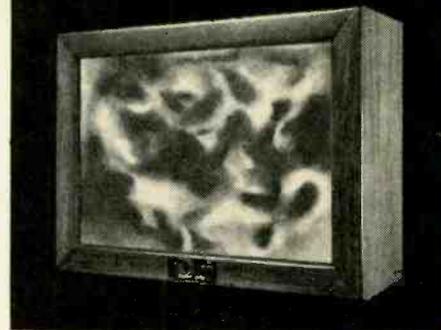

ASSEMBLED KIT FORM
\$54.95 \$44.95
\$5 DOWN — \$5 MONTH

Walnut finished cabinet included
Shipped REA Collect

Easy to build, easy to install. All transistor AUDIO-COLOR adds a visual dimension to musical enjoyment. A brilliantly moving panorama of color casts dancing images on a soft frosted screen, reflecting rising and falling volume with each beat of the music. Here's a truly unique and exciting new musical experience. Make check or money order to CONAR.

SEND FOR FREE CONAR CATALOG

CONAR Division of National Radio Institute
Dept. MC7C, 3939 Wisconsin Ave., Washington, D.C. 20016

for PROFITABLE,
TIME-SAVING
SERVICING

OF: Black & White TV 
Color TV 
AM and FM, Tube or
Transistor Home, Portable
and Auto Radios 
Communications
equipment &
Home
Appliances 
Hi-Fi
Components 



B&K PROFESSIONAL TEST EQUIPMENT

WITH SIGNAL INJECTION AND IN-AND-OUT OF CIRCUIT
MEASURING TECHNIQUES
Send today for your free copy of Catalog AP22

B&K
DIVISION OF
DYNASCAN


DS-602

1801 WEST BELLE PLAIN AVENUE, CHICAGO, ILL. 60613
Telephone: (312) 327-7270 • Cable Address: BANDKCO


Circle 115 on reader's service card

4 ways to increase your income

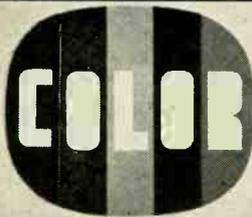RCA Institutes, Inc. offers these four comprehensive home study courses especially designed to help build your income immediately!



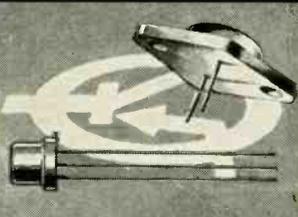
COLOR TV Add profitable color TV to your skills with this home training course, newly revised to include information on the latest techniques, receiver circuitry and equipment. Train under the direction of RCA Institutes... experts in Color TV home study training.



TRANSISTORS You get the necessary background for semiconductor technology including characteristics of tunnel diodes, rectifiers and other solid state devices. Transistor trainer also available.



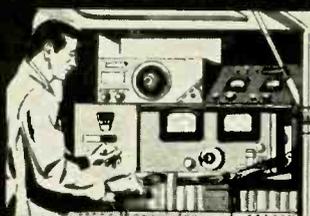AUTOMATION ELECTRONICS Trains you for the many applications of automation electronics in industry and government including Photoelectronics, Digital Computer Techniques, Synchros and Servomechanisms, Automatic Control Systems, and many more!



MOBILE COMMUNICATIONS Trains you to service and maintain 2-way radio communications on land, sea, and air! Gives you the technical foundation for space communications!

Take advantage of RCA's Liberal Tuition Plan. You only pay for lessons you order; and have no long-term obligations. Licensed by New York State Education Department. Approved for Veterans.

RCA INSTITUTES, INC.

A Service of Radio Corporation of America
350 West Fourth Street, New York, N. Y. 10014



The Most Trusted Name in Electronics

SEND THIS COUPON NOW FOR COMPLETE FREE INFORMATION

RCA INSTITUTES, INC. Home Study School, Dept. REA-N7
350 West Fourth Street, N. Y., N. Y. 10014

Without obligation, rush me free information on the following RCA Home Training Course: **COLOR TV** _____ **TRANSISTORS** _____ **MOBILE COMMUNICATIONS** _____ **AUTOMATION ELECTRONICS** _____

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

Shrink on the Insulation

(continued from page 61)

handles, I used two sizes of tubing, telescoping them.

Plastic tubing on tools serves the dual purpose of insulation and identification. That's why I used two colored bands (red and gray) on the pliers, and a gray band on the shaft of the screwdriver in Fig. 3. When several technicians are working in a shop there is never any question of whose tools are where—the bright bands tag them instantly. You may want to choose your own color code and use it on all your tools. The colored bands are applied after the base insulation is shrunk on, in the same manner.

You can use a soldering gun or iron to shrink tubing over a soldered joint. That is how I insulated the resistor, space lug and soldered joint of Fig. 4. After slipping the tubing into place over the joint, touch it in several spots with the hot iron to start the shrinking, then rub the iron all over the surface of the plastic. The tubing will shrink only where the heat is applied directly, so use your iron on all parts of the sleeve. Work slowly; the plastic will not burn, scorch or melt from the heat of the iron, and not enough heat will be transmitted to weaken the soldered joint or seriously affect the value of a resistor.

I am not sure, however, that I would want to try this with a diode or transistor, although manufacturers' literature does show semiconductors encapsulated with the material. In general, heat can be controlled more precisely with the hot-air guns used in production runs.

Clean your iron of solder before a shrink job; solder will stick to plastic. If any solder *does* get on the tubing, pick it off to avoid short-circuit possibilities.

More applications

Another quick and easy job with shrinkable tubing is terminal insulation of unused wires, as in the second wire from the top, Fig. 4. Most of us are now replacing rectifier tubes with solid-state silicons. This leaves us with the rectifier filament leads dangling from the transformer. Common sense tells us that we may need 5 volts ac some day, so we do not cut these leads off short; we insulate them and tuck them away. The best way to insulate them is to cut off the bare ends of such leads and shrink a bit of tubing over them, leaving about 1/4" of plastic tube extended. I do this with a match, holding the shrinkable tub-

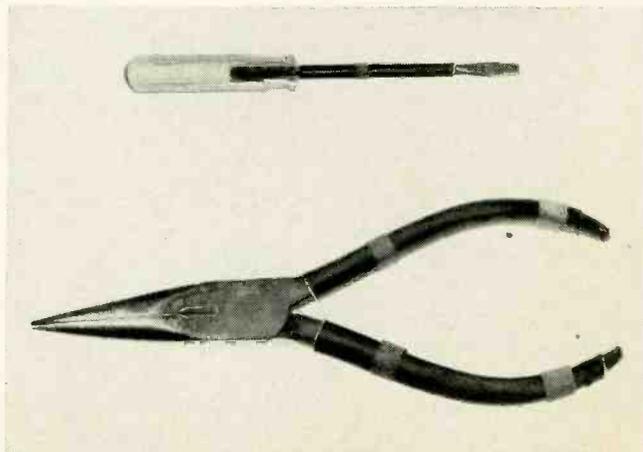


Fig. 3—Insulation on tool handles can be shrunk on in an oven at 350°F for five minutes. Use bands for identification.

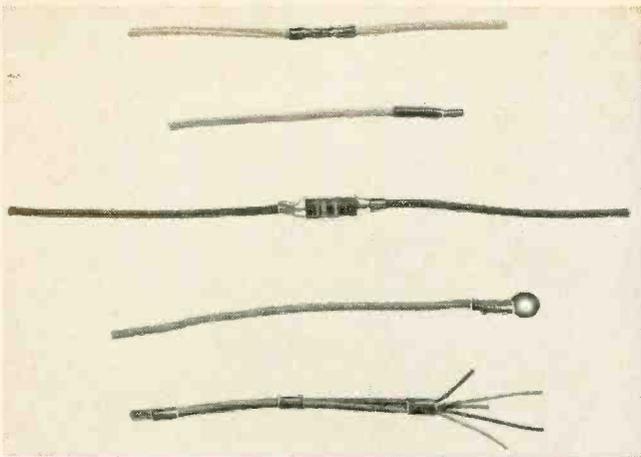


Fig. 4—Top to bottom: insulated splice; lead termination; encapsulated resistor; insulated solder lug; cabled wires.

ing in the heat but not in the flame over the match. In this way, the tubing does not burn, but shrinks evenly. While tubing that is shrunk will not flare up, it will burn slowly in direct flame.

If you have a pair of transformer or other leads, you can insulate both ends at once with one piece of tubing as described above; just make sure that no bare ends are left when you trim the wires. You can get shrinkable terminations with sealed ends made specifically for this purpose. I feel, however, that this is an unnecessary refinement unless you plan to dip the ends in a glass of water—or leave the wires out of doors.

Shrinkable tubing helps solve another major problem—weatherproofing coax-cable connectors. Dampness gets into the cable where it enters the connector and into the connector shell itself. This can be prevented by using large-diameter shrinkable tubing over the whole connector, and extending it back along the cable for an inch or so. The cable and connector must be absolutely dry before the tubing is shrunk on.

A common chassis problem is high-voltage arcing between closely spaced solder lugs on tube bases or cable connectors. These components can be difficult to handle, especially the newer tube sockets with ten connections. You can slip sleeving over each lead before it is soldered, and later shrink it into place. The tubing won't come off and will withstand the roughest handling. This is a good trick to prevent future troubles—like corona discharge in TV high-voltage supplies and chassis-arcing horizontal sweep circuits. If future servicing is required, you can cut off the insulation with a knife.


In another application, I shrank tubing on an exposed screw end in a scope circuit where there was a possibility of high-voltage wires rubbing and shorting out. The plastic gripped tightly on the screw threads and will not come off until I am ready to remove the screw.

Still more applications

An interesting noninsulation possibility is the cabling of several leads, as in the bottom illustration of Fig. 4. Here, very short bits of tubing are shrunk at intervals over groups of wires, giving underchassis work a highly professional look. This kind of shrinking is best done with the soldering iron.

Do you have a whip antenna with no protective ball on the end? Shrink on a half-inch or so of brightly colored

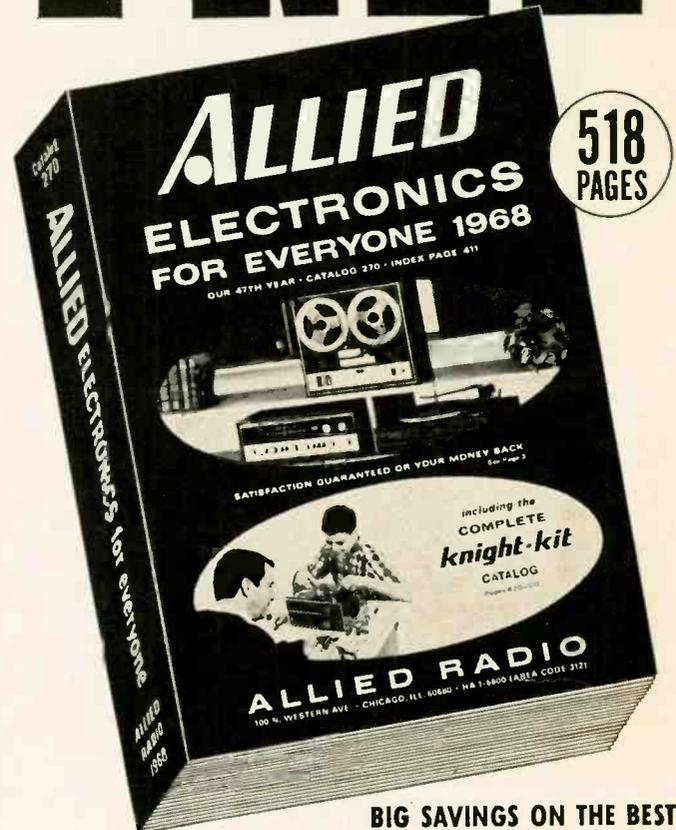ALLIED NEW 1968 CATALOG & BUYING GUIDE FREE



BIG SAVINGS ON THE BEST IN ELECTRONICS FOR EVERYONE

Here it is! The world's most famous catalog of electronic equipment featuring hundreds of new and exclusive items and special Allied values.

518 pages—including the complete Knight-Kit Catalog—picturing, describing, and pricing thousands of items. The most complete inventory ever assembled of Hi-Fi, Radios, Tape Recorders, CB, Electronic Equipment, Parts and Tools... *all at money-saving low prices.*

NO MONEY DOWN • UP TO 2 YEARS TO PAY!

- Stereo Hi-Fi
- Famous Knight-Kits®
- Tape Recorders & Tape
- CB 2-Way Radios
- Walkie-Talkies
- FM-AM & AM Radios
- Shortwave Receivers
- Portable TV
- Phonographs
- Amateur Equipment
- Intercoms & PA
- Automotive Electronics
- Test Instruments
- TV Antennas & Tubes
- Power Tools, Hardware
- Tubes, Transistors
- Parts, Batteries, Books




**WRITE
FOR YOUR
COPY TODAY!**

ALLIED RADIO, Dept. 2L
P.O. Box 4398, Chicago, Illinois 60680

Send me your free catalog for 1968

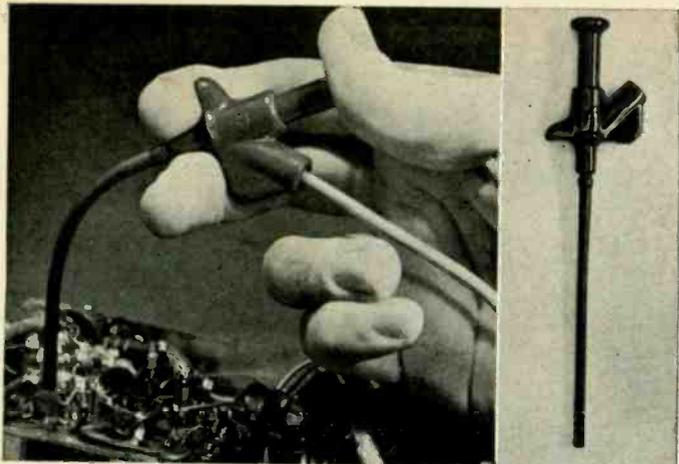NAME Please Print
ADDRESS
CITY
STATE ZIP CODE



Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?



Available through your local distributor, or write to:

RYE INDUSTRIES INC.

124 Spencer Place, Mamaroneck, N.Y. 10543

Circle 118 on reader's service card

\$147

Shrink on the Insulation

(continued from page 85)

tubing and you'll prevent scratches.

I have used tubing in a manner that the manufacturer probably never thought of—to make an emergency flexible coupling between two shafts. I joined a variable-capacitor shaft and a panel-bearing shaft. The angular displacement between the shafts was not great, but a solid coupling could not be used. I forced a length of 1/2" I.D. tubing over the ends of the shafts and shrank it. I was careful not to heat the material not actually on the shafts, since I have noticed that heating reduces the flexibility of the material. The coupling is still in place; the capacitor is not adjusted frequently—it is the drive control on an amateur transmitter.

The methods of heating described above—soldering gun, match, oven—are of course expedients. The manufacturers recommend more sophisticated equipment, generally hot-air guns with controlled temperatures and a variety of tips to meet special requirements. For the small user, however, the makeshifts suggested are entirely adequate.

You will find that, inch for inch, shrinkable tubing is considerably more expensive than tape or spaghetti. Nevertheless, so little is used for each application that the overall cost is not excessive, and the ease with which the tubing is handled bears no relation to its cost.

If you have run-of-the-mill insulation problems or odd-ball experimental needs, you will find that shrinkable plastic tubing is a great help. It is certainly the modern way to insure good electrical and mechanical protection in your electronics work.

R-E

TECHNOTES

OLYMPIC CTC-19, -20, -21 COLOR CHASSIS

COMPLAINT: Severe misconvergence of the blue field. (The blue convergence is out of tolerance by 1/4 to 1/2 inch.)

REMEDY: Check R802, a 100-ohm, 1-watt resistor located next to selenium rectifier CR801 on the convergence board. It may have changed value due to over-heating caused by excessive current flow before horizontal convergence coil T801 is properly adjusted. Normally, the ferrite slug in T801 should be about 1/4 to 5/16 inch from the top of the coil form.)

If resistor R802 is discolored or burnt, replace it with two 100-ohm, 1-watt resistors in series so that the new value of R802 is 200 ohms, 2 watts.—*Olympic Service Bulletin*

LINE ADJUSTMENT TRANSFORMER

A 12.6-volt filament transformer with its secondary connected in series with a TV or appliance line cord (as in Fig. 1) can be used to raise or lower the applied line voltage by 12. With a vtvm (set on 150 volts ac) across the output

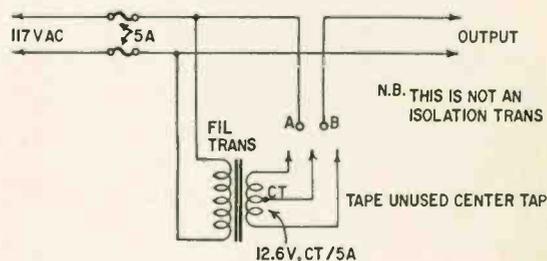


Fig. 1

leads, connect the 12-volt secondary leads to A and B. Connected one way, the input voltage will be boosted by 12; reversing the connections subtracts 12 from the line voltage.

(Fig. 2 shows how a switch and ac receptacle can be added to make the unit easier to use.—*Editor*) Mount the transformer (and switch and receptacle, if desired) in a

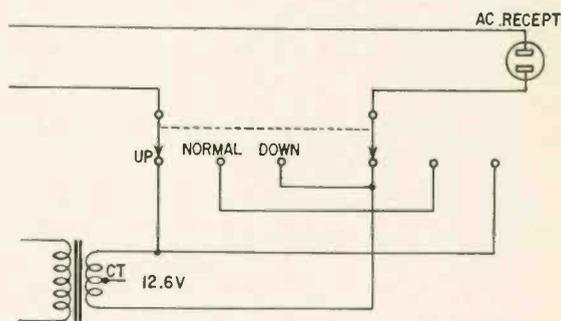


Fig. 2

small metal box with a number of small holes drilled in it for ventilation. Use strain-reliefs and grommets where wires enter the box.

A 5-ampere transformer will handle the average color set (around 350 watts). For higher wattage requirements, add 30% to the desired rating and divide by 120 to find the minimum transformer current rating.—*Admiral Service News Letter*

R-E

ELECTRONICS IN THE MODERN AUTO

continued from page 45

The three thermistor sensors, R4, R5 and R6 in Fig. 4, are disc-type semiconductor devices composed of a blend of metal oxides with a very large negative temperature coefficient. Shunting resistors R1 and R2 are necessary to obtain the correct resistance decrease for a given temperature increase. The three sensors, in series, form one leg of a voltage divider circuit. Small changes in resistance of the sensors cause proportional changes in the voltage input to the amplifier. The temperature dial rheostat (R3), located in the other leg of the voltage divider, sets the operating point of the circuit.

In the Bendix system, various electronic, electrical and mechanical units work together in much the same way as the human brain's muscle mechanism; that is, by sensing and reacting. For example, if a 70° temperature is dialed when the inside temperature is 75° and the outside is 65°, the system will take in outside air until the required cooling is achieved. If, on the other hand, the outside temperature is 75°, the air conditioner will take over the task. And, if the interior temperature is 65°, the process is reversed; the heater will come on.

Speed controls

Engine-speed controls are more appropriately called electrovacuum systems. They are mentioned here, however, because we can expect electronics to be used more extensively in these systems within the next few years. At this time, three systems are in use: (1) the Perfect Circle Speedostat used on Chevrolet, Chevelle, Chrysler, Dodge, Plymouth, Lincoln, Mercury, Oldsmobile, and Rambler; (2) the AC Electro-Cruise used on Buick and Pontiac, and (3) the Marquette System used on Ford and Thunderbird. Bendix Radio Division also is working on an automatic speed control. We can expect this unit to use more electronic components.

These systems all operate in the same general manner: the car is brought to the desired speed; the control system is enabled; the system then maintains the car's speed by automatically controlling the accelerator, and, finally, the system is disabled when the brake pedal is depressed. There are variations of this basic pattern such as "resume speed" capabilities and "retard speed" capabilities. They all serve to give the driver a break from the monotonous task of maintaining the car's speed on long stretches of open road.


Miscellaneous

Several less vital items have been borrowed from the electronics field and incorporated into the electrical systems of late-model autos. For example:

- 1) Printed circuits are often used to wire the dashboard instrument cluster.
- 2) Fusible links are installed at critical points to protect the car's wiring harness.
- 3) Multiwire plugs reduce the chance of wiring error and simplify component replacement.
- 4) And, in many models, the old push-pull switches are being replaced by toggle type and thumbwheel switches and controls.

In the next few years, semiconductors and integrated circuits are sure to find automotive application in the following areas: windshield-wiper speed controls; liquid-level detectors (gas, oil, etc.); odometers; spare-tire pressure indicators, collision warning detectors and brake anti-skid sensors.

R-E

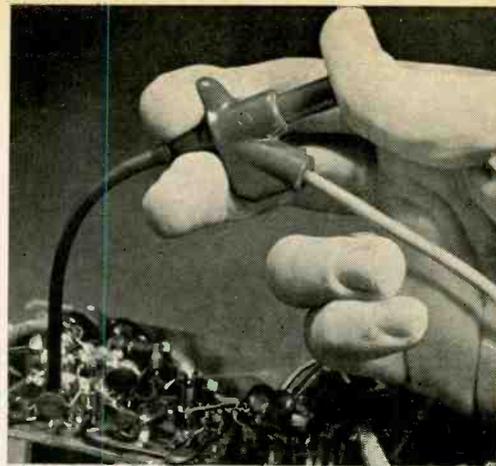

Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?



Available through your local distributor, or write to:

RYE INDUSTRIES INC.

124 Spencer Place, Mamaroneck, N.Y. 10543

Circle 118 on reader's service card

\$147



**BRAND NEW EDITION
FALL AND WINTER
RADIO-TV
ELECTRONICS
CATALOG**



**THE WORLD'S MOST
FAMOUS CATALOG OF
ELECTRONIC EQUIPMENT!**

YOUR BUYING GUIDE FOR:
• Stereo & Hi-Fi Systems & Components • Tape Recorders • Electronic Parts, Tubes, Tools • Phonos & Records • Ham Gear • Test Instruments & Kits • Cameras & Film • PA • Citizens Band • Radio & TV Sets • Musical Instruments

SEND FOR YOURS TODAY!

MAIL TODAY TO:


BURSTEIN-APPLEBEE

Dept. REK, 1012 McGee, Kansas City, Mo. 64106

Name _____
Address _____
City _____ State _____ Zip Code _____

DO YOUR FRIEND A FAVOR... ALSO INCLUDE HIS NAME AND ADDRESS IN ENVELOPE WHEN MAILING YOUR REQUEST

Circle 119 on reader's service card

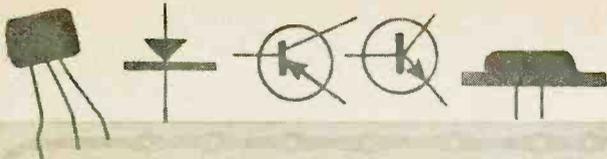

TEST TRANSISTORS IN SECONDS in circuit

TR139
89⁵⁰



Also check all
transistors, diodes,
and rectifiers out
of circuit for true AC beta
and Icbo leakage.

Your best answer for solid state servicing, production line testing, quality control and design.

Sencore has developed a new, dynamic in-circuit transistor tester that really works—the TR139—that lets you check any transistor or diode in-circuit without disconnecting a single lead. Nothing could be simpler, quicker or more accurate. Also checks all transistors, diodes and rectifiers out of circuit.

BETA MEASUREMENTS—Beta is the all-important gain factor of a transistor; compares to the gm of a tube. The Sencore TR139 actually measures the ratio of signal on the base to that on the collector. This ratio of signal in to signal out is true AC beta.

ICBO MEASUREMENTS—The TR139 also gives you the leakage current (Icbo) of any transistor in microamps directly on the meter.

DIODE TESTS—Checks both rectifiers and diodes either in or out of the circuit. Measures the actual front to back conduction in micro-amps.

COMPLETE PROTECTION—A special circuit protects even the most delicate transistors and diodes, even if the leads are accidentally hooked up to the wrong terminals.

NO SET-UP BOOK—Just hook up any unknown transistor to the TR139 and it will read true AC beta and Icbo leakage. Determines PNP and NPN types at the flick of a switch.

Compare to laboratory testers costing much more. . . . \$89.50

See America's Most Complete Line of Professional
Test Instruments — At Your Distributor Now.



NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

SENCORE

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 120 on reader's service card

X-Ray Radiation

(continued from page 55)

"cook" until the suspected component fails. Never resort to this practice in servicing a color set.

6. In the customer's home, check the power-line voltage at the wall outlet to make sure it doesn't exceed the input voltage rating of the receiver. If the power-line voltage is excessive, ask the power company to adjust the line voltage to the proper level. Or else set the transformer tap as specified by the manufacturer so that the receiver is operating within the specified ratings.

Additional research

Some further rules have been propounded by the Pinellas County Health Department (Tampa-St. Petersburg area) in Florida. There, extensive tests have been conducted by a health physicist, George McCall. They have resulted in a 3-hour radiation-safety course which will be given to technicians in that county.

McCall's test results (unverified in other independent tests) indicate that there may be dangers to service technicians from the neck of the picture tube during certain adjustments. According to McCall, when the yoke is retracted, high-speed electrons are deflected to the wall of the picture-tube neck, causing emission of a ¼-inch-wide beam of radiation around the circumference of the neck.

To avoid the possibility of this type of exposure, the Pinellas County Health Department is recommending these additional rules:

1. From a local medical supply house, buy a small quantity of leaded plastic sheeting, of the type used for dental X-ray aprons. The lightest-weight material (¼ millimeter) is okay. This should be draped over the set or tube during servicing. (It provides protection from implosion, too.)

2. For protection of the eyes against both implosion and X-rays, wear a pair of good safety glasses during servicing.

McCall explains that these precautions are particularly important if the voltage is above the manufacturer's specified level—a condition which never should be allowed to exist.

The "X-ray menace" recently was put into perspective by Dr. Lauriston Taylor, president of the NCRP. Testifying before a Congressional committee, he said:

"Television equipment generally is made so as to reduce radiation to an unimportant level, certainly for the general public and usually for the service man. Steps to insure this include heavying-up of the glass, adding high-atomic-number materials to the glass, placing metal barriers at strategic points in the set, enclosing the set in a box, and so on. It takes very little material to attenuate any X-rays produced in television equipment and it can be considered a blunder when something goes wrong and this is not accomplished.

"It would be my guess that even working with the defective television sets, such as those that have been publicized recently, there would be probably small risk to the service man at a bench, primarily because of the small likelihood of any appreciable portion of his body remaining in close proximity to the source of radiation. This again is not to say it is good, but to point out that it might not be as bad as some recent news stories have indicated. . . . The protective steps are so readily simple that a rudimentary manual could give the user most, if not all, of the information that he would need."

R-E

SERVICING HINTS ON NEW COLOR TV SETS

(continued from page 38)

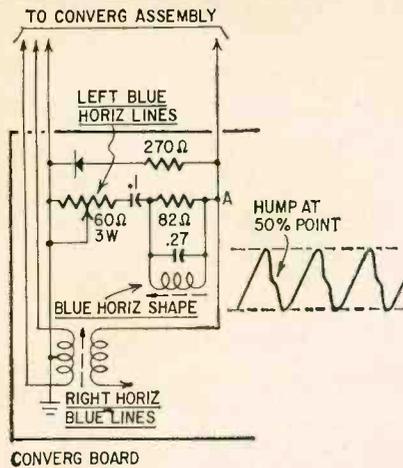


Fig. 6—To set blue-shaping coil, put scope from point A to chassis. Then adjust the slug for hump at mid point in trace.

point A in Fig. 6 and ground; you should see a trace like that at the right in the figure. Then adjust the coil slug for a bend at the 50% point on the waveform slope. For the receiver shown, the waveform is approximately 45 volts peak to peak.

You should take a few other precautions to prevent overload of the horizontal system:

Never turn the set on with the plate cap disconnected from the horizontal-output tube.

Never turn the set on with the yoke unplugged.

Never turn the set on with the damper tube removed from its socket.

Never replace the horizontal oscillator tube immediately after the set has been in operation. Give the output tube a chance to cool off. With a hot output tube there will be immediate conduction and the necessary bias will be delayed until the oscillator tube heats up. In the meantime the output tube will be overloaded and its life shortened.

Purity and convergence

If you follow the manufacturer's setup procedures on the new color receivers, you will get near-perfect black-and-white and color pictures. You don't have to tolerate color shading in b-w pictures because of circuit limitations. With rare-earth phosphors being used in nearly all new color CRT's, you get brilliant whites and perfect blacks.


In today's sets, the initial setup adjustments (if properly made) will remain fairly stable for many months. During routine servicing calls, however, part of your procedure should be to check b-w reception, to make sure no objectionable shading exists on the screen. If it does, check the degaussing system as outlined earlier and degauss the entire screen area. If color shading *still* exists, recheck purity and dc convergence. Only slight touchups should be required.

Make sure you also check the age system, the color-killer settings, and focus, for misadjustment of any of these can detract from peak performance. The horizontal lines obtained for good focusing are not as sharply defined as in b-w receivers. Still, careful adjustment of the focus control or voltages will make the lines clearly evident and will help make the picture crisp and sharp.

Today's color receivers are better than ever, and will produce better pictures. But they'll do this only if you set up and service them properly.

In some later color receivers the blue shaping coil isn't adjustable. The idea is to prevent tampering and overloading the horizontal-output system. This type of coil is set at the factory and should not require changing except when the horizontal-output transformer is replaced.

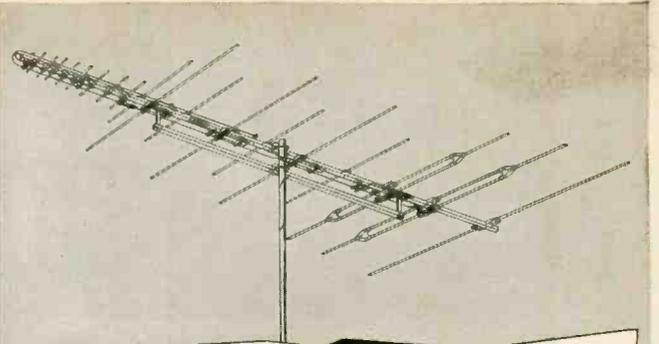A typical blue shaping circuit is shown in Fig. 6; this is a portion of the Silvertone 7190 series. To adjust the coil, connect an oscilloscope between



3-Way Combination FREE SPACE STANDING WAVE MAGNETIC ANTENNA

ZEROS IN
YOUR SIGNAL—

Discriminates Between
Desired Signal and
Unwanted Noise!

Here is an antenna with the unique ability to discriminate between the desired signal and unwanted noise! A complete absence of minor lobes and an extremely high front to back ratio are characteristics of these antennas. This is made possible by the development of the Free Space Standing Wave Magnetic Drive Antenna system (F.S.M.). The outstanding electrical qualities, combined with the simplified mechanical construction of this system yields a total performance package unparalleled in today's market. 4 models, 60-inch to 180-inch boom, all modestly priced.

UNEXCELLED!

UHF — VHF — FM — COLOR

INVESTIGATE NOW!

S&A Electronics Inc.

Manufacturers of the TARGET ANTENNA

210 West Florence Street
Toledo, Ohio 43605

Circle 122 on reader's service card

AND MICROCIRCUITS

V_{CES} — 25 volts
 I_C 500 mA

The CS2369, an npn diffused silicon planar transistor similar to the 2N2369, is designed for low-power, large-signal audio applications. Maximum voltage and current ratings are:


V_{CBO} 40 volts
 V_{CEO} 15 volts
 V_{EBO} 4.5 volts
 I_C 500 mA

Complete electrical, large- and small-signal characteristics are available from the manufacturer, Continental Device Corp., 12515 Chadron Avenue, Hawthorne, Calif. 90250.

THE "WOW" DIODE

A new silicon planar epitaxial sub-miniature diode has been developed for high-speed switching and core-driver applications. The diode, called W-O-W, for "without whiskers," features high conductance, high mechanical strength

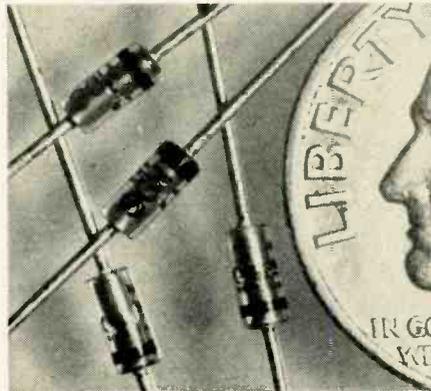and long-term stability. Electrical characteristics are maintained under high-temperature reverse-bias conditions. The hermetically sealed package is a



dual-stud, fused glass-to-metal design. Further information is available from Hughes Semiconductor Devices, 500 Superior Ave., Newport Beach, Calif. R-E

GET IT from GOODHEART!

EVERYTHING UNCONDITIONALLY GUARANTEED!

Brand new VHF revrs in original cartons; look exactly like the familiar BC-453 Command Revrs but are 9-tube superhet 108-135 mc AM revrs and very easy to power & control without touching anything inside the unit; you can even connect an S-Meter externally. We furnish schematic and complete instructions on all pin connections and also a spline tuning knob. A.R.C. Type No. R13B. No tuning dial; use graph of freq. vs. knob turns. 2 μ V sensitivity; 2 RF, 3 IF stages. Shpg wt 9 lbs for Los Angeles. BRAND NEW...\$22.50 R32 is same but w/adjustable squeleh...\$27.50

DZ-1 Superhet revr 15-70 & 100-1500 kc. 89.50
 A.R.C. 12 \pm 22 Command revr 540-1000 kc. 14.95
 A.R.C. 12 \pm 22 Command revr 540-1000 kc. 17.95
 APR-4Y AM/FM Revr mod. to 115 v 50/60 cy with pwr plug, book, tuners 38-1000 mc195.00
 CV-253/ALR Tuner brand new 38-1000 mc175.00
 APR-4Y with CV-253340.00
 P.U.R. for tuners 957-2200 and 2175-4000 mc.
 AT pwr sply good for AIT-13 w/data 49.50
 RA-62-B is AT pwr sply for SCR-522 only 17.95
 TDQ xmir 45 W Po A2, A3, 115-156 mc. 295.00
 TDZ xmir 30 W Po A2, A3, 225-400 mc.295.00
 LM-14 freq. meter, .01% 125 kc-20 mc. 57.50
 BC-221 freq. meter 69.50
 TS-323/UR freq. meter 20-480 mc., .001%169.50

ALL-BAND SSB RCVR BARGAIN: Hallerstatters R-45/ARR-7.. 550 kc to 43 mc continuous. Voice, CW, MCW, aligned, grtl. w/book; 2-RF, 2-IF's, S-meter; noise limr; 3 xtl, 3 non-xtl selective choices. Less pwr sply 149.50
 60 cy pwr sply: \$30. SSB product detector: \$20

TRANSISTORIZED LV REGUL. PWR SPLIES
 Univ. TQ36-1: Dual 0-50 vdc, 1A, metered119.50
 Dres-Barnes 62-143: 1/2-32 vdc, 15A, metered129.50
 Dres-Barnes 62-121: 1/2-36 vdc, 15A, metered149.50

ATT. PHYSICS. ENGRG DEPT PROFS: ATT. STANDARDS-LAB MANAGERS: We have many desirable exotic things for you at budget-stretching prices. Examples: National Cesium-Beam Freq. Standard puts out 10 dbm to 50 ohms at 0.1, 5, 100 & 500 mc w/accuracy 5 parts/100 billion. Honeywell Microvolt Potent. I&N Wenner Pot. Water Calorimeters at peanut prices. E & Pwr. Ph Angle Dynamometer Transfer Standards. NBS Traceable certified. Fluke & Kintel digit-dial pwr splies. Counters. DVM's. PLEASE ASK FOR YOUR NEEDS AS SPECIFICALLY AS POSSIBLE. We have no overall catalog.

TIME PAY PLAN: Any purchase totaling \$160.00 or more, down payment only 10%


Above is a small sampling of our terrific inventory. We ALSO BUY! We want Tektronix scopes, Hewlett-Packard eqpt., Aeronaut, radio-shop eqpt., etc. ... AND Military Communications of all kinds.

R. E. GOODHEART CO. INC.
 Box 1220-RE, Beverly Hills, Calif. 90213
 Phones: Area 213, office 272-5707, messages 275-5342

Circle 125 on reader's service card

CANADIANS: Ordering is easy . . . we do the paperwork . . . try a small order

SARKES TARZIAN TV TUNER 41mc

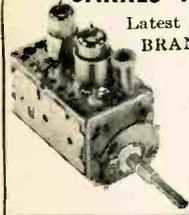


Latest Compact Model—good for all 41 mc TV's.
 BRAND NEW—MONEY BACK GUARANTEE

Best TUNER "SARKES TARZIAN" ever made—last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date.

COMPLETE with Tubes & Schematic . . . \$7.95

HIGHWAVE AM-FM PORTABLE RADIO

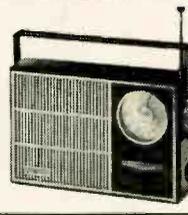

Elegance in Ebony & Chrome

14 Transistors - A Powerhouse of Quality Reception with AFC Operates on 4 "C" Cells
 22" Telescoping FM Antenna & Personal listening attachment
 Money refund - If not better than any Known Brand selling for even twice the price

8"x5 1/4"x2 1/4" - 4 lbs
 FREE - extra set of batteries

COMPLETE . . . \$19.50

IBM COMPUTER SECTIONS

8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.
 Incl. — Transistors, Condensers, Resistors, Heat Sinks, Diodes, Etc.
8 for \$1
100 for \$10


- | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|---|--|---|--|---|--|--|--|--|--|--|---|---|---|--|---|--|---|--|--|---|---|---|--|---|--|--|---|---|--|---|---|--|--|---|---|--|--|--|--|
| <input type="checkbox"/> 1000—ASST. HARDWARE KIT \$1
screws, nuts, washers, rivets, etc. | <input type="checkbox"/> 300 — ASSORTED HEX NUTS \$1
2/56, 4/40, 5/40, 6/32, 8/32 | <input type="checkbox"/> 250—ASST. SOLDERING LUGS \$1
best types and sizes | <input type="checkbox"/> 250—ASST. WOOD SCREWS \$1
finest popular selection | <input type="checkbox"/> 250 — ASST. SELF TAPPING SCREWS #6, #8, etc. | <input type="checkbox"/> 150—ASST. 6/32 SCREWS and 150 6/32 HEX NUTS | <input type="checkbox"/> 150—ASST. 8/32 SCREWS and 150—8/32 HEX NUTS | <input type="checkbox"/> 150—ASST. 2/56 SCREWS and 150—2/56 HEX NUTS | <input type="checkbox"/> 150—ASST. 4/40 SCREWS and 150—4/40 HEX NUTS | <input type="checkbox"/> 150—ASST. 5/40 SCREWS and 150—5/40 HEX NUTS | <input type="checkbox"/> 500—ASSORTED RIVETS
most useful selected sizes | <input type="checkbox"/> 500—ASSORTED WASHERS
most useful selected sizes | <input type="checkbox"/> 100—ASST. RUBBER BUMPERS \$1
for cabinet bottoms & other uses | <input type="checkbox"/> UNIVERSAL 4" PM SPEAKER \$49¢
Alnico 5 magnet, quality tone | <input type="checkbox"/> 100 — ASST. RADIO KNOBS \$1
all selected popular types | <input type="checkbox"/> 100 — ASST. TUBULAR CONDENSERS .001 to .47 to 600 v. . . | <input type="checkbox"/> 3—ELECTROLYTIC CONDENSERS
most popular number 50/30—150v | <input type="checkbox"/> 15 — G.E. #NE-2 TUBES
Neon Glow Lamp for 101 uses | <input type="checkbox"/> CLEAN UP THE KITCHEN "JACKPOT" Big Deal \$1
only one to a customer | <input type="checkbox"/> CHAPT ZU DI MITZIA "JACKPOT" double your money back if not completely satisfied . . . \$1 | <input type="checkbox"/> 50 — ASST. TERMINAL STRIPS all types, 1-lug to 6-lug . . . \$1 | <input type="checkbox"/> 25 — INSTRUMENT POINTER KNOBS selected popular types . . | <input type="checkbox"/> 5 — I.F. COIL TRANSFORMERS sub-min for Transistor Radios . . . | <input type="checkbox"/> 5 — AUDIO OUTPUT TRANSFORM Sub-min for Trans Radios | <input type="checkbox"/> 4 — TOGGLE SWITCHES SPST, SPDT, DPST, DPDT | <input type="checkbox"/> 32'—TEST PROD WIRE deluxe quality, red or black | <input type="checkbox"/> 10 — STANDARD TRANSISTORS \$1
NPN & PNP 2N404, 2N414, etc. | <input type="checkbox"/> 10—ASSORTED DIODE CRYSTALS \$1
1N34, 1N48, 1N60, 1N64, etc. . . | <input type="checkbox"/> 3 — TOP BRAND SILICON RECTIFIERS 1 amp, 1000 PIV . . . \$1 | <input type="checkbox"/> 5 — TOP HAT SILICON RECTIFIERS 500ma-400v — big value . . | <input type="checkbox"/> 100—ASST 1/4 WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 100 — ASST 1/2 WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 70 — ASST 1 WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 35 — ASST 2 WATT RESISTORS \$1
stand. choice ohmages, some in 5% | <input type="checkbox"/> 50 — PRECISION RESISTORS \$1
asst. list-price \$50 less 98% . . | <input type="checkbox"/> 20 — ASS'TED WIREWOUND RESISTORS, 5, 10, 20 watt . . . \$1 | <input type="checkbox"/> 100 — ASST. MICA CONDENSERS \$1
SRS some in 5% | <input type="checkbox"/> 5 — PNP TRANSISTORS \$1
general purpose, TO-5 case | <input type="checkbox"/> 5 — NPN TRANSISTORS \$1
general purpose, TO-5 case | <input type="checkbox"/> 10 — G.E. SAPPHIRE NEEDLES \$1
4G, V8-11, etc. (\$25.00 value) |
|---|--|---|--|---|--|--|--|--|--|--|---|---|---|--|---|--|---|--|--|---|---|---|--|---|--|--|---|---|--|---|---|--|--|---|---|--|--|--|--|

MARKET SCOOP COLUMN

- Mallory Electrolytic Condensers sparkling new—all sold at 3 for \$1
- | | |
|--|-----|
| <input type="checkbox"/> 3 — 50/50/50mfd — 450/250/250v | \$1 |
| <input type="checkbox"/> 3 — 100/80/20mfd — 300/300/300v | \$1 |
| <input type="checkbox"/> 3 — 250/200/50mfd — 175/175/175v | \$1 |
| <input type="checkbox"/> 3 — 80/40/20mfd — 300/300/300v | \$1 |
| <input type="checkbox"/> 3 — 200/200/40mfd — 200/150/150v | \$1 |
| <input type="checkbox"/> 3 — 80/40/40/40mfd — 150/150/150/25v | \$1 |
| <input type="checkbox"/> 3 — 1000/1000/500mfd — 35/35/20v | \$1 |
| <input type="checkbox"/> 3 — 50/10/160mfd — 450/400/250v | \$1 |
| <input type="checkbox"/> 3 — 40/40/40mfd — 450/300/150v | \$1 |
| <input type="checkbox"/> 3 — 30/200/4/4mfd — 475/475/475/25v | \$1 |
| <input type="checkbox"/> 3 — 150/100/100mfd — 350/350/50v | \$1 |
| <input type="checkbox"/> 3 — 50/40/30/30mfd — 450/350/300/300v | \$1 |

MERCHANDISE WANTED in any quantity — TUBES (all types) — RADIO & TV PARTS — EQUIPMENT finished or unfinished — immediate cash. Please send samples, quotes & amounts — only new merchandise bought.

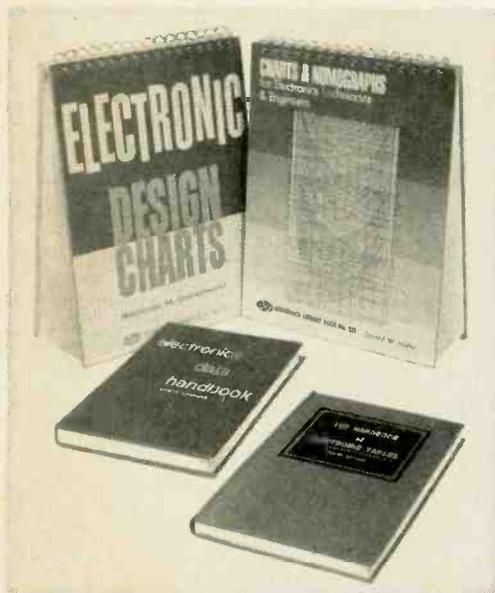A FREE 10-day trial to prove you can solve any electronics problem with these 4 databooks . . . and save \$5.00 in the process.



Very Probably the Most Helpful Electronics Reference Package Ever Offered!

These four comprehensive databooks will put immediate answers at your fingertips to speed you through any of your electronics projects faster and more efficiently. Now you will have instant answers — charts, nomographs, tables, formulas, key data — all engineered by specialists to meet your specific needs.

Here is the first place to look for authoritative answers to your toughest electronics problems — whether you are working with theoretical applications or practical projects. You focus quickly on the answers you want, reducing hours of figuring to seconds. The great value of these databooks is in their organization. Every conceivable type of problem is covered. They will never be out-of-date. You'll keep them at your elbow continually . . . to save time, effort and trouble.

Save \$5.00

Order at our risk for FREE 10-day Examination. SEND NO MONEY! Simply fill in and mail the handy NO-RISK coupon below for these helpful volumes! What's more, if you take all four volumes, you may have them at the special money-saving combination price of only \$16.80 — instead of their regular list price of \$21.80. You save \$5.00.

Save an extra \$1.00

Send your check or money order with your order for the complete set of 4 databooks. You save us billing costs, which we'll pass on to you. We pay postage and you deduct an extra \$1.00 off the combination price of \$16.80 (Same return privileges apply).

HERE ARE THE 4 DATA-PACKED BOOKS YOU RECEIVE . . . AT A \$5.00 SAVING!

ELECTRONIC DESIGN CHARTS by Norman H. Crowhurst. 128 pages — 50 different charts give you more information in less time. Save hours of design . . . simplify design procedure . . . solve electronics problems quickly, and easily. Permanent spiral binding keeps large, 8½ x 11" pages standing flat for ready reference. A valuable working tool for engineers and technicians. Cloth bound. \$5.95 if ordered separately. Order Book G-110.

CHARTS AND NOMOGRAPHS by Donald W. Moffat. 96 pages of instant solutions to hundreds of electronics problems. Avoid tedious calculations that delay your work. Simply turn to the appropriate page, put your ruler in place and read off the correct answers for a whole family of solutions simultaneously. Large, stand-up, 8½ x 11" format specifically designed for ease of use. Cloth bound. \$5.95 if ordered separately. Order Book G-121.

ELECTRONICS DATA HANDBOOK by Martin Clifford. 160 pages of the most needed electronics formulas and data gathered, arranged and coordinated for easy reference. An indispensable reference. Cloth bound. \$4.95 if ordered separately. Order Book G-118.

THE HANDBOOK OF ELECTRONICS TABLES by Martin Clifford. A valuable new approach for accurate solutions to a wide range of electronics problems. This 160-page reference eliminates the need for mathematical computations, formulas, slide rules. All answers have been worked out for you in easy-to-use, accurate, electronic tables. Cloth bound. \$4.95 if ordered separately. Order Book G-125.

OTHER HELPFUL BOOKS FOR EVERYONE IN ELECTRONICS

Electronic Designer's Handbook: A Practical Guide to Transistor Circuit Design by T. K. Hemingway—

Very probably the best book on transistor circuit design ever written for the practicing circuit designer. This up-to-date handbook provides a complete reference on transistor circuit design. Part I provides extremely helpful, detailed coverage of the transistor used as a switch, and as a small-signal amplifier. The designer will find Part II of particular value for its description of several unusual circuits and the straightforward discussion on how novel designs can be synthesized and modified to serve in a number of practical applications. The content is specifically intended to show the reader how to design his own circuits. Describes examples of the design of circuits, and shows how to simplify the theoretical analysis process which leads to practical designs. Typical values of transistor parameters are used in step-by-step examples of how to design basic circuits. The chapters on linear sweep and constant current circuits provide information not normally found in books on transistor circuit design. Contains much data of interest to designers looking for data they can draw upon to develop new and unique circuits. This book is specifically oriented to serve the needs of the practical design engineer, whether he be an "apprentice," or an "oldtimer." It shows how a designer's mind really works to achieve a circuit. 296 pps., 200 illus.

Order Book C-228 only \$8.95

Electronic Engineering Measurements Filebook;

Scrupski—A single source of measurement principles and practices, compiled for the express interest of electronic design engineers. This is not a book on the usual generalities of electronic tests and measurements, but rather a collection of detailed techniques, complete with test setups, waveforms, mathematical analyses, etc., of how to measure those specific parameters deemed most important in electronic circuit design. It concentrates on specialized and accurate measurement techniques used in a wide variety of applications by electronic equipment engineers. In almost every case, the

parameter measurements described cannot be made with procedures in general practice.

Order Book C-131 only \$9.95

Electronic Circuit Design Handbook: EEE Editors—

A carefully-planned, authoritative source of over 400 different, tried and tested circuits selected on the basis of their originality, novelty, and usefulness. This detailed compilation of practical design data provides the answer to the need for an organized gathering of proved circuits that can serve as "thought-starters" for design engineers. 256 pps., 19 sections; over 500 illus. 8½ x 11".

Order No. C-101 only \$14.95

Transistors for Audio Frequency: Guy Fontaine—

A practical reference and guide on the design of transistor circuits for use in audio frequency applications. The author has done a remarkable job of bridging the gap between transistor physics and practical design, providing qualitative formulations for designing circuits to serve specific applications. Discussions of network configurations and mathematical calculations are relatively simple, and the numerous physical models used as examples greatly aid comprehension. One of the many outstanding features is the use of multicolored diagrams throughout, adding considerable value and meaning to the illustrative content. Another feature is the treatment of concentration curves. 284 pps., 462 illus.

Order C-224 only \$9.50

CATV System Engineering Second Edition: William

A. Rheinfelder—The first and only engineering handbook on cable television system design, authored by a leading design engineer and foremost expert on the subject. For anyone interested in wired community TV systems, here is a veritable bible on the subject. Liberal use of design charts and graphs make the content especially valuable to engineers in video amplifier system applications. 256 pps., 140 illus.

Order TAB-98 only \$12.95

PUBLISHER'S GUARANTEE

Put the information in these books to work for you for 10 days. If they don't prove to be worth several times their cost, return them and we'll cancel invoice.

NO RISK COUPON — MAIL TODAY

TAB Books, Blue Ridge Summit, Pa. 17214

Please send me all 4 Databooks for only \$16.80.

Also send me: TAB-98 C-101 C-131 C-224 C-228 G-110

G-118 G-121 G-125

I enclose \$

Please invoice on 10-day FREE trial

Name

Company

Address

City State Zip

SAVE POSTAGE BY REMITTING WITH ORDER! RE 117


Circle 126 on reader's service card

WOOFING THE TWEETER

continued from page 42

mounted on the paperboard rear cover by passing a length of hookup wire around them and through two holes in the cover.

To stuff the cabinet, a slab of 1-inch foam rubber (made for pillows) was cut into proper-size pieces with scissors. Each piece was wrapped in plastic food-wrap before being put into place. (Sound waves travel with relative ease through foam rubber, but when a pressure wave impinges upon the air-tight plastic, it must either move the plastic or be reflected. The plastic moves because its inertia and that of the rubber behind it is low. The rubber is compressed. Inasmuch as the rubber reacts at a different rate, work is done, and the wave's energy is partially absorbed.)

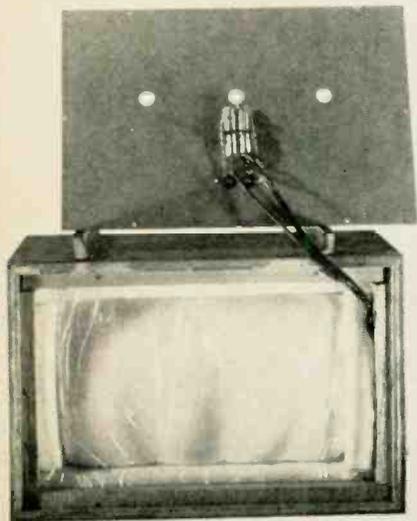

Plastic food wrap covers foam rubber to enhance compression and decompression of the enclosure. Speaker is behind padding.

Pieces to fit the top, bottom, and sides of the cabinet were wrapped and pushed into place. Two pieces were cut to lie flat against the front panel on either side of the speaker. A half-circle cut from the end of each piece made them fit the contour of the speaker. The next slab was cut full-length, and needed only a rectangular hole in the middle to let it slip over the magnet frame. The one after that was identical, and the next one needed no hole at all. A final slab (not shown in the photo) had a hole cut to accept the capacitors, and was used to compress the lot. (CAUTION: Don't use this type of stuffing in the same cabinet with a tube-type radio, TV, or amplifier. It is allergic to heat. And it could catch fire!)

R-E



PERMOFLUX ANNOUNCES A BRAND NEW HEADPHONE the "HM" SERIES

The entire audible spectrum, from the resounding bass smoothly thru the soothing middle ranges to the clear tingling highs, is awaiting you in the miniature ear-speakers, as these headphones comfortably engulf your ears. Feather-like in weight, fully adjustable, the superior Permoflux quality is now available at popular prices. A wide selection of impedances.

All ear speakers are fully warranted for life.

STANDARD OF THE WORLD

Permoflux Corp.

P.O. Box 6364, Dept. RE 11
GLENDALE, CALIFORNIA

Circle 127 on reader's service card

COMPLETE TUNER OVERHAUL

995

ALL LABOR AND PARTS
(EXCEPT TUBES & TRANSISTORS)*

VHF

UHF

COLOR

U-V

TRANSISTOR

COLOR TUNERS

GUARANTEED COLOR ALIGNMENT — NO ADDITIONAL CHARGE

Simply send us the defective tuner complete: include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days. UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only. Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.) And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

CASTLE

TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago 45, Illinois
41-96 Vernon Blvd., Long Island City 1, N. Y.


For service in Canada write to Chicago or use reader service card in this magazine.
*Major parts are charged extra in Canada.

Circle 128 on reader's service card

ELECTRIC EELS OPEN ZOO

Westinghouse electronic equipment was "plugged" into a tank of electric eels to officially open the new Pittsburgh Aqua-Zoo. An electric eel is a living battery—positive at the head and negative at the tail. When it detects food or an approaching enemy, it switches to full power and unleashes its death-dealing high voltage.

ELECTRONICS

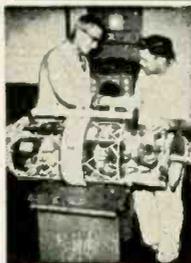

Engineering-Technicians

Bachelor of Science Degree, 30 Months
Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
 - Electrical Engineering (B.S. Degree)
 - Mechanical Engineering (B.S. Degree)
 - Civil Engineering (B.S. Degree)
 - Architecture (B.S. Degree) (36 Months)

The Nation's increased demand for Engineers, Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.

Approved for Veterans
DAY AND EVENING CLASSES



1215 Van Ness Avenue
San Francisco, California

Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name

Address

City

State

Olson®



FREE

Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS' Fantastic Value Packed Catalog**—Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____
 GIVE ZIP CODE _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

OLSON ELECTRONICS, INC.

749 S. Forge Street Akron, Ohio 44308

Circle 130 on reader's service card

NOTEWORTHY CIRCUITS


TREMOLO CIRCUIT FOR GUITAR AMPLIFIER

We receive a steady trickle of letters requesting information on adding a vibrato or tremolo circuit to an ordinary tube-type PA or hi-fi amplifier so it can be used with an electric guitar. *Vibrato* is a regular variation in frequency and circuits for producing it are not readily adapted to ordinary amplifiers.

Tremolo, a regular variation in amplitude or volume, is relatively easy to add to most amplifiers as indicated by this circuit from *Funkschau* (Munich, Germany).

The tremolo signal is generated by half of a 12AX7—or any similar triode—connected as a phase-shift oscillator. The usual ground connection for the output grids is lifted and the junction of the resistors is connected to the arm of the TREMOLO STRENGTH control. The tremolo signal is injected into both output grids in phase to modulate the push-pull audio signal.

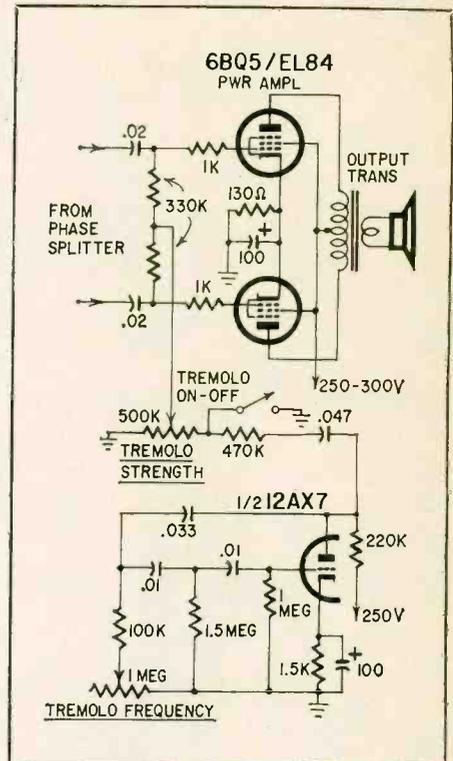The TREMOLO STRENGTH control sets the modulation depth. The TREMOLO FREQUENCY control adjusts the tremolo signal over a range of approximately 2–30 Hz.



U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known—World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

ORDER DIRECT FROM AD OR WRITE FOR CATALOGS

STANDARD DIAL TELEPHONE

• (ITEM #715) -- Standard, commercial telephone same as used throughout U.S.A. Attractive polished black, like new condition. Use as extension phone to private systems or connect several phones together for local intercom systems. Full instructions are furnished. Wt. 9 lbs. Original Cost \$24.50. F.O.B. **\$5.95**



STEP-BY-STEP AUTOMATIC SWITCH


• (ITEM #738) -- Amazing "up-and-around" electro-magnetic telephone switch. Dial any bank pair from 1 to 100. Make your own telephone system. Can also be used to remotely control up to 100 circuits over a single pair of wires.
 • One of our 100% STAR bargains. Comes complete with data, one dial and one line bank. Size, 5" x 7" x 13". Wt. 16 lbs. Cost Gov't Over \$75.00. Complete; Switch, cover, dial, line bank, instructions..... F.O.B. **\$9.95**



TYPICAL BUYS FROM OUR 1967 CATALOGS

- \$ 350.00 - Geared 2-hp Battery Golf Car Motor **\$24.95**
- \$ 15.00 - Westinghouse DC Ammeter, 0 to 300..... **\$ 7.11**
- \$ 40.00 - vacuum Pressure Pump, 12-VDC **\$11.95**
- - - 80-MW Walkie-Talkies, Per Pair **\$19.60**
- - - Deluxe, Multi-Range, AC/DC Tester **\$ 8.98**
- \$4000.00 - Carrier Telephone Amplifier System **\$13.91**

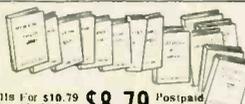SPECIAL SALE Correspondence Course in ELECTRICAL ENGINEERING



Sells for \$10.79 Outside U.S.A. **\$8.79** Postpaid In U.S.A.

• (ITEM #A181) -- Wonderful chance to obtain technical training at Amazing Low Cost! Lincoln Engineering School has suspended its Correspondence Course because of increased quoting costs. We offer a limited number of the school's complete Electrical Engineering Course but without the examination paper grading service. The course consists of 14 lesson unit books. Each book has the regular exams, and in a separate section, "Standard Answers" to each exam question.

• Course is well written, easy to understand, profusely illustrated. Reader's Digest size, easy to carry and study in spare time. Many Lincoln Engineering School students holding excellent jobs as a result of E.E.S. training. Course contains latest information on transistors, silicon diodes, etc. Additional book on how to build and operate a "Home Laboratory and Experimental Bench" furnished with each course.

SEND 25¢ COIN OR STAMPS FOR 3 MAIN CATALOGS

All Items FOB Lincoln Money Back Guaranteed

SURPLUS CENTER

DEPT. RE-117 LINCOLN, NEBR. 68501

Circle 131 on reader's service card

EMERGENCY LIGHT SYSTEM


Reliable emergency lighting is a must for many public buildings and a valuable asset in homes. During power failures it can prevent panic, injuries and possible loss of life. The diagram, from a G-E data sheet on the C106 SCR, shows a simple automatic emergency lighting system.

The lamp is a type 1073 normally used in automobile back-up lights. It is powered by a 12-volt storage battery. When ac power is on, the 100-μF capacitor is charged through D1 and R1. This places a negative voltage on the SCR gate and keeps it from conducting and lighting the lamp. The battery is

kept charged by rectifier D2.

When the ac power is interrupted, the capacitor discharges and the SCR is turned on by the positive gate voltage developed by current flow through R1, D1 and R3. Battery current flows through the lamp, the SCR and the transformer secondary. When ac power is restored, the capacitor recharges and turns off the SCR and lamp.

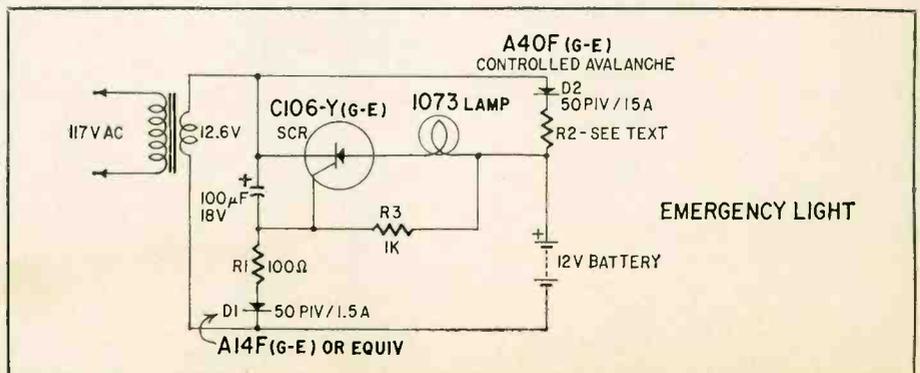
Current-limiting resistor R2 should be selected to limit the battery charging current to the required level. The battery rating should be adequate to power the 2-amp lamp at full brilliance for an adequate period of time. **R-E**



TRY THIS ONE

RADIO KNOB POINTERS

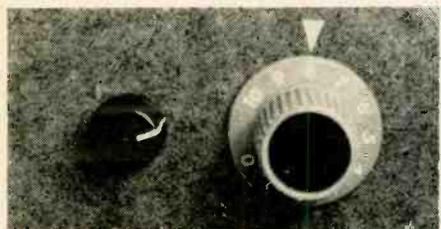When making pointers for radio knobs and panels it's a tough job to do neat work by cutting grooves and filling the grooves with white crayon or paint. An easier way is to cut your pointers from Scotch plastic tape and then stick




the pointers onto the knobs or panels, as shown in the photo.

Cut your pointers any size and shape, and stick them wherever you want them. It's surprising how long they last. To remove them just pull them off and your knobs and panels are left scratchless. Plastic tape comes in various colors, so use light colors on dark knobs and panels, and vice versa. —Art Trauffer

PROTECT DRILL BITS

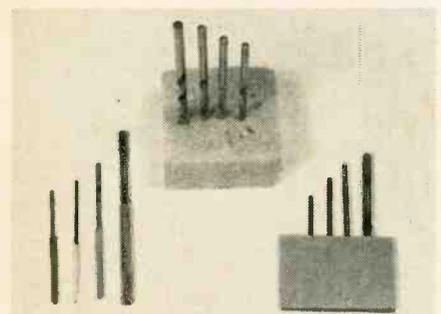If you don't own a drill index, be sure to store your small drills somehow so they don't become chipped and dull by banging around inside a drawer or tool caddy. There are many ways to do this. Spaghetti may be slipped over each



drill. For small drills, the corrugations inside a sheet of cardboard may be used. A block of Styrofoam plastic also works well. Just push the drills into it. This method works for any small tool with a sharp edge. —Don Lancaster R-E

THIS SPACE CONTRIBUTED BY THE PUBLISHER



The Voice. Anybody's voice. Your voice. It has a special quality and timbre all its own. But.

If it should become hoarse or if a cough should persist, find out what the reason is. Promptly. It could be a warning signal of cancer. And cancer is easier to cure when it's detected early.

Frank Sinatra knows the seven warning signals of cancer. Do you? 1. Unusual bleeding or discharge. 2. A lump or thickening in the breast or elsewhere. 3. A sore that does not heal. 4. Change in bowel or bladder habits. 5. Hoarseness or cough. 6. Indigestion or difficulty in swallowing. 7. Change in a wart or mole.

If a signal lasts longer than two weeks, see your doctor without delay.

It makes sense to know the seven warning signals of cancer.

It makes sense to give to the American Cancer Society.



Are You A 3rd-Grade Reader?

A noted publisher in Chicago reports there is a simple technique of rapid reading which should enable you to double your reading speed and yet retain much more. Most people do not realize how much they could increase their pleasure, success and income by reading faster and more accurately.

According to this publisher, anyone, regardless of his present reading skill, can use this simple technique to improve his reading ability to a remarkable degree. Whether reading stories, books, technical matter, it becomes possible to read sentences at a glance and entire pages in seconds with this method.

To acquaint the readers of this publication with the easy-to-follow rules for developing rapid reading skill, the company has printed full details of its interesting self-training method in a new booklet, "How to Read Faster and Retain More," mailed free. No obligation. Send your name, address, and zip code to: Reading, 835 Diversey Parkway, Dept. 684-01N, Chicago, Ill. 60614. A postcard will do.

Circle 132 on reader's service card

SCHOOL DIRECTORY

for a professional career

Tri-State graduates hold important engineering and business administration posts throughout the U. S. This professionally-oriented small college has outstanding placement record. Four-quarter year permits degree in three years. Excellent faculty. Well-equipped labs. Beautiful 300-acre campus. Accredited. Small classes. Modest costs. One-year Drafting-Design Certificate program. Enter Jan., March, June, Sept. For Catalog, write Director Admissions indicating career interest.



TRI-STATE COLLEGE
24117 College Avenue, Angola, Indiana 46703

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology and Electronic Technology curricula both available. Assoc. degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Feb. Sept. Dorms. campus. High school graduate or equivalent. Catalog.



VALPARAISO TECHNICAL INSTITUTE

Dept. C, Valparaiso, Indiana 46383


Learn Electronics for your SPACE-AGE EDUCATION at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech, in sunny Southern California.

COLLEGE OF ENGINEERING. Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

A & P SCHOOL. Practical experience on real aircraft. One-year course prepares you for F. A. A. A & P certificate. **WRITE TODAY FOR CATALOG.**

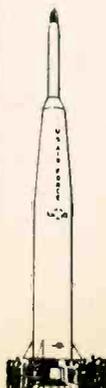NORTHROP INSTITUTE OF TECHNOLOGY
1199 W. Arbor Vitae, Inglewood, Calif.



ENGINEERING MATHEMATICS

NOW! A NEW WAY TO LEARN—I. H. S. I. WAY. A complete home study course in engineering math to help you get the position you want—**MORE MONEY—MORE RESPECT.**

COURSE PREPARED BY COLLEGE PROFESSORS

who have lectured to thousands of men on math and engineering. You learn at home quickly, easily—**AS FAST** as you want.

YOU SIGN NO CONTRACTS

Pay only if satisfied—you owe it to yourself to examine the **INDIANA HOME STUDY INSTITUTE COURSE IN ENGINEERING MATH.**

FREE BONUS—if you join now, a refresher course in basic arithmetic.

Write for Brochure—No Obligation.

THE INDIANA HOME STUDY INSTITUTE
Dept. RE-11, P.O. Box 1189
Panama City, Fla. 32401

MARKET CENTER

GENERAL

CONVERT ANY TELEVISION to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. RELCO-A25, Box 10563, Houston 18, Texas

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656

FREE ELECTRONICS (new and surplus) Parts catalog. We repair multimeters. BIGELOW ELECTRONICS, Bluffton, Ohio 45817



TUNAVERTERS
POLICE, FIRE, AIR-CRAFT, MARINE AND AMATEUR CALLS ON YOUR BROADCAST RADIO! Tunable RF converters. 6-1 reduction tuning.

See complete listing in Sept. RE, page 84
HERBERT SALCH & CO., WOODSBORO RE11, TEX. 78393

INTEGRATED CIRCUIT SALE

Selling Like Crazy

ICS TO-5/TO-46 RTL, Gates, Buffs., FFs, Adders etc with 8 hole test socket 100 asstd. \$10.95
ICs, TO-85 Flatpacks DTL/RTL Some Plated include Auger Test Socket, 100 asstd. \$12.95
Flatpacks, All Gold Plated w/socket, 100 \$15.95
Half Packs of above, \$5.95, \$6.95 & \$8.50. (Less test socket. Extra test sockets, \$1.00 each)
All ICs sample test over 50-80% good. Schematics, identification & test info. included.
Hi-Gain (Darlington) Amplifier, TO-18 NPN. Similar 2N398 Tested 7 for \$2.95
Field Effect Trans. (FET) P channel Similar 2N3277 TO-5, tested 4 for \$2.95, U-Test 10 for \$2.95
Dual Trans. (Diff. Amplif) 6 lead choice TO-5/18 NPN/PNP, Sim. 2N2060 Tested 7 for \$2.95, U-Test 50 for \$5.95, 100 for \$8.95, asstd. NPN Sil. Power HV TO-3, TO-66, TO-59 20MHZ Choice 7 for \$2.95, U-Test 50 Asstd. \$6.95
Microcleared Relay 3/8" sq x 1 1/4" Ax. leads. Norm. open 3000 ohm coil, pick on 6V 3 ma. 4 for \$2.95
Memory Plane 5" x 8" with 4000 wired toroid bits . . . Perfect. \$9.75; Damaged plane . . . \$3.75
Memory Plane 10" x 10" with 10,000 wired toroid bits, perfect \$15.00. Damaged plane \$5.00
Matrix Board 2" x 3" 100 wired toroids \$2.00
Memory Info. included, Add 1 lb. Postage.
Nuvistors, #7895 with socket panel 4 for \$2.95
Lampdriver, SCR Module w 6-10V lamp 6 for \$2.95
Jumbo Silic. Trans. Asst. Over 1000 TO-5, 18, 46, 52, 66, 3, 4, 6, 8 lead devices incl. mostly Trans. duals, Darl. FETs, SCRs, ICs & power types & diodes. Sample test 50 to 90% good. Including Pomona Flare top test socket. Postage 3 lbs. \$19.50; Half Pack of above, less socket \$9.95

Free Goody Bag with \$10 order (25¢ postage)

Add postage for heavy items, others ppd. California orders 5% sales tax.

Catalog now ready. All mdse. guaranteed

MIKE QUINN ELECTRONICS

Bldg. 727 Langley Street
Oakland Airport, Calif. 94614

Circle 141 on reader's service card

TREASURE HUNTERS! PROSPECTORS! Relco's new instruments detect buried gold, silver, coins. Kits, assembled models. Transistorized. Weighs 3 pounds. \$19.95 up. Free catalog. RELCO-A25, Box 10839, Houston, Texas 77018

BACK-ISSUES, Electronic, Scientific Magazines. SEMCO, Box 130, Roxboro, Quebec, Canada

WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000

Wanted, HEATHKIT Q-METER, HAROLD MURRAY, Box 74, Neffsville, Pa. 17556

Wanted, BLONDER AUDIO BATON. PERE, 2143 Pressler, Akron, Ohio 44312

"TAB" • SILICON ONE-AMP DIODES

Full Leads Factory Tested & Gtd! U.S.A. Mfg

Piv/Rms	50/35	100/70	200/140	300/210
400/280	600/420	800/560	900/630	
1000/700	1100/770	1700/1000	2400/1680	
50 Piv	70	100	175	
PRV 7A	25A	PRV 7A	25A	
50	.45	.75	500	2.50
100	.65	1.15	600	2.75
200	1.00	1.60	700	3.00
300	1.50	2.00	800	3.60
400	2.00	2.50	900	4.30
				5.90

SILICON POWER DIODES & STUDS

D.C. Amps	50 Piv	100 Piv	200 Piv	600 Piv
15	35 Rms	70 Rms	140 Rms	420 Rms
45	.22	.40	.65	1.20
160	.45	.75	1.15	1.85
250	2.25	2.65	3.50	6.50
	3.50	4.50	6.00	12.25

TERMS: Money Back Guarantee
Our 22nd Year. \$2 Min.
Add Shipping Charges
111 Gx LIBERTY ST., N. Y., N. Y. 10006
Send 25¢ Phone: REEtor 2-6245 for Catalog

NAVY MARINE BAND WALKIE TALKIE

TRANS. & RECEIVER—Crystal controlled, can be operated on any one channel in freq. range 2.3 to 4.5 MC. Voice (A3) communication only; output of Trans. is 0.2 watts & satisfactory communication between units should be maintained up to approx. one (1) mile. With tubes: 1/185, 1/185, 2/1T4, 3/384. Voltages required: 67.5 VDC 3 MA; 135 VDC 4 MA; 1.5 VDC 225 MA for REC. —67.5 VDC 1.5 MA; 135 VDC 19 MA; 1.5 VDC 225 MA; & —6 VDC 30 MA for TRANS. Waterproof plastic case w/space for batt. or power supply. Telescoping antenna 8 ft. has special loading coil, complete w/tubes, antenna. 2 crystals FT-243 (no choice of freq.) headphones, carbon mic., canvas cover, & manual. Size: \$9.95
3 x 8 x 2 1/2" Wt.: 3 lbs.
"DAV" MODEL—Same as above, but with direction finding loop circuit for homing; & lip. mic. Ply. wood case w/ carrying straps. Wt.: 11 lbs. \$12.95
Dry Charge Battery N-T-6 1/above Pow. Sup. \$3.95
Vibrator Power Supply 1/MAB & DAV—New \$6.95
Prices F.O.B. Lima, O.—25% Deposit on C.O.D.—BIG FREE CATALOG—Send for your copy now. Dept. RE

FAIR RADIO SALES

1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

TRANSISTOR BOARDS

#103 2EA 2N706, 6EA IN917 . . . 6 Boards \$3.00
#101 6EA 2N711 . . . 2 Boards \$3.00
#301 3EA 2N1411 . . . 4 Boards \$3.00
Above, new, minimum salvageable lead length 1/2 in.
Audio Tape, 1/4 in. 1 1/2 mil, approx. 4000 ft., 2 reels \$7.50
Shipped Prepaid Continental U.S.A.

88-108 MC F.M. RECEIVER

10 TUBE CRYSTAL CONTROLLED F.M. RECEIVER WITH TUBES VOLUME TONE CONTROLS 4 WATT OUTPUT. 115 V 60 CYCLE. METAL CABINET 8H x 10D x 12W. WITH DIAGRAM LESS CRYSTAL AND SPEAKER. REMOVED FROM SERVICE BY STORECAST OUTFIT THAT WENT SOLID STATE. \$14.50 EA: 2 for \$25.00 PLUS SHIPPING.

LEED'S RADIO, 57 WARREN ST., N.Y.C. 10007
Tel: (212) 267-3440

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Aerovox Corporation (Distributor Div.)	16
Allied Radio Corp.	85
Amperex Electronic Corp.	Second Cover
Arco Electronics (A Division of Loral Corporation)	5
Arrow Fastener Co., Inc.	82
Artisan Organs	82
B & K (Division of Dynascan Corporation)	83
Barker Products Co. (Audio Division of Component Manufacturing Service, Inc.)	24
Brooks Radio & TV Corp.	92-93
Burstein-Applebee Co.	87
Capitol Radio Engineering Institute, The	46-49
Castle TV Tuner Service, Inc.	95
CLASSIFIED	98-101
Cleveland Institute of Electronics	15, 18-21
Conar (Div. of National Radio Institute)	83
Cornell Electronics Co.	100
Datuk Corporation, The	82
Delta Products, Inc.	67
DeVry Institute of Technology (A Subsidiary of Bell & Howell)	7
EICO Electronic Instrument Co., Inc. Third Cover Electro-Voice, Inc.	6
Finney Co.	79
GC Electronics Co.	14
Goodheart Co. Inc., R. E.	93
Graham School of Electronics	2
Great Lakes Insurance Co.	81
Heald Engineering College	95
Heath Company	68-71
International Crystal Mfg. Co., Inc.	102
Jensen Tools and Alloys	81
Lafayette Radio Electronics	89-90
Mallory Distributor Products Company (Div. of P. R. Mallory & Co., Inc.)	23
Mike Quinn Electronics	98
Music Associated	92
National Radio Institute	8-11
National Technical Schools	13
Olson Electronics, Inc.	96
Perma-Power Company	73
Permotlux Corp.	95
Poly Paks	101
Quietrole Co.	82
Radar Devices	1
RCA Electronic Components and Devices Tubes	Fourth Cover
RCA Institutes	28-31, 84
RCA Parts and Accessories	17
Reading Improvement Program	97
Rye Industries, Inc.	86, 87
S & A Electronics Inc.	91
Sams & Co., Inc., Howard W.	25, 65-66, 78
Score	81, 88
Solid State Sales	99
Sony Corp. of America	22
Sony/Superscope	63
Sprague Products Company	26
Suprex Electronics	64
Surplus Center	96
Sylvania (Subsidiary of General Telephone & Electronics)	27
TAB Books	94
Turner Microphone Company, The	80
United Radio Co.	99
Warren Electronic Components	100
Weller Electric Co.	72
Winegard Co.	12
MARKET CENTER	98-101
Arcturus Electronics Corp.	
Edmund Scientific Co.	
Fair Radio Sales	
Leed's Radio	
McGee Radio	
Salch & Co., Herbert (Marketing Division of Tompkins Radio Products)	
TAB	
Terado Corporation	
SCHOOL DIRECTORY	97
Indiana Home Study Institute, The	
Northrop College of Science & Engineering	
Tri-State College	
Valparaiso Technical Institute	

ELECTRONICS

BARGAINS in Canadian Electronic equipment and surplus. Send \$1.00 for giant catalogs. ETCO, Box 741, Dept. R, Montreal, Canada

JAPAN DIRECTORY. Electronics, general products. Location services. Single replacement parts. Trade paper subscriptions. \$1.00 today. NIPPON SHOGYO, Box 6266, Spokane, Wash. 99207

TUBES. "Oldies", latest. Lists free. STEINMETZ, 7519 Maplewood, Hammond, Indiana 46324

RECEIVING & INDUSTRIAL TUBES. TRANSISTORS. All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and SAVE! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

Discharge IGNITION, PHOTOFLASH. Free catalog parts, kits. TRANSPARK, Carlisle, Mass. 01741

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

MESHNA'S TRANSISTORIZED CONVERTER KIT Converts car radio to receive police & fire. 35-50Mc or 100-200Mc. (one Mc tuning) with simple step instructions \$5.00. MESHNA, No. Reading, Mass. 01864

TV CAMERAS: Assembled and kits. Also plans, vidicons, lenses, scan coils, etc. NEW catalog 10¢. ATV RESEARCH, Box 453, Dakota City, Nebr. 68731

GIANT JAPANESE ELECTRONICS CATALOG. \$1. DEE, 10639A Riverside, North Hollywood, Calif. 91602

AUDIO - HI-FI

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. STEREO-PARTI, 1616-R Terrace Way, Santa Rosa, Calif. 95404

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 239R East 149th St., N.Y., N.Y. 10451

TAPE RECORDER SALE. Brand new, latest models. \$10.00 above cost. ARKAY SALES, 1028-E Commonwealth Ave., Boston, Mass. 02215

STEREO TAPES. Save up to 60% (no membership fees, postpaid anywhere USA). Free 60-page catalog. We discount batteries, recorders, tape accessories. Beware of slogans "not undersold," as the discount information you supply our competitor is usually reported to the factory. SAXITONE, 1776 Columbia Road, Washington, D. C. 20009

TAPEMATES makes available to you ALL 4-TRACK STEREO TAPES—ALL LABELS—postpaid to your door—at tremendous savings. For free brochure write TAPEMATES CLUB, 5727 W. Jefferson Blvd., Los Angeles, Calif. 90016

HAMMOND STEREO-REVERBERATION! Mechanism—\$4. CAL'S, Box 234, Dearborn, Michigan 48121

LIKE MUSIC WITHOUT COMMERCIALS? Completely wired 67 KHz SCA (background music) adapter Model SCA-2 for \$34.95. Five tuned circuits, two silicon transistor amplifier and ratio detector. Four connections to your FM receiver. Instructions included—No adjustments. Operates on 6 to 12 Volts DC. Size: 2½ x 3 x ¾ inches. Dealer inquiries invited. Available installed in a nationally advertised six tube AM-FM radio for \$59.95. Also available installed in a nationally advertised ten transistor AM-FM portable for \$79.95. Texas residents add 2% sales tax. KENZAC CO., P.O. Box 66251, Houston, Texas 77006

RADIO YESTERYEAR. Complete broadcasts of all the old favorites. One Hour sample tape \$5. Catalogue \$1 (refundable). Sample page 10¢. E. CHARMER, Box Eleven, Highbridge Station, Bronx, New York 10452

INVENTIONS & PATENTS

INVENTIONS-IDEAS developed. Cash/Royalty sales. Member: UNITED STATES CHAMBER COMMERCE, Raymond Lee, 230-U Park Avenue, New York City 10017

BUSINESS AIDS

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books. Invoices, job tickets, phone message books, statements and file systems. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656.

1,000 Business Cards, "Raised Letters" \$3.95 postpaid. Samples. ROUTH, 5717 Friendswood, Greensboro, N. C. 27409

DIAGRAMS, service information, Radio \$1.00, Television \$1.50. SUPREME, 1760 Balsam, Highland Park, Ill. 60035

TWO-WAY RADIO SERVICE INVOICE FORMS—Detailed. Free Sample Form No. 50 and Catalog. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

Attention: TV Service Dealers. HIGHLY DETAILED TV SERVICE ORDER FORM STOPS PRICE COMPLAINTS BEFORE THEY START. FREE CATALOG AND SAMPLE NO. 206. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

Attention: TV Service Dealers. TV SERVICE CONTRACTS FORMS. Free Catalog and Samples No. 105. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

"PROFIT GUARD" BOOKKEEPING SYSTEM FOR TV SERVICE. Complete—easy to use. Free Catalog and Sample No. 1800 Page. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

ALL OUR TRANSISTORS & RECTIFIERS ARE GUARANTEED TO WORK.

Our semiconductors have full factory length leads, are American made, unused, and in good physical condition. Our technical descriptions and pictures are accurate.

Our transistors are checked for voltage & gain to insure our customers a good transistor within the category we advertise. We will stand on our reputation for quality devices and service.

1 AMP Top Hat & Epoxy

PRV	AMP
100	.07
200	.09
400	.12
600	.18
800	.22

PRV	AMP
1000	.35
1200	.50
1400	.65
1600	.80
1800	.90

TRIACS

TO-66
5 AMPS

PRV
100
200
300
400
500

- 10 WATT ZENERS. 3—200V. State desired voltages Ea. \$75
- 50 WATT ZENERS. 6—200V. State desired voltages ...\$175
- SILICON BILATERAL SWITCH. Replaces two SCR's by firing in either direction when breakdown voltage is exceeded. Used in light dimmers, etc. 2/\$1.00
- 1000 PRV at 3A full wave bridge\$3.50
- NEON LIGHT of NIXIE TUBE DRIVERS. An NPN TO-18, Si Transistor with a V_{CEO} of 120 3/\$1.00
- SIM. to 2N2875 (PNP). Silicon 20 watts with 30 MHz cut off \$75
- HIGH-VOLTAGE NPN 150V VBCBO at 2.5A, hi gain in TO-66 pack \$75

Silicon Power Rectifiers

PRV	3A	12A	20A	40A
100	.09	.30	.40	.75
200	.16	.50	.60	1.25
400	.20	.70	.80	1.50
600	.30	1.00	1.20	1.80
800	.40	1.25	1.50	2.30
1000	.55	1.50	1.80	2.70

MORE INTEGRATED CIRCUITS



- SR FLIP FLOPS \$.90
- JK FLIP FLOPS \$1.15
- DUAL NAND NOR GATES ... \$1.00
- SR Clocked FLIP FLOPS ... \$1.15
- SRT FLIP FLOPS \$1.15
- 8 INPUT NAND NOR GATES .. \$1.00
- DUAL AND GATE \$1.00
- QUAD NAND NOR GATES ... \$1.00

TO-85 flat pack with holder. Guaranteed to work. They come complete with schematic, elect. characteristic sheet and some typical applications.



Silicon Control Rectifiers TO-66 pack

PRV	3A	7A	20A
50	.35	.45	.70
100	.50	.65	1.00
200	.70	.95	1.30
300	.90	1.25	1.70
400	1.20	1.60	2.10
500	1.50	2.00	2.50
600	1.80	2.40	
700	2.20	2.80	
1000		4.00	

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage, Average Wt. per package ½ lb. Allow for C.O.D. Minimum Order \$3.00

POST OFFICE BOX 74 D
SOMERVILLE, MASS. 02143

Send For Our Fall Catalog Featuring Transistors, Rectifiers And Components

Circle 143 on reader's service card

SILICON RECTIFIER SALE

IMMEDIATE DELIVERY

FULLY GTD AMERICAN MADE NEWEST TYPE FULLY TESTED

1 AMP SILICON "TOPHAT" & EPOXY DIODES
LOW LEAKAGE FULL LEAD LENGTH

PIV/RMS 50/35 .05 ea.	PIV/RMS 100/70 .07 ea.	PIV/RMS 200/140 .10 ea.	PIV/RMS 300/210 .12 ea.
PIV/RMS 400/280 .14 ea.	PIV/RMS 500/350 .19 ea.	PIV/RMS 600/420 .24 ea.	PIV/RMS 700/490 .25 ea.
PIV/RMS 800/560 .30 ea.	PIV/RMS 900/630 .40 ea.	PIV/RMS 1000/700 .50 ea.	PIV/RMS 1100/770 .70 ea.

ALL TESTS AC & DC & FWD & LOAD
SILICON POWER DIODE STUDS

D.C. AMPS	50 PIV 35 RMS	100 PIV 70 RMS	150 PIV 105 RMS	200 PIV 140 RMS
3	.08 ea	.12 ea	.16 ea	.22 ea
12	.25	.50	.65	.75
35	.65	1.00	1.25	1.40
100	1.00	1.20	1.50	1.75
160	2.50	3.00		3.75

D.C. AMPS	300 PIV 210 RMS	400 PIV 280 RMS	500 PIV 350 RMS	600 PIV 450 RMS
3	.27 ea	.29 ea	.37 ea	.45 ea
12	.90	1.30	1.40	1.65
35	2.00	2.35	2.60	3.00
100	2.50	3.50	4.00	5.00
160	4.25	4.75	5.10	Ask

"SCR" SILICON CONTROLLED RECTIFIERS "SCR"

PRV AMP	7	15	25	16	25
25	.50	.75	1.00	250	1.75
50	.60	.90	1.25	300	2.00
100	.80	1.25	2.50	400	2.40
150	.90	1.50	3.00	500	2.75
200	1.25	1.80	2.25	600	3.40
					4.00
					4.50

SPECIALS! SPECIALS!

Westinghouse 160 AMP, 500 PIV SILICON HI-POWER STUD RECTIFIER IN1666. Limited quantity. \$5.10 ea. 10 for \$45.00

100 Different Precision Resistors 1/2-1-2 Watt 1/2%-1% TOL \$1.25

Asst transistor Kit. P.N.P.—N.P.N. All popular types. Unchecked 100 for \$2.95 500 for \$9.95

Computer Grade Condenser 15,500 MFD 12 VDC American Mfg. .75 ea. Type IN34 DIODE GLASS .07 ea 100 for \$3

Money Back guarantee. \$2.00 min. order. Include additional \$ for postage. Send check or money order. C.O.D. orders 25% down.

Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • 212 OR 3-2620

Circle 144 on reader's service card

MARKET CENTER

REGISTRY AND JOURNAL for TV APPLIANCE AND EQUIPMENT DEALERS. Keeps record of daily sales by make, model, serial, etc. Stops inside theft. Provides quick reference. Free catalog and sample page No. 1700. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill.

WANTED! TV-RADIOMEN to learn aircraft electronics servicing. Numerous job openings everywhere. Write: ACADEMY AVIONICS, Reno/Stead Airport, Reno, Nevada

HIGHLY EFFECTIVE HOME STUDY COURSE in Electronics Engineering Mathematics with circuit applications. Earn your Associate in Science degree. Free literature. COOK'S INSTITUTE OF ELECTRONICS ENGINEERING, P.O. Box 36185, Houston, Texas 77036 (Established 1945.)

HIGHLY EFFECTIVE HOME STUDY REVIEW for FCC commercial phone exams. Free literature. COOK'S SCHOOL OF ELECTRONICS, P.O. Box 36185, Houston, Texas 77036

ASSOCIATE DEGREE IN ELECTRONICS earned, first half by correspondence and second half in residence. Free catalog. GRANTHAM INSTITUTE, 1505 N. Western Ave., Hollywood, Calif. 90027

EDUCATION/ INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING. New home study course covering all make electronic organ including transistors. Experimental kits—schematics—trouble-shooting. Accredited NHSC-GI Approved. Write for free booklet. NILES BRYANT SCHOOL, 3631 Stockton Blvd., Dept. F, Sacramento 20, Calif.

WRITE NOW FOR 1968 SENT FREE

McGEE'S CATALOG

1001 BARGAINS IN SPEAKERS—PARTS—TUBES—HIGH FIDELITY COMPONENTS—RECORD CHANGERS—Tape Recorders—Kits—Everything in Electronics 1901 McGee Street, Kansas City (RE), Missouri 64108

FREE ARCTURUS CATALOG
A Trusted name in Electronics Since 1925
Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices.

ARCTURUS ELECTRONICS CO.

502-22nd St., Dept. RE, Union City, N. J. 07087

8 PIECE TOOL KIT

69¢

in original mfr's bags and boxes

- 10 Shipping
- contains 4 Bristle Wrenches
- 1 Hex Blade
- 2 Alignment (tuning) Tools

CORNELL TUBES

1 YR. GUARANTEED

Mutual Conductance Lab-Tested, Individually Boxed, Branded and Code Dated. Tubes are new, or used and so marked.

33¢

PER TUBE

100 TUBES OR MORE: 30¢ PER TUBE

Special!

With every \$10 Order

25¢

per tube

No Limit from this list:

6AG5	6SN7
6AQ5	6CB6
6AU6	6J6
6W4	6W6

INTERFERENCE TV TRAPPER

SUPPRESS PICTURE INTERFERENCE CAUSED BY:

- AUTO IGNITION
- AIRPLANES
- APPLIANCES
- NEON SIGNS
- OIL BURNERS
- AMATEUR RADIO TRANSMITTERS

159¢

TV LIFESAVER! STOP TUBE BURNOUTS!

179¢

SILICON RECTIFIERS

all purpose ELECTRONIC CLEANER

89¢

plus 20¢ shipping

CORNELL TUBE CARTONS

HIGH GLOSS CLAY COATED RED & BLACK WITH BUILT IN DIAGONAL PARTITIONS

SIZE	PRICE PER 10 CARTONS	PRICE PER 100 CARTONS
11,000	.29	2.59
11,000	.39	3.49
5,500	.59	5.29
2,750	.89	7.99

TUBE SUBSTITUTES \$1.25

RADIO-TV TUBE TESTER

289¢

plus 30¢ shipping

TEST and REPAIR TV & RADIO SETS APPLIANCES

NEW EASY TO USE! COLOR TV DEGAUSSER

395¢

plus 40¢ shipping

BARGAIN CORNER

Solder Iron	1.49
Elect Tape	.89
Epoxy (pr.)	.79
Diode Kit	.39
Noise Filter	.89
Neon Tester	.59
Solder	.39
Antenna Coupler	1.89
Battery Charger	4.95

SILICON RECTIFIERS

all purpose ELECTRONIC CLEANER

89¢

plus 20¢ shipping

NEW PRACTICAL TV TRAINING COURSE

ONLY \$3.50

plus 50¢ shipping charges

Both above courses \$6.00

PRESTIGE & SUCCESS ARE YOURS AS AN ELECTRONIC EXPERT

FOR CORNELL CUSTOMERS ONLY by special arrangement with the publisher, these amazing bargains are available

COMPLETE RADIO SERVICING AND BASIC ELECTRONICS COURSE ONLY \$3.00

NEW PRACTICAL TV TRAINING COURSE ONLY \$3.50

Both above courses \$6.00

CORNELL ELECTRONICS CO.

Dept. RE 11 4217 University Ave., San Diego, Calif. 9 2 1 0 5

TERMS: Add 3c per tube shipping. Orders under \$5.00 add 3c per tube shipping plus 50c handling. Canadian orders add approximate postage. Send 25% deposit on C.O.D. orders. No C.O.D. orders under \$5.00 or to Canada. No 24 hr. free offer on personal check orders. 5-DAY MONEY BACK OFFER

SEND FOR FREE CATALOG

Circle 145 on reader's service card

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.
NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.
 Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for February issue must reach us before December 10th.
WORD COUNT: Include name and address. Name of city (Des Moines) or state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8-10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write **ELKINS INSTITUTE**, 2603E Inwood Road, Dallas, Texas 75235


"SLEEP-LEARNING." Send for free brochure, "What's It All About." **TAPES**, Box-190RE, Quincy, Mass. 02169

WATCH REPAIRING. Learn to repair American and Swiss watches in spare time at home. Tuition \$5 monthly. Diploma awarded. Free sample lesson. No obligation. **CHICAGO SCHOOL**, Dept. REL, Fox River Grove, Ill. 60021

Top Paying Jobs—Guidance Manual \$1. **CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY**, 263E Adelaide St. W., Toronto

GOVERNMENT SURPLUS

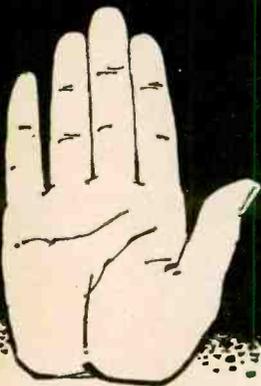72 page illustrated Government Surplus Radio, Gadgeteers Catalog 25¢. **MESHNA**, Nahant, Mass. 01908



Are you holding up the U.S. MAIL?

YOU ARE if you don't help your Post Office by using Zip Code in the address you are writing to, and in your own return address so others can zip their mail to you.

Published as a public service in cooperation with The Advertising Council.

AC POWER FROM YOUR CAR OR BOAT BATTERY

Standard home electricity (60 cycle, 117 volts) for small appliances, record players, tape recorders, tools, etc.

Inverters from 25 to 600 watts, priced as low as \$15.95.

See your Electronics Parts Dealer, or write



terado CORPORATION
 1053 Raymond Ave., St. Paul, Minn. 55108

Business Opportunities

PICTURE TUBE REBUILDING PLANT: 500 tubes per month. Color, monochrome. Complete inventory, modern, operating. Illness forces sale. \$28,000 value. \$18,000. terms. Will train. CRT, 5837 Wardlow Rd., Long Beach, Calif.

UNUSUAL BARGAINS EXCELLENT XMAS GIFTS!

GIANT WEATHER BALLOONS



"Balls of fun" for kids, traffic stoppers for stores, terrific for amateur meteorologists. Create a neighborhood sensation. Great backyard fun. Exciting beach attraction. Made of heavy duty neoprene. Inflate with vacuum cleaner or auto air hose; or locally available helium for high rise.

Stock No. 60.588EH . . . (8' diam.) . . . \$2.00 Ppd.
 Stock No. 60.532EH . . . (16' diam.) . . . \$7.00 Ppd.

NICKEL-CADMIUM BATTERY BARGAINS

Terrific value—used government surplus. Quick-charge, lightweight 6-volt nickel-cadmium battery. 4-amp. hour capacity. Almost unlimited life—thousands of discharge-charge cycles with minute deterioration. Charges fully in approx. 1 hr. with Edmund Charger Kit. Hundreds of uses for hobby, photography, model building, industry, etc. Only few drops of water yearly for full maintenance. Req. minimum of electrolyte-sealed to prevent loss. Delivers nearly 100% output at below freezing. Maintains constant voltage through major portion of capacity. Five vented 1.2 volt cells strapped in 3 polypropylene bands. 3 1/2"x2"x8". 10 & "Jumbo" 275 Ampere Hour Batteries also available. Write for info.



ONE NEW 1.2 VOLT NICKEL-CADMIUM CELL . . . \$15.00 Ppd.
 Stock No. 40.798EH . . . 5 3.95 Ppd.
 CHARGER KIT FOR 6-VOLT BATTERY . . . \$ 8.00 Ppd.
 Stock No. 70.807EH . . .

Order by Stock No. Check or M. O.—Money-Back Guarantee.
EDMUND SCIENTIFIC CO. 300 EDCORP BLDG. BARRINGTON, N.J. 08007

CLIP AND MAIL COUPON TODAY

SEND FOR FREE CATALOG "EH"

EDMUND SCIENTIFIC CO.
 300 EDCORP BUILDING
 BARRINGTON, N.J. 08007

Completely new 1968 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many war surplus items: for hobbyists, experimenters, workshop, factory. Mail coupon for catalog "EH".



NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____

Circle 146 on reader's service card

MONEY BACK GUARANTEE

TRIAC

6 amp	PRV	Sale	PRV	Sale
	<input type="checkbox"/> 100	1.45	<input type="checkbox"/> 400	2.75
	<input type="checkbox"/> 200	1.95	<input type="checkbox"/> 500	3.15
	<input type="checkbox"/> 300	2.25	<input type="checkbox"/> 600	3.50
	<input type="checkbox"/> 50	1.00		

Sale—"TEXAS" INTEGRATED CIRCUITS TO89 ADAPTER WITH DATA SHEETS

15 846 FLAT PACK

- SR Clocked Flip Flops 88¢
- 7360 Quadruple 2-input NAND/NOR Gate
- 15833 Dual 4-input Expander
- 15846 Quadruple 2-input NAND Gate
- 7430 8-input Positive NAND Gate
- 7450 Dual EXCLUSIVE-OR Gate with Expander inputs
- 7470 Single-phase J-K Flip-flop
- 7370 Dual EXCLUSIVE-OR Gate
- 15832 Dual 4-input Expandable Buffer
- 15830 Dual 4-input Expandable NAND Gate
- 7474 dual, D-type, edge-triggered flip-flop
- 7453 Quad AND/OR Invert
- SN15848 Fast-rise-time J-K/R-S Flip-flop
- 7492 Divide-by-12 Counter

1. AMP 800 PRV SUBMINIATURE RECTIFIERS 5 for \$1

1 AMP SILICON RECTIFIERS

PIV	Sale	PIV	Sale	PIV	Sale
50	5¢	800	23¢	1800	99¢
100	7¢	1000	40¢	2000	1.50
200	9¢	1200	59¢	3000	1.90
400	11¢	1400	69¢	4000	2.50
600	19¢	1600	89¢		

ZENER RECTIFIERS

1 WATT 49¢
 10 WATTS 1.00

Volts	Volts	Volts	Volts
5.4	10	43	100
6.2	20	47	110
8.0	22	51	120
9.1	24	56	130
10	27	62	150
12	30	68	160
13	33	75	180
15	36	82	200
16	39	91	

1 AMP MINIATURE SILICON RECTIFIERS

Glass! Epoxies!

PIV	Sale	PIV	Sale
100	9¢	600	22¢
200	12¢	800	27¢
400	17¢	1000	39¢

- FACTORY TESTED \$1 SEMI-KON-DUCTORS**
- 2—85 WATT 2N424 PLANAR silicon, TO-53 npn \$1
 - 3—40W NPN SILICON MESA 2N1648, transistor \$1
 - 4 2N170 TRANSISTORS, by GE, npn for gen'l rf. \$1
 - 15 3 Amp RECT's, studs, silicon, to 800 V no test \$1
 - 4—2N255 POWER TRANSISTOR EQUALS. \$1
 - 10 PNP SWITCHING TRANS'RS, 2N104, no test \$1
 - 2N3088 "N" Channel FET'S Very High Input Z. \$1
 - 5 2N107 TRANS'RS, by GE, npn, pop, audio pak \$1
 - 3—2N1613 3W NPN SIL. 120 mc, by "Rheum" . . . \$1
 - 3—45 AMP POWER RECTIFIERS, stud, silicon. . . \$1
 - 5 2N706 500MW, 300MC NPN transrs, TO18 \$1
 - 10 PNP SWITCHING TRANSISTORS, no test. TO8 \$1
 - 25 TOP HAT RECTIFIERS, silicon, 750 ma, no test \$1
 - 4 BIDIRECTIONAL TRANSISTORS, 2N1641 . . . \$1
 - 10 NPN SWITCHING TRANS'RS, 2N338 no test \$1
 - 15 PNP TRANS'RS, CK722, 2N35, 107, no test \$1
 - 15 NPN TRANSISTORS, 2N35, 170, 440, no test \$1
 - 30 TRANSISTORS. rf. lf, audio osc-ifs, TO5 no test \$1

SPEAKERS 2 \$1 For PHOTO CELL \$1

8 ohms. 2 1/4" For PHOTO CELL \$1

FOR OUR "XMAS" BARGAIN CATALOG ON:

10¢ Semiconductors Poly Paks Parts

POLY PAKS

TERMS: send check, money order, include postage—avg. wt per pak 1 lb. Rated, net 30 days. CODs 25%
 P.O. BOX 942R
 SO. LYNNFIELD, MASS. 01940
 "PAK-KING" of the World

Circle 147 on reader's service card

The Model 6000 Modular Frequency Meter will measure frequencies 10 KHz to 600 MHz with .000125% accuracy. Special plug-in modules allow the instrument to be used as an audio frequency meter from 500 Hz to 20 KHz full scale and in addition to be used as a dc voltmeter (10,000 ohms/volt).

The wide variety of plug-in oscillator accessories and range modules makes the Model 6000 adaptable to a number of jobs in the field and in the laboratory. Portable, battery operated with rechargeable batteries.

Model 6000 with 601A charger, less plug-in modules.....\$195.00

INTERNATIONAL MODEL 6000 FREQUENCY METER

measures frequencies 10 khz to 600 mhz with accuracy as close as .000125%




Range Modules (Mixers)
\$25.00 to \$45.00 each

Oscillator Modules
(Crystal Controlled For
Frequency Measurement)
\$30.00 to \$90.00 each

Special Modules
Audio Frequency\$45.00
DC Voltmeter..... 25.00



where accuracy counts!

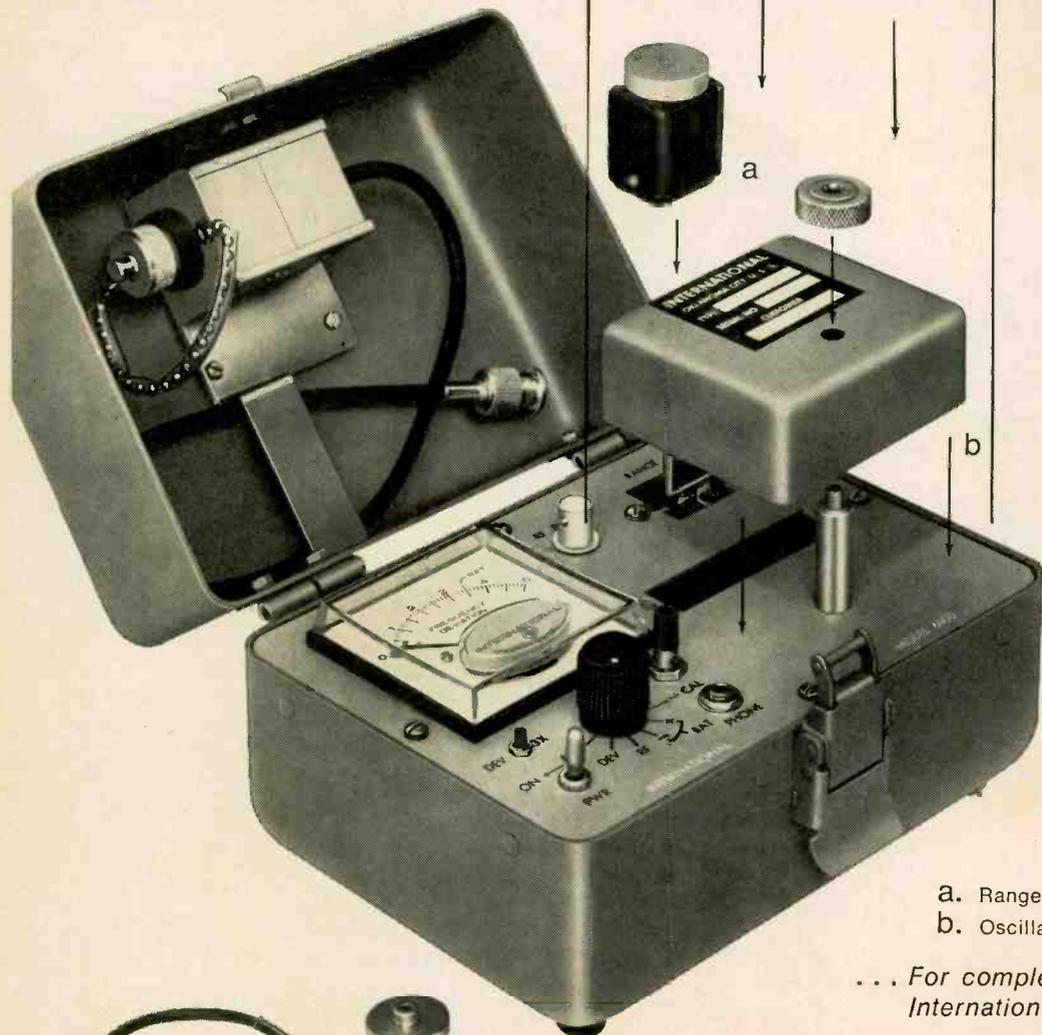

- a. Range Modules
- b. Oscillator Modules

... For complete information write International today.



Circle 148 on reader's service card

EICO Makes It Possible

Uncompromising engineering—for value does it!
You save up to 50% with Eico Kits and Wired Equipment.



Cortina Stereo

Engineering excellence, 100% capability, striking esthetics, the industry's only **TOTAL PERFORMANCE STEREO** at lowest cost.

A Silicon Solid-State 70 Watt Stereo Amplifier for \$89.95 kit, \$129.95 wired, including cabinet. Cortina 3070.

A Solid-State FM Stereo Tuner for \$89.95 kit, \$129.95 wired, including cabinet. Cortina 3200.

A 70-Watt Solid-State FM Stereo Receiver for \$159.95 kit, \$239.95 wired, including cabinet. Cortina 3570.



Eicocraft

The newest excitement in kits. 100% solid-state and professional. Fun to build and use. Expandable, interconnectable. Great as "jiffy" projects and as introductions to electronics. No technical experience needed. Finest parts, pre-drilled etched printed circuit boards, step-by-step instructions.



Electronic Siren \$4.95, Burglar Alarm \$6.95, Fire Alarm \$6.95, Intercom \$3.95, Audio Power Amplifier \$4.95, Metronome \$3.95, Tremolo \$8.95, Light Flasher \$3.95, Electronic "Mystifier" \$4.95, Photo Cell Nite Lite \$4.95, Power Supply \$7.95, Code Oscillator \$2.50, FM Wireless Mike \$9.95, AM Wireless Mike \$9.95, Electronic VOX \$7.95, FM Radio \$9.95, AM Radio \$7.95, Electronic Bongos \$7.95.



Citizen's Band

Two years ahead! Model 7923
All Solid-State 23-Channel 5W Transceiver, 4 exclusives: dual-crystal lattice filter for razor-sharp selectivity; efficient up-converter frequency synthesizer for advanced stability; precision series-mode fundamental crystals; Small: only 3"H, 8"W, 8¼"D. \$189.95 wired only.
The best buy in tube-type CB—"Sentinel-Pro" 23-channel dual conversion 5W Transceiver \$169.95 wired only.



EICO Trans/Match (Model 715) is a professional test set designed for complete checking of ham and CB equipment. Kit \$34.95; Wired \$49.95.

Truvohm

Professional Portable Multimeters by EICO. The industry's greatest V-O-M values. Designed, made to Eico's high standards of professionalism. Each complete with batteries & test leads. Backed 100% by famous EICO warranty.

- Model 100A4, 100,000Ω/V, \$34.95.
- Model 30A4, 30,000Ω/V, \$19.95.
- Model 30A3, 30,000Ω/V, \$15.95.
- Model 20A3, 20,000Ω/V, \$12.95.
- Model 4A3, 4000Ω/V, \$8.95.
- Model 1A1, 1000Ω/V, \$5.95.




Automotive

EICO 888—Car/Boat Engine Analyzer. For all 6V/12V systems; 4, 6, 8-cyl. engines.

Now you can keep your car or boat engine in tip-top shape with this solid-state, portable, self-powered universal engine analyzer. Completely tests your total ignition/electrical system.

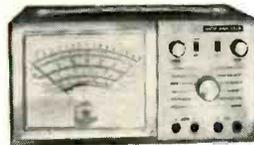Complete with a Tune-up & Trouble-shooting Manual. Model 888; \$44.95 kit, \$69.95 wired.



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7 non-skip ranges on all 4 functions. With exclusive Uni-Probe.® \$29.95 kit, \$49.95 wired.

Test Equipment **EICO**

100 best buys to choose from.

"The Professionals"
—laboratory precision at lowest cost.

Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. \$109.95 kit, \$149.95 wired.

FREE 1968 CATALOG

EICO Electronic Instrument Co., Inc.
131-01 39th Ave., Flushing, N.Y. 11352 RE-11
 Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer.

Name _____
Address _____
City _____
State _____ Zip _____

Circle 149 on reader's service card

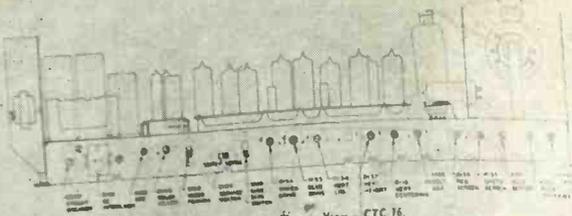


Fig. 1 - Rear Chassis View - CTC 16



Fig. 2 - Rear Chassis View - CTC 16X

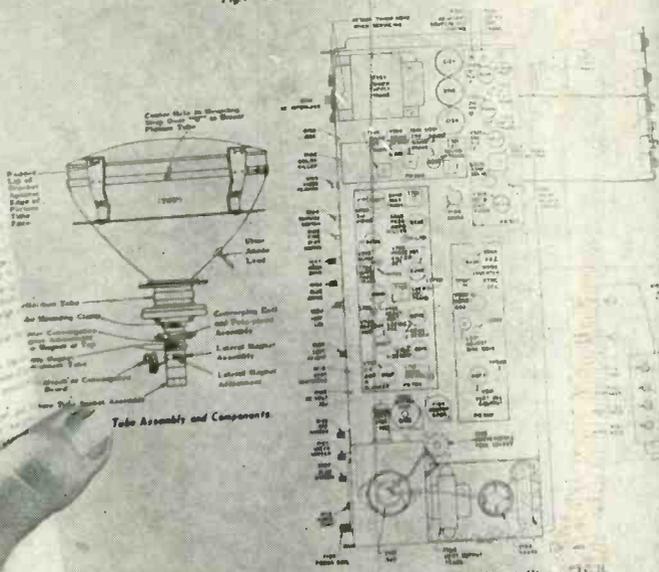


Fig. 4 - Top Chassis View - CTC 16


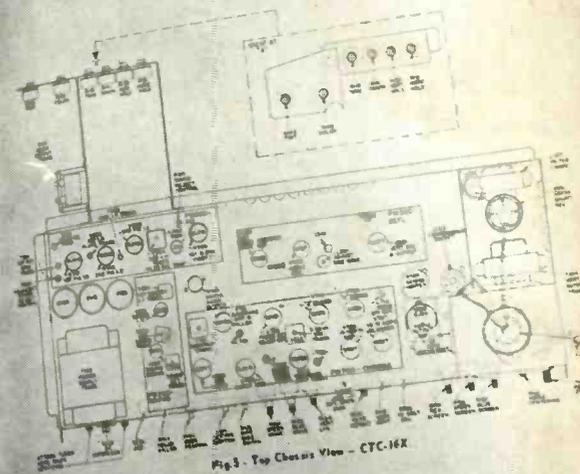


Fig. 3 - Top Chassis View - CTC 16X

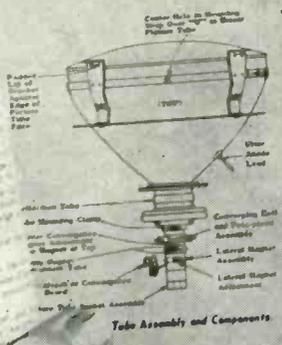

Tube Assembly and Components

You need this guide for RCA Color Home Service Calls!

RCA'S NEW FIELD SERVICE GUIDE, ERT-200 helps you make all adjustments on all RCA color sets from 1955 to 1966 that can be performed in the home ... including step-by-step procedure for replacing a color picture tube.

Three part index lets you look up the set you are working on by model number, name or chassis number. You'll find the ERT-200 Field Service Guide indispensable. There's nothing like it on house calls for RCA color sets.

WHAT THIS GUIDE CONTAINS:

- Schematics on all RCA color sets from 1955 to 1966
- Field service adjustments (AGC, linearity, centering, etc.)
- Convergence, purity and black and white setup adjustments
- Parts lists
- Wave forms keyed to test points for majority of chassis
- Top and rear chassis views
- Photos of typical receivers
- Index of models from CTC2 through CTC20
- Separate section on tuner schematics
- Separate section on remote tuner schematics


See your RCA Tube Distributor today and arrange to get your copy.



FIELD-SERVICE GUIDE

RCA COLOR-TV RECEIVERS

1955-1966

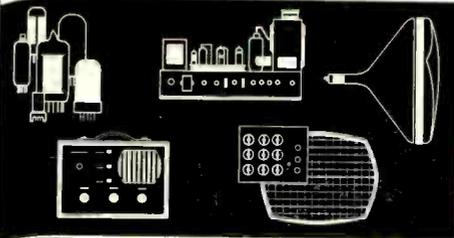

FEATURES:

- Field Service Adjustments - CTC 20 through CTC 20A
- Top and Rear Chassis Views
- Schematic Diagram
- Vacuum Tube Voltmeter Test Points
- Emergency Section on Power Substitution
- Parts Lists
- Comprehensive Index of Model Number, Model Name and Chassis Number

RCA Electronic Components and Devices, Harrison, N.J. 07029



The Most Trusted Name in Electronics