

Radio-Electronics®

TELEVISION • SERVICING • HIGH FIDELITY


A GERNSBACH PUBLICATION

Troubleshoot Color TV



Scrap Up Pay Action

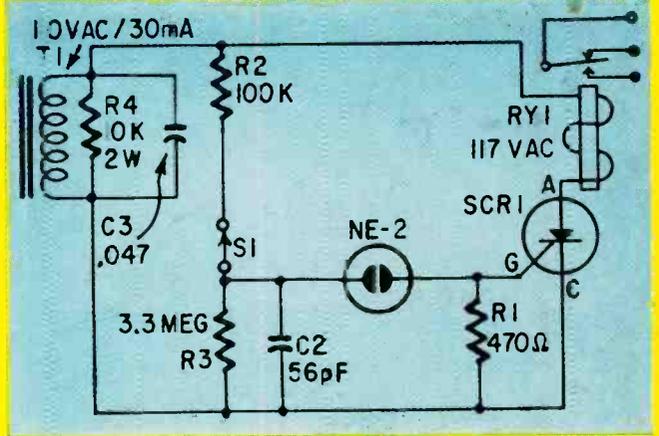
A0768 510076BLU022000A57
A L BALUKA
220 DOWNING DR
FLORISSANT MO 63031



BUILD —


Automatic Windshield Wiper-Pause Controller

(see page 32)

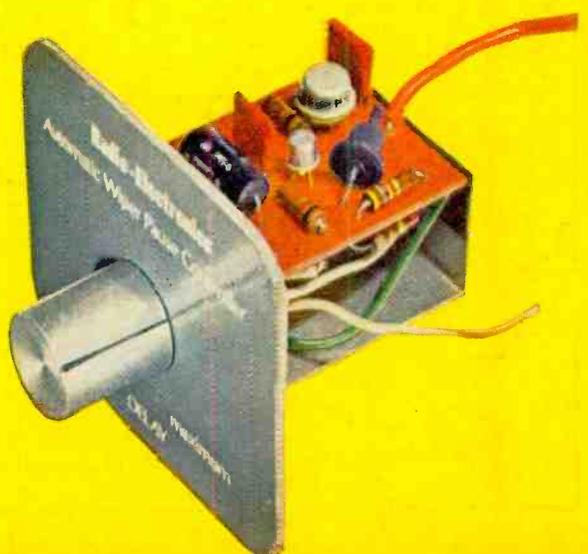

EICO Makes It Possible

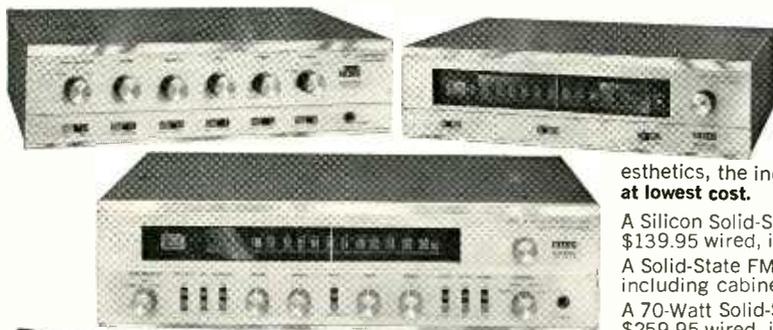Uncompromising engineering—for value does it!
You save up to 50% with Eico Kits and Wired Equipment.



Cortina Stereo

Engineering excellence, 100% capability, striking aesthetics, the industry's only **TOTAL PERFORMANCE STEREO** at lowest cost.

A Silicon Solid-State 70 Watt Stereo Amplifier for \$99.95 kit, \$139.95 wired, including cabinet. Cortina 3070.

A Solid-State FM Stereo Tuner for \$99.95 kit, \$139.95 wired, including cabinet. Cortina 3200.

A 70-Watt Solid-State FM Stereo Receiver for \$169.95 kit, \$259.95 wired, including cabinet. Cortina 3570.



Eicocraft

The newest excitement in kits.

100% solid-state and professional. Fun to build and use. Expandable, interconnectable. Great as "jiffy" projects and as introductions to electronics. No technical experience needed. Finest parts, pre-drilled etched printed circuit boards, step-by-step instructions.



Electronic Siren \$4.95, Burglar Alarm \$6.95, Fire Alarm \$6.95, Intercom \$3.95, Audio Power Amplifier \$4.95, Metronome \$3.95, Tremolo \$8.95, Light Flasher \$3.95, Electronic "Mystifier" \$4.95, Photo Cell Nite Lite \$4.95, Power Supply \$7.95, Code Oscillator \$2.50, FM Wireless Mike \$9.95, AM Wireless Mike \$9.95, Electronic VOX \$7.95, FM Radio \$9.95, AM Radio \$7.95, Electronic Bongos \$7.95.



Citizen's Band

Two years ahead! Model 7923
All Solid-State 23-Channel 5W Transceiver. 4 exclusives: dual-crystal lattice filter for razor-sharp selectivity; efficient up-converter frequency synthesizer for advanced stability; precision series-mode fundamental crystals; Small: only 3"H, 8"W, 8¼"D. \$189.95 wired only.

The best buy in tube-type CB—"Sentinel-Pro" 23-channel dual conversion 5W Transceiver \$169.95 wired only.

EICO Trans/Match (Model 715) is a professional test set designed for complete checking of ham and CB equipment. Kit \$34.95; Wired \$49.95.



Truvohm

Professional Portable Multimeters by EICO.

The industry's greatest V-O-M values. Designed, made to Eico's high standards of professionalism. Each complete with batteries & test leads. Backed 100% by famous EICO warranty.

- Model 100A4, 100,000Ω/V, \$34.95.
- Model 30A4, 30,000Ω/V, \$19.95.
- Model 30A3, 30,000Ω/V, \$15.95.
- Model 20A3, 20,000Ω/V, \$12.95.
- Model 4A3, 4000Ω/V, \$9.95.
- Model 1A1, 1000Ω/V, \$5.95.



Automotive

EICO 888—Car/Boat Engine Analyzer.

For all 6V/12V systems; 4, 6, 8-cyl. engines.

Now you can keep your car or boat engine in tip-top shape with this solid-state, portable, self-powered universal engine analyzer. Completely tests your total ignition/electrical system.

Complete with a Tune-up & Trouble-shooting Manual. Model 888; \$44.95 kit, \$69.95 wired.



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7 non-skip ranges on all 4 functions. With exclusive Uni-Probe.® \$29.95 kit, \$49.95 wired.

Test Equipment

100 best buys to choose from.

"The Professionals"
—laboratory precision at lowest cost.

Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. \$109.95 kit, \$149.95 wired.

FREE 1968 CATALOG



RE-7

EICO Electronic Instrument Co., Inc.
283 Malta Street, Brooklyn, N.Y. 11207
 Send me FREE catalog describing the full EICO line of 200 best buys, and name of nearest dealer

Name _____
Address _____
City _____
State _____ Zip _____

Circle 7 on reader's service card

www.americanradiohistory.com

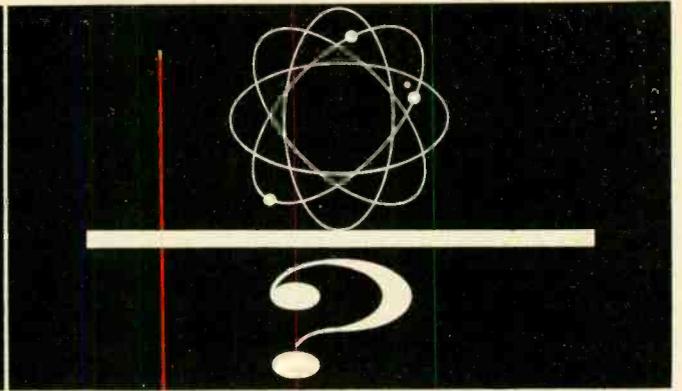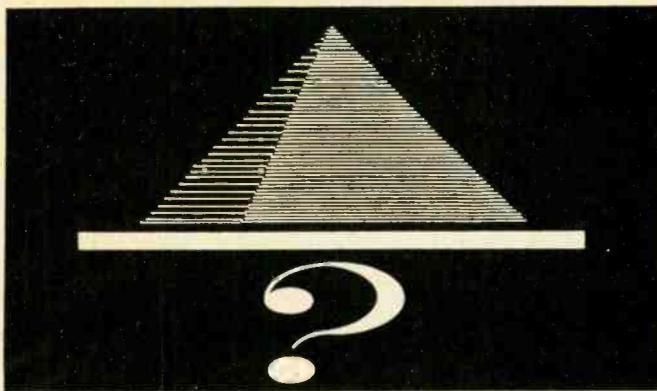

WHAT IS THE COMMON DENOMINATOR OF
 AN ANCIENT EGYPTIAN PYRAMID AND
 ▲ A MODERN ELECTRONICS CAREER?
A STRONG FOUNDATION!

The ancient pyramids were built on strong foundations and thus have endured extensive changes in their environment. How about your electronics career? Is it built on a solid foundation of knowledge and understanding? Can the foundation under your electronics career endure the rapid changes now occurring in the electronics industry?

Grantham's strong-foundation educational program in electronics engineering technology leads to non-obsolescent skills — to skills which are based more on reasoning than on merely doing — and leads to the Degree of *Associate in Science* in Electronics Engineering. As many as five of the six semesters in the educational program can be completed by *correspondence*. And technicians who have had at least one full year of practical experience may obtain credit for the resident semester, thus qualifying for the ASEE degree in only five semesters, all by correspondence.

Earn Your FCC License & Associate Degree

You have heard and read, over and over again, about how important an FCC license is to your success in electronics. It is certainly true that an FCC license is important — sometimes essential — but it's not enough! Without further education, you can't make it to the top. Get your FCC license without fail, but don't stop there. To prepare for the best jobs, continue your electronics education and get your degree.

This kind of thinking makes good common sense to those who want to make more money in electronics. It also makes good common sense to prepare for your FCC license with the School that gives degree credit for your license training — and with the School that can then take you from the FCC license level to the DEGREE level. (The first two semesters of the six-semester Grantham degree curriculum prepare you for the first class FCC license and radar endorsement.)

Grantham School of Electronics

1505 N. Western Ave. 818 18th Street, N.W.
 Hollywood, Calif. 90027 or Washington, D.C. 20006
 Telephone: Telephone:
 (213) 469-7878 (202) 298-7460

Accreditation, and G.I. Bill Approval

Grantham School of Electronics is *accredited* by the Accrediting Commission of NHSC, and is *approved* under the G.I. Bill. For seventeen years, Grantham has been preparing men for successful electronics careers.

A Four-Step Program to Success

It's your move, and the move you make today can shape your future. Begin now with a step in the right direction — Step #1 — and then follow through with Steps #2, #3, and #4.

Step #1 is a simple request for full information on the Grantham Associate Degree Program in Electronics. You take this step by filling out and mailing the coupon shown below. We'll send full information by return *mail*. No salesman will call.

Step #2 is earning your FCC first class radiotelephone LICENSE and radar endorsement. You complete this step in the first two semesters of the Grantham educational program.

Step #3 is earning your ASEE DEGREE. This degree is conferred when you have earned credit for all six semesters of the Grantham curriculum.

Step #4 is getting a better job, greater prestige, higher pay on the basis of your extensive knowledge of electronics.

It's your move! Why not begin with Step #1.

Grantham School of Electronics RE 7-68
 1505 N. Western Ave., Hollywood, Calif. 90027

Please mail me your free catalog, which explains how Grantham training can prepare me for my FCC License and Associate Degree in electronics. I understand no salesman will call.

Name _____ Age _____
 Address _____
 City _____ State _____ Zip _____

Circle 8 on reader's service card

LOOKING AHEAD

By DAVID LACHENBRUCH

"Newspaper of the air"

The concept of a non-facsimile TV "newspaper" is under investigation by the "Future of TV" Committee of the National Association of Broadcasters, it has been revealed by John F. Dille, Jr., chairman of the committee. In place of the print-out device required by home fax, the "electronic newspaper" system would have a memory circuit housed in the TV set or alongside it. The newspaper would be transmitted continuously in TV frames rather than pages. The viewer, at his convenience, would turn on his set and press the "index" button. An index frame would appear on his TV screen, outlining what had been transmitted that day. Then the reviewer would press the appropriate button for whatever he wished to read—news, sports, comics, obituaries—and the proper frame would appear on the screen.

Electronic contraceptive

The intra-uterine device, or IUD has been widely hailed as the best hope for population control in underdeveloped countries. It's a small mechanical device which prevents conception when properly inserted in the uterus. RCA recently was granted a patent on an electronic IUD which helps overcome some shortcomings of the mechanical version—possible insertion, displacement or loss. The RCA patent covers a tiny oscillator built into the IUD, which gives off signals when under test by an electromagnetic instrument—one type of signal if the device is properly placed, other types of signals if distorted or out of position. Of course, if the IUD is missing, there's no signal. To permit physicians to determine whether the IUD is correctly in place, women merely would walk past a detection instrument operated by a technician. If the proper signal is detected, everything is in order.

Airborne CATV

The semi-glamorous name "Quasi-Laser" is applied to a new system proposed to solve the problems of big-city cable television. To avoid the extremely high costs of laying underground cables to connect apartment buildings in high-density areas, the new proposal is to send the signals through the air. The plan which Chromalloy American Corp. and Laser Link Corp. are proposing to the FCC for testing in Brooklyn, N.Y., involves sending a wide band of information—12 or 20 TV channels—via the "upstairs" frequencies. These frequencies are so high that they are presently unassigned to any service and will not result in crowding the portion of the spectrum now used. The frequencies proposed are in the area of 42 GHz, below the infrared light spectrum.

A new method of modulation is claimed to make it possible to beam wide bands of information at low power from a high point for several miles in all kinds of weather. Low-cost receiving antennas on building tops would receive the signals, which would be reconverted to TV carrier frequencies. To divert signals to lower buildings not within line-of-sight to the transmitter, Laser Link would use metallic "mirrors" on high build-

ings, deflecting signals to lower ones. The "Laser Link" name is derived from the fact that frequencies being used are toward the end of the spectrum occupied by light waves.

More on X-rays

Radiation-conscious TV set manufacturers have compiled a summary of factory quality-control tests on color sets from July 1, 1967, to March 3, 1968. Of 19,225 sets tested, 11,696 were found to emit no measurable radiation; 7525 tested below 0.5 milliroentgen (mR) per hour at 5 cm. Only four showed radiation above the unofficial standard of 0.5 mR. The four were corrected before leaving the factory.

Remote without motors

A new remote-control system that will appear on some Motorola solid-state color sets this summer substitutes semiconductor devices for motors or stepping relays. The heart of the system is an encapsulated "memory module" containing a neon bulb, which acts as an electronic switch, a capacitor and an insulated gate field effect transistor (IGFET). The capacitor's charge is varied up or down in response to the direction of the control desired (for example, to increase or decrease volume), providing a continually variable control. The capacitor is capable of retaining a charge for 1000 hours or more, thereby assuring its ability to hold at any desired setting.

Although Motorola demonstrated the system with volume control only, its color remote unit is expected to have three infinitely variable non-motorized controls, plus such conventionally activated functions as channel change (still motorized) and off-on. Elimination of the mechanical channel selection function presumably must await the widely anticipated arrival of variable-capacitance diode tuning for the American 82-channel TV system.

Cassette-leggers?

The zooming popularity of the easy-to-operate cassette recorder has some of the record companies worried. What concerns them is the danger of a roll-your-own trend, as consumers begin to make their own recordings from the radio. RCA Victor Vice President Norman Racusin, who heads the Record Division, told a recent merchandisers' convention that the cassette represents the first serious threat to the recording industry. He called for legislation or changes in marketing or technology to head off massive bootlegging. There already are several brands of combination radio and cassette recorders on the market and it's believed that some major manufacturers plan to incorporate stereo cassette decks in their forthcoming phonograph consoles.

The reel-to-reel recorder never was considered a serious threat by record manufacturers because of its relatively limited market. But now they envision a possible invasion of the marketplace by tens of millions of simple, low-cost units, and you can expect a top-priority attempt to head off subrosa recording by cassetteers. R-E

Radio-Electronics

July 1968 • Over 60 Years of Electronics Publishing

FEATURE

Looking Ahead 2 David Lachenbruch
Current happenings with future overtones

CONSTRUCTION PROJECTS

Build For Your Car: Automatic Windshield-Wiper Pause Controller 32 .. S. B. Gryniewicz
It's the pause that counts

Build Rhythm Lights For Psychedelic Music . . . 34 R. T. Montan'e
Add groovy sights to today's sounds

Soup-Up Your Relays With SCR Drivers ... 36 .. Lyman E. Greenlee

20 Unijunction Transistor Applications—II . . . 38 R. M. Marston
Final on UJT's ... how they work ... and some more circuits for you to play with

Build An IC Decade Divider 55 .. Dewey W. Eppley
Math electrified with IC's

An Unusual Diode Oscillator 68 .. Irving M. Gottlieb
Relaxation circuits need not be confined to neon lamps

Build High Efficiency Lab Power Supply 80 Melvin Chan & Robert Brock
Zero to 6 amps without a ripple

Do It Yourself Language Lab 86 Byron G. Wels
A cord that speaks

SERVICING

In The Shop ... With Jack 24 Jack Darr

TV Interference Traps Simplified 46 ... Matthew Mandl
How to catch a herringbone in your trap

Color Blanking Circuits 49 Robert L. Goodman
Trace without retrace

Color TV Trouble Shooter Guide 52 Vic Bell

Service Clinic 70 Jack Darr

Equipment Report: Sony TC-230 Stereo Tape Recorder 66

GENERAL ELECTRONICS


Hall Effects In Solid 42 .. John Potter Shields
An old shoe on a new footing

Capacitors As Transducers 59 J. Merino y Coronado
Reactance counts

Signal and Voltage Indicators 83 Leo G. Sands
Eyes for your eyes


DEPARTMENTS

CB Troubleshooter's Casebook 88	New Products 75	Noteworthy Circuits 92
Correspondence 12	New Test Equipment 77	Reader's Service 72
New Audio Equipment 76	New Tubes and Semiconductors 90	Try This One 93
New Literature 78	News Briefs 6	

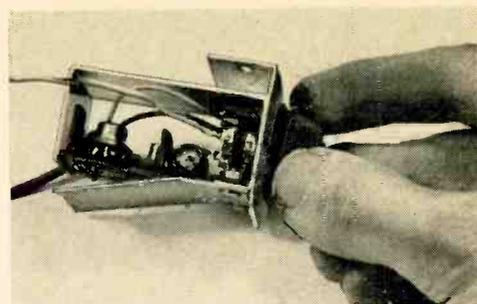


Now there's no need to reach for the windshield wiper knob every few seconds when driving through light mist or on slush-covered roads. You can set this Automatic Pause Controller to obtain any desired pause between sweeps, while the wiper still operates at normal speed.

See page 32

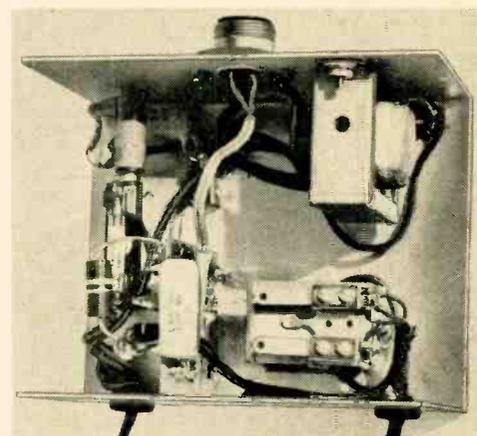

Power relays are useful in dozens of projects, but usually lack sensitivity because of heavy contacts. Find out how to soup-up relay sensitivity and trigger 30-amp jobs as little as 200 μ A.

See page 36

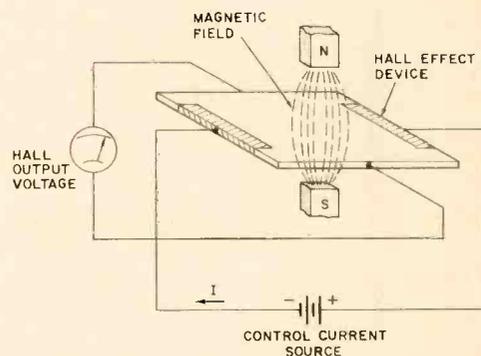

Hall-effect devices are growing in number as today's technology makes possible new uses for Hall's 19th-century discovery. Learn about this important principle, and its applications in science and industry.

See page 42


RADIO-ELECTRONICS, JULY 1968, Volume XXXIX, No. 7
 Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302.
 Editorial, Advertising, and Executive offices: 200 Park Ave. S., New York, N. Y. 10003. Subscription Service: Boulder, Colo. 80302.
 Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U. S. and possessions, Canada, \$6.
 Pan-American countries, \$7. Other countries, \$7.50. Single copies: 60c. ©1968, by Gernsback Publications, Inc. All rights reserved.
 POSTMASTER: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302




Member.
 Institute of High Fidelity.
 Radio-Electronics is indexed in
Applied Science & Technology
Index (formerly Industrial
Arts Index)



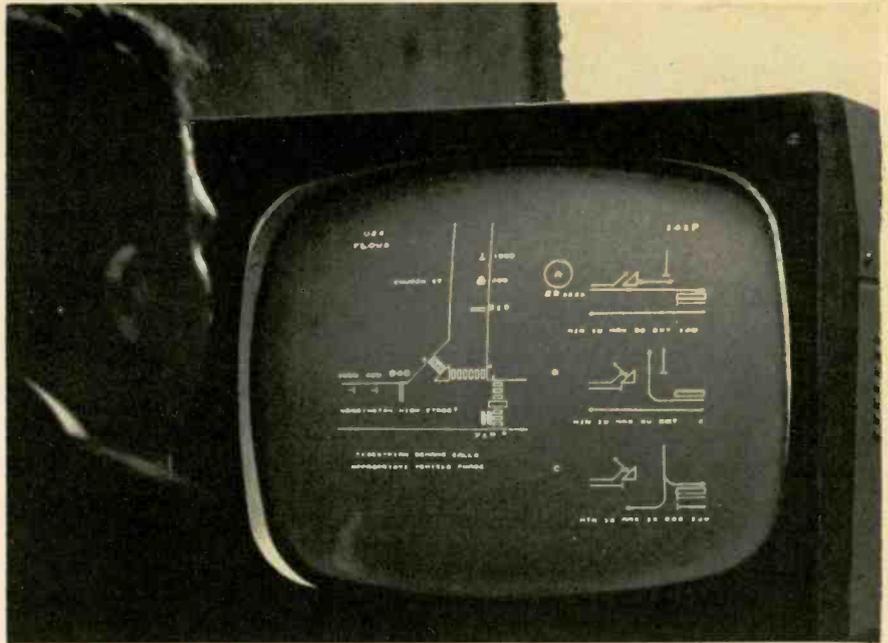Telephone uses IC's—An experimental electronic telephone recently shown by Bell Labs uses hybrid integrated circuits and a tone ringer instead of an electro-mechanical bell. Buttons for Touch-Tone dialing are behind the earpiece. Automatic voice loudness circuits in the handset are among the features in the new design.




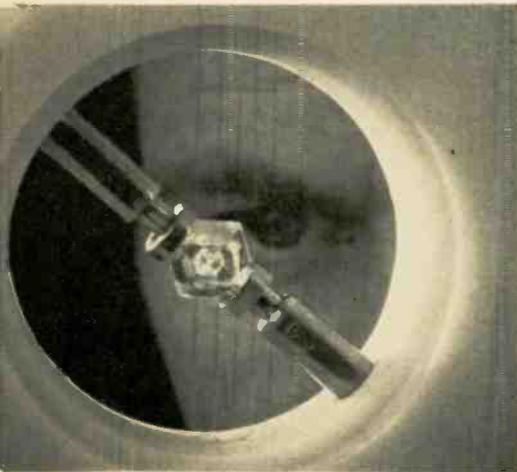Computer monitors London traffic—Street names, traffic flow, pedestrian crossings and other information are shown on this computer-controlled display system to be installed in New Scotland Yard for experimental control of traffic. Marconi Company will build and install system.



Light transducer—Light transmission through a "sandwich" of this crystal and Polaroid sheet can be varied by changing voltage applied to the crystal. The crystal (hexamethylenetetramine) is compressed for studying electro-optic and piezoelectric effects that influence light polarization. General Motors Research Labs "grew" material from original "seed" crystal.

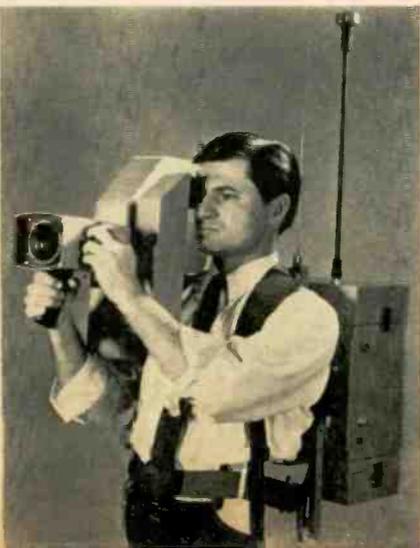
Lightweight color TV camera—An 18-lb digital-control unit has been developed by CBS Labs for coverage of 1968 presidential conventions. A base station can focus, center and provide color registration for six cameras via microwave signals at a distance of nearly 3 miles.



NEWS BRIEFS

Single-gun color TV tube—Sony's new Trinitron tube utilizes a single electron gun with three in-line cathodes. Electron beams are electrostatically converged through a vertically slitted aperture grill to vertical phosphor stripes on the screen. Sony claims tube has twice the brightness of conventional tubes. Company plans to introduce Trinitron sets to the US market in 1969.

TRINITRON COLOR TUBE

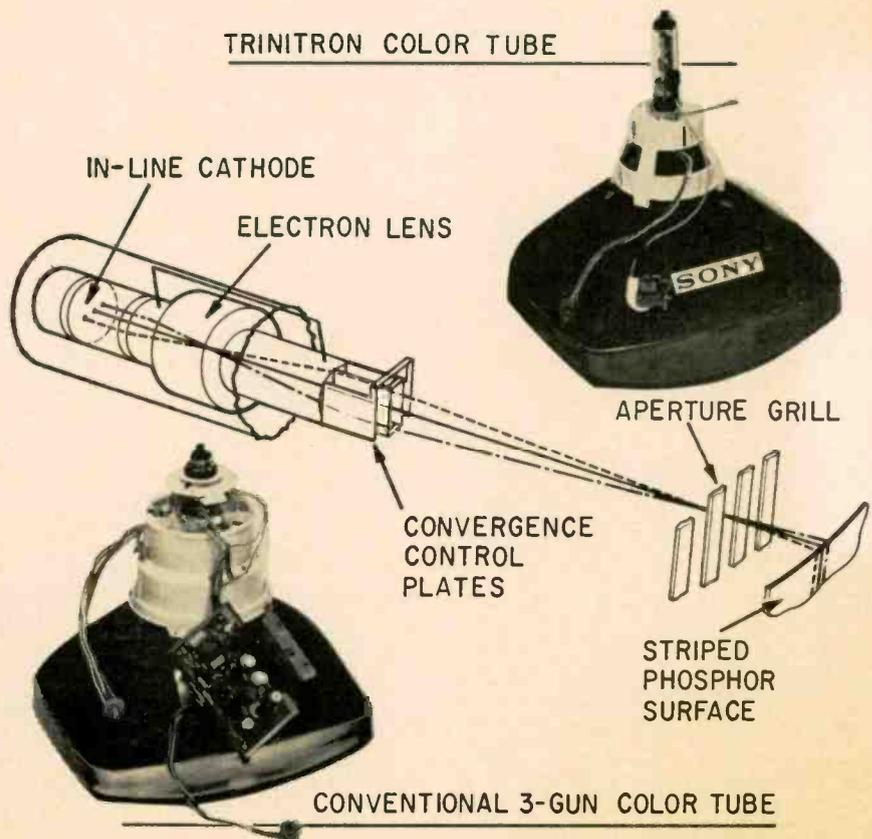

Here's a new, complete ICS course in TV Servicing that costs less than \$100.

With the first two texts, you can repair 70 percent of all TV troubles.

You need no previous experience to take this complete, practical course in TV Repairing.

You don't even have to know a vacuum tube from a resistor. Yet in a matter of months, you can be doing troubleshooting on color sets!

Course consists of 6 texts to bring you along quickly and easily. 936 pages of concise, easy-to-follow instruction, plus 329 detailed illustrations. You also receive a dictionary of TV terms geared directly to course material so you'll understand even the most technical terms. The dictionary will come in handy even after you've finished your course.


Instruction is simple, very easy to grasp. Photos show you what a TV screen looks like when everything is normal, and what it looks like when trouble fouls it up. The texts tell you how to remedy the problem, and why that remedy is best.

Quizzes are spotted throughout the texts so you

can check your progress. At the end of the course, you take a final examination. Then you get the coveted ICS® diploma, plus membership in the ICS TV Repairman Association.

By the time you've finished the course, you should be able to handle tough, multiple TV problems, on color sets as well as black and white.

This new TV Servicing and Repair Course has been approved by National Electronic Associations for use in their Apprenticeship program. Because of its completeness, practicality and price, it is the talk of the industry. The cost is less than \$100—just slightly over ½ the price of any comparable course on the market today. Remember, the sooner you get started on your course, the sooner you'll be turning your spare time into real money. Fill out the coupon today. And we will rush to you all information, no obligation.

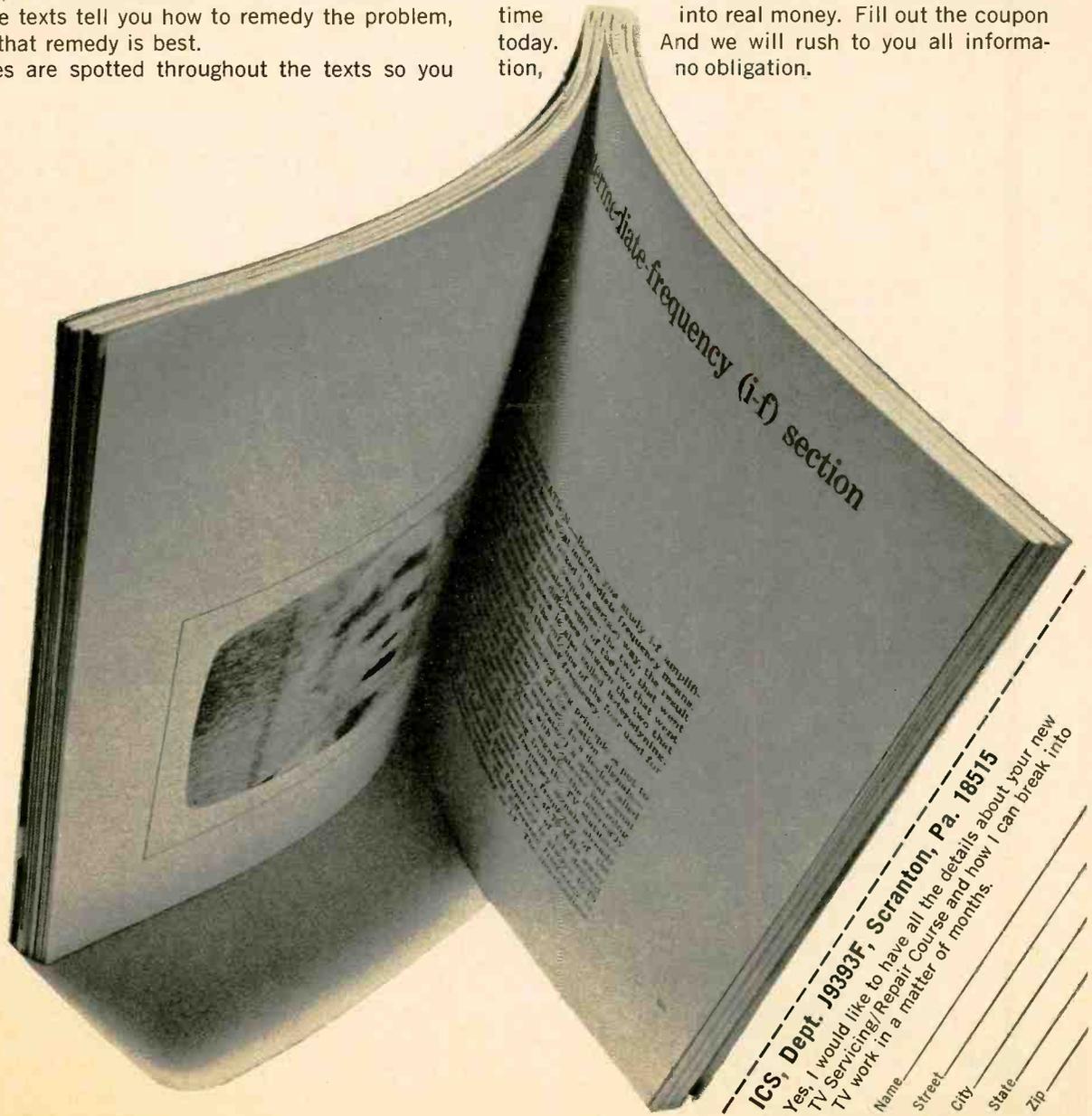

ICS, Dept. J9393F, Scranton, Pa. 18515

Yes, I would like to have all the details about your new TV Servicing/Repair Course and how I can break into TV work in a matter of months.

Name _____
Street _____
City _____
State _____
Zip _____

Circle 9 on reader's service card

One of a series of brief discussions
by Electro-Voice engineers



ADDING "HIGHS" TO HIGH POWER PA

JOHN R. GILLIOM
Chief Engineer, Loudspeakers

Sound system intelligibility can often be a complex problem since it will vary with ambient noise level and type, usable system level and response, and room reverberation. As a result, there are probably thousands of sound systems with marginal effectiveness despite more than sufficient power handling capacity to overcome the measured noise.

The reason for the failure of these systems often lies in the design of the typical high power PA driver. Most drivers rated at 50 watts or more have relatively massive voice coil and diaphragm assemblies. This sharply limits high frequency response, particularly in the 2 to 7 kc range. Since this range contributes significantly to intelligibility, the loss of highs has serious consequences under severe noise conditions.

Happily, most noise decreases in intensity with rising frequency, thus helping overcome the problem. But, if a driver with flat or rising response in the 2 to 7 kc region is used, much higher intelligibility can be assured often with a significant reduction in the amount of power needed.

To achieve this desired high frequency response, E-V PA drivers have unusually light voice coil assemblies that maintain high efficiency to 7 kc yet handle up to 60 watts of power (in the case of the model 1829). This power handling capacity has been obtained by the use of high temperature materials that maintain strength without adding to the moving mass. Careful design of the loading plug, plus the use of relatively large Indox V ceramic magnets also insures better voice penetration, even when used on conventional reentrant trumpets.

To further increase efficiency, E-V has also developed a series of compound horns that have proved unusually effective in high noise environments. Each side of the driver diaphragm is coupled to a separate horn. The highs (above 1 kc) are propagated from a short horn mounted coaxially with the large reentrant bass horn. This assures minimum high frequency losses due to internal reflections plus a sharp reduction in distortion at high levels.

Two such horns are available: the wide-angle FC100 (CDP*) and the concentrating AC100 for extended reach. 30, 40, and 50 watt compound drivers are offered for either type. This combination of low-mass drivers and high-efficiency horns has been found to contribute significantly to improved intelligibility under adverse noise conditions.

For reprints of other discussions in this series,
or technical data on any E-V product, write:
ELECTRO-VOICE, INC., Dept. 783E
613 Cecil St., Buchanan, Michigan 49107



Circle 10 on reader's service card

NEWS BRIEFS

MAGNETIC POLLUTION

If you think you've got problems with air and water pollution, pity the scientists at the National Bureau of Standards. They've been forced from a Washington, D.C., lab site by magnetic pollution. To make precise volt and ampere determinations and conduct other sensitive tests, NBS needs a magnetically "clean" environment. Growing interference in Washington from new buildings with high iron and steel content and from more automobiles in the area made a move to Maryland necessary. The new lab site is in a uniform earth's field, and is constructed with magnetically "transparent" materials.

SOLID-STATE

HIGH-VOLTAGE RECTIFIERS

A color TV set with solid-state circuitry throughout will be introduced by Motorola this summer. The only vacuum tube in the company's Quasar line will be replaced with a solid-state high voltage rectifier. Existing Quasar models can be updated with a high-voltage module. Other 1969 models will also use the solid-state rectifier.

ELECTRICAL PLUG STANDARDS SET

Uniform standards for electrical plugs and receptacles have been established by the National Electrical Manufacturers Association. The new configuration makes it impossible, for example, to plug a 125-volt device into a 250-volt receptacle or a 30-amp load into a line rated at 15 amperes.

DIAMOND HEAT SINKS

Experiments at Bell Labs show that diamonds are also a semiconductor's best friend. Engineers have found that certain diamonds displace more heat than copper when used as heat sinks. Consequently, a silicon diode on a diamond chip will handle about four times more power. Low-cost, 1/10-carat industrial diamonds are used.

FUTURE TELEPHONE SIGNALS

Your telephone conversations will be chopped into 8000 or more coded digital pulses when the telephone industry adopts the pulse code modulation technique, according to General Telephone & Electronics. A carrier system using the technique has been developed by the company. Speech signals are converted into coded pulses for transmission over telephone lines. A detector at the receiver end recovers the original voice conversation. Greatly improved fidelity and efficiency are claimed over the present method of transmission over lines. **R-E**

Radio-Electronics

200 PARK AVE. SOUTH
NEW YORK, N. Y. 10003
HUGO GERNSBACK (1884-1967)
founder

M. HARVEY GERNSBACK, publisher
ROBERT CORNELL, editor
Robert F. Scott, W2PWC, senior editor
John R. Free, associate editor
Jack Darr, service editor
I. Queen, editorial associate
Matthew Mandl, contributing editor
David Lachenbruch, contributing editor
Linda Albers, assistant to editor
Wm. Lyon McLaughlin,
technical illustration director
Bruce Ward, production manager
Sandra Esteves, production assistant
G. Aliquo, circulation manager

Cover by Harry Schlack

RADIO-ELECTRONICS is published by
Gernsback Publications, Inc.
President: M. Harvey Gernsback
Vice President-Secretary: G. Aliquo

ADVERTISING REPRESENTATIVES

EAST

John J. Lamson,
RADIO-ELECTRONICS, 200 Park Ave. South
New York, N. Y. 10003, 212-777-6400

MIDWEST/N.S. Car., Ga., Tenn.

Robert Pattis, the Bill Pattis Co., 4761 West
Touhy Ave., Lincolnwood, Ill. 60646,
312-679-1100

W. COAST/Texas/Arkansas/Oklahoma

J. E. Publishers Representative Co., 8380
Melrose Ave., Los Angeles, Calif. 90069,
213-653-5841; 420 Market St., San Francisco,
Calif. 94111, 415-981-4527

UNITED KINGDOM

Publishing & Distributing Co., Ltd., Mitre
House, 177 Regent St., London W.1, England

SUBSCRIPTION SERVICE: Send all subscription correspondence and orders to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302. For change of address, allow six weeks, furnishing both the old and new addresses and if possible enclosing label from a recent issue.

MOVING? Or writing about subscription? Be sure to fill out form below.

For FASTEST service on address change, missing copies, etc., attach old mailing label in first space below. Otherwise please print clearly your address as we now have it.

OLD ADDRESS (Attach old label if available)

Name

Address

City State

Zip Code

NEW ADDRESS

Name

Address


City State

Zip Code

Mail to: RADIO-ELECTRONICS
Subscription Dept. Boulder, Colo. 80302

Circle 11 on reader's service card →

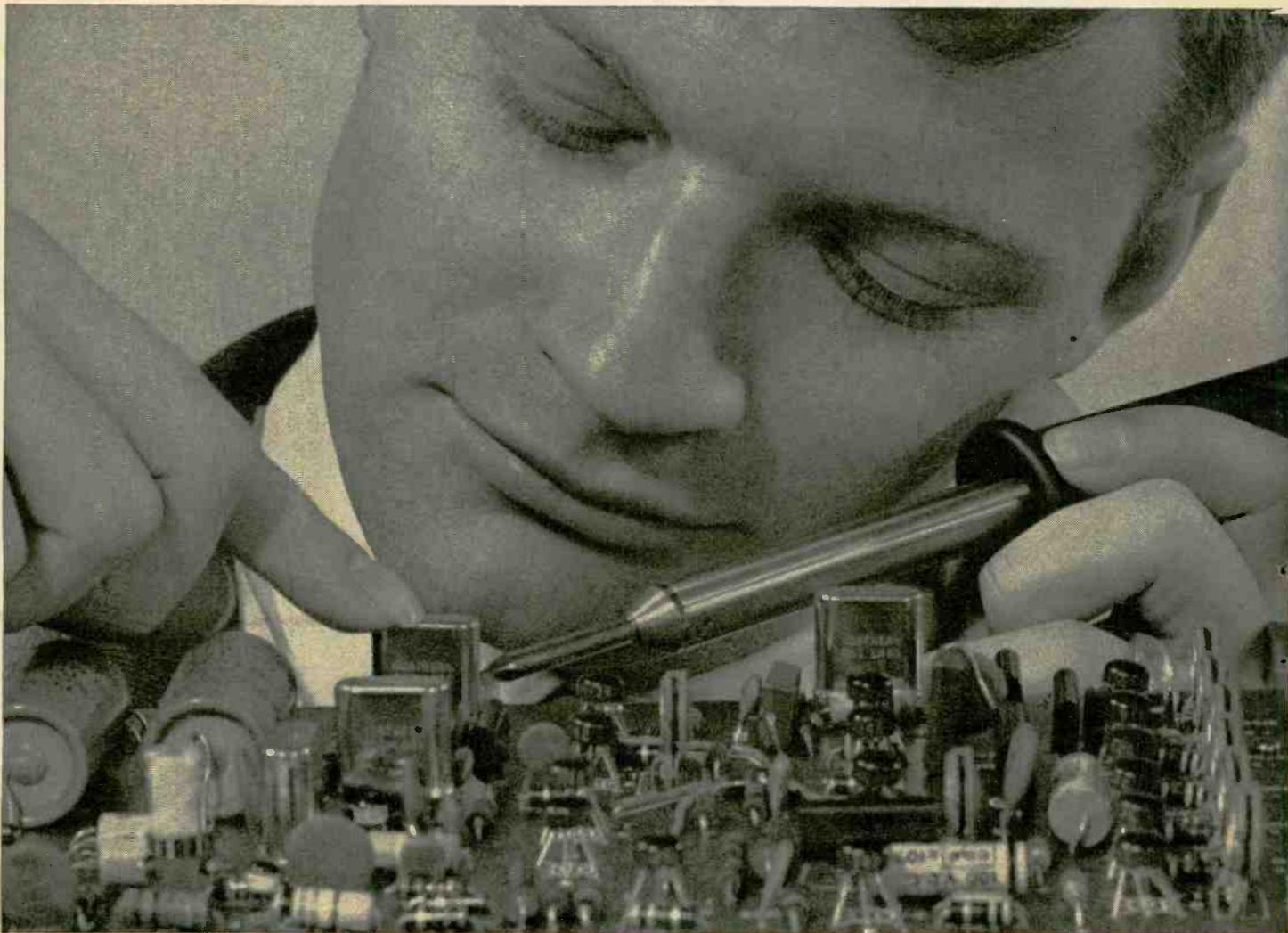**NRI “hands-on” training
in communications
can give you as much as
2 years of on-the-job
experience.**



EARN YOUR FCC LICENSE – OR YOUR MONEY BACK

NRI Communications training programs will qualify you for a First Class Commercial Radiotelephone License issued by the FCC. If you fail to pass the FCC examinations for this license after successfully completing an NRI Communications course we will, on request, refund in full the tuition you have paid. This agreement is valid for the period of your active student membership and *for six months* after completion of your training. No school offers a more liberal FCC License agreement.

Experience is still your best teacher

*...here's how you get it with
unique NRI training at home*

Ask any teacher, job counselor, engineer, technician or prospective employer about the need for practical application of theory in Electronics. He'll tell you Electronics is as much a "hands-on" profession as dentistry or chemistry. That's how you learn at home with NRI. You prove the theory you read in "bite-size" texts, by actual experimentation with the type of solid-state, transistor and tube circuits you'll find on the job today — *not* hardware or hobby kits. You introduce circuit defects, analyze results, discover quickly the kind of trouble-shooting and design techniques that will make you employable in Electronics.

Train with the leader — NRI

NRI lab equipment is designed from chassis up for effective, fascinating training — not for entertainment. The fact that end results are usable, quality products is a bonus. In Communications, for example, you build and analyze, stage by stage, your own 25-watt phone/cw transmitter. It's suitable for use on the 80-meter amateur band, if you have an interest in ham radio. In TV-Radio Servicing your practical training gives you your choice of monochrome or color TV sets. All training equipment is included in the low tuition — you pay nothing extra. Discover for yourself the ease, excitement and *value* of NRI training. Mail postage-free card today for new NRI Catalog . . . or use the coupon below. No obligation. No salesman will call on you. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.

APPROVED UNDER NEW GI BILL

If you have served since January 31, 1955, or are in service now, check GI line on postage-free card or in coupon.

MAIL THIS COUPON IF CARD IS GONE



NATIONAL RADIO INSTITUTE

Washington, D.C. 20016

Please send me your new NRI Catalog. I understand no salesman will call and there is no obligation.


Name _____ Age _____

Address _____


City _____ State _____ Zip _____

Check for facts on new GI Bill

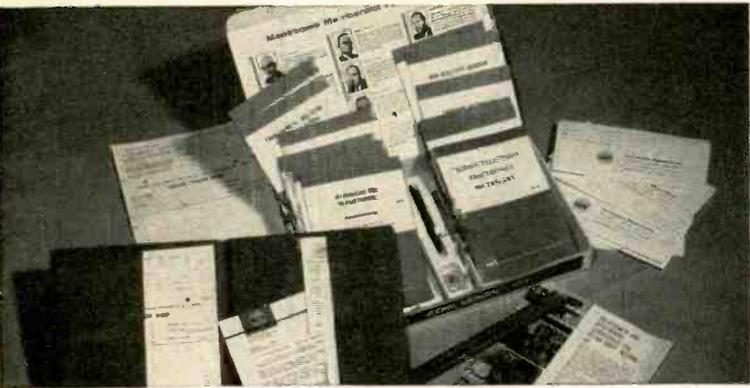ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL



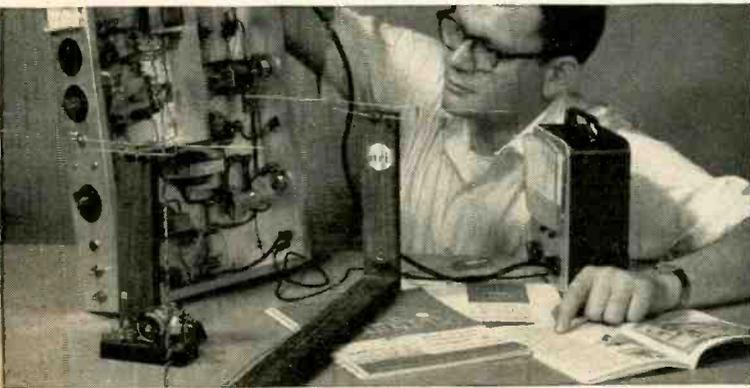NRI Achievement Kit is educator-acclaimed and the original "starter" kit in home study training. Imitated but never duplicated, this kit is designed and personalized for you and your training objective. It has one purpose — to get you started quickly and easily.



"Bite-Size" Texts average an easily-digested 40 pages of well-illustrated, scientifically prepared subject matter in the course of your choice. Questions in each book are carefully hand-graded and returned to you with helpful instructional notes. You get unlimited personal help from the day you enroll.

Designed-For-Learning Equipment

Like this phone-cw transmitter (Kit #7 in the Communications course) is engineered from chassis up to demonstrate principles you must know. NRI does not use modified hobby kits for training, but the finest parts money can buy, professionally and educationally applied.

new Sams books

Bench Servicing Made Easy (2nd Ed.)



by Robert G. Middleton. The outstanding authority on TV servicing presents the most unique and practical approach to fast, efficient repairs. This book goes far beyond mere theory to provide you with a step-by-step guide for locating defective components in any TV circuit. Completely updated to include the latest tube and transistor circuits. This is the TV troubleshooting book

for progressive servicemen. It is practical, time-saving, invaluable; packed with the successful experience gained directly at the author's own workbench. 176 pages; 5½ x 8½". **\$3.95**
Order 20658, only.....



Advanced & Extra-Class License Handbook

by Howard S. Pyle, W7OE. Contains all the information you need to obtain the Advanced- or Extra-Class amateur radio license. Makes it easier for present holders of lower-grade licenses to prepare for the top amateur licenses. Covers: Requirements for Advanced and Extra-Class licenses; building up code speed; advanced data you'll need to know to pass the exams; includes information on power supplies, r-f oscillators, frequency multiplication and r-f amplification, the radiating system, modulation, and advanced principles of electricity, r-f, and a-f. Includes sample questions for each exam. **\$3.95**
176 pages; 5½ x 8½". Order 20649, only.....

Electrical & Electronic Signs & Symbols

by Robert G. Middleton. This remarkable book is more than a simple enumeration of the technical symbols used in electricity and electronics. While it describes and explains basic signs and symbols used in schematics, abstract diagrams, graphs, mathematical formulas, etc., it goes further, explaining how symbols are constructed, how they are used to convey meaning, and how they relate to what they symbolize. Also covers dimensional analysis, machine or computer logic, and analogies. **\$3.95**
160 pages; 5½ x 8½". Order 20633, only.....

INSTRUMENTATION TRAINING COURSE


Vol. 1. Pneumatic Instruments

Edited by the Howard W. Sams Technical Staff. Covers theory, construction, alignment, installation, and operation of many types of pneumatic control instruments. Explains the basic principles of link/lever mechanisms, pressure sensitive devices, liquid level measurement, and flow measurement. Describes self-balancing instruments and explains the variations of moment-balance and free-balance mechanisms. Describes pressure control using controllers with proportional action, and reset and derivative modes. Examines in detail typical examples of control instruments. Invaluable for instrument training programs; a handy reference for all who are involved with industrial controls. **\$8.95**
192 pages. 8½ x 11". Order 20621, only.....

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.
4300 WEST 82nd ST. • INDIANAPOLIS, INDIANA 46268

Circle 14 on reader's service card

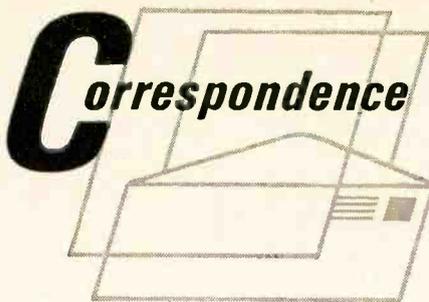

Correspondence

enjoyed the article on the IC audio amplifier and would like to see more articles of this kind.

ROBERT H. KLAPHEKE
Louisville, Ky.

Write to Break-In, Box 1733, Christchurch, New Zealand, and they'll fill you in.

AC/DC CALIBRATOR IS NOT A POWER SUPPLY

I built the "Ac/Dc Calibrator for Scope and Voltmeter" by Peter E. Sutheim (February 1968) and it works very well. I do get a flicker on the neon bulb sometimes on dc—is that normal? It occurred to me that the calibrator might be used to power a 10-volt transistor radio, etc. with low current drain if a suitable filter could be added. Is this practical? If so, could you send me a sketch of a filter with part values?

JAMES R. SNYDER
Red Bank, N. J.

Flickering is a pretty common phenomenon in neon lamps. It shouldn't make any difference to the calibrator's operation unless the terminal voltage changes substantially during the flickering. You can power a transistor radio from the calibrator. The 10-volt terminal won't do, because the drain of a typical transistor radio (around 10 mA) would drag the voltage down to 7 or lower.

You can power the radio from the 100-volt terminal by using a dropping resistor of about 10,000 ohms, 2 watts in series between the terminal and the red (positive) battery lead of the radio. Between the two radio battery leads, connect an electrolytic capacitor of 100 to 500 µF, 15 volts. This should work nicely, but never disconnect the radio with the calibrator turned on. If you do, the load will be removed and the voltage across the added electrolytic will rise to 100 volts and destroy it.

To be completely safe, you would have to use a 100-µF, 150-volt capacitor across the battery leads, which is large and expensive. It can be done, but it's probably more satisfactory to build a simple little unregulated power supply for a few bucks.

ZENER WATTAGE

As a military instructor who on occasion teaches semiconductors, I must challenge the statement appearing in your article, "Update Your Solid-State TV Servicing," by Matthew Mandl (February 1968). It says: "The replacement [Zener diode] can

(continued on page 14)

IN THE SOUP WITH BLACK NOISE

The article, "Testing With Black Noise" by Peter E. Sutheim (April 1968), reminds me of a similar device which I developed in collaboration with my classmate, Sarkes Tarzian, while we were undergraduates at the University of Pennsylvania in 1923. We found that the tin coating on the soup can was too thin to form an effective Faraday shield . . . we had to enclose it in a piece of heavy aluminum foil with the edges gathered together to form a sack, fastened around the cable with a spring clothespin. Unfortunately, I can't seem to remember the purpose of our device. In those days, we had neither white or black noise, only purple noise.

RALPH A. KRAUSS
Philadelphia, Pa.

Thanks for your suggestion on improving Sutheim's methods. The diagram specified a black bean soup can. If you are substituting parts you may run into the trouble you mentioned. The device can also be used to test purple noise, with suitable filters, but nowadays there is very little need for this.

FIRE DETECTOR

I would like to see your magazine publish an article on fire-detection systems for buildings. Anything in this order proposed for the future?

WILLIAM C. METLER
New Shrewsbury, N. J.

Apparently your letter and our editorial efforts crossed in the mail, William. See June 1968 for a complete write up of Heathkit's new Wireless Alarm System Kit. Their system will protect you against smoke and unauthorized entry as well as fire.

AMATEUR RADIO

The April 1968 Noteworthy Circuits has an item on FET audio band-pass filters. In this article, *Break-In*, a New Zealand magazine, was mentioned. Could you please furnish me with the address of this magazine and any other information you have. I also



HAAAAH PROOF

THE SHURE UNIDYNE IV is the newest and premier member of the famed Unidyne family of true cardioid dynamic microphones which have pickup symmetrical about microphone axis at all frequencies . . . in all planes. The Unidyne IV is so rugged that it can withstand a Karate chop. Reinforced, cushioned cartridge withstands severe impacts and vibrations . . . the diaphragm can take the full force of a leather-lunged Karate yell! Trouble-free Cannon-type connector. Exceptionally easy to service in the field. The strongest, most durable Unidyne yet! Send for all the facts: Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Ill. 60204.

Available in two models: Model 548 (hand-held), at \$100.00 list; Model 548S (with On-Off switch and swivel connector for stand use), at \$105.00 list.

Circle 13 on reader's service card

© 1968 SHURE BROTHERS, INC.

Delta Launches the COMPUTACH*



The
Great
One!

*An exclusive computer-tachometer for precise RPM measurement in easy-to-build Kit form!




ONLY
\$29.95
ppd.

Delta, pioneers in CD ignition who produced the fabulous MARK TEN®, now offer a precise computer-tachometer which obsoletes any type tachometer on the market today! You achieve unbelievable accuracy in RPM readings due to the advanced, solid-state electronic matched components used in the computer, coupled with the finest precision meter in the world. Works on all 2, 3, 4, and 6 cylinder 2 cycle and with 4-6-8 cylinder—4 cycle 12 volt engines.

- ▲ 0-8000 RPM range
- ▲ Perfect linearity — zero parallax
- ▲ Adjustable set pointer
- ▲ Wide angle needle sweep
- ▲ Translucent illuminated dial
- ▲ Chrome plated die-cast housing
- ▲ All-angle ball & socket mounting
- ▲ Use it with ANY ignition system
- ▲ Meter: 3 1/8" dia. X 3 3/8" deep
- ▲ Calibration kit included, no test eqpt. needed.

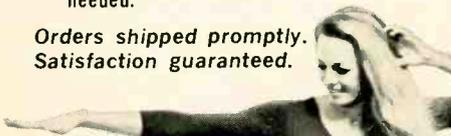Orders shipped promptly.
Satisfaction guaranteed.



DELTA PRODUCTS, INC.
Send check today!
P.O. Box 1147 RE / Grand Junction, Colo. 81501

Enclosed is \$ _____ Ship ppd. Ship C.O.D.
Please send:

COMPUTACH® Kits @ \$29.95 ppd
Sold in Kit Form ONLY!

Name _____
Address _____
City/State _____ Zip _____

Circle 12 on reader's service card

CORRESPONDENCE

(continued from page 12)

be of larger wattage, but must have the same voltage rating as the original. . .” Because this statement is not very specific, I feel it is a dangerous generalization. The simple regulator of Fig. 8, page 37, specifies a 5.6V Zener, but does not give the type number or specify wattage. A glance at the Dickson Diode Zener Diode Reference Chart shows that 5.6V Zeners are available with ratings from 250 mW to 50 watts.

This test current is usually appreciably less than the current that would produce maximum rated device dissipation. Device operation at appreciably less than the specified test current could possibly cause operation of the device at, or near the knee of, its characteristic curve, where its operation (if at all) would be unpredictable. The opposite extreme, operation at levels appreciably in excess of I_z could cause operation approaching maximum device dissipation levels. The higher case temperatures in most cases would make device derating mandatory for long service life. The 1000-ohm error-sensing resistor in Fig. 8 would limit current available to the Zener diode to a maximum of 12 to 20 mA, respectively, depending upon the assumptions that only the Zener is considered to be shorted or that both the Zener and the series pass transistors are considered to be shorted. With maximum available currents of these magnitudes, it is highly unlikely that anything Zeners in a range other than 400-mW to 1-watt would work effectively in this circuit.

M/SGT HAROLD L. STEPHENS
APO San Francisco

WIDER THE BAND, THE HIGHER THE FI?

I read with interest the article, “The Wider the Band, the Higher the Fi?” by Peter E. Sutheim (October 1967). I got lost in a few places during the interacting-phase discussions, so perhaps the idea presented below was discussed in the article, even though I didn’t recognize it.

In square-wave testing, the square wave displayed is considered to include some finite number of multiples of the fundamental. Although some authorities place this number at 40, 10 is the commonly accepted figure. If an amplifier having poor response at 10 kHz is tested with a 1-kHz square (or sawtooth) wave, rounding of the leading corners of the waveform is ob-

servable. Most high-frequency musical sounds (castanets, blocks, etc.) are not sine waves but sharp transients whose waveforms more closely resemble short pulses or sawtooths.

If the same criteria held true for these waveforms as for test waveforms (which would seem logical), then a 20-kHz castanet sound will require a frequency response of at least 200 kHz to be reproduced accurately. It may require as much as 800 kHz! Whether or not the amplifiers driving the source or speaker dynamics prevent these waves from reaching the listener undisturbed is a consideration outside my knowledge and experience.

NOEL NYMAN
Seattle, Wash.

Your comments raise two points. First, you are correct that the vast majority of musical waveforms are not sinusoids but repetitive pulses of one sort or another. Since we’re talking not about absolutes but about relative matters, in quantitative terms, the question “How short?” becomes important. So the first point is, Does music actually contain waveforms with rise times sufficiently steep to require amplifier frequency response that goes substantially beyond 20 kHz? The second point is: even if conventional musical instruments do produce significant amounts of energy above 20 kHz, can that energy make any difference to us, assuming we accept the conventionally agreed-on upper hearing limit of 15 to 20 kHz? (And that has not been successfully challenged, at least not on the basis of single-tone hearing tests.)

The only reason for producing spectacularly flat response out to 100 to 200 kHz would seem to be so that you can get nice-looking 10-kHz square waves on an oscilloscope, but that has little relevance to what we hear. Until someone demonstrates that human beings can hear sounds above 20 kHz, the question of whether musical instruments produce them is only academic.


OPERATIONAL AMPLIFIER

The informative article “Operational Amplifier” by Thomas H. Lynch (May 1968) had a few areas that require clarification with regard to Signetics products. The NE515 is a differential amplifier selling for \$4.15 in dual in-line packaging. Our key device in the classification of operational amplifiers is the 516, available for \$9.35. Our complete op amp line includes the 5709, 5710, 5711 Signetics versions of the Fairchild 709, 710 and 711. Com-

(continued on page 16)

breakthrough

Breakthrough

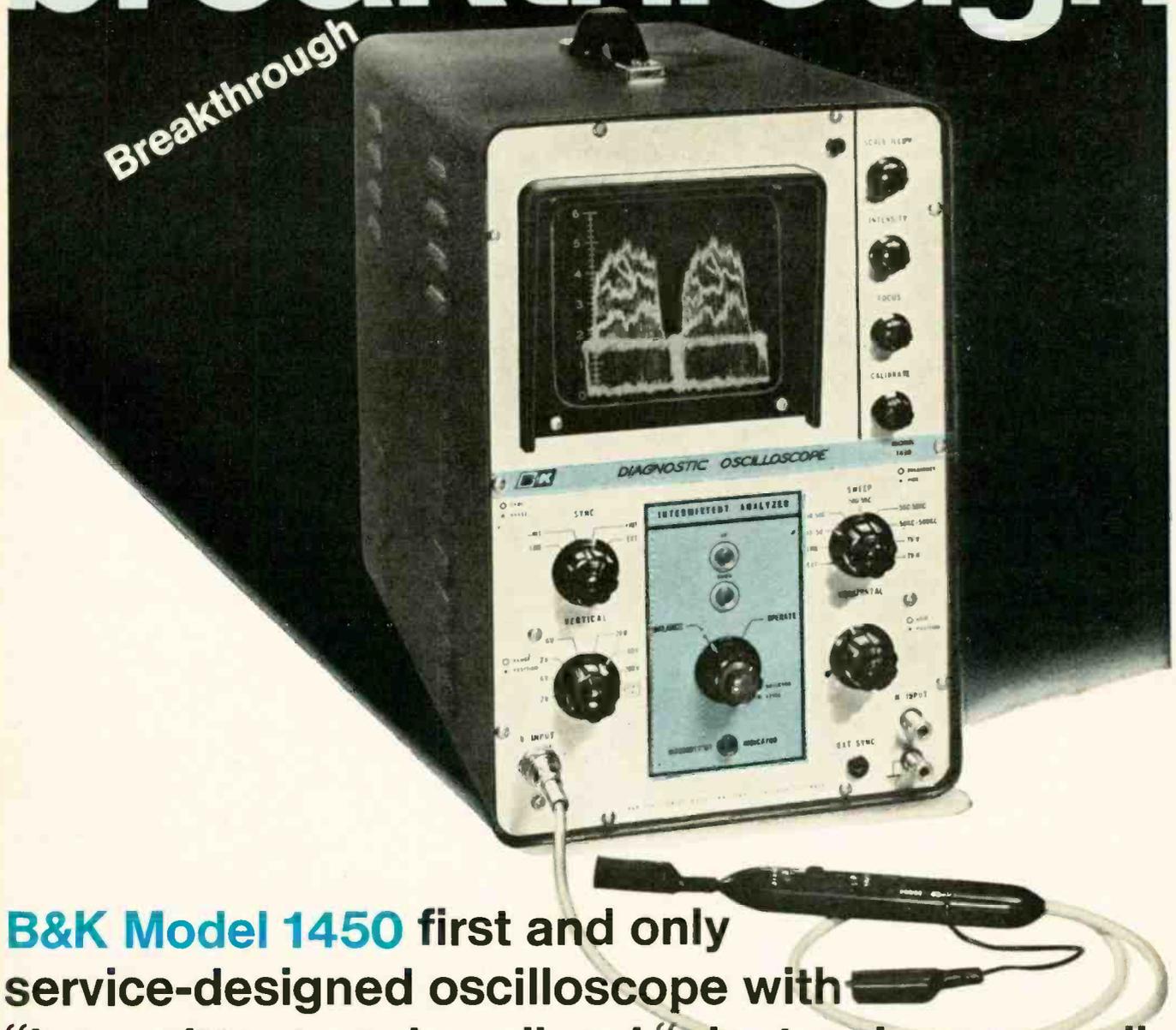

B&K Model 1450 first and only service-designed oscilloscope with "intermittent analyzer" and "electronic memory"

That elusive intermittent . . . how many hours have you spent trying to locate the source of the problem—how much time was wasted testing each circuit when you could have been doing more productive work? Now, B&K know-how and engineering genius have come through for you.

Result . . . the intermittent analyzer in the Model 1450 Diagnostic Oscilloscope. It will tell you *if* and *where* an intermittent occurs—even without your being there! The electronic memory will keep the intermittent indicator "on" until you return. Think of the time and money it saves.

The easiest to use 'scope ever built, its unique screen gives error-free direct readings of peak-to-peak voltages—it syncs automatically at any signal level—easily displays color reference signal. Convenient for use as a vectorscope too, all inputs and controls are on the front panel.

Deluxe in every respect, the 1450 is another B&K innovation that will make your time more profitable in solid state and color TV service. Years-ahead planning for present and future use . . . the best-value all-around 'scope you can buy. With probe. Net, \$279.95

INTERMITTENT MONITOR. Designed to supplement the indicators on the 1450, this plug-in monitor can be placed anywhere in your shop. It flashes and buzzes when an intermittent occurs . . . and projects a professional image to your customer. Net, \$24.95




B&K Division of Dynascan Corporation
1801 W. Belle Plaine Avenue • Chicago, Illinois 60613



Where Electronic Innovation Is A Way Of Life
Circle 15 on reader's service card

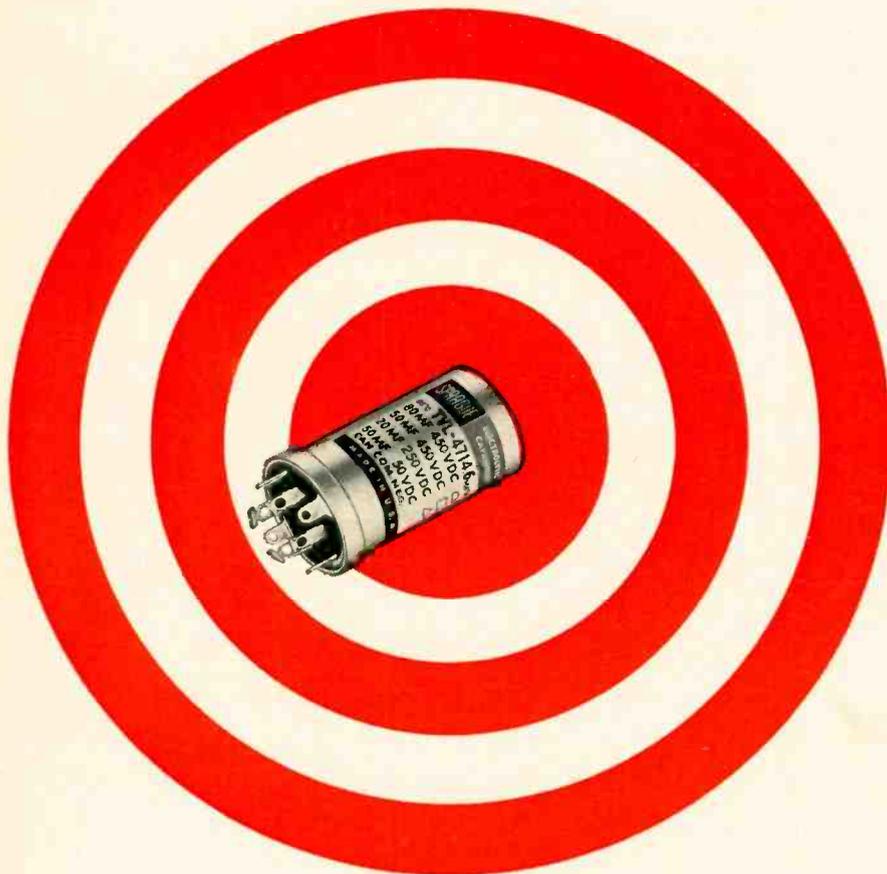IT TAKES AN EXACT REPLACEMENT TO HIT THE MARK IN COLOR TV SERVICE



TWIST-LOK® Capacitors
come in the right ratings so you can
make exact replacements

Ask your Sprague distributor for a copy of Sprague's comprehensive Electrolytic Capacitor Replacement Manual K-109 or write to:
Sprague Products Company, 81 Marshall St., North Adams, Mass. 01247.

P.S. You can increase your business 7½% by participating in EIA's "What else needs fixing?" program. Ask your distributor or write to us for details.

CS-8128



Circle 16 on reader's service card

CORRESPONDENCE
(continued from page 14)

plete data are available from the undersigned.

ELLIOT KANTER
Signetics Corp.
Rolling Meadows, Ill.

HORSEFLIES, TRACTORS AND MR. KIRCHHOFF

I certainly pity the poor fellow who is trying to obtain an understanding of the current and voltage relationships in an ac circuit on the basis of the article, "Horseflies, Tractors and Mr. Kirchhoff" (March, 1968). He will have a lot to "unlearn" when he finally is exposed to a truthful and responsible presentation of the subject. I wish to call attention to the fourth paragraph in the last column on page 71, beginning with the words, "The meter reads the highest voltage . . ."

There is *never* an instant when the voltage across one component is 7.1 and across the other component it is 2.9 volts (if a voltage of 10 volts peak to peak is applied to the circuit, as postulated in the beginning of the article). To see this, it is only necessary to plot two sine waves of equal amplitude, displaced 90° with respect to each other, and then add them up.

WALTHER RICHTER
CONSULTING ELECTRICAL ENGINEER
Milwaukee, Wis.

I read, with amusement, "Horseflies, Tractors and Mr. Kirchhoff" by Wayne Lemons (March 1968). I wonder, though, what Messrs. Kirchhoffs, Pythagoras and Bean would have to say about this: Two resistors of different values tied together in a circle, the voltage across each resistor is zero, the sum of the voltages around the loop is, of course, also zero, and all is well. However, put a changing magnetic field through the loop, perhaps by placing the loop around the core of a transformer, and it's a different story. The changing magnetic field induces a current in the loop, the same current in each resistor. The sum of the voltages around the loop is no longer zero.

Don't think harshly of Mr. Kirchhoff, though. The sum of the voltages around a loop is always zero if there is no magnetic field present. Messrs. Faraday or Maxwell could have told him that the sum of the voltages around a loop is actually equal to the time derivative of the magnetic flux through the loop. Oh, well.

HOWARD G. SCHIFFMAN
Westwood, Mass.
R-E

Zenith Tubes...

life-tested for greater dependability!




ZENITH TV PICTURE TUBES are rigorously tested at elevated line voltages for lengthy periods. Just one reason you can be sure of Zenith's great reliability and long life that better satisfies your customers. More than 200 Zenith quality tubes—for color TV, black-and-white TV, or special purposes—are in the complete line.

ZENITH "ROYAL CREST" CIRCUIT TUBES undergo over 1½ million hours of life-testing every month. Under actual operating conditions, they must meet the same quality standards as Zenith original parts—to perform with unrivaled dependability. Choose from a full line of more than 900 top-quality Zenith tubes.

Order all genuine Zenith replacement parts and accessories from your Zenith distributor

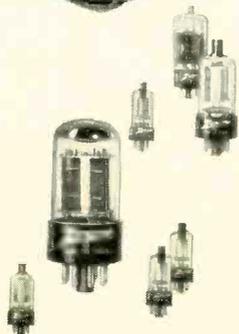Exciting Surprises
for You—
and Your Family!
Fun for all!
Get the details
at your Zenith
Distributor's
Parts Department.



Zenith B&W replacement picture tubes are made only from new parts and materials except for the glass envelope in some tubes which, prior to reuse, is inspected and tested to the same high standard as a new envelope. Some color picture tubes contain used material which, prior to reuse, is carefully inspected to meet Zenith's high quality standards.

BEST YEAR YET TO SELL THE BEST





ZENITH

*The quality goes in
before the name goes on*

**“Get more
education
or
get out of
electronics**

...that’s my advice.”

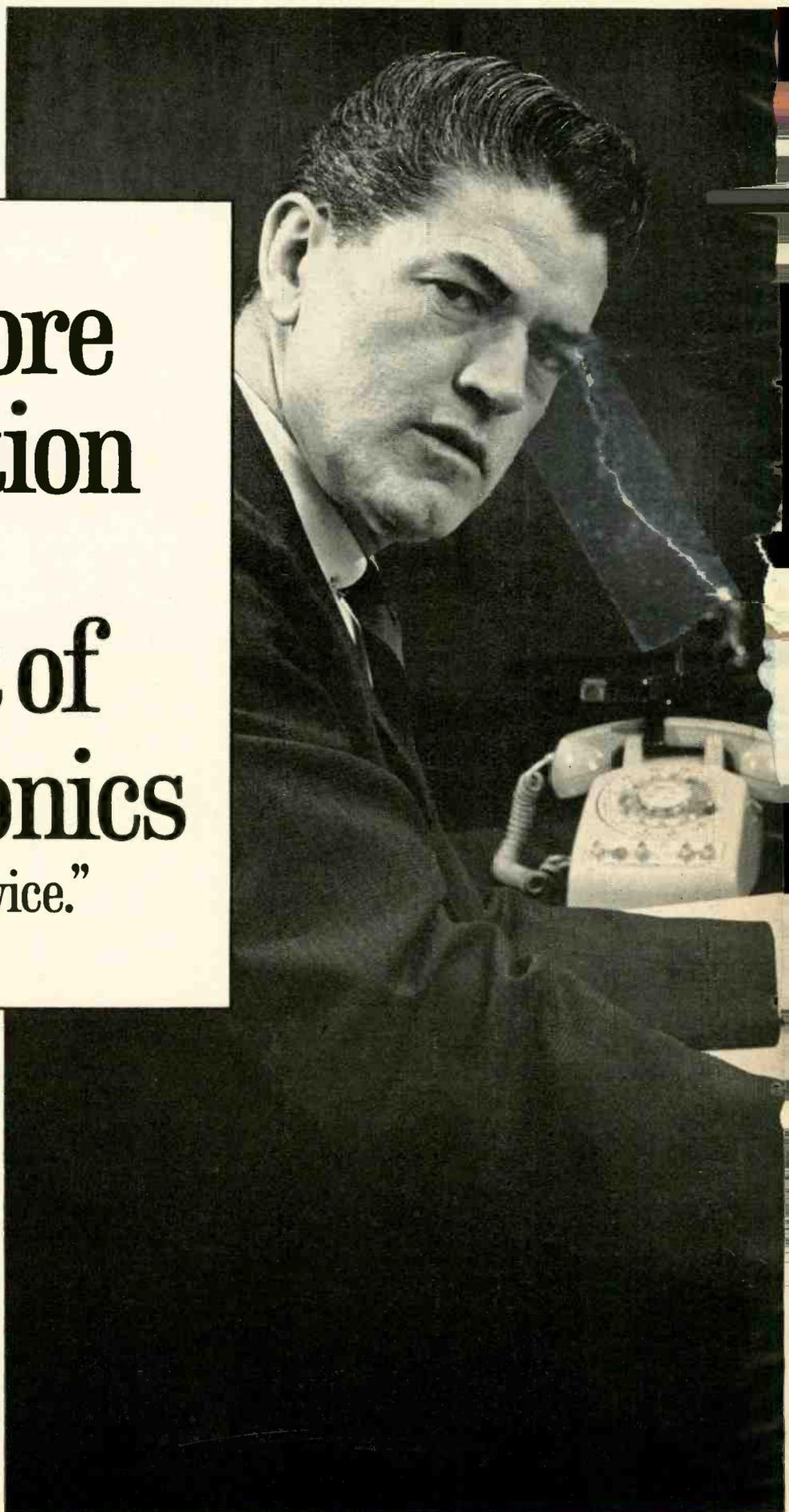

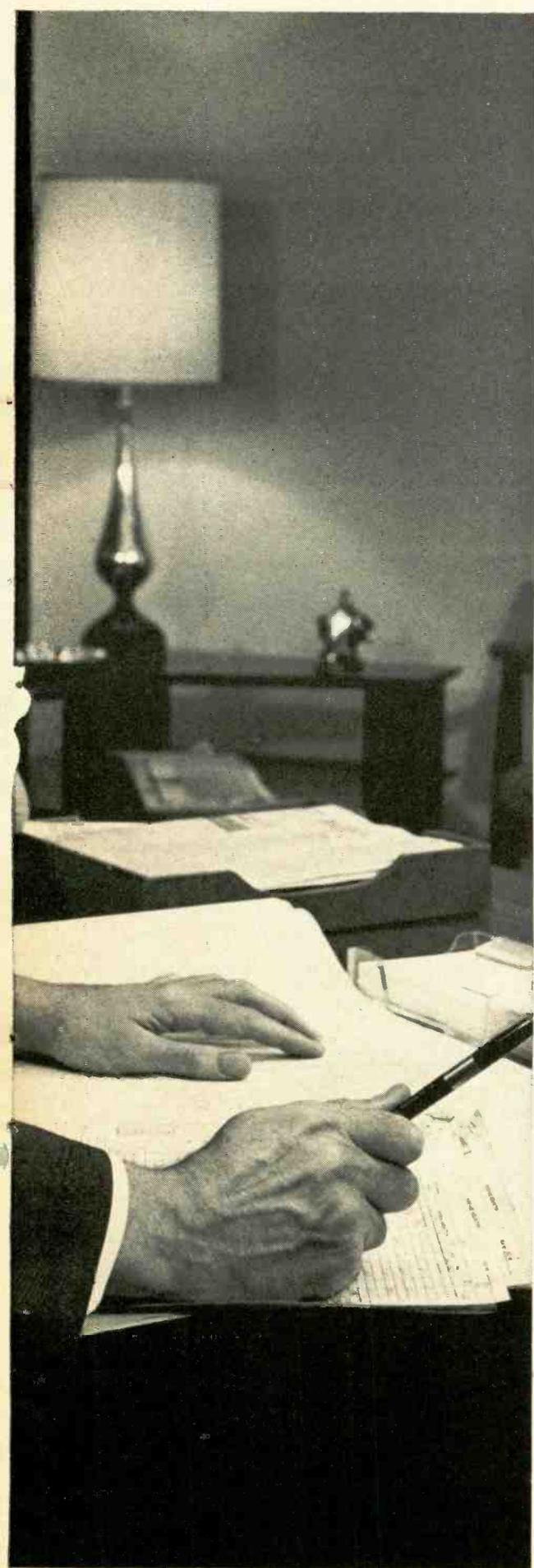

Ask any man who really knows the electronics industry.

Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff.

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Airmail postpaid card for your copy. If card is detached, use coupon below or write: CREI, Dept. 1407G, 3224 Sixteenth Street, N.W., Washington, D.C. 20010.

Founded 1927



Accredited Member of the National Home Study Council



**CREI, Home Study Division
McGraw-Hill Book Company
Dept. 1407G, 3224 Sixteenth Street, N.W.
Washington, D.C. 20010**

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

EMPLOYED BY _____

TYPE OF PRESENT WORK _____ G.I. BILL

- I am interested in Electronic Engineering Technology
- Space Electronics Nuclear Engineering Technology
- Industrial Electronics for Automation
- Computer Systems Technology

APPROVED FOR TRAINING UNDER NEW G.I. BILL

Look What's New



NEW
Kit
IT-18
\$24⁹⁵

NEW HEATHKIT In-Circuit Transistor Tester


At last, a realistic price for in-circuit testing of transistors! The new Heathkit IT-18 Tester has the facilities you need and it costs a lot less. It measures DC Beta in-or-out-of-circuit in 2 ranges from 2 to 1000 (the spec. commonly used by mfrs. and schematics to determine transistor gain). It tests diodes in-or-out-of-circuit for forward and reverse current to indicate opens or shorts. Measures transistors out-of-circuit for ICEO and ICBO leakage on leakage current scale of 0 to 5,000 uA. Identifies NPN or PNP devices, anode and cathode of unmarked diodes; matches transistors of the same type or opposite types. Cannot damage device or circuit even if connected incorrectly. Big 4½" 200 uA meter. 10-turn calibrate control. Completely portable, powered by "D" cell (long battery life). Front panel socket for lower power devices. Attached 3' test leads. Rugged polypropylene case with attached cover. Build in 2 hours. 4 lbs.

NEW
Kit
IP-18
\$19⁹⁵



NEW HEATHKIT 1-15 VDC Regulated Power Supply


Labs, service shops, hams, home experimenters . . . anybody working with transistor circuitry can use this handy new Heathkit All-Silicon Transistor Power Supply. Voltage regulated (less than 40 mV variation no-load to full-load; less than 0.05% change in output with input change from 105-125 VAC). Current limiting; adjustable from 10-500 mA. Ripple and noise less than 0.1 mV. Transient response 25 uS. Output impedance 0.5 ohm or less to 100 kHz. AC or DC programming (3 mA driving current on DC). Circuit board construction. Operates 105-125 or 210-250 VAC, 50/60 Hz. 6 lbs.

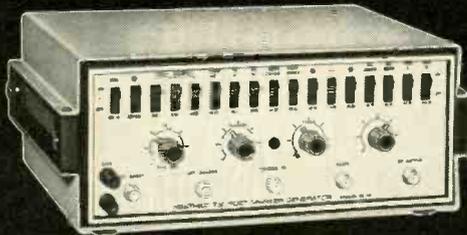

NEW
Kit
IG-14
\$99⁹⁵

NEW HEATHKIT Crystal-Controlled Post Marker Gen.

Fast, accurate color TV and FM alignment at the touch of a switch! 15 crystal-controlled marker frequencies. Select picture and sound IF's, color bandpass and trap freqs., 6 dB points, FM IF center freq. and 100 kHz points. Use up to six markers simultaneously. Birdie-type markers. Trace and marker amplitude controls permit using regular 'scope. 400 Hz modulator. Variable bias supply. Input and output connectors for use with any sweep generator. Also has external marker input. BNC connectors. Solid-state circuit uses 22 transistors, 4 diodes. Two circuit boards. Handsome new Heathkit instrument styling of beige and black in stackable design. Until now, an instrument of this capability cost hundreds of dollars more. Order your IG-14 now, it's the best investment in alignment facilities you can make. 8 lbs.

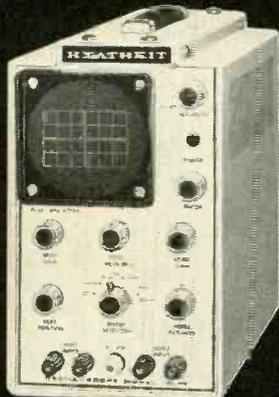

NEW
Kit
IO-17
\$79⁹⁵

NEW HEATHKIT Low-Cost 5 MHz 3" 'Scope

Here is the wideband response, extra sensitivity and utility you need, all at low cost. The Heathkit IO-17 features vertical response of 5 Hz to 5 MHz; 30 mv Peak-to-Peak sensitivity; vertical gain control with pull-out X50 attenuator; front panel 1 volt Peak-to-Peak reference voltage; horizontal sweep from internal generator, 60 Hz line, or external source; wide range automatic sync; plastic graticule with 4 major vertical divisions & 6 major horizontal; front mounted controls; completely nickel-alloy shielded 3" CRT; solid-state high & low voltage power supplies for 115/230 VAC, 50-60 Hz; Zener diode regulators minimize trace bounce from line voltage variations; new professional Heath instrument styling with removable cabinet shells; beige & black color; just 9½" H. x 5½" W. x 14½" L.; circuit board construction, shipping wt. 17 lbs.



NEW
Kit
IM-17
\$21⁹⁵

NEW HEATHKIT Solid-State Portable Volt-Ohm Meter

There's never been a better buy in meters. Solid-state circuit has FET input, 4 silicon transistors (2 used as diodes), and 1 silicon diode. 11 megohm input on DC, 1 megohm on AC. 4 DC volt ranges, 0-1000 v, with ±3% accuracy; 4 AC volt ranges, 0-1000 v. with ±5% accuracy. 4 resistance ranges, 10 ohms center scale x1, x100, x10K, x1M, measures from 0.1 ohm to 1000 megohms. 4½", 200 uA meter with multicolored scales. Operates on "C" cell and 8.4 v. mercury cell (not included). Housed in rugged black polypropylene case with molded-in cover and handle and plenty of space for the three built-in test leads. An extra jack is provided for connecting accessory probes to extend basic ranges. Controls include zero-adjust, ohms-adjust, DC polarity reversing switch, continuous rotation 12-position function switch. Easy-to-build circuit board construction completes in 3-4 hours. 4 lbs.

From Heath

NEW HEATHKIT AJ-15 Deluxe Stereo Tuner

For the man who already owns a fine stereo amplifier, and in response to many requests, Heath now offers the superb FM stereo tuner section of the renowned AR-15 receiver as a separate unit. The new AJ-15 FM Stereo Tuner has the exclusive design FET FM tuner for remarkable sensitivity, the exclusive Crystal Filters in the IF strip for perfect response curve and no alignment; Integrated Circuits in the IF for high gain, best limiting; elaborate Noise-Operated Squelch; Stereo-Threshold Switch; Stereo-Only Switch; Adjustable Multiplex Phase, two Tuning Meters; two variable output Stereo Phone jacks; one pair variable outputs plus two fixed outputs for amps., recorders, etc.; front panel mounted controls; "Black Magic" panel lighting; 120/240 VAC operation. 18 lbs. *Walnut cabinet AE-18, \$19.95.

NEW HEATHKIT AA-15 Deluxe Stereo Amplifier

For the man who already owns a fine stereo tuner, Heath now offers the famous amplifier section of the AR-15 receiver as a separate unit. The new AA-15 Stereo Amplifier has the same superb features: 150 watts Music Power; Ultra-Low Harmonic & IM Distortion (less than 0.5% at full output); Ultra-Wide Frequency Response (± 1 dB, 8 to 40,000 Hz at 1 watt); Ultra-Wide Dynamic Range Preamp (98 dB); Tone-Flat Switch; Front Panel Input Level Controls; Transformerless Amplifier; Capacitor Coupled Outputs; Massive Power Supply; All-Silicon Transistor Circuit; Positive Circuit Protection; "Black Magic" Panel Lighting; new second system Remote Speaker Switch; 120/240 VAC. 26 lbs. *Walnut cabinet AE-18, \$19.95.

NEW HEATHKIT 2-Meter AM Amateur Transceiver

2-Meters at low cost. And the HW-17 Transceiver has 143.2 to 148.2 MHz extended coverage to include MARS, CAP, and Coast Guard Auxiliary operation. Output power of tube-type transmitter is 8 to 10 watts, AM. 4 crystal sockets plus VFO input. Relayless PTT operation. Double conversion solid-state superhet. Receiver has 1 μ V sensitivity with prebuilt, aligned FET tuner, ANL, Squelch, "Spot" function, and lighted dial. Signal-strength/relative power-output meter. Battery saver switch for low current drain during receiving only. 15 transistor, 18 diode, 3 tube circuit on two boards builds in about 20 hours. Built-in 120/240 VAC, 50-60 Hz power supply and 3" x 5" speaker; low profile aluminum cabinet in Heath gray-green; ceramic mic. and gimbal mount included. 17 lbs. *Optional DC mobile supply, HWA-17-1, \$24.95.

NEW HEATHKIT Home Protection System

Customize your own system with these new Heathkit units to guard the safety of your home and family. Warns of smoke, fire, intruders, freezing, cooling, thawing, pressure, water, almost any change you want to be warned about. Your house is already wired for this system, just plug units into AC outlets. Exclusive "loading" design of transmitters generates unusual signal which is detected by the Receiver/Alarm. Solid-state circuitry with fail-safe features warns if components of system have failed. Any number of units may be used in system. Receiver/Alarm has built-in 2800 Hz alarm and rechargeable battery to signal if power line fails (built-in charger keeps battery in peak condition). Receiver accepts external 117 VAC bells or horns. Smoke/Heat Detector-Transmitter senses smoke and 133°F. heat (extra heat sensors may be added to it). Utility Transmitter has several contacts to accept any type switch or thermostat to guard against any hazard except smoke. All units feature circuit board construction and each builds in 3-4 hours. All are small and finished in beige and brown velvet finish. Operating cost similar to that of electric clocks. Invest in safety now with this unique new low-cost Heathkit system.

NOW, THE TUNER AND AMPLIFIER OF THE FAMOUS HEATH AR-15 RECEIVER ARE AVAILABLE AS SEPARATE COMPONENTS



NEW Kit
AJ-15
\$189⁹⁵*



NEW Kit
AA-15
\$169⁹⁵*

NEW
Kit
HW-17
\$129⁹⁵*




GD-77
Receiver /
Alarm
\$39⁹⁵

NEW



GD-87
Smoke /Heat
Detector-
Transmitter
\$49⁹⁵

GD-97
Utility
Transmitter
\$34⁹⁵

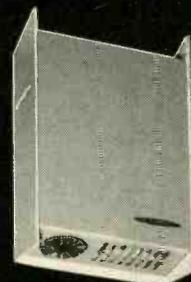

NEW

FREE 1968 CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-7
Benton Harbor, Michigan 49022
In Canada, Daystrom Ltd.

Enclosed is \$ _____, plus shipping.

Please send model (s)
 Please send FREE Heathkit Catalog.
 Please send Credit Application.

Name _____

Address _____

City _____

State _____

Zip _____

Prices & specifications subject to change without notice.

CL-327


In the Shop . . . With Jack

By JACK DARR

THE CASE OF THE "M-SHAPED" SYNC

Seeing spots before your eyes?

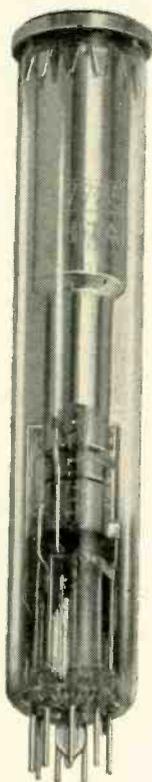It's time to replace your worn-out vidicon



Prices and quality have never been better.

The quality: brand-new Toshiba and Hitachi, fully guaranteed in factory-sealed cartons.

The price: (distributor cost)

Hitachi 7735-A vidicon \$34.50

Toshiba 7038-H vidicon \$29.50

Hitachi separate mesh vidicon 8507 \$74.50

Replacement vidicon for

Sony and Panasonic 7262.....\$29.50

All vidicons sold in lots of 5 (10% more for lesser quantities). Act today. These prices apply for a limited period. Write for GBC's free Encyclopedia of CCTV equipment.

GBC Closed Circuit TV Corp.
89 Franklin St., N.Y. 10013
(212) 966-5412



See us at the N.E.W. Show Booth #2230

Circle 19 on reader's service card

THE TV SET THAT "ISN'T WORKING quite right" is the worst kind. Nothing visible that you can put your finger on—just a sort of "10% off" in performance. So, you can have a problem, and not notice it in time.

I got into this with a Motorola TS-908 color chassis. I put in a new color picture tube and cooked the set on the bench for half a day. It worked beautifully. About a week after it had gone home, the irate owner called me: "It isn't working right! It

jumps in and out. The color acts funny, too."

Well, this wasn't much of a description to go on, but a look at the set itself showed me what "jumps in and out" was—unstable horizontal sync! This, of course, affected the color by fouling up the burst-phase timing and so on. So, back to the shop.

On the bench, the horizontal hold control showed a very peculiar reaction. Overall range was pretty bad, and the horizontal sync was jittery. So, up scope and at 'em!

Poking around in the horizontal afc circuit, I saw a very odd-looking waveform. Tracing this back, I got the same thing on the grid of the first sync clipper. The sync pulse (Fig. 1), instead of being nice and sharply peaked, was a distinct "M" and pretty jittery. In fact, it jittered so badly that it was hard to photograph; I had to "technically augment" the negative with a soft lead pencil to show the actual waveshape of the pulse.

While scratching around in that circuit, I found that the +200-volt line also had a 10-15-volt p-p sawtooth on it. This was jittery, too. Well, well. Things were looking up.

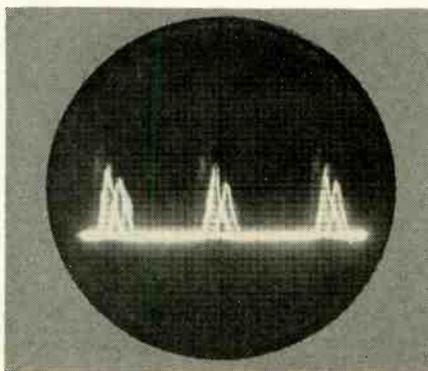


Fig. 1—This agc keying pulse strayed into the horizontal afc and color apc circuits, causing jittery sync and color.

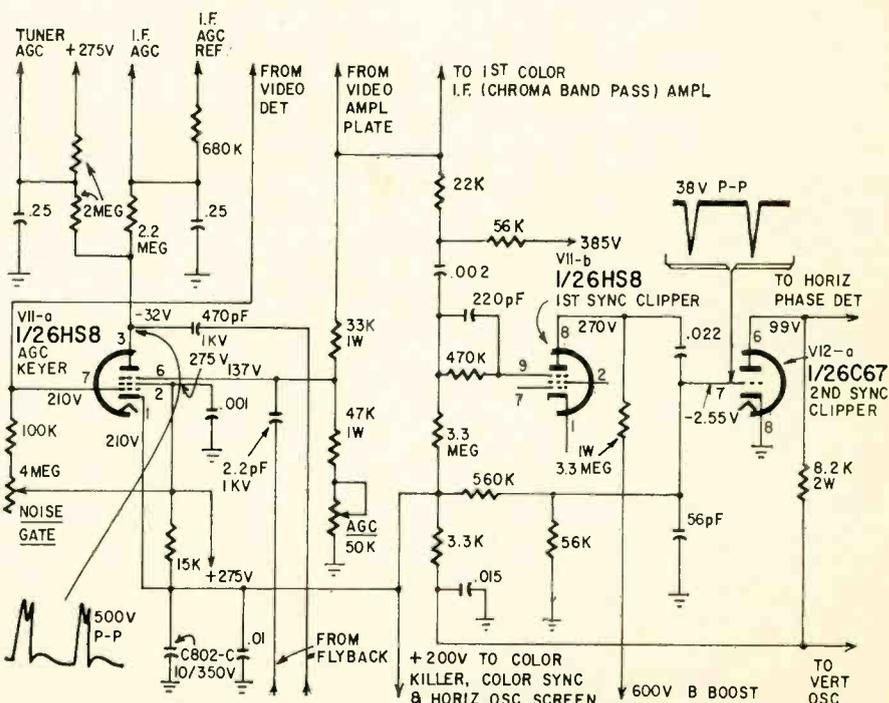


Fig. 2—Agc and sync circuits in the Motorola TS-908 color TV chassis. Unstable horizontal sweep and jittery color were caused by a defective filter capacitor (C802-c) which permitted the agc keying pulses to appear on the 200-volt line.



B&K MODEL 970 TRANSISTOR EQUIPMENT ANALYST

SERVICE AM & FM AUTO & TRANSISTOR EQUIPMENT AT A PROFIT!

Jobs that used to be unprofitable now go so quickly that you can make good money handling them! There are millions of auto radios and transistor radios in the field—portables, auto and table models, plus hi-fi and communications equipment. Instead of turning them away, you can turn them into money-makers with the B&K Model 970 Radio Analyst.

The 970 is effective because it's *accurate* and *complete*. Using the famous B&K signal injection technique, this all-in-one instrument provides the required dc power, lets you test power and signal transistors in and out of circuit; generates RF and audio signals, and includes a rugged, accurate VOM. Four functions in one compact package—with solid state reliability, B&K professional quality.

LOW INVESTMENT—QUICK RETURN

See your B&K Distributor or write for Catalog AP22-R

Net \$199⁹⁵



B & K DIVISION OF DYNASCAN

1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

Circle 20 on reader's service card

FEATURES:

BUILT-IN POWER SUPPLY

Auto Radios—High current, low-ripple, for transistor, hybrid, and vibrator types.

Transistor Portables— $1\frac{1}{2}$ to 12 volts for battery substitution—plus separately variable voltage tap for bias.

QUICK AND ACCURATE TESTING OF POWER AND SIGNAL TRANSISTORS

In-Circuit—stage by stage DC signal injection and sensitive metering of power supply current.

Out-of-Circuit—Direct Beta and Leakage meter scale readings. Easy balancing or matching.

VERSATILE SIGNAL GENERATORS

RF Generators—provide broadcast and IF frequencies for both AM and FM bands.

Audio Generator—for AM or FM modulation of the RF signals, and for troubleshooting audio circuits.

RUGGED VOM

Volt-OHM-Milliammeter—with rugged, taut band meter—provides correct ranges for easy, fast servicing of all home and auto radios, as well as transistor portables.

MODEL ACP-1



**NEW! SOLID STATE
Compressor-Preamp**

Kit \$18.50* • Wired \$26.50*

- Use with any Tape Recorder for automatic control of recording level.
- Add modulation punch to Amateur Radio and CB Transmitters
- Use with any P.A. System for constant output level and reduce annoying feedback.

30 db compression range ■ 20 to 20,000 cps response ■ Low-noise high-impedance FET input stage ■ 5-transistor and 1-diode circuit ■ Adjustable input and output levels ■ MIL-type circuit board and easy-to-follow instructions ■ Easily installed in mike line ■ 3-way jacks for PTT operation ■ Attractive 2½ x 3 x 4¼ metal cabinet.

*Less battery. Postpaid in U.S.A. when check or M.O. included with order. Sorry no C.O.D. California orders must add 5% sales tax.



CARINGELLA ELECTRONICS, Inc.
P.O. Box 327 ■ Upland, California 91786
Phone 714-985-1540

Circle 21 on reader's service card

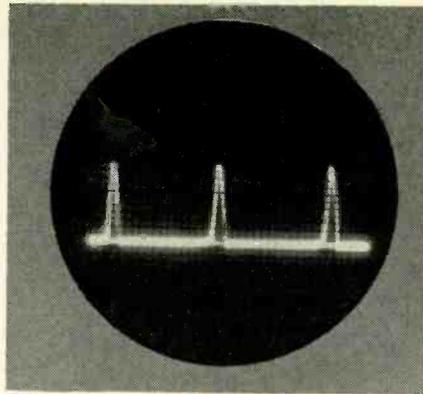


Fig. 3—The correct pulse on the first sync-clipper grid is 34 volts peak-to-peak.

This kind of junk floating around on what should be a nice clean dc supply line always means trouble, and the kind that means an open capacitor somewhere. Using the scope in the agc and sync circuits (Fig. 2), we traced the trouble to C802-c, a 10- μ F electrolytic connected to the cathode of the 6SH8 (V11-a) agc keyer tube—the 200-volt B+ source.

Hooking the scope to the sync-clipper grid, I bridged a new 10- μ F electrolytic across C802-c; the "M" shape of the waveform "flipped up" and the twin peaks merged to form a much better-looking sharp spike (Fig. 3)! The horizontal sync improved, the color lock went back to normal and

things looked better all around.

Now, wha' hopen? The 6HS8 agc tube was keyed by a pulse from the flyback, as usual. This keying pulse *did* have a normal "M" shape, according to the waveform shown on the schematic. Apparently, the lack of proper bypassing on the agc tube's cathode was letting this "M"-shaped pulse stray into the other circuits. The slight delay in the pulse, together with the deformation of the peak of the pulse, was causing the horizontal a/c, burst keyer and a lot of other things to go nuts trying to keep up with it! They would key first on one peak of the "M", then the other, and I got the jitter.

So, I replaced C802. If you find a bad section of a multiple electrolytic, replace the whole thing! Whatever condition exists inside the can and that made one section go bad will very soon get the others, and then you have a nice, free callback.

If there's a moral to this, it should be, "Look 'em over *very* carefully before you let 'em out of the shop!" Look out for those "just a little bit off" things, such as weak vertical sync or horizontal sync, jitters, and the like. After the average set owner has paid for repairs, he gets just a little more sensitive than he was before! So, be darn sure the thing's working *right* before you let it out of that door! **R-E**

the
best buy
for the
money



the sound approach to quality



3700 S. Broadway Pl., Los Angeles, Calif. 90007
69-41 Calamus Ave., Woodside, N. Y. 11377
Exclusive Canadian Distr. —
Perfect Mfg. & Supplies Corp. Ltd.

**KENWOOD
KA 2000**

40 WATT SOLID STATE STEREO AMPLIFIER

\$89.95

including cabinet



and KENWOOD dependability, too!

Circle 22 on reader's service card

GOOF- PROOF

VOM



Here's the most foolproof volt-ohm-milliammeter ever made. Protection approaches 100%. It's the VOM you will want to have on hand where inexperienced people are running tests . . . or will reach for yourself on those days when you're all thumbs. The 260-5P will save you all kinds of headaches from burned out meters and resistors, bent pointers, and inaccuracies caused by overheating.

Combined Protection You Won't Find In Any Other VOM

1. Reset button pops out to indicate overload.
2. You cannot reset circuits while overload is present.
3. Protective circuit does *not* require massive overloads which can cause hidden damage to the instrument.
4. All ranges are protected except those not feasible in a portable instrument—1000 and 5000 volts DC and AC; 10 amp DC.

SIMPSON 260-5P

ONLY \$94.00

Write for Bulletin 2076

Ranges—The 260-5P has the same ranges and takes the same accessories as Simpson's famous 260-5 volt-ohm-milliammeter.



DIVISION

Simpson

INSTRUMENTS THAT STAY ACCURATE

SIMPSON ELECTRIC COMPANY

5200 W. Kinzie Street, Chicago, Ill. 60644 • Phone: (312) 379-1121
Representatives in Principal Cities See Telephone Yellow Pages
Export Dept.: 400 W. Madison St., Chicago, Ill. 60606 Cable, Simelco
In Canada: Bach-Simpson Ltd., London, Ontario
In India: Ruttonsha-Simpson Private Ltd., Vikhroli, Bombay

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

How to get into One of the hottest money-making fields in electronics today— servicing two-way radios!



HE'S FLYING HIGH. Before he got his CIE training and FCC License, Ed Dulaney's only professional skill was as a commercial pilot engaged in crop dusting. Today he has his own two-way radio company, with seven full-time employees. "I am much better off financially, and really enjoy my work," he says. Read here how you can break into this profitable field.

More than 5 million two-way transmitters have skyrocketed the demand for service men and field, system, and R&D engineers. Topnotch licensed experts can earn \$12,000 a year or more. You can be your own boss, build your own company. And you don't need a college education to break in.

HOW WOULD YOU LIKE to start collecting your share of the big money being made in electronics today? To start earning \$5 to \$7 an hour... \$200 to \$300 a week... \$10,000 to \$15,000 a year?

Your best bet today, especially if you

don't have a college education, is probably in the field of two-way radio.

Two-way radio is booming. Today there are more than *five million* two-way transmitters for police cars, fire department vehicles, taxis, trucks, boats, planes, etc. and Citizen's Band uses—

and the number is still growing at the rate of 80,000 new transmitters per month.

This wildfire boom presents a solid gold opportunity for trained two-way radio service experts. Many of them are earning \$5,000 to \$10,000 a year *more* than the average radio-TV repair man.

Why You'll Earn Top Pay

One reason is that the United States Government doesn't permit anyone to service two-way radio systems unless he is *licensed* by the Federal Communications Commission. And there simply aren't enough licensed electronics experts to go around.

Another reason two-way radio men earn so much more than radio-TV service men is that they are needed more often and more desperately. A home radio or television set may need repair only once every year or two, and there's no real emergency when it does. But a two-way radio user must keep those transmitters operating at all times, and *must* have their frequency modulation and plate power input checked at regular intervals by licensed personnel to meet FCC requirements.

This means that the available licensed experts can "write their own ticket" when it comes to earnings. Some work by the hour and usually charge at least \$5.00 per hour, \$7.50 on evenings and Sundays, plus travel expenses. A more common arrangement is to be paid a monthly retainer fee by each customer. Although rates vary widely, this fixed charge might be \$20 a month for the base station and \$7.50 for each mobile station. A survey showed that one man can easily maintain at least 100 stations, averaging 15 base stations and 85 mobiles. This would add up to at least \$12,000 a year.


Be Your Own Boss

There are other advantages too. You can become your own boss—work entirely by yourself or gradually build your own fully staffed service company. Instead of being chained to a workbench, machine, or desk all day, you'll move around, see lots of action, rub shoulders with important police and fire officials and business executives who depend on two-way radio for their daily operations. You may even be tapped for a big job working for one of the two-way radio manufacturers in field service, factory quality control, or laboratory research and development.

How To Get Started

How do you break into the ranks of the big-money earners in two-way radio? This is probably the best way:

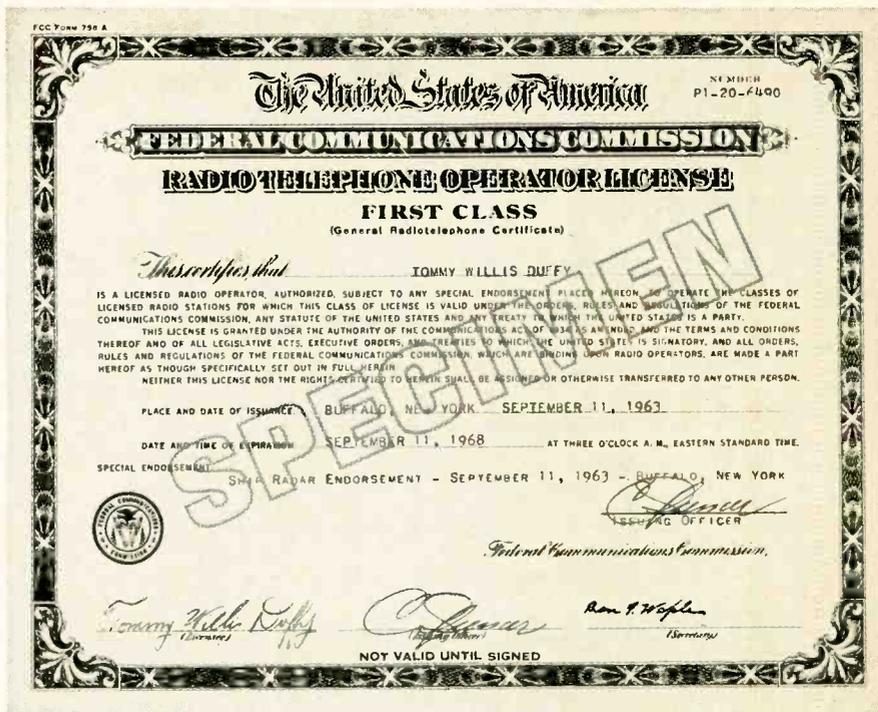1. Without quitting your present job, learn enough about electronics fundamentals to pass the Government FCC Exam and get your Commercial FCC License.
2. Then get a job in a two-way radio service shop and "learn the ropes" of the business.
3. As soon as you've earned a reputation as an expert, there are several ways you can go. You can move *out* and start signing up and servicing your own customers. You might become a franchised service representative of a big manufacturer and then start getting into two-way radio sales, where one sales contract might net you \$5,000. Or you may even be invited to move *up* into a high-prestige



THIS COULD BE YOUR "TICKET" TO A GOOD LIVING. You must have a Commercial FCC License to service two-way radios. Two out of three men who take the FCC exam flunk it... but nine out of ten CIE graduates pass it the first time they try!

salaried job with one of the major manufacturers either in the plant or out in the field.

The first step—mastering the fundamentals of Electronics in your spare time and getting your FCC License—can be easier than you think.

Cleveland Institute of Electronics has been successfully teaching electronics by mail for over thirty years. Right at home, in your spare time, you learn electronics step by step. Our AUTO-PROGRAMMED™ lessons and coaching by expert instructors make everything clear and easy, even for men who thought they were "poor learners." You'll learn not only the fundamentals that apply to all electronics design and servicing, but also the specific procedures for installing, troubleshooting, and maintaining two-way mobile equipment.

Get Your FCC License... or Your Money Back!

By the time you've finished your CIE course, you'll be able to pass the FCC License Exam with ease. Better than nine out of ten CIE-trained men pass the FCC Exam the first time they try, even though two out of three non-CIE men fail. This startling record of achievement makes possible the famous CIE

warranty: you'll pass the FCC Exam upon completion of your course or your tuition will be refunded in full.

Ed Dulaney is an outstanding example of the success possible through CIE training. Before he studied with CIE, Dulaney was a crop duster. Today he owns the Dulaney Communications Service, with seven people working for him repairing and manufacturing two-way equipment. Says Dulaney: "I found the CIE training thorough and the lessons easy to understand. No question about it—the CIE course was the best investment I ever made."

Find out more about how to get ahead in all fields of electronics, including two-way radio. Mail the bound-in postpaid reply card for two FREE books, "How To Get A Commercial FCC License" and "How To Succeed In Electronics." If card has been removed, just send us your name and address on a postcard.

ENROLL UNDER NEW G.I. BILL


All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, OR are in service now, check box on reply card for G.I. Bill information.

CIE Cleveland Institute of Electronics
1776 E. 17th St., Dept. RE-50, Cleveland, Ohio 44114

A Leader in Electronics Training... Since 1934 • Accredited Member National Home Study Council



BUILD FOR YOUR CAR:

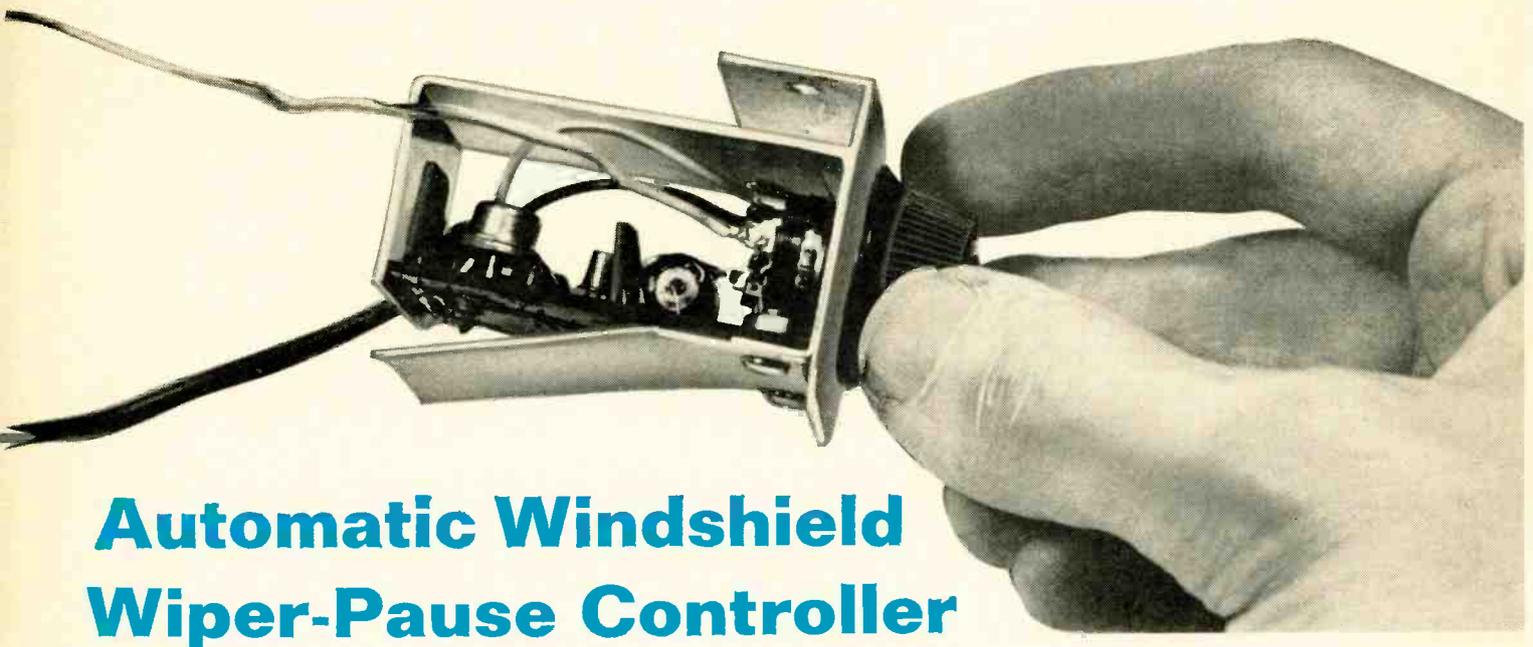

Automatic Windshield Wiper-Pause Controller

Wipe . . . 1 . . . 2 . . . 3 . . . Wipe . . . 1 . . . 2 . . . 3 . . . Wipe

By **S. B. GRYNKEWICZ**


LIVES THERE A DRIVER WHO HASN'T encountered this: A light mist hangs in the air. Traffic is just heavy enough so that those @#!90-drivers-in-a-hurry periodically whizzing by you leave a thin coating of dirt on your windshield.

If you're like me, you hate to see those wiper blades flicking back and forth, wearing away, and giving a grit-polish to an expensive windshield. Turning the wipers on and off and reaching for the knob every few minutes didn't appeal to me, so I decided to let electronics do the job.

With this Automatic Pause Controller (APC), you can operate the windshield wiper at its normal speeds in a normal manner (no pause between sweeps) or set the control knob to obtain a desired pause between sweeps . . . 1 second, 2 seconds . . . 15 seconds . . . It's the pause that makes the difference. However, each sweep occurs at normal speeds.

The unit will not operate with vacuum-operated wipers. Electric wipers have been in vogue for the past 15 years, and unless you have an older

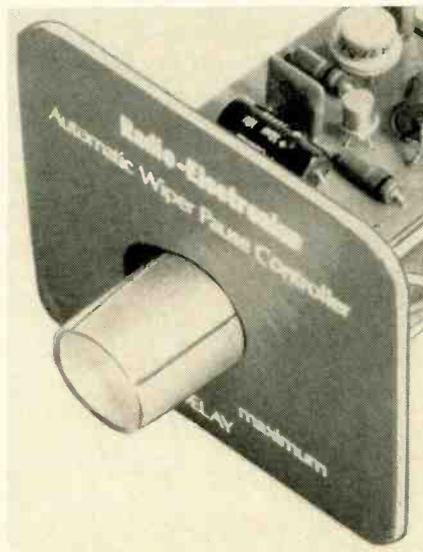car the chances are you can use APC. Federal regulations require that all cars built after 1967 have two-speed wiper systems.



Mechanical layout of the automatic wiper-pause controller is not critical. See variation above. Build it to fit your car.

All windshield-wiper motors have a built-in cam-operated "park" switch (S3 in Fig. 1) to keep the wiper motor running until the wiper blades return to their park position; even after the wiper switch on the dashboard is turned off. It's this cam-activated switch that makes the APC possible.

Two silicon semiconductors, a unijunction transistor (Q1) and a silicon-controlled rectifier (SCR1) are used in the APC. The SCR, which switches the wiper motor on, is triggered by preset pulses from relaxation oscillator Q1. Once the SCR conducts, it stays on until its anode voltage is zero with respect to its cathode.

Operation of the relaxation oscillator is simple. When power is applied to the APC through S1 (S2 off), C1 begins to charge to the supply voltage through R1 and R2. The charge across C1 also appears across the emitter and base 1 of Q1. When the charge reaches a critical level, it drains off through Q1's emitter, base 1 and R3 until the emitter drops enough to stop conducting. (The critical level depends upon the transistor's characteristics.) Capacitor C1 recharges and the cycle is re-

peated. Value of R1 and C1 and the setting of R2 determine the charging time. The greater the value of resistance and capacitance, the longer it takes to charge the capacitor and the longer the pause between wiper sweeps.

When Q1's emitter voltage goes positive enough, current flows through R3, Q1's base 1 and base 2, and R4. The greater the current flow, the greater the voltage drop across R4. This voltage is also across the SCR's gate and cathode. When the voltage drop across R4 reaches a sufficient level it causes the SCR to conduct and turn on the windshield wiper motor.

Once the motor starts to operate, the cam-activated switch closes and keeps the motor running even though it shorts out the SCR and halts its conduction. The motor will continue to operate until the cam opens S3. When S3 opens, the motor will remain at rest until the SCR is fired once again by another pulse.


To operate the wipers in a normal manner simply close S2. When S2 is closed it overtakes the APC regardless of the setting of S1 and R2. However, both S1 and S2 must be off for the wipers to remain at rest. Note: On many cars S2 is actually a 3-position switch (off, low, high). If you are fortunate enough to own a Cadillac you have still another position (medium) at your disposal.

Capacitors C2 and C3 and diode D1 prevent the SCR from "false" firing due to inductive kickback from the motor when it is shut off, and prevent other undesirable effects brought on by switching transients.

Construction

A 1½" x 2" printed circuit board was used, but a plain perforated board and push-in terminals can be substituted.
(continued on page 79)

PARTS LIST	
C1	50- μ F, 15-volt electrolytic capacitor
C2	0.1- μ F, 25-volt disc capacitor
C3	1- μ F, 25-volt disc capacitor
R1	33,000 ohms (15,000 ohms for 6-volt systems)
R2	Linear potentiometer, 50,000 ohms with switch S1
R3	51 ohms, 5%
R4	1000 ohms (replace with jumper for 6-volt systems)
All resistors ½ watt	
Q1	Unijunction transistor (2N2646, GE, Motorola or similar)
SCR1	Silicon controlled rectifier (MCR2604-4, Motorola or similar)
D1	Silicon rectifier, 200-volt or higher PIV (1N2069 or similar)
S1	spst, (on R2)
S2	Standard wiper switch (see text)
MISC	small piece of perforated board, aluminum sheet, knob, wire, solder.

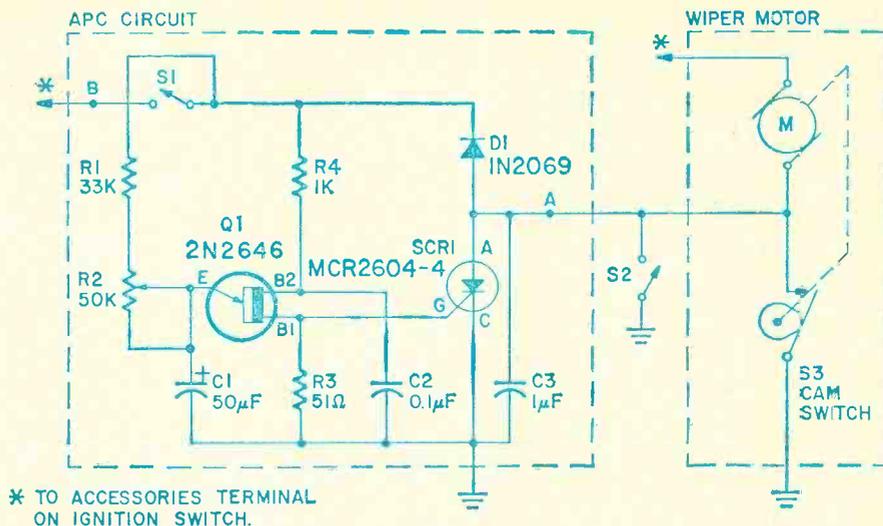

FOR 6-VOLT SYSTEM, REPLACE R4 WITH JUMPER WIRE, REDUCE R1 TO 15,000 OHMS



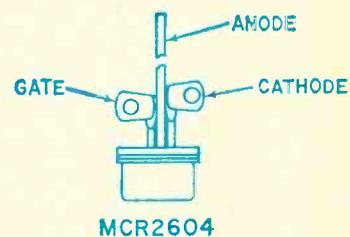


Fig. 1—Unijunction transistor controls the wiper by firing the SCR at regular intervals.

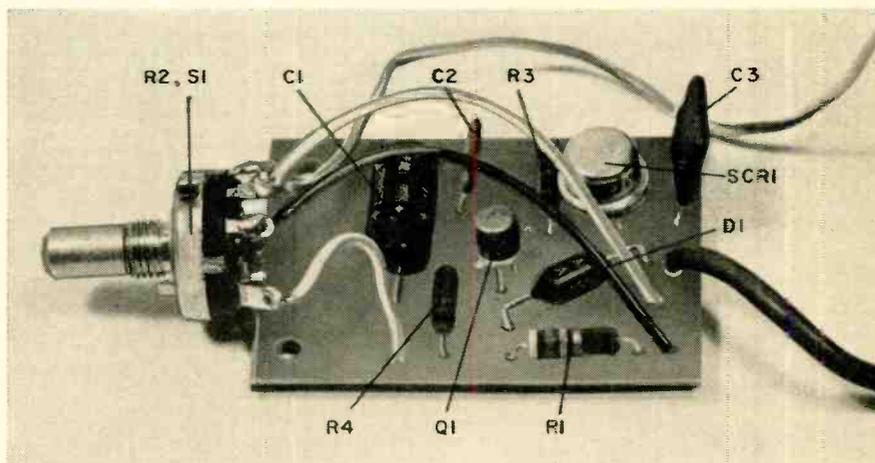


The APC can be built on a PC board or a perforated board for point-to-point wiring.

Fig. 2—For cars with 12-volt positive-ground system. See text for 6-volt operation.

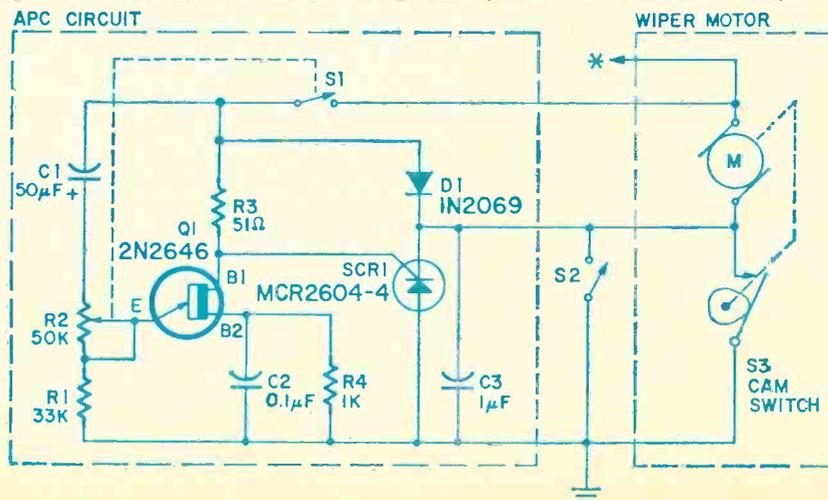

Simple project adds light patterns

BUILD RHYTHM LIGHTS

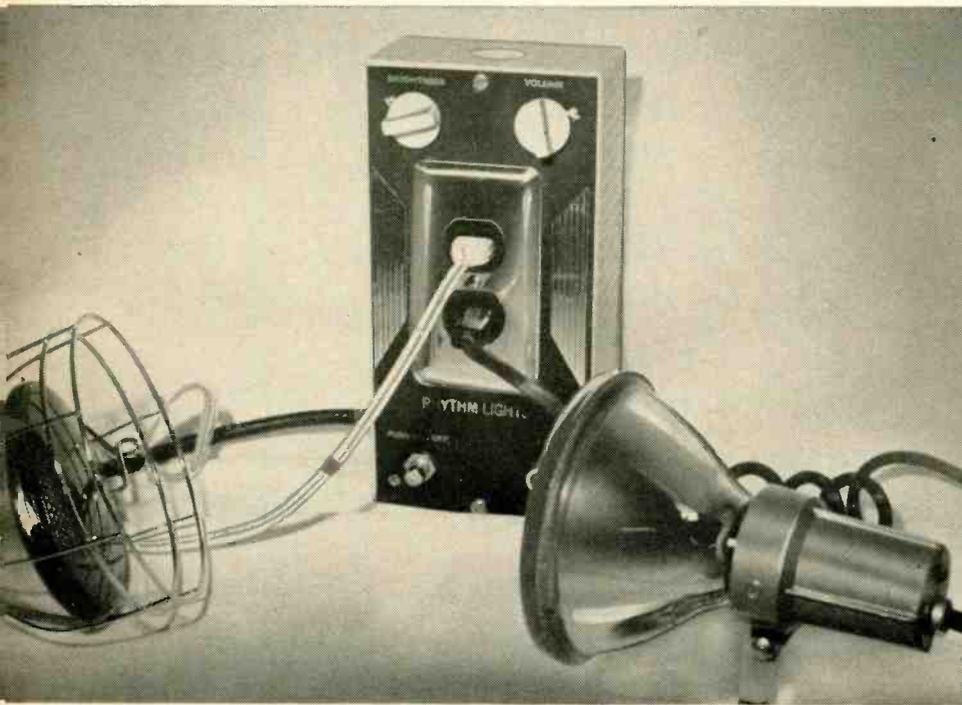


TODAY'S POP MUSIC IS WILD AND EXCITING. Tie into it with a light-and-music show! Put Rhythm Lights near live musical instruments—or radio or hi-fi—and flood lamps will fill the room with color in rhythm with the music.

This sound-to-light converter is all solid-state for trouble-free operation. No special wiring is necessary—just place the unit near the sound and the lights flash dynamically filling the room
(continued on page 71)

PARTS LIST

- C1, C4—500-pF, 150-volt ceramic capacitor
- C2, C3, C5—10- μ F, 12-volt, electrolytic capacitor
- C6, C12—100 μ F, 12-volt, electrolytic capacitor
- C7—2000- μ F, 20-volt, electrolytic capacitor
- C8, C11—0.1- μ F, 150-volt, paper capacitor
- C9—0.047- μ F, 150-volt, paper capacitor
- C10—0.008- μ F, 150-volt, paper capacitor
- D1—1N34-A diode
- D2, D3, D4, D5—Diode, at least 500 mA, 100 piv (Lafayette 19H5001 or similar)
- D6, D8—1N4001 diode
- D7—1N4003 diode
- D9, D10, D11, D12—Diode, at least 1.5 amps, 200 piv (RCA 40267 or similar)
- D13—Pnpn trigger diode, T1-42 or similar
- F1—Fuse, 5 amps, and holder
- Q1, Q2—2N3391 transistor
- Q3—2N669 transistor
- Q4—2N3528 silicon controlled rectifier
- R1—2.2-megohm resistor
- R2—10,000-ohm resistor
- R3, R5—1-megohm resistor
- R4—4700-ohm resistor
- R6—2200-ohm resistor
- R7—100-ohm resistor
- R8—68,000-ohm resistor
- R9—39,000-ohm resistor
- R10—5000-ohm, 8-watt resistor
- R11—10,000-ohm potentiometer
- R12—250,000-ohm potentiometer
- R13—5600-ohm resistor

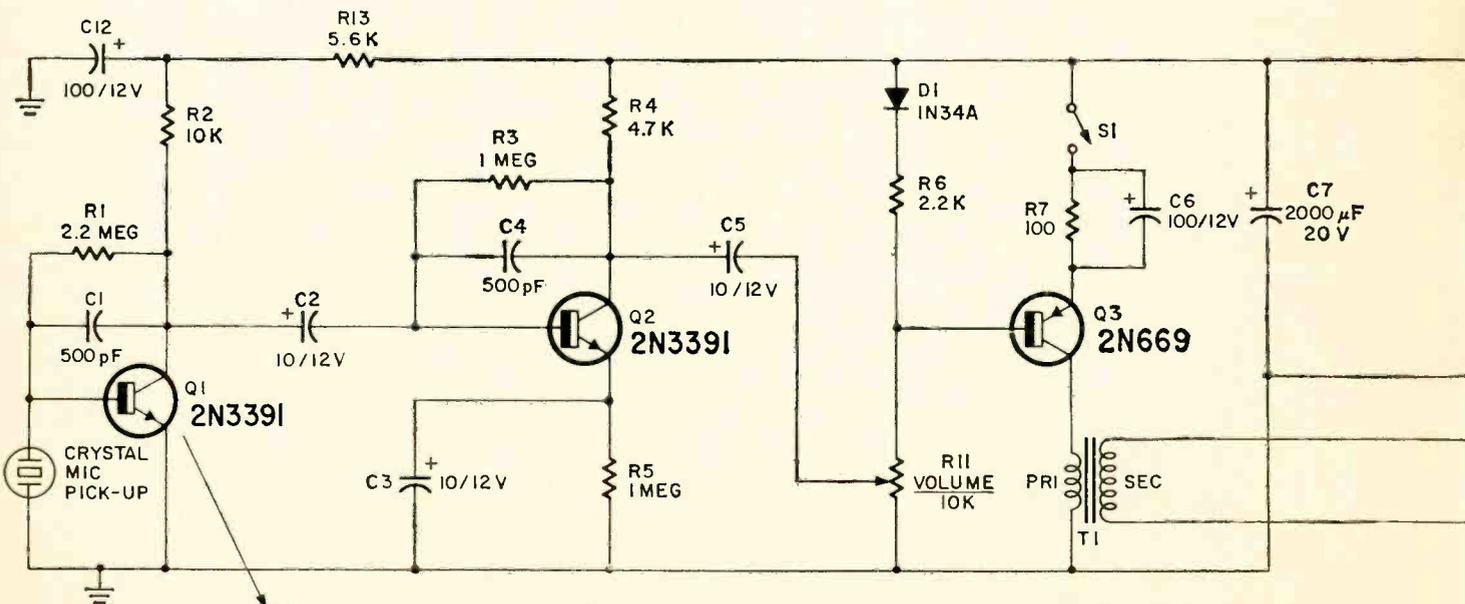

ECB BOTTOM VIEW OF 2N3391 Fig. 1—Transformers isolate the signal and power section's low and high voltages. Transistors Q1 and Q2 may be substituted with similar types, as stage design isn't critical.

to party music By R. T. MONTAN'E

FOR PSYCHEDELIC MUSIC


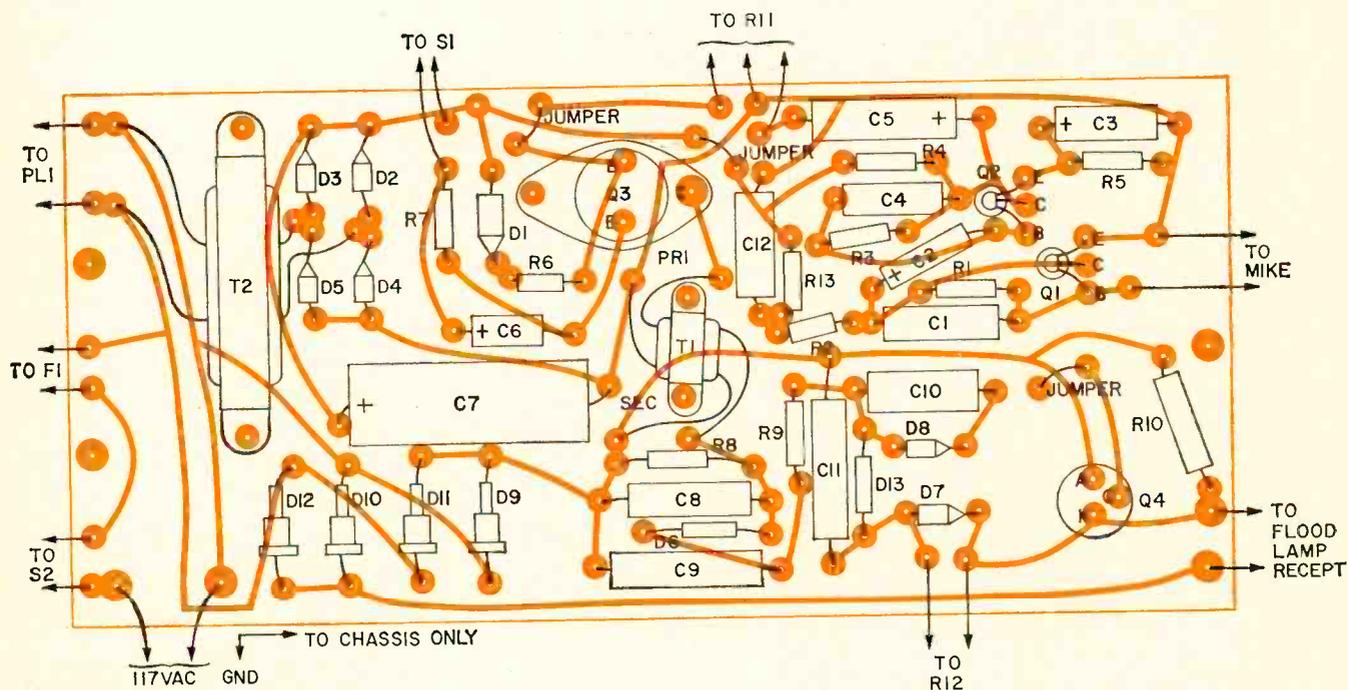


Fig. 2—Lay out parts on the board and solder carefully before mounting board to chassis. Watch electrolytic and diode polarities.

S1, S2—S.p.s.t switches
 T1—Interstage audio transformer, primary 10,000 ohms, secondary 200 ohms (Allied Radio 54E2386 or similar)
 T2—Filament transformer, primary 117 volts,

secondary 12 volts, at least 1 amp (Allied Radio 54B4136 or similar)
 PL1—Neon lamp with series resistor for 117 Vac operation
 MISC—High-impedance crystal microphone;

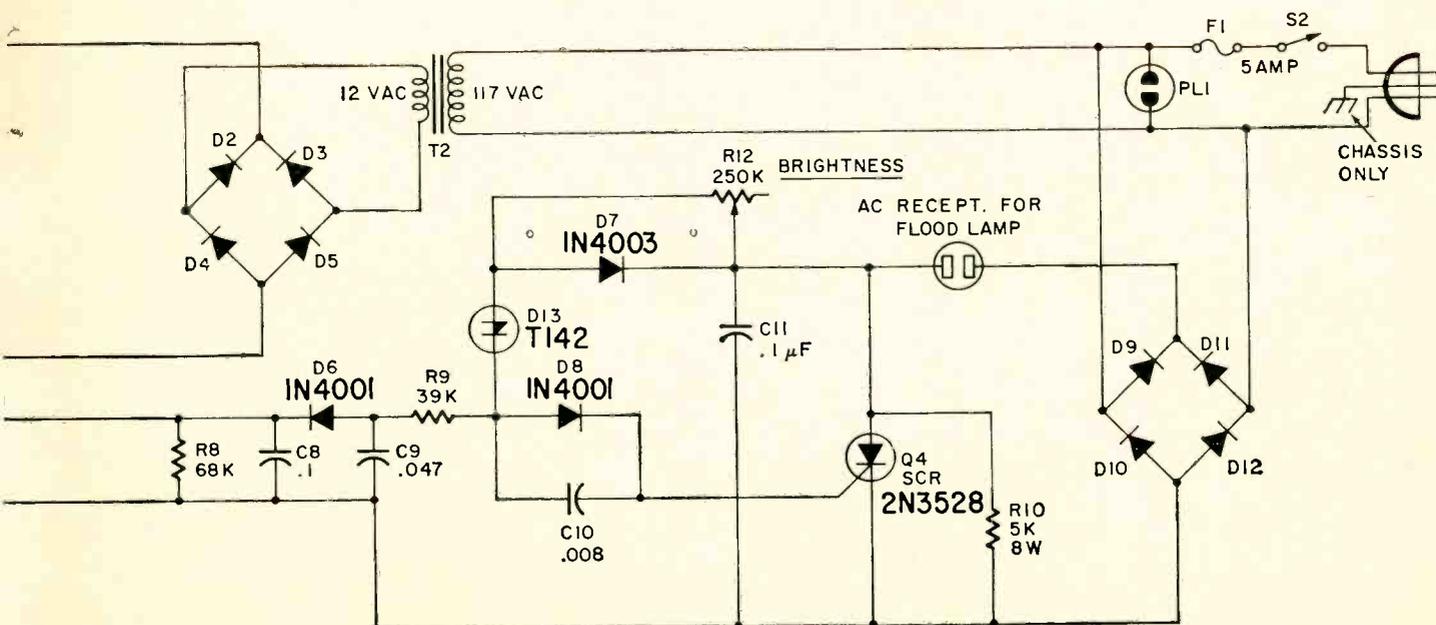5" x 10" x 3" aluminum chassis (Bud AC-404 or similar) with bottom plate (Bud BPA-1591 or similar; 4-2" standoffs; 3-conductor line cord; ac receptacle; hardware and wire.



SOUP-UP YOUR RELAYS

By LYMAN E. GREENLEE

ARE YOU AT YOUR WIT'S END TRYING to find a sensitive relay with husky contacts to complete a pet project? If so, you've probably found that relay sensitivity (rated in milliwatts input per single-pole contact) drops sharply as contact current rating increases. Really sensitive relays with heavy contacts are generally very expensive or not readily available. If this is your problem, don't despair, I may have a simple solution.

You can use an ordinary power relay and multiply its sensitivity many times by using an SCR to drive it. Typically, a relay handling up to 30 amps at 600 volts can be triggered by only 200 μ A at 0.8 volt on the SCR gate. The basic SCR/relay circuits in Figs. 1 and 2 work well, but must be modified to make them immune to power-line transients that are produced when oil burners, air conditioners and similar devices are turned on or off.

In Fig. 1 resistors R1 and R2 form a voltage divider to limit gate

current to a safe value. The SCR, one of G-E's low-cost C106 series, will carry up to 2 amps. This is adequate to handle power relays that switch 30 amps at up to 600 volts. When S1 is closed, the gate is biased on; the SCR conducts on positive half-cycles of the ac input voltage and keeps the relays energized. The SCR stops conducting on the next half-cycle following the opening of S1.

If we add a diode and capacitor as in Fig. 2, we have a self-locking circuit. When S1 is closed momentarily, the SCR fires and keeps the relay energized until released by opening S2. S1 and S2 may be momentary-contact switches with S1 normally open and S2 normally closed.

A locking circuit such as this is useful in alarms and similar devices. Reset (by opening S2) may be either manual or automatic. The value of R3 is selected to clamp the voltage across C1 at about 120 volts dc. R4 is the surge-limiting resistor for D1—a 200-piV, 500-mA silicon diode.

The circuits in Figs. 1 and 2 are okay for experimenting, but are not

practical because they are subject to random triggering by transients. So let's see how we develop a practical, reliable circuit.

Noise-immune circuits

First, in Fig. 3 we add transformer T1 to isolate the relay coil and SCR from the power line. This, in itself, does not eliminate all random triggering, so a filter (R5-C4-C5) is connected in the primary circuit. The drop across R5 is about 20 volts when the relay is energized. Idling or "relay off" current will produce a drop of about 10 volts across R5.

Resistor R4 and capacitor C3 provide additional filtering across the secondary of T1. A NE-2 neon lamp isolates the SCR gate from the triggering circuit. The advantage of using the neon lamp is that the gate cannot be triggered until the lamp is conducting. Thus random pulses below the firing voltage of the lamp cannot trigger the SCR.

Resistor R3 and C2 eliminate any secondary or electrostatic discharge

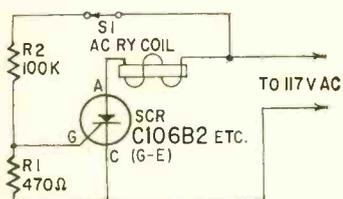


Fig. 1—Basic SCR relay driver. Switch S1 carries only the SCR gate current.


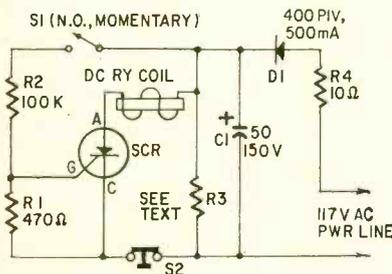


Fig. 2—A locking-type circuit. Closing S1 triggers the SCR and locks-in the relay. Opening S2 releases the relay.

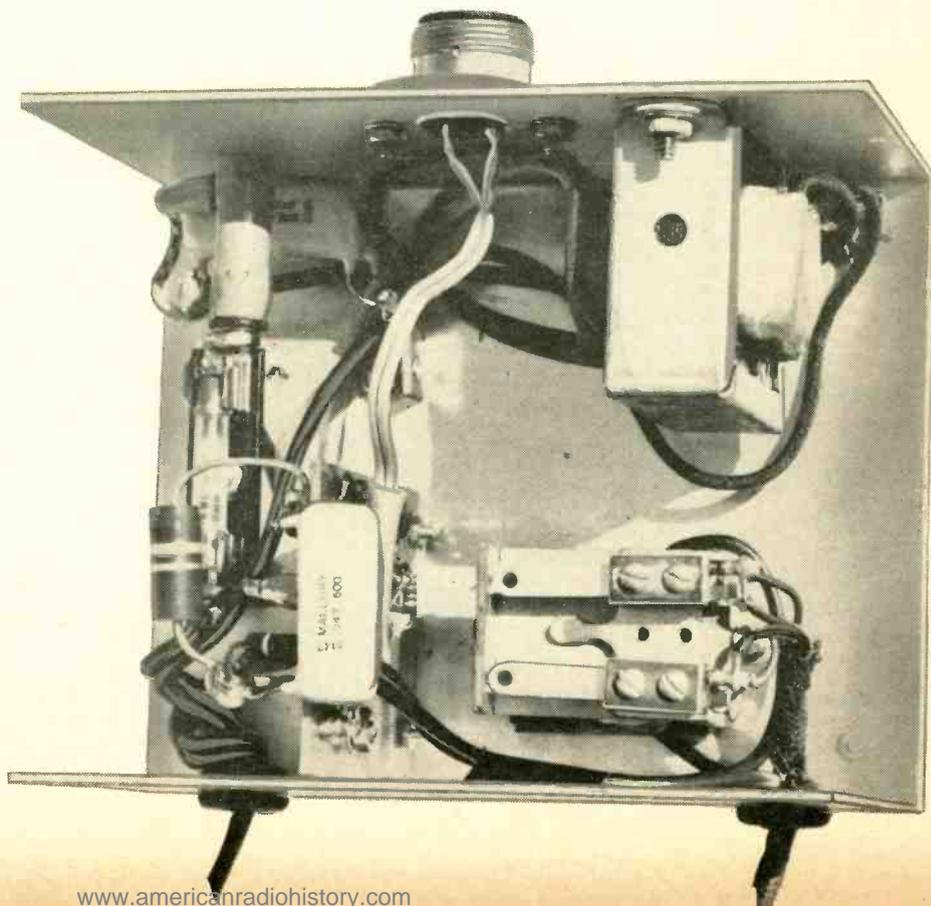A typical SCR/relay combination as in Figs. 3 and 4 fits neatly in a small metal box. The trigger leads run to the switch or LDR through the connector.



with a 200-microampere, 0.8-volt signal

WITH SCR DRIVERS

across the NE-2. An electrostatic charge will lead to false triggering. The optimum value of R3 is around 3.3 megohms, but it may be reduced to as low as 1 megohm, if necessary, to eliminate secondary glow in the lamp.

The stray capacitance of long leads to the tripping contacts (S1) will tend to drive the NE-2 and make necessary the use of lower values for R3. Use the shortest possible length of low-capacitance, low-leakage cable to connect S1 to the circuit. If R3 has to be less than 1 megohm, you will have to move the control circuit closer to S1 or use leads with lower capacitance.

The circuit in Fig. 3 is useful for many relay applications in which the actuator is an on-off switch capable of handling 200 μ A. This includes such low-current devices as meter relays where contact current is limited. Easy to construct, it can be fitted into a 5" x 4" x 3" utility box with room to spare. The relay may be almost any 117-volt ac type with contact combinations handling up to 10 amps. Its contacts may range up to 6-pole double-throw for polarity reversing, line transfer and

other complex switching. Heavier relays may require a larger box.

The C106 SCR will handle up to 2 amps but should be used on an adequate heat sink when used to drive a relay whose coil draws more than about 300 mW.

Parts layout is not critical except for R4 and R5. They get quite hot and must be kept away from the other components, particularly the SCR. The SCR, C2, C3, R2, R4 and the NE-2 are all mounted on a 1 3/4" x 2" piece of linen Bakelite board. Use a heat sink when soldering the SCR into the circuit. A fuse is desirable but can be eliminated if space is needed for a larger relay.

Note that no part of the circuit is grounded or connected to the metal case. If grounded duplex ac receptacles are available, use a three-wire ac cord and ground the case through the third wire in the cord.

If you use a different relay or transformer, adjust the value of R5 for about a 10-volt drop when the SCR is cut off and not more than 20 volts when it is conducting and the relay is

energized. Adjust R4 to balance the load and allow about 100 volts across the coil of the relay when the SCR is conducting.

Using temperature or light control

Figure 4 shows how the circuit can be modified so the relay can be triggered at any predetermined level of light or temperature. Here, the resistance of R2-a, R2-b and the LDR or thermistor in series is equal to 100,000 ohms, the value of R2 in Fig. 3. R2-a is adjusted to compensate for the resistance added by the LDR or thermistor. Potentiometer R2-b is selected to limit SCR trigger current to a safe value at the minimum resistance of the LDR and R2-a in series. R6 controls the sensitivity.

The circuit can be adjusted to provide 200 μ A at 0.8 volt to trigger the SCR at any desired light or temperature level. The 5AJ/NE-86 (G-E) neon lamp has been doped with a radioactive material so it has low firing-voltage characteristics that are independent of light intensity. R-E

Parts List (Fig. 3)

- R1—470-ohm, 1/4-watt resistor
- R2—100,000-ohm, 1/2-watt resistor
- R3—3.3 meg, 1/2-watt resistor
- R4—10,000-ohm 2-watt resistor
- R5—500-ohm, 5-watt resistor
- C2—56-pF 500-volt mica capacitor
- C3, C4, C5—.047- μ F, 600-volt Mylar capacitor
- NE1—NE-2 neon lamp
- F1—1/4-ampere, slow-blow fuse
- T1—Isolation transformer, 117-volt primary, 110-volt 30-mA secondary (Olson Electronics No. T-173 or equal)
- RY1—General-purpose ac relay, 115-volt coil, 10 amp or heavier contacts as needed.
- SCR1—C106-B2 silicon controlled rectifier (G-E)

Additional parts for Fig. 4

- NE1—5AJ/NE-86 (G-E)
- R2-a, R2-b—100,000-ohm miniature pot or as required to match the LDR or thermistor resistance. Be sure that the SCR gate is not overloaded at the minimum setting of R2-a. Select R2-b to keep the minimum circuit resistance at 100,000 ohms.

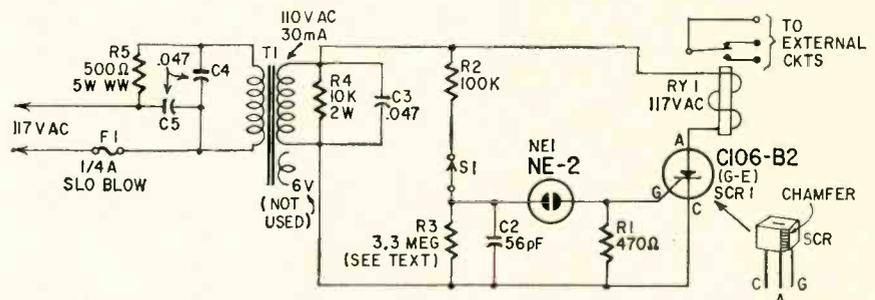


Fig. 3—This improved SCR/relay circuit is extremely sensitive but is immune to noise and transients on the power line. The neon lamp isolates the SCR from the trigger.


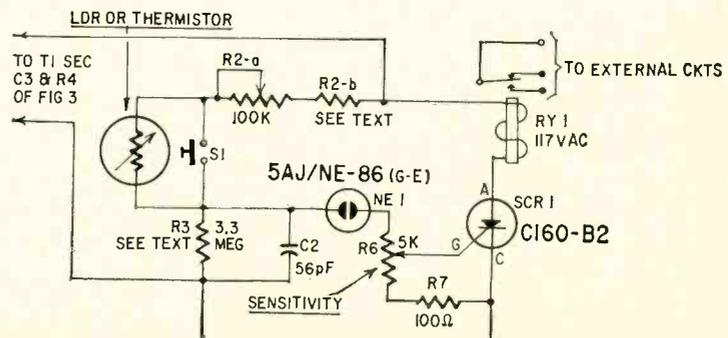


Fig. 4—How Fig. 3 is modified so relay can be controlled by a desired level of light falling on a photocell or by temperature change sensed by a thermistor.

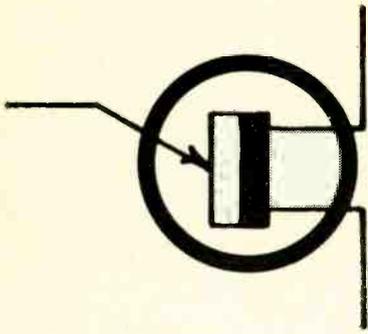

20 UNIJUNCTION

Part II of 2 parts—to acquaint you

IN PART I OF THIS SERIES (JUNE 1968) you were introduced to the unijunction transistor. You saw how it works, and were given 11 applications for it. Here are 9 more. For your convenience, the basing diagram (Fig. 1) and the characteristics (Table 1) of the 2N2646 UJT used in these circuits are shown once again.

Diode-pump counter

Circuit shown in Fig. 2 acts as a frequency divider or counter, but gives a nonlinear staircase output. It has the advantage, however, that counting is almost independent of the shape of the input signal.

With no input applied, Q1 is cut off and C3 charges via R3, C2 and D1; C2 and C3 act as a voltage divider,

and a fixed fraction of the supply voltage appears across C3. When an input pulse is applied, Q1 is driven to saturation and C2 is discharged via Q1 and D2; C3 is prevented from discharging by D1. When the pulse is removed again, C2 again charges via D1 and C3, and places another fraction of the supply voltage on C3.

Thus, at the end of each pulse, the C3 voltage increases by a fixed step (smaller than the previous one) until eventually the UJT fires, discharges C3, and the counting cycle starts over again. Pulse shape has virtually no effect on circuit operation.

The division ratio, $\frac{f_{out}}{f_{in}}$, is roughly equal to $\frac{C2}{C2 + C3}$. The ratio is,

however, affected by a number of variable factors, including operating frequency, so the values of these two components are best found by trial and error. Once components have been selected, the circuit will give stable division over quite a wide range of input frequency variation. Stable division ratios up to 10 to 1 can be easily obtained.

Synchronized frequency divider

Divider shown in Fig. 3 generates precise frequency or timing-interval signals. Positive-going pulses from a 100-kHz crystal oscillator are fed, via C1, to base 2 of Q1. R1 is adjusted so that the UJT locks firmly to an operating frequency of 10 kHz, the 100-

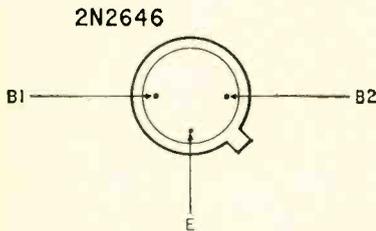


Fig. 1—Base connections of 2N2646 UJT. B2 is electrically connected to case.

Table 1—2N2646 Characteristics	
Emitter reverse voltage (max)	30 volts
Interbase voltage (max)	35 volts
Peak emitter current	2 amps
Rms emitter current	50 mA
Power dissipation (max)	300 mW
Intrinsic standoff ratio (η)	0.56–0.75
Interbase resistance (R_{BB})	4,700–9,100 ohms
Peak-point emitter current (I_{EP}) (max)	5 μ A (1) 25 μ A (2)
Valley-point current (I_V) (min)	4 mA
Case	TO-18
(1) GE	
(2) Motorola	

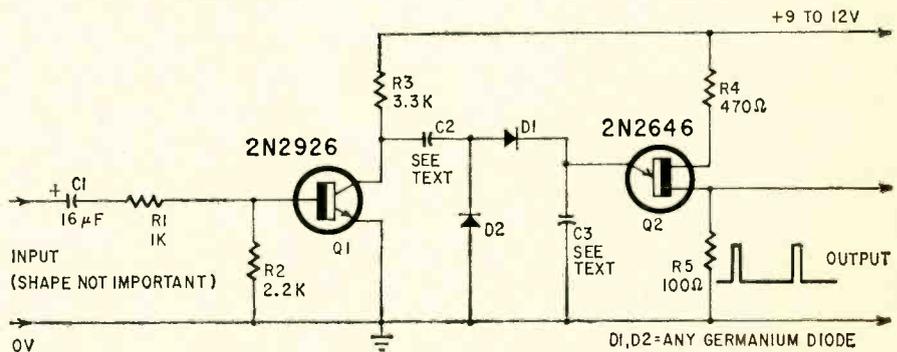


Fig. 2—Diode pump counter.

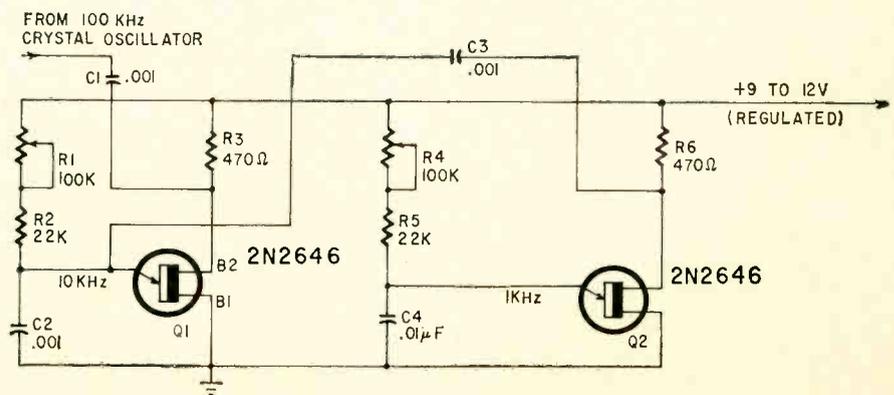


Fig. 3—Synchronized frequency divider.

TRANSISTOR APPLICATIONS

further with this useful solid-state device

By R. M. MARSTON

kHz signals acting as sync pulses. The 10-kHz signal from Q1's emitter is fed to Q2 via C3, and R4 is adjusted so that Q2 locks to an operating frequency of 1 kHz. Thus, the circuit makes available standard frequencies (and timing intervals) of 100 kHz (10 μ sec), 10 kHz (100 μ sec), and 1 kHz (1-msec). Stability is very good if a Zener-regulated power supply is used for this circuit.

Division ratios other than 10 can be obtained by adjusting R1 and R4. Outputs can be taken, via a high-impedance emitter-follower buffer stage, from the emitter of each UJT and from the crystal oscillator.

Wide-range square-wave generators

The unijunction transistor can be used as the heart of a whole range of waveform generators. Figs. 4 and 5 show how it can be used to generate square waves.

In Fig. 4, Q2 and Q3 form an npn bistable multivibrator or divide-by-2 circuit. At the end of each UJT cycle, the positive-going pulse from R4 is fed to the emitters of Q2 and Q3 and causes the multivibrator to change state. Two cycles of the UJT produce a single complete cycle of the multivibrator. The multivibrator output, taken from either collector, is therefore a perfect square wave at half the UJT frequency. The two collector signals are opposite in phase.

Fig. 5 shows the pnp version of the same circuit. In this case, the circuit uses the negative-going pulses from R3 to trigger the bistable multivibrator, but the two circuits are otherwise similar to each other.

It's important to note that in both these circuits C2 and C3 are of equal value — approximately $\frac{C1}{100}$. That is, if C1 is 0.1 μ F, C2 and C3 should be .001 μ F (1000 pF). C2 and C3 should, however, have a minimum value of about 100 pF.

Both circuits (Figs. 4 and 5) will

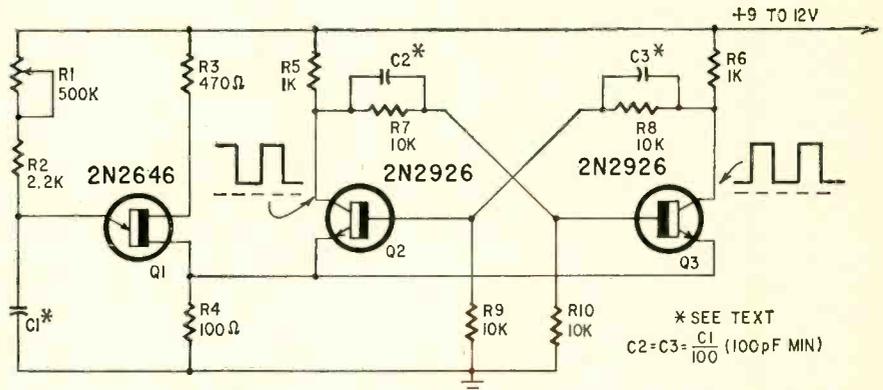


Fig. 4—Wide-range square-wave generator employing npn transistors.

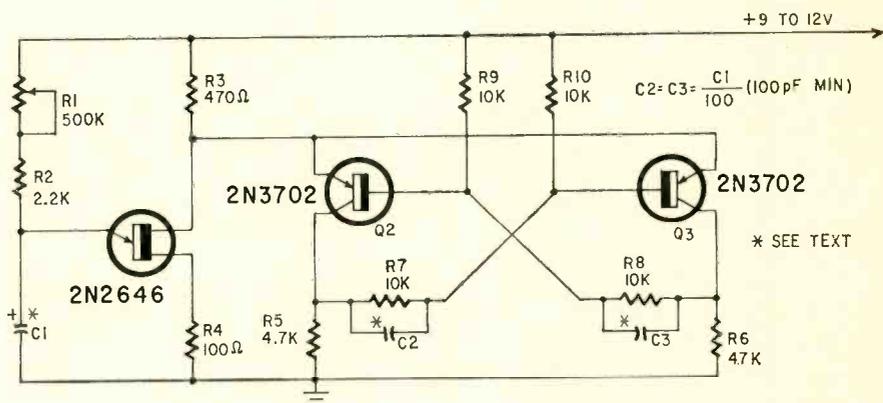


Fig. 5—Pnp transistors in a square-wave generator.

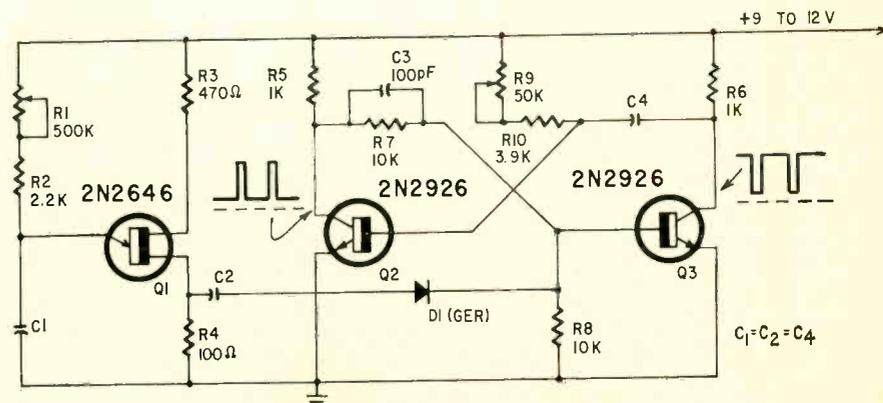


Fig. 6—Variable-frequency pulse generator.

generate square waves over a 100:1 frequency range, using a single set of component values.

Variable-frequency pulse generator

The circuit of Fig. 6 generates a constant-width pulse that can be varied in repetition frequency over a 100:1 range. It may, for example, generate a pulse with a constant width of 500 μ sec, at repetition frequencies ranging from 10 to 1,000 Hz. The actual pulse width can be adjusted, on any particular range, over a 10 to 1 range, i.e., from 50 to 500 μ sec.

In this quite simple circuit, Q2 and Q3 are wired as a monostable or one-shot multivibrator, with pulse width controlled by R9, R10 and C4. The multivibrator is triggered by positive-going pulses fed from R4 to Q3 base via C2 and D1. Thus, repetition frequency is controlled by the UJT, and pulse width by the multivibrator.

Different sets of C1-C2-C4 values are needed for each range of operation, but all three capacitors will usually be of equal value. The main point here is that the maximum period of the pulse must be less than the minimum period of the UJT cycle. Otherwise the pulse will not be ended by the time a new trigger pulse arrives, and stable operation will not be obtained.

Pulse outputs can be taken from either collector, the two outputs being opposite in phase.

Variable on/off-time pulse generator

This circuit (Fig. 7) generates a series of pulses in which the on and off times are independently controlled. Furthermore, each can be varied over a 100:1 range.

The circuit is similar to the square-wave generator of Fig. 4, Q2 and Q3 forming a bistable multivibrator that is triggered by positive-going pulses from R6. In the circuit of Fig. 7, however, two different C1 charging circuits (R1-R2 and R3-R4) are available, and the multivibrator operates diode gates that select the charging circuit that may be used at any particular moment.

Assume that when the power is turned on, Q2 is on and Q3 is off. Q2's collector is at zero volts, so D4 is forward-biased and D3 is thus back-biased. No charge current flows to C1 via R3-R4. Q3's collector is at near full positive supply potential, so D2 is back-biased. D1 is thus forward-biased and C1 charges via R1-R2 only. At the end of this timing cycle, the UJT fires and triggers the multivibrator, so

Q2 switches off and Q3 switches on. D2 is forward-biased and D4 is back-biased, so R1-R2 are cut out of circuit and C1 charges via R3-R4 only. At the end of this new cycle, the circuit goes back to its original state.

C2 and C3 are of equal value and equal to $\frac{C1}{100}$, down to a minimum value of about 100 pF. When C1 is 0.1 μ F, the on and off times of the output pulse can be individually controlled over the approximate range 500 μ sec to 50 msec.

Variable frequency/M-S ratio generator

Figure 8's circuit generates a series of pulses in which both the mark/space (on time/off time) ratio and the frequency can be independently varied over a wide range. If, for exam-

ple, the M-S ratio is set at 9 to 1, the operating frequency can be varied from, say, 10 to 1000 Hz without any resulting change in M-S ratio.

Similarly, if the operating frequency is set at, say, 100 Hz, the M-S ratio can be varied over the range 1 to 100 or 100 to 1 without any resulting change in operating frequency.

Both frequency and M-S ratio can be simultaneously varied, without interaction. This type of generator is used at the transmitter end of analog proportional two-channel remote-control systems, such as the "Galloping Ghost"—a radio control system.

In Fig. 8, Q2 and Q3 form a super-alpha-pair (Darlington pair) emitter follower, and permit a sawtooth output to be taken at low impedance from the R6-R7-R8 chain without affecting the operating frequency of Q1. This sawtooth is then

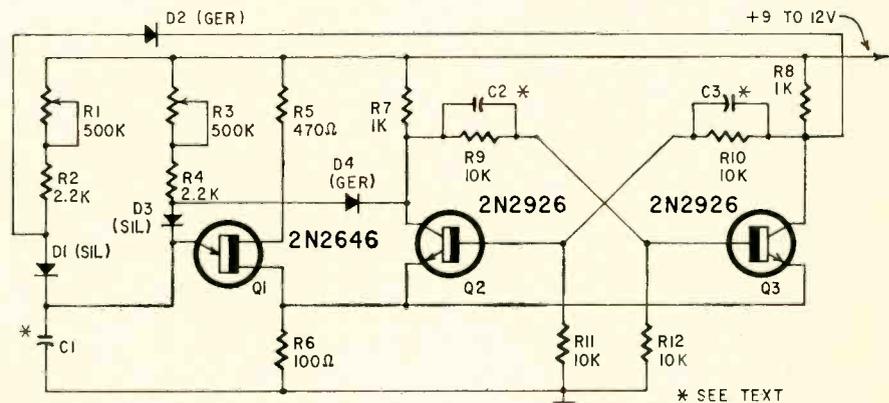


Fig. 7—Variable on/off-time pulse generator.

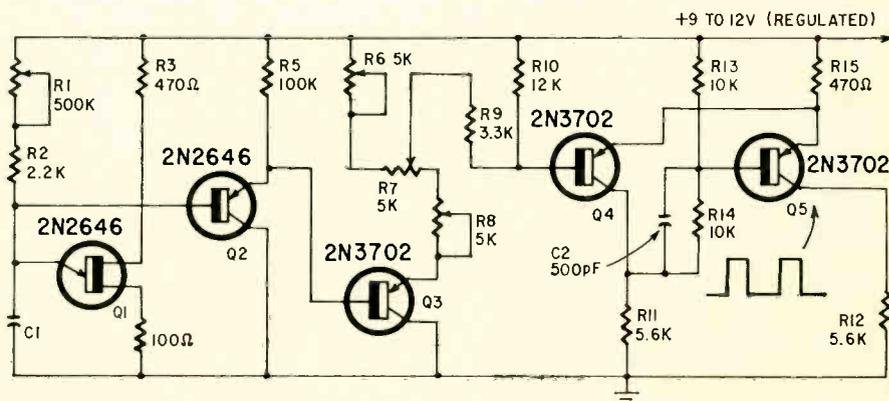


Fig. 8—Variable frequency, mark-space ratio generator.

fed, via R9, to the Schmitt trigger formed by Q4 and Q5. By adjusting R7 the Schmitt can be made to fire at different points on the sawtooth, and so generate different M-S pulse signals at Q5's (or Q4's) collector. R6 and R8 allow the maximum and minimum mark-space ratios to be preset. Different frequency ranges can be selected via C1—as in the case of all UJT circuits given in this article.

Radio control enthusiasts will have noticed that this circuit uses a total of five transistors, compared to the three used in some other pulsers. That's because this circuit is designed to give a total lack of channel interaction—an advantage you don't get with other less-complex circuits.

One-shot lamp/relay driver

For most lamp or relay sequen-

tial operations, where you want switching or delay times of only a few seconds, the unijunction offers no real advantage over conventional transistor circuits. It's only when you want very long sequential periods—ranging from tens of seconds up to several minutes—that the UJT is really useful. Fig. 9 shows just such an application.

This is a one-shot lamp or relay operator. The lamp is normally off, but as soon as you operate a pushbutton it comes on, and stays on for a preset period that can be adjusted from about 4 seconds to 8 minutes. At the end of that period, the lamp switches off and the circuit resets, ready for the next pushbutton operation that you select.

Q2 and Q3 form a bistable multivibrator in which Q2 is normally on and Q3 is off. Thus, Q2's collector is at zero volts, so D2 is forward-biased and

D1 is back-biased. Capacitor C1 is prevented from charging via R1-R2. Q3's collector is at near full positive supply voltage, so no forward bias is applied to Q4, and the lamp is off. (R11-D3-R12 form a voltage divider, and insure that the small voltage at Q3's collector is not enough to turn transistor Q4 on.)

When start pushbutton S1 is momentarily operated, Q2's base is shorted to ground and the bistable multivibrator changes state. Q2 goes off, removing the forward bias from D2. C1 now takes on a charge via R1-R2-D1. Transistor Q3 goes on, drives Q4 hard (via D3-R12) and switches the lamp on. After a preset period, the UJT fires, and the positive-going pulse from R4 is fed to Q2's base via C2 and D4, turning Q2 back on and resetting the circuit to its original condition, with D2 forward-biased and the lamp off.

Only lamps or relays with operating currents less than 300 mA can be used in this circuit. Q4 can, however, be used to drive a power transistor to handle larger currents, so long as the collector current of Q4 is limited to less than 300 mA by a series resistor.

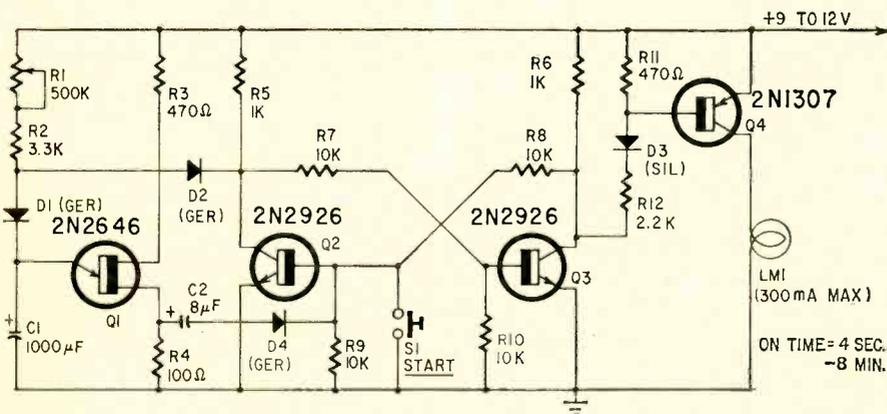


Fig. 9—One-shot lamp or relay driver.

Variable on/off-time lamp flasher

Another sequential UJT lamp-driving circuit is shown in Fig. 10. Here, the on and off times of the lamp can be individually varied over the approximate range of 4 seconds to 8 minutes (giving a maximum possible cycle period of 16 minutes). Operation is repetitive.

The circuit is like the one in Fig. 7, with the addition of the lamp-driving transistor stage given in Fig. 9. Maximum output current is again limited to about 300 mA. The on time of the lamp is controlled by potentiometer R3 and the off time is controlled by potentiometer R1.


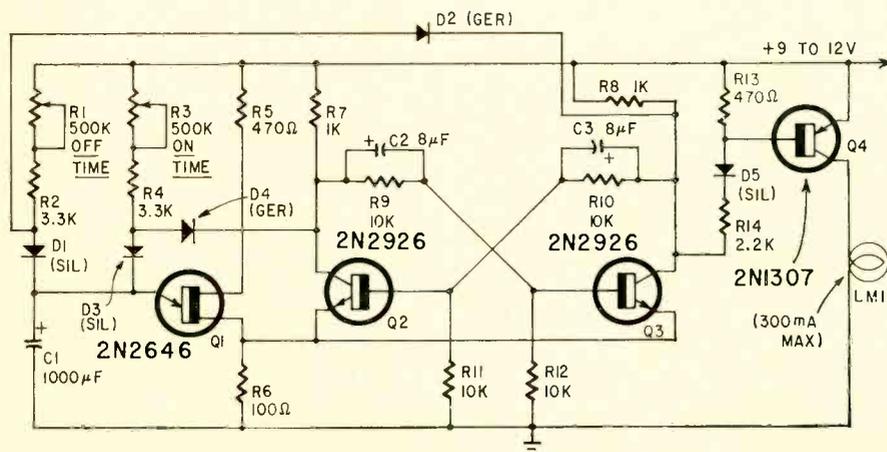


Fig. 10—Variable on/off-time lamp flasher.

Conclusions

If you decide to build any of these circuits, bear a couple of points in mind: Power supplies must be well filtered and reasonably stable. That doesn't mean they have to be fully regulated; it simply means that they may give trouble if they contain a lot of ac, or if you use batteries that are half dead. In most circuits, I've designed the UJT sections to cover a 100:1 frequency range. As a result, control may be coarse; if it's too coarse, wire a 10,000-ohm "fine" control in series with the main potentiometer. If you want a range less than 100:1, increase the value of the fixed series control resistor.

R-E

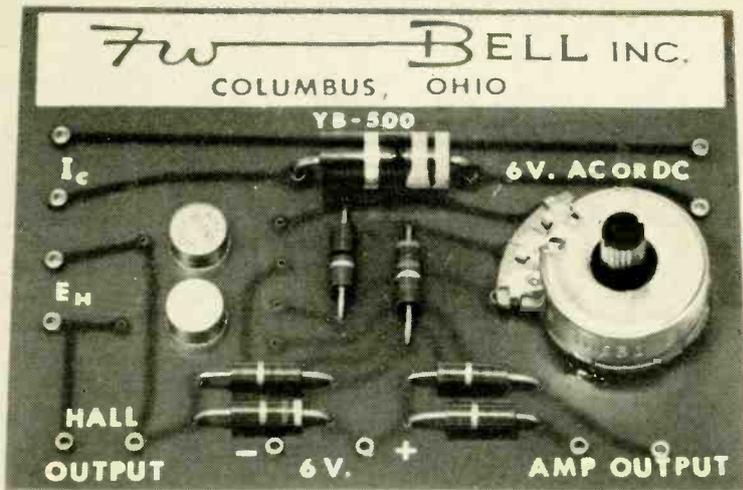

**Introducing the Hall Effect
—a most useful phenomena
for science and industry**

HALL EFFECT IN SOLID

By JOHN POTTER SHIELDS

ELECTRONICS IS RICH WITH MARVELOUS "effects." Many of them, decades old, have remained laboratory curiosities until the time was ripe—until there was a need for them, or suitable materials were discovered to make applications of the effects practical. The thermoelectric effects of Peltier and Seebeck are among the most fascinating. They have been known since the mid-19th century, but practical thermoelectric coolers had to await the coming and application of sophisticated semiconductor materials.

Something similar happened with

the Hall effect. At first poorly understood and considered virtually useless, the Hall effect now has a secure and deserved place in several areas of the electronics industry.

What is the Hall effect?

The whole Hall-effect story started in 1878 with a Mr. Edward H. Hall. He discovered that, when current is passed through a metal strip subjected to an intense magnetic field, a minute voltage is developed along the edges of the strip. Mr. Hall also noted that this rather strange effect is relatively weak in such materials as iron and gold, but much stronger in the

metals bismuth and tellurium.

More recently, it has been found that this effect is much more pronounced in a variety of semiconductor materials, including, for example, silicon, germanium, indium antimonide and indium arsenide.

Figure 1 gives an idea of the basic Hall-effect concept. The Hall-effect device proper is fabricated from a thin slice of semiconductor material to which are attached suitable electrodes and conducting leads. This assembly is encapsulated in a protective coating to protect it from contamination. As shown, the Hall-effect device has four leads. Two are connected to the con-

Fig. 1—Control current and the magnetic field interact to generate a voltage between opposite edges of a Hall crystal.


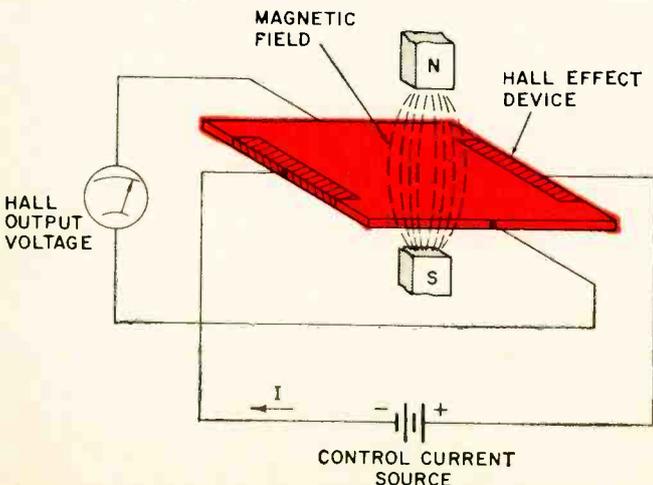


Fig. 2-a—Outside a magnetic field, charge carriers are uniformly distributed in the Hall element and voltage is zero.

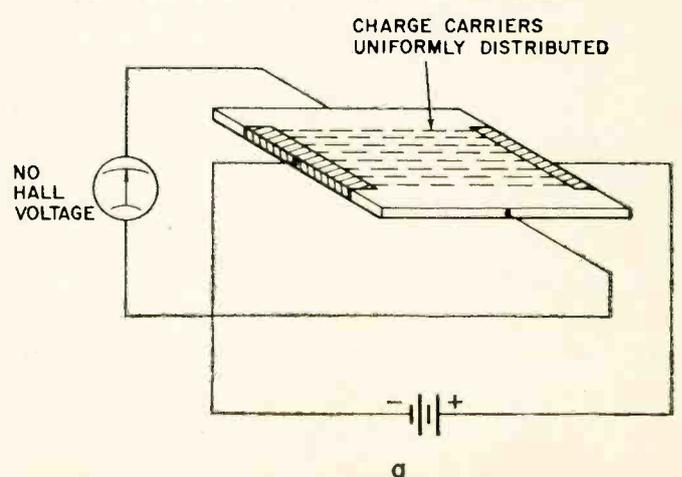

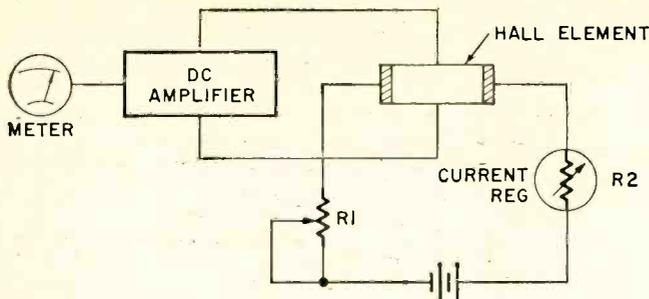


Fig. 3—Basic setup for measuring magnetic field strength with Hall device. As battery ages, R2 regulates current.

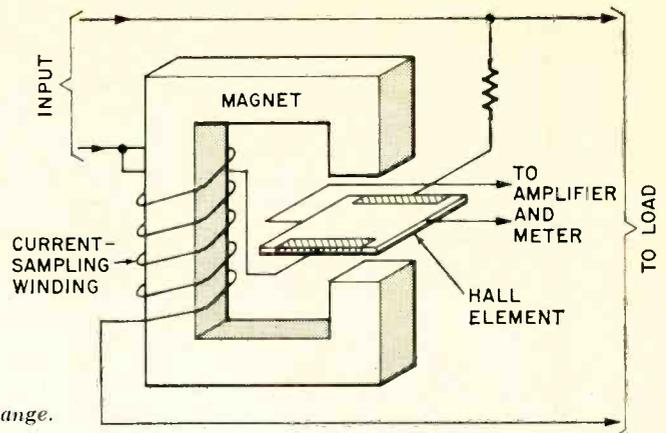


Fig. 4—Hall-effect wattmeter responds to frequencies over a wide range.

control-current source, while the other two leads deliver the Hall voltage.

When the Hall-effect device is placed in a magnetic field and the control current is applied to it, a voltage appears across its Hall-voltage terminals. The amount of Hall voltage developed is directly proportional to the intensity of the magnetic field and the amplitude of the control current. For example, if the magnetic field intensity is doubled while holding the control current at a constant value, the Hall output voltage will double.

Similarly, the Hall output voltage will double if the value of control current is doubled while the magnetic field strength is held constant. Doubling both the magnetic field intensity and control current, the Hall voltage will increase four times, the Hall voltage thus being a product of the magnetic field and control current.

To see more clearly how a Hall-effect device works, let's take a look at Fig. 2, which gives us an "X-ray view" of Hall-effect operation. In Fig. 2-a, no magnetic field is applied to the Hall-effect device. Under these conditions, the control current passing through it

causes a flow of charge carriers, either electrons or holes, down the length of the device. Since no charge carriers collect at the edges of the Hall-effect device, no Hall voltage is developed.

In Fig. 2-b, the setup is the same except that a magnetic field is applied. Notice that the charge carriers are now deflected so that they strike one edge of the Hall-effect device. This causes a difference in potential between its two edges. If we now reverse the polarity of the magnetic field (north pole for south pole and vice versa) the charge carriers will be deflected in the opposite direction, as shown in Fig. 2-c. This will reverse the polarity of the Hall output voltage. A good analogy of this deflection of charge carriers is the cathode-ray tube, in which a beam of electrons is deflected by a magnetic field within the tube.

The Hall output voltage obtainable from a typical Hall-effect device is small—in the neighborhood of 100 millivolts or so with a magnetic field strength of 1000 gauss. Therefore, it is generally necessary to amplify the Hall output voltage.


Now that you are aware of what

the Hall-effect device is and how it operates, just what is it good for? Perhaps its most obvious application is in the measurement of magnetic field intensity. Fig. 3 shows a simple arrangement for this. The Hall-effect element is supplied with its rated control current by the battery. Potentiometer R1 is adjusted to supply the rated control current while current regulator R2 maintains a constant value of control current as the battery ages.


The Hall-voltage output signal is applied to a direct-coupled amplifier, which amplifies the signal and applies it to a calibrated meter. The direct-coupled amplifier is generally a balanced (differential) type, so that in the absence of a magnetic field the slight residual Hall voltage can be zeroed out, and the meter will be deflected only when the Hall-effect device is in a magnetic field. There are, of course, more complicated Hall-effect magnetic-field measuring arrangements, but the basic principle just described is generally followed.

The Hall-effect wattmeter is another Hall-effect device. The Hall-effect wattmeter has an advantage over

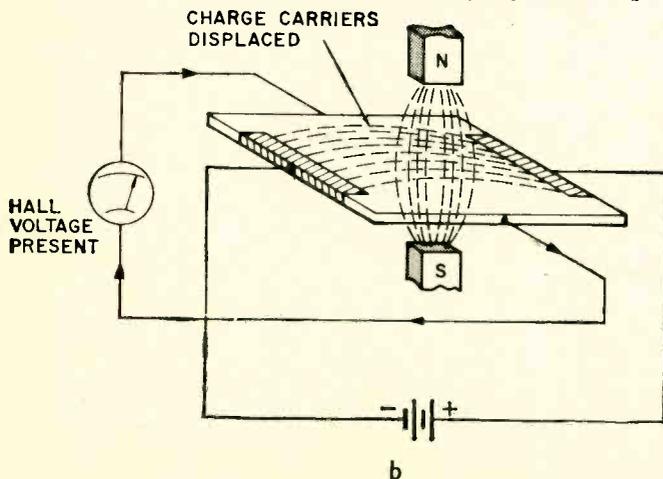A magnetic field perpendicular to plane of the Hall element (b) deflects charge carriers, producing a potential difference



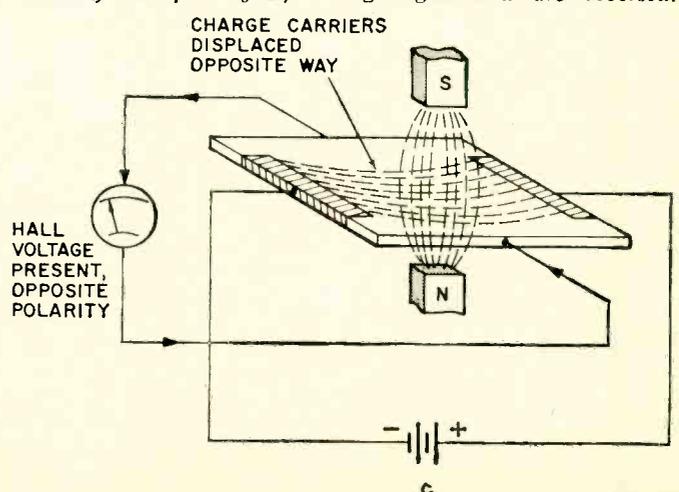ence between opposite edges. When the magnetic poles are reversed, the polarity of voltages generated are reversed.



conventional direct electromagnetic-movement type wattmeters in that it will respond equally well to a much wider range of frequencies (for example, 10 to 100,000 Hz). Fig. 4 shows the basic arrangement of the Hall-effect wattmeter. As you can see, the Hall-effect device is placed between the pole pieces of an electromagnet whose winding is in series with the load to which the wattmeter is connected. The Hall-effect element's control current is derived directly from the supply voltage through a current-limiting resistor. By this hookup, the element's control current is proportional to the supply voltage while the magnetic field applied to the element is proportional to the load current. Since the Hall output is the product of the applied magnetic-field intensity and control-current intensity, its value indicates the power consumed by the load: $\text{power} = \text{voltage} \times \text{current}$.

Metal detector

Figure 5 shows how the Hall effect may be applied to detect ferrous (iron and steel) objects. This type of metal detector, while sensitive only within about an inch, is nevertheless very useful as a ferrous-object counter, etc. It responds to both stationary and moving ferrous objects and, unlike photocell detectors, can operate in cloudy atmospheres which would disable photocell systems.

As you can see from Fig. 5, the Hall-effect element is mounted with a permanent magnet in a small U-shaped assembly. When a ferrous object comes close to the open ends of the U, it shortens the magnetic path between the ends of the U. As a result the magnetic field applied to the Hall element is increased. This in turn produces a larger Hall output voltage, which is amplified and can then be used to energize a relay or as a electromechanical counter.

The Hall effect can also be used to measure extremely small mechanical movements. As shown in Fig. 6, the Hall-effect element is mounted midway between two small permanent bar magnets. In this position, there is minimum Hall output voltage from the element, because magnetic fields of equal strength and the same polarity (north-north) are on each side of the Hall element. If the Hall element is displaced to one side, there will be a stronger magnetic field on one side of the Hall element and a Hall output voltage will be generated. If the element is moved to the opposite side of center, a Hall output voltage will also be generated, but of opposite polarity. Thus, this arrangement will register the amount and the sense of the movement.

As shown in Fig. 7, the Hall effect can also be used for current measurement. As you know, any conductor carrying an electric current has a magnetic field around it. The intensity of the field is proportional to the current strength. By placing the Hall element in the gap of a flux concentrator (a device which concentrates a magnetic field into a small area) placed around the conductor, the conductor's magnetic field will be applied to the

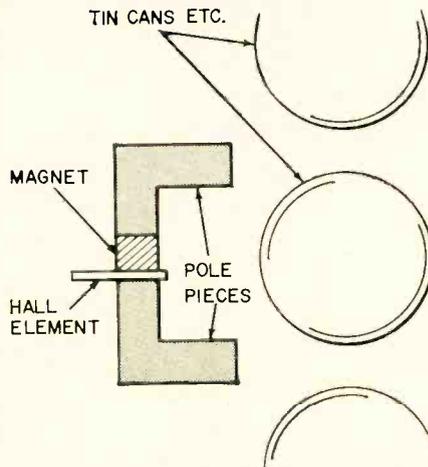


Fig. 5—Sensitive to changes in magnetic flux, the Hall device is useful for counting ferrous objects such as beer cans.

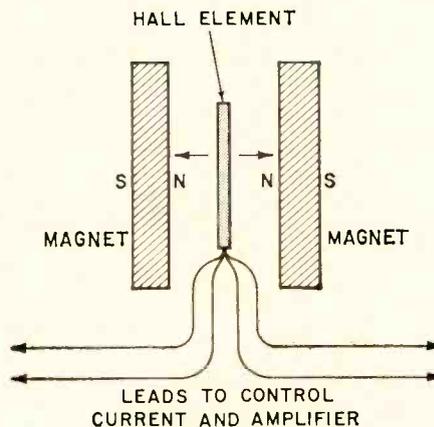


Fig. 6—Minute movements of Hall device or magnets can be detected and measured.

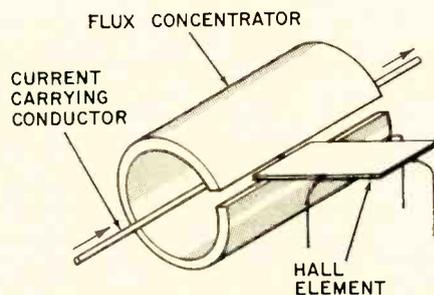


Fig. 7—Magnetic field around conductor (or ion beam, see "Some Commercial Applications") is concentrated on Hall device and the output is measured as current.

(north-north) are on each side of the Hall element. The Hall output voltage will be proportional to the strength of the magnetic field around the conductor, which, in turn, is proportional to the current flowing through the conductor. The Hall output voltage is amplified and applied to a meter calibrated in amperes or milliamperes.

There are other useful applications for the Hall-effect, but the ones we've mentioned are probably the most common.

Experimenting with the Hall effect

Now that you have a good understanding of the Hall effect and how it is used, you might like to try putting it to practical use.

You will need a Hall-effect element. An inexpensive source is the F. W. Bell Co., 1356 Norton Ave., Columbus, Ohio 43212. I used one of Bell's BH-700 Hall-effect elements in all the following experiments. It is available direct from the manufacturer for \$10.75.

To boost the low Hall output voltage obtained from the Hall-effect element, a dc amplifier is required. There are, of course, a number of circuits that can do the job, and the simple differential (balanced) transistor amplifier shown in Fig. 8 will do the job nicely. This circuit is identical to that of the completely packaged printed-circuit amplifier available from the F. W. Bell Co. as part of their Hall Pak Kit. The kit, available for \$21.95, also contains one BH-700 element, two small bar magnets and an instruction booklet with applications.

The amplifier can be powered by a 9-volt transistor-radio battery, with a 6-volt lantern battery supplying the Hall control current. The output of the amplifier can be applied to either a vtvm with a low range of 5 volts or less, or to a 100- μ A meter. Now, on to the experiments.

Measuring magnetic field strength

With the element, batteries and amplifier connected as shown in Fig. 8, apply power to the amplifier and control current to the Hall element. With no magnetic materials near the Hall element, adjust the amplifier's balance control, R1, for a mid-scale meter reading. Bring a small permanent magnet near the Hall element. The meter deflects, indicating the presence of a Hall output voltage from the element. As the magnet is moved closer to or farther from the Hall element, the Hall output voltage will vary proportionally, as indicated by the meter. Notice that the direction of meter movement

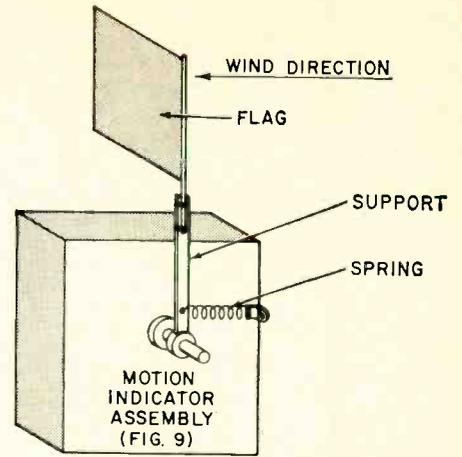
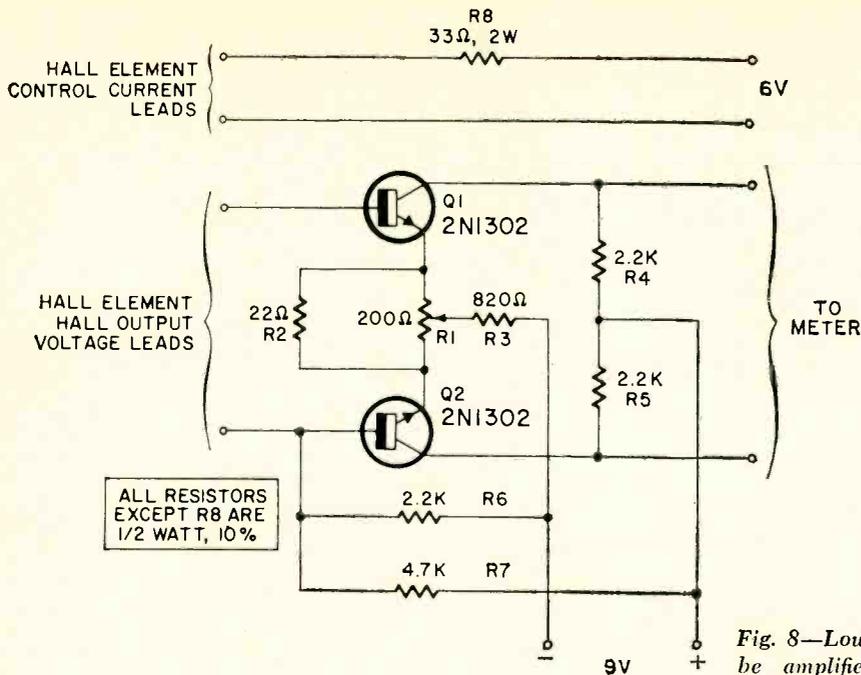


Fig. 10—Using the shaft-position indicator (Fig. 9) to show wind velocity.

Fig. 8—Low output voltage from Hall-effect element can be amplified with this differential amplifier circuit.

is determined by the polarity of the magnetic field.

A noncontacting position indicator

Here's a Hall effect project for which you can find a number of applications. Basically a direction-sensing rotational-motion indicator, it can be used as a wind-speed indicator, a liquid-level indicator, for "electronic scales," or as a source of low-frequency ac signals, to name but a few.

Figure 9 shows the setup. A small permanent-magnet rotor (type DM-662, Dura Magnetics, 5354 Whitford Rd., Sylvania, Ohio, 43560; \$1.45) is mounted on a shaft supported between two panel bearings so that it rotates freely when the extended portion of the shaft is turned. A BH-700 Hall-effect element is mounted approximately $\frac{1}{16}$ " from the edge of the rotor, as shown in Fig. 9. When the shaft is rotated, the rotor edge moves past the Hall element, generating a

Hall output voltage proportional to the magnetic field intensity at the edge of the rotor. The Hall output voltage will vary from a maximum negative value, decrease to zero, then rise to a maximum positive value. The polarity and amplitude of the Hall output voltage will depend on the position of the shaft.

This arrangement is better than devices such as a potentiometer-type position indicator, because there is no wiper to wear down a wire or carbon resistance element. Also, there is less friction on the rotating shaft and less torque is required to turn it.

Now let's put our little gadget to several practical uses. Fig. 10 shows the position indicator as a wind-speed gage. The shaft of the indicator is fitted with a small clamp to which is attached a metal flag. A spring is attached to the bottom of the flag support. The spring returns the flag to its rest position when no pressure is applied to the flag. Spring tension is ad-

justed so that the rotor is turned approximately 45° when there is maximum wind pressure.

The differential amplifier is connected to the Hall output-voltage leads of the element. With power applied to the amplifier, its balance control, R1, is adjusted for a zero meter reading when the flag is at rest. Moving the flag with a finger should cause the meter to read upscale. If the meter reads backward, simply reverse its leads for correct polarity.

To calibrate the meter scale, take it to a clear spot outdoors. Check with your local weather bureau to obtain the current wind speed, and adjust the indicator's spring tension to get an appropriate meter reading. By "appropriate," I mean a half-scale meter reading for a 50-mph wind, quarter-scale reading for 25 mph, or less for lower velocities.

Figure 11 shows how the position indicators can be used to furnish low-
(continued on page 93)

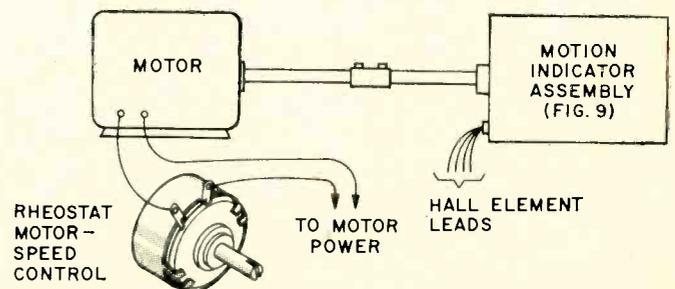
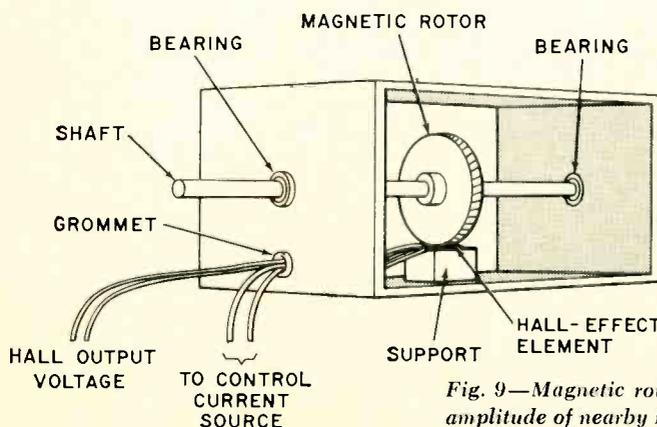


Fig. 11—Spinning shaft in Fig. 9 generates alternating voltage.

Fig. 9—Magnetic rotor supported on freely rotating shaft changes polarity and output amplitude of nearby Hall element. Setup can be used to sense direction or indicate speed.

TV INTERFERENCE

How to identify and cure TVI from adjacent channels

By **MATTHEW MANDL**

CORRECTLY ADJUSTED I. F. TRAPS ARE vital to proper operation of a TV receiver. They help shape the i.f. response curve, eliminate interference from adjacent-channel stations and prevent the i.f. carrier of the station being received from causing interference (sound bars) in the picture.

In most areas around the coun-

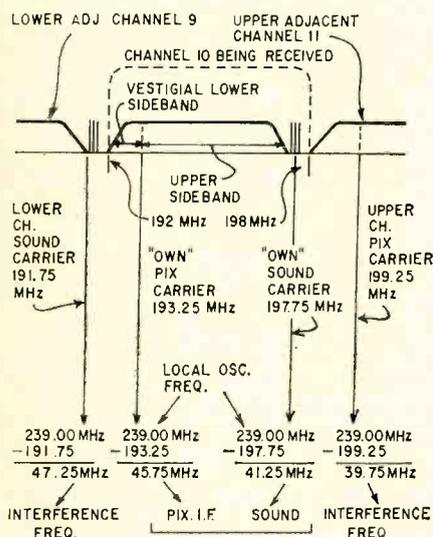


Fig. 1—Distribution of other signals in and around TV channel 10. The intermediate and interference frequencies are identical on all other television channels.

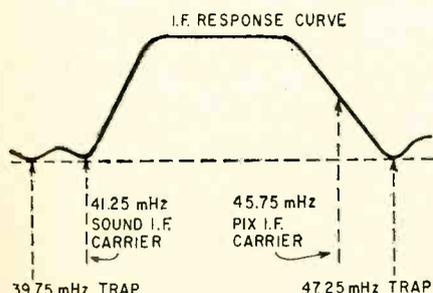


Fig. 2—Typical TV i.f. response curve showing the carrier and trap frequencies.

try, adjacent-channel traps are probably the most neglected of all TV circuits. Adjacent channels are not assigned to two stations in any one area, so there is no continuing problem of adjacent-channel interference.

For the purpose of this article, adjacent channels are those with no separation between the upper limit of one channel and the lower limit of the next channel above it. For example channel 2 (54–60 MHz) and channel 3 (60–66 MHz) are adjacent channels. Channel 4 (66–72 MHz) is the upper adjacent channel to channel 3 but channel 5 (76–82 MHz) is not the upper adjacent channel to channel 4 because there is a 4-MHz gap between the upper end of channel 3 and the lower end of 4.

Complaints of interference are common when portable TV sets are taken into an area between two metropolitan TV centers that have stations on adjacent channels. Sometimes the complaints are blamed on automobile ignition noise or other man-made interference. While these may be contributing factors, adjacent-channel interference is often the culprit and should not be ruled out.

However, the problem situation is equally serious on console-type sets in "midway" areas or when a CATV system brings in adjacent-channel stations from distant areas. On interference complaints, always check the traps, not only to minimize interference, but also to make sure that a mistuned trap is not affecting the overall response curve and cutting down on fine detail in the picture. This happens when a trap is mistuned and falls within the i.f. bandpass curve.

Why traps?

An understanding of why traps are necessary will help you diagnose symptoms. On both vhf and uhf channels the local-oscillator signal in the tuner heterodynes (mixes) with the incoming sound and picture carriers to produce the sound and picture i.f. sig-



Fig. 3—Herringbone pattern superimposed on the picture is result of sound interference from the lower adjacent channel.

nals. If adjacent channels produce reasonably strong signals in the area, their sound and pix carriers can ride into the tuner and also mix with the local oscillator. The result is the production of spurious signals which ride through the video i.f. stages and produce interference in the form of bars, herringbone lines and double images. At the same time the desired station's own sound i.f. signal must be trapped to prevent it getting to the picture tube and producing horizontal bars.

The entire mixing process is shown in Fig. 1 for channel 10 as an example. Here, the channel-10 picture carrier of 193.25 MHz mixes with the local-oscillator frequency of 239 MHz to produce the picture i.f. of 45.75 MHz, which is now standard with almost all receivers.

Channel 10's sound carrier of 197.75 MHz also mixes with the local-oscillator frequency of 239 MHz, and the result is the 41.25-MHz sound i.f. carrier. Note, however, that the lower adjacent channel (9) has its sound carrier near the start of the channel-10 picture carrier. If this lower adjacent-channel sound carrier mixes with the local oscillator the result is a signal with a frequency of 47.25 MHz. Similarly, if the upper-channel picture carrier mixes with the local-oscillator frequency, an interference signal is produced, now having a frequency of 39.75 MHz.

The tuner operates the same way when turned to other channels. The channel-3 picture carrier, for instance,

TRAPS SIMPLIFIED

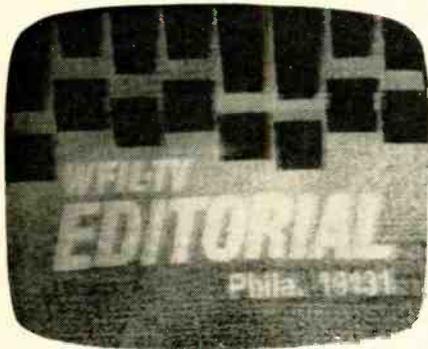


Fig. 4—TVI from upper adjacent channel results in "floating" background picture. TVI blanking produces framing lines.

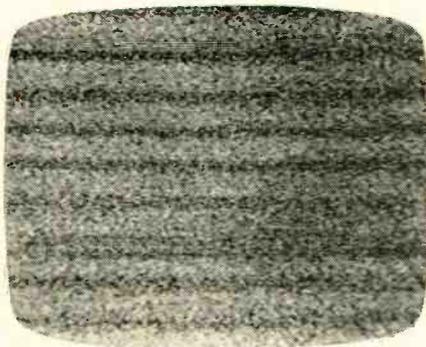


Fig. 5—Interference of faint sound bars can be traced to adjacent TV station by tuning the set toward next higher channel.

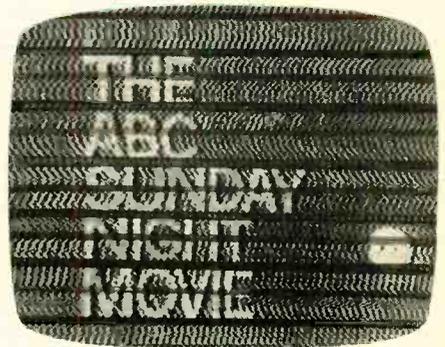


Fig. 6—Multiple interference. Herringbone pattern and horizontal bars are due to sound and lower channel traps.

is 61.25 MHz, and now the local oscillator is 107 MHz. When these two mix, the resultant is again a 45.75-MHz pix i.f. Note the trap frequencies which result when channel 3 is tuned:

107.00 MHz local oscillator at channel 3
 67.25 MHz channel-4 picture
 39.75 MHz interfering signal

107.00 MHz local oscillator at channel 3
 59.75 MHz channel-2 sound
 47.25 MHz interfering signal.

Misadjusted traps can also interfere with the i.f. bandpass. Fig. 2 is a typical i.f. response curve showing the dips which result with properly tuned traps. The picture i.f. is higher than the sound i.f. due to the mixing process when the set oscillator is higher in frequency than the incoming signal. Hence, the lower adjacent-channel trap is *higher* in frequency than the upper adjacent-channel trap, as was also shown in Fig. 1.

If the 47.25-MHz trap is tuned too low in frequency it will put a dip on the right slope of the response curve, affecting fine detail and crispness. Similarly, if the 41.25-MHz sound trap is shifted higher in frequency, it will cut into the left-hand slope of the curve, attenuating low video frequencies and causing large objects in the television picture to appear smeared.

In solid-state portable receivers, the bandpass determines how many

traps are used. Some receiver designs call for a 3-MHz or 3.2-MHz bandpass. This is sufficiently narrow to permit elimination of all traps except perhaps the 47.25-MHz lower adjacent-channel trap. If a wider bandpass is used, all three traps are necessary for best results.

Thus, with standard i.f.'s of 45.75-MHz picture and 41.25-MHz sound, the traps will be 41.25 MHz, 39.75 MHz and 47.25 MHz. On rare occasions, however, a special trap may be used where the receiver is found to be susceptible to a specific interfering frequency. This special trap may have a frequency of 37.5 MHz instead of the usual 39.75 MHz. Such a change from the normal is usually indicated on the schematic of the television receiver in question.

Symptom identification

Lower adjacent-channel interference is shown in Fig. 3. Note the herringbone pattern. The constant change of the interfering signals shifts and wiggles the lines constantly.

Interference from the upper adjacent channel causes the interfering picture to be visible, as in Fig. 4. With the interfering picture not properly synchronized, faint "framing" lines may be visible as the vertical and horizontal blanking of the interfering signals shifts across or up the screen. The phasing may be such that the blanking bars appear white against a dark background on the TV screen.

The fine-tuning control can be adjusted to favor the interfering station to accent symptoms and make identification easier. If very faint shifting bars are visible, tune toward the upper channel and note if the interference increases. Similarly, for very faint herringbone lines, shift the fine tuning toward the lower adjacent channel to see if the lines become more visible.

If the 41.25-MHz sound trap is not adjusted, you will see horizontal bars that change with sound intensity and frequency. The sound bars will not be evenly spaced nor will they stay in one position for any length of time. If the sound carrier produces a stronger signal than the video, you may see faint sound bars (Fig. 5) and not the video. Sound bars on weak stations are a positive indication of the need for trap adjustment.

When both the lower adjacent-channel trap and the sound trap (41.25 MHz) are maladjusted, multiple interference patterns may result, as shown in Fig. 6. Such multiple symptoms may not occur for each channel tuned in because of frequency gaps between some stations. Channels 4 and 5, for instance, are separated by 4 MHz; channels 6 and 7 by 86 MHz and channels 13 and 14 by over 200 MHz.

Trap circuits

In tube-type receivers, traps were often found in various sections of the i.f. amplifiers (to minimize loading effects). Because of the low-impedance

characteristics of transistors, however, all traps can be included in the input to the first video i.f. amplifier. In many cases a trap consists of a series capacitor and variable inductor, as shown for the solid-state Sylvania AO7-1 receiver of Fig. 7. A series-resonant circuit has a low impedance for the signal to which it is tuned, hence shunts such an interfering signal. The complete trap circuit consists of C1 and slug-tuned L1. Inductor L2 and C2 are not part of the trap circuit, but comprise part of the i.f. resonance tuning.

Note the low value of R1, the series isolating resistor. Where multiple traps are used, several such low-value resistors will be found in the solid-state systems. If traps do not function, the fault is rarely with such resistors or associated parts, but rather with the slug-tuning mechanism.

Full trapping is used in the Airline 1967-A receiver shown in Fig. 8, where L1, L2 and L3 are slug-tuned coils. Transformer T1 is used between the tuner input and the base of the first picture i.f. stage using an npn transistor.

Some receivers have two traps tuned to the same frequency to provide maximum interference reduction. An example of this is the twin 47.25-MHz traps (Fig. 9) in the Magnavox T908 chassis. Here, a series-resonant 47.25-MHz trap (L2-C2-C3) is connected across the tuner output to shunt the unwanted signal to ground. In addition, a parallel-resonant absorption-type trap (L3-C1) is coupled to i.f. input coil L4 to "suck out" the interference frequency. Some sets use two traps for 41.25-MHz sound rejection.

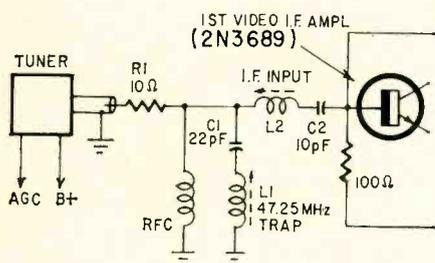


Fig. 7—i.f. input circuit of a Sylvania AO7-1 solid-state TV. Trap C1-L1 is used to reject adjacent-channel sound.

Fig. 8—i.f. input of a receiver with full trapping. The Airline GEN-1967-A set has i.f. traps for adjacent-channel sound and video and for accompanying sound.

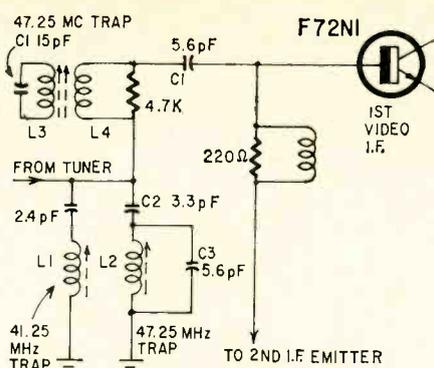
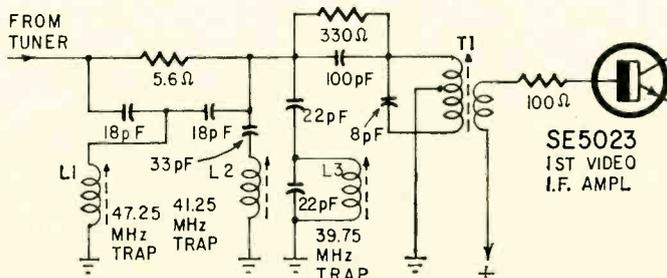


Fig. 9—The Magnavox T-908 has a series-resonant shunt trap and a parallel-resonant absorption trap to obtain better adjacent-channel signal rejection.

tion. The Magnavox T908 chassis does not have a 39.75-MHz adjacent-channel video trap.

At first glance, trap L2-C2-C3 appears to be a parallel-resonant circuit coupled to the i.f. circuit by C2. If this were the case, it would boost the 47.25-MHz signal it is intended to attenuate. However, the parallel-resonant circuit L2-C3 is tuned to some frequency higher than 47.25 MHz so it appears as an inductor at all frequencies below resonance. Thus L2-C3 appears as an inductor in series with C2. This series-resonant combination can be tuned to the desired frequency (47.25 MHz) by adjusting the slug in the coil.

Adjustments

A trap can usually be adjusted without test equipment by watching the screen while slowly turning the trap tuning slug clockwise or counterclockwise. Initially try to determine which type of interference is present and adjust only the appropriate trap. Check results for several stations and for slight variations of the fine-tuning control.

If meters are used, a vtm can be placed across the video detector output and a signal injected into the tuner or the first i.f. stage. The signal frequency should correspond to that of the trap. In such procedures the agc line should have a fixed bias applied

(2 or 3 volts, depending on the average bias for the receiver). The trap is then tuned for a minimum reading on the vtm. It is very important that the signal used for trap adjustments be as accurate as possible.

Sometimes adjacent-channel interference cannot be eliminated from receivers having only a single trap. The most likely causes are poor i.f. alignment and improper antenna orientation. If the antenna checks out all right, use a sweep and marker generator to realign the stages to obtain the curve recommended in the receiver service notes. If the i.f. bandpass is too wide, gain will be down and adjacent-channel interference will be difficult to eliminate. With proper realignment, there should be greater contrast and less interference.

What about color sets?

Trap adjustment procedures are the same in solid-state color receivers. Color sets have the full quota of traps because of the wider i.f. bandpass needed to handle color signals. Before adjusting the traps, however, make sure the antenna system is properly oriented and is providing a good signal. With a weak signal, the colors will not be vivid with normal fine-tuning control settings. If the fine tuning is advanced to increase color contrast, some wiggly lines may appear as well as herringbone interference from the adjacent channel. It is also a good idea to check the setting of the color-killer control as well as the color-killer tube if slight instability occurs in fine detail.

To check operation of the killer control, set the channel selector to an unused station and back off on the color-killer control (usually counterclockwise). Now advance the killer control slowly until no colored snow appears on the screen. Check operation of the tint control during color reception to make sure it has full range. If the tint control produces a black-and-white picture for its extreme range settings, back off slightly on the color-killer control. If the slight herringbone pattern still persists for normal color levels (with good signal input from the antenna), try adjusting the traps to clear up the interference.

For horizontal-bar interference, remember that sound interference produces bars that vary in intensity in sync with the sound coming from the speaker. If the pattern remains fixed, a circuit may be oscillating and generating a fixed interfering frequency. In one color receiver the killer circuit produced colored horizontal bars because of a faulty transistor!

R-E

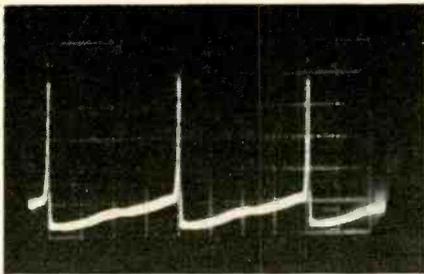


Fig. 8—Negative-going vertical retrace pulse (10 volts p-p) taken from vertical output transformer shown in Fig. 7.

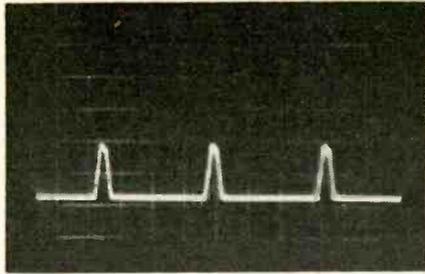


Fig. 9—Horizontal blanking pulse (4 volts p-p) taken from cathode circuit of horizontal discharge tube in Fig. 7.

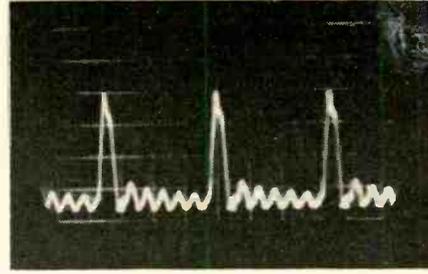


Fig. 11—Shorting of diodes X2 or X3 makes horizontal blanking pulse ring. Six-volt p-p signal taken on TR1 collector.

During the active-scan interval, the diode is forward-biased by the 680,000-ohm resistor connected to B+. The diode then directly connects the delay-line output to the 0.22- μ F capacitor and to the grid of the video output stage. Should the blanking diode short, a multiple ghost image appears on the screen. This is caused by the horizontal blanking pulse making the delay line ring.

During the negative-pulse portions of the blanking waveforms, however, the diode is turned off, disconnecting the video output of the delay line. In place of video, negative-going pulses are fed to the video output grid. These pulses cut off that stage, and of course the CRT—regardless of the setting of the contrast or brightness controls.

G-E CB chassis blanking

Vertical blanking in this receiver is developed (Fig. 5) by positive-going vertical pulses from the plate circuit of the vertical output stage. The sequence is through R539, C531 and R147 to the CRT red cathode. These pulses are then coupled from the red cathode to the blue and green cathodes via the drive controls.

Horizontal blanking is applied to a different stage (Fig. 6). Positive-going horizontal flyback pulses are coupled and shaped by C107, R145, C104 and R146 from the horizontal output transformer to the base of Q701, the second video amplifier. Di-

ode CR101 is connected to the junction of C104 and R146.

The negative portion of each horizontal pulse forward biases CR101, making it conduct. The negative portion of the flyback pulse, which contains some ringing, is removed by CR101. Accordingly, only the remaining positive pulse is fed to the base of Q701. This pulse is amplified by Q701 and the video output stage. Finally, it appears at the CRT cathodes as a positive-going blanking pulse, which cut off the CRT beams during retrace.

Zenith's 20X1C38 color chassis doesn't use direct CRT blanking. Instead (Fig. 7) both horizontal and vertical blanking pulses are fed to a video amplifier stage.

A negative-going vertical retrace pulse (Fig. 8) is taken from the vertical output transformer and fed to the emitter of transistor TR1, the video driver, through diode X3. Horizontal blanking is done with a positive-going pulse (Fig. 9) from the cathode circuit of V18-c, the horizontal discharge tube. The pulse is applied to base TR1's.

If transistor TR1 shorts or otherwise fails to pass signals, the Y or luminance signal disappears from the screen, leaving only color-difference information and retrace lines (Fig. 10). If the set is tuned in to a black-and-white program, the killer tube removes color-difference information and you get nothing but a blank raster on the screen.

If diode X2 or X3 shorts, the hor-

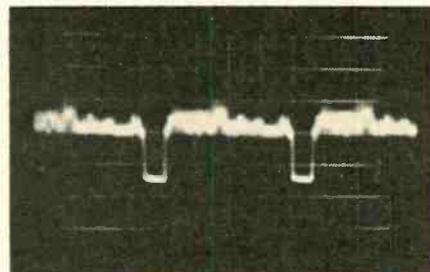


Fig. 13—Proper retrace blanking at CRT grid-cathode circuit. Total p-p amplitude is 8 volts, cutting off CRT beams.

izontal blanking pulse rings, as shown in Fig. 11 (taken on TR1's collector), and the picture looks like Fig. 12.

Both pulses—the negative vertical and the positive horizontal—have the same effect on transistor TR1; each produces a negative pulse in the collector circuit of the transistor. This negative pulse is coupled to the grid of yellow amplifier V7, and causes a positive pulse in that tube's plate circuit. Since the plate is de-coupled to the three CRT cathodes, the large positive pulse makes the cathodes positive with respect to their grids, and the beams are blanked. Fig. 13 shows horizontal blanking pulses and video at the CRT grid-cathode circuit.

Most blanking circuit troubles are simple if you understand their operation. A scope is the most effective tool with which to troubleshoot blankers. But you should also be aware of what the picture looks like with proper and improper blanking pulses. **R-E**

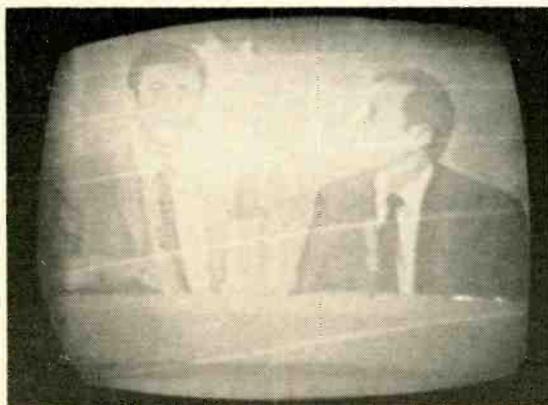


Fig. 10—Failure of video driver in Fig. 7 removes the luminance (Y) signal from screen.

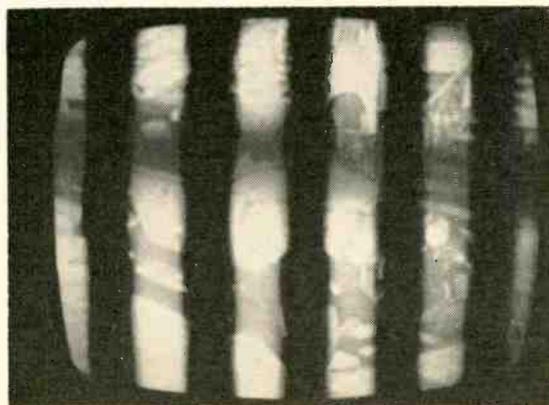


Fig. 12—Screen displays ringing bars caused by diode failure generating Fig. 11 waveform picture.

COLOR TV TROUBLE

Practical benchman's approach to servicing shortcuts

By VIC BELL


ABOUT 80% OF COLOR CHASSIS NOW use the same basic physical circuits and electrical configuration. Consequently, their problems are often identical. Even those chassis using a radically different physical layout are often electrically similar and therefore plagued by the same problems.

Some of the problems these sets develop are "easy" while others are downright tricky. In either case, the novice or pro may have difficulty finding his way around the schematic or the chassis.

If the chassis which has you stumped is not a common one, check the schematic. The chances are good that the circuitry is similar and with only a little more effort you can chase down the trouble. The troubles described here are not caused by tubes but you must understand that tubes can cause almost any conceivable trouble and we will assume that you have substituted all possible suspects. Don't forget to use your best test equipment first: eyes, nose and hands. These three tools will be the quickest road to a lot of repairs. Use them regularly and you will find a surprising number of troubles before you could warm up your scope.

Complaint: Color only—screen blank on black-and-white. This trouble can cause a lot of wasted time unless you are on the ball and look for all the symptoms. Do not overlook the fact that the screen is not blank all the time; color programing does come through when the color control is advanced. The cause can be an open or short almost anywhere beyond the color takeoff point but the most common cause is an open delay line.

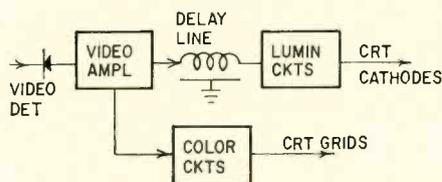Remedy: Most delay lines have only three leads; one is grounded. Connect a jumper between the two that are not grounded. If the delay line is open, the picture should appear almost



normal with the jumper in place.

Delay lines can often be repaired since they are simply a single-layer coil. Opens usually occur at or near the terminals. The grounded terminal is connected to a copper-foil cylinder on which the coil is wound.

Complaint: Poor focus. When the focus on a color set is poor but can be changed, the CRT is bad or, more likely, the focus voltage is wrong. When focus can't be controlled, it generally means that the focus voltage is nonexistent or is not reaching the CRT focus grids.

The horizontal-output pulse voltage is passed through a transformer (the focus coil), rectified (by a tube or a selenium rectifier), filtered with a 130-pF capacitor and applied to the CRT focus grid.

Remedy: If it appears that you have no focus voltage, give a light tug on the wire (usually black) going into the CRT socket. The lead may be loose and will pull out. Then all you



have to do is replace the socket. If the lead doesn't pull out, try a continuity check just to be sure.

A good socket calls for other checks. The first is a voltage check. You should have about 5,000 volts positive at the output end of the rectifier. Other problems in this area usually leave burned components, so they aren't difficult to track down. When the focus coil is bad, it too is usually burned.

Don't try to measure the front-to-back resistance on a selenium focus rectifier. This unit is actually a number of selenium cells in series and the forward resistance appears to be about the same as the back resistance. A good "sniff" will tell you more about seleniums.

Complaint: Insufficient height and width—little or no sync. These symptoms generally indicate that something is wrong in the B+ circuitry. The offending part is almost always an open voltage-doubling capacitor. In our typical color set, the unit is a 160- μ F, 250-volt single-unit can.

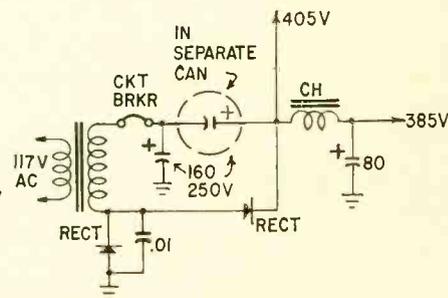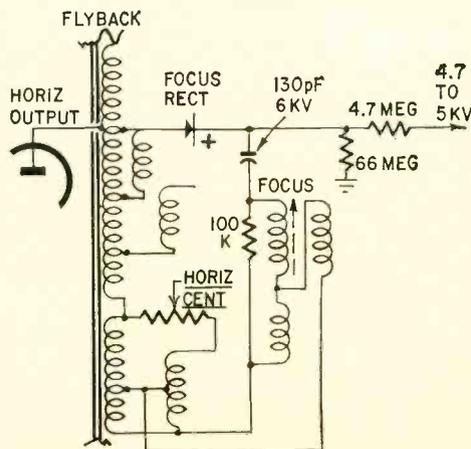Remedy: Using a similar capacitor to bridge the suspect will confirm the suspicion if the capacitor is open. Shorts rarely develop and will open



the circuit breaker, and sometimes ruin the rectifiers when they do.

If the voltage doubler is completely open, the set will not function at all. A few quick voltage measurements will still lead you to the faulty

SHOOTER GUIDE

part, however, and the same bridging technique proves the fault. If you are looking for the screen or the speaker to come to life when the capacitor is connected to the circuit, be sure the volume is turned up and that the brightness and screen controls are at their normal settings. The best way to be sure the suspected capacitor is at fault is to monitor the voltage while jumpering the part. *The set may have more than one faulty component!*

Complaint: No high voltage—burned smell. When the flyback transformer burns, it may or may not be obvious.

Remedy: Late models often have the flyback "tire" insulated with a material that does not burn under normal conditions. If you suspect the flyback has burned, feel the "tire" gently. If it is "crunchy", peel the silicone back slightly. If the flyback is burned, this will make it obvious.

All bad flybacks don't look bad nor are all bad-looking flybacks faulty. A few drops of wax which have dripped from a transformer is sometimes normal. If you must replace a flyback, be sure the high-voltage cap and associated wiring are in good shape. All tubes in the horizontal and high-voltage section should also be replaced since any one of these could be intermittent and cause flyback failure. Heat may have damaged selenium focus rectifiers in extreme cases and these should also be replaced to prevent future difficulties.

Complaint: Circuit breaker trips—either immediately or after the set has operated normally for a few seconds or a few minutes.

Causes and remedies: If the circuit breaker trips as soon as the set is turned on, the most likely suspect is one of the B+ rectifier diodes. No need to disconnect the diodes; a quick check with the ohmmeter will show a short. Make sure you check the diode both ways.

Another common cause is a 0.0033- μ F, 1600-volt capacitor used

between the vertical output plate and one side of the yoke in some vertical amplifiers. This sometimes shorts. The convergence wiring may have to be replaced in the area of the capacitor and the resistor feeding the vertical circuit.

If the horizontal-output plate starts to turn red, the trouble may be the tube itself, the high-voltage rectifier or the horizontal oscillator. A quick check of output-tube grid voltage should show about -55 to -45 volts. A more positive voltage usually indicates oscillator trouble. Voltage and resistance checks in the oscillator circuit will pinpoint the trouble. Be sure to check the output grid coupling capacitor for leakage.

Another frequent offender, and last on many technicians' lists, is the circuit breaker itself. One good check is to simply short out the breaker for a short period.

Complaint: Blooming. Very likely this condition is caused by excessive drain on the high-voltage supply rather than on the high-voltage source, as is more common in b-w sets. Measure voltages at all elements of the CRT to

pin down the exact area of the problem.

Causes and cures: The most frequent offenders are the color-difference (R - Y, G - Y, B - Y) amplifier and the drive circuits in the luminance-channel output section. Anything that reduces the drive at the CRT cathodes or increases the voltage at the CRT grids can cause blooming and possible loss of raster.

An open heater in one of the color-difference amplifiers, for example, can cause B+ in that stage to go high enough to cause loss of the raster. Similarly, an open cathode resistor (common to all color-difference amplifier circuits), a shorted coupling capacitor in the grid of any of these stages, or a plate load resistor greatly reduced in value causes loss of raster conditions. Again, simple voltage checks will isolate the problem area.


If the video amplifier or the associated CRT cathode-drive circuitry is suspected, these areas can be isolated by operating the service switch. If a horizontal line appears at a normal setting of the screen controls, the drive circuitry is probably normal. Also, the color amplifier can be disregarded. All suspicion would be placed on the last video amplifier and direct-coupled stages ahead of it.


These are the only stages isolated from the CRT when the service switch is operated.

When the trouble has been traced to the drive circuits, look for an open resistor. You may save time by checking the resistors located in the kine-bias switch circuit first; a 5600- or 6800-ohm resistor will usually be found open. Also, don't fail to check the kine bias switch for failure.

Don't overlook checking the high voltage. A no-raster condition often presents itself even when the high voltage is normal. Check the B+++ voltage. It should be about 1200 volts and can be measured at the screen controls. The B+++ rectifier is often the culprit when this is low (800 volts indicates a shorted B+++ rectifier).

Complaint: No color—Loss of

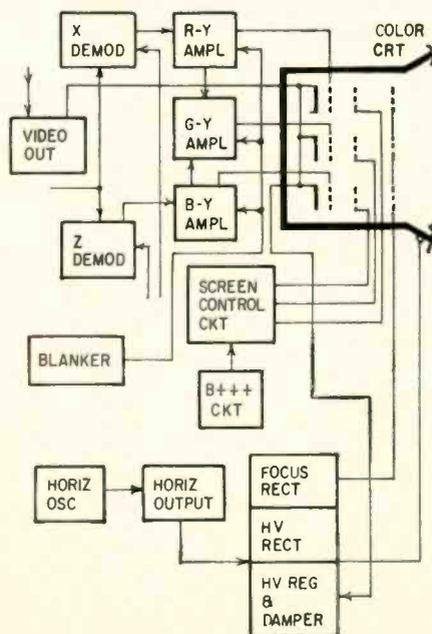

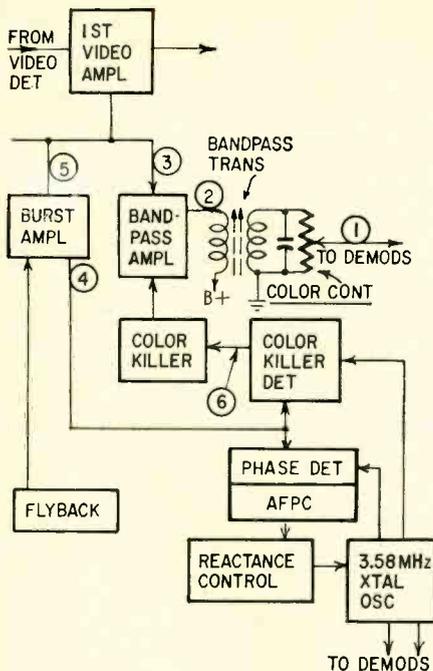

color is a common trouble which is easy to localize and repair because very few stages are involved in a no-color problem.

Before you start troubleshooting, make sure the color-killer adjustment is turned up and that the color-level or color-intensity control is fully open. This may solve the problem before you go any further.

Causes and cures: There is no reason to suspect the demodulators or color amplifiers since a malfunction there usually causes a color problem rather than a color loss and may cause color temperature trouble on black-and-white programs.

If the problem is related to color sync, the killer circuit usually activates and cuts off color. Consequently, the search can be immediately narrowed to the color oscillator and sync circuits. Frequently, only a reactance-coil adjustment is required to restore normal operation.

If you still haven't found the trouble, it's time to use a scope. A convenient starting test point is the arm of the color control just ahead of the demodulators. Then proceed as shown in the diagram above.

An open bandpass transformer is a frequent cause for loss of color. A continuity check will show if it is the culprit.

Complaint: Insufficient height. This problem often reflects troubles in the convergence circuits. Defects in the vertical oscillator can be localized quickly by voltage and resistance measurements and waveform checks.

Causes and cures: The convergence circuitry represents the total load (or a substantial portion of it) on

FIVE COLOR TROUBLESHOOTING TIPS

Color only—raster blank on black-and-white: Check for open delay line.

Poor focus: Measure focus voltage. Check CRT.

Blooming and possible loss of raster: Trouble not always in high-voltage section. Check color-difference amplifiers and luminance drive circuits.

No color: Check color controls. Check color oscillator and sync circuits.

Insufficient height: First test vertical circuits, then convergence circuitry.

the cathode circuit of the vertical output stage. If the stage does not have a separate cathode resistor, the resistance from cathode to ground will be around 5600 ohms in most sets. A higher resistance indicates a possible defect in one or more of the convergence controls.

To determine whether a convergence control is causing insufficient height, pull the convergence-board plug and connect a 120-ohm resistor from pin 2 (cathode circuit) on the convergence socket to ground. If height returns to normal the trouble is on the convergence board.

A cathode-bypass electrolytic, usually 50 μ F, is also a frequent cause of trouble. Try shunting it with a similar type. If the sweep returns to normal the capacitor is bad.

Some sets have a cathode resistor shunting the convergence circuitry. If it has darkened or appears to have been overheated, replace it with a higher-wattage unit of the same resistance.

In many circuits, the B+ voltage to the vertical output transformer is dropped through a 3 to 5-watt resistor ranging from around 500 to 1500 ohms, depending on the set. A change in resistance can cause a drop in vertical sweep voltage.

Check for a leaky capacitor in the feedback network between the vertical

output plate and the oscillator grid. Leaky capacitors generally cause the raster to collapse but they can be responsible for insufficient height.

Checking the output transformer can be a real problem. If the B+ and sweep waveform are good, there is every reason to believe that the output transformer is bad. The only sure check is to substitute it. Since the yoke is easily substituted, try this before a transformer change.


The rest is "Old Hat"

Most of the circuits in a color set have been mentioned in this article. But what about the rest? If you've been working on black-and-white sets, you should have no trouble. Agc, tuner, afc and i.f. circuits are all similar and display symptoms identical to corresponding malfunctions in black-and-white sets.

If you get stuck, look for variations of the problems discussed here. When you come to the end of your rope again, start over, you have probably skipped something too obvious.

And finally, don't forget that two tubes could be bad or that one of your new tubes could be bad. It happens every day and can be the toughest trouble you will ever encounter if you don't keep it foremost in your mind.


R-E

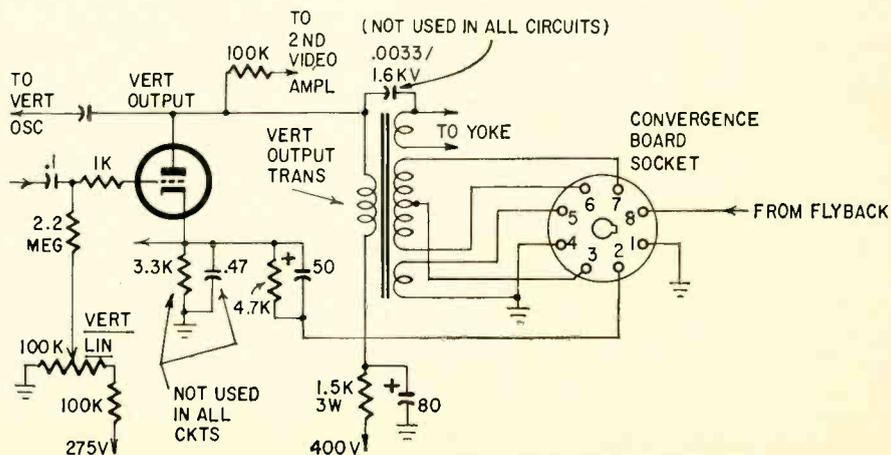

BUILD AN IC DECADE DIVIDER

Use with signal generator or frequency counter . . . divides any frequency by 10

By DEWEY W. EPPLEY

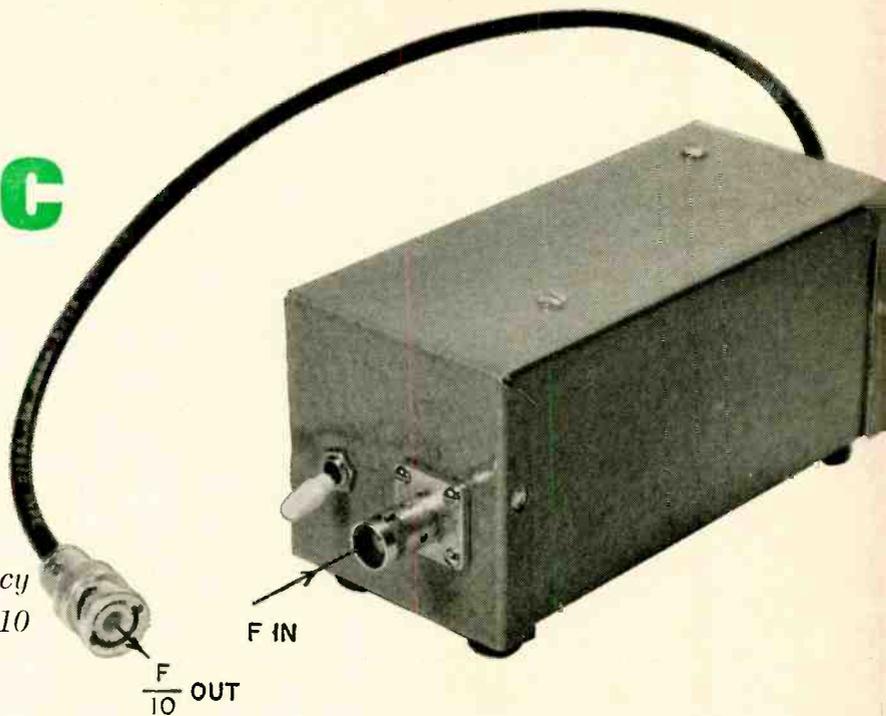

WANT TO UPGRADE THAT OLD 100-KHz electronic counter to 1 MHz? Then read on and find out how you can easily and cheaply construct a battery-powered, in-line type decade divider (semiconductor cost less than \$7.50). At the same time you will get a chance to work with a few of the many applications afforded by today's low-priced logic circuits.

The μ L914

This article deals with only two of the many IC's available at very low cost. First is the Fairchild μ L914, priced at only \$0.80 in an epoxy package. The manufacturer calls this module a "Dual Two Input Nand/Nor Gate," but don't let this fool you—it has many applications. Fig. 1 shows

the base connections and internal components of the μ L914. Pin 8, identified by a flat spot on the epoxy case, is the positive supply voltage input. Pin 4 (counted in the same fashion as tube pins are numbered) is the ground terminal. Pins 1 and 2 are inputs to the transistor bases for one section, while pins 3 and 5 are the corresponding inputs for the other section. Pin 7 is the collector output for the first section, and pin 6 has the same function for the second section.

The μ L914 is a dandy amplifier. All it needs is a 3-volt supply—positive to pin 8 and negative to pin 4. A low-level input signal (high side through a capacitor to either pin 1 or 2, low side to ground) will produce an amplified output at pin 7 to ground. The unused input is left floating.

Note the use of that phrase "low-level input." Actually the output is linear until the input is about 150 mv. Levels exceeding this value will result in an overdriven, clipped output. In no case should the level at the input pin exceed ± 4 volts.

What about the other half of the device? Well, you can either hook it in cascade by connecting pin 7 to 3 or 5 or you use it for another function. If you desire a noninverted output, cascade the amplifiers—since each amplifier inverts output with respect to the input pulses.

Now for another application—the Schmitt trigger. This circuit has the unique property of changing output level when the input exceeds a certain value, then returning to the


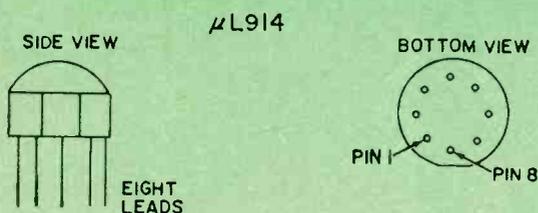


Fig. 1—The lowest cost version of the μ L914 is the epoxy package, shown here along with its internal schematic.

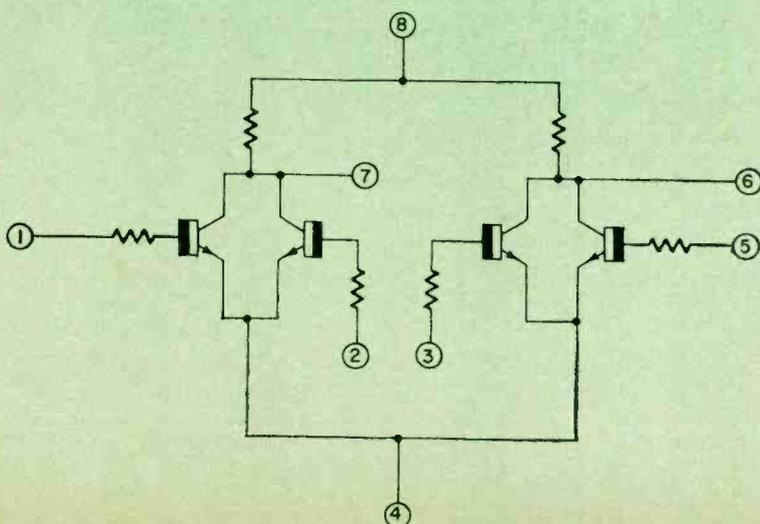

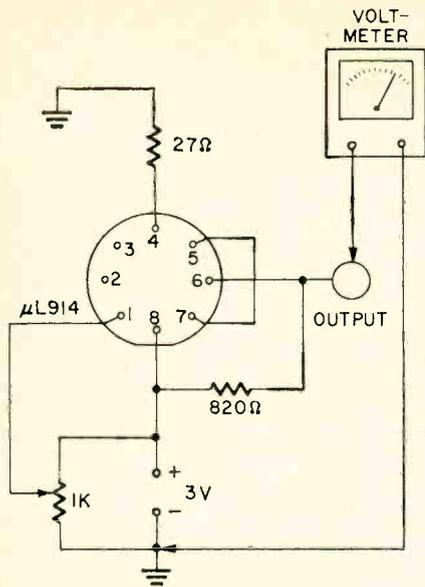


Fig. 2—External circuit connections shown will adopt μL914 as a Schmitt trigger. Critical firing point is determined by adjusting pot while monitoring output.

original level when the input falls below the critical value. Since the transition from one state to the other is very rapid, the output is very nearly a square or rectangular wave with a sine-wave input. Furthermore, the Schmitt trigger does not care what type of waveform it sees so long as the triggering level is exceeded.

For the μL914 to act as a Schmitt trigger several things must be done externally. First, since emitter coupling is needed, pin 4 is not connected directly to ground, but through a 27-ohm resistor. Also, to provide the necessary hysteresis, one collector resistor is shunted with an 820-ohm resistor. Finally, pin 7 is connected to either pin 5 or pin 3. Now the circuit should look like Fig. 2.

Apply a voltage from the wiper of a potentiometer connected across the 3-volt supply to pin 1. Hook a voltmeter across pin 6 to ground. You will see that, at the critical point, a slight variation in input level results in a sharply defined output change.

The MC790P

The second type of logic circuit used in this project is the J-K flip-flop or binary. A flip-flop is a bistable device; that is, it has two stable states. A J-K flip-flop is a more sophisticated device; retained explanation is beyond the scope of this article. Instead you might call the J-K a black box. In addition to the power supply terminals the black box has four inputs and two outputs. The outputs are called 1 and 0 and are complementary. That is, if there is a high level at the 1 output, the 0 output must be low-level and vice-versa. One of the inputs is labeled the S or SET input. Another input is the C or CLEAR input. The next input is called the T or TOGGLE input. The final input is the PRECLEAR input.

The PRECLEAR input is not used in this application, so it is simply grounded. The particular module used is the Motorola MC790P, which contains two flip-flops in one package.

Grounding the CLEAR input will

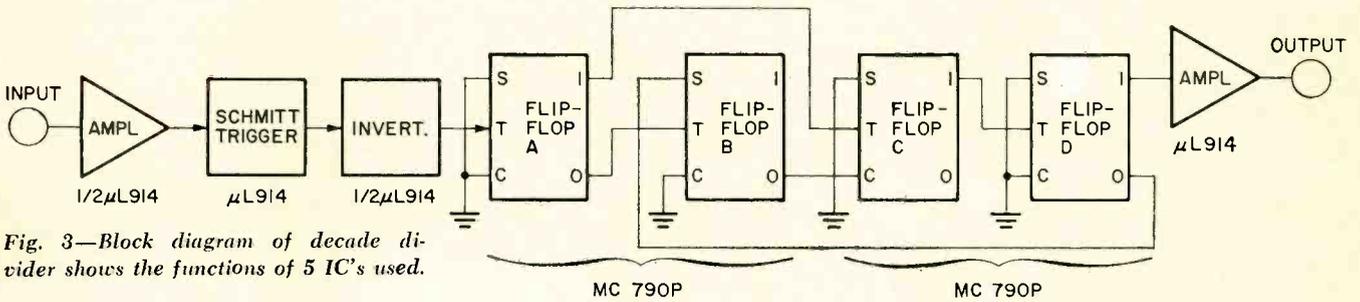


Fig. 3—Block diagram of decade divider shows the functions of 5 IC's used.

PARTS LIST

IC1, IC2, IC5—Fairchild μL914 integrated circuit
 IC3, IC4—Motorola MC790P integrated circuit (Both IC's available from Semiconductor Specialists, Inc., P.O. Box 8725, O'Hare International Airport, Chicago Ill. 60666,

which has a minimum order of \$3.00)
 B1, B2—1.5-volt C cells
 C1, C2—.01- μF disc capacitor, any voltage rating
 R1—82,000-ohm, $\frac{1}{4}$ - or $\frac{1}{2}$ -watt resistor, 10%
 R2—27-ohm, $\frac{1}{4}$ - or $\frac{1}{2}$ -watt resistor, 10%
 R3—820-ohm, $\frac{1}{4}$ - or $\frac{1}{2}$ -watt resistor, 10%

S1—S.p.s.t. toggle or slide switch
 J1, J2—Input and output coaxial jacks, BNC or other as desired to match existing equipment
 MISC.—Aluminum box 5" x 2 $\frac{1}{4}$ " x 2 $\frac{1}{2}$ " (Bud CU2104A or similar); 1/16" or 1/8" perforated board, battery holder, connectors.

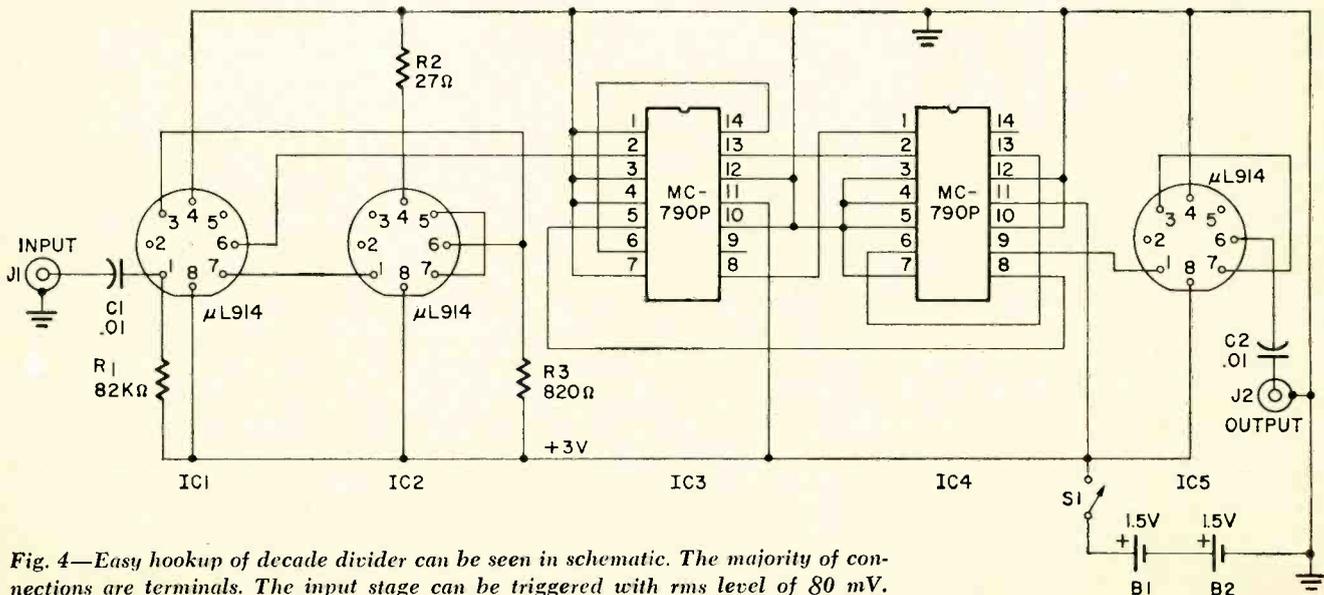


Fig. 4—Easy hookup of decade divider can be seen in schematic. The majority of connections are terminals. The input stage can be triggered with rms level of 80 mV.

reset the unit to its normal condition, when the first clock or toggle input pulse arrives. In this condition the 1 output has a logic 1 and the 0 output has a logic 0. Now if the SET input is grounded, the flip-flop will change states at the next clock pulse, and the 1 output will have a logic 0 out. If both the clear and set inputs are grounded, the device will change output states with each input toggle pulse. Since it requires two pulses to return the unit to the original condition, the input frequency has been divided by a factor of 2 by the flip-flop.

Through the use of an ingenious interconnection system devised by logic designers, the state of the flip-flops can be set so division by practically any number is possible. In this application four flip-flops are interconnected to give division by 10. You can easily see that if the units did not have interconnections—instead, a straight output from one flip-flop to the input of the next—the division would be $2 \times 2 \times 2 \times 2$, or 16.

Divider circuit

A block diagram of the decade divider is shown in Fig. 3, and the complete schematic in Fig. 4. The first stage is half of a μL914 . The extra resistor from pin 8 to pin 1 provides a bias voltage on the base of the input transistor, producing greater sensitivity. Use of an 82,000-ohm resistor permits triggering the stage with an rms input level of 80 mv or less.

Output taken from pin 7 is directly connected to the input of the Schmitt trigger whose output is the rectangular

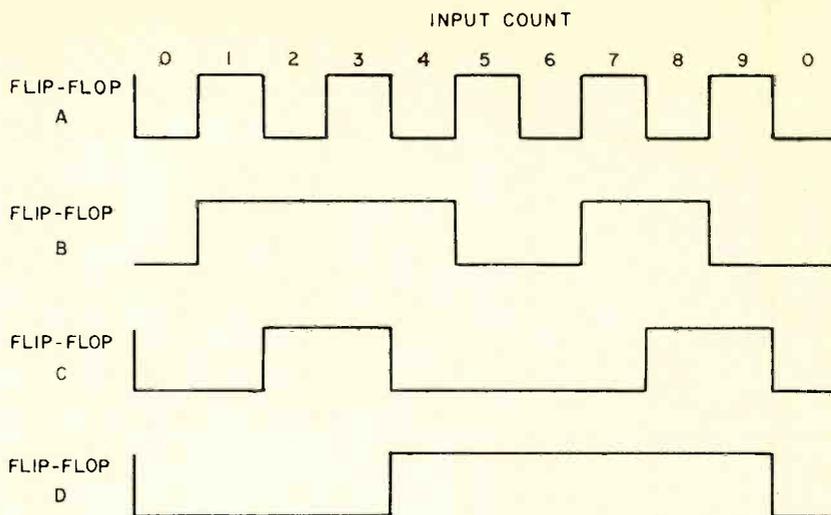


Fig. 5—Divider action is shown by these flip-flop output waveforms.

waveform described before. This waveform is inverted by the second half of the first μL914 . The inversion stage is desirable for isolation from the Schmitt trigger. The negative-going slope—that is, the transition from a high level to a low level—is used to trigger the TOGGLE input of the first flip-flop. The remaining flip-flops are interconnected, as stated before, to produce a total division by 10. Fig. 5 shows the output waveforms of each flip-flop with respect to the various input pulse counts.

The final circuit consists of a μL914 with both halves operating as a cascade amplifier. This gives the required isolation or minimum loading of the flip-flops. Although the prototype does not have an output capacitor it would probably be advisable to

install a 0.01- μF unit (C2) in series with the output.

Construction

All ready? Begin by cutting a piece of $\frac{1}{16}$ " or $\frac{1}{8}$ " phenolic or glass fiber board about $\frac{1}{8}$ " smaller on all dimensions than the inside of your aluminum box. Lay out the components on the board approximately as shown in Figs. 6, 7 and 8. Placement isn't really critical here (a bonus when using IC's). On the first version of this unit I used a double-sided printed circuit board, but the care and precision required to make and wire the board was later deemed prohibitive. It is much simpler to drill holes for the leads to stick through and then bend and solder on the reverse side of the

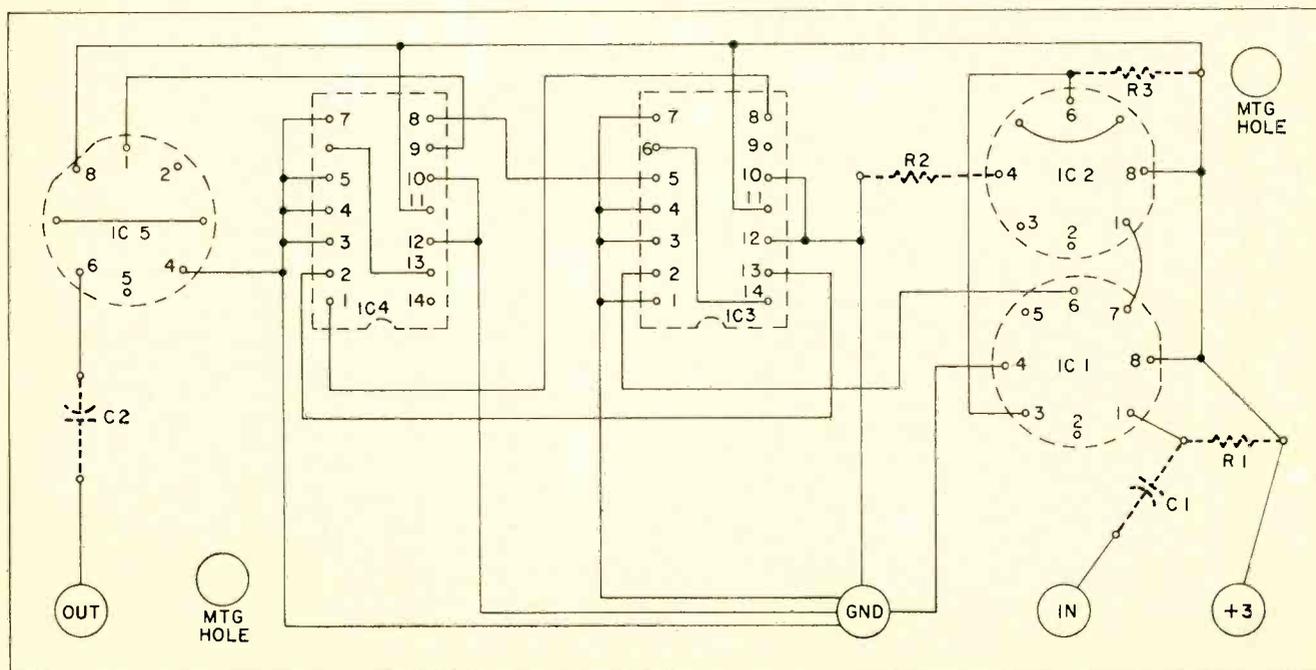


Fig. 6—Author used a glass fiber board for parts mounting; a perforated phenolic board would do just as well.

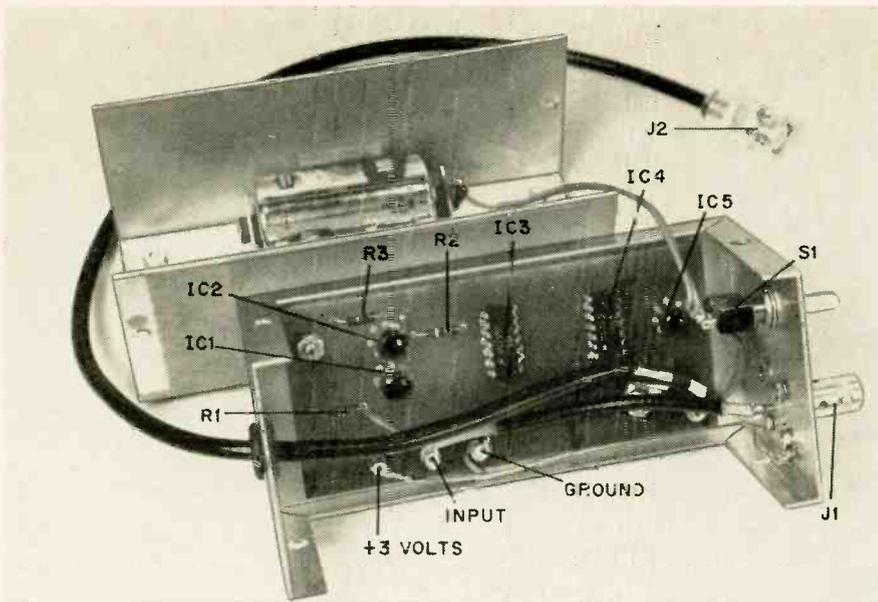


Fig. 7—Circuit board should be just a little smaller than the aluminum box you use. Mount the board on standoffs. Carefully recheck pin indentifications.

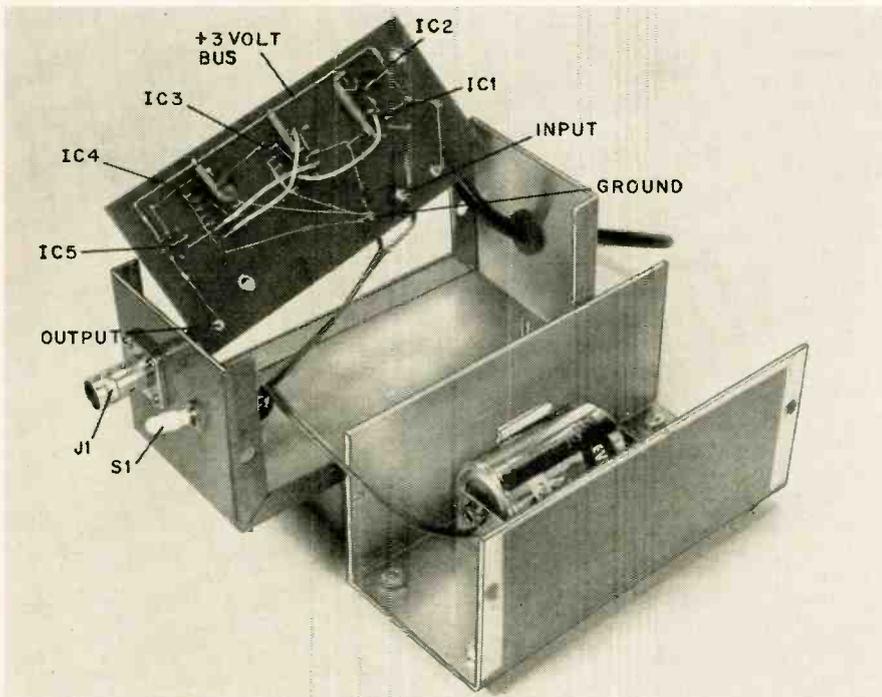


Fig. 8—An underside view of the board before final installation in the box.

parts mounting board.

The easiest approach for mounting the μ L914 is to lay out a $\frac{3}{8}$ " diameter circle and drill through with a No. 60 drill every 45 degrees around the circle. The MC790P is a rectangular package with two rows of 7 pins. The rows are spaced 0.3" apart and pin to pin spacing in the row is 0.1". Again use a No. 60 drill. Pin numbers are shown in Fig. 9.

One word of caution: It is very easy to mistake pin numbering after the MC790P is inserted in the board. Take extra care in identifying pins before you solder.

Figure 6 shows all the wiring on

the underside of the board. Use this illustration rather than Fig. 7 or 8, as minor wiring differences are evident. If you elect to omit the terminals, simply drill larger holes for the input and output leads and solder in the same fashion as the integrated circuits.

Double-check the wiring after you finish the board. When you are satisfied everything is in order, make a temporary test setup. Connect an oscillator—set to approximately 100 kHz—to your frequency counter. Observe the frequency readout on the counter. Now connect the oscillator to the input of the decade divider and apply 3 volts to the positive bus and

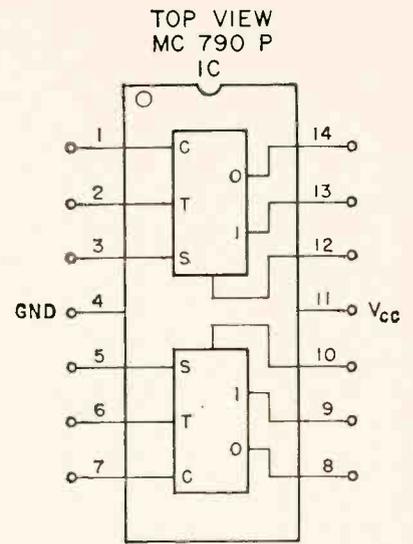


Fig. 9—Pin connections for the Motorola MC790P integrated circuits (IC3, IC4).

ground. Connect the decade divider output to the counter. The counter should read exactly $\frac{1}{10}$ th the previous reading. You may have to increase the level of the oscillator at this frequency because of the relatively small value of the input capacitor.

Troubleshooting

I have constructed several decade dividers and have found no difficulties. If you have any difficulties, troubleshoot the unit with your scope. Output at pin 7 of the first μ L914 should be a clipped sine wave, the amount of clipping depending upon the input level. The output of the Schmitt trigger (pin 6 of the second μ L914) is a rectangular waveform with an amplitude of approximately 1.5 volts p-p. The inverter output, pin 6 of the first μ L914, will be the inversion of the Schmitt trigger output. There is some tendency for a scope to couple in noise, but with a little care to keep leads short you should be able to see the on/off states of the flip-flop.

Once you have established that the circuit is working, the board can be mounted in the box. Drill holes through the board and the box for the mounting bolts. Use a spacer or a nut on the bolts to hold the board away from the metal. Although the unit pictured uses a miniature toggle switch for the power switch, there is plenty of room for a standard size switch. Mount a connector on the box which will mate your counter input cable and mount the corresponding mate on the end of a piece of coax line connected to the output. Install the battery holder in the bottom of the box, connect your wires and you are ready to measure frequencies up to 1 MHz. **R-E**

Capacitors As Transducers

They can be made to count, measure and gauge

by J. MERINO Y CORONADO*

A CAPACITOR IS NOT JUST AN ELECTRONIC component wired into a circuit. Dozens of kinds of unusual capacitors are used in labs and along production lines throughout labs and industry. They count objects, gauge liquid levels or pressures, measure vibration or angles of rotation. Capacitors of this type are classified as capacitive *transducers*.

A transducer is a device with two input terminals and two output terminals. It converts mechanical energy to electrical, or vice versa, according to a known law. It is reversible, which means that both the input and output are interchangeable.

The cartridge in an inexpensive phonograph is a good example of a piezoelectric transducer: the mechanical vibrations of the needle are transmitted to a piezoelectric element (usually made of Rochelle salt or of a certain type of ceramic containing titanates). The element generates electrical charges when twisted by the movement of the needle. Conversely, if we put an alternating voltage across the cartridge, the crystal will produce vibrations and sound, which is a form of mechanical energy.

The *condenser microphone* (Condenser is an old name for *capacitor*, which has persisted in conjunction with microphones.) is a capacitance transducer that transforms the mechanical energy of sound waves into electrical energy to operate an amplifier. In its simplest form it consists of a thick, fixed, circular metallic plate in front of which is a very thin conductive diaphragm separated from the plate by an insulating ring a few thousandths of an inch thick (Fig. 1). The diaphragm moves back and forth with the variations in air pressure caused by sound. As the distance between diaphragm and plate varies, the electrical capacitance of the microphone varies proportionally.

A battery of usually 50 volts or more is connected to the plate and diaphragm in series with resistor R. An increase in capacitance allows the microphone to admit more electrons from the battery. A decrease forces

some electrons from the mike back to the battery.

As everyone knows, a flow of electrons is an electric current and this current produces (Ohm's law) a variable voltage (E) across resistor R. This voltage is applied to the grid of an amplifier tube or to a transistor.

The condenser microphone is reversible. If an alternating voltage is applied between the diaphragm and plate in Fig. 1, the diaphragm will move accordingly, pushed by variations in electrostatic force, and, if the signal voltage is audio, a sound will be heard. This is the principle behind electrostatic loudspeakers.

It is possible to increase the capacitance of a capacitor in three ways. Two are mechanical methods: increasing the area of the plates, or decreasing the distance between them. The first is used in rotary variable-tuning capacitors with meshing plates. The second is used in the compression-type of trimmer capacitor.

Figure 2 shows two forms of capacitance transducer widely used for industrial and scientific purposes. In a we see a cylindrical configuration, in b, a flat or plane transducer.

If one electrode is movable, both types produce a variation of capacitance linearly proportional to the amplitude of the movement (arrows).

The capacitance of both transducers can be readily computed from the following formulas:

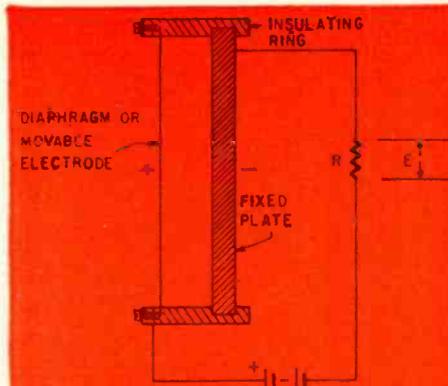


Fig. 1—Common capacitive transducer is the capacitor (condenser) microphone.

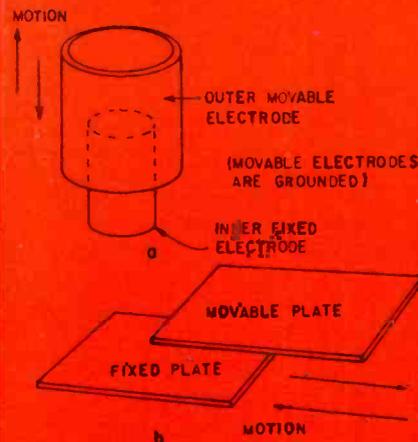


Fig. 2—Two forms of displacement-measuring capacitors. (a) cylindrical; (b) plane. Moving element varies the capacitance by changing effective plate area.

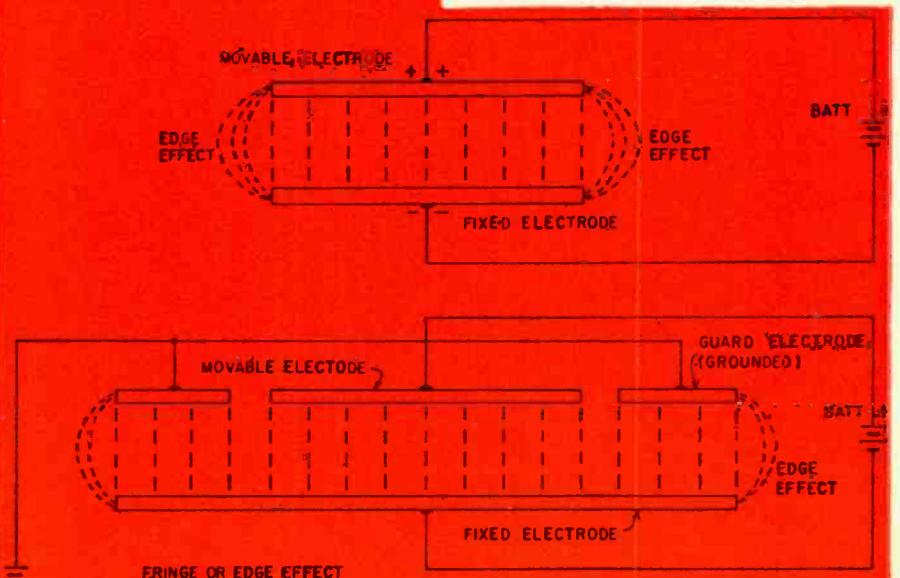


Fig. 3—Edge-effect capacitance (top) is prevented by grounded guard electrodes.

*Research physicist and professor of acoustics and electronics, Institute of Geophysics and Polytechnic Institute of Mexico.

For the cylindrical configuration we use:

$$C_{(pF)} = 0.644 KL / \log(b/a)$$

in which L is the length in inches of the overlapping portions of the cylinders. The constant K is the dielectric constant of the material between the cylinders. The inner diameter of the outer cylinder is b , and a is the outer diameter of the inner cylinder, which is also in inches.

For a capacitor made of two plane parallel plates the capacitance in picofarads is computed by

$$C_{(pF)} = 0.225 KA/D$$

where A is the area in square inches of the portion of the movable plate which is actually over the fixed one, D is the distance in inches between the two plates, and K is, as before, the dielectric constant of the material between the plates. (For air it is very nearly 1.)

Plane parallel plates and cylindrical capacitors are much used in industry and science to measure linear displacements.

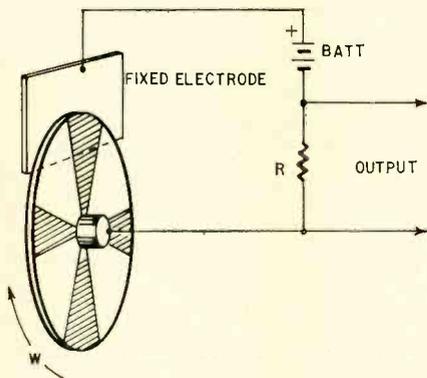


Fig. 4—Variation of rotary meshing-plate variable capacitor is used to generate audio tones . . . useful in electronic organs.

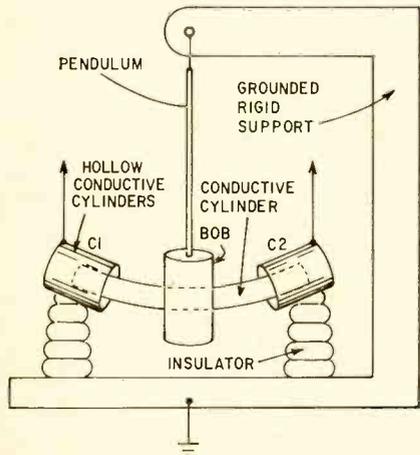


Fig. 5—This capacitive pendulum can measure very small tilts or vibrations. Transducers are cylindrical type (Fig 2a).

To measure angles of rotation, variable capacitors of the type found in radios are used, because their capacitance changes linearly with the angle, provided the rotor plates are semicircular and measurements are made between 15% and 85% of the rotation angle.

There is a third way to change the capacitance of a capacitor: to change the dielectric.

Oil, for instance, has a dielectric constant of 25.8. For distilled water the constant is 81.07. An air capacitor will have 25.8 times its capacitance when it is in alcohol, or 81.07 times its capacitance when submerged in distilled water. (Tap water cannot usually be used because the minerals dissolved in it make it too conductive.)

Not all the capacitive transducers used for instrumentation purposes are built in the simple form shown in Fig. 2. The electrostatic lines of force at the edges of the plates or cylinders are not parallel, but bulge outward, pro-

ducing stray capacitances that make the actual capacitance greater than the computed value. This *edge effect* or fringing must be kept to a minimum, since some transducers are made to measure capacitance variations of the order of 0.2 pF. This is accomplished by using a third, grounded electrode, called a *guard ring* or guard electrode. Fig. 3 shows the edge effect and how to eliminate it with a guard electrode for a capacitive transducer using plane plates, one of which moves either up and down or in and out, perpendicular to the plane of the paper. The arrangement is similar for cylindrical capacitive transducers.

If the rotor shaft of a variable capacitor of the type used in ordinary radios is coupled to a rotating piece of machinery, rotation angles from 0° to some 150° can be measured. The coupling can be made to multiply the angle of rotation by a known factor—as by the use of gears, levers, or pulleys and strings.

The transducer itself may have many forms. In most cases it has a guard electrode. Very small angles can be measured.

A capacitive transducer used to generate audio tones works on the same principle as the condenser microphone. In Fig. 4, W is a wheel of bakelite or any convenient insulating material. This wheel has sectors of aluminum foil connected to the shaft, which is grounded.

In front of these is a fixed metallic plate or screw. As the wheel rotates, the capacitance between the conductive sectors and the fixed plate or screw varies and so does the charge. An alternating voltage appears across resistor R , with a frequency equal to the number of revolutions per second of the wheel multiplied by the number of sectors. This frequency can be amplified and measured with a frequency meter, and we have an electrostatic tachometer. The same principle is used to generate musical tones in some types of electronic organs.

Measuring vibrations and tilting

Capacitive transducers are much used in instruments for measuring vibrations caused by passing vehicles or heavy machinery, or tilting caused by heavy loads in bridges or buildings. The principle of a tilt meter or vibration meter is shown in Fig. 5. The bob of a pendulum carries a curved metal cylinder that moves in or out of two lateral hollow cylinders mounted on porcelain or bakelite insulators. The two fixed cylinders and the grounded movable cylinder together make up a differential capacitor.

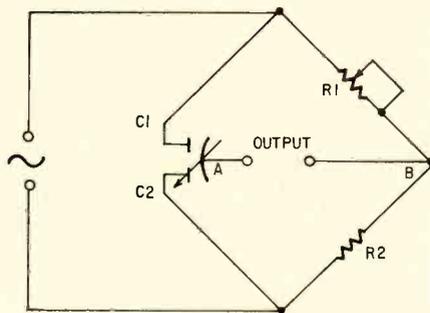


Fig. 6—This ac bridge is detecting device for capacitive "tiltmeter" (Fig. 5). $C1$ and $C2$ are cylindrical transducers; changing voltage across A, B is amplified.

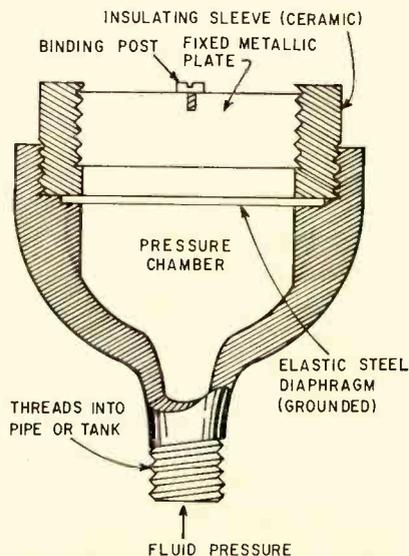


Fig. 7—Pressure sensitive capacitive transducer (similar to condenser mike).

If the pendulum support is tilted or otherwise set in motion, the capacitance between the pendulum and one of the other plates increases, while it decreases by the same amount between the pendulum and the second fixed electrode. A simple ac bridge can be used to measure and record such variations. In Fig. 6, C1 and C2 are halves of the differential capacitor in a tilt or vibration meter. If R1 is adjusted so that the bridge is *not* balanced when the pendulum is at rest, an ac voltage is present between points A and B. This is called the *carrier voltage*, and it is amplitude-modulated when the pendulum moves. The modulated waves are amplified and detected in the usual way to be recorded or telemetered to another receiver.

Guard electrodes are a must in this type of instrument. In Fig. 5 they are not shown for simplicity.

Some time ago I designed and built a very sensitive seismograph using this principle.

Capacitive pressure gauges

When the indicator or recording device is at some distance, or when the pressure variations in pipelines carrying fluids are to be used for remote control, capacitance transducers are second to none.

A pressure-sensitive transducer is shown in Fig. 7. It has a movable elastic metal diaphragm, grounded for obvious reasons. An insulating ceramic or porcelain sleeve holds a fixed conductive plate, strong enough to stand the full pipeline pressure in case the diaphragm fails. It is made quite stiff, with a resonant frequency of 10 kHz or higher to reduce its response to vibrations or shock. The pressure gauge is nothing but a condenser microphone working at high pressures.

Level measurement of liquids in tanks

For this a simple cylindrical capacitor is used. The inner electrode is a rod or heavy metal cylinder, 1" or 2" in diameter. The outer electrode is a metal tube with holes in it, grounded to the tank (Fig. 8), while the inner rod is insulated. Nonconductive liquids cause the capacitance to increase according to their level and dielectric constant. For conductive liquids such as water or saline solutions, the inner rod is covered with plastic or any other type of convenient insulating material.

A simple ac bridge measures capacitance variations, as described in Fig. 6. More elaborate devices are often used in these applications, such

as the trf receiver that is shown in Fig. 9, to measure distance, rotation, pressure or liquid level in a tank. A very stable rf oscillator is coupled to a resonant input circuit in an rf amplifier. The capacitor of this tuned circuit is the capacitive transducer (in series or in parallel with a fixed or adjustable capacitor used for calibration or adjustment). A linear detector and power amplifier complete the instrument. Its output is used to operate a recording instrument or another controlled device of some kind.

The resonance curve of trf receivers is very much like Fig. 10. The "receiver" used to measure capacitance variations is *never* tuned to resonance, but to one side of the curve where its slope may be considered linear, let us say to the point marked 0 in the figure. The corresponding point, O', is the operating point. An increase in capacitance from 0 to B displaces the operating point to B' and the output of the detector decreases. Very rapid va-

riations in capacitance can be measured by this method.

A phase-sensitive detector (Fig. 11) is used with capacitive transducers in many industrial and scientific instruments and applications.

What about using a superhet? This more complex receiver is used to measure very small variations in capacitance. One grid of a mixer tube is fed by the output of a crystal-controlled oscillator, while the other is fed by a variable-frequency oscillator whose frequency is controlled by variations in capacitance caused by a capacitive transducer.

In this way a variable i.f. is obtained. When both oscillators have the same frequency, the i.f. difference is zero. As soon as the capacitance of the transducer changes, the frequency of the variable oscillator shifts and an i.f. is produced in the mixer. Differences in frequency of a few hertz are easily detected by ear or by a frequency counter. **R-E**

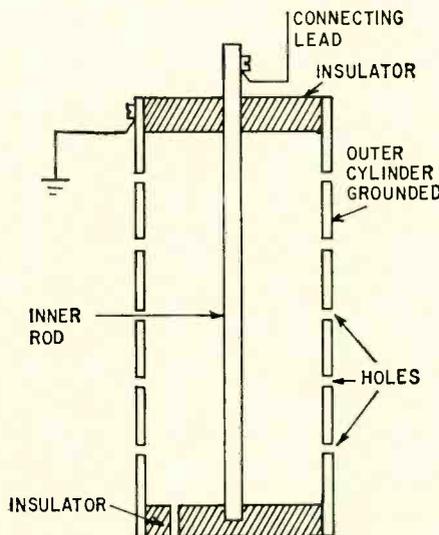


Fig. 8 (left)—This device provides a continuous indication of liquid level without moving parts. Nonconductive liquids vary the capacitance between two electrodes.

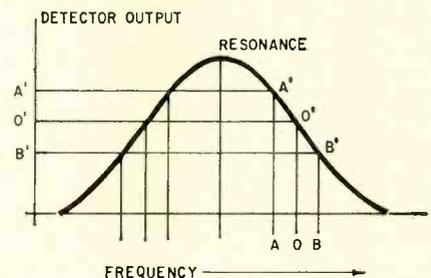


Fig. 10—In slope detection, carrier is tuned to point 0. Capacitance changes may cause carrier shift to points A or B.

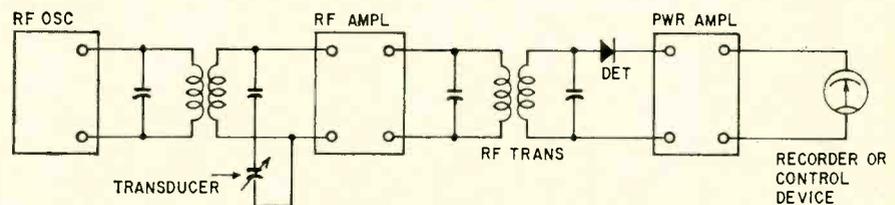


Fig. 9—Tuned radio frequency (TRF) method uses capacitive transducer to generate amplitude, phase or frequency variation in rf carrier for detection, amplifying.


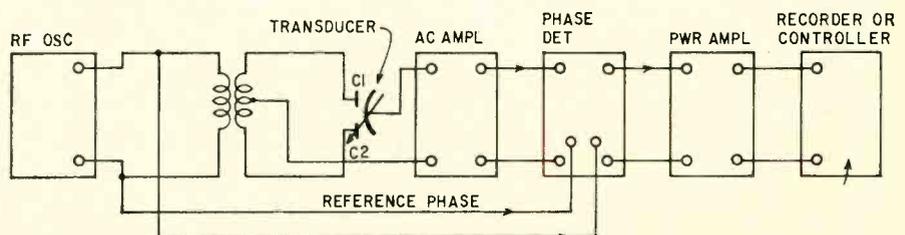


Fig. 11—Transducers C1 and C2 are used in phase-detector (discriminator) circuits.

There's more than one road to success.

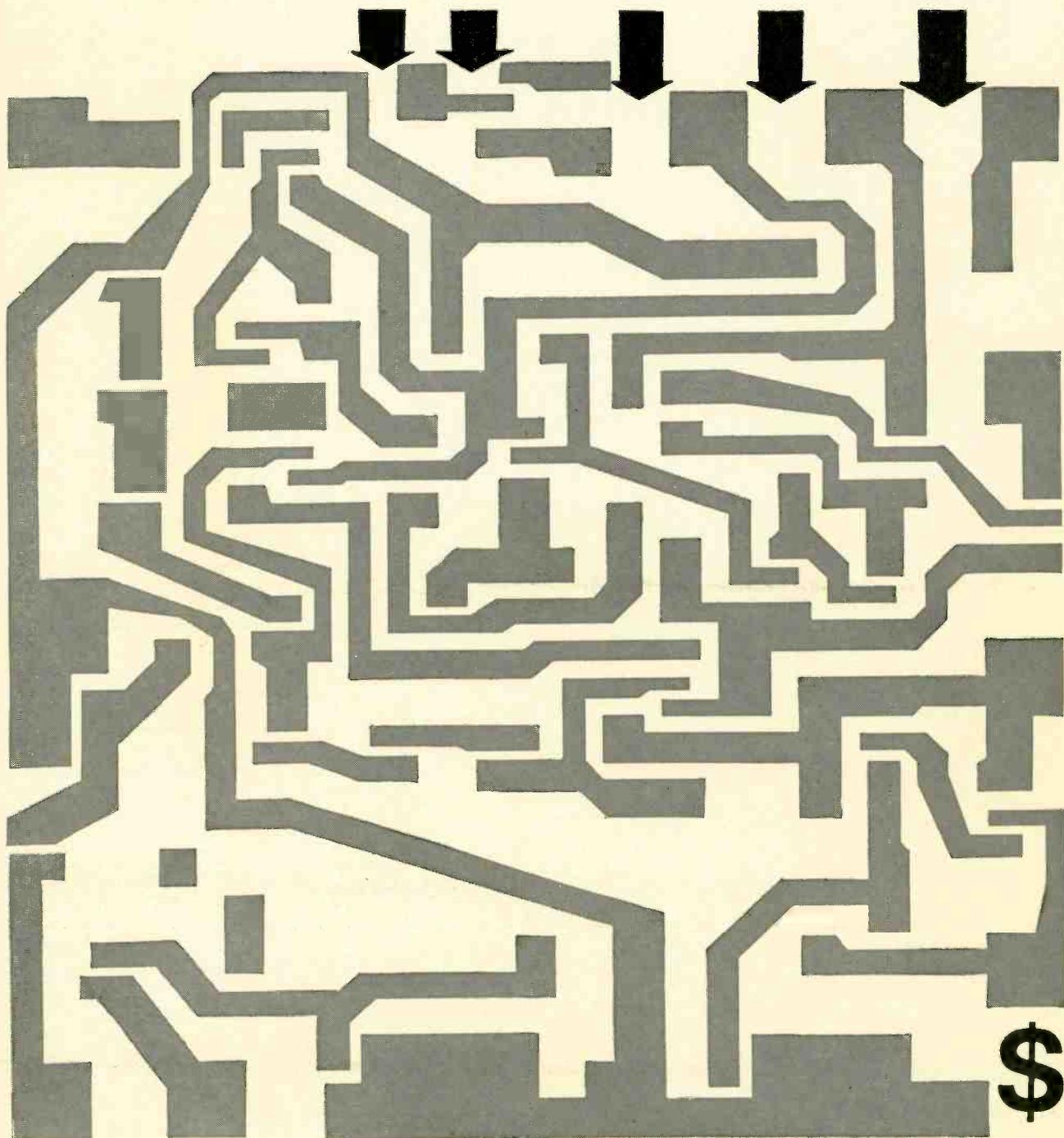

An integrated circuit enlarged several thousand times

RCA Institutes can help find the one best for you!

Are you trying to find your way through a maze of career possibilities? Find out how RCA Institutes can start you on your way toward a well paying job in electronics. Send the attached card today!

Learn electronics at home faster, easier, almost automatically— with RCA AUTOTEXT

Are you just a beginner with an interest in the exciting field of electronics? Or, are you already earning a living in electronics and want to brush-up or expand your knowledge in a more rewarding field of electronics? In either case, AUTOTEXT, RCA Institutes' own method of Home Training will help you learn electronics more quickly and with less effort, even if you've had trouble with conventional learning methods in the past.

THOUSANDS OF WELL PAID JOBS ARE OPEN NOW TO MEN SKILLED IN ELECTRONICS!

Thousands of well paid jobs in electronics go unfilled every year because not enough men have taken the opportunity to train themselves for these openings. RCA Institutes has done something positive to help men with an aptitude and interest in electronics to qualify for these jobs.

HOME STUDY CAN TRAIN YOU FOR REWARDING CAREER OPPORTUNITIES

To help fill the "manpower gap" in the electronics field, RCA Institutes has developed a broad scope of Home Training courses, all designed to lead to a well paying career in electronics in the least possible time. You also have the opportunity to enroll in an RCA "Career Program" exclusively created to train you quickly for the job you want! Each "Career Program" starts with the amazing AUTOTEXT Programmed Instruction Method. And, all along the way, your program is supervised by RCA Institutes experts who become personally involved in your training and help you over any "rough spots" that may develop.

VARIETY OF KITS ARE YOURS TO KEEP

To give practical application to your studies, a variety of valuable RCA Institutes engineered kits are included in your program. Each kit is complete in itself, and yours to keep at no extra cost. You get the new Programmed Electronics Breadboard for limitless experiments, including building a work-

ing signal generator, multimeter, and a fully transistorized superheterodyne AM receiver.

ONLY FROM RCA INSTITUTES— TRANSISTORIZED TV KIT— VALUABLE OSCILLOSCOPE

All students receive a valuable oscilloscope. Those enrolled in the Television program receive the all-new transistorized TV Kit. Both at no extra cost and only from RCA Institutes.

CHOOSE THE "CAREER PROGRAM" THAT APPEALS MOST TO YOU

Start today on the electronics career of your choice. Pick the one that suits you best and mark it off on the attached card.

- Television Servicing
- Telecommunications
- FCC License Preparation
- Automation Electronics
- Automatic Controls
- Digital Techniques
- Industrial Electronics
- Nuclear Instrumentation
- Solid State Electronics
- Electronics Drafting

ADVANCED TRAINING

For those already working in electronics, RCA Institutes offers advanced courses. You can start on a higher level without wasting time on work you already know.

UNIQUE TUITION PLAN

With RCA Institutes Training, you progress at your own pace. You only pay for lessons as you order them. You don't sign a long-term contract. There's

no large down-payment to lose if you decide not to continue. You're never badgered for monthly payments. Even if you decide to interrupt your training at any time, you don't pay a single cent more.

CLASSROOM TRAINING ALSO AVAILABLE

If you prefer, you can attend classes at RCA Institutes Resident School, one of the largest of its kind in New York City. Coeducational classroom and laboratory training, day and evening sessions, start four times a year. Simply check "Classroom Training" on the attached card for full information.

JOB PLACEMENT SERVICE, TOO!

Companies like IBM, Bell Telephone Labs, GE, RCA, Xerox, Honeywell, Grumman, Westinghouse, and major Radio and TV Networks have regularly employed graduates through RCA Institutes' own placement service.

**SEND ATTACHED POSTAGE PAID
CARD TODAY. FREE DESCRIPTIVE
BOOK YOURS WITHOUT OBLIGATION.
NO SALESMAN WILL CALL.**

All RCA Institutes courses and programs are approved for veterans under the New G.I. Bill.

RCA INSTITUTES, DEPT. RE-78
320 West 31st Street,
New York, N.Y. 10001

Accredited Member National Home Study Council

RCA

EQUIPMENT REPORT

Sony TC-230 Stereo Tape Recorder

Circle 25 on reader's service card



SONY'S TC-230 IS JUST THE KIND OF tape recorder that warms my equipment lover's heart. It is a beautiful piece, remarkably free of the little stupidities and oversights that often creep into an otherwise good device.

Technically, the TC-230 is excellent, both by measurement and by listening test. Most attractive are the 50-dB signal-to-noise ratio, about the highest ever attained in a medium-priced home machine, and the wide frequency response even at slow tape speeds. The TC-230 records and plays at $7\frac{1}{2}$, $3\frac{3}{4}$ and $1\frac{1}{8}$ ips.

Most unusual feature of the 230 is that it can be easily made to serve as a complete home music center. Besides the usual microphone and "line" (high-level) inputs, it has a pair of RIAA-equalized phono inputs, into which any ordinary stereo phono pickup can be plugged. By adding a record changer and perhaps a tuner, you have a compact but complete stereo system . . . including four-track stereo tape recording and playback. The direct phono inputs make it unusually easy to copy discs onto tape. No external amplifier or preamp is needed.

Sound quality is somewhat limited by the small speakers and the 4-watt-per-channel output of the built-in amplifiers, but it is remarkably clean and well balanced. While I had the machine for testing I set it up in a large

loft to play some tapes for friends. Several of them were astonished at the fullness and naturalness of the reproduction via the built-in speakers. However, you can plug external speakers of your choice into a pair of jacks provided on the back panel. There is also a stereo headphone jack, on the front panel. If for any reason more amplifier power is needed, the output of the machine can be fed into an external amplifier.

Cardioid mikes are supplied with

MANUFACTURER'S SPECIFICATIONS

Tape Speeds: $7\frac{1}{2}$, $3\frac{3}{4}$, $1\frac{1}{8}$ ips
Reel size: up to 7"
Tracks: four, stereo or mono
Frequency response: 30–18,000 Hz at $7\frac{1}{2}$ ips
30–12,000 Hz at $3\frac{3}{4}$ ips
30–6,000 Hz at $1\frac{1}{8}$ ips
Signal-to-noise ratio: better than 50 dB at peak recording level, $7\frac{1}{2}$ ips
Flutter and wow:
less than 0.1% at $7\frac{1}{2}$ ips
less than 0.15% at $3\frac{3}{4}$ ips
less than 0.2% at $1\frac{1}{8}$ ips
Harmonic distortion: less than 3% at 0 dB recording level and 0.775-volt output level
Inputs: microphone—low impedance, 0.14 mV; auxiliary (tuner), 100,000 ohms, 44 mV; phono (equalized)—2 mV (voltage figures are for 0-dB recording level)
Outputs: line—into 10,000 ohms or higher, 1.1 V during playback; 0.87 V during recording
headphone—into not less than 8 ohms speaker—4 watts maximum per channel
Dimensions: (Model 230) 17" x $9\frac{5}{8}$ " x 14"
Weight: (Model 230) 29 lb
Power consumption: 55 watts
Price: Model 230: \$229.50
Model 230W: \$209.50
Model SS-23: \$69.50

the TC-230 rather than the usual omnidirectionals. They allow for flexibility in mike placement, and are particularly useful in typical home recording setups and other locations having considerable reverberation and background noise.

Controls for the Sony TC-230 are few and simple. They have a solid feel with promise of long, reliable operation. A pause control stops the tape without "switching" the electronic circuits, allowing for clickless stops and starts. It can be locked in the pause position indefinitely, and released with a slight downward push.

Volume control (a single unit for both recording and playback) has two sections, one for each channel, friction-coupled so that both knobs turn as one unless one of them is held. This arrangement is easy to use and serves simultaneously for volume and channel balance. A single tone control provides variable treble boost or cut during playback only. A noise-suppressor switch puts in a fixed upper-high-frequency cut to reduce tape hiss. Equalization is switched automatically as tape speed is changed.

Recording function is fitted with a mechanical interlock to prevent accidental tape erasure. A red indicator lamp in the level-meter assembly lights when the machine is set to record. A digital counter helps keep track of the position of a particular recording.

The recorder is so easy to thread that one can hardly speak of threading. In the stop position of the transport control, the capstan pinch roller drops out of the way, below the tape path. It is unnecessary to fumble the tape into or around anything. Simply grab the end, run it around the head housing and onto the takeup reel.

I was especially impressed with the sturdiness of the TC-230. It seems to have been built to be kicked around a bit. It is a heavy machine, but that heaviness is reassuring.

Except for the fact that it has only two heads and so cannot make sound-on-sound or echo recordings, the TC-230 is a very desirable all-around tape recorder, especially if you like to make and play tapes away from your hi-fi system with a minimum of fuss.

Another model, the TC-230W, cased in walnut and without speakers, has the same tape deck and electronics package. An accessory speaker system, SS-23, is available for the TC-230W.—*Peter Suiheim* **R-E**

The cool new "C." It has more life.

When the horizontal deflection tube in a color TV set goes dead, chances are you've been replacing it with our 6JE6-A.

(You learn by hard experience what's best. Who needs callbacks?)

But this doesn't mean that what's best can't be made even better. At least it doesn't to Sylvania electronic engineers.

That's the reason for our third-

generation 6JE6-C. (We skipped "B" altogether.)

The "C" is the new workhorse of color television.

We've given the plate wings.

It's been so designed that it acts as a superior heat sink. It holds more heat. Radiates it out from a larger surface. Dissipates it more quickly.


The new tube runs

cooler and has longer life.

And it still costs the same as the "A".

It should mean fewer replacement calls.

Try the "C" and see.

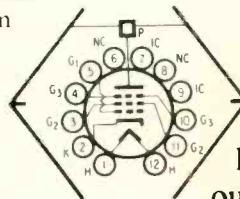


SYLVANIA
A DIVISION OF
GENERAL TELEPHONE & ELECTRONICS

Big plate fins absorb heat and radiate it out of the tube.



Circle 26 on reader's service card

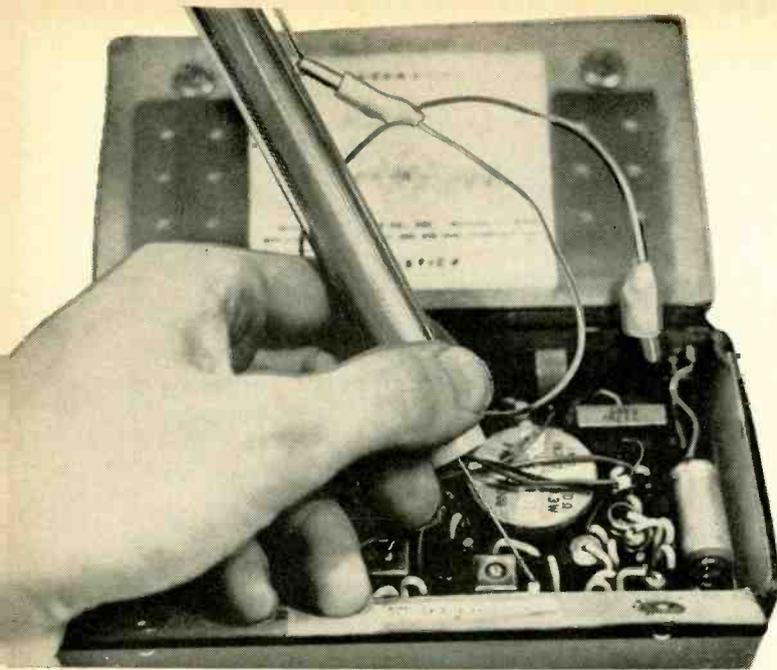

AN UNUSUAL DIODE OSCILLATOR

Solid-state analog for a neon-lamp pulse generator

By IRVING M. GOTTLIEB

THE GLOW-LAMP RELAXATION OSCILLATOR—one of the simplest and most useful of all electronic circuits—has one drawback in today's electronic technology. Its relatively high operating voltage (around 70 volts minimum) makes its use impractical in semiconductor devices.

After a lot of research, I came up with a solid-state equivalent of the glow lamp. To qualify, it had to be cheap, operate at voltages in the same range as transistors (6 to 10 volts) and work in a relaxation oscillator circuit using no more than the resistor and capacitor needed for the neon glow lamp.

Solution of the problem was not simple. Such standard semiconductor devices as four-layer diodes, unijunction transistors, tunnel diodes, avalanche transistors and SCR's all qualify, in one or more respects, as solid-state analogs of the neon lamp. None, however, comply completely with the original specifications.

Glowlamp oscillator

In the relaxation oscillator circuit of Fig. 1, capacitor C begins to charge through resistor R as soon as the switch is closed. The voltage across the capacitor rises exponentially and, without the neon lamp, for all practical purposes will eventually reach the battery-voltage level. However, before this value can be reached, the gas in the lamp ionizes (fires) and abruptly begins to discharge the capacitor. The discharge continues until the voltage across the capacitor drops to the point

where the gas in the lamp de-ionizes and extinguishes the lamp. (The de-ionization or extinguishing voltage is only a few volts lower than the ionization or firing voltage.)

The capacitor, now rid of the short circuit produced by the ionized lamp, resumes its charging cycle. Thus, after the relatively long initial charging time, repetitive charge-discharge cycles occur with peak amplitude equal to the firing voltage minus the extinguishing voltage.

Solid-state switch

I felt that the avalanche transistor would satisfy all conditions as a replacement for the glow lamp if its breakdown voltage (see Fig. 2) could be reduced to a value much lower than

the several tens of volts of commercially available units. Aside from the incompatibility with transistor circuit supply voltages, the big disadvantage of breakdown voltages of 25 to 50 is the high power that the junction must dissipate.

High power dissipation develops heat which, in turn, leads to unreliable and unstable oscillations. Clearly, what was needed was a transistor with reverse-voltage breakdown below 10 volts. After some seeking, I found that such transistors are produced but they are not readily identifiable from their published characteristics.

Circuit designers rarely consider the *reverse-breakdown* ratings of the emitter-base diode in conventional transistors because most transistor applications do not involve this param-

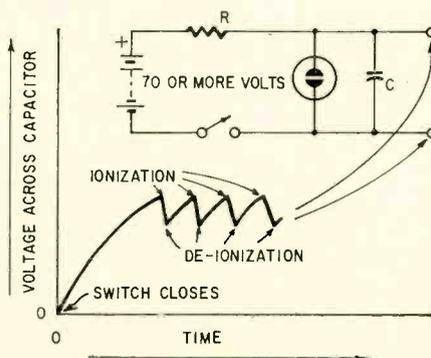


Fig. 1—Glow-lamp relaxation oscillator and output waveform. High voltage need makes lamp impractical for solid state.


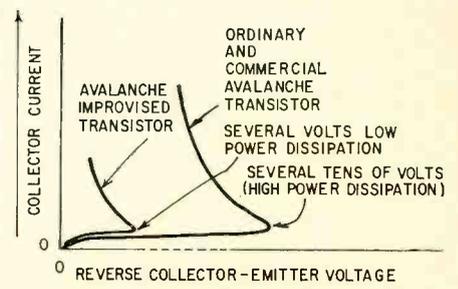


Fig. 2—Comparative $I_C-V_{CB (rev.)}$ curves for ordinary and avalanche transistors and for the avalanche transistor adapted for use as a low-voltage oscillator. Low power dissipation aids circuit stability.

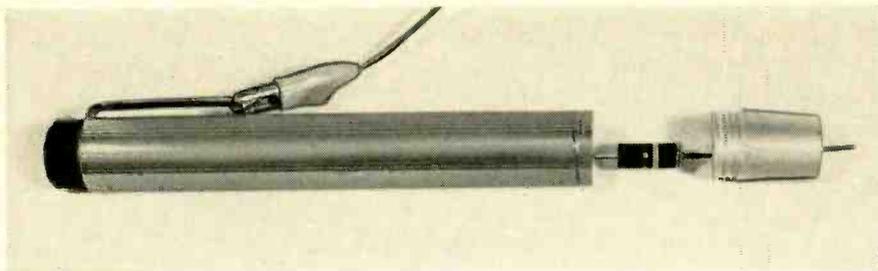

Use the solid-state "glow-lamp" oscillator as signal injector to test radios and amplifiers. The 47K series resistor in the hot output lead minimizes circuit loading.

ter. Keep in mind for a moment that this breakdown potential is only 4 or 5 volts for many transistors. A second important fact about transistors is that the connections to collector and emitter can be *interchanged*. This was done in some circuits in the early days of the junction transistor. Some of the first junction transistors had an alpha of about 0.925 in a grounded-base circuit. The same transistor would develop an alpha around 0.875 when the emitter and collector connections were interchanged, together with bias polarities.

Thus, it can be demonstrated (Fig. 3) that the transistor is a bilateral device, capable of producing power gain in both directions. [At

least one manufacturer of solid-state SSB transceivers uses the bilateral characteristic of transistors to simplify circuit design.—*Editor*] Most modern transistors have very high alphas in the intended connection and relatively low alphas when the collector and emitter leads are interchanged. Therefore, all we need is a transistor that will develop sufficient current gain when emitter and collector are transposed.

After much research and experimentation, I found that the 2N3643 (Fairchild) filled the bill nicely. It is a low-cost epoxy-encapsulated silicon npn transistor. When connected as a two-terminal device as in Fig. 4 (no connection to the base) strong oscillations develop as the result of the 4- or

5-volt breakdown of the reverse-biased emitter-base diode.*

As an avalanche device the 2N3643, with its breakdown potential of only a few volts, is much more stable, more practical and less costly than commercial units with breakdown voltages many times higher.

The circuit of the low-voltage avalanche oscillator is shown in Fig. 5. By merely transposing the emitter and collector, together with voltage polarities, we have a solid-state "neon lamp" with ionization and de-ionization potentials of only 4 or 5 volts. As a pulse generator, it is extremely useful as a low-cost substitute for such more complex and expensive devices as feedback oscillators and multivibrators.

In addition, this diode oscillator is superior to the glow lamp in all respects. It is immune to electrostatic and electromagnetic fields, light, mechanical shock and vibration and is much less affected by temperature than are glow lamps. **R-E**

*This bias appears across the base-emitter junction as a result of the collector-emitter voltage being polarized for forward conduction. This is the normal operating mode for avalanche transistor oscillators. For details, refer to "avalanche transistor" and "charge, carrier or collector multiplication" in semiconductor manuals, handbooks and textbooks.

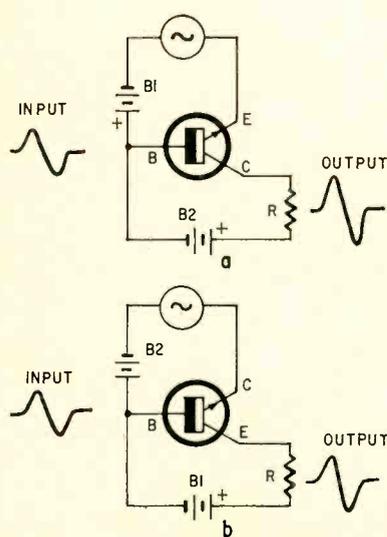


Fig. 3—An npn grounded-base transistor amplifier (a) has high power and voltage gains with slight current loss. Transposing emitter and collector and reversing bias polarities (b) results in considerable current loss, moderate voltage gain and possibly some power gain as well.


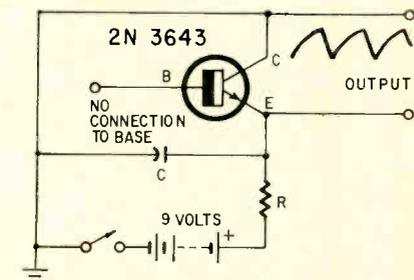
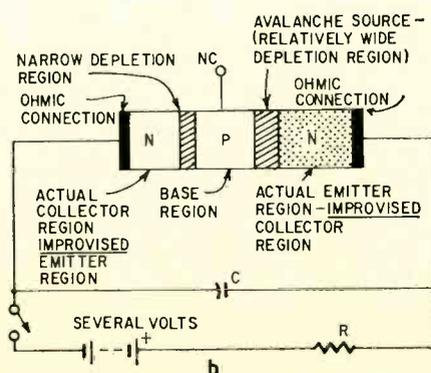


Fig. 5—Circuit of the solid-state "glow-lamp" oscillator. Pulse rates up to about 100 kHz are possible with appropriate values of R and C. Frequency is about 1 kHz when R is 1200 ohms and C is 1 μ F.

Fig. 4—Avalanche oscillators. In a conventional transistor (a), the depletion region (an area spanning a pn junction and containing comparatively few free electrons) around the collector-base junction is very wide and the one around the base-emitter junction is narrow. The improvised avalanche transistor at b operates with a much lower power supply and with emitter and collector transposed.

There's no substitute
for **SUCCESS...**

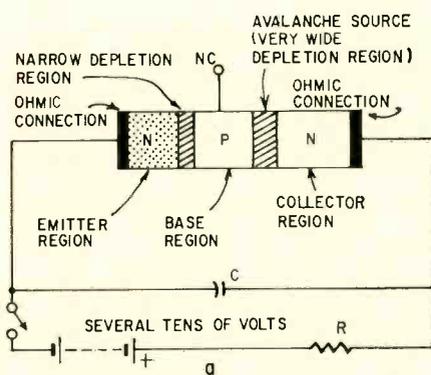

JAMES WONG—Research Engineer
Heald Engineering College Graduate

or IN-CLASS INSTRUCTION!

In electronics, it's the training that makes the difference. Employers require well-trained men and the first thing checked is where you gained your knowledge.

HEALD GRADUATES have many job offers with starting salaries often in excess of \$10,000 per year. AND advancement is rapid.

GET STARTED NOW. Be a
DRAFTSMAN---12 months
TECHNICIAN---15 months
ENGINEER (B.S. Deg.)---30 months
ARCHITECT (B.S. Deg.)---36 months

YOU are eligible for HEALD ENGINEERING COLLEGE if you have a high school education or the equivalent.

Increased income starts with success-- success starts with your move to Heald. Send now for FREE brochures with more information on Heald in San Francisco and your future in Engineering.

FREE LIFETIME PLACEMENT SERVICE
VETERAN APPROVED



WRITE TODAY FOR DETAILS

HEALD Engineering College

1215 Van Ness Ave., San Francisco, California 94109

Please send me information about:

- ARCHITECTURE
ENGINEERING: Civil Electrical
Electronic Mechanical
TECHNOLOGY: Electronic Engineering
Technician (FCC)
Radio-Television Technician (FCC)
DRAFTING: Mechanical Electrical
Structural
I am interested in Day Evening courses
Also send an application.

NAME _____ AGE _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____ PHONE _____

Service Clinic

By JACK DARR

Matching speakers

I have a mail-order TV set with a 10-watt audio output. I'd like to hook up two 3.2-ohm speakers, rated at 10 watts each, to the output. The set now has three speakers, 6-8 ohms, and one 6AQ5 tube. —R. K., Glendale Heights, Ill.

Your three original speakers are hooked in parallel; therefore, your output transformer has a 3-ohm impedance. If you want to get full power, you'll have to replace the original transformer with one rated at 5,000 ohms plate to 6-8 ohms voice coil. Then, you can hook the two new speakers in parallel and get 6 ohms.

Incidentally, if your set has a single 6AQ5 tube (electrical equivalent of 6V6) you have only about 4.5 watts of power! Not 10. Advertising men often get carried away! The RCA tube manual shows only 4.5 watts *maximum* power from a single 6V6/6AQ5.

By the way, 5 watts of audio power is a good deal—more than you can stand to use in the average room. However, if you do want more, I'd suggest building a small two-tube push-pull output stage, using two 6V6's, with their own power supply, and mounting this somewhere inside the cabinet. For a schematic on such a booster, use the push-pull output stage of any PA system of this wattage, hi-fi, radio set, etc. Standard circuit.

No contrast

I'm working on a Motorola TS-534 chassis, and the contrast is very poor. Even with the contrast control all the way up, it's pale. Schematic calls for +75 volts on the video amplifier plate and I'm reading +160 volts. The agc keyer grid calls for +70 volts; I read +150. Could this be agc trouble? —M.M., Hawk Run, Pa.

High plate voltage on an amplifier stage (of any kind) with normal

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. S., New York 10003.


supply voltage means only one thing—low plate *current*. This, of course, means low stage *gain*.

Several things can cause this: incorrect grid bias, low plate-load resistors, weak tube, and so on. In this set, your voltage is fed through 10,000- and 12,000-ohm resistors in series (see diagram). This also feeds dc to the grid of the keyer, thus accounting for the higher than normal voltage there.

In some of these chassis, we've found the plate dropping resistors burned up, from a short in a previous 12BY7 video-amplifier tube. Check those resistors; if okay, check the control grid voltage on the video-amplifier tube. This should be almost zero.

You can make a gain check on this stage with an audio signal. Feed in about 1.5 volts p-p, and check for an output 45-50 volts p-p on the plate. Any values can be used, as long as you get a gain ratio of about this much. Loss of contrast can be loss of gain in a video-amplifier stage; it can also be weak signal *input*. Check the grid signal, on a normal TV channel. If this isn't up around 1.5 volts p-p, your trouble is "farther forward"—i.f., tuner, antenna or agc.

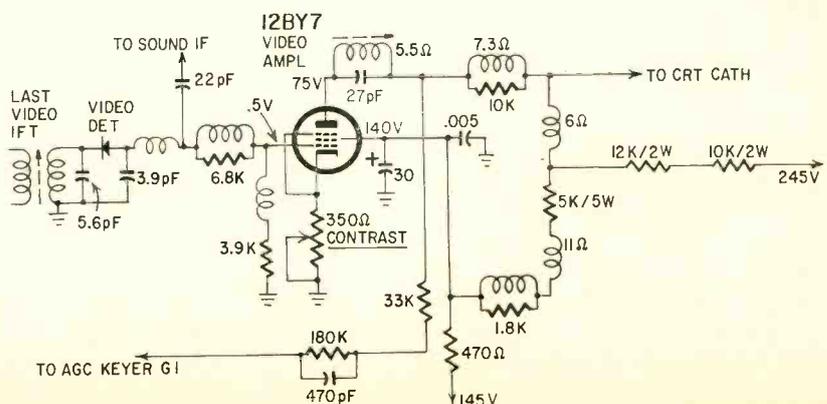Check the agc by overriding it. Also, check that 8.2-meg resistor from the 245-volt B+ line to the agc line. If the resistor changes in value, it'll cause trouble. **R-E**



Circle 27 on reader's service card

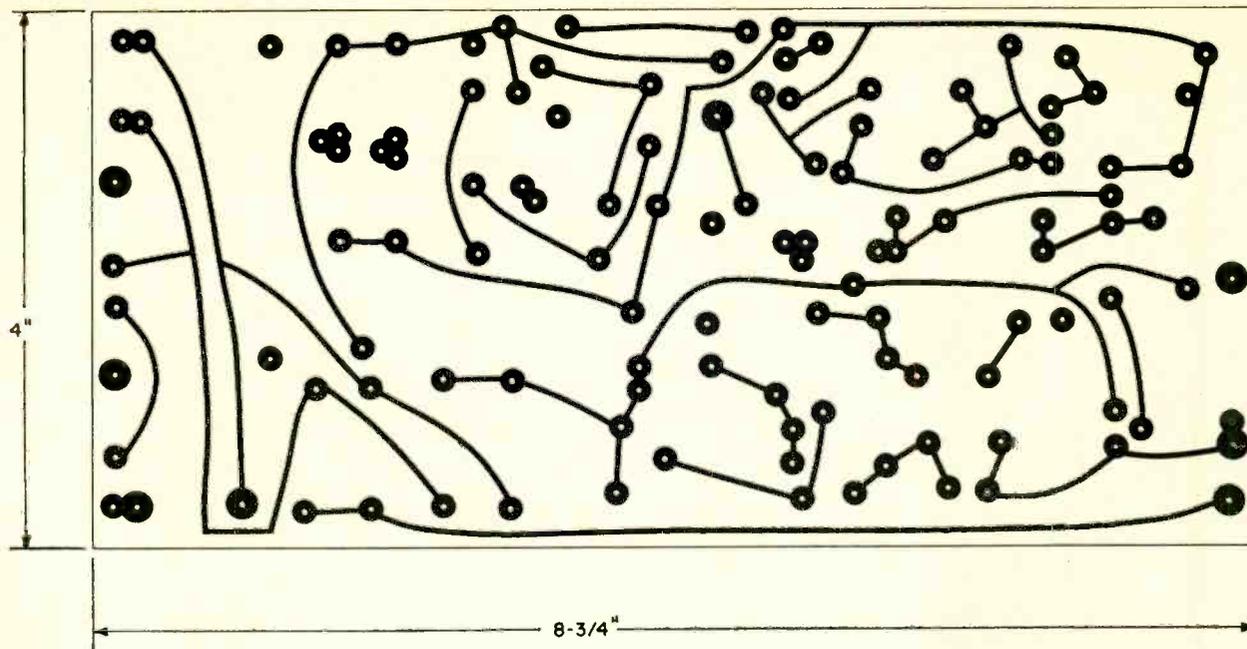


Fig. 3—Use this pattern to make the printed board for Rhythm Lights. You will need a copper-clad board 9½" x 5½", a pint of etching liquid, 1/16" resist tape, 3/16" resist circles, and a plastic container in which to immerse the board for etching.

BUILD RHYTHM LIGHTS

(continued from page 35)

with a brilliant color array.

Assembly and wiring of Rhythm Lights is easy. All the components are laid out on a printed-circuit board which is enclosed in a simple, one-piece chassis. All components used are available at most electronic distributors.

Circuit operation

A crystal microphone picks up sound from radio, hi-fi or musical instruments. The high-impedance microphone is directly coupled to transistor Q1 (Fig. 1); this transistor is a grounded-emitter stage with feedback from collector to base for stability. A 100-pF capacitor (C12) decouples the power supply from this low-level first stage. The signal next goes to transistor Q2. Resistor R3 established Q2's operating point and capacitor C4 reduces high-frequency signals. Final amplification takes place at transistor Q3. Volume is controlled by 10,000-ohm pot R11, which acts as part of the bias network for Q3. Diode D1 compensates for temperature effects on Q3.

Transformer T1 isolates the low-voltage amplifier stages from the high-voltage, lamp-driving stage. The signal is rectified by diode D7. Capacitors C8 and C9 limit the frequency response to about 500 Hz. Trigger diode D13, and R12—BRIGHTNESS—set the level at which the SCR (Q4) conducts. The

SCR drives the lamps to various brightness levels and is powered through bridge rectifier circuit D9–D12.

Neon lamp PL1 indicates power is on. Transformer T2 supplies 12 volts for the amplifier.

Construction

If you use the printed board layout shown in Fig. 3 you should have no trouble with assembly. Parts placement is shown in Fig. 2. I put the assembled board in an aluminum chassis covered with contract paper on which I lettered the names of the controls. I punched a hole in one end of the chassis for the microphone.

All controls and the flood-lamp receptacle are mounted on the front cover. Use a three-wire power cord for safety—the ground wire should be connected internally to the chassis and go to a grounded receptacle. Keep all wires insulated and cover all line-voltage terminals with electrical tape to reduce possible accidents. A neat wiring job can keep you out of trouble.

The microphone can be mounted externally or you can mount it inside the chassis as I did. Sensitivity of the amplifier is good; therefore, mike location isn't critical. Transistors Q1 and Q2 are soldered directly into the printed circuit board—be sure to heat sink the leads when soldering. A low-wattage soldering iron is recommended. Use a heat sink with SCR Q4; this precaution will extend its life.

Four standoffs are used to mount the printed board to the cover. The cover in turn is screwed to the aluminum chassis with sheet-metal screws. Transformer T1 and T2 are mounted on the printed board. Very little hardware is needed for the construction, wiring is simple, so assembly time is not long. If good quality components are used, your Rhythm Lights should operate satisfactorily for many years.

Using Rhythm Lights

Apply power to the unit and turn on S2. Turn BRIGHTNESS and VOLUME controls fully counterclockwise. Then plug a flood light or spotlight into the receptacle. Advance the BRIGHTNESS control until the light barely glows. Furnish music at a normal level and turn up VOLUME until the music turns on the light. For best results, two 150-watt flood lamps of different colors should be used in a semi-dark room. The results are dramatic.

Switch S1 is a remote on-off device. You can use lamp cord of almost any length, since only 12 volts dc is present in the circuit. This switch opens the emitter circuit of the final amplifier stage (Q3), disconnecting the input signal. Lamp intensity can still be controlled, however, with the BRIGHTNESS control. Another effect you might want to try: Hook up a string of Christmas-tree lights to the unit. Use your imagination; you'll find many interesting applications for Rhythm Lights. **R-E**

RADIO-ELECTRONICS READER'S SERVICE

Here's how you can get manufacturers' literature fast.

1. Tear out the post card on the facing page. Clearly print or type your name and address.

Include zip code! Manufacturers will not guarantee to fill your requests unless your zip code is on the reader service card.

2. Circle the number on the card that corresponds to the number appearing at the bottom of the **New Products, New Literature** or **Equipment Report** in which you are interested.

For literature on products **advertised** in this issue, circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested. Use the convenience index below to locate quickly a particular advertisement.

3. Mail the card to us (no postage required in U.S.A.)

Advertisements in this issue offering free literature (see the advertisement for products being advertised):


ALLIED RADIO CORPORATION (Pg. 92)	Circle 121
AMPEREX ELECTRONIC CORPORATION (Pg. 7)	Circle 11
ARCTURUS ELECTRONICS CORPORATION (Pg. 94)	Circle 124
ARTISAN ORGANS (Pg. 81)	Circle 110
B & K (Division of Dynascan Corporation) (Pg. 15)	Circle 15
B & K (Division of Dynascan Corporation) (Pg. 25)	Circle 20
BROOKS RADIO & TV CORPORATION (Pgs. 90-91)	Circle 120
BURSTEIN-APPLEBEE COMPANY (Pg. 89)	Circle 116
CARINGELLA ELECTRONICS, INC. (Pg. 26)	Circle 21
CLEVELAND INSTITUTE OF ELECTRONICS (Pgs. 28-31)	Circle 24
CLEVELAND INSTITUTE OF ELECTRONICS (Slide Rule) (Pg. 81)	Circle 108
CORNELL ELECTRONICS COMPANY (Pg. 96)	Circle 129
DELTA PRODUCTS, INC. (Pg. 14)	Circle 12
DELTA PRODUCTS, INC. (Pg. 84)	Circle 112
EDMUND SCIENTIFIC COMPANY (Pg. 95)	Circle 126
EICO ELECTRONIC INSTRUMENT COMPANY, INC. (Cover II)	Circle 7
ELECTRO-VOICE, INC. (Pg. 6)	Circle 10
EUPHONICS MARKETING (Pg. 89)	Circle 117
GAVIN INSTRUMENTS, INC. (Subsidiary of Advance Ross Corporation) (Cover III)	Circle 150
GBC CLOSED CIRCUIT TV CORPORATION (Pg. 24)	Circle 19
GRANTHAM SCHOOL OF ELECTRONICS (Pg. 1)	Circle 8

HEALD COLLEGES (Pg. 70)	Circle 27
HEATH COMPANY (Pgs. 22-23)	Circle 18
HEATH COMPANY (Pg. 79)	Circle 107
INDIANA HOME STUDY INSTITUTE, THE (Pg. 85)	Circle 113
INTERNATIONAL CORRESPONDENCE SCHOOLS (Pg. 5)	Circle 9
INTERNATIONAL CRYSTAL MFG. COMPANY (Pg. 98)	Circle 149
KARLSON RESEARCH AND MANUFACTURING (Pg. 90)	Circle 118
KENWOOD (Pg. 26)	Circle 22
KENZAC (Pg. 94)	Circle 125
MOSLEY ELECTRONICS, INC. (Pg. 88)	Circle 115
MUSIC ASSOCIATED (Pg. 81)	Circle 109
OLSON ELECTRONICS, INC. (Pg. 93)	Circle 123
POLY PAKS (Pg. 97)	Circle 130
QUIETROLE COMPANY (Pg. 92)	Circle 122
READING IMPROVEMENT PROGRAM (Pg. 91)	Circle 119
SAMS & COMPANY, INC. HOWARD W. (Pg. 12)	Circle 14
SHURE BROTHERS (Pg. 13)	Circle 13
SIMPSON ELECTRIC COMPANY (Pg. 27)	Circle 23
SOLID STATE SALES (Pg. 95)	Circle 127
SPRAGUE PRODUCTS COMPANY (Pg. 16)	Circle 16
SYLVANIA (Subsidiary of General Telephone & Electronics) (Pg. 67)	Circle 25
TAB BOOKS (Pg. 82)	Circle 111
VACO PRODUCTS COMPANY (Pg. 77)	Circle 106
WARREN ELECTRONIC COMPONENTS (Pg. 96)	Circle 128
WELLER ELECTRIC COMPANY (Pg. 87)	Circle 114
ZENITH (Pg. 17)	Circle 17

NEW PRODUCTS

More information on new products is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader's Service Card facing page 72 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.

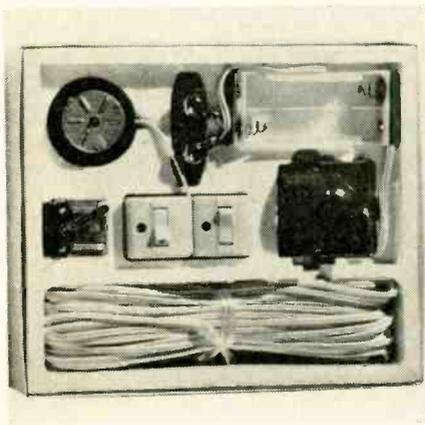
BURGLAR & FIRE ALARM, Model SW-391. Easy-to-install system protects your home or business against fire and



theft. Operates 24 hours a day on its own power supply. (No power is used unless alarm is activated.) Kit includes motor-type siren, 1 fire-sensing switch, 1 door or window switch, 1 master switch, 1 door override switch, terminal block, battery holder and 100 feet of wire. Complete with instructions. \$19.98—Olson Electronics, Inc.

Circle 46 on reader's service card

SIMULATED COMPUTER, Digi-comp II. This model digital computer is designed to solve problems; is said to be the first mechanical computer that has automatic switch action. Requiring no

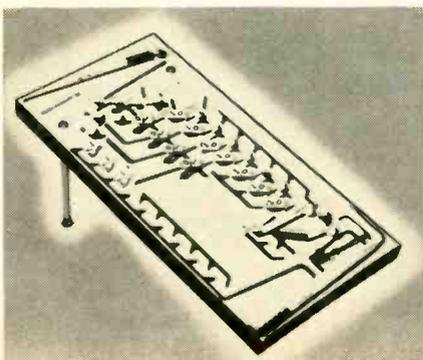


JULY 1968

power source, the unit visually simulates electric currents of an electronic computer by marbles rolling through its mechanism. Features a 4-unit memory register, 3-unit multiplier-quotient register, 7-unit accumulator register and an overflow switch. \$16.—Edmund Scientific Co.

Circle 47 on reader's service card

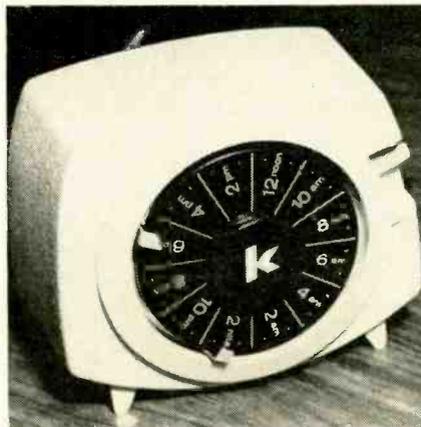
ALL-PURPOSE TIMER. Designed to handle loads of up to 185 watts, the



device turns lights and appliances on or off at preset times. The operation automatically repeats every 24 hours. Minimum "on" interval is 15 minutes, maximum is 23¼ hours. No special wiring is needed . . . equipment to be controlled is simply plugged into the timer. Supplied with 6' line cord. \$8.77—ALLIED RADIO CORP.

Circle 48 on reader's service card

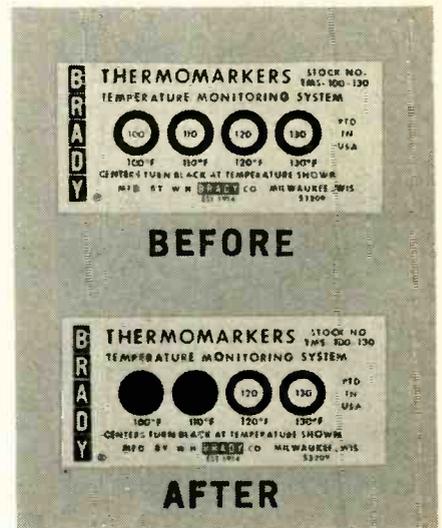
PLASTIC FILM MARKERS, Thermo-markers. Markers with one heat-indicating circle are 7/8" square. They are available from 100°F in 10° intervals per marker through 500°F. Markers with four progressively higher heat-indication circles are 7/8" x 1¼" and range from 100°F. When temperature at each circle is attained, the circle turns permanently black. Thermomarkers are suitable for



monitoring temperatures where more elaborate methods are impractical and accuracy is essential.—W. H. Brady Co.

Circle 49 on reader's service card

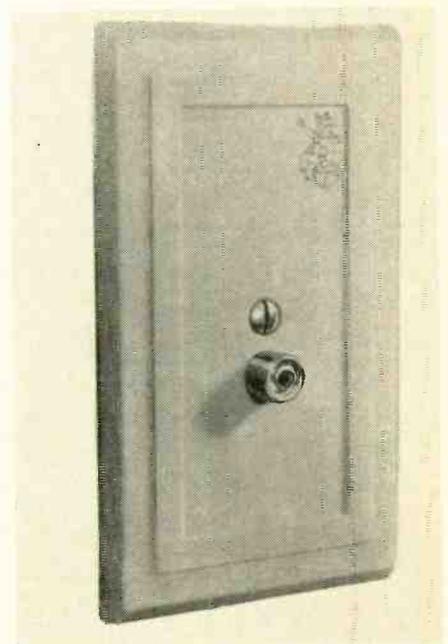WALL TAPS, Model MC-1 with no resistors and an swr of 1.5/1 or better is used as a single lead-in outlet. One to four taps possible to coax lead-in. For larger amplified systems, three wall tap models are available in varying isolation



values with a low insertion loss and an swr of 1.5/1 or better. All feature solderless connections with crimp-on ferrules. Taps may be mounted in a plaster ring or in a standard electrical box.—Mosley Electronics, Inc.

Circle 50 on reader's service card

NEW AUDIO EQUIPMENT


RECEIVER/TURNTABLE, *Nocturne Plus*, Model SC 7. Combination of a 60-watt AM/FM/FM-stereo Nocturne receiver with a professional Dual 1009SK automatic turntable in walnut case. Enables use of any speaker system regardless of size, efficiency or impedance. Re-



ceiver will drive up to four speakers simultaneously. Employs a MOSFET FM front end for better performance. Microcircuits in the i.f. strip for good performance with stereo separation and noise rejection, ultra-sensitive AM delivers clear broadcast reception without noise or fading. \$450.00—Harman-Kardon, Inc.

Circle 51 on reader's service card

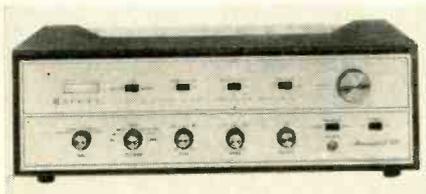
AMPLIFIER KIT, *Scott LK-60B*. 120 watts, solid-state stereo. If a wiring error has been made, a fail-safe circuit absorbs excess power when the unit is first turned on. It causes a light bulb to glow thus warning the kit-builder that he



must recheck wiring. Uses pre-tested components including heat sinks, printed circuit boards and silicon output transistors. Features circuit monitor, rumble and scratch filters, headset output, and dual-speaker switch for selecting main, remote or both sets of speakers.—H. H. Scott, Inc.

Circle 52 on reader's service card

STEREO AMPLIFIER, *PCA-6A-25*. Assembled unit 20-watt comes ready to use when connected to a sound source and speaker system. Circuit has a three-stage dc-coupled power amplifier with a thermistor for temperature stabilization. Also available as a two-piece assembly for mounting into compact phonographs (PCA-6A-25S CS). Load impedance: 8 ohms; input impedance: 500,000 ohms; input sensitivity: 0.5V; power output:

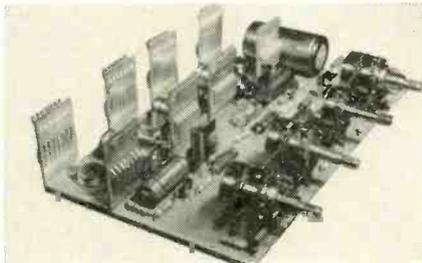

10W (per channel) at 1 kHz and 8 ohms; current: 35 mA (idle) 560 mA (max.). Frequency response: 30 Hz–50 kHz at –3 dB.—Amperex Electronic Corp., Distributor Sales Dept.

Circle 53 on reader's service card

AM/FM STEREO RECEIVER, *LR-1500T*. Offers 63-transistor performance using 4 IC's, each containing 5 transistors and 2 resistors, 2 high-performance field-effect transistors, 41 transistors, 40 diodes and 2 thermistors. Power output: 175 watts IHF at 4 ohms; harmonic distortion:



under 1%; frequency response: 20–20,000 Hz. Power bandwidth: 25–35,000 Hz; selectivity: 40 dB at 400 Hz; S/N ratio (100% modulation): 68 dB. Spurious response rejection: 95 dB; sensitivity: 1.5 μ V. Output impedance: 4–8–16 ohms. \$279.95—Lafayette Radio Electronics

Circle 54 on reader's service card

VIDEO TAPE RECORDER AND CAMERA. Battery-operated and easy to carry, the recorder is about the size of a small attaché case. VTR weighs only 11



lb and operates on a self-contained battery. It records black-and-white pictures, with sound, for immediate playback on CV-2000 series video tape recorders. Device uses a 20-minute, $\frac{1}{2}$ " tape with a 7 $\frac{1}{2}$ " ips speed. Only 2 buttons are used

for simple operation. Video camera connects to VTR with single cable for video, sound and power. Total price, including VTR, camera, zoom lens, microphone, battery and charger, is \$1250.—Sony Corp. of America

Circle 55 on reader's service card


AUTOMATIC TURNTABLE, *Module SLx*. Has a new light and thin tone arm to permit a counterbalance of small size and light weight and to keep tracking force to a minimum. Features Synchro-Lab motor, magnetic cartridge with diamond stylus, cueing and pause control, adjustable stylus pressure gauge, over-



sized turntable, interchangeable spindles. Compact unit is housed in a simulated walnut and ebony case highlighted by silver trim. \$69.50—Garrard, Div. British Industries Corp.

Circle 56 on reader's service card

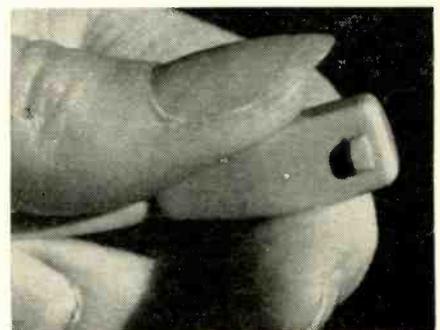SUBMINIATURE MICROPHONE, *Micro-Mike*. Self-shielded against external fields, it has a nominal impedance of 5000 ohms at 1 kHz. Response is from 400 to 5000 Hz and typical sensitivity is 80 dB below 1 volt per dyne/sq cm rms pressure. Measuring only 1" x 0.365" x 0.285", the new microphone is ideal for




pocket transmitters, tape recorders or other applications where extremely small size and weight are important. The 3-wire shielded cable supplied matches the flesh-colored plastic case.—Unex Laboratories

Circle 57 on readers' service card

NEW TEST EQUIPMENT

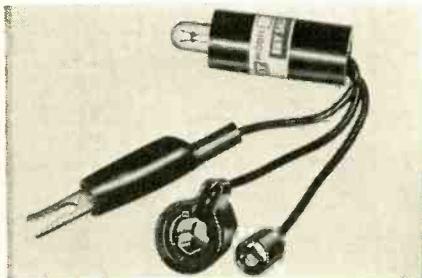MINIMUM-CATHODE-CURRENT INDICATOR, No. MCC-1. Permits technicians to replace or adjust horizontal output tubes for minimum cathode current quickly, easily and accurately. Has



universal application and can be used with all novar, compactron octal and noval tubes in use as horizontal outputs. After attaching the indicator as directed its bulb will glow and the tube can be adjusted for minimum output. \$3.00—Eby Sales Co., Inc.

Circle 58 on reader's service card


PUSHBUTTON BATTERY-OPERATED VOM, Model 601 Type I. Measures dc voltage, ac rms values, resistances, ac/dc, decibels on 10 ranges and the condition



of its batteries. Accuracy: $\pm 2\%$ on dc and $\pm 3\%$ for ac. Frequency response on ac is 50 Hz to 50 kHz. Decibels: -40 dB to +60 dB. Four functional pushbutton selector switches are located at the left side of the aluminum front panel for easy selection of dc volts (+) ohms; dc volts (-) ohms; ac volts and low-power ohms. A complement of AA penlight cells powers the unit, and are furnished with each set. Price is \$125, complete with test probes and operating instructions. Leather carrying case is available at \$14.70.—Triplett Electrical Instrument Co.

Circle 59 on reader's service card

COLOR ALIGNMENT GENERATOR, Model 865 Deluxe Color Commander. New instrument provides nine patterns. The three-bar color pattern eliminates all but the three bars used for color demodulator alignment: Red (R - Y) is at 90°; blue (B - Y) at 180°, and green (R - Y) at 270°. Calibrated crosshatch display provides a pattern with a 3:4 aspect ratio: 15 horizontal and 20 vertical lines. Unit is styled in a smart, luggage-type case featuring a large storage area for probes,

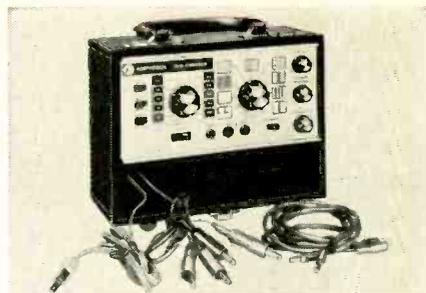

tubes, etc. Operates on 117 V ac or on self-contained batteries. Automatic shut off when lid is closed. \$189.95 less batteries.—Amphenol Distributor Div.

Circle 60 on reader's service card

The Enforcer

Pack a powerful punch for solving special fastening problems. For instance, take the **Vaco Pow'Rivet**, the first major advancement in blind rivet design. Adapts itself to over-size holes assuring a powerful clamp up action every time. Only 4 sizes do the job of 11 ordinary type rivets

Or maybe you have wiring problems involving splicing, connecting, or terminating. **VACO SOLDERLESS TERMINALS** are available in hundreds of different sizes and styles, both insulated and non-insulated, for guaranteed fast and dependable service.

SNAP RINGS? We have them, both internal and external, for retaining those tricky bearings, pinions, gears.


See your local Vaco distributor for your supply of special fasteners in handy see-thru paks . . . plus the right tools for easy application.

VACO Products Company
510 N. Dearborn Street
Chicago, Illinois 60610

Circle 106 on reader's service card

New Test Equipment
continued

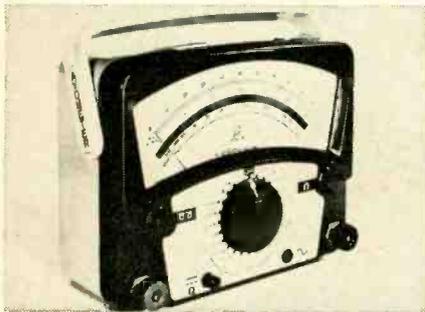
MULTIMETER, AVOMeter Model 16. Has 36 ranges and features 20,000-ohm/volt sensitivity. Metal-film resistors are used throughout, guaranteeing an accuracy of 1%. Unit is fully protected by a



velocity-actuated cutout in addition to solid-state protection of the rectifier and fused resistance ranges.—Whittaker Corp., Gencom Div.

Circle 61 on reader's service card

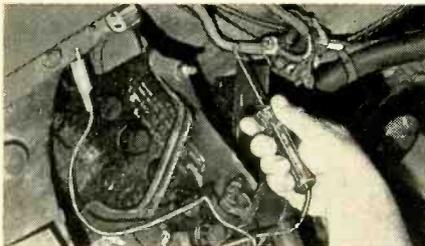
CIRCUIT TESTER, No. TK 550. Tests 6- and 12-volt circuits for automotive electrical systems, lamps, bulbs, wire connectors, field coils, switches, etc. Consists of a pointed prod attached to a han-



dle which has a ground wire with alligator clip. If circuit being tested is alive, the handle lights up when the prod pierces a wire's insulation. \$2.50.—VACO Products Co.

Circle 62 on reader's service card

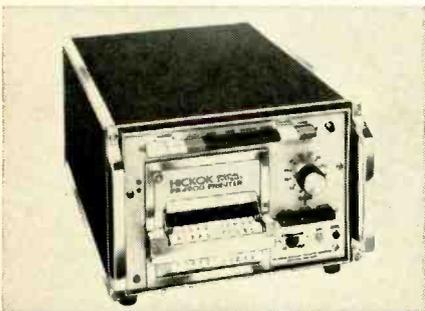IC DIGITAL[®] PRINTER, Model PR-4900. Records voltage, frequency, time period, resistance, capacitance or event counts. Up to 10 lines of numeric and coded data can be printed from one or



two independent digital systems. Print can be remote, local or at calibrated time intervals. Maximum print rate from external command pulses is 1/sec.—Hickok Electrical Instrument Co. R-E

Circle 63 on reader's service card

NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader's Service number are free for the asking. Turn to the Reader's Service Card facing page 72 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

TECHNICAL DATA BROCHURE. 80 pages of data on 15 functions in the MTLT I IC family and 9 functions which feature a typical propagation delay of 10 nanoseconds. High-speed MTLT II IC circuits have a propagation delay of 6.0 nanoseconds. Sections are indexed by function, and an introduction to each section provides reader with typical characteristics, breadboarding suggestions, package dimensions and additional information.—Motorola Semiconductor Products, Inc.

Circle 64 on reader's service card

NEON GLOW LAMPS. 8-page illustrated brochure gives a complete description of how to evaluate and apply glow lamps. It includes discussions on light output, lamp longevity, and external conditions acting on the glow lamp. Features an ionization time vs percent over-voltage graph, a circuit drawing showing various breakdown measurements and a compilation of clearly defined, relevant terms. Charts give breakdown voltages, lamp measurements and electrical characteristics.—Signalite, Inc.

Circle 65 on reader's service card

HI-FI LOUDSPEAKER SYSTEM COMPONENTS. Instruction Note No. 242 gives information for custom assembly or upgrading of 2-, 3- and 4-way loudspeaker systems. Six-page folder has charts illustrating specs and hookup procedures for 25 systems with comparisons of orchestral frequency ranges. Also describes 26 loudspeaker components. Instructions include: circuit connections, mounting system components, constructing acoustic enclosures, adjusting balance controls and locating speaker systems within a room.—Jensen Manufacturing Div./The Muter Co.

Circle 66 on reader's service card

ELECTRONIC COURSE. You can break into electronics. It will call for some training, but you won't have to quit your job or turn your life upside-down to get it. CIE will teach you at home. Auto-programmed lessons help you to master the electronics you will need for a rewarding career. Two free books. *HOW TO SUCCEED IN ELECTRONICS* and *HOW TO GET A COMMERCIAL FCC LICENSE*, tell about careers in the field and how you can prepare for them in your spare time.—Cleveland Institute of Electronics

Circle 67 on reader's service card

COLOR ELECTROLYTIC CAPACITORS. Six-page brochure lists over 250 wide-range electrolytics of the single-, dual-, triple- and quadruple-section types. These units will replace 2500 varieties. Listing provides a blank space beside each rating which is useful in inventory taking, price notations, product movement indication, etc.—Cornell-Dubilier Electronics

Circle 68 on reader's service card

SHORT-FORM CATALOG. 25-page book covers major product categories such as jacks, plugs, switches, connectors, indicating devices and audio accessories. Information is condensed. The electronic components illustrated and described are items stocked by Switchcraft's nationwide network of industrial distributors. Covers computers, analyzers, transmitters, receivers, intercoms, etc.—Switchcraft, Inc.

Circle 69 on reader's service card

COLOR TV COILS. Four-page cross-reference guide for 12 new color TV coils is now available. Listing provides exact replacements for 550 video and chroma coils for sets produced by virtually all manufacturers. Guide is easy to follow, informative and to the point. This booklet will be useful to TV service technicians, hobbyists and do-it-yourselfers who need a quick-reference guide to replace coils on color TV's.—J. W. Miller Co.

Circle 70 on reader's service card

BASE STATION ANTENNAS, Models BB-2534 and BB3450. First model covers 25-35 MHz and second covers 34-50 MHz. Brochure gives specs, features, benefits and ordering instructions. Also lists a variety of mobile antennas in 25-50-MHz range.—New-Tronics Corp.

Circle 71 on reader's service card

POTENTIOMETERS, RESISTORS, 32-page illustrated catalog includes photos, engineering drawings and descriptions of field-assembled controls, sound-system attenuators and many more. Complete technical specs and dimensional information are included. Special section describes military-qualified potentiometers.—Clarostat Mfg. Co., Inc., Distributor Div.

Circle 72 on reader's service card

PHONOGRAPH NEEDLES/ACCESSORY PRODUCTS, Form 6707. 14th edition of catalog and reference guide provides complete information on phonograph needles plus expanded line of accessories, including reel-to-reel tapes, cassettes, and tape recorder, tape cartridge, guitar and record accessories. Needles are indexed by cartridge number and/or manufacturer, competitive needle number and by phonograph model. 44-page catalog includes photos, specs and features.—Recoton Corp.

Circle 73 on reader's service card

1967/68 CB CATALOG, No. C-175. 12 pages of CB equipment, antennas and accessories. Lists features, model numbers and nearest stores for ordering convenience. Flyers also available.—Mosley Electronics Inc. R-E

Circle 74 on reader's service card

Write direct to the manufacturers for information on items listed below:

NOISE CALCULATOR. Ten scales incorporated in this slide rule-type noise calculator enable the user to perform various noise computations. Included are scales to determine thermal noise voltage and current developed by a resistor; shot-noise voltage and current developed by a transistor or diode junction, and noise figure for a given source resistance from the spectral density. Other scales permit conversion of resistor noise index to $\mu V/V$ and determination of noise in a given bandwidth from the spectral density. Available when requested on your company letterhead from: **Quan-Tech Laboratories**, 43 South Jefferson Road, Whippany, N.J., 07981.

MANUFACTURING QUALITY CONTROL. 120-page programed workbook provides practice problems and assignments in quality-control training. Furnishes the major essentials plus simplified data based on experience in actual industrial applications and production situations. Emphasis is on methodology and philosophy of statistical control as a practical working tool. Available without charge if requested on your company letterhead from: **Advertising Dept., General Instrument Corporation**, P.O. Box 600, Hicksville, New York 11802.

Windshield Wiper Pause Controller
(continued from page 33)

tuted, wiring and parts layout is not critical. However, you must observe polarity of the capacitors and must hook up D1, Q1 and SCR1 properly.

A minor modification of the SCR is necessary to allow insertion into the board. Carefully cut off the solder lugs brazed to the end of the gate and cathode terminals. The SCR is not mounted flush with the board, but inserted only enough to make a good solder connection to the shorter gate terminal. You can shorten the longer terminal after soldering it to the board.

Mounting brackets can be made from 1/2" aluminum sheet, cut and bent as shown. The mounting bracket can be custom fitted for installation on the bottom edge of your dashboard if you don't want to drill any new holes on the dashboard's face. The sides of the unit should be left open to help dissipate heat. Insulation paper or plastic tape should be used where necessary to prevent short circuits. A coat of paint will dress up the mounting bracket. Install a suitable pointer knob to match the car's decor to complete the construction.

Installation

Mount the APC within easy reach of the driver. Since the APC circuit is grounded through its metal case, as are most automobile electrical devices, it is necessary for the case to make good electrical contact with the dashboard. If for any reason a good ground connection cannot be made in this manner, run a wire (about No. 20) from the APC's ground bus to a good ground on the car. Connect the B lead from S1 to the accessories terminal of the ignition switch, or to a lead already attached to this terminal, if you can't get to the ignition switch. Connect the A lead from the anode of the SCR to the windshield wiper motor switch S2. Use No. 16 stranded wire for the A lead. A smaller gauge wire (about No. 20) can be used for the B lead.

If the wiper-motor switch is not accessible in your car or if you prefer not to work under the dash, connect the number 16 wire directly to the wiper motor wire going to the dashboard switch.

A schematic for constructing an APC for a 12-volt positive-ground system is shown in Fig. 2. For 6-volt operation, reduce R1 to about 15,000 ohms and replace R4 with a jumper wire. [Positive ground circuit and modification for 6-volt operation were not tested.—Editor.]

R-E

**15 CRYSTAL MARKERS
3 SWEEP RANGES
ONLY \$135**




**New Heathkit IG-57
Solid-State Color TV
Marker/Sweep Generator**

The IG-57 combines the features of both a post marker and a sweep generator for less than you'd expect to pay for just one of these functions.

- Three linear sweep ranges for TV tuned circuits in sound IF, color bandpass, video IF circuits and proper overall RF/IF response • External attenuator provides 1, 3, 6, 10 and 20 dB steps up to 70 dB maximum • Can also be used with external sweep or marker • 15 crystal-controlled markers provided for color bandpass alignment; picture and sound carrier frequencies for channels 4 and 10; FM tuner, FM IF and discriminator alignment; TV sound IF adjustments
- All crystals included • Completely isolated 1-15 VDC variable voltage supply for positive or negative bias • Built-in 400 Hz modulation for trap adjustment and checking and adjusting FM tuners • Phase Control and Trace Reverse Switch so markers will appear from left to right as in set manufacturer's instructions, regardless of scope used • Blanking Switch eliminates return sweep and provides base line • Circuit Board Construction — three circuit boards, 27 transistors, 3 silicon diodes, 2 crystal diodes and 2 Zener diodes combine to make assembly faster with less chance of error • Bias and Scope Horiz. leads, Attenuator, Demod In, Scope Vert., RF and Demodulator cables included in kit.

Kit IG-57, 14 lbs. \$135.00

IG-57 SPECIFICATIONS — Marker frequencies: 100 kHz; 3.08, 3.58, 40.8, 4.50 MHz, ±.01%. 10.7, 39.75, 41.25, 42.17, 42.50, 42.75, 45.00, 67.25, 193.25 MHz ±.005%. Modulation frequency: 400 Hz. Input impedances: External Marker, External Sweep, & Attenuator — 75 ohm. Demod In — 220 k ohm. Output impedances: Marker Out, Sweep Output & Attenuator — 75 ohm. Scope Vert — 22 k ohm. Bias voltage: Positive or negative 15 volts DC at 10 milliamperes. Type of marker: Birdie. Controls: Bias control with pull-on/push-off switch; Marker/Trace — dual concentric; Sweep Width/Sweep Center — dual concentric; Marker Out — concentric with Sweep Range switch; Phase. Switches: Rocker type — separate switch for each of the above listed frequencies; Blanking, On/Off; Trace Reverse; Modulation On/Off. Transistor — Diode Complement: (19)-2N3692 transistor. (7)-2N3393 transistors. (1)-2N3416 transistor. (3)-silicon diode rectifiers. (2)-crystal diodes. (1)-13.6 volt zener diode. (1)-20 volt zener diode. Sweep frequency ranges and output voltage: LO Band — 2.5 to 5.5 MHz ± 1 dB at 0.5 volts RMS fundamentals, and 10.7 MHz on harmonics. IF Band — 38 to 45 MHz ± 1 dB, at 0.5 volts RMS, fundamentals. RF Band — 64 to 72 MHz ± 1 dB at 0.5 volts RMS fundamentals, and 192 to 198 MHz on harmonics. Attenuator: Total of 70 dB of attenuation in seven steps — 1, 3, 6, 10, 20 and 20 db. Power requirements: 120 volts, 60 Hz AC at 20 watts. Dimensions: 13 3/4" W. x 5 1/2" H. x 12 1/2" D.

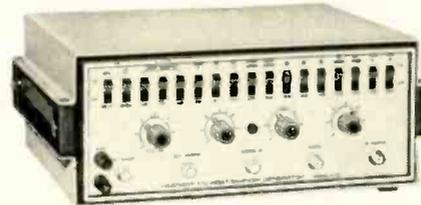

DON'T NEED THE SWEEP?
The IG-14 has the same features and specifications — without the sweep.

Kit IG-14
12 lbs. shpg. wt.
\$99.95



Free 1968 Heathkit Catalog
Describes these and over 300 other kits for test, stereo/hi-fi, color TV, SWL, Amateur Radio, CB, Marine, Educational, home and hobby. Save up to 50% the easy and enjoyable Heathkit way. Just mail coupon or write: Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-7
Benton Harbor, Michigan 49022

Enclosed is \$_____ plus shipping.
Please send model (s) _____

Please send 1968 Heathkit Catalog.

Name _____ (please print)

Address _____

City _____ State _____ Zip _____

(Prices and specifications subject to change without notice) TE-182

Circle 107 on reader's service card

Build High Efficiency Lab Power Supply

Solid-state dc supply delivers zero to 6 amperes into 15-ohm load

By MELVIN CHAN and ROBERT BROCK

A LABORATORY PROBLEM REQUIRED A variable-voltage dc power supply capable of delivering from zero to 6 amperes into a 15-ohm load. Ripple voltage could not exceed 1%. We wanted a supply that was more efficient than most and did not require exceptionally large filter capacitors. Fig. 1 shows the circuit of the supply that met our requirements. Ripple is only 0.1% at full load.

If we had used a conventional supply with brute-force filtering, we would have needed 50,000 to 100,000 μF to hold ripple down to 1%. On the other hand, power supplies using simple series-element regulation waste a lot of power. Fig. 2-a shows that the power dissipated in the filtering and regulating circuits rises from approximately 80 watts at 1 ampere to 160 watts at 3 amps and then drops to around 60 watts at 6 amps. Too, efficiency increases linearly with load current and reaches approximately 45% at a mid-range current of 3 amps (see Fig. 2-b).

Compare these curves with those in Fig. 3 showing the performance of the supply shown in the schematic. Note that the power dissipated within the supply (Fig. 3-a) ranges linearly with output current from 0 (zero current) to 30 watts with a 6-amp load current. Efficiency (Fig. 3-b) ranges from 75% at 1 amp to 95% at 6 amps. Total effective filter capacitance is only 1650 μF instead of the 50,000 to 100,000 μF required for a brute-force filter in such a supply.

The circuit

The voltage source is a 6-amp variable-voltage autotransformer. The selected ac voltage is fed to a full-wave bridge rectifier assembly (D1), filtered to reduce ripple to about 6 volts peak to peak at full load and then applied to the control-current network consisting of these components: D2, R3, C3, C4, Q2 and Q1.

The transistors are connected in a Darlington "super alpha" configuration to reduce control-current requirements. Zener diode D2 is selected for

an operating voltage that slightly exceeds the amplitude of the initially filtered ripple voltage and provides the filtered bias voltage for the base of Q2. Capacitor C3 charges rapidly

through D2 toward a voltage level which is the difference between the Zener voltage of D2 and the input voltage at point A. Capacitor C4 charges more slowly through R3 and

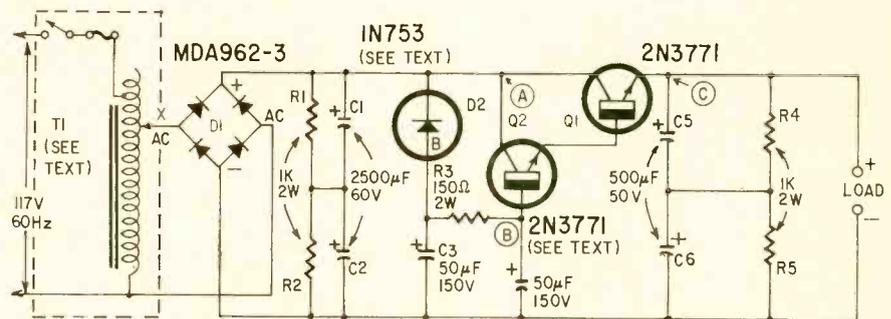


Fig. 1—High-efficiency dc supply for delivering up to 6 amps into 15-ohm load. C4, the 50- μF electrolytic tied to Q2's base, is part of current-control network.

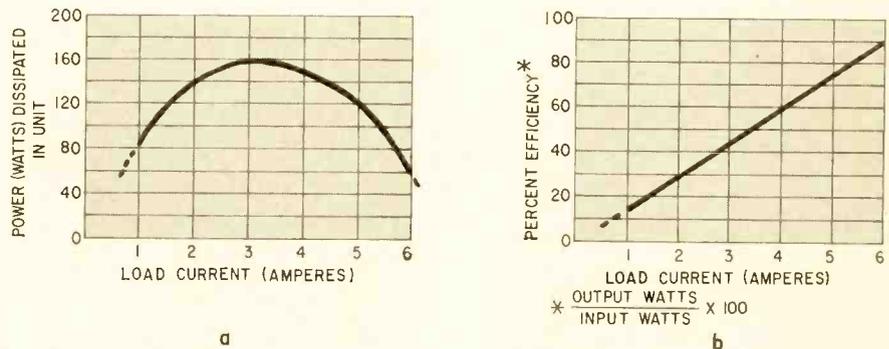


Fig. 2—Performance curves for a conventional series-regulated variable-voltage supply driving a 15-ohm load. Fig. 2-a shows dissipation. Fig. 2-b, efficiency.

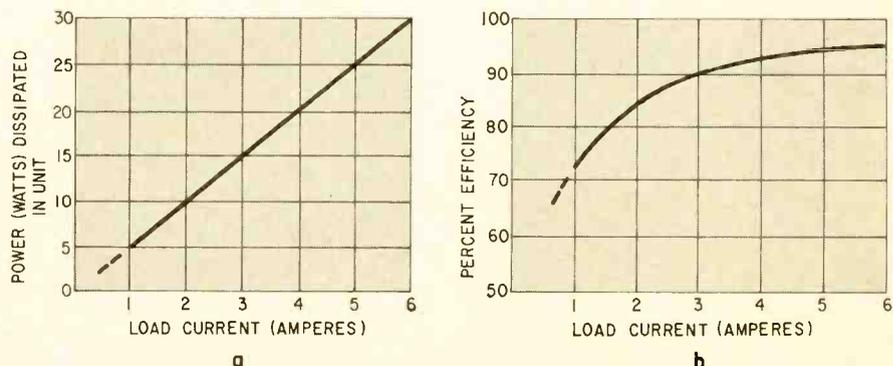


Fig. 3—Dissipation in the supply in Fig. 1 is shown in graph a; efficiency in b.

D2 toward the charge voltage on C3. Transistor Q2's base bias is the difference between the voltage at point A and the charge on C4.

The load voltage at point C equals the voltage at B minus the total base-to-emitter voltage drops of Q1 and Q2. Capacitors C5 and C6 reduce residual ripple voltage to less than 0.1% at full load (6 amps).

Resistors R1 and R2 equalize the voltages across C1 and C2 and discharge these capacitors when the supply is turned off. Resistors R4 and R5 perform the same functions for C5 and C6. (A single 1250- μ F, 120-volt capacitor could have replaced C1 and C2 and eliminated R1 and R2 but was not readily available. Similarly, a single 250- μ F, 100-volt capacitor could have replaced C5 and C6 and eliminated R4 and R5.)

This power supply can be used for any fixed-load applications requiring variable voltages, good filtering and high efficiency within its voltage-current ranges. Its voltage regulation is poor but this is unimportant when driving fixed loads.

Construction hints

A severe shock hazard and a possibility of damaging the equipment exist when the power supply is used to drive a separately grounded load. This hazard may be eliminated by using a 1:1 isolation transformer between the ac power line and the autotransformer.


Parts for the supply can be purchased for around \$50 (including \$20 for TI). Transistor Q1 should be mounted on a 35-watt heat sink. Transistor Q2 may be a 2N3771 or a less expensive transistor such as the Motorola MJ2255 (8 amps, 120 watts), MJ2801 (10 amps, 120 watts) or any similar npn transistor whose I_c is 1 ampere or higher. It, too, should be mounted on a heat sink.

The full-wave bridge rectifier assembly (D1) is rated at 200 piV, 10 amps. It may be a molded assembly such as the Motorola MDA962-3 or may be made up of individual 200-piV, 10-amp diodes. Zener diode D2 may be a 1N753 (6.2 volts \pm 10%, 400 mW), a Z1106 (6.8 volts, 20%) or a 1N4735 (6.2 volts, 20%).

The fuse and switch are assumed to be parts of the autotransformer assembly. If they are not, install a 10-amp, 120-volt d.p.s.t. switch. Ground the transformer through a three-conductor line cord and plug to the ac power receptacle. A 6-amp, 125-volt fast-blow fuse inserted at X between the transformer and D1 will provide short-circuit protection. **R-E**

LOOK! A NEW ELECTRONICS SLIDE RULE

with complete instruction program

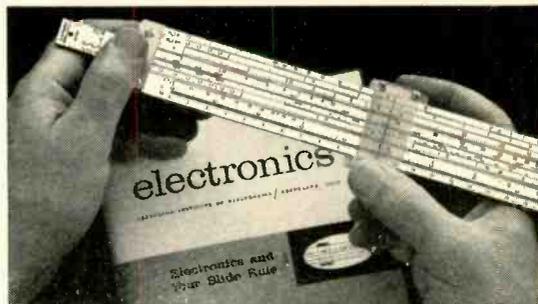

Here's a great *new* way to solve electronic problems accurately, easily... a useful tool for technicians, engineers, students, radio-TV servicemen and hobbyists. The Cleveland Institute Electronics Slide Rule is the only rule designed *specifically* for the exacting requirements of electronics computation. It comes complete with an illustrated Instruction Course. You get four AUTO-PROGRAMMED lessons... each with a short quiz you can send in for grading and consultation by CIE's expert instructors.

See for yourself. Learn how to whip through

all kinds of reactance, resonance, inductance, AC and DC circuitry problems in seconds... become a whiz at conventional computations too!

This all-metal 10" rule is made to our rigid specs by Pickett, Inc... comes complete with top grain leather carrying case and Instruction Course. A \$50 value for less than \$25. Send coupon for FREE illustrated booklet and FREE heavy vinyl Pocket Electronics Data Guide. Cleveland Institute of Electronics, 1776 E. 17th St., Dept. RE-154, Cleveland, Ohio 44114.

GET BOTH FREE!



ELECTRONICS SLIDE RULE

Send coupon today →

Cleveland Institute of Electronics

1776 E. 17th St., Dept. RE-154, Cleveland, Ohio 44114

Send FREE Electronics Slide Rule Booklet. Special Bonus: Mail promptly and get FREE Pocket Electronics Data Guide too!

NAME _____ (Please Print)

ADDRESS _____ CITY _____ STATE _____ ZIP _____

A leader in Electronics Training... since 1934

Circle 108 on reader's service card

ENJOY THE "MUSIC ONLY" FM PROGRAMS

M. A. D.

MUSIC ASSOCIATED'S DETECTOR
NO COMMERCIALS—NO INTERRUPTIONS



It's easy! Just plug Music Associated's Sub Carrier Detector into multiplex jack of your FM tuner or easily wire into discriminator. Tune through your FM dial and hear programs of continuous commercial-free music you are now missing. The Detector, self-powered and with electronic mute for quieting between selections, permits reception of popular background music programs no longer sent by wire but transmitted as hidden programs on the FM broadcast band from coast to coast. Use with any FM tuner. Size: 5 1/2" x 9". Shipping weight approx. 7 lbs.

KIT \$49.50
(with pre-tuned coils, no alignment necessary)

WIRED \$75.00 (Covers extra \$4.95 ea.)

Current list of FM Broadcast stations with SCA authorization \$1.00

MUSIC ASSOCIATED

65 Glenwood Road, Upper Montclair, N. J. Phone: (201)-744-3387 07043

Circle 109 on reader's service card
www.americanradiohistory.com

"REAL PIPE ORGAN TONE"

acclaim thousands of satisfied users
ASSEMBLE THIS MAGNIFICENT ELECTRONIC ALL-TRANSISTOR ORGAN YOURSELF AND SAVE



Kit prices from \$1850. 12 models available... church & theater styles

THREE-MANUAL SPECIALISTS

Save dealer profit and factory labor

- **FUN TO ASSEMBLE & EASY TO PLAY**
Pay as You Build — Play as You Build
You don't have to be a professional organist to make your Artisan sound great.
- **FINEST SOUND** — independently keyed oscillators, independent sets of tone generators, independent amplifiers & speakers (will play thru large stereo system.)
- **CREATE YOUR OWN SOUND** — plug-in voicing filters, adjustable vibrato and voices; percussions, sustain, reverberation.
- **HEAR IT YOURSELF** — the "King of the Kits" — SEND ORDER FOR "Greg Rister at the Mighty Artisan" (12" stereo LP) — \$4.00 p.p.p.
- **LEARN ALL ABOUT IT** — send for Artisan's giant 260 page ORGAN BUILDERS MANUAL — packed with information, pictures, prices — \$5.00 p.p.p. (fully refunded with first order).

Write:
Artisan Organs
factory showroom
1372-R East Walnut Street,
Pasadena, California 91106
(213) 449-0814

Artisan ORGANS

the original kit organ

Circle 110 on reader's service card

NOW—Color-Coded Schematics for 1500 TV Sets . . . at an Unbelievable 1.3¢ Per Set!

Yes, now you can speed-repair 1500 popular TV receivers for just about 1¢ each . . . with the serviceman-proved COLOR-CODED TV COLORGRAMS.

If you've heard about TV Colorgrams, then you know they were a real bargain at their original total price of \$102.50. Now, at this special price of only \$19.95, they're almost a steal.

What are TV COLORGRAMS?

They're amazing new color-coded charts that help you isolate TV receiver difficulties and with less effort than you ever dreamed possible. Each COLORGRAM chart is clearly color-coded to show signal-flow, continuity, test points, and voltages. The entire ground conductor is shown in its own distinctive color. Every component in the circuit is clearly identified, and its relationship to other components made readily recognizable. COLORGRAM charts let you concentrate on that small portion of the set most likely to be the cause of the trouble. There's no time wasted working back and forth between schematic and set looking for test points . . . wading through superfluous information . . . identifying components incorrectly. With COLORGRAMS, everything is there, before your eyes, and very often looking just as it does in the set.


What does a TV COLORGRAM Service-Pak include?

Everything you need to service a whole series of TV sets!



Typical COLORGRAMS SERVICE-PAK sold for \$1.95. You get 50 such PAKS . . . plus 148-page Index . . . for only \$19.95!

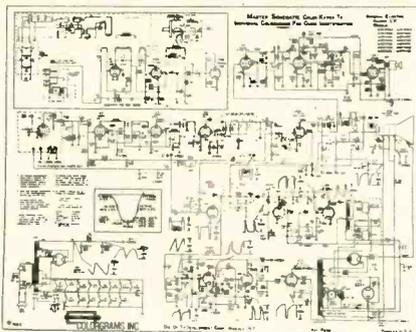First of all, the Pak includes COLORGRAM charts for IF, Video, Audio, Vertical and Horizontal (showing sync and sweep circuits), B+ distribution and AGC circuits. You use the Video chart if you have a Video problem, the Audio chart if you have an Audio problem, etc.



Easy to read complete master schematic is color-keyed to the colors used in the Colorgram Charts.

Second, the Pak includes color-keyed master schematic providing an overall view of the receiver circuit. It shows the Tuner, IF, Video, Audio, Vertical and Horizontal sections, color-keyed to the colors used in individual COLORGRAM charts. It also shows test points, waveforms, voltage, resistance, capacitance, practical alignment data, etc.

CONTENTS


ADMIRAL	(25 CHASSIS,	179 MODELS)
EMERSON	(24 CHASSIS,	100 MODELS)
G. E.	(9 CHASSIS,	332 MODELS)
MAGNAVOX	(1 CHASSIS,	27 MODELS)
MOTOROLA	(8 CHASSIS,	63 MODELS)
PHILCO	(24 CHASSIS,	122 MODELS)
R. C. A.	(125 CHASSIS,	539 MODELS)
WSTGHSE.	(27 CHASSIS,	183 MODELS)

Third, the Pak includes a Rapid Repair Manual that is an effective guide to the use of the COLORGRAM System. It contains original manufacturer's service notes, special instructions, circuit modifications, parts list, and parts numbers. Other practical service data in the Guide are a Pictorial Tube and Component Location Chart, and a Tube Failure Guide.

What do I get for my money?

50 complete Service-Paks . . . each Pak containing data on approximately 30 TV sets. PLUS, as an added bonus,

we'll include the 148-page MASTER-INDEX and Cross Reference Replacement Parts Guide which lists all 1500 TV sets you can quickly repair with TV COLORGRAMS. It describes the black-and-white receivers of Admiral, Emerson, General Electric, Magnavox, Motorola, Philco, RCA, and Westinghouse. These receivers are cross-referenced (by IBM data-processing) to nine replacement parts manufacturers . . . Aerovox, Centralab, Clarostat, G. C., Merit, Stancor, Thordarson, Triad, and TVD, covering over 25,000 parts listings. This INDEX gives you the newest, fastest, clearest,

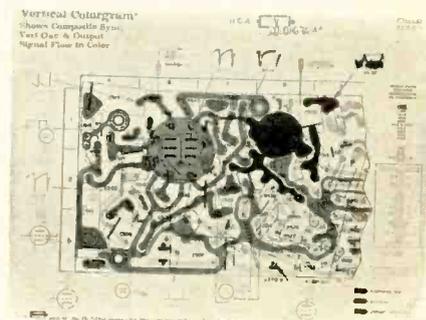

Each Colorgram chart is color-coded to show signal flow and continuity—just like a road map!

most practical approach to obtaining the correct replacement part in a hurry.

MONEY-BACK GUARANTEE

So sure are we that the data in these invaluable Service-Paks will save you time and money we're offering them on a guaranteed money-back basis. Order at our risk for 10-day examination. Put the data in these schematic-packed guides to work for you for 10 days. If they don't prove to be worth several times their cost, return them and we'll refund the full purchase price. Simply fill in and mail the NO-RISK coupon below, with your check or money order, to obtain these time-saving, money-making manuals.

NO RISK COUPON — MAIL TODAY

TAB Books, Blue Ridge Summit, Pa. 17214

I enclose \$19.95 for which please send me your complete 50-Package Colorgrams Schematic offer postage prepaid. I understand I must be completely satisfied or you will refund my money if the package is returned in 10 days.

Name

Company

Address

City

State

Zip

RE 78

Circle 111 on reader's service card


Signal and Voltage Indicators

Cut cost of experimental projects by using substitutes for expensive meters

By LEO G. SANDS

IN THE LONG-GONE AND OFTEN-lamented days right after World War II, inexpensive surplus equipment virtually flooded the parts market. Every experimenter worth his salt had a large and highly varied collection of voltmeters. Often selling for a couple of dollars or less, top-quality movements were available in almost any size, shape or range. Today, however, the well-mined mother lode of military voltmeters has pretty much played out, and the cost of a new one for the latest experimental project often can equal the combined cost of all other components.

Fortunately, there is a way around the dilemma. Many types of common indicator tubes and other indicating devices can be used for signal and voltage displays. Probably the most well known of these money-savers is the electron-ray indicator tube often called a "magic eye." Used in AM radio circuits as long ago as the late '30's, the indicator still is used in test instruments and in some FM tuners. It has several other possible uses as a voltage indicator as well.

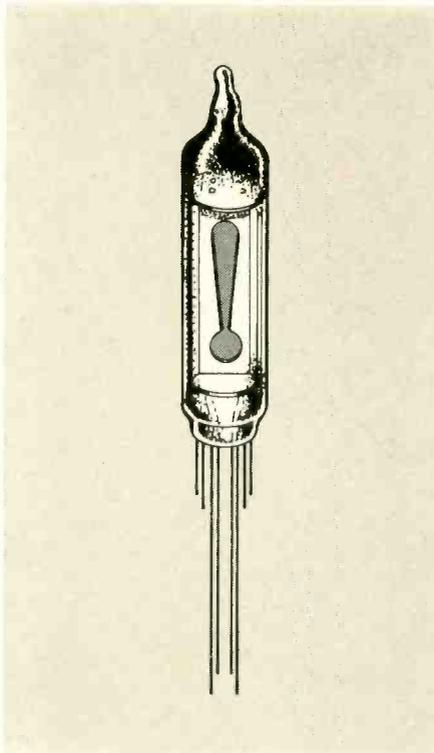

The original electron-ray indicator tube was the 2E5 with a 2.5-volt heater, and its 6.3-volt counterpart—the 6E5—shown in Fig. 1-a. The plate of one triode section (a dc amplifier) is connected internally to the ray-control electrode (grid). The plate of the second triode is known as the target.

When the voltage at the amplifier-triode grid is zero, the circular target at the end of the tube glows a bright green, except for the shaded triangular wedge known as the shadow. As the grid is made negative, the shadow gets smaller. When grid voltage reaches approximately -6.5 to -8 (depending upon target voltage), the entire screen is green, and the shadow angle is zero. If the grid is made more negative, the edges of the illuminated area overlap. (The 6U5/6G5 is similar, but the grid voltage for zero shadow angle is about -22 .)

Indicator bars

More novel is the type 6AL7GT indicator tube which displays two glowing rectangular bars divided into four


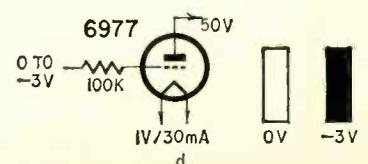
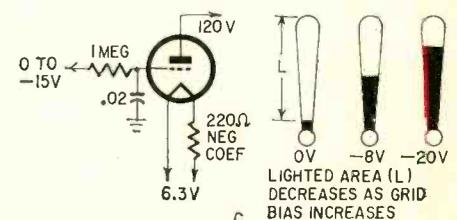
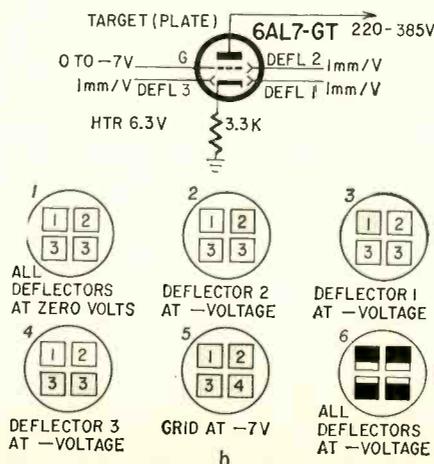


Fig. 1 (a-d)—"Magic eye" tubes provide a variety of these small signal display patterns. (1M3/DM70 is shown at c.)

The TRUE electronic solution to a major problem of engine operation!

DELTA'S FABULOUS MARK TEN®

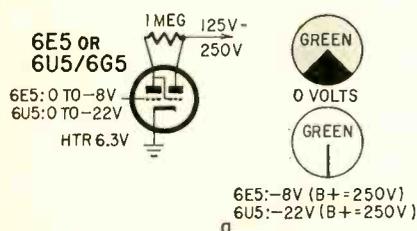

Only \$44.95 ppd.
In easy-to-build Deltakit®
Only \$29.95 ppd.

CAPACITIVE DISCHARGE IGNITION SYSTEM

You've read about The Mark Ten in *Mechanix Illustrated*, *Popular Mechanics*, *Electronics* and other publications!

Now discover for yourself the dramatic improvement in performance of your car, camper, jeep, truck, boat — any vehicle! Delta's remarkable electronic achievement saves on gas, promotes better acceleration, gives your car that zip you've always wanted. Find out why even Detroit has finally come around. In four years of proven reliability, Delta's Mark Ten has set new records of ignition benefits. No re-wiring! Works on literally any type of gasoline engine.

Why settle for less when you can buy the original DELTA Mark Ten, never excelled and so unique that a U.S. Patent has been granted.

READY FOR THESE BENEFITS?

- ▲ Dramatic Increase in Performance and in Fast Acceleration
- ▲ Promotes more Complete Combustion
- ▲ Points and Plugs last 3 to 10 Times Longer
- ▲ Up to 20% Mileage Increase (saves gas)

LITERATURE SENT BY RETURN MAIL
BETTER YET — ORDER TODAY!



P.O. Box 1147 RE • Grand Junction, Colo. 81501
Enclosed is \$ _____ Ship ppd. Ship C.O.D.
Please send:

- Mark Tens (Deltakit®) @ \$29.95
(12 VOLT POSITIVE OR NEGATIVE GROUND ONLY)
- Mark Tens (Assembled) @ \$44.95
- 6 Volt: Negative Ground only.
- 12 Volt: Specify Positive Ground Negative Ground

Car Year _____ Make _____
Name _____
Address _____
City/State _____ Zip _____

Circle 112 on reader's service card

segments. As shown in Fig. 1-b, this tube has a target (plate), a grid and three deflector electrodes. The grid varies the brilliance of the illuminated bars. Deflectors 1 and 2 control the size of the shadow on segments 1 and 2, and deflector 3 controls segments 3 and 4. The width of shadow area produced by each deflector is about 1 mm/volt.

The 1M3/DM70 tuning indicator displays an illuminated bar which is reduced in length through application of a negative grid voltage. As shown in Fig. 1-c, this tube employs a directly heated cathode which can be energized from 6.3 volts ac through a 220-ohm, negative-coefficient resistor.

The type 6977 indicator tube shown in Fig. 1-d also displays a glowing bar, the brilliance of which is reduced as the grid is made more negative. At a grid voltage of about -3, the glow is extinguished. This is also a filament-type tube drawing 30 mA at 1 volt ac or dc.

Then, of course, there are neon lamps which glow when a high enough

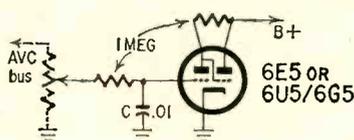


Fig. 2—Maximum avc voltage in AM receiver causes the smallest shadow angle.

voltage is applied initially (striking voltage) and continue to glow until voltage is reduced to a certain level (extinction voltage). Neon lamps are used as pilots, gates, oscillators, voltage regulators and excess-voltage indicators, to name a few.

Having reviewed briefly some basic types of voltage-indicating tubes, let's now see how they may be incorporated into some simple—and useful—circuits. In most cases, the full parts list is omitted, but no trouble should be had in duplicating any or all of them.

Type 6E5 and 6U5/6G5 tubes often are used as tuning indicators in AM receivers, connected directly to the avc bus as in Fig. 2. When the receiver is correctly tuned to a station, avc voltage is maximum, and the shadow angle is smallest. Use a 6E5 if avc measures from 0 to -8 volts maximum; a 6U5 can be used for voltages to -22.

Adding a pot (dotted lines) makes a simple S-meter. Use a dial scale with the pot and calibrate it in S-units or microvolts. Then, with a signal tuned in, adjust the pot for zero shadow angle and read the pot setting.

Another application for the 6E5 or 6U5/6G5 is as an FM-receiver tuning indicator. It can monitor limiter voltage using the same circuit as in Fig. 2, but with the input connected to the limiter grid-return circuit instead of the avc bus. A more meaningful indication is obtained by monitoring discriminator or ratio-detector dc voltage (Fig. 3). The cathode pot is adjusted for zero shadow angle when the receiver is correctly tuned to a station; off channel, the shadow angle increases.

The 6AL7-GT is a popular FM-receiver tuning indicator. In the typical circuit shown in Fig. 4, the grid and deflector 1 are biased negative by the cathode resistor. Deflector 3 is connected to the limiter grid return, and deflector 2 is connected to the discriminator or ratio detector as in Fig. 3. The illuminated bars are of equal length and shortest when the receiver is correctly tuned (deflector 2 at zero voltage and deflector 3 at maximum negative voltage).

The circuit of Fig. 2 can be used as

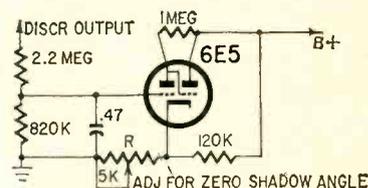


Fig. 3—FM discriminator or the ratio-detector voltage is monitored and pot R adjusted for zero shadow angle.

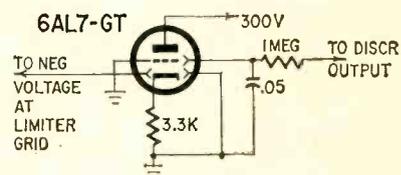


Fig. 4—6AL7 light bars are shortest when deflector 2 has zero voltage and deflector 3 has a maximum negative voltage.

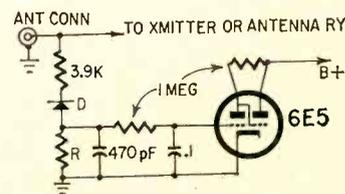


Fig. 5—Transmitter monitor: Output is rectified by the diode. Voltage across R controls 6E5 shadow width.

a dc vtvm by calibrating the pot dial scale in terms of voltage for zero shadow angle. It can be used as an ac vtvm by connecting a diode from the arm of the pot (anode) to ground (cathode) or in series with the hot end of the pot (cathode toward voltage being measured).

Electronic indicator tubes also can be used to monitor CB and ham transmitter circuits. Relative transmitter output can be monitored with a 6E5 using the circuit shown in Fig. 5.

The output signal is tapped at the antenna connector and rectified by a high-frequency diode; the resulting dc voltage appearing across R is monitored by the 6E5. Sensitivity is changed by altering the value of R. Signal strength determines the width of the shadow, and proper (upward) modulation is indicated by further reduction or overlapping of the shadow angle.

An 1M3/DM70 also can be used as a relative rf-output indicator. As shown in Fig. 6, rectified rf is fed to the indicator grid, causing the illuminated

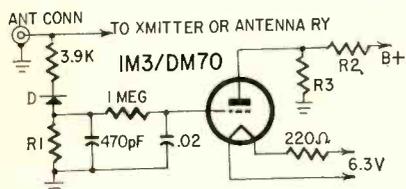


Fig. 6—Transmitter output varies the bar width in 1M3/DM70. Rectified rf signal appears on the indicator grid.

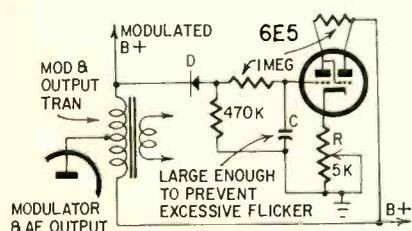


Fig. 7—Overmodulation indicator: The modulated B+ is rectified and fed to the grid of 6E5, varying the shadow angle.

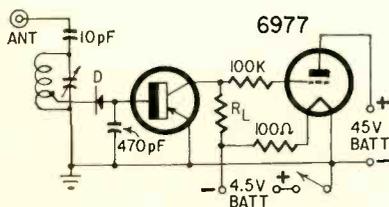


Fig. 8—Field-strength/wavemeter: rectified rf signal forward biases the transistor, lighting the 6977 indicator lamp.

bar to enlarge with increased output and upward modulation. The value of R1 is selected to provide the desired range. Values of R2 and R3 should be chosen to reduce B+ to 150–170 volts at the plate of the indicator.

Overmodulation indicator

A 6E5 can be used as a CB overmodulation indicator (Fig. 7). Here, modulated B+ voltage is tapped from the modulation transformer and fed to the 6E5 grid through diode D. Since modulated B+ voltage ordinarily is positive, the diode conducts only on negative overmodulation peaks, causing the shadow angle to flicker. Pot R is

used to balance out diode leakage current in the circuit.

In Fig. 8 a 6977 tube is used as the indicator in a combination field-strength/wavemeter. Diode D rectifies the rf signal and forward-biases the transistor, causing the 6977 to glow. The tube glows when the tuned circuit is resonant and is dark at other times.

What else you can do with indicator tubes depends upon your imagination. Just keep in mind that they're simply vtvm's without a calibrated scale. Using the basic circuits of Fig. 1 and adapting the examples shown and described, you should be able to save the cost of an expensive meter in many of your experimental projects. **R-E**

SCHOOL DIRECTORY

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology & Electronic Technology curricula both available. Associate degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept. Feb. Dorms. campus. High school graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. C, Valparaiso, Indiana 46383



distinguished graduates

hold important engineering and business administration posts throughout U.S. Professionally-oriented college with outstanding placement record. Four-quarter year permits degree in three years. Fine faculty. Modern labs. Small classes. 300-acre campus. Accredited. Approved for vets. Modest costs. Enter Sept., Jan., March, June. For Catalog, write Adm. Director.



TRI-STATE COLLEGE
2478 College Avenue, Angola, Indiana 46703

Learn Electronics for your SPACE-AGE EDUCATION at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech, in sunny Southern California.

COLLEGE OF ENGINEERING. Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

A & P SCHOOL. Practical experience on real aircraft. One-year course prepares you for F. A. A. A & P certificate. WRITE TODAY FOR CATALOG. NORTHROP INSTITUTE OF TECHNOLOGY

1199 W. Arbor Vitae, Inglewood, Calif.



LEARN TECHNICAL WRITING

for prestige, high pay, advancement

WRITE YOUR WAY TO SUCCESS. Electronics, aerospace, glamour industries need trained writers now. Technical Writing is one of the highest paying careers NOT requiring college. The demand for trained writers is growing with thousands needed in all areas.

ATWS WILL TRAIN YOU AT HOME AT LOW COST. ATWS home training is fast moving, fascinating, easy-to-follow. Includes

everything you need to become a top-notch Tech Writer. Low cost. Send today for free career book and sample lesson. No salesman will call. APPROVED FOR VETERANS.

AMERICAN TECHNICAL WRITING SCHOOLS, Dept. RE-78
5512 Hollywood Boulevard, Hollywood, California 90028



ELECTRONIC TECHNICIANS!

Raise your professional standing and prepare for promotion! Win your diploma in

ENGINEERING MATHEMATICS

from the Indiana Home Study Institute

We are proud to announce two great new courses in Engineering Mathematics for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master engineering mathematics and actually enjoy doing it!

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA HOME STUDY INSTITUTE

Dept. RE-7, P.O. Box 1189, Panama City, Fla. 32401

Do It Yourself Language Lab

Put your tape recorder to work and learn another language

By BYRON G. WELS

IF YOUR YOUNGSTER IS FACING THE problem of foreign-language study at school for the first time, you know that the largest hurdle is memorizing the necessary words and phrases. In school, the teacher can convey usage and sentence structure. But it's the student's job to learn the words.

At our house, it became the whole family's problem, for whenever an odd minute was available, we had to start vocabulary drill. Something had to be done, and we solved the problem.


To begin with, you need a small tape recorder with a slow speed: 3¾ ips is good, 1⅞ even better. The machine must have capstan drive.

The next step is to buy a couple of packs of file cards. Use the 3" x 5" cards if your machine runs at 1⅞ ips speed, 5" x 7" for 3¾ ips. Remove the head cover from the tape machine, and place a card so it "bottoms" on the tape transport's base plate. Hold the card near the head, and mark the position of the bottom of the head gap on the card, and the location of the top of the gap (see the drawing).


Now stick a length of recording tape across the bottom of the card, placed so it completely covers the gap area. To do this, paint a line of cement (preferably rubber cement) on the bottom of the card. Place the tape (dull side down) on a piece of paper, and smear some rubber cement on the back of the tape. When both the card and tape have dried, pass the tape to the card. Place it right the first time. Tape and card will not readily slip, and they will be bonded permanently. Trim the excess tape off both ends with a razor blade. With the tip of a finger, rub the excess cement from the card. Be sure not to leave any traces of cement on the surface of the tape or card—it can literally gum up the works.

Repeat this on as many cards as you have words to be learned. When you have finished applying the tape to the cards, set up the tape recorder, and remove the supply and takeup reels.

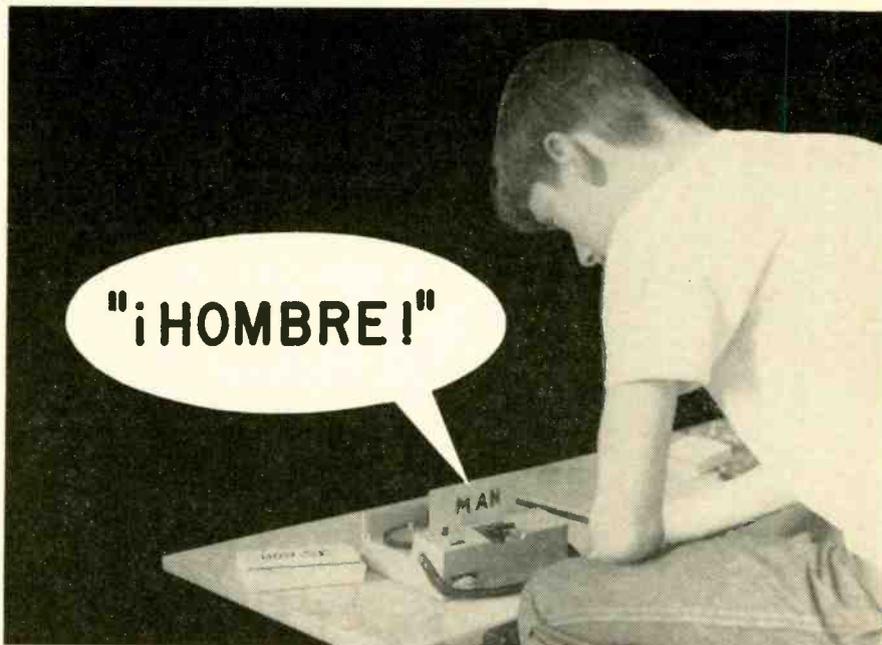Place a card in the head area, and put the machine in the record mode. Slide the card toward the capstan and capstan idler until the card is caught in the pinch between the two. They will pull the card past the heads and eject it at the other side. While the card is



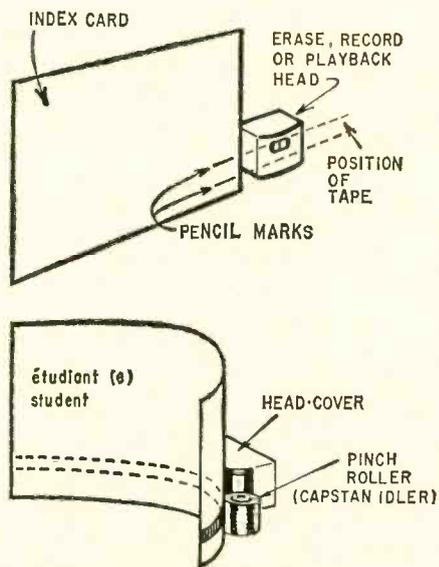Languages are easier when correct pronunciation is heard while reading English word.



To prepare language cards, remove tape-head cover and position file card near head and flush with baseplate. Mark top and bottom of playback-head gap on card. Next, apply rubber cement to the card (where marked) and the glossy side of tape. Carefully position tape on card, removing all excess glue. Record words while feeding cards between capstan and capstan idler. Write words on card backs.

moving past the heads, speak the foreign word correctly into the microphone. If your pronunciation, or your youngster's is less than perfect, enlist the aid of someone who pronounces the language correctly.) It is now recorded on the tape at the bottom of the card.

After the card has been expelled out the other side, write the word in English on the card. Continue this procedure until you have recorded all the words in your vocabulary list.

Foreign words often look perplexing when spelled. It is sometimes difficult to tie the spelling to the pronunciation, so it helps to write the word in the foreign tongue on the back of the card.

To use the language lab, take the cards in any order and sit down in front of the tape recorder. Read the English word written on the face of the card. Try to say it aloud in the foreign language. Then slip the card into the tape machine to hear proper pronunciation.

This process makes learning fun, as it should be. Our other kids, quite taken with the system, have asked us to prepare language cards for them.

Ich am having une bon tiempo with the whole chose! **R-E**

COMING NEXT MONTH

A series of articles designed to tell all about two-way radio and shortwave listening, and how to benefit from emergency, land mobile and other VHF transmissions.

LISTEN IN ON AIRCRAFT, FIRE, POLICE AND WEATHER REPORTS . . . More than 5 million licensed 2-way radio users are on the air now. VHF receivers and converters are readily available to let you tune in on this ever increasing activity. Know what features to look for when you buy.

GETTING STARTED IN 2-WAY RADIO . . . Going on the air is easier than ever. Virtually no one is excluded from mobile communications. Giant corporations, small business and individuals can be accommodated. How modern CB and commercial gear works, how to select and how to service equipment.

IS YOUR SKY PIECE FIRST CLASS? . . . Today's CB transceiver equipment is the best that engineers can design. But the best of equipment is worthless unless the antenna system can efficiently transmit the signal to where it is needed. An explanation of how to select the right antennas for specific mobile applications, how to install them and how to check out the entire system.

TUNING IN THE WORLD ON SHORTWAVE . . . There's fascinating activity on the shortwave bands . . . propaganda from Radio Peking, a Japanese language course for English-speaking audiences, guided tours of foreign lands, etc. Get to know how to select, what features to look for and about how much you will have to pay for a receiver.

COMPUTERIZE YOUR CAR LIGHTS . . . First of a three-part series tells how to build a miniature computer into your car to instantly tell you when a lamp burns out and whether you've forgotten to turn the lights on or off. Estimated cost is about \$20.

DIPPER AND CRYSTAL OSCILLATOR . . . Experimenters, hams and shortwave fans will find many uses for this dipper construction project. A single, inexpensive transistor circuit is used to check the resonant frequency of a tank, or to find the value of an unknown coil or capacitor.

THE CASE OF THE MYSTERIOUS FLYING GLITCH-HAUSEN . . . Another unusual problem in a color TV receiver comes to light. Trouble in a set under repair manages to find its way into a set being repaired nearby. Something new—certain TV ailments could be catching.

ADJUSTING AUTOMATIC CHROMA CONTROL CIRCUITS . . . TV men have patiently explained for years that nothing is wrong with a color receiver when flesh tones change from pink to green after changing channels. The problem is usually a long line of "unequals." They range from studio color cameras to lighting conditions. Now, to help solve this problem, color TV set manufacturers have introduced automatic chroma control circuits. Learn how the new circuits work and how to service the sets using them.

TROUBLE-SHOOTING TV DETECTOR DIODES . . . Solid-state diodes play an important part in the detection systems of black-and white and color TV receivers. Because of their two-terminal simplicity, one expects little trouble from these tiny units. Yet diodes do develop open circuits and changes that seriously affect picture quality and sound. Learn how detector diodes function in TV receivers and how to recognize the problems they can cause.

PLUS—Still more feature articles, news and departments. Don't miss

August Radio-Electronics

Weller®

...the soldering tools professionals depend on



The original Dual Heat Soldering Guns

Preferred by technicians for their fast heating copper tips, exclusive trigger-controlled dual heat, and high soldering efficiency. Available in 3 watt-age sizes, each with spotlight.

100/140-watt Model 8200, 145/210-watt Model D-440, and 240/325-watt Model D-550. Also in complete kits:



Utility Kit includes Weller 100/140 watt gun, extra tips, tip-changing wrench, flux brush, soldering aid and solder. **Model 8200PK**



Heavy-Duty Kit features Weller 240/325 watt gun with soldering, cutting and smoothing brush, soldering aid and solder. **Model D-550PK**

Dependable MARKSMAN Irons in a size for every job



Ideal for deep chassis work and continuous-duty soldering, Marksmann irons outperform others of comparable size and weight. All five feature long-reach stainless steel barrels and replaceable tips.


- 25-watt, 1¾-oz. Model SP-23 with 1/8" tip (In kit with extra tips, soldering aid, solder—Model SP-23K)
- 40-watt, 2-oz. Model SP-40 with 1/4" tip
- 80-watt, 4-oz. Model SP-80 with 3/8" tip
- 120-watt, 10-oz. Model SP-120 with 1/2" tip
- 175-watt, 16-oz. Model SP-175 with 5/8" tip

Complete Weller Line includes replacement tips and solder

WELLER ELECTRIC CORPORATION, Easton, Pa.
WORLD LEADER IN SOLDERING TOOLS
Circle 114 on reader's service card

NEW COAX MATCHING TRANSFORMER

For UHF/VHF
Color/B&W TV

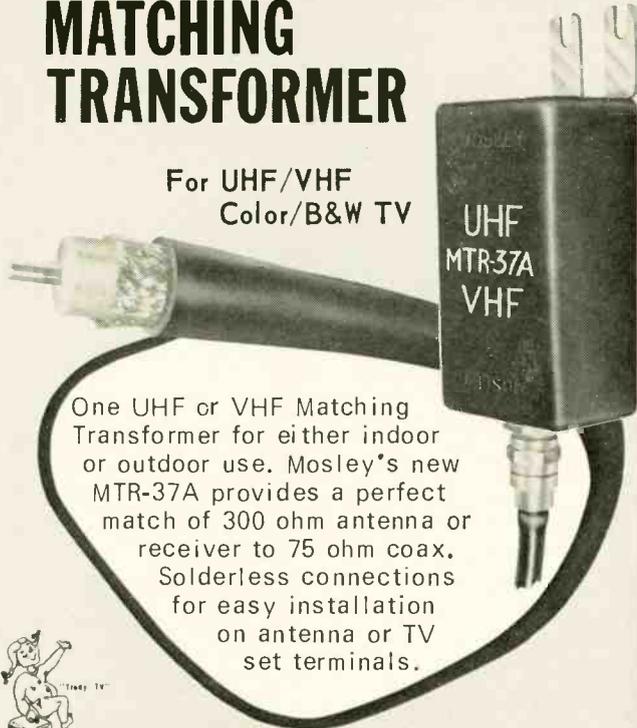

One UHF or VHF Matching Transformer for either indoor or outdoor use. Mosley's new MTR-37A provides a perfect match of 300 ohm antenna or receiver to 75 ohm coax. Solderless connections for easy installation on antenna or TV set terminals.




Write Dept. 160A for FREE detailed brochure.

Mosley Electronics, Inc. 4610 N. Lindbergh Blvd.,
Bridgeton Missouri 63042

Circle 115 on reader's service card

EIGHT INSTRUMENTS IN ONE

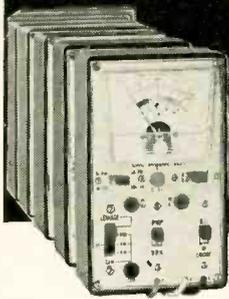

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212

Factory Wired & Tested — \$19.50
Easy-to-Assemble Kit — \$13.50

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

NAME _____ RE-7

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EMC


ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York 12, New York
Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

CB Troubleshooter's Casebook

Compiled by
Andrew J. Mueller*

Case 1: No receive; only motorboating.

Common to: Hallicrafters CB-20.

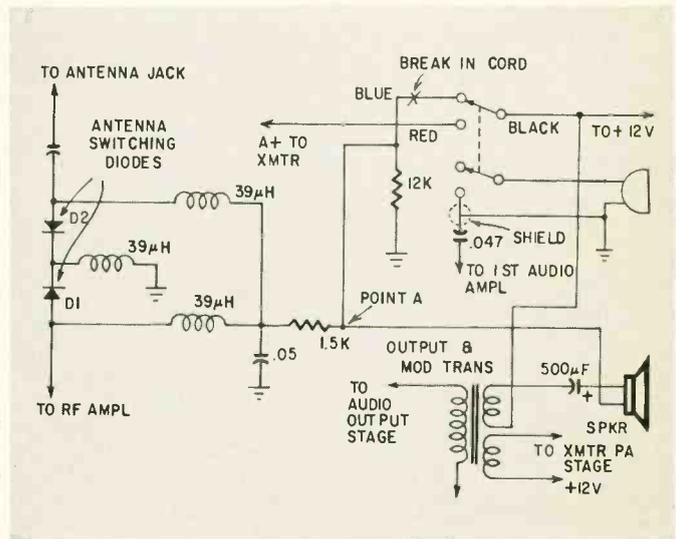


Remedy: Replace or repair microphone cord.

Reasoning: When the blue wire in the mike cord opens, the speaker circuit isn't completed directly. In addition, A+ voltage isn't fed to the antenna switching diodes. This produces feedback through D1 and D2, which causes motorboating. The quickest way to find this problem is to measure the voltage at point A instead of first bridging the electrolytics.

Case 2: At high volume, receiver motorboats.

Common to: Johnson II.

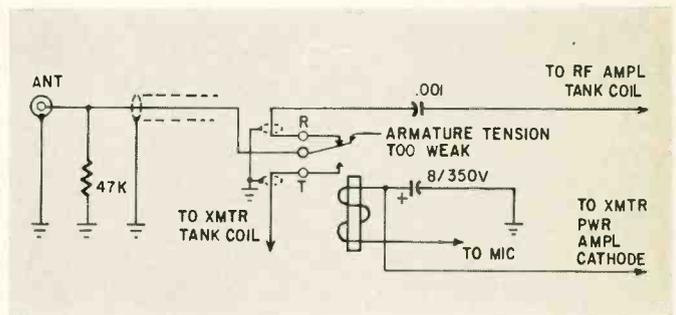


Remedy: Repair or replace T-R relay.

Reasoning: The transmit-receive relay is the most common trouble. At high volume levels, the whole chassis vibrates. Without proper tension, the relay armature will also vibrate. This causes the incoming signal to break up at the audio rate. Replace the relay to eliminate future trouble.

* Service manager, Tel-Air Communications, Inc., Pewaukee, Wis.

Case 3: Distorted and low modulation. Receive OK.

Common to: Ray-Tel TWR-1.

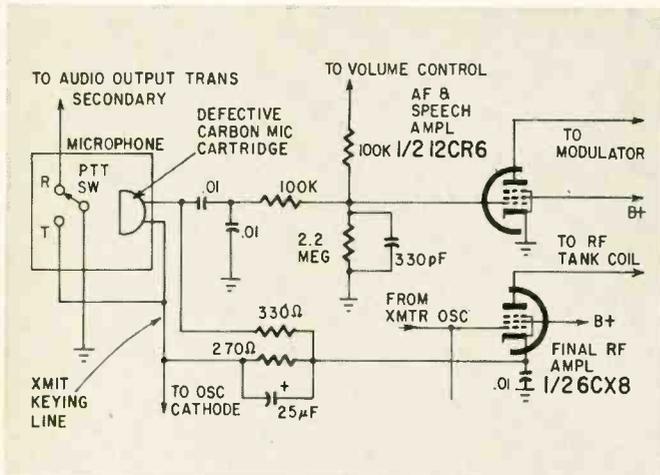


Remedy: Replace microphone cartridge.

Reasoning: Even though carbon mikes are hard to damage, they still fail occasionally. When this happens, the mike output signal becomes weak and distorted rather than disappearing. To check, substitute a new mike cartridge and note any difference.

Case 4: Distorted modulation. Receive OK.

Common to: Gonset G-12.

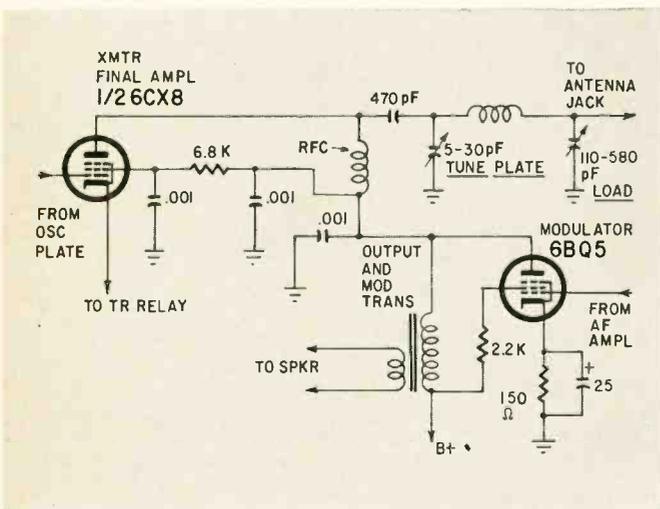

Remedy: Replace the final tube, VI.

Reasoning: This tube frequently becomes microphonic; its elements vibrate when modulation is applied, causing distortion to the modulated rf signal. You can easily be misled to believe the problem is in the audio section when it is really in the PA stage. All tubes should be substituted first before checking separate sections of the modulator and other audio sections.

R-E

THE ELECTRONIC INDUSTRY'S MOST CURRENT 1968 CATALOG

FREE!



ALL NEW...
SPRING AND SUMMER
ELECTRONICS CATALOG

YOUR BUYING
GUIDE FOR:

- Stereo & Hi-Fi Systems & Components
- Tape Recorders
- Phonos, Radios, & TV's
- Cameras & Film
- PA
- Ham Gear
- Test Instruments & Kits
- Citizens Band
- Electronic Parts, Tubes & Tools.

SEND FOR YOURS TODAY!



MAIL TODAY TO . . .

BURSTEIN-APPLEBEE

DEPT. RES 3199 MERCIER STREET KANSAS CITY, MO. 64111

Name _____

Address _____

City _____ State _____ Zip Code _____

DO YOUR FRIEND A FAVOR... ALSO INCLUDE HIS NAME AND ADDRESS IN ENVELOPE WHEN MAILING YOUR REQUEST

Circle 116 on reader's service card



Now...
low cost
Ultrasonic
Area Protection

Euphonics Intrusion Alarm

This new, simplified Intrusion Alarm System projects an invisible ultrasonic beam which will cover and protect any desired area. Any person moving within its range will trigger it immediately.

The Euphonics A-1 Intrusion Alarm is the ideal, low cost protector of homes, apartments, offices, stores and thousands of commercial / industrial establishments. Write for details and prices. Also available: AN-1 Annunciator; MA-2 (12 VDC) marine model.

Euphonics MARKETING Dept. RE-7
202 Park Street • Miami Springs, Florida 33166

Circle 117 on reader's service card

GET INFORMATION "too hot to handle"

Learn about the new scientific and patented miracles in sound by



**WIDE SCREEN STEREO
DEEPEST TRUE PITCH BASS
DYNAMICS WITHOUT DISTORTION
UNIFORM WIDE AREA COVERAGE
MICROWATT SENSITIVITY
AND MORE**

FREE LITERATURE

WRITE OR PHONE

KARLSON RESEARCH & MFG.
Box 117, W. Hempstead L.I., N.Y.
Tel. 516-489-3641


Circle 118 on reader's service card

NEW TUBES AND SEMICONDUCTORS

IC DUAL PREAMPLIFIER

The Mallory MIC 0103 is a silicon monolithic integrated-circuit dual audio preamplifier for magnetic transducer inputs such as stereo automotive tape players. It consists of two iden-

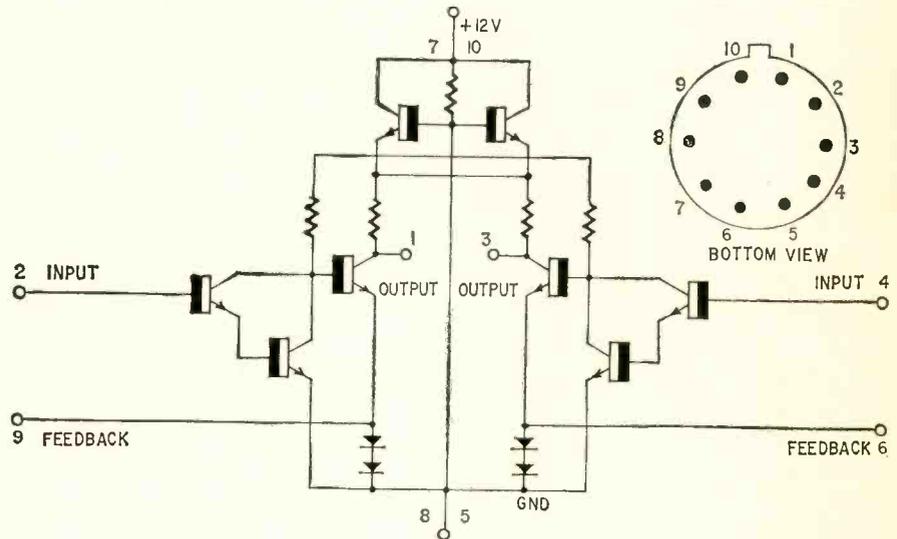
tical amplifiers and transistor and Zener-diode voltage regulators. A voltage regulator provides a constant voltage for the Darlington-pair input circuit. A second regulator provides voltage for the output transistors. Diodes in the emitters of the output



HOTTEST

VALUES EVER OFFERED!

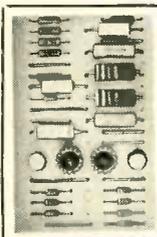FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to "\$1" Buys **FREE GIFT WITH EVERY ORDER**



IBM COMPUTER SECTIONS
8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.
Incl. — Transistors, Condensers, Resistors, Heat Sinks, Diodes, Etc.
**8 for \$1
100 for \$10**

- 2—G.E. PIECES OF EQUIPMENT \$1
stacked with over 200 useful parts
- 15 — G.E. #NE-2 TUBES \$1
Neon Glow Lamp for 101 uses ..
- BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee .. \$5
- 7 — TV ELECTROLYTIC CONDENSERS desirable types .. \$1
- 15 — ASST. ROTARY SWITCHES all popular types \$20 value .. \$1
- 4 — 50' HANKS HOOK-UP WIRE \$1
assorted colors ..
- 50 — ASST. TERMINAL STRIPS \$1
all types, 1-lug to 6-lug ..
- 25 — INSTRUMENT POINTER KNOBS selected popular types .. \$1

- 1000 — ASST. HARDWARE KIT \$1
screws, nuts, washers, rivets, etc.
- 300 — ASSORTED HEX NUTS \$1
2/56, 4/40, 5/40, 6/32, 8/32 ..
- 250 — ASST. SOLDERING LUGS \$1
best types and sizes ..
- 250 — ASST. WOOD SCREWS \$1
finest popular selection ..
- 250 — ASST. SELF TAPPING SCREWS #6, #8, etc. .. \$1
- 150 — ASST. 6/32 SCREWS and 150 6/32 HEX NUTS .. \$1
- 150 — ASST. 8/32 SCREWS and 150-8/32 HEX NUTS .. \$1
- 150 — ASST. 2/56 SCREWS and 150-2/56 HEX NUTS .. \$1
- 150 — ASST. 4/40 SCREWS and 150-4/40 HEX NUTS .. \$1
- 150 — ASST. 5/40 SCREWS and 150-5/40 HEX NUTS .. \$1
- 500 — ASSORTED RIVETS \$1
most useful selected sizes ..
- 500 — ASSORTED WASHERS \$1
most useful selected sizes ..
- 100 — ASST. RUBBER BUMPERS \$1
for cabinet bottoms & other uses ..
- 100—ASSORTED RUBBER GROMMETS best sizes .. \$1

- 100—RESISTORS 1/2W your choice \$1
10, 22, 39, 120, 220, 680Ω
1.5k, 2k, 3.6k, 3.9k, 4.7kΩ, 6.8k, 8.2k, 33k, 220k, 2.2 meg. Ω ..
- 200 — IRC, 22 meg, 1/3W .. only \$1
- TRANSISTOR RADIO asst type \$1.50
good, bad, broken, as-is, potluck ..
- TAPE RECORDER — assorted types good, bad, broken, as-is, potluck .. \$4
- CHAPT ZU DI MITZIA "JACKPOT" double your money back if not completely satisfied .. \$1
- 10 — SPEAKER PLUG SETS deluxe type, 2 conductor .. \$1
- 10 SETS — DELUXE PLUGS & JACKS asst. for many purposes .. \$1
- 10 — SETS PHONO PLUGS & PIN JACKS RCA type .. \$1
- 10 — SURE-GRIP ALLIGATOR CLIPS 2" plated .. \$1
- 100 — ASST. MICA CONDENSERS some in 5% .. \$1
- 50 — ASSORTED PRINTED CIRCUIT SOCKETS best types .. \$1
- 40 — ASSORTED TV KNOBS all standard types, \$20 value .. \$1
- CLEAN UP THE KITCHEN "JACKPOT" Big Deal .. \$1
only one to a customer ..

MARKET SCOOP COLUMN We Bought Out a Factory

- AMPLIFIER 110v AC-DC, 5 Watt \$3
Wired — Phono, Comb. Intercom, etc. needs 3-12AX7, 2-50L6-as is
- 5 POUNDS ELECTRONIC PARTS \$1
Fine asst-too numerous to mention
- MOTOROLA PWR TRANSFORM 110v, CT 150/150v, 6.3v .. \$1
- 10 — TRANSFORMERS assorted \$1
Audio Outputs, Chokes, I, F, 's, etc.
- 10 — ASST. RADIO & TV TUBES \$1
Wire a good number ..
- 50 — ASSORTED TRANSISTORS \$1
big factory scoop-sold as-is
- 20—ELECTROLYTIC CONDENSERS \$1
Fine asst-too numerous to mention
- 20 — ASST. VOLUME CONTROLS \$1
All desirable good types ..
- 100 — RADIO & TV SOCKETS \$1
Asst. — too numerous to mention
- 100 — RADIO & TV KNOBS \$1
Asst. — too numerous to mention
- 5 POUNDS OF HARDWARE \$1
Fine asst-too numerous to mention

IMMEDIATE DELIVERY ... Scientific light packing for safe delivery at minimum cost.
HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Tearsheets will be returned as packing slips in your order, plus lists of new offers.

Name

Address

Cost of goods

Shipping

estimated

TOTAL

Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024

212-874 5600
TELEPHONE

transistors provide bias and feedback for the input circuit through the magnetic pickups. Equalization can be provided either by loading the outputs with series RC networks or through capacitive feedback network. The equivalent circuit and basing diagram are shown.


Specifications (per channel) are:
 Supply voltage 9 to 24
 Supply current (@ 12 V) 10 to 15 mA
 Operating temperature -30° to 60°C
 Voltage gain 57 to 63 dB
 Harmonic distortion (@ 0.2 V output) 1%
 Harmonic distortion (@ 1.0 V output) 5%
 Input impedance 20K min.
 Output impedance 2.5 to 3.5K
 Channel separation 50 dB

HORIZONTAL OUTPUT TUBE

The 6LF6 is a 12-pin version of the 6KG6 anti-sniwet horizontal output tube that operates at low B+ voltages. Designed for color TV sets, this tube operates on B+ voltages as low as 280 with electrical characteristics sufficiently flexible to permit its use as a

replacement for the 6LB6. Amperex's 6LF6 uses a "cavi-trap" anode that eliminates Barkhausen oscillations and prevents snivets.

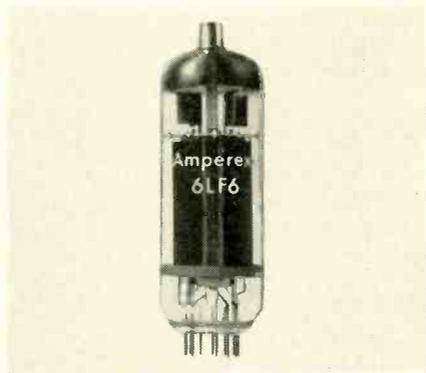Operating at low voltage and high current, the tube elements run cool. In addition, the massive plate structure is designed to take abuse. For example, this tube can be operated for 15 min-



utes without drive; a few seconds without drive will damage or destroy conventional horizontal output tubes. Complete specifications and application data may be obtained from Amperex Electronic Corp., Semiconductor and Receiving Tube Div., Slatersville, R.I. 02876. **R-E**

Are You A Slow Reader?

A noted publisher in Chicago reports there is a simple technique of rapid reading which should enable you to increase your reading speed and yet retain much more. Most people do not realize how much they could increase their pleasure, success and income by reading faster and more accurately.


According to this publisher, many people, regardless of their present reading skill, can use this simple technique to improve their reading ability to a remarkable degree. Whether reading stories, books, technical matter, it becomes possible to read sentences at a glance and entire pages in seconds with this method.

To acquaint the readers of this publication with the easy-to-follow rules for developing rapid reading skill, the company has printed full details of its interesting self-training method in a new booklet, "How to Read Faster and Retain More" mailed free to anyone who requests it. No obligation. Send your name, address, and zip code to: Reading, 835 Diversey Parkway, Dept. 684-017, Chicago, Ill. 60614. A postcard will do.

Circle 119 on reader's service card

SHANNON RECORDING TAPE

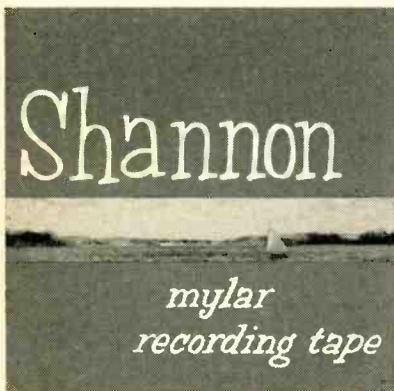We just acquired Exclusive Selling Rights on "SHANNON" Dupont Mylar RECORDING TAPE WE OFFER — Every Store, School, Studio and Tape User — INTRODUCTORY SLASHED PRICES!



<input type="checkbox"/>	2½" — 225'\$.15
<input type="checkbox"/>	3" — 225'17
<input type="checkbox"/>	3" — 300'24
<input type="checkbox"/>	3¼" — 600'49
<input type="checkbox"/>	5" — 600'52
<input type="checkbox"/>	5" — 900'67
<input type="checkbox"/>	5" — 1200'86
<input type="checkbox"/>	5" — 1800' 1.29
<input type="checkbox"/>	7" — 1200'69
<input type="checkbox"/>	7" — 1800'99

<input type="checkbox"/>	7" — 2400'\$ 1.59
<input type="checkbox"/>	7" — 3600' 2.78
<input type="checkbox"/>	CASSETTE 60 minutes89
<input type="checkbox"/>	CASSETTE 90 minutes 1.54
<input type="checkbox"/>	CASSETTE 120 minutes 1.97

<input type="checkbox"/>	2½" TAPE REEL crystal clear	.04
<input type="checkbox"/>	3" TAPE REEL "	.05
<input type="checkbox"/>	3¼" TAPE REEL "	.06
<input type="checkbox"/>	5" TAPE REEL "	.12
<input type="checkbox"/>	7" TAPE REEL "	.14

<input type="checkbox"/> RECORDING TAPE SPICER \$1.49 handy, accurate, compact ...	<input type="checkbox"/> 4 — TV ALIGNMENT TOOLS \$1 most useful assortment	<input type="checkbox"/> 3 — TOP BRAND SILICON RECTIFIERS 1 amp, 1000 PIV \$1	<input type="checkbox"/> 100 — ASST ¼ WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> UNIVERSAA MICROPHONE \$2 regular/remote/single & dual plug	<input type="checkbox"/> \$15.00 TELEVISION PARTS "JACKPOT" best buy ever \$1	<input type="checkbox"/> 20 — ASST. PILOT LIGHTS #44, 46, 47, 51, etc. \$1	<input type="checkbox"/> 100 — ASST ½ WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> 100 — MIXED DEAL "JACKPOT" Condensers, Resistors, Surprises ... \$1	<input type="checkbox"/> 110° R.C.A. FLYBACK TRANS For all type TV's incl. schematic \$3	<input type="checkbox"/> 32' — TEST PROD WIRE deluxe quality, red or black \$1	<input type="checkbox"/> 70 — ASST 1 WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> 4 — TOGGLE SWITCHES SPST, SPDT, DPST, DPDT \$1	<input type="checkbox"/> 110° TV DEFLECTION YOKE for all type TV's incl schematic \$3	<input type="checkbox"/> 50 — ASSORTED #3AG FUSES popular ampere ratings \$1	<input type="checkbox"/> 35 — ASST 2 WATT RESISTORS \$1 stand. choice ohmages, some in 5%
<input type="checkbox"/> 10 — ASSORTED SLIDE SWITCHES SPST, SPDT, DPDT, etc. \$1	<input type="checkbox"/> 90° FLYBACK TRANSFORMER for all type TV's incl schematic \$2	<input type="checkbox"/> 50 — TUBULAR CONDENSERS asst. .001 to .47 — 400v to 1000v \$1	<input type="checkbox"/> 50 — PRECISION RESISTORS asst. list-price \$50 less 98% .. \$1
<input type="checkbox"/> 20 — EXPERIMENTER'S COIL "JACKPOT" assorted for 101 uses \$1	<input type="checkbox"/> 90° TV DEFLECTION YOKE for all type TV's incl schematic \$2	<input type="checkbox"/> 3 — ELECTROLYTIC CONDENSERS most popular number 50/30 — 150v \$1	<input type="checkbox"/> 20 — ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt \$1
<input type="checkbox"/> 50 — TUBE CARTONS (colored) assorted sizes for Popular Tubes .. \$1	<input type="checkbox"/> 70° FLYBACK TRANSFORMER for all type TV's incl schematic \$2	<input type="checkbox"/> 5 — I.F. COIL TRANSFORMERS 456-ke for Transistor Radios \$1	<input type="checkbox"/> 50 — ASST. DISC CERAMIC CONDENSERS popular numbers .. \$1
<input type="checkbox"/> ALL AMERICAN TUBE KIT 12BA6, 12BE6, 12AV6, 50C5, 35W4 — total list \$9.70 \$2	<input type="checkbox"/> 70° TV DEFLECTION YOKE for all type TV's incl schematic \$2	<input type="checkbox"/> 5 — AUDIO OUTPUT TRANSFORM Sub-min for Trans Radios \$1	<input type="checkbox"/> 20 — ASST. DIODE CRYSTALS fine assortment, popular types ... \$1
<input type="checkbox"/> 3 — TOP BRAND 35W4 TUBES \$1	<input type="checkbox"/> 100' — TV TWIN LEAD-IN WIRE 300 ohm, deluxe heavy duty, clear \$1	<input type="checkbox"/> 3-½ MEG VOLUME CONTROLS with switch, 3" shaft \$1	<input type="checkbox"/> 10 — STANDARD TRANSISTORS assorted popular types \$1
	<input type="checkbox"/> 1 — LB SPOOL ROSIN-CORE SOLDER 40/60 top quality \$1	<input type="checkbox"/> 7 — ASSORTED VOLUME CONTROLS with switch \$1	<input type="checkbox"/> 50 — ASSORTED MYLAR CONDENSERS popular selected types .. \$1

Circle 120 on reader's service card


SAVE \$3⁰⁰

ON ALLIED ELECTRONIC LIBRARY

Complete 14 Volume Set only \$625

(\$9.25 if purchased separately)

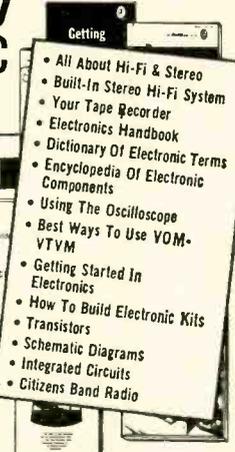Fourteen expertly written, authoritative books—an extremely useful library developed especially for you by Allied's, Electronic Experts.



ELECTRONIC BOOKS FOR HOBBY, SCHOOL, OR HOME STUDY!

RUSH ME THE SET! ALLIED ELECTRONIC LIBRARY
Fill out coupon, enclose check or money order for \$6.25, and mail to

Dept. 2G

ALLIED RADIO, P.O. Box 4469, Chicago, Ill. 60680
Post Paid (please print) 23 PC 7409EP

NAME _____
First Middle Last

ADDRESS _____

CITY _____

STATE _____ ZIP _____

Circle 121 on reader's service card

QUIETROLE



The Original Control and Switch Lubri-Cleaner

The oldest, most reliable and efficient product obtainable for positive lubrication and cleaning of TV Tuners, Controls and Switches. Harmless to plastics and metals. Zero effects on resistance and capacity. **Non-inflammable—non-conductive—non-corrosive.**

The Choice of Better Servicemen, Everywhere.

For Color and Black and White

Available in Aerosol or Bottle
Product of
QUIETROLE COMPANY
Spartanburg, South Carolina

Circle 122 on reader's service card

NOTEWORTHY CIRCUITS


VISITOR OR INTRUDER ALARM

This photoelectric alarm was developed to alert the busy housewife to the approach of visitors or intruders. The photocell and exciter lamp are aligned on opposite sides of a walk or driveway so anyone approaching the house breaks the light beam. The circuit, described by R. F. Adams in the *Clairex Photocell Forum*, is set up so the alarm sounds for 5 seconds and then shuts off automatically.

Circuit operation is simple. When S1 is first closed, power is applied to the exciter lamp and to the transformer primary and the heater in

transformer and the heater in RY2. The bell starts ringing. After a 5-second delay—determined by the delay characteristic of RY2—the contacts in RY2 close and apply power to the LDR and the coil of RY1. Light falling on the LDR causes RY1 to pull in, disconnecting the bell transformer and resetting the alarm.

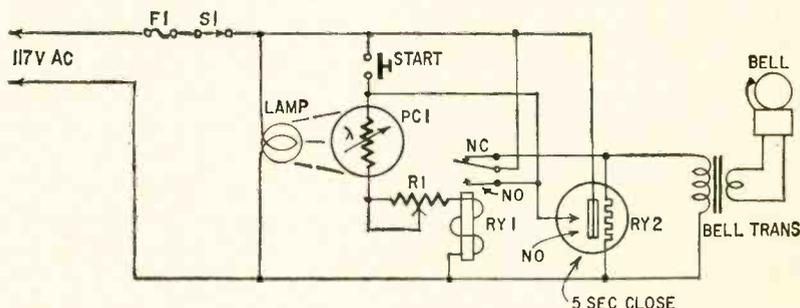The photocell, pot and RY1 have not been specified because the characteristics of each must be determined by the characteristics of the other two. The most important factors are the photocell's maximum power dissipation rating and the relay sensitivity. For example, assume that we select a CdS photoconductive cell whose re-



time-delay relay RY2 through the normally closed contacts of RY1. The bell will start ringing and can be turned off by pushing the START button.

Pushing the button applies line voltage across photocell PC1,—a light-dependent resistor (LDR), current-limiting potentiometer R1 and the coil of relay RY1. The relay is energized, opening its normally closed contacts to disconnect the bell transformer and RY2. RY1 locks in through its normally open contacts. Now, RY1 remains energized as long as light continues to fall on the photocell.

Whenever anyone breaks the light beam, the LDR's resistance rises sharply and RY1 opens. The normally closed contacts now feed power to the

sistance at 2 foot-candles is 1500 ohms and whose maximum dissipation is 500 mW. This limits the current through the cell to 18 mA. With the line voltage at 120 maximum, we can take 12 mA as the maximum current through the cell, pot and relay coil. Thus, the total series resistance is 10,000 ohms.

Catalogs show several 2500-ohm sensitive relays that operate at 10 mA. Therefore, with a 2500-ohm relay and 1500-ohm photocell, the minimum resistance of the pot is 6000 ohms. A 10,000-ohm, 2-watt pot will do. RY2 is a thermostatic delay relay with a 115-volt heater and normally open contacts. These relays are available with delays ranging from 2 seconds to 3 minutes.

NEW TV-TYPE TUBE SHOWN


A novel TV-type tube whose images can be held for long periods with the power off and erased with an outside light source was recently demonstrated by RCA. The experimental device may simplify electronic equipment for displaying stock quotations, airline schedules, computer data and

other information that changes periodically instead of constantly. The unit, called a cathode ray storage tube, has a photochromic instead of a phosphor layer on its inside face. Photochromic materials do not emit light like phosphors but change color when struck by an electron beam. Information "written" on the tube will remain about a half hour before fading.

TRY THIS ONE

SEVEN-PIN MINIATURE SOCKETS FIT POWER TRANSISTORS

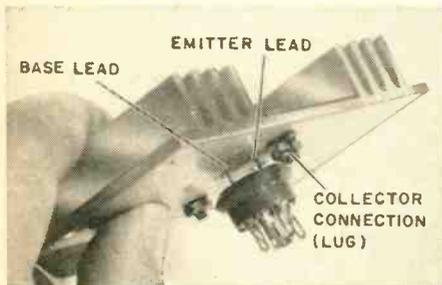The base and emitter leads of TO-3 ("diamond" case style) power transistors are about the same thickness as seven-pin miniature tube pins, and it turns out that their spacing is such that you can fit a whole seven-pin socket right onto the transistor (see photo). If you wish, you can remove individual clips



from the complete socket and use them.

If you use a whole socket, you may want to break off the unused connections to prevent confusion and wiring errors. Or, if you like, use them as tie-points.—*Peter E. Sutheim*

SPARE-FUSE HOLDER

A standard 1/4"-I.D. rubber grommet inserted in a hole near an active fuse makes a handy holder for a spare. This size grommet will hold the widely used 3AG type fuse with a snug grip. The mounting hole should be reamed a



little oversize if the fuse is difficult to insert or remove. Be sure the spot you choose to mount the holder is clear of obstructing components and leads inside the chassis.—*Robert E. Kelland* R-E

HALL EFFECT IN SOLID


(continued from page 45)

frequency ac signals from less than 1/60 cycle per second upwards to 100 Hz or more. The shaft of the position indicator is coupled to the shaft of a small, variable-speed motor. The speed of the motor is controlled by rheostat R, and the Hall output-voltage leads from the Hall-effect element are connected to an amplifier.

As the motor spins the rotor past the Hall-effect element, a Hall output

SOME COMMERCIAL APPLICATIONS OF HALL-EFFECT DEVICES

The measurement of magnetic field strength with Hall generators (crystals) can be carried out with a number of measuring instruments of different sensitivities. One typical magnetic-field-strength meter is the Magnatest Hall Effect Instrument. It can be used for field measurements on magnet systems, measuring magnetic leakage flux, nondestructive material testing, and determining the magnetic behavior of individual grains of

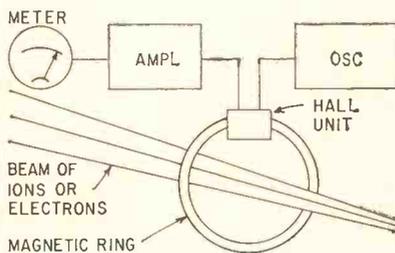

various orientations in transformer core materials.

A simple and handy device for measuring small direct currents is sketched in the diagram. A small magnetic core is arranged around the current carrier, and the Hall unit is inserted in an air gap. When the dc input to the Hall crystal is supplied by a small battery, it is possible to measure currents down to 100 mA without amplification. With an amplifier, currents as small as 5 mA, such as ion- and electron-beam currents, can be measured.

If the Hall crystal is placed in a waveguide so that the electric field is parallel to its surface and the magnetic field is perpendicular to it, the output of the Hall unit will be proportional to the magnetic field strength. This output can be amplified and used to drive a wattmeter calibrated to read microwave power.

voltage is generated. It will vary in accordance with the varying magnetized edge of the rotor as it passes by the element. The rate of these variations is determined by the speed of the rotor, which, in turn, is governed by the motor speed.

From here, you're on your own. The number of applications for Hall-effect elements seems to be limited only by imagination. So dig in! R-E



FREE

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog—Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____
 GIVE ZIP CODE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

OLSON ELECTRONICS, INC.
 904 Forge Street Akron, Ohio 44308

Circle 123 on reader's service card

U.S. GOV'T ELECTRONIC SURPLUS

- Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

ORDER DIRECT FROM AD OR WRITE FOR CATALOGS

STANDARD DIAL TELEPHONE

- (ITEM #715) -- Standard, commercial telephone same as used throughout U.S.A. Attractive polished black, like new condition. Use as extension phone to private systems or connect several phones together for local intercom system. Full instructions are furnished. Wt. 9 lbs. Original Cost \$24.50. F.O.B. \$7.50

STEP-BY-STEP AUTOMATIC SWITCH

- (ITEM #738) -- Amazing "up-and-around" electro-magnetic telephone switch. Dial any bank pair from 1 to 100. Make your own telephone system. Can also be used to remotely control up to 100 circuits over a single pair of wires.
- One of our FOUR STAR bargains. Comes complete with data, one dial and one line bank. Size 5" x 7" x 15". Wt. 16 lbs. Cost Gov't Over \$75.00. Complete; Switch, cover, dial. line bank, instructions..... F.O.B. \$9.95

TYPICAL BUYS FROM OUR 1968 CATALOGS

- \$ 350.00 - Geared 2-hp Battery Golf Car Motor \$26.95
- \$ 15.00 - Westinghouse DC Ammeter, 0 to 300 \$ 7.11
- \$ 40.00 - Vacuum/Pressure Pump, 12-VDC \$11.95
- - - 80-MW Walkie-Talkies, Per Pair \$19.60
- - - Deluxe, Multi-Range, AC/DC Tester \$ 8.98

SPECIAL SALE

Correspondence Course In ELECTRICAL ENGINEERING

Sells For \$10.79 Outside U.S.A., **\$8.79** Postpaid in U.S.A.

- (ITEM #A181) -- Wonderful chance to obtain technical training at Amazing Low Cost! Lincoln Engineering School has suspended its Correspondence Courses because of increased operating costs. We offer a limited number of the school's complete Electrical Engineering Course but without the examination paper grading service. The course consists of 14 lesson unit books. Each book has the regular exams, and in a separate section, "Standard Answers" to each exam question.
- Course is well written, easy to understand, profusely illustrated. Reader's Digest size, easy to carry and study in spare time. Many Lincoln Engineering School students holding excellent jobs as a result of L.E.S. training. Course contains latest information on transistors, silicon diodes, etc. Additional book on how to build and operate a "Home Laboratory and Experimental Bench" furnished with each course.

Send 25¢ Coin Or Stamps For Catalogs
 All Items FOB Lincoln Money Back Guarantee

SURPLUS CENTER
 DEPT. RE-078 LINCOLN, NEBR. 68501

MARKET CENTER

GENERAL

RUBBER STAMPS—80¢, Line Photo Stamps \$7.50. RAYCO STAMP, P.O. 185, Marshall, Texas 75670

MAGNETS. All types. Specials—20 disc magnets, or 2 stick magnets, or 10 small bar magnets, or 8 assorted magnets, \$1.00. MARYLAND MAGNET COMPANY, 5412-G Gist, Baltimore, Maryland 21215.

AC POWER FROM YOUR CAR OR BOAT BATTERY

Standard home electricity (60 cycle, 117 volts) for small appliances, record players, tape recorders, tools, etc.



Inverters from 25 to 600 watts, priced as low as \$15.95.

See your Electronics Parts Dealer, or write

terado CORPORATION
1053 Raymond Ave., St. Paul, Minn. 55108

"ARCTURUS" SALE

- Tube bargains, to name just a few:
#6146 \$2.95 | #5725/6AS6 79¢; 3 for \$2.00 | #6AQ5 61¢
 - #6360... 3.50 | #5842/417A... 2.50 | #6BQ7 94¢
 - #6688... 3.50 | #5847/404A... 2.50 | #6CG7 59¢
 - #6939... 3.50 | #1AX2 49¢; 3 for 2.00 | #6J6... 49¢
 - #7025... .59 | #6K7... 39¢; 3 for 1.00 | #6T8... 88¢
 - #7788... 3.75 | #12B6 59¢; 3 for 1.49 | #6U8... 76¢
 - #2D21... .49 | #25L6 59¢; 3 for 1.49 | #12AU7 59¢
 - Tube cartons: 6AU6 etc. size, \$1.95 per 100. 6SN7 etc. size, \$2.35 per 100. 5U4GB size, \$2.75 per 100. 5U4G size, .03¢ each.
 - Obsolete tubes: #UX200, \$1.69; #80, \$1.20; #10Y, 69¢
 - 7 inch 90 degree TV bench test picture tube with adapter. No ion trap needed. Cat. #7BP7, \$7.99.
 - Silicon rectifier octal-based long-range replacement for 5U4, 5Y3, 5AS4, 5AW4, 5T4, 5V4, 5Z4. With diagram. Cat. # Rect 1, 99¢ each.
 - Silicon rectifier replacement, octal based, for 0Z4. Cat. # Rect 2, 99¢ each.
 - 10 silicon rectifiers, 750 MA., 50 to 300 p.i.v. Cat. # 330F, 99¢ each.
 - RCA-110 degree flyback transformer, latest type. Produces 10 KV. Includes schematic diagram application for any TV. Cat. # BR-1 \$2.99.
 - 5 transistor circuit boards containing up to 6 transistors plus diodes, resistors, capacitors, etc. Cat. # TB10, 99¢
 - Needles: values such as # AS22 sapphire, 39¢; diamond, 99¢
 - Color yokes, 70 degree for all around color CRT's. Cat. # XRC70, \$12.95. 90 degree for all rectangular 19 to 25 inch color CRT's. Cat. # XRC90, \$12.95.
 - Transistorized U.H.F. tuners used in 1965 to 1967 TV sets made by Admiral, RCA, Motorola, etc. Removable bearing may vary from one make to another. Need only 12 volts d.c. to function. No filament voltage needed. Easy replacement units. Cat. # U.H.F. 587, \$4.95
 - Flyback transformer in original carton. Made by Merit or Todd. Most with schematic drawing of unit. Please do not request specific type. Cat. # 506, 99¢ each.
 - Kit of 30 tested germanium diodes. Cat. # 100, 99¢
- Send for our free catalog listing thousands of similar best buys in tubes, parts, kits, transistors, rectifiers, etc. Orders under \$5.00, add 50¢ handling charge. Include 4% of dollar value of order for postage. Canadian postage \$1.00 extra

ARCTURUS ELECTRONICS CORP.

502-22nd St., Union City, N.J. 07087 Dept. MRE
Phone: 201-UN 4-5568

Circle 124 on reader's service card

MATHEMATICAL TOPICS for Tradesmen, Businessmen. Improve your ability. Write LEE'S SERVICE, 1224 Shakespeare Ave., Bronx, New York 10452

WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000

PANELISTS AT HOME WANTED BY NEW YORK RESEARCHER. Leading research firm seeking people to furnish honest opinions by mail from home. Pays cash for all opinions rendered. Clients products supplied at no cost. For information write: RESEARCH 669 Mineola, N.Y. 11501 Dept. LN-24

AUSTRALIA WANTS YOU! Government Assisted Passage. Unlimited Opportunities. Latest Government Information and Forms. \$1.00 AUSTCO, Box 3623-RE, Long Beach, California, 90803

LIKE MUSIC WITHOUT COMMERCIALS?

The SCA-2B Sub-Carrier Adapter makes it possible for you to enjoy the background music transmitted on a 67KHz sub-carrier on many FM stations. (These programs cannot be heard on a FM set without an adapter) In the US there are approximately 400 FM stations authorized by the FCC to transmit the 67KHz programs. If you are within 50 miles of a city of 100,000 or more, it is probable that you are within the satisfactory reception range of one or more of these stations. If in doubt write for a list of such stations in your area.



Patent Pending

Sub-Carrier Adapter, Model SCA-2B with two 36" shielded cables. Price \$39.95.
117 Volt AC Operated Power Supply, PS-9, Price \$4.95.

SCA-2B FEATURES

SIZE: 4" x 2 3/4" x 1 1/2". • Simple plug-in connections to your FM tuner/amplifier. (If your FM tuner does not have a multiplex output jack, we supply hook-up information). • No installation adjustments • All silicon transistors • Operates from our PS-9 Power Supply or 6 to 12 volts D.C.

One Year Factory Guarantee

For Custom Installations: Completely Wired SCA-2 PC card (size: 2 1/2" x 3" x 3/4") with installation instructions for \$34.95.

Write for Dealer Quantity Discounts.

Also available in a General Electric Model T1220B table radio. This is a 6 tube, 3 transistor, AM/FM radio with a four-inch speaker for \$59.95.

Send order to KENZAC Co.

P.O. Box 66251, Houston, Texas 77006

Circle 125 on reader's service card

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corporation 92
Amperex Electronic Corporation 7
Arcturus Electronics Corporation 94
Artisan Organs 81

B & K (Division of Dynascan Corporation) 15, 25
Brooks Radio and TV Corporation 90-91
Burstein-Applebee Company 89

Capitol Radio Engineering Institute, The ... 18-21
Caringella Electronics, Inc. 26
CLASSIFIED 94-97
Cleveland Institute of Electronics 28-31, 81
Cornell Electronics Company 96

Delta Products, Inc. 14, 84

Edmund Scientific Company 95
EICO Electronic Instrument Company, Inc. Cover II
Electro-Voice, Inc. 6
EMC (Electronic Measurement Corporation) ... 88
Euphonics Marketing 89

Gavin Instruments, Inc. (Subsidiary of Advance Ross Corporation) Cover III
GBC Closed Circuit TV Corporation 24
Grantham School of Electronics 1

Heald Colleges 70
Heath Company 22-23, 79

International Correspondence Schools 5
International Crystal Mfg. Company 98

Karlson Research and Manufacturing 90
Kenwood 26
Kenzac 94

Mosley Electronics, Inc. 88
Music Associated 81

National Radio Institute 8-11

Olson Electronics, Inc. 93

Poly Paks 97

Quietrole Company 92

RCA Electronic Components and Devices Tube Division Cover IV
RCA Institute 62-65
Reading Improvement Program 91

Sams & Company, Inc., Howard W. 12
Shure Brothers 13
Simpson Electric Company 27
Solid State Sales 95
Sprague Products Company 16
Surplus Center 93
Sylvania (Subsidiary of General Telephone & Electronics) 67

TAB Books 82

Vaco Products Company 77

Warren Electronic Components 96
Weller Electric Company 87

Zenith 17

MARKET CENTER 94-97

Fair Radio Sales
Meredith Separator Company
Sydmur Electronics Specialties
Terado Corporation

SCHOOL DIRECTORY 85

American Technical Writing Schools
Indiana Home Study Institute, The
Northrop Institute of Technology
Tri-State College
Valparaiso Technical Institute

ELECTRONICS

BRAND NEW TUBES. World's lowest prices on Radio, TV-industrial-special purpose tubes. Write for free parts catalog. UNITED RADIO CO., Newark, N.J.

RECEIVING & INDUSTRIAL TUBES, TRANSISTORS, All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and SAVE! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

Discharge IGNITION, PHOTOFLASH. Free catalog parts, kits. TRANSPARK, Carlisle, Mass. 01741

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

Type "L" PLUG-IN For Tektronix Scopes, \$65. GREENLEE, 430 Island Beach, Merritt Island, Florida 32952

INTEGRATED CIRCUIT KITS; COMPUTER LOGIC KITS; Others. Free catalog. KAYE ENGINEERING, Box 3932-D, Long Beach, Calif. 90803

PROXIMITY Switch. Detects nearness of human body! Free information. ZONAR, 860 Reed, Claremont North, Calif. 91711

New Sensitive TREASURE METAL DETECTORS. New low prices. Professional models from \$29.95 to \$129.50. Write for free catalog today. JETCO ELECTRONICS, Box 132-RE, Huntsville, Texas. 77340

JAPANESE ELECTRONICS NEW PRODUCTS MONTHLY! Only \$1. Satisfaction/Refund. DEE 10639-RE Riverside, North Hollywood, Calif. 91602

SHORT PROOF power supply—0.1 ohm ohmmeter—power diode curves. Use your Battery Eliminator/Charger and new E/I CONTROLLER! Plans \$3.50. Kits. ALSYNCO, Dept. RE-81, 171 S. Main, Natick, Mass. 01760

LIGHT DIMMER Motor Control Kit. Continuous control, includes 10 AMP Triac, General Electric SC45B, Trigger Circuit, Pot, with Push Switch, Schematic. \$3.95. MURPHY, 204 Roslyn, Carle Place, N. Y. 11514

BLACK or WHITE FLUORESCENT LIGHT, battery operated. For mineral hunters or campers. Free construction article. Enclose self-addressed stamped envelope. MILWAUKEE ELECTROMAGNETICS, Box 4476 Dept. C., Milwaukee, Wisc. 53207

AUDIO — HI-FI

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 239R East 149th St., N.Y., N.Y. 10451

TAPE RECORDER SALE. Brand new nationally advertised brands, \$10.00 above cost. Amazing discounts on stereo components. ARKAY Electronics, 1028-E Commonwealth Avenue, Boston, Mass. 02215

TAPEMATES makes available to you ALL 4-TRACK STEREO TAPES—ALL LABELS—post-paid to your door—at tremendous savings. For free brochure write TAPEMATES CLUB, 5727 W. Jefferson Blvd., Los Angeles, Calif. 90016.

SPEAKER REPAIR. Hi-Fi, guitar, organ speakers reconed good as new at fraction of new speaker price. For details and Reconing Center in your area write WALDOM ELECTRONICS, INC. 9155-4, Dept. RE. 4625 W. 53rd St., Chicago, Ill. 60632

Design MODIFICATION or CONSTRUCTION of Audio and communication equipment. Write: GABRIELSEN, Box 3175, Scottsdale, Arizona 85257

CUT DOWN ON MOBIL IGNITION NOISE. DON'T BE FOOLED BY IMITATIONS! Get the ORIGINAL



SYDMUR SOLID STATE "CD" IGNITION SYSTEM!
High Quality Components used throughout. Fiberglass Printed Circuit Board. Unitized Construction. Simplified Kit Assembly.
Construction Article in Nov. 1966 Popular Electronics
Thousands of satisfied customers.
Write for Free Literature TODAY.
COMPAC Assembled . . . \$34.75*
COMPAC KIT 24.95*
*Add 75c for mailing and handling
N.Y. State Residents add Sales Tax.
SYDMUR ELECTRONICS SPECIALTIES
1268 E. 12th St. Brooklyn, N.Y. 11230
(Also Available in Canada)


UNUSUAL BARGAINS

... MANY U. S. GOV'T SURPLUS

NEW SURPLUS Ni-Cd BATTERIES

Save more than 50%. Long life—accept 300 charge and discharge cycles. 1.25 Volts per cell—750 milliampere hours capacity. Excel. charge retention. Hermetically sealed. Indefinite storage life. Multiple cells welded in series—easily cut. Combine to form battery. 7/8" dia. x 5 1/2" high. Spec. price for 100 up. Low-cost charger separate.

Order #	Cells	DC Volt.	Price Ppd.
40.088EH	1	1.25	\$ 1.50
40.092EH	2	2.50	2.75
60.033EH	3	3.75	3.60
60.034EH	4	5.00	4.80
60.703EH	(Battery Charger)		3.25

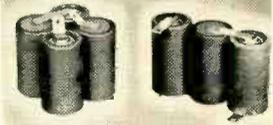

TOP-QUALITY LOW-COST STROBE



Create spectacular psychedelic lighting effects with this genuine electronic strobe. Perfect for parties, special occasions, experiments, perfect for combos, night clubs, dances, exhibitions. Adjusts from 1 to 10 short-duration flashes per second—not a make-shift mechanical device. Amaze friends with old-time movie effects. Best party ice-breaker ever—"freeze" the action and "un-freeze" your guests. Practical touch-check action of moderate-speed machinery. Xenon lamp gives one million flashes. 6 1/2" diam. reflector. Uses reg. 110-120 volt A.C. current. Handmade solid walnut cabinet, 9 1/2"x8 3/4" by 4". Send for Bulletin #73—describes other startlingly new unique lighting effects. Stock No. 70.989EH \$79.95 Ppd.

Order by Stock No. Check or M. O.—Money-Back Guarantee. 300 EDCORP BUILDING, EDMUND SCIENTIFIC CO. BARRINGTON, N.J. 08007

CLIP AND MAIL COUPON TODAY

EDMUND SCIENTIFIC CO. 300 EDCORP BLDG. BARRINGTON, N.J. 08007
148 PAGES — 1000's OF BARGAINS!
Completely new 1968 edition. New of electrical and electromagnetic parts, items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many war surplus. Items for hobbyists, experimenters, workshop, factory. Mail coupon for catalog "EH".

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

Circle 126 on reader's service card

YOUR SERVICE AND QUALITY LEADER

We promise to supply you with the highest quality products at the most attractive prices with the fastest service in the industry.

AVALANCHE MODE TRANSISTORS, used for TRIGGERING SCR's, with diagram 3/\$1.00

ZENERS

1 Watt 7-33V \$.50
10 Watt 6-200V \$.75
50 Watt 7-200V \$ 1.75

SIM TO 2N3429 (NPN) S1, 7/8" stud, min Hfe of 30, 7.5 amps, 175 watts, Vce of 75. \$ 1.75

1 AMP Top Hat & Epoxy

PRV	AMP	PRV	AMP
100	.07	1000	.35
200	.09	1200	.50
400	.12	1400	.65
600	.18	1600	.80
800	.22	1800	.90

TRIACS

TO-66
5 AMPS



PRV	AMP
100	.90
200	1.40
300	1.75
400	2.25
500	2.60

N-CHANNEL PLASTIC TO-18 FET's. Low noise, low leakage, 25 volts source to gate, 50 ma gate current, gain to 9000µ mhos. \$ 1.00

SILICON BILATERAL SWITCH. Replaces two SCR's by firing in either direction when breakdown voltage is exceeded. Used in light dimmers, etc. 2/\$1.00

1000 PRV at 3A full wave bridge \$3.50

CADMIUM SELENIDE PHOTO CONDUCTIVE CELLS. Dark resistance of 500 megohms. Sensitivity of 1-4.99 µa/ft candle with data sheet \$ 1.00

500 Hfe PLASTIC TRANSISTORS (NPN) TO-18, S1 unit sim to 2N3565. 4/\$1.00

SIM. to 2N2875 (PNP). Silicon 20 watts with 30 MHz cut off \$.75

HIGH-VOLTAGE NPN 150V VBCBO at 2.5A, hi gain in TO-66 pack \$.75

Silicon Power Rectifiers

PRV	3A	12A	20A	40A
100	.09	.30	.40	.75
200	.16	.50	.60	1.25
400	.20	.70	.80	1.50
600	.30	1.00	1.20	1.80
800	.40	1.25	1.50	
1000	.55	1.50	1.80	

INTEGRATED CIRCUITS



LINEAR CIRCUITS
FM IF AMPLIFIERS \$2.00
702C WIDE BAND DC AMPL. \$4.50
709C OPERATIONAL AMP. \$4.50
710C HI SPEED DIFF. COMPARATOR \$5.00
711C DUAL COMPARATOR \$5.50

DIGITAL CIRCUITS
SR FILP FLOP. \$.90
SR CLOCKED FLIP FLOP \$1.15
8 INPUT NAND NOR GATE \$1.00
DUAL NAND NOR GATE \$1.00
DUAL AND GATE \$1.00
OR EPANDER \$1.00

NEON LIGHT of NIXIE TUBE DRIVERS. An NPN, TO-18, Si Transistor with a VBCBO of 120 3/\$1.00

UNIUNCTIONS
Similar to 2N2419 Rbb of 5-7, stand off ratio of .6 and Ip of 12, with data sheet \$1.50

Silicon Control Rectifiers TO-66 pack Studs

PRV	3A	7A	20A	70A
50	.35	.45	.70	
100	.50	.65	1.00	4.00
200	.70	.95	1.30	8.00
300	.90	1.25	1.70	
400	1.20	1.60	2.10	12.00
500	1.50	2.00	2.50	
600	1.80	2.40	3.00	16.00
700	2.20	2.80	3.00	

Terms: FOB Cambridge, Mass. Send check or Money Order. Rate companies 30 days net. Include Postage, Average Wt. per package 1/2 lb. No COD's. Minimum Order \$3.00

Circle 127 on reader's service card

SILICON RECTIFIER SALE

IMMEDIATE DELIVERY
FULLY GTD NEWEST TYPE
AMERICAN MADE FULLY TESTED



1 AMP TOP HAT AND EPOXIES

PIV	SALE	PIV	SALE	PIV	SALE
50	.05	800	.18	1800	.80
100	.07	1000	.27	2000	1.20
200	.08	1200	.40	3000	1.40
400	.10	1400	.52	4000	1.85
600	.14	1600	.67		

"SILICON POWER DIODE STUD MOUNT"

PIV	3A	6A	12A	50A	100A	160A
50	.06	.16	.20	.50	.85	2.25
100	.07	.21	.25	.73	1.05	2.65
200	.09	.29	.38	1.23	1.60	3.50
400	.15	.39	.49	1.45	2.50	4.25
600	.19	.53	.73	1.75	3.75	6.50
800	.29	.74		2.20		
1000	.38	.85	1.10	2.60		

"SCR" SILICON CONTROLLED RECT "SCR"

PRV	7	16	25	PRV	7	16	25
AMP	AMP	AMP	AMP	AMP	AMP	AMP	AMP
50	.45	.60	.70	400	1.60	1.85	2.10
100	.65	.85	1.00	500	1.95	2.35	2.50
200	.95	1.20	1.30	600	2.35	3.50	3.75
300	1.25	1.45	1.70	700	2.75	4.25	

SPECIALS! SPECIALS!

Westinghouse 160 AMP, 500 PIV SILICON HI-POWER STUD RECTIFIER IN1666. Limited quantity. \$5.10 ea. 10 for \$45.00

100 Different Precision Resistors 1/2-1-2 Watt 1/2%-1% TOL \$1.25

Asst transistor Kit. P.N.P.—N.P.N. All popular types. Unchecked 100 for \$2.95 500 for \$9.95

Computer Grade Condenser 15,500 MFD 12 VDC American Mfg. .75 ea.

NEW DIODE KIT ALL POPULAR TYPES IN34, IN34A, IN48, IN60, IN64 etc. 100 for \$ 4.00 BEST QUALITY 500 for \$15.00

Money Back guarantee. \$2.00 min. order. Include additional \$ for postage. Send check or money order. C.O.D. orders 25% down.

Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • 212 OR 3-2620

Circle 128 on reader's service card

MARKET CENTER

RENT 4-track open reel tapes—all major labels—3,000 different—free brochure. STEREO-PART I, 55 St. James Drive, Santa Rosa, Ca. 95401

INVENTIONS & PATENTS

MANUFACTURERS NEED NEW ITEMS! B. F. Goodrich, Black & Decker, South Bend Tackle and other million dollar corporations have authorized us to locate new products. For details regarding development, sale, licensing of your patented/unpatented invention, write: THE RAYMOND LEE ORGANIZATION, 230-U Park Avenue, New York City 10017

INVENTIONS WANTED. Patented; Unpatented. GLOBAL MARKETING, 2420-AE 77th Ave., Oakland, Calif. 94605

BUSINESS AIDS

TWO-WAY RADIO SERVICE INVOICE FORMS—Detailed. Free Sample Form No. 50 and Catalog. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

Attention: TV Service Dealers. HIGHLY DETAILED TV SERVICE ORDER FORM STOPS PRICE COMPLAINTS BEFORE THEY START. FREE CATALOG AND SAMPLE NO. 206. OELRICH PUBLICATIONS, 6554 W. Higgins, Chicago, Ill. 60656

EDUCATION/ INSTRUCTION

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write ELKINS INSTITUTE, 2603E Inwood Road, Dallas, Texas 75235

CORNELL One Year TUBES Guaranteed

Tubes are new or used and so marked.

Lab-tested. Individually Boxed. Branded and Code Dated.

OZ4	3BZ6	6AB4	6AT6	6BA6	6BQ6	6CG7	6EA7	6K7	6SN7	6X4	12AD6	12BE6	12SQ7	77
1B3	3DG4	6AC7	6AT8	6BC5	6BQ7	6CG8	6EM5	6G7	6SQ7	6X8	12AE6	12BF6	25L6	78
1J3/1K3	5U4	6AG5	6AU4	6BD6	6BZ6	6CM7	6F6	6S4	6SR7	7A7	12AF6	12BH7	25Z6	84/6Z4
1H5	5U8	6AK5	6AU5	6BG6	6C4	6CZ5	6GH8	6SA7	6U7	7A8	12AT7	12BL6	35W4	5687
1L4	5V4	6AL5	6AU6	6BJ6	6C6	6D6	6H6	6SH7	6U8	7B6	12AU7	12BY7	35Z3	6350
1T4	5Y3	6AN8	6AV6	6BL7	6CB6	6DA4	6J5	6SJ7	6V6	7C5	12AX7	12C5	50L6	6463
1U4	6A6	6AQ5	6AW8	6BN4	6CD6	6DE6	6J6	6SK7	6W4	7N7	12BA6	12CA5	24	7044
1X2	6A8	6AS5	6AX4	6BN6	6CF6	6DQ6	6K6	6SL7	6W6	7Y4	12BD6	12SN7	27	

Other tubes and CRT's at low prices—send for free list

NO SUBSTITUTIONS WITHOUT YOUR PERMISSION • YOUR ORDER FREE IF NOT SHIPPED IN 24 HRS.

TRANSISTORS

FAIRCHILD

SEMICONDUCTOR

FOR—RADIO—TV—HI-FI—REPAIRS

ORDER CORNELL PART NO	PNP	NPN	MIXED OSC CONV	IF	AF DRIVER
REPLACEMENT FOR	112	113	114	115	116
	AAJ	GE 11	GE 12	GE 13	GE 14
	AAJ	AAJ	AAJ	AAJ	AAJ
	79	79	69	69	79

Prestige & Success are yours as an ELECTRONIC EXPERT

COMPLETE RADIO SERVICING AND BASIC ELECTRONICS COURSE ONLY \$3.00 (1970 - 50 parts and charge)

NEW PRACTICAL TV TRAINING COURSE ONLY \$3.50 (1970 - 50 parts and charge)

Both above courses \$6.00

TUBE CARTONS

HIGH GLOSS RED & BLACK With Built in Diagonal Partitions

SIZE	FOR TUBE SIZE	PRICE PER 10 CARTONS (Shipping Inc)	PRICE PER 100 CARTONS (Shipping Inc)
MIN.	6AU6	.29	2.59
GT.	6SN7	.39	3.49
LG. GT	5U4GB	.59	5.29
G.	5U4G	.89	7.99

100 TUBES OR MORE: 30c PER TUBE

Special! With every \$10 Order 25c per tube (No Limit) from this list.

6AG5	6CB6	6SN7
6AU6	6J6	6S4

FREE Send for CORNELL'S NEW 1968 CATALOG!!! PICTURE TUBES! MANY NEW ITEMS!!! FREE

all purpose ELECTRONIC CLEANER 89c plus 20c shipping

CORNELL

Dept. RE-7, 4217 UNIVERSITY AVE. SAN DIEGO, CALIFORNIA 92105

TERMS: ORDERS OVER \$5.00: Add 3c per tube shipping. Prepay in full and avoid C.O.D. charges. Send \$3.00 deposit on C.O.D. orders. No 24 hr. free offer on personal checks orders. ORDERS UNDER \$5.00: Add 3c per tube shipping plus 50c handling. CANADIAN AND FOREIGN ORDERS: Add approximate postage. NO C.O.D. orders. COMBINE VARIED ITEMS TO BRING YOUR ORDER OVER \$5.00

LEARN TECHNICAL WRITING—at home. High paying prestige careers not requiring college. Growing demand, all industries for tech writers now. Low monthly tuition. Easy to understand. FREE career book, sample lesson. APPROVED FOR VETERANS. AMERICAN TECHNICAL WRITING SCHOOLS, Dept. REC-28, 5512 Hollywood Blvd., Hollywood, Calif. 90028

MASTER WATCHMAKING at home. Free sample lesson. CHICAGO SCHOOL, Dept. RET, Fox River Grove, Illinois 60021

FCC FIRST CLASS PHONE License in five weeks guaranteed. Day or Night classes. Write ELECTRONICS INSTITUTE, 2202 West Erwin, Tyler, Texas 75701


Highly effective HOME STUDY COURSE in Electronics Engineering Mathematics with circuit applications. Earn your Associate in Science Degree. Free literature. COOK'S INSTITUTE OF ELECTRONIC ENGINEERING, P.O. Box 517, Monticello, Ky. 42633 (Established 1945)

DOUBLE BONUS PLUS ANY \$100* ITEM FREE
 WORTH OF \$25! TRANSISTORS RECTIFIERS RESISTORS CONDENSERS DIODES ETC.
 Add 25¢ for handling
BOTH FREE WITH ANY \$10 ORDER
 * or item totalling \$1.00.)

World Famed BREVETTATA TEAR GAS PISTOL
 Appearance of this tear gas weapon is similar to real gun. It is ideal for people who work in lonely dark locations and require protection. Men give this gun to wives and daughters for night security. Many industrial applications. Shooting of gun stops aggressor without permanently injuring him. It fires six cartridges without reloading. Each gun comes with six tear gas shells and six blanks for practice and is shipped prepaid. Gun unit prices include 12 shells and all shipping costs. and this pistol is not intended for sale or possession in any locality where it is prohibited by law. Not sold to minors.
 1 Gun-unit at \$13.07
 2 Gun-units at \$22.86 (\$11.43 ea.)
 3 Gun-units at \$29.94 (\$9.98 ea.)
 4 Gun-units at \$35.16 (\$8.79 ea.)
 Extra boxes of ten tear gas shells at \$1.50 per box (prepaid with gun orders). Extra boxes of blanks at \$1.25 per box.
MEREDITH SEPARATOR CO.
 Dept. REL, 310 W. 9th St., Kansas City, Mo. 64105




TELEVISION TELEMETER
 TELEMETER PAY TELEVISION PROGRAM SELECTOR—
 Choice of 3 programs that are tone operated in the VHF band, with provisions for depositing the amount of money required for each program and indicated on the coin register that also shows a credit balance when an over-payment is made. A pre-recorded tape will give program information when desired. With Tubes: 1/12BH7, 1/6BA8, 1/6BE6, 2/6U8; 4" speaker, coin mechanism, tape magazine, etc. Size: 15 x 7 x 7"; Wt.: 25 lbs. #100175 **\$14.95**
LM NAVY TYPE FREQUENCY METER
 125-20,000 KC crystal calibrated indicating equipment, heterodyne type. Used, as is may need minor parts replacement; \$24.95—Used, with all parts: \$29.50.
 Prices F.O.B. Lima, O. — 25% Deposit on COD's — BIG FREE CATALOG — Send for your copy now. Dept. RE
FAIR RADIO SALES
 1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

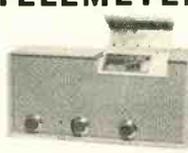

New! SILICON CONTROLLED RECTIFIERS
 PRV AMP AMP
 50 30 48
 100 48 70
 200 70 1.05
 300 1.05 1.60
 400 1.30 2.10
 500 1.60 2.80
 600 1.90 3.00
1N3716/TD3 Actual Size
 Used in many oscillator and amplifier circuits



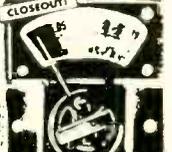100 MICROAMP PANEL METER
 Made in U.S.A!
 D'Arsonval Meter Movement
2.99 ea.
 New! Originally designed to be used with radio tube detectors! Basic meter movement 100µA. 2 mounting holes for easy installation in panel. Size: 2 1/2" x 1 1/4". Mounting centers 1 1/2" x 1 1/2". Ideal for builders, hobbyists, labs, etc. Hurry, at this fantastic price they won't last long!



EPOXY TRANSISTORS & IC's
 Fairchild, Motorola, Texas, Bendix
 4-2N3563 NPN, 600MC, 200MW \$1
 4-2N3643 NPN, 250MC, 350MW \$1
 3-8-5000 SW, 3Amp, PNP \$1
 4-2N4313 PNP 600MC, 200MW \$1
 3-2N3565, 500HFE, NPN, 200MC \$1
 3-2N4265, 400HFE, NPN, 350MC \$1

STEREO PREAMP **4.95**
 ★ 8 TRANSISTORS
 ★ Ready to Play thru tape Amplifier, radio, TV
 ★ Volume, Tone, Controls sw
IGNITION TRANSISTOR **1.99**
 T036
 15-AMP
 2N1100
 BVCCO Volts 100




CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.
 NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items) 30¢ per word . . . no minimum.
 Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for September issue must reach us before July 5th.
 WORD COUNT: Include name and address. Name of city (Des Moines) or state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8-10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

1 AMP TOP HAT AND EPOXIES
 PIV Sale PIV Sale PIV Sale
 50 5¢ 800 15¢ 1800 22¢
 100 7¢ 1000 29¢ 2000 1.25
 200 8¢ 1200 42¢ 3000 1.50
 400 10¢ 1400 55¢ 4000 1.95
 600 15¢ 1600 69¢
Actual Size
1 AMP MICROMINIATURE SILICON RECTIFIERS
 PIV Sale PIV Sale
 50 7¢ 600 20¢
 100 9¢ 800 25¢
 200 12¢ 1000 39¢
 400 17¢
2 AMP SILICON RECTIFIERS
 PIV Sale PIV Sale
 200 12¢ 1000 45¢
 400 16¢ 1200 59¢
 600 19¢ 1400 69¢
 800 29¢ 1600 89¢
SILICON POWER STUD RECTIFIERS
 PIV 3A 6A 12A 55A
 50 .06 .16 .20 .50
 100 .07 .22 .25 .75
 200 .09 .30 .39 1.25
 400 .16 .40 .50 1.50
 600 .20 .55 .75 1.80
 800 .30 .75 .90 2.30
 1000 .40 .90 1.15 2.70
SOLITRON DEVICES
5 AMP Epoxy Rectifiers
 PIV Sale PIV Sale
 50 19¢ 600 59¢
 100 25¢ 800 69¢
 200 39¢ 1000 89¢
 400 45¢
'GLASS AMP' ONE AMP SILICON RECTIFIERS
 PIV Sale PIV Sale
 50 5¢ 600 19¢
 100 7¢ 800 21¢
 200 9¢ 1000 32¢
 400 12¢ 1200 45¢
 PRV may be exceeded without the rectifier breaking down.

CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

{ @ .30 Non-Commercial Rate } = \$
 No. of Words { @ .60 Commercial Rate } = \$

Total Enclosed \$ _____
 Insert _____ time(s)
 Starting with _____ issue

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____
 SIGNATURE _____
 MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT.,
 200 PARK AVE. SOUTH, NEW YORK, N.Y. 10003

Payment must accompany order unless placed through accredited advertising agency 28

10¢ FOR OUR "SUMMER" BARGAIN CATALOG ONE
 Semiconductors Poly Paks Parts
 TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rate net 30 days. CODs 25%.
POLY PAKS
 P.O. BOX 942R
 SO. LYNNFIELD, MASS.
 "PAK-KING" of the World
 Circle 130 on reader's service card

**NEW
FROM
INTERNATIONAL**



FM-2400 FREQUENCY METER

- For Mobile Or Base Station Use
- Tests Predetermined Frequencies 25 - 470 MHz
- Portable . . . Use It Anywhere

The FM-2400 is designed for testing, and adjustment of mobile and base station transmitters and receivers at predetermined frequencies between 25 and 470 MHz. The FM-2400 provides an accurate standard frequency signal to which the transmitter can be compared. This same signal is applied to the associated receiver(s), thereby assuring an accurate frequency adjustment on all parts of the communications system.

Up to 24 crystals may be inserted into the meter for the selection of the frequencies required for testing of the system transmitters and receivers. The frequencies can be those of the radio frequency channels of operation,

and/or of the intermediate frequencies of the receiver between 100 KHz and 100 MHz. Self contained unit. Battery operated.

FM-2400 (meter only).....	\$395.00
RF Crystals with temperature run.....	\$23.50 ea.
IF Crystals 200 - 2,000 KHz.....	See Catalog*
2,001 - 13,000 KHz.....	See Catalog*

*WRITE FOR FREE CATALOG





CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

Circle 149 on reader's service card

RADIO-ELECTRONICS

Gavin gives you more gain per dollar!

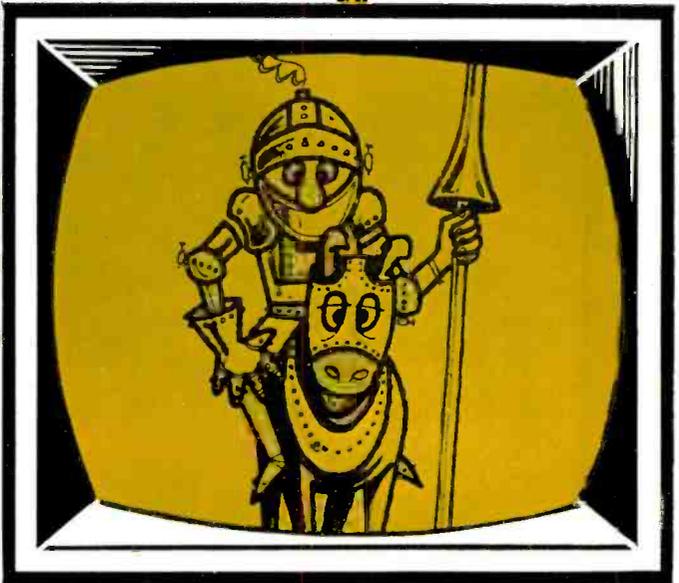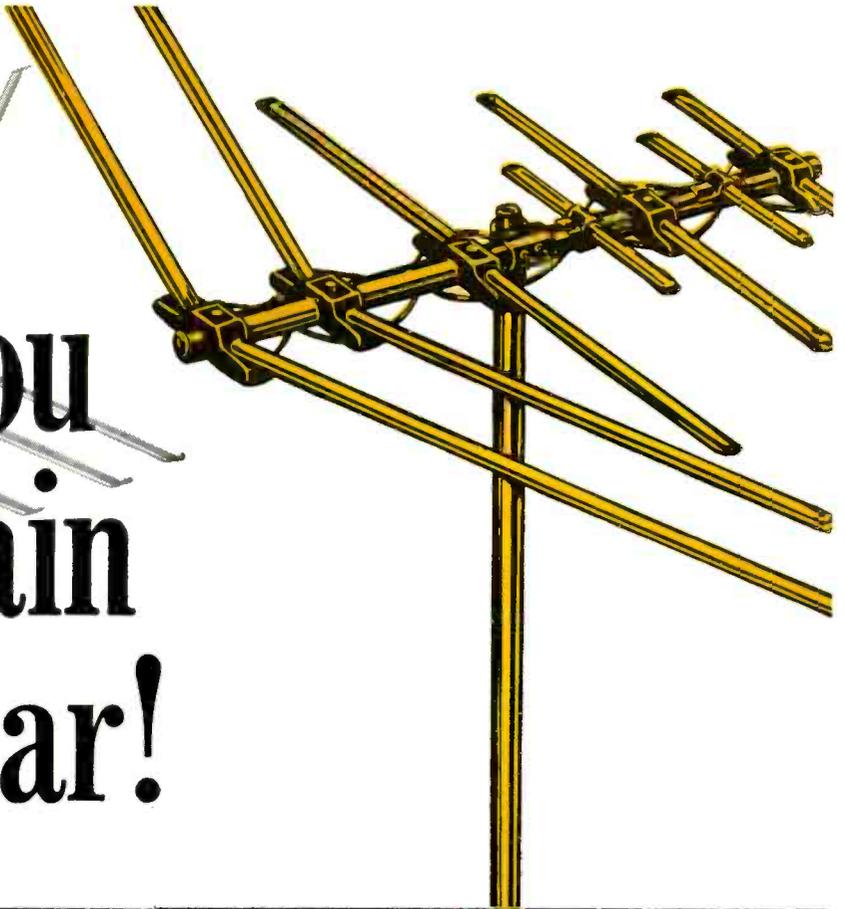

Side By Side Tests Prove...

...that model for model, dollar for dollar, the new Gavin V-Yagi design outperforms any other type of antenna you can buy.

Here's how the test works: We hoist your favorite antenna up on our specially equipped van. We check the signal pick-up on a field strength meter and a color receiver simultaneously. Then, we replace your antenna with a Gavin antenna costing the same or less. The results are eye opening.

Ask us to set up a side-by-side test for you. Invite a representative of the antennas you now handle to observe the demonstration—or set it up himself if he likes. The field strength meter tells the truth no matter who's asking the questions.

Once you see this test, you'll probably switch to Gavin. What are you waiting for?

Circle 150 on reader's service card



GAVIN INSTRUMENTS, INC.

Subsidiary of ADVANCE ROSS CORP.
Somerville, N. J. 08876 U. S. A.

How to improve your trouble-shooting of transistorized circuits!

RCA prepared this Guide specifically to keep you abreast of the latest transistor technology in the electronic service industry.

Chapters include:

- Transistor Amplifier Principles
- Basic Amplifier Considerations
- Transistor Radio Circuits
- Transistor Television Circuits
- Servicing Transistor Circuits

When you understand transistorized circuits, you trouble-shoot faster and more accurately, a fact your customers will appreciate.

Available with your purchases of RCA Entertainment Receiving Tubes from your participating RCA Tube Distributor.
RCA Electronic Components, Harrison, N. J.

RCA

RCA Transistor Servicing Guide 1A1673.

