

60c ■ OCT. 1970

# Radio-Electronics®

FOR MEN WITH IDEAS IN ELECTRONICS

## New 4-channel


## stereo techniques

Build FM stereo multiplex generator

Pro's tape recording quiz

Get better sound from your stereo

**Special  
Issue  
Stereo  
1971**

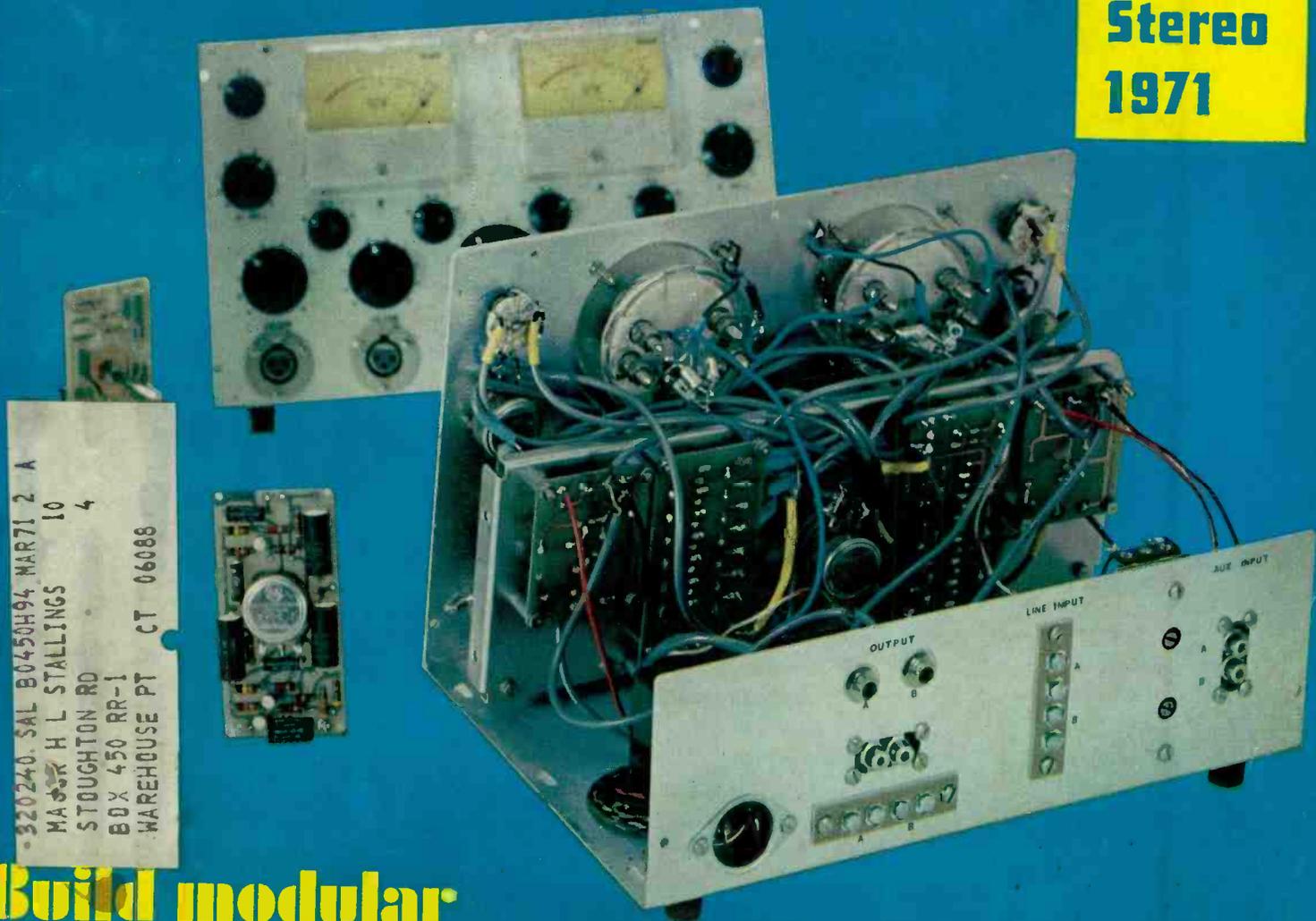

320240. SAL B0450H94 MAR71 2 A  
 MAJOR H L STALLINGS 10 4  
 STOUGHTON RD  
 BOX 450 RR-1  
 WAREHOUSE PT CT 06088

## Build modular 6-channel stereo mixer preamp

A  
**GERNSBACK**  
PUBLICATION

# Performance

**\*Audio magazine says:**


“It is extremely attractive with its base and dust cover, both of which are optional accessories, and it performs superbly. In over twenty hours of use, the unit performed flawlessly, with never a fault in its changing operations during that time. Naturally, we cannot test any equipment to destruction and still produce a number of profiles each month. However, Garrard’s reputation practically guarantees continued high-quality performance for years, and any user should be completely satisfied with this model, which represents the culmination of many years of turntable manufacture.”

# Price

**\*\*Stereo Review says:**

“At a time when most automatic turntable prices are soaring, it is encouraging to note that the price of the SL95B is unchanged from that of the SL95 (\$129.50). A number of different bases are available ranging in price from \$6.50 to \$19.95. A dust cover that fits all bases is \$6.50.”

# Unbeatable combination

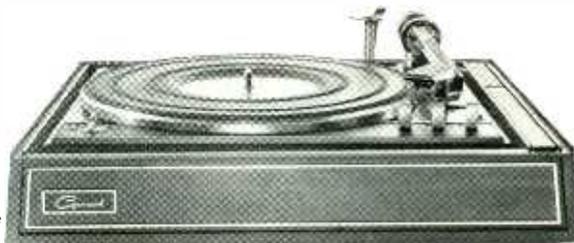

\* Reprinted with permission from the March 1970 issue of Audio ©

\*\* Reprinted with permission from the March 1970 issue of Stereo Review ©

# Garrard's SL95B

Automatic Turntable \$129.50.

For literature write Garrard, Westbury, N.Y. 11590  
British Industries Co.

Circle 1 on reader service card

Put More "GO POWER" into Your Electronics Career —

MOVE AHEAD


from Technician to

ENGINEER

by studying at home with

GRANTHAM SCHOOL OF  
ENGINEERING

"the college that comes to you"

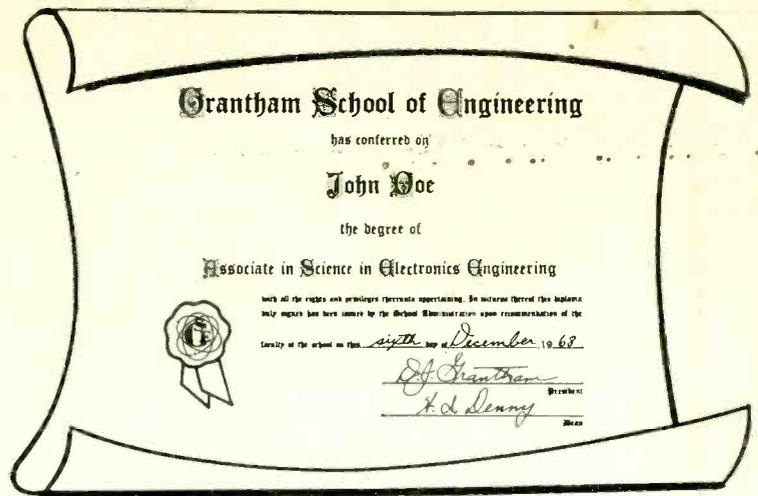

Earn a DEGREE in Electronics Engineering

The GRANTHAM educational program in ELECTRONICS ENGINEERING is designed to upgrade electronics technicians to the engineering level, mostly by home study.

While you continue your present employment, you can really learn electronics engineering and earn an ACCREDITED DEGREE. Upgrade your income and prestige by upgrading your electronics education at the college level.

GRANTHAM'S strong-foundation educational program in electronics engineering is designed especially for the working technician. This program, offered mostly by home-study, leads to non-obsolescent skills—to skills based on reasoning—and leads to the DEGREE of Associate in Science in Electronics Engineering (the ASEE Degree).

This accredited degree program consists of four "correspondence semesters" of 100 lessons each, a total of 400 lessons. All except the last ten of these lessons are completed entirely by correspondence. However, after you have completed Lesson 390 you must then attend a two-week Graduation Seminar at the School. It is during this attendance that you complete Lessons 391 thru 400 and receive your ASEE Degree.

#### Accreditation and G. I. Bill Approval

Grantham School of Engineering is accredited by the Accrediting Commission of the National Home Study, is approved under the G. I. Bill, and is authorized under the laws of the State of California to grant academic degrees.

### Grantham School of Engineering

• Established in 1951 •

1505 N. Western Ave.  
Hollywood, Calif. 90027

Telephone:  
(213) 469-7878



#### Earn Your FCC License Along the Way

You have heard and read, over and over again, about how important an FCC license is to your success in electronics. It is true that an FCC license is important—sometimes essential—but it's not enough! Without further education, you can't make it to the top. Get your FCC license without fail, and then continue your electronics education to earn your degree. It makes good sense to prepare for your FCC license with the School that includes the FCC license preparation as an incidental part of your degree program.

In the Grantham ASEE Degree program, FCC-license and radar-endorsement preparation are integrated into the first two semesters for the benefit of those students who have never obtained such a license.

### Find out how you can advance in electronics

● Mail the coupon below for our free Bulletin ●

#### Grantham School of Engineering

RE-10-70

1505 N. Western Ave., Hollywood, Calif. 90027

Gentlemen:

Please mail me your free Bulletin which explains how the Grantham educational program can prepare me for my FCC license and Associate Degree in Electronics Engineering. I understand no salesman or counselor will call.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

I have been in electronics for \_\_\_\_\_ years.

Circle 2 on reader service card

# NEW & TIMELY

## The FERPICS are Coming

MURRAY HILL, N.J.—Think of an erasable, reusable 35-mm slide on which an operator can electronically erase all or part of the image, add new material, and reproject a new image on the screen.


Scientists at Bell Laboratories are investigating these devices which store images until they are electronically erased or changed.

Called ferpics (ferroelectric ceramic picture devices), the devices are made of material first announced by Sandia Corporation.


The ferpic device is a sandwich structure consisting of transparent electrodes, a photoconductive film and a thin plate of fine-grained ferroelectric ceramic. To change

an image is stored in the form of variations of transparency across the film. In a ferpic the image is stored as a variation of the "birefringence" of the ceramic plate—as a variation in the way the plate transmits polarized light.

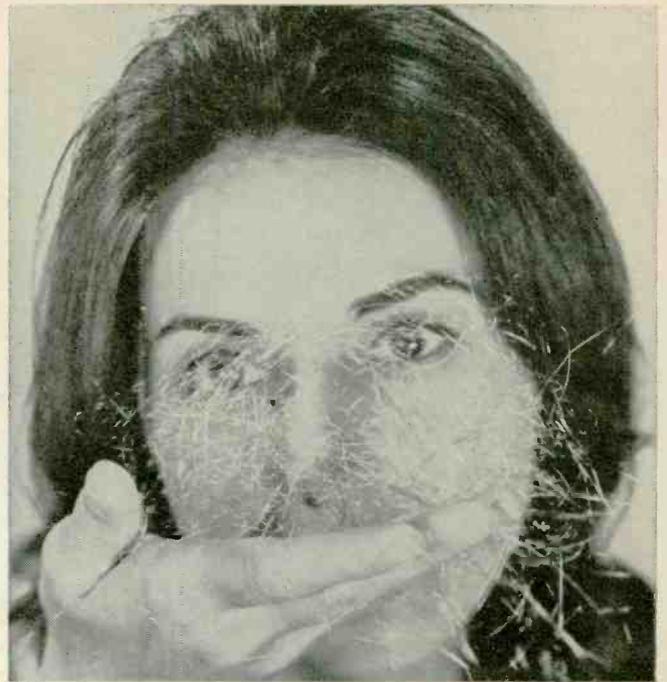In one mode of operation, a scanned laser beam records an image on the photoconductive film—one picture element at a time as in a TV picture. A voltage applied to the transparent electrodes develops a field across the ceramic. When the field is removed, the image remains stored on the ceramic plate. The image stored in the ferpic device can be viewed by putting light polarizing sheets



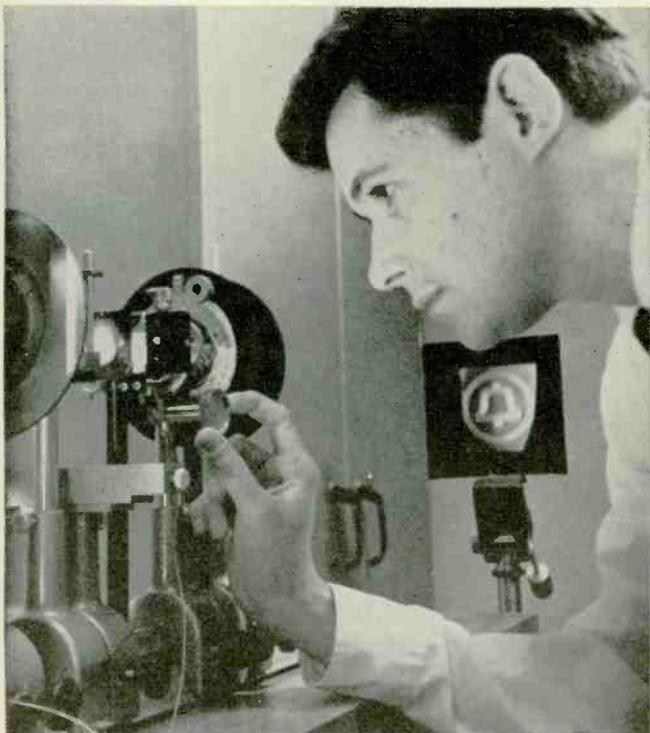**HANDFULL OF MEMORIES**—Ann Karagines examines 250 feet of magnetically plated Mini-Wire at Honeywell's Aerospace Division in St. Petersburg, Florida. The wire, which is only two thousandths of an inch in diameter, has been combined with medium-scale integrated circuits in a new computer memory being tested at the division.



**FERPIC FOCUS ADJUSTMENT** is made by Juan Maldonado on image of Bell System symbol projected onto small screen.

the stored information in this simple structure, a new technique, called "strain-biasing" was developed at Bell Labs. The basic ferpic sandwich is bonded to a transparent substrate which is then flexed so as to stretch or "strain" the material.

In an ordinary film slide

over it, or the image can be projected on a screen using polarized light in a conventional projection system.

To erase the image, the entire structure is flooded with light in the presence of a reversed electric field; the plate is then ready to store another image.

The device is being explored in the hope of obtaining efficient, low-cost solid-state information displays with features that are difficult to obtain in present display systems. Because the image stored in the ferpic

device can be projected, very large displays can be obtained. Also ferpic slides can retain images for a long time without electrical power. A TV set must be fed signals continuously to retain an image; once power stops, the image fades.



**ORIGINAL PHOTO** (above) is conventional photo. **FERPIC STORED IMAGE** (below) shows loss of detail and clarity.



At the present stage of development ferpic devices can store and display, with high resolution, black and white images that fade only slowly. Thus present ferpics are suitable for the display of, for example, written text or figures, since such applications, while exploiting the unique image storage capabilities of the device, would not place severe demands on the speed or lifetime of the ceramic material. ★

## Faster Fax

SADDLE BROOK, N.J.—A new, low cost, high speed facsimile telecommunications unit that can cut telephone costs by as much as one-half has been introduced by Magnavox Systems, Inc. Called Magnafax 860, the new unit is a two-

(continued on page 12)

# Radio-Electronics

FOR MEN WITH IDEAS IN ELECTRONICS

October 1970 • Over 60 Years of Electronics Publishing

## HI-FI—STEREO—AUDIO

- New 4-Channel Stereo Techniques . . . . . 33** . . . . . Walter Salm  
*The latest word on the newest sound*
- Get The Most Out Of Your Stereo System . . 40** . . . . . Peter Sutheim  
*What you can do to make your system better*
- How To Buy Audio Tape . . . . . 43** . . . . . Byron Wels  
*All recording tape is not the same*
- Constant-Speed Motors For Tape Recorders 49** . . . . . Al Williams  
*Hysteresis-synchronous for better speed control*
- Tape Recording Facts And Falacies . . . . . 53** . . . . . David K. Kirk  
*Check your tape recording awareness*

## BUILD ONE OF THESE

- Six-Channel Stereo Mixer-Preamp . . . . . 36** . . . . . George Hanchett  
*Modular solid-state unit does most anything*
- Low-Cost FM Stereo Multiplex Generator 63** . . . . . Al Franson  
*Ideal for setting up solid-state receivers*

## TELEVISION

- In The Shop . . . . . 24** . . . . . Jack Darr  
*Ripple and noise*
- Modular TV Sets Chart . . . . . 44** . . . . . Stanton R. Prentiss
- Kwik-Fix Troubleshooting Charts . . . . . 45** . . . . . Forest H. Belt  
*4-types of focus stages*
- R-E Reference Manual . . . . . 58** . . . . . James A. Gupton, Jr.  
*How to install TV antennas*
- Service Clinic . . . . . 84** . . . . . Jack Darr  
*Solutions to reader problems*

## GENERAL ELECTRONICS


- Looking Ahead . . . . . 4** . . . . . David Lachenbruch  
*Current happenings with future overtones*
- Editorial . . . . . 6**  
*Veteran's benefits for technical courses*
- Equipment Report . . . . . 26** . . . . . Jack Darr  
*Heathkit IG-57 postmarker sweep generator*
- How To Putter With The PUT . . . . . 50** . . . . . R. W. Fox  
*Try these circuits using the programmable unijunction transistor*
- Blueprint For Progress . . . . . 68** . . . . . L. L. Farkas  
*Your future in the electronics industry*

## DEPARTMENTS


- |  |           |                          |           |                               |           |
|--|-----------|--------------------------|-----------|-------------------------------|-----------|
| CB Troubleshooter's Casebook . . . . . | <b>76</b> | New & Timely . . . . .   | <b>2</b>  | New Products . . . . .        | <b>70</b> |
| Coming Next Month . . . . .            | <b>82</b> | New Books . . . . .      | <b>48</b> | New Semiconductors . . . . .  | <b>87</b> |
| Correspondence . . . . .               | <b>16</b> | New Literature . . . . . | <b>75</b> | Noteworthy Circuits . . . . . | <b>92</b> |



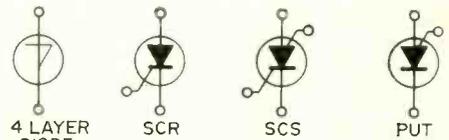4-Channel Stereo is here. Take a careful look at the latest developments in this exciting area. . . . see page 33



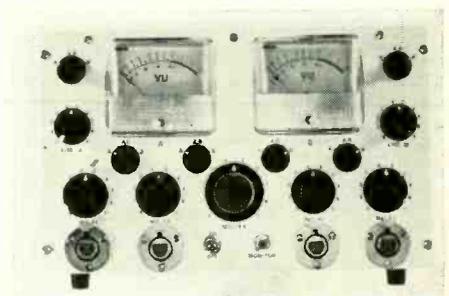How to Use the PUT (programmable unijunction transistor). Try some of these circuits. . . . see page 50



Stereo Mixer Preamp is solid-state dream unit. If you make tape recordings you need one. . . . see page 36

RADIO-ELECTRONICS, OCT. 1970. Vol. 41, No. 10  
 Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302  
 Editorial, Advertising, and Executive offices: 200 Park Ave. S., New York, N.Y. 10003. Subscription Service: Boulder, Colo. 80302.  
 Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U.S. and possessions, Canada, \$6.  
 Pan-American countries, \$7. Other countries, \$7.50. Single copies 60¢. © 1970 by Gernsback Publications, Inc. All rights reserved.  
 POSTMASTER: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.



Radio-Electronics is indexed in  
*Applied Science & Technology*  
*Index (formerly Industrial*  
*Arts Index)*

# LOOKING AHEAD

Volume 41 Number 10

RADIO-ELECTRONICS . . . FOR MEN WITH IDEAS IN ELECTRONICS

October 1970

by **DAVID LACHENBRUCH**  
CONTRIBUTING EDITOR

## Technicians and X-rays

A little-publicized survey by the U.S. Department of Health, Education and Welfare so far has indicated that there may be no grounds for fears that service technicians are exposed to excessive amounts of X-radiation from color television receivers.

The tests are being conducted with the cooperation of technicians in Baltimore. At press time, surveys had been completed in about 50 shops and HEW was hoping to enlist about 50 more. In the tests, technicians used a new type of dosimeter to determine their exposure to radiation. The tiny instruments were mounted in eyeglass frames, on finger rings and on belts, to measure radiation exposures at various vital points of the body.

At the halfway point in the tests, Dr. Robert L. Elder, acting director of HEW's Division of Electronic Products, Bureau of Radiological Health, told us that analysis of the dosimeters showed "no significant exposure" to radiation of technicians servicing color sets. "To date there has been no radiation which warrants action."

Dr. Elder also said that the survey showed that technicians were being extremely diligent—at least in Baltimore—in checking high-voltage in every service job and setting it to the manufacturers' specifications.

How about the U.S. Surgeon General's admonition to "sit 6 to 10 feet away from color TV sets?" Dr. Elder indicated that this rule is being modified slightly with the improvement in new color sets, less radiation-prone replacement parts and good radiation discipline by technicians. "It's a guide, not a mandate," he said. To those who inquire, HEW is saying: "If you are concerned about possible radiation, sit 6 to 10 feet away and call a service technician."

## Causes of radiation

While we're on the subject, another HEW study has found that the "predominant cause of X-radiation" in color sets is excessive high voltage on the picture tube. HEW made lab studies of sets which flunked factory radiation tests between June and September 1969 (there were 22 of them). The studies showed that none of the sets emitted excessive radiation when the high voltage was held down to the manufacturer's suggested maximum. On the basis of preliminary data, the studies indicated that Japanese-made color tubes "may be more poorly shielded than their American counterparts." Since the tests were made, Japanese glass manufacturers have increased the X-ray resistant content of their tube envelopes.

## 1970 TV-model sales

There's a recession on, but it hasn't affected total TV sales as much as you might think. Sales of 1970 model television sets totaled about 11.9 million units, only five percent below the record 12.55 million 1969 models sold. Of course, the difference was that black-and-white sales went up (about six percent) while color sales declined (16 percent) from the 1969 model year. And within the color category, portables—particularly foreign-made—accounted for a far greater percentage of sales than ever before.

Color sets carrying American manufacturers' brand names declined by 18 percent in the 1970 model year, while U.S.-brand monochrome sets dipped 14 percent. On

the other hand, so-called "foreign brand" imports (sets without American manufacturers' names on them) increased their sales 12 percent in color and a big 170 percent in black-and-white during the 1970 model year.

## Another videoplayer system

A dark-horse entry in the home videoplayer sweepstakes could be ABTO Inc. This firm, jointly owned by American Broadcasting Companies and Technical Operations Inc., was originally formed to sell to television stations an optical process which permits the recording and playback of color programming on black-and-white motion picture or slide film.

ABTO now is discussing a home version, in which a color television set would use a film-scanning system to produce color from low-cost Super-8 monochrome film cartridges. As an added plus, the TV-film player would be able to show conventional color home movies on a color TV screen. ABTO is interested in marketing the film system only, not the hardware.

## Higher speed facsimile

Relatively low-cost facsimile systems which use regular voice telephone lines now have become accepted items of equipment in many offices, large and small. Their major drawback, particularly where long-distance telephone lines are used, heretofore has been their slow speed—normally six minutes to transmit one 8½-x-11-inch page. But now a speed-up is coming.

The first to announce a faster office fax machine available for sale has been the Magnavox Corporation (see New & Timely, this month, for full details).

Other high-speed machines are on the way. Xerox is expected soon to introduce a 4-minute version of its 6-minute Telecopier. Comfax is developing a somewhat more elaborate machine which can transmit and receive a standard letter-size page in as little as 90 seconds.

## TV fires evaluated

How big a problem is posed by burning television receivers? National Electronics Association has released results of a survey of its own service technician members which differ rather sharply from the "clear-and-present-danger" philosophy expressed in the recent report of the National Commission for Product Safety. NEA's survey covered the period of January 1 to March 30, 1970, but was projected to cover the entire United States.

On the basis of its survey, NEA made these projections: Some 4,000 television failures occur each year which show signs of combustion. Only about 20% of these, or 800, involve any fire which is not contained within the cabinet. With some 87 million TV sets now in use, the figure comes to less than one one-thousandth of one percent. Any TV set fire is one too many, but NEA's data seems to indicate a good safety record considering the number of sets in use and the amount of time the average family spends with the TV set.

NEA gave this breakdown of the causes of television set fires: On-off switch area, 38%; high-voltage and horizontal-output transformer area, 33%; short circuits causing power-supply overloads, 13%; miscellaneous, 16%. Since the report of the National Commission on Product Safety, Underwriters' Laboratory and the television manufacturing industry have developed new and tighter fire safety standards for receivers and components. **R-E**

# Instant inventory.

Keep electronic components handy with Mallobin® Benchtop Organizers. Each Mallobin contains a popular assortment of electronic components in a stackable, interlocking plastic case. Fifteen partitioned drawers keep parts neat. And each drawer is color coded and labeled for quick location of the part you want.

Mallobins come with selected components including all types of fixed capacitors, MOL and wire-wound resistors, carbon and wire-wound controls. In addition to regular Mallobins, custom assortments are available.

Ask your Mallory distributor for Mallobin prices and details today.


**MALLORY**

**MALLORY DISTRIBUTOR PRODUCTS COMPANY**

a division of P. R. MALLORY & CO. INC.

Box 1558 Indianapolis, Indiana 46206; Telephone: 317-650-5353

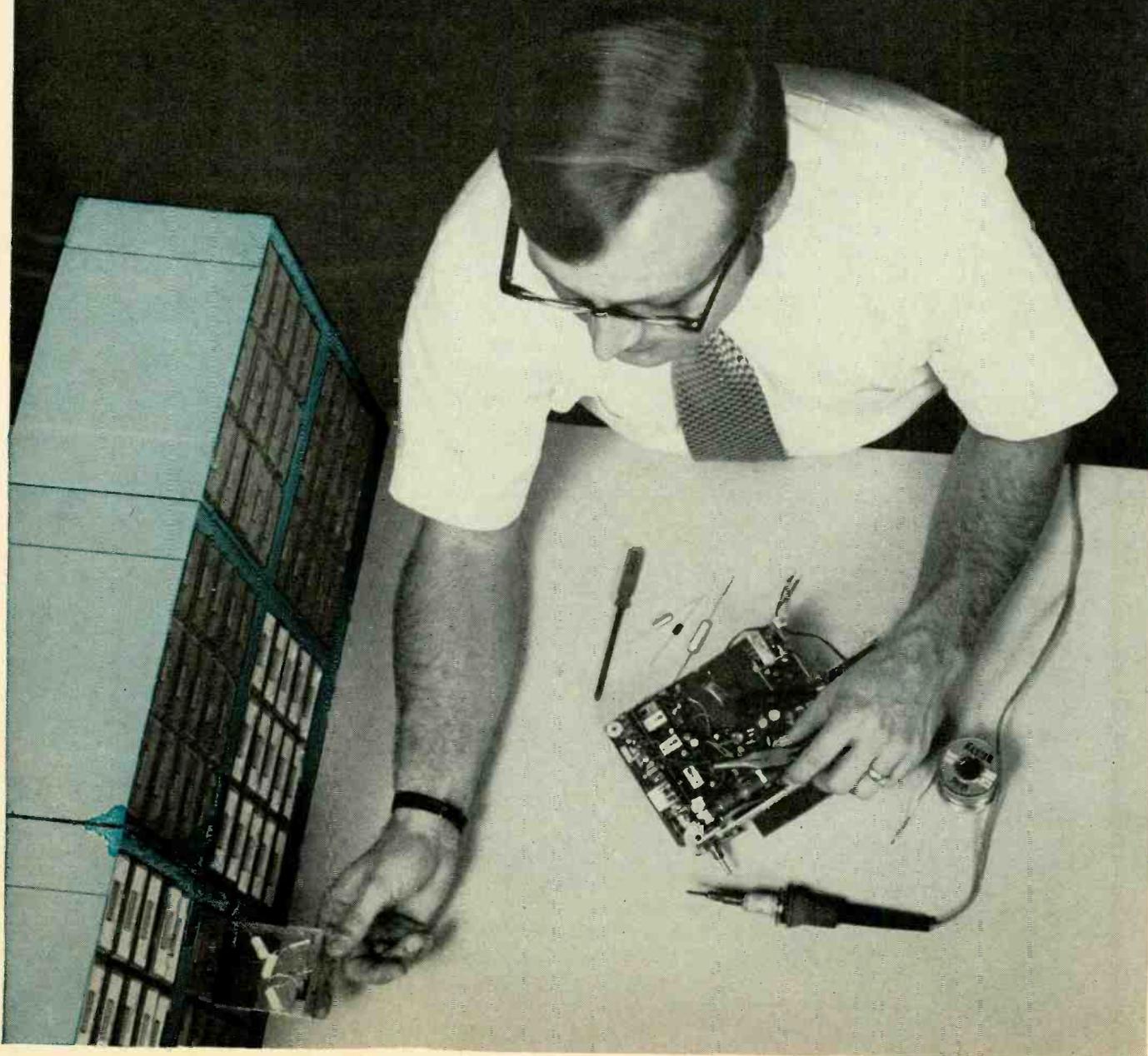Batteries **Capacitors** Cassette Tapes **Controls** **Resistors** Semiconductors • Sonalart® • Switches • Timers • Vibrators



Circle 3 on reader service card

# Editorial

## Veterans Educational Benefits

If you're a recent veteran, there are many kinds of educational benefits that are available to you. They are particularly important if you wish to increase your knowledge of electronics. Through the Veterans Administration it is possible to obtain up to \$175 per month for 36 months (a grand total of \$6400), to use toward your further education in electronics. This applies to both resident and home-study (correspondence) courses.

If you now know nothing about electronics, you can start with a basic course and go on through whatever specialty interests you. If you are already at the technician level, you can take specialized courses in communications, radar, broadcasting, computers, etc. As long as the school is approved (check with your local Veterans Administration Office) you will be entitled to financial assistance. In all instances, the school offering the course you are interested in can tell you if it is approved by the VA. They can also spell out the exact benefits you can expect to receive.

A reminder; in many instances these benefits will cover the complete cost of a correspondence course. So if you can't attend a resident school, don't write off further education as impossible. If you do take a correspondence course, all electronic equipment normally supplied with the course is included and is yours to keep.

Don't let this opportunity pass you by. These benefits are available to you for a limited time after your discharge from military service. If there's a school you want to attend, follow it up now. It's your future—get the training you need to make the most of it.

## Radio-Electronics

**HUGO GERNSBACK** (1884-1967)  
founder

**M. HARVEY GERNSBACK**,  
editor and publisher

**LARRY STECKLER**, managing editor

**Robert F. Scott**, W2PVG  
senior technical editor

**Jack Darr**, service editor

**I. Queen**, editorial associate

**Matthew Mandl**, contributing editor

**David Lachenbruch**, contributing editor

**Joan Washington**, editorial assistant

**Vincent P. Cicenia**, production manager

**Barbara Rosefelt**, production assistant

**H. Matysko**, circulation

Cover by Harry Schlack

RADIO-ELECTRONICS is published by Gernsback Publications, Inc. 200 Park Ave. South New York, N.Y. 10003 (212) 777-6400

President: M. Harvey Gernsback  
Secretary: Bertina Baer

### ADVERTISING SALES

#### EAST

Stanley Levitan, Eastern Sales Mgr.  
N.Y.C. (212) 777-6400

#### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen,  
6319 N. Central Ave.  
Chicago, Ill. 60646  
(312) 792-3646

#### PACIFIC COAST/Mountain States

J. E. Publishers Representative Co.,  
8560 Sunset Blvd., Suite 601  
Los Angeles, Calif. 90069  
(213) 659-3810

420 Market St. San Francisco, Calif.  
94111, (415) 981-4527

#### SOUTHEAST

E. Lucian Neff Associates  
25 Castle Harbor Isle  
Fort Lauderdale, Florida 33308  
(305) 566-5656

**SUBSCRIPTION SERVICE:** Send all subscription orders and correspondence to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302.

**MOVING?** For change of address, allow six weeks, furnishing both the old and new addresses and if possible attaching label from a recent issue below. Otherwise please print clearly your name and address exactly as it appears on your label.

**ATTACH LABEL HERE**

name (please print)

address

city


state

zip code

Mail to: RADIO-ELECTRONICS  
SUBSCRIPTION DEPT., BOULDER, COLO. 80302

Circle 4 on reader service card →
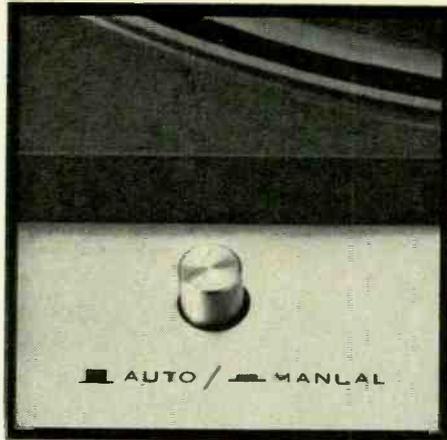
# There wasn't room for a big improvement. So we made a little one.



Our engineers made three changes in Sony's popular PS-1800 playback system. They added a little button called "Automatic/Manual"; streamlined its appearance and added "A" after the PS-1800. Obviously, none of these, earth-shaking changes.

You might never use the little button labeled "Automatic/Manual," unless you ran across a non-standard record where the recorded material goes too far into the normally "dead" space surrounding the label. Such records are few and far between. If you run up against one of them, the automatic tonearm return on the Sony would ordinarily lift and return just *before* the record's end. However, if you push the button to "Manual" the arm will track the entire record until you lift it off by hand (or push the reject button).

The styling change means that this superb playback instrument will enhance any room. And the "A" will help you identify it as the new model when you visit your hi-fi specialist.

What's more important is what our engineers didn't do to the PS-1800; what they left well


enough alone. The servo control DC motor that keeps wow and flutter at an inaudibly low 0.08; rumble down 60dB (ARLL). A variable pitch control from  $\pm 4\%$  (if you don't need it, the built-in strobe disc assures that the variation is indeed tuned out). And the balanced, low mass tone arm is capable of tracking virtually any cartridge at its lowest recommended tracking force.

Not to mention the automation system, which uses a remarkable new solid-state device, the Sony Magnetodiode (SMD). Automatically, it lifts and returns the arm without imposing any drag on the arm during play. The SMD eliminates a variety of mechanical linkages formerly necessary for this function. And there's a reject button (on the front panel so you don't have to lift the dust cover to get at it).

The price of the PS-1800A? No change. \$199.50 (suggested list), includes turntable, arm, base and dust cover (cartridge not included). Sony Corporation of America, 47-47 Van Dam Street, Long Island City, New York 11101.

## SONY® PS-1800A



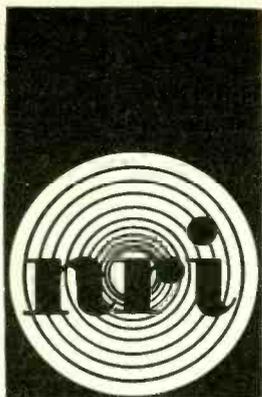

## GET A FASTER START IN THE COURSE YOU CHOOSE WITH NRI'S REMARKABLE ACHIEVEMENT KIT


When you enroll with NRI we deliver to your door everything you need to make a significant start in the Electronics field of your choice. This remarkable, new starter kit is worth many times the small down payment required to start your training. And it is only the start . . . only the first example of NRI's unique ability to apply 50 years of home-study experience to the challenges of this Electronics Age. Start your training this exciting, rewarding way. No other school has anything like it. What do you get? The NRI Achievement Kit includes: your first set of easy-to-understand "bite-size" texts; a rich, vinyl desk folder to hold your training material in orderly fashion; the valuable NRI Radio-TV Electronics Dictionary; important reference texts; classroom tools like pencils, a ball-point pen, an engineer's ruler; special printed sheets for your lesson answers—even a supply of pre-addressed envelopes and your first postage stamp.

# ***Learning electronics at home is faster, easier, more interesting with new achievement kit***

Only NRI offers you this pioneering method of "3 Dimensional" home-study training in Electronics, TV-Radio . . . a remarkable teaching idea unlike anything you have ever encountered. Founded more than half a century ago—in the days of wireless—NRI pioneered the "learn-by-doing" method of home-study. Today, NRI is the oldest, largest home-study Electronics school. The NRI staff of more than 150 dedicated people has made course material entertaining and easy to grasp. NRI has simplified, organized and dramatized subject matter so that any ambitious man—regardless of his education—can effectively learn the Electronics course of his choice.
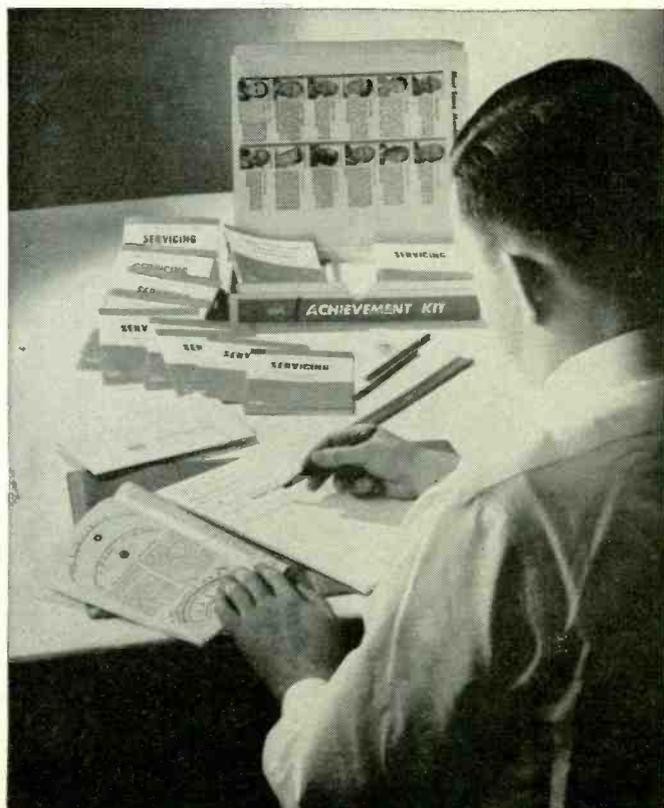
### **DISCOVER THE EXCITEMENT OF NRI TRAINING**

Whatever your reason for wanting knowledge of Electronics, you'll find the NRI "3 Dimensional" method makes learning exciting, fast. You build, test, experiment, explore. Investigate NRI training plans, find out about the NRI Achievement Kit. Fill in and mail the postage-free card. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016



## ELECTRONICS COMES ALIVE AS YOU LEARN BY DOING WITH CUSTOM TRAINING EQUIPMENT

Nothing is as effective as learning by doing. That's why NRI puts so much emphasis on equipment, and why NRI invites comparison with equipment offered by any other school, at any price. NRI pioneered and perfected the use of special training kits to aid learning at home. You get your hands on actual parts like resistors, capacitors, tubes, condensers, wire, transistors and diodes. You build, experiment, explore, discover. You start right out building your own professional vacuum tube voltmeter with which you learn to measure voltage and current. You learn how to mount and solder parts, how to read schematic diagrams. Then, you progress to other experimental equipment until you ultimately build a TV set, an actual transmitter or a functioning computer unit (depending on the course you select). It's the practical, easy way to learn at home—the priceless “third dimension” in NRI's exclusive Electronic TV-Radio training method.



## SIMPLIFIED, WELL-ILLUSTRATED “BITE-SIZE” LESSON TEXTS PROGRAM YOUR TRAINING

Lesson texts are a necessary part of training, but only a part. NRI's “bite-size” texts are as simplified, direct and well-illustrated as half a century of teaching experience can make them. The amount of material in each text, the length and design, is precisely right for home-study. NRI texts are programmed with NRI training kits to make things you read come alive. As you learn, you'll experience all the excitement of original discovery. Texts and equipment vary with the course. Choose from major training programs in TV-Radio Servicing, Industrial Electronics and Complete Communications. Or select one of seven special courses to meet specific needs. Check the courses of most interest to you on the postage-free card and mail it today for your free catalog.

Available Under  
**NEW  
GI BILL**

If you served since  
January 31, 1955, or  
are in service, check GI  
line in postage-free card.
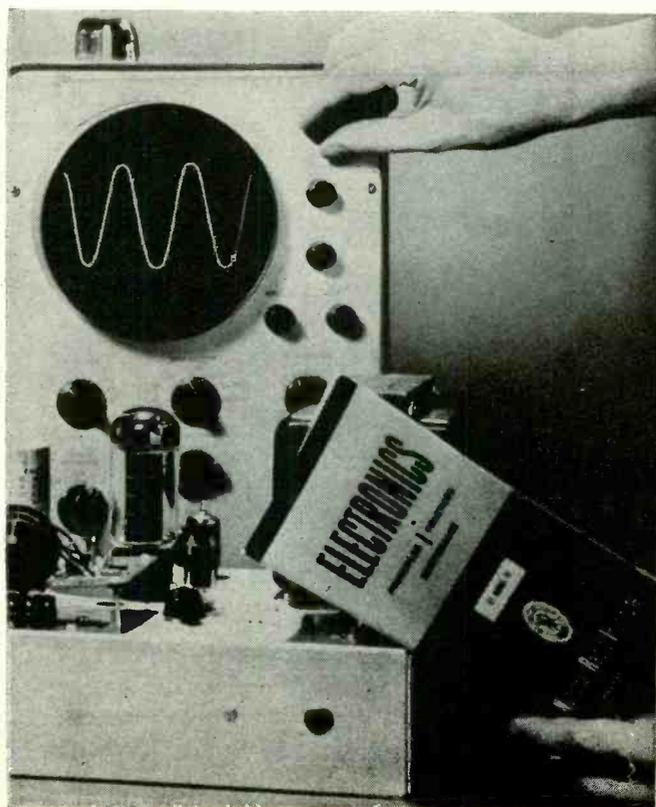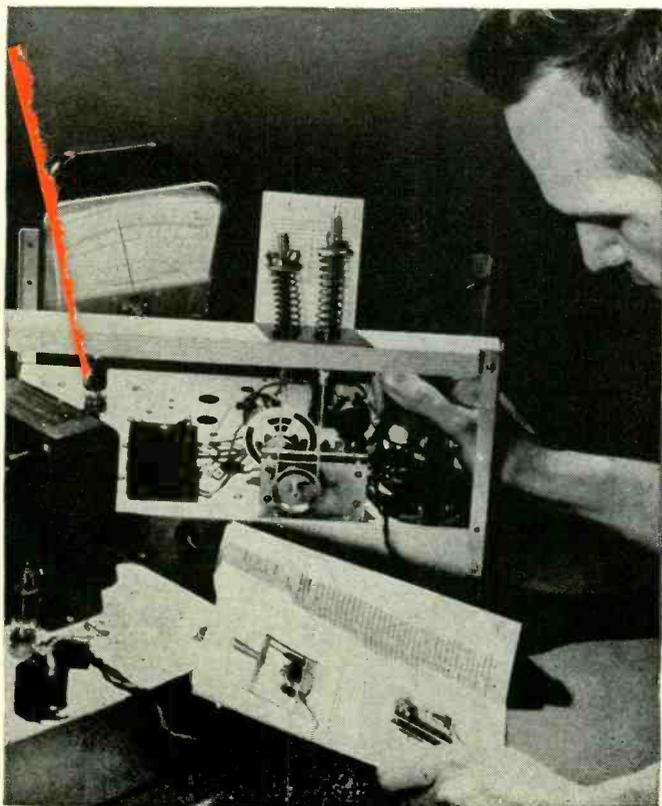
## *custom training kits “bite-size” texts*



# only MASTER offers you 32 choices



Choose your combination: with or without switches and safety shields . . . four different wattages . . . 120 or 230 volts. Snap-in, rugged ceramic elements are encased in stainless steel, easily changed in seconds. Compressed air or inert gas concentrates precisely controlled heat up to 1000° exactly where you want it. The perfect tool at an unbeatable price . . . as low as \$75! Send for your complete FREE Catalog of flameless Heat Guns, Blowers and Torches.

## MASTER HEAT TORCHES

Racine, WI 53403

Circle 5 on reader service card

## New & Timely

(continued from page 2)

speed model which offers the user the option of a 3 minute or 6 minute transmission for

full-page documents (drawings, proofs, financial and priority reports, photographs) through a telephone coupling.

The two-speed model offers a significant reduction in both telephone line charges and operator time while operating in the 3-minute setting, and the 6-minute mode provides improved resolution and picture quality. In addition, the 6-minute setting permits the Magnafax 860 to speak to a wide number of facsimile devices installed in the USA. ★



## Teleconsultation Is Now



TV PSYCHIATRIC CONSULTATION shows how system will operate in Boston.

BOSTON, MASS.—Television now links two large Greater Boston teaching hospitals in a way never attempted anywhere before.

Massachusetts General Hospital in Boston and the Veterans Administration Hospital, 25 miles away in Bedford, share their expertise over closed-circuit television. The unique venture embraces all three purposes of each institution: patient care, physical education, and research.


Dr. John H. Knowles, General Director of the MGH, and John J. Whalen, Director of the V. A. Hospital, primarily a psychiatric institution, announced the project recently. Newsmen watched a program beamed between the two hospitals. After a successful pilot period of two months, the project is now open on a regular basis.

The psychiatrist and patient at Bedford will also be able to see whoever is at the MGH Teleconsultation room.

The two-way nature of the system enables either of the two hospitals to seek medical or allied medical consultations. Residents in training at MGH—in dermatology, for example—with their instructor will be able to see skin disorders that would be rare or non-existent to MGH. At the same time, the Bedford patient will gain by the consultation that is part of the demonstration. And, an engineer at the MGH could examine a chart shown by an engineer at Bedford in addition to hearing a word description of a hospital engineering program. Medical and non-medical teaching programs

(continued on page 14)

Circle 7 on reader service card →

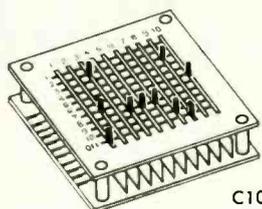

C10-20A WITHOUT EXTENSIVE WIRING

## PROGRAM YOUR AUDIO SYSTEM

THIS HIGH DENSITY MATRIX SELECTOR SWITCH eliminates hundreds of soldered joints and hours of labor when you pre-program, select monitor audio systems or insert components in breadboarding circuits. Useful in applications from EKG equipment to water sprinkler time control systems; also in electrical component testers, numerical control for machine tools or to control, transmit and receive frequency.

### THIS COUPON WORTH \$10.00

OFF REGULAR \$25.00 PURCHASE PRICE OF A C10-20A

Mail this coupon and get a C10-20A Matrix Selector Switch with 100 crosspoints for only \$15.00 postpaid. (Regularly \$25.00) No COD's. Check or money order must accompany order.

MAIL TODAY! OFFER LIMITED

## CHERRY

CHERRY ELECTRICAL PRODUCTS CORP.  
3618 Sunset Avenue, Waukegan, Illinois 60085

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 6 on reader service card

# ANY NUMBER CAN PLAY.

The time is tomorrow. The name is TEAC. The machines are the Simul-trak™ Series TCA-40. And they're here today.

This series of tape decks combines the best features of high-quality quarter-track, two-channel operation with four-channel stereo capability. It's the best of two worlds, in three versions, four channels.

All three models feature four-channel playback, as well as regular two-channel playback with auto reverse. What's more, Models 40 and 41 can be modified later to the full four-channel capability of Model 42, at moderate cost. Meanwhile, any one of these machines is compatible with your present equipment; no modifications or reassembly are necessary.

So what are you waiting for?



Simul-trak™ surrounds you with sound – and gives you a headstart on tomorrow.

## TEAC

TEAC Corporation of America • 2000 Colorado Ave. • Santa Monica, Calif. 90404
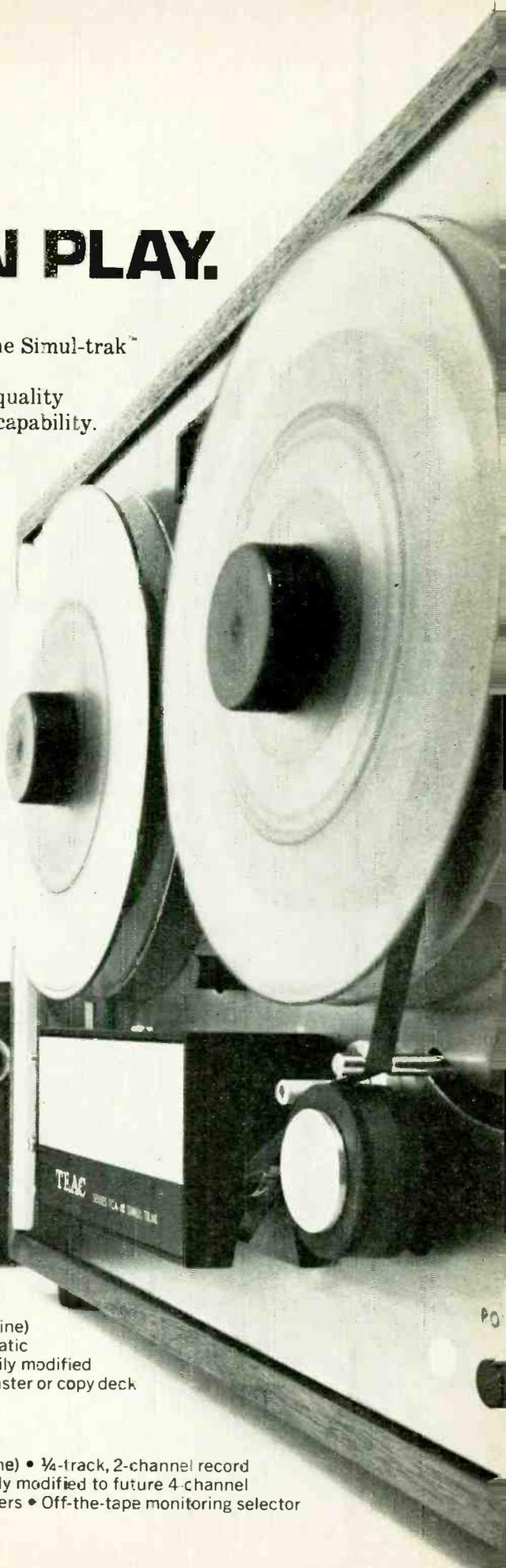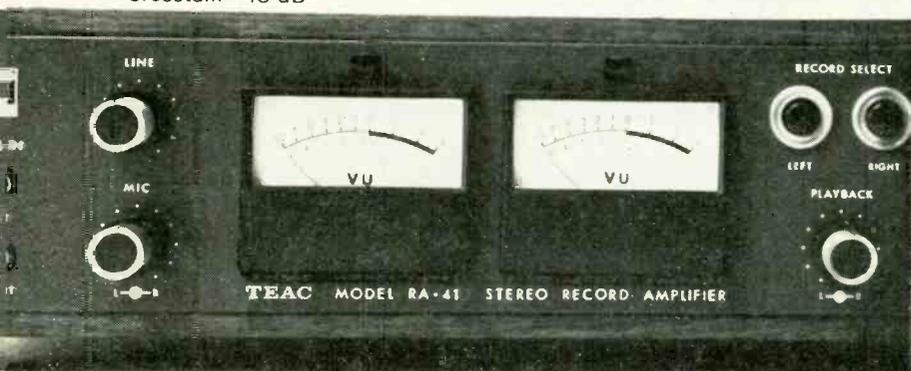
### General Specifications

- Speeds – 7½ and 3¾ ips
- Motors – 1 hyst. sync., 2 outer rotors
- Wow and Flutter – 0.12% @ 7½ ips
- Freq. Response – ±3 dB 50-15,000 Hz @ 7½ ips
- S/N Ratio – 50 dB
- Crosstalk – 48 dB



### TCA-40

- ¼-track, 2-channel stereo playback, plus 4-channel stereo playback (in-line)
- ¼-track, 2-channel erase and record heads for future "step-up"
- Automatic reverse for uninterrupted playback of conventional 2-channel tapes
- Readily modified to TCA-41 or 42
- Built-in solid-state preamplifiers
- Ideal for duplication master or copy deck

### TCA-41 *(Illustrated)*

- ¼-track, 2-channel stereo playback, plus 4-channel stereo playback (in-line)
- ¼-track, 2-channel record
- Automatic reverse for uninterrupted playback of 2-channel tapes
- Readily modified to future 4-channel recording capability, or TCA-42
- Solid-state playback and record preamplifiers
- Off-the-tape monitoring selector

### TCA-42


- ¼-track, 2-channel stereo playback, plus 4-channel stereo playback (in-line)
- ¼-track 2-channel stereo record and 4-channel stereo record (in-line)
- Automatic reverse for uninterrupted playback of 2-channel tapes
- Total of 8 separate solid-state playback and record preamplifiers
- Off-the-tape monitor selectors



# TRUE TRIGGERED SWEEP OSCILLOSCOPE/VECTORSCOPE
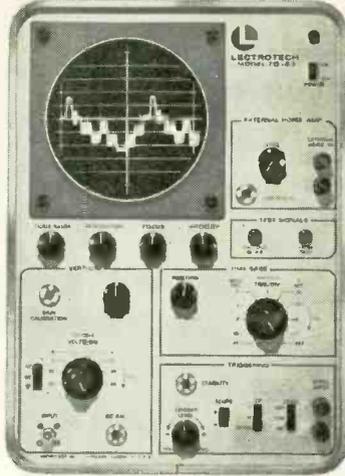
## MODEL TO-50

- DC to 10 mhz frequency response
- .02 volt sensitivity
- Calibrated vertical attenuator
- Calibrated time base
- Supplied with combination Direct/Lo-Cap probe
- 5 X magnifier
- Automatic triggering mode
- 5" flat face tube edge-lit graticule



One Year Warranty  
Made in U.S.A. **339<sup>50</sup>**



See your distributor or write Dept. RE-10  
**LECTROTECH, INC.**  
4529 N. Kedzie Ave., Chicago, Illinois 60625

Circle 8 on reader service card

## New & Timely

(continued from page 12)


will also be developed between the two institutions.

Physicians at the hospital in Boston have examined some 1,700 patients at the airport since the system originated. Both airport employees and passengers have availed themselves of the ser-

vice aimed at making optimal use of the busy physician's time by eliminating travel to the airport medical station.

Late in the spring of 1969, Dr. Thomas F. Dwyer, an MGH psychiatrist, began interviewing psychiatric patients over the closed-circuit network. ★

## New Coast-Guard Radar-TV

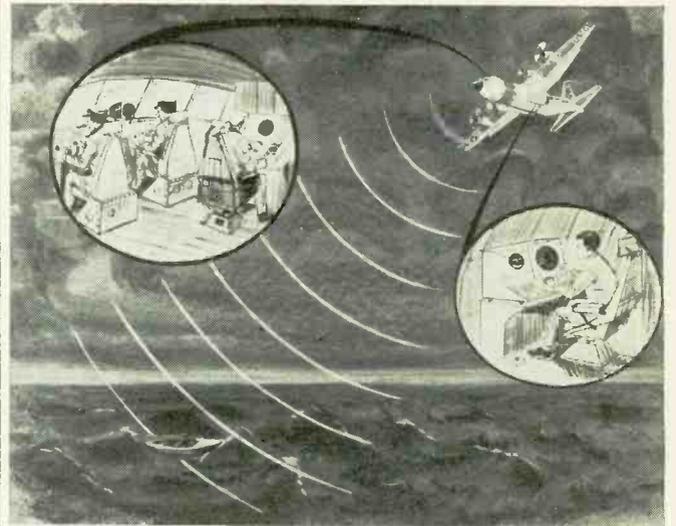

WASHINGTON, D.C.—A new airborne search radar which converts radar information to daylight viewing will increase the U.S. Coast Guard's capabilities for small craft searches and rescues.

The new system, called Search and Rescue Airborne Radar, will be built by the AIL division of Cutler Hammer for the Coast Guard to detect objects as small as a 16-foot fiberglass boat in five-foot seas at distances of 10 miles from the searching Coast Guard aircraft. The system is designed to detect these objects in clear weather as well as heavy fog and rain.

The system will have a scanning antenna that will turn 300 revolutions per minute, a rate five times greater than that of today's operational radars. The resultant increase in radio beams, reflected by the consistency of the targets looked at, will reduce the interference from random objects in the ocean, such as wave crests which might normally appear on the radar scope as targets. Distinguishing this random "sea return" from small targets has been a major problem in the past.

One of the most important features of the system will be the conversion of the radar information to a television screen. This will be the first development of a motion compensated system that converts radar blips to a TV type bright display on board a flying aircraft.

The relationship of small targets to other targets which appear on the radar screen will be accentuated because of a new design which takes the relationship of the input to the output amplifier logarithmically instead of linearly. **R-E**

FOR ALL FIRE • POLICE • SECURITY • INDUSTRIAL • BUSINESS USE



**we get thru — where others fail**  
OPERATES ANYWHERE—INDOORS, OUTDOORS... STEEL BLDGS.

**SONARCOM**  
FM TRANSCEIVERS

**Model 2301 \$375<sup>00</sup>**  
132-174 MHz  
VHF-FM 1 CHANNEL  
1 pair of crystals and 1 set of standard batteries.

**Model 2301A \$475<sup>00</sup>**  
132-174 MHz  
VHF-FM 2 CHANNELS  
1 pair of crystals and 1 set of standard batteries.

**Model 2302 \$595<sup>00</sup>**  
450 to 470 MHz  
UHF-FM 1 CHANNEL  
1 pair of crystals, 1 set of standard batteries and Tone.

**Model 2303A \$475<sup>00</sup>**

32.5-41 — 42-50 MHz  
Available in 2 Frequency Ranges  
LF-FM 2 CHANNELS\*  
1 pair of crystals, 1 set of standard batteries less tone\*

\*Model 2303A available with tone at additional charge.

Professional performance! Perfectly designed for efficient dependable and continuous heavy duty use. Provides instant voice contact with base stations mobile units and other portable transceivers • Compatible with all 2-way systems • Receiver and transmitter operates on independent frequencies • sensitive, noise immune squelch • external connections for antenna, earphone and charger • 1.6 watt output. FCC TYPE ACCEPTED & D.O.C. APPROVED—U.S. BUREAU OF MINES APPROVED

**SONAR RADIO CORPORATION**

73 Wortman Avenue, Brooklyn, N.Y. 11207

Please send information on the SONARCOM. Dept. 219

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 9 on reader service card



## Want to **tie up** the service market?

Start with the Channel Master Opti-Vue Color CRT with the three year warranty, one TV set that needs a picture tube, and one customer.

Tell your customer how Opti-Vue guarantees the finest color he's ever seen for a full three years--- not just one or two. And how, just in case something should go wrong, he gets a free replacement. So it may cost a little more, but it's worth it. And the price is right, too!

Now, you've secured the part of the set he's most worried about he's sure to call you when any other part fails. You've tied up all his service business for a full three years by taking care of his knott est prob em, and, not unimportantly, your customer's very happy with his new color vision!

So go ahead and tie one on with

**OPTI-VUE**  
The line with 3 year warranty!

**CHANNEL MASTER**

Div. of Avnet, Inc., Ellenville, N.Y. 12428

# ANNOUNCING

## An All New MIGHTY MITE Tube Tester

*Now Checks more tubes and it's faster than ever before with*


- all solid state FET circuitry for instant-on action . . . first time in tube tester history
- New solid action push button function switches to speed up every test



Here is the latest version of the famous Sencore Mighty Mite tube tester; it's updated and streamlined in appearance and performance. No more wasted time waiting for the tube tester to warm up when you have a hot troublesome tube in your hand ready to test. The TC154 Mighty Mite VI is instant-on with no meter drift. New FET circuitry still enables you to read grid leakage up to 100 megohms because it too is a high impedance device like a vacuum tube. New circuitry permits even higher sensitivity check on heater to cathode leakage; from 180,000 ohms to 300,000 ohms. The Mighty Mite still checks for shorts between each and every tube element with the famous stethoscope shorts check. New two-toned vinyl-covered and brushed steel presents a truly professional instrument. See your Sencore distributor today and ask him for the new all solid state Mighty Mite. Only Sencore has it.

Over 60,000 Mighty Mites now in use.

Only \$99.50

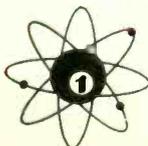

### SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

3200 Sencore Drive, Sioux Falls, So. Dakota 57107

Circle 11 on reader service card



#### HOW TO FIND PARTS

I was sorry to read about John Sikara's complaint in the Correspondence Column about the difficulty in obtaining parts for construction articles.

I would like to suggest a method for the readers to find their parts. The first stop is, of course, their normal distributor from whom they can pick up all the standard parts. The second move is to find a distributor for the manufacturer of the parts they are missing. This usually can be done by checking the catalogues, yellow pages of the telephone book, or calling the nearest sales office or representative of that company. Then order the missing parts from that distributor. In some cases it may mean a delay of several weeks but the distributor can get the parts. If the parts still can not be purchased, then write directly to the company that makes them at the place they are made. The last resort, of course, is for the builder to write to the author in care of the magazine.

RICHARD W. FOX  
Applications Engineer  
General Electric Company  
Auburn, New York, 13021

#### 8-TRACK-DATA NEEDED

As a subscriber, I appeal to you or your readers for information—schematics and operating instructions—covering 8-track player/recorder manufactured by Kalof Electronics, Van Nuys, Calif. It is model U.T. 801, Serial No. D 1054. Will appreciate any information anyone has on subject player/recorder.

BOB SPICER  
P. O. Box 191  
Fort Gaines, Ga. 31751

#### OLD COPIES AVAILABLE


I have several vintage copies of *Radio News* magazine, forerunner of *RADIO-ELECTRONICS*. Available are issues for the years 1924, '25, '26, '27 and '28. I have all issues for the year 1925 and one copy of the March 1940 issue.

HAROLD DISHMAN  
Route 5  
Maryville, Tenn.

(continued on page 22)

WE HAD JUST REPRINTED OUR LITERATURE . . .  
 ADDING OUR FIFTH NEW PLANT . . .  
 WHEN WE DID IT AGAIN . . . PRECISION TUNER SERVICE

**ADDS** Springfield, Mass.

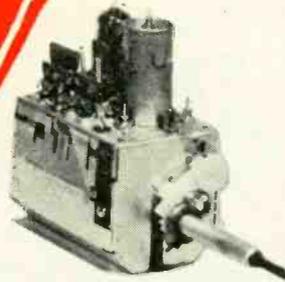

**does  
its  
thing**



**...again!**

**For YOU:  
MORE &  
FASTER  
PROFIT**

YOU can offer this specialized, expert service. Quality Tuner Service is our bag, man! Experienced, conscientious PTS craftsmen with sophisticated, precision (and expensive) tools and equipment mean faster PROFIT for you with PTS 8-hour service . . . .

**TURNOVER**

. . . . No doubt about it! PTS mails your tuner back the SAME DAY it is received! Now less in-transit time, too!

**Precision  
Tuner Service**



. . . and now with even shorter in-transit time!

VHF or UHF

**\$8.95**

UV Combo's

**\$14.95**

Major Parts, Tubes, Transistors charged at Net Price

**CUSTOMIZED REPLACEMENTS AVAILABLE FOR \$12.95 UP (NEW OR REBUILT)**


FIRST TO OFFER 365-DAY GUARANTEE!  
 COLOR — BLACK & WHITE — TRANSISTOR TUNERS — ALL MAKES GUARANTEED COLOR ALIGNMENT — NO ADDITIONAL CHARGE

For fastest service, send faulty tuner with tubes, shields and all broken parts to:

HOME OFFICE—	Box 272—Bloomington, Ind. 47401	Tel. 812/824-9331
EAST—	Box 334—W. Springfield, Ma. 01089	Tel. 413/734-2737
SOUTHEAST—	4451 N.W. 37th Ave., Miami, Fla. 33142	Tel. 305/633-0002
SOUTHWEST—	Box 7332—Longview, Tex. 75601	Tel. 214/753-4334
WEST—	Box 1431—Turlock, Calif. 95380	Tel. 209/632-2928

FREE JOB CARDS FREE SHIPPING LABELS

Circle 12 on reader service card

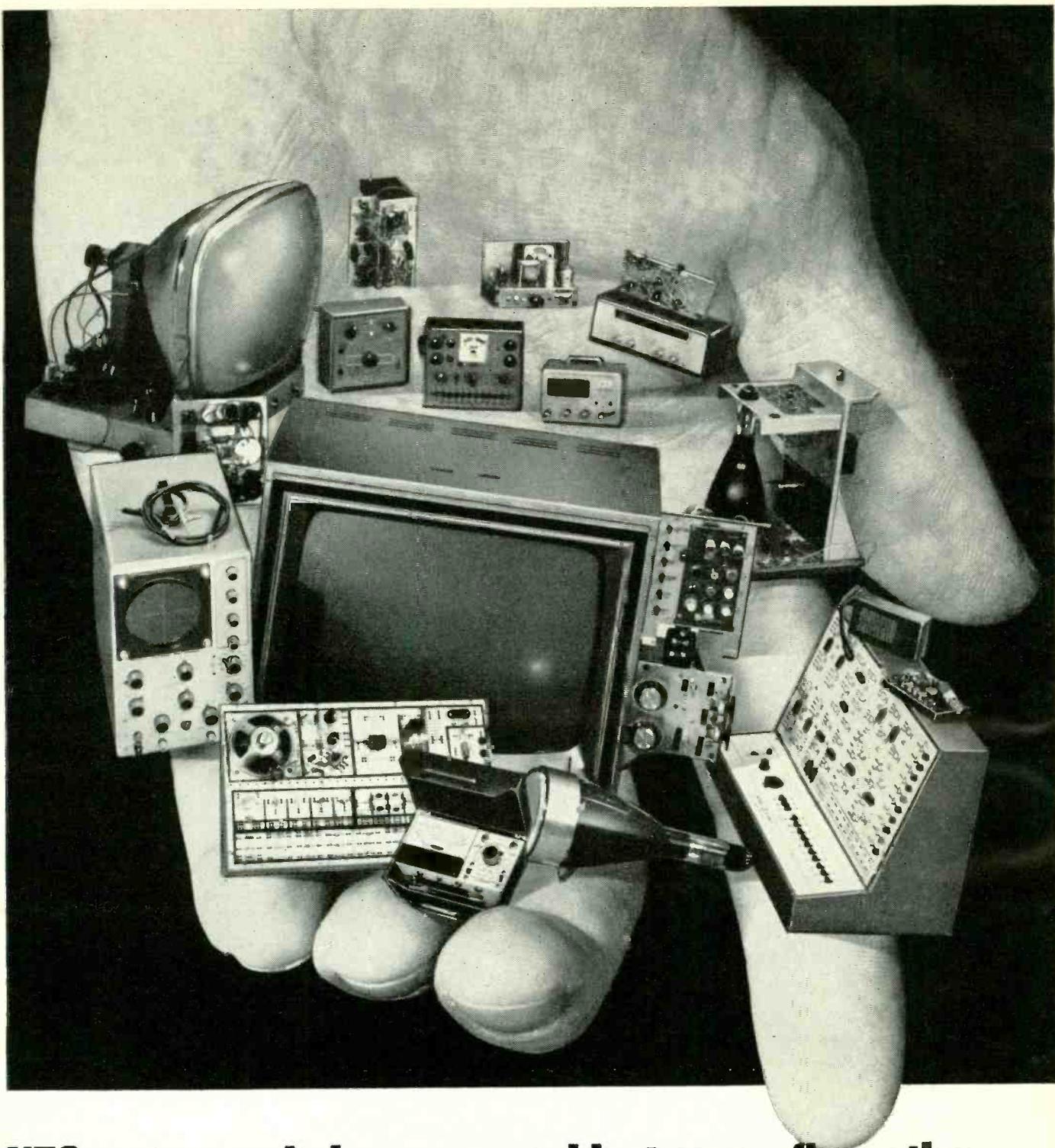

## NTS puts a whole new world at your fingertips.

NTS home training can put a whole new way of life in the palm of your hand. A new, exciting job, a much bigger income is now easily within your reach.

NTS training is something special. We provide all the kits you need for the most effective training. National Technical Schools sends kits with every course, and teaches you to build and test a


wide range of professional equipment — the same kind of equipment you'll actually use on the job. That's the NTS "Project Method" — training that's practical and in-depth. You learn everything from fundamentals to the latest innovations. From beginning to end, NTS makes it fascinating and fun to learn this way. And all you need is a little

spare time and an interest in electronics.

Each year, men are moving into important new jobs, or their own businesses, straight out of NTS electronics training. NTS is what's happening to men everywhere. Check the coupon. Take hold of the career you want most. Do it now. No obligation. No salesman will call.

**We pack your electronics course with kits to make your training fast. You'll enjoy every minute of it.**

## NTS COLOR TV SERVICING

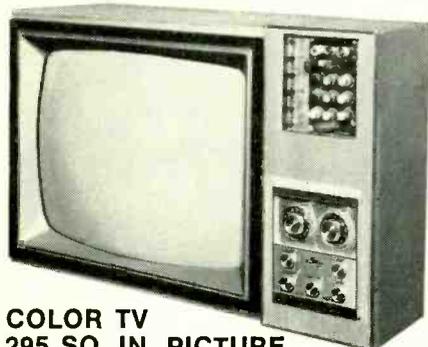


**COLOR TV  
295 SQ. IN. PICTURE**

NTS training provides an easy way to become a professional home-entertainment service technician. You receive a big screen Color TV with many unique features. The unit even includes self servicing equipment that permits you to make all normal test operations. No additional test equipment is needed for adjusting your set. In addition you get an AM-SW radio, Solid-State radio, Field-Effect Transistor Volt-Ohmmeter, and Electronic Tube Tester. You learn about Electronic principles and trouble shooting, hi-fi, multiplex systems, stereo, and color TV servicing.
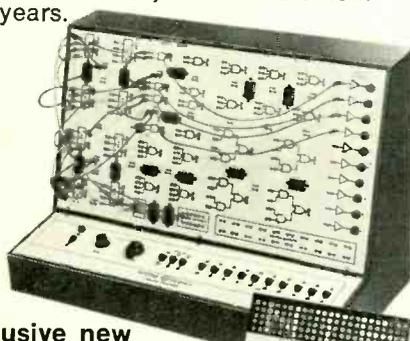
## NTS COMPUTER ELECTRONICS

This is the future. And it's happening now. The number of computers will increase many times in the next few years.



**Exclusive new  
Compu-Trainer®**

If card is missing check coupon and mail for free color catalog and sample lesson. Now.

### **National Technical Schools**

4000 S. Figueroa St., Los Angeles, Calif. 90037

Please rush Free Color Catalog and Sample Lesson, plus information on course checked below. No obligation. No salesman will call.



NTS offers a solid grounding in computer operation, wiring, data processing and programming. One of the 10 important kits included is our exclusive Compu-Trainer®. It's a fully operational computer logic trainer — loaded with integrated circuits — the first ever offered in home study. It introduces you quickly to how, what, when and why of computers . . . from theory to practical servicing techniques. This unit is capable of performing 50,000 operations per second.

## NTS ELECTRONICS COMMUNICATIONS


Choose from two exciting courses to get into the big-paying fields of transmitting and receiving equipment: (1) The FCC License Course. (2) The Master Course in Electronic Communications (more comprehensive, with Citizens' Band Two-Way-Radio). Either Communications program qualifies you for your FCC First Class Commercial Radio-Telephone License — *NTS assures you will pass this FCC exam within six months after successfully completing your course or your tuition is refunded.* Kits include an Amateur-Phone 6 Meter VHF Transceiver — NTS exclusive, 6 transistor Solid-State Radio, Volt-Ohmmeter (fully transistorized).



**5 Watt AM Transmitter/  
Receiver**
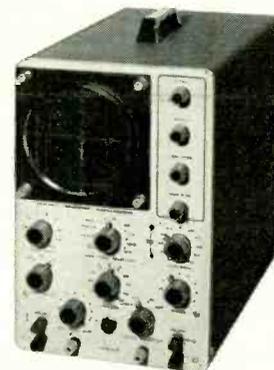
## NTS AUTOMATION/ INDUSTRIAL ELECTRONICS

Let NTS put you into the age of electronic controls. Systems Automation is rapidly becoming the emphasis of modern industry. Your NTS training in automation electronics includes equipment like a 5" wide band Oscilloscope. You also get the new NTS Electronics Lab. It's an exclusive NTS experimental laboratory — a complete workshop that simplifies learning about solid-state, miniature and integrated circuits.



**5" Oscilloscope**

## CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in facilities devoted exclusively to technical training. Check box in coupon.

**NATIONAL TECHNICAL SCHOOLS**  
WORLD-WIDE TRAINING SINCE 1905

4000 South Figueroa Street  
Los Angeles, Calif. 90037, U.S.A.

## APPROVED FOR VETERANS

Accredited Member: National Association of Trade and Technical Schools; National Home Study Council.

- Master Course in Color TV Servicing
- Color TV Servicing
- Master Course in TV & Radio Servicing
- Practical TV & Radio Servicing
- Master Course in Electronic Comm.
- FCC License Course
- Master Course in Electronics Tech.
- Industrial and Automation Electronics
- Computer Electronics
- Basic Electronics

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- Check if interested in Veteran Training under new G.I. Bill
- Check if interested only in Classroom Training at Los Angeles

Dept. 206-100

**PRINTED-CIRCUIT PATTERNS**

I quite enjoy your magazine, especially the many fine construction articles you have presented in the past. However, I am experiencing difficulty in having negatives of the printed-circuit layouts reproduced, due to copyright laws which commercial print shops must abide by.

I would appreciate your sending me a release to photocopy the printed circuit layouts for photo-etching my boards.

HOWARD F. GARRISON  
Englewood, Colo.

*The photocopy shop is right. For them to go ahead and duplicate without permission does violate the copyright laws. However, it is our intent, when we present a printed circuit layout, to have our readers use the pattern to make boards for their own personal use. Therefore, we do authorize readers to use these patterns and make copies of them for their convenience in the construction of the particular article described; provided this is not for manufacture and is for their personal use.—Editor*

**WHY NOT TUBES?**

I want to congratulate your

magazine for the challenging projects that are published in its pages. But I notice that most of the electronics magazines publish only construction articles based on solid-state components. I agree that this type of project has its advantages over the tube-based ones, but I feel that tubes are not yet out and that the reader should have a chance to acquire some practical background on the operation of tube equipment.

Also, many readers have various amounts of tubes on hand and the surplus market is loaded with inexpensive ones. So how about some articles with vacuum tubes?  
UBALDO ORGNERO  
Calgary, Canada

*We agree that tubes are not dead, but in many instances there is little excuse for using them. The transistor is often easier and less expensive to use, and always smaller. When you use tubes you have a much more complex power supply associated with the circuitry too.*

*We will present articles using tubes whenever the use of tubes gives the reader a tangible advantage; perhaps in high-frequency applications or extremely high-power circuits, otherwise we will continue to present projects based on solid-state components.—Editor*

**KWIK-FIX MIXUP**

Two errors appeared in the June 1970 issue that should be of interest to all readers.

In the Kwik-Fix article, page 44, second column; the first paragraph reads "Both horizontal and vertical blanking are applied to the emitter of Q1 by R6. R5 and C2 shape the horizontal pulse. These positive-going pulses bias the transistor completely off for their duration. That makes high-amplitude negative-going pulses in the collector."

This is erroneous; there is no inversion when a signal is applied to the emitter. Applying a positive-going pulse to the emitter is the same as applying a negative-going pulse to the base.


The second sentence in the second column of the same article on page 44 reads "L2 and L4 are a matched load for the load line." Actually L4 is the peaking coil of V2.

B. J. BROWN  
Trion, Ga.

**R-E**

**IN THIS ISSUE**

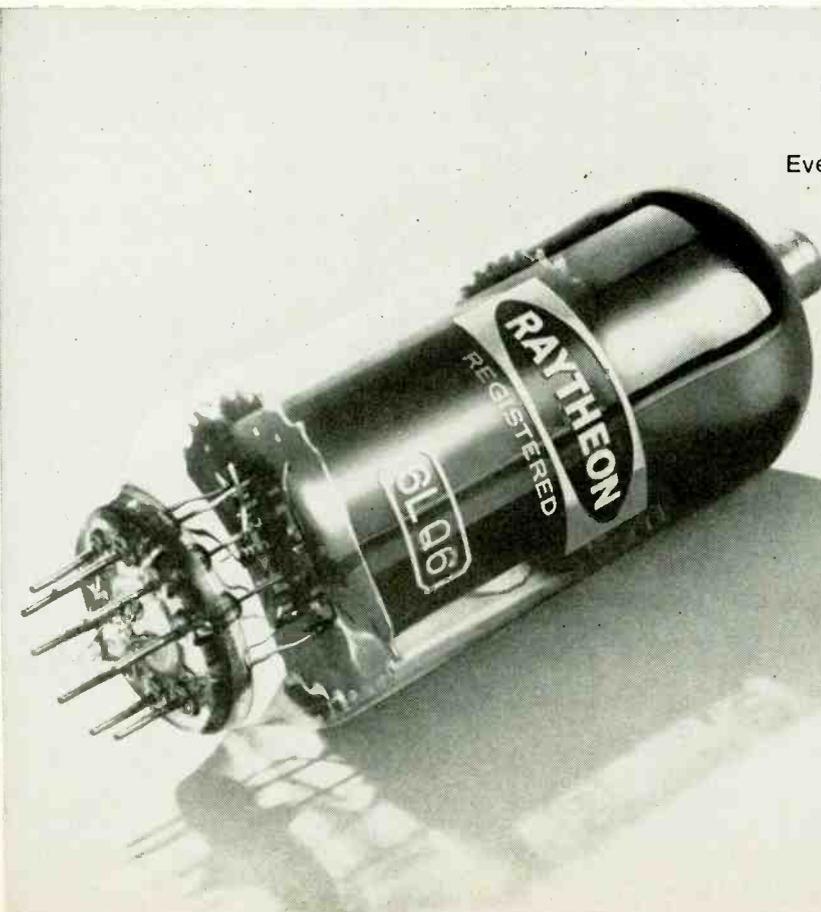**Stereo system not delivering top performance. Better take a look at the article starting on page 40. Peter Sutheim tells how to get better sound from your stereo system.**




# 99.99% reliable


Every now and then, one of our tubes fizzles—and somehow it's the one you install. Even we don't know how you happen to receive that particular tube. But we do know that it doesn't happen more than once in thousands of times. Raytheon receiving tubes—including Raytheon Tubes for Imported Sets—have to be extra reliable. Because, Raytheon is the leading independent supplier of receiving tubes to independent servicemen. We don't have competing service trucks or retail outlets. So, we depend on you just as much as you depend on us.



Circle 13 on reader service card

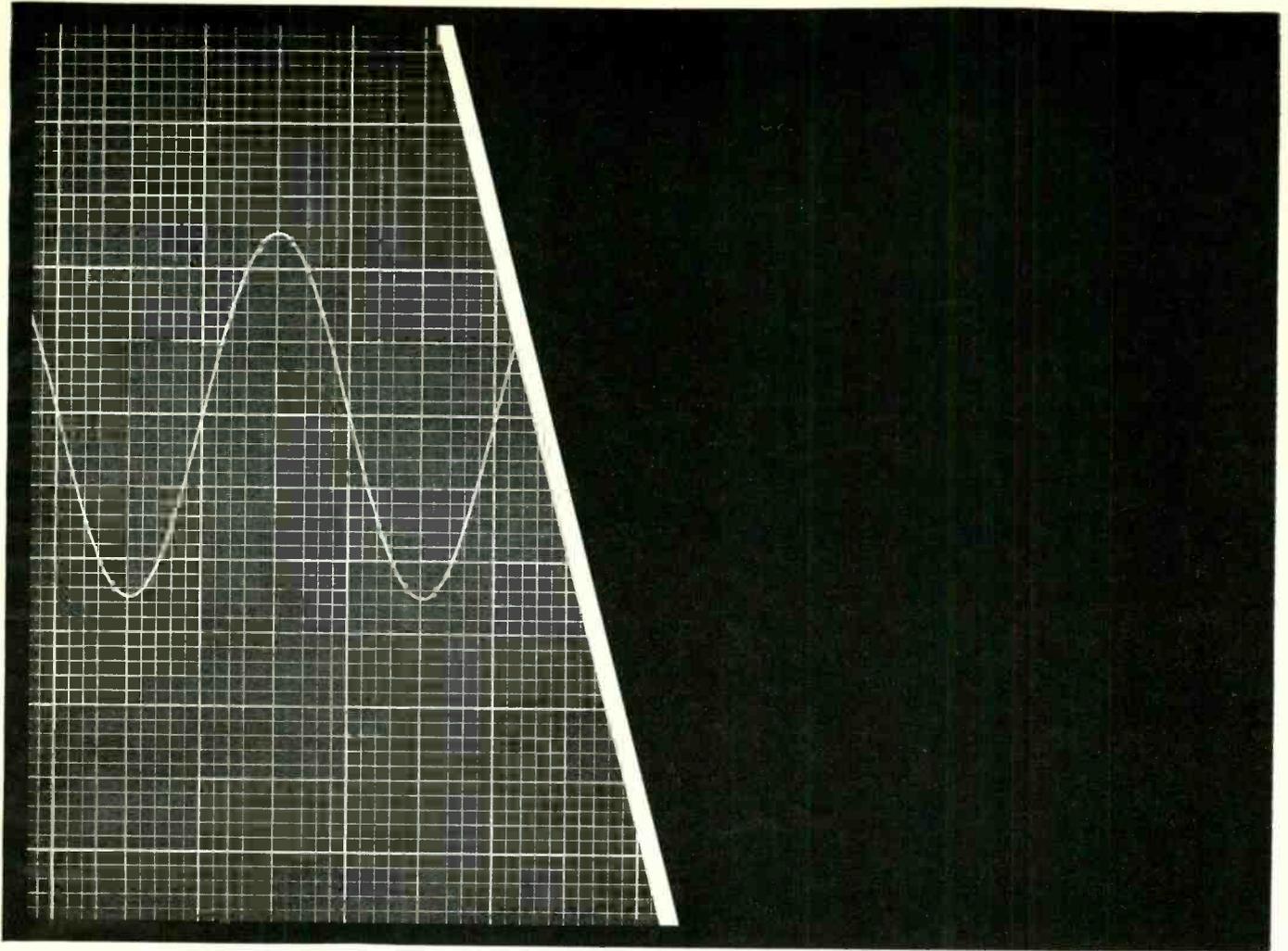
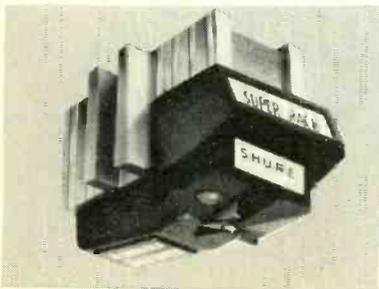
## Finally! A visually perfect sine wave!



The sine wave above was generated by Shure's design computer—it looks like the sine wave that was generated by the *Shure V-15 Type II Improved Super Track Cartridge* in the Hirsch-Houck testing laboratories . . . "the first cartridge we have tested to have done so," according to their published report. This perfect sine wave was generated during the playing of the heavy bass bands on the Cook Series 60 test record at  $\frac{3}{4}$  gram, and the 30 cm/sec 1,000 Hz band of the Fairchild 101 test record at 1 gram. They were impressed, and we were pleased. And we'll be pleased to send you the full Hirsch-Houck Report on the "trackability champion." Shure Brothers Inc., 222 Hartrey Ave., Evanston, Ill. 60204.



Circle 14 on reader service card

# In the Shop . . . With Jack

By JACK DARR  
SERVICE EDITOR



## another great new idea

# reversible ratchet handles

for Xcelite "99" tools

These two unique plastic (UL) handles extend the usefulness of all Xcelite Series "99" tools, make welcome additions to any "99" set.

Both regular (99-1R) and Tee (99-4R) types accept more than 60 individually available nutdriver, screwdriver, and special purpose snap-in blades to speed and simplify assembly and service work.

Fully enclosed ratchet mechanism is built to highest socket wrench quality standards. Recessed reversing shift operates at the flick of a thumb. Patented spring chuck holds blades firmly.

*nationwide availability through local distributors*

REQUEST BULLETIN N670

Made in U.S.A.

# XCELITE

XCELITE, INC., 10 Bank St., Orchard Park, N. Y. 14127  
In Canada contact Charles W. Pointon, Ltd.

Circle 15 on reader service card

## Ripple and Noise; Unfiltered Rig

"Ripple" is what you have left over after you get through filtering the dc power supply. Like all leftovers, it can cause trouble. Turkey hash for 6 days in a row is monotonous. It's not the actual 60- or 120-Hz ripple itself which causes the trouble—of course you can get a faint hum-bar or two in the picture, but this isn't the worst of it.

The presence of 60-Hz ripple indicates far more serious trouble. When this is above normal limits, your dc power supply filtering, or more accurately, decoupling, is a long way from being good enough. In all electronic circuits, one thing is common to all stages—the dc power supply. With the great number of different spikes, pulses, signals of all frequencies, and so on, that you have, it is absolutely imperative that you get rid of them after you've used them! If any of them is allowed to get into another stage, you'll really find some weird and unusual troubles.

This is caused by *feedback*. Even if it is only from the output of a stage to its input, this can cause oscillation or instability. If they happen to get back in the right phase, it can cause degeneration and "mysteriously" reduce the gain of a stage. If the feedback signal comes from a stage with different signals, we get some real howlers.

Example—a horizontal-frequency sawtooth or spike signal getting into the video amplifier stage. This causes horizontal shading of the raster—one side is darker than the other. Vertical-frequency feedback causes shading from top to bottom. If this is strong enough, you get the odd symptom of the picture "going out from top to bottom" as the brightness is turned off, as if you were pulling a shade down over it. The key clue in such cases is the *nature* of the effect. Side-to-side shading is coming from the horizontal circuits; top-to-bottom shading from the vertical.

In either case, the basic cause is the same—feedback. Feedback happens because the filtering is not good enough. In the "source-stage" this signal, after we've used it to sweep the screen, has to go *somewhere*. It's supposed to go back to the (common) power-supply, and from there straight to ground.

This signal is "ac." It goes to ground because the normal impedance of the dc power supply is *very* low. For example, a 50- $\mu$ F capacitor has 63.7 ohms reactance at 50 Hz. At 5000 Hz, only 0.637 ohm. At 15,750 Hz, this gets down to about 0.2 ohm or so. (This is why you will see a greater 60-Hz ripple

than the other frequencies—the lower the frequency the greater the reactance of a capacitor  $X_c = \frac{1}{2\pi fC}$ . In practical circuits, you'll find several capacitors totaling 200- to 300- $\mu$ F or more, and a total impedance of practically zero ohms.

We've got to keep this impedance very low to prevent feedback at *any* frequency. The used signals must be "drained off" to keep them out of mischief. Think of this in terms of plain old resistance. If we had a 100 mA signal flowing through a 100 ohm resistance, we'd develop a 10-volt ripple. This will actually cause the plate voltage (or collector voltage) of stages fed from this line to vary 10 volts. You can see what kind of trouble that would cause!

The easiest way of finding this kind of trouble is with your scope. Just touch the direct probe to the hot terminals of all electrolytic capacitors anywhere near the circuit which is showing signs of trouble. A good trick is to set the scope up for a certain deflection at 1.0 volt p-p. Any ripple greater than this is very apt to cause trouble. Don't confine your efforts to 60-Hz ripple alone! Anything you see on there, except a nice straight "dc line" means trouble!

In tube circuits, you'll find 6 to 8 volts of ripple (60-Hz) at the rectifier output. However, at the filter output this had better be down to about 1.0 volt p-p maximum. One volt of ripple in a 300- to 400-volt circuit won't be too bad simply because of the very small *percentage*. In transistor power supplies, with their far lower voltages, a 1.0-volt ripple means difficulties; percentage again. Solid-state power supply circuits use very large filter capacitors. You'll find several thousand microfarads of filter capacitance.


The quickest check in a tube circuit is to bridge a good capacitor across the suspected unit. Look for the ripple to disappear. If it does, replace the capacitor. **DO NOT** (Repeat: **DO NOT**) bridge large filter capacitors across transistor power supply circuits. Turn it off, hook up the new unit, then turn it back on. The charging surge of a 2000- $\mu$ F capacitor is fearsome and can easily blow a fuse or pop a transistor.

Sometimes the ripple won't go away, but will merely drop a little when a new capacitor is bridged across the old one. If this happens, the old capacitor probably has a high power factor (loss of filtering efficiency) and it will have to be taken completely out of the circuit and replaced by a good one to clear up the trouble. **R-E**

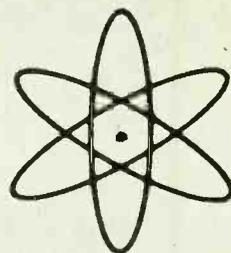**don't miss this opportunity**

**If You Have What It Takes  
to Qualify for Training in Electronics  
We'll Not Only Train You...**

**We'll Help You Finance  
Training and Help Place You  
In the Job You Want!**



Just a few short years ago, who could have imagined electronic marvels like the micro-miniaturized printed circuit, no larger than the head of a pin . . . battery-powered heartbeat regulators . . . computers that make split-second calculations it would take the human brain years to duplicate! This is the amazing world of technology.

The demand for trained Electronics Specialists and Draftsmen is increasing every year! These are well-paid, prestige positions with practically unlimited opportunities for advancement. In 12 months or less, United Technical Institute can prepare you to take your place in this dynamic, expanding field. You can study right at home, in your spare time and at your own pace — or attend a UTI resident school near you.

Because UTI is an eligible institution under the Federally Insured Student Loan Program, you may attend the Institute on a government-guaranteed educational loan. And after you finish your training, we can help you find your first position!


**Accredited Member of National Association of Trade and Technical Schools. Approved for Veteran Training.**

Get the facts now! Just clip the coupon and send today for a **FREE**, fact-filled book describing the exciting opportunities in electronics, and how you can qualify for them. We'll rush your book by return mail so you can read it and decide for yourself. No obligation, of course. But don't delay — clip the coupon for your free book today! →

	<b>United Technical Institute</b>	
	division of Career Academy	
	125 W. Wells St. Milwaukee, Wis. 53203	Dept. 07N215205
	Please rush me your free 28 page booklet with all the details on your Electronics course	
Name _____	(Please print)	Age _____
Address _____		
City _____		State _____ Zip _____
Phone _____		
I am interested in: <input type="checkbox"/> Classroom Study <input type="checkbox"/> Home Study <input type="checkbox"/> Facts on GI Bill		


Circle 16 on reader service card

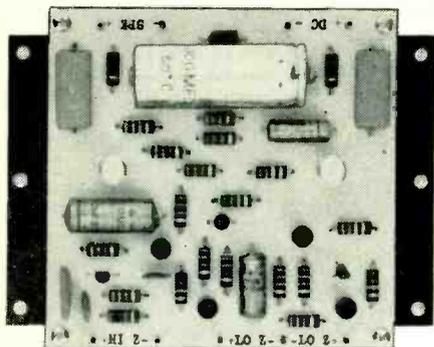**SPECTRUM PRODUCTS PRESENTS  
HIGH QUALITY POWER AMPLIFIERS  
AT MANUFACTURERS PRICES**



**ONE FET AND 7 SILICON TRANSISTORS.**  
**POWER OUTPUT.** 25 watts RMS at 8 ohm load. (35 watts IHF music power)  
**FREQUENCY RESPONSE.** — 1DB from 10Hz to 50,000Hz at full RMS output.  
**DISTORTION.** Less than one (1) percent.  
**THREE INPUT CHANNELS.** One megohm FET high impedance input, and two (2) low impedance inputs.  
**INPUT SENSITIVITY.** High impedance .5 volt for full RMS output. Low impedance .25 volt for full RMS output. Low impedance 1.5 volt for full RMS output.  
**TRANSISTORIZED TEMPERATURE SENSOR.** Holds idle current at a constant 10 ma. preventing thermal damage.  
**DC OPERATING VOLTAGE.** 45 volts.  
**DC OPERATING CURRENT.** 10 ma. idle, 1 ampere at full IHF output.  
**OVERALL DIMENSIONS,** 4x4x2 inches. **PRICE.** \$16.50

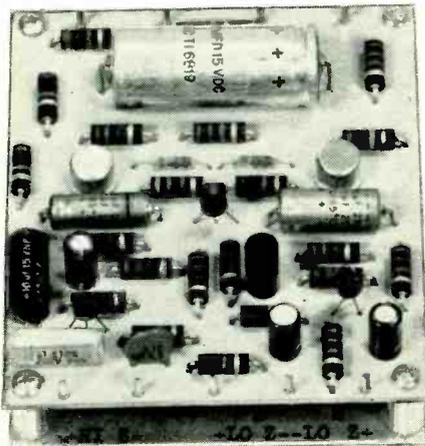**SPECTRUM PRODUCTS  
PRESENTS THE NEW  
SELECTRA-MATIC POWER AMPLIFIER**



**ONE FET AND 7 SILICON TRANSISTORS.**  
**SELECTRA-MATIC.** Automatically lets you select any power from 1.5 to 15 watts RMS at 8 ohm load. (22 watts IHF music power)  
**FREQUENCY RESPONSE.** 3DB from 10Hz to 50,000Hz at full RMS output.  
**DISTORTION.** Less than 1 percent.  
**THREE INPUT CHANNELS.** One megohm FET high-impedance input. Two low-impedance inputs.  
**INPUT SENSITIVITY.** (35 volt supply) High impedance .25 volt for full RMS output. Input (1) Low impedance .5 volt for full RMS output. Input (2) Low impedance .05 volt for full RMS output.  
**TRANSISTORIZED CURRENT CONTROL.** Automatically holds distortion at a minimum.  
**TRANSISTORIZED TEMPERATURE SENSOR.** Holds idle current at a constant 20 ma. thus preventing thermal damage.  
**DC OPERATING VOLTAGE.** Anywhere from 12 to 35 volts.  
**DC OPERATING CURRENT.** 20 ma. idle. 750 ma. at full IHF output.  
**OVERALL DIMENSIONS.** 3 x 3½ x 1½ inches.  
**PRICE.** \$16.50, two (2) for \$31.00


**SATISFACTION GUARANTEED  
SPECTRUM PRODUCTS P.O. BOX 2562  
CULVER CITY, CALIFORNIA 90230**

Circle 17 on reader service card

# EQUIPMENT REPORT
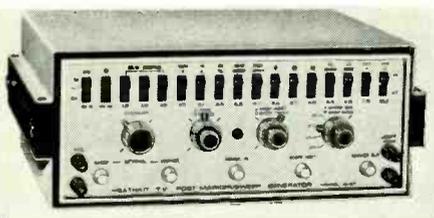
## Heathkit IG-57 Post-Marker Sweep Generator

For manufacturer's literature, circle No. 21 on Reader Service Card.



THE MORE THINGS A SINGLE TEST INSTRUMENT can do, the more valuable it is in the service shop. The Heathkit IG-57 TV Post-Marker Sweep Generator certainly meets this evaluation. With this versatile test instrument, you can use sweep-alignment techniques on any standard piece of electronic equipment "with the greatest of ease" and accuracy.

Many technicians have hesitated to use sweep alignment in the past, simply because it was such a hassle getting everything hooked up; also because of a nagging doubt that it wasn't accurate! Previous methods of putting markers on the sweep curve caused several troubles, the worst of which was actual distortion of the curve by the markers. In the end, we actually did not know whether we had helped alignment or made it worse.

With the system used in the IG-57, this doubt is gone. It uses the "post-marker" circuit; this is the only way in which frequency markers can be added to sweep-response curves without distortion of or interference with the actual frequency response of the unit being aligned. The markers are put on the curve *after* it has gone through the tuner circuits. A special "marker-amplifier" and mixer circuit is used. The marker frequencies cannot affect the response of the tuned circuits. Amplitude of the curve and the markers can be controlled individually.

Above all, the whole thing is *simple*. Two cables connect to the TV set, sweep input and output, and two to the scope, vertical and horizontal inputs. Turn it on and away you go. To further reduce clutter on the bench, the IG-57 even has two dc bias supplies on its front panel: many alignment instructions specify a fixed bias, especially in color TV i.f.'s. No separate bias box is needed. The dc voltage goes to 15 volts, and the polarity can be reversed, if necessary, for use with transistor forward-bias age, etc.

The list of specifications for the IG-57 is fascinating. The instrument provides three sweep ranges: low, 2.5 to 5.5 MHz, for color bandpass and sound i.f. alignment. The 10.7-MHz i.f. of FM tuners can be swept by the 2nd harmonics on LOW. Next, IF for TV i.f. alignment covers 38 to 49 MHz, on fundamentals. Finally, the RF sweep goes from 64 to 72 MHz (channel 4) and a high band (192-198 MHz, channel 10) on the harmonic. All these have a minimum signal output of 0.5 volt (500,000  $\mu$ V) which is, as one of my colleagues used

to say, "enough to blow a signal through an inch pine plank!"

However, as in all sweep alignment, it is the markers which are the most important. Marker *accuracy* is the key to the usefulness of any sweep generator, and the thing which has caused us the most trouble in the past.

The IG-57 meets this requirement by using crystal oscillators. There are 16 of these, each individually controlled by switches on the top of the front panel.

One very important part of the i.f. sweep alignment procedure is now much simpler—trap alignment. This is vital in color TV alignment. A misplaced trap can cause color suckouts and a multitude of other problems. (For a test, try running the 41.25-MHz trap up on the side of the curve till it gets the color carrier, and you'll find out!) With the crystal markers, the three most important traps—39.75, 41.25 and 45.75 MHz, can be tuned right on the nose.

For additional help in this, as well as in sound i.f., sound detector, stereo FM and aft alignment, a 400-Hz signal can be modulated onto the marker signal. The trap is simply tuned until audio modulation is at its lowest point, and there you are—the trap is now at its maximum attenuation. Or a sound detector is aligned for maximum AM rejection, which is the "right place."

Special connecting cables and probes are used. These have tiny clips for connecting into the circuits. An rf probe is used for i.f. and rf alignment, and a demodulator probe can be used at intermediate points through the TV i.f. (specified in some manufacturer's alignment instructions, for link and trap alignment). Incidentally, these probes are light and small.

Frequency modulation (sweep) is done with an all-electronic circuit using a controllable inductor. No more mechanical sweeps, with hums and buzzes. Tiny toroidal cores coupled to the inductor control the amount of frequency deviation (sweep width) and the centering. These two things are controlled by a concentric dual-knob on the panel, for one-hand operation. Incidentally, the "curve height" ("Trace Height") and marker pip amplitude ("Marker Height") are also a concentric dual control. This makes adjustment of the curve height on the scope and the marker heights on the curve *very easy*. A separate seven-step attenuator is provided for regulating the output signal voltage. This has 1.0-dB, 3.0-dB, 6.0-dB, two 10-dB and two 20-dB positions. Any or all of these can be used simultaneously. With this accurate attenuator, the scope can be calibrated in dB; this makes alignment with markers set "so many dB down" from a given point very simple.

The IG-57 is available from Heath as a ready-made instrument or in kit form. **R-E**

# Newest SAMS Books

## Hi-Fi Stereo Servicing Guide

by ROBERT G. MIDDLETON. A complete guide to effective hi-fi and stereo servicing. Provides the basis for a full understanding of hi-fi tuner and amplifier circuitry and procedures for servicing this type of equipment. The proper use of audio test and measurement equipment and the basic principles of acoustics are also given. Covers all hi-fi components (except record players and tape recorders). Order 20785, only... \$3.95

## ABC's of Avionics

by LEX PARRISH. Provides a basic understanding of avionics—the electronic equipment used to insure the safety of crew and passengers. The type of equipment and the techniques employed in private aircraft operations are featured. Discusses requirements for basic communications, navigation aids, instrument flight aids, weather guidance, and flight control safety devices. Order 20764, only... \$3.50

## Mobile-Radio Systems Planning

by LEO G. SANDS. Here is practical, basic information about various types of mobile-radio systems, how they work, their capabilities and limitations, system requirements, licenses, channels, band and frequency selection, transmitter-receiver selection, antenna systems, and accessories. Includes an invaluable system-requirements form for planning a mobile-radio system. Order 20780, only... \$4.50

## Transistor-TV Servicing Made Easy

by JACK DARR. This practical guide will help you become skilled in the special techniques of transistor-TV servicing. Covers tools and equipment required; transistors and transistor-servicing techniques; power supplies; horizontal and vertical sweep circuits; video i-f and output circuits; agc and sync-separator problems; tuners; audio circuits; and selecting replacement transistors. Order 20776, only... \$4.95

## Security Electronics

by JOHN E. CUNNINGHAM. Explains the operating principles of modern electronic devices and systems used to provide security against crime. Describes intrusion alarms and intrusion-detection devices. Includes chapters on the detection of hidden metal objects, announcement of detected intrusions, bugging, debugging, and speech-scrambling systems, and future developments. Order 20767, only... \$4.50

## How to Hear, Police, Fire, and Aircraft Radio

by LEN BUCKWALTER. After World War II, police, fire, and aircraft radio moved to the less crowded vhf bands, and the "police band", which was found in many older radios, was silenced. Few listeners had receivers capable of covering the vhf band, because they were relatively expensive. With the advent of solid-state circuitry, a wide variety of relatively low-cost monitoring equipment is available. This book is a guide to the selection and use of vhf radio. Order 20781, only... \$3.50

## 101 Questions and Answers About Transistor Circuits

by LEO G. SANDS. Answers the most commonly asked questions about transistor circuitry. Explains transistor nomenclature, biasing, the three basic circuit configurations, input and output impedances, current and voltage gain, and other basic considerations. Covers power supplies and circuits; af circuits; rf circuits, and oscillators. Order 20782, only... \$3.50

## 1-2-3-4 Servicing Automobile Stereo

by FOREST H. BELT. This book first applies the ingenious "1-2-3-4" repair method to both mechanical and electrical equipment. It then proceeds to cover the electronic and mechanical principles of automobile stereo, fm multiplex and tape cartridge systems. Finally, the book shows how to apply the method to auto stereo systems. Order 20737, only... \$3.95

## North American Radio-TV Station Guide, 6th Edition

by VANE A. JONES. Lists all radio and TV stations in the U.S., Canada, Mexico, and the West Indies. Includes operating a-m, fm, and television stations, as well as those that are about to start operating, or are temporarily off the air. Separate listings arranged by geographical location, frequency (or channel), and call letters make this guide the most useful one available. Order 20779, only... \$2.95



## Aviation Electronics, 2nd Edition

by KEITH W. BOSE. This practical handbook for aircraft owners, pilots, technicians, and engineers explains the design, operation, and maintenance of aviation electronics equipment. Covers automatic direction-finders, distance-measuring equipment, omnirange, ATC transponders and weather radar, communications and instrument-landing systems, and related devices and systems used in aviation today. Order 20743, only... \$9.95

## 1-2-3-4 Servicing Transistor Color TV

by FOREST H. BELT. The "1-2-3-4 Method" is a simple, logical, step-by-step process that helps do the service job the right way and the easy way. In this book, the fundamentals of transistor color TV are covered, followed by a detailed explanation of how to apply the method for quick troubleshooting and easy repairs. Order 20777, only... \$4.95

## Questions & Answers on Short-Wave Listening

by H. CHARLES WOODRUFF. A helpful guide to the interesting world of listening afforded by short-wave receivers. Questions and answers cover international short-wave broadcasting, frequencies, and services; how short-wave is transmitted; how short-wave is received; and how short-wave receivers are constructed and operated. Order 20783, only... \$3.50

### HOWARD W. SAMS & CO., INC.

Order from your Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. RE-100  
4300 W. 62nd St., Indianapolis, Ind. 46268

Send books checked at right. \$\_\_\_\_\_ enclosed

Send FREE 1970 Sams Book Catalog

Name \_\_\_\_\_

PLEASE PRINT

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

- |                                |                                |
|--------------------------------|--------------------------------|
| <input type="checkbox"/> 20785 | <input type="checkbox"/> 20777 |
| <input type="checkbox"/> 20764 | <input type="checkbox"/> 20767 |
| <input type="checkbox"/> 20780 | <input type="checkbox"/> 20781 |
| <input type="checkbox"/> 20776 | <input type="checkbox"/> 20782 |
| <input type="checkbox"/> 20743 | <input type="checkbox"/> 20737 |
| <input type="checkbox"/> 20783 | <input type="checkbox"/> 20779 |

Circle 18 on reader service card

**Hunting for a better job?**

**Here's the  
license  
you need  
to go after  
the big ones**



**A Government FCC License can help you bring home up to \$10,000, \$12,000, and more a year. Read how you can prepare for the license exam at home in your spare time—with a passing grade assured or your money back.**

**I**F YOU'RE OUT TO BAG A BETTER JOB in Electronics, you'd better have a Government FCC License. For you'll need it to track down the choicest, best-paying jobs that this booming field has to offer.

Right now there are 80,000 new openings every year for electronics specialists—jobs paying up to \$5, \$6, even \$7 an hour... \$200, \$225, \$250, a week... \$10,000, \$12,000, and up a year! You don't need a college education to make this kind of money in Electronics, or even a high school diploma.

But you *do* need knowledge, knowledge of electronics fundamentals. And there is only one nationally accepted method of measuring this knowledge... the licensing program of the FCC (Federal Communications Commission).

**Why a license is important**

An FCC License is a legal requirement if you want to become a Broadcast Engineer, or get into servicing any other kind of transmitting equipment—two-way mobile radios, microwave relay links, radar, etc. And even when it's not legally required, a license proves to the world that you understand the principles involved in *any* electronic device. Thus, an FCC "ticket" can open the doors to thousands of exciting, high-paying jobs in communications, radio and broadcasting, the aerospace program, industrial automation, and many other areas.

So why doesn't everyone who wants a good job in Electronics get an FCC License and start cleaning up?

The answer: it's not that simple. The government's licensing exam is tough. In fact, an average of two out of every three men who take the FCC exam fail.

There is one way, however, of being pretty certain that you will pass the FCC exam. And that is to take one of the FCC home study courses offered by Cleveland Institute of Electronics.

CIE courses are so effective that better than 9 out of 10 CIE graduates who take the exam pass it. That's why we can back our courses with this iron-clad Warranty: Upon completing one of our FCC courses, you must be able to pass the FCC exam and get your license—or you'll get your money back!

**They got their licenses and went on to better jobs**

The value of CIE training has been demonstrated time and again by the achievements of our thousands of successful students and graduates.

**2 NEW CIE CAREER COURSES**

**1. BROADCAST (Radio and TV) ENGINEERING**... now includes Video Systems, Monitors, FM Stereo Multiplex, Color Transmitter Operation and CATV.

**2. ELECTRONICS ENGINEERING**... covers steady-state and transient network theory, solid state physics and circuitry, pulse techniques, computer logic and mathematics through calculus. A college-level course for men already working in Electronics.

Ed Dulaney, Scottsbluff, Nebraska, for example, passed his 1st Class FCC License exam soon after completing his CIE training...and today is the proud owner of his own mobile radio sales and service business. "Now I manufacture my own two-way equipment," he writes, "with dealers who sell it in seven different states, and have seven full-time employees on my payroll."

Daniel J. Smithwick started his CIE training while in the service, and passed his 2nd Class exam soon after his discharge. Four months later, he reports, "I was promoted to manager of Bell Telephone at La Moure, N.D. This was a very fast promotion and a great deal of the credit goes to CIE."

Eugene Frost, Columbus, Ohio, was stuck in low-paying TV repair work before enrolling with CIE and earning his FCC License. Today, he's an inspector of major electronics systems for North American Aviation. "I'm working 8 hours a week less," says Mr. Frost, "and earning \$228 a month more."

**Send for FREE book**

If you'd like to succeed like these men, send for our FREE 24-page book "How To Get A Commercial FCC License." It tells you all about the FCC License... requirements for getting one... types of licenses available... how the exams are organized and what kinds of questions are asked... where and when the exams are held, and more.

With it you will also receive a second FREE book, "How To Succeed In Electronics." To get both books without cost or obligation, just mail the attached postpaid card. Or, if the card is missing, just mail the coupon below.

**ENROLL UNDER NEW G.I. BILL.** All CIE courses are available under the new G.I. Bill. If you served on active duty since Jan. 31, 1955, or are in service now, check box on reply card for complete details.

**CIE Cleveland Institute of Electronics**

1776 E.17th St., Cleveland, Ohio 44114

Accredited Member National Home Study Council  
A Leader in Electronics Training... Since 1934



**Cleveland Institute of Electronics**

1776 East 17th Street, Cleveland, Ohio 44114

Please send me without cost or obligation:

Your 44-page book "How to Succeed In Electronics" describing job opportunities in Electronics today, and how your courses can prepare me for them.

Your book on "How To Get A Commercial FCC License."

I am especially interested in:

- Electronics Technology
- Broadcast Engineering
- First Class FCC License
- Electronic Communications
- Industrial Electronics
- Electronics Engineering


Name \_\_\_\_\_ (PLEASE PRINT)

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

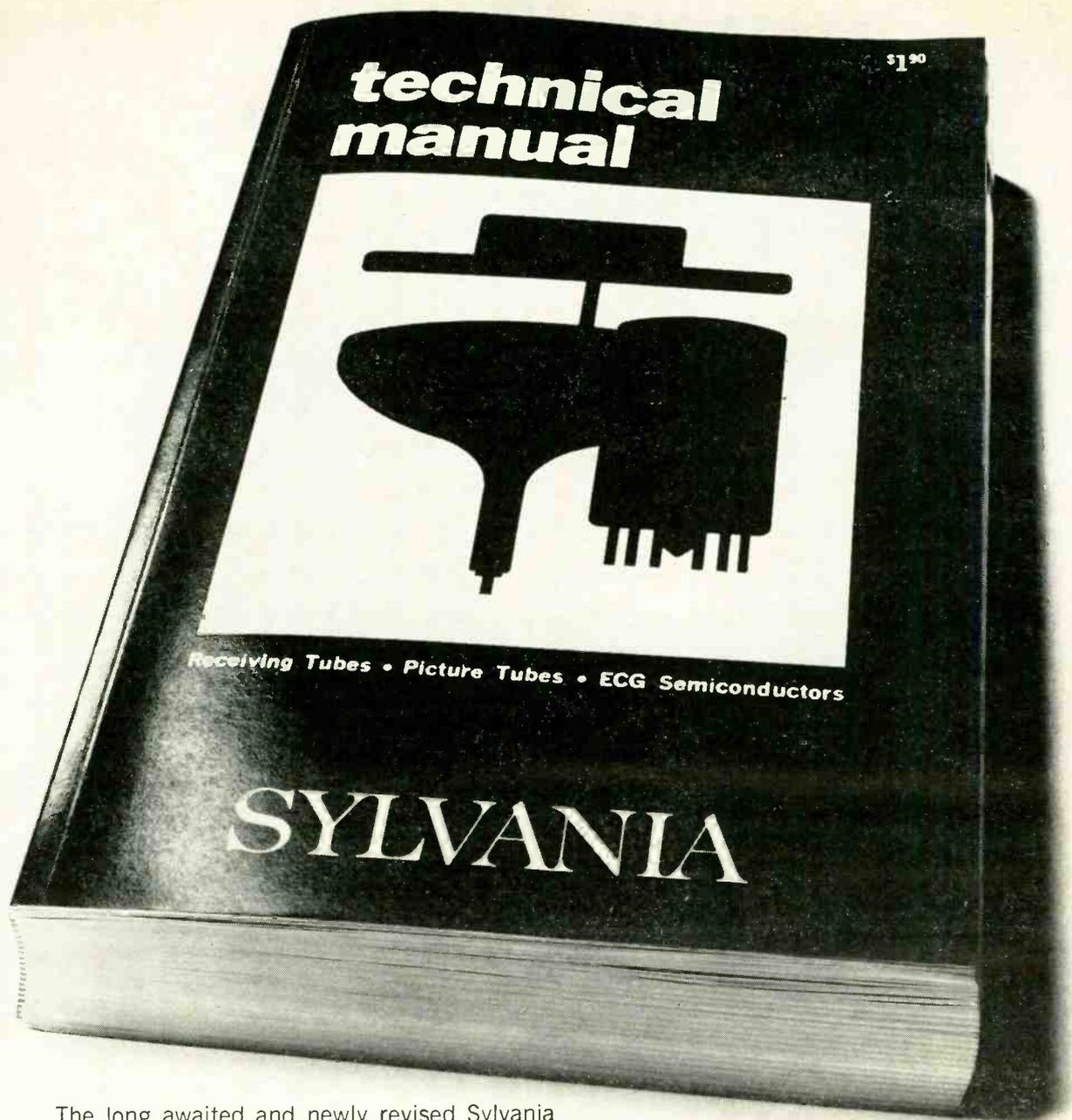Check here for G.I. Bill information RE-83



The long awaited and newly revised Sylvania Technical Manual is out. Complete and unexpurgated. The fantasy of every Independent Service Technician. Written anonymously by an agile team of Sylvania engineers. 32,000 components described in breathtaking detail. Including thousands of unretouched diagrams and illustrations. Discover the unspeakable thrill of new color TV Tubes, listed as never before. The ecstasy of 28,000 ECG Semiconductors.

From exotic Deflection Oscillators to a lurid account of Transistors and Rectifiers.

This book has what you want. Components for the man who knows what to do with them.

The 14th Edition of the Sylvania Technical Manual is not available in any bookstore. Your Sylvania Distributor is discreet. Speak to him.

# “Electrifying”

**SYLVANIA**  
GENERAL TELEPHONE & ELECTRONICS

You better get ready for it, and get ready to answer lots of questions; quad is coming and it's the hottest thing in home entertainment since the stereo record was invented.

It's still very new and doesn't even have a permanent name yet. People are calling it quadrasonic stereo, four-channel stereo, tetraphonic sound, surround sound and who-knows-what-else. All the names are descriptive, but most of them are too tongue-twisting to become a household word. We're betting on the simplest of all: "Quad" and the broadcasts will be "quadcasts." Quad is fairly simple in itself—it just adds two more audio channels to the at-

A mediocre amplifier and a couple of relatively inexpensive speakers will do the job.

But if this is all there is to quad, why not simply take existing two-channel stereo recordings, pipe some of the signal through a pair of inexpensive reverb units, and then through the second amplifier and speakers? Why not indeed? In fact, this technique will work very well for the vast majority of existing stereo recordings, and properly used, will prevent existing record and tape collections from becoming obsolete.

But true quad is much more than simple reverberation. In a recent Audio Engineering Society meeting devoted to quad, some spectacular demonstration tapes were played, amply demonstrating the dramatic ping-ping/pong-pong effect possible. Most spectacular of all was the motorcycle that ran in circles around the huge RCA recording studio where the meet-

audio techniques, quad is probably as much an advance over conventional stereo as stereo was over mono. That's a whopping conclusion to make, but quad in one giant step puts huge concert-hall acoustics in the living room. We've bemoaned for years the fact that we'd never be able to recreate concert hall acoustics in the home. Various speaker manufacturers have tried, with limited degrees of success. Now it's possible.

Comparisons to two-channel stereo come easily. Quad is now approximately where stereo was in 1956-57. There's good reproduction equipment available; you can use two stereo amplifiers or one of the limited runs

# New 4-channel stereo techniques

by WALTER G. SALM

4-channel stereo is here to stay. Here's the latest on what's happening in this new race for solid sound that surrounds the listener

ready-existing stereo pair. The first stereo pair continues as before, coming out of a pair of matched speakers at the front of the listening room. The two new channels are rear-of-the-room-speakers, facing forward.

In its classic form, quad adds two channels of room reverberation—the minute echoes, phase and time delays that are characteristic of the hall where the recording was made. This can be done by placing an additional pair of microphones somewhere behind the original stereo pair, recording two extra channels on the tape, and playing them back through a second stereo amplifier and the two rear speakers. Treated this way, the extra two channels don't have to be the same high-quality you have up front.

ing had assembled. That particular tape pointed up more than anything else the true effectiveness of surround sound.

There's no shortage of recorded material. Most record companies today keep their eight- (and 16-) channel master tapes in the vault, and these masters can be remixed into four-channel any time they're needed. Thus we will see lots of re-releases of well-known stereo recordings in quad. New masters are made with quad in mind, and many recordings of contemporary music can really make full use of this room-filling illusion. A few classical works—very few—were originally scored with orchestral elements in the rear of the concert hall. Quad lets the audiophile hear this music the way it was written, something he can't do with conventional stereo. Even so, such recordings sound hopelessly gimmicked up; after all, who ever heard trumpets blaring from the rear of the living room?

As an improvement in existing

of new four-channel amplifiers, and there are program sources, at least on tape. As was the case with stereo in 1956, tape is the only readily available source of quad program material right now. Like 1956, conversion heads for four-channel playback are expensive, as are add-on preamplifiers. Like 1956, there's talk about compatible, single-groove discs and compatible FM broadcasts. Disc multiplexing techniques are being proposed, and at least one inventor, Peter Scheiber, claims to have devised the "ultimate solution," although it's far from perfect (and turns out not to be true four-channel).

There are debates raging about quad's true effectiveness, and wouldn't reverb-fed rear speakers be cheaper,

just as effective and solve all these problems? And so it goes.

Here's what's happening now. Tape equipment is in the forefront, as it was in 1956. Companies now producing quad playback-capable equipment include: Crown International, Teac, H. H. Scott, 3M and Telex/Viking. Ampex has produced quad equipment for professional use, machines that will handle both 1/2-inch and 1/4-inch tape, but an Ampex consumer quad unit may not be far away. At the CES show in New York Ampex showed a four-channel cassette player. Kenrich Purchasing, an importer of Japanese cassette recorders, plans to market an inexpensive quad conversion kit for cassette surround sound.

#### 4-track in a cartridge

Possibly the easiest single format to work with for home entertainment use is the 8-track, continuous-loop cartridge. This cartridge has sufficient tape width to accommodate two four-channel programs with interleaved tracks, making playback heads easier and cheaper to build. Bearing this out have been twin announcements by Motorola and RCA. Motorola said it had a four-channel stereo 8-track tape player for the car and would be introducing it later this year. No mention was made of where the tapes were to come from.

At virtually the same time, RCA unveiled a living-room quad system also based on the 8-track cartridge. This one was more realistic, since RCA can make its own quad tape cartridges very easily and demonstrated some new ones in the prototype demonstration.

The basic unit looks little different from any living-room version of a cartridge player. It has two speakers built into its cabinet, but also has two outboard speakers at the rear of the listening room. And there in lies the difference. The same unit can be used with four outboard speakers, as is another unit that has no built-in speakers.

The cartridge machine is compatible with conventional 2-channel stereo tapes. All it takes is a flip of a front-panel switch to go from quad to old-fashioned stereo. The track arrangement is 1-3-5-7 for sequence A with 1 as left front, 3 left rear, 5 right



**TYPICAL 4-CHANNEL STEREO AMPLIFIER.** This one is the H. H. Scott model 499. Several other manufacturers have announced similar gear.

front and 7 right rear. At the end of sequence A, the head shifts down and plays tracks 2-4-6-8. Program time is halved by the quad format so a double-length tape becomes instead standard album-length. Presumably the tapes will be priced somewhat higher than standard 2-channel cartridges and because of the use of four tracks, will have half the playing time. Tapes should be available now.






One of the few amplifiers on the scene so far is the Scott "Quadrant"—a 35-watt-per-channel unit with an impressive number of front-panel controls and a staggering price tag of

\$600.00. Interestingly, the unit has two different stereo headphone jacks—one for the front speaker pair and one for the rear speaker pair. The front-pair jack is used when listening to conventional 2-channel stereo. Eventually, such amplifiers will no doubt have a single headphone jack with choices of various blends for both two-channel monitoring and the most suitable mix for casual listening, and the owner will make his choice.

The broadcast situation is far from clear. Even as we go to press, there's every chance that the FCC will grant that all-important experimental broadcast approval. In the meantime, the only quadcasts that have been legally possible have been via two stereo FM stations paired up with rented telephone lines. The listener needs two complete stereo receiver setups to listen to these limited quadcasts. Sound familiar? Other systems are available, but won't be heard by the public until the FCC issues the necessary experimental license.


Latest word on the status of single-station broadcast is that no one can seem to make up their minds as to what is desirable and not. It's generally conceded that if a station's going to broadcast quad, then its SCA channel must go. SCA is that special service channel with a 67-kHz subcarrier that carries background music or other special programs to paying customers. SCA has in fact become the focal point of disputes between proponents of different kinds of quad transmission systems, and often the feuders have other, SCA-bred axes of their own to grind.

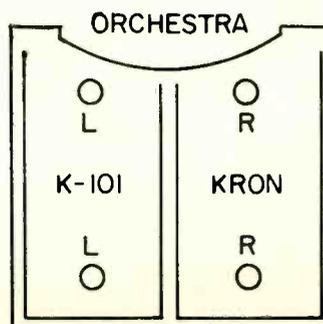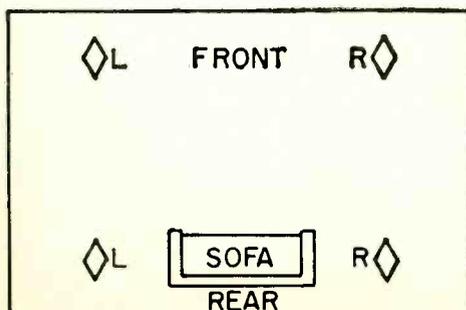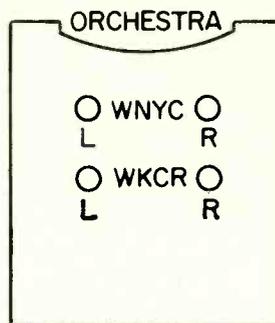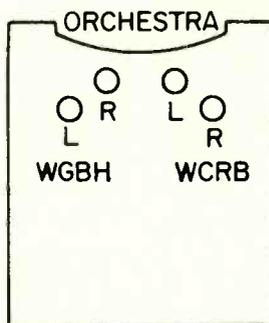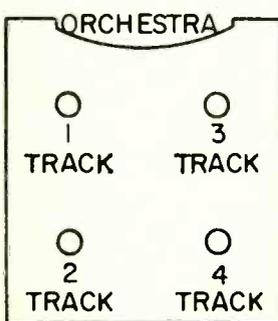A basic system suggested by William Halstead ("Mr. Multiplex")



**RECORDING, BROADCAST AND PLAYBACK techniques are shown on the left as they are now being used.**

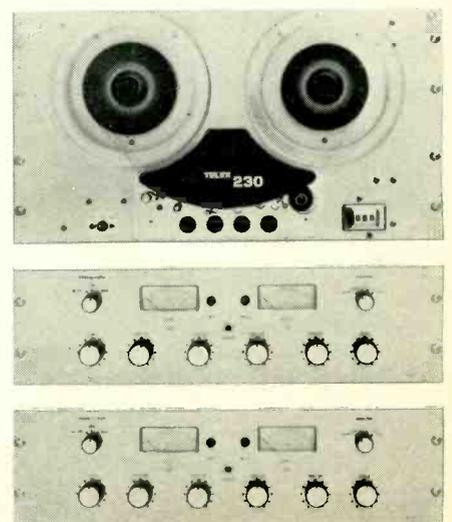**FOUR-CHANNEL TAPE, reel-to-reel is the Telex Quad/Sonic Model 230 below. QQ transport is for playback only; QQR handles both recording and playback.**



working with Leonard Feldman, uses two 8-kHz-wide subchannels for the two rear speakers, with subcarrier frequencies at 69 and 89 kHz. This technique has a certain amount of overlap with the allotted SCA channel (59 to 75 kHz), so the SCA capability is automatically eliminated in stations that quadcast. One serious problem here is the fact that any quad decoder for such a system would also be capable of picking up SCA channels, because of this overlap between SCA and the lower of the two quad subchannels.

To avoid any outcries of "SCA piracy," Feldman has installed a tiny reed relay in the quad decoder circuit that automatically mutes the detector's output when a 67-kHz subcarrier is received. This idea easily wins the Rube Goldberg medal and does nothing to stop the tinkerer who wants to bridge across the relay to get SCA.

Another technique, formally proposed to the FCC by McMartin Industries and later withdrawn, uses a form of time-division multiplexing (TDM). This technique intermixes the two signals at a 19-kHz rate. Channel bandwidth is held to 8-kHz per channel and in the playback, sampling is locked to the 19-kHz stereo pilot signal. This signal envelope embraces good old 67-kHz as a center frequency (suppressed) and is amplitude-modulated to prevent any eavesdroppers from illicitly picking up SCA broadcasts which happen to be McMartin's bread and butter. Main problem with the TDM technique is phase distortion. Add just one tiny bit of phase delay because of propagation conditions and the signal separation

goes to pieces.

Actually, there's little reason not to adapt the Halstead/Feldman system by converting both channels to AM with suppressed carriers—the same transmission method used for the FM stereo subchannel. This way, quad decoders wouldn't pick up SCA, reed-relays notwithstanding, and broadcast modulation level could be held at reasonable proportions.

Some people, both in the FCC and out, are understandably nervous about the proposed additional use of the FM band. Anything above the assigned 150-kHz bandwidth is dangerous, they believe, and might cause co-channel interference. Not so. The actual bandwidth in use would never go above 150-kHz, simply because bandwidth use is a function modulation percentage. In the present setup, a station broadcasting mono FM can use 100% modulation which effectively eats up that full 150-kHz. If the station broadcasts FM stereo, it reduces its main-channel modulation to 80%, uses 10% for the 19-kHz pilot and 10% for the L - R stereo information on the subchannel. If the station carries SCA, it reduces the main channel another 10%. This brings us down to 70% main-channel modulation.

If two quad channels were to be added, they would each probably require 10% modulation. Since SCA can't be carried during a quadcast, there's 10% available right there. Chop off another 10% from the main carrier—leaving 60% and we have our quadcast setup. What would this do to signal-to-noise ratio? Not much. Each 10% reduction in main-channel modulation

results in a loss of about 1.5 dB of S/N ratio—a cheap price to pay for so much extra sound. Thus a quadcasting station would have about 1.5 dB poorer S/N ratio on its main channel than would a stereo station carrying SCA.



### What will happen?


What actually happens will probably follow the pattern set in 1956-1961. Someone will propose a definite system that will be fully compatible with conventional stereo and mono reception. A limited number of decoders will be produced and sold at a premium price to experimenters who will use them to listen to perhaps one or two hours a week of test quadcasts. Other systems will be proposed, in increasing numbers. The closer the FCC comes to making a decision, the more companies will get into the act—each one with a quad transmission system of its own. Ultimately, the system selected as the industry standard will not be one of those that had had experimental quadcast experience, but will be one of convenience, and possibly one that will still permit SCA transmission!

But perhaps the Commission will recognize the fact that SCA is no longer a matter of life and death for many FM stations the way it was 10 years ago. FM stations are making it on their own now, and many are making it in the big leagues.

The FM-FM quadcasts that have taken place so far raise another interesting question: what is the optimum microphone placement for quad recording and broadcasts? In three  
*(continued on page 86)*

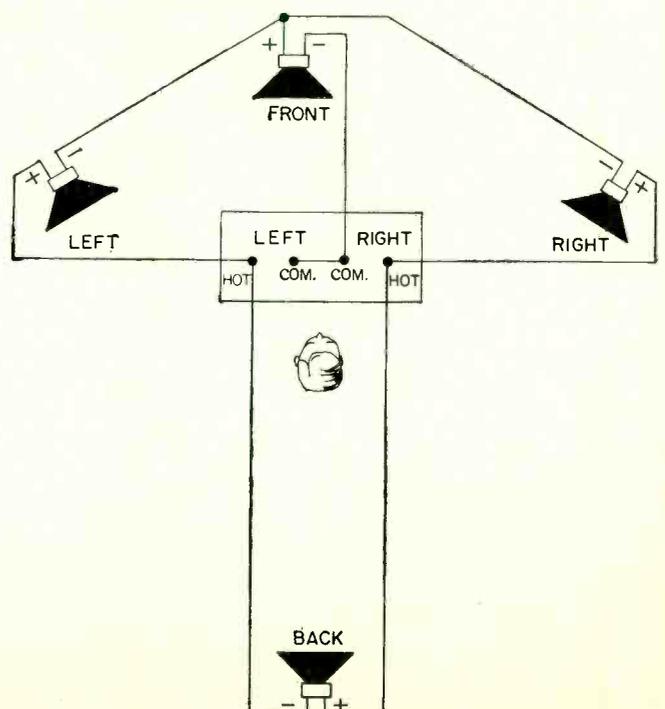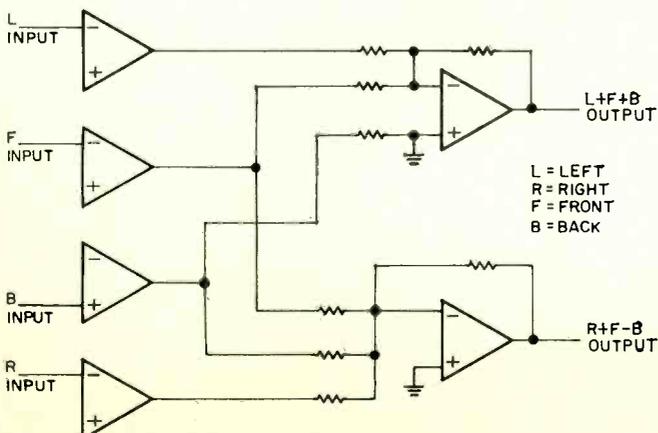**SYSTEM USED BY DYNACO to add front (F) and back (B) information to left and right channels. SPEAKER ARRANGEMENT for turning existing 2-channel system into pseudo 4-channel. All you must add are two additional speakers and a special matrix network (shown below). When using this arrangement adjust the amplifier balance control for minimum sound in the back speaker when monophonic material is being played.**



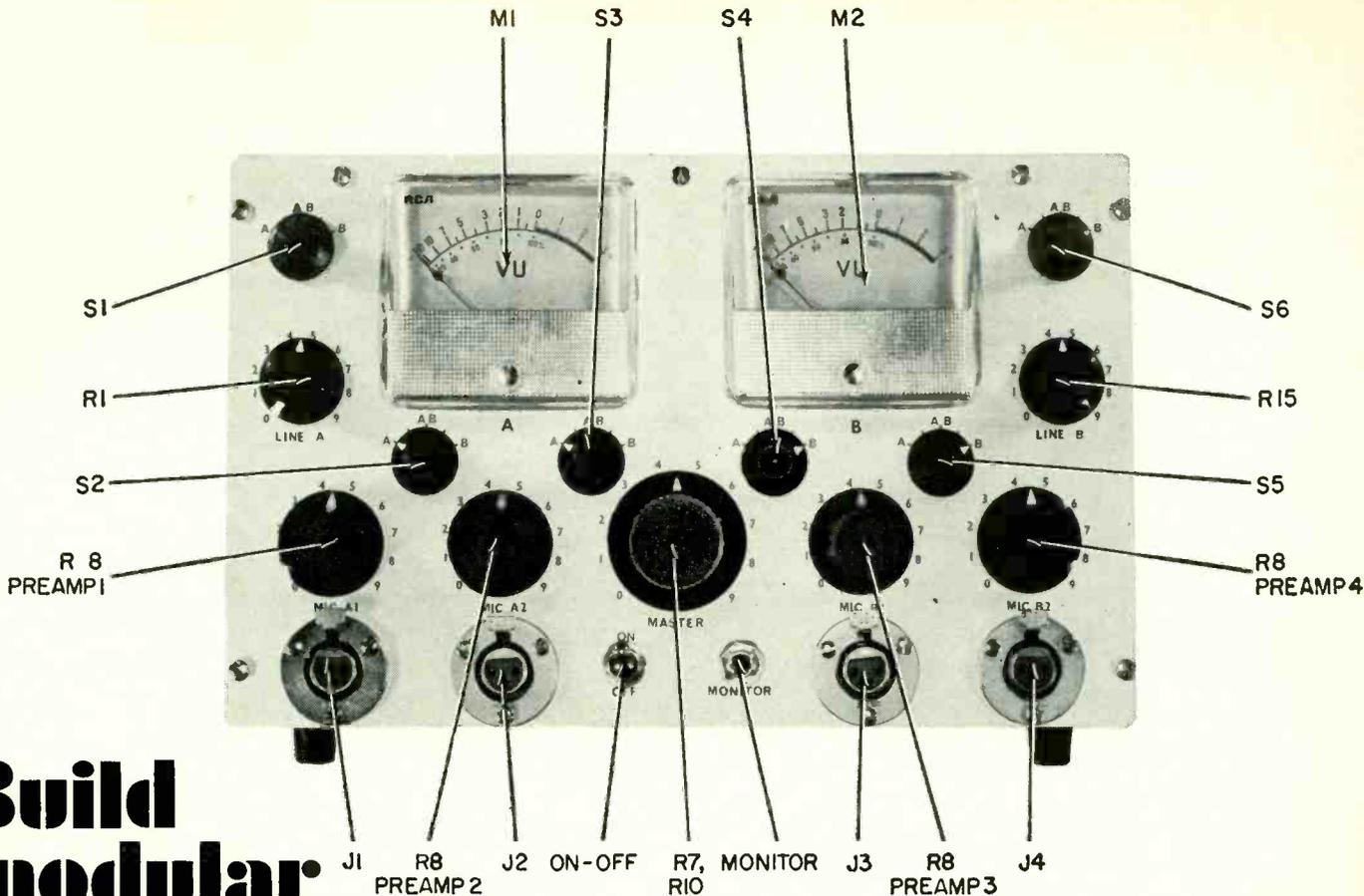

# Build modular 6-channel stereo mixer preamp


by GEORGE D. HANCHETT, Senior Engineer, RCA Solid State Div.

THIS STEREO PREAMPLIFIER AND mixer is particularly interesting to those who want to make high-quality tape recordings. The preamp has four microphone and two line inputs that can be switched to left, right, or both channels. In addition, two auxiliary inputs are provided, one for each channel. The auxiliary inputs cannot be switched. All inputs that can be switched are controlled from the front panel. The two auxiliary inputs are controlled from the rear of the unit. Each output channel has its own VU meter.

The stereo preamplifier and mixer is made up of three basic circuits and a minimum of inter-connecting wiring. The three circuits are a high-dynamic-range microphone
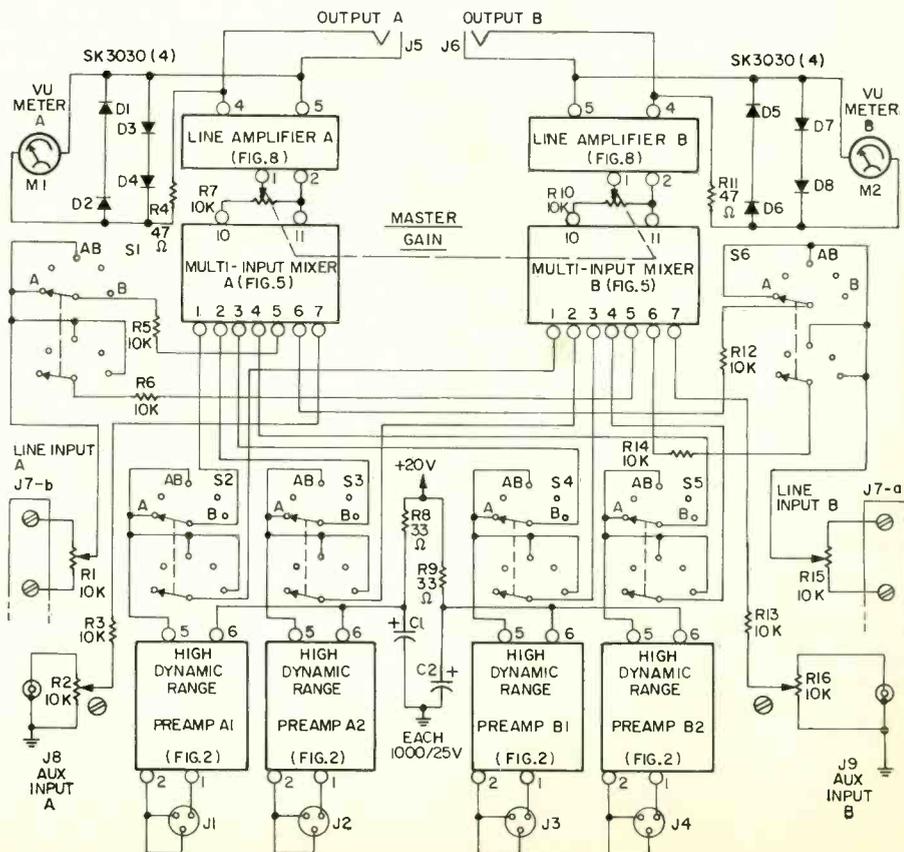
### PARTS LIST (Fig. 1)

- C1, C2—1000  $\mu$ F, 25 volts, electrolytic
- D1 through D8—SK3030 (RCA)
- M1, M2—VU meter
- R1, R2, R7, R10, R15, R16—potentiometer, 10,000 ohms (R7, R10 is a dual linear pot)
- R3, R5, R6, R12, R13, R14—10,000 ohms,  $\frac{1}{2}$  watt, 10%
- R4, R11—47 ohms,  $\frac{1}{2}$  watt, 10%
- R8, R9—33 ohms,  $\frac{1}{2}$  watt, 10%
- S1 through S6—rotary switch, 2 poles, 5 positions, shorting type
- J1, J2, J3, J4—microphone jacks
- J5, J6—phone jack
- J7—4-lug terminal strip (screw terminals)
- J8, J9—phono jack



preamp, a multi-input mixer, and a headphone or line amplifier. A block diagram of the total unit is in Fig. 1.

The output of each microphone preamp (see Fig. 1) is fed to a switch which can connect it to channel A, the left channel, channel B, the right channel, or both channels (A and B) simultaneously. The output of these switches as well as the line input for each channel is fed into the multi-input mixers. A master gain control combines or gangs the outputs from the mixers installed in each channel and passes the combined signal to the line amplifiers. The diode limiting circuit used with each VU meter keeps the meter from being damaged during the charging of the large coupling capacitors in the line-amplifier. Two R-C power-supply filters consisting of R8 and C1, and R9 and C2 assure circuit stability. Each filter services two microphone preamplifiers.

The stereo preamplifier and mixer is made up of a number of circuits as described above. The description of each of the three circuits includes circuit boards and component placement diagrams. The individual circuit boards and the interconnecting wiring required for the stereo preamp

### CIRCUIT BOARDS

A complete set of 8 circuit boards needed to build this unit are available for \$10. Order 1070B-1. A set of 4 boards for building a mono version are \$6. Order 1070B-2. Boards are G-10 glass-epoxy, undrilled. Photo negative for making your own boards containing all board patterns is \$1.50. Order from Photolum Corp., 118 E. 28 St., New York, N. Y.

and mixer may be assembled as desired by the builder to form the kind of custom unit he needs.

The high-dynamic-range microphone preamplifier, intended to be used with low-impedance dynamic microphones, will handle loud passages of music and close talking without adverse effect on the output. The amplifier has a gain of 1500 to 2000 and can provide a maximum undistorted output voltage of 2 volts rms to a load impedance of 500 ohms or more. The maximum undistorted input is 400 mV rms. The frequency response is flat from 20 Hz to 30 kHz.

The circuit for the high-dynamic-range microphone preamp are in Fig. 2. The preamplifier consists of two stages of current-stabilized amplifiers separated by a gain control and an R-C filter, consisting of R7 and

C5, that prevents motorboating. Resistors R5 and R12, placed in the emitter circuits of transistors Q1 and Q2, improve the frequency response of the preamplifier by providing some emitter degeneration. The output of the preamplifier is shunted with resistor, R15, to make the circuit compatible with the zero-point switching capability used in the master preamp. The output impedance of the preamp is low. The table shows the value of R1 to use with microphones of various impedances.


The printed-circuit-board layout for the microphone preamp is in Fig. 3. A photograph of a completed board showing parts placement is in Fig. 4. All ground connections in this circuit must be made to the same point, as shown in Fig. 3, to avoid forming ground loops. This common-ground feature is built into the printed-circuit

TABLE I

Microphone Impedance	R1 (ohms)
200	220
500	560
4,000	R1 not used

R1 connected across microphone input jack.
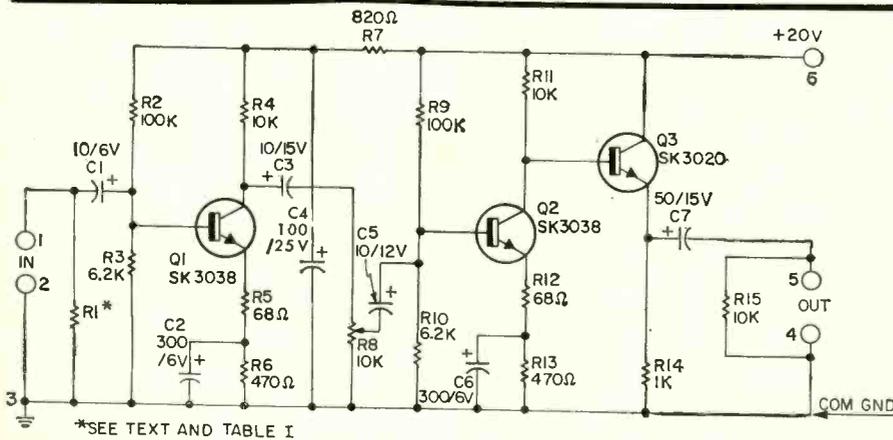
## Modular construction lets you build a custom mixer-preamp that meets your needs precisely, or duplicate the unit described here



### PARTS LIST (Fig. 2)

- C1, C5—10  $\mu$ F, 6 volts, electrolytic
- C2, C6—300  $\mu$ F, 6 volts, electrolytic
- C3—10  $\mu$ F, 15 volts, electrolytic
- C4—100  $\mu$ F, 25 volts, electrolytic
- C7—50  $\mu$ F, 15 volts, electrolytic
- Q1, Q2—SK3038 (RCA)
- Q3—SK3020 (RCA)
- All Resistors  $\frac{1}{2}$ -watt 10%
- R1—see table I and text
- R2, R9—100,000 ohms
- R3, R10—6200 ohms
- R4, R11, R15—10,000 ohms
- R5, R12—68 ohms
- R6, R13—470 ohms
- R7—820 ohms
- R8—potentiometer, 10,000 ohms, audio taper
- R14—1000 ohms


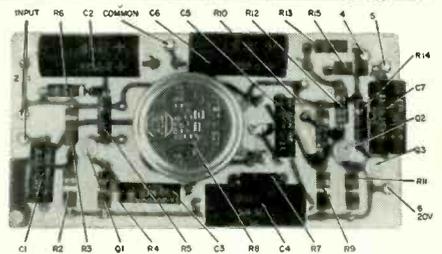


FIG. 1—(FACING PAGE) BLOCK DIAGRAM of complete mixer preamp. FIG. 2—(LEFT) MICROPHONE PREAMP schematic. Three transistors are used. FIG. 3—(BELOW) CIRCUIT BOARD PATTERN for the mike preamp. FIG. 4—(ABOVE) PHOTO OF ASSEMBLED BOARD showing parts placement details.

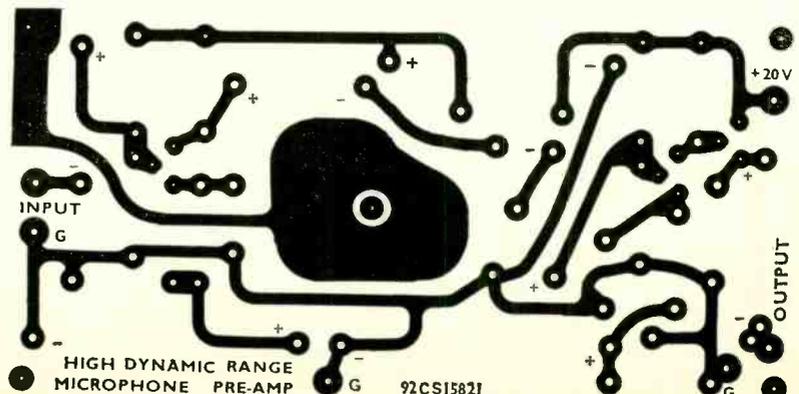

board and must be followed if some method of circuit construction other than the printed board is used. In addition, all preamplifier connections to external circuits should be made to the same ground point.

**Multi-input mixer**

The multi-input mixer is designed to mix the inputs from up to seven sources, usually microphones, for input to an amplifier, recorder, or other piece of audio equipment. The mixer has a gain of approximately unity and, therefore, has no effect on the system in which it is installed. If more than seven inputs are required, as many as three mixers can be wired in parallel.

**How it works**

The circuit for the multi-input audio mixer is in Fig. 5. The resistance network shown at the left not only provides the mixing function but also to make possible zero-point switching of the inputs.

In the zero-point switching, as used in this unit, the capacitors at the output of the microphone preamps as well as the input capacitor of the mixer are kept charged. This is done

by connecting a resistor across the output and input. Thus there is no disturbance, no cracks or pops, when inputs are switched in or out. The amplifier portion of the circuit, shown at the right in the schematic, is current stabilized by the emitter resistor. This resistor is not bypassed, and provide a greater degree of degeneration and reducing the overall gain of the mixer to unity.

Some adjustment of resistor values is required if less than seven inputs are used. Table II shows these re-

**TABLE II  
RESISTANCE VALUES**

No. of inputs	R17	R18
2	8.2k	120 ohms
3	7.5k	110 ohms
4	6.8k	91 ohms
5	6.8k	82 ohms
6	6.2k	75 ohms
7	6.2k	68 ohms

sistor values for from 2 to 7 inputs. When three or more mixers are paralleled to accommodate more than seven inputs, not only must the outputs of the mixers be paralleled but the ground

points on each circuit board must be connected. The gain of the mixer thus connected is somewhat less than unity.

Component placement and circuit board pattern for the multi-input mixer are in Figs 6 and 7 along with a photograph of a completed board.


**Headphone or line amplifier**

The headphone or line amplifier is very useful when the power amplifier is located some distance from the microphone. If preceded by a microphone preamp, the amplifier makes a very useful remote pickup. It is also very useful for driving the line inputs of tape recorders.


The headphone or line amplifier has a voltage gain of 100 and can drive any line impedance of 250 ohms or more. It has a maximum undistorted output of 3 volts rms into a 500-ohm line and has a frequency response flat from 20 Hz to more than 25,000 Hz. The input impedance is 1,800 ohms.

**Amplifier operation**


The circuit for the headphone or line amplifier is in Fig. 8. The interconnection of the transistors in the

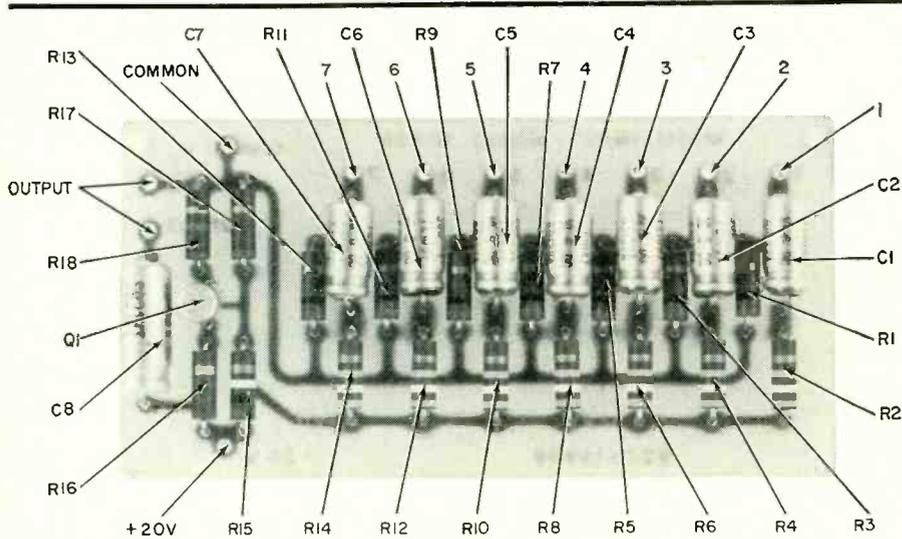

**FIG. 5—(BELOW) CIRCUIT** of multi-input audio mixer. Two are needed to build the unit described in this article. **FIG. 6—(RIGHT) CIRCUIT BOARD PATTERN** for the audio mixer. **FIG. 7—(ABOVE) PHOTO OF MIXER** shows parts placement on the circuit board. Refer to Fig. 1 for interconnection details of the complete preamp.

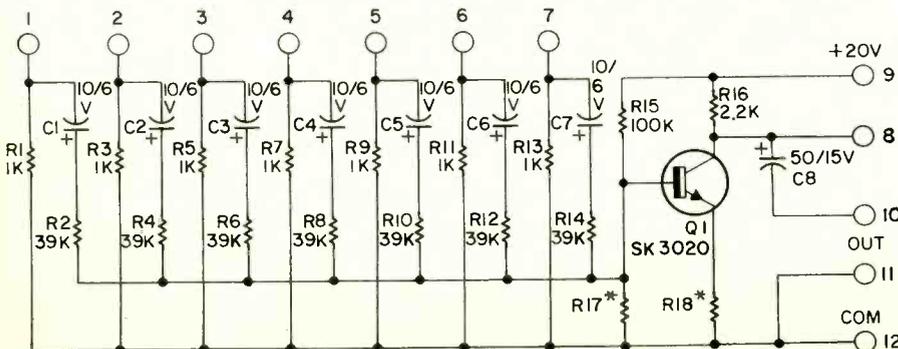


\*SEE TEXT AND TABLE II

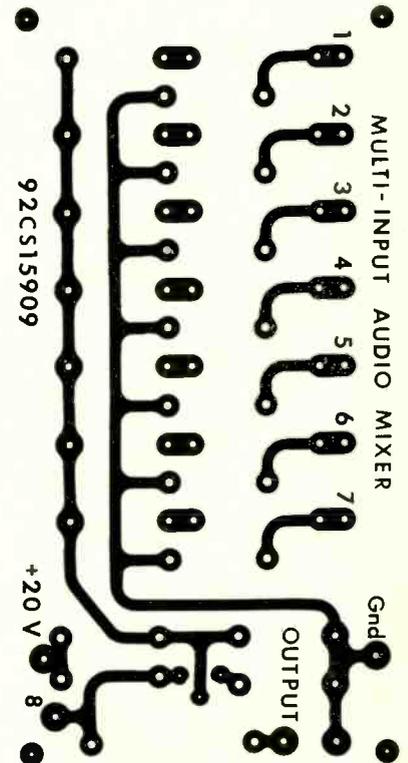



**PARTS LIST  
(Fig. 5)**

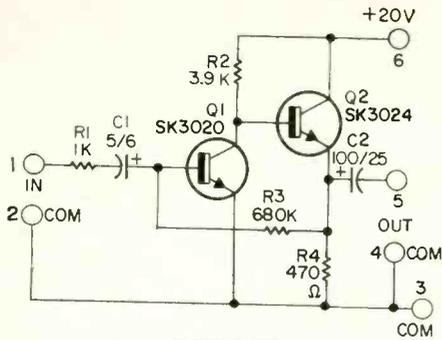- C1 through C7—10  $\mu$ F, 6 volts, electrolytic
- C8—50  $\mu$ F, 15 volts, electrolytic
- Q1—SK3020 (RCA)
- R1, R3, R5, R7, R9, R11, R13—1000 ohms, 1/2 watt, 10%
- R2, R4, R6, R8, R10, R12, R14—39,000 ohms, 1/2 watt, 10%
- R15—100,000 ohms, 1/2 watt, 10%
- R16—2200 ohms, 1/2 watt, 10%
- R17, R18—see table II and text




**PARTS LIST**  
(Fig. 8)


- C1—5  $\mu$ F, 6 volts, electrolytic
- C2—100  $\mu$ F, 25 volts, electrolytic
- Q1—SK3020 (RCA)
- Q2—SK3024 (RCA)
- R1—1000 ohms, 1/2 watt, 10%
- R2—3900 ohms, 1/2 watt, 10%
- R3—680,000 ohms, 1/2 watt, 10%
- R4—470 ohms 1/2 watt, 10%

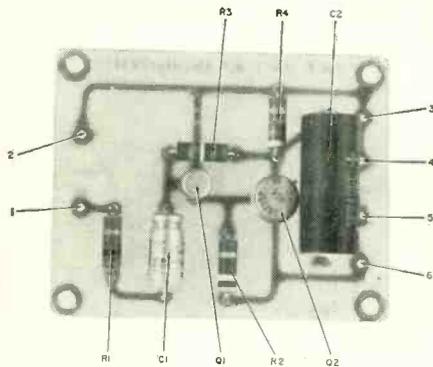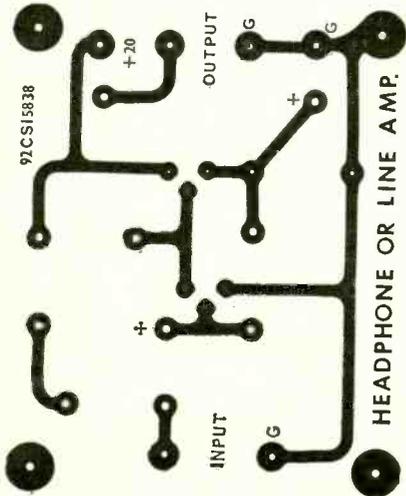


**FIG. 8—(TOP) LINE AMPLIFIER** circuit uses two transistors. **FIG. 9—(CENTER ABOVE) CIRCUIT BOARD** pattern for the line amplifier is shown actual size. **FIG. 10 (ABOVE) COMPLETED BOARD** showing parts placement. See Fig. 1 for circuit board interconnections.

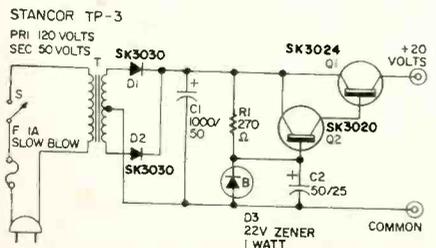

**FIG. 11—POWER SUPPLY** is regulated circuit. It is built right on the main chassis of the mixer reamp as you can see in the photo at the right.

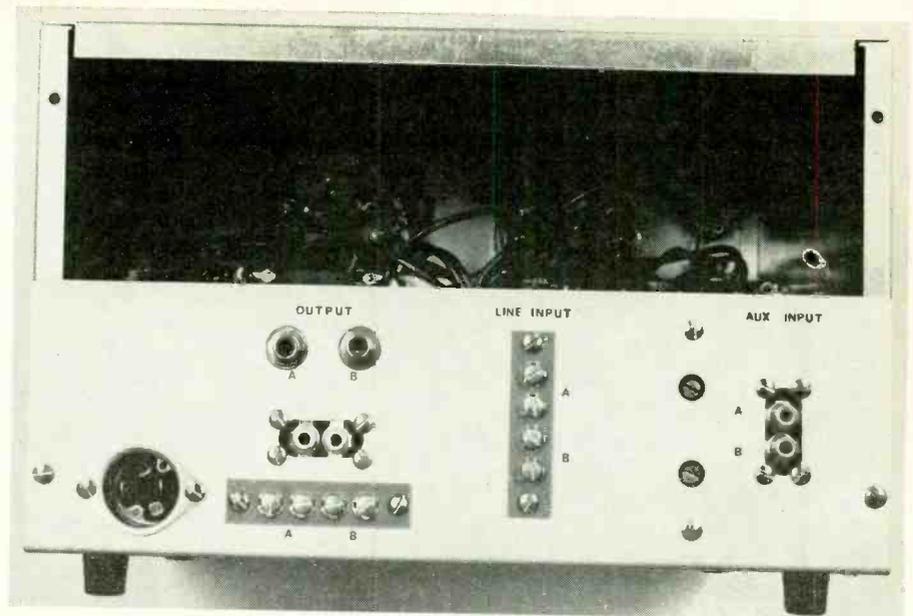

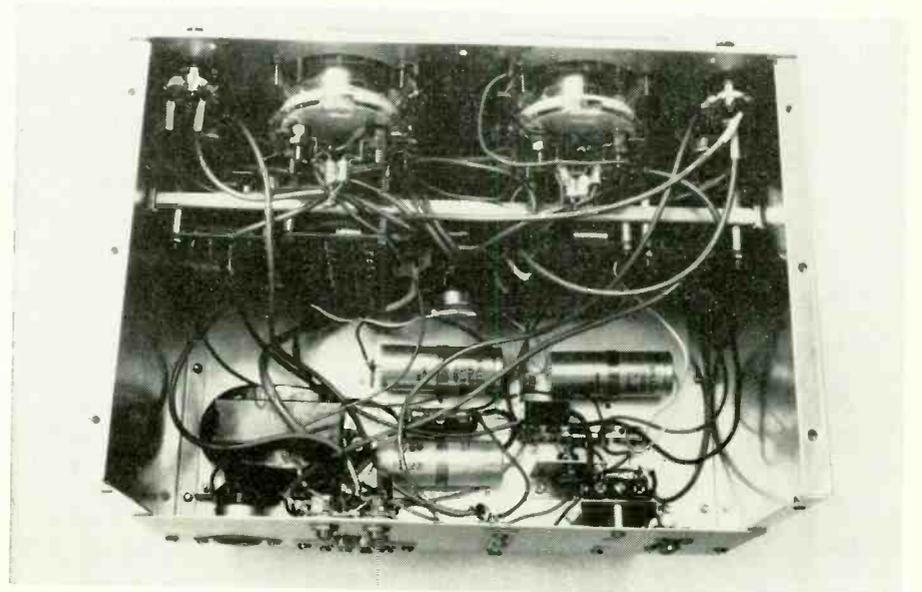**FROM THE REAR OF THE MIXER-PREAMP** you can see the auxiliary input and line input jacks. Three sets of outputs were connected in parallel to provide connectors for all likely applications.



**LOOKING IN FROM THE TOP** you can see the power-supply components in the lower right of the photo. The two VU meters are at the top. Most of the jumble of wiring consists of leads connecting outputs to the circuit boards.

amplifier makes the operating condition of the amplifier self-adjusting, (i.e.; the amplifier can maintain itself in a stable operating state in spite of variations in power-supply voltage and ambient temperature. Stability is insured by feedback through R3. If Q1's emitter current should increase, the base voltage of Q2 would decrease because of the additional voltage drop in R3. However, the decreased base voltage of Q2 results in a drop in Q2's emitter current, a reduction of feedback voltage to Q1, and hence a decrease in Q1's collector current. This decreased collector current causes an increase in Q2's base voltage that compensates for the original decrease and the amplifier is stabilized. The interconnection of transistors just described also makes possible the low

output impedance of the amplifier.

The printed circuit board pattern for this circuit, and a photo of a completed board, are in Figs. 9 and 10.




### Power supply is last

A simple power supply completes the unit. This supply is shown in Fig. 11. It is assembled directly on the chassis of the unit and is not built onto a circuit board. Once you have completed the power supply, selected the desired number of input, mixer and output boards you can proceed to assemble your custom mixer-preamp. We are sure you will enjoy it.

This article is presented through the courtesy of the RCA Solid-State Hobby Circuits Manual, HM-91, \$1.95, which will be published early this fall.

**R-E**

# Get better from your

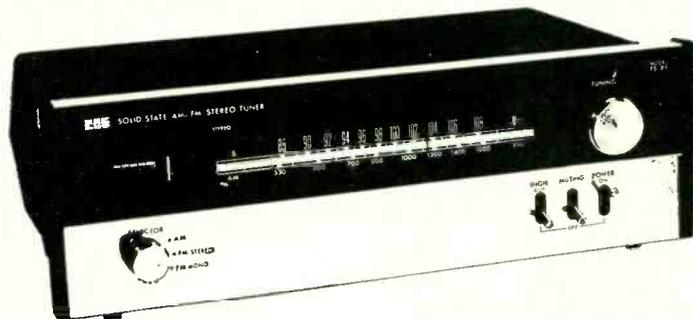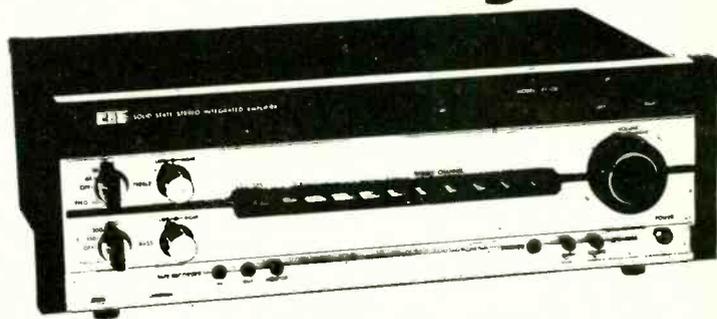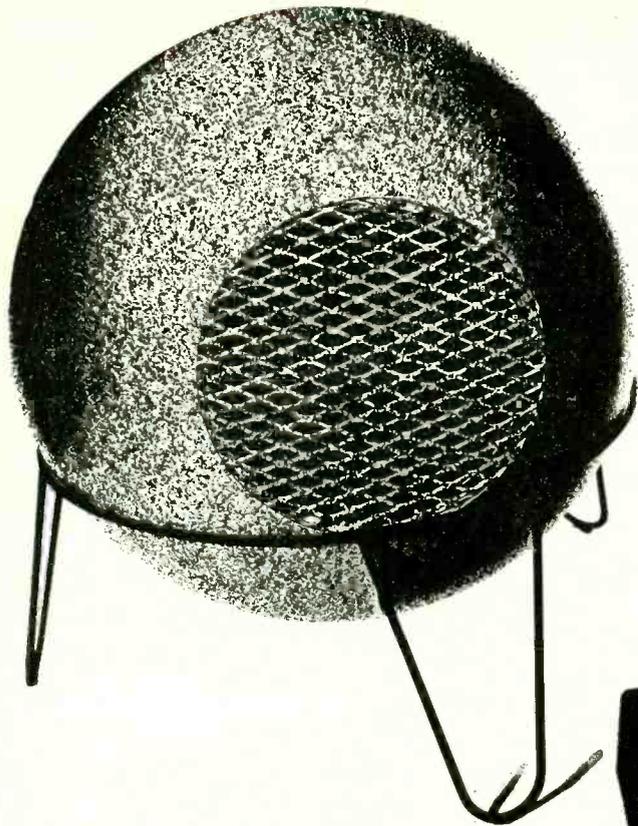

*A do-it-yourself guide to maintenance and simple adjustments to get the best from your stereo rig.*

by **PETER SUTHEIM**

This article is one of a series intended as a sort of supplement to the operating booklet that comes with hi-fi components. The manuals are often pretty short on information that doesn't have to do directly with turning the unit off or on, using the controls, and such basics. Since most customers for hi-fi components are not at all technically inclined, the makers feel it's pointless to take up space describing maintenance and the more subtle adjustments. But for those who enjoy getting a feel for the equipment they use, the warning, "no user-serviceable parts inside" does not need to apply.

One caution before we begin, though. Nothing in this article is in-

tended to contradict anything in the instruction manuals. We may suggest occasional lubrication, for example; but if your booklet says very explicitly *not* to oil this or that, then don't oil it. They know more about what they've made than you do, or than we do.

This month we discuss tuners and amplifiers. Later we will cover such components as speakers, record players and tape recorders.

### **Keeping the amplifier fit**

Well-designed transistor amplifiers tend to deteriorate a lot less with age than tube amplifiers do, partly because of the inherently long life of transistors when they are not abused, and partly because of lower voltages and lower temperatures in solid-state equipment. There is usually not as much preventive maintenance to do in solid-state gear.

It is important, though, especially in dusty or smoggy regions, to clean air vents, grilles and heat sinks. Heat held in by restricted air flow can cause premature failure of transistors and other parts, especially in marginally designed equipment. Use a whisk-broom, brush, rag, or vacuum cleaner.

Noisy or intermittent switches and controls can sometimes be fixed

by cleaning the contacts. Seldom-used switches and controls are the most likely to cause trouble. Often just twisting the switch or control rapidly from one stop to the other several times is enough. Sometimes you will have to use a switch and control cleaner, or some ethyl chloride, to help dissolve dirt. Inspection of a switch will sometimes turn up the cause for intermittent operation—bent or corroded contacts, dirt, a bad solder connection.



A fairly common cause for noisy volume and tone controls in transistor amplifiers is dc leakage through the control. The tendency to use relatively low-resistance controls in solid-state amplifiers (10,000 ohms, for example) requires coupling capacitors of 5 or 10  $\mu$ F, typically. In all but the most expensive equipment, these are electrolytics, which tend to leak more than other types of capacitor. Leakage also tends to increase with age and temperature. The only answer is to replace the offending capacitors. If you can afford to, use tantalum capacitors, which have far less leakage current for a given capacitance.

Many early solid-state amplifiers and preamps had objectionably noisy phono preamp stages. It is sometimes




**Harman-Kardon's Citation 12 120-watt. The latest in stereo power amplifiers.**

# sound STEREO

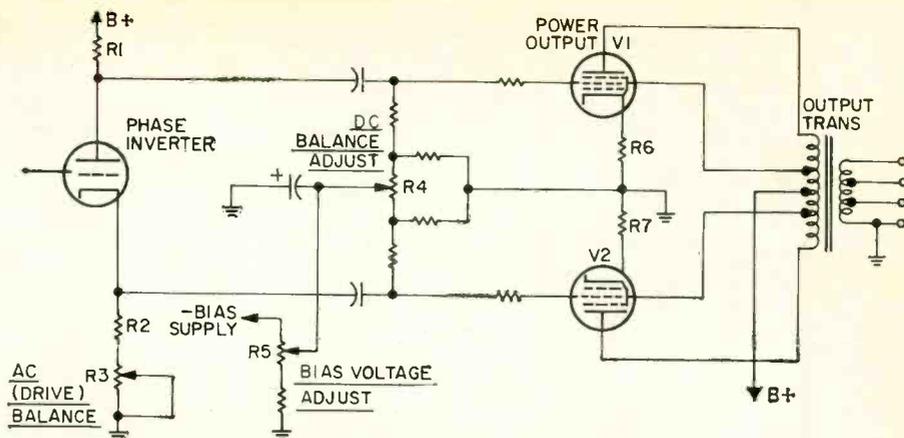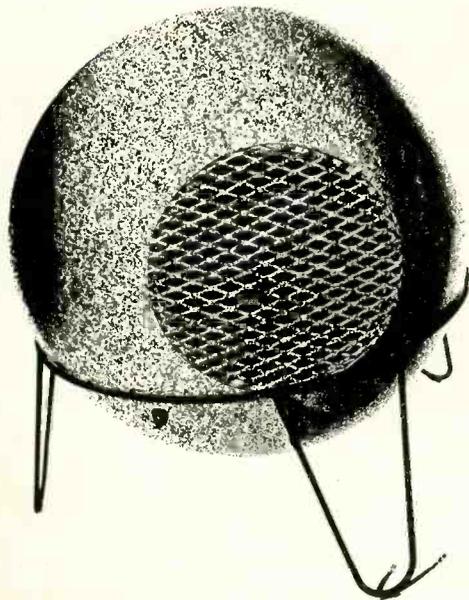

**Fig. 1—ADJUSTMENTS IN HI-FI AMPLIFIER.** Not all amplifiers have all these adjustments. Usually, R2 plus R3 equals R1. Pot R3 sets equal drive to tubes V1 and V2. R5 sets the dc bias level, while R4 sets equal cathode currents through R6-R7.

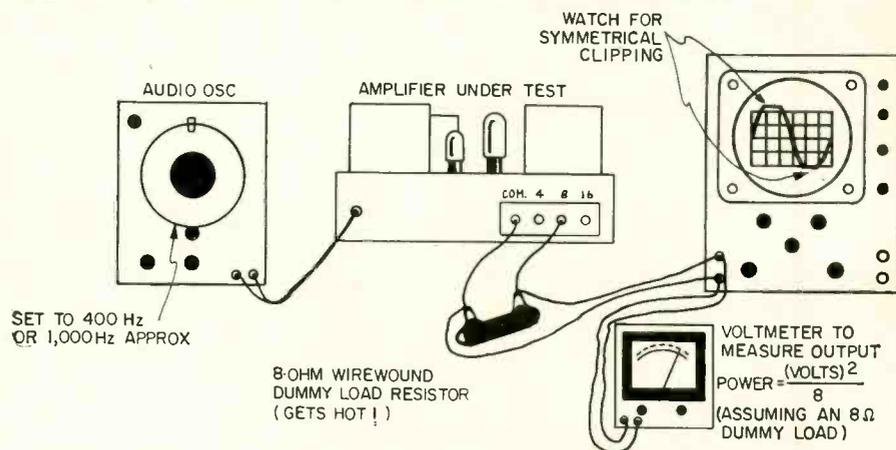

**Fig. 2—POWER AND OUTPUT BALANCE CHECK.** Asymmetrical clipping not correctable by balance adjustments is probably developed in earlier stage. To measure power output, adjust the 400- or 1000-Hz input signal to just below point where clipping is seen on scope. Square the voltage reading and divide it by the value of the load resistor.

possible to improve them with newer transistors. The General Electric or Sprague 2N3391-A is a good, low-noise, low-cost silicon planar npn transistor now being used by many manufacturers; it can replace other silicon npn types probably without any changes in circuitry. An even better transistor is the Fairchild SE4010, though it may be harder to come by. Both cost well under \$1.00.

Several designs used the RCA 2N2613, a pnp germanium transistor especially recommended for low noise. Performance was sometimes disappointing; buying a handful of 2613's and finding the one with the lowest noise may bring significant improvement. A possible replacement is a silicon pnp transistor by Fairchild, the 2N4250 (or its brother and sister, the 2N4248 and 2N4249). Depending on the circuit, this may require some changes in first-stage bias-resistor values. Its gain is very high even at collector currents around  $10\mu\text{A}$ , where noise is extremely low. The 2N4248-50 series also cost well under \$1.00.

Sometimes replacing first-stage emitter, base and collector resistors with some of better quality helps. Any resistor with dc flowing through it is a

potential source of extra noise. Ohmite, IRC or Allen-Bradley composition resistors are likely to be better than unknown or "bargain" resistors. It is impossible to tell by looking at a resistor how noisy it is, so pulling out resistors and replacing them with new ones is a gamble. But it may be worth the effort if you are annoyed by hiss.

If yours is a tube amplifier, much of what has been said about cleaning applies to it also. If the tubes are more than about 3 years old, replace them. Use matched pairs in output stages unless your amplifier provides dc balance adjustments. Run through the balance and bias adjustment (Fig. 1) in any case; follow the manufacturer's instructions. The idea is to get the two push-pull output tubes in each channel to draw equal current through the output transformer primary winding. Since the currents drawn by each tube flow in opposite directions, the magnetic fluxes they generate in the transformer core cancel each other. This reduces distortion and extends the bass power capability.

Several tube amplifiers provide metering terminals or some other way of adjusting output-stage current. Another good way to check is to set the

amplifier up for a power measurement (as in Fig. 2—400- or 1,000-Hz tone to the input, 8-ohm resistor and scope across the output), and adjust the tone level and the output-stage balance until the clipping of the output waveform is symmetrical. Still a third way is to connect a harmonic distortion meter to the amplifier output and adjust the bias and balance controls for minimum distortion at a power output near the rated maximum.

A few amplifiers have adjustments for balancing the signal drive to the two sides of the push-pull output stage (Fig. 1 again). These too should be checked after the tubes are replaced, and checked again after the first hundred hours' use. The symmetrical-clipping test can be used here, but the best way is to adjust for lowest harmonic or intermodulation distortion.

If an amplifier does not meet its power or distortion specifications (at rated line voltage) after you have replaced its tubes, perhaps some resistors have drifted off their original values, paper capacitors have become leaky, or electrolytics have become inefficient. If you can, check supply voltages against the schematic. They

should be within 10% of their specified values. If they seem low, and you know your line voltage is normal, replace the electrolytic filter and decoupling capacitors. This should also help cure hum or instability that may have developed over the years.

But don't be too hard on an old amplifier. First of all, remember that a 10% drop in power (as from an original rating of 20 watts down to 18) is only 1/2 dB, and completely inaudible. A loss of even half the power (3 dB) may not be noticeable in many situations. Secondly, many amplifiers were (and are) sold on the basis of exaggerated or "best of the run" figures. If this is the first time you've made measurements on your old amplifier, you may be discovering that it never did perform as well as you were led to believe.

The noise level of the pre-amplifier stages can vary enormously with the tube used. Not all 12AX7's are the same. By general consensus in the industry, the quietest are the ones made by Telefunken in Germany; several manufacturers imported them for inclusion in original equipment, often stamping them with their own brand names. Such premium tubes may be available as replacements if you write to the manufacturer. Good bets also are the ECC83 tubes (European type number corresponding to the American 12AX7) made by Mullard (British) and Amperex (Dutch). The American premium versions of the 12AX7 never quite came up to the standard set by the European types, although the G-E or RCA 7025 may be worth trying. If you have the money and the patience, buy several and find the ones that have the lowest hiss, hum and "flicker noise". If your amplifier uses 12AX7's in tone-control or other later stages as well, you can safely use the noisier tubes there, where the signal level is higher and less susceptible to tube noise.


## Tuners

For tuners with vacuum tubes, replace all the tubes if they are more than about 3 years old. In all tuners except the Marantz 10B, which uses i.f. filters instead of tuned transformers, it would be wise to follow tube replacement with an alignment job. FM alignment, especially in a stereo multiplex tuner, is much more critical than AM alignment, and the safest procedure is to follow the manufacturer's service instructions.

In general, though, you can check i.f. alignment easily enough by tuning in a weak station, or by weakly coupling a signal generator to the i.f. strip. Assume, if you use a generator, that the i.f. strip is basically tuned to

the correct frequency (that is, 10.7 MHz). It is probably more accurate than your generator, so connect a vtvm (switched to a relatively low dc range) between the last limiter grid and ground, and introduce a weak signal from the generator. Then tune the generator until the meter peaks (or until the tuner's own signal-strength meter peaks). Don't worry if the generator's dial reads something other than 10.7 MHz. This way you'll avoid the risk of unnecessarily realigning the whole i.f. strip to a new frequency, with possibly very evil effects on the tuner's performance. It is important to use a weak signal for peaking the alignment of an FM i.f. strip. Strong signals will cause limiter stages to saturate, and when they do, their tuning characteristic will be very broad and the peak hard to find. You can also use a weak FM broadcast station for the same purpose.

Aligning the detector in a high-quality tuner is more difficult, and best done with a sweep generator and a scope, with the help of the manufacturer's service manual. It is best to leave the ratio detector or discriminator alone unless you have reason to believe that it's seriously out of whack (if, for example, there is audible distortion on almost all FM stations, or if you've diddled with the alignment already). Fig. 3 shows a

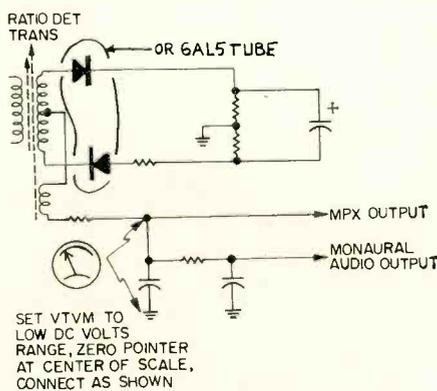

**Fig. 3—TOUCHING-UP FM DETECTOR.** With input from FM generator or station, adjust secondary slug for zero output.

quick "field expedient" method for at least "centering" the detector with a signal generator or FM station as the signal source, and a vtvm.

If the dial calibration is off, check to see whether it's off by a linear amount (a certain fraction of an inch) all the way across the dial. If so, the error is probably due to dialcord slippage, or some other kind of mechanical slippage. Slipping dial cords can often be restored just by cleaning them with a greaseless solvent, like isopropyl alcohol or ethyl chloride. Or perhaps the pointer has simply slipped slightly. Even if it

hasn't, you can sometimes restore dial calibration reasonably well by sliding the pointer to the correct spot on the dial when the tuner is centered on a station whose frequency you know. (Remember that FM broadcast station frequencies are far more accurate than service-type signal-generator calibrations.)


If the calibration seems to be precise at one end of the dial or in the middle, but off by an increasing amount elsewhere, the error is almost certainly due to a drift of value of some component in the oscillator tank circuit. It is often possible to restore accurate calibration by juggling *very slightly* the adjustment of the oscillator coil and the oscillator trimmer, but this can be tricky and time-consuming. Under no circumstances make any gross adjustments unless you know exactly what you are doing and why you are doing it, otherwise you may have a full-scale alignment job on your hands. If the error is not serious it is sometimes better to play it chicken and live with it, or to move the dial pointer slightly to "split the difference" in the calibration error.

If you choose to replace the dial cord altogether, be sure to make an accurate sketch of how it is installed before you remove the old cord, else you may have several hours' intensely frustrating work ahead.

Unless you have had experience, leave the multiplex section alone. Any kind of alignment work on a multiplex decoder requires at least an accurate source of 19-kHz and 38-kHz signal. The procedure is too long to go into here. Numerous books and articles dealing with the adjustment of stereo multiplex decoders have been published.

Many complaints of poor FM reception are due not to the tuner but the antenna and lead-in. An outdoor antenna should be inspected at least once a year, especially in industrial areas where corrosive pollution runs high, or in seacoast locations. The polyethylene insulation of twin-lead deteriorates with exposure to sun and air pollutants, and its electrical loss increases. Connections between the lead-in and the antenna or lightning arrester can corrode and break. Insulating blocks on the antenna itself can become coated with conductive salts, greatly decreasing the effectiveness of the antenna.

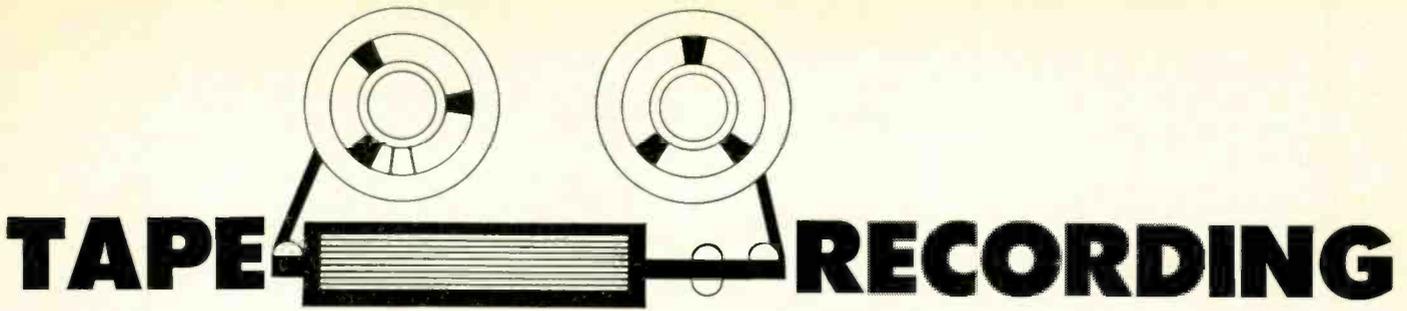Other things change with time, too; a new tall building may have altered reception conditions in your home, and that could be responsible for worsened quality on some stereo stations. A change of antenna location, or a different antenna, may be needed to solve the problem. **R-E**



# TAPE RECORDING

## how to buy audio tape

*There's more to magnetic tape than the box it's packed in.  
Here's the story on what goes into those white boxes.*

by **BYRON G. WELS**

YOU'VE BOUGHT YOUR FIRST TAPE RECORDER, and now you want to buy tape, so you can put it to use. You're faced with a fantastic assortment of brands, types, lengths, thicknesses and prices. Chances are, if you're like most people, you will try a bit of this and a bit of that, until finally you learn what you like and what you don't like. However, although this process works, it is horribly expensive. You can often get stung by the cost until you learn, and more costly, you might even entrust a valuable recording session to a shoddy tape and wind up losing money and recording.

In this article, we will outline what to look for and what to look out for in tape, so if you do spot a bargain and go for it, you'll at least know what you're getting and won't be surprised.

### Prerecorded tapes

The newcomer (and many old hands) at tape recording look upon a tape machine more as a means to play music than to record it, and this is fine. These people invest in "albums" of prerecorded tapes, collecting the music they like.

But you've got to be on your guard. Today, most tape albums are sealed in plastic wrap, and you can't open the package to look at what you're getting, let alone listen to the tape before you buy! The best rule here is to know what you are buying beforehand. You can do this by listening to your better FM music stations, those that announce the name of the tape producer and the number of the tape either before or after

playing. This gives you the chance to listen and judge in advance. Another good rule is to stick to the names you know, both in producers and performers.

Because artists' fees are high, some of the smaller music producing companies will go abroad and hastily organize a "pickup" symphony orchestra to play into a recorder. This master tape is then brought back home for processing, duplicating and sale. Such tapes can be spotted by the fact that the box will rarely mention the performing orchestra, featuring the title of the work for a big play instead! Somewhere on the box, if you can find it, the orchestra will be identified. But if you spot a name like the "Lower Slobovia Penultimate Symphonette," watch your step.

Another thing to watch for are certain key words. "Suite" and "Excerpts" both imply abbreviated versions of a work. Unfortunately, we often accept such words as part of the actual title. However, "Swan Lake Ballet Suite" means a shortened version of the full ballet. The word "Suite" is French for *fast*. Another trick word is "Overture" or in French, if you want to add class to your record or tape box, "Ouvreture." This is really just an introduction, not an entire opera.

Finally, take a look at what you've bought when you get home. Maybe you bought a box that's a full 7 inches across, and maybe it contains a reel 7 inches in diameter, but you might find a huge plastic hub at the center, up to 4 or 5 inches across. The result? A heck of a lot less music than you expected!

If you can get stung with re-

corded tapes, the problem is even worse for blank tape. Let's take a look at what's generally available.

First, you've got to choose your base material. This is the plastic on which the oxide recording medium is applied. You have a choice of acetate or Mylar, in varying thicknesses. The acetate is more prone to breakage and embrittlement, unless you go for the thicker base. Of course, using a thicker base means that they can't put quite as much tape on each reel!

The Mylar is far longer-lasting and in the thin 1/2-mil and thinner 1/4-mil varieties you get a lot more on each reel. Of course, you pay more, and if you set the record level too high you may get print through. That is, the recorded information on the tape is transferred to the next layer, with all kinds of echo effects that were never recorded in the first place!

More critical is the oxide itself. How well has it been designed, how well has it been milled, and how good a binder has been used in making it adhere to the base? These are all critical factors. Why? If the oxide hasn't been properly milled, it will be lumpy, and each lump will make the tape rise from the head, causing dropouts in your recording. If the binder isn't good, the oxide will shed, again leaving blank spots in your tape. It can also speed head wear.

Chances are that if you buy a name brand, you'll get good quality. Your choice really depends to a great extent on what you plan to use the tape for. But you also ought to select your tape to fit the application in light of what that application is. If you anticipate recording level problems, use a high-output tape. If

you're going to be recording long sessions with no opportunity to clean the heads, use sandwich tape, in which the oxide is sandwiched between two layers of plastic, the top layer being very thin. No oxide touches the heads, so there's no need to clean.

### White-box tape

As Barnum said, "There's one born every minute." White-box is tape that is usually sold in a plain white box, with no manufacturer's name or reputation to back it up.

It's usually sold at a comparatively low price, and usually there are more than enough customers ready to shell out their money for this stuff. What white-box tape is, however, is a story in itself.

Usually it's computer tape that was 1 or 2 inches wide and reslitted to the required 1/4 inch. Unfortunately, computer tape is required only to register the fact that it has been magnetized or not magnetized. The fidelity of this stuff is often not suited to audio work. Sometimes, white-box is reslitted video tape, which has a better frequency response but can bring other problems. The safest rule is to stay away from this stuff.

Another good source for the white-box packages is mill ends or rejects. When a tape manufacturer starts or finishes a run of tape he must adjust his coaters. Until they are set properly, quality will suffer. However, he can and does sell these mill

ends or rejects to the white-box people. Fortunately, many tape manufacturers have begun to realize that they are actually doing themselves a disservice by this practice, and simply throw away the subgrade material.


### Testing tape

The proof of the tape pudding is usually in the playing, but there are tests that you can use to find out how good (or bad) a reel of tape is.

One good test is to take a look at the new reel of tape, holding it up to an even, strong light. The layers of tape on the reel should be smooth and even, with no sign of buckling. If you see a slight "hump" in the tape, unwind it to that point to see whether you've got a buckling overwind or a splice.

Next, unwind about 4 or 5 feet of the tape in a room where the air is quite still, and let it hang from the reel. If the tape does not hang evenly, with no "pulling" to either side, this indicates that the tape slitters were dull and that the tape has "warped" as a result. Such tape may jump the idlers during a session.

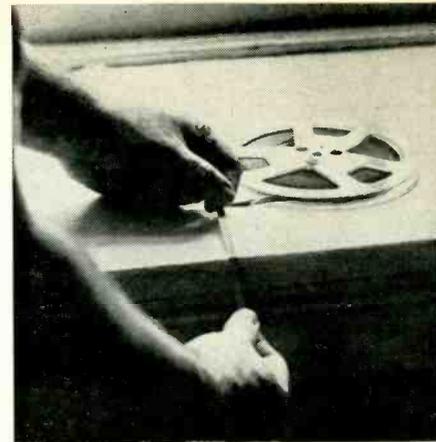Next, draw the tape tightly over a straight edge, such as a table edge. Look carefully for any sign that the oxide has flaked off. As a final test of shedding, place the tape on a flat surface, oxide side up. Press a piece of pressure-sensitive tape over the oxide, and pull it away quickly. Examine the



**IF OXIDE FLAKES OFF** when you run it over a table edge, it could be a bad buy. tape carefully under a good light to see if any oxide pulled off.

Tape recording is a wonderful hobby, but it can be marred by a poor purchase. Know what you're going to buy, and then go to the store and buy it. Remember, you're buying tape—not fancy four-color packages, not low prices—just good, high-quality recording tape.

And watch out for glib, smooth-talking salesmen, too. They do not always have your best interests at heart! Some stores give the salesmen what are called "P.M.'s" or Push-Merchandise bonuses. If they sell products so listed, it's more money in their pockets, so don't be fooled.

More than anything, else, remember to *Caveat* the heck out of Emptor!

**R-E**

## MODULAR TV SETS (A rundown of the new sets)

MOTOROLA	Panel	Circuits	ZENITH	Panel	Circuits
(TS-915-'19) Quasar Solid State Color	AFC B D E F G H L M S	AFC discriminator & amplifiers Video IF amps., AGC amp., video det., video det amp., 4.5 MHz det. Audio demods. & output amps. Noise inv., AGC gate, sync sep., vert. sync inv. & oscillator, 1st video amp., 2nd video amp., brightness stabilizer Color gate pulse former, horz. osc., horz. output Vert. pincusion amp., H. reg. amp. & driver Vert. limiter & Vert out., vert. and horz. convergence assy. RGB demodulators, RGB video driver, blanker amp., blanker out., brightness controls RGB video out. amplifiers & drive adjust. ACC amp., color killer amp., color IFs, color oscillator output & drivers	(Solid State) 22AB55 Monochrome	150-20 (IF Assy.) 150-204 (Sound Mod.) 9-22 (Video-sound Mod.) 9-23 (Sync-AGC Mod.) 9-24 (Vert. Mod.) 9-25 (Horz. Mod.)	Three IFs, video det., & driver Sound IC demodulator, amplifier Video out, sound driver, sound output AGC gate, AGC out, AGC delay, noise gate driver, noise gate, sync limiter Vert. osc., vert. driver, vert. output AFC, horz. osc., horz. driver
MOTOROLA (Hybrid) CTV5, CTV6 Quasar 2 Color	BA FA HA KA SA ZA	Video IFs, video amp., audio IC, audio out. Sync. sep., vert. osc./out., H. phase det., horz. osc., horz. driver Convergence assembly AFC discriminator & output Color sync & osc, col. killer, ACC amp., 2nd video amp., sync & AGC takeoff, color IFs, RGB demodulators, volt. rg., RGB video outputs Transistor supply regulator (+20 volts) with foldback current limiting	HEATHKIT (Solid State) GR-270, GR-370 Color	IF Assy. Luminance Board Sound Board Video Out Board AGC/Syn Board Chroma Board Osc. Circuit Board AFT Circuit Board Convergence Board Vert. Osc. Board Horz. Osc. Board Horz. Out Board	Three IFs & video detector, driver Lum. Amps., blanker, brightns lim. & control, dot generator IC amp.-discriminator, driver, audio out. IC demodulator, lum. amp., RGB outputs AGC inv., gate & gated amp., AGC amp., RF AGC, noise inv., sync gate, sync. sep. ACC amp., color killer, 1st & 2nd color amps., band pass amp. Burst amp., ACC, APC phase diodes, IC 3.58 MHz oscillator, CW amp. IC amp., discriminator, RLC circuits for dynamic convergence Vert. switch, vert. predriver, linearity clamp, vert. driver Phase splitter, AFC diodes, horz. osc. SCR HV drivers, HV regulator
ZENITH (Hybrid) 4B25C17,19 Color	Panel 9-23 (AGC Module) 9-27 (Sub-Gen. Module Assy.) 9-37 (Chroma Mod.) 150-166 (IF Assy.)	AGC gate, AGC delay, AGC output, noise gate driver, noise gate, sync limiter IC subcarrier oscillator, APC, ACC, output amp. IC chroma amp. & IC demodulator Three IFs, Audio Det., Video Det., 1st video amp.	RCA (KCS 184, 177,176) Solid State Monochrome	Panel Pix Module Video Module Sound Module	Dynamic convergence assy. 2nd color amplifier & IC demodulator IF amps, video detector, video drivers, AGC circuits Video out, sync, AGC keyer IC sound det., amp., audio output
ZENITH (Hybrid) 12B14C52 Color	Panel S-85579 (Conv. Assy) 9-47 (Color Module)	Dynamic convergence assy. 2nd color amplifier & IC demodulator			

Focus stages—four major versions in color chassis



NEW R-E EXCLUSIVE

# Kwik-Fix™ picture and waveform charts

by Forest H. Belt & Associates\*

SCREEN SYMPTOMS AS GUIDES

WHERE TO CHECK FIRST

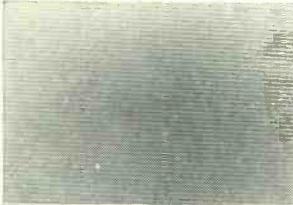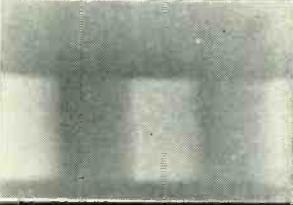SYMPTOM PIC	DESCRIPTION	VOLTAGE	WAVEFORM	PART
	For reference: Raster lines in focus (closeup)	Normal	Normal	Normal
	Raster out of focus and shaded (closeup)	Focus anode of CRT	No help	Bleeder resistor
	No raster	Focus anode of CRT	No help	Focus rectifier
	Raster out of focus (with picture)	Focus anode of CRT	No help	100k resistor (diagram B)
	No raster	Focus anode and no tube current	No help	Focus transformer

\*an Easy Read™ feature by FOREST H. BELT & Associates © 1970

**NOTES:**

Screen symptoms are only of marginal help in tracking down trouble in focus stages.

Study the screen as you turn the FOCUS control. Only helpful clues are at the points indicated.

Check focus voltage or horizontal-output cathode current as indicated.

For quick check, test or substitute parts shown as most likely cause of the screen symptom you see.

**THE STAGES**

All color picture tubes except recent small-screen types require a high dc focus voltage. Its value must be at all times from 18-20 percent of whatever value of high voltage is applied. If the high voltage varies, the focus voltage must vary with it. Otherwise, there will be poor focus at high and low brightness. In practice, that means focus voltage must vary from about 4200 to 5500 volts dc.

Color picture tubes use electrostatic focus. This makes a "dry" circuit; that is, there's NO normal current flow to or from the focus electrode in the CRT. The only electron flow in the entire focus stage is a very tiny current where there's a bleeder resistor. That's normally a very large value—66 megs or more.

Focus voltage is developed by rectifying a high-energy

pulse taken from the plate of the horizontal output tube. Its value is usually about 5000 volts peak to peak (p-p). The pulse is fed to the focus rectifier anode, usually directly from the horizontal output plate. Only in an occasional chassis is there a small bit of flyback winding between horizontal output plate and focus rectifier.

The stage in diagram A has the control potentiometer across part of the flyback winding. The pot slider picks off enough of the pulse to develop the correct value of dc at the output of the 1V2 focus rectifier. This version is seldom used anymore.

Diagram B is popular in middle-age color sets. Sometimes a solid-state rectifier is used in place of the tube. The distinctive part is the focus transformer, which has a movable core in part of the windings. The rectifier anode is

### DC VOLTAGES AS GUIDES

Voltage change	to zero	very low	low	slightly low	slightly high	high
Diagram A V1 cathode Normal— 20% of HV	R1 open V1 open					
Diagram A focus anode lead Normal— 20% of HV	R1 open R2 open V1 open	R1 leaky* V1 socket bad	R1 faulty* R2 arcing* CRT socket (pin 9)	R2 v. high	R3 open	
Diagram B V1 or X1 cathode Normal— 20% of HV	V1 open X1 open V1 socket bad T2 shorted	C1 shorted X1 shorted T2 shorted	T2 open R1 open CRT socket (pin 9)	R3 open R2 high C1 open		
Diagram B focus anode lead Normal— 20% of HV	R2 open			R2 v. high		
Diagram B H-O Tube cathode current Normal— 200–240 mA						C1 shorted T2 shorted X1 shorted
Diagram C focus anode lead Normal— 20% of HV	R1 open	R1 faulty		R2 faulty*	R1 open R2 faulty* R3 open	
Diagram D focus anode lead	R1 open R2 open		R1 v. high		R2 open R3 open	

**NOTES**

\*erratic voltage usually depicts internal arcing.  
 Use this guide to help you pinpoint the faulty part.  
 Measure each key voltage with vtvm and high-voltage probe.  
 Measure key current with current function of vom.  
 For each, move across to the column that best describes the  
 change you find.  
 Notice which parts the chart says might cause that change.

Finally, notice which parts are repeated in whatever combination of voltage changes you find.  
 Test those parts individually for the fault described.  
 NOTE: Use the chart rows for the diagram closest like the focus stage you're servicing.  
 NOTE: All these voltage guides assume the high voltage is within 1000 volts of normal.

driven from the horizontal output plate, as in other focus stages. The focus-transformer windings are fed out-of-phase with each other, and at a different phase than the voltage pulses at the rectifier anode. The adjustable core determines how much and what phase of pulse is fed to the rectifier *cathode* through the 130-pF capacitor. The net dc at the cathode depends on the relative values and phases of pulses applied to the rectifier. The core adjustment therefore in effect controls dc focus voltage.

Some early models—and a few small-screen recent ones—use a focus stage like diagram C. A specially built divider resistor develops focus dc directly from the high-voltage source. That takes care of tracking very simply; focus voltage is automatically a fixed percentage of the high voltage at all times. A high-value potentiometer at the ground end of the bleeder provides manual adjustment.

In diagram D, a voltage sextupler, of the half-wave variety, builds an input pulse voltage into the 25 kV dc needed for the color picture tube second anode. A tap in the voltage multiplier picks off about 30 percent of the total voltage value for focus. Divider resistors and a pot set the exact value of dc sent to the CRT focus anode. This version is found in recent-model solid-state color receivers.

### SIGNAL BEHAVIOR

There is only one "signal" or waveform in any of these focus stages. That's the high-energy pulse from the horizontal output tube plate. It is above 5 kV p-p, far beyond the rating of almost any scope or probe. You seldom need to know its voltage, anyway.

If you want to view the pulse waveform, clip the scope probe tip *to the insulation* of one of the leads. The lead from the plate cap of the horizontal output tube is fine, if

the connection is direct. **DO NOT LET THE PROBE TIP TOUCH** the terminals or windings of the focus-transformer or fly-back. If a focus transformer is used, the pulse taken at one of its leads (see Waveform Guide) varies considerably in shape and size as the core is adjusted.

### DC DISTRIBUTION

Actual dc voltage in a focus stage may be different from that given on the schematic for the chassis. So much depends on the particular CRT. But the difference won't be great. A lot also depends on the value of the high voltage. That, in turn, depends on the settings of the screen and drive controls, brightness, and in some sets the contrast.

Dc focus voltage is usually fed to pin 9 of the picture tube. There may be a series resistor, or none. Since no current flows, the value doesn't affect dc voltage. The resistor is mainly a filter to smooth out any pulse "hash" that gets past the rectifier.


To stabilize the load on the focus rectifier and pulse-supply circuits, there is often a bleeder. Changes in its value, or in the values of any resistors in series with it, can alter focus voltage seriously.

### SIGNAL AND CONTROL EFFECTS


Controls are of three main types. One is the potentiometer version shown in diagram A. This kind has almost disappeared. It was dangerous because so much hot rf from the flyback was present. The control didn't last long, either.

More popular is a different kind of potentiometer hookup, shown in diagrams C and D. A pot in a resistive divider network has a comparatively small dc voltage—only a few thousand volts, and dc at that.

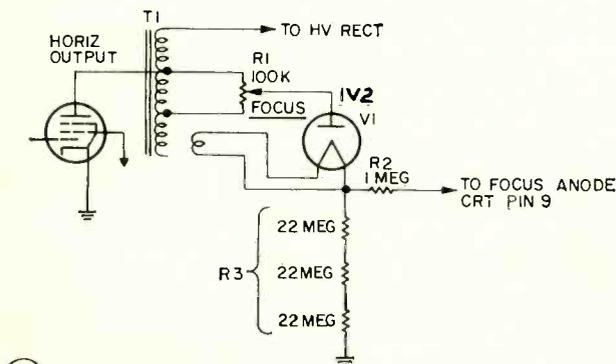
The third type of focus control is the adjustable-core




(A)

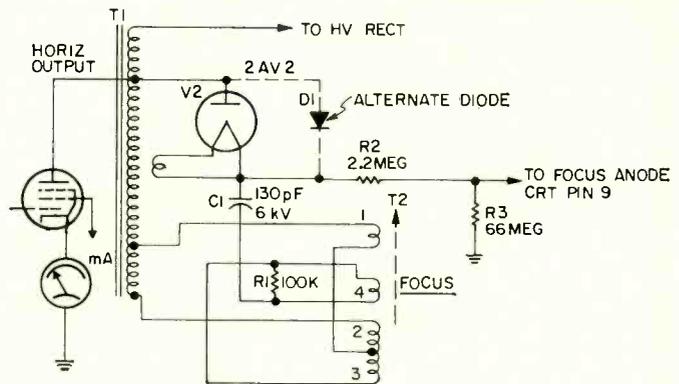

(B)

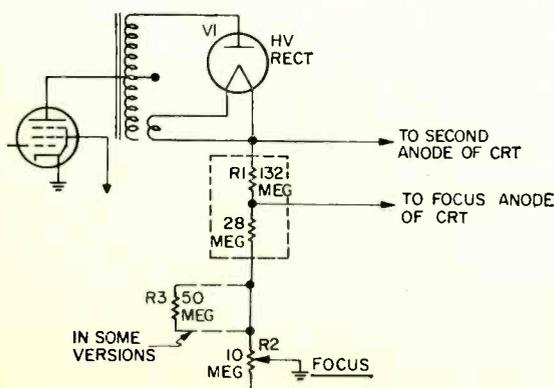

(C)

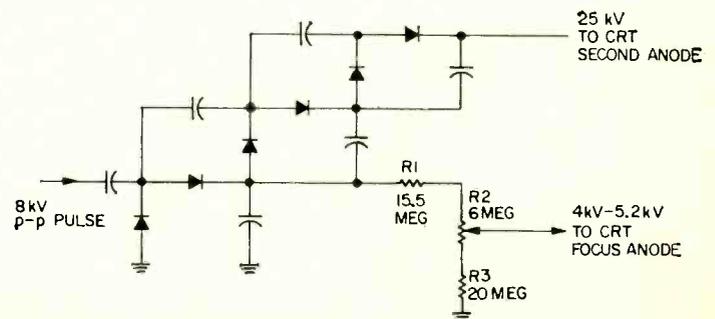

(D)

focus transformer (diagram B). Its operation has been explained: it controls dc output of the rectifier by altering the net pulse voltages applied to the focus rectifier.

The object of any focus control is to vary the average focus voltage to suit the CRT and the settings of other controls in the chassis. To a small extent, the video in the station signal can affect focus voltage. If you put a dc meter on focus voltage, you'll see it vary with brightness content of the picture. More brightness over the screen loads down the high voltage, so the focus shifts downward enough to track. The high-voltage regulator should take care of voltage shifts, but small changes are normal as scenes change.

### QUICK TROUBLESHOOTING

The quickest way to spot a focus problem is to look at a blank raster on the picture-tube screen. If the set has a SERVICE switch with a RASTER position, use that. Or, turn the AGC control to produce a whiteout. Or, just pull an i.f. tube temporarily.

If horizontal scanning lines are not clear and sharp, turn the focus control in both directions. One way should bring the raster to sharp focus. If not, the set has focus trouble.

For a first check, measure the high voltage with a normally bright raster. If it is within 1000 volts of the value recommended by the manufacturer, yet the raster will not focus, the trouble is definitely in the focus stage. The high voltage must be within tolerance before you can make any meaningful tests in the focus circuits. That's because, one way or another, the focus stage gets its drive from the sweep-and-high-voltage section.

Compare the two voltages to their normal values. If the high voltage is, say, 10 percent low, and focus voltage is perhaps 50 percent low, that points to focus trouble.

If both voltages are either high or low by the same percentage, the trouble is common to both. The horizontal output tube, flyback, B-plus, boost voltage—all could affect the pulse reaching the HV and focus stages.

You can measure focus voltage conveniently at pin 9 of the socket for standard color picture tubes. Or, it may be easier to reach at the focus-rectifier socket or terminal, or at the hot end of the 66-meg resistor. Most high-voltage probes or voltmeters can read focus voltage accurately.

While you're near the CRT socket, take a look at pin 9.

This terminal often corrodes, turning green and sometimes eating the wire through. The cure is a new CRT socket, and then fill the pin-9 socket terminal with silicone grease to keep air from it.

### SPECIAL CLUES

If focus voltage drops to a very low value or zero, there can be no raster. With focus voltage at about 50 percent of normal, you probably can see fuzzy blobs of color—the highlights of the picture—floating around the screen. But be sure high voltage is up; if it's not, you can't do a thing with the focus stage.

If the high voltage is only half of normal and the horizontal output tube overheats, a selenium focus rectifier may be shorted. Also check for a shorted pulse-coupling capacitor (diagram B). Shorted turns in the focus transformer can overload and destroy the flyback.

Cathode current in the horizontal output tube is a good clue. Measure it. If it is high, yet the circuit tries to produce high voltage, disconnect the focus transformer. If it's shorted, disconnecting it returns the cathode current and high voltage almost to normal.

If high voltage is normal and cathode current within reasonable limits, yet focus voltage is very low or zero, suspect an open focus rectifier. The solid-state type rarely opens. Usually, they partially short and overload the flyback and output tube.


A change in value of a high-resistance bleeder can raise or lower focus voltage. If a plastic-encased one goes bad, use an exact duplicate.

Check potentiometers. The kind in diagram A is especially critical. Never spray it to clean it. If contact gets poor, or the element starts arcing to ground, replace the pot. Use a thick sheet of polyethylene film between the control and the mounting—it increases the insulation path.

It's best to replace pots in divider circuits, too, if they begin to get scratchy. Cleaning rarely lasts more than a few days (or hours). They can also change value, which upsets the voltage.

If sets with voltage multipliers (diagram D), any high-voltage trouble also affects focus voltage. If an individual rectifier in one of these goes bad, it's a good idea to replace the whole "board-full" of rectifiers. All of them have probably been subjected to overload. **R-E**

## WAVEFORMS AS GUIDES

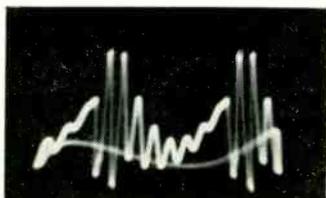

### WF 1 Normal Unknown V p-p

This waveform is sample picked up by holding scope probe near focus transformer (diagram B). It has little practical value for diagnosis. It varies in shape and peak-to-peak amplitude as the core of the focus transformer is adjusted. The changes verify that the core is affecting coupling in the transformer, but the changing value of dc voltage at the rectifier cathode tells you the same thing. Changing parts values elsewhere in the circuit have little or no effect on the waveform. See DC Voltages As Guides for better help in diagnosis.

## NEW BOOKS

**LOGIC CIRCUITS**, by N. M. Morris. McGraw-Hill Book Co., 330 West 42 St., New York, N.Y. 10036. 199 pages, 6 x 9 in. \$13.50.

A general guide to design and use of logic devices and systems with chapter review questions for self-study. Chapters describe numbering systems and codes, arithmetic processes, the flip-flop, counting systems and hardware. Advantages of Karnaugh map method are described.

**MOTOROLA COLOR TV SERVICE MANUAL**, by Forest H. Belt. Tab Books, Blue Ridge Summit, Pa. 17214. 160 pp., 8½ x 11". Softcover, \$4.95.

Covers all models using TS-907-TS-924 chassis. First chapters are on monochrome purity, gray-scale tracking, static and dynamic convergence adjustments, as well as tuner repair. Remaining chapters are devoted to analysis of each chassis.


**HANDBOOK OF PRACTICAL ELECTRONIC TESTS AND MEASUREMENTS**, by John D. Lenk. Prentice-Hall, Inc., Englewood Cliffs, N.J. 07632. 302 pages, 6¼ x 9¼ in. \$15.

Guide to most practical electronic test and measurement procedures encountered by electronic technicians. Covers component tests and quantity measurements. Generally, a quick procedure with simple equipment is described along with a detailed lab procedure. **R-E**



# Constant-Speed Motors for Tape Recorders

by AL WILLIAMS\*

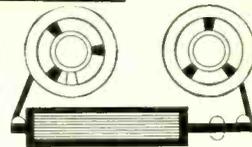

THIS SUMMER, IF YOU LIVE IN A REASONABLY large city, you found that at various times many of your appliances—from toasters to refrigerators, to blenders—were working at something less than maximum efficiency. Worse, some of your high-fidelity equipment did not work up to standard. It wasn't the fault of the appliances or components. The plain fact is that there were serious voltage drops at certain times of the day. Actually, voltage under the best conditions may vary considerably from the standard 115 to 120-volts supposedly delivered to your household outlets.

It's not just a summer problem, when air conditioners create a tremendous demand on available power. It can happen almost anywhere, anytime. A case in point is a busy ski area in Southern Vermont. During the evening, with every lodge filled to capacity, there is a definite loss in light levels compared with other times of the year.

A serious voltage drop can affect tape recording quality. The problem can be as sticky for the amateur home recordist as for the professional working on location. Let's take a look at specifics and the part that the motor drive—and hysteresis synchronous motors—can do to help the situation.

The fundamental task of a transport system is the smooth, constant movement of recording tape through the tape head contact area. Achieving and maintaining this movement under varying ambient conditions is the transport designer's challenge.

Some of the annoying results of inadequate transport design include change in key or pitch of recorded audio information and random fluctuations detectable as wow and flutter. These problems can occur due to ac input power line variations as well as loading changes within the transport system.

The drive motor is the prime mover in the transport system. All tape speed deviations, whether stationary or time varying ones, can ultimately be referred back to the drive motor. Therefore, the essential specification for a tape transport drive mo-

tor is constant speed. In terms of practical design the linkage between drive motor and the rest of the tape transport system will typically involve belts or friction wheels. And in order to keep a reserve of momentum at the point of contact between the tape and drive system (the capstan), inertia is supplied with a flywheel attached to the capstan shaft directly.

The flywheel removes short term disturbances in the transport motion, but its average angular velocity must be maintained with the drive motor.

The types of motors or motor systems which might be selected by the designer include **dc motors** with mechanical or electronic regulation; **ac induction motors**; and **ac synchronous motors**.

Dc motors with governors are widely used in and generally restricted to low cost portable battery operated recorders, but have been used, occasionally, in component class recorders where battery supplies are not used. The disadvantages of the dc system include brush and contact noise if mechanical regulation is employed, the need to supply dc, and usually some additional circuitry such as amplifiers and/or filters. Remote control of motor speed is a possible but very minor advantage of the dc system.

Ac induction motors of single- or two-phase design are often found in a variety of tape recorders primarily because of their simplicity and low cost. In the single-phase induction motor the rotor speed is highly dependent on the ac source voltage and will change significantly with minor changes in source voltage. A two-phase induction motor may be coupled with a detector and servo amplifier to provide motor speed control. This approach is complicated, costly, and commonly relegated to control functions such as head motor speed in video recorders.

Ac synchronous motors represent a class of motors that are self-correcting relative to rotor speed and consequently deserve first consideration in tape transport design especially for the component type recorder. A "self-correcting" mechanism implies some form of servo system which will oppose fluctuations in both input power and output load in order to maintain some predetermined characteristic in the overall system output. A servo system is comprised of a detector and feedback mechanism usually incorporating amplification.

*Comparative transport performance* has proven the superiority of the hysteresis synchronous motor particularly in large cities where ac voltage fluctuations are extreme during high demand periods of the day and in heavy industrial locations where extreme fluctuations may be more frequent if not more severe. While the amplitude of the ac power undergoes large changes, the frequency (60 Hz standard) remains closely controlled. Such circumstances clearly suggest preference of the synchronous motor over ordinary induction motors in selecting a tape transport drive. The transport speed of Concord MK series decks has been controlled to within 0.7% for ac power fluctuation of between 100 and 128 Vac and within 1.0% over an 80 to 140 Vac range, surpassing the dynamic range of either ac induction or dc servo-controlled machines tested under identical circumstances.


The hysteresis synchronous motor takes special advantage of the phenomenon of hysteresis for detection of an error signal and generation of a correction signal. Hysteresis as related to the synchronous motor means the lag in magnetic effect which in the synchronous motor is used to store and compare the phase of the angular velocity of the rotor with the electrical phase of the ac source, some of which flows in the stator windings. The synchronous motor then performs magnetic amplification of the correction signal that subsequently alters the angular velocity of the rotor just enough to eliminate the error signal. This process is a dynamic one taking place on a continuous basis. The result is a phase lock between the frequency of the ac source and the frequency (rpm) of the rotor. Once locked in phase the motor speed is highly dependent on the frequency of the ac source and remarkably independent of the voltage level of the ac source. Phase lock will be lost only when the ratio of motor load to input power is excessive. In addition to the basic synchronous motor windings, others are included which serve two important purposes, that of self-starting and dynamic damping in case of large sudden changes in rotor load. Hence, the hysteresis synchronous motor is a self-contained closed loop phase lock servo system that can furnish constant speed over a wide range of power levels.

\*Chief Engineer

Concord Electronics Corp.
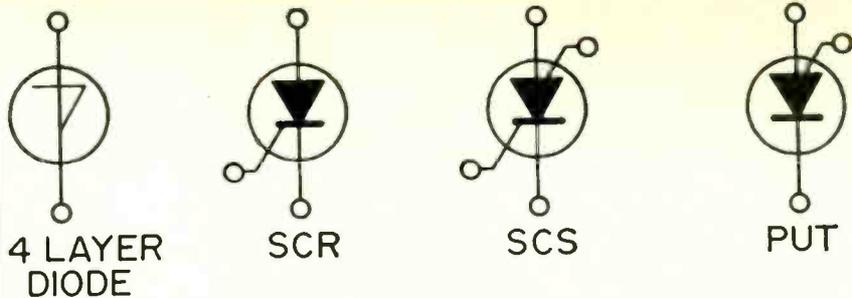
# How To

The PUT or complementary SCR is new solid-state device. Here is how it works and how to use it.



# Putter With The Put

by R. W. FOX

About three years ago, the General Electric Company introduced the fourth member of the pnpn structure. This device has been called both a Programmable Unijunction Transistor (PUT), since it may be used in place of the unijunction transistor, and a complementary SCR. The former name is to show a major use of the device while the latter is a more descriptive name. General Electric has at present two devices on the market, the D13 Complementary SCR and the D13T PUT. These two devices are specified for their respective tasks, but to a degree may be interchanged. This article is devoted mainly to the D13T PUT. Several of the applications and much of the theory can apply equally to both devices. Included are theory, UJT replacement, switching circuits and many examples of their use.

## Theory of the PUT

In Fig. 1, the equivalent circuit shows the two transistor analogue of a pnpn structure. For an SCR, the gate is the base of the npn transistor, but for the PUT the gate is the base of the pnp transistor. This is the difference between a PUT (and/or a complementary SCR) and an SCR. The theory follows normal thyristor theory for turn-on, turn-off and latching, etc.

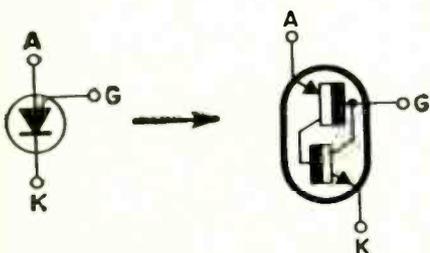


Fig. 1—PROGRAMMABLE UNIUNCTION transistor and its equivalent circuit.

The device is turned on by making the gate negative with respect to the anode by a little more than the diode offset voltage so that enough anode current exists through the first pn junction (i.e., the anode-anode gate junction) to cause regeneration to oc-

cur. This current can be considered base current for the pnp transistor. The current required to trigger is typically on the order of a microampere. The current at which regeneration takes place is defined as the peak-point current ( $I_P$ ). As the regeneration causes the anode-cathode voltage to collapse the device switches to the conducting state. The time for device turn-on is about 50 to 100 nanoseconds. (This turn-on, it should be noted, is an order of magnitude faster than the conventional unijunction transistor.) This results in a steep pulse for high di/dt SCR trigger applications. The device is now in the on-state, and in this region there are two parameters of great interest. These parameters (shown in Fig. 2) are  $I_V$  or valley current and  $I_H$  or

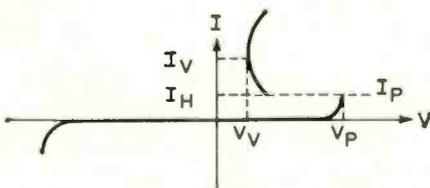


Fig. 2—ANODE-CATHODE CHARACTERISTICS based on the  $I_V$  and  $I_H$  parameters.

holding current. Valley current is the point at which the PUT starts out of saturation, however, because of the beta shifts in the two transistors, the device will remain in conduction until the holding current is reached. The device at this point returns to a non-conducting state.

## The PUT in relaxation oscillators

Figure 3 shows a typical PUT relaxation oscillator. This circuit has two allowable states. State 1 will be for the PUT in the off or non-conducting state and state 2 will be for the PUT in the on-state.

First let's analyze the steady state conditions. Assume that the PUT is in state 1. After sufficient time the capacitor will be charged to  $(V_{AA} - R_A I_{CL})$ , where  $I_{CL}$  is capacitor leakage current. The anode-cathode voltage would be  $(V_{AA} - R_A I_{CL} - R_L I_L)$ , where  $I_L$  is the cathode leakage current

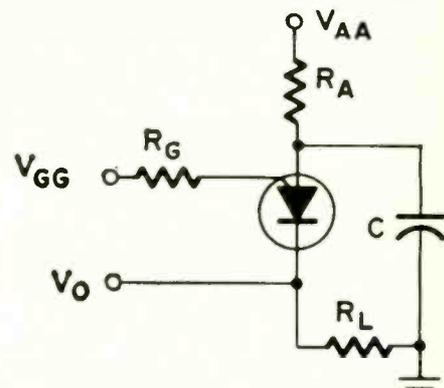


Fig. 3—A PUT RELAXATION OSCILLATOR. Like most circuits of this type, the active element is either on or off.

(which usually may be neglected). The voltage would be  $(V_{GG} - R_G I_{G0})$ , where  $I_{G0}$  would be the gate current with device off. (At room temperature  $I_{G0}$  will be less than 10 nanoamperes). If this state is allowed then:

$$V_{AA} - R_A (I_L + I_{CL}) < V_{GG} - R_G I_{G0} + V_T \quad \text{Eq. 1}$$

Where  $V_T$  is the gate offset voltage to trigger.

If this equation is satisfied then this state is a permissible state, and the output voltage ( $V_O$ ) is  $I_L R_L$ . Assuming that  $I_L$ ,  $I_{CL}$ , and  $I_{G0}$  are negligible, Equation 1 reduces to:

$$V_{AA} \leq (V_{GG} + V_T) \quad \text{Eq. 2}$$

Equation 2 points out vividly that as long as the anode supply voltage is less than the effective gate source voltage ( $V_{GE} \Delta V_{GG} - V_T$ ) the PUT will remain non-conducting.

If the PUT is initially in state 2, then the following relationships will hold:

$$V_{GG} = (R_G + R_L) I_G + R_L I_{AK} \quad \text{Eq. 3}$$

$$V_{AA} = (R_A + R_L) I_G + R_L I_G \quad \text{Eq. 4}$$

$$V_G = R_L (I_G + I_{AK}) \quad \text{Eq. 5}$$

Where  $I_{AK}$  is anode-cathode current and  $V_F$  is the forward voltage drop.

$$\text{If } I_{AK} > I_H \quad \text{Eq. 6}$$

then the PUT will remain in conduction.

If  $V_{GG}$  is applied to the circuit of Fig. 3 and then  $V_{AA}$  is applied, capacitor C will charge exponentially toward  $V_{AA}$ . If Equation 2 is satisfied then the PUT

does not turn-on. If, on the other hand  $V_{AA} > (V_{GG} + V_T)$  then it may be possible for the PUT to turn on. As the capacitor charges the current through  $R_A$  decays exponentially. When  $V_C = (V_{GG} + V_T)$  the current through  $R_A$  is:

$$I_A = (V_{AA} - V_C) / R_A \quad \text{Eq. 7}$$

It is at this point the PUT will trigger, if at all. For the PUT to be triggered

$$I_A \geq I_P \quad \text{Eq. 8}$$

For if  $I_A$  is less than  $I_P$  then regeneration cannot occur and the device remains in State 1.

If regeneration occurs then the anode-cathode voltage collapses and  $V_C$  appears across  $R_L$ . Voltage  $V_C$  will now follow  $V_C$  on an exponential decay less the forward drop of the PUT to one of two end points. The first is the case where equation 6 holds; the second where it does not. It can be seen, if the capacitor has been discharged, and Equation 6 still holds, then, as a consequence the PUT will remain conducting. In the other case, as the capacitor discharges, there will be a point in the discharge at which the anode current has dropped below the holding current. At this point the PUT returns to State 1 and the capacitor is recharged through  $R_A$ . This is the free-running relaxation oscillator.

### PUT fudge factors

In the above discussion,  $I_P$ ,  $I_V$ ,  $V_T$  and  $V_{GG}$  were assumed. The parameters, though, are not just single numbers that are merely plugged into equations. Each of these may be varied over a considerable range.

#### Factor No. 1—Stand-Off Ratio ( $\eta$ )

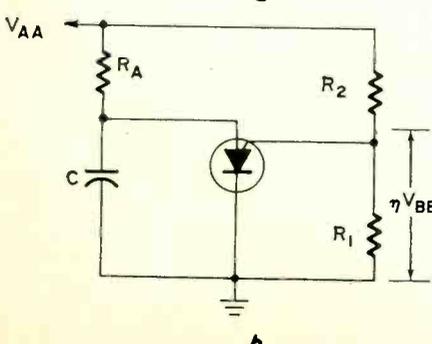
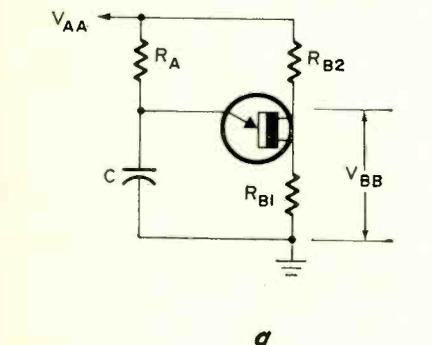


Fig. 4-a—A UJT RELAXATION OSCILLATOR and (b) a comparable PUT circuit.

In the above example two power supplies were used for the relaxation oscillator. In a conventional unijunction circuit (Fig. 4-a) only one supply is used and the peak capacitor voltage at turn-on is expressed as a function of the inter base voltage ( $V_{BB}$ ). However, between UJT's of the same type this function, the stand-off ratio ( $\eta$ ), varies by 10 to 20%. With the PUT each and every peak-point will be essentially the same and the designer may pick his peak-point over the range from 0.1 to 0.9. The stand-off ratio is merely the ratio of resistors in divider  $R_1$ - $R_2$  in Fig. 4-b. Thus, for the PUT, the stand-off ratio is:

$$\eta = R_2 / (R_1 + R_2) \quad \text{Eq. 9}$$

#### Factor No. 2—Peak Point Current ( $I_P$ )

Peak-point current is a function of gate source impedance and temperature, one is an advantage but one a disadvantage. As gate source impedance and temperature are raised the peak-point current decreases. Temperature compensation will be discussed in a later section. Figure 5-a and 5-b show

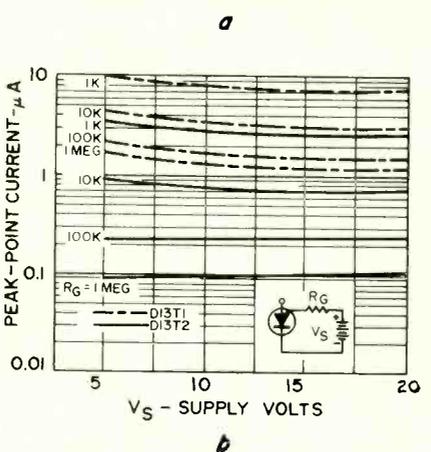
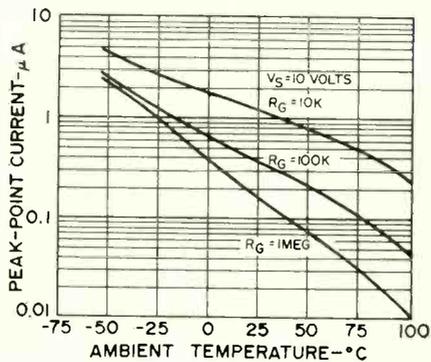


Fig. 5—PEAK-POINT CURRENT is a function of gate source impedance and of temperature. Chart (a) plots peak-point current against temperature and chart (b) against supply voltage ( $V_S$ ) for different values of gate source impedance  $R_G$ .

the typical variations of peak-point current with changes in temperature and  $V_S$  (gate supply volts) for different values of gate series resistance ( $R_G$ ).

#### Factor No. 3—Valley Current ( $I_V$ )

Valley current can be varied the same way the peak-point current is

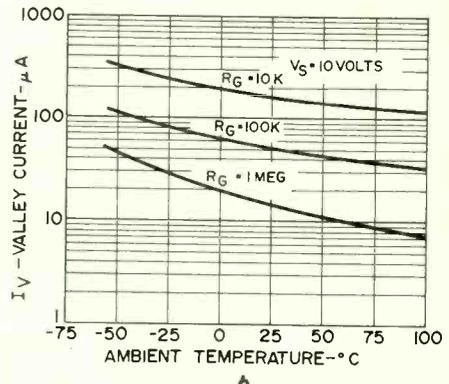
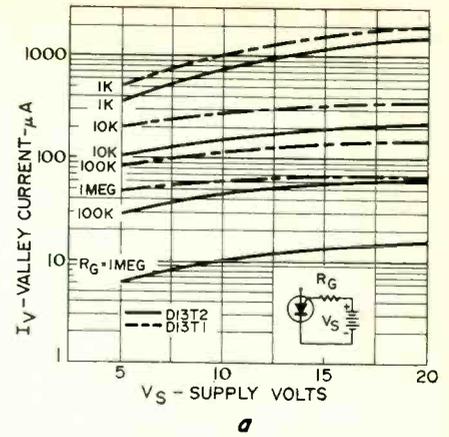


Fig. 6—VALLEY CURRENT characteristics, for given gate impedance, varies with  $V_G$  (chart a) and temperature (b).

varied. Figures 6-a and 6-b show this variation.

#### Factor No. 4—Offset Voltage ( $V_T$ )

Since the PUT, like most thyristors, is current triggered, the offset voltage is a function of gate source impedance. In reality this offset is due to the diode voltage drop between anode and gate, hence it is a function of temperature. Figure 7 shows the

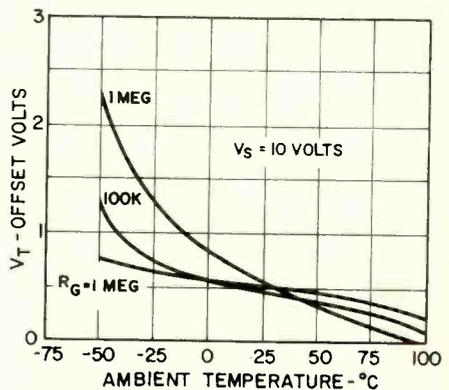


Fig. 7—TRIGGER OFFSET VOLTAGE for a programmable unijunction transistor varies with ambient temperature level and with the series impedance at the gate.

typical variation of  $V_T$  with gate source impedance and temperature.

### Replacing UJT's with PUT's

In many cases a designer will wish to replace a UJT with a PUT to obtain a cost or performance advantage. Using the PUT (DI3T) in a cir-

circuit in place of an unijunction is easily understood. Figure 8-a shows a basic unijunction circuit. Figure 9-a shows the identically same circuit except the unijunction transistor is replaced by the D13T plus the resistors R1 and R2. Comparing the equivalent circuits of Figs. 8-b and 9-b, it can be seen that both circuits have a diode connected to a voltage divider. When this diode is forward biased in the unijunction transistor, R1 becomes strongly modulated to a lower resistance value. This action generates a negative resistance characteristic between the emitter (E) and base one (B1). After the diode conducts, the regeneration inherent in a thyristor causes the PUT to switch on. This generates a negative resistance characteristic from anode to cathode simulating the modulation of R<sub>1</sub> in the conventional unijunction.

Resistors R<sub>12</sub> and R<sub>11</sub> (Figure 8-a) are generally unnecessary when the D13T replaces a conventional UJT. This is illustrated in Fig. 9-c. Resistor R<sub>11</sub> is often used to bypass the interbase current of the unijunction which would otherwise trigger the SCR. Since R1 in the case of the PUT (D13T), can be returned directly to ground there is only the peak-point current of the PUT (about 1μA) to bypass. Resistor R<sub>12</sub> is used for temperature compensation and for limiting the dissipation in the UJT during capacitor discharge. Since R2 (Fig. 9) is not modulated, R<sub>12</sub> can be absorbed into it. The result is the circuit of Fig. 9-b which contains the same number of components as the UJT circuit but at a lower cost and with better performance.

Resistors R1 and R2 have been removed from the pulse circuit, there is no reason why they cannot be changed in impedance to change the peak-point and valley currents as required by the application.

### Applications of the PUT

The PUT with its flexibility can be tailored to fit many places where a UJT would not be acceptable; but before proceeding to some examples of this type of circuitry, there is a need to examine some final UJT applications of the PUT.

It was noted above and shown in Fig. 5 and 6 that peak and valley current were functions of gate source impedance. Since they both decrease with increase in gate source impedance there could be a problem if we wish to vary them independently. Figure 10 shows some variations on the gate circuitry.

In normal UJT circuitry the interbase resistance is normally about 10,000 ohms, with the PUT impedance level as a design factor. Figure 10-a shows a high-impedance divider which gives low I<sub>p</sub> and low I<sub>v</sub>. If you want characteristics closer to the UJT's, use the circuit in Fig. 10-b. Remembering that at the peak-point the anode (point E) of the PUT (D13T) is above the gate potential by V<sub>T</sub>. Thus the diode is reversed biased and the gate source impedance is high (1-megohm in this case). But at the valley-point the gate is near cathode potential (point B1), so that the diode is forward biased and the gate source impedance is low (about 1000 ohms).

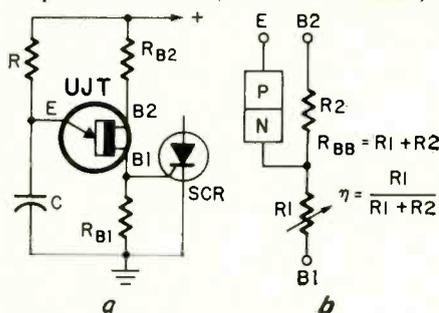


Fig. 8-a—A TYPICAL UNIUNCTION driving an SCR. b—UJT equivalent circuit and (c) negative-resistance characteristic.

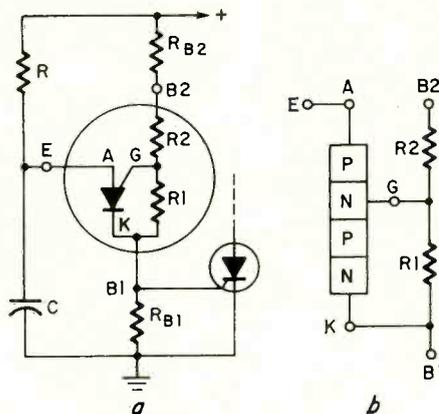


Fig. 9—HOW A PUT REPLACES UJT in circuit in Fig. 8-a. b—UJT equivalent circuit using programmable unijunction. c—The simplified PUT version of Fig. 8-a.

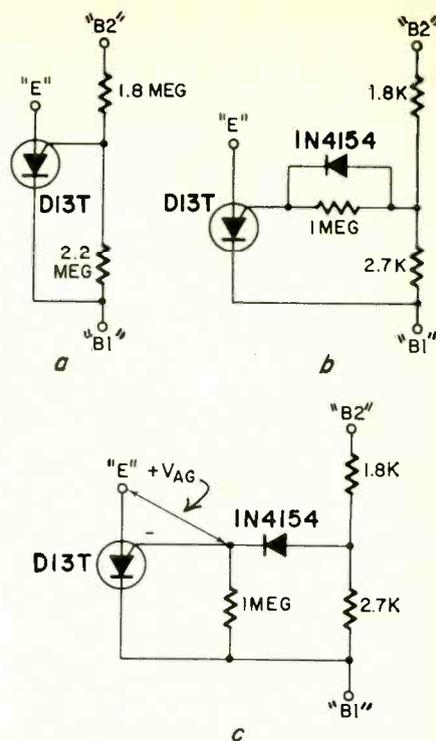


Fig. 10—TYPICAL UNIUNCTION circuit configurations. a—For low I<sub>p</sub> and low I<sub>v</sub>. b—Use paralleled diode and resistor for low I<sub>p</sub>-high I<sub>v</sub> and (c) for low I<sub>p</sub> and high I<sub>v</sub> with temperature compensation.

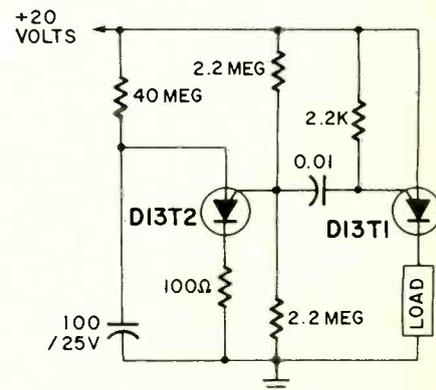


Fig. 11—A ONE HOUR TIMER using a pair of PUT's. The first does the timing; the second one triggers the load circuit.


This circuit has a low I<sub>p</sub> and relatively high I<sub>v</sub>.

Figure 10-c shows a similar diode network that provides temperature compensation of V<sub>T</sub>(V<sub>AG</sub>). When the peak-point is approached, the trigger point is when

$(V_E - V_T) = (V_{GG} - V_D)$  Eq. 10 where V<sub>GG</sub> is the effective gate source voltage; V<sub>D</sub> is the diode forward drop. Equation 10 shows that temperature compensation is obtained when the diode's temperature coefficient is the same as V<sub>T</sub>.

In Fig. 11 there is shown a one-hour timer using a single D13T2 PUT for timing and to develop a trigger pulse for the D13T1 at the end of the delay.

(continued next month)

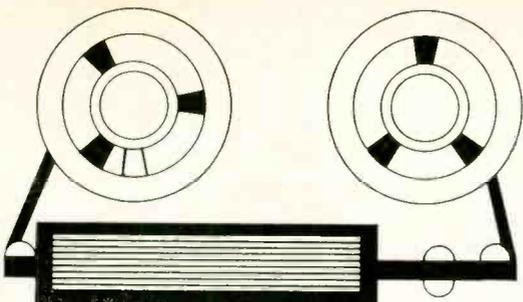

# TAPE RECORDING

by DAVID K. KIRK

PERHAPS IT'S BECAUSE NOBODY HAS yet decided what magnetic fields really are. Maybe the reason is simply the comparative youth of the system. The fact remains that magnetic tape recording is both the most fascinating and the most mystifying aspect of modern audio. If you find this hard to swallow, try your hand at these.

**The upper limit of recorded frequency range is set by the length of the record head gap.** False. At high frequencies, only one side of the record head gap needs to be operative to place a related signal pattern on the tape. Most audio recorders have a record bandwidth of well over 40 kHz at 7½ ips and record their own high-frequency bias. Pull the tape along at 1 ips and you will hear it.

The effect can be quite annoying to anyone trying to edit a 15 ips tape, where it is necessary to rock the tape slowly back and forwards across the playback head. The main factor limiting overall bandwidth is the *replay* head gap, where the "trailing edge" recording effect does not apply.

**Storing tape without rewinding reduces print-through.** True but how many followers of this common studio practice realize why? The general theory, and it's wrong, is that post-echo rather than pre-echo is printed when the tape is stored without rewinding and post-echo is less audible, being drowned in the decay of the transient that caused it. Actually, print-through travels in both directions by equal degrees, causing equal amounts of pre- and post-echo.

Then why does storage without rewinding work? Because print-through is largely a temporary effect that disappears after a few seconds out of contact with the responsible field. Storing tape before rewinding means that a program must be rewound a few minutes before playback. This act alone gives the print-through time to decay. On some tape transports, the time lag between the tape leaving the feed reel and reaching the play head is great enough for the

(continued on page 58)

## facts and fallacies

*You probably don't know all the answers, but if you get all of these right, class yourself an expert!*



**REEL-TO-REEL TEAC A-7010 is typical of high-quality professional-type equipment for home use.**


Second in a series...

# Can you solve these problems in electronics?

They're a cinch after you've taken RCA Institutes' new communications electronics program.

It includes new preparation for the FCC license plus the assurance of your money back if you fail to get it.


This one is quite elementary.

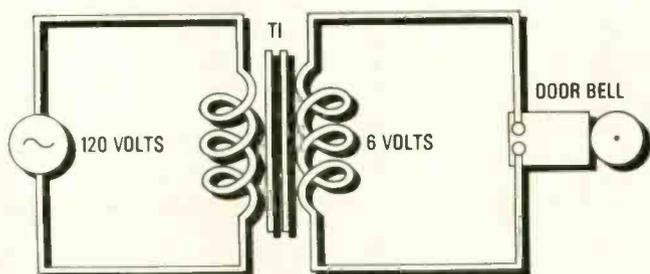

**In this door bell circuit, which kind of transformer is T<sub>1</sub> — step-up or step-down?**

Note: if you had completed only the first lesson of any of the RCA Institutes Home Study programs, you'd easily solve this problem.

This one is more advanced.

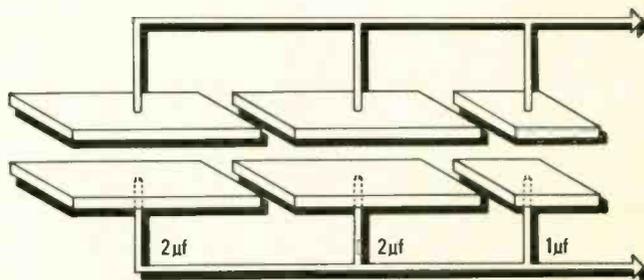

**What is the total capacitance in the above circuit?**

Note: you'd know the solution to the problem if you'd taken only the first two lessons in RCA's new Communications Electronics Program.

These are the lessons that prepare you step-by-step for an FCC License.

This license is a requirement for servicing all types of transmitting equipment and can help open doors to jobs commanding high income in communications, radio and broadcasting, aerospace, industrial automation and many others.

**For a rewarding career with good pay, take that first step now. Send for complete information—mail the attached card.**

Answers: Step-down.  
5 μf

# RCA Institutes Autotext learning method makes problem-solving easier... gets you started faster towards a good-paying career in electronics

Are you just a beginner with an interest in electronics? Or, are you already making a living in electronics, and want to brush-up or expand your knowledge? In either case, RCA has the training you need. And Autotext, RCA Institutes' own method of Home Training will help you learn more quickly and with less effort.

## Wide Range of Courses

Select from a wide range of courses. Pick the one that suits you best and check it off on the attached card. Courses are available for beginners and advanced technicians.

- Electronics Fundamentals
- Black & White Television Servicing (Transistorized TV Kit Available)
- Color Television Servicing (Color TV Kit Available)
- FCC License Preparation
- Automatic Controls
- Automation Electronics
- Industrial Electronics
- Nuclear Instrumentation
- Electronics Drafting
- Computer Programming

## Plus these new up-to-the-minute courses


- Semiconductor Electronics
- Digital Electronics
- Solid State Electronics
- Communications Electronics
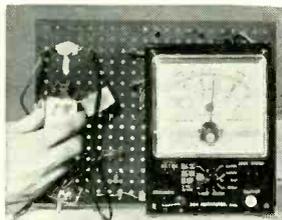
## Prepare for good paying positions in fields like these

- Television Servicing
- Telecommunications
- Mobile Communications
- CATV
- Broadcasting
- Marine Communications
- Nuclear Instrumentation
- Industrial Electronics
- Automation
- Computer Programming
- Solid State
- Electronics Drafting



Build and keep this valuable oscilloscope.



In the new program on Solid State Electronics you will study the effects of temperature and leakage characteristics of transistors.



## Variety of Kits—Yours to Keep

A variety of RCA Institutes engineered kits are included in your program of study. Each kit is yours to keep when you've completed the course. Among the kits you construct and keep is a working signal generator, a multimeter, a fully transistorized breadboard superheterodyne AM receiver, and the all-important oscilloscope. These 4 kits are at no extra cost. Compare this selection with other home study schools.

## Two Convenient Payment Plans

Pay for lessons as you order them. No contract obligating you to continue the course. Or, you can take advantage of RCA's convenient monthly payment plan. No interest charges!

## Classroom Training Also Available

RCA Institutes operates one of the largest technical schools of its kind. Day and evening classes. No previous training is required. Preparatory courses are available. Classes start four times a year.

## Job Placement Service, Too!

Companies like Bell Telephone Labs, GE, Honeywell, IBM, RCA, Westinghouse, Xerox, and major radio and TV networks have regularly employed graduates through RCA Institutes' own placement service.

## All RCA Institutes courses and programs are approved for veterans under the new G.I. Bill.

## Send Attached Postage Paid Card Today. Check Home Study or Classroom Training.

Accredited Member National Home Study Council.

IF REPLY CARD IS DETACHED, SEND THIS COUPON

### RCA Institutes Inc.

Home Study Dept. 758-010-0  
320 West 31 Street  
New York, N. Y. 10001

Please send me FREE illustrated career catalog.

Name \_\_\_\_\_ Age \_\_\_\_\_  
(please print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

(continued from page 53)

print to fall below audibility; so no need for preplayback winding.

**Magnetic tape wears out. False.** Run a brand new tape through a recorder with clean heads and measure the frequency response. Rewind, clean the heads once more, and measure again. The 7–20-kHz response should be at least 2 dB up on the virgin figures. Far from wearing out, professional and high-quality tape actually improves with age, the oxide coating smoothing out to a level, dust-free surface. By contrast, most new tapes are covered in a fine powder of loose excess oxide. This clogs the record and play heads, causing high-frequency attenuation. A brand new tape should always be fast-wound a few times before serious use.

**The best way to dub a tape is backwards.** This one is true, strange though it may seem, and is applied by at least one major tape recording manufacturer. Run any recording backwards and you will notice an apparent lack of high frequencies that makes you reach for the treble boost. The reason is that the reversed tape is devoid of sudden transients; our ears are climbing relatively slowly up what would naturally be the decay. The sudden cutoff at the “end” of each transient has little impact on our ears. Under normal conditions, the ampli-



**VARIABLE NOISE FILTER** is featured in Ampex AX-300. Other versions offer automatic threading too.

fiers would be prone to “ringing” on the leading edge of strong transients. Reversed, the only sudden change they have to make is in downward level.

**Residual head magnetism builds up over several hours. False, or at best only half true.** The major cause of residual head magnetism is dc from the tape amplifier reaching the record and/or play heads. This occurs to some extent in almost all recorders, particularly where a high-value capacitor is in circuit close to the heads. A degaussed head can become remagnetized within minutes, depending on the circuit design, input load and operational switching sequence.

**A 30 Hz–20 kHz +3 dB frequency response gives better quality than 30 Hz–12 kHz +3 dB.** This may be true of amplifiers but with tape equipment is a very false assumption indeed. When a manufacturer or service engineer sets the bias current of a recorder, he usually goes for wide frequency range simply because the customer, reared on specifications, expects it.

Most studios, however, rightly set the bias at a higher level in order to secure maximum signal-to-noise ratio and minimum distortion for a particular brand or (tape is very variable) individual reel of tape. Studios appreciate that lifting the high-frequency response to extremes inevitably brings in an extra octave of noise, both from the tape and from the preemphasis circuits. It's no good throwing figures at the public.

A dealer who wants to guarantee himself regular customers should let them hear an A-B comparison of two machines, one biased for maximum frequency range at 3% distortion, the other for maximum signal-to-noise ratio at around 1.5% distortion. Most people will go for the latter because most people don't like hiss. [A few so-called non-professional recorders (e.g., Tandberg's model 6000) offer extended frequency response with excellent signal-to-noise ratios and low distortion. Also, Dolby noise reducers



**RECORD AMPLIFIERS ARE STACKED** below the tape deck in the Roberts model 771X.

(Advent, Harmon-Kardon) now permit extended response without tape hiss.—EDITORS]

**Quarter-track systems produce more hiss than 1/2-track. False.** When you switch from a 1/4-track playback head on a stereo recorder to a 1/2-track head, the hiss will go up, not down as a lot of people seem to expect. The 1/2-track head theoretically produces 3 dB more hiss than the 1/4-track, so an A-B test on background noise alone will show 1/2-track to be the “inferior” system. The important fact is that 1/2-track produces a full 6 dB increase in signal level and, when the 3 dB hiss is allowed for, this makes a 3 dB improvement in signal-to-noise ratio. It is the latter 3 dB that counts.

Finally a question the reader might like to puzzle over. The answer requires nothing more than a basic understanding of equalization. When asked to make copies of a 3 3/4 ips master on 15 ips speed-to-speed equipment for later playback at 3 3/4 ips, for what speed do you set (a) the equalization of the playback machine and (b) the preemphasis of the recorder? **R-E**

## COLOR TV ANTENNA INSTALLER'S GUIDE


This month Section II of your Radio-Electronics Reference Manual continues to grow. We present the final part of an article on TV antenna installation.

If you wish, you can purchase a special hardcover binder to keep your Reference Manual pages together. It has a dark blue fabric cover and is gold-stamped Radio-Electronics Reference Manual. The cost is \$1.00 postpaid. Order from N. Estrada, 17 Slate Lane, Central Islip, L. I., N. Y. 11722.
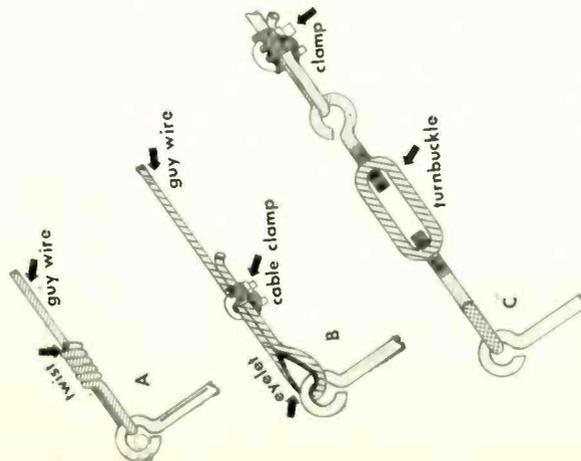
# ANTENNA INSTALLER'S GUIDEBOOK

by JAMES A. GUPTON, JR. (PART II)

wire-twist connections that will secure any antenna. A disadvantage of wire-twist fastening is the difficulty in removal for antenna or motor repairs. Use cable clamps for fastening the guy wires to the mast guy rings. If you want to do a real bang-up job, use cable clamps and turnbuckles at the anchor eyebolts. Cable clamps are all that is really



*Three methods of fastening guy wire to guy ring or eyebolt. A wire wrap will hold OK but may cause trouble if mast must be lowered for antenna repairs. Use a cable clamp or a clamp and turnbuckle for easy installation and guy tension adjustments. The drawings show the correct way to install cable clamps. Cable's free end passes under the bight.*


needed at the anchor points, but the turnbuckles permit easy guy wire tension adjustment without freeing the ends of the guy wire. This prevents the antenna from falling if the guy wires get away from you.

After attaching the guy wires to the guy rings on the mast, be sure you keep the wire in the original loops or hanks. Hours can be wasted trying to straighten out the kinks and tangles if the loops are allowed to unravel. Now the antenna is carried to the roof. Tall antennas are definitely a two-man job.

WIND VELOCITY (miles per hour)	PRESSURE ON ANTENNA (pounds per square ft.)	CITY	WIND (max. mph)
10	0.25	ALBANY, N. Y.	71
20	1.0	CHARLESTON, S. C.	76
30	2.3	CHICAGO, ILL.	87
40	4.0	HATTERAS, N. C.	110
50	6.3	MIAMI, FLA.	132
60	9.0	MINNEAPOLIS, MINN.	92
70	12.3	MOBILE, ALA.	87
80	16.0	MT. WASHINGTON, N. H.	188
90	20.3	NEW YORK, N. Y.	99
100	25.0	NORTH PLATTE, NEB.	72
110	30.3	WASHINGTON, D. C.	62

wire and unroll it towards the side guy-anchor eyebolt. Run all the remaining guy wire through the eyebolt and let it hang down from the roof. Repeat the process for the top guy point and each of the remaining guy wires.

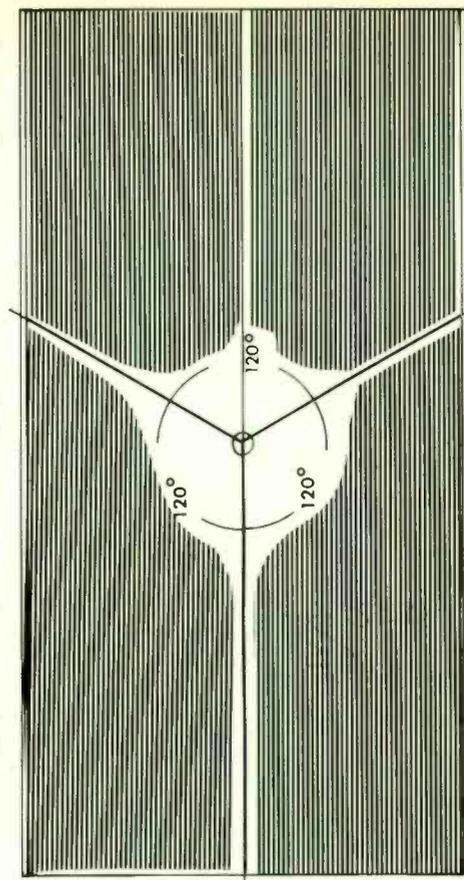
Each guy anchor point now has guywires threaded through the eye-



*In a 3-wire guy system, guy points are 120 degrees apart around mast base. Number of guys used depends on the height and type of mast.*


Of course there are two ways to erect tall antennas. One is to use telescoping mast sections. The telescoping mast is base mounted and the first 10-foot section guyed. By standing on a stepladder, the topmost section is hand-pulled out of the nest of mast sections. It is securely locked to the top of the second section with a through-hole bolt. The second section is then hand raised and also through-hole bolted to the bottom section, and the two topmost sets of guy wires pulled straight and fastened. While this sounds easy, it is very difficult to do—almost impossible for one man.

Here is a better way. Try mounting the base mount and turning the mast holder down the roof ridge in the direction the antenna and mast will lay. Remember the guy-anchor eyebolt must be in the opposite direction. Now bring up the antenna assembly and lay the mast section along the ridge of the roof. Very long mast sections will cause the antenna hang over the roof edge. Have someone hold up the antenna

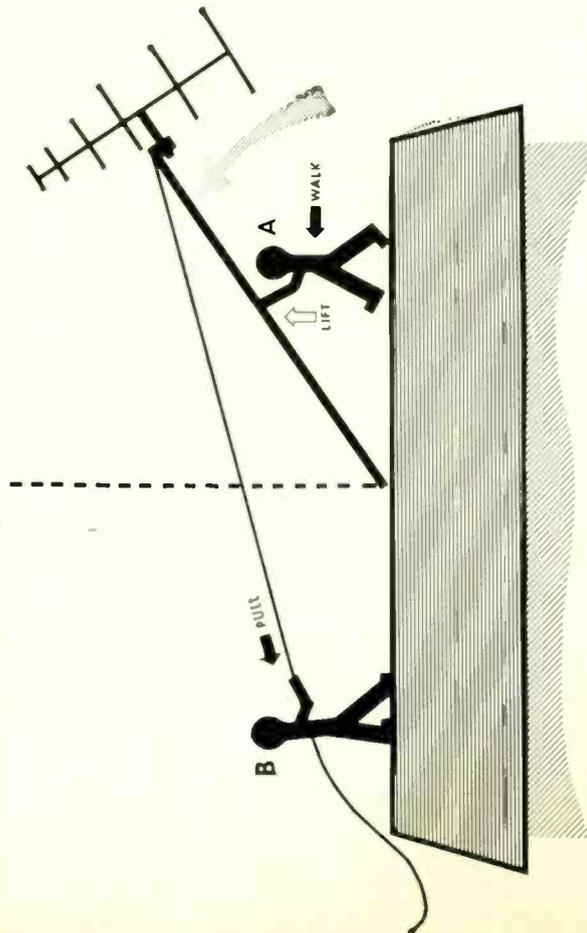

Masts of 20 or 30 feet must have guys at intermediate levels (see page II-16). Man B maintains tension on all guys on same side of mast.

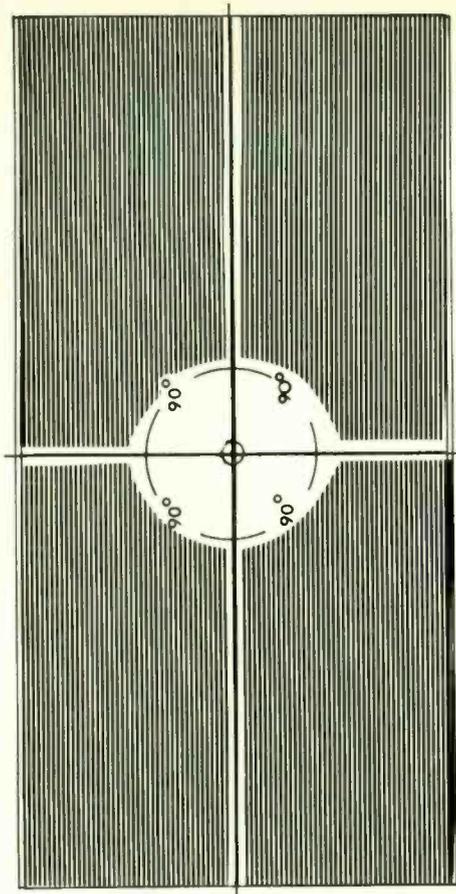section for shorter masts. Insert the mast into the mast holder and run the through-hole bolt through holder and mast. Now take a roll of guy



#### 4 WIRE GUYING

The guy points should be same distance from mast base. If impractical, then guys on opposite sides should make same angle with vertical.

It's a good idea to have someone to play out the guy wire at each side anchor point, but not essential. With one man located at the roof ridge guy anchor point and you at the antenna motor point, the antenna is now ready to be erected.

Lift the antenna over your head while the second man pulls up the slack on the guy wires. The walk-up process simply means that as you walk towards the mast base pushing the antenna mast upward, your partner keeps a constant tension on the guy wires. This push-pull action allows the antenna and mast to rise upward while tension on the guy wires prevents the mast bending from the antenna weight.

Once the mast has been raised to a vertical position, it is easy to

WIRE SIZE	WIRE TYPE	WEIGHT PER 1000 FT.	APPROX. STRENGTH / LB.
$\frac{1}{16}$ " dia.	6 STRAND, GALVANIZED	8.2	130
$\frac{1}{8}$ " dia.	6 STRAND, GALVANIZED	31.8	540
$\frac{3}{16}$ " dia.	6 STRAND, GALVANIZED	72.9	1,150
No. 12	COPPERWELD, SOLID	54.6	510

hold it steady while your partner quickly applies tension to all guywires and completes a temporary fastening at the anchor eyebolts. Check the straightness of the antenna mast. Any bowing of the mast can be corrected by alternately increasing and decreasing tension on opposing guy wires. Be sure the antenna is pointing North for correct motor alignment. Now secure all guy wires by tightening with cable clamps.

One bit of advice in the use of turnbuckles. Most of us are prone to adjust turnbuckles to drum-tight tension. Leave just a little slack or sag in the guy wires to permit a very slight mast movement. An unyielding antenna mast will collapse in high winds while the flexible mast will yield and spring back without collapsing.

### Antenna mast grounding

According to the National Electrical Code, the mast and metal supporting structures of the antenna must be permanently and effectively grounded, without an intervening splice or connection. In addition, the code requires all conductors of a lead-in or transmission line to be provided with a lightning arrester when the lead-in conductors are enclosed in a continuous metallic shield and the metallic shield is appropriately grounded. The grounding conductors must be copper, aluminum, copper-clad steel, bronze, or any corrosion-resistant material. Grounding conductors may or may not be insulated but must be securely fastened in place.


The ground conductor must be run as straight as possible from the antenna mast and/or lightning arrester to the grounding electrode. The code further specifies that the grounding conductor must be at least No. 10 solid copper wire or No. 8 solid aluminum wire.

The only acceptable ground electrodes are: cold water underground ground pipes (providing they are metallic construction and not plastic). The grounding electrode may be of iron or steel with a minimum 5/8-inch diameter; non-ferrous rod or pipe may be used with a 1/2-inch diameter minimum. The pipe must be driven below the permanent moisture level or at least 8 feet unless rock formations prevent it being driven to this depth. If you run into rock formations, the grounding electrode can be buried horizontally at a depth of 4 feet.

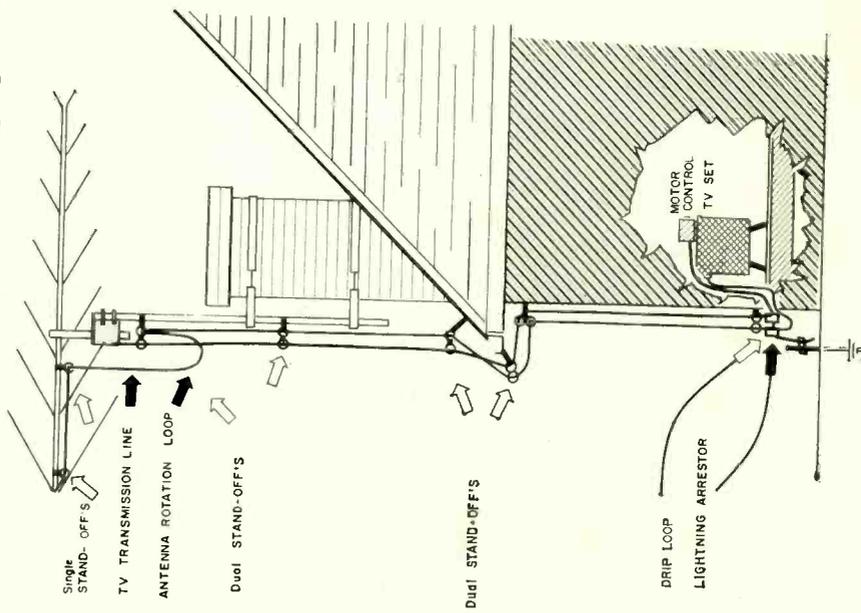1. The lightning arrestors must be grounded and can share a common ground with the mast. The proper place for the ground is at the point of entrance to the house.

line; this is particularly true for uhf signals.

To connect the 300 ohm-line to the antenna, strip the insulation down the middle 6 inches. This permits the line to spread wide enough for the antenna terminals. Form a half loop on the stripped wire with the open end on the right. The loop will close when the antenna screws or wing nuts are tightened, thus making a secure connection. Seal the transmission line contacts with wax or paint. This prevents trouble later from copper oxide forming and reducing signal strength.



*Typical TV antenna installation. Stand-offs prevent lead-in and rotor cables from rubbing metal gutter. Special lightning arresters are made for use on rotator cables. Make all grounds to water pipe or ground rod driven close to the point where the cables enter the house.*

The 300-ohm twinlead is run along the antenna to the mast using clip-on standoffs to support the wire. Make all turns gentle curves

2. Only the mast and supporting metal parts must be grounded; the antenna is **not required to be grounded**. Therefore, if you have a TV set of the transformerless variety, commonly called ac-dc, you could have a "**hot**" chassis **shorted to ground through the tuner's antenna coil**. This can be prevented by insulating the antenna from the mast or by installing additional high resistance-capacitance networks in series with your TV set's antenna terminals.

This can be eliminated if you have an ohmmeter. Just check the ac line plug for direct connection to the TV set's chassis. If there is no low-resistance path from plug to chassis, you are o.k. In event there is a low-resistance path to the chassis, mark that prong of the plug and always insert the grounded prong into the wide slot or ground connection of your wall receptacle.

3. Check your insurance agent about your home-owners insurance coverage for TV antennas and the grounding requirements of your insurance company. This way, you **know** your insurance will cover your antenna installation in case of lightning, wind-storm, or other damage.

### Running transmission lines


Most antennas have a characteristic impedance of 300 ohms, and to effectively transfer the maximum amount of signal energy to the set, the antenna should "see" a 300-ohm impedance. Shielded coaxial cable has a number of advantages over 300-ohm twinlead: it can be run close to metal objects without interference, and it will not pick up ghost-causing secondary signals or interference from automobile ignitions.

If you decide to use coaxial cable, which has an impedance of 75 ohms, it's a good idea to purchase an antenna with a 75-ohm impedance. Then, unless the TV set has a 75-ohm input terminal, you can use a 75-to-300-ohm matching transforming transformer at the set. Otherwise, a 300-ohm antenna requires a matching transformer installed between the antenna and coax and another transformer at the set.

There are many varieties of 300-ohm transmission line suitable for vhf reception. When both uhf and vhf signals are to be received, shielded 300-ohm twinlead or uhf foamline 300-ohm twinlead is best. These heavy-duty lines eliminate signal fade due to moisture on the

instead of sharp angles. (Uhf signals are inclined to travel on the surface of the conductors and the surface effect permits the signal to leave the wires at sharp right-angle turns. Stand-offs on the mast hold the transmission line and "stand-off" the line from the effects the mast may have on high frequency signals.

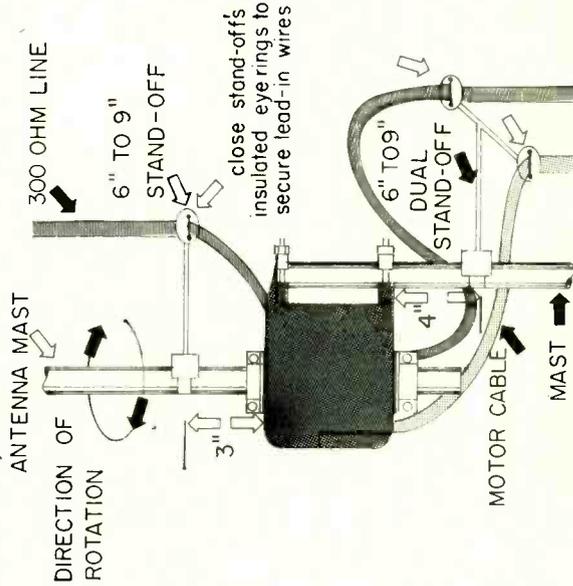When the transmission line nears the rotor motor, it is anchored firmly to the mast with a stand-off, then formed into a "rotation loop". You must have sufficient slack to permit 360° rotation. It could break the line in two if not enough loop slack is formed. (Most motors rotate clockwise.)



*Lead-in breakage due to flexing by wind and antenna rotation can be prevented by using stand-offs directly above and below rotor. Be sure that loop permits antenna to turn through 360° without putting strain on lead-in.*


Carrying the assembled antenna and rotor motor to the roof is a two man job for fringe antennas. One man should be on the roof to pull the antenna up as the second man climbs the ladder, guiding the antenna. When the antenna is on the roof, it is raised to a vertical position, lifted above the chimney clamp and gently lowered until the bottom of the mast engages the lower chimney clamp. Tighten both clamps lightly. Turn the antenna to North by rotating the mast and motor assembly. Now firmly tighten the chimney-mount clamps.

R-E
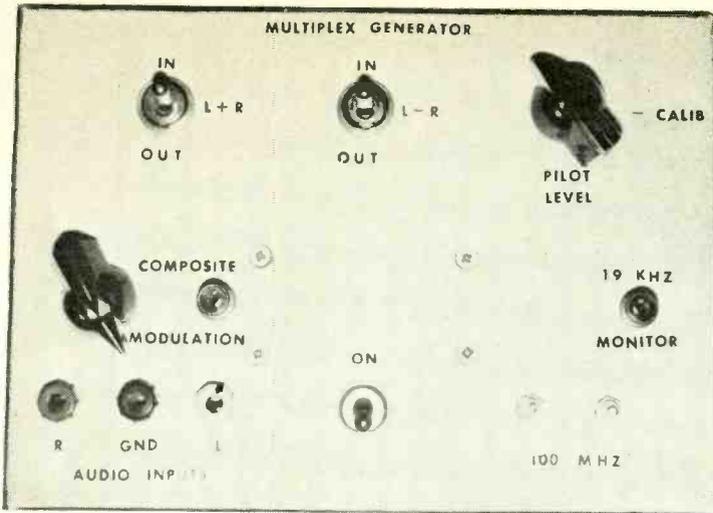
# Build FM stereo multiplex generator

by AL FRANSON

With the popularity of FM stereo receivers, test equipment to align these sets is a must for service technicians and anyone interested in building FM receivers. To get good stereo separation from a receiver, a multiplex generator is much better than adjusting the set by "ear."



The stereo generator described here is designed for low cost and simplicity. It compares favorably to commercial units in stereo performance, but does not have self-contained audio signals or i.f. test signals. Only a 1-kHz signal and a general-purpose scope are required for aligning this generator. An FM receiver should also be available. The generator provides over 30 dB stereo separation between 300 and 20,000 Hz. Total parts cost is around \$50, but many parts are common and can be found in your spare parts box.

This unit does have an rf output to check an entire receiver's performance without an external rf generator. The high-frequency oscillator works at  $106 \pm 2$  MHz and is frequency modulated by a variable-capacitance diode. A regulated power supply is incorporated and gives exceptional rf stability.

## Theory of operation

A basic understanding of FM stereo transmission will aid the user in understanding the generator operation and design theory. The FCC controls the method of stereo transmission. The baseband spectrum is shown in Fig. 1. The

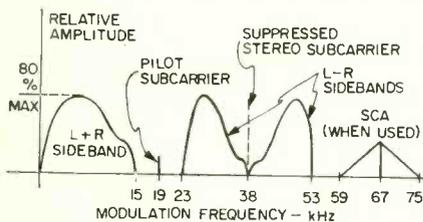


Fig. 1—FREQUENCY SPECTRUM in a frequency modulated stereo broadcast.

monaural information or average left plus right (L+R) signal is contained in the 0 to 15 kHz useful audio range. The L-R information required for stereo demodulation is transmitted as an amplitude modulated 38-kHz suppressed-subcarrier signal. This will result in frequency components  $\pm 15$  kHz around 38 kHz, or 23 to 53 kHz. The 38-kHz subcarrier must be reinserted in the correct phase at the receiver to obtain the complete stereo information. To do this, a low-level 19-kHz pilot signal is transmitted which has a definite phase relationship with the original 38-kHz subcarrier at the transmitter. This pilot

phasing is one of the most important properties of the transmitted composite signal and is discussed in greater detail in the section on alignment procedures.

A few FM stations also transmit a 67-kHz storecast subcarrier. This signal is a frequency modulated subcarrier occupying the spectrum from 59 to 75 kHz. This subcarrier was not included in this generator since it has nothing to do with aligning stereo separation of a receiver.

The composite baseband signal shown in Fig. 1 now frequency modulates the rf carrier between 88 and 108 MHz at a maximum deviation of  $\pm 75$  kHz peak. Broadcast stations use pre-emphasis of the audio inputs which increases the level of audio frequencies above 2 kHz. This makes a de-emphasis necessary in stereo FM receivers to restore correct frequency response. This pre-emphasis at the transmitter occurs before multiplexing. In other words, the subcarriers previously mentioned are not pre-emphasized. This makes it unnecessary to include pre-emphasis in a stereo generator which is used for alignment purposes. If pre-emphasis is desired, it can be applied to the audio input signals before they are fed to this generator.

## Circuit description

Transistor Q1 in Fig. 2 operates as a 19-kHz oscillator with the exact frequency of oscillation determined by the twin-T feedback network. The twin-T network makes a very stable oscillator once R2 is adjusted for 19 kHz. The 11-volt peak-to-peak output of the oscillator (Fig. 3) is fed to a phase-shift network through

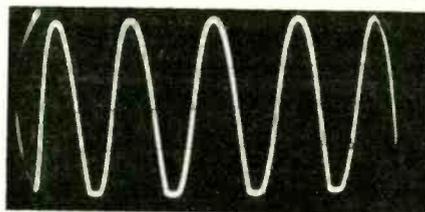


Fig. 3—PILOT SUBCARRIER signal generated in 19-kHz Twin-T oscillator Q1. buffer amplifier Q2. The phase-shifter is also isolated from the summer through buffer amplifier Q3. The phase-shifter provides a means of correcting phase relationship between the 19-kHz pilot and the 38-kHz subcarrier. The range of phase shift available is about  $120^\circ$ . A maximum

phase shift variation of  $90^\circ$  is necessary.

Transistor Q4 is the doubler amplifier which delivers two equal but opposite polarity signals to diodes D1 and D2 which full-wave rectify the 19-kHz signal. Germanium diodes are used for highest rectification efficiency. This distorted waveform (shown in Fig. 4) is

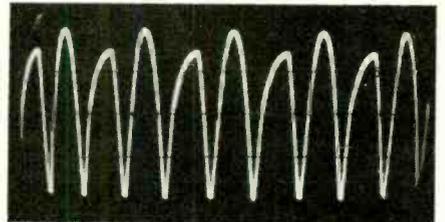


Fig. 4—DISTORTED SIGNAL results when 19-kHz subcarrier is rectified.

passed through an active bandpass filter consisting of Q5, Q6, and Q11. This is a twin-T filter which has excellent selectivity. The filter output is shown in Fig. 5.


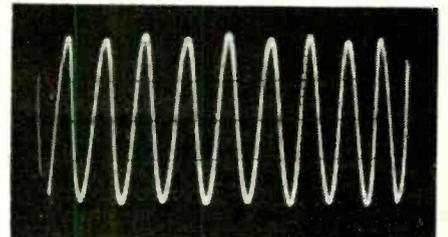


Fig. 5—THE STEREO SUBCARRIER is cleaned up by sharp 38-kHz Twin-T filter.

The two audio inputs representing left and right channels must be conditioned to give L+R and L-R signals for proper stereo transmission. The left and right inputs are fed to the summer, Q10, which is a feedback amplifier that provides greater than 20 dB isolation between L and R inputs. The actual isolation is partially determined by the generator internal impedances used to feed the L and R signal inputs. Source impedances below 100 ohms should be used to give greater than 40 dB isolation. Transistor Q7 is operated as an inverter to give -R at its output. This is summed with L by Q8 to give R-L at its output. R31 and R22 must be adjusted to give proper stereo separation.

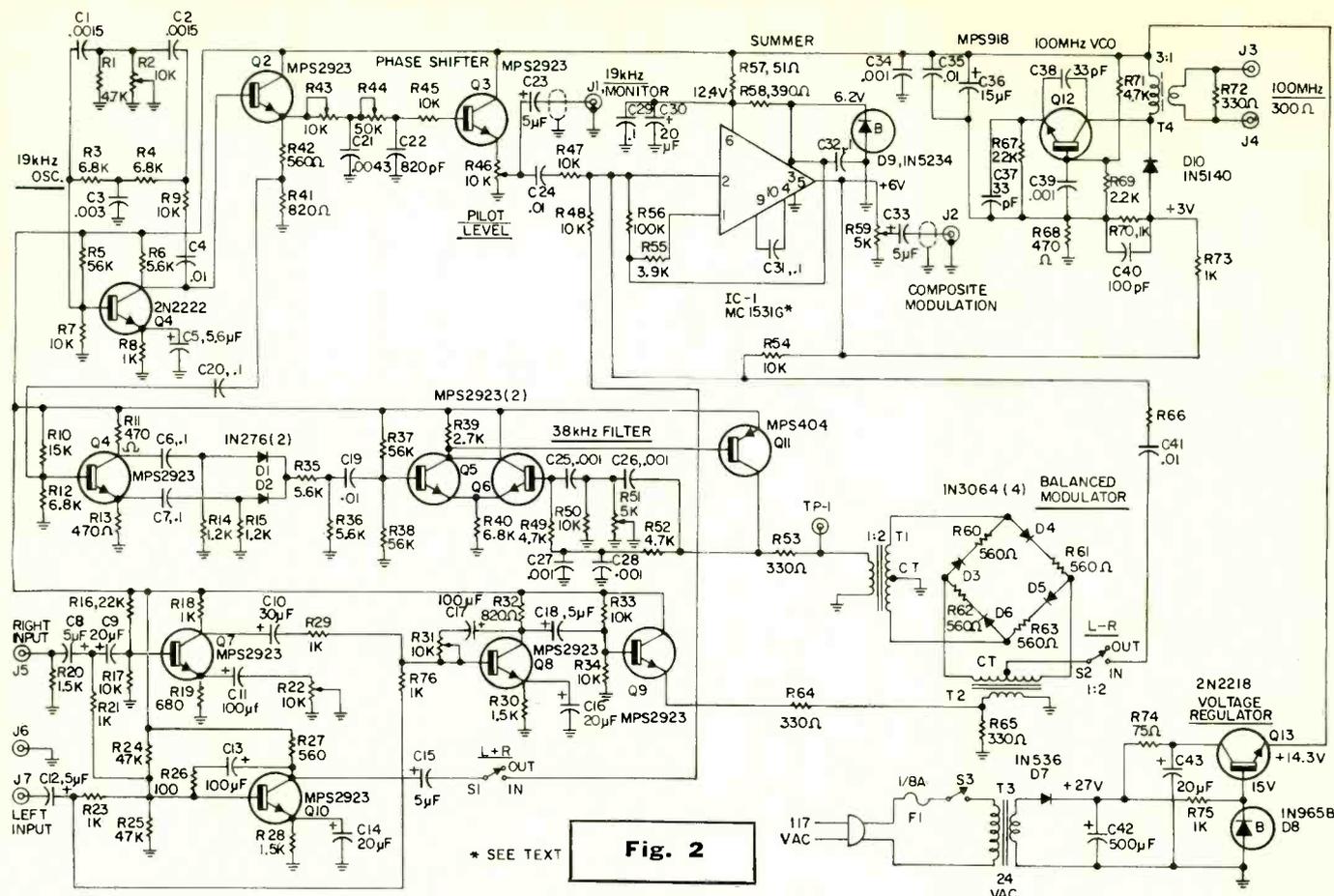The R-L signal is used to modulate the 38-kHz subcarrier delivered by Q11. This is done with a ring modulator with



All resistors 1/4 watt, 5% unless noted

- R1, R49, R52, R71—4700 ohms
- R2, R22, R31, R43, R46—potentiometer, 10,000 ohms, linear taper
- R3, R4, R12, R40—6800 ohms
- R5, R37, R38—56,000 ohms
- R6, R35, R36—5600 ohms
- R7, R9, R17, R33, R34, R45, R47, R48, R50, R54—10,000 ohms
- R8, R18, R21, R23, R29, R70, R73, R75, R76—1000 ohms
- R10—15,000 ohms
- R11, R13, R68—470 ohms
- R14, R15—1200 ohms
- R16—22,000 ohms
- R19—680 ohms
- R20, R28, R30—1500 ohms
- R24, R25—47,000 ohms
- R26—100 ohms
- R27, R42, R60, R61, R62, R63—560 ohms
- R32, R41—820 ohms
- R39—2700 ohms
- R44—potentiometer, 50,000 ohms, linear taper
- R51, R59—potentiometer, 5000 ohms, linear taper
- R53, R64, R65, R72—330 ohms
- R55—3900 ohms

- R56—100,000 ohms
- R57—51 ohms
- R58—390 ohms
- R66—27,000 ohms
- R67, R69—2200 ohms
- R74—75 ohms, 5 watts
- C1, C2—1500 pF, 2%, mica
- C3—3000 pF, 2%, mica
- C4, C19, C24, C35, C41—.01  $\mu$ F, ceramic
- C5—56  $\mu$ F, 15 volts, tantalum
- C6, C7, C20, C29, C31, C32—.01  $\mu$ F, ceramic
- C8, C12, C15, C18, C23, C33—5  $\mu$ F, 6 volts, tantalum
- C9, C14, C16, C30, C43—20  $\mu$ F, 50 volts, tantalum
- C10—30  $\mu$ F, 15 volts, tantalum
- C11, C13, C17—100  $\mu$ F, 6 volts, tantalum
- C21—4300 pF, 5% mica
- C25, C26, C27, C28—1000 pF, 2%, mica
- C34, C39—1000 pF, ceramic
- C36—15  $\mu$ F, 20 volts, tantalum
- C37, C38—33 pF, 5%, mica
- C40—100 pF, 5%, mica
- C42—500  $\mu$ F, 30 volts
- C22—820 pF, 5%, mica
- T1, T2—Three 60-turn windings on CF111-06 core (see text), Newark Electronics Stock No. 59F1510. \$2.05

- T3—24 volts, 0.3 amp transformer (B.A. #13A903)
- T4—3-turn primary, 1 turn secondary, #26 enameled wire, 3/16" dia form, brass slug
- S1, S2, S3—spst toggle switch
- D1, D2—1N276 diode, Hughes
- D3, D4, D5, D6—1N3064 diode, TI
- D7—1N536 rectifier, G.E.
- D8—1N965B, 15-volt Zener, I.R.
- D9—1N5234, 6.2-volt Zener, Mot.
- D10—1N5140, Mot. or MV1624 (see text)
- Q1—2N2222, Mot.
- Q2, Q3, Q4, Q5, Q6, Q7, Q8, Q9, Q10—MPS2923, Mot.
- Q11—MPS404, Mot.
- Q12—MPS918, Mot.
- Q13—2N2218, T.I.
- IC-1—MC1531G op amp, Mot. or MC1709C (see text)
- J1, J2—phone jacks
- J3, J4—teflon feedthru
- J5, J6, J7—banana jacks
- F1—1/8 amp fuse
- Case—3" x 5" x 7" aluminum minibox (Bud CU3008A)
- Miscellaneous: 12 pin printed circuit connector, 300 ohm twinlead, fuse holder, 1/16" single sided p.c. board—4 1/2 x 6 inches.

diodes D3-D6. This type modulator is doubly balanced with two center-tapped transformers so the 38-kHz component is canceled at the output as desired. The output of the modulator consists of the amplitude modulation components of the 38-kHz suppressed subcarrier. Resistors R60-R63 are used to improve balance or carrier suppression. The carrier is more than 40 dB below the input, which is adequate.

Transformer T1 must respond past 50 kHz without any resonances. Most commercial audio interstage transformers do not meet this requirement. Therefore, a special toroid transformer was designed. The construction details for this transformer are in Fig. 6 on page 67.

Transformer T2 can be identical to T1. I used a commercial 2:1 center tapped transformer instead. At audio frequencies below 300 Hz the reactance of T2's primary introduces an undesired phase shift which results in decreased stereo separation. This can be improved only at the expense of a larger transformer winding or by reducing R65 and R64 which requires more transistor current. A higher current transistor could be used for Q9.

The total composite modulation consists of L+R audio, L-R information on the 38-kHz suppressed subcarrier, and the 19-kHz pilot signal. These are summed together by operational amplifier IC1. An op amp is used to give

greater than 60 dB isolation between the three inputs. Summing resistors R47, R48, and R66 can be varied to adjust the individual gains of each input. The individual gain is equal to R54 divided by the series resistor. I used an MC1531G which is rather expensive. Newer and cheaper op amps are available, such as the MC1709C, and can be used instead.

The summer output modulates variable-capacitance diode D10, which is part of the resonant tank circuit of the 100-MHz oscillator. The diode, a Motorola 1N5190 Epicap, makes this a voltage-controlled oscillator which results in an FM signal output. The center fre-

(continued on page 67)

## MULTIPLEX GENERATOR

(continued from page 64)

quency of the oscillator can be varied about  $\pm 2$  MHz by adjusting the slug in T4. My unit oscillated between 102 and 106 MHz. The exact frequency will be affected by stray wiring capacitance and layout. Be sure to prevent ground currents from modulating the oscillator. This is the reason for the decoupling consisting of R68, C35, and C36. The oscillator is especially susceptible to 19-kHz ground currents. Too much leakage will cause the pilot to be transmitted even though R46 is set at minimum. The oscillator output can be suitably loaded with a 300-ohm twin lead. Diode D10 can be any of a number of 10-pF units now available. One low cost unit is the MV1624 (\$1.42). The difference in operation between it and the 1N5140 (\$5.85) will be a slight difference in modulation sensitivity but should be negligible.

A regulated dc power supply and an ac rectifier circuit is used. The Zener diode reference provides a low output impedance. This is necessary to keep both oscillators at their correct frequencies and prevent power line modulation of oscillator Q12.

### Construction and alignment

The circuit layout is not critical except for the 100-MHz oscillator, for which component leads should be kept to an absolute minimum. A piece of 300-ohm twin lead connects the oscillator coil to the feedthru terminals in the chassis. The circuit board is laid out so it can be unplugged from the chassis. It is held in place by one screw and a threaded standoff to the chassis.

The first step in aligning this generator is to set the frequency of the 19-kHz oscillator. The easiest way to do this is to monitor the signal at J1 with an electronic counter while adjusting R2. Another way was devised which doesn't require a counter. A 19-kHz signal is available in all multiplex demodulators when the FM radio is tuned to a station broadcasting stereo. This signal can be used to compare with the generator pilot frequency using the simple phase detector shown in Fig. 7. R2 is adjusted until the phase-detector output contains a low-frequency beat note. This oscillator can be adjusted for a beat note of around 2 Hz which is plenty accurate—meaning the two frequencies are within 2 Hz of each other. One of the phase detector inputs should be greater than 4 volts p-p to turn the diodes on. The chassis cover should be in place for this test in case stray capacitance changes the oscillator frequency. This requires an access hole in the side or back of the unit for adjusting R2.

Next, the 38-kHz filter is aligned by adjusting R51 for maximum output at Q11's collector. Oscillation in this type of active filter is possible. Therefore, the 19-kHz oscillator should be disabled by shorting R7 and checking to see that no signal appears at Q11. The ac voltage at Q11's collector should be near 10 volts

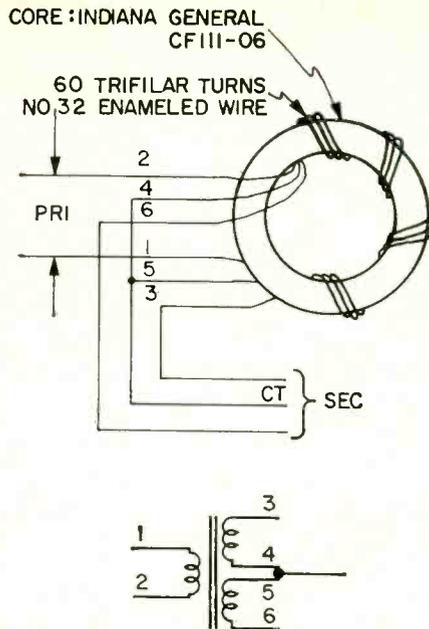


Fig. 6—TOROIDAL CONSTRUCTION increases bandwidth without resonances.

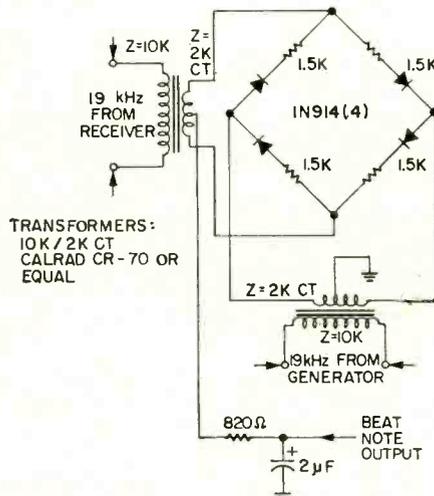


Fig. 7—SIMPLE PHASE DETECTOR eases adjustment of the 19-kHz oscillator.

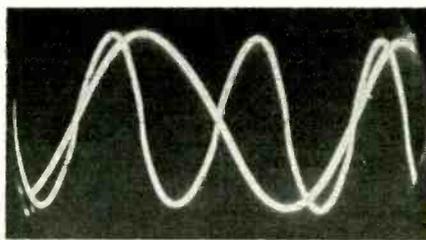


Fig. 8—PILOT AND SUBCARRIER are in phase in this double-exposure photo.

p-p and can be adjusted by selecting the value of R41.

The next step is to adjust the phase relationship between the pilot signal and 38-kHz subcarrier. To do this, you must either sync the scope on one of the signals or use a chopper input on the scope if available. The chopped input method allows direct viewing of both waveforms simultaneously. I used another method. The scope is externally synchronized by the 38-kHz signal at test point TP-1. Then the 38-kHz waveform here is viewed on the scope and the scope set-

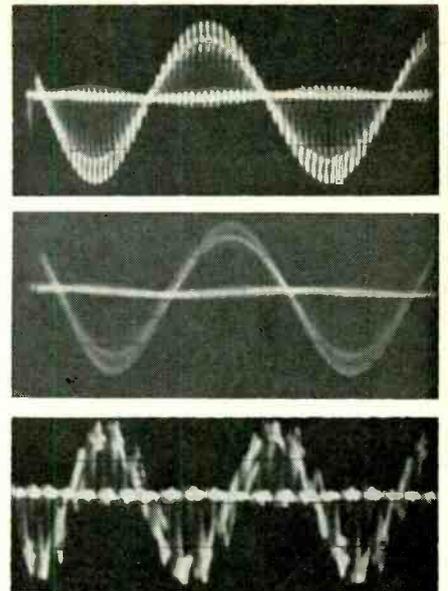


Fig. 9—MODULATION WAVEFORMS. a—Left-only or right-only signal with 1-kHz input at zero pilot level. b— and c— Waveforms at J2 with right or left inputs at 500 and 5000 HZ, respectively.

tings adjusted so the sine-wave zero crossing occurs at the center of the grid. Next the scope input is placed at J1 and R3, R4 are adjusted for a zero crossing of 19-kHz at the same point as the 38-kHz waveform. This is shown by the double exposure photo in Fig. 8. Now the pilot signal transmitted is in the proper phase relationship for stereo demodulation.

The audio mixing circuits must now be adjusted to give proper stereo separation. First apply a 1-kHz signal to the left channel. The pilot level is turned to minimum. The L+R and L-R switches must be closed. With the scope input at J2, adjust R31 until one of the 1-kHz envelopes is minimum in amplitude as shown in Fig. 9-a. Figures 9-b and 9-c show the same point for audio input frequencies of 500 Hz and 5 kHz respectively. These photos demonstrate a separation of about 40 dB. Next, remove the signal from L and apply to R only. A waveform similar to Fig. 9 will appear at J2 when R22 is adjusted for maximum separation.

The only calibration remaining is the 19-kHz pilot level required to give the proper oscillator deviation. I determined this with the help of an FM stereo receiver. For this measurement the L+R and L-R switches are in the OUT positions. Somewhere in the receiver multiplex you can check the 19-kHz level being received from the discriminator with a scope. Knowing this level, you can receive the signal from this multiplex generator and adjust the pilot level to equal that from a broadcast station. The exact level is not extremely important but some multiplex demodulators are sensitive to pilot level as separation is affected. I found that 0.2 volt p-p 19 kHz at J1 output is correct and should be accurate enough for alignment. At this point the knob on the PILOT LEVEL control was adjusted to read "CALIBRATE." I found it convenient to place

(continued on page 83)

# CAREERS in ELECTRONICS

## *blueprint to your future*

*You're a technician today, but you don't have to still be a technician tomorrow. Here are some of the other doors open to you*

by L. L. FARKAS\*

Last month we introduced the service technician to several other kinds of jobs that he is qualified to handle. This month we present ten more opportunities for the future. They take training, but they are available.

### Computer field engineer/programmer

The technician who has worked on computers and has a good knowledge of their theory and operation can often find a job as a computer field engineer. In this position he will service computers leased or sold by a computer company within a certain region. Such service includes preventive maintenance, troubleshooting and repair, and helping the customer determine what additional equipment he may need to perform specific tasks.

Normally the computer company hiring a technician will send him to school to learn the intricacies and operation of their product. It will help the technician also to learn computer programming. With this additional knowledge he can help his customer further in establishing various programs which in turn may mean the sale of additional computer components or subsystems.

Computer programming courses are available at many schools and all the technician needs is the desire to enroll in such a course and the tenacity to complete it. If he happens to be working on computers at the time, he can readily obtain programming experience that will help him progress on the job.

### Equipment sales

The equipment sales field can be interesting and profitable to the technician who has sales ability. There is, of course, the job of salesman in an electronic supply house, where knowledge of part characteristics and usage is a must.


Here the technician must know what new parts are available and can be used, or what substitutions can be made to meet a customer's design or operating requirements. He may also work as a salesman of various types of electronic equipment or electronic systems. In this last function he will often have to contact top officials of companies and government to whom he will have to demonstrate and sell his product. To do this effectively he will have to be able to speak well, but over and above this, he

\*Martin Marietta Corp., Vandenberg Operations

must know how to plan and implement a good presentation or demonstration.

The training for this type of work, besides gaining a thorough technical knowledge of the equipment, includes courses on salesmanship, audio-visual aids, creative thinking and psychology. Again, such courses are generally offered by community evening programs.

### Junior or associate engineer

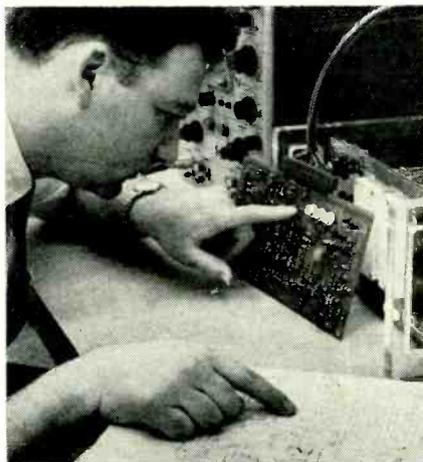

Courtesy Cleveland Institute of Electronics

To the technician who wants to further his career in the technical area of electronics the next logical step is to become a junior or associate engineer. In the past there were many opportunities for promotion to this level simply on the basis of experience on the particular equipment or system being produced. In the last few years, however, companies have tightened their educational requirements so that promotion to a junior or associate engineer level requires at least an associate science degree that includes courses in math, physics and chemistry.

Most companies encourage technicians to update their education to this level. Some firms offer refunds or provide loans for college tuition. The smart technician will take advantage of such help. Even at the rate of one course per semester, credits accumulate fast and soon the technician will find he has gained the education that permits him to progress.

### Radio operator

An electronic technician can also become a good radio operator. Certainly it shouldn't take him long to learn the operation and maintenance of commu-

nications transmitters and receivers, motor generators, radar and other electronic equipment used for communications and navigation. Radio operator jobs can be found at fixed installations, such as a shore or airport radio station, in aircraft and on ships. Some operators are also used in airplane blind-landing systems.


The radio operator must pass an examination given by the Federal Communications Commission to obtain a radio telephone or telegraph operator's license. For the telegraph endorsement the operator must take a code test in which his code sending and receiving skill is checked. For all licenses he must pass a test on the theory and operation of equipment and his knowledge of communication laws.

A radio operator on board a ship or aircraft is an officer with great responsibility. He must insure that his equipment is always in good operating condition and be ready to make emergency repairs.

A number of technical schools provide courses leading to a radio operator's license. Subjects covered include basic electricity, theory and operation of communications components and systems, theory and operation of radar systems and code practice. In most cases the electronic technician covers these courses pretty fast, needing only the code practice and a knowledge of FCC laws to meet the requirements of the FCC examinations.

Of course, if your hobby is amateur radio, you may be able to short-cut the education span since you'll already have acquired most of the necessary knowledge and practice in communications.

### Circuit draftsman

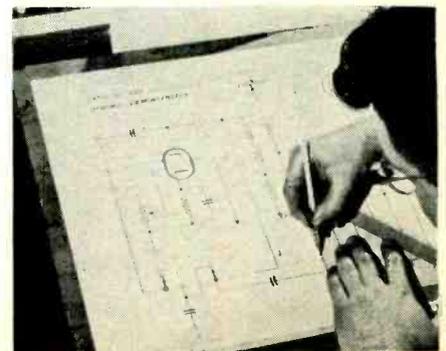

Courtesy RCA Institutes

An interim step between a tech-

nician and engineer can be taken via the drafting route. Here the technician can work on layouts of electronic circuits and, in some cases, as he gathers knowledge and experience, he may be given some original circuit design.

This type of job requires a basic knowledge of drafting methods which can be obtained in high schools or in trade school evening classes. Of course, if the technician wants to progress from there to engineering he will also have to acquire the training and education indicated for junior and associate engineers.

### Broadcast or television engineer



Courtesy Cleveland Institute of Electronics

The electronic technician looking for different and interesting work should investigate technical positions with radio broadcasting or television stations. He can work in the studios, the master control room, in the field or at the transmitter.

The studio engineer sets up microphones and cameras, and then controls gain and mixes audio or video channels. The master control engineer monitors and switches programs from different studios, field pickups or other remote locations. The field engineer puts on broadcast or television programs from remote or field locations. He uses portable or mobile equipment to make pickups from the ground, air or from ships.

Transmitter engineers must have an FCC operator's license since they handle the operation, maintenance and repair of one or more high-powered transmitters. Maintenance engineers handle the maintenance, troubleshooting and repairs of all radio broadcast or television electronic equipment, except perhaps in the area of the field engineer. The field engineer, distant from station facilities, must not only operate his field equipment, but also do all the maintenance and emergency repairs to insure "the show always goes on."

Training for all these areas is based upon a series of courses, usually given at a technical school, which progresses from electronic and electrical component basics to broadcast and television systems. In this type of work the electronic technician can usually start as a maintenance engineer and then, as he gains experience with equipment, assume the position at the station that fit his interests and temperament. Often he does

not have to take the formal training, obtaining all the information he needs by self-study and practice.

### Instructor



Courtesy RCA Institutes

A natural evolution from technician on a specific electronic subsystem or system is that of an instructor on that equipment. Having worked on the hardware, troubleshoot its defects and performed its maintenance, the technician should be able to tell others about it. However, teaching calls for certain capabilities:

- The teacher should be able to describe the components of the equipment and discuss their theory of operation. This is not as easy as it sounds, for often a man can keep a piece of equipment operational without knowing exactly how it works. Thus before doing any teaching the technician must review the equipment in detail to make sure that he understands exactly how it operates.

- The teacher must have the skill of imparting his knowledge to his students. Most companies using technical instructors provide a short course in methods of presentation which include handouts, visual aids and practice in the best ways of making the subject interesting.

Part of the instructor's job entails gathering the technical material he needs and compiling it in a student guide. This guide can vary from a series of outlines and line drawings to a detailed book of instructions, depending on the time allocated for its completion.

To do this effectively, the technician should be able to write on technical subjects and to organize his written material. He should also be able to create or arrange visual aids to enhance his presentation. Public speaking experience or training will also help to make his lectures informative, while courses on effective writing or technical writing will be invaluable in handling his written work.

Other tasks that the instructor must perform are: to write examinations, test his students, then grade the papers. An analysis of the results will then help him determine the success of the course. A number of training and evaluation methods can be learned by taking a basic education course.

### Training coordinator

Just as important as the instructor

on an educational program is the training coordinator. He plans and establishes the technical training program for his company. This entails determining the need for courses, obtaining course outlines, scheduling the courses, arranging for classrooms and necessary classroom equipment and insuring competent instructors are assigned. Once classes are organized he must enroll students, review student guides, even monitor classes to check on the quality of the instruction. Finally, he must establish and keep records on the results of examinations taken by the students so technical personnel can be fully trained to perform required tasks.

To do this type of work a technician must be able to plan and take care of details. Rather than performing many of the functions, he coordinates them. He must also be able to set up and maintain records and communicate with supervisors to make sure they are aware of the training program and have taken the steps necessary to make their workers attend the courses. For the evaluation of courses he should be capable of putting himself in the place of the students and, based upon his own knowledge of the technical subjects, determine whether the instructor is providing the explanation and details necessary to understand the subject. Here the technician's experience will provide a basis of reference. Educationally, a course in business management will be useful in providing data on planning and implementation of various types of tasks and handling personnel.

### Technical writer

If a technician has an aptitude for writing he can become a technical writer. Having worked with test procedures he should have a good idea of their form and content. Of course he does not necessarily have to originate them. Rough test procedures, or at least test specifications, are generally written by engineers. His task is then to place them in the step-by-step format used by technicians in testing equipment. With his experience he should have little difficulty.

Another technical writing area is handbooks and technical manuals. These are more complex than test procedures as they generally cover simplified equipment operation, theory of component functions, setup and operation of equipment and maintenance routines.

Normally the technical writer works with the engineers who designed the equipment and then with the men who set the first model in operation. He gathers a great deal of technical information from which he writes a rough draft of the manual. Once this draft has been reviewed by various project personnel, the writer corrects and finalizes the manual, making sure illustrations and photographs are included to clarify the text.

A number of courses and books on technical writing are available in evening education programs.

Probably one of the toughest jobs a  
(continued on page 90)



## Nothing replaces the reality of personal "in-class" instruction.

It builds your confidence through thorough preparation.

Professional success depends upon the quality of your training. You owe yourself the best. Anything less will be costly, takes much longer and requires more effort from you.

Take the shortest distance between you and your career. You'll be ahead in every way.

FREE LIFETIME PLACEMENT  
VETERAN APPROVED



# HEALD

## Engineering College

1215 Van Ness Ave.,  
San Francisco, California 94109

Oldest and Largest Institution of its kind in the United States. (Since 1863)

Please send information on:

**HEALD ENGINEERING COLLEGE**  
Bachelor of Science Degree Courses (36 months)

- Electronic Engineering
- Electrical Engineering
- Mechanical Engineering
- Civil Engineering  Architecture (42 months)

**HEALD INSTITUTE OF TECHNOLOGY**  
A division of Heald Engineering College

- Technology Diploma Courses
- Electronic Engineering Technician (FCC) (15 months)
- Radio-Television Technician (FCC) (15 months)
- Mechanical Drafting (12 months)
- Electrical Drafting (12 months)
- Structural Drafting (12 months)

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_  
Zip \_\_\_\_\_ Phone \_\_\_\_\_

Circle 20 on reader service card

# NEW PRODUCTS

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card on page 92 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.


**BUDGET AUTOMATIC TURN-TABLE**, Garrard model SL72B, includes all features of Garrard's top unit. Uses a low-mass tubular aluminum pickup arm that floats almost friction free on needle pivots. The adjustable counterweight is isolated from the arm to damp out resonances. Has three fingertip tabs for operation. One for automatic



play of up to six records, the second turns the motor on and off, and the third activates cueing and pausing, viscously damped in both manual and automatic modes, with viscous damped tonearm descent in the automatic mode for the first time in turntables. Also features an anti-skating device and a sturdy record support platform.—\$89.50—Garrard British Industries Co, Westbury, NY 11590

Circle 31 on reader service card

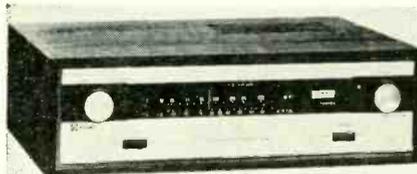**STEREO AM/FM TUNER KIT**, model KG-/96, Easy-to-follow instructions require soldering connections between circuit boards. Includes all silicon



transistors a tuning meter and edge-lit tuning dial. FM-IHF sensitivity, 3µV; AM, 50µV. Complete kit plus dipole antenna, \$79.95—Allied Radio Corp. 100 N. Western Ave., Chicago, Ill. 60680.

Circle 32 on reader service card

**FIX-IT TOOLS**, with special applications in the servicing of radio, TV and hi-fi sets include a pair of long (20 3/4") fixed handle, hollow-shaft nutdrivers with hex openings of 3/16" and 1/8" to simplify work on color TV tuners, bezels, and other components where the only access is through the back of the set. Two interchangeable 3/16" and 1/8" external hex Palnut driver shanks which fit all Xcelite 99 handles including Tee and ratchet



type are also offered.

For fast tip cutting of fine wires, a pair of miniature close-cutting diagonal pliers, 4 inches long, for electronic assembly operations as well as service work.—Xcelite Inc., Orchard Park, New York, NY, 14127

Circle 33 on reader service card


**STEREOPHONES**, model SP-8: Earcups are soft rubber cushions, headband has easy-to-adjust design, transducers are 2 inches. Frequency response is 25-18,000 Hz with 0.3 watts output, im-



pedance is 8 ohms. 11 ounces complete with 6-foot coiled cord and standard 1/4" phone plug. In kit form, \$8.95—EICO Electronic Instrument Co., 283 Malta St, Brooklyn, N.Y. 11208

Circle 34 on reader service card

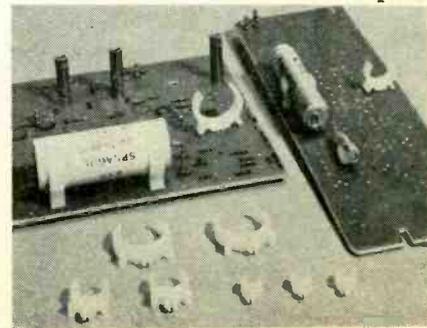**COMPONENT CLIPS—Hold Tite**, feature a split bulb at its base that locks into printed electronic assembly boards to hold and insulate capacitors, resistors, lamps, batteries, fuses and other parts.



# Special introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

	404/437 <b>SOURCEBOOK OF ELECTRONIC CIRCUITS</b> by J. Markus Pub. price, \$19.75 Club price, \$14.75		A494/754 <b>ENGINEERING MANUAL, 2/e</b> by R. H. Perry Pub. price, \$12.50 Club price, \$10.65
	391/432 <b>DISPLAY SYSTEMS ENGINEERING</b> by H. R. Luxenberg & R. L. Kuehn Pub. price, \$16.50 Club price, \$11.95		A523/401 <b>CHARACTERISTICS AND OPERATION OF MOS FIELD-EFFECT DEVICES</b> by P. Richman Pub. price, \$10.00 Club price, \$8.50
	A286/507 <b>SOLID-STATE ELECTRONICS</b> by R. G. Hibberd Pub. price, \$9.50 Club price, \$7.95		A037/604 <b>DIGITAL LOGIC AND COMPUTER OPERATIONS</b> by Baron & Piccirilli Pub. price, \$14.50 Club price, \$11.95
	389/608 <b>PRINCIPLES OF DATA COMMUNICATION</b> by Lucky, Weldon & Salz Pub. price, \$14.50 Club price, \$11.60		350/434 <b>DIGITAL COMPUTER USER'S HANDBOOK</b> by M. Klerer & C. A. Korn Pub. price, \$27.50 Club price, \$23.35
	A347/506 <b>ELECTRONIC DIGITAL TECHNIQUES</b> by P. M. Kintner Pub. price, \$12.50 Club price, \$10.65		A565/031 <b>AMPLIFIER HANDBOOK</b> by R. F. Shea Pub. price, \$37.50 Club price, \$29.50
			A637/377 <b>TRANSISTOR CIRCUIT DESIGN</b> by Texas Instruments, Inc., Staff Pub. price, \$16.50 Club price, \$13.95
			A126/070 <b>PRINTED CIRCUITS HANDBOOK</b> by C. F. Coombs, Jr. Pub. price, \$17.75 Club price, \$14.95
			A610/037 <b>MODERN COMMUNICATION PRINCIPLES</b> by Stein & Jones Pub. price, \$15.00 Club price, \$12.75
			A259/607 <b>COMMUNICATION SYSTEM ENGINEERING HANDBOOK</b> by D. H. Hamsher Pub. price, \$29.50 Club price, \$24.95

**ANY ONE**  
of these great professional books  
for only \$ **1.00**  
VALUES FROM \$9.50 to \$37.50

Special \$1.00 bonus book comes to you with your first club selection

## Save time and money by joining the Electronics and Control Engineers' Book Club

HERE is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

How the Club operates: Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections—or if you want no book at all for that month—you notify the Club by returning the convenient card enclosed with each *Bulletin*.

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

## MAIL THIS COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB  
582 Princeton Road, Hightstown, N.J. 08520

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. I am to receive the bonus for just \$1.00, and my first selection at the special Club price shown. These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books during the next two years at special Club prices (approximately 15% below list).

Write Code No. of  
bonus book  
here

Write Code No. of  
first selection  
here



Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

E 33145

Circle 61 on reader service card

## COMPUTER BOARD SPECIAL

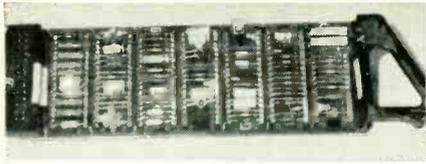

Stock No. B9082

Honeywell Computer boards, 4½"x12". Transistors, diodes, zeners, capacitors, precision resistors, heat sink, trimmers etc. 2 Different boards \$1.00. 3 lb.

Stock No. B9093

Honeywell Power Board contains 4 2N1137B 80 watt PNP power transistors, 8 Top Hat diodes, 8 precision resistors and 4 1N642 diodes \$1.25 ea. 2 lb.

Stock No. 9094

Honeywell Boards 5½" x 6". Loaded with late no. transistors, diodes, resistors and capacitors. 2 different boards \$1.00. 2 lb.

### COMPUTER GRADE CAPACITORS

B2040 Sangamo or Pyramid 4¼" x 1¾"		
4000 MFD 50V	.50	5/2.00
B2039 Pyramid 4¼" x 3" 6000 MFD		
75V	.75	3/2.00
B4016 FET Field Effect Transistor To-18		
25 Volt Source to Gate N Channel	.50	5/2.00
B4017 Tunnel Diode Similar to 1N3717	.50	5/2.00

**\$1.00 FREE WITH \$10.00 ORDER**

Lots of other items—send for free flier; all merchandise fully guaranteed. Please include postage; excess will be refunded.




**DELTA ELECTRONICS CO.**

BOX 1, LYNN, MASSACHUSETTS 01903  
Circle 62 on reader service card

Easy to remove. Dimpled sides assure a tight holding action. Clips snap into holds .125" to .156" diameter. Available in sizes ¼", ⅜", ½", and ¾". Made of virgin nylon, will accommodate over-size parts as well.—Lorain Tool & Mfg. Co., 1817 Iowa Ave., Lorain, Ohio 44052.

Circle 35 on reader service card

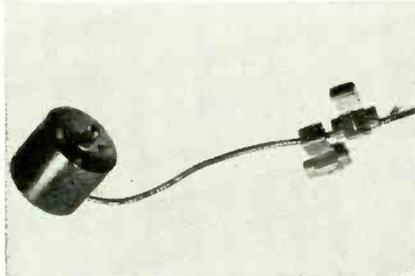**COLOR TV SERVICE ACCESSORY, model B-150.** Single-Brite gun control, permits the restoration of color picture balance when a single color gun weakens prematurely. The potentiometer-type device lets the technician adjust the bias between the G1 and G2 grid leads of the weakened gun, per-




mitting color intensity variation as needed for balanced picture. Easy installation requires two simple connections and no soldering.—Perma-Power Div., Chamberlain Mfg. Corp, 845 Larch Ave., Elmhurst, Ill. 60126

Circle 36 on reader service card

**FOGHORN/HAILER, Model MD-19** has 5 functions. Is a foghorn, boathorn,

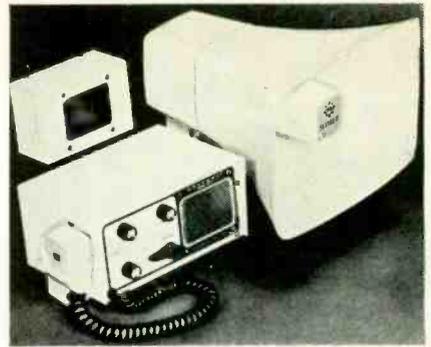hailer, listener, and with MDA-19-1 speaker becomes an intercom. Has push-to-talk mike and weather-proof speaker



with mounting base. Operates from 12 V. Includes mounting bracket and 20 ft. of cable. Kit \$84.95, accessory speaker \$9.50.—Heath Co. Benton Harbor, Mich.

Circle 37 on reader service card

**PROFESSIONAL TAPE DECK, model CAD5,** tape cassette recorder incorporates the Dolby-B noise reduction



processor as part of the record and play-

# LUBRA CLEAN

## ...A T.V. TUNER CLEANER THAT REALLY WORKS!

### MADE ESPECIALLY FOR TELEVISION TUNERS

Finally, a tuner cleaner that really works. Apply LUBRA CLEAN and let it do the work for you. Physical cleaning and polishing contacts is no longer necessary. Simply apply—and LUBRA CLEAN continues to polish and lubricate tuner contacts for months after all other cleaners and lubricants have failed. Sold at leading dealers and distributors for \$2.98 per tube.

**PATENTED TELEVISION TUNER CONTACT CLEANER**


**THE ONLY PATENTED TELEVISION TUNER CONTACT CLEANER**



## LUBRA CLEAN COMPANY

P. O. BOX 926 - MARTINSVILLE, VA. 24112 - PHONE (703) 638-1211

Circle 63 on reader service card

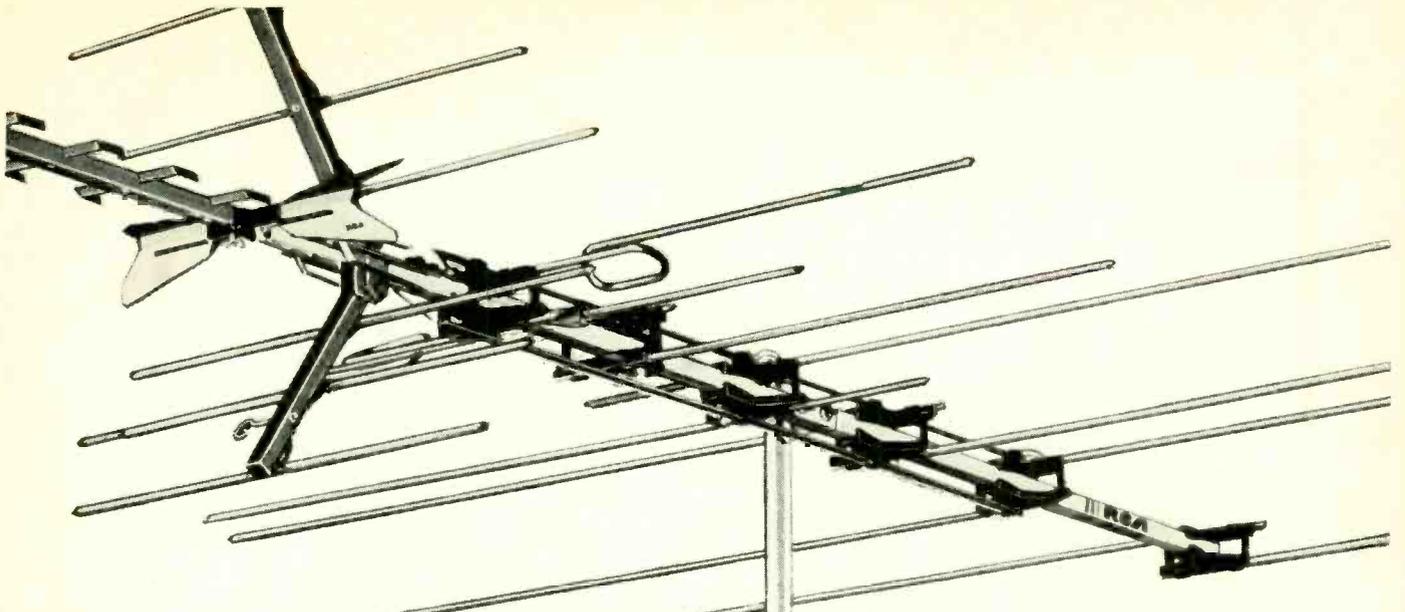

**The new Permacolor antenna from RCA has:**

**“Long-lasting” element/ feed line connections.**

**Waterproof, polypropylene insulators that pivot.**

**Integrated UHF bow tie.**

**Rigid, square boom.**

**Tough vinyl finish.**

**That ought to prove RCA is serious about the antenna business.**

So serious we've set up a new production facility at our Memphis plant. But before we manufactured a single antenna, our engineers literally started designing from scratch. The result? Permacolor.

Here are just a few reasons why RCA Permacolor antennas are different, and are an improvement over what you're now selling,

1. Durable connections/Perma-tuned circuits. All active elements (many perform more than one function) are solidly connected to a symmetrical aluminum feed line by riveted straps. This reduces reception failure due to flimsy or intermittent connections.
2. “Single unit” insulator/element. Insulators are polypropylene. Elements extend 5½ inches into the insulators. Elements and insulators pivot as a unit—lock in place—have no loose connections. No high stress points.
3. Bow tie and 110° corner reflector UHF Section integrated into a single downlead for better UHF reception.
4. Easy installation. Simply unfold and install. Permacolor antennas go up in one piece. No bag of bolts. Nothing to take apart and reassemble. Snap-off elements let you quickly tailor the antenna to reception requirements.
5. Tough, handsome blue and gold vinyl coating protects against weather and airborne chemicals.

The new RCA Permacolor Antenna is the antenna you can put up for good. See it now at your RCA Parts and Accessories distributor.

Parts and Accessories, Deptford, N.J.


**RCA**

# Introducing the world's only \$339 triggered scope.

Before you say you don't need a triggered scope, look what's happening to TV servicing: tubes are out, transistors and IC's are in.

With tubes you could play hit-or-miss, knowing the tube would take the overload. Try the same thing now, and good-bye transistors.

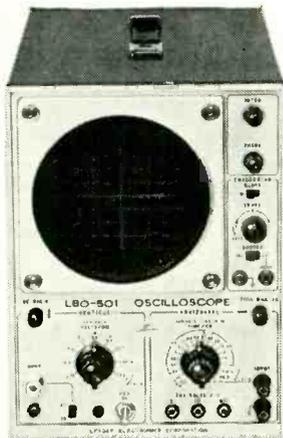For new-era circuitry, Leader introduces a new-era troubleshooter. A triggered scope, just like the ones the TV designers use.



Now the wave shape is locked in and continuously displayed. Now you can look at a waveform containing high and low frequency components. Now you can determine voltage directly and instantly.

Before you say \$339 is a lot of bread, look what it buys: Leader's LBO-501 5-inch triggered scope, with a bandwidth of DC to 10MHz and a solid state package.

Going like hotcakes at your Leader distributor.

## Seeing is believing.


### LEADER INSTRUMENTS

37-27 27th Street, Long Island City, N.Y. 11101, (212) 729-7411

Circle 64 on reader service card
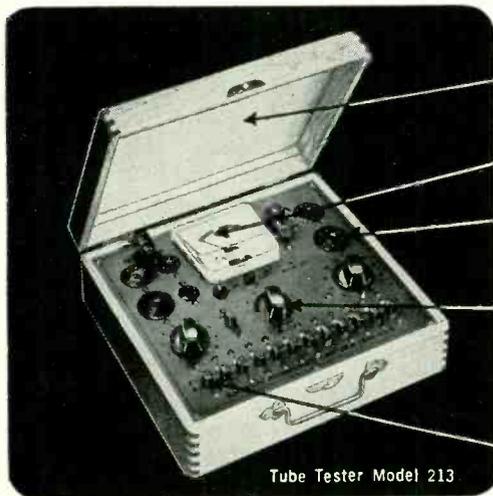
# NO COMPETITORS

Nobody else but **EMC** designs in so much value



Compact, lightweight portability. Use it on the bench or in the field.

Full-view meter gives direct, clear-cut quality indications.

Three heavy-duty controls for quick set-up of all tests. Check a fistful of tubes in the time it often takes to test one.

12 slide switches for individual selection of tube pins provides versatility in testing, prevents obsolescence.

Full complement of sturdy sockets accepts compactron (12-pin), nuvistor, novar, 10-pin, 9-pin, octal, loctal, and miniature tubes.

Precise programming. Only one socket per tube-base configuration prevents accidental plug-in.

THE MODEL 213 saves you time, energy, money ■ Checks for shorts, leakage, intermittents, and quality ■ Tests all tube types including magic eye, regulator, and hi-fi tubes ■ Checks each section of multi-purpose tubes separately ■ Gives long, trouble-free life through heavy-duty components, including permanently etched panel ■ Your best dollar value in a tube tester. Available in high-impact bakelite case with strap: \$33.40 wired; \$21.90 in kit form. Wood carrying case (illustrated) slightly higher.

# EMC

ELECTRONIC MEASUREMENTS CORPORATION  
625 Broadway, New York 12, New York  
Export: Pan-Mar Corp., 1270 B'way, N. Y. 1, N. Y.

EMC, 625 Broadway, New York 12, N. Y.  
Rush me FREE catalog describing all EMC value-loaded test instruments and name of local distributor.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

RE-10

back electronics. Extends in frequency response beyond 12.5 kHz. Acts as a compressor/expander only without its inherent weakness. The Dolby processor boosts low-level, high-frequency signals before they are recorded and then attenuates these signals in a mirror image during playback. Electronic speed control assures minimum speed variation with reduction of wow and flutter. Professional sliding potentiometers set recording level and the recording over-modulation light works in conjunction with the dual recording meters and flashes when the sound level is too high. Automatic digital counter with pushbutton reset, records and-plays back in mono and stereo, pushbutton switches for all functions.—\$229.95—Harman-Kardon, Inc. 55 Ames Court, Plainview, LI, N.Y. 11803

Circle 38 on reader service card


**COMPACT TV CAMERA, model TVC-500.** Develops clear, sharp monochrome pictures in video or rf signal at a switch-selected output. Video is viewed on a monitor but when the camera is switched to rf output, the pictures are displayed on a standard TV receiver. Simple screwdriver adjustment selects output frequency covering channels 2 through 6. Output level on a composite



signal is 1.4 V p-p, video is 1 V p-p. Rf output is greater than 29.5 dBmV (30mV) and impedance is 75 ohms. Horizontal resolution of center is 550 lines on video and 300 on rf output. Each 6 pound camera is supplied with a 25 mm F/1.8 lens. Wide angle and telephoto are available. \$325.00—Jerrald Electronics Corp., 401 Walnut St., Philadelphia, Pa. 19105

Circle 39 on reader service card

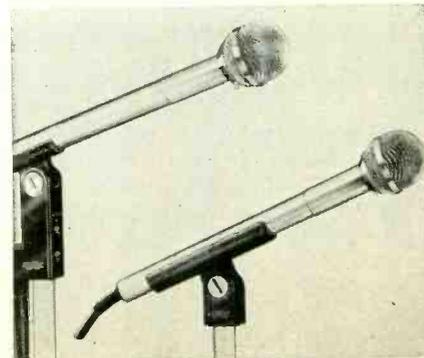
**PROFESSIONAL MICROPHONES, models 860 and 860s.** Ball-head omnidirectional dynamic mikes incorporate an integral "pop" and "blast" filter. The



RADIO-ELECTRONICS
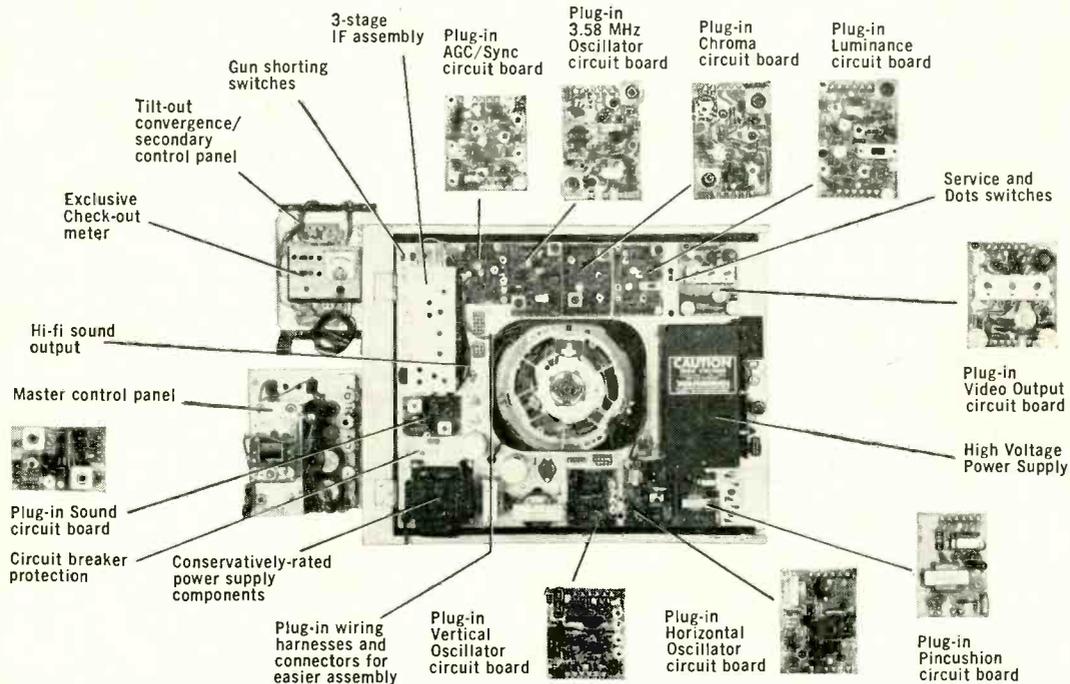
# Modular Color Television!

Exclusive Modular Design... Circuit Boards snap in and out in seconds for easy assembly, simple servicing



**New Expedited 48-Hour No-Charge Warranty Service Plan for Solid-State TV Modules!** Special service facilities have been established at the factory and all Heathkit Electronic Centers to expedite service and return of Solid-State TV circuit modules within two working days. During the 90-day warranty period, TV modules will be serviced or replaced with no charge for labor or parts. After the initial 90-day warranty period expires, TV modules will be serviced or replaced at a fixed charge of \$5.00 per module for labor and parts for a period of two years from date of original kit purchase.



Add extra convenience and versatility to your new GR-270 or GR-370 Solid-State Color TV with this new ultrasonic remote control kit. Lets you turn the set on and off, adjust volume, change VHF channels and adjust color and tint from the comfort of your chair. Assembles and installs complete in just a few hours and the built-in meter on the receiver makes final adjustment a matter of minutes.  
Kit GRA-70-6, 6 lbs. .... \$64.95\*

## Choose One Of These Handsome, Factory Assembled Cabinets

3 models in 295 sq. in.


**Luxurious Mediterranean Cabinet...** factory assembled of fine furniture grade hardwoods and finished in a flawless Mediterranean pecan. Statuary bronze trim handle. 30-1/32" H x 47" W x 17 3/4" D. Assembled GRA-304-23, 85 lbs. .... \$129.95\*



**Deluxe Early American Cabinet...** factory assembled of a special combination of hardwoods & veneers and finished in classic Salem Maple. 29-21/32" H x 37 1/4" W x 19 3/4" D. Assembled GRA-303-23, 67 lbs. .... \$114.95\*




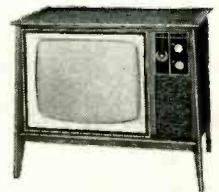**Contemporary Walnut Cabinet...** factory assembled of fine veneers & solids with an oil-rubbed walnut finish. 29-17/32" H x 35-13/16" W x 19 7/8" D. Assembled GRA-301-23, 56 lbs. .... \$74.95\*




3 models in 227 sq. in.

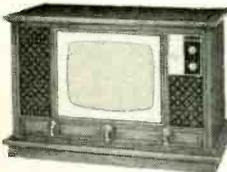
**Exciting Mediterranean Cabinet...** assembled using fine furniture techniques and finished in stylish Mediterranean pecan. Accented with statuary bronze handle. 27-31/32" H x 41 7/8" W x 19-9/16" D. Assembled GRA-202-20, 70 lbs. .... \$114.95\*



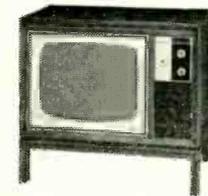**Contemporary Walnut Cabinet and Base Combination.** Handsome walnut finished cabinet sits on a matching walnut base. Cabinet dimensions 20-31/32" H x 31-7/16" W x 18 5/8" D. Base dimensions 7 3/4" H x 27 3/4" W x 18 5/8" D. Assembled GRA-203-20 Cabinet, 45 lbs. \$49.95\* GRS-203-6 above cab. w/ matching base, 58 lbs. .... \$59.95\*



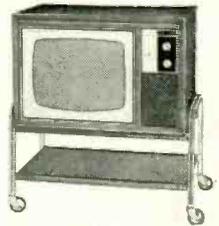**Handy Roll-Around Cart and Cabinet Combination.** Features the GRA-203-20 walnut cabinet plus a walnut-trimmed wheeled cart with storage shelf. Assembled GRA-203-20 Cabinet, 45 lbs. .... \$49.95\* GRA-204-20 Roll-Around Cart, 18 lbs. .... \$19.95\* GRS-203-5, Cart & Cabinet Combo, 58 lbs. \$59.95\*



**NEW FREE 1971 CATALOG!**  
Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, guitar amplifiers, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

**HEATHKIT**  
a Schlumberger company

HEATH COMPANY, Dept. 20-10  
Benton Harbor, Michigan 49022

Enclosed is \$ \_\_\_\_\_, plus shipping.

Please send model (s) \_\_\_\_\_

Please send FREE Heathkit Catalog.  Please send Credit Application.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

\*Mail order prices; F.O.B. factory. Prices & specifications subject to change without notice. CL-392



It's yours  
**FREE**  
for the  
asking!



**BA**  
GIANT 260 PAGE  
1971  
RADIO-TV  
ELECTRONICS  
CATALOG


YOUR BUYING GUIDE FOR EVERYTHING IN ELECTRONICS!

Write to:  
BURSTEIN-APPLEBEE CO.,  
DEPT. RE-10, 3199 MERCIER ST.,  
KANSAS CITY, MO. 64111

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip Code \_\_\_\_\_

Circle 69 on reader service card

## UNEXCELLED! THE UVM ANTENNA

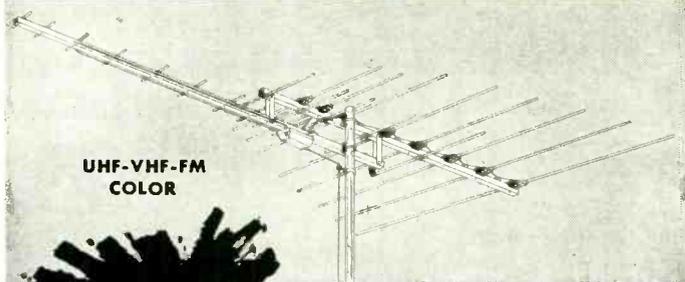

UHF-VHF-FM  
COLOR

**COMPLETELY  
NEW!**

Combination  
UHF-VHF-FM Antennas

*for superior performance.*

Tuned and engineered featuring a LOG PERIODIC VHF section incorporating a PATENTED MAGNETIC WAVE design for UHF. Discriminate between desired signal and unwanted noise. An absence of minor lobes and extremely high front to back ratio are characteristics of these antennas. Mechanical features include all new fittings and special alloy aluminum tubing for added strength. Six models available.

Write or phone for complete information.

**S & A ELECTRONICS, INC.**

210 W. Florence St. Phone (419) 693-0528 Toledo, Ohio 43605

Circle 70 on reader service card

# COMING NEXT MONTH

NOVEMBER 1970

## ■ Lowdown on Alarm Systems

Quick guides to which system is best suited to your application. Plus how they work details and installation tips for everyone.

## ■ Mini-Kits Are Fun

You name the circuit—it's probably available as a mini-kit. These low-cost circuits are a fun-packed introduction to electronics.

## ■ Careers With Computers

A look at the opportunities in the computer field today. Based on an interview with Ken Strandberg, manager of G-E's Field Engineering Department.

## ■ PLUS:


Jack Darr's Service Clinic  
How To Putter With The PUT  
Power Tool Reference Manual

**MULTIPLEX GENERATOR**  
(continued from page 67)

an access hole in the chassis to permit external adjustment of T4's slug. This allows changing the oscillator frequency to a spot where no local station is operating.

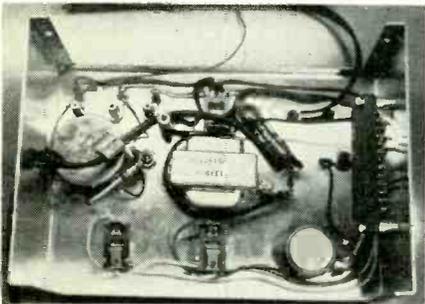
**Using the generator**

The composite modulation output is used mainly for applying the stereo signal to a multiplex demodulator for checking it separately. For this, the 19-kHz level is not calibrated and must be set to a predetermined level which the discriminator will supply from broadcast stations. This is also true for the remaining composite signal level. The audio input levels to the generator must be kept below about 1.5 Vrms or saturation occurs.



**POWER TRANSFORMER AND JACKS** are on front panel with the pots and switches.

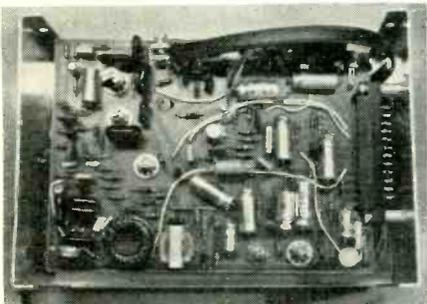Receiver separation versus frequency can be checked between 300 Hz and 20 kHz with this generator. This also provides a convenient way to determine if the receiver de-emphasis circuit is correct. The easiest way to measure receiver separation is to apply an audio tone to only R or L of the generator and measure the ratio of outputs on L and R at the receiver.



**COMPONENTS ON PLUG-IN BOARD** are visible when the rear cover is removed.

The rf VCO in this unit is very convenient. It lets you check the effect of i.f. amplifier selectivity on overall separation. It also lets the technician adjust a multiplex unit incorporated in the radio without disconnecting it. A direct connection from the rf output is not required as the receiver will pick up the signal from a few feet away.

This stereo generator will result in a professional alignment job on any FM stereo receiver. Its relatively low cost and versatility make it a valuable piece of test equipment for any technician.

R-E

**Precision**  
**S**  
**Line**


Precision has led the field in quality and dependability for 25 years.

**Greatest value in sound**  
**for every PA application**

• Most trouble-free line in the industry, Precision offers a complete range of amplifiers in every power range including mobile, and a complete line of accessories. From the smallest office to large auditorium or industrial installations, Precision gives maximum flexibility and performance.



S-10

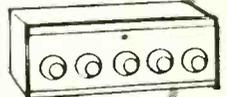

S-30MAC

S-25-30  
60-100

**DIVISION OF PRECISION ELECTRONICS, INC.**  
9101 KING STREET, FRANKLIN PARK, ILLINOIS 60131

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_


**MAIL THIS COUPON NOW!**

Circle 71 on reader service card

**Unsolder it**  
**with the**  
**Endeco**  
**300**

**Pencil**  
**Desoldering**  
**Iron**

MODEL  
300

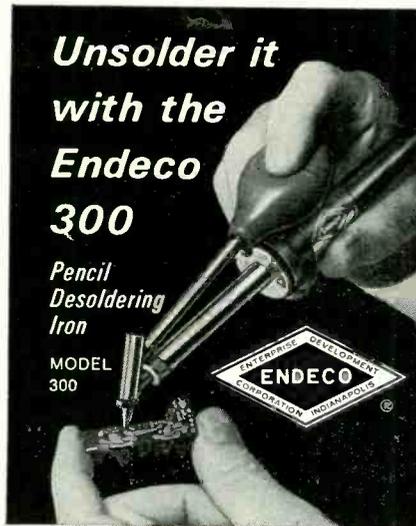

**Removes miniature soldered components in seconds—without damage**

Hollow tip fits over connection; vacuums all solder for easy removal of component. Leaves terminals and mounting holes clean. Then, with 360° contact, it resolders faster, better than regular irons. Handles miniature and standard components in PC boards and conventional wiring. Self-cleaning. All parts replaceable. 40 watts, 120-v. Standard tip supplied, 5 other tip sizes available. Pays for itself. \$11.95 net East of the Rockies. ®

Larger model available. See your distributor or write:

**ENTERPRISE DEVELOPMENT CORPORATION**  
5127 E. 65th St. • Indianapolis, Ind. 46220

Circle 72 on reader service card

**PUNCH #2** **TUN-O-FOAM**  
**KEEPS CLEANING**  
**& LUBRICATING CONTACTS EACH**  
**TIME THE CHANNEL IS CHANGED**



**IT REALLY WORKS!**


**6 MONTH NO CALLBACK GUARANTEE!**

**CHEMTRONICS** **1260 RALPH AVE.**  
**BROOKLYN, N.Y. 11236**

For Export: Roburn Agencies Inc., New York, N.Y.

Circle 73 on reader service card

# This Christmas Give Security

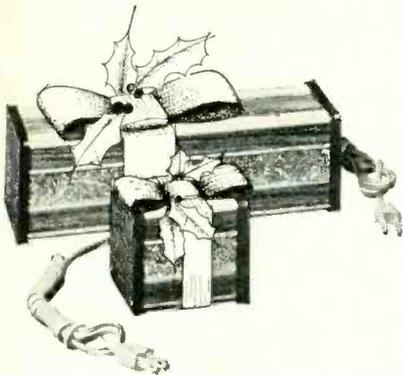

Gift selection can be a problem. This year give a gift that will be truly appreciated . . . **Security.** DeltaAlert ultrasonic intrusion detection security.

Burglary and vandalism are constant threats to your home, office or shop. With DeltaAlert on the job, you have dependable and economical security. A silent ultrasonic blanket guards 150 to 300 square feet of critical space in the home or business.

When the ultrasonic blanket is disturbed by motion the system is activated, lights go on, and the separate DeltaHorn emits an ear-splitting noise . . . frightening off even the boldest intruder.

These sturdy units, finished in handsome walnut veneer, are maintenance free and plug right into the wall socket. The DeltaHorn plugs directly into the DeltaAlert. Small, the DeltaAlert is only 10 $\frac{3}{8}$ " w x 3 $\frac{1}{4}$ " d x 3 $\frac{1}{4}$ " h and the DeltaHorn, 3 $\frac{1}{4}$ " square, the units blend inconspicuously into your decor.

This Christmas, give a lasting gift of security . . . security for your friends, your family and yourself.

Order your DeltaAlert Security today!

DeltaAlert Only **\$69<sup>95</sup>** ppd.  
DeltaHorn Only **\$24<sup>95</sup>** ppd.

"Delta Products, One Of America's Finest Names In Electronics"

DP 70-21

**DELTA PRODUCTS, INC.**

P.O. Box 1147 RE / Grand Junction, Colo. 81501  
(303) 242-9000

Please send me literature immediately:

Enclosed is \$ \_\_\_\_\_  Ship ppd.  Ship C.O.D.

Please send: \_\_\_\_\_ DelAlert(s) @ \$69.95 ppd.

Please send: \_\_\_\_\_ DeltaHorn(s) @ \$24.95 ppd.

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 74 on reader service card

## POWER SUPPLIES

SINGLE: PS-61C  
DOUBLE: PS-62C  
TRIPLE: PS-63C



- Economical, continuously variable power supplies by BLULYNE.
- Modern walnut finished cabinets with beige panels.
- Excellent regulation and ripple characteristics.
- Single, dual, and triple units available.
- Short circuit protected—electronic current limiting. Short circuit cannot harm unit.
- Grounding cord for added safety.
- Floating outputs on all units—ground either plus or minus.
- Uses include life testing, production line testing, schools, labs, experimentors use, instructors, technicians, engineers, troubleshooting, battery elimination, and many more valuable uses.

### PS-61C Single Unit

Plus or Minus 1—15 VDC, 0-700 mA. Usable to 1000 mA.

Ripple: less than 0.005Vrms max.

### PS-62C Double Unit

Same characteristics as Single unit above for EACH of two outputs.

Two completely independent supplies to be used in any combination.

Up to 30 VDC—Up to 2 Amps.

### PS-63C Triple Unit

Same characteristics as Single unit above for EACH of three outputs.

Three completely independent supplies to be used in any combination.

Up to 45 VDC—Up to 3 Amps.

All supplies are fully safety designed.

PS-61C ..... \$49.95  
PS-62C ..... 74.95  
PS-63C ..... 99.95

Write for illustrated literature on this and other BLULYNE products.

Blulyne Electronics Corporation  
Dept. R. 3 Sand Springs Road  
Williamstown, Mass. 01267

Circle 75 on reader service card

# Olson

## ELECTRONICS

# FREE

## Catalog

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS Fantastic Value Packed Catalog — Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

GIVE ZIP CODE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON ELECTRONICS**  
Dept. LJ, 260 S. Forge Street  
Akron, Ohio 44308

Circle 76 on reader service card

# Service

By JACK DARR  
SERVICE EDITOR

## Signal Tracing Transistor TV

I've read a lot of articles, including some of yours and I still haven't found an easy way to check a transistor TV, stage by stage, with only a vtvm. I've been doing this for years in tube TV's. Why can't I do it in solid-state stuff?—H. J., Highland Falls, N.Y.

Several reasons. First and most important, is the different *method of construction*—PC boards vs terminal-point wiring. Second, the transistors are soldered in. Can't pull 'em and replace with a known good one without a lot of trouble.

So! Use the same methods you've used for so long, but use a different *test-instrument*. The scope! It is just as simple as a vtvm. When you find out where the *signal stops*, then use the vtvm.

## Dark Bars On Left Of Raster

I have a Zenith 14N27 portable, which has a dark bar at the left side of the raster. I can move it back and forth with the horizontal hold control. It has what looks like vertical retrace lines near the top of the screen. My customer says this has been there ever since he got the set.

All tubes have been replaced, parts checked, shields tightened, etc.—B. T., Bayonne, N.J.

After you recheck the horizontal afc and run a complete horizontal oscillator/afc setup adjustment, and check the afc tube grid bypass capacitor, check the yoke. In a very few cases, we've found that a defective yoke can cause troubles something like this. Never pinned down the exact cause; could be too much air-gap or something in one of the windings, but a new yoke often cures it.

## Too Much Capacitance?

Following a suggestion of yours in the Service Clinic quite a while ago, I added more capacitance to the filters of a TV set to get out a 120-Hz humbar in the picture. I had to add 400  $\mu$ F, but I got rid of it. Isn't this too much?—A.D., N.J.

Not if you got rid of the hum! There's no such thing as too much capacitance in a filter circuit; at least not if you still have hum-bars which are a definite indication that there isn't enough capacitance in the circuit.

It's possible that if you took every one of the original capacitors out of the circuit and checked them very

# Clinic

carefully you'd find high power-factor in several of them. This reduces the "filtering efficiency" of the unit. However, if the operation is satisfactory with the added capacitance, I'd take it.

## Open Transistor?

*I'm studying TV repair. The other day I replaced an open transistor in the output of a stereo amplifier. It wouldn't work! Collector voltage read normal. I took the new transistor out and it tests ok!—R. G., Tulsa, Okla.*

Most likely possibility (because it happened to me only the other day!) is a completely bad contact on the lug which makes the collector connection on the output transistor collector! Most of these are bolted in, and any oxide, coating, etc. on the case of the transistor (the collector contact) will keep the solder-lug from making good contact.

Test from the case of the transistor instead of the lug. If you can't get any voltage on it, put a good sharp lockwasher between the lug and the case and tighten well, or scrape the case clean at that point.

## Super Hearing Aid

*I have a customer who wants to get a mike and amplifier, battery-operated, with a "rifle-type" mike that he can point at the preacher, so he can hear church services. Could I use one of the little cassette tape-recorders, or something like that?—A. A., Vienna, Va.*

Doubt if one of those little recorders would have enough gain. Better idea would be to use a small IC amplifier. Motorola has one in their HEP IC booklet, called a "Super High Gain Amplifier." It uses a HEP-580 IC. Should have ample gain to drive a single earphone from any good mike.

The whole thing could be mounted in the case from a junked transistor radio, with the batteries, using the original earphone jack. **R-E**

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. S., New York 10003.

## DON'T SETTLE FOR A HIT AND MISS IGNITION SYSTEM



### Install a JUDSON ELECTRONIC MAGNETO


It offers the combined advantages of both the standard transistorized and capacitive discharge systems in one simplified patented circuit. Provides better performance, a smoother running engine and keeps your car in tune. Installed in twenty minutes.

Write Today for Literature

**JUDSON** RESEARCH & MFG. CO. CONSHOHOCKEN, PA. 19428

Circle 77 on reader service card

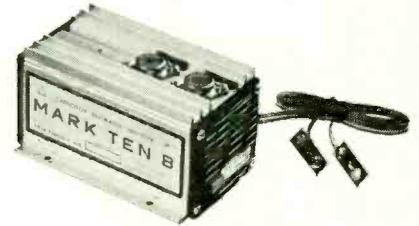**Mark Ten B... the gift for the man who has everything. It's new! It's practical! It's different!**



Christmas comes but once a year, but car problems continue year round. So why not give the gift that provides continuing pleasure and satisfaction ... the Mark Ten B CD System.

Keeping your car in tune is important to the life of the car. What did your last tune-up cost? More and more, tune-ups are becoming a major maintenance expense, costing \$60 and up. Now you can eliminate two out of three tune-ups (that's real savings). Delta's all new Mark Ten B CD System is made especially for foreign cars and modern American engines suffering from smog control devices, rough idle and poor fuel mix. The system is completely sealed, with handy switch for instant conversion. Quick installation — no rewiring. The Mark Ten B actually pays for itself in dollars saved.

You may even want to give yourself a Mark Ten B Christmas.

Order today!

"Delta Products, One Of America's Finest Names In Electronics"

Mark Ten B Only **\$59<sup>95</sup>** ppd.  
(12v neg only)

Standard Mark Ten **\$44<sup>95</sup>**

GET BETTER TV RECEPTION  
ELIMINATE SNOW WITH

## TUN-O-BRITE

the heavy duty tuner spray with built-in polishing action!



**CHEMTRONICS**

1260 Ralph Ave.  
BROOKLYN,  
N.Y. 11236

Circle 90 on reader service card

DP 70-22  
**DELTA PRODUCTS, INC.**  
P.O. Box 1147 RE / Grand Junction, Colo.  
(303) 242-9000

Please send me literature immediately:   
Enclosed is \$\_\_\_\_.  Ship ppd.  Ship C.O.D.  
Please send:  
\_\_\_ Mark Ten B @ \$59.95  
\_\_\_ Standard Mark Ten (Assembled) @ \$44.95  
\_\_\_ 6 Volt: Neg. Ground Only \_\_\_ Positive Ground  
\_\_\_ 12 Volt: Specify \_\_\_ Negative Ground  
\_\_\_ Standard Mark Ten (Deltakit) @ \$29.95  
(12 Volt Positive Or Negative Ground Only)  
Car Year \_\_\_\_\_ Make \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City/State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 74 on reader service card

# Find the trouble faster...



## with Triad's latest Service Aid No. 5: "Fast Ways to Restore a Raster."

Here's an easy-to-read 8-page Service Aid which will get you to the heart of the trouble faster than any treatise of its type for professional TV servicemen. Uses a direct and comprehensive approach to horizontal and high voltage problems. Helps you find the trouble and tells you how to correct it. Has many service tips that will prevent call-backs. Includes valuable information on both color and black-and-white TV.

Write for your copy today — and also for Service Aid No. 4 on "Understanding Related Circuits — Multiple Trouble." Previous Service Aids (or PTM's) are either being revised or have been updated into No. 5. See your Triad Distributor for all your replacement transformer needs, and get the Triad Catalog & Replacement Guide while you're at it. Triad Distributor Division, 305 North Briant Street, Huntington, Ind. 46750.



**NEW TRIAD  
1971/72  
CATALOG AND  
REPLACEMENT  
GUIDE**

**Triad Distributor Division  
of Litton Industries**

Circle 78 on reader service card

### 4 CHANNEL STEREO (continued from page 35)

cities—Boston, New York and San Francisco—FM stations have used three different pairing and placement techniques, each for its own good reasons. In Boston the four microphones, which carried live concerts of the Boston Symphony Orchestra, were ranged more as a "curtain of sound" than as a true quad pickup. One station used the left and right mikes placed at the left half of the stage, while the other took left and right channels for the right half of the stage. This way, both stations had a two-channel stereo signal of sorts, even though the total quad effect lacked true surround sound placement, directivity and separation. The stations involved were educational station WGBH-FM and commercial WCRB-FM.

In New York, FM Guide Publisher Harry Maynard introduced quad on his weekly show for stereo buffs, "Men of High Fidelity." New York City-owned WNYC-FM carried the front left and right channels and Columbia University station WKCR carried the rear two channels. Understandably, the WKCR signal left something to be desired for the majority of listeners who couldn't set up two complete FM stereo systems in their living rooms. But WNYC-FM did provide a full two-channel (and mono) signal for conventional listening setups. This program and its successors were rebroadcast weekday afternoons so stereo dealers could demonstrate quad in their showrooms.

In San Francisco, a one-shot broadcast by Pacifica station KPFA and Metromedia's KSAN carried left front and rear on one station; right front and rear on the other. The thinking here was that the stereo dealer could most easily arrange two stereo consoles along opposite walls of his store. Actually, it looks like an ideal arrangement to keep either station from gaining a competitive edge during the experimental quadcast. Later, the Bay Area quadcast gauntlet was picked up by KLOL and KRON, both commercial stations, who interestingly use the same split as in the KPFA/KSAN quadcasts. The Chicago and Cleveland areas are next on the list, and one program packaging company is selling a single syndicated one-hour quad concert by the Boston Symphony Orchestra.

The quad disc is the biggest question mark of all. There are private inventors and engineers with huge laboratories all bent on a single quest—the single-groove quad disc. They're convinced it's possible, just as they were convinced in 1956 that a true two-channel program could be put into a

**World's  
Number  
One  
Trusted  
Name  
Brand**

**"NO NOISE"**

- TECHNICIANS' FIRST CHOICE  
OVER CHEAPER SUBSTITUTES!**
- VOLUME CONTROL & CONTACT RESTORER
  - TUNER-TONIC with PERMA-FILM
  - EC-44 FOR ELECTRICAL CONTACTS
  - TAPE-RECO HEAD CLEANER
  - FRIGID-AIR CIRCUIT COOLER

All Guaranteed Non-Flammable, No Carbon Tet, Non-Toxic, Non-Drift Tuner Cleaner And Guaranteed Not To Affect Plastics.

The Only Brand Perfect For  
Color TV and Black & White

FREE extender assembly for pin-point application supplied with ALL NO-NOISE PRODUCTS.

**Electronic Chemical Corp.**  
813 Communipaw Ave. / Jersey City, N. J. 07304

Circle 79 on reader service card

## Build this magnificent Schober Theatre Organ

for only

\*\$1730!



\*Includes finished walnut console. Amplifier, speaker system, optional accessories extra. Only \$1258 if you build your own console.

You couldn't touch an organ like this in a store for less than \$3500—and there hasn't been a musical instrument with this vast variety of genuine Theatre Organ voices since the days of the silent movies! If you've dreamed of the grandeur of authentic big-organ sound in your own home, you won't find a more satisfying instrument anywhere—kit or no kit.

You can learn to play it. And you can build it, from Schober Kits, world famous for ease of assembly without the slightest knowledge of electronics or music, for design and parts quality from the ground up, and—above all—for the highest praise from musicians everywhere.

Send right now for your copy of the full-color Schober catalog, containing specifications of the five Schober Organ models, beginning at \$499.50. No charge, no obligation—but lots of food for a healthy musical appetite!

The Schober Organ Corp., Dept. RE-83,  
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog and free 7-inch "sample" record.
- Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 80 on reader service card

RADIO-ELECTRONICS

single record groove. They may be right. But there are just as many skeptics around now for quad as there were for stereo in 1956. They may be right.

So far, whatever results that have been publicly demonstrated have left much to be desired. The long-awaited public unveiling of Peter Scheiber's disc came at the March AES meeting before standing-room-only crowd in RCA's spanking-new recording studios. Those of us who heard it came away convinced that the Schieber disc just doesn't have what it takes for true quad.

Scheiber's technique is supposed to condense quad's four channels into two stereo channels that are fully compatible with all conventional types of playback equipment. A master disc would be cut with the same Westrex stereo cutting head, and the record would be played back with any conventional stereo cartridge—even the cheapest crystal types. The output signal would be processed through a black box (patent applied for) decoder which would have four-channel output to feed a quad amplifier (or two stereo amplifiers if you will).

The same technique would compress quad into two ordinary stereo tracks on tape or into an FM station's conventional two-channel FM stereo broadcast. The secret of all playback would be in the little black box decoder. Equipment without the decoder would simply play back a normal two-channel program. The whole idea sounds especially captivating since its compatibility would eliminate a lot of headaches and retrofitting now seen as needed for quad playback.

The system, alas, isn't all it's cracked up to be. In Scheiber's own words, it's a "psycho-acoustic effect." Purists take note: it's a **psycho-acoustic** effect; not the real thing. But you don't have to be a purist to be convinced of the system's shortcomings.

What it does is place the apparent sound source at any two selected speakers out of the four at a given instant, with some other assorted sounds coming from the other two, with lots of spillover. The Scheiber system is perhaps best described as "2½ channels of stereo." It's definitely not true quad.

So the search goes on. Familiar names are in the fray again. Jerry Minter is back with his multiplexing technique. Columbia Records is working on something that's still a closely guarded secret. And there are others, names that may someday be household words, or simply inventors that won't quite make the grade.

In the meantime, the smart money's on tape and FM. **R-E**

# NEW SEMICONDUCTORS

## MOS IC FOR TV SYNC

The HSUB0525 is the first MOS IC developed for digitally controlling the horizontal and vertical deflection in TV receivers. It takes a 1.08-MHz crystal oscillator signal and divides the frequency down to produce accurate and stable horizontal, vertical and composite blanking pulses while eliminating variable resistors and potentiometers in the control circuitry of the horizontal and vertical generators.

The IC is particularly suited to

cable or closed-circuit TV and TV test instruments such as bar and raster generators, as well as for CRT character displays. It is compatible with commercial TV sync systems when used in conjunction with proper vertical sync separators.

This new Hughes IC is housed in a standard 10-lead TO-5 package and is priced at \$15.00 each in 100-or-more lots. For further information, contact Hughes MOS Div., 500 Superior Ave., Newport Beach, Calif. **R-E**

# FREE!

## Lafayette's 1971 Golden Jubilee Catalog



**50th**  
**LRE**  
**anniversary**

**468 PAGES**

*Your 1st Guide  
To Everything  
in Electronics*

- Stereo/Hi-Fi Components • Musical Instruments and Amplifiers
- Photography Equipment • Ham and CB Gear • Public Address Systems
- Tools and Test Equipment • Educational and Optical Equipment
- Black and White/Color Televisions • Police and Fire Monitor Receivers
- Books and Parts

Plus Thousands of Additional Items



Send For Your Free 1971 Lafayette Catalog Today!

LAFAYETTE Radio ELECTRONICS Dept. 17100  
P. O. Box 10, Syosset, L. I., N. Y. 11791

Mail This  
Coupon Today  
For Your  
1971 Catalog  
No. 710

Send Me the Free Lafayette Golden Jubilee 1971 Catalog 710  
Name ..... 17100  
Address .....  
City .....  
State ..... Zip .....  
(Please include your zip code)

Circle 81 on reader service card

# MARKET CENTER

## ELECTRONICS

**TUBE sale.** To 90% off all brands. Laboratory-type CCTV oscilloscopes, generators, tubes testers. 85% off. Model PD-160 \$700.00; you pay \$105.00. Mail order only. Free list. J. Knight TV, 612 Gaines Ave., Hot Springs, Ark. 71901

**RECEIVING & Industrial Tubes, Transistors.** All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request **FREE** Giant Catalog and **SAVE!** ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

**INTEGRATED CIRCUIT KITS**—Free Catalog. **FRAZIER & ASSOCIATES**, 3809 Surfwood Road, Malibu, Calif. 90265.

**CONVERT** any television to sensitive big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **RELCO-A25**, Box 10563, Houston, Texas 77018

**B & K**, Sencor test equipment, discount prices. Free catalog and price sheet. **FORDHAM RADIO**, 265 East 149th Street, Bronx, NY 10451

**COLOR Organ Kits** \$3.25 to \$7.50. Power Supplies \$2.75. Catalog. **MURPHY**, 204 Roslyn Ave., Carle Place, N.Y. 11514

**RADIO and TV Tubes** 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free Catalog. **CORNELL** 4217-E University, San Diego, California 92105

**DISCHARGE Ignition, Photoflash.** Free catalog parts, kits. **TRANSPARK**, Carlisle, Mass. 01741

**TUBES**—Lowest prices. Foreign-American. Obsolete, receiving, special purpose, transmitting tubes. Send for tube, parts catalog. **UNITED RADIO COMPANY**, 56-R Ferry St., Newark, N.J. 07105

**JAPANESE NEW PRODUCTS MONTHLY!** \$1.00 Refundable. **DEERE**, 10639 Riverside, North Hollywood, Calif. 91602

**EXPERIMENTERS**, Radio control enthusiasts, Bramco five tone reed relays. Standard frequencies. Brand new, boxed \$4.00 each. **E.S.P.**, 8913 Cermak Rd., N. Riverside, Ill. 60546

## AUDIO - HI-FI

**CASSETTES CASH IN ON** a tremendous All-year round market. Send for lowest pricing and details. Include \$1.00 for 2 cassettes samples. **DICATION PRODUCTS**, P.O. Box DPK, Hallandale, Fla. 33009

**FM BACKGROUND MUSIC ADAPTER.** Compact line-powered **MUSICON** MX-7 plugs into any FM Tuner or Receiver. Optimized design guarantees 5 years of commercial-free music without adjustments! Works with your equipment or we refund. Send stamped self-addressed envelope for SCA stations in your area. Lowest price ever . . . \$35 postpaid from **K-LAB**, Box 572R, S. Norwalk, Conn. 06856

**STEREO TAPE TRANSPORT**—7" reel—2 speeds—pause control—made for famous manufacturer—50 to 15,000 Hz with rec/play and erase heads. Without case. Send M.O. or check for \$19.50 to **STEREO CENTER**, 218 Columbia St., Utica, N.Y. 13502. \$2.50 for prepaid shipping and insurance.

**CLASSIFIED COMMERCIAL RATE** (for firms or individuals offering commercial products or services). 70¢ per word . . . minimum 10 words.  
**NON-COMMERCIAL RATE** (for individuals who want to buy or sell personal items) 30¢ per word . . . no minimum.  
**FIRST WORD and NAME** set in bold caps at no extra charge. Additional bold face at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for December issue must reach us before Oct. 5.

## CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .30 Non-Commercial Rates } = \$ \_\_\_\_\_  
 { @ .70 Commercial Rate } = \$ \_\_\_\_\_  
 No. of Words in bold caps @ .10 = \$ \_\_\_\_\_

Total Enclosed \$ \_\_\_\_\_

Insert \_\_\_\_\_ time(s)

Starting with \_\_\_\_\_ issue

Payment must accompany order unless placed through accredited advertising agency

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 200 PARK AVE. SOUTH, NEW YORK, N.Y. 10003

## ADVERTISING INDEX

**RADIO-ELECTRONICS** does not assume responsibility for any errors which may appear in the index below.

READER SERVICE CARD NO.	PAGE
Allied Radio Corp.	75
Blulyne Elec. Corp.	84
Brooks Radio & TV Corp.	76-7
Burstein-Applebee Co.	82
Castle TV Tuner Service	Cover III
Channel Master	15
Chemtronics	83
Chemtronics	85
Cherry Electrical Products Corp.	12
Cleveland Institute of Electronics	28-31
Compusad, Inc.	92
CREI, Home Study Division of McGraw-Hill Book Co.	65-6
Crystek, Division of Whitehall Electronics	92
Delta Electronics Co.	72
Delta Products Inc.	84, 85
Electronic Chemical Corp.	86
EMC, Electronic Measurement Corp.	74
Enterprise Development Corp.	83
(Garrard) British Industries Corp.	Cover II
Grantham School of Electronics	1
Heald Engineering College	70
Heath Co.	78-81
International Crystal Mfg. Co.	Cover IV
Judson Research & Mfg. Co.	85
Lafayette Radio Electronics	87
Lakeside Industries	92
Leader Instrument Corp.	74
Lechtrotech, Inc.	14
LubraClean Co.	72
Mallory Distributor Products Co.	5
Master Appliance Co.	12
McGraw-Hill Book Co.	71
Mosley Electronics, Inc.	76
Music Associated	92
National Radio Institute	8-11
National Technical Schools	18-21
Olsen Electronics, Inc.	84
Precision Electronics	83
Precision Tuner Service	17
Raytheon Co.	22
RCA Institutes	54-57
RCA Parts & Accessories	73
Rye Industries, Inc.	77
S & A Electronics	82
Sams & Co., Howard W.	27
Schober Organ Co.	86
Sencore	16
Shure Bros., Inc.	23
Sonar Radio Corp.	14
Sony Corp. of America	7
Spectrum Products Co.	26
Sylvania	32
TEAC Corp. of America	13
Triad Distribution Division of Litton Inds.	86
United Technical Institute, Division of Career Academy	25
Xcelite Inc.	24
<b>MARKET CENTER</b>	<b>88-91</b>
Edmund Scientific Co.	88
Fair Radio Sales	
Mongram Publishing Co.	
Park Electronic Products	
Polypaks	
Solid State Sales	
Supreme Publications	
Surplus Center	
<b>SCHOOL DIRECTORY</b>	<b>89</b>
Edison Technical College	
Tri-State College	
Valparaiso Technical Institute	

It's The Biggest! It's The Most Popular PENNY SALE IN THE INDUSTRY!


# ONE CENT



**99¢**  
Each  
2 for \$1.01

Type	Description	Case	Type	Description	Case
<input type="checkbox"/> 900	Buffer	F	<input type="checkbox"/> 960	Dual buffer	5
<input type="checkbox"/> 900*	Dual Buffer	F	<input type="checkbox"/> 923/940	J-K flip flop	5
<input type="checkbox"/> 903	Dual 3 input gate	F	<input type="checkbox"/> WC210**	2-3 in line driver	F
<input type="checkbox"/> 903*	Dual 3 input gate	F	<input type="checkbox"/> WC215**	J-K flip flop	F
<input type="checkbox"/> 904*	Dual half adder	N	<input type="checkbox"/> WC226**	Triple 3 in. gate	F
<input type="checkbox"/> 908	Full adder	5	<input type="checkbox"/> WC227**	10 In. Diode expand	F
<input type="checkbox"/> 909	Buffer	5	<input type="checkbox"/> WC261**	Dual 4 In. gate	F
<input type="checkbox"/> 910	Dual two input gate	5	<input type="checkbox"/> WC266**	Quad 2 input gate	F
<input type="checkbox"/> 912	Half adder	5	<input type="checkbox"/> SG-43	Dual 3 In. gate	F
<input type="checkbox"/> 913	Shift register	5	<input type="checkbox"/> SG-123	Expandable 8 In. gate	N
<input type="checkbox"/> 914/921	Dual 2 input gate	5	<input type="checkbox"/> SG-163	Triple 2 in. bus driver	N
<input type="checkbox"/> 925	Dual 2 in. w/expand	F	<input type="checkbox"/> NE-124**	R-S-T binary	F
<input type="checkbox"/> 926	Hi speed 923	F			

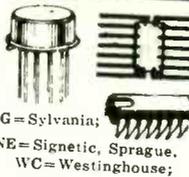Code: \* 2 identical ICs in 1 pak. \*\* DTL, otherwise RTL. F=flat pak; N=dual inline; 5=TO-5 case.



SG=Sylvania;  
NE=Signetic, Sprague.  
WC=Westinghouse;

## TEXAS-NATIONAL DTL TTL ICs!

Type	Description	Sale
<input type="checkbox"/> SN7350F*	Quad 2 input gate	.99
<input type="checkbox"/> SN7400N	Quad 2 input gate	.99
<input type="checkbox"/> SN7404N	Hex inverter	1.19
<input type="checkbox"/> SN7430F	8 Input Nand gate	.99
<input type="checkbox"/> SN7440F	Dual 4 In. Nand buffer	.99
<input type="checkbox"/> SN7441N	BCD-to-Decimal decoder-drvr	5.95
<input type="checkbox"/> SN7442N	BCD-to-Decimal decoder	5.95
<input type="checkbox"/> SN7470F	J-K flip flop	.99
<input type="checkbox"/> SN7472N	J-K master flip flop	.99
<input type="checkbox"/> SN7473N	Dual J-K master slave flip flop	1.49
<input type="checkbox"/> SN7474N	Dual 'D' type edge triggered flip flop	1.49
<input type="checkbox"/> SN7475N	Quad bi-stable latch	3.95
<input type="checkbox"/> SN7490N	Decade counter	4.95
<input type="checkbox"/> SN7492N	Divide by 12 counter	4.95
<input type="checkbox"/> SN7493N	4 Bit binary counter	4.95
<input type="checkbox"/> SN7302F*	Dual J-K flip flop with preset	1.29
<input type="checkbox"/> SN7304*	Dual J-K flip flop with preset & clear	1.49

\* DTL, others TTL. F=flat pak. N=dual inline

IBM 4000 Bit MEMORY Only  
core plane, from computer #1401. **\$8.50**

FAIRCHILD 741CAM\* Only **\$2.50**  
Same as 709 with frequency compensation.

## FALL-CHRISTMAS LIMELITERS

<input type="checkbox"/> 2-FT. finished fiber optic lite pipe	\$1.00
<input type="checkbox"/> 709 OP Amplifier	\$1.49
<input type="checkbox"/> 2-N CHANNEL plastic PETS 2N3819 Texas	\$1.19
<input type="checkbox"/> 2-UNIJUNCTION transistors 2N4891	\$1.19
<input type="checkbox"/> 1-IG MOS FET P channel 2N4353	\$1.00
<input type="checkbox"/> 3-TRIGGER photo elec cells pancake	\$1.19
<input type="checkbox"/> 5 CLAIREX photo elec cells pancake	\$1.00
<input type="checkbox"/> 8-1 AMP 1000 PIV sil. rectifiers	\$1.19
<input type="checkbox"/> 10-1 AMP 800 PIV rectifiers	\$1.19
<input type="checkbox"/> 4 NIXIE tube driver transistors 2N4409	\$1.00
<input type="checkbox"/> 2-7-AMP 200 PRV scr's	\$1.19
<input type="checkbox"/> 2-WATT G-E PA237 audio amp	\$3.98
<input type="checkbox"/> 1-WATT WESTINGHOUSE WC384 audio amp	\$1.49
<input type="checkbox"/> 1-15-AMP Triac 200 PRV	\$1.49
<input type="checkbox"/> NE161J One shot multivibrator Signetic	\$1.79
<input type="checkbox"/> 2 MICRO reed switches 1" long	\$1.00
<input type="checkbox"/> 100 Transistors asst npn-ppn-pwr-no test	\$1.98
<input type="checkbox"/> WESTINGHOUSE positive volt regulator 0 to 40 VDC	\$1.19

10¢ Catalog on Fiber Optics, 'ICs', Semis, Parts

Terms: add postage. Rated: net 30, cod's 25%  
Phone Orders: Wakefield, Mass. (617) 245-3829  
Retail: 211 Albion, St., Wakefield, Mass.

## POLY PAKS

P.O. BOX 942R  
LYNNFIELD, MASS  
01940

Circle 89 on reader service card

## AMAZING OFFER

### RADIO & TV SERVICE DATA



Your best, complete source for all needed RADIO and TV diagrams and helpful servicing data. Most amazing values. Only \$2.50, \$3, \$4, per giant volume. Cover all important makes, models of all periods. Use this entire ad as your no-risk order form.

--- NO-RISK ORDER COUPON ---

## TELEVISION SERVICE MANUALS

Supreme TV manuals are best for faster, easier TV repairs. Lowest priced. Factory data on practically all sets. Complete circuits, all needed alignment facts, wiring-board diagrams, waveforms, voltages, production changes, and double-page schematics. Only \$3 and \$4 per large annual manual. Check volumes wanted, send entire advertisement as your order form.

- New 1970 COLOR TELEVISION Manual, only \$4.
- New 1970 B-W TV, \$4
- 1969 B-W TV, \$4
- 1968 TV, \$4
- 1967 TV, \$4
- 1966 TV, \$3
- 1965 TV, \$3
- 1964 TV, \$3
- 1963 TV, \$3
- Additional 1965 TV, \$3
- Additional 1962 TV, \$3
- 1961 TV Manual, \$3
- Additional 1959 TV, \$3
- 1958 TV Manual, \$3
- 1957 TV, \$3
- 1955 TV, \$3
- 1954 TV, \$3
- 1951 TV, \$3
- Master Index to all TV & Radio Manuals, 25¢

## RADIO DIAGRAM MANUALS

Get these low-priced radio manuals and simplify all repairs. Cover everything you may need from recent radios to prewar old-timers; all type radios, stereo combinations, transistor portables, FM-AM, and auto sets. Large schematics, all needed alignment facts, printed boards, voltage data, dial stringing, hints. Volumes are big, 8-1/2 x 11", about 190 pages, each

**\$2.50**

- 1966,  1965,  1964,  1963,  1962,  1961
- 1960,  1959,  1958,  1956,  1955,  1954
- 1953,  1952,  1951,  1950,  1948,  1946
- 1942,  1941,  1940,  1926-38. EACH, \$2.50
- 1965 Auto Radios,  Simplified Servicing, \$1.50
- Also  New 1967-1969 Combined Radio Volume, \$4.00.

## SUPREME PUBLICATIONS

1760 Balsam Road, Highland Park, ILL., 60035  
Rush today TV and Radio manuals checked in no-risk order form of this ad. Send postpaid. I am enclosing full price. Satisfaction guaranteed.

Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
City: \_\_\_\_\_ State: \_\_\_\_\_

# SCHOOL DIRECTORY

## EDISON TECH Train With Confidence

Occupational Training Specialists Since 1945—Engineering and Vocational Technicians in Demand Intensive industry-oriented programs in Electronics Engineering Technology (Associate Degree in 72 wks); Electronics Technology; Graduates in demand—train Television Technology. Graduates in demand—train with confidence. Accredited by the Accrediting Commission, National Association of Trade and Technical Schools. Approved for Veterans. Write for Cat. RE10. EDISON TECHNICAL COLLEGE  
4629 Van Nuys Bl. Van Nuys (Los Angeles) CA 91403

## distinguished graduates

hold important engineering and management posts throughout U.S. Professionally-oriented college with outstanding placement record. Four-quarter year permits degree in three years. Dedicated faculty. Modern labs. Small classes. 400-acre campus. Accredited. Approved for vets. Moderate total costs. Enter Jan., March, June, Sept. For Catalog, write Director of Admissions, indicating career preference.

**TRI-STATE COLLEGE**  
24100 College Avenue, Angola, Indiana 46703

## GET INTO

## ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology & Electronic Technology curricula both available. Associate degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept. Feb. Dorms, campus. High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. C, Valparaiso, Indiana 46385



## INTEGRATED CIRCUITS / RECTIFIERS SEMICONDUCTORS / TRIACS

### TRIACS

PRV	1A	10A
100	.50	1.00
200	.80	1.40
300	1.10	1.80
400	1.40	2.20
500	1.75	3.00

ER900 TRIGGER DIODES. These bidirectional trigger diodes are one of the best and cheapest methods to trigger SCR's and triacs... 3/\$1.00

### UNIUNCTIONS!

Similar to 2N2419. RBB of 5-7 stand off ratio of .6 and ip of 12 with data sheet \$ .80

N-CHANNEL FET'S TO-18 plastic units, low noise, low leakage, 25 volts source to gate, 50 ma gate current Gain to 9000  $\mu$ mo's. \$ .60

2N4303. P channel FET with a Q ms of 2000  $\mu$ ohms ..... \$ .95

MM 2260. An NPN TO-5 silicon unit used for video output circuits in transistorized TV's, with a gain of 35 and Vcb of 75 \$ .75

### MOUNTING HARDWARE KITS.

These kits are used to mount our SCR's Zeners and Rectifiers etc. 6x32 stud (3, 12 amp rectifiers,

7A SCR's) 6 sets/\$1.00  
1/4x28 stud (30 amp. rectifiers, 20 amps SCR's) 4 sets/\$1.00

### MRTL IC's

908 FULL ADDER	.75
912 HALF ADDER	.50
913 REGISTER	.50
940 JK FLIP FLOP	.50

### TTL IC SERIES

DECADE DIVIDER	\$3.95
RF 112 Dual JK Flip Flop	1.25
MC 415 JK Flip Flop	.85
MC 400 Dual 4 input NAND/NOR gate	.70
4 Bit Storage Register	1.25
9301 MSI ONE-OF-TEN DECODER	2.95

### Silicon Power Rectifiers

PRV	3A	12A	30A
100	.09	.24	.50
200	.16	.35	.80
400	.20	.45	1.20
600	.30	.70	1.50
800	.40	.85	1.80
1000	.50	1.10	2.20

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage. Average Wt. per package 1/2 lb. No. C.O.D.'s. Minimum Order \$3.00

### FIBRE OPTICS

1/32" 2.5 mil. fibers in PVC packet. \$ .33/ft.

### COMPLETE LIGHT GUIDE BUNDLE

consisting of an 11" length of 1/32" dia. fiber optics with bound ends. \$2.00 ea.

### Controlled Avalanche or Epoxy Rectifiers 1 AMP.

PRV	PRV
100   .07	600   .16
200   .09	800   .20
400   .11	1000   .30

### Silicon Control Rectifiers

PRV	3A	7A	20A	70A
50	.30	.35	.70	
100	.40	.55	1.00	4.00
200	.60	.80	1.30	8.00
300	.80	1.00	1.70	
400	1.00	1.30	2.10	12.00
500	1.25	1.60	2.50	
600	1.50	1.90	3.00	16.00

### BIGGER AND BETTER BARGAINS.

Send for our latest catalog featuring Transistors and Rectifiers; 325 Elm St., Cambridge, Mass.

# SOLID STATE SALES

Post Office Box 74D

Somerville, Mass. 02143

Tel. (617) 547-4005

Circle 86 on reader service card

# MARKET CENTER

ented/unpatented invention. Write: **RAYMOND LEE ORGANIZATION**, 230-U Park Avenue, New York City 10017

## GOVERNMENT SURPLUS

**DIFFERENT? YOU BET. INDUSTRIAL AND GOVERNMENT ELECTRONIC SURPLUS AT LOWEST PRICES. GET OUR LATEST LIST NOW! STARTRONICS, BOX 17127, PORTLAND, OREGON 97217.**

**JEeps** Typically from \$53.90 . . . Trucks From \$78.40 . . . Boats, Typewriters, Airplanes, Multimeters, Oscilloscopes, Transceivers, Electronics Equipment. Wide Variety, Condition. 100,000 Bid Bargains Direct From Government Nationwide. Complete Sales Directory and Surplus Catalog \$1.00 (Deductible First \$10.00 Order). **SURPLUS SERVICE**, Box 820-REL, Holland, Michigan 49423

## WANTED

**QUICK CASH . . .** for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! **BARRY**, 512 Broadway, New York, N.Y. 10012, 212 WALKER 5-7000

## GENERAL

**SPEAKER RECONING**, replacement grill cloth, vinyl covering, hardware. For price list send self-addressed, stamped envelope. **CREATIVE SOUND PRODUCTS**, 262A Cranze Place, Akron, Ohio 44310

**UNSATISFACTORY** "live" recordings? Inexpensive new products for improved microphone fidelity and flexibility are available. Write **RUSSOUND, Inc.** Dept. 3, Box 1015, Framingham, Mass. 01701

**NEW BSR** record changers; \$13.00. McDonald 300-18.00; 400-\$20.00; 500-\$25.00; AM/FM component system-\$50.00. **DAVIS**, Dept. RE, 2737 Third Ave., Bronx, N.Y. 10451

**741P TEXAS INSTRUMENT OPERATIONAL AMPLIFIERS**—\$2.00 plus postage. **BALL ELECTRONICS**, Box 68, South Willington, Conn. 06265

**RENT** 4-track open reel tapes—all major labels—3,000 different—free brochure. **STERIOPARTI**, 55 St. James Drive, Santa Rosa, Calif. 95401

**SAVE** over 331/3 on a pair of one of the World's Best Speaker Systems. Shipped Direct to you from factory. Try them in your home for thirty days. **KGLL, INC.** Water Street, Lewiston, Maine 04240

## EDUCATION/ INSTRUCTION

**TV TUNER REPAIRS**—Complete Course Details, 12 Repair Tricks, Many Plans, Two Lessons, all for \$1. Refundable. **FRANK BOCEK**, Box 3236 (Enterprise), Redding, Calif. 96001

**"HDW TO INCREASE TRANSISTOR RADIO REPAIR PROFIT."** Write **X T R**, Box 1556, Las Vegas, Nev. 89101

**MEMORIZE**, Study: "1970 Test Answers" for FCC First and Second Class License.—plus—"Self-Study Ability Test." Proven. \$5.00. **COM-MAND**, Box 26348-E, San Francisco, Calif. 94126

**ELECTRONICS** Engineering. Day or evening classes. Bachelor of Science Program evenings. Associate in Science Program day or night. If you are married or if you must work for a living while obtaining your education, this is the college for you. Approved for Veterans. **WESTERN STATES COLLEGE OF ENGINEERING**, 970 West Manchester Avenue, Inglewood, Calif. 90301

**FCC** First Class license in six weeks: Nation's highest success rate-approved for Veterans Training. Write **ELKINS INSTITUTE**, 2603 E Inwood Road, Dallas, Texas 75235

## INVENTIONS & PATENTS

**INVENTORS**: Protect your ideas! Free "Recommended Procedure". **WASHINGTON INVENTORS SERVICE**, 422X Washington Building, Washington, D.C. 20005

**INVENTIONS** Wanted. Patented; Unpatented. **GLOBAL MARKETING**, 2420-AE 77th Ave., Oakland, Calif. 94605

**FREE** "Directory of 500 Corporations Seeking New Products". For information regarding development, sale, licensing of your pat-

## BACK ISSUES WANTED

of the following magazines: *Television, Television News, Short Wave Craft, Short Wave and Television, Radio and Television, Radio News*. Also other magazines on the same subjects. Pre 1950 only. Quote exact dates, titles and prices in first letter.

Monogram Publications, Inc., 21839 So. Avalon Blvd., Torrance, Ca. 90502

## BLUEPRINT TO PROGRESS

(continued from page 69)

technician can tackle is that of a freelance writer of technical material. This is a highly competitive area, for his material must match or even surpass the standards of writing in the field. Furthermore the subjects he chooses and the way he handles them must attract the attention of editors.

But even with the best of presentation, the market is limited. Unless the writer can produce a terrific amount of good material, he will have a difficult time making a living. He may be able to obtain a contract to do one or more spe-

cific jobs that will pay well for a short time. One such area is writing technical films; but the competition is fierce and the chances of landing such a job are fairly limited.

Requirements for free-lance writing include the ability to plan and write clearly, but even more, an aptitude for recognizing a salable subject and the incentive and energy to do the research necessary to make an article or book interesting and different. There are any number of writing courses at colleges and correspondence schools that will give a technician the basic tools he needs. But he must be ready to serve a long apprenticeship before his material will be regularly requested and paid for.

The different positions discussed do not exhaust all the possibilities open to a technician seeking to progress from an hourly to a salary position. They should, however, indicate that the path is definitely not closed. Assuming he has begun his education program early to anticipate openings, he then should indicate his qualifications to his supervisors and his readiness to move into a salaried position. With his technical experience he should have a decided advantage.

R-E

**FREE Catalog** Of The **WORLD'S** FINEST GOV'T SURPLUS ELECTRONIC BARGAINS

Now **BIGGER** and **BETTER** Than Ever!

—MAIL THIS COUPON NOW—

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

CITY: \_\_\_\_\_ STATE: \_\_\_\_\_ ZIP: \_\_\_\_\_

For your **FREE** copy, fill out coupon and mail. Dept. RE

**FAIR RADIO SALES**  
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

### PEP'S Dollar Sale

**\$1 Money Back guarantee \$1**

<p><b>1 Amp Silicon Rectifier</b> choice of package</p> <p><b>Bullet—Miniature Glass-Metal</b></p> <p><input type="checkbox"/> 5-800V units \$1.00</p> <p><input type="checkbox"/> 4-1000V units \$1.00</p> <p><input type="checkbox"/> 3-1200V units \$1.00</p>	<p><b>7 AMP SCR</b></p> <p><input type="checkbox"/> 4-50V units \$1.00</p> <p><input type="checkbox"/> 3-100V units \$1.00</p> <p><input type="checkbox"/> 2-200V units \$1.00</p> <p><input type="checkbox"/> 1-500V unit \$1.00</p> <p><input type="checkbox"/> 1-800V unit \$1.50</p>
<p><b>3 AMP Epoxy Package</b></p> <p><input type="checkbox"/> 10-100V units \$1.00</p> <p><input type="checkbox"/> 5-400V units \$1.00</p> <p><input type="checkbox"/> 2-1000V units \$1.00</p>	<p><b>20 AMP SCR</b></p> <p><input type="checkbox"/> 2-50V units \$1.00</p> <p><input type="checkbox"/> 1-300V unit \$1.50</p> <p><b>Gen Purpose PNP Germ Transistor Similar to 2N404</b></p> <p><input type="checkbox"/> 8 For \$1.00</p>

<p><b>TRIACS</b></p> <table border="1"> <tr><td>PVR</td><td>10A</td></tr> <tr><td>100</td><td>1.00</td></tr> <tr><td>200</td><td>1.40</td></tr> <tr><td>300</td><td>1.90</td></tr> <tr><td>400</td><td>2.30</td></tr> <tr><td>500</td><td>2.75</td></tr> </table>	PVR	10A	100	1.00	200	1.40	300	1.90	400	2.30	500	2.75	<p><b>SILICON STUD MOUNT</b></p> <p><b>20 AMP</b></p> <p><input type="checkbox"/> 3-100V units \$1.00</p> <p><input type="checkbox"/> 1-1000V unit \$1.50</p>
PVR	10A												
100	1.00												
200	1.40												
300	1.90												
400	2.30												
500	2.75												

**I.C. SUMMER SPECIAL**  
14 Lead Dual In-Line Pkg.  
Perform same function as 700 series

Master Slave Flip Flop 75¢ @—\$-3.00  
Quad 2 Input Nand Gate 75¢ @—\$-3.00

16 Bit Memory Cell—\$4.25  
14 Lead Dual In-Line Pkg.

**CIRCUIT BOARD COLOSSAL**  
3 different groupings to choose from  
Typical samples below

A) 200 diodes—7 transistors—over 50 resistors—complete with board!

B) 32 transistors—over 100 resistors—capacitors—S.C.R.'s over 15 diodes—complete with board! Price \$1.75

C) 22-11 lead dual in-line I.C.'s—over 50 diodes—capacitors—4 transistors—over 50 resistors—complete with board! Price \$2.50

FULL WAVE BRIDGES				
PRV	2Amp	3Amp	5Amp	10Amp
50V	1.25	1.35	1.50	1.70
100V	1.50	1.60	1.75	1.95
200V	1.75	1.85	2.00	2.20
400V	2.00	2.10	2.25	2.45
600V	2.50	2.60	2.75	2.95
800V	3.00	3.10	3.25	3.45

**PARK ELECTRONIC PRODUCTS**  
P. O. Box 78 N. Salem, N. H. 03073  
Tel. (603) 893-0276  
NO SALES TAX WE PAY POSTAGE

Circle 87 on reader service card

RADIO-ELECTRONICS

# U.S. GOV'T ELECTRONIC SURPLUS

Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government surplus electronic units and components at a fraction of their original acquisition cost.

## IBM COMPUTER POWER SUPPLY

• (ITEM #22-934) -- Expensive, regulated unit. Fine for college labs, research labs, service shops, etc. Pure DC over a wide range of voltages. 10" output voltages: 0, 12, 30, etc. Wide range of AC voltages available.

• Three transformers, filters, transistor load regulation system. Independent all-line voltage regulators. Contains five separate voltage systems. Unit is furnished without small "regulating card" which can be easily made or bought in-house. Data and circuit diagrams furnished. 30" x 12" x 10". 125 lbs.

Cost Gov't Over \$100.00 **\$24.95**

ONCE-IN-A-LIFETIME SPECIAL

## BURGLAR-FIRE ALARM SYSTEM



• (ITEM #1135-A) -- Dual alarm system gives warning of fire or break-in. Operates on 115-VAC. Control unit, 2" x 1/2" x 1/2". Alarm bell, 100 Hz. wire, instructions. 8 1/2" x 7 1/2" x 7 1/2" lbs.

**\$29.95**

## STANDARD DIAL TELEPHONE

• (ITEM #715) -- Standard, commercial telephone same as used throughout U.S.A. Attractive polished look, like new condition. Extension phone to private systems or connect several phones together for local intercom system. Full instructions are furnished. 30", 9 lbs.



Original Cost. **\$74.95**

## STEP-BY-STEP TELEPHONE SWITCH

• (ITEM #71-906) -- Amazing telephone selector switch. Great experimental item. When used with two-wire telephone dial will select any number from 0 to 100. Make intercom or private system. Use to turn on remote lights, start motors, etc. Complete with contact bank. 12 1/2" x 6" x 5" (4 lbs.). Cost (over \$90.00).



**\$6.29**

• Telephone dial for use with above switch. Order as (Item #700) **\$1.97**

## MAGNETIC DIGITAL COUNTER (12 to 18-VDC)



• (ITEM #21-958) -- Use to count electrically. Use to count number of times door is opened after business is closed, to show changing prices, laboratory uses, etc. Will count 1 for each pulse and will transfer 10th count to next unit. 4 1/2" x 1 1/2" x 1 1/2".

Orig. Cost **\$4.99**

## TYPICAL BUYS FROM OUR 1970 CATALOGS

- \$ 10.00 115-Volt DPDT Relays..... **\$1.69**
- \$101.00 Regulated Transformer, Wide Range..... **\$14.91**
- \$ 75.00 20-Relay Telephone Panel..... **\$4.39**
- \$250.00 Gyroscope, Twin Rotor, 24V..... **\$9.89**

## AC PROGRAM TIMING CLOCK

• (ITEM #158) -- Zenith 115-Volt unit. Use for periodic signaling, with clocks, classes, turn on radio, etc. Adj. clock permit ON-OFF switching any time in 24-hour period. Also has "skip-a-day" feature. Can be multiple programmed. 15-amp. contacts. 8 1/2" x 6 1/2" x 4". (8 lbs.).



Cost Gov't Over \$30.00 **\$15.75**

## SNAP AROUND VOLT-OHM-AMMETER

• (ITEM #21-944) -- Measures AC current without opening the line. Simply press handle and snap the probe around the conductor. Reads currents from .25 to 125-amps. Appliances, etc. Three current ranges, two voltage ranges. With case, test leads. 7 1/2" x 3 1/2" x 1 1/2".



**\$36.90**

Reg. Price \$39.95 (2 lbs.)

## SPECIAL SALE

### Correspondence Course In ELECTRICAL ENGINEERING



**\$8.79** Prepaid in U.S.A.  
**\$10.79** Outside U.S.A.

• (ITEM #A180) -- Obtain technical training at low cost! Lincoln Engineering School has suspended its Correspondence Courses because of rising costs. A limited number of Electrical Engineering Courses are available, but without the examination grading service. The course consists of 15 lesson books, each with associated exams and standard answers. Book describing prize-winning Home Experimental Laboratory Book furnished at no extra cost.

## RUNNING TIME METER

• (ITEM #21-88) -- Record number of operating hours of electric lights and electrical devices such as refrigerators, furnaces, etc. Records total hours, totals run hundreds up to 9,999.99 hours. For 115-volt, 60-cycle. Size 4 1/2" x 3 1/2" x 2 1/2". Shipping weight 2 lbs.



**\$4.39** Cost Over \$29.00

## COMPUTER TRANSISTORS ON HEAT SINKS

IBM Computer Quality Units

• (#22-928) -- Unit consists of one 150-watt power transistor on heavy, ribbed, aluminum heat sink. Many experimental uses. (1 lb.).



Cost Gov't Over \$10.00 **\$1.99**

• (#22-915) -- Unit consists of two 150-watt power transistors, two coils, several diodes, capacitors, resistors, etc. on heavy, ribbed aluminum heat sinks. Ideal for use as motor speed control. (4 lbs.).



Cost Gov't Over \$15.00 **\$4.91**

SEND 25c COIN OR STAMPS FOR CATALOGS


Order Direct From Ad. Money Back Guarantee.

## SURPLUS CENTER

DEPT. RE 100 LINCOLN, NEBR. 68501

# 1000's OF UNUSUAL SCIENTIFIC BARGAINS including... SPECIAL UNIQUE PSYCHEDELIC LIGHTING for Fun, Profit, Effects!

## CHROMATIC "MACHINE-GUN" STROBE

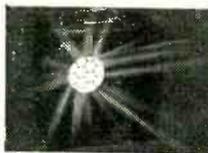

Red, Green, Blue & White light barrage the eyeballs every 6 seconds with this low-cost mechanical strobe that can run continuously without fear of burning up. Dazzling effects over 500 ft. sq. area. Created by rotating color wheel in front of 100W 120v reflector floodlamp (incl.)—elements seem to flash on & off as colors fluctuate. Turns store windows, posters, parties into flashing, pulsating productions. Convection cooled. Walnut cabinet, brass handle. Reg. house current.

Stock No. 71.271EH (9 X 10 X 6 1/2")... **\$28.50 Ppd.**


## PSYCHEDELIC LIGHTING HANDBOOK



100 information packed pages! Fully explains latest in psychedelic lighting equipment, techniques, developments. Covers all facets of psychedelic light-show production including strobes, black lights, projectors, crystals, organic slides, mirrors, color organs, polarized color, light boxes. Music-Vision, etc. 8 1/2" x 11" looseleaf paper for 3 ring binder.

Stock No. 9100EH... **\$3.00 Ppd.**

## LONG-WAVE BLACK LIGHT FIXTURE

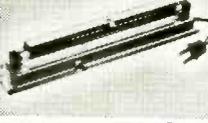

Extremely versatile, compactly designed, long wave (3200-4000 angstrom) black light (ultraviolet) fixture—eliminates harmful shorter wave ultraviolet rays. Use to identify minerals, fungi, bacteria—check for surface flaws, oil and gas leakage—perfect for displays with fluorescent paper, paints, chalk, crayons, trace powder. Incl. adjustable aluminum reflector, push-pull switch, connecting plug. Mount vert., horiz., or on corner. 10" L., 1 1/2" W., 1 1/2" H.

Stock No. 70.364EH... **\$12.50 Ppd.**  
No. 60.124EH... REPLACEMENT BULB... **\$4.75 Ppd.**


## MIRRORED BALLS BOUNCE LIGHT



Yesterday's hallrooms echo in mirrored lights that ricochet to the beat of today's discotheque. Up to 1,000 lustrous, clear, hand-made glass mirrors on each ball create fantastic lighting effects. Motorized—they cast reflections that blow the mind! Ideal for light shows, displays, restaurants, hotels, and modern stores.

Stock No. 71.066"EH" (12" Diam.)... **\$30.00 Ppd.**  
Stock No. 85.180"EH" (16" Diam.)... **\$75.00 FOB**  
Stock No. 71.065"EH" (8" Diam.)... **\$17.50 Ppd.**

## NICKEL-CADMIUM BATTERY BARGAIN!

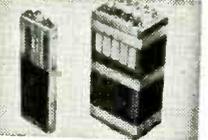

Terrific value—slightly used car's surplus. Lightweight 5 cell, 6 volt, 4 Amp-hour battery with almost unlimited life. Extremely high current output. Recharges in 1 hour with Edmund kit. Won't deteriorate when left discharged. Minimum maintenance—few drops of water per year. Rugged, shock- and-vibration resistant nylon case. Delivered partially charged, filled with electrolyte. 3 1/2" x 2 1/2" x 9 1/2".

Stock No. 70.942EH... (BATTERY)... **\$15.00 Ppd.**  
Stock No. 70.807EH... (CHARGER KIT)... **\$ 8.00 Ppd.**

## GLASS FIBER OPTICS KIT



Low-cost kit perfect for experimenting. Variety of pieces, items, accessories. Contains 9" bundle of unjacketed, 2.5mil fibers (about 600); twelve 6" plastic fibers (20mil); 5 ft. X 0.087" dia. coil of PVC jacketed (about 200, 2.5mil fibers); 1 ft. light guide w/polished ends & heat-shrink tips; coherent, hex., rod (1 1/2" X 1/4" dia.); 1 1/2" rod; heat-shrink material (5") x 1/2" dia. X .110" thick, polished face plate; 1/2" dia. glass plate; 5/8" penlight & adapter (needs 2 A cells, not incl.); plano-convex lens; instr.

Stock No. 71.285EH... **\$10.00 Ppd.**

## 1st LOW-COST VACUUM PUMP!




Nothing like it! Top-quality hand-held pump produces & maintains 25" of vacuum. Has instant release tab. 1 1/2" diam. stainless gauge (0-30"). 100's of uses—siphon noxious fluids, evacuate bell jars and castings, clean, retrieve, lift, sterilize objects, demonstrate Magdouburg hemispheres, bleed fuel lines, check leaks, etc. Lifts 40 lbs. with included "T" Lifter (2 1/2" diam. cup)—much more w/larger cup.

Stock No. 71.301EH... **\$12.00 Ppd.**  
No. 71.300EH (without gauge/lifter)... **5.50 Ppd.**
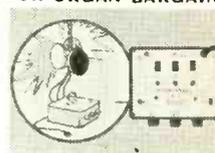
## 3-CHANNEL COLOR ORGAN BARGAIN!

Create tremendous variety of unusual & beautiful lighting effects with this low-cost electronic lighting unit (500 W. per channel). Compare with others selling for twice the price. Has pilot light, plus individual sensitivity controls and channel indicator lights. Can operate ten 150 W. "spots" or 200 Christmas lights. Uses reg. house current—attaches to audio source w/RCA-type phone plug. 5 1/2" x 6 3/4" x 2 1/2". 2 1/2 lbs. Thermal setting plastic case. 6-ft. cord. Including complete instructions.



Stock No. 71.223EH... **\$44.50 Ppd.**

## 3" ASTRONOMICAL TELESCOPE

See moon spots, orbits-stars, planets of Venus, planets close up, 60 to 180 power. Aluminized and overcoated 3" diameter f/10 primary mirror, ventilated cell. Equatorial mount with locks on both axes. Equipped with 60X eyepiece and mounted Barlow lens. AX finder telescope built-in tripod.



FREE: "STAR CHART", 272-page "HANDBOOK OF HEAVENS"; "HOW TO USE YOUR TELESCOPE!"  
Stock No. 85.050EH... **\$29.95 Ppd.**  
Stock No. 85.105EH... 4 1/2" **\$94.50 FOB**  
Stock No. 85.086EH... 6" **\$239.50 FOB**

## ROTATING MULTI-COLORED LIGHT


Dazzling colors stream endlessly from constantly rotating light. Faceted, transparent globe has lowered drum inside with red, green, blue & yellow stars. Bulb heat rotates drum which projects flickering star points on walls, ceilings, etc. while individual globe facets present constantly changing array of brilliant colors. 9 1/2" star—approx. 12" high on bell-shaped base. Surprisingly light. Easily placed on table, TV, fireplace, or Xmas tree top.



Stock No. 71.000EH... **\$7.00 Ppd.**
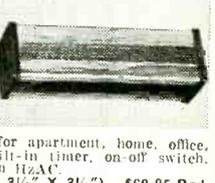
## PLUG-IN ULTRASONIC ALARM/LIGHTER

Silent, economical, easy to install. No special attachments or electrician needed. Just plug in socket—then plug lights and/or alarm into it. Activates when it "hears" someone's footsteps automatically. Ultra-sensitive up to 30 ft. Sensitivity control can adjust out pet noise. Convenient for night light—eliminates fumbling or injury in darkness. Ideal for apartment, home, office, plant. Walnut finish with built-in timer, on-off switch. 5KHz frequency—110-130Hz, 60 Hz AC.



Stock No. 71.283EH (10 1/2" X 3 1/4" X 3 1/4") **\$69.95 Ppd.**

## 1st QUALITY OPAQUE UNDER \$200

Terrific Buy! Top Quality! Projects brilliant, sharp 4 1/2" ft. sq. image from 8" using up to 5"x3" color, b&w illustrations. Retains all original colors, proportions. Enlarges drawings, coins, maps, etc. Revolutionary peanut-size quartz halogen lamp (50 hr. life), 200mm anastigmatic lens (f3.5, 8" F.L.) unique internal reflecting system give maximum brightness, entire field focused. Can be used upside down. Turbo-cooled. 5 1/2 ft. cord.



Stock No. 71.272EH (Wt. 11 1/2 lbs.)... **\$89.75 Ppd.**

## QUICK OCR "GO... NO-GO" TEST!

New, low-cost way to save time & money in OCH operations by detecting improper characters, lines, spacing before problems occur. Two 2 1/2mm reticles with handy, pocket-sized 6X Comparator for checking ANSI size I-M-X character set. Bred with transp. red ink. Quickly, easily check character size, shape, skew & spacing; line spacing & skew; stroke width; voids, smudges, peaks, valleys, marks, English & metric scales.



No. 41.350EH (With Comparator) **\$34.50 Ppd.**  
SIZE I RETICLE ONLY... **30.642EH... \$11.00 Ppd.**  
SIZE IV RETICLE ONLY... **#30.643EH... \$10.75 Ppd.**

## MAIL COUPON FOR GIANT FREE CATALOG

148 PAGES—1000's OF BARGAINS Completely new 1971 edition. New items, categories, illustrations. Dozens of electrical and electromagnet parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many war surplus items. Mail coupon for our giant "EIT" EDMUND SCIENTIFIC CO. 300 EDCORP BUILDING BARRINGTON, N.J. 08007


NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

# EDMUND SCIENTIFIC CO. 300 EDCORP BLDG. BARRINGTON, NEW JERSEY 08007

ORDER BY STOCK NUMBER • SEND CHECK OR MONEY ORDER • MONEY-BACK GUARANTEE

**Rebuild Your Own Picture Tubes?**  
With Lakeside Industries precision equipment you can rebuild any picture tube!  
For complete details, mail coupon.

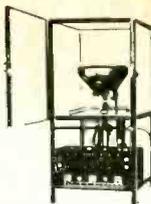Lakeside Industries  
5234 N. Clark St.  
Chicago, Ill. 60640  
Phone 312-271-3399  
NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_ ZIP \_\_\_\_\_



**AMAZING NEW ELECTRONIC COMPUTER NOW AVAILABLE FOR PERSONAL USE... AT AN UNPRECEDENTED LOW PRICE!**

For family fun or individual instruction, there's nothing quite like the all-new, all solid-state **COMPULOGICAL TUTOR!** Anyone from 8 to 80 can enjoy it while quickly learning digital logic and all other aspects of computer operation. No prior math required. In 20 minutes time, you'll be solving intricate problems just like computer professionals. You'll be entertained and enlightened as you proceed to learn binary numbers, fundamentals of Boolean algebra, logic-building blocks and symbols, truth tables, computer circuits, error-detecting logic, storage, programming and many other fascinating computer operations. It adds, subtracts, multiplies and divides... in millionths of a second. Shows how to apply computer to practical problems of accounting, economics and finance. Perfect for home, school and office. Master assembly board equipped with appropriate inputs and outputs, plus all circuits, controls and transistorized logic blocks (modules) required to work hundreds of problems. Big instruction manual simply presents basic computer concepts, with all problems and experiments clearly diagrammed and explained. Desk-size, portable, uses standard flashlight cells (not provided). Order for yourself, your family, and for gifts to youngsters, students, business executives, others. It's new... different... unique! Only \$69.95 postpaid and fully guaranteed. Free full-color brochure.



**COMPUSAD, INC.**  
16 Wetmore St. • P.O. Box 10  
New York Mills, N.Y. 13417

Use coupon below

Please send at once \_\_\_\_\_ Compulogical Tutor(s) at \$69.95, postpaid, with the understanding that if I am not more than satisfied in every way, I may return the Tutor(s) for a full refund.

- Full remittance enclosed; send postpaid. (Please Add Sales Tax Where Applicable)
- \$10 deposit enclosed; send C.O.D. for balance plus postage and fees.
- Send free color brochure at no obligation.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 82 on reader service card

ENJOY THE "MUSIC ONLY" FM PROGRAMS

**M. A. D.**

MUSIC ASSOCIATED'S DETECTOR for continuous, commercial-free music with ANY FM tuner or receiver



Kit \$49.50 Wired \$75.00 Cover \$4.95 List of FM Stations with SCA authorization \$1.00. Excellent F.M. Monaural Tuner with M.P.X. Jack \$50.00  
MUSIC ASSOCIATED  
65 Glenwood Rd.,  
Upper Montclair, N.J. 07043  
phone 201-744-3387


# NOTEWORTHY CIRCUIT

## SAFETY SWITCH FOR MINI-BIKES

One index of the ever-increasing popularity of the minibike with the younger set—particularly those too young to own or operate cars—is the number of injuries noted by hospitals and pediatricians. Many of these injuries occur when the rider's clothes

switch made by sealing two contacts in each end of a 5-inch length of glass or plastic tubing bent in the form of a "V". One contact on each end is grounded to the frame and the other goes to the high side of the coil or to the "hot" lead to the spark plug.

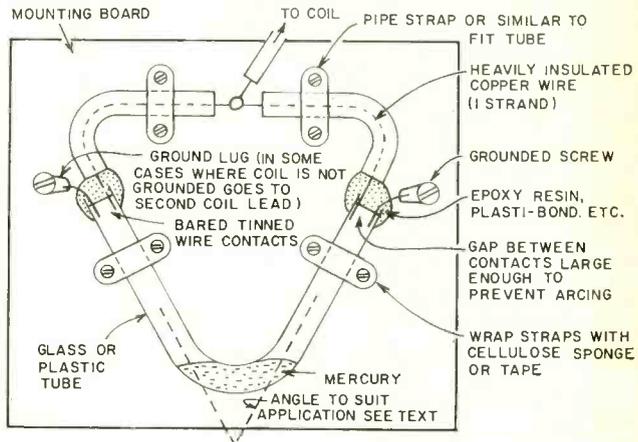The switch is clamped to a piece of 1/4" plywood and mounted vertically



or some part of his person gets caught in the rear-wheel spokes or between the chain and sprocket after a spill. Being aware that the rider does not have time to cut the ignition when he realizes he is about to spill; Mr. Lindsey Ford, Balwyn, Australia developed a simple switch that kills the engine when the bike tips.

The diagram shows how he described the switch in *Electronics Australia*. It is actually a simple mercury

switch across the frame parallel to the handlebars. It should be wrapped in foam rubber to protect against shock and enclosed in a small box to protect against the elements and gas and oil spillage from the engine. The angle of the "V" is determined by the type of vehicle. If the angle is too large, the ignition will short out on a normal leaning turn. If it is too small, the ignition might not cut off if the rider takes a spill on a hill.

**R-E**

# NOW... YOU CAN ZIP-ORDER

Amateur, Monitor and CB

## CRYSTALS

Your dealer has a new, fast, direct-factory ZIP Crystal Purchase Certificate that enables you to get the Amateur Controlled Quality Crystals you want mailed direct to you promptly. Ask about it.



**CRYSTEK**  
formerly Texas Crystals

DIVISION OF WHITEHALL ELECTRONICS CORPORATION

1000 Crystal Drive

Fort Myers, Florida 33901

4117 W. Jefferson Blvd.

Los Angeles, California 90016

Circle 83 on reader service card





# COMPLETE TUNER SERVICE

Castle, the pioneer of television tuner overhauling, now offers the following services to solve ALL your television tuner problems.

## OVERHAUL SERVICE — All makes and models.

VHF or UHF tuner (1960 or later)	\$9.95
TRANSISTOR tuner	\$9.95
COLOR tuner (Guaranteed color alignment . . . no additional charge)	\$9.95

Overhaul includes parts, except tubes and transistors.

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

Dismantle tandem UHF and VHF tuners and send in defective unit only.

Remove all accessories . . . or dismantling charge may apply.

## EXCHANGE REPLACEMENTS

When our inspection reveals that original tuner is unfit for overhaul, we offer an exact replacement (new or rebuilt) as low as \$12.95 exchange, depending on type. If exact replacement is not available in our stock we custom rebuild the original at the exchange price.

## PROFESSIONAL "CONTACT OVERHAUL" KIT

Do your own minor tuner overhauling by using this professional kit of chemicals. Enables you to recondition the switching contacts with the same advanced cleaning, polishing and lubricating materials used by Castle. Attain the same professional results we do . . . in most cases you can do this right in the customer's home.

Safe for all types of tuners, one kit will process several.

Order Now . . . or write for more information.



Dealer Net \$5.50

## UNIVERSAL REPLACEMENTS Prefer to do it yourself?



STOCK No.	HEATERS	SHAFT Min.* Max.*	I.F. OUTPUT Snd. Pic.	PRICE
CR6P	Parallel 6.3v	1 3/4" 3"	41.25 45.75	8.95
CR7S	Series 600mA	1 3/4" 3"	41.25 45.75	9.50
CR9S	Series 450mA	1 3/4" 3"	41.25 45.75	9.50
CR6XL	Parallel 6.3v	2 1/2" 12"	41.25 45.75	10.45
CR7XL	Series 600mA	2 1/2" 12"	41.25 45.75	11.00
CR9XL	Series 450mA	2 1/2" 12"	41.25 45.75	11.00


\*Supplied with max. length selector shaft (measured from tuner front apron to tip) . . . you cut to suit.

These Castle replacement tuners are all equipped with memory fine tuning and UHF position with plug input for UHF tuner. They come complete with hardware and component kit to adapt for use in thousands of popular TV receivers.
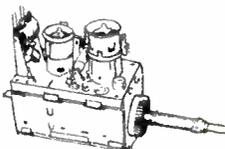
## EXACT REPLACEMENTS


Purchase outright . . . no exchange needed. \$15.95 ea.

Castle replacements made to fit exactly in place of original tuner. Available in the following popular numbers.



### ZENITH

175-168	175-740	175-1104	175-1156
175-204A	175-750	175-1105	175-1157
175-264	175-752	175-1106	175-1160
175-268	175-754	175-1118	175-1161
175-711	175-755	175-1121	175-1162
175-716	175-756	175-1122	175-1163
175-718	175-758	175-1131	175-1164
175-719	175-759	175-1132	175-1165
175-721	175-761	175-1134	175-1168
175-722	175-762	175-1151	
175-738	175-763	175-1154	
175-739	175-764	175-1155	

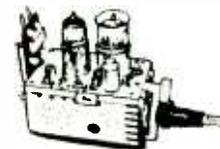

### RCA

KRK 103A	KRK 123D
KRK 103C	KRK 127AB
KRK 103F	KRK 127BA
KRK 107A*	
KRK 107B*	
KRK 107C*	
KRK 107D*	
KRK 107E*	
KRK 108A*	
KRK 108B*	
KRK 108D*	
KRK 108E*	

\*Supplied with new channel indicator skirt knob, original illuminated dial is not used.

Order EXACT REPLACEMENTS, UNIVERSAL REPLACEMENTS and "CONTACT OVERHAUL" KITS out of Main Plant (Chicago) only. Overhaul Service, Exchange Replacements and Custom Rebuilding available from New York or Chicago.

## CASTLE TV TUNER SERVICE, INC.

MAIN PLANT: 5715 N. Western Ave., Chicago, Illinois 60645  
EAST: 130-01 89th Rd., Jamaica, N.Y. 11418

Circle 84 on reader service card



# cash in on a GROWING NEW business...



CRYSTAL MFG. CO., INC.  
10 NO. LEE • OKLA. CITY, OKLA. 73102



## SERVICE MICROWAVE OVENS

Thousands of new microwave ovens are sold each year for commercial or home use. As oven sales continue to climb a brand new opportunity opens for those presently engaged in radio and television servicing. It's an opportunity to supplement your present income . . . or start an entirely new servicing business.

A majority of the franchised "fast food" eating establishments are using microwave ovens. Hundreds of restaurants are discovering the oven that will bake a potato in five minutes, heat precooked frozen food in minutes. Homeowners everywhere are becoming aware of the electronic oven which cuts cooking time from hours to minutes . . . even seconds. Prepare yourself now for this new servicing and maintenance business.

International Crystal Mfg. Co., a pioneer manufacturer of microwave ovens, has information regarding this space-age opportunity for skilled technicians. Write today for complete details.

ADDRESS INQUIRIES TO:  
**SERVICING INTERNATIONAL CRYSTAL MFG. CO., INC.** 10 North Lee Oklahoma City, Okla. 73102

*Circle 85 on reader service card*