

60c ■ JAN. 1973

# Radio-Electronics

FOR MEN WITH IDEAS IN ELECTRONICS

## SPECIAL ISSUE - COLOR TV 1973

**COLOR TV TEST JIGS**

Leave The Pix Tube Behind

**AUTOMATIC COLOR CONTROLS**

See How They Work

**ADD-ON DIGITAL READOUT**

Tells Receiver Frequency


**NEW TV CIRCUITS FOR '73**

Make Color Pictures Great

**COLOR TV-TOMORROW**

Birds-Eye-View Of The Future

GERNSBACK  
PUBLICATION

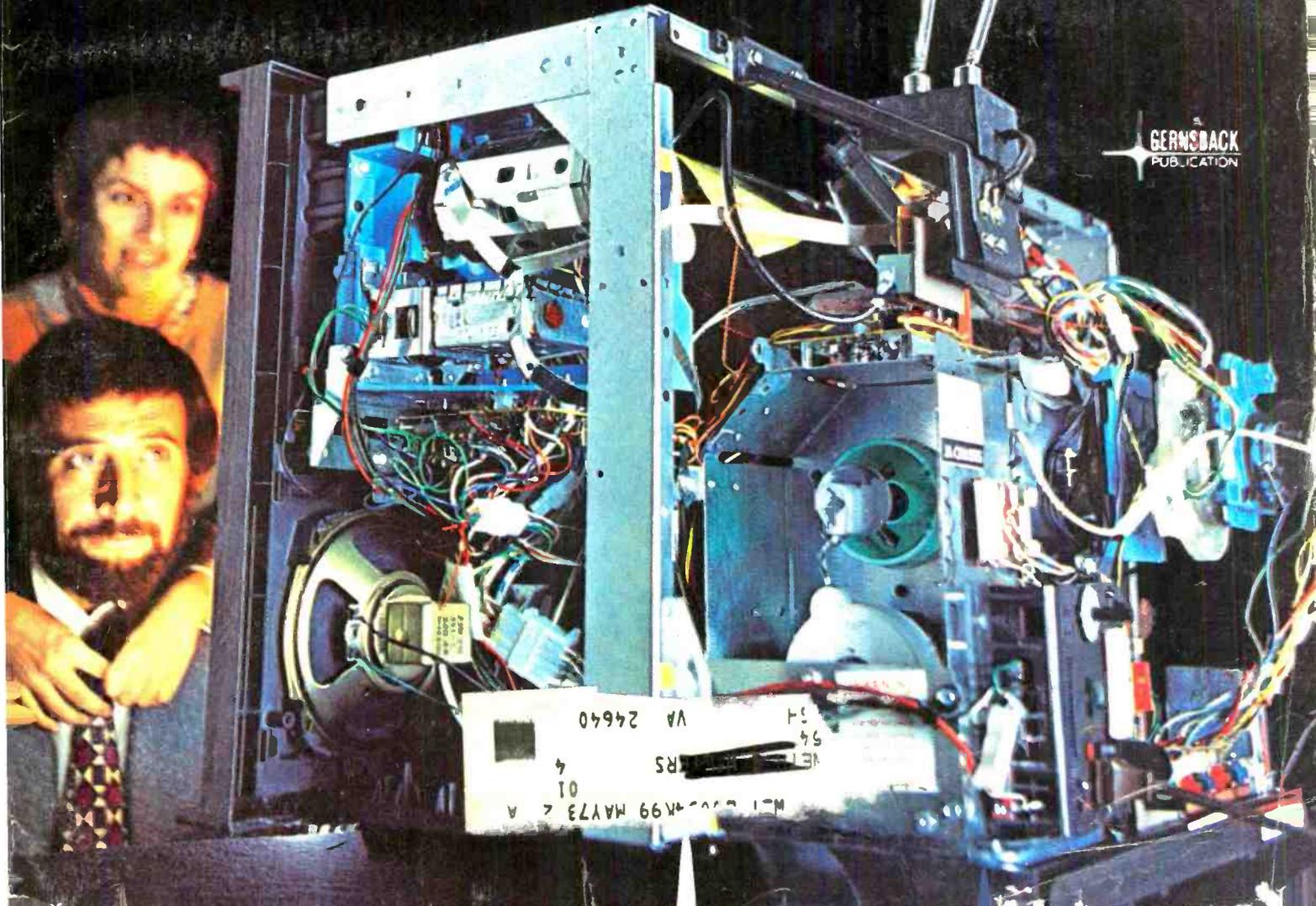

*Pioneering again.....Castle presents a sensational NEW Timesaver for the Professional TV Service Technician..... Speed Testing by signal substitution. A new, simplified approach to signal circuit analyzing.....*

# TV TUNER SUBBER™



Transistorized Test Unit substitutes the tuner in defective TV Receiver to prove whether original tuner is good or bad. Performs tests normally made using elaborate and expensive signal generating equipment and oscilloscopes . . . but much more simply, with easily understood results. Tests that are, in fact, so simple that they can be made right in the home, in most cases without removing the tuner or chassis from cabinet.

Use with any 40MHz receiver . . . black and white or color . . . tube or transistor.

Completely self contained and battery operated; Mk. II, all solid state, improved version of original "subber." Uses L.E.D. indicator, has higher gain with wide range control affording more than 40db of gain reduction. Use on the bench or in the home . . . anywhere.

Substitutes the VHF tuner and tests the UHF tuner. Provides signal to simplify testing of tuner, i.f. system and AGC system. Comes complete with extension cables and instructions.

**Unsolicited praise bestowed this revolutionary device includes:**

*" . . . works good. I know it will save hours in my TV Service . . . you are to be commended . . ."*

*" . . . in one month . . . TV Tuner Subber . . . already paid for itself — twice! Thanks much!"*

*" . . . received only Ch. 5, and not good. Used the new Castle TV Tuner Subber and got all channels . . . original tuner removed for service!"*

**TV TUNER SUBBER MK. II net \$31.95** Contact your distributor.


Include \$1.50 shipping and handling on prepaid mail orders: we will ship C.O.D.



**CASTLE TV TUNER SERVICE, INC.**

5715 N. Western Ave., Chicago, Illinois 60645 • Phone: (312) — 561-6354

Circle 1 on reader service card

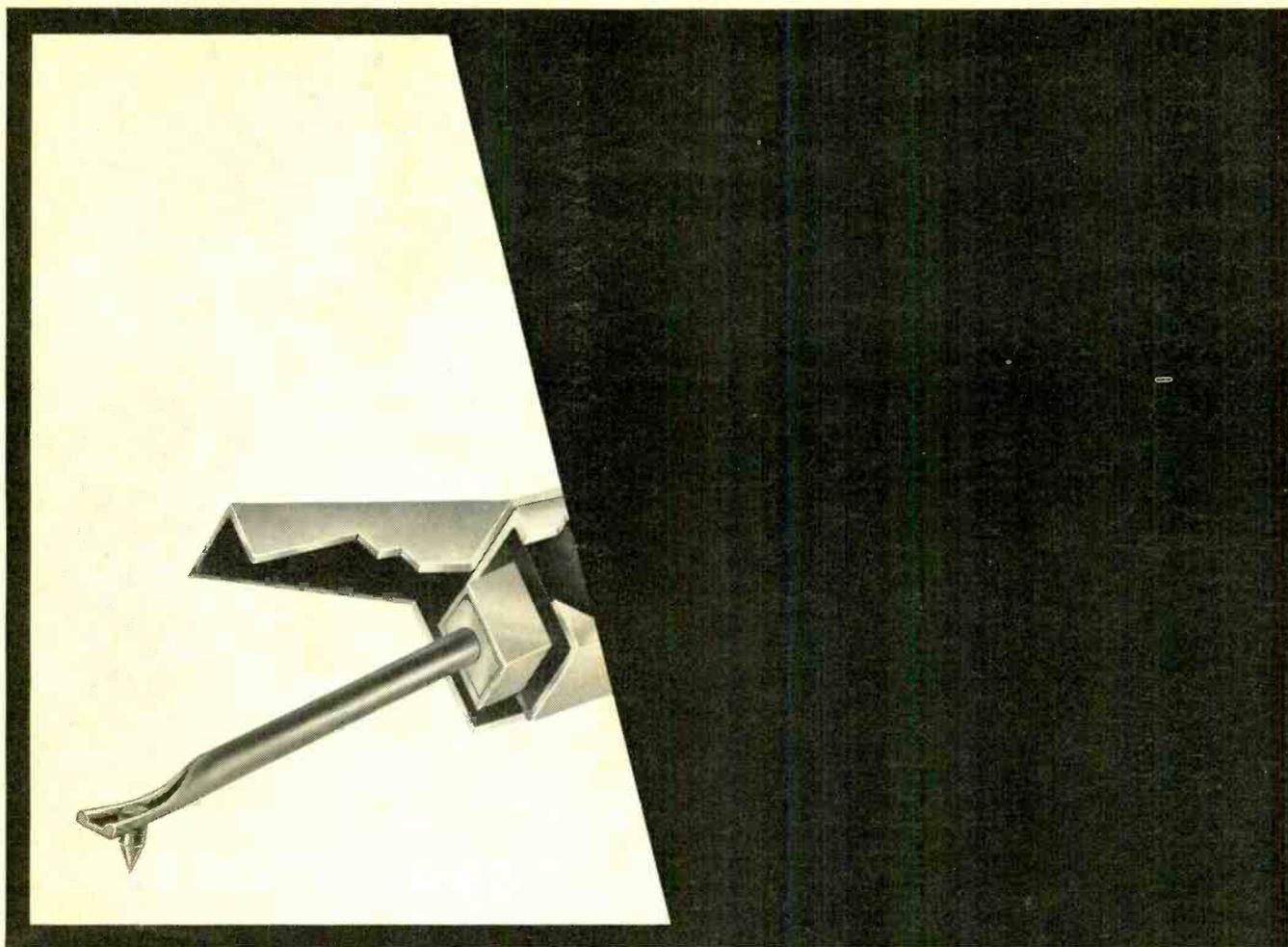

## Straight talk about a stylus



Listen carefully and you can still hear some audiophiles refer to the record stylus as... "the needle." Although we are not about to quibble over semantics, we would like to go on record, so to speak, as observing that the stylus of today bears no more resemblance to a needle than it does to a ten-penny nail. In fact, it is probably the most skillfully assembled, critically important component in any high fidelity system. It must maintain flawless contact with the undulating walls of the record groove — at the whisper-weight tracking forces required to preserve the fidelity of your records through repeated playings. We put everything we know into our Shure Stereo Dynetic Stylus Assemblies — and we tell all about it in an informative booklet. "Visit To The Small World Of A Stylus." For your copy, write:

Shure Brothers Inc.  
222 Hartrey Ave., Evanston, Ill. 60204




Circle 2 on reader service card

JANUARY 1973 • RADIO-ELECTRONICS 1

There's  
an **Amperex**  
replacement tube  
for any socket in any set  
you're likely to service...

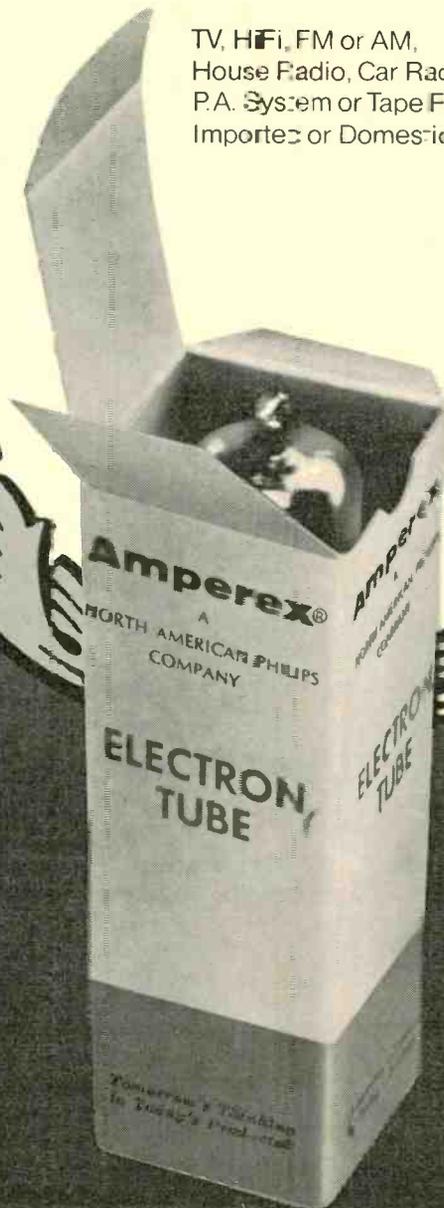TV, HFi, FM or AM,  
House Radio, Car Radio,  
P.A. System or Tape Recorder.  
Imported or Domestic!



AMPEREX SUPPORTS THE INDEPENDENT SERVICE DEALER

**Amperex**

TOMORROW'S THINKING IN TODAY'S PRODUCTS

A NORTH AMERICAN PHILIPS COMPANY

AMPEREX ELECTRONIC CORPORATION, DISTRIBUTOR SALES, HICKSVILLE, NEW YORK 11802

# Radio-Electronics

FOR MEN WITH IDEAS IN ELECTRONICS

January 1973

## COLOR TELEVISION

- 33 **Next Ten Years of Color TV**  
An expert takes a look at tomorrow. *by Bob Gerson*
- 40 **New Circuits For '73**  
A peek at the newest circuits and how they work.  
*by Steve Leckerts*
- 45 **Automatic Color Controls**  
How the various types operate. *by Harold Stevens*
- 60 **Step-by-Step Troubleshooting**  
Inside the AFPC detector. *by Art Margolis*
- 68 **TV Service Clinic**  
Demodularize modular color TV. *by Jack Darr*
- 70 **Reader Questions**  
R-E's Service Editor solves reader problems.

## TEST EQUIPMENT

- 22 **Equipment Report**  
B & K Model 501A curve tracer.
- 56 **Color TV Test Jigs**  
Put one in your shop and leave the pix-tube behind.  
*by Eugene Cunningham*

## AUDIO HI-FI STEREO

- 62 **Zero-Distortion Stereo Preamp**  
Part II: Final construction details. *by Gary Kay*

## GENERAL ELECTRONICS

- 4 **Editorial**  
Serviceability—It's good for everyone.
- 6 **Looking Ahead**  
Tomorrow's news today. *by David Lachenbruch*
- 53 **State Of Solid State**  
New developments in solid-state electronics today.  
*by Lou Garner*
- 88 **Appliance Clinic**  
Interlocks and mental blocks. *by Jack Darr*
- 37 **Add-On Digital Readout**  
Tells ham-receiver frequency precisely.  
*by Larry R. Houghton*


## DEPARTMENTS

- |                   |                         |
|-------------------|-------------------------|
| 26 Letters        | 82 New Products         |
| 12 New & Timely   | 97 Next Month           |
| 90 New Books      | 111 Reader Service Card |
| 80 New Literature | 100 Service Notes       |

102 Try This
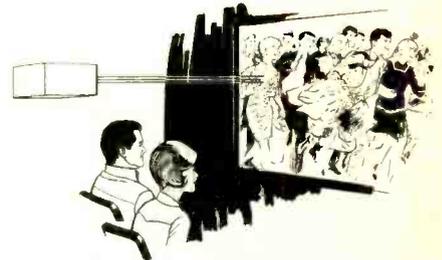
### ON THE COVER

HERE'S A TECHNICIAN'S-EYE-VIEW of the modern color TV receiver. The particular set shown in a G-E JA chassis table model. We feel that this photo symbolizes color TV 1973 to our readers and so we have presented it in this fashion. Obviously, we do not think anyone really sits and watches their color set with the back off.



TV IN THE YEARS TO COME is an ever intriguing subject. Take the laser projection system illustrated here. For more details on what the future might be expected to hold .....see page 33

Hugo Gernsback (1884-1967)  
founder

M. Harvey Gernsback, editor-in-chief  
and publisher

Larry Steckler, editor, CET

Robert F. Scott, W2PWG technical editor, CET

Jack Darr, service editor, CET

Louis E. Garner, Jr., semiconductor editor

I. Queen, editorial associate

Matthew Mandl, contributing editor

David Lachenbruch, contributing editor

James A. Gupton, Jr., photographic electronics

Vincent P. Cienia, production manager

Nancy Gipson, production assistant

H. Matysko, circulation

Cover photograph by Walter Herstatt  
Cover design by Marius Trinque

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics, January 1973, Vol. 44, No. 1. Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York City 10003. Second-class postage paid at New York, N. Y. and additional mailing office. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$7. Pan-American countries, \$8. Other countries, \$8.50. Single copies 60¢. © 1972 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, Colo. 80302.

---

# editorial

## *serviceability—something for everyone*

I had the honor recently of being asked to serve on a National Electronics Association (NEA) serviceability panel. I had heard about serviceability before. General Electric has used it in their color TV advertising and at various Association meetings, groups of technicians would get together to discuss serviceability problems. But this was my first experience on an actual panel.

The panel consists of a group of certified electronic technicians (CET's) who sit down with the set to be rated. There is a complete checklist that is used by the panel members and every aspect of the set that pertains to rapid, accurate service is spelled out and checked. For example, "Is more than one tool required to remove the back of the set?" "Are all service controls accessible through and identified through the back of the set and identified on the chassis? Do non-module transistors plug in? Does shielding interfere with service procedures?"

Each question has a point rating and for the set we checked—a Panasonic CT-70—a maximum total of 805 points was possible. The set received 723 for a serviceability rating of 89.8%.

But the important thing is not the rating that a particular set earns. It is the effects of the rating system that is really meaningful.


1. **The technician benefits**—every technician—the reason is simple. The manufacturer wants his newest set to get as good a rating as possible so the technician will tell his customers how good that brand of set is. To help their ratings, some manufacturers are already making improvements and additions to chassis to enable them to earn higher ratings.
2. **The set owner benefits.** He gets a set that is easier to repair and therefore less expensive to maintain. With the current ever-increasing cost of a service call mandated by the ever-increasing expenses of operating a business and keeping proficient, trained people available; the faster the technician can do the job, the less it will cost. Cut 30 minutes off a repair job and a customer can benefit rather substantially.
3. **The set maker benefits.** He gets word-of-mouth advertising or can use the serviceability rating in his own advertising.

The end result is wider acceptance and cooperation with the serviceability program. At the October meeting of NEA's Board of Directors, ISCET, the International Society of Certified Electronic Technicians, was assigned to administer the serviceability project. ISCET will appoint a new national committee made up of 20 technicians who will perform all official in-plant inspections of TV receivers, stereo phonos, radios and other electronic products ordinarily serviced by independent service technicians.

The beneficiaries will be the consumer who gets his set back from the repair shop sooner; the manufacturer whose product is more easily repaired; and the service technician who can be more efficient and who can charge a legitimate price for the repair rather than having to charge for a lot of wasted time due to poor thought given to "how can this be repaired should it need it?" before the product was built.

Serviceability is indeed something for everyone.

—Larry Steckler, Editor

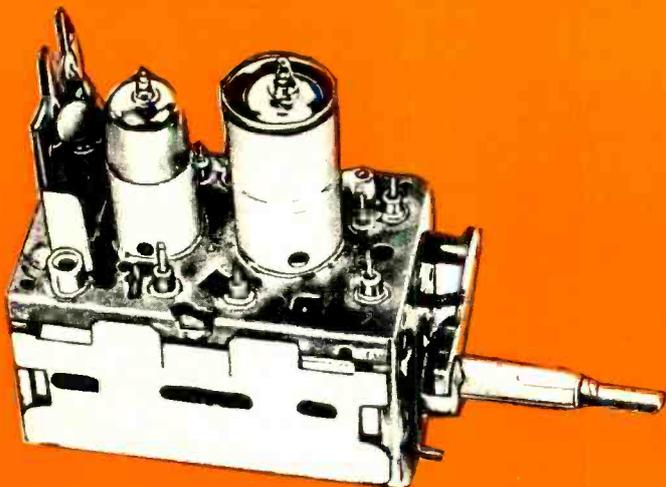

# \$9.75

ALL PARTS  
INCLUDED

ONE YEAR GUARANTEE

## TUNER SERVICE CORPORATION

**PROVIDES YOU WITH A  
COMPLETE SERVICE FOR  
ALL YOUR TELEVISION  
TUNER REQUIREMENTS.**

### REPAIR

VHF Or UHF Any Type \$9.75.  
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged at cost.

Fast efficient service at our 10 conveniently located service centers.

All tuners are cleaned inside and out, repaired, realigned and air tested.



### TUNER SERVICE CORPORATION FACTORY-SUPERVISED TUNER SERVICE

Backed by the largest tuner manufacturer in the U.S.—SARKES TARZIAN, Inc.

<b>HEADQUARTERS</b> .....	537 SOUTH WALNUT ST., Bloomington, Indiana 47401	TEL: 812-332-7251
<b>ARIZONA</b> .....	2629 NORTH FIRST AVE., Tucson, Arizona 85717	TEL: 602-791-9243
<b>CALIFORNIA</b> .....	SARKES TARZIAN, Inc. TUNER SERVICE DIVISION 10654 MAGNOLIA BLVD., North Hollywood, Calif. 91601	TEL: 213-769-2720
<b>FLORIDA</b> .....	1505 CYPRESS ST., Tampa, Florida 33606	TEL: 813-253-0324
<b>GEORGIA</b> .....	938 GORDON ST., S. W., Atlanta, Georgia 30310	TEL: 404-758-2232
<b>INDIANA</b> .....	817 N. PENNSYLVANIA ST., Indianapolis, Ind. 46204	TEL: 317-632-3493
<b>KENTUCKY</b> .....	2920 TAYLOR BLVD., Louisville, Kentucky 40208	TEL: 502-634-3334
<b>NEW JERSEY</b> .....	547-49 TONNELE AVE., Jersey City, New Jersey 07307	TEL: 201-792-3730
	(On U. S. Highway 1 & 9)	
<b>TENNESSEE</b> .....	1215 SNAPPS FERRY RD., Greeneville, Tennessee 37743	TEL: 615-639-8451
	1703 LAMAR AVE., Memphis, Tennessee 38114	TEL: 901-278-4484
<b>VIRGINIA</b> .....	4538 PRINCESS ANN ROAD, Norfolk, Virginia 23502	TEL: 703-855-2518

WATCH US GROW

### REPLACE

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

All shafts have a maximum length of 12" which can be cut to 1½".

Specify heater type parallel and series 450mA or 600mA.

### CUSTOMIZE

Customized tuners are available at a cost of only \$15.95.

Send in your original tuner for comparison purposes to:

Circle 3 on reader service card

# looking ahead

## Report from Tokyo

A recent trip to Japan has served to reaffirm our earlier impression that that country has a very long technological lead over the United States in consumer electronic products, particularly television. Quite possibly the reason is that consumer products are the lifeblood of the Japanese electronics industry, whereas in this country products for the home are secondary to industrial and government electronics.

Whatever the reason, the mere act of watching color television in a Japanese home or hotel can be a real bringdown for an American chauvinist. Color consistency is uniformly excellent from channel to channel—and there are plenty of channels—with hardly any need to make adjustments when changing stations, and never when programs change on a single channel. The main reason for this appears to be the general high quality of transmission standards, paced by the engineering-minded tax-supported NHK network, with ultra-modern computerized equipment and a large and dedicated engineering staff. NHK paces the rival commercial networks and stations, and the competition has produced healthy results.

It's fashionable to make odious comparisons between the American 525-line NTSC color system and the 625-line PAL system used in most European countries. But the color pictures from the 525-line NTSC standards in Japan hold their own against any European pictures, including the excellent ones produced in the United Kingdom and the Netherlands.

Developments in color receivers come rapidly in Japan, and often are put into production while American

manufacturers are debating the financial wisdom of adding similar innovations. For example, in 1972, almost all color sets sold in Japan's domestic market were all-solid-state, while the percentage sold by American manufacturers was just above 20%. The Japanese are now taking another step forward, to color sets coming close to 100% IC. One color set uses 17 ICs; another has 90% of its circuitry on 10 ICs.

The use of wide-angle short color tubes is spreading rapidly in Japan. Virtually every manufacturer is offering sets with 110-degree (or 114-degree, in the case of Sony) deflection, with extremely shallow space-saving cabinets. So far, in the U.S., only one manufacturer is offering one model with 110-degree deflection. The shallow set, obviously, has more sales value in Japan, where livingrooms are small.

The Japanese public is responding to quality color and innovative design. It's estimated that close to 80% of Japan's TV-equipped homes now have color sets, as opposed to a little over 60% in the United States. In 1972, the Japanese public bought about 6 million color sets and fewer than 3 million black-and-white (in the U.S., color and monochrome sales were about evenly divided). The manufacture of black-and-white sets in Japan, in fact, is rapidly disappearing. Increasingly, Japanese TV manufacturers are making or buying their monochrome sets in such lower-wage countries as South Korea and Taiwan.

As labor costs rise, production of television in Japan is becoming increasingly automated. One new Sony Trinitron TV factory we inspected near Nagoya, along with its companion picture-tube plant five miles away, is completely computer-con-

trolled, and virtually all manufacturing processes from the unloading of components through life-testing of completed sets to loading the sets on trucks are automatic.

In 1970 and 1971, Japan was the world's leading producer of television receivers (1972 results aren't in yet). Japanese exports of sets to the United States declined sharply in 1972, because of rising costs and the revaluation of the yen, but a healthy domestic market and an increase in exports to Europe are now taking up most, if not all, of the slack.

The Japanese may have the edge in TV repair service, too. Most people work six days a week and, with the labor shortage in Japan, wives increasingly are working. In most cases, manufacturers operate their own captive service organizations. Many promise same-day TV service—and they're open 365 days a year.

## Another flat picture

Zenith has demonstrated what it calls "the first matrix device to produce a TV picture of sufficient quality to warrant comparison with a cathode-ray tube." The device shown was a thin-panel gas-discharge display only 0.63 inches thick, which provides horizontal resolution of 260 lines, vertical resolution of 350 lines. It actually showed only part of a television picture, 2.4 inches wide by 6.3 inches high. The panel has 80 columns and 212 rows of gas cells which glowed in various intensities of red when excited by varying voltages.

The contrast ratio is an acceptable 40 to 1, while brightness is eight foot-lamberts, considerably below that of existing TV sets but bright

enough for viewing in a normally lit room. A full line of cells is addressed at the same time, in contrast to the spot principle of cathode ray tubes. The incoming video signal is stored in 80 individual capacitors which control current sources for each column.

Is this the flat TV display of the future? Zenith's research vice president, Dr. Robert Adler, was noncommittal: "What we have learned is encouraging. However, there are many problems to be solved before these panels can be considered for product use. The present panel produces a red monochrome picture, and three colors must be generated in the panel. Each column of the display requires a driver which, in a commercial unit, would mean 1500 separate drivers. This will require integrated circuits that will handle the needed voltage. And finally, much higher luminance and better power utilization will be required."

## Number please

Two newly introduced sets by Sharp use the screen to provide a giant channel-number display when the station is tuned. The number occupies about half the screen. The new sets are 17 and 19 inches, and are both remotely controlled. The channel identification remains on the screen for slightly more than a second after the channel is tuned. Sharp has already hinted that it will introduce another version which gives the time in a digital display on the screen upon command. The six pre-set uhf channels are identified as U-1, U-2 etc, not by frequency.

by David Lachenbruch  
CONTRIBUTING EDITOR

# There must be an easier way...



## There is: Sylvania's Chek-A-Color test jig.

TV servicemen were never meant to be movingmen.


But, that was before antique, modern and French Provincial units that included hi-fi, tape decks and record players were built around a large-screen color TV set.

Getting those units to the shop can be a big job.

That's why we developed our two Chek-A-Color test jig units. One, our full-house model, gives everything you need to test a chassis. The other is a basic unit that practically lets you design your own test jig.

All you have to take back to the shop is the electronic guts of the TV monsters.

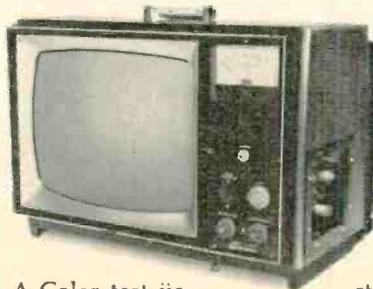Regardless of the size of the original picture, Chek-A-Color lets you see it on a benchtop 14-inch



(diagonal) screen. It adapts to both high and low focus voltage sets and a full line of adapters lets you test over 5,000 different models.

A front-panel switch controls a yoke programming system that gives you a range of impedances and/or deflection voltages to closely match both tube and solid-state systems.

For actual testing, a convenient meter lets you measure anode voltage and a speaker lets you check sound performance.

Since Chek-A-Color handles tube, hybrid and solid-state chassis, there won't be many complete cabinets to lug.

With a Chek-A-Color test jig all you have to take is the chassis. Get the picture? Sylvania Electronic Components,

lets you see it on a benchtop 14-inch

**GTE SYLVANIA**

100 First Avenue, Waltham, Mass. 02154

# NOW you can train at home building a NEW 25" Solid State Color TV engineered by NRI for learning and trouble-shooting

*So much better for learning TV servicing than any hobby kit, because NRI designed and created it as an educational tool.*

Unlike hobby kits which are designed for creating a TV set as the end product, NRI built its exclusive 25" Solid State Color TV kit as a real training kit. You can introduce and correct defects . . . for trouble-shooting and hands-on experience in circuitry and servicing. The kits include a wide-band oscilloscope, color bar crosshatch generator, transistorized volt-ohmmeter and other valuable equipment that can soon have you earning \$5 to \$7 an hour servicing color sets in your spare time.

Handsome woodgrain cabinet, at no extra cost. (Offered only by NRI)

New square-cornered Sylvania picture tube

100% solid state chassis

6-position detented UHF channel selector




Modular construction with plug-in circuit boards

Automatic degaussing


Automatic fine tuning

Automatic color control

Automatic tint control

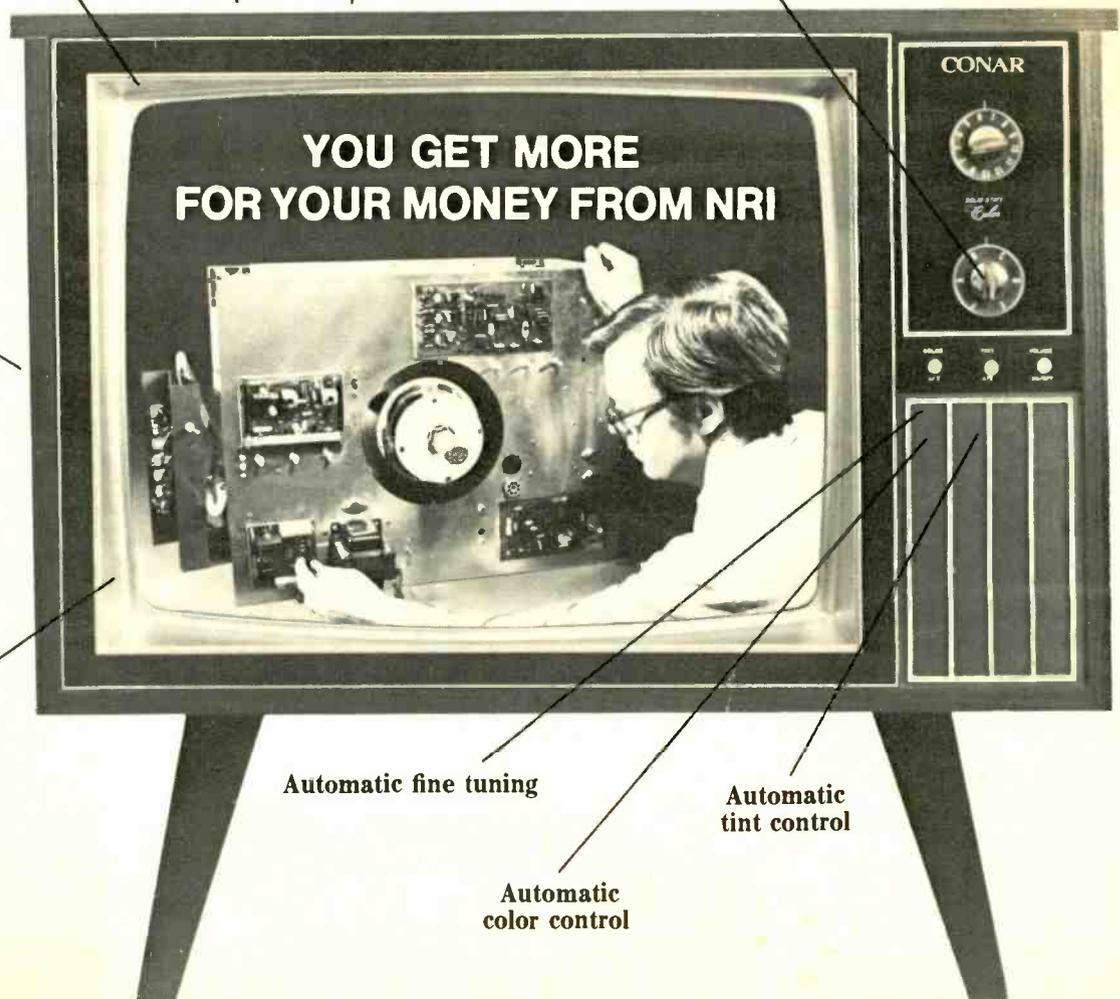
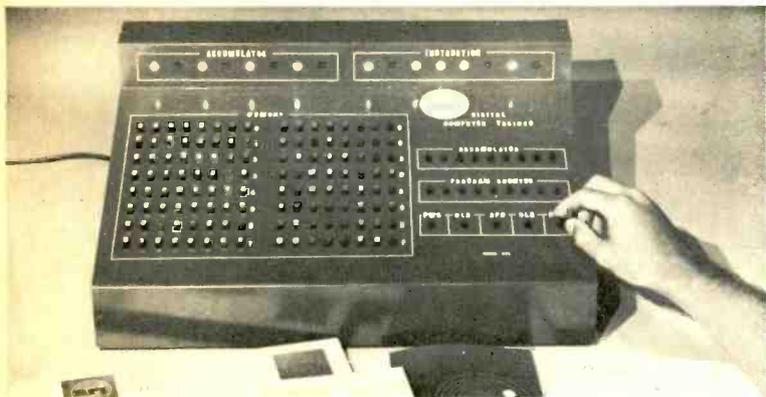
# NRI FIRSTS make learning Electronics fast and fascinating—to give you priceless confidence



**FIRST** to give you a complete programmable digital computer, with memory, you build yourself . . . to learn organization, operation, trouble-shooting and programming. This remarkable computer is one of ten training kits you receive with the new NRI Complete Computer Electronics Course.



**FIRST** to give you true-to-life experiences as a Communications Technician. Every fascinating step you take in NRI Communications training, including circuit analysis of your own 15-watt, phone/cw transmitter, is engineered to help you prove theory and later apply it on the job. Studio equipment operation and trouble shooting become a matter of easily remembered logic.



**FIRST** to give you completely specialized training kits engineered for business, industrial and military Electronics Technology. Shown is your own training center in solid-state motor control and analog computer servo-mechanisms. Telemetering circuits, solid-state multivibrators and the latest types of integrated circuits are included in your course.

The NRI color TV and digital computer kits are the latest in a long line of "firsts" for NRI. For more than fifty years, NRI has been providing unique 3-dimensional home-study training that has helped hundreds of thousands of students reach their goals quickly and easily.

What NRI provides is a combination of kits and bite-size texts that give you hands-on experience while you are learning. The texts average only 40 pages each, and they are fully illustrated. You are taken step-by-step from the first stages into the more advanced theory and techniques . . . with an expert instructor ready at all times to provide valuable guidance and personal attention. (The level of personal attention provided is more than you would receive in many classrooms.) Once you've grasped the fundamentals, you move with confidence and enthusiasm into new discoveries in the fascinating world of electronics.

You start out with NRI's exclusive Achievement Kit, containing everything you need to get moving fast. Lessons have been specifically written so that experiments build upon one another like stepping stones. You can perform a hundred experiments, build hundreds of circuits . . . as you learn to use the professional test equipment provided, building radios and TV sets, transmitter or computer circuits. It's the priceless "third dimension" in NRI training . . . practical experience.

## Train with the leader—NRI

Compare training kits, texts, techniques and overall training . . . and you'll find that you get more for your money from NRI. Whatever your reason for wanting more knowledge of Electronics, NRI has an instruction plan that will meet your needs. Choose from major programs in Advanced Color TV Servicing, Complete Computer Electronics, Industrial Electronics and the other special courses designed to meet specific needs. With NRI home training, you can learn new skills while you're still working at your present job . . . and turn yourself into the man in demand.

### GET FACTS ABOUT GI BILL

If you have served since January 31, 1955, or are in service now, check GI line on postage-free card.

## Send for free NRI catalog

MAIL THE POSTAGE-FREE CARD FOR THE FREE NRI CATALOG IN THE FIELD OF YOUR CHOICE. YOU WILL BE UNDER NO OBLIGATION. NO SALESMAN WILL CALL.

If the card has been used, write direct to:



**NRI TRAINING**


3939 Wisconsin Ave.  
Washington, D.C. 20016

# new & timely
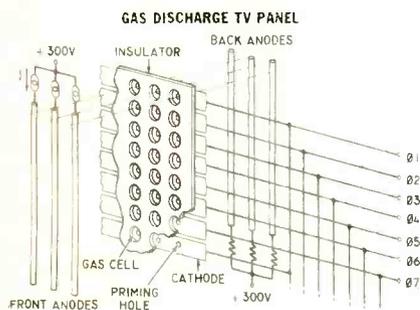
## Zenith demonstrates flat TV using a neon-tube array

A new thin-panel television display using gas-discharge tubes (tiny neons, in this case) was demonstrated by Zenith Radio at the IEEE Conference on Display Devices in New York City October last. The experimental display demonstrated is 2.4 inches wide and 6.3 inches high, and has 212 rows and 80 columns of gas tubes. Thickness is only 0.63 inch. Peak luminance is 8 foot-lamberts and usable contrast ratio 40 to 1.

Though peak brightness is lower than that of a standard TV set, the new panel produces a picture that is easily visible under normal room lighting. It is "the first matrix device to produce a TV picture of sufficient quality to warrant



**MUCH MAGNIFIED AND SIMPLIFIED** view of the thin-panel television display. To get an idea of the real size, remember that there are 80 columns in the 2.4-inch width of the display.

comparison with a CRT," Zenith's vice-president of research, Dr. Robert Adler, told the conference.


The system uses the crossbar approach, as seen in the drawing. A full horizontal line of cells is addressed at one time, in contrast to the sequential dot-by-dot lighting of the conventional picture tube. The video signal for each line is stored in each of the vertical columns. These discharge simultaneously for each line. Variation of charge in the capacitors produces a wide-range gray scale.

Dr. Adler pointed out that much remains to be done before the experimental system can be put to commercial use. The present picture is red, and panels for two more colors must be produced. Since each column requires a separate driver, a full-width display would have to have 1500 drivers. This will necessitate development of integrated circuits that can handle the required voltages. Luminance will have to be increased and better power utilization achieved, said Dr. Adler.
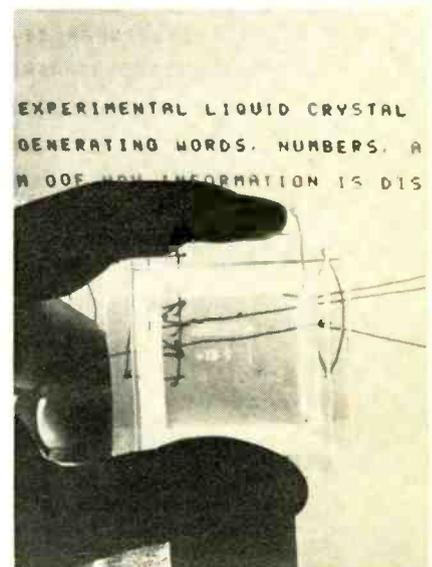
## New display device uses liquid crystals

Laser-driven liquid crystal displays are now being considered for use at Bell Labs in an experimental remote black-board system for exchanging hand-written information over the telephone lines.

The liquid crystal cells, or light valves, are made with two sheets of glass about the size of 35-mm projector slides. The inner surface of the glass plates is coated with a thin film of indium-tin-oxide that absorbs light from a focused laser beam and converts it to




**A LIQUID CRYSTAL SLIDE**, containing information written by laser light. Behind is a screen on which a duplicate of the information is projected with an ordinary slide projector.

heat. The liquid crystal between the plates is of the type called cholesteric, a mixture of 90% MBBA (p-methoxybenzylidene-p-n-butylaniline) plus 10% cholesteryl nonanate.

The laser beam is controlled by two devices, a scanning galvanometer that scans horizontally and an acoustic-optic deflection modulator, which supplies the vertical sweep and turns the laser light source on and off during character generation. The beam heats the portion of the light valve's metallic layer directly ahead of it, turning the area of the liquid crystal in contact with it from transparent to a frosty white. If the light valve is located in a slide projector, the frosted portion stops the light, giving a black-and-white display on an ordinary movie screen.

The images remain on the crystal for weeks, or until erased with an audio voltage (about 35 volts at 1.5 kHz) is applied via the conducting indium-tin-oxide layers.

*(continued on page 14)*

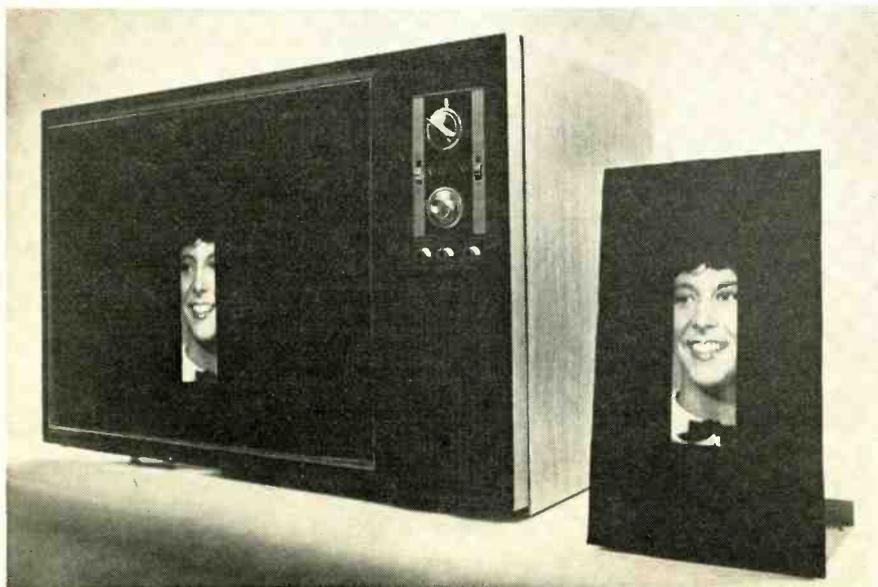

**THE THIN-PANEL DISPLAY COMPARED** with an equivalent area on a 25-inch TV set. The brightness of the TV set has been turned down to match that of the thin-panel picture.



# FREE

send today for the *all-new*

# Olson

## 1973 CATALOG

**NOW** the only catalog offering a wide selection of the best of **THE FAMOUS ELECTRONIC BRANDS** plus the exclusive Olson values!

ALL-NEW ANNUAL

## save now on everything in electronics

### YOUR COMPLETE BUYING GUIDE

Big! Beautiful (many full-color pages)! Value-packed! Your one dependable source for everything in audio and electronics. Enjoy every buying advantage at Olson: low money-saving prices, fastest shipment, personal service, satisfaction guaranteed or money back.

### Olson Exclusive Values

Besides the best of the famous brands you'll find 100's of money-saving items sold only by Olson. See our all-new TELEDYNE stereo line, recorders & radios, parts bargains.

- Stereo components & the newest in 4-channel
- Tape recorders & recording accessories
- Radios & phonographs of all kinds
- Money-saving do-it-yourself kits
- Auto electronics & accessories
- Citizens Band two-way radios
- VHF & UHF police/fire monitors
- Amateur radio station equipment
- Public address & intercom systems
- Test Gear • Parts bargains
- Electronic security equipment
- TV-FM antennas & accessories
- Books, tools, hardware, parts
- Batteries, transistors, tubes, wire, cable, & more!

**FREE**



### MAIL COUPON NOW

OLSON ELECTRONICS Dept. LB, 260 S. Forge St., Akron, Ohio 44327

Rush FREE 1973 Olson catalogs to:

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

more of the best  
of everything  
in electronics

**Olson Electronics**  
where the values are!

Circle 4 on reader service card

# new 19-piece midget reversible ratchet offset screwdriver set



3-3/4" heavy duty, stainless steel reversible 20-tooth ratchet with short turning radius for close work.

Unique 6" spinner/extension has drive socket insert in handle for ratchet. Use also as regular screwdriver with bits.

1/4" hex to 1/4" square adapter bit permits use of ratchet or spinner/extension with Xcelite Series 1000 or other 1/4" sq. drive sockets.

16 precision made, alloy steel bits with knurled spinner tops . . . 12 Allen hex type, 2 slotted screw bits, 2 Phillips bits.

**FREE STICK-ON INITIALS** personalize the sturdy plastic case and help prevent loss or mix-up.

No. XL-70 Set

Made in U. S. A.



Also 5-Piece Kit (No. XL-75) Reversible ratchet with 3/16" and 1/4" slotted screw bits, #1 and #2 Phillips bits, all in a durable plastic, pocket size, snap fastener case.

nationwide availability through local distributors

REQUEST BULLETIN N770



XCELITE, INC., 10 Bank St., Orchard Park, N. Y. 14127  
In Canada contact Charles W. Pointon, Ltd.

Circle 5 on reader service card

# new & timely (continued from page 12)

## Service Association Merger Makes substantial progress

The Merger Committees of NATESA and NEA met jointly Friday evening and Saturday, September 29 and 30, 1972, at the Admiral Ben Bow Hotel, Memphis, Tenn. to discuss problems associated with merging the two associations. Morris Finneburgh, Sr., acted as Chairman and Coordinator.

ment contacts and publicity, and that Mr. Glass would be in charge of internal and administrative affairs.

The Joint Committee agreed unanimously on continuation and maximum support of the CET program and development of a "shop certification" program similar to that initiated by NATESA.

A second Joint Committee meeting was set for the first week of December



**THE JOINT COMMITTEE.** Standing, left to right: Clifford Shaw, Gerald Hall, Paul Dontje, Edward Gorman, George Weiss and Emmett Hughes. Seated: Charles Couch, Leroy Ragsdale, M. L. Finneburgh, Sr., Norris Brown, Virgil Gaither.

Present were Leroy Ragsdale (Arkansas), Gerald Hall (Milwaukee), Clifford Shaw (Virginia), George Weiss (Chicago), and Edward Gorman (New York) of the NATESA merger committee, and NEA committee members Norris Brown (Houston), Charles Couch (Florida), Virgil Gaither (California), Emmet Hughes (Kansas) and Paul Dontje (Denver).

Plans were set up for a sub-committee to develop a package including a constitution, by-laws and procedure for the election of a board of directors and officers. The name NESDA (National Electronic Service Dealers Association) was tentatively proposed for the new organization.

It was agreed unanimously that Frank Moch of NATESA and Richard Glass of NEA would be Executive Vice Presidents of the new organization, with the suggestion that Mr. Moch would be responsible for public relations, govern-

ment contacts and publicity, and that Mr. Glass would be in charge of internal and administrative affairs.

## "Talking feet" transmit signals for therapeutic study

Shoes rivalling the famous one used on television by Maxwell Smart are being constructed by technicians in the Royal Aircraft Establishment in Farnborough, England. Their objective differs from Maxwell's—they are making the shoes to permit doctors to measure improvements in patients with hip joint diseases. Previously this could be done only by using cumbersome walkways based on a weightbridge principle. In the newer system, the patient simply walks around while the shoes transmit data on the loads and stresses involved in walking.

The soles of the shoes are made up of flexible metal filigree sheets sand-

(continued on page 16)

# AT YOUR DESK OR ON THE MOVE... MITS HAS A CALCULATOR FOR YOU!

## THE 1200 SERIES



ACTUAL SIZE  
5 1/4" H x 3 1/4" W x 1 1/2" D  
Hi-impact ABS case

### PRICES:

1206 (6 digits) Assembled \$59.95  
1209 (9 digits) Assembled \$79.95  
1212 (12 digits) Assembled \$99.95

**AC ADAPTER** Equips any MITS 1200 Series pocket calculator for operation from 117 VAC... \$6.95

## 1230 & 1240

Send for our newest 4-function calculators, the 1230 & 1240 - both are 12-digit desk top models featuring Sperry gas discharge displays, true credit balance sign display with leading zeros suppressed, and automatic overflow indication. In addition to the standard functions, the 1240 has a memory storage register and fixed decimal point from 0 to 5 places.

1230 Kit: \$89.95  
1240 Kit: \$119.95

Use Your BankAmericard or Master Charge

NOW A 12-DIGIT CAPACITY IN A POCKET CALCULATOR FOR \$59.95. ADDS... SUBTRACTS... MULTIPLIES... DIVIDES... INSTANTLY & ELECTRONICALLY!

Everyone can use it... now you can figure, in minutes, what might have taken hours the old way... credit balances, budgets, income taxes, percentages, monthly statements, grocery lists, and on & on.


3 MODELS, ALL WITH 12-DIGIT CAPACITY

The 1212 displays 12 digits... the highest display capacity of any pocket calculator we know of... 9,999,999,999.99. The 1209 displays 9 digits; the 1206, 6 digits.

### CHECK THESE FEATURES

- Four Functions!
- Bright LED Display!
- Raised Keys!
- 100% American Made!
- Leading Zero Suppression!
- Fixed Decimal Output!
- True Credit Balance Sign Display!
- Chain and Mixed Operation!
- Automatic Display Cut-off!
- Clear and Clear Entry Keys

## THE 7400

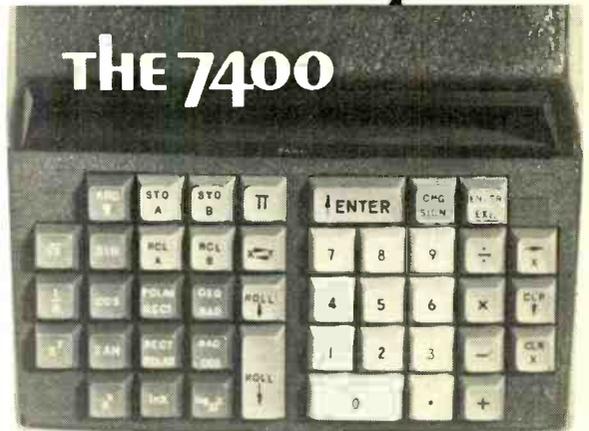

### THE MOST POWERFUL SCIENTIFIC DESK CALCULATOR FOR UNDER \$500.00

The price of the 7400 is low enough to make a desk top computer available to almost anyone.

SIGNIFICANT FEATURES NOT FOUND IN MOST COMPETITIVE MACHINES

- DYNAMIC RANGE: 10-99 to 10<sup>99</sup>
- DATA STORAGE: 2 Auxiliary Storage Registers plus up to 7 push-up Stack Registers.
- Roll up and roll down keys for complete control of operational stack
- Interfacing provisions for printer and programmer
- Correct X (Allows the operator to correct one digit, without re-entering the whole problem)
- Polar to Rectangular conversion and Rectangular to Polar conversion

DISPLAY: Either full floating or scientific notation, 14 large, easy-to-read digits.

SIZE: 8 1/2" x 12" x 3 1/2"

WEIGHT: 4 lbs.

7400A 3 Registers ..... Kit \$299.95  
Assembled \$379.95  
7400B 5 Registers ..... Kit \$319.95  
Assembled \$399.95  
7400C 7 Registers ..... Kit \$339.95  
Assembled \$419.95

### PRICES INCLUDE CARRYING CASE

MITS will repair any 7400 for a fee of \$25.00 for a 5-year period after the normal 1-year warranty has expired.

# MITS®

WRITE OR MAIL COUPON FOR  
ADDITIONAL INFORMATION:

## Micro Instrumentation & Telemetry Systems, Inc.

5404 Coal Ave., S.E., Albuquerque, New Mexico 87108

505/265-7553

Circle 6 on reader service card

ENCLOSED IS CHECK  KIT  
FOR MODEL # \_\_\_\_\_  ASSEMBLED

AMOUNT OF CHECK \$ \_\_\_\_\_  
Include \$5.00 for postage and handling.

Please send information on entire MITS line.

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE & ZIP \_\_\_\_\_


R1-73

# YOKES for every use

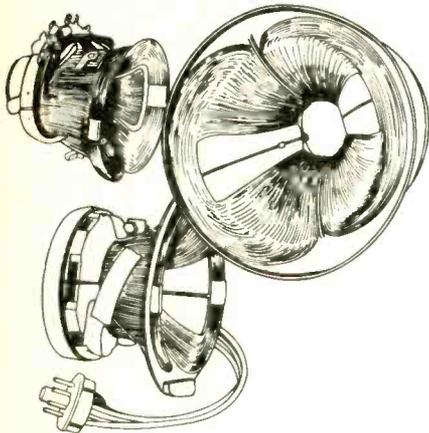

Triad makes a variety of deflection yokes for the majority of the television receivers in use today—some complete with plug, leads and network for specific application; others with toroidal winding for multi-purpose use (YT's); "mini-yokes" for color sets; and smaller ones yet for use in domestic and foreign sets with 20 mm. CRT neck size. Triad-Utrad makes many of the original yokes used today in popular color TV receivers. The replacement units reflect the sound engineering and workmanship that goes into the original.

# FLYBACKS too.

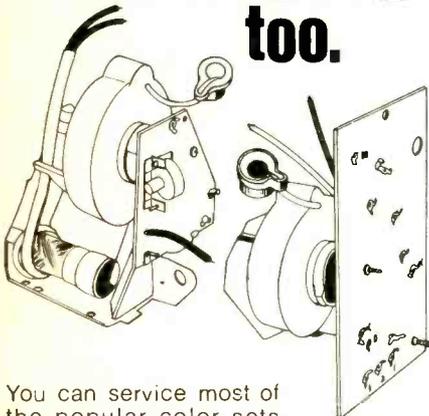


You can service most of the popular color sets with a Triad exact replacement flyback. For your convenience, we carry a great many flybacks for new black-and-white sets—both domestic and foreign—and also most of the older models. All of these are listed in Sams Photofacts and Counter Facts. Have your distributor refer to his counter copy for the recommended Triad replacements in the sets you are working on. And, be sure to get the Triad TV Replacement Guide. Write to Triad-Utrad Distributor Division, 305 N. Briant St., Huntington, Ind. 46750.

 **TRIAD-UTRAD DISTRIBUTOR**  
Litton 305 North Briant Street, Huntington, Indiana 46750

Circle 7 on reader service card

# new & timely (continued from page 14)

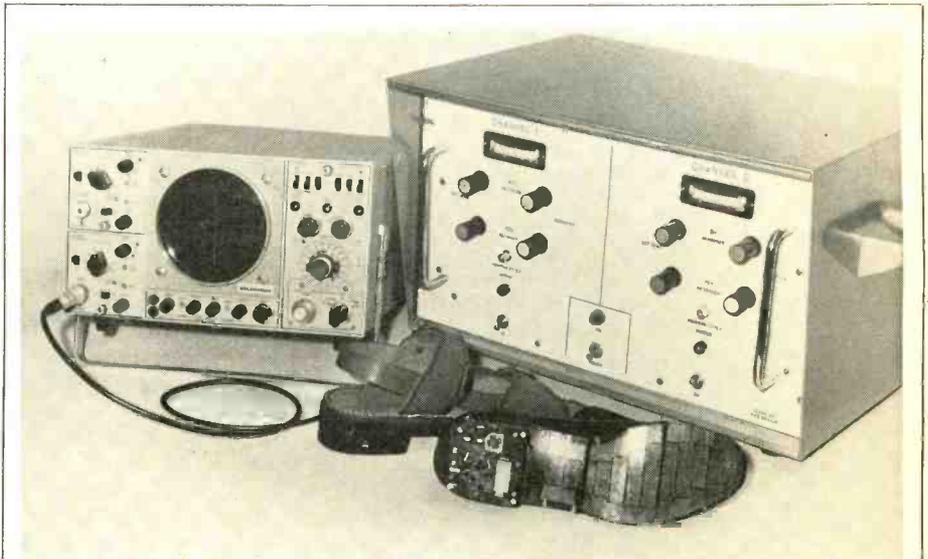

wicked between layers of spongy rubber. When the patient walks the rubber compresses, reducing separation between the sheets. Changes in capacitance resulting from the pressure modulate an oscillatory circuit in the heel of the shoe, and the signals are coupled inductively to a pickup wire strung around the room.

The photograph shows the two receivers, one for the right and one for the left foot, and the scope on which the signals are displayed. The shoes are in the foreground. Like those of Maxwell Smart, they have all the electronics—plus the battery—in the heel (with the capacitive sensors in the sole). **R-E**

**Radio-Electronics** is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, N.Y. 10003 (212) 777-6400  
President: M. Harvey Gernsback  
Secretary: Bertina Baer

## ADVERTISING SALES

**EAST**  
Stanley Levitan, Eastern Sales Mgr.  
Radio-Electronics  
200 Park Ave. South  
New York, N.Y. 10003  
(212) 777-6400

**MIDWEST/Texas/Arkansas/Okla.**  
Ralph Bergen  
The Ralph Bergen Co.  
6319 N. Central Ave.  
Chicago, Ill. 60646  
(312) 792-3646

**PACIFIC COAST/Mountain States**  
Jay Eisenberg  
J.E. Publishers Representative Co.,  
8560 Sunset Blvd.,  
Suite 601,  
Los Angeles, Calif. 90069  
(213) 659-3810  
420 Market St.,  
San Francisco, Calif. 94111  
(415) 981-4527

**SOUTHEAST**  
E. Lucian Neff Associates  
25 Castle Harbor Isle,  
Fort Lauderdale, Florida 33308  
(305) 566-5656

## MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH  
LABEL  
HERE


name (please print)

address

city state zip code

Mail to: Radio-Electronics  
SUBSCRIPTION DEPT., BOULDER, COLO.  
80302

SONY

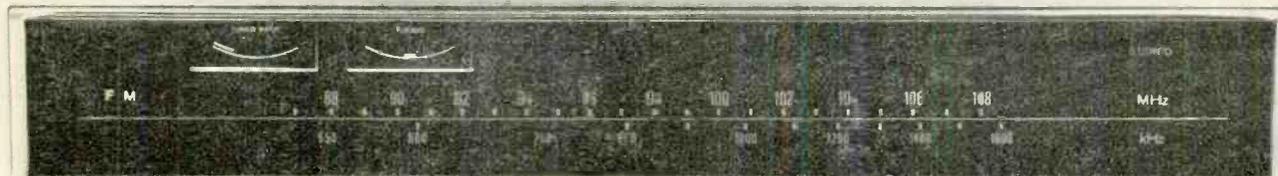

POWER



FM STEREO / FM-AM TUNER  
ST-5150  
SOLID STATE

HI-BLEND



MUTING



FUNCTION



TUNING



## Introducing our home-made tuner

The new Sony ST-5150, FM stereo/FM-AM tuner. It uses nothing but transistors, and FETs, and integrated circuits, and solid-state filters that we made ourselves. That way we can be sure of having whatever components our circuitry demands rather than having to adapt our circuit ideas to the available components.

In our front end, for instance, a new type junction FET in the mixer and RF stages contributes exceptionally high sensitivity (2.0 $\mu$ V, IHF), overload capability, image rejection (70dB), cross-modulation rejection, and low internal noise.

In the IF section, newly-developed, high-reliability Sony ICs give the 5150 a superior capture ratio (1.0dB),

AM suppression (56dB) and signal-to-noise ratio (70dB). And our solid-state IF filters contribute to the tuner's excellent selectivity (70dB, IHF) as well as its long-term stability (they never need realignment).


For optimum stereo separation and durability, we use still another high-reliability IC, and newly-designed, coil units, in the FM multiplex section. Even the AM section has one of our ICs, and more of our triple-tuned solid-state filters, for high sensitivity, minimum distortion and superior signal-to-noise ratio.

And the 5150 has all the features you need to make the most of this performance: signal-strength & center-channel meters plus multipath

scope outputs, for more accurate tuning; a high-blend switch and defeatable muting to help you pick up weaker signals, when you want them (and by-pass them, when you don't); a 75-ohm coax antenna connector for cleaner reception in areas with lots of interference.

Yet the price, (we also save you money by making our own semiconductor) is only \$229.50\*. The TA-1150, a superb integrated amplifier, matches the 5150's performance, appearance and price, \$229.50\* Sony Corporation of America, 47-47 Van Dam Street, Long Island City, N.Y. 11101. \*Suggested retail price.

**SONY® ST-5150**

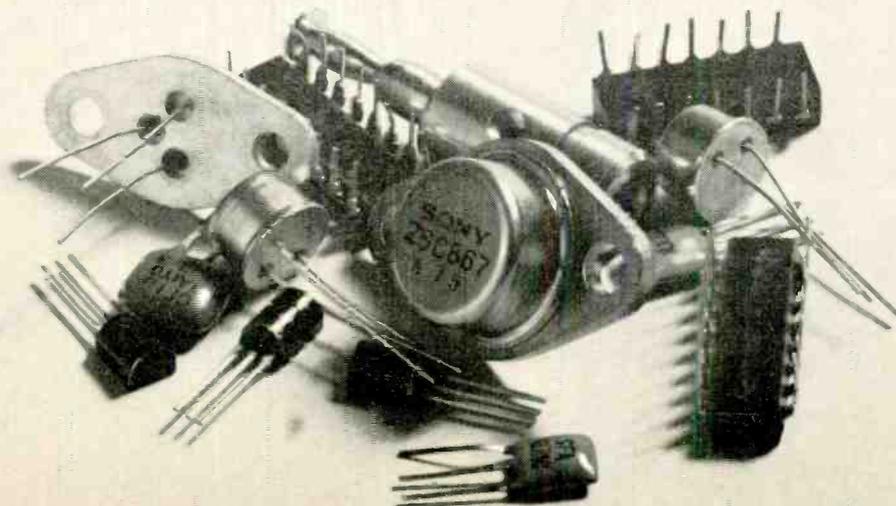

Circle 8 on reader service card

# PREPARE FOR A WHOLE NEW CAREER IN HOME ENTERTAINMENT ELECTRONICS



## ...AS YOU BUILD YOURSELF A BELL & HOWELL SOLID STATE COLOR TV!

For free information, mail postage-free card today!

## A complete at-home learning program in home entertainment electronics!

Send for free information now about this complete, learn-at-home program in home entertainment electronics prepared for you by skilled instructors at Bell & Howell Schools.

### Work on this exciting "hands on" project integrated into your learn-at-home program!

As part of your complete electronics education, you build and keep a Bell & Howell solid state color television set. This important project gives you valuable "hands on" experience with solid state circuitry—the kind of *practical* experience you'll need to build a successful career.

### Attend special "help sessions" ... talk to your instructors in person!

If you'd like some personal advice at any point in your program, you can arrange to attend a special "help session" and talk over special problems with a qualified Bell & Howell Schools instructor.

### Master the most up-to-date solid-state circuitry

As color TV moves more and more in the direction of *total* solid-state circuitry, you'll be thoroughly familiar with the most advanced "trouble-shooting" techniques for these sophisticated circuits.

### Fix stereo systems ... FM-AM radios ... phonographs ... tape recorders

The thorough knowledge of electronics you gain from completing this course and building your own color TV set will be enough to service almost any type of home entertainment electronic device—even some that aren't on the market yet!

### Earn extra part time income — or start a business of your own!

The skills you acquire through this brand-new program can help you earn extra money—or start a business of your own in color TV servicing. We've helped many thousands of people start new careers or businesses of their own in electronics.

### Exclusive Electro-Lab® — yours to keep!

To make sure you get practical experience with instruments used daily by professionals, we've integrated into your program three precision instrument kits you assemble yourself and keep: a Design Console, an Oscilloscope and a Transistorized Meter. (See details at right.)

**For Free Information,  
Mail Card Today!**



#### ■ Bell & Howell Solid State 25-inch color TV.

Ultra-rectangular 315 sq. inch screen lets you view more of the image. 25,000 volts . . . 46 transistors . . . 57 diodes . . . 4 IC's with another 54 transistors and 15 diodes . . . 3 stage solid-state, high-gain IF . . . 24 channel detent UHF/VHF power tuning . . . varactor UHF tuner . . . automatic fine tuning.

■ **Design Console** Use this to rapidly "bread-board" circuits without soldering. Equipped with built-in power supply . . . test light . . . speaker . . . patented plug-in modular connectors.

■ **Oscilloscope** Portable 5-inch wide-band oscilloscope offers bright, sharp screen images . . . calibrated for peak-to-peak voltage and time measurements . . . 3-way jacks for leads, plugs, wires.

■ **Transistorized Meter** Combines most desired features of vacuum-tube voltmeter and quality multimeter. Registers current, voltage and resistance measurements on a large, easily-read dial. Features sensitive, 4-inch, jewel bearing d'Arsonval meter movement.

345

If card has been removed, write:

An Electronics Home Study School  
DeVRY INSTITUTE OF TECHNOLOGY



ONE OF THE  
**BELL & HOWELL SCHOOLS**

4141 Belmont, Chicago, Illinois 60641

If paging speakers all seem about alike to you...wait 'til you get to the top of the ladder to install them!



Electro-Voice Paging Speakers ...  
If you pay less it may cost you more!

How many trips up the ladder does it take you to finally install a paging speaker? (Be honest and include the times you drop hardware, and the extra trips to change level or positioning). Good news! E-V has made paging speaker installation easier and faster.

Now you need fewer tools and less time to get better sound. Speaker base removes for easy mounting, and it won't fall apart in your hands in the process. There are no screw terminals to short out, pigtailed are already attached, no transformer cover plates to unscrew, and final speaker positioning is simple and positive.

All this and great sound in the bargain. Plus competitive prices on every model. More than a dozen from which to choose. Write today for our catalog or see your nearby Electro-Voice sound merchant.

ELECTRO-VOICE, INC., Dept. 136E,  
613 Cecil Street, Buchanan, Michigan 49107  
In Europe: Electro-Voice, S. A., Romerstrasse 49, 2560 Nidau, Switzerland  
In Canada: EV of Canada, Ltd., Ontario

**Electro-Voice**

a Gulton  
COMPANY

Circle 9 on reader service card

# equipment report

## B&K model 501A Transistor Curve Tracer



Circle 26 on reader service card

THE TRANSISTOR CURVE TRACER IS THE latest of the laboratory instruments (the first was the oscilloscope) to turn up on the service bench. B&K has brought it out, quite literally, in a "Black-Box" it calls *Model 501A*. In engineerese, a Black-Box is any complex piece of equipment in a simple-looking box with a couple of terminals that will do a lot of things. Inside, it's very complex but it's simple to operate.

The model 501A is built in a flat, "lay-down" case. This makes it very easy to use; all controls are very accessible. All you need is any standard service scope. The 501A provides the calibration. Setting up can be done in about 30 seconds, and the scope controls aren't moved from then on. All adjustments are made with the curve-tracer controls.

Its purpose is simple: it tests transistors. It does this by "making them work," just as if they were in a circuit. The display indicates normal or abnormal operation. It will tell you instantly if a transistor is good, leaky, open, shorted, or has any other defect. It is purely a Go/No-Go test, and as useful as all of these tests are.

The 501A has two TO-5 transistor sockets with three banana jacks for each socket. The B&K FP-3 probe can be plugged into the jacks. The probe has three swiveled pins, very sharp and spring-loaded, making ideal for

penetrating coatings, etc., on solder joints. It can also be used "one-handed" so that the other hand can be used to set the tracer controls.

This is the part that impresses me more than anything else. The probe lets you make valid *in-circuit* tests, a vital consideration with today's equipment. You can actually "go into" a three or four-stage transistor amplifier to get a check on *each* transistor without disconnecting anything! This is a test that has been very difficult to make in the past, and one that will be more and more necessary in the future.

Explained as briefly as possible, a curve-tracer applies a swept collector voltage to the transistor (in the 501A, up to 100 volts at 100 mA). A staircase of current steps is applied to the base, from 1.0  $\mu\text{A}$  per step up to 2.0 mA per step. This causes the scope to display a "family" of curves, one for each step of base current. This is the key pattern: no family, no work.

Ac and dc beta, gain, load-lines, leakage, shorts, opens and collector voltage breakdown can be read from the family of curves. In other words, curve, GO; no curve, NO GO. Reverse breakdown voltage can also be tested and read from the scope. Diodes of all kinds—Zeners, rectifiers, detectors, switching diodes can be checked. FET's of all types (J-FET's, MOS-FET's,) plus UJT's and SCR's can all be tested the same way and with the same ease. For FET testing, voltage steps are provided on the step selector switch.

A polarity switch is mounted on the panel for testing npn or pnp transistors. Just below this is the selector switch for hooking up either the right or left transistor socket or probe-jacks. This is very useful for matching transistors of all kinds. The two transistors are plugged into the sockets, and a curve is set up on the screen for either one. The selector switch is then flipped to the other side; if the transistors match, the curve will remain the same. Even complementary-symmetry output transistors (pnp/npn) can be checked for matching. All you need to


(continued on page 96)

# Radio Shack Solid State Math!


# 29 TRANSISTORS

Equal

# 15000 TRANSISTORS!

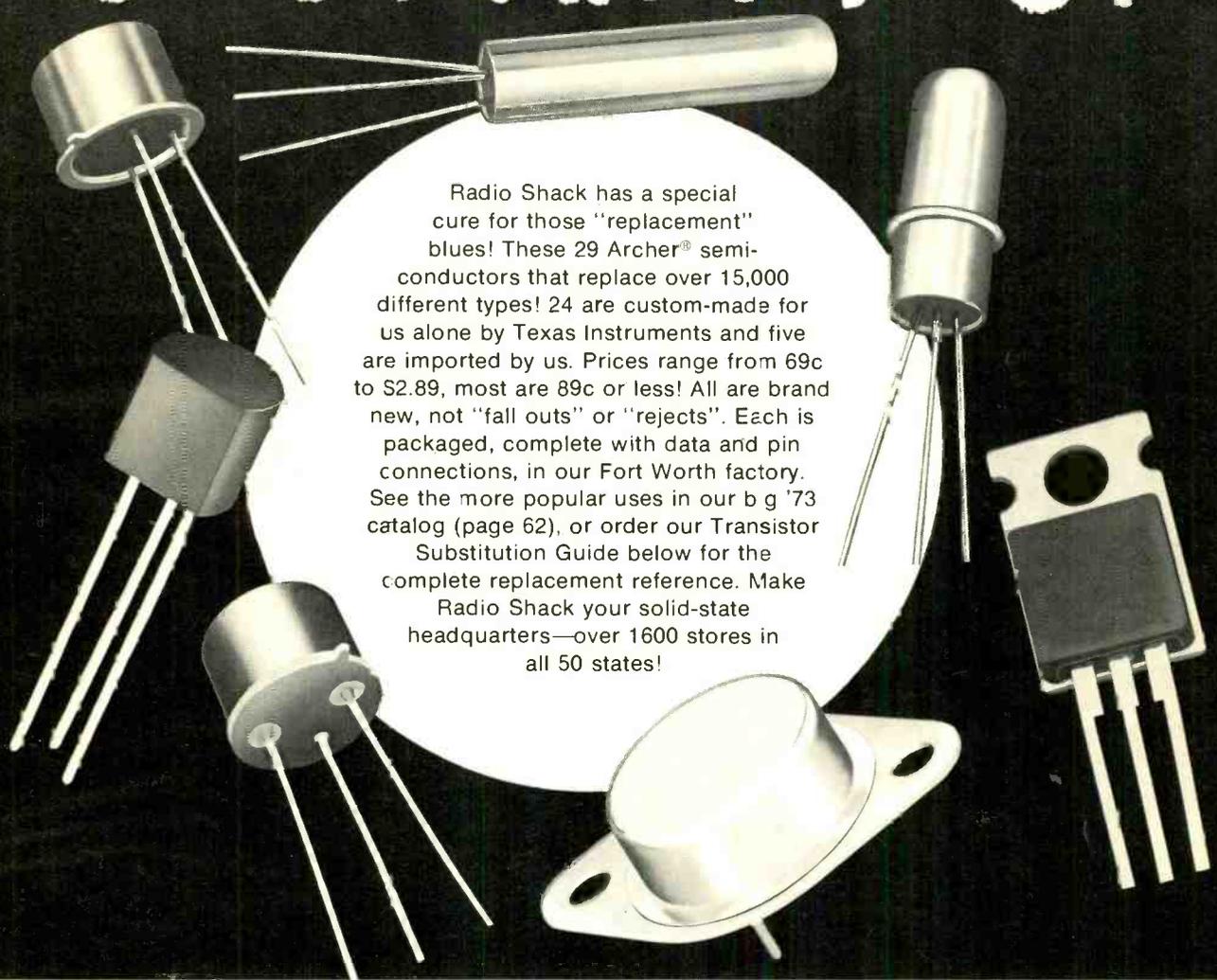

Radio Shack has a special cure for those "replacement" blues! These 29 Archer® semi-conductors that replace over 15,000 different types! 24 are custom-made for us alone by Texas Instruments and five are imported by us. Prices range from 69c to \$2.89, most are 89c or less! All are brand new, not "fall outs" or "rejects". Each is packaged, complete with data and pin connections, in our Fort Worth factory. See the more popular uses in our b g '73 catalog (page 62), or order our Transistor Substitution Guide below for the complete replacement reference. Make Radio Shack your solid-state headquarters—over 1600 stores in all 50 states!

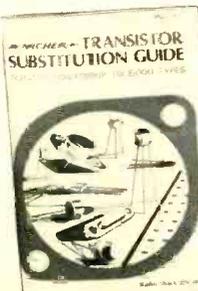

Dept. LB. 123  
2617 W. 7th St., Fort Worth, Texas 76107

Rush me \_\_\_\_\_ Archer Transistor Substitution Guides at \$1.00 each postpaid (plus applicable sales taxes).

Check or money order for \$ \_\_\_\_\_ enclosed.

Send FREE Catalog

Please PRINT Clearly.

Name \_\_\_\_\_ Apt. # \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip

## Radio Shack®

and ALLIED RADIO STORES

A TANDY CORPORATION COMPANY

P. O. Box 1052, Fort Worth, Texas 76107

Circle 10 on reader service card

JANUARY 1973 • RADIO-ELECTRONICS 23



# 10 exciting new Heathkit projects you can assemble yourself ...and save!

(There are 350 more in your  
free '73 Heathkit Catalog)



## NEW Heathkit 21V Color TV — Solid-State Plus Detent UHF Tuning... 499.95\* less cabinet

Power detent selection of all VHF and any 12 pre-selected UHF channels; exclusive angular tint control for consistently better flesh tones; voltage controlled varactor UHF tuner & MOSFET VHF tuner for unmatched sensitivity; black matrix tube, built-in dot generator, convergence panel and volt-ohm meter — full remote control options, too. It's Heathkit TV at its finest in a space-saving size.

Kit GR-271, less cabinet, 121 lbs. .... 499.95\*  
Assembled GRA-501-21, table model cabinet shown,  
tough walnut Marlite® finish, 33 lbs. .... 54.95\*

## NEW Heathkit 30 MHz Counter... 169.95\*

Gives 1 Hz to over 30 MHz counting on a full 5-digit readout with 8-digit capability. The lighted overrange indicator makes misreading virtually impossible. Stable timebase circuitry assures accuracy better than ±3 ppm from 22° to 37° C. Diode protected J-FET gives improved triggering over 100 mV to 150 V input range. Solid-state circuitry mounts on one large board.

Kit IB-1100, 6 lbs. .... 169.95\*

## NEW Heathkit 2½-Digit VOM... 79.95\*

Four overlapping ranges to measure voltages from 10 mV to 1000 V on DC (either polarity), 10 mV to 700 V rms on AC, 10 uA to 2.5 A on AC or DC current. Five resistance ranges measure from 1 ohm to 2 megohms. Front panel polarity switch reverses inputs without changing leads.

Kit IM-1202, 6 lbs. .... 79.95\*

## NEW Heathkit/Thomas Spinnet Organ with two 44-note keyboards... 689.95\*

Full 44-note keyboards for Solo and Accompaniment, exclusive Color-Glo keys that light up to indicate notes and chords. There are six solo stops, five accompaniment stops, plus both regular and a new "light" vibrato effects. Other features include keyboard jacks for private earphone listening or use of a tape cassette deck. Cabinet is shipped fully assembled, includes bench.

Kit TO-1160, 211 lbs. .... 689.95\*



See them all  
in this NEW  
FREE CATALOG

## NEW Heathkit Dual-Range Visual/Audible Fish Spotter... 99.95\*

Super-bright flasher can be set to read from 0-60' and 0-240' for greater definition and accuracy. Audible alarm can be set to sound at any depth in between. Runs on lantern batteries (not supplied).

Kit MI-2901, 9 lbs. .... 99.95\*

## NEW Heathkit 8-Channel VHF Band- Scanning Monitor with digital readout... 119.95\* less crystals

Crystal-controlled monitor tunes any selected 9 MHz segment of the 146 through 174 MHz band — gives you police, fire, marine, ham 2-meter, etc. Features manual or automatic scanning with numerical readout; priority channel; built-in speaker and rear-panel jack for remote speaker; gimbal bracket for either base-station or mobile use. Operates on either 120/240 VAC or 12 VDC. Includes crystal OSC/Mixer signal source for easy alignment. Order up to eight Crystal Certificates with kit.

Kit GR-110, 9 lbs. .... 119.95\*  
GRA-110-1, Crystal Certificate, postpaid ..... each 4.95\*

## NEW Heathkit Engine Analyzer... 64.95\*

For 3, 4, 6 and 8-cylinder engines. Includes leads and accessories for testing conventional, transistor, and magneto ignition systems, regardless of voltage or grounding. Uses 3 "C" batteries (not included).

Kit CM-1050, 9 lbs. .... 64.95\*

## NEW Heathkit C-D Ignition System... 39.95\*

Increases spark-plug and point life up to 50,000 miles on any car or truck using a 12-volt, negative ground system. Automatically varies spark duration. Screw-on terminals make installation easy; external pushbutton lets you override system without removing leads.

Kit CP-1060, 4 lbs. .... 39.95\*

## NEW Heathkit 6-Digit Electronic Alarm Clock... 54.95\*

Displays hours, minutes and seconds on highly visible cold-cathode readout tubes. A gentle "beeper" alarm can be set for 24-hour cycle and features a snooze switch that gives you seven more minutes of sleep before the alarm sounds off again. Conventional 12-hour or 24-hour international time display.

Kit GC-1005, 4 lbs. .... 54.95\*

## NEW Heathkit Dolby® Cassette Deck... 249.95\*

A kit-form cassette deck utilizing the famous Dolby® noise reduction system. Accommodates the greater fidelity and dynamic range of chromium dioxide cassettes. Independent switches provide Dolby on/off and regular or CrO<sub>2</sub> bias control. Domestic-make tape transport comes preassembled for easy kit building.

Kit AD-1530, 21 lbs. .... 249.95\*

Send For Free '73 Heathkit Catalog

HEATHKIT ELECTRONIC CENTERS — ARIZ.: Phoenix, 2727 W. Indian School Rd.; CALIF.: Anaheim, 330 E. Ball Rd.; El Cerrito, 6000 Potrero Ave.; Los Angeles, 2309 S. Flower St.; Pomona, 1555 Orange Grove Ave. N.; Redwood City, 2001 Middlefield Rd.; San Diego (La Mesa), 8363 Center Dr.; Woodland Hills, 22504 Ventura Blvd.; COLO.: Denver, 5940 W. 38th Ave.; CONN.: Hartford (Avon), 395 W. Main St. (Rte. 44); FLA.: Miami (Hialeah), 4705 W. 16th Ave.; GA.: Atlanta, 5285 Roswell Rd.; ILL.: Chicago, 3462-66 W. Devon Ave.; Downers Grove, 224 Ogden Ave.; IND.: Indianapolis, 2112 E. 62nd Ave.; KANSAS: Kansas City (Mission), 5960 Lamar Ave.; MD.: Baltimore, 1713 E. Joppa Rd.; Rockville, 5542 Nicholson Lane; MASS.: Boston (Wellesley), 165 Worcester St.; MICH.: Detroit, 18645 W. Eight Mile Rd. & 18149 E. Eight Mile Rd.; MINN.: Minneapolis (Hopkins), 101 Shady Oak Rd.; MO.: St. Louis, 9296 Gravois Ave.; N.J.: Fair Lawn, 35-07 Broadway (Rte. 4); N.Y.: Buffalo (Amherst), 3476 Sheridan Dr.; New York City, 35 W. 45th St.; Jericho, L.I., 15 Jericho Turnpike; Rochester, Long Ridge Plaza; OHIO: Cincinnati (Woodlawn), 10133 Springfield Pike; Cleveland, 5444 Pearl Rd.; PA.: Philadelphia, 6318 Roosevelt Blvd.; Pittsburgh, 3482 Wm. Penn Hwy.; TEXAS: Dallas, 2715 Ross Ave.; Houston, 3705 Westheimer; WASH.: Seattle, 221 Third Ave.; WIS.: Milwaukee, 5215 Fond du Lac.

HEATH COMPANY, Dept. 20-1  
Benton Harbor, Michigan 49022

HEATH  
Schlumberger

Please send FREE Heathkit Catalog.  
 Enclosed is \$ \_\_\_\_\_, plus shipping.  
Please send model(s) \_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices & specifications subject to change without notice.  
\*Mail order prices; F.O.B. factory. CL-450

# THE FIRST CROWN PREAMPLIFIER



IC 150

What would happen to a preamplifier design, if the design engineer could free himself from stereotyped ideas and start fresh with only a list of customers' requests? Well, at CROWN that has just happened, and the result is the IC150, an exciting "new concept" control center with simplified circuitry, controls that are easy to understand and use, several exclusive features, unsurpassed quality, and — to top it all off — a lower price tag.

Crown Engineers discovered that pre-amp switches don't *need* to pop ... that there is something *better* than the stereo mode switch ... that the phono preamp *can* be dramatically improved ... and, that by using IC's, a versatile high-quality, advanced-performance preamplifier *can* be priced to beat inflation.

Of course, the true uniqueness of such an innovative design cannot be appreciated by *reading* about it. The only answer is to experience the IC150 yourself. Let us tell you where Crown's "new concept" is being introduced in your area. Write today for a list of locations.

World's quietest phono preamp  
Infinitely variable stereo panorama control  
Silent switching and automatic muting  
at turn-on and turn-off  
Integrated circuit modules  
Industry's lowest distortion levels  
Full range tone and loudness controls  
Guaranteed phase response  
3-year parts and labor warranty  
Will drive *any* amplifier  
\$269, walnut enclosure \$33



D 150

Ask your dealer also about Crown's new companion D150 power amplifier, which delivers 200 watts IHF output at 8 ohms or 350 watts at 4 ohms. No amp in this power range - however expensive - has better frequency response or lower hum, noise or distortion. It offers performance equal to the famous DC300, but at medium power and price. It's worth listening into!

Exported as  
AMCRON



BOX 1000, ELKHART, INDIANA 46514, U.S.A.

Circle 11 on reader service card

26 RADIO-ELECTRONICS • JANUARY 1973

# letters


## MORE ON THE FUNCTION GENERATOR

Several problems crept into the **Radio-Electronics** Function Generator story (September and October 1972). The pulse waveform is shown upside down in the photos. On the overlays, timing capacitors C11 through C16 are shown interchanged; the largest capacitor goes with the lowest frequency at the top of the instrument. The input POWER callouts should, of course, go up with the input terminals on the fuse and power transformer.

Resistor R27, the 1-megohm pulse unbalancing resistor should go to +10 volts as called out in the schematic. The PC overlay and master has this going to -10, which gives you one-third amplitude and very noisy pulse putput. Carve and jumper the PC board so that this resistor runs to +10.

There is enough linearity variation from IC to IC that you'll want to custom calibrate your frequency dial to match the particular IC you are using. A larger value resistor for R10, perhaps 1000 ohms or 1200 ohms should be used unless your particular IC will not provide enough range. This improves linearity and makes the control setting easier and more stable.

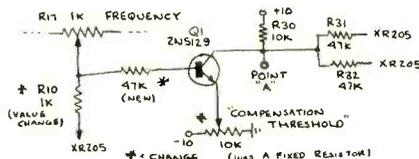The amplitude compensator shown seems to work only with certain XR-205 chips. A better circuit looks like this:



Note that all we've done is add a series resistor to the base of Q1 and exchange the old 4700-ohm R29 fixed resistor to ground for an adjustable PC pot. This setup will work with any IC used. You adjust things so the voltage at point A stays near ground for FREQUENCY dial settings from 1 through 6. Above 6 it should start smoothly swinging positive, ending up with +8 or more when your frequency dial reads 10. For more correction at the high end, reduce R31 and R32, and vice versa. The new pot decides when in the FREQUENCY dial rotation the correction begins. Amplitude compensation only affects the sinewave distortion and the high frequency triangle and ramp size; it is bypassed in

the square and pulse modes.

All of the commercially available kits have picked up all of these additions and corrections and include a slightly heavier power supply than the original called for.

DON LANCASTER  
Phoenix, Ariz.

## NEED SERVICE DATA

They have opened a new Radio & TV Repair Course here in high school for juniors and seniors. We are in need of a complete set of Sams Service notes from 1 to date, or we would accept 500 to date. We are also in need of used test equipment of all kinds. We will be glad to pay a reasonable price and will answer all letters.

RALPH DOROUGH, Instructor  
Killeen High School  
Vocational Building  
3101 Clinkenbeard Dr.  
Killeen, Texas

## WHO ARE THEY?

I have a question about the article "State Of Solid State." **Radio-Electronics**, October, 1972. At one point the text mentions Signetics and Integrated Systems Inc. At another point the text mentions EXAR IC's. Are EXAR and Integrated Systems the same? I am most interested in building a low-cost speedometer and tachometer. Could you provide information on a source for IC circuits?

ROBERT N. SLEIGHT  
Laramie, Wyo.

EXAR and Integrated Systems are indeed the company. The correct full name and address is EXAR Integrated Systems Inc., 733 North Pastoria Ave., Sunnyvale, Calif. 94086.


I have not, at this date, seen any circuit diagrams that would meet your needs for the speedometer. We are, however, negotiating with an author for the purchase of his article on a digital IC tachometer. Tentatively, this story is scheduled for publication in our April 1973 issue.—Editor

## NO MORE SUPPLIERS?

I recently ordered some parts from Newark Electronics. Their reply to me was "We no longer accept orders from individuals. Therefore we are returning your order."

STEVEN W. RUSSELL

R-E

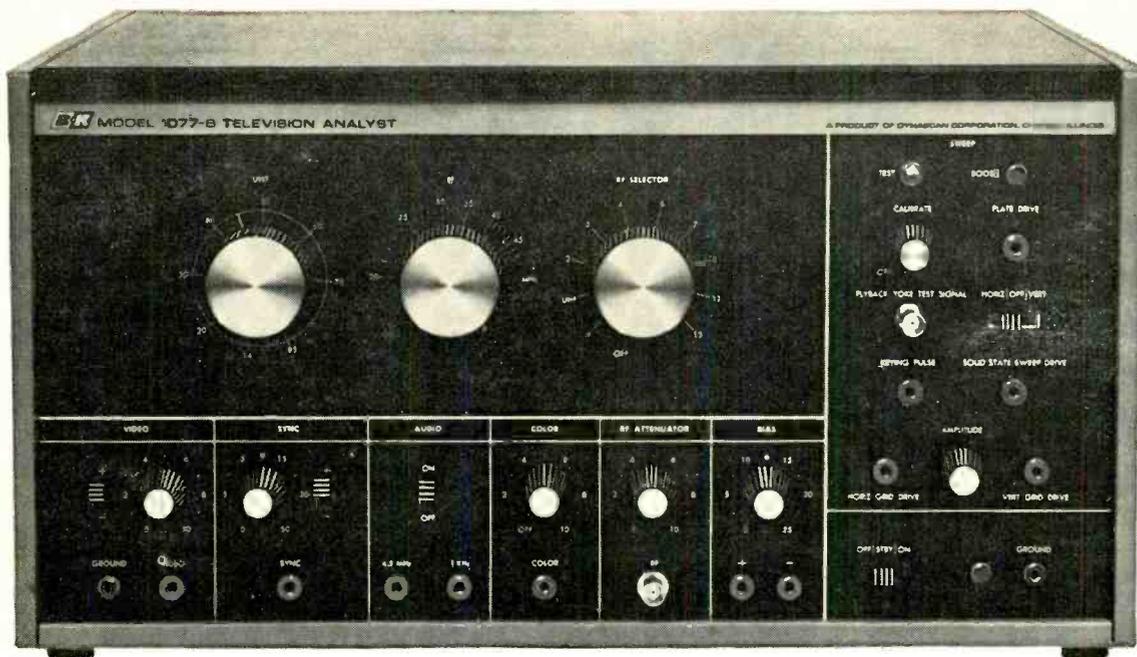

## Who said B & K couldn't improve the only complete Television Analyst?

Now there is a new model... the 1077-B, with solid state sweep drive.

The B & K Television Analyst has become standard equipment in repair shops everywhere. And for good reason. It's the quickest, simplest way to test every stage of any TV.

But even classic instruments have to keep up with the times.

That's why we've added a solid state sweep drive in our latest model. It can check any new transistorized color set on the market today.

It's so easy, too. Because the unique B & K signal substitution technique eliminates the need for external scopes or wave-form interpretation.

Whether it's tubes or transistors, VHF or UHF, simply inject the appropriate test pattern or any other known signal. The new Model 1077-B, with its exclusive flying spot scanner, checks everything from the antenna terminals to the input of the picture tube.

Ask your distributor about the new Television Analyst. Only B & K makes it. And now B & K makes it even better.


Model 1077-B \$399.95



Product of DYNASCAN CORPORATION  
1301 W. Belle Plaine, Chicago, Illinois 60613

RCA Institutes Home Training may be
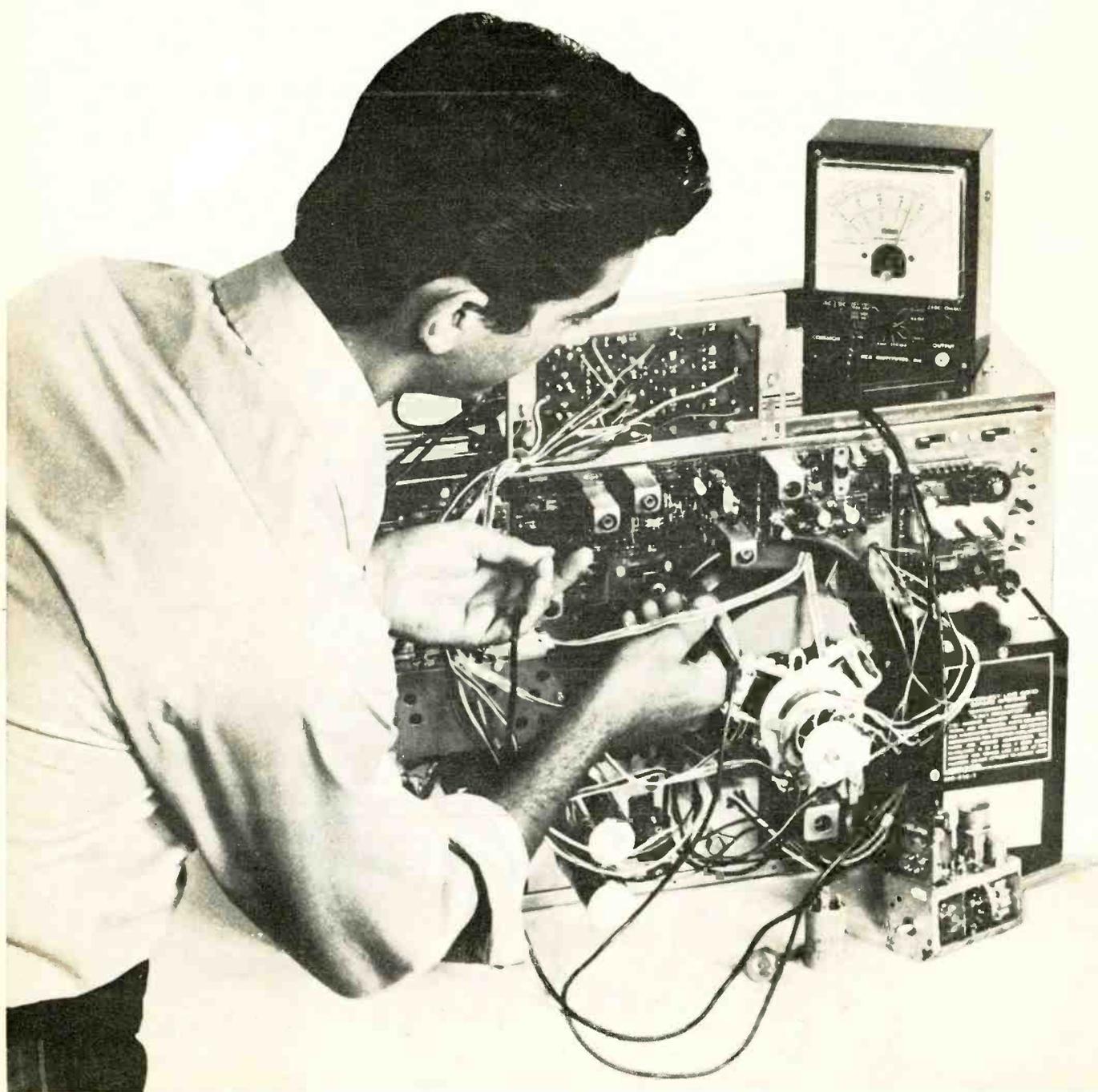
# your best investment for a rewarding career in electronics



## 1 LEADER IN ELECTRONICS TRAINING

For over half a century, RCA Institutes, Inc., a subsidiary of RCA, has been a leader in resident school technical training in electronics. For many years, it has offered home study training in electronics.

## 2 RCA AUTOTEXT TEACHES ELECTRONICS RAPIDLY, EASILY

Beginner or refresher, AUTOTEXT, RCA Institutes' own method of programmed Home Training will help you learn electronics rapidly, easily.

## 3 WIDE CHOICE OF CAREER PROGRAMS

Start today preparing for an electronics career. On the attached card is a list of "Career Programs," each of which starts with the amazing AUTOTEXT method of programmed instruction. Look the list over, pick the one best suited to you and check it off on the card.

## 4 SPECIALIZED ADVANCED TRAINING

For those already working in electronics or with previous training, RCA Institutes offers advanced courses. You can start on a higher level without wasting time on work you already know.

## 5 PERSONAL SUPERVISION THROUGHOUT

All during your program of home study, your exams are reviewed and your questions are answered by RCA Institutes instructors who become per-

sonally involved in your efforts and help you over any "rough spots" that may develop.

## 6 HANDS-ON TRAINING

To give practical application to your studies, a variety of valuable kits are included in many programs. In RCA's Master TV/Radio Servicing Program, you will actually build and keep an all solid-state black and white TV set, and a color TV set. You also construct an oscilloscope which is yours to keep and use on the job.

## 7 FCC LICENSE TRAINING — MONEY BACK AGREEMENT

Take RCA's Communications Career Program — or enter with advanced standing and prepare immediately for your 1st, 2nd, or 3rd class FCC Radio Telephone License examinations. RCA Institutes money-back agreement assures you of your money back if you take, and fail to pass, the FCC examination taken within 6 months after completing the course.

## 8 CONVENIENT PAYMENT PLANS

You get a selection of tuition plans. And, we are an eligible institution under the Federally Insured Student Loan Program.

## 9 RCA INSTITUTES IS FULLY ACCREDITED

RCA Institutes is licensed by N.Y. State and is accredited by the Accrediting Commission of the National Home Study Council. Its courses of study, faculty and instructional facili-

ties are approved by the State Education Department. In addition, all RCA Institutes courses and programs require the approval of the RCA Institutes Board of Technical Advisers who represent various technical, research and educational activities of RCA Corporation.

**Approved by N.Y. State Education Dept. for the training of veterans.**

**SEND ATTACHED POSTAGE PAID CARD TODAY! FREE DESCRIPTIVE BOOK YOURS WITHOUT OBLIGATION!**

If reply card is detached, send this coupon

RCA INSTITUTES, INC.  
DEPT. 758-301-0  
320 W. 31 ST.  
NEW YORK, N.Y. 10001

Please send me FREE illustrated career catalog. I understand that I am under no obligation.

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_

Veterans: Check here

# RCA

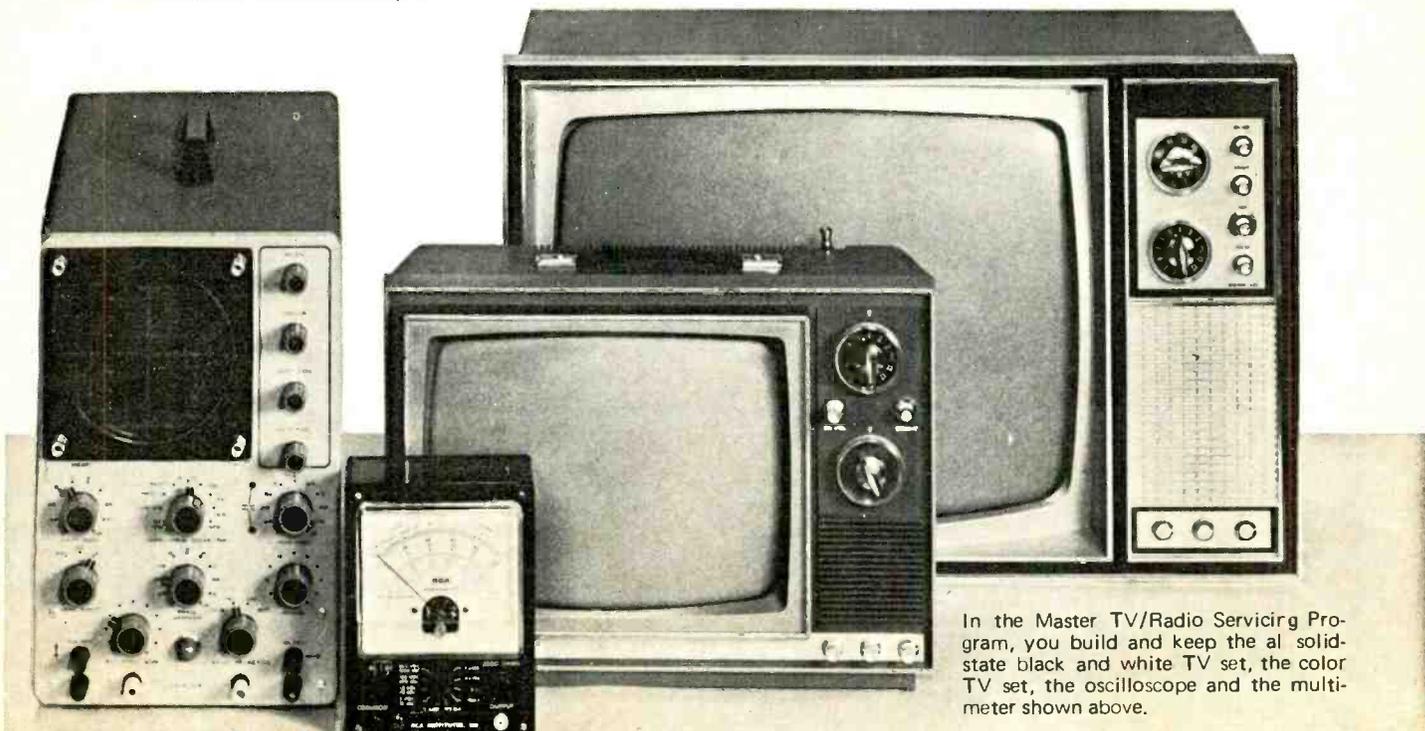

In the Master TV/Radio Servicing Program, you build and keep the all solid-state black and white TV set, the color TV set, the oscilloscope and the multi-meter shown above.

# Speaker super market? Super speaker market.



In a super market, you get a big selection, low prices, nationally-advertised merchandise. Make Quam your speaker super market.

Pick the size, power handling capacity, and price you need to match the function: public address, background music, intercom, outdoor, or whatever. We have 60,000 speakers, 135 different models, ready to transfer from our shelf to your wagon.

What makes a super speaker market? Super performance speakers. That's Quam, too. We use only top grade materials, stringent quality control, and advanced manufacturing methods to make sure our speakers work the way your customer expects them to.

Quam Nichols Company  
Chicago, Illinois 60637  
Phone: (312) 488-5800

Write for a copy of  
our super new  
Catalog 72




## Quam: *The Sound Decision*

Circle 13 on reader service card
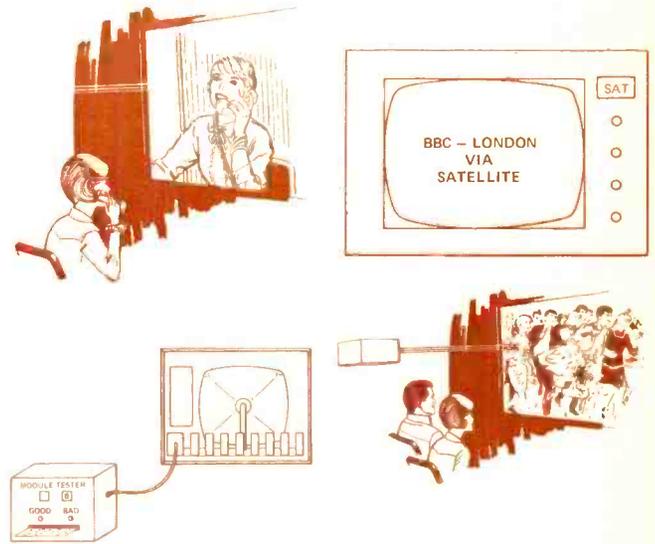
# the next ten years of color TV

by **BOB GERSON**

*Although we've seen many advances in television technology, these are nothing compared to what we see in a glimpse into the future*



IN THE YEAR 1972 COLOR TELEVISION FINALLY CAME OF AGE. By mid-year more than 56% of all television owning homes in America had at least one color set. Considering all the innovations we've seen since 1964 when color had its first million-sales year wouldn't you think we've about come to the age of stability in development. Well you might think so, but you'd be wrong, dead wrong.

Monochrome television hit a 50% American home saturation level in 1953, just 4 years after the first million-set sales year. But far from marking an innovation plateau,


that half-way mark proved to be more like a springboard. In the last 3 years alone we've seen such new concepts as the pocketable-portable, the pop-up screen and the battery portable complete entertainment center, including monochrome television-FM/AM radio-cassette recorder. For color television in the coming decade we can expect changes, innovations and improvements that will make such marvels of today as the latest versions of the black-surround matrix picture tube and one-button tuning seem pale in comparison.

## **wall-sized pictures with projection systems**

Wall-sized television pictures, today available only for theatre use, will be commonplace in homes where the family gathers for program viewing. A trio of high performance, low-power lasers will scan in red, green and blue to provide life-size images in life-like color.

Permanent, ceiling mounted screens automatically drop down when the projector is turned on, roll back up into the recessed housing when the show is over. New, highly reflective screen coatings will afford projectors the brightness lacking in the systems of today, permit projector tele-viewing in normal room light.

Less pretentious but equally impressive will be rear-screen projectors offering color television pictures with four to five-foot diagonal viewing areas. In many homes the entire system will be mounted inside a wall with a mirror-prism arrangement to direct the output from high efficiency light-valve projection tubes up and out to the screen. A control on the wall-hung liquid-crystal screen will change the transparency of the screen itself so that it may, if properly installed, serve as a window (at one extreme setting) or a perfect reflecting mirror (at the other end). As an extra cost option the consumer will be able to purchase a screen which shows "an indistinguishable from the original" painting when it's not being used for TV watching.

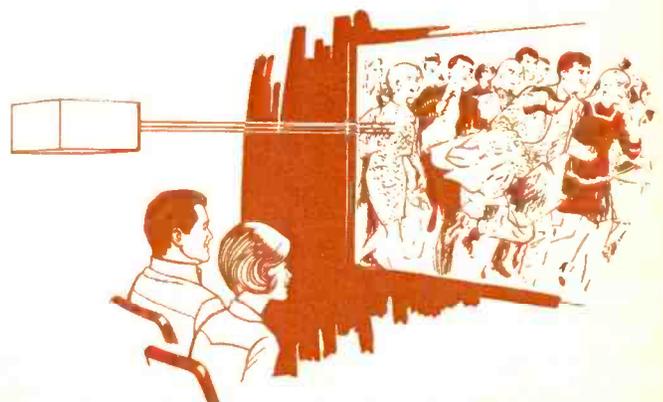

**LASERS AND PROJECTION TECHNOLOGY** may be combined to bring the long-awaited television "picture-on-the-wall" into the viewers' home.

---

## shortwave television

"This is the BBC in the North American service. Tonight we take you live to Buckingham Palace where we shall watch as the Queen greets her guests at her annual birthday ball." Yes, the Queen from London, sunrise services on Easter morning from the Vatican in Rome, the Bolshoi Ballet direct from a stage in Moscow, plus, unfortunately, an endless barrage of graphs, charts and statistics showing how this or that developing country exceeded its production quotas of shoes, wheat, eggs or what have you, thanks to "The Leader's" new five-year plan.

A whole new world of visual DX'ing will open for the dedicated hobbyist as well as the knob twiddler. Virtually every major country and many of the smaller ones as well, will have direct-to-you color television transmission via satellite. For the consumer, reception will mean an investment of \$50 to \$500 in equipment, with the price dependent on the degree of sophistication of the equipment and the installation ability of the owner. For multi-family home dwellers an understanding landlord will be a must.

In addition to a television receiver, the shortwave viewer will need a roof-mounted steerable-dish antenna and a tuner-converter. The cost and expertise required for successful stationary satellite launching will, at first, handcuff prospective amateur ham telecasters. But enough state-wide clubs will start considering such a move—one will actually put in a launching request with NASA—that the FCC will organize and oversee the placing of amateur-use satellites in strategic locations above the U.S.



TV VIA SATELLITE direct to you will require a roof-top converter fed by a dish or other high-gain antenna aimed at the fixed satellite.

---

## display devices

There'll be no substitute for the picture tube in the decade to come, but there will be alternatives and innovations. Super-thin conventional color television receivers will have cathode ray tubes with the electron gun mounted at right angles to the screen. The result will be a 19-in. set thin enough to fit on a standard bookcase shelf. Deflection plates inside the tube will divert the electron beam, causing it to sweep across the tube face.

The "hang it on the wall" television display will get here at last. Thanks to the perfection of plasma technology the industry will realize the dream of television as a picture

in a frame. The display itself will be a glass sandwich containing pockets of gas and a network of wires. The gas trapped in each nearly microscopic pocket will glow in either red, blue or green when addressed by a current from the wires running through it. Initially the screen will hang on a wall and be connected to the remotely located chassis by wires. But innovations in microelectronics will permit the insertion of all electronic circuitry in the frame itself. With power supplied by a compact microwave transmitter plugged into any convenient nearby outlet, the need for any exposed wiring will be eliminated.

---

## random-access television

The coming combination of cable television with computer time-sharing techniques will shatter the channel number barrier, giving each television set owner a virtually limitless viewing choice.

In addition to the standard entertainment offerings available for the watching from commercial television, the viewer of the future will have access to hundreds of special interest programs, shopping & hobby guides, mini-tours of possible vacation sites, and of course first-run feature films and Broadway shows.

The heart of random access television will be the touch button telephone-type keyboard accessory. By tapping in the right series of numbers, tomorrow's televiewer will be able to bring any available program offering into his living room. Every urban community will have program

repositories. Some municipally run like a library, will provide this service free. Most, however, will be commercial enterprises who will charge for the programs on a per-show basis, with billing handled through the cable operator. Program viewing costs will vary greatly depending on the material, but the charge for the average new movie or stage show will run around \$5. In many instances the consumer will find that his special interest programming can be dialed up for free from businesses hoping to catch its buying interest.

Interested in a new appliance, wardrobe, automobile or planning a family outing? Just punch in for a free, full-color run down on the latest fashions now on sale in your local department store, the hottest fastback coming from Detroit or the fun and luxury at a seaside resort.


---

## *fiddle-free TV*

The button, knob and switch will be a fond relic of the 1970's as far as the television receivers of tomorrow are concerned. Except for channel changing and volume levels the television owner will have no adjustments to make. The set itself will automatically adjust its brightness to ambient room light, then compensate its contrast to the brightness. An inconspicuous sensor will constantly monitor the set's picture quality, compare it with reference signals being transmitted along with the program and adjust hue and tint accordingly. There will of course have to be an automatic mode override for the consumer who insists on exercising his preferences. But manual adjustments will be tucked well out of sight.

There'll be no need for channel indicators on the set itself. Each station will be transmitting its identification during the vertical blanking interval. The number and call letters will show up in a corner of the screen for a 6 to 10-second display, then fade. A touch on the designated spot on the electronic tuner or the remote control unit will cause the identification to reappear.

The solid-state chassis modules of tomorrow, like the receiving tubes of yesterday, will be consumer replacable. In the exceptional event that the set does malfunction, the consumer will remove suspected modules and take them out for testing. A popular accessory at \$25 will be the testing computer. A 3"x5"x2" black box, the computer plugs in to a "service" jack at the rear of all new sets. A magnetic program card gives the computer the operating parameters for each module in the set. The computer checks the modules, displays the number of the malfunctioning one on its 2-digit alphanumeric readout.

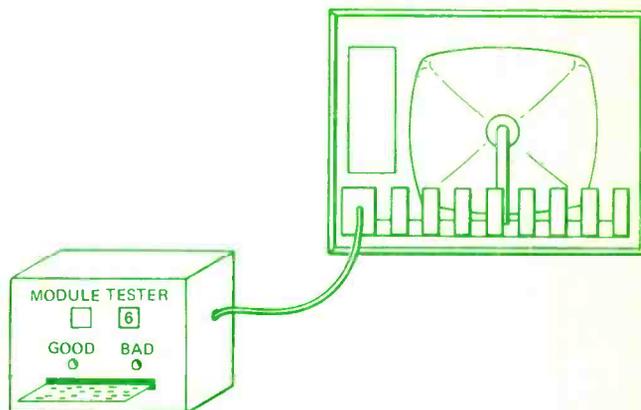

**MINI-COMPUTER MODULE TESTER** plugs into jack on TV set and quickly checks out all circuits and identifies weak or defective modules.

---

## *more than a program source*

The prime function of a television receiver is, and probably always will be, to provide a display of entertaining and informative programming produced for mass consumption. Today this is really the only function. But tomorrow the television set will have as many uses as the ubiquitous quarter-inch electric drill has attachments and the set will be called on to do nearly as many jobs.

This revolution in utility has already started with the introduction of the Cartrivision home video tape player and the Magnavox Odyssey. Cartrivision, through rental and sale tapes, gives the consumer a personalized alternative to commercial programming. Odyssey turns a television set into a playing field for tennis, hockey and other games. But these are just the beginning.

---

## *telephone message center*

Your television set will become your home message center. Your telephone will be equipped with an audio-video answering device. Using touch-tone telephones, callers to your home will be able to leave the usual recorded audio message, then follow by punching out detailed instructions, times, dates, etc. When you get home you'll play the message back on your television set, listen to the audio through the speaker and watch as the written portion is spelled out on the screen.

Advances in cable technology will permit direct interconnection of any two, or more, sets on the same system. With appropriate game attachments at each end, home owners miles apart will use their sets to match skills in games as complex as chess or as simple as tic-tac-toe. Keyboard attachments will allow housewives to swap recipes, light pens will permit direct transmissions of designs and sketches, and with a camera accessory you will be able to treat your neighbor to your family's latest theatrical experiment.



**FLAT-SCREEN TV** and picture phone form audio-visual message center.





# Digital Readout for

0 2 8 6 . 7  
 6 5 0 8 . 2  
 8 7 5 0 . 2  
 2 5 0 7 6 . 8  
 7 6 0 7 . 5

# SSB Receivers

Read frequency of incoming signal within 100 Hz while eliminating usual errors in reading dial.

by LARRY R. HOUGHTON\*, K8ZVF

THE RECENT PROLIFERATION OF LOW-COST FREQUENCY counters has attracted the attention of many amateur radio operators. Hams have always had an interest in knowing their exact operating frequency and for good reason. Regulations require strict adherence to amateur band edges and sub-band allocations. Locating a net or the frequency for a prearranged schedule is much easier when accurate frequency indication is available. It is natural then to see hams attempting to adapt these counters to their home stations.

### Direct signal counting

The enterprising amateur radio operator can, however, face a number of application problems in his quest for accurate and reliable indication of receiver frequency. To begin with, he must know *what* his counter is going to count and what it means. A number of hams overlook the fact that a receiver does not always have a single signal at the operating or listening frequency. Let's look at the block diagram of a conventional dual-conversion superhet, single side-band receiver (Fig. 1) to see why.

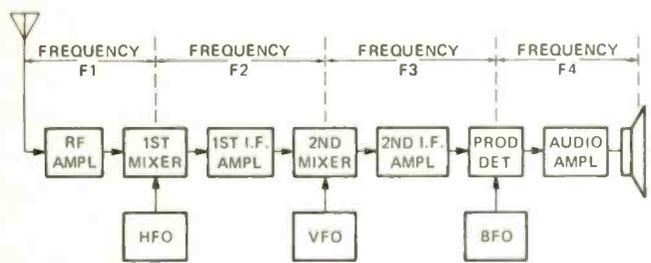


FIG. 1—TYPICAL SSB RECEIVER is a double-conversion superhet with fixed-frequency hfo.

In a typical receiver like this, received signals at frequency F1 coming from the antenna are successively amplified and converted to other frequencies, F2, F3, and F4. The ultimate output is recovered audio at frequency F4. So, in this receiver the only signal at the listening frequency is F1. Can it be counted directly and displayed? Possibly. External amplification would be required to raise incoming signals from the microvolt level to approximately a quarter of a volt, sufficient to trigger most counters. In effect, the counter would be driven directly by received signals which, of course, are not always present. The counter would read out or display a frequency only when signals were tuned in.

Besides the possible intermittent display, another problem exists in direct counting. Incoming SSB signals are *not* at a single frequency. A number of frequencies are present, represented by an audio bandwidth spaced either above or below the zero-beat or suppressed carrier frequency, depending on whether an upper or lower sideband signal has been received. A typical USB (upper sideband) spectrum might appear as in Fig. 2. The resultant counter readout would show a random

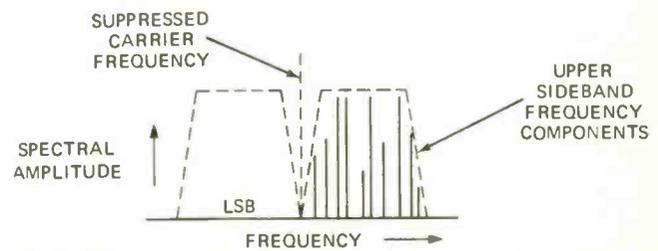


FIG. 2—FREQUENCY SPECTRUM of an incoming upper-sideband signal. When the lower sideband is transmitted, the energy distribution is a mirror-image of the upper sideband.

shift as the spectral components varied with time.

Incoming CW signals are at a single frequency but, of course, are only present during key-down at the transmitting end. The single-frequency carrier of tuned-in AM or FM signals is always present except during fading conditions.

Besides intermittent and random displays, one other direct-counting problem should be considered. When the received signal is amplified to a frequency counter's trigger level undesirable receiver operation might result. The presence of high-level signals at the receiver's frequency would be like having a transmitter operating next door. Front-end overload could occur, resulting in intermodulation distortion. Other distortion or spurious products could also be generated through radiation and ground loop paths; all in all, an undesirable method of frequency indication.

### Vfo counting

For a better approach, refer to the other frequencies present within the receiver in Fig. 1. In this SSB receiver, three signals (heterodyne-, variable-, and beat-frequency oscillators) are generated for converting incoming high frequency rf signals to audio frequencies. What is the relationship between these frequencies and the receiver's listening frequency? Keeping in mind how a superheterodyne receiver works, let's examine this relationship.

The hfo (heterodyne-frequency oscillator) is normally crystal controlled and changes frequency when a different

\*Chief Engineer, Communications, Heath Company

band is switched in. Depending on a receiver mixing scheme, the received signal (frequency) is either added to or subtracted from the hfo frequency. The bfo generates one of two different fixed frequencies depending on USB or LSB operation. The vfo frequency changes as the receiver is tuned. Its frequency has a definite relationship to the listening frequency. Can we count it and know the operating frequency? Yes indeed, but with a couple of limitations.

Suppose the vfo covered a 500-kHz range by tuning from 2.000 MHz to 2.500 MHz. Each band segments of the receiver would then cover 500 kHz. If the vfo frequency varied in the same direction as the receiver was tuned, the vfo frequency could be counted and displayed. For example, if a band segment started at a whole megahertz, say 21 MHz, the vfo frequency would be at 2.000 MHz. The counter display would show "2.000". The "2" would be ignored (or not displayed) and by knowing the position of the receiver's bandswitch, the listening frequency would be interpreted as 21.000 MHz. Tuning the receiver's vfo to 2.250 MHz would change the display to 2.250 MHz and would be interpreted as 21.250 MHz.

Another complication occurs if the vfo tunes "backwards", that is, it changes frequency in the direction opposite to receiver tuning. The vfo counter display would not have an easily interpreted frequency. Frequency inversion can be used either by frequency mixing or digital techniques but still does not offer the ultimate answer.

The greatest drawback to the vfo counting method has to do with accuracy. Accuracy, in this application, infers better frequency indication than obtainable with mechanical dials. The receiver's operating frequency is determined not only by the vfo but by the hfo and bfo frequencies as well. For the vfo frequency to give an accurate indication, each hfo and bfo frequency must be very close to their "design" values.

Refer again to Fig. 1. If *subtractive* mixing is used in the 1st and 2nd mixers, the simple equation that shows the relation between the operating frequency F1 (SSB suppressed carrier frequency) and the three oscillator frequencies in the receiver is  $F1 = hfo - vfo - bfo$ . For example, if the hfo frequency is 18.000 MHz, the vfo is set at 2.500 MHz, and the bfo frequency is 1.500 MHz, the receiver is tuned to (18.000 - 2.500 - 1.500) or 14.000 MHz. Assuming that is the true frequency, then the hfo and bfo oscillator crystals are exactly right. Now suppose the receiver is switched to another band. The vfo and bfo frequencies do not change, only the hfo frequency. Suppose you switched to the 80-meter band where the new frequency should be 3.500 MHz. A hfo frequency of 7.500 MHz would be necessary for the vfo counter to show the "correct frequency":  $7.500 - 2.500 - 1.500 = 3.500$  MHz. If the hfo crystal happened to be low by 1000 hertz (a reasonable assumption in amateur-grade equipment), the true frequency would be  $7.499 - 2.500 - 1.500$  or 3.499 MHz. This error would not be apparent because only the vfo frequency is being counted and displayed.

Hfo and bfo crystals can be "pulled" (trimmed or adjusted) in some oscillator designs so their frequencies can be set exactly to what they should be. However, warmup drift and crystal aging can introduce additional errors, again unapparent when only the vfo is counted.

### Frequency mixing

The next step toward greater accuracy and reliability in counting receiver frequency is to generate the operating frequency as indicated by the receiver's mixing scheme. In our previous example of a subtractive mixing scheme, a signal at the operating frequency can be generated and counted as shown in Fig. 3.

The output of Mixer A is tuned to the difference frequency between the hfo and vfo. This signal is then subtractively mixed with the bfo. The resultant is a signal equal in frequency to F1, the operating frequency. Additive mixing can also be used depending on the individual receiver's mixing scheme.

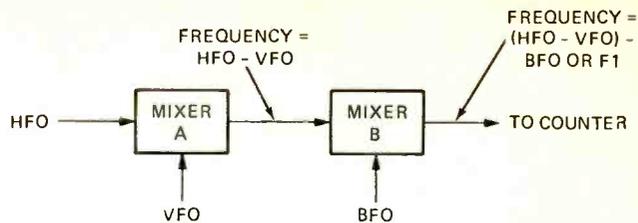


FIG. 3—MIXING SCHEME for generating a signal equal to that to which the receiver is tuned so the counter operates constantly.

Using the mixing method for receiver frequency counting eliminates the errors possible in vfo counting. Hfo and bfo frequencies need not be exact and drift does not become a factor because the generated signal changes by the same amount. Accuracy then is only limited by the counter used. This method has been described previously<sup>1,2</sup> and has been successfully used by hams.

Careful construction techniques are called for when using such a mixer. Receiver overload problems have already been mentioned and can occur using this technique. In addition, the outputs of each mixer (A and B in Fig. 3) require tuned circuits. Thus, the mixer has to be bandswitched along with the receiver.

### Calculating receiver frequency

The main advantage of the mixing method just described is that of accuracy. No matter what the individual oscillator signals happen to be, the final displayed frequency, within the counter's accuracy, is the receiver's true operating frequency. When digital techniques replace mixing (an analog process), this accuracy can be retained without the attendant disadvantages.

Such a technique is used in Heath's new SB-650 Digital Frequency Display.<sup>3</sup> By counting each oscillator frequency individually and arithmetically calculating the result, no new frequencies need be generated. The equation  $F_{operating} = hfo - vfo - bfo$  is solved digitally rather than by an analog approach. And because no tuned circuits are needed, the SB-650 does not have to be bandswitched.

The SB-650 counts each of the receiver oscillator inputs, Fig. 4, in an up/down counter controlled by an internal clock

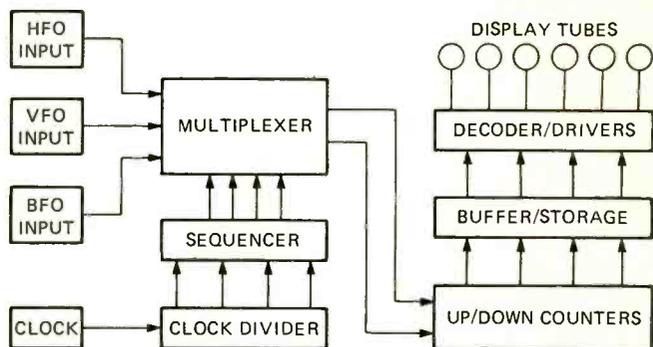


FIG. 4—BLOCK DIAGRAM OF THE SB-650 digital frequency display. Device needs three input frequencies to indicate the frequency to which a typical SSB receiver is tuned.

through a sequencer and multiplexer. Timing signals derived from the clock via the sequencer, select input signals in the proper sequence, direct them to the up/down counter, and tell the counter when to count up and down.

Updated calculations and display occur every 160 milliseconds or approximately six times per second. The sequencer provides four 40 millisecond time periods; three for counting the input signals and one for display updating and counter reset, Fig. 5. During time period T<sub>1</sub>, the hfo signal is directed

<sup>1</sup>Macleish "A Frequency Counter for the Amateur Station", *QST*, October 1970.

<sup>2</sup>Macleish, Pattison, Hejhall, "The Rec/Counter", *QST*, May 1971.

<sup>3</sup>Patent applied for.

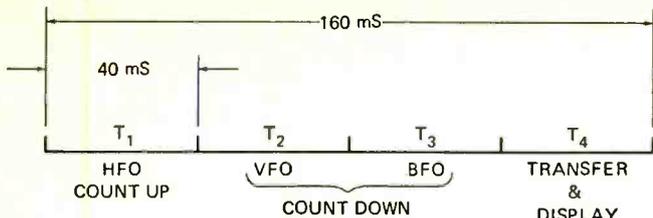


FIG. 5—THE SB-650 COUNTING SEQUENCE. The hfo signal—higher than the incoming signal—is counted; then the vfo and bfo frequencies are subtracted so correct frequency is shown.

by the multiplexer to the count-up input of the up/down counter which is given a count-up command. During  $T_2$  and  $T_3$ , the vfo (called LMO in Heath SB-series equipment) and bfo are respectively directed to the count-down input. At the beginning of period  $T_2$ , the up/down counter contains the hfo count accumulated during  $T_1$ . Now the counter counts "backwards", in effect subtracting from the stored hfo count. The bfo signal is then subtracted during the next period. At the end of  $T_3$ , the up/down counter contains in binary form a number equal to  $\text{hfo} - \text{vfo} - \text{bfo}$ , the receiver frequency. During period  $T_4$ , this number is transferred to storage buffers, decoded to the equivalent decimal number, and displayed on indicator tubes. After the number has transferred, the up/down counter is automatically reset to zero, ready for the next counting sequence.

The SB-650 digital frequency display was designed specifically for operation with Heath's SB-line receivers and transceivers, plus the HW-100 and 101 transceivers. These units are dual conversion using subtractive mixing. The SB-650 construction manual describes minor modifications to provide the display with the three oscillator signals from each receiver or transceiver<sup>4</sup>.

The SB-650 displays receiver frequencies on 80 through 10 meter amateur bands to 100 hertz. Its accuracy is specified as within 100 hertz plus or minus one count or another 100 hertz. Calibration is achieved by setting the internal clock for the correct frequency display after zero-beating the receiver with WWV at 15 MHz or CHU at 7.335 MHz. In most cases, this zero-beat will be within 25 hertz. It depends on the operator's ability to hear and detect true zero-beat. The plus or minus one count error is inherent with any asynchronous

<sup>4</sup>The SB-650 is available in kit form for \$179.95. Additional information on the SB-650 can be obtained by writing Heath Company, Benton Harbor, Mich. 49022.

counter (where the signal source and the counter's timing signals are not synchronized).

When transceiving, both transmit and receive frequencies are the same in the SSB mode. However, in the CW mode the bfo shifts about 1000 hertz during transmit. Since the SB-650 counts the bfo, it will display the CW carrier frequency during transmit.

The SB-650 has been designed for SSB and CW operation; a receiver operating in the AM mode does not require a bfo, hence the frequency displayed would be higher than the operating frequency. This can be better understood by looking at the basics of SSB and AM demodulation.

An SSB signal as shown in Fig. 2 has no carrier. To extract the modulation (as an audio frequency), the receiver essentially reinserts a carrier. This is done by mixing the bfo and intermediate frequency (i.f.) in a product detector. The output is audio. In other words, both bfo and nominal intermediate frequencies are identical and any variations in the i.f. are detected as audio components in the received signal.

In the AM mode, the bfo is not needed because the carrier (converted now to the intermediate frequency) is present. An incoming AM signal is demodulated by detecting the amplitude variations with a diode. After filtering out the i.f. (carrier), only audio frequencies remain.

Recall the simple formula,  $F = \text{hfo} - \text{vfo} - \text{bfo}$ . The SB-650 performs this operation even if one of the inputs is missing (equals zero). This, then, is what happens in AM operation. With the bfo shut off, the SB-650 display would only show hfo minus vfo. This is also equal to the operating frequency plus the bfo frequency.

Heath Company does not provide instructions for other makes of equipment, since it has no control over their designs. Operation of the SB-650 with other receivers depends on two criteria. First, the receiver must be subtractive-type single or dual conversion where the received signal is subtracted from either the hfo or vfo. Secondly, the loading of the receiver's oscillators by the SB-650 must not degrade its normal performance. Heath units are not degraded due to sufficiently high oscillator signal levels.

Low-cost frequency counters and counting techniques are now within reach of most amateurs. They can be applied to receivers a number of ways depending on the desired accuracy and reliability. Technology is now offering the amateur radio operator the long sought means of accurate frequency indication.

R-E

### NO RASTER, NO HIGH VOLTAGE


*I've got sound, but no raster, in a Sony 5-303W TV. Dc voltages a little high all over. All haywire on the horizontal oscillator, and zero on base and emitter of horizontal emitter-follower and driver. No waveforms on scope on the last two.—L.W. Memphis, TN*

Zero voltage on the emitters of the horizontal emitter-follower and driver indicate no conduction in these transistors. No waveforms here shows why—the horizontal oscillator isn't running.


You say you have about 8 volts on both base and emitter of the oscillator transistor, but read zero on the base of the emitter-follower. This is very odd. The base-emitter junction of the emitter-follower is in the emitter return circuit of the oscillator—directly coupled to it! So, you could have a break in the PC board conductor between these points, or an open 100-ohm resistor in sets using that part. Or the emitter-follower transistor could have an open base-emitter junction.

There is a very small winding on the horizontal oscillator coil that goes to ground, too. If this winding is open, or has a bad ground connection, it stops the feedback and kills the oscillator. However, if the circuit is complete, you

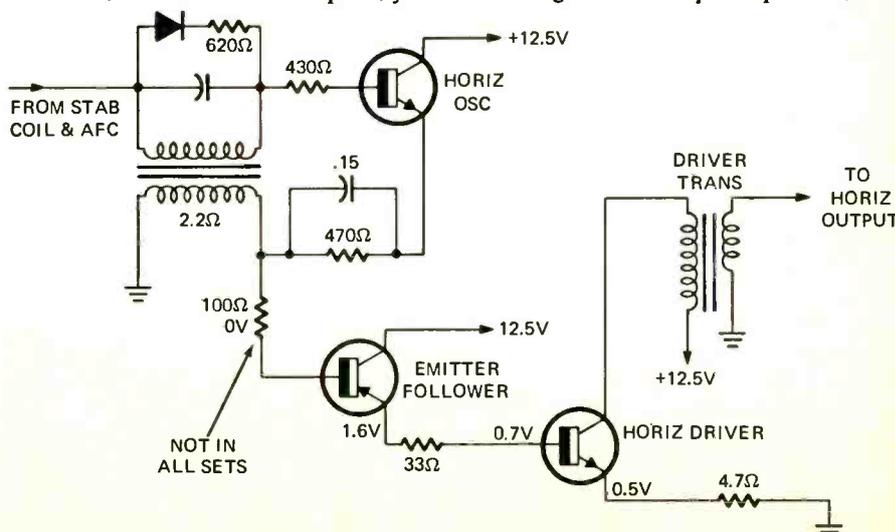should read that 8 volts on the base of the emitter follower. Normal resistance reading from the emitter-follower base to ground should be about 2.2 ohms, through the transformer secondary winding. Check for open capacitors, etc.



# NEW TV CIRCUITS FOR '73

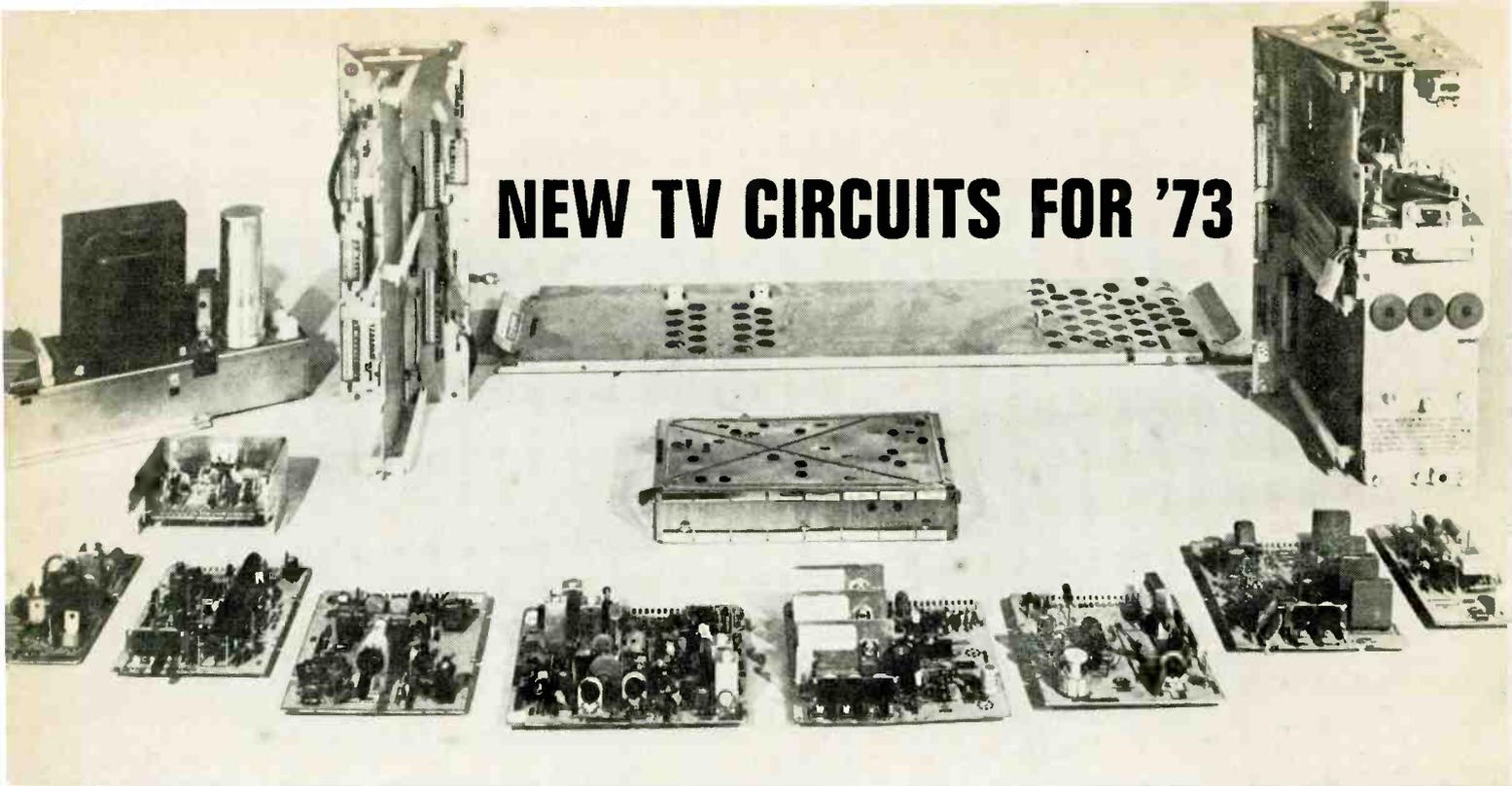

THERE ARE SOME REALLY INTERESTING circuits in the new sets many of which indicate future trends. The major manufacturers all have modular chassis with 70 to 95% of their components mounted on plug-in modules. The now noticeable impact of consumerism is moving TV instrument design toward increased serviceability and safety. The arrival of IC technology has resulted in a higher degree of sophistication within the same penny-pinching guide lines that have dictated in the past. Let's look at some of the circuit features which show the direction in which we're pointed, avoiding the host of automatic and semi-automatic color controls that have appeared in great profusion, as these will be the subject of a separate article.

## Power supplies

Last year Motorola introduced an electronic power supply that is synchronized to run at the horizontal line frequency 15,734 Hz\*. From listening around we are led to understand that this is a definite trend, and in the next few years we will see everyone gravitating to this type of supply. Transformer core material can be drastically reduced because of the higher operating frequency, and careful design will increase efficiency since normally wasted power can be conserved. Because the bulky power transformer has disappeared Motorola has been able to put most of the supply on a single module. In its place is a transformer resembling a flyback in construction. The switching type circuit includes voltage regulation and overload protection

circuitry. Efficiency is vastly improved in switching regulators because the active devices are encouraged to be either on or off where power dissipation is at an absolute minimum. Regulation is effected by changing duty cycle rather than varying the wasteful dissipation in series power resistors and transistors. Interestingly, the circuit maintains power line isolation, those of us who have ever forgotten to take the proper servicing precautions when working on a hot chassis will well appreciate. Fig. 1

is the block diagram of the supply showing how the oscillator transformer isolates the chassis from the power line by the absence of chassis ground connections in its primary circuit.

Sony's thoughts along these lines are different taking advantage of the already needed horizontal deflection—high voltage system to generate the receiver's 18-, 27.5- and 170-volt supplies. Windings on the flyback feed rectifiers and filters to supply the set's dc power. It's not perpetual motion though and an independent low-drain


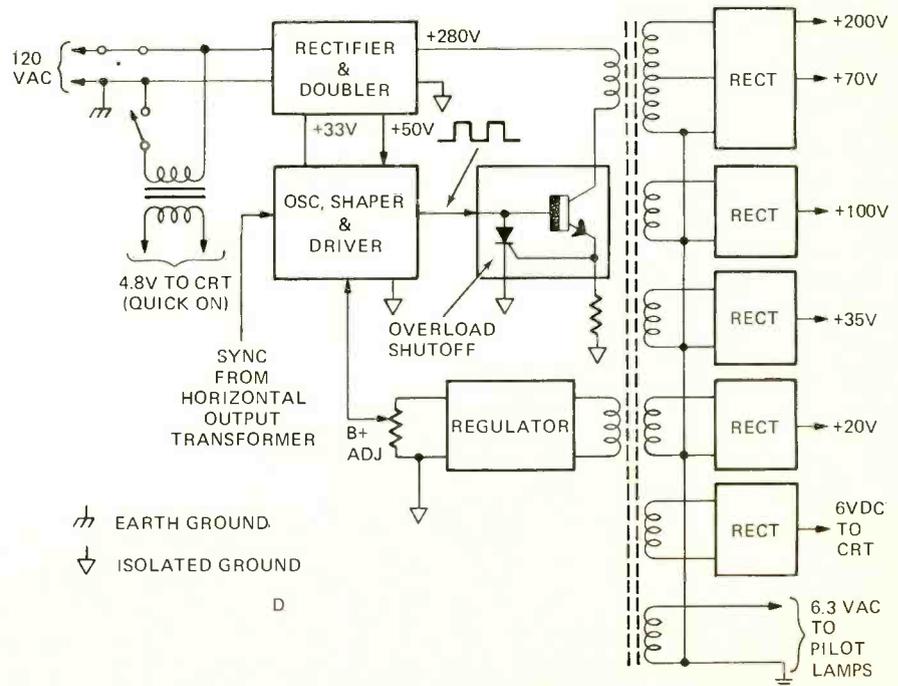


FIG. 1—ELECTRONIC POWER SUPPLY used by Motorola is presented here in block-diagram form. It operates at 15,734 Hz.

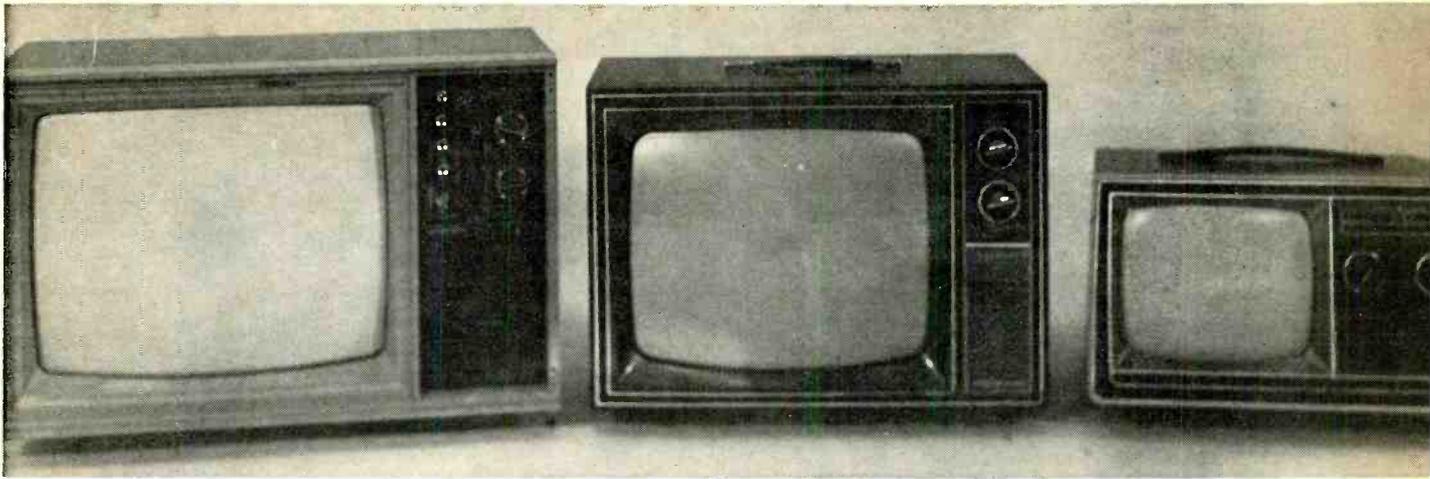\*See New Color Circuits for '72, Radio-Electronics, January 1972



Here's a preview of the latest circuits from the '73 color sets. There are nine in all ranging from an electronic power supply to a new kind of horizontal alignment adjustment to a special high-voltage indicator

by STEVE LECKERTS

130 volt supply is needed to get things started. The horizontal oscillator itself is powered from the same 18 volts it helps to generate. The 130-volt supply is used only to start the oscillator and then is automatically disconnected. Fig. 2 shows how it works. At turn-on the charging current through R555 and C531 supplies temporary power to the oscillator to get it going. When C531 is fully charged the 130-volt supply is effectively isolated from the oscillator and power is supplied by the self generated 18 volts through R536 and D510. The diode prevents the 18 volt supply bus from draining current from the 130-volt line used for turn-on. The resistor drops the horizontal oscillator voltage down to 12 volts. For troubleshooting the horizontal oscillator, horizontal deflection or high voltage circuitry the oscillator supply will have to come from some other source like an external supply. One

convenient method for troubleshooting is to make the temporary dotted connections bridging a 3900-ohm 5-watt resistor around C531 connecting the 130-volt supply as the main power source for the oscillator. This modification causes a loss of efficiency so should be removed after the repair is completed.

**Push-to-adjust horizontal**

This is a feature that is not a trend setter because it doesn't save the manufacturer money, is not required by law, nor can be expected to be popular with the buyer, but certainly makes the horizontal alignment adjustments simple to do without the usual assortment of clip leads. It also allows a quick accurate centering of the hold control. The importance of this adjustment is overlooked by many. While the control may have been haphazardly adjusted under strong signal

conditions, as the picture gets weaker the nominally  $\pm 120$ -Hz horizontal pull-in range becomes severely narrowed. This is because the reduced signal to noise has the effect of reducing the loop gain of the AFPC loop that reduces pull-in range. The second reason for the importance of this adjustment is that even at high rf signal levels the amplitude of impulse noise that will knock the receiver out of horizontal sync will depend on the control setting. Fig. 3 depicts the optimum and off-centered operating


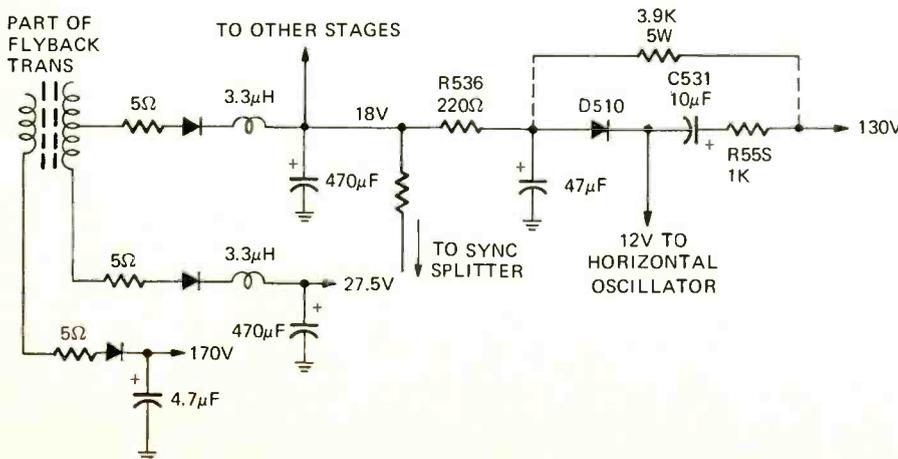


FIG. 2—HORIZONTAL DEFLECTION SYSTEM in Sony receiver is used to generate 18-, 27.5- and 170-volt supplies.

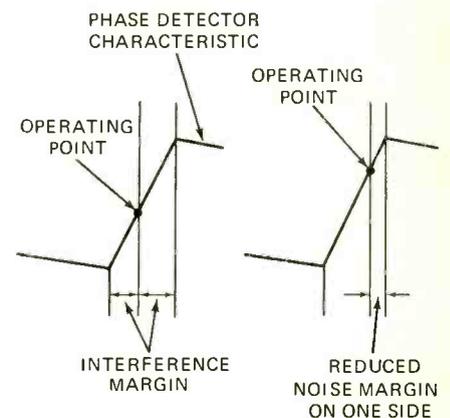

a) IDEAL CENTERED ADJUSTMENT b) OFF-CENTERED ADJUSTMENT

FIG. 3—REDUCED NOISE REJECTION is caused by misadjustment of horizontal circuit.

points of the horizontal afpc phase detector characteristic. When the operating point is off-centered a smaller disturbance will cause the detector to move past one end of the positive operating slope of this characteristic where loss of sync occurs. This simply

means that a smaller disturbance will send the mis-adjusted set annoyingly out of sync. Fig. 4 is G-E's approach. On their modular JA chassis used in 10-, 16- and 19-inch receivers they have included a sync shorting switch on the horizontal hold control dis-

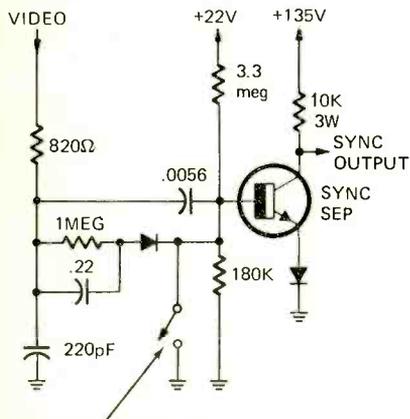


FIG. 4—SYNC DISABLE SWITCH is used by GE in their modular JA chassis.

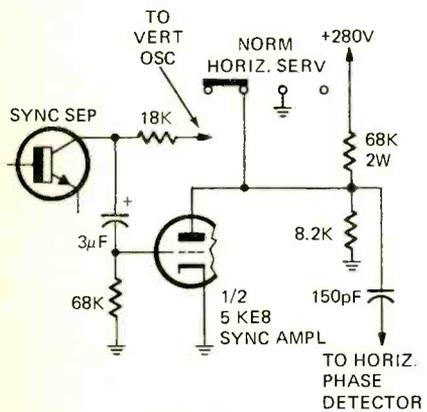


FIG. 5—ANOTHER SYNC DISABLE switch circuit. This one is used by Magnavox.

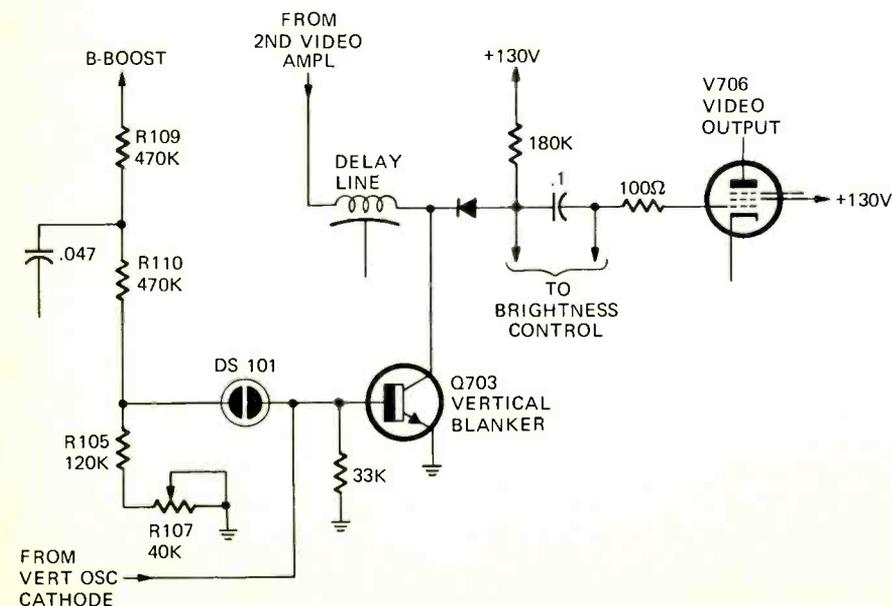


FIG. 6—HIGH-VOLTAGE PROTECTION CIRCUIT is used by RCA in their CTC-63 chassis. If high-voltage becomes excessive, the picture blacks out.

abling the sync when the shaft is pushed in. The control can then be adjusted for a floating picture so that its right and left edges are vertical and are slipping by as slowly as possible. This assures that the horizontal oscillator is close to a free running frequency of 15,734 Hz giving the ideal situation of Fig. 3. Magnavox uses the center position on their service switch as shown in Fig. 5 to short the plate of the sync amplifier to ground.


### Hold down circuits

Because of the recent X-ray scare the department of Health, Education and Welfare is issuing requirements for public protection from radiation. One of the requirements is that a non-usable picture be produced if there is a malfunction that causes excessive high-voltage. On some RCA sets when an over-voltage condition is sensed the horizontal oscillator is pulled low in frequency. The design is such that the picture cannot be put back in sync by any adjustment or misadjustment of the customer or factory controls. This circuit must be separate from the high-voltage regulator since one of the important things it must do is protect against a malfunction in the regulator. The circuit can be easily tested by shorting two chassis test points. Another approach is used by RCA in their CTC 63 shown in Fig. 6. The high voltage is sensed by applying the B-Boost to the voltage divider R109, R110, R105, R107. R107 is factory adjusted and sealed. When the voltage is excessive neon lamp DS101 is fired turning on the vertical blanking transistor. The picture is black which is about as unwatchable as you can get. It should be remembered when servicing this chassis that a defect in the

protection circuit or high-voltage circuits have to be considered as possible causes of loss of video. The neon lamp will be lit if the protection circuit is blanking the picture. Philco's protection system monitors the typically 26,500-volt kinescope anode supply. If the voltage goes above 30,000 volts the guard circuit disables the horizontal oscillator. The receiver is shut down and remains inoperative until repaired.
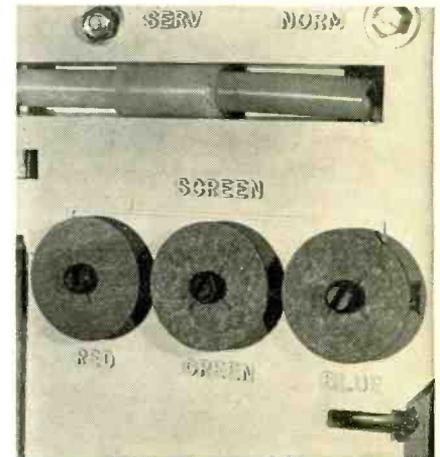
### Uhf varactor tuners

In reaction to the FCC's tuner parity requirements the manufacturers have been busy developing both detented and varactor tuned uhf front ends to make uhf tuning as easy as vhf. The varactor tuners presently



NEON LAMP below blue screen control glows when G-E chassis high voltage operates.

seem to be showing up in remote control equipped sets since they can be preset to a fixed number of channels. The reverse voltage on a series of varactor diodes electronically determines their capacitance controlling the tuning. The mechanically stable diodes take the place of the rotating tuning gang eliminating mechanical wear. Motorola uses a 13-position switch on their uhf wheel allowing remote selection of the same number of channels. Each position contacts a pre-set 30,000-ohm potentiometer by slip rings to tune the varactors to the chosen channel. Four varactor diodes are used in this tuner's resonant lines. RCA has a similar 8-channel system while Dumont, Emerson and Admiral use 6-channel selection. The last three tuners appear to be identical. Varactor tuners open up many possibilities such as automatic search modes now available on some similarly tuned FM receivers. There are such possibilities as digital indicating systems to display channel numbers on the TV screen or digital display, with the selection of the display generated by the same dc voltage or potentiometer that does the varactor tuning. Although frequency dial-in as presently available on 2 or 3



bility of their circuitry, it is possible to cause device damage by this practice. To provide a good servicing aid and to discourage this arcing test GE in their transistor deflection MA 25 inch chassis has mounted a neon lamp in the high voltage compartment visible from the rear. The lamp glows when high voltage is present, a good basic

### Vertical oscillator

An unusual configuration is used in the vertical oscillator of the GE MA modular chassis. The two transistors Q700 and Q701 in Fig. 8 are connected analogously to the internal construction of a PUT or programable unijunction transistor. When the receiver is first turned on C709 is un-

R711 and the base-to-emitter junction of the vertical buffer Q702. As the capacitor discharges the current through the pair falls reducing the regenerative gain until the configuration can no longer maintain its latched condition. The transistors now revert to their non-conductive states and the cycle begins anew. The base of Q701 is an ideal place to insert the vertical sync pulse. A negative pulse here will cause the oscillator pair to turn on early synchronizing its cycle with the vertical sync timing. In the analogous pnpn PUT device the anode corresponds to Q701's emitter, its gate to the base of Q701 and the cathode to the emitter of Q701.

### Light activated controls

As television receivers become more automatic and color picture tubes become brighter, the idea of semi-automatically controlling brightness becomes impossible to ignore. After an initial adjustment of the brightness control, lowering ambient room light could lower picture brightness and vice versa. Magnavox is the first to bring this automated refinement into practical fruition. In addition to controlling brightness, contrast and chroma level are also changed to keep the picture properly proportioned. Fig. 9 shows the guts of the system. The videomatic light dependent resistor (LDR) becomes functional when the videomatic switch is turned on, ungrounding the LDR. The LDR in parallel with the SENSOR RANGE adjustment pot R211 are part of a voltage divider. Change in ambient light intensity has two effects in the Videomatic module. Let's assume an increase in room light has lowered the resistance of the LDR sensor. One effect is the lowering of current in the optical coupler's LED lowering the light emitted by the diode and the resistance of its coupled LDR. This LDR in series with the parallel combination of the 47- $\mu$ F capacitor and 4700-ohm resistor is in parallel with the 1000-ohm collector load of the 2nd luminance amplifier stage. The net effect then is a lowering of the collector load of this amplifier by the increase in ambient light lowering the stage's gain. The reduction in gain lowers both picture brightness and contrast, the proportioning determined by the ratio of unbypassed resistance to the bypassed 4700-ohm resistor. Returning to the Videomatic module the same increase in ambient light reduces the base voltage on the PNP emitter follower. The reduced output of this follower is routed to the color module biasing the acc demodulator in a direction to decrease the color level.

That wraps up nine important new circuits to see service in '73. **R-E**


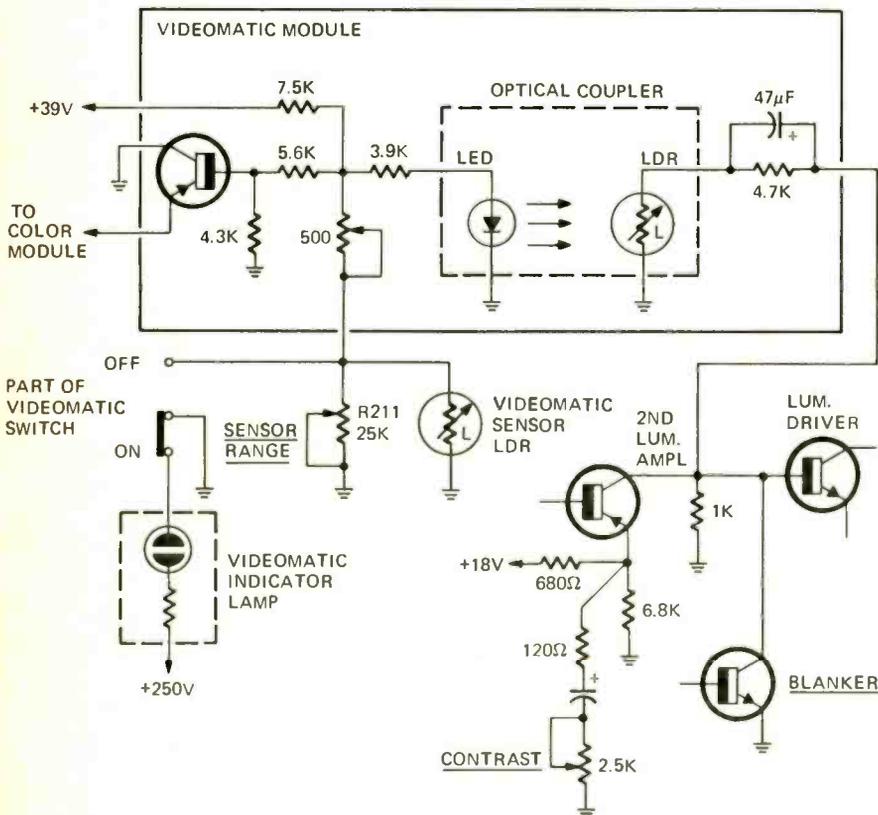


FIG. 9—VIDEOMATIC SYSTEM used by Magnavox controls automatic changes in brightness, contrast, and chroma level.

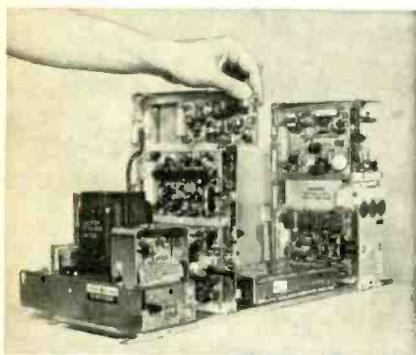

TEN PLUG-IN MODULES contain 66% of the total electronics components in this new color chassis from General Electric.

and effective idea. On this same chassis protection for the high voltage regulator is provided by using an SCR to open a circuit breaker in the secondary of the power transformer when the regulator is overloaded. The SCR gating circuit is designed so that occasional high voltage arcs will not trigger it. Sustained arcs however will open the breaker.

charged and both transistors are non-conductive. C709 charges with a time constant determined by its value and the combined resistance of R712 and the vertical hold control. C712 has a negligible effect on the charging time since it is 22 times smaller than C709. When the emitter of Q701 reaches the voltage on its base plus the base-to-emitter junction voltage the device starts to conduct, and because of its regenerative connection to Q700 the transistor pair turns on. The positive feedback of the transistor pair is explained as follows: As the base-to-emitter junction becomes forward biased its collector current increases from zero. Since the collector current of this transistor is also the base current of Q700 it also begins to conduct. The collector current of Q700 is in a direction to pull down the base voltage of the upper transistor turning it on harder, completing the feedback path. This action continues rapidly until the devices latch. When triggered on, all the terminals of the two transistors can be considered shorted together. C709 now discharges through

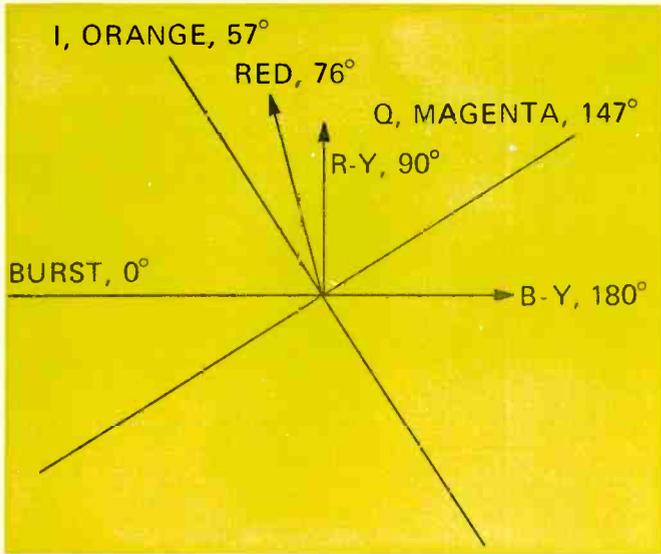


FIG. 1—COLOR phase diagram of a transmitted color signal showing I, Q, red and R - Y vectors

# AUTOMATIC COLOR CONTROLS

Almost every color TV maker is using some sort of automatic color control. Here's an introductory look at some of the circuits in the '73 color sets

by HAROLD STEVENS


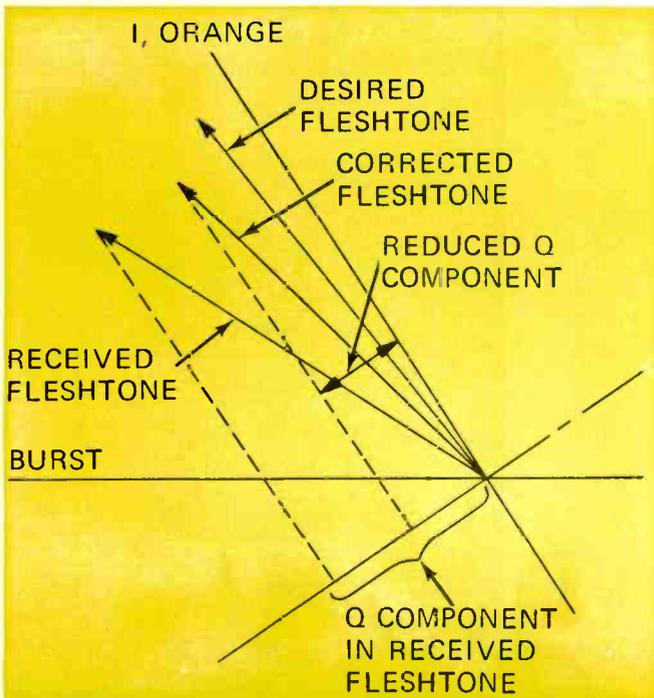


FIG. 2—FLESHSTONE errors are related to the Immaginary I and Q signals that do not actually exist in the receiver.

INSTAMATIC, ACCUCOLOR, PHILCOMATIC, ATC, One Touch. . . what's it all about. There is quite a bit of confusion surrounding automatic color and other systems. By listening to salesmen you usually get deeper into limbo. Let's delve into the mysteries of these systems and also try to determine what has created the need for them in the first place. All these systems are basically automatic tint correction schemes in various combinations with automatic frequency control and preset or narrowed range contrast, brightness, color and tint controls.

Stemming from the apparent inability of the TV stations from transmitting flesh tints of equal phase, not only from station to station, but from production to commercial, the automatic tint circuits are the center of some controversy. The problem is partly created by the fact that the signal is reprocessed at the point it is transmitted, which of course may be far from the originating source. When the sync and burst is reinserted errors occur. There have been several experiments with VIR (vertical interval reference) signals placed on the 20th line of the transmitted signal. Some say that the TV receiver should be equipped to operate on such a VIR signal to make error correction nearly perfectly. Others feel, that because of the complexity of the equipment needed to make corrections at the receiver it is logical that the stations use the VIR signal to correct the signals before they get on the air. We agree with the latter since the station should be responsible for doing everything within their power to transmit

*(continued on page 50)*

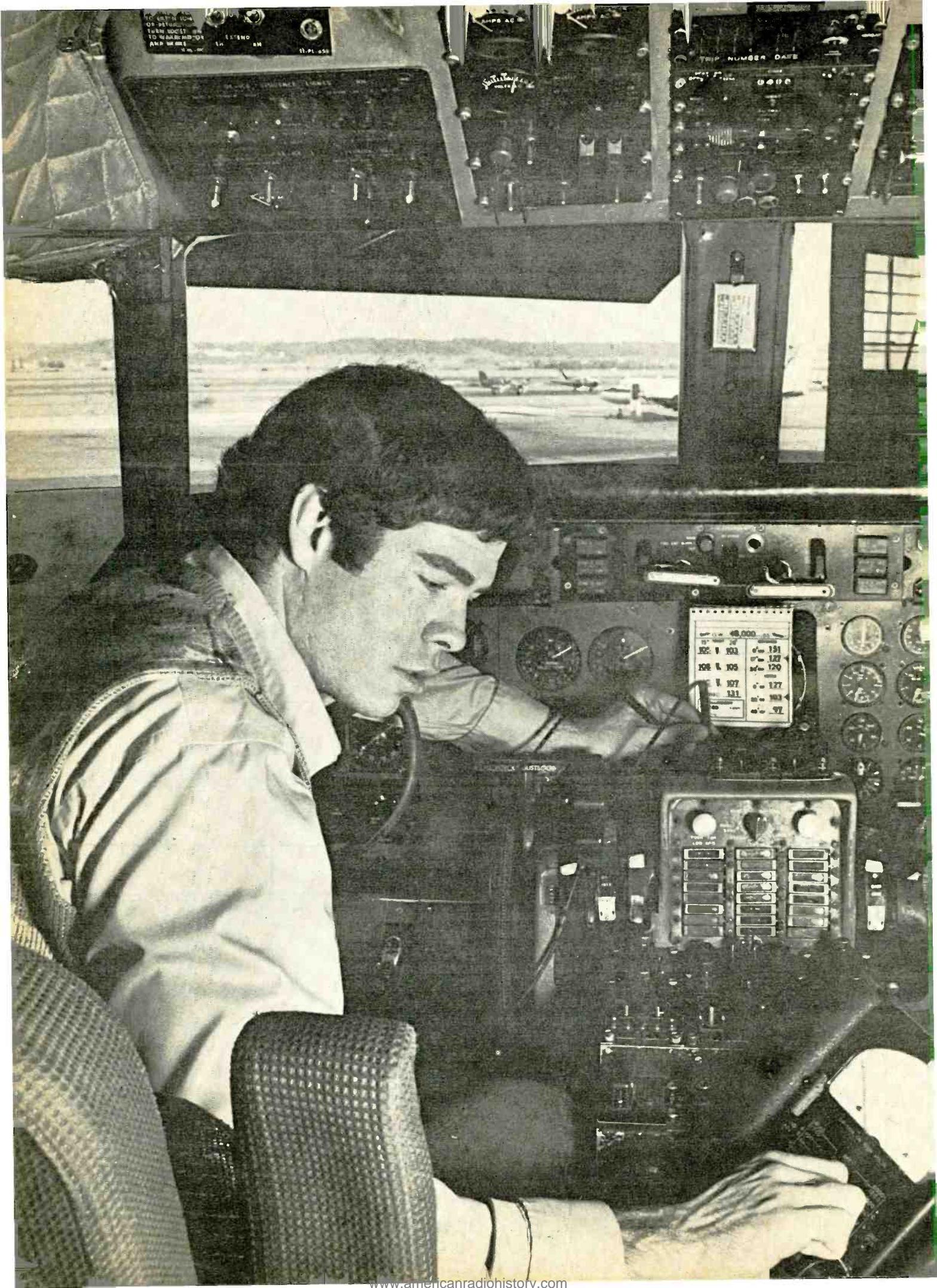

FOR THE USE OF THE  
PILOT IN THE  
OPERATION OF THE  
TURBO SUPERCHARGER  
AND ENGINE  
U.S. AIR FORCE  
11-PL-558

SAFETY

TRIP NUMBER DATE

48,000	
102 V 102	131
108 V 108	127
108 V 107	127
131	103
	97

## ADVANCED ELECTRONICS CAREER TRAINING AT HOME

Modern aircraft are loaded with vital electronic equipment. There is equipment for communications, direction finding, instrument landing and for many other functions to insure safe operation of the aircraft.

The man who checks out this equipment has to be an expert. Many lives depend on his specialized knowledge as an engineering technician. His work is interesting and exciting and he enjoys top pay in his field.

# Consider a career In advanced electronics

Aeronautical and Navigational Electronics is just *one* of the advanced electronics programs CREI offers. There are *seventeen* others. All of the programs, except a brief introductory course, are college-level. The programs cover every major field of electronics today.

If you want to qualify for the highest paying level of technical employment in electronics, we invite you to consider the unique home study programs of CREI. Here is a list of just some of the CREI programs: *Communications Engineering • Computer Engineering • Missile & Spacecraft Guidance • Radar & Sonar • Television Engineering • Nuclear Instrumentation & Control • Digital Communications • Industrial Electronics • Electronic Systems Engineering • Microwave Communications • Satellite Communications • Cable Television Engineering*

For over 45 years, CREI programs have been recognized by industry and government as effective home study training in advanced electronics.

**Qualifications to enroll.** To qualify for enrollment in a CREI program, you must be a high school graduate (or equivalent). You should also be working in electronics or have previous training in this field.

**Send for FREE book.** If you are qualified, send for CREI's newly published book describing your career opportunities in advanced electronics. This full color book is filled with facts about career opportunities for you.

**Capitol Radio Engineering Institute**  
**A Division of McGraw-Hill Continuing Education Co.**  
3939 Wisconsin Avenue, Washington, D. C. 20016



Accredited Member, National Home Study Council

CREI, Dept. E1401D  
3939 Wisconsin Avenue  
Washington, D. C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

If you have previous training in electronics, check here

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_

Veterans and servicemen, check here for G. I. Bill information

**CREI**  
**CAPITOL**  
**RADIO**  
**ENGINEERING**  
**INSTITUTE**

WASHINGTON, D.C.



a technically correct signal.

Anyway while the experimentation and discussion goes on we are stuck with second best. Everybody has jumped on the bandwagon with automatic tint correction to automatically bring flesh tones closer to their ideal hues. The system works but we don't get something for nothing. It turns out these automatic correction schemes introduce a form of distortion. However with most average pictures, and without a side by side comparison the overwhelming opinion is that the distortion is small. Because of the profusion in which these circuits have appeared plus the useful function they perform it behooves us to understand the basics of their operation and some of their specific applications.

Once the explanation of the two phase diagrams Fig. 1 and 2 are understood, the rest is easy. Fig. 1 is the phase diagram of a transmitted color signal showing the I, Q, red and R - Y vectors. Color TV uses a quadrature modulation system so called because amplitude and phase information can be encoded and demodulated from the same carrier by using two demodulators with a phase shift of 90 de-

grees between their carrier inputs. The important point is that we can create a modulated signal that is shifted in both phase and amplitude. In this case the amplitude is chosen to represent the color amplitude or saturation while the phase information represents the hue or color. The reason we always see the I and Q carriers on these diagrams is that these are the two phases of 57° and 147° with respect to the burst that the transmitter uses to generate the chroma signal. On this diagram any particular angle of a drawn vector corresponds to a different hue. The I vector happens to correspond to orange close to the flesh tones we are so interested in, and the Q vector corresponds to magenta. For illustration we have included a red vector that has an angle of 76 degrees clockwise from the reference burst. The receiver, by comparing the instantaneous phase of the chroma signal to the burst sent during the horizontal blanking interval determines the hue at any given moment. In the early days of color television, receivers would actually demodulate along the I and Q directions and then convert these into red, blue and green drive

signals by a rather complex matrix. Experience with the animal soon led to the simpler method of detecting along the R - Y and B - Y axis. Located 90° from the burst is R - Y and at 180° B - Y, where Y represents the black and white or luminance signal. If the received color signal is demodulated along these 90 and 180 degrees axes, upon adding back in the luminance signals we have reproduced the red and blue signals. A simple matrixing produces the G - Y from the other two color difference signals and we're set. The I and Q vectors are just used as points of reference and in fact do not actually exist in the receiver unless they are produced by matrixing for some purpose. In Fig. 2 we will relate flesh tone errors to these two imaginary I and Q signals. It turns out these two are indeed convenient for reference since the I vector is very close to the flesh tones that cause trouble. In this diagram we have labeled one vector "desired flesh tone." This is the angle which in our particular imaginary receiver represents flesh tone. This is the angle at which we want a received flesh tone to coincide. Because of some source of error, however, we actually

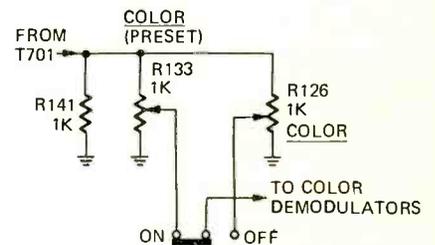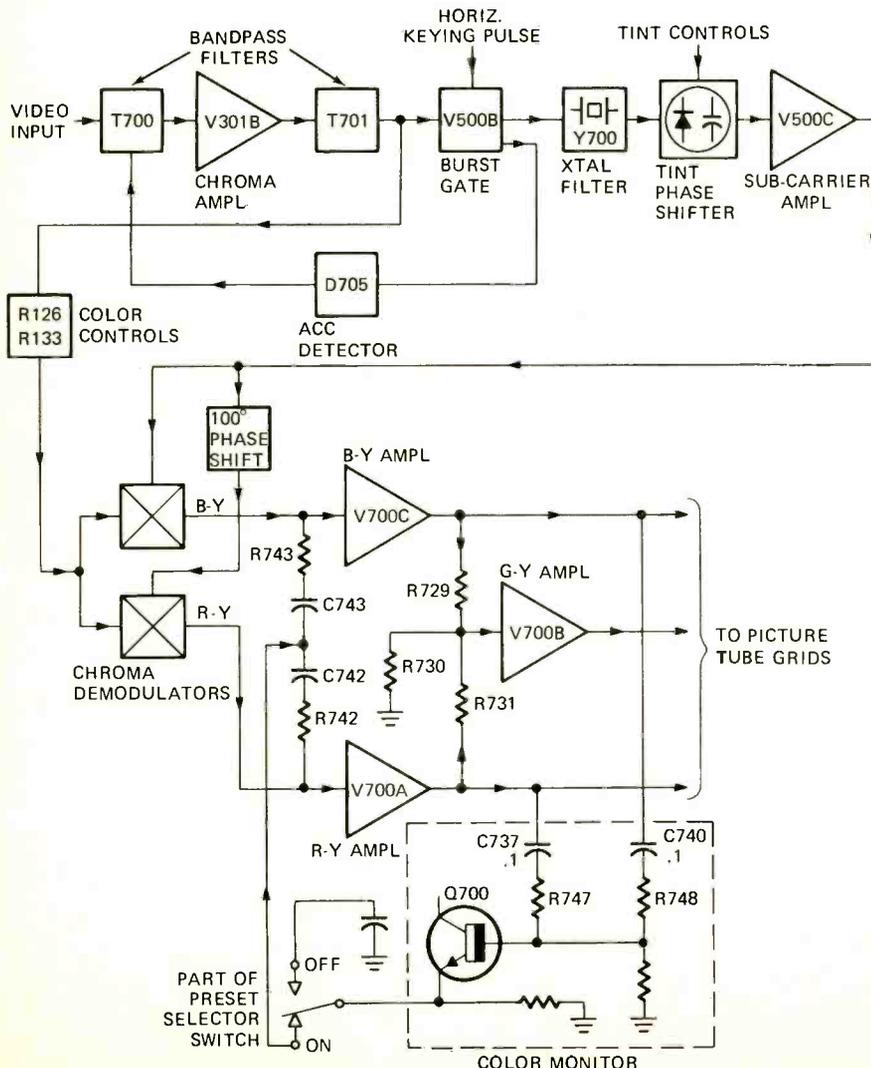


PART OF PRESET SELECTOR SWITCH

FIG. 3—(left) BLOCK DIAGRAM of the color-processor circuit used by Admiral. It is a ringing-type system.

FIG. 4—(above) COLOR CONTROL scheme in Admiral receivers is a simple attenuator with the color control the variable element.

FIG. 5—(below) THIS AUTOMATIC TINT circuit is used by Admiral. They call it their "Color Monitor."

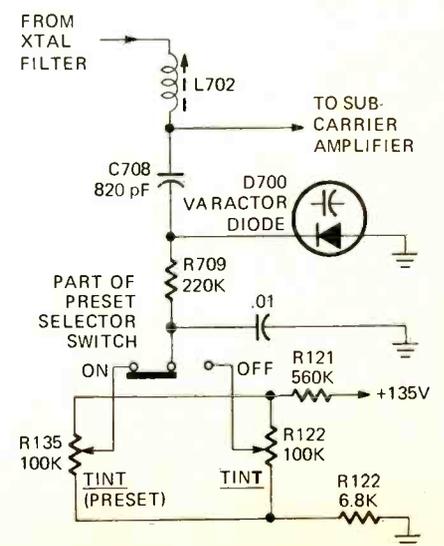

receive a fleshtone at an angle indicated by the "received fleshtone" vector. Now what we want to do is to rotate this vector as close as possible to the desired fleshtone vector. Any vector can be broken up into components on two other axis. We can take the received fleshtone vector, for example and break it up into two components along the I and Q angles by drawing perpendicular lines to these two from the end of the vector. Note the Q component results in the corrected vector shown in the diagram. This one is much closer to the desired fleshtone and we have reduced the error. It can be shown mathematically that one way to produce this effect is by doing two things. First change the demodulation angle between the R-Y and B-Y vectors. The R-Y axis is rotated counter-clockwise in the vicinity of 70° and the B-Y axis shifted clockwise toward 200° increasing the angle between the two. The second thing that has to be done is to reduce the amplitude of the blue signal. This is the most popular method used to produce automatic tint correction. The other ways to reduce the Q or non-fleshtone components will be discussed when they appear. You can think of the effect by viewing the unmodified phase diagram as a circle with all colors having equal magnitudes. The modified diagram then becomes an ellipse with the minor axis corresponding to the Q vector. The circle has been squashed at its middle to reduce phase angles away from the fleshtones. This is why we say this system creates distortion since the various

hues are changed depending on their particular phases.

### Who is doing what

Admiral-Color Master is the name of this system. When it's switched in four things happen. The automatic frequency control is activated, the front mounted color and tint controls are disconnected with the rear mounted color and tint controls functionally replacing them, a blue light is lit, and of course the color monitor or flesh tone correction scheme turned on. Fig. 3 is the block diagram of Admiral's color processor. It is a ringing type system as the regenerated 3.58-MHz carrier is produced by ringing a crystal filter by passing the burst signal through it. The system does not use a color killer since lack of burst information will produce no sub-carrier. The color difference signals are applied to the picture tube grids. The required red, blue and green signals are produced in the picture tube by inserting the luminance or Y signal at the cathodes. The G-Y signal is formed by a simple voltage divider matrix from the B-Y and R-Y signals as suggested earlier. Fig. 4 shows the color control scheme is simply an attenuator with the color control the variable element. The preset operates by switching between the wiper of the front mounted color control and the rear mounted preset. The tint control circuit of Fig. 5 is the type of system which is going to predominate in the future. It's significance is that it is a dc control. There is no ac signal appearing on the con-

trol itself. This gives the manufacturer a great deal of freedom in placing the control since he does not have to worry about the effect of the cable length and its exact positioning. Also there are the cost savings of eliminating coaxial runs and the reduced number of shield connections. The scheme works by the position of the tint control determining the reverse bias of the varactor diode and in turn it's capacitance. Since D700 is part of an LC phase shifter, varying its capacitance changes the shift through the network having the desired effect. Again the Color Master switches in the preset control by selecting its wiper. In this system the front-mounted controls are completely disconnected and have no effect when Color Master is activated. Return now to Fig. 3 Admiral's version of automatic tint circuitry. Color Monitor. This first system we're looking at works differently than the widened phase angle method we discussed previously. Here we mix the correct proportion of B-Y and R-Y signals to reproduce the Q signal we are trying to reduce. In this instance the Q signal is not imaginary but real since we have reformed it. The matrixed signal at the base of auto tint transistor Q700 is fed back to the inputs of the B-Y and R-Y amplifiers. The Q components of the color signal find themselves in the degenerative feedback path of these amplifiers reducing the Q amplitude and correcting the fleshtones.

In Admiral's M20 modular chassis the Color Master system has the same

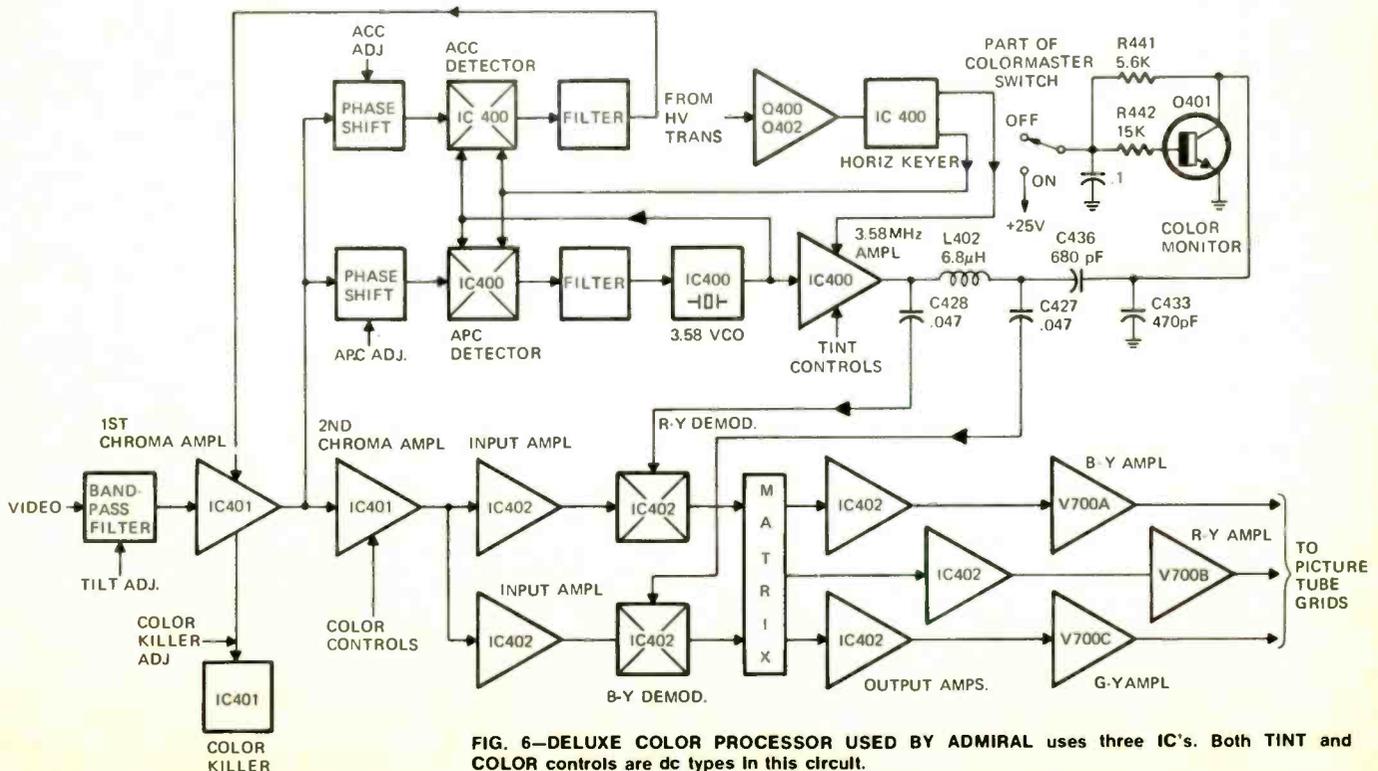


FIG. 6—DELUXE COLOR PROCESSOR USED BY ADMIRAL uses three IC's. Both TINT and COLOR controls are dc types in this circuit.

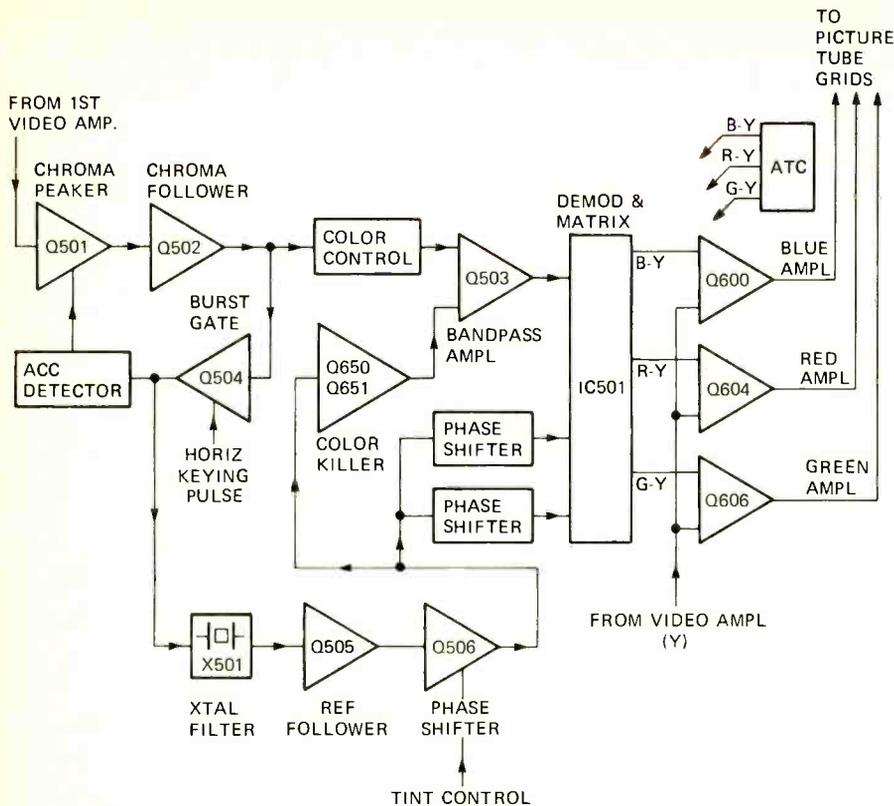


FIG. 7—GE COLOR PROCESSOR is used in many '73 chassis. The "One-Touch" circuit includes TINT, COLOR controls and the TINT LOCK circuit.

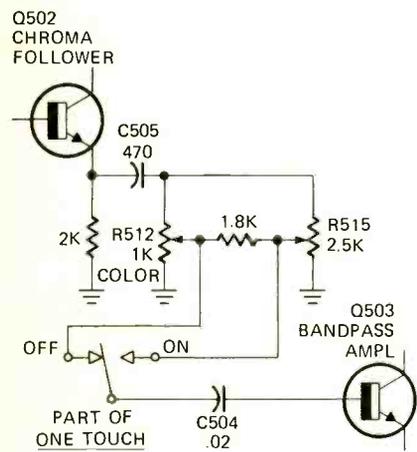


FIG. 8—CLOSE-UP OF COLOR CONTROL used in GE JA chassis. This is a part of the "One-Touch" color system.

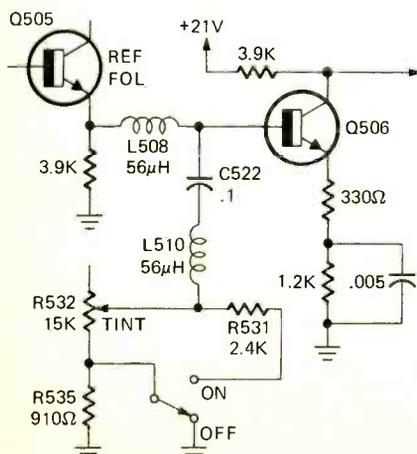


FIG. 9—THIS TINT-CONTROL CIRCUIT is also a part of the GE "One-Touch" color system. It too, is used in the JA chassis.

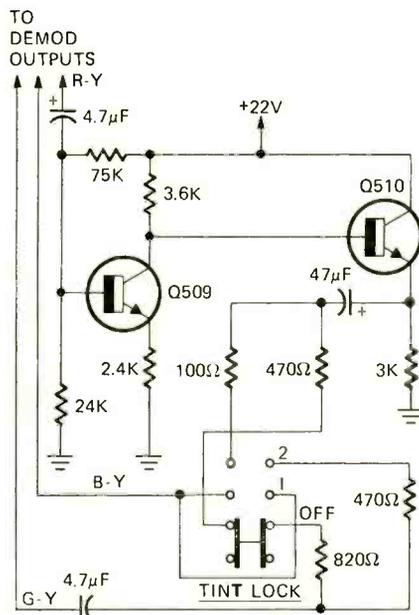


FIG. 10—TINT-LOCK CIRCUIT changes the color difference matrixing in the right ratios to reduce the Q component in GE color sets.

effect but the automatic tint circuits work differently. The presets operate exactly as before. Fig. 6 is the block diagram of the M20 processor. This system uses three IC's. IC400 is the subcarrier regenerator which produces the 3.58 MHz subcarrier by the action of a phase-locked-loop operating on the keyed burst. This is a more theoretically ideal system and is a good illustration of where integrated circuits prove their worth. Both tint and color controls are dc types in this circuit. The *Color Monitor* in this receiver

works by switching Q401 on or off. When the transistor is off C436 and C433 are series connected to ground and when the transistor is on C436 is effectively connected directly to ground. This changes the phase shift of the sub-carrier reference to the B-Y demodulator.

**DuMont**—As far as we could tell the DuMont system is identical to the previous one, except that it is called *Dumatic*.

**Emerson**—Again this system "*Permacolor*" is similar to Admiral's with two variations. First the aft system is activated separately from *Permacolor* and has its own switch. In addition to the Color and Tint presets there are brightness and contrast presets. All these systems are tested by setting the tint controls to give greenish or purplish faces. When the tint correction circuits are turned on a shift toward the normal flesh tones should be seen.

**General Electric**—The "*One Touch Color*" system is featured on their JA 10- 16- and 19-inch sets and the MA 25-inch modular chassis. Fig. 7 is the block diagram of the JA one-chip (IC) color processor with Figs. 8, 9 and 10 showing the color control, tint control and Tint Lock circuits. In the GE system when *One Touch* is turned on, a neon lamp is lit, the color and tint ranges are narrowed and apc is enabled. The tint correction scheme called *Tint Lock* is activated by a separate switch with two degrees of correction selectable. The color control is prejudiced by the setting of the 2.5K pot in Fig. 8 when *One Touch* is activated. The color control now has a more limited range and while the control is going to be closer to normal setting if misadjusted, some range of control is left in the user's hands. The tint control works similarly with a reduced range by switching some resistors. Incidentally note that this receiver uses a RGB system where the luminance or Y signal is combined with the color difference signals ahead of the picture tube. The *Tint Lock* system works by switching in a two stage matrixing amplifier as shown in Fig. 10. This changes the color difference matrixing in the right ratios to reduce the Q component.

The *One Touch* system in the MA chassis (Fig. 11) gives the same results. Again a three position *Tint Lock* switch is used with Off, 1 and 2 positions. This gives a choice of the normal 104° or widened 135° demodulation angle. The tint control range is reduced to about 40 degrees while maintaining the average tint level. The color gain range is also reduced while maintaining the same average dc level. This chassis uses a two-chip (TC) color processor. IC601 contains the

(continued on page 71)

# the state of

## SOLID STATE

*A glimpse into the future at what's on store for semiconductors  
and at what's new in semiconductors and associated hardware.*

by LOU GARNER  
SEMICONDUCTOR EDITOR

FOR NEARLY TWO DECADES, NOW, we've enjoyed playing a "guessing game" with the electronics industry. From time to time, we've predicted new developments in technology, guessed at the introduction of unique devices, and projected the manufacture of various solid-state products. Back in the early 1950's, for example, in an elementary book on transistors, we predicted that . . . *within a minimum of five, a maximum of ten, years, more transistors than vacuum tubes would be used in the manufacture of new electronic equipment.* Written at a time when a so-called "low-cost" experimenter's transistor sold for \$7.50 each (that's right, *seven dollars* and fifty cents!), and more reliable units hit the fifty dollar, or better, mark, this prediction brought guffaws from tube manufacturers, gales of laughter from vacuum-tube circuit designers, and even skeptical smiles of disbelief from semiconductor producers.

*But the prediction came true!!!*

Our batting average, over the years, has been a little better than fair-to-middling. Of all the predictions made, 97.3% have been fulfilled, although not necessarily within the time limits we projected; however, 89.6% did come true within the predicted time limits.

### The crystal ball game

Following established tradition, we're climbing out on the proverbial limb with the following predictions for 1973:

- *Low-cost LED's other than red and infrared.* While the prices of some light-emitting diodes have dropped considerably, the cost of green and yellow devices remains quite high, but we now foresee a significant reduction

in the prices of LED's furnishing other than red (or infrared) light. You can expect a 2-color LED too. It changes from red to green as the applied voltage is increased.

- *A new solderless breadboarding system.* Although a number of specialized solderless breadboards have been developed over the years, few have involved complete systems, including components as well as a chassis. We predict, then, the introduction of a new and unique breadboarding system ideal for the assembly of equipment designs using IC's and readily adaptable to discrete component circuits as well.

- *Inexpensive programmable solid-state electronic calculators for small business and consumer applications.*

The overwhelming success of the pocket electronic calculator using LSI circuitry will lead, we feel, to the introduction of low-cost programmable calculators, with special programs for, say, real estate dealers, insurance salesmen, and income tax preparers. Offhand, we project a selling price of under \$200.00, retail.

- *A new electronic accessory for automobiles.* Heretofore, the majority of solid-state automotive accessories have been simply semiconductor versions of previously existing products. The transistorized ignition system, IC voltage regulator, or solid-state radio are typical examples. We foresee the introduction of a completely new auto accessory made possible by advanced semiconductor technology and possibly incorporating a special LSI chip as well as digital displays.

- *The development of a new manufacturing technology.* The actual cost of materials in most semiconductor devices, even complex LSI's, is but a

few cents. Such factors as yield rate, assembly, and testing contribute to selling prices in the multidollar range. We envision a significant development which may drop the eventual cost of IC's to the price of single transistors.

- *Low-cost solid-state electronic calculators.* The handwriting is clear on this one. Although (as this is written) electronic calculators are now selling in the \$60.00 to \$150.00 price range, we feel that mass manufacturing economies will drop the price below \$50.00 before the end of 1973, virtually driving low-cost electromechanical calculators off the market.

- *A significant breakthrough in electro-optical display arrays.* We find the vision a little blurred on this forecast, but have a feeling it has something to do with TV sets. Could be digital, however.

- *An exciting new solid-state crime fighting product.* With the crime rate increasing in most areas, we'll keep our fingers crossed on this prediction, hoping we're right.

That's it for 1973—next January we'll see how we made out.

### FET circuits revisited

Last September, you may recall, we featured a pair of interesting FET circuits abstracted from *FET Design Ideas*, Bulletin CB-145, a valuable 20-page booklet published by Texas Instruments, Inc. (P.O. Box 5812, Dallas, Tex. 75222), promising to review other circuits in the future. In accordance with our promise, and in response to numerous reader requests, we are pleased to feature two more circuits from the TI booklet—a wide-band amplifier and a MOSFET video i.f. amplifier, illustrated in Figs. 1 and 2, respectively.



paper and positioning each Mini-Mount on a suitable flat surface, such as a copper-clad ground plane board, as shown in Fig. 4. Component

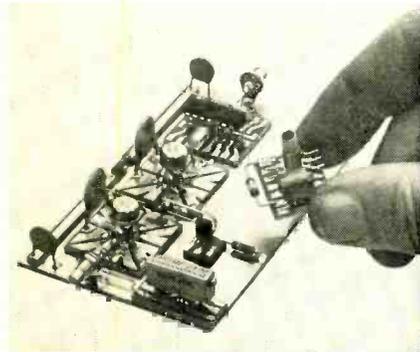


FIG. 4—ASSEMBLING AN EXPERIMENTAL circuit using Mini-Mounts.

interconnections are made using conventional hook-up wire and lap solder joints.

The adhesive-backed elements may be purchased separately in packages of ten or twenty units, depending on type, for \$3.80/package, or as part of prepared kit assortments. Currently, the manufacturer is offering three basic kits: the **STARTER KIT** at \$6.50, which includes 15 assorted Mini-Mount elements and a 3" X 4" ground plane, the **EXPERIMENTER KIT** at \$28.50, which includes 75 assorted elements and a 3" X 4" ground plane, and the **PROFESSIONAL KIT** at \$75.00, which includes 250 assorted Mini-Mounts and a 4" X 8" ground-plane board. A fixed charge of \$1.50 per order covers postage and handling; in addition, the 5% California sales tax applies to orders from state residents. An illustrated 4-page brochure describing the Mini-Mount system is available on request.

### Device/product news

Texas Instruments, Inc. (P.O. Box 5012, Dallas, Tex. 75222) has expanded its TMS0100 family of "calculator-on-a-chip" MOS/LSI integrated circuits to nine standard devices. Designed for use in low-cost calculators, the units are offered in both 8- and 10-digit versions. Each comprises all the basic circuitry needed for a standard calculator, except for power supply, readout, and keyboard; included are a program ROM, RAM storage, an input encoder, control and timing circuits, and output decoders, as illustrated in Fig. 5. Basically similar, the different versions vary in type of roundoff provided, error and overflow fonts, seg blanking, and keyboard-entry systems.

Also from TI . . . a new precision level-detector IC featuring an adjustable threshold level. Designated the SN72560, the new device, Fig. 6, allows designers to adjust the trip point to the most appropriate level for par-

ticular circuit needs, thus making it suitable for most level-detection applications requiring Schmitt trigger action. The unit's low input current of only 2 nA and high output current of 100 mA make it ideal in applications for interfacing between low-level systems and TTL, lamps, solenoids, relays, SCR's, or triac systems where precision level detection is required. It may be operated by typical logic supplies or by popular battery voltages ranging from 2.0 to 6.0 volts, but output voltages may be as high as 25 volts if required. Offered in both 8-pin plastic DIP's and 8-lead metal cases, the SN72560 is specified to operate over the 0° to 70° C. industrial temperature range.

RCA's Electronic Components group (415 South Fifth St., Harrison, N.J. 07029) has announced a new line of solid-state microwave diodes. Characterized as CW Transferred-Electron Oscillator (TEO) devices, the sixteen diodes in the line include four types at each power level: 10 mW, 30 mW, 60 mW and 120 mW. All utilize gallium arsenide (GeAs) chips and are intended for the direct conversion of dc power into C- and X-band microwave energy in suitable circuits with 8 to 15 volts input. An Engineering Note, MED-310, *How to Use the Transferred Electron Diode Characterization Data*, as well as a technical bulletin describing the devices, types S3012 through S3027, is available from RCA's Commercial Engineering department at the address given above.

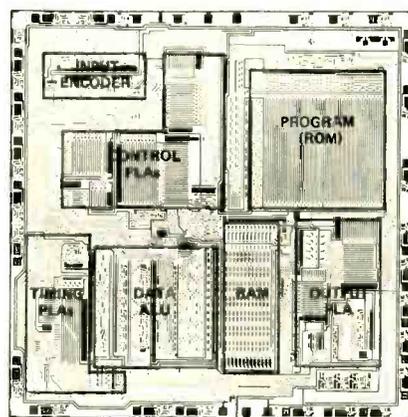


FIG. 5—TI's "CALCULATOR-ON-A-CHIP" element layout—blocks designate the various circuit functions.

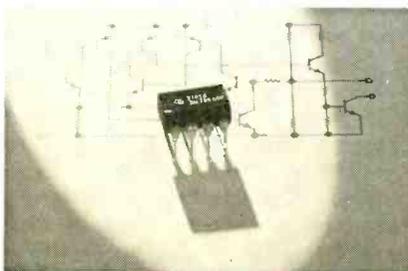


FIG. 6—TYPE SN72560 PRECISION level detector recently introduced by TI.

Twelve new fast-recovery silicon rectifiers are now available from RCA's Solid State Division (Route 202, Somerville, N.J. 08876). Designated developmental types TA8411 through TA8422, the units are offered with prV ratings of 100V, 200V, 400V, and 600V, at current ratings of 6, 12 and 20 ampere. Both forward-polarity (cathode connected to stud) and reverse-polarity (anode connected to stud) types are available, with the latter identified by an "R" suffix added to the type number. Assembled in hermetic DO-4 or DO-5 (stud) packages, all types are intended for use in high-speed inverters, choppers, high-frequency power supplies, "free-wheeling" diode circuits, and other high frequency applications.

A monolithic phase-locked loop IC designed for general purpose tone and frequency decoding has been introduced by Exar Integrated Systems, Inc. (750 Palomar, Sunnyvale, Calif. 94088). Identified as type XR-567, the new device operates over a 0.01 Hz to 500 kHz frequency band and has a logic compatible output which sinks up to 100 mA of load current. Illustrated in Fig. 7, the XR-567 comprises

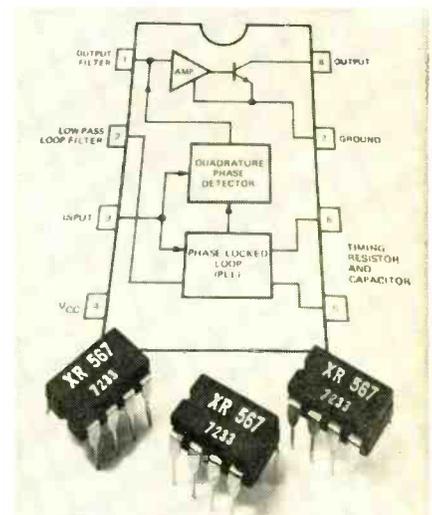


FIG. 7—EXAR NEW XR-567 IC, a monolithic phase-locked loop IC.

a phase-locked loop (PLL), a quadrature AM detector, a voltage comparator, and an output logic driver. Its bandwidth is adjustable from 0 to 14 percent, while its center frequency can be adjusted over a 20:1 range by a single external resistor. The device may be used as a dual-time-constant tone decoder, as a narrow-band FM demodulator with carrier detection, as a standard dual-tone decoder, and as a FSK decoder. It is offered in both 8-pin TO-99 metal cans and 8-pin dual-in-line packages, and is available in versions with either military or commercial temperature ratings.

That closes out the book for January, but, lest we forget—**HAPPY NEW YEAR!!** **R-E**

WHAT'S A "COLOR TV TEST JIG?" AN extremely handy thing for servicing color TV sets. For those who haven't seen one yet, a test jig consists of a color picture tube, mounted in a cabinet. The deflection yoke, convergence yoke, and convergence board are mounted on the tube and cabinet. This is connected to the chassis with extension cables. Many jigs have a built-in, permanently-connected voltmeter for monitoring the high voltage. Others have a built-in dc milliammeter for monitoring the all-important cathode current of the horizontal output tube. One even has its own built-in color-bar generator!

The jig sits on the bench in the shop (or above it). When a color TV set must be serviced in the shop, only the chassis need be brought in. The

eration. It could also be used for those sets with "reparable" modules, such as Zenith, Motorola, etc. After the defective modules have been brought back to the shop, and the bad parts replaced, they could be tested on the jig. This, of course, would apply mainly to the shops specializing in service for one make.

Practically all major U.S. manufacturers provide test jigs for their own products. RCA was the first to provide them. For a long time, RCA has used the same standard plugs on their yoke and convergence cables, so that any RCA chassis can be operated on the same test jig. Color sets of other makes can also be operated on this jig, by using conversion adapter cables, to fit the Molex and any other specialized plug-socket combination.

on one end and the smaller socket on the other, (also vice versa) takes care of the differences in base sizes. So, a single jig of either type will be usable on a great many sets.

The question arose concerning the smaller picture tubes, some of which have different basing; the General Electric 11WP22, with all three cathodes internally connected, and a few others. The answer, of course, is that most of these are in *small sets*, and won't need a jig! They can be "carried-in" to the shop for service. In an emergency, for making a substitution test of the picture tube, a simple adapter harness could be used. This is one that hasn't come up in actual operation as yet, but it might.

Let's see how this test instrument can be used. The chassis is brought in,

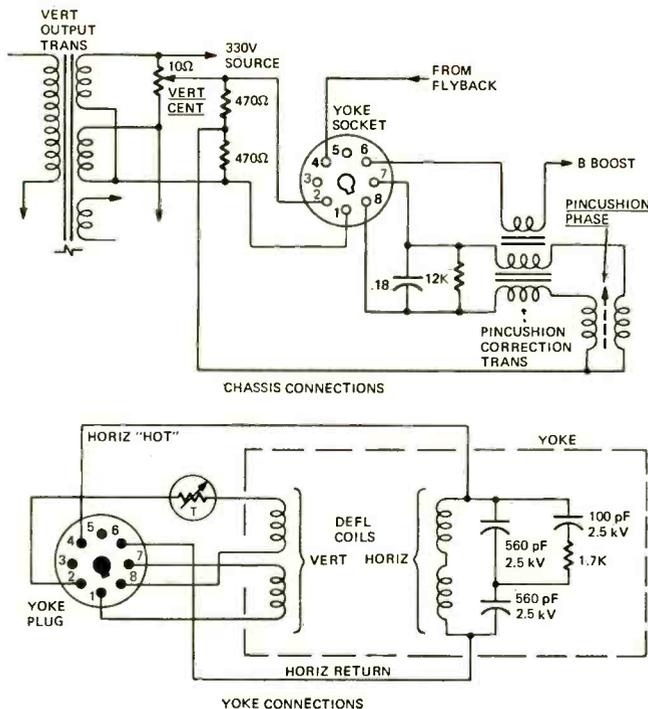


FIG. 1—DEFLECTION-YOKE CONNECTIONS on Sylvania D-12 chassis. Note pin-cushion correction network between vertical deflection coils.

# Color

A color test jig is a great technicians' helper on Here's what's available

massive cabinet and picture tube are left in the home. With some of the 9-foot long credenza type cabinets used today, this can be very handy! The chassis can be pulled and brought in by one man. So, this can effect a real saving in the operating cost of a service call. The outside technician can work alone, without a helper or an extra technician, which could be another time-saver. If there are two technicians on a call, the chances are they'll spend a good deal of time *arguing* about what the trouble is!

The ultimate in test jigs, for some of the new modular sets, would be a complete unit, with all modules. In difficult cases, this could be used to check out problems by plugging the suspected modules into the "known-good" jig and checking for normal op-

RCA has a program called "ICTJ" (Industry Compatible Test Jig). They publish a handbook which lists all of the adapter cables needed to connect color TV sets of other makes to their standard jigs. At this writing, sets of 37 different manufacturers, including several of the bigger import brands, are covered. The ICTJ Handbook is updated at regular intervals.

Luckily for us (and for those who build test jigs) the vast majority of color picture tubes are standardized. The bases of all of the 70° round tubes are the same, and so are the 19-, 23- and 25-inch rectangular 90° types. Thus jigs with round tubes can be used to test sets built for the rectangular types, and vice versa. A simple extension harness having a "big base"

set up in a convenient position on the bench, and connected to the test jig. This requires a minimum of four cables. One for the deflection yoke, one for the picture-tube socket, one for the high-voltage lead and, most important, a good **GROUND!** If you forget the last one, you'll be most rudely reminded of it the first time you touch the jig and the chassis at the same time. The older jigs are in metal cabinets; the new compact jigs are in plastic, but hook up the ground anyhow! (I have attached dual ground leads to mine, using heavy clips. That way, if I knock one off, moving the chassis, I've got a spare.) (The "belt and suspenders" method.)

## The convergence board

In a lot of sets, the convergence

board can be left unhooked. The only ill effect will be a slight mis-convergence, mainly dynamic, at the edges. All of the commercial test jigs have static convergence magnets. Manufacturer's jigs, such as RCA, etc. have the complete convergence yoke and control board, of course. Mis-convergence can be ignored while servicing. In any case, convergence adjustments should **not** be done on the jig; the excess capacitance of the extension cables will cause mis-convergence when the set is put back together.

The worst problem in leaving the convergence board off will be in those sets where the vertical output tube cathode circuit returns to ground through the convergence circuitry. In these, you'll see a loss of height, verti-

flyback was replaced! If this kind of problem comes up, the set's own convergence yoke and board can be taken off, brought to the shop and slipped onto the tube in the test jig, for easier servicing.

**Special hookups**

The worst problem, of course, is in using the test jig on sets of a different make. This is where the cross-reference Handbooks, such as RCA's ICTJ book and others come in very handy. However, in emergencies, you can hook up practically all sets, by checking the deflection yoke connections.

There are at least four leads which must be properly hooked up. The horizontal deflection coil will have two, the "hot" and the return

pins 7 and 8 on the yoke socket, to complete the circuit. Any pincushion distortion, like misconvergence, can be ignored.

You can always check your jig hookup by remembering what the problem was in the home. For example, if the set was brought in for a sync problem, and now you have no vertical sweep, no high voltage, etc, this is a jig problem, and must be corrected before you can get on with the rat-killin'.

There is one problem, on all jigs, which you will notice, and which should be ignored. This will also show up when using a color set on its own picture tube, with extension cables, for that matter. This is a distinct smearing of fine horizontal detail in the picture. I've christened this "Jig-smear". It's

# TV Test Jigs

*time-saver that can replace the outside color TV service calls. and how you can use 'em.*

by EUGENE CUNNINGHAM

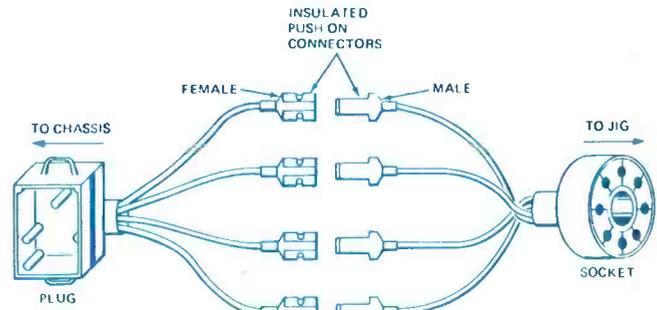


FIG. 2—HOME-MADE ADAPTER CABLES can be used to match almost any color TV set to your test jig. Matching plugs and sockets and insulated push-on connectors do the trick.

cal linearity, etc. In most of these, a dummy load can be used; this plugs into the convergence socket, completing whatever circuits would be left open in this particular chassis.

Actually, true convergence-trouble is uncommon, in the sense of part-failures. Most of it is due to mis-adjustments. Real trouble can always be identified by a few tests. If any control has no effect on the lines it's supposed to control, that's it. Check for defective controls, coils, wiring, clamp-diodes, **and** for the presence of the convergence pulse waveforms with the proper amplitude **and** polarity! One problem was solved by discovering, with the scope, that the convergence pulses were present, but were inverted! Someone had reversed the wiring to a pulse winding when the

leads. In some chassis, there will be a center-tap on the horizontal deflection coil. The later jigs have this connection on their yokes; in many cases, it can be left open without trouble. The inductance of the horizontal yoke winding is usually close enough to the original so that it will work.

For the vertical winding in the yoke, most sets use only two leads, hot and return. The main problem here is getting these hooked up so that the picture is right side up. Actually, it doesn't make any real difference, but it looks funny. In a few chassis, you'll find pincushion-correction networks connected between the two vertical windings of the yoke. Fig. 1 shows such a circuit, as used in Sylvania's D-12 chassis. This can be hooked up for test purposes by shorting between

caused by the added shunt capacitance of the picture-tube extension cable, in the video circuits. It is not too bad, but it must be recognized, so that you don't waste time checking video stages, alignment, etc. when it is not necessary! You can check out a couple of chassis which do have good horizontal resolution, and see exactly what I mean.

**Emergency adapter cables**

It should be possible to hook up any "standard" U.S.-built chassis to a test jig, if you have the right cables. In an emergency, you can make up this cable. Fig. 2 shows a rough sketch of how this could be done. The socket fits the yoke plug on the cable from the jig's yoke. The socket is of whatever type is used on the TV set. The

leads from the jig-yoke socket should be plainly tagged "H-Hot", "H-Ret" (urn) "H-CT", etc. By putting push-on connectors on these, and mating connectors on the leads from the "set-socket", as shown, you can cross-connect the two together so that each lead goes to the right pin of the set socket. (Insulate them! They bite!)

The schematic diagram will show you how the set is hooked up. By tracing each lead out as to its function, it should be fairly simple to match the connections.

### Tube-type jigs vs transistor type

As a general rule, color sets with transistor deflection circuitry cannot be used on the same jig used for testing tube-type color sets. There is some disagreement about this among test-jig

### Commercial test jigs

The first test-jigs were simply cabinets and yokes, plus the picture tubes, from old TV sets. Later on, as this became more popular, special cabinets were built for them, as you'll see. Fig. 3 shows the RCA 10J102/-104 test jig, with its built-in high-voltage meter. With the *ICTJ Handbook*, and suitable adapter cables, this will handle any tube-type color set, including several of the more popular imports.

Lately, a new item has been added. This is the portable test-jig, 10J103 (tube) or 10J105 (transistor) seen in Fig. 5. It uses an 18-inch color picture tube, and has the built-in high-voltage meter, and all of the features of the bigger jigs. The cabinet is made of high-impact plastic, and has feet so that it will stand anywhere on

As I said before, practically all of the major U.S. setmakers provide test-jigs for use with their own sets. Adapter cables for different models of their line are available. Magnavox, for example, provides a continuously updated cross-reference, and conversion data, for the necessary adapter cables to use the jig with newer models. These can be bought from the Magna-Par parts depots, ready-made, or assembled in the shop, using the right plugs, sockets, etc.

### Universal test jigs

There are companies who make test jigs for use with sets of all makes. Some of these make the jigs for the manufacturers.

**The Pix-O-Scope jigs.** The Pix-O-Scope Company, 3311 Shelby St., In-

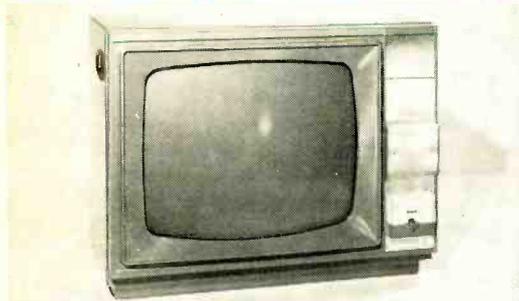


FIG. 3—RCA 10J102/104 TEST JIG has dc voltmeter.



FIG. 4—ADAPTO-SCOPE universal yoke connector.

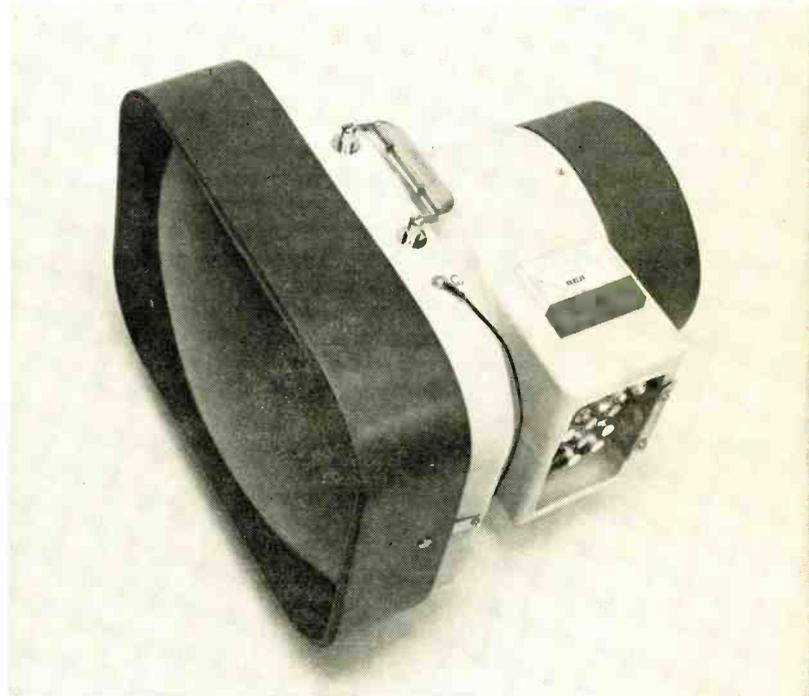


FIG. 5—RCA PORTABLE JIGS. One for tube, the other for solid-state sets.

manufacturers. The deflection components for the tube-type jigs (and sets) have quite a bit higher impedance than their transistor-type counterparts.

RCA does not recommend trying to use tube jigs on solid-state stuff. They have two versions; in the large-tube type, the 10J102 matches all tube type RCA sets back to the CTC-7, including the 21-inch round, and 19-, 20-, 23- and 25-inch rectangulars. The 10J104 is used for the transistor color sets. It has the same yoke and associated components as solid-state CTC-40 chassis.

Other jig-makers have different ideas. The statements and claims here are those given us by the companies, and most of them have been checked out.

the bench. A carrying handle is included, for case in moving this compact jig to any place needed. It can even be carried into the customer's home; this is mainly for the purpose of using the jig's picture tube as a sub, to convince the owner that his picture tube really is bad.

RCA does not recommend trying to "convert" tube-type jigs for use with solid-state deflection components. However, their engineers tell me that it is **not** necessary to buy two complete test-jigs! You can buy the tube-type jig, and a set of the "neck components" (deflection and convergence yokes, convergence board, etc) of the type used in the transistor sets. If needed, these can be installed on the picture tube already in the jig, in about 10-15 minutes.

dianapolis, Ind. 46227, makes three test jigs for tube-type sets. The basic version is the P-1 seen in Fig. 6. It comes completely assembled ready to go. All necessary cables are provided; high-voltage and pix-tube socket extensions, a 21-25-inch pix-tube socket adapter, and their patented *Adapto-Scope* yoke hookup lead (Fig. 4). This allows the connection of the P-1 jig to any standard color TV yoke. This is done by plugging the standard color-coded leads into the yoke-socket on the TV chassis; red for "horizontal hot"; blue for "horizontal return"; yellow, "vertical hot"; Yellow with tracer, "vertical return".

No convergence board is used. The static magnets are mounted on the tube-neck, including a blue lateral. For initial setup, the yoke is adjusted

for best red purity, and the blue lateral magnet set for best center convergence. A special "zero-focus-voltage" color picture tube, Sylvania type TT-15B90 is used. The focus electrode is grounded; a special ground lead is provided in the pix-tube extension cable for this purpose.

The model P-2 Pix-O-Scope jig uses the same cabinet and tube as the P-1, with a high-voltage voltmeter added. This meter can also be used to read direct current. A HV DISCONNECT switch, and jack for the meter leads, is on the meter panel, as seen in Fig. 7.

The model P-3 Pix-O-Scope jig has all of the features of the first two models, plus a built-in volt-ohmmeter, and a color-bar generator. This is shown in Fig. 8. The color-bar generator controls are accessible from the

company carries a complete line of adapter and conversion cables, so the Pix-O-Scope jig can be used with any set. No convergence board is used, as I said, but convergence-load adapters for any make are also listed. (In fact, the company engineers say that a common 50- $\mu$ F, 250-volt capacitor will do!) Another comment was about checking of focus voltage, in high-voltage focus chassis. This can be done by disconnecting the jig's high-voltage lead (allowing the high-voltage to drift) and using the test-jig high-voltage lead as a meter-lead, to read the focus voltage on the TV chassis.

For color sets, with solid-state deflection type the Pix-O-Scope company is making a special jig, exactly like the rest, but called PT-1, PT-2, etc. These will work with any transistor color set,

and the yoke-lead, pix-tube extension, high-voltage lead, etc. are included. The static magnets, including the blue lateral, are mounted on the tube. (Comment; a standard convergence yoke and control board could be added to this, if it should prove necessary, it seems to me)

Telematic has a complete cross-reference listing of adapter cables to match the Econo-Jig to any tube-type color set. Special convergence load adapters are also listed.

For transistor color sets, the company claims that these can be used on the Econo-Jig with their model TA-2000 Series *Transverters*. These are matching transformers, designed to plug into the tube-type yoke and convert it for servicing transistor sets. A special model of the Econo-Jig, the

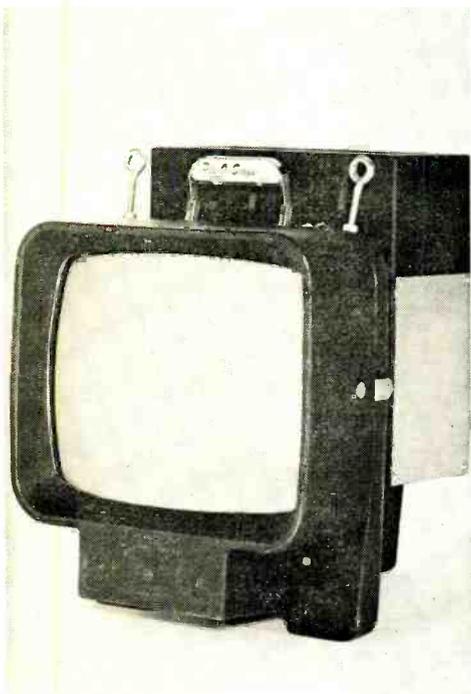


FIG. 6—PIX-O-SCOPE P-1 universal test jig.

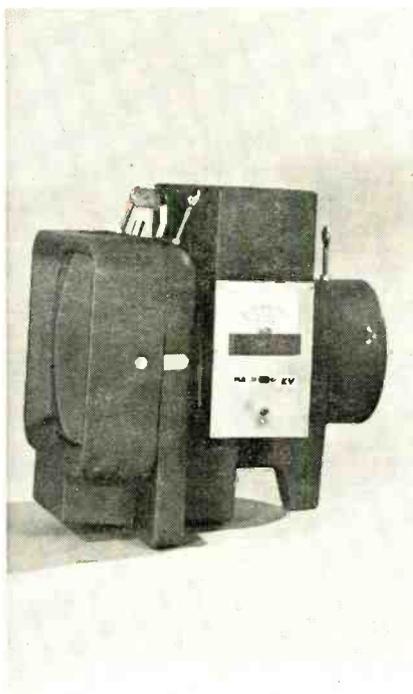


FIG. 7—THE P-2 JIG with built-in meter.



FIG. 8—THE P-3 JIG is the deluxe model.



FIG. 9—TELEMATIC ECONO-JIG is a kit.

front.

All of these jigs are housed in the same type of cabinet made of heavy impact-resistant plastic, with special legs molded on the bottom so that the jig will sit steady on the bench. A carrying handle is mounted on the top. Eyebolts are provided so that they can be hung from the ceiling over the bench, for added convenience. Even the Pix-O-Scope's shipping carton is a dual-duty thing. It is made of extra-heavy cardboard, and instructions are included for cutting this down and bolting it to the floor of the service truck, so that the jig can be carried safely, if you want to take it to the customer's home.

A comprehensive cross-reference listing of all major color set manufacturers is provided with each jig. The

such as RCA CTC-40, Motorola Quasars, etc.

#### Jig in kit form

Fig. 9 shows the components of the Econo-Jig EJ-190; only jig furnished in kit form (as far as I know!) It is made by the Telematic Div., U. X. L. Corp. 2245 Pitkin Ave., Brooklyn, N.Y. 11207 and is furnished without the picture tube. Any standard 19-inch color tube can be used. (Telematic suggests that the technician might have a used one on hand, or could pick up a rebuilt one at a reasonable price.)

The Econo-Jig EJ-190 is built into a metal case, fitted with a carrying handle and eyebolts, so that it can be moved, or hung from the ceiling as desired. A universal 90° yoke is used,

TA-390, built for use on transistor color TV chassis only, will be brought out very soon, probably by the time you read this.

#### Conclusion

So, that's about it. I certainly hope I didn't miss anybody! On the whole, from using one for quite a few years, I can vouch for the fact that a test-jig IS a worth-while unit to have.

The portable test-jig is a fairly new development. While its use as a portable, in the home, will probably not be as common as its bench use, it certainly could be a valuable aid to hard diagnoses, both in the home, and in the shop. One in particular that comes to my mind is using the jig's yoke as a substitute for a suspected defective yoke in the set! **R-E**



# SHOOTER'S GUIDE

frequency must be precise for correct color rendition. be working properly. Here's how to troubleshoot it fast.

is to touch up the 3.58-MHz transformer.

The clip lead is attached across the base and emitter of the burst amplifier.

This kills the burst input to the detector. The vtvm is attached to an end of the detector load resistors. About  $\pm 20$  volts should be read. If

it's not, the oscillator is not operating properly. Test it.

When the voltage is present, tune the 3.58-MHz transformer for maximum voltage. The oscillator is good.

Next step is to unhook the clip lead. Your vtvm should show a marked increase in voltage as the burst pulses enter the circuit. If there is no increase, the burst amplifier is defective. Test it. However, should there be an increase while you are there, tune the burst transformer for maximum voltage.


If there is a reactance circuit between the detector and the oscillator, the next step is to ground the reactance input from the detector. There is usually a test point provided for this part of the alignment as it is important and goes out of perfect alignment easily.

When the reactance input is shorted, the oscillator runs free. Watch the TV screen and you'll see the colors roll out of sync. Adjust the reactance output transformer until you attain "float by" of colors. If you can't get it, the oscillator can't run at 3.58 MHz. Test the frequency-controlling components of the oscillator, especially the crystal.

When "float by" is attained, the reactance and oscillator are good. Remove the clip lead. The colors should snap into place. If they do not, the reactance circuit is defective. Test it.

If you should remove the jumper from the output of the detector into the reactance or oscillator and the colors should start moving faster, then there is a malfunction in the detector itself. There is an imbalance and the wrong dc correction voltage is being developed.

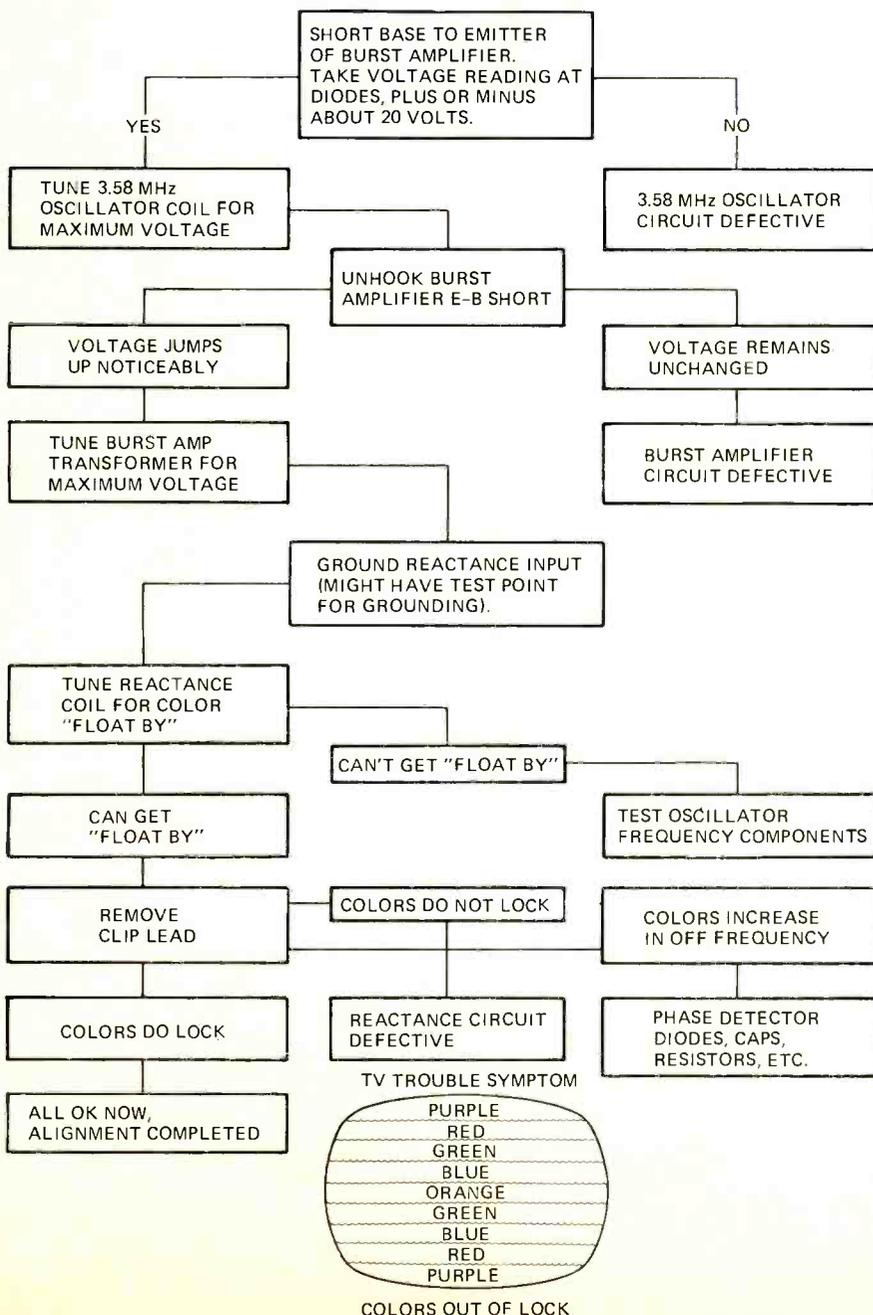Test the diodes first. Even a slight leakage in one could cause the wrong dc voltage to be produced. Make sure the twin load resistors are both the correct value and closely matched. Test the two 330-pF input capacitors and the CW input capacitor. If you don't find anything wrong here, the detector is defective. **R-E**




# BUILD A "ZERO DISTORTION" STEREO PREAMP

by GARY KAY

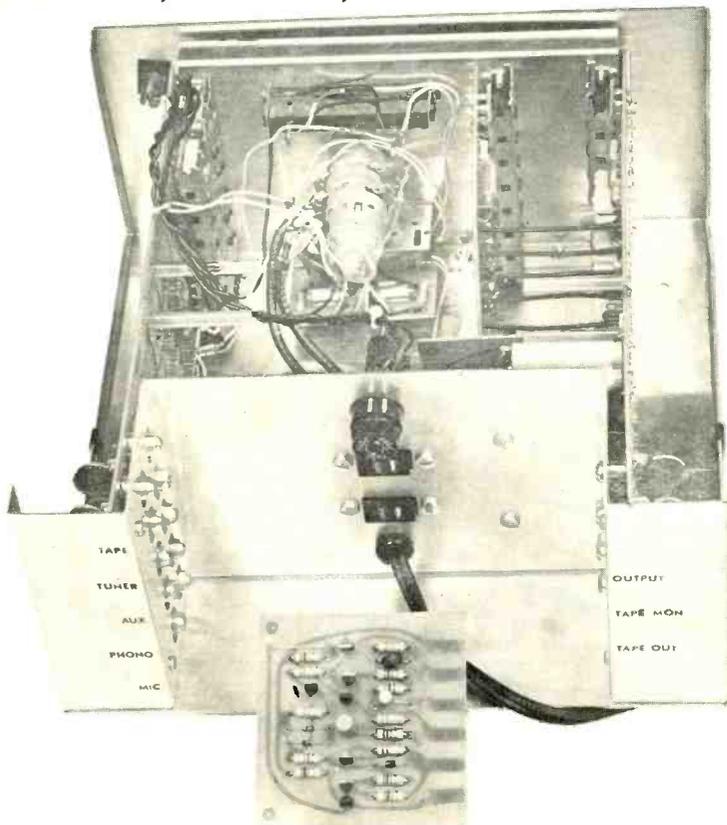*Part 2—The wrap-up of construction details on the novel laboratory-grade stereo preamplifier featured in last month's issue.*

The photographs and parts placement layouts wrap-up the story on the stereo preamplifier featured on last month's cover. Designed around discrete semiconductors instead of IC's, this lab-quality stereo preamplifier uses a modular concept based on plug-in PC boards for simplicity, ease of construction and troubleshooting; and push-button bass, treble and function controls for versatility and resetability.




THIS VIEW OF THE PREAMPLIFIER shows how the cable connectors (phono-type jacks) are recessed for protection against mechanical damage. The input connectors are on the left; output on the right.

The following parts for this preamp are available from Southwest Technical Products Corp., 219 W. Rhapsody, San Antonio Texas 78216. Complete set of 9 printed-circuits, drilled, with socket clips. No. 198-cb \$17.50  
Set of 9 circuit boards, socket clips, 3 pushbutton switches, and volume control (dual control with push-pull switch). No. 198-SW \$34.50  
Complete kit of all parts including cabinet and front panel. No. 198-k \$69.50
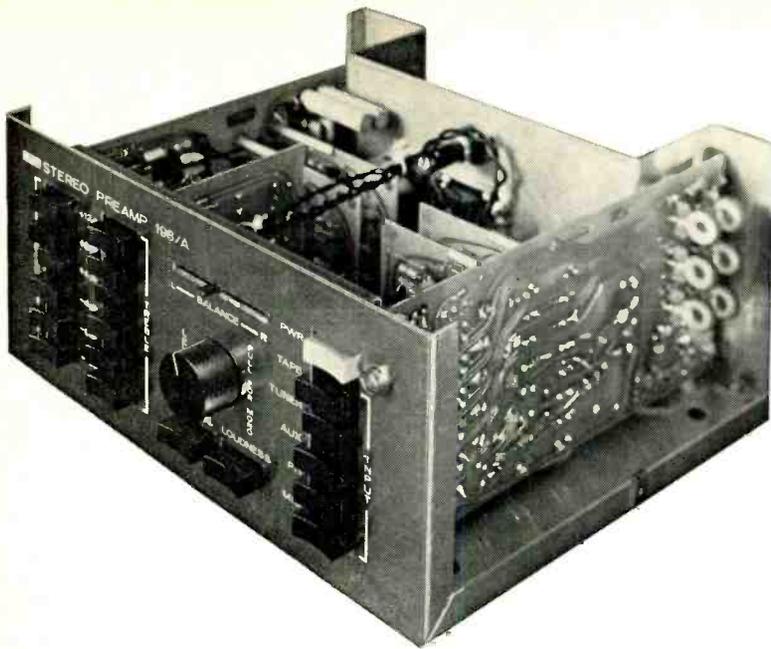
## PARTS LIST

R1 thru R6—1 megohm ¼-W 10%  
R7 thru R12—250,000-ohm trimmer  
R13, R14—22,000-ohm ½-W 5%  
R15, R16—51,000-ohm ½-W 5%  
R17, R18—2,200-ohm ½-W 5%  
R19, R20, R59, R60—100,000-ohm ½-W 5%  
R21, R22—750,000-ohm ½-W 5%  
R23, R24, R27, R28, R61, R62—10,000-ohm trimmer  
R25, R26—1,000-ohm ½-W 10%  
R29, R30—10,000-ohm audio taper pot with 5,000-ohm tap with pull switch  
R31, R32—470-ohm, ½-W 10%  
R33, R34—300,000-ohm ½-W 5%  
R35, R36—150,000-ohm ½-W 5%  
R37, R38—82,000-ohm ½-W 5%  
R39, R40—8,200-ohm ½-W 5%  
R41, R42—15,000-ohm ½-W 5%  
R43, R44—30,000-ohm ½-W 5%  
R45, R46—10,000-ohm ½-W 5%  
R47, R48—3,300-ohm ½-W 5%  
R49, R50—6,800-ohm ½-W 5%  
R51, R52—18,000-ohm ½-W 5%  
R53, R54—180,000-ohm ½-W 5%  
R55, R56—68,000-ohm ½-W 5%  
R57, R58—33,000-ohm ½-W 5%  
R63—10,000-ohm linear taper slide pot  
R64, R65—47-ohm ½-W 10%  
R66—68,000-ohm ½-W 10%  
R\*, R\*—47,000-ohm ¼-W 10%

C1, C2—.0068-μF polystyrene  
C3, C4—.0015-μF polystyrene  
C5, C6—4.7-pF disc  
C7, C8, C37, C38—20-pF disc  
C9, C10—.0047-μF polystyrene  
C11, C12—.0082-μF polystyrene  
C13, C14—0.012-μF metalized polycarbonate  
C15, C16—0.022-μF metalized polycarbonate  
C17, C18—0.22-μF metalized polycarbonate  
C19, C20—0.12-μF metalized polycarbonate  
C21, C22—0.082-μF metalized polycarbonate  
C23, C24—220-μF @ 6.3V electrolytic  
C25, C26—.0062-μF polystyrene  
C27, C28—.0039-μF polystyrene  
C29, C30—.0024-μF polystyrene  
C31, C32—240-pF polystyrene  
C33, C34—390-pF polystyrene  
C35, C36—620-pF polystyrene  
C39, C40—1-μF 15 volt electrolytic  
C41, C42—1000-μF 25 Vdc electrolytic  
C43, C44—500-μF 15 Vdc electrolytic  
C45, C46—0.1-μF  
D1 thru D4—1N5060 silicon diode or equal  
D5, D6—15-V 1-W Zener diode, Motorola 1N4744 or equal



- \*S3—5-station dpdt tandem plus 1 station push-to-lock pushbutton switch
- \*S1, S2—6-station dpdt pushbutton switch
- \*S4, S5—dpdt pushbutton switch
- S6—spst pull switch mounted on the rear of level control
- F1— $\frac{1}{4}$ -amp fuse
- T1—24-volt 80 mA ct transformer 117 Vac primary
- LM1—neon lamp NE-2

**Parts List No. 195 Preamp Module**

Q1, Q2, Q6, Q7—2N5210 Motorola

- Q3, Q4, Q5—2N5087 Motorola
- D1—4.7-V 400mw Zener diode Motorola MZ-70-4.7 or equal
- D2, D3—1N914 diode or equal
- C1—4.7- $\mu$ F tantalum electrolytic
- C2—5-pF disc
- C3—33- $\mu$ F @ 6-V electrolytic
- R1, R3, R9, R10, R11, R13—1000-ohm  $\frac{1}{2}$ -W 10%
- R2—47,000-ohm  $\frac{1}{2}$ -W 10%
- R4, R5—22,000-ohm  $\frac{1}{2}$ -W 10%
- R6—15,000-ohm  $\frac{1}{2}$ -W 10%
- R7—8200-ohm  $\frac{1}{2}$ -W 10%


- R8—10,000-ohm  $\frac{1}{2}$ -W 10%
- R12—4700-ohm  $\frac{1}{2}$ -W 10%

\*S1 through S5 are being custom-made for Southwest Technical and no substitutes are available.

The two 47,000-ohm resistors are used only on the two input modules and are connected across capacitor C3 (see Fig. 1) on the foil side of the board.

**R-E**

All boards shown one-half actual size.

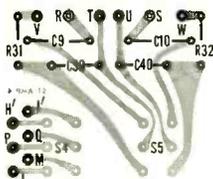

# One of our most successful students wrote this ad!

Harry Remmert decided he needed more electronics training to get ahead. He carefully "shopped around" for the best training he could find. His detailed report on why he chose CIE and how it worked out makes a better "ad" than anything we could tell you. Here's his story, as he wrote it to us in his own words.


## By Harry Remmert

**A**FTER SEVEN YEARS in my present position, I was made painfully aware of the fact that I had gotten just about all the on-the-job training available. When I asked my supervisor for an increase in pay, he said, "In what way are you a more valuable employee now than when you received your last raise?" Fortunately, I did receive the raise that time, but I realized that my pay was approaching the maximum for a person with my limited training.

"Education was the obvious answer, but I had enrolled in three different night school courses over the years and had not completed any of them. I'd be tired, or want to do something else on class night, and would miss so many classes that I'd fall behind, lose interest, and drop out.
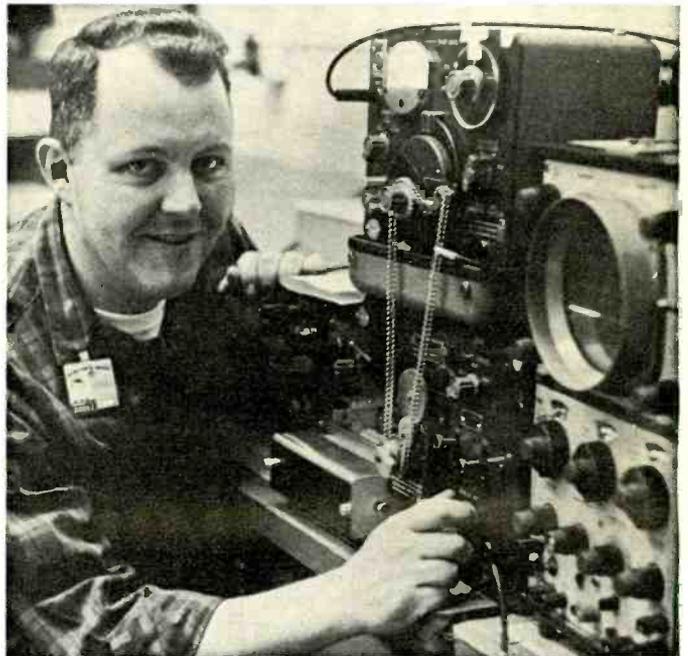
### The Advantages of Home Study

"Therefore, it was easy to decide that home study was the answer for someone like me, who doesn't want to be tied down. With home study there is no schedule. I am the boss and I set the pace. There is no cramming for exams because I decide when I am ready, and only then do I take the exam. I never miss a point in the lecture because it is right there in print for as many re-readings as I find



Harry Remmert gives his CIE Electronics course much of the credit for starting him on a rewarding career. He tells his own story on these pages.

necessary. If I feel tired, stay late at work, or just feel lazy, I can skip school for a night or two and never fall behind. The total absence of all pressure helps me to learn more than I'd be able to grasp if I were just cramming it in to meet an exam deadline schedule. For me, these points give home study courses an overwhelming advantage over scheduled classroom instruction.

"Having decided on home study, why did I choose CIE? I had catalogs from six different schools offering home study courses. The CIE catalog arrived in less than one week (four days before I received any of the other catalogs). This indicated (correctly) that from CIE I could expect fast service on grades, questions, etc. I eliminated those schools which were slow in sending catalogs.

### FCC License Warranty Important

"The First Class FCC Warranty\* was also an attractive point. I had seen "Q" and "A" manuals for the FCC exams, and the material had always seemed just a little beyond my grasp. Score another point for CIE.

\*CIE backs its courses with this famous Money-Back Warranty: when you complete a CIE license preparation course, you'll be able to pass your FCC exam or be entitled to a full refund of all tuition paid. Warranty is valid during completion time allowed for your course.

"Another thing is that CIE offered a complete package: FCC License and technical school diploma. Completion time was reasonably short, and I could attain something definite without dragging it out over an interminable number of years. Here I eliminated those schools which gave college credits instead of graduation diplomas. I work in the R and D department of a large company and it's been my observation that technical school graduates generally hold better positions than men with a few college credits. A college degree is one thing, but I'm 32 years old, and 10 or 15 years of part-time college just isn't for me. No, I wanted to *graduate* in a year or two, not just *start*.

"When a school offers both resident and correspondence training, it's my feeling that the correspondence men are sort of on the outside of things. I wanted to be a full-fledged student instead of just a tag-a-long, so CIE's exclusive home-study program naturally attracted me.

"Then, too, it's the men who know their theory who are moving ahead where I work. They can read schematics and understand circuit operation. I want to be a good theory man.

"From the foregoing, you can see I did not select CIE in any haphazard fashion. I knew what I was looking for, and only CIE had all the things I wanted.

### Two Pay Raises in Less Than a Year

"Only eleven months after I enrolled with CIE, I passed the FCC exams for First Class Radiotelephone License with Radar Endorsement. I had a pay increase even before I got my license and *another* only ten months later.

"These are the tangible results. But just as important are the things I've learned. I am smarter now than I had ever thought I would be. It feels good to know that I know what I know now. Schematics that used to confuse me completely are now easy for me to read and interpret. Yes, it is nice to be smarter, and that's probably the most satisfying result of my CIE experience.

### Praise for Student Service

"In closing, I'd like to get in a compliment for my Correspondent Counselor who has faithfully seen to it that my supervisor knows I'm studying. I think the monthly reports to my supervisor and generally flattering commentary have been in large part responsible for my pay increases. My Counselor has given me much more student service than "the contract calls for," and I certainly owe him a sincere debt of gratitude.

"And finally, there is Mr. Tom Duffy, my instructor. I don't believe I've ever had the individual attention in any classroom that I've received from Mr. Duffy. He is clear, authoritative, and spared no time or effort to answer my every question. In Mr. Duffy, I've received everything I could have expected from a full-time private tutor.

"I'm very, very satisfied with the whole CIE experience. Every penny I spent for my course was returned many

times over, both in increased wages and in personal satisfaction."

Perhaps you too, like Harry Remmert, have realized that to get ahead in Electronics today, you need to know much more than the "screwdriver mechanics." They're limited to "thinking with their hands" . . . learning by taking things apart and putting them back together . . . soldering connections, testing circuits, and replacing components. Understandably, their pay is limited—and their future, too.

But for men like Harry Remmert, who have gotten the training they need in the fundamentals of Electronics, there are no such limitations. He was recently promoted, with a good increase in income, to the salaried position of Senior Engineering Assistant working in the design of systems to silence submarines. For trained technicians, the future is bright. Thousands of men will be needed in virtually every field of Electronics from two-way mobile radio to computer testing and troubleshooting.

### Send for Complete Information — FREE

Many men who are advancing their Electronics career started by reading our illustrated school catalog, "Succeed in Electronics." It tells of the many electronics careers open to men with the proper training. And it tells which courses of study best prepare you for the work you want.

If you're "shopping around" for the training you need to move up in Electronics, this interesting book may have the answers you want. We'll send it to you FREE. With it, we'll also include our other helpful book, "How To Get A Commercial FCC License."

To get both FREE books, just fill out and mail the reply card. For your convenience, we will try to have a representative call. If card is missing, use coupon below.

#### APPROVED UNDER G.I. BILL

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

### Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Please send me your two FREE books:

1. Your school catalog, "Succeed in Electronics."
2. Your book on "How To Get A Commercial FCC License."

I am especially interested in:

- |   |  |
|---|--|
| <input type="checkbox"/> Electronics Technology                 | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering                  | <input type="checkbox"/> Industrial Electronics    |
| <input type="checkbox"/> First Class FCC License                | <input type="checkbox"/> Electronics Engineering   |
| <input type="checkbox"/> Electronics Technology with Laboratory |  |

Name \_\_\_\_\_ (Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

Veterans & Servicemen: Check here for G. I. Bill information

RE-12

### For men with prior electronics training . . . Electronics Engineering Course

. . . Covers steady-state and transient network theory, solid-state physics and circuitry, pulse techniques, computer logic and mathematics through calculus. A college-level course for men already working in Electronics.

Circle 14 on reader service card

# R-E's Service Clinic

## De-modulate the new modular TV receivers

*Modular TV and the technician—the technician wins!*

by JACK DARR  
SERVICE EDITOR

NORMALLY THIS COLUMN IS PRETTY noncontroversial and I like it that way. We are all concerned with various ways of doing the same things. However, once in a while I have to express some opinions—purely personal opinions, of course, but based on quite a lot of experience in doing the things that the opinions are about!

What started all this was a couple of clippings the Editor handed me. They contained some pretty gloomy predictions for the future of electronics servicing.

Being a grouchy old man who has been actively engaged in this business for too close to 50 years, I get a distinct sense of *deja vu*\* every time I hear these things. For one thing, I've *been* hearing them at intervals of about 5 years ever since I started!

**Argument:** “\_\_\_\_\_sets will require more highly skilled technicians because they'll break down less often but be harder to fix.” The words in the blank this time were “solid-state”, but I've heard the same things with color TV; black-and white TV; and, if you go back far enough Ac-powered *radios!* (ca 1927!)

**Rebuttal:** One: it *will* take more skill on the part of the technician. But the American electronics technician, so far, has taken everything they've thrown at him in his stride! TV, color TV, transistors, integrated circuits—you name it, put it in a set and we'll fix it. Between the manufacturers who give us data, the test equipment people who give us instruments to check 'em with, and the native bull-headedness of the U.S. Service Technician who will not admit that there is anything he can't fix, we make out, and I firmly believe we always will. From experience, solid-state sets run about the same MTBF (mean time between failures) as the others. (From actual tests, including time-and-motion testing of many sets, I *will* say that the overcrowded solid-state PC-board sets run something like 1.6 times the *service-time* per set, compared to terminal-  
(\*That's French for “You've been here before, Bub!”)

strip construction. The PC-board type, with parts on one side and wiring on the other, **is more difficult to repair**, due to the extra time needed to locate and identify the parts to be tested. The actual (mechanical) job of replacing a part is slower, due to the difficulty of getting parts into crowded chassis, working leads through tiny holes, etc.

So we do have a problem there. But, as usual, we develop the special skills, and the tool-makers give us the special tools we need. Most of us have reduced that average 1.6 time differential to the minimum by now. For technicians reading this, I might say that you're not going to fix these sets with a pair of gas-pliers and a 150-watt soldering iron! The special tools are absolutely necessary, and you might as well get with it. It's the only way.

**Argument:** Modular TV's will require much less skill to service than the conventional type. Quote: “—they can go down to the corner drug store, buy a module the size of a pack of cigarettes, plug it in, and drive us out of business!” Ho, hum. Remember the Drug-Store Tube-Testers, fellers? They said the same thing about them. I do not know of any competent technician who was driven out of business by these things.

**Concession:** the actual “plug-in” operation *could* be done by the proverbial 10-year old boy (If he didn't manage to break the module in two trying.) But it will require a skilled *technician* to tell him *which* module to replace.


**Rebuttal No. 2:** Quote: “You'd have to carry a tremendous stock of modules to service all makes of set.” **RIGHT!** This is correct. The stock of modules would be impractical for anyone, with the possible exception of a Government project of some kind.

To finish off the argument about the drug-store, pack-of-cigarette modules once and for all, let me say just *one word*—**STANDARDIZATION**. That did it. For this to have any effect

*(continued on page 70)*

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

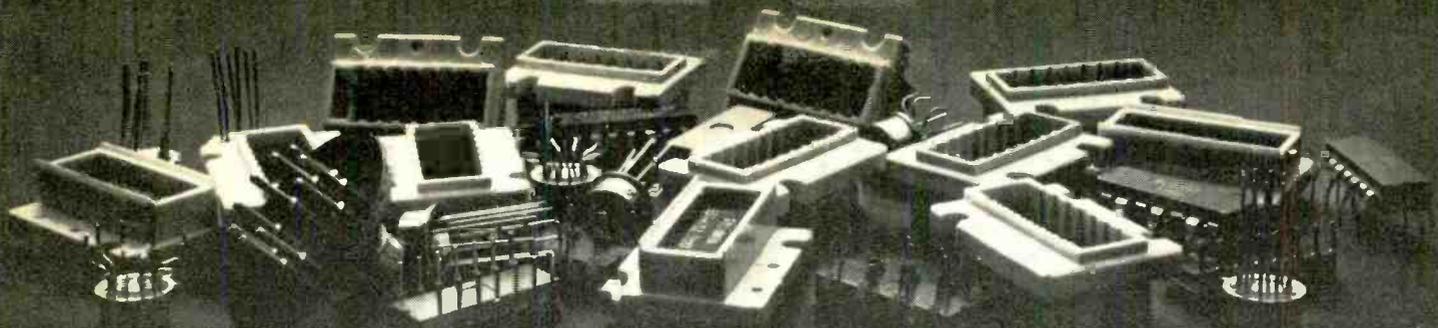If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, New York 10003.



## Our 28 ICs replace...

To Be Replaced	ECG Replacement	To Be Replaced	ECG Replacement
CA3077	712	1M3078A	724
CA3078	712	1M3078B	724
CA3079	712	1M3078C	724
CA3079A	712	1M3078D	724
CA3079B	712	MC13031	725
CA3079C	712	MC1303P	725
CA3079D	712	MC1304P	718
CA3079E	712	MC1304PQ	720
CA3079F	712	MC1305P	720
CA3079G	712	MC1305PQ	720
DM-26	721	MC1327P	722
DM-30	721	MC1327PQ	722
EX4553	722	MC1314G	704
FF274	715	MC1328G	707
FL274	712	MC1328P	713
GE-IC2	712	MC1328PQ	713
GE-IC3	705A	MC1357P	708
GE-IC4	714	MC1358P	712
GE-IC5	713	MFC6010	703A
GE-IC6	715	N5111	708

## and hundreds more.

Integrated circuits are still pretty new in TV and stereo equipment.

But Sylvania's ECG Semiconductor program really has those applications pinned down.

Today, just 28 of our ICs will replace over 300 type numbers.

We don't do it by magic, or by offering an "almost as good" replacement.

We do it by assigning our own part number to just one high quality IC that can be used to replace dozens of others.

And to make it easy for you,

we've put together a replacement guide that tells you which of our ICs to use where.

Your customer won't know that you're not carrying 300 different ICs.

All he'll know is that you fixed his set fast, and fixed it right.

The fact that you only needed 28 IC replacements is your secret.

And ours.

In servicing, that can be the secret of success.

Sylvania Electronic Components, Waltham, Mass 02154.

**GTE SYLVANIA**

**SERVICE CLINIC**

*(continued from page 68)*

at all, every manufacturer of electronic equipment would have to agree to freeze designs, and use identical modules for given functions.

If you think this is going to happen in the foreseeable future, just pick up two of the reference books that are in every shop. One a Receiving Tube Manual, and two, a Transistor Cross-Reference Guide. I don't know how many tubes there are, now, but the last figure I had on transistors was something like 36,000 "different"

types. (It is demonstrably true that about 40 general-purpose replacement transistors will work in place of practically all of these). So if they are going to standardize, I have only one question: "When are they going to start?" Note that I didn't even mention standardization of IC's; you can't even find a cross-reference listing on the things. Only factory part numbers. Standardization? It is to laugh!


As a matter of fact, in one of the better-known brands of modular TV, even the maker's own modules are not standardized yet. One function comes in 5 different versions, three of which are not interchangeable. Another unit

in the same chassis has been modified 26 times.

We are moving toward a "Service-Oriented Economy." With the growing number of complex devices in daily use, there is no other way we can go. So, the *skilled technician* is going to become more and more important. Without his skill in diagnosing and repairing failures, the economy would come to a screeching halt. To me, this type of work is just as difficult, and just as important, as design.

Don't tell me that the "module-plugger" is going to replace the "Tube-Puller." You know where he went. (By the way, so far there are no Drug-Store Module Testers—at least not yet.) Once more may I be a bit redundant; If we are to have all of this standardization, *when are they going to start?* R-E
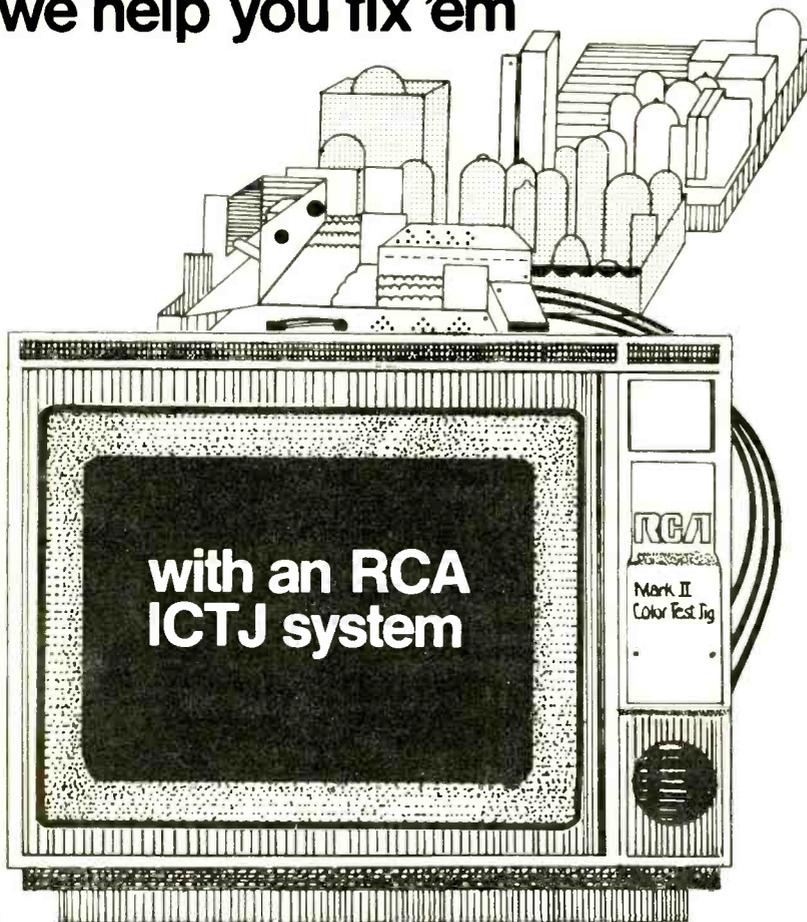
## As fast as you get 'em we help you fix 'em



Sound like the TV serviceman's dream? It is. RCA's Industry Compatible Test Jig is a complete testing system that lets you service more than 90% of *all* color TV console chassis on the market—and updates you as new ones come along.

Here's how: The RCA ICTJ system includes the test jig itself (in bench or portable models), plus a handy cross-reference manual that specifies the right adaptors for each set. Choose from more than 100 adaptors and cables available (optional extra) to meet your needs. But most important, as the new models need service, you'll be kept up to date with new inserts for the manual and any necessary new adaptors will be made available. So whatever's coming, you'll be ready.

See your RCA Parts and Accessories distributor today for full information.

Parts and Accessories, Deptford, New Jersey 08096



Circle 15 on reader service card

## reader questions

### 3A3C INTERNAL HOOKUP

An alert reader found that RCA 3A3C tubes will not work properly in Sylvania DO-5 color chassis. The RCA tube uses pins 1, 3, 5 and 8 as internal (continued on page 72)

**FREE** catalog  
over  
**1000**  
unique tools,  
handy kits,  
precision  
instruments,  
technical  
supplies.

Our 20<sup>th</sup> year of service to the World's finest craftsmen and technicians.

**National Camera**  
2000 West Union Ave. Dept. G88  
Englewood, Colorado, 80110

Send a **FREE** copy of the nc Flasher

name \_\_\_\_\_

address \_\_\_\_\_

city \_\_\_\_\_

state \_\_\_\_\_ zip \_\_\_\_\_

**National Camera**  
2000 West Union Ave. Dept. G88  
Englewood, Colorado, 80110

Circle 16 on reader service card

## AUTOMATIC COLOR CIRCUITS

(continued from page 52)

chroma bandpass amplifier, the reference oscillator, the acc circuit and the color killer. On IC602 are the chroma demodulators, the color summing matrix and the three output difference amplifiers. Fig. 11 shows the dc tint control and the Tint Lock system used on this chassis. The tint control is a dc type and works similarly to the varactor Admiral circuit we looked at

earlier. The reference oscillator output of IC601 first feeds the tint control circuit. The output of phase shift amplifier Q602 is shifted by  $52^\circ$  by C656 and L646 feeding one input to the demodulator chip. A  $-52^\circ$  phase shift is produced by L642 and C657 to drive the other demodulator input. The total demodulation angle is  $52 - (-52) = 104^\circ$ . Diodes Y631, Y632, Y633 and Y634 are operated by the Tint Lock switch to change the angles. In the first switch position Y631 and Y633 are turned on paral-

leling L643 and L646 increasing the positive shift. C657 and C658 are also paralleled increasing the negative shift. In the second Tint Lock position L644 and C659 come into play with the demodulation angle reaching the maximum 160 degrees.

**Motorola**—Here the name is Instamatic controlling a pilot light, AFT, preset contrast, preset color intensity, preset hue, preset brightness and a background and demodulation phase angle shift circuit. Motorola's modular TS-934 chassis uses two IC's with

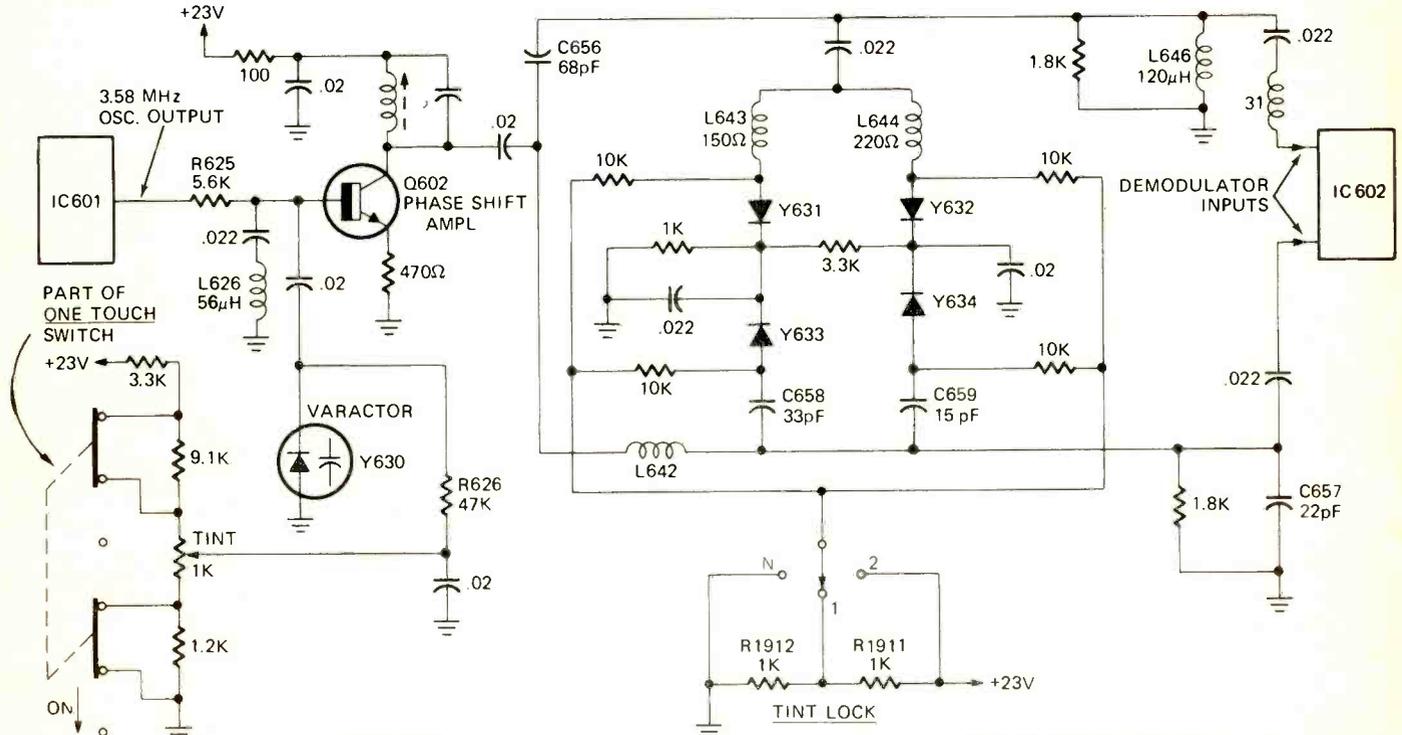


FIG. 11—THE ONE-TOUCH CONTROL is General Electric's latest user control for satisfactory color at flick of a switch.

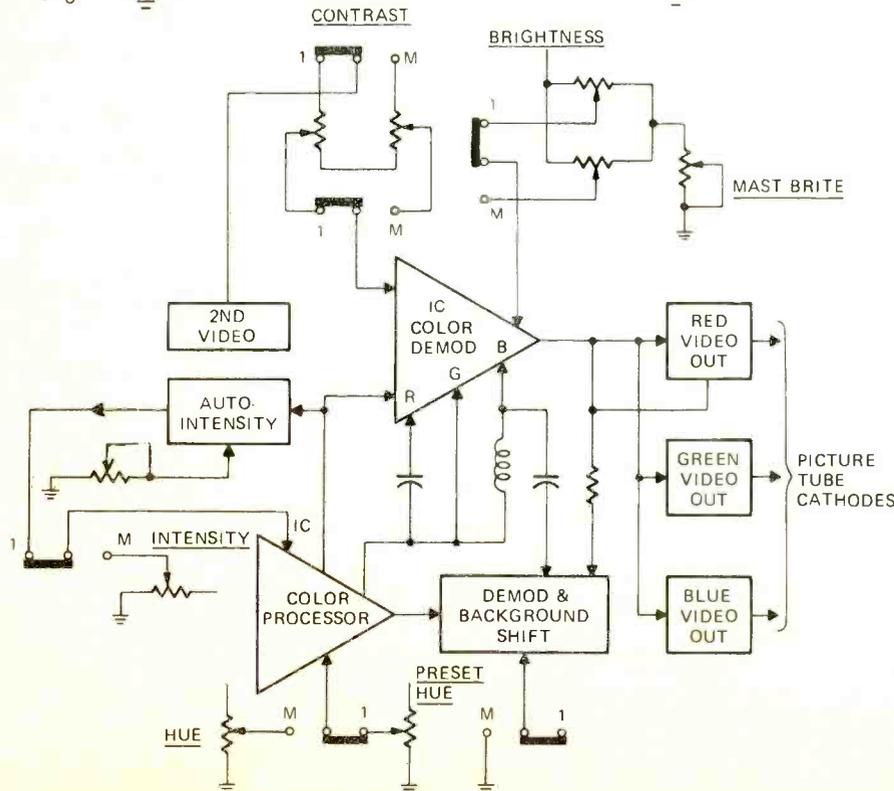


FIG. 12 (left)—INSTAMATIC COLOR in Motorola TS-934 chassis. The circuit uses two IC's and approximately eight transistors.

about eight additional transistors not counting the video color outputs. Fig. 12 is a block diagram of the system. Fig. 13 is the automatic color intensity circuit used in this chassis. In the manual mode the color control directly adjusts color gain. In this mode there is no acc automatic color control action. When switched to Instamatic the acc is connected. This circuit looks at the color signal from the color processor IC amplifier, rectifies it and uses the developed voltage to control the gain of the color amplifier. The preset color intensity control adjusts the color level to which the acc circuit will regulate. In Fig. 14, the tint correction circuit, Q6 is an AND gate which enables the circuit when both the Instamatic switch is on and a color signal is sensed. When both con-

(continued on page 98)

# ELECTRONIC TECHNICIANS!

Raise your professional standing  
and prepare for promotion! Win  
your diploma in

## ENGINEERING MATHEMATICS

from the Indiana Home  
Study Institute

We are proud to announce two great  
new courses in Engineering Mathematics  
for the electronic industry.

These unusual courses are the result of  
many years of study and thought by the  
President of Indiana Home Study, who  
has personally lectured in the classroom  
to thousands of men, from all walks of  
life, on mathematics, and electrical and  
electronic engineering.

You will have to see the lessons to ap-  
preciate them!

NOW you can master engineering  
mathematics and actually enjoy doing it!

**WE ARE THIS SURE:** you sign no  
contracts—you order your lessons on a  
money-back guarantee.

In plain language, if you aren't satis-  
fied you don't pay, and there are no  
strings attached.

Write today for more information and  
your outline of courses.

You have nothing to lose, and every-  
thing to gain!

### The INDIANA HOME STUDY INSTITUTE

Dept. RE-1, P.O. Box 1189, Panama City, Fla. 32401

Circle 18 on reader service card

## READER QUESTIONS

(continued from page 70)

connections, to support the cathode  
structure. The original Sylvania 3A3C  
tube does not use these pins.

When used in the DO-5 chassis,  
the RCA 3A3C's lasted only about 90  
days. The internal connections shunted  
the heater dropping resistor, resulting  
in excessive heater voltage. (Inciden-  
tally, all of the 3A3A tubes shown in  
my manuals do use internal connec-  
tions on these pins. Possible cure:  
move the 4.7-ohm dropping resistor to  
unused pins; 6, for example)

Thanks to Donald H. Pomeroy,  
Milestone Laboratories, Manchester,  
N.H. for this one.

## NO HIGH VOLTAGE

*I've got a weird condition in an  
Admiral 1H2 portable. The fuse blew; I  
replaced it. Now, there's no high volt-  
age, and the screen grid resistor of the  
33GY7 gets very hot; smokes. I tried a  
new 33GY7, and got a raster for a mo-  
ment, then it went out and the resistor  
smoked again.—D.Q., Omaha, Neb.*

Take a very close look at the  
plate connection of the 33GY7 socket  
on the circuit board; the plate connec-  
tion of the pentode output section,  
that is. I believe you'll find that this

will be pretty dark-looking, and prob-  
ably have a very bad solder-joint. Re-  
melt it and add fresh solder.

Your output tube plate con-  
nection is probably opening. So you  
have no plate, and all of the current  
flows to the screen grid. There is only  
a 1-watt 560-ohm resistor here, and  
this promptly gets very hot. Double-  
check: read screen voltage at turn-on;  
if it jumps to normal, then drops to  
zero, this is it.

## INTERMITTENT BRIGHTNESS

*I thought this one would be simple  
but it wasn't. In an RCA CTC-15, the  
raster would go out. Move the 12BY7  
video output tube, and it came back. I  
replaced the tube; got about a week and  
the same thing. So, I replaced the tube  
socket, and I've still got the same prob-  
lem! The 12BY7 goes dim and out goes  
the raster. N.P.S., Greencastle Pa.*

It is simple (he said hopefully!)  
I've had the same thing in my own  
ancient RCA. Try this: run a jumper  
wire, solid No. 20 at least, from the  
ground terminal of the 12BY7 heater  
to the nearest ground. Now, for luck,  
run another from the hot 6.3 volt  
socket terminal to the nearest lance on  
the board; toward the front of the  
video board, brown wire.

I think this will cure it. There is a  
(continued on page 78)

# INTERNATIONAL Frequency meter FM-2400CH

- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

The **FM-2400CH** provides an  
accurate frequency standard for  
testing and adjustment of mobile  
transmitters and receivers at pre-  
determined frequencies.

The FM-2400CH with its extended range  
covers 25 to 1000 MHz. The frequencies  
can be those of the radio frequency channels  
of operation and/or the intermediate fre-  
quencies of the receiver between 5 MHz and  
40 MHz.

Frequency Stability:  $\pm .0005\%$  from  $+50^\circ$   
to  $+104^\circ\text{F}$ .

Frequency stability with built-in thermometer  
and temperature corrected charts:  $\pm .00025\%$   
from  $+25^\circ$  to  $+125^\circ$  (.000125% special 450  
MHz crystals available).

Self-contained in small portable case. Complete  
solid state circuitry. Rechargeable batteries.

**WRITE FOR CATALOG!**



FM-2400CH (meter only).....	\$595.00
RF crystals (with temper- ature correction).....	24.00 ea.
RF crystals (less temper- ature correction).....	18.00 ea.
IF crystals.....	catalog price




CRYSTAL MFG. CO., INC.  
10 NO. LEE • OKLA. CITY, OKLA. 73102


Circle 19 on reader service card
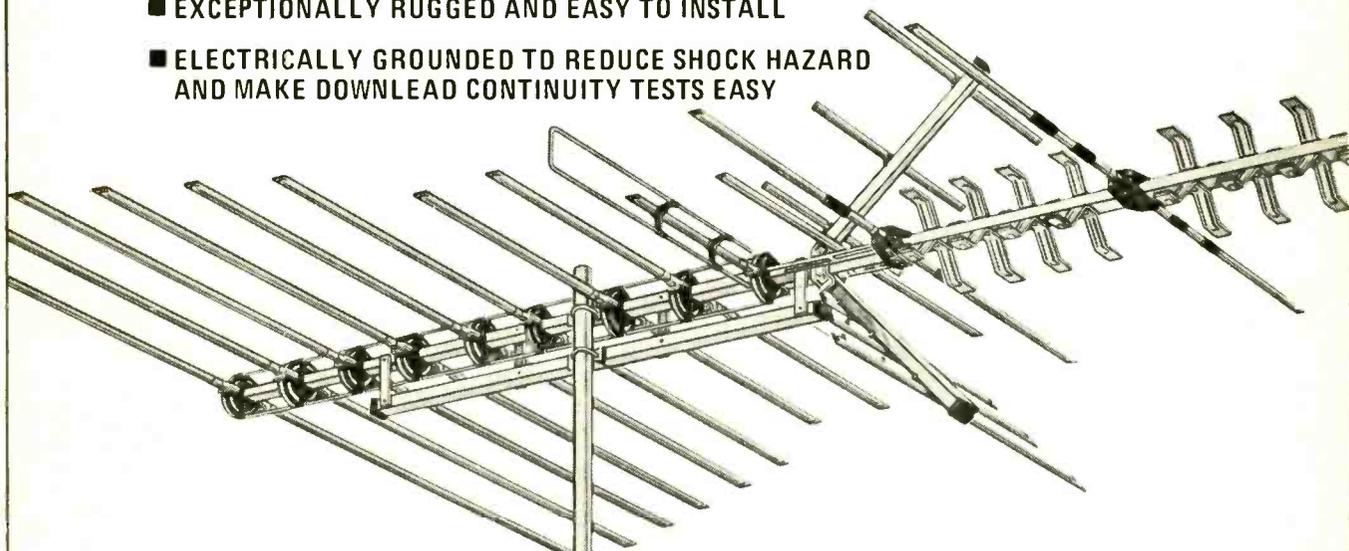
# Our tests show The Jerrold Super VU-Finder Is The Best In The Industry!

- MORE GAIN AND FLATTER RESPONSE FOR UNSURPASSED COLOR RECEPTION
- EXCEPTIONALLY RUGGED AND EASY TO INSTALL
- ELECTRICALLY GROUNDED TO REDUCE SHOCK HAZARD AND MAKE DOWNLEAD CONTINUITY TESTS EASY



## WE WANT YOUR PROFESSIONAL OPINION.

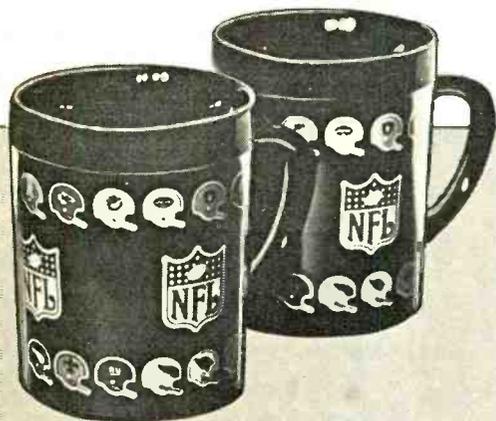

**FREE! A PAIR OF  
HANDSOME NFL COFFEE MUGS**

Just fill out the coupon and mail it to us with the instruction sheet from a Jerrold VU-931S, VU-932S, VU-933S, VU-934S, VU-935S, VU-936S or VU-937 antenna. We will send you two NFL coffee mugs FREE!

**FOR EVALUATING THE NEW  
JERROLD SUPER VU-FINDER.**



**JERROLD ELECTRONICS CORPORATION**  
P.O. Box A, 401 Walnut St., Phila., Pa. 19105/(215) 925-9870

Please send me a free pair of NFL coffee mugs. Enclosed is an instruction sheet from the following Super VU-Finder antenna. (model) \_\_\_\_\_



- 1 Before trying the Super VU-Finder, I was using the following antenna:  
(make) \_\_\_\_\_ (model) \_\_\_\_\_
- 2 In my opinion the Super VU-Finder is:  BETTER  WORSE  
because: \_\_\_\_\_
- 3 Comments: \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

NAME \_\_\_\_\_  
COMPANY NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

COUPON MUST BE POSTMARKED BEFORE JAN. 31, 1973  
LIMIT ONE SET TO A CUSTOMER

Circle 20 on reader service card

# Great careers

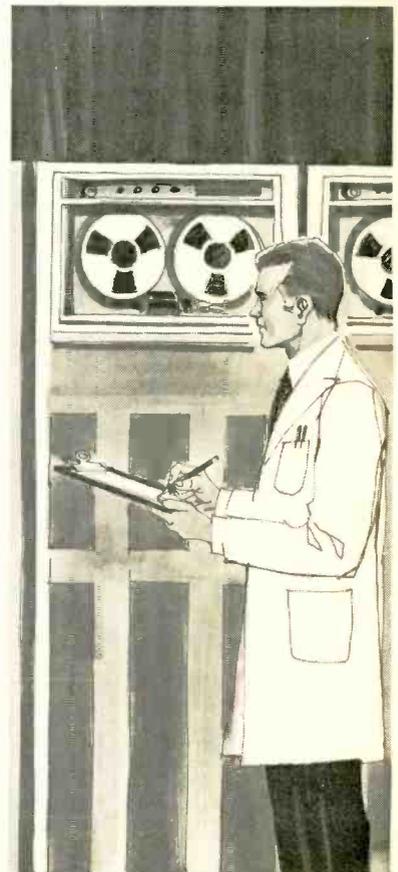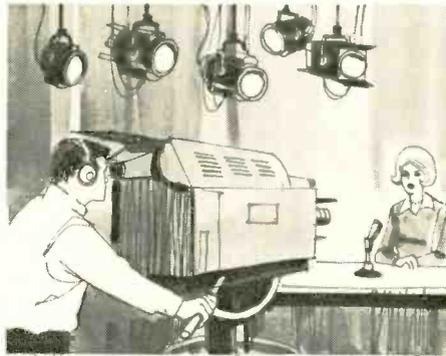

## Join the high-paid electronics technicians who got their start through NTS Home Training.

Your home can become your own private classroom-workshop. NTS sends you everything you need to learn valuable technical skills in electronics. You get easy-to-grasp lessons, comprehensive kit manuals, large fold-out charts, and more. Plus the finest professional equipment available today. It's all included in your tuition, yours to keep.

You'll work with commercially-designed equipment, and school training material. Cash in on the tremendous opportunities in the expanding, exciting world of electronics.


If your field is television, you might decide to join a first-class TV repair center. Or start a shop of your own. Or specialize in industrial applications of television. Once you master an area of electronics, the direction you take is really up to you. And you'll be able to use the test instruments you built yourself.

It all begins at home, with NTS Project Method Training. Check card or coupon today for free full-color NTS Catalog and complete details. No obligation. No salesman will call.
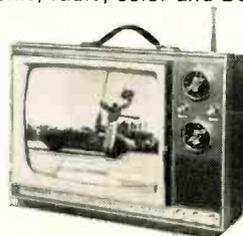
### NTS COLOR AND B&W TV SERVICING


Build the largest most advanced color TV made! It's a Heath! Over-all solid-state design, 315 sq. in. ultra-rectangular screen, 24 channel detent UHF/VHF power tuning, matrix picture tube, built-in self-servicing features, "Instant On," A.F.T., solid-state VHF tuner, and much more! This is a commercial set, the kind you'll encounter in the field — and not for training purposes only. Also build and keep AM-SW Radio, Solid-State Radio, FET Volt-Ohmmeter, and Electronic Tube Tester. Learn trouble-shooting, stereo multiplex systems, radio, color and B&W TV servicing.

**Solid-state B&W TV**  
74 sq. in. picture (cabinet included)



Learn advanced solid-state circuitry as you build this B&W TV receiver. Course covers the full range of home entertainment electronics.

### NTS AUDIO ELECTRONICS SERVICING

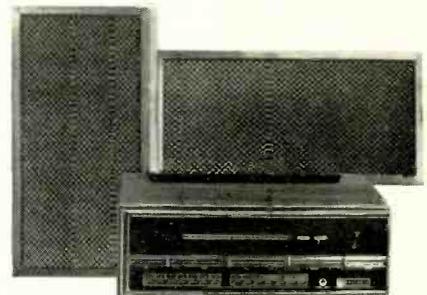


#### Solid-state Heath Stereo Receiver and Speakers

Learn sound theory — how it works in home radio, 4-channel, and more! Set up a spectacular music system. Learn about sound distortion, amplification and control, loud-speaker baffles, problems of system installation, etc. Included is Volt-Ohmmeter, In-Circuit Transistor Tester and solid-state Radio. Prepare yourself for great opportunities in the Home Entertainment Industry!
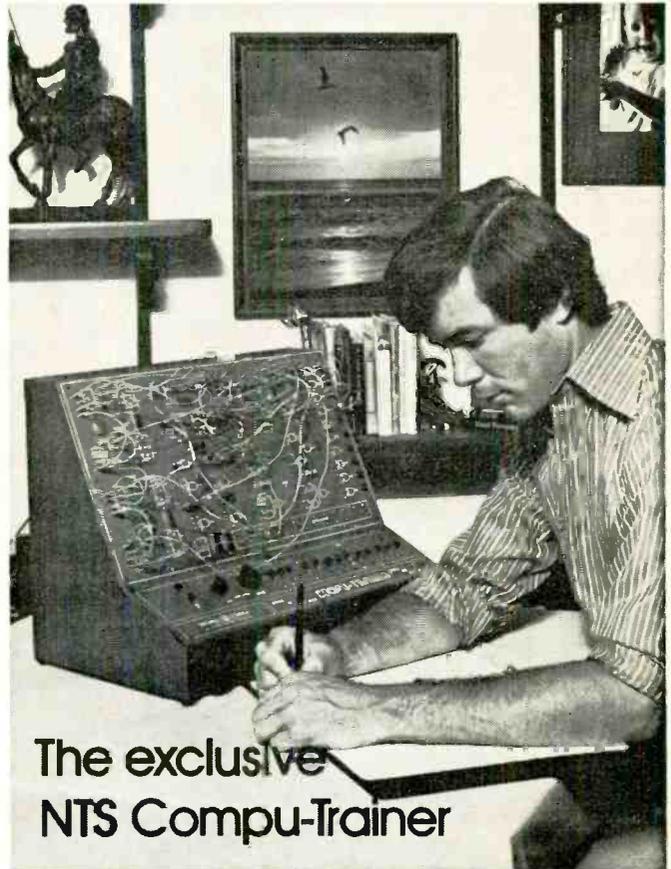
# begin at home.



**New solid-state  
315 sq. in. color TV**



**The exclusive  
NTS Compu-Trainer**

## NTS COMPUTER ELECTRONICS

Build and operate the exclusive NTS Compu-Trainer! Loaded with integrated circuits, it teaches you the how, what, and why of computers — faster, more thoroughly. You perform all wiring and patch-cording. No shortcuts! No pre-wired circuit boards. Also receive an FET Volt-Ohmmeter and a 5" wide-band Solid State Oscilloscope.

## NTS ELECTRONIC COMMUNICATIONS

Gain the prestige and earning power of owning an FCC First Class Radio Telephone License! Two exciting courses in the fields of transmitting and receiving. Experiment with an amateur phone 6-meter VHF transceiver, NTS exclusive 6-transistor solid-state radio and a fully transistorized volt-ohmmeter.

**5-watt AM transmitter/receiver.**



## NTS AUTOMATION/ INDUSTRIAL ELECTRONICS

Systems automation is the future of the industry — and you can play an important role! Enter the age of electronic controls by training on the NTS Electro-Lab — a complete workshop. Also receive a Solid State 5" wide-band professionally rated Oscilloscope. Build five industrial controls to regulate motor speed, temperatures, pressure, liquid level and much more.

**5" Solid State Oscilloscope**



## CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training at Los Angeles in sunny Southern California. NTS occupies a city block with over a million dollars in facilities devoted exclusively to technical training. Check box in coupon.


## APPROVED FOR VETERANS

Accredited Member: National Association of Trade and Technical Schools; National Home Study Council.

## NATIONAL TECHNICAL SCHOOLS

Resident & Home Study Schools  
World-Wide Training Since 1905  
4000 S. Figueroa St., Los Angeles, CA 90037

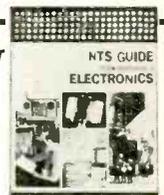**Please rush Free Color Catalog and Sample Lesson, plus information on course checked below. No obligation. No salesman will call.**



### National Technical Schools

Resident & Home Study Schools  
World-Wide Training Since 1905  
4000 S. Figueroa St., Los Angeles, CA 90037

- Master Course in Color TV Servicing
- Color TV Servicing (For Advanced Technicians)
- Master Course in B&W TV & Radio Servicing
- Master Course in Electronic Communications
- Practical Radio Servicing
- FCC License Course
- Master Course in Electronics Technology
- Automation & Industrial Electronics
- Computer Electronics Dept.-206-013
- Basic Electronics
- Audio Electronics Servicing

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- Check if interested in Veteran Training under new G.I. bill.
- Check if interested ONLY in Classroom Training at Los Angeles.

## READER QUESTIONS

(continued from page 72)

hairline crack *somewhere* in the heater circuit, and this is the fastest way to get it.

### FLYBACK REPLACEMENT

If you have to replace the flyback in a Zenith 19DC20 hybrid chassis, you can save a great deal of time. The new flyback will come with the wires already soldered on it. *Don't* use them! Unsolder the original wires at the flyback terminal board. Take the old one out, put the new one in, and

then remove the wires one at a time, and resolder the original wires. They'll be of the same colors.

If you do it in this way, you won't even have to pull the chassis. Otherwise, you'll have to pull the chassis, and spend quite a little time threading some of those wires underneath and getting at some tight places.

### HOT OUTPUT TRANSISTORS

*I've replaced the output transistors in a Zenith stereo, 20AT30Z. Now the new ones get hot and the tone is lousy. Driver transistor is OK. I changed it for the one in the other channel. New transistors match.—B.D., Billings, Mont.*

You have bias trouble, I'd say. Check the bias diode, marked CR451 on the board. If it is *open*, you'll lose the proper bias, the output stage will be unbalanced, and get hot. If this is it, you can replace it with a plain silicon diode, such as RCA SK-3030. Your midpoint voltage (at the speaker connection, before going through the capacitor) will settle down somewhere around 14.5 volts. It must be roughly half of the supply voltage, which is about 28 volts.


### VIDEO DETECTOR BLOWS

*I've got a Truetone MIC3919C portable, which has blown three video detector diodes in about two months. I can't find any trouble in the set; no shorts in the last i.f. transformer, etc.—R.Q., Ariz.*

Try replacing the original glass diode with a 1N64. This is how we cured the same trouble a long time ago in an old GE model with the same symptoms. Or use an RCA SK-3091 that has a 40-volt peak rating. Some of the imported diodes seem to have this problem. They short, without apparent reason. So use a higher-rated diode.

This one is in the last i.f. transformer can. The old ceramic 1N64 will be "push-fit" in here, but it can be done. R-E

## LEARN THE BURGLAR ALARM BUSINESS!!!

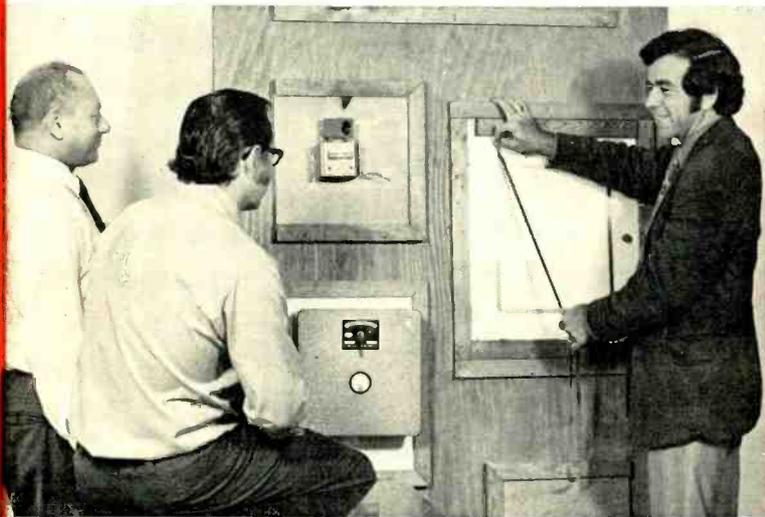

Burglar alarm installation is one of the most rapidly growing industries today. The tremendous publicity associated with security systems has created a widespread demand for installation of alarm systems.

A formal program has not been previously available to an individual seeking training in this profitable field. Now Ademco, the world's leading manufacturer of burglar alarm equipment offers you an opportunity to learn alarm installation techniques even if you have little or no experience in the alarm field. In just two short days you can be ready to install your first alarm!

Seminars are held throughout the year at Ademco's plant in Syosset, New York and at various locations throughout the country. All sessions are limited in attendance, so reservations should be made well in advance.

**FOR FURTHER INFORMATION CONTACT:  
ALARM DEVICE MANUFACTURING CO.**

A DIVISION OF PITTSWAY CORPORATION



**165 Eileen Way, Syosset, N.Y. 11791  
Area Code 516-921-6700**

## A LITTLE SQUIRT stops all the noise.

A squirt of Quietrole from the handy Spray Pack silences any moving T.V. part. Cleans as it lubricates, too. Guarantees quiet, trouble-free operation. Absolutely safe for any black and white or color set. Try it and see why it's preferred by top servicemen everywhere.

Also available in bottles, and the new silicone—"Silitron."



Product of  
**QUIETROLE**  
COMPANY

Spartanburg, South Carolina

Circle 22 on reader service card

# RCA's TV Sweep Chanalyst checks every VHF channel.

And this complete system has other features you need to restore new-set performance.



- Concerned about CATV, CCTV, MATV? WR-514A checks all VHF channels for tuner malfunction
- Precision attenuator permits peak fringe area reception adjustment
- Versatile snap-on probe allows fast, accurate alignment technique
- One-year warranty on parts and labor... local replacement parts availability

Unit combines the functions of a sweep/marker generator, marker adder. RF, IF, video and special Chromo-Align sweep signals permit checking of VHF tuners and alignment of IF, video and color bandpass amplifiers. That's why we call the RCA WR-514A a complete system.


Yours for only \$380\* including RF output cable, three direct cables, connector adapter, VF/IF 75-ohm input head, and two direct termination units. Ask your distributor if he offers easy payment terms.

Together with the bonus accessories offered below, you will have just what you need for TV alignment procedures.

To get the special bonus offer, simply mail the WR-514A warranty card to RCA Test Equipment Headquarters, Harrison, N.J. 07029. Offer subject to withdrawal without notice. See your RCA Distributor for a demonstration of the RCA TV Sweep Chanalyst. Application Notes and other technical data are also available — on request.

\*Optional Distributor Resale Price

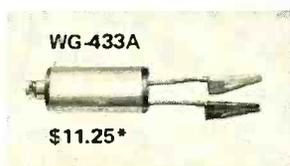**Special bonus offer—3 accessories worth \$42.25\* free with purchase of an RCA WR-514A**




**WG-433A**  
\$11.25\*

MIXER-INPUT ADAPTER



**WG-434A**  
\$15.00\*

VIDEO/CHROMA BANDPASS DETECTOR

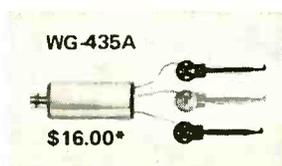

**WG-435A**  
\$16.00\*

LINK/IF DETECTOR

# RCA

**Electronic Components**

Circle 23 on reader service card



# HEAR MUFFS

Telex headphones and headsets give you that comfortable feeling of assurance when you monitor broadcasts or communications. Signals come through loud and clear — intelligibly and reliably.

Telex professional monaural or stereo headphones incorporate audiometric-type transducers that are impervious to temperature or humidity changes and provide you with absolute performance consistency day in, day out. These sensitive dynamic transducers produce high output levels with minimum consumption of transmission power. Available in single or dual muff configuration and with noise cancelling dynamic or carbon boom microphones.

You'll never miss a cue or program buss with a Telex Announcers Earset®. Inconspicuous for 'on camera' work, it has practically become standard in the industry. And the Sportscaster headset, with a dynamic, broadcast quality, boom microphone assures precise voice transmission for live, remote broadcasts.

Or you can select a Teleset®, Twinset® or Earset® for lightweight, comfortable and inexpensive private monitoring. And for special applications in business or home, industry or institution, Telex makes a listening device to fit your requirements. Available at better sound dealers or write for free information.

PRODUCTS OF SOUND RESEARCH

**TELEX®**

COMMUNICATIONS DIVISION  
9600 ALDRICH AVENUE SOUTH  
MINNEAPOLIS, MINNESOTA 55420



CANADA: DOUBLE DIAMOND ELECTRONICS, LTD., Ontario  
EUROPE: ROYAL SOUND COMPANY, INC., 409 North Main Street, Freeport, N.Y. 11520 U.S.A.  
INTERNATIONAL: TELEX EXPORT DEPT., 9600 Aldrich Ave. So., Minneapolis, Minn. 55420 U.S.A.

Circle 24 on reader service card

## new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

**CAPACITOR AND BALL-DRIVE CATALOG SHEET** illustrates the Jackson Brothers line of air-dielectric variable tuning and trimmer capacitors and reduction drives available for use with them.—M. Swedgal, 258 Broadway, New York, N.Y. 10007.

Circle 31 on reader service card

**1973 ANNUAL CATALOG No. 730**, features 2-channel and 4-channel stereo high-fidelity components, Citizens-band 2-way radio equipment. Lists amplifiers, decoders, decoder/amplifiers, receivers, tuners, modular hi-fi systems, the latest in record changers, speaker systems, tape recorders. Includes cameras and photographic accessories, electronic test equipment, auto supplies, books, microscopes, telescopes. Over 18,000 new major brand electronic parts.—Lafayette Radio Electronics Corp., 111 Jericho Turnpike, Syoset, L.I., N.Y. 11791.

Circle 32 on reader service card

**COLOR TV ELECTROLYTIC REPLACEMENT GUIDE, M-945** lists Sprague Types TVL and PCL aluminum electrolytics intended for color TV servicing and 54 leading color TV manufacturers along with the catalog numbers of the TVL/PCL units which fit their respective chassis. All capacitors are identified by catalog number, capacitance, dc working voltage, dimensions and the number of color TV set makes in which it is used.—Sprague Products Co., Marshall St., N. Adams, Mass. 01247.

Circle 33 on reader service card

**ELECTRONICS CATALOG**, 180 pages featuring home entertainment products, audio equipment, Citizens-band 2-way radios, test equipment, antennas and hobby kits. Also lists thousands of hard-to-find or specialized electronic items for hobbyists, experimenters, technicians or anyone wanting a wide selection of parts, accessories and maintenance items. New products being introduced for 1973 include stereo and four-channel amplifiers, receivers, adapters and tape decks; speaker systems, CB radios, stereo radios, scanning monitor receivers and a miniature electronic calculator.—Radio Shack, Dept. R-26, 2617 W. Seventh St., Fort Worth, Tex. 76107.

Circle 34 on reader service card

**ELECTRONIC PARTS CATALOG**, for hobbyists, experimenters and do-it-yourselfers of both beginner and sophisticated level. 16-page catalog, low-price, high-quality components. In addition, a number of electronic kits are described. These include burglar alarms, lamp flashers, rectifier tester and more.—Cortland Electronics, Inc., 16 Hudson St., New York, N.Y. 10013.

R-E

Circle 35 on reader service card

# Up-to-the-minute service information\* from Sams

\*Selected portions of manufacturers' servicing data bound in convenient book format

## Transistor Radio Servicing Data

Designed for the service technician, Sams Transistor Radio volumes are published monthly. Each volume in the series contains schematics, parts lists, pictorial presentations, troubleshooting data, plus other information on up to 17 of the latest transistor radio receivers and other youth products. Includes data you need to service virtually any receiver mass-marketed in the U.S.A. The Photofact® Annual Index lists the equipment covered in each volume.

\$3.25 each.

## Modular Hi-Fi/Stereo Servicing Data

What the transistor radio series does for transistors, this series does for hi-fi and stereo components and compacts. Issued monthly, each volume includes schematics, pictorial presentations, pertinent servicing data and parts lists for up to 13 of the latest modular components — tuners, receivers, amplifiers, etc. Covers virtually all equipment mass-marketed in the U.S.A.

\$3.95 each.

## Scanner-Monitor Servicing Data

Contains comprehensive servicing data for 30 of the most popular UHF and VHF receivers now in use, including B&K, Browning, Johnson, Midland, Pace, Pearce-Simpson, Penneys, Realistic, Sonar, and Teaberry. As the first guide ever released for scanners and monitors, it is an invaluable aid for service technicians. Its last-minute information includes schematics, voltages, alignment, parts lists, crystal formula data, pictorial presentations, and general troubleshooting information.

No. 06557

\$4.95



## Special Discount Offer

All of the above are available from your Sams Distributor. Ask him how you can save 30¢ a volume on Transistor Radio Series and Modular Hi-Fi/Stereo Series by contracting for each volume as it is issued.



**HOWARD W. SAMS & CO., INC.**

4300 West 62nd St. • Indianapolis, Ind. 46268

Circle 25 on reader service card

# new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

**SSB/AM MOBILE CB TRANSCEIVER, Sidebander II**, is 40% smaller, 20% lighter and 23% lower in price than its earlier version. The new 32-channel




transceiver features a full 15 watts PEP power input to the transmitter final amplifier stage, a four-function back-lighted meter, rf gain control, signal clarifier, public address facility and a plug-in mi-

crophone. An accessory 117-volt ac power supply is available.—**Linear Systems, Inc.** 220 Airport Blvd., Watsonville, Calif. 95076.

Circle 36 on reader service card

**MINIATURE SOUND STUDIO, model 9100**, 6-head, 4-track tape deck has digital IC's in the deck's transport system to insure computer-type, feather-touch operation. Professional capabilities include bi-directional recording with automatic reverse and repeat playback; built-in head demagnetizer; photo-electronic shutoff; precision molybdenum heads; three motors; tape-counter memory; three oscillators; tape select switch which increases current by 30% for low-noise, high output tapes; line microphone mixing; echo, S.O.S. and S.W.S. capability with level controls. Signal-to-

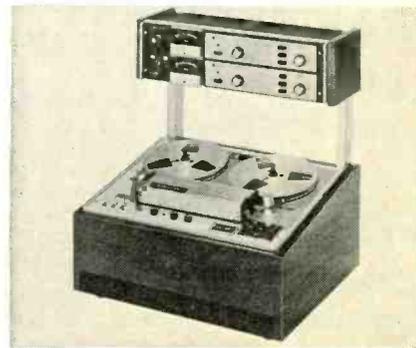noise ratio better than 50 dB; wow and flutter less than 0.06%; frequency response 45 Hz to 21kHz  $\pm$  3db at 7½ ips.



Two-year parts warranty. \$699.95.—**Dokorder, Inc.**, Dept. P, 11264 Playa Court, Culver City, Calif. 90230.

Circle 37 on reader service card

**FM MULTIPLEX STEREO GENERATOR, model LSG-231**, has a pilot signal frequency of 19-kHz with  $\pm$  2 Hz accuracy.

## Judge for Yourself!

Compare specifications... in the receiver... in the transmitter of our FM-2101 series



FCC Type Accepted Parts 15, 21, 89, 91, 93

25 WATT ALL SOLID STATE VHF-FM BUSINESS RADIO

Sonar's latest receiver design uses a Dual-Gate Field Effect Transistor, a Dual Monolithic Crystal Filter and a "best grade" Ceramic Filter. **Result? . . . better sensitivity, more intermodulation rejection and the smoothest sounding radio in its class** ■ You choose from Noise Activated Squelch, Continuous Tone Squelch or Sequential Two-Tone Squelch ■ Listen to clear "Voice-Fidelity" audio ■ The transmitter sounds better because of the Sonar engineered microphone and speech circuitry ■ Choose the powerful 25 watt or the economical 10 watt model ■ A 110VAC operated regulated power supply is available for base station use ■ Our prices includes mobile mount hardware, detachable microphone, and 1 pair of precision cut crystals ■ These 4 flexible units allow you to custom design a mobile or base model to fit your specific needs. Why don't you visit your local dealer or write.

10 WATTS 1 channel \$350.00  
OUTPUT 4 channels 395.00

25 WATTS 1 channel \$450.00  
OUTPUT 4 channels 495.00

**SONAR RADIO CORPORATION** 73 WORTMAN AVE., BROOKLYN, N.Y. 11207

Sonar has a complete line of VHF-FM-2 way radios —Base, mobile or hand held portable operation for new systems or adding on existing systems.



PROFESSIONAL  
DEPENDABILITY  
PERFORMANCE

You always will  
get thru!

ready for action  
in the toughest  
situations

VHF-FM  
TRANSCEIVER  
PORTABLE  
(132-174 MHz)

A compact, lightweight, versatile transceiver. Ideal as a companion piece to the FM-2100. It is better designed and better built by Sonar for durability and long life use.

- Provides immediate voice contact with base stations, mobile units and other portable transceivers
- Compact with ALL 2-way systems
- Fast charge snap-in battery pack operated on independent frequencies
- Receiver and transmitter can be used with 1 pair crystals less batteries

\$375.00

# Leader outduals them all!

## LBO-505 DUAL CHANNEL/ DUAL TRACE SOLID STATE OSCILLOSCOPE

**MODEL LBO-505 \$559.95**

Price Includes:  
2 LPB-8X Direct Lo/Cap Probes  
2 Terminal Adapters — BPX  
1 Set of Test Leads



**The more you see... the more you believe.**

Accuracy! Performance! Exclusive, Leader-developed features! That's what makes the LBO-505 the Number One Dual Channel/Dual Trace Scope. You get triggered and automatic sweep. AC or DC coupling per channel. 15MHz bandwidth. Maximum horizontal speed of 0.1 microseconds/cm (10X magnification). 10MVp-p/cm vertical sensitivity. Separate or simultaneous display in sweep mode of channels 1 and 2, alternating, chopped, added algebraically and vector (X-Y). The triggered sweep range extends from 1 $\mu$ s/cm to 0.5s/cm, calibrated in 17 steps. Scale illumination is continuous with front panel control.

How can you use the LBO-505 most efficiently? You'll find more ways than you can think of ... at first. It makes troubleshooting a breeze! Compare 2 signals simultaneously — input and output, for color, monochrome, audio and much more. Check gain, loss, distortion, phase shift, frequency ... you name it. Do your own thing. The LBO-505 belongs on every bench and in every lab. Feature-for-feature, price-for-price, job-for-job ... it outduals them all!

*Send for new catalog. See your distributor.*

# Leader

**INSTRUMENTS CORP.**

37-27 Twenty-Seventh Street  
Long Island City, New York 11101  
(212) 729-7410


Circle 62 on reader service card

JANUARY 1973 • RADIO-ELECTRONICS

83

# Pix-Mate™ the crt tester you can afford to take along

only ... \$34.95

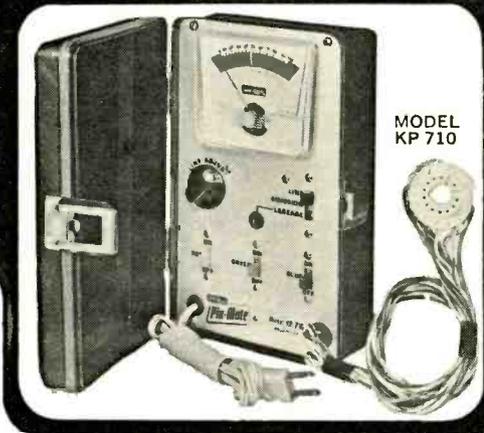

- A quality CRT tester with individual test for each gun.
- Compare guns for emission.
  - Test for leakage and shorts.
  - Legible 3 color scale.
  - Compact, portable, rugged.
  - Avoid recalls, check the CRT on every call.

WRITE US!

## TeleMatic

### take along the time savers

- PIX-MATE • CRYX-MATE • GEN-MATE
- SOUND-MATE • TRACE-MATE

### The Caddy-Mate Line.

2245 PITKIN AVE., BROOKLYN, N. Y. 11207

Circle 63 on reader service card

## Why pay an answering service when you can own your own?



Dictaphone has a machine to make sure you never lose another cent through a missed phone call or a garbled message. In fact, we have a whole line of them.

They're called Ansafones. You can buy one outright or possibly lease it for about what you're paying your answering service now. And it works for you 24 hours a day, 7 days a week.

For a free brochure describing how much an Ansafone can help you, mail this coupon now.

### ▶ Dictaphone

Box L-1-34, 120 Old Post Road, Rye, New York 10580

Please send me full details of the Ansafone line.

Name \_\_\_\_\_

Company \_\_\_\_\_ Phone \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

Ansafone and Dictaphone are registered trademarks of Dictaphone Corp.

Circle 64 on reader service card

The 1-kHz audio signal is accurate to  $\pm 1\%$ . Signal separation is rated at 50 dB with output voltage at 0 to 3 Vrms continuously variable. Useful in the field or on the bench. Easy to operate, compact



and complete with tilt stand; has a dual power supply and measures 8"W x 12"D x 3½"H. Weighs 5.5 lbs. \$229.95.—**Leader Instruments Corp.**, 37-27 Twenty-Seventh St., Long Island City, N.Y. 11101.

Circle 38 on reader service card


**STYLUS CLEANING KIT, No. R40052**, contains a unique brush designed to assist in removing dirt and foreign matter without harming the delicate stylus point and a special cleaning-fluid formulation



in a convenience container. The product is designed to increase the life of both stylus and records. \$2.50.—**Robins Industries Corp.**, 75 Austin Blvd., Commack, L.I., N.Y. 11725.

Circle 39 on reader service card

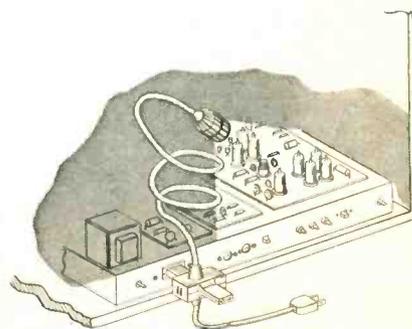**CHEATER CORD AND TROUBLE LAMP**, feeds power to the TV, stereo or any unit being tested through a standard or polarized interlock without the need for cheater cords. A flexible, high voltage, insulated goose-neck supports a pow-




erful and compact spot light that can be positioned to illuminate any part of the set. The interlock also affords a convenient auxiliary outlet for any ac feeding or extension and can be used whether plugged into chassis or not. Constructed

of thoroughly insulated and heat resistant materials. \$9.95.—**Michelin International**, P. O. Box 6743, Los Angeles, Calif. 90022.

Circle 40 on reader service card

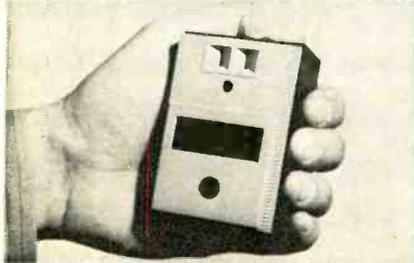**BROWN-OUT PROTECTOR**, model EP-110. Plug device into wall outlet and appliance into the monitor. When line voltage drops below 100 volts, it automatically disconnects equipment from the line. When power returns to normal, the



device reconnects the equipment. A built-in time delay prevents short duration line drops from disconnecting and restarting equipment. \$19.95.—**Logitek, Inc.**, 42 Central Dr., Farmingdale, N.Y. 11735.

Circle 41 on reader service card

**ELECTRONIC IGNITION SYSTEM**, Tiger 500 capacitive-discharge solid-state ignition system comes with a dual ignition switch and fits into a 4" x 4" x 3" box. Provides instant starting under all weather conditions, eliminates tune-ups,

extends the life of spark plugs and points, improves gasoline mileage, accel-



eration and performance. Can be added to any 12 V negative-ground gener-

ator/alternator system without any rewiring. \$49.95.—**Tri-Star Corp.**, Dept. NR, P. O. Box 1946, Grand Junction, Colo. 81501.

Circle 42 on reader service card

**INSTRUMENT REPAIR KIT**, model JTK-90, more than 60 precision tools with emphasis on watchmakers' tools and electronic assembly tools in the smaller sizes. Kit includes various type screwdrivers; 5-piece spline blade set; precision 10-piece knife set; hand vise; wire stripper-cutter; adjustable wrench; soldering tools; watchmakers' anvil; hand blower; 20-piece miniature drill set; miniature high-intensity lamp and much more. Packaged in a deluxe attache case, hardwood construction, black Mar-

# CHANNELLOCK

Gives You More In Hand Tools Including

THE  
HANDIEST  
PLIERS  
OF THEM  
ALL

Ask any good mechanic. He'll tell you his CHANNELLOCK tongue and groovers are the handiest pliers he owns. Try one . . . you'll agree. A word of caution: be SURE you're getting the original, genuine CHANNELLOCK. It's the only tongue and groove plier with machined, smooth working, undercut channels that never jump out. Look for the CHANNELLOCK trade mark on the handle. GET ALL THE FACTS. Send for our catalog . . . yours for the asking.



TOOLS BY  
**CHAN NEL LOCK**

MEADVILLE, PA. 16335

A NEW BREED OF MAN!

**MARTIN  
CAIDIN'S  
CYBORG**

IN THE EXPLOSIVE  
TRADITION OF  
THE ANDROMEDA STRAIN  
AND  
THE TERMINAL MAN

NOW IN PAPERBACK FROM  
WARNER PAPERBACK LIBRARY

\$1.25



\$1.25

Circle 65 on reader service card

Circle 66 on reader service card

# START THE NEW YEAR WITH A GREAT BARGAIN!

GET THESE TWO TV TECH AID BOOKS AT REDUCED PRICES:

1971 B&W BOOK — NOW \$4.95  
1970-BOOK FORM — NOW \$4.95

TV TECH AID BOOKS ARE FILLED WITH THE LATEST QUICK-SERVICING INFO ON COLOR TV, B&W TV, AND STEREO

TV Tech Aid Takes you right to the source of the trouble without guess work and wasted time. In each monthly issue you receive over 40 actual causes and cures of color and B&W TV trouble symptoms. You also receive timely and complete information about circuit modifications and other valuable service data.

USE THE COUPON BELOW TO PLACE YOUR 1973 SUBSCRIPTION (12 ISSUES \$7.95) OR VALUABLE BACK ISSUES

SEND YOUR CHECK OR MONEY ORDER TO:

TV TECH AID

P. O. Box 603  
Kings Park  
N.Y. 11754

- 1969 12 Issues \$4.95    1970-Book Form \$4.95  
 1971 B&W Book \$4.95    1971 12 Issues \$5.95  
 1972 12 Issues \$7.95    1973 All New 12 Issues \$7.95

Name.....  
Address.....  
City.....  
State.....Zip.....

Circle 67 on reader service card

Now...the most enjoyable do-it-yourself project of your life—A Schober Electronic Organ!



You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models with kit prices from \$500 to around \$2,000, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded adult to learn to play, yet completely satisfying for the accomplished professional. And there are accessories you can add any time after your organ is finished—lifelike big auditorium reverberation, automatic rhythm, presets, chimes, and more.

Join the thousands of Schober Organ builder-owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!


The Schober Organ Corp., Dept. RE-110  
43 West 61st Street, New York, N. Y. 10023

Please send me Schober Organ Catalog.  
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME.....  
ADDRESS.....  
CITY.....STATE.....ZIP.....

Circle 68 on reader service card

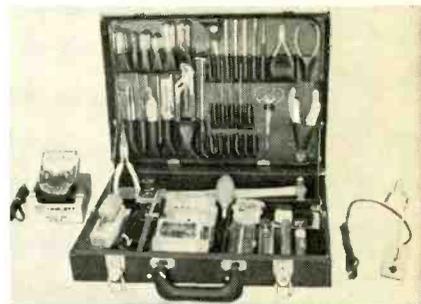velon covering and brass hardware. Room for spare parts and special tools and a pocket for documents and instruction manuals. With Triplett #310 vom



\$225. Without tester \$175.—Jensen Tools & Alloys, 4117 N. 44th St., Phoenix, Ariz. 85018.

Circle 43 on reader service card

ULTRASONIC MOTION DETECTOR, has a range of 25 to 30 feet. Has powerful signal and high quality filtering system to



eliminate problems caused by outside interference. Operates from 12Vac. In event of power failure, built-in recharge-



12 REASONS YOUR CAR NEEDS A TIGER 500

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration & performance - Spark plugs and points last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - Unconditional guarantee for original owner - Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back.

Assembled ..... \$49.95  
Post Paid in U.S.A.

Send check or money order with order to:


**Tri-Star Corporation**

Dept. R, P. O. Box 1946  
Grand Junction, Colorado 81501  
DEALER INQUIRIES INVITED  
Circle 69 on reader service card

able batteries provide 12 hours of standby operation. All wire terminals and the sensitivity adjustment switch are guarded by a protective cover.—**Alarm Device Mfg. Co.**, 165 Eileen Way, Syosset, L.I., New York 11791.

Circle 44 on reader service card

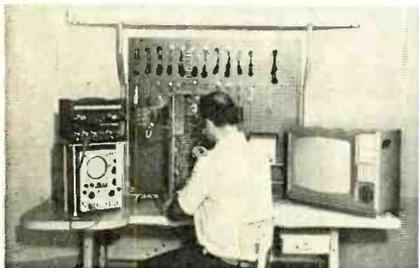**REPAIR SERVICING BENCH**, includes a green peg-board that stores test cables, work tools and meters for easy reach and reference. Optional items include locked drawer for reference material, storage area shelf, swivel posture chair, solder iron holster, locking 360° turntable. Nearly shadowless low-wattage lighting is built in. Master indicating 15-



amp fused/switch package is available. For safety, 8 grounded 110V outlets and pre-punched holes for adding standard dc or other receptacles are included. Assembly space: 35 sq. ft., 82" H x 84" L x 82" D. Weight, 175 lbs.—**Alden Systems Co., Inc.**, P. O. Box A, Turnpike Rd., Westboro, Mass. 01581.

Circle 45 on reader service card

**DISCOUNT  
PRICES  
TEST  
EQUIPMENT**

**B&K**

**SENCORE  
Leader**

**Shure and Electro-Voice  
Microphones  
I.E.C./Mullard  
Tube Specials**

Catalog & Prices on Request

**FORDHAM** Radio Supply  
Company, Inc.




265 E. 149 Street, Bronx, N.Y.  
Tel: (212) 585-0330

**RCA**

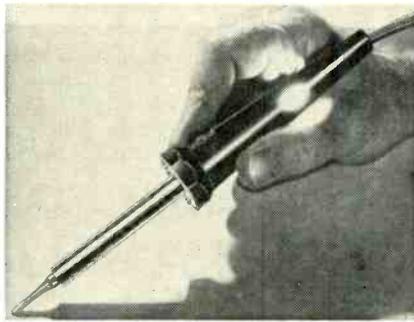**DISTRIBUTORS OF ELECTRONIC SUPPLIES**

Circle 70 on reader service card


**SOLDERING IRON**, model 540 is a 20-40-watt pencil soldering iron designed for constant use in electronic production, repair and maintenance and for "do-it-yourself" kit building. A built-in



light inside the handle shows operation at either 20 or 40 watts.

Unbreakable handle, burn-resistant cord set, stainless steel element, solid-state control and ironclad tips. 8½ in. long, weighs 2 oz., two- and three-wire cords are offered. Under \$8.00 with one tip.—**Endeco**, 5127 East 65th St., Indianapolis, Ind. 46220.

Circle 46 on reader service card

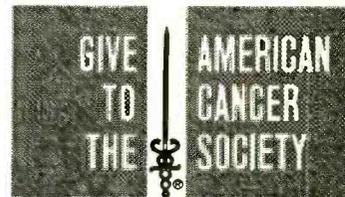

**FREE**



**The World's Largest  
Consumer Electronics Catalog**

The world's Foremost consumer electronics catalog is yours for the asking! Over 25,000 items . . . jam-packed with illustrations and descriptions of the very latest in Hi-Fi, CB, Tape recorders, Radios, Television, Electronic Parts, Technical Publications.

**Everything in Electronics For Home, Business,  
Industry PLUS The Latest in 4-Channel Stereo!**

**LAFAYETTE 1973 CATALOG 730**

**Our 52nd Year**

**Stores From Coast-to-Coast**

**MAIL  
THE  
COUPON  
TODAY**

**LAFAYETTE RADIO ELECTRONICS**  
P.O. Box 10, Dept. 17013  
Syosset, L.I., N.Y. 11791

**Send For Your Free Lafayette Catalog Today!**



Send me the **FREE** LAFAYETTE Catalog 17013

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 71 on reader service card

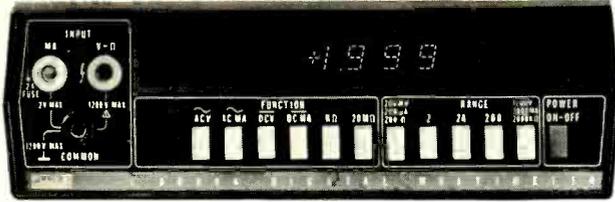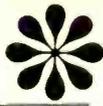

## \* New low cost digital multimeter \$299

- 26 ranges to measure ac/dc voltages from 100 microvolts to 1200 V, ac/dc currents from 100 nanoamperes to 2 amperes and resistance from 100 milliohms to 20 megohms.
- Basic dc accuracy, 0.1%.
- Guaranteed for one full year.

Fluke gives you the best specs and strongest warranty on the market today for the lowest cost of ownership ever.


- Wide choice of options including rechargeable battery pack, digital printer output, deluxe test leads, high-voltage probe, RF probe, 200-amp ac current probe, carrying case, dust cover and rack mounts.
- Unique self-zero feature eliminates offset errors.
- Rugged high-impact case with securely mounted internal electronics.
- Service centers throughout U.S., Canada, Europe and Far East for 48-hour turnaround repairs.



P. O. Box 7428,  
Seattle, Washington 98133.

Get all the details from your nearest Fluke sales office. Dial toll-free 800-426-0361 for address of office nearest you.

Circle 72 on reader service card

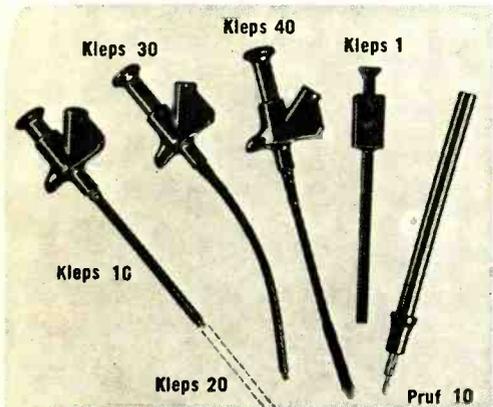

## Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

**Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 3/4" long. **\$1.19**  
**Kleps 20.** Same, but 7" long. **\$1.39**  
**Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. **\$1.47**  
**Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. **\$2.39**  
**Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. **\$.99**  
**Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. **\$.79**  
 All in red or black — specify. For additional information, write for complete catalog of — test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:



**RYE INDUSTRIES INC.**  
130 Spencer Place, Mamaroneck, N.Y. 10543  
In Canada: Rye Industries (Canada) Ltd.

Circle 73 on reader service card

88 RADIO-ELECTRONICS • JANUARY 1973

# appliance clinic

## INTERLOCKS AND MENTAL BLOCKS

by JACK DARR  
SERVICE EDITOR

THE DIAGNOSIS OF TROUBLE IN ANY AUTOMATIC APPLIANCE looks like a big job, at first. Automatic washers, dryers, and others seem to be pretty complicated. They are, but if you'll take what is often an unusual step—Thinking!—it will be a lot easier. There are always certain key reactions that will help give you a handle on the problem.

The basic principle of this is the same in all types of machinery. First, find out what the thing *is* doing—then, recheck to find out what it *isn't* doing. A lot of these will turn out to be interlocked. That is, if one thing isn't there, this will make something else stop.

All of these units have certain "inputs"; ac power, hot water, cold water, gas, and so on. These *must* be present, and in the right quantities, or the thing isn't going to work, or won't work properly. It's built that way, intentionally. They "interlock". This feature prevents the machine from going through a normal cycle if one or more of the normal inputs is missing.

In automatic washers, the machine will stop if there isn't enough water in the tub, during a certain part of the cycle—rinse, for example. Conversely, it will also stop if there *is* water in the tub when it shouldn't be there—at the point when the machine should go into spin. The excess water in the tub would put a very heavy drag on the cylinder in the high-speed spin cycle; so, this is interlocked with the water-level indicator.

This can happen if the drain hose or pump is clogged. The pump cannot drain the tub; so, the machine will simply stop and sit there waiting for someone to come along and fix it. A similar thing could happen to a dryer. These have two thermostats; one closes when the drum is too cool, to bring the dryer up to proper temperature. The other, normally closed, opens if the drum temperature goes too high, to avoid burning up things. If the vent of the dryer becomes clogged, with a bird's nest or something like that, the air can't get out of the machine. With the circulation blocked, the inside temperature will rise, and the up-per-cutoff thermostat will turn the whole thing off.

These are all simple things, but very important. I can vouch for that. Not too long ago, a certain Wife said to her husband, "My washer won't work." "What's the matter?" said Certain Husband, who had only written four books and two correspondence courses on electrical appliances. "How do I know?" replied Wife. "It goes through the wash cycle fine, then stops on rinse."

"OK" said Certain Husband, going down the basement steps with something else on his one-track mind. He ran the timer switch on the washer through the whole cycle, and noticed that all he got in rinse was a buzz. "Call George and ask him to check it," he called back upstairs to his Wife. "After all, it's still in warranty!" and he left for

town to troubleshoot a few Tough Dogs.

When he came home that evening, he was met at the door by a Wife wearing a very wide grin. "Here" she said, handing him a piece of paper. "George left this note for you!" Printed on it, in large block letters, was "TRY TURNING THE WATER ON NEXT TIME, GENIUS!"

Being blessed with perfect 20-20 hindsight, I (woops—he) immediately knew what had happened. He'd rigged up a Plumber's nightmare on the cold-water cock, so that water could be drawn for various things. Since this leaked, as could be expected, he'd formed a habit of turning it off at the sill-cock. This of course, turned off the cold-water supply to the washer at the same time.

Here's what had happened. The machine had gone through wash cycle since this used only hot water. However, the rinse cycle required warm water; both hot and cold valves open at once. Without the cold water, the machine had not filled to the correct level, by the time it was ready to go into the rinse cycle. So, with this interlock open, it had simply shut itself off and sat there waiting for further instructions.

To avoid this kind of embarrassing contretemps in the future, watch out for that mental block. Don't take anything for granted. Check for the presence of all of the necessary inputs to the machine; ac, hot, cold water, gas, free vent, clear drain, and so on. These are all simple things, and if you make a methodical checkout on them, you'll fix about 75% of the "mysterious troubles" that such machinery is prone to.

Always check the simple things first and save the complicated ones for later on when it becomes apparent that they're necessary. **R-E**

## NEA NATESA MEMBERSHIP PROGRAM

NEA -- 1309 West Market St. -- ITTA Bldg., Indianapolis, Ind. 46222

NATESA -- 5908 South Troy Street, Chicago, Ill. 60629

Service Dealer \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Per \_\_\_\_\_

All New Members must be signed up and approved by either NEA, or NATESA. (First Year dues paid -- \$35.00). (Dual Membership not acceptable).

EACH approved NEW NEA or NATESA Member will receive "gifts" from sponsors listed below in excess of \$40.00 (Retail Selling Price).

NEA and NATESA shall have the sole jurisdiction as to the pro-rating of "Gift Certificates" to their respective District, States or specific areas. Their decision shall be final.

We are very grateful to the Sponsors of this program and suggest our theme, "Support Your Supporters" be carried out.

SPONSORS:

AMPEREX ELECTRONIC CORP.  
TECH SPRAY  
THE FINNEY CO.  
ELECTRONIC DEVICES INC.  
INTERNATIONAL RECTIFIER


For further information as to how you can take advantage of this amazing offer, fill out and send the coupon to either NEA or NATESA. (Check preference)

MEMBERSHIP DRIVE ends March 31, 1973.

# WANTED... BURGLAR & FIRE PROTECTION

by

**audiotex**

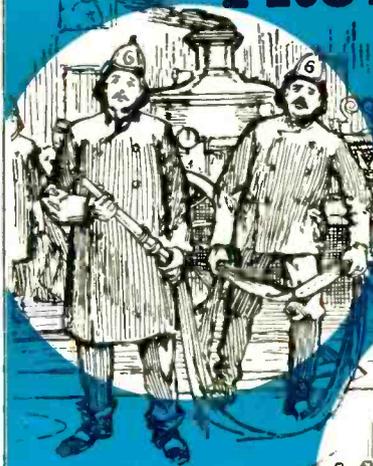


## Magna-Sentry

**BURGLAR & FIRE ALARM**  
Low cost protection for you  
and your valuables.


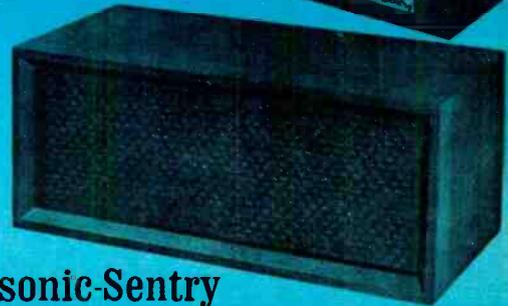
## Electro-Sentry

**BURGLAR ALARM**  
Professional type  
Do-It-Yourself protection  
for your home and business



## Ultrasonic-Sentry

**BURGLAR ALARM**  
Protects you with harmless invisible ultrasonic waves.

Take this ad to your electronic supplier for your copy of "SECURITY AND YOU" for only 50¢.



**GC ELECTRONICS**  
DIVISION OF HYDROMETALS, INC.  
ROCKFORD, ILLINOIS 61101 U.S.A.



Circle 74 on reader service card  
JANUARY 1973 • RADIO-ELECTRONICS 89

# AT LAST! PROFESSIONAL HOME PROTECTION EVERYONE CAN INSTALL AND AFFORD.

Model FC-100  
**\$69.95**  
WIRED



- Start your custom Burglar/Hold-up/Fire Alarm System with the FC-100. Add on Sensors, Alarms and Accessories to suit your own needs.
- "Do-it-Yourself" Installers Handbook included. No technical knowledge needed — No soldering.
- 100% Professional in Design, Reliability, Performance.



## 'Fail Safe'-SYSTEM BY EICO

A New Concept in "Do-it-Yourself" Home Protection

### FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card or send 25¢ for First Class mail service.



EICO, 283 Malta Street, Brooklyn, N.Y. 11207

Circle 75 on reader service card

# new books

**RADIO AMATEUR OPERATING HANDBOOK**, by Marshall Lincoln, W7DQS. Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, Ind. 46268. 8 1/2 x 5 1/2 in. 160 pp. Softcover, \$4.95

This book deals primarily with the communications function of amateur radio. It intends to help the reader understand and master the methods developed through years of experience by thousands of other amateur radio operators. Subjects covered include making yourself understood, identification and logging requirements, observing frequency boundaries, utilizing propagation effects, DX operating, operating across the border.

**NEW IC FET PRINCIPLES & PROJECTS**, by Ken Sessions and Don Tuite. TAB Books, Blue Ridge Summit, Pa. 17214. 5 1/2 x 8 1/2 in. 160 pp. Hardcover, \$6.95; Softcover, \$3.95.

This instructional projects book contains a wealth of information to aid in understanding and using the newest FET and IC components. After the introductory groundwork explaining FET's and how they work, the book describes basic circuits that use FET's as amplifiers and then, complete with schematics and parts lists, shows how to construct 12 basic FET circuits.

**PRACTICAL DESIGN WITH TRANSISTORS, SECOND EDITION**, by Man-nie Horowitz. Howard W. Sams & Co., Inc., 4300 West 62nd St., Indianapolis, Ind. 46268. 5 1/2 x 8 1/2 in. 288 pp. Softcover edition \$6.95.

This up-dated edition contains most of the information needed by the engineer and technician to plan basic transistor circuits for modern electronic equipment. The book supplies enough factual material to complete independent circuit designs. Math is presented when necessary, but the derivations have been excluded. With the aid of this book, anyone with a working knowledge of algebra and radio electronics should have no difficulty in designing a transistor circuit.

# QUANTITY BUYING POWER

FREE \$1 BUY WITH EVERY 10 YOU ORDER

Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

- KNOB SPECIAL**
- 100 — ASSORTED RADIO KNOBS All standard types ... \$1
  - 50 — TV KNOBS — POPULAR TYPES Mostly Selector & Fine Tuning ... \$1
  - 25 — VERTICAL LINEARITY KNOBS Long stank ... \$1
  - 20 — VERTICAL LINEARITY KNOBS ... \$1
  - 25—KNURLED RADIO KNOBS Hard to get ... \$1
  - 40 — DELUXE RADIO KNOBS Choice assortment ... \$1
- ANY 6 KITS FOR \$5

- TRANSISTOR RADIO *asst type* \$1.50
- TAPE RECORDER—assorted types good, bad, broken, as-is, potluck ... \$4
- 300 — ASST. 1/2 W RESISTORS Top Brand, Short Leads, Excellent Selection ... \$1
- 100—ASST 1/4 WATT RESISTORS stand, choice ohmages, some in 5% ... \$1
- 100—ASST 1/2 WATT RESISTORS stand, choice ohmages, some in 5% ... \$1
- 70 — ASST 1 WATT RESISTORS stand, choice ohmages, some in 5% ... \$1
- 35 — ASST 2 WATT RESISTORS stand, choice ohmages, some in 5% ... \$1
- 50 — PRECISION RESISTORS asst. list-price \$50 less 98% ... \$1
- 20 — ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt ... \$1
- 10—ASSORTED SLIDE SWITCHES SPST, SPDT, DPDT, etc. ... \$1

- 12" UNIVERSAL SPEAKER \$4.89
- 10" PHILCO SPEAKER \$2.99
- 8" UNIVERSAL SPEAKER \$2.99
- 5" UNIVERSAL TWEETER \$1.29
- UNIVERSAL 4" PM SPEAKER \$1
- 2 1/2" x 4" SPEAKER \$6.95 Ea.
- 4" X 6" "QUAM" 16 OHM SPEAKER Large magnet ... \$1.79
- RONETTE STEREO CARTRIDGE \$2
- STEREO HEADPHONES \$5.95
- COLOR POWER TRANSFORMER \$6.95
- 4—50' HANKS HOOK-UP WIRE \$1
- 100'—SPOOL SPEAKER WIRE \$1.50
- 10 — ASST. RADIO & TV TUBES \$1
- 5 — AUDIO OUTPUT TRANS-FORM Sub-min for Trans Radios \$1
- 5 — I.F. COIL TRANSFORMERS \$1
- 6" UNIVERSAL SPEAKER \$1.29 Ea.
- ALL AMERICAN TUBE KIT \$2.99
- 70° COLOR TUBE BRIGHTNER \$3.95
- 90° COLOR TUBE BRIGHTNER \$4.95

**SARKES TARZIAN TUNER**  
41mc

Latest Compact Model good for all 41 mc TV's.  
BRAND NEW—

Best TUNER "SARKES TARZIAN" ever made—last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date.  
COMPLETE with Tubes \$7.95

- UHF TUNER — TRANSISTOR TYPE \$3.95
- STANDARD TUNER — TRANSISTOR (GUIDED GRID) \$1
- PHILCO TV TUNERS \$4.95
- GE — TV TUNERS \$5.95
- GE — STANDARD COIL TV TUNER \$7.95
- TV TUNERS VHF/UHF all new \$7.95
- ALL NEW TV TUNER Standard makes — less tubes \$1

- 2 — COLORBURST QUARTZ-CRYSTAL For Most Color TV sets 3579.545 KC \$1.89
- 2 — ELECTROLYTIC CAPACITORS CD — 40/40 MFD — 450 Volts \$1
- SPECIAL TUBE BUY \$1
- 1—6" x 9" HEAVY DUTY 10 OZ. SPEAKER Ceramic Type \$3.69
- 5 ASSTD. GLOBAL VARISISTOR Popular replacements for most COLOR TV \$1
- 10 — SETS PHONO PLUGS & PIN JACKS RCA type \$1
- 8—PRINTED CIRCUIT IF TRANS-FORMERS 4-Lug, 456 KC \$1
- 25 — 3900-OHM-7w RESISTOR 10% Corning glass \$1
- 20 — .47-600V CONDENSERS White Ceramic C.D.-American \$1
- STEREO TONE ARMS Most popular type—turn over cartridge \$2
- CO-AX CABLE RG59U grey or black 250'—\$9 100'—\$3.69 50'—\$1.89
- 4 — TV ALIGNMENT TOOLS Most useful assortment #1 \$1
- 4 — TV ALIGNMENT TOOLS #2 For Color TV \$1.49
- 6 — TV COLOR ALIGNMENT TOOLS Most popular type \$2.79
- 5 — 9 VOLT MOTORS Excellent for hobbyist \$1
- 200' — #24 SOLID PUSH BACK WIRE Yellow or Black excellent buy \$1
- UNIVERSAL TV ANTENNA Back of set mounting 5 section rods \$1.98

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost. HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Terms will be returned as packing slips in your order, plus lists of new offers. **Minimum Order \$3.00**

Name .....  
Address .....  
Cost of goods .....  
Shipping estimated .....  
TOTAL

Please specify refund on shipping overpayment desired:  CHECK  POSTAGE STAMPS  MERCHANDISE (our choice) WITH advantage to customer

**BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024** 212-874 5600 TELEPHONE

**FAX**, by Daniel M. Costigan. Chilton Book company, 100 East 42nd Street, New York, N.Y. 10017. 6 x 9 1/4 in. 270 pp. Hardcover, \$10.00.

Facsimile, or "Fax" for short, is the system by which graphics are transmitted by radio waves or by wire from one place to another. Although this system is not new, it is coming closer to its full potential as new scientific developments and more efficient hardware are made available. This book brings it all into focus. The author presupposes some small knowledge of mechanics and electronics on the part of the reader and although the book is not directed to the electrical engineer, even he can find in it portions that are useful.

**TRANSISTOR SPECIFICATIONS MANUAL, FIFTH EDITION**, by Howard W. Sams Engineering Staff, Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis, Ind. 46268. 8 1/2 x 11 in. 160 pp. Softcover, \$4.50

This is the 5th edition of this book and contains the electrical and physical parameters along with the manufacturers of nearly 10,000 transistor types. The manual is an excellent reference for engineers, technicians, or anyone who enjoys working with transistors. It can alleviate the long and sometimes fruitless search for the source of electrical and physical information dealing with specific transistor types. The manual has specifications, lead-identification and outline sections.

**HANDBOOK OF SIMPLIFIED SOLID-STATE CIRCUIT DESIGN**, by John D. Lenk. Prentice-Hall, Inc., Englewood Cliffs, N.J. 07632. 6 1/4 x 9 1/4 in. 310 pp. Hardcover, \$12.00.

Design theory and analytical procedures are kept to the barest minimum sufficient for a working, functional knowledge of the circuit. Coverage includes complete procedures for breadboarding, testing and final circuit completion. The six major chapters treat basic design rules, audio amplifiers, operational amplifiers with IC's, radio frequency circuits, wave-forming and waveshaping circuits and power-supply circuits. R-E

# NEW EICO TR-410 Solid-State Triggered Sweep 10MHz Oscilloscope \$379.95

Never before has so much been built into a low cost solid state triggered sweep scope!



INCLUDES EXCLUSIVE DUAL PROBE

EICO introduces the first laboratory quality, high performance, wideband Triggered Sweep Oscilloscope, at a price you can afford!

Use as Vectorscope for Color TV Servicing ■ 3 calibration voltages (2, 5 and 10) ■ Quick connect BNC connector at Vertical Input ■ Front panel adjustable Horizontal and Vertical DC Balance Controls ■ Vertical and Horizontal selection of AC or DC modes of amplification ■ Sweep synchronized Gate Output ■ Flat faced CRT ■ Z Axis input ■ Rear panel astigmatism control ■ Edge lit calibrated screen ■ Operates on a standard 120 volt, ± low 100 volt or a 220-230 volt line.

## FREE 1973 EICO CATALOG

For name of nearest dealer and free catalog check reader service card or send 25¢ for prompt first class mail service. EICO-283 Malta St., B'klyn, N.Y. 11227



Circle 75 on reader service card

### SHANNON MYLAR RECORDING TAPE

3" - 225' .. .19	CASSETTE C-60 .. . . .59
3 1/4" - 600' .. .58	CASSETTE C-90 .. . . .1.00
5" - 600' .. .62	CASSETTE C-120 (TDK) 1.97
5" - 900' .. .80	8 - Track - 64 Min. - 1.29
5" - 1200' .. .97	8 - Track - 80 Min. - 1.59
5" - 1800' .. 1.49	8 - Track - Cleaner - 1.49
7" - 1200' .. .77	
7" - 1800' .. 1.12	3" TAPE REEL .... .06
7" - 2400' .. 1.79	3 1/4" TAPE REEL .... .07
7" - 3600' .. 2.95	5" TAPE REEL .... .14
	7" TAPE REEL .... .15

### CANADIANS: Ordering is easy - we do the paperwork - try a small order

**IBM COMPUTER SECTIONS**  
8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.  
Incl. - Transistors  
Condensers  
Resistors, Heat Sinks,  
Diodes, Etc.  
**8 for \$1**  
**100 for \$10**

### WESTINGHOUSE ALL TRANSISTOR HOME/OFFICE MESSAGE CENTER

Leaves messages for other for replay . . . Built in speaker/microphone for talk-into convenience . . . Records up to 8 minutes of messages . . . Illuminated signal shows when a message is waiting. Control adjusts playback volume without affecting recording volume . . . Capstan Drive;  
**BRAND NEW SOLD AS IS \$7.95**

### MARKET SCOOP COLUMN

- SIMPSON 2 1/2" ROUND PANEL METERS Model 125 (0-100 DC Milliammeters) .. \$3.95
- SIMPSON 2 1/2" ROUND PANEL METERS Model 125 (0-10 DC Milliammeters) .. \$3.95
- ASTATIC PICKUP MODEL 700-89T Contains 89T ceramic cartridge LIST PRICE \$17.00 .. \$2.95
- 20 - DIPPED MYLAR CAPACITORS .01-600V .. \$1
- 20 - DIPPED MYLAR CAPACITORS .033-600V .. \$1
- 20 - DIPPED MYLAR CAPACITORS .0033-1000 V .. \$1
- 20 - DIPPED MYLAR CAPACITORS .047-400 V .. \$1
- 15 - MOLDED TUBULAR CAPACITORS .068-400 V .. \$1
- 20 - DIPPED MYLAR CONDENSERS .0039-400 V .. \$1
- 10 - SPRAGUE "ORANGE DROP" CAPACITORS .0056-2000 Volt .. \$1
- 1 - 20 FT. COILED GUITAR CABLE With plugs .. \$2.95
- 1-CASSETTE TYPE DYNAMIC MICROPHONE with universal plugs-200 Ohms .. \$2.49
- HEAVY DUTY COLOR FOCUS RECTIFIER 14,000 PIV @ 1 ma .. \$1
- UTAH "CELESTA" 3-WAY CO-AX SPEAKERS 8"-10oz. Mag.-30 Watts .. \$16.95
- UTAH "CELESTA" 3-WAY CO-AX SPEAKERS 12"-20oz. Mag.-45 Watts .. \$24.95


- COLOR-TV RECTIFIER - Used in most color sets- 6500 kv .. \$1.95
- 10 - STANDARD TRANSISTORS NPN & PNP 2N404, 2N414, etc. .. \$1
- 10-ASSORTED DIODE CRYSTALS 1N34, 1N48, 1N60, 1N64, etc. .. \$1
- 6 - TOP BRAND SILICON RECTIFIERS 1 amp. 1000 PIV .. \$1
- 5 - PNP TRANSISTOR general purpose, TO-5 case .. \$1
- 5 - NPN TRANSISTORS general purpose, TO-5 case .. \$1
- 50 - ASSORTED TRANSISTORS big factory scoop-sold as-is .. \$1
- TV TWIN LEAD-IN 300 ohm 500' - \$7.100-\$1.50 50' .. \$1
- 12-MINIATURE ELECTROLYTIC CONDENSERS For Transistor & miniature work .. \$1
- 6 - MINIATURE ELECTROLYTIC CAPACITORS 5 MFD-150 V .. \$1
- 3-ELECTROLYTIC CONDENSERS 100 mfd.-100 V, 50 mfd.-75 V .. \$1
- 2-ELECTROLYTIC CONDENSERS C.D. 500 mfd-200 volts .. \$1
- 2-ELECTROLYTIC CONDENSERS UNECAP .. 2000/1000 Mfd .. \$1
- 2 - ELECTROLYTIC CONDENSERS 80/50mfd-450V, 20mfd-250V, 150mfd-25V .. \$1
- 2 - ELECTROLYTIC CONDENSERS 200/30/4 mfd - 350V .. \$1
- COLOR CONVERGENCE ASSEMBLY Universal type-good for most sets .. \$2.49

- WESTINGHOUSE FM TUNER (12DT8 Tube) .. \$2.99
- WESTINGHOUSE FM TUNER #476-V-015D01 .. Transistor .. \$3.99
- 300 - ASSORTED HEX NUTS 2/56, 4/40, 5/40, 6/32, 8/32 .. \$1
- 250 - ASST. SOLDERING LUGS best types and sizes .. \$1
- 250 - ASST. WOOD SCREWS finest popular selection .. \$1
- 250 - ASST. SELF TAPPING SCREWS #6, #8, etc. .. \$1
- 150 - ASST. 6/32 SCREWS and 150 6/32 HEX NUTS .. \$1
- 150 - ASST. 8/32 SCREWS and 150-8/32 HEX NUTS .. \$1
- 150 - ASST. 2/56 SCREWS and 150-2/56 HEX NUTS .. \$1
- 150 - ASST. 4/40 SCREWS and 150-4/40 HEX NUTS .. \$1
- 150 - ASST. 5/40 SCREWS and 150-5/40 HEX NUTS .. \$1
- 500 - ASSORTED RIVETS most useful selected sizes .. \$1
- 300 - ASSORTED WASHERS most useful selected sizes .. \$1
- 100 - ASST. RUBBER BUMPERS for cabinet bottoms & other uses .. \$1
- 100-ASSORTED RUBBER GROMMETS best sizes .. \$1

**RCA 110° FLYBACK TRANSFORMER**  
We scooped the Market Latest type - standard for all 110° TV's  
RCA's design of large Coil produces 18KV - assuring adequate width Incl. Schematic Diagram application for any TV  
List price \$13.00  
Your price .. \$3  
10% off in lots of 3

- 110° TV DEFLECTION YOKE \$3.95 for all types TV's incl schematic
- "COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE .. \$5.95
- 90° FLYBACK TRANSFORMER \$2.95 for all type TV's incl schematic
- 90° TV DEFLECTION YOKE \$2.95 for all type TV's incl schematic
- 70° FLYBACK TRANSFORMER \$2 for all type TV's incl schematic .. \$2
- 70° TV DEFLECTION YOKE for all type TV's incl schematic .. \$2
- SHARP 110° FLYBACK & YOKE COMBINATION #8FT-582 Good for most portable TV. \$5.00
- 90° COLOR YOKE For all Rectangular 19 to 25" Color CRT's \$10.95
- RCA COLOR FLYBACK Part #113382 (Stancor #HO-601C) \$12.95

Circle 76 on reader service card

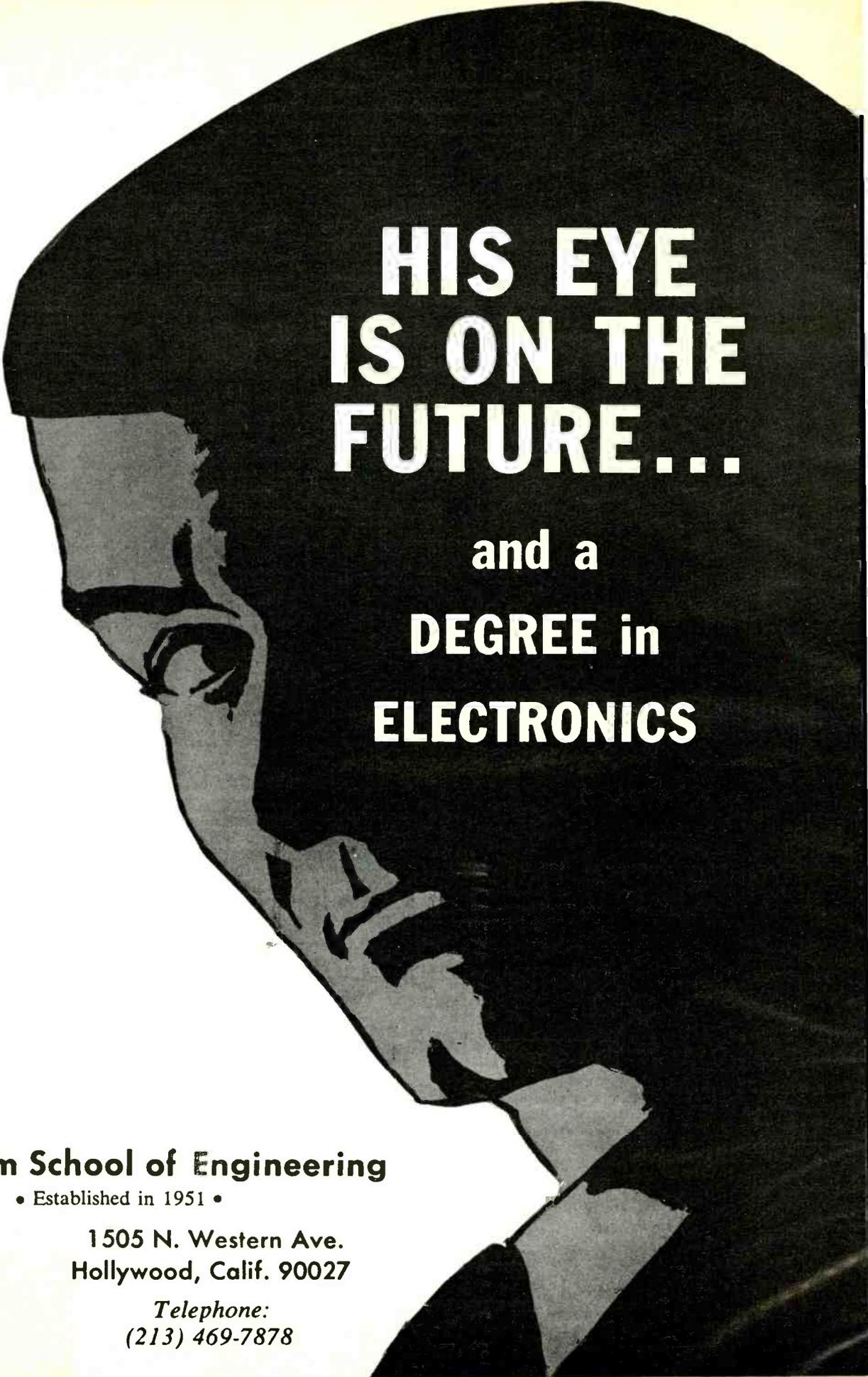

**HIS EYE  
IS ON THE  
FUTURE...**

**and a  
DEGREE in  
ELECTRONICS**

**Grantham School of Engineering**

• Established in 1951 •



1505 N. Western Ave.  
Hollywood, Calif. 90027

*Telephone:*  
(213) 469-7878

**What's in YOUR future? Where will you be one year from today –  
or in two years, or five years?**

Your future is shaped by the steps you take today. Keep your eye on the future as you plan. Take steps that should bring greater enjoyment and satisfaction in your work and greater financial rewards. Move ahead in ELECTRONICS – the Science of the Seventies – by

## **STUDYING AT HOME**

Grantham offers a college-level program in Electronics Engineering, mainly by home study. This program consists of four correspondence courses (called correspondence semesters) which logically follow each other, preparing you for different levels of employment as you advance in your electronics career. Upon completion of the four correspondence semesters (and a two-week seminar held at the School), you are awarded the A.S.E.T. Degree – *the Degree of Associate in Science in Engineering Technology* – with a major in electronics. (Then, you may continue for the B.S.E.E. Degree through further residential training in engineering subjects and transfer credits in the humanities.)

## **WHO IS GRANTHAM?**

Grantham School of Engineering is a college-level institution, teaching mainly by correspondence, authorized under the laws of the State of California to grant academic degrees. We are "*the college that comes to you.*" Mail the postcard or coupon for our free bulletin which contains complete information.

### **Grantham School of Engineering** RE-1-73

1505 N. Western Ave., Hollywood, Cal. 90027

Please send me your free Bulletin which explains how the Grantham educational program can prepare me for a *degree* in electronics.

- I am a beginner in electronics.  
 I am an experienced electronics technician.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**EQUIPMENT REPORT**  
(continued from page 22)

do is flip both the socket-selector switch and the polarity switch at the same time. This can be done with one hand.

Another very useful thing the 501A will do is catch those "weirdo" transistors that we run into now and then. In one of my normal unusual coincidences, I ran into a "weirdo" while running the tests on the 501A. I checked a pair of brand-new, high-quality transistors. They didn't work too well (in a comp-symm output on a


little stereo amplifier). Pulling them, I checked for balance. I found that one was good, meeting the specs in every way. The other read a very low beta on a conventional transistor checker.

Putting it on the 501A, I could see why. The thing refused to turn on at the point where it should. I had to turn the base-current up to more than five times the normal amount before I could get the thing to conduct. I'm not going to try to explain *why* it did this, but I did *catch it*, and did find out that it was defective in a very short time.

This instrument is going to be a great help to us in using all kinds of

solid-state equipment, even industrial-electronics gadgetry. It should be quite essential in solid-state television servicing. You'll find that the in-circuit curves won't look too much like the out-of-circuit curves. However, from what I have seen so far, the main thing is that a transistor which will display a family of curves in-circuit is probably good. Because it is a "cold" check without power applied to the chassis, it should be very useful when we must bring a chassis to the shop for servicing. Another use would be in connection with those reparable modules showing up in increasing numbers. All in all, the 501A is a very worth-while addition to our instrumentation. **R-E**

# TV TUNER SERVICE

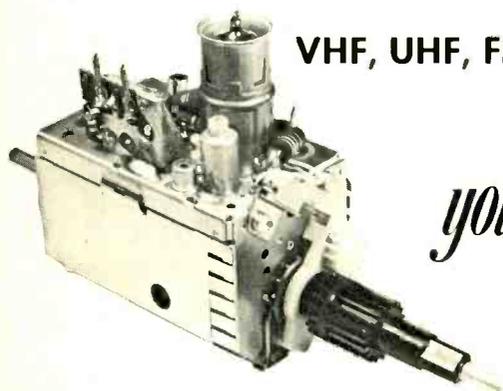

VHF, UHF, FM or IF-Subchassis. . .  
. . . All Makes

*you get...*

**Fast 8 hr. Service!**

## You owe it to yourself

to try P.T.S. We are the fastest growing, oldest and now the largest tuner service company in the world. Here is what you get.

1. Fastest Service—8 hr.—in and out the same day. Overnight transit to one of our six plants, for parts, tuners or IF-modules.
2. All tuners cleaned inside and out, repaired, realigned and air tested.
3. On IF-modules all stages checked, all traps set with high calibre test equipment.
4. Fine Quality! Your customers are satisfied and you are not bothered with returning your units for rework!
5. Lower Cost! Up to \$5.50 less than other tuner companies!
6. Friendly, helpful personalized service!

## 1 YEAR GUARANTEE



FIRST TO OFFER 365-DAY GUARANTEE!  
COLOR—BLACK & WHITE—TRANSISTOR TUNERS—  
ALL MAKES  
GUARANTEED COLOR ALIGNMENT—  
NO ADDITIONAL CHARGE

LIKE TO DO IT YOURSELF?

PTS makes all tuner parts available to you.

Send one dollar (redeemable) for our TUNER REPLACEMENT GUIDE AND PARTS CATALOG

- 60 pages of top information
- Blow-up of all tuners
- Largest exact tuner replacement guide
- Antenna Coil Replacement Guide
- Multi-fit Replacement Tuner Shaft Guide

**We offer you finer, faster...**

**Precision Tuner Service**

P. O. Box 272—Bloomington, Ind. 47401  
P. O. Box 6771—Jacksonville, Fla. 32205  
P. O. Box 41354—Sacramento, Calif. 95841  
P. O. Box 3189—Springfield, Mass. 01103  
P. O. Box 7332—Longview, Tex. 75601  
P. O. Box 4145—Denver, Colo. 80204

Tel. 812/824-9331  
Tel. 904/389-9952  
Tel. 916/482-6220  
Tel. 413/734-2737  
Tel. 214/753-4334  
Tel. 303/244-2818

Circle 77 on reader service card

For fastest service, send faulty unit with tubes, shields and all broken parts to:  
**PTS ELECTRONICS, INC.**


VHF-UHF-FM \$ 9.95  
UV-COMBO \$16.95  
IF-MODULE \$12.50  
Major Parts charged at Net Price

CUSTOMIZED REPLACEMENTS AVAILABLE FOR \$12.95 UP (NEW OR REBUILT)



"I have some bad news for you, Mrs. Benson! You know those lines you thought were crayon marks. . . ."

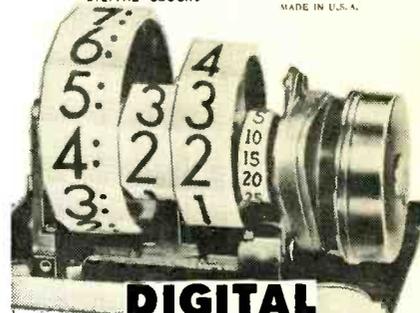**TYMETER**  
"Time At A Glance"  
DIGITAL CLOCKS



**DIGITAL CLOCK MOVEMENTS**

#130..12 HOUR #131..24 HOUR

DIGITS RESETTABLE INDIVIDUALLY

Available in 50, 60 cy., all voltages, AC. UL approved motor, cord. One Year Guarantee.



**SECOND BY SECOND 12 and 24 Hour READ OUT DIGITAL CLOCK**

Complete Line of Count-Up and Count-Down Digital Computers

CATALOG ON REQUEST

**PENNWOOD NUMECHRON CO.**  
TYMETER ELECTRONICS  
DIVISION OF LCA CORPORATION  
7749 FRANKSTOWN AVE. PITTSBURGH, PA. 15208

Circle 78 on reader service card

# next month

FEBRUARY 1973

## ■ Semiconductor Interchangeability Directory

Need a replacement for a standard 2N type transistor? Here is the first part of a directory that will list standard 2N types and several brands of direct replacements. This is one directory you will use frequently.

## ■ All About Dual-Trace Oscilloscopes

See how they operate and what you can do with them. A dual-trace scope can speed some service jobs while others may be almost impossible without one of these new instruments.

## ■ Wonderful World Of Infrared


What's new; what's happening; how does it work! A state-of-the-art report on the latest news in the exciting field of infrared.

## ■ Microprogrammable IC Clock

An MOS MSI chip is the entire clock. See how the chip functions; how you can use it in real applications; how it interfaces with readout devices.
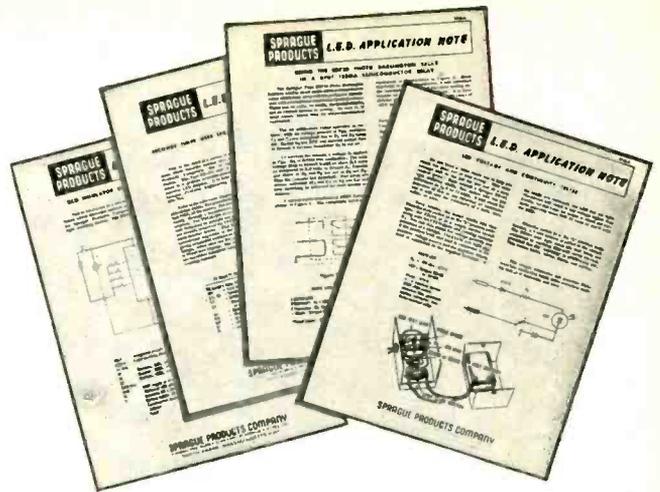
### PLUS:

**Build Your Own Low-Cost Keyboards**  
**Jack Darr's Service Clinic**  
**State of Solid State**  
**Step-By-Step Troubleshooting**



# FREE

## L.E.D. Application Notes to help you do new things with new circuits!

Now . . . get four **free** Application Notes hot-off-the-press that describe various uses and circuits for Sprague LED devices. Notes cover a BCD simulator, seconds timer, voltage and continuity tester, and an all-solid-state semiconductor relay. They've been prepared specifically to help open up a new world of electronic experimentation for **YOU**.

Ask your distributor for copies, or write our Guy Ezelle at Sprague Products Co. Better yet, fill out and mail coupon today!

### Sprague Products Company

81 Marshall St., North Adams, Mass. 01247

Attention: Mr. Guy Ezelle

YES . . . send me free L.E.D. application notes on:

- BCD Simulator     Voltage & Continuity Tester  
 Seconds Timer     Semiconductor Relay

Name .....

Address .....

City .....

State .....

Zip .....

**SPRAGUE**  
THE MARK OF RELIABILITY

68-2117

Circle 80 on reader service card  
JANUARY 1973 • RADIO-ELECTRONICS 97

# EDI

**THOUSANDS OF BARGAINS—TOP VALUES IN Electronic Parts**

Transistors, Modules, Speakers, Stereo, HI-FI, Photo Cells and thousands of other Electronic Parts. Send for **FREE** Catalog

**ELECTRONIC DISTRIBUTORS INC.**  
Dept. TA-2, 4900 Elston  
Chicago, Ill. 60630

RUSH CATALOG

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

Circle 84 on reader service card

## TUNE-IN

on these TOP-RATED "NO-NOISE" PRODUCTS

PROVEN PERFORMANCE FOR COLOR AND B/W

**FIRST**, simply spray parts with **SUPER SPRAY BATH**. Dissolve and flush away grease, dirt, oil and oxidation—penetrative action cleans and restores all component parts.

**THEN**, follow with **VOLUME CONTROL AND CONTACT RESTORER** for special attention to volume controls, push button assemblies, band switches, relays and other electrical contacts.

**"NO-NOISE" products are guaranteed non-flammable, no carbon tet, non-toxic—safe for plastics.**

For Tuners (incl. wafer type) use **TUNER TONIC With Perma Lube** OR **SUPER LUBE** for further cleaning and lubrication—economical, a little does a lot.

Other Famous "NO-NOISE" Products  
• EC-44 • Frigid Air • Tape Reco Head Cleaner


Often imitated but never duplicated

**ELECTRONIC CHEMICAL CORP.**  
813 Communipaw Avenue Jersey City, N. J. 07304


Circle 83 on reader service card

### AUTOMATIC COLOR CIRCUITS


(continued from page 71)

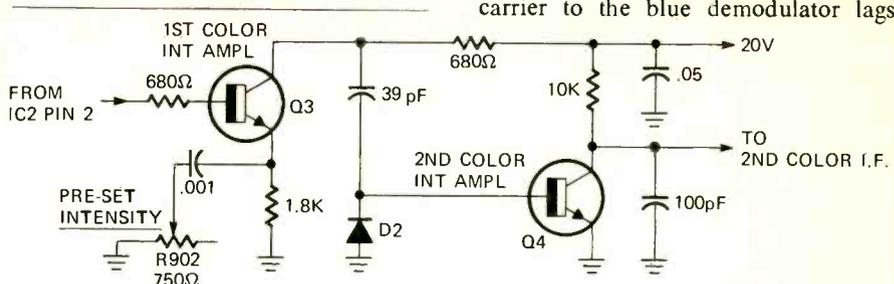

**FIG. 13—AUTOMATIC COLOR INTENSITY CIRCUIT** by Motorola. The preset INTENSITY control adjusts the acc level. Rectified voltage from the color processor controls color amplifier.

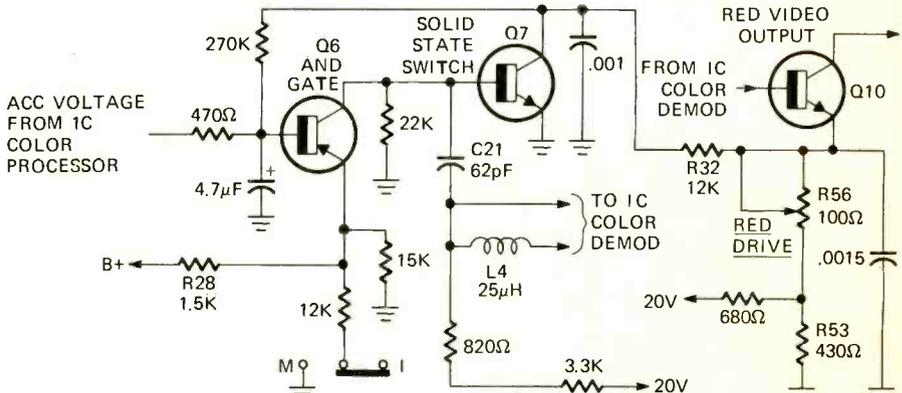

**FIG. 14—TINT CORRECTION CIRCUIT** alters phase of subcarrier to blue demodulator.

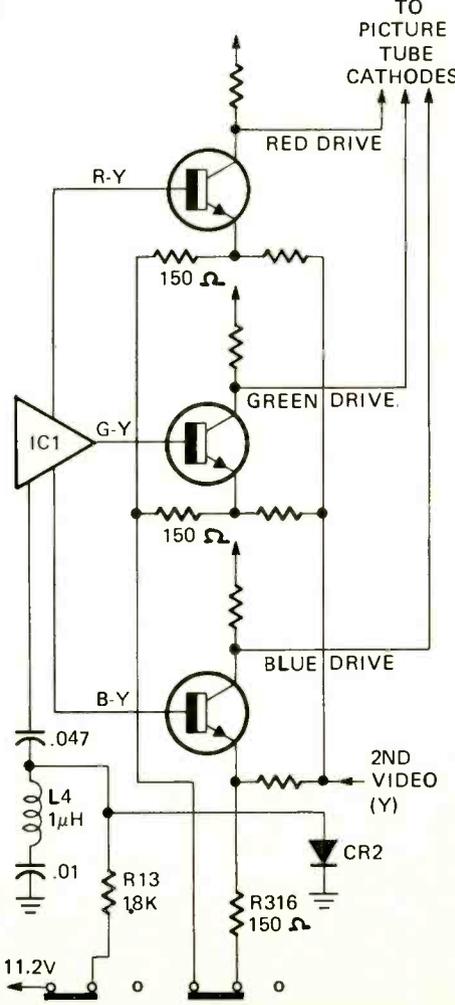

**FIG. 15—TINT CORRECTION SCHEME** in the RCA CTC48 color television chassis.

ditions coincide Q6 is turned on grounding C21. The phase of the subcarrier to the blue demodulator lags

increasing the demodulation angle. When Q6 is on solid-state switch Q7 also conducts grounding the end of R32 connected to its collector. Because of this resistor's connection to the red video output transistor emitter the red drive increases completing the tint correction.


**Philco**—Although Philco schematics were not available as we write this the literature says that the Philcomatic Master Control activates preference controls to allow variations in color, tint, contrast and brightness. From the description it is not clear whether these are switched in presets or reduced range controls. We'll have to clear this up at a later date.

**RCA**—RCA uses reduced range controls to retain some feel of operating controls and to allow minor variations in their settings. The tint correction scheme of the CTC48 chassis is shown in Fig. 15. In the on position the forward bias of CR2 is interrupted inserting L4 into the circuit. The connections of this circuit to the demodulator portion of one of the two ICs used produce counterclockwise R - Y and clockwise B - Y rotations as described at the beginning of this article. In addition R316 the 150-ohm resistor in the emitter circuit of the blue drive transistor is opened. Since this reduces the stage gain the second condition for the reduction of the Q components is satisfied.

That's about all we have room for in this issue. The remaining automatic color circuits will be described in a separate article in a future issue. R-E

# BRAND NEW CATALOG THOUSANDS OF SURPLUS BARGAINS
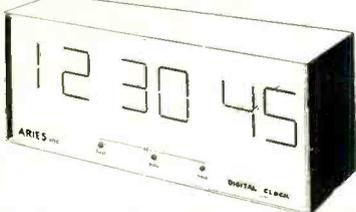
## GIANT 2-1/2" NUMERAL "NIXIE" CLOCK KIT



New! For factories, offices, and commercial establishments, and those people who like large displays, characters appear as a bright continuous line which can be read from distances as great as 150 feet. All drive circuits are solid state, and unit employs new custom LSI clock chip. Indicates hour, minutes, and seconds. May be wired for 24 hour or 12 hour operation with a simple jumper change. Kit offered complete with or without case for custom installations. Parts include P.C. board, sockets, solid state components, hardware, resistors, caps, viewing filter, etc.

Sh.Wt. 15 lbs.

With Case GNNC/C \$98.50  
Without Case GNNC \$84.50

## LOW-PRICED 6-DIGIT CLOCK KIT



New, low-priced digital clock with General Electric 7-segment numeric display tubes, in a styled walnut wood cabinet. In 1972, the B&F nixie display clock made history by being the first and only clock with electronic hours, minutes, and seconds display under \$100. Now we have broken the \$50 price barrier for 1973, and we doubt that anyone in the near future will be able to match this super-low price! This economy is made possible by a new large-scale integration chip, custom-designed for a six-digit clock. Clock has BCD output for external devices. May be wired for 24 or 12 hour operation with only a simple jumper change. Complete with all parts, sockets, instruction manual, and real wood case. Only a soldering iron and a screwdriver are required.

Sh.Wt. 5 lbs. LPDCW \$47.50

## SANKEN HIGH POWER, HIGH PERFORMANCE HYBRID VOLTAGE REGULATORS

These hybrid regulators are easy to use, requiring no external components. Excellent for operational amplifier supplies, logic supplies and other high performance applications. All regulators have less than 50 millivolts ripple and better than 1% line and load regulation, some models far exceeding this specification.

- SI3120E 12 Volts, 1 Ampere .....\$2.25
- SI3150E 15 Volts, 1 Ampere .....\$2.25
- SI3240E 24 Volts, 1 Ampere .....\$2.25
- SI3050E 5 Volts, 1 Ampere .....\$2.25
- SI3554M 5 Volts, 3 Amperes .....\$7.00

## WIRE-WRAP COMPUTER WIRE

New surplus from a large computer company. Solid silver-plated OFHC copper conductor. Special high-temperature, thin-wall insulation of teflon, and other quality materials. Extremely rugged and flexible wire-wrap wire. In addition to usual applications, can be used for effective breadboarding, and wherever quick stripping of solid wire is desired. Different colors are now available. State first, second, and third choice of colors. Shipping weight per 500' is 1 lb.

Conductor Size	Order No.	500'	1000'	10,000'
30	WWW30(ft.)	\$5.00	\$9.00	\$75.00
26	WWW26(ft.)	\$6.00	\$11.00	\$95.00
24	WWW24(ft.)	\$6.50	\$12.00	\$100.00

## ROTARY THUMBWHEEL SWITCH



Brand new digital switch, available with output in straight decimal form, or BCD. Widely used to set up predetermined counts or intervals, digital values or digital-to-analog values. Prices quoted are per section, or decade.

DECIMAL OUTPUT (10-position) RTSDCO \$2.35  
BINARY-CODED DECIMAL OUTPUT RTSBDC \$2.35

## HIGH-TEMP. POWER TRANSISTOR

2N1015D NPN Silicon 200W  
Power Amplifier 200V 10A \$2.00  
10 for \$17.50 or 100 for \$150.00




## SANKEN HYBRID AUDIO AMPLIFIER MODULES.

We have made a fortunate purchase of Sanken Audio Amplifier Hybrid Modules. With these you can build your own audio amplifiers at less than the price of discrete components. Just add a power supply, and a chassis to act as a heat sink. Brand new units, in original boxes, guaranteed by Band F, Sanken, and the Sanken U.S. distributor. Available in three sizes: 10 watts RMS (20 watts music power), 25 watts RMS (50 watts M.P.), and 50 watts RMS. (100 watts M.P.) per channel. Twenty-page manufacturer's instruction book included. Sanken amplifiers have proved so simple and reliable that they are being used for industrial applications, such as servo amplifiers & wide band laboratory application:

- SI1010Y 10 watt RMS amplifier, industrial grade.....\$4.75
- SI1025A 25 watt RMS amplifier, industrial grade.....\$14.75
- SI1050A 50 watt RMS amplifier, industrial grade.....\$22.50
- SI1025E 25 watt RMS amplifier, economy grade.....\$14.00
- SI1050E 50 watt RMS amplifier, economy grade.....\$21.00
- Transformer for stereo 10-watt amplifiers (2 lbs.).....\$3.95
- Transformer for stereo 25 or 50 watt amplifiers (5 lbs.).....\$5.95
- Set of (3) 2000 mfd 50V capacitors for 10-watt stereo.....\$4.00
- Set of (3) 2200 mfd 75V capacitors for 25 or 50 watt amplifiers \$5.00
- 4 Amp Bridge Rectifier, suitable for all amplifiers.....\$2.00
- Complete kit for 100 watt RMS stereo amplifier (200 watt music) including two 50-watt Sanken hybrids, all parts, instructions, and nice 1/16" thick, black anodized and punched chassis.....\$88.00
- Same for 50 watt RMS stereo amplifier, includes two 25 watt Sankens, etc.....\$58.00
- Same for 20 watt RMS stereo, includes two 10-watt Sankens, etc.....\$30.00


## ELECTRONIC PRESET COUNTER

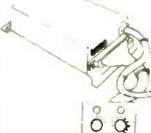

This counter is from a copying machine. It uses two Durant electro-mechanical decade counters, and includes a nice power supply, etc. Two rotary switches allow the unit to be preset with any number from 1 to 50. When the number of pulses in reaches this count, a relay opens, shutting off the controlled unit. Should be useful for coil winders, and other applications requiring shut-off at a predetermined count. The parts alone at our low price represent a "steal", as the unit has high quality switches, silicon rectifiers, transformers, etc.

Preset Electronic Counter (6 lbs.).....\$6.75

## NOW OUT

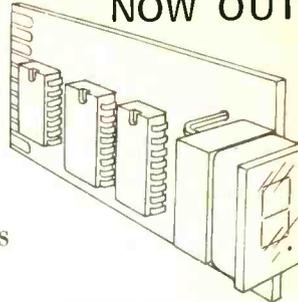

## DCU KITS

### DECADE COUNTING UNITS WITH READOUTS

Always one of B & F's most popular items, now revised to include drilled boards, I.C. sockets, and right-angle socket for readout. Arranged so that units can be stacked side by side and straight pieces of wire bussed through for power, ground and reset. Several different units are available as follows:

- 7490 Basic 10 MHz counter. Used in frequency counters and events.
- 74196 Same as 7490 except presettable 50 MHz unit. Used where higher speed and/or presettable is required.
- 74192 Bi-Directional Counter, 32 MHz operation. Has two input lines, one that makes the unit count up, the other down. Uses include timers, where the counter is preset to a number and counts down to zero, monitoring a sequence of events, i.e., keeping track of people in a room by counting up for entries and down for departures.
- 7475 Adds latch capability. Used in counter so displays continue displaying frequency while new frequency is being counted for uninterrupted display.
- 7447 Basic decoder module. Drives basic seven segment display which is included for all modules.

### NEWEST DCU!

This DCU combines all of the features of our other counting units, that is, high speed counting, up/down operation, storage, and preset. In addition it includes a comparator (7485) and a thumbwheel switch in order to provide comparison and preset capability. With this combination you can do the following:

- 1) Count up or down at speeds to 33 MegaHertz.
- 2) Store previous count during new count.
- 3) Preset to any number, count down (or up) and generate a logic level when count of zero is reached. Stack several units and generate logic level for any count greater than zero.
- 4) Preset to zero, count up (or down) and generate a logic level for any number greater or equal to the number preset in the thumbwheel switch. Stack several DCU's and generate a logic level showing whether number is greater than, equal to, or less than numbers preset on switches.

7490 7447 Counter	\$8.25
7490 7475 7447 Counter	\$9.25
74196 7475 7447 Counter	\$10.25
74192 7447 Counter	\$9.25
74192 7475 7447 7485 Universal DCU	\$14.50

## FUNCTION GENERATOR KIT

IMPOSSIBLE? A \$700.00 function generator for \$99.00? But true! The new, low-cost EXAR-205 monolithic waveform generator makes this price possible. Our kit uses two generator circuits - one is a carrier generator, and produces sine, triangle, square, sawtooth, ramp and pulse waveforms. The second is a modulation generator, for amplitude or frequency modulation of the output waveforms. Output frequency range is from 20 Hz to 1.5 megahertz. Modulation is switch-selectable for internal AM, internal FM, or external modulation.

Model AR-620K Function Generator ..... \$99.00

NEW!  
Available  
February 1, 1973



## EPOXY RECTIFIERS

- 1 Amp 400 Volts 8 FOR \$1.00
- 2.5 Amp 1000 Volts 4 FOR \$1.00

[ ] Send \$.25 for latest super catalog.

### ALL ITEMS WHERE WEIGHT NOT SPECIFIED

POSTAGE PAID IN THE U. S. A.  
Phone in charges to (617) 531-5774 or (617) 532-2323.  
BankAmericard - Mastercard. \$10.00 minimum. No C.O.D.'s please.

CHARGES WELCOME

\$10.00  
Minimum  
Charge




## B. & F. ENTERPRISES

Phone (617) 532-2323

P.O. Box 44, Hathorne, Massachusetts 01937



**ARE PRICES ON ELECTRONICS COMPONENTS REALLY GOING UP?** Of course, no one knows for sure, but we are of the opinion that they are. The recession in the electronics components business is truly over; sales are at a new record. Our, and other "independent distributors" ability to negotiate low prices because of manufacturers' overcapacity is greatly reduced. Many items, such as TTL devices, LED's, and MOS LSI are rationed. Our advice? Place your order now for a good stockpile of components while the hobbyist's paradise still exists.

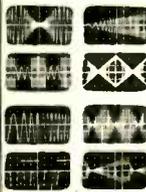

**WAVEFORM GENERATOR, BF-5**  
Just one of these BF-5 devices produces sine, square, triangle, ramp and sawtooth waveforms without additional active components. By adding a second BF-5, you can create amplitude, frequency or phase modulated varieties of these waveforms. They are able to replace large discrete waveform generators costing from \$200.00 to \$1300.00. At the same time, they greatly reduce system weight and power consumption. Full technical data, P.C. layout, assembly, and hook-up instructions included.

BF-5 WAVEFORM GENERATOR..... \$9.75



**GENERAL ELECTRIC PA-234, 1.4-WATT POWER AMPLIFIER..... \$1.25**

This amplifier is housed in a plastic dual in-line package with a tab for heat transfer.


Has only four active terminals, and requires only one capacitor for stabilization. Compatible with 8, 16, or 22-ohm loads. Applications include P.A. systems, phonos, movie projectors, TV, AM and FM receivers. **GENERAL ELECTRIC PA-265, 5-WATT VOLTAGE REGULATOR.** Housed in plastic dual in-line package with staggered leads and power tab. Usable over wide range of input and output voltages, input voltages to 37 volts and outputs from 3 to 30 volts. Usable in a wide variety of circuits.

PA-234 POWER AMPLIFIER \$1.25  
PA-265 VOLTAGE REGULATOR \$1.25

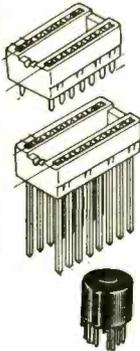**SUPER QUALITY I.C. SOCKETS**


Sockets made by T.I. and Cinch. All are low-profile, compact types.

- 14 Pin Dip Solder Tale Sockets  
3 for \$1.25 16 for \$5.00
- 16 Pin Dip Solder Tale Sockets  
2 for \$1.00 13 for \$5.00
- 14 Pin Dip Gold Wire Wrap Sockets  
2 for \$1.25 10 for \$5.00
- 16 Pin Dip Gold Wire Wrap Sockets  
2 for \$1.50 8 for \$5.00
- 10 Pin To-5 Gold Sockets (Cinch)  
2 for \$1.00 13 for \$5.00



**SINGLE CHIP 7-SEGMENT DISPLAY COUNTER, AND DECODER.** That's right!

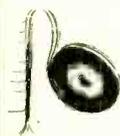A single chip TTL decade counter with latches, BCD outputs, a 7-segment decoder driver, AND a 7-segment LED display (with decimal) on top. Only 0.15" thick (not counting pins), the chip mounts in a standard 16-pin DIP socket. Digits are 0.270" high and can be latched in during the next count or blanked.  
0.27 DLD ..... \$15.00



**SPECTRA - STRIP FLAT BONDED**

We know this is what everyone wants for their home-brew projects, because they always ask for it. We now have over 5 by 10<sup>6</sup> feet, but it won't last long, so order now before it's all gone. We don't want any broken hearts. Specs: 20 conductors, 24 AWG, 7 strands, size is .88" x .044". We could give all its virtues, but most people know them or could easily look it up in any industrial electronics house catalogue.

Sh. Wt. 1 lb./10 feet... Order No. SSFBRC (ft.)  
Price: \$35/1 ft. \$1.00/3 ft. \$5.00/18 ft.  
\$30.00/100 ft. \$55.00/200 ft. \$100.00/400 ft.  
\$200.00/900 ft. \$500.00/2000 ft.



**70 WATT RMS AUDIO AMPLIFIER BASIC PACKAGE. STEREO \$5.50**

Take advantage of Signetic's NE540 power driver, (class AB amp). Designed for 35 watts RMS per channel. Distortion .5% frequency response, ±.5db 20Hz to 100Hz. NE540 requires two power transistors, a 2N5296 (NPN) and a 2N6109 (PNP), supplied per NE 540. Kit package includes (2) NE540, (2) 2N5296, (2) 2N6109, information on P.C. board layout, parts and circuitry, and a list of miscellaneous small parts required to build the 70 watt amplifier for stereo.

- NE540 \$2.25/ea.
- 2N5296 35 watt NPN .75/ea.
- 2N6109 40 watt PNP .75/ea.
- 70 watt Stereo Kit \$5.50/ea.
- 35 watt Mono Kit \$2.95/ea.

**HARD-TO-GET DIGITAL I.C.'s SALE**


- 7447 BCD To-7 Segment Decoder Driver \$1.06
- 7490 Decimal Counter..... \$ .76
- 7485 Comparator..... \$1.25
- 74192 Up-Down Counter..... \$1.45
- RCA CD4001 Quad 2-Input Nor Gate (Cosmos)..... \$1.25
- RCA CD4007 Complementary Pair & Inverter..... \$1.50
- RCA CD4010 Hex Buffer..... \$1.50

**MISCELLANEOUS SEMICONDUCTORS, SALE**

- MUS 4988 Silicon Uni-lateral Switch. Useful for voltage-sensitive switch, sweep generators, etc. \$1.00
- MUS A65 PNP High-Current Darlingon Transistor. Super high gain in a small package. 2/\$1
- MPS A14, NPN, SAME AS ABOVE 2/\$1.00

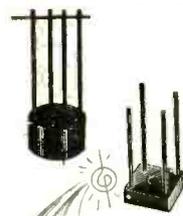**COMPACT BRIDGE**

- 2 Amp 200 Volt \$ .60
- 2 Amp 400 Volt \$1.00
- 2 Amp 600 Volt \$1.50
- 2 Amp 800 Volt \$2.00
- 2 Amp 1000 Volt \$2.50
- 4 Amp 400 Volt \$1.50
- 4 Amp 600 Volt \$2.00
- 4 Amp 800 Volt \$2.50



**PLASTIC FIBER OPTICS.**

Plastic optical monofibers are conveniently card-mounted and available in five different fiber diameters. Excellent supplement for B and F Fiber Optic Kits to provide additional fiber optic material. Fibers available in diameters of .005" (250 ft. card). Offer design versatility to R&D and product engineers. Specifications - maximum cont. oper. temp. - 170 degrees Fahrenheit, acceptance angle - 67 degrees, numerical aperture - 0.55, transmission range - 0.4 to 1.5 microns. YOUR CHOICE - \$1.00

**TIMER, 0 to 2.75 MINUTES GENERAL TIME.**

New packaged timers, for 115V, 60 Hz. Timer is set for 2.75 minutes (165 seconds) of operation. At the end of operating cycle, a SPDT switch is closed. May be reworked to provide any time delay between 0 and 2.75 minutes. Makes a useful lab or sequence timer. Latest design with current list price of \$15.00

Sh. Wt. 1 lb. TGT \$2.75 ea.  
2TGT \$5.00/2

**SGS TAA 621 AUDIO AMPLIFIER**

I.C. audio amplifier in 14 pin DIP package, provides up to 4 watts power with proper heat sink, and 28 Volt supply. Can be used at 12 Volts with reduced output power. - \$1.95 ..... 6 for \$10.00

**LOGIC AND OPERATIONAL AMP SUPPLIES**



- Figure A, potted logic supply, 5 Volts at 1 Ampere, short circuit proof, ultra high regulation, ultra low ripple ..... \$16.00
- Figure A, potted Op Amp supply, +15 Volts, and -15 Volts at 0.5 Amperes. Mfg. by Analog Devices, similar to their model 902. Short circuit proof, ultra high performance. .... \$29.00
- Figure B, 5 Volt 1 Amp supply, regulated by Fairchild 9305, short circuit protected. .... \$9.75
- Same as above, in kit form ..... \$7.75
- Mating connector for above ..... \$1.00
- 5 Volt 5 Amp regulated supply, by Blulyne, (not shown). .... \$29.00



**CALCULATOR CHIP SPECIAL!!!**

One of the largest manufacturers of MOS Integrated Circuits has discontinued his three-chip set in favor of a single chip. This is the hobbyist's gain, since he can now obtain this fully tested, highly flexible set at a fraction of what even the largest calculator manufacturers pay. Consists of three 24-pin I.C.'s, has debounced input, eight-digit capacity, decoded seven-segment output. Full data included. 8-Digit Floating-Point Calculator Set.....\$9.75



**FAIRCHILD VOLTAGE REGULATORS**

This is the UA 7800 Series. Three terminal regulator, with thermal overload protection and internal current limiting, making it essentially blow-out proof. Because simple circuitry is used with this device, designing regulated power supplies is duck soup. Output is rated at 0 to 1 ampere; maximum input voltage is 35 volts. Choice of voltages: 5, 6, 8, 12, 15, 18, or 24 Volts. Order as 7805, 7806, 7808, etc.

Voltage Regulator (Specify Voltage).....\$2.00



**SHRINK TUBING.**

B and F has a truckload of shrink tubing, but we still expect it to go fast. If you have ever used shrink, you know it is indispensable for electronic construction. Made a wire too short? Just splice and shrink tubing over it and it will look like new. Pins too close? Same solution. Excellent results with hot-air gun, soldering iron, or even a match. This is polyolefin type where outer wall shrinks, inner wall melts to encapsulate wire.

SHRINK TUBING ASSORTMENT, 25 feet each, of 1/8, 3/16, 1/4-inch tubing ..... \$5.00

**SPECIAL I.C.'S, PHASE LOCKED LOOPS**

- NE560 Phase Locked Loop ..... \$4.65
  - NE561 Phase Locked Loop ..... \$4.65
  - NE562 Phase Locked Loop ..... \$4.65
  - NE565 Phase Locked Loop ..... \$4.65
  - NE566 Function Generator/Tone Encoder. .... \$4.65
  - NE567 PLL/Tone Decoder ..... \$4.65
  - NE595 Four Quadrant Multiplier. .... \$3.75
  - NE555 Timer, 2u Sec to 1 hour, Special... \$1.25
- [ ] Send \$.25 for latest Catalog.

ALL ITEMS WHERE WEIGHT NOT SPECIFIED

POSTAGE PAID IN THE U.S.A.  
Phone in charges to (617) 531-5774 or (617) 532-2323.  
BankAmericard - Mastercharge. \$10.00 minimum. No C.O.D.'s please.



\$10.00 Minimum Charge



**B. & F. ENTERPRISES**

Phone (617) 532-2323  
P.O. Box 44, Halthorne, Massachusetts 01937

CHARGES WELCOME

# NO COMPETITORS

Nobody else but **EMC** designs in so much value



Tube Tester Model 213

Compact, light-weight portability. Use it on the bench or in the field.

Full-view meter gives direct, clear-cut quality indications.

Three heavy-duty controls for quick set-up of all tests. Check a fistful of tubes in the time it often takes to test one.

12 slide switches for individual selection of tube pins provides versatility in testing, prevents obsolescence.

Full complement of sturdy sockets accepts compactron (12-pin), nuvistor, novar, 10-pin, 9-pin, octal, loctal, and miniature tubes.

Precise programming. Only one socket per tube-base configuration prevents accidental plug-in.

THE MODEL 213 saves you time, energy, money ■ Checks for shorts, leakage, intermittents, and quality ■ Tests all tube types including magic eye, regulator, and hi-fi tubes ■ Checks each section of multi-purpose tubes separately ■ Gives long, trouble-free life through heavy-duty components, including permanently etched panel ■ Your best dollar value in a tube tester. Available in high-impact bakelite case with strap: \$36.90 wired; \$23.90 in kit form. Wood carrying case (illustrated) slightly higher.

EMC, 625 Broadway, New York 12, N.Y.  
Rush me FREE catalog describing all EMC value-loaded test instruments and name of local distributor.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_


CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

RE-1




ELECTRONIC MEASUREMENTS CORPORATION  
625 Broadway, New York 12, New York

## COMPUTER BOARD MONTH

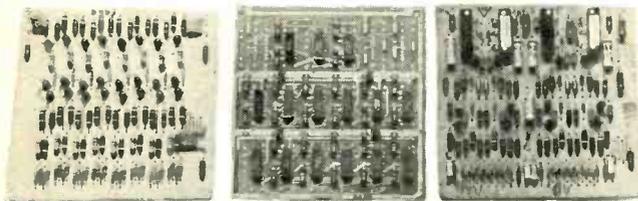

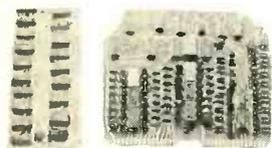Three boards, one loaded with transistors, one loaded with integrated circuits, and one with from two to five trimpots, all with diodes, capacitors, and many other components. Each board 5½" x 5½".  
STOCK NO. J9380, 3 boards as above, \$2.00. 9 boards, \$5.00



### NEW FAIRCHILD TTL, DTL, MSI IC BOARDS

BRAND NEW computer boards, with 31 FAIRCHILD ICs, 32 MOTOROLA 2N4401, 32 FAIRCHILD 2N2369A, all marked,

for a total catalog value of over \$108.00. Hex inverters, gates, flip flops, 2 One of ten decoders, a dual full adder (MSI). Six pulse transformers and many more components. An unusual set of two boards. Sockets available (2 per board).

STOCK NO. J9421 2 Boards as above, \$6.50 2 sets \$12.00  
STOCK NO. J9422, set of 4 sockets (edge connectors) \$1.00

### AN OLD FAVORITE, "HONEYWELL BOARDS"

New lot of HONEYWELL boards, 4½" x 12". Loaded with all kinds of components.

STOCK NO. J9082 2 different boards, \$1.00, 12/5.00



Include sufficient postage, excess will be refunded. Send for new 48 page catalog loaded with other items. Minimum order \$3.00



**DELTA ELECTRONICS CO.**


BOX 1, LYNN, MASSACHUSETTS 01903  
Phone (617) 388-4705

Circle 86 on reader service card

# try this
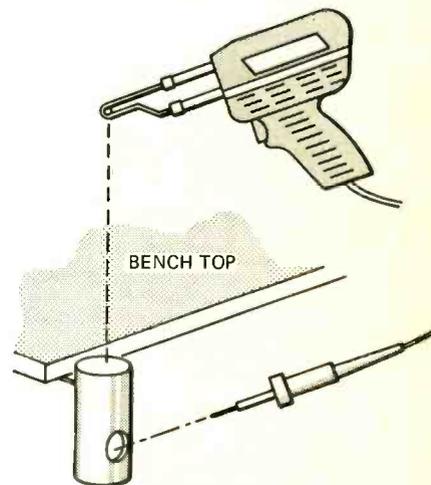
## SOLDERING GUN HOLDER

Here is a soldering gun holder that swings out of the way when not in use. It also serves as a soldering-pencil holder and holds both instruments at the same time. It consists of a piece of brass pipe (kitchen sink or face bowl drain) and an angle bracket assembled




as shown in the drawing. Drill a hole near the bottom edge of the pipe for a pencil iron—you need only one hole because the pencil iron goes in the side and comes out the bottom. Mount the holder under the edge of the bench where it can be moved out of the way when not in use.—J. F. Harris R-E

For  
faster  
service

USE  
ZIP  
CODE

on  
all  
mail

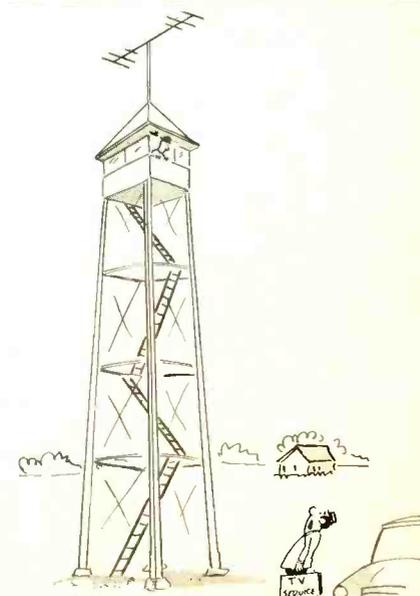

"Bring your TV down, \$10.00. If I go up there, \$50.00."



## U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

### 23-Channel, 5-Watt, CB Base Station Transceiver



Limited Sale\*

List Price \$149.95 Reg. Catalog \$109.90 **\$99.90**

• (ITEM #M13-891-RE) - Special savings on CB Base Station Transceiver ideal for Contractors, Construction Co's., Road Builders, etc. Full legal power (5-watts) gives you dependable radio contact with all your CB equipped vehicles in the field. Equipped with crystals for all 23 CB channels, none extra to buy! Latest design, solid state circuitry for trouble-free performance, long range, exceptional clarity.

• Operates on 110-VAC, equipped with complete controls; on-off-volume, illuminated channel selector, full variable squelch, transmit/modulate indicator light. Built-in 4" x 2 1/2" dynamic speaker. Dynamic microphone with coil cord furnished. Jocks provided for microphone, external speaker, external antenna. 11" x 7 1/2" x 4 1/2". (10 lbs.)

### IBM COMPUTER POWER SUPPLY

• (ITEM #22-984) - Expensive, regulated unit. Fine for college labs, research co's., service shops, etc. Pure DC over a wide range of voltages. DC output voltages 6, 12, 48, etc. Wide range of AC voltages available.

• Finest transformers, filters, transistor load regulation system. Independent of line voltage fluctuations. Contains five separate rectifier systems. Unit is furnished without small "regulating card" which can be easily made or can be by-passed. Data and circuit diagrams furnished. 30" x 12" x 10". (125 lbs.)

Cost Gov't Over \$500.00 **\$24.95**

ONCE-IN-A-LIFETIME SPECIAL



### STANDARD DIAL TELEPHONE

• (ITEM #715) - Standard, commercial telephone same as used throughout U.S.A. Attractive polished black, like new condition. Use as extension phone to private systems or connect several phones together for local intercom system. Full instructions are furnished. Wt. 9 lbs.



Original Cost \$24.50 **\$8.79**

### STEP-BY-STEP TELEPHONE SWITCH

• (ITEM #738) - Amazing telephone selector switch. Great experimental item. When used with two-wire telephone dial will select any number from 0 to 100. Make intercom or private system. Use to turn on remote lights, start motors, etc. Complete with contact bank. 13" x 6" x 5". (16 lbs.) Cost Over \$90.00



**\$8.95**

• Telephone dial for use with above switch. Order as (Item #700)..... **\$1.97**

### 200 AMP., 50 VOLT, SILICON DIODE

• (ITEM #22-963) - A Four Star Buy! New, leading make. Heavy duty units excellent for use in 12 or 24-volt fast chargers, high current power supply systems, etc. 2 1/2" x 1 1/2" x 1 1/4". 3/16" - 16 S&C mounting threads. (1 lb.)

List Over \$15.00

**\$4.99**

### SPECIAL SALE Correspondence Course In

#### ELECTRICAL ENGINEERING



**\$8.79** Prepaid in U.S.A.  
**\$10.79** Outside U.S.A.

• (ITEM #A180) - Obtain technical training at low cost! Lincoln Engineering School has suspended its Correspondence Courses because of rising costs. A limited number of Electrical Engineering Courses are available, but without the examination grading service. The course consists of 15 lesson books, each with associated exams and standard answers. Book describing prize winning Home Experimental laboratory Bench furnished at no extra cost.

### RUNNING TIME METER

• (ITEM #2188) - Record number of operating hours of electric lights and electrical devices such as refrigerators, furnaces, etc. Records total hours, tenths and hundredths up to 9,999.99 hours. For 115-volt, 60-cycle. Size 4 1/2" x 3" x 2 1/4". Shipping weight 2 lbs.



**\$4.39** Cost Over \$29.00

### COMPUTER TRANSISTORS ON HEAT SINKS

IBM Computer Quality Units

• (#22-918) - Unit consists of two 150-watt power transistors, 2 pots, several diodes, capacitors, resistors, etc. on heavy, ribbed aluminum heat sink. Ideal for use as motor speed control. (4 lbs.)



Cost Gov't Over \$35.00 **\$4.91**

All Items F.O.B. Lincoln, Nebr.  
Order Direct From Ad. Money Back Guaranteed.

**SURPLUS CENTER**

Dept. RE-013, Lincoln, Nebr. 68501

# market center

## ELECTRONICS ENGINEERING & INSTRUCTION

FREE brochure. FCC license. Key Tests-Answers. **ACADEMY OF COMMUNICATIONS TECHNOLOGY** RE-173, Box 389, Roswell, NM 88201

**TV TUNER REPAIRS**—Complete Course Details. 12 Repair Tricks. Many Plans. Two Lessons, all for \$1. Refundable. **FRANK BOCEK**, Box 3236 (Enterprise), Redding, CA 96001

**AVIATION ELECTRONICS TECHNICIAN**—Prepare for exciting career in new field of "Avionics". Train at nation's largest aeronautical school. Indicate if eligible for G. I. Benefits. **SPARTAN AIRSCHOOL**, International Airport, MNW, Tulsa, OK 74151

**SHORTCUTS To Success!** Highly Effective, Profitable Short Courses. (75 Choices). Study At Home. Diploma Awarded. Our 27th Year. Free Literature. **CIEE-E**, Box 10634, Jackson, MS 39209

**HIGH SCHOOL DIPLOMA** for adults. Earn State Diploma. Accepted by Civil Service, business, colleges. Low cost. No tedious study. Money-back guarantee. DETAILS: **H-S PROGRAM**, Suite 2507, 1221 Avenue of Americas, New York, NY 10020

## TAPE & RECORDERS

**RENT** 4-track open reel tapes—all major labels—3,000 different—free brochure. **STEREO-PARTI**, 55 St. James Drive, Santa Rosa, CA 95401

## PLANS AND KITS

**CONVERT** any television to sensitive big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **RELCO-A25**, Box 10563, Houston, TX 77018

**ANTIGRAVITY DEVICE**. Brochure rushed free. **AGD**, Box 3062-RE, Bartlesville, OK 74003

**ELECTRONIC ORGAN KITS, KEYBOARDS** for music synthesizers and organs. Independent and divider tone generators, diode keyer systems. I. C. circuitry. Many components. 25¢ per catalog. **DEVTRONIX ORGAN PRODUCTS**, Dept. B, 5872 Amapola Drive, San Jose, CA 95129

**FREE Kit Catalog:** Scramblers, Tone Encoders and Decoders, Alarms, Sounders, Automatic Telephone Recorder Phone Patch, IC Kits and more **KRYSTAL KITS**, Hwy 102 East, Bentonville, AR 72712

## FOR SALE

**FREE catalog** New Electronic Devices! World's Smallest Transmitter \$19.95! Telephone Answerer \$49.50! Telephone Recording Device \$19.95! "Bug" Detector \$59.50! Many more! **SONIC DEVICES**, 69-29R Queens Blvd., NY 11377

## BUILD A "SPACE-AGE" TV CAMERA!


ONLY KNOWN SOLID-STATE CAMERA IN KIT FORM! Also available factory assembled. • Ideal for experimenters, industry, education, etc. • High quality performance backed by over seven years of lab and field testing. • Fully Guaranteed. • Completely self-contained. • Connects to any TV set without modification. • Easy-to-follow assembly manual. • Model XT-1A, Series D complete with vidicon tube \$116.95 pp. Many other kits, parts and plans also available.

PHONE or WRITE for CATALOG... DIAL 402-987-3771

BOX 453-RE **ATV Research** DAKOTA CITY, NEBR. 68731

**GIANT B-7971 NIXIES (2)** with 2 sockets and driver board containing hi voltage transistors. Complete plug-in board as removed from operational equipment. Schematics included. Unbelievable but true . . . just \$2.50 for the complete package.

#72S-10 **\$2.50**

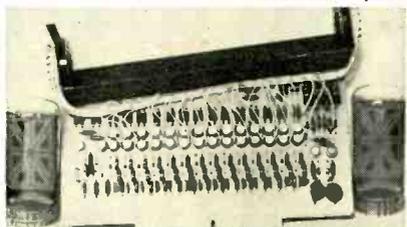

**ALPHA-NUMERIC keyboard** removed from unused IBM Selectric machines. Bargain price at only \$8.00



### 15 IC BONANZA

Brand new DTL dual inline (DIP) package, factory marked ceramic type. The price is too good to be true. Fully guaranteed and with specs.

930 Dual 4 input NAND gate similar to	7420
931 Clocked flip flop	74110
932 Dual 4 input Expand Buff	7440
933 Dual 4 input expander	7460
936 Hex Inverter	7405
945 JK Flip Flop	74110
946 Quad 2 input gate	7400
962 Triple 3 input gate	7410

15¢ each. Buy \$100 worth and deduct 10% 24 hour delivery guaranteed.

Please add postage for above.

JOHN MESHNA JR.

PO Box 62, E. LYNN, MASS. 01904

Circle 89 on reader service card

CB Two-Way radios—SBE's 23 Channel-mobile transceiver. All Crystals Supplied. Fully Warranted. \$99.95 check or M.O. (information on request), **CB RADIO EQUIPMENT**, P.O. Box 611, Fairfield, CT 06430.

FREE Catalog lists resistors, tubes, transistors, rectifiers, condensers, tools, tuners, etc. etc. **Hytron Hudson**, Dept. RE 2201 Bergenline Ave., Union City, NJ 07087.

PHOTOFLASH: FT 106C, 800 $\mu$ F, trigger coil—\$12.50. Catalog. **TRANSPARK** Dept. R., Carlisle, MA 01741

ELECTRONICS Parts \$25 Bonanza \$7.65 P.P. **DIAMOND** Box 5542 Toledo, OH # 43613

PREFINISHED aluminum enclosure, 15Vdc@25MA supply, Universal printed board, toggle switch, cord, Full line Brochure; for professional projects \$24.00; **INSTANT INSTRUMENTS**, 306 River Street, Haverhill, MA 01830

RECORD TELEPHONE CONVERSATIONS AUTOMATICALLY. LEAVE RECORDER UNATTENDED. **ROBERT'S BOX 49RE**, PARKRIDGE, IL 60068

LOGIC Probe with LED display \$20.00 post-paid U.S. Order from **UTI** POB 252 Waldwick, NJ 07463

EXPERIMENTERS. Find out how to tell type of transistors on surplus IBM boards without test equipment. Send \$1.00 for booklet Tran-25, **RESTEK**, 525 Copper Ridge, Richardson, TX 75080

HOBBYISTS-RIDICULOUS PRICES IC's, transistors, diodes, capacitors, chassis, solder, wire terminals, etc. **FREE CATALOG H & R INDUSTRIES** P O 413 Tewksbury, MA 01876

EVERYTHING IN SEMICONDUCTORS YOUR CHOICE FROM OVER 300 POPULAR DEVICES. IF YOU DON'T SEE IT HERE, ASK FOR IT.

PART #	MOTOROLA REF	DESCRIPTION	CASE STYLE	PRICE 1-89
D3	103	Zener Diode 6.2V 1W 5%	DO-7	\$.70
D4	104	Zener Diode 9.1V 1W 5%	DO-7	.70
D5	105	Zener Diode 12V 1W 5%	DO-7	.76
D7	135	GE Diode 1N60 Subst.	DO-7	.16
D8	165	Sel Dual Diode Com. Cathode	8	.38
R2	153	SI Pwr Rect 200V 15A	DO-4	1.32
R7	159	SI Rect Ax lead 800V 2.5A	DO-41	.40
R9	161	SI Rect Ax lead 50V 3A	20	.66
R11	170	SI Rect Ax lead 1000V 2.5A	DO-15	.55
R47	100	B- Boost Rectifier 800V	—	.60
R49	—	6500 volt Focus Rectifier	30	1.20
GT3	3	GE RF Tr PNP 250 MHZ	TO-18	.77
GT6	231	GE Pwr Tr PNP 15A	TO-36	1.36
GT7	232	GE Pwr Tr PNP 7A	TO-3	1.65
GT8	233	GE Pwr Tr PNP 15A	TO-36	2.97
GT9	652	GE Audio Ampl. PNP	TO-5	1.10
GT36	639	GE Drift-Field PNP	TO-18	.99
GT38	641	GE RF Ampl. NPN	TO-5	.88
GT40	643	GE Audio Pwr Ampl. PNP	TO-66	1.15
ST2	51	SI RF Tr PNP 150 MHZ	TO-5	.77
ST5	54	SI RF Tr NPN 30 MHZ	TO-5	.66
ST6	55	SI RF Tr NPN 200 MHZ	TO-92	.70
ST7	56	SI VHF Osc. NPN 750 MHZ	TO-92	.88
ST11	240	SI Pwr Tr NPN 300V 10V	TO-66	1.20
ST14	243	SI Med Pwr Tr NPN 60V 3A	TO-5	1.10
ST17	246	SI Med Pwr Tr PNP 60V 3A	TO-220	1.32
ST18	247	SI Pwr Tr NPN 70V 10A	TO-3	1.70
ST20	310	SI Unijunction Tr 300mW	TO-92	.99
ST25	703	SI Audio Pwr Ampl. NPN	TO-66	1.76
ST28	704	SI Audio Pwr Ampl. NPN	TO-3	1.43
ST42	721	SI Audio Ampl. PNP 800 MHZ	TO-92	1.50
ST69	3001	SI RF Pwr Tr NPN 65V 5W	TO-5	2.30
FET1	801	Fet Audio N Channel	TO-46	.99
FET2	802	Fet RF N Channel	TO-46	.99
FET3	803	Fet Audio RF P Channel	TO-46	2.10
TH5	320	Thyristor (SCR) 30V 800ma	TO-18	.60
BR1	175	Full Wave Bridge 50V 3A .750/.800Rd	60	

Terms: Add 25¢ for postage Minimum Order 2 Dollars. Send 10¢ for Complete catalog.

**GF Electronics**  
P.O. Box 14  
Greenwood, Mass. 01880

Circle 90 on reader service card

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services) \$1.00 per word . . . minimum 10 words.  
NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 70¢ per word . . . no minimum.  
FIRST WORD and NAME set in bold caps at no extra charge. Additional bold face at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for March issue must reach us before Dec. 29.

### CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .70 Non-Commercial Rates } = \$ \_\_\_\_\_  
                  { @ \$1.00 Commercial Rate } = \$ \_\_\_\_\_  
                  No. of Words in bold caps @ .10 = \$ \_\_\_\_\_

Total Enclosed \$\$ \_\_\_\_\_

Insert \_\_\_\_\_ time(s)

Starting with \_\_\_\_\_ issue

Payment must accompany order unless placed through accredited advertising agency 28

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 200 PARK AVE. SOUTH, NEW YORK, N.Y. 10003




# FREE

**SUTTE** CATALOG
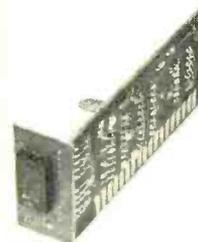
## Winter Readout Sale

Our super versatile LED readout counter kit with MAN-1 type readout, plug-in construction, parallel inputs and latch storage circuit. Get yours and build that digital instrument now during this special sale. Circuit board readout and three IC's only



**\$9.95**

Limit 4 per customer with copy of this ad only.

## CLOSE OUT

LIMITED QUANTITY—150 Watt RMS Stereo Power Amplifier. Two of our "Universal Tiger" amplifiers with two separate power supplies built into a 5 1/4 inch relay rack panel. Completely assembled, tested and guaranteed. Pilot production run showed that redesign was needed to reduce assembly cost, so we are offering these at a clearance price of \$175.00. . . . Shipping weight 30lbs.



## LIMITED QUANTITY

Battery Charger Kits—6 & 10 Amp. Just the thing to keep the battery in your car or truck in peak condition during the cold months. This heavy duty charger has a steel case, full wave rectifier, automatic circuit breaker, insulated copper battery clamps and many other deluxe features. Wiring is all push-on terminal for easy construction. You only will need a screwdriver.

Kit #B-6 6 Amp **\$11.90** 10 lbs.  
Kit #B-10 10 Amp **\$15.90** 12 lbs.



**SOUTHWEST TECHNICAL PRODUCTS CORPORATION**

DEPT. RE


219 W. Rhapsody, San Antonio, Texas 78216

Circle 91 on reader service card

# IC PRICES SLASHED
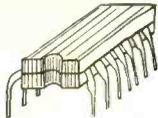
## FACTORY FIRSTS

NATIONALLY KNOWN BRANDS SATISFACTION GUARANTEED



DIGITAL TTL	
7400N	22¢
7401N	22¢
7402N	22¢
7403N	22¢
7404N	24¢
7410N	22¢
7420N	22¢
7430N	22¢
7440N	22¢
7441N	\$1.20
7442N	\$1.15
7447N	\$1.02
7451N	22¢
7453N	22¢
7454N	22¢
7472N	35¢
7473N	46¢
7474N	42¢
7475N	72¢
7476N	50¢
7486N	52¢
7490N	72¢
7492N	72¢
7493N	72¢
7495N	\$1.05
74107N	47¢
74121N	51¢

"5% OFF TTL IC PRICES AT 100 PCS TTL ICS MIXED.

### LINEAR INTEGRATED CIRCUITS

DIP or TO-5 709...38¢, 10/\$3.50, 710...38¢, 10/\$3.50, 741...40¢, 10/\$3.70, 748...43¢, 10/\$3.95 TO-5 only 723...90¢, 10/\$8.25, Dual 741 (558) TO-5 90¢, 10/\$8.25, Dual 741 (558) Mini-DIP 75¢, 10/\$6.75 LM 309K TO-3 \$2.25 5/\$10.00

### GENERAL PURPOSE TRANSISTORS

2N5134 Si NPN or 2N5138 Si PNP...15¢ 8/\$1.00  
2N3055 Si NPN Power .....\$1.00 10/\$9.50

### 1 AMP SILICON SUBMINIATURE RECTIFIERS

1N4001 50 PIV, 1N4002 100 PIV, 1N4004 400 PIV 1N4005 600 PIV.....10/\$1.00, 100/\$7.50  
1N4007 1000 PIV ..... 7/\$1.00, 100/\$9.95

### SILICON SIGNAL DIODES

1N4148 (1N914 equiv.) ....20/\$1.00, 100/\$4.00

### RTL INTEGRATED CIRCUITS

uL900, uL914 & uL923 Mix \$5/\$1.00, 100/\$15.00

### READOUT TUBES

5 Volt 7 Segment Readout Tube \$2.95. Counting and Display Kit (Readout Tube +7490+7475+7447) \$5.25, 3 Kits for \$15.00

### 1/2 WATT 10% RESISTORS

Pick Values 4¢ 25/75¢ 100/\$2.50 500/\$11.25

Free Catalog—Large Quantity Discounts—Orders Less Than \$10.00 Add 25¢—Others Postpaid

## DIGI-KEY

PRICE PACESETTER FOR QUALITY IC'S

BOX 126H

THIEF RIVER FALLS, MN56701

Circle 92 on reader service card

**A NEW INSTRUMENT TO USE WITH YOUR SCOPE**

### MULTITRACER

Use with your present Oscilloscope to trace Resistor, Capacitors, Transformers, Diodes, Transistors, Zeners, Triodes, most Semiconductors, IC's, etc. • Also shows continuity, in-circuit and go/no go checks. • Complete with diagrams and instructions. No internal scope connections. • For mediums or small production runs or for hobbyist, experimenter, engineer, or ham.

ONLY \$19.95—CHECK OR MONEY ORDER W-I-V PAY MORE!

BOX 14, LESCO ELECTRONICS, SKOKIE, ILL. 60076

## Technical Excellence in Electronics.

On our small, friendly campus the emphasis is on Living as well as Learning. Extra-curricular social activities, student clubs, a student operated radio station, student government, new dormitory and a full sports program help provide a world of your own in which to prepare for tomorrow. Associate Degree in Engineering Electronics, B.S. obtainable, G.I. approved.



**VALPARAISO TECHNICAL INSTITUTE**

Dept. C, Yellowstone Trail, Valparaiso, Indiana 46383

## Brand New First Quality COMPONENTS

below manufacturer's prices

### TEFLON WIRE & CABLE at PVC prices

Introductory Offer:

Ten 50 ft. rolls, assorted colors, single conductor—  
#18 or 20 .....\$18.00 per asst.  
#22 thru 32 .....\$11.00 per asst.

### SHIELDED TEFLON CABLE

Smooth Teflon jacket over all—ideal for snaking long runs. 50 ft. rolls.

1 con. #18	\$ 4.00
1 con. #22, 26 or 30	\$ 3.00
2 con. #18, thru 26	\$ 9.00
3 con. #18 thru 26	\$12.00
4 con. #22 and 24	\$18.00

### SPECIAL!

### TANTALUM CAPACITORS

Stock up with mil grade, hermetic sealed, low leakage capacitors below ordinary aluminum cost. 40 standard values from 1 to 100 mf. \$10.00 per asst.

### RELAY SALE! \$1.50 each

12 vac dpdt	120 vac spst
24 vac 4pst	12 vdc 4 pdt
24 vdc 4pdt	125 vdc 6 pdt

Reed Relay 12-24 vdc spst—All 7 for \$9.00

### POWER SUPPLY KITS

Everything you need to D.C. power your next project—from 9 to 90V, \$4.95 and up. Write for listing.

Terms: Send check or MO with order for ppp shipment. Rated firms: Net 30 days

## NUTMEG

ELECTRONIC SALES

235 WEST STATE STREET  
WESTPORT, CONN. 06880 (203) 227-2800

Circle 93 on reader service card



NOW build your own Capacitor Discharge Ignition System for as little as \$11.45! Circuit diagram included with special ignition transformer.

TR-200 transformer  
6 or 12 volts 11.45

Complete COMPAC KIT  
6 or 12 volts 25.95

(as described in

POPULAR ELECTRONICS—Nov. 1966)

FREE LITERATURE on all SYDMUR "CD" Systems.

SYDMUR—1268 E. 12 St.,  
Brooklyn, N.Y. 11230

### TRANSISTOR TESTER

"IN CIRCUIT"—Model 85

\$19.95 Prepaid

Places transistor into actual operation. Operates upon contact. Clear speaker tone—no visual observations to make. Tests transistors in or out of the circuit. Money back guarantee.

Extender Cable Included with Tester

UNITED SALES, DEPT. 8690  
BRIGHTWOOD, WASHINGTON, D.C. 20011

## F.C.C. EXAM MANUAL

The Original Test-Answers exam manual that prepares you at home for FCC First and Second class licenses. Includes Updated multiple choice tests and key Schematic diagrams. PLUS - "Self-Study Ability Test." -- ONLY: \$9.95 Postpaid

COMP. AND PRODUCTIONS P.O. BOX 26348 - E  
RADIO ENGINEERS DIVISION SAN FRANCISCO, CALIF. 94126

## ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

READER SERVICE CARD NO.	PAGE
21	Alarm Device Mfg. Co..... 78
	Amperex..... 2
85	Aries, Inc..... 103
	Bell & Howell Schools..... 18-21
79	B.F. Enterprises..... 99
81	B.F. Enterprises..... 101
12	B & K, Division of Dynascan Corp..... 27
76	Brooks Radio & TV Corp..... 90-91
1	Castle TV Tuner Service, Inc..... Cover II
66	Channellok, Inc..... 85
14	Cleveland Institute of Electronics..... 64-67
	CREI, Division of the McGraw-Hill Continuing Education Co..... 46-49
11	Crown International..... 26
86	Delta Electronics..... 102
82	Delta Products, Inc..... 100
64	Dictaphone Corp..... 84
87	Edmund Scientific Co..... 110
83	Electronic Chemical Corp..... 98
84	Electronic Distribution, Inc..... 98
75	EICO, Electronic Instrument Co..... 90, 91
	EMC, Electronic Measurements Corp..... 102
9	Electro-Voice, Inc..... 22
72	John Fluke Mfg. Co., Inc..... 88
70	Fordham Radio Supply Co..... 87
74	GC Electronics..... 89
	Grantham School of Engineering..... 92-95
	GTE Sylvania Electronic Components... 7, 69
100	Heath Co..... 24-25
18	Indiana Home Study Institute..... 72
19	International Crystal Mfg. Co..... 72
20	Jerrold Electronics..... 73
71	Lafayette Electronics..... 87
62	Leader Instruments..... 83
6	Micro-Instrumentation Telemetry Systems, Inc..... 15
16	National Camera Supply Co..... 70
	National Radio Institute..... 8-11
	National Technical Schools..... 74-77
4	Olson Electronics..... 13
	Panasonic..... Cover III
78	Pennwood Numechron..... 96
77	PTS Electronics, Inc..... 96
13	Quam-Nichols..... 32
22	Quietrole..... 78
10	Radio Shack..... 23
	RCA Institutes..... 28-31
15	RCA Parts & Accessories..... 70
23	RCA Electronic Components Test Equipment..... 79
73	Rye Industries, Inc..... 88
25	Sams & Co., Howard W..... 81
68	Schober Organ..... 86
2	Shure Bros..... 1
61	Sonar Radio..... 82
8	Sony Corp. of America..... 17
80	Sprague..... 97
63	Telematic..... 84
24	Telex..... 80
7	Triad-Utrad Distributor..... 16
69	Tri-Star Corp..... 86
3	Tuner Service Corp..... 5
67	TV Tech Aids..... 86
65	Warner Paperback Library..... 85
88	Winegard..... Cover IV
5	Xcelite..... 14
	MARKET CENTER..... 104-109
	ATV Research Corp..... 104
	Barta-DREI..... 107
	Command Productions..... 106
	Digi-Key..... 106
	Fair Radio Sales..... 109
90	G.F. Electronics..... 105
	Lakeside Industries..... 107
	Lesco Electronics..... 106
89	Meshta Electronics, John Jr..... 104
93	Nutmeg Electronic Sales..... 106
	PAIA Electronics..... 109
	Polypaks..... 108-109
94	Solid State Sales..... 107
91	Southwest Technical Products..... 105
	Southwest Technical Products..... 109
	Surplus Center..... 104
	Sydmur Electronics..... 106
	United Sales..... 106
	Yeats Appliance Dolly Sales Co..... 109
	SCHOOL DIRECTORY..... 106
	Valparaiso Technical Institute..... 106

**ELECTRONIC Ignition**—Various Types. Information 10¢. **ANDERSON ENGINEERING**, Epsom, NH 03239

**B & K**, Sencor test equipment, discount prices. Free catalog and price sheet. **FORDHAM RADIO**, 265 East 149th Street, Bronx, NY 10451

**FREE CATALOG OF ELECTRONIC BARGAIN PARTS**, SEND TO: **KNESS ELECTRONICS** 3236 N. ELSTON, CHICAGO, IL 60618

**CANADIAN Surplus Catalog** \$1.00. **ETCO ELECTRONICS**, 464B McGill, Montreal, Canada

**THE HORN SPEAKER** monthly newspaper for vintage radio and phonograph buffs 50¢ each, \$3.00 yearly. Box 12, Kleberg, TX 75145

**SEMICONDUCTOR** and parts catalog. **J. & J. ELECTRONICS**, Box 1437, Winnipeg, Manitoba, Canada

**MANUALS** for Govt. surplus radios, test sets, scopes, teletypes. List 50¢. **BOOKS**. 4905 Roanne Drive, Washington, DC 20021

**DIGITAL ELECTRONICS!** Complete schematics, parts lists, theories—Discrete Component Digital Clock, \$3.00—Sound Sensitive Switch, \$1.50. Increase technical competence, hobby skills—Complete course in Digital Electronics is highly effective, \$10.00 Free Literature. **DY-NASIGN**. Box 60R2, Wayland, MA 01778

**JAPANESE** new products monthly! \$1.00. Refundable. **DEERE**, 10639 Riverside, North Hollywood, CA

## BUSINESS OPPORTUNITIES

**START SMALL HIGHLY PROFITABLE ELECTRONIC PRODUCTION AT HOME. INVESTMENT, KNOWLEDGE UNNECESSARY.** Postcard brings facts. **BARTA-RAH**, Box 248, Walnut Creek, CA 94597

## INVENTIONS & PATENTS

**INVENTIONS** Wanted Patented; Unpatented. **GLOBAL MARKETING**, 2420-AE 77th Ave., Oakland, CA 94605

## TUBES

**RECEIVING & INDUSTRIAL TUBES, TRANSISTORS**, All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request **FREE** Giant Catalog and **SAVE!** **ZALYTRON**, 469 Jericho Turnpike, Mineola, NY 11501

**XENON STROBELIGHT FLASHTUBES** FT106 50W \$2.50, 2/\$4.00, 10/\$16.00, 100/\$125.00. Plans 50¢. **MINDLIGHT P.O.** Box 2846RE, Van Nuys, CA 91404

**TUBES** Receiving Factory Boxed, Low Prices, Free Price List. **TRANSELETRONIC INC.** 1306 40th Street, Brooklyn, N.Y. 11218. Telephone 212-633-2800.

**RADIO** and TV Tubes 36¢ each. One year guaranteed. Plus many unusual electronic bargains. Free Catalog. **CORNELL** 4217-E University, San Diego, CA 92105

**SAVE** money on parts and transmitting-receiving tubes, foreign-domestic. Send 25¢ for Giant Catalog. Refunded first order. **UNITED RADIO COMPANY**, 56-R Ferry Street, Newark, NJ 07105

**TUBES-IEC 70% DISC. 5 FREE WITH EA. 50. SENCORE, EICO, MALLORY, HEP, SHURE.** ALSO CARTRIDGES, NEEDLES LOWEST PRICES. FULL GUARANTEE. **M & K ELEC. DIST.**, 135-33 Northern BLVD., NYC 11354

### REBUILD YOUR OWN PICTURE TUBES?

With Lakeside Industries precision equipment, you can rebuild any picture tube!

For complete details, send name, address, zip code to:

**LAKESIDE INDUSTRIES**  
3520 W. Fullerton Ave.  
Chicago, Ill. 60647  
Phone: 312-342-3399



## WANTED

**QUICK CASH** . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! **BARRY**, 512 Broadway, New York, NY 10012, 212 Walker 5-7000

**WANTED:** Old radios, tubes—24, 47, 80's; pre 40's. **M.E. SCOTT, M.D.**, Box 3608, Radford, VA 24141

## HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do. **Barta-DREI**, Box 248, Walnut Creek, CA 94597.

### SCHOTTKY IC's

74S00—.99	74S64—.99
74S03—.99	74S73—1.95
74S04—.99	74S74—1.75
74S05—.99	74S107—1.95
74S08—.99	74S108—1.95
74S10—.99	74S112—1.95
74S11—.99	74S113—1.95
74S20—.99	74S114—1.95
74S22—.99	74S153—1.95
74S40—.99	74S157—1.95
74S51—.99	

### TRANSISTOR SPECIALS

2N965	PNP	6E	TO-18	.15W	7V	.1A	300MHZ	40Hte	5/\$1.00
2N1605	NPN	6E	TO-5	.15W	24V	.1A	14MHZ	125	5/\$1.00
2N2360	PNP	6E	TO-33	.06W	20V	.05A		980	32 \$.50
2N5324	PNP	6E	TO-3		60W	250V	10A	20	35 \$1.50
2N10150	NPN	SI	TO-82	150W	200V	7.5A		.025	10 \$1.45
2N2015	NPN	SI	TO-36	150W	50V	10A		.012	26 \$.90
2N3584	NPN	SI	TO-66	35W	250V	2A		10	100 \$1.50
2N3055	NPN	SI	TO-3	115W	100V	15A		.01	50 \$1.00
2N3772	NPN	SI	TO-3	150W	60V	30A		.2	30 \$1.25
2N5296	NPN	SI	TO-220	36W	40V	4A		.8	60 \$.50
2N6109	PNP	SI	TO-220	36W	40V	4A		.8	60 \$.55
2N4898	PNP	SI	TO-66	25W	40V	4A		4	46 \$.60
MJ2251	NPN	SI	TO-66	10W	225V	.5A		10	40 \$.70

### PRINTED CIRCUIT BOARD

3 1/4" x 6" single sided paper epoxy board 1/16" thick unetched

3 boards/\$1.00

### MAN-1 LED

5 Volt READOUTS  
\$4.50

8223 field prog. ROM	\$8.00
1101 256 bit RAM	\$4.00

### Full Wave Bridges

PRV	2A	6A
200	.95	1.25
400	1.15	1.50
600	1.35	1.75

### TANTULUM CAPACITORS

4.7 MFD at 20V	5/\$1.00
10 MFD at 20V	4/\$1.00
4.7 MFD at 100V	\$.50
10 MFD at 100V	\$.75
200 PRV 15A full wave rectifier	\$.95

### TTL IC SERIES

7400—.25	7475—.100
7401—.25	7476—.60
7402—.25	7480—.65
7403—.25	7481—1.25
7404—.28	7483—1.25
7408—.25	7486—.60
7410—.25	7490—1.00
7413—.75	7492—.79
7416—.48	7493—.79
7420—.25	7495—.90
7426—.32	74107—.60
7430—.25	74121—.70
7440—.25	74122—.85
7441—1.30	74154—1.75
7442—1.50	74182—1.10
7446—1.50	74192—1.75
7447—1.50	74193—1.75
7448—1.25	8570—1.90
7450—.25	8590—1.90
7460—.25	9309—1.95
7472—.40	9312—1.95
7473—.75	9322—1.95
7474—.50	

14 Pin DIP sockets	3/\$1.00
16 Pin DIP sockets	.60

### TEN TURN TRIM POTS

500ohm, 10K, 20K, 25K	
50K	\$.75 3/\$2.00

### Silicon Power Rectifiers

PRV	1A	3A	12A	50A
100	.06	.09	.24	.90
200	.07	.12	.20	1.25
400	.09	.16	.35	1.50
600	.11	.20	.50	1.80
800	.15	.28	.70	2.30
1000	.20	.35	.90	2.75

### DECADE COUNTER KIT

CONSISTING OF:  
1—NIXIE TUBE and SOCKET  
1—7490 1—7475 1—7441  
Special priced at \$4.75

### LINEAR CIRCUITS

LM309K 5V 1A regulator	\$2.25
PA234 1W audio amp.	\$1.25
PA264—5 Watt regulator	\$1.25
703 RF—IF amplifier	\$.75
709C operational Amp	\$.39
741 operational Amp	\$.39
SE 501 Video Amp	\$1.00
748 Adjust 741	\$.44
Dual 709	\$.95
723 Regulator	\$.75
TVR 2002 high power	
703	\$1.00
723 RF—IF amp.	\$1.00
CA3065 FM/TU amp.	\$1.35
565 phase lock loop	\$3.35
566 Function gen.	\$3.25
567 Tone decoder	\$3.25
560 phase lock loop	\$3.25
561 phase lock loop	\$3.25
555 $\mu$ s to 1 hour timer	\$1.19
5558 dual 741 (Mini-DIP)	.88

### Silicon Control Rectifiers

PRV	6A	10A	20A	70A
50	.25	.32		
100	.30	.45	1.00	3.50
200	.50	.75	1.25	6.50
300	.60	.90	1.50	
400	.70	1.10	1.75	9.50
500	.80	1.25	2.00	
600	.90	1.40	2.25	11.00

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage. Average Wt. per package 1/2 lb. No. C. O. D.'s. Minimum Order \$3.00

Send for our fall catalog featuring Transistors and Rectifiers; 325 Elm St., Cambridge, Mass.

**Give Happiness  
The United Way**

**OLID**

Post Office Box 74D

**TATE**

Somerville, Mass. 02143

**ALES**

Tel. (617) 547-4005

Circle 94 on reader service card



**EXCLUSIVE ECONOMY-PACKED**  
**DOUBLE BONUS Sale**  
**BONUS #1**  
**Free \$25**  
 Add 25¢ for handling PAK

ICs, DIODES  
 TRANSISTORS  
 RECTIFIERS  
 TUBES  
 CONDENSERS  
 KNOBS, ETC.

PLUS CHOOSE  
 ANY ITEM  
 \$1 OR LESS  
 FREE

**BOTH FREE WITH ANY \$10. ORDER**

**PHILCO 11 TRANSISTOR  
 AM RADIO CHASSIS**



Use as:  
 • Mike amplifier  
 • Phono amplifier  
 • Tape amplifier  
 • Covers 555 Kcs to 1500 Kcs Broadcast band

Only **\$5.95**

One of the most versatile AM Radio and multi-purpose amplifiers we have seen at Poly Paks famous "Economy" price. Measures only 4 1/2" x 3 1/2" x 2" high. With tuning capacitor, IC circuit, loopstick, ant., volume control with switch, AC and phono-mike jacks. Separate switch for changing from AM radio to amplifier. Uses either 110V plug-in adapter (not with unit) and a 9-volt battery power. Exceptional sensitivity and power. Feeds into 16 ohm speaker. Complete with spec sheets, diagrams, and hookup ideas. **BUY 2 FOR STEREO**

**8 TRANSISTOR  
 AMPLIFIER CHASSIS**  
 Only **\$3.95**



Same as above, except no AM radio section. Completely wired! With built-in preamp, mike, phono and tape inputs. Color-coded wires with diagram and hookups. Works off 9VDC transistor battery. Excellent fidelity. Shpg. wt. 1-lb.

**AC-DC CHARGER CONVERTER** — Only **\$1.98**  
 Converts above 11-and-8-transistor chassis from 9VDC to 110VAC. Easy to hook in. Use as "NICAD" battery charger too (with instructions). Size: 2 1/4" x 1 1/4" x 1 1/4". 1-lb.

**5-IN. "HI-FI" PM SPEAKER** — Only **\$1.98**  
 5-ounce ceramic, cylindrical magnet. Twin voice, coil, 4 and 8 ohms. 50-16,000 cycles. Shpg. wt. 3 lbs.

**TEXAS 4-WATT AUDIO AMPLIFIER** **\$3.95** 3 for **\$9**  
 Type SN76024. Good up to 70 Hz. 4 W. into an 8-ohm load. High input impedance, VCC 9V to 24. DIP pak with heat sink. 16 transistors, 6 diodes.

**BRAND NEW LOWEST PRICES**  
**GENERAL ELECTRIC** **\$2.95** 3 for **\$6.00**  
**3-WATT AUDIO AMP**

Delivers 3.5 watts continuous, 10 watts peak. With heat sinks; micro-mini size: 3/4" x 1/2" x 1/2". 9 to 30V supply. High sensitivity. 8 to 16 ohms.

**IT'S NEW! 12-DIGIT "CALCULATOR ON A CHIP"** **\$2.50** 3 for **\$3.5**

Sorry, can't name U.S. maker! Type SD5001. Similar to Mostek 6012. Outperforms Texas 8-digit TMS-1802. Features: 40-pin DIP; not 6, not 3, but only single "calculator chip". 12-digit capacity; adds, subtracts, multiplies, divides, fixed point (0, 2, 3 or 4 decimal places), chain operations, leading zero blanking, 7-segment decoded display output, overflow lockout, and negative sign output. Drives incandescent, fluorescent, Nixies, and LED readouts, complete with instruction booklet.

**RADIATION SURVEY INSTRUMENT**  
**\$9.95**  
 Wt. 3 lbs; size 5x4x8 1/2".

**Victoreen 710B**, measures Gamma radiation from 0.1-50 roentgens/hr. This surplus C-D meter is new, guaranteed and comes with a complete manual of instructions, theory of operation, circuitry, detailed parts list. The 20  $\mu$ A meter is calibrated in roentgens per hour, indicating the presence of gamma radiation. Three multiplier scales (Victoreen 100,000 meg; 10,000 meg; 1,000 meg decade) matched within  $\pm 2\%$

**LED READOUTS**  
**\$4.50** 3 for **\$12**  
 0-9 plus letters, for SN7446 or SN7447. Snap in 14-pin DIP socket. 3/4" x 3/4" x 3/4", characters: 1/4" x 9/16", 6V, 20-mils per seg. Characters: 1/4" x 3/16". Famous MAN-1 type. Sockets .50 ea.

**Lowest prices on COUNTING SYSTEM**  
 Includes SN7441, SN7475, SN7490, 0 to 9 National Nixie tube, sheets. **\$4.50** 3 for **\$12.00**

Type G, 1/2" dia. x 1 1/2" high, Mounts 1/4" immersion-proof high frequency. Allen Bradley 'MICRO-POTS' **\$2 for \$1**

75	2.0K	7.5K	25.K	2 for \$1
100	2.5K	10.K	75.K	
500	5.0K	20.K	100.K	5 Meg

We stock Locknut Bushing & Screwdriver types at same low prices.

**ALLEN BRADLEY'S 'TRANSISTOR' POTS** Type F, Screwdriver adjust.  

75	250	1.0K	7.5K	25.K	100K	Any
100	500	2.5K	10.0K	50.K	2 Meg	2 for \$1
200	750	5.0K	20.0K	75.K	5 Meg	\$1

Retail: 16-18 Del Carmine St., Wakefield, Mass. Terms: add postage, cod's 25%. Retd: net 30. Phone Orders: Wakefield, Mass. (617) 245-3829. C.O.D.'S MAY BE PHONED IN


**POLY PAKS** P.O. BOX 942R Lynnfield, Mass. 01940

**reader questions**

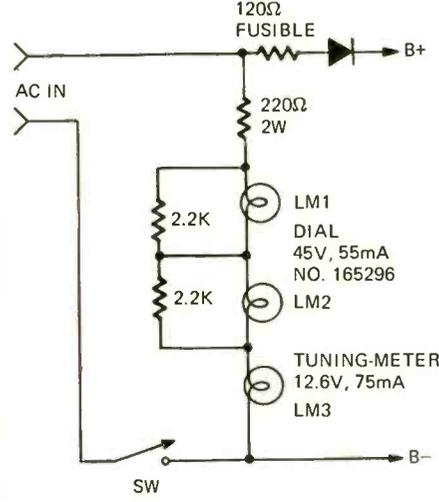**PILOT LIGHTS OUT**

An RCA RZC-275W radio came in. The only thing wrong with it is the pilot lights. I've checked the circuit, without a schematic, and can't figure it out.—P.L., St. Cloud, Minn.

The schematic for this is in Sams 1075-6 if you need it. The pilot-light circuit is a bit unusual (see diagram). This



uses two 45-volt lamps which draw 55-mA apiece. These are shunted by a pair of 2200-ohm resistors and are in series with the tuning-meter lamp, a 12.6-volt 75-mA type. This whole string is across the 117-volt line, with a 220-ohm 2-watt resistor in series.

These are special lamps; the 45-volt types are RCA part No. 165296, and the 12.6-volt one is No. 165295.

**CRYSTALS? OSCILLATOR OR FILTER?**

This isn't a regular question about a problem, but it's been bugging me for some time. Why isn't a crystal used alone in a color set, instead of being used as an oscillator? I get different opinions from people.—R.R., Dyess AFB, Tex.

A crystal, to simplify things, can be thought of as a very sharp resonant circuit. The "Q" (figure of merit) is tremendous. So, we can use one to lock the frequency of an oscillator, by substituting the crystal for the resonant circuit.

We can also use it as a very narrow filter, by putting it in series with the incoming signal. In quite a few sets, they pass the actual 3.58-MHz burst itself through the crystal, and then amplify it in the following stage.

With either method, we come out with what we must have: a signal which is locked to the station burst frequency for reference. **R-E**

**GOVERNMENT SURPLUS ELECTRONICS**

**RT-70/GRC RECEIVER — TRANS.**  
 47 to 58.4 MHz, FM continuous tuning; also 2 pre-set chan., Voice, power output 500 MW., 18 Tubes; power req.: 90 VDC @ 80 MA. 6.3 @ 360 MA. 6.3 @ 160 MA. (See available accessories below) Size: 5 x 13 x 8". Wt.: 17 lbs. Price— **\$22.95**  
 Used.....

**AM-65/GRC AF AMPLIFIER**—Three channel audio freq. Amplifier used for Interphone and radio monitoring of various types of GRC Rec-Trans.; 7 Tubes; power req.: 135 VDC 35 MA. and 6, 12, or 24 VDC. (See below for accessories) Size: 4 1/4 x 13 x 7 3/4"; Wt.: 15.5 lbs. Price—Used. **\$14.95**

**PP-282/GRC POWER SUPPLY** — 24 Volt, used with RT-70 & AM-65. This unit plugs inside the AM-65 and supplies voltages for both units. Size: 4 1/4 x 6 x 3"; Wt.: 6 lbs. Price — Used ..... **\$5.95**

**COMBINATION DEAL—RT-70, AM-65, & PP-282**—All three items for Just **\$35.00**

**TECH MANUALS**, including Schematics: For RT-196 or RT-70 ... \$7.50 Each. Manual w/Schematic for AM-65 ... \$5.00 Schematics Only ... \$1.00 Ea. H-33/PT HANDSET—Used ... \$5.95—Unused ... \$7.95

All Prices are F.O.B., Lima, Ohio — Dept. RE  
 SEND TODAY FOR OUR NEW CATALOG!

**FAIR RADIO SALES**  
 1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Now Get **MUSIC ONLY FM Programs**  
 Convert ANY FM TUNER to receive uninter-rupted commercial free music being broadcast by many stations.

New three transistor plus "Phase locked loop" IC circuit gives you perfect reception. No tuned circuits, or critical adjustments. The 1 1/2" x 4" circuit board is powered from the tuner supply. +9 to 12 Volts DC @ 10 Ma. required.

Kit Only **\$14.50**  
 With Squelch **\$19.50**  
 Wired & Tested **\$25.00**  
 With Squelch **\$29.95**  
 Plus postage and Insurance. THOUSANDS SOLD

Free list of FM stations with SCA authorizations included. (List alone \$ .25)

**Southwest Technical Products Corp.**  
 BOX 32040 • SAN ANTONIO, TEXAS 78284

**PAIA's Surf Synthesizer**

The roar of the surf electronically synthesized and played through your hi-fi.

No. 3711K **\$11.95**

Other Kits:  
 NO. 3721 ELECTRONIC WIND CHIMES ..... **\$ 16.95**  
 NO.1710 SOLID STATE BIRD ..... **\$ 6.95**  
 Plus electronic music accessories and many more.  
 Please add 50¢ postage & handling to orders.  
 Write for FREE Catalog

**PAIA ELECTRONICS**  
 BOX R14359, OKLAHOMA CITY, OK 73114

**YEATS appliance dollies**

**MOST VERSATILE color TV TRUCK DEVELOPED!**

NO LIFTING

ROLLS UP & DOWN STAIRS

DeLuxe Model No. 14 **\$89.50**  
 ORDER YOURS TODAY!  
 FREE illustrated brochure

**Yeats Appliance Dolly Sales Co.**  
 1307 W. FOND DU LAC AVE.  
 MILWAUKEE, WIS. 53205



LIVE IN THE WORLD OF TOMORROW... TODAY! NEW PRODUCTS, NEW MATERIALS, NEW IDEAS!

# UNUSUAL & PHYSICAL SCIENCE BUYS

UNIQUE HARD-TO-FIND BARGAINS FOR FUN, STUDY OR PROFIT

## TAPE-SLIDE SYNCHRONIZER



Coordinate tape recordings with slide series. Hook up stereo recorder to remote control projector and TSS—then record what you wish for each slide. Playback and TSS AUTOMATICALLY changes slides in synch. w/tape. Your presentation "gives itself". Perfect for sales meetings, lectures, & vacations, parties... anywhere.

\*"talking albums" of child's growth—a new dimension to recollections, parties... anywhere.  
Stock No. 41,222EH ..... \$21.95 Ppd.  
6-FT CONNECTOR CORDS ..... \$4.75 Ppd. each  
Kodak Proj. (#60,804EH) Airquilt (#60,805EH)

## NEW ELECTRONIC CALCULATOR—\$99.50



Terrific American-made value w/big machine capabilities. Add, subtract, multiply, divide, do mixed calculations—silent answers in mill-seconds. 8 digit entry & readout w/10-digit cap. Auto. precise to the decimal. Also features fixed decimal, constant key underflow, zero suppression, minus sign for true credit balance, error correction, keyboard roll over memory. Solid state; modular contr., only 3-lb. Year guarantee (normal use).  
No. 78,000EH .... (6 1/2 x 9 x 2" Ht) ..... 99.50 Ppd.

## ULTRA LOW PRESSURE SENSOR



Big surplus bargain—tiny electrical pressure switch activated by only 0.02 psi air or 1/4" or less water pressure. Single pole, normally open. 10 ma DC contact rating. 30v AC/DC (usual loads require sensitive relay or solid state control). Use as sensor, switch, control, counter, edge guide, instrument alarm. Long life (1,000,000 operations), impervious to shock, vibration. 1" sq. polycarbonate case. 3/16" diam. barbed pressure ports. Wt.—10 grams.  
ORIGINAL COST \$11.50.  
Stock No. 41,623EH ..... \$3.95 Ppd.

## FEATHERWEIGHT TREASURE FINDER



Best, easiest to use solid state metal detector at its price. U.S. model Only 3 lbs! 6" head detects penny at depth of 8", silver dollar at 8", bag of coins at 18". Works thru dirt, sand, wood, water (30" deep), rock with no power loss. Detects "find" with "sound off" loud-speaker. Ready to go. One tuner control: all trans.; adjust stem; perfect balance. Includes 9v batt. FREE TREASURE GUIDE To 101 Treasure Sites.  
Stock No. 80,175EH ..... \$39.95 Ppd.

## NEW! ELECTRONIC DIGITAL COMPUTER KIT!



Solve problems, play games, predict weather with this actual working model of giant electronic brains. Amazing new fun way to learn all about computer programming, logic, decimal, binary systems. Laws of Sets—even do your own programming after completing simplified 116 page step-by-step assembly diag. Instructive booklet. Includes step-by-step assembly diag. Circuits easily changed. Readout from illuminated control panel. Req. 2 "D" batt. (not incl.). Best model—for home, school, industry.  
No. 71,434EH ..... (11" x 12 1/2" x 4") ..... \$31.50 Ppd.



**MAIL COUPON FOR GIANT FREE CATALOG!**  
164 PAGES • MORE THAN 4,000 UNUSUAL BARGAINS

Completely new 1973 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many surplus items.

**EDMUND SCIENTIFIC CO.**  
Barrington, N.J. 08007  
Please rush Free Giant Catalog "EH"

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## 130 EXPERIMENTS IN OPTICS... PHOTOGRAPHY



Optix(R) Experiments Kit is a complete optical & photography lab for 130 exciting experiments. Lets you recreate the periscope, telescope, microscope, kaleidoscope! Build a 35mm reflex camera with interchangeable lens system! Make, develop photographic film! Enjoy the fun and fascination of having your own optics lab. Fully illustr 112-pg manual, 8 1/2 x 11", clearly explains usage of this stimulating kit's 114 precision engineered components.  
Stock No. 71,646EH ..... \$21.00 Ppd.

## DIGITAL COMPUTER LOGIC LAB




Fascinating new way to learn computer types, binary systems, truth tables, logic. Make ring counter, shift register and binary counter. Play with reaction timer, electronic coin flipper. Experiment with memory, counting & arithmetic circuits, 4 assembled module circuits (clock, solid-state NAND gates, flip-flop, display), 20 patch cords for 100's of circuits—23 computer experiments. No electronic knowledge needed! 74 pg. illustr. manual explains all. Req. 6v batt. (not incl.).  
Stock No. 71,403EH ..... \$39.75 Ppd.

## TERRIFIC BUY IN HE-NE LASERS



Low price on 0.5mW Laser (random mode); 0.9mm beam dia. (at 10M, 16mm) belies its quality. New cold aluminum cathode tube for more life stability (nl beam): 9000-hr tube life under normal cond.) Ready to plug in, turn on. Starts instantly. Safe, easy for holography, interferometry, wavelength, small beam divergence.  
Stock No. 79,020EH ..... 88.50 Ppd.  
0.7mW (SINGLE TEMoMODE), 0.8mm BEAM DIA.  
Stock No. 79,024EH ..... \$99.50 Ppd.

## SLIDE-SHOW "BRAIN & VOICE"

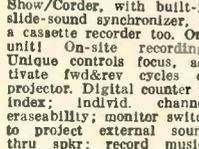


Show/Corder, with built-in slide-sound synchronizer, is a cassette recorder too. One unit! On-site recording! Unique controls focus, activate fwd/rev cycles on projector. Digital counter to index; indiv. channel eraseability; monitor switch to project external sound thru spkr; record music, narration at same time. 10-level vol. control. AC/DC. Incls cable for Kodak Carousel (K), patch cord (radio, hi-fi), earphone, remote mike, blank cassette, 4 "C" batt. instrs.  
No. 71,619EH .. (9x8 1/2x2 1/2) .. (5 1/4 lb.) .. \$171.50 Ppd.

## FLEXIBLE IMAGE TRANSMITTER



Hi-resolution image-transmitter lets you see remote, inaccessible lighted areas; thru pipes, tubes, any 3/4" opening no matter how intricate. Provides clear, wide sighting. 7X magnifying eyepiece focuses from less than 1/2" away. Ideal for monitoring hazardous processes, surveillance instr., 4,000 coherent glass fibers gooseneck sheathing.  
demonstr. fiber optics. Over (0.02"), 3/8" dia. semi-rigid  
Stock No. 80,857EH ..... \$40.00 Ppd.

## 3" ASTRONOMICAL TELESCOPE

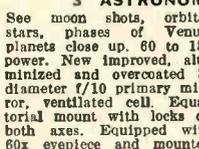


See moon shots, orbitars, stars, phases of Venus, planets close up. 60 to 180 power. New improved, aluminumized and overcoated 3" diameter f/10 primary mirror, ventilated cell. Equatorial mount with locks on both axes. Equipped with 60x eyepiece and mounted Barlow lens. 3x finder telescope, hardwood tripod. Included FREE: "STAR CHART": "HOW TO USE YOUR TELESCOPE"  
Stock No. 85,050EH ..... \$32.95 Ppd.  
Stock No. 80,162EH ..... DELUXE 3" ..... \$61.50 Ppd.  
Stock No. 85,105EH ..... 4 1/2" ..... \$99.50 FOB  
Stock No. 85,086EH ..... 6" ..... \$239.50 FOB

## MEASURE TEMPERATURE REMOTELY




Electronic thermometer gives instant temperatures from inches to 1000-ft. off. Push button, read one of 3 separate temps. (Can connect to 3 plug-in probes). Reads from -22 to +122°F and -30 to +45°C. Accuracy ±1%. Incls 2 solid-state waterproof probes (one w/18" cable, one 15-ft.). 100's of uses in home, lab, industry. Req. "D" batt. (not incl.). Walnut fin. cab. instrs.  
Stock No. 71,741EH ..... (8 1/2 x 4 1/2 x 6 3/4") ..... \$40.90 Ppd.  
EXTRA 15-FT. TEMPERATURE PROBE ..... \$4.95 Ppd.  
Stock No. 41,839EH ..... \$2.35 Ppd.

## KNOW YOUR ALPHA FROM THETA!

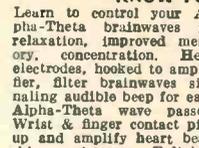

Learn to control your Alpha-Theta brainwaves for relaxation, improved memory, concentration. Head electrodes, hooked to amplifier, filter brainwaves signaling audible beep for each Alpha-Theta wave passed. Wrist & finger contact pick up and amplify heart beat, skin resistance. Reliable, easy-to-use trainer unit offers features comparable to many higher-priced modes. Completely safe. Most people can learn Alpha rhythm control in 10-12 hrs with full instructions included.  
Stock No. 71,606EH ..... \$120.00 Ppd.

## POWERFUL 22 OZ. RANGEFINDER!

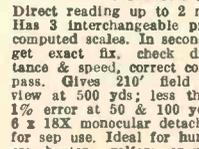


Direct reading up to 2 mi. Has 3 interchangeable pre-computed scales. In seconds, get exact fix, check distance & speed, correct compass. Gives 210° field of view at 500 yds; less than 1% error at 50 & 100 yds. 6 x 18X monocular detaches for sep use. Ideal for hunters, butlers, golfers, eng'rs., contractors, estimators. Weatherproof. 2-yr warranty.  
No. 71,648EH .. (11 1/2 x 11") ..... \$35.75 Ppd.  
No. 71,649EH CASE HOLSTER ..... \$7.75 Ppd.

## GET POLICE, AIRCRAFT CALLS




Your standard AM home or car radio can get exciting 2-way police, fire, local aircraft calls, etc. from UHF bands via Converters. No interconnecting wires needed—just put solid state Converter near set. Easy instrs incl. Ea. Kit req. 9v batt (not included). POLICE & FIRE CONVERTER KIT — LO BAND. Operates in the 30-50 MHz band.  
Stock No. 41,828EH ..... \$8.25 Ppd.  
AIRCRAFT CONVERTER KIT. Operates in the 108-136 MHz band ..... \$7.75 Ppd.  
Stock No. 41,827EH ..... \$8.25 Ppd.

## UNDERWATER MICROPHONE BUY

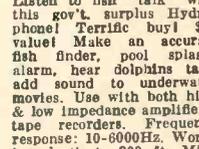

Listen to fish "talk" with this govt. surplus Hydrophone! Terrific buy! \$40 value! Make an accurate fish finder, pool splash-alarm, hear dolphins talk, add sound to underwater movies. Use with both high & low impedance amplifiers, tape recorders. Frequency response: 10-6000Hz. Working depth to 300 ft. Minimum sensitivity 1000 Hz at depths of 60 or 300 ft. Operating temperature range: 0 to 35°C. Fungus and shock resistant. Includes leads (approx. 8' long) and instrs. Cable not incl. Wt. 2 oz.  
Stock No. 41,739EH ..... \$2.00 Ppd.

## 1st LOW-COST VACUUM PUMP!

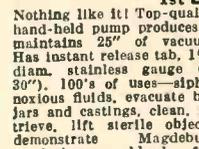


Nothing like it! Top-quality hand-held pump produces & maintains 25" of vacuum. Has instant release tab, 1 1/4" diam. stainless gauge (0-30"). 100's of uses—siphon noxious fluids, evacuate bell jars and castings, clean, relieve, lift, sterile objects, demonstrate Magdeburg hemispheres, bleed fuel lines, check leaks, etc. Lifts 40 lbs. with included "T" Lifter (2 1/2" diam. cup)—much more w/larger cup.  
Stock No. 71,301EH ..... \$12.00 Ppd.  
No. 71,300EH (without gauge/lifter) ..... 5.50 Ppd.

## ASTRONOMICAL TELESCOPE KITS



Grind your own mirror for powerful telescopes. Kit contains fine annealed pyrex mirror blank, tool, abrasives, diagonal mirror, and eyepiece lenses. Instruments you build range in value from \$75.00 to hundreds of dollars.  
Stock No. 70,003EH .... 4 1/2" diam. 3/4" thick \$10.75 Ppd.  
Stock No. 70,004EH .... 6" diam. 1" thick \$16.95 Ppd.  
Stock No. 70,005EH .... 8" diam. 1 1/2" thick \$24.50 Ppd.  
Stock No. 70,006EH 10" diam. 1 3/4" thick 30 lbs \$44.50 FOB  
Stock No. 70,007EH 12 1/2" diam 2 1/4" thick 46lbs \$72.50 FOB

## "FISH" WITH A MAGNET

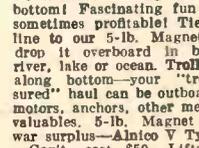

Go treasure hunting on the bottom! Fascinating fun & sometimes profitable! Tie a line to our 5-lb. Magnet—drop it overboard in bay, river, lake or ocean. Troll it along bottom—your "treasured" haul can be outboard motors, anchors, other metal valuables. 5-lb. Magnet is war surplus—Alnico V Type—Gov't. cost \$50. Lifts over 150 lbs. on land—much greater weights under water.  
Stock No. 70,571EH ..... \$14.00 Ppd.  
Stock No. 70,570EH 3 1/2" LBS ..... \$8.75 Ppd.  
Stock No. 85,152EH 15 1/2" LBS ..... \$39.95 F.O.B.

**EDMUND SCIENTIFIC CO.** ORDER BY STOCK NUMBER • SEND CHECK OR MONEY ORDER • MONEY-BACK GUARANTEE  
**300 EDSCORP BLDG. BARRINGTON, NEW JERSEY 08007**

# You get hot pressed ferrite heads and direct-drive motors in some of our new Hi-Fi cassette decks.

## And Dolby in all of them.

Now when you buy a Panasonic Hi-Fi cassette deck, the Dolby™ noise reduction system is included in the deal. Plus a lot more.

Our Model RS-276US has Hot Pressed Ferrite heads. That last 10 times longer than the ordinary kind. And provide broader frequency response. A direct-drive DC brushless motor to cut wow and flutter to under 0.1%. And Dolby.

You can also get Dolby in our Model RS-277US. With a 3-pole, 2-coil bi-directional motor. Which is responsible for our continuous automatic reverse. That lets you play an entire cassette. Without flipping it over.

**RS-276US** Freq. Resp. 20 Hz—15 kHz with normal tape; 20 Hz—17 kHz with CrO<sub>2</sub> tape. Wow and flutter under 0.1%. S/N better than 60 dB (Dolby).

**RS-277US** Freq. Resp. 20 Hz—13 kHz with normal tape; 20 Hz—14 kHz with CrO<sub>2</sub> tape. Wow and flutter under 0.25%. S/N better than 55 dB (Dolby).

**RS-263US** Freq. Resp. 30 Hz—13 kHz with normal tape; 30 Hz—14 kHz with CrO<sub>2</sub> tape. Wow and flutter under 0.2%. S/N better than 55 dB (Dolby).

Dolby is also available in our economy deck, Model RS-263US. Which happens to be about the lowest priced Dolby unit made. But Dolby isn't all it has. There's Memory Rewind. It's a switch

that lets you return to the exact point on the tape you want to replay. Without sifting through a lot of stuff you don't want. A lockable pause control. Two VU meters. Slide volume controls.


In case you were wondering about chromium dioxide (CrO<sub>2</sub>) tape, the answer is yes. These decks have a special switch for normal or CrO<sub>2</sub> tape.

So go and visit your franchised Panasonic Hi-Fi dealer. And take a look at our new cassette decks. You'll find one you like. As long as you like Dolby.

FOR YOUR NEAREST FRANCHISED PANASONIC HI-FI DEALER, CALL TOLL FREE 800 243-8300. IN CONN., 1-800 882-8500.

DOLBY IS A TRADEMARK OF DOLBY LABORATORIES INC.

## Panasonic. Hi-Fi Cassette Decks

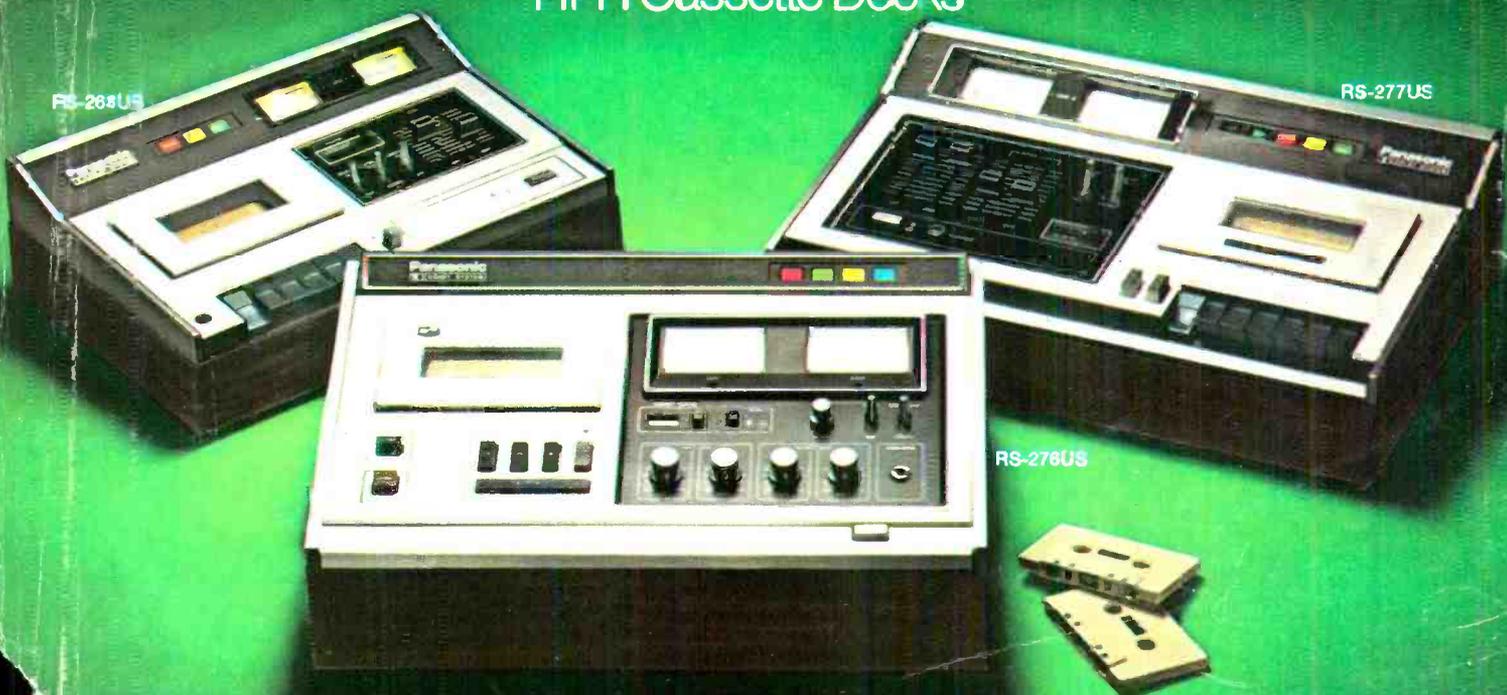

# WINEGARD HAS PULL!

Pull enough to bring in those distant stations—those hard-to-get channels—pull enough to feed more than one set! Try Winegard's CW-980 Color-Wedge VHF-UHF-FM model, with its optional antenna-mounted solid state preamplifier, for the ultimate in TV reception.

Or, for strong-signal areas, try one of Winegard's smaller models. They offer the same high quality, the same protective gold finish, the same two-year replacement policy. If the Winegard name is on the box, you can be confident it's an antenna with real "pull"—and that's the name of the game!

## Winegard Antennas For Trailers and Boats



SR-20T

Specially designed SENSAR solid-state antenna for boats & recreational vehicles—extra strong construction.

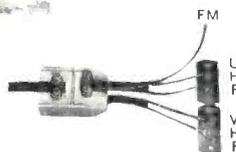
## Winegard Accessories For Complete Systems...



**BC-782 BOOSTER-COUPLER**  
Solid-State Booster-Couplers for all-channel TV and FM signals to 2 to 4 sets.




**CC-282 COUPLER**  
All-Channel non-amplified couplers to connect two sets to one antenna.



**CS-380 BAND SEPARATOR**  
Band separators to connect 75 or 300 ohm downlead to 300 ohm UHF, VHF & FM terminals.

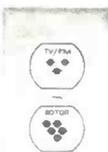**TR-35 TV OUTLET**  
TV outlets in a variety of models for all-channel TV and FM reception plus rotor.



**AC-823B CARTRIDGE PRE-AMPLIFIER**  
Antenna-mounted pre-amplifiers in 8 models for all-channel, UHF, VHF-FM and FM use, each in its own weather-proof housing.



HA-130

Winegard's new "Hideaway" Travel antenna for trailers, boats, campers, folds like an umbrella for travel!



**WINEGARD**  
TELEVISION SYSTEMS

Winegard Company — 3000 Kirkwood Street • Burlington, Iowa 52601  
Warehouses in Hartford, Los Angeles, Burlington

Circle 88 on reader service card