

COMPLETE PLANS—BUILD YOUR OWN COMPUTER

75¢ ■ MAY 1976

Radio-^{IND}Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

BUILD ONE ONE OF THESE

- ★ 8080 Microcomputer
- ★ Ignition For Your Car

LEARN SOMETHING NEW

- ★ About Function Generators
- ★ Komputer Korner
- ★ Understanding Graphs

HI-FI-STEREO

- ★ Phase Response In Speakers
- ★ R-E Lab Test Reports
Lafayette Stereo Receiver
Marantz 2325 Receiver


TELEVISION

- ★ MATV Accessories Roundup
- ★ Jack Darr's Service Clinic
- ★ Service Problems Solved
- ★ Equipment Reports



**'WHEN I
STARTED
USING PTS,
IT WAS LIKE
GAINING
TWO HOURS
A DAY'**

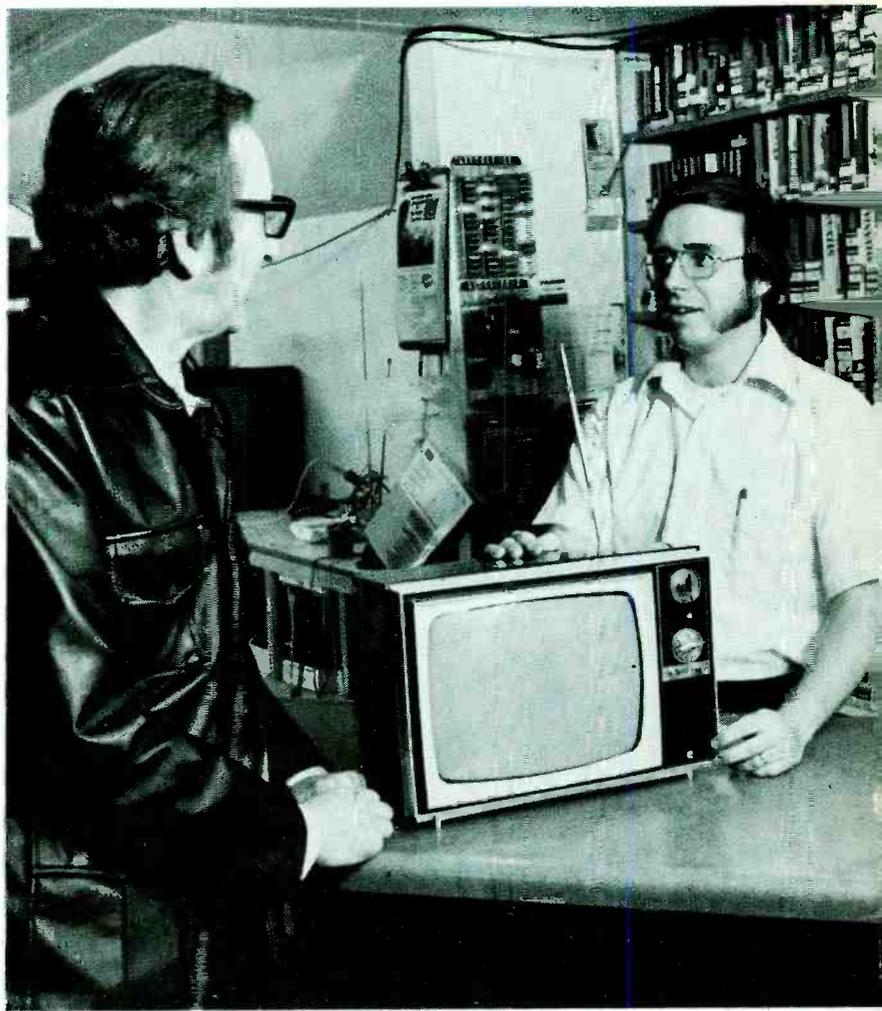Ron Baysinger / Service Manager
Preferred TV / Indianapolis



That's not an uncommon testimonial from hundreds of PTS customers all over the country. Just consider how much time you spend on the average tuner repair in your own shop. That's how much shop time you could gain for each tuner job you turn over to your nearest

PTS Service Center. Taking the tuner repair load outside, frees up inside time for more business and greater income. We can repair most any tuner of the thousands in use, have most repairs ready in one day and guarantee the work for one year.



ELECTRONICS, INC.
PRECISION TUNER SERVICE

Consult the white pages of your telephone directory for the address and number of your nearest PTS Service Center. General Headquarters: Bloomington, IN - Birmingham - Phoenix - Los Angeles - San Diego - San Jose (CA) - Sacramento - Arvada (CO) - Jacksonville - Tampa - Indianapolis - Kansas City (KS) - Metairie (LA) - Silver Spring (MD) - Boston - Springfield (MA) - Detroit - Grand Rapids (MI) - Minneapolis - St. Louis - E. Paterson (NJ) - Buffalo (NY) - Long Island - Charlotte (NC) - Cincinnati - Columbus (OH) - Cleveland - Toledo - Oklahoma City - Portland (OR) - Pittsburgh - Philadelphia - Montreal - Memphis - Houston - Longview (TX) - Salt Lake City - Norfolk - Seattle - Milwaukee.

Circle 1 on reader service card

Can anyone beat the Altair System?



We doubt it.

When it comes to microcomputers, Altair from MITS is the leader in the field.

The Altair 8800 is now backed by a complete selection of plug-in compatible boards. Included are a variety of the most advanced memory and interface boards, PROM board, vector interrupt, real time clock, and prototype board.

Altair 8800 peripherals include a revolutionary, low-cost floppy disk system, Teletype™ line printer, and soon-to-be-announced CRT terminal.

Software for the Altair 8800 includes an assembler, text editor, monitor, debug, BASIC, Extended BASIC, and a Disk Operating System. And this software is **not just icing on the cake**—it has received industry wide acclaim for its efficiency and revolutionary features.

But MITS hasn't stopped with the Altair 8800. There is also the Altair 680—complete with memory and selectable interface—built around the new 6800 microprocessor chip. And soon-to-be-announced are the Altair 8800a and the Altair 8800b.

MITS doesn't stop with just supplying hardware and software, either. Every Altair owner is automatically a member of the Altair Users Group through which he has access to the substantial Altair software library. Every Altair owner is informed of up-to-date developments via a free subscription to **Computer Notes**. Every Altair owner is assured that he is dealing with a company that stands firmly behind its products.

After all, we didn't become the leader by messing around. Shouldn't you send for more information or visit one of our Altair dealers?

Altair Coupon

Please send me the following information:

- Your latest catalog and price list
- Software information package
- Please include a list of your dealers

NAME _____

ADDRESS _____


CITY _____ STATE & ZIP _____



mits

2450 Alamo S.E. Albuquerque, N.M. 87106

Vaco.

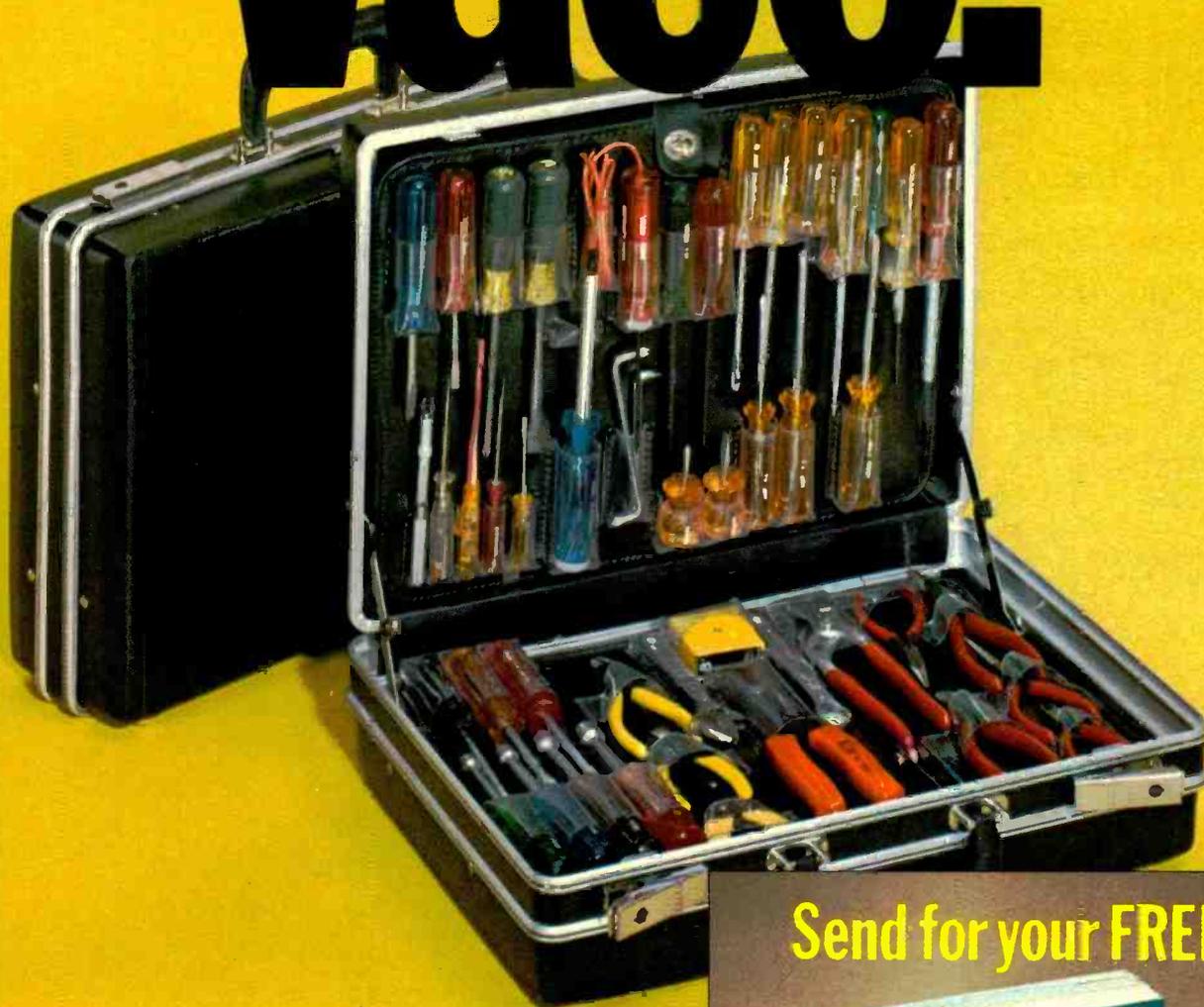

Super Case


Vaco means value and variety.

Like our Super Case. A great value with great variety. 48 professional problem-solving tools from screwdrivers and nutdrivers to pliers, wrenches, crimping tools, and more! All right at hand. And all unconditionally guaranteed.

You'll find the Super Case and all the other fine Vaco tools in our exciting new 64-page Bicentennial Catalog FREE for the asking! Just write:

Vaco Products Co., 510 N. Dearborn St., Chicago, Illinois 60610.

Send for your **FREE**

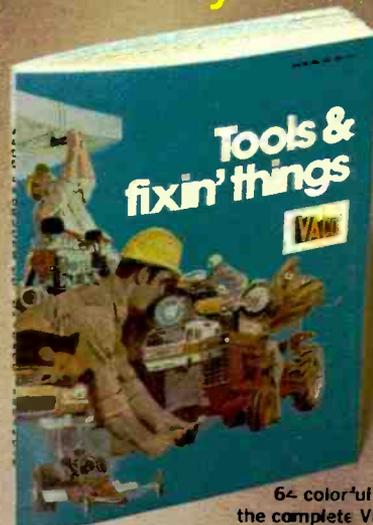

64 colorful pages with the complete Vaco selection.

1976 VACO catalog!

Circle 3 on reader service card

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

MAY 1976 Vol. 47 No. 5

SPECIAL FEATURES

- 33 **Build Dyna-Micro 8080 Computer**
Complete plans of a microprocessor that's easy to build and use. **by Jon Titus**
- 37 **MATV/CATV Accessories**
The working parts of antenna systems up close. **by Warren Roy**

BUILD ONE OF THESE

- 47 **Electronic Ignition For Your Car**
Solid-state system can be used with any standard ignition coil. **by Dick Pace**

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Preview of tomorrow's news today. **by David Lachenbruch**
- 18 **Komputer Korner**
Input-output devices. **by Jon Titus, David Larsen & Peter Rony**
- 60 **Using Charts & Graphs**
How they work and how you can make the most of them. **by Irving Gottlieb**
- 69 **State-Of-Solid State**
Microprocessor IC's and systems. **by Karl Savon**

HI-FI STEREO AUDIO

- 43 **Linear Phase Response**
A new parameter for measuring speaker-system performance. **by Len Feldman**
- 50 **R-E Lab Tests Lafayette LR-2200**
This new receiver comes up with a "very good" rating. **by Len Feldman**
- 56 **R-E Lab Tests Marantz 2325**
A new stereo receiver runs the gamut at our test lab. **by Len Feldman**

TELEVISION


- 24 **Equipment Report**
American Technology ATC-10 Color Generator.
- 30 **Equipment Report**
Hewlett-Packard 3476A Digital Multimeter.
- 40 **All About Function Generators**
"Part I" Everything you always wanted to know about how they work and how to use them. **by Charles Gilmore**
- 63 **Service Clinic**
Loop circuits—circuits that control themselves. **by Jack Darr**
- 87 **Reader Questions**
R-E's Service editor Solves reader problems.

DEPARTMENTS


- | | | | |
|-----|----------------------------------|----|-------------------------|
| 110 | Advertising Index | 6 | New & Timely |
| 12 | Advertising Sales Offices | 86 | New Literature |
| 14 | Letters | 78 | New Products |
| 93 | Market Center | 89 | Next Month |
| | 113 Reader Service Card | | |

ON THE COVER

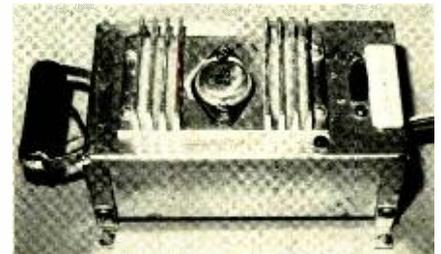The computer hobbyist needs a better machine. So we've introduced the "dyna micro." It's an 8080 architecture on a single circuit board. We'll be presenting complete plans and construction information starting on page 33 in this issue.



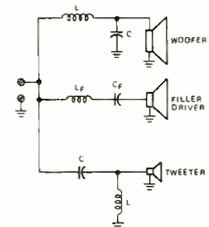SOLID-STATE IGNITION for your car isn't a difficult project. This unit is easy to build and works with almost any standard ignition coil. see page 47



PHASE RESPONSE in speaker systems is an important measurement. Here's how a third speaker can fill the null between woofer and tweeter. see page 43

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies 75c. © 1976 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Secret picture tube

Around the television industry it had been rumored for some time that Zenith was up to something big in picture tubes. Suspicion grew after an unusually large number of new picture tube patents were issued to Zenith scientists and engineers. Then *Television Digest*, a trade publication, broke the story that Zenith had developed a "radically new picture tube, re-engineered from glass to gun, yoke to mask," that would provide high performance at considerably lower cost than present designs.

Zenith finally confirmed that it did indeed have a new color tube that would be introduced in the 19-inch size in some sets late this summer, in other sizes next year. It indicated that the development took four years of intensive effort, in cooperation with Corning Glass Works, and that Zenith considered the new tube to be a major weapon against the inroads now being made by imports in the 19-inch size. Although Zenith hasn't yet released details, it's understood that the new tube presents a picture with a distinctive appearance, that it's lighter in weight than present types and that many operations in its production may be automated.

No picture tube

Getting rid of the picture tube completely is the goal of inventor William Glenn, whose previous contributions to television have been made at General Electric and CBS Labs. Glenn is now director of New York Institute of Technology's Science and Technology center, and he's working on a high-brightness projection television system that uses a charge-coupled device (CCD) instead of an electron gun.

The Glenn TV will be about the size of a Kodak Carousel projector and will be based on light-valve (or Eidophor) principles that use an external

light source rather than a CRT to provide illumination for the projected picture. Glenn plans to use a CCD chip to modulate a membrane about the size of a 35-mm slide. A projection lamp is aimed through the membrane. The surface of the membrane is deformed by the CCD chip in accordance with the video signal. Actually, there would be three chip-membrane combinations—one for each color—converged by dichroic mirrors.

Glenn feels that his projector could make possible pictures of virtually any size, viewable in room light. "We've made small pieces of chips that work, but we don't have television resolution yet," he says, but he notes that CCD chips with adequate resolution have already been made for developmental TV cameras. He estimates he'll have his tubeless TV in about three years.

More on projection

An increasing number of projection TV systems are coming on the market, most of them offered by small companies and based on the use of small-screen color sets, lens systems and directional Kodak Ektalite screens. Most major manufacturers have sat by with little real interest (exception—Sony, which has its own TV projector). Now the majors are beginning to stir. The most enthusiastic, apparently, is the Admiral Group of Rockwell International, whose president, Charles Urban, says: "There are so many reasons projection TV's going to fly that it's beyond the imagination. I've seen a lot of interesting ideas. Our Science Center is working on it. You'll start seeing prototypes of high-brightness systems in about a year and a half."

In addition, Zenith is understood to be underwriting development of special fresnel lenses for projection television, and General Electric is believed to be giving the projection concept another long look. Once there's a major

breakthrough permitting the use of an ultra-bright light source (such as the Glenn project), projection TV could be off to the races.

New TV services

The White House Office of Telecommunications Policy has urged the FCC, broadcasters and television set manufacturers to start looking into new services that could be provided by home television without degradation of the broadcast signal. Based on a specially commissioned study made by the University of Denver, a concerted effort was urged to develop "ancillary signals for television."

The Denver study specifically dealt with three major projects: The first was stereophonic sound for television. It estimated that 10 to 25 percent of TV set buyers might be willing to pay \$50 to \$100 extra for stereo television sets. The second was a special captioning service for the nation's 13,000,000 people with hearing problems and 7,000,000 with limited knowledge of English. The captions would be receivable only on sets with special converters (at probably \$55 to \$110 installed) or on new sets equipped with captioning circuits (at \$30 to \$50 extra). The third was Teletext services that use the TV screen to display graphic material transmitted in the vertical interval between pictures. The report says Teletext should reach the commercial stage in the next 5 to 10 years.

One of the proposals promises to get prompt attention from the FCC. In response to an earlier petition by Public Broadcasting Service, the Commission has already proposed a special captioning system for the deaf and said it will move quickly to implement the proposal unless "compelling arguments" are offered against it. The PBS system would reserve line 21 of the vertical interval for captions, which could be decided by optional TV set circuitry.

High-speed TV

A new, economical system for closed-circuit TV educational courses in the school or home has been developed by Peter Goldmark, president of Goldmark Communications Corp. It will be placed in service this fall in six community college districts across the country. Called Rapid Transmission & Storage (RTS), the system uses videotape or broadcast television. The tape system, RTS I, will be used this fall and makes possible the storage of up to 60 different half-hour programs on a single one-hour videotape reel—and up to 30 may be shown simultaneously and directed to different monitors.

The RTS Mark II system, to come later, provides for over-the-air transmission of similar information during nighttime non-program hours. A 30-minute course is transmitted in 12 seconds and stored in a special cassette recorder at the student's home for playback at will. The transmission speed of the Mark II system will make it possible to transmit 2,800 different half-hour lessons during an eight-hour period on a single channel.

AM stereo coming

The National AM Stereophonic Radio Committee (NASRC), an industry-wide organization, has set up shop to test various proposed systems to bring two ears to AM. Three systems have been proposed so far: RCA proposed one using frequency-modulated left-and-right information. Sansui and Comm Associates proposals use sideband approaches. Kahn Research Laboratories has also proposed a sideband system in the past and says it will urge immediate standardization of its system by the FCC, rather than submit it to testing by NASRC.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

HOW TO SAVE HUNDREDS OF DOLLARS ON PARTS. PAINLESSLY.

At CSC, we've developed a family of ingenious Design Mate™ test equipment that gives you professional quality and precision at very *un*professional prices. Each unit can save you money—and time—in a number of interesting ways. For more information on these, or any other CSC products, see your dealer or write for our catalog and distributor list.



SAVE MONEY AND TIME WITH DESIGN MATE 1

This precision all-in-one unit combines a solderless plug-in breadboarding system with a built-in better-than-1%-regulated variable 5-15V supply and 0-15V voltmeter. Gives you everything you need to design and test circuits faster than you ever could before. Saves money by eliminating lead damage and heat damage to components. Lets you re-use parts over and over again, to save even more. All for just \$49.95*


STRETCH YOUR BUDGET FURTHER WITH DESIGN MATE 2

Precision function generator lets you test all kinds of equipment, with 1Hz-100kHz signals. Low-distortion sine waves, high-linearity triangle waves, fast-rise-time square waves. Five decade ranges, accurate to 5% of dial setting, with variable 100mV-10V P-P output and constant 600-ohm impedance. At \$64.95* it's a lot of signal for very little money.

SAVE MORE MONEY AND TIME WITH DESIGN MATE 3

Accurate R/C bridge helps you use "bargain" components. Quickly and easily measures resistance 10 ohms-10 meg; capacitance 10pF-1μF—both in decade ranges to within 5% of dial setting. Simple, 2-control operation and positive LED indication make measurements in seconds. At \$54.95* it pays for itself in no time.

CONTINENTAL SPECIALTIES CORPORATION

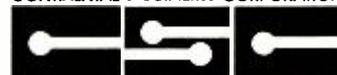

EASY DOES IT

44 Kendall Street, Box 1942
New Haven, CT 06509 • 203-624-3103 TWX: 710-465-1227
West Coast office: Box 7809, San Francisco, CA
94119 • 415-421-8872 TWX: 910-372-7992
Canada: Len Finkler Ltd., Ontario

Electronic sales downtrend reversed at end of 1975

The year 1975 ended on an up-beat in all categories of consumer electronic products sales, except automobile radios, says Jack Wayman of the Electronic Industries Association (EIA). This was in contrast to the figures for the year, which were significantly lower than in 1974. In the final December sales week, television was up 19.8 percent, radio was up 66.2 percent and compact and component phonograph systems was up 10 percent.

The EIA reports color television sales for the whole of 1975 just short of 6.5 million, down 17 percent from 1974. Black-and-white TV sales were just below 5 million, down 16.4 percent from 1974. The AM and FM radio sales totalled approximately 25.5-million units in 1975, lower by 22.8 percent from the almost 33-million units sold in 1974. Automobile radio sales of about 9.2-million units were down 14.1 percent from the 1974 figures.

Total radio sales to dealers in 1975 were almost 34.7 million, a drop of 20 percent from 1974 sales. Compact and component phonograph sales to dealers, in round figures, were 3.4-million units, off 22.7 percent from the 4.4-million 1974 sales.

CSEA names Norman Woelfel new executive director

The California State Electronics Association has announced the appointment of Norma J. Woelfel as successor to Howard G. Wooliscroft, the present executive director of the association. CSEA is a 21-year-old statewide trade association of more than 1,000 sales and service retailers of electronic home entertainment equipment.

Ms. Woelfel joins CSEA after 13 years with the California Moving and Storage Association, where she was assistant director. She is a second-year graduate of the U.S. Chamber of Commerce's Institute for Organizational Management, a member of the American Society of Association Executives and of the California society of the same name, serving for several years on its Executive Board. Until Mr. Wooliscroft's formal retirement later this year, she will assume title of assistant executive director of CSEA.

NESDA check shows big jump in number of service technicians

Figures submitted to the National Electronic Service Dealers Association by the ten major state or city licensing boards around the country indicate that the total number of service technicians in the United States has increased to 196,347—an increase of 6.5 percent—during 1975. At the same time, the number of busi-

nesses engaged in electronic servicing declined about 9 percent, from 72,165 in early 1975 to 66,000 at the beginning of 1976.

The increase in the number of service technicians is due to the recession, believes NESDA executive vice president Dick Glass, CET. "I think that the statistic showing 196,000 technicians is correct," he said. "My opinion is that the recession has cut overtime for many technicians working full time in other industries and has caused others to lose their jobs or be laid off. Many have therefore obtained licenses to obtain income with repair work, either for themselves or as employees of existing firms."

Radio tracking to help wolves

A Red Wolf Recovery Program has been organized by the U.S. Fish and Wildlife Service, cooperating with the Louisiana Wild Life and Fisheries Commission and the Texas Parks and Wildlife Department, with the object of preventing the wolf from becoming extinct.



TWO MEMBERS of the Red Wolf Recovery Program recording the vocal responses of a wolf—and any friends he might meet—on a Uher 4000 portable open-reel tape recorder.

As part of the program, wolves are fitted with collars carrying radio transmitters. Their movements are then monitored with the idea of gaining more knowledge of their wanderings and habits. The receivers are directional and make it possible to get a good idea of the whereabouts of the animal being tracked.

Technician apprenticeships initiated in Wisconsin

Through the cooperation of the Wisconsin Electronic Service Association (WESA), the Wisconsin Department of In-

dustry, Labor and Human Relations and the Waukesha County Technical Institute, a Radio and Television Technicians Apprenticeship Program is being carried on in Wisconsin.

Apprentices will be indentured to qualified electronic service establishments in the State for a working period of 8,320 hours (approximately four years). The apprentice normally starts at 50 percent of the skilled rate for technicians and receives raises in accordance with a schedule that forms part of the apprenticeship indenture.

While working, the student will study at a certified school, or if no school is available, will take 576 hours of instruction through home study from the Waukesha County Technical Institute. Upon successful completion of all the requirements of the apprenticeship, the apprentice will receive a diploma from the Wisconsin Division of Apprenticeship and Training.

FCC moves to expand, localize Emergency Broadcast Service

The Emergency Broadcast Service (EBS) is a means for distributing emergency information swiftly to licensees and regulated services of the FCC, non-government entities and the general public. It is made up of AM, FM and TV broadcast stations operating on a voluntary, organized basis during emergencies.

At the national level, the EBS already effectively provides the President with a means of speaking immediately to all the people of the country in any time of grave national emergency. The FCC has now moved to increase the usefulness of the system by increasing its use at the state and local level for day-to-day emergencies—fires, floods or other disasters.

A key element in the plans is the establishment of single EBS points that public safety officials can contact to get emergency messages on the air—a CPCS (Common Program Control Station) that will pass the messages on to other EBS stations. This can save valuable minutes that would be lost in contacting stations individually, especially in emergencies such as tornadoes or flash floods.

New two-tone attention signal for emergency broadcast stations

The FCC established April 15, 1976 as the date at which broadcast stations (other than non-commercial educational FM's with not more than 10-watts power) must be equipped to generate (encode) and detect (decode) the new two-tone inter-station Emergency Broadcast System attention signal. The EBS is a system

(Continued on page 12.)

To SBE

in·no·va·tion

is not just another word

In fact, "innovation" is *the* word that guides SBE engineers in their quest for better ways to improve personal communications equipment.

An example of SBE innovation at its imaginative best is OPTI/SCAN. This compact 10-channel scanning monitor requires no crystals but is capable of scanning over 16,000 radio frequencies between 30 MHz and 510 MHz.

The secret of such electronic wizardry lies in the unique use of digital frequency synthesis, combined with an exclusive optical scanner and program card system. The "memory" for specific frequencies to be monitored is programmed in 10-frequency groups on a small plastic card no larger than a credit card. Frequency bands can be mixed on the same card; and frequency groups to be scanned can be changed instantly simply by replacing one pre-programmed card with another.

SBE innovation has transformed the scanning monitor from a fixed, inflexible unit of limited range and scope into an infinitely versatile electronic marvel that puts a limitless range

of frequencies at your fingertips, wherever you are, wherever you may travel.

The same innovative skill and imagination that goes into OPTI/SCAN is reflected in the full SBE line of communications equipment: citizens band, land mobile, marine and special application.

Discover how *you* can benefit from SBE's electronic innovations.



SBE Better Communications through Creative Technology[®]

For information write: SBE, Inc., 220 Airport Blvd., Watsonville, CA 95076

INTERNATIONAL OFFICES: E.S. Gould Marketing Co. Ltd., Quebec, Canada/Linear Systems S.A. Geneva 1, Switzerland

Circle 5 on reader service card

www.americanradiohistory.com


Where do the pros get their training?



Almost half of the successful TV servicemen have home study training and with them, it's NRI 2 to 1.

It's a fact! Among men actually making their living repairing TV and audio equipment, more have taken training from NRI than any other home study school. More than twice as many!

A national survey*, performed by an independent research organization, showed that the pros named NRI most often as a recommended school and as the first choice by far among those who had taken home study courses from any school. Why? Perhaps NRI's 60-year record with over a million students . . . the solid training and value built into every NRI course . . . and the designed-for-learning equipment originated by NRI provide the answer. But send for your free NRI catalog and decide for yourself.

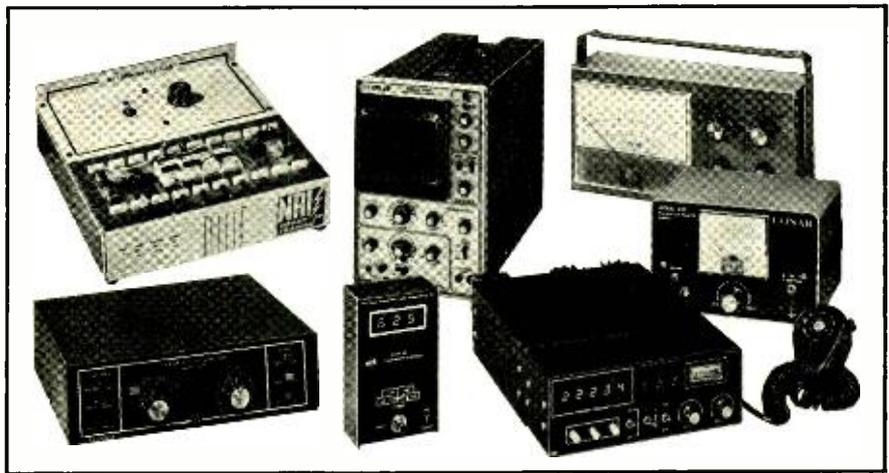

**25" Diagonal Color TV...
And 4-channel
Quadraphonic Stereo.**

As a part of NRI's Master Course in color TV/Audio servicing, you build a 25" diagonal solid state color TV with console cabinet. As you build it, you perform stage-by-stage experiments designed to give you actual bench experience. And you get a Quadraphonic system with 4 speakers. NRI's instruments are a cut above the average, including a transistorized volt ohm-meter, triggered sweep 5" oscilloscope, CMOS digital frequency counter and digital integrated circuit color TV pattern generator. They're top professional quality, designed to give you years of reliable service. You can pay hundreds of dollars more for a similar course and not get a nickel's worth extra in training and equipment.

**Widest Choice of
Courses and Careers.**


NRI doesn't stop with just one course in TV/Audio servicing. You can pick from five different courses (including an advanced color course for practicing technicians) so you can fit your training to your needs and your budget. Or, you can go into Computer Technology, learning on a real, digital computer you build yourself. Communications with your own 500 channel digitally-synthesized VHF transceiver. Aircraft or Marine Electronics. Mobile radio, and more.

**Free Catalog...
No Salesman Will Call.**

Send the postage-paid card for our free color catalog showing details on all NRI electronics courses. Lesson plans, equipment, and career opportunities are fully described. Check card for information on G.I. benefits. No obligation, no salesman will call. Mail today and see for yourself why the pros select NRI two to one!

If card is missing, write,

*Summary of survey results upon request.

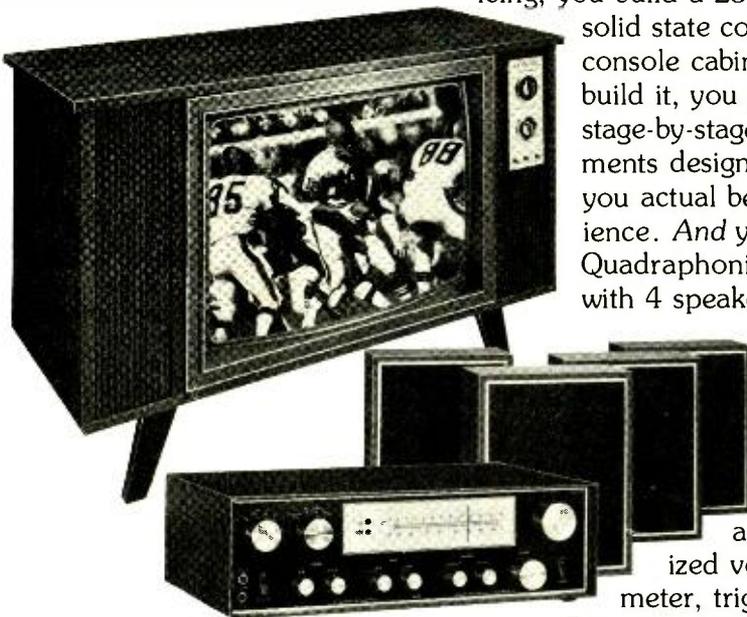

**Two Famous Educators...
NRI and McGraw-Hill.**

NRI is a part of McGraw-Hill, world's largest publishers of educational material. Together, they give you the kind of training that's geared for success . . . practical know-how aimed at giving you a real shot at a better job or a business of your own. You learn at home at your convenience, with "bite-size" lessons that ease learning and speed comprehension. Kits designed to give you practical bench experience also become first-class professional instruments you'll use in your work.



NRI SCHOOLS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016

that can keep the nation informed of national, state or local emergencies.

In November, 1974, the FCC amended its rules to substitute a two-tone signaling system (a transmission with two audio-tones) for the system then in use—two 5-second carrier breaks followed by a 1000-Hz tone for 15 seconds.

There was some opposition to the April 1 date from broadcasters' associations, who felt that more time should be allowed to make the changeover. They also demurred at the possible costs, which the National Broadcasters Association said could run to \$700. The FCC's reply was that when the carrier-break system went into effect in 1967, the FCC put out public notices stating that a two-toned technique, expected to prove superior to the carrier-break, was being developed and might make obsolete the emergency broadcast receivers then in operation. Thus, in effect, the industry had been put on notice for eight years. As to price, combination encoder-decoders were available at prices as low as \$195, therefore the cost was neither exorbitant nor prohibitive.

Servicers support attack on in-warranty injustices

The Florida Electronics Service Association has pledged \$1,000 in support of the Electro TV court-suit in California. The suit is aimed at forcing manufacturers to stop violating California law by soliciting service repair work below cost.

The question has been asked: Why go too low—if in-warranty payment rates are too low, why not simply refuse to service the brands involved? Some service concerns can do just that. But many warranty repair stations are also sales firms and are agents for only the one or two brands they sell. To refuse to handle in-warranty repairs on those brands—even if the rates are below cost—would mean that the customer would have to call a direct competitor to have the in-warranty work done.

Another case is that of a shop that handles all the repair work for a department store. The store obviously wants to handle all its repair business through one shop—not two or three. If the shop will not handle the unprofitable brands, the department store will be inclined to drop it and find one to which it can channel all the repairs.

For these reasons many service groups are supporting the litigation with cash. The Orange County chapter of the California State Electronics Association (CSEA) donated \$1,000 to the fund, and a single shop in Los Angeles contributed \$500. Other donations of \$100 and \$50 have come in from all over the country.

The National Electronic Service Dealers Association (NESDA) has set up a special fund for the in-warranty war-chest, and asks interested groups to send their donations to: SIS—Electro TV Fund, c/o the Finney Co., M. L. Finneburgh, Jr., EHF, 34 W. Interstate St., Bedford, OH 44146.

Federal Trade Commission rule helpful to mail-order customers

Under a new Trade Regulation Rule of the FTC, mail-order merchants will be required to make deliveries within a reasonable time, notify the customer if his order has to be delayed, and return his money if requested.

The Rule provides that if a mail-order seller is unable to ship merchandise within the time stated in his offer (or if no time is specified, within 30 days) he must notify the buyer of the delay and give him the option of cancelling the order and having the purchase money refunded.

The buyer must be provided with a cost-free device—such as a postcard or postage-paid envelope—for this purpose. If the buyer does not respond, it will be assumed that he has consented to an additional 30-day delay. For any longer delay, the customer's express consent must be gained; otherwise the money is to be refunded.

The Rule also makes provision for indefinite delays if agreed to by the customer, though a refund must be made if requested any time during the delay. It also requires sellers of mail-order merchandise to have a reasonable basis for claims about shipping time.

In the event of a violation, the FTC can obtain a court order for compliance or they could have the company fined \$10,000 for each day of non-compliance. However, it is still legally debatable whether the FTC can go *directly* to Federal Trade Court.

Nationwide emergency channel adopted for police use

The FCC has designated 155.475 MHz as a nationwide emergency channel frequency for use in police emergency communications networks operated under statewide law-enforcement plans. The action was initiated on request of the APCO (Associated Public Safety Communications Officers).

Several states, APCO stated, now employ statewide emergency channels. It has been demonstrated that police can respond more effectively by using such common facilities. The 155.475 MHz frequency is limited to state police systems.

Operations on 155.475 MHz that are not now limited to emergency communications may continue until January 1, 1985.

Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback
editor-in-chief and publisher

Larry Steckler, CET, editor

Robert F. Scott, W2PWG, CET,
technical editor

Arthur Kleiman, associate editor

Jack Darr, CET, service editor

Leonard Feldman
contributing high-fidelity editor

David Lachenbruch, contributing editor

Karl Savon, semiconductor editor

Vincent P. Cicenia, production manager

Donna L. Glass, production assistant

Harriet I. Matysko, circulation director

Sheila Wertling, circulation assistant

Arline R. Bailey, advertising coordinator

Cover photo by Walter Herstatt

Cover design by Louis G. Rubsamen

Radio Electronics is a member of the Institute of High Fidelity and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics magazine is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback

Vice President: Larry Steckler

Treasurer: Carol A. Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

EAST

Stanley Levitan, Sales Manager
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Jim Reilly
The Ralph Bergen Co.
6319 N. Central Ave.
Chicago, IL 60646
(312) 792-3646

PACIFIC COAST Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
Sales Mart Building
1485 Bayshore Blvd., Box 140
San Francisco, CA 94124
(415) 467-0125

SOUTHEAST

J. E. Publishers Representative Co.
(214) 387-2424

TUNER SERVICE CORPORATION

SUBSTITUNER



JUST
\$44.95
U.S.A. ONLY
WITH CABLES

ONE YEAR
GUARANTEE

STILL ONLY



\$9.95
U.S.A. ONLY

FEATURES

- A UHF Tuner with 70 channels which are detented and indicated just like VHF channels.
- A VHF Hi Gain Solid State Tuner.
- AC Powered.
- 90 Day Warranty.

Demonstrate the **SUBSTITUNER** to your customers and show improved reception with their TV sets.

You may place your order through any of the Centers listed below.

REPAIR

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$ 9.95
UHF/VHF COMBINATION (U.S.A. ONLY) \$15.00

MAJOR PARTS AND SHIPPING CHARGED AT COST

- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

UNIVERSAL REPLACEMENT TUNER \$12.95 (U.S.A. ONLY)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10½" which can be cut to 1½".
- Specify heater type parallel and series 450 mA or 600 mA.

CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (U.S.A. ONLY)
- Send in your original tuner for comparison purposes to any of the centers listed below.

FLASH

NOW AVAILABLE—TUNER SERVICE PARTS CATALOG

OF ALL SARKES TARZIAN VHF AND UHF TUNERS, INCLUDING EXPLODED VIEW DRAWINGS. OVER 200 PAGES. ORDER YOUR COPY TODAY. SEND \$2.50 WITH ORDER TO BLOOMINGTON HEAD OFFICE.



WATCH US GROW

HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812-334-0411
ARIZONA	TUCSON, ARIZONA 85713	1528 S. 6th Ave.	Tel. 602-791-9243
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601	10654 Magnolia Boulevard	Tel. 213-769-9720
	BURLINGAME, CALIF. 94010	1324 Marston Road	Tel. 415-347-5728
	MODESTO, CALIF. 95351	123 Phoenix Avenue	Tel. 209-521-8051
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813-253-0324
	MIAMI, FLORIDA 33150	7641 N.W. 7th Avenue	Tel. 305-754-1352
	FT. LAUDERDALE, FLORIDA 33315	1045 W. 23rd Street, Bay 16	Tel. 305-522-0914
GEORGIA	ATLANTA, GEORGIA 30310	646 Evans Street, S.W.	Tel. 404-758-2232
ILLINOIS	CHAMPAIGN, ILLINOIS 61820	405 East University Street	Tel. 217-356-6400
	DOLTON, ILLINOIS 60419	1507-09 E. 142 Street	Tel. 312-841-4444
	SKOKIE, ILLINOIS 60076	5110 West Brown Street	Tel. 312-675-0230
INDIANA	INDIANAPOLIS, INDIANA 46024	112 West St. Clair Street	Tel. 317-632-3493
KENTUCKY	LOUISVILLE, KENTUCKY 40205	2244 Taylorsville Road	Tel. 502-452-1191
LOUISIANA	SHREVEPORT, LOUISIANA 71104	5025 Highland Avenue	Tel. 518-221-3027
MARYLAND	BALTIMORE, MARYLAND 21215	5505 Reisterstown Rd., Box 2624	Tel. 301-358-1186
MASSACHUSETTS	SPRINGFIELD, MASSACHUSETTS 01108	405 Dickinson Street	Tel. 413-788-8206
MISSOURI	ST. LOUIS, MISSOURI 63132	10500 Page Avenue	Tel. 314-429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue No. 1	Tel. 702-384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	1189 Pennsylvania Avenue	Tel. 609-393-0999
	JERSEY CITY, NEW JERSEY 07307	57-49 Tonnetta Ave. Hwy. 1 & 9	Tel. 201-792-3730
NEW YORK	ROCHESTER, NEW YORK 14615	37 Pullman Avenue	Tel. 716-647-9190
NORTH CAROLINA	GREENSBORO, NORTH CAROLINA 27401	2914 East Market Street	Tel. 919-273-6276
OHIO	CINCINNATI, OHIO 45216	7450 Vine Street	Tel. 513-621-5080
	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216-741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Avenue, P.O. Box 10111	Tel. 503-222-9059
PENNSYLVANIA	PITTSBURGH, PENNSYLVANIA 15209	503 1/2 Grant Avenue	Tel. 412-821-4004
TENNESSEE	MEMPHIS, TENNESSEE 38111	3158 Barron Avenue	Tel. 901-458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Road	Tel. 214-327-8413
VIRGINIA	NORFOLK, VIRGINIA 23513	3295 Santos Street	Tel. 404-855-2518
CANADA	ST. LAURENT, QUEBEC, CANADA, ALBERTA		

IF YOU WANT TO BRANCH OUT INTO THE TV TUNER REPAIR BUSINESS, WRITE TO THE BLOOMINGTON HEADQUARTERS ABOUT A FRANCHISE.

Circle 6 on reader service card

INTRODUCING THE FAST WORKING COUNTERS FROM HICKOK.



**Four affordable, deluxe
counters — one for every need.**

- MODEL 380.**
1 Hz to 80 MHz, 10 ppm **\$259**
- MODEL 380X.**
1 Hz to 80 MHz, 1ppm **\$385**
- MODEL 385.**
1 Hz to 512 MHz, 10ppm **\$499**
- MODEL 385X.**
1 Hz to 512 MHz, 1ppm **\$625**

Perfect for communications, CB, audio and digital work, servicing and laboratory applications.

Full 7-digit display with automatic decimal, full autoranging. **SPEED READ** mode updates display 5 times each second to aid tuning and adjustments.

Resolution is 1 Hz to 10 MHz, and 10 Hz to 80 MHz. Models 385, 385X feature a built-in prescaler to take you all the way to 512 MHz. Models 380X, 385X incorporate temperature compensated crystal oscillators with 1 ppm accuracy.

See these exciting new counters at your distributor now!

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

Circle 7 on reader service card

letters

AMERICAN TV STANDARDS

I note with horror that the changing of American TV standards is being seriously considered ("Looking Ahead", February issue). While it is true that the present system was developed in the middle 30's and the color system added to it in the early 50's, the system isn't all that bad. Consider:

- The information bandwidth in the present system is 4.2 MHz. Color sets normally pass about 3.5 MHz of it; black-and-white sets more like 2.5 to 3 MHz.
- The color signal consists of two variables, called I and Q, corresponding more or less to red-blue and green-purple separations. The I signal bandwidth is 1.5 MHz, the Q is 500 kHz. Most sets use 600 kHz for both.

- The soundtrack is required to have frequency response from 50 to 15,000 Hz —the same as "hi-fi" FM. Most sets come with amplifiers and speakers of quality similar to that of a portable transistor radio.

Clearly, if receiver manufacturers were convinced that the people would pay more for higher quality, they'd make sets that could take full advantage of this 25- to 35-year-old set of standards. Such a set wouldn't cost much more. But there are a few other reasons, all due to the TV stations and the networks:

- Many programs are on film, which has an inherent contrast limit compared to TV—film does not look "live." Most film uses an optical sound system, developed in the twenties. The frequency response, distortion, and signal-to-noise ratio are decidedly inferior to that of the transmitter.

- Networks limit audio frequency response from any source to about 200 to 5000 Hz, and signal-to-noise is well below the transmitter capability.

- Network shows delayed for viewing in the western half of the U.S. are played back one generation down, no matter what the source. This often causes color banding, usually seen as stripes of off-color or color contrast changes, especially in the red hues (which include most skin tones).

- Local newsfilm is 16 mm or super-eight, with the limited resolution already mentioned. Some improvement is made on the audio track of super-eight by use of magnetic recording, but it is partially offset by the even slower film speed.

- Electronic news-gathering (ENG) equipment, which uses videotape instead of film, uses less than one-fourth of the capability of the television channel, since the increased bandwidth would increase

the complexity, size, weight, and cost of those items.

- Almost all pay-TV "movie packages" are played from videocassettes, which have less than half the resolution the channel can provide. This degradation is obvious on almost any receiver.

If we were to go to a 1000-line system, we would no longer be compatible with Canada, Mexico, or Japan, just to name a few, and anything we presently have on videotape would be obsolete—we could scan-convert it, but that wouldn't improve it. The thought of "Let's Make A Deal" on a 10-foot screen makes me ill. Incidentally, the main resolution limitation on our present system is in the vertical direction, since that's across the lines, while the horizontal is continuous. Vertical resolution could be doubled by going to a 4:1 interlace instead of the present 2:1, and still be compatible with all the TV sets in the country. Such an arrangement could be switched on and off at will by the TV station, FCC consenting.

Let's hope that nobody's serious about all this. Look at the picture from an Advent 7-foot screen projector set—it ain't half bad. And there's always the movies.
JAMES REIGER
Ridgecrest, CA

COMPUTER HOBBYISTS

To me, the most critical thing in the hobby market right now is the lack of good software courses, books and software itself. Without good software and an owner who understands programming, a hobby computer is wasted. Will quality software be written for the hobby market?

Almost a year ago, Paul Allen and myself, expecting the hobby market to expand, hired Monte Davidoff and developed Altair BASIC. Though the initial work took only two months, the three of us have spent most of the last year documenting, improving and adding features to BASIC. Now we have 4K, 8K, EXTENDED, ROM and DISK BASIC. The value of the computer time we have used exceeds \$40,000.


The feedback we have gotten from the hundreds of people who say they are using BASIC has all been positive. Two surprising things are apparent, however. 1) Most of these "users" never bought BASIC (less than 10% of all Altair owners have bought BASIC), and 2) The amount of royalties we have received from sales to hobbyists makes the time spent of Altair BASIC worth less than \$2 an hour.

Why is this? As the majority of hobbyists must be aware, most of you steal

(continued on page 16)

Sleeper!

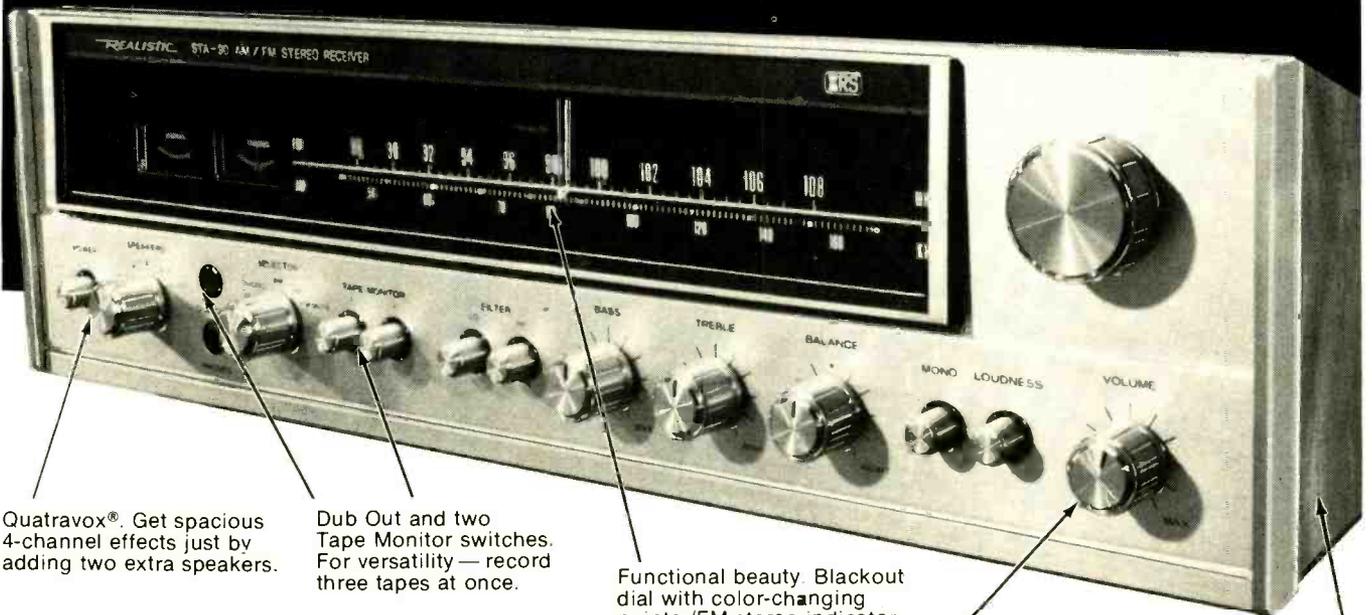The Realistic® STA-90 Will Change Your Ideas About Who's #1 in Hi-Fi Features, Value and Style!




Quatravox®. Get spacious 4-channel effects just by adding two extra speakers.

Dub Out and two Tape Monitor switches. For versatility — record three tapes at once.

Functional beauty. Blackout dial with color-changing pointer/FM stereo indicator.

Solid metal knobs.

Walnut veneer case.

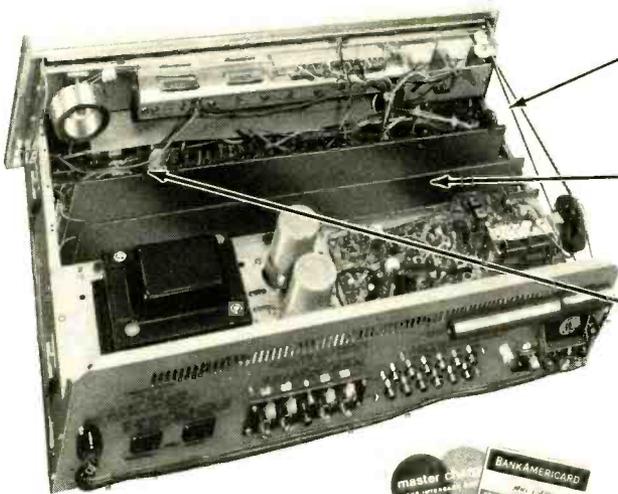

Dual-Gate MOSFET FM. Gets weak stations and still resists overload. Superior to FET designs.

Phase-locked loop FM stereo demodulator. For wider channel separation, almost zero distortion.

Direct-coupled amplifiers for powerful bass even at 20 Hz. 44 watts per channel, minimum RMS at 8 ohms from 20-20,000 Hz, with no more than 0.5% total harmonic distortion.

Amplifier Specs

Power Bandwidth: 17-35,000 Hz
 Response: 20-20,000 Hz \pm 2 dB
 IM Distortion: 0.3% at 30W
 Phono Overload: 150 mV
 Hum and Noise (dB):
 Phono 1, -60
 Aux 1, -75

FM Tuner Specs

Sensitivity: 2.0 μ V IHF
 S/N Ratio: 65 dB
 Separation: 35 dB at 1 kHz
 Total Harm. Dist.: 0.8%
 Capture Ratio: 2 dB
 Selectivity: 60 dB

Only 359.95 at participating stores and dealers. Prices may vary at individual stores. U.L. listed. Ask for 31-2063. See what a Sleeper looks like — today!




SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack®

A TANDY CORPORATION COMPANY
 OVER 4000 STORES • 50 STATES • 8 COUNTRIES

FREE 164-Page Catalog. Write to Radio Shack, P.O. Box 1052, Dept. 720, Ft. Worth, TX 76101

Circle 8 on reader service card

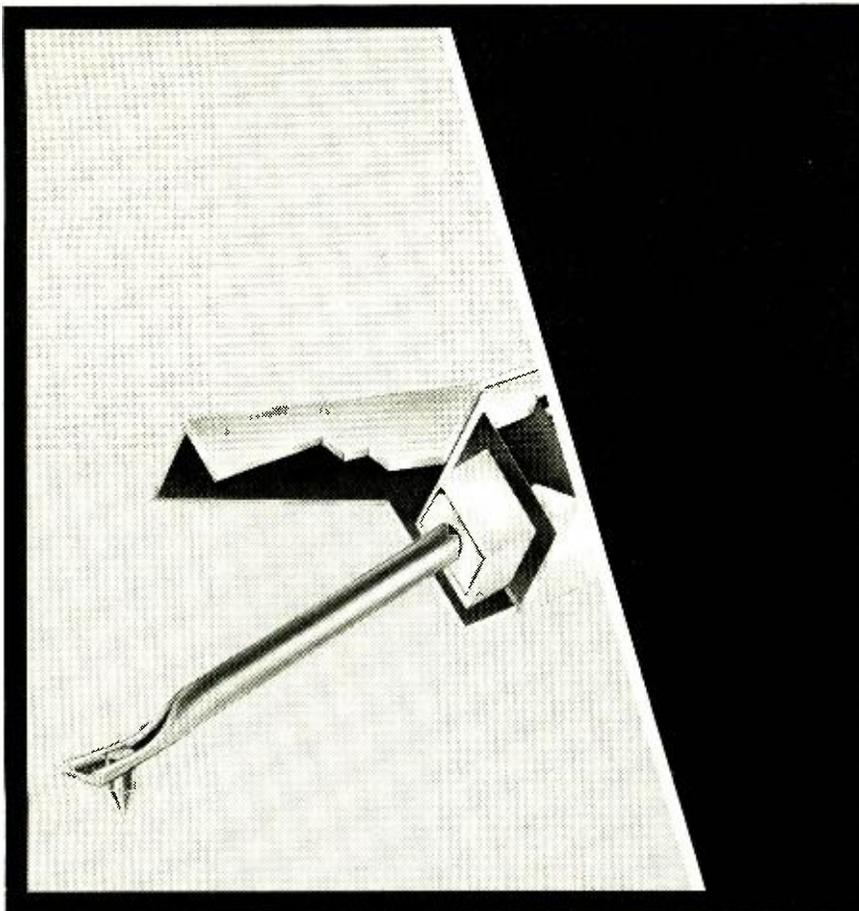

This...protects your most expensive hi-fi investment.

Recognizing that a penny saved is a penny earned, may we suggest that trying to economize by putting off the replacement of a worn stylus could be like throwing away five dollars every time you play a record. (Multiply that by the number of records you own!) Since the stylus is the single point of contact between the record and the balance of the system, it is the most critical component for faithfully reproducing sound and protecting your record investment. A worn stylus could irreparably damage your valuable record collection. Insure against this, easily and inexpensively, simply by having your dealer check your Shure stylus regularly. And, when required, replace it immediately with a genuine Shure replacement stylus. It will bring the entire cartridge back to original specification performance. Stamp out waste: see your Shure dealer or write:



Look for the name SHURE on the stylus grip and the words "This Stereo Dynetic® stylus is precision manufactured by Shure Brothers Inc." on the box.

Shure Brothers Inc.
222 Hartrey Ave., Evanston, IL 60204
In Canada: A. C. Simmonds & Sons Limited



Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

Circle 9 on reader service card

LETTERS

(continued from page 14)

your software. Hardware must be paid for, but software is something to share. Who cares if the people who worked on it get paid?

Is this fair? One thing you don't do by stealing software is get back at MITS for some problem you may have had. MITS doesn't make money selling software. The royalty paid to us, the manual, the tape and the overhead make it a break-even operation. One thing you do do is prevent good software from being written. Who can afford to do professional work for nothing? What hobbyist can put 3-man years into programming, finding all bugs, documenting his product and distribute for free? The fact is, no one besides us has invested a lot of money in hobby software. We have written 6800 BASIC, and are writing 8080 APL and 6800 APL, but there is very little incentive to make this software available to hobbyists. Most directly, the thing you do is theft.

What about the guys who re-sell Altair BASIC, aren't they making money on hobby software? Yes, but those who have been reported to us may lose in the end. They are the ones who give hobbyists a bad name, and should be kicked out of any club meeting they show up at.

I would appreciate letters from any one who wants to pay up, or has a suggestion or comment. Just write me at 1180 Alvarado, SE, #114, Albuquerque, New Mexico 87108. Nothing would please me more than being able to hire ten programmers and deluge the hobby market with good software.

BILL GATES
General Partner, Micro-Soft
Albuquerque, NM

OOOOPS!

In your February, 1976, Computer Korner example on page 88, it appears that you have mixed up your architecture and the direction of the moves.

With architecture B; to move A to output requires:

- 02 (move A to C)
- 07 (move C to output)

But if C contains needed data, the instructions should be:

- 06 (move C to B) not B to C
- 02 (move A to C)
- 07 (move C to output)
- 04 (move B to C)

PHILLIP L. EDELSBERG
Systems Analyst
Indianapolis, IN

R-E

DON'T MISS THEM!

This month's hi-fi test reports include two stereo receivers. One is the Marantz model 2325 and the other is Lafayette's model LR-2200. See how these two receivers match-up against each other. Turn to pages 50 and 56 for the complete story and full specifications.

16 ways to move ahead in electronics!



Choose the one that's just right for you...the one that can make your future more rewarding, more secure, more enjoyable...starting now! These ways to move ahead are yours from Electronics Technical Institute...the finest electronics home study courses and programs ever offered!

Fundamental Electronics

Get a solid foundation for entering the fast-moving world of electronics where today is great, and tomorrow will be greater. Learn it the simple, easy, step-by-step, programmed way called *Autotext*, exclusive with ETI!

Electronics Drafting

Learn a vitally needed specialty that translates new technological concepts and developments to the practical drawing board. Become a specialist-in-demand, through ETI's training. Learn it at home...get your future moving now!

Color TV Servicing

There's a real future waiting for the established color television technician. You become that technician through this program that takes you step-by-step to *theoretical and practical* mastery of color TV. Get your tomorrow started today!

Master TV/Radio Servicing

Here is true "master" preparation for a career that can take you as far as you want to go into radio and television servicing, both black and white, and color. The helpful, practical ETI way can be your way to more money, security, success!

Communications

ETI's communications program opens up a whole range of career development possibilities in electronics. Solid-state receivers, solid-state audio equipment, communications equipment, CATV, as well as preparation for FCC-licensed positions in commercial broadcasting and mobile communications. You can find a real future here!

Industrial Electronics

You open great career opportunities through this program, as instrumentation technician, electronic equipment maintenance technician, electronic calculating machine technician and audio technician. It also prepares you to move into and up in communications, automation and industrial electronics!

Digital Technology

Join the digital revolution which is radically altering our lives today and tomorrow. Get solidly trained in the new digital specialties that can lead to a real future as a digital control technician, electronic calculating machine technician, field representative, computer sales representative, manufacturer's representative.

Electronics Technology

Learn electronics across the board! You'll be ready for real career advancement with training that can lead to technical positions in communication, automation and industrial electronics, and can also help you in sales positions, management and administration.

Computers

ETI offers training opportunities in Computer Technology and Computer Programming. Learn at home, and get ready to enter a field where incredible developments are sure to continue. It's practical, useful—the step-by-step ETI way!

Advanced Electronics

Want greater challenges and career advancement? This course is for you. It can be valuable preparation not only for a technical career, but also for the fields of sales, management and administration. Make your move now!

Digital Electronics—Advanced

Here's a special course for those already in the field of digital electronics, ready to move into more advanced areas. This is how to move up in sales, management and administration. Here's your tomorrow!

Black and White TV Servicing—Advanced

This can be your own "advance" course to black-and-white TV competence from A to Z. You'll construct a receiver yourself, if you wish. A key to lifetime success!

Industrial Instrumentation—Advanced

Move up in the world...the wonderful electronics world! This course opens up a whole range of careers in the industrial field, as instrumentation technician, laboratory technician, process control technician or electronic calculating machine technician. Get ready...and go!

Color TV Servicing—Advanced

Here is the "graduate" course in color TV for those who already know television fundamentals. You'll learn color TV from top to bottom, build your own set if you choose. A great way to build your future!

Solid-State Electronics—Advanced

Applications of transistors are increasing all the time and the transistor may be a breakthrough

comparable in importance to the development of nuclear energy. Solid-state can mean your solid career development, too, through ETI!

FCC License Preparation

Here is real down-to-earth practical preparation to take your 3rd, 2nd or 1st class Federal Communication Commission Radio-telephone License examinations. Get yourself ready now for any of the FCC-licensed positions involving broadcasting, mobile communications, microwave communications links, marine communications equipment or in many other positions in solid-state, communications, CATV. Get ready for tomorrow...today!

Get all the facts...free!

Send the coupon now for ETI's colorfully illustrated new



44-page catalog giving you all the details. You owe it to yourself. There's no obligation, and no salesman will call. Send for yours today!

Electronics Technical Institute

Division of Technical Home Study Schools

Electronics Technical Institute, Dept. 2-479-056
Little Falls, New Jersey 07424

Send me the Electronics Technical Institute Catalog.

Name _____ (please print)
Address _____
City _____ State _____ Zip _____

Interested in another field? Check the Technical Home Study School program that interests you most. No salesman will call. PLEASE CHECK ONLY ONE.


Typewriter and Office Machine Repair Locksmithing
 Upholstery and Decorating Legal Investigation
 Accident and Insurance Claim Adjusting Security/Alarm Business
 Outdoor Careers in Conservation Photography

Check here for information on Veterans Benefits.
 Check here for information on learning by cassettes.

Circle 10 on reader service card

The IMSAI 8080.

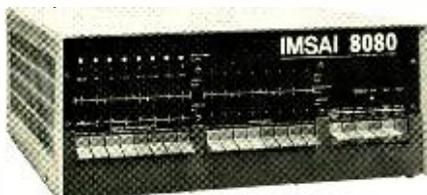A commercial yet personally affordable computer.



If you thought you could never afford a computer at home, think again. The IMSAI 8080 is built for rugged industrial performance. Yet its prices are competitive with Altair's hobbyist kit. Fully assembled, the 8080 is \$931. Unassembled, it's \$599.

The IMSAI 8080 is made for commercial users, and it looks it. Inside and out. The cabinet is attractive, heavy gauge aluminum. The heavy duty lucite front panel has an extra 8 program controlled LED's. It plugs directly into the Mother Board without a wire harness. And rugged commercial grade paddle switches are backed up by reliable debouncing circuits.

The system is optionally expandable to a substantial system with 22 slots in a single printed circuit board. And the durable card cage is made of commercial-grade anodized aluminum.

The IMSAI 8080 power supply produces a true 20 amp current, enough to power a full system. You can expand to a powerful system with 64K of software protectable memory plus an intelligent floppy disk controller. You can add an audio tape cassette input device, a printer plus a video terminal and a teletype. And these peripherals will function with an 8-level priority interrupt system. BASIC software is available in 4K, 8K and 12K.

Get a complete illustrated brochure describing the IMSAI 8080, options, peripherals, software, prices and specifications. Send one dollar to cover handling to IMS. The IMSAI 8080. From the same technology that developed the HYPERCUBE Computer architecture and Intelligent Disk systems. Dealer inquiries invited.

IMS

IMS Associates, Inc.
1922 Republic Avenue
San Leandro, CA 94577
(415) 483-2093

Circle 11 on reader service card

KOMPUTER KORNER

How to interface the microcomputer with input/output devices.

DAVID LARSEN, PETER RONY,
and JOHN TITUS*

THE VARIOUS DATA PATHS IN A MICROCOMPUTER consists of the data input, data output, external device addressing, in and out function pulses, and interrupt signals. These are the vital lines of communication between the microcomputer and the "outside world", for example, those signal lines that are necessary to interface the micro-processing unit (MPU) to the input/output or I/O devices that you would like to control.

What is an I/O device?

Some useful definitions include the following:

input/output—General term for the equipment used to communicate with a computer and the data involved in the communication.¹

I/O—Abbreviation for input-output.²

I/O device—Input/output device. Any digital device, including a single integrated-circuit, that transmits data to or receives data or strobe pulses from a computer. The in and out functions are always

when serving as an output device, may require up to four device-select lines from the microcomputer. Therefore, the fact that we can generate 256 different input and 256 different output device-select pulses does not necessarily mean that we can address 512 different "devices." A more reasonable number is of the order of 50 to 100 different devices.

Device-select pulses are inexpensive and easy to implement. We encourage you to use them as often as possible as you attempt to substitute computer software for integrated circuit hardware. We shall repeat this theme often: software vs. hardware. There exists a tradeoff between the two, but your main objective in using microcomputers will usually be to substitute software for hardware. When you do so, the only penalty that you may pay is time—it takes time to execute computer instructions. If you can accept the delays inherent in computer programs, then you can vastly simplify the circuitry required to accomplish a specific interfacing task.

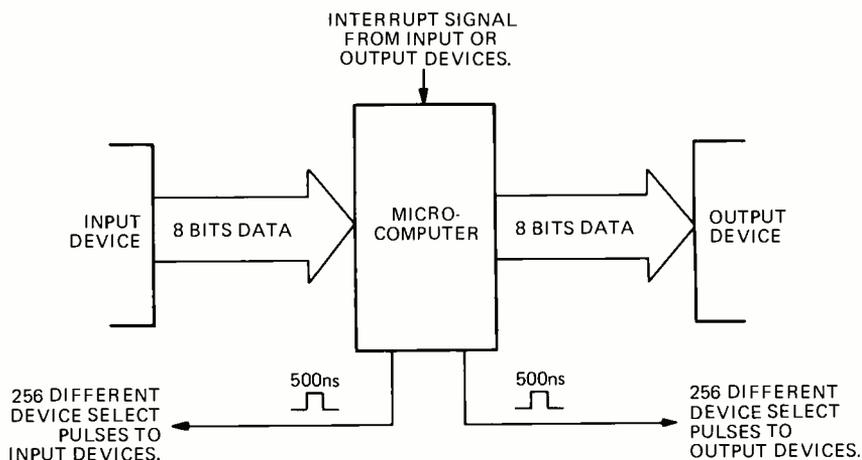


FIG. 1

referenced to the computer.³

The traditional view of an I/O device is that it is somewhat large or complex. Card readers, magnetic tape units, cathode-ray tube displays and teletypes certainly fit such a description. However, a single integrated circuit such as a latch, shift register, counter or small memory can also be considered to be an I/O device to a computer.

Another important point is that several device-select pulses may be required to interface a single I/O device. For example, a 74198 shift register has a pair of control inputs that determine whether the register shifts left, shifts right, or parallel-loads 8-bits of data. This IC also has a clock input and a clear input. Thus a single 74198,

*This article is reprinted courtesy American Laboratories.

Interfacing

Interfacing can be defined as the joining of members of a group (such as people, instruments, etc.) in such a way that they are able to function in a compatible and coordinated fashion. By "compatible and coordinated fashion," we usually mean synchronized. Some important definitions include the following:

synchronous—In step or in phase, as applied to two devices or machines. A term applied to a computer where a sequence of operations is controlled by equally spaced clock signals or pulses.²

synchronous computer—A digital computer that has all ordinary operations controlled by equally spaced signals from a master clock.²

(continued on page 22)

mail-order pride!...

The new Heathkit Spring Catalog describes over 400 top-value electronic kits you can build for pride and satisfaction that's priceless!


Learn electronics the easy, effective low-cost way with the **Heathkit Continuing Education Series**. Four individual learning programs — DC Electronics, AC Electronics, Semiconductor Devices and Digital Techniques provide a detailed overview of modern electronics. Study when you want... without pressure or deadlines. Each program includes text, records and parts for experiments.



Our **IM-4100** counts frequency to 30 MHz, period to 99.999 seconds, events to 99,999. Has bright five-digit readout with gate lamp and overrange indicator, built-in input attenuation, three-way AC or DC operation. You can count on it for value!



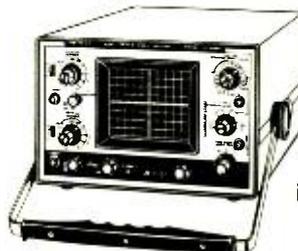The **IO-4550** is a lab-grade dual-trace DC-10 MHz scope at a low build-it yourself price. It features digitally-controlled time base, automatic triggering, extra bright trace and faster writing time. It's all the scope you need for most any lab or service application.



The **ET-3300** laboratory breadboard puts a lot of design versatility on your bench. Solderless sockets, built-in 5 and 12-volt power supplies, dual ground and power bus strips make solid-state circuit design fast, easy and precise.



Read all about them... PLUS over 400 other easy-to-build electronic kits

MAIL COUPON TODAY!

FREE!
HEATHKIT CATALOG
The world's largest selection of quality electronic kits



- Test and Measuring Instruments
- Marine and Automotive Accessories
- Amateur Radio
- Color TV
- Audio Components


Heath Company, Dept. 20-17
Benton Harbor, Michigan 49022

HEATH	
Schlumberger	
Heath Company Dept. 20-17 Benton Harbor, Michigan 49022	
Please send me my FREE Heathkit Catalog.	
Name _____	
Address _____	
City _____	State _____
	Zip _____
CL-596A	

Circle 100 on reader service card

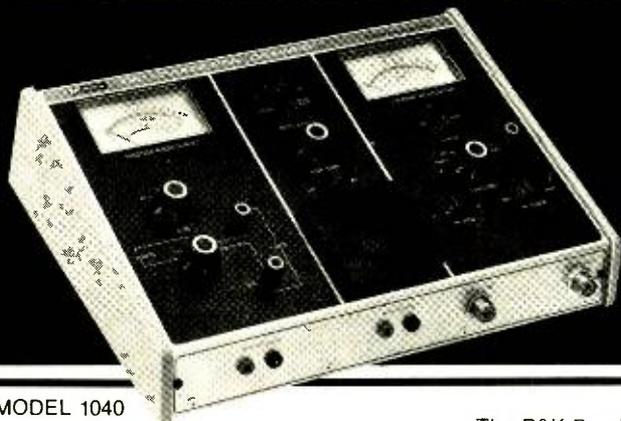Get in on the CB Service BOOM with the B&K Test Bench





WITH THE MODEL 1040 CB SERVICEMASTER IT'S EASY, IT'S FAST AND IT'S PROFITABLE.

MODEL 1040
\$250

The B&K-Precision CB Servicemaster is designed for rapid programmed testing and trouble shooting of any CB transceiver.

It functions as a test center and enables you to quickly check all of the significant performance characteristics of the transceiver with one hook-up—in a matter of minutes.


When used with a scope and signal generator, you can:

- Measure signal-to-noise ratio of CB receiver
- Measure audio output power
- Measure audio distortion percentage
- Measure receiver sensitivity
- Check AGC
- Measure effectiveness of CB noise limiter or blanker (when used with an impulse noise generator)
- Measure squelch threshold
- Measure adjacent channel rejection
- Measure transmitter AM power output—even mobile!
- Measure SSB power output with TRUE peak-reading RF wattmeter
- Check AM modulation
- Check SSB modulation with a two-tone test—the only accurate way!
- Measure antenna SWR—even mobile!
- Check the transceiver in the car to determine if the problem is in the antenna system or the transceiver

You can save \$500—\$1,500 in equipment costs because the CB Servicemaster eliminates many of the test instruments you would otherwise need for CB servicing. These instruments, or their functions, are built into the unit:

- Audio wattmeter
- Audio generator
- Distortion meter
- RF Wattmeter/dummy load
- DB meter
- SWR bridge


These instruments—which you should have, if you don't own them already, are all you need to get the maximum use from your CB Servicemaster. And the B&K CB Servicemaster is compatible with most oscilloscopes, frequency counters, signal generators and power supplies on the market today.

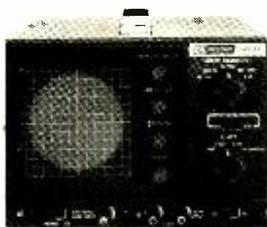

MODEL 1403A—3", 5 MHz Recurrent Sweep Oscilloscope

Checks CB modulation and provides viewing of 27MHz CB waveform when used with the Model 1040. Small, compact and inexpensive, it frees other scopes for more effective use.


Model 1403A \$198.

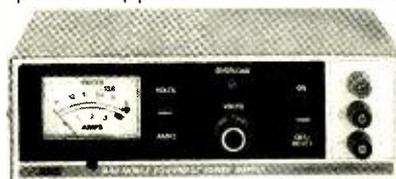

MODEL 1640—Regulated Power Supply

Designed especially for CB and other mobile equipment, the 1640 eliminates changes in supply voltage due to load variations. A stable power supply is essential to precise testing of the transceivers. Less than 0.8% variation from zero to full load 3 amps continuous, 5 amps surge. Adjustable to any output from 11 to 15 VDC. Suppressed zero scale for greater accuracy. Overload protected.


Model 1640 \$100

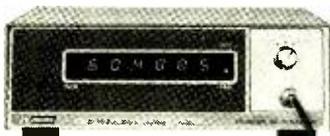

MODEL 1801—Digital Frequency Counter

To quickly determine the exact frequency of a CB channel, the 1801 automatically displays it for you in large, easy-to-read digits. You can tune oscillators precisely (to 1Hz, if necessary), conduct audio frequency analysis tests. Six digit display is updated five times per second. Accuracy to 1Hz guaranteed to 40MHz; 60MHz typical.

Model 1801 \$240.

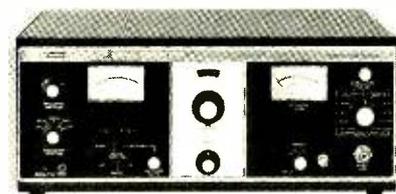

MODEL 2040—CB Signal Generator

Covers all 23 channels, AM and SSB with built-in capability of 64 additional channels for future FCC assignments. Ultra-stable crystal-controlled, phase-locked-loop frequency generation. Has 10 ppm accuracy, 1 μ V to 100 MV output in calibrated 10 dB increments for receiver sensitivity measurements. Includes EIA standard noise test signal generator to check receiver noise suppression. Internal 400, 1000 and 2500 Hz modulating frequencies—can also be externally modulated. Internal protection against 5W RF input.

Model 2040 \$475

For additional information, contact your B&K-Precision distributor for our comprehensive brochure describing the operation of the Model 1040 CB Servicemaster and the CB Service Center—or write us for your free copy.

B&K PRECISION

DYNASCAN CORPORATION
Makers of Cobra CB Equipment

1801 W. Belle Plaine Ave.
Chicago, IL 60613 • (312) 525-3990
In Canada: Atlas Electronics, Toronto

Circle 12 on reader service card

7623

MAY 1976

21

synchronous operation—Operation of a system under the control of clock pulses.³

synchronization pulses—Pulses that are originated by the transmitting equipment and introduced into the receiving equipment to keep the equipment at both locations operating in step.²

computer interfacing—The synchronization of digital data transmission between a computer and one or more external input/output devices.³

Although the details of computer interfacing vary with the type of computer employed, the general principles of interfacing apply to a wide variety of computers. Such principles include the following:

- The digital data transmitted between a computer and an I/O device are either individual clock pulses or else full data words.
- The computer and the I/O device are both clocked devices. At the very least, the I/O device has a single flip-flop that is set or reset by the computer. All data transmission operations are synchronized to the internal clock of the computer.
- The computer sends synchronization pulses, called device-select pulses, to the I/O device. These pulses are generated by the computer program and are usually quite short—for an 8080 microcomputer operating at 2 MHz, they last for only 500 ns. The pulses synchronize and select at the same instant of time.
- Individual device-select pulses are sent

to individual input or output devices. This is called *external device addressing*. The pulses are used for latching data output and strobing data input.

• Computer program operation can be interrupted by the transmission of a clock pulse from an I/O device to a special input line to the computer. This is called *interrupt generation*. Upon being interrupted by an external I/O device, the computer goes to a computer subroutine that responds to, or *services*, the interrupt.

• Full data words can be output from, or input into, the accumulator register. For the 8080 microcomputer, a full data word contains 8 bits. Output data from the accumulator is available for only a very short period of time and usually must be latched. Input data into the accumulator is acquired over a very short period of time and usually must be strobed into the accumulator.

Interfacing basically consists of the synchronization of parallel input or output data via the use of the 512 device-select pulses. (See Fig. 1.) Hardware is required to tie the MPU to the external device and is just as important as the microcomputer software. We shall tackle both of these facets of microcomputer interfacing in detail in subsequent columns. **R-E**

References

1. *Microprogramming Handbook* (Santa Ana, CA: Microdata Corporation, 1971).
2. Rudolf F. Graf, *Modern Dictionary of Electronics*, Howard W. Sams and Company, Inc., Indianapolis, IN, 1972.
3. *Bugbook III* (Derby, CT: E & L Instruments, 1975).


Solid-State News

National Semiconductor has submitted a 4K RAM memory that is different from the competition.

The MM5270 Tri-Share™ 4096 × 1 bit RAM is packaged in an 18 pin DIP in contrast to the industry standard 22 pin packages. Three functions share the use of a single lead—read/write, logical chip select and V_{cc}. One lead is also used for both data input and output.

The 18-pin packages can be squeezed in with a density nearly twice that possible with the 22-pin packages. National claims memory system costs are kept low because of the savings in PC cards, card frames, connectors and wiring. The cost of the memory package itself is lower. The access and cycle times are 200 ns and 400 ns, respectively.

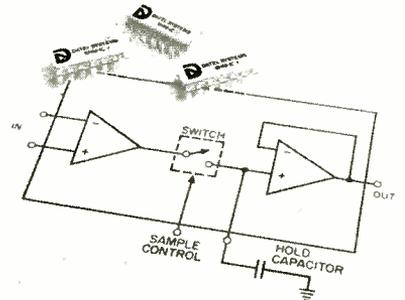RCA has also joined the NMOS memory field with the MW70011D 1024 x 1 bit static RAM. The device is pin compatible with the AMS70011 and has a 60 ns maximum access-time and 180 ns maximum cycle-time. Also planned is a 4096 bit dynamic RAM.



DATEL SYSTEMS SHM-IC-1 high performance sample-and-hold.

Both the National and RCA chips are TTL compatible except for the chip select input.

The SHM-IC-1 from Datal Systems is a high performance sample-and-hold that uses only an external storage capacitor. Sample-and-hold systems are used in sampled data control systems, in the reconstruction of sampled waveforms and for data acquisition.

Acquisition time is 4 μs with a .001 μF capacitor; the signal droop is 50 mV/s. The capacitor can be lowered to 100 pF for a faster 2 μs acquisition time, but droop also increases in the same ratio.

Three blocks make up the sample and hold. A high gain input differential amplifier, the electronic sampling switch, and an output buffer amplifier. The SHM-IC-1 sells for \$29 in small quantities.

Revolutionary New Wiring "Pencil" Makes Interconnections in 1/3 the Time!


- Create Finished Wired Circuits in Hours, Not Days
- For Breadboarding, Prototypes and Production
- Interconnects Circuit Elements in Digital and Analog Circuits

Easy for anyone — just hook up your components using the insulated "solder thru" wire (your choice of blue, red, green or clear). Wire feeds off a replaceable spool thru the P173 tool body and out of a steel tip so fine it easily routes wire around even the smallest I.C. lead. A touch of the iron, with solder, completes the joint.

Available accessory items include P179WS Wire Spacers for neat routing, tenth-tenth Micro-Vectorboards®, circuit Padboards and frames, like the 3677-6 and 51X-1. Order a P173 Now! Supplied with two 200' spools of AWG solder thru wire (1 red, 1 green), complete instructions. **\$9.50**


At your Vector distributor
Mail orders, add \$2 shipping and handling charge.
California residents add 6% sales tax.

VISIT OUR BOOTH 2122 AT ELECTRO '76

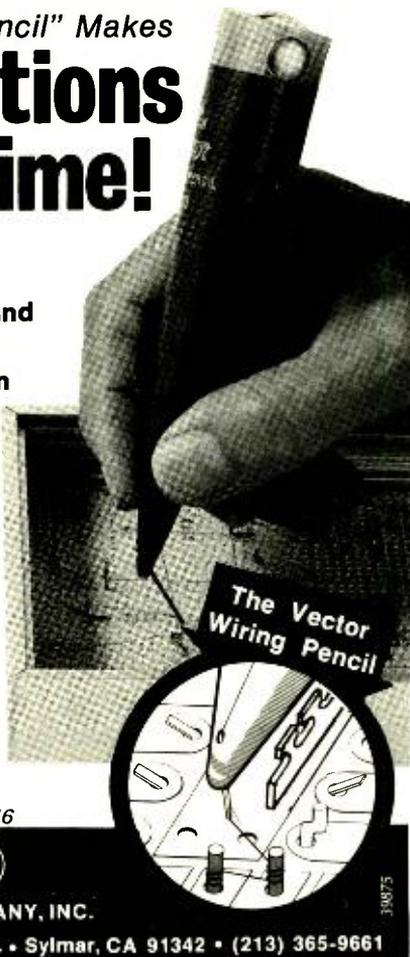

Vector W P DIVISION
ELECTRONIC COMPANY, INC.
12460 Gladstone Ave. • Sylmar, CA 91342 • (213) 365-9661

POWER

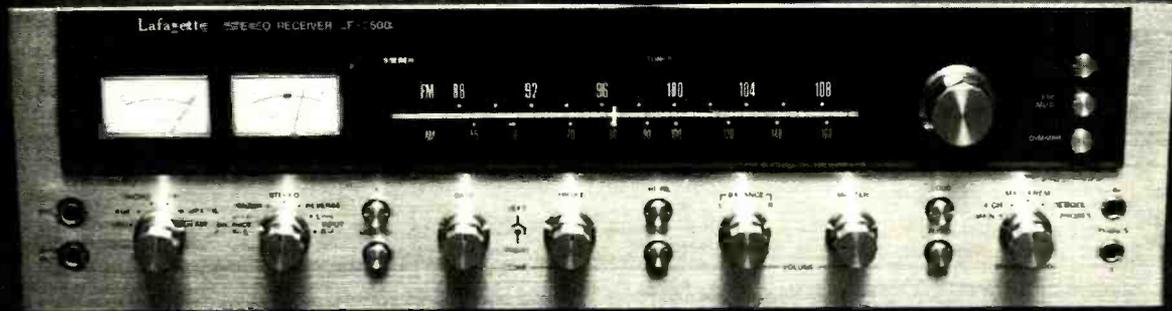

IN DRESS ATTIRE.

There's plenty of power packed in this beautiful receiver. Muscle your receiver needs for more than just sound volume. Power produces clear distortion-free sound. And it gives it to you even at low volume.

The Lafayette LR-3500 has a well-developed 47 watts per channel minimum RMS. Both channels driven at 8 ohms from 20-20,000 Hz with no more than 0.5% total harmonic distortion.

The top of the Lafayette line, the LR-3500 AM/FM stereo FM receiver has all the features you've come to expect as the trappings of power. It has state-of-the-art electronics, complete power controls to personalize the sound. And many convenience features like dual tape monitors, and FM mute.

Power is yours with the Lafayette LR-3500. It's \$399.95 at your Lafayette dealers. There are dealers coast to coast. Or shop from our free catalog.

The Lafayette LR-3500 can make your dreams for power come true.

Electrically Speaking,
Who Knows Better Than

Lafayette

Radio Electronics & Shopping Centers

© Lafayette Radio Electronics Corporation 1976 • 111 Jericho Turnpike, Syosset, N.Y. 11791


Circle 14 on reader service card

ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

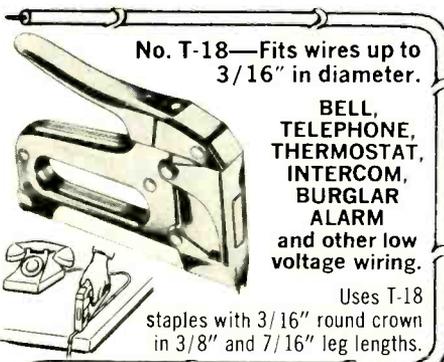
SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!



No. T-18—Fits wires up to 3/16" in diameter.

BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.

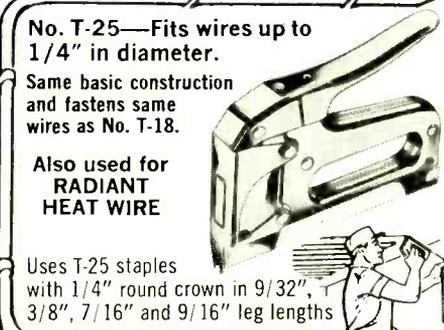Uses T-18 staples with 3/16" round crown in 3/8" and 7/16" leg lengths.




No. T-25—Fits wires up to 1/4" in diameter.

Same basic construction and fastens same wires as No. T-18.

Also used for RADIANT HEAT WIRE

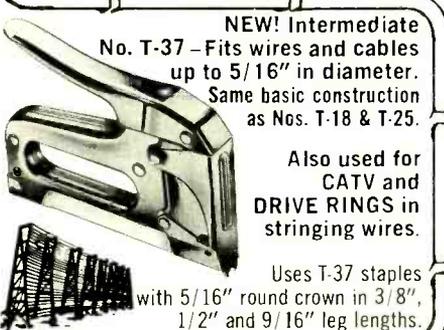Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths




NEW! Intermediate No. T-37—Fits wires and cables up to 5/16" in diameter.

Same basic construction as Nos. T-18 & T-25.

Also used for CATV and DRIVE RINGS in stringing wires.

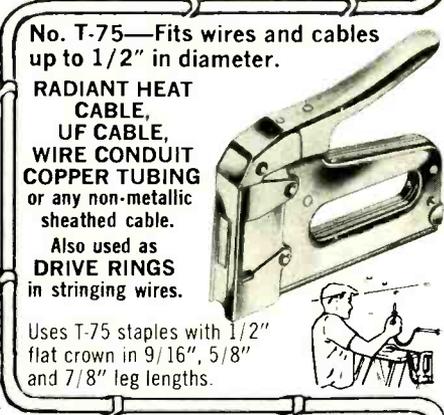Uses T-37 staples with 5/16" round crown in 3/8", 1/2" and 9/16" leg lengths.



No. T-75—Fits wires and cables up to 1/2" in diameter.

RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.

Also used as DRIVE RINGS in stringing wires.

Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

equipment reports

American Technology Corp. ATC-10 Color Pattern Generator



Circle 97 on reader service card

THE AMERICAN TECHNOLOGY CORP., 225 Main St., Canon City, CO 81212, is one of the new "high-technology" companies in the test-equipment field. Their first instrument is a color-bar pattern generator, model ATC-10. This is an all solid-state instrument, using the newest digital IC techniques to produce not only the stock test patterns, but several new ones. Its a versatile instrument that will do all of the regular things, and many others as well; its really a "Color-Bar-Plus" generator!

The ATC-10 uses 31 digital IC's, an IC-regulated DC power supply, and is well made. For stability, all frequencies, line-widths and spacing are crystal controlled. Due to the crystal control, all patterns are as solid as a rock.

All of the standard test patterns can be used for purity, convergence and color alignment. The ATC-10 provides 10 x 10 dot, crosshatch, vertical and horizontal lines, and the standard 10-bar gated rainbow color patterns.

Now for the new patterns. There is a Hatchdot—a crosshatch with a single dot in the exact center. There is also a Hatchdots pattern—a crosshatch with center dot and a "frame" of dots all the way around the edges. Handy for centering and linearity adjusting. By the way, the center dot in the dots pattern is isolated—the dot above and below the center is blanked out so that you can identify it instantly.

In the 10-bar color-bar pattern, the 6th (blue) bar is "flagged"—there is a blank in the center that saves a lot of counting! The ATC-10 actually has three color-bar patterns in all. The next one is called Vector. This is the 10-bar pattern with the luminance signal blanked out. It produces much sharper vectoroscope patterns. The last one is really useful. This one is called 3.58 Monitor and it is the ten-bar pattern once more, but this time the burst has been blanked out. You will see exactly the same effect you get when you ground the burst-amplifier grid to let the TV set's

3.58 MHz oscillator free wheel. You can do this without taking the back of the set off. If the color bars float or fall out of sync, you definitely know that the 3.58 MHz oscillator is or isn't able to run on-frequency.

The next color pattern is one called Red Raster. It's a 3.58 MHz signal that is 67.5-degrees away from the burst. You do not have to do anything to the receiver aside from turning the color control up. (Painless purity!) Turn the color-control down and the brightness up, and you get a clear white raster for checking gray-scale adjustments. For another test like this, turn to the GRAY QUAD position. This displays a screen divided into four segments—white, light gray, dark gray and black. This can also be used to check deflection yoke polarity. If the white quadrant isn't in the lower right corner, one of the yoke windings is reversed. There are eleven different test patterns in all. Since all of these have their chroma and sweep frequencies tightly phase-locked, the stability is excellent. Another automatic circuit prevents over-modulation.

The RF output of the ATC-10 is on channel 2, crystal controlled. If channel 2 is used in your area, you can change to channel 3 by installing another crystal. The RF output of the ATC-10 can be varied from 15 μ V to 90,000 μ V at 75-ohms output, and 180,000 μ V on the 300-ohm output. There is also an IF crystal-controlled output at 45.75 MHz. To obtain this, just pull out on the RF gain-control knob.

Both 75- and 300-ohm output cables are provided. These two cables and the line cord stow in a compartment provided in the back of the case. The 75-ohm IF output can be used to check the tuner in any TV set. In sets with the IF input soldered, just hook the cable right across the terminals. There is ample output.

Video signals, in either sync polarity are available from a separate jack. These too are variable, from 0 to 1.8 volts P-P. Both IF, RF and video outputs may be used at the same time. One novel use for this is to feed the video signal directly to one trace of a dual-trace scope and feed the signal picked up from the TV set to the lower trace input. (The signal may be fed to the TV antenna input or IF input.) This will let you use the burst signal from the video for phase checks, bandwidth and several other things in the TV set circuitry. The luminance pedestal in the color-bar pattern is a good square wave. By tracing this through the TV set's video circuitry, you can check damping, bandwidth, frequency and phase response. Works in other stages as well, of course.

(continued on page 30)

Now you can order GE TV parts over the phone, toll-free*, and charge them to your credit cards.



Now simply call in your GE TV part order toll-free* and charge it to your Master Charge or BankAmericard account (give number and expiration date on the phone). Your order can be processed immediately.

This new arrangement eliminates costly COD charges, time-consuming credit checks or having to send cash with an order. This easy order procedure is just one more example of General Electric's on-going dedication to making your business easier.

*TOLL FREE TELEPHONES NOW AVAILABLE IN MOST STATES.

Send in this coupon for the handy brochure covering GE's toll-free phone numbers and other support programs.

We're making it our business to make your business easier.

"DUTCH" MEYER
 GENERAL ELECTRIC COMPANY
 TELEVISION BUSINESS DEPARTMENT
 COLLEGE BOULEVARD
 PORTSMOUTH, VA. 23705

Please send me the brochure covering GE's toll-free phone numbers and other support programs.

NAME _____
 SERVICE COMPANY _____
 ADDRESS _____
 CITY _____
 STATE _____
 ZIP _____



performance
 TELEVISION

GENERAL  ELECTRIC

Engineers design electronic circuits —so can you!

**Only CREI offers you a choice
of 18 home study programs
in electronics with circuit design,
plus special arrangements
for engineering degrees**

Circuit design is perhaps the one qualification that distinguishes advanced technical personnel and engineers from the average electronics technician.

If you can design electronic circuits, you can more readily understand the circuitry of all types of electronic equipment. Thus you can more easily handle the repair and maintenance of such equipment, as well as assist in the development of new electronic systems.

The ability to design electronic circuits to solve practical engineering problems is one of the most valuable skills you can possess. Those with this ability are sought after and command positions of far greater responsibility, prestige and pay than the average technician.

If you are going to have a worthwhile career in the field of electronics, the ability to design circuits is a skill you will want to acquire.

Circuit design in all CREI programs

CREI covers circuit design in its home study programs in electronics. This is one of the factors that makes CREI training different from most other home study schools. CREI programs, of course, are college level—the same level of training you will find in any college or university offering programs in electronic engineering technology.

CREI training, however, is designed for home study. The programs give you effective, step-by-step training to help you move up in your career in electronics by using your spare time for technical self improvement.

Unique Design Lab

CREI gives you both theory and practical experience in circuit design with its Electronic Design Laboratory Program. The professional equipment included in this program allows you to construct, test out and correct the circuits you design until you have an effective circuit.

This Lab Program helps you understand advanced electronics. It also gives you practical experience in many other important areas of electronics, as in prototype construction, breadboarding, test and measurement procedures, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

Career Training at Home

Only CREI offers this unique Lab Program. It is a complete college lab and, we believe, better than you will find in most colleges. The "Lab" is one of the factors that makes CREI training interesting and effective. And the professional equipment in this program becomes yours to keep and use throughout your professional career after you complete the training.

Engineering Degree

CREI offers you special arrangements for earning engineering degrees at certain colleges and universities as part of your home study training program. An important advantage in these arrangements is that you can continue your full time job while "going to college" with CREI. This also means you can apply your CREI training in your work and get practical experience to qualify for career advancement.

Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

FREE Book

In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describing your opportunities in advanced electronics and the details of CREI home study programs.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this **FREE** Book describing your opportunities and CREI college-level programs in electronics



Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.




NEW!

TeleMatic

SONY

PICTURE TUBE BRIGHTENER

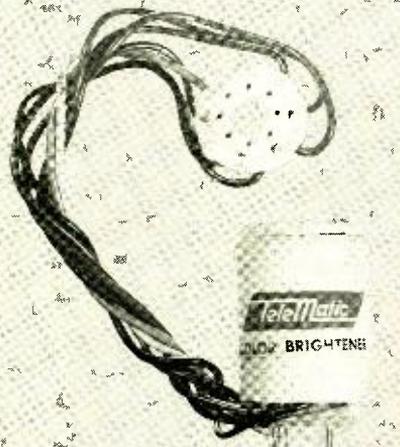

The option to replacing expensive Sony color picture tubes. (For most popular models.)

Another first from the pioneers in service test equipment.

FOR MORE INFORMATION WRITE:

TeleMatic
 2862 Fulton Street
 Brooklyn, NY 11207

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

My supplier is: _____

SOLD THROUGH DISTRIBUTORS ONLY

Circle 17 on reader service card

EQUIPMENT REPORTS
 (continued from page 24)


Finally, horizontal or vertical trigger signals for a scope can be obtained from front-panel jacks. For checking horizontal sync, burst, etc., use — sync polarity; for looking at the scan period of the sweep, use + sync polarity on the scope.

Before I forget to mention it, the panel and controls of the ATC-10 are an excellent example of human engineering. Knobs are large enough to get hold of, and they're all very plainly marked. The use of push-pull switches makes for a compact yet handy panel layout. Only four knobs are needed, and three banana jacks for the trigger signals. BNC connectors are used for RF, IF and the video outputs. These are at each end and out of the way.

It's a very easy instrument to use. When I first hooked it up, I obtained some very peculiar patterns! Then, I found that I had the RF cable in the video jack and that the TV set was on Channel 8. After reading the plainly marked panel and hooking it up right, it worked much better! Speaking of reading, you get not one but two instruction books with the ATC-10. One covers in-home servicing (including a darned good basic course in convergence!) and the other covers in-shop techniques using a scope. A great many previously difficult tests can be made with the precise patterns from this instrument—DC restoration, demodulation angle, vector-scope patterns, bandwidth, phase shift, and many more. All of these are covered in simple terms in the well-written manuals.

The instrument has a two-year warranty on it. Price is in the ball-park for an instrument that will do as many things as the ATC-10 will. The firm told me that this instrument had been field tested by several TV technicians, and their reports were used in the final design. This testing was carried on for over a year and a half period. **R-E**

Hewlett-Packard 3476A Digital Multimeter

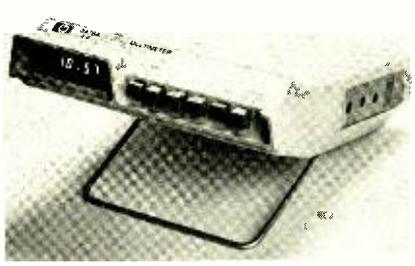

Circle 98 on reader service card

I OPENED THE BOX AND SAID TO MYSELF "Oh, good! Someone has sent me a beautiful *shoulder purse!*" A closer look showed a modest little bug at one side and the name Hewlett-Packard. Unzipping the case, I pulled out a little light gray plastic case. This turned out to be the newest thing in portable digital multimeters; Hewlett-Packard's 3476A digital multimeter. It's not at all the conventional instrument, the case is flat and very thin.

The 3½ digit bright red LED display is at one side and six pushbuttons at the other. The test leads plug into the right side of the case.

The small size is made possible by the use of new technology. This includes tantalum-nitride precision resistor networks that eliminates the need for more expensive and bulky discrete precision resistors in the dividers. The circuitry is on only one PC board although the 3476A has full autoranging capability on all of its five functions: DC volts, AC volts, DC current AC current and resistance. The decimal point and polarity indications are automatic and so is the zeroing. All you have to do is touch the test prods to the circuit and note the reading.

Ranges cover everything needed. You can read DC voltages from .0001 volt (100 microvolts!) up to 1,000 volts, and AC voltage from the same low point up to 700 volts RMS. Accuracy on DC volts is 0.5% or better; on AC volts, 0.6% or better. Current ranges, both AC and DC cover from ±0.11 A up to 1.1A. The AC volts range is rated up to 10 kHz with good accuracy.

The shoulder purse turned out to be a very cleverly designed carrying case. With this, the instrument can be hung around your neck. Opening it up will let you see the display and controls. Both hands are free to do the testing. Ample space is provided to hold the instrument, test leads and accessories. It is a very good-looking accessory.

The 3476A is the AC-powered version and the 3476B can be powered from AC or rechargeable batteries. The power supply is the only difference.

There are several useful features built-in. Using the 3476A in the *AUTO-RANGE* mode, it will set itself to whatever range is needed to display the voltage or resistance across the test prods. If you want to, you can take one reading and press the *HOLD* button. This locks the instrument on that range so that you can take several readings around the same stage without waiting. This doesn't take too much time since it updates very rapidly, but in the *HOLD* position it's even faster.

Another handy though too often neglected feature is the test leads. An instrument must be easy to connect into or across a circuit if it's to be of any use. The instrument comes with a pair of stout test prods and a neat little plastic pouch that contains a whole array of different screw-in tips, clips, spade lugs, etc., to make hooking the leads to any type of circuit construction very easy. They're easy to change and they make this instrument even more versatile.

The price of the 3476A is even more impressive. It's only \$225.00 for the 3476A AC version. This is quite a bit less than many other instruments with the same ratings. This has been made possible by the use of only two chips—one is the tantalum-nitride film resistor pack and the other a N-MOS control chip that does everything else! It contains the counters, buffer storage, display circuits, 3,500 bits of ROM and all of the solid-state analog switching for the autorange circuitry and so on and on. All in all, quite a piece of fine test gear. **R-E**

RADIO-ELECTRONICS

The Black Watch kit

At \$29.95, it's

★**practical**—easily built by anyone in an evening's straightforward assembly.

★**complete**—right down to strap and batteries.


★**guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



The Black Watch by Sinclair is unique. Controlled by a quartz crystal . . . powered by two hearing aid batteries . . . it's also styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash . . . just touch the front of the case to show hours and minutes and minutes and seconds in bright red LEDs.

The Black Watch kit is unique, too. It's rational—Sinclair have reduced the separate components to just four.

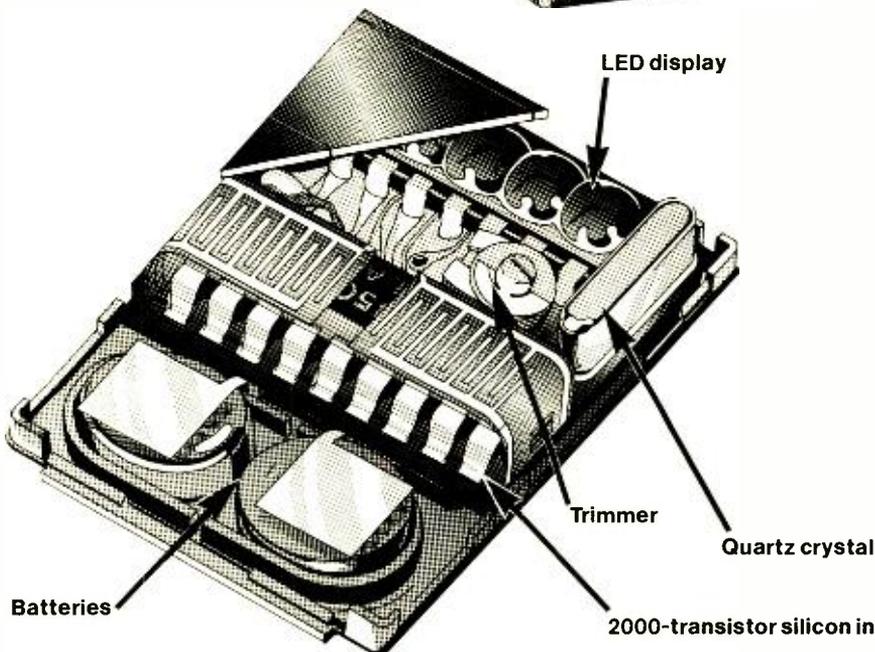It's simple—anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.



Complete kit \$29.95!

The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra—see order form)
11. full instructions for building and use.

All you provide is a fine soldering iron and a pair of cutters.

Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit within 10 days undamaged and we'll refund the cost of your kit without question.

Please send me _____ Sinclair Black Watch kit(s) at \$29.95 (Plus \$2.50 per unit, shipping and handling). Stainless steel band \$4.00. Available assembled kit \$49.95.

Enclosed is my check for _____

Name _____

Address _____

Mail to: Sinclair Radionics Inc., RE-5 375 Park Ave., New York, N.Y. 10022
N.Y. Residents add sales tax.

sinclair
SINCLAIR RADIONICS

375 Park Avenue
New York, N.Y. 10022



Until now, the toughest part of CB servicing was getting the part.

Sylvania's ECG™ semiconductor replacement line has 138 devices for the transistors, diodes, rectifiers, integrated circuits and modules you need for Citizen's Band repairs.

And they're all at your Sylvania Distributor.

That means you can spend your time in the shop instead of in search of the right parts house. It can also make the difference between turning away a potential customer, and turning out a profitable repair job.

The latest ECG Semiconductor Replacement Guide and Supplement cross-references CB devices by original manufacturer's part numbers. In practically all cases, you'll find a direct replacement, not a part that's "something like" the original.


So don't waste valuable time hunting for parts when you can have ECG's electronics supermarket right in your own shop.

We're helping you make it.

GTE SYLVANIA

See us at Newcom Booth #L7911

Circle 18 on reader service card

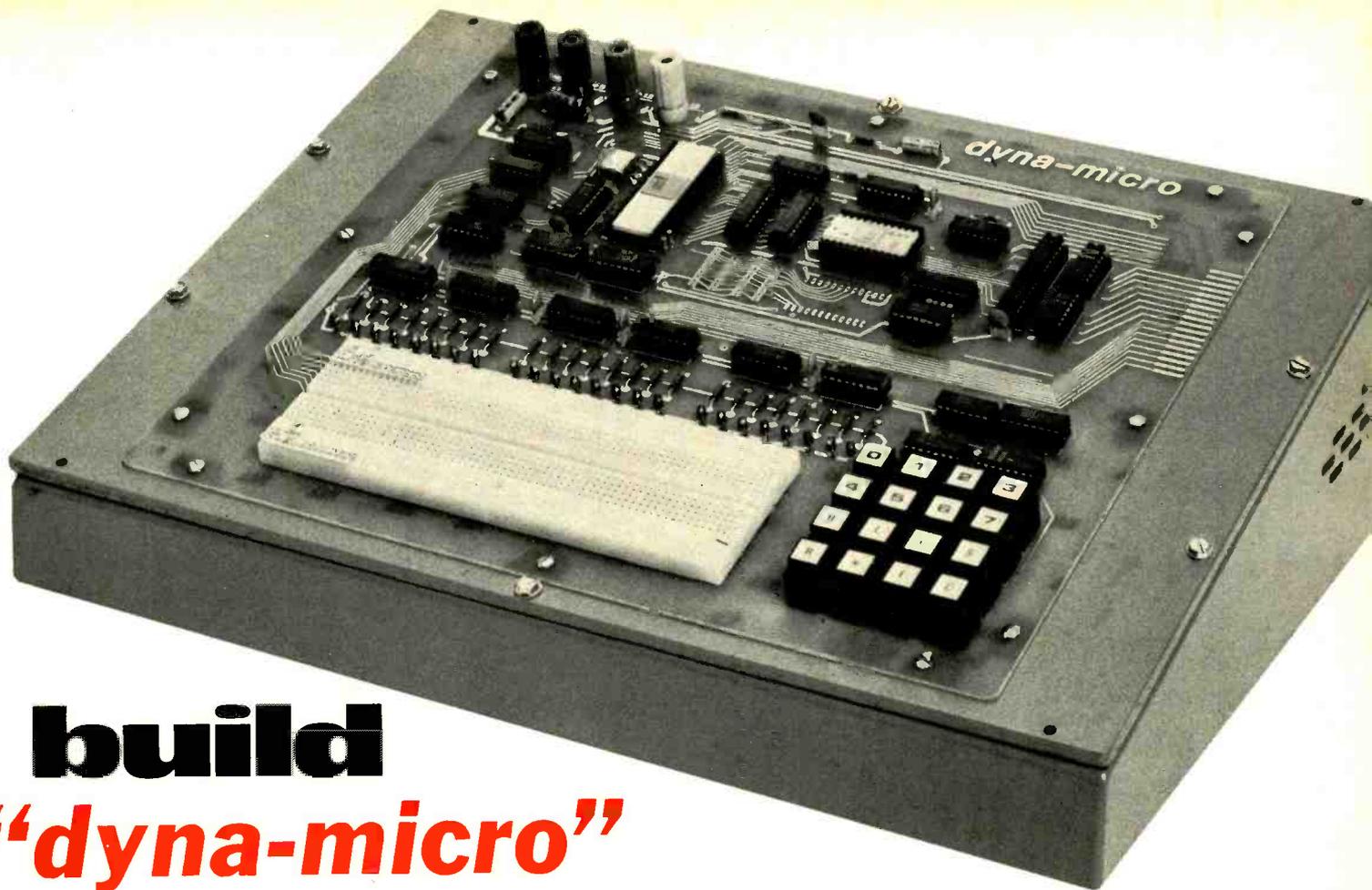

build “dyna-micro” an 8080 microcomputer

Complete with keyboard for data entry, LED readout of the address and data, breadboard socket for experimenting, 500-bytes of PROM and 500-bytes of RAM, expandable to 65K and self-contained power supply

JOHN TITUS

MANY EXPERIMENTERS, HOBBYISTS AND professionals are interested in learning about microcomputers and how they work, but the cost of a development system can be high and even inexpensive systems may require an expensive peripheral such as a teletypewriter to get them to work. None of the available systems have any easy hardware breadboarding capability and none have a series of experiments to teach you both interfacing and software fundamentals.

The Dyna-Micro is a complete microcomputer using the 8080A microprocessor chip. It isn't a stripped-down version of another system since it was designed specifically for the beginner. This system has been designed to teach you about microcomputers whether you're a high-school student or a digital design engineer—both will learn a great

The Dyna-Micro has many features that make it easy to use. These features include:

- Complete, software controlled “front-panel.”
- Fully-encoded keyboard input containing 15 keys.
- Three, eight-bit output ports with LED indicators.
- Complete solderless breadboarding area that provides easy access to all the bus signals.
- 500-bytes of Read/Write memory (R/W) and 500-bytes of Programmable Read Only Memory (PROM).
- Edge connector provided for future memory expansion.

deal about computers. With the Dyna-Micro, you won't be spending your time wire wrapping a prototype or debugging a complex “hobby” system, you'll be doing hardware and software experiments to learn more about the microcomputer revolution.

The Dyna-Micro won't run FORTRAN, BASIC, editors, assemblers or other complex software in its present form. It isn't meant for that. You can, however, expand the memory if you want to. By the time you finish the experiments, you will know how this is done.

All the Dyna-Micro functions, including the keyboard, are contained on a single 10" × 12" printed-circuit board. The power supply is external.

Using the Dyna-Micro

The Dyna-Micro is one of the easiest

- NOTES:
1.  INDICATES SK-10 SOCKET CONNECTION.
 2.  INDICATES SOLDER PAD AVAILABLE FOR USER.
3. IC9 AND IC15 ADDRESS LINES ARE IN PARALLEL WITH THOSE OF IC10.

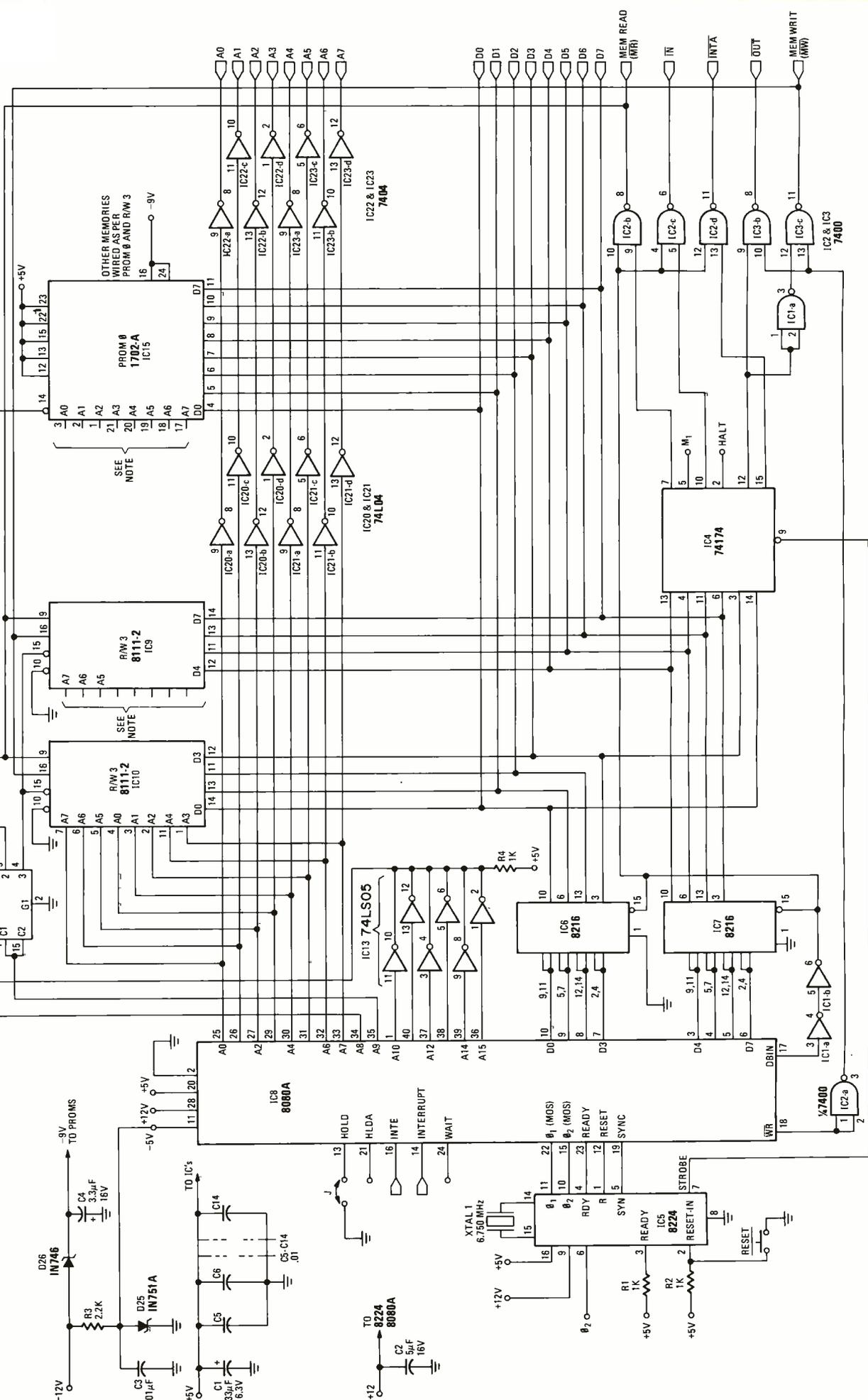


FIG. 1—CENTRAL PROCESSOR shows 8080A microprocessor and associated components. Power supply is external while voltage regulator is on-board.

to use microcomputers since it uses a software controlled "front-panel." Data is entered through a 15-key keyboard and data is displayed by LED's. The keyboard is used to enter address and memory data, to examine the contents of any memory location and to start your program from any location desired. The software to do this is pre-programmed in a 1702A PROM and is called the Keyboard Executive or KEX program.

Since the 8080A microcomputer uses 16-bits of address and 8-bits of data, the LED display registers are divided into groups of 8-bits each. The KEX program uses OUTPUT 1 for the highest 8-bits of address (HI) and OUTPUT PORT 0 for the lowest 8-bits of address (LO). OUTPUT PORT 2 is used to display data. With 16 address-bits, up to 65,536 words (commonly referred to as 65K) of memory may be addressed and added to the basic 8080

system. The Dyna-Micro uses only 1K of memory, more than enough for all the experiments and for most of your own needs when getting started. The memory is segmented, with the first 500-bytes being PROM and with the next 500-bytes being R/W. Table 1 shows how the memory is divided between PROM and R/W.

The output ports and the keyboard input are used in conjunction with the KEX program, but since they are not

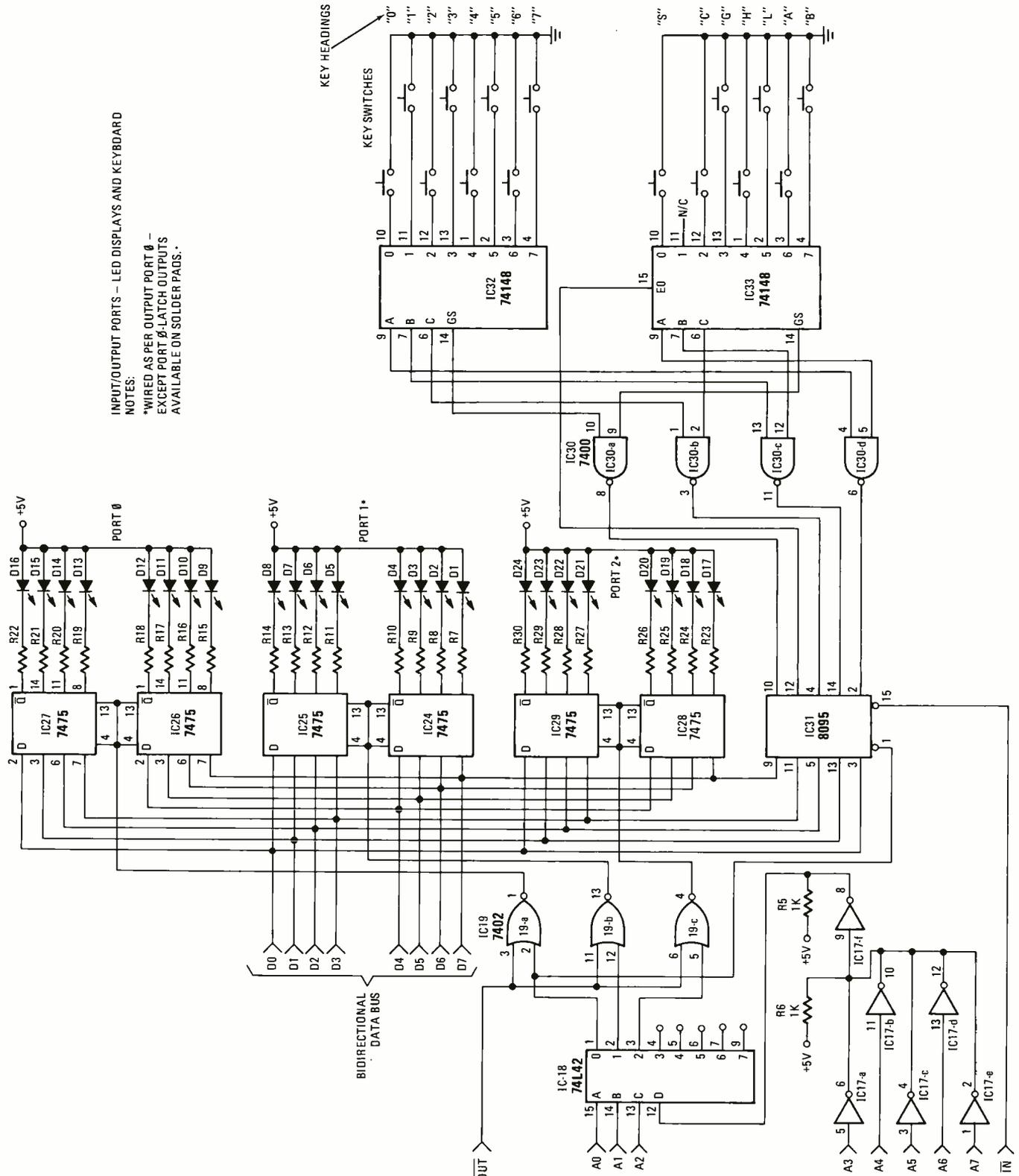



FIG. 2—INPUT/OUTPUT SECTION of the Dyna-Micro contains the keyboard and LED display.

hardwired, you can use them for data input and output with your own software. This is easily done with the software as we'll see later. Additional input and output ports are easily added by breadboarding them on the SK-10 socket or connecting them to the edge connector.

Interfacing experiments are all done on the SK-10 socket. All you will need to do the experiments are some no. 24 jumper wires and the necessary integrated circuits. No additional soldering or wire wrapping is necessary with the Dyna-Micro.

Construction

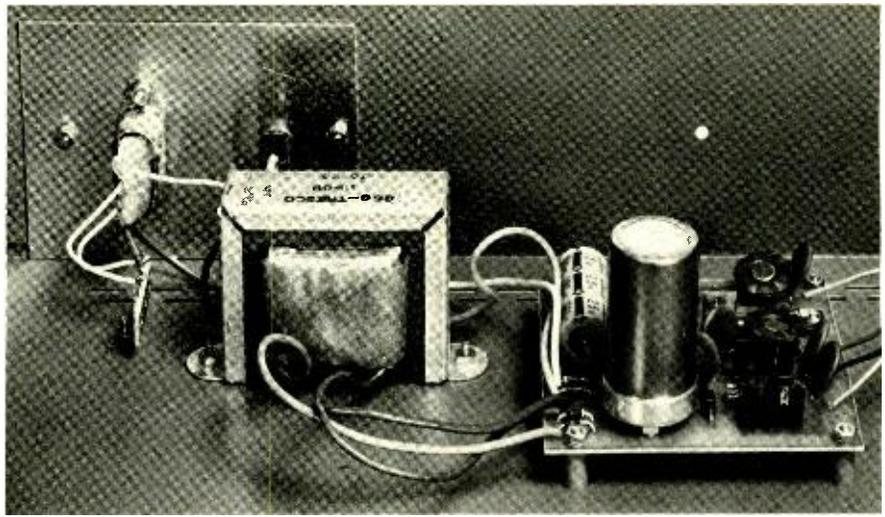The Dyna-Micro is constructed on a single printed-circuit board and it will be built and checked-out in stages to assure proper operation. These checks are fairly simple and all that is required is a voltmeter and a means of detecting for TTL level pulses. A monostable and LED will work quite well for this purpose. An oscilloscope is not needed,



THE DYNA-MICRO POWER SUPPLY provides +5 volts at 1.5 amps and ±12 volts at 150 mA. You can design and build your own or purchase assembled supplies from surplus dealers.

but might be helpful if you have one.

The schematic diagram of the Dyna-Micro is divided into two sections—the central processor unit and the I/O

(Input/Output) section. The schematic diagram of the central processor unit is shown in Fig. 1 and the I/O section is shown in Fig. 2.

All the components of the Dyna-Micro, including the keyboard, are contained on a single 10" × 12" printed-circuit board. A double-sided board is used to minimize the number of jumper wires necessary for construction.

The power supply should be constructed first. If an assembled supply is purchased, it should be tested. The power supply must be capable of providing +5 volts at 1.5 A, and ±12 volts at about 150 mA. The power supply may be purchased from one of the many suppliers or from a surplus house. It should be ready before construction proceeds since it will be used to check the sections as we go along.

Mount the capacitors, resistor and Zener diodes in the voltage regulator section of the PC board. Be sure that the binding posts are in the upper-left corner when the board is in front of you. The +12 volts is used only by the 8080A and the 8224 crystal clock IC. The -12 volts is used by the voltage regulator circuitry to obtain the -5 volts for the 8080A chip and the -9 volts for the 1702A type PROM's. After soldering in the parts, connect the power supply and check for the voltages at the power supply to be sure that there aren't any shorts. Check for +12 volts at pin 28 of the 40-pin socket and at pin-9 at IC5 (both sockets will not be soldered in at this time). You can also check for -5 volts at pin 11 of the 40-pin socket. The -9 volts will not be present unless a PROM is in one of the sockets.

The clock circuit uses an Intel 8224 integrated circuit. This is a crystal clock oscillator that provides the proper MOS clock levels for the 8080 system. It also contains circuitry for a TTL level clock (Ø2), RESET and

(Continued on page 74)

PARTS LIST

- R1, R2, R4, R5, R6—1000 ohms, ¼ W, 10%
- R3—2200 ohms, ¼ W, 10%
- R7—R30—220 ohms, ¼ W, 10%
- C1—33 µF/6.3V electrolytic
- C2—5 µF/50V electrolytic
- C3, C5-C14—0.01 µF disc ceramic
- C4—3.3 µF/16V electrolytic
- D1-D24—Small red LED (Hewlett-Packard 5082-4484, Monsanto MV5075B, or equal.)
- D25—1N751A, 5.1V Zener
- D26—1N746, 3.3V Zener
- IC1, IC22, IC23—SN7404 Hex inverter
- IC2, IC3, IC30—SN7400 Quad 2-input NAND gate
- IC4—SN74174—Quad type-D flip-flop
- IC5—8224 Clock generator (Intel)
- IC6, IC7—8216 Bus driver (Intel)
- IC8—8080A CPU (Intel) (Must be "A" version)
- IC9, IC10—8111-2 RAM memory (Intel)

- IC13, IC17—SN74LS05 Open-collector hex inverter
- IC14—SN74LS155 Dual 2-to-4 line decoder
- IC15—1702A PROM memory (Intel)
- IC18—SN74L42 BCD to decimal converter
- IC19—SN7402 Quad 2-input NOR gate
- IC20, IC21—SN74L04 Hex inverter
- IC24-IC29—SN7475 Bistable latch
- IC31—DM8095 or SN74365 Buffer
- IC32, IC33—SN74148 8-to-3 line priority encoder
- S1-S16—Keystitches with legends
- XTAL—6.750 MHz crystal, HC-18/U holder
- Solderless breadboard—SK-10 IF18
- Chassis—10" x 12" x 3" (Bud type AC-413)
- Misc.—Binding posts, IC sockets, hardware
- Optional IC's for expanded memory**
- IC11, IC12—8111-2 RAM memory
- IC16—1702A PROM memory

Keystitches are available from Solid State Systems, Inc., P.O. Box 617, Columbia, MO 65201. Order type LM or LFW-LT, with legends shown in Fig. 7.

Breadboarding socket is available from Circuit Design, Inc., Box 24, Shelton, CT 06484.

Power supplies are available from

The following kits are available from Circuit Design, Inc., Box 24, Shelton, CT 06484. Phone 203-735-8774. All kits, except MMD-1IC, MMD-1 PROM, and MMD-1 RAM come complete with construction details, experiments, and tutorial material.

#MMD-1CBK—Etched, plated-through PC board, keyboard parts and breadboarding socket. \$125 postpaid.

#MMD-1K—Complete kit of parts including 1702A PROM preprogrammed with KEX software. \$350 postpaid.

#MMD-1A—Completely assembled and tested system. \$500 postpaid

#MMD-1IC—Microprocessor IC set includes one 8080A CPU, one 8224 clock generator, two 8216 bus drivers, two 8111-2 RAM memory, one 1702A PROM preprogrammed with KEX. \$100 postpaid.

#MMD-1 PROM—Additional 256-word PROM (1702A). \$40 postpaid.

#MMD-1 RAM—Additional 256 words of RAM (8111-2). \$15 postpaid.

A user's group has already been formed for the Dyna-Micro. Interested people should contact:

Dr. Frank Settle, Jr.
Digital Directions
Box 1053
Lexington, VA 24450



understanding MATV accessories

There's a lot of individual parts in a MATV system. Here we look at the most important ones and see what it is that they do and how best to use them

WARREN ROY

THERE ARE MORE THAN 30 DIFFERENT kinds or categories of equipment that go into a MATV system. The individual items vary from antennas and rotators, to distribution amplifiers and power supplies, to connectors and cables. You need every one of these items to assemble a complete working system. In this article we will take a look at the more common elements; discuss their important characteristics and applications; and try to provide some guidelines to us when buying them.

Start at the top

We'll start with the antenna, the top of the iceberg in a MATV system. For the purposes of this article we'll look at broadband antennas as opposed to the single-channel antennas used in some systems. The single-channel approach works well where the stations to be received lie in different directions from the receiving antenna or where the signal from one station is much stronger than another. But in many systems a single broadband antenna is all that is needed.

The antenna selected must provide adequate signal levels for all of the channels to be received. Obviously, the further the antenna is located from the transmitters, the more gain, and therefore the more elaborate it must be. Most antenna manufacturers provide a full range of antennas to cover all

possible circumstances. We suggest that you get an antenna that exceeds the minimum requirements. In other words, get an antenna that's one step better than you need.

Almost all modern antennas are made of aluminum and are anodized or otherwise plated or coated to protect against corrosion. In most instances a VHF/UHF antenna will do the job. But if there are no active UHF channels in your area, you can use a simpler and less costly VHF-only antenna. When using either a VHF only or a VHF/UHF antenna there is one possible complication. Does the antenna cover the FM radio band or does it drop out those signals? If your customer wants FM reception, obviously you'll have to use an antenna that does provide that coverage.

Preamps fight snow

Preamps for weak signals are a must in many fringe areas. The preamp should be mast mounted and provide a lot of gain. At the same time it must have a low noise figure. Preamps are available that provide one wide-band amplifier or as many as three separate amplifiers in one package. The separate amplifier approach offers the benefits of greater reliability and protection from strong signal overloads. Since noise is the most important specification in a preamplifier, make sure you select one with the lowest noise figures

you can obtain.

One important point to remember. A preamp can improve a snowy picture by reducing fading and loss of color and compensating for losses in the transmission line. But it cannot make a poor picture perfect.

Since the preamp contains a transistor amplifier it also requires a source of dc power. This is frequently provided by a separate power supply, located inside the house, that feeds the needed voltage up the transmission line to the amplifier. Older units may require a separate power supply connection, but this type unit is almost never seen any more.

By selecting a preamp that also converts a 300-ohm input to a 75-ohm output you can kill two birds with one stone—amplify the signal and reduce snow in the picture and match the antenna to the coax cable of the antenna system at the same time.

Filters and traps

Filters and traps are used in the head-end of many MATV systems to eliminate undesired signals and provide interference-free signals. A wide variety of equipment is available. Some are fixed, others are variable. The fixed ones are designed to cover a specific frequency range, such as individual television channels. The variable type can be tuned to any given frequency in its range.

Traps and filters

Bandpass filters permit the desired range of frequencies to pass through unobstructed, yet severely attenuate all other signals. The ideal filter has sharp slopes that make it possible to attenuate even nearby unwanted signals.

Traps are actually the opposite of a bandpass filter. They are designed to attenuate some specific undesired frequency. A good trap must have a high Q, making it extremely selective. The more selective it is, the better it can eliminate the undesired frequency without having any great effect on the wanted signals.

System amplifiers


The more sets you have connected to an antenna system the more signal you need to feed them all and have them deliver clear snow-free pictures. Remember, no matter how good the antenna itself is, there is a finite limit to how much signal it can pick up. When the demands on the system exceed this, we must use an amplifier to make up the difference. The amplifier also compensates for losses caused by the coaxial cables used in the system.

While these amplifiers are selected to deliver enough gain to operate the system, an equally important operating parameter is the noise figure of the amplifier. Amplification must be relatively



BOOSTER MOUNTS ON MAST and connects between lead in and transmission coax. In typical installations the antenna should be mounted further above the chimney.

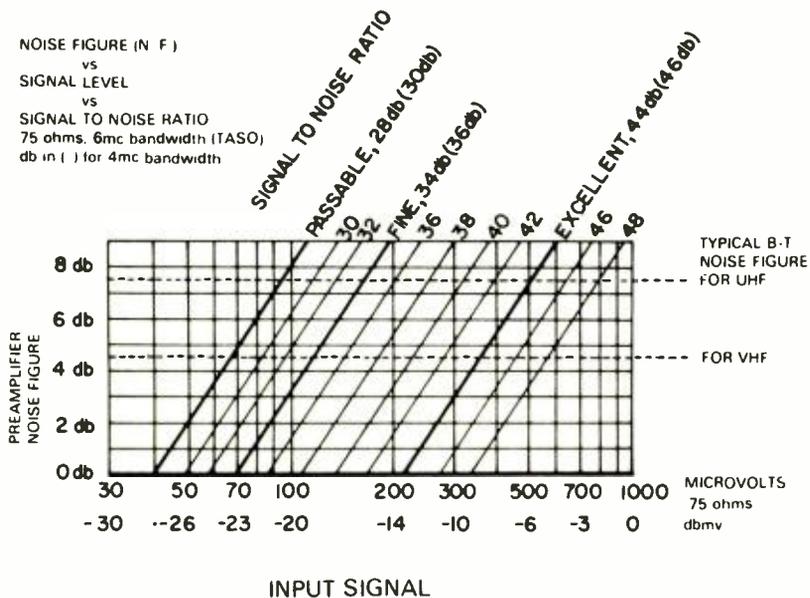NOISE FIGURE (IN F)
vs
SIGNAL LEVEL
vs
SIGNAL TO NOISE RATIO
75 ohms, 6mc bandwidth (TASO)
db in () for 4mc bandwidth




Signal-to-noise ratio, noise figure and signal level are interrelated as shown on the nomograph.

Anybody working in TV knows that snow (noise) can be seen in a TV picture when antenna signals are low, one can also see that snow increases gradually as the signal level is decreased, and that it is a matter of personal judgment when the snow is so bad as to render a picture unusable. The industry some years ago got together and showed TV pictures to a large group of average people

asking them to rate picture quality in the presence of noise. Out of this study came the TASO (Television Allocation Study Organization) report with the finding that a signal to noise ratio of 34 db means a fine picture to an average viewer, a 28 db ratio means a passable picture and so on.

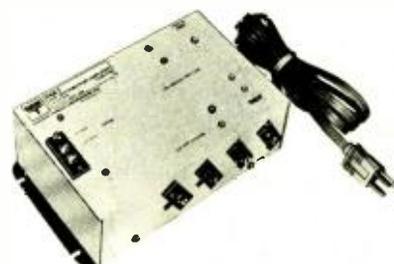
The TASO study used a bandwidth of 6 MHz, some people now favor a bandwidth of 4 MHz, (the difference is indicated on the nomograph) however, this is of minor importance to most users of the graph.



TYPICAL DISTRIBUTION AMPLIFIER provides four separate outputs. Watch the noise figure when selecting one of these.



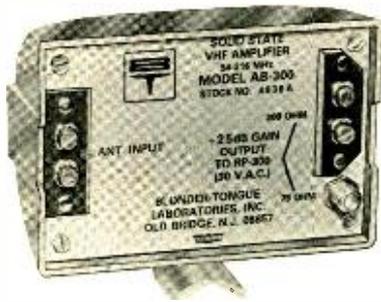REMOTE POWER SUPPLY feeds amplifier operating voltage right up the TV transmission cable. This approach is the most common one.



MAST MOUNTED VHF amplifier offers either 300-ohm or 75-ohm outputs. Normally, you would use the 75-ohm output.

noise free or the result will be worse than what you have without any gain at all.

About splitters

The first piece of equipment we encounter next is the splitter. The coaxial cable that carries the signal from the distribution amplifier toward the set is called the main trunk line. Some MATV systems have only a single trunk line, but it is much more common and practical to find that the signal is separated into individual lines that run directly to the sets in various parts of the house.

This kind of splitting usually re-



REMOTE POWER SUPPLY is typical of this type unit. It provides DC for the transistor circuitry in the preamp.

quires a two-, three- or four-way splitter. Even if the plans call for only two outlets it may be wise to use a three-way splitter so that you can easily add another outlet at some later date. In strong signals areas use back-matched splitter/mixers. Back-matching provides a good match for reverse current flow, minimizing the possibility of signals re-entering the system.

Tapoff styles

The tapoff delivers the signal from the distribution lines to the TV sets. At the same time it keeps the sets from interfering with each other. Each set in a MATV system ideally gets about the same amount of signal, but there will be more signal available at outlets that are closer to the distribution amplifier than at outlets that are further away. By using variable-isolation wall tapoffs, it is relatively easy to balance this differ-

ence in signal strength out.

In most applications four types of tapoffs are most commonly used: the wall tap, the line drop tap, the directional coupler and the pressure tap.

The wall tap is the one that you are the most likely to see and use as part of an MATV system. It is used in much the same way as an electrician uses an AC outlet. In a new building, the distribution amplifier runs inside the wall and the tap is mounted in a standard electrical box inside the wall. In existing buildings it is not always possible or



DISTRIBUTION AMPLIFIERS are usually located inside the building and provide up to four outputs.


practical to snake transmission coax through the walls and in these instances the distribution coax can be run along the baseboard or the surface of the wall. The tapoff is then enclosed in a special surface-mounting housing.

Wall taps


Three types of wall taps are available. There's a 300-ohm outlet, a 75-ohm outlet, and a dual outlet. The correct one to use depends on two factors: the number of outlets required per room and the signal strength in the area.

Generally, it is best to use a 75-ohm output with a matching transformer. In strong signal areas the 300-ohm line between the outlet and the set will pick up signals directly and can cause ghosts, and interference. Using coax cable and 75-ohm outlets prevents this since the cable is shielded from direct signal pickup.

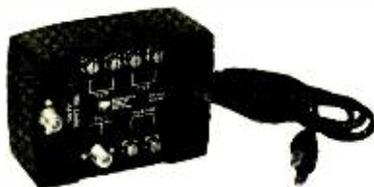In some systems you will have to provide an outlet or outlets for both television and FM. In these instances you'll want to use a dual 300/75-ohm tapoff. The 75-ohm section is used for TV and the 300-ohm section for FM.



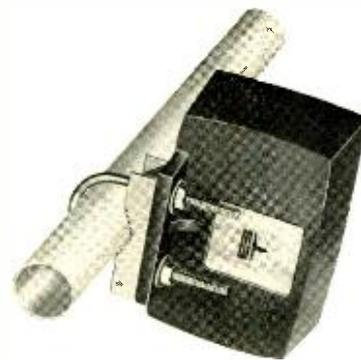THIS SPLITTER AMPLIFIER provides three television outputs and one FM output. It works from 75-ohm coax.



MAST MOUNTED PREAMPS and matching devices are usually housed right on the mast, and close to the antenna.

Line drop taps

The line drop tap is used in attics and crawl spaces. Each line-drop tap provides up to four drop lines to carry the signal to the set. The drop lines can be run directly to the set and the matching transformers or they can be run to a 0-dB wall tap. The line-drop tap is most commonly used in schools, motels, and hospitals.

The pressure tap is used outdoors where distribution lines are strung between poles, under the gables of apartments or other external systems.

The circuitry inside directional couplers incorporates design techniques that assure excellent impedance matching at all terminals, high accuracy of coupling and low insertion loss. Directional coupler tapoffs provide attenuation of 40 to 60 dB to signals leaving the line and returning because of receiver mismatch or disconnection.

This directional coupler circuitry is available in line tapoff configurations with one, two or four taps to the line.

Band separators

These devices are used in all channel (UHF/VHF) MATV systems to separate the UHF signal from the VHF signal before it is fed into the TV set. Unlike splitters that divide the signal equally, band separators contain circuitry to separate one band from another.

Terminators

The end of each 75-ohm distribution cable must be terminated with a 75-ohm resistor to prevent signals from traveling back up the line and causing ghosts on the individual TV sets.

That about wraps up our coverage of the important elements of MATV systems. We did not cover every item, but did look at the important ones, and the part that they play in a total system. **R-E**

The function generator is now occupying more service benches than ever before. This series of articles will cover the fundamentals, specifications, operation and applications of this instrument



all about function generators

CHARLES GILMORE*

INTRODUCED TO THE LABORATORY IN THE 1950's as a multi-thousand-dollar instrument, the function generator had dropped in cost to a \$250-plus product by the early 1970's. This generator has always been a popular laboratory signal source because of its numerous waveforms (sine, square, and triangle being the most popular), its low output-impedance, its wide frequency range, and versatile frequency control. The past year has seen function generators in the \$100 range introduced. These will be serious contenders for the slot on the service bench now filled by the classic sine-wave oscillator. That instrument may soon be relegated to high-precision audio testing where ultra-low distortion (below 0.05%) is required. The standard bench generator will then be a function generator covering the 0.1-Hz to 1-MHz range or more and providing at least, sine, square, and triangle waveforms.

Fundamentals

The function generator produces waveforms very differently from the classical sine/square oscillator. In classic higher-frequency instruments, an L-C circuit is used in the basic oscillator. Square waves are obtained from squaring circuits acting on the sine wave. If low-frequency waveforms are desired, the twin-T R-C oscillator or some other variation of an R-C oscillator is usually employed. The function generator's requirement of an extended frequency range is not easily met by either of these two classic circuits.

This new generator must span from millihertz (thousandths of a hertz) to megahertz, and has evolved through a completely different technique. Note we are discussing a generator, as opposed to an oscillator, which implies a basic sinusoidal source. A simple block diagram of the function generator is shown in Fig. 1. The circuit's uniqueness is apparent on first inspection. The signal source itself is not a sine wave oscillator but a triangle generator. After passing the triangle through a special circuit (called a sine shaper), a sine wave of 1/2 to 2 percent total harmonic distortion is produced.

*Manager Design Engineering, Heath Co., Benton Harbor, Mich.

The heart of the function generator is the triangle generator, the design of which is based on the special voltage-time characteristics of a capacitor charged by a constant-current source. Fig. 2-a shows the well known voltage-time curve on a capacitor when charged through a resistor from a constant-voltage source. Fig. 2-b shows the voltage-time curve of a capacitor charged from a source of constant current. If there is no stray resistance across the capacitor (usually ensured by using extremely low-leakage capacitors), the voltage across the capacitor increases linearly as time increases. Obviously, this curve may be reversed. As shown in Fig. 2-c, if the capacitor is discharged at a constant current rate, a linearly decreasing voltage will be produced.

A triangle generator may be created by first charging a capacitor with a constant-current source until a desired positive peak voltage is reached. At this point, the charging constant-current source is turned off and a discharging (oppositely polarized) constant-source is turned on. When the voltage across the capacitor is reduced to the desired negative peak by the discharging constant-current source, this source is turned off and the charging source is again turned on. The voltage across the capacitor will again begin to increase. The waveforms associated with this operation are shown in Fig. 3. A level-detecting circuit that monitors the triangle amplitude signals the reversal of the constant-current generators when the desired peak positive and negative voltages are reached. The output of this level-detecting circuit is used as the wave source.

Note that the phase relationship of the square wave is constant with respect to the triangle wave and is 90° out of phase with the triangle wave zero crossing.

In practice, one or two switched current

sources may be used. For example, if the charging constant current source has a current I , and the discharging current source has a current $-2I$, only the discharging current source need be switched. As the capacitor is charged, with the discharging current source off, the rate of charge will be determined by the current I . When both current sources are on, the net current will be

$$I - 2I = -I;$$

thus the rate of discharge will be exactly opposite and equal to the rate of charge.

At any point in time the voltage across the capacitor is given by

$$E = (T \times I) / C,$$

E (volts) is the voltage across the capacitor, T (seconds) is the time of charge, I (amperes) is the charging current, and C (farads) is the value of capacitance being charged. Rearranging this expression, we have

$$T = (E \times C) / I$$

which gives the time for either the positive or negative slope of the triangle wave.

This expression shows that two parameters control the time required to reach a desired limit voltage E : C and I . The greater the charging current, the shorter the time; or the smaller the capacitor, the shorter the time. In most function generators both variables are employed. The capacitance is varied for purposes of range changing, usually in decade steps. The current amplitude is continuously varied by the front panel dial. Frequently this current can be varied by as much as a thousand to one, giving a wide range of frequency control to the front panel dial without a change in the RANGE (capacitor) setting. The upper frequency limit is determined by the maximum current available from the current source and the minimum value of the range capacitor.

At the lower frequency limit, the lowest

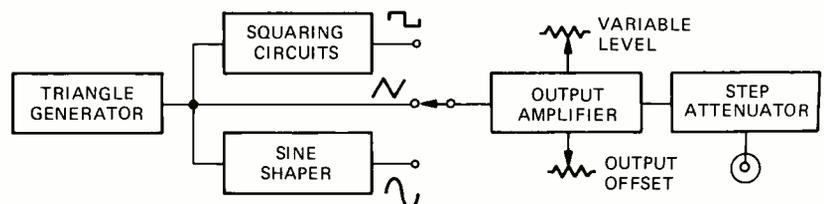


FIG. 1—FUNCTION GENERATOR, BLOCK DIAGRAM. A TRIANGLE WAVE generator is the basic signal source. Sine and square waves are produced from it by shaping.

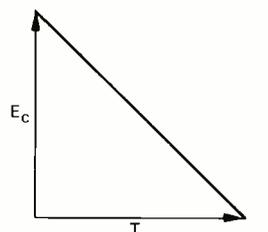
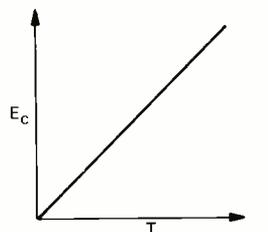
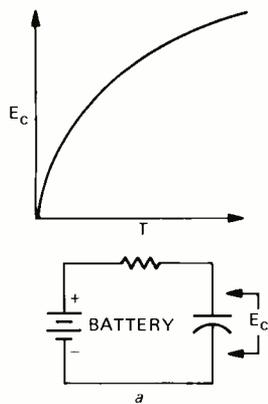


FIG. 2-a—CAPACITOR VOLTAGE WHEN charged from a constant voltage. 2-b—Same capacitor charged from constant current source. 2-c—Discharge curve at constant current rate.

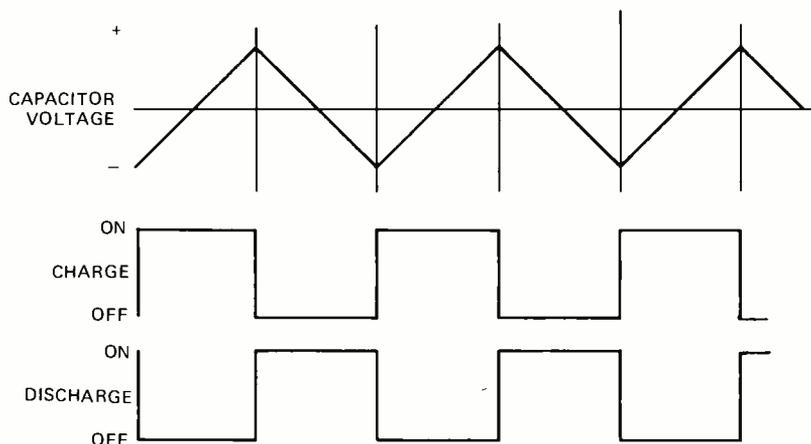


FIG. 3—VOLTAGE ACROSS CAPACITOR vs time is shown in top waveform. The bottom waveforms are those of the constant-current generators that produce the triangle wave.

feasible current that may be reliably drawn from the current sources and the largest range capacitor determine the frequency. This large capacitor must still be of extremely high quality to preserve the linearity of the triangle waveform. As an example, presume the constant current generators may be varied over the range of 1 microampere to 1 milliampere (1,000 μA), the largest capacitor is 5 μF , and the limit voltage is 10. Using the expression $T = (E \times C)/I$:

$T = (10 \text{ V} \times 5 \mu\text{F} / 1\mu\text{A} = 50 \text{ Sec.}$
But this is only the time for the positive slope. To complete a triangle wave, a negative slope must be generated as well. The time or period of the triangle becomes twice the above calculated rate, or 100 seconds. A cycle that has a period of 100 seconds has a frequency of 0.01 Hz or 10 millihertz.

To reach the highest frequency, a much smaller capacitor is chosen, but the same 10 volt limit is used. Assume a 50 picofarad (0.00005 μF) capacitor. Using the same formula gives

$$T = (10\text{V} \times 0.00005 \mu\text{F}) / 1000 \mu\text{A} = 0.0000005 \text{ sec.}$$

or 0.5 microsecond. Again, this time must be doubled to arrive at the period of the triangle wave. This gives a time of 1 microsecond or a frequency of one megahertz. Thus, in this example the generator has an operating range of 10 millihertz to 1 megahertz or 100 million to one.

As the basic waveform is not a sine-wave, the sine wave must be synthesized by some form of circuitry. The usual method of creating the sine wave is to shape the triangle wave with a circuit called a sine shaper. A simplified schematic diagram of a sine shaper and the associated waveforms is shown in Fig. 4. The technique is to increase the load on a high impedance triangle source as the level of the triangle waveform increases, thus distorting the triangle wave to approximate a sine wave with a series of straight line segments.

At levels below E1 (see Fig. 4), none of the diodes conduct and this portion of the triangle waveform is passed through the shaper undistorted. As the voltage level of the triangle wave reaches and exceeds the value E1, diode D1 conducts and the triangle source, of resistance R, is loaded by resistance R1. As the output voltage of the source continues to increase, diode D2 will conduct when the output voltage exceeds

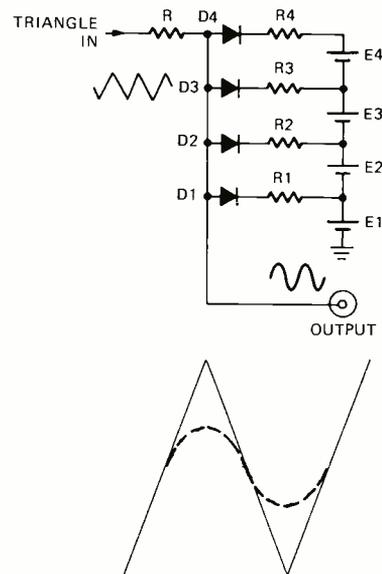


FIG. 4—THE WAVE SHAPING CIRCUIT that makes a sine wave from a triangle wave.

E2. When diode D2 conducts, the triangle source is now loaded by the parallel combination of R1 and R2. This increased loading further reduces the amplitude of the triangle source and further decreases the slope of the wave. This process continues until all diodes are conducting and the triangle source is completely loaded. As the triangle reaches its peak and reverses, the action of the sine shaper is reversed. As each diode stops conducting, the load on the triangle source is decreased.

The number of diodes determines the number of break-points shaping the sine wave, and so determines the purity of the wave. Typically, function generators are not known for their ultra-low distortion, and total harmonic distortion figures of 0.1 to 3 per cent are common. Note that figures of this order are usually quite acceptable for all but the most exacting audio work. Fig. 5 shows a typical aberration

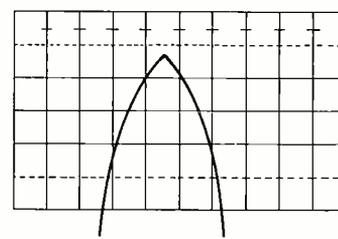


FIG. 5—THE MANUFACTURED WAVE departs somewhat from perfect sine wave form.

tion the sine shaper leaves at the crest of a sine wave. Such a peak will not substantially increase the total harmonic distortion of the sine wave, but may be quite noticeable when the waveform is viewed on an oscilloscope.

Referring to the simple block diagram, (Fig. 1) the three waveforms are selected by a waveform selection control and then applied to the output amplifier. This amplifier is somewhat more sophisticated than those in the output stages of the simple sine/square generator. As a typical amplifier must pass a square wave of one megahertz or more, its bandwidth must be nine to ten times that value.

Generally, an amplifier of fairly high gain, reduced by negative feedback, is used to obtain the low output impedance required of a function generator. Not only must the amplifier pass frequencies in the tens of megahertz, it is also required to faithfully reproduce signals whose frequencies are in the milli or microhertz region. This requirement dictates a DC-coupled amplifier.

Other frequent requirements for these amplifiers are: 10-volt peak-to-peak output into 50 ohms (2 watts); 20-volt peak-to-peak output into an open circuit; and short-circuit protection. Often a user-variable DC voltage is combined with the waveform entering the output amplifier so the user may add a DC bias or offset to the signal. The output amplifier is usually followed by some form of attenuator to decrease the output signal amplitude to a desired value. Generally, variable level controls are placed before the output amplifier and step attenuators are placed after it.

What has just been described is basic to most function generators; however, the function generator is commonly adorned with an abundance of "neat" features that vary from one manufacturer to another. Usually these features involve modifications to or additional controls on the triangle generator to produce such effects as swept frequency operation, variable symmetry waveforms, voltage (external) control of the oscillator, gated bursts, single cycle, and triggered start points.

Specifications

A common ground of understanding about specifications used in reference to function generators is needed before comparisons can be made. As in any complex instrument, the specifications that elaborate on the basic device are those that enable the user with a thorough understanding to obtain maximum usefulness from his purchase. Of course, a solid understanding of the basic specifications is also helpful when attempting to utilize even the simplest function generator.

Frequency range

As noted previously, the frequency range of function generators is controlled by two variables, the range selector and a continuously variable front panel dial. Typically the range control will be in decade steps, although some lower-cost generators have used steps that are a factor of 100. The specified frequency range for the generator will usually be from the lowest frequency that may be obtained (variable dial set at its lowest point and the range switch set in the lowest position) to the highest frequency that may be obtained (controls in the opposite settings). When selecting a generator for its low-frequency capability, the low-frequency limit should be considered, as the accuracy of the frequency setting at the low-frequency point will be rather poor. Frequency range specifications for the function generator will also note the frequency ratio given by the variable dial. Common ranges of control are 10:1, 100:1 and 1000:1. 1000:1 is popular, especially as it permits sweeping the complete audio range of 20 Hz and 20 kHz without step range changes.

Frequency stability, accuracy

Frequency stability is usually given for two different time spans. A short-term specification will be given for some time period such as 10 minutes, and long-term stability will be given for a period of 24 hours. Frequency stability specifications may be deleted on lower cost function generators.

The accuracy of the frequency setting is usually given as a percentage of full scale. For example, a generator with a frequency accuracy rated at 3% of full scale is set on the X1K range. The variable dial has a 100:1 range, (0.1 to 10), and the dial is set at the "1". The generated frequency will be 1 kHz \pm 300 Hz (3% of full scale setting of 10 kHz). The "0.1" setting on the dial yields a frequency of 100 Hz \pm 300 Hz! The accuracy is often specified only over the first decade, with the additional decades strictly for wide manual frequency control.

Frequency control (external)

In addition to the variable dial and the range switch, many function generators offer frequency control from an external voltage source that duplicates the variable dial. Such an external control is known as a voltage controlled generator (VCG). A controlling voltage (such as 1 to 10 volts) is specified for the specified range of frequencies.

The maximum rate at which the VCG may be controlled is specified by the -3dB bandwidth of the VCG circuits as well as the slew rate specifications, which tell the maximum rate of change at which the VCG can be operated. The VCG specification indicating the degree of match between the theoretical frequency of the generator and the actual frequency caused by the controlling voltage is called VCG linearity. VCG linearity is usually expressed as a percent of maximum control voltage. The input impedance of the VCG is often in the one to ten-kilohm range.

Swept frequency mode

On more sophisticated function generators, a second generator with a sawtooth waveform which will give swept-frequency operation of the main generator, may be included. When this feature is present, the sweep generator will have a frequency range of its own, although its range is not usually as wide as that of the main generator. Frequently the rate of this generator will be given in time rather than in frequency, to assist in its use as a time base.

Other generator controls

Another control found on function generators is one to trigger the start of a single cycle externally. Some generators having trigger capability also have the ability to trigger a single cycle and define the phase of the start point with a level control. This allows the user to start the wave from at +90°, for example. The ability to gate permits the generator to output an integral number of cycles of the desired waveform during the presence of a DC gating signal. Gated cycles of the generator start and stop at zero crossing, usually on the positive-going slope of the triangle waveform.

Generators having a subgenerator for

sweeping purposes may have a multiple cycle or burst mode. In this mode, the period of the subgenerator gates the main generator, again producing an integral number of cycles.

Sine wave harmonic distortion

The major specification applied to the sinewave output of a function generator is the total harmonic distortion (THD). THD will frequently be specified over a limited frequency range (such as 20 Hz to 20 kHz), as the ability to measure THD above a few hundred kHz and below a few Hz is limited. A specification indicating that all harmonics are below 30 dB, for example, may be given for frequencies above 100 kHz.

Triangle linearity

Triangle linearity indicates the degree to which the positive or negative slopes of the triangle waveform conform to a perfect straight line, and is given in one of two ways. The manufacturer may specify a triangle linearity of 95%, indicating the triangle waveform will not deviate from a perfect waveform by more than 5% of the full scale value. Other manufacturers specify maximum nonlinearity. A maximum nonlinearity of 5% would be the same specification as a 95% linearity specification. High degrees of linearity (1% to 0.5%) are obtainable at a price, but 5% nonlinearity is sufficient for most applications.

Square wave rise and fall

The rise and fall time of a square wave is defined as the time required for the wave edge to travel between its 10% and 90% voltage points. The rise and fall times lie in the 100-nanosecond range for 1-MHz generators and may be as fast as 10 nanoseconds on 10 to 30-MHz function generators. Rise and fall times will be consistent across the generator frequency range.

Time symmetry


Time symmetry specifies the time match between the positive and negative-going slopes of the triangle wave. Any deviation from a perfect match will cause some increase in total harmonic distortion of the sinewave and will effectively add DC offset to the sine, square, and triangle waves. Time symmetry is not specified in the same manner by all manufacturers. A specification of 2% time symmetry indicates the symmetry of the waveforms is such that the duty cycle of the positive pulse of the square wave will not be less than 48% nor more than 52%. This is alternately specified by noting that two of the narrowest pulses (positive or negative) would make up at least 96% of the period of the cycle.

Vertical precision or flatness

Another important feature of the function generator is the inherent flatness of the output amplitude. Flatness indicates the maximum variation in output amplitude with variations in frequency, including range changes. With the exception of the uppermost range, most function generators give flatness specifications in the tenths of a dB. Frequently the uppermost frequency range of the sinewave output

(continued on page 88)

Linear Phase Response

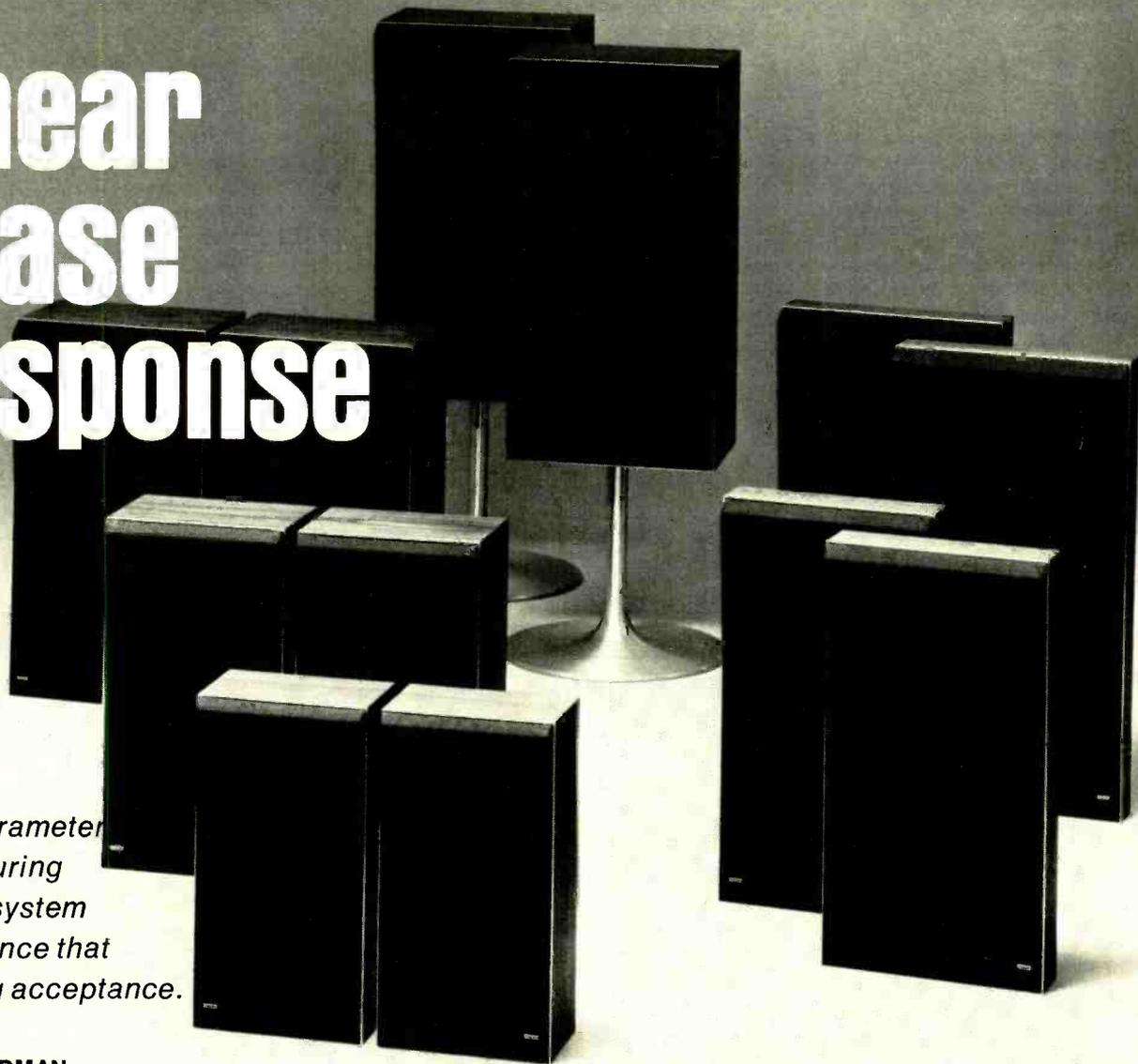

*A new parameter
for measuring
speaker system
performance that
is gaining acceptance.*

by **LEN FELDMAN**
CONTRIBUTING HI-FI EDITOR

ANYONE WHO HAS EVER CONNECTED A pair of speaker systems to a stereo amplifier knows they need proper phasing. If the stereo pair is connected out of phase, we know that one speaker cone (or set of cones in a multi-driver system) will "push" air while the other "pulls". The result is a combination of loss of apparent bass and of vague positioning of instruments in the stereo sound field. The reason for the loss of bass is fairly obvious. Since low, bass tones are fairly non-directional (bass sound seems to fill a listening room rather than originate from a pin-point location), when recordings are made the left channel microphone or microphones pick up as much of the bass energy as the right channel mikes. In reproduction, both speakers are expected to deliver approximately the same bass energy. If the bass tones coming from one speaker are out of phase with those coming from the other, the wave fronts tend to cancel each other

and there is a noticeable absence of bass in the reproduced music.

But what about the other effect? Why—when speakers are out of phase—do we find it difficult to pin-point instrument locations in the reproduced music? Despite early studies (which suggested that the human ear is not sensitive to "phase errors" in complex waveforms) an increasing amount of recent evidence suggests that, indeed, phase linearity (or, more simply, correct relative time relationships of all tones and their harmonics) is a necessary ingredient of true high-fidelity sound reproduction. It is simple enough to insure that left and right speaker systems are operating "in phase" (there's a 50-50 chance of correct connection to begin with, and if you suspect an out-of-phase connection you just reverse the wires to one of the speaker systems). But there's much more to "phase linearity" than that. Remember, most modern high-fidelity

speaker systems consist of two or more drivers. We have woofers, tweeters, and in some cases mid-range drivers as well as super-tweeters, each attempting to reproduce a given portion of the audio spectrum. How about the phase relationship between these various drivers *within* a given speaker system?

Some manufacturers have come to the conclusion that the various speaker elements in a multi-driver system must be arranged so that all audio frequencies arrive at the listener's ear in correct time (or phase) relationship. The very nature of woofers and tweeters makes this difficult if all drivers are mounted on a common baffle, in a single plane, as illustrated in Fig. 1. Because the woofer cone is deeper than that of the tweeter, sounds produced by the woofer arrive at the listener's ear a fraction of a second later than those produced by the tweeter. Some manufacturers (such as Dahlquist in their DQ-10 design) have sought to compensate for this by

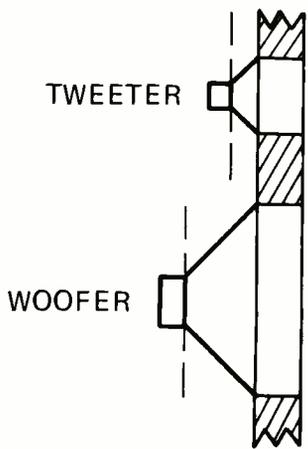


FIG. 1—DIFFERENT CONE DEPTHS of woofer and tweeter cause the two wave fronts to reach the ear at different times.

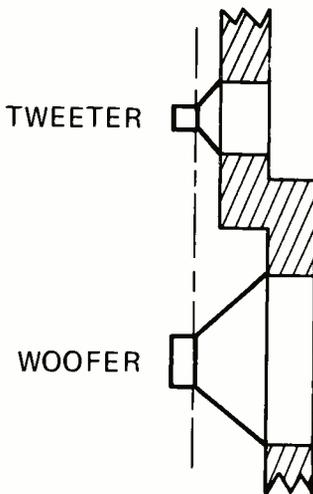


FIG. 2—OFFSETTING THE SPEAKERS is a way some manufacturers try to improve phase linearity between woofer and tweeter.

positioning the various drivers on different surfaces or planes, as illustrated in the diagram of Fig. 2.

What of the crossover network?

Recently, I had an opportunity to visit the well known Danish electronic firm of Bang & Olufsen. There, certain additional facts regarding phase distortion in speaker systems were brought to light most dramatically. Much of what follows is based upon original research by the famous acoustical engineer Erik R. Madsen who was, for many years, chief engineer at B & O and serves as a consultant to the firm these days. As he pointed out in a paper at the 1973 Audio Engineering Society convention in Rotterdam, the chief cause of phase distortion in a loudspeaker system arises not from the physical disparity between the positioning of the different drivers, but from the action of passive crossover networks that are used in the majority of today's commercially available loudspeaker systems.

A simple crossover system is shown in Fig. 3. It provides a 6-dB/octave slope in response at the selected crossover frequency (1 kHz in our example),

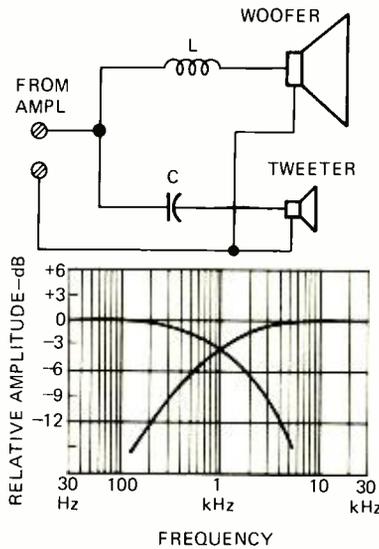


FIG. 3—CIRCUIT AND RESPONSES of a 6dB/octave standard crossover network.

feeding low frequencies to the woofer and high frequencies to the tweeter. Note that at the crossover point itself, relative amplitude is down 3 dB for each driver, so that the *sum* of energy delivered to the two drivers is the same as at frequencies outside the crossover region. With a simple crossover such as this, overall phase response of the system will be quite good—even in the region of crossover. If a square wave at 1 kHz were fed into such a system (and assuming that the drivers were otherwise perfect in response), the output waveform from the woofer would look like the waveform drawn in Fig. 4-a while the output from the tweeter would have the appearance of Fig. 4-b. Add these two components together and you have the waveform of Fig. 4-c—a perfect square wave with no phase distortion.

The problem with using such a moderate-sloped crossover network is that it requires woofers and tweeters to operate effectively (with low distortion and flat frequency response) well outside their intended regions of best performance. Since the contribution of

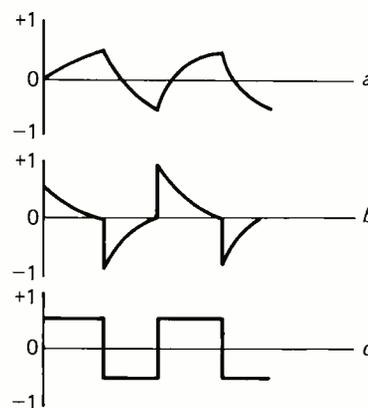


FIG. 4—WITH SQUARE-WAVE INPUT applied to a 6 dB/octave crossover, the outputs of the woofer (a) added to those of the tweeter (b) produce an accurate replica (c) of the original square-wave input signal.

each driver can be heard at least until it is 12 dB below reference program level, the overlap region in a 6 dB/octave crossover arrangement extends for a full four octaves, as illustrated in Fig. 5-a.

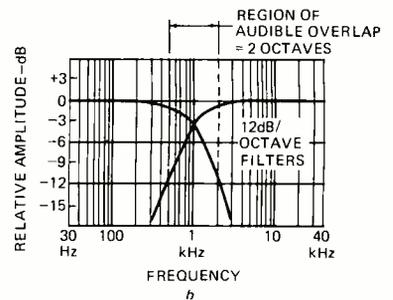
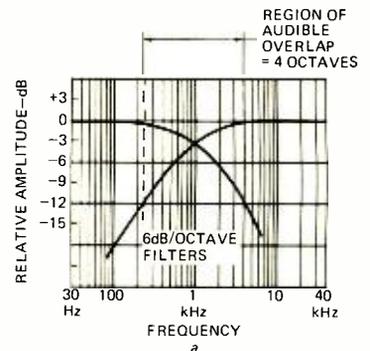


FIG. 5—COMPARING CROSSOVERS. The range over which drivers must work efficiently is twice as great (4 octaves) for 6 dB/octave networks as is the range for 12 dB/octave units (only 2 octaves).

If a steeper rate of roll-off—such as 12 dB per octave—were employed, overlap would need to extend only for a total of two octaves, as shown in Fig. 5-b and optimum performance of each driver would not have to be extended so far outside its "normal" frequency region. For this reason, most better systems do utilize 12 dB/octave crossover networks (some even employ 18 dB/octave slopes). But here is where the problem arises. When such a network is used, the phase angle of the waveform fed to the woofer goes in a negative direction as the crossover frequency is approached, while that for the tweeter goes positive, as shown in Fig. 6. Thus, although single-amplitude plots (without regard to phase) of the output voltages of a 12 dB/octave network, as shown earlier in Fig. 5-b, suggest that total energy output of the system in the

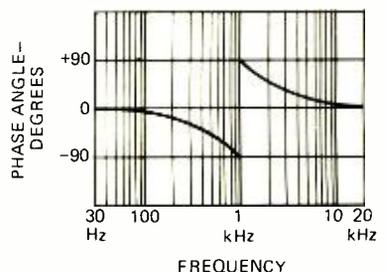


FIG. 6—PHASE RESPONSE of the high-frequency section of a 12 dB/octave unit is 180 degrees out of phase with that of the low-frequency section of the same network.

region of the crossover frequency will be "flat", yet if outputs are plotted with regard to amplitude and phase, the actual output energy in the crossover region appears as in Fig. 7 because of the cancelling effect of the out-of-phase outputs from the two legs of the crossover network.

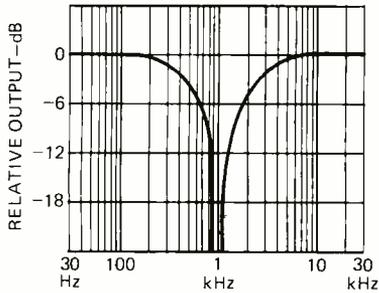


FIG. 7—PHASE ANGLES INTRODUCED by the 12 dB/octave network create a sharp cancelling null at the crossover frequency when the phases of the sections are reversed.

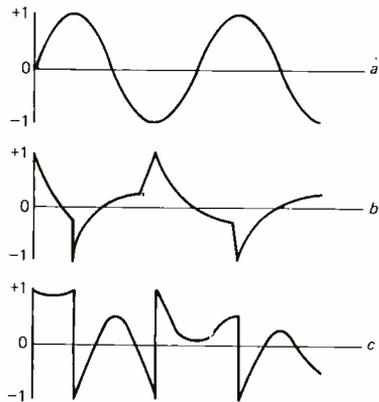


FIG. 8—MATHEMATICAL ADDITION OF woofer input waveform (a) and tweeter input waveform (b) from a 12 dB/octave crossover results in the distorted square wave of (c).

When a square wave is fed to such a system, the output from the woofer will theoretically appear as shown in Fig. 8-a, that of the tweeter as shown in Fig. 8-b, and the composite waveform will appear as shown in Fig. 8-c—not at all like the square wave input signal with which we started.

Some manufacturers have been aware of this out-of-phase problem for some time. One attempt at correction has been to reverse the phase of the tweeter with respect to the woofer (or,

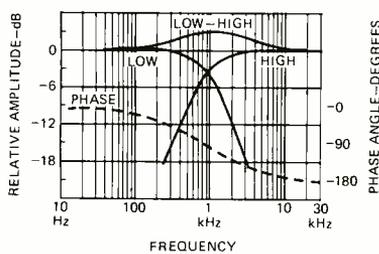


FIG. 9—REVERSING RELATIONSHIP of phases in the tweeter and woofer of a 12 dB/octave network results in an increase of output at the crossover frequency rather than the desired and correct level output.

in the case of 3-way systems, the mid-range with respect to the woofer). As can be seen from the composite diagram of Fig. 9, this produces a peak in total energy output in the frequency region of the crossover instead of a null. Because of the phase response characteristics over the entire frequency band (shown as a dotted line), application of a square wave to a system arranged

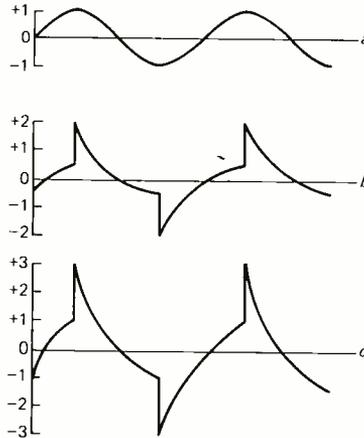


FIG. 10—SQUARE WAVE APPLIED TO the out-of-phase connected crossover network and producing conventional waveforms in the woofer (a) and tweeter (b) sections, give the distorted result of (c) when added.

in this manner would result in the woofer output shown in Fig. 10-a, the tweeter output in Fig. 10-b and the composite output shown in Fig. 10-c—still a long way from the desired square wave shape.

Bank & Olufsen's solution

The answer to the problem of phase linearity in speaker design was discovered by Erik Baekgaard, who read a paper on his work at an AES convention in London. It is represented in a new line of speakers which were demonstrated to me while I was in Denmark. Design work on these speakers was led by Esben Kokholm, of B & O and I have since had an opportunity to evaluate them in my own laboratory.

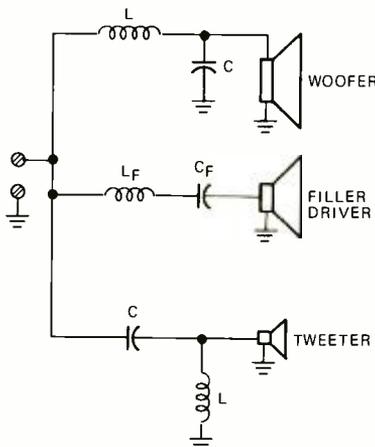


FIG. 11—A NOVEL SOLUTION of the problem is the B & O approach—a third unit with a series-connected circuit tuned to the crossover frequency to fill the null there.

In addition to the usual woofer, mid-range and tweeter, this family of speaker systems employs what B & O calls a "filler driver". The general form of crossover network used is that of Fig. 11. Note that the center circuit is neither a low-pass or a high-pass filter, but rather a series resonant arrangement that provides a peaked response to the filler driver (or phase-link speaker, as they call it) at the crossover frequency and a roll-off of 6 dB per octave above and below that frequency. Added to the responses of a conventional 12 dB/octave network, we have the composite crossover network response shown in Fig. 12. The theoretical

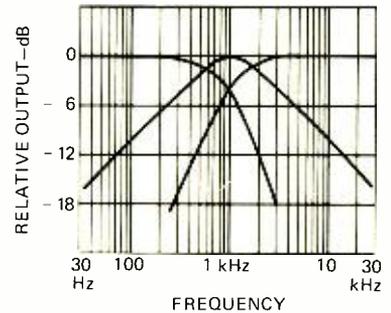


FIG. 12—THE COMPOSITE RESPONSE of the woofer, filler driver and tweeter in the new Bang & Olufsen crossover network.

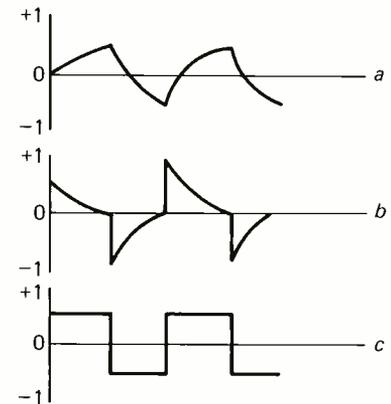


FIG. 13—APPLYING SQUARE WAVE TO the B & O network results in the response at (a) for the woofer, (b) for the filler, and (c) for the tweeter, and adding them gives the result in (d), or the original square wave.

outputs from the three drivers are now as shown in the three parts of Fig. 13. When these are added together graphically, we do come up with an exact replica of the original square-wave input waveform.

Having achieved a solution to the crossover problem, the people at B & O were not about to ignore the driver positioning problem mentioned earlier. While they maintain that flat-baffle positioning produces less phase distortion than that introduced by conventional crossover networks, they nevertheless were looking for as near perfect a phase response characteristic as possible. Accordingly, they developed a new front-baffle shape (actually precision molded of high density foam resin which, they

claim, is superior in damping and acoustic qualities to wood) which slants the woofer upward so that wavefronts produced by it arrive at the listener's ear at the same time as those produced by the other drivers. The principle is shown diagrammatically in Fig. 14. In the floor-standing versions of the new B & O speakers, a special pedestal is recommended, with which the listener can actually tilt the entire speaker box forward or back from the vertical, depending upon where he or she is seated in relation to the speakers, and even to compensate for different "ear heights".

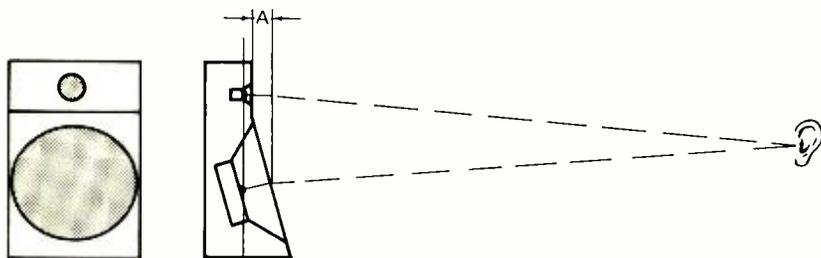


FIG. 14—ANGLED FRONT BAFFLE compensates for the phase delay caused by difference in depths of woofer and tweeter.

Does it make a difference?

Obviously, we don't listen to square waves, and it can be argued that when listening to complex musical waveforms some of these fine points tend to be obscured. I can only tell you that in comparison tests made with three other speaker system types (all popular, well-accepted brands) I was able to sense better localization of stereo images, better transient response with certain program material, and a more natural sounding overall musical quality.

How much of the improvement is a result of the linear phase response of these new systems and how much is simply the result of otherwise excellent driver selection, enclosure design and generally good speaker system design I am not prepared to say. The fact is that "hearing memory" in humans is extremely poor. We tend to listen to our favorite speakers and to convince ourselves that we are hearing reality. This happened in my listening tests, too. I

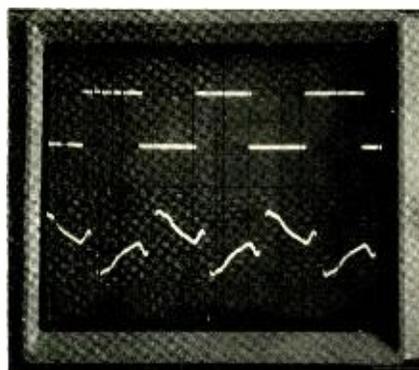


FIG. 15—SQUARE-WAVE SIGNAL IS reproduced by actual conventional speaker system much as shown in the theoretical mathematical addition of Fig. 8-c.

was perfectly content with what later proved to be the somewhat vague stereo localization of music using a well-known speaker pair—until I pushed the A-B switching arrangement and listened to the linear-phase units for comparison. Suddenly, the previous pair's sound wasn't quite as gratifying.

The square-wave drawings shown in earlier diagrams are purely theoretical, and derived mathematically. I was curious to see if results could be duplicated in practice, allowing for the fact that my lab is anything but an anechoic chamber and that microphone place-

ment would have a great bearing on the results. I therefore hooked up a square-wave generator to my system, placed a calibrated microphone at what I thought was an optimum spot in front of my regular lab speaker, and photographed what was picked up by the microphone. The results are shown in the scope photo of Fig. 15. Without moving the microphone, I carefully replaced my regular speaker with the sample M-70 model from Bang & Olufsen and repeated the experiment. The

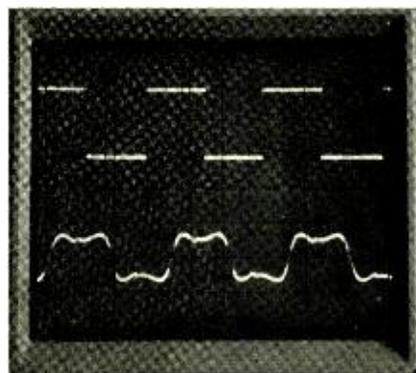


FIG. 16—TEST SETUP OF FIG. 15 with the new B & O speaker system. Output more closely resembles the square-wave input.

scope photo of Fig. 16 shows the results I then obtained. Maybe Bang & Olufsen has something here!

R-E

DON'T MISS IT!

This month's in-depth hi-fi test reports include the Marantz model 2325 stereo receiver and the Lafayette model LR-2200 stereo receiver.

RCA closes Harrison tube plant, oldest in world

"A sharp decline in demand for receiving tubes in the face of the continuing shift to solid-state devices in consumer, industrial and defense electronic systems" was given by Paul B. Garver, head of RCA's Distributor and Special Products Division, for the July closing of RCA's last tube manufacturing facility, at Harrison, NJ, July 30. Industry sales have declined almost 80 percent since 1966, he said, with replacements in older electronic equipment responsible for most of the present volume.

The Harrison plant was opened by Thomas Edison in 1882, to manufacture electric light bulbs. Ten years later, it was acquired by General Electric, who continued to manufacture lamps until 1918 when the first radio tubes were made. Throughout the 1920's, G-E continued to supply tubes to the various manufacturers of radios. In 1930 the plant was purchased by an RCA subsidiary, RCA Radiotron Co., and the tubes were called Radiotrons.

At its peak, the Harrison plant had a work force of more than 7,000 (as compared to a recent figure of 1,100 employees) and made 87 million tubes in one 12-month period. Besides mass-producing tubes for consumer use, the plant made special ones for industrial, military and aerospace equipment, some in rather small quantities.

RCA, now the sole source for about 110 types of receiving tubes, plans to meet as far as possible all future requirements for these types, and will continue to sell replacement receiving tubes.




550,000 calls-per-hour on new telephone central system

The world's highest-capacity long distance telephone switching system went into action in Chicago last January 17. The new facility, No. 4 Electronic Switching System (ESS), has a peak capacity of 550,000 calls-per-hour. This works out to a little over 9,000 calls-per-minute, or 150 calls-per-second.



BELL LABORATORIES TECHNICIAN Mike Haverly inserts circuit packs in the "brain" of the No. 4 ESS System, the 1A central processor. The ribbon-like strips snaking down the front of the control unit are actually cables connected to test equipment.

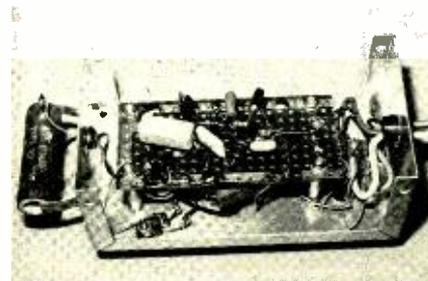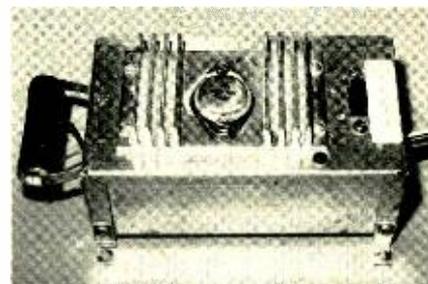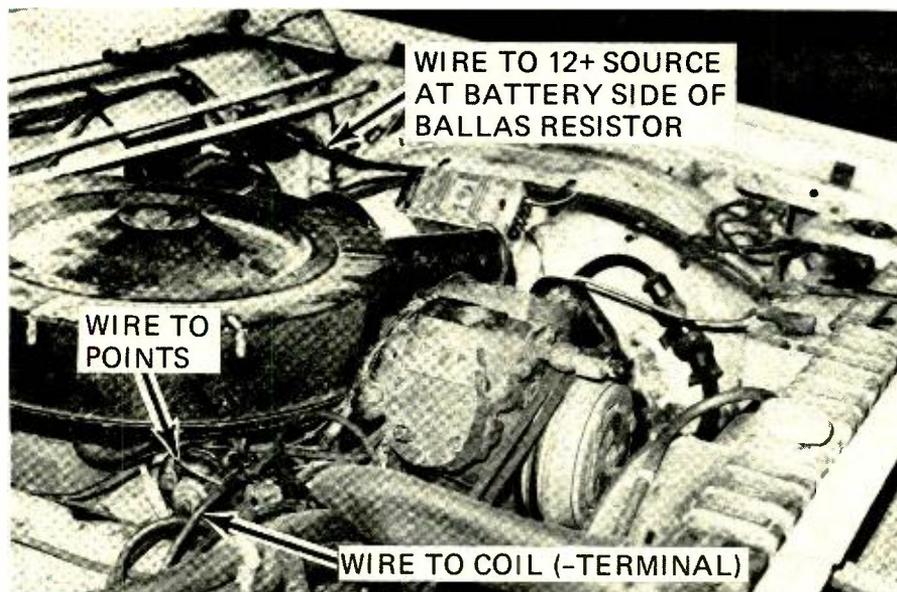Build This Solid State Ignition System For Your Car



This electronic ignition can be used with any standard ignition coil to provide a constant-amplitude spark

DICK PACE

TRANSISTOR IGNITION SYSTEMS WERE INTRODUCED by Ford as optional equipment in 1966. A year later, GM offered similar systems. Chrysler developed a system so economical and reliable that it was supplied as standard equipment on all models, beginning in 1973. Other manufacturers are following this lead, and electronic ignitions are becoming standard on most cars. The prime advantage of these systems is that they provide high peak voltage to drive the spark plugs.

The circuit to be described has several advantages over previous types. Most transistor ignition systems require special coils; this project is designed for use with any standard ignition coil.

It provides a constant-amplitude spark at engine speeds in excess of 6,000 RPM. At low speeds, spark duration is relatively long. This minimizes pollution and increases engine efficiency. At high speeds, spark duration is shorter, allowing time to charge the coil fully. (At high speeds, long spark duration is not necessary for thorough fuel burning.)

Since this ignition system is triggered by the ignition points on the car, point wear is virtually eliminated. A convenient switch enables you to operate the car from its regular ignition system in the unlikely event of circuit failure. Finally, the unit is

very stable. The spark duration is computed automatically so that once turned on by the car's points, shutdown occurs at the right instant. Previous transistor ignition projects were turned both on *and* off by the points.

Essentially, this is an electronics project rather than an automotive one. Except for hooking up the transistor ignition system, no changes are required to the automobile. All parts are readily available, for under \$30.

How it works

When the points are closed in a conventional auto ignition system, current flows through the coil, charging it. When the points open, current is interrupted. The collapse of the magnetic field creates high voltage across the points. The voltage rise (about 200 volts peak) is stepped up by the coil, which is actually a transformer, about 100 times (to about 20,000 volts) to fire the spark plugs. The capacitor serves to slow the rate of voltage rise across the points and to form a resonant tank circuit, together with the coil. The capacitor and the coil resonate in damped oscillations until the stored energy is spent. Should the points close before the energy were completely dissipated, the points would arc.

When you add this transistor circuit to the ignition system, it is power trans-

istor Q4 (see Fig. 1) that interrupts current to the coil, rather than the points.

Transistors Q1 and Q2 form a monostable or one-shot multivibrator with some modifications. A monostable multivibrator is a pulse generator that operates only when triggered. It has two states, stable and unstable.

In its stable state, Q1 is "off," with 12 volts at its collector, and Q2 is "on," with the collector at ground. (All the transistors act as saturation switches. Either they are completely on or completely off.) Q3, a PNP, is "on," because current flows through the collector-emitter junction of Q2, R8 and the base-emitter junction of Q3. Q4 is "on" because current flows through its base-emitter junction from collector emitter current of Q3 through R9.

When a pulse is applied to the base of Q1, it turns on and its output immediately goes to ground. Therefore, the plus end of C1 also goes to ground. Since the voltage or charge across the capacitor cannot instantly go to ground, the minus side of the capacitor goes to -12 volts.

This negative voltage turns off Q2 by reverse-biasing it. Q2 will not stay off for a fixed period of time. The collector of Q2 is now at battery voltage and the base of PNP Q3 is at battery voltage (equal to its emitter voltage) and is turned off. Base current to Q4 stops and Q4 turns off, interrupting the current in the coil.

While the sparkplug is firing, R3 is (relatively) slowly charging the minus end of C1 in a positive direction. Current is flowing through R6, keeping Q1 on. Eventually, the minus end of C1 reaches +0.6 volts and turns Q2 on. This removes the voltage from the base of Q1 and it turns off. At this point in time, Q2, Q3 and Q4 are all on.

The pulse that determines when Q1 turns on comes from the ignition points in the car. When the points are closed, the junction of R1 and R4 is at ground. When the points open, +12 volts appears at R4 through R1. Capacitor C6 differentiates the voltage, forming a positive spike that turns on Q1. R1 (40 ohms) allows about ¼-amp of current to flow through the points when they are closed. This is not

enough current to cause contact wear but is enough to prevent the points from oxidizing, which could cause the system to fail. The charge time across the points capacitor (condenser?) through R1 is fast enough to be insignificant.

The spark is not turned off by the points. Spark duration is determined independently by the circuit time constants. The on time of the multivibrator is determined by C1 and R3 by the formula $T_{on} = 0.8RC$. This "on" time is relatively independent of supply voltages because when the capacitor charge increases, the available recharge current also increases.

The above formula assumes that C1 is fully charged. The recharge of C1 is through R2. In most multivibrator applications, a constant-duration output is

desired. An attempt to operate the monostable multivibrator faster than a certain rate will cause the output pulse to become narrower, because capacitor C1 has not had time to fully recharge through its charge resistor R2. This problem is utilized to advantage in this circuit. R2 would normally be a smaller value (about 470 ohms) to allow for quick recharge. In this circuit it is made larger to increase C1 charge time. Thus, as engine speed is increased to exceed 900 RPM, the spark duration begins to narrow or shorten in time. The duration is about 1.7 milliseconds at 700 RPM, about 1.4 milliseconds at 2,000 RPM and only 0.75 milliseconds at 6,000 RPM.

The result is a long spark at low speeds, which will result in thorough combustion,

PARTS LIST

All resistors 10% carbon unless noted

- R1—40 ohms, wirewound, 10 watts
- R2—2700 ohms, ¼ watt
- R3—1000 ohms, ½ watt
- R4—1000 ohms, ¼ watt
- R5, R6—3300 ohms, ¼ watt
- R7—75 ohms, wirewound, 5 watts
- R8—22 ohms, ½ watt
- R9—10 ohms wirewound, with brackets, 25 watts (Mallory type 2.5HJ or equivalent)
- R10—150 ohms, ½ watt
- R11—220 ohms, ½ watt
- R12—470 ohms, ½ watt
- C1—2.7 μ F, \pm 10% high-quality tantalum (Mallory TAC 275K025P04 or equal.)
- C2—0.1 μ F ceramic, 50 V or higher, -20 +80%
- C3—470 μ F, 25-50 V, -20+80% electrolytic

- C4, C5—.01 μ F, \pm 20% ceramic, 50 V or higher
- C6—.068 μ F, 50 or 100 V, Mylar
- C7—0.22 μ F 50 or 100 V, Mylar
- C8—0.22 μ F, 400 or 600 V, Mylar
- Q1, Q2—transistor, NPN, 2N2222A, HEP S-0015 or equivalent (previous number HEP 736)
- Q3—transistor, driver, PNP, MJE371, HEP S-5006 or equivalent (previous number HEP 700)
- Q4—transistor, NPN high-voltage, high-power, MJ423, HEP S-5020 (previous number HEP 707)
- D1, D2—Zener diodes, 150 volts, ½ or 1 watt, 10%. HEP Z0442 or equivalent
- S1—switch, 3PDT slide (non-shorting) 3 A, 125 V. (Stackpole 55-34, Workman SW-14 or equivalent)

Miscellaneous:

- Case—aluminum "Minibox" 5¼ x 3 x 2⅞-inch
- Circuit board. Make your own PC board or use perforated board with push-in clips.
- Heat sink for TO-3 case (Q4). Burstein-Applebee catalog No. 12A2229-9 or any type with equivalent radiating surface.
- Silicone grease for Q3 and Q4
- Coil dope for Q4
- TO-3 transistor socket for Q4. (Radio Shack 276-029 or equivalent)
- One-inch standoffs for printed-circuit boards.
- Barrier strip or strain relief for wires going to car
- Printed-circuit board L-brackets for mounting case to car.

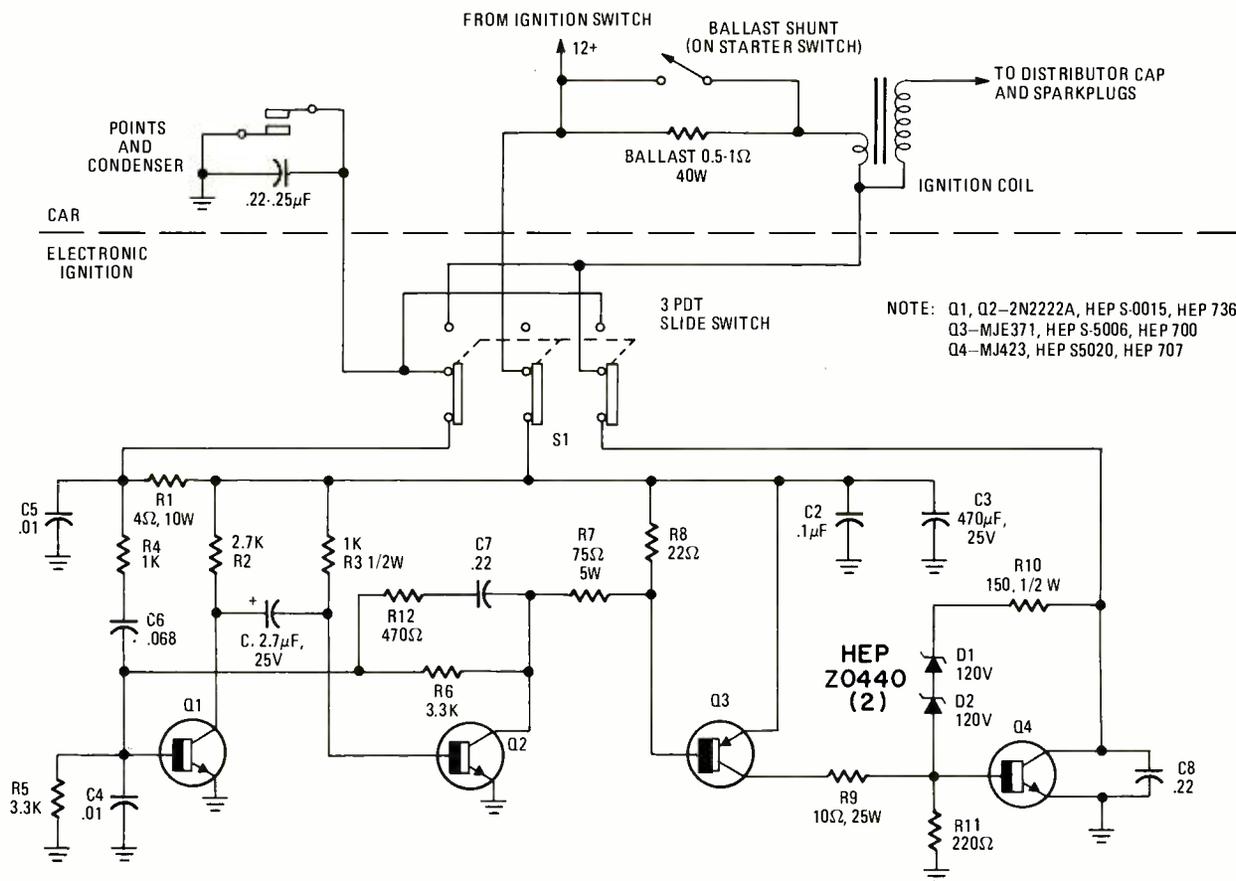


FIG. 1—THE FOUR-TRANSISTOR ELECTRONIC IGNITION SYSTEM.

and a short spark at high speeds. This short spark allows a longer charge time for the ignition coil at high speeds than with points. Points have about a 50% duty-cycle or a nearly square-wave output. An attempt to have the points open for a shorter time would cause point arcing as the coil would not have discharged completely. A transistor can be turned on while the coil is still charged and sparking, without any problem.

While standard ignition systems rapidly lose voltage above 2,000 RPM, this system insures virtually constant output voltage to over 6,000 RPM. (See Fig. 2).

Standard ignition systems sometimes have a problem known as point bounce at high speeds. Points operating at high speeds tend to rickochet slightly, causing an erratic charge and discharge of the coil. This erratic point operation could cause the electronic ignition to operate erratically, but circuitry is included in the system to prevent this problem. Basically, the circuit prevents the unit from retriggering for a fixed period after the spark has ended. This effectively places an upper speed limit on the engine at about 10,000 RPM. The network is formed by C7, R12

and R5. When the monostable multivibrator is in its unstable state, there is a charge on C7, with +12 volts on its right side through R4. When Q2 turns on, -12 volts appears at the base of Q1. This discharges through R5. Until it does, the unit will not trigger. When the points close, a negative voltage appears at the base of Q1 from differentiation capacitor C6. This adds to the negative charge from C7 and further prevents premature operation.

R10, D1 and D2 form a protective network to prevent excessive voltage from destroying Q4. D1 and D2 are Zener diodes in series, giving a Zener voltage of 300. R10 provides isolation and circuit limiting. If the voltage across the diodes exceed 300, the Zeners conduct and the current flows into the base of Q4, turning it on slightly to limit the voltage at its collector. The gain of Q4 is utilized to lower requirements of the Zeners.

C8 allows a controlled buildup of voltage when Q4 turns off and effectively limits the voltage to about 220 to 270. The unit will work without it but the waveform is uncontrolled and spiky. The initial spike, if not limited by the Zener circuit, will go above the breakdown voltage of the transistor and eventually cause it to fail.

C2, C4, C5 are RF and transient filters. C3 is a power supply ripple filter. The switch is used to bypass the unit, in case of component failure, for tuneup purposes or for comparison. When switched to the bypass position, the +12 volt supply is removed; the points and coil are switched out of the circuit and connected to each other.

Construction

A conventional aluminum box can be used to house the unit. The circuit layout is not critical. Most of the components can be mounted on a circuit board. While a pre-patterned board was used for the original, a perforated board with clips will be fine, or you can make a printed circuit board. D1, D2, D11 and C8 can be wired point-to-point near Q4 using a terminal strip. Mount Q4 to a heat sink, using a TO-3 socket. Heatsink Q3 by fastening it with a screw to the case. Don't forget the mica insulators and silicone grease. Wipe off excess silicone grease and coat transistor Q4 with coil dope, especially where it meets the case, to prevent water splashing from shorting across the transistor. Mount R9 outside the case with brackets; it gets quite hot. Wires running to the engine should be passed through a strain relief, or a barrier strip can be used. Use No. 18 gauge stranded wire.

In choosing transistors, there is nothing really critical about Q1 or Q2. Q3 is not critical, but should have low leakage. If you substitute, be sure to use silicon transistors that will saturate easily at the required currents. If Q2 does not saturate, for example, the unit will oscillate. The collector-base voltage ratings should be 35 volts or better. Use discretion in substituting for Q4. Here we need a high-voltage power transistor, at least 300 collector-emitter volts, high current capability, operating from 3.5 amps to 5 amps, with some gain and a low saturation voltage ($V_{ce\ Sat.}$). The Motorola HEP 707 and HEP-S5020 have these characteristics. Many high-voltage transistors do not.

When selecting parts remember that the unit will be operated in temperature extremes from -10°C to 100°C or greater.

Bench Testing

This unit, or other electronic ignition systems, can be bench tested without a car or even a distributor. You will need:

1. Ignition coil of the type for use with the ignition system under test.
2. a single spark plug
3. squarewave generator
4. audio amplifier
5. ballast resistor or a 1/2- to 1-ohm 25 to 50-watt resistor
6. oscilloscope with attenuator probe
7. 12-volt power supply
8. 500 μ F 25V capacitor
9. clip leads

The coil and ballast resistor are connected to the unit and power supply as they would be in the car.

The squarewave generator and amplifier replace the points. For ignition systems that use points, connect the generator to the amplifier and connect the amplifier through a 500 μ F, 25V or larger capacitor to the points input (minus to the amplifier, plus to the system). Adjust the amplifier volume control for a 12-volt peak-to-peak squarewave. The capacitor is to keep the 12 volts DC out of the amplifier. Ignition systems without points, such as those with a pickup coil, should be connected direct to the squarewave generator, since these units are very sensitive.

Connect the scope probe to the primary terminal of the ignition coil. Connect a sparkplug to the secondary. Don't forget to ground the spark plug. RPM is determined by the formula for a 4-cycle engine:

$$\text{Hz} = \frac{\text{RPM}}{60} \times \frac{\text{No. of cylinders}}{2}$$

$$\text{Hz} = \frac{\text{RPM}}{15} \text{ for a V8}$$

Operate the squarewave generator from 40 to 400 Hz.

Installation

The unit can be attached to the car with "L" brackets. Mount the unit in a dry location in the engine compartment, well away from the exhaust manifold and other hot spots. Connect the wires to the car as shown in the schematic (Fig. 1).

At the ignition coil, remove the wire that goes to the points. Connect the collector of Q4 to this coil terminal. Fasten the point wire to its input (junction of R1 and R4). Connect the +12V terminal to the car's ignition circuit. It can be attached to the battery side of the ballast resistor in cars that have it, or to an ignition terminal at the fuse block (not an accessory or battery terminal). Some cars (typically GM) use a piece of resistance wire in the lead to the coil (+) terminal for ballast resistance. Others (frequently foreign cars) have the ballast resistor inside the coil. Only in these cars can the +12 volts be taken from the coil's plus terminal.

Tune-up

Follow manufacturers specifications on tune-ups. Timing can be set with the switch at "normal". If you use the dwell meter technique to set the points, be sure to set

(continued on page 85)


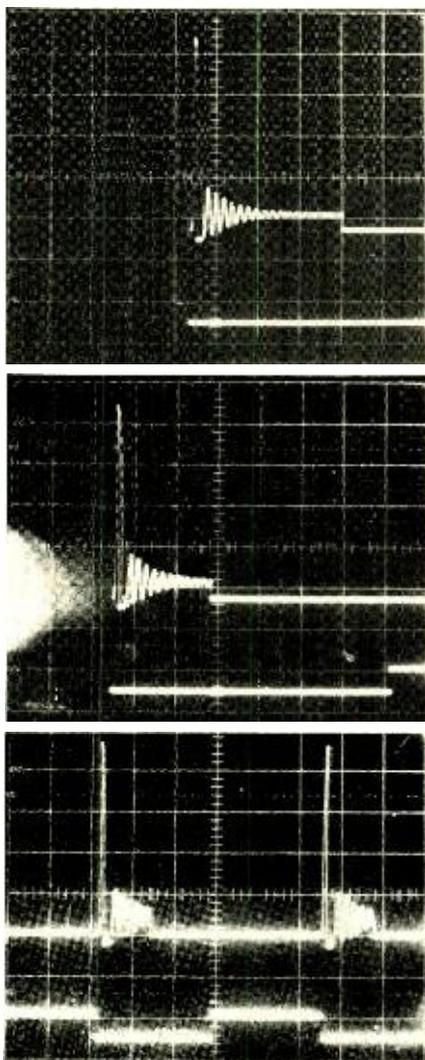


FIG. 2—WAVEFORMS, COIL PRIMARY Top—Spark duration at 600 RPM (idling speed) 1.7 ms; middle, at 2,000 RPM (highway speed) 1.4 ms; bottom—6,000 RPM (faster than most cars can go) 0.75 ms. Horizontal divisions are 0.5 milliseconds; vertical ones, 50 volts.

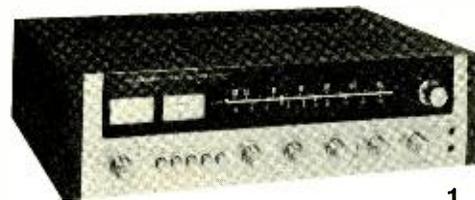

Tests Lafayette LR-2200


LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

WHEN THE NAME LAFAYETTE IS MENTIONED in electronic circles, most people think of a national network of retail stores that sell all types of consumer electronic equipment from ham gear to hi-fi. In fact, the people who run Lafayette also consider themselves to be a major manufacturer of electronic equipment and their line of high-fidelity amplifiers, tuners, receivers and other hi-fi components is as broad as that of some of the better known makers of sound equipment. Furthermore, since they act as supplier and retailer, they claim to offer more performance per dollar in their hi-fi equipment than do some of their competitors who have to first make a profit in selling to dealers before the dealer applies his or her profit.

We chose to investigate their moderately priced LR-2200 receiver because it seemed to offer good features and power output for its under \$300.00 price. The receiver, shown in Fig. 1, follows a traditional front panel design approach with a well illuminated dial area that lights up when power is applied. Frequency calibration is minimal, with marks supplied only every 2 MHz apart of the FM scale. To the left of the tuning scales are a pair of tuning meters—one for signal strength indications on AM or FM, the other for center-of-channel tuning when listening to FM. The usual stereo indicator lights up between the frequency scales and the meters when a stereo FM signal is received. A tuning knob is located to the right of the dial scales and is coupled to a fairly effective flywheel for ease of tuning.

Along the bottom of the control panel are six major rotary knobs. The first of these, at the left, is a program selector. The master volume and balance controls are located near center of the panel. The bass and treble controls are of the dual concentric, clutch type so that individual tonal control of each channel is possible. At the lower right is a speaker mode knob that includes a power-off position as well as a position for synthesizing 4-channel effects from stereo program sources if two pairs of speakers are connected in the same room. Alternatively, two pairs of speakers may be arranged as "main" and "remote" for stereo reproduction in two different locations. Small pushbuttons located between the two left-most knobs take care of such functions as loudness,

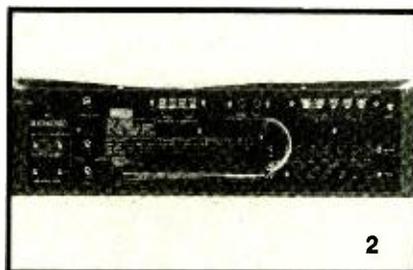hi-cut filtering, stereo/mono switching and activation of either or both of the available tape-monitor circuits. The rear panel, shown in Fig. 2, has switched and



unswitched convenience AC receptacles at the left, the required input and tape out jacks at the upper right and a loop-stick ferrite AM antenna that can be retracted from chassis surface for better AM reception. Adjacent to the phono input jacks is a slide switch that alters phono input sensitivity from 2.5 millivolts to 6.0 millivolts to better accommodate cartridges of widely varying outputs. The main pair of speakers are connected via a barrier-type terminal strip while connection of a second pair of speakers (or rear speakers if the pseudo-quadriphonic effect is desired) is made by means of phono-type pin plugs. A screw-terminal strip accepts outdoor AM or FM antennas and two of the terminals are connected by a removable jumper that couples to a line cord-capacitor arrangement that serves as

an indoor FM antenna. A chassis ground terminal, left and right speaker fuses and a power line fuse complete the rear panel layout. Connection of possible associated equipment is illustrated in the diagram of Fig. 3.

Figure 4 is a photo of the internal layout of the LR-2200 receiver. Four major circuit board modules are used: a large one for the FM and AM tuner section, one for the preamplifier and voltage amplifier plus tone control section, a third module for the power amplifiers, and a fourth module that houses the power supply.

Circuit highlights

The FM front-end of the LR-2200 employs a four-section variable capacitor for tuning, a dual-gate FET as an RF amplifier, a junction FET as a mixer and a bipolar device as a local oscillator. Two ceramic filters are used to tune IF frequencies with IF amplification accomplished by one bipolar transistor and pair of IC stages. Most of the multiple decoding circuitry is contained in a single IC. The AM circuitry consists largely of a multipurpose IC, with IF frequencies tuned by another ceramic filter. Phono preamplifiers and equalizers are IC's (one per channel), while voltage amplification and tone control stages of the popular feedback type employ discrete bipolar devices. The input stage of each power amplifier section is a differential ampli-

MANUFACTURER'S PUBLISHED SPECIFICATIONS

FM TUNER SECTION:

IHF Sensitivity: 1.75 μ V. Alternate Channel Selectivity: 60 dB. Capture Ratio: 1.5 dB. Signal-to-Noise Ratio (Mono): 70dB. Distortion (Mono): 0.5%. IF Rejection: 80 dB. Image Rejection: 80 dB. Spurious Rejection: 90 dB. Stereo FM Separation: 40 dB @ 1 kHz. FM Mute Defeat Level: 8-10 μ V.

AM TUNER SECTION:

IHF Sensitivity: 20 μ V (external antenna). Alternate Channel Selectivity: 45 dB. Signal-to-Noise Ratio: 45 dB. Image Rejection: 60 dB.

AMPLIFIER SECTION:

Power Output: 27 watts-per-channel, 8 ohms, from 20 Hz to 20 kHz. Rated THD: 0.5%. Input Sensitivity: Phono: 2.5 mV/6.0 mV. High Level Inputs: 250 mV. Phono Overload: 130 mV/60 mV. Hum and Noise: Phono: 60/65 dB (depending upon sensitivity); High Level: 80dB. Tone Control Range: Bass: \pm 12 dB @ 50 Hz; Treble: \pm 10 dB @ 10 kHz. High Filter: -10 dB @ 10 kHz.

GENERAL SPECIFICATIONS:

Power Consumption: 83 watts, 105-120V, 50/60 Hz. Dimensions: 17½" wide by 5" high by 12¾" deep. Net Weight: 17 pounds. Retail Price: \$299.95.

TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Lafayette

Model: LR-2200

FM PERFORMANCE MEASUREMENTS

SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE

	R-E Measurement	R-E Evaluation
IHF sensitivity, mono: (μ V) (dBf)	2.4 (13.0)	Fair
Sensitivity, stereo (μ V) (dBf)	10.0 (25.4)	Good
50 dB quieting signal, mono (μ V) (dBf)	3.0 (14.9)	Very good
50 dB quieting signal, stereo (μ V) (dBf)	35.0 (36.3)	Good
Maximum S/N ratio, mono (dB)	70	Excellent
Maximum S/N ratio, stereo (dB)	65	Very good
Capture ratio (dB)	1.6	Very good
AM suppression (dB)	50	Fair
Image rejection (dB)	82	Very good
IF rejection (dB)	80	Very good
Spurious rejection (dB)	88	Good
Alternate channel selectivity (dB)	61	Good

FIDELITY AND DISTORTION MEASUREMENTS

Frequency response, 50 Hz to 15 kHz (\pm dB)	0.75	Excellent
Harmonic distortion, 1 kHz, mono (%)	0.35	Very good
Harmonic distortion, 1 kHz, stereo (%)	0.5	Very good
Harmonic distortion, 100 Hz, mono (%)	0.35	Very good
Harmonic distortion, 100 Hz, stereo (%)	0.5	Very good
Harmonic distortion, 6 kHz, mono (%)	0.6	Good
Harmonic distortion, 6 kHz, stereo (%)	0.8	Excellent
Distortion at 50 dB quieting, mono (%)	1.2	Good
Distortion at 50 dB quieting, stereo (%)	0.5	Very good

STEREO PERFORMANCE MEASUREMENTS

Stereo threshold (μ V)	10	Fair
Separation, 1 kHz (dB)	40	Excellent
Separation, 100 Hz (dB)	42	Excellent
Separation, 10 kHz (dB)	28	Good

MISCELLANEOUS MEASUREMENTS

Muting threshold (μ V)	10	Fair
Dial calibration accuracy (\pm kHz @ MHz)	200 @ 88	Good


EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION

Control layout	Fair
Ease of tuning	Good
Accuracy of meters or other tuning aids	Very good
Usefulness of other controls	Good
Construction and internal layout	Very good
Ease of servicing	Excellent
Evaluation of extra features, if any	Good

OVERALL FM PERFORMANCE RATING

Good to very good

fier followed by a power module, or thick film hybrid IC that operates from a ± 34 volt DC supply. The familiar passive network developed by Dynaco some years ago is used to develop "out of phase" outputs for the "rear" speakers when the receiver is used in the 4-channel mode. Critical tuner, preamp and voltage amplifying stages are powered from a well regulated source of +13 VDC that uses a series transistor and a Zener diode in the now familiar regulating arrangement.

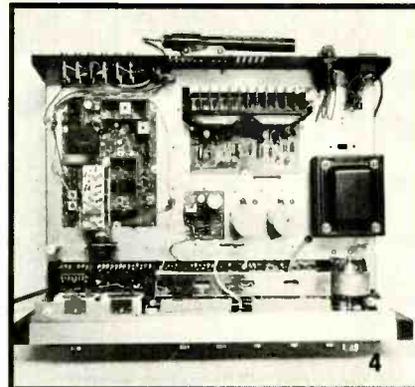


Laboratory FM measurements

Results of our FM performance measurements are listed in Table I and may be compared with those published by the manufacturer. It should be noted that Lafayette seems to be a bit behind the times, or is reluctant to publish all the specifications now required by the new FM Tuner Measurement Standards. Or, perhaps, they have not had sufficient time to amend or add to their manuals, which may have been published before the new standards went into effect last May. While usable sensitivity fell short of the 1.75 μ V claimed (which would have equaled 10.25 dBf if Lafayette has used the new power reference as we do), the 2.4 μ V figure (13.0 dBf) obtained is considered quite acceptable for a unit in this price class. While distortion figures were not as low as those measured for more expensive sets, Lafayette is to be complemented in keeping stereo distortion as low as it measured (0.8%) at 6 kHz, where most other low-cost sets produce greater distortion. Separation was excellent, measuring exactly the 40 dB claimed at mid-frequencies and even a bit better at the low end. Smooth transition from mono to stereo at about 10 μ V (25.4 dBf) is just about the optimum point of switching for a set with this quieting characteristic. AM suppression was acceptable, though not outstanding, but this is offset in part by the low measured capture ratio. Used with a good outdoor antenna (Lafayette should not have encouraged use of an indoor linecord antenna by supplying that jumper), the FM performance of this receiver in most signal areas will be hard to distinguish from that of sets costing much more.




Laboratory amplifier measurements

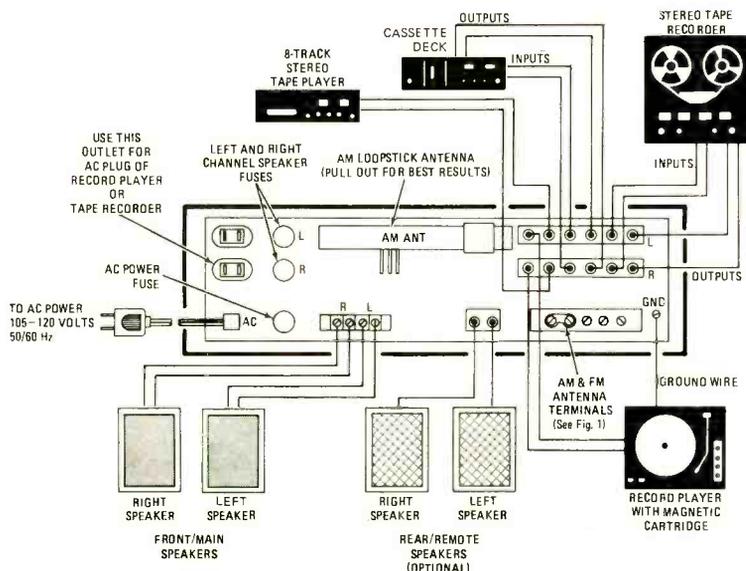If we had to rate the amplifier section and the tuner section of this receiver separately we would probably favor the amplifier section. One tends to view those power modules skeptically, but they certainly delivered what was ex-



The better the training the better you'll

Send for
FREE
illustrated
career
guide

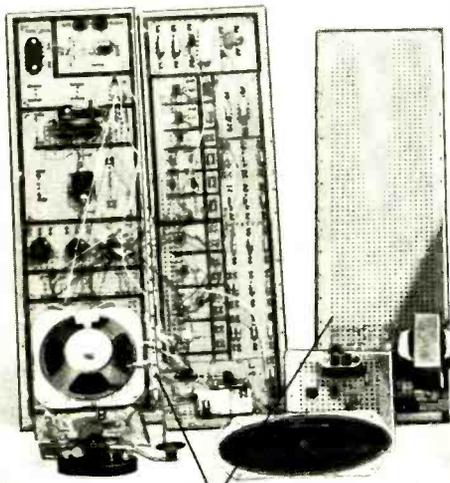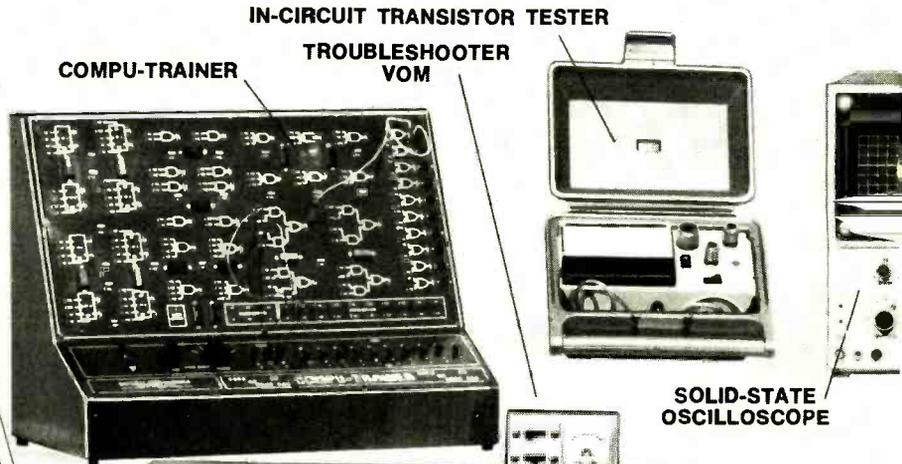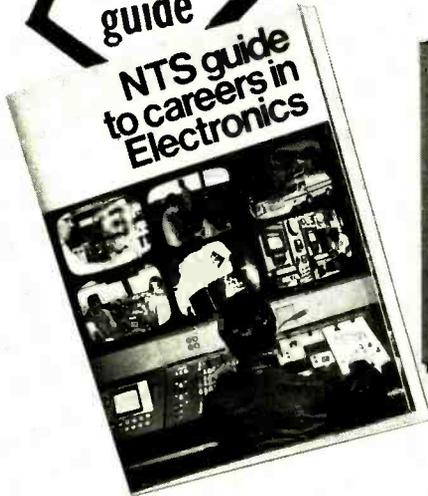

ELECTRO-LAB



(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.


This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

and the equipment be equipped.

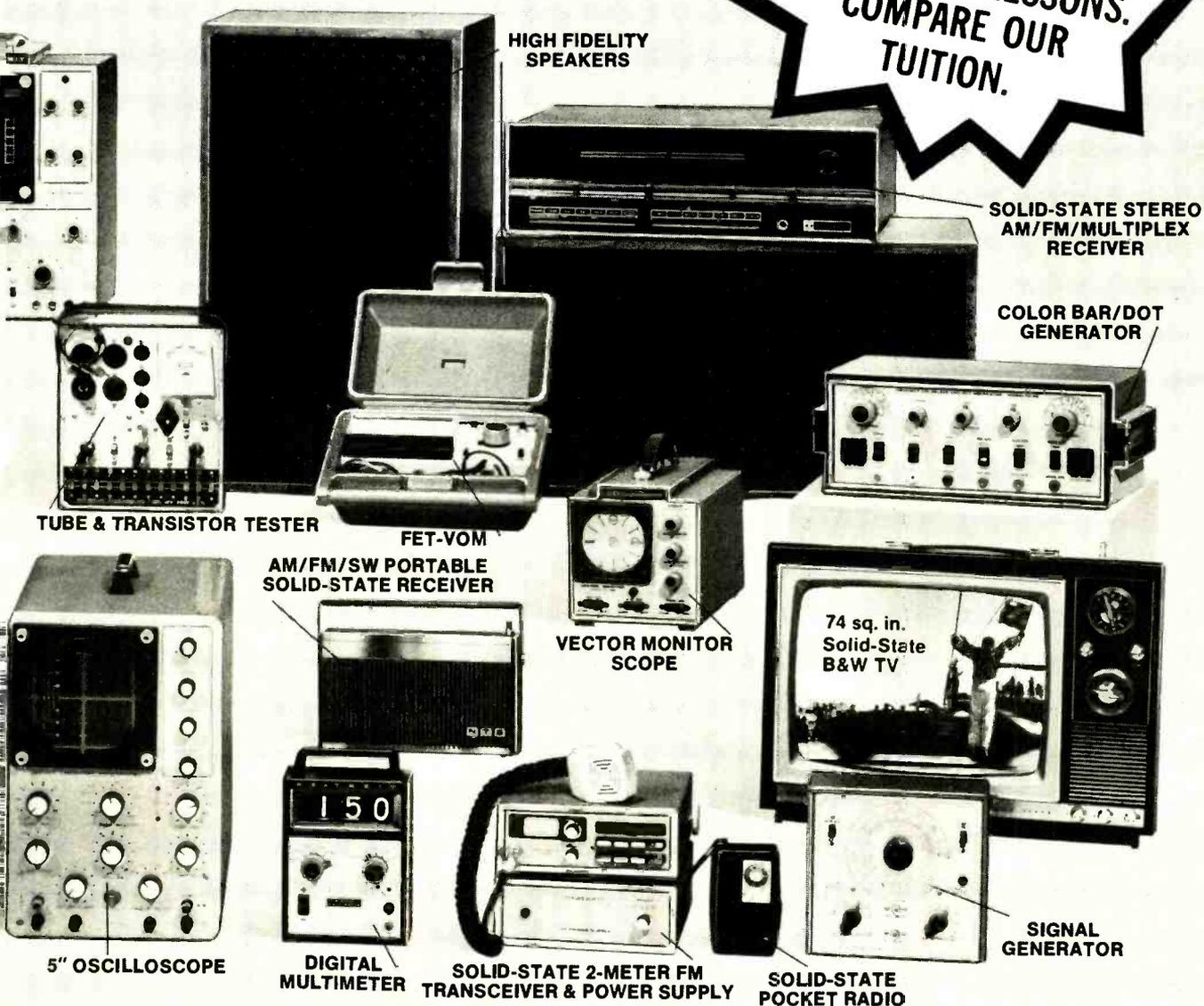COMPARE OUR
KITS AND LESSONS.
COMPARE OUR
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-056
4000 South Figueroa St., Los Angeles, Calif. 90037

Please send FREE Color Catalog and Sample Lesson.
NO OBLIGATION. NO SALESMAN WILL CALL.

- | | |
|---|--|
| <input type="checkbox"/> Color TV Servicing | <input type="checkbox"/> Electronics Technology |
| <input type="checkbox"/> B & W TV and Radio Servicing | <input type="checkbox"/> Computer Electronics |
| <input type="checkbox"/> Electronic Communications | <input type="checkbox"/> Basic Electronics |
| <input type="checkbox"/> FCC License Course | <input type="checkbox"/> Audio Electronics Servicing |


NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service _____

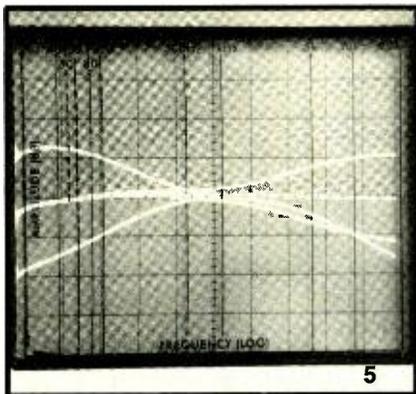- Check if interested in G.I. Bill information.
 Check if interested ONLY in classroom training in Los Angeles.



pected of them and then some. Results of our amplifier measurements are shown in Table II. The amplifier delivered 37 watts into each 8-ohm load before reaching rated THD of 0.5%. At the rated output of 27 watts-per-channel at mid-frequencies, harmonic distortion measured 0.15% though there was a tendency for the THD to rise with decreasing power output levels, suggesting the presence of a small amount of notch or crossover distortion.

Ordinarily, we would consider an overload capability of only 67 mV for the phono inputs as being on the low side but since Lafayette does offer a lower sensitivity setting for high output cartridges (at which setting overload capability increased to 160 mV) we cannot fault the phono circuits on this point.

The spectrum analyzer scope photo of Fig. 5 shows the range of control of the bass and treble controls and the action of the high-cut filter circuit which has no greater slope than the treble control when the latter is turned fully counter clockwise. We would not be overly critical of this point if the beginning of the filter action were set to a higher pivot or turn-over frequency, but as you can see from the superimposed curves of Fig. 5, the cut action begins almost at the same frequency as does the treble action. The behavior of the loudness control is depicted

TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Lafayette**

Model: **LR-2200**

AMPLIFIER PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
POWER OUTPUT CAPABILITY		
RMS power/channel, 8-ohms, 1 kHz (watts)	37	Excellent
RMS power/channel, 8-ohms, 20 Hz (watts)	30	Very good
RMS power/channel, 8-ohms, 20 kHz (watts)	33	Excellent
RMS power/channel, 4-ohms, 1 kHz (watts)	43	Good
RMS power/channel, 4-ohms, 20 Hz (watts)	38	Very good
RMS power/channel, 4-ohms, 20 kHz (watts)	41	Very good
Frequency limits for rated output (Hz-kHz)	10-32	Excellent
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.15	Very good
Intermodulation distortion, rated output (%)	0.076	Excellent
Harmonic distortion at 1 watt output, 1 kHz (%)	0.5	Good
Intermodulation distortion at 1 watt output (%)	0.053	Excellent
DAMPING FACTOR, AT 8 OHMS	36	Excellent
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA \pm -dB)	1.4	Fair
Maximum input before overload (mV)	65/160	Good
Hum/noise referred to full output (dB) (at rated input sensitivity)	67/67	Excellent

TABLE III

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Lafayette**

Model: **LR-2200**


OVERALL PRODUCT ANALYSIS

Retail price	\$299.95
Price category	Low-Medium
Price/performance ratio	Very good
Styling and appearance	Excellent
Sound quality	Good
Mechanical performance	Good

Comments: While the control layout of this receiver is generally well executed, we found it awkward to have to switch through the FM MPX filter position to get from FM muting to unmuted FM operation. The muting switch should have been a separate control. The use of pin-jacks for one set of speakers and screw terminals for the other strikes us as a poor choice, since few, if any, separately purchased speaker systems come with pin cables of this sort.

Aside from these cosmetic and human engineering problems, the LR-2200 performed well for its price category. The inclusion of two full tape monitor

Marantz Model 2325

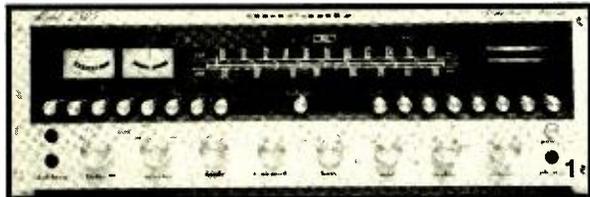

IF YOU'LL CHECK THE DIMENSIONS OF THIS hefty top-of-the-line stereo receiver from Marantz you'll find that it measures exactly the same as their popular model 4400 4-channel receiver reviewed in these pages some months ago and weighs four pounds less than that quadriphonic model. Styling is similar, too, with the easily identified thumb-wheel "gyro-touch" fly-wheel tuning arrangement (as Marantz calls it) identifying the product the mo-

ment you look at its attractively finished, precision machined front panel and matching metal knobs and buttons as shown in Fig. 1. The blacked-out dial area lights up in a soft blue color when power is applied, revealing a linearly calibrated FM dial scale, an AM dial scale and a 0-100 reference logging scale. Multicolored illuminated words appearing just above the dial scales spell out the program source selected, a red colored word indicates when

stereo is selected for other program sources by means of the front-panel MODE switch. To the left of the dial scale area are a pair of meters, each of which performs a double function. The center-of-channel tuning meter doubles as a multi-path indicator when a button is depressed, while the signal-strength meter is also used to calibrate the built-in Dolby noise reduction circuitry when that feature is selected. Centered below the dial scale, but still in the dark panel area, is a slide BALANCE control that operates horizontally from left to right. Its knob resembles the knobs of the two clusters of push-button and sub-controls located at the left and right ends of the front-panel. The left cluster of eight knobs and buttons includes a switch that selects left- or right-channel meter-monitoring of the Dolby calibration, a

TABLE II continued

HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, \pm -dB)	15-65	Very good
Hum/noise referred to full output (dB)	83	Excellent
Residual hum/noise (min. volume) (dB)	93	Very good
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	see Fig. 5	Good
Action of secondary tone controls	
Action of low frequency filter(s)	
Action of high frequency filter(s)		Poor
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	2.3/5.3	
Input sensitivity, auxiliary input(s) (mV)	220	
Input sensitivity, tape input(s) (mV)	220	
Output level, tape output(s) (mV)	210	
Output level, headphone jack(s) (V or mV)	430 mV	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		Very good
Adequacy of input facilities		Very good
Arrangement of controls (panel layout)		Fair
Action of controls and switches		Good
Design and construction		Very good
Ease of servicing		Excellent
OVERALL AMPLIFIER PERFORMANCE RATING		Very good

TABLE III continued

circuits is worthwhile, and rarely found on receivers in this price class. The high-cut filter might just as well have been omitted, since it is no more useful in reducing noise than the already available 6 dB-per-octave treble controls. The parallel connection of one of the tape out circuits on the front panel is handy when friends bring over their tape decks for dubbing of your favorite tapes.


FM reception was better than we would have guessed from reading the "numbers" but we did experience one or two cases of poor selectivity on the dial. We do object to the labelling of the mode switch. One of the positions is identified as "4 channel," suggesting four independent amplifiers, which of course are not present in this strictly stereo receiver.

As for power output, the LR-2200 is conservatively rated and more than meets its claims. The unit was found to be thermally stable even after running for several hours at high volume levels and with continuous sine-wave test signals. This Lafayette receiver offers good to very good value for the budget minded audiophile who wants control flexibility, reliable performance and good styling without having to purchase more power than he or she rightly needs. The unit will drive medium to high efficiency speaker systems to adequate sound levels for serious listening in all but the very largest home listening areas.

pair of knobs for Dolby "play" calibration, another pair for "record" calibration of Dolby, a button that actuates a 400-Hz built-in tone generator useful for calibrating the Dolby circuitry and two more buttons that select either the TAPE 1 or TAPE 2 monitor circuits and choose either source or tape to be fed through to the rest of the amplifier circuitry.

The right-most cluster of pushbuttons includes one that converts the meter to a multipath indicator, HIGH-FILTER and LOW-FILTER buttons, a HIGH-BLEND switch (for reducing noise during stereo FM listening), a LOUDNESS switch, and FM MUTING switch and individual speaker switches for MAIN and REMOTE pairs of speaker systems connected to the receiver.

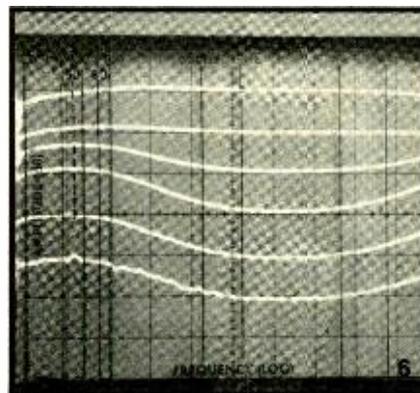in the scope photo of Fig. 6 and is typical of this type of circuit where manufacturers choose to emphasize both low and high frequencies at low volume settings.



A summary of our reaction to the LR-2200 will be found in Table III, together with our overall product analysis. In our view, whether you consider Lafayette a retailer or a manufacturer, their LR-2200 qualifies as a worthwhile product in its price category. **R-E**

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

FM TUNER SECTION:

FM Quieting: 30 dB for 1.8 μ V; 55 dB for 5.0 μ V; 70 dB for 50 μ V. **Harmonic Distortion** (mono): 0.15%; (stereo): 0.3%. **Selectivity:** 80 dB. **Capture Ratio:** 1.25 dB. **Image, Spurious and IF Rejection:** 100 dB. **AM Suppression:** 65 dB. **Stereo Separation:** (1 kHz): 42 dB.

AMPLIFIER AND PREAMPLIFIER SECTION:

Power Output: 125 watts minimum continuous average power per channel into 8 ohm loads, from 20 Hz to 20 kHz at no more than 0.15% total harmonic distortion. **IM Distortion:** 0.15%. **Damping Factor:** 70. **Frequency Response** (High Level) 20 Hz to 20 kHz \pm 0.25 dB. **Input Sensitivity:** (phono): 1.8 mV; (high level): 180 mV. **Equivalent Input Noise:** 1.5 μ V. **Dynamic Range:** (phono): 96 dB. **Tone Control Range** (bass, 50 Hz): \pm 15 dB; (treble, 15 kHz): \pm 15 dB; (mid-range 700 Hz): \pm 6.0 dB.

GENERAL SPECIFICATIONS:


Power Requirements: 120 VAC, 50/60 Hz, 550 watts maximum. **Dimensions:** 19 1/4" wide by 5 3/4" high by 18" deep (including knobs). **Net Weight:** 49 lbs. **Suggested Retail Price:** \$799.95.

The lower gold-anodized section of the panel contains eight rotary controls, some of which are dual concentric types for individual control of each channel. Such dual knobs are used for the BASS, TREBLE and MID-RANGE tone controls, while single knobs are used for master VOLUME, program SELECTOR, MODE switch, TONE MODE and DOLBY selector switches.

The TONE MODE switch requires a bit of explanation. It has positions for defeating the tone controls, and for inserting tone control circuitry in its normal form (with turnover points set at the usual mid-frequency region). In addition, there are positions that vary the crossover point of both the TREBLE control (to 4 kHz) and the BASS control (to 250 Hz) or combinations of both. In this way, a single knob is used to duplicate the function of at least two and sometimes three separate controls on other sophisticated amplifiers and receivers we have seen. As for the DOLBY switch, it is placed in the DOLBY FM position for listening to properly decoded Dolby FM broadcasts, in the PLAY position for playing back

other Dolbyized program sources or in the OFF position by bypassing of Dolby circuitry entirely, in the RECORD I position for making a Dolbyized recording of a non-Dolby program source and—you guessed it—in the RECORD II position for making a non-Dolbyized recording of a previously Dolby encoded program source.

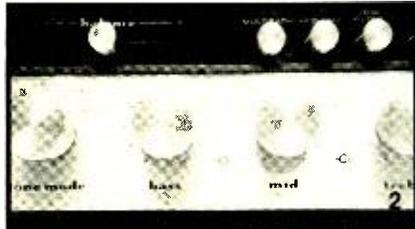Have we (or Marantz) left anything out? We strongly doubt it. The interesting combination of tone-mode and tone control knobs is shown in detail in the photo of Fig. 2. A pair of DUBBING IN and OUT



jacks on the front-panel duplicate the TAPE 2 jacks on the rear panel and are useful for connecting a tape deck without having to gain access to the rear panel once the unit has been permanently installed.

A view of the rear panel is shown in Fig. 3. Speaker connection terminals for MAIN



and REMOTE speaker systems are of the push-to-insert-wire type and are color coded. Below the speaker connectors are SWITCHED and UNSWITCHED convenience AC receptacles and a power line FUSE post. A MUTING threshold control is screwdriver adjustable and varies the signal strength at which interstation noise muting is overcome. Terminals for AM, 75-OHM and 300-OHM FM external antenna connections are spring loaded and similar to those used for speaker connection.

What Marantz chooses to call an FM QUADRADIAL OUTPUT jack is simply an FM detector output jack that provides access to the composite FM audio signal that may be needed some day for connection to a discrete 4-channel FM adaptor. A pair of screwdriver-adjustable controls are used to adjust the FM Dolby level to correspond with tones transmitted by FM stations who broadcast Dolby programs for that purpose. The usual complement of input and tape output jacks, plus a pivotable AM ferrite bar antenna complete the rear-panel layout. The flexibility of the receiver is indicated by Fig. 4 which shows how the receiver fits into a complete system and how many additional program sources can be connected to it.

Circuit description

A view of the inside of the chassis of the model 2325 is shown in Fig. 5. The power transformer is one of the most massive we have ever seen in a one-piece receiver. Power output stages are mounted on large heat sink assemblies, one on each side of the chassis. Amplified signals from the RF amplifier are fed to a triple-tuned Butterworth filter and then to an FET mixer stage. A five-section tuning-capaci-

TABLE I

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Marantz**

Model: **2325**

FM PERFORMANCE MEASUREMENTS

SENSITIVITY, NOISE AND FREEDOM FROM INTERFERENCE

	R-E Measurement	R-E Evaluation
IHF sensitivity, mono: (μ V) (dBf)	2.1 (11.8)	Good
Sensitivity, stereo (μ V)	27.0 (34.0)	Fair
50 dB quieting signal, mono (μ V)	4.0 (17.4)	Very Good
50 dB quieting signal, stereo (μ V)	55.0 (40.2)	Poor
Maximum S/N ratio, mono (dB)	74.0	Excellent
Maximum S/N ratio, stereo (dB)	72.0	Excellent
Capture ratio (dB)	1.2	Very Good
AM suppression (dB)	65	Excellent
Image rejection (dB)	100+	Superb
IF rejection (dB)	100	Superb
Spurious rejection (dB)	100+	Superb
Alternate channel selectivity (dB)	82	Excellent

FIDELITY AND DISTORTION MEASUREMENTS

	R-E Measurement	R-E Evaluation
Frequency response, 50Hz to 15 kHz (\pm dB)	1.0	Very Good
Harmonic distortion, 1 kHz, mono (%)	0.10	Very Good
Harmonic distortion, 1 kHz, stereo (%)	0.50	Fair
Harmonic distortion, 100 Hz, mono (%)	0.09	Excellent
Harmonic distortion, 100 Hz, stereo (%)	0.90	Fair
Harmonic distortion, 6 kHz, mono (%)	0.12	Very Good
Harmonic distortion, 6 kHz, stereo (%)	0.27	Very Good
Distortion at 50 dB quieting, mono (%)	0.67	Fair
Distortion at 50 dB quieting, stereo (%)	0.60	Good

STEREO PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
Stereo threshold (μ V) (dBf)	27 (34.0)	Poor
Separation, 1 kHz, (dB)	44	Excellent
Separation, 100 Hz (dB)	39	Excellent
Separation, 10 kHz (dB)	30	Excellent

MISCELLANEOUS MEASUREMENTS

	R-E Measurement	R-E Evaluation
Muting threshold (μ V) (dBf)	12-70 (27.0-43.3)	Fair
Dial calibration accuracy (\pm kHz @ MHz)	0.15 @ 108	Very Good

EVALUATION OF CONTROLS, DESIGN, CONSTRUCTION

	R-E Evaluation
Control layout	Excellent
Ease of tuning	Very Good
Accuracy of meters or other tuning aids	Excellent
Usefulness of other controls	Very Good
Construction and internal layout	Excellent
Ease of servicing	Good
Evaluation of extra features, if any	Good

OVERALL FM PERFORMANCE RATING

Good

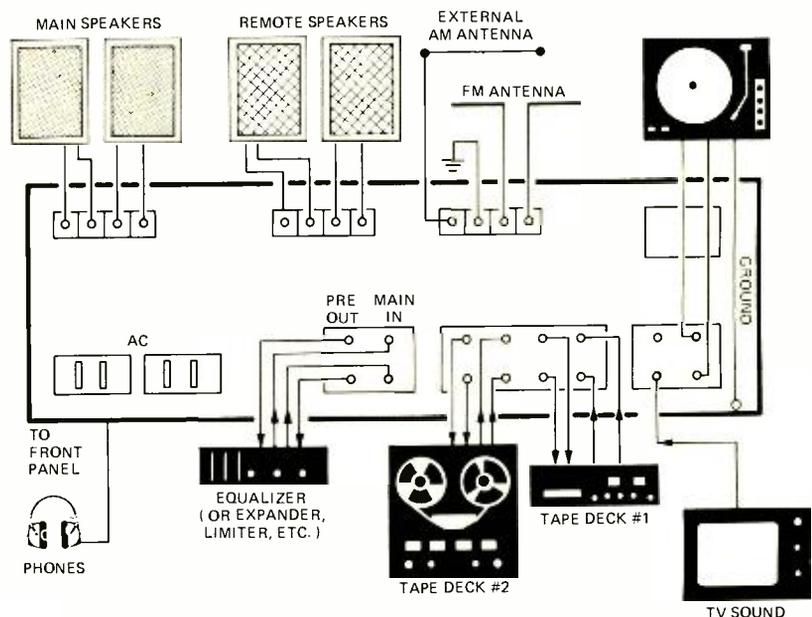


TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Marantz**

Model: **2325**

AMPLIFIER PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
POWER OUTPUT CAPABILITY		
RMS power/channel, 8-ohms, 1 kHz (watts)	140.0	Very good
RMS power/channel, 8-ohms, 20 Hz (watts)	133.0	Excellent
RMS power/channel, 8-ohms, 20 kHz (watts)	125.0	Good
RMS power/channel, 4-ohms, 1 kHz (watts)	N/A	—
RMS power/channel, 4-ohms, 20 Hz (watts)	N/A	—
RMS power/channel, 4-ohms, 20 kHz (watts)	N/A	—
Frequency limits for rated output (Hz-kHz)	11-20	Very good
DISTORTION MEASUREMENTS		
Harmonic distortion at rated output, 1 kHz (%)	0.10	Excellent
Intermodulation distortion, rated output (%)	0.11	Excellent
Harmonic distortion at 1 watt output, 1 kHz (%)	0.022	Excellent
Intermodulation distortion at 1 watt output (%)	0.004	Excellent
DAMPING FACTOR, AT 8 OHMS	73	Very good
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA \pm ___dB)	0.5 dB	Very good
Maximum input before overload (mV)	125	Good
Hum/noise referred to full output (dB) (at rated input sensitivity)	71	Excellent
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, \pm ___dB)	20-20, 0.25	Excellent
Hum/noise referred to full output (dB)	95	Superb
Residual hum/noise (min. volume) (dB)	99	Excellent
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	See Fig. 7	Very good
Action of secondary tone controls	See Fig. 8	Very good
Action of low-frequency filter(s)		Good
Action of high-frequency filter(s)		Good
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	2.05	
Input sensitivity, auxiliary input(s) (mV)	187	
Input sensitivity, tape input(s) (mV)	187	
Output level, tape output(s) (mV)	187	
Output level, headphone jack(s) (V or mV)	Not measured	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		Excellent
Adequacy of input facilities		Very good
Arrangement of controls (panel layout)		Excellent
Action of controls and switches		Very good
Design and construction		Excellent
Ease of servicing		Good
OVERALL AMPLIFIER PERFORMANCE RATING		Very good

all the way through to the loudspeaker outputs. The output stage consists of four push-pull parallel complementary-symmetry power transistors (NPN-PNP pairs). Electronic protection circuits sense excessive output current and voltage conditions and limit the signal to the driver transistors to a safe, predetermined value. Thermal compensation circuits are also provided and a relay protects speakers in the event of transistor failure and also eliminate pops and transient bursts when the unit is turned on or off.

Laboratory FM measurements

Considering the price and quality of Marantz receivers, we have often wondered why that company steadfastly refuses to quote specifications in accordance with accepted new standards. For that matter, they did not even subscribe to the old IHF standards that everyone else used for years before the new, universally accepted (by IHF, IEEE and EIA) standards became official. We don't know what they claim for usable sensitivity in the case of the 2325, since they insist on giving quieting figures only—which do not take into account distortion at low signal strengths.


By our more standardized measurement, IHF usable sensitivity was 2.1 μ V (11.8 dBf) in mono and a rather unimpressive 27.0 μ V in stereo. This is also the point at which the circuits switch from mono to stereo automatically—and far too late in our opinion. A signal level 55 μ V (40.2 dBf) was required to produce 50 dB of quieting in the stereo mode—again not particularly outstanding in view of the price and features of this otherwise excellent piece of equipment.

It wasn't long before we realized that this particular set was not optimally aligned, as evidenced by some of the other test readings (particularly stereo distortion) listed in Table I. Despite certain performance failings in FM, other performance factors such as rejection of IF, image rejection and spurious rejection were excellent—as good or better than claimed. Signal-to-noise ratio in mono and stereo was also superb. Generally, those tests which involve weak signals were the ones that turned up poor performance, indicating clearly that the front end of our sample was not properly aligned.

Laboratory amplifier measurements

The amplifier, which of course involves no alignment, did much better than the tuner section, as evidenced by the measured results listed in Table II. The output power of 125 watts-per-channel proved to be the limit at the high frequency end of the spectrum (20 kHz) rather than at 20 Hz. Unlike many amplifiers whose rated power is determined primarily by the power supply resulting in limitations at the low-frequency end of the spectrum, the Marantz 2325 delivered 133 watts-per-channel at 20 Hz with both channels driven—at a rated THD of only 0.15%. IM and THD at the low-power levels were so low as to be barely measurable on our equipment.

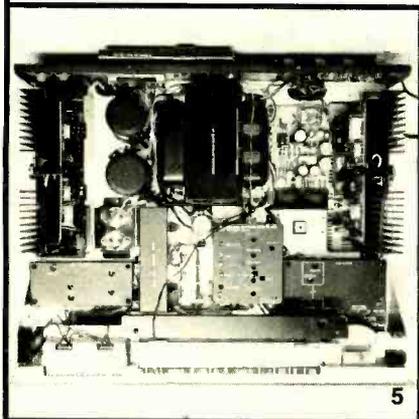In quoting phono hum and noise specifications as well as overload capabilities, Marantz again takes off on a path of its
(continued on page 65)



tor is used to tune the RF stage and local oscillator. The IF amplifier consists of eight ceramic-filters and eight IF stages including four limiter stages. Symmetrical diode limiting is used. The stereo composite signal derived from the linear FM detector and amplified by the buffer stage is first fed to an FET muting circuit and

then to the phase-locked-loop stereo demodulator IC circuit where it is decoded into left and right channel signals.

The AM tuner section consists of one IC and three transistors. A three-section variable capacitor is used for AM tuning and automatic AGC circuits are applied to RF and IF sections.

The Dolby system circuitry is a single-process two-channel circuit with inputs and outputs determined by the setting of the front-panel Dolby selector switch. The phono preamp-equalizer section provides RIAA equalization and 40 dB of gain (at 1 kHz) for phono input signals. Tone control amplifiers are of a continuously variable feedback type and turnover frequencies are determined by the TONE MODE switch explained earlier. Filters provide high- and low-frequency roll-off at a 12 dB-per-octave slope with the 3-dB points set at 9 kHz and 50 Hz.

Power amplifier stages are direct-coupled from the input differential stage

Make Graphs Work for You

Graphs contain a lot of information that can be easily misinterpreted. Understanding graphs and interpreting them correctly is easy if you know how.

by IRVING M. GOTTLIEB

GRAPHS ARE USED EXTENSIVELY IN THE TECHNICAL LITERATURE of electronics. When we see a graph depicting the relationship between a cause and its effect, we know we have encountered a fast and effortless educational mechanism. At a single glance, the behaviour of a device or system becomes clearly obvious. *But, does it?* The following scenario, though fictional, accurately discloses some misleading interpretations that can be both plotted into, and misread from graphs.

A project engineer for a large firm wanted to develop a complex system. The easiest way to get the ball rolling was to collect "building blocks" from the company's file of circuits already used for other projects. One functional block of the system required a simple low-frequency amplifier with priority on faithful response. In other words, such an amplifier had to be *linear* (input signal amplitude vs. output signal amplitude). For the purpose at hand, all other performance parameters, such as frequency response beyond a few hundred Hz, power output, gain, etc., need not be considered for the first go-around. Four departments were requested to submit examples of linear amplifiers that they had previously used. Compliance with this request was inordinately fast—perhaps *too* fast, as we shall see.

Department "A" submitted the graph shown in Fig. 1. Departments "B", "C", and "D" submitted the curves respectively illustrated in Figs. 2, 3, and 4. All claimed the amplifiers had a linear transfer characteristic as evidenced by the graphs. Although all of the graphs were valid plots of output power vs. input voltage, only one was acceptable. Let's analyze these "linear" amplifiers and see where the three unacceptables went astray.

Interpreting graphs

It cannot be said that the graph of Fig. 1 is not linear—it obviously does show a straight line relationship between the input signal voltage and the output power delivered by the

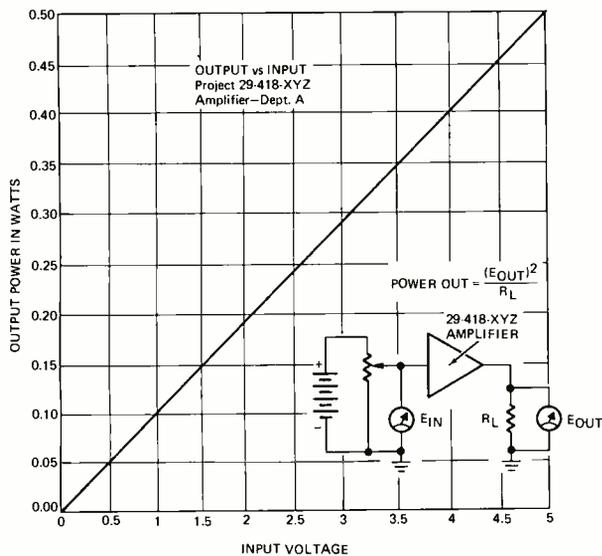


FIG. 1—STRAIGHT LINE CURVE does not necessarily describe the performance of a linear amplifier.

amplifier. But, unfortunately, such a relationship does not describe a linear amplifier. In a linear amplifier, the output power is proportional not to the input voltage, but rather to the square of the input voltage. Indeed, in any circuit, not necessarily an amplifier, power increases as the square of the voltage monitored across a constant resistance. So, we see, department A made an incorrect interpretation of their graphically-linear curve. Actually, had their amplifier been linear, it would have plotted out as shown in Fig. 5.

The plotter of Fig. 2 from department B did not forget about the square law relationship between voltage and

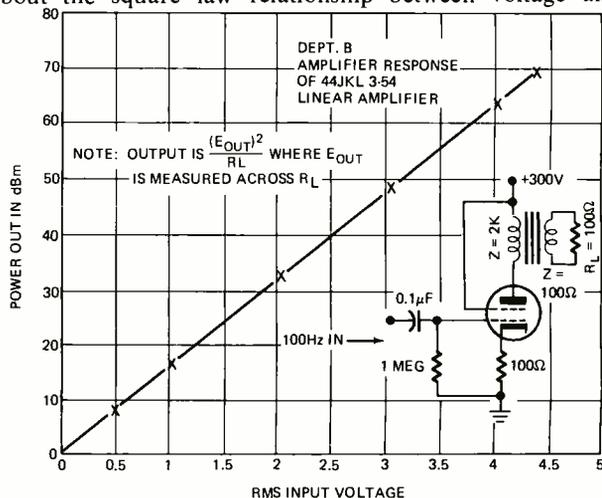


FIG. 2—STRAIGHT LINE CURVE may not be a linear graph. Vertical axis is marked off in logarithmic units.

power. However, to translate this relationship from mathematics to graphics, he used dBm units for power. Enclosed with his straight line curve was an explanation of how he obtained a straight line relationship. This, he accomplished by adjusting the bias networks in the amplifier. Alas, this amplifier, too, was relegated to the "circular file." Even with the uniformly-spaced coordinates of his graph and the use of the logarithmically derived dBm units, a little study reveals something very much wrong. For example, if the amplifier develops 20 dBm when the input signal is 1.25 volts, we shouldn't see 40 dBm for 2.5 volts input (40 dBm represents *ten times* as much power as 20 dBm. No hi-fi amplifier is this!

Having been momentarily caught off guard by department B, the project engineer inspected the graphical results of department C's amplifier (Fig. 3). With a chip-on-the-shoulder attitude, he noted the use of semi-log paper. This should have solved the oversight of department B's plotter—but hold on a minute! It happens that the technique used by department C is exactly equivalent to the erroneous plot submitted by department B. A little contemplation shows that both must be faulted for the same reason—non compliance with the square law relationship between voltage and power. More exasperated than hopeful, the project engineer turned his attention to the work of the next "contestant", department D.

Another straight line plot (Fig. 4)—but did it represent the transfer characteristics of a linear amplifier? The answer was speedily forthcoming, for it was seen that any time the

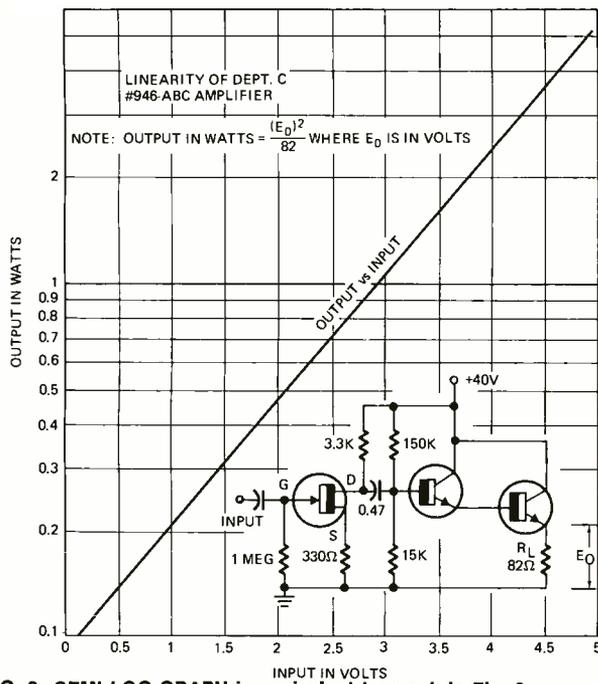


FIG. 3—SEMI-LOG GRAPH is equivalent to graph in Fig. 2.

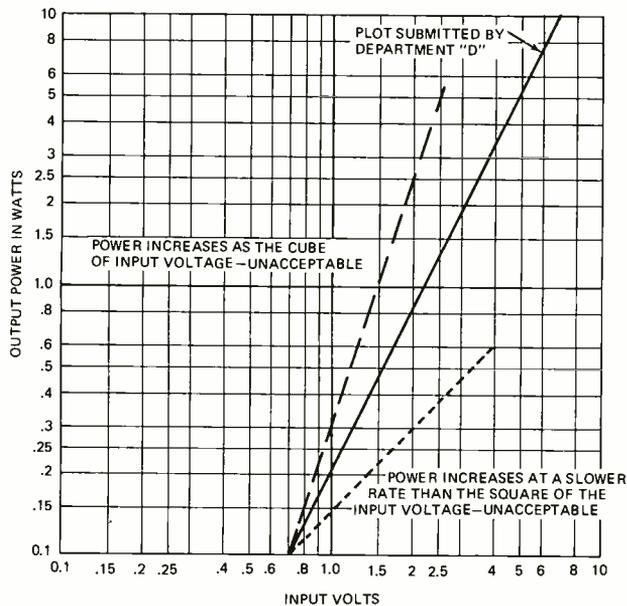


FIG. 4—LINEAR AMPLIFIER is described by solid line plot. Curve is plotted on log-log graph paper.

input voltage doubles, the output-power quadruples. This was recognized as clear evidence of the required square-law relationship. However, a straight line plot on log-log paper does not necessarily reveal a square-law relationship. For example, the dashed and dotted lines superimposed on Fig. 4 indicate other than square law functions. So, log-log paper is great, if such plots are interpreted with a practiced eye. Significantly, once it is determined that the slope of the straight line does represent the square-law relationship, we know that the amplifier is very linear indeed! This is because the slightest departure from the square-law is readily recognized as a *change in the slope of the graph*. Note that to make a similar evaluation of the curve of Fig. 5, many coordinate points and much computation would be required to determine whether the curvature is just right.

The log-log plot shown in Fig. 4 does, however, leave us in the dark concerning the operation of the amplifier at low levels. To convey full information, graphs should start at the origin—the zero-zero point. But, how does one define the

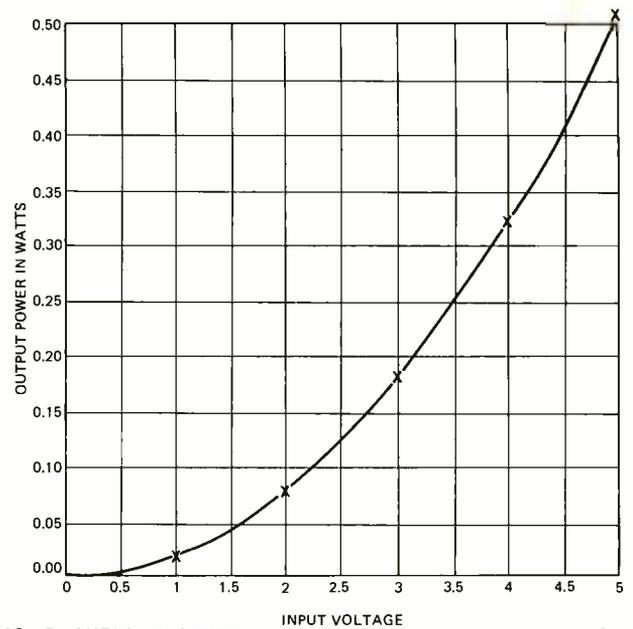


FIG. 5—CURVE PLOTTED on conventional graph paper describes linear amplifier.

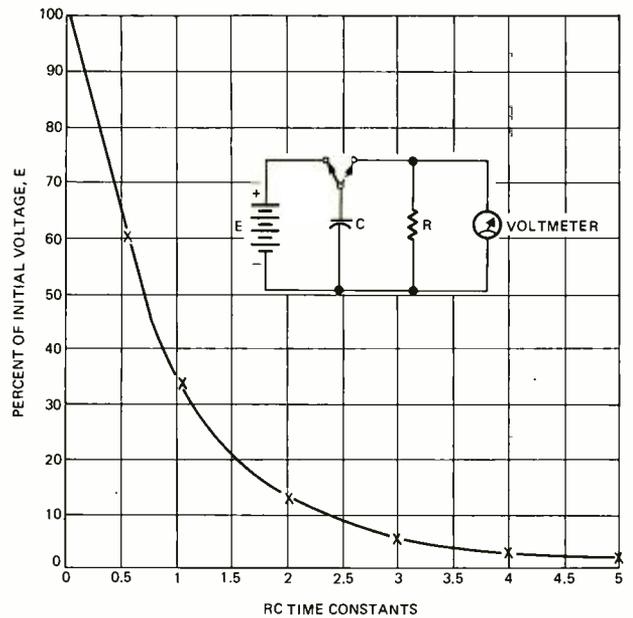


FIG. 6—VOLTAGE across a discharging capacitor presented on conventional graph paper.

origin of log-log graph paper wherein the left-bottom corner is never 0-0? Here, experience and common sense must be used. In Fig. 4, the characteristic of the amplifier is shown over an output range of 0.1 watt to ten watts. Thus, we see its performance down to one-hundredth of the highest power plotted. And if the relationship had been plotted on a three-cycle graph, rather than two, the plot would have extended down to 0.01 watt, or one thousandth of the highest power plotted. Not bad, but for the purist who must see the action right down to zero-zero, the log-log graph will forever frustrate him regardless of the number of cycles used.

Log graphs

Open almost any engineering textbook to the chapter on *transients* or *energy storage*, and the chances are good that you'll find graphs similar to that shown in Fig. 6. This graph tells us what percentage of original voltage is left in a charged capacitor C after a discharge path is provided by a resistance R. Time is scaled off in R-C units, otherwise known as time constants. (To determine actual elapsed time in seconds, simply evaluate the R-C product—thus; if R = 100,000

ohms and $C=5.0$ microfarads, then one time-constant = $1 \times 10^5 \times 5 \times 10^{-6} = 5 \times 10^{-1}$ or 0.5 second). The curve of Fig. 6 has the following shortcomings:

- Many points must be plotted to produce an accurate plot.
- The measurement of coordinate values is difficult.
- After two, and most certainly three time-constants, both plotting and reading become increasingly difficult.

Consider next, the same function plotted on semi-log paper. In Fig. 7, the plot is made on two-cycle paper. Note that the time constant corresponding to 1% of the initial capacitor voltage can be accurately determined. And with

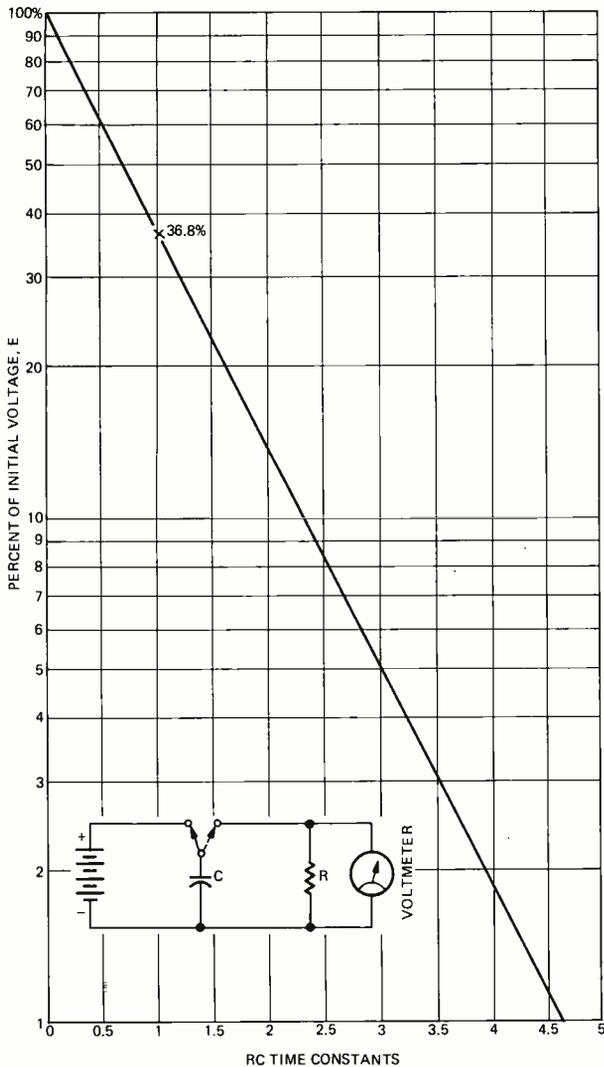


FIG. 7—SEMI-LOG PLOT of the voltage across a discharging capacitor.

three-cycle paper, the range could be extended down to 0.1% of the initial voltage. Another aspect of this graphical technique is that we only need know two coordinates to lay out such a "curve" for any number of time constants. It happens that we already know those two points! At zero time, the capacitor voltage is 100%. And it is a mathematical axiom that one time-constant always corresponds to a capacitor voltage of 36.8%. We do not even have to know the values of R or C to make this straight-line plot. Even if the plot on ordinary graph paper shown in Fig. 6 were desired, it would be wise to first construct the semi-log graph. With this procedure, we avoid measurements and math.

An interesting and useful straight-line graphical technique is illustrated in Fig. 8. This is the plot of the reactance of an electrolytic capacitor as a function of frequency. In other words, it is a plot of $1/2\pi fC$. A quick inspection of this log-log graph tells us that this is not the best of capacitors for

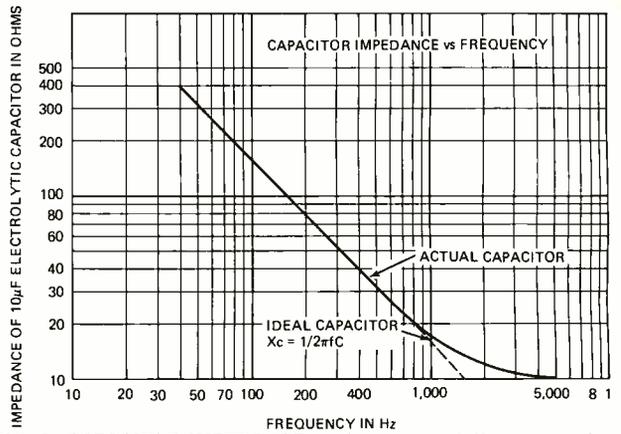


FIG. 8—CAPACITOR IMPEDANCE vs. frequency plotted on semi-log graph paper.

hi-fi amplifier circuits or for the output capacitor of a regulated power supply. The change in the slope of the plot in the 7 kHz to 10 kHz region, and thereafter, indicates that the impedance of this capacitor no longer obeys the law, $X_c = 1/2\pi fC$ for these higher frequencies. The practical aspect of this is that the bypass or filter-action of this capacitor becomes progressively worse at higher frequencies. Note that this phenomenon is not obvious in the "conventional"

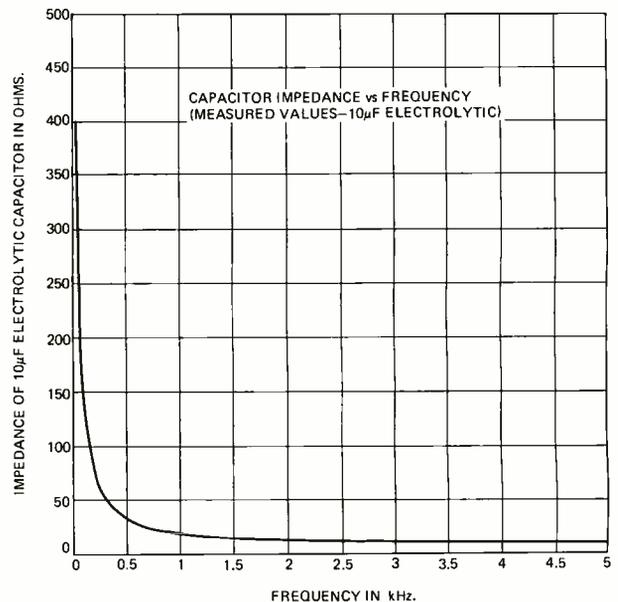


FIG. 9—CONVENTIONAL plot of capacitor impedance vs. frequency. Data is identical to that shown in Fig. 8.

plot of Fig. 9. Here, several or more computations would be required in order to discover the poor high-frequency performance. To make matters even worse, Fig. 9 is both difficult to plot and to read.

When to use which graph

A natural question is when to use conventional, semi-log or log-log graph paper. First, it is permissible to use any type of graph to represent any relationship! All three techniques can display cause and effect information. The subtle trap lying in our pathway is the interpretation of the shape of the plotted curve. With regard to straight line graphs on log paper, the following rules apply:

Semi-log paper: Use for exponential functions. This includes the equations for the charge and discharge of voltage or current in R-C or L-R circuits. Plot voltage or current on the vertical axis. Plot time units on the horizontal axis. The plotted "curve" will then be a straight line.

(continued on page 90)

R-E's Service Clinic

Loop circuits

A circuit that controls itself

by JACK DARR
SERVICE EDITOR

A LOT OF "LOOP CIRCUITS" ARE USED IN electronics; feedback loops, control loops, and on and on. We find a lot of them in TV and radio. By a "loop circuit" I mean a function consisting of an active circuit (amplifier, oscillator) and a control circuit. The output of the circuit is used to control its own action. When we find trouble in such a circuit, we must remember that it could be one of two things: a fault in the active circuit or a fault in the control circuitry.

Let's look at the basic test method we must use. We have a circuit with two parts. So, we can't tell which one is the guilty one as is. To isolate the trouble we disable the control circuitry and let the controlled circuit run free to see if we can get a normal output from it. If it will do this, we know that the fault is in the control circuit; if it still won't work, the fault is in the active circuit.

A good example of this is the horizontal oscillator and AFC circuit. This is a servo-loop; the phase of the reference signal is compared to the phase of the horizontal sync signal. The result is a small DC voltage directly proportional to the phase error. This voltage is used to control the frequency of the horizontal oscillator. (Yes; this is a phase-locked loop. The horizontal multivibrator type of oscillator is actually a voltage-controlled oscillator.) Figure 1 shows a block diagram.

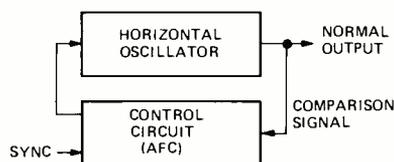


FIG. 1

Troubleshooting

Suppose the horizontal oscillator won't run on-frequency. We have two possibilities; either the horizontal oscillator has a bad part which is throwing it off-frequency or a fault in the AFC Automatic (Frequency Control) circuit is pulling it off frequency. So, we kill the AFC by grounding the output of the phase detector.

In the tube-type multivibrator circuit, we have an open grid that isn't really needed in the oscillator itself. The AFC control voltage is applied to

this grid. If the frequency goes high, the AFC develops a voltage that pulls it back on. If it goes low, the voltage is of opposite polarity. If the oscillator is running right on frequency, this grid will be zero volts. To clamp this and kill the AFC, we simply ground this grid.

Now check to see if the oscillator will run on-frequency under this condition. Adjust the frequency control (horizontal hold) to see if you can get a *single* picture, with straight sides. If you can, the oscillator is definitely able to run on-frequency. This picture will float from side to side since there is no control, but if you can see that there is only one picture, that's it. We've cleared the oscillator circuit.

Now put the AFC back in. The picture should snap in sync and hold. If it falls *out* of sync, we know that there is a fault in the AFC circuit. In only two steps we have isolated the cause of the trouble. This narrows it down to about 4 or 5 components—the AFC diode unit and a few resistors and capacitors.

AFPC

There are several other common circuits that are actually identical to this one. The Automatic Frequency and Phase Control (AFPC) in a color TV set works exactly like the horizontal AFC. All tests and reactions are the same. The only difference is in the observed symptoms. In this case the color will fall out of sync while the picture remains locked.

To break the control loop and let the 3.58 MHz oscillator free-wheel, just kill the control voltage. In most sets this is done by grounding the grid of the burst amplifier. Now adjust the frequency control(s) to see if you can make the colors straighten up and hold momentarily. Note the similarity of the color-rainbows to a picture out of sync horizontally. Out of sync, they make slanting lines of red, green and blue. As the frequency control is adjusted, they will become fewer and wider, and slant less.

If the oscillator can be adjusted to the right frequency, the bars will straighten up and the colors lock in momentarily. If you can *not* make them lock in, the oscillator is not able

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included, we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, N.Y. 10003.



**save on gas!
save on tune-ups!
save on maintenance!**

Electronic ignition is "IN"! So says Detroit.

Update your car with either a TIGER CD or a TIGER I breakerless system.

Enjoy the benefits of better gas mileage, quicker starting, elimination of tune-ups, 50,000 miles on points and plugs, and reduced maintenance expenses.

TIGER MAX CD	\$69.95
TIGER 500 CD	59.95
TIGER SST CD	42.95
SIMPLIKIT CD	31.95
TIGER I	45.95

Postpaid U.S.A. only.

Tri-Star Corporation

Dept. WW, P.O. Box 1727
Grand Junction, Colorado 81501
Circle 19 on reader service card

to run on the precise frequency we need. For example, if the bars start to straighten up but then turn around and start slanting more instead of straightening up and then slanting in the opposite direction, the oscillator can't run at the right frequency (crystal slightly off frequency, etc.)

If you can get this reaction, then the oscillator circuit is working. If you put the AFPC back in the circuit and the color sync is still poor, go directly to the color sync circuits themselves—the burst amplifier, AFPC diodes, and so on. The details of the circuit differ in many sets, but if you'll check it out, the basic reaction is always the same—the burst is compared to the frequency of the 3.58 MHz oscillator and the resulting control voltage used to lock the color in place.

We could draw a block diagram of this circuit, but it would look just like Fig. 1, so we won't bother. Only the operating frequency is different!

AGC

Another loop that is often unrecognized is the IF and its AGC circuit. The IF is a multi-stage amplifier with its gain controlled by the amplitude of the video signal from its output. This is fed back to the input, once again in the form of a small DC control voltage.

Here, it controls the gain of the circuit so that it will neither clip nor drop below a certain level.

Test methods are exactly the same though with one minor difference. We have been killing the control by grounding things to clamp the active device input at zero. Now we have to use a definite value of DC voltage to clamp the control loop. If we have what we think is an IF problem, its symptoms will be no picture at all or a distorted picture—too dark, too light, etc.

So, we clamp the control voltage so that the IF amplifier is held at maximum gain. Now, we use the same old simple method—look at the picture! If we can get a good picture, this shows that the IF stages are able to amplify the signal properly.

How do we know exactly what voltage and polarity we need to do this? Look at the schematic! The bias voltages shown on the IF amplifiers are read at *no-signal input*. In this condition, they are at *maximum gain*. This may be a very low DC voltage or quite high and of either polarity. The last is especially true in solid-state TV sets. Just check the voltage shown on the schematic and hook up a bias box to the AGC test point. This will always be somewhere in the grid return circuit

(continued on page 68)

Now you can stock only 300 semiconductors instead of 112,000.

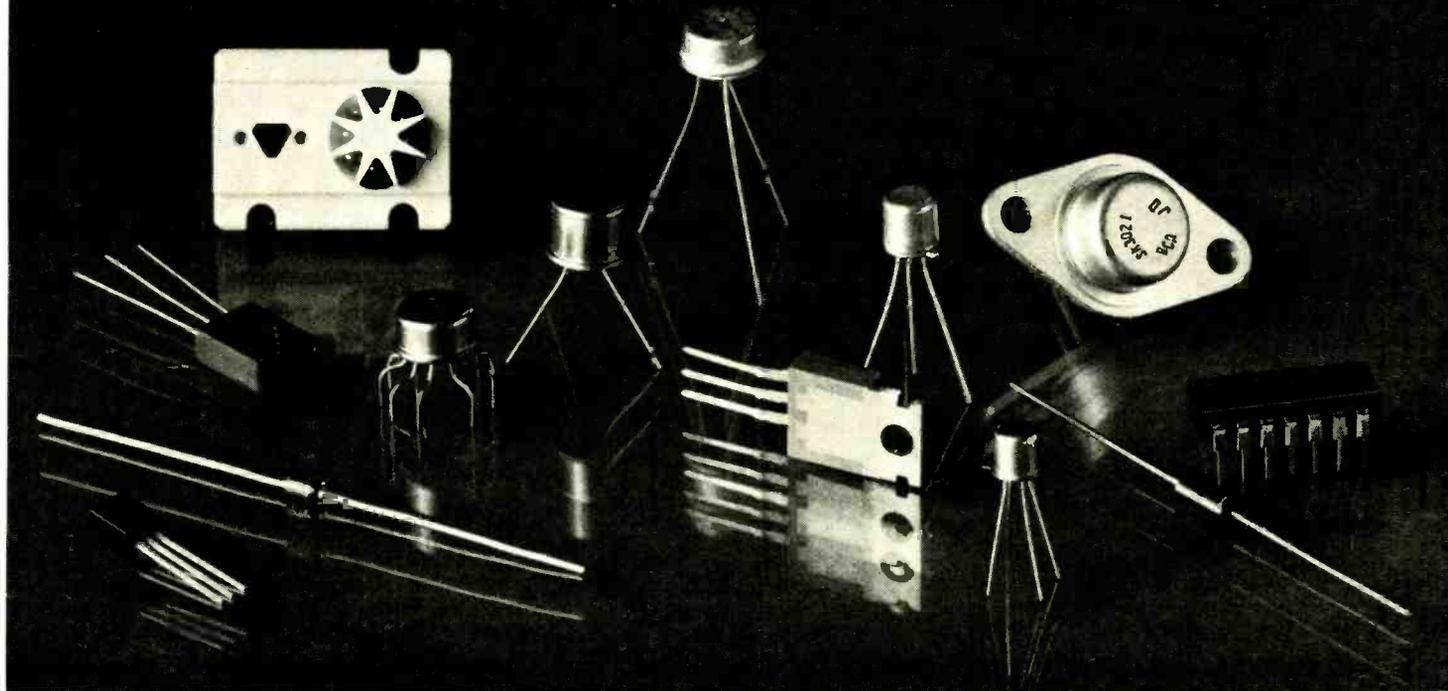


TABLE III

RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Marantz

Model: 2325

OVERALL PRODUCT ANALYSIS

Retail price	\$799.95
Price category	High
Price/performance ratio	Good
Styling and appearance	Excellent
Sound quality	Very good
Mechanical performance	Excellent

Comments: We especially appreciated the tone control permutations available on this receiver. With its selectable crossovers for both bass and treble plus the extra mid-range control it comes close to being able to adjust response for almost any listening situation or component deficiency, much like the separate graphic equalizers can do. Clearly, the amplifier has enough power to drive virtually any speaker system to loud, clean listening levels and it seemed adequately protected in terms of thermal overload and accidental shorts. We suspect that in our sample, FM performance, and particularly stereo FM performance, was not up to standards and that a minor realignment could have brought things into line. Stereo switching takes place at too high a level, preventing reception of weaker stations in that mode. Stereo sensitivity was also poorer than on receivers costing far less, all of which suggests that quality control must have missed a few points on this one. We very much doubt if this is a design fault, having measured any number of Marantz tuners and receivers that do much better on FM and stereo FM. It is our policy, however, to "call them as we see them", since an unsuspecting consumer could just as easily have ended up with this particular unit.

Performance of the amplifier section and preamplifier section, on the other hand, was as near perfect as anything we've heard from an all-in-one receiver. The front-panel control arrangement is sensibly organized, considering the number of control features, tape monitoring facilities, and the like.

(continued on page 66)

**MATHEMATICS
ADVANCED MATHEMATICS
ELECTRONICS
ENGINEERING MATHEMATICS**

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has *personally* lectured in the classroom to *thousands* of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing it!

WE ARE THIS SURE:—you order your lessons on a money-back guarantee.

In plain language, *if you aren't satisfied you don't pay*, and there are no strings attached.

Write today for more information and your outline of courses.


You have nothing to lose, and everything to gain!

**The INDIANA
HOME STUDY INSTITUTE**

P.O. BOX 1189

PANAMA CITY, FLA 32401

Circle 20 on reader service card

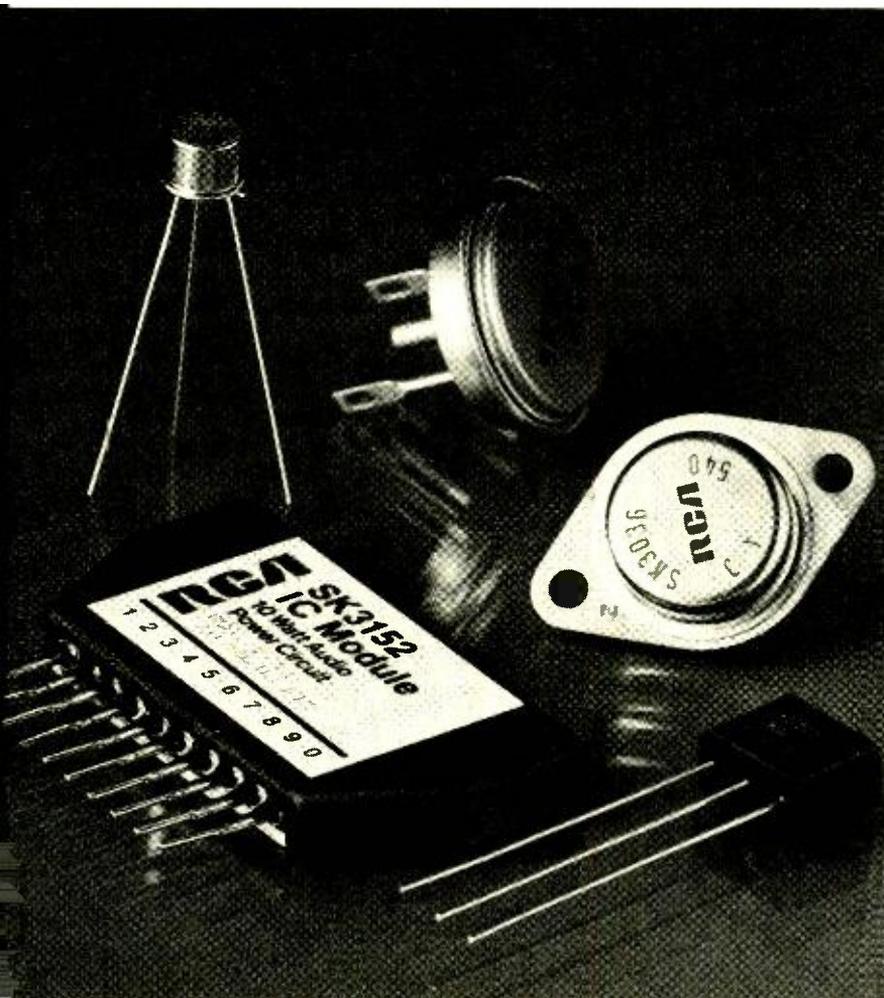

With RCA's SK Series you need stock fewer different semiconductors than you'd have to with any other major brand. Because our 300 devices can replace 112,000. And they're all immediately available.

OEM Quality. You don't have to be concerned about quality with RCA SK's. They measure up to strict AQL Standards to protect you from time-wasting callbacks. Lets you make more calls. And more profits.

See your RCA Distributor for a copy of the new RCA SK Replacement Guide. Or send \$1.00 to RCA Distributor and Special Products Division, P.O. Box 85, Runnemede, N.J. 08078. Phone: (609) 779-5735.


RCA SK Replacement Semiconductors

R-E LAB TEST REPORTS


(continued from page 65)

own. This time, the numbers are at least translatable to ones we are all more accustomed to reading. For example, when Marantz says that phono input noise is 1.5 μ V and that input sensitivity for full output is 1.8 mV, it is easy enough to establish a ratio of these two numbers, take a log of the ratio and multiply by 20 to get the S/N ratio in dB. It works out to 61.5 dB, but why not state that in the first place. In fact, we measured an impressive 71 dB for this important specification. In the case of overload capability of the preamp-

equalizer section, Marantz comes up with a figure called dynamic range, which they define as the ratio of input overload voltage to equivalent input noise. Happily, our scientific calculator could translate all this to a millivolt figure for phono overload which turns out to be about 95 millivolts, given their "96 dB dynamic range" specification. Again, our test sample did much better than that, with overload of the phono inputs occurring at about 125 millivolts—not the highest we have measured for a receiver but certainly good enough. Additional lab measurements are shown in Table II and, generally speaking, the amplifier section of this receiver comes off looking a lot better than the tuner section. While no measurements are presented in

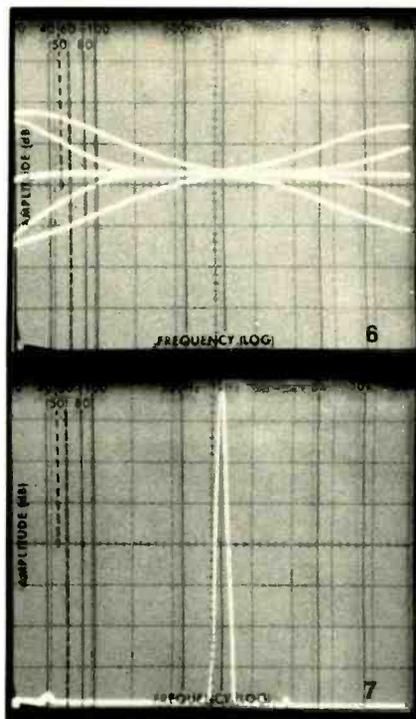

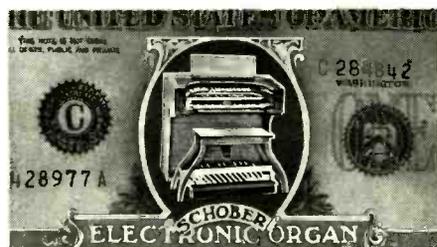terms of the Dolby circuitry effectiveness, we found it easy to calibrate these circuits for use with FM reception and recording. It should be noted that when the Dolby FM position is selected, FM de-emphasis is automatically switched from 75 microseconds to 25 microseconds as it should be.
(continued on page 76)



You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put your special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ... and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from \$650 to \$2850, and you can purchase in sections to spread costs out... or have two-year time payments.

Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see Schober quality.)

The Schober Organ Corp., Dept. RE-150
43 West 61st Street, New York, N.Y. 10023

Please send me Schober Organ Catalog.
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____

Circle 23 on reader service card



You Can Pick Up A Small Pin With These Precision Matched Points



Send For Our Free Catalog

Exactly matched teeth and jaws. Dentists would call it "perfect occlusion." You'll call it the niftiest long nose plier you've ever used. Precision made of high polished, drop forged steel. Smooth working moving parts. Long compact handles for extra reach in tight spots. Blue dipped plastic cushion grips. CHANNELLOCK. Expert craftsmanship in every detail.

CHANNELLOCK, INC., • Meadville, Pa. 16335


CHAN NEL LOCK

No. 738 G Long-Reach Needle Nose Plier

Circle 22 on reader service card

MOS KIM-1

microcomputer system

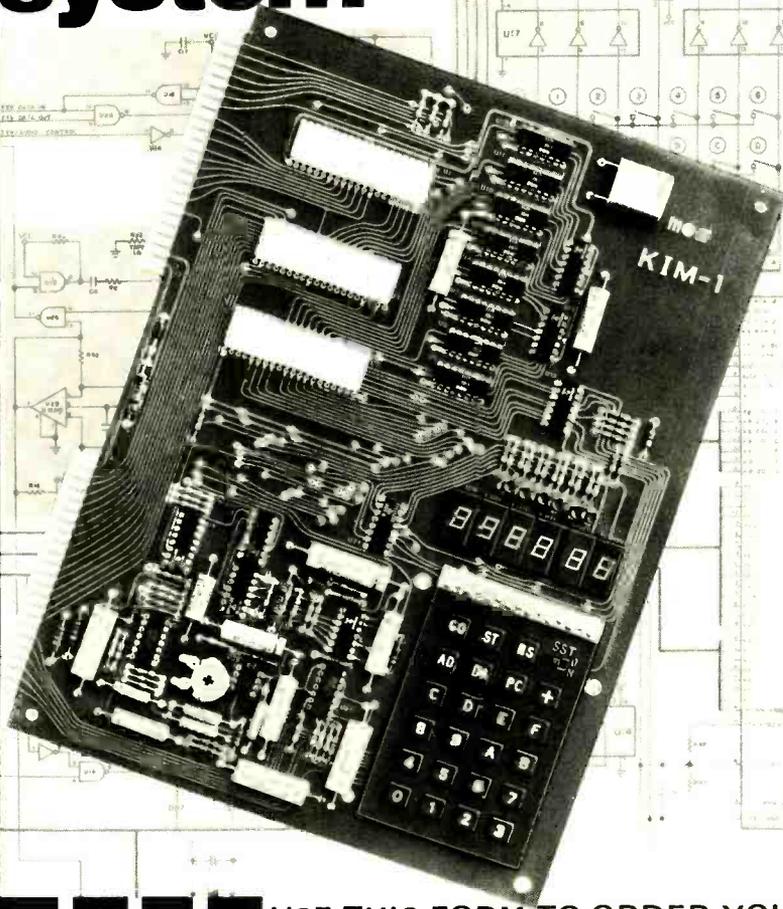

- A COMPLETE MICROCOMPUTER
- ONLY \$245
- NOT A KIT!
 - FULLY ASSEMBLED
 - FULLY TESTED
 - FULLY WARRANTED
- OPERATES WITH
 - KEYBOARD & DISPLAY
 - AUDIO CASSETTE
 - TTY
- KIM-1 INCLUDES
 - HARDWARE
 - KIM-1 MODULE WITH
 - 6502 μ P ARRAY
 - 6530 ARRAY (2)
 - 1 K BYTE RAM
 - 15 I/O PINS
 - SOFTWARE
 - MONITOR PROGRAMS (STORED IN 2048 ROM BYTES)
 - FULL DOCUMENTATION
 - KIM-1 USER MANUAL
 - SYSTEM SCHEMATIC
 - 6500 HARDWARE MANUAL
 - 6500 PROGRAMMING MANUAL
 - 6500 PROGRAMMER'S REFERENCE CARD

USE THIS FORM TO ORDER YOUR KIM-1 TODAY!

RE4

Send to:

MOS
MOS TECHNOLOGY, INC.
KIM-1, 950 Rittenhouse Rd.
Norristown, PA 19401

Please ship me _____ KIM-1 Systems: at a cost of \$245.00 per system plus \$4.50 for shipping, handling and insurance (U.S. and Canada only) PA residents add 6% sales tax.

(International sales subject to U.S. Commodity Control Regulations.
Add \$20.00 per system for shipping and handling of international orders.)

My check or money order is enclosed for \$ _____

Name _____

Address _____

City _____ State _____ Zip _____

EIGHT INSTRUMENTS IN ONE



- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212

Factory Wired & Tested—\$26.95
Easy-to-Assemble Kit—\$17.95

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:

Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me **FREE** catalog of the complete value-packed EMC line, and name of local distributor.

NAME _____ RE-5

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N. Y. 10012

For
faster
service

USE
ZIP
CODE

on
all
mail

SERVICE CLINIC (continued from page 64)

of the first IF amplifier stage if you don't have a schematic.

If you have a good strong signal, you may see that the picture shows signs of overload—too dark and with bending or buzz. If you see this, vary the control voltage toward the direction of reduced gain. If you can find a setting that gives you good picture and sound, this clears the IF stages. Go and scratch around in the AGC circuitry for the trouble.

There are quite a few other circuits that turn out to be loops. For example, the boost voltage in the horizontal output stage is one form of a loop. This voltage is developed by the high pulse-voltage from the plate of the horizontal output tube. It also serves as the *plate voltage* of that same stage. So, you can't have one without the other. Low boost-voltage produces a low output that produces low boost.

When you run into mysterious symptoms, look around carefully and see if the circuit is some form of a loop. If it is, then divide and conquer—kill the control voltage and then see if the active circuit will work. This will tell you instantly where to look for the cause of the trouble!

R-E

the SALE of the year!

We've moved to a larger location and we're celebrating with our lowest prices ever.

We carry a complete line of B & K, RCA, HICKOK, SENCORE, SIMPSON, LEADER, EICO . . . all at incredible discount prices.

A. RCA COLOR BAR GENERATOR Model WR 508. Reg. \$89.50 **NOW \$59.50.**

B. B & K DIGITAL MULTIMETER Model 280. Reg. \$117 **NOW \$99.95.**

C. HICKOK FREQUENCY COUNTER. Model 380. Reg. \$259. **NOW \$219.**

6 x 9 Air Suspension Speakers with grills

D. COAXIAL w/3" TWEETER.

10 oz. ceramic magnet; \$9.95 each, 2 for \$18.

20 oz. ceramic magnet; \$12.95 each, 2 for \$24.

E. WITH WHIZZER.

10 oz. ceramic magnet; \$6.95 each, 2 for \$12.

20 oz. ceramic magnet; \$9.95 each, 2 for \$18.

Indoor/Outdoor Weather resistant 5" Horn

F. 12 Watts peak power for CB & Stereo. Includes 10' speaker cable. \$7.99 each, 2 for \$15.



YOUR ONE STOP DISCOUNT CENTER. We have CB radios in stock! Complete line of tubes, tools and electronic supplies. Send for **FREE** 108 page catalog.



FREE

6 piece precision screwdriver set with every order.

Send check, money order or for Master Charge include MC card No. and expiration date. Minimum order \$50. Add \$2 for shipping and insurance.

FORDHAM

RADIO SUPPLY CO., INC.
855R Conklin St., Farmingdale, N. Y. 11735
Tel: (516) 752-0050

State of SOLID STATE

KARL SAVON
SEMICONDUCTOR EDITOR

LET THERE BE NO DOUBT ABOUT IT! THE microcomputer is a full-fledged member of the computer clan. All the basic functional processes are found on a single or a compatible series of integrated circuits. "Micro" is much less a characterization of the processing power than the physical size and fabrication process. As a computer, the micro carries out a programmed sequence of arithmetic and data-shuffling instructions in a way that completes a useful task. The task may be a scientific calculation, thousands of calculations, or intelligent control of a simple or complex piece of machinery.

Logic designers are learning a new discipline—programming—and leaving their AND's and NOR's behind. Many sequential logic systems that were controlled by gates and flip-flops are now done cheaper and quicker with the μ P. They are cropping up all over in electronic sales, appliances, pinball machines, auto ignition controls, games, communication controllers, medical instruments, and test equipment. Updating and logic flaws are corrected by changing a few lines of program code rather than costly circuit redesign.

But although the microcomputer is aptly named, you would be a little optimistic to expect it to replace an IBM370 or a large scale minicomputer system. Here lies one of the principal areas of confusion quite evident in discussions with people new to this revolutionary art. In general, the μ C is slower and more awkward in carrying out its computer assignments than its bigger brothers. They are the most economical when the job is small or medium sized. When the project acquires large dimensions, the computer may be the lowest cost item on the list. Outshading it will be the expensive peripherals.

There are wide variations in speed capability, in memory addressing, and instruction repertoire. Remember though that speed alone is not the selection criterion. Overall ability to do the prescribed job at the lowest cost is the objective. Some applications are best handled by 4-bit microprocessors. If there is not much computation to be done the use of an 8-bit machine would unnecessarily up the cost.

Then there are the NMOS types, a notch up including the latest with depletion mode loads. Here we have the Intel 8080 and Motorola's 6800 at 2 μ S, the Signetics, 2650 at 4.8 μ S, the Fairchild F8 at 2 μ S, and Electronic Arrays' 9002 with a 2 μ S add time.

Continuing, we come to a group of

elite devices which have been designed to be building blocks for the larger machines. These are the 2 and 4-bit slice machines with their microprogrammability and higher prices. On this list you'll find the TI L SBP0400 at 1 μ S, and the TTL group including the MMI 5701 (0.2 μ S), the Intel 3002 (0.15 μ S), and AMD's 2900 (0.125 μ S). They are in a class by themselves and are not chips you are likely to build into a home project.

[Already a number of processors have become popular with users. Notably the Intel 4040 and 8080, the Rockwell PPS-4, and the Motorola 6800 have been taken into the confidence of manufacturers.] Speed is largely governed by the monolithic process. Silicon-gate MOS seems like it will be the dominant process for a while. Using PMOS are Mostek's MK5065, Rockwell's PPS-8 and National's SCAMP, which have add times of 7, 4, and 28 microseconds respectively.

In an effort to dominate a segment of the market, each manufacturer has developed a specific computer organization or architecture which he feels best meets particular needs. Some of the latest types are designed to take a crack at minicomputer applications. General Automation has a new GA-16 system that uses two NMOS chips by Synertek. The new machines are software compatible with their versatile SPC-16 minis. Also in the mini category are Motorola's 10800 ECL, MMI's system 300 Micromini, and TI's 9900. Texas Instruments is one of the stronger contenders with a sophisticated line of hardware and software designed around the 9900. Just as minicomputers are creeping up on the big boys, micros are closing in on the minis. μ C's are today about where the mini was 10 years ago.

Micros are in their third generation of development. Concentration is now on putting the clocks on the processor chip and using single voltage supplies. The AMI 9209, TI's TMS-1000, the Rockwell PPS-1, and National's SCAMP are all efforts in this direction. Slower PMOS is used so they can sell close to calculator chip prices. National's PACE has most of the features of the earlier IMP16 on one chip reducing costs. The comparison reference for all these is the Intel 8080, the most widely used of all μ P's. San Francisco's BART system has just finished development on an automatic fare collection system using the 8080.

The μ P is only one element of a complete μ C system. It receives the lion's share of attention because its design dictates the performance limitations of the entire system to which it is connected. Designers have learned to shun types with an incomplete supporting family. When

micros first came out the designer had his hands full figuring out driver, multiplexing, and decoder circuitry. Newer devices have this critical logic on the chip. The total package count has been slashed. Interface problems have been reduced to cookbook procedures.

Understandably there is general confusion as the manufacturers huddle and reduce their prices and update their designs. Designers are uneasy that the model they are working with today will be obsoleted by next year's model. The rapidly changing technology makes it very hard to keep up. Choosing the right machine is no easy task. But using one of the leading types is a pretty sure bet. Hands on experience is vital for real solid evaluation and fortunately distributors are setting up so—they can run benchmark programs for your application on competitive machines.

When the dust clears, for an unbelievable few dollars you will see products that make life more fun. And the general purpose computer will be introduced as a mind expanding tool for both you and your school-age child.

Microcomputer news

We might as well finish up with some μ C related items.

Processor Technology Co. (2465 Fourth St., Berkeley, CA 94710) has put together an operating system for program development on Intel 8080 systems. The program listing is available for \$3 and paper tapes will be sent to computer clubs or societies.

Software Package No. 1 requires 6K of memory plus additional space for user storage of source and object files.

The operating system will keep track of 6 program files that are assigned names by the programmer. A line oriented editor is part of the package. Two assembly passes convert the mnemonic program listing produced with the editor into machine code which can then be executed by the EXEC command. The operating system will provide an output to program 1702A PROM's.

IASIS, Inc. (110 First St., Suite B, Los Altos, CA 94022) has developed a six-volume programmed learning course on microcomputers. It specifically covers the Intel series in detail starting with the 4004, through the 4040, the 8008, and the 8080. The course proceeds with 700 pages beginning with binary arithmetic through microcomputer assemblers and prototype systems.

Additional learning materials include wall-size system charts, pocket reference books, and programming pads. The introductory course is \$99.50 and has a 15-day money back guarantee. **R-E**

Learning with CIE is



Free School Catalog

Plus Free Booklet on FCC Licenses

Mail attached postcard today
for FREE information
about career electronics.

YES! I want your FREE "Education-by-Mail" career information.

I am especially interested in:

- Electronics Technology Industrial Electronics
 FCC License Preparation Electronics Engineering
 Color TV Maintenance Other _____

PRINT NAME _____

ADDRESS _____ APT. _____

CITY _____

STATE _____ ZIP _____ AGE _____

AREA CODE & PHONE NO. (_____) _____

Check box for G.I. Bill information. RE-73

- Veteran On Active Duty

CIE Cleveland Institute
of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

Find out about CIE's home study courses in Electronics for beginner, intermediate, advanced college level... the value of an FCC License and how to get one. No obligation. FREE.



Radio Electronics




Printed in U. S. A.

**Attention Veterans
and Military Personnel:**

All CIE *career*
courses are
approved under
the G.I. Bill for

**educational
benefits**

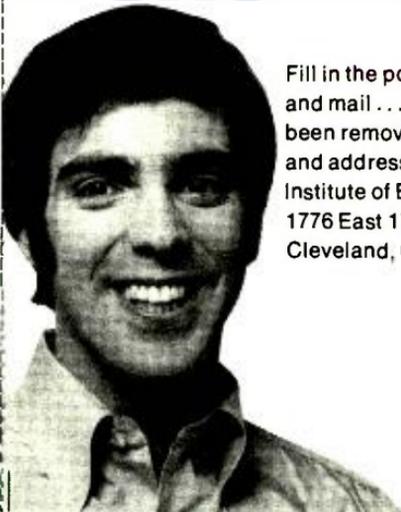Fill in the postpaid reply card
and mail . . . TODAY. If card has
been removed, send your name
and address to: Cleveland
Institute of Electronics, Inc.,
1776 East 17th Street,
Cleveland, Ohio 44114.



BUSINESS REPLY MAIL
No postage stamp necessary if mailed in the United States

Postage will be paid by—

CIE

Cleveland Institute of Electronics, Inc.
1776 East 17th Street
Cleveland, Ohio 44114

FIRST CLASS
Permit No. 8685
Cleveland, Ohio



Electronics no picnic.

**It takes work.
And a few
sacrifices.
But
it's worth it!**

The minute you start your CIE course you'll see why CIE is different than other home-study schools.

Because as a CIE student you'll get the kind of electronics training that prepares you for a career, not just a job. We'll give you a meaningful, well-rounded foundation in electronics theory and practice. And with our special Auto-Programmed® Lessons, we'll make sure you grasp the key theories and methods of modern Electronics. No "fun and games" frills. No time-wasting, superficial lesson material. No "snap" exams.

We'll challenge your thinking.

We have to. Because after you graduate, employers will expect you to really know how to analyze and troubleshoot virtually all kinds of electronics equipment. Some employers of electronics personnel have told us that our graduates have what it takes.

That's why we're so thorough. We've got a 40-year reputation to uphold and we're going to keep it by giving our students the best *independent home-study* training we can.

Sure, some of our weaker students drop out. (Learning Electronics with CIE is no free ride.) But you can bet on this... the ones who do make it are ready! Ready to go out and make it in the rewarding world of Electronics. And that's the reason you want to learn, isn't it?

You can have attractive job opportunities

There have already been many exciting developments and breakthroughs in

Electronics and some people might assume there will be no new frontiers... no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you'll find electronics skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications.

Importance of an FCC License

If you want to work in commercial broadcasting... television or AM or FM broadcasting... as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

But even if you aren't planning a career which involves radio transmission of any kind, an FCC "ticket" is valuable to have as Government certification of certain technical skills. It's a job credential recognized by some employers as evidence that you know your stuff.

A good way to prepare for your FCC License exam is to take one of the CIE career courses which include FCC License preparation. We are confident you can successfully earn your license, if you're willing to put forth an effort,

because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates have passed their FCC exams!

So if you are serious about getting ahead in Electronics... if you are willing to put in the extra work... get in touch with us.

We have many *career* courses for you to select from. If you already have some electronics training, you may want to skip our beginner-level courses and enroll in an intermediate program. Or, if you're really hot, there's a tough, college-level course called "Electronics Engineering" that can make you even better.

Send today for FREE school catalog

Send today for our FREE school catalog and complete package of *independent home-study* career information. For your convenience, we will try to have a representative call to assist in course selection. Mail reply card or coupon to CIE... or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114.

Do it TODAY.

G.I. Bill Benefits

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

CIE **Cleveland Institute of Electronics, Inc.**
1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

Yes, I want your FREE school catalog and career information package today.

I am especially interested in:

- | | | |
|--|--|-------|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> Industrial Electronics | RE-72 |
| <input type="checkbox"/> FCC License Preparation | <input type="checkbox"/> Electronics Engineering | |
| <input type="checkbox"/> Color TV Maintenance | <input type="checkbox"/> Other _____ | |
| <input type="checkbox"/> Mobile Communications | | |

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____ Age _____

Check box for G.I. Bill information. Veteran On Active Duty

Circle 27 on reader service card

DYNA-MICRO

(continued from page 38)

constantly be fed to the bus. With these two pins grounded, apply power and depress the keys, one at a time. The binary data for each keyswitch will be indicated on the LED's at all of the output-ports simultaneously. Note that the most significant bit, D7, will be on whenever one of the keys is depressed. This is often called a 'flag' since it is used to flag down the computer and tell it that one of the switches is ready with data.

The lower-left reset (R) key will not output any data since it is hardwired to the 8224 clock chip. You can check this key's operation by testing the voltage at pin 1 of IC5, the 8224 clock chip. It should normally be at about zero volts and will rise to 3 volts when the R key is depressed.

If all the keys operate correctly, peel off the protective backings and apply them to the tops of the keys.

After the power supply, voltage regulator, clock, LED display and keyboard sections have been tested, install the remaining parts. Remember to add the 0.01 μ F decoupling capacitors. If

you are only going to be using 256 words of R/W memory, at least to start, be sure that it is correctly installed in the locations allocated for IC9 and IC10. If you have not already done so, obtain one of the 1702A PROM's with the Keyboard Executive (KEX) software in it. Preprogrammed PROM's are available (see parts list) and if you already have a 1702A PROM, it may be programmed from the listing provided. There are currently a number of 1702A type PROM's available. These are the 4702A and the 8702A. These are pin-for-pin equivalents of the 1702A, but their access times are slower. The 1702A PROM's or equivalents should have a maximum access time of about 1.3 ms to work with the Dyna-Micro. If you purchase a "surplus" PROM, be sure that these conditions are met.

The PROM containing the KEX software must be placed in the location allocated for IC15. It will not work correctly if placed in the location for IC16 since the addresses will be incorrect.


Next month, the foil patterns, component placement diagram, schematic diagram of the monostable-LED circuit and the final check procedures will be given. **R-E**

THE YOUNGEST REVOLUTIONARY



From the deep jungles of jumbled software, from the rivers of mysterious circuits, he came. Mini-Micro Designer. He was tough and smart. And he glowed with purpose. To teach the people microcomputers.

Learn from the leader in the modern electronics revolution. E&L's Mini-Micro Designer (MMD-1) comes with a series of educational "modules" that teach you how to design and use a microcomputer. And you get complete documentation and full software support. MMD-1 features the 8080A central processor chip, direct keyboard entry of data/instructions, LED status indicators, and all the apparatus needed to make your first microcomputer. Novice or expert, MMD-1 gets you into action fast. Put a revolutionary on your side. Send for more information today.

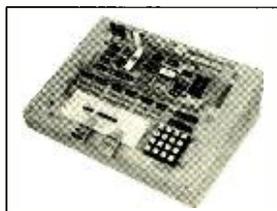

Prices start at \$125.00 in kit form.

CIRCUIT DESIGN, INC.

Division of E&L Instruments
P.O. Box 24
Shelton, Conn. 06484

Circle 28 on reader service card

FREE catalog
over 2000
unique tools,
handy kits,
precision
instruments,
technical
supplies.

Over 24 years of service to the world's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.

 **National Camera**
2000 West Union Ave., Dept. GBA
Englewood, Colorado 80110
(303) 789-1893

Circle 29 on reader service card

ALL YOU NEED FOR SERVICING CB RADIOS



... at a price you can afford.

To get started in the CB radio repair business you need several expensive test instruments or the all-in-one Zodiac U-2 CB Transceiver Service Instrument with which you can do the following:

- Check frequencies
- Measure modulation
- Check antenna SWR
- Generate AF/RF signals
- Measure power output
- Align receivers
- Tune transmitters
- Measure field strength

This compact combination bench/field instrument can be set to generate crystal-controlled RF signals and will measure 210 different frequencies—including all existing and proposed Class D channels.

In addition, you will need a 13.8-volt regulated power supply for operating CB Transceivers under test, on the bench. If you buy a Zodiac U-2 now, we will give you the power supply FREE*. Send check or money order for \$895 (in New York add appropriate sales tax) or \$100 deposit plus your written authorization to charge \$795 to your Master Charge card (be sure to give full card number) to:

ZODIAC COMMUNICATIONS CORP.

626 Chrysler Bldg., New York, NY 10017 Phone: 212/697-9585

Complete money back guarantee
if not totally satisfied.

*Offer expires July 30, 1976

Circle 30 on reader service card

Sphere Offers You A Real Computer!

A REAL COMPUTER IS:


1. A SYSTEM: One that begins at the beginning with an attractive chassis to put everything in and consists of:
 - A. CPU—To give the greatest computing power for the lowest cost ever. Motorola 6800 Microprocessor. The most advanced microprocessor available today.
 - 1K PROM...The Computer Operating Program turns on instantly.
 - 4K RAM...For storage and operating capacity for many programs.
 - REAL TIME CLOCK...To program and monitor events outside and inside the computer.
- B. CRT—To display in human language on video everything going on inside the computer. (512 characters total in 16 lines by 32 characters.)
- C. KEYBOARD—So you can talk to your Computer as fast as you can type. (72 keys of alpha-numeric style typewriter keyboard.)

2. AND A REAL COMPUTER ALLOWS YOU TO: Record and reload programs and data with inexpensive audio cassette recorder.
 - D. SIM BOARD—So you can interface to teletype, audio cassette recorders and phone. (RS232c, TTL, TTY at 60ma and 20ma (Teletype), Modem, and 2 cassette recorders.
3. A REAL COMPUTER ALLOWS YOU TO: Add more memory so you can do more processing and have more storage space
 - E. 16K MEM BOARD—About 20 pages of close type-written material (more memory up to 64K is available if needed.)
4. A REAL COMPUTER ENDS UP BY ALLOWING YOU TO: Remember huge quantities of information, and then print it out on paper when you need reports, records, checks, P.O.s, Invoices, etc., etc., etc.
 - F. PIM BOARD—To interface the computer with the line printer and floppy disk storage.
 - G. FLOPPY DISK—To remember 1/2 million characters (about 150 pages of typed material) on line with the computer.
 - H. LINE PRINTER—To print 65 lines per minute on 8 1/2" wide paper up to 4 legible copies.

THAT'S A COMPUTER!!!!


Please Contact One Of Our Distributors—

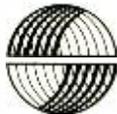Computer Way—Huntington Beach, California
 Bargain Electronics—LaMeda, California
 Comput-O-Mat Systems—Rye, New York
 The Computer Workshop, Inc.—Montgomery County, Maryland
 Computer Mart Corporated—Boston, Massachusetts
 The Computer Mart of New York—New York City, New York
 Comunicacions S.A.—San Jose, Costa Rica
 Computer Country—Denver, Colorado



SPHERE CORPORATION

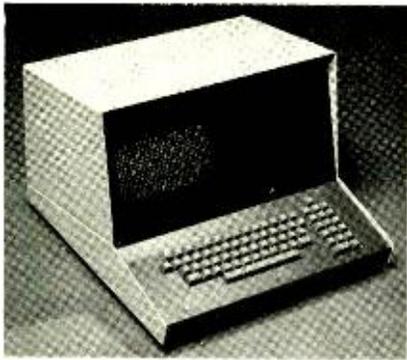
791 South 500 West Bountiful, Utah 84010
 (801) 292-8466



Circle 61 on reader service card

R-E LAB TEST REPORTS

(continued from page 66)

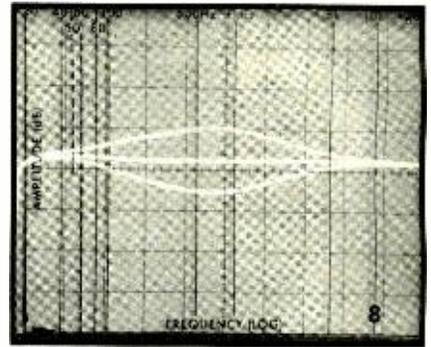

Having convinced ourselves that the tuner section was not up to par in this sample, most of our listening and further experimenting was confined to tape and record sources. These were reproduced cleanly and solidly, with no evidence of distortion or problems in reproducing difficult musical transients. Range of tone controls in both turnover positions is shown in the scope photo of Fig. 6. Our spectrum analyzer was also used to display harmonic distortion content of a 1 kHz signal delivered by the amplifier at 125 watts output (rated power) per channel. Results are shown in the photo in Fig. 7, and distortion content is seen to consist of minute amounts of 2nd and 3rd order harmonic signals, each more than 75-dB below the desired 1 kHz output. Total range of the mid-range tone control is plotted in Fig. 8.

R-E



WORLD'S SMALLEST ELECTRONIC CALCULATOR \$19.95!

Does Everything Big Ones Do

Small but mighty! 8-digit, 4-function electronic calculator even has automatic % key . . . for only \$19.95. Take it anywhere. Carry it in your pocket or purse — it's 2/3 the size of a pack of cigarettes. This 3 1/2-ounce dynamo features floating decimal, constant key, lead zero depression, clear entry, more! At Edmund's low price, the unit comes with a Ni-Cad rechargeable battery pack that can plug into any AC outlet. No need for special recharging adapters. Calculator overall is just 2 x 3 1/2 x 1/16" with plenty of room for most fingers. Another Edmund first with advanced technology. **\$19.95** ppd.
 STOCK NO. 1945EH..... Only

COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007

SEND FREE   172 PAGE CATALOG 'EH'
 Charge my BankAmericard
 Charge my Master Charge
 Interbank No. _____
 Card No. _____
 Expiration Date _____
 30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.
 City _____ State _____ Zip _____

Send me: _____
 ELECTRONIC CALCULATOR(S)
 @ \$19.95 ea. (No 1945EH) \$ _____
 Service and handling charge \$ _____ \$1.00
 Enclosed is check, m. o. in amount of \$ _____
 Signature _____
 Name _____ Please print
 Address _____
 State _____ Zip _____

We'll Bend Over Backwards To...



SPEED UP PRODUCTION OF YOUR COMPONENT LEAD BENDING OPERATIONS.



1. MEASURES EXACT BEND SPACING
2. STRAIN RELIEF CLAMPING
3. MAKES PRECISION BENDS FOR EASY INSTALLATION

CALL OR WRITE TODAY FOR FREE, COMPLETE INFORMATION.



HARWIL COMPANY
 903 Colorado Ave.
 Santa Monica, Ca. 90401
 (213) 394-4710

Circle 63 on reader service card

GIANT FREE CATALOG!

NEW 172 Pages Over 4,500 Un-usual Bargains for Hobbyists, Schools, Industry



JUST CHECK COUPON!

EDMUND SCIENTIFIC CO.
 300 EDSCORP BUILDING
 Barrington, N. J. 08007
 (609) 547-3488
 America's Greatest Science • Optics • Hobby Mart

HELPING TO DEVELOP AMERICA'S TECHNOLOGY FOR OVER 30 YEARS.
 Circle 62 on reader service card

ONE RIG DOES IT ALL!

Tube and Solid State

**THE UNIVERSAL
PJS-298**

33KV LEADED GLASS 19" CRT

EIA recommended to protect against
dangerous X-radiation

BUILT-IN SPEAKERS

Easy audio checking

40 KV METER

50aU sensitivity monitoring

FRONT CONNECTORS


Convenient cable plug-in

~~\$298.98~~ VALUE

SPECIAL INTRODUCTORY OFFER

\$229.95

COMPLETE WITH CRT

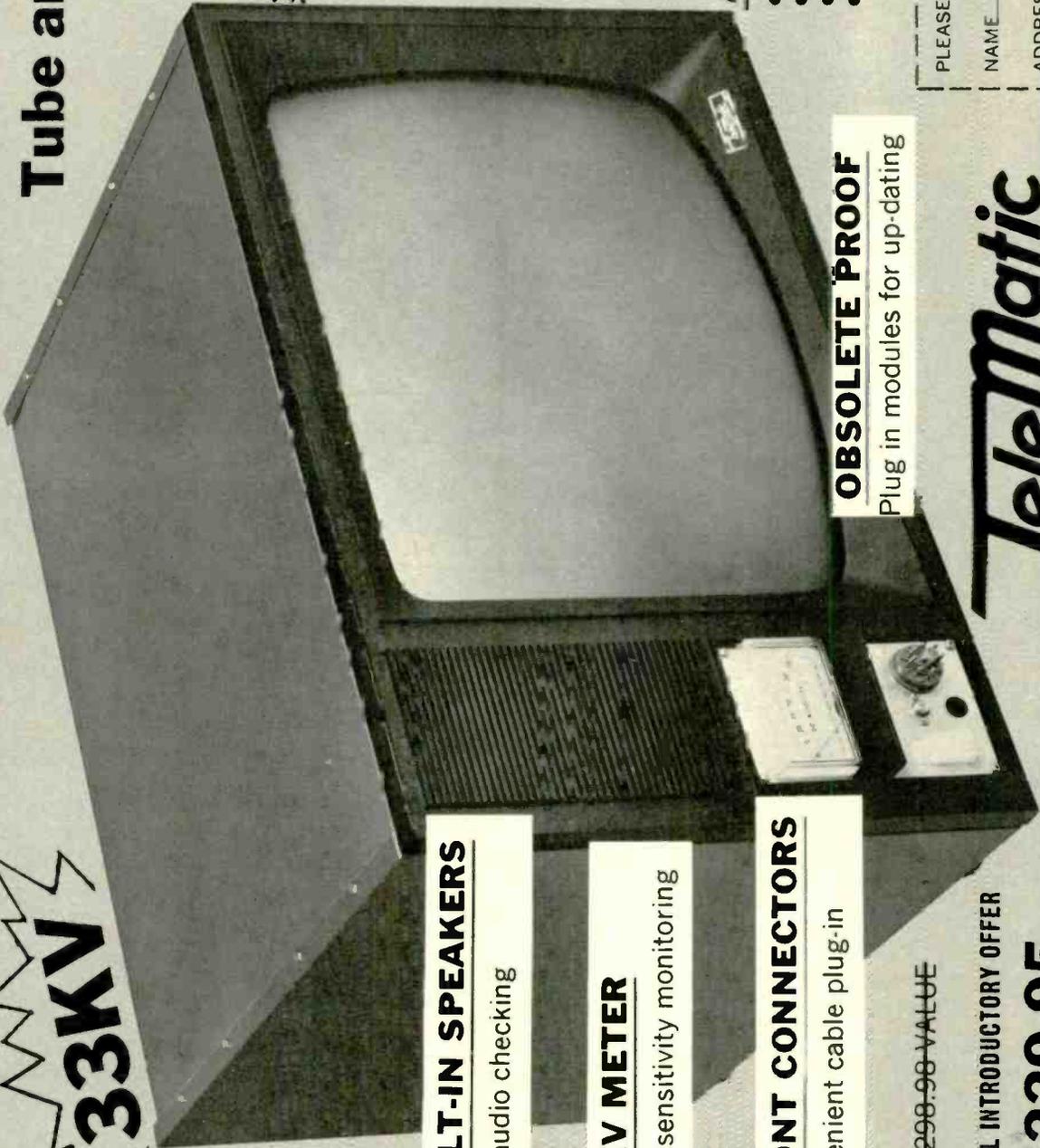

A MUST FOR TODAY'S SERVICING

ACCESSORIES INCLUDE:

- CRT 90° Extension
- Yoke Extension
- Transverter
- Convergence Load
- Universal Yoke
- Convergence Assembly
- Blue Lateral Assembly
- Anode Extension

OBsolete PROOF

Plug in modules for up-dating

PLEASE SEND ME MORE INFORMATION

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

TeleMatic

2468 FULTON ST., BROOKLYN, NY 11207

Circle 64 on reader service card

new products

how often
could you use
an Xcelite®
"99"?




it's every
tool you
need 99%
of the time...
an Xcelite original!

it's a screwdriver




...for slotted, Phillips, Frearson, Bristol, clutch head, Scrulox® screws; in inch and metric size Allen hex and Allen hex ballpoint socket types; and Pozidriv® style.

it's a nutdriver

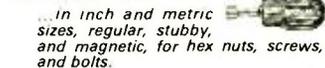

...in inch and metric sizes, regular, stubby, and magnetic, for hex nuts, screws, and bolts.

it's a reamer

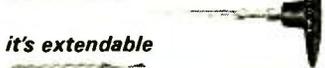

it's extendable



...for greater reach and torque.

5 DIFFERENT HANDLE STYLES


...regular and Tee, with and without reversible ratchet; junior, and stubby; all with Xcelite's unique spring device for quick blade insertion and removal. All shockproof, breakproof (UL).

85 INTERCHANGEABLE BLADES

...all the popular types and sizes. All precision-made, genuine Xcelite quality. Fit all five handles.

IN SETS, KITS, OR PIECEMEAL

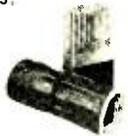...roll-up service kits, compact, stand-up, plastic-cased sets; or individually as needed.



in stock at leading
electronic distributors... nationwide

**Weller-Xcelite
Electronics Division**



The Cooper Group

P. O. BOX 728,
APEX, NORTH CAROLINA 27502

Circle 78 on reader service card

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

FET MULTIMETER. The LEM-75 is a battery-operated full-sized FET multimeter that is both portable and AC operable. It offers wide range of use for most every electronic application, employs a large 4½ inch mirror scale and has an input impedance of 10 megohms. There are full scales of 0.3 V and 30 μ A, AC and DC. Minimum sensitivities are 10 mV and 1 μ V on both AC and DC for checking and servicing extremely sensitive low voltage and low current parameters of most advanced solid-state devices in use today. The LEM-75 is supplied with an AC adapter for field or work bench use.




The unit features a \pm DC polarity switch; 8 AC and DC current ranges; and peak-to-peak voltage from 0 to 2,800 Volts. The dB range is -15 to +62 dBm (0 dB=1 mV/600 ohms); and 7 ranges of resistance from 0.2 to 500 megohms. \$149.95 complete with an LPB-13 heavy-duty test probe and the LPS-169 AC adapter. The optional, LP-05 thermistor probe (\$21.00) is useful in measuring ambient temperatures in solid-state circuits from -50°C to 250°C.

The LEM-75 measures 8¼ inches high by 6 inches wide by 5½ inches high. It also has a tilt viewing stand and weighs 5½ lbs.—Leader Instruments Corp., 151 Dupont Street, Plainview, NY 11803.

Circle 31 on reader service card

BOOKSHELF SPEAKER SERIES. Consists of three models, available in both walnut and vinyl, features excellent dispersion, smooth frequency response, clean transient attack and good efficiency. A two-way system in a closed-box baffle, the driver package in each unit utilizes 2-inch aluminum-coned tweeters with frequency response to 40 kHz and a woofer system employing a conical aluminum dome to provide the extended range, improved transients and wide dispersion. In all models the woofer is driven full range.

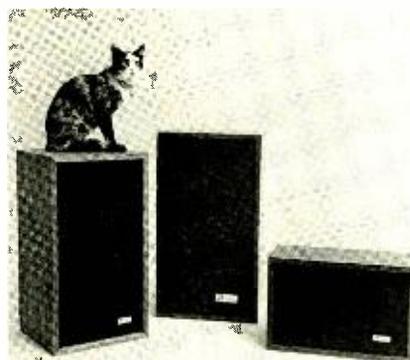The H-80V (Corinthian walnut vinyl) and H-80W (American walnut) use 8-inch woofer with the aluminum tweeter and a capacitor feed to the tweeter cutting in at 4.5 kHz; low-frequency cutoff is at 70 Hz, 17¼ × 11½ × 8 inches. Suggested list prices: H-80V—\$72.00 each, H-80W—\$87.00 each.



The H-100V and H-120W use a 12-inch woofer with two aluminum tweeters and a capacitor feed to the tweeters cutting in at 2.5 kHz; low-frequency cutoff is at 40 Hz. 25 × 14¼ × 11½ inches. A tweeter-level control on the rear panel permits adjustment for optimum balance in a particular room environment. H-120V—\$135.00 each, H-120W—\$156.00 each.—Hegeman Laboratories, Inc., 555 Prospect Ave., East Orange, NJ 07017.

Circle 32 on reader service card

CAR STEREO COMPONENT SYSTEM, Stamp 50, consists of a separate power amplifier, an under-the-dash preamp/equalizer and a 2-way speaker system with crossover net-



works. The Stamp 50 is a high-performance high-fidelity system designed to parallel the
(continued on page 80)

When you install a B-T Booster outside, you get a lot of new boosters inside.

The service technician's job is a tough one. Customers are always grumbling about the high cost of TV service calls. And they complain about poor reception—even when it's almost impossible to get a good signal.

But now and then a TV service technician wins one. And one of the products that can make him a winner, and create customer goodwill, is a Blonder-Tongue outdoor booster.

B-T Boosters can produce a dramatic improvement in picture quality, particularly on color and especially in difficult reception areas. After 25 years of making outdoor boosters, B-T is number one in sales, and enjoys the finest reputation for making

products of highest performance and reliability. B-T Boosters do cost a bit more than competition, but they perform and last longer. And that's what makes satisfied customers.

The VAULTER, for example, is the number one outdoor booster today in the B-T line... and in the entire industry. This ultra-high performance, all-channel amplifier offers the ideal combination of lowest possible noise figure (4.6dB, VHF; 7.0dB, UHF) and high gain (15dB). While it can't make unusable, snowy pictures perfect, it can reduce fading, loss of color, overcome cable loss and reduce lead-in cable noise. It can even feed more than one TV set from the same antenna in fringe reception areas. It

has separate U/V inputs and a coax output. Finally, it's specially designed for lightning prone areas.

The B-T line consists of 5 all-channel models (including the popular VOYAGER); 5 VHF models and 4 UHF boosters (the ABLE-U2b is a favorite).

See your B-T distributor for details. And see why you can count on boosters inside, when you install B-T Boosters outside. Blonder-Tongue Laboratories, Inc., One Jake Brown Road, Olc Bridge, N.J. 08857.




BLONDER-TONGUE



Circle 26 on reader service card

www.americanradiohistory.com

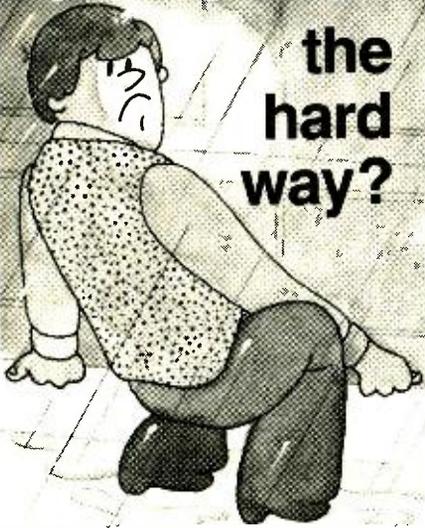Are you,
of all people,
still opening
your garage



the
hard
way?

Anybody who's into electronics

certainly should be getting the everyday convenience and family security of automatic garage door operation... especially now, with Perma Power's great Electro Lift opener... made to fit in the trunk of your car, designed for easy handling and simple do-it-yourself installation. Available now at a surprisingly low price from your distributor.



P.S. Show off your opener to your friends and neighbors. You'll probably be able to pay for yours with what you make installing openers for them.

Perma Power

Chamberlain Manufacturing Corporation
Perma Power Division
5740 North Tripp Avenue, Chicago, Illinois 60646
Telephone (312) 539-7171

Circle 67 on reader service card

NEW PRODUCTS (continued from page 78)

performance quality of home stereo components. It can be installed in a car, van, boat or airplane.

The DC-coupled Stamp 50 amplifier delivers 20-35 watts RMS per channel (40 to 70 watts in stereo). Distortion less than 0.3% THD, 20 Hz to 20 kHz at full output.

The PEQ50 preamp/equalizer has separate high- and low-frequency controls level and LED indicator. The input accepts an FM/FM stereo signal source and all 8-track and cassette players. The 6 3/4-inch rear-mounting woofers are complemented by forward-placed hemispherical Mylar dome radiating tweeters.

Speaker grilles, all wiring, crossover components and owners' installation manual are included in the kit. \$388.00.—**AudioMobile, Inc.**, 3625 McArthur Blvd., Santa Ana, CA 92704.

Circle 33 on reader service card

LIQUID CRYSTAL DISPLAYS. Standard digit sizes are 2, 4, 6, and 8 in., with large sizes up to 12 in. available on special order.

Single- and multi-digit assemblies are available with integral lighting or in a reflective-mode for external front lighting. The units are completely self-contained requiring only BCD inputs to generate numerics, and use less than 50 milliwatts of power per digit



exclusive of lighting. Excellent legibility with contrast ratios greater than 10 are achieved in ambients of up to 300 foot-candles with back lighting, and in any ambient, including direct sunlight, in the reflective mode.

Applications include message boards, process control "score boards", clocks, arrival/departure boards, and other uses requiring large numeric readouts—**North Hills Electronics, Inc.**, Glen Cove, NY 11542.

Circle 34 on reader service card

NEW SEMICONDUCTOR TESTER, the model 520B, features a new HI-LO Power Drive



system, is AC-powered and designed for maximum operating convenience for technicians at the service bench.

4 DIGIT ALARM CLOCK KIT

Contains all parts, alarm speaker, switches and PCB. 12 hour 60 Hz only.

Kit with 0.25" readouts \$13.95
Kit with 0.5" readouts \$16.95
Transformer for above \$ 2.00
(12V CT 500mA.)

6 DIGIT CLOCK KIT

12/24 Hour 50/60 Hz

Contains all parts, switches, PCB and instructions.

Kit with 0.25" readouts \$12.95
Kit with 0.5" readouts \$17.50
Transformer for above \$ 1.00
(9V 500mA.)

CLOCK CHIPS

MM5314 12/24 hour, 50/60 Hz. mux . . . \$ 3.75
MM5316 4-digit alarm, 40 pin dip . . . \$ 4.25
MK50380 4-digit alarm, 40 pin dip . . . \$ 4.95
MK50250 4-6 digit alarm, 28 pin dip . . . \$ 4.95

LED DISPLAYS

FND-503 0.5" Com Cathode \$ 1.50
FND-70 0.25" Com Cathode \$ 0.60
DL747 0.6" Common Anode \$ 2.75
DL707 0.3" Common Anode \$ 1.25

MISC. COMPONENTS

220 uF / 25V Electrolytic - PC type. . . 4 / \$ 1.00
1000 uF / 25V Electrolytic - PC type. . . 3 / \$ 1.00
1N4148 diodes PCB leads 40 / \$ 1.00
0.01uF / 50Volt Disc caps - PCB leads . . 30 / \$ 1.00
Slide switch, SPDT mini 4 / \$ 1.00

TERMS:

Send check or money order. No COD. Minimum order, \$5.00 - Orders under \$15.00 add 75¢ for postage and handling. Texas residents add 5% sales tax. Overseas countries add 20% for Air Mail. (Remit U.S. Funds only).

sabtronics
INTERNATIONAL

P.O. Box 64683, Dallas, Texas 75206, U.S.A.

Circle 68 on reader service card

FREE burglar — fire alarm catalog



over 500
systems,
detectors,
controls,
sounders,
tools, locks,
supplies

TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 96 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today.



mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

Circle 69 on reader service card

gain amplifier for meter readout. Distortion may be measured as low as 0.1% while signal-to-noise ratio can be determined from 70 dB. Signal levels may be read from 100 μ V to 300 V. The amplifier is effective to 200 kHz and measurements are possible up to and including the 10th harmonic of 20 kHz.

The LDM-170 also features a high-pass filter with a cutoff at 500 Hz; plus 6dB octave attenuation. It also features output terminals for scope connection to observe waveforms or for use as a preamplifier in low-level circuitry. The LDM-170 is 6 1/2" H x 12 1/2" W x 12" D and weighs 13 lbs. It operates on 115/230-V, 50/60-Hz power supply. \$549.95.—**Leader Instruments Corp.**, 151 Dupont St., Plainview, NY 11803.

Circle 39 on reader service card

DIGITAL ELECTRONIC STOPWATCH, model 1671, is designed for use in simple start/stop

and time in/time out applications, it is ideal for industrial time and motion studies, excellent for use in the research lab. You start,



stop and reset with one hand, and it times to 59 minutes, 59.9 seconds (with automatic

recycle) in increments of 1/10 second. Fail-safe design means timing cannot be accidentally reset. Electronics are solid-state. Compact (4.45 x 2.46 x 1.46"), lightweight (6 oz.) and durable for use in the field or lab, the watch's bright 5-digit LED display gives excellent readability under most light conditions. Neck strap and replacement AA batteries are included. \$49.95.

For under eighty dollars, you can get a watch (model 1669) with all the features detailed above, plus standard split-action for partial event times. You can freeze times on a partial event while you continue to measure total elapsed time (allows for timing of two "happenings" or participants in a single event). Rechargeable NiCad batteries, AC charger and leather carrying case are included. \$79.95.

The deluxe model 1653, similar to above but with no recharger, comes with four replaceable alkaline batteries to provide 18 hours of continuous operation. It allows for a series of individual event times without losing total elapsed time. Its 6-digit display is bright neon orange with $\pm 0.001\%$ accuracy. \$149.95. These three, and six other electronic digital stopwatches, are available by mail, postpaid.—**Edmund Scientific Co.**, 380 Edscorp Bldg., Barrington, NJ 08007.

Circle 40 on reader service card

LAFAYETTE L-8 3-WAY PEDESTAL SPEAKER, the L-8 is a three-way design employing a 10-inch woofer with a massive 4-lb. magnet structure, a 1 1/2-inch solid aluminum voice coil, and a 5-inch sealed-back mid-range speaker and four super tweeters positioned in front and either side to provide 270° sound dispersion.

The columnar enclosure incorporates an internal tuned duct for high acoustic effi-

EDLIE'S BARGAIN BONANZA ONLY HIGHEST QUALITY PRODUCTS

- SPECIAL BUY AMPEX 60 minute cassette tapes only .99¢ each 3 for \$2.69 12 for only \$8.99**
- Single conductor SHIELDED WIRE #22 Gauge good for Microphone or stereo cable. Gray color only 25 ft for \$1.00 100 foot for only \$3.39**
Same wire as above with 2 conductors and two shields 25 ft for \$1.25 100 foot for only \$4.39
- (N017) COPPER CLAD BOARDS!** Copper on one side, 1/16" thick. Excellent quality for either production or experimental work.
B) 4"x16 1/8" .99¢ ea. 3/\$2.69
D) 8x16 1/8" \$1.19 ea. 3/\$2.99
E) 6 3/8"x17 1/2" \$1.19 ea. 3/\$2.99
- (N134) 8 ROTARY SWITCHES** Some multiple gang. \$1.00
- (N128) 13 MINIATURE ELECTROLYTIC CAPACITORS \$1.00** Axial & upright, popular values.
- (N144) TRANSISTOR REPAIR KIT \$1.19** Various parts used to repair transistorized devices.
- (N336) TO-3 TRANSISTOR SOCKETS 12 for \$1.00**
- (N164) 4 ROLLS OF WIRE \$1.00** Approx. 25 ft. per roll, 20-28ga.
- (N140) TAPE RECORDER SPARE PARTS KIT \$2.95** Parts for repairing most tape recorders: capacitors, meter, pilot lamp, jacks, and MUCH MORE.
- (N167) 10 MINIATURE POTENTIOMETERS \$1.00**
- (N182) 2 MISC METERS \$1.00** Miniature.
- (N156) 60 DISC CAPACITORS \$1.00** Asst. from .0001 to .1, most 600v, Z5U, NPO, N750, etc.



SURPLUS TUBES

All guaranteed for 1 full year. ANY 3 FOR \$1.25

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard makers as RCA, GE, etc.

- | | | | |
|------|------|-------|-------|
| 3A3 | 6AQ7 | 6DE4 | 12AE7 |
| 3AF4 | 6AT6 | 6DR7 | 12AL5 |
| 3BN6 | 6AU6 | 6DW4 | 12AU7 |
| 3DG4 | 6AV6 | 6EB8 | 12AV6 |
| 3KT6 | 6AX4 | 6EM7 | 12BE6 |
| 3Q4 | 6AX5 | 6GF7 | 12BH7 |
| 4BC5 | 6AY3 | 6GH8 | 18FW6 |
| 4BN6 | 6BA6 | 6K6 | 25L6 |
| 4B8U | 6BG6 | 6K11 | 35EH5 |
| 4BZ7 | 6B8 | 6LB6 | 36AM3 |
| 5V6 | 6BQ6 | 6SN7 | 50A5 |
| 6AF4 | 6BZ6 | 6T8 | 50L6 |
| 6AG5 | 6CB6 | 6W4 | |
| 6AG7 | 6CG7 | 6X4 | |
| 6AL5 | 6CM7 | 10EW7 | |

- (N147) 4 lb. GRAB BAG SPECIAL \$1.00** Full of exotic and exciting electronics parts.
- (N155) TUBE BONANZA! \$1.00** 20 asst. popular tubes, untested.
- (N142) 50 PRECISION RESISTORS \$1.00** All 1%, 1/2w and 1w, low and high ohmages.
- (N150) 15 HI-FI KNOBS \$1.00** Every one superb! Purchased from Harmon, Kardon, Fisher, etc.
- (N102) CALCULATOR KEYBOARD \$2.95** Wild Rover C-1380. Can be used with CT5001. 4 function, clear, clear entry and constant. 7 cm x 9 cm.
- (N175) 70 1/2w CARBON RESISTORS \$1.00** Asst. values. Some 5%.
- (N154) 150 CUT LEAD RESISTORS \$1.00** Carbon, all leads long enough for soldering.
- (N149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00**
- (N132) 20 DUAL POTS \$1.00**

MONEY BACK GUARANTEE
Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

WRITE FOR FREE 1976 VALUE PACKED CATALOG
Listing thousands of components, tubes, transistors, IC's, kits, test equipment.

BONUS FREE CAPACITOR KIT With Every \$5 Purchase

THIS MONTH'S SPECIALS!

- 74\$15 Schottky 3 inp pos AND. O.C. 45¢
- 739 Dual lo-noise pre-amp 85¢
- N8815A Dual 4 inp. NOR 2 for \$1.00

TTL

- | | | | |
|-------------------------------|--------|--------------------------------|-----|
| <input type="checkbox"/> 7400 | 16¢ | <input type="checkbox"/> 7446 | 80¢ |
| <input type="checkbox"/> 7401 | 18¢ | <input type="checkbox"/> 7447 | 80¢ |
| <input type="checkbox"/> 7402 | 23¢ | <input type="checkbox"/> 7448 | 80¢ |
| <input type="checkbox"/> 7403 | 23¢ | <input type="checkbox"/> 7473 | 49¢ |
| <input type="checkbox"/> 7404 | 23¢ | <input type="checkbox"/> 7474 | 49¢ |
| <input type="checkbox"/> 7405 | 23¢ | <input type="checkbox"/> 7475 | 85¢ |
| <input type="checkbox"/> 7406 | 23¢ | <input type="checkbox"/> 7476 | 53¢ |
| <input type="checkbox"/> 7410 | 23¢ | <input type="checkbox"/> 7490 | 79¢ |
| <input type="checkbox"/> 7411 | 27¢ | <input type="checkbox"/> 7492 | 79¢ |
| <input type="checkbox"/> 7413 | 40¢ | <input type="checkbox"/> 7493 | 69¢ |
| <input type="checkbox"/> 7420 | 23¢ | <input type="checkbox"/> 7495 | 79¢ |
| <input type="checkbox"/> 7430 | 23¢ | <input type="checkbox"/> 74121 | 57¢ |
| <input type="checkbox"/> 7440 | 30¢ | <input type="checkbox"/> 74122 | 57¢ |
| <input type="checkbox"/> 7442 | \$1.12 | <input type="checkbox"/> 74123 | 67¢ |

LINEARS

- LM309K 5v la reg. \$1.15
- 555 Timer 75¢
- 556 Dual 555 \$1.00
- 566 Function gen. \$1.75
- 567 Tone decoder \$1.95
- 741 comp. op amp 39¢
- 2102 1024 bit RAM \$4.95
- 8038 volt cont osc \$4.25

CLOCK CHIPS WITH DATA

- (MM5314) 6 dig clock \$4.95
- CT 7001 Alarm & Date \$5.95

LED'S

- (N223) 10 Asst LEDs \$1.00
- (N242) 5 Jumbo Green LEDs \$1.00
- (N242) 5 Med Yellow LEDs \$1.00
- (N001) 5 Jumbo Red LEDs \$1.00
- (N011) 5 Med Red LEDs \$1.00
- (N012) 5 Mini Red LEDs \$1.00
- (N293) DL707 (equiv.) 7 seg red LED, .3" char, comm anode \$1.00
- (N007) DL747 7 seg red LED, .6" char, comm anode \$1.95
- (N013) MAN 5 (equiv.) 7 seg green LED, .27 char, comm anode \$1.49
- (N006) D.L. 704 (equiv.) same as D.L. 707 except comm-cath \$1.35

IC BREADBOARDS & TERMINALS

- Boards have .042 holes. Made of 1/16" polyester glass.
- (N8663) 3"x4" 94¢
 - (N8664) 3"x6" \$1.29
 - (N8665) 4"x6" \$1.65
 - (N8666) 4"x8" \$2.12
- Push-in terminals
- (NP6601-20) pkg 20/90¢
 - (NP6601-100) pkg 100/\$2.89
- Push-in flanged pins
- (N86602-20) pkg. 20/90¢
 - (N86602-100) pkg. 100/\$2.89
- Push-in flea clips
- (N86603-20) pkg. 20/90¢
 - (N86603-100) pkg 100/\$2.89
 - (N008) 14 pin DIP sockets 3 for \$1.00
- (N1104) IC REMOVAL AND INSERTION TOOL \$4.95
- "Pul-n-ertic" extracts and inserts IC's without damage.

BEST IN NEW ELECTRONICS BOOKS!


- Cber's Handy Manual 48 p. \$1.50
- Microprocessor/Microprogramming Hdbk. 294 p. 170 il. \$6.95
- Modern Guide to Digital Logic. 294 p. 222 il. \$6.95
- Basic Digital Electronics. 210 p. 117 il. \$4.95
- RF & Digital Test Eqmpt. You Can Build. 252 p. 217 il. \$5.95
- Practical Circuit Design for the Experimenter. 196 p. 119 il. \$4.95
- Master Hdbk. of 1001 Pract. Electr. Circs. 602 p. 1250 il. \$9.95
- CB Radio Operator's Guide. 256 p. 139 il. \$5.95
- Build Your Own Working Robot. 238 p. 117 il. \$5.95
- CB Schematic Servicing Manuals, each 200 p. \$5.95. Vol. 1 Kris, Browning, Hy-gain, J.C. Penney, (Pinto); Vol. 2 Teaberry, Unimetrics, Sears-Simpson, Siltornix; Vol. 3 E.F. Johnson, (Messenger), SBE/Linear, Sonar, Royce.
- Zenith Color TV Schematic/Svcng Manual, Vol. 4 196 p. \$5.95
- Introduction to Medical Electronics 320 p. 126 il. \$7.95
- Modern Electronics Math. 602 p. 424 il. \$9.95
- Impedance. 196 p. 90 il. \$5.95
- Aviation Electronics Handbook. 406 p. 227 il. \$8.95
- Switching Regulators/Power Supplies. 252 p. 128 il. \$6.95
- RCA Color TV Schematic/Svcng Manual Vol. 5 196 p. \$5.95
- Central Htg./Air Conditioning Repair. 320 p. 285 il. \$6.95
- MOSFET Circuits Guidebook. 196 p. 104 il. \$4.95
- Microelectronics. 266 p. 228 il. \$5.95
- Build-It Book of Miniature Test/Meas. Instr. 238 p. 151 il. \$4.95
- 21 Simple Transistor Radios You Can Build. 140 p. 122 il. \$3.95
- Op Amp Circuit Design & Applications. 280 p. 239 il. \$6.95
- Digital Logic Electronics Handbook. 308 p. 226 il. \$6.95
- Shooting with the Dual-Trace Scope. 224 p. 252 il. \$5.95
- Electronic Conversions. Symbols/Formulas. 224 p. \$4.95
- RC Modeler's Handbook—Giders/Sailplanes. 196 p. \$4.95
- Electronic Music Circuit Guidebook. 224 p. 180 il. \$6.95
- TV Schematics: Read Between the Lines. 252p. 188il. \$5.95
- Ham Novice Class License Study Guide. 224 p. 57 il. \$5.95
- Ham General Class License Study Guide. 448 p. 125 il. \$7.95
- Ham Advanced Class Lic. Study Guide. 252 p. 109 il. \$5.95
- Advanced Applics. for Pocket Calculators. 304 p. 275 il. \$5.95
- TV Troubleshooter's Handbook. 448 p. over 300 il. \$4.95
- Radio Control for Models. 350 p. 417 il. \$6.95
- Tower's International Transistor Selector. 140 p. \$4.95
- CATV Circuit Engineering. 294 p. 138 il. \$14.95
- Handbook of Multichannel Recording. 322 p. 196 il. \$7.95
- 111 Digital & Linear IC Projects. 210 p. 275 il. \$5.95
- Integrated Circuits Guidebook. 196 p. 119 il. \$5.95
- Jack Barr's Service Clinic No. 3. 252 p. 124 il. \$4.95
- 4 Channel Stereo—From Source to Sound. 252 p. 102 il. \$4.95
- Color TV Studio Design & Operation. 168 p. 69 il. \$9.95
- Practical CB Radio T. shooting Repair. 210 p. 166 il. \$5.95
- Computer Programming Handbook. 518 p. 114 il. \$8.95
- Auto Electronics Simplified. 256 p. 202 il. \$5.95
- The Complete Auto Electric Handbook. 210 p. 139 il. \$5.95
- Color TV Case Histories Illustrated. 238 p. 219 il. \$5.95
- The Home Appliance Clinic. 195 p. 61 il. \$4.95
- Amat. Filmmaker's Hdbk. Sound Sync/Scoring. 210 p. \$5.95
- The Complete FM 2-Way Radio Hdbk. 294 p. 111 il. \$6.95
- Directional Broadcast Antennas. 210 p. 60 il. \$12.95
- Troubleshooting With EVM & Scope. 238 p. 185 il. \$5.95

SEND NO MONEY! We'll invoice you on 10-DAY FREE TRIAL. Clip entire ad to order. 100% guaranteed or your money refunded.

TAB BOOKS DEPT RE-56, P.O. BOX 40, BLUE RIDGE SUMMIT, PA. 17214

Circle 73 on reader service card

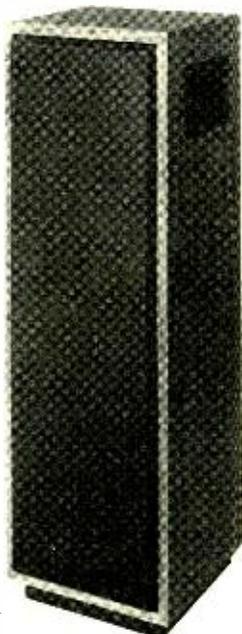ciency and improved bass response. Frequency response of the L-8 is 30-20,000 Hz. Nominal impedance is 8 ohms. Multistage RLC crossovers are used at frequencies of 2300 and 6000 Hz providing 12dB per octave. Mid- and high-frequency controls on rear



panel are used to adjust output for room acoustics. Power handling capacity is 30 watts RMS, 50 watts, program material. The cabinet is finished on four sides in a mar-proof walnut finished laminate over solid 3/4-inch acoustic wood and has a removable

LEADER 5" QUALITY SCOPES COST LESS THAN EVER!

And They're Complete With Accessories!



LBO-506
5" Dual Trace/Dual Channel Automatic Triggered Scope
It's all automatic; h'z't'l sweep, vert'l input & trigger (TV-V, TV-H). Features sep./simul. sw. mode; X5 mag; X-Y display; direct RF input; 10MHz b'width; sync's to 35MHz 10mV-20 Vp-p/cm vert'l sens. in 11 calib. steps. Probes, leads, adapters incl.

A Trend Setter! \$569.95



LBO-505
5" Trig Dual Trace/Dual Chan. Scope 15MHz Bandwidth
Outduels them all! With auto & trigg sweep; AC or DC c'pl'd per ch; 100 nsec/cm max. speed (X10mag.); sep. or simul. sweep mode display of ch 1 & 2, alter.; chop., algebra added, and vector (x-y); Sweep Range: 1µsec/cm to 0.5sec/cm, 17 steps calib. Probes, leads, adapt's. incl.

THE BEST... \$669.95



LBO-502
5" Triggered Scope w/ Graded Scale
Ideal for most every electronic application; with easy pushbutton operation; 1-2-5 graded scale readings & 15 MHz b'width. Has auto and trig sweep, 17 steps calib.; X5 mag; and 10mV to 20mVp-p/cm vert. sensitivity. Complete with probe, leads and adapter.

SAVE \$80.00 NOW \$449.95




LBO-511
5" Solid State General Service Scope
Features recurrent sweep w/automatic sync and calib vert'l input — has 140° phase control; and TV-V & TV-H w/4 sweep ranges to 100kHz. DC coupling and push-pull amps provide distortion-free stability across the 10MHz b'width. Complete with probe, leads and adapter.

SAVE \$50.00 NOW \$299.95

LEADER
Instruments Corp.

"Put us to the test"
151 Dupont Street. Plainview. N.Y. 11803 516-822-9300
In Canada, Omnitronix Ltd. Quebec
Circle 75 on reader service card

AM Comes Alive!

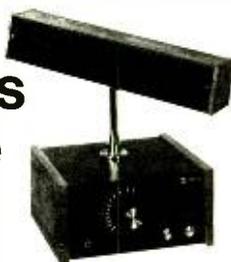

The McKay Dymek DA 5 shielded ferrite loop AM antenna has a solid state preamp with tuning and sensitivity controls.

Overcomes the two most common AM reception problems: strong local stations "hiding" weaker distant stations close on the dial, and interference from TV and electrical sources.

Improves inherent long range capabilities of AM—programs listenable from hundreds of miles.

Increases signal strength 4 to 8 times—really sharpens up AM performance in typical hi-fi receivers and tuners.

Factory direct — \$175.00 (US), ten day money back guarantee. Lease plan, BankAmericard and Master Charge welcome. For more information or to place your order, call toll free:


Nationwide 800/854-7769
California 800/472-1783

MK McKay Dymek Co.
675 North Park Ave.
Pomona, CA 91766

price subject to change without notice

Circle 74 on reader service card

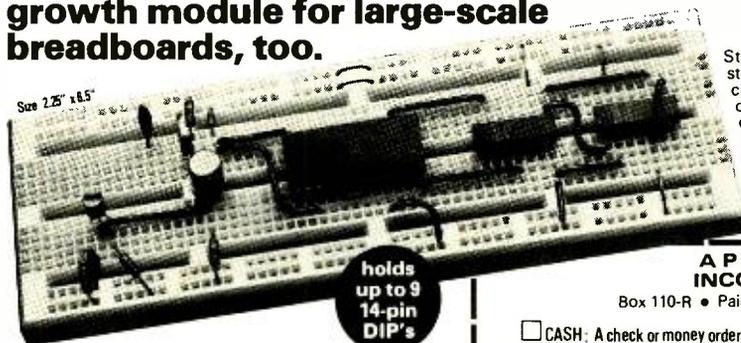use Super-strip™ for all circuit sizes ...it's a complete mini breadboard... it's a capacity growth module for large-scale breadboards, too.



Size 2 1/2" x 4 1/2"

holds up to 9 14-pin DIP's

Start with one Super-strip for small-size circuits... add more only when expanded capacity is needed. Mounts quickly on boards up to 1/8" thick.

ALL IN ONE SUPER-STRIP — you get an integral 8-bus distribution system plus room for lots of components in a matrix of 840 solderless, plug-in tie points.

Super-strip is the world's greatest "quick-change artist" for building, testing and modifying experimental circuits. No lost time doing tedious soldering — just plug in virtually any DIPs and discretes where you want them and interconnect with any solid wires up to #20. Then change anything in your circuit at will. Just unplug, move, plug in again — undamaged — where desired. Reuse everything, every time.

Buses may be used for voltage, ground, reset lines, clock lines, shift command, etc. Link buses together when grouping several Super-strips to form large-scale breadboards.

CALL YOUR A P DISTRIBUTOR TODAY

If no distributor in your area, call the factory or mail the convenient order form at right.



A P PRODUCTS INCORPORATED
Box 110-R • Painesville, OH 44077
216/354-2101 • Dealer inquiries invited

A P PRODUCTS INCORPORATED

Box 110-R • Painesville, OH 44077

- CASH: A check or money order is enclosed.
 P.O.: (Attach coupon). F.O.B. factory; Net 30.
 Charge B.A. Charge M.C.

ACCOUNT NUMBER

AND ABOVE NAME (MC) GOOD THRU

SIGNATURE

PRINT NAME

ADDRESS

CITY STATE ZIP

Quantity	Part Number	\$ Each	\$ Total
	923252 (nickel-silver terminals)	\$17.00	
	923748 (gold-plated terminals)	\$18.90	

SHIPPING/HANDLING	Merchandise Total
Up to \$10.00..... \$1.00	
10.01 to 25.00..... 1.50	Sales Tax (OH & CA)
25.01 to 50.00..... 2.00	
50.01 to 100.00... 2.50	Shipping (see chart)
100.01 to 200.00... 3.00	

Total Amount Enclosed

All orders subject to acceptance at factory

MAY 1976

FREE EICO CATALOG

346 Ways To Save On Instruments, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

**EICO—283 Malta Street,
Brooklyn, N.Y. 11207**

*Leadership in creative electronics
since 1945.*



Circle 77 on reader service card

brown foam grille. It measures 37½ inches high x 12½ x 12½ inches cross-sectionally. \$169.95.—**Lafayette Radio Electronics Corp.**, 111 Jericho Turnpike, Syosset, NY 11791.

Circle 41 on reader service card

HOME MUSIC SYSTEM. The *model RH-606* 8-track record/playback, AM/FM stereo system is one of four in the Pioneer *Centrex Series* of seven having recording capabilities. Automatic or manual program change,



lighted program and recording indicators are among features. Unit has magnetic phono input jacks, 120-volt AC outlet, front-panel microphone and headphone jacks. The two-way acoustic suspension speakers have foam grilles. \$280.—**Pioneer Electronics of America**, 1555 E. Del Amo Blvd., Carson, CA 90746.

Circle 42 on reader service card

MAGNETIC-MOUNT CB ANTENNAS. The 39-in. *Liberty series* are designed for fast attachment and removal that helps prevent thefts. The need for mounting holes or brackets is eliminated with these virtually theft-proof antennas that magnetically clamp to any 4 square-foot metallic surface on cars, trucks, RV's, or boats. (Not recommended for soft vinyl tops). The husky base magnet has



40 lb. holding power which prevents crawling or dislodgement and is ABS encapsulated to prevent surface scratches.

The *Liberty I (Model 10-275)* has a fiber glass whip, and the *Liberty II (Model 10-285)* features a weather-resistant stainless steel whip with base-load coils.

Both models have extra-distance radiation patterns and corrosion resistant stainless steel whip spring and marine-type hardware,

16 ft. coax transmission cable with a PL-259 plug, plus a capacitive impedance match that eliminates the need for matching transformers. \$27.95.—**Breaker Corp.**, Marketing Dept., 1101 Great Southwest Parkway, Arlington, TX 76011.

Circle 43 on reader service card

HAND-HELD DIGITAL MULTIMETER measures capacitance along with AC and DC volts and resistance. Called the *model 21*, this palm-sized instrument has four DC voltage ranges with 1 mV resolution; Four AC voltage ranges with 1-mV resolution; Four resistance ranges with 1-ohm resolution and four capacitance ranges with pF resolution. Other features and specifications include: 0.27" LED displays 3½ digit readout (up to 2,000 counts); simplified five-step calibration.

Designed for field or bench operation, the *model 21* operates from 4 rechargeable Ni-Cad batteries. (An optional converter for line operation is also available). Inside the high-impact polycarbonate case, the *model 21* uses all components laid down to withstand impact and shock. Only standard compo-

(continued on page 86)

BETTER THAN A THIRD HAND!



PANAVISE TILTS, TURNS, AND ROTATES TO ANY POSITION. IT HOLDS YOUR WORK EXACTLY WHERE YOU WANT IT.

PanaVise has great strength yet is gentle enough to firmly hold delicate objects.

Quite possibly the finest new tool you will buy this year, PanaVise is built to exacting professional standards. We guarantee it!

Illustrated is the Electronics Vise Model 396. Three other bases and a wide variety of heads are available. All interchangeable! Buy a basic unit, then add on to create your system.

Available through your dealer.
Write for a free catalog.

PANAVISE® Dept. 22E
10107 Adella Ave., South Gate, CA 90280
In Canada: 25 Toro Rd., Downsview, Ont. M3J 2A6



A Division of Colbert Industries

Circle 78 on reader service card

AUTOMOTIVE IGNITION SYSTEM
(continued from page 49)

the unit in the "bypass" position while setting the points.


Point contact wear is almost completely eliminated with the unit. Other point wear factors should be considered. The rubbing block surface of the points can wear. It is important to follow the car manufacturers instructions on lubricating the distributor cam surface during tune-up. Some cars have a lubricating wick; this should be replaced. On other cars, a thin layer of grease is put on the cam. If the rubbing block does wear, it will retard ignition timing somewhat. (The author has not experienced any rubbing block wear problems.)

Another possible source of failure is breakage of the points tension spring from age and fatigue. I have never seen this happen. However, it is probably good preventive maintenance to replace the points every 50,000 miles.

Due to the more positive spark from the unit, sparkplug life should be a little longer with this unit than with a standard ignition. **R-E**



Versatility Quality Low cost.

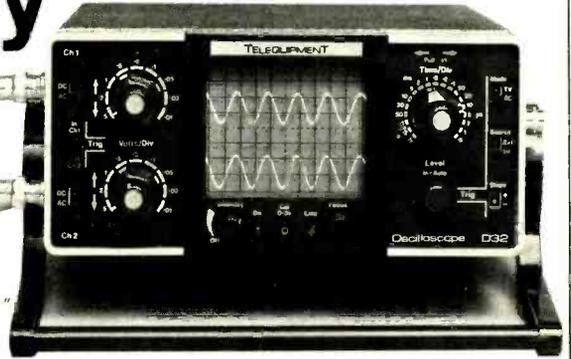

- Telequipment D32 4"x9"x11" (105mm x 230mm x 288mm)
- Dual Trace
- Automatic selection of chopped or alternate modes
- Automatic selection of tv line or frame display
- Weighs only 10 lbs. (4.5 kg)
- Versatile AC, DC or battery operation
- \$1050 includes 10x probes and batteries

For complete information, write to Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97077



U.S. Sales Price FOB Beaverton, Oregon

Circle 79 on reader service card

Help!

There's not enough space to tell how great PAIA Kits are. We have ingenious designs for Mixers, Guitar Effects Boxes, Portable Amplifiers, Synthesizers! With Step-by-Step Instructions

— SEND FOR FREE CATALOG —
PAIA ELECTRONICS, DEPT. 5-R
1020 W. WILSHIRE BLVD.
OKLAHOMA CITY, OK 73116

Circle 80 on reader service card

SOLID STATE...BREAKERLESS ELECTRONIC IGNITION.

The BEST...The ULTIMATE of All Ignition Systems

ALLISON 'OPTO-ELECTRIC'

- ★ No Breaker-Points or Condenser to EVER wear out or need any maintenance.
- ★ Once installed and properly timed your Distributor will give you **CONTINUOUS PEAK PERFORMANCE!**

● The Allison OPTO-ELECTRIC System ELIMINATES the Points and Condenser, replacing them with an Opto-Electronic Trigger, using a Light-Emitting Diode and Phototransistor. This System operates on a BEAM of LIGHT. There is NO "Breaker-Point Wiper-Arm" to wear down. Point bounce and erosion are completely eliminated thereby giving longer Timing ACCURACY than any System using "Mechanical" Breaker-Points. (and No Timing Fluctuation as with Magnetic Impulse Units). ACCURATE Timing gives the BEST in Engine EFFICIENCY...and that's the name of the Game for the BEST in GAS MILEAGE and ECONOMY.

● The Allison's "Built-In" DWELL never needs adjustment, it is PRE-SET to supply the OPTIMUM Performance at BOTH High and Low speeds. The RPM capability of the "OPTO-ELECTRIC" unit exceeds that of any known automotive internal combustion engine. Positive spark intensity and duration helps eliminate "misfire" and extends the Spark-Plug life.

● The Allison "OPTO-ELECTRIC" was engineered to OUT-LAST the LIFE OF YOUR CAR. Only the Highest Grade Solid-State Components are used. UNAFFECTED by Moisture or Vibration! Easier engine starting under ANY Weather Condition. Solid, DEPENDABLE PERFORMANCE.

★ Installed in your Distributor in same location as Points. **COMPLETE INSTRUCTIONS FURNISHED.** (Not Necessary to Dismantle your Distributor)

● America's Oldest and Largest Manufacturer of Opto-Electronic Ignition Systems.

★ **ORDER with CONFIDENCE . . . FACTORY-BACKED 10-YEAR** Free Repair or Replacement on ANY Defects in Materials or Workmanship.

★ **SAVE! ORDER FACTORY DIRECT**

- Send Check or M.O. State Make, Year, Engine Size, (4, 6, or 8-cylinder).
- You may use your **MASTER CHARGE** or **BANKAMERICARD**. Send us (1) Your Number, (2) Interbank No., (3) Exp. Date **MC or BA Card Holders. ORDER by TOLL FREE PHONE: (800) 423-6525, Ext. 2** (When in Continental U.S.A.)

★ Before Buying any other Type Ignition system. **Send Postcard for our FREE BROCHURE.**

★ If you have already installed a "Capacitive-Discharge" Ignition **Modernize and Increase its Efficiency . . . CONVERT YOUR "C-O" UNIT TO BREAKERLESS! Opto-Electric "TRIGGER UNIT" . . . Only \$34.95.**


Only \$59.95 COMPLETE (Calif. Res. add Tax) **...that's EVERYTHING!** Including Postage & Insurance.

ALLISON AUTOMOTIVE COMPANY 1267 - E9 East EDNA PL., COVINA, CAL. 91722

Our BEST Salesmen are the USERS of our ALLISON System!

Circle 81 on reader service card

SPEAKERS AT \$600 A PAIR?

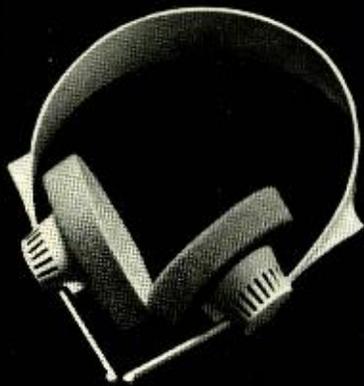

OR THESE AT \$49.75* A PAIR?

If your ears are ready for \$600 speakers, but your budget isn't, we have a way to satisfy both. Sennheiser headphones. Using the same acoustic design principles that have made our professional microphones industry standards, Sennheiser Open-Aire® headphones reproduce sound with a realism most loudspeakers can't begin to approach. With wide, flat response. Low distortion. Excellent transient response (even in the bass region!) And sheer intimacy with the music. All without sealing in your ears. Whether you're waiting for that pair of \$600 speakers or just curious about a pair of headphones some experts have compared with \$1000 speakers... the answer's at your audio dealer's.

*Manufacturer's suggested list for Model HD414. Deluxe Model HD424 also available at \$79.75.

SENNHEISER
ELECTRONIC CORPORATION

10 West 37th Street, New York 10018 (212) 239-0190
Manufacturing Plant: Bissendorf/Hannover, West Germany


Circle 82 on reader service card

NEW PRODUCTS

(continued from page 84)

nents available off-the-shelf and a single PC board are used in the model 21.

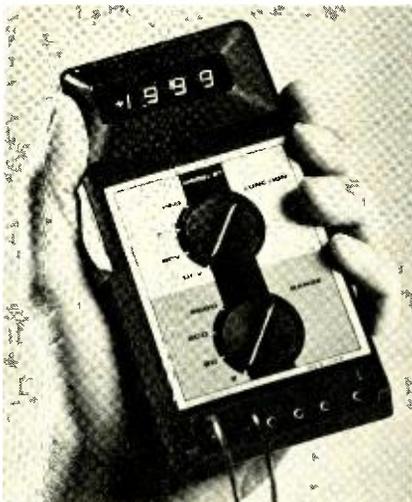To conserve battery charge life, the model 21 has a push-to-read button on the side of the case. The unit remains off until the



switch is depressed. For continuous operation, the push-to-read switch can be locked into the "on" position. An optional push-to-read probe is also available. \$189.00, complete with battery charger and belt carrying case, batteries and test leads.—Data Tech, a Division of Penril Corp., 2700 South Fairview, Santa Ana, CA 92704. **R-E**

Circle 44 on reader service card

MIXER

PREAMP

REDUCED TO
\$99⁵⁰


**MODEL CLOSE-OUT
SUPPLY LIMITED**

Boost your sound system with 5 mic input channels and feed programs to remote locations. Broadcast quality, silicon, solid state, VU meter, 600 ohm unbalanced or balanced (optional).

Few are left at this price. Send for spec sheet/order form now.

BELL dia

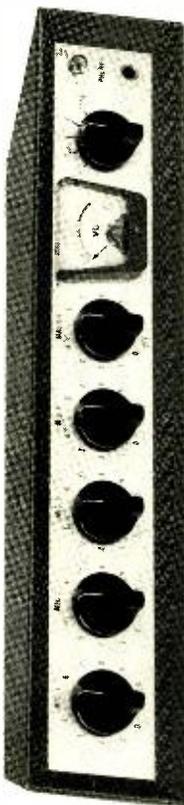BELL P/A PRODUCTS CORP.
1200 NORTH FIFTH STREET
COLUMBUS, OHIO 43201
PHONE (614) 299-1487



Circle 83 on reader service card

new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

SHORT-FORM CATALOG reviews the Wavetek line of test instruments. Included are function generators, phase meters, signal generators, sweep/signal generators, transmission test equipment, CATV test instruments, X-Y display oscilloscopes, attenuators, RF detectors and generator modules.—Wavetek, PO Box 651, San Diego, CA 92112 or PO Box 190, Beech Grove, IN 46107.

Circle 45 on reader service card

CRYSTAL GUIDE is a 68-page wealth of information listing replacement crystals for standard and synthesized CB rigs, monitor and scanner receivers and 2-meter amateur gear. All you need to know is the make and model number of the equipment or the manufacturers' part number of the desired crystal to select the correct replacement from the CTS Knights line.

Section I is a 26-page listing for standard CB rigs, Section II is an 18-page listing for synthesized equipment. Section III introduces the formulas needed to calculate the frequency of crystals needed to monitor specific channels. Section IV lists crystals for 2-meter amateur gear made by twelve manufacturers.—CTS Knights, Inc., 400 Reimann Ave., Sandwich, IL 60548.

Circle 46 on reader service card

TAB BOOKS CATALOG. The latest edition lists the hundreds of books and booklets published under the TAB and Gernsback Library labels. The contents page breaks down the many listings into thirty categories for easy location of books on any desired subject.—TAB Books, Blue Ridge Summit, PA 17214.

Circle 47 on reader service card

MAGAZINE FOR ELECTRONIC MUSIC USERS, Polyphony, is a quarterly periodical primarily directed toward the user of electronic musical equipment rather than toward the designer. About one-third of the material in each issue will be contributed by readers. The current issue of Polyphony will be sent free upon request. Subscription price is \$2.00 per year.—Polyphony, c/o PAIA Electronics, Inc., 1020 W. Wilshire Blvd., Oklahoma City, OK 73116. **R-E**

Circle 48 on reader service card

MDA...

Dedicated to the idea that "No disease is incurable... there are only diseases whose cures are yet to be found." Support the research programs of the **Muscular Dystrophy Association**

reader questions

LOSS OF VERTICAL SWEEP

I've got a black-and-white portable with no vertical sweep at all. I want to make a quick-check of the vertical output transformer and yoke. Can I use a separate 6.3 volt filament transformer to feed a signal into the output tube? This set has a series heater string.—J.G., Arlington, VA.

If you feed the test signal into the grid of the vertical output tube, OK. If you feed it directly to the plate, either disconnect the plate voltage or use a good-sized blocking capacitor (0.25 or 0.5 μ F.)

TOO MUCH RIPPLE IN PICTURE

I wrote you before about checking the excessive ripple in the picture of a Gambles TV2-3701 black-and-white TV. You suggested checking ripple on the power-supply filters. That was it! I had to add 80 μ F of extra capacitance to get rid of it! Works now. Thanks.—J.W., Hastings, MI.

Glad to hear I was right.

EXCESSIVE WIDTH

The raster in this Sylvania D05-14 is so wide that I can see only 8 vertical lines of a crosshatch pattern! All of the DC voltages seem to check out all right. I tried reducing the screen grid voltage of the horizontal output tube. That didn't work!—C.M., Diamond Bar, CA.

Well, there went one of my favorite ways of reducing excess width! So now what? In several cases this chassis has shown excessive width if that VDR from the pin-3 cathode of the 6CL8 high-voltage regulator tube to ground goes bad. This is part No. 38-15257-9. Replace with exact factory duplicate; couldn't find a listing on it. R-E

The Money Generator



GENERATES MONEY FOR YOU!

PAT PEND.

It's a DOG FIGHTER, TOO!

The Model ATC-10 is much more than a color bar pattern generator. It should be called a portable multi-purpose TV diagnostic and servicing aid, but that's too much of a mouthful. We would have nicknamed it the Dog Fighter (instead of the Money Generator), but that might be misinterpreted to mean that it's only useful in the shop. The versatile ATC-10, a portable, moderately-priced instrument, combines the most essential features of a color bar pattern generator, a TV analyzer, and a substitute tuner plus several brand new "dog fighting" and timesaving innovations. With all this extra versatility, however, the ATC-10 is human engineered with only four simple-to-master controls.

Two illustrated brochures describe the ATC-10. The first brochure describes the many unique and unusual features which make the ATC-10 a "dog fighter" and a time-saver. The second brochure illustrates the timesaving (money making) potential of the ATC-10 by comparing its capabilities with 18 competitive instruments. In all, 33 respective performance features are evaluated. We think the results of this evaluation will be a surprise to many. It clearly illustrates how costly it is for most TV service shops to purchase or continue to use less versatile equipment and shows how the ATC-10 has the potential of returning its \$299.95 purchase price in as little as 3 to 4 months.

These brochures are yours for the asking — write direct for immediate reply.

American Technology Corporation

225 Main, Dept. 5C, Canon City, CO 81212

MARKET SCOOP COLUMN

- HIGH VOLTAGE POWER TRANSISTOR Equip. HEI 707
List price \$16.00 2²⁹
- ZENITH 19 D20 2⁰⁰
- AMPLIFIER PART #121-743 1⁰⁰
- 2-SILICON NPN TRANSISTOR HEI-S0015 List \$1.75
- 1-SILICON NPN TRANSISTOR (SK3334-HEI-S0004) 1⁰⁰
- 1N4757A 1 Watt -50 V 1⁰⁰
- 4-ASSTD. PHILCO SWITCHES -PUSH TYPE #TY2-3-4, & Sig. Sw. With knobs latest type 2⁵⁹
- POWER TRANSFORMER (1P7-18) 110V Pri., -12V Sec. Used in many transistor Power SUPPLIES 2²⁹
- COMPLETE CONVERGENCE ASSY.—Inc. Yoke, Board & Plug Conn. Adaptable to most 90° sets 3⁹⁵
- COLOR DELAY LINE—Used in most color sets 1⁸⁹
- Silicon NPN HV TRANSISTOR ICA-SK-3021—Hep-240 1⁰⁰
- ICA-SK-3026—Hep-241 Transistor Specials—Your Choice SK3006, SK3018, SK3020 SK3122, SK3124 1⁰⁰
- Transistor Specials—Your Choice SK3009, SK3024, SK3040 1⁹⁸
- WAHL-CORDESS SOLDER IRON Complete with Auto Charger, Fast Heating, Compact 17⁹⁵
- 5—Audio Output TRANSFORM Sub-min for Trans Radios 1⁰⁰
- 5—I.F. Coil TRANSFORMERS 456-ke for Transistor Radios 1⁰⁰
- 8" UNIVERSAL SPEAKER Top quality Special Buy EA.
- 10"—UNIVERSAL SPEAKER Large Magnet—Top quality 4⁹⁵
- 8" UNIVERSAL SPEAKER Large Magnet—Special Buy 2⁹⁹
- 2 1/2"x4" SPEAKER 69[¢]
- 4"x6" "QUAM" 16 OHM SPK. Large magnet Special BUY (10 for \$10) 1⁷⁹
- 8" HEAVY DUTY 10 OZ. SPEAKER Ceramic Type—8 Ohm 4⁵⁰
- 1—6"x9" Heavy Duty 10 oz. Speaker Ceramic Type 4⁵⁰
- 3—ELECTROLYTIC CONDENSERS—100/80/20 MFD—500 Volts 2⁰⁰
- 6—Top Brand Silicon RECT. 1 amp., 1000 PIV 1⁰⁰

- RCA 110° FLYBACK TRANSFORMER, For Blk. & Wht. sets —18KV—For all types TV's, Inc. schem. 4⁹⁵
- 110° TV DEFECTION YOKE for all types TV's incl schematic 4⁹⁵
- "COMBINATION SPECIAL" #95 RCA 110° FLYBACK plus 110° DEFECTION YOKE 6⁹⁵
- 90° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.) 2⁹⁵
- 70° FLYBACK TRANSFORMER for all type TV's (Blk. & Wht.) 2⁰⁰
- 70° TV DEFECTION YOKE for all type TV's (Blk. & Wht.) 2⁰⁰
- OLYMPIC & SHARP FLYBACK Part #8T592 Equip. Stancor #110-408—Thorlaxson #29335 2⁰⁰
- 90° COLOR YOKE For all Rectangular 19 to 25" Color CRT's 7⁹⁵
- 70 COLOR YOKE For all round color CRT's 5³⁵
- DELMONICO NIVICO COLOR FLYBACK Part #A20411-B 7⁹⁵
- WESTINGHOUSE FM TUNER #476-V-015D9 1 Transistor (121018 Tube) 3⁹⁹
- WESTINGHOUSE FM TUNER UHF TUNER—Transistor Type Used in all TV sets 2⁹⁵
- G.E. UHF TUNER—TRANSISTOR TYPE Model #85X1 3⁹⁵
- ADMIRAL TV TUNER Model #94C393-1 (2HA5-4LJ8) Model #T94C411-2 (Transistor) 7⁹⁵
- WELLS GARDNER TUNER Part #7A 120-1 (AGST-2HA7 Tubes) 7⁹⁵
- G.E.—TV TUNER (2GK5-4LJ8) Model #EP 8611 9⁹⁵
- PHILCO UHF/VHF TUNER Transistorized 2⁰⁰
- 100° GREY SPEAKER WIRE 2 Cond., mini zip, 101 uses 2⁹⁹
- UNIVERSAL TV Antenna Back of set mounting 5 section rods 1⁷⁹
- BLUE LATERAL Magnet Assy. Replacement for most color TV's 1⁰⁰
- 5-10K-2 WATT BIAS POTS Used in solid state application 1⁰⁰
- COLOR CONVERGENCE ASSY. Universal type—good for most sets 2⁴⁹
- 3 SPEAKER—W WAY SELECTOR SWITCH—Wall Mount 1⁰⁰
- 7 TUBE AM-FM STEREO AMPLIFIER CHASSIS. Completely assembled—with tubes AS IS needs slight adjustments 12⁹⁵
- 10—MINI ELECTROLYTIC Cond For Transistor miniture work 1⁰⁰

- SOLID STATE STEREO DISCO MIXER Features talkover—Qing both channels—slide control 139⁹⁵
- SPECIAL PRICE 139⁹⁵
- HIGH VOLTAGE POWER TRANSISTOR Equip. HEI 707 2²⁹
- List price \$16.00
- 1—VARCO STEREO CARTRIDGE Model TYS-1B with holder 2⁹⁵
- 2—ELECTROLYTIC CONDENSERS 80/100/60 MFD—160V 1⁰⁰
- 2—ELECTROLYTIC COND 200/30/4—mfd—350V 1⁰⁰
- 3—ELECTROLYTIC COND 100 mfd.—100V, 50 mfd.—75V 1⁰⁰
- 2—ELECTROLYTIC COND 40 mfd.—500V, 40 mfd.—400V 1⁰⁰
- 8—MINI PILOT BULBS With 8" Leads—6.3V 30MA (5000 Hrs) 1⁰⁰
- 8—MINI PILOT BULBS With 12" Leads—6.3V, 150MA (5000 Hrs.) 1⁰⁰
- 32—TEST PROD WIRE DELUXE QUALITY red & black 1⁰⁰
- 1—COLOR POWER TRANSFORMER RCA 26R150 special 6⁹⁵
- 2—Crestburst Quartz-Crystal For most color TV sets 3579.545 KC 1⁸⁹
- 5 ASST GLOBAL VARISTOR Popular replacements for most COLOR TV 1⁰⁰
- COLOR-TV RECTIFIER—1 set In most color sets—6500 kv 3 for 1⁹⁵
- 4—TV ALIGNMENT TOOLS most useful assortment #1 1⁰⁰
- 4—TV ALIGNMENT TOOLS For Color TV #2 1⁴⁹
- 6—TV COLOR ALIGNMENT TOOLS Most popular type 2⁷⁹
- TV TWIN LEAD-IN 300 ohm 500'—\$7 100'—\$1.50, 50' 1⁰⁰
- CO-AX CABLE RG59U (Black) 250'—\$10, 100'—\$4.50, 50' 2⁶⁹
- 5—DUAL DIODE—MOST POPULAR TYPES Common cathode or Series connected 2⁵⁰
- 15—DIPPED MYLAR CAP. .01—600V 1⁰⁰
- 15—DIPPED MYLAR CAP. .033—600V 1⁰⁰
- 15—DIPPED MYLAR CAP. .033—1000V 1⁰⁰
- 15—DIPPED MYLAR CAP. .047—400V 1⁰⁰
- 15—Molded Tubular Capacitors .056—400V 1⁰⁰
- 15—DIPPED MYLAR Condensers 1.0039 400V 1⁰⁰

Test Equip. Special Discount Prices

- BK** **TEICO** **Leader** **SENCDRE**
- TRANSISTOR RADIO asst type good, bad, broken, as-is, potluck 1⁵⁰
- TAPE RECORDER assorted types good, bad broken, as-is, potluck 4⁰⁰
- 200 ASST. 1/2 WATT RESISTORS Top Brands, Short Leads, Excellent Selection 1⁰⁰
- 75—ASST 1/4 WATT RESISTORS stand, choice ohmages, some in 5% 1⁰⁰
- 100—ASST 1/2 WATT RESISTORS stand, choice ohmages, some in 5% 1⁰⁰
- 70—ASST 1 WATT RESISTORS stand, choice ohmages, some in 5% 1⁰⁰
- 35—ASST 2 WATT RESISTORS stand, choice ohmages, some in 5% 1⁰⁰
- 50—PRECISION RESISTORS asst. list-price \$50 less 98% 1⁰⁰
- 20—ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt 1⁰⁰
- 250—ASST SOLDERING LUGS best types and sizes 1⁰⁰
- 250—ASST WOOD SCREWS finest popular selection 1⁰⁰
- 250—Asst Self Tapping SCREWS #6, #8, etc. 1⁰⁰
- 100—ASST 6/32 SCREWS and 100—6/32 HEX NUTS 1⁰⁰
- 100—ASST 8/32 SCREWS and 100—8/32 HEX NUTS 1⁰⁰
- 100—ASST 2/56 SCREWS and 100—2/56 HEX NUTS 1⁰⁰
- 100—ASST 4/40 SCREWS and 100—4/40 HEX NUTS 1⁰⁰
- 100—ASST 5/40 SCREWS and 100—5/40 HEX NUTS 1⁰⁰
- 500—ASSORTED RIVETS most useful selected sizes 1⁰⁰
- 100—ASST RUBBER BUMBERS for cabinet bottoms—other uses 1⁰⁰
- 100—ASST RUBBER GROMMETS best sizes 1⁰⁰
- 1—KENWOOD TWEETER Special Buy—4" Round 4⁷⁹

IMMEDIATE DELIVERY Scientific light packing for safe delivery at minimum cost. HANDY WAY TO ORDER Send check or money order, add extra for shipping. Lists of new offers will be returned in your order. Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 529 Columbus Ave., New York, N.Y. 10024 TELEPHONE 212-874 5600

Circle 85 on reader service card

FUNCTION GENERATORS

(continued from page 42)

will decrease in output amplitude by as much as -2 dB when changed from the lowest to highest frequency. This -2 dB roll-off is due to filtering circuits used in the output amplifier to eliminate high-frequency discontinuities present in the synthesized sine wave.

Amplitude symmetry (DC offset)

As noted before, lack of time symmetry can cause an apparent DC offset in the output signal. The output signal may also have DC offset contributed by lack of symmetry in the limit detectors, and DC offset contributed by amplifying stages elsewhere in the generator. Amplitude symmetry is usually specified as a percentage match between the peak positive and negative amplitudes of a wave.

Output specifications

The output impedance, the maximum peak-to-peak output voltage, and the clipping level of the output voltage are all of interest to the potential user. The common output impedance of a function generator is 50 ohms. This value is chosen to permit driving low-impedance loads and to minimize reflections on the 50-ohm coaxial cables commonly used to connect the generator to a load. This is especially important when fast rise time square waves are used. Some lower-cost generators have sacrificed 50-ohm output impedance

to reduce their price. These generators specify the 600-ohm output impedance common in the older sine/square oscillators.

The peak-to-peak output voltage of the generator is specified into the rated load impedance as well as into an open circuit. The open circuit voltage will be twice that of the loaded output voltage when the output impedance of the generator is the same as the rated load impedance. A common value of peak-to-peak output voltage is 10 volts minimum into the rated load. The value varies from manufacturer to manufacturer, and sometimes from model to model, and should be clearly noted when purchasing a function generator.

Frequently the sum of the peak output signal and the variable DC offset signal will exceed the peak limits of the output amplifier. When this condition occurs, the desired waveform may be clipped or otherwise distorted. Limit detectors are offered on some models of function generators, and a rare few offer an output amplifier with enough dynamic range to handle both the signal and the DC offset signal. The vast majority of function generator manufacturers expect the user to keep track of this condition.

Offset control

The offset control permits a variable amplitude/variable polarity DC bias to be applied to the output signal. This is usually a ± 5 volt offset signal. Generally, offset signals will not be attenuated with an increase in attenuation of the variable attenuator, but will be attenuated by the

step attenuator. On some generators, offset may not be turned off, and some generators have switched position allowing the user to return to a signal symmetrical about zero volts. Offset is not available on all generators and is frequently deleted from low-cost units.

Attenuator

The amount of attenuation and the type of attenuators vary considerably from generator to generator as well as from manufacturer to manufacturer. The simplest attenuators are nothing more than a single variable control, offering as little as 20-dB attenuation and a maximum of 40 to 60 dB. Other function generators combine a variable control with 20-dB range with a step attenuator offering 10 or 20 dB per step. Step attenuations vary from one 20-dB section to six or seven 10-dB sections. Of course, the more attenuation sections available, the better. The maximum output voltage is usually known only to be greater than some specified value (say 10 volts) but not to be an exact voltage. For this reason, most attenuators are calibrated in decibels of attenuation rather than in voltage steps. The user interested in the exact signal voltage at the load should measure it separately.

Often the variable attenuator may appear to give more total attenuation than specified by the manufacturer. Use of the function generator at greater than specified attenuation levels may result in an output waveform with excessive distortion, resulting from high-frequency signals

(continued on page 92)

FOR COMPLETE MEASURING CONFIDENCE

A NEW STANDARD IS BORN

High accuracy you can trust
Versatile measuring capabilities
An efficient, easy to operate meter
All at an affordable price
That's the DVM38 . . . The complete DVM that sets new performance standards in 4 key areas.

A NEW ACCURACY STANDARD

The 3 1/2 digit, .1% accuracy is backed by a 15 meg Ω input impedance, compared to 10 meg Ω input of conventional DVM's, which guarantees up to 50% greater accuracy with 1/3 less circuit loading on every measurement for high accuracy you can trust.

A STANDARD IN CAPABILITIES

The DVM38 is more accurate in MORE circuits with these versatile ranges: 100 μ V to 2000V DC, 1KV AC; .01 Ω to 20 meg Ω ; 0.1 μ A to 2A . . . Plus

HI and LO ohms and a 50KVDC range with accessory Hv probe.

A NEW STANDARD IN SPEED AND EASE OF OPERATION

Large pushbuttons and callouts - no need to hunt and peck. Large 4" L.E.D.'s with direct readout, down to V and mV indicators. SINGLE STEP AUTO-RANGING for maximum resolution and efficiency. 2KV DC protection minimizes downtime.

THE AFFORDABLE STANDARD

There are few .1% DVM's less expensive - there are none as complete in this price range, plus backed by a LIFETIME guarantee against factory workmanship errors.

THE DVM38 A NEW STANDARD IN DVM'S FOR SPEED, VERSATILITY AND ACCURACY.

DVM38 BACKED BY SENCORE'S 100% MADE RIGHT LIFETIME GUARANTEE
SENCORE 3200 Sencore Drive, Sioux Falls, S.D. 57107
Phone: 1 605-339 0100 TWX 910-660-0300

Circle 86 on reader service card

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$.89
- Kleps 20.** Same, but 7" long. \$1.49
- Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.79
- Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. \$2.59
- Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$.99

All in red or black - specify. (Add 50¢ postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.
127 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.
Circle 87 on reader service card

next month

JUNE 1976

■ Build Super-Pong & Bumper

Two TV games that are fun to build and exciting to play. They connect into the video circuits of your TV set. IC circuitry. Complete plans and instructions start in this issue.

■ Video Discs & Tape

They are still just a little further down the road as far as in-home devices go; but they'll be here soon. Here's a report on where they stand today.

■ Ball Lightning And How To Make It

You build a giant Tesla generator, of course, out in the desert and then. . . . But you'll have to read about this one for yourself. By the way have you ever seen 5- and 10-foot long electrical discharges?

■ Hi-Fi Test Gear

A fresh look at test equipment for hi-fi gear. See the equipment and how it is used.

PLUS

Lab Tested Hi-Fi Equipment Tests

More On Building The 8080
Microcomputer

Jack Darr's Service Clinic

If You Work In Electronics:

GRANTHAM OFFERS YOU College-Level Training and a college degree.

Electronic Circuit Design, Engineering Analysis (including mathematics thru calculus), Classical and Solid-State Physics, Engineering Design, etc., etc., are all part of the Grantham home-study degree program in Electronics Engineering.

PUT PROFESSIONAL RECOGNITION IN YOUR CAREER.

By adding college-level home training and a college degree to your experience, you can *move up* to greater opportunities in electronics.

Grantham offers the A.S.E.T. degree by correspondence. After earning this degree, you may continue with additional correspondence plus a 3-day residential seminar and certain transfer credits, to earn the B.S.E.T. degree. Then, the B.S.E.E. is available through further study.

GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study

Mail the coupon below for free bulletin.

Grantham School of Engineering RE 5-76
2000 Stoner Ave., Los Angeles, CA 90025

I have been in electronics for _____ years. Please mail me your free bulletin which gives details concerning your electronics degree programs.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____


Circle 88 on reader service card





INTERNATIONAL FM 2400CH

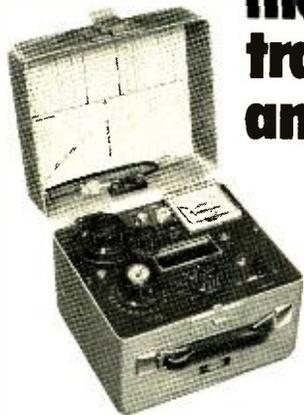FREQUENCY METER for testing mobile transmitters and receivers



- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz. The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: $\pm .0005\%$ from $+50^\circ$ to $+104^\circ\text{F}$.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^\circ$ to $+125^\circ$ (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only) \$595.00
 RF crystals (with temperature correction) 24.00 ea.
 RF crystals (less temperature correction) 18.00 ea.
 IF crystals catalog price



International Crystal Manufacturing Company, Inc.

10 North Lee, Oklahoma City, Oklahoma 73102

Circle 89 on reader service card

CHARTS & GRAPHS

(continued from page 62)

Log-log paper: Use for power functions—those involving "x" raised to a power, "n". This embraces all square-law equations, such as those connecting power and voltage or current. Example: $\text{Ln } P=I^2R$, I corresponds to "x", and "n" is 2. Plot I on the horizontal axis vs. P on the vertical axis. The plotted "curve" will then be a straight line.

Interestingly, log-log plots are also straight lines for reciprocal functions. Commonly-encountered reciprocal functions are the Ohm's law equations, $I=E/R$ and $R=E/I$. In the first equation, assume E is constant, then plot I on the vertical axis and R on the horizontal axis. In the second equation, assume E is constant, then plot R on the vertical axis and I on the horizontal axis.

Another reciprocal function is the equation connecting capacitive impedance or reactance, X_c , with capacitance, C, and frequency, f. This equation is $X_c = \frac{1}{2\pi fC}$. Plot X_c on

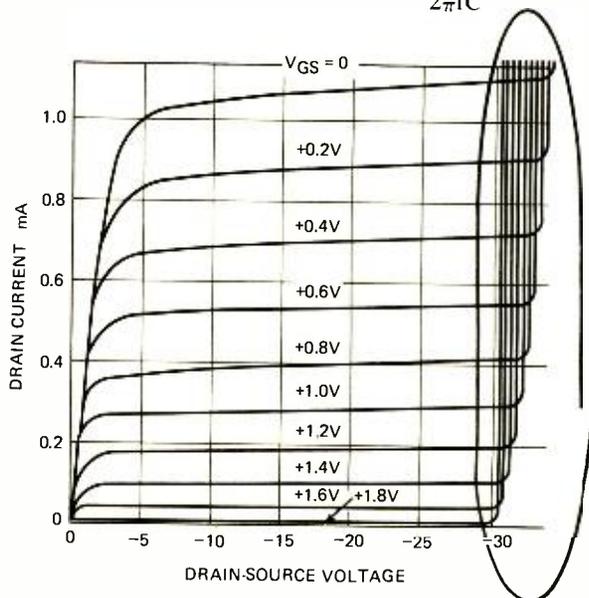


FIG. 10—CHARACTERISTIC CURVES of a typical junction FET. Circled portion is sometimes omitted.

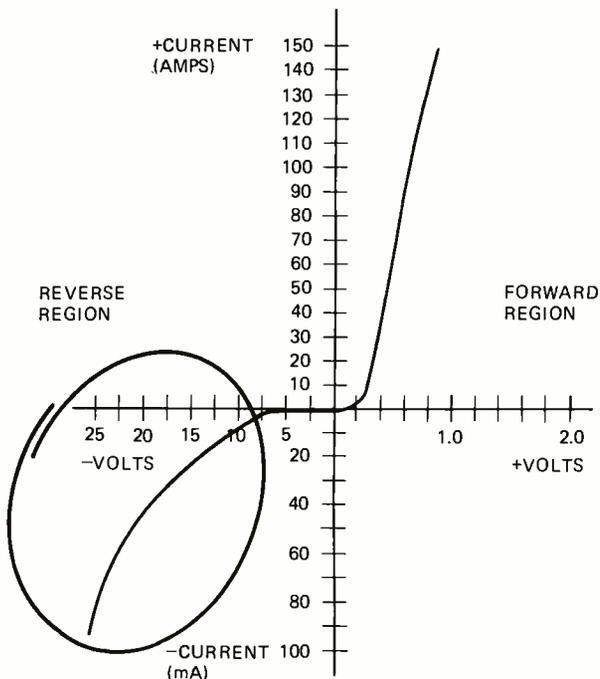


FIG. 11—BEHAVIOR of a Schottky diode. Circled portion is sometimes omitted.

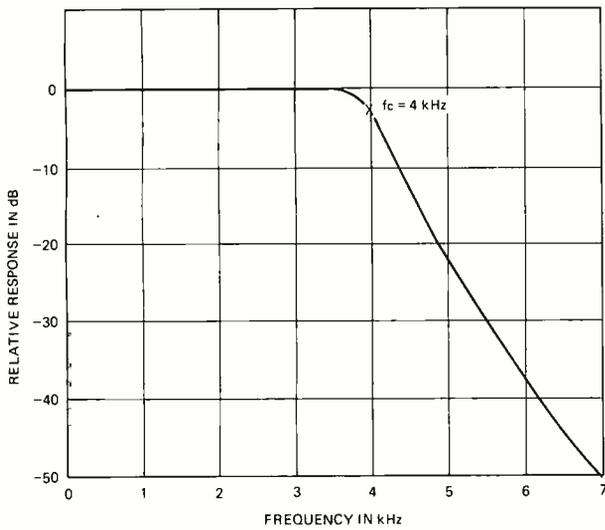


FIG. 12—RESPONSE of a 4-kHz low-pass filter plotted on conventional graph paper.

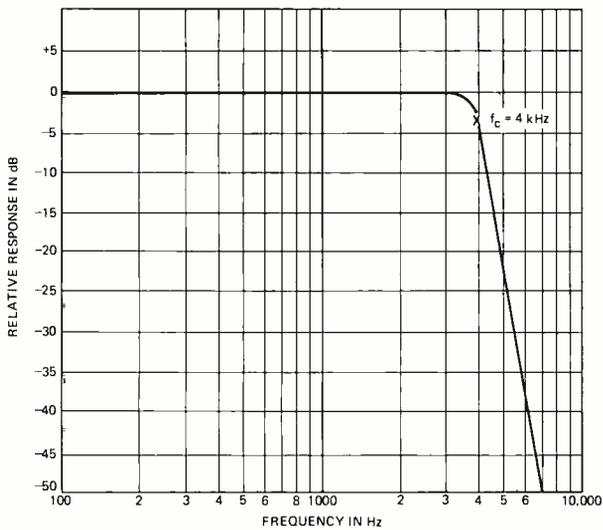


FIG. 13—SEMI-LOG GRAPH of response of same filter as in Fig. 12.


the vertical axis, and either f or C on the horizontal axis. (Actually, the reciprocal function is a power function in which the power of the exponent is -1 . Thus, another way of writing the equation for capacitive impedance is $X_c = (2\pi fC)^{-1}$.)

Some graphical entrapments stem from incompleteness. Because of sales department specmanship or engineering department laziness, the encircled portions of the graphs in Figs. 10 and 11 are sometimes absent. This can lead to dire application results. There is nothing to warn us of the limits of allowable drain-source voltage for the FET. And unless you had reason to suspect otherwise, the inordinately low reverse avalanche voltage of the Schottky rectifier could lead to fireworks.

Graphs depicting the frequency response of tuned circuits, filters and other devices are often deceiving. Consider, as an example, the two plots of the same 4 kHz low-pass filter shown in Figs. 12 and 13. Both display the same information with respect to the "skirt". Yet, the semi-log plot of Fig. 13 appears to show much greater selectivity than is revealed by Fig. 12. Heightening the illusion, we see that the passband is geometrically longer in the semi-log plot than in the conventional plot. And that is despite the fact that a log scale has the ability to compress range! A filter maker would be guilty of no chicanery at all by showing the performance of his filters on semi-log plots. He would simply be putting his best foot forward!

R-E

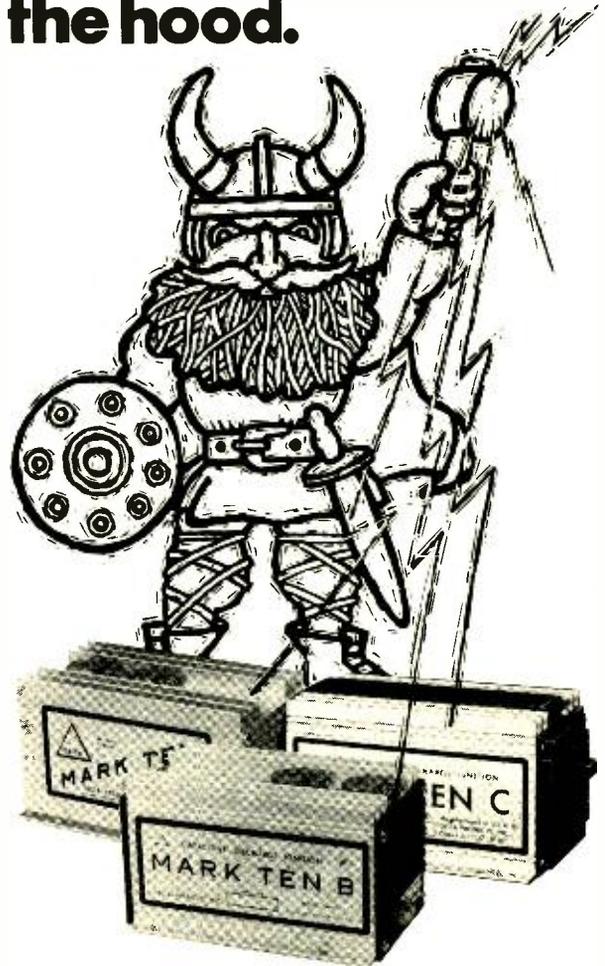Mark Ten Electronic Ignitions put lightning under the hood.



It's like having a bolt of lightning under the hood of your car when you feel it burst into action. And that's not all you'll feel with one of Delta's three HOT, HOT ignition systems. You'll feel the contentment of knowing your car will start INSTANTLY no matter how hot or cold the weather, the relief of fast, safe entry onto teaming freeways with POWERFUL ACCELERATION, and the satisfaction of pocketing all that money you'll save, not only from INCREASED GAS MILEAGE, but from all the TUNE-UPS you can forget about (at least 2 out of 3). And that's just for starters. Send today for free, color brochure jam-packed with helpful facts on how Delta's Mark Ten, Mark Ten B and Mark Ten C Capacitive Discharge Electronic Ignitions can help make driving a better experience for you.

I want to know more about Mark Ten DCI's. Send me complete non-sense information on how they can improve the performance of my car.

Name

Address

City State Zip



DELTA PRODUCTS, INC.

P.O. Box 1147, Grand Junction, Colo. 81501
(303) 242-9000 Dept. RE

Circle 90 on reader service card

The Great Time Saver!

SUPER FROST-AID FINDS INTERMITTENTS FAST!



Intermittents can eat up valuable servicing time, but not if you use Super Frost Aid. Just let the set "cook" for 20 minutes and then give each suspected component a blast of Super Frost-Aid. When you hit the problem part, the symptom will change dramatically.

Super Frost-Aid cools to -70° F, leaves no residue. Cools twice as many components per can. Is also great for locating PC board cracks. Try it, you'll never want to be without it.


CHEMTRONICS INCORPORATED
45 HOFFMAN AVE., HAUPPAUGE, N. Y. 11787 • (516) 582-3322

Our business is improving yours!
Circle 91 on reader service card

WE'RE ON TRIAL

But, you're the judge.

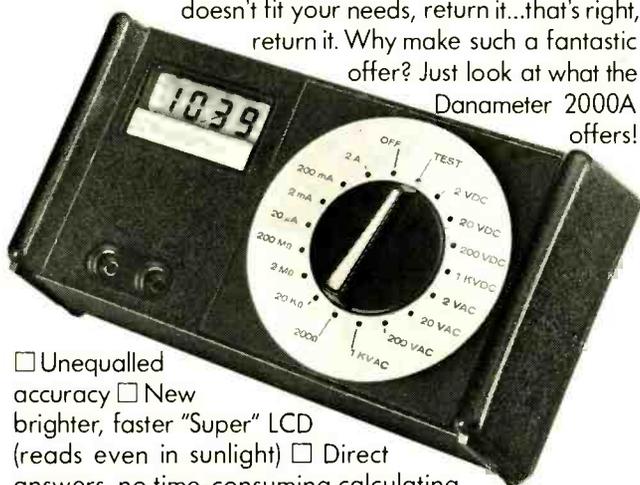To introduce you to Dana's quality tested Danameter® 2000A we're offering you a **thirty day free trial** period to use our DVM and judge its new reliable features. If it doesn't fit your needs, return it...that's right, return it. Why make such a fantastic offer? Just look at what the Danameter 2000A offers!



- Unequaled accuracy
 - New brighter, faster "Super" LCD (reads even in sunlight)
 - Direct answers, no time-consuming calculating
 - 1 full year battery life
 - LSI-CMOS circuitry
- And best of all...it costs only \$199.50!

Send for more details now...put us on trial. The new Danameter 2000A will come out ahead! For immediate action, call Cliff Hamilton at 714/833-1234.

DANA
Others measure by us.

Circle 92 on reader service card

FUNCTION GENERATORS

(continued from page 88)

that capacitively bypass the attenuator and add to the desired signal.

Trigger output

A second output is frequently found on the function generator. This output is a square wave or a spike of a fixed level. The trigger signal is related to the leading edge of the square wave at the main output. This signal may be used to trigger such external devices as an oscilloscope, for example, in situations where the main output signal is attenuated below the point that would allow it to be used for this purpose. Often these trigger outputs are not 50-ohm amplifiers but are TTL outputs. Therefore, the user must remember that the waveform may not pass through zero volts, and may be of variable source impedance.

Other features

On the more exotic generators, features such as remote programmability, digital display of frequency, logarithmic frequency sweep, amplitude modulation, and variable symmetry control may be had, to mention a few of the more popular options. Most of these features will not be found on the low-cost function generators for a few years to come. Generators employing these features must be considered more than simple replacements for the sine/square oscillator. **R-E**

Have a heart.

Some say we're becoming a nation of mannequins. Nothing but heartless, mindless clothes racks, no longer caring about, or for, each others' needs.

Blind to the suffering of the sick and the old. Deaf to the pleas of the disadvantaged.

If that's true, then pity us. Because it's not so much those of us who need help who are the handicapped. It's those of us who won't give it.

Have a heart. Write Volunteer, Washington, D.C. 20013. There's a very human need for whatever you can do.



Volunteer.
It'll make you a better human being.

A Public Service of The National 4 The Red Cross

For faster service

USE ZIP CODE

on all mail


VISTA DIGITAL CROSSHATCH

Gives professional, accurate Color T.V. convergence. Digital IC's coupled with a crystal time-base oscillator provide precise horizontal & vertical lines at broadcast frequencies. Accurate 8 x 7 dot or crosshatch pattern A.C. power 2 x 3 3/4 x 6 in. Wt. 24 oz. Fits in tool kit.

COMES COMPLETE WITH ALL PARTS, CASE, CRYSTAL AND GUIDE TO ASSEMBLY & USE.

KIT
\$31.95

COMPLETELY ASSEMBLED
\$41.95

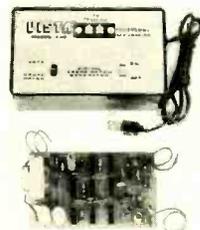

Shipping Prepaid in USA
NY State Add Sales Tax

PHOTOLUME CORP.
118 EAST 28 STREET
NEW YORK, N.Y. 10016

Circle 93 on reader service card

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.40 per word . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 85¢ per word . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

NOTICE TO MAIL ORDER BUYERS

Under a new Trade Regulation Rule of the FTC that became effective February 2, 1976, mail-order merchants are required to make deliveries within a reasonable time, notify the customer if his order has to be delayed, and return his money if requested.

The rule provides that if a mail-order seller is unable to ship merchandise within the time specified in his ad (or if no time is specified, within 30 days) he must notify the buyer of the delay and give him the option of cancelling the order and having his purchase money refunded.

The buyer must be provided with a cost-free device for this purpose such as a postpaid postcard or return envelope. If the buyer does not respond, it will be assumed that he has consented to an additional 30-day delay. For any longer delay, the customer's

express consent must be gained; otherwise the money is to be refunded.

The rule also makes provision for indefinite delays if agreed to by the customer; though a refund must be made, if requested any time during the delay. It also requires sellers of mail-order merchandise to have a reasonable basis for any claims they make about shipping time.

Penalties are severe. The FCC can go to court to get an order for compliance by a company or they could have a company fined up to \$10,000 for each day of non-compliance.

The rule *does not apply* to COD orders.

If you have a documented complaint send it to: Federal Trade Commission, Bureau of Consumer Protection, Washington, DC 20580.

BUSINESS OPPORTUNITIES

OWN YOUR OWN PICTURE TUBE REBUILDING BUSINESS

With Lakeside Industries re-building equipment you can rebuild any picture tube!

For complete details send name, address, zip code to
LAKESIDE INDUSTRIES
3520 W. Fullerton Ave.
Chicago, Ill. 60647
Phone: 312-342-3399



HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do. Barta-BE, Box 248, Walnut Creek, CA 94597.

EDUCATION & INSTRUCTION

ELECTRONICS DESIGN NEWSLETTER

★ Logic Design Techniques
★ Digital & Linear Design Theory & Procedures
★ Construction Projects

Learn Design Techniques!

Write for FREE CATALOG of parts & kits

Subscription \$6 Sample Copy \$1

VALLEY WEST Box 2119-L Sunnyvale, CA 94087

FCC License Study Guide. New, 377 pages. Includes 1465 FCC-type questions, with answers and discussions, covering third, second, and first class radiotelephone exams. \$8.95 postpaid. **GSE PUBLICATIONS**, 2000 Stoner Ave., Los Angeles, CA 90025

FREE educational electronics catalog. Home study courses. Write to: **EDUKITS WORKSHOP**, Dept. 278G, Hewlett, NY 11557

INTRODUCING The MICRO-ALTAIR



The complete Computer System that requires just a keyboard and TV monitor for use.

The MICRO-ALTAIR is:

The hardware — video terminal interface board, CPU/ROM/ RAM board, backplane, power supply and cabinet.

The software — video driver, debugger, operating kernel, supplied on ROM.

The personal computer system — complete, expandable, no loose ends — a complete and powerful tool.

THE SOLUTION BOX FROM POLYMORPHIC SYSTEMS.

Applications include smart terminals, data acquisition systems, games, accounting, front-end for a larger computer-anywhere a little processing is required.

COMPLETE SYSTEM (EXCEPT FOR MONITOR AND ASCII KEYBOARD) \$575.00 KIT. DELIVERY 60 DAYS — SERIAL I/O AND CASSETTE OPTIONS AVAILABLE.



Go to your local computer store and compare

Video Terminal Interface — characters are stored in on-board memory. Entire screen may be read or written in 20 milliseconds. Software includes a text editing system with scrolling and insert and delete by character or line.

VTI/32	32 character line	\$160 00 kit	\$230 00 assembled
VTI/64	64 character line	\$185 00 kit	\$260 00 assembled
VTI/SK	Socket kit for VTI kit	\$ 15 00	

Delivery — 30 days

Analog Interface — 1 or 2 channels of analog output with 10 bits of resolutions 0-10V or -5V with bipolar option. 6 bits of latched digital output and 8 analog comparators for software controlled A/D conversions.

ADA/1	1 analog output	\$135 00 kit	\$175 00 assembled
ADA/2	2 analog outputs	\$185 00 kit	\$235 00 assembled
ADA/SK	Socket kit for ADA kit	\$ 10 00	

Delivery — 30 days

All prices and specifications subject to change without notice. Prices are USA only. Calif. residents add 6% sales tax. Add 5% shipping, handling, and insurance.

POLYMORPHIC SYSTEMS

737 S. Kelllogg, Goleta, CA 93017 (805) 967-2351

BankAmericard and Master Charge Accepted

Circle 99 on reader service card

BURGLAR/fire alarm experts needed for cars, homes, industry. Learn high profit systems installation at home spare time. Simple, quick, complete. Free information by mail. No salesman. **SECURITY SYSTEMS MANAGEMENT SCHOOL**, (homestudy), Dept. 7339-056, Little Falls, NJ 07424

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—Tests Answers for FCC 1st and 2nd class Radio-telephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money-back guarantee.



COMMAND PRODUCTIONS P.O. BOX 26348 E
RADIO ENGINEERING DIV SAN FRANCISCO, CAL 94126

PASS FCC examinations! New question-answer book covers First-Third licenses. Proven method, guaranteed. \$7.00. **EXAMS**, Box 5516-FD, Walnut Creek, CA 94596

EDUCATIONAL electronic kits. Electronic games. From \$7.75. Send stamp. **NBL-R**, Box 1115, Richardson, TX 75080

BE A BURGLAR/FIRE ALARM EXPERT



Learn at home how to install burglar/fire alarm systems in cars, homes, businesses. Big money. Growing demand with increased crime, violence, car thefts, arson. Nationally accredited course. Simple, clear, hands-on training, tools furnished. FREE facts by mail. No salesman. Write **SECURITY SYSTEMS MANAGEMENT SCHOOL**, Div. Tech. Home Study Schools, Dept. 7479-056 Little Falls, NJ 07424.

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 260415

MANUALS for Govt. surplus radios, test sets, scopes. List 50¢ (coin). **BOOKS**, 7218 Roanne Drive, Washington, DC 20021

FOR SALE

RECONDITIONED test equipment. \$0.50 for catalog. **WALTER'S TEST EQUIPMENT**, 2697 Nickle, San Pablo, CA 94806

DEMA ELECTRONICS INTERNATIONAL ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

MONTHLY SPECIALS			
1101	1.49	555 Timer	55
1103	2.95	566 Dual Timer	85
5260	1.49	565 Ph. Lk. Loop	1.35
5261	1.69	566 Func. Gen	1.35
5262	2.95	567 Tone Dnc. Ph.	1.45
2102	1.95	Lk. Loop	1.45
7400 TTL			
7400	1.14	7445	85
7456	35	7446	85
7407	35	7447	75
7412	55	7448	75
7417	39	7451	19
7420	17	7453	19
7421	31	7464	35
7423	31	7465	35
7438	35	7474	35
7439	41	7475	59
7441	106	7480	65
7442	80	7483	75
7444	93	7485	108
7490	59	7490	59
7495	79	7495	79
74100	1.25	74100	1.25
74105	1.50	74105	1.50
74166	1.50	74166	1.50
74170	2.40	74170	2.40
74181	3.00	74181	3.00
74184	2.19	74184	2.19
74185	2.19	74185	2.19
74190	1.30	74190	1.30
74196	1.29	74196	1.29
74198	1.80	74198	1.80
74199	1.80	74199	1.80
74200	5.60	74200	5.60
CMOS			
4000	26	4010	59
4001	26	4011	59
4002	26	4012	26
4006	1.45	4013	49
4009	26	4014	1.54
4008	1.89	4015	1.50
4009	60	4016	56
4017	1.24	4024	90
4018	1.55	4025	26
4027	65	4027	65
4028	99	4028	99
4035	1.35	4035	1.35
4066	96	4066	96
4068	38	4068	38
LINEAR IC'S			
LM300	80	LM340K	1.80
LM301	45	LM340T	1.55
LM302	85	LM370	1.15
LM304	90	LM380	96
LM307	30	LM390	1.95
LM308	90	LM381	1.57
LM309K	1.25	LM382	1.65
LM310	1.13	A709	32
LM311	95	A710	45
LM319	1.24	A723	65
LM320K	1.30	A739	1.10
LM324	1.54	A741	1.55
LM339	1.60	A747	69
A748	40	A748	40
555	2.95	555	2.95
556	2.95	556	2.95
557	2.95	557	2.95
738	2.95	738	2.95
739	2.9		

NEW CLOCK KITS!



MODEL OC1032


JUMBO DIGITS
ALARM CLOCK
1.2" Bright Yellow
Color Readouts

Features: 12/24 Hour Display, 24 Hour Alarm Set, 10 Min Snooze Switch, AM/PM Indicator
Kit Includes: Woodlike Color Plastic Case, 4 Digit 1.2" Neon Display with AM/PM, TMS 3834 Alarm Chip, 2 pcs. double sided PC Boards, 16 transistors, all other components, Transformer and speaker

SPECIAL \$35.90

THE MOST POPULAR

MM5314 KIT

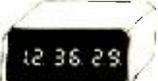

WITH A NEW CASE!!

Features: 12/24 Hour Display
50/60 HZ Input 6 Digits Readout

Kit Includes: Grey Color Plastic Case MM5314 Clock Chip PC Boards and Transformer, 6 Green Color 0.4" Tube Readouts, All other transistor Drivers and other Components.

Special Only \$19.95 ea.



MODEL OC1030

4 DIGIT
ALARM CLOCK KIT
0.5" Green Color
Readouts

Features: 12/24 Hour Displays, 24 Hour Alarm Set, 10 Min Snooze Switch, AM/PM Display.
Kit Includes: Orange Color Plastic Case, 0.5" LO8132 Green Color Readouts PC boards with transformer, all electronic parts with speaker.

Only \$28.50




MODEL CT7001

WITH ALARM
MONTH AND DATE

CLOCK KIT
use 0.5" LED Displays

without case **Only \$28.50 ea.**

CT Case \$7.50 Additional

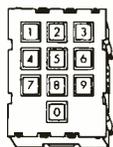

TOUCH TONE KEYBOARD

no electronic parts
10 key switches only

LIMITED QUANTITY
Only \$4.50 ea.


* * NEW ITEMS * *

National MM5330 4 1/2 digits DVM chip \$12.50 ea.
Character Generator TI TMS2501 Static USASCII 64 x 5 x 7 \$8.50 ea.
Motorola MC 1733 Video Amp. I.C. \$1.20 ea.
Monsanto MAN5491 Bipolar Led Orange or Green .50 ea.
LM 566 Voltage Controlled Oscillator \$1.60 ea.
NE540 Power Driver \$2.20 ea.
8038 Intersil Function Generator \$6.00 ea.
MM5315 Stopwatch Clock Chip \$4.60 ea (MM5309)
MOS2521 Metric Converter Calculator Chip \$4.00 ea.
TIP32 PNP Power Transistor TO-220 Type 10 for \$5.00

ROCKWELL A4001 I.C.

ELECTRONIC SLIDE RULE SCIENTIFIC CALCULATOR KIT !!

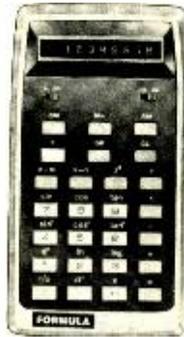Kit Includes: Rockwell A4001 IC
HP 9 Digit LED Readouts
Complete Keyboard with Case
PC Board with all Electronic Parts
Instructions and Batteries



Dimension: 32.5mm(H) x 77mm(W) 145mm (L)
1 9/32 in (H) x 3 1/32 in (W) x 5 23/32 in (L)

SPECIAL FUNCTION

- Trigonometric functions (sin, cos, tan)
- Inverse trigonometric functions (sin⁻¹, cos⁻¹, tan⁻¹)
- Radian or degree selectable
- π constant
- Logarithms (ln, log)
- Anti logarithms (e^x)
- Power functions (y^x)
- Reciprocal (1/x)
- Square root (\sqrt{x})
- Display recall

SPECIFICATION

- 9 digit HP Red Led Displays
- 8 digits capacity for data entry or results
- (10⁸ ~ 10⁸)
- Full floating point
- Dome keyboard for excellent response and preventing double entry input

BASIC FUNCTION

- Algebraic mode operation
- Constant operations
- Repeat Operations
- Chain operations
- Change sign operation
- Display and Y register exchangeable
- One accumulating memory
- Display and memory exchangeable

AC adapter for the unit
\$4.50 ea.
* postage \$1.50 per unit.

ONLY \$28.⁵⁰

LINEAR I.C.

LM 309K	5V 1A Regulator	1.00
LM 340T	Pos. 1A V. Regulator (5V, 6V, 12V, 15V.)	1.00
LM 380	2W Audio Amp	1.00
LM 381	Lo Noise Pre Amp	1.00
LM 555	Timer Mini Dip	.55
LM 556	Dual 555 Timer	.85
LM 565	Phase Locked Loop	1.50
LM 567	Tone Decoder	1.50
UA 709	Operational Amp	.20
UA 741	Comp Op Amp	.25
LM 747	Dual 741 Op Amp	.55
LM 1458	Dual Comp Op Amp	.55
LM 3900	Quad Op Amp	.50
DM 8864	9 Digit Led Driver	1.40
75492	HEX MOS to Led Digit Drivers	.60
75491	Quad Seg. Drivers	.60

BARGAINS OF THE MONTH!

MM5316 ALARM CLOCK KIT #401
Kit includes MM5316 chip, transistors, 4 green color displays, (0.25"), P.C. board, switches, transformer and all electronic parts. Speaker and Case not included.

ONLY \$16.50

ASSORTED TRANSISTOR BAG #402
Approx 300 pcs untested photo transistors. Photo Diodes, NPN, PNP, FET AC, also LED. Mixed. Only \$7.00

1 AMP RECTIFIERS BY FAIRCHILD #403
IN4001 - IN4007 Assorted, unmarked. Approx 300 pcs. Only \$7.00

MONSANTO MAN84 COMMON ANODE
Yellow Color 7 segment LED.
10 pcs for \$6.00

I.C. SOCKETS ASSORTMENT

16 Sockets includes
14 pins - 6 pcs, 16 pins - 6 pcs, For
24 pins - 2 pcs, 28 pins - 2 pcs. Only \$6.00

COMPUTER KEYBOARDS



Standard Teletype Keyboards with gold plated contact switches. All switches are independent and allow you to connect into any form of output. **Only \$22.50**

MODEL B (RCA) only \$35.50

Full ASCII Decoded output with electronic parts and specially designed Die-Cast case

PLASMA GAS DISCHARGE JUMBO 1.2 READOUTS DISPLAYS



Bright Orange Color for
Clocks, Supply Voltage
170V D.C.

4 1/4"

ONLY \$11.90 each.

Transformer for the above readouts \$1.00 ea.



7 SEGMENT LED

MONSANTO
0.4" Common Anode
Green or Yellow Color
only \$1.80 ea.
* * SPECIAL 10 for \$15.00

DL 707 0.3" Common Anode Red	\$1.30 ea.
DL 727 0.5" Common Anode Double Digits	\$2.80 ea.
DL 747 0.6" Common Anode Red	\$2.50 ea.
HP 0.3" Common Cathode Red	\$1.20 ea.
(BUY 10 for \$10.00)	
Fairchild FND 70 0.25" Common Cathode	.60 ea.
Fairchild FND 503 0.5" Common Cathode	1.60 ea.

TRANSFORMERS



12V AC 300 MA output Wall
Type Adapter (designed for
clock with limited space) \$2.50ea

12V-0-12V- or 24V 1 Amp out-
put \$2.25ea



0-0.8V-12V 300 MA output (for
our fluorescent tubes) \$2.50ea

18V 1 amp output \$2.50ea

0-3V-12V-24V 500MA output
(for CT 7001 Drive LD 8132 Readouts)
2.50 ea

0-15V-160V 150MA output
(for Gas discharge Readouts) 1.00 ea

MINIMUM ORDER \$10.00. California residents add 6% sales and 1.50 to cover postage and handling.

Out-of-state and overseas countries add \$2.50.

SEND CHECK OR MONEY ORDER TO:

FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 679-5162

STORE HOURS 10-7 Monday - Saturday

Circle 103 on reader service card

PRECISION, adjustable, solid-state power supply. ± 15 VDC at 1 1/2 amps, regulated simultaneously with 10 VDC at 3 amps unregulated, plus over 900 parts worth \$400.00, 120 transistors. Semiconductor characteristics, circuit diagrams included. New Cartridge VTR electronic units. \$19.95 plus \$1.50 shipping. 50¢ per brochure. **MADISON ELECTRONICS COMPANY, INC.**, P.O. Box 369, D101, Madison, AL 35758

MICRO "spy" microphones 1/4 x 3/16 in. apx. 5K ohms \$12.50. Many other micro parts available. Catalog 25¢. **MICRATEC, P.O.** Box 13257, Houston, TX 77019

PRINTED CIRCUIT
Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.
Send stamp & address label for flyer
TRUMBULL
833 Balra Dr., El Cerrito, CA 94530



MICRO MINI MIKE
WIRELESS MICROPHONE

World's smallest; solid state, completely self-contained. Picks up and transmits most sounds without wires up to 350 ft. through FM Radio. Use as mike, amp, alarm & alert sys., hot line, etc. Money back guar. B/A, M/C cds, COD ok. \$14.95 plus \$1.00 post. & hdlg. Calif. res. add tax. **AMC SALES, Dept. 19, Box 928 Downey, Ca. 90241.**

RECORDS-TAPES! Discounts to 73%; all labels; no purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main St., Dept. 3-56, New Rochelle, NY 10801

ALTAIR 8800 Plug-ins * 8K RAM kit**, static, exceptionally low power (extra low standby), fast no wait or refresh states, low price. *** **Prototyping Board**, massive heat sink, regulator *** **8800 Octal Encoder Board kit** no extra I/O board or software needed. *** **Microprocessor Coding Form Pads**. Send for latest information and * **Low Prices** * **ELECTRONIC CONTROL TECHNOLOGY**, Box 6, Union, NJ 07083

HIGHEST QUALITY PARTS
Fully Guaranteed

7400N TTL
SN 7400N SERIES

7400	.18	7438	.38	74151	1.05
7401	.18	7440	.20	74153	1.20
7402	.19	7442	.99	74154	1.35
7404	.19	7450	.22	74155	1.10
7405	.29	7473	.42	74157	1.10
7406	.35	7474	.42	74161	1.30
7408	.23	7475	.80	74163	1.50
7410	.18	7476	.49	74164	1.50
7416	.35	7483	.99	74174	1.50
7417	.40	7486	.42	74175	1.55
7418	.25	7490	.70	74176	1.10
7420	.20	7493	.85	74177	1.15
7425	.40	74107	.32	74180	.90
7427	.34	74121	.50	74191	1.40
7430	.24	74122	.47	74192	1.40
7432	.27	74123	.89	74194	1.30
7437	.43	74150	.99	74195	.90

CMOS
CD 4001 SERIES

4001	.25	4049	.65
4007	.25	4050	.65
4009	.59	74C00N	.39
4010	.59	74C02N	.55
4011	.25	74C04N	.75
4013	.47	74C10N	.65
4016	.56	74C20N	.65
4017	1.25	74C42N	2.15
4023	.25	74C74	1.15
4025	.25	74C107N	1.25
4029	1.30	74C161	3.25

LINEAR & MISC. IC'S

LM741CH	.28	INTEL-2102	3.00
LM723CH	.45	NE555B	.68
LM309K	1.50		

TRIM POTS (per our choice) 14/8.99
1 POLE 7 POS. MIN. SWT. 1.15

KITS **EXAR** **IC'S**

XR555CP	1.07	XR1310P	3.20
XR556CP	1.85	XR210	5.20
XR2240CP	4.80	XR215	6.60
XR205	8.40	XR567CP	1.75
XR100K	80.00		

POWER RECTIFIERS

VOLTS	1.5A	3A	10A	20A	30A
100	.09	.14	.30	.40	.56
200	1.00	.20	.35	.47	.80
400	1.11	.25	.50	.52	.98
600	.12	.30	.70	.91	1.20
800	.15	.35	.90	1.17	1.52
1000	.20	.45	1.10	1.43	1.90

NPN & PNP SIL. TRANSISTORS

2N2222 (TO-46)	.21 ea. or 5/1.98
2N3903	.20 ea. or 5/1.98
2N3904	.22 ea. or 5/1.98
2N3905	.20 ea. or 5/1.98
2N3906	.22 ea. or 5/1.98

ZENERS 1/2 W.

3V, 3.3V, 3.9V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 8.2V, 15V	.22 ea. or 5/1.99
---	-------------------

ZENERS 1W.

3.3V, 5.1V, 6.2V, 6.8V, 15V	.27 ea. or 4/1.99
-----------------------------	-------------------

G.P. SIL. DIODES

1N456	.13 ea. or 100/11.00
1N457	.14 ea. or 100/11.80
1N458	.15 ea. or 100/12.50
1N459	.16 ea. or 100/13.00

RECTIFIERS

1N4001	.08 ea. or 100/ 6.00
1N4002	.09 ea. or 100/ 7.00
1N4003	.10 ea. or 100/ 8.00
1N4004	.11 ea. or 100/ 9.00
1N4005	.12 ea. or 100/10.00
1N4006	.13 ea. or 100/11.00
1N4007	.15 ea. or 100/12.00

LED DISPLAYS
CC or CA red, green or yellow, small or large numbers — Small - \$1.79 Large - \$2.99

SWITCHING DIODES
(Special Price)

1N4148 35/1.00	1N914B 15/1.00
----------------	----------------

EM PAK SPECIAL
1N4001-4007 type. No shorts, no opens, all more than 50V. 60/1.98
NPN SIL TO-92 TRANSISTORS 20/1.00

NOTE: EM PAK products carry no guarantee and are unmarked. All other products are marked and fully guaranteed.

Min. Order — \$5.00. Please send check or money order with purchase order. Calif. residents add 6% sales tax. Write for large quantity prices.

ELECTRONIC MATERIALS CO.
Div. PC & B Industries, Inc.
1877 West Carson Street
Torrance, Ca. 90501
(213) 328-8532

QUALITY ELECTRONIC COMPONENTS
NEW DISCOUNT SCHEDULE SAVES YOU EVEN MORE!

AMD 8080A \$39.95 **2102 \$1.99**
MICROPROCESSOR 1024 Bit Random Access Memory
0-70°C 480 ns Clock Period 500 ns Typical, 1000 ns Max Access Time

INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400	.21	7413	.30	74174	.98	4001	.23	4073	.23
7401	.21	7414	.30	74175	.93	4002	.23	4075	.23
7402	.21	7405	.69	74176	.99	4006	1.23	4081	.62
7403	.21	7416	.32	74177	.79	4007	.23	4082	.23
7404	.21	7480	.70	74180	.70	4008	.79	4502	.79
7405	.21	7482	.70	74181	2.15	4009	.44	4510	1.14
7406	.25	7483	.70	74182	.79	4010	.44	4511	1.05
7407	.25	7485	.89	74184	2.19	4011	.23	4514	2.80
7408	.21	7486	.28	74185	2.19	4012	.23	4515	2.80
7409	.21	7489	2.19	74188	3.50	4013	.40	4516	1.23
7410	.21	7490	.44	74189	3.50	4014	.96	4518	1.14
7411	.21	7491	.70	74190	1.23	4015	.96	4520	1.14
7412	.21	7492	.44	74191	1.23	4016	.40	4527	1.46
7413	.25	7493	.44	74192	.88	4017	1.05	4528	.88
7414	.89	7494	.70	74193	.88	4018	1.05	4585	1.23
7416	.25	7495	.70	74194	.88	4019	.23	LM309K	1.80
7417	.25	7496	.70	74195	.88	4020	1.14	LM307N	1.28
7420	.21	74100	1.28	74196	.88	4021	1.14	LM340T-5	1.25
7421	.25	74107	.30	74197	.88	4022	.96	LM340T-6	1.25
7423	.35	74109	.33	74198	1.49	4023	.23	LM340T-8	1.25
7425	.35	74121	.33	74199	.89	4024	.84	LM340T-12	1.25
7426	.25	74122	.44	74201	1.09	4025	.23	LM340T-15	1.25
7427	.33	74123	.61	74219	.58	4026	1.68	LM340T-18	1.25
7428	.28	74125	.40	74265	.67	4027	.40	LM340T-24	1.25
7430	.21	74126	.70	74366	.67	4028	.89	LM3900N	.88
7432	.25	74132	.70	74367	.67	4029	1.14	NE536T	3.24
7433	.30	74141	.88	74368	.67	4030	.23	NE540L	2.04
7437	.25	74145	.70	74392	.88	4031	1.14	NE555V	.88
7438	.25	74147	1.63	74540	.88	4034	3.50	NE556A	.88
7440	.21	74148	1.30	74541	.61	4035	1.14	NE560B	3.83
7441	.88	74150	1.16	74542	.61	4036	1.14	NE561B	3.83
7442	.33	74151	.70	74543	.61	4041	.79	NE562B	3.83
7443	.63	74153	.65	74544	.61	4042	.79	NE565A	1.25
7444	.63	74154	1.03	74549	.81	4043	.70	NE566V	1.28
7445	.70	74155	.70	74592	.88	4044	.70	NE570V	1.36
7446	.70	74156	.70	75493	1.09	4046	1.86	uA709CV	.44
7447	.70	74157	.70	75494	1.19	4049	.40	uA710CA	.44
7448	.70	74160	.88	8093	.40	4050	.40	uA711CA	.53
7450	.21	74161	.88	8094	.67	4051	1.26	uA720CA	.60
7453	.21	74162	.88	8095	.67	4052	1.26	uA741CV	.44
7454	.21	74163	.88	8096	.67	4053	.72	uA747CA	.70
7460	.21	74164	.96	8097	.67	4060	1.58	uA748CV	.49
7470	.30	74166	1.28	8098	.67	4066	.79	MC1458V	53
7472	.30	74170	2.64	82525	2.19	4071	2.3	2102	2.65
7473	.30	74173	1.42	4000	.23	4072	.23	2102	49.95

AP SUPER STRIP II—Universal Breadboarding
Element with 840 Solderless Plug-In Tie-Points
\$17.00

IC TEST CLIPS
14 pin TC-14 \$4.50
16 pin TC-16 \$4.75
24 pin TC-24 \$13.85 TC-16 TC-24

In a hurry? Try these high-performance All-Circuit Evaluators

obsoletes ordinary breadboards All solderless plug-in tie-points

7 models for fast building and testing of circuits

On all models... simply plug in your components and interconnect with 22-gauge solid wire. All models accept all DIP's, TO-5's and discretes with leads up to .032" diameter.

Multiple buses can easily be linked for power and ground distribution, reset and clock lines, shift command, etc. Bases: gold-anodized aluminum. Terminals: non-corrosive nickel-silver. Four rubber feet included.

ACE Model No.	Tie Points	DIP No.	Parts Capacity	Board Size (Inches)	Price Each
200-K (kit)	728	8 (16's)	2	4.91/6.5/9/16	\$18.85
200 (assem.)	878	8 (16's)	8	4.91/6.5/9/16	28.95
201-K (kit)	1032	12 (14's)	2	4.91/6.5/7	24.95
212 (assem.)	1224	12 (14's)	8	4.91/6.5/7	34.95
218 (assem.)	1760	18 (14's)	10	6.1/2.7/1/8	64.95
227 (assem.)	2712	27 (14's)	28	6.6/3/1/4	59.95
236 (assem.)	3648	36 (14's)	36	4.10/4.9/1/4	70.95

BISHOP GRAPHICS Printed Circuit Drafting
Aids are now available from Digi-Key

MONSANTO MAN 64 AL
0.4 INCH RED 7-SEGMENT DISPLAY
60¢ **1702 AL**
ERASABLE PROM WITH QUARTZ WINDOW
\$13.50

SILICON TRANSISTORS
MPS918, MPS930, MPS2222A, MPS2369A, MPS2712, MPS2907A, MPS3392, MPS3393, MPS3394, MPS3395, MPS3396, MPS3397, MPS3398, MPS3399, MPS3400, MPS3641, MPS3642, MPS3643, MPS3644, MPS3646, 2N3904, 2N3906, 2N4124, 2N4126, 2N4401, 2N4403, 2N4404, 2N4405, 2N5087, 2N5089, 2N5091, 2N5092, 2N5093, 2N5133, 2N5134, 2N5137, 2N5138, 2N5139, 2N5210, 2N5964 .16, .51, .55/10, .51, .55/10, .51, .55/10 of some part no.

MPI102 .36 \$30.60 / C 2N5457 .48 \$41.00 / C MPIA13 .28 \$24.00 / C 2N3055 .99 \$85.00 / C

ELECTROLYTIC CAPACITORS

Radial Lead	Axial Lead	Axial Lead
1uf/50v .08 .65/10	1uf/50v .11 .90/10	47uf/25v .17 1.30/10
2.2uf/50v .08 .65/10	2.2uf/50v .12 1.00/10	100uf/16v .37 3.01/10
3.3uf/50v .08 .65/10	3.3uf/35v .12 .95/10	100uf/25v .20 1.55/10
4.7uf/25v .08 .65/10	3.3uf/50v .12 1.00/10	100uf/50v .29 2.30/10
4.7uf/50v .08 .70/10	4.7uf/25v .12 .90/10	220uf/16v .20 1.55/10
10uf/25v .08 .70/10	4.7uf/35v .12 .95/10	220uf/25v .29 2.30/10
10uf/50v .10 .75/10	10uf/16v .11 .90/10	330uf/16v .29 2.35/10
20uf/50v .09 .70/10	10uf/25v .12 1.00/10	330uf/25v .32 2.55/10
22uf/50v .12 1.00/10	10uf/35v .14 1.15/10	470uf/16v .37 3.01/10
100uf/6.3v .09 .75/10	22uf/16v .12 1.00/10	470uf/25v .37 3.01/10
100uf/16v .11 .85/10	22uf/25v .13 1.05/10	1000uf/16v .39 3.15/10
100uf/25v .13 1.10/10	33uf/25v .14 1.15/10	1000uf/25v .56 4.50/10
	47uf/16v .14 1.15/10	2200uf/16v .62 4.95/10

DISC CAPS **1/2 WATT ZENER DIODES**

100pf/500v .04 .36/10	1N5226B 3.3v .15 \$11/C	1N5236B 7.5v .15 \$11/C
220pf/500v .04 .36/10	1N5227B 3.6v .15 \$11/C	1N5237B 8.2v .15 \$11/C
470pf/500v .04 .37/10	1N5228B 3.9v .15 \$11/C	1N5238B 8.7v .15 \$11/C
1000pf/500v .04 .40/10	1N5229B 4.3v .15 \$11/C	1N5239B 9.1v .15 \$11/C
2200pf/500v .04 .42/10	1N5230B 4.7v .15 \$11/C	1N5240B 10v .15 \$11/C
4700pf/500v .04 .45/10	1N5231B 5.1v .15 \$11/C	1N5241B 10v .15 \$11/C
10000pf/500v .04 .47/10	1N5232B 5.6v .15 \$11/C	1N5242B 12v .15 \$11/C</

TTL PLASTIC DUAL-IN-LINE I.C.

SN7400N	.15	SN74126N	.49
SN7401N	.15	SN74128N	.84
SN7402N	.15	SN74132N	.99
SN7403N	.15	SN74136N	.64
SN7404N	.18	SN74141N	.93
SN7405N	.18	SN74142N	3.00
SN7406N	.34	SN74143N	3.98
SN7407N	.34	SN74144N	3.98
SN7408N	.18	SN74145N	.98
SN7409N	.18	SN74147N	2.30
SN7410N	.15	SN74148N	1.90
SN7412N	.30	SN74150N	1.94
SN7413N	.45	SN74151N	.64
SN7414N	.99	SN74152N	.69
SN7416N	.27	SN74154N	1.04
SN7417N	.32	SN74155N	.79
SN7420N	.15	SN74156N	.74
SN7422N	.15	SN74157N	.65
SN7423N	.27	SN74159N	3.50
SN7425N	.27	SN74160N	.99
SN7426N	.27	SN74161N	.99
SN7427N	.27	SN74162N	.99
SN7428N	.39	SN74163N	.99
SN7430N	.15	SN74164N	1.10
SN7432N	.24	SN74165N	1.10
SN7433N	.37	SN74166N	1.23
SN7437N	.25	SN74167N	2.98
SN7438N	.25	SN74170N	2.98
SN7440N	.15	SN74172N	8.15
SN7442N	.48	SN74173N	1.30
SN7443N	.85	SN74174N	1.05
SN7444N	.85	SN74175N	.90
SN7445N	.79	SN74176N	.79
SN7446AN	.79	SN74177N	.79
SN7447AN	.79	SN74178N	.79
SN7448N	.79	SN74179N	1.95
SN7450N	.15	SN74180N	.72
SN7451N	.15	SN74181N	2.25
SN7453N	.15	SN74182N	.69
SN7454N	.15	SN74184N	1.95
SN7460N	.15	SN74185AN	1.85
SN7470N	.28	SN74186N	13.95
SN7472N	.32	SN74188N	4.75
SN7473N	.32	SN74190N	1.15
SN7474N	.32	SN74191N	1.15
SN7475N	.48	SN74192N	1.05
SN7476N	.34	SN74193N	1.05
SN7480N	.44	SN74194N	.99
SN7481AN	.99	SN74195N	7.90
SN7482N	.74	SN74196N	.95
SN7483AN	.74	SN74197N	.87
SN7484AN	1.95	SN74198N	1.69
SN7485N	.99	SN74199N	1.69
SN7486N	.33	SN74221N	1.50
SN7489N	2.24	SN74246N	1.95
SN7490AN	4.47	SN74247N	1.85
SN7491AN	.48	SN74248N	1.85
SN7492AN	.48	SN74249N	1.75
SN7493AN	.47	SN74251N	1.40
SN7494N	.76	SN74265N	.85
SN7495AN	.72	SN74278N	2.45
SN7496N	.75	SN74279N	.85
SN7497N	2.85	SN74283N	1.75
SN74100N	1.20	SN74284N	5.50
SN74104N	.43	SN74285N	4.50
SN74105N	.43	SN74290N	.85
SN74107N	.30	SN74293N	.85
SN74109N	.74	SN74298N	1.98
SN74110N	.54	SN74351N	1.92
SN74111N	.74	SN74365N	.69
SN74116N	1.36	SN74366N	.95
SN74120N	1.40	SN74367N	.95
SN74121N	.37	SN74368N	.69
SN74122N	.42	SN74390N	1.40
SN74123N	.68	SN74393N	1.40
SN74125N	.49	SN74490N	1.90

TTL LOW POWER SCHOTTKY PLASTIC DUAL-IN-LINE I.C.

SN74LS00N	.29	SN74LS83AN	1.49
SN74LS01N	.29	SN74LS85N	1.75
SN74LS02N	.29	SN74LS86N	.59
SN74LS03N	.29	SN74LS90N	1.15
SN74LS04N	.35	SN74LS91N	1.25
SN74LS05N	.35	SN74LS92N	1.15
SN74LS08N	.29	SN74LS93BN	1.15
SN74LS09AN	.29	SN74LS95AN	1.60
SN74LS10N	.29	SN74LS96N	1.75
SN74LS11N	.29	SN74LS107N	.59
SN74LS12N	.29	SN74LS109N	.59
SN74LS13N	.29	SN74LS112N	.59
SN74LS14N	1.48	SN74LS113N	.59
SN74LS15N	.29	SN74LS114N	.59
SN74LS20N	.29	SN74LS122N	.90
SN74LS21N	.29	SN74LS123N	1.10
SN74LS22N	.29	SN74LS124N	3.00
SN74LS26N	.40	SN74LS125N	.75
SN74LS27N	.35	SN74LS126N	.75
SN74LS28N	.35	SN74LS132N	1.25
SN74LS30N	.29	SN74LS136N	.59
SN74LS32N	.40	SN74LS138N	1.68
SN74LS33N	.40	SN74LS139N	1.68
SN74LS37N	.40	SN74LS145N	1.35
SN74LS38N	.40	SN74LS151N	1.30
SN74LS40N	.25	SN74LS153N	1.30
SN74LS42N	1.20	SN74LS155N	1.45
SN74LS47A	1.20	SN74LS156N	1.45
SN74LS48N	1.20	SN74LS157N	1.35
SN74LS49N	1.20	SN74LS158N	1.25
SN74LS51N	.29	SN74LS160N	2.25
SN74LS54N	.29	SN74LS161N	2.25
SN74LS55N	.29	SN74LS162N	2.25
SN74LS63N	1.75	SN74LS163N	2.25
SN74LS73N	.49	SN74LS164N	1.98
SN74LS74N	.55	SN74LS168N	2.75
SN74LS75N	.75	SN74LS169N	2.75
SN74LS76N	.49	SN74LS170N	2.95
SN74LS78N	.49	SN74LS174N	1.45

C/MOS

CD4000AE	.15
CD4001AE	.19
CD4002AE	.19
CD4006AE	1.30
CD4007AE	.19
CD4008AE	.99
CD4009AE	.48
CD4010AE	.48
CD4011AE	.19
CD4012AE	.19
CD4013AE	.19
CD4014AE	.19
CD4015AE	.15
CD4016AE	.42
CD4017AE	1.19
CD4018AE	1.15
CD4019AE	.45
CD4020AE	1.15
CD4021AE	1.20
CD4022AE	1.05
CD4023AE	.19
CD4024AE	.85
CD4025AE	.19
CD4026AE	1.75
CD4027AE	.48
CD4028AE	.48
CD4029AE	.99
CD4030AE	.42
CD4033AE	1.80
CD4035AE	1.20
CD4040AE	1.20
CD4042AE	.70
CD4043AE	.50
CD4044AE	.50
CD4049AE	.45
CD4050AE	.45
CD4051AE	1.25
CD4052AE	1.25
CD4053AE	1.25
CD4055AE	1.50
CD4056AE	1.50
CD4060AE	1.75
CD4066AE	.70
CD4069AE	.29
CD4071AE	.25
CD4072AE	.35
CD4073AE	.35
CD4075AE	.35
CD4076AE	1.24
CD4081AE	.25
CD4082AE	.35
CD4084AE	1.25
CD4085AE	1.25
CD4086AE	1.25
CD4087AE	1.25
CD4088AE	1.25
CD4089AE	1.25
CD4090AE	1.25
CD4091AE	1.25
CD4092AE	1.25
CD4093AE	1.25
CD4094AE	1.25
CD4095AE	1.25
CD4096AE	1.25
CD4097AE	1.25
CD4098AE	1.25
CD4099AE	1.25

LED'S

LITRONIX	
DL16	6.70
DL34M	7.25
DL44M	5.25
L155	6.98
DL701	1.95
DL702	1.95
DL704	2.30
DL707	1.70
DL707R	1.70
DL727	4.75
DL746	2.75
DL747	2.75
DL749	2.75
DL750	2.75
IL-1	1.05
IL-5	1.15
IL-12	.69
IL-15	1.25
IL-16	1.40
IL-74	.82
IL-100	5.45
ILD-74	1.61
ILQ-74	3.10
ILA-30	1.29
ILA-55	1.42
ILCA-2-30	2.80
ILCA-2-55	1.75
ILCT-6	2.20
RL2	.23
RL2-02	.48
RL2-03	.48
RL2-04	.48
RL20-48	.48
RL20-02	.48
RL20-03	.48
RL20-04	.48
RL21	.42
RL21-02	.42
RL21-04	.42
RL22-04	.28
RL50-D1	.28
RL50-02	.28
RL50-03	.28
RL54	.21
RL55	.29
RL55-5	.35
RL209	.29
RL-4003	.32
RL-4403	.32
RL-4415	.55
RL-4484	.19
RL-4850-1	.27
RL-5034-1	.19
RL-5054-2	.52
RL-5054-5	.19
GL-56	.60
GL-4484	.75
GL-4850	.75
DL-30	.33
DL-31	.33
RLC-200	.54
RLC-201	.54
RLC-210	.59
RLC-400	.53
RLC-410	.59
IRL-40	1.30
IRL-60	.53
AIR-18	3.75
LPT-100	.59
LPT-100A	.69
LPT-100B	.84
LPT-110	.74
LPT-110A	.94
LPT-110B	1.09
DPCA	
LL7	.19
LSL16L	.35
LSL26L	.35
LSL13L	.35
LSL3L	.45
LSL4L	.75
LSL8L-1	.65
LSM6	.45
OPL211	.25
OPL212	.25
DSL1	.55
DSL16L	.35
SLA7	2.95
TEXAS INSTRUMENTS	
T1L103	7.00
T1L111	1.20
T1L112	.99
T1L120	.65
T1L209A	1.19
T1L211	.45
T1L220	.24
T1L221	.22
T1L222	.49
T1L223	.49
T1L302	9.95
T1L303	4.95
T1L304	4.95
T1L305	7.95
T1L306	8.95
T1L308	8.95
T1L309	8.95
T1L311	11.95
T1L312	1.70
T1L313	1.70
T1L32	.90
T1L63	.75
T1L78	.60
FAIRCHILD	
FC0802	.65
FC0806	.70
FC0820A	.80
FLV117	.18
FLV310	.55
FLV410	.55
FND357	1.75
FND500	1.75
FND507	1.75
FND807	3.00
FNS700	.60
FPT100	.70

MOS & BI-POLAR MEMORIES

AYS-1013P	7.75	8 Bit UART
AYS-2376	19.95	88 x 3 x 9 Keyboard Encoder
MF1101AP	3.50	MOS RAM 256 Bit
MF1103-P	3.95	MOS RAM 1024 Bit
MF1404AT	3.25	Dual 512 Dynamic Shift Register
MF1404AT	3.00	1024 x 1 Dynamic Shift Register
MF1702AR	15.50	Static 256 x 8 PRDM
MF2102P	3.50	1D24 x 1 Static RAM 500 NS
MF8008R	17.95	MOS 8 Bit CPU 500 KHZ
MM6300J-1	5.95	256 x 4 PRDM (open collector)
MM6300J-1	5.95	256 x 4 PRDM Tristate
MM6305J-1	11.95	512 x 4 PRDM (open collector)
MM6305J-1	11.95	512 x 4 PRDM Tristate
MM6701D	34.95	4 Bit Expandable Bipolar C.P.U.
COM2D17	8.95	8 Bit UART
COM2502	8.50	8 Bit UART
COM2601	23.50	Universal Synchronous Receiver Transmitter
TMS3112NC	6.00	Hex 32 Bit Static Shift Register
TMS3113NC	6.00	Dual 133 Bit Static Shift Register
TMS3133NC	7.50	1024 Bit Static Shift Register
TMS3409NC	4.95	Quad 8 Bit Dynamic Shift Register
TMS4024NC	10.95	64 x 9 Fifo
TMS4030NL	14.95	4K Dynamic RAM Plastic 300 NS
TMS4030JL	16.95	4K Dynamic RAM Ceramic 300 NS
TMS4033NL	4.50	(2102-1) 1024 Bit Static RAM 450 NS
TMS4035NL	3.75	(2102) 1024 Bit Static RAM 400 NS
TMS4050NL	15.00	(18 PIN) 4K Dynamic RAM Plastic 300 NS
TMS4060NL	16.00	(22 PIN) 4K Dynamic RAM Plastic 300 NS
TMS4103NC	12.00	Input/output interface for 8080
TMS8080NC	29.95	
TMS5501JL	29.95	
4096DC	17.50	(16 PIN) Isoplanar 4K Dynamic RAM 350 NS
F8 KIT	295.00	8 Bit MPU Evaluation Kit
3342PC	5.50	Quad 80 Bit Static Shift Register
38140C	17.95	Digital Voltmeter Chip
2533PC	7.95	1024 Bit Static Shift Register 1.5 MHZ
93415PC	16.95	Bipolar 1K RAM 40 NS Open Collector
93425PC	16.95	Bipolar 1K RAM 40 NS Tri-State
93427PC	4.95	Tri-State 256 x 8 PRDM
93436DC	15.75	Tri-State 512 x 4 PRDM
93436DC	15.75	Open Collector 512 x 4 PRDM
LCM1001	149.95	Texas Instruments Microprocessor Learning Module

LINEARS

LM300H	.69	Voltage Regulator
LM301AH	.35	General Purpose Operational Amplifier
LM301AN-8 (Mini Dip)	.39	General Purpose Operational Amplifier
LM304H	.75	Precision Voltage Negative Regulator
LM305H	.78	Positive Voltage Regulator
LM307H	.28	Operational Amplifier
LM307 N-8 (Mini Dip)	.28	Operational Amplifier
LM308H	1.25	Precision Operational Amplifier
LM308AN	2.75	Precision Operational Amplifier
LM309H	.75	Five Volt Regulator
LM309K (TO3)	1.34	Five Volt Regulator
LM310H	1.09	Voltage Follower
LM311H	1.40	Voltage Comparator
LM318H	1.50	Precision High Speed Operational Amplifier
LM323K	7.50	3 Amp 5 volt Regulator
LM324N	1.10	Quad op amp
LM324N	1.20	Quad Comparator
LM555N-8 (Mini Dip)	.48	Timer
LM556N-14	.99	Dual Timer
LM709CN-14	.29	Operational Amplifier

7400N TTL

SN7400*	13	SN7453N	27	SN74150N	110
SN7401N	16	SN7454N	41	SN74151N	125
SN7402N	21	SN7455N	21	SN74152N	135
SN7403N	16	SN7460N	22	SN74154N	125
SN7404N*	16	SN7470N	45	SN74155N	121
SN7405N	24	SN7471N*	69	SN74156N	130
SN7406N	15	SN7472N	35	SN74157N	130
SN7407N	45	SN7473N*	37	SN74158N	175
SN7408N	25	SN7474N*	32	SN74161N	145
SN7409N	25	SN7475N*	32	SN74163N	135
SN7410N*	26	SN7476N*	59	SN74164N	165
SN7411N	30	SN7479N	50	SN74165N	165
SN7412N	42	SN7480N	50	SN74166N	170
SN7413N	85	SN7482N	175	SN74167N	550
SN7414N	70	SN7483N	115	SN74170N	300
SN7418N	40	SN7485N	112	SN74172N	180
SN7417N	43	SN7486N	95	SN74173N	170
SN7420N	21	SN7488N	350	SN74174N	195
SN7421N	39	SN7489N	300	SN74175N	195
SN7422N*	150	SN7490N*	89	SN74176N	90
SN7423N	37	SN7491N	60	SN74177N	90
SN7425N	43	SN7492N	82	SN74180N	105
SN7426N	31	SN7493N*	57	SN74181N	355
SN7427N	37	SN7494N	91	SN74182N	95
SN7429N	42	SN7495N	91	SN74184N	230
SN7430N	75	SN7496N	91	SN74186N	200
SN7432N	41	SN7497N*	400	SN74188N*	500
SN7437N	47	SN74100N*	100	SN74189N	600
SN7388N	40	SN74107N	189	SN74190N	150
SN7439N	25	SN74121N*	45	SN74191N	150
SN7440N	21	SN74122N	49	SN74192N*	119
SN7441N	10	SN74123N*	70	SN74193N*	99
SN7442N	108	SN74125N	60	SN74194N	145
SN7443N	105	SN74126N	80	SN74195N	120
SN7444N	10	SN74132N	300	SN74196N	200
SN7445N	10	SN74136N	180	SN74197N	100
SN7446N	115	SN74141N	115	SN74198N	225
SN7447N*	79	SN74142N	400	SN74199N	225
SN7448N	99	SN74143N	450	SN74200N	200
SN7450N	26	SN74144N*	450	SN74202N*	200
SN7451N	27	SN74145N	115	SN74251N	250
SN7452N*	27	SN74147N	300	SN74284N	600
		SN74148N	250	SN74285N	600

CONSUMER ELECTRONICS



exelar

DIGITAL WATCH
This watch is manufactured by National Semiconductor. It provides 5 functions: hours, minutes, seconds date. A.M. indicator dot. Accuracy is assured to 5 seconds per month by precision quartz crystal. It's something should go wrong with the watch, repair is assured within 48 hours after it is received. Complete with steel black leather band.

ES4-Y5
3 MICRON GOLD PLATE BEZEL
\$29.95
NOT A KIT



Novus

DIGITAL ALARM CLOCK
This 4 digit Novus Alarm Clock is a very reliable and smartly styled unit. It provides such features as an alarm setting any minute of the day, a 7 minutes snooze alarm, a power-failure indicator, and even an A.M. P.M. indicator.

\$19.95
NOT A KIT

74LS00 TTL

74LS00	39	74LS51	39	74LS151	155
74LS02	39	74LS73	65	74LS153	189
74LS04	45	74LS74	65	74LS157	155
74LS05	45	74LS76	79	74LS162	225
74LS08	39	74LS83	219	74LS164	225
74LS10	39	74LS86	45	74LS181	359
74LS13	79	74LS90	125	74LS190	285
74LS14	219	74LS92	125	74LS191	285
74LS20	39	74LS93	125	74LS192	285
74LS26	49	74LS95	219	74LS193	285
74LS27	45	74LS96	189	74LS194	225
74LS28	49	74LS107	65	74LS195	225
74LS30	39	74LS112	65	74LS257	189
74LS32	45	74LS132	155	74LS260	55
74LS40	39	74LS136	65	74LS279	79
74LS51	39	74LS138	189	74LS270	595

CMOS

CD4000	25	74C04N	75
CD4001	25	74C10N	65
CD4002	25	74C20N	65
CD4006	25	74C30N	65
CD4007	25	74C42N	215
CD4009	59	74C73N	150
CD4010	59	74C75N	150
CD4011	25	74C90N	300
CD4012	25	74C95N	150
CD4013	47	74C107N	125
CD4016	56	74C151	290
CD4017	135	74C154	300
CD4019	55	74C157	215
CD4020	149	74C160	325
CD4022	175	74C161	325
CD4023	23	74C163	300
CD4024	150	74C164	325
CD4025	150	74C173	275
CD4027	69	74C193	280
CD4028	165	74C194	280
CD4029	60	74C200N	39
CD4030	95	74C202N	55

OPTO ELECTRONICS

R - RED
G - GREEN
Y - YELLOW
O - ORANGE

DISCRETE LEDES

XC209R	5\$1	XC526R	5\$1	XC111R	5\$1
XC209G	4\$1	XC526G	4\$1	XC111G	4\$1
XC209Y	4\$1	XC526Y	4\$1	XC111Y	4\$1
XC209O	4\$1	XC526O	4\$1	XC111O	4\$1

125" dia. 185" dia. 190" dia.
200" dia. 200" dia. .085" dia.

MINIATURE TOGGLE

DPDT	ON	OFF	NO	NC	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
74LS10	ON	OFF	NO	NC	221	306	286	187	176											
74LS10	ON	OFF	NO	NC	222	286	276	188	181											
74LS10	ON	OFF	NO	NC	121	275	195	143	130											
74LS10	ON	OFF	NO	NC	122	206	165	121	110											

LINEAR

LM300N	80	LM1351N	165
LM301N	10	LM1414N	175
LM302N	35	LM1486N	65
LM303N	35	LM1496N	95
LM304N	100	LM1556N	185
LM305N	95	LM1811N	195
LM307N	35	LM1821N	195
LM308N	100	LM1920N	235
LM308CN	100	LM1920N	235
LM309N	110	LM3065N	69
LM309K	125	LM3065N	69
LM310N	110	LM3065N	69
LM310CN	110	LM3065N	69
LM311H	90	LM3558N	100
LM311N	90	LM3558N	100
LM318CN	150	LM7555N	125
LM319N	300	NE560B*	500
LM319D	300	NE561B*	500
LM320K-5	135	NE562N	39
LM320K-12	135	NE565N*	125
LM320K-15	135	NE566CN*	195
LM320T-5	175	NE567H*	125
LM320T-8	175	NE567H*	125
LM320T-12	175	LM7030N	45
LM320T-15	175	LM709H	29
LM320K-5	995	LM709N	29
LM320K-12	995	LM710N	29
LM320K-15	995	LM711N	39
LM340K-5	195	LM723N	35
LM340K-12	195	LM723H	55
LM340K-15	195	LM733N	100
LM340K-24	195	LM739N	129
LM340T-5	175	LM741CH	35
LM340T-12	175	LM741CN	35
LM340T-15	175	LM741CN	35
LM340T-18	175	LM747H	79
LM340T-12	175	LM747N	79
LM340T-15	175	LM749N	39
LM340T-18	175	LM749N	39
LM350N	00	LM1303N	90
LM351CN	65	LM1304N	119
LM357N	115	LM1305N	140
LM370H	115	LM1307N	85
LM373N	325	LM1310N	295

DISPLAY LEDES

FND500	FND70	DL707	MAN 2	MAN 3	MAN 4	MAN 7	DL747	DL338
MAN 1	COMMON ANODE	270	\$3.25	MAN 74	COMMON CATHODE	300	\$1.50	
MAN 2	5 x 7 DOT MATRIX	300	4.95	DL707	COMMON ANODE	300	\$1.50	
MAN 3	COMMON CATHODE	125	39	DL747	COMMON ANODE	600	2.25	
MAN 4	COMMON CATHODE	187	195	DL750	COMMON CATHODE	600	2.25	
MAN 7	COMMON ANODE	300	1.50	DL338	COMMON CATHODE	110	1.25	
MAN 75	COMMON ANODE-YELLOW	300	2.50	FND70	COMMON CATHODE	250	50	
MAN 77	COMMON ANODE	300	1.50	FND500	COMMON ANODE	600	1.75	
MAN 78	COMMON ANODE	300	1.50	FND500	COMMON ANODE	500	1.75	

THUMBWHEEL SWITCHES

Order: Order desired switch or switches and add number of switches for each quantity desired.

Part No.	Description	Price	Part No.	Description	Price
SW 10	10 Position	\$2.50	SW 10	10 Position	\$2.50
SW 12	12 Position	\$3.00	SW 12	12 Position	\$3.00
SW 15	15 Position	\$3.50	SW 15	15 Position	\$3.50
SW 20	20 Position	\$4.50	SW 20	20 Position	\$4.50

KITS EXAR ICS

Includes monolithic function generator IC, PC board, and assembly instruction manual.

XR-2206KA SPECIAL \$17.95

XR-2206KB SPECIAL \$27.95

Same as XR-2206KA above and includes external components for PC board.

TIMERS	STEREO DECODERS	WAVEFORM GENERATORS	MISCELLANEOUS
XR-555CP	XR-1310P	XR-205	XR-2205CP
XR-200P	XR-1310EP	XR-205	XR-2207CP
XR-555CP	XR1800P		
XR-2556CP			
XR-2240CP			
XR-210			
XR-215			
XR-567CP			
XR-2567CP			

50 PCS. RESISTOR ASSORTMENTS \$1.75 PER ASST.

ASST.	5 ea.	10 OHM	12 OHM	15 OHM	18 OHM	22 OHM	24 OHM	27 OHM	30 OHM	33 OHM	36 OHM	39 OHM	43 OHM	47 OHM	51 OHM	56 OHM	62 OHM	68 OHM	75 OHM	82 OHM	91 OHM	100 OHM	
ASST. 1	5 ea.	27	33	39	47	56	68	82	100	120	150	180	220	270	330	390	470	560	680	820	1K	1.4	1.8
ASST. 2	5 ea.	180	220	270	330	390	470	560	680	820	1K	1.4	1.8	2.2	2.7	3.3	3.9	4.7	5.6	6.8	8.2	10K	
ASST. 3	5 ea.	1K	1.5K	1.8K	2.2K	2.7K	3.3K	3.9K	4.7K	5.6K	6.8K	8.2K	10K	12K	15K	18K	22K	27K	33K	39K	47K	56K	
ASST. 4	5 ea.	82K	10K	12K	15K	18K	22K	27K	33K	39K	47K	56K	68K	82K	100K	120K	150K	180K	220K	270K	330K	390K	
ASST. 5	5 ea.	150K	180K	220K	270K	330K	390K	470K	560K	680K	820K	1K	1.2M	1.5M	1.8M	2.2M	2.7M	3.3M	3.9M	4.7M	5.6M	6.8M	
ASST. 6	5 ea.	100K	120K	150K	180K	220K	270K	330K	390K	470K	560K	680K	820K	1K	1.2M	1.5M	1.8M	2.2M	2.7M	3.3M	3.9M	4.7M	
ASST. 7	5 ea.	2.7M	3.3M	3.9M	4.7M	5.6M	6.8M	8.2M	10M	12M	15M	18M	22M	27M	33M	39M	47M	56M	68M	82M	100M	120M	

14 PCS. POTENTIOMETER ASSORTMENTS

ASST.	A 2 ea.	10 OHM-20 OHM	50 OHM-100 OHM	200 OHM-500 OHM	1K-500K	
ASST. B 2 ea.	1K	2K	5K	10K	20K	50K
ASST. C 2 ea.	50K	100K	200K	500K	1M	2M

Each assortment contains 14 pcs of 10 turn pots. All pots are available in single unit quantities. \$9.95 ea.

ZENERS - DIODES - RECTIFIERS

TYPE	VOLTS	PRICE	TYPE	PRICE			
1N4745	3.3	100m	4100	1A0005*	800 PIV	1 AMP	101.00
1N4751	5.1	400m	4100	1A0006*	800 PIV	1 AMP	101.00
1N4752	5.6	400m	4100	1A0007*	1000 PIV	1 AMP	101.00
1N4753	6.2	400m	4100	1N3600	50	200m	61.00
1N4754	6.8	400m	4100	1N4185	15	100m	121.00
1N4755	15	400m	4100	1N4154	35	10m	121.00
1N5232	5.6	500m	28	1N4724	5.6	1w	28
1N5234	6.2	500m	28	1N4735	6.2	1w	28
1N5235	6.8	500m	28	1N4738	6.8	1w	28
1N5236	7.5	500m	28	1N4738			

CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case Style	Price
CY1A	1 000 MHz	HC231U	\$4.95
CY2A	2 000 MHz	HC231U	\$4.95
CY3A	4 000 MHz	HC181U	\$4.95
CY7A	5 000 MHz	HC181U	\$4.95
CY12A	10 000 MHz	HC181U	\$4.95
CY14A	14 318.18 MHz	HC181U	\$4.95
CY19A	18 000 MHz	HC181U	\$4.95
CY22A	20 000 MHz	HC181U	\$4.95
CY30B	32 000 MHz	HC181U	\$4.95

CLOCK CASES

Nicely styled cases complete with red bezel for use in such applications as desk clocks, car clocks, alarm clocks, instrument cases.

DIMENSIONS: W-4" L-4 1/4" H-2"

\$5.95

64 Key Keyboard

\$24.95

The keyboard is composed of 64 Magnetic Reed Switches, in one molded unit. It is unbranded with each SPST switch brought out to two pins.

HD0165 Keyboard Encoder ROM **\$7.95**

JOYSTICK

These joysticks feature four 100K potentiometers, that vary resistance proportional to the angle of the stick. Sturdy metal construction with plastics components only at the movable joint. Perfect for electronic games and instrumentation.

\$9.95 ea

MOS LSI DEVICES

CLOCK CHIPS

MM5309	6 Digit, BCD Outputs, Base PWR	\$5.95
MM5311	6 Digit, BCD Outputs, 12 or 24 Hour	4.95
MM5312	4 Digit, BCD Outputs, 1 PPS Output	4.95
MM5313	6 Digit, BCD Outputs, 1 PPS Output	4.95
MM5314	6 Digit, 12 or 24 Hour, 50 or 80 Hz	4.95
MM5316	4 Digit, Alarm, 1 PPS Output	6.95
MM5318	Video Clock Chip, For Use With MM5841	9.95
CT7001	6 Digit, Calendar, Alarm, 12 or 24 Hour	6.95

CALCULATOR CHIPS

MM5725	6 Digit, Four Function, Less Decimal	\$2.95
MM573R	8 Digit, 5 Function: +, -, x, /, %	2.95
MM5759	8 Digit, 4 Function, Floating Decimal	2.95
CT5001	12 digit 4 Function	3.95
CT5005	12 digit 4 Function with Memory	5.95
CT5030	12 digit 4 Function and	7.95

MISC. MOS

MM5320	TV Camera Sync Generator	19.95
MM5841	Video Generator For MM5318	18.00
MM5330	4 1/2 Digit DVM Chip	9.95
MK5007	Complete 4 Digit Counter	116.95
LD110, LD111	3 1/2 Digit Voltmeter Chip Set	\$25.00
MC1408L7	7 Bit Digital To Analog Conv.	9.95

DL728

The DL728 is a dual 0.5" common cathode red display. It is ideal for use with clock chips, as segments are already multiplexed.

\$2.95

1/16 VECTOR BOARD

0.1" Hole Spacing P-Pattern Price

Part No	Length	Width	1-19	20-49	
PHENOLIC	64P44 062XXXP	4.50	6.50	11.72	15.54
	169P44 02XXXP	4.50	17.00	3.89	3.32
EPOXY	64P44 062	4.50	6.50	2.07	1.86
GLASS	64P44 062	4.50	8.50	2.56	2.31
	169P44 062	4.50	17.00	5.04	4.53
	169P44 062	8.50	17.00	19.23	8.26
EPOXY GLASS	169P44 062C1	4.50	17.00	6.80	6.12
COPPER CLAD					

VECTOR WIRING PENCIL

Vector Wiring Pencil P173 consists of a hand held featherweight (under one ounce) tool which is used to guide and wrap insulated wire. Fed off a self-contained replaceable bobbin, onto component leads or terminals installed on pre-punched "P" Pattern Vectorboard. Connections between the wrapped wire and component leads, pass or terminals are made by soldering. Complete with 250 FT of red wire.

\$9.50

REPLACEMENT WIRE — BOBBINS FOR WIRING PENCIL

W36-3-A-Pkg. 3	250 Ft. 36 AWG GREEN	\$2.40
W36-3-B-Pkg. 3	250 Ft. 36 AWG RED	\$2.40
W36-3-C-Pkg. 3	250 Ft. 36 AWG CLEAR	\$2.40
W36-3-D-Pkg. 3	250 Ft. 36 AWG BLUE	\$2.40

1 1/4" x 1 1/2" XFEMERS

That were designed for clock type applications. 110 Vac primary @ 60 Hz. Secondarys: 8-10 Vac @ 30 mA-50 mA. 50 Vac @ 30 mA-50 mA. Excellent for miniature power supplies & gas discharge displays.

SPECIAL \$7.95

MOLEX PINS

PINS USED AS INEXPENSIVE SUBSTITUTE FOR SOCKETS

SPECIAL	100/1.49
SPECIAL	1000/12.00

MICROPROCESSOR COMPONENTS



8080		8080A	
8080	8 Bit CPU	1101	256K1
8080	Super 8080	2111	1024K1
8080A	Super 8080	2101	256K1
		2102	1024K1
		2107	4096K1
		2111	256K1
		2101	1024K1
		7489	16K4
		8101	256K4
		8111	256K4
		8589	16K4
		91102	1024K1
		74200	256K1
		93410	256K1
		5262	2048K1

SR'S		RAM'S	
2504	1024 DYNAMIC	\$9.00	
2518	HEX 32 BIT	7.00	
2519	HEX 40 BIT	4.00	
2524	512 DYNAMIC	2.95	
2525	1024 DYNAMIC	6.00	
2527	DUAL 256 BIT	3.95	
2529	QUAD 512 BIT	4.00	
2532	QUAD 80 BIT	3.95	
2533	1024 STATIC	7.95	
3341	FIFO	6.95	
74LS670	16K4 REG	3.95	

UART'S		PROMS				
AY-5-1013	20K 8AUD	\$6.95	1702A	2048	FAMOS	15.95
			5203	2048	FAMOS	14.95
2513	CHAR GEN	11.00	82S23	32K8	OPEN C	6.00
7488	RANDOM BITS	3.50	82S123	32K8	TRISTATE	5.00

BUILD YOUR OWN JOLT MICROCOMPUTER IN JUST 3 HOURS OR LESS FOR \$159.95

A COMPLETE MICROCOMPUTER IN A SINGLE CPU KIT INCLUDES: • An MOS Technology MCS6502 NMOS microprocessor • 512 bytes of program ROM, and 64 bytes of interrupt vector RAM • 1K bytes of mask programmed ROM containing DEMON, a powerful debug monitor • 26 programmable I/O lines • Internal RC clock, or crystal controlled clock with user supplied crystal • Serial I/O ports for use with a teleprinter current loop driver/receiver, or an EIA standard driver/receiver • Expandable address and data buses • Hardware interrupt • Control panel interface lines available on card connector • Complete assembly manuals and sample programs

JOLT ACCESSORY KITS

JOLT RAM Card — Fully static 4,096 bytes of RAM with 1 microsecond access time and on-board decoding. **\$199.95**

JOLT I/O Card (Peripheral Interface Adapter) — 2 PIA LSI chips, 32 I/O lines, four interrupt lines, on-board decoding and standard TTL drive. Fully programmable. **\$95.50**

JOLT Power Supply — Operates at +5, +12 and -10 voltages. Supports JOLT CPU, 4K bytes of RAM and JOLT I/O card — or, CPU and 8 I/O cards. **\$99.95**

JOLT +5V Booster Option — Fits onto JOLT Power Supply card. Supports CPU, 8K bytes RAM and 8 I/O CPU and cards. **\$24.95**


JOLT Universal Card — Same size (4 1/4" x 7") same form factor as other JOLT cards. Completely blank, drilled to accept 14, 16, 24 or 40 pin sockets. **\$24.95**

JOLT Accessory Bag — Contains enough hardware to connect one JOLT card to another, flat cable, connecting card spacers, hardware, etc. **\$39.95**

JOLT Resident Assembler — Fully symbolic, single pass resident assembler, all mnemonic compatible with timesharing assemblers. Delivered on four 1702A PROMs, ready for plugging into JOLT PROM card. **\$149.95**

JOLT 1702A PROM Card — Sockets for 2,048 bytes of PROM memory. Place anywhere in memory with jumper selectable addresses. **\$99.95**

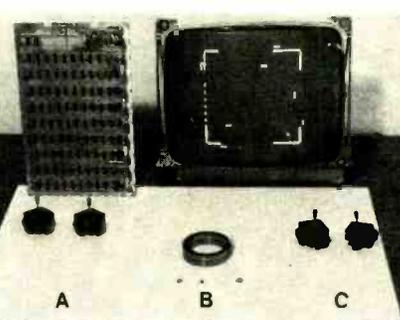NOW: YOUR OWN VIDEO GAME FOR THE ENTIRE FAMILY



This game comes pre-tested with two PROFESSIONAL Kraft joysticks. Joysticks allow 2 dimensional player control (rather than only one dimension, such as up and down.) If you require more than two players, order extra joysticks. All that's required is a 5V/2A power supply, a harness, and speaker. Comes with schematics, wiring information, and all necessary documentation. Game gives 1V composite video output, perfect for any TV monitor. Game designed so one, two, three, or four players can play at the same time. You can even play against the HOUSE. Score for each person is shown on TV set. These boards are production over runs of a well known video game manufacturer, and are not rejects, or in any way inferior to one presently being sold in games for over \$1,000.00.

KIT A — \$179.95 PROFESSIONAL game P.C. board, and 2 PROFESSIONAL joysticks. P.C. board size is 10 1/2" x 17". This is the same PROFESSIONAL game as seen in commercial establishments. Don't confuse it with the simple games sold in stores, or with analog kits.

ACCESSORY B — \$3.95 Six feet of ribbon cable, three SPST switches (coin simulator, house/player, and start switch), for those of you who don't have extra wire or switches to build the harness.

ACCESSORY C — \$39.95 Two additional PROFESSIONAL Kraft joysticks, for third and fourth player.

DIGITAL CLOCK KIT — 3 1/2" INCH DIGITS

This clock features big 3 1/2" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2" LEDs. The clock operates from 117 VAC, has either 12 or 24 hr. operation. The 6 digit version is 27" x 3 1/2" x 1 1/2", and the 4 digit is 18" x 3 1/2" x 1 1/2". Kit comes complete with all components, case and transformer. Specify 12 or 24 Hr. When Ordering.

4 DIGIT KIT	\$49.95	4 DIGIT ASSEMBLED	\$59.95
6 DIGIT KIT	\$69.95	6 DIGIT ASSEMBLED	\$79.95

ELECTRONIC CRAPS

Electronic craps is an entirely electronic game featuring a dice "roll down" with 14 LED's form two dice that roll when actuated by a push button. Dimensions are 6 1/2" x 3 1/2" x 1 1/2".

\$19.95 Per Kit
\$24.95 Assembled

ELECTRONIC ROULETTE

This kit comes complete with all components, including the case and line cord. Electronic Roulette, is entirely electronic, and features 32 LED's that form a wheel, that is actuated by a push button switch. Dimensions are 6 1/2" x 6 1/2" x 1 1/2".

\$29.95 Per Kit
\$34.95 Assembled

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.
California Residents — Add 6% Sales Tax — Data Sheets 25c each
Send a 13c Stamp (postage) for a FREE 1976 Catalog

JAMES

P.O. BOX 822, BELMONT, CA. 94002
PHONE ORDERS — (415) 592-8097

AUTOTEL™

WARNING LIGHTS ARE NOT ENOUGH



AN AUDIBLE ALARM INDICATING POTENTIAL ENGINE DAMAGE

AUTOTEL is an efficient (15 ma current standby) device by which every owner of an automobile, truck or vehicle equipped with indicator lights for temperature and oil pressure can be assured of a reliable warning before an impending failure.

AUTOTEL, by means of an audible signal (70 db pulsing) immediately forewarns the vehicle operator of a malfunction or failure, allowing time to correct and prevent major engine failures. It is programmed so there is no sound during normal operating conditions.

AUTOTEL features CMOS circuitry, packaged in a 2 1/2" x 5 1/4" x 1 1/4" case. The kit comes complete with all components, hardware and case to hook directly into your car's warning light system.

\$9.95 Per Kit **\$14.95 Assembled**

IMC 3 1/2 DIGIT DVM KIT

DIMS 3" W, 1 3/4" H, 2 1/4" D



This 0-2 VDC, .05 per cent digital voltmeter features the Motorola 3 1/2 digit DVM chip set. It has a 4" LED display and operates from a single +5V power supply. The unit is provided complete with an injection molded black plastic case complete with bezel. An optional power supply is available which fits into the same case as the 0-2V DVM allowing 117 VAC operation.

A. 0-2V DVM with Case **\$49.95**
B. 5V Power Supply **\$14.95**

JE700 CLOCK

The JE700 is a low cost digital clock but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6" x 2 1/2" x 1". It utilizes a MAN72 high brightness readout, and the MM5314 clock chip.

12 or 24 Hour
\$17.95
Per Kit

JE803 PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN75 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels, or circuit damage will result.

\$9.95 Per Kit
printed circuit board

ELECTRONIC CRAPS

Electronic craps is an entirely electronic game featuring a dice "roll down" with 14 LED's form two dice that roll when actuated by a push button. Dimensions are 6 1/2" x 3 1/2" x 1 1/2".

\$19.95 Per Kit
\$24.95 Assembled

ELECTRONIC ROULETTE

This kit comes complete with all components, including the case and line cord. Electronic Roulette, is entirely electronic, and features 32 LED's that form a wheel, that is actuated by a push button switch. Dimensions are 6 1/2" x 6 1/2" x 1 1/2".

\$29.95 Per Kit
\$34.95 Assembled

Continental Specialties

PROTO BOARD 100
A low cost, big 10 IC capacity breadboard kit with all the quality of OT sockets and the best of the Proto Board series... complete down to the last nut, both and screw. Includes 2 OT-355 Sockets, 1 OT-358 Bus Strip, 2 5-way binding posts, 4 rubber feet, screws, nuts, bolts, and easy assembly instructions.

\$19.95

Olson ELECTRONIC PARTS AND ACCESSORIES

TL-477. Soldering Iron	2.99
VC-274. 12-Pc. Volume Control Kit	.49c
XM-501. 40-Pc. Terminal Strip	.79c
XM-370. 7 Seg. L.E.D. Display	1.29
TR-446. 25-Pc. Ass'td. SCR	1.49
SW-555. 90-120 V AC Relay	.59c
SW-156. Ctr.-Off Toggle Switch DPDT. Pkg. 2	2.49
SW-460. 3 Button Push Switch	.24c
SW-636. Thermostatic Switch 50-600 NO	.39c
SW-752. Unimax 15A Switch SPST	.49c
SW-587. 5A Toggle SPST NO	.39c
SW-431. Phone Type Lever Switch 4 SPST	.62c
SW-632. Reed Switch W/Magnet SPST. Pkg. 10	1.29
MO-359. 130 RPM Timing Motor 120V AC	.49c
TT-092. 2500 OHM Output Transformer	.64c
TF-047. 6 V 1/2 A. Filament Transformer	.44c
TF-050. 12V .2A Filament Transformer	.47c
KN-030. 25-Pcs. Assorted Knobs	.49c
ME-182. 0-1 Ma Panel Meter 1 3/8" Mtg. Hole	.89c
ME-205. 0-200 UA. Panel Meter 1 5/16 x 5/8"	.74c

Send to: Olson Electronics, Dept. LK 260 S. Forge St., Akron, Ohio 44327. Allow For Postage. COD 20% Deposit. Residents of the following states please add Sales Tax: Ca. 5%, Fl. 4%, Ga. 3%, Il. 4%, Ky. 5%, Ma. 5%, Mi. 4%, Mo. 3%, N.Y. 4%, Oh. 4%, Pa. 6%, Tx. 4%.

FREE! Please send me Olson catalog CB catalog Both. Print

NAME _____
 ADDRESS _____
 CITY _____
 STATE _____ ZIP _____

Circle 108 on reader service card



— econofrace —
 EQUIP YOUR LAB OR SHOP WITH A GENUINE QUALITY FEMTOOSCOPIC CURVE TRACER. MEASURE VOLT, AMPLITUDE, PHASE, PERIOD, MATCH PAIRS, ETC. USES LATEST CMOS CIRCUITRY. COMPLETE WITH BATTERY. COMPARES WITH TRACERS SELLING FOR \$150.00 OR MORE AND EASIER TO OPERATE. SEND CHECK FOR \$39.99 PLUS \$1.00 FOR POSTAGE & HANDLING. COLD. RIS. ADD 3 1/2% SALES TAX. MONEY BACK GUARANTEE.
lab science
 PO BOX 1972
 BOULDER, CO. 80302

ELECTRONIC kits, optoelectronics, linear & digital IC's, transistors, loads of components, at low, low prices! SN7400 10¢, 741 29¢, DL747 \$1.95, 1% resistors 100/\$1. Catalog 25¢. **DIAMONDBACK ENGINEERING**, PO Box 194, Spring Valley, IL 61362

C-MOS PROBE

will convert your voltmeter into a sensitive FET INPUT millivoltmeter. Complete kit \$11.25 plus shipping. Also - Temp Meters - Power Supplies - Design Consoles.




DIAC SCIENTIFIC INSTRUMENTS BOX 1054R - LIVERMORE - CA 94550

FREE catalog. Ultrasonic devices, LED's, transistors, IC's, strobe lights, UART's, memories, digital thermometers, unique components. **CHANEY'S**, Box 15431, Lakewood, CO 80215

KEYBOARDS, for synthesizers, organs. Three octave. \$65. **BRINKWOOD ELECTRONICS**, Box 26A, Sandy Spring, MD 20860

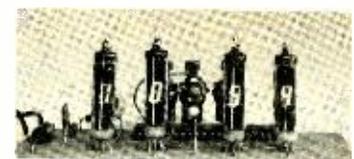USED OSCILLOSCOPES TEST EQUIPMENT
 FREE INFORMATION
American Calibration Services
 Box 8104 • Athens, GA 30601



CLOCK KIT \$14.00

Includes all parts with MM5316 chip, transformer, drilled & etched PC board, all except case. #SP-284 \$14 or 2/\$25

ASCII KEYBOARD, brand new w/paperwork \$45.00

AA NICAD CELLS brand new \$1.25 each 9/\$9.00

C-MOS LINEAR all brand new RCA

301	\$.60	747	\$.82	CLOCK CHIPS
307	.52	748	.50	MM5314 \$3.00
324	1.80	1458	.96	MM5316 3.00
339A	1.60	3401	.80	7001 8.00
741	.50	555	.60	

POWER SUPPLY KIT

Puts out 24-12-6 volt DC 2 amps. Includes xfmr, line cord, filter, silicon bridge. #PK-2B \$9.00

B & L HELIUM NEON GAS LASER

Fully assembled, runs on 115 volts AC. Less Laser tube. \$15.00

POWER AMP TRANSFORMER \$9.00

115 volts input, output of 96 VCT 2 amps. \$9.00 each 3/\$25

Please add shipping cost on above. FREE catalog

Meshna SURPLUS ELECTRONIC MATERIAL
 P.O. Box 62
 19 ALLERTON STREET
 E. LYNN MASS. 01904

Circle 109 on reader service card

IT'S ABOUT TIME

4-DIGIT ALARM CLOCK KIT NO. 1 **\$13.95** (with PC Board)



- FEATURES**
- Direct drive display outputs
 - Current control regulation-on chip
 - Low power brightness control - on chip
 - RFI eliminating slowup circuitry
 - Sleep radio feature
 - 24-Hour "Snooze" alarm
 - Independent digit setting
 - Non-multiplexed output circuitry

12 VAC CT 1/2 amp transformer for Kit No. 1\$2.00

KIT NO. 2

Complete kit with components, PC Board, transformer, wood grain case, and filter for display window. Includes 25 inch readouts **\$21.50**



KIT NO. 3

Complete kit with components, PC Board, transformer, wood grain case, and filter for display window. Includes .5 inch readouts. **\$22.50**

* Components for Kit No. 2 or Kit No. 3 sleep radio feature, add .95.


SCIENTIFIC KITS TIME BASE

4-DIGIT DECADE COUNTER KIT **\$19.95**



One chip 4 digit decade counter kit, with both 7 segment and BCD output. **KIT 012**

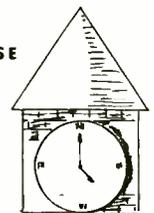1. Chip features internal oscillator for scanning speed.
2. Overflow and count extent outputs.
3. Transfer, reset, count, blanking and true compliment control inputs.
4. PC Boards can be cascaded to 8-12-16, etc. digits.
5. Kit includes counter chip, drive circuit for 4 cathode type displays and PC Board. (For readout board see (FND70-FND503-MAN74)



1 Mhz crystal chain time base divider. Outputs: 1 Mhz-100 Khz-10Khz-1Khz-100 Hz-10Hz-1 Hz-0.1 Hz. Accuracy better than .005% with proper adjustment.

KIT 013 complete C Mos with PC Board. **\$15.75**
KIT 014 Same as Kit 013, but with TTL. **\$13.75**

KIT 015-60 Hz chain time base using line frequency as reference. Accuracy 0.1-0.05%. Outputs 10 Hz 1 Hz-0.1 Hz. Complete with C Mos shaping circuit and PC Board**\$7.75**



KIT 016-10 Mhz frequency counter kit, together with Kit 012 and 013 or 014 or 015 and display board makes a nice accurate frequency counter. Complete with PC Board and lead for overflow, Mhz, Khz indication..... **\$16.50**

LSI INTEGRATION

MM5314	6 digit digital clock 24 pin dip w/spec.	\$ 3.75
MM5316	4-6 digit alarm clock 40 pin dip w/spec.	\$ 4.25
7002	4 digit counter/latch decoder; 7 segment and BCD outputs. 28 pin dip w/spec.	\$12.50
7005	4 digit counter/latch decoder; 7 segment output only. 24 pin dip w/spec.	\$ 9.50
7007	4 digit counter/latch decoder with BCD output only. 16 pin dip w/spec.	\$ 7.00
70250	4-6 digit alarm clock 28 pin dip w/spec.	\$ 5.50
70380	4 digit non-multiplexed radio alarm clock featuring direct drive display output 40 pin dip w/spec.	\$ 6.50
PC Board for 70250		\$ 4.25
PC Board for 70380		\$ 4.75

RADIO-ELECTRONICS

ALTAJ ELECTRONICS
 P.O. Box 38544R, Dallas, Texas 75238
 TERMS: Check or money order. No COD.
 Telephone (214) 278-3561
 Texas Residents Add 5%

DVM
 1.999 V. as basic with polarity indication, together with Kit 012 and a 4 digit display board, you have a DVM with 1 M ohm input impedance, and if properly adjusted, 1% accuracy. Includes components & PC Bd.
KIT 017 \$13.50

Circle 110 on reader service card

AT LAST!

4 & 6 DIGIT PC BOARDS

- PC Board for 4 digit display MAN series or DL707
- PC Board for 6 digit display MAN series or DL707
- PC Board for 4 digit display FND503
- PC Board for 6 digit display FND503
- PC Board for 4 digit display DL747
- PC Board for 6 digit display DL747
- PC Board for 4 digit display DL727
- PC Board for 6 digit display DL727
- PC Board for 4 digit display FND70

- \$1.75
- \$2.25
- \$2.00
- \$3.00
- \$2.50
- \$3.00
- \$2.25
- \$3.00
- \$1.75



All PC display Boards are multiplexed for adding additional digits.



DL747
Jumbo .6 in. high, and only 20mA per segment.
\$2.75



DL727
One of our best readouts .5 in. high, 20 mA per segment. Common anode.
\$3.75

DL707



Red, .30 in. high 15 mA per segment. Common anode \$1.25



DL33
If you like an array of displays, we have it. 10mA per segment. Common Cathode.
\$1.45



HP7730
.33 in. high, red very bright readout. 25mA per segment. Common anode.
\$1.20



BURROUGHS 12 DIGIT
.25 in. high orange digit. 160V DC. Free skt. \$3.25



FND503
New .5 in. display by Fairchild. Common Cathode.
\$1.60
5 for \$7.50



LEDs
Mini red .12
Jumbo red .15
Jumbo green .20
Jumbo yellow .25

**MAN'S GREEN
MAY RED
MANS YELLOW**

Why not make a clock in 3 diff. colors. .27 in. high. Common anode. \$1.25

DISPLAY SPECIAL



\$1.30

Fully multiplexed, common cathode. Goldplated. Ideal for mini 6 digit clock.

THE KING OF ALTAJ

INTRODUCING:

FATIMA

FOUR DIGIT TEMPERATURE KIT

FATIMA, the first in a series of time sharing kits to interface with THE KING.



FATIMA - FEATURES: **\$19.95**

- 1) 4-digit temperature display
- 2) Fahrenheit or Centigrade
- 3) Temperature 10 sec. display; time 20 sec. display
- 4) Complete C-Mos application
- 5) Kit uses 7002 4-digit counter

Kit includes all components, PC Board and instructions for interfacing with THE KING 6-digit alarm clock.

Watch next issue for yet another addition!

THE KING - FEATURES:

- 1) 6 digit, 12 hr. 60 cycle or 24 hr. 50 cycle alarm clock
- 2) Time sharing capability for display of additional information.
- 3) Built-in alarm generator and automatic output for intensity control of LEDs.
- 4) Single 12v. supply and a minimum of interface components.
- 5) AM-PM and automatic power failure indications.
- 6) 10 minute snooze
- 7) Complete data and construction manual enclosed.

THE KING **\$23.50**



- Kit No. 70250-1R (Red readouts)
- Kit No. 70250-1G (Green readouts)
- Kit No. 70250-1Y (Yellow readouts)
- Kit No. 70250-2R (DL727 readouts) ...\$28.50
- Kit No. 70250-3R (DL747 readouts) ...\$28.50

All kits include Components, PC Boards, Transformer, and Case.

CSG 100



new Proto Board \$19.95
(Complete Kit)
(Allow 2 weeks for Delivery)

We now offer a full line of Continental Specialties Proto Boards, Clips, Monitors, etc.

LOOK!

From Altaj to you, a special offer.

Power Supply Kit : 5Volt 1Amp. Reg. Line regulation .005% Load regulation 50mV

Kit includes Components, PC board, Transf., Fuse Pilot Light
Nothing else to buy: **\$5.50**

TTL

- 7400 - .16
- 7402 - .16
- 7404 - .16
- 7406 - .24
- 7408 - .16
- 7410 - .16
- 7413 - .49
- 7420 - .16
- 7427 - .24
- 7430 - .16
- 7437 - .39
- 7438 - .35
- 7440 - .16
- 7442 - .69
- 7447 - .89
- 7448 - .89
- 7453 - .16
- 7473 - .37
- 7474 - .37
- 7475 - .65
- 7476 - .39
- 7483 - .85
- 7490 - .69
- 7492 - .75
- 7493 - .75
- 7495 - .75
- 7496 - .75
- 74121 - .38
- 74123 - .75
- 74151 - .75
- 74153 - .89
- 74154 - .95
- 74161 - .99
- 74163 - 1.19
- 74164 - 1.89
- 74165 - 1.49
- 74174 - 1.29
- 74175 - 1.39
- 74181 - 2.75
- 74192 - 1.25
- 74193 - 1.25
- 74195 - .79
- 74197 - .79

CMOS

- CD4000 - .24
- CD4001 - .24
- CD4002 - .24
- CD4006 - 1.49
- CD4007 - .24
- CD4008 - 1.15
- CD4009 - .59
- CD4010 - .55
- CD4011 - .24
- CD4012 - .24
- CD4013 - .59
- CD4014 - 1.49
- CD4015 - 1.19
- CD4016 - .59
- CD4017 - 1.29
- CD4018 - 1.49
- CD4019 - .59
- CD4020 - 1.59
- CD4021 - 1.49
- CD4022 - 1.19
- CD4023 - .24
- CD4024 - .99
- CD4025 - .24
- CD4026 - 1.49
- CD4027 - .59
- CD4028 - .99
- CD4029 - 1.39
- CD4030 - .49
- CD4032 - .24
- CD4033 - 1.49
- CD4034 - 3.25
- CD4035 - 1.39
- CD4037 - 4.50
- CD4040 - 1.59
- CD4041 - .89
- CD4042 - .79
- CD4043 - .80
- CD4044 - .59
- CD4047 - .59
- CD4049 - .59
- CD4050 - .59
- CD4066 - .99
- CD4077 - .39
- 74C02 - .29
- 74C04 - .29
- 74C107 - 1.29

\$ DOLLAR DAYS

FORD SOLID STATE MODULES

Module contains 2 transistors plus other components. Used as audio pre amps. With specs 4/\$1

TANTALUM CAPS

4.7 MFD 10VDC. Axial. 10/\$1

ELECTROLYTIC CAPS

220 MFD 25 VDC. PC type 5/\$1

DUAL ELECTROLYTIC CAPS

1500 MFD + 2000 MFD 30VDC. Metal can, twist lock. 2/\$1

CERAMIC DISC CAPS

.01 MFD 50 VDC 20/\$1
68 MFD 50 VDC 20/\$1

12 VDC REED RELAY

Coil is 500 OHM. SPST-NO. Sub-mini. EA. \$1

PUSH BUTTON SWITCHES

Miniature momentary switches 4/\$1

POLAROID FILTERS

Pale green in color. 2.3 x 12 in. Use with various readouts 2/\$1

TRANSFORMER SPECIAL NO. 1

Mini. size. 8 VAC 400 MA under load \$1



CPU

- 8008 8 bit parallel CPU 19.50
- 2102 1K Static RAM for 8008 2.25
- MM5203 2K UV erasable PROM 12.25

LED DRIVERS

- 75491 Seg. .35
- 75492 Dig. .45

6 Function Calculator Chip
Chip No. 7020 with direct segment drive. 8 digit.

Priced to sell: **\$2.25**

TRANSISTORS

- 2N3055 NPN 115W TO3 Power 0.85
- RCA200V 115W TO5 Power NPN 1.25
- GE D40C1 NPN Parl. Cut Lead 0.25
- 2N4443 SCR 400V 8Amp TO220 0.65
- 2N2222 NPN Gen. Ampl. 0.20
- 2N3904 NPN Driver 0.15
- 2N3906 PNP Complim. 2N3904 0.15
- 2N4400 NPN Low level noise 0.20
- 2N5401 PNP Nixie driver 0.25

GE Transistor Assortment
TO98 cased Darling., SCRs, NPN, PNP, etc. Tests show very high yield.

- 50 for \$0.95
- 100 for \$1.75
- 300 for \$5.00

Satisfaction Guaranteed.

LIGHTS

MUSIC
60 Watt COLOR ORGAN

Completely self-contained unit, with 120 volt power cord included.

\$1.50

TTL BOARDS

MEMOREX computer boards with TTL's Diodes and Transistors, etc.

5 Boards containing 150-250 IC's.

\$3.95

FM Transformer Ast.

Includes FORD 19 KHZ, 38 KHZ, Osc. coils, etc. Used in AM FM car radios. All new 10 PC. ASSMT.

\$1.00

DIODES

- 1N4004 400PIV 15 for 1.00
- 1N4007 1000PIV 10 for 1.00
- 1N746 3.3Zen. 4 for 1.00
- 1N4148 Switch 20 for 1.00



LINEARS

- 555 Timer Mini dip. 0.45
- 8038 Functional generator 4.25
- RCA 3043 FM, IF, Aud. Preamp. 1.20
- 565 Phase Lock Loop 0.95
- 567V Tone Decoder 1.50
- LM723 Pos. Volt. Reg. 0.55
- LM309 5v. lamp Reg. 1.10
- LM741 Operational Amp. 0.25

NEW MANAGEMENT!

- Free Postage
- No Minimum Order
- 48 Hour Service
- 24 Hour Phone Service

WE ARE EAGER TO SERVE YOU!



ALTAJ ELECTRONICS

P.O. Box 38544R, Dallas, Texas 75238

TERMS: Check or money order. No COD.

Telephone (214) 278-3561

Texas Residents Add 5%



Circle 110 on reader service card

Integrated Circuits

7400 TTL	17	SN74LS170N	2.73
SN7400N	19	SN74LS192N	2.10
SN7404N	17	SN74LS197N	1.26
SN7408N	23	SN74LS202N	1.98
SN7410N	17	SN74LS290N	1.05
SN7416N	39	SN74LS670N	3.15
SN7420N	17		
SN7430N	17		
SN7438N	37	8200 TTL	
SN7440N	17	NB890N	1.88
SN7447N	78	NB234N	1.10
SN7447AN	78	NB267N	1.48
SN7451N	17	NB855N	1.13
SN7459N	17		
SN7474N	39	CA3018	1.00
SN7475N	69	CA3026	1.00
SN7489N	3.00	CA3045	90
SN7493N	65	CA3046	95
SN74107N	39	CA3047	90
SN74121N	49	CA3054	1.00
SN74145N	89	CA3082	1.90
SN74150N	95	CA3089	2.25
SN74154N	1.10	LM701AN	35
SN74157N	1.15	LM301AH	35
SN74161N	1.35	LM307N	35
SN74162N	1.35	LM308N	89
SN74163N	1.35	LM309K	1.25
SN74164N	1.45	LM311H	90
SN74166N	1.35	LM339N	1.55
SN74174N	1.40	LM350N	1.00
SN74175N	1.10	LM351N	60
SN74181N	3.55	LM380N	1.25
SN74190N	1.25	LM710N	65
SN74195N	1.15	LM723N	44
SN74198N	2.20	LM733N	89
SN74251N	2.50	LM741N	35
SN74299N	1.65	LM7303N	82
		LM2111N	1.95
		LM3900N	55
		MC1458V	59
74LS00 TTL	27	NE540L	5.00
SN74LS00N	29	NE550N	65
SN74LS08N	27	NE553B	2.30
SN74LS20N	27	NE555V	43
SN74LS38N	42	NE566A	1.00
SN74LS37AN	32	NE566A	1.95
SN74LS50N	94	NE567V	1.85
SN74LS50AN	94	NE567V	1.75
SN74LS593N	94	SN75450CN	47
SN74LS595N	1.30	SN75451CN	39
SN74LS107N	42	SN75452CN	39
SN74LS132N	1.50	SN75453CN	28
SN74LS151N	1.28	SN75454CN	37
SN74LS157N	1.35		
SN74LS160N	1.96		

TERMS:
\$5.00 min. order U.S. funds.
Calif. residents add 6% tax.



Same Day Shipment
First line parts only, guaranteed satisfaction.
Broad line of IC's and other components at low factory prices. Try us. You'll like the quality and service.


CMOS	25	8	24	CLOCKS	3.60
CD4000	25	14	29	MM5312	4.80
CD4011	25	16	32	MM5313	3.60
CD4012	25	16	32	MM5314	3.30
CD4013	75			MM5316	4.35
CD4017	2.00			MM5375A	4.80
CD4020	2.30			CT701	5.80
CD4027	85	14	24	MM7370	4.25
CD4049	62	16	25		
CD4050	62	18	30	DISPLAY LEADS	
		14	37	MAN1	1.90
		24	42	MAN2	30
		36	48	MAN3	1.95
		36	48	MAN7	1.35
		40	1.30	MAN72	1.95
				MAN74	1.35
				DL707	1.35
				DL727	2.35
				DL747	1.80

FREE—
Send for your copy of our 1976 Quest Catalog.

IC Update Master
1976 integrated circuit data manual with free quarterly updates. Complete IC data from all manufacturers devices. **14,000 cross references.** Everything you need to select IC's in one hardbound manual **\$30.00 complete with Update service.**
Money Back Guaranteed if not satisfied within first week

Digital Clock Kit \$12.95
6 digit large LED readout.
Add \$1.50 for transformer and \$3.00 for PC board.
A tremendous value!

Freedom to the Altair!

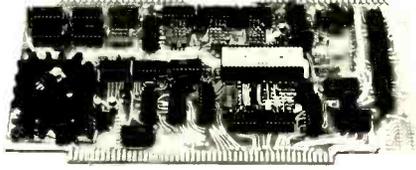

This single, versatile card could very possibly meet all the input/output needs of your 8800 system. Our 3P+S has two 8-bit parallel I/O ports, with full handshaking logic, and a serial I/O, with a data rate that can be set between 35 and 9600 Baud. Give your system the freedom to simultaneously interface such devices as a teletype, a TV typewriter, a modem, plus one more parallel device. Our 59 pg. detailed and descriptive owner's manual is \$4.00, fully refundable should you purchase the 3P+S. Kit Price, \$125.

Write Us. For details on our other compatible 8800 plug-in modules.

D Processor Technology
6200-G Hollis Street
Emeryville, CA 94608

Circle 112 on Reader Service Card

Circle 113 on Reader Service Card

CB SPECIALS—R.F. DRIVERS—R.F. POWER OUTPUTS—FETS

2SC481	1.85	2SC767	15.75	2SC866	5.85	2SC1449-1	1.60	40081	1.50
2SC482	1.75	2SC773	.85	2SC1013	1.50	2SC1475	1.50	40082	3.00
2SC495	1.10	2SC774	1.75	2SC1014	1.50	2SC1678	5.50	SK3068	4.85
2SC502	3.75	2SC775	2.75	2SC1017	1.50	2SC1679	4.75	SK3046	2.15
2SC517	4.75	2SC776	3.00	2SC1018	1.50	2SC1728	2.15	SK3047	3.75
2SC614	3.80	2SC777	4.75	2SC1173	1.25	2SC1760	2.15	SK2095	3.50
2SC615	3.90	2SC778	3.25	2SC1226A	1.25	2SC1816	5.50	SK3048	3.25
2SC616	4.15	2SC797	2.50	2SC1237	4.50	2SC1908	7.70	SK3054	1.25
2SC617	4.25	2SC798	3.10	2SC1239	3.50	2SC1957	1.50		
2SC699	4.75	2SC781	3.00	2SC1243	1.50	2SF8	3.00	2SK19	1.75
2SC710	.70	2SC789	1.00	2SC1306	4.75	HEP-S 3001	3.25	2SK30	1.00
2SC711	.70	2SC796	3.15	2SC1306-1	4.90	2SD235	1.25	2SK33	1.20
2SC735	.70	2SC799	4.25	2SC1307	5.75	MRF8004	3.00		
2SC756	3.00	2SC802	3.75	2SC1307-1	6.00	4004	3.00	3SK40	2.75
2SC765	9.50	2SC803	4.00	2SC1377	5.50	4005	3.00	3SK45	2.75
2SC766	10.15	2SC839	.85	2SC1449	1.30	40080	1.25	3SK49	2.75

JAPANESE TRANSISTORS

2SA52	.60	2SB187	.60	2SC458	.70	2SC815	.75	2SC1569	1.25
2SA316	.75	2SB235	1.75	2SC460	.70	2SC828	.75	2SC1756	1.25
2SA473	.75	2SB303	.65	2SC478	.80	2SC829	.75		
2SA483	1.95	2SB324	1.00	2SC491	2.50	2SC830	1.60	2SD30	.95
2SA489	.80	2SB337	2.10	2SC497	1.60	2SC839	.65	2SD45	2.00
2SA490	.70	2SB367	1.60	2SC515	8.00	2SC945	.85	2SD65	.75
2SA505	.70	2SB370	.65	2SC535	.75	2SC1010	.80	2SD68	.90
2SA564	.50	2SB405	.85	2SC536	.65	2SC1012	.80	2SD72	1.00
2SA628	.65	2SB407	1.65	2SC537	.70	2SC1051	2.50	2SD88	1.50
2SA643	.85	2SB415	.85	2SC560	2.50	2SC1061	1.65	2SD151	2.25
2SA647	2.75	2SB461	1.25	2SC605	1.00	2SC1079	3.75	2SD170	2.00
2SA673	.85	2SB463	1.65	2SC620	.80	2SC1096	1.20	2SD180	2.75
2SA679	3.75	2SB471	1.75	2SC627	1.75	2SC1098	1.15	2SD201	1.95
2SA682	.85	2SB474	1.50	2SC642	3.50	2SC1115	2.75	2SD218	4.75
2SA699	1.30	2SB476	1.25	2SC643	3.75	2SC1166	.70	2SD300	2.50
2SA699A	1.75	2SB481	2.10	2SC644	.70	2SC1170	4.00	2SD313	1.10
2SA705	.55	2SB492	1.25	2SC681	2.50	2SC1172B	4.25	2SD315	.75
2SA815	.85	2SB495	.95	2SC684	2.10	2SC1209	.55	2SD318	.95
2SA816	.85	2SB507	.90	2SC687	2.50	2SC1213	.75	2SD341	.95
		2SB511	.70	2SC696	2.35	2SC1226	1.25	2SD350	3.25
				2SC712	.70	2SC1243	1.50	2SD352	.80
2SB22	.65			2SC713	.70	2SC1293	.85	2SD380	5.70
2SB54	.70	2SC206	1.00	2SC732	.70	2SC1308	4.75	2SD389	.90
2SB56	.70	2SC240	1.00	2SC733	.70	2SC1347	.80	2SD390	.75
2SB77	.75	2SC261	.65	2SC739	.70	2SC1383	.75	2SD437	5.50
2SB128	2.25	2SC291	.65	2SC739	.70	2SC1383	.75		
2SB135	.95	2SC320	2.00	2SC715	1.75	2SC1409	1.25		
2SB137	4.50	2SC352	.75	2SC762	1.90	2SC1410	1.25		
2SB172	.55	2SC353	.75	2SC783	1.00	2SC1447	1.25		
2SB175	.55	2SC371	.70	2SC784	.70	2SC1448	1.25		
2SB178	1.00	2SC372	.70	2SC785	1.00	2SC1507	1.25		
2SB186	.60	2SC394	.70	2SC793	2.50	2SC1509	1.25		

POWER-TRANSISTORS HIGH-VOLT. TV. TYPE

BU204	1300V	3.90	BU207	1300V	5.40	2SC1172B	1100V	4.25
BU205	1500V	4.70	BU208	1500V	6.25	2SC1308	1100V	4.95
BU206	1700V	5.90	2SC1170	1100V	4.00	2SC1325	1100V	4.95

OEM SPECIALS

1N270	.10	2N960	.55	2N2219A	.30	2N2913	.75	2N3740	1.00	2N4401	.20
1N914	.10	2N962	.40	2N2221	.25	2N2914	1.20	2N3771	1.75	2N4402	.20
		2N967	.50	2N2221A	.30	2N3916A	3.65	2N3772	1.90	2N4403	.20
		2N173	1.75	2N2222	.25	2N3919	.50	2N3773	3.00	2N4409	.20
		2N178	.90	2N2222A	.30	2N3953	.30	2N3819	.32	2N4410	.25
		2N2327A	1.15	2N2270	.40	2N3954	.70	2N3823	.70	2N4416	.75
		2N334	1.20	2N2322	1.00	2N3955	.75	2N3856	.20	2N4441	.85
		2N336	.90	2N2323	1.00	2N3957	1.00	2N3866	.85	2N4442	.90
		2N338A	1.05	2N2324	1.35	2N3963	3.40	2N3903	.20	2N4443	1.20
		2N398B	.90	2N2325	2.00	2N3964	.50	2N3904	.20	2N4852	.55
		2N404	.30	2N2326	2.85	2N3975	6.50	2N3905	.20	2N5061	.30
		2N443	1.75	2N2327	3.80	2N3993	.20	2N3906	.25	2N5064	.50
		2N456	1.10	2N2328	4.20	2N3994	.17	2N3925	3.75	2N5130	.20
		2N501A	3.00	2N2329	4.75	2N3414	.17	2N3954	3.50	2N5133	.15
		2N508A	.45	2N2368	.25	2N3415	.18	2N3954A	3.75	2N5138	.15
		2N555	.45	2N2369	.25</						

S. D. SALES CO. P. O. BOX 28810 DALLAS, TEXAS 75228

ALARM CLOCK KIT SIX DIGIT LED

Thousands of hobbyists have bought and built our original clock kit and were completely satisfied. But we have received many requests for an alarm clock kit with the same value and quality that you have come to expect from S.D. So, here it is!

THE KIT INCLUDES:

- 1 Mostek 50252 Alarm Clock Chip
- 6 Hewlett Packard .30 in. common cathode readouts.
- 15 NPN Driver Transistors
- 1 Etched and Drilled P.C. Board set
- 1 Step Down Transformer
- 2 Switches for time set
- 2 Slide Switches for alarm set and enable
- 1 Filter Cap
- 4 1N4002 Rectifiers
- 1 1N914 Diode
- 1 .01 Disc Cap
- 15 Resistors
- 1 Speaker for alarm
- 1 LED lamp for PM indicator.

\$16.50
(COMPLETE KIT)

Why pay MORE MONEY for our competitor's clock that has LESS DIGITS that are SMALLER in size?

Please take note that we use only first run parts in our kits and include ALL the necessary parts. Not like some of our competitors who use retested readouts and chips or who may not even include switches in their kits.

60 Hz. Crystal Time Base FOR DIGITAL CLOCKS \$5.95 S. D. SALES EXCLUSIVE!

The kit you have been waiting for is here NOW, and at an unbelievable price! Thanks to S.D. Sales you can turn that digital clock of yours into a superbly accurate, DC operated, time piece.

KIT FEATURES:

- A. 60 Hz output with accuracy comparable to a digital watch.
- B. Directly interfaces with all MOS clock chips.
- C. Super low power consumption (1.5 Ma typ.)
- D. Uses latest MOS 17 stage divider IC.
- E. Eliminates forever the problem of AC line glitches.
- F. Perfect for cars, boats, campers, or even for portable clocks at ham field days.
- G. Small size, can be used in existing enclosures.

Kit includes crystal, divider IC, P.C. Board plus all other necessary parts and specs.

BUY TWO FOR \$10.00

2102 1K RAM's - 8 FOR \$12.95

New units — We bought a load on a super deal, hence this fantastic price.
Units tested for 500NS Speed.

INTEL 1702A 2K ERASEABLE PROM'S \$6.95

We tell it like it is. We could have said these were factory new, but here is the straight scoop. We bought a load of new computer gear that contained a quantity of 1702A's in sockets. We carefully removed the parts, verified their quality, and are offering them on one heck of a deal. First come, first served. Satisfaction guaranteed.

MV-50 TYPE LED's

by LITRONIX
10 for \$1
Factory Prime!

3 DIGIT LED ARRAY — 75c

by LITRONIX
DL33MMB, 3 MAN-3 Size Readouts in one package. These are factory prime, not retested rejects as sold by others. compare this price! 75c 3 for \$2.

SALE ON CUT LEAD SEMICONDUCTORS

Leads were cut for PCB insertion. Still very useable.

1N914/1N4148	100/\$2
1N4002 1 Amp 100 PIV	40/\$1
1N4745A 16V 1W Zener	20/\$1
EN2222 NPN Transistor	25/\$1
EN2907 PNP Transistor	25/\$1
2N3904 NPN Driver Xstr.	25/\$1
2N3392 GE Pre-amp Xstr.	25/\$1
C103Y SCR, 800MA, 60V.	10/\$1

ALL NEW.
UNUSED.
SOME ARE
HOUSE #

SLIDE SWITCH ASSORTMENT

Our best seller. Includes miniature and standard sizes, single and multi-position units. All new, first quality, name brand switches. Try one package and you'll reorder more. Special — 12 for \$1 (Assortment)



DISC CAP ASSORTMENT

PC leads. At least 10 different values. Includes .001, .01, .05, plus other standard values.
60 FOR \$1



UPRIGHT ELECTROLYTIC CAPS

47 mfd 35 V-10/\$1 68 mfd 25V-8/\$1
Brand new by Sprague. PC leads.

RESISTOR ASSORTMENT

1/4 W 5% and 10% . PC leads.
A good mix of values. 200/\$2



1000 MFD FILTER CAPS

Rated 35 WVDC. Upright style with P.C. leads. Most popular value for hobbyists. Compare at up to \$1.19 each from franchise type electronic parts stores. S.D. Special 4 for \$1



FAIRCHILD BIG LED READOUTS

A big .50 inch easy to read character. Now available in either common anode or common cathode. Take your pick. Super low current drain, only 5 MA per segment typical.

FND - 510	Common Anode	YOUR CHOICE
FND - 503	Common Cathode	\$1.50 ea. 6 for \$7.50

DUAL 741C (5558) OP AMPS

Mini dip. New house numbered units by RAYTHEON.
4 FOR \$1

FET'S BY TEXAS INSTRUMENTS — SPECIAL 5 for \$1

#TIS-75 but with an internal house number. TO-92 plastic case. N. Channel, Junction type FET.

We do not sell junk. Money back guarantee on every item. No C.O.D. Texas Res. add 5% tax. Postage rates went up 30%! Please add 5% of your total order to help cover shipping.

S. D. SALES CO.

P. O. BOX 28810
DALLAS, TEXAS 75228

Spring-Pac super SALE! Each pac only \$1.98

All pacs are first quality (no fallout), tested and guaranteed.

Memory pac 4 MMS016 MOS TO-5 512 BIT shift registers from NATIONAL - with data \$1.98	Flip-Flop pac 10 assorted Flip-Flops, Dual JK's, RST's, and low power FF's, with data \$1.98	Comparator pac 5 assorted DIP's--LM311, 710, 711, with data \$1.98
TTL Gates 15 assorted DIP's 7400 series-7420, 7430, 7440, etc...All prime, marked parts, with data \$1.98	LED pac 10 assorted discrete LED's-green, red, and infra-red, with data. \$1.98	Transistor pac 40 assorted TO-92 plastic transistors--PNP's and NPN's, mostly Fairchild house marked. \$1.98
Regulators 4 LM723 DIP variable regulators, 2-40V, with data \$1.98	Diodes 100 Germanium computer signal diodes with leads trimmed for PCB mounting. \$1.98	Resistors 100 1/2 watt 5% resistors of any single standard value from 2.7 ohm to 1M ohm \$1.98
Linear pac 8 assorted linears in mini-DIP or TO-5+741 op amp, LM307 op amp, LM 703 RF-IF amp, with data and circuits \$1.98	DIP RC Network 50 assorted 14 and 16 pin IC packages containing precision resistors and capacitors-no data available \$1.98	Switches 8 SPST momentary contact push button N.O. Red button fits in approx. 1/4" panel, with lock washer and mounting nut. \$1.98

LED Display pac
2 DL33 - 3 digits each, approximately .1" magnified digits in a 12 pin DIP, with data **\$1.98**

Buy 5 pacs for \$9.90 and pic-a-pac for \$10

The above are special offerings from Babylon Electronics, and will be shipped third class. See bottom of ad for ordering instructions.

Specials

DIP TRIMMER
-12 turn trim pots which plug into a DIP socket
-5K and 200K
-1/4" x 1/4" x 1/4"
-4 leads spaced .3" x .2"

Each \$.65 10 for \$4.95

25K Trimmer
Printed Circuit Board Type
Each \$.20
10 for \$1.50

TRANSISTOR
2N3904 - HEF736
TO92 PLASTIC - NPN
300 MW - 60V - 8100-300
NEW - FAIRCHILD - MARKED
EACH \$.15 10 FOR \$1.00

1 AMP RECTIFIER
1N4007 SALE EACH \$.13
10/ \$1.00

NPN TO3 POWER TRANSISTORS
2N3055: PD-115W; VCE-60V;
HFE-50; FT-30K.
Each \$.90 10 for \$6.95
410 (RCA) 200V-10A
2N3772 70V-30A (max.)
Each \$1.75 10 for \$15.00

CMOS

CD4001	.29	CD4023	.29
CD4002	.29	CD4024	1.50
CD4009	.59	CD4025	.34
CD4010	.59	CD4030	.65
CD4011	.29	74C20	.65
CD4013	.69	74C42	2.00
CD4015	1.98	74C157	2.50
CD4016	.69	74C195	1.00
CD4019	.69		

2102-2 MOS
1024 BIT MEMORY
14 PIN DIP ON CARRIERS
Each \$3.00 10 for \$27.00

1 Amp OP AMP
Similar to National LH0021
General purpose operational amplifier in a TO-3 package. Capable of large output currents.
\$4.50 each 5/\$20.00

Capacitors
PCB vertical mount electrolytic capacitors.
2" long, 3/4" dia.
59c ea. 10 for \$5.00

More Memories
1702-2048 BIT PROM. 2K static units. Ultra-violet light erasable. EACH \$9.95

SPACE AGE CLOCK KIT
Instructions & parts - 12 or 24 hour format.
Four digit clock kit includes all parts for complete clock: 3 1/2" x 2":
-FND 70 readouts
-MMS314 clock chip & all transistors, etc.
-extruded aluminum case
-cord with transformer plug

\$16.95

POTTER BRUMFIELD
Type KHP Relay
4 PDT 3A Contacts

Your BANKAMERICARD welcome here

24V DC . \$1.50 (650 coil)
120V AC. \$1.75 (10.5 MA coil)

Mail orders to: **BABYLON ELECTRONICS**
P.O. Box 41778 Sacramento, CA 95841
Phone (916) 334-2161
TWX # 910-367-3521

Send a stamp for our flyer listing more money-saving bargains!

All IC's are new and fully tested. Leads are plated with gold or solder. Due to increased costs, orders under \$7.00 add \$1.00 postage and handling. Residents of California add sales tax. Orders are shipped within 2 workdays - kits are shipped within 10 days. \$10 minimum order on C.O.D.'s.

MONEY BACK GUARANTEE ON ALL GOODS!

NEW! Low-cost, full feature 4kx8 kit!

ECONORAM™ \$89.95

Other manufacturers have picked up on our buffered addresses and data outputs...and they've started using hysteresis on the data in lines, too...and static operation...but we've got the recipe on keeping the price down. ALTAIR 8800 PLUG-IN COMPATIBLE. Onboard regulation, sockets for all ICs, lots of bypassing, low power consumption (1A typ), double sided, industrial quality board, instructions. Like Bill says, "the only thing we skimped on was the price!"

Software in a kit for 8080s: \$159.95

4kx8 at a bargain: NAKED RAM \$79.95

The "ECONORAM" is 4k bytes of erasable ROM, pre-programmed with editor, assembler, and monitor routines for the 8080. Or order the board unprogrammed...and put your own software into a memory that does not forget. LOW POWER OPERATION...ALTAIR 8800 PLUG-IN COMPATIBLE. Comes with quality parts, instructions, and software listing. Listing available separately for \$2.95.

Microcomputer Power Supply
\$44.95 brings you 5V at 5 Amps, +12V at 1/2A, -12V at 1/2A, and an adjustable negative bias supply. Foldback current limiting and crowbar overvoltage protection. 1% regulation on the 5 volt line guaranteed. Same size as the JOLT power supply card. With chassis & hardware but no line cord.
For 117VAC, 60 Hz.
ADD 8 LBS SHIPPING

Do you know how to get our FLYER? It's EASY!

GODBOUT CIRCLE THE READER SERVICE # BELOW.

BILL GODBOUT ELECTRONICSBOX 2355**OAKLAND AIRPORT, CA 94614.**
Terms: Add 50¢ to orders under \$10. Add shipping where shown. Cal res add tax. Mastercharge®/Bankamericard®: (415) 357-7007, 24 hrs.

Circle 127 on reader service card

ELECTRONIC STROBE CIRCUIT BOARD

This circuit board is the heart of a portable electronic strobe, made by a well known camera maker. It has a DC to DC converter to charge a cap to 370V from a 3v battery, and the trigger transformer to fire the strobe tube. It is complete except for the tube, storage cap & battery. The boards that we have are pre-inspection boards; that is, we find that about 50% are operable as-is. The others just have solder splashes to be removed or bent leads. We provide the PC layout and schematic.

This board is the basis for a portable strobe light, using the strobe tube below. By adding the Light Activated SCR, below, it can be used as a slave strobe. By using a smaller storage cap, a strobe-tach for psychedelic effects can be made, with a max. flash rate of about 20 per second. Also handy for a portable emergency light. It is a very compact 2" x 2" x 1" high.

STOCK NO. R6311 \$3.95 each, 2/6.00

FLASH TUBE

A Krypton/Xenon flash tube made by Honeywell for use in their portable strobe units. A perfect mate for the PC board above. Energy input: 50 watt-sec, Max flash voltage: 400v, trigger voltage: 4kv, life: 100,000 flashes. 2" long, .18" diameter.

STOCK NO. R9244 \$2.50 each, 2/4.50

SPECIAL! flash tube & PC board \$6.00 a set, 2 sets/\$11.00

LIGHT ACTIVATED SCR, triggered by light falling on a lens which acts as the gate. 200v rating. Use with above board or any flash to make a slave strobe. With reprint from PE/ Elec. Exp. Handbook on "Light Activated Slave Strobe Trigger".

STOCK NO. R4118 \$1.50 each, 2/2.50
LASCR, flash tube, & PC board \$7.50/set, 2 sets/14.00

Send for our free catalog. Phone orders welcome. MASTERCARD & BANKAMERICARD accepted. ALL numbers must be included to process order. Minimum order \$5. Include sufficient postage; excess will be refunded.

DELTA ELECTRONICS CO.
P.O. BOX 2, AMESBURY, MASS. 01913
Phone (617) 388-4705

Circle 117 on reader service card

RADIO-ELECTRONICS

Poly Pak's BUY 'EM FROM THE "BARREL" AND SAVE!

100'S OF BARRELS PURCHASED!



THE BIGGEST INFLATION-FIGHTING VALUE EVER! TEST 'EM YOURSELF 'N SAVE!

For the first time anywhere, Poly Pak merchandisers introduce a new way in buying the economical way. Raw stock from the "barrel". Remember

the "good ole days"? They're back again. The same way merchandisers throughout the United States buy from various factories... their over-

runs in barrels. Poly Pak has done the same. Therefore you are getting the same type of material as the RE-TESTERS DO!

NEVER BEFORE! U-TEST EM-N-CHOOSE EM IC'S

Order by Cat. No. and Type No.

7400 SERIES

Cat. No. SR3170

Type	Sale
SN7400	50 for \$1.98
SN7401	50 for 1.98
SN7402	50 for 1.98
SN7403	50 for 1.98
SN7500	50 for 1.98

MONEY BACK GUARANTEE PER PAK!

NEW FACTORY ARRANGEMENTS! Why mix 'em? They decided to "bag" same types, then throw bags into barrels. WE DON'T TEST! You test 'em yourself. Buy types of your choice at BAREIL PRICES!

LINEARS

Cat. No. SR 3171

LM300H	30 for \$1.98
LM307V	50 for 1.98
LM308V	30 for 1.98
LM311V	50 for 1.98
LM315V*	30 for 1.98
LM319V	30 for 1.98
LM324N	30 for 1.98
LM339N	30 for 1.98
LM351V	30 for 1.98
LM356V	30 for 1.98
LM377N	40 for 1.98
LM380N	30 for 1.98
LM390N	30 for 1.98
LM381N	30 for 1.98
LM382N	30 for 1.98
LM385V	30 for 1.98
LM386V	30 for 1.98
LM387N	30 for 1.98
LM388N	30 for 1.98
LM389N	30 for 1.98
LM500N	30 for 1.98

BARREL KIT #1
SN7400 DIP IC'S
75 for \$1.98
Marked 14 and/or with 16 pin dips, may include gates, registers, flip flops, counters. Who knew! (MARS) TESTED SATISFACTION!
Cat.No. SR2415 Untested.

BARREL KIT #2
LINEAR OP AMPS, DIPS
75 for \$1.98
Untested
May include 709's, 741's, 703's, 680 series, 656 includes marked and unmarked.
Cat.No. SR2416

BARREL KIT #3
1N4148/814 SWITCHING DIODES
100 for \$1.98
You never saw this before. Imagine famous switching diodes at these prices!
Cat.No. SR2418 Untested.

BARREL KIT #4
"4000" RECTIFIERS
100 for \$1.98
Untested.
These are the famous micro miniature rectifiers of the 1N4000 series. May include 25, 50, 100, 200, 400, 600, 800 and 1000 volters.
Cat.No. SR2417

BARREL KIT #5
SCRS, TRIACS, QUADRACS
40 for \$1.98
All the famous plastic power tab type raw factory stock! All the 10 amp types.
Cat.No. SR2419 Untested.

BARREL KIT #7
VOLUME CONTROL BONANZAI
40 for \$1.98
100% good
Singles, duals, variety of values, styles, big ones - small ones.
Cat.No. SR2421

BARREL KIT #8
SUBMINIATURE IF TRANSFORMERS
100 for \$1.98
100% good.
Amazing, includes 45Ks, ops, antenna, who knows? From transistor radio manufacturers.
Cat.No. SR2422

BARREL KIT #10
ROMS-REGISTERS
50 for \$1.98
Untested
28 to 40 pin devices, marked, internal factory numbers.
Cat.No. SR2424

BARREL KIT #12
POWER TAB TRANSISTORS
40 for \$1.98
Untested.
PNP, plastic TO220 type. Assorted 2N numbers.
Cat.No. SR2426

BARREL KIT #13
RESISTOR NETWORKS
60 for \$1.98
Untested.
By Corning Glass, in 14-pin dip packs.
Cat.No. SR2427

BARREL KIT #15
MOSFET TRANSISTORS
60 for \$1.98
All 4 leaders. TO-18 case. Includes UHF transistors too!
Cat.No. SR2429

BARREL KIT #17
LINEAR & 7400 DIPS
100 for \$1.98
Untested.
Marked/unmarked, internal numbers of raw factory stock.
Cat.No. SR2431

BARREL KIT #19
DIPPED MYLARS
60 for \$1.98
100% good.
Finest capacitors made, shiny finish. Imagine factory dumping 'em in barrels.
Cat.No. SR2597 100% good

BARREL KIT #20
LONG LEAD DISCS
150 for \$1.98
Factory distributor stock "nucleon sale" prime, marked poly. Long leads.
Cat.No. SR2598 100% good

BARREL KIT #25
METAL CAN TRANSISTORS
100 for \$1.98
Untested.
Includes TO-5, TO-18, etc., assorted 2N numbers, unmarked etc.
Cat.No. SR2603

BARREL KIT #26
PLASTIC TRANSISTORS
100 for \$1.98
Untested.
Type TO-92 (TO-18), all manufacturers, variety of 2N's.
Cat.No. SR2604

BARREL KIT #30
PREFORMED RESISTORS
250 for \$1.98
We got barrels of 1/4 and 1/2 watt resistors for you. You'll get even amount. 187's, 100's, 100's of 2N3505. We have 10 barrels.
Cat.No. SR2608 100% good

BARREL KIT #31
METALLIC RESISTORS
100 for \$1.98
100% good.
Made mostly by Corning, the finest resistor made. Mostly 1/2 watters, 1% to 5% tol., & a barrel of values.
Cat.No. SR2609

BARREL KIT #32
TRANSISTORS WITH A HOLE IN IT
50 for \$1.98
Untested.
Can't name factory but we bought barrels of 25 watters with mtz. hole in middle. PNP's and NPN's.
Cat.No. SR2610

BARREL KIT #35
NEON LAMPS
40 for \$1.98
100% good.
Famous NE-2's. All prime, but factory made millions and barreled 'em. Your advantage.
Cat.No. SR2613

BARREL KIT #36
GERMANIUM DIODES
200 for \$1.98
Untested.
Famous maker, popular item. Never grows old. But this is the way the RE-TESTERS buy 'em from the factories.
Cat.No. SR2614

BARREL KIT #37
1 AMP "BULLET" RECTIFIERS
100 for \$1.98
Untested.
Famous style, asst. voltages, silicon, axial, includes all types of voltages to 1KV.
Cat.No. SR2615

BARREL KIT #38
2 AMP RECTIFIERS
75 for \$1.98
Untested.
"CYLINDER" type, silicon. Micas, includes 2 voltages up to 1KV.
Cat.No. SR2616

BARREL KIT #39
2N3055 HOBBY TRANSISTORS
15 for \$1.98
100% good.
From factory to you, these are the best. We have 2N3055's. We have 10 barrels.
Cat.No. SR2617

BARREL KIT #40
PNP HIGH-POWER TRANSISTORS
20 for \$1.98
Popular germanium TO-3 case units, now available at "good ole barrel" prices.
Cat.No. SR2618 100% good

BARREL KIT #46
G.E. 3.5 WATT AMPLIFIERS
25 for \$1.98
Untested.
Hobby type, factory all-outs, we purchased them in barrels. These are unknowns.
Cat.No. SR2624

BARREL KIT #50
SIGNAL SILICON DIODES
200 for \$1.98
Includes many, many types of switching, signal silicon types, all axial leads. Some may be zeners.
Cat.No. SR2628

BARREL KIT #51
HOBBY OPTO COUPLERS
40 for \$1.98
We got 1,000's unknown both the sensor or transmitter may be good, or both. WE DON'T KNOW! We don't know the types, 1500' is 20% inclusion.
Cat.No. SR2629

BARREL KIT #52
DISCS!
500 for \$1.98
Cat.No. SR2630 100% good
The bargain of a lifetime! First time ever offered by Poly Pak for the economy-minded bargain hunter.

BARREL KIT #53
JUMBO RESISTOR PAK
100-pc. \$1.98
Cat.No. SR2721
Assortment of metal films, precision carbon, metal oxide powders, from 1/8 watt to 7 watts. Color coded & 100% good. Worth \$10.

BARREL KIT #58
SLIDE SWITCHES
30 for \$1.98
All shapes, sizes, spat, dpdt, momentary, etc. tremendous shop pak for 100's of switching projects.
Cat.No. SR2726 100% good

BARREL KIT #59
POWER TRANSISTORS
40 for \$1.98
15 watt Bendix B-5000 pellet transistors, non, all good, purchased from a pretester, have millions at 100% good.
Cat.No. SR2727

BARREL KIT #60
DTL'S IC'S
75 for \$1.98
Untested.
This is prime barrel material. Who wants DTL's? 930, 936, 940's. Your gain is our loss. They're marked too.
Cat.No. SR2728

BARREL KIT #61
POLYSTYRENE CAPS
100 for \$1.98
Finest caps made. As a guarantee we bought 10 barrels from factory, mixed values, all good.
Cat.No. SR2729

BARREL KIT #65
MIXED READOUTS
15 for \$1.98
Factory returns - such numbers as MAN-4's, MAN-7's, MAN-3's, 11 barrels & no time to separate.
Cat.No. SR2733 Untested.

BARREL KIT #68
2 WATERERS
100 for \$1.98
100% good.
Nobody seems to want 'em! So many suppliers don't count, but throw 'em in the barrel. It's a 412 gold mine. All marked.
Cat.No. SR2735

BARREL KIT #71
CAPACITOR SPECIAL
100 pcs. \$1.98
Untested.
Emptied stockrooms into barrels of mylars, poly's, micas, maddis, plastics, ceramics, discs, etc. Nifty 100% good.
Cat.No. SR2738

BARREL KIT #73
TRANSISTOR ELECTROS
50 for \$1.98
It "bugs" us why the factories dump 'em in barrels. We don't wish to separate wide ass voltages & values up to 300 mV.
Cat.No. SR2747

BARREL KIT #75
400MW ZENERS
100 for \$1.98
Factory out of biz! Amazing offer. 6, 8, 10, 12 to 15V. You test. Hermetically sealed glass pak. Double plug.
Cat.No. SR2740

BARREL KIT #76
4-WATT ZENERS
100 for \$1.98
Untested.
Factory same as 400mw's. Never-to-see-again offer. 6, 8, 10, 12, 15V. under glass. Double plug.
Cat.No. SR2741

BARREL KIT #77
"BROWN" BODY TRANSISTORS
40 for \$1.98
Untested.
G-E 1-10 series, has hi-voltage. Datasheets, hi-current, npn's. Factory line discontinued. Power tabs.
Cat.No. SR2742 Untested.

BARREL KIT #78
"RED" BODY TRANSISTORS

VIDEO CAMERA KIT

A UNIQUE ALL SOLID STATE CAMERA KIT
FEATURING A... 100 X 100 BIT
SELF SCANNING CHARGED
COUPLED DEVICE

INCLUDES THE FOLLOWING
UNIQUE FEATURES...
FOUND IN FAR MORE
EXPENSIVE CAMERAS
IF AVAILABLE

- LOW VOLTAGE SUPPLY (OR BATTERIES) +3 AND +15 VOLTS
- SENSITIVE TO INFRARED AS WELL AS VISIBLE LIGHT
- MAY BE USED FOR SURVEILLANCE WITH AN IR LIGHT SOURCE
- EXCELLENT FOR STANDARD SURVEILLANCE WORK BECAUSE OF ITS LIGHT WEIGHT AND SMALL SIZE
- ALL COMPONENTS MOUNTED ON TWO PARALLEL 3" X 5" SINGLE SIDED BOARDS TOTAL WEIGHT UNDER 2 LBS.
- MAY BE WIRED BY PERSON WITH SOME TECHNICAL EXPERIENCE IN 4-8 HRS



SUPER UNBELIEVABLE
ONLY **\$225.00**

ADD \$2.00 POSTAGE AND HANDLING PLUS \$6.00 FOR ALL IC SOCKETS (Optional)

MAY BE USED WITH AMATEUR RADIO FOR VIDEO

USED FOR CHARACTER RECOGNITION FOR COMPUTERS WITH EXTERNAL CIRCUITS

MAY BE USED IN A VARIETY OF UNDERWATER, HIGH ALTITUDE, AND IN MAGNETIC ENVIRONMENT BECAUSE THERE IS NO HIGH VOLTAGE OR MAGNETIC DEFLECTION

WE SUPPLY ALL SEMICONDUCTORS, BOARDS, DATA SHEETS, DIAGRAMS, RESISTORS AND CAPACITORS

SORRY, WE DO NOT SUPPLY THE CASE, BATTERIES (OR SUPPLY THE LENSES (NOT SUPPLIED) DEPENDS UPON THE USE


F8 MICROPROCESSOR KIT

WE'VE GOT THE F8 MICROPROCESSOR KIT, ONE OF THE MOST ADVANCED MCU SYSTEMS ON THE MARKET TODAY FOR ONLY **\$179.00**

The three chip microprocessor system has the following advantages:

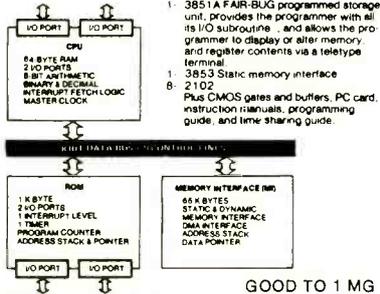- 1) Driven by +5 and +12 volt power supply
- 2) Two I/O ports on the CPU chip, AND ROM, making 32 bidirectional lines
- 3) 84 bytes of fast RAM scratchpad built into the CPU chip
- 4) A built in clock generator and power on reset built into the CPU chip
- 5) A programmable internal timer built into the ROM chip
- 6) 80% of the instructions are 1 byte
- 7) TTL/IO compatibility
- 8) consumes less than 300mw of power per chip
- 9) A local interrupt with automatic address vector
- 10) expandable to 64K bytes (21 or 81 of memory)
- 11) 20 mil loop & RS - 232 included.

The F8 kit has enough parts and instructions to demonstrate microprocessor programs up to 1K byte, and to debug those programs



- We supply:
- 1. 3850 CPU
 - 1. 3851A FAIR-BUG programmed storage unit, provides the programmer with all its I/O subroutines, and allows the programmer to display or alter memory, and register contents via a teletype terminal
 - 1. 2853 Static memory interface
 - 8. 2102 Plus CMOS gates and buffers, PC card, instruction manual, programming guide, and time sharing guide.

- 1. 1K BYTE 2 I/O PORTS 1 INTERRUPT LEVEL 1 TIMER PROGRAM COUNTER ADDRESS STACK & POINTER
- 64 KBYTES STATIC DYNAMIC STATE INTERFACE DATA INTERFACE ADDRESS STACK & POINTER DATA POINTER

GOOD TO 1 MG

PARTS! CORNELL TUBES!
FREE Send For FREE
CORNELL'S New Color Catalog
48 Pgs. New Items IN LOTS OF 100
4215 E. UNIVERSITY AVE. SAN DIEGO, CALIF. 92105

33¢ per tube
36¢ per tube
ORDER FREE IF NOT SHIPPED IN 24 HOURS!

PLANS & KITS

TV Ping Pong game. Plays through you set's antenna terminals: Plans \$3.25. ARS SYSTEMS, Box 61922, Sunnyvale, CA 94088

SOFTWARE! Software! and Interface kits can change your computer into a useful and enjoyable investment. Hundreds and hundreds of Dynamic Programs for the Businessman, Engineer and Game Enthusiast. Send \$1 for samples catalog. SRI, PO Drawer C. Marcy, NY 13403

AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning, Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE, Catalog \$1. Information Unlimited, Box 626, Lord Jeffery Court, Amherst, N.H. 03031.

DIAGRAMS, servicing material, most radio-television sets, \$2.50. Immediate shipment. BEITMAN, 1760 Balsam, Highland Park, IL 60035

COLOR bar generator kit \$39.95. 16 patterns. Plans \$5. WORKSHOP, Box 393R, Bethpage, NY 11714

ELECTRONIC kits for home or school project. Select from over 50 kits. Many under \$5.00. Send \$1.00 for catalog. Refundable with first order. GRAYMARK, 1751 McGaw Ave., Irvine, CA 92714

ELECTRONIC

MUSIC SYNTHESIS / ANALOG PROCESSING

- PLANS & KITS
- CIRCUIT THEORY
- INDUSTRIAL R&D TECHNIQUES
- PARTS & COMPONENTS

featuring STATE-OF-THE-ART technology, and professional-lab quality designs at LOW COST BUILD:

- Ultra wide range universal V C O
- Voltage controlled filters & amplifiers
- Jovstick controlled filters & taders
- plus MUCH MUCH MORE

Free Information... send self addressed, stamped envelope to

C F R ASSOCIATES

P O Box F Newton, N H 03858

"the oldest name in synthesis for the experimenter"

BUILD that electronic organ you always wanted at a price you can afford. Third edition of "Organ Builder's Guide," pictured product kit line, circuits, block diagrams, design rationale using IC divider and independent generators with diode keying. \$3.00 Postpaid. Also, free brochure on keyboards. DEVTRONIX ORGAN PRODUCTS, Dept. B, 5872 Amapola Drive, San Jose, CA 95129

ALTAIR 8800 OWNERS

Is your Altair:

- Slow to start-up
- Writing all 0's or 1's into memory
- Having troubles running BASIC

Our 'CPU Clock Fix-kit' may solve your problems. Good clock pulses are a must. Send for your kit today!
Only \$15 postpaid. Brochure available.

PARASITIC ENGINEERING
P.O. Box 6314, Albany, CA 94706

WANTED

QUICK cash... for electronic equipment, components, unused tubes. Send list now! BARRY, 512 Broadway, New York, NY 10012, 212 Walker 5-7000

GIVE YOUR FAIR SHARE THE UNITED WAY

TRANSISTOR SPECIALS

2N3585 NPN Si TO-66	\$.95
2N3772 NPN Si TO-3	\$ 1.80
2N4201 PNP Si TO-3	\$.85
2N5086 PNP Si TO-92	4/5 \$ 1.00
2N4898 PNP TO-66	\$.60
2N404 PNP GE TO-5	5/5 \$ 1.00
2N3919 NPN Si TO-3 RF	\$ 1.50
MPSA13 NPN Si TO-92	3/5 \$ 1.00
2N3767 NPN Si TO-66	\$.70
2N4222 NPN Si TO-18	5/5 \$ 1.00
2N3055 NPN Si TO-3	\$.80
2N3904 NPN Si TO-92	5/5 \$ 1.00
2N3906 PNP Si TO-92	5/5 \$ 1.00
2N5298 NPN Si TO-220	\$.50
2N6109 PNP Si TO-220	\$.55
2N3866 NPN Si TO-5	\$.75
2N4222 NPN Si TO-18	5/5 \$ 1.00
2N6517 NPN TO-92 S	3/5 \$ 1.00

C/MOS (DIODE CLAMPED)

74C02-.26	4013-.45	4028-.95
74C10-.30	4015-1.24	4029-1.20
4001-.24	4017-1.15	4030-.49
4002-.24	4018-1.24	4035-1.50
4006-1.35	4019-.50	4042-.75
4007-.24	4022-1.24	4046-2.75
4008-.50	4024-.95	4047-3.50
4010-.50	4025-.24	4050-.49
4011-.24	4026-1.90	4055-1.95
4012-.24	4027-.55	4066-1.00

LED READOUTS

FND 500-5" C C	\$ 1.75
HP 7740-3" C C	\$ 1.40
MAN-4-25" C C	\$ 1.20
MAN-7-3" C A	\$ 1.25
DL 747-6" C A	\$ 1.95
NS 33-3 dig. array	\$ 1.75

Full Wave Bridges

PRV	2A	6A	25A
200	95	1.25	2.00
400	1.15	1.50	3.00
800	1.35	1.75	4.00

CD 110 LINEAR 256 X BIT SELF SCANNING CHARGED COUPLED DEVICE **\$125.00**

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$ 6.90
Si 1020 G 20 WATTS	\$ 13.95
Si 1050 G 50 WATTS	\$ 24.95

LINEAR CIRCUITS

LM 309K 5V 1A REGULATOR	\$ 1.00
723 140+40V REGULATOR	\$.54
3011748 HI Per. Op. Amp	\$.28
320T5, 12, 15, OR 24V NEGATIVE REG	\$ 1.50
741A or 741C OP AMP	\$.31
709C OPER. AMP	\$.25
307 OP AMP	\$.25
CA 3047 HI PER OP AMP	\$.85
CA 3069 HI PER OP AMP	\$ 3.25
340T-5, 8, 12, 15, 18, 24V POS REG TO 220	\$ 1.20
101 OPER AMP HI PERFORMANCE	\$.75
LM 308 Oper. Amp. Low Power	\$ 1.05
747-DUAL 741	\$.85
555-DUAL TIMER	\$.95
537 PRECISION OP AMP	\$ 2.60
540-70W POWER DRIVER	\$ 2.60
LM 3900-QUAD OP AMP	\$.49
LM 324-QUAD 741	\$ 1.50
560-PHASE LOCK LOOP	\$ 2.50
561-PHASE LOCK LOOP	\$ 2.50
565-PHASE LOCK LOOP	\$ 1.80
566 FUNCTION GEN	\$ 2.50
567-TONE DECODER	\$ 1.50
LM 1310N FM STEREO DEMOD	\$ 2.75
8038 IC VOLTAGE CONT. OSC.	\$ 3.90
LM370-AGC SOUELCH AMP	\$ 1.15
555-2µs-2 HR TIMER	\$.53
553 QUAD TIMER	\$ 2.50
FCD 0-10V SOLATOR	\$.80
1458 DUAL OP AMP	\$.85
LM 380-2W AUDIO AMP	\$.80
LM 377-2W Stereo Audio Amp	\$ 2.50
LM 381-STEREO PREAMP	\$ 1.00
LM 382-DUAL AUDIO PREAMP	\$ 1.00
LM 311-HI PER COMPARTOR	\$.95
LM 319-Dual Hi-Speed Comp	\$ 1.10
LM 338-QUAD COMPARTOR	\$ 1.25

TRIACS

PRV	1A	10A	25A	15A	6A	35A
100	40	70	130	40	50	120
200	70	110	175	60	70	160
400	110	160	230	100	120	220
600	170	230	360	150	300	

SCR'S

Send \$25 for our catalog featuring Transistors and Rectifiers 145 Hampshire St. Cambridge, Mass
--

TANTULUM CAPACITORS

22UF 35V 5/51.00	6.8UF 35V 3/51.00
47UF 35V 5/51.00	33UF 25V \$.40
68UF 35V 5/51.00	30UF 6V \$ 51.00
2UF 35V 4/51.00	150UF 20V \$.50

CT7001 ALARM CLOCK CHIP \$5.75

FPA 711-7 LEVEL Diode Array Optical Text Readers \$5.95

NATIONAL MOS DEVICES

MM1402-3.20	MM5057-4.00
MM1403-3.20	MM5058-4.95
MM1404-2.50	MM5060-4.95
MM5013-7.75	MM5061-4.30
MM5016-3.50	MM5556-6.25
MM5017-4.75	MM5558-6.25
MM5055-4.00	MM5210-1.95
MM5056-4.00	MM5260-2.95

TTL IC SERIES

74L00-26	7476-35
7400-14	7480-48
7401-15	7483-75
7402-15	7485-105
7403-15	7486-34
7404-18	7480-49
7405-18	7487-49
7406-35	7482-49
7407-33	7483-49
7408-18	7485-74
7409-18	7486-79
7410-15	74107-34
7411-25	74121-38
7412-30	74123-74
7413-45	74125-54
7414-45	74126-54
7416-33	74150-92
7417-33	74151-69
7420-15	74153-79
7425-27	74154-105
7426-24	74157-105
7427-27	74157-75
7430-15	74161-95
7432-24	74164-110
7437-29	74165-110
7438-29	74173-135
7440-15	74175-95
7442-59	74177-75
7445-79	74181-230
7446-87	74192-110
7447-87	74193-110
7448-85	74194-115
7472-28	74195-74
7473-34	74196-95
7474-35	75324-1.75
7475-49	75491-1.10

ALCO MINATURE TOGGLE SWITCHES

MTA 106 SPDT	\$ 1.20
MTA 206 DPDT	\$ 1.70

INTEL 8080 CPU	\$37.50
8008 8 BIT MICRO PROCESSING CHIP (with Data Book)	\$19.00
2102-11024 BIT RAM	\$ 2.60
5202A UV PROM	\$12.50
MM5203 UV PROM	\$12.50
1702A UV PROM	\$12.50
5204-4K PROM	\$24.95
MINATURE MULTI-TURN TRIM POTS 100, 500, 5K, 10K, 25K, 50K, 100K, 200K	\$ 7.5 ea.
3/2.00	
MULTI-TURN TRIM POTS Similar to Bourne 3010 style 1/4", x 1/4", x 1/4", 50, 100, 1K, 10K, 50K ohms	\$1.50 ea.
3/84.00	
LIGHT ACTIVATED SCR's TO-18 200V 1A	\$1.75

PRINTED CIRCUIT BOARD

4 1/2" x 6" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched

5 \$ 60 ea.	5/82.20
VECTOR BOARD 1" SPACING 4 5/8" x 6 5/8" SHEET	\$ 1.50
4 WATT IR LASER DIODE	\$ 7.95
2N5460 P FET	\$.45
2N5457 N FET	\$.46
2N 4891 UJT	\$.45
TIS 43 UJT	\$.35
ER 900 TRIGGER DIODES	4/81.00
2N 6028 PNP UJT	\$.65

VERIPAC PC BOARD

This board is a 1/4" single sided paper epoxy board, 4 1/2" x 6 1/2", DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with busses for power supply connector. \$5.25

MY 5891 YELLOW-GREEN

BIPOLAR LED	\$ 1.25
MT-2 PHOTO TRANS.	\$.60
RED, YELLOW, GREEN OR AMBER LARGE LED's	ea. \$.20
14 PIN DIP SOCKETS	\$.35
16 PIN DIP SOCKETS	\$.36
MOLEX PINS.	1000/\$1.00
1000/\$8.00	
6 PIN MINI DIP SOCKETS	\$.30
10 PIN TO 5 TEFLON PC SOCKETS	\$.60
10 WATT ZENERS 3.9, 4.7, 12, 18 OR 22V	ea. \$.60
1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 OR 22V	ea. \$.25

Silicon Power Rectifiers

PRV	1A	3A	12A	50A	125A
100	.06	.14	.30	.80	
200	.07	.20	.35	1.15	4.25
400	.09	.25	.50	1.40	6.50
600	.11	.30	.70	1.80	8.50
800	.15	.35	.90	2.30	10.50
1000	.20	.45	1.10	2.75	12.50

REGULATED MODULAR POWER SUPPLIES

+ - 15VDC AT 100ma

115VAC INPUT	\$24.95
5VDC AT 1A, 115VAC INPUT	\$24.95
12VDC AT .5A	\$24.95
IN 4148 (IN914)	15/\$1.00
1103, 1024 bit RAM	\$2.75
NEC 6003 2048 bit RAM	\$6.00
1101 256 bit RAM	\$1.40
7469 RAM	\$2.30
7 POLE 1 THROW TO-5 MINATURE ROTARY SWITCH	\$.95

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage Minimum Order: \$5.00, COD'S \$20.00

SOLID STATE SALES

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

P O BOX 74 D
SOMERVILLE, MASS. 02143 TEL. (617) 547 4005

5% OFF ON ORDERS OVER \$50.00
10% OFF ON ORDERS OVER \$100.00
15% OFF ON ORDERS OVER \$250.00

MAY SPECIALS

TTL

7400	\$.14	7451	.17	74154	1.25
7401	.16	7453	.17	74155	1.07
7402	.15	7454	.17	74156	1.07
7403	.16	7464	.35	74158	1.79
7404	.19	7465	.35	74160	1.39
7405	.19	7470	.30	74161	1.25
7406	.35	7472	.30	74162	1.49
7407	.35	7473	.35	74163	1.39
7408	.18	7474	.35	74164	1.59
7409	.19	7475	.57	74165	1.59
7410	.16	7476	.39	74166	1.49
7411	.25	7483	.79	74170	2.30
7413	.55	7485	1.10	74173	1.49
7416	.35	7486	.40	74174	1.62
7417	.35	7489	2.48	74175	1.39
7420	.16	7490	.59	74176	.89
7422	.26	7491	.97	74177	.84
7423	.29	7492	.71	74180	.90
7425	.27	7493	.60	74181	2.98
7426	.26	7494	.94	74182	.79
7427	.29	7495	.79	74184	2.29
7430	.20	7496	.79	74185	2.29
7432	.23	74100	1.30	74187	5.95
7437	.35	74105	.44	74190	1.35
7438	.35	74107	.40	74191	1.35
7440	.17	74121	.42	74192	1.25
7441	.98	74122	.45	74193	1.19
7442	.77	74123	.85	74194	1.25
7443	.87	74125	.54	74195	.89
7444	.87	74126	.63	74196	1.25
7445	.89	74141	1.04	74197	.89
7446	.93	74145	1.04	74198	1.79
7447	.89	74150	.97	74199	1.79
7448	1.04	74151	.79	74200	5.90
7450	.17	74153	.99		

LOW POWER TTL

74100	\$.25	74151	\$.29	75L90	\$1.49
74102	.25	74155	.31	74L91	1.45
74103	.25	74171	.25	74L93	1.69
74104	.25	74172	.19	74L95	1.69
74106	.25	74173	.49	74L98	2.79
74110	.25	74174	.49	74L164	2.79
74120	.33	74178	.79	74L165	2.79
74130	.33	74185	1.25		
74L42	1.49	74186	.69		

HIGH SPEED TTL

74H00	\$.25	74H21	\$.25	74H55	\$.25
74H01	.25	74H22	.25	74H60	.25
74H04	.25	74H30	.25	74H61	.25
74H08	.25	74H40	.25	74H62	.25
74H10	.25	74H50	.25	74H72	.39
74H11	.25	74H52	.25	74H74	.39
74H20	.25	74H53	.25	74H76	.49

8000 SERIES

8091	\$.53	8214	\$1.49	8811	\$.59
8092	.51	8220	1.49	8812	.89
8095	1.25	8210	2.19	8822	2.19
8121	1.80	8510	1.16	8830	2.19
8123	1.43	8551	1.39	8831	2.19
8130	1.97	8552	1.19	8816	.25
8200	2.13	8554	2.19	8880	1.19
8210	2.79	8810	.69	8263	5.79
				8267	2.59

9000 SERIES

9002	\$.15	9309	\$.79	9601	\$.89
9301	1.03	9312	.79	9602	.79

CMOS

4000A	\$.26	4017A	1.19	4066A	.89
4001A	.25	4020A	1.49	4068A	.44
4002A	.25	4021A	1.39	4069A	.44
4004A	1.35	4022A	1.10	4071A	.26
4007A	.26	4023A	.25	4072A	.35
4008A	1.79	4024A	.89	4073A	.39
4009A	.57	4025A	.25	4075A	.39
4010A	.54	4027A	.59	4078A	.39
4011A	.29	4028A	.98	4081A	.26
4012A	.25	4030A	.44	4082A	.35
4013A	.45	4035A	1.27	4528A	1.60
4014A	1.49	4042A	1.47	4585A	2.10
4015A	1.49	4049A	.59		

74C00	\$.22	74C74	\$1.04	74C162	\$2.93
74C02	.26	74C76	1.14	74C163	2.66
74C04	.44	74C107	1.33	74C164	2.66
74C08	.88	74C151	2.61	74C173	2.61
74C10	.35	74C154	1.15	74C195	2.66
74C20	.35	74C157	1.76	80C95	1.15
74C42	1.61	74C160	2.48	80C97	1.11
74C71	1.04	74C161	2.93		

POCKET CALCULATOR

5 function plus constant — addressable memory with individual recall — 8 digit display plus overflow — battery saver — uses standard or rechargeable batteries — all necessary parts in ready to assemble form — instructions included.



Calc. Kit. Kit only \$10.95
Batteries (alkaline, disp.) 2.00
Adapter 60Hz 3.95
Kit, Batteries & Adapter 15.95

741 Comp Op Amp mDIP .26

6 DIGIT LED CLOCK KIT

INCLUDES:
MM314 clock circuit
6 FND70 LED displays (.250" red 7 segment)
All necessary transistors, resistors & capacitors
1 double sided PC board accommodates LED's & clock circuitry
Schematic & instructions
Does not include 12V-300 ma transformer, switches & case \$11.95

ALARM CLOCK CHIP

MMS375AA 4-6 digit, 12 hour, 60Hz snooze alarm, brightness control Capability, alarm tone output 24 pin DIP \$4.95

8038 FUNCTION GENERATOR

Voltage controlled oscillator — sine, square, triangular output, 16 pin DIP with data \$3.95

7001 CLOCK CHIP

4-6 digit, 12-24 hr. alarm, timer and date circuits — with data \$6.95

RESISTOR KIT

CARBON FILM ± 5%
1/4 OR 1/2 WATT
455 RESISTORS 44 VALUES
SUPPLIED IN A 15 DRAWER, 60 COMPARTMENT STORAGE CABINET — TABLE OR WALL MOUNT, READY TO USE
\$24.95 ea.
\$1.00 SHIPPING & HANDLING
SHIPPED VIA UPS OR PARCEL POST



R	QTY	R	QTY	R	QTY	R	QTY
1.5	5	68	5	1.0K	20	10K	20
3.3	5	100	10	1.5K	10	15K	10
6.8	5	150	10	2.2K	20	22K	10
10	10	220	10	2.7K	10	27K	5
15	5	270	5	3.3K	20	33K	10
22	5	330	10	3.9K	10	39K	10
33	5	470	20	4.7K	20	47K	10
47	10	680	10	6.8K	10	68K	10

CT5005 CALCULATOR CHIP

12 digit — 4 function with memory — chain operation \$1.39

UNIVERSAL BREADBOARD

Silver plated copper circuit board 3-1/2" x 5-1/2" — 2 rows of 27 holes for DIP IC's — space for transistors, resistors & capacitors. Versatile and simple for breadboarding IC circuits \$1.50 ea. 50 pins 1.00 ea.



UV ERASABLE PROM

1702A — 2048 bit static PROM 256x8 elect programmable & erasable TTL/DTL comp. \$14.95

RESISTOR ASSORTMENT

R (OHMS)

R	QTY	R	QTY	R	QTY	R	QTY
1.0K	20	10K	20	100K	20	1.5M	5
1.5K	10	15K	10	1.5M	10	2.2M	5
2.2K	20	22K	10	2.2M	10	3.3M	5
2.7K	10	27K	10	2.7M	5	4.7M	5
3.3K	20	33K	20	33K	10		
3.9K	10	39K	10	47K	10		
4.7K	20	47K	10	680K	10		
6.8K	10	68K	10	1.0M	20		

NEW ITEMS

TTL	PRICE	LOW POWER SCHOTTKY	PRICE
74132	\$.89	741500	\$.36
74H101	.58	74LS02	.36
74H102	.58	74LS04	.36
74H103	.63	74LS08	.38
74H106	.63	74LS10	.36
74H108	.63	74LS20	.36
		74500	\$.38
		74502	.45
		74503	.38
		74504	.45
		74508	.52
		74510	.38
		74520	.38
		74522	.38
		74532	.52
		74574	.38

METAL FILM RESISTORS

±1% 1/4 WATT

QTY	PRICE EACH	MINIMUM 10 PER VALUE	PRICE PER VALUE
0 - 10	\$.20		
10 - 100	.20	\$.15	
100 - 1000	.10	\$.09	
1000 -	.10	.08	

RESISTANCE (OHMS)

22.6	71.5	182	887	11.8K	40.2K
23.7	78.7	187	1.15K	13.0K	45.3K
25.5	84.5	191	1.5 K	15.0K	48.7K
30.9	105	205	2.49K	18.2K	54.9K
34.8	110	232	3.57K	19.1K	60.4K
40.2	115	243	4.75K	19.6K	64.9K
45.3	137	499	5.49K	22.6K	69.8K
51.1	147	604	6.04K	24.9K	84.5K
61.9	158	715	7.15K	28.0K	
64.9	178	806	8.25K	37.4K	

Data sheets on request. With order add \$.30 for items less than \$1.00 ea.

TANALUM CAPACITORS SOLID-DIPPED +20%

.1 mid 35V .25 ea.	6.8 mid 6V .30 ea.
.33 mid 35V .25 ea.	6.8 mid 50V .40 ea.
1 mid 35V .25 ea.	10 mid 25V .40 ea.
2.2 mid 20V .25 ea.	15 mid 10V .40 ea.
2.2 mid 35V .30 ea.	33 mid 10V .40 ea.
4.7 mid 16V .30 ea.	47 mid 6V .40 ea.

MISC. DEVICES

546	AM Radio receiver subst. DIP	\$.75
2513	64 x 8 x 5 character generator	\$11.00
CA3046	Transistor array 14 pin DIP	.89

LINEAR CIRCUITS

L100	Red LED	.15
L101	Red LED	.15
300	Pos V Reg (super 723) TO-5	\$.71
301	Hi Peril Op Amp mDIP TO-5	.29
302	Volt follower TO-5	.53
304	Neg V Reg TO-5	.97
305	Pos V Reg TO-5	.71
307	Op AMP (super 741) mDIP TO-5	.26
308	Micro Pwr Op Amp mDIP TO-5	.89
309K	5V IA regulator TO-3	1.35
310	V follower Op Amp mDIP	1.07
311	Hi peril V Comp mDIP TO-5	.95
319	Hi Speed Dual Comp DIP	1.13
320T	Neg Reg 5, 12, 15, TO-3	\$1.39
322K	Neg Reg 5, 2, 12 TO-3	1.70
320C	Precision Timer DIP	1.70
324	Quad Op Amp DIP	1.52
339	Quad Comparator DIP	1.58
340K	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-3	1.69
340T	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	1.49
372	AF-IF Strip detector DIP	2.93
376	Pos V Reg mDIP	2.42
380	2w Audio Amp DIP	1.13
380-8	6w Audio Amp mDIP	1.52
381	Lo Noise Dual preamp DIP	1.52
382	Lo Noise Dual preamp DIP	.71
550	Pre V Reg DIP	.89
555	Timer mDIP	.89
556A	Dual 555 Timer DIP	1.49
560	Phase Locked Loop DIP	3.95
562	Phase Locked Loop DIP	3.95
565	Phase Locked Loop DIP TO-5	2.38
566	Function Gen mDIP TO-5	2.25
567	Tone Decoder mDIP	2.66
703	RF IF AMP mDIP	.45
709	Operational AMP TO-5 or DIP	.26
710	Hi Speed Volt Comp DIP	.35
711	Dual Difference Compar DIP	.26
723	V Reg DIP	.62
733	Diff. video AMPL TO-5	.89
739	Dual Hi Peril Op Amp DIP	1.07
741	Comp Op Amp mDIP TO-5	.32
747	741 Dual Op Amp DIP or TO-5	.71
748	Freq Adj 741 mDIP	.35
1304	FM Mulps Stereo Demod DIP	1.07
1307	FM Mulps Stereo Demod DIP	.74
5556/		
MC1456	Int. compensated Op Amp mDIP	1.59
1458	Dual Comp Op Amp mDIP	.62
1800	Stereo multiplexer DIP	2.48
LH2111	Dual LM 211 V Comp DIP	1.70
3900	Quad Amplifier DIP	.35
MM5020	Jump green	.22
7524	Core Mem Sense AMPL DIP	.71
7525	Dual core mem sense AMPL DIP	.98
8038	Voltage contr. osc. DIP	4.25
8864	9 DIG LED Cath Drrv DIP	2.25
75150	Dual Line Driver DIP	1.75
75451	Dual Peripheral Driver mDIP	.35
75452	Dual Peripheral Driver mDIP	.35
75453	(351) Dual Periph Driver mDIP	.35
75491	Quad Seq Driver for LED DIP	.71
75492	Hex Digit driver DIP	.80

MEMORIES

1101	256 bit RAM MOS	\$.150
1103	1024 bit RAM MOS	3.95
1702A	2048 bit static PROM UV eras.	17.95
2102-2	1024 bit static RAM	4.25
5203	2048 bit UV eras PROM	17.95
5260	1024 bit RAM	2.49
5261	1024 bit RAM	2.69
5262	2048 bit RAM	5.95
7489	64 bit ROM TTL	2.48
82523	Programmable ROM	3.69
74200	256 bit RAM tri-state	5.90
F93410	256 bit bipolar RAM	2.19

CALCULATOR & CLOCK CHIPS

5001	12 DIG 4 funct fix dec	\$2.49
5002	Same as 5001 exc btry power	2.79
5005	12 DIG 4 funct w/mem	2.99
MMS725	8 DIG 4 funct chain & dec	1.98
MMS736	18 pin 6 DIG 4 funct	4.45
MMS738		

C-MOS

4000	6/1 20	4043	1 25
4001	4 1 25	4044	2 25
4002	5 1 25	4046	2 00
4006	1 25	4047	2 00
4007	4 1 25	4053	2 1 50
4008	1 25	4050	2 1 50
4009	2 1 00	4051	1 50
4010	2 1 00	4053	1 75
4011	4 1 00	4071	3 1 00
4012	4 1 00	4073	3 1 25
4013	3 1 00	4081	2 1 50
4014	1 00	4089	2 1 50
4015	1 10	4020	1 00
4016	2 1 35	4043	1 00
4017	1 10	4044	1 00
4018	2 1 25	4412	1 25
4020	1 20	4416	1 50
4021	1 25	4426	1 75
4022	1 25	4428	2 25
4023	4 1 00	4441	2 00
4024	2 1 50	4443	2 00
4025	4 1 00	4507	2 1 00
4027	2 1 00	4508	1 00
4028	5 1 00	4510	1 00
4029	1 25	4511	1 85
4030	2 1 00	4512	1 65
4033	1 90	4513	2 00
4035	1 25	4518	1 50
4040	1 35	4519	1 50
4041	1 25	4520	1 25
4042	1 25	4528	1 60

MC1303L Dual Stereo PreAmp 1.00

DTL IC's

930	6/1 00	9300	
931	4 1 00		
932	7 1 00	9300	1 00
933	5 1 00	9301	1 25
935	5 1 00	9304	1 00
936	7 1 00	9313	1 00
938	4 1 00	9316	1 00
944	4 1 00	9318	1 25
945	6 1 00	9321	1 75
949	6 1 00	9334	2 00
952	4 1 00		
953	5 1 00		
957	4 1 00		
958	4 1 00	9300	2 1 50
962	5 1 00	9308	5 00
9693	5 1 00	9316	1 00
9099	7 1 00	9318	1 00
915R	4 1 00	9319	1 00
958C/MUL	5 75	9602	1 00
960C/MUL	7 50	9615	2 75

LINEAR IC's

Package Codes	H-T05	K-T03	M-Mini 8pin	N-Dip 14pin	
300H	V Reg	1 00	556N	Dual Timer	1 35
301H	Op Amp	3 1 00	565N	Pk Lock Loop	1 00
301N	Op Amp	4 1 00	567M	Tone Decoder	1 85
302H	V Fol	1 85	700H	Linear	2 1 50
304H	Neg Reg	1 00	703H	RF/IF Amp	1 50
305H	V Reg	1 25	709H	Op Amp	3 1 25
306H	V Comp	2 40	709N	Op Amp	3 1 25
307H	Op Amp	3 1 25	715A	V Comp	3 1 25
307M	Op Amp	2 1 25	711H	Dual Comp	2 1 00
308H	Op Amp	2 75	711N	Dual Comp	2 1 00
309H	Op Amp	1 00	715A	Linear	3 25
309K	5-V Reg	1 00	716H	Audio Amp	3 25
310H	V Fol	1 55	723H	V Reg	2 1 10
310M	V Fol	1 85	723N	V Reg	2 1 10
311H	V Comp	1 00	725H	Ins Op Amp	3 75
311M	V Comp	2 1 75	733H	Dir Vid Amp	1 00
312H	Op Amp	2 00	733N	Dir Vid Amp	1 00
318H	Dual Comp	2 00	739N	Dual Aud Pre Amp	1 15
3207-5V	Neg Reg	1 25	740H	FET Op Amp	7 00
3207-6V	Neg Reg	1 25	741H	Op Amp	3 1 00
320K-12V	Neg Reg	1 50	741M	Op Amp	3 1 00
324M	Quad Op Amp	2 50	747H	Dual Op Amp	1 00
324N	Quad Op Amp	2 50	747N	Dual Op Amp	1 50
339N	Lo V Quad Comp	1 00	748M	Op Amp	3 1 25
340T-5V	Pos Reg	1 25	749N	Dual Aud Pre Amp	1 50
340T-8V	Pos Reg	1 50	749M	Dual Op Amp	3 00
340T-12V	Pos Reg	1 25	781N	Gain Cont IF Amp	2 00
340T-15V	Pos Reg	1 25	1414N	Dual Dir Comp	1 50
340T-18V	Pos Reg	1 25	1458M	Quad Op Amp	1 50
370N	AGC/Sg Amp	1 75	2900N	Quad Amp	1 00
373N	AM/FM IF Det	1 30	3065N	TV Snd Sys	2 1 50
380M	Audio Amp	1 00	3069N	Quad Op Amp	1 00
381N	Dual Pre Amp	1 40	4136N	Quad 741	0 00
531H	Op Amp	2 1 00	4558M	Dual 741	2 1 25
555M	Timer	2 1 00	AH001N	DPST Analog Sw	4 00

JADE Co

Offers Top Quality Products at these low, low prices.

Satisfaction Guaranteed or your Money Refunded.

MEMORY

P-1101A	256w x 1b st RAM	2 25
P-1103A	1024w x 1b st RAM	2 75
C-1702A	256w x 1b Eras PROM	15 00
P-2102	1024w x 1b St RAM	2 00
N2431Y	Sub System	2 50
IM-2505K	512b Shift Reg	2 00
IM-5003C	Quad Driver	4 00
MM-5013	1024b Shift Reg	4 00
MM-5203	256w x 8b ROM	15 00
5314	24 pin 6 Dg Clock	4 00
5316	40 pin 4 Dg Alarm	5 75
IM5600cp	32w x 1b ROM	3 00
C-8008	8b CPU	21 50
C-8080A	8b CPU	35 00
N8223B	256b PROM	3 50
N8225B	64b Scratch Pad	2 00
TM3002LR	100b Shift Reg	4 00
TMS3132NC	144b Shift Reg	3 00
93403DC	16w x 4b RAM	4 00

IC Sockets

	Low Pro	Standard	Wire Wrap
10		4 1 00	--
14	4 1 00	4 1 25	3 1 00
16	4 1 25	3 1 00	3 1 25
24	3 1 00	3 1 25	2 1 25
28		3 1 25	2 1 25

WANT TO PLAY VIDEO GAMES ON YOUR OWN TV?

Write us today for a free catalogue with complete listing of video games and other kits along with all I.C.'s, Discretes, Diodes, Resistors, pots, hardware, grab bags - you name it.

TTL IC's

7400	6/1 00	7443	1 00
7401	6/1 00	7445	2 1 35
7402	5 1 00	7446	2 1 45
7403	5 1 00	7447	2 1 50
7404	5 1 00	7448	2 1 75
7405	5 1 00	7450	5 1 00
7406	3 1 00	7451	5 1 00
7407	3 1 00	7453	5 1 00
7408	4 1 00	7454	5 1 00
7409	4 1 00	7460	5 1 00
7410	6 1 00	7470	3 1 00
7411	4 1 00	7475	2 1 00
7412	4 1 25	7473	3 1 00
7413	2 1 15	7474	3 1 00
7414	2 1 40	7475	2 1 00
7416	3 1 25	7476	3 1 00
7417	3 1 25	7479	1 00
7418	4 1 25	7480	2 1 00
7420	5 1 00	7482	2 1 85
7422	1 10	7483	2 1 40
7423	3 1 10	7485	2 1 85
7425	3 1 25	7486	2 1 85
7426	3 1 00	7488	3 50
7427	3 1 00	7490	3 00
7428	2 1 00	7490	2 1 00
7429	3 1 25	7491	1 00
7430	5 1 00	7492	2 1 00
7432	4 1 25	7493	2 1 00
7433	2 1 25	7494	2 1 70
7437	3 1 25	7495	2 1 60
7438	3 1 25	7496	2 1 50
7439	3 1 25	7497	3 75
7440	5 1 00	7498	1 00
7441	2 1 65	74107	3 1 00
7442	2 1 00	74109	2 1 00

TTL IC's

74110	1 75	74176	1 00
74111	1 75	74177	1 00
74116	2 00	74180	1 00
74120	1 75	74181	2 1 0
74121	3 1 10	74182	1 00
74122	3 1 10	74184	2 25
74123	2 1 25	74185	2 00
74125	3 1 35	74186	7 00
74126	3 1 35	74187	5 25
74128	1 00	74190	2 00
74132	1 00	74191	1 15
74136	2 1 70	74192	1 00
74141	1 00	74193	1 00
74145	1 00	74194	1 00
74146	1 90	74195	2 1 50
74150	1 90	74196	1 00
74151	2 1 50	74197	1 00
74153	2 1 50	74198	1 45
74154	1 10	74199	1 10
74155	1 00	74200	5 50
74157	2 1 45	74201	1 35
74158	2 00	74202	2 00
74159	2 95	74205	2 1 50
74160	2 00	74273	2 00
74161	2 1 85	74278	2 40
74162	1 50	74279	1 00
74163	1 00	74283	1 65
74164	1 05	74284	5 00
74165	1 00	74285	5 00
74166	1 25	74293	1 00
74167	1 50	74298	1 00
74170	2 00	74305	2 1 50
74171	1 35	74366	1 00
74172	1 10	74174	1 00
74175	1 00	74368	2 1 50

TTL IC's

74390	1 75	Low Power	74LS04	3 1 15	74LS194	2 00
			74LS05	3 1 15	74LS195	2 00
			74LS10	3 1 00	74LS196	2 50
		High Speed	74LS11	3 1 00	74LS197	2 00
			74LS14	4 1 00	74LS248	1 75
			74LS10	4 1 00	74LS249	1 90
			74LS30	3 1 00	74LS250	1 90
			74LS42	1 35	74LS260	2 1 50
			74LS40	3 1 00	74LS261	1 85
			74LS42	1 35	74LS262	2 1 85
			74LS51	3 1 00	74LS263	1 90
			74LS54	3 1 00	74LS264	2 1 70
			74LS55	3 1 00	74LS265	1 00
			74LS71	4 1 00	74LS266	1 00
			74LS72	2 1 15	74LS267	4 75
			74LS73	1 90	7520	2 1 50
			74LS74	2 1 00	7522	2 1 50
			74LS75	2 1 00	7523	2 1 50
			74LS76	2 1 50	7524	1 85
			74LS77	1 35	7525	1 25
			74LS78	2 1 50	7526	2 1 50
			74LS79	1 50	75110	1 25
			74LS81	1 40	75113	1 25
			74LS82	1 50	75114	1 25
			74LS85	1 50	75150	1 25
			74LS86	2 50	75151	1 50
			74LS87	1 00	75152	1 25
			74LS88	1 00	75153	1 50
			74LS89	1 00	75154	1 50
			74LS90	1 00	75155	1 50
			74LS91	1 00	75156	1 50
			74LS92	1 00	75450A	3 1 00
			74LS93	1 00	75451	3 1 35
			74LS94	1 00	75452	3 1 35
			74LS95	1 00	75453	3 1 25
			74LS96	1 00	75454	2 1 00
			74LS97	1 00	75460	1 60
			74LS98	1 00	75491	3 1 25
			74LS99	1 00	75492	2 1 00
			74LS100	3 1 15		
			74LS101	3 1 15		
			74LS102	3 1 15		
			74LS103	3 1 15		
			74LS104	3 1 15		
			74LS105	3 1 15		
			74LS106	3 1 15		
			74LS107	3 1 15		
			74LS108	3 1 15		
			74LS109	3 1 15		
			74LS110	3 1 15		
			74LS111	3 1 15		
			74LS112	3 1 15		
			74LS113	3 1 15		
			74LS114	3 1 15		
			74LS115	3 1 15		
			74LS116	3 1 15		
			74LS117	3 1 15		
			74LS118	3 1 15		
			74LS119	3		

ZENER DIODES 500 mW - 5%

V 1-9 10up		V 1-9 10up	
IN5223B	2.7 45 40	IN5246B	16 45 40
IN5224B	2.8 45 40	IN5247B	17 45 40
IN5225B	3.0 45 40	IN5248B	18 45 40
IN5226B	3.3 45 40	IN5249B	19 45 40
IN5227B	3.6 45 40	IN5250B	20 45 40
IN5228B	3.9 45 40	IN5251B	22 45 40
IN5229B	4.3 45 40	IN5252B	25 45 40
IN5230B	4.7 45 40	IN5253B	25 45 40
IN5231B	5.1 45 40	IN5254B	27 45 40
IN5232B	5.6 45 40	IN5255B	28 45 40
IN5233B	6.0 45 40	IN5256B	30 45 40
IN5234B	6.2 45 40	IN5257B	33 45 40
IN5235B	6.5 45 40	IN5258B	36 45 40
IN5236B	7.5 45 40	IN5259B	39 45 40
IN5237B	8.2 45 40	IN5260B	43 45 40
IN5238B	8.7 45 40	IN5261B	47 45 40
IN5239B	9.1 45 40	IN5262B	55 45 40
IN5240B	10 45 40	IN5263B	56 55 50
IN5241B	11 45 40	IN5264B	60 55 50
IN5242B	12 45 40	IN5265B	62 55 50
IN5243B	13 45 40	IN5266B	68 55 50
IN5244B	14 45 40	IN5267B	75 55 50
IN5245B	15 45 40		

7400N TTL

1-9 10up		1-9 10up		1-9 10up	
7400N	14 .13	7470N	.40 .30	74152N	1.04 .94
7401N	18 .16	7472N	.40 .30	74153N	.85 .75
7402N	18 .16	7473N	.42 .32	74154N	.88 .78
7403N	18 .16	7474N	.44 .40	74155N	1.02 .92
7404N	21 .19	7475N	.55 .50	74156N	1.02 .92
7405N	20 .19	7476N	.44 .40	74157N	.90 .80
7406N	36 .28	7477N	.80 .75	74158N	1.00 .90
7407N	36 .28	7481N	1.30 1.25	74160N	1.02 .92
7408N	28 .21	7482N	.98 .96	74161N	1.10 1.00
7409N	28 .21	7483N	.82 .76	74162N	1.40 1.30
7410N	22 .18	7484N	1.90 1.70	74163N	1.16 .90
7411N	20 .16	7485N	1.20 1.08	74164N	1.16 .90
7412N	34 .32	7486N	.44 .40	74165N	1.20 1.10
7413N	45 .42	7489N	2.20 2.10	74166N	1.20 1.10
7414N	98 .95	7490N	.56 .51	74167N	5.00 4.50
7416N	35 .32	7491N	.84 .78	74168N	1.20 1.30
7417N	35 .32	7492N	.56 .50	74173N	1.66 1.50
7418N	30 .27	7493N	.62 .56	74174N	1.00 .90
7420N	15 .14	7494N	.88 .80	74175N	.96 .90
7421N	30 .26	7495N	.80 .72	74176N	1.08 1.00
7422N	30 .26	7496N	.75 .68	74177N	1.08 1.00
7423N	37 .36	7497N	5.00 4.50	74178N	1.42 1.30
7425N	30 .23	74100N	1.00 1.00	74179N	1.80 1.70
7426N	28 .26	74104N	1.00 .90	74180N	1.12 1.02
7427N	28 .26	74105N	1.00 .90	74181N	2.00 1.70
7428N	40 .38	74107N	.40 .36	74182N	1.00 .90
7430N	26 .20	74109N	.40 .36	74184N	2.80 2.50
7432N	32 .30	74110N	1.00 .90	74185N	3.00 2.70
7433N	44 .40	74111N	1.00 .90	74188N	5.00 4.80
7437N	25 .24	74112N	2.00 1.80	74189N	1.20 1.30
7438N	29 .27	74118N	2.00 2.00	74191N	1.20 1.10
7439N	44 .40	74119N	4.00 3.60	74192N	.98 .90
7440N	17 .16	74121N	.60 .54	74193N	.92 .88
7441N	85 .83	74122N	.48 .43	74194N	1.36 1.23
7442N	40 .38	74123N	.75 .68	74195N	1.35 1.20
7443N	72 .65	74126N	.50 .45	74196N	1.40 1.30
7444N	72 .65	74126N	.50 .45	74197N	1.40 1.30
7445N	90 .81	74128N	.50 .45	74198N	1.40 1.30
7446N	90 .81	74129N	.92 .85	74199N	2.40 2.30
7447N	98 .90	74136N	.80 .72	74200N	9.00 8.00
7448N	98 .90	74141N	1.70 1.50	74221N	1.36 1.25
7450N	14 .13	74148N	1.10 1.00	74247N	2.40 2.20
7451N	14 .13	74147N	1.90 1.70	74251N	1.90 1.80
7452N	14 .13	74148N	1.50 1.35	74278N	2.90 2.60
7454N	14 .13	74150N	1.52 1.40	74279N	.66 .60
7459N	20 .18	74151N	1.02 .92	74298N	2.00 1.8P
7460N	14 .13				

HIGH SPEED TTL

74H00N	.33	74H20N	.33	74H52N	.36	74H73N	.80
74H01N	.25	74H21N	.33	74H53N	.36	74H74N	.80
74H04N	.33	74H22N	.33	74H54N	.36	74H76N	.75
74H05N	.33	74H23N	.33	74H55N	.36	74H102N	.75
74H08N	.40	74H24N	.36	74H60N	.36	74H103N	.95
74H10N	.33	74H50N	.36	74H71N	.75	74H106N	.95
74H11N	.33	74H51N	.36	74H72N	.75		

LOW POWER TTL

74L00N	.24	74L51N	.24	74L90N	1.62
74L02N	.24	74L20N	.33	74L73N	1.51
74L03N	.39	74L42N	1.33	74L74N	.90
74L04N	.33				

74LS00

1-9 10up		1-9 10up		1-9 10up	
74LS00N	.36 .35	74LS55N	.39 .38	74LS161N	3.00 2.70
74LS01N	.44 .40	74LS56N	.55 .54	74LS162N	3.00 2.70
74LS02N	.36 .35	74LS74N	.56 .54	74LS163N	3.00 2.70
74LS03N	.45 .43	74LS76N	.65 .64	74LS170N	5.80 5.30
74LS04N	.44 .40	74LS78N	.92 .90	74LS174N	2.20 2.00
74LS05N	.45 .44	74LS79N	2.08 2.00	74LS177N	2.40 2.20
74LS06N	.38 .37	74LS107N	.51 .58	74LS181N	3.69 3.58
74LS08N	.44 .40	74LS109N	.92 .86	74LS190N	2.85 2.70
74LS10N	.36 .35	74LS112N	.58 .55	74LS191N	2.85 2.70
74LS11N	.46 .42	74LS113N	.92 .85	74LS192N	2.50 2.40
74LS15N	.58 .55	74LS114N	1.91 .88	74LS194N	2.25 2.20
74LS20N	.44 .40	74LS123N	6.00 1.50	74LS195A	2.40 2.20
74LS21N	.58 .54	74LS138N	1.89 1.80	74LS196A	2.76 2.50
74LS22N	.58 .54	74LS139N	2.00 1.80	74LS197A	2.20 2.10
74LS27N	.44 .40	74LS141N	1.68 1.50	74LS251A	2.08 1.90
74LS28N	.39 .38	74LS151N	8.00 1.79	74LS252A	2.42 2.20
74LS32N	.45 .44	74LS157N	5.51 1.54	74LS257A	1.89 1.80
74LS38N	.58 .53	74LS158N	6.81 1.60	74LS258A	2.06 1.90
74LS51N	.39 .38	74LS160N	3.00 2.70	74LS260A	.44 .40
74LS54N	.58 .54				

SCHOTTKY TTL

74S00	.44	74S32	.80	74S113	1.50	74S174	3.30
74S01	.76	74S50	.65	74S114	1.20	74S175	2.90
74S02	.60	74S50	.76	74S133	.80	74S181	6.00
74S03	.75	74S51	.80	74S138	2.20	74S189	4.40
74S04	.55	74S50	.80	74S139	2.20	74S194	3.30
74S05	.76	74S50	.80	74S140	8.00	74S194	3.30
74S08	.80	74S50	.80	74S152	2.20	74S251	2.20
74S09	.76	74S74	.90	74S153	3.40	74S253	2.40
74S10	.55	74S76	1.15	74S157	2.40	74S257	2.40
74S11	.65	74S78	1.16	74S158	2.40	74S258	2.40
74S15	.76	74S85	6.10	74S160	9.00	74S260	1.20
74S20	.65	74S86	2.50	74S161	4.70	74S260	1.20
74S21	.76	74S112	1.00	74S172	6.00	74S289	4.00
74S30	.80						

9300 SERIES

9300PC	1.00	9318PC	2.30	9366PC	1.75	9318L	3.50
9301PC	1.20	9321PC	1.20	9310L	1.50	9312L	1.50
9304PC	1.50	9322PC	1.30	9310L	1.60	9312L	1.80
9306PC	6.90	9324PC	2.00	9310L	2.80	9312L	2.80
9308PC	2.50	9328PC	1.80	9312L	2.80	9312L	2.80
9309PC	1.60	9334PC	2.95	9310L	3.20	9313L	4.00
9310PC	1.50	9338PC	3.30	9311L	4.20	9313L	4.20
9311PC	2.30	9340PC	5.00	9314L	1.80	9314L	6.50
9312PC	1.20	9341PC	4.10	9314L	1.70	9314L	6.50
9314PC	1.30	9343PC	3.30	9316L	3.20	9316L	6.00
9316PC	1.50	9360PC	1.75	9318L	3.50	9316L	6.20

WAVEFORM GENERATOR KIT

EXAR XR205K \$25.00

Here's a highly versatile lab instrument at a fraction of the cost of conventional unit. Kit includes 2 XR205 IC's, data & applications, PC board (etched and drilled, ready for assembly) and detailed instructions.



LINEAR IC's

H-T-O-5	N-DIP	M-MINI-DIP	D-CER-DIP	K-T-O-3	
LM105H	3.90	LM311H	1.20	LM7100H	90
LM108H	4.90	LM311D	1.90	LM7100N	90
LM114H	3.00	LM311M	1.75	LM7110H	90
LM300H	1.20	LM312N	1.75	LM7110N	90
LM301A	1.20	LM312P	1.50	LM7150H	90
LM301AH	.50	LM318M	2.40	LM7150D	4.60
LM301AM	.80	LM324N	1.90	LM723CH	.60
LM301AN	1.10	LM331N	1.25	LM723CN	.65
LM301M	.95	LM336K	2.40	LM725CH	1.50
LM302H	1.20	LM339N	1.20	LM725CN	5.00
LM302H	1.20	LM320-5T	2.90	LM733CH	1.40
LM305H	.85	LM320-5T	2.50	LM733CD	3.50
LM305AH	1.05	LM320-12K	2.90	LM733CN	1.40
LM305N	1.00	LM320-12T	2.50	LM735CH	3.90
LM305N	1.00	LM340-5K	2.60	LM741CD	1.25
LM306N	.95	LM340-6K	2.60	LM741CM	.99
LM307H	.60	LM340-8K	2.60	LM747CH	.75
LM307M	1.50	LM340-12K	2.60	LM747CN	.90
LM308H	.85	LM340-18K	2.60	LM748CM	5.50
LM308AH	5.00	LM340-18K	2.60	LM777CH	2.15
LM308D	2.25	LM340-24K	2.60	LM777CN	1.50
LM308M	1.00	LM555CM	7.00	LM3046CN	.95
LM309H	1.75	LM556CM	1.30	LM3047CN	1.50
LM309N	1.50	LM567CM	1.70	SG4501T	2.40
LM310H	1.50	LM709CH	.75	SG4501N	2.40
LM310M	1.80	LM709CN	.75	LM5000K	7.60

C-MOS

P/N	1-9 10up	P/N	1-9 10up	P/N	1-9 10up
4000AE	24 .23	4027AE	55 .53	4070AE	60 .59
4001AE	24 .22	4028AE	55 .88	4071AE	25 .23
4002AE	24 .22	4029AE	65 .50	4072AE	34 .31
4004AE	4.00 3.99	4030AE	44 .40	4073AE	.38 .35
4006AE	1.30 1.20	4032AE	2.00 1.94	4075AE	.38 .35
4007AE	24 .23	4035AE	1.25 1.14	4076AE	1.24 1.22
4008AE	1.79 1.65	4040AE	1.58 1.50	4077AE	.70 .69
4013AE	.45 .40	4041AE	1.82 1.75	4078AE	.38 .35
4010AE	.50 .49	4042AE	.78 .75	4081AE	.25 .23
4011AE	24 .23	4043AE	.85 .80	4082AE	.34 .31
4012AE	24 .22	4044AE	.80 .75	4085AE	1.30 1.25
4013AE	.45 .40	4045AE	2.75 2.70	4088AE	1.20 1.25
4014AE	1.45 1.34	4048AE	1.43 1.42	4099AE	2.90 2.89
4015AE	1.24 1.23	4049AE	.68 .53	4507AE	.60 .55
4016AE	.50 .49	4050AE	.58 .53	4508AE	2.20 2.19
4017AE	1.15 1.07	4051AE	1.49 1.48	4509AE	1.45 1.44
4018AE	1.24 1.23</				

PRINTER BREAKS PRICE BARRIER



\$425

Post Paid
in U.S.

mp-40

- Completely assembled and tested
- 64 character ASCII
- Up to 40 columns
- Ordinary roll paper
- Includes parallel I/O interface and power supply

MICRO PERIPHERALS, INC.

P.O. BOX 22101, SALT LAKE CITY, UT 84122
1-801-566-0201

- SEND PRINTERS @ \$425 ea.
UTAH RESIDENTS ADD 5% SALES TAX
- ENCLOSED IS CHECK/M.O. FOR
- BANKAMERICARD # _____
- MASTER CHARGE # _____
EXPIR. DATE _____ MC INTERBANK # _____
- SEND LITERATURE

NAME _____
ADDRESS _____
CITY _____ STATE/ZIP _____
mpi/P.O. BOX 22101/SALT LAKE CITY/UT 84122

Circle 126 on reader service card

FOR THE MUSIC BUFF SGS-ATES MONOLYTHIC RHYTHM GENERATORS

Designed specifically for electronic organs and other musical instrument designs. Constructed on a single chip, supplied in 24-pin DIP package.

- Low power dissipation: < 120 mW
 - Drives 8 sound generators (instruments)
 - Mask programmable reset counts: 24 or 32
 - Down beat output
 - External reset
 - Open drain outputs
 - Standard music content available
- Detailed 25-pg. applications book, only \$5.95

M252B1AA

15 programmable rhythms (not available in combination) . . . \$15.00 **16-PIN**



M253B1AA
12 programmable rhythms (also available in combination) . . . \$19.50 **24-PIN**

ABSOLUTE MAXIMUM RATINGS

V _{GG} *	Source supply V	-20 to 0.3	V
V _I	Input voltage	-20 to 0.3	V
I _O	Output cur't. any pin	3	mA
T _{stg}	Storage temp.	-65 to 150	°C
T _{op}	Operating temp.	0 to 70	°C

*With respect to V_{SS} pin voltage

16-PIN Socket...\$28 24-PIN Socket...\$60
16-page data sheet for both devices only \$5.00.

IF IT ISN'T INDUSTRIAL QUALITY OR BETTER, WE WON'T SELL IT TO YOU.

SEND CHECK OR MONEY ORDER TO:



P.O. BOX 2208P
CULVER CITY, CA 90230 •(213) 641-4064

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

READER SERVICE CARD NO. PAGE

15	Allison Automotive Co.	85
83	American Technology Corp.	87
12	AP Products	83
26	Arrow Fastener	24
85	Bell P/A Products	86
96	B&K, Division of	
22	Dynascan Corp.	20,21
91	Blonder Tongue Laboratories	79
27	Brooks Radio & TV Corp.	87
66	Castle Electronics, Inc.	Cover IV
92	Channellock, Inc.	66
66	Chemtronics	92
92	CIE, Cleveland Institute of Electronics	70-73
90	Continental Specialties Corp.	5
72	CREI, Division of McGraw-Hill Continuing Education Center	26-29
62,94	Dana Laboratories, Inc.	92
70	Delta Products	91
77	Edlie Electronics	82
28	Edmund Scientific	76,112
10	Edsyn	81
88	EICO, Electronic Instrument, Inc.	84
18	E&L Instruments, Inc.	74
63	Electronics Technical Institute, Division of Technical Home Study Schools	17
100	EMC, Electronics Measurement Corp.	68
7	Fordham Radio Supply Co.	68
11	General Electric	25
20	Grantham School of Electronics	89
89	GTE Sylvania—Electronic Components	32
14	Harwill	76
75	Heath Co.	19
74	Hickok Electrical Instruments Co.	14
24	IMS	18
69	Indiana Home Study Institute	65
29	International Crystal Mfg. Co.	90
8	Lafayette Radio Electronics Corp.	23
79	Leader Instrument Corp.	83
78	McKay Dymek Co.	83
67	MITS, Micro-Instrumentation Telemetry Systems, Inc.	1
93	MOS Technology, Inc.	67
8	Mountain West Alarm Co.	80
87	National Camera Co.	74
68	NRI, Division of McGraw-Hill Continuing Education Center	8-11
5	National Technical Schools	52-55
23	PAIA Electronics, Inc.	85
86	Panavise, Division of Colbert Ind.	84
82	Perma Power	80
9	Photolume Corp.	92
95	PTS Electronics, Inc.	Cover II
61	Radio Shack	15
73	RCA-Distributor & Special Prod. Div.	64,65
80	Rye Industries	88
17,64	Sabtronics International, Div. of Euraytrading	80
19	SBE	7
86	Schober Organ Corp.	66
82	Sencore, Inc.	88
9	Sennheiser Electronics	86
95	Shure Brothers	16
61	Sinclair Radionics, Inc.	31
73	Southwest Technical Products	Cover III
80	Sphere Corp.	76
17,64	Tab Books	82
19	Tektronix, Inc.	85
	Telematic, Inc.	30,17
	Tri-Star Corp.	64

READER SERVICE CARD NO. PAGE

6	Tuner Service Corp.	13
3	Vaco	2
13	Vector Electronics Corp.	22
65	Weller-Xcelite Electronics Division	78
30	Zodiac Communications	75

MARKET CENTER

105	Active Electronics	97
110	Altaj	100-101
	AMC Sales	96
	American Calibration Services	100
	American Used Computer Corp.	94
121,122,123	Ancrona Corp.	109,110,111
116	Babylon Electronics	104
	Karel Barta	93
	CFR Associates	106
	Command Productions	94
	Cornell Electronics	106
	Dage Scientific Instruments	100
117	Delta Electronics	104
124	Dema Electronics	94
104	Digi-Key	96
125	Electronic Materials	96
103	Formula International	92
127	Bill Godbout Electronics International	104
	Information Unlimited, Inc.	106
119	International Electronics Unlimited	107
120	Jade	108
106,107	James Electronics Lab Science	98-99
	Lakeside Industries	93
109	Meshna Electronics, John Jr.	100
126	Micro-Peripheral, Inc.	110
114	New-Tone Electronics	102
102	Nexus Trading	94
108	Olsen Electronics	100
	Parasitic Engineering	106
99	Polymorphic Systems	93
118	Poly Paks	105
113	Processor Technology Corp.	102
112	Quest	102
	Saxitone Tape Sales	94
115	SD Sales	103
	Security Systems	94
	Solid State Sales	106
101	Stanley Lin	94
	Trumbell	96
	Valley West	93

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print)

address

city state zip code

Mail to: **Radio-Electronics SUBSCRIPTION DEPT., BOULDER, COLO. 80302**

CMOS/LSI FROM STANDARD MICROSYSTEMS

COM2502/H COM2017/H

Universal Asynchronous Receiver/Transmitter

Performs all receiving and transmitting functions of asynchronous data communications. Duplex mode, baud rate, data word length, parity mode, and number of stop bits are independently programmable. There may be 5, 6, 7, or 8 data bits, odd/even or no parity, and 1 or 2 stop bits or 1.5 stop bits when utilizing a 5-bit code. COM2017/H, COM2502/H. Prices: COM2502/H, \$13.20; COM2502P, \$8.00; COM2502H, \$14.20; COM2502HP, \$9.00; COM2017, \$13.20; COM2017P, \$8.00; COM2017H, \$14.20; COM2017HP, \$9.00. **Package: 16-Pin Plastic, High Speed**

COM2601

Universal Synchronous Receiver/Transmitter

Performs all the receiving and transmitting functions associated with synchronous (STR, 8SC, 8I-Sync and interleaved bi-sync) data communications. TTL compatible, duplex mode, baud rate, data word length, parity mode, receiver sync character and transmitter sync character are independently programmable. Double buffered and generates the sync character received and sync character transmitted signals. Interfaces with all synchronous peripherals. **High Speed Operation - 250K baud, 200NS strobes**. **Hermetic DIP Package**

COM5016 COM5016T

DUAL BAUD RATE GENERATOR Programmable Divider

Generates 32 externally selectable frequencies, the full spectrum of 16 asynchronous/synchronous baud rates. Selectable frequencies externally selected by four address inputs. Internal reprogrammable ROM allows the generation of other frequencies from other crystal frequencies or input frequencies. The 4 address inputs on each divider section may be strobe (150ns) or DC loaded. Full duplex (independent transmitter and receiver frequencies) operation is possible. Divides any modulo up to (2¹⁵-1). The COM5016 can be driven by either an external crystal or TTL logic level inputs; COM5016T is driven by TTL logic level inputs only. **Price: COM5016, \$12.00; COM5016T, \$11.70**

- 18 pin ceramic DIP package
- On chip crystal oscillator or external frequency input
- Choice of 2 x 16 output frequencies
- 16 asynchronous/synchronous baud rates
- Direct UART/USRT compatible
- Full duplex communication capability
- Re-programmable ROM allows generation of other frequencies
- TTL, MOS compatibility

CR2376-XX

Keyboard Encoder Read Only Memory

Contains all the logic necessary to encode single pole single throw keyboard closures into a usable 9-bit code. **Price: \$20.00**

- Outputs directly compatible with TTL/DTL or MOS logic
- External control provided for output polarity selection.
- External control provided for selection of odd or even parity.
- Two key roll-over operation.
- One integrated circuit required for complete keyboard assembly.
- Static charge protection on all input and output terminals.

Package: 40-Pin DIP

10 Channel Multiplexer NMX 5010

Ten (10) n-channel silicon-gate, low-resistance, MOS enhancement-mode field-effect transistors fabricated on a single silicon chip. Source regions of the individual transistors are internally connected in such a way as to provide the user with maximum flexibility in switching applications. A separate substrate terminal is provided so as to enable one to choose the desired threshold voltage associated with the individual n-channel MOSFETs over a relatively wide range of values. The SMC-NMX-5010 is assembled in a standard 24-lead ceramic dual-in-line package. **Price: \$12.00**

CAL 1022

Twelve Digit Printing Calculator

Contains all logic functions required to interface with a SEIKO 102/104 or equivalent printer. Performs functions consistent with a general-purpose business machine, including the basic four functions, one memory and percentage. One line of output buffering allows the 1022 to be calculating or accepting keyboard entries simultaneously with a print operation. **Price: \$60.00**

Package: 40-Pin Ceramic DIP

MM5316

DIGITAL ALARM CLOCK CIRCUIT

MM5316 utilizes line frequency (50 or 60 Hz) as its timing base, and provides a variety of timing functions suitable for a digital alarm clock, digital clock radio, and other applications. Four display modes are provided (hours and minutes, minutes and seconds, alarm, and sleep) 12 or 24-hour display format 24-hour alarm setting 9 minute snooze alarm Pre-settable 59 minute sleep timer AM/PM outputs (12 hr. format) Flashing clock for seconds indication All counters resettable Power failure indication Direct interface to fluorescent tubes or liquid crystal displays. Also operates with LEDs. Alternate to AMI 1998. **Price: 1, 4, \$4.95 5, up, \$4.50**

MATSUO

DIPPED TANTALUM CAPACITORS

MFD	WVDC	1-9	10up	50up	MFD	WVDC	1-9	10up	50up
.1	35	\$.30	\$.25	\$.20					
.15	35	\$.30	\$.25	\$.20	4.7	35	\$.40	\$.32	\$.26
.22	35	\$.30	\$.25	\$.20	6.8	35	\$.40	\$.32	\$.26
.33	35	\$.30	\$.25	\$.20	10	16	\$.38	\$.30	\$.24
.47	35	\$.30	\$.25	\$.20	10	35	\$.40	\$.32	\$.26
.68	35	\$.30	\$.25	\$.20	15.0	35	\$.95	\$.64	\$.56
1.0	35	\$.30	\$.25	\$.20	22.0	16	\$.40	\$.32	\$.26
1.5	35	\$.35	\$.28	\$.23	33.0	20	\$.95	\$.64	\$.56
2.2	20	15.0	15.0	15.0	47	20	1.50	1.05	1.05
3.3	35	\$.38	\$.30	\$.24	68.0	16	1.40	1.05	1.05

XR FUNCTION GENERATOR

XR-2206KA SPECIAL \$16.95. Includes monolithic function generator IC, PC board, and assembly instruction manual.

XR-2206KB SPECIAL \$26.95. Same as XR-2206KA and includes external components for PC board.

HIGH QUALITY CARBON FILM RESISTORS

From 10 ohm to 10 megohms % Watt 5% \$1.69 per 100

Only in multiples of 100 per value - 150 different values in stock

OHM	OHM	OHM	OHM	OHM	OHM
10	100	1K	10K	100K	1M
11	110	1.1K	11K	110K	1.1M
12	120	1.2K	12K	120K	1.2M
13	130	1.3K	13K	130K	1.3M
15	150	1.5K	15K	150K	1.5M
16	160	1.6K	16K	160K	1.6M
18	180	1.8K	18K	180K	1.8M
20	200	2K	20K	200K	2M
22	220	2.2K	22K	220K	2.2M
24	240	2.4K	24K	240K	2.4M
27	270	2.7K	27K	270K	2.7M
30	300	3K	30K	300K	3M
33	330	3.3K	33K	330K	3.3M
36	360	3.6K	36K	360K	3.6M
39	390	3.9K	39K	390K	3.9M
43	430	4.3K	43K	430K	4.3M
47	470	4.7K	47K	470K	4.7M
51	510	5.1K	51K	510K	5.1M
56	560	5.6K	56K	560K	5.6M
62	620	6.2K	62K	620K	6.2M
68	680	6.8K	68K	680K	6.8M
82	820	8.2K	82K	820K	8.2M
91	910	9.1K	91K	910K	9.1M

PULSE GENERATOR

Interdesign 1101: 0.1Hz - 2MHz, 0.5V Output, var. width, line or battery operation \$159.00

SPDT MINIATURE TOGGLE SWITCH

105D 115V 5A Rating \$.95

CONTINENTAL SPECIALTIES DESIGN AIDS

QT SOCKETS & BUS STRIPS

Plug in wire test modify build without soldering! Use the same components all the way from the "idea stage" to final design. Leads stay clean, not bent, twisted or loaded with solder. Expand or contract to meet your needs. Easily snapped on or off your breadboard. The fastest, most reliable way to try out new ideas or rejuvenate old ones. All are compatible with digital or linear ICs, in TO5's, DIP packs and discrete components.

QT-59S \$12.50
QT-47S \$10.00
QT-35S \$8.50
QT-47B \$2.25
QT-18S \$4.75
QT-12S \$3.75
QT-7S \$3.00

PROTO-BOARDS

QT Sockets and Strips combined into a variety of versatile ProtoBoards. Make all circuit and power interconnections with inexpensive solid #22 wire. Aluminum base plates offer solid, ground plane work surfaces. Rubber feet prevent scratching. 5-way binding posts tie into systems or power supply grounds. All are compatible with digital or linear ICs, in TO5's, DIP packs and discrete components.

Lowest priced solderless breadboard kit on market today, 6 14-pin DIP IC capacity \$15.95
PB-100 The popular mini-breadboard kit with 10 IC capacity and low, low price Complete kit \$19.95
PB-101 A compact mini-breadboard at a mini-price, but with expanded 10 14-pin DIP capacity \$29.95
PB-102 mid-size, mid-price \$39.95
PB-103 Everything you need, 2,250 solderless tie points at less than \$0.27 ea. Four 5-way binding posts; one grounded, 24 14-pin DIP capacity; 10 distribution buses; 2 horizontal with 40 contacts each, 3 vertical with 50 contacts each \$59.95
PB-104 3,060 solderless tie points at only \$0.26 ea. 32 14-pin DIP capacity to build an entire system, including power supplies. Four 5-way binding posts; one grounded, three floating. Rubber feet. 14 distribution buses; 4 horizontal with 50 contacts each, 10 vertical with 50 contacts each \$79.95
PB-203 & PB-203A with built-in regulated short-proof power supplies
PB-203 5V, 1AMP regulated power supply (same as PB-203), \$75.00
PB-203A 5V, 1AMP regulated power supply (same as PB-203), +15V, 1/2AMP regulated power supply, -15V, 1/2AMP regulated power supply \$120

PROTO CLIPS

For foolproof, short-proof, power-on DIP in-circuit testing. Bring leads up from crowded circuit boards, for fast signal-tracing, testing, analog injection even wiring unused circuits into existing boards. Unique gripping teeth provide slip-proof connections or test-equipment probes free your hands for other work.

PC-14 (14-pin) \$4.50 ea.
PC-16 (16-pin) \$4.75 ea.
NEW! PC-24 (24-pin) \$8.50 ea.

LOGIC MONITOR

Check logic levels without an expensive scope. The Logic Monitor brings ICs to life as it tests DTL, TTL, ECL and CMOS \$84.95

DESIGN MATES

DESIGN MATE 1 with built-in, regulated, metered power supply to supply unregulated circuit test. \$49.95
DESIGN MATE 2 Complements Design Mate 1. Produces clean, accurate wave forms with variable amplitude and frequency controls. \$64.95
DESIGN MATE 3 Saves design time by measuring and selecting capacitors and resistors to better than 5% Instantly! \$54.95

2N125	1.40	2N1534	1.00	2N2526	4.40
2N173	2.10	2N1535	1.05	2N2527	4.40
2N293	60	2N1543	3.40	2N2538	2.40
2N321	50	2N1544	1.40	2N2600	7.00
2N324	55	2N1549	1.80	2N2605	4.80
2N336	1.00	2N1551	3.90	2N2605A	5.80
2N338A	80	2N1552	3.90	2N2606	3.60
2N388A	82	2N1554	1.90	2N2608	2.05
2N389	8.90	2N1557	1.70	2N2646	1.00
2N393	3.70	2N1613	.40	2N2647	1.50
2N398B	1.04	2N1619	3.90	2N2648	8.90
2N404	30	2N1693	13.90	2N2688	9.00
2N417	85	2N1711	.40	2N2708	.30
2N456	1.30	2N1715	.70	2N2712	.30
2N481	4.90	2N1720	4.80	2N2713	.14
2N487	1.10	2N1893	.36	2N2714	.44
2N508A	40	2N1907	4.80	2N2715	1.00
2N611A	3.50	2N1924	1.25	2N2716	.20
2N512B	2.90	2N1934	9.30	2N2754	5.00
2N514	6.90	2N1935	7.20	2N2802	9.70
2N562A	5.00	2N2060	2.05	2N2833	3.90
2N577C	5.50	2N2080	4.90	2N2860	16.00
2N681	2.80	2N2081A	2.50	2N2857	3.00
2N683	2.90	2N2100	2.90	2N2880	10.90
2N697	2.80	2N2102	4.50	2N2890	3.50
2N697A	5.00	2N2143	1.50	2N2893	9.70
2N699	.66	2N2147	1.40	2N2894	6.00
2N700	3.50	2N2148	.68	2N2895	1.26
2N705	.60	2N2152	3.00	2N2903	4.10
2N706B	40	2N2192	.60	2N2904	.36
2N711	.34	2N2192A	.66	2N2904A	.38
2N718	.60	2N2193	.44	2N2905	.36
2N718	.28	2N2197	2.40	2N2905A	.38
2N718A	.31	2N2217	.80	2N2906	.20
2N720A	50	2N2218	.25	2N2906A	.21
2N741	2.80	2N2218A	.28	2N2907	.16
2N744	.35	2N2219	.29	2N2908	1.26
2N829	2.80	2N2219A	.36	2N2911	21.00
2N834	.35	2N2221	.24	2N2913	.89
2N859	7.90	2N2221A	.25	2N2925	.20
2N894	2.90	2N2222	.24	2N2926	.14
2N918	1.40	2N2225	1.10	2N2947	14.10
2N929	.26	2N2259	1.10	2N2949	5.90
2N930	.28	2N2270	.40	2N2950	6.00
2N960	.45	2N2289	3.60	2N2958	1.90
2N962	.45	2N2290	5.80	2N2969	30.90
2N967	.45	2N2291	5.80	2N2975	3.95
2N976	1.70	2N2323A	2.00	2N3022	11.90
2N984	.95	2N2326	3.30	2N3053	.34
2N1035	1.80	2N2356	5.90	2N3054	.80
2N1132	.20	2N2356A	6.90	2N3055	.84
2N1136	40	2N2359	1.90	2N3060	2.95
2N1137A	1.80	2N2368	.28	2N3066A	1.19
2N1143	1.90	2N2369	.28	2N3107	.78
2N1168	.65	2N2369A	.28	2N3117	1.50
2N1204	1.40	2N2376	.70	2N3178	9.00
2N1302	.50	2N2440	3.45	2N3202	15.90
2N1303	60	2N2465	7.40	2N3209	8.90
2N1305	50	2N2468	1.00	2N3227	2.30
2N1307	.65	2N2475	.54	2N3239	2.90
2N1400	.70	2N2476	.70	2N3247	3.90
2N1404	.48	2N2483	.28	2N3250	.49
2N1408	50	2N2484	.25	2N3307	8.50
2N1420	4.50	2N2492	4.00	2N3308	6.50
2N1456	2.40	2N2501	.95	2N3351	1.90
2N1521	80	2N2511	1.98	2N3323	11.50
2N1523	6.00	2N2518	5.90	2N3324	.80

PREMIUM QUALITY TRANSISTORS

IF IT ISN'T INDUSTRIAL QUALITY OR BETTER, WE WON'T SELL IT TO YOU.

2N3325	.70	2N3663	.21	2N3824	1.00	2N4032	1.90
2N3368	.80	2N3667	.18	2N3824	1.00	2N4037	7.00
2N3375	.40	2N3668	.22	2N3851	7.40	2N4041	1.35
2N3390	.40	2N3668	.28	2N3702	.30	2N4058	4.25
2N3391	.41	2N3669	.19	2N3705	.32	2N4059	6.00
2N3392	.20	2N3670	5.50	2N3706	.21	2N4059	6.00
2N3393	.20	2N3671	3.90	2N3707	.18	2N4060	.25
2N3394	.20	2N3672	2.60	2N3708	.28	2N4061	2.25
2N3395	.22	2N3684	1.80	2N3709	.22	2N4062	2.50
2N3396	.24	2N3684	1.80	2N3710	.22	2N4063	1.85
2N3397	.28	2N3685	1.24	2N3711	.18	2N4064	3.85
2N3398	.26	2N3686	1.24	2N3712	.18	2N4065	2.25
2N3399	.28	2N3687	2.40	2N3713	1.20	2N4066	1.25
2N3400	.28	2N3688	1.80	2N3714	.22	2N4067	1.05
2N3401	.22	2N3689	1.80	2N3715	.22	2N4068	1.05
2N3402	.24	2N3690	1.80	2N3716	.22	2N4069	2.70
2N3403	.26	2N3691	1.80	2N3717	.22	2N4070	3.00
2N3404	.28	2N3692	1.80	2N3718	.22	2N4071	3.00
2N3405	.28	2N3693	1.80	2N3719	.22	2N4072	3.00
2N3406	.28	2N3694	1.80	2N3720	.22	2N4073	3.00
2N3407	.28	2N3695	1.80	2N3721	.22	2N4074	3.00
2N3408	.28	2N3696	1.80	2N3722	.22	2N4075	3.00
2N3409	.28	2N3697	1.80	2N3723	.22	2N4076	3.00
2N3410	.28	2N3698	1.80	2N3724</			



CD-4 DEMODULATOR



TRUE FOUR CHANNEL SOUND

Southwest Technical Products is proud to offer the most advanced CD-4 demodulator available. Our new CD-4 has characteristics superior to anything previously available thanks to the QSI-5022 integrated circuit used in the unit. This IC and the balance of the circuit was designed by Quadracast Systems Inc. under the direction of Mr. Lou Dorren. The QSI-5022 contains all the sub-system functions needed to demodulate a CD-4 disc, from the phono cartridge input to the output drive for the four power amplifiers. It may be used with either an RIAA equalized magnetic cartridge, or a semiconductor cartridge with flat equalization.

INEXPENSIVE

Now anyone can afford to add discrete true 4 channel sound to their system. You no longer need be satisfied with matrix techniques that produce acoustical enhancement, but not true 4 channel sound. The Southwest Technical Products CD-4 demodulator when added to your system will produce four channel sound from a CD-4 encoded disc that will equal, or surpass anything you can buy—no matter what the price.

EASY INSTALLATION

The SWTPC demodulator connects

between the cartridge and the volume-tone control portion of your system. If you did not want tone controls, actually all that would be needed in addition to our CD-4 demodulator would be volume controls for the front and rear amplifiers. The demodulator is self powered from any 115 Volt 60 Cycle line. When normal stereo discs are played on your system a muting system automatically turns off the rear channels. A manual override 2 or 4 channel selector switch is provided on the rear panel.

SIMPLE CONSTRUCTION

As shown in the photograph, the vast majority of the parts mount on the epoxy-fibreglass circuit board. Part numbers and package outlines printed on the top of the board make proper assembly quite simple. Anyone with a minimum of electronic experience should be able to assemble this project without any problems. A copy of the article describing the CD-4 demodulator and assembly instructions are supplied in the kit.

CD-4 Demodulator Kit.....\$50.00 ppd

CD-4 CARTRIDGE

For those who do not already own a CD-4 cartridge, we are offering the "Technics" EPC-451C semiconductor

strain-gauge cartridge at a special low price when purchased with our new CD-4 demodulator kit. This cartridge features a Shibata-type stylus and excellent response out to 50 kHz. This eliminates any chance of "carrier drop-out", or "carrier crosstalk" which result in abnormal noise or distorted sound. The EPC-451C produces a high output (about 30 times that of an average magnetic cartridge) and does not pick up hum from magnetic, or electrostatic fields. Easily replaced stylus.

EPC-451C CD-4 Cartridge.....\$25.00 ppd

TEST RECORD

Lou Dorren has recorded a special test record for Southwest Technical Products Corp. that will allow you to properly adjust your CD-4 demodulator for the best possible sound. This special test and demonstration record is yours for only \$5.00 when purchased with the CD-4 demodulator kit.

CD-4 Test Record.....\$5.00 ppd

WANT MORE INFORMATION?

Send the coupon below and \$0.50 and we will send you by return mail a copy of the article describing our new CD-4 kit along with our catalog of other kit projects.



CD-4 DEMODULATOR

MAIL THIS COUPON TODAY

- Enclosed is \$ _____ or BAC # _____
- or Master Charge # _____ Bank # _____ Expire Date _____
- CD-4 Demodulator Kit Cartridge Test Record

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

\$0.50 Enclosed for catalog & CD-4 Data

Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284


Circle 95 on reader service card

A question for the professional TV Service Technician

What is the signal NOW?

After all the amplifying, levelling, compensating and distributing . . . is it what it is supposed to be?

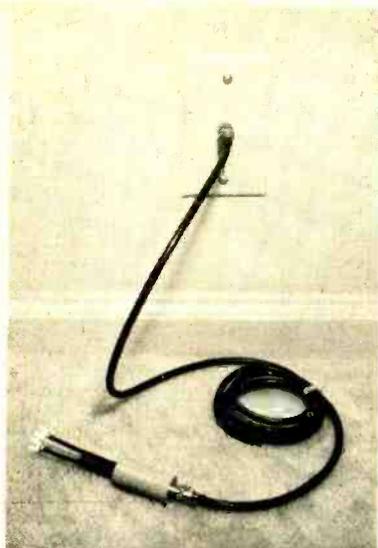You are a professional TV Service Technician . . . and see this "wire coming out of the wall" all the time. Maybe you assume that the signal is O.K. . . . *but do you know?*




Now you can put an end to your guessing about the signal level.

Here is a field strength meter designed exclusively for you . . . at the right price!

MEZZER™ Model TVS

service dealer net \$69.95

- Simple to operate, minimum of operating adjustments.
- Principle of operation similar to output meter and attenuator system of expensive signal generators.
- Standard signal level for proper color reception (1mV to 4mV - 0dBmV to + 12 dBmV) clearly indicated for instant identification.
- Measures signals from 300uV to 30,000uV.
- Uses ordinary 9v transistor batteries, low current consumption ensures low cost per measurement.
- IC amplifier and meter driver circuits.
- Electronic voltage regulation.
- Quasi-peak detector.
- LED/IC battery status system, shows when batteries are below operating voltage.
- Sturdy, high impact ABS plastic case for field use.
- Made in USA.

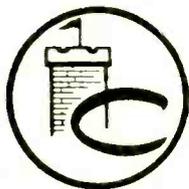

Castle products — advanced technology — modern styling — and they work!

See your stocking distributor . . . or write for more details and complete specifications.

CASTLE ELECTRONICS, INC.

5715 N. Western Ave., Chicago, Ill. 60645
Ph. (312) 728-1800

In Canada: Len Finkler Ltd., Ontario

Circle 96 on reader service card