

BUILD A LOGIC PROBE FOR \$16

\$1.00 ■ MAR. 1977

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

a look at
NEW HI-FI GEAR
for tomorrow's audiophile

get rid of it—
RF INTERFERENCE
in your hi-fi

build a portable
ACTION FOOTBALL GAME
using IC's

easy to build
DIGITAL CLOCKS
using modules

phase-locked-loop
SYNTHESIZERS
channel CB

LEN FELDMAN REPORTS— Binaural and Biphonic Sound


Sitting in this new JVC experimental 4-channel biphonic chair, our Contributing High-Fidelity Editor becomes one of the first to experience listening to binaural sound without wearing headphones



Multimeters ★ Komputer Korner
r's Service Clinic
Solid State ★ Equipment Reports
ed Reports on
hi 610 Preamp and Garrard GT-55 Turntable

308196 DRK 6450M000 14 A JUN78
LLOYD DARKNELL 03
6450 MYRTLEWOOD DR
SAN JOSE CA 95129

GERNSBACK
PUBLICATION

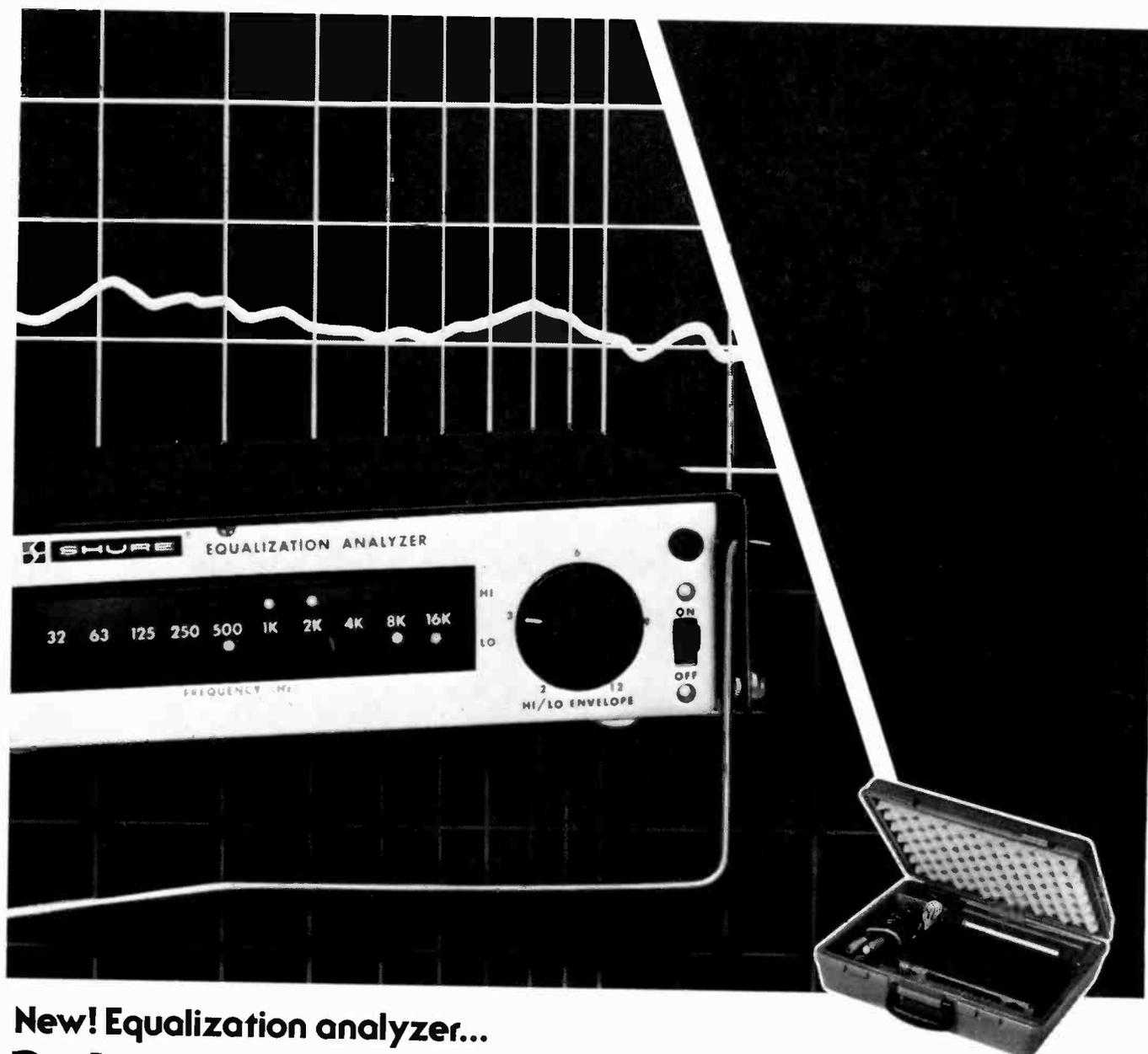

New! Equalization analyzer...
Balance a system...Balance a budget.

Quick and accurate adjustment of sound system frequency response is finally within the reach of most budgets. The Shure M615AS Equalization Analyzer System is a revolutionary breakthrough that lets you "see" room response trouble spots in sound reinforcement and hi-fi systems—without bulky equipment, and at a fraction of the cost of conventional analyzers.

The portable, 11-pound system (which includes the analyzer, special microphone, accessories, and carrying case) puts an equal-energy-per-octave "pink noise" test signal into your sound

system. You place the microphone in the listening area and simply adjust the filters of an octave equalizer (such as the Shure SR107 or M610) until the M615 display indicates that each of 10 octaves are properly balanced. You can achieve accuracy within ± 1 dB, without having to "play it by ear."

Send for complete descriptive brochure AL558.

Shure Brothers Inc.
 222 Hartrey Ave.
 Evanston, IL 60204

In Canada:
 A. C. Simmonds & Sons Limited

MANUFACTURERS OF HIGH FIDELITY COMPONENTS, MICROPHONES, SOUND SYSTEMS AND RELATED CIRCUITRY.

TECHNICORNER

The M615 Analyzer's display contains 20 LEDs that indicate frequency response level in each of 10 octave bands from 32 Hz to 16,000 Hz. A rotary hillo envelope control adjusts the HI LED threshold relative to the LO LED threshold. At minimum setting, the resulting frequency response is correct within ± 1 dB. Includes input and microphone preamplifier overload LEDs. A front panel switch selects either flat or "house curve" equalization.

The ES615 Omnidirectional Analyzer Microphone (also available separately) is designed specifically for equalization analyzer systems.

SHURE[®]

CIRCLE 23 ON FREE INFORMATION CARD

Suddenly, you're the most versatile shop in town.

With this little 25-pound test jig, you can adapt to over 10,000 color sets, 59 different brands. Delta 70° and 90° tube, hybrid, transistor, SCR sweep. Anode voltages to 30kV and more. Regular 4.5kV and 7.1kV focus voltages.

And our new optional In-Line Test Kit lets you handle more than 100

precision in-line chassis, including RCA, Magnavox, Admiral and Sears. (We're the first test-jig manufacturer to offer a kit like this.)

CK3000 comes to you fully assembled, pretested and ready to use. Just plug it in, and you're in business. See it now, at your Sylvania distributor.

GTE Sylvania, Electronic Components Group, 100 First Avenue, Waltham, Massachusetts 02154.

The Sylvania CK3000



Simply the most versatile test jig you can buy.

GTE SYLVANIA

The Control of Power by Sansui.

For the audiophile who wants the finest matched stereo amplifiers and stereo control preamplifiers, Sansui offers the answer — its Definition Series. Look at two of these outstanding components. The Sansui BA 3000 is designed with plenty of power to handle those bursts of percussion and those dynamic fortissimos that give you concert hall presence. The CA 3000 controls and features are a true joy for the creative pro and audiophile who wants to tailor the music to his own personal preferences.

This extraordinary pair is designed for the most demanding tasks; recording studios, sound reinforcement and audiophile home listening. The Definition Series offers the clearest, cleanest fidelity available anywhere. Top of the line Sansui BA 5000, called the "Monster," is one of the most powerful amplifiers available today: 300 watts per channel min. RMS into 2, 4 and 8 ohms from 20 to 20,000 Hz with no more than 0.1% THD.

For complete information on the entire Definition Series visit your local Sansui dealer soon or write directly to us.

The CA 3000 phono preamplifier is within ± 0.2 dB of RAA equalization curve. Offers everything desirable in a preamplifier and more. Triple tone controls. Left and right input and output channel meters. Tape controls for copy and playback. Sensitivity controls. Phono-input capacitance selector.

The BA 3000 stereo amplifier 170 watts per channel, min. RMS, both channels driven into 8 ohms from 20 to 20,000 Hz with no more than 0.05% THD. Safety abounds: 4 jumbo heat sinks (Sansui patent pending); triple protection circuits for ample power protection; and front panel LED power/protection indicator on the front panel to show safe operation. Specially damped output power meter.

Each Definition Series component comes with a test data sheet, complete with all performance characteristics. And Sansui offers a limited 5 year warranty.

SANSUI ELECTRONICS CORP.
 Woodside, New York 11377 • Gardena, California 90247
 SANSUI ELECTRIC CO., LTD., Tokyo, Japan
 SANSUI AUDIC EJRCE S.A., Antwerp, Belgium
 In Canada: Electronic Distributors

Sansui

CIRCLE 56 ON FREE INFORMATION CARD

Radio-Electronics®

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

Electronics publishers since 1908

MARCH 1977 Vol. 48 No. 3

HI-FI STEREO

- 37 **Binaural and Biphonic Sound Today**
Precise spatial effects are possible. Read about a new JVC system that makes it work. by **Len Feldman**
- 40 **Tomorrow's Hi-Fi Gear**
What happened at the Tokyo and New York Hi-Fi shows—Sennheiser infra-red headphone link and more. by **Len Feldman**
- 43 **Get Rid of RFI**
It can really destroy hi-fi reproduction but can usually be cured. Discover what you can do to stop this kind of interference. by **Len Feldman**
- 47 **R-E Lab Tests Garrard GT-55**
A new multiple play turntable system rates high in our report.
- 49 **R-E Lab Tests Nakamichi 610 Preamp**
Outstanding quality in performance and construction.

BUILD ONE OF THESE

- 54 **Easy To Build Digital Clocks**
Semi-kits speed assembly. Roundup of available modules. by **Fred Blechman**
- 60 **Action Football Games**
Plays like the real thing. IC circuit-board construction makes it easy to duplicate. by **Rudy Graf & George Whalen**
- 76 **Tone Probe for IC Testing**
Checks digital IC's. Audible tones tell you high or low. Costs under \$16.00. by **Larry Fort**

TEST EQUIPMENT

- 34 **R-E Reports on Data Precision 175**
A digital multi-meter worth looking at.
- 69 **All About Analog Multimeters**
Part III—Concluding section of this comprehensive report. by **Charles Gilmore**
- 87 **R-E reports on Heath IP-2718**
New power supply works well. You build it from a kit.
- 94 **R-E reports on Switchcraft 1002**
Cable tester that really does a job.

CB RADIO

- 58 **Phase-Locked Loop**
Part II—How Motorola's XC3390 PLL frequency synthesizer works. by **Robert F. Scott**

GENERAL ELECTRONICS

- 4 **Looking Ahead**
Tomorrow's news today. by **David Lachenbruch**
- 22 **Komputer Korner**
Stacking computer data. by **Tim Barry**
- 52 **Auto Search Finds the Cassette Program**
New circuit looks for and looks on to the music passage you want to hear. by **Karl Savon**
- 80 **State-Of-Solid State**
Music generating and synthesizing IC's. by **Karl Savon**

TELEVISION


- 81 **Service Clinic**
Lightning protection. by **Jack Darr**
- 82 **Reader Questions**
R-E's Service Editor solves reader problems.

DEPARTMENTS

- | | | | |
|-----|---------------------------|-----|--------------|
| 108 | Advertising Index | 6 | New & Timely |
| 12 | Advertising Sales Offices | 102 | New Books |
| 109 | Free Information Card | 88 | New Products |
| 14 | Letters | 103 | Next Month |

ON THE COVER

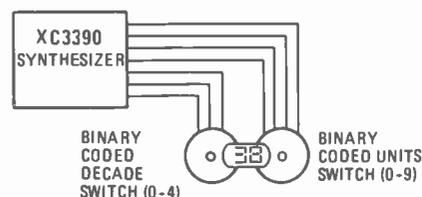That's Len Feldman sitting in JVC's special biphonic chair. If you want to know what he is hearing, see our special story starting on page 40.



PLL FREQUENCY SYNTHESIZERS are hot. Here's how BCD switches deliver binary signals to the synthesizer IC..... see page 58



INFRARED SIGNALS link these headphones to the amplifier. For the story behind them and other new equipmentsee story on page 40

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies \$1.00. © 1977 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

Video horserace is on: The Japanese government, prodded by parliament, has urged videocassette recorder manufacturers to establish a single standard system. Although four separate, and incompatible, systems have already been introduced on the Japan home market, the race seems to be narrowing down to two somewhat similar—but, once again, incompatible—systems. These are the Sony Betamax, which has a large lead in terms of number of machines produced, and the Japan Victor Corporation (JVC) VHS, or Video Home System. The VHS currently offers two-hour recording and playing time on a single cassette, compared with one hour for the Betamax, but it's known that Sony is preparing a new version of Betamax that will double the playing time of its standard cassette.

Japanese manufacturers are choosing up sides, and since no American manufacturers are known to be preparing their own entries in the field, this should set the pace for this country. In addition to JVC, the VHS system now has been chosen by Hitachi and Sharp. Matsushita, Japan's No. 1 television set maker and JVC's parent company, has its own system (VX-2000), but it has indicated that it may add VHS. Mitsubishi is also believed to be in the VHS camp. Toshiba and Sanyo are pushing another system (V-Cord II), but Toshiba is waivering and presumably will decide between VHS and Betamax. The question in many minds is whether Sony has enough momentum going for its Betamax to offset a massive challenge from VHS. How important are these Japanese maneuvers to us? Well, one major American manufacturer (which asks not to be identified) has told us that it will manufacture videotape decks to the specifications of the format that wins in Japan.

VTR turn-off: Three home videocassette recorders are now on sale in the United States—Sony's Betamax, Sanyo's V-Cord II and Quasar's "Time Machine" VR-1000. The strong success of Betamax, whose sales last year totaled 25,000 to 30,000 units and exhausted virtually all supplies, is worrying the movie makers, as evidenced by the suit filed by Universal Pictures and Walt Disney Studios against Sony (**Radio-Electronics**, February, 1977). Now the Motion Picture Association of America is looking into the situation, seeking a technological—rather than legal—solution to the problem. The MPAA has signed a contract with Bell & Howell for the development of a system that would make it impossible for consumers to tape certain copyrighted programs.

The idea would be to transmit along with the program (probably in the vertical interval between pictures) a signal which would prevent home videotape machines from recording. This would be a lock-and-key situation, requiring special equipment at both the transmitting and receiving ends, and appears to pose some legal as well as technical problems. The electronics work may be the simplest part. After technical specs are developed, it would be necessary to get FCC approval

for the transmission of the special anti-taping signal and Congressional legislation to require all VTR manufacturers to include in their products circuits which would automatically make it impossible to record programs which are transmitted with "no-no" signals. Or MPAA could try to get VTR manufacturers to agree to include such circuitry voluntarily. Fat chance.

Warwick becomes Sanyo: Sanyo Electric of Japan has purchased Warwick Electronics, which manufactures television sets, mainly for Sears Roebuck. This latest purchase of an American television manufacturer by foreign interests leaves only seven American-owned TV makers in a field which once had more than 100. The remaining U.S.-owned manufacturers are Admiral Group (part of Rockwell International), General Electric, Curtis Mathes, RCA, Sylvania, Wells-Gardner and Zenith. There are actually 10 if you include Andrea Radio Corp., which is principally a regional manufacturer in New York; Heath Co., which makes TV kits, and Advent, manufacturer of consumer projection TV.

Other acquisitions of American TV companies by foreign-controlled organizations in recent years have been Matsushita Electric's purchase of Motorola's TV business (now Quasar) and North American Philips' acquisition of the Magnavox Co. The television-manufacturing portion of Warwick, which was controlled by Whirlpool Corp., has been re-named Sanyo Manufacturing Corp. What is left of Warwick, unaffected by the sale, is now Thomas International, manufacturer of Thomas electronic organs. Sanyo plans to continue the manufacture of color TV consoles in the former Warwick Forrest City, Ark. plant. The purchase puts Sanyo into contention for the title of third-largest supplier in the American television market (Sanyo also markets here under its own brandname and various private labels). Other contenders for the No. 3 spot are Magnavox, Sony and Matsushita (the latter selling under Panasonic, Quasar and private labels).

LCD TV projection: Television manufacturers are watching with interest a project by Hughes Aircraft, that could conquer one of the major problems of home projection TV—lack of brightness. Hughes' Dr. Alex Jacobson heads a team which has developed a breadboarded color TV projector using a liquid-crystal light valve to modulate the beam of an external light source, such as a xenon arc lamp. (Existing home projectors use cathode-ray tubes as light sources.) The color projector has three LCD's—one for each color—and uses dichroic mirrors to converge the picture into a single lens system. There are still some technical problems, but the Hughes engineers are confident they'll have a pre-production prototype of a reasonably priced super-bright projector within a year.

continued on page 101

TUNER SERVICE CORPORATION


SUBSTITUNER



\$4995
U.S.A. ONLY

WITH CABLES

ONE YEAR
GUARANTEE

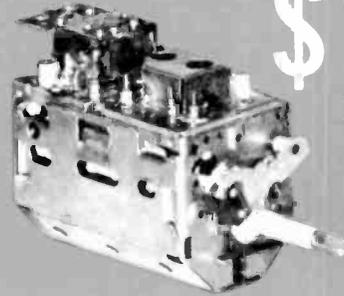

\$1095
U.S.A. ONLY

FEATURES

- A UHF Tuner with 70 channels which are detented and indicated just like VHF channels.
- A VHF Hi Gain Solid State Tuner.
- AC Powered.
- 90 Day Warranty.

Demonstrate the ***SUBSTITUNER*** to your customers and show improved reception with their TV sets.

You may place your order through any of the Centers listed below.

REPAIR

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$10.95
UHF/VHF COMBINATION (U.S.A. ONLY) \$17.95

MAJOR PARTS AND SHIPPING CHARGED AT COST

- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

UNIVERSAL REPLACEMENT TUNER \$13.95 (U.S.A. ONLY)

- This price buys you a complete new tuner built specifically for this purpose.
- All shafts have a maximum length of 10 1/2" which can be cut to 1 1/2".
- Specify heater type parallel and series 450 mA or 600 mA.

CUSTOMIZE

- Customized tuners are available at a cost of \$14.95 and up (U.S.A. Only).
- Send in your original tuner for comparison purposes to any of the centers listed below.



WATCH US
GROW

HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812/334-0411
ALABAMA	BIRMINGHAM, ALABAMA 35212	5623 1st Avenue, North	Tel. 205/592-8150
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91301	10654 Magnolia Boulevard	Tel. 213/769-2720
	SAN MATEO, CALIF. 94402	600 S. Amphlett Boulevard	Tel. 415/348-3292
	MODESTO, CALIF. 95351	123 Phoenix Avenue	Tel. 209/621-8051
FLORIDA	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813/253-0324
	FT. LAUDERDALE, FLORIDA 33309	3516 N.W. 10th Avenue	Tel. 305/566-4882
GEORGIA	ATLANTA, GEORGIA 30310	646 Evans Street S.W.	Tel. 404/756-2292
ILLINOIS	URBANA, ILLINOIS 61801	908 E. Main Street	Tel. 217/384-2052
	SKOKIE, ILLINOIS 60076	5190 West Brown Street	Tel. 312/675-0230
INDIANA	INDIANAPOLIS, INDIANA 46204	111 West St. Clair Street	Tel. 317/632-3493
KENTUCKY	Louisville, Kentucky 40205	2244 Taylorsville Road	Tel. 502/452-1191
LOUISIANA	SHREVEPORT, LOUISIANA 71104	2423 Southern Ave.	Tel. 318/221-3027
MASSACHUSETTS	SPRINGFIELD, MASSACHUSETTS 01108	405 Dickinson Street	Tel. 413/788-8206
MISSOURI	ST. LOUIS, MISSOURI 63132	957 Page Avenue	Tel. 314/429-0633
NEVADA	LAS VEGAS, NEVADA 89102	412 Western Avenue	Tel. 702/384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	1139 Pennsylvania Avenue	Tel. 609/993-0999
	JERSEY CITY, NEW JERSEY 07307	547-49 Tonnelle Avenue Hwy 1 & 2	Tel. 201/792-3730
NEW YORK	ROCHESTER, NEW YORK 14615	37 Pullman Avenue	Tel. 716/647-9180
NORTH CAROLINA	GREENSBORO, NORTH CAROLINA 27405	2914 East Market	Tel. 919/273-6276
OHIO	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216/741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Ave., P.O. Box 10141	Tel. 503/222-9059
PENNSYLVANIA	PITTSBURGH, PENNSYLVANIA 15209	515 Grant Avenue	Tel. 412/821-4004
TENNESSEE	MEMPHIS, TENNESSEE 38111	3158 Barron Avenue	Tel. 901/458-2355
TEXAS	DALLAS, TEXAS 75218	11340 Garland Road	Tel. 214/327-8413
CANADA	ST. LAURENT, QUEBEC H4N-2L7	305 Decarie Boulevard	Tel. 514/748-8803
	CALGARY, ALBERTA T2H-1Y3	P.O. Box 5823, Stn. "A"	Tel. 403/243-0971

IF YOU WANT TO BRANCH OUT INTO THE TV TUNER REPAIR BUSINESS, WRITE TO THE BLOOMINGTON HEADQUARTERS ABOUT A FRANCHISE.

CIRCLE 51 ON FREE INFORMATION CARD

Sun's magnetic field determined by Pioneer 11

Scientists studying data returned by Pioneer 11—now on its way to Saturn—have been able for the first time to determine the structure of the sun's magnetic field. According to the data, it's roughly spherical, envelops the entire solar system (probably as far out as the orbit of the planet Pluto), extends several billion miles above the sun's north and south poles and is split into northern and southern hemispheres by a thin sheet of electric current.

Previous data, from spacecraft traveling in or near the earth's orbit, had recorded confusing and apparently contradictory data. Pioneer 11 was able to make its discoveries because it traversed a hitherto unknown region of space high above the earth's orbit. On its way to Saturn, the spacecraft had been thrown 100 million miles above the earth's plane by Jupiter's gravity while flying by that planet.

The northern and southern magnetic fields of the sun, explained Dr. Edward J. Smith of the Jet Propulsion Laboratory, Pasadena, CA, to a meeting of the American Geophysical Union, are separated by a warped sheet of electric current. The currents tend to circle the sun in the inner solar system, but gradually turn and flow outward in the outer part of the system. As the sun rotates, the warped sheet appears to move up and down, above and below the plane of the earth's orbit. Thus, a spacecraft might at different times see a field in one direction, no field or one in the opposite direction depending on whether it was below, in, or above the sheet of current.

Mysterious source jams radios

Amateur and commercial radio stations have been troubled during the late summer and fall months of 1976, by a powerful pulse transmission. This appeared on several frequencies, and was heard in both the United States and Europe. It was not clear whether the source was one station operating on different frequencies, or several stations. One educated guess is that three stations were involved.

One New Jersey amateur reported an unmodulated pulse signal on about 14.2 MHz. It spread out enough to be audible over about 300 kHz. Severe interference (as an amateur understands the word) was confined to a few kilohertz on each side of the peak. (He had also heard of the same type of interference on the 7-MHz band.)

Using a directional antenna and checking with a California friend who also had a directional antenna, the source was located roughly in the northern part of



QUAD INCREASES MUSIC APPRECIATION

BOOKER T. GIBSON, teacher at the Valley Stream South High School, NY, after "some discouraging moments in teaching" seventh- and eighth-grade students music appreciation by traditional methods, decided that he "had to use some new ways. . . . So," he says, "I started to bring my own SQ full-logic equipment to school."

The students reacted to the modern approach and their enthusiasm spread to parents and eventually to the school administration, who finally bought a permanent SQ quad system for the classroom. Mr. Gibson, a former jazz pianist who is a lover of classical music, says, "I think it's helped tremendously in increasing the enthusiasm of my students for all types of music."

European Russia, possibly in the Leningrad area. Purpose of the transmission was not clear. "It sounded like an ionosphere sounder," he said. Power was high and the signal was strong, though few other signals were heard from the same direction.

Commercial and maritime stations also reported the same type of transmission. One East Coast station measured the signals at different times on 12.393, 16.523, 22.080 and 22.032 MHz. Interference was strong on the peak frequencies, dropping off to each side. This type of thing, the informant pointed out, was not uncommon—signals were often encountered where they apparently had no business being. The usual procedure in such cases was to inform the FCC, who would track down the interference and take any necessary steps.

Inquiries made around the middle of November indicated that at that time the interference had not been heard for a week or two. It was suggested that the

station or stations may have shut down or been shifted to a non-interfering frequency after the publication of articles on the subject by the Washington Star and the New York Times.

CB workshops begin operation in 1977

A series of training workshops in CB servicing (including the second class radiotelephone license) will be conducted by Forest Belt in various parts of the country during 1977. Mr. Belt is a leading teacher and writer on electronic subjects, and a former editor of *Radio-Electronics*.

The workshops are divided into two parts:

Section A devotes three days to fundamentals of CB communication, AM and single-sideband transmitters and receivers, 40-channel phase-locked-loop circuits, frequency synthesizers, etc. Trouble-shooting techniques, performance measurements, alignment, and tran-

continued on page 12

Find semiconductors fast.



With the new, updated Mallory PTC Semiconductor Product Guide.

Instead of looking all over for replacement semiconductors, just open the guide.

There's new indexing and cataloging for fast, easy access to the electrical and physical parameters of each PTC product. Plus, a listing of thousands of semiconductors, each cross-referenced to Mallory PTCs.

It's the authoritative source-book and cross-reference for transistors, zener diodes, diodes, high-voltage rectifiers, color crystals, integrated circuits, field-effect transistors.

Now it's easier than ever to get Mallory performance and reliability in your semiconductor replacement parts.

See your Mallory distributor or give him a call, today.

MALLORY

MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.

Box 1284, Indianapolis, Indiana 46208; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • DURATAPE® • Resistors • Semiconductors • SONALERT® • Switches • Fastening Devices
DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

CIRCLE 65 ON FREE INFORMATION CARD

NRI BRINGS "POWER-ON"
 TRAINING TO YOUR HOME...
 FOR QUICKER, EASIER
 LEARNING AND
 FASTER EARNING

NRI FIRSTS

First and only school with designed-for-learning Quadraphonic Audio Center with four SP14 speaker systems. This solid state SQ™ system is designed so that you perform meaningful experiments at every stage of assembly . . . for thorough training in audio technology.



™Trademark of CBS, Inc.

You get trouble-shooting experience from the chassis up . . . with NRI's unique training equipment.


The "firsts" described here are typical of NRI's over 63 years of leadership in electronics home training. When you enroll as an NRI student, you get the technical knowledge and the priceless confidence of "hands-on" experience sought by employers in communications, TV-audio servicing, computers, and industrial and military electronics. NRI training is designed for your education . . . from the educator-acclaimed Achievement Kit sent the day you enroll, to bite-size, well illustrated, easy-to-read lessons programmed with designed-for-learning training equipment.

NRI Firsts make learning at home fast and fascinating. More than a million have come to NRI for home training. Professional TV/Audio technicians who learned their profession through home training rate NRI as first choice by far, over any other school.

SEND FOR THE FREE FULL-COLOR CATALOG . . . for full details on NRI home training. There is no obligation . . . *no salesman will call.*

First with an electronics Discovery Lab™. This self-contained advanced solid-state lab gives you fast, hands-on access to fully-powered semiconductor circuitry. NRI is the only school with all these modern solid state component experiments in: bipolar and field effect transistors, Zener diodes, light-emitting diodes, SCR's and phototransistors.


™McGraw Hill CEC

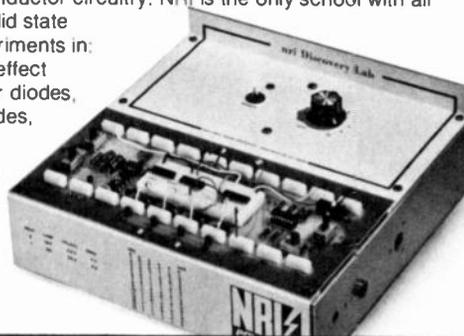

First and only school with new Optical Transmission System engineered to allow you to analyze digital and analog signal transmission via light beam. Systems you build use LED and phototransistor technology, simulating basic principles of laser communications as used in video disc home entertainment systems.

First and only school with designed-for-learning 25" diagonal solid state Color TV complete with cabinet. This solid state set was designed by NRI's own engineers from the chassis up so that students can perform over 25 in-set experiments during construction, including valuable "Power-On" trouble-shooting.

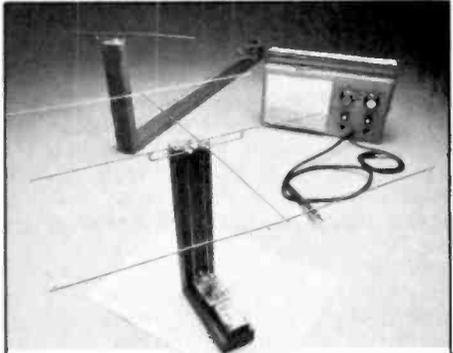First and only school with a portable CMOS digital frequency counter engineered by NRI to give you experience in the newest types of digital systems coming into expanded use in consumer electronics.



First and only school with an Antenna Applications Lab engineered to give you a thorough understanding of practical communications antenna requirements. You assemble and test several different types of antennas and matching sections, measuring gain and radiation patterns.



First and only school with a solid state regulated power supply engineered by NRI to give you experience with modern power supply designs; to give you a premium power supply for your NRI Transceiver, or to use in trouble-shooting mobile equipment.



First and only school with designed-for-learning, 400-channel, digitally-synthesized VHF Transceiver to give you the only fully-up-to-date 2-meter equipment for complete training in commercial, amateur, and CB communications. The design incorporates circuitry and components representative of the latest state of the art. Circuitry is on five plug-in circuit cards to take full advantage of NRI "Power-On" training.

First and only training with an actual programmable digital computer to give you the only home training in machine-language programming . . . essential to trouble shooting digital computers. Extra Memory Expansion Kit doubles memory size for practice in advanced programming techniques.



If card is missing, write to:

NRI Schools
 McGraw Hill Continuing
 Education Center
 3939 Wisconsin Ave.
 Washington, D.C. 20016

sistor and integrated circuit testing will also be covered.

Section B, an advanced two-day workshop, covers FM communications and equipment as used in marine, police, taxi and other two-way mobile systems. A Second Class Radiotelephone option is offered. The radiotelephone license is necessary for any technician who services CB or other transmitting equipment.

Workshops will be held in Indianapolis, IN, January 24-28; in Oakland, CA, February 28-March 4; San Diego, CA, March 7-11; Phoenix, AZ, April 4-8; Denver, CO, April 11-15, and San Antonio, TX, April 25-29.

For further details, schedule of locations, rates, enrollment applications, etc., write Forest Belt's Training Workshops, Box 69120, Indianapolis, IN 46268.

Sharon Penix, Samuel Ford are Gernsback Award winners

This month's first-prize winner of the Gernsback Award, a check for \$150 sent to an outstanding student in each of eight leading electronics home study schools, is Samuel R. Ford. He enrolled in the National Technical Schools' Master Course in Color-TV Servicing in March 1975 and had finished three quarters of the course by the middle of 1976. Ms. Penix, this month's second-prize winner, and Mr. Ford, the school says, have "received excellent grades on all lessons completed."



SAMUEL R. FORD

Samuel R. Ford was born and has lived all his life in Hagerstown, MD, with the exception of four years with the Navy in the Orient. In high school, he was "fortunate enough to complete three years of a four-year electronics course," and has had a year and a half of a college physics major. He started his course with

National Schools in March, 1975.

Mr. Ford has been working for the Burroughs Corp. for the last four years, and is now a senior field engineer responsible for the maintenance of about 70 computer terminals and a like number of minicomputers and peripheral adjuncts. The most pleasing thing about his career, he says, is being "constantly challenged by the diversity of the electronic/mechanical repairs I am called on to make."

Mr. Ford has been married 10 years and has an 8-year-old son. Besides electronics, he is interested in astronomy, classical music and guitar.



SHARON ROSE PENIX

Sharon Rose Penix is not professionally in the electronics field, but lives on an Indiana farm, occasionally engaging in the farm work by driving trucks for her father during the harvest season. Her husband works on construction as an operating engineer. She started the course in December, 1975, and had finished three-fourths of it by June, 1976.

A CB'er, her call is KPJ 8579. She uses the CB equipment on the farm and when camping (the Penix's designed and built their own recreational vehicle, "which is difficult to distinguish from a factory model"). Other hobbies, furthered by the rural environment, are flower gardening and attracting wild life to the property. She also collects antique clocks.

Ms. Penix's object in studying radio and television is threefold: First, she is interested in learning more of the "magical world" of electronics. Her second object is to learn a skill that could be an aid to employment; and last—and more immediately important—she wants to keep her own TV and electronic equipment in working order.

Ms. Penix receives a model 280 digital multimeter donated for the purpose by B & K.

R-E

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, KOD-6694
 editor-in-chief and publisher
Larry Steckler, KTX-3644, CET, editor
Robert F. Scott, CET, W2PWG,
 KXK-8533, technical editor
Arthur Kleiman, KTZ-3288,
 managing editor

Jack Darr, CET service editor

Leonard Feldman

contributing high-fidelity editor

Karl Savon, semiconductor editor

David Lachenbruch, contributing editor

Rudolph F. Graf, contributing editor

George Whalen, contributing editor

Vincent P. Cicienia, production manager

Dale Allinson, production assistant

Harriet I. Matysko, circulation director

Sheila Werthing, circulation assistant

Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen

Cover photo by Walter Herstatt

Radio Electronics is a member of the Institute of High Fidelity and is indexed in Applied Science & Technology Index and Readers Guide to Periodical Literature.



Radio-Electronics magazine is published by Gernsback Publications, Inc. 200 Park Ave. S., New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback

Vice President: Larry Steckler

Treasurer: Carol A. Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

EAST

Stanley Levitan, KZA-5580, Sales Manager
 Radio-Electronics
 200 Park Ave. South
 New York, NY 10003
 (212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen, KXD-8396
 Jim Reilly
 The Ralph Bergen Co.
 6319 N. Central Ave.
 Chicago, IL 60646
 (312) 792-3646

PACIFIC COAST Mountain States

Jay Eisenberg, KYF-3277
 J.E. Publishers Representative Co.,
 8732 Sunset Blvd.,
 4th Floor,
 Los Angeles, CA 90069
 (213) 659-3810
 Sales Mart Building
 1485 Bayshore Blvd., Box 140
 San Francisco, CA 94124
 (415) 467-0125

SOUTHEAST

J.E. Publishers Representative Co.,
 214-387-2424

When you're serious about CB only the BEST will do!



All GC CB accessories are 40 channel approved!

SEE THE COMPLETE LINE OF GC CB ACCESSORIES AT YOUR FAVORITE CB DEALER TODAY!

IMPROVE THE PERFORMANCE OF YOUR RIG! COLORFUL CATALOG ILLUSTRATES AND DESCRIBES NEARLY 150 CB ACCESSORIES—ALL 40 CHANNEL APPROVED! FOR YOUR FREE COPY, SEE YOUR FAVORITE CB DEALER TODAY!



GC ELECTRONICS
DIVISION OF HYDROMETALS, INC.
ROCKFORD, ILLINOIS 61101 U.S.A.



METERS...

CB MULTI-METER SWR/PWR & MODULATION METER

Measures R. F. Power in two scales: 0-100 watts, or 0-1000 watts, as well as VSWR and relative modulation. Front panel switches.
Cat.No. 18-155



SWR/FS METER

Accurately measures SWR and FS for peak system performance. For mobile or base station application.
Cat.No. 18-155



MIKES...

POWER BASE MIKE

Built-in two stage amplifier increases range of any transceiver by boosting modulation up to 50 times. Excellent with AM and SSB also. Designed for use with modern, solidstate transceivers, but will greatly increase modulation of older tube type transceivers as well.
Cat.No. 18-000



POWER HAND MIKE

Rugged, powerful, dependable. Power amplified modulation punches through "skip" and interference to increase range. Solid-state circuitry withstands temperature extremes.
Cat.No. 18-010



ANTENNA ACCESSORIES...

TWO POSITION COAX ANTENNA SWITCH

Easy switching of directional to omnidirectional antenna. No changing of connectors from ground-plane to beam antenna. Accepts PL-259 coax connectors. May be used for 52 ohm CB or switching 72 ohm Ham antennas up to 1000 watts.
Cat.No. 18-710



CB ANTENNA MATCH

Improves reception range and permits you to match your system even in adverse weather conditions! Tunes your antenna system to perfect SWR to allow all transmission power to leave antenna. Accepts PL-259 coax connectors. Equipped with dual SWR adjustment controls.
Cat.No. 18-716



THE CB PROFIT GENERATOR



Hickok introduces the first low-cost RF generator designed specifically for 40 channel CB service.

Model 256 \$199.

Here's every signal you need to service CBs with easy precision tuning over all 40 CB channels. Four additional bands cover 100 kHz to 16 MHz to cover any IF. A counter output gives exact frequency monitoring for precision control. Calibrated RF attenuator output provides stable signals from under 1 microvolt to over 100,000 microvolts. An internal modulator gives a 1 kHz, 0-100% tone, and there are provisions for 20 Hz to 10 kHz external modulation. It's all the RF Generator you need, so why pay more? See your Hickok distributor for more information or contact us directly.

Part of the

HICKOK
Comm Line

the full line of professional CB service instruments.

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland Ohio 44108
(216) 541-3060 • TWX 810-421-8286

Letters

NEW BRAINWAVE APPLICATION

Brainwave detection ("Mindpower: Alpha"; July, August, September and October, 1976, issues) has one unexplored area of great usefulness. Alpha and certain other brainwaves tend to signal a lack of concentration on the senses. This can be dangerous when one is driving or operating complex machinery. Using such brainwave detectors in an *opposite* direction to sound a jolting alarm for possible lack of attention could be a great safety innovation.

Some readers may like to look into developing a simple, portable, lack-of-attention or sleep alarm based on brainwave techniques. This should be welcomed by long-distance truck drivers, guards and workers operating almost automatic (and thus boring) machinery—all of which represent danger due to a lack of attention or sleep.

PETER LEFFERTS
Electro-Audio Research Labs
San Martin, CA

SR-51 CALCULATOR

I am another one of the many owners of the Texas Instruments SR-51 calculator. While reading the September 1976 issue of *Radio-Electronics*, I noticed the letter from E. G. Lemmon in the "Letters" column. I had also read Thomas Cox's letter earlier.

As with many calculator owners, I have been exploring the hidden capabilities of my calculator. It may be true that the memory capability of this calculator is as stated in the owner's manual, but I have discovered that there are several uses for the second function key that were not mentioned in my owner's manual.

I found that after pressing the following keys; "2nd", "1", "cos", the display showed an unfamiliar number without a decimal point. After some experimentation, I determined that the display was the same number that was being displayed as before except that it was justified to the least significant digit, or the right hand-digit, instead of the most significant digit. This means that the last three digits that are not normally displayed can be seen. (The calculator calculates to thirteen decimal places, but can accommodate only ten digits in the display.)

A way to demonstrate this is to press the "pi" key. The display should read 3.141592654. After pressing the "2nd", "1", "cos" keys, the number 1592653590 is on the display. These numbers are recognized as pi with the first three digits removed. To return the calculator to its normal operation, press any function key. As far as I can tell, no data is lost in the process, except from operator malfunction.

Some other interesting functions are; "2nd", "1", summation; "2nd", "1", exchange; "2nd", "1", "tan". These all turn off the display for various amounts of time. The first for about one minute-ten seconds; the second, as far as I can tell, indefinitely; and the third for about four seconds. If the operator wishes to return his calculator back to normal operation, just turn the calculator off and then back on again.

The SR-51 may have limited memory, but for me it is an unlimited source of entertainment.

STEVEN L. BUCHHOLZ
Davis, CA

DIODE POLARITY WRONG?

When I built the Electronic Stopwatch (from the November 1975 and February 1976 issues) I found that all diodes (D1—D7) on the printed-circuit board layout have the wrong polarity indicated. The diodes must be reversed in order for the stopwatch to function properly. I completed the stopwatch and am very pleased with the way that it operates. Keep up the good work.

GABRIEL ROTTER
Roseville, MI

We are happy that you were able to troubleshoot the stopwatch and correct the problem. It appears that you are confused about the accepted method of marking diode elements on schematics and parts placement diagrams. On schematics and any other places where the symbol is used, the arrowhead indicates the anode and the bar indicates the cathode. In addition, the cathode terminal may be marked with a plus sign. This indicates the terminal of the diode that will show a positive voltage or polarity when an alternating voltage is applied to the other terminal.—Editor

COUNTDOWN TIMER QUERIES

(A number of readers questioned apparent discrepancies between the schematic diagrams and board layouts for the Digital Countdown Timer in the August and September 1976 issues. Most of the questions were among those included in letter below. Answers—supplied by author George R. Baumgras—appear in italics.—Editor)

The following errors were noted in the Digital Countdown Timer articles in the August and September issues:

1—IC8. Bottom layout shows pins 2 and 3 tied together but not on the schematic.

2—IC9 has the same function as IC8 but pins 2 and 3 are not tied together in the bottom layout. Is one of these wrong?


The 7490 and 7492 can be reset with either pin. Rather than leave an unused floating input to an active circuit, the two

continued on page 16

A new stay-in-touch system for all outdoorsmen.

Hunters

More than doubles the hunting area.

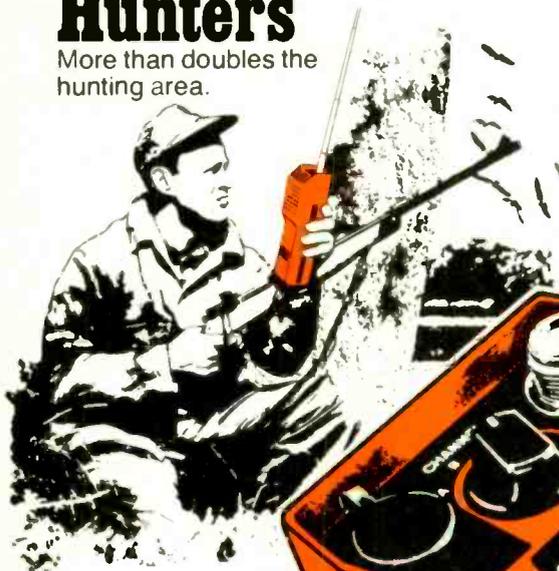

Now, handic's new Outdoor Communicators take 2-way voice contact outdoors.

For hunters, Outdoor Communicators enlarge the game area in a single stroke. They allow the hunting party to spread out of sight-range while still keeping voice contact. And the bright, visible handi orange is an added safety factor in the field.

For boaters, Outdoor Communicators are a great way to zero in on fish when you're out with friends in other boats. Or to chat away idle hours while waiting for a strike. And, because they carry their own power, they're ideal for sailboat purists.


Campers can keep the whole family in touch in the biggest park, zoo, or at the beach. Just push a button to talk and you know exactly where everyone is at any time.

You have four basic units to choose from, with up to 6 channels, 5 watts of power, and a range of 16 miles.

Outdoor Communicators start at \$59 and accept a raft of accessories, including rechargeable ni-cad batteries, Universal Cassette for converting your Outdoor Communicator to a mobile unit or base station, plus numerous antennas for every task.

Boaters

Stay in voice contact over water.

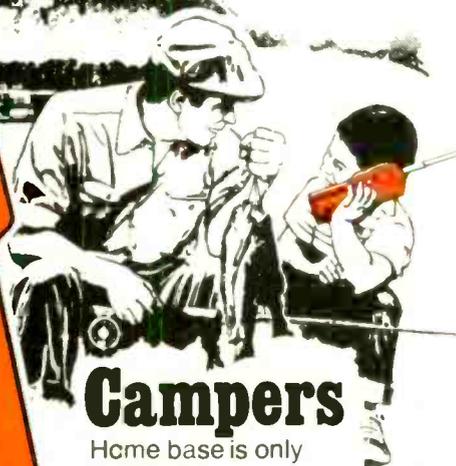

Campers

Home base is only words away.



Outdoor Communicators™



handic®

handic USA, Inc., 14560 N.W. 60th Ave., Miami Lakes, FL 33014

THE ORANGE EQUIPMENT KNOWN FOR PROFESSIONAL QUALITY THE WORLD OVER

handic USA, Inc.
14560 N.W. 60th Ave., Miami Lakes, FL 33014

Please send me more information:

NAME _____
 ADDRESS _____
 CITY _____
 STATE _____ ZIP _____

CIRCLE 77 ON FREE INFORMATION CARD

LETTERS

continued from page 14

inputs should be tied together. This is done during the circuit-board layout.

3—IC9. Bottom layout shows a wire going from pin 4 to pin 13 of IC10. Actually pin 4 is not connected to anything inside the IC. So why the hookup?

"No-function" pins are often used to simplify board layout but are not shown on the schematic. In this case, IC9 pin 4 should go across to IC9 pin 12.

4—The terminal of IC2-b that connects to IC9 pin 1 is not numbered.

Should be pin 6.

5—IC9. On the bottom layout, pin 4 goes to pin 13 of IC10. Since pin 4 is not used internally in IC9, I believe that the whole connection is wrong and pin 12 of IC9 should have been used. Is this correct?

The connection is correct as noted in question 3.

6—IC5, pin 3 goes to pin 2 of IC4 in the bottom layout. I think it should have been pin 2. Is this correct?

IC5 pins 2 and 3 go to IC4 pins 2 and 6. Also refer to question 1.

7—IC5. Pin 5 on the schematic is going to pin 13 of IC6. Pin 5 is the V_{cc} connection so this is not correct. I think it should have been pin 8, not pin 5.

Correct.

8—IC14 has pins 6 and 7 tied together on the bottom layout but not on the schematic?

9—IC16 has pins 2 and 3 tied together on the bottom layout but not on the schematic?

Refer to answer to questions 1 and 2.

10—IC 16. Pin 4 on the schematic goes to ground. Actually, it is not connected inside the IC. Is this necessary?

Should be IC16 pins 6 and 7.

11—IC17. Pins 6 and 7 tied together on bottom layout but not in the schematic?

Refer to answer to questions 1 and 2.

12—IC17. Pin 3 goes to ground on bottom layout but not in schematic?

Refer to answer to question 3. IC17 pin 3 connects to ground on the other side of the board.

13—IC15. R6 is marked 11K on the schematic and 1K in the parts list. Which is correct?

Should be 1K.

14—IC15. Pins 6 and 7 tied together to ground on bottom layout but not in the schematic. Which is correct?

IC15 pin 6 is not connected to pin 7. It goes to IC16 pins 1 and 14.

15—IC15. Pin 11 is tied to pins 1 and 2 on the schematic but pin 10 is tied to 1 and 2 on the bottom layout. Which is correct?

16—IC15. Pins 10 and 11 are tied together on the schematic but not on the bottom layout?

IC15 pin 11 connects to IC15 pins 1, 2 and 10. Add this connection to bottom layout.

17—IC4. Schematic shows pins 2 and 6 tied together and then to pin 2 of IC5. Bottom layout has the connection made to pin 3 of IC5. Which is correct?

Either is correct. Refer to answers to questions 1 and 2.

18—IC6. The resistor connected to pin 6 should be R27, not R20.

Correct. Should be R27, 3.3K.

19—Capacitor C4 is listed as 2.2 μF in the parts list and 22 μF on the schematic. Which is correct?

The correct value is 2.2 μF as in the parts list.

20—Top view of the control board. The EN and ADD labels are reversed on the left side of the board.

OK as shown.

21—On the alarm board we have three 1N4000 diodes. The outlines indicate axial-lead types. Actually, a 1N4000 is a 10-watt, stud-mount 7.5-volt Zener. Shouldn't these diodes be 1N4001's?

Yes. They should be 1N4001's or similar.

WILLIAM L. SCHREIBER
Fullerton, CA

R-E

Rural fire departments using scanning monitors

The fire department of Wicasset, ME, has recently purchased 11 scanning monitors, and a department in Whitefish, MT, bought 21 units, reports RCA's Distributor and Special Products Division, which makes the units in portable, base and mobile models. Scanners are also being used by fire departments in Markleville, IN; Lakewood, NJ; Auburn, VA and Kingston, PA.

The scanners tune continuously over several emergency frequencies and then lock in on any one that is transmitting. They are especially useful on mobile units, alerting the crew to an emergency immediately without having to wait for a message from headquarters.

Fire Chief Gordon Merry of Wicasset reports that members of his department are now able to keep in much better contact with all local fire, police and ambulance calls. In three recent emergencies, he says, the scanners were especially useful. Calls for an ambulance came in on the wrong frequency. Had it not been for the scanners, he said, the calls would have been missed.

240,000 telephone calls an hour switched in new central office

With its 1,000th local-service electronic switching system (ESS), the Bell System initiated its first large-capacity central office switching system, the 1A ESS. The new system went into action last October in Chicago.

The system operates around a new information-processing control unit, the 1A Processor, which operates at more than twice the speed of the earlier No. 1 ESS machines. With its maximum speed of 240,000 calls an hour, the No. 1A ESS becomes the highest-capacity local

switching system in the world. The processor is also used in the No. 4 ESS for long-distance switching.

The new processor is so designed and constructed that it can easily replace the No. 1 processor used in No. 1 ESS exchanges, wherever the call-handling capacity needs to be increased. It can even be switched in without interruption to the telephone service.

Decimal computations abandoned by new sexagesimal calculator

A sexagesimal calculator (one that counts by sixties instead of by tens) has



THE BABYLONIAN MATHEMATICIANS would have welcomed the new Canon calculator.

been introduced by Chafitz, Inc., of Rockville, MD. The instrument, called the *Time Machine*, was designed to automatically add, subtract, multiply and divide hours,

minutes, seconds and tenths of seconds without the cumbersome conversions required with a decimal calculator. In the numerous applications where time is calculated, the instrument reduces calculating time by 50 percent or more. It is, of course, equally useful in other applications requiring circular measurement by degrees, minutes and seconds.

The instrument has both manual and automatic modes, and also converts hours, minutes, etc., to decimal form and vice-versa. A calculator that handles sexagesimal computations as one of its functions has been announced previously (from Casio), but this is the first instrument to make such calculations its primary feature. It sells for about \$50. R-E

Independent News Company, Inc. is pleased to announce a Retail Display Plan available to all retailers interested in earning a display allowance on Radio-Electronics magazine and who purchase the magazines from suppliers other than Independent News Co., Inc., or the publisher.

To obtain details and a copy of the formal contract please write to Director, Retail Sales Division, Independent News Co., Inc., 75 Rockefeller Plaza, New York, N.Y. 10019. Under the display plan in consideration of your acceptance and fulfillment of the terms of formal contract to be sent to you upon your request you will receive a display allowance of 10% of the cover price per copy sold by you. This plan will become effective with all issues of Radio Electronics delivered to you subsequent to the date your written acceptance of the formal Independent News Co., Inc. Retail Agreement is received and accepted by our Company.

40-CHANNEL MOBILE CB AT RADIO SHACK® RIGHT NOW!



**But that's not the only reason
for buying the Realistic® 452
at the nationwide CB supermarket.**

Count on Radio Shack to be right on top of 40-channel CB, with the kind of full-featured values you've come to expect from our Realistic brand. The new TRC-452 gives you effective mobile communications over all 40 channels — the original 23 and the new 17. No crystals to buy — it has a frequency synthesizer with phase-locked loop circuitry. That means ultra-precise frequency control on receive and transmit and dependable service even under rugged on-the-road conditions. For 16 years

Realistic CB's have been designed to meet challenging conditions, and the TRC-452 is no exception. Adjustable RF gain for best reception of strong and weak signals. Switchable automatic noise limiter and adjustable squelch. Illuminated S/RF meter and channel selector. LED modulation indicator. With plug-in dynamic mike, universal mounting bracket, power cable for any 12 VDC positive or negative ground vehicle. Only \$139.95*. So when you go 40-channel — go Realistic!

*Price may vary at individual stores and dealers.



JUST SAY
"CHARGE IT"
AT MOST STORES

SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack®

A TANDY CORPORATION COMPANY • FORT WORTH, TEXAS 76107

Radio Shack operates as Tandy International Electronics in Australia, England, Belgium, Holland, Germany, France, and as Tandy Radio Shack in Japan.

Learn electronics easier... with HEATHKIT


MONEY-BACK GUARANTEE

We're so confident you will enjoy and benefit from these five courses, that if for any reason you are dissatisfied, we will refund the full purchase price of the course text material.

Unique Heathkit Electronics Courses are designed to provide you with a complete overview of basic and advanced electronics.

You learn at your own pace, without pressure or deadlines, and all material is presented in a clear, logical, step-by-step fashion. It's the ideal, effective way to learn about electronics if you're a beginner, or to "brush up" on the latest techniques and theory.

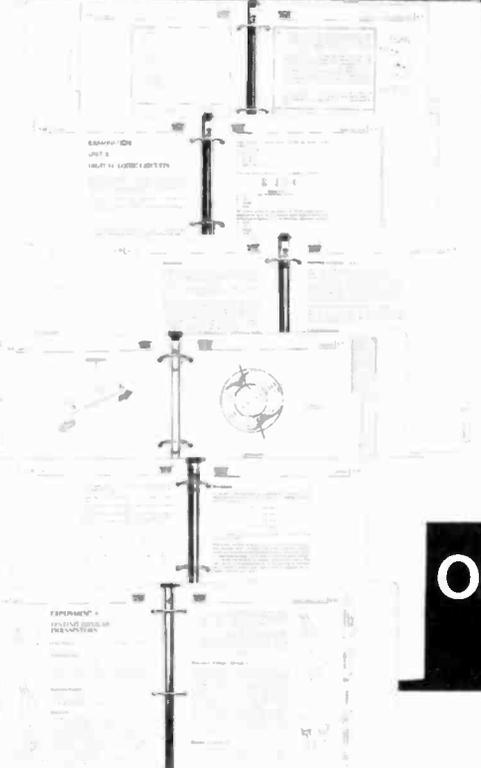Courses start as low as **\$39⁹⁵** (less trainer)



Thousands of people just like you have already learned electronics the easy Heathkit way — and you can, too. The secret is our efficient approach to self-learning with easy, step-by-step "programmed" instructions; audio records to introduce and reinforce key concepts; self-evaluation quizzes to test your understanding; and interesting experiments that let you learn the easy "hands-on" way. All you need is a record player, small tools and a VOM. The optional Heathkit experimenter/trainer is specifically designed to help you do the experiments in each course, and when you finish the course, you can use it to design and breadboard your own circuits. After completing each course, you can take the optional final exam (passing grade 70%) and receive both a Certificate of Achievement and Continuing Education Units, a nationally recognized way of acknowledging participation in non-credit adult education.

**ORDER NOW
and SAVE!**

Buy Any Single Course
with Trainer and —
SAVE \$9⁹⁵

Buy Courses 1 thru 4
with Trainer and —
SAVE \$24⁹⁵

IMPORTANT NOTE: These courses and trainers may qualify for a Federal Tax Deduction. Treasury Regulation 1.162-5 permits an income tax deduction for educational expenses undertaken to: (1) maintain or improve skills required in one's employment or other trade or business, or (2) meet express requirements of an employer or a law imposed as a condition to retention of employment, job status or rate of compensation. In many instances, your employer may re-imburse you in part or in total for taking these courses.

ORDER NOW — get this

FREE WELLER SOLDERING IRON!

Comparable
\$795
VALUE!

Your BONUS for promptness—this FREE \$7.95 comparable value Weller pencil-style 40-watt soldering iron—perfect for assembling your Experimenter/Trainer, other Heathkit projects and a thousand-and-one soldering jobs around the house!

**FREE SOLDERING IRON
OFFER EXPIRES APRIL 30, 1977**

FIRST CLASS
PERMIT NO.
395
Benton Harbor, Mich.

BUSINESS REPLY MAIL (No Postage Stamp Necessary if Mailed in the United States)

Postage Will Be Paid By

HEATH COMPANY

Dept. 20-271

Benton Harbor, Michigan 49022

HEATH

Schlumberger

Order Form/Agreement

HEATH COMPANY, Dept. 20-271, Benton Harbor, Michigan 49022

Please send me the items checked below and include my FREE \$7.95-value Weller Soldering Iron (GDP-1105).

- Send one course (checked below) with the Experimenter/Trainer (ET-3100) at the special price of only \$89.95 plus \$3.00 shipping and handling.
 - DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103)
- Send me the Electronic Circuits Course (EE-3104) with the Experimenter/Trainer (ET-3100) at the special price of only \$99.95 plus \$3.00 shipping and handling.
- Send all four of the courses above (EE-3101, 3102, 3103, 3104) with the Experimenter/Trainer at the special price of just \$199.95 plus \$4.50 shipping and handling.

In addition, please send the following courses (less trainer):

- DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103) for just \$39.95 plus \$1.50 shipping and handling each.
- Electronics Circuits (EE-3104) for just \$49.95 plus \$1.50 shipping and handling.
- Send me the Digital Techniques Course (EE-3201) with its Experimenter/Trainer (ET-3200) for only \$109.95 plus \$3.00 shipping and handling.
- Also send me the IM-17 VOM kit for just \$32.95 plus \$1.50 shipping and handling.

I enclose check money order for \$_____ Michigan residents add 4% sales tax.

Charge to my: BankAmericard Acct. No. _____ Exp. Date _____

Master Charge Acct. No. _____ Exp. Date _____

If Master Charge, include Code No. _____

Signature: X _____

NAME (please print) _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Radio Electronics PC-121

ORDER TODAY-WE PAY POSTAGE!

Remove this label from card, dampen and use on your envelope instead of a stamp and YOU SAVE 13¢ IN POSTAGE!



Only Heathkit Electronics Courses give you all of these practical advantages

- Clear, step-by-step learning instructions
- Audio recordings to personalize text material
- Electronic parts and experimenter/trainer for "hands-on" experiments
- Up-to-date theories and applications on every subject
- Certificate of Achievement plus Continuing Education Units
- Possible qualification for tax exemption (see other side)
- Courses for everyone — from beginners to engineers

Start enjoying the advantages of knowing more about electronics today! Order now!



faster...at lower cost... Self-Learning Courses!

COURSE 1: DC Electronics

An ideal introduction to electronics. Covers current, voltage, resistance, magnetism, Ohm's law, electrical measurements, DC circuits, inductance and capacitance. Discusses matter, atoms, current, flow, voltage rises and drops, series and parallel connections, magnetic fields, voltage dividers, network theorems, more. Includes text, records and 56 parts for 20 different experiments. Average completion time, 20 hours. 2.0 Continuing Education Units and certificate for passing optional final exam.

Course EE-3101 39.95

COURSE 3: Semiconductor Devices

Essential for understanding latest solid-state equipment. Covers fundamentals, diodes, zener diodes, special diodes, bipolar transistor operation and characteristics, FET's, thyristors, integrated circuits and optoelectronics. Discusses holes, current flow, N and P types, biasing, tunnels and varactors, PIN, IMPATT, gain, cutoff and leakage current, SCR's, bi-directional triodes, light sensitive and light emitting devices, more. Includes text, records and 27 parts for 11 different experiments. Average completion time, 30 hours. 3.0 Continuing Education Units and certificate for passing optional final exam.

Course EE-3103 39.95

COURSE 2: AC Electronics

Provides an understanding of most commonly used circuits. Covers alternating current, AC measurements, capacitive and inductive circuits, transformers and tuned circuits. Discusses waveforms, period and frequency, meters, scopes, series and parallel circuits, RC filters, dividers, phase shifts, reactance, vectors, transformer theory and characteristics, series and parallel resonance, more. Includes text, records and 16 parts for 8 different experiments. Average completion time, 15 hours. 1.5 Continuing Education Units and certificate for passing optional final exam.


Course EE-3102 39.95

COURSE 4: Electronic Circuits

Outstanding explanations of basic circuits. Covers basic amplifiers, special purpose amplifiers, operational amplifiers, power supplies, oscillators, pulse circuits, modulation and demodulation. Discusses amplifier functions and configurations, class of operation, audio characteristics, video amplifiers, buffers, IF's, rectifiers, voltage multipliers, voltage regulation, basic oscillators, RC waveshaping, clipping, AM, FM and SSB, modulation fundamentals and more. Assumes knowledge of courses 1 through 3 or equivalent and requires an oscilloscope for some experiments. Includes text, records and over 110 parts for 18 different experiments. Average completion time, 30 hours. 3.0 Continuing Education Units and certificate for passing optional final exam.

Course EE-3104 49.95

LEARN DIGITAL TECHNIQUES

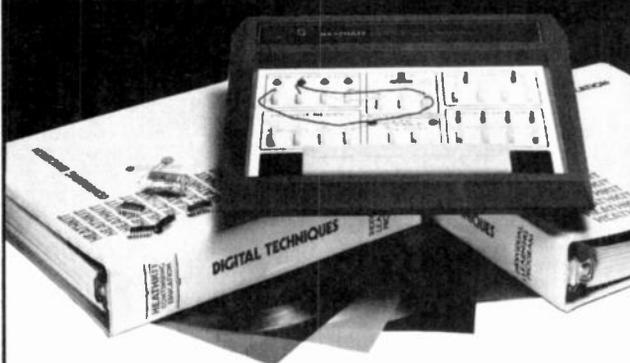

Our most advanced self-learning course prepares you for the world of computers and microprocessors, with particular emphasis on circuit design. Covers digital fundamentals, semiconductor devices for digital circuits, digital integrated circuits, Boolean algebra, flip-flops and registers, sequential logic circuits, combinational logic circuits, digital design and digital applications. Discusses TTL, ECL, CMOS, PMOS, NMOS; integrated circuits; SSI, MSI and LSI; ROM's, PLA's, microprocessors,

computers and more. Assumes completion of Heathkit courses 1 through 4 above, or equivalent knowledge. The special digital techniques experimenter/trainer helps you perform all the experiments in the course, and when you complete the course, build and design your own circuits. Course includes text, records and 44 parts for 24 different experiments. Average completion time, 40 hours. 4.0 Continuing Education Units and a certificate for passing final exam.

ORDER DIGITAL TECHNIQUES PROGRAM AND TRAINER \$109⁹⁵

HEATH IM-17 VOLT-OHM METER

All Electronic Learning Programs require a VOM to make electrical measurements. We suggest the Heath IM-17 as the ideal "all-purpose" unit. All solid state with FET input for better accuracy. Portable battery operation, zero and ohms adjust, accessory probe jack. Comes with DC polarity switch, three test leads; batteries not included. Easy 3 hour assembly.

ORDER KIT IM-17 \$32⁹⁵



HEATHKIT EXPERIMENTER/TRAINER

For use with Heathkit Electronics Courses 1 through 4 — helps you perform all the experiments quickly and easily. Has solderless breadboarding sockets, dual variable power supply for positive and negative voltages, sine and square wave signal source, center-tapped line transformer. After you complete the course, the trainer is ideal for experimenting and breadboarding with your own circuit designs.

Kit ET-3100 \$59⁹⁵

HEATH

Schlumberger

Order Form/Agreement

Heath Company, Dept. 20-271
Benton Harbor, Michigan 49022

Please send me items checked below and include FREE \$7.95-value Weller Soldering Iron (GDP-1105). (See Order Card)

Send one course (checked below) with the Experimenter/Trainer (ET-3100) at the special price of only \$89.95 plus \$3.00 shipping and handling.

DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103)

Send me the Electronic Circuits Course (EE-3104) with the Experimenter/Trainer (ET-3100) at the special price of only \$99.95 plus \$3.00 shipping and handling.

Send all four of the courses above (EE-3101, 3102, 3103, 3104) with the Experimenter/Trainer at the special price of just \$199.95 plus \$4.50 shipping and handling.

In addition, please send the following courses (less trainer):

DC (EE-3101) AC (EE-3102) Semiconductors (EE-3103) for just \$39.95 plus \$1.50 shipping and handling each.

Electronics Circuits (EE-3104) for just \$49.95 plus \$1.50 shipping and handling.

Send me the Digital Techniques Course (EE-3201) with Its Experimenter/Trainer (ET-3200) for only \$109.95 plus \$3.00 shipping and handling.

Also send me that IM-17 VOM kit for just \$32.95 plus \$1.50 shipping and handling.

Michigan residents add 4% sales tax.

I enclose check money order for \$_____ ; or, Charge to my:

BankAmericard Acct. No. _____ Exp. Date _____

Master Charge Acct. No. _____ Exp. Date _____

If Master Charge, include Code No. _____

Signature: X _____

Name (please print) _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Radio Electronics ED-105

KOMPUTER KORNER

Stacks—what they are and how they're used

TIM BARRY

MICROCOMPUTER USERS THESE DAYS ARE CONSTANTLY bombarded with a bewildering supply of new jargon. In addition to the normal proliferation of new hardware terms, we now have to cope with words from software design, systems analysis, and a whole herd of other less well defined disciplines. One of the most commonly used (and abused) terms these days is *stack*. The hardware represented by this picturesque term is often endowed with rather mysterious qualities. Vague utterances about "pushing" and "popping" blend together with questions about "balancing" and "nesting" to create an ample atmosphere of confusion. In this article we will look at two principal types of stacks and how they operate. In doing this we will hopefully dispel some of the myths surrounding these extremely versatile devices.

What is a stack?

In the most general terms, a stack can be considered to be any serial storage system. A stack will have an input end and an output end. All data placed into the stack must pass one element at a time through the input end

of the stack. Once an individual data element is in the stack, it can only be accessed by removing preceding or succeeding data elements until it reaches the output end of the stack. The order in which data is placed into and removed from the stack differentiates between two different types. Figure 1 illustrates the two different types.

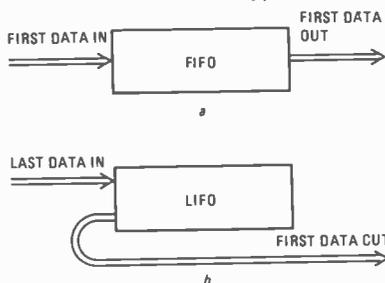


FIG 1

The first type we will discuss is probably the easiest to understand. In these days of crowded facilities and long lines, we, as people, all spend plenty of time in FIFO

(First In, First Out) stacks. The data entered into the input end of a FIFO emerges from the output end in the same order in which it was entered. (See Fig. 1-a.) The principal use of FIFO's is to store arriving data for later use. The next time you are waiting in line, you can reflect on the fact that you are participating in a genuine computer buzz word.

The second type of stack is less commonly encountered in our day to day experiences. A LIFO (Last In, First Out) stack returns data in the opposite order from which it was entered. (See Fig. 1-b.) This means that all the data in the LIFO must be removed before the first data element entered can be recovered. For example, consider an empty bus. Assume that each passenger who gets on the bus goes to the back and no one gets off enroute. When the bus unloads, it should behave like a LIFO, with the last passenger that entered being the first one off. LIFO's are most commonly used in computer programming to save program data and subroutine return addresses.

continued on page 24

Treat yourself to a new direct reading DVM today.



DVM35

POCKET PORTABLE
ANALOG REPLACEMENT
3-digit, 1% DCV,
Battery or AC
Only \$134



DVM36

LAB ACCURATE
POCKET PORTABLE
3½ digit, .5% DCV,
Battery or AC
Only \$158



DVM32

BENCH & FIELD MASTER
3½ digit, .5% DCV,
Battery or AC
Only \$198




DVM38

"PRIME" STANDARD
AT YOUR FINGERTIPS
3½ digit, .1% DCV,
Auto-Ranging
Only \$348

A COMPLETE LINE OF DVMs TO FILL YOUR EVERY NEED OR WANT.

You can be sure more times in more circuits, under more adverse conditions, with greater versatility, accuracy, and meter protection than any other digital multimeters on the market today; and for less money too. 10 Day Free Trial: Try any of these famous DVMs for 10 days. If the DVMs in use don't prove exactly what we say, return them to your Sencore FLPD Distributor.

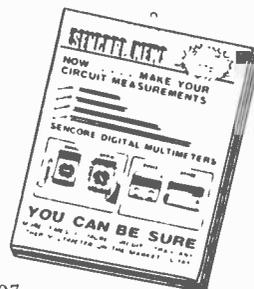Want more information? We would like to tell you all about the Sencore DVMs by sending you a 24-page Sencore News, a six-page brochure, and the name of your nearest Sencore Distributor today... simply write or circle reader's service number.



SENCORE

CIRCLE 19 ON FREE INFORMATION CARD

3200 Sencore Drive, Sioux Falls, SD 57107

If you can see a difference, imagine what you'll hear.



Magnified, you can see record vinyl wearing away.



With same magnification, record vinyl shows no wear.

You're looking at the solution to one of the oldest problems in audio—how to protect records from wear, while at the same time preserving full fidelity.

It's called Sound Guard,* and it's remarkable.

Independent tests show that discs treated with Sound

distortion as "mint condition" discs played once.


A by-product of dry lubricants developed for aerospace applications, Sound Guard preservative is so smooth it reduces friction, yet so thin (less than 0.000003") it leaves even the most fragile groove modulations unaffected.

Len Feldman in Radio Electronics reports "At last!


The long awaited record-care product has arrived.

It preserves frequency response

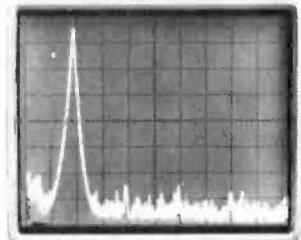
in a kit complete with a non-aerosol pump sprayer and



Test record played first time.

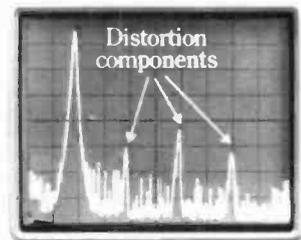

After 100 plays without Sound Guard.

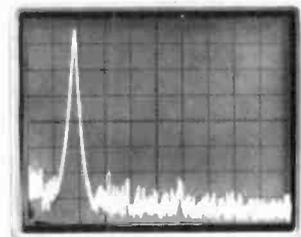

Identical test record after 100 plays with Sound Guard.

Guard preservative played 100 times display the same full amplitude at all frequencies and the same absence of surface noise and harmonic

while reducing distortion and surface noise." It's effective and safe for all discs, from precious old 78's to the newest LP's.

Sound Guard preservative,

velvet buffing pad, is available in audio and record outlets.

Sound Guard® keeps your good sounds sounding good.



*Sound Guard is Ball Corporation's registered trademark for its record preservative. Copyright ©Ball Corporation, 1976.

CIRCLE 44 ON FREE INFORMATION CARD

VALUE & PERFORMANCE

EICO's 30 Years Experience
Assures More Electronics Value
For Your Money!

TEST INSTRUMENTS



NEW!

EICO 388 COLOR BAR GENERATOR

Pocket-size, battery operated with LED Indicator. MOS LSI IC provides 9 digitally controlled, stable patterns. Crystal controlled chroma and timing oscillators. Simply connects to TV's VHF antenna terminals.

Wired \$89.95

EICO 390 FUNCTION/SWEEP GENERATOR

Outstanding features include: Sine, Square, Triangle Waveforms; 2 Hz to 200 KHz frequency range; Linear and Log Sweep; Calibrated attenuator, VCO for External Frequency Control; BNC Front Panel Output.

Wired \$169.95

CB ACCESSORIES



NEW!

EICO 700 CB FREQUENCY COUNTER

Compact in-line mobile frequency counter for the serious CB'er/Hobbyist. Operates automatically on transmit. 10 Hz to 30 MHz. **\$99.95**

EICO LR-3 "LONG RANGER" INLINE PREAMP

Bring in those distant/weak signals. Boosts receiver sensitivity up to 20 db. Automatic transmit/receive switching. **\$29.95**

EICO CM-2 "CHANNEL MONITOR" AUTO-SWITCH

Automatically silences car radio when CB call is received/transmitted. **\$29.95**

EICOCRAFT® IC KITS

**EC-5000
SCA
ADAPTOR KIT
ONLY \$12.95**



Convert your FM radio or receiver to pick up the official FCC-licensed background music service (SCA). IC decoder/adaptor permits hearing uninterrupted, commercial-free music broadcast by many FM stations (For personal, non-commercial use only).

IC PROJECT KITS NOW AVAILABLE

EC-5100 ESP Tester \$10.95
EC-5200 "Decision Maker" \$9.95
EC-5400 Stereo Power Amplifier \$10.95
EC-5500 Stereo Pre-Amp \$9.95
EC-5600 Electronic Lock \$11.95
EC-5700 Universal Power Amp \$8.95

HOBBY/AUTOMOTIVE



NEW!

BW-300 ALPHA BRAINWAVE MONITOR

Lowest cost, battery operated, professional Biofeedback System. IC Circuit design features an active filter and 5-microvolt sensitivity. Complete with stethoscopic earphone, electrode headband and instructions. **Kit \$34.95 Wired \$59.95**

885 "TUNEMASTER" ENGINE ANALYZER

Automatic all-in-one test bench for all 6 or 12 volt ignitions—conventional or transistorized. Giant 6" meter with 6 color coded scales. Complete with tune-up and trouble-shooting manual. **Wired \$59.95**

BURGLAR/FIRE ALARMS



SS-500 BURGLAR/FIRE ALARM SYSTEM

Professional Security System designed for easy do-it-yourself installation. Features EICO FC-100 Control Center with AC/DC automatic transfer to battery operation. Complete system includes Installation Handbook. Add additional sensors, bells, to suit your own needs. **\$159.95**

SD-75 BATTERY OPERATED FIRE/SMOKE ALARM

Ionization-type detector gives earliest possible fire warning. Mounts directly to ceiling with 2 screws. "Beeps" when battery needs replacement. U.L. listed. **\$39.95**

FREE EICO CATALOG

The more you know about electronics, the more you'll appreciate EICO. Every EICO product is designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"BUILD-IT-YOURSELF" and save up to 50% with our famous electronic kits.

For the latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO-283 MaMa Street, Brooklyn, N.Y. 11207

Leadership in creative electronics since 1945.



KOMPUTER KORNER

continued from page 22

FIFO operation

FIFO stacks are most commonly encountered in computer I/O systems and data acquisition systems. They are used to match the data transfer rates between two systems. In this type of application they are often referred to as *storage buffers*. The need for these devices arises when data is transmitted in bursts which are too fast for the receiving device to process. The FIFO is used to store the data in the order in which it arrives during the entire burst. The receiver (usually a computer) can then process the data from the FIFO at its own rate. A common FIFO application of this type is found in computer disk systems. Data to be transferred to or from a disk must be transferred at a higher rate than most computers can manage. To solve this problem, a FIFO buffer is used. The disk transfers a block of data into the FIFO at high speed. The computer can then use the data at its own rate.

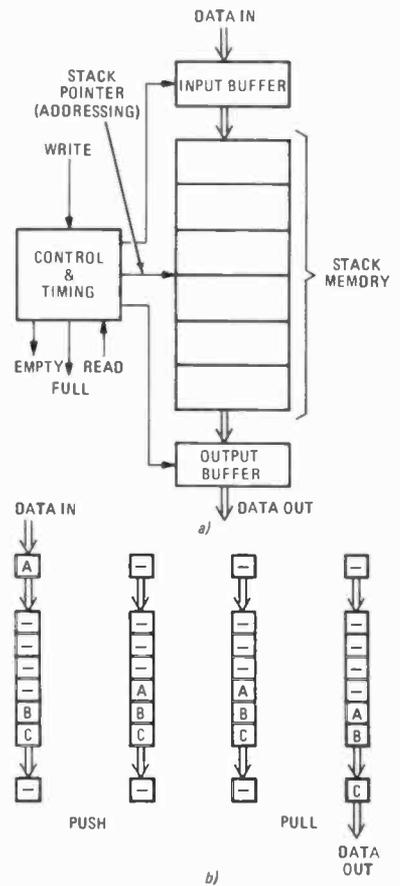


FIG 2


FIFO's can be implemented in either hardware or software. Hardware FIFO's are actually available as LSI integrated circuits from several semiconductor manufacturers. They contain data buffers, registers, a memory, and all required control logic. The block diagram of a typical FIFO (simplified to 6 locations) is shown in Fig. 2-a. In operation, the FIFO accepts data into the input buffer. It then *pushes* the data down in memory until it rests in the first empty location in the memory. When data is read

continued on page 26



WIRE WRAPPING TOOL

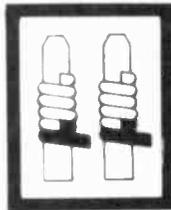For AWG 30, .025" (0,63mm) sq. post,
"MODIFIED" wrap, positive indexing,
anti-overwrapping device



OK MACHINE & TOOL CORPORATION

3455 Conner St., Bronx, N.Y. 10475 / (212) 994-6600 / Telex 125091

NEW

**HOBBY-WRAP
Model BW-630**



Battery
**wire
wrapping
tool**

\$34⁹⁵
ONLY (batteries
not included)
**COMPLETE WITH BIT
AND SLEEVE**


NEW

**HOBBY-WRAP
Model BW-630**



Battery
**wire
wrapping
tool**

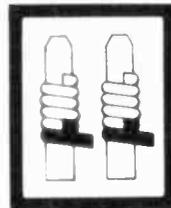\$34⁹⁵
ONLY (batteries
not included)
**COMPLETE WITH BIT
AND SLEEVE**



WIRE WRAPPING TOOL

For AWG 30, .025" (0,63mm) sq. post,
"MODIFIED" wrap, positive indexing,
anti-overwrapping device.



OK MACHINE & TOOL CORPORATION

3455 Conner St., Bronx, N.Y. 10475 / (212) 994-6600 / Telex 125091


from the FIFO, the first data element in the memory is *pulled* into the output buffer. All other data in the memory is then moved down one. If the FIFO becomes full or empty, it sets flags to indicate these conditions. A graphical illustration of a FIFO operation is shown in Figure 2-b.

A FIFO can be implemented using software instead of hardware. In this case subroutines are used to perform the push and pull operations. The flow chart for the push subroutine is shown in Fig. 3-a and the pull subroutine is shown in Fig. 3-b. In actual use, these two programs will both share a

common block of the computer's main memory for the FIFO stack. They will keep track of where the data in the FIFO is by using a *stack pointer*. A stack pointer always indicates the memory address of the most recent data element entered into the stack. (This is true of both FIFO's and LIFO's.)

When the push subroutine is executed, the stack pointer is incremented by one and the new value returned to the memory. The data passed to the subroutine is then transferred into the stack memory at the address now indicated by the stack pointer. For a pull operation, the stack pointer is first tested to see if the stack is empty. If it is, an error flag is set and the subroutine returns. If it is not empty, the data at the first memory address of the stack is obtained. The stack pointer is then decremented by one and re-stored in the

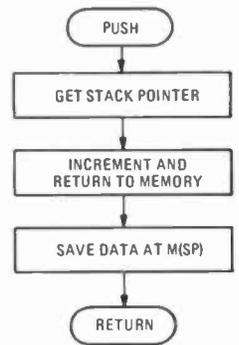memory. All the data in the FIFO is moved down one in the memory. The routine then returns to the calling program with the data.



a

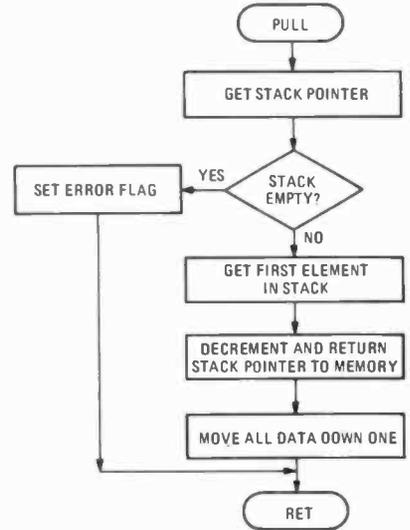


FIG 3

LIFO operation

The LIFO stack is most commonly encountered in systems programming and microcomputer subroutine systems. In systems programming (particularly language processors), the LIFO is used to store data and operands during the evaluation of arithmetic and algebraic expressions. In microcomputer subroutine systems, the LIFO is used to hold program data and subroutine return addresses.

The hardware required to implement a LIFO consists of the same basic hardware we saw used in the FIFO. It is simply connected together in a different configuration. (See Fig. 4-a.) In operation, the data is received into the input buffer just as before. However, all the other data in the LIFO is now pushed down one to make room at the top for the new element. For an output operation, the top element of the stack is *popped* into the output register and all the other data is then moved up in the memory. These LIFO operations are illustrated in Fig. 4-b.

Implementing the LIFO can also be done in software. The flowchart for the push subroutine is shown in Fig. 5-a and the pop subroutine is shown in Fig. 5-b. As with our software FIFO, the software LIFO routines will share a common memory area and stack pointer. When the push subroutine is called,

continued on page 32

Whenever You've Got To...

Tighten,

Hold,

Cut...Strip,

Drive,

Grip,

Pound

or

Cut

You Need Help...

... the dependable help of tools by CHANNELLOCK. Precision made to ease the job. Drop forged of tough, high grade steel to last. Beautiful, high polish finish to make you proud to own them. CHANNELLOCK. Craftsmanship in every detail (at no premium cost).

MEET THE REST OF THE FAMILY SEND FOR OUR FREE CATALOG

CHAN NEL LOCK

CHANNELLOCK, INC., • Meadville, Pa. 16335

Performance features at a price you can afford— and fully backed by Tektronix

Only Telequipment offers you:

TEKTRONIX GUARANTEE

The Telequipment family of oscilloscopes is fully guaranteed by Tektronix, the world's leading oscilloscope manufacturer. This guarantee means that during your first year of ownership, if there are any defects in Telequipment parts or workmanship, you can bring your oscilloscope to any of 35 Tektronix Service Centers across the United States for fast repair by experts—free of charge.

PERFORMANCE FEATURES YOU NEED AT A PRICE YOU CAN AFFORD

Model D61a Designed for portability and easy operation, the D61a is a dual trace 10 MHz 'scope for only \$595. For easy, accurate viewing, the D61a features automatic triggering and bright, stable waveforms on an 8 x 10 cm display.

Model S61 NEW from Telequipment, the S61 is a 5 MHz single trace oscilloscope featuring automatic triggering and 8 x 10 cm display for \$375. This lightweight (14 lb.) instrument has a straightforward, easy to read front control panel—well suited for education applications.



Model D32 When you demand an extremely portable 'scope, the D32 is ideal. Battery or ac line operated, this 10 MHz dual trace 'scope weighs only 10 lbs. An optional shoulder strap or attaché carrying case can be used to take your 'scope into the field. The \$750 price includes batteries and probes.

IDEAL FOR MANY APPLICATIONS

If you're servicing pocket calculators, TV, radio, microwave ovens, alarm systems or dozens of other consumer products, Telequipment 'scopes can do the job for you. Easy viewing and operating make Telequipment ideal for classroom use too.

TELEQUIPMENT... THE CHOICE FOR YOU

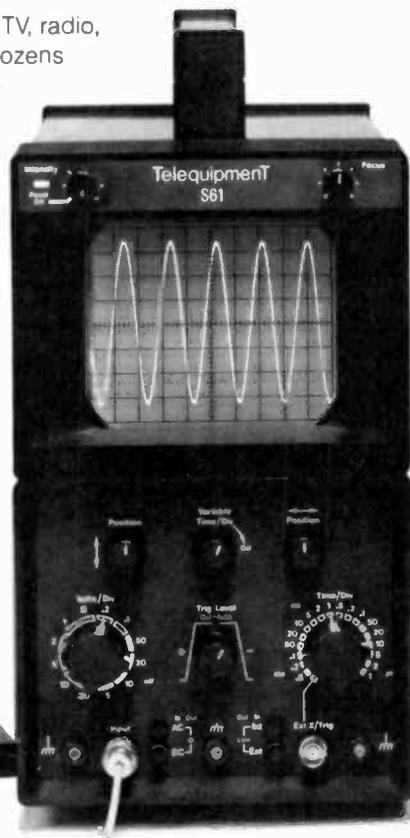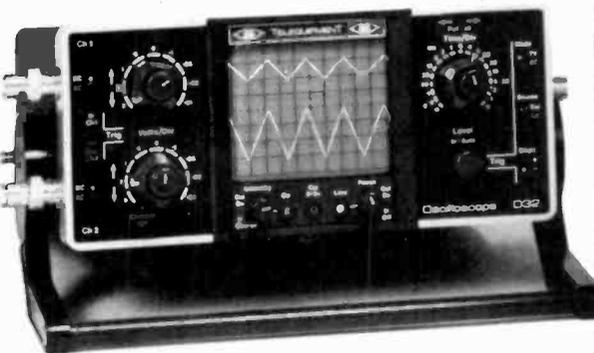Performance features at a price you can afford, plus full backing by Tektronix make Telequipment a wise choice when you're looking for low-cost oscilloscopes.




For more information about Telequipment oscilloscopes, contact your nearest Tektronix Field Sales Office, or write Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97077. For immediate information, call Bill Glaze at Tektronix: (503) 644-0161, extension 7163.



Telequipment is a division of Tektronix U.K. Ltd., a wholly owned subsidiary of Tektronix, Inc. U.S. Sales Price F.O.B. Beaverton, Oregon.

CIRCLE 35 ON FREE INFORMATION CARD

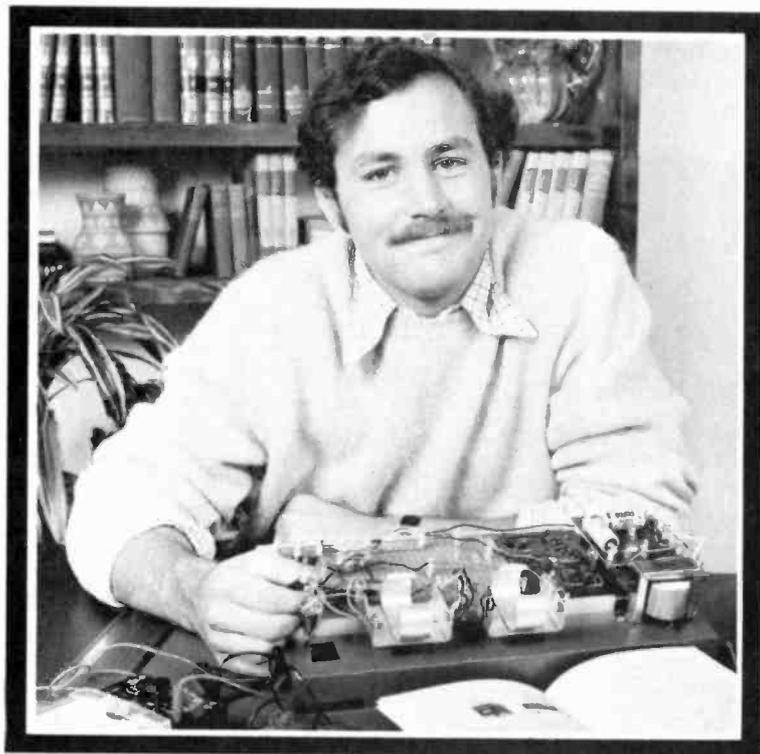**CIE has
a terrific idea
for a few people
who know what
they want.**



If you want success in electronics . . . if you want the skills people are glad to pay for . . . find out about CIE training. It's a terrific idea that can get you on your way to success in electronics troubleshooting.

Let's face it, learning valuable new skills isn't something you just breeze through. Especially in a modern technological field like electronics troubleshooting. You've got to really want success if you're going to build your skills properly.

But, oh boy, the rewards when you do! In today's world, the ones who really *know* electronics troubleshooting find that people . . . even industries . . . look for their help.

What about you? How much do you want the thrill of success . . . of being in demand? Enough to roll up your sleeves and work for it?

Why it pays to build troubleshooting skills.

Suppose the automated production controls on an assembly line break down. Imagine how much money the manufacturer can lose when help doesn't come *fast!* And it takes a skilled electronics troubleshooter to move in . . . locate the problem . . . solve it . . . and get the lines moving again.

Or take a TV station. Breakdowns are costly in broadcasting where time is money. Viewers won't sit forever waiting for sound or the picture to come back. Before they change channels, the station needs to get back on the air again — with the help of a skilled troubleshooter.


No question about it. Building new skills in electronics troubleshooting is an investment in your future. It's well worth the effort.

Why you should get CIE to help you do it.

Troubleshooting starts with *ideas* . . . principles. CIE's Auto-Programmed® Lessons help you get the idea — at your own most comfortable pace. Step by step at home, you explore each principle — each theory — until you understand it thoroughly and completely. Then you start to use it.

How CIE helps you turn ideas into reality.

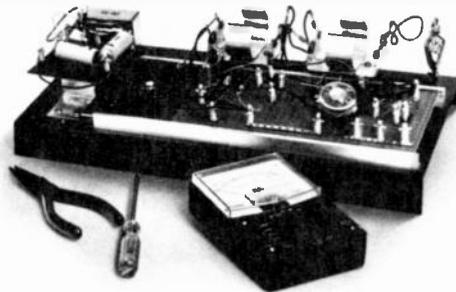If you're a beginner, you start with CIE's Experimental Electronics Laboratory. You actually perform over 200 experiments to help you grasp the basics. Plus you use a 3-in-1 Precision Multimeter to get your first taste of the testing, checking, analyzing steps you take in troubleshooting!



How 3 practical steps help you build troubleshooting skills.

You'll take your first practical step in professional troubleshooting when you build your own 5MHz triggered-sweep, solid-state oscilloscope.

As a trained troubleshooter, you'll use your oscilloscope the way a doctor uses his X-ray machine. As a student, you learn how to "read" waveform patterns on a big, 8cm. x 10cm. screen . . . how to "lock them in" for closer study . . . how to understand and interpret what they tell you.

Your second practical, skill-building step begins when you get your Zenith 19-inch diagonal, solid-state color TV — featuring nine removable modules! Now's your chance to apply the new skills you learned with your oscilloscope!

With CIE's guidance, you perform actual service operations — the kind you'd handle on the job as a trained troubleshooter! Using the TV, you learn to trace signal flow . . . detect and locate malfunctions . . . restore perfect operating standards . . . just as you would with any sophisticated electronics equipment.



Finally, step three rounds out your experience as you work with a completely solid-state color bar generator — actually a TV signal transmitter that produces ten different display patterns on your TV screen!

You study a gated color bar rainbow . . . crosshatch lines . . . dot patterns.

You explore digital logic circuits . . . observe the action of a crystal-controlled oscillator!

This practical, "hands on" training takes concentration and effort. But it's enjoyable and rewarding. And it's a great way to prepare for a troubleshooting career!

Why it's important to get your FCC License.

For some troubleshooting jobs, you *must* have your FCC License. For others, employers often consider it a mark in your favor. It's government-certified proof of specific knowledge and skills!

Almost 4 out of 5 CIE graduates who take the exam get their Licenses. More than half of CIE's courses can prepare you for it . . . and the broadest range of career opportunities!

Free catalog!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name of this magazine. We'll send you a copy of CIE's FREE school catalog — plus a complete package of independent home study information! For your convenience, we'll try to have a representative call to help you with course selection. Mail the card or coupon . . . or write: CIE, 1776 East 17th Street, Cleveland, Ohio 44114.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES . . . I want to succeed in electronics. Send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information!

NAME (please print) _____

ADDRESS _____ APT. _____

CITY _____

STATE _____ ZIP _____

AGE _____ PHONE (area code) _____

Check box for G. I. Bill information:

Veteran Active Duty

RE-05

Mail today!

Gold-ens



Gold plated connector cables for the perfectionist.

- Highest degree of electron transfer and longevity will never corrode or add resistance with age.
- Spring steel strain reliefs.
- Ultra-low capacitance cables.

\$8.00 per matched pair, 1 meter length.
From the people who brought you Discwasher.

At audio specialists worldwide.

discwasher inc.
Columbia, Mo. 65201

CIRCLE 74 ON FREE INFORMATION CARD

KOMPUTER KORNER continued from page 26

the stack pointer is incremented by one and the new value returned to the memory. The data passed to the subroutine is then transferred into memory at the address indicated by the stack pointer. For a pop operation, the stack pointer is first tested to see if the stack

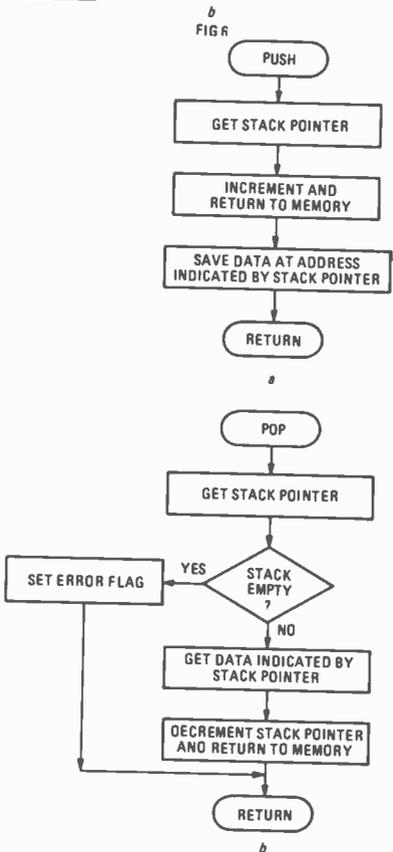
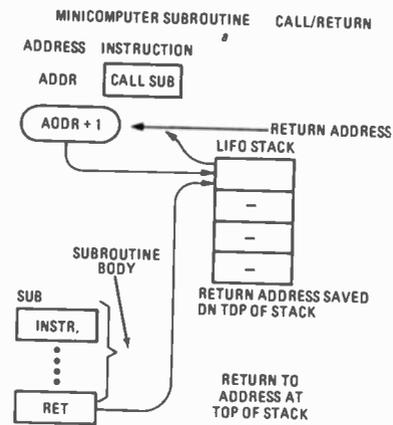
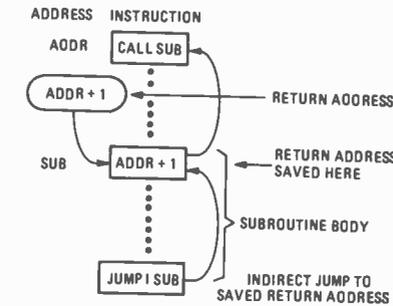


FIG 5

is empty. If it is, an error indicator flag is set and the routine returns. If the stack is not

empty, the data at the address indicated by the stack pointer is obtained. The stack pointer is then decremented by one and the new value stored in the memory. The routine then returns to the calling program with the data.

Stacks and microcomputers

As mentioned earlier, many microcomputers use stacks to implement their subroutine systems. This arose because of the unsuitability of the normal minicomputer way of saving return addresses. When a subroutine is called, most minicomputers save the return address of the calling program in the top location of the subroutine called. A return can then be executed by performing an indirect jump to the first location in the subroutine. (See Fig. 6-a.) This works great in systems where the subroutines are located in read/write memory. It's not so hot when the subroutines are to be located in read only memory. Since most microcomputers make extensive use of ROM, something had to be done. Enter the LIFO.

When a LIFO is used for the subroutine structure everytime a subroutine is called, its return address is pushed onto the stack. When a subroutine return is executed, the top address in the stack is popped into the program counter, thus transferring control to that location. (See Fig. 6-b.) Now this means that all subroutines must be returned in the

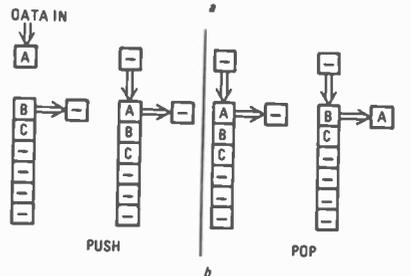
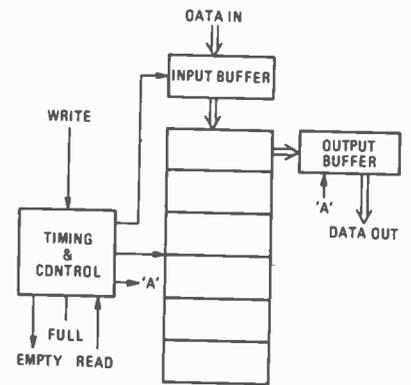


FIG 4

opposite order in which they were called if proper program operation is to be maintained. The number of subroutine calls executed before a return is executed is called nesting. Thus the phrase, "My program is nested five deep", means that the program has called five subroutines before the first return has been executed.

Microcomputer designers took two basic approaches to implementing the LIFO stack for return addresses. The first way was to build the LIFO in as part of the CPU hardware. This method required no special

continued on page 86

SAVE UP TO 50% ON PARTS.

Hobbyist or professional, there are probably a lot of circuits you build just for the fun of it. And a lot you'd like to build, but never get around to.

One reason is the cost of parts. Parts you buy for one project, but can't re-use... because you haven't time to take them carefully apart. Or because of heat and mechanical damage that occur when you do.

Now, there's an easier way that can save you big money on parts *and hours on every project*, as well: *Proto-Board® Solderless Breadboards*.

Now, assembling, testing and modifying circuits is as easy as pushing in—or pulling out—a lead. IC's, LED's, transistors, resistors, capacitors... virtually every kind of component... connect and interconnect instantly via long-life, nickel-silver contacts. No special patch

MODEL	NO. OF TIE-POINTS	14-PIN DIP CAPACITY	SUGG LIST *	OTHER FEATURES
PB-6	630	6	\$15.95	Kit — 10-minute assembly
PB-100	760	10	19.95	Kit — with larger capacity
PB-101	940	10	29.95	8 distribution buses, higher capacity
PB-102	1240	12	39.95	Large capacity, moderate price
PB-103	2250	24	59.95	Even larger capacity, only 2.7¢ per tie-point
PB-104	3060	32	79.95	Largest capacity, lowest price per tie-point
PB-203	2250	24	75.00	Built-in 1% regulated 5V, 1A low ripple power supply
PB-203A	2250	24	120.00	As above plus separate 2-amp +15V and -15V Internally adjustable regulated outputs

*Manufacturer's suggested list
Prices and specifications subject to change without notice.

cords or jumpers needed—just lengths of ordinary #22-30 AWG solid hookup wire.

Circuits go together as quickly as you can think them up. And parts are re-usable, so as your "junk box" builds, you build more and more projects for less and less money.


Before you invest in your next project, invest in a CSC breadboard. See your dealer or order by phone: 203-624-3103 (East Coast) or 415-421-8872 (West Coast)—major charge cards accepted. You've got nothing to lose... and a lot to gain.

CONTINENTAL SPECIALTIES CORPORATION



44 Kendall Street
Box 1942, New Haven, CT 06509
203-624-3103 TWX 710-465-1227
West Coast office: Box 7809, San Francisco, CA
94119 • 415-421-8872 TWX 910-372-7992

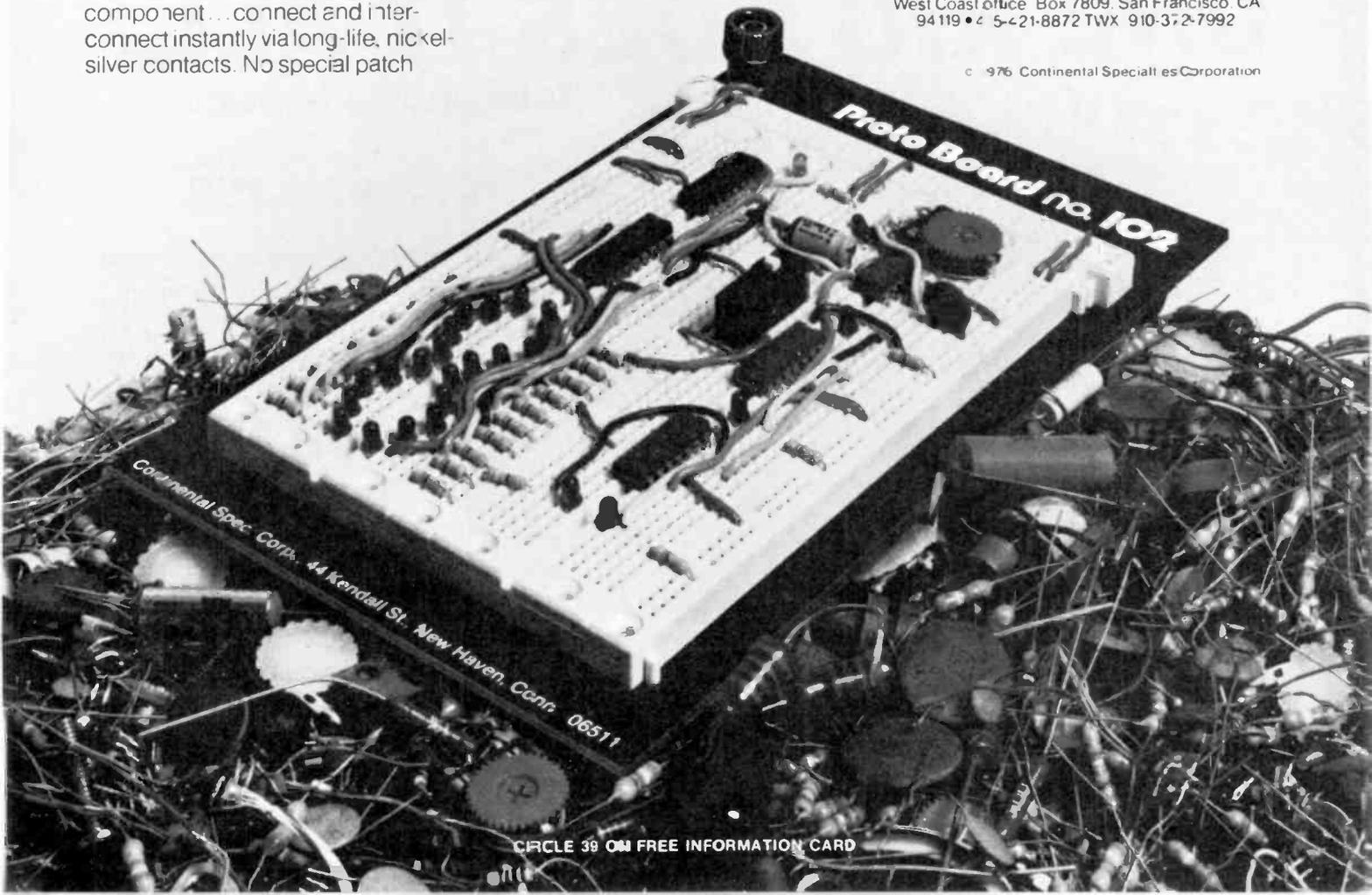© 1976 Continental Specialties Corporation



CIRCLE 39 ON FREE INFORMATION CARD

equipment reports

Data Precision Model 175 Digital Multimeter



CIRCLE 79 ON FREE INFORMATION CARD

THE DATA PRECISION CORPORATION REFERS to their model 175 as a "miniature portable 3½ digit multimeter". They couldn't be more accurate. Miniature and portable are the only words to describe it. The model 175 is only 3.5 deep × 5.5 wide × 1.5-inches high. If you've already gone all metric, 9 × 13 × 4.5

mm. The case is the only little thing about it. The LED display is almost ½-inch high, and bright.

It has all of the functions and ranges needed for a full-sized digital multimeter. AC and DC volts can be read from a 100-millivolt full-scale range up to 1,000 volts. Due to the automatic overranging, this will let you read up to a 100% overrange. The display on the 100-mV scale will read up to 199.9. Only on the highest scale, 1,000 volts, is overrange capability inoperative. The limit on AC volts is 500.

For resistance and current ranges, the overrange works. On the 10-megohm resistance scale, resistance up to 19.99 megohms will be displayed. The AC and DC current ranges are calibrated in milliamperes, and can be read up to 199.9 mA. The lowest resistance range is 100 ohms full-scale, maximum reading 199.9 ohms. Low- and high-voltage ohms scales are used; maximum

voltage of 2.5 volts on HI and 300 mV on LO. This can be set up by the function switch on any ohms range. Incidentally, for the accident-prone, the ohms ranges are able to withstand up to 250-volts RMS AC or DC without harm. As long as you stay out of the raw boost circuits, you're OK.

There are only the two controls and the switch on the front panel. The rest is taken up by the LED readout. The test leads plug into miniature banana jacks at the right side of the case, near the back. The whole thing is so compact that you can easily hold the instrument and the common test-lead in one hand, and the hot test-lead in the other. They have thoughtfully provided a wrist strap with a pivoted ring, to slip over your arm so that you won't drop it. This makes it very nice for getting readings in dark places. You don't have to shine your penlight on the meter to read it! (Where do you get the third hand to read it!) *continued on page 87*

ONE RIG DOES IT ALL!

33KV

Tube and Solid State

THE UNIVERSAL
PJS-298

33KV LEADED GLASS 19" CRT

EIA recommended to protect against dangerous X-radiation

BUILT-IN SPEAKERS

Easy audio checking

40 KV METER

50aU sensitivity monitoring

FRONT CONNECTORS

Convenient cable plug-in

\$298.98 VALUE

SPECIAL INTRODUCTORY OFFER

\$229.95

COMPLETE WITH CRT

OBSOLETE PROOF

Plug in modules for up-dating

TeleMatic

2849 FULTON ST., BROOKLYN, NY 11207
PHONE: (212) 827-1500

ACCESSORIES INCLUDE:

- CRT 90° Extension
- Yoke Extension
- Transverter
- Convergence Load
- Universal Yoke
- Convergence Assembly
- Blue Lateral Assembly
- Anode Extension

SOLD THROUGH DISTRIBUTORS ONLY

PLEASE SEND ME MORE INFORMATION

M-7

NAME _____

ADDRESS _____

CITY _____

STATE _____


ZIP _____

ELECTRONICS BOOK CLUB

invites you to take this
1624-page electronics library
for only

\$ **1.99**

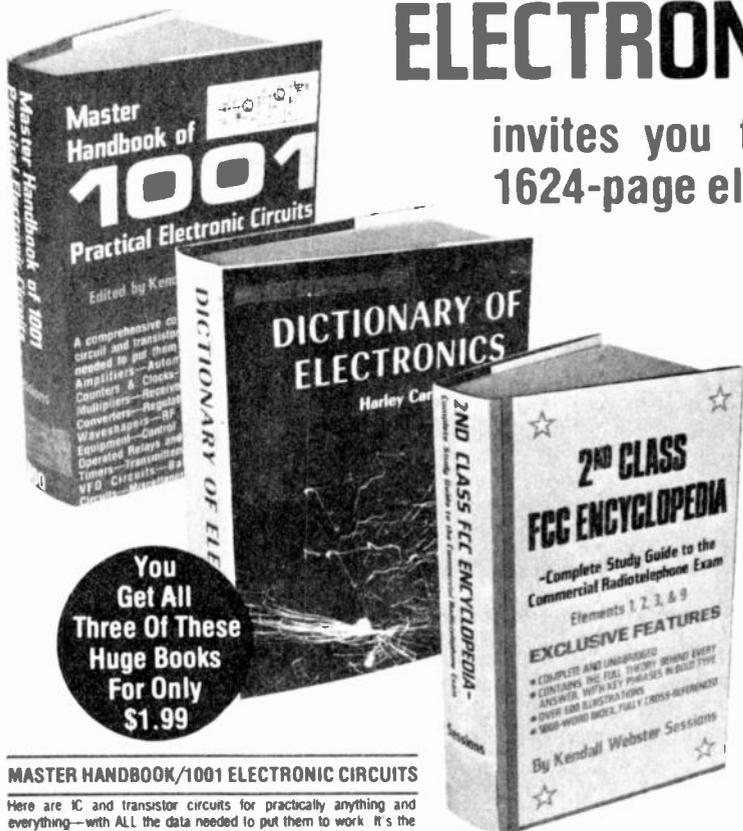with a Trial
Membership in
the Book Club
that Saves you
25% to 75% on
a wide selection of
electronics books



You
Get All
Three Of These
Huge Books
For Only
\$1.99

- ✓ Only \$1.99 for all three!
- ✓ Regular List Price \$33.85.
- ✓ Top-Quality Hardbinding
- ✓ Features huge quick-find index
- ✓ Over 2300 illustrations
- ✓ Contains over 800,000 words
- ✓ 1624 data-packed pages

MASTER HANDBOOK/1001 ELECTRONIC CIRCUITS

Here are IC and transistor circuits for practically anything and everything—with ALL the data needed to put them to work. It's the ideal schematic sourcebook for all active technicians, engineers, experimenters, amateurs—for anyone who must occasionally or regularly construct or adapt electronic circuits for any purpose whatsoever. Each circuit diagram has every component carefully labeled, and every schematic is accompanied by all the info you need to construct the circuit for use in your own individual application. If there are coils to be wound, you'll find full and complete coil-winding details right there on the spot. If special parts are required, you won't have to invest a lot of time and effort before the fact, for it's all there before you in condensed captions. The circuits included are completely up-to-date, and have been designed, built, tested, reworked as necessary, and perfected. You'll find any circuit you're ever likely to need in the pages of this rich volume. Includes an ultracomplete 22-page cross-reference index so you can quickly find the circuit you need. The schematics are classified according to general application. If you're in the business of servicing/repairing commercially built electronic equipment, you're going to especially appreciate the comprehensive Appendix of IC substitutions, which includes base diagrams for most popular ICs, and gives you all the info you need to adapt the IC packages of one manufacturer to the circuit applications of another. 602 pgs., over 1250 illus.

2ND CLASS FCC ENCyclopedia

Truly a one-volume electronics library all by itself—a 602-page supercourse in electronics that belongs on the bookshelf of everyone in electronics. It's as sweeping and all-encompassing as the FCC exam itself. It's a "quick-guide" to learning the answers to the 2nd and 3rd Class FCC exams (plus Element 9, for the broadcast endorsement), as well as an intensive, non-nonsense series of courses that can make you the master of any held related to radio communication. A special feature of this unique guide is the short-form, long-form answer format to hundreds of FCC-posed questions. Whenever possible the answer to a question is divided into the shortest answer needed to satisfy the FCC requirements, a longer answer then shows how any similar question may be answered, and is included for reference or for more complete understanding. Questions appear in italicized type. A boldface type section in most answers enables you to immediately extract from the detailed discussion that portion which directly answers the specific question. These "theory packets" amount to an extremely comprehensive educational approach to the FCC exam, and are just one of the many ways in which this book is one of the easiest-to-use of all radio courses. An extremely complete 5000-word index, fully cross-referenced, provides instant access to any rule, formula, circuit diagram, or technical explanation. 602 pgs., over 600 illus.

DICTIONARY OF ELECTRONICS

This huge, quality dictionary is a handy reference that will serve most of your needs—extremely useful in whatever connection you have with electronics. Defines most all of the electronic terms you will run across in your everyday reading—from alpha particles through zoom lens—including those found in radio, TV, communications, radar, electronic instrumentation, broadcasting, industrial electronics, etc. The concise but clearly written definitions from all the various branches of electronics are of value to technicians, engineers, hobbyists, experimenters, and students. It provides full, complete and easily understandable explanations of thousands of specific electronics terms. A unique feature is the cross-indexing, whereby key words contained in the definitions (words that are defined more fully elsewhere in the book) are printed in small capitals so the user is not left in the dark by any definition. Appendices provide you with still more data—an extensive list of units and abbreviations, graphic symbols used in schematics, component color codes, db conversion tables, data on the electromagnetic spectrum, tube base diagrams, etc. 420 pgs., 487 illus.

Let us send you these three practical, time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club.

Here are quality hardbound volumes, each especially designed to help you increase your knowledge, earning power, and enjoyment of electronics.

These handsome, hardbound books are indicative of the many other fine offerings made to Members important books to read and keep—volumes with your specialized interest in mind.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, broadcasting, electronics as a hobby—you will find Electronics Book Club will help you get the job you want, keep it, improve it or make your leisure hours more enjoyable. With the Club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase your enjoyment of electronics, too.

This Special Offer is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of direct interest to you. Members are annually offered over 50 authoritative books on all phases of electronics.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours—that it is possible to keep up

with the literature published in your areas of interest—and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway—without the savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 3-volume Electronics Library for 10-day inspection. YOU NEED SEND NO MONEY! If you are not delighted, return them within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, P.O. Box 10 Blue Ridge Summit, Pa. 17214

TYPICAL CLUB SELECTIONS (and List/Club prices)
Microprocessor Microprogramming Handbook \$9.95/\$5.95—VHF/UHF Fire, Police, Ham Scanners Service Manual \$9.95/\$5.95—Modern Guide To Digital Logic \$9.95/\$5.95—CB Radio Schematic Servicing Manuals—3 Volumes \$26.85/\$9.95—Color TV Trouble Factbook \$8.95/\$4.95—CBer's Handbook Of Simple Hobby Projects \$6.95/\$3.95—Modern Electronics Math \$12.95/\$8.95—Electronic Music Circuit Guidebook \$9.95/\$5.95—Build Your Own Working Robot \$8.95/\$5.95—Intro to Medical Electronics \$9.95/\$8.95—21 Simple Transistor Radios You Can Build \$6.95/\$3.95—Ham Radio Advanced Class License Study Guide \$8.95/\$4.95—Aviation Electronics Handbook \$11.95/\$7.95—Practical CB Radio Repair \$8.95/\$5.95—Radio Astronomy for the Amateur \$8.95/\$5.95

Facts About Club Membership

- The 3 introductory books carry a publishers retail price of \$33.85. They are yours for only \$1.99 (plus postage and handling) with your Trial Membership.
- You will receive the Club News describing the current Selection, Alternates and other offerings, every 4 weeks (13 times a year).
- If you want the Selection, do nothing; it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- Personal service for your account—no computers used!
- To complete your Trial Membership, you need buy only four additional monthly selections or alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices plus a small postage and handling charge. Prepaid orders shipped postpaid.
- Continuing Bonus: If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.99 will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

ELECTRONICS BOOK CLUB

P.O. Box 10
Blue Ridge Summit, Pa., 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send my 3-volume Electronics Library, invoicing me for only \$1.99 plus shipping. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months, after which I may cancel my Membership at any time.

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(This offer valid for new Members only. Foreign and Canada add 10%) RE-37

CIRCLE 1 ON FREE INFORMATION CARD

CB servicing is PROFITABLE with the B&K-PRECISION 40-channel CB Test Bench



MODEL 1040
\$250

The B&K-PRECISION CB service-master is designed for rapid programmed testing and trouble shooting of any CB transceiver—even 40-channel models!

When used with a scope and signal generator, you can:

- Measure signal-to-noise ratio of CB receiver
- Measure audio output power
- Measure audio distortion percentage
- Measure receiver sensitivity
- Check AGC
- Measure effectiveness of CB noise limiter or blanker (when used with an impulse noise generator)
- Measure squelch threshold
- Measure adjacent channel rejection on any channel
- Measure transmitter AM power output—even mobile!
- Measure SSB power output with TRUE peak-reading RF Wattmeter
- Check AM modulation
- Check SSB modulation with a two-tone test—the only accurate way!
- Measure antenna SWR—even mobile!
- Check the transceiver in the car to determine if the problem is in the antenna system or the transceiver

You can save \$500—\$1,500 in equipment costs because the CB Servicemaster eliminates many of the test instruments you would otherwise need for CB servicing. These instruments, or their functions, are built into the unit:

- Audio wattmeter • Audio generator • Distortion meter • RF wattmeter/dummy load • DB meter • SWR bridge

These instruments—which you should have, if you don't own them already, are all you need to get the maximum use from your CB Servicemaster. And the B&K-PRECISION CB Servicemaster is compatible with most oscilloscopes, frequency counters, signal generators and power supplies on the market today.



MODEL 1403A—3", 5 MHz
Recurrent Sweep Oscilloscope

Checks CB modulation and provides viewing of 27MHz CB envelope when used with the Model 1040. Small, compact and inexpensive, it frees other scopes for more effective use. \$209




MODEL 1640—Regulated Power Supply

Designed especially for CB and other mobile equipment, the 1640 eliminates changes in supply voltage due to load variations. A stable power supply is essential to precise testing of the transceivers. Less than 0.8% variation from zero to full load, 3 amps continuous, 5 amps surge. Adjustable to any output from 11 to 15 VDC. Suppressed zero scale for greater accuracy. Overload protected. \$100



MODEL 1801—
Digital Frequency Counter

To quickly determine the exact frequency of a CB channel, the 1801 automatically displays it for you in large, easy-to-read digits. You can tune oscillators precisely, conduct audio frequency analysis tests. Six digit display is updated five times per second. Accuracy guaranteed to 40MHz; 60MHz typical. \$240

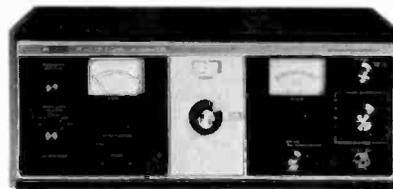

MODEL 2040—40-Channel CB Signal Generator

Covers all 40 channels, AM and SSB with built-in capability. Ultra-stable crystal-controlled, phase-locked-loop frequency generation. Has 5 ppm accuracy. Output attenuator and vernier provide calibrated outputs from 100,000 μ V to 0.1 μ V for receiver sensitivity measurements. Includes EIA standard noise test signal generator to check receiver noise suppression. Internal 400, 1000 and 2500 Hz modulating frequencies—can also be externally modulated. Internal protection against 5W RF input. \$475

B&K PRECISION DYNASCAN CORPORATION
Makers of Cobra CB Equipment

6460 W. Cortland Avenue, Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics, Ontario

For additional information, contact your B&K-PRECISION distributor for our comprehensive brochure describing the operation of the Model 1040 CB Servicemaster and the CB Service Center—or write us for your free copy.


CIRCLE 71 ON FREE INFORMATION CARD

ADD DIMENSION TO STEREO

Binaural/Biphonic Sound

A recent revival of an old technique that provides precise spatial localization of sound sources. JVC's recent introduction of a combination headphone/microphone brings this technique within easy grasp of the home recordist

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

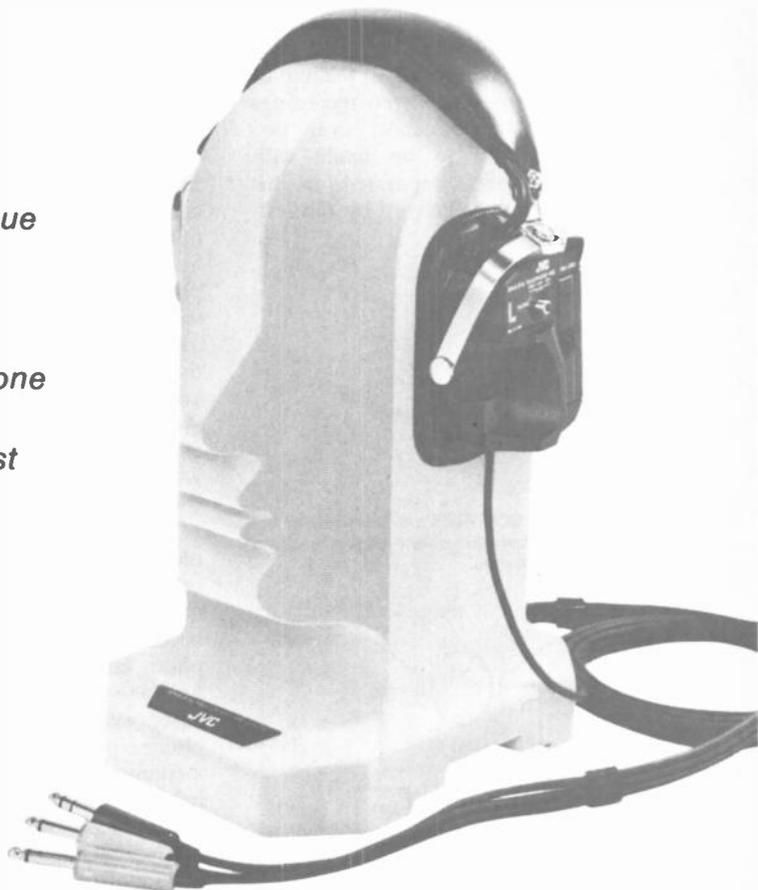

BACK IN THE EARLY 1930'S, BELL LABORATORIES performed extensive research into the nature of human hearing and, more specifically, the "binaural" effect. As most readers are probably aware, the reason that we can localize or perceive the direction of sounds is that we have two ears. Until recently, it was thought that two factors help us to determine angular directions from which sounds reach us—the difference in time of arrival of a sound to our two ears, and the difference in amplitude of the sound reaching our left and right ears. These factors are illustrated in Fig. 1. Sound waves approaching us from the left arrive at the left ear first, with sound reaching the right ear a small fraction of a second later. Since the sound has also travelled a greater distance to reach the right ear, it will be somewhat diminished in intensity as well.

More recent studies have shown that a third factor influences our ability to

localize sounds. When the early Bell Lab studies were being performed, the question arose as to why we are able to detect the difference between a sound coming from directly in front of us and one coming from directly behind. It was at first supposed that since both kinds of sounds arrive at both ears simultaneously, and with equal intensity, that we must subconsciously be turning our heads ever so slightly to establish an angular difference (and hence a different time of arrival) that then gives us the final clue as to the source of the sound. More recently, studies have shown that there is another factor involved. Because of the construction of our outer-ear (the auricle, or pinna), the frequency response of our overall hearing is "poorer" for sounds reaching us from behind, compared with sounds reaching us from in front. The "baffle" formed by the outer ear attenuates "highs" reaching us from behind.

Dummy-head microphones

In those early Bell Lab experiments, a dummyhead was fitted with two microphones, each located where the ears would normally be. Sounds picked up by each microphone were amplified by a separate amplifier and reproduced over a pair of headphones, as shown in Fig. 2. The sensation was very much as though the listener wearing the headphones was "transported" to the position in space occupied by the dummy head. Not only were angular directions of sounds clearly discernible, but listeners were able to determine, quite accurately, the *distances* to the sound source. In other words, there was a total and complete sound field perceived by listeners wearing the headphones.

Years passed and, as we know, binaural sound reproduction was given little or no attention. In the early 1950's, attention was turned to stereophonic sound. The chief reason why binaural

sound was regarded as impractical as a home entertainment music system was its need for headphone listening. Most people preferred listening to music reproduced over free-standing loudspeakers. If a binaural recording (using a dummy-head microphone arrangement) were to be played back over a stereo system, one would lose almost all perception of sound localization. The reason for this is obvious. The sounds originally intended for *only* the left ear are heard in both ears when reproduced via speaker systems, and the same is true of those sounds intended for only the right ear.

In order to synthesize a feeling of spread or separation, stereo recordings intended for reproduction over two loudspeakers had to be made with microphones widely separated. In this way, the sounds picked up by the left-

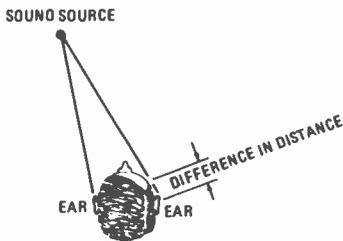


FIG. 1—SOUND SOURCES are localized by the time difference between sound waves reaching the left and right ears.

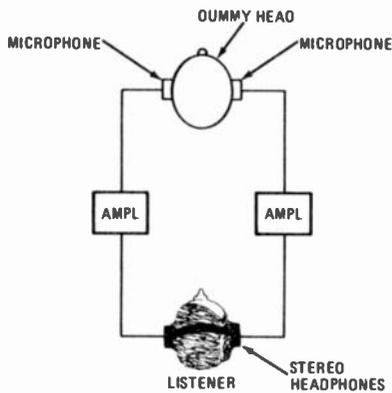


FIG. 2—BINAURAL REPRODUCTION requires microphones to be located where the human ears would normally be.

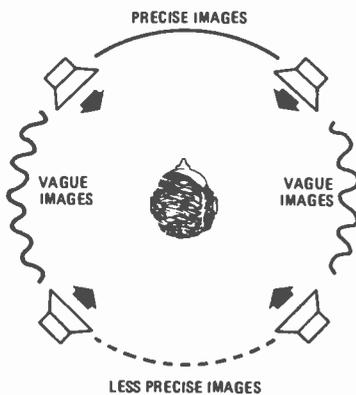


FIG. 3—QUADRIPHONIC SYSTEM is incapable of providing precise localization of sound sources.

channel microphone would be substantially different from those picked up by the right microphone.

As stereo recording technology advanced, all attempts to recreate a true "sound field" have just about vanished. Most stereo recordings today contain a mixture of multi-channel monophonic recordings (often, combined from 16, 24 or even more microphone channels). Such recordings can "fool" the listener into visualizing a two-dimensional sound plane, with musical instruments or vocalists "positioned" across a wall of sound. But the typical stereo recording, reproduced over conventional stereo hi-fi equipment cannot offer sound in three dimensions. The sense of distance is lacking.

Recent interest in 4-channel sound reproduction arose because of this deficiency in conventional stereo reproduction. But even 4-channel recordings, however carefully engineered, fail to provide true 360-degree sound fields with total realism and with distances from the listener to the sound source that are still difficult to ascertain with any precision. The ability to perceive sound sources, even in a discrete 4-channel system, is limited. (See Fig. 3.)

Renewed interest in binaural

Several factors have recently contributed to renewed interest in binaural sound recording and reproduction. For one thing, headphone listening has become quite popular and many audiophiles listen to stereo programming via headphones a good deal of the time. Also, compact high-performance microphones have been developed which facilitate the construction of "dummy head" dual-microphone systems that more nearly duplicate the physical dimensions and shape of the human head and ear. Finally, there has been a growing interest in live recording both in Japan and in the United States as more and more audiophiles take to the field with high-quality portable stereo cassette decks to record live events, musical or otherwise. As anyone who has tried to do a live stereo recording in the field is well aware, the problem of microphone placement, monitoring of the recording as it is being made, and the like, can discourage even the most enthusiastic of recordists.

After extensive research, JVC (Japan Victor Company) developed and is marketing an unusual headphone/microphone combination they call the model HM-200E. A close-up view of this product is shown in Fig. 4. In addition to housing a dynamic-type air-tight headphone, each earpiece is also fitted with an omni-directional electret microphone that is surrounded by a plastic molded "outer ear" or pinna designed to provide much the same frequency response and attenuating characteristics

as the human ear. A tiny battery compartment houses a penlight battery for powering the microphone in each earpiece. The cable terminates in three phono-plugs—the usual stereo headphone plug and one single-circuit plug for each microphone.

The robot-looking "head" shown in

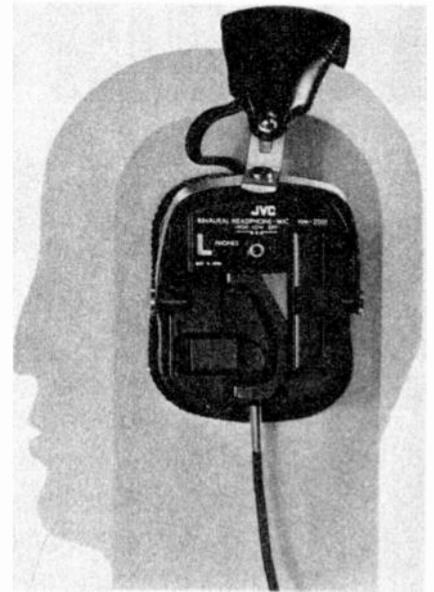


FIG. 4—JVC MODEL HM-200E contains microphone and baffle combination with characteristics that approximate the human ear.

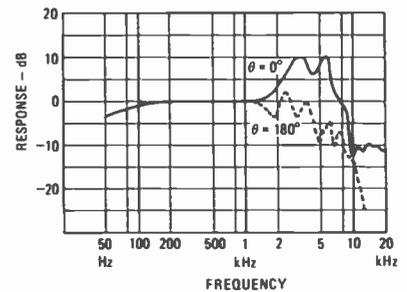


FIG. 5—MICROPHONE FREQUENCY RESPONSE at 0° and 180° with HM-200E fitted on human head.

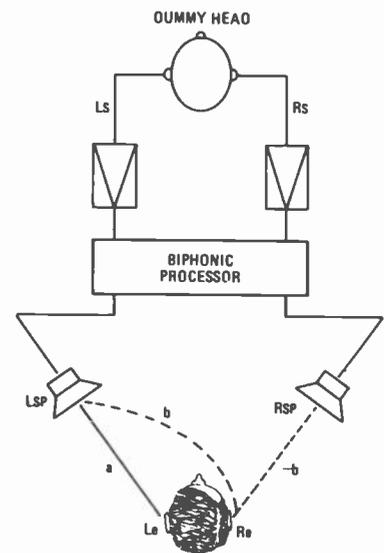


FIG. 6—BIPHONIC PROCESSOR permits binaural reproduction via speakers.

Fig. 4 is actually the microphone stand supplied with each *HM-200E*. It is made of a plastic material coated with a felt-like substance that is intended to approximate the density of a human head. The underside of the head is equipped with a variety of tapped screw-threads to fit any standard microphone stand (including the $\frac{3}{8}$ -inch standard used in the U.S.). So, the phone/microphone combination can be used to record either while wearing the combination on your *own* head or by mounting them on the supplied dummy head and pointing it in the right direction.

Because the headphones are the sealed or air-tight type, it is even possible to monitor sounds that are to be recorded while recording is taking place without inducing acoustic feedback between the microphones and the dynamic headphone transducers.

While the product may seem rather obvious and simple, a great deal of study went into its development. Primary considerations had to be given to the time difference between the arrival of sounds at each microphone for different incident angles, level-difference characteristics and frequency response. Comparisons had to be made between these characteristics observed on a scientifically accurate "dummy head", the same characteristics as observed when fitting the product on the listener's head, and those characteristics as observed when the product is fitted to the supplied "microphone stand" head. The frequency response at angles of 0 degrees and 180 degrees (the characteristic which enables us to distinguish between "front" and "rear" sounds) of the *model HM-200E* fitted on a human head is shown in Fig. 5.

Binaural sound from speakers

JVC's research into binaural sound has gone much beyond the development of the headphone/microphone system just described. Recognizing that it would be desirable if some of the spatial qualities of true binaural sound could be reproduced via a pair of stereo loudspeakers (or even a quadraphonic array of four speakers), they have developed an electronic processor that, under ideal listening conditions, can actually make it possible to enjoy the effects of binaural sound over a pair of loudspeakers.

As we stated earlier, the problem in listening to binaural sound over speakers is basically one of psychoacoustic crosstalk. Both ears end up hearing material intended for one ear alone, and in unprocessed form, binaural sound played over speakers sounds not much better than mono. If, however, precisely calculated amounts of out-of-phase, delayed and frequency-equalized left-channel information could be cross-

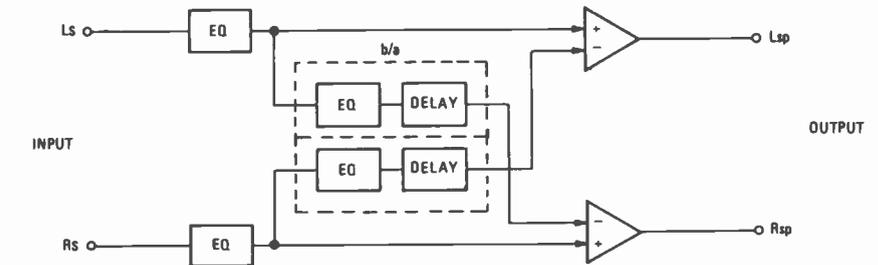


FIG. 7—BIPHONIC PROCESSOR is comprised of equalization and delay circuits.

coupled to the right-speaker channel and vice versa, it might be possible to create the binaural effect even when listening through speakers.

The principle is shown in Fig. 6 and a simplified block diagram of the binaural-stereophonic processor is shown in Fig. 7. Although the processor does restrict listener position to a very small area in the listening room, we can attest to the fact that it really does work. For the first time in our own listening experience, we were actually conscious of distances from sounds heard, as well as of their angular relationship in space.

Another interesting effect of the binaural-stereophonic processor is the expanded sound field that it gives to conventional stereophonically recorded program sources. As illustrated in Fig. 8, a listener actually feels that sounds are coming from beyond the speakers themselves—an effect that may someday be quite useful, especially in situations

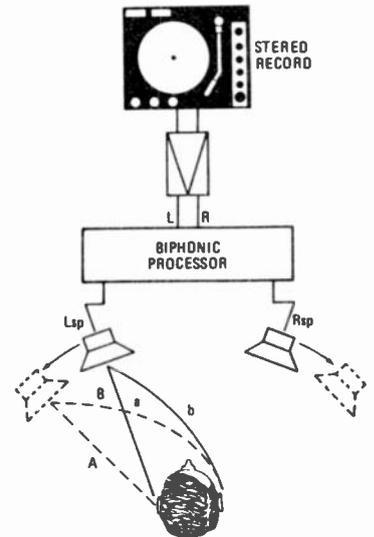


FIG. 8—SOUND FIELD of conventional stereophonic program material is expanded by biphonic processor.

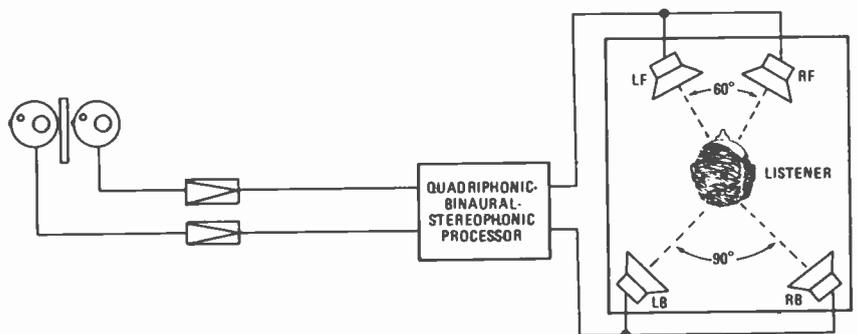


FIG. 9—4-CHANNEL BINAURAL reproduction via speakers is possible with quadraphonic-binaural-stereophonic processor.

where physical distance between speakers in a listening room is less than adequate because of limitations imposed by the room or its decor.

Taking the idea a step further, JVC explored the possibility of processing quadraphonically recorded material to create a binaural-listening experience. They concluded that even when binaurally recorded material is played back via the processor over a pair of speakers, sound images that should be localized behind the listener are still localized in a rather vague manner and the listener senses sound images over little more than a 180-degree angle in front of him.

They proposed to solve this problem by what they call a quad-binaural-stereophonic system using dual artificial

heads as shown in Fig. 9. Reproduced sounds "heard" by the microphones in the front head are reproduced from speakers placed in front of the listener, while those sounds picked up by the microphones in the rear head are reproduced over the speakers positioned at the rear of the listener. In this listening arrangement, they found that best results are obtained when the front speakers form an arc of 60 degrees with respect to the listener, while rear speakers are positioned at 90 degrees.

Neither of the two processors (the two-channel or four-channel version) is currently available to consumers, though that situation may, of course, change if the company feels that there is growing interest in such unique

continued on page 104

Tomorrow's Hi-Fi Gear

A look at future hi-fi equipment revealed at conventions in Tokyo and New York.

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

TRYING TO PREDICT WHAT TECHNOLOGICAL paths the high-fidelity industry will follow in the coming years is, at best, a risky business. An industry that has managed to triple its sales volume in less than half a decade is too dynamic and too diverse to lend itself to firm prophecies, as is evident if one examines the optimistic prognostications made for quadriphonic sound just a few years ago and compare them with the present state of apathy regarding 4-channel sound reproduction.

Nevertheless, two recent events took place within the audio industry that may serve as fairly good indicators of things to come in hi-fi. The first of these was a mammoth consumer high-fidelity show held at the giant Harumi convention center in Tokyo, Japan, that I was fortunate enough to attend, if only briefly. The second event was the annual Audio Engineering Society convention held in New York in the late autumn of 1976 that I also attended. These two events, as far apart geographically as any two happenings could be, had several things in common. Chiefly, they provided a glimpse of products and concepts that we are likely to see brought to commercial reality in the coming months and years. So, rather than devote this story to a single audio development, I would like to briefly discuss several innovative products and ideas that caught my fancy, either in Tokyo or in New York.

Headphones without wires

Popularity of stereo headphone listening has been growing ever since John Koss first introduced his somewhat crude looking stereophones in the late 1950's. One of the disadvantages of

headphone listening has been the physical constraints that are imposed upon the listener who wears the phones. The long cable (neatly coiled as it may be) that connects the phones to the familiar front-panel phone jack confines the wearer to a limited area within the listening room (few cables are longer than 10 feet or so). Now, Sennheiser Electronics Corporation has developed a "wireless" set of stereophones that are shown in Fig. 1. While the company had



FIG. 1—SENNHEISER MODEL HDI-434 infrared stereo headphone.

earlier shown a monophonic version of the wireless phones, their introduction of a stereo version occurred at the AES convention mentioned earlier.

The phones work on a completely invisible infrared light with a wavelength of 930 nanometers that is frequency modulated by a carrier of 95 kHz for one channel, 250 kHz for the other channel. Pre-emphasis of 50 micro-seconds is used. The transmitter, model SI-434, shown in Fig. 2, uses twelve light-emitting diodes to trans-

form the audio signal into infrared light. These special GaAs diodes can be modulated up to several hundred kHz, but 50 kHz deviation has been standardized as the maximum frequency modulation swing for these units.

The audio signal to be transmitted is applied to the transmitter unit by

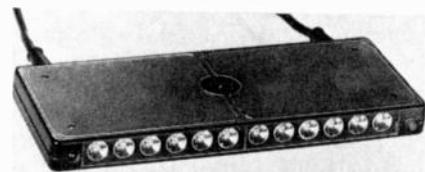


FIG. 2—SENNHEISER MODEL SI-434 infrared stereo transmitter.

connecting a plug to the normal stereo output jack of the amplifier or receiver. An audio output of 1.5 volts is required for a full 50-kHz deviation of the light carrier. The transmitter is powered by connection to a regular 120-VAC socket. An example of a working transmitter modulator circuit for an audio frequency modulated carrier set to 95 kHz is shown, schematically, in Fig. 3.

At the receiver (headphone) end of the system, two dynamic transducers are driven by the built-in infrared light receiver. A switch allows the user to select both phones to be activated by the left channel, the right channel or in the stereo mode. This feature makes it possible for the phones (model HDI-434) to be used for two different programs. For example, the original and the translated sound track of a foreign language film could be "received" simultaneously and selectively assigned to both earpieces. One of the two



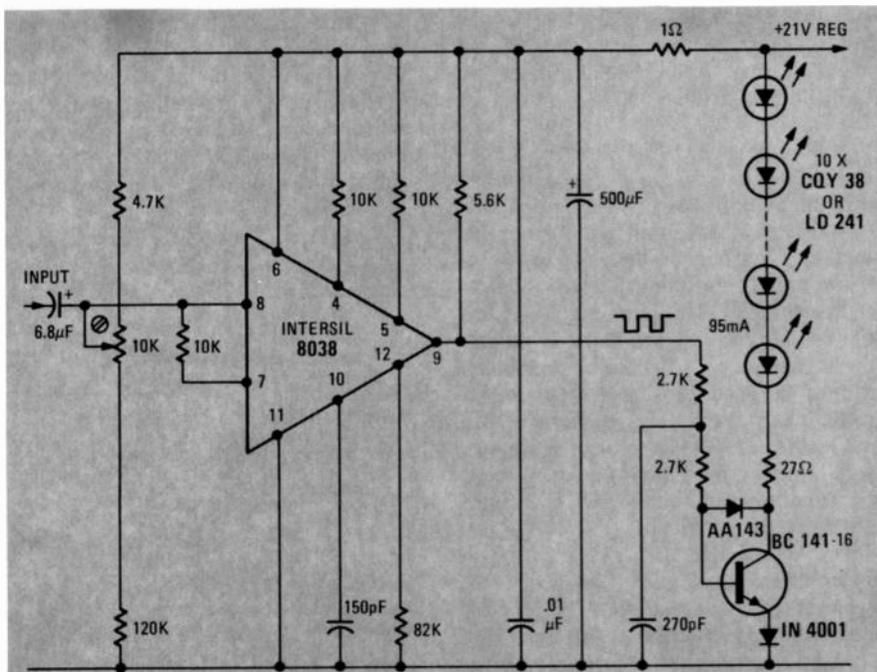


FIG. 3—INFRARED TRANSMITTER uses an IC function generator to frequency-modulate the LED's.

earpieces is also equipped with separate fader/volume controls for left-right channel balancing. A block diagram of the receiver setup for one channel of the headphones is shown in Fig. 4. Tentative pricing for the phones is \$209.00 while the infrared transmitter module is expected to sell for around \$184.00.

In our visit to Sennheiser's exhibit at the AES show we donned the phones and walked about the rather large room in which the units were being demonstrated. There was no fading whatsoever and, even more significant, unlike RF transmissions that have been attempted in the past for similar applications, there is no audible interference or multipath distortion no matter where one is situated in the room. We were informed that in very large listening areas, additional transmitters can be used in one

room without creating problems. The power of the radiated light simply adds together for greater area coverage. A synchronizing jack on each transmitter permits connection of a second transmitter for such cascading of infrared light-emitting units.

Binaural and Bi-Phonic sound

Long before quadraphonic sound was introduced to audiophiles, experimenters (such as Bell Laboratories) had done considerable work with binaural sound reproducing systems. For those not familiar with the term "binaural", Fig. 5 shows the technique.

An artificial or "dummy" head, equipped with a pair of microphones located where our ears normally would be is used to record a live musical or other audible event in the standard two-

channel format. When the recording is played back and listened to via headphones, spacial positioning of sounds is extremely precise. (After all, in real life we have only two ears with which to localize the sources of sound we hear and we manage to do so with pin-point accuracy.)

The reason why binaural recordings have not been more popular in the past is because most people prefer to listen to music via speakers rather than headphones and, in order to provide reasonable spatial information using speakers, stereophonic recordings employ microphones that are placed much further apart than the distance between our two ears. This is done to compensate for the fact that the speakers will also be placed far apart during listening and the fact that *both* of the listener's ears will be subjected to sounds from *both* speakers (as opposed to the binaural technique in which the listener hears only left-channel information via a headphone placed on his or her left ear and right-channel information via the right earphone).

One of the persistent problems in conventional stereophonic playback has been the inability to recreate sounds that have perceivable front-to-back localization. Stereo, in effect, creates two-dimensional sound rather than three dimensional sound, as might be the case with classical binaural recording and reproduction. It is this failing of stereo that prompted experiments with quadraphonic sound. But even 4-channel sound, using the usual two-up-front, two-in-the-rear speaker placement suffers from an inability to create convincing side images and an inability to recreate accurately those sound images

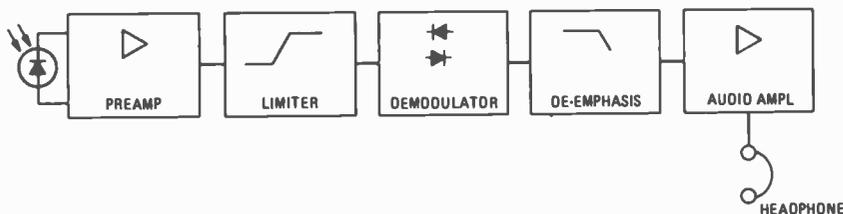


FIG. 4—INFRARED RECEIVER uses limiter and de-emphasis circuits in the same way as a standard FM receiver does.

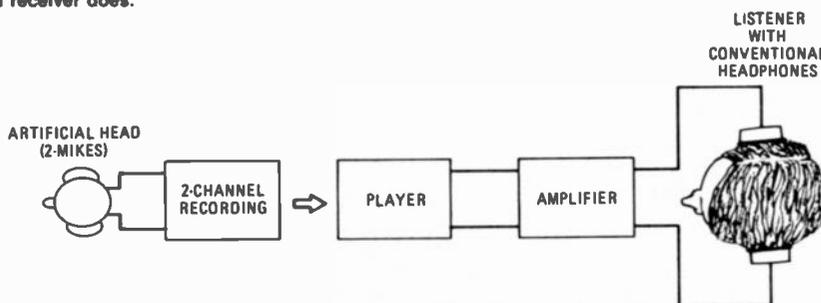


FIG. 5—BINAURAL SOUND SYSTEM provides precise spatial positioning of sounds.

that were intended to be close-in to the listener.

At the Tokyo high-fidelity show, a major portion of JVC's exhibit space was given over to demonstrations of two newly developed recording and reproducing systems. The first of these is known as Bi-Phonic (short for Binaural-Phonic) and involves the playing of tapes or discs that have been recorded in the classical binaural method (using dummy head equipped with microphones instead of ears). Interposed between the record or tape player and the amplifier which drives a pair of loudspeakers is a device called a "Bi-Phonic Processor". This processor transforms binaural signals into stereophonic signals by means of a complex equalizing and time delay system. The effect produces a convincing sound field from only a single pair of loudspeakers that actually "wraps" sound around the listener over at least a 180 degree arc. A simple block diagram of this approach is shown in Fig. 6.

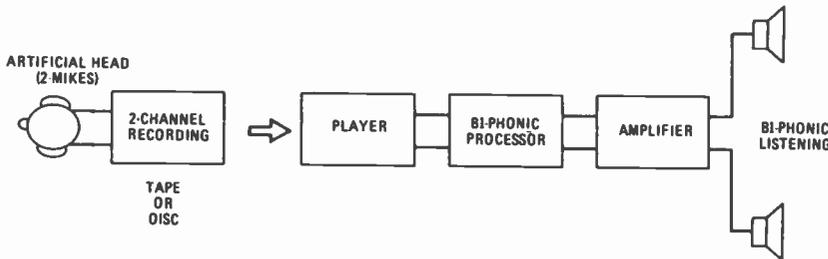


FIG. 6—BI-PHONIC SOUND SYSTEM is similar to binaural system except that speakers are used for playback rather than headphones.

Taking the binaural-to-stereo approach a step further, JVC also demonstrated a system they call Q-Bi-Phonic. In this system, two artificial heads are used. They are placed in close proximity—12 to 15 inches apart. Both face forward (towards the performance) and there is a special baffle between them. The front head is clearly forward oriented, while the rear head is less so, because of the interposed baffle. Each head produces a pair of binaural signals. Rather than being played back in binaural fashion, each pair of signals is fed through a special processing unit that again incorporates equalizing and time delay circuits to produce two pairs of signals. These signals are then suitable for quadriphonic loudspeaker presentation. This processor effectively produces a "binaural-to-quadriphonic" transformation, thus enabling the arti-

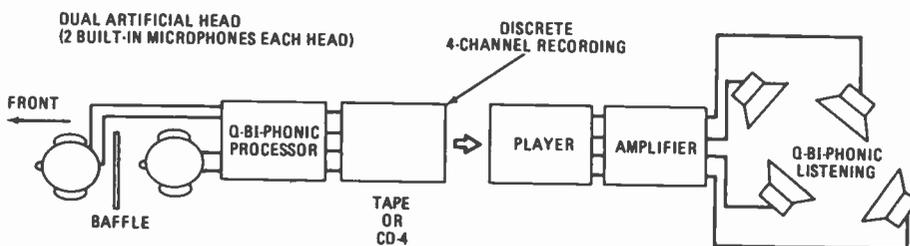


FIG. 7—Q-BI-PHONIC SYSTEM is the 4-channel version of the bi-phonic system.

cial head signals to be played back over loudspeakers set up in a normal 4-channel array. A block diagram of the Q-Bi-Phonic arrangement is shown in Fig. 7.

Bi-Phonic and Q-Bi-Phonic both represent elaborations on stereo and quadriphonic technology. Based upon our own listening tests, both systems require that the listener be located within a fairly small area along the axis of left-right symmetry. This is essential because the spatial phasors produced by either the Bi-Phonic or Q-Bi-Phonic processors cannot be accurately recreated over a wide lateral range. Listeners who are not located close to the axis of symmetry will, however, hear the traditional stereo or quadriphonic sound as they would normally be perceived.

Our experience with these two new approaches to sound recording and reproduction suggest that both offer considerable challenge in the recording studio for innovative record producers. We were treated to some very specta-

cular effects using these systems, particularly in the case of the Q-Bi-Phonic system, and, from all indications, JVC's American counterpart intends to promote this idea in the United States within the near future.

PWM audio amplifier

Switching back to this side of the world and the AES convention, we listened to a paper delivered by Mr. T. Suzuki, of the Sony Corporation, that concerned the development of a highly efficient audio amplifier using pulse-width modulation (PWM) instead of the conventional linear, analog signal amplification. If this sounds somewhat like the Class-D amplifier approach that was recently introduced in this country by Infinity Systems Corporation, it is, except that in Sony's version they have incorporated the new vertical-field-effect

power transistors in this amplifier. Sony maintains that the vertical-FET, with its wide area of safe operation, excellent high-frequency response and good pulse-response due to absence of storage time in signal transfer, is particularly suited to the so-called Class-D amplifier design.

The basic pulse-width modulation amplifier is shown in the simple block diagram of Fig. 8. The amplitude of the

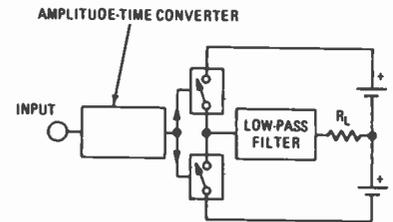


FIG. 8—PWM AMPLIFIER uses an amplitude-time converter to pulse-width modulate the output stage.


input audio signal varies the width of pulses by an amplitude-time converting circuit. The pulse signal then controls the switching elements of the power stage. The output of the power stage is passed through a low-pass filter to the load. Since the power stage is either the saturated or cut-off, there is, in theory, no loss of energy in its operation. Compared to a conventional linear amplifier, this system requires an additional amplitude-time conversion circuit and a low-pass network. In addition, since it is called upon to handle square-wave signals, suppression of unwanted RF radiation becomes necessary to make the amplifier commercially practical.

A more detailed block diagram and waveform diagram is shown in Fig. 9. A squarewave generator is used as the source of the high-frequency switching signal. The carrier is converted to a triangular waveform by means of an integrator circuit. This triangular-shaped carrier is added to the audio input signal and passed through a saturating high-gain amplifier to obtain a series of pulses whose time duration is directly proportional to the amplitude of the input audio signal. These pulse signals are then amplified by a pulse amplifier power stage and then demodulated by means of a low-pass filter. Suppression of the high-frequency switching carrier and its sideband components is also accomplished by the low-pass demodulating filter though, in a practical realization of the amplifier, extensive shielding of the entire amplifier was required to prevent RF radiation.

The particular prototype that was shown was no larger in size than a small preamplifier and yet was able to produce in excess of 100 watts-per-

continued on page 96

HI-FI

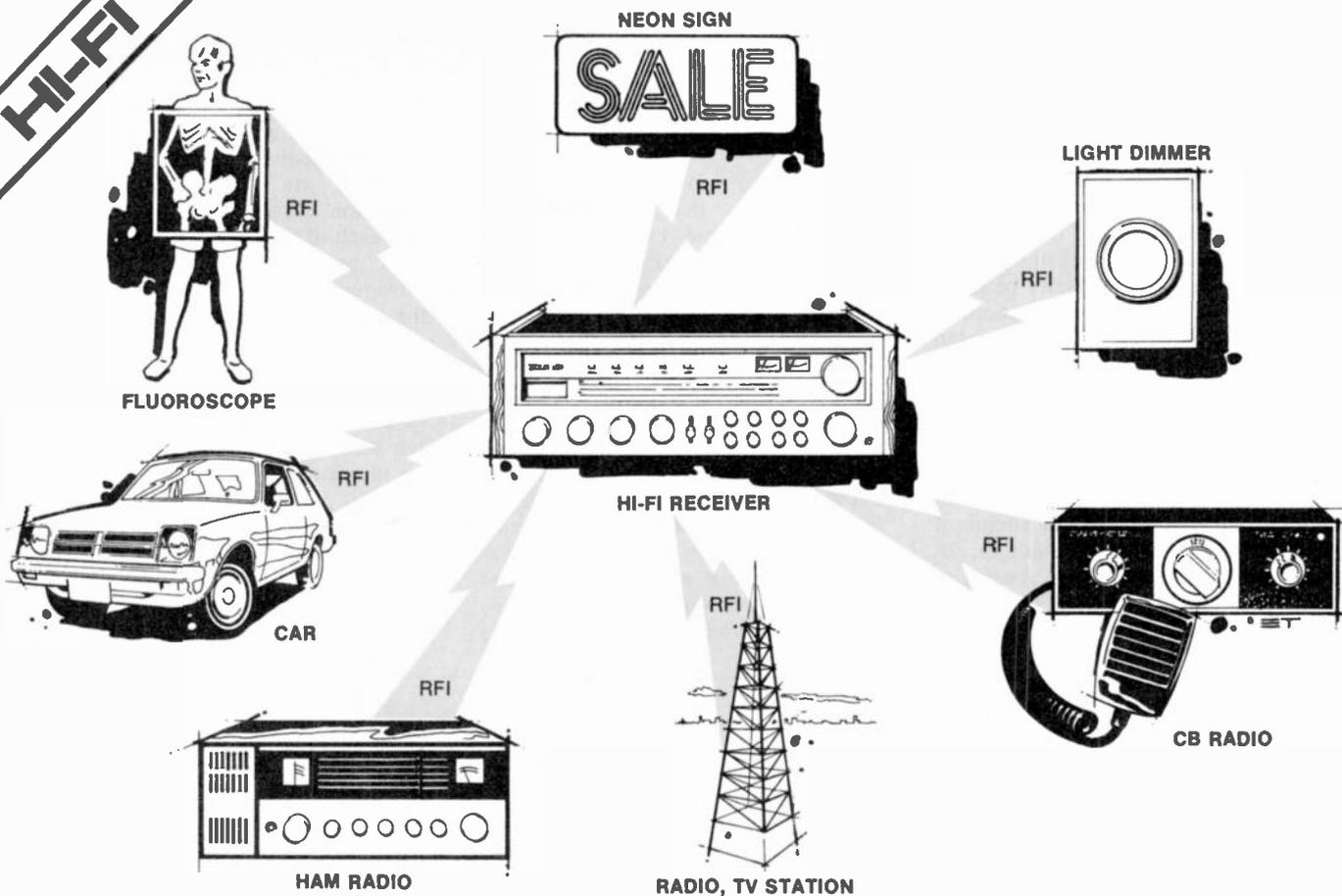

Getting Rid Of RF

Don't despair when RF interference invades your hi-fi system. Here are some steps you can take to get rid of it.

IF YOU SUDDENLY HEAR A "GOOD BUDDY" warning of the imminent approach of Smokey over your expensive stereo hi-fi system while you are trying to audition a disc, don't get the idea that you are being singled out as a solitary victim by your neighborhood CB'er. You are just one of hundreds of thousands of victims of RFI (Radio Frequency Interference). In the last year alone, the FCC has received nearly 100,000 complaints regarding interference that degrades TV performance, intrudes upon the sounds of hi-fi and generally makes owners of home entertainment equipment miserable. In most cases, the FCC is powerless to do anything about the problem, especially since this sort of interference can and does take place even when the offending transmission equipment is operated within legal power limits. Even in cases where CB'ers use linear amplifiers to increase radiated power beyond authorized limits, the FCC is so understaffed (and CB usage has been proliferating at such a fast clip) that they would not be able to look into a specific complaint for months, if at all.

The Consumer Electronics Group of

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

the Electronics Industry Association (EIA) has been considering this growing problem for some time and recently, they prepared a comprehensive booklet entitled *Electronic Technician's Interference Handbook, Audio Rectification*. Much of the material contained in this article is paraphrased from the final draft of that booklet, while some comes from personal experience with the problems of interference we have encountered over the past few years ourselves.

The most common type of audio interference encountered in hi-fi (and occasionally in TV) equipment found in the home is due to a phenomenon known as audio rectification. Audio rectification is the detection of modulated RF signals by an audio circuit of a radio, preamplifier, amplifier, or tape deck electronics that appear as unwanted or disturbing audio signals at the speaker output terminals. Since not all RF interference is created by RF transmitting equipment, the most com-

mon forms of interference can be divided into two groups: signals emanating from RF transmitting sources (radio or TV stations, amateur radio operators, CB operators, paging systems) and interference from electrical equipment or appliances (X-ray and diathermy equipment, neon signs, light dimmers, thermostats, commutators and switches).

The first category of equipment is usually not within direct reach of the "victim", and curing of interference problems from RF transmitting equipment is largely confined to working on the actual equipment experiencing the interference. The second category is more likely to be located within your house or apartment and, by turning off the suspected interfering source, it can at least be localized and identified.

Interference from the first group will prove more difficult to diagnose, because its point of entry into an audio device can be anywhere from the antenna to the speakers. Interference can be picked up by long connecting cables acting as antennas or a component acting as a detector, or it may be

transmitted through the AC power lines, especially if the source of interference is in the same building as yours. Detection will then take place in the power-supply circuit of the audio equipment with the same disturbing effect on the listener.

Since the majority of interference problems occur because of nearby interfering equipment, there is little point in taking your receiver, amplifier or other equipment to a factory or authorized warranty service station. The technician at such service centers will be completely frustrated in trying to solve the problem remotely, because it would be impossible to duplicate the problem. Audio rectification happens with the best of equipment, and its absence is no indication that one piece or brand of equipment is better than another. In fact, equipment with higher sensitivity and gain is a better prospect than some inexpensive, low-gain audio equipment.

Correcting external interference

Before digging inside your receiver, amplifier or tape deck, there are several simple remedies you should try first. Check connecting audio (shielded) cables and replace overly long ones with shorter ones, wherever possible. If the interference is noticed only when the pick-up arm or the turntable is touched, a ground wire between the pick-up arm and preamplifier chassis ground is called for. If the phonograph pick-up headshell is bakelite or plastic, a small piece of foil or metal between the cartridge and headshell that is grounded to the metal portion of the pick-up arm or to the metal base of the turntable, may help. (See Fig. 1.) If the metal or

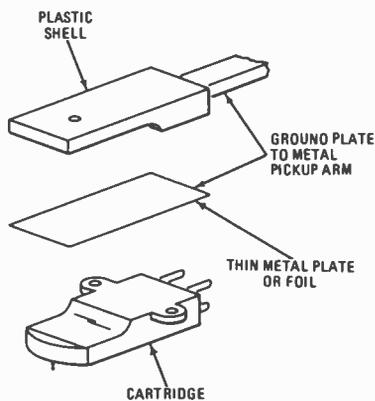


FIG. 1—GROUND PLATE between cartridge and pick-up arm may reduce interference.

foil alters the tracking force, this should be readjusted to maintain proper cartridge performance.

If the interference occurs when holding a microphone (but not when you place it on a table), a ground wire between the microphone shell and the preamplifier or amplifier chassis is called for. A "buzz" recorded on tape when using a hand-held microphone

can also be caused by a defective or poorly shielded microphone, but this can be verified by making a recording in a location where the identified RFI is not present.

Interference is often caused by long speaker cables that can act as an antenna. In some extreme cases of strong RFI, the interference persisted (and was heard over the speakers) even after the entire system was turned off! Replacing unshielded speaker cables with shielded cable or installing a small capacitor across the speaker will often cure this problem. The audio purist will, of course, object to altering the load seen by the amplifier in this manner, but most modern amplifiers can tolerate fairly large values of capacitance across speaker terminals before oscillation occurs. Even so, it would be a good idea to check with a scope connected across the speaker terminals for any evidence

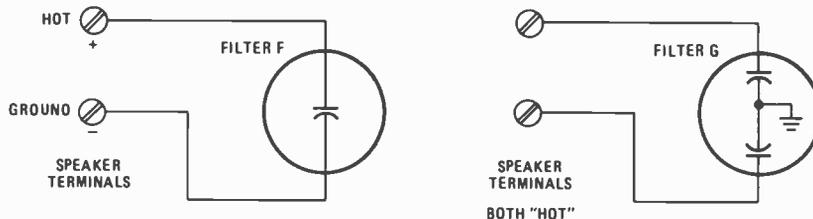


FIG. 2—LONG SPEAKER WIRES can act as a receiving antenna for RFI. Capacitors mounted across speaker terminals will eliminate this problem. Normal connection is shown as Filter F, and Filter G shows connection for strapped amplifiers.

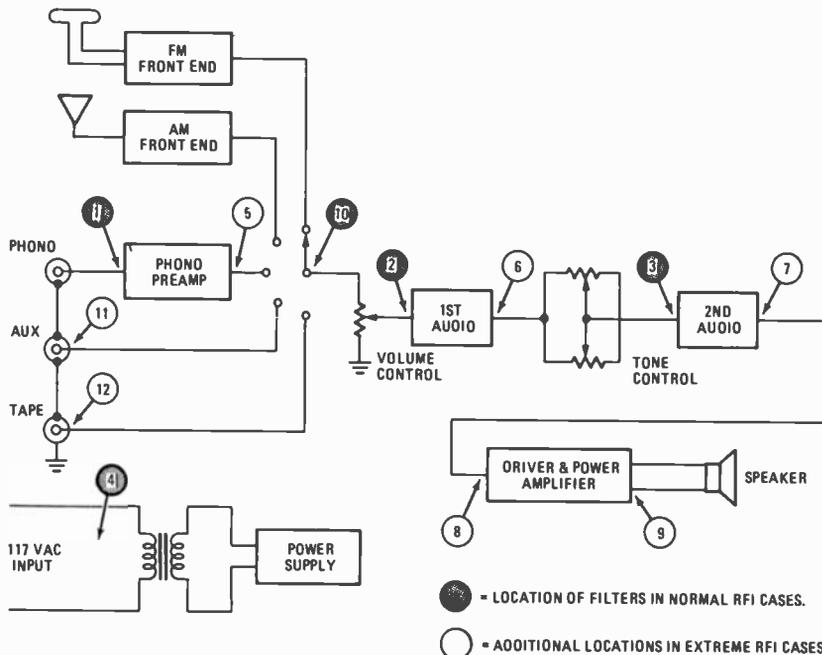


FIG. 3—FILTER LOCATIONS in AM/FM/Phono equipment.

of oscillation before you run into a case of blown tweeter voice coils!

If you want to play things completely safe, you might try increasing the capacitance across the speaker terminals (while observing the scope trace) until evidence of high-frequency oscillation just begins. Final total capacitance should then be no more than half of the value required before oscillation takes

place. Where speaker output terminals of the amplifier consist of a "hot" and a "ground" terminal, the capacitor should be connected as shown in Fig. 2-a. If both terminals at the output of the amplifier are "hot", use the configuration shown in Fig. 2-b, recalling that each of the two capacitors involved must be double the required value previously determined as needed to stop the interference. Such arrangements where both terminals are "hot" occur in some amplifiers that have been "strapped" for higher power (as in the case of some quadriphonic units that can be switched to 2-channel operation for increased output power.

Internal equipment modifications

If the few corrective steps enumerated above fail to eliminate or sufficiently reduce audio rectification, it's time to look inside your amplifier, receiver,

preamplifier or tape equipment and to check for a few obvious causes. Check first for bad ground connections and poor solder joints. Sometimes, electrolytic capacitors that have been in service for many years develop a high internal-resistance. Paralleling a fresh capacitor across the suspected one will eliminate this as a possible source.

If the interference still persists at this

TABLE I—RFI TROUBLESHOOTING CHART FOR AM/FM/PHONO EQUIPMENT.


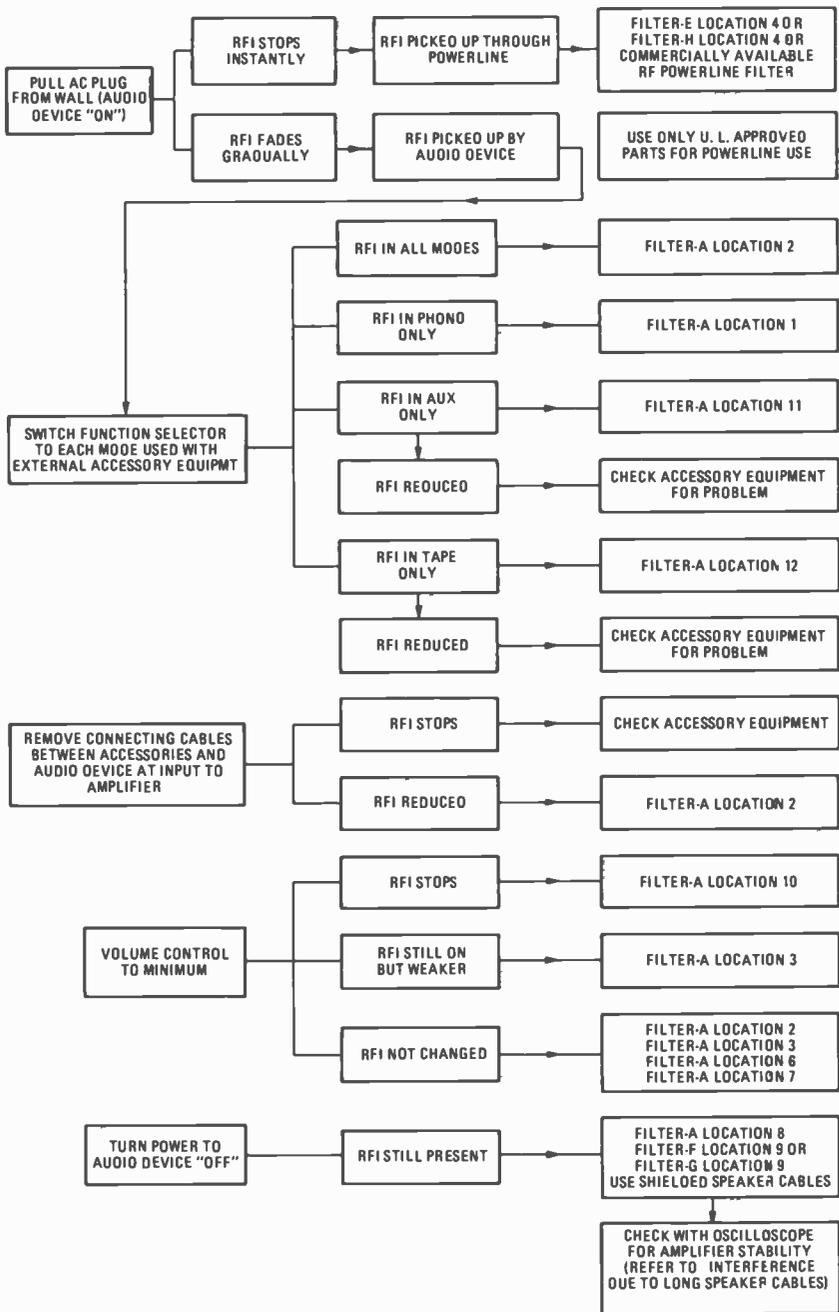


TABLE II—RFI TROUBLESHOOTING CHART FOR TAPE RECORDERS.

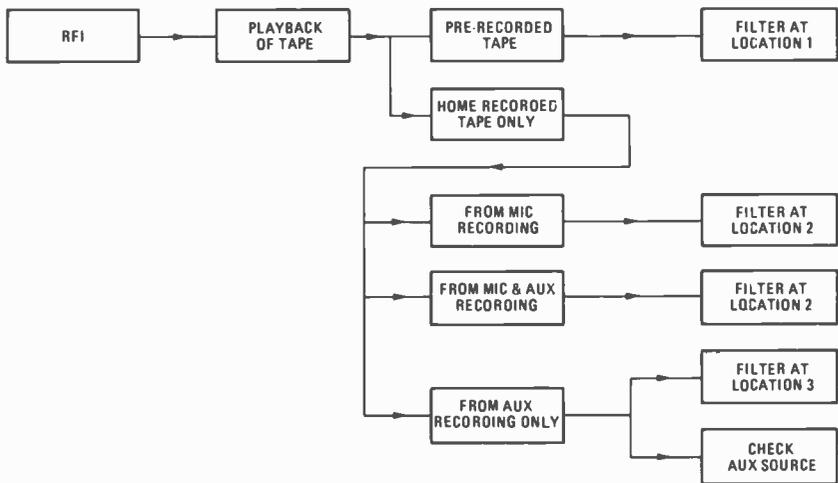

point, it's time to consider adding one or more filter networks. Table I is a troubleshooting chart that will help you to isolate AM, FM and phono interference-problems logically. Associated with Table I is Fig. 3, which is a simplified block diagram of a typical home hi-fi installation. The circled numerals indicate points of insertion of various filter circuits as called out in Table I. Filters are designated by the letters A through H.

Table II is a troubleshooting chart designed to help you analyze and correct RFI problems that occur in connection with the use of tape equipment, and Fig. 4 shows the location of possible corrective filters. The filter identified as "A" should be used for correcting tape RFI problems.

Filter networks

The most effective RFI filter, from practical experience, is a "pi" filter-network consisting of a series RF-coil and two shunt capacitors. Suggested values for this filter, designated as Filter A in the troubleshooting chart of Table I, are shown in Fig. 5.

In mild cases of RFI, a single bypass capacitor between the base and emitter may be sufficient. This configuration is designated as Filter B in Fig. 6. Another fairly effective way to suppress RFI is through the installation of an L-type filter in the collector circuit, shown as Filter C in Fig. 6.

A coil inserted in series with the emitter leg of an audio input transistor, as shown in Fig. 7, may help in very mild cases of RFI. If such a remedy is used (Filter D), the coil should not be bypassed. This filter is the least desirable because of difficulty of installation in printed circuits and because of the possibility of oscillation that might take place in some circuits after it is installed.

Filters designated as E and H are generally used when it has been ascertained that RFI is coming in through AC power lines. Wiring diagrams for these two filters are shown in Fig. 8. In cases where the line cord is part of an indoor antenna system, there may already be a pair of coils wired in series with each side of the line cord. In that case, either Filter E or Filter F should be wired between these existing coils and the primary of the power transformer, as shown in Fig. 9.

Filters F and G have already been discussed and illustrated (see Fig. 2) in relation to speaker-cable pick up of RFI.

Filter installation

Several precautions should be observed whenever adding any of the filters illustrated. Install the filter network as close to the input of the audio stage that follows the so-called RFI

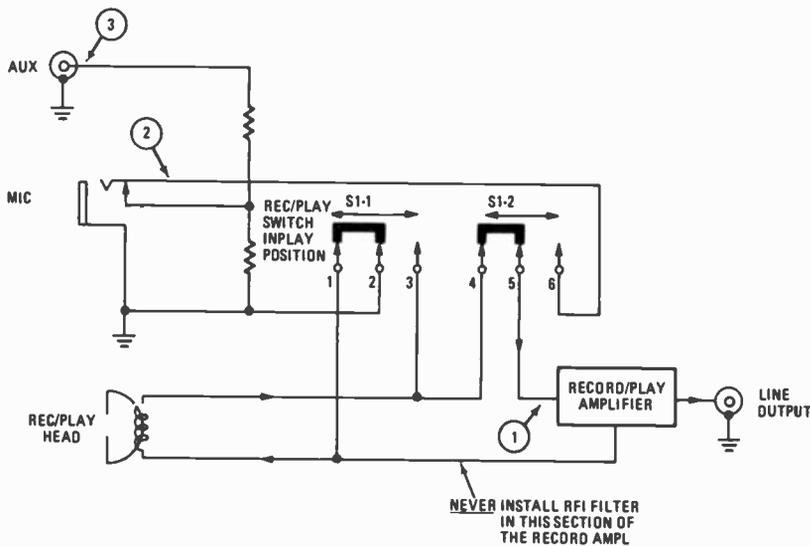


FIG. 4—FILTER LOCATIONS in tape recorders.

Safety comes first

In your eagerness to solve your RFI problems, don't overlook the importance of component safety. Use only U.L. approved components, especially when installing filters across the power-line input of the equipment. Capacitors rated at 400 VDC are *not* safe for 120

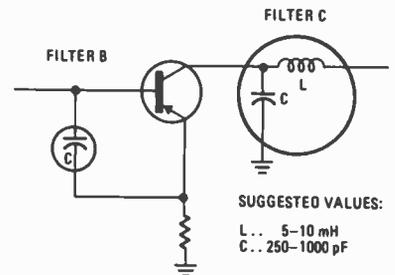


FIG. 6—FILTER B AND FILTER C. Filter B consists of single bypass capacitor between base and emitter. Filter C is an L-type filter in the collector circuit.

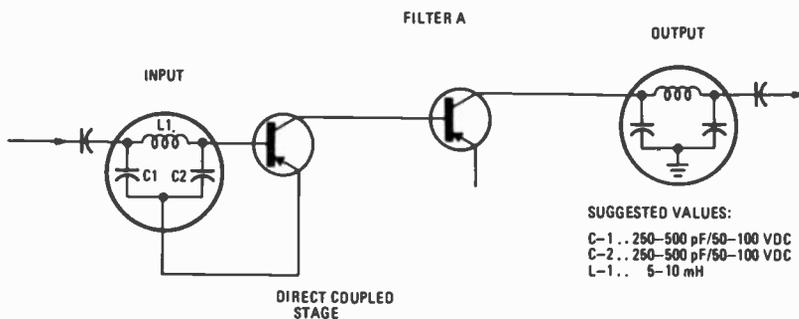


FIG. 5—FILTER A is a pi-filter network, which is very effective in the reduction of RFI. This network is usually inserted in the base and collector circuits.

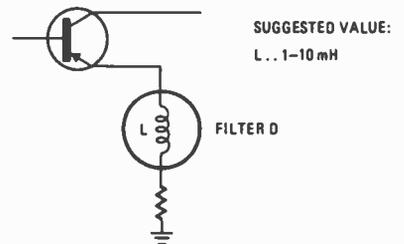


FIG. 7—FILTER D consists of a coil inserted in the emitter circuit.

pickup point (close to the base of the transistor or grid of a tube in the preamp of a receiver, for example). Use physically small components; small ceramic capacitors are preferable to paper capacitors. Keep all capacitor and coil leads (ground leads as well as "hot" leads) as short as possible. Long leads may compound the RFI problems instead of solving them. Install only as many filters as are found to be absolutely necessary. Too many filters may also do more harm than good.

It is advisable to run a frequency response check before and after filter installation to make sure that RFI filters have not changed gain or frequency response of the audio component significantly. A capacitor value that is suitable in a low-impedance circuit will not be a good choice in a high-impedance circuit.

IC's often pick up RF interference. Because of the feedback circuits incorporated in many IC applications, RFI filters should be installed both at the signal inputs and outputs of IC's, where they are suspect.

If RFI originates at the tape recorder source only, it must be determined whether it shows up only during playback of home recorded tapes or on commercially recorded tapes as well. In the former case, the RFI is actually recorded on the tape itself and will be heard whenever or wherever that tape is

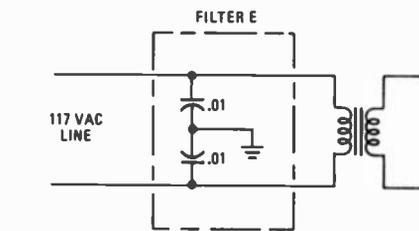


FIG. 8—FILTER E OR FILTER H should be used when the interference is coming through the AC power line.

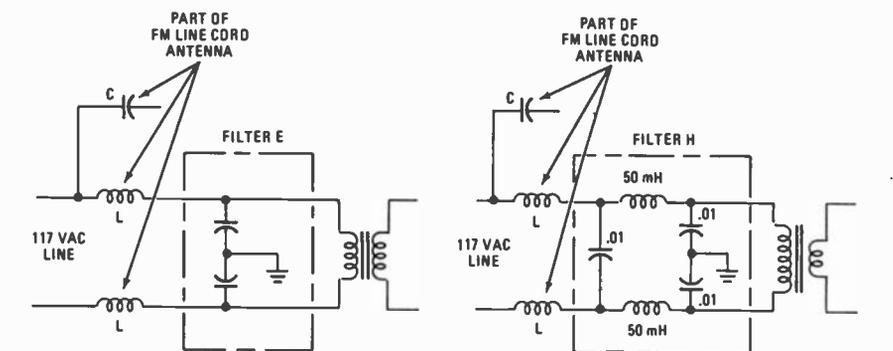
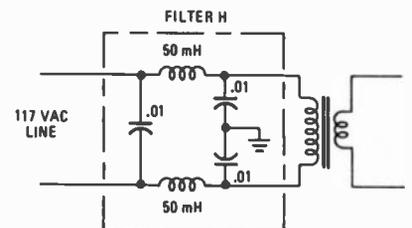


FIG. 9—CONNECTION OF FILTERS E AND H when coils are already attached to the AC power line, as is the case when the power line is also being used as an indoor antenna.

played back. A filter at the microphone preamp input will be necessary in such cases.

To avoid ground loops, shunt and bypass capacitors should be grounded to the emitter of the transistor when such filters are installed in the base circuit of a transistor stage.

VAC. Capacitors must be rated specifically for line bypass applications and suitable for continuous operation at 125-150 VAC, RMS, 60 Hz. Mount components carefully to avoid possible shorts or arcing.

RF chokes are made by several

continued on page 97

Radio-Electronics

Tests Garrard

GT-55 Turntable



CIRCLE 99 ON FREE INFORMATION CARD

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

IT IS NOW SOME SEVEN YEARS OR SO SINCE THE Garrard division of Plessey Incorporated first introduced their *model Zero-100* multiple-play turntable. That unit had the distinction of being the first model that provided true tangential tracking of the pickup arm as the arm was pivoted across the surface of a record. Tracking error of a cartridge's stylus had long been recognized as one of several distortion producing causes in record reproduction and Garrard sought to eliminate this source of distortion. The only other way to eliminate this form of distortion is by constructing a pickup arm that travels across the grooves, as is now the case for the Rabco (Harmon-Kardon) *model ST-7* and the Bang & Olufsen Beogram *model 4002*. Both of these models sell for considerably more than the new *GT-55*.

The new *GT-55* is shown in Fig. 1. It features a newly designed magnesium light-weight pickup arm that rides on jewelled vertical-pivot bearings and horizontal ball-bearings. While the headshell is a permanent part of this arm, a slide-in cartridge carrier, equipped with four slide-contacts, is removable and it is this carrier that retains the cartridge. A separate plastic stylus-alignment gauge is supplied for positioning the cartridge in the carrier to provide optimum stylus positioning and overhang.

Pickup arm balance is achieved by means of a counterweight that is screwed into the rear of the arm. When balance is achieved (with cartridge mounted), a rotatable indexing ring on the counterweight is set to zero. The entire counterweight is then screwed forward until the index reads desired downward tracking force, in grams.

A magnetic anti-skate control on the base of the turntable is completely free of mechan-

ical linkage to any portion of the pickup arm and uses a magnet of varying diameter that is wrapped around the base of the arm. The anti-skate control has two calibration scales: one for use with elliptical stylus cartridges, the other for cartridges equipped with CD-4 (Shibata, etc.) stylus tips.

A cueing-speed control is located on the base, beneath the center of the arm, and permits the user to adjust the rate of descent or ascent of the pickup arm when the cueing lever is used. Further along the base is a lever that locks or releases the arm from its rest post.

Four lever operated controls are located at the right front of the turntable base. A detailed view of these controls is shown in Fig. 2. The leftmost lever is the CUE control.



The second lever, labelled AUTO, is used to initiate the playing cycle and to reject a record at any time during play. The SIZE lever selects record sizes (7, 10 or 12 inches) so that the pickup arm is properly indexed. The rightmost MODE lever has an OFF position, as well as positions for MANUAL play, AUTOMATIC (multiple play) and REPEAT play. When repeat play is selected, a single record will be replayed so long as the MODE switch is


left in this position or, in the case of a stack of records, the last record in the stack will be repeated until some other mode is chosen.

At the lower left of the turntable base is a SPEED lever that selects 33 $\frac{1}{3}$ or 45 RPM, and a continuous control that varies the selected speed by $\pm 3\%$. (See Fig. 3.) The speed and



pitch controls are completely electronic. Unlike Garrard's earlier "zero-tracking" models, the *GT-55* is belt driven by a DC servo-controlled motor. The center front of the turntable base has a viewing window for strobe markings that can be seen for precise speed adjustment. Illumination of the strobe markings is provided for.

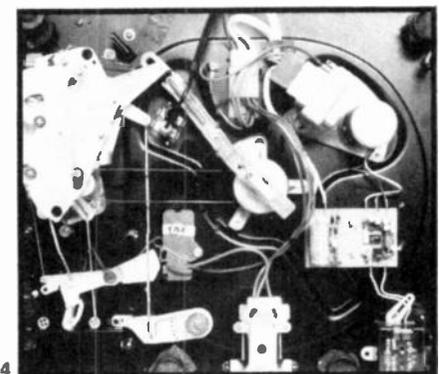The underside view of the *GT-55* shown in Fig. 4 reveals that the designers of this unit have been able to considerably simplify the mechanism over previous models. The DC




motor, near the upper right in the photo, is connected to an electronic circuit board that provides speed regulation. A secondary belt may be observed running from the turntable center-spindle leftward to the cycling and pickup arm linkages.

The platter itself, viewed from the underside in Fig. 5, is a dynamically balanced die-cast zinc-alloy unit. The two cutouts visible in

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Platter Diameter & Type: 11 $\frac{1}{2}$ -inches, die-cast, zinc-alloy, dynamically balanced. **Platter Weight:** 4.0 lbs. **Drive Motor:** 1000 RPM DC servo-controlled. **Drive System:** Belt. **Speeds:** 33 $\frac{1}{3}$ and 45 RPM, with variable ($\pm 3\%$) pitch control. **Pickup Arm:** magnesium, with articulated (constant tangent) headshell. **Balance & Tracking Force:** adjustable counterweight. **Anti-skating Adjustment:** magnetic, with settings for elliptical and CD-4 stylus shapes. **Pickup Arm Friction:** Vertical: 20 milligrams; Horizontal: 30 milligrams. **Effective Pickup Arm Mass:** 19 grams (assuming 5 gram cartridge). **Minimum Tracking Force:** 0.75 grams. **Tracking Force Range:** 0 to 3.0 grams. **Wow and Flutter:** 0.05%. **Rumble:** -66 dB (DIN "B"). **Cueing:** adjustable speed, damped in both directions. **Maximum Record Stack:** 6. **Dimensions:** (chassis) 15 $\frac{5}{16}$ W \times 14 $\frac{1}{8}$ -inches D. **Height Above Motor Board:** 4 $\frac{3}{8}$ -inches. **Clearance Below Motor Board:** 1 $\frac{7}{8}$ -inches. **Weight:** 16 lbs. **Suggested Retail Price:** \$249.95. (Optional Base BW-40: \$15.95; Dust Cover D-40: \$9.95. Optional Combination Base & Dust Cover, BDC-8: \$39.95).

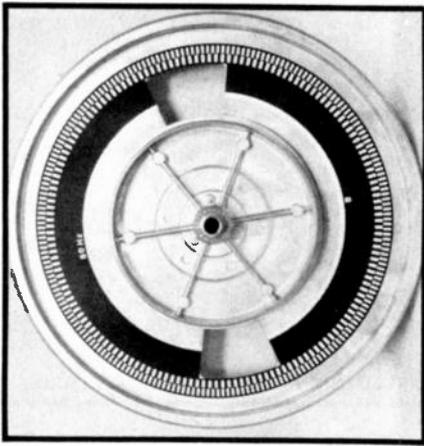

It is difficult to ascribe the low distortion reproduction we heard to any one feature of the GT-55, and we must take the company's word for it that tangential tracking is an important factor here. But, whatever the contributing design factors, we must complement the designers of this "second generation" Garrard turntable system for having

succeeded in a total redesign that seems trouble free and, in our opinion, is capable of providing years of reliable record playing service.

Our overall product evaluation will be found in Table II, together with summary comments regarding our reaction to the GT-55. R-E

the photo permit relatively simple installation of the flexible rubber drive-belt after the turntable has been mounted on the center spindle. Multiple-play as well as single-play spindles are supplied with the unit, as is a 45 RPM adaptor. A rear support post combines with the multiple-play center spindle to provide two-point support when stacking records.

Laboratory measurements

There are really only three measurements that are significant when measuring performance of a turntable. These are speed accuracy, signal-to-noise, and wow-and-flutter. Although Garrard does not specifically say so, we presume that their wow-and-flutter specification was measured on the basis of a WRMS (Weighted, Root-Mean-Square) measurement, and our measurements were made accordingly. On that basis, we did a bit better than Garrard claimed, measuring 0.04% as opposed to the claimed 0.05%.

As for rumble, using the DIN "B" weighting curve, we read an excellent -68 dB as opposed to the -66 dB claimed. By way of comparison, we should note that the best readings we have ever obtained for rumble (with the most expensive, single-play direct-drive turntable systems around) were just above -70 dB.

Once the 33 $\frac{1}{3}$ RPM speed was adjusted by means of the PITCH control, we detected absolutely no drift in speed over a test period of one hour. Line-voltage variations of $\pm 10\%$ (from 120 volts) similarly had no effect on speed accuracy. The PITCH control on our sample provided +3.5% and -4.0% variation, somewhat greater than that specified. A complete listing of our laboratory measurements appears in Table I.

Use and listening tests

We used the Garrard GT-55 with a variety of phono cartridges, ranging from a CD-4 type that required 2.0 grams of downward tracking force to a moving-coil type that normally is intended to track at less than 1.0 gram. Each of these cartridges was accommodated with no problem and tracked very well at recommended forces. The record changing cycle of the GT-55 is extremely smooth and noise free and we noted that there was considerably less "drag" on the drive mechanism during the cycling than we were accustomed to seeing with other multiple-play machines. Cueing-lever action is precise and we were able to interrupt play of records and resume playing with a maximum error of no more than one groove width.

TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **GARRARD**

Model: **GT-55**

TURNTABLE SYSTEM MEASUREMENTS

PERFORMANCE CHARACTERISTICS	R-E Measurement	R-E Evaluation
Wow-and-flutter (% WRMS)	0.04	Excellent
Rumble, unweighted (dB)	50	Very good
Rumble, (DIN weighted "B") (dB)	68	Very good
Speed adjustment range (\pm %)	+3.5, -4.0	Useful
Speed build-up time (rotations)	<1.0	Excellent
COMPONENT MATCHING CHARACTERISTICS		
Tracking Force Range (___ to ___ grams)	0-3	
Anti-skating Force Range (___ to ___ grams)	0-3	
Available speeds (RPM)	33 $\frac{1}{3}$, 45	
Drive System	Belt	
Motor Type	DC servo	
Power Requirements	<10(watts)	
Pick-up arm wiring capacitance (per channel) (pF)	23	
MISCELLANEOUS EVALUATIONS		
Adequacy of Controls		Excellent
Automatic features, performance		Very good
Speed stability		Superb
Vertical pickup arm friction		Good
Lateral pickup arm friction		Good
Quality of Construction		Excellent
OVERALL TURNTABLE SYSTEM RATING		Very good

TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Garrard**

Model: **GT-55**

OVERALL PRODUCT ANALYSIS

Retail price	\$249.95 (Base and dust cover are extra.)
Price category	High
Price performance ratio	Very Good
Styling and appearance	Excellent
Sound quality	Excellent
Mechanical performance	Excellent

Comments: Garrard's emphasis of their articulated pickup-arm head is, perhaps, unfortunate, for there is so much else going for this totally redesigned unit that readers of their literature may lose sight of its other virtues. The departure from a synchronous motor (however many poles it might have) to a DC servo motor that is electronically controlled is, to us, a more significant breakthrough. The low mass magnesium pickup-arm is another significant breakthrough that would be important even if it did not include the "true-tangent" feature. Belt drive for a multiple-play turntable system is no longer unique, but Garrard's excellent execution of this principle, plus their use of a second belt to actuate the pick-up arm cycling and motion, is an improvement over earlier linkages and results in one of the smoothest changing cycles we have ever seen. Truly, their claim that the pickup arm is handled more gently than could be done by the steadiest of hands is well founded. The one thing we wish Garrard had been able to achieve with their new design is somewhat simpler installation. The typical purchaser of a multiple play turntable is, perhaps, not as sophisticated or mechanically inclined as is the purchaser of a single-play machine and confrontation with the many "loose parts" (including the platter, the C-ring that must be removed and replaced, the belt which must be properly installed and the center-spindle which must be pre-lubricated) may be discouraging to some. Once the installation has been accomplished, however, the GT-55 performs extremely well, has fewer parts that can go wrong than did its predecessor, and measures well in all the major areas that determine ultimate turntable performance.

Nakamichi 610 Preamplifier



CIRCLE 101 ON FREE INFORMATION CARD

NAKAMICHI RESEARCH, INC. IS BEST KNOWN IN this country for their high-performance stereo cassette decks. The foremost deck in their line is the *model 1000*—a three-headed deck that has, in the few years since its introduction, become the standard machine against which all others are compared. More recently, the company has begun to produce other audio products such as monitor loudspeakers, microphones, phono pickups and now, wholly electronic components such as a power amplifier and the preamplifier control unit that we tested for this report.

The *model 610*, shown in Fig. 1, is a sloped unit that provides excellent visibility and accessibility to its operating controls and switches when positioned on a table-top. Centered at the top of the unit are two peak level meters that are calibrated over a wide

range, from -40 dB to $+10$ dB. Fast attack time (120 milliseconds) and slow decay (1.5 seconds) make these meters particularly suited to indicate program peaks. Three OUTPUT switches to the left of the meters, when used in conjunction with an available remote control box (*model RM-610*), permit instant comparisons and selection of three speaker systems or of three associated power amplifiers.

Since circuitry is divided into line-A and line-B switching, as well as left-right stereo channels, inputs may be assigned to the line-A or line-B busses or may be mixed by means of the pushbuttons just below the OUTPUT switches. This cluster of eight buttons at the left also introduces a series of test tones at frequencies of 1 kHz, 3.16 kHz and 10 kHz and, by simultaneously depressing more than

1 button, frequencies of 4.16 kHz, 11 kHz and 14.16 kHz are also available. The last button activates a pink-noise generator that can be directed to the outputs for a variety of system checks and tests.


The TONE LEVEL control just below this cluster of buttons adjusts the amplitude of test tones or pink noise while the large MASTER control just below sets overall output level and is equipped with a reference marker that can be set to any dB level for quickly resetting the MASTER control. A headphone jack is located to the left of the MASTER control, since a self-contained headphone amplifier is included in the *model 610*.

Two rows of buttons below the meters assign inputs to the line-A or line-B bus. Provision is made for two phono inputs, a pair of mikes, tuner, aux and three tape decks for each line bus. Below the input selectors are five microphone level controls (in addition to the mike 1 and mike 2 inputs, a fifth "blend" microphone can be connected for L+R assignment), and each microphone can be phase-inverted (since microphone wiring is not standardized) by a pushbutton located above each microphone level control.

A power on/off button is located at the upper right, while below are four buttons for SOURCE or any of the three tape monitor settings. Four more buttons just below the source-monitor switches are used in conjunction with the phase-check buttons to provide L-only, L-R, L+R and R-only phase checks. A balance control is located below these buttons, and below it is a separate MONITOR control that alters signal levels at the separate monitor output jacks (independent from the line outputs).

The rear panel, shown in Fig. 2, has a vertically oriented surface that contains the line and monitor outputs, the previously listed inputs and tape outputs, the five microphone inputs, a ground terminal and two convenience AC outlets. The tape and line output terminals are completely unaffected by the BALANCE, MONITOR level, and MASTER level controls. These controls are simply there to control monitoring sound systems during recording.

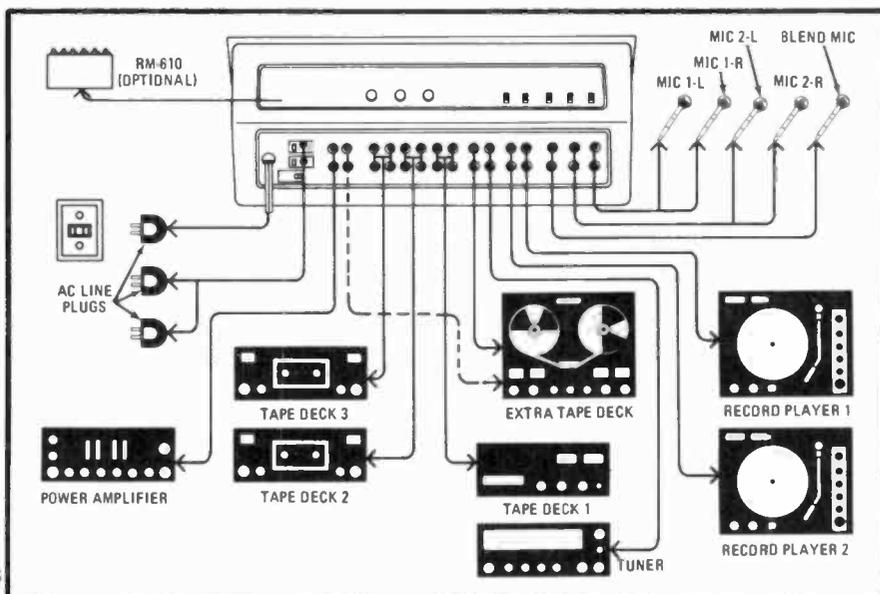The sloped section above contains three output-level matching controls, phono input-impedance switches (200, 50,000 and 100,000 ohms), and microphone attenuator switches with positions for 15 or 30 dB attenuation in case all microphones used do not have equal sensitivities.




MANUFACTURERS PUBLISHED SPECIFICATIONS:

Frequency Response: Mike: 30 Hz—100 kHz, $+0$, -1.5 dB; Phono: 30 Hz—15 kHz, ± 0.3 dB; High Level: 20 Hz—100 kHz, $+0$, -1.5 dB. **Input Sensitivity:** Mike: 0.2 mV; Phono: 1 mV; High Level: 75 mV. **Maximum Input Level:** Mike: 1 volt; Phono: 250 mV; High Level: 50 volts. **Signal-To-Noise Ratio:** (IHF A-weighting): Mike: Better than 53 dB, referenced to 0dB; Phono: Better than 80 dB, referenced to 1 mV. **Distortion:** Mike: Less than .01% at all frequencies up to 10 kHz; Phono: less than .005% at all frequencies up to 10 kHz; High Level: Less than .005%. **Dimensions:** 15.75 wide \times 6.70 high \times 9.33-inches deep (400 \times 170 \times 237 mm). **Weight:** 15½ pounds (7 kg).

Some idea of the variety of components that may be used with the *model 610* is illustrated in Fig. 3.

Circuit configuration

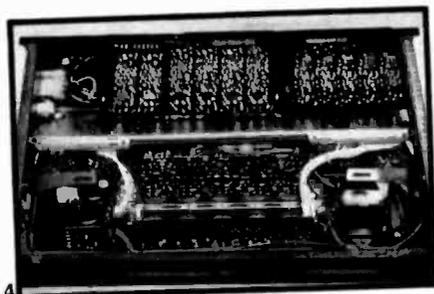As can be seen from the photo of the internal layout of the 610 (Fig. 4), Nakamichi has managed to incorporate a vast amount of circuitry into a relatively small space while retaining reasonable access to the many circuit boards involved in the assembly of the product.



A particularly interesting circuit section is the phono preamplifier/equalizer. First, its rated sensitivity is a low 1.0 mV, which means that there is enough gain so that it can be used with many of the moving coil cartridges that have been gaining in popularity in recent years. A basic schematic layout of the phono-preamp section is shown in Fig. 5. The first stage employs a unique "triple transistor" circuit. The three transistors are arranged in a parallel configuration that provides a signal-to-noise improvement of around 5 dB above that of conventional designs. Selected low-noise silicon units are used for these "first stage" transistors, which act as a single transistor with very low internal impedance in a common-emitter configuration. A second common-emitter stage, Q4, with current supplied by constant current source Q6, establishes a low distortion current drive for the final stage. The output stage of the phono section is a complimentary Class A circuit with bias set by the Q5 collector to emitter voltage. Proper RIAA equalization is provided via the negative feedback loop, which ties the output signal to the emitter of the first triple-transistor stage.

Laboratory measurements

Table I summarizes measurements and lists reference levels applicable to the Nakamichi 610. Microphone input sensitivity (without attenuation) was measured as 0.2 mV for a 0-dB meter reading, exactly as specified. It should be noted that the phono preamplifier signal-to-noise ratio recorded (-83 dB, IHF A-weighted) was measured with respect to a 1-mV input sensitivity. Most other preamplifiers have an input sensitivity of around 2.0 to 2.5 mV, so that if the S/N were specified with respect to that higher input level (typical of moving magnet cartridge nominal outputs), the figure would be between 89 and 91 dB! Carrying this still further, if a 10 mV input signal reference were used (many manufacturers quote S/N with respect to this high input figure), S/N would be an incredible 103 dB!

The few distortion figures listed in Table I are actually residual distortion contained in our source signal.

Use and listening tests

Since there are nineteen different inputs to

TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Nakamichi**

Model: **610**

PREAMPLIFIER/CONTROL PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
OUTPUT LEVELS		
Monitor out at 0-dB (volts)	1.0	
Line out at 0 dB (volts)	0.316	
Record out at 0 dB (volts)	0.316	
Headphone out at 0 dB (mW/8-ohms)	40.0	
Maximum monitor out at clipping (volts)	6.0	Very good
Maximum line out at clipping (volts)	6.0	Very good
Maximum record out at clipping (volts)	6.0	Very good
Maximum phones out at clipping (mW/8 ohms)	320	Good
DISTORTION MEASUREMENTS		
(Master volume @ -20dB, line out @ 2 volts, 1kHz)	0.0025*	Superb
Mike inputs (%)	0.0025*	Superb
Phono inputs	0.0025*	Superb
High level inputs	*Limit of test equipment	
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA ± dB)	0.2	Excellent
Maximum input before overload (mV)	270	Excellent
Hum/noise referred to full output (dB) (at rated input sensitivity)	83 (IHF "A")	Superb
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, ± dB)	20-80, 1 dB	Excellent
Hum/noise referred to full output (dB)	88	Very good
Residual hum/noise (min. volume) (dB)	95	Excellent
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	1.0/1.0	
Input sensitivity, auxiliary input(s) (mV)	75	
Input sensitivity, tape input(s) (mV)	230	
Output level, tape output(s) (mV)	316	
Output level, headphone jack(s) (V or mW)	40 mW	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		Superb
Adequacy of input facilities		Superb
Arrangement of controls (panel layout)		Excellent
Action of controls and switches		Excellent
Design and construction		Superb
Ease of servicing		Good
OVERALL PREAMPLIFIER/CONTROL PERFORMANCE RATING		Superb

the *model 610*, attempting to describe everything you can do with this preamp would require more space than a single test report warrants. Here are just a few of them. You can do live recording with up to five microphones on as many as three separate tape decks simultaneously with independent mon-

itoring capability. You can combine live and prerecorded inputs, such as three mikes and a tape deck or a phono input source. You can mix two stereo sources, such as a pair of phonos, a tuner plus a tape deck, or any combination of these. A-B comparison of any two sources, such as tape versus disc, tape

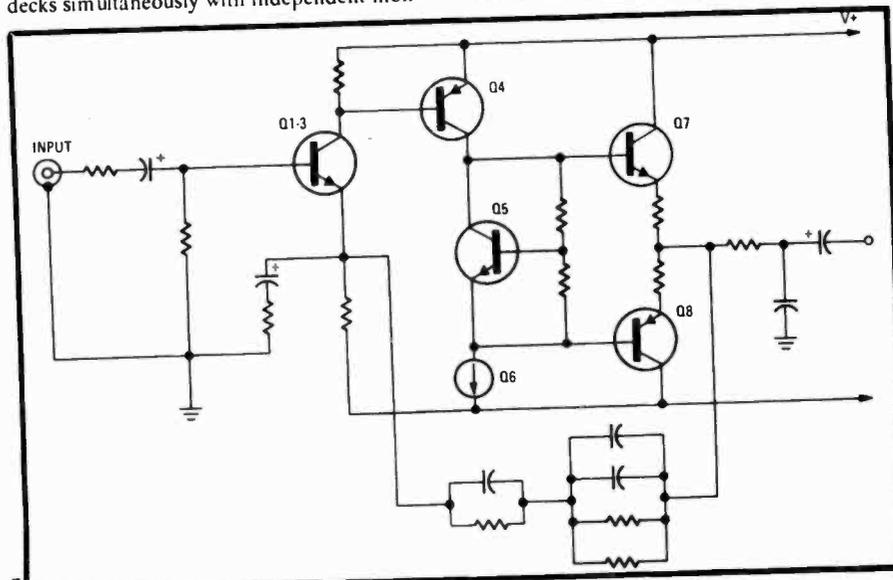


TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: **Nakamichi**

Model: **610**

OVERALL PRODUCT ANALYSIS

Retail price	\$570 (\$550 In silver finish)
Price category	Medium-high
Price/performance ratio	Excellent
Styling and appearance	Superb
Sound quality	Superb
Mechanical performance	Excellent

Comments: As you might gather from glancing at our Evaluation column above and in Table I, we were tremendously impressed with the design, construction and performance of the Nakamichi 610. We hasten to point out, however, that the emphasis on this unit is understandably towards the serious tape recordist, rather than to the passive audiophile. If you crave elaborate tone controls, filters, loudness controls and the like, this is *not* the preamp/control unit for you. But if you normally play your music flat, own a tape deck or two, and like to do some live recording, the 610 can well serve not only as your basic preamp but as your mixing console as well. The incorporation of the test tones and the pink noise generator was truly an inspiration as far as we are concerned. Comparing the sound of "pink noise" in an A-B test is still one of the best methods we know for evaluating the response of a component system by ear and even the few frequencies from 1 kHz to 14.6 kHz supplied by the test-tone circuitry are enough to help you calibrate or align tape heads and the rest of your tape recording circuitry should that become necessary. The tones serve as a ready means of comparing different tape formulations and their performance on your given machine, too.

Considered strictly as a preamplifier, the performance of the 610 is as close to that of a "straight wire with gain" as anything we have ever measured. Our test equipment, as good as it is, was simply not able to indicate meaningful distortion figures, since its own signal distortion is known to be around 0.0025% and that reading was obtained using any of the input terminals of the 610.

Controls are logically arranged on the sloped front panel, though a few minutes of familiarization are needed to operate the unit with assurance. Nakamichi recently introduced a matching power amplifier, *model 620*, and had previously introduced their *model 600* stereo cassette deck. These three items, placed side by side or mounted in a special rack available from the company, represent a flexible home recording system that any serious recordist would be proud to own and use.

versus FM and so forth becomes simple and meaningful, with the aid of the independent level matching controls at the monitor outputs. All of these intricate interconnection schemes are accomplished by the push of a few buttons—no juggling of patch cords, cables and the like.

Used alone, with a pair of good quality headphones (in remote recording situations where the balance of a stereo monitoring system is not available), we were able to do on-location monitoring of a recording and, unlike the headphone outlets supplied on some lesser preamps, there was plenty of gain and power available to drive our 8-ohm phones so that we could hear the full dynamic range of the sound sources we were mixing during that session. While we did not have the optional *RM-610* remote control

box available for our tests, we can easily see that its addition (for around \$75.00) would add even more versatility to this "dream" preamp.

As for sonic qualities of program sources fed through it strictly for musical listening purposes, we compared FM signals received from one of the few "clean signal" stations in our area by feeding them directly to our high quality power-amp and to that same power amp via the line inputs and outputs of the *model 610* preamp. With levels adjusted carefully, we, as well as several other listeners subjected to the same test, could not detect any audible difference between the two setups. If a preamp control unit is intended to process signals with absolutely no coloration or alteration, this one comes as close to doing so as anything we have ever heard. If, on the

Higher hi-fi recording group goes back to direct-on-disc

A Canadian record company, Nimbus 9 Productions Ltd., has abandoned the tape-recording stage of disc production. The new direct-on-disc albums, bearing the Umbrella trademark, will be sold in the United States by Audio-Technica, the phono cartridge firm.

According to Jon Kelly, general manager of Audio-Technica, bypassing the tape recording stage eliminates problems of distortion, limited dynamic range, and of course, tape noise. Because engineers mix and record the studio performances direct onto a master disc, Kelly points out: "Musicians and engineers must display a high degree of professionalism. There is no room for error.

Records were expected to be available early this winter. Discs will cost \$12.95 at retail. Umbrella's first release through Audia-Technica will be a rock album by the Toronto group "Rough Trade," a six-piece ensemble. Later releases will include classical and percussion offerings.


Large-screen TV viewers now have stereo vision

Three-dimensional wide-screen projection television was demonstrated to the Society of Motion Picture and Television Engineers at their conference in New York recently. The demonstration was accompanied by a technical paper by television consultant and video experimenter Bruce D. Stephens.

Mr. Stephens' technique combines two

WHAT IS PINK NOISE?

Pink noise, for those unfamiliar with the term, is random-frequency noise that contains equal energy in each octave in the audio spectrum, from 20 Hz to 20 kHz. So-called white noise is also random-frequency noise, but it contains equal amplitudes of all audio frequencies. To modify white noise so that it contains equal energy in each octave, the random noise must have its amplitude attenuated at a constant rate of 3-dB per octave. Such a noise signal is extremely useful in comparing sound qualities of different components and loudspeakers. When listening to pink noise through an audio system, even minute changes in overall response can be detected by a clear change in the overall character of the noise heard. In the photo shown, a spectrum analyzer was swept

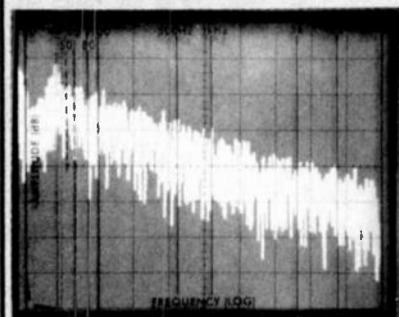

from 20 Hz to 20 kHz while a pink-noise signal was applied to the vertical input. The results clearly show the 3 dB-per-octave slope of the frequencies contained in the pink-noise signal from the Nakamichi 610 preamplifier.

other hand, you insist upon a variety of equalizing and tone controlling functions, you can always buy a separate graphic equalizer which could be outboard-connected to the *model 610* via one of the tape monitor circuits. You would still have two such circuits available for two tape decks.

Our summary comments regarding the Nakamichi *model 610* will be found, together with our overall product analysis, in Table II.

R-E


well known devices, the General Electric single-lens *Light Valve* color television projector and the Marks Polarized Corp. 3-D film projection *Polarator*, to produce a new effect.

The two slightly differing left-eye and right-eye images, positioned one above the other in a single film or video frame, are projected through the *Light Valve* projector and the *Polarator*, then redirected toward the screen so that they are superimposed.

One of the superimposed pictures is horizontally, the other vertically, polarized. The viewer wears a pair of inexpensive viewing spectacles of the type used in 3-D movies. These act as a decoder, allowing each eye to see only the picture intended for it.

R-E

New For Cassettes

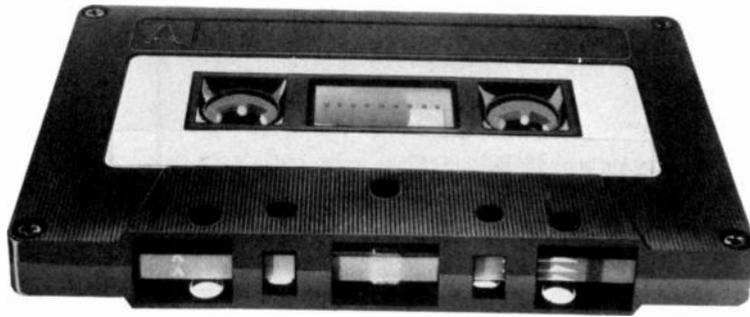

Automatic Program Search

New system for cassette decks automatically switches deck from fast forward or rewind mode to play at the beginning of recorded passages

KARL SAVON
SEMICONDUCTOR EDITOR

GETTING CLOSE TO THE SELECTION YOU want is not too difficult using the footage indicator on a cassette tape. But then there is the annoying trial and error hunting to first find the precise selection, and then to locate its opening bars. A turns-counter works providing you have the number of turns written down, that you remembered to reset it at the beginning of the tape and, of course, that your machine has one.

Sharp Electronics has an interesting alternative in their GF-6000 Cassette Recorder and MW/SW/FM Receiver combination. It incorporates the APSS (*Automatic Program Search System*) that is designed to quickly get you to the beginning of the next tape selection or back to the beginning of the one in progress.

What identifier can be found on most tapes that would serve as a beginning-of-selection marker? Sharp's answer is the blank interval between recorded segments. APSS looks for these blank segments in either the fast forward or rewind modes and switches back to the normal playback mode when it finds one.

Pushing the FWD-APSS button starts a fast-forward operation in the conventional way by retracting the pinch roller

from the capstan and engaging the fast-forward gear with the take-up reel. The only mechanical difference is that the function is latched by the APSS lock-plate that can be released by applying power to a solenoid-type plunger. The system runs at 10 to 30 times normal playback speed until the electronics senses a blank interval in the tape. When this occurs, the plunger is activated and the fast-forward gear is disengaged. The action is identical when the fast-rewind mode is selected.

How it works

The circuit details are shown in the schematic in Fig. 1 and the waveforms in Fig. 2. In the playback mode, equalizer amplifier IC2 is fed from the record/playback head. Part of its output signal drives the APSS preamp IC4. Power is applied to the preamp only during APSS operations. Amplified signals from the tape are coupled to the base of Q111 through C177. Both the base and emitter of the transistor are connected to the +12-volt (+B1) supply so that when the output of IC4 exceeds $1 V_{be}$ (one base-to-emitter junction potential of approximately 0.6 volt), transistor Q111 turns on. Each time Q111 conducts, it supplies a relatively

high-current pulse into its collector load—the R177-C179 network. In effect, C179 is charged through the 33-ohm emitter resistor R176, but discharges through the 8.2K resistor R177.

Very much like a diode peak detector rectifies a signal, transistor Q111 peak detects and amplifies the signal from the tape. Whenever a signal is present, the collector of Q111 is very close to 12 volts. The output of this transistor drives the base of Q112. Transistors Q112 and Q113 form a regeneratively-switched schmitt trigger. An input sufficient to start Q112 into conduction quickly causes it to go fully on while Q113 turns off. As the collector of Q112 is lowered, the emitter voltage of Q113 and Q112 is reduced. Transistor Q112 then conducts more heavily because of its increased base-to-emitter potential, and things spiral or rather regenerate so that the circuit latches.

Notice the way the collector of Q113 feeds the emitter of the following Q114 stage through capacitor C180. The emitter and base of this device are both referenced from the positive supply so it is biased off. Further, the positive pulse coupled to its emitter when Q113 goes off is in a direction to keep it off, so nothing happens here yet. As long as

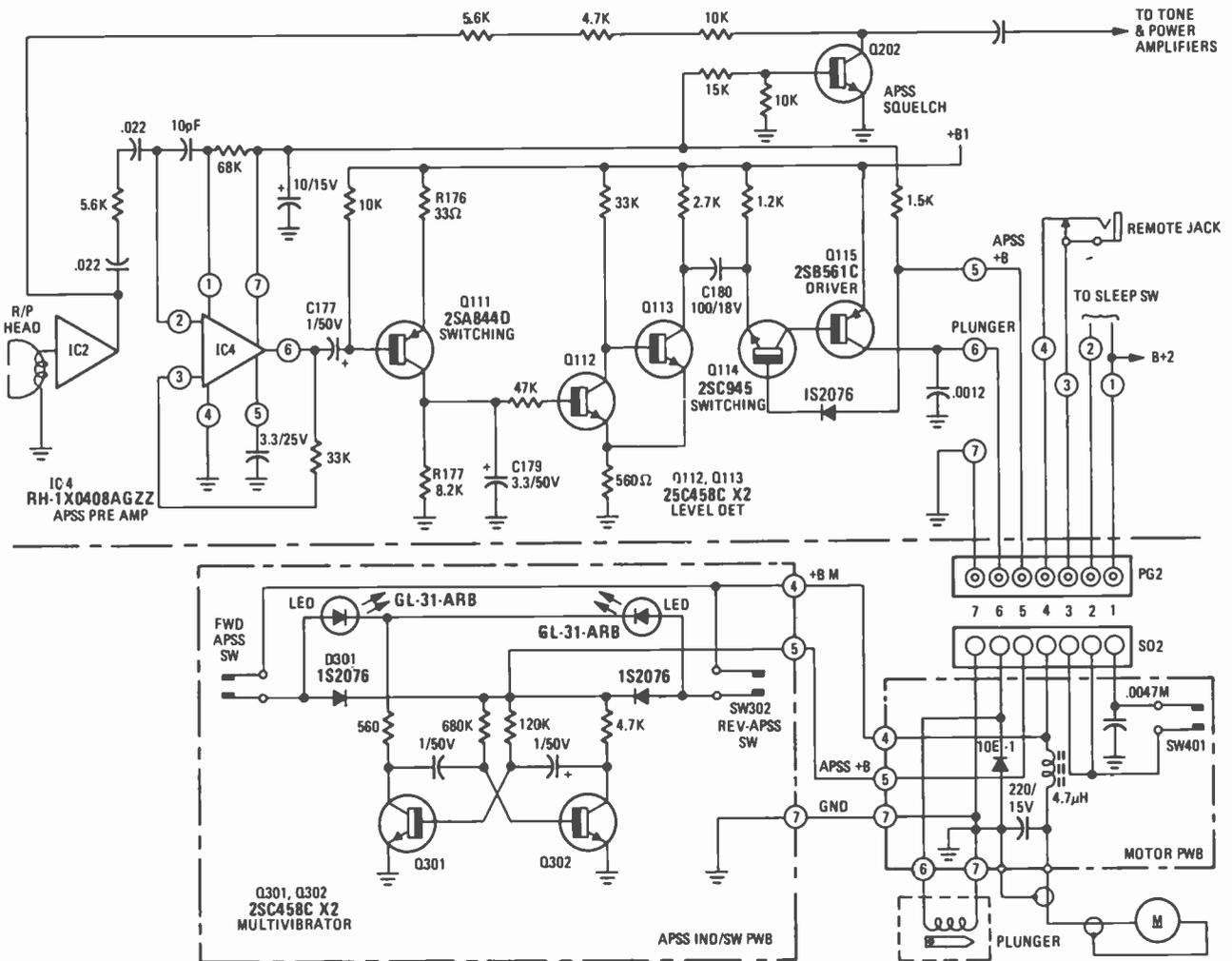


FIG. 1—APSS CIRCUIT detects blank intervals in program material and switches cassette deck from fast forward to play mode.

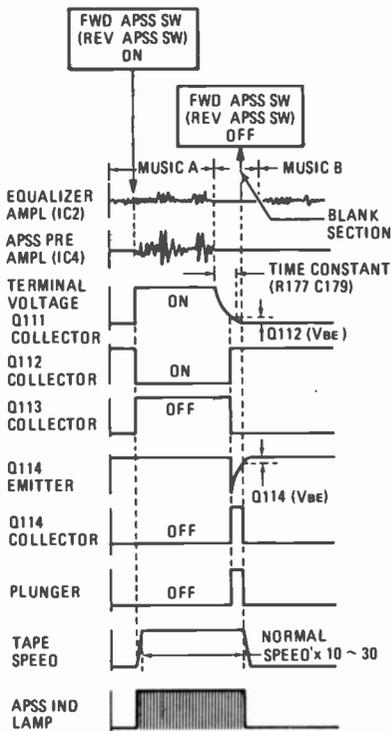


FIG. 2—WAVEFORMS of the APSS circuit. Circuit detects blank interval between recorded passages.

Q114 is off, driver transistor Q115 is also off. Transistor Q115 drives the solenoid that disengages the fast-forward gear.

As the high-speed search continues, a drive current is sent to squelch transistor Q202 (not shown). The base current of transistor Q202 is derived simply by a resistor from the APSS +B supply. Signals are blocked from reaching the speaker by Q202 whenever an APSS search is in progress.

Assuming that a blank segment of tape has been reached, let's retrace the circuit operation: The signal from the playback head is amplified by IC4 and it now consists only of low-level noise of insufficient amplitude to overcome the base-to-emitter threshold of Q111. This transistor no longer provides current pulses to the R-C network in its collector circuit. The network discharges as shown in the waveforms of Fig. 2. Discrimination against temporary nulls in program material is provided by the time constant of the R-C network. A minimum of a one-to-three second blank interval at normal playback-speed is necessary for the APSS circuit to detect. The range in time is because of


the three-to-one variation in fast tape speed.

Base drive to transistor Q112 falls below its conduction level and Q112-Q113 switches to its opposite state with Q113 on. The negative pulse generated at the collector of Q113 turns on Q114 for a time interval determined by the coupling network. During the time it takes to charge C180, Q114 and Q115 remain on.


The circuit can be fooled by a prolonged soft music or blank passages. A second or third operation of the button may be required in such cases. Complete misses of the blank leader occur if the button is pressed when the tape happens to be less than 10 playing seconds away from the leader.

Two LED's indicate operation of the circuit, one for each tape direction. Switch contacts S301 are closed by the FWD-APSS button. Power to IC4 and the squelch transistor is supplied through the switch contacts and diode D301. Transistors Q301 and Q302 are an astable multivibrator that flashes the LED indicator. The bottom waveform in Fig. 2 represents the pulsing of the LED during the search time.

R-E

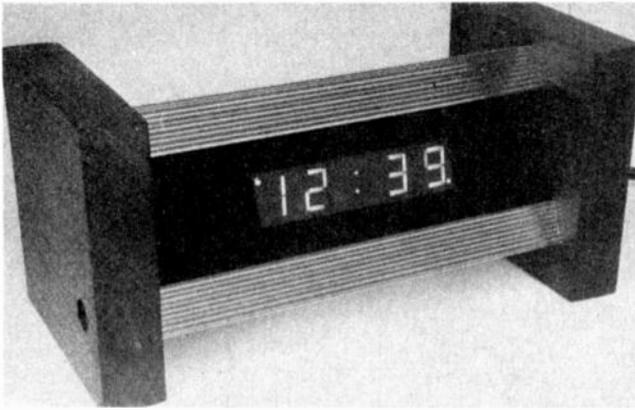

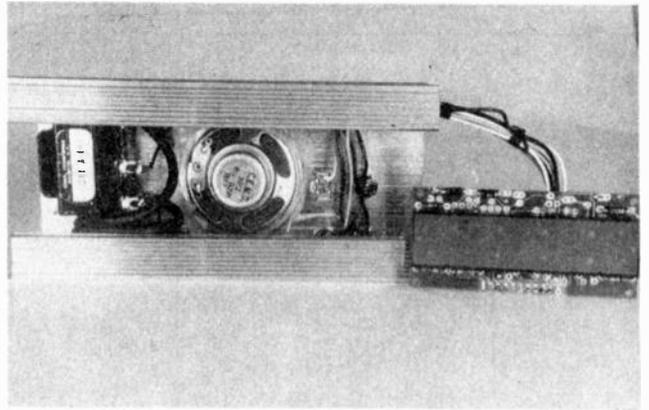THE INTERFAB DC-60 CLOCK comes complete with chassis and end blocks, which make a case of excellent appearance.



INTERIOR VIEW, INTERFAB DC-60N. Speaker comes mounted to the case. Transformer is a Signal model 241-3-16, supplied with the kit. Alarm circuit is not installed.

Easy-to-Build Digital Clocks

Preassembled clock modules are the heart of these full-featured LED clocks.

They are built by simply adding switches and a transformer

FRED BLECHMAN

FIFTEEN YEARS AGO, IF YOU WANTED TO BUILD AN ELECTRONIC digital clock to display hours, minutes and seconds, it took hundreds of parts, a hopeless maze of wiring and would have cost at least \$150 for parts. In the early '60's, when the first IC's became popular, you could build the same clock with 12 IC's and about 70 additional discrete parts—still a lot of wiring—at a cost of about \$75. Then along came LSI (*Large Scale Integration*), and its application resulted in IC's designed specifically for clocks and watches.

From a large stable of contenders, a few thoroughbreds emerged, among them the National Semiconductor MM5314 and MM5316. These IC's contained various clock functions, but they still needed a variety of parts for signal and display conditioning to end up with a clock. Kits appeared on the market in abundance for \$12 and up, with a wide spectrum of digit sizes and features—but most of them still required a lot of careful soldering and hours to assemble and troubleshoot. (See "Digital Clock Kit Roundup", *Radio-Electronics*, August and September 1976 issues.)

The latest advance in electronic digital clock design is the full-featured, pre-tested "clock module" with almost all the electronic parts preassembled on a common board. All you need to add is a transformer and switches for a complete clock!

The first three clock modules to appear on the market are the National Semiconductor MA1001 and MA1002 (both with 0.5-inch-high digits) and the Fairchild FCS8100 (with 0.8-inch-high digits). The MA1001 series, released in December 1975, is already obsolete and has been replaced by the slightly smaller MA1002 series. Some MA1001A's are still available at

a reduced price (see parts list). Functionally, the MA1001A and the MA1002A are identical—the physical difference is that the large 40-pin MM5385 IC package has been removed from the display side of the board and now appears as a small circular black "blob" on the back. Figures 1 and 2 show the physical dimensions of these two modules. The Fairchild FCS8100, recently released, is roughly a half-inch wider and higher, since it has digits 60 percent higher. See Fig. 3 for its physical dimensions and pin connections.

Features and assembly

The MA1001A and MA1002A have the same features: 1. Bright 3½-digit 0.5 inch red LED 12-hour display showing



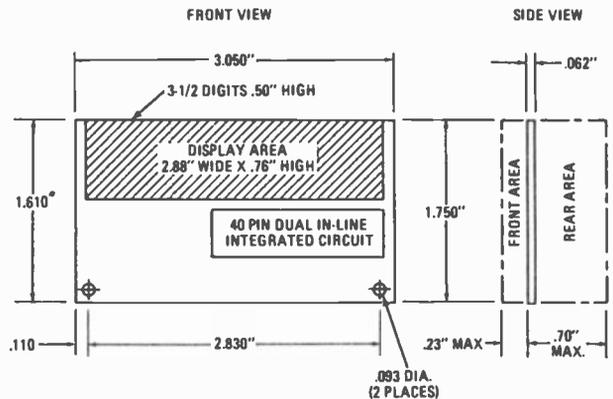



FIG. 1—PHYSICAL DIMENSIONS of the MA1001A.

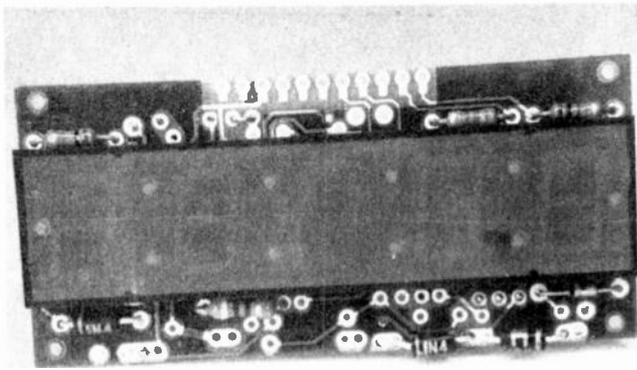

MA1002A DIGITAL CLOCK MODULE.

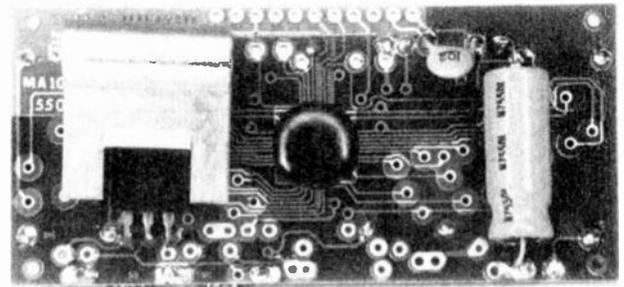

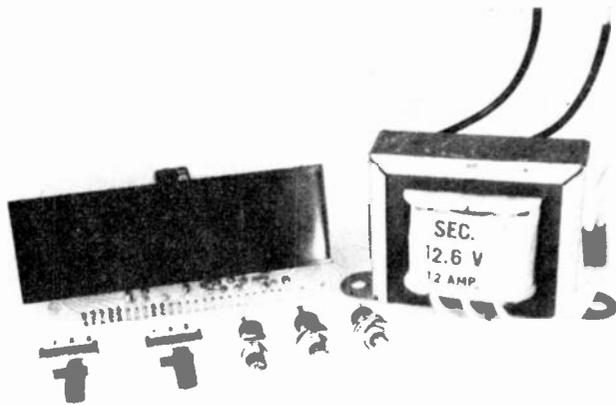THE MA1002A MODULE, REAR VIEW. The "black blob" seen in the center is the IC.



FAIRCHILD FCS8100 MODULE with transformer and switches.



FAIRCHILD FCS8100 clock with the controls mounted on top.

hours and minutes, but with seconds displayed on demand. 2. Alarm and 9-minute "snooze". 3. Alarm-on indicator. 4. PM indicator allows setting alarm for 24-hour repeat. 5. External radio can be controlled with 59-minute "sleep" function. 6. Direct drive of display—no radio interference. 7. Brightness control capability. 8. A 1-second flashing colon. 9. Power failure indication—the entire display flashes on and off.

Other versions of the MA1001 and MA1002 (identified by the suffix letters B,C,D,E,F,G & H) offer a variety of built-in options, such as 24-hour display, 50-Hz input, and alarm tone output (requiring a special earphone). For simplicity, only the MA1001A and the MA1002A full-feature clock-radio 12-hour 60-Hz modules are covered in this article.

Figure 4 shows the external wiring to the MA1001A or

MA1002A, and the connection points on the modules are shown in Figs. 5 and 6. The HOLD function is not shown wired, since it is also available by closing the SECONDS display switch and holding down the SLOW SET switch until you want counting to resume. Wiring is shown for maximum brightness; a 50K potentiometer wired to vary the resistance from MA1001A pin-6 or MA1002A pin-4 to V_{DD} will cause the


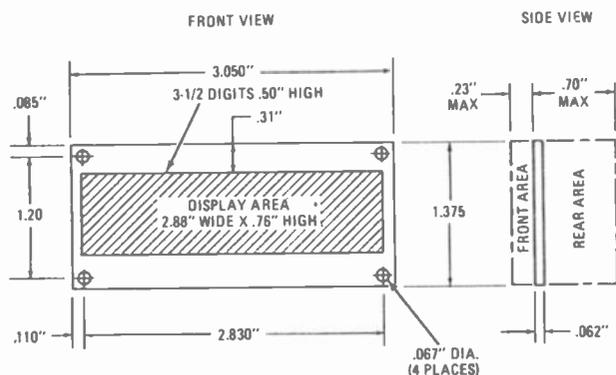


FIG. 2—THE MA1002A is smaller than the MA1001A.

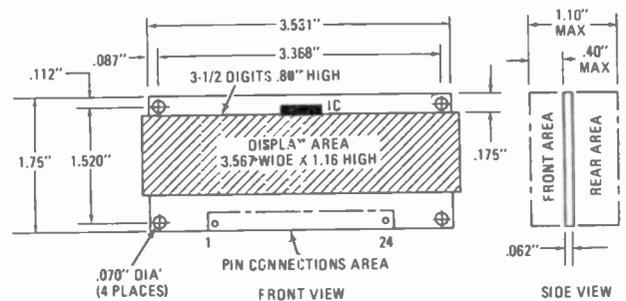

PIN	FUNCTION	PIN	FUNCTION
1	SLEEP DISPLAY INPUT	13	SNOOZE INPUT
2	ALARM DISPLAY INPUT	14	ALARM OUTPUT
3	SECONDS DISPLAY INPUT	15	ALARM OFF INPUT
4	SLOW SET INPUT	16	SLEEP OUTPUT
5	FAST SET INPUT	17	NO CONNECTION
6	50 OR 60 Hz SELECT	18	V_{DD} (MINUS TEST POINT)
7	12 OR 24 HOUR SELEC	19	NO CONNECTION
8	CENTER TAP (LED COMMON)	20	NO CONNECTION
9	CENTER TAP (LED COMMON)	21	NO CONNECTION
10	12.6 VAC (V_{DD})	22	OUTPUT (MINUS)
11	12.6 VAC (V_{SS})	23	ALARM SET INDICATOR—ANODE
12	12.6 VAC (V_{SS})	24	ALARM SET INDICATOR—CATHODE

FIG. 3—THE FAIRCHILD FCS8100. Physical dimensions and pin connections.

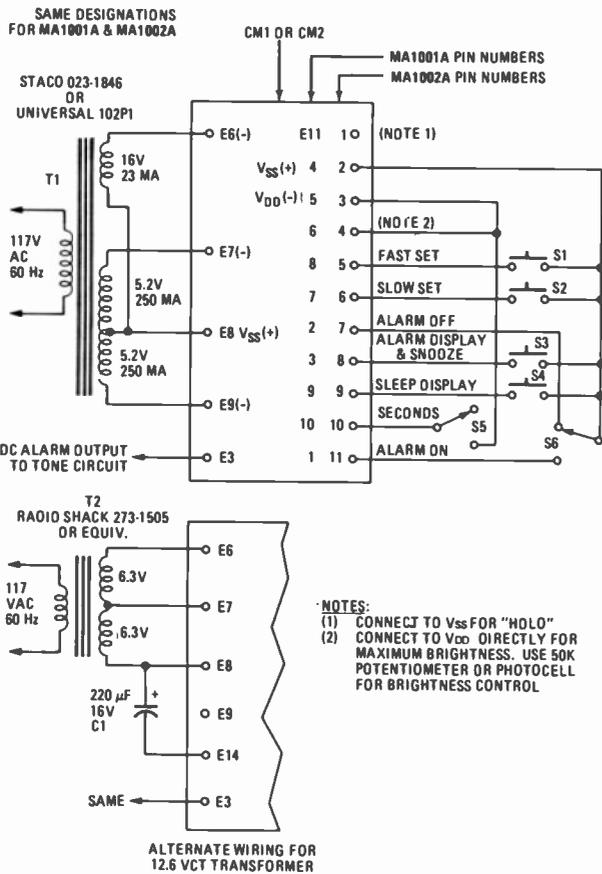


FIG. 4—THE WIRING DIAGRAM for either the MA1001A or MA1002A, showing how to substitute for the special transformer specified.

brightness to vary from dark (high resistance) to bright (no resistance). This suggests the use of a photocell to automatically dim the display at night—but be careful! The photocell must have specific light response to give you the proper brightness variation. The photocell shown in the parts list has been selected for this use.

The transformer specified in the National Semiconductor data sheet for these modules is a special model. Two sources are given in the parts list. However, a standard 12.6-volt center-tapped transformer (less expensive, but larger than the specified special transformer) can be used if wired as shown in Fig. 4. By adding C1 (220 μF 16V) electrolytic capacitor as shown, the brightness is increased to the level obtained with the special transformer, and without any sacrifice in performance.

Unfortunately, some of the pin connections are scattered around on the board, so be very careful in using the drawings as a guide; some discrete components near the connection points have been shown to help you. Although only the front of these modules are shown, they have a printed circuit on both sides, with plated-through holes, so you can solder to either the front or back side of the connection holes.

The Fairchild FCS8100 12-hour clock radio module is built around the FCM 3817A digital clock IC. It features: 1. 3½-digit 0.8-inch LED red display showing hours and minutes, with seconds on command. 2. Operation from 50 or 60-Hz line using a standard 12.6-volt center-tapped transformer. 3. Built-in alarm tone. 4. Alarm on indicator. 5. AM and PM indicators that permits setting the alarm for 24-hour repeat operation. 6. 9-minute "snooze". 7. External radio can be controlled with 59-minute "sleep" function. 8. Direct drive—no RFI. 9. Power failure protection for 10 seconds. 10. Power failure indication after 10 seconds—AM indicator blinks, and display reads 12:00. 11. 1-second flashing colon.

Figure 7 shows the external wiring to the FCS8100 module. A transistor driver is built into this module, and the jumper

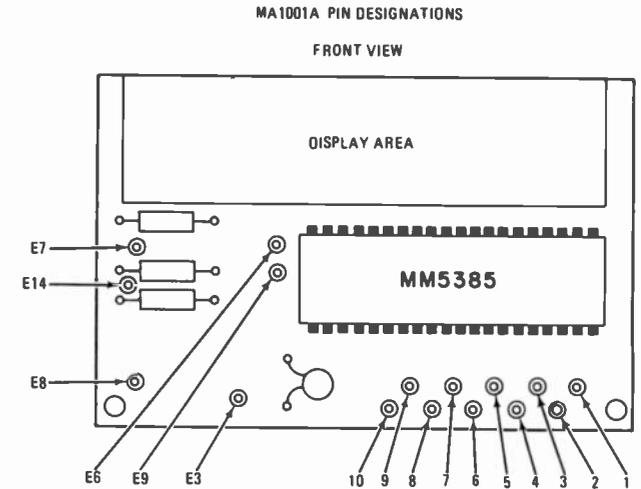


FIG. 5—PIN CONNECTIONS of the MA1001A.

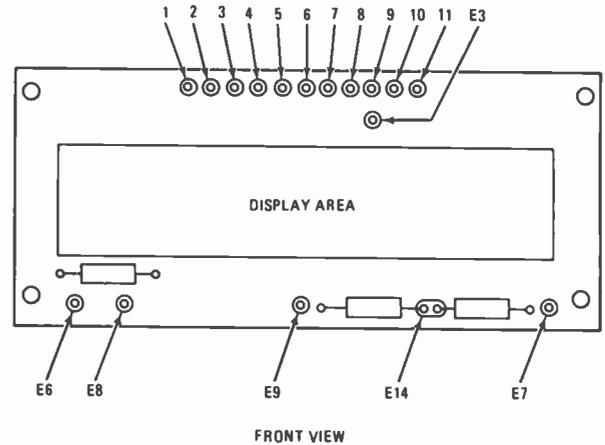


FIG. 6—PIN CONNECTIONS for the MA1002A.

between pins 14 and 16 is necessary to operate the transistor for the alarm function (the sleep-output pin is internally connected to the driver-transistor input). Since this module has a built-in tone oscillator connected to the alarm circuitry, all you need to do to hear the alarm is connect a small speaker and 33-ohm resistor in series between pins 9 and 22. Now, whenever the alarm switch S6 is placed in the ON position and the alarm-set time and real time coincide, you'll hear a 700-Hz (approximate) tone from the speaker.

The MA1001A or MA1002A modules have only direct current at their alarm outputs (E3). Therefore, a tone oscillator is required to drive a small speaker. Figure 8 shows such a circuit. Power for this oscillator is derived from the transformer (E8 and E9), using D1 and C2 as a rectifier and filter. This isolates the power supply of this circuit from the clock IC, which is a problem if power is taken directly from the alarm output pin. Instead, the alarm output (pin E3) only provides control voltage to the oscillator, with very little current drain (less than 0.5 mA). The speaker emits a loud, pleasant tone when the alarm is activated.

Although you can make an operating clock from one of these modules by wiring just the transformer and switches to the appropriate module points with a small-tip soldering iron in about 30 minutes (once you've identified the module terminals), the real "rub" is the packaging—mounting the various switches and the transformer and speaker in some kind of enclosure. Since this can take considerably more time than building the clock, the modern-style case offered in the parts list is highly recommended. It is made from an anodized aluminum and walnut end-blocks, held together with one long screw. All necessary mounting and speaker grille holes are punched and tapped, and even a red plastic bezel is included.

PARTS LIST

- CM1—National Semiconductor MA1001A Clock Module. (Jade Co., 2007 West Carson, Torrance, CA 90501. \$9.95 each plus \$1.00 shipping and handling per order. California residents add 60¢ tax for each module.)
- CM2—National Semiconductor MA1002A Clock Module. (Interfab, 27963 Cabot Road, Laguna Niguel, CA 92677. \$12.50 each, plus \$1.00 handling and shipping charge per order. California residents add 75¢ tax for each module. Order DC-60 MA1002A Clock Module.)
- CM3—Fairchild FCS 8100 Clock Module. (Interfab. Order DC-60 FCS 8100 Clock Module. \$18.00 each, plus \$1.00 shipping and handling per order. California residents add \$1.08 tax for each module.)
- T1—Special transformer, Universal 102P1 (Universal Transformer Co., 4211 W. Lawrence Ave., Chicago, IL 60630, \$5.00) or Staco 023-1846 (Staco, Inc., 2240 E. Third St., Dayton, OH 4421, \$8.75). 117V, 60 Hz input.
- T2—Transformer, 12.6V CT output, 117V 60 Hz input (Radio Shack 273-1505 or equal.)

- S1, S2, S3, S4—Pushbutton switches, normally open. (Radio Shack 275-1547 or equal.)
- S5, S6—SPDT switch (subminiature toggle, Radio Shack 275-613, or slide switch, Radio Shack 275-402 or equal.)
- C1—220- μ F, 16V electrolytic (used only with T2). (Radio Shack 272-1006 or equal.)


OPTIONAL ALARM PARTS

- R1—33 ohms, $\frac{1}{4}$ watt
 R2—6,800 ohms, $\frac{1}{4}$ watt
 R3—1000 ohms $\frac{1}{4}$ -watt,
 C2—470- μ F, 16V electrolytic
 C3—047- μ F, 16V disc
 C4—1 μ F, 16V electrolytic
 D1—1N4001 silicon diode
 IC—NE555 integrated circuit timer
 SPKR—Miniature 2-inch, 8-ohm speaker (Radio Shack 40-245 or equal.)
 CASE—Black plastic, with aluminum faceplate $6\frac{1}{4} \times 3\frac{3}{4} \times 2$ inches. (Radio Shack 270-627, or equal.)

COMPLETE KITS AND OPTIONS

Interfab Corp., 27963 Cabot Road, Laguna Biguel, CA 92677, offers the following: (California residents, add 6 percent sales tax on merchandise price. All orders, add \$1.00 shipping

- and handling per total order.)
- DC-60N—MA1002A Complete Kit. Including decorator extruded aluminum case (Specify, gold, silver or black) with all holes drilled; walnut end blocks, finished, drilled and tapped; clock module; all switches; all alarm parts; transformer; pre-cut switch wires; solder; red plastic bezel, line cord and grommet, mounting hardware and instructions. \$28.00 complete
- DC-60F—Fairchild FCS 8100 Complete Kit. \$31.00.
- DC-60C—Case and endblocks, pre-drilled, with case assembly hardware. Includes bezel. Specify case color. \$6.95.
- RAC-60—Remote control appliance option. Operates from Sleep or Alarm outputs to control AC appliance. Plugs into 117 volt AC line. All parts, including box, line cord, plug, jack, relay, switch, diodes, transistor and cable. \$7.00
- TB-60—Timebase option for car use. All parts and printed circuit board. \$4.95
- DCD-60—Automatic dimmer option, Special photocell. \$1.00

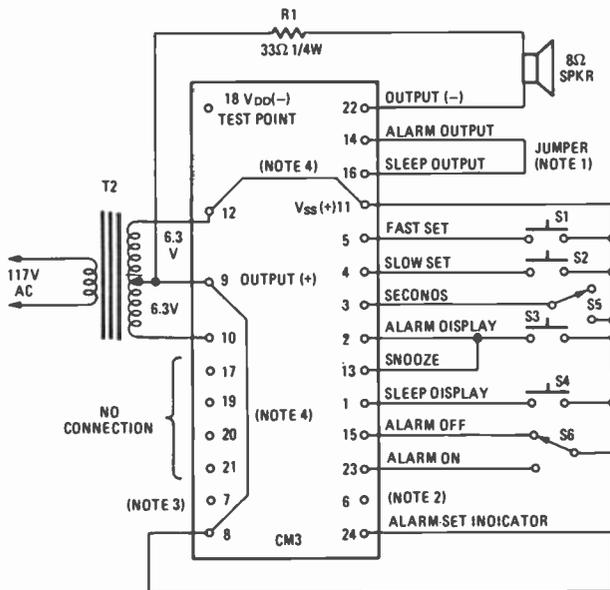

- NOTES: (1) SIGNAL VOLTAGES USED TO ENABLE "ON-BOARD" DRIVER TRANSISTOR AT PIN 22 (OUTPUT MINUS).
 (2) CONNECT TO V_{SS} FOR 50 Hz OPERATION.
 (3) 24-HOUR FORMAT CONNECTION NOT USED WITH THIS 3-1/2 DIGIT DISPLAY.
 (4) CONNECTED TOGETHER ON MODULE PRINTED CIRCUIT.

FIG. 7—THE FAIRCHILD FCS 8100 clock module. Wiring diagram and connections for speaker.

With this case, the whole job from box to finished clock should take less than an hour!

A complete kit, including *everything* (even solder) for an MA1002A or FCS8100 clock, is also available at a saving over buying individual parts. Various options are also offered. The Appliance Option allows an AC device (such as a coffee maker) to be turned on by the sleep or alarm outputs from the clock. The Timebase Option allows you to operate your clock from a 12 volt DC source, such as in your car, van or dune-buggy—it generates a 60-Hz signal using an MM5369 IC and a 3.58 MHz crystal and feeds it to your clock. The dimmer

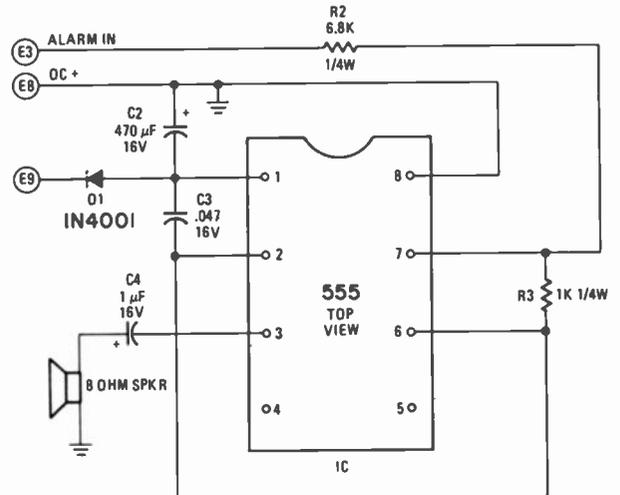


FIG. 8—AN ALARM TONE CIRCUIT for units using the MA1001A or the MA1002A.

option was mentioned previously.


If you want to "customize", feel free. Several clocks shown in the photos may give you some ideas. The clear plastic cube-shaped clock was built by Peter Hillen, National Semiconductor field applications engineer, using an MA1001A module, as a demonstrator unit. He used the special transformer specified by National in their literature, and used toggle and pushbutton switches for display functions and time-setting. Very modern in appearance, the clear case (it's actually tinted red) shows all the interior parts making it a unique decorator conversation piece.

Using the controls

The switch and display functions of all the modules are essentially the same. The FAST switch moves the minutes ahead rapidly, while the SLOW switch moves the minutes ahead—you guessed it—slowly. The SECONDS switch "shifts" the display to show the last digit of the minutes, and the

continued on page 99

Using PLL for CB Frequency Synthesizers

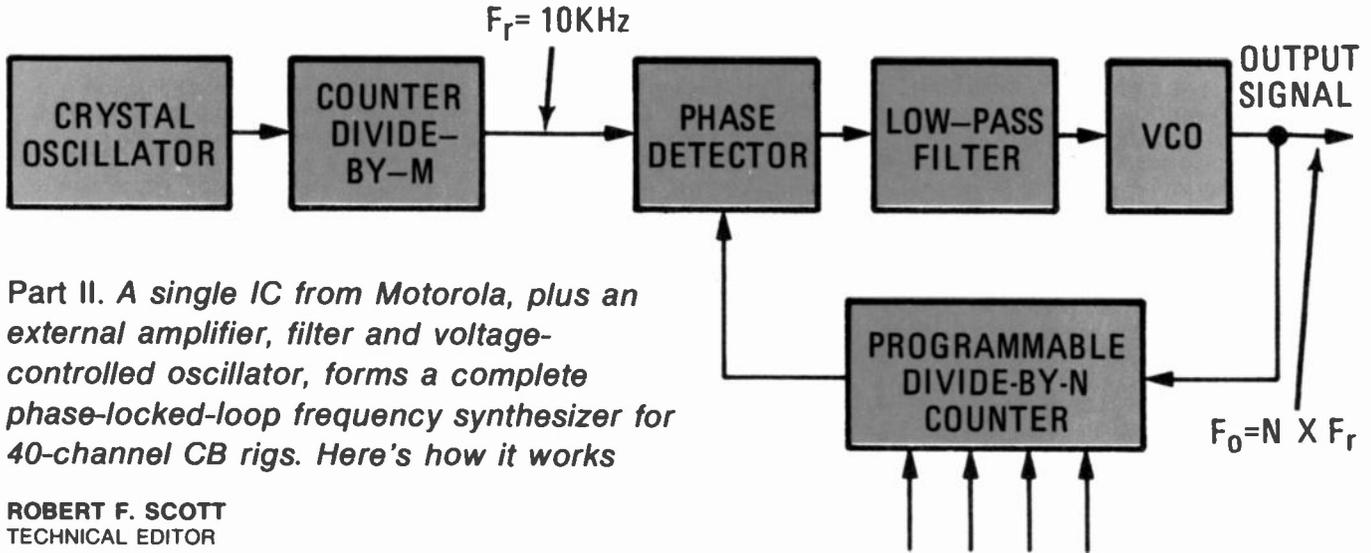

Part II. A single IC from Motorola, plus an external amplifier, filter and voltage-controlled oscillator, forms a complete phase-locked-loop frequency synthesizer for 40-channel CB rigs. Here's how it works

ROBERT F. SCOTT
TECHNICAL EDITOR

LAST MONTH, WE REVIEWED THE BASIC phase-locked loop as applied to frequency synthesis and saw how the Nitron NC6402 digital PLL IC can be applied to a 40-channel CB rig. Now, as we promised, we'll take a look at the Motorola XC3390 phase-locked loop frequency synthesizer for CB radios.

The device is in a 24-pin plastic package with a 724 case configuration. It requires only one crystal to generate all transmit and receive frequencies in a 40-channel transceiver using a double-conversion superhet receiver. Channel selection can be by means of voltages from a binary-coded switch or from a 7-segment digital display. Figure 1 shows how the XC3390 fits into a typical CB transceiver.

When the transceiver is in the transmit mode, the synthesizer generates the channel carrier-frequency and feeds it to the exciter—a low-level RF voltage or power amplifier. In the receive mode, the synthesizer develops the oscillator

injection frequencies for a double-superheterodyne receiver with first and second IF's of 10.695 MHz and 455 kHz, respectively. The first and second mixer injection frequencies are on the low side of the channel carrier and the first IF, respectively.

Figure 2 shows the sections of the XC3390 and how they are used to generate the carrier frequencies for the transmitter. The reference signal is developed by a precise and highly stable crystal oscillator. This is the signal that is processed to provide the various precise signal frequencies needed in the transmit and receive processes. It is divided by 2 and by 3 to develop new precise signals on 15.36 and 10.24 MHz. The latter signal is divided by 2,048 to develop the 5-kHz reference that, as we saw last month, is needed as the reference for the frequency synthesizer as it develops signals for the 10-kHz spaced CB-channels.

Now, let's look at the VCO. It

operates in the range of 16.725 to 17.165 MHz—10.695 MHz below the channel carrier frequency—to prevent birdies and spurious frequency modulation due to RF feedback when transmitting. The VCO output frequency f_v is summed in a balanced modulator with the 10.24-MHz output of the divide-by-3 circuit to develop the exciter drive signal f_c —a signal that ranges from 26.965 MHz for Channel 1 to 27.405 MHz for Channel 40.

The 15.36-MHz output of the divide-by-2 circuit is mixed with f_v to produce a *difference* frequency f_m ranging from 1.365 to 1.805 MHz, depending on the channel selected. This signal frequency is fed to a divide-by-n circuit where it is divided by a number between 273 and 361 to develop an output at precisely 5 kHz when the loop system is in lock. (The divide-by-n circuit is a programmable divider whose operation is controlled by the binary number (n_{PL}) appearing on the program lines.) It is this 5-kHz signal that is compared to the 5-kHz reference obtained by dividing the 30.720-MHz reference frequency by 3 and then by 2,048. Any frequency or phase error develops a correcting current that—after being filtered and amplified—pulls the VCO back on frequency.

If the PLL system is out-of-lock, the phase detector develops an auxiliary signal that gates off the exciter drive signal. This prevents the transmitter from radiating an off-channel signal;

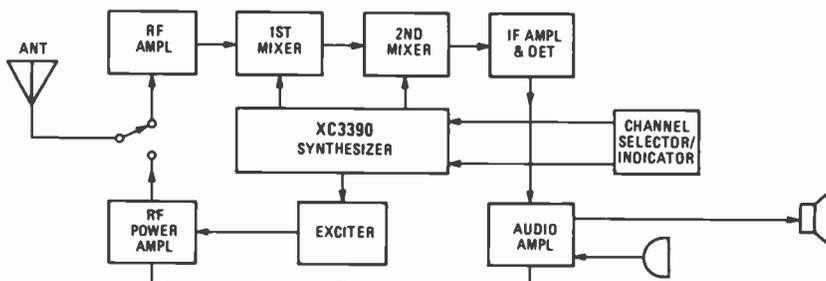


FIG. 1—CB TRANSCEIVER block diagram showing location of XC3390 phase-locked-loop.

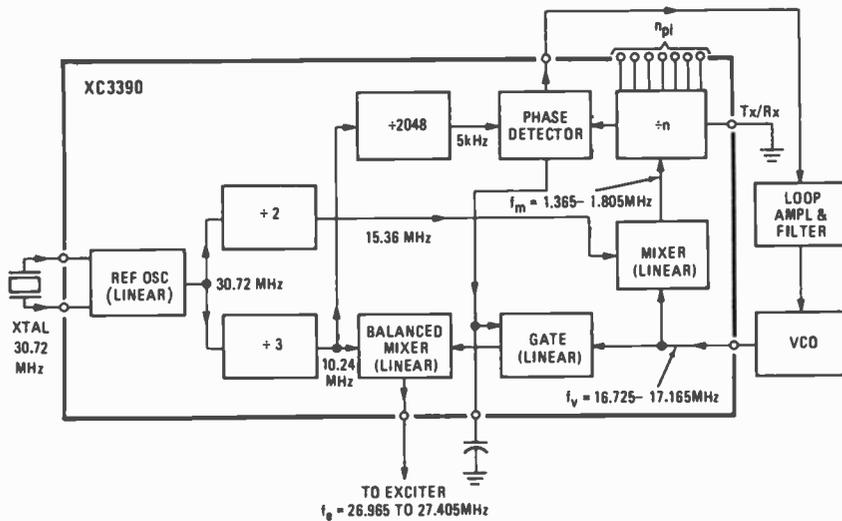


FIG. 2—MOTOROLA XC3390 phase-locked-loop IC requires external VCO, loop amplifier and filter. Frequencies are programmed via the $\div n$ counter

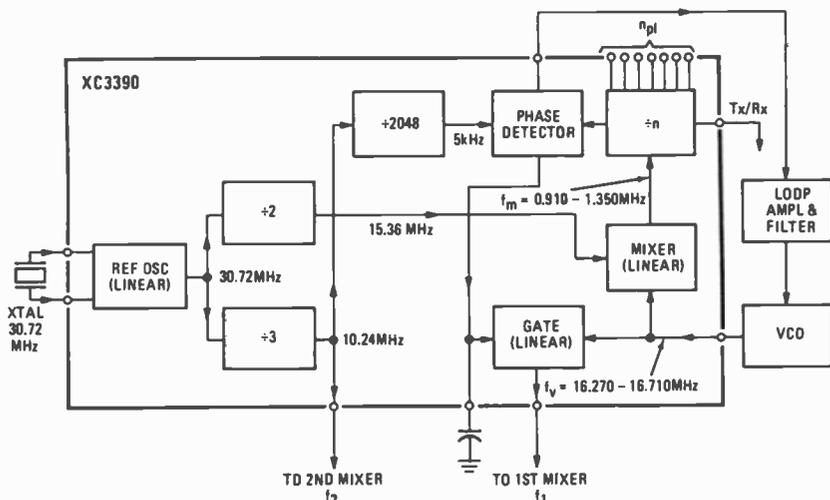


FIG. 3—RECEIVE FREQUENCIES generated by the phase-locked-loop synthesizer.

TABLE I

Channel Number	Decimal Equivalent (n_{pl})	Program Line Data Entries							
		D6	D5	D4	D3	D2	D1	D0	
1	0	0	0	0	0	0	0	0	
2	2	0	0	0	0	0	1	0	
3	4	0	0	0	0	1	0	0	
4	8	0	0	0	1	0	0	0	
5	10	0	0	0	1	0	1	0	
6	12	0	0	0	1	1	0	0	
7	14	0	0	0	1	1	1	0	
8	18	0	0	1	0	0	1	0	
9	20	0	0	1	0	1	0	0	
10	22	0	0	1	0	1	1	0	
22	52	0	1	1	0	1	0	0	
24	54	0	1	1	0	1	1	0	
25	56	0	1	1	1	0	0	0	
23	58	0	1	1	1	0	1	0	
26	60	0	1	1	1	1	0	0	
27	62	0	1	1	1	1	1	0	
30	68	1	0	0	0	1	0	0	
35	78	1	0	0	1	1	1	0	
40	88	1	0	0	1	1	0	0	

either during the initial lock-up time or if the VCO should develop an output frequency that would result in a signal being developed on an unassigned frequency (as in the 20-kHz gap between Channels 3 and 4), or in the event of loop failure.

How the receiver works

During the receive mode, the synthesizer generates the frequencies shown in Fig. 3. The 5-kHz reference input to the phase detector, which remains constant during the transmit and receive modes, is obtained by dividing 30.72 MHz by 3 and then by 2,048. The output of the divide-by-2 is 10.24 MHz—455 kHz below the first IF.

When in the receive mode, the VCO operates between 16.270 and 16.710—10.965-MHz below the channel carrier fed to the first receiver mixer. A part of the VCO output is mixed with the 15.360-MHz output of the divide-by-2 to develop a mixer output frequency f_m ranging from 910 kHz to 1.350 MHz. The programmable divide-by- n operates over a range of 182 to 270 as determined by the binary-coded number on the program lines.

Binary channel selection

When in the transmit mode, the TRANSMIT-RECEIVE switch grounds the Tx/Rx terminal on the IC. The binary number on the synthesizer program-lines equals the program-line number (n_{pl} , a digital number) plus 273. Channel 1 requires a divide number of 273 so the binary number on the program line will be zero. Table I shows the relationship between channel numbers, n_{pl} and the binary equivalent as applied to the program lines.

When receiving, the Tx/Rx terminal is taken high and the divide-by- n number equals the program-line number plus 182. Thus n in the programmable divider varies from 182 for Channel 1 to 270 for Channel 40.

Figure 4 shows how the binary signals for the program lines can be developed.

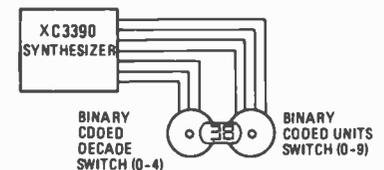


FIG. 4—BINARY SIGNALS for the program lines can be developed by either BCD switches.

There are two separate binary-coded rotary switches; one to develop a binary 0 through 4 for the decade portion of the channel number and the other to develop a binary 0 through 9 for the units portion.

In a future issue, we are going to take a look at the PLL frequency synthesizer in the General Electric model 3-5800A mobile CB transceiver.

R-E

Build With IC's

Action Football Game

This portable game uses a random-chance circuit and a play chart with realistic odds. The key to playing this game is to pick the right offensive and defensive play strategy

TO A TRUE FOOTBALL FAN, ANY MONTH having more than 27 days is a *great* time to enjoy football! Unfortunately, the real thing is available for just a few short months—barely enough to satisfy the pigskin addict's craving. Before you can say "Statue-of-Liberty play", the bowl games come and go, the goalposts are torn down and discussions with friends turn to rehashing events of the past season's games.

If you're tired of stale verbal "reruns" of past gridiron glories, invite your football buddies to join you for an evening in playing a fast-paced game of electronic football that pits your skill against that of your opponent, while bringing in the element of chance that so often means success or failure on the playing field!

The game is built around a unique random-chance "chaser" circuit using sixteen specially matched neon lamps and two integrated circuits. When in operation, a "count" is circulated through the chaser circuit so rapidly that all lamps appear to be flickering on and off at the same time. However, only one of the sixteen lamps is really on at any given millisecond. This means that if the count is stopped, just one lamp will remain glowing; the others will be extinguished. This is important because the lamps serve as indicators for reading the results of plays that you and your opponent select and run.

You, as the offense, for example, pick a play. There are sixteen possible outcomes for that play. Now, your opponent picks a defense and there are sixteen possible outcomes for his choice! The plays and results are all contained on a printed chart that fits under the 16-

**RUDOLF F. GRAF AND
GEORGE J. WHALEN**
CONTRIBUTING EDITORS

lamp line-up of the game. For any given play, the chart gives a statistically weighted ratio of risk-to-reward. That is, for plays that usually succeed, the chart gives better odds for success, although yardage gains will be smaller than in riskier plays. Conversely, for plays that are harder to pull off, yardage gains are greater and there's a chance of a touchdown, *but* the possibilities of failure are greater, too.

In devising the play chart, we consulted several football authorities (and we are particularly indebted to coach Curtis Blake of Colgate University for his expert assistance in setting up the play-chart odds). Of course, as in the real thing, there are possibilities of blocked kicks, interceptions and fumbles. That's why the element of skill in picking the *right* offensive or defensive play strategy is so strong in this game. While the circuitry may appear simple, the game is to be played by shrewd competitors who know the *right* plays to pick and who can stand the consequences. It's hot action for people who *really* know football!

How it works

The random-chance "chaser" circuit shown in Fig. 1 uses sixteen neon lamps arranged so that they form a series of cascaded *neon lamp astable multivibrators*. Each astable has two lamps, two resistors and two coupling capacitors.

Figure 2 shows one such astable multivibrator stage. When the supply voltage is applied to the circuit, the

voltage across lamps NE1 and NE2 begins to increase as the stray capacitance that is in parallel with the lamps charges up through R1 and R2. The *firing voltage* of one of the lamps will be reached first, since it is extremely unlikely that both will reach their trigger potentials at precisely the same time. Assuming that NE1 lights first, as that lamp goes into conduction, the voltage across it suddenly decreases to the *maintaining voltage*. Accordingly, a positive voltage pulse appears across R1, and this is coupled via capacitor C1 to the cathode of NE2. This pulse is approximately equal to the difference between the firing and maintaining voltages of lamp NE1. The pulse drives the cathode of NE2 positive, effectively reducing the potential difference across NE2 and preventing it from glowing. The voltage appearing across NE1, meanwhile, is approximately equal to its maintaining voltage so that it is glowing.

Shortly thereafter, however, capacitor C1 discharges permitting the voltage across NE2 to increase toward its firing potential. As this potential is reached, NE2 conducts and glows. When this happens, the voltage between its electrodes is reduced to the maintaining-voltage level. This causes a positive pulse to appear across R2, which is then coupled back to the junction of the NE1 cathode and R1. The pulse amplitude represents the difference between NE2's firing and maintaining voltages. However, since NE1 is only at its maintaining voltage, the sudden positive pulse at its cathode sharply decreases the potential difference between the lamp's electrodes, causing NE1 to extinguish. At this point, NE1 switches to the

PARTS LIST

All resistors are $\frac{1}{4}$ watt, 10%, unless noted.

R1—330,000 ohms

R2-R17—1.5 megohms, 5%

R18—1000 ohms

C1—10 μ F, 150-volt electrolytic

C2-C17—.05 μ F, 50-volt radial-lead disc ceramic

D1—silicon rectifier, 200 PIV, 1 amp (International Rectifier 10D6, RCA SK3017A, or equal.)

NE1-NE16—miniature neon lamp (G-E 5AB-B, or equal.)

IC1, IC2—16-diode array (Fairchild FSA2510)

S1, S2—single-pole normally closed pushbutton switches

Misc.—PC board, playchart, game board, playing pieces, vinyl case.

The following parts are available from:

National Mentor Corp.

Box 53

Wykagyl Station

New Rochelle, NY 10804

A basic parts kit consisting of the neon lamps, IC's, woodgrain case and playchart for \$29.00 postpaid. Order No. FBL-1.

A complete parts kit that includes everything in the FBL-1 kit, plus all resistors, capacitors, diode, PC board for the main game circuit, pushbutton switches, line cord, etc., for \$39.00 postpaid. Order No. FBL-2.

NE1-NE16—16 neon lamps for \$10.00

IC1, IC2—two 16-diode arrays for \$7.50

PC board for main game circuit, \$5.50

Walnut woodgrain predrilled case for \$10.00

Playchart, game board and playing pieces on a pressure sensitive adhesive-backed stock for \$2.75.

high-resistance state and stops glowing, while NE2 is now at its maintaining voltage and is glowing. Note also that capacitor C2 has coupled the output pulse appearing across R2 to the next lamp in the chain. This means that this lamp will now go through the cycle of being inhibited from firing, then firing and extinguishing NE2 in the same sequence and manner as that just

described.

As shown in Fig. 1, the identical stages of the circuit are connected as a "ring", with the output capacitor of the last stage feeding back into the first stage. This means that the "count" circulates rapidly through the ring causing the lamps to flicker in sequence, but giving the appearance that they're all flickering at the same rate.


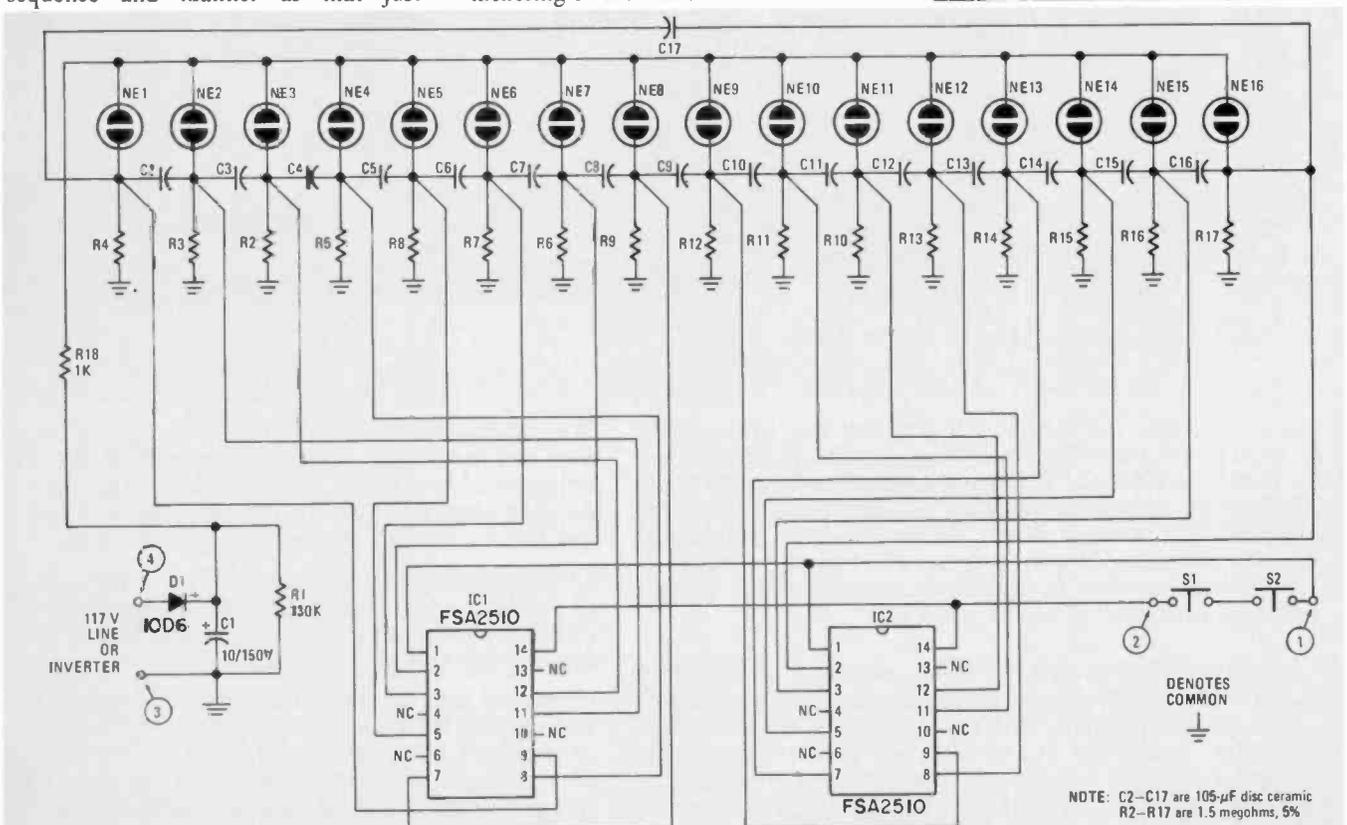
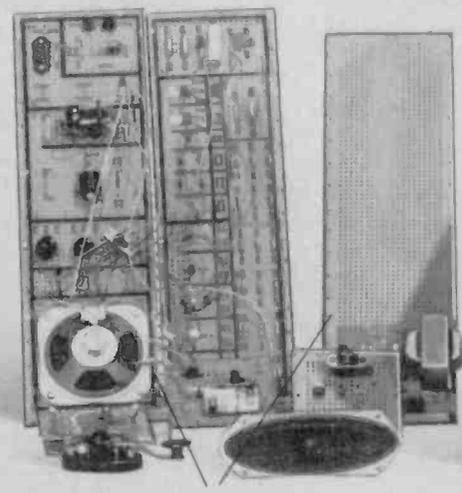
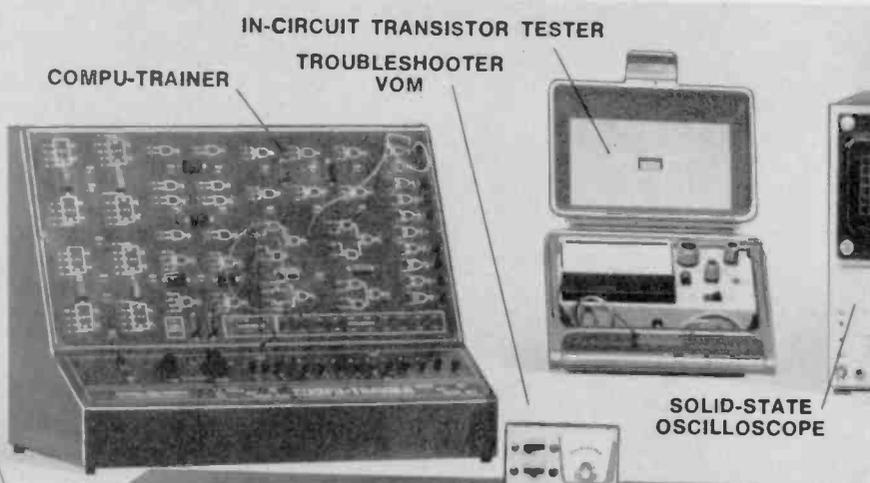


FIG. 1—GAME CIRCUIT uses neon lamps in astable multivibrator configuration. Switches S1 and S2 should have been shown as normally closed.

The better the training the better you'll

Send for
FREE
illustrated
career
guide

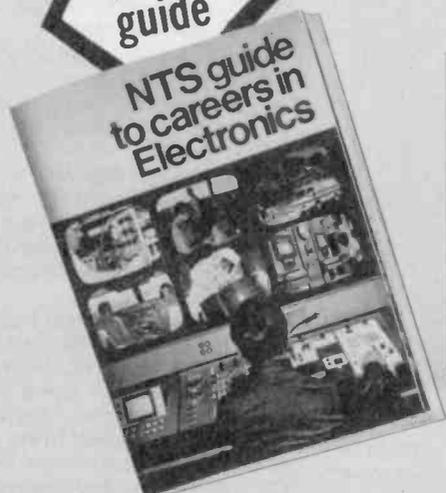

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath GR-2001 computerized color TV (25" diagonal)** with varactor diode tuning and digital read-out channel selection; (optional programming capability and digital clock avail.).

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.


This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

and the equipment be equipped.

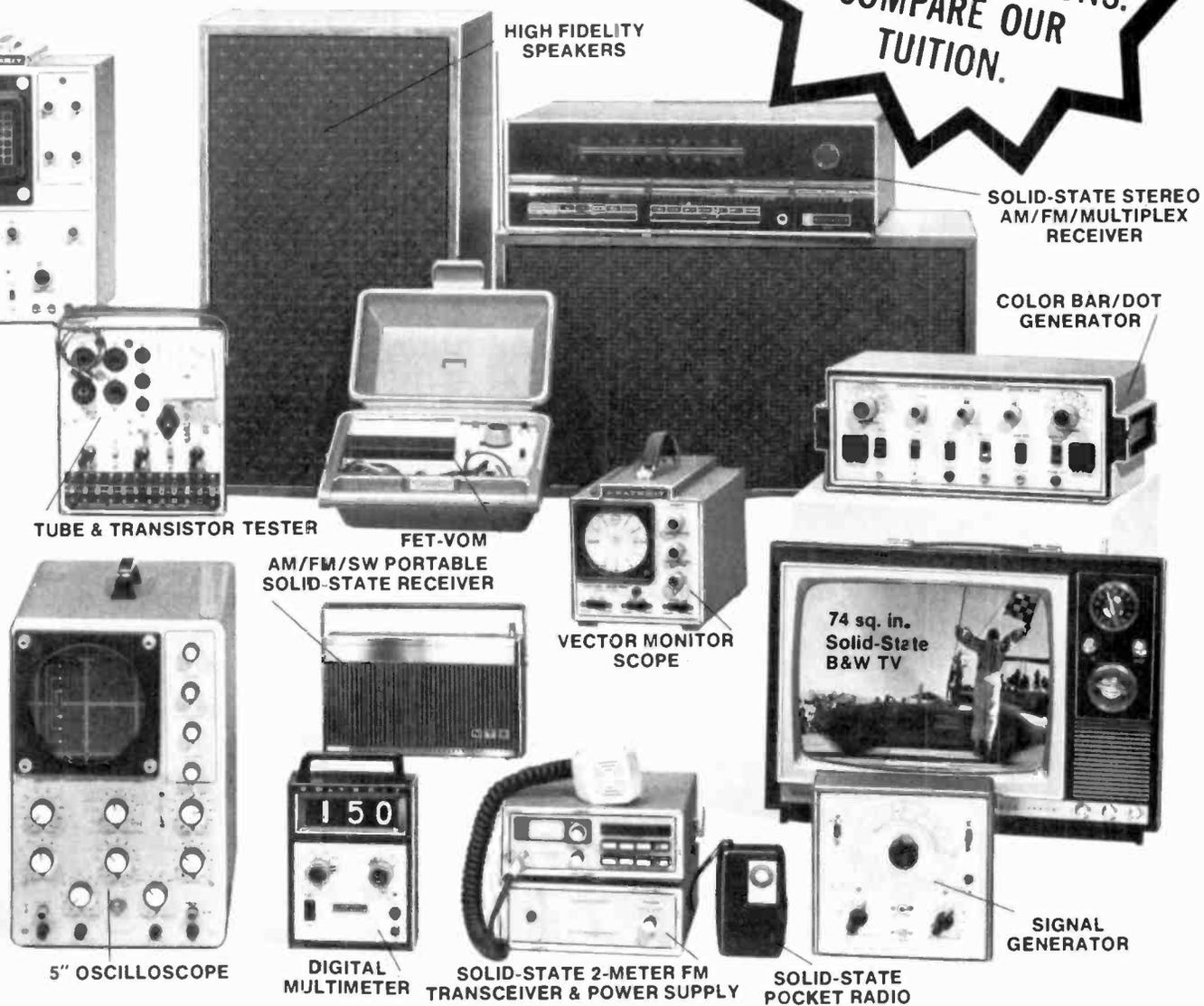**COMPARE OUR
KITS AND LESSONS.
COMPARE OUR
TUITION.**



HIGH FIDELITY SPEAKERS

SOLID-STATE STEREO AM/FM/MULTIPLEX RECEIVER

COLOR BAR/DOT GENERATOR

TUBE & TRANSISTOR TESTER

FET-VOM AM/FM/SW PORTABLE SOLID-STATE RECEIVER

VECTOR MONITOR SCOPE

5" OSCILLOSCOPE

DIGITAL MULTIMETER

SOLID-STATE 2-METER FM TRANSCEIVER & POWER SUPPLY

SOLID-STATE POCKET RADIO

SIGNAL GENERATOR

tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL
APPROVED FOR VETERAN TRAINING
 Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS
 TECHNICAL-TRADE TRAINING SINCE 1905
 Resident and Home-Study Schools
 4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS Dept. 206-037
 4000 South Figueroa St., Los Angeles, Calif. 90037
 Please send FREE Color Catalog and Sample Lesson.
 NO OBLIGATION. NO SALESMAN WILL CALL.

Color TV Servicing
 B & W TV and Radio Servicing
 Electronic Communications
 FCC License Course

Electronics Technology
 Computer Electronics
 Basic Electronics
 Audio Electronics Servicing

NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service _____

Check if interested In G.I. Bill Information.
 Check if interested ONLY in classroom training in Los Angeles.

This is only half the story, for now we must be able to stop the "count" at a random point so that only one lamp remains glowing while all the others are off. This is possible with the diode gating provided in the integrated circuits, IC1 and IC2.

There are a total of 16 series-connected diode-pairs with IC1 and IC2. Two diode-pairs are connected, as

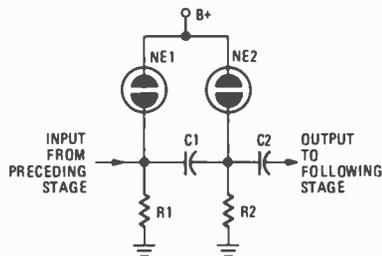


FIG. 2—BASIC ASTABLE MULTIVIBRATOR stage built around neon lamps.

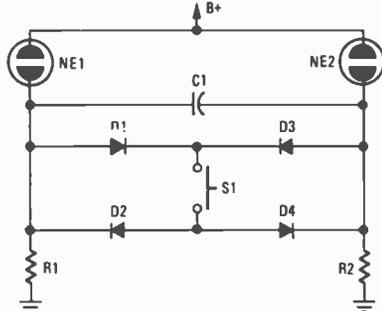


FIG. 3—DIODES are used to stop multivibrator operation.

shown in Fig. 3, to each astable stage of the chaser. The anode-cathode junction of D1 and D2 is connected to the junction of the NE1 cathode, R1 and C1, while the anode-cathode junction of D3 and D4 connects to the junction of C1, R2 and the cathode of NE2. The common anodes and cathodes of the diodes respectively connect to the terminals of switch S1. When switch S1 is open, no current flows through the diodes because the anodes are connected only to other anodes, and cathodes are connected only to other cathodes. During this time, the chaser is in the free-running "chase" mode described earlier.

However, if switch S1 is closed, all capacitors in the circuit are suddenly shorted because diodes D1-D4 and D2-D3 respectively and immediately appear in series across C1 (as well as across all the other capacitors in the circuit). In effect, all of the stages are suddenly inhibited so that only the lamp that is on at the time switch S1 is closed remains on. The count cannot be transferred until switch S1 is opened.

Referring back to Fig. 1, IC1 and IC2 provide a total of 32 diodes to interconnect the 16 lamp-stages. Switch S1 is actually an AND function formed by the series connection of two normally-closed pushbutton switches, S1 and S2.

This means that to get the chaser to run, either you or your opponent must press a button. However, to get the chaser to stop, both you and your opponent must release. This "added extra" contributes to the randomness of the circuit.

The power supply of the game uses a conventional halfwave rectifier, D1 and filter capacitor C1. Resistor R18 serves only as a protective current-limiter to buffer the supply against inadvertent short-circuiting. Resistor R1 is a bleeder resistor for the filter capacitor.

Portable operation

There's no reason to stay indoors to play football, if the game is equipped with the accessory battery/inverter supply shown in Fig. 4. Using but a single

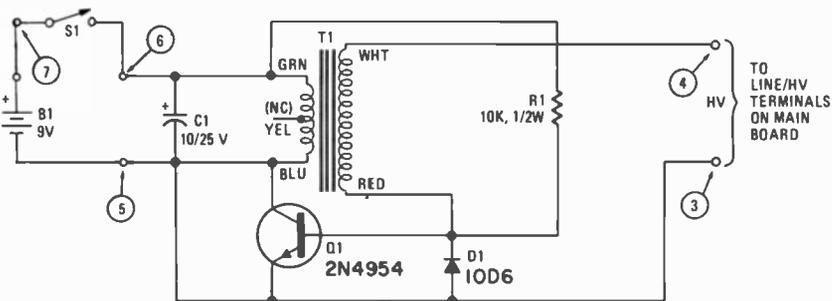


FIG. 4—OPTIONAL BATTERY INVERTER allows portable operation.

transistor, a 9-volt alkaline battery, a transformer and a few other parts, this supply delivers a high-frequency non-sinusoidal voltage of approximately 100 volts RMS. This input is applied to rectifier diode D1 and filter capacitor C1, providing adequate DC for several hours of operation.

The inverter circuit operates as follows: When toggle switch S1 is closed, current is supplied to the emitter-base junction of Q1, through R1. Transistor Q1 conducts a current pulse through its collector, storing energy in T1 and also inducing a voltage in the output winding that momentarily turns off Q1. The collapse of the magnetic field in T1 induces a voltage pulse across the output winding that is stepped-up by the turns ratio of the transformer. Diode D1 prevents the base of Q1 from going excessively negative, and also serves as the return path for the current to flow back to the transformer output winding. When the output pulse has passed, Q1 again conducts because of the bias supplied through R1, and

NOTE

This game can be powered directly from the AC-line only if it is safely enclosed within a completely insulated housing, such as the wood-grain vinyl case shown in the accompanying photos. If you do not use an insulated case, a 1:1 power-line isolation transformer should be added to minimize shock hazard.

another cycle commences.


Construction

The Football Game circuit is contained on a 4 × 8-inch printed-circuit board that speeds and simplifies assembly. (See Fig. 5.) Importantly, the board also holds the sixteen indicator lamps in the correct physical alignment so that they will slip through holes in the case and be accurately aligned with the columns of the play chart that will later be affixed to the top of the case. Figure 6 shows the parts layout on the printed-circuit board. The 16 coupling/timing capacitors (C2 through C17), 16 resistors (R2 through R17), and the two IC diode arrays are mounted on the non-foil side of the board, as are the power-supply

PARTS LIST OPTIONAL BATTERY INVERTER

- R1—10,000 ohm, 1/2 watt, 5%
- C1—10μF, 25-volt electrolytic
- D1—silicon rectifier, 200 PIV, 1 amp (International Rectifier 10D6, RCA SK3017A, or equal.)
- Q1—2N4954 transistor
- S1—SPST toggle switch
- T1—miniature transformer; 1000-ohm CT primary, 200,000-ohm secondary (Radio-Shack No. 273-1376 or equal.)
- B1—9-volt alkaline battery
- Misc.—PC board, battery holder, battery terminal clips, etc.

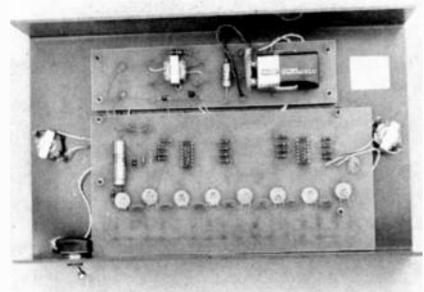components (diode D1, filter capacitor C1 and resistors R1 and R18). The neon lamps are soldered to the foil side of the board, thus making it possible to install the board with the foil side facing the case. (This prevents accidental contact with components and conductors that operate at line voltage.) The two inte-



MAIN CIRCUIT BOARD mounts next to battery inverter board.

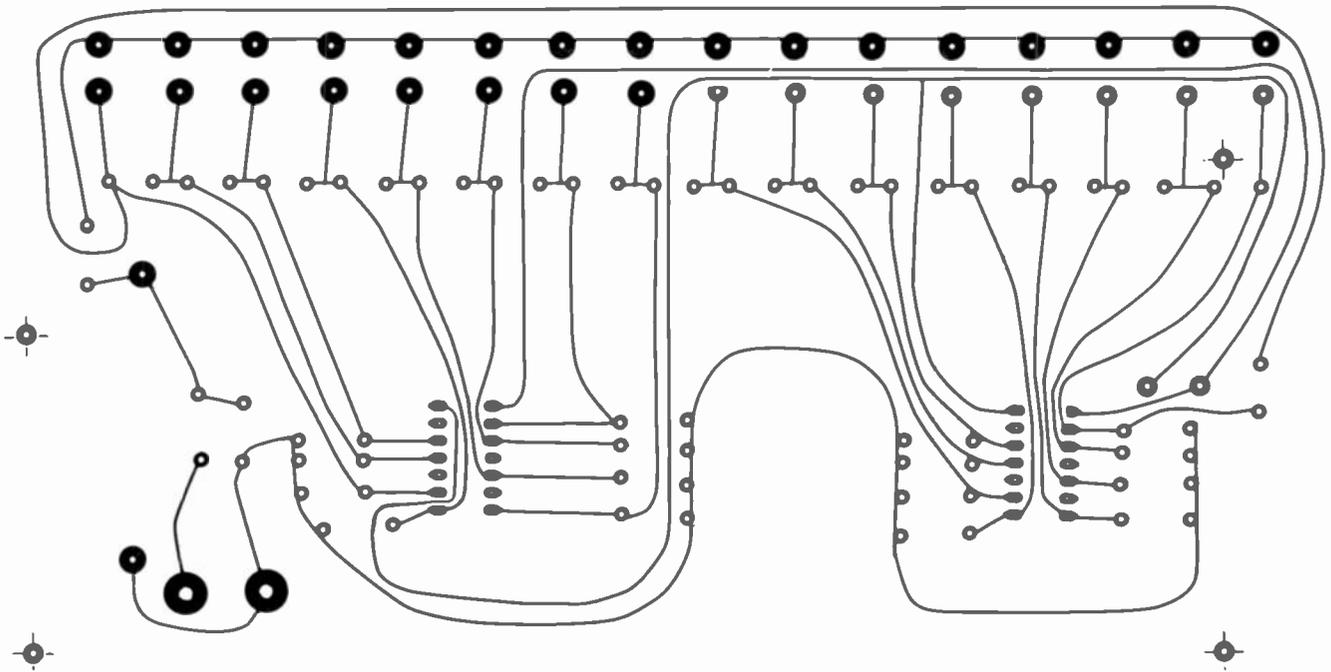


FIG. 5—FOIL PATTERN of game board shown full-size.

grated circuits (IC1 and IC2) are installed directly on the board, without sockets (although sockets may be used, if you prefer). A low-wattage soldering iron should be used to solder the components to the board.

To install the lamps, slide their lead wires through the board from the foil side, pressing gently but firmly until the point of maximum downward travel is reached. Board holes are spaced so that the lamps will be lead-supported about 3/16-inch above the foil side of the board. When the board is installed, only the topmost portion of each lamp will jut through the case holes. Switches S1 and S2 are installed on the case at either end and connected in series to the points 1 and 2 as shown in Fig. 6. The 117 VAC line-cord enters the case through a hole in the rear and solders directly to the board at points 2 and 3. The line is thus completely insulated from any components you touch. No on-off switch is included for AC-line operation, and so, the highest degree of isolation from the line is maintained. The unit is turned on by plugging it into an

AC outlet and shut off by removing the plug. If you choose the inverter, its leads connect to the points 2 and 3 on the board instead of the line cord. Switch for the inverter then mounts in the case hole for the line cord.

The assembled board is supported in the case on four 1/2-inch screws fitted with 1/4-inch insulated spacers. Flat-head screws are used, and holes in the case are counter-sunk so that no hardware protrudes above the case top surface. When the board has been mounted in


the case and wiring has been completed, the play chart is installed on the case top. Next, prepare the playing field and game pieces. You can either cut these from a sheet of paper and use them as they are, or you can glue the sheet to a stiffening cardboard and cut the pieces out afterward. Be sure to cut out the center of the play selector and ball with a sharp knife or razor blade. The play chart, playing field and play pieces are shown in Fig. 7. A full-size pre-printed play chart, playing field and pieces with a self-adhesive backing is available (see parts list).

If portable operation is desired, assemble the optional battery inverter circuit. The foil pattern for this board is shown in Fig. 8, and the component placement diagram is shown in Fig. 9. The assembly procedure for this board is straightforward.

Playing the game

You start by flipping a coin to see who kicks off. The player winning the toss will receive. His opponent places the ball marker on his 40-yard line. The play selector is moved to the row labelled KICKOFF on the chart and the kicker's button is pressed. The light remaining on when the kicker releases his button indicates the kick's distance. If it went, say 48 yards, the ball marker is placed on the receiving team's 12-yard line. The play selector is now placed on KICK RET and the process is repeated to see how many yards the receiver, by pressing his button, makes on the runback. (If the kick goes into the end zone, the receiver takes the ball on his 20-yard line with no runback).

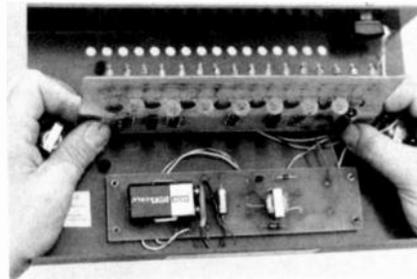At this point, the offensive player has a first down with four tries to go 10-yards and make another first down. He



NEON LAMPS mount through holes drilled in front panel.


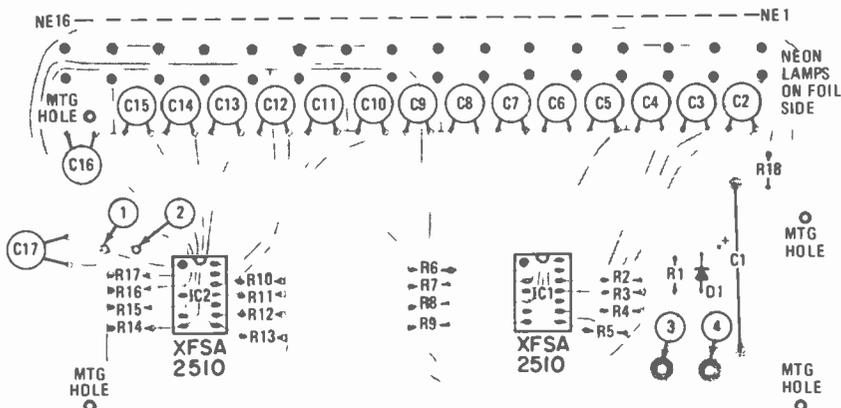


FIG. 6—COMPONENT PLACEMENT of main PC board.

Analog Voltmeters

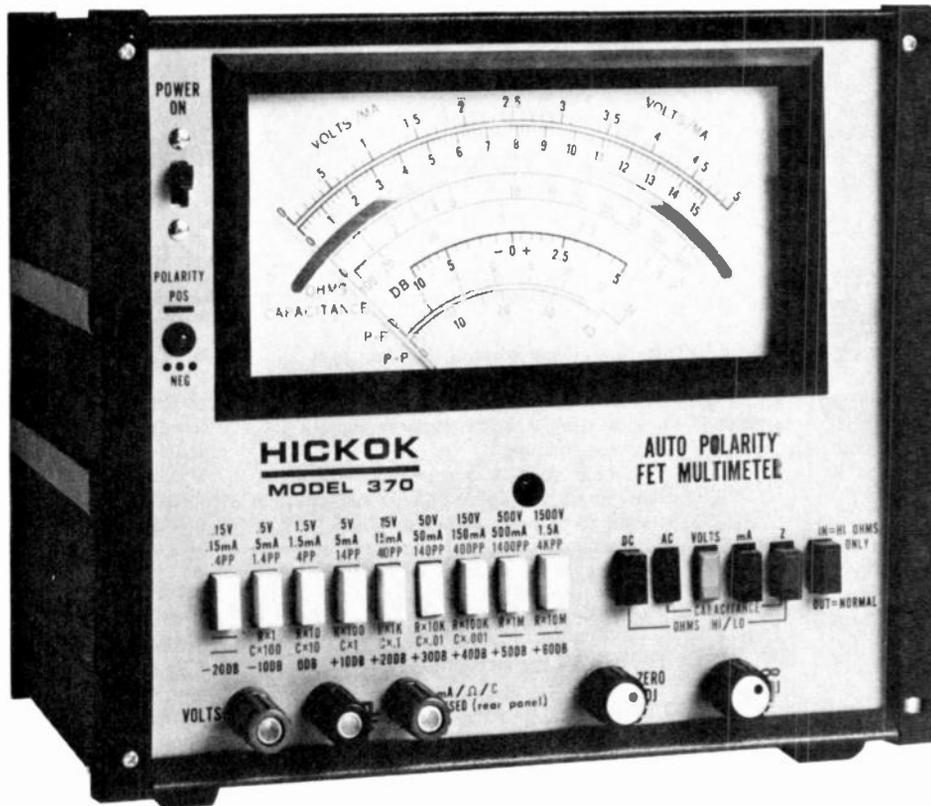

Part III. The analog voltmeter is alive and well. Here's a rundown of the different types currently available—their features, specifications and applications

CHARLES GILMORE*

THE FIRST TWO PARTS OF THIS ARTICLE discussed the different types of analog voltmeters and their features and specifications.

This concluding part of the article completes the discussion on specifications and introduces various applications.

Ohmmeter ranges

The TVM ohmmeter ranges are identical to those of the VTVM. They have a 10-ohm center scale and have ranges from $R \times 1$ ohms to $R \times 1$ Meg. The TVM adds additional specifications to the ohmmeter. First, the maximum open circuit voltage of the ohmmeter is specified. This is especially true if the TVM has selection of HI and LOW ohms. A maximum open circuit voltage is then given for both high and low ohms operation. The ohmmeter specifications may also give the maximum source current. This specification is useful if there are critical components in the circuits that might be dam-

*Manager Design Engineering, Heath Co., Benton Harbor, MI.

aged by excessive currents. The common terminal of the TVM is usually negative, but if the manufacturer does not indicate this in the specifications or on the terminals of the meter itself, it is a good idea to check it out after purchase and note the information where it can easily be seen.

Input impedance

In the DC function the input impedance of the TVM is most commonly 10 megohms. A few still have an input impedance of 11 megohms.

The AC input impedance of the TVM is composed of the same DC resistance used on the DC input with a shunt capacitance specified. The shunt capacitance ranges from a low of 30 to 40 pF on the very best of TVM's to 100 pF on the more common units. It should be noted this input capacitance does not disappear when the DC mode is used. When measuring the DC component of a signal, this capacitance may cause some disruption to the AC characteristics of the circuit. Unfortunately, few if any manufacturers specify

the input capacitance of the DC voltmeter.

The ammeter

Specifications for both the AC and DC ammeter are very much alike. Not all TVM's have the ammeter function, and the lack of ammeter specifications indicates a lack of the function. Ammeter specifications indicate the insertion loss when the meter is placed in the circuit. This may be given in two ways. First, the manufacturer may note that the ammeter has a certain maximum voltage drop. Second, the manufacturer may indicate the insertion resistance and give the information necessary to calculate the voltage drop. Some manufacturers give both. The insertion resistance may be greater than expected in the high-ampere ranges, as the lead and connector resistances become appreciable.

Accuracy of the ammeter closely follows the accuracy of the lowest voltage scales of the meter. An additional error figure is often given for the lowest value of shunt resistance (highest current range),

as high-accuracy shunts at low resistance are very difficult to make.

Frequency response of the AC ammeter closely follows the frequency response of the lowest range of the AC voltmeter. There may, however, be an additional derating for the high values of shunt resistance (lowest current ranges), as the distributed capacitance and the high value of the shunt resistance cause additional loss of high frequencies.

Ammeter ranges for TVM's run from $10\mu\text{A}$ to 1A full scale. A few TVM's offer wider ranges than this; however, they are not common. Up to 10-ampere ranges are offered on some TVOM's designed with *appliance service* in mind.

Probes

Normally the probes provided with the TVM are not as exotic as those supplied with the VTVM. The most common one is the simple test probe with a test lead terminated in a banana plug, or sometimes in a tip plug. Occasionally some TVM's offer the VTVM probe. An 11-megohm input impedance is often a clue to a special probe.

AC rejection

A few TVM manufacturers specify the AC rejection of the DC ranges. This specification indicates the number of full scale overloads of a certain frequency AC (usually 60 Hz) which may be applied without affecting the DC reading.

Protection

As the TVM, especially TVOM's, are often used in situations where accidental contact with high voltages can occur (most commonly either the 120 or the 240 VAC power line), protection of the DC voltmeter and other functions is important. Protection is accomplished and specified in a number of ways. The manufacturer may simply state that the meter is protected from momentary overloads of 220 volts AC or DC on any range. This protection takes the form of back-to-back diodes at appropriate places in the circuit.

Additional instrument protection is given by a set of back-to-back diodes across the meter movement itself. These diodes prevent the movement from being destroyed by a continuous overload. Ohmmeters are protected by diodes, and a fuse may provide additional protection. Ammeter shunts are often fuse protected. These fuses may be difficult to obtain, and acquiring a few spares is wise.

Some of the TVM's, especially the TVOM's, have a ruggedized taut-band meter movement. Such an instrument will come through a fall onto a hard surface undamaged or at least with minor repairable damage, while conventional meters would be seriously damaged.

Scales

A typical TVM scale is shown in Fig. 12. Note the BATTERY TEST position. The dB scale is calibrated in dBm. (Zero dBm is one milliwatt on 600 ohms, or 0.774 volts). A small center-zero scale is given for null measurements.

Controls

The number of controls and the selection of functions are highly dependent on

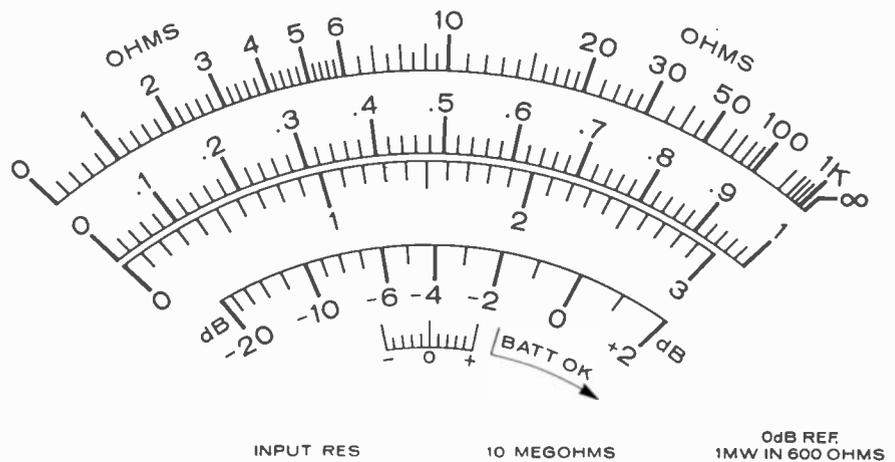


FIG. 12—THIS TYPICAL TVM SCALE is from the Heathkit IM-104 TVOM. Besides ohms and volts, it has a short zero-center scale and a battery check position.

the functions offered by the particular TVM. Function selection is by rotary switch and/or push buttons. Range selection on the TVM frequency includes a battery test position.

A zero control is common to TVM's. The range of this control is sufficient to permit zero centering the meter as well as left-hand zeroing. An ohmmeter adjustment may not be included on a meter that utilizes internal constant current generators in its ohmmeter function.

The meter movement

As noted in the section on meter protection, some TVM's employ the taut-band meter movement. Those not indicating this type of meter movement use the regular moving-coil or D'Arsonval meter. Most manufacturers specify the size of the meter. A four- to five-inch meter is common and adequate for most laboratory and field service applications. Meter displays smaller than that become difficult to read, especially when there are a number of scales clustered on the face. Meters larger than five inches are useful in some shop or laboratory applications. A mirror-backed meter aids in resolution, but rarely does the TVM offer accuracy requiring a mirror-backed meter.

Amplifier outputs

Good laboratory TVM's have two different forms of outputs. There may be a DC voltage directly proportional to the meter movement. Such an output may be 100 mV, or 1 volt for a full-scale meter deflection. This type of output is handy for driving a strip-chart recorder or perhaps some form of limit detecting circuit. The second form of output is a signal taken from the meter amplifier prior to being applied to the rectifier. Such an output may be used to drive a set of headphones, for example, to listen to a circuit as well as to measure it. Such outputs usually have a few kilohms source impedance.

Floating inputs

A floating input is one not connected to the earth side of the power line. Generally this indicates the impedance to ground (usually a very high resistance with a small shunt capacitance) from both the high and the low (common) terminals of the voltmeter input is the same. Such a

feature allows the voltmeter to be operated without one side of the voltmeter attached to ground. This is particularly handy for measuring voltage drops across circuit elements which have both terminals above ground. A maximum limit is given to this floating capability when the instrument is line operated. Battery operation automatically provides floating operation.

Accessory probes

Many manufacturers offer high-voltage probes to extend the useful DC voltage range of the meter, and RF probes to extend the useful frequency range of the AC voltmeter. These probes are often not interchangeable from one manufacturer to another. Close attention to the specifications of the voltmeter with which they are intended to be used is wise.

Battery operation

As noted in the section on floating inputs, battery operation is a useful feature when the instrument is operated with both inputs above ground. This feature is also used to eliminate unwanted signals present on a common ground system. This is desirable when the common input to the TVM is common to earth ground. Battery operation is also essential to field operation and is therefore a part of every TVOM. Batteries do tend to spoil after a time and can damage the instrument when they do. This feature also adds to the price.

Special current measurement

As noted in the theoretical discussion on ammeters, a few special types are available. These special ammeters are generally dictated by some special application. However, the ammeter in the Weston model 670, which does not require opening the circuit to make the current measurement, is especially useful for service work. Ammeters with special high current ranges are available for special applications. Generally such special scales come at the expense of some other feature or ranges.

Automatic polarity indication

Some of the more sophisticated TVM's have polarity indicators instead of a DC polarity reversal switch. Polarity reversal is indicated by the change of the polarity indicators from + to - or vice versa. Polarity indicators are disabled when AC measurements are being made.

Ohmmeter features

As noted before, many TVM ohmmeters offer both high and low resistance measurements. In addition to the high and low measurements, some TVM's offer an ohmmeter polarity reversal switch. The polarity reversal switch permits a quick check when forward biasing a semiconductor junction in a circuit, or when a semiconductor is being tested for shorts or opens.

The AC voltmeter

The ranges of the AC voltmeter cover a wider range than those of either the VTVM or the TVM. Ranges extend from the 0.1 to 10 mV area to the 300 to 1,000 volt area. The ranges of the AC voltmeter are also calibrated in decibels. Zero dB is 0.774 volt for zero dBm.

AC voltmeter accuracy is specified in one of two ways. First, the voltmeter may be given an accuracy specification at a single frequency and a frequency response specification to cover the operating band of frequencies for the instrument. The total operating range of the voltmeter may be subdivided into a number of ranges with a different response for each range. Second, the voltmeter may be given an accuracy specification for the entire range of operation. Usually this form of specification is reserved for the higher-priced meters. Accuracy may be specified as a percentage of reading plus a percentage of full scale for the AC voltmeter. Again the accuracy may be broken down by the frequency ranges of the meter.

The frequency response of the AC voltmeter is from the 10 to 20 Hz region to

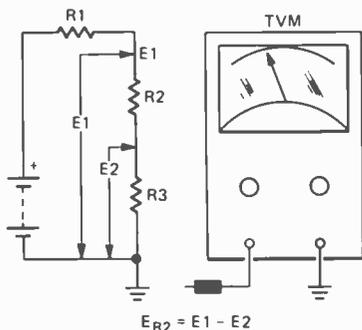


FIG. 13—IF THE METER IS GROUNDLED, the voltage across "floating" resistor R2 cannot be measured directly, but voltage from ground at the two ends can be measured and the drop found by a simple subtraction.

the 1 to 4 MHz area. The exact extent of response may vary with the voltage range being discussed. The frequency response of the AC voltmeter is better than that either the TVM or the VTVM.

A 10-megohm input impedance shunted by 10 to 40 pF is common for the AC voltmeter. A few AC meters offer a lower input impedance. The input capacitance changes with the voltage ranges selected on some meters. This feature can cause a change in the circuit impedance when the meter is switched through its ranges, due to a change in capacitive loading.

The response time of the AC voltmeter indicates the time for the meter to settle within its rated accuracy. This specification indicates the time associated with the rectifier circuit. The response time indicates that the voltmeter may, or may not,

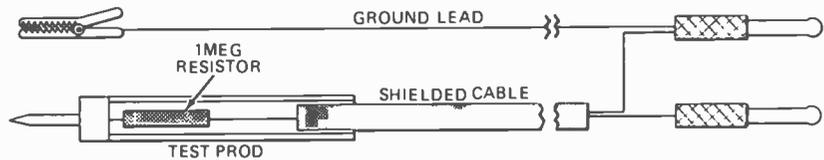


FIG. 14—AN ISOLATING TVM PROBE places a low-capacitance resistor in series, reducing the load on the circuit. Since, unlike the VTVM, the TVM is not calibrated to allow for a resistor in the probe, voltage readings will be low by 9 percent.

be used as a VU meter, which requires a 0.3 second maximum response time.

AC voltmeters frequently feature amplifier outputs; the meter may also be used as a high-gain test amplifier. The output impedance of these amplifiers is either 50 or 600 ohms. Other features include an output proportional to the meter deflection (either 100 mV or 1V), filtering that may be switched in to eliminate high-frequency response, battery operation for portability and elimination of ground currents, linear dB scales, mirror-backed meters for ease in making high resolution measurements, and a true RMS converter. Generally, such options are available only on higher-priced units, and some, such as the true RMS converter, are expensive.

Regular and special applications

The electronic analog multimeter is used where it is necessary to measure a voltage, current, or resistance to an accuracy of two percent or less. This, in fact, is most of the time, especially for the home experimenter or the consumer products service shop. Some industrial service and laboratory situations require greater accuracy. The digital multimeter should be considered for those applications.

As noted previously, the analog meter is definitely the best display device when the desired information is trend. Numerous situations exist in the alignment of an FM receiver/transmitter, for example, where the procedure calls for peaking the output of a stage. An analog meter proves its worth here and should always be carried for this purpose if for no other. Other examples of trend measurement are found in the same FM receiver/transmitter alignment procedure. For example, many oscillator circuits and some output stages require their supply current to the stage be reduced to a minimum, or "dipped." This too is a measurement of trend.

The DC output of the receiver discriminator is zero when the discriminator transformer is tuned to the center frequency of the IF strip. The zero offset capability of the TVM or VTVM is especially handy for this measurement, as the discriminator output voltage is of one polarity for frequencies above the IF center-frequency and of opposite polarity for frequencies below it. An analog voltmeter is needed to set the output of the discriminator at zero. This same "nulling" procedure is used in a number of bridge circuits, where an analog voltmeter with zero offset is also called for.

A common problem is the need to make a floating measurement when the meter's common terminal is connected to earth ground. A solution to this requires making two measurements, one at each end of the circuit, and subtracting the readings. When this technique is used, the

difference between two large numbers is a small number with the same error as the large numbers. For example, the voltage drop across R2 of Fig. 13 is needed. E₁ is measured as 90 volts and E₂ is measured as 85 volts. The voltage drop across R2 is determined to be 5 volts. Examining the errors involved in the measurements, the 150-volt range of a 3% VTVM gave each of the high voltage measurements a ± 4.5 volt error. This error shifts the floating voltage of R2 by ± 4.5 volts. The accuracy of the difference between E₁ and E₂ depends on the linearity of the meter. Linearity is not often specified, but 1% of full scale is a good figure to use. The 5-volt drop across R2 can therefore vary by as much as ± 1.5 volts.

Many alignment and test procedures call for a specific type of voltmeter, frequently the VTVM. The 10-megohm TVM is a good substitute if the circuit is known not to need the isolation of the 1-megohm probe tip resistor of the VTVM. It is wise not to convert such measurements to digital multimeter measurements. Often the added resolution of the digital meter causes needless confusion. If a 10-megohm TVM is the only instrument available, a special probe can be made. This probe with the additional 1-megohm resistance at its tip reduces all measurements by 9%. However, the measurements are still valid with a *known* 9% error especially if these test points will not tolerate the capacitive loading of a 10-megohm 100-pF TVM. Fig. 14 depicts the construction of such a probe.

The in-circuit current meter is useful for troubleshooting. For example, presume one of ten integrated circuits soldered to a printed circuit board is shorted internally, enough to make the power supply enter current foldback. The normal method of servicing is to replace or disconnect each integrated circuit from the power rail until the power supply recovers. With the in-circuit current measurement, the current to each integrated circuit is measured. The shorted device is identified as the one drawing a large current. The defective component is replaced, saving considerable work. Needless to say, this technique is applicable to many other similar situations in both discrete and integrated designs.

Sources of error

The analog voltmeter, like any other instrument, is capable of introducing errors in the circuit being analyzed. These are fundamentally of two types, errors introduced by the operator and those caused by some characteristic of the instrument.

Errors in reading are the most common operator errors. Simple errors are often made from a misreading of scale

continued on page 104

If you can't go to college for your career in electronics —read this!

CREI brings college-level training to you with eight educational advantages, including special arrangements for engineering degrees

The best way to qualify for top positions and top pay in electronics is obviously with college-level training. The person with such training usually steps more quickly into an engineering level position and is paid considerably more than the average technician who has been on the job several years.

A regular college engineering program, however, means several years of full-time resident training—and it often means waiting several years before you *can even start your career*. This, of course, is difficult if you must work full time to support yourself and your family.

If your career in electronics is limited without college-level training, take a look at the advantages a CREI home study program can offer you.

1. Convenient Training

CREI brings the college to you. Through the convenience of home study, you receive exactly the same level of training you will find in any college or university offering programs in electronic engineering technology. With CREI, however, you can “go to college” whenever you have spare time at home or on the job.

2. Specialized Programs

With CREI, you enjoy the advantage of *specialized* training. That is, your program will include only those courses directly applicable to your career in electronics. We omit such courses as English, social studies and other subjects, which are usually required in resident schools. Therefore, with CREI, you move ahead faster to the more interesting and useful part of your training.

3. Practical Engineering

CREI programs give you a *practical engineering* knowledge of electronics. That is, each part of your training is planned for your “use on the job.” By using your training, you reinforce the learning process. And by demonstrating your increased knowledge to your employer, you may qualify for faster career advancement.

4. Engineering Degrees

CREI offers you a number of special arrangements for earning engineering degrees at recognized colleges and universities. You can earn college credit while you are taking your CREI program or apply later, whatever is best for your career plans.

Career Training at Home

5. Unique Laboratory

Only CREI offers you the unique Electronic Design Laboratory Program. This complete college laboratory makes learning advanced electronics easier and it gives you extensive practical experience in many areas of engineering, including design of electronic circuits. No other school offers this unique program. It is a better "Lab" than we have found in many colleges. And the professional equipment included in the program becomes yours to keep and use throughout your professional career.

6. Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

7. Prepared by Experts

Experts in industry and technical organizations of government develop CREI programs. Each part of your training is developed by a recognized expert in that area of electronics. That means you get the most up-to-date and practical instruction for your career.

8. Industry Recognition

That CREI training is recognized by industry and government is evident from the fact CREI provides training to advanced technical personnel in over 1,700 technical organizations. Many subsidize the training of their employees with CREI. If there is any question about the advantages of CREI training for you, ask your employer or any engineer to evaluate the outline of a CREI program for you.

Other Advantages

Of course, there are many other advantages to CREI training. For example, throughout your training, CREI's staff gives you personal instruction for each step of your program. And in many industrial areas, both in the U. S. and abroad, CREI Field Service Representatives provide a number of important personal services for your training and your career.

FREE Book

There isn't room here to give you all of the facts about career opportunities in advanced electronics and how CREI prepares you for them. So we invite you to send for our free catalog (if you are qualified). This fully illustrated, 80 page catalog describes in detail the programs, equipment and services of CREI.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.



Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.



BUILD

Tone Probe for Testing Digital IC's

This easy-to-build test instrument costs less than \$16 and emits an audible tone to denote low and high logic-levels

LARRY FORT

HAVE YOU EVER COMPLETED A DIGITAL circuit project only to find that something is wrong? It's no problem if you have an oscilloscope, particularly one with a triggered sweep, but if your scope isn't too good, troubleshooting digital circuits will be difficult.

What if all you have is a voltmeter? They're fine for low-speed circuits where a signal stays at a given level long enough for the meter to react and settle at a reading, but fast pulses and high repetition rates make meters almost useless.

A logic probe then, is almost indispensable if you're building projects that use digital circuits, because you must be able to tell whether inputs and outputs are high, low or floating. Many probes are available today, but most of them use some kind of visual indication to tell the signal level. If your hands are steady and you have your wits about you, it's possible to look away from what you're probing to determine the signal level, then immediately return your attention to the probe and start again at the next lead. If not, you're in trouble unless you have a *tone probe*.

The tone probe described here uses sound to tell the status of the signal being probed. That means you can probe difficult points rapidly and know each signal level without any distractions. It has the added advantage of detecting intermittent problems just by the sound "pattern" changes that occur as you manipulate other components of the circuit.

There are really only three voltage levels of interest. A voltage level of less than 0.8 is considered *low* for almost all DTL and TTL families of digital IC's. Voltages greater than 2 volts are considered *high*, and any voltages between 0.8 volts and 2 volts are not guaranteed to be either high or low and can cause noise problems. The tone probe has an input circuit that senses the condition of the signal and produces either a low-pitched tone for low-level signals, or a high-pitched tone for high-level signals.

Any signal between these two produces no tone.

An important consideration for all logic probes is that they must have a high input impedance so they will not load down the circuit under test. A low input-impedance can cause a good circuit to malfunction.

The tone probe is powered by the circuit-under-test rather than being self-powered, for two reasons: The supply voltage affects the switching points to some extent; and it is necessary to have a ground lead to all probes so the inconvenience of clipping one or more wires for B+ is insignificant.

How it works

Figure 1 shows the schematic diagram. Resistors R1 and R2 form a voltage divider that supplies about 1.5 V

to resistors R3 and R4. Resistor R3 supplies some base drive to Q1, causing it to conduct. Transistor Q1's collector will be near ground and D1 is reverse-biased, thus no current flows through D1 to IC1.

Transistor Q1 is the low-level input detector. When the circuit-under-test forces the voltage at the junction of resistors R1 and R2 below approximately .5 V, Q1 stops conducting. Its collector rises toward +5 V through R7. This action forward-biases D1 and supplies current to IC1. IC1 is the popular 555 one-shot. It is connected to run in the astable mode. When R7 and D1 supply current to IC1 pin 7, IC1 oscillates at a low frequency.

Transistor Q2 is the high-level detector. Resistors R5 and R6 form a voltage divider that provides approximately 1.6

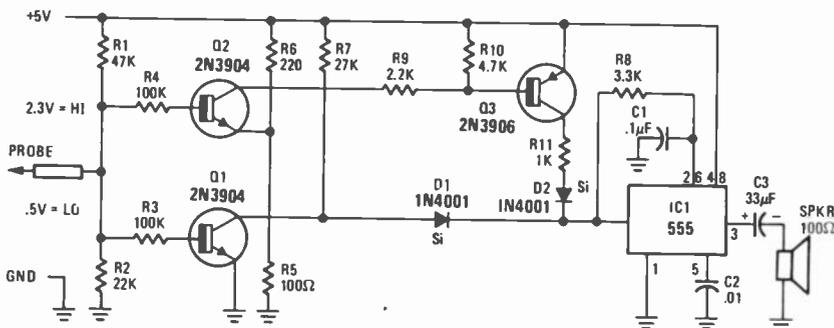


FIG. 1—THE TONE PROBE uses a 555 IC and three transistors.



PARTS LIST

All resistors are 1/4-watt, 10%.

R1—47,000 ohms
R2—22,000 ohms
R3,R4—100,000 ohms
R5—100 ohms
R6—220 ohms
R7—27,000 ohms
R8—3300 ohms
R9—2200 ohms
R10—4700 ohms
R11—1000 ohms
C1—0.1 μF
C2—.01 μF
C3—33 μF

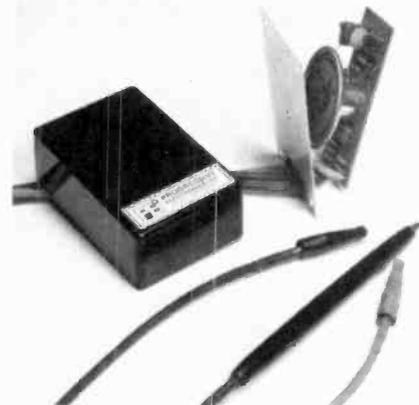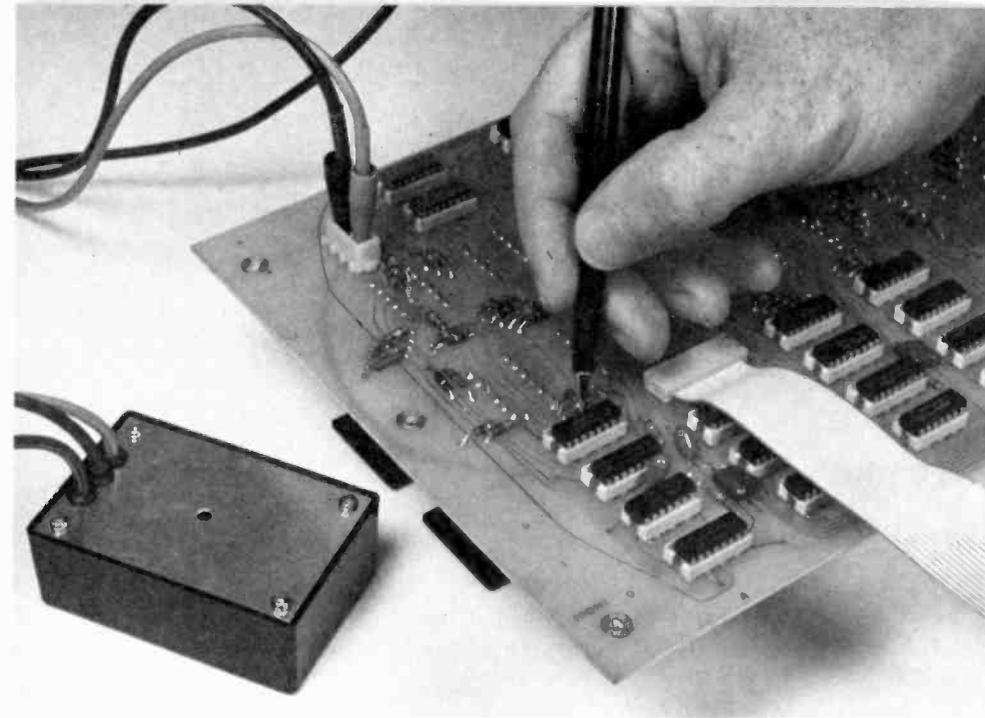Q1,Q2—2N3904
Q3—2N3906
D1,D2—1N4001
IC1—555 timer
Misc.—5-volt power supply, 1 1/2-inch speaker (100-ohm), probe, circuit board or perforated board, 3 × 2 × 1-inch box.

The following items are available from Progressive Electronics, Inc., 432 South Extension, Mesa, AZ 85202. A pre-cut and pre-drilled printed-circuit board—\$2.50. A complete kit of parts, including case—\$15.75.



TONE PROBE shown removed from its case. Cover fits against speaker, holding assembly in place.

A small amount of epoxy glue or silicon rubber sealant secures the rear of the speaker magnet to the component side of the board. When installed in the case, the cover is compression fit to the speaker.

The three leads have a knot just inside the cover of the box to act as a strain relief. The probe can be either a commercially available replacement probe or it can be made from a ball-point pen.

Checkout

To check the tone probe, a 5-volt supply is needed as well as a 1,000-ohm potentiometer. Connect the supply to the + and - leads of the probe. Connect the outside terminals of the pot across the power supply and rotate the pot so the center terminal is at ground (-). Connect the probe to the center terminal on the pot and check for a low-frequency tone. Turn the pot, increasing the voltage until the tone just quits. Measure this voltage. It should be between 0.4 and 0.6 V. Increase the voltage further until a high-pitched tone just starts. Measure this voltage. It should be between 1.7 and 2.0 V.

If your probe triggers within these limits it is functioning correctly. If it does not test correct, check for proper value resistors in R1, R2, R5 and R6.

If the probe does not make any sound, check IC1, Q1 and Q3. Also make sure D1 and D2 are connected in the right direction.

Using the probe

After attaching the tone probe to a power source, touch the probe to each of the leads of the integrated circuit being checked. A high-pitched tone will be heard if there is a high-level signal (2 volts); a low-pitched tone will be heard if there is a low-level signal (0.8 volt). No tone will be heard if the signal is between these two voltages. To check the tone probe, touch the end of the probe to the B+ source—a high-pitched tone should be heard.

R-E

V for the emitter of Q2. With the probe low or floating, the base-emitter junction of Q2 is reverse-biased and no collector current flows. If the circuit-under-test changes state and goes high, Q2 begins to conduct at about 2.3 V.

With Q2 conducting, R9 supplies base drive to Q3, causing it to conduct. The input signal causes Q1 to return to a conducting state and removes from IC1 the drive that causes it to oscillate at a low frequency. Transistor Q3 now supplies this drive current through R11 and D2. Resistor R11, being much smaller than R7, sends more current to IC1 and it oscillates at a much higher rate, producing a high-pitched tone.

Construction

The probe layout is not critical and may be built on perforated board or on a printed-circuit board made from the layout (Fig. 2) supplied.

All components, including the speaker, mount on the printed circuit board.

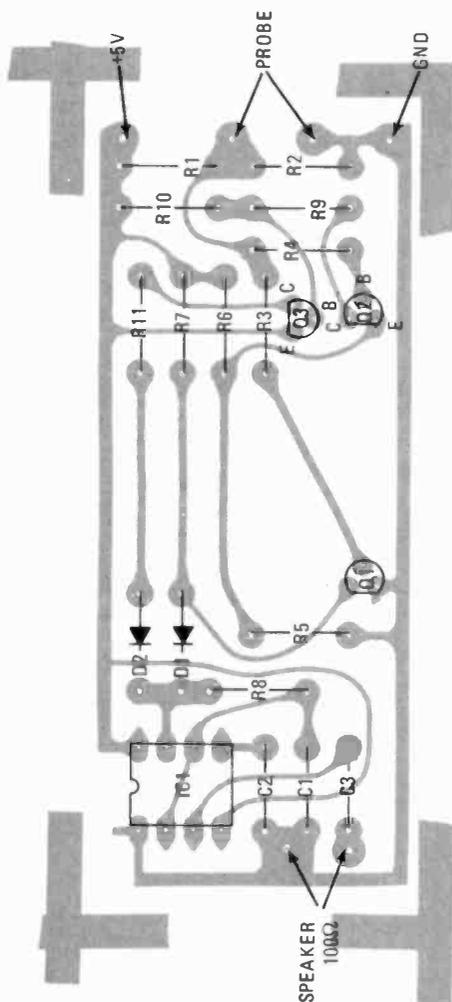


FIG. 2—PRINTED-CIRCUIT foil pattern. The board measures 6 × 2 5/8 in. (15.2 × 6.0 cm.)

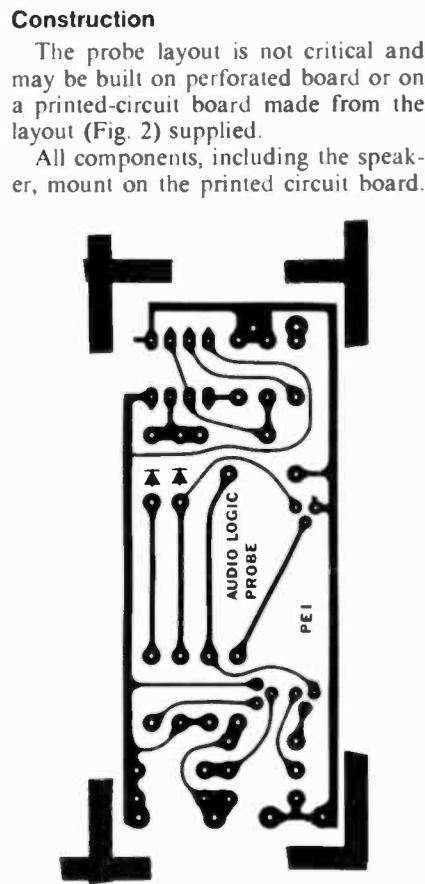


FIG. 3—COMPONENT PLACEMENT diagram.

State of SOLID STATE

An in-depth look at two rhythm generators designed for electronic organs, new microcomputer boards and a programmable scientific calculator plug-in board are featured this month

KARL SAVON
SEMICONDUCTOR EDITOR

SOME YEARS AGO I PURCHASED A FAIRLY DELUXE SOLID-STATE ELECTRONIC organ. Solid-state meant that all the active devices in the instrument were transistors. The IC was not yet a reality. There was still a good crop of tube jobs around at the time. Oh boy! This was the epitome of home music making; it even had a little box in its innards that put an alternating-note xylophone into the percussion lineup! Press enough tabs and even a simple single-note melody line played in some semblance of cadence impressed the uninitiated.

With a couple of weeks or months of developmental ground work, you (or better still an organ manufacturer) can now take a handful of IC's and put together a tone and percussion generator that gives the older units a run for their money. The performance output per dollar of parts is unprecedented, even with continuing inflation.

The rhythm generator has always been an exciting add-on or add-in to the organ. Inability to play in time is a common fault of many amateur musicians. If they want to stop for a few beats to figure out that next chord, they simply do so and nothing much happens. Try to play with a group or listen to yourself on a tape recorder and you immediately know that you're doing something wrong. The rhythm generator is a big help in this situation. It acts as a metronome and forces you to learn to keep an even tempo. The first time you try to play along with one of these gadgets you may be in for a rude awakening.

At the time I bought my instrument, rhythm generators were expensive discrete multiple stage shift-register gizmos with slews of decoding diodes, switches, and wire.

Well, the IC rhythm generator has arrived. Ever-expanding memory products and technology have brought prices down to where consumer product makers are using them. The products will do new tricks and the manufacturer's costs are usually reduced. Toss the rhythm generator in with other music and standard monolithic devices and you can build an amazingly versatile wonder in a deceptively small container. Frequency dividers, flip-flops, and oscillator chips are natural additions to the mix.

Integrated rhythm generators

American Microsystems Inc. and more recently SGS-ATES Semiconductor Corporation have announced rhythm generators designed specifically for organs and other electronic instruments. These are not conglomerations of standard digital circuits but one-chip devices with only one application in mind.

Both manufacturers' devices are largely read-only-memories with the various rhythm patterns embedded in their cells. Supporting circuitry reacts to input controls and supplies the independent instrument outputs.

The AMI S9660 will drive seven rhythm instruments—that is, seven different, usually percussion simulation generators such as electronic versions of drums, cymbals, or bells. The rhythm pattern is 64 bits long—a unique nonrepeating 64-count sequence can be generated for

each of seven selected rhythms, for each of the seven instrument outputs.

Figure 1 is the block diagram of the AMI S9660. One of the most fundamental things that must be done on the chip is to generate the 64 separately decoded beats for the maximum length rhythm pattern. That is done by a six-stage counter which is fed from a divide-by-two and an on-the-chip oscillator that is externally frequency controlled

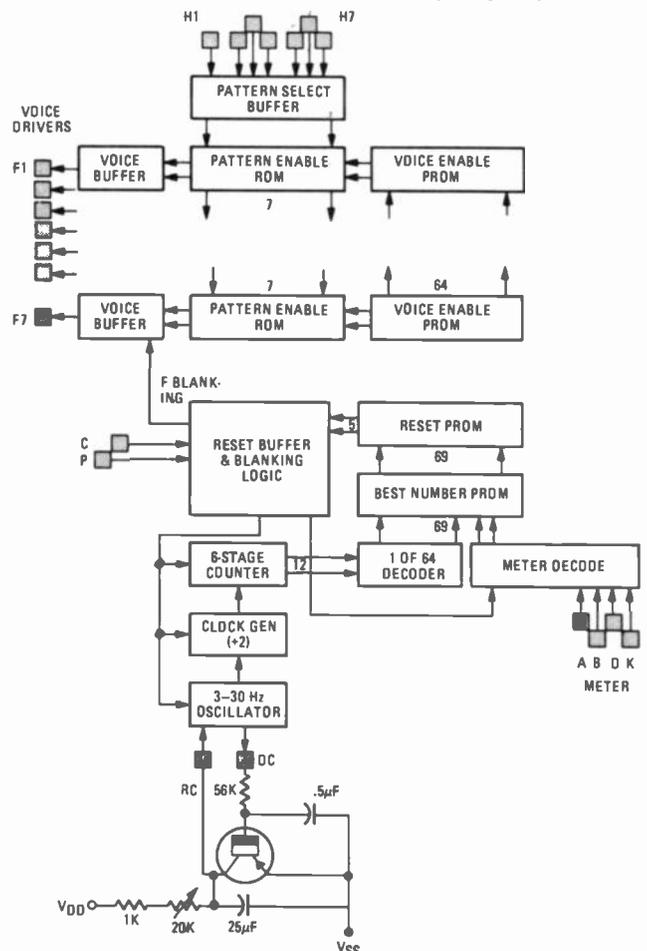


FIG. 1—AMI S9660 BLOCK DIAGRAM.

over a 3 to 30-Hz range. Terminal RC connects from the oscillator to the external resistor-capacitor frequency determining network. Base current to an external PNP transistor from terminal DC (dump charge) discharges the capacitor during the oscillator cycle. The six-stage counter steps through 64 independent states. (This maximum number of states is simply calculated as two to the sixth power.) There will be 64 different combinations of ones and zeros showing up in the counter's six stages. It is the job of the 1-of-64 decoder to detect and produce an independent output for each of these 64 counter states. The counter has 12 inputs, one for each complemented and uncomplemented stage of the counter, and 64 outputs. Each of the outputs activates one word in a 64-word read-only-memory. For this discussion, read-only-memory is synonymous with PROM. The memories are programmed during processing by using specially prepared masks.

Enough flexibility is built into the chip to generate all common rhythms. A 64-bit count is just not right for many of them, so the generator must be able to change the maximum sequence length. The S9660 has five mask programmable reset options. Normally the fifth one is reserved for the 64 unshortened count. These reset options are stored in a portion of the ROM. After programming, the five reset options are selected by the ABDK meter input terminals. V_{cc} (ground) is connected to one of the four terminals to select the first four meters. If none of the leads are activated the default 64-bit count is implemented.

Typically the timing could be programmed as follows: A might be $\frac{3}{4}$ time. A total of 36 bits can be broken into 9 bits for each of 4 measures. Three bits are assigned to each of the three beats per measure. The idea is to provide the maximum possible bits-per-beat for each meter within the 64-bit limit, consistent with the intricacies of the final rhythm. If B were set for $\frac{3}{4}$ time, 2 measures could be separated into 20 bits each. The number of bits in each measure must be a multiple of 5 in this case. This allows four bit divisions for each of the 5 beats, allowing timing outputs at $\frac{1}{16}$ -note intervals. D, programmed for $\frac{3}{4}$ time, could have a total 48-bit count with again 4 bits assigned to each beat, in this case 6 beats per measure. K could also be $\frac{3}{4}$ time like A but with 4 bits/beat. A 48-bit sequence is required by 4 measures \times 3 beats/measure \times 4 bits/beat. And finally the full 64 count selected if all inputs are unconnected might be $\frac{4}{4}$ time with 4 bits/beat, 4 measures, 4 beats/measure and 4 bits/beat: $4 \times 4 \times 4 = 64$.

At this point the decoded sequences have been generated and the device must be able to select the particular rhythms and generate the seven outputs.

Each of the 64 programmed words in the voice-enable PROM contains in its ones and zeroes the binary information as to which of the seven instrument outputs is to be activated at which of the maximum of 64 counts. Each of the seven instruments may contain an entirely different and independent rhythm as desired.

The seven H inputs address the pattern-enable portion of the ROM. A pattern is selected by applying V_{cc} to one of seven pins. The voice buffers are fed by the selected programmed ROM patterns. An interesting feature is that the rhythms may be combined by overlaying them by enabling more than one pin at a time. Overlaid outputs are logically OR'ed so that an output occurs when at least one of the overlapped patterns is enabled during a particular interval. The output voice drivers interface with transistors and provide low-resistance paths to V_{cc} when activated.

When held at V_{DD} the C reset input holds all outputs off. Applying the supply voltage starts the count at its beginning. This feature can be used as a synchronized trigger connected, say, to an organ-pedal sensing circuit.

The S9660 is built with AMI's ion-implant process. Starting out with the standard P-channel process, two ion implant steps are tacked on. Transistor thresholds are reduced to -1.5 volts by the first implant. Power consumption is reduced and TTL compatible input and outputs are the result. Constant-current load devices with +3.5 volt thresholds are selectively produced with the second implant. Higher speeds for the same current are possible with constant current loads. Accurately controlling threshold (the gate-to-source voltage at which the channel begins to turn on) increases the yield. Yield refers to how many of the pellets processed turn out to be good ones at the end of the line.

Internal pull-up resistors to V_{DD} are provided on all inputs except the oscillator input. The S9660 comes in a 28 pin dual-in-line package. The V_{DD} supply is operated between -8 and -13 volts.

A particular set of IC rhythm sequences is programmed by punching 54 IBM cards. Five cards are punched for the five reset short count inputs (N,K,D,B,A). Seven cards are punched for each H

rhythm select input. Each of the seven cards for each H input contains the sequence (64 bits or less) for each instrument plus identification recognized by the programming machine. So these last cards total 7×7 plus the other five for the total 54.

Besides the S9660, AMI makes a number of other music-oriented products. The S2555 Music Frequency Synthesizer generates seven notes of the equally tempered scale, dividing down a 2.1 MHz input clock. The S2556 used with the S2555 supplies the other six notes of the scale. The equally tempered scale is the widely adopted harmonic compromise system. The same thirteen frequencies per octave can be used whatever the key.

American Microsystems Inc. is located at 3800 Homestead Road, Santa Clara, CA 95051.

An offering from SGS-ATES

The SGS-ATES M252 and M253 are similar monolithic circuits. The M252 has a 3840-bit PROM, which will store 15 rhythm patterns for eight instruments. Since the patterns may be up to 32 beats each, this calculates to $15 \times 32 \times 8 = 3840$ bits. The M252 will store 12 rhythm patterns for the same 8 instruments and 32 beats, and so uses a smaller 3072-bit memory.

The interesting thing is that the smaller memory device is packaged in the bigger DIP! The M252 comes in a 16-pin DIP but the M253 is mounted in a 24-pin package. The reason is that the M253 has its 12 patterns selected by connecting the input pin for the pattern to V_{SS} . Only one terminal is enabled at a time so 12 terminals are tied up in the process. This is simple for the user because all he does is provide an uncodded series of SPDT pushbuttons. Double-throw switches are needed to return the unused inputs to V_{GG} . The M252 with 15 rhythms uses binary coded 1-2-4-8 weighted select inputs. Four terminals then select the full 15 combinations. The difference between the 12 and 4-pin input terminal count is 8, precisely the difference in pins between the 16 and 24 pin packages.

Both devices are either purchased with standard patterns programmed in or are specially mask programmed to a user's preference. The standard version of the M252 includes the following rhythms: Waltz, Tango, March, Swing, Slow Rock, Rock Pop, Shuffle, Beguine, Cha Cha, Samba, Bossa Nova, Jazz Waltz, Foxtrot, Mambo, and Bajon. The 253 in its standards version leaves off the last four and adds the Rhumba.

Both the M252 and M253 use external clocks to feed a phase generator and a divided stage and then a 5-stage counter with its decoders. The general scheme is similar to the AMI chip. Five stages instead of six are adequate because the beat sequence is half as long. The decoder controls the read-only memory and the reset logic. Mask programming can shorten the 32 counts to 24 only. Other shorter counts are implemented by using output 8 to reset the counter. It will simultaneously generate a downbeat and reset signal, a single beat, which shortens the sequence to the number count at which it occurs.

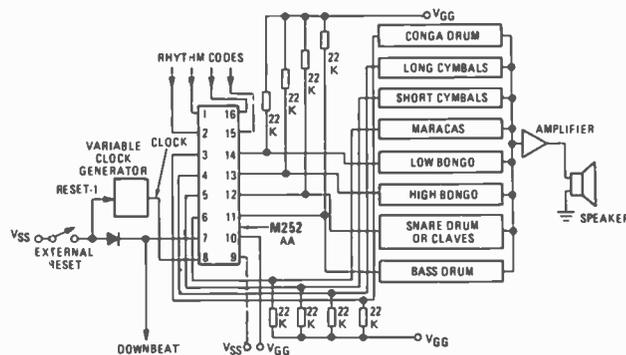


Fig. 2—SGS-ATES MODEL M252 rhythm generator.

Figure 2 shows a typical setup of the standard content M252 device with the suggested external instruments. If space separation for stereo effects is desired, the instruments can be split and summed differently into two or more amplifiers rather than the hookup shown. By combining two chips, the number of rhythms, the number of instruments, or the total number of beats can be extended.

Figure 3 shows the rhythm extension scheme. The 1-2-4-8 encoded inputs feed the corresponding terminals on the two chips in parallel. A coded 16-weight input is added to give the extended control. Thirty rhythms require five bits to control them since 2^4 is only 16. The added input simply selects which of the chips is to be activated. Both

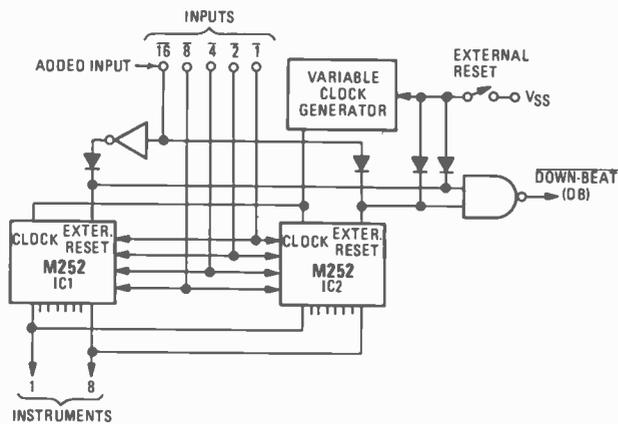


FIG. 3—RHYTHM DOUBLING SCHEME.

reset inputs are fed through diodes but chip-1 has an inverter in its reset path. This way one device is held at reset and the other allowed to operate, depending on whether the 16 input is high or low. To increase the number of rhythms with the M253, which is not binary coded, the two chips are operated with their outputs paralleled. The inputs are renumbered from 1 to 24 and no further select logic is needed.

The number of instruments can be increased by operating the two devices' clock inputs in parallel, resetting them at the same time and clocking them with the same generator, keeping them phase-locked. Rhythm programming is different for the two circuits so there are eight different instrument patterns from each chip for a total of 16 in all.


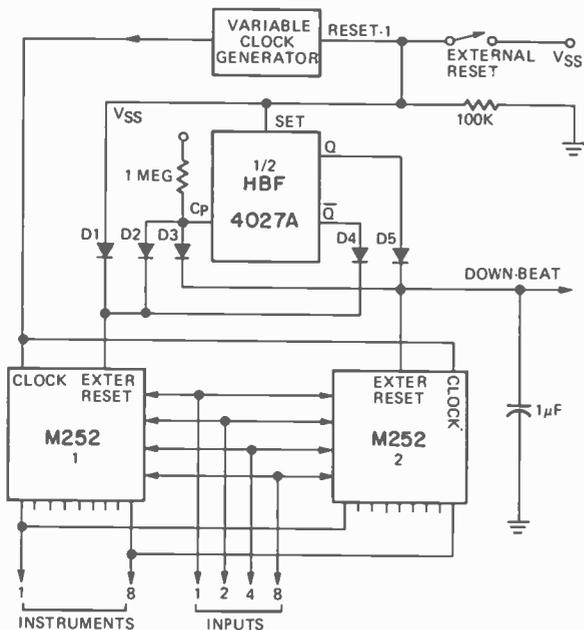


FIG. 4—LENGTHENING THE COUNT.

Figure 4 details the count lengthening scheme. A maximum of 64 beats is possible. The idea here is to let the two generators work sequentially. One-half of a 4027A dual J-K master-slave flip-flop is used to hold one generator reset while the other goes through its 32 counts. The flip-flop then changes state and the other rhythm generator takes over with its 32-bit sequence. Isolation diodes (D2 & D3) are connected to the flip-flop clock input from the reset terminals of each generator. It is the reset signal at the end of the 32nd pulse that signals the termination of one sequence and toggles the flip-flop. Since the output devices are open-drain and normally off, the eight instrument outputs on chip-1 can be wired directly in parallel with those on chip-2.

Mask programming information for the SGS-ATES circuits are written into a truth-table form. A table is filled out for each instrument, with 8 columns, one for each instrument.

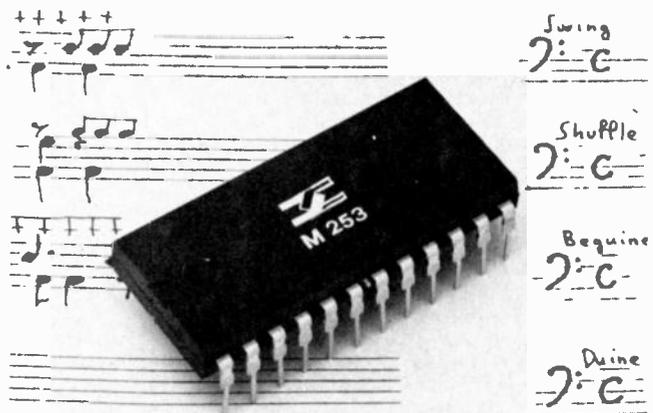Standard +5 and -12-volt supplies are used and maximum current drain is 15 mA. ON output resistance is less than 500 ohms. Down-beat trigger signals are available on the external reset/down-beat



RHYTHM ON A CHIP—THE M253.

terminal. Driving a lamp from this signal gives visual indication at the start of each sequence.

P-channel silicon gate processing is used and both ceramic and plastic packages are available. Small-quantity prices for the M252 and M253 are \$15 and \$19.50 respectively. The prices drop by a third for quantities between 100 and 999. Further information is available from SGS-ATES Semiconductor Corp., 435 Newtonville Avenue, Newtonville, Mass. 02160.

Microprocessor news

Martin Research, authors of the book *Microcomputer Design*, offer a set of PC boards which form a bus-oriented system so that any board may be plugged into any position on the bus. If you want to expand the system you add the board at the next empty slot. This is the same sound philosophy used by some well-known minicomputer companies.

They have a *Mike 2-1* CPU Board, which holds the 8008 chip, a crystal-controlled oscillator, and the timing generation circuits. The *Mike 2-20* Console Board has six seven-segment displays and a twenty-key calculator-type keyboard. The output display can be read in octal, decimal, or hexadecimal (base 16). The *Mike 2-3* PROM/RAM board holds 1K of RAM and 2K of PROM.

MR's basic system uses 256 words of RAM and 256 words of PROM. It is preprogrammed with the *Mike 2* monitor that is used to write instructions into and read instructions from any location in memory using the keyboard.

The *Mike 203A*, which includes the 8008 microprocessor sells for \$269.95 in kit form and \$319.95 assembled (and tested). For details write to Martin Research, 1825 S. Halsted Street, Chicago, IL 60608.

Scorpia Laboratories SC-440

This is an externally programmable scientific calculator plug-in circuit board that interfaces with TTL. It works with ASCII inputs and has multiplexed BCD outputs. It can be used tied to instrumentation for data-reduction tasks that do not need the complexity of a microcomputer and the necessary software. In effect the software is built into the calculator chip. Or it can be a microcomputer satellite as a hard-wired data-reduction peripheral. Keyboards, accessory RAM/ROM memory cards, a low-cost cassette, a 3½ digit DVM/DMM and a 40-MHz frequency counter are being developed.

Scorpia's SC-441 is a 42-pin module designed to interface instruments with BCD outputs, such as digital voltmeters or clocks with microprocessors on 4, 8, or 16-bit data busses. It also allows retrofitting BCD instruments to become remotely controlled transmitters, using the recently standardized Universal Interface Bus.

It is useful in reading and storing in memory the time of the measurement as well as the readings of temperature, pressure, flow, liquid level or pH. The SC-440 is also useful in security alarm and payroll computing systems.

The SC-440 costs \$300 in single units and drops a third over 50. The single unit price of the SC-441 is \$100. Scorpia Laboratories Inc., 46 Liberty Street, Brainerd Station, Metuchen, N.J. 08840.

Calculator display drivers

National's DS8864 has nine independent LED digit drivers that will sink up to 50 mAs from a common cathode display operating in a multiplexed mode. Drive current is typically 0.9 to 1.2 mA, which will interface with most MOS calculator chips. The LED to MOS interface chip also includes a battery-condition sense circuit that lights up the leftmost decimal point when the battery is low.

R-E

R-E's Service Clinic

Lightning protection

Be safe rather than sorry

JACK DARR
SERVICE EDITOR

THERE'S AN OLD SAYING THAT GOES: "Lightning never strikes twice in the same place; because when it hits the second time, the place isn't there any more". Unfortunately, in solid-state circuitry, this isn't true. We're running into more repeated failures of the same parts due to lightning transients than ever before. This is the bane of designers' and technicians' lives. One harried technician wrote us a pitiful story of having replaced the same IC in a well-known make six times under warranty, and twice after the warranty ran out!

Unfortunately, there isn't any such thing as a true "lightning *arrester*". The only thing these gadgets can do is shunt the current off to ground through a small arc-gap, destroying themselves in the process. In the case of a direct hit, it's just too bad. The current is so tremendous that the place literally isn't there. I've seen a 6-inch square heavy ceramic fuse block, two big fuses, the brass holders, and everything except the ends of the wires completely disintegrated after a lick like this. (This occurred in a radio transmitter atop a mountain.) The cabinet looked as if someone had thrown about 5 pounds of flour in it!

However, for the smaller hits that cause sharp line-transients, we can help things a little. We can't stop them but we can hold the damage down quite a lot. There are devices that will help.

Chassis modifications

One of these is the super-fast action varistor, such as the GE-750 from General Electric, that is connected directly across the AC line where it comes into the chassis. These are specially designed metal-oxide devices and are called *GE-MOV* varistors. In normal operation, they have a very high resistance so that they have no effect on the circuit. When a transient spike comes along, they break down very quickly and become a short circuit across the line ("crowbar" effect). G-E's Application Note on these gives a response-time of less than 50 nanoseconds for the type V130LA1.

That's one; another method recommended by set-makers is the installation of chokes in the AC line. The idea of these is to offer a high resistance to very sudden changes of current, such as a transient spike. Bypass capacitors to

ground are also used for the same reason; they provide a low-impedance path to ground for the spikes.

Zenith has a set of recommendations for problems like this. In their 19DC12 and 23DC14 chassis, they tell you to replace the original line chokes (95-2920) with one of higher inductance, 95-2964. In Issue 72-73 of *Tech-Topics*, they also recommend moving some of the low-level leads going to the 9-97 color module—one of the parts that have suffered repeated damage in areas where thunderstorms are frequent. It looks to me as if they are figuring on reducing the chance of the spikes being coupled into the module circuit by inter-lead capacitance.

Paraphrasing the instruction for this, several leads of the control plug and socket are changed. This requires the use of an 868-2 (Molex HT-1010-2B) pin-extraction tool. For the 19DC12 chassis, here are the changes (Fig. 1) that should be made:

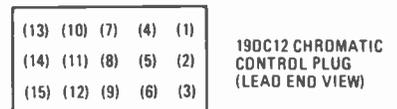


FIG 1

1. Remove the orange wire from pin 4 and place it in the empty pin-10 position.
 2. Remove the black wire from pin 13 and place it in pin 4.
 3. Remove the green wire from pin 5 and place it in pin 12.
 4. Remove the blue wire from pin 6 and place it in pin 13.
- (1 and 2 in the original layout are the leads to the AC switch. The leads on 5 and 6 go to the color circuits, and for goodness sake don't forget to change the leads in both plug *and* socket! It would also be a good idea to stick a note on the chassis saying that this modification had been made!)

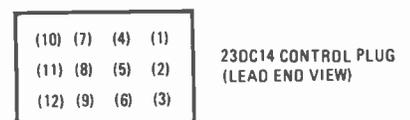


FIG 2

- In the 23DC14 control plug (Fig. 2) these changes should be made:
1. Remove the white-green wire from

This column is for the service technician's problems—TV, radio, audio or industrial electronics. We answer all questions submitted by service technicians on their letterheads individually, by mail, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Avenue South, New York, NY 10003

pin 4 and place it in the empty pin 7 position.

2. Remove the black wire from pin 10 and place it in pin 4.
3. Remove the green wire from pin 5 and place it in pin 10.
4. Remove the white/black wire from pin 11 and place it in pin 5.
5. Remove the violet wire from pin 6 and place it in pin 11.

Be sure to get the right plug in the 23DC14. This is P203, which is the 12-pin connector and not the 15-pin "Secondary Control Plug" P204.

Other manufacturers have similar "fixes" for these problems, for they've

all run into them. If you have trouble, check with the nearest distributor for the brand and ask them what the factory recommends. If you can't get anything, you might go ahead and add the *GE-MOV* varistor and the bypass capacitors, as well as the chokes in the AC line. I've always been a "belt-plus-suspenders" man; a bit extra can't hurt.

Antennas

Cable systems are usually pretty well protected against lightning. The spikes have to travel through so many things that they dissipate before they get to


you. However, if the set is used with an outside antenna, there are several things that must be done to make it as safe as possible from damage.

For the most important, the mast or tower must be well grounded. Drive at least a 4-foot ground rod and tie or bolt this to the mast. There is a very handy thing available that I wish I had when I was putting up antennas. This is a combined base and ground-rod. It's driven into the ground up to the flange, and the mast simply dropped over the stud on top. Since practically all antennas are well-grounded by the mounting bolts, a properly installed mast makes a very good lightning rod!

The other essential is a good UL approved lightning arrester, which should be mounted on the wall as close as possible to the place where the lead-in enters the house. If this is close to the bottom of the mast, you can use this ground. If it's more than a few feet away, drive *another* ground rod directly below the arrester and run a short heavy ground wire to it.

One more precaution. If a certain location seems to get more than its share of lightning damage, check the grounding of the AC line at the point where it enters the house. There should be an 8-foot ground-rod directly under the "service entrance" box. These ground rods are sometimes hard to drive all the way. Some careless workmen have been known to drive them only about 24-inches and hit a rock. Then they cut off the top of the rod and go away! This is *not* sufficient grounding for protection. (Ask me how I know. I did this, and lightning promptly hit the place and scattered the motor of my water-pump all over the basement! The well-casing made a good ground! There is now a full 8 feet of ground rod at my place; I had to drive three of them before I got one all the way in through the rocks but it's there and we haven't had any more of this kind of trouble.)

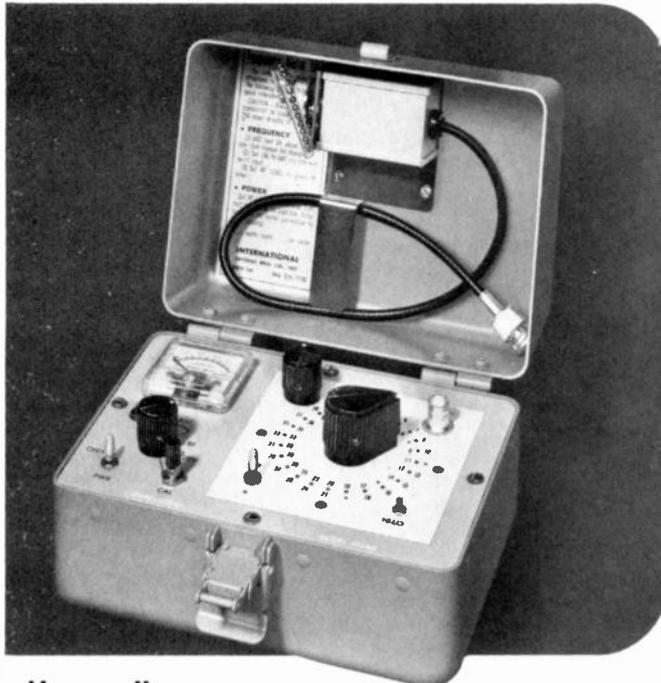There is only one really effective way of eliminating lightning damage; pull the line plug and disconnect the antenna! This is quite safe, unless you take a direct hit on the house. If this happens, you will have so many other worries, you'll forget the TV set! R-E



International's 6024B 40 Channel CB Frequency Meter

- Secondary Frequency Standard
- Signal Generator
- Power Meter

The 6024B provides three test instruments in one convenient case for professional servicing on all makes of Citizens Radio transceivers.

1. Secondary Frequency Standard, 26.965 to 27.405 MHz, and 27.235 to 27.405 MHz. Counter circuit zero to 2500 Hz.
2. Signal Generator 26.965 to 27.405 MHz.
3. Dummy Load/Power Meter, up to 5 watts.

Complete with connecting cable, dummy load, rechargeable battery and charger.

\$425.

Cat. No. 035311



International Crystals are available from 70 KHz to 160 MHz.

Write for information,
ICM
M/S Dept. P.O. Box 32497
Oklahoma City, Okla. 73132



INTERNATIONAL CRYSTAL MFG. CO., INC.
10 North Lee / Oklahoma City, Okla. 73102

CIRCLE 75 ON FREE INFORMATION CARD

reader questions

LOSS OF VERTICAL SWEEP

I've got a black-and-white portable with no vertical sweep at all. I want to make a quick-check of the vertical output transformer and yoke. Can I use a separate 6.3-volt filament transformer to feed a signal into the output tube? This set has a series heater string.—J.G., Arlington, VA.

If you feed the test signal into the grid of the vertical output tube, OK. If you feed it directly to the plate, either disconnect the plate voltage or use a good-sized blocking capacitor (0.25 or 0.5 μ F.)

ALTERNATOR WHINE IN STEREO

We're running into problems with stereo tape players, mainly in GM cars where the player is mounted on the left side of the dash. It seems to be a three-phase ripple loaded with harmonics, from the alternator, and coupling into the tape-player. Have you heard of this problem before?—J.H., Orangeburg, SC.

I've run into this a long time ago in two-way radio receivers. We just called it "alternator whine", and it is pretty hard to get out. We finally made up some L-C filters enclosed in metal boxes connected this in the line from the alternator output. This killed it.

You can get these filters all ready made now: J.W. Miller C-503-E, and others. I'm pretty sure these are L-C filters and not difficult to install.

LOSS OF WIDTH

The picture is perfect on this Zenith 16H27, but it isn't wide enough. I've checked all of the regular things; new tubes and so on. No go. The drive voltage

1 out of 2 who have it don't know it...

Do you?

21 million Americans have high blood pressure. But 50 percent of those who have it, don't know it.

When blood pressure goes higher than it should, and stays high, it sets the stage for heart attack or stroke.

Most cases of high blood pressure can be controlled with drugs and other advances in treatment. That's why you should see your doctor regularly. Only he can tell if you need help.

A public service message from your Heart Association



now... 97% ACTIVE INGREDIENTS

Plus
WARMER SPRAY FOR MORE CLEANING POWER

TUN-O-WASH has long been the industry standard in tuner degreasers. Now, it's better and more economical than ever.

No, we haven't tampered with the famous TUN-O-WASH formula. That's too good to change. What we have changed is the propellant. We now use carbon dioxide (CO₂) as a propellant. This permits us to fill the can with 97% active ingredients, compared with only 65% active ingredients before this development. The can is the same size, but you get more cleaning power for your money.

There are other advantages to using CO₂ as a propellant. **FIRST**, the spray comes out 10° warmer. Everyone knows that heat increases solvent action. **SECOND**, the particles of solvent come out in larger drops, making for a wetter spray. And, finally, CO₂ enables us to maintain a uniform 70 pound pressure until the can is completely empty.

This is another first from the electronics industry's leading chemical manufacturer.

CHEMTRONICS INCORPORATED

45 HOFFMAN AVE., HAUPPAUGE, N.Y. 11787 • (516) 582-3322

CIRCLE 78 ON FREE INFORMATION CARD

THERE'S A BETTER WAY TO GO.

Energy shortages tell us we have to change our driving style.

Now! It doesn't mean we have to go back to horse and buggy days. But it does mean we have to make

every drop of gas give us the most go for our money. Anyone with horse sense knows that a well-tuned car gets better mileage, and in times of fuel shortages, better mileage means a lot.

The Mark Ten B Capacitive Discharge System keeps your car in better tune so it burns less gas.

Using Mark Ten B is more than horse sense. It's the

smart move under the hood, helping a nation survive an energy crisis and keeping you on the road. Delta Mark Ten. The best way to go.



DELTA PRODUCTS, INC.

One Delta Way, Dept. RE
Grand Junction, Colo. 81501
(303) 242-9000

I want to know more about Mark Ten CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name _____

Address _____

City _____ State _____ Zip _____

CIRCLE 46 ON FREE INFORMATION CARD

from the horizontal oscillator is low, and the oscillator plate voltage is too. B+ seems to be OK. In fact, the +265-volt source that feeds the horizontal oscillator reads +300 volts. This should be easy, but it isn't!—J.M., Marina del Rey, CA.

Old Saying: "Ought to be ain't is!". Sometimes I think there's no such thing as an easy one. Let's see.

Your grid drive to the 6DQ6 is low and this could cause it: low plate voltage on horizontal oscillator may be the cause. This stage is *not* fed from the B+265-volt source; it's fed from the boost, which should be +700 volts. Check the damper stage, particularly the boost

capacitor. Also; there is a tricky one in this chassis. Check that 40- μ F electrolytic capacitor on the *cathode* of the 6DQ6. If this is open, you'll get a degenerative feedback that will reduce the output. Scope it to make sure.

TOO MUCH RIPPLE IN PICTURE

I wrote you before about checking the excessive ripple in the picture of a Gambles TV2-3701 black-and-white TV. You suggested checking ripple on the power-supply filters. That was it! I had to add 80 μ F of extra capacitance to get rid of it! Works now. Thanks.—J.W., Hastings, MI.

EXCESSIVE WIDTH

The raster in this Sylvania D05-14 is so wide that I can see only 8 vertical lines of a crosshatch pattern! All of the DC voltages seem to check out all right. I tried reducing the screen grid voltage of the horizontal output tube. That didn't work!—C.M., Diamond Bar, CA.

Well, there went one of my favorite ways of reducing excess width! So now what? In several cases this chassis has shown excessive width if that VDR from the pin-3 cathode of the 6CL8 high-voltage regulator tube to ground goes bad. This is part No. 38-15257-9. Replace with exact factory duplicate; couldn't find a listing on it.

120-HZ HUM BARS

If you see two hum-bars in the picture, you have a bad filter capacitor—right? Not Always! I had them in an old tube-type Sears color TV set. Checked all electrolytic capacitors by substitution revealed nothing. Scope showed the typical "writhing" ripple with one hump crawling up the other. The peak-to-peak amplitude of this ripple wasn't too bad, either.

So; what is it? The *filter choke* is *shorted*. Not to ground, but the windings were shorted. After finding this, I remembered that I had found the same thing in an RCA about a year ago! Watch for this.

Thanks to Leon Caldwell, Caldwell TV, Mena, AR.

HIGH-VOLTAGE FLUCTUATION

This RCA CTC-22 chassis has a 12CT3 damper tube instead of the solid-state device used in others. The high-voltage fluctuates oddly; it will be going good, then for no apparent reason it'll bloom and then go black. The high-voltage drops to about 4kV. Cathode current of output tube holds steady at about 180 mA. I suspect the pulse regulator. New tubes no help. Any ideas?—W.L., Fairmont, WV.


I believe I'll go with you. Check that little capacitor from the plate of the 17KV6 regulator to the screen. I don't know exactly what it's for but I suspect it somehow.

(Feedback: That was it! I took it out, checked it and it was bad. Seemed to have gone up in capacitance from 15 pF to about 28–30 pF. Replaced it and the thing works. How did you know?)

(I guessed!)

GREEN RASTER

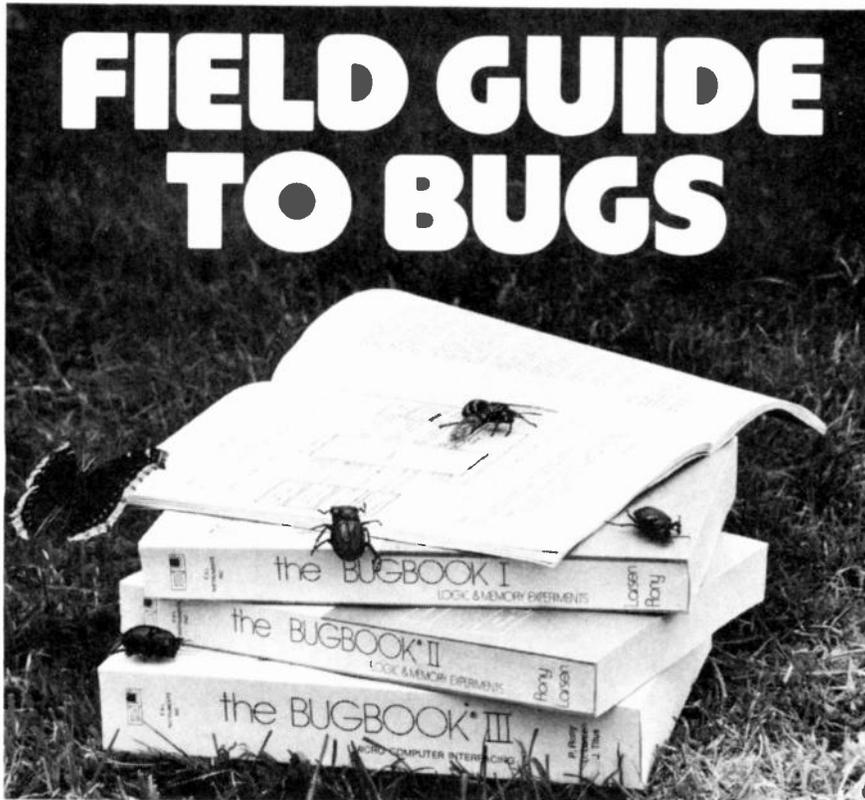This G-E CA chassis has all kinds of intermittents! Horizontal bars on the screen, the raster turns green and finally you lose focus, high-voltage and everything. If I pull the high-voltage lead to the picture tube, the high-voltage comes back. Found that when the problem shows up, the picture tube grid voltages



FIELD GUIDE TO BUGS

Complete Bugbook® library.

Now only \$43.95* including the new BRS-1 on the 555 Timer.

In a world crawling with bugs, it's good to have the Bugbooks by your side. Good to have just five books dedicated solely to teaching you digital electronics . . . from ground zero on up. From fundamental logic and memory experiments to interfacing with microprocessors. The Bugbooks are E&L Instruments' pioneering approach to mastering today's pulse-quick world of micro-electronics. With an approach that's simple and straightforward. Clear. Complete. Well-illustrated. And as fresh as tomorrow's circuit design. In all, some 1500 pages. They're the Bugbooks. Don't ven-

ture a step farther into the world of digital electronics without them. Because the place is crawling with bugs.

E&L's complete library of Bugbooks is now available through local computer stores. These stores also carry E&L's full line of breadboarding and microcomputer equipment. Stop in today . . . and start going bugs.



E&L INSTRUMENTS, INC.
61 First Street, Derby, Ct 06418
(203) 735-8774

Dealer inquiries invited.

*Suggested resale price U S A

all jump up to about + 400 volts. Checked the blanker and other stages, no luck. I'm learning, and any help will be appreciated.—L.M., Hopalong, NJ.

You'll learn, all right! This is kind of a tough one to start on, though. Now: you have found the cause of the symptom; now look for the cause of the cause. This will probably be one of two things. The basic cause is something that kills the plate current of the color-difference amplifier stages.

Check these: one, the 270-ohm cathode resistor of the difference-amplifier stages. This is common to all three and if one end has a bad solder joint, it opens the cathode circuits. Two: in these chassis, the heater supply for both difference-amplifier tubes goes through a wire jumper on top of the PC board. Check this for a bad solder joint.

WIDE SCANNING LINES

There are 5 or 6 horizontal lines in the center of the raster in this E0-2 Sylvania that are much wider-spaced than the rest. Vertical adjustments do nothing. Oddity: rolling the picture downward, the wide-spaced lines stay where they are! Could this be the deflection yoke?—G.D., San Juan Capistrano, CA.

Try turning the horizontal hold control on a blank raster. If this affects the

position of these lines, suspect something in the pincushion circuitry. There is a resistor, R377, shunted across the pin-transformer that may be bad.

HALF A PICTURE

Here's a confusing one! I have the right half of the picture on the screen in this Magnavox T-940 chassis. The trouble is that the right half is on the left side of the screen and the right half is blank! Not blank, but black; no raster! Any suggestions?—H.S., Universal City, TX.

I have a silly cartoon over my desk on exactly the same problem! While the Professor is trying to figure out what's causing it, his wife pushes the cabinet to the left; this centers the picture! I don't think this is what's wrong here. (Did you try it, though? Never can tell!)

OK: Seriously. This chassis uses a pair of diodes in the horizontal centering circuit, with the centering control across them. This is in the horizontal deflection yoke circuitry. It sounds as if the raster is being deflected far too much to the left. Check the diodes, the bypass capacitors and the control itself for an open circuit. One of these has gone, I'd say.

MULTIPLE PROBLEMS

I changed the picture tube in this RCA CTC-16; now I've got several problems!

Picture is dim when first turned on, but comes up to normal brightness after a few minutes. Contrast is poor; AGC has very little effect, color is odd, and for a fast one, the horizontal hold is very touchy. It falls out of sync, but it can be restored by just touching the hold control. Give me some hints as to what's doing this!—J.C., Ft. Worth, TX.

You've got problems, and the problems have got problems! For openers, I believe I'd ignore the others and fix the horizontal hold problem. You just might clear up a whole lot of them when you do. All of the rest could be due to incorrect phase of the horizontal oscillator!

Suspect the AFC diode unit first. Replacement is the fastest way. If this doesn't get it, check the PC board conductors and that little 51-pF coupling capacitor from the sync separator to the AFC diode unit.

VERTICAL OUTPUT TRANSISTOR

I need a replacement for the vertical output transistor in a G-E UA-4104 WD. There was another type in it. Can't find a substitute. What will do this?—J.I., High Point, NC.

The original is a G-E ES15X91. An RCA SK-3104 or Motorola HEP S5015 should replace it. Same spec's and plenty of voltage rating. R-E

TIGER .01

Introduced three years ago, our "Tiger .01" is still one of the finest amplifiers available in its power class. This amplifier introduced our 100% complementary circuit which has become a standard feature in many of the better amplifiers. This combined with an output triple produces a circuit that can honestly be rated as having less than .01% IM distortion at any level up to 60 Watts. Relatively low open loop gain and a conservative amount of negative feedback results in clean overload characteristics and good TIM characteristics.

Other features are volt-amp output limiting, plus three fuses and an overheat thermostat. Despite the "budget" price an output meter is standard equipment. Each channel measures 4 1/4 x 5 x 14. Four will mount in a standard width relay rack for four channel systems.

SPECIFICATIONS

60 Watts—4.0 or 8.0 Ohm load Minimum RMS from 20 Hz to 20 KHz with less than .05% Total Harmonic Distortion.

IM Distortion less than .01%
Damping Factor 50 or greater 20 Hz to 20,000 Hz.
Hum and Noise -90 dB

207/B Amplifier (single channel) \$110.00 PPD
207/B Amplifier — Kit \$ 77.50 PPD



Southwest Technical Products Corp.
219 W. Rhapsody, Dept. FM
San Antonio, Texas 78216

user operations and solved most problems associated with the subroutine system. The main drawback of this method was imposed by the semiconductor processing technology. With the stack on the same chip as the processor, there wasn't a lot of room left. This meant that the number of elements in the LIFO had to be limited. The result was a limit on the amount of program nesting that could be performed without filling the stack and losing return addresses. On most processors the user was limited to seven unreturned subroutine calls. This limitation also meant that stack usage had to be limited to subroutine return addresses alone. This denied the user access to many of the other features a stack can provide.

To solve these two problems, some manufacturers decided to implement the LIFO as part of the system main memory. They provided the stack pointer and the automatic increment/decrement hardware. The user then supplied the address of the memory block to be used as the LIFO. This is accomplished by loading the top address of the selected memory block into the stack pointer. From then on the stack functions automatically.

This certainly solved the nesting problem. Most systems have far more memory than a properly functioning program will ever need for subroutine nesting. It also makes the stack available for other uses. This allows you to use the stack to save registers, pass data to

and from subroutines, and lots of other useful functions. However, there is no such thing as a free lunch. If you are going to manipulate data in the stack you have to balance the stack pointer.

Balancing the stack pointer simply means that it must be pointing to the correct return address when a subroutine return is executed. Failure to do this can result in your program accidentally using the data you meant to pass back in the stack as the return address. This type of error can result in some really interesting program execution. Balancing the stack requires that you pay close attention to the order in which data is entered and removed from the stack. Under normal operations, the data must always be removed in the opposite order in which it was entered. You must also be certain that no programs accidentally write data into the area you have reserved as the stack. It is also a good idea to make sure the stack doesn't grow too large and encroach on other program storage. The easiest way to avoid most of these problems is to assign the stack to the top 100 bytes of your system memory and leave it alone. This will probably be far more stack than you ever need and it will save you a lot of time you would otherwise have to spend computing exact stack usage.

Summary

Stacks provide you with a convenient way to solve many design problems. The FIFO and LIFO offer different characteristics for use in different applications. They can both save you much time and make it easier to implement a variety of system functions. If

your computer uses a memory LIFO stack for subroutine return addresses, with a little practice you will discover ways to use it to make your programs more efficient. Whether hardware or software, the stack is a useful new tool for the designer. **R-E**

1977 CB sales will exceed all previous years combined

More CB radios will be bought in the United States in 1977 than in all of CB's previous 28 years added together, says John Sodolski, vice president of the communications division of the Electronic Industries Association (EIA). He expects sales to approach the ten million mark for 1977, and estimates that retail sales of CB radios, antennas and accessories should top \$2 billion for the year.

Only about three million CB radios were sold between 1958—when the FCC allocated 23 channels for Citizens radio—and 1973, when the sudden upsurge began. Sales exceeded a million in 1973, then doubled each succeeding year, hitting nearly five million in 1975.

Unlike some industry predictors, Mr. Sodolski believes that 23-channel radios will continue to be popular, especially during the earlier part of 1977, before the supply of 40-channel sets catches up with the demand. Favorable pricing and the realization that the 23-channel radio satisfies the needs of a majority of the people in many parts of the country are the important factors that will keep the 23-channel sets moving, he says. **R-E**

The complete VOM line.

NEW

WV-518B
\$39.95



- All ranges and functions fuse-protected against burnout, (Except 5A ac/dc current ranges)
- Taut-band meter with 30,000 Ω /Vdc sensitivity
- New, modern styling, tilt stand, high-impact case

VIZ makes the industry's most complete line of VOMs.

From our \$9.95 Handyman VOM, all the way to our new \$267.00 3½-digit autopolarity multimeter, VIZ VOMs and VoltOhmysts® are rugged, stable, and designed for long life and top-notch service.

There's a VIZ VOM to fit your need.

See them at your VIZ distributor.

VIZ Test Instruments Group
of VIZ Mfg. Co.

335 E. Price St., Phila. PA 19144

© VIZ

6822

Formerly
VIZ
Instruments

EQUIPMENT REPORTS
continued from page 34

hold the penlight? You don't; you hold it between your teeth just as you always did.)

The model 175 is powered by self-contained rechargeable batteries. All of the very complex "works" are on only two boards, one for the logic, and the other for the display. A proprietary LSI/MOS IC performs all of the logic functions required by the A/D converter. Due to the extensive use of MOS circuitry, the total power consumption is less than 1.0 watt when used with the AC powered battery charger, and 0.6 watt on battery alone. The battery is good for up to 6 hours of normal operation with a full charge, and it can be recharged overnight; 12 hours. When the battery needs charging, the decimal point of the display *blinks* continuously!

The inherent high accuracy of the digital multimeter is taken full advantage of here. On DC volts, the accuracy is 0.1%. On AC volts between 50 Hz and 500 Hz, the accuracy 0.4%. To verify this, a complete set of the final test calibration readings is packed with every instrument. Specification limits are given and the actual test reading logged. On the 1,000 volt range of the one we reviewed, for example, the spec was +998 to +1002 volts. Anywhere between these limits, OK. The actual reading was 1,000 volts. Each instrument is given a burn-in test for 8 hours, and the calibration is then rechecked.

Everything else is automatic. The decimal point is automatically positioned correctly. On all DC measurements the polarity indicator is automatic. As is customary in DMM's, the resistance is read out in 1000 ohms, except for the very lowest range, 100 ohms. Overrange greater than 100% is indicated by a blanked display, leaving only the decimal point and polarity indicator lit.

Overload protection is provided as mentioned. If you accidentally go too far while reading AC or DC currents, they have provided a 2.0-ampere fuse located inside the handle of the red test prod! Just unscrew the black tip and the fuse pops out. Be sure to use only fast-blow type fuses for replacement. A spare fuse and push-on clips are also provided. The whole thing—meter, charger, test leads and all—can be stowed in a handy zipper carrying case.

There is a small pull-out stand on the underside of the case, to raise the front panel to an easier viewing angle. This folds for storage. A very detailed instruction manual comes with each instrument. This gives not only the correct method of operation, but a circuit description, parts lists, calibration data and a schematic with parts layout.

A very useful little instrument, and very reasonably priced for one with this kind of accuracy and reliability. **R-E**

Heath IP2718 Tri-Power Supply

THE HEATH COMPANY HAS INTRODUCED QUITE a range of power supplies for bench and experimental use. A typical example of these is their new IP-2718 "Tri-Power" supply. This supply is intended for general experimental work in either analogue or digital circuitry. TTL and similar devices use a 5-volt DC power supply. The IP-2718 has one:




CIRCLE 50 ON FREE INFORMATION CARD

regulated by an IC voltage regulator that also provides internal protection against overload, short-circuits and high-temperature conditions. Its current or voltage can be read on the panel meter.

For analogue circuits requiring a positive and negative DC voltage, there are two completely isolated 20-volt DC supplies. Each of these has a maximum output of 500 mA and can be continuously varied from 0 to 20 volts by the front-panel controls. Current or voltage in each supply can be read on the meter. These, too, are tightly regulated by transistor voltage regulators. The regulation is specified as less than 0.1% variation from full load to no load. Filtering is good; the maximum ripple level is only .005 V (5.0 millivolts RMS.)

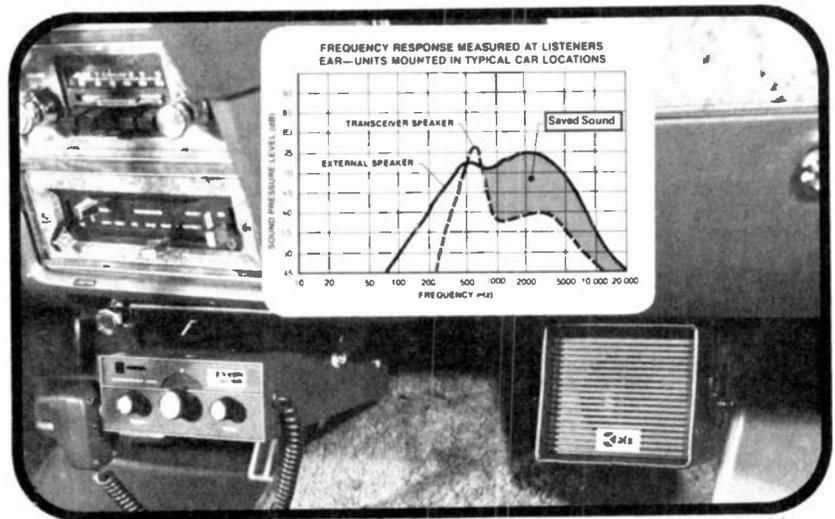All three of the DC supplies (one 5-volt and two 20-volt supplies) are completely isolated from each other and from the instrument ground. They can be tied together in *continued on page 94*



external speakers save lost CB sound

Notice what happens to the high frequencies? You lose them mounting the average CB under the dash. The speaker points down into the floor insulation. Sound is lost. With the addition of an acoustically designed "KRIKET" external speaker, also mounted under the dash but pointing at the driver, the high frequencies come through.

The consonant sounds are in the high frequencies. And they spell the difference between voice intelligibility and just plain noise. That's why you hear remarkably better with a "KRIKET" external speaker. It's the single best accessory you can add to any CB transceiver—23 or 40 channel—to improve enjoyment of it.

Available at CB Dealers everywhere.

afs/Kriket Speakers

World Wide Headquarters
Acoustic Fiber Sound Systems, Inc.
7999 Knue Road Suite 116
Indianapolis, IN 46250
(317) 842-0620

Exclusive Canadian Distributor
Persona Communications L.T.D.
1149 Pioneer Road
Burlington Ontario, Canada
(416) 629-5373

All AFS*/KRIKET® speakers are manufactured in the U.S.A. using American materials and craftsmen.

Copyright 1976 Acoustic Fiber Sound Systems, Inc

NEW—REVOLUTIONARY TOOL

SLIT-N-WRAP

WRAPS
INSULATED WIRE
FOUR TIMES FASTER

NO Prestripping
NO Precutting
Spool Fed Wire

Users say:

"Your P180 tool really does just what you said it would—We're very satisfied."

"We're shifting nearly all our wrapping over to Slit-N-Wrap."

The spooled wire passes thru the tool past a slitting edge next to the wrap post. A narrow longitudinal cut is made in the insulation where it passes the square post corner. The bared copper is indented by the sharp edge. (7 turns equal 28 contacts.) Insulation is slit where wrapped, but not between terminal posts when fed straight out of the tool.


Model P180 with two 100' spools of 28 gage wire \$24.50

Battery powered Model P180-4T includes charger and wire \$75.00

110V Model P160-4T \$80.00



view of unwrapped wire end .025 sq. post

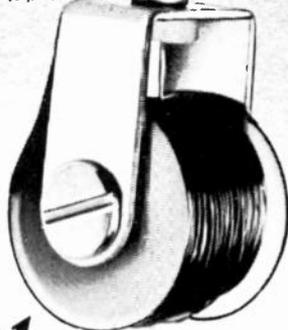

Vector

ELECTRONIC COMPANY
12460 Gladstone Avenue
Sylmar, CA 91342

If unavailable locally, factory order. Add \$2.00 shipping and handling charge.
California residents add 6% sales tax.


491076

CIRCLE 83 ON FREE INFORMATION CARD

new products

More information on new products is available from the manufacturers of items identified by a Free Information number. Free Information Card follows page 108.

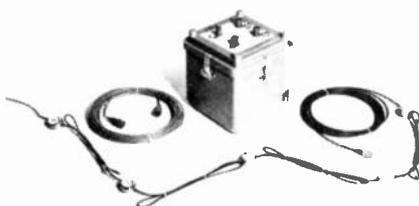INTRUSION DETECTOR, model T-10 buried-line unit protects an area up to 400 feet long and 10 feet wide. It is intended for direct burial in the ground of parking lots, driveways, sidewalks, or



any other surface for total concealment. It can be adjusted so it is not triggered by any weight of less than 50 pounds—Mountain West Alarm Co., 4215 North 16th Street, Phoenix, AZ 85016

CIRCLE 84 ON FREE INFORMATION CARD

WIRE-WRAP TOOL, Hobby Wrap model BW-630, is a battery-powered tool for wire wrapping 30 AWG wire onto standard DIP socket terminals. The tool comes complete with a built-in bit and sleeve for producing the preferred "modified" style wrap. Weighs 11 ounces and



runs on any size "C" batteries. Price—\$34.95—OK Machine And Tool Corp., 3455 Conner St., Bronx, NY 10475

CIRCLE 85 ON FREE INFORMATION CARD

CB SERVICE MONITOR, Measurements model CB-27E is a low-cost instrument for trouble shooting and aligning CB transceivers. Used to check transceiver frequencies and offset from mid-channel frequencies measured by the front panel meter and calibrated against internal frequency standard by zero-beating with the built-in speaker. Additional channels in the 27-MHz spectrum can be added if assigned. When powered with optional NiCad battery, the CB-27E can check the transceiver without removing it from the vehicle. An incremental tuning range of ± 5 kHz is provided for simulated SSB

receiver tests. Features include 455-kHz crystal IF output with modulation and output level control, and provision for two additional intermediate frequencies. Monitor and transmitter



are both protected against overloading if transmitter is accidentally keyed; 1-kHz sinewave AM internal modulation and jack for external modulation covering speech frequencies; built-in transmitter meter. Price—\$495.00—Edison Electronics Div., Dept. 27E, Grenier Field, Manchester, NH 03103

CIRCLE 86 ON FREE INFORMATION CARD

TVI FILTERS. Trapper 45 is a compact low-pass TVI filter designed for average situations, eliminates CB-caused TVI on channels 2 and 5. Attenuation is 45 dB at 54 MHz, and 40 dB at 81 MHz. Trapper 100, super strength, low-pass TVI filter is intended for severe interference prob-




lems. Attenuates 100 dB at 54 MHz, and 75 dB at 81 MHz—Channel Master, Div. of Avnet, Inc., Ellenville, NY 12428

CIRCLE 87 ON FREE INFORMATION CARD

SLIDE MOUNT. Universal key-lock unit, model CBLM-520, safe guards CB radios against theft. It is designed for use with all automobile CB transceivers, and mounts easily under the dashboard or on the floor. Both the mount and radio can be easily unlocked and removed when not in use. The unit comes complete with male and

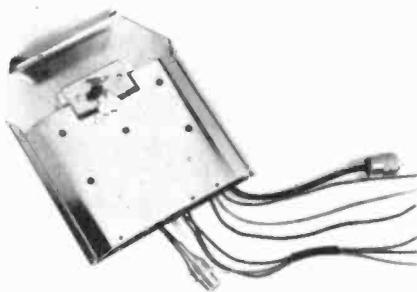female coaxial cable connectors, 3-wires,



mounting hardware, screws, and key. \$14.50—**RMS Electronics, Inc.**, 50 Antin Place, Bronx, NY 10462

CIRCLE 88 ON FREE INFORMATION CARD

CB TRANSCEIVER, *Bobcat 23*, features a ceramic filter, a dual-conversion receiver, an S/RF meter, a front-panel switch to control the




public address system, automatic noise limiter with manual override, solid-state circuitry and

crystals for all 23 CB channels.

Specifications include a power output of 4 watts, 100% modulation, sensitivity of 0.5- μ V for a 10 dB signal-to-noise ratio, frequency tolerance within 0.005% and input voltage of 13.8 VDC positive or negative ground. The unit measures 2 $\frac{3}{16}$ x 5 $\frac{7}{8}$ x 8 $\frac{1}{4}$ -inches and weighs 3 $\frac{1}{2}$ lbs.—**Pearce Simpson**, Division of Gladding Corp., P.O. Box 520800, Biscayne Annex, Miami, FL 33152.

CIRCLE 89 ON FREE INFORMATION CARD

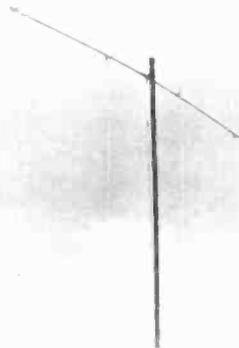CB BEAM ANTENNA. The fiberglass *Mega-Beam style 4104*, resists the harshest environmental conditions, provides a low VSWR over the entire bandwidth. The fiberglass elements



exceed metal in reducing precipitation static.—**The Shakespeare Co.**—Antenna Group, 2805 Millwood Ave., Columbia, SC 29250

CIRCLE 90 ON FREE INFORMATION CARD

MICROCOMPUTER KIT, *model 80A1*. Designed around the Z-80 microprocessor and runs at 2.5 MHz. The board provides a complete microcom-



puter, requiring only a power supply and terminal device, or the 100-pin edge connector may be plugged into an *Altair* or *IMSAI* bus in place of the 8080 based CPU board. The kit form retails for \$450.00 and the assembled unit for \$600.00—**Quay Corp.**, Box 386, Freehold, NJ 07728

CIRCLE 91 ON FREE INFORMATION CARD

"COMPUTERIZED" COLOR TELEVISION SYSTEM, *Model GR-2001* lets you program your entire viewing schedule for two 12 or 24-hour periods, as it automatically switches to the right channel at the right time. If you have an outdoor antenna system you can even program the *GR-2001* to rotate your antenna automatically for best reception on each channel.

Programming is done through a front panel keyboard that lets you select up to 32 channel changes and times during the two 12- or 24-hour periods, in any sequence—VHF to UHF, up or down—without tuning through in-between channels. An on-screen digital readout shows the times and channel numbers as you program them into the set, and flashes the time and

a revolutionary concept in kit building ... THE PROGRAMMABLE CLOCK KIT! \$29.95

SYSTEM 5000 is the first full-feature timepiece available in programmable form. After the circuit has been assembled and tested, all that is necessary is to add the appropriate switches and jumpers to easily program the system for the desired functions. The system may be expanded or reprogrammed at any time.

This represents a revolutionary concept in adaptability and flexibility. Build an Alarm/Clock/Calendar or a full feature Desk or Radio Station clock. Use the DUPLICATE TIME REGISTER to monitor GMT, another time zone or as an elapsed timer. Add the optional relay to control AC or DC accessories. The possibilities are limited only by your imagination.

features

TIME OF DAY REGISTER • DUPLICATE TIME REGISTER • FOUR YEAR CALENDAR • month/day, or day/month format • ALARM WITH SPEAKER TONE OUTPUT • ADDITIONAL ALARM — use for "his and hers" alarm or activate an accessory at a preset time • 10 MINUTE SNOOZE & 10" REMINDER • 3 FUNCTION ALARM OUTPUT SELECT — tone, relay, or relay then tone • ONE HOUR DOWN COUNTER • BRIGHT FLUORESCENT DISPLAY — .5" easy to read digits with AM/PM • AUTOMATIC DISPLAY DIMMING • POWER FAILURE INDICATION • 12 & 24 HOUR DISPLAY • BLINKING OR STEADY COLON • SIMPLE FORWARD AND REVERSE TIME SETTING •

DIRECT DRIVE ELIMINATES RFI • SINGLE 9 VOLT BATTERY BACKUP • DISPLAY SECONDS CONTROL • HOLD AND RESET CONTROLS • 50/60 HZ • 700 WATT RELAY OPTIONAL

SYSTEM 5000 includes all components, 2 time setting switches, and complete assembly and programming manuals. Switches for additional functions and relays are not included but are available as options.

RELAY OPTION — \$4.00

Includes 700 watt relay and all interface components. Will control appliances, stereos, etc.

SWITCH OPTION — \$3.75

Contains 4 black SPST pushbuttons, 2 black DPDT pushbuttons, and 2 black SPST slide switches. Programs all major features.

CASE OPTION — \$11.00

Hard finished, solid walnut cabinet complete with faceplate and rear panel.

Send your check or money order today for fast delivery. Add \$1.00 per clock to cover shipping and insurance. Money back guarantee on all products if not fully satisfied. N.J. residents add 5% sales tax. Use your Master Charge or BankAmericard. Phone orders accepted.

digital concepts

DIGITAL CONCEPTS CORPORATION
249 Route 46, Saddle Brook, N.J. 07662
201/845-7101

add a new dimension to time itself with SERIES 2000 Decorator Clocks



A bright Fluorescent display provides easy to read numbers that brighten and dim automatically according to the light. The clear Acrylic tube with Acrylic or Hardwood end blocks gives these clocks a unique look of simple elegance. AM/PM & power failure indication. Seconds display button. 3" x 3" x 5 1/4". 50/60 HZ.

Specify blue or green display, 12 or 24 hour time, and choice of Hardwood — Walnut, Zebrawood, or Rosewood.

FACTORY ASSEMBLED — 1 YEAR WARRANTY
EC-2001 Solid Acrylic "Time Capsule" \$59.95
EC-2002 Acrylic & Hardwood \$49.95

COMPLETE KITS — 90 DAY WARRANTY
EC-2001-K Solid Acrylic NEW! \$39.95
EC-2002-K Acrylic & Hardwood SPECIAL! \$34.95


CIRCLE 57 ON FREE INFORMATION CARD

Don't Get Caught With Your MODULES DOWN

Increase Your Profits By Utilizing Our Module Rebuilding Program

Consider these features!

- **Original Parts.** We use ONLY original parts. Brands we rebuild include Magnavox, Admiral, GE, Montgomery Ward, Quasar, RCA, Zenith and others.
- **Quality.** Only professionally trained technicians will handle your modules. All modules are tested, temperature cycled, retested and airtested.
- **Protective Packaging.** Rebuilt modules are returned to you in polyethelene skin packaging for protection during shipping and storage.
- **Fast Service.** Quick, reliable service is our tradition.
- **One Year Warranty.** One year limited warranty on workmanship and parts.

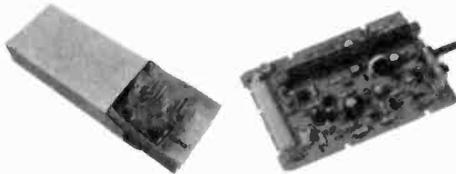

PTS ELECTRONICS, INC.

P.O. Box 272 Bloomington, IN 47401 812-824-9331

OR, check the white pages for the location of the PTS branch nearest you.

CIRCLE 55 ON FREE INFORMATION CARD

channel number whenever the channel changes. Other convenient features include a separate audio IF circuit which provides "hi-fi" quality sound and an audio output jack which



enables you to hook up the GR-2001 to your stereo system. The system is \$849.95 in kit form and can be custom-installed or used with one of five optional furniture-quality cabinets in a variety of styles.—Heath Co., Dept. 350-06, Benton Harbor, MI 49022

CIRCLE 93 ON FREE INFORMATION CARD

ANTENNA TUNER, Model "Back Talk" is said to tune up to four antennas and provide up to four times the talk power. Eliminates transceiver damage caused by excess power feedback, shorts or mismatched antennas. The tuner



tunes the antennas, not the coax. Thus, coax signal radiation is eliminated. The antenna is easily installed and recommended for multi-antenna installations, trucks, mobile homes, base stations. Measures 2 1/4 x 4 3/8 x 3 1/4 inches, weighs 12 ounces and comes with two PL-258 plugs, 9-inch coax and one PL-259 connector. Suggested retail \$49.95—Norcom Electronics Inc., P.O. Box 332, Northfield, OH 44067

CIRCLE 94 ON FREE INFORMATION CARD

PREAMPLIFIER, Model PT-2 is a versatile, base station receiving preamplifier that tunes all ham and CB frequencies from 1.8 MHz through 54 MHz. It is meant to be used with a transceiver and provides full station control. Improves reception of weak signals by boosting sensitivity and signal-to-noise ratio while receiving.



Bypasses itself automatically when the transceiver is transmitting. FET amplifier gives superior cross-modulation protection. Provides master power control for station equipment. \$69.95—Ameco Equipment Co., 275 Hillside Ave., Williston Park, NY 11596 R-E

CIRCLE 95 ON FREE INFORMATION CARD

Car Starting Problems?

- ... Won't Start Because of WEAK BATTERY?
- ... Won't Start Because of COLD WEATHER?
- ... Won't Start Because of WET WEATHER?



Coil Foil

AUTOMATIC STARTING BOOSTER

... is the ANSWER to these Problems!

* GIVES YOU "Sure-Fire" STARTS EVERY TIME...

If your Cold or Weak Battery can turn the Engine over just ONCE... COIL/FOIL will START your Car, even under the worst weather conditions, by Automatically providing a STRONG Spark from its OWN Power Source.



No one in your Family need ever be STRANDED with a Car that WON'T START! No more running the Car Battery "DEAD" trying to start the Car! COIL/FOIL uses its own Power (2-Dry Cell Batteries, not included) ONLY in Starting, and Batteries usually last a Year.

• TESTED and APPROVED by Leading Automotive Magazines and Authorities!

• Comes with... FACTORY WARRANTY. Copy available on written request. ADVANCED ELECTRONICS, N.V., 1625 EYE ST., N.W., Washington, D.C. 20006

• ORDER NOW! ... and never be caught with difficult Starting AGAIN! Install the COIL/FOIL and prove to yourself that it works or your money back.

SPECIAL
Introductory Offer
Only
\$1995



• EASY-TO-INSTALL (only 4-Wires & 2-Bolts). Fits ALL Vehicles with Battery/Coil Systems.

• COIL/FOIL Prolongs Car Battery Life... and reduces wear and tear on Starter-Motor and Ring-Gear.

ADVANCED ELECTRONICS, N.V.
P.O. Box 1579 - RA, 2, Washington, D.C. 20013

Please RUSH _____ COIL/FOIL Units to:

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

• MAKE/YEAR of Vehicle _____
Add \$2 for Postage, Insurance & Handling. Canadian & Foreign Add \$3.

Enclosed: Check, M.O. in amount \$ _____
30-DAY "NO RISK" TRIAL... SATISFACTION GUARANTEED
or Return Unit in 30 days for Full Refund.

CIRCLE 17 ON FREE INFORMATION CARD


CIRCLE 100 ON FREE INFORMATION CARD →

FREE

HEATHKIT CATALOG!

The world's largest selection of superior quality electronic products in money-saving easy-to-build kit form.

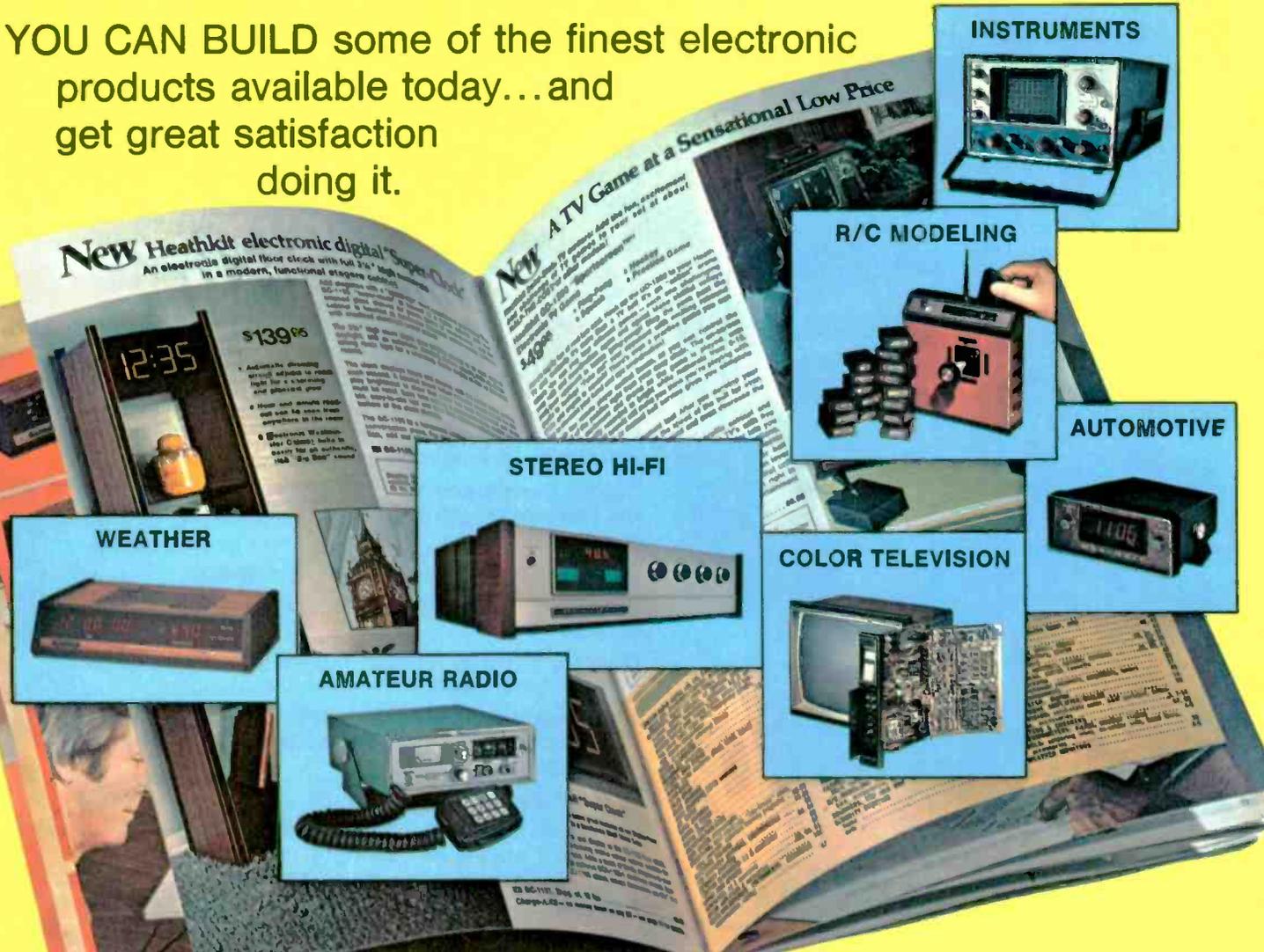YOU CAN BUILD some of the finest electronic products available today...and get great satisfaction doing it.



WEATHER

STEREO HI-FI

AMATEUR RADIO

R/C MODELING

AUTOMOTIVE

COLOR TELEVISION

INSTRUMENTS

FREE!

HEATHKIT CATALOG

Featuring nearly 400 top quality, easy-to-build electronic kits. Stereo hi-fi, color TV, automotive and marine accessories, security systems, short-wave radio and more. PLUS special buys on fully assembled, famous-brand CB radios!

HEATH

Schlumberger

Heath Company, Benton Harbor, Michigan 49022

Please rush me my FREE copy of the new Heathkit Catalog I am not on your mailing list.

Name _____

Address _____

City _____

State _____

Dept. 20-27 _____

Zip _____

Radio Electronics

I'd like to do a favor for a friend—send another catalog to:

Name _____

Address _____

City _____

State _____

Dept. 20-273 _____

Zip _____

CL-623

FREE!

Send for the largest catalog of electronic kits available today.



Discover for yourself the enjoyment that can be experienced when you build one of our many quality kits — all are easy to build with our famous step-by-step assembly manuals.

Kitbuilding is a rewarding pastime that is both creative and satisfying. We have nearly 400 kits for you to choose from in our new FREE catalog.

Stereo Hi-Fi. 2 and 4 channel components, digital and analog tuners, speaker systems, everything for the casual listener or the serious audiophile.

Color TV. From small cart-size portables to a futuristic "computerized" console model with a programmable memory.

Amateur and Shortwave Radio. From Code Practice Oscillators to a Digital Broadbanded SSB Transceiver... everything for beginner or Pro!

Digital Clocks and Weather Instruments. Fun to build kits tell you what's going on...by the numbers!

Radio Control Gear. 3, 4, 5 and 8-channel systems, all with instant plug-in frequency change.

Auto Test Equipment. Keep your car in top shape all year 'round.

Outdoor Fun Kits. Programmable digital stopwatch. Deluxe metal locator/treasure finder.

Test Equipment. Scopes, VTVM's, DMM's, Counters, Generators and Power Supplies for all your test and service needs.

WE WON'T LET YOU FAIL

The world famous Heathkit assembly manual (included with every kit) makes kit assembly easy regardless of whether you're building a color TV or a tabletop lamp dimmer. And technical help, if you need it, is just a phone call away.

PUT STAMP
HERE

The Post Office
will not deliver
mail without postage

HEATH COMPANY

BENTON HARBOR, MI 49022

Send For Your Copy Today!

FREE!

96 pages of fun to build electronic kits...HI-FI, Color TV, Amateur and Shortwave Radio, Digital Clocks and Weather Instruments, Test Equipment, Auto and Marine Accessories, more!

Heath Company, Dept. 10-27
Benton Harbor, Michigan 49022

When you've got a pace,
you've got the world by the ears.

AMAZING!
WORLD'S BEST
CONTRIBUTOR



WE DON'T PROMISE. WE DELIVER.

AS A DEALER, YOU PROBABLY KNOW THAT MOST DISTRIBUTORS CLAIM TO BE "THE BEST". AND YOU'RE PROBABLY GETTING A LITTLE TIRED OF PROMISES THAT REMAIN JUST THAT. PROMISES.

AT BENNIES WE'VE BUILT A NATIONAL REPUTATION AS A DISTRIBUTOR YOU CAN COUNT ON. AND WE'VE DONE IT WITH HARD WORK. NOT WITH PROMISES.

WE DELIVER WITH FAST, COURTEOUS SERVICE, A MULTI-MILLION DOLLAR INVENTORY OF THE CB INDUSTRIES TOP BRAND PRODUCTS, AND WEEKLY PROFIT BUILDING SPECIALS YOU HAVE TO SEE TO BELIEVE.

JUST SEND \$5.00 (DEDUCTIBLE FROM YOUR FIRST ORDER IF MADE WITHIN 90 DAYS) AND YOUR TAX NUMBER FOR OUR GIANT NEW 248 PAGE CATALOG, AND LET US GO TO WORK FOR YOU. SORRY, CATALOG OFFER IS AVAILABLE TO DEALERS ONLY.

**FOR THE COMPLETE LINE OF PACE
40 CHANNEL CITIZENS BAND RADIOS CONTACT**
Serving Quality-Conscious Dealers and Distributors Coast to Coast



BENNIES

**WAREHOUSE DISTRIBUTION CENTER
R.D.1 BERWICK, PA. 18603 717-759-2201**

*** PUT THE "IGNITION OF THE FUTURE" ON YOUR CAR TODAY!**

MODERNIZE and Bring Your Car "UP-TO-DATE" with the MOST EFFICIENT Ignition ever invented!

*** End "Tune-Up" Problems FOREVER** caused by Points and Condenser



U.S. Patents Pending

ALLISON XR-700

with the Exclusive...Solid-State Voltage Regulator.

The ONLY Ignition System that has COMPLETELY overcome the Problems that have baffled the Auto Industry for Years!

SO RELIABLE (99.9+%)... SO PERFECTED... that it will soon be STANDARD on most Future new Cars!

ALLISON Rated #1 by Official Testing Laboratory as the BEST "Fuel Saving" Ignition System of ALL the Different Ignition Systems Tested!

* The "XR-700" is a COMPLETELY NEW Ignition System employing the Most Advanced Technology, that replaces the inefficient Points and Condenser with an infrared Light Beam to Trigger the Latest type of Solid-State Power Components. Once installed... "XR-700" has NO moving Parts to wear out or adjust. It works without Friction or wear. Not affected by Dirt, Oil, Moisture, Vibration or extreme Engine Temperatures! **RUGGED and RELIABLE!**

* The "XR-700" is engineered to OUTLAST YOUR CAR!

* The "XR-700" produces the MAXIMUM "High Energy" Long Duration Spark... from your present car's Ignition Coil. This permits the Positive Firing of Spark Plugs, even under the most Adverse conditions. Also, Eliminates "Engine Misfire," resulting in more COMPLETE COMBUSTION! Thus you get IMPROVED Fuel Mileage, a HIGHER Performance Level... keeps Plugs FROM FOULING and gives LONGER Plug Life!

Customers Report:

- ★ **"IT MORE THAN PAYS FOR ITSELF!"**
- ★ INCREASES Gas Mileage up to 30%!
- ★ SAVES Money on Costly "Tune-Ups"!
- ★ Gives Continuous PEAK Performance!
- ★ QUICKER Starting in Any Weather!
- ★ Smoother Running... Faster Acceleration!
- ★ Plugs Last Up to 4-Times LONGER!"

* Reliability PROVEN in Millions of Customer Miles to be so exceptionally GOOD... that every "XR-700" has a LIFETIME WARRANTY! FREE Repair or Replacement for as long as you OWN the Unit!... and even if you CHANGE Cars, Allison will supply you the necessary PARTS to fit ANY Point-Type Distributor... FREE! (Include \$2 for Postage & Handling).

* FITS ALL CARS, Domestic & Foreign, 4, 6 or 8-Cylinder.

★ **DO-IT-YOURSELF... EASY INSTALLATION!** The New "XR-700" is Completely Factory Assembled... Thoroughly TESTED! New Precision "Drop-in" Mounting Bracket, with color-coded, "Snap-together" wire connections No Distributor Removal necessary Protected Against Incorrect Hook-up!

● Thousands sold at \$59.95 ● ONLY **\$39.95** COMPLETE (Cal. Res. add Tax) NOW! Allison's Production Technology offers you the same Premium Quality XR-700 at this SPECIAL LOW Price... THAT'S EVERYTHING... INCLUDING POSTAGE & INSURANCE

★ **ORDER WITH CONFIDENCE...** install the "XR-700", and prove to your own SATISFACTION that it is as advertised, or return it within 30 days for a FULL Refund of the Purchase Price

* **SAVE! ORDER FACTORY DIRECT.** Send Check or M.D., State Car Make, Year, No. Cylinders

* MASTER CHARGE or BANKAMERICARD Card Holders: ORDER by TOLL-FREE PHONE. (800) 423-6525, Ext. 2 or Send us (1) Your Number, (2) Interbank No., (3) Exp. Date.

* **SEND FOR FREE BROCHURE and Comparison Sheet.**

"CB" USERS: The "XR-700" completely ELIMINATES the Major Cause of Primary (Ignition Noise) Interference.

* If you have already installed a "Capacitive Discharge" Ignition
 * Convert your "C.D." Unit to BREAKERLESS!
 INCREASE ITS EFFICIENCY with "XR-CD"...only \$29.95

* America's Oldest and Largest Manufacturer of Opto-Electronic Ignition Systems. ©

ALLISON AUTOMOTIVE CO.

1267 - RA, East EDNA PL., COVINA, CAL. 91722

CIRCLE 22 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 87

series for higher voltage, or in parallel for a higher current rating. So, for the 20-volt supplies, you could have a +40-volt supply at 500 mA., a 20 volt supply at 1.0 amp or, by connecting in series and using the center tap as common, a \pm 20-volt supply for CMOS and similar equipment. Voltage and current can be read in each "channel" with the selector switch for the meter.

All three supplies are current-limited at a point slightly above the maximum rated output, for protection against accidental shorts in the load.

A novel circuit is used with the two 20-volt supplies that allows the two supplies to operate either independently or to track each other. A selector switch is used for this purpose. In the INDEPENDENT position, the controls can be used to adjust the A or B supplies to any voltage between 0 and 20 volts. There is no interaction—each one is isolated from the other. If you want to make one supply "track" the other at a preset difference, move the switch to the TRACKING position. The control for the B supply is a dual concentric-type with a small red inner knob. To get a preset difference, say the B supply 5-volts greater than the A supply, set the switch to TRACKING and move the meter switch to read the voltage of A. Set the red knob to make this read say 10 volts. (You must hold the black outer knob to do this; this is intentional!) Now move the meter switch to read the voltage of the B supply and adjust the black control knob for the B supply to make the voltage read 15 volts. From this point on, both voltages will increase or decrease in step; the tracking error is claimed to be only 1%.

In the TRACKING position, the A control is disconnected; the red inner knob of the dual control sets A voltage. In the INDEPENDENT position, the red knob is disconnected and only the A control adjusts the A voltage. This is not as complicated as it sounds; in operation it's very easy!

The IP-2718 is available in kit form, with the customary excellently-detailed Heathkit construction manual that tells you in detail just what to put where. It can also be purchased in fully assembled and tested form. For the serious experimenter, the versatility of this power supply will make things a lot easier. It has all of the necessary protective circuits to save the day in case of problems. It's easy to use; the terminals will accept banana plugs, terminal lugs or even old fashioned pieces of bare wire in emergencies. A very handy little instrument, that occupies only a little space on the bench.

R-E

Switchcraft Q-Chek QC-1002 Cable Tester

THE SWITCHCRAFT COMPANY HAS LONG BEEN known for their comprehensive line of plugs, jacks, switches and many more useful things. Now they have brought out a very handy piece of specialized test equipment. This is the Q-Chek model QC-1002 audio cable tester. (One suspects that this is a refinement of a production-line quality control test unit! It would be admirably suited for this.) It's a



CIRCLE 82 ON FREE INFORMATION CARD

portable unit that will quickly check out practically all types of cables and plugs used in audio work. The unit is very compact, and battery-powered so that it can be used anywhere.

The QC-1002 will check any kind of audio cable with up to 5 conductors plus a shield, for opens, shorts or even mis-wiring. The panel of the Q-Chek has eleven sets of jacks, divided into two sections and coded for fast identification. These are all numbered in pairs. The connectors range all the way from the miniature phone jacks up to the 5-pin DIN plugs used on many tape recorders, etc.

Testing is pretty simple; even I can do it. You plug one end of the cable into a matching jack in the INPUT section on the left, and the other end into the matching jack on the OUTPUT section. There are six pushbuttons across the bottom of the panel. All you do is push one button for each conductor in the cable. Start with the one marked COM; this checks the shield for continuity. If it's good, the pushbutton lights up. If cable one has three conductors, depress the pushbuttons marked 1, 2 and 3. If they all light, the cable is good.

For finding an intermittent connection, just hold the pushbutton down and bend the cable back and forth. If the light blinks, you've found it. If you have a job that calls for making up a number of multi-lead cables, testing them is a breeze. It will catch any mis-wired plugs. If you push button 3 and button 2 lights up, something is wrong. If pushing 2 makes both 2 and 3 light, you have a short between these two leads or a jumper in the plug, which they warn you about in the instructions.)

If you run into a cable with a plug not included on the panel, the company has adapters available that will convert them to types which can be tested. If the cable has a male plug on one end a female on the other, conversion adapters for this are also on hand. The Switchcraft catalogue No. A-404D lists a great many of these adapters. In the lid of the Q-Chek's case, spring clips are provided for holding up to 18 adapters.

If you do audio work, this unit can save a great deal of time and trouble. In specialized work such as language labs, that are now showing up in high schools as well as colleges, you may have to check a great number of cables. This unit will do it. The model QC1002 comes complete with carrying case, instructions, 9-volt battery and seven separate audio adapters; and is priced at \$186.00.

R-E

Electronic-communications contributors honored

The Radio Club of America, at its annual meeting and banquet in New York City last November, awarded its Armstrong Medal to Captain Wm. G.H. Finch, USN, retired, "for significant contributions to radio art and science." Captain Finch is the holder of more than 180 patents on facsimile, teleprinting and kindred subjects.

The Club's Sarnoff Citation, "for important contributions in electronic communications," was awarded to Fred Link, pioneer in mobile two-way radio communication and founder of Link Radio. A special Pioneer Award was presented to Harold Beverage for his early developments of the Beverage antenna and diversity reception; and Morgan McMahon, publisher of the Vintage Radio books, received the Ralph Batcher Memorial Award for his and his wife's work in preserving the history of radio.

Twenty-five members were elevated to the grade of Fellow in the Club. These included such well known figures as Lewis A. Bondon, founder and president of Prodelin, Inc.; Thomas A. Campobasso, vice president of the international sales division, Collins Radio; Francis T. Cassidy, Jr., general manager of ITT domestic communications operations; Richard E. Horner, president of E.F. Johnson Co.; Samuel McConoughey, chief of the mobile services division, FCC; R.D. Mignault, president of Pye Electronics, Canada; Charles E. Summers, manager, IBM private radio services; and William J. Weisz, president, Motorola, Inc.

The Radio Club of America, the world's oldest radio communications society, was founded in 1909, and has about 670 active members.

National Service Managers elect O'Shanna president

Robert J. O'Shanna, director of service of the Alemite Instrument Div., Stewart-Warner Corp., was elected president of the National Association of Service Managers at their annual conference last October. Mr. O'Shanna has held several offices in the Association, and as a member of the Education Committee, has been instrumental in having service management seminars set up at the University of Wisconsin and at Syracuse University in New York.

Edwin L. Penar, national service manager of Dole Refrigerating Co., Lewisburg, TN, was elected vice president. James Britton, service manager, Hartford Div., Stanadyne, Inc., of Hartford, CN, was named second vice president. Charles K. Lins, director of area service for Bell and Howell in Dallas, was named secretary, and William P. Zabler, Sears, Roebuck national service manager, was named treasurer.

Five-year warranty for new Sylvania picture tubes

GTE-Sylvania Color Bright 85 picture tubes are now being sold with a five-year limited warranty. Sylvania is said to be the first manufacturer to offer a limited warranty of this extent on any grade of TV tube.

R-E



LEADER LCG-396

VTR PROBLEM SOLVER

The New NTSC Color Bar Pattern Generator
Designed For The Newest VTR Systems!

- Provides all signals necessary to precisely time, test, evaluate and judge all standard NTSC, MATV, CATV, color and b&w video
- Synchronization intensity and chroma signals variable by 20% to extend use into R&D and broadcast areas
- Generates 8 fixed color bars, dot, crosshatch, centerline signal, white raster and red raster.
- Adjustable scanning control permits progressive and interlaced scanning checks
- Utilizes digital integrated circuitry and includes composite video output with 2 switch selectable channels
- Particularly useful for testing servicing and maintaining the newest VTR systems

At under \$900 it's far less than competitive testers.

LEADER
Instruments Corp.

Tests More... Tests Better... for Less!

151 Dupont Street, Plainview, N.Y. 11803 (516) 822-9300
West Coast: 7733 Densmore Ave. Van Nuys, Calif. 91406 (213) 989-2782 In Canada: Omnitron Ltd. Montreal, Quebec

CIRCLE 27 ON FREE INFORMATION CARD

You'll lose money

IF YOU DON'T ATTEND
NESDA'S 1 DAY

PROFITABLE
SERVICE
MANAGEMENT SCHOOL

Thousands of struggling servicers have discovered how to make more money and gain control of their businesses by attending NESDA PSM Schools.

PSM Schools will be held on Sundays, preceding the Forest Belt Training Workshops in major cities around the country from February thru August. Write for info: NESDA, 1715 Expo Lane, Indianapolis, IN 46224

CIRCLE 81 ON FREE INFORMATION CARD

PAIA

WE'RE FAMOUS FOR OUR
SYNTHESIZERS

but did you know we also have


"OZ" MINI-ORGAN, PHLANGER, ARTICULATORS (FOR "TALKING" GUITAR), COMPUTER MUSIC INTERFACES, PROGRAMMABLE RHYTHM UNITS, ENCEPHALO GRATIFICATION GENERATOR (EGG), COMPUTER BASED MUSIC SYNTHESIS SYSTEMS, PLUS

"POLYPHONY" THE MAGAZINE FOR THE ELECTRONIC MUSIC ENTHUSIAST. . . . AND MORE IN OUR FREE CATALOG

PAIA ELECTRONICS DEPT. 3-R
BOX 14359, OKLAHOMA CITY, OK 73114

CIRCLE 3 ON FREE INFORMATION CARD

NEW! D.V.M. KIT

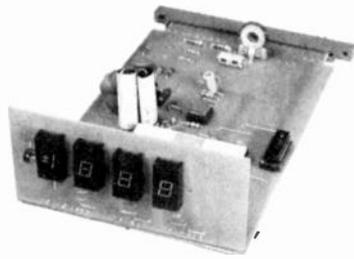

Convertible into Multimeter

KIT FEATURES BASIC 2 RANGE D.V.M. ACCURATE TO 1%. CIRCUITS FOR ADDITIONAL VOLTAGE RANGES, OHMS, D.C. CURRENT, AND A.C. VOLTS CAN BE ADDED. PARTS MOUNT ON EDGE CARD CONNECTOR P.C. BOARD. DISPLAY BOARD HAS EASY TO READ 1/3" LED'S AND CAN BE REMOTE MOUNTED.

KIT CONTAINS • 2 P.C. Boards • Signal Converter • Digital Processor • Op. Amp • Inverter • 3-Drivers • 4-LED Displays •

Basic D.V.M. Kit \$39.90
(POWER SUPPLY NOT INCLUDED)

Send Check Or Money Order. Add \$1 for Postage and Handling in U.S. N.J. Residents Add 5% Tax.

J. B. Electronics Inc.
Box 321
Short Hills, N.J. 07078

CIRCLE 43 ON FREE INFORMATION CARD

TOMORROW'S HI-FI GEAR

continued from page 42

channel of audio power at approximately 0.1% total harmonic distortion while remaining comfortably cool to the touch. Figure 10 illustrates the output stage dissipation of the PWM amplifier

the PWM approach only at maximum output, but since peak conditions (under musical listening conditions) are attained only for short periods of the total listening time, the PWM amplifier is seen to offer increased average efficiency or much lower average dissipation when used for music reproduction purposes.

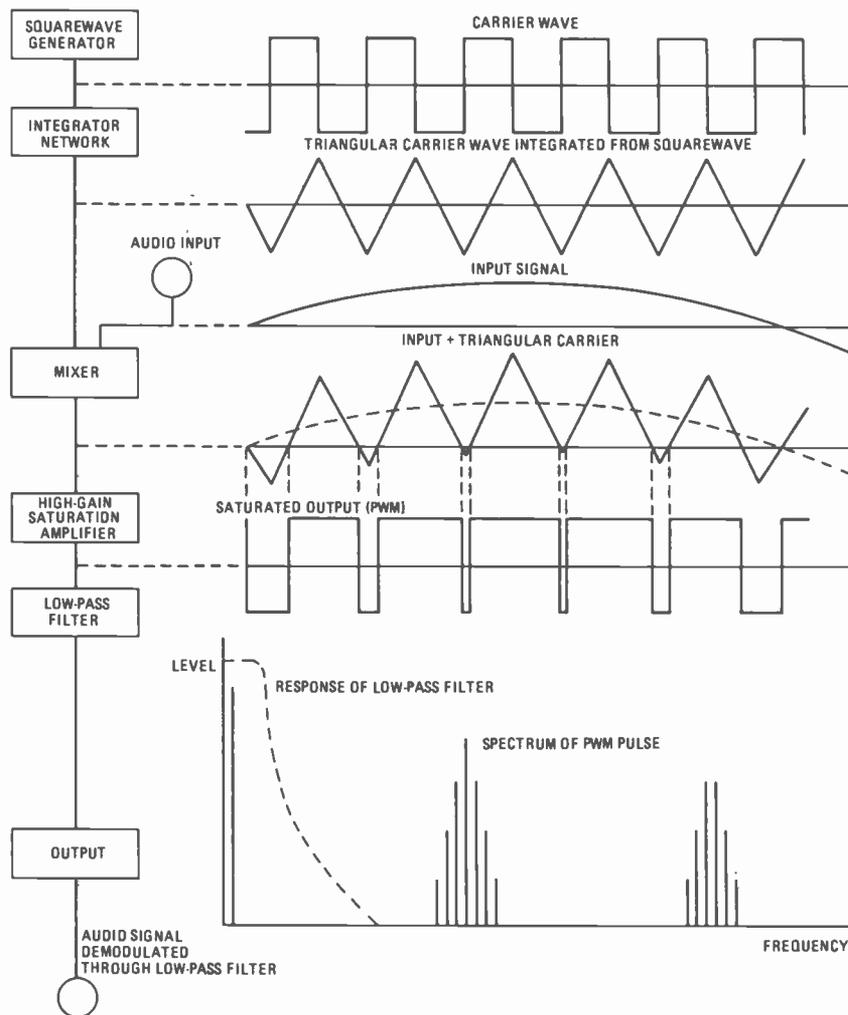


FIG. 9—WAVEFORMS at each stage of the PWM amplifier.

as compared with that of a conventional Class-B amplifier, each expressed or

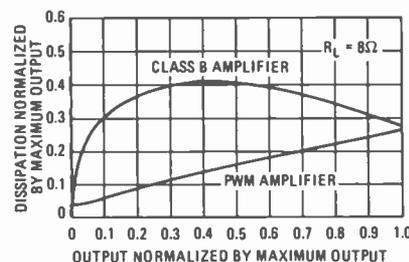


FIG. 10—POWER DISSIPATION of the PWM amplifier versus the conventional Class-B.

normalized in terms of maximum rated output. From this plot we see that the efficiency of the PWM amplifier is much higher than that of a Class-B amplifier operating in its ideal conditions over most of its power range. Class-B efficiency approaches that of

These are but a few of the innovative product ideas and circuit developments that I saw on opposite sides of the world and they suggest that the state of the audio art is hardly dormant. At that, we have only been able to skim the surface of the technology involved in each of these devices or products. As each reaches commercial reality in the marketplace, we hope to explore them in greater depth—either by devoting a full article to each, or by testing and reporting upon the resulting products themselves in future test reports. R-E

Polaris

40 KV

DUAL RANGE

Probe

Current & Voltage Reading
For Today...
And Tomorrow!

MODEL 651 **\$29⁹⁵**

RANGE NO. 1: 40,000 VOLTS DC
RANGE NO. 2: 0-400 MA DC

Send literature and name of my distributor.

Polaris New York
2849 FULTON STREET
BROOKLYN, N.Y. 11207

Name _____
Address _____
City _____ State _____
Zip _____

HIGH BLOOD PRESSURE.

Treat it...and live.

The National High Blood Pressure Education Program,
U.S. Department of Health, Education, and Welfare.

GET RID OF RFI
continued from page 46

manufacturers and are available from most electronic supply houses, especially those dealing in industrial electronic components. Because physical size is important, miniature or subminiature coils should be used. Capacitors should be disc ceramic types, of the HiK or TC type, and their size must be small, too.

Some final suggestions

If interference is known to originate from CB equipment, it might be a good idea to borrow a CB rig (unless you already own one) and operate it near the audio equipment while trying to cure the problem. By so doing, you won't have to wait for the interfering signal to come "on the air" to ascertain whether your attempts at a cure have been successful. If you are successful, record what parts you added to your equipment by adding them to the schematic diagram of your hi-fi component.

Remember, it is not always possible to cure RFI problems completely. In many cases only a reduction of interference may be possible, despite your best efforts, but reducing the problem is better than no solution at all. We know of at least one case in which just about all of the solutions we have outlined were attempted with no success. The listener was located directly across the street from a local FM transmitter tower. This frustrated audiophile had just about given up, and loved his hi-fi music enough to move to another location. Having disassembled his hi-fi in preparation for the move, he had stored all the components in his bedroom, which faced another exposure, away from the transmitter tower. Before packing the gear in shipping cartons, he decided to hook the units up for one last listen and, you guessed, the RFI was gone!

R-E




"Now that you've built your TV Typewriter, your minicomputer, your digital clock, and your CB transmitter, do you think you're ready to tackle a broken toaster?"

In any hi-fi system, the one component most likely to wear out is the phono cartridge. Or more specifically, the phono stylus.

While you're relaxing to your favorite music, the stylus is riding miles of groove, withstanding accelerations that would black out an astronaut.

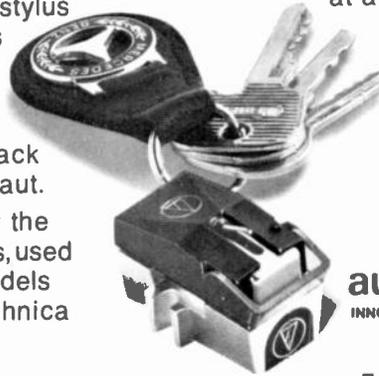Which is why the Shibata stylus, used on the top models of Audio-Technica



cartridges, is so important. Its shape reduces tracking pressure at any given tracking force. Even with a setting as high as 2 grams it will outlast an elliptical stylus tracking at a fraction of a gram. Which means the good sound of Audio-Technica lasts longer. And so do your records.


Audio-Technica with a Shibata stylus: lower cost per record/mile and better sound in the bargain!

audio-technica 
INNOVATION / PRECISION / INTEGRITY

When you shop for better sound ask about good mileage!

AUDIO-TECHNICA U.S., INC., Dept. 37E, 33 Shiawassee Ave., Fairlawn, Ohio 44313
Available in Canada from Superior Electronics, Inc.

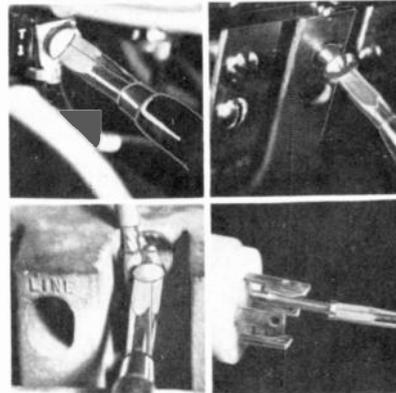Use Quick-Wedge to install a bus, connect a motor, mount a p.c. board, cinch up a connector



They do all that ordinary screwdrivers do, PLUS they hold and start the screw



QUICK-WEDGE 17 sizes
Screw-holding screwdrivers
Unconditionally guaranteed.
BUY A SET TODAY

See your dealer or write to:
Kedman Company, P.O. Box 25667,
Salt Lake City, Utah 84125

© Copyright 1977

CIRCLE 80 ON FREE INFORMATION CARD

"My father built this Schober Organ for me!"



You'd be proud to buy her an organ this good... but how would you feel if you'd also built it? It's a special kind of satisfaction. The gift of a lifetime of magnificent music, crafted with your own hands!

And you can do it! You need no prior electronic or mechanical abilities. Just the capacity to follow instructions. Every step is clearly detailed, every component is supplied. You'll find the assembly process as enjoyable as the music which follows!

And what music! For this is a truly fine instrument you will build. Far superior to most "ready-made" organs... easily comparable to others at twice the price. Kit costs range from \$650 to \$2850 for all basic components, and you can purchase it in sections to spread costs out... or have two-year time payments.

Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see the quality of Schober).

The Schober Organ Corp., Dept. RE-100
43 West 61st Street, New York, N.Y. 10023

Please send me Schober Organ Catalog.
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.


NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CIRCLE 32 ON FREE INFORMATION CARD

MARCH 1977

Nothing is Faster and Easier than ACE for circuit breadboarding.

Used to be you'd get a circuit idea, lay out a pc board, print it, solder everything together, troubleshoot, change your layout, try a new board, and spend absolutely too much time breadboarding. Now A P ACE All Circuit Evaluators let you breadboard in a fraction of the time. Make your changes immediately. Keep full leads on your components. Avoid the heat damage possible with repeated soldering and desoldering. And have a pattern for your board—if you need a board—sitting in front of you. In about as long as it takes to sketch a schematic. Get cooking with ACE. ACE. The All Circuit Evaluator from A P Products.

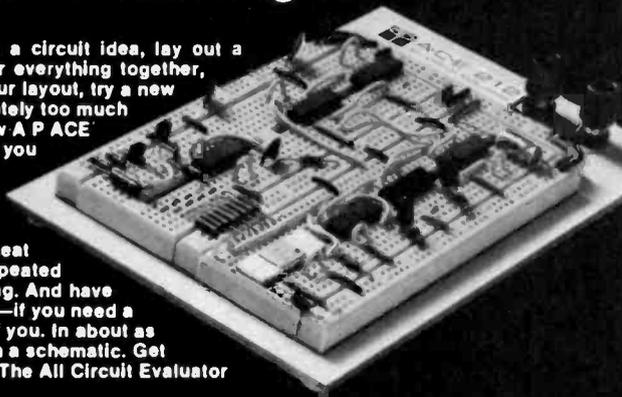

Part No.	ACE Model No.	Tie Points	DIP Capacity	No. Buses.	No. Posts	Board Size (inches)	Price Each
923333	200-K (kit)	728	8 (16's)	2	2	4.9/16x5-9/16	\$18.95
923332	208 (assem.)	872	8 (16's)	8	2	4.9/16x5-9/16	28.95
923334	201-K (kit)	1032	12 (14's)	2	2	4.9/16x7	24.95
923331	212 (assem.)	1224	12 (14's)	8	2	4.9/16x7	34.95
923326	218 (assem.)	1760	18 (14's)	10	2	6-1/2x7-1/8	46.95
923325	227 (assem.)	2712	27 (14's)	28	4	8x9-1/4	59.95
923324	236 (assem.)	3648	36 (14's)	36	4	10-1/4x9-1/4	79.95

Order from your A P distributor today.
Our distributor list is growing daily.
For the name of the distributor nearest you
call Toll-Free 800-321-9668.




Send for our complete A P catalog,
The Faster and Easier Book.

A P PRODUCTS INCORPORATED

Box 110-R Painesville, OH 44077 (216) 354-2101 TWX: 810-425-2250

CIRCLE 7 ON FREE INFORMATION CARD

★ **FREE!** ★

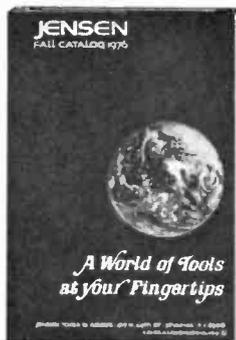

NEW CATALOG OF HARD-TO-FIND PRECISION TOOLS

Jensen's new 128-page catalog is jam-packed with more than 2800 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, instrument mechanics, schools, laboratories and government agencies. This wanted catalog also contains Jensen's world-famous line of more than 40 tool kits. Plus 10 pages of useful "Tool Tips" to aid in tool selection. Send for your free copy today!

JENSEN TOOLS and ALLOYS
4117 N. 44th Street, Phoenix, Arizona 85018

A BLISS & LAUGHLIN Industry

CIRCLE 12 ON FREE INFORMATION CARD

FREE catalog
over 2000



unique tools,
handy kits,
precision
instruments,
technical
supplies.

Over 24 years of service to the world's finest
craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.



National Camera
2000 West Union Ave., Dept. GBA
Englewood, Colorado 80110
(303) 789-1893

CIRCLE 2 ON FREE INFORMATION CARD

ACTION FOOTBALL

continued from page 68

to reach, or go beyond, the goal line. The same holds true for a field goal attempt. If a field goal falls short, the ball is taken by the opposing player at his 20-yard line. If either a field goal or a punt is blocked, the opposing player takes possession at the line of scrimmage.

If the ball is fumbled, the play selector is moved to FUMBLE on the chart and the buttons are activated to see if the offensive team retains possession or not. If the result is LOSE, the opposing player takes over at the line of scrimmage. If it is KEEP, the offensive player loses the down but continues to play.

A pass can be complete with the yardage indicated, incomplete with no yardage or intercepted. If it is intercepted, the ball is first advanced to the point of interception according to the yardage shown in the chart. Then, the play selector is moved to INT RUNBACK and the buttons are actuated to determine how many yards the opposing player runs back the interception. If the intercepting player fumbles on the runback, the fumble play is used to tell whether he keeps possession at the point of interception, or loses the ball. If there is pass interference, the offensive team gets a first down at the point of the interference, which is indicated by the yardage shown on the chart.

As in actual football scoring, touch-downs count six points, field goals three and extra points one. Conversion attempts are determined by using the extra-point play to see if the kick is good or no good. You can, of course, vary the rules as you wish. You might decide, for instance, to permit two-point conversions.

Quarters can be determined by setting a kitchen timer to an agreed-on period or by limiting each player to a certain number of plays, say 16 or 20. In this case, only actual plays from scrimmage count. Kickoffs, kick returns, interception runbacks and conversion attempts are not included. At the start of the second half, the player who kicked off at the beginning of the game now receives the ball.

R-E

Your contribution

helps make tomorrow
better than today
for the handicapped.

Give to

Easter Seals



for crippled
children
and adults

DIGITAL CLOCKS
continued from page 57

seconds. When this switch is closed, the FAST switch becomes ZERO SECONDS AND HOLD and the SLOW switch becomes HOLD COUNT. If all three of these switches are closed at the same time, the display changes to 12:00 AM. This peculiar "programming" allows you to make any of these modules into a 24-hour "stopclock" that will count and display by the second, and can even be controlled and reset remotely! To do this, use toggle or slide switches instead of pushbutton switches. Hint: Small toggle switches will mount in the same 1/4-inch diameter hole as miniature pushbutton switches.

The ALARM DISPLAY switch is also used as the SNOOZE switch. When this switch is closed, the alarm time is displayed, and is advanced by the FAST and SLOW switches to the desired time. (Be careful that you don't overlook AM or PM designation, or your alarm will be 12 hours off!). With the ALARM ON switch closed, when the real time matches the alarm-set time, the alarm will sound. By pressing the ALARM DISPLAY/SNOOZE switch, the alarm will stop for 9 minutes, then go on again. This can be repeated for up to one hour from the original alarm time. Of course, the ALARM OFF switch disables the alarm at any time. If this switch is turned off when the alarm sounds, and then turned right back on again, the alarm will automatically go on again in 24 hours! In other words, you can set the alarm for the next day when you get up, instead of before going to sleep . . . when you might forget.

Although all these modules are able to turn a radio on and off automatically, this requires a SLEEP TIMER display switch (shown in the wiring diagram, and included in the kit offered in the parts list), a MODE selector switch, and, in the case of the National modules, external driving circuitry. Also, because of the power requirements, this could mean a different power transformer, and you would need specific information on the radio circuit requirements. Therefore, these applications are not covered in this article. Although each of these modules is a versatile "brain" about which a lot more could be written, the main features and uses are covered. If you want more specific information, contact National Semiconductor Corp. (2900 Semiconductor Drive, Santa Clara, CA 95051), Fairchild Semiconductor Consumer Products Group (4001 Miranda Ave., Palo Alto, CA 94304) or Interfab Corp. (See parts list). R-E

THE UNFINISHED JOB

I asked you for some ideas on why I had several odd symptoms in an RCA CTC-38. You said "Check the electrolytic filter capacitors for any sign of signal." I did, and found that it was the one you said, on the + 140 volt line! However, the filter capacitor itself wasn't bad. It had been replaced but whoever did it just forgot to solder the lugs of the can to the chassis! Fixing this up stopped all the trouble. Thanks very much.—H.Y., Martinez, GA.

The moral of this is "Don't stop working on the a job until you're through!")

HALF A PICTURE MISSING!

I've got a real screwball in this Zenith 19EC45. The top half of the picture is perfect; no compression, no stretch. The whole bottom half is gone. It's just black! What the heck is this?—J.G., Crystal Springs, AR.

Real simple *after* you find out what it is! This set has an OTL (Output Transformer Less) two-transistor vertical output stage with dual-polarity DC power supply. (Just like the OTL circuits you find in transistor stereo amps, and so on.) So, there are two output transistors. Each one scans one half of the screen. If one should open or develop a bad contact in the socket, this is the reaction you'll see. If you lost the bottom half, go and check Q708. This is the transistor in the middle of the heat sink. That's it.

■ MATHEMATICS ■ ELECTRONICS
■ ENGINEERING MATHEMATICS
■ ADVANCED MATHEMATICS
■ ADVANCED ENGINEERING MATHEMATICS

These unusual courses are the result of many years of research and teaching by the President of INDIANA HOME STUDY INSTITUTE, who has *personally* lectured in the classroom to *thousands* from all walks of life on mathematics, electrical and electronic engineering.

- You must see these lessons to appreciate them!
- NOW you can master mathematics and electronics and actually *enjoy* doing it!
- WE ARE THIS SURE:—you order your lessons on a *money-back guarantee*.

WRITE TODAY for more information and your outline of courses. You have everything to gain and nothing to lose!

LICENSED BY THE STATE BOARD OF INDEPENDENT POST-SECONDARY VOCATIONAL, TECHNICAL, TRADE AND BUSINESS SCHOOLS.

THE INDIANA HOME STUDY INSTITUTE
EASTERN DIVISION
P.O. BOX 1189
PANAMA CITY, FLA. 32401

CIRCLE 31 ON FREE INFORMATION CARD

EIGHT INSTRUMENTS IN ONE



- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Transistor Analyzer Model 212
Factory Wired & Tested—\$28.24
Easy-to-Assemble Kit—\$19.21

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:
Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.
Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

NAME _____ RE-3

ADDRESS _____

CITY _____ ZONE _____ STATE _____


EMC

ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N. Y. 10012

FOR FAST TROUBLE-SHOOTING

"FERRET"

TV MINI-ANALYZER

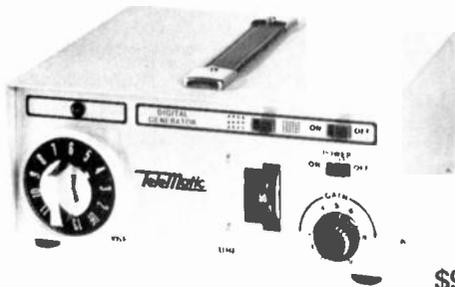

\$99.95

SG-785

- VHF/UHF Subber
- I.F. - Video Troubleshooter
- Convergence Generator
- Dots and Cross-Hatch Patterns

The "FERRET" is a multi-functional instrument for fast, efficient trouble-shooting and adjustment of all Color and B&W tvs. It is ideal for both shop and field work. (Cables included.)

TeleMatic 2849 Fulton St., Brooklyn, N.Y. 11207

Please send more information.

R3

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____

SOLD THROUGH DISTRIBUTORS ONLY
 CIRCLE 52 ON FREE INFORMATION CARD

DISTORTION

The right channel sounds awful in this Truetone 4DC6325. Left channel OK. The scope shows a funny waveform in the right channel with a sine wave on the input. (See diagram.) I pulled



both transistors in that channel, checked them out of circuit and they were good! Help!—MDO, Ink., AR.


The output stages in this amplifier use small thermistors in the bias networks. It's very likely that one of these has been shorted out by a solder bridge! This has happened to me. Check the resistance across the terminals of each; should be a about 22 ohms. The waveform you drew shows a very bad case of crossover distortion and bad transistors are one cause of this: so, your test was correct.

VERTICAL RETRACE

I wrote you some time ago about a vertical retrace problem in a Sears TV set. I checked everything you suggested. Still had 'em. Finally, in desperation, I moved the vertical centering control. This raised the raster so that the retrace was hidden! I figured that I'd lose too much of the picture, so I ran the setup adjustment on the vertical size, linearity and shape controls. Much to my surprise, I found that I had a perfect raster—full, linear, and no retrace lines!

Do you think that the set came from the factory this way, or was it one of the Sears service technicians who had previously worked on it?—R.K., Middleburg Heights, OH.

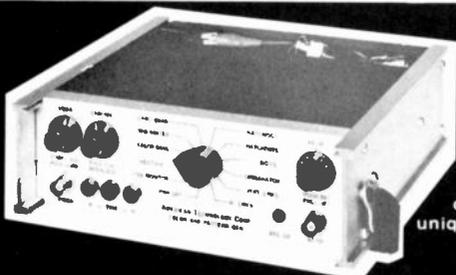Well, you've got one of two choices. Take your pick! R-E



Patents Pending covering 13 unique features.

Why use the ATC-10 General Television Servicer?

Because for an investment of \$299.95, the ATC-10 provides most of the combined features of a conventional color bar pattern generator, an Analyst and a substitute tuner. You get time savings bonus features too, like the RED RASTER, 3.58 MONITOR, GRAY QUAD, and multi-purpose HATCHDOTS patterns.

Al Flynn, proprietor of Al Flynn Radio TV Repair Service, Inglewood, California says . . .
 "Versatility makes the ATC-10 generator a money maker. The ATC-10 is what TV repairmen have needed for ten years."

Write for more information on the ATC-10 General Television Servicer, or try it at our risk

— 30 day shop trial —

if not 100% satisfied in every way, return for instant refund in full.

American Technology Corporation

225 Main Street, Dept. 3C, Canon City, CO 81212

For your convenience, we accept Master Charge, BankAmericard and COD phone orders. Same day shipment! (303) 275-8991, Ext. 3

CIRCLE 59 ON FREE INFORMATION CARD



GO DIGITAL, GO DANAMETER®

(The New VOM For Today's Needs.)

- 0.25% Accuracy
- Full Overload Protection
- Really Drop-Proof
- Full One Year Battery Life



Dana Laboratories, Inc.

2401 Campus Dr, Irvine, Ca 92715, (714) 833-1234

CIRCLE 63 ON FREE INFORMATION CARD

AM stereo soon? The FCC could act to establish an AM stereo radio service as soon as the end of this year, in the opinion of Washington observers. An industry-wide National AM Stereo Radio Committee (NASRC) has studied a number of proposed systems and was scheduled to start field-testing them over radio stations in February.

Game problems: The hottest new electronic product since CB may be running into an unexpected problem: Are video games injurious to television sets? The first rumblings were heard from television dealers who found that after leaving games on the screen all day for many days, the outlines of the game perimeters were "burned" into the picture tube screen. They reported these problems to the set manufacturers, who immediately began to envision thousands of picture-tube warranty replacements due to the use of games, and got their engineers and lawyers working to figure out what to do about it.

The Federal Trade Commission got wind of the potential problem and quietly started an investigation, questioning TV set, game and picture tube manufacturers. The investigation has been inconclusive so far, but the Canadian government's Consumer and Corporate Affairs Department issued a public warning that "prolonged use of the games may cause the game pattern to remain as a ghost during regular TV viewing," explaining that this was the result of "phosphor exhaustion" caused by fixed lines on the screen. An American catalog house, Service Merchandise Corporation, is sending its game customers a letter telling them that the extent of the problem isn't known, but suggesting that games be turned off when play is completed and that normal viewing habits be maintained, to give the set a "rest."

Sounds like a regular epidemic of trouble—except that so far as we can determine there have been no complaints from consumers. The Electronic Industries Association (EIA), which is conducting its own investigation, has heard of none. The Council of Better Business Bureaus says it is aware of the potential for trouble but hasn't received any complaints, and game and TV makers say they've heard only scattered complaints, but these were from stores which leave the games on for protracted periods, and not from consumers.

(Radio-Electronics is interested in this problem too. If you have had some personal experience with any instance of a TV game display damaging a picture tube, tell us about it. Send us full details, including manufacturer, model number, screen size, hours of use per day and room lighting. Send your data to Radio-Electronics Magazine, TV Games Data, 200 Park Avenue South, New York, NY 10003. Letters can not be acknowledged. We will publish the collected data in a future issue.—Editor)


The biggest worry, of course, is that the big game sales started just last year and there hasn't been enough experience yet to determine the long-term effects, if any. Television set makers, increasingly nervous about thousands of potential claims, are preparing to put disclaimers in their warranties to indicate that the terms cover only the use of the sets to view programs. Until the problem is better defined, there's a simple precaution which probably will prevent any potential damage: Turn down the brightness and contrast.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

Put Professional Knowledge and a COLLEGE DEGREE

in your Electronics Career through

HOME STUDY

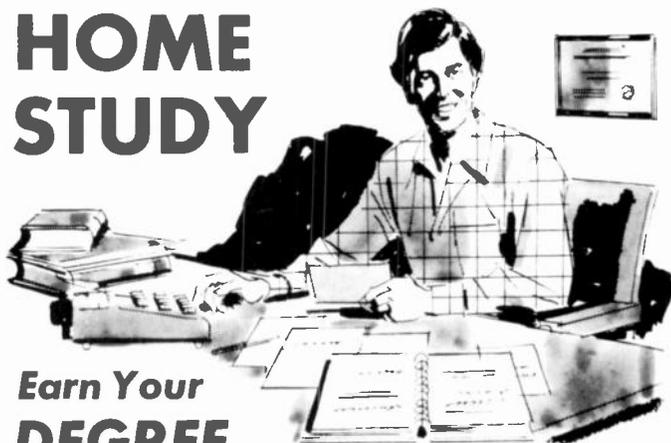

Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of independent study.

The Grantham correspondence degree program in electronics is comprehensive. It begins with basics, written in very simple language, and continues through the B.S.E.E. degree level. Throughout the entire program, heavy emphasis is placed on clear explanations written in great detail, progressing from the simple to the complex, in easy steps.

Our free bulletin gives complete details on the curriculum, the degrees awarded, the requirements for each degree, and how to enroll.

GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 90025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study
Mail the coupon below for free bulletin.

Grantham School of Engineering RE 3-77
2000 Stoner Ave., Los Angeles, CA 90025

I have been in electronics for _____ years. Please mail me your free bulletin which gives details concerning your electronics degree programs.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

CIRCLE 13 ON FREE INFORMATION CARD

FREE burglar — fire alarm catalog



over 900 systems, detectors, controls, sounders, tools, locks, supplies

TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 64 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today. (Outside U.S., send \$1.00.)



mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

CIRCLE 8 ON FREE INFORMATION CARD

For faster service

USE ZIP CODE

on all mail

new books

CB UPDATE, by Mike Wendland. Sheed, Andrews & McMeel, Inc., 6700 Squibb Road, Mission, KS 66202. 5 1/4 x 8 in., 140 pp, \$3.95 softcover.

Good Buddies and would be Good Buddies alike will find this up-to-now look at the hottest hobby in America intriguing. It contains valuable information for both longtime CB'ers and those with newly acquired ears. The author begins with a brief history of CB radio explaining how the Arab oil boycott and the double-nickels speed limit precipitated the CB mania. Once used only by a handful of businessmen and backroad coyote hunters, CB radios today are the truckers' best friend and a handy tool for thousands of motorists.

The book covers the ABC's of CB as well as the more technical aspects. The author explains AM and SSB operations, gives advice on operating etiquette, provides details of proper antenna mounts and the variety of useful tips. He also tells how to operate a unit from a home base, even in an apartment. Of particular interest will be the glossary of CB terms in the back of the book. Other helpful appendices include a guide to the 10-code and a copy of the FCC Rule and Regulations, Part 95.

CB RADIO, Tab Editorial staff. Tab Books, Blue Ridge Summit, PA 17214. 7 x 10-in., 210 pp, \$5.95 softcover.

This is volume 4 in a series of CB Radio Schematic/Service Manuals. This one covers Pace, Fanon/Courier and Dynascan (Cobra). It's a complete rundown on servicing data on more than 30 CB transceivers. A valuable reference for any technician looking at the service and repair of CB radio equipment.

THE RADIO AMATEUR'S HANDBOOK. Fifty-third (1976) Edition. Edited by Bob Myers and The Headquarters Staff of the American Radio Relay League. Newington, CT 06111. 6 1/2 x 9 1/2 in., 705 pp including Index. Softcover. \$6.00 in U.S. and Possessions, \$7.00 in Canada and \$8.00 elsewhere. Hardcover clothbound \$10.00 in U.S. and Possessions, \$11.00 in Canada and \$12.00 elsewhere.

Like the fifty-two previous editions, the ARRL Handbook is destined to be one of the most sought-after publications in the electronics field. It is chock full of material for beginners, advanced amateurs and electronics engineers alike. Readers of the Handbook will be pleasantly surprised at the number of new construction projects in this edition. Among them are a two-band solid-state transmitter, a 2-kW 2-meter amplifier and a communications receiver with digital readout. Hundreds of drawings, charts and photographs are used to present the material.

CB RADIO, Second Edition, Revised, by Leo G. Sands. A. S. Barnes & Co., Inc., Box 421, Cranbury, NJ 08512. 5 1/2 x 8 1/2-in., 192 pp, \$8.95 hardcover.





This is a basic introduction to the fascinating world of CB updated and revised with all the latest rules, "lingo," and equipment. The following topics are covered fully: getting started; selecting equipment; cost of equipment; power sources for the house, vehicle, boat and walkie-talkie; antennas; installation; maintenance and repair; and efficient use of air time.

Special features include a license application form, official 10-code, CB operator lingo, trucker's CB lingo, abbreviations, and protecting yourself with CB radio.

CBer's HANDYBOOK OF SIMPLY HOBBY PROJECTS, by Robert M. Brown. Tab Books, Blue Ridge Summit, PA 17214. 5 1/8 x 8 1/4-in., 168 pp. Softcover: \$3.95.

This book contains 114 easy-to-build performance boosters for every CB'er including mobile and base station antennas, direction finders, modulation boosters, RF preamplifiers and converters, noise limiters, clippers, squelch switches, audio compressors and limiters plus 101 other useful and novel operating aids. Most of the projects can be built for under \$5.00 using new parts. A soldering iron and normal hand tools are all that are needed to build any of these projects.

R-E

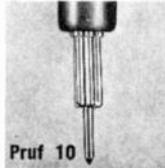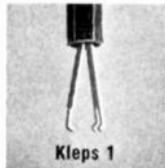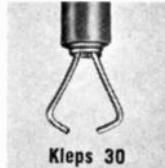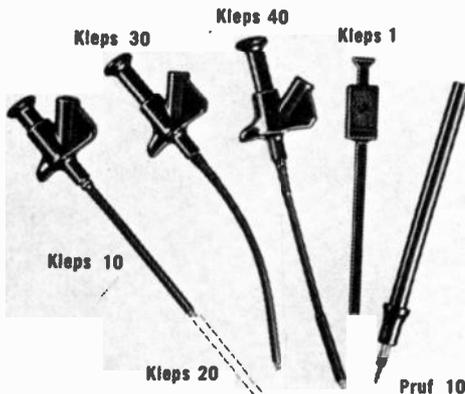

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

Kleps 10. Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 3/4" long. \$1.39

Kleps 20. Same, but 7" long. \$1.49

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.79

Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. \$2.59

Kleps 1. Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$.99

Pruf 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$.89

All in red or black - specify. (Add 50¢ postage and handling.)

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.

129 Spencer Place, Mamaroneck, N.Y. 10543

In Canada: Rye Industries (Canada) Ltd.

CIRCLE 25 ON FREE INFORMATION CARD



next month

APRIL 1977

■ Build A Computer

It's all on one circuit board: 2650 IC, 1024 bytes of PROM expandable to 4K, 2048 bytes of RAM, cassette interface at 300 baud, video display interface and more.

■ Experiment With EXAR Function Generator IC

Build almost any kind of generator you can think of—sine, square, triangle, FM, AM, and PSK.

■ IC Data Sheet For Reticon SAD-1024

See how it works and what you can do with this "Bucket Brigade Delay" device.

■ Build Teleswitch

First of series of telephone associated projects. This one lets you turn electrical devices on and off when you're away from home, by using the nearest telephone.

PLUS

Komputer Korner

Phase-Locked Loop For CB

Jack Darr's Service Clinic

Dynamic Range Enhancement

Hi-Fi Lab Test Reports

the shocking truth



The world of electronics is becoming both larger and smaller. As its essential hardware is rapidly decreasing in size, the demand for competent technicians is rapidly increasing, especially in communications and marine technology.


The Jensen Beach Campus of Florida Institute of Technology offers an Associate of Science degree in Electronic Technology concentrating on the specialized skills needed in modern marine and communications applications. Students in this program receive broad academic training in electronics as well as diverse practical experience qualifying them for various career opportunities in industry.

To learn more about F.I.T.'s Associate of Science degree in Electronic Technology, return the coupon below today.

Florida Institute of Technology
720 S. Indian River Drive
Jensen Beach, Florida 33457

Name _____
Address _____
City _____ State _____
Zip _____ Phone _____
Age _____ Veteran Area Code _____

REFP 2/77

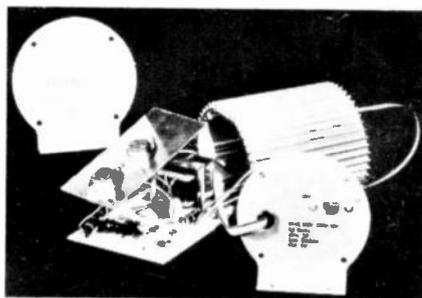

FROM KIT TO CAR IN 80 MINUTES!

Electronic ignition is "in." Update your car with the TOPS in power, efficiency and reliability — the TIGER SST capacitive discharge ignition (CD).

The TIGER delivers everything other CD's promise — and more: quicker starting, more power, more gas mileage, tune-ups eliminated, lifetime plugs and points, reduced repairs and pollution.

The TIGER can be built and installed in your car in 80 minutes. The TIGER is unique!

The TIGER comes with a switch for TIGER or standard ignition for 12V negative ground only.


Simpli-Kit \$21.95
POST PAID U.S.A.

WE ACCEPT:
Mastercharge or BankAmericard.
Send check or money order with order to:

Tri-Star Corporation

DEPT. FF, P.O. Box 1727
Grand Junction, Colorado 81501

CIRCLE 4 ON FREE INFORMATION CARD

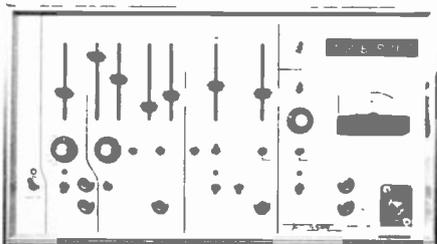

MODEL 100A AUDIO RESPONSE PLOTTING SYSTEM and general purpose sweep/tone burst/pulse generator consists of two sine/square/triangle function generators, pulse generator, frequency counter and peak amplitude measurement sections. It is primarily intended to generate a frequency response plot on an X-Y recorder or scope.

Time base generator offers symmetrical or independent control of the positive and negative sides of the ramp providing a duty cycle of .7% to 99.3%. Frequency range is .0035Hz to 100kHz. Amplitude is 15Vpp into 500Ω with -5VDC offset. The time base output drives the X axis of an X-Y recorder. Manual mode provided for setup.

Audio sweep generator provides manual frequency adjustment or log/linear sweep of 20Hz to 20kHz. Blanking mode produces zero reference line on X-Y recorder or tone burst. Amplitude is 15 Vpp into 500Ω or 10 Vpp into 8Ω.

Pulse generator frequency range is .0035Hz to 525kHz. Pulse width is adjusted independent of frequency from 4 seconds to 40 nanoseconds. Outputs are complementary TTL.

Peak amplitude measurement section measures internal or external signals from mike to power amp level. Amplitude output drives Y axis of X-Y recorder.

Frequency counter is 6 digit, line triggered, and reads either internal or external. Sensitivity is 50 mv peak at 20kHz.

Dimensions: 8 x 14 x 3. Shipping Weight 9 lbs.
\$550, stock to 30 days. Warranty: 1 year.

FIDELITY SOUND

1894 Commercenter W. #105
San Bernardino, Ca 92408
(714) 889-7623

CIRCLE 61 ON FREE INFORMATION CARD

RADIO-ELECTRONICS

104

ANALOG VOLTMETERS

continued from page 71

or range. This is quite common, especially with the crowded scales of a versatile multi-function meter. For example, it is easy to have the voltmeter set on the 15-volt range and take the reading from the 50-volt scale. A more subtle version of this problem is to take a 1.5-volt AC reading from the 15-volt scale rather than the special scale provided for the 1.5 VAC range.

Errors in reading can be generated from parallax. Parallax is the difference in readings obtained by viewing the meter from different angles. Generally, errors due to parallax are important only when high-precision measurements are being made. Where parallax is a severe problem, a mirror-backed meter scale helps maintain all readings from a single point.

Another operator error is to make measurements with the probe tip switch in the wrong position. Either the switch is in the DC position, (which places one megohm in series with the probe) and the measurement is either AC volts or ohms, or DC measurements are made without the series resistance and all measurements are 10% high.

Resistance measurements made with current still flowing in the circuit are invalid. The ohmmeter, in the final analysis, measures voltage. Any extra current in the resistance being measured sets up a voltage, which is a source of error. If the meter is not protected, there may also be damage to the ohmmeter circuits.

Resistance measurements made on transformer windings (or other highly inductive components) are susceptible to two problems. The first is caused by a lack of transformer knowledge. The operator discards a good transformer because the resistance of a winding appears to be low. What has been forgotten is the reflected impedance from the other windings. The second problem is caused by the high inductance itself, and is normally a problem only with power transformer primaries and high-voltage secondaries. When the ohmmeter is disconnected from the winding, the magnetic field collapses. This collapse causes a high voltage to appear at the winding terminals. The high voltage can cause electrical shock, damage to the ohmmeter, or both.

Polarity errors are common and come in two forms. First, the user may have the meter set for one polarity and assume another. The second polarity error is associated with ohmmeter measurements: The operator fails to consider the effects ohmmeter polarity may have on a circuit containing semiconductor junctions. If the presence of semiconductor junctions in the measurement is suspected, a simple check is reversal of the test leads. Significantly different resistance readings indicate the presence of semiconductor junctions.

Improper interpretation of the decibel scales often leads to error.

In the area of errors introduced by the meter itself, circuit loading is probably the most common. Often a simplistic view of the VTVM or the TVM is taken, and the presumption is that the electronic voltmeter does not load the circuit at all. Although the electronic voltmeter may be substantially better than the VOM, it still loads the circuit. Looking at the simple DC case, it is apparent

that a 10-megohm voltmeter loads a one-megohm source enough to produce a 10 percent error in the reading. This is if DC only is taken into consideration.

If the AC component of the signal is also considered, capacitive loading must also be considered. The meter input capacitance often presents a low-impedance resistive load of the divider. As noted earlier, this must be taken into consideration when making DC as well as AC measurements. This is especially true when dealing with a circuit where the loss of AC shifts the DC values of the circuit. The self-biasing stages of a transmitter are an example of such a case. The isolating resistance of the VTVM is most necessary in these cases.

There are times when the VOM is actually better than the TVOM or the VTVM. For example, the VTVM has an 11-megohm input impedance when used on the 1,500-volt range; however, a VOM with 20,000 ohms per volt input impedance has 20,000 × 1500, or 30 megohms input impedance. When measuring a high-voltage supply, this may be of considerable advantage. The VOM may have the further advantage of having an even higher voltage range (4 to 5 kV for example), and the circuit loading caused by these ranges is even less than that of the VTVM or TVM.

The analog voltmeter is truly not dead nor dying. Although many of its functions are being replaced by the digital multi-meter, there are still many places where the analog instrument is adequate. **R-E**

BIPHONIC SOUND

continued from page 39

products in the future. In a recent visit to JVC's headquarters in New York City, we were treated to yet another experience in sound reproduction. To best illustrate the effects of their binaural-stereophonic and quadriphonic-binaural-stereophonic processors and program material, they devised a special listening chair (see cover photo), equipped with four small speakers in front of and behind the chair's occupant. Despite the obvious fidelity limitations of the small speakers constructed into the framework of the experimental chair, the sound images created by these carefully positioned speakers were beyond description.

At the moment, there are only a few records recorded binaurally in this country, though in Japan it is reported that some twenty such special discs are already available. If interest in binaural sound increases, we may well see additional offerings of such discs in this country and may, perhaps, even witness the resurrection of an old form of sound recording and reproduction that has been dormant for more than forty years. **R-E**

Poly Pak's EXCLUSIVE

Avg. Ship. Wt. 6 ozs.

\$1.98

Every kit carries a money back guarantee!



YOUR CHOICE OF ANY KIT INCLUDES "100%" MATERIAL TOO!!!!

100'S OF BARRELS PURCHASED!

For the first time anywhere, Poly Pak merchandisers introduce a new way in buying the economical way. Raw stock from the "barrel". Remember the "good ole days"? They're back again. The same way merchandisers

throughout the United States buy from various factories... their overruns in barrels. Poly Pak has done the same. Therefore you are getting the same type of material as the RE-TESTERS DO!

TEST 'EM YOURSELF 'N SAVE!

OP AMP SPECIALS

- LM301M 5 for \$1.19
- LM301V 5 for 1.19
- LM307V 4 for 1.19
- LM308V 2 for 1.19
- LM309H 3 for 1.19
- LM322N 3 for 3.00
- LM324N 3 for 3.00
- LM339N 3 for 1.19
- LM370N 3 for 2.50
- LM373N 3 for 5.00
- LM377N 3 for 4.00
- LM380V 2 for 1.19
- LM555N 3 for 1.19
- LM565N 3 for 2.50
- LM703H 4 for 1.19
- LM709H 2 for 1.19
- LM723N 2 for 1.19
- LM741V 4 for 1.19
- LM747H 2 for 1.19
- LM748V 5 for 1.19
- LM1800N 3 for 2.50
- LM3900N 3 for 1.19
- LM4250N 3 for 2.50

- LM381N 3 for 4.00
- LM555N 3 for 1.19
- LM565N 3 for 2.50
- LM703H 4 for 1.19
- LM709H 2 for 1.19
- LM723N 2 for 1.19
- LM741V 4 for 1.19
- LM747H 2 for 1.19
- LM748V 5 for 1.19
- LM1800N 3 for 2.50
- LM3900N 3 for 1.19
- LM4250N 3 for 2.50

Buy 10 BARREL KITS and choose the 11th Free

BARREL KIT #200 MINI BLOCK CAPACITORS 100 for \$1.98

BARREL KIT #203 CALCULATOR KEYBOARDS 10 for \$1.98

BARREL KIT #201 PLUGS, SOCKETS RECEPTACLES 100 for \$1.98

BARREL KIT #201 6V INDICATORS w/leads 15 for \$1.98

BARREL KIT #200 DIGIT READOUT MODULES 5 for \$1.98

BARREL KIT #195 CARBO-FILM RESISTORS 75 for \$1.98

BARREL KIT #188 400 Parts \$1.98

BARREL KIT #189 KEYBOARD CHIPS 10 for \$1.98

BARREL KIT #184 1/4 WATT METAL FILM 150 for \$1.98

BARREL KIT #182 JUMBO RED LEADS 15 for \$1.98

BARREL KIT #187 ROMS-RAMS-REGISTERS 1-lb. \$1.98

BARREL KIT #186 LONG LEAD DISCS 4 ozs. \$1.98

BARREL KIT #183 MINI TRIM POTS 30 for 1 oz. \$1.98

BARREL KIT #161 TPO-PLASTIC TRANSISTORS 25 for \$1.98

BARREL KIT #160 V. REGULATORS 15 for \$1.98

BARREL KIT #159 MODULAR SWITCHES 25 for \$1.98

BARREL KIT #158 MAGNIFIED MAN-3'S 12 for \$1.98

BARREL KIT #157 MOLEX CONNECTORS 75 for \$1.98

BARREL KIT #154 CLOCK CHIPS 20 for \$1.98

BARREL KIT #146 ROCKER SWITCHES 25 for \$1.98

BARREL KIT #161 TRANSISTORS 25 for \$1.98

BARREL KIT #160 V. REGULATORS 15 for \$1.98

BARREL KIT #159 MODULAR SWITCHES 25 for \$1.98

BARREL KIT #138 PANEL SWITCHES 30 for \$1.98

BARREL KIT #135 MICRO MINI LAMPS 20 for \$1.98

BARREL KIT #134 CALCULATOR CHIPS 15 for \$1.98

BARREL KIT #146 ROCKER SWITCHES 25 for \$1.98

BARREL KIT #131 TANTALUM ELECTROS 30 for \$1.98

BARREL KIT #128 MINI DIP ICS 75 for \$1.98

BARREL KIT #144 RCA PHONO PLUGS 40 for \$1.98

BARREL KIT #118 MINI SCRS 50 for \$1.98

BARREL KIT #115 MOLEX SOCKETS 200 for \$1.98

BARREL KIT #112 MICRO MINI LEADS 40 for \$1.98

BARREL KIT #109 TERMINAL STRIPS 100 for \$1.98

BARREL KIT #104 SLIDE VOLUME CONTROLS 10 for \$1.98

BARREL KIT #127 AXIAL ELECTROS 40 for \$1.98

BARREL KIT #143 75-PC TRANSISTORS 15 for \$1.98

BARREL KIT #93 MALF WATERS 200 for \$1.98

BARREL KIT #92 3 AMP EPOXY RECTIFIERS 100 for \$1.98

BARREL KIT #91 SILVER MICAS 100 for \$1.98

BARREL KIT #88 LITRONICS LED READOUTS 10 for \$1.98

BARREL KIT #87 NATIONAL IC BONANZA 100 for \$1.98

BARREL KIT #86 HOBBY LEADS 40 for \$1.98

BARREL KIT #83 PHOTO ELECTRIC CELLS 10 for \$1.98

BARREL KIT #81 SUBMINI RESISTORS 200 for \$1.98

BARREL KIT #76 1-WATT ZENERS 100 for \$1.98

BARREL KIT #75 400MW ZENERS 100 for \$1.98

BARREL KIT #73 TRANSISTOR ELECTROS 50 for \$1.98

BARREL KIT #71 CAPACITOR SPECIAL 100 pcs. \$1.98

BARREL KIT #68 2 WATERS 100 for \$1.98

BARREL KIT #65 MIXED READOUTS 10 for \$1.98

BARREL KIT #61 POLYSTYRENE CAPS 100 for \$1.98

BARREL KIT #58 SLIDE SWITCHES 30 for \$1.98

BARREL KIT #56 POWERS! POWERS! 100 for \$1.98

BARREL KIT #54 LED READOUTS 10 for \$1.98

BARREL KIT #40 DIGITAL TRANSISTORS 20 for \$1.98

BARREL KIT #39 2N3055 HOBBY TRANSISTORS 15 for \$1.98

BARREL KIT #37 1 AMP "BULLET" RECTIFIERS 100 for \$1.98

BARREL KIT #36 GERMANIUM DIODES 200 for \$1.98

BARREL KIT #35 NEON LAMPS 30 for \$1.98

BARREL KIT #31 METAL RESISTORS 100 for \$1.98

BARREL KIT #30 PREFORMED RESISTORS 200 for \$1.98

BARREL KIT #27 PREFORMED DISCS 100 for \$1.98

BARREL KIT #26 PLASTIC TRANSISTORS 100 for \$1.98

BARREL KIT #25 METAL CAN TRANSISTORS 100 for \$1.98

BARREL KIT #20 LONG LEAD DISCS 100 for \$1.98

BARREL KIT #19 DIPPED MYLARS 60 for \$1.98

BARREL KIT #12 POWER TAB TRANS 40 for \$1.98

BARREL KIT #11 POWER TAB TRANSISTORS 40 for \$1.98

BARREL KIT #10 LINEAR & 7400 DIPS 100 for \$1.98

BARREL KIT #9 SUBMINIATURE IF TRANSFORMERS 100 for \$1.98

BARREL KIT #14 PRECISION RESISTORS 200 for \$1.98

BARREL KIT #8 4000V RECTIFIERS 100 for \$1.98

BARREL KIT #7 VOLUME CONTROL BONANZA! 30 for \$1.98

BARREL KIT #6 PNP, plastic TO220 type. Assorted 2N numbers. Cat.No. 3R2426 Untested.

BARREL KIT #4 "4000V" RECTIFIERS 100 for \$1.98

BARREL KIT #3 1N4148/914 SWITCHING DIODES 100 for \$1.98

BARREL KIT #2 LINEAR OR AMPS. DIPS 75 for \$1.98

BARREL KIT #1 SN7400 DIP IC'S 75 for \$1.98

BARREL KIT #5 SCRS, TRIACS, QUADRACS 30 for \$1.98

BARREL KIT #4 "4000V" RECTIFIERS 100 for \$1.98

BARREL KIT #3 1N4148/914 SWITCHING DIODES 100 for \$1.98

BARREL KIT #2 LINEAR OR AMPS. DIPS 75 for \$1.98

BARREL KIT #1 SN7400 DIP IC'S 75 for \$1.98

BARREL KIT #1 SN7400 DIP IC'S 75 for \$1.98

BARREL KIT #1 SN7400 DIP IC'S 75 for \$1.98

Cat. No. 2R1981

Poly Paks Inc., Wakefield, Mass., U.S.A. 1977

Poly Paks C-R-A-C-K-S

Prices

Now! INCREDIBLE PRICES

BUY ANY 10 TAKE 15%

BUY 100 TAKE 25%

TYPE SALE	SN7442N .53	SN7494N .78	SN74160N .88
SN7400N \$0.16	SN7445N .69	SN7495N .78	SN74161N .88
SN7401N .16	SN7446N .79	SN74100N .98	SN74162N .99
SN7402N .16	SN7447N .69	SN74106N .65	SN74163N 1.39
SN7403N .16	SN7448N .76	SN74107N .33	SN74164N .97
SN7404N .16	SN7449N .16	SN74112N .59	SN74165N .89
SN7405N .18	SN7450N .16	SN74113N .65	SN74166N .79
SN7406N .20	SN7451N .16	SN74114N .65	SN74167N .79
SN7407N .25	SN7452N .16	SN74115N .65	SN74168N .79
SN7408N .25	SN7453N .16	SN74116N .65	SN74169N .79
SN7409N .18	SN7454N .16	SN74117N .65	SN74170N .79
SN7410N .16	SN7455N .16	SN74118N .65	SN74171N .79
SN7411N .25	SN7456N .16	SN74119N .65	SN74172N .79
SN7412N .45	SN7457N .16	SN74120N .65	SN74173N .79
SN7413N .45	SN7458N .16	SN74121N .65	SN74174N .79
SN7414N .32	SN7459N .16	SN74122N .65	SN74175N .79
SN7415N .32	SN7460N .16	SN74123N .65	SN74176N .79
SN7416N .29	SN7461N .16	SN74124N .65	SN74177N .79
SN7417N .29	SN7462N .16	SN74125N .65	SN74178N .79
SN7418N .29	SN7463N .16	SN74126N .65	SN74179N .79
SN7419N .29	SN7464N .16	SN74127N .65	SN74180N .79
SN7420N .29	SN7465N .16	SN74128N .65	SN74181N .79
SN7421N .29	SN7466N .16	SN74129N .65	SN74182N .79
SN7422N .35	SN7467N .16	SN74130N .65	SN74183N .79
SN7423N .35	SN7468N .16	SN74131N .65	SN74184N .79
SN7424N .35	SN7469N .16	SN74132N .65	SN74185N .79
SN7425N .35	SN7470N .16	SN74133N .65	SN74186N .79
SN7426N .35	SN7471N .16	SN74134N .65	SN74187N .79
SN7427N .35	SN7472N .16	SN74135N .65	SN74188N .79
SN7428N .35	SN7473N .16	SN74136N .65	SN74189N .79
SN7429N .35	SN7474N .16	SN74137N .65	SN74190N .79
SN7430N .35	SN7475N .16	SN74138N .65	SN74191N .79
SN7431N .35	SN7476N .16	SN74139N .65	SN74192N .79
SN7432N .35	SN7477N .16	SN74140N .65	SN74193N .79
SN7433N .35	SN7478N .16	SN74141N .65	SN74194N .79
SN7434N .35	SN7479N .16	SN74142N .65	SN74195N .79
SN7435N .35	SN7480N .16	SN74143N .65	SN74196N .79
SN7436N .35	SN7481N .16	SN74144N .65	SN74197N .79
SN7437N .35	SN7482N .16	SN74145N .65	SN74198N .79
SN7438N .35	SN7483N .16	SN74146N .65	SN74199N .79
SN7439N .35	SN7484N .16	SN74147N .65	SN74200N .79
SN7440N .35	SN7485N .16	SN74148N .65	SN74201N .79
SN7441N .35	SN7486N .16	SN74149N .65	SN74202N .79
SN7442N .35	SN7487N .16	SN74150N .65	SN74203N .79
SN7443N .35	SN7488N .16	SN74151N .65	SN74204N .79
SN7444N .35	SN7489N .16	SN74152N .65	SN74205N .79
SN7445N .35	SN7490N .16	SN74153N .65	SN74206N .79
SN7446N .35	SN7491N .16	SN74154N .65	SN74207N .79
SN7447N .35	SN7492N .16	SN74155N .65	SN74208N .79
SN7448N .35	SN7493N .16	SN74156N .65	SN74209N .79
SN7449N .35	SN7494N .16	SN74157N .65	SN74210N .79
SN7450N .35	SN7495N .16	SN74158N .65	SN74211N .79
SN7451N .35	SN7496N .16	SN74159N .65	SN74212N .79
SN7452N .35	SN7497N .16	SN74160N .65	SN74213N .79
SN7453N .35	SN7498N .16	SN74161N .65	SN74214N .79
SN7454N .35	SN7499N .16	SN74162N .65	SN74215N .79
SN7455N .35	SN7500N .16	SN74163N .65	SN74216N .79
SN7456N .35	SN7501N .16	SN74164N .65	SN74217N .79
SN7457N .35	SN7502N .16	SN74165N .65	SN74218N .79
SN7458N .35	SN7503N .16	SN74166N .65	SN74219N .79
SN7459N .35	SN7504N .16	SN74167N .65	SN74220N .79
SN7460N .35	SN7505N .16	SN74168N .65	SN74221N .79
SN7461N .35	SN7506N .16	SN74169N .65	SN74222N .79
SN7462N .35	SN7507N .16	SN74170N .65	SN74223N .79
SN7463N .35	SN7508N .16	SN74171N .65	SN74224N .79
SN7464N .35	SN7509N .16	SN74172N .65	SN74225N .79
SN7465N .35	SN7510N .16	SN74173N .65	SN74226N .79
SN7466N .35	SN7511N .16	SN74174N .65	SN74227N .79
SN7467N .35	SN7512N .16	SN74175N .65	SN74228N .79
SN7468N .35	SN7513N .16	SN74176N .65	SN74229N .79
SN7469N .35	SN7514N .16	SN74177N .65	SN74230N .79
SN7470N .35	SN7515N .16	SN74178N .65	SN74231N .79
SN7471N .35	SN7516N .16	SN74179N .65	SN74232N .79
SN7472N .35	SN7517N .16	SN74180N .65	SN74233N .79
SN7473N .35	SN7518N .16	SN74181N .65	SN74234N .79
SN7474N .35	SN7519N .16	SN74182N .65	SN74235N .79
SN7475N .35	SN7520N .16	SN74183N .65	SN74236N .79
SN7476N .35	SN7521N .16	SN74184N .65	SN74237N .79
SN7477N .35	SN7522N .16	SN74185N .65	SN74238N .79
SN7478N .35	SN7523N .16	SN74186N .65	SN74239N .79
SN7479N .35	SN7524N .16	SN74187N .65	SN74240N .79
SN7480N .35	SN7525N .16	SN74188N .65	SN74241N .79
SN7481N .35	SN7526N .16	SN74189N .65	SN74242N .79</

FORDHAM

BEST BUYS

SENCORE TEST EQUIPMENT

Sencore TF40 Pocket Cricket Portable Transistor & FET Tester

One simplified, safe test for all transistors and FETs. 99.9% reliable with complete leakage test on meter. And the Pocket Portable is the only one that has it. No set-up information is needed. Total test takes seconds. Identifies transistor polarity, FET or bipolar transistor. Identifies all 3 leads everytime. Includes test tone indicator.



CB41 Portable CB Performance Tester

Tests SWR, RF power and % modulation. Tells if a CB rig is getting out as far as possible . . . if it needs servicing.



CB42 Total CB Automatic Analyzer

The complete CB service bench, simplified for quick troubleshooting and performance testing. Performs 12 receiver tests; 12 transmitter tests. Single digital readout for all tests. Combines five units in one: 1) Frequency Counter; 2) RF-IF Generator; 3) Audio Generator; 4) Digital RF Wattmeter; and 5) special CB Tester.



PS43 Port-A-Pak Power Supply/Battery Eliminator

Combines advantages of rechargeable batteries with an AC operated supply for any 12 volt service need.

FOR PRICING AND TO PLACE YOUR ORDER:

Call collect for Mr. Louis (516) 752-0050
Master Charge, BankAmericard and C.O.D.'s accepted

FORDHAM RADIO SUPPLY CO., INC.
855R Conklin St.
Farmingdale, N.Y. 11735

YOUR ONE STOP DISCOUNT CENTER



FREE

148 page catalog of over 3000 items . . . test equipment, CB, tools, tubes, components and a full line of electronic supplies

Test Equip. Special Discount Prices



Leader
SCENCORE

- RCA 110 FLYBACK TRANS. For Bk & Wht. sets 18KV. 3.95
- 110 TV DEFLECTION YOKE for all types TV. 4.95
- "COMBINATION SPECIAL" RCA 110 FLYBACK & YOKE. 6.95
- 90 COLOR YOKE for rect. 19 to 25" CRTs. 7.95
- 70 COLOR YOKE for round color CRT's. 5.95
- UHF TUNERS Transistor type used in all TV sets. 2.95
- GE UHF TUNERS Transistor Type Model 85X4. 3.95
- ADMIRAL TUNER-Model 94C393-1 (2H45-4J8). 7.95
- ADMIRAL TUNER Model T94C441-3 (Transistor). 7.95
- GE TV TUNER Model #EP86X11 (Series). 7.95
- PHILCO UHF/VHF TUNER Transistor type. 9.95
- ZENITH TUNER Model 175-1164 or 175-1151. 9.95
- BLUE LATERAL MAGNET ASSY Repl. for most TV. 1.79
- COLOR DELAY LINE Used in most TV. 1.69
- ZENITH SILICON STICK RECTIFIER Part #103-215. 4.95
- ZENITH TRIPLER-Part #212-109 Same as EC6501. 3.95
- 3-POLARIZED CHEATER CORDS Brown. 1.00
- COLOR POWER TRANSFORMER RCA Part #201150. 7.95
- 2-COLORBURST CRYSTALS (3579.545KC). 1.89
- 3-COLOR TV RECTIFIER 6500KV. 1.95
- 6-TV ALIGNMENT KIT most popular type. 2.79
- 4-TV ALIGNMENT KIT useful asst. 1.00
- 5-DUAL DIODE most popular type (Common or Series). 2.50
- VU "T" PANEL METER 0-20 db Scale. 1.00
- CO-AX CABLE RG59 (Bk.) (250-\$10.00) 50'. 2.69
- HI VOLTAGE POWER TRANSISTOR Equip. to Hep 207. 2.29
- TRANSISTOR RADIO asst. types (good, bad, broken, as-is). 1.50
- TAPE RECORDERS asst. types (good, bad, broken, as-is). 4.00
- 100' GREY SPEAKER. 2.00
- WIRE. 2.00
- UNIVERSAL TV ANTENNA back of set type (5 section). 2.99
- 3-ZENITH VIDEO AMPLIFIER Part #121-743. 2.00
- WAHL CORDLESS SOLDER IRON (complete with charger). 1.79
- 8" HEAVY DUTY 10 OZ. SPEAKER ceramic type 8 ohm. 5.50
- 6" 9" HEAVY DUTY 10 OZ. SPEAKER ceramic type 8 Ohm. 5.50
- STEREO HEADPHONES HI FI Quality with plug. 4.95
- TACHOMETER 2 1/4" SQUARE PANEL METER 1-VDC 0-6000 RPM. 2.00
- CASSETTE TYPE MIKE Universal Plug-200 Ohms. 2.99
- 5 ZENER DIODES 1N4757A-1 W-50 V. 1.00
- B & K DIGITAL METER Model #240. 85.00
- 2-HEP 50015 SILICON TRANSISTORS. 1.00
- 1-HEP 55004 SILICON NPN TRANSISTOR. 1.00
- 1-HEP 55011 OR HEP 55012 HV TRANSISTORS. 1.00
- TRANSISTOR SPECIALS ECG-108-ECG-116-ECG-129A-ECG109. 1.00
- TRANSISTOR SPECIALS ECG-121-ECG-128-ECG-154. 1.00
- GE IC3 OR IC4 INTEGRATED CIRCUIT Equip ECG116. 1.00
- COLOR TUBE BRIGHTNER 70 ... \$3.95. 90. 4.95
- 6-SILICON RECTIFIERS 1 Amp-1000 PIV. 1.00
- 7 TUBE AM FM STEREO AMPLIFIER CHASSIS complete with tubes as is. 9.95
- DELUXE PILLOW SPEAKER with plug. 2.49
- TUNER SPRAY 16 Oz. Can. 1.59
- 8-MINI PILOT BULBS (6.3V-30Ma) or (6.3V-150Ma). 1.00
- 3" 15" SPEAKER TV replacement. 1.39
- 3-ELECTROLYTIC COND. 300MFD-250V. 2.50
- 3-ELECTROLYTIC COND. 100/80/20 Mfd-300V. 2.00
- 3 PACK IRISH CASSETTE TAPES C-60 ... \$1.50. C-90. 2.50

Minimum Order \$5.00 Immediate Delivery

BROOKS RADIO & TV CORP.
529 Columbus Ave., New York, N.Y. 10024
TELEPHONE 212-874 5600

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

17	Acoustic Fiber Sound Systems	87
22	Advanced Electronics	90
74	Allison	94
59	American Audioport	32
7	American Technology	100
7	AP Products	98
	Audio-Technica	97
71	B&K-Div. of Dynascan	36
92	Bennies Warehouse Distribution Center	93
78	Chemtronics	83
	CIE-Cleveland Institute of Electronics	28-31
10	Channellock	26
9	Cobra-Div. of Dynascan	Cover IV
39	Continental Specialties	33
	CRFI-Div. of McGraw-Hill Continuing Education	72-75
63	Dana Labs	100
46	Delta Products	83
57	Digital Concepts	89
18	Edmund Scientific	126
6	EICO	24
64	E&I. Instruments	84
1	Electronics Book Club	35
	EMC-Electronics Measurement	99
61	Fidelity Sound	104
14	Florida Institute of Technology	103
72	GC Electronics	13
13	Grantham School of Electronics	101
	GTE Sylvania-Consumer Renewal	1
77	Handic of USA	15
100	Heath	91-92, 18-21
16	Hickok Electrical Instruments	14
31	Indiana Home Study Institute	99
75	International Crystal	82
43	JB Electronics	96
12	Jensen Tools and & Alloys	98
80	Kedman	97
27	Leader	95
65	Mallory	7
8	Mountain West Alarm Supply	102
2	National Camera Supply	98
	National Radio Institute (NRI)-Div. of McGraw-Hill Continuing Education Center	8-11
	National Technical Schools	62-65
81	Nesda	95
21	OK Machine & Tool	25
3	PAIA Electronics	95
55	PTS Electronics	90
	Radio Shack	17
25	Rye Industries	102
56	Sansui	2
19	Scencore	22
32	Schober Organ	97
33	Shakespeare	Cover III
23	Shure Brothers	Cover II
44	Soundguard	23
69	Southwest Technical Products	85
35	Tektronix	27
54,53,52	Telematic-Div. of UXL	34,96,100
4	Tri-Star	104
51	Tuner Service	5
36	V.I.Z. Mfg.	86
83	Vector Electronics	88

MARKET CENTER AD INDEX

40	Active Electronics	121
	AMC Sales	112
	Amateur Radio Supply	118
	Amatic Used Computer	118

Free Information Number Page

45	Babylon Electronics	116
	Karel Barta	112
41	Brooks	108
	Burdex Security	112
	CFR Associates	114
	Cornell Electronics	114
	Command Productions	105
	Dage Scientific Instruments	105
49	Delta Electronics	116
	Devtronix Organ Products	105
70	Digi-key	117
15	EDI	105
28	Fordham Radio Supply	107
38,5	Formula International	124,125
	Financial Management Associates	105
34	Godbout Electronics	118
	Information Unlimited	112
47	International Electronics	115
11,24	James Electronics	122,123
	Johnson-Smith	118
	Lab Science	112
	Lakeside Industries	118
30	Meshna	120
37	Morrow's Micro-Stuff	120
29	New-Tone	114
48	Optoelectronics	113
	Olson Electronics	112
	P.P.G. Electronics	105
26	Poly Paks	106
58	Quest	114
76	Radio Hut	119
	Ruple-Songer Electronics	112
73	SD Sales	111
42	Solid State Sales	116
20	Surplus Center	112
67	Tracy Design	118
	Trumbell	118
62	TV Tech Aids	120
60	Utep Marketing	118
	Valley West	105
	Visulex	112
	Wersi Electronics	105

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE

name (please print) _____
address _____
city state zip code _____

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80302

S.D. SALES CO.

P.O. BOX 28810 - C
DALLAS, TEXAS 75228

Z-80 CPU CARD KIT
FOR IMSAI/ALTAIR

\$149.^{KIT}

From the same people who brought you the \$89.95 4K RAM kit. We were not the first to introduce an IMSAI/ALTAIR compatible Z-80 card, but we do feel that ours has the best design and quality at the lowest price.

The advanced features of the Z-80 such as an expanded set of 158 instructions, 8080A software compatibility, and operation from a single 5VDC supply, are all well known. What makes our card different is the extra care we took in the hardware design. The CPU card will always stop on an M1 state. We also generate TRUE SYNC on card, to insure that the rest of your system functions properly. Dynamic memory refresh and NMI are brought out for your use. Believe it or not, not all of our competitors have gone to the extra trouble of doing this.

As always, this kit includes all parts, all sockets, and complete instructions for ease of assembly. Because of our past experience with our 4K kit we suggest that you order early. All orders will be shipped on a strict first come basis. Dealers inquiries welcome on this item.

Kit shipped with 2 MHZ crystals for existing 500NS memory. Easily modified for faster RAM chips when the prices come down.

Kit includes Zilog Manual and all parts.

JUMBO
LED
CAR
CLOCK

\$16.95
KIT

You requested it! Our first DC operated clock kit. Professionally engineered from scratch to be a DC operated clock. Not a makeshift kluge as sold by others. Features: Bowmar 4 digit .5 inch LED array, Mostek 50252 super clock chip, on board precision time base, 12 or 24 hour real time format, perfect for cars, boats, vans, etc. Kit contains PC Board and all other parts needed (except case). 50,000 satisfied clock kit customers cannot be wrong!

FOR ALARM OPTION ADD \$1.50
FOR XFMR FOR AC OPERATION ADD \$1.50

60 HZ CRYSTAL TIME BASE FOR DIGITAL CLOCKS
S.D. SALES EXCLUSIVE!

KIT FEATURES:

- A. 60HZ output with accuracy comparable to a digital watch.
- B. Directly interfaces with all MOS Clock Chips.
- C. Super low power consumption. (1.5 ma typ.) **\$5.95 or 2/\$10.**
- D. Uses latest MOS 17 stage divider IC.
- E. Eliminates forever the problem of AC line glitches.
- F. Perfect for cars, boats, campers, or even for portable clocks at ham field days.
- G. Small Size, can be used in existing enclosures.

KIT INCLUDES CRYSTAL, DIVIDER IC, PC BOARD
PLUS ALL OTHER NECESSARY PARTS & SPECS

50HZ CRYSTAL TIME BASE KIT - \$6.95

All the features of our 60HZ kit but has 50HZ output. For use with clock chips like the 50252 that require 50HZ to give 24 hour time format.

SPECIAL

THIS MONTH'S SPECIALS!

- 300.00 KHZ CRYSTAL - \$1.50
 - 8080A - CPU CHIP by AMD - \$19.95
 - 82S129 - 256 x 4 PROM - \$2.50
 - N.S. 8865 OCTAL DARLINGTON DRIVERS 3 for \$1.00
 - Z-80 - CPU by ZILOG - \$69.95
 - MM5204 - 4K EPROM - \$7.95
- Prices in effect this month ONLY!*

SPECIAL

4K LOW POWER RAM BOARD KIT
THE WHOLE WORKS - \$89.95


Imesai and Altair 8080 plug in compatible. Uses low power static 21L02-1 500ns. RAM's, which are included. Fully buffered, drastically reduced power consumption, on board regulated, all sockets and parts included. Premium quality plated thru PC Board.

7400-19c	7411-29c	7451-19c	7490-65c	74153-75c
74LS00-49c	7413-50c	7453-19c	74LS90-95c	74154-1.00
7402-19c	7416-69c	7473-39c	7492-75c	74157-75c
74LS02-49c	7420-19c	7474-35c	7493-69c	74161-95c
7404-19c	7430-19c	74LS74-59c	7495-75c	74164-1.10
74L04-29c	7432-34c	7475-69c	7496-89c	74165-1.10
74S04-44c	7437-39c	7476-35c	74121-38c	74174-95c
74LS04-49c	7438-39c	7480-49c	74123-65c	74181-2.50
7406-29c	7440-19c	7483-95c	74132-1.70	74191-1.25
7408-19c	7447-85c	7485-95c	74S138-1.95	74192-1.25
7410-19c	7448-85c	7486-45c	74141-75c	74193-1.00
TTL INTEGRATED CIRCUITS				

STICK IT!
in your clock
in your DVM, etc.!

Huge Special Purchase
Not Factory Seconds
As sold by others!

\$3.95

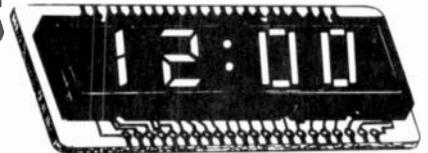

4 JUMBO .50" DIGITS ON ONE STICK!

(with colons and AM/PM Indicator)

BUY 3 for \$10.

BOWMAR 4 DIGIT LED READOUT ARRAY

The Bowmar Opto-Stick. The best readout bargain we have ever offered. Has four common cathode jumbo digits with all segments and cathodes brought out. Increased versatility since any of the digits may be used independently to fit your applications. Perfect for any clock chip, especially direct drive units like 50380 or 7010. Also use in freq. counters, DVM's, etc. For 12 or 24 hour format.

UP YOUR COMPUTER!

21L02-1 1K LOW POWER 500 NS STATIC RAM
TIME IS OF THE ESSENCE!

And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02-1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off. **8 for \$12.95**

\$12.95 S.D. SALES EXCLUSIVE! **\$12.95**
MOS 6 DIGIT UP-DOWN COUNTER

40 PIN DIP. Everything you ever wanted in a counter chip. Features: Direct LED segment drive, single power supply (12 VDC TYP.), six decades up/down, pre-loadable counter, separate pre-loadable compare register with compare output, BCD AND seven segment outputs, internal scan oscillator, CMOS compatible, leading zero blanking. 1MHZ. count input frequency. Very limited qty. **WITH DATA SHEET**

WESTERN DIGITAL UART

No. TR1602B. 40 pin DIP
This is a very powerful and popular part.

NEW-\$6.95 with data
LIMITED QUANTITY



RESISTOR ASSORTMENT

1/4 W 5% and 10%
PC leads. A good mix of values. 200/\$2.

1702A 2K ERASEABLE PROMS - \$6.95

We tell it like it is. We could have said these were factory new, but here is the straight scoop. We bought a load of new computer gear that contained a quantity of 1702 A's in sockets. We carefully removed the parts, verified their quality, and are offering them on one heck of a deal. First come, first served. Satisfaction guaranteed! U.V. Eraseable. **\$6.95 each 4 for \$25**

TERMS:

Money Back Guarantee. No COD. Texas Residents add 5% tax. Add 5% of order for postage and handling. Orders under \$10. add 75c. Foreign orders: US Funds ONLY!

SLIDE SWITCH ASSORTMENT



Our best seller. Includes miniature and standard sizes, single and multi-position units. All new, first quality, name brand. Try one package and you'll reorder more. **SPECIAL 12/\$1.**

MOTOROLA POWER DARLINGTON

Back in Stock!

Like MJ3001. NPN 80V. 10A. HFE 6000 TYP. TO-3 case. We include a free 723C volt reg. with schematic for power supply. **SPECIAL-\$1.99**

CALL YOUR BANK AMERICARD OR MASTER CHARGE ORDER IN ON OUR CONTINENTAL UNITED STATES TOLL FREE WATTS:

1-800-527-3460
Texas Residents Call Collect
214/271-0022

S.D. SALES CO.
P.O. BOX 28810 C
Dallas, Texas 75228

For orders over \$15.00 Choose \$1.00 FREE mdse.

CIRCLE 73 ON FREE INFORMATION CARD

MARCH 1977

VOICE ACTIVATED SWITCH



99c Activates devices such as lights, tape recorders etc. Comes with 5' leads 3 x 1" Operates on 4.5 VDC. Shpg. wt 1/2 lb.

Reg. 1.98 **XM-556**

Volume Controls



VC-274

49c

- 12 Piece Kit
- Less Than 5c Each
- 12 Popular Values
- Various dia. & lengths
- Some Have Switches

Reg. \$1

Red LED's



5 PAK

PL-233


59c

• Large Dome Type • 10mA • 2 Volt

Emits red light. Long life, hi-quality. Shpg. wt 1/4 lb.

Reg. 1.19

TA-879 Limit 3 Pkgs. with this ad

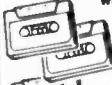

60-Minute Blank Cassettes

29c

180 minutes of recording time for less than 1c per minute. Stock up now! Shpg. wt. 1/2 lb.

Reg. 3/1.49

HARDWARE AND COMPONENTS

1/4 RPM Timing Motor 115V AC	MO-277	Reg. .89	.39
1 RPM Timing Motor 115V AC	MO-289	Reg. .89	.39
3-6V DC Hobby Motors Kit of 5	MO-333	Reg. 2.00	.59
2-Speed Motor 115V AC	MO-336	Reg. 4.98	2.49
3600 RPM Motor 115V AC	MO-361	Reg. 3.00	.99
4000 RPM Appliance Motor 115V AC	MO-395	Reg. 2.98	.99
6V Panel Lamp 1-Red 1-Green	PL-065	Reg. 1.79	.79
6V 30 ma. Lamp W/Leads Pkg. 2	PL-270	Reg. .89	.59
6V Mini-Screw Base Bulb, Pkg. 2	PL-271	Reg. .69	.59
12V. Bi-pin Mini Bulbs, Pkg. 2	PL-273	Reg. 1.19	.59
12V. Cheater Cord, Pkg. of 2	WW-061	Reg. 1.29	.59
Terminal Strips, Pkg. 40 Ass'd.	XO-501	Reg. 1.30	.50
25B474 Output Transistor	TR-174	Reg. 3.79	1.19
Fairchild 703 Type IC	TR-293	Reg. .99	.39
Fairchild 717 Type IC	TR-294	Reg. .99	.39
IC Grab Bag, 10 Ass'd. Types	TR-422	Reg. 1.19	.50
Calculator IC Chip, Nortec 4202	TR-424	Reg. 6.00	2.99
SCR Grab Bag, 25 Ass'd. Types	TR-446	Reg. 2.69	.90
Cadmium Photo Cells, Pkg. of 2	TR-512	Reg. .90	.49
Motorola Amplifier IC, 8 Pin D.I.P.	TR-513	Reg. 1.29	.59
Aluminum Heat Sink 1 1/2 x 1/2 x 1/2	XM-027	Reg. .49	.29
12 Digit Calculator IC	XM-330	Reg. 6.00	1.49
20 Key Calculator Keyboard	XM-339	Reg. 2.69	1.39
3-7 Seg. L.E.D., Green, Comm. A	XM-341	Reg. 2.49	1.39
3-7 Seg. L.E.D., Yellow, Comm. A	XM-342	Reg. 2.00	1.19
3-7 Seg. L.E.D., Red, Comm. A	XM-370	Reg. 1.49	.79
Sperry 9 Digit Display	XM-399	Reg. 2.00	.99
3-7 Seg. L.E.D., Red, Comm. K	XM-414	Reg. 5.00	1.00
11 Calculator Keyboard, 20 Key	XM-524	Reg. 1.29	.59
16 Key Switch Pad, Less Keys	XM-525	Reg. 1.49	.69
23 Key Switch Pad, Less Keys	XM-528	Reg. 1.50	.49
Calculator Keys, Pkg. of 20 Ass'd.	LL-083	Reg. 1.98	1.00
455 KHz IF Transformer, Pair	SW-154	Reg. 2.19	1.49
Toggle Switch Kit, Pkg. 3 Ass'd.	SW-406	Reg. 1.79	.99
Mini Toggle Switch D.P.D.T. 3A	SW-409	Reg. 1.29	.69
See-Saw Rocker Switch D.P.D.T. 3A	SW-423	Reg. 1.89	1.09
Center-Off Mini Toggle S.P.D.T. 3A	SW-460	Reg. .29	.19
Three Level Push Switch, 8A	SW-463	Reg. 1.69	.49
Mercury Switch, S.P.D.T. 5A	SW-641	Reg. 2.00	.69
117V AC Relay, Mini, S.P.D.T. 2A	SW-773	Reg. .59	.49
Mini Rocker Switch, S.P.S.T. 1A	SW-814	Reg. 1.59	.69
Leaf Switch, S.P.D.T. 5A, Pkg. 2	SW-838	Reg. .90	.40
Heavy Duty Toggle, 3 P.D.T. 10A	SW-840	Reg. 2.00	.69
117V AC Solenoid, 1" Travel	SW-846	Reg. 1.20	.59
Slide Switch, D.P.D.T. Pkg. of 2	SW-850	Reg. 1.29	.79
11 PC Slide Switch Kit	TF-048	Reg. 3.00	.90
6 & 12V. Trans., 117V. PRI. 5A SEC.	TF-050	Reg. 1.79	.60
12 & 10V. Trans., 117V. PRI. 2A SEC.	TT-076	Reg. 2.00	1.29
6.3V. Trans., 117V. PRI. 1A. SEC.			

FREE CATALOG

Olson electronics

260 SO. FORGE ST.
DEPT. LV, AKRON, OHIO 44327

NAME _____

ADDRESS _____ CITY STATE _____

ZIP _____

Send Olson Catalog

Free PA Catalog Ship The Following

How Many	Stock Number	Description	Price	Total

ENCLOSE POSTAGE AND SALES TAX

Send for your information packet today -

TV games kits P/C boards

visulox P.O. Box 4204R Mountain View, CA 94040

which also includes circuit functions, component line-up, and accessories. Information Packet \$1.00 (refundable with order).

ECONOMY kits, TVT-III (4 page) \$114.75; screen read \$11.65; manual cursor \$9.50; cassette interface \$28.50; motion detector (ultrasonic) assembled \$16.95. Free catalog. **ELECTRONIC DISCOUNT SALES, 138 N. 81st Street, Mesa, AZ 85207**

OSCILLOSCOPE kit. Assemble your own 5" scope. Combined simple instructions and operating manual included. Special price \$69.95. Send check or M/O: **ELECTRONIC TECHNICAL INSTITUTE, Little Falls, NJ 07424, Dept. 2739**

CIRCUIT BOARDS

Circuit boards made to order from your drawings and photos. Johnson CB's and Duo-Scan monitors - Ten-Tec equipment enclosures. M-Tron crystals - National Semi-conductor Calculators - Custom Digital Designing - Hickok Test Equipment - Consumer Cable and Wire

All products sold below suggested retail prices. Send \$5.00 for catalog, refundable on first order.

Special of the month	Johnson Duo-Scan Monitor	\$169.95
R/S Electronics	Suggested retail	88.00
1019 E. Clay	R/S Electronics price	80.00
Decatur, IL 62521	Special this month	3.00 each
Ill. reg. add 5% tax	Crystals for Duo-Scan (specify desired frequencies)	

RADAR detector kit. Ultra sensitive X-Band police radar detector kit. Complete instruction booklet. Completed unit price \$89.95. Kit price \$39.00. Send check or money order to: **RADAR KIT, P.O. Box 31433, Dallas, TX 75231, Department K1**

LIGHT pen cursor control for TVT-II works with or without cursor boards. Complete kit \$12.50. **Micro-Lite, RFD 1, Box 30, North Stonington, CT 06359**

BUSINESS OPPORTUNITIES

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do. **Barta-BO, Box 248, Walnut Creek, CA 94597.**

FOR SALE

SEMICONDUCTOR and parts literature, J. & J. ELECTRONICS, Box 1437R, Winnipeg, Manitoba, Canada. U.S. Inquiries Invited.

IC-101 CURVE TRACER

STILL BEING THE LOWEST COST FULL FUNCTION CURVE TRACER ON THE MARKET. ATTACHES TO YOUR SCOPE IN SECONDS, USED BY EDUCATORS, PROFESSIONALS AND HOBBYISTS ALL OVER THE WORLD. 90 DAY MONEYBACK GUARANTEE.

lab science

STILL ONLY \$39.50 ADD \$2 P&H

COLOR. RES. ADD 3% SALES TAX

PO BOX 1972, BOULDER, COLO. 80306

SURPRISE! Build Inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! **GBS, Box 100B, Greenbank, WV 24944**

MICRO MINI MIKE™ WIRELESS MICROPHONE

World's smallest! solid state, self-contained. Picks up and transmits most sounds without wires up to 300 ft. through FM Radio. Use as mike, amp, alarm & alert sys. hot line, baby sitter, etc. Money back guar. B/A, M/C cds, COD ok. \$18.95 plus \$1.00 post. & hdlg. Calif. res. add tax. Mail orders only. Qty. Disc. Avail. **AMC SALES, INC. Dept. , Box 928 - Downey, Calif. 90241**

FREE catalog. IC's, Semi's. **CORONET ELECTRONICS, 649A Notre Dame W., Montreal, Que. Canada, H3C-1H8. US Inquiries.**

U.S. GOV'T ELECTRONIC SURPLUS

Nationally Known - World Famous **SURPLUS CENTER** offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition costs.


AUTOMATIC BATT. CHARGER



• (ITEM #11-018) - Charges 12-volt batteries at 2-ampere rate. Turns off when battery reaches full charge. Turns on when battery is low, automatically. Can be mounted permanently in engine compartment. 5 1/2" x 3 3/4" x 2 1/4"

\$12.95 (3 1/2 lbs.)

SNAP-AROUND VOLT-AMMETER

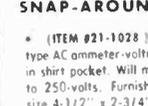

• (ITEM #21-1028) - "MINIPROBE" clamp type AC ammeter-voltmeter. Small enough to carry in shirt pocket. Will measure 0 to 50 amperes, 0 to 250-volts. Furnished with test leads. Overall size 4-1/2" x 2-3/4" x 1" (1 lb.) List \$33.00

\$22.95


STANDARD DIAL TELEPHONE



• (ITEM #715) - Same as used on commercial systems in U.S.A. Use as extension to private system. Connect several together for local intercom system. Instructions furnished.

\$8.79 Original Cost \$24.50 (9 lbs.)

RUNNING TIME METER

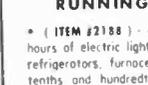

• (ITEM #2188) - Record number of operating hours of electric lights, electrical devices such as refrigerators, furnaces, etc. Records total hours, tenths and hundredths to 9,999.99 hours. For 115-volts, 60-cycles 4 1/4" x 3" x 2 1/2" (12 lbs.)

Cost \$29.00 **\$4.39**

SPECIAL SALE Correspondence Course In ELECTRICAL ENGINEERING



Prepaid in U.S.A. **\$11.79** Outside U.S.A. **\$12.79**

• (ITEM #9-181) - Technical training at low cost! Lincoln Engineering School suspended Correspondence Course because of rising costs. Limited number of Electrical Engineering Courses are available without exams and grading services. Consists of fifteen lesson books, each with associated exams and standard answers. Book showing how to build prize-winning Home Experimental Laboratory Bench included at no extra cost.

ALL ITEMS SHIPPED F.O.R. LINCOLN, NEBR.
Order Direct from Ad - Send For FREE Catalog

SURPLUS CENTER

DEPT. RE-037 LINCOLN, NEBR. 68501

CIRCLE 20 ON FREE INFORMATION CARD

CANADIAN discount and factory clearouts catalog. Top brand stereo equipment, calculators, test gear, CB & communications, telephones. Factory dumps—government surplus. Amazing bargains. Unusual items. Rush \$1. **ETCO-RE, 521 5th Ave., NYC, 10017**

AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning, Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus **INFO UNLTD PARTS SERVICE, Catalog \$1. Information Unlimited, Box 626, Lord Jeffery Court, Amherst, N.H. 03031.**

RADIO & TV tubes 36c each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. **CORNELL, 4217-E University, San Diego, CA 92105**

MANUALS for Govt. surplus radios, test sets, scopes, List 50c (coin). **BOOKS, 7218 Roanoke Drive, Washington, DC 20021**

Burglar. Smoke Fire Alarm Catalog

• Billions of dollars lost annually due to lack of protective warning alarms.

FREE CATALOG Shows you how to protect your home, business and person. Wholesale prices. Do-it-yourself. Free engineering service.



Burdex Security Co.

Box 82209 Dept. RE Lincoln, Ne. 68501

6 Digit LED Clock Kit - 12/24 hr.

\$9.95 QTY. 12
ea. OR MORE

\$10.95 QTY.
ea. 6-11

\$11.95 QTY.
ea. 1-5

KIT INCLUDES
 • INSTRUCTIONS
 • QUALITY COMPONENTS
 • 50 or 60 Hz OPERATION
 • 12 or 24 HR OPERATION

6-LED Readouts(FND-359 Red, com. cathode)
 1-MM5314 Clock Chip (24 pin)
 13 Transistors
 3 Switches
 6 Capacitors
 5 Diodes
 9 Resistors
 24 Molex pins for IC socket

LARGE .4" DIGITS!
 ORDER KIT #850-4
 AN INCREDIBLE VALUE!

"Kit #850-4 will furnish a complete set of clock components as listed. The only additional items required are a 7-12 VAC transformer, a circuit board and a cabinet, if desired."

Printed Circuit Board for kit # 850-4 (etched & drilled fiberglass) \$2.95
 Mini-Brite Red LED's (for color in clock display) pkg. of 5 1.00
 Molded Plug Transformer 115/10 VAC (with cord) 2.50
 NOTE: Entire Clock may be assembled on one PC Board or Board may be cut to remote display.
 Kit # 850-4 will fit Plexiglas Cabinet II.

6 Digit-LED Clock-Calendar-Alarm Kit

This is a complete, top of the line, Kit for the person that wants the best. Some of the many features and options are: 12/24 time, 28-30-31 day calendar, alternates time (8 sec) and date (2 sec) or can display time only and date on demand, 24 hr alarm - 10 minute snooze, alarm set indicator, 50/60 HZ. line operation or use with Xtal time base (#TB-1), built in OSC for battery back-up / AC failure, Aux. timer, CHOICE OF DIGITS.

Kit #7001B 6 - .4" Digits \$39.95
 Kit #7001C 4 - .6" Digits & 2-" [Seconds] \$42.95
 Kit #7001X 6 - .6" Digits \$45.95

Kits are complete (less cabinet) including PC boards, power supply, IC socket, 9 switches, 16 transistors and all parts required for above features and options [All #7001 Kits Will Fit Cabinet I]

MOBILE LED CLOCK

12 OR 24-HOUR OPERATION

12 VOLT AC or DC POWERED FOR FIXED OR MOBILE OPERATION.

SIX LARGE .4" DIGITS!

KIT OR ASSEMBLED



MODEL 2001

ACCURATE TIME WITH ADJUSTABLE XTAL TIME BASE

Approx. Size: 1 3/4" H x 4" W x 4 1/2" D

BATTERY BACK-UP FOR POWER FAILURE OR TRANSPORTING FROM HOUSE TO CAR ETC.

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM.
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24 Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOLDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY - TWO WIRE NO POLARITY HOOK UP
- OPTIONAL CONNECTION TO BLANK DISPLAY (Use When Key Off in Car, Etc.)
- TOP QUALITY PC BOARDS & COMPONENTS • EXCELLENT INSTRUCTIONS
- MOUNTING BRACKET INCLUDED

KIT # 2001 COMPLETE KIT (Less 9V Battery) **29.95** EA 3 OR MORE **\$27.95** EA 115 VAC Power Pack #AC-1 **\$25.00** EA

ASSEMBLED UNITS WIRED & TESTED (ORDER # 2001 WT (LESS 9V BATTERY) **\$39.95** EA 3 OR MORE **\$37.95** EA Assembled Units May Be Mixed With Kits for Qty. Price

CPU 8080A

\$19.95 ea.

NS8080AD

Micro Processor Chip

Prime National LSI

40 Pin socket

\$.50 with each 8080A!

450 ns MEMORY

Fairchild 1K Ram

low, low, low power.

2102L1PC \$1.95ea.

25-99 \$1.75 ea.

100-199 \$1.60 ea.

200 or more \$1.45 ea.

JUMBO RED LED's 12/\$1.00 50/\$3.95

PRINTED CIRCUIT BOARDS for CT-7001 Kits sold separately with assembly info. PC Boards are drilled Fiberglass, solder plated and screened with component layout. Specify for # 7001B or # 7001C (Set of 2) \$7.95

JUMBO DIGIT CLOCK KIT

A complete Kit (less Cabinet) featuring: six .5" digits, MM5314 IC, 12/24 Hr. time, 50/60 HZ., Plug-Transformer, Line Cord, Switches, and all Parts.

[Ideal Fit in Cabinet II] **\$19.95** 2/\$38. ea.

JUMBO DIGIT CONVERSION KIT

Convert small digit LED clock to large .5" displays. Kit includes 6-.5" LED's, Multiplex PC Board & easy hook-up info.

Kit #JD-1CC For common Cathode **\$9.95** ea. 2/\$19.
 Kit #JD-1CA For common Anode

SEE THE WORKS Clock Kit

Clear Plexiglas Stand

- 6Big 4" digits
- 12 or 24 hr. time
- 3 set switches (back)
- Plug transformer
- all parts included



Plexiglas is Pre-cut & drilled Size: 6" H, 4 1/2" W, 3" D
A SUPER LOOKING CLOCK!
 Kit #850-4-CP **\$23.50** ea. 2/\$45.

Fairchild Super Digit FND-359

4" Char. Mt. 7 segment LED RED Com. Cath. Direct pin replacement for popular FND-70.
95¢ ea, 10/\$8.50
100/\$79.00

SET OF 6 FND-359 WITH MULTIPLEX PC BOARD \$6.95

25 AMP BRIDGE \$1.95 ea. 3/\$5.00

TELEPHONE FORMAT KEYBOARD BY Chometrics

2-1/4" x 3" 5/32" thick **\$4.95** 6/\$28.

Visit Our Store at 823 S. 21st. Avenue, Hollywood, Fl.

SCHOTTKY
 TTL
 74500 \$35
 74501 40
 74504 55
 74595 60
 74509 56
 74510 40
 74520 50
 74522 45
 74540 45
 74550 45
 74551 55
 74560 85
 74564 56

LED DRIVERS
 7447 \$9.95
 7448 \$9.95
 75491 \$6.66
 75492 \$6.66

VOLTAGE REGULATORS
 LM 309H TO 5 \$9.95
 LM 309K TO 3 1.25

DTL
 930 \$0.09
 932 \$0.09
 937 \$0.09

DIGITAL CLOCK IC's
 MM5312 \$4.95
 MM5314 3.95
 MM5375 AB 3.95
 CT 7001 7.95
 CT 7002 13.95
 50380 2.95
 MM5369 2.50

XTAL
 3.579545 MHZ \$1.95

PRESCALE
 119C0DC \$15.95
 95H90 9.95

DIODES
 IN 4002 1A, 100 PIV 12/\$1.00
 IN 4005 1A, 600 PIV 17/\$1.00
 IN 4007 1A, 1000 PIV 10/\$1.00
 RECTIFIER 2.5A, 1000 PIV 4/\$1.00
 IN 914 SIL SIGNAL 20/\$1.00
 IN 4148 (1N914 Equiv.) 20/\$1.00
 DYAC 28V 4/\$1.00

PLUG TRANSFORMERS
 12VAC at 150 MA \$2.50
 12VAC at 500 MA 3.50
 7 VAC at 1.75VA 2.50

LINEAR
 555 TIMER 2/\$1.00
 556 DUAL TIMER .95
 565 PLL 1.75
 566 FUNCTION GEN. 1.75
 567 TONE DECODDER 1.75

IC SOCKETS
 PINS 1-24 \$25 100
 8 \$25 \$22 \$20
 14 25 22 20
 16 21 28 26
 18 31 28 26
 24 50 45 40
 28 60 55 50
 40 75 70 65

COMPUTER
 8080A CPU 19.95
 1702 E Prom 8.95
 5203 E Prom 8.95
 2102L1PC 1K Ram 1.95

EXAR
 XR 2556 \$1.75
 XR 2567 \$1.95

TRANSISTORS
 2N2222 TO-18 5/\$1.00
 2N2514 TO-5 2/\$1.00
 2N2712 TO-98 5/\$1.00
 2N3415 TO-92 5/\$1.00
 2N3704 TO-92 5/\$1.00
 2N4400 TO-92 5/\$1.00
 2N4125 TO-92 5/\$1.00
 2N4249 TO-92 5/\$1.00
 2N4437 TO-92 5/\$1.00
 2N6027 PUT 2/\$1.00
 2N5457 N J-Fet 2/\$1.00

DISCRETE LED'S
 JUMBO RED
 12/\$1.00
 50/\$3.95
 100/\$7.50

PC TRIM POTS
 25K 6/\$1.00
 4.7K 6/\$1.00
 95c
 4/\$3.00

NYLON WIRE TIES
 8" TIE-WRAP 100/\$1.95
 4" TIE-WRAP 100/\$1.75

MOLEX PINS
 REEL OF 1000 \$8.50
 STRIP OF 100 1.25

MISC. PRIME IC's
 FAIRCHILD 9315 (74161) \$9.95
 75234 DUAL COARSE SENSE AMP 1.50
 MM502H TO-5 SHIFTER 95c

7-SEG LED COMMON CATHODE

COLOR HT. DEC PT. P.REA
 FND-359 RED 4" RHDP \$9.95
 FND-503 RED 5" RHDP \$1.35
 DL-750 RED 6" LHDP \$1.95
 XAN-654 GREEN 6" NDP \$1.95
 XAN-664 RED 6" NDP \$1.95

COMMON ANODE

DL-747 RED 6" LHDP \$1.95
 MAN-72 RED 3" LHDP \$1.25
 XAN-81 YELLOW 3" RHDP \$1.75
 XAN-351 GREEN 3" RHDP \$1.50
 XAN 361 RED 3" RHDP \$1.50
 XAN 362 RED 3" LHDP \$1.50
 XAN-662 RED 6" NDP \$1.95
 XAN-692 RED 6" NDP \$1.95

Form Inexpensive Sockets 100 for \$1.25 Reel of 1000 - \$8.50

60 HZ. XTAL TIME BASE KIT

Will enable Digital Clock or Clock Cal. Kits to operate from 12VDC. Uses MM5369 and 3.58MHZ. XTAL. Req. 5-15VDC/2.5 MA. 1" x 2" PC Board. Easy 3 wire hookup Accuracy: +/- 2 PPM
 #TB-1 [adjustable]
 Complete kit \$4.95 ea
 Wired & Cal. \$9.95 ea

60 HZ. XTAL TIME BASE KIT

PLEXIGLAS CABINETS

Black, White or Clear Cover

Great for Clocks or any LED Digital project. Clear-Red Chassis serves as Bezel to increase contrast of digital displays.



CABINET I

3" H, 6 1/4" W, 5 1/2" D

CABINET II

2 1/2" H, 5" W, 4" D

\$6.50 ea. 2/\$12. ANY SIZE! 2 1/2" H, 5" W, 4" D COLOR

3" x 6" x 1 1/8" RED OR GREY PLEXIGLAS FOR DIGITAL BEZELS **95¢** ea. **4/\$3**

OPTOELECTRONICS, inc.
 BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056



ORDER BY PHONE OR MAIL
 COD ORDERS WELCOME
 [\$1.00 CHG.]
 Orders Under \$15 Add \$1.00 Handling
 Fla. Res. Please Add 4% Sales Tax.

WE PAY ALL SHIPPING IN CONTINENTAL USA - OTHERS ADD 5% TO 10% FOR AIRMAIL

QUEST ELECTRONICS

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

7400TL	59	NE540L	3.90	CD4044	2.00	8T20	4.00
SN7400N	17	SN74157A	1.75	CD4049	52	8T25	2.75
SN7402N	17	SN74158	1.75	CD4086	85	8T28	3.20
SN7404N	17	SN74159	1.75	CD4088	25	8T37	2.45
SN7410N	17	SN74160	1.75	CD4091	40	8T48	4.45
SN7418N	63	SN74161	1.75	CD4092	40	8T52	4.45
SN7420N	17	SN74162	1.75	CD4093	40	8T58	4.45
SN7430N	20	SN74163	1.75	CD4094	40	8T62	4.45
SN7432N	20	SN74164	1.75	CD4095	40	8T68	4.45
SN7438N	45	SN74165	1.75	CD4096	40	8T72	4.45
SN7447N	60	SN74166	1.75	CD4097	40	8T78	4.45
SN7450N	17	SN74167	1.75	CD4098	40	8T82	4.45
SN7474N	35	SN74168	1.75	CD4099	40	8T88	4.45
SN7476N	45	SN74169	1.75	CD4100	40	8T92	4.45
SN7490N	30	SN74170	1.75	CD4101	40	8T98	4.45
SN7498N	45	SN74171	1.75	CD4102	40	8T102	4.45
SN7499N	45	SN74172	1.75	CD4103	40	8T108	4.45
SN7499N	45	SN74173	1.75	CD4104	40	8T112	4.45
SN7499N	45	SN74174	1.75	CD4105	40	8T118	4.45
SN7499N	45	SN74175	1.75	CD4106	40	8T122	4.45
SN7499N	45	SN74176	1.75	CD4107	40	8T128	4.45
SN7499N	45	SN74177	1.75	CD4108	40	8T132	4.45
SN7499N	45	SN74178	1.75	CD4109	40	8T138	4.45
SN7499N	45	SN74179	1.75	CD4110	40	8T142	4.45
SN7499N	45	SN74180	1.75	CD4111	40	8T148	4.45
SN7499N	45	SN74181	1.75	CD4112	40	8T152	4.45
SN7499N	45	SN74182	1.75	CD4113	40	8T158	4.45
SN7499N	45	SN74183	1.75	CD4114	40	8T162	4.45
SN7499N	45	SN74184	1.75	CD4115	40	8T168	4.45
SN7499N	45	SN74185	1.75	CD4116	40	8T172	4.45
SN7499N	45	SN74186	1.75	CD4117	40	8T178	4.45
SN7499N	45	SN74187	1.75	CD4118	40	8T182	4.45
SN7499N	45	SN74188	1.75	CD4119	40	8T188	4.45
SN7499N	45	SN74189	1.75	CD4120	40	8T192	4.45
SN7499N	45	SN74190	1.75	CD4121	40	8T198	4.45
SN7499N	45	SN74191	1.75	CD4122	40	8T202	4.45
SN7499N	45	SN74192	1.75	CD4123	40	8T208	4.45
SN7499N	45	SN74193	1.75	CD4124	40	8T212	4.45
SN7499N	45	SN74194	1.75	CD4125	40	8T218	4.45
SN7499N	45	SN74195	1.75	CD4126	40	8T222	4.45
SN7499N	45	SN74196	1.75	CD4127	40	8T228	4.45
SN7499N	45	SN74197	1.75	CD4128	40	8T232	4.45
SN7499N	45	SN74198	1.75	CD4129	40	8T238	4.45
SN7499N	45	SN74199	1.75	CD4130	40	8T242	4.45
SN7499N	45	SN74200	1.75	CD4131	40	8T248	4.45
SN7499N	45	SN74201	1.75	CD4132	40	8T252	4.45
SN7499N	45	SN74202	1.75	CD4133	40	8T258	4.45
SN7499N	45	SN74203	1.75	CD4134	40	8T262	4.45
SN7499N	45	SN74204	1.75	CD4135	40	8T268	4.45
SN7499N	45	SN74205	1.75	CD4136	40	8T272	4.45
SN7499N	45	SN74206	1.75	CD4137	40	8T278	4.45
SN7499N	45	SN74207	1.75	CD4138	40	8T282	4.45
SN7499N	45	SN74208	1.75	CD4139	40	8T288	4.45
SN7499N	45	SN74209	1.75	CD4140	40	8T292	4.45
SN7499N	45	SN74210	1.75	CD4141	40	8T298	4.45
SN7499N	45	SN74211	1.75	CD4142	40	8T302	4.45
SN7499N	45	SN74212	1.75	CD4143	40	8T308	4.45
SN7499N	45	SN74213	1.75	CD4144	40	8T312	4.45
SN7499N	45	SN74214	1.75	CD4145	40	8T318	4.45
SN7499N	45	SN74215	1.75	CD4146	40	8T322	4.45
SN7499N	45	SN74216	1.75	CD4147	40	8T328	4.45
SN7499N	45	SN74217	1.75	CD4148	40	8T332	4.45
SN7499N	45	SN74218	1.75	CD4149	40	8T338	4.45
SN7499N	45	SN74219	1.75	CD4150	40	8T342	4.45
SN7499N	45	SN74220	1.75	CD4151	40	8T348	4.45
SN7499N	45	SN74221	1.75	CD4152	40	8T352	4.45
SN7499N	45	SN74222	1.75	CD4153	40	8T358	4.45
SN7499N	45	SN74223	1.75	CD4154	40	8T362	4.45
SN7499N	45	SN74224	1.75	CD4155	40	8T368	4.45
SN7499N	45	SN74225	1.75	CD4156	40	8T372	4.45
SN7499N	45	SN74226	1.75	CD4157	40	8T378	4.45
SN7499N	45	SN74227	1.75	CD4158	40	8T382	4.45
SN7499N	45	SN74228	1.75	CD4159	40	8T388	4.45
SN7499N	45	SN74229	1.75	CD4160	40	8T392	4.45
SN7499N	45	SN74230	1.75	CD4161	40	8T398	4.45
SN7499N	45	SN74231	1.75	CD4162	40	8T402	4.45
SN7499N	45	SN74232	1.75	CD4163	40	8T408	4.45
SN7499N	45	SN74233	1.75	CD4164	40	8T412	4.45
SN7499N	45	SN74234	1.75	CD4165	40	8T418	4.45
SN7499N	45	SN74235	1.75	CD4166	40	8T422	4.45
SN7499N	45	SN74236	1.75	CD4167	40	8T428	4.45
SN7499N	45	SN74237	1.75	CD4168	40	8T432	4.45
SN7499N	45	SN74238	1.75	CD4169	40	8T438	4.45
SN7499N	45	SN74239	1.75	CD4170	40	8T442	4.45
SN7499N	45	SN74240	1.75	CD4171	40	8T448	4.45
SN7499N	45	SN74241	1.75	CD4172	40	8T452	4.45
SN7499N	45	SN74242	1.75	CD4173	40	8T458	4.45
SN7499N	45	SN74243	1.75	CD4174	40	8T462	4.45
SN7499N	45	SN74244	1.75	CD4175	40	8T468	4.45
SN7499N	45	SN74245	1.75	CD4176	40	8T472	4.45
SN7499N	45	SN74246	1.75	CD4177	40	8T478	4.45
SN7499N	45	SN74247	1.75	CD4178	40	8T482	4.45
SN7499N	45	SN74248	1.75	CD4179	40	8T488	4.45
SN7499N	45	SN74249	1.75	CD4180	40	8T492	4.45
SN7499N	45	SN74250	1.75	CD4181	40	8T498	4.45
SN7499N	45	SN74251	1.75	CD4182	40	8T502	4.45
SN7499N	45	SN74252	1.75	CD4183	40	8T508	4.45
SN7499N	45	SN74253	1.75	CD4184	40	8T512	4.45
SN7499N	45	SN74254	1.75	CD4185	40	8T518	4.45
SN7499N	45	SN74255	1.75	CD4186	40	8T522	4.45
SN7499N	45	SN74256	1.75	CD4187	40	8T528	4.45
SN7499N	45	SN74257	1.75	CD4188	40	8T532	4.45
SN7499N	45	SN74258	1.75	CD4189	40	8T538	4.45
SN7499N	45	SN74259	1.75	CD4190	40	8T542	4.45
SN7499N	45	SN74260	1.75	CD4191	40	8T548	4.45
SN7499N	45	SN74261	1.75	CD4192	40	8T552	4.45
SN7499N	45	SN74262	1.75	CD4193	40	8T558	4.45
SN7499N	45	SN74263	1.75	CD4194	40	8T562	4.45
SN7499N	45	SN74264	1.75	CD4195	40	8T568	4.45
SN7499N	45	SN74265	1.75	CD4196	40	8T572	4.45
SN7499N	45	SN74266	1.75	CD4197	40	8T578	4.45
SN7499N	45	SN74267	1.75	CD4198	40	8T582	4.45
SN7499N	45	SN74268	1.75	CD4199	40	8T588	4.45
SN7499N	45	SN74269	1.75	CD4200	40	8T592	4.45
SN7499N	45	SN74270	1.75	CD4201	40	8T598	4.45
SN7499N	45	SN74271	1.75	CD4202	40	8T602	4.45
SN7499N	45	SN74272	1.75	CD4203	40	8T608	4.45
SN7499N	45	SN74273	1.75	CD4204	40	8T612	4.45
SN7499N	45	SN74274	1.75	CD4205	40	8T618	4.45
SN7499N	45	SN74275	1.75	CD4206	40	8T622	4.45
SN7499N	45	SN74276	1.75	CD4207	40	8T628	4.45
SN7499N	45	SN74277	1.75	CD4208	40	8T632	4.45
SN7499N	45	SN74278	1.75	CD4209	40	8T638	4.45
SN7499N	45	SN74279	1.75	CD4210	40	8T642	4.45
SN7499N	45	SN74280	1.75	CD4211	40	8T648	4.45
SN7499N	45	SN74281	1.75	CD4212	40	8T652	4.45
SN7499N	45	SN74282	1.75	CD4213	40	8T658	4.45
SN7499N	45	SN74283	1.75	CD4214	40	8T662	4.45
SN7499N	45	SN74284	1.75	CD4215	40	8T668	4.45
SN7499N	45	SN74285	1.75	CD4216	40	8T672	4.45
SN7499N	45	SN74286	1.75	CD4217	40	8T678	4.45
SN7499N	45	SN74287	1.75	CD4218	40	8T682	4.45
SN7499N	45	SN74288	1.75	CD4219	40	8T688	4.45
SN7499N	45	SN74289	1.75	CD4220	40	8T692	4.45
SN7499N	45	SN74290	1.75	CD4221	40	8T698	4.45
SN7499N	45	SN74291	1.75	CD4222	40	8T702	4.45
SN7499N	45	SN74292	1.75				

INTERNATIONAL ELECTRONICS UNLIMITED

10% OFF WITH \$25 ORDER
15% OFF WITH \$100 ORDER
 THESE DISCOUNTS APPLY TO TOTAL OF ORDER — SPECIALS INCLUDED

TTL					
7400	.13	7451	.17	74153	.89
7401	.16	7453	.17	74154	1.20
7402	.15	7454	.17	74155	.97
7403	.15	7460	.35	74156	.97
7404	.16	7464	.35	74157	.99
7405	.19	7465	.30	74158	1.79
7406	.20	7470	.30	74160	1.23
7407	.28	7472	.30	74161	.97
7408	.18	7473	.35	74162	1.39
7409	.19	7474	.28	74163	1.09
7410	.16	7475	.49	74164	.99
7411	.25	7476	.30	74165	.99
7413	.43	7483	.68	74166	1.25
7414	.65	7485	.88	74170	2.10
7416	.35	7486	.40	74173	1.49
7417	.35	7489	2.25	74174	1.23
7420	.16	7490	.43	74175	.97
7422	.30	7491	.75	74176	.89
7423	.29	7492	.48	74171	.84
7425	.27	7493	.48	74180	.90
7426	.26	7494	.78	74181	2.45
7427	.29	7495	.79	74182	.79
7430	.20	7496	.79	74184	1.90
7432	.23	74100	.98	74185	2.20
7437	.25	74105	.44	74187	5.75
7438	.25	74107	.37	74190	1.15
7440	.15	74121	.38	74191	1.25
7441	.89	74122	.38	74192	.95
7442	.59	74123	.65	74193	.85
7443	.73	74125	.54	74194	1.25
7444	.73	74126	.58	74195	.74
7445	.73	74132	.89	74196	1.25
7446	.81	74141	1.04	74197	.73
7447	.79	74145	1.04	74198	1.73
7448	.79	74150	.97	74199	1.69
7450	.17	74151	.79	74200	5.45

LOW POWER

74100	.29	74151	.29	74190	1.40
74102	.29	74155	.29	74191	1.20
74103	.23	74171	.29	74193	1.50
74104	.29	74172	.45	74195	1.50
74106	.29	74173	.56	74198	2.25
74110	.29	74174	.54	74164	2.25
74120	.29	74178	.75	74165	2.30
74130	.29	74185	1.09		
74142	1.39	74186	.65		

LOW POWER SCHOTTKY

741500	.36	741532	.38	741595	2.09
741502	.36	741540	.45	7415107	.59
741504	.36	741542	1.40	7415164	2.20
741508	.36	741574	.59	7415193	2.20
741510	.36	741590	1.30	7415197	2.20
741520	.36	741593	1.30		

HIGH SPEED

74100	.25	74122	.25	74161	.25
74101	.25	74140	.25	74162	.25
74104	.25	74144	.25	74174	.39
74108	.25	74150	.25	741101	.58
74110	.25	74152	.25	741102	.58
74111	.25	74153	.25	741103	.60
74120	.25	74155	.25	741106	.72
74121	.25	74160	.25	741108	.72

SCHOTTKY

74500	.59	74508	.68	74522	.65
74502	.59	74510	.65	74532	.68
74503	.59	74520	.65	74574	.68
74504	.72				

8000 (NATIONAL)

8091	.61	8230	1.49	8811	.65
8092	.61	8230	2.19	8812	1.02
8095	1.25	8236	1.49	8822	2.19
8121	.80	8530	1.16	8830	2.19
8123	1.43	8552	2.19	8831	2.19
8200	2.33	8563	.62	8836	.29
8214	1.49	8810	.70	8860	1.19

8000 (SIGNETICS)

8263	5.79	8267	2.59		
------	------	------	------	--	--

9000

9002	.40	9309	.79	9601	.61
9301	1.03	9312	.79	9602	.79

DVM CHIP 4 1/2 DIGIT
 MM5330 — P channel device provides all logic for 4 1/2 digit volt meter. 16 pin DIP with data **\$9.95**

IC BREADBOARD
 Accommodates 5 1/4 pin IC's with additional interconnection holes. 1/16" phenolic with silver plated copper circuits. 2 5/16" x 1 6/16" **\$1.60 ea.**

UNIVERSAL BREADBOARD
 Silver plated copper circuit board 3 3/16" x 5 1/16" 2 rows of 27 holes for DIP IC's — space for transistors, resistors & capacitors. Versatile and simple for bread-boarding IC circuits **\$1.50 ea.**

SHIFT REGISTERS

MM5011	1024 bit accum. dyn.	1.75
MM5016	500/512 bit dyn.	1.59
SLS-4025	Quad 25 bit	.99
7504	1024 bit multiple read dyn.	3.95

IC SOCKETS
Solder Tail - low profile

8 pin	\$.17	24 pin	.42
14 pin	.20	28 pin	.59
16 pin	.22	40 pin	.69
18 pin	.29		

WIRE WRAP - gold plate
 14 pin .49

AUTO CLOCK KIT
 6 digit .375" red led's
 Operates from 12V DC or AC
 Crystal control for high accuracy
 Supplied with case & mounting bracket
 Contains internal 9V battery for operation of timing circuit (without display) when removed temporarily from power.
 Uses S314 clock circuit
 Supplied with all necessary components and assembly instructions
\$33.95
COMPLETELY ASSEMBLED \$44.95

MARCH SPECIALS

2518	Hex 32 static shift reg.	\$3.95
MV108	Led clear lens TO-18	.15
7410	Triple 3 input NAND gate	.12
7430	Quad 2 input NAND buffer (o.c.)	.17
7442	BCD to decimal decoder	.39
7453	Exp. AND-OR-INVERT gate	.14
7474	Dual D flip-flop	.19
7493	4 Bit binary counter	.35
74121	One shot .29	
74153	Dual four-input multiplexer	.69
301	Hi Perf OP AMP mDIP TO-5	.21
311	Hi Perf V Comp mDIP TO-5	.69
723	V Reg DIP	.46

1702A 2048 bit static PROM elect. prog. - UV eras. 24 pin **\$6.95**

2102 1024 BIT STATIC RAM DTL/TTL comp. 16 pin **\$1.49**

99¢ SPECIALS

KEYBOARD
 20 KEYS
 2 SLIDE SW
 3" x 3 1/2"
99¢ ea.

5 VOLT REGULATOR
 340 T (7805)
 TO-220 **99¢**

CALCULATOR DISPLAY
 9 MAN 3 M ON PC BOARD
 RED 7 SEG .127" LED
 17 TERMINAL BOARD **99¢**
 1/2" x 2 1/2"

LARGE RED LED
12/99¢

OP AMP
 741
 mini DIP **5/99¢**

EDGE CONNECTOR
6/99¢
 ELCO MODULAR UNIT
 6 PIN 3 POSITION
 WIRE WRAP GOLD PLATE

MEMORIES

1101	256 bit RAM MOS 16 pin	1.39
1103	1024 bit RAM MOS dynamic 18 pin	1.95
1702A	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
2102	1024 bit RAM static 16 pin	1.95
5203	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
5260	1024 bit RAM MOS dynamic 16 pin	1.95
5261	1024 bit RAM MOS dynamic 16 pin	1.95
7489	64 bit ROM TTL 16 pin	2.25
82523	256 PROM-SCHOTTKY 16 pin	3.69
F93410	256 bit RAM bi-polar 16 pin	1.95
74187	1024 bit ROM TTL 16 pin	5.75
74200	256 bit RAM tri-state 16 pin	5.45

4 Digit Clock Kit
 MMS312 and 4 NS71 .27" displays 12-24 hours, 50-60 Hz. One P.C. board accommodates clock, displays, and all necessary transistors, resistors, capacitors, diodes, 2 switches, complete instructions and schematics for assembly.
CK4-2 \$10.95
Mark I \$13.95
 A six digit clock kit with one double sided P.C. board accommodates MMS314 clock chip and 6 FND359 .375" displays. 12-24 hour, 50-60 Hz. Contains all necessary components, 3 switches and complete assembly instructions with schematics. Connections for remote displays.

CLOCK CHIPS

MM5311	6 digit multiplexed BCD, 7 seg, 12-24 Hr, 50-60 Hz — 28 pin	4.45
MM5312	4 digit multiplexed BCD, 7 seg, 1pps, 12-24 Hr, 50-60 Hz — 24 pin	3.95
MM5314	6 digit multiplexed 12-24 Hr, 50-60 Hz 24 pin	4.45
MM5316	4 digit, 12-24 Hr, 50-60 Hz, alarm 40 pin	4.95
IS375AA	4-6 digit, 12 hour, 60 Hz snooze alarm brightness control capability, alarm tone output — 24 pin	4.95
CT7001	6 digit, 12-24 Hr, 50-60 Hz, alarm, timer and date circuits — 28 pin	6.95

DISPLAYS

MAN1	\$1.95	DISCRETE LED'S	
MAN2	1.95	ME4	\$1.29
MAN3A	.19	MV50	.12
MAN5	2.25	NSL101	.12
MAN6	2.49	NSL102	.15
MAN7	1.49	MV5020	.15
MAN8	2.25	RFD	.15
MAN66	2.25	GREEN	.15
DL10A	2.19	AMBER	.15
FND500	1.89	CLEAR	.15
NS71E	1.39		

CALCULATOR CHIPS

CT5002	12 digit, 4 function fixed decimal battery operation — 40 pin	1.95
CT5005	12 digit, 4 function plus memory, fixed decimal — 20 pin	2.49
MM5725	8 digit, 4 function, floating decimal 18 pin	1.98
MM5736	6 digit, 4 function, 9V battery operation — 18 pin	2.95
MM5738	8 digit, 5 function plus memory and constant floating decimal, 9V battery operation — 21 pin	3.45
MM5739	9 digit, 4 function, 9V battery operation — 22 pin	3.95

SPECIAL DEVICES

372	AF-IF Strip Detector DIP	2.93
546	AM Radio Receiver Subsystem DIP	.75
1310	FM Stereo Demodulator DIP	2.90
1496	Balanced Modulator-Demodulator	.99
1800	Stereo multiplexer DIP	2.48
ULN2208	FM Gain Block 34db (typ) mDIP	1.18
ULN2209	FM Gain Block 48db (typ) mDIP	1.35
2513	Character Generator 64x8x5 DIP-24	10.20
3046	Transistor Array DIP-14	.73

OPTO ISOLATORS

MCD2	Opto isolator diode	1.09
MCT2	Opto isolator transistor	.70

TANTALUM CAPACITORS
 Solid dipped +20%

.1 mfd	35V	\$.25	10 mfd	16V	\$.40
.33 mfd	35V	.25	10 mfd	25V	.45
1 mfd	35V	.25	15 mfd	10V	.40
1 mfd	20V	.25	15 mfd	20V	.45
2.2 mfd	35V	.30	22 mfd	16V	.45
3.3 mfd	35V	.30	33 mfd	10V	.40
4.7 mfd	16V	.30	47 mfd	6V	.40
6.8 mfd	6V	.30	56 mfd	6V	.45
6.8 mfd	50V	.40	150 mfd	15V	.50

MULTIPLE DISPLAYS

NSN31	3 digit .12" red LED	1.79
HP5082	5 digit .11 red LED	3.49
7405		
HP5082	4 digit .11 red LED	3.25
7414		
SP-425-09	9 digit .25 gas diode	1.79

LINEAR CIRCUITS

300	Pos V Reg (super 723) TO-5	\$.71
301	Hi Perf Op Amp mDIP TO-5	.29
302	Volt Inverter TO-5	.53
304	Neg V Reg TO-5	.71
305	Pos V Reg TO-5	.80
307	Op AMP (super 741) mDIP TO-5	.86
308	Micro Pow Op Amp mDIP TO-5	.29
109K	5V 1A regulator TO-3	1.35
310	V follower Op Amp mDIP	1.07
311	Hi perf V Comp mDIP TO-5	.95
319	Hi Speed Dual Comp DIP	1.13
1701	Neg Reg 5, 12, 10-220	1.39
170K	Neg Reg 5, 12, 10-220	1.39
322	Precision Timer DIP	1.70
324	Quad Op Amp DIP	1.52
339	Quad Comparator DIP	1.58
340K	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-3	1.69
	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	1.49
340T	Pos V reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	2.93
372	AF-IF Strip detector DIP	2.93
373	AM/FM/SSB Strip DIP	2.42
376	AF-IF Strip detector DIP	.68
380	2w Audio Amp mDIP	1.20
380-8	.5w Audio Amp DIP	1.35
381	Lo Noise Dual preamp DIP	1.75
382	Lo Noise Dual preamp DIP	1.75
531	High New rate Op Amp	2.95
540	Power driver TO-5	4.95
550	Pres V Reg DIP	.79
555	Timer mDIP	.45
556A	Dual 555 Timer DIP	1.19
568	Phase Locked Loop DIP	3.39
562	Phase Locked Loop DIP	3.39
565	Phase Locked Loop DIP TO-5	1.18
566	Function Gen mDIP TO-5	1.95
567	Tone Decoder mDIP	1.95
709	Operational AMP TO-5 or DIP	.36
710	Hi Speed Volt Comp DIP	.35
711	Dual Difference Compar DIP	.26
723	V Reg DIP	.69
733	DH, video AMPL TO-5	.82
739	Dual Hi Perf Op Amp DIP	1.07
741	Comp Op Amp mDIP TO-5	.32
747	741 Dual Op Amp DIP or TO-5	.71
748	Freq Adj 741 mDIP	.35
1458	Dual Comp Op Amp mDIP	.62
1800	Stereo multiplexer DIP	2.48
3900	Quad Amplifier DIP	.49
7524	Core Mem Sense AMPL DIP	.71
7525	Core Mem Sense AMPL DIP	.90
8038	Voltage contr. osc. DIP	4.25
8864	9 DIC Led Cath Drive DIP	2.25
75150	Dual Line Driver DIP	1.75
75451	Dual Peripheral Driver mDIP	.35
75452	Dual Peripheral Driver mDIP	.35
75453	(351) Dual Periph Driver mDIP	.35
75491	Quad Seq Driver for LED DIP	.71
75492	Hex Digit driver DIP	.80

Data included with order on request. Add \$.30 ea. if item is priced below \$1.00

FREE CATALOG AVAILABLE ON REQUEST
 Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge

Babylon-Pac super SALE! Each pac only \$1.98

All pacs are first quality (no fallout), tested and guaranteed.

Linear pac 8 assorted linear ICs in mini-DIP or 14-741 or 14-741 op amp, LM307 op amp, LM701 RI-IF amp, with data and circuits \$1.98	Flip-Flop pac 10 assorted Flip-Flops, Dual JKs, RS, T, and low power FF's, with data \$1.98	Regulators 4 LM233 DIP variable regulators, 2-40V, with data \$1.98	LED pac 10 assorted discrete LEDs--green, red, and infrared, with data \$1.98
Comparator pac 5 assorted DIP 5-LM311, 710, 711, with data \$1.98	100 Resistors 100 of any single standard value of resistors, 1/4 watt, 1% or 5% tolerance \$1.98	Trim pots 12 miniature & subminiature PCB potentiometers, assorted values from 1K to 25K, by Pioneer, Stackpole, etc. \$1.98	Capacitors 20 50V poly electrolytic capacitors, 275V electrolytic, 1R-100M, leaded, 508 unmounted, same \$1.98
Linear pac 8 assorted linear ICs in mini-DIP or 14-741 or 14-741 op amp, LM307 op amp, LM701 RI-IF amp, with data and circuits \$1.98	DIP RC Network 50 assorted 14 and 16 pin IC packages containing precision resistors and capacitors, no data available \$1.98	CMOS pac 30 untested CMOS ICs, all factory marked \$1.98	739 pac 5 linear-- Dual low noise stereo amplifier 739, with data \$1.98
Transistor pac 40 assorted 10-62 plastic transistors--PNP's and NPN's, mostly Fairchild, with data \$1.98	Buy 5 pacs for \$9.90 and pic-a-pac for \$1.00	Axial Rectifiers 30 dual power diodes, 50V, 1A, 100mA, 100V, 100mA, 100V, 100mA, 100V, 100mA \$1.98	IC Assortment 100 untested ICs, all DIP, mostly TTL--some marked, housemarked, or unmarked \$1.98

COMPUTER/PARTS BOARDS

One of the best ways to accumulate a quantity of costly parts is to remove them from computer boards. With miniaturization, good boards are getting scarce. We have several sets, that are outstanding values. set to the left contains an average of over 100 transistors, 200 diodes, 300 1/2 watt resistors, plus many zeners, and assorted caps. Semi-conductors are all RCA or TI.

STOCK NO. R9160 set of 4, \$5.00. set of 10, \$10.00

SOPHISTICATED PARTS BOARDS

This set of boards has 35 High Noise Immunity TTL ICs, 2 12 volt reed relays, 2 24 volt reed relays, 20 small signal transistors and SCRs, many large plastic power transistors and SCRs, 2 rectifier bridges, large lot of rectifier and small signal diodes, plus loads of 1/2 watt resistors and all kinds of capacitors. We supply pin data for the ICs.

STOCK NO. M5277 set of 5 boards \$6.00 2 sets \$11.00

TRANSFORMER— 12 Volts, 1 Amp, with 7/2 3 wire rubber line cord.

STOCK NO. M6439 \$3.95 ea. 2/7.00

We accept **MASTERCHARGE & BANKAMERICARD**. Include bank number & expiration date. Minimum charge order \$15.00. Minimum prepaid order \$5.00. Include sufficient postage. Excess will be refunded. Send for our 96 page catalog.

DELTA ELECTRONICS CO.

P.O. BOX 2, AMESBURY, MASS. 01913

BOOKS

Learn Microprocessing!

- An Introduction to Microcomputers by Adam Osborne \$7.50
- An Introduction to Microcomputers Volume II: Some Real Products \$12.50
- 8085 Programming for Logic Design by Adam Osborne \$7.50

Complete Set of Three for \$25.00

160 MHz PRESCALER - 2 DUAL D ECL FF W/ DATA AND SCHEMATIC KIT--NO CASE NO POWER SUPPLY \$1.95

SPACE AGE CLOCK KIT

Instructions & parts - 12 or 24 hour format. Four digit clock kit includes all parts for complete clock: 3 1/2" x 2 1/2" - F70 70 readouts - IM5314 clock chip & all transistors, etc. extruded aluminum case - cord with transformer plug \$16.95

MOLEX TRIACS

500	\$ 4.50
1000	8.00
2000	15.00
5000	35.00
10000	70.00
25000	150.00

Send a stamp for our flyer listing more money saving bargains, including microprocessors!! P.O. Box 41778 4811 Myrtle Ave. Sacramento, CA 95841 Phone (916) 334-2161

59¢ each

Orders under \$7.00 add \$1.00 postage and handling. Residents of Cal. add sales tax. Orders shipped promptly. \$10 minimum on C.O.D.s.

BABYLON ELECTRONICS

CIRCLE 45 ON FREE INFORMATION CARD

CIRCLE 49 ON FREE INFORMATION CARD

2708 PROM	\$55.00
2527 STATIC SHIFT REG.	\$1.95
2618-HEX 37 BIT SR	\$2.50
2102-1 1024 BIT RAM	\$1.80
5280-4K DYNAMIC RAM	\$10.50
5202A UV PROM	\$10.50
MM5203 UV PROM	\$10.50
1702A UV PROM	\$10.50
5204-4K PROM	\$18.05
MINIATURE MULTI-TURN TRIM POTS	100, 500, 2K, 10K, 100K, 200K, 1 Meg. \$.75 each 3/22.00
MULTI-TURN TRIM POTS Similar to Bourns	3010 style 3/16" x 5/8" x 1 1/4" 50, 100, 1K, 10K, 50K ohms \$1.50 ea. 3/24.00
LIGHT ACTIVATED SCR's	TO 18, 200V 1A \$ 1.75
TRANSISTOR SPECIALS	
2N3585 NPN Si. TO 66	\$.95
2N3772 NPN Si. TO 3	\$ 1.60
2N4908 PNP Si. TO 3	\$ 1.00
2N6056 NPN Si. TO 3 Darlington	\$ 1.70
2N5085 PNP Si. TO 92	4.10
2N4898 PNP TO 66	\$.80
2N404 PNP GE TO 5	5/5 1.00
2N3919 NPN Si. TO 3 RF	\$ 1.50
MPS4 13 NPN Si. TO 92	3/5 1.00
2N3767 NPN Si. TO 66	\$.70
2N2222 NPN Si. TO 18	5/5 1.00
2N2055 NPN Si. TO 3	\$.80
2N3904 NPN Si. TO 92	5/5 1.00
2N3906 PNP Si. TO 92	5/5 1.00
2N5296 NPN Si. TO 220	\$.50
2N6109 PNP Si. TO 220	\$.55
2N3638 PNP Si. TO 5	5/5 1.00
2N6517 NPN TO 92	3/5 1.00
CMOS (DIODE CLAMPED)	
74C02	22 4015 95 4035 1.10
74C10	22 4016 40 4042 78
74C193	150 4017 105 4047 2.00
4001	22 4018 1.00 4049 40
4002	22 4019 25 4050 40
4006	120 4022 95 4055 1.50
4007	22 4024 75 4066 80
4009	42 4027 40 4071 22
4010	42 4028 83 4076 70
4011	22 4029 110 4081 22
4012	22 4030 22 4520 1.15
4013	40

PRINTED CIRCUIT BOARD

4 1/2" x 6 1/2" SINGLE SIDED EPOXY BOARD .116" thick, unclamped \$5.00 ea. 5/52.20

7 WATT LD-65 LASER DIODE IR \$8.95

2N 3820 P FET	\$ 45
2N 5457 N FET	\$ 45
TS 15 4J JT	\$ 35
ER 900 TRIGGER DIODES	4/1 100
2N 6028 PROG. UJT	\$ 65
8 PIN DIP SOCKETS	\$ 24
14 PIN DIP SOCKETS	\$ 25
16 PIN DIP SOCKETS	\$ 28
18 PIN DIP SOCKETS	\$ 30
24 PIN DIP SOCKETS	\$ 40
40 PIN DIP SOCKETS	\$ 60

VERIPAC PC BOARD

This board is a 176" single sided paper epoxy board, 4 1/2" x 6 1/2" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or 18 DIP IC's with buses for power supply connector \$8.00

MM 5691 YELLOW GREEN BIPOLEAR LED \$1.25
FP 100 PHOTO TRANS \$1.50
RED YELLOW, GREEN OR AMBER LARGE LED's ea \$ 20
10X LED PINS 1000/\$1.00

10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 12, 15, 18, 22, 100, 150 or 200V . ea \$.60

1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 OR 22V . ea \$.25

MC6803 MODEM CHIP \$13.00

Silicon Power Rectifiers

PRV 1A	3A	12A	50A	125A
100 06	14	30	80	370
200 07	20	35	115	425
400 09	25	50	140	650
600 11	30	70	180	850
800 15	35	90	230	1050
1000 20	45	110	275	1250

SILICON SOLAR CELLS

2 1/2" diameter

4V at 500 ma. . . \$4.00 ea., 6/\$22.50

REGULATED MODULAR POWER SUPPLIES

15 VDC AT 100ma \$7.95
115VAC INPUT

5VDC AT 1A 115VAC INPUT \$24.95
12 VDC AT 5 AMP \$24.95
IN 4148 116914 15 \$11.00

TANTALUM CAPACITORS

250P 20V 50% 4.7	\$1.75
470P 35V 50% 100	\$1.75
CBME 30V 50% 1.1	22UF 35V \$.40
11A 75V 50% 1.0	370UF 35V \$.40
220UF 30V 50% 1.0	70UF 6V \$51.00
170UF 35V 50% 1.0	100UF 1.5V \$.60
	1300UF 1.5V \$.50

M/001 ALARM CLOCK CHIP \$5.75

NATIONAL MOS DEVICES

MM1402 1 75	MM5057-2 25
MM1403 1 75	MM5058-2 25
MM1404 1 75	MM5060 2 75
MM5013 2 50	MM5061-2 50
MM5016 2 50	MM5555 4 75
MM5017 2 70	MM5556 4 75
MM5055 2 25	MM5210 1 95
MM5056 2 25	MM5260 1 75

TTL IC SERIES

7400	15	7442	52	74126	40
7401	15	7445	70	74151	70
7402	15	7446	70	74153	65
7403	15	7447	70	74154	110
7404	20	7448	70	74155	70
7405	20	7450	20	74157	70
7406	25	7472	33	74161	85
7407	25	7473	35	74164	95
7408	25	7474	35	74165	105
7409	21	7475	49	74173	140
7410	15	7476	35	74174	95
7411	20	7480	35	74175	92
7412	70	7483	70	74177	79
7413	45	7485	88	74180	70
7414	70	7486	30	74181	210
7415	25	7489	185	74190	120
7417	25	7490	45	74191	120
7420	20	7491	70	74192	85
7425	28	7492	50	74193	85
7426	25	7493	45	74194	85
7427	30	7494	70	74195	75
7430	20	7495	70	74196	88
7432	25	7496	70	74197	125
7437	25	74107	32	74279	50
7438	25	74121	38	75234	175
7440	16	74123	65	75491	65
7441	85	74125	40	75492	65

MINIATURE DIP SWITCHES

C1S 206 4 Four SPST switches in 2mg minidip package \$1.75

LTS 206 8 Eight SPST switches in a 16 pin DIP package. \$1.95

AY 5-1013-A30K ser. pin. bar. ser. uni. versal UART \$6.95

ALCU MINIATURE TOGGLE SWITCHES

MTA 106 SPDT	\$1.20
MTA 206 DPDT	\$1.70

Full Wave Bridges

PRV 2A	6A	25A
200	75	1.75 2.00
400	95	1.50 2.00
600	120	1.75 2.00

SANKEN AUDIO POWER AMPS

S-1010 G 10 WATT	\$ 3.95
S-1020 G 20 WATTS	\$15.95
S-1050 G 50 WATTS	\$27.95

CCO 110 LINEAR 756 XI BIT SELF SCANNING CHARGED COUPLED DEVICE \$99.00

CCD 701 100 x 100 CHARGE COUPLED DEVICE \$135.00

LINEAR CIRCUITS

LM307 Op Amp	\$.30
LM309K 5V 1A REGULATOR	\$.95
723 40 + 40VV REGULATOR	\$.50
301 748 Hi Pe Op. Amp	\$.75
320T 5.12 15 or 24V NEG REG	\$1.15
700C Op Amp	\$.31
741A or 741C OP AMP	\$.31
710 COMPARATOR	\$.35
CA 3047 Hi PeL Op. Amp	\$.95
340T 5, 6, 8, 12, 15, 18, 24V POS REG. TO 220	\$1.10
101 OPER. AMP. HI PERFORM	\$.75
LM308 Op. Amp., Low Power	\$.95
747 DUAL JAT	\$.65
556 DUAL TIMER	\$1.00
537 PRECISION OP AMP	\$1.70
LM3900 QUAD OP AMP	\$.49
LM324 QUAD 741	\$1.50
561 PHASE LOCK LOOP	\$2.00
561 PHASE LOCK LOOP	\$2.00
565 PHASE LOCK LOOP	\$1.25
566 FUNCTION GEN.	\$1.65
567 TONE DECODER	\$1.50
LM1310N FM STEREO DEMOD.	\$2.75
8038 IC VOLTAGE CONT OSC	\$3.90
LM370 AGC SQUELCH AMP	\$1.15
555 2ur 2 HR TIMER	\$.45
553 QUAD TIMER	\$2.50
FCB 810 OPTO-ISOLATOR	\$.80
1458 DUAL OP AMP	\$.60
LM380 2W AUDIO AMP	\$.95
LM377 2W Stereo Audio Amp	\$2.50
LM381 STEREO PREAMP	\$1.50
LM382 DUAL AUDIO PREAMP	\$1.50
LM311 HI PER. COMPARATOR	\$.90
LM319 Dual Hi Speed Comp.	\$1.25
LM339 QUAD COMPARATOR	\$1.50

TRIACS SCR'S

PRV 1A	10A	25A	1.5A	6A	35A
100	40	70	1.30	40	50 1.20
200	70	110	1.75	60	70 1.60
400	110	160	2.60	1.00	1.20 2.20
600	170	230	3.60	1.50	3.00

Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage, Minimum Order \$5.00, COD'S \$20.00




SOLID STATE SALES

P.O. BOX 740
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

RADIO-ELECTRONICS

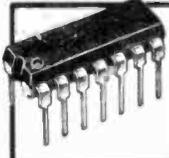

DIGI-KEY CORPORATION
Quality Electronic Components
Double-Digit Discounts
Save You Even More

2102-1 \$1.99	8080A \$24.95	LM3909 69¢
-------------------------	-------------------------	----------------------

NATIONAL SEMICONDUCTOR CLOCK MODULES

MA1010A 12 Hour (AM-PM) Version . . . \$13.00
MA1010C 24 Hour Version . . . \$13.00

MA1002A 12 Hour (AM-PM) Version . . . \$10.50
MA1002C 24 Hour Version . . . \$10.50

0.5" High LED Digits



Special transformer and 6 switches, when ordered with module add \$3.45.


0.84" High LED Digits



Special transformer and 6 switches when ordered with module add \$3.45

Hobby-Wrap-30 \$5.95

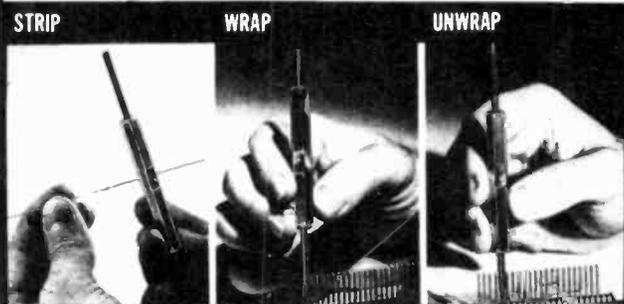Strips, Wraps and Unwraps 30 ga. wire on standard wire wrapping pins



MA1002 & MA1010 Series Electronic Clock Modules

The MA1002 & MA1010 Series Electronic Clock Modules are assembled and pretested modules which combine a monolithic MOS-LSI integrated clock circuit, 4-digit LED display, power supply and other associated discrete components on a single printed circuit board to form a complete electronic clock movement. The user need only a transformer and switches to construct a digital clock for application in clock-radios, alarm or instrument panel clocks. Time-keeping may be from 50 or 60 Hz inputs and 12 or 24 hour display formats may be chosen. Direct LED drive eliminates RF interference. Time setting is made easy through use of "Fast" and "Slow" scanning controls.

The MA1002A and MA1010A have a 12 hour display with an AM and PM indicator. The MA1002C and MA1010C have a 24 hour display.

Features include alarm "on" and "PM" indicators, "sleep" and "snore" timers and variable brightness control capability. The modules are extremely compact the MA1002 measuring 1.375" by 3.05", the MA1010 measuring 1.75" by 3.75". This small size is achieved by bonding the I.C. to the back of the circuit board.

It is highly recommended that the transformer be obtained with the clock module as it is a special dual secondary type not otherwise readily available.

Double Digit Discounts Save You Even More!

ACE201-K \$24.95
1,032 SOLDERLESS PLUG-IN THE POINTS CAPACITY: 1P TO 12 14-PIN DIP'S
TWO 5 way binding posts
Size: 4-9/16" by 7/8"
Kit Form

ENTIRE ROCKWELL CALCULATOR LINE ON DISCOUNT IN OUR LATEST CATALOG

SLIDE SWITCHES
Single Pole Single Throw
15 1.20/10 10.00¢
Double Pole Double Throw
23 2.00/10 19.00¢

BATTERY HOLDERS
1-AA . . . 26¢
2-AA . . . 42¢
1-C . . . 35¢
2-C . . . 42¢
1-D . . . 35¢
2-D . . . 42¢

BISHOP GRAPHICS Printed Circuit Drafting Aids are now available from Digi-Key

RADIAL ELECTROLYTICS

47/50V .08	65/10	22/50V .12	1.00/10	330/25V .23	1.86/10
1/50V .08	65/10	100/6.3V .09	75/10	470/10R .21	1.71/10
2.2/50V .08	65/10	100/10V .10	77/10	470/16V .23	1.81/10
3.3/50V .08	65/10	100/16V .11	85/10	470/25V .29	2.85/10
4.7/50V .08	65/10	100/25V .13	110/10	1000/10V .24	1.96/10
4.7/50V .08	65/10	100/50V .21	171/10	1000/16V .29	2.35/10
10/16V .08	65/10	220/10V .13	1.08/10	1000/25V .47	3.33/10
10/25V .08	65/10	220/16V .15	1.16/10	2200/10V .42	3.33/10
10/50V .10	75/10	220/25V .21	1.71/10	2200/16V .58	4.30/10
22/16V .08	67/10	220/50V .29	2.35/10	2200/25V .58	4.67/10
22/25V .09	70/10	330/10V .15	1.16/10	3300/16V .89	7.14/10
		330/16V .21	1.66/10		

INTEGRATED CIRCUITS - TTL, CMOS, LINEAR & MOS

7400 21	7476 32	74181 2.15	4012 23	4520 1.14
7401 21	7480 70	74182 2.79	4013 40	4527 1.68
7402 21	7487 70	74184 2.19	4014 .96	4528 .88
7403 21	7489 70	74185 2.19	4015 1.26	4581 1.72
7404 21	7485 89	74188 3.50	4016 .40	2102-1 1.99
7405 21	7486 .28	74189 3.50	4017 1.05	8080A 24.95
7406 25	7489 2.19	74190 1.23	4018 1.05	CA 3044 .75
7407 25	7490 44	74191 1.23	4020 1.14	LM211W 1.25
7408 21	7491 70	74192 88	4020 1.14	LM309K 1.80
7409 21	7492 44	74193 88	4021 1.14	LM324A 1.28
7410 21	7493 44	74194 88	4022 96	LM340T-5 1.25
7411 21	7494 70	74195 88	4023 73	LM340T-6 1.25
7412 21	7495 70	74196 88	4024 84	LM340T-8 1.25
7413 25	7496 70	74197 88	4025 23	LM340T-12 1.25
7414 89	74100 1.28	74198 1.49	4026 1.68	LM340T-15 1.25
7416 25	74107 30	74199 1.23	4027 40	LM340T-18 1.25
7417 25	74109 33	74201 1.09	4028 89	LM340T-24 1.25
7420 21	74121 35	74279 55	4029 1.14	LM3900N 88
7421 25	74122 44	74365 67	4030 23	LM3909N 69
7422 35	74123 61	74366 67	4031 1.26	MCI1456V 1.00
7423 35	74125 40	74367 67	4033 3.50	MCI1458V 53
7426 25	74126 40	74368 67	4035 1.14	MC3302P 1.15
7427 33	74132 70	8093 40	4040 1.14	NES36T 3.24
7428 28	74141 88	8094 40	4041 79	NES40L 7.04
7430 21	74145 70	9095 67	4042 79	NES55V 48
7432 25	74147 1.63	8096 67	4043 70	NES56A 88
7433 30	74148 1.30	8097 67	4044 70	NES50B 3.83
7437 25	74150 1.16	8098 67	4046 1.86	NES61B 3.83
7438 25	74151 70	75150 1.16	4049 40	NES62B 3.83
7440 21	74153 65	75450 88	4050 40	NES65A 1.25
7442 53	74154 1.03	75451 61	4051 1.26	uA711CA 44
7443 63	74155 70	75452 81	4052 1.26	uA711CA 44
7445 70	74156 70	75453 61	4053 1.26	uA723CA 60
7446 70	74157 70	75454 61	4060 1.58	uA733CA 75
7447 70	74160 88	75401 61	4066 79	uA741CV 44
7448 70	74161 88	75492 84	4071 23	uA741CA 40
7450 21	74162 88	75493 1.09	4072 23	uA748CV 49
7451 21	74163 88	75494 1.19	4073 23	uA780SCU 1.25
7452 21	74164 96	80925 2.19	4075 23	uA780SCU 1.25
7454 21	74165 1.15	4000 .23	4081 23	uA780SCU 1.25
7459 21	74166 1.26	4001 .23	4082 23	uA7812CU 1.25
7460 21	74170 2.64	4002 .23	4083 23	uA7812CU 1.25
7470 30	74173 1.42	4006 1.23	4510 1.14	uA7824CU 1.25
7472 30	74174 96	4007 23	4511 1.05	uA7824CU 1.25
7473 30	74175 96	4008 79	4514 2.80	uA7824CU 1.25
7474 30	74176 79	4009 44	4515 2.80	uA7824CU 1.25
7475 49	74177 79	4010 44	4516 1.23	uA7824CU 1.25
		4011 .23	4518 1.14	

NEW
Hobby-Wrap
Model HW-630

Battery wire wrapping tool

\$34.95
ONLY
COMPLETE WITH BIT AND SLEEVE

WIRE WRAPPING WIRE IN BULK
Red or Black 30 ga. Kynar

100	\$2.00	500	\$8.50	1000	\$15.00
-----	--------	-----	--------	------	---------

SILICON DIODES

1N4001	64/10	5.50/¢	\$49/M
1N4002	66/10	5.50/¢	\$51/M
1N4003	68/10	5.80/¢	\$52/M
1N4004	70/10	5.95/¢	\$54/M
1N4005	82/10	7.05/¢	\$63/M
1N4006	90/10	7.75/¢	\$68/M
1N4007	99/10	8.60/¢	\$77/M
1N4148	40/10	3.50/¢	\$29/M

DATA BOOKS

TTL IC's 595 p. . . . \$4.00
Linear IC's 957 p. . . . \$5.00
CMOS IC's 256 p. . . . \$3.00
Transistors 288 p. . . . \$3.00
Memory IC's 592 p. . . . \$3.00
Interface IC's 464 p. . . . \$4.00
Volt. Regs. 128 p. . . . \$3.00
Linear Appl. 1 432 p. . . . \$4.00
Linear Appl. 2 246 p. . . . \$3.00
Audio 196 p. . . . \$3.00

PERF BOARD
0.1" spacing between holes

4 1/2" x 6"	\$1.71
4 1/2" x 17"	\$4.25

TERMINALS
for above perf board
\$1.50/¢

LED LAMPS

MS15053 T-1 1/8"	18 \$15/¢
MS15056 T-1 1/8"	18 \$15/¢

LED DISPLAYS

FND357 CC 375"	\$1.35
FND500 CC 500"	\$1.35
FND 507 CA 500"	\$1.35
FND800 CC 800"	\$2.50
FND807 CA 800"	\$2.50

AXIAL ELECTROLYTICS

47/10V 11	90/10	33/25V 14	1.15/10	330/16V 29	2.35/10
1/20V 11	90/10	33/50V 19	1.52/10	330/25V 32	2.54/10
3.3/25V 12	95/10	47/16V 14	1.15/10	470/16V 32	2.55/10
3.3/50V 12	1.00/10	47/25V 17	1.30/10	470/25V 37	3.00/10
4.7/25V 12	90/10	47/50V 20	1.37/10	1000/10V 29	2.85/10
4.7/50V 12	1.00/10	100/10V 14	1.13/10	1000/16V 39	3.15/10
4.7/50V 12	1.00/10	100/16V 17	1.30/10	1000/25V 56	4.50/10
10/25V 12	1.00/10	100/25V 20	1.55/10	2200/10V 50	3.96/10
10/50V 14	1.15/10	100/50V 29	2.30/10	2200/16V 62	4.50/10
22/16V 12	1.00/10	220/10V 18	1.42/10	2200/25V 79	6.36/10
22/25V 13	1.05/10	220/16V 20	1.55/10	3300/16V 95	7.63/10
22/50V 17	1.32/10	220/25V 29	2.35/10	4700/16V 1.09	8.70/10
33/16V 12	1.00/10	220/50V 40	3.23/10	10000/10V 1.15	9.19/10
		330/10V 14	1.16/10		

WIRE-WRAPPING TOOL
\$5.95
Wraps, Unwraps & Strips 30 ga. Wire

1/8" & 1/4" WATT 5% CARBON FILM RESISTORS
5¢ each in multiples of 5 per value
\$1.70/100 & \$12.00/1000 of same value
1 ohm thru 1.0 megohm

I.C. SOCKETS

8 Pin Solder	17	1.60/10
14 Pin Solder	20	1.90/10
16 Pin Solder	22	2.10/10
18 Pin Solder	29	2.75/10
24 Pin Solder	38	3.60/10
28 Pin Solder	45	4.25/10
40 Pin Solder	63	6.50/10
8 Pin W-W	24	2.30/10
14 Pin W-W	26	2.50/10
16 Pin W-W	30	2.85/10
18 Pin W-W	40	3.70/10
24 Pin W-W	46	4.10/10
28 Pin W-W	112	10.00/10
40 Pin W-W	92	8.75/10

SILICON TRANSISTORS

MPS918	MPS990	MPS2222A	MPS2369A	MPS2712	MPS2907A	MPS3392
MPS3393	MPS3394	MPS3395	MPS3563	MPS3565	MPS3638	MPS3638A
MPS3640	MPS3641	MPS3645	MPS3646	2N3904	2N3906	2N4124
2N4126	2N4401	2N4403	2N4410	PN4888	2N6587	2N6589
PN5134	PN5137	PN5138	PN5139	2N5120	PN5964	16, 51, 55, 10, 513, 60/100 of same part no.
MPF102	.36	530.60/¢	2N5457	48	\$41.00/¢	MPS1A13 .78
						\$24.00/¢
						2N3055 .99
						585.00/¢

1/2 WATT ZENER DIODES

1N5226B 3.3v	15 \$11/¢	1N5236B 7.5v	15 \$11/¢
1N5227B 3.6v	15 \$11/¢	1N5237B 8.2v	15 \$11/¢
1N5228B 3.9v	15 \$11/¢	1N5238B 9.1v	15 \$11/¢
1N5229B 4.3v	15 \$11/¢	1N5239B 10.0v	15 \$11/¢
1N5230B 4.7v	15 \$11/¢	1N5240B 10.5v	15 \$11/¢
1N5231B 5.1v	15 \$11/¢	1N5241B 11.5v	15 \$11/¢
1N5232B 5.6v	15 \$11/¢	1N5242B 12.5v	15 \$11/¢
1N5233B 6.0v	15 \$11/¢	1N5243B 13.5v	15 \$11/¢
1N5234B 6.5v	15 \$11/¢	1N5244B 14.5v	15 \$11/¢
1N5235B 6.8v	15 \$11/¢	1N5245B 15.5v	15 \$11/¢

HARDWARE

2-56 1/4 Screw	99/¢	7.20/M
2-56 1/2 Screw	99/¢	7.65/M
4-40 1/4 Screw	55/¢	3.60/M
4-40 1/2 Screw	60/¢	4.05/M
6-32 1/4 Screw	65/¢	4.40/M
6-32 1/2 Screw	75/¢	4.85/M
8-32 3/8 Screw	90/¢	5.85/M
8-32 5/8 Screw	99/¢	7.00/M
9-36 Hex Nut	55/¢	3.80/M
10-36 Hex Nut	55/¢	3.75/M
10-32 Hex Nut	60/¢	4.00/M
8-32 Hex Nut	60/¢	4.15/M
No. 2 Lockwasher	85/¢	5.75/M
No. 4 Lockwasher	45/¢	3.00/M

Wafers are meant to be inserted in a .063" maximum thickness board and have .043" diameter pins on .156" centers.

NEW

CATALOG NUMBER	DESCRIPTION	PRICES	
		1-10	11-99
13-0001	12 pos. rt. angle connector	60	.50
13-0002	12 position wafer	60	.50
13-0003	9 pos. rt. angle connector	60	.50

SPECIAL! 1000 Molex IC terminals for \$7.50 2000 for \$13.50

SPECIAL! Motorola 741 Mini Dip 35¢-10 for \$3.00

LINEAR

ELECTROLYTIC CAPACITORS			
WORKING (uF)	VOLTS DC	\$	
10	16, 35, 50	.16	
20	16, 35, 50	.16	
30	16	.16	
50	16, 35	.22	
100	16, 35, 50	.25	
200	16	.22	
500	16	.34	
1000	16	.52	
2200	16	.80	

NE501A 2.80
NE555A .50
A710CA .60
A741V .40
A747CA 1.10
A748CV .74
A723CA 1.00
MC1468L 3.90

Red Led & Mfg. Hardware
T1-3/4
1-10 .35 11-100 .29

MINIATURE FILM CAPACITORS

VALUE (uF)	1-14	15-50	\$1 100
001	.10	.10	.06
0047	.10	.10	.06
01	.10	.10	.06
05	.19	.17	.15
1	.20	.18	.16
22	.25	.23	.21

These units are made by International Components Corp. All units 100 V.

FIXED POWER SUPPLY KITS

Specifications	#0810	#1210	#1610
Input Voltage (50-500Hz)	105 125v	105 125v	110 125v
Output Voltage	5v ± 5%	12v ± 5%	15v ± 5%
Output Current (I _o ± 25% Cl)	1.5A Max	1.5A Max	1.1A Max
PRICE	\$14.00	\$14.50	\$14.50

INDEFINITE SHORT CIRCUIT PROTECTION Price includes Pre-drilled G10 Board All Parts and Transformer.

DISPLAY BEZELS

CATALOG NUMBER	FILTER COLOR	PRICE	QUANTITY
905.80	Red	\$2.75	137
910.80	Red	2.80	200
915.80	Red	2.90	400
920.80	Red	2.90	400
920.70	Amber	2.95	400

These bezels are heat resistant plastic with a black mottle finish. Filters are circular polarized type.



SOCKETS

LOW PROFILE

These sockets are from TI

NUMBER OF PINS	5-10	11-18
14	.25	.30
16	.28	.34
24	.46	.55
28	.56	.68

TRANSISTORS

2N3638A	P	5	TO-92	25
2N2222A	N	5	TO-18	20
2N5133	N	05	TO-18	25
2N5494	N	7	TO-220	105
2N4401	N	60	TO-92	60
2N4403	P	60	TO-92	30
TIP32	P	3	TO-220	105

TRIMMER POTENTIOMETERS

These are 5/8" diameter thru-mount trimmer potentiometers

VALUES OHMS
100 50K 1K 5K 10K 20K 25K 250K 50K 100K 500K 1M 10M

PRICE TABLE	1-10	11-100	100
	30	79	27

TERMS \$10.00 Min. Order. Orders less than \$25.00 add \$1.00 postage & handling. Master Charge & Bank Americard.

MOLEX IC TERMINAL

100 for \$1.00	300 for \$2.60	500 for \$4.28
200 for \$1.80	400 for \$3.40	800 for \$5.00
700 for \$5.90	900 for \$7.40	
800 for \$5.00	1,000 for \$8.20	

Reel of 50,000 \$ 270.00

REGULATOR CIRCUITS

MC7805CP	5 volt regulator @ 1.5A max	1.99
MC7812CP	12 volt regulator @ 1.5A max	2.00
MC7815CP	15 volt regulator @ 1.5A max	2.00

16 Page Catalog 25¢

DIODES

1N4001	10/51 00
1N4002	10/51 00
1N4146	10/51 00
1N5401	5/52 00 (3A 100PIV)
1N746-739A	5.3000

TRACY DESIGN CORP.
15870 SCHAEFER • DETROIT, MI 48227 • (313) 838 2501

ALL AN ASR 33 IS AND MORE!
OLIVETTI 318 TELETYPEWRITER
BUILT-IN PAPER TAPE I/O
KEYBOARD PLUS 10 KEY PAD
HEAVY DUTY BUT QUIET \$950
NATIONAL SERVICE + SHIPPING

A REAL COMPUTER VIDEO - IDEAL FOR ALPHANUMERIC WORK
1 VOLT P TO P INPUT
ANTI-GLARE SCREEN
GREEN PHOSPHOR
12" DIAGONAL SCREEN
\$150 + \$25 SHIPPING

KITS: ADM-3, RIM-1, RSC SC/MP, INKAT 8080, SUTPE TERM, 6800 INTERCEPT JR, SMOKE M-16, TARBELL CASSETTE INTERFACE.

TO ORDER: 1. ENCLOSE CHECK FOR FULL PRICE PLUS SHIPPING (IN MASS, ADD 5% SALES TAX)
2. CLEARLY IDENTIFY SHIPPING ADDRESS.
3. DESCRIBE ITEM BY MODEL #
1 DAY SHIPMENT IF BANK CHECK OR MONEY ORDER

COMPUTER WAREHOUSE STORE
WRITE FOR OUR CATALOG
DEPT R, P.O. BOX 68, KENMORE STA., BOSTON, MA 02215 671/261-2701

FREE catalog. Unique components, kits, calculators, digital thermometers, ultrasonics, strobes, Ni-Cad's, LED's, transistors, IC's. CHANEY'S, Box 27038, Denver, CO 80227

PRINTED CIRCUIT
Positive Acting Photo Resist; Carbide bits; Bubble etchers; Artwork; Epoxy Glass Boards.
Send stamp & address label for flyer
TRUMBULL
833 Balra Dr., El Cerrito, CA 94530

MARCH Goodies: 555-39¢, 741-29¢, 747-49¢, Fairchild jumbo LED's red 12/\$1.00, green 8/\$1.00, 2x2cm solar cells \$1.50, 2N3055-88¢, 309K-88¢ 1N914-20/\$1.00, 2N3393-10/\$1.00. Free catalog. Our third year. DIAMOND-BACK, Box 194R, Spring Valley, IL 61362

BACK issue magazines. Over 200 titles, 1890 to 1976. Send stamped envelope. Free list. EVERYBODY'S BOOKSHOP, Dept. RE, 317 West 6th, Los Angeles, CA 90014

Looking for **BIRD** RF PRODUCTS?
AMATEUR RADIO SUPPLY
SEATTLE
6213 13th Ave. So., 98108
(206) 767-3222

PROFESSIONAL unscramblers—use with any scanner. Free information. CAPRI ELECTRONICS, 8753R Windom, St. Louis, MO 63114

Mystery Electronic Top
Spins for days at 2,500 rpm on invisible power. Best new gadget in years. Baffling brain-buster. Bugs the brightest. Perpetual Motion? UFO? Psychic Power? Anti-gravity? Scientific Break-Thru From Space? Magic, Mystery, Science combined. Spins without energy loss! Never wears out. Fun at parties, science classes, etc. Complete with secret, scientific explanation. Send \$6.95 each + \$1.00 shipping Johnson Smith Co. Dept. 543, Mt. Clemens, Mich. 48043

NAME brand digital/analog test equipment. Discount prices. Free catalog. SALEN ELECTRONICS, P.O. Box 82, Skokie, IL 60076

PICTURE TUBE MACHINE
We buy and sell PTV and CRT's. FREE estimating. No money. COMPLETE REPAIR. INC. BUY WITH CONFIDENCE FROM THE ORIGINAL MEGA.

For complete details send name address zip code to:
LAKE-SIDE INDUSTRIES
3520 W. Fullerton Ave
Chicago IL 60647
Phone 312-342-3399

Red Cross. The Good Neighbor.

PARTS

NEW AND SURPLUS PARTS
IC's-RES-CAPS-SWITCHES
P C BOARDS & CHEMICALS
COMPUTER PARTS
T V GAMES
CALC & LCD WATCH PARTS

KITS

MUSIC SYNTHESIZER KITS
PHASE SHIFTERS
AUDIO KITS AND PARTS
POWER SUPPLIES & KITS
CALCULATOR KITS
ORGAN/SYNTH KEYBOARDS

SERVICES

CIR. BOARD FABRICATION
C. BOARD COOKBOOK-6.50
METAL FAB. & SUPPLIES
CUSTOM AUDIO DESIGN

SEND 13¢ STAMP FOR
1977 CATALOG
UTEP
DEP. 3-BOX 26231
S.L.C., UT. 84125
CIRCLE 60 ON FREE INFORMATION CARD

GODBOUT

BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

74LS TTL

1/5 THE POWER OF TTL BUT NO SPEED PENALTY					
00	\$0.36	22	\$0.38	124	\$2.50
01	0.36	27	0.38	132	1.50
02	0.36	30	0.36	138	1.38
04	0.42	32	0.38	139	1.38
08	0.38	37	0.53	155	1.38
10	0.36	38	0.53	157	1.25
11	0.38	42	1.25	160	1.85
20	0.36	74	0.56	162	1.85
21	0.38	75	0.85	163	1.85

JUST IN! 74LS14...\$1.38

AN OFFER YOU CAN'T REFUSE!

We wanted to put together an exceptional offer on memories for our customers...so we're selling new full spec 2102L1s (super low power version of the 2102), guaranteed 450 ns or faster over the full temp range...at 10/\$15! ALL ORDERS MUST BE POST-MARKED BEFORE 3/31/77 TO TAKE ADVANTAGE OF THIS SPECIAL OFFER.

WE SELL KNOWLEDGE!

The Adam Osborne & Associates book on microcomputers are recognized as tops in their field. Lucid and complete, these are now available from our p.p.d. in the USA, or buy all 3 books for \$25 p.p.d.

"AN INTRODUCTION TO MICROCOMPUTERS, VOL. 1" book #2001. Clearly covers all the basics...\$7.50

"VOLUME 2" book #3001. Covers latest up and up print II's, re. la ing 100's of types of data...\$12.50

"BOBO PROGRAMMING FOR LOGIC DESIGN" Book #4001. Demystifies the art of programming...\$7.50

LIMITED QUANTITY SPECIALS

The following are *limited qty.* subject to prior sale:
DISCRETE RED 2" LEDs.....12/\$1.00
14511 CMOS BCD-to-7-segment decoder/latch/driver, no extra transistors needed.....\$2.00 each
MC4324 Bxpral dual VCC (TTL compat)...\$2.00 each

TERMS: Add 50¢ orders under \$10, over \$10 add 5% NO COD. Cal res add tax. Mastercharge® and BankAmericard® orders: call 415-562-0636, 24 hours.

CIRCLE 34 ON FREE INFORMATION CARD

RADIO-ELECTRONICS

Radio Hut

TERMS: Money Back Guarantee. No COD's. Texas Residents add 5% Tax. Add 5% of order for postage and handling. Orders under \$10.00 add 75c. Foreign Orders: US Funds ONLY!

For your convenience, call your BankAmericard or Master Charge order in on our Continental United States Toll Free Watts: 1-800-527-2304.

Texas Residents call collect: 214-271-8423.
P. O. Box 64783 Dallas, Texas 75206



DARLINGTONS by Motorola
MJ3001 NPN 80V-10amps 150 Watts \$1.35
MJE1103 NPN 80V-5 amps 70 Watts 3/\$1.00

NE555 .45
NE565 1.00
NE566 1.00
NE567 1.19
NE556 1.00

DIODES
IN54A Germanium Signal 12/1.00

MOS TO LED DRIVERS
75491 Quad .40 75492 Hex .40

LM3900 .39
LM324 .39
1458 (5558)
2/1.00

C103B 1 amp 200V SCR .49
General Purpose Silicon Switching 50/1.00

UNTESTED DIODES

A good assortment of 1 amp rectifiers. Good Yield. 50 for \$.60 - 100 for \$.95.

BATTERY CLIP

Standard 9V battery clip - 15 for \$1.00.

WATERGATE SPECIAL

Telephone relay automatically starts and stops tape recorder. No batteries required. Kit

complete with drilled PC Board. PARTS AND CASE -

SATISFACTION GUARANTEED
ONLY \$10.95

PLASMA Discharge Display
By National Electronics
12 DIGIT DISPLAY, 4" character
Neon Orange in color
Specs Included Only \$.79
Money Back Guarantee

Complete Power Supply Kit for above, including P.C. Board XFMR, and Instructions. Only \$3.25
Money Back Guarantee

VOLTAGE REGULATORS

Pos.	Pos.	Neg.	Neg.
LM340-6	LM340-15	7905	7915
LM340-8	LM340-18	7906	7924
LM340-12	LM340-24	7912	

Your Choice Only \$.85.

TRANSISTORS

2N4400	6/1.00	2N5401	6/1.00
2N2907	House	2N3055	.69

Numbered PC Lead 15/1.00

180 \wedge 1/4	20K \wedge 1/4
330 \wedge 1/4	22K \wedge 1/4
330 \wedge 1/8	27K \wedge 1/4
470 \wedge 1/4	33K \wedge 1/4
680 \wedge 1/4	39K \wedge 1/2
1K 1/4	43K \wedge 1/4
1.2K \wedge 1/4	47K \wedge 1/4
2.2K \wedge 1/4	56K \wedge 1/4
3.3K \wedge 1/4	82K \wedge 1/4
3.9K \wedge 1/4	100K \wedge 1/4
4.7K \wedge 1/4	150K \wedge 1/4
6.8K \wedge 1/4	220K \wedge 1/4

3N201

PROTECTED DUAL GATE N-CHANNEL FET FOR LOW NOISE, VHF PREAMP APPLICATIONS - Only \$.80

TTL ASSORTMENT

Most are 7400 Series
Good Yield Reported
50/99

All resistors are PC Lead but are not pull offs
5% - 100 min. order Each value
No Mix - 99¢ 100

HARDWARE

New, includes 2-56, 4-40, 6-32 and 8-32 screws and nuts. A very useable selection
1/2 pound \$1.50
1 pound 2.60

ELECTROLYTIC CAPS

2200 UF 35VDC Upright PC Lead \$.29
1000 UF 35VDC Upright PC Lead \$.29

FCM 7010 SPECIAL
4 DIGIT DIRECT DRIVE RADIO ALARM CHIP
SIMILAR TO MK50380
ONLY \$3.75

DIODES BY MOTOROLA

2-1/2 AMP 1000 VOLT
8 for \$1.00
Limited Quantity

LM309K \$1.50
NE565 1.00
NE555 .45
LM3900 .35

LOW POWER SCHOTTKY

74LS00	.25	74LS74	.49
74LS02	.25	74LS90	.85
74LS04	.30	74LS132	.90
74LS08	.25	74LS138	.89
74LS10	.25	74LS139	.89
74LS11	.32	74LS155	.90
74LS20	.31	74LS157	1.00
74LS21	.33	74LS162	1.39
74LS22	.33	74LS163	1.39
74LS27	.30	74LS175	1.09
74LS30	.31	74LS193	1.09
74LS32	.33	74LS258	1.09
74LS37	.40	74LS367	.70
74LS38	.35	74LS368	.70

BRIDGES

1 amp	50V	.85
4 amp	50V	.95
6 amp	50V	1.10
10 amp	50V	1.25
25 amp	50V	1.39

FND 359
COMMON CATHODE DIRECT REPLACEMENT FOR FND 70 BUT LARGER .40 IN. CHARACTER
Only \$.90
6 for \$4.95

FCS 8000
COMMON CATHODE 12 HOUR 3-1/2 DIGIT ARRAY
Includes AM/PM Indicator and Colon.
.80 in. character
\$4.95

PLASTIC READOUT FILTER

Originally used in desk top calculators. Perfect for LED and other type of readouts. With peel-off protective coating. AMBER in color 5-5/8 x 1-3/8. 6/\$1.00.

TTL 100% GUARANTEED! OR YOUR MONEY BACK.

7400	.19	7425	.30	7454	.19	74100	\$1.00
7401	.19	7426	.27	7470	.38	74123	.65
7402	.19	7427	.19	7472	.25	74125	.47
7403	.19	7432	.34	7473	.25	74141	.75
74L04	.29	7437	.39	7474	.39	74145	\$1.00
7404	.19	7438	.39	7475	.59	74154	\$1.00
7406	.29	7440	.19	7480	.49	74161	.95
7408	.19	7442	.65	7485	.95	74163	\$1.10
7409	.19	7443	.65	7490	.75	74164	\$1.10
7410	.19	7444	.69	7491	.75	74174	.95
7411	.29	7446	.89	7492	.75	74175	\$1.80
7413	.50	7447	.85	7493	.70	74180	.80
7420	.19	7450	.24	7494	.95	74191	\$1.25
7430	.19	7451	.19	7495	.75	74192	\$1.25
7421	.19	7453	.19	7496	.89	74193	\$1.00
7423	.39					74195	.69

CALL OUR TOLL FREE NUMBER 1-800-527-2304.
FOR QUANTITY DISCOUNT INFORMATION!

CMOS SALE

PRICES SLASHED - ALL PARTS ARE 100% PRIME

CD4000	.16	CD4023	.16	CD4053	.90
CD4001	.16	CD4024	.70	CD4056	1.00
CD4002	.16	CD4025	.19	CD4058	.90
CD4007	.16	CD4027	.39	CD4060	1.00
CD4009	.45	CD4028	.75	CD4066	.69
CD4010	.45	CD4029	.99	CD4069	.30
CD4011	.16	CD4030	.16	CD4071	.16
CD4012	.16	CD4035	.99	CD4076	.99
CD4013	.29	CD4040	1.00	CD4102	.68
CD4014	.75	CD4041	.69	CD4116	.39
CD4015	.75	CD4042	.59	CD4507	.40
CD4016	.29	CD4043	.60	CD4512	.50
CD4017	.80	CD4044	.59	CD4516	.85
CD4018	.80	CD4049	.35	CD4518	.85
CD4019	.39	CD4050	.35	CD4520	.85
CD4021	.90	CD4051	.90	CD4528	.80
CD4022	.90	CD4052	.90	CD4911	.30



AM/FM RADIO \$10

Plugs into wall, add your 2 speakers and you're ready to go. Calibrated sio motion am/fm tuning dial. Has stereo amps for use with phono or tape inputs to give stereo output. Solid state new.

H.H. SCOTT Misc Etched & Drilled P.C. Boards Asst. 15—\$1.00

GOULD NICADS NEW
 "AA" Cells 10—\$10.00
 Sub "C" Cells 5—\$7.00

GREEN LED 4—\$1.00
YELLOW LED
 w/MOUNT COLLAR 3—\$1.00

GALLIUM ARSENIDE
 IRLED EMITTER \$1 or 6/\$5.00

40 PIN SOCKET FOR MM5314- 5316-UART—Etc. 2/\$1.00

MAGNETIC RECORDING TAPE
AUDIO 1/4"
 3600 ft \$1.50 or 10 \$12.00
 1800 ft \$1.15 or 10 \$10.00
 MESHNA, PO BOX 62, E. Lynn Ma 01904

CIRCLE 30 ON FREE INFORMATION CARD

Computer People:



Announces a CPU board + front panel


Compatible with the standard S-100 buss, supported by over a dozen manufacturers. Upgrade your existing machine, or create your own system using other S-100 buss peripherals and a motherboard.

having minicomputer capabilities

Like a minicomputer, you may examine and alter registers, memory, and I/O locations while the program is running thanks to our "Control Halt" mode; with the "Slow Step" mode, you can step through a program from 1 step/minute to 65,000 steps/minute, giving true minicomputer capabilities.

that makes debugging much easier.

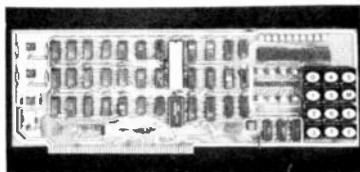Also includes unambiguous 7 segment readouts and a 12 key keyboard for easy loading and examination.



ASSEMBLED, TESTED, WARRANTED 1 YR. \$325
 KIT FORM \$250
 COMPLETE DOCUMENTATION PACKAGE \$ 5

CIRCLE 37 ON FREE INFORMATION CARD

SPRING SALE

100 Ass't'd Resistors (Cut Leads)	\$1.00
20 Ass't'd Wire Wound Resistors	\$1.00
20 Assorted Controls	\$1.00
20 Ass't'd Filter Cond. (Trans. Work)	\$1.00
10 HV Anode Leads—Small Cup	\$1.00
2-HV Anode Leads Large Cup	\$1.00
2-BOOST RECTIFIERS	\$1.00
2-8 KV FOCUS RECTIFIERS	\$1.00
10-1N34A CRYSTAL DIODES	\$1.00
5-UHF LOOP ANT. 18" Lead	\$1.00
2-SHUNT REG. HOODS (6BK4 Etc.)	\$1.00
3-Audio Output Xfms.	\$1.00
4 CRT Harness Color 19"23"25" CRT	\$1.00

1-21" CRT Converg. Assembly	\$1.00
1-25" CRT Converg. Assembly	\$1.00
10-500 Ohm Controls TAB Mount	\$1.00
10-1000 Ohm Controls TAB Mount	\$1.00
2-500 Mid. 50 VOLTS Axial	\$1.00
4-42-40 Mid. 150 Volts (P.C.)	\$1.00
25 Ass't'd Plate Caps	\$1.00
1-BSR 8TCS Cart. With Needles	\$1.00
1-75-300 Ant. Match. Xfmr.	\$1.00
2-UHF TUNERS DETENT TYPE	\$1.00
3-Ass't'd UHF TUNERS	\$1.00
1-3.58 MHZ COLOR CRYSTAL	\$1.00
2-PL 259 CB CONNECTORS	\$1.00
3-66 MEG. HV RESISTOR	\$1.00
5-ANT. CLOTHESPINs	\$1.00
10-RCA PHONO PLUGS	\$1.00
2-ASST'D SLIDE SWITCHES	\$1.00
1-UNDER PILLOW SPKE. 6 FT. LEAD-PLUG	\$1.00

ZENITH	
COLOR YOKE-S-89750	\$7.95
VIDEO IF STRIP-150-115	\$7.95
COLOR FLYBACK S-964530-2	\$6.95
ZENITH B/W YOKE-95-2874 (OTHERS)	\$6.95
VOLTAGE TRIPLER-212-139	\$7.95
VOLTAGE TRIPLER-212-109	\$2.95
2-15 MEG FOCUS CONTROL	\$1.00
1-CONV. DIODE PAK	\$1.00
1-45 KV HV STICK	\$3.95

COLOR FLYBACK XFMRs.	
MAGNAVOX 361374-1	\$5.95
PHILCO 32-10132-1	\$2.95 Each
RCA 136640	\$2.95
RCA 137545	\$2.95
GRAB BAG JAP FLYBACKS	2 for \$1.00

COLOR YOKES	
REPL. DY 95AC-Y-109. (LESS COVER)	\$6.95
GEN. ELECT. 76X8	\$1.50
70%- (21" CRT ROUND)	\$3.95
SYLVANIA 51-35809-2	\$6.95
SYLVANIA 51-29986-2	\$6.95
SYLVANIA 51-38553-2	\$6.95
SYLVANIA 51-33657-4	\$6.95
PACK BELL 290545-2E	\$6.95
FLEETWOOD 70F1811	\$6.95

ANTENNA EQUIPMENT	
1000 FT. 300 Ohm FOAM 7 Str.-100 Mil.	\$24.95
1000 FT. COAX CABLE (BLACK)	\$38.95
2-2 SET COUPLERS-300 OHM	\$3.00
2-4 Set COUPLERS-300 Ohm	\$4.50
2-BEHIND SET ANT (UNIV.)	\$5.00
UHF-VHF SPLITTER	\$1.49
UHF-VHF-FM-300 OHM SPLITTER	\$1.99

DIST. FOR B/K TEST EQUIPMENT
 DIST FOR SBE-CB-RADIOS
SEND FOR FREE CATALOG

TUBES UP TO 80% OFF
 MINIMUM ORDER \$50.00

Orders under \$50.00—\$2.00 shipping & handling

SEND CHECK OR M.O.

TV TECH SPECIALS
 P.O. BOX 603
 KINGS PARK, LI., NEW YORK 11754
 PHONE 516-269-0805

COLOR CRT BOOSTERS

70%-COLOR CRT BOOSTER	\$4.49 Ea.
3-70%-COLOR CRT BOOSTER	\$12.50
90%-COLOR CRT BOOSTER	\$4.95
90%-COLOR CRT BOOSTER	\$12.95
SONY COLOR CRT BOOSTER	\$3.75

DIODES-RECTIFIERS-

100-2.5 AMP. 1000 PIV	\$9.95
10-15KV FOCUS RECTIFIERS	\$4.50
WELLER CORD. SOLD. IRON	\$13.95
WAHL CORD. SOLD. IRON	\$13.95
WELLER 8200 PK KIT ONLY	\$10.95
30 WATT PEN. SOLD IRON	\$2.19

AUDIO EQUIP.

3-C-60 IRISH CASSETTE TAPES	\$1.49
3-C-90 IRISH CASSETTE TAPES	\$1.98
MONO TONEARMS	\$1.69 Ea.
3 WAY SPEAKER KIT WIRE	\$7.79
50 FT. SPEAKER WIRE	\$9.99
100 FT. SPEAKER WIRE	\$1.89
DYN. CASSETTE MIKE 200 OHM	\$1.89 Ea.
CB mike-600 OHM 5 Ft. Cord.	ONLY \$5.49

SPEAKERS

4X6 (16 OHMS)	ONLY \$1.19 Ea.
4" SQ	ONLY \$7.79 Ea.
3" SQ	ONLY \$7.79 Ea.
5 1/4"-5 Oz/MAG.	\$3.95 Ea.
5X7" SPEAKER	\$2.49
6X9-20 OZ. MAG.	\$10.95
6X9-10 OZ. MAG.	\$9.95
2" SQUARE	\$6.69

ZENITH IC CHIPS

REPL. 221-62	4 for \$5.00
REPL. 221-46-221-51	4 for \$5.00
REPL. 221-69	4 for \$5.00

25-ASST'D AXIAL LEAD COND.	\$3.95
25-ASST'D FILTER CANS	\$3.95
10 TEST LEADS COLOR CODED 15"	\$1.69
6-ASST'D ALIGN. TOOLS	\$1.00

TUNERS-NEW

PHILCO TRANS. 76-14340-1	\$3.95
SYLV. 5GJ7-3HQ5 (STAND COIL)	\$3.95
G.I. PAR. WAFER 6GS7-6HA5	2 for \$5.00
CURT. MATHS SERIES-6CG8-3GK5	\$3.25 Ea.
CURT. MATH PAR. 6GJ7-6HA5	\$3.25
REPL. ECG. VOLTAGE TRIP.	\$6.95 Each

REPL. DIAMOND NEEDLES

SHURE-N3D	\$2.95 Ea
SHURE-N-44	\$2.95
SHURE-N-75	\$2.95
SHURE-N-91	\$2.95
PICKERING-V-15-GREY	\$2.95
PICKERING-V-15-ORANGE	\$2.95
25 ASSORTED NEEDLES (GRAB BAG BOXED)	\$4.95
12 SPADE NEEDLES CARDED	ONLY \$2.49
BSR-45 SPINDLE FLAT	ONLY \$5.59 Ea.
89T-CARTRIDGE	\$1.29
12 ASST'D CKT. BREAKERS	\$5.95
1 Lb. SOLDER 60/40	\$4.95
CHEMTRONICS TUN-O-WASH 24 OZ.	\$2.99
CHEMTRONICS TUN-O-FOAM 8 OZ.	\$2.19
CHEMTRONICS TUN-O-POWER 8 OZ.	\$2.39
ZEN. VERT TRANS 121-758	\$2.95
ZEN. SPACE COMMAND "600" S-94463-HAND TRANS.	\$8.95

2-200 Mid. 175 Volts Rad. Leads	\$1.69
2-500 Mid. 200 V (CANS)	\$1.89
PHILCO FOCUS BLOCK 35-1390-6	\$2.50
PHILCO FOCUS BLOCK 35-1390-1	\$2.50
6-33 Mid. 350 V.-AXIAL	\$2.59
6-100 Mid. 250 Volts Axial	\$2.79
6-6 Ft. Cheater Cords	\$2.98

SENTURIAN TRAFFIC RADAR DETECTOR	
LIST PRICE \$89.95	YOUR COST \$54.95
SBE BRUTE-34 CB	\$69.95
SBE CATALINA III 29CB	\$74.95
SBE FORMULA D 26CB	\$89.95
SBE FORMULA D "TOUCH COM"	\$169.95
KRACO CB KCB 1300	\$74.95
KRACO KCB 1307	\$99.95
KRACO KCB 2330	\$119.00
KRACO KCB 2340	\$239.95

CIRCLE 62 ON FREE INFORMATION CARD

TTL 7400N

SN7400N	.15	SN74121N	.36
SN7401N	.15	SN74122N	.36
SN7402N	.15	SN74123N	.59
SN7403N	.15	SN74125N	.45
SN7404N	.18	SN74126N	.45
SN7405N	.18	SN74128N	.85
SN7405N	.18	SN74132N	.64
SN7406N	.34	SN74136N	.64
SN7407N	.34	SN74141N	.93
SN7408N	.18	SN74142N	.370
SN7409N	.18	SN74143N	3.98
SN7410N	.15	SN74144N	3.98
SN7411N	.21	SN74145N	.89
SN7412N	.28	SN74147N	1.68
SN7413N	.41	SN74149N	1.25
SN7414N	.79	SN74150N	9.99
SN7416N	.26	SN74151N	.63
SN7417N	.31	SN74153N	.63
SN7420N	.15	SN74154N	.99
SN7421N	.21	SN74155N	.78
SN7422N	.21	SN74156N	.69
SN7423N	.27	SN74157N	.64
SN7425N	.27	SN74159N	2.50
SN7426N	.24	SN74160N	8.99
SN7427N	.27	SN74161N	.89
SN7428N	.35	SN74162N	.89
SN7430N	.15	SN74163N	.89
SN7432N	.24	SN74164N	1.10
SN7433N	.35	SN74165N	.99
SN7437N	.23	SN74166N	1.19
SN7438N	.23	SN74167N	2.98
SN7440N	.15	SN74170N	1.75
SN7442N	.38	SN74172N	8.75
SN7443N	.85	SN74173N	1.29
SN7444N	.85	SN74174N	.99
SN7445N	.74	SN74175N	.89
SN7446AN	.78	SN74176N	.79
SN7447AN	.78	SN74177N	.78
SN7448N	.74	SN74178N	1.25
SN7450N	.15	SN74179N	1.60
SN7451N	.15	SN74180N	.69
SN7453N	.15	SN74181N	9.99
SN7454N	.15	SN74182N	.69
SN7460N	.15	SN74184N	1.89
SN7470N	.28	SN74185AN	1.85
SN7472N	.27	SN74186N	6.95
SN7473N	.31	SN74188N	3.50
SN7474N	.31	SN74190N	1.09
SN7475N	.48	SN74191N	1.09
SN7476N	.34	SN74192N	.88
SN7480N	.39	SN74193N	.88
SN7481AN	.99	SN74194N	.94
SN7482N	.59	SN74195N	.99
SN7483AN	.69	SN74196N	.93
SN7484AN	1.65	SN74197N	.83
SN7485N	.88	SN74198N	1.69
SN7486N	.32	SN74199N	1.69
SN7489N	1.95	SN74221N	1.20
SN7490AN	.45	SN74246N	1.95
SN7491AN	.64	SN74247N	1.85
SN7492AN	.66	SN74248N	1.75
SN7493AN	.46	SN74249N	1.75
SN7494N	.74	SN74251N	1.40
SN7495AN	.69	SN74265N	.85
SN7496N	.69	SN74278N	2.45
SN7497N	2.85	SN74279N	.59
SN74100N	.99	SN74283N	1.45
SN74104N	.43	SN74284N	4.50
SN74105N	.43	SN74285N	4.50
SN74107N	.29	SN74290A	.85
SN74109N	.49	SN74293N	.85
SN74110N	.54	SN74298N	1.98
SN74111N	.74	SN74351N	1.92
SN74116N	.75	SN74365N	1.65
SN74120N	1.40	SN74366N	.65
		SN74367N	.65
		SN74368N	.65
		SN74390N	1.40
		SN74490N	1.90

ZENER DIODES

IN4728—IN4752A	19
(1 watt molded)	
IN746A—IN759A	15
(400 MW)	

TTL LOW POWER SCHOTTKY

SN74LS00N	.25	SN74LS138N	1.49
SN74LS01N	.25	SN74LS139N	1.49
SN74LS02N	.25	SN74LS145N	1.25
SN74LS03N	.25	SN74LS151N	1.25
SN74LS04N	.30	SN74LS153N	1.25
SN74LS05N	.30	SN74LS155N	1.45
SN74LS06N	.25	SN74LS156N	1.45
SN74LS09N	.25	SN74LS157N	1.25
SN74LS10N	.25	SN74LS158N	1.20
SN74LS11N	.25	SN74LS160N	1.95
SN74LS12N	.25	SN74LS161N	1.95
SN74LS13N	.69	SN74LS162N	1.95
SN74LS14N	1.35	SN74LS163N	1.95
SN74LS15N	.25	SN74LS164N	1.98
SN74LS20N	.25	SN74LS168N	2.25
SN74LS21N	.25	SN74LS169N	2.25
SN74LS22N	.25	SN74LS170N	2.80
SN74LS26N	.40	SN74LS174N	1.40
SN74LS27N	.30	SN74LS175N	1.40
SN74LS28N	.30	SN74LS181N	3.50
SN74LS30N	.25	SN74LS190N	1.95
SN74LS32N	.37	SN74LS191N	1.95
SN74LS33N	.39	SN74LS192N	1.95
SN74LS37N	.39	SN74LS193N	1.95
SN74LS38N	.39	SN74LS194A	1.40
SN74LS40N	.30	SN74LS195A	1.40
SN74LS42N	1.10	SN74LS196N	1.45
SN74LS48N	1.10	SN74LS197N	1.45
SN74LS47N	1.10	SN74LS221N	2.95
SN74LS48N	1.10	SN74LS240N	2.50
SN74LS49N	1.10	SN74LS241N	2.50
SN74LS51N	.25	SN74LS242N	2.40
SN74LS54N	.25	SN74LS243N	2.40
SN74LS55N	.25	SN74LS244N	2.50
SN74LS63N	1.75	SN74LS247N	1.30
SN74LS73N	.49	SN74LS248N	1.30
SN74LS74N	.49	SN74LS249N	1.30
SN74LS75N	.69	SN74LS251N	1.55
SN74LS76N	.49	SN74LS253N	1.55
SN74LS78N	.49	SN74LS257N	1.60
SN74LS83AN	1.49	SN74LS258N	1.50
SN74LS85N	1.75	SN74LS261N	2.95
SN74LS86N	.58	SN74LS266N	.59
SN74LS90N	.99	SN74LS279N	.75
SN74LS91N	1.15	SN74LS283N	1.40
SN74LS92N	1.10	SN74LS290N	1.35
SN74LS93BN	.99	SN74LS293N	1.35
SN74LS95AN	1.60	SN74LS295AN	1.75
SN74LS96N	1.75	SN74LS298AN	1.75
SN74LS107N	.49	SN74LS324AN	2.25
SN74LS109N	.55	SN74LS352AN	1.45
SN74LS112N	.49	SN74LS353AN	1.70
SN74LS113N	.49	SN74LS365AN	.75
SN74LS114N	.49	SN74LS366AN	.75
SN74LS122N	.89	SN74LS375AN	.75
SN74LS123N	1.09	SN74LS368AN	.75
SN74LS124N	1.95	SN74LS375AN	.80
SN74LS125N	.75	SN74LS386AN	.59
SN74LS126N	.75	SN74LS395AN	1.95
SN74LS132N	1.25	SN74LS670AN	2.95
SN74LS136N	.55		

We offer the largest variety of current production Texas Instruments and Fairchild Semiconductor only 74LS devices from stock. Even through the competition for current production major manufactured 74LS devices is limited, we are dedicated to provide the best prices possible. As our costs decrease, we pass the savings on to you, our customer.

TEXAS INSTRUMENTS DATA BOOKS

STK NO.	DESCRIPTION	PRICE
LCB1011	Understanding Solid State Electronics	2.95
LCB1041	Linear & Interface Applications	6.95
LCC4041	Power Data Book	3.95
LCC4111	TTL Data Book	3.95
LCC4131	Transistor & Diode Data Book	4.95
MCC4151	Linear & Interface I.C. Data Book	3.95
LCC4161	TTL Supplement Data Book	1.95
LCC4191	Optoelectronics Data Book	2.95
LCC4200	Semiconductor Memories Data Book	2.95

FAIRCHILD DATA BOOKS

Linear Integrated Circuits Data Book	2.95
Low Power Schottky & Macrologic TTL	1.75
MOS/CMOS/N-MOS/P-MOS & charge coupled Devices Interface Data Book	2.50
Full Line Condensed Catalogue	1.00
Microelectronic & MOS Data Book	1.95

GENERAL INSTRUMENT DATA BOOK

Microelectronic & MOS Data Book	2.95
---------------------------------	------

STANDARD MICROSYSTEMS

COM2502	8 Bit Uart	7.95
COM2601	Universal Synchronous Receiver Transmitter	23.50
COM2017	8 Bit Uart	8.50

MOS & BI-POLAR MEMORIES

FAIRCHILD		
2102-IP	1K Static Ram 1024X1 (450NS)	2.50
3342PC	Quad 64 Bit Static Shift Register	4.50
3347PC	quad 80 Bit Static Shift Register	4.50
3341APC	4X64 Mos Fifo	4.50
4096-SDC	1 mhz Shift Register Isoplanar 4K Dynamic Ram (350 NS) 16 pin	10.50
TEXAS INSTRUMENTS		
TMS0117NC	Decimal Arithmetic Processor	10.00
LCM1001	Microprocessor Learning Module	149.95
TMS3113NC	Dual 133 Bit Static Shift Register	4.95
TMS3112NC	Hex 32 Bit Static Shift Register	4.95
TMS4024NC	64X9 Fifo	8.95
TMS4030NL	4K Dynamic Ram Plastic 300 NS (22 Pin)	9.95
TMS4050NL	4X Dynamic Ram Plastic 300 NS (18 Pin)	9.95
TMS4060NL	4K Dynamic Ram Plastic 300 NS (22 Pin)	9.95
TMS4103NC	64X5X7 ASCII Character Generator Column Output	10.00
TMS8080JL	8 Bit N-channel Microprocessor	29.95
GENERAL INSTRUMENT		
AY5-1013P	8 Bit Uart	6.95
AY5-2376	8X3X9 Keyboard Encoder	15.95
M.I.L.		
MF1403AT	Dual 512 Dynamic Shift Register	2.95
MF1404AT	1024X1 Dynamic Shift Register	2.75
MF1702AR	256X8 Static Prom	12.95
MF8008R	Mos 8 Bit Cpu 500 Khz	12.95

CMOS

CD4000BE	.10
CD4001BE	.19
CD4002BE	.14
CD4006BE	1.19
CD4007BE	.18
CD4008BE	.85
CD4009BE	.39
CD4010BE	.39
CD4012BE	.18
CD4013BE	.39
CD4014BE	.95
CD4015BE	.95
CD4016BE	.39
CD4017BE	.99
CD4018BE	1.09
CD4019BE	.44
CD4020BE	1.09
CD4021BE	1.15
CD4022BE	.95
CD4023BE	.19
CD4024BE	.69
CD4025BE	.18
CD4026BE	1.45
CD4027BE	.44
CD4028BE	.79
CD4029BE	.89
CD4030BE	.39
CD4033BE	1.70
CD4034BE	2.95
CD4035BE	1.05
CD4040BE	1.05
CD4041BE	.69
CD4042BE	.65
CD4043BE	.50
CD4049BE	.39
CD4050BE	.39
CD4051BE	1.20
CD4052BE	1.20
CD4053BE	1.25
CD4055BE	1.35
CD4056BE	1.50
CD4060BE	1.50
CD4066BE	.65
CD4068BE	.25
CD4069BE	.25
CD4070BE	.25
CD4071BE	.25
CD4072BE	.30
CD4073BE	.30
CD4075BE	.30
CD4076BE	1.10
CD4078BE	.25
CD4081BE	.25
CD4082BE	.30
CD4085BE	.75
CD4086BE	.75
CD4502BE	1.20
CD4507BE	.54
CD4510BE	1.10
CD4511BE	1.50
CD4512BE	1.20
CD4516BE	1.19
CD4518BE	.95
CD4519BE	.89
CD4520BE	.89
CD4528BE	1.25
CD4531BE	1.25
CD4539BE	1.20
CD4555BE	.75
CD4556BE	.75
CD4558BE	1.80
74C85/40085PC	1.20
74C160/40160PC	1.65
74C161/40161PC	.65
74C162/40162PC	1.65
74C163/40163PC	1.65
74C174/40174PC	1.50
74C175/40175PC	1.50
74C193/40193PC	1.65
74C193/40193PC	1.65
74C194/40194PC	1.50
74C195/40195PC	1.50

LED's

Litronix		
IL1	1.05	
IL5	1.15	
IL12	.69	
IL74	.82	
RL2	.23	
Texas Instruments		
TIL111	.99	
TIL112	.95	
TIL113	1.25	
TIL114	1.15	
TIL117	1.30	
TIL118	.80	
TIL119	.85	
TIL138	2.25	
TIL139	2.25	
TIL209A	1.20	
TIL211	.39	
TIL220	.20	
TIL221	.19	
TIL222	.35	
TIL23	1.98	
TIL24	3.95	
TIL302	3.98	
TIL303	3.98	
TIL304	3.98	
TIL305	4.95	
TIL306	7.95	
TIL307	7.95	
TIL308	7.95	
TIL309	7.95	
TIL311	8.95	
TIL312	1.60	
TIL313	1.60	
TIL31	1.50	
TIL32	.85	
TIL63	.95	
TIL76	.60	
TIL81	1.20	
LS601	2.10	
Fairchild		
FCD802	.60	
FCD806	.60	
FCD810	.75	
FCD820A	.75	
FLV117	.18	
MV5054-1	.18	
FND357	1.75	
FND500	1.75	
FND507	1.75	
FND807	3.00	
FNS700	.60	

Plastic Power Transistors

TIP29A	45	TIP116	.80
TIP30C	59	TIP117	.90
TIP31A	52	TIP121	1.25
TIP32A	55	TIP122	1.50
TIP33C	90	TIP125	1.35
TIP41A	65	TIP127	1.60
TIP42A	75	TIP295S	.89
TIP47	88	TIP305S	.85

7400N TTL

SN7400N	16	SN7498A	35	SN74154N	1.00
SN7401N	16	SN7498B	22	SN74155N	99
SN7402N	21	SN7470G	45	SN74157N	99
SN7403N	16	SN7472N	39	SN74159N	1.25
SN7404N	18	SN7473N	37	SN74161N	99
SN7405N	24	SN7474N	32	SN74163N	99
SN7406N	20	SN7475N	50	SN74165N	1.10
SN7407N	29	SN7476N	32	SN74167N	2.10
SN7408N	25	SN7477N	5.00	SN74169N	2.10
SN7409N	25	SN7478N	39	SN74170N	8.95
SN7410N	18	SN7479N	35	SN74171N	1.50
SN7411N	30	SN7480N	2.49	SN74172N	1.50
SN7412N	33	SN7481N	4.50	SN74173N	1.50
SN7413N	45	SN7482N	3.49	SN74174N	99
SN7414N	35	SN7483N	70	SN74175N	99
SN7415N	33	SN7484N	89	SN74176N	90
SN7416N	38	SN7485N	49	SN74177N	90
SN7417N	35	SN7486N	49	SN74178N	2.49
SN7420N	21	SN7487N	75	SN74179N	95
SN7421N	33	SN7488N	75	SN74180N	1.95
SN7422N	39	SN7489N	49	SN74181N	2.00
SN7423N	47	SN7490N	79	SN74182N	2.00
SN7424N	29	SN7491N	79	SN74183N	2.00
SN7425N	29	SN7492N	89	SN74184N	2.00
SN7426N	29	SN7493N	89	SN74185N	2.00
SN7427N	37	SN7494N	89	SN74186N	2.00
SN7428N	46	SN7495N	1.00	SN74187N	2.00
SN7429N	27	SN7496N	1.00	SN74188N	2.00
SN7430N	26	SN7497N	1.00	SN74189N	2.00
SN7431N	31	SN7498N	1.00	SN74190N	2.00
SN7432N	37	SN7499N	1.00	SN74191N	2.00
SN7433N	27	SN7500N	1.00	SN74192N	2.00
SN7434N	27	SN7501N	1.00	SN74193N	2.00
SN7435N	27	SN7502N	1.00	SN74194N	2.00
SN7436N	27	SN7503N	1.00	SN74195N	2.00
SN7437N	27	SN7504N	1.00	SN74196N	2.00
SN7438N	27	SN7505N	1.00	SN74197N	2.00
SN7439N	25	SN7506N	1.00	SN74198N	2.00
SN7440N	15	SN7507N	1.00	SN74199N	2.00
SN7441N	29	SN7508N	1.00	SN74200N	2.00
SN7442N	58	SN7509N	1.00	SN74201N	2.00
SN7443N	25	SN7510N	1.00	SN74202N	2.00
SN7444N	15	SN7511N	1.00	SN74203N	2.00
SN7445N	26	SN7512N	1.00	SN74204N	2.00
SN7446N	81	SN7513N	1.00	SN74205N	2.00
SN7447N	69	SN7514N	1.00	SN74206N	2.00
SN7448N	69	SN7515N	1.00	SN74207N	2.00
SN7449N	26	SN7516N	1.00	SN74208N	2.00
SN7450N	26	SN7517N	1.00	SN74209N	2.00
SN7451N	27	SN7518N	1.00	SN74210N	2.00
SN7452N	27	SN7519N	1.00	SN74211N	2.00
SN7453N	27	SN7520N	1.00	SN74212N	2.00
SN7454N	20	SN7521N	1.00	SN74213N	2.00

MANY OTHERS AVAILABLE ON REQUEST
20% Discount for 100 Combined 7400's

CD4000	25	CD4001	25	CD4002	25
CD4003	25	CD4004	25	CD4005	25
CD4006	25	CD4007	25	CD4008	25
CD4009	25	CD4010	25	CD4011	25
CD4012	25	CD4013	25	CD4014	25
CD4015	25	CD4016	25	CD4017	25
CD4018	25	CD4019	25	CD4020	25
CD4021	25	CD4022	25	CD4023	25
CD4024	25	CD4025	25	CD4026	25
CD4027	25	CD4028	25	CD4029	25
CD4030	25	CD4031	25	CD4032	25

LINEAR

LM3000	80	LM3001	35	LM3002	35
LM3003	35	LM3004	35	LM3005	35
LM3006	35	LM3007	35	LM3008	35
LM3009	35	LM3010	35	LM3011	35
LM3012	35	LM3013	35	LM3014	35
LM3015	35	LM3016	35	LM3017	35
LM3018	35	LM3019	35	LM3020	35
LM3021	35	LM3022	35	LM3023	35
LM3024	35	LM3025	35	LM3026	35
LM3027	35	LM3028	35	LM3029	35
LM3030	35	LM3031	35	LM3032	35
LM3033	35	LM3034	35	LM3035	35
LM3036	35	LM3037	35	LM3038	35
LM3039	35	LM3040	35	LM3041	35
LM3042	35	LM3043	35	LM3044	35
LM3045	35	LM3046	35	LM3047	35
LM3048	35	LM3049	35	LM3050	35
LM3051	35	LM3052	35	LM3053	35
LM3054	35	LM3055	35	LM3056	35
LM3057	35	LM3058	35	LM3059	35
LM3060	35	LM3061	35	LM3062	35
LM3063	35	LM3064	35	LM3065	35
LM3066	35	LM3067	35	LM3068	35
LM3069	35	LM3070	35	LM3071	35
LM3072	35	LM3073	35	LM3074	35
LM3075	35	LM3076	35	LM3077	35
LM3078	35	LM3079	35	LM3080	35
LM3081	35	LM3082	35	LM3083	35
LM3084	35	LM3085	35	LM3086	35
LM3087	35	LM3088	35	LM3089	35
LM3090	35	LM3091	35	LM3092	35
LM3093	35	LM3094	35	LM3095	35
LM3096	35	LM3097	35	LM3098	35
LM3099	35	LM3100	35	LM3101	35
LM3102	35	LM3103	35	LM3104	35
LM3105	35	LM3106	35	LM3107	35
LM3108	35	LM3109	35	LM3110	35
LM3111	35	LM3112	35	LM3113	35
LM3114	35	LM3115	35	LM3116	35
LM3117	35	LM3118	35	LM3119	35
LM3120	35	LM3121	35	LM3122	35
LM3123	35	LM3124	35	LM3125	35
LM3126	35	LM3127	35	LM3128	35
LM3129	35	LM3130	35	LM3131	35
LM3132	35	LM3133	35	LM3134	35
LM3135	35	LM3136	35	LM3137	35
LM3138	35	LM3139	35	LM3140	35
LM3141	35	LM3142	35	LM3143	35
LM3144	35	LM3145	35	LM3146	35
LM3147	35	LM3148	35	LM3149	35
LM3150	35	LM3151	35	LM3152	35
LM3153	35	LM3154	35	LM3155	35
LM3156	35	LM3157	35	LM3158	35
LM3159	35	LM3160	35	LM3161	35
LM3162	35	LM3163	35	LM3164	35
LM3165	35	LM3166	35	LM3167	35
LM3168	35	LM3169	35	LM3170	35
LM3171	35	LM3172	35	LM3173	35
LM3174	35	LM3175	35	LM3176	35
LM3177	35	LM3178	35	LM3179	35
LM3180	35	LM3181	35	LM3182	35
LM3183	35	LM3184	35	LM3185	35
LM3186	35	LM3187	35	LM3188	35
LM3189	35	LM3190	35	LM3191	35
LM3192	35	LM3193	35	LM3194	35
LM3195	35	LM3196	35	LM3197	35
LM3198	35	LM3199	35	LM3200	35

74LS00 TTL

74LS00	29	74LS01	29	74LS02	29
74LS03	29	74LS04	29	74LS05	29
74LS06	29	74LS07	29	74LS08	29
74LS09	29	74LS10	29	74LS11	29
74LS12	29	74LS13	29	74LS14	29
74LS15	29	74LS16	29	74LS17	29
74LS18	29	74LS19	29	74LS20	29
74LS21	29	74LS22	29	74LS23	29
74LS24	29	74LS25	29	74LS26	29
74LS27	29	74LS28	29	74LS29	29
74LS30	29	74LS31	29	74LS32	29
74LS33	29	74LS34	29	74LS35	29
74LS36	29	74LS37	29	74LS38	29
74LS39	29	74LS40	29	74LS41	29
74LS42	29	74LS43	29	74LS44	29
74LS45	29	74LS46	29	74LS47	29
74LS48	29	74LS49	29	74LS50	29
74LS51	29	74LS52	29	74LS53	29
74LS54	29	74LS55	29	74LS56	29
74LS57	29	74LS58	29	74LS59	29
74LS60	29	74LS61	29	74LS62	29
74LS63	29	74LS64	29	74LS65	29
74LS66	29	74LS67	29	74LS68	29
74LS69	29	74LS70	29	74LS71	29
74LS72	29	74LS73	29	74LS74	29
74LS75	29	74LS76	29	74LS77	29
74LS78	29	74LS79	29	74LS80	29
74LS81	29	74LS82	29	74LS83	29
74LS84	29	74LS85	29	74LS86	29
74LS87	29	74LS88	29	74LS89	29
74LS90	29	74LS91	29	74LS92	29
74LS93	29	74LS94	29	74LS95	29
74LS96	29	74LS97	29	74LS98	29
74LS99	29	74LS00	29	74LS01	29

CLOCK CHIPS

MM5309	6 Digt. BCD Outputs, Reset Pin	\$9.95
MM5311	6 Digt. BCD Outputs, 12 or 24 Hour	\$9.95
MM5312	4 Digt. BCD Outputs, 1 PPS Output	4.95
MM5314	4 Digt. 12 or 24 Hour, 50 or 60 Hz	4.95
MM5316	4 Digt. Alarm + PPS Output	4.95
MM5318	Video Data Chg. For Use With MM5341	9.95
CT7001	6 Digt. Calendar, Alarm, 12 or 24 Hour	5.95

DATA HANDBOOKS

7400 Pin-out & Description of 5400/7400 ICs \$2.95
CMOS Pin-out & Description of 4000 Series ICs \$2.95
Linear Pin-out & Functional Description of 7400 Series ICs \$2.95
ALL THREE HANDBOOKS \$6.95

FAIRCHILD TECHNOLOGY KITS FAIRCHILD

• Complete Specifications on back of each kit
• Packaged for WALL DISPLAY APPEARANCE
• Dealer's Inquires Invited — Price List Available

7205 - Stop Watch Chip \$19.95

FTK0001	0.5" High Common Cathode Digit	\$1.00
FTK0002	0.5" High Common Anode Digit	1.00
FTK0003	0.5" High Common Cathode Digit	7.75
FTK0004	0.8" High Common Cathode Digit	2.00
FTK0005	0.8" High Common Anode Digit	2.00

0.8" HIGH DISPLAY ARRAYS

FTK0010	12 Hour, 3 1/2 Digit Clock Display	7.00
FTK0011	24 Hour, 4 Digit Clock Display	8.00

LED LAMPS

FTK0020	10 Red LED Lamps	1.00
FTK0021	5 Mixed Colored LED Lamps	1.00
FTK0022	10 LED Mounting Clips	1.00
FTK0023	5 Three Piece LED Mounting Adapters	1.00

PHOTO TRANSISTORS

FTK0030	5 Flat Lens Photo Transistors	1.00
FTK0031	5 Round Lens Photo Transistors	1.00
FTK0032	3 Flat Lens Photo Darlington	1.00
FTK0033	3 Round Lens Photo Darlington	1.00

PHOTO ARRAYS

FTK0040	9-Element Tape Reader Array	16.00
FTK0041	12-Element Card Reader Array	24.00
FTK0042	Reflective Opto Coupler	4.00

COUPLERS

FTK0050	3 General Purpose Opto Couplers	1.00
FTK0051	Damington Opto Coupler	1.00

MOS CLOCK CIRCUITS

FTK0400	Digital Clock Calendar Circuit (FCM7001)	7.00
FTK0401	Digital Clock Calendar with BCD Outputs (FCM7002)	7.00
FTK0402	Direct Drive Digital Clock Circuit with AC Output (FCM3817A)	5.00
FTK0403	Direct Drive Digital Clock Circuit with DC Output (FCM3817D)	5.00
FTK0405	Direct Drive Digital Clock Calendar Circuit (FCM7015)	6.00

WITS

FTK0106	Automobile Clock Kit	40.00
---------	----------------------	-------

DISCRETE LEADS

XC209	Red	10S1	XC111	Red	10S1
XC209	Green	4S1	XC111	Green	4S1
XC209	Orange	4S1	XC111	Yellow	4S1
			XC111	Orange	4S1

DISCRETE LEADS

XC22	Red	10S1	XC556	Red	10S1
XC22	Green	4S1	XC556	Green	4S1
XC22	Yellow	4S1	XC556	Yellow	4S1
XC22	Orange	4S1	XC556	Orange	4S1
SS12	RT	4S1	XC556</		

CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case/Style	Price
CY1A	1 000 MHz	HC33 U	\$5.95
CY2A	2 000 MHz	HC18 U	\$5.95
CY3A	4 000 MHz	HC18 U	\$4.95
CY7A	5 000 MHz	HC18 U	\$4.95
CY12A	10 000 MHz	HC18 U	\$4.95
CY14A	14 318.18 MHz	HC18 U	\$4.95
CY19A	18 000 MHz	HC18 U	\$4.95
CY22A	20 000 MHz	HC18 U	\$4.95
CY30A	32 300 MHz	HC18 U	\$4.95

XR-2260KB KH \$27.95

XR-2206KA KH \$17.95

WAVEFORM GENERATORS		TIMERS	
XR 205	\$4.40	XR 555CP	\$ 99
XR 2206CP	4.49	XR 320P	1.55
XR 2207CP	3.85	XR 556CP	1.85
		XR 2556CP	3.20
		XR 2240CP	3.25
		XR 2240CP	3.25
		XR 210	5.20
		XR 215	6.00
		XR 567CT	1.95

CONNECTORS

PRINTED CIRCUIT EDGE-CARD

156 Spacing-Tin-Double Read-Out

Bifurcated Contacts — Frits 054 to 070 P.C. Cards

15/30	PINS (Solder Eyelet)	\$1.95
18/36	PINS (Solder Eyelet)	\$2.49
22/44	PINS (Solder Eyelet)	\$2.95
50/100 (100 Spacing)	PINS (Solder Eyelet)	\$6.95

25 PIN-D SUBMINIATURE

DB25	PLUG	\$3.25
DB25	SOCKET	\$4.95

3 1/2 DIGIT DVM KIT



This 0-2 VDC .05 per cent digital voltmeter features the Motorola 3 1/2 digit DVM chip set. It has a 4 LED display and operates from a single +5V power supply. The unit is provided complete with an injection molded black plastic case complete with Bezel. An optional power supply is available which fits into the same case as the 0.2V DVM allowing 117 VAC operation.

- A. 0-2V DVM with Case \$49.95
- B. 5V Power Supply \$14.95

VECTOR WIRING PENCIL

Vector Wiring Pencil P173 consists of a hand held featherweight (under one ounce) too which is used to guide and wrap wires. It is a red off a self contained replaceable bobbin onto component leads or terminals installed on a punched P1 Pattern Vectorboard. Connectors between the 1/16 spaced wire and component leads or terminals are made by soldering. Complete with 250 FT. of red wire \$9.95

REPLACEMENT WIRE — BOBBINS FOR WIRING PENCIL

W36-3 A Pkg 3	250 ft. 36 AWG GREEN	\$2.40
W36-3 B Pkg 3	250 ft. 36 AWG RED	\$2.40
W36-3 C Pkg 3	250 ft. 36 AWG CLEAR	\$2.40
W36-3 D Pkg 1	250 ft. 36 AWG BLUE	\$2.40

1/16 VECTOR BOARD

Part No.	Material	4.50	6.50	1.72	1.54
PHENOLIC	64P44 082XXP	4.50	17.00	3.69	3.32
	169P4 021XXP	4.50	6.50	2.07	1.86
LPO+V	64P44 082	4.50	8.00	2.56	2.31
GLASS	169P44 082	4.50	17.00	5.04	4.53
	169P4 082	4.50	17.00	9.23	8.26
EPD+V GLASS	169P44 082C1	4.50	17.00	6.80	6.12
COPPER CLAD					

HEAT SINKS

285-CB	Beryllium Copper Heat Sink with Black Finish for TD 5	\$.25
291-.36H	Aluminum Heat Sink for TD 220 Transistors & Regulators	\$.25
680-75A	Black Anodized Aluminum	\$1.60

HEXADECIMAL ENCODER 19-KEY PAD



\$10.95 each

63 KEY KEYBOARD



\$19.95

HD0166 16 LINE TO FOUR BIT PARALLEL KEYBOARD ENCODER \$7.95

JOYSTICK



*5K Pots \$6.95
*100K Pots \$7.95

MICROPROCESSOR COMPONENTS

8080A	CPU	\$19.95	MC6800L	8 Bit MPU	\$35.00
8212	8 Bit Input/Output	4.95	MC6820L	Periph Interface Adapter	15.00
8216	Bi-Directional Bus Driver	6.95	MC6810AP1	128 x 8 Static RAM	6.00
8224	Clock Generator/Driver	10.95	MC6830L7	1024 x 8 Bit ROM	18.00
8228	System Controller - Bus Driver	10.95			

CPU S		RAM S	
8008	8 Bit CPU	1101	256 x 1
8080	Super 8008	1103	1024 x 1
8080A	Super 8008	2101	256 x 4
		2102	1024 x 4
		2107	4096 x 1
		2111	256 x 4
		2100	1024 x 1
		2104	16 x 4
		2105	256 x 4
		2106	1024 x 4
		2107	4096 x 1
		2108	256 x 4
		2109	1024 x 4
		2110	256 x 4
		2111	1024 x 4
		2112	256 x 4
		2113	1024 x 4
		2114	256 x 4
		2115	1024 x 4
		2116	256 x 4
		2117	1024 x 4
		2118	256 x 4
		2119	1024 x 4
		2120	256 x 4
		2121	1024 x 4
		2122	256 x 4
		2123	1024 x 4
		2124	256 x 4
		2125	1024 x 4
		2126	256 x 4
		2127	1024 x 4
		2128	256 x 4
		2129	1024 x 4
		2130	256 x 4
		2131	1024 x 4
		2132	256 x 4
		2133	1024 x 4
		2134	256 x 4
		2135	1024 x 4
		2136	256 x 4
		2137	1024 x 4
		2138	256 x 4
		2139	1024 x 4
		2140	256 x 4
		2141	1024 x 4
		2142	256 x 4
		2143	1024 x 4
		2144	256 x 4
		2145	1024 x 4
		2146	256 x 4
		2147	1024 x 4
		2148	256 x 4
		2149	1024 x 4
		2150	256 x 4

Continental Specialties

Proto Board 100 \$19.95

THE MINI-BREADBOARD BUDGET KIT \$29.95

Proto Board 182 \$39.95

Proto Board 183 \$29.95

Proto Board 184 \$39.95

Proto Board 185 \$39.95

Proto Board 6 \$15.95

LOGIC MONITOR \$84.95

SPECIAL!

Q1 995

Q1 598

Q1 475

Q1 478

Q1 355

Q1 358

Q1 185

Q1 125

Q1 85

Q1 75

Q1 type

Q1 585

Q1 590

Q1 475

Q1 178

Q1 355

Q1 358

Q1 185

Q1 125

Q1 85

Q1 75

holes

12.50

2.00

10.00

2.25

3.00

2.00

4.50

3.50

3.50

3.40

GEMINI-68 The Unique Microprocessing System

ALL BOARDS BUS EXPANDABLE

Uses standard size 4 1/2" wide boards, dual 22 pin edge connector Fully buffered and tristatable address and data buses

STAND ALONE CPU BOARD — Has 384 bytes of RAM on board, serial I/O (RS-232 and 20 ma current loop, cycle stealing direct memory access (DMA), built in software — selectable echo-back capability Part # SA-CPU Board \$279.95

CPU BOARD — Same as above but only has 128 bytes of RAM on board-used with 8K RAM board listed below Part # Gemini 68 CPU Board \$259.95


8K RAM BOARD — Uses low power static RAMS, 500ns cycle time, 1.5 Amps Max Part # Gemini 68 RAM Board \$269.95

8K EPROM BOARD — Uses 5204 EPROMS by AMI or NATIONAL Shipped with all decode and miscellaneous I/O, excepts the 5204 EPROMS Part # Gemini 68 EPROM Board \$ 89.95

NOT A KIT — ALL BOARDS ARE COMPLETELY ASSEMBLED, BURNED-IN AND TESTED COMES WITH COMPLETE DOCUMENTATION

Allow approximately four weeks to delivery

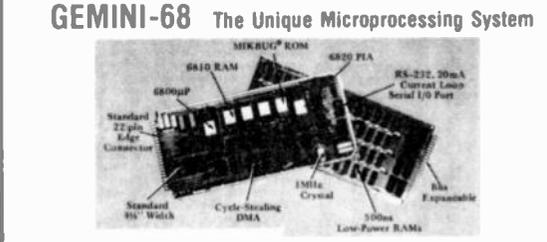\$5.00 Minimum Order — U.S. Funds Only Spec. Sheets - 25¢ — Send 24¢ Stamp for 1977 Catalog
California Residents — Add 9% Sales Tax Dealer Discount Available — Request Pricing



JE700 CLOCK

The JE 700 is a low cost digital clock but is a very high quality unit. The unit features a simulated walnut case with dimensions of 12" x 12" x 1 1/2". It utilizes a MAN72 high brightness red and the MMS314 clock chip.

\$17.95

JE500 KIT - ALL COMPONENTS & CASE \$34.95 WIRE & ASSEMBLED \$39.95

DIGITAL CLOCK KIT — 3 1/2" INCH DIGITS

4 DIGIT KIT \$49.95 4 DIGIT ASSEMBLED \$59.95
6 DIGIT KIT \$69.95 6 DIGIT ASSEMBLED \$79.95

This clock features big 3 1/2" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2 LED's. The clock operates from 117 VAC, has either 12 or 24 hr operation. The 6 digit version is 27" x 3 1/2" x 1 1/2" and the 4 digit is 18" x 3 1/2" x 1 1/2". Kits come complete with all components, case and transformer. Specify 12 or 24 Hour When Ordering.

JE803 PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic schemes. TTL, DTL, RTL, CMOS, it can verify the power it needs to operate directly off the circuit under test. Drawing a scant 10 mA, it uses a MAN73 readout to indicate any of the following states by these symbols: L (LOW), 0 (PULSE), P (The Probe can detect high frequency pulses to 25 MHz. It can be used at MOS levels or circuit ground with result.

\$9.95 Per Kit

printed circuit board

T5L 5V 1A Supply

This is a standard TTL power supply using the well known W309N regulator. It provides a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package including the hardware for only

\$9.95 Per Kit

NOW OPEN SATURDAYS

James ELECTRONICS

1021-A HOWARD AVE., SAN CARLOS, CA. 94070
PHONE ORDERS WELCOME — (415) 592-8097
All Advertised Prices Good Thru March

DIP SWITCH

These switches have a seven SPC slide switches in a molded case. They are ideally suited for microprocessor applications. \$1.95

Timeband

A Division of Photo Camera and Telephoto Corporation

DIGITAL ALARM CLOCK \$16.95

- 24-Hour Alarm
- DOZE Button
- 100% Solid State
- Large Red LED Display (8 high)
- AM/PM Indicator
- Seconds Display at touch of button
- SPECIFY BLACK OR IVORY

DIGITAL WATCHES

Ladies Watch

- 8 Function
- Bracket Styling
- 1 Year Guarantee
- Model 900
- Specify Gold or Chrome

\$59.95

EXLAR Mens Watch

- Quartz Crystal
- Black Leather Band
- Manufacturer Guarantee
- Specify Gold or Chrome

\$25.00

5 FUNCTION ELECTRONIC CALCULATOR RADOFIN MODEL 8P

\$8.95

FEATURES

- 8 Digit Display
- 5 Functions consist of addition, subtraction, multiplication, division, percentage with constant on all functions with full floating decimal point
- Power source is 1 piece 9V DC Battery 009P jack for AC adapter
- 8 Back-spring plated metal plastic cabinet

DIGITAL STOPWATCH

Bright 6 Digit LED Display
Times to 99 minutes 59.99 seconds
Crystal Controlled Time Base
Three Stopwatches in One
Times Single Event Split & Taylor
Size 4.5" x 2.15" x .90" (4 1/2" outside)
Uses 3 Penne Cells

Kit — \$39.95
Assembled — \$49.95
Heavy Duty Carry Case \$5.95

DIGITAL QUARTZ CAR CLOCK

Complete 1 1/2" mounting bracket of the injection molded case down to the three conductive pins. 0-3 and all components including MMS314 clock chip. Features quartz accuracy of 0.1 degree 35 high LED display and P.C. Board. Works on any 12 volt system — motor cycles, boats, vans, micro buses, & 10s and 100s.

Kit: \$29.95
Assembled: \$39.95

CASE ONLY (includes hardware mounting bracket and bezel) \$5.95

DIMENSIONS: 1 1/2" x 1 1/2" x 1 1/2"
12 or 24 HOUR MODE

JE700 CLOCK

The JE 700 is a low cost digital clock but is a very high quality unit. The unit features a simulated walnut case with dimensions of 12" x 12" x 1 1/2". It utilizes a MAN72 high brightness red and the MMS314 clock chip.

\$17.95

115 VAC

This large digit clock (6 Hours & minutes) 3 seconds) features the MMS314 clock chip. It operates from 117 VAC and will operate in either a 12 or 24 hour mode. The clock is complete with a walnut grain case and has fast set slow set and hold time set features.

JE500 KIT - ALL COMPONENTS & CASE \$34.95 WIRE & ASSEMBLED \$39.95

DIGITAL CLOCK KIT — 3 1/2" INCH DIGITS

4 DIGIT KIT \$49.95 4 DIGIT ASSEMBLED \$59.95
6 DIGIT KIT \$69.95 6 DIGIT ASSEMBLED \$79.95

This clock features big 3 1/2" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2 LED's. The clock operates from 117 VAC, has either 12 or 24 hr operation. The 6 digit version is 27" x 3 1/2" x 1 1/2" and the 4 digit is 18" x 3 1/2" x 1 1/2". Kits come complete with all components, case and transformer. Specify 12 or 24 Hour When Ordering.

JE803 PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic schemes. TTL, DTL, RTL, CMOS, it can verify the power it needs to operate directly off the circuit under test. Drawing a scant 10 mA, it uses a MAN73 readout to indicate any of the following states by these symbols: L (LOW), 0 (PULSE), P (The Probe can detect high frequency pulses to 25 MHz. It can be used at MOS levels or circuit ground with result.

\$9.95 Per Kit

printed circuit board

T5L 5V 1A Supply

This is a standard TTL power supply using the well known W309N regulator. It provides a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package including the hardware for only

\$9.95 Per Kit

Smallest and lightest duplex radio for paramedics.

A new Emergency Medical Service (EMS) full duplex/multiplex portable radio now aids the paramedic in lifesaving operations. The new Motorola APCOR is the smallest and lightest of its type now available. Weighing only 13 pounds, it can be carried easily to the scene of almost any emergency.



THE APCOR EMS RADIO in a simulated emergency situation.

Duplex/multiplex operation makes possible simultaneous transmission of ECG (electrocardiogram) and voice information from the patient to the hospital. Other features of the APCOR radio are: two watts of audio power, extended range via vehicular repeaters, a full hour of continuous operation, 1-hour rechargeable bat-

tery, private-line squelch encode/decode capability and reliable plug-in modules.

New patents improve test instrument

Two new patents of interest to electronic service technicians have been granted to engineers of Sencore, Inc., Sioux Falls, SD.

Patent No. 3,990,002, proudly displayed by Robert Baum, Sencore Engineering Director, is on a simplified yoke and flyback tester. With it, a TV technician can check flyback transformer and deflection yokes in-circuit and out-of-circuit by simple ringing counts from full excitation to 25 percent decay. The rings are converted into voltage steps and applied to a simple analog meter, making it possible to design a tester with a GOOD-BAD scale.



SENCORE ENGINEERS Marvin Westra and Robert Baum, with their patents and the devices in which they are embodied.

Patent No. 3,990,008 is used in the Sencore DVM32 digital portable multimeter, to preserve battery life. A circuit installed in the test lead input and excited by a very small fraction of a volt turns on the digital display. Since the display draws 100 milliamperes as against only 10 for the operating circuit, battery life is roughly ten times as long as that of digital multimeters that are not turned off when no testing voltages are applied.

New device eliminates converter on 20-channel CATV systems

Magnavox has announced a new device, an isolation amplifier, that makes a 20-channel converter unnecessary when used with a Magnavox 25-inch varactor-tuned color-TV set. It is designed for Cable TV (CATV) markets that carry more than the normal 12-VHF channels and use the eight midband CATV channels B through I. The converter had been necessary to prevent possible electronic tuner interference to other cable-system users, a possibility the isolation amplifier eliminates.

If users are subscribers to a Home Box Office (HBO) system transmitting a scrambled signal, a converter will still be necessary to unscramble the signal and receive the channels, unless the HBO uses an electronic filtering system.

Isolation amplifier kits (which must be installed by a service technician) for the Magnavox STAR system and the Videomatic Touch-Tune units are available at Magnavox dealers, with a suggested retail price of \$14.95.

R-E

COMPLETE UNIT . . . NOT A KIT!

HARDEN

12 DIGITS
DESK TOP
CALCULATORS
BY ROCKWELL
reg. \$69.50

Special
Only
\$29.50



- * Uses LCD with backup light.
- * 5 functions +, -, x, ÷, %.
- * With accumulating true memories.
- * Full floating decimal points, or fixed.
- * 12 digits, silver color LCD display.
- * Leading zero suppression.
- * Overflow indicator.

Model DT/12 A Uses 110V AC.
Model DT/12 B Uses 220V AC.


Add \$2.50 postage for this item.



TV Games

Direct
Sales Only

\$58⁵⁰

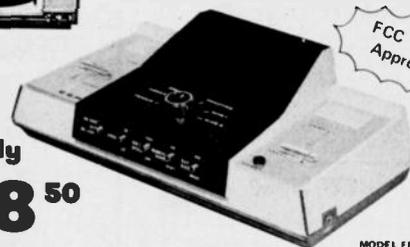

USES 6 C SIZE BATTERIES (Not Included)

JUST SIMPLY HOOK THE OUTPUT LEAD OF THE UNIT TO THE ANTENNA INPUT OF YOUR TV SET AND YOU'RE READY TO PLAY!

FEATURES:

- * 4 Games—Tennis, Hockey, Racquet Handball and Single Handball.
- * Adjustable bat size.
- * Automatic or manual serve.
- * 20° or 40° ball angles.
- * Pair of extension control units optional (3.00 each)
- * Auto counter display on the screen.

- * 3 different beeps:
Ball against bat-high beep
Ball against boundary-low beep
Ball out of play-2 low beeps.

California residents add 6% sales tax.

SEND CHECK OR MONEY ORDER TO



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 679-5162

STORE HOURS 10-7 Monday - Saturday

3/77

For Postage
Add \$2.50 For Each Set

RCA STEREO SALE

MODEL RCA 102

AM-FM MONO TUNER AMP




3 WATT OUTPUT
All Solid State
With Indicator
And Power Supply
ONLY \$12.00 EACH

ADD \$1.00 POSTAGE FOR THIS ITEM

AM-FM STEREO TUNER AMP

MODEL RCA 103

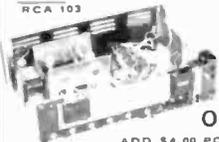


20 WATT PER CHANNEL
2N3055X4
All Solid State
With Dial Indicator
110V AC INPUT
ONLY \$55.00 EACH

ADD \$4.00 POSTAGE FOR THIS ITEM

STEREO AM-FM MUX TUNER AMP

MODEL RCA 104

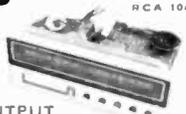WITH BUILT IN 8 TRACK PLAYER
USES HITACHI I.C. POWER AMP
4W PER CHANNEL OUTPUT
All Solid State with a Beautiful Panel.



ONLY \$55.00 EACH
110V AC 50/60 HZ INPUT

ADD \$3.00 POSTAGE TO THIS ITEM

STEREO AM-FM MUX TUNER AMP

MODEL RCA 105

4 WATT PER CHANNEL
All Solid State
With a Vertical Panel
All Brand New with Power Supply
ONLY \$45.00 EACH



110V AC 50/60 HZ INPUT
ADD \$3.00 POSTAGE FOR THIS ITEM

STEREO AM-FM MUX TUNER AMP

MODEL RCA 106

5 Watt Per Channel Output
Uses Sanyo STK011 Hybrid Power Amp and RCA Hybrid Drivers. Two separated dials for AM and FM with slide volume control and signal indicator.
ONLY \$40.00 EACH

110V AC 50/60 HZ INPUT

ADD \$3.00 POSTAGE FOR THIS ITEM

8 TRACK STEREO TAPE PLAYERS

Complete Stereo Players With Built-In Pre-Amp

110V AC 50/60 HZ INPUT
ONLY \$7.50 EACH

ADD \$1.50 POSTAGE FOR THIS ITEM

RCA 12 WATT PER CHANNEL FM-AM MUX TUNER AMP

All brand new but no case.
Special Price \$35.00 each

ADD \$4.00 POSTAGE FOR THIS ITEM

COMPUTER GRADE CAPACITOR



5600 MFD 60V \$2.20
6000 MFD 75V \$3.50
10000 MFD 50V \$3.50
15500 MFD 75V \$4.95
39000 MFD 12V \$1.50

COMPLETE ALARM CLOCK

* 4 Digits 0.5" LED with brightness control
* 12 Hour display with AM/PM Indication
* True 24 hour alarm with repeatable snooze
* Power failure indication for power interrupt



MODEL EC 400

(Not A Kit)

Only \$22.50

ON SALE \$17.50 ea.

CLOCK KIT




MOST POPULAR MM5314 KIT

WITH A NEW CASE!!
Features: 12/24 Hour Display
50/60 HZ Input 6 Digits Readout
Kit Includes: Grey Color Plastic Case
MM5314 Clock Chip PC Boards and Trans-
former, 6 Green Color 0.3" Tube Readouts.
All other transistor Drivers and other Com-
ponents.

Special Only \$19.95 ea.

SW AUDIO AMP KIT

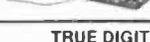USE 2 LM380
with Volume Control
POWER SUPPLY 6VDC
only \$5.00 ea.



TRUE DIGITAL CASSETTE RECORDER

For Computer Control of Both Start/Ready/Start Write operation. Speed Tolerant Recording less than 1 soft error in 10⁸. Built in interface. 8 Bit parallel from input/output. Direct compatible with 3 P+S board. Read and write speed 125 bytes/sec. using standard Phillips cassette. Made by Electronic Processors. New surplus with manual.



LIMITED STOCK \$79.50

Mating connectors available at \$4.60 ea.



12 VDC Relay
SPDT 4 amp
\$1.25 ea.

MINI SIZE
12V RELAY
DTDT 500
\$1.40 ea.



NI-CD RECHARGEABLE BATTERIES

AA SIZE 1.2V \$1.25 each
C SIZE 1.2V \$1.50 each
F SIZE 1.2V \$2.50 each



ALL GUARANTEED GOOD

AUTO ALARM KIT



The Crimelighter Auto Alarm is an electronic, self controlled auto protection system, normally mounted within the glove box of an automobile.

Two minutes after turning off the ignition, the alarm automatically turns itself "on". When the auto is re-ignited, the horn will sound after a 10-45 second entry delay. The automobile owner, by inserting the ignition key, will activate the alarm. Once activated, the alarm will sound for two minutes before automatically turning off. The alarm then resets and is ready to again protect the vehicle from unwanted entry.

FEATURES Simple installation 5 wires. Automatically turns on when auto is parked. Adjustable entry time. Extended exit time to allow for uncrushed exit from vehicle. Numerous applications include protection of boats, campers, trailers, motorcycles, trucks. Cannot be deactivated by "hot wiring" an auto. Cannot be turned off without ignition key. Negative ground only.

ONLY \$10.00 per kit Completed Unit \$16.00

SPECIAL THIS MONTH

CPU	8080A	\$19.50
UART	TR1402A	\$ 7.50
PROMS	1702A	\$ 8.95
ROM'S	2513	\$ 9.00
RAM'S	1103	\$ 1.00
RAM'S	21L02-1	\$ 1.90

19 KEY ALPHANUMERIC KEYBOARD


STANDARD SIZE
KEY TOPS
WITH
UNENCODED
SPST KEYS
ONLY \$9.95 EACH

QUARTZ CRYSTALS

1MHz Computer Crystals \$4.25 ea.
3.58 MHz Color TV Crystals \$1.25 ea.
Use with Natick MM 5369 to make a perfect time base for clock.

150UA METER

only
\$1.50 ea.

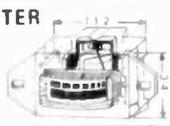

QUAD VOLUME CONTROL

4 100K Volume pot in one unit. Very resistance proportional to the angle of the stick. Perfect for electronic games or model remote control.
only \$5.50
Knob for Joystick 50¢ ea.



ELECTRONIC SWITCH KIT

CONDENSER TYPE



Touch on Touch Off
use 7473 I.C.
and 12V relay
\$5.50 each

FM WIRELESS MIC KIT



Transmit range up to 500 ft.
Easy to assemble
\$4.50 each

Sub-Mini Size
Condenser Microphone
\$2.50 each




ASCII KEYBOARD ENCODER CHIP

G1 AY-53600
40 pin DIP package, 4 level, 10 BITS per level, encoding for up to 90 keys. Latched data outputs and control signal output, TTL compatibility for all controls.
WITH DATA ONLY \$15.00 EACH

COMPUTER KEYBOARDS



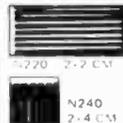Standard Teletype Keyboards with gold plated contact switches. All switches are independent and allow you to connect into any form of output.
63 Keys - 19.50
60 Keys - 14.50



SOLAR CELL

Large Size \$3.00 each (85MM, 200MA, 420MV)
Small Size \$1.50 Each (143MM, 100MA, 430MV)

SAE DIP SWITCHES

Part No 1004 692 4XSPST SW
1008 692 8XSPST SW

4 Toggle SPST Switches on a Mini-DIP 18 pins Only \$1.50 ea
8 Toggle SPST Switches on a DIP 16 pins Only \$2.60 ea

SUBMINIATURES TOGGLE SWITCHES

SPDT On/Off \$1.30 ea.
DPDT On/Off \$1.50 ea.
3PDT On/Off \$1.75 ea.
Mini Size Rocker Type Also Available at the Same Price

EECO BCD THUMBWHEEL SWITCHES

8 positions \$1.25 ea.
10 positions \$2.15 ea.
12 positions \$2.50 ea.

PUSH-BUTTON SWITCH

RED COLOR N/OPEN 4/5.00
BLACK COLOR N/CLOSE 2/5.00
LARGE QTY. AVAILABLE

SOLIO STATE ELECTRONIC BUZZER

Mini Size 1/4" x 3/4" Supply voltage 1.5V 12V
Ideal for Alarm or Tone Indicator
\$1.50 each or 2/\$2.50

MINIMUM ORDER \$10.00. California residents add 6% sales tax. All orders add 10% postage for out of state. Overseas countries add 15% of total order for postage. SEND CHECK OR MONEY ORDER TO:



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 679-5162

STORE HOURS 10-7 Monday - Saturday



**AMAZING & HARD-TO-FIND
SCIENCE BUYS!
ALTERNATE ENERGY
SPACE AGE · HOBBIES**

SUPER POWER FOR ANY AM RADIO

Antenna assist has pulled in stations up to 1000 miles* off! No wires, clips, grounding. Solid state—no elec., batts., tubes. No. 72,095EH \$19.95 Ppd. **ULTRA SELECT-A-TENNA (OVER 1000* MILES)** No. 72,147EH.....\$24.95 SUBJ. TO LOCAL COND.



SAVE 50%! 8 x 20 MONOCULAR

Top quality Spy Scope, a \$30 value, now \$14.95! Special purchase saves you 50%. 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove box. No. 1568EH.. \$14.95 Ppd.



SEE MUSIC IN PULSATING COLOR

3-Channel Color Organ lets you modulate 3 independent strings of colored lamps w/ intensity of your music "Audio" light show flashes, responds to rhythm, pitch!



No. 42,309EH (ASSEMBLED).....\$18.50 Ppd.
No. 42,336EH (UNASSEMBLED).....\$15.95 Ppd.

NASA-CHOSEN FOR APOLLO/SOYUZ

The Astronauts used this super 20X60 binocular (modified) to view Earth! Big 60 mm objective lenses; 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics, more!



No. 1556EH(9 1/2 x 8 1/2"; 47.5 oz) \$99.95 Ppd.

110V FUEL MISER RECLAIMS HEAT

Save your 40% wasted heat to warm a basement, garage, rec rm. at no extra cost! Direct it your way instead of up the chimney! Fan-forced clean hot air via easy ducting!



No. 19,194EH (5" DIA.) Shpg. 17 lb...\$121.50 FOB
No. 19,195EH (6" DIA.);

KNOW YOUR ALPHA FROM THETA!

For greater relaxation & concentration, monitor your Alpha/Theta brainwaves w/aud. or vis sig. on Biosone II. Feats. of \$200-up units incl 3 feedback modes! 4-lb



No. 1668EH (9 1/2 x 5 1/4 x 4 1/4").....\$149.95 Ppd.
No. 71,809EH (FOR BEGINNERS).....\$59.95 Ppd.

PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18 1/4" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100X over omnidirection mikes. Catch sounds never bef. heard; highest signal to noise ratio poss. 5 1/2 lb.



No. 1649EH (REQ. 29V BATT.).....\$299.00 Ppd.

AN ULTRA-MINIATURE AM RADIO!

About the size of a small matchbox. Amazing volume & clarity (depends on locale). Insert earplug (incl) & directional AM mini marvel plays! Runs ab. 100 hrs. on 2 hear. aid batts (incl). (LESS THAN 1 1/4 OZ.!) No. 1976EH ..\$14.95 Ppd.



CAN'T SLEEP, RELAX? TRY THIS!

Electronic sound conditioner simulates 4 kinds of soothing sounds of ocean surf & rain; "white" sound helps mask unwanted noise. Medical tests proved analgesic effects! No. 71,997EH \$89.95 Ppd.



QUALITY DETECTOR UNDER \$40

Our fully transistorized BFD unit can locate a quarter at 18". Powerful 6 trans-oscillator-amplifier circuit. Comp. to others priced 50% more! Aluminum, just 2 lb. No. 80,222EH \$39.95 Ppd.



**THERE IS NO OTHER TELESCOPE LIKE IT!
THE NEW EDMUND 4 1/4", f/4
NEWTONIAN WIDE FIELD
REFLECTOR TELESCOPE**

Clear, bright, spectacular wide angle views of stars, moon, comets... easy to use... portable!

IN SECONDS YOU'RE SCANNING THE ASTOUNDING UNIVERSE, able to see and study the breath-taking cosmos as perhaps you never have before! awesome vastness, unbelievable orderliness, stark silent beauty! All the fascinating heavenly mysteries are yours to enter and explore! This new reflector telescope makes it easy for everyone to span a thousand light-years to space-age enjoyment of the heavens and outdoors. No complicated set-up! Just insert the eyepiece focus, and its big 3 1/2" field of view gives you more stars in a single view than any other type of telescope. Bright, crisp, finely resolved images to capture your interest and imagination! It's probably the easiest to use telescope ever—over your shoulder, in your lap, on a tripod. Or just rotate the spherical base on its own mount for use on a table, car hood. Take it anywhere (only 17" x 10 lb.) Top quality optical system: 4 1/4", f/4 parabolic primary mirror (1/4 wave, 17" F.L.), pre-ignited 1/4 wave diagonal on a coated optical window seals optics from moisture and dust. 28mm Kellner eyepiece (gives 15X higher without other eyepiece or Barlow). Fast focusing (25' to infinity). Bright Scharfianian red (doesn't impair night vision) adj. carrying strap. A first scope must be an ideal second scope!

There is no other telescope like it. NO. 2001EH \$149.95 Ppd.

**FOR GREATER RELAXATION, CONCENTRATION,
listen to your Alpha and Theta brainwaves!**



No. 1689EH

Do-It-Yourself Kit #61069EH.....\$37.50 ppd.
Low Cost 'Starter' Unit #71809EH.....\$59.95 ppd.

Do it with an amazing biofeedback monitor. This ultra-sensitive sensor detects brain signals, lets you monitor (hear and see!) your Alpha and Theta brainwaves. Great aid to relaxation, concentration. This portable (8 x 3 x 4") lightweight (24 oz.) metal unit has a unique electrode headband to slip on or off in seconds without messy creams or solutions. Hooked to amplifier, it filters brainwaves, and signals an audible beep for each Alpha or Theta wave passed. You get both audio and visual (L.E.D.) feedback with this reliable, completely safe unit. It operates on two 9v transistor batteries, offers features comparable to many costlier models. A comprehensive instruction booklet is included.

No. 1689EH JUST \$99 Ppd.

**LOW COST, HIGH QUALITY
INFRA-RED EYE**

Binocular Style, \$329.95; Standard, Only \$299.95



A must for Infra-red crime detection surveillance, security system alignment, I.R. detection, laser checking, night-time wildlife study—any work requiring I.R. detection and conversion to the visible spectrum. Self-contained scope (11 x 14 1/4 x 3") includes I.R. light source (for up to 90° sight at night!), 6032 I.R. converter tube, 1/3.5 telephoto lens, adjustable triplet eyepiece, an adapter for use with your car's cigarette lighter—more! Bright 1.6X image (Binocular style gives super-bright 2.5X). Focuses from 10' to infinity, runs on 6 or 12v DC.

Not for sale to Cal. residents other than authorized by U.S. Armed Forces, law enforcement agencies or solely for scientific research and education purposes.

STANDARD STYLE, STOCK NO. 1683EH ONLY \$299.95 Ppd.
BINOCULAR STYLE, STOCK NO. 1685EH JUST \$329.95 Ppd.



**GIANT FREE
164 PG. CATALOG**



4500 UNUSUAL BARGAINS
FOR HOBBYISTS,
SCHOOLS, INDUSTRY

COMPLETE AND MAIL COUPON NOW

EDMUND SCIENTIFIC CO. 300 Edscorp Bldg., Barrington, N. J. 08007

Send me the following:

Stock No. Quantity Price Ea.

SEND FREE 164 PG CATALOG "EH"
Charge my American Exp
 BankAmericard Master Cng

Interbank No. _____

Card No. _____

Expiration Date _____

30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund.

Signature _____

Address _____

City, State, Zip _____

Stock No.	Quantity	Price Ea.

Add handling charge \$ _____ 1.00

Enclosed is _____ check,

_____ M.O. in amount of \$ _____

EDMUND SCIENTIFIC CO.

300 Edscorp Bldg., Barrington, N.J. 08007 • (609) 547-3488
America's Greatest Science • Optics • Hobby Center

CIRCLE 18 ON FREE INFORMATION CARD

Shakespeare's White Knight. The best antenna going. And coming.

Shakespeare comes on strong for the new 40 channel era. With high performance CB antennas that turn on the power on all 23 or 40 channel CB transceivers.

Shakespeare's new White Knight Antenna combines the rugged, mechanical strength of gleaming white fiberglass with precision engineered electronic components. Components like the high quality loading coil permanently fused in a solid polycarbonate thermoplastic base. Totally impervious to the environment. And pre-tuned to an SWR of 1.9 to 1 or less over the 40 channel band (1.3 to 1 or less at the center). To assure maximum range and peak performance everytime you key the mike. That's what sets the White Knight antenna apart from all the others.

Ride full tilt into the 40 channel era with the new White Knight CB Antenna. And take the Shakespeare performance route home.

The White Knight Antenna, Style 4125/available in a variety of pre-assembled mounting styles. Complete with cables and connectors. Under \$25.

Shakespeare

Coming on strong for the Knights of the Road.

Shakespeare Company/Antenna Group, P.O. Box 246, Columbia, S.C. 29202
In Canada: Len Finkler Ltd., Ontario.

CIRCLE 33 ON FREE INFORMATION CARD

The 40-channel Cobra 29XLR. From the sleek brushed chrome face to the matte black housing, it's a beauty. But its beauty is more than skin deep. Because inside, this CB has the guts to pack a powerful punch.

The illuminated 3-in-1 meter tells you exactly how much power you're pushing out. And pulling in. It also measures the system's efficiency with an SWR check. In short, this Cobra's meter lets you keep an eye on your ears.

The Digital Channel Selector shows you the channel you're on in large LED numerals that can be read clearly in any light. There's also switchable noise blanking to reject short-pulse noise other systems can't block. The built-in power of DynaMike Plus. Automatic noise limiting

and Delta Tuning for clearer reception.

And the added protection of Cobra's nationwide network of Authorized Service Centers with factory-trained technicians to help you with installation, service and advice.

The Cobra 29XLR. It has 40 channels. And it has what it takes to improve communications by punching through loud and clear on every one of them. That's the beauty of it.



Punches through loud and clear.

Cobra Communications Products
DYNASCAN CORPORATION
6460 W. Cortland St., Chicago, Illinois 60635

Write for color brochure
EXPORTERS: Empire • Plainview, N.Y. • CANADA: Atlas Electronics • Toronto

PUNCH AND BEAUTY



CIRCLE 9 ON FREE INFORMATION CARD