

48783

**SPECIAL  
TEAR OUT SECTION  
COMPUTER DIGEST**

# Radio - HOW TO STOP STATIC ELECTRICITY


# Electronics

\$1.75 AUGUST 1984

COMPUTERS - VIDEO - STEREO - TECHNOLOGY - SERVICE
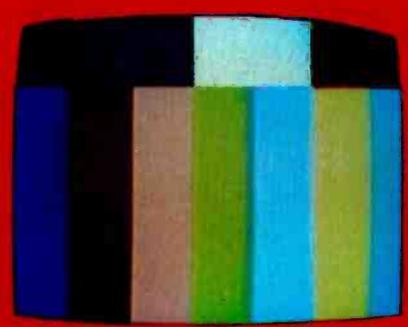
## BUILD THIS NOVEL COLOR-BAR GENERATOR.



A simple plug-in ROM cartridge for your Atari 2600 videogame produces all the test patterns of a conventional color-bar generator



## ELECTRONICS AND YOUR
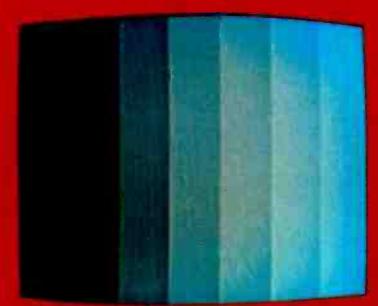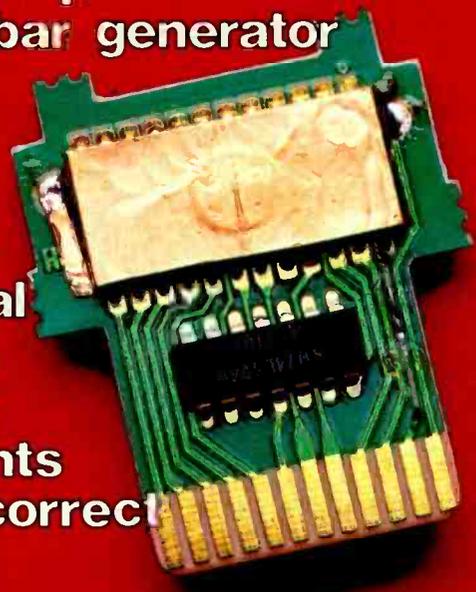
## HEART.

Here's a look at the electrical impulses that drive your heart and the electronic instruments that measure and correct those impulses



## BUILD AN INFRA-RED TRANSMITTER AND RECEIVER.

An infra-red based remote-control system

## DO SOMETHING NEW WITH YOUR TIMEX 1000!

How to use the Timex 1000 as a control computer around the house

Attention retailers:  
See page 112 for special display allowance plan.

★ CMOS Analog Switches

★ Designing With Linear IC's ★ New Idea

★ Of-Solid-State ★ Hobby Corner

★ Service Clinic ★ Drawing Board

\*\*\*\*\*S-DIGIT 13760  
585280 0V0 03265092 14 A SEP84  
08\*EP  
JOSEPH L OZVOLD  
326 STEIN DR  
ENGLICOTT  
NY 13760

# Now! Get a best-seller from the best name in scopes!

**100 MHz dual time base scope.** Easy-to-read CRT; bright, full-sized 8x10 cm; 14 kv accelerating potential complete with BEAM FIND, separate A/B dual intensity controls, FOCUS and TRACE ROTATION.

**Wide range vertical sensitivity.** Choose from 2 mV/div (1x probe) to 50 V/div (10x probe); color-keyed for 1x and 10x probes; variable control increases scale factor by 2.5 to 1.

**Two 100 MHz, high sensitivity channels.** 3.5 ns risetime; dc to  $\geq$  100 MHz bandwidth from 5 V/div to 5 mV/div; extended sensitivity of 2 mV/div at  $\geq$  90 MHz.

**A/B sweep selection.** Calibrated A sweeps from 50 ns/div to 0.5 s/div; B sweeps from 50 ns/div to 50 ms/div; variable control for up to 2.5 to 1 reduction and 10x magnification for sweeps to 5 ns/div.

**Dual time base measurements.** Select either A or B sweeps, or both alternately with A intensified by B.

**B trigger slope and level.** Use B trigger level to select B-triggered or run-after-delay modes; use B TRIGGER SLOPE to select transitions.



1-800-426-2200

## Your order is toll-free!

With its 2200 scope line, Tek tops them all in quality, performance and popular appeal! The 60 MHz single time base delay 2213A, the 60 MHz dual time base 2215A and the 100 MHz dual time base 2235 offer unprecedented reliability and affordability, plus the industry's first 3-year warranty\* on labor and parts. CRT included.

The cost: just \$1200 for the 2213A, \$1450 for the 2215A, \$1650 for the 2235.† Even at these low prices, there's no

scrumping on performance. You have the bandwidth for digital and analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. Delayed sweep, too. All scopes are UL Listed and CSA approved.

You can order, or obtain literature, through the Tek National Marketing Center. Technical personnel, expert in scope applications, will answer your questions and expedite delivery.

Direct orders include operator's manual, two 10X probes, 15-day return policy and worldwide service backup.

**Order toll free:  
1-800-426-2200,  
Ask for Kay.**

In Oregon, call collect: (503) 627-9000.  
Or write Tektronix, Inc.  
P.O. Box 1700  
Beaverton, OR 97075

**Tektronix**  
COMMITTED TO EXCELLENCE


# Probably the second most important book you can turn to for guidance.

Electronics dealers and repair experts know they can depend on Philips ECG® Replacement Semis to fit and to work—reliably.

And they know they can depend on the new ECG Semiconductor Master Replacement Guide to save them time, money and aggravation when ordering the parts they need.

545 pages. 3,100 ECG Semiconductor types. More than 700 new products including transient voltage suppressors, micro-processor ICs, thermal cutoffs, solid state relays and more.

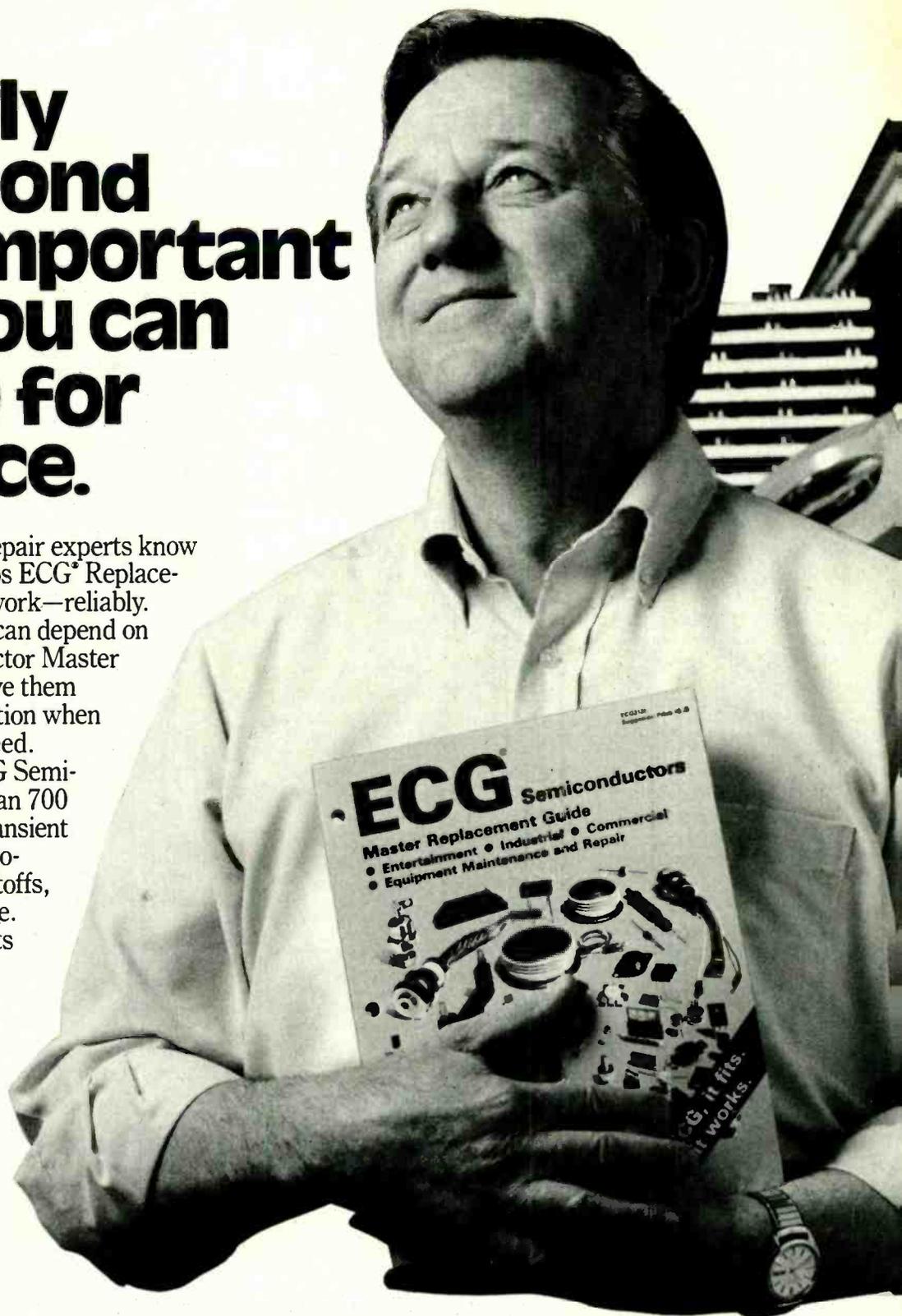It's the only book of its kind you'll ever need this year, and you can get it from your nearest ECG distributor. Just call **1-800-225-8326** toll-free for his name and phone number (in Massachusetts, call 1-617-890-6107).



## If it's ECG, it fits. And it works.

# Philips ECG

A North American Philips Company

CIRCLE 47 ON FREE INFORMATION CARD

# Because they are built to last...

## Global breadboarding sockets are guaranteed for a lifetime.

For more than a decade, Global Specialties' solderless breadboarding has set the standard for quality, durability and dependable performance. Now, we offer a lifetime guarantee. If a Global breadboarding socket fails to perform according to your needs, you merely return it to Global Specialties. We will send you a replacement free of charge. *No questions asked.*


This unconditional guarantee is offered because our breadboarding sockets provide outstanding performance, indefinitely. All of our sockets are made in the United States in our own factory, employing the latest equipment, manufacturing methods and quality control procedures. Each socket and bus strip is molded of high quality plastic material to provide superior strength and durability. Precision-formed contacts and tie-points made from nickel-silver assure excellent contact every time.

Seven sockets and three bus strips are included in our QT Series. Our new UBS-100 and UBS-500 models and our Experimentor line include socket and bus strip contact arrangements in single modular breadboards.


The industry's largest selection, unmatched quality and economy have earned Global solderless breadboarding sockets the reputation for being number one with professionals, hobbyists and students. Now, the unconditional lifetime guarantee is your assurance that when you buy from Global you receive maximum durability and trouble-free performance. Unlike some manufacturers who require that you purchase by mail, our nationwide network of distributors permits you to see and inspect our products before you buy.

See your electronics distributor or for the name of your local distributor, call our toll-free "Where To Buy" number: 1-800-243-6077.

### Introducing the UBS Series

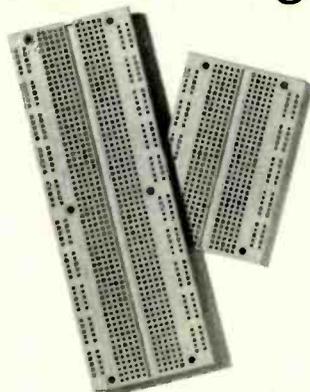

*Two new solderless breadboarding sockets have been added to the Global line. The new UBS-100 is now the largest socket in the line, with 840 tie-points and the smaller UBS-500 has 430 tie-points. Each includes two rows of bus strips on each side for power and ground connections and the UBS sockets are made of the highest grade plastic material to insure maximum resistance to warping and breaking.*

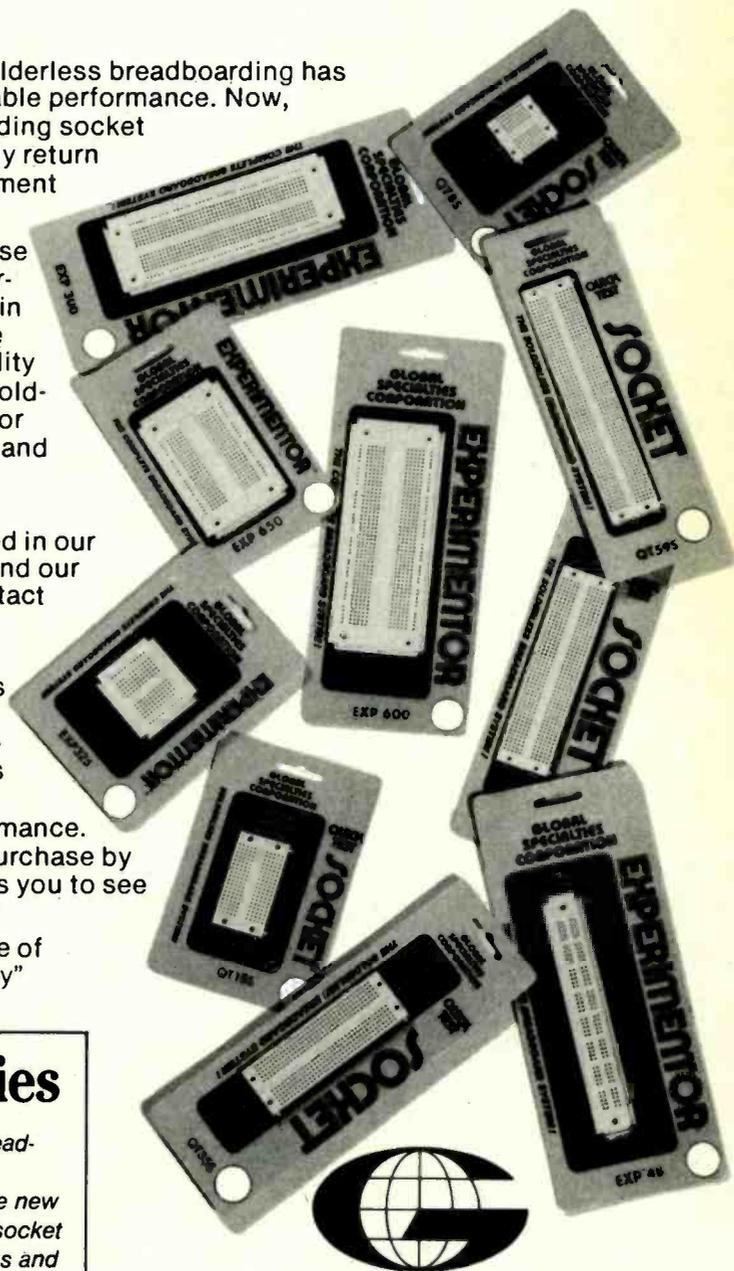

**GLOBAL SPECIALTIES**  
An Interplex Electronics Company

70 Fulton Terrace  
New Haven, CT 06512-1819  
(203) 624-3103 TWX: 710-465-1227

OTHER OFFICES: San Francisco (415) 648-0611,  
TWX: 910-372-7992; Europe: phone Saffron-Walden  
0799-21682, TLX: 817477; Canada: Len Finkler  
Limited, Downsview, Ontario.

CIRCLE 33 ON FREE INFORMATION CARD

<b>SPECIAL FEATURE</b>	73	<b>HUGO GERNSBACK: A MAN WITH VISION +</b> On the 100th anniversary of his birth, <i>Radio-Electronics</i> looks back at the life of its founder. <b>Robert A. W. Lowndes</b>
<b>BUILD THIS</b>	41	<b>COLOR-BAR GENERATOR</b> Turn your Atari 2600 into a color-bar generator with this novel cartridge. <b>Jerry Lawson and Dan McElroy</b>
	57	<b>INFRARED TRANSMITTER AND RECEIVER</b> This easy-to-build project lets you add remote control to just about anything. <b>Steven M. Margolin</b>
<b>TECHNOLOGY</b>	4	<b>VIDEO ELECTRONICS</b> Tomorrow's news and technology In this quickly changing industry. <b>David Lachenbruch</b>
	44	<b>CURING STATIC ELECTRICITY</b> All about static electricity, and the ways that that dangerous phenomenon can be controlled. <b>Elliot S. Kanter</b>
	49	<b>ELECTRONICS AND YOUR HEART</b> Learn about the heart, and the role electronics plays in that wonder of biology. <b>Ray Fish, Ph.D., M.D.</b>
<b>CIRCUITS AND COMPONENTS</b>	14	<b>DESIGNER'S NOTEBOOK</b> One gate circuits. <b>Robert Grossblatt</b>
	20	<b>NEW IDEAS</b> An award-winning project from one of our readers.
	33	<b>DRAWING BOARD</b> Finishing up the sinewave generator. <b>Robert Grossblatt</b>
	66	<b>DESIGNING WITH LINEAR IC'S</b> Part 4. Differential and instrumentation amplifiers, and how to use them. <b>Joseph J. Carr</b>
	69	<b>CMOS ANALOG SWITCHES</b> These IC's offer an elegant solution to what used to be a very complicated problem. <b>Robert Grossblatt</b>
	76	<b>HOBBY CORNER</b> Some pointers on component specifications. <b>Earl "Doc" Savage, K4SDS</b>
	84	<b>STATE OF SOLID STATE</b> A power-supply monitor. <b>Robert F. Scott</b>
<b>VIDEO</b>	86	<b>SERVICE CLINIC</b> Fixing the tough ones. <b>Jack Darr</b>
	86	<b>SERVICE QUESTIONS</b> Radio-Electronics' Service Editor solves technicians' problems.
<b>RADIO</b>	82	<b>COMMUNICATIONS CORNER</b> A new era In personal communications. <b>Herb Friedman</b>
<b>COMPUTERS</b>	53	<b>INTERFACING THE ZX-81</b> Part 2. This month we look at the software needed to control the interface. <b>Neal Bungard</b>
	80	<b>COMPUTER CORNER</b> A look at the MTX512. <b>Lou Frenzel</b>
	80	<b>COMPUTER DIGEST</b> A look at IBM compatibility, diagnostic software for disk drives, and lots more!
<b>EQUIPMENT REPORTS</b>	21	<b>Iwatsu SS-5702 Dual-Trace Oscilloscope</b>
	30	<b>Regency Model Z30 Programmable Scanner</b>
	32	<b>B&amp;K Model 1851 Frequency Counter</b>
<b>DEPARTMENTS</b>	12	<b>Advertising and Sales Offices</b>
	112	<b>Advertising Index</b>
	113	<b>Free Information Card</b>
	15	<b>Letters</b>
	90	<b>Market Center</b>
	37	<b>New Products</b>
	6	<b>What's News</b>

## ON THE COVER

A color-bar generator is one of those pieces of equipment that is needed only occasionally. But when that device is needed, nothing else will do in its place. That is, until now. This month we present an inexpensive alternative—a plug-in cartridge for your Atari 2600 that generates color bars and other patterns required for proper color-TV alignment. To learn more about it, turn to page 41.



**INFRARED COMMUNICATIONS** is used these days in a wide variety of a remote-control applications. This month we'll show you how you can add remote control to just about anything by building an infrared transmitter/receiver pair. The story starts on page 57.

## COMING NEXT MONTH On Sale August 21

- **Sonic Motion Detector.** It uses sound to detect motion. Great for use with a burglar alarm.
- **Electronics Measurements in Medicine.** A look at the electronic instruments used to monitor our health.
- **What's New in Batteries.** A look at the current state-of-the-art.
- **And lots more!**

*Radio-Electronics*, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$14.97. Canada, \$17.97. Other countries, \$22.47 (cash orders only, payable in U.S.A. currency). Single copies \$1.75. © 1984 by Gernsback Publications, Inc. Your Own Computer, Your Own Software, Computer Digest, and Receiving Satellite Television are registered trademarks. All rights reserved. Printed in U.S.A.

**POSTMASTER:** Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

# VIDEO ELECTRONICS

DAVID LACHENBRUCH  
CONTRIBUTING EDITOR



## STEREO TV

Sets designed for the new Multichannel Television Sound (MTS) are beginning to arrive, well in advance of any substantial amount of MTS broadcasting. The new audio system, called BTSC (after the EIA's Broadcast Television System Committee, which selected the standards), permits broadcasting in stereophonic sound, as well as on a Separate Audio Program (SAP) channel. The mono SAP channel may be broadcast at the same time that stereo is being transmitted on the main channel. One of the first uses for the SAP channel may be to supply sound in a second language.

Sound was an important feature in the 1985-model TV set introductions. RCA introduced 18 TV sets—fifteen 25-inch models and three projection sets—with stereo-sound systems and built-in multichannel tuning, capable of receiving stereo sound or the separate channel. They are relatively high-priced sets, starting at more than \$1000. RCA says multichannel sound tuning adds \$50 to \$75 to the price of the set. Zenith chose a different approach. Although it introduced only two sets with built-in MTS, 20 of its new models—all of its sets with stereo amplifiers—are consumer adaptable with the addition of a special converter (see photo). The converter contains a 2-watt-per-channel stereo amplifier and can utilize the TV set's speakers, external speakers, or an external audio amplifier. The converter is controlled by the TV set's remote control. When stereo and/or a SAP soundtrack is being transmitted, the audio system in the converter takes over for the set's amplifier. Zenith's converter-amplifier carries a suggested list price of \$179.95.

General Electric also has a converter, or adaptor, which is easily attached to the back of eight TV models in both its 1984 and 1985 lines. Those sets have much of the stereo circuitry built in, along with the needed pilot lights to show when a stereo or SAP program is being transmitted. GE's adaptor will sell for less than \$100. Panasonic and Quasar both have introduced a few high-priced MTS models, as well as relatively low-priced 19-inch monophonic sets designed to receive the SAP and the main channel, for bilingual listening. Zenith introduced SAP sets in both 13- and 19-inch sizes. In addition to its consumer-convertible sets, Zenith says more than 3,000,000 of its sets produced since late 1981 may be quickly adapted to multichannel sound by a service technician.

MTS broadcasting may be much slower in coming than MTS sets. TV stations must modify their transmitters and add other special equipment. It's doubtful that there'll be much MTS broadcasting before mid-1985.

## POLAROID GOES VIDEO

Like its competitor Eastman Kodak, Polaroid has announced it will introduce a combination video camera-recorder that uses the new 8mm videocassette later this year. The 8mm cassette is about the size of a standard audio cassette and can record for up to 90 minutes. Polaroid's camcorder will be made for them by Toshiba, while Kodak's will be built by Matsushita (which also will make a similar unit for GE). The Polaroid unit, unlike Kodak's, uses a CCD solid-state pickup in place of a tube, and has an optical viewfinder in place of an electronic one. As a result, Polaroid's camcorder weighs less than four pounds, making it the lightest such combination announced to date. Kodak's model weighs nearly six pounds. Kodak's camcorder is due late this summer, Polaroid's before year's end.

R-E



V-222


# HI-PERFORMANCE PORTABLE OSCILLOSCOPES

ALL FEATURE 6" RECTANGULAR CRT  
Full 2 year parts & labor warranty.

## HITACHI

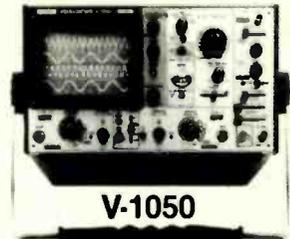**\$599<sup>95</sup>**

V-422  
DC to 40 MHz,  
1mV/div, dual-trace,  
DC offset function



V-1050

**\$1,249<sup>95</sup>**

V-1050F  
100 MHz Quad Trace  
w/delay sweep

**\$499<sup>95</sup>**

V-222  
DC to 20 MHz,  
1mV/div, dual-trace,  
DC off. func., Alt.  
magnify function

**\$439<sup>95</sup>**

V-212  
DC to 20 MHz,  
1mV/div, dual-trace

**\$939<sup>95</sup>**

V-650F  
60 MHz Dual Trace  
w/delay sweep

PRICE DOES NOT INCLUDE  
PROBES. PROBES \$50. A PAIR  
WHEN PURCHASED WITH SCOPE.  
\$15 SHIPPING WITHIN  
CONTINENTAL U.S.



- 77
- 0.3% Accuracy
  - Manual or Autorange
  - 10A + mA Range
  - Beeper
  - "Touch-Hold" Function

**\$129<sup>00</sup>**

WE CARRY A FULL  
LINE OF FLUKE  
MULTI-METERS.  
IN STOCK NOW

- 0.5% Accuracy
- Manual or Autorange
- 10A + 300 mA Range
- Beeper



**\$99<sup>00</sup>**

75

- 0.7% Accuracy
- Autorange Only
- 10 Amp Only

**\$85<sup>00</sup>**

73



# FLUKE 70 SERIES MULTIMETERS

- Analog Display • Rotary Knob • Volts AC & DC
- Resistance to • 32 MΩ • 10 Amps • Diode Test
- 3200 Counts • Fast Autoranging • Function Annunciators in Display • Power-Up Self Test
- 2000+ Hour Battery Life w/ Power Down "Sleep Mode"
- New Test Leads • VDE & UL Approval



TOLL FREE HOT LINE  
**800-223-0474**

212-730-7030

26 WEST 46th STREET, NEW YORK, N.Y. 10036

THE TEST EQUIPMENT SPECIALISTS

# ADVANCE ELECTRONICS

# WHAT'S NEWS

## FCC approves system of verifying commercials

The FCC has approved an application by the Audicom Corp. of New York, NY, for transmitting television and radio commercials so encoded that the identity, source, and time of any such transmission can be known. The decoded information is automatically transmitted to a central computer for immediate and continued access by users of the system. The encoding uses inaudible signals placed in the soundtracks of tapes, film, or other recordings.

The system is expected to provide advertisers with indisputable proof that what they paid for actually ran as ordered. It should eliminate guesswork and time-consuming verification procedures—problems that have long hampered advertisers' and broadcasters' accountability efforts.

Besides advertising, the new system has applications in monitoring the use of copyright

and syndicated materials, and in efforts to combat piracy of tapes or other recordings.

## Automatic test system includes analysis

A new GE software package, known as Test Manager, or TMGR, makes it possible to automate almost completely the testing of many types of heavy industrial equipment.

Automatic test equipment is widely used in the field today. But the usual type simply acquires data, which then must be analyzed and acted on by the technician. TMGR handles the routine tests—it issues orders to call up remotely operated sensors and retrieves, stores, and displays data from them.

But unlike older systems, TMGR performs detailed engineering analyses on the data it receives—while the test is still going on. "A test engineer gets performance results immediately—not after days

or even weeks of calculation from the raw data."

## Multiple-picture TV proposed at conference

A method of viewing several pictures on the same TV screen at the same time was proposed at the 18th annual Society of Motion Pictures and Television Engineers (SMPTE) winter meeting by Joseph S. Nadan, of Philips Laboratories.

That is made possible by a new integrated-circuit development by N.V. Philips of the Netherlands. Called an integrated circuit frame-store charge-coupled-device, it adds memory to the receiver.

The multiple picture-in-picture (MPIP) would allow a viewer to see nine channels at a time on the TV screen. Or he could pull up one station as the "main" program and monitor three others in a strip on the side of the screen. Likewise, he could fill the screen with one picture, leaving only one small box in an upper corner of the screen to monitor another station. By pressing a button, the small screen could become the larger one, and vice versa.

## New AM stereo adapter receives "All-Four"

Kahn Consumer Products, Inc., of Garden City, NY, has made agreements with several AM-stereo broadcasters to purchase and promote a new AM-stereo adapter. The adapter will make any car radio that receives only the Motorola AM-stereo system able to receive AM-stereo broadcasts from all four of the FCC-accepted AM stereo systems.

A Kahn spokesman said that the new product was developed to satisfy consumer demand, as well as to block Motorola's efforts to monopolize the AM-stereo market by capitalizing on Motorola's longstanding relationships in Detroit.

The new adapter is named the "All-Four" to indicate that it will convert single-system Motorola receivers to all-system stereo reception. In quantities of 1,000 it is expected that the "All-Four" can be delivered at a price not exceeding \$6.50.

## US-Israel grants for joint research

The governing board of the US-Israel Binational Industrial Research and Development (BIRD) Foundation has approved funds for eight research projects to be undertaken jointly by private companies from each country, reports the Department of Commerce.

The eight projects, valued at approximately \$8.5 million, include development of improved, high-speed micro-electronic signal processors; an advanced voice-telephone message system; a computerized comprehensive training program for use in electronics laboratories; a comprehensive software application package for industrial organizations; video mapping systems; a polymer heart-valve prosthesis; a diagnostic system for the detection of parasitic diseases, and finally a management software system for the printing industry.


## New products from space research program

A long-range basic research program aimed at making products that cannot be produced on Earth was announced jointly by James Beggs, administrator of the National Aeronautics and Space Administration, and Louis W. Lehr, chairman and chief executive officer of 3M. The first efforts will be directed toward advancing the state of the art in processing organic materials in a low-gravity and high-vacuum environment.

The first actual space experiments, which could occur as early as this month, will investigate the prospects for growing crystals from organic materials that cannot be crystallized on Earth because of gravity, and development of thin films with novel properties.

Answers will be sought in three areas of research, says a 3M spokesman: "The effects of gravity and high vacuum on materials processes we know we can do on Earth; processes we know we can't do, and some 3M proprietary technologies." The results could have applications in a wide range of fields.

*continued on page 12*

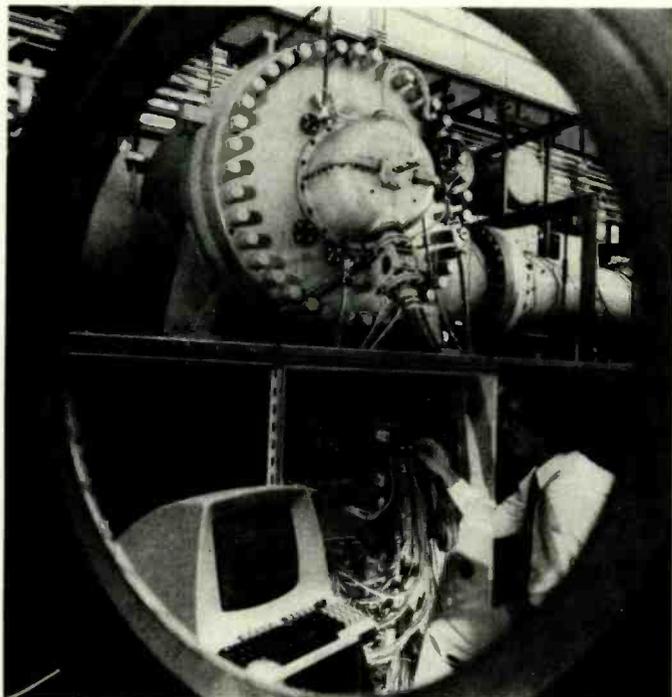

GE SYSTEMS ANALYST Michael Foley prepares a large compressor for performance tests at GE's Fitchburg, MA, Turbine and Compressor Department. The new software program analyzes the data as it is being collected, thus avoiding the days or even weeks of tedious calculations that might otherwise be required.

# The West Coast Alternative!

FRIENDLY SERVICE — KNOWLEDGEABLE AND COURTEOUS SALES PEOPLE



**PROBES INCLUDED!**  
(We Don't Charge Extra for what the Manufacturer Includes FREE!)



**2 YEAR WARRANTY!!**



**HITACHI**  
Hitachi Denshi, Ltd.

**100 MHz QUAD TRACE**  
RHNHY1050F List Price: \$1595.00  
**\$1279**

**60MHz TRIPLE TRACE**  
RHNHY050F List Price: \$1195.00  
**\$985**

**40 MHz DUAL TRACE**  
RHNHY422 List Price: \$885.00  
**\$649**

**20 MHz DUAL TRACE**  
RHNHY222 List Price: \$695.00  
**\$545**

**BK PRECISION** DYNASCAN CORPORATION

**1 YEAR WARRANTY**

**100 MHz 8 TRACE**  
RNBKP1500P List Price: \$1995.00  
**\$1645**

**80MHz QUAD TRACE**  
RNBKP1570P List Price: \$1395.00  
**\$1145**

**60 MHz TRIPLE TRACE**  
RNBKP1500P List Price: \$1150.00  
**\$1045**

**40 MHz DUAL TRACE**  
RNBKP1540P List Price: \$950.00  
**\$795**

**FLUKE** DIGITAL MULTIMETERS  
from **PRIORITY ONE ELECTRONICS**  
**YOUR AUTHORIZED FLUKE INDUSTRIAL DISTRIBUTOR**



**3 YEAR WARRANTY!**

**SERIES 70**  
**Autoranging**  
3 1/2 Digit With Analog Bar Graph

- Full 3200 count instead of the normal 2000
- ULTRA-Fast analog bar graph
- Beeper included in the 75 & 77
- True touch and hold on the 77

RHFLU73 7% accur. **\$85**  
RHFLU75 5% accur. **\$99**  
RHFLU77 3% accur. **\$129**

RHFLUC70 Custom Helister (included w/FLU74) **\$ 9.00**  
RHFLUC71 Soft Vinyl Case **\$ 9.00**

**8060 SERIES**  
4 1/2 Digit .05% DMM


- True RMS • dBm range (8060 only)
- Relative reference and continuity test
- .01 to 200KHz frequency range (8060 only)
- Conductance range • One year warranty!

RHFLU8060A w/Freq and Continuity Test **\$349**  
RHFLU8062A 4 1/2 Digit 05% DMM **\$279**

RHFLUA81 115V AC adaptor/Battery Eliminator **\$ 20.00**  
RHFLUBJ10 10A Current shunt **\$ 30.00**  
RHFLUC00 Vinyl carrying case **\$ 10.00**



**BK PRECISION**

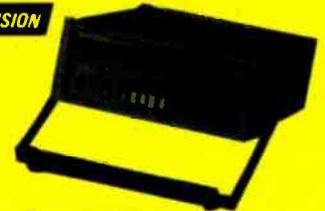

**Signal & Pulse Generators:**

Part Number	Description	List Price	OUR PRICE
RNBKP3010	1 MHz Function Generator	\$229.00	<b>\$189.95</b>
RNBKP3015	200 KHz Sweep/Function Generator	\$281.00	<b>\$225.00</b>
RNBKP3020	2 MHz Sweep/Function with Pulse	\$394.00	<b>\$319.95</b>
RNBKP3025	5 MHz Sweep/Function Generator	\$468.00	<b>\$369.00</b>
RNBKP3030	5 MHz Sweep/Funct. Lin/Log Sweep	\$671.00	<b>\$549.00</b>
RNBKP3300	5 MHz Pulse w/Pulse Burst	\$390.00	<b>\$295.00</b>

**Frequency Counters:**

RNBKP1805	80 MHz Frequency Counter	\$290.00	<b>\$229.00</b>
RNBKP1822	175 MHz Frequency Counter	\$450.00	<b>\$325.00</b>
RNBKP1851	520 MHz Frequency Counter	\$575.00	<b>\$459.00</b>
RNBKP1855	1.2 GHz Frequency Counter	\$750.00	<b>\$599.00</b>

**GSC LP-1 LOGIC PROBE**  
50 nS Response time  
With Pulse and Memory Modes!



**WAS \$50.00**  
**NEW LOW PRICE:**  
**\$19.95**

**PRIORITY ONE ELECTRONICS**

9161 Deering Ave., Chatsworth, CA 91311

Terms (Check, VISA, MasterCard or Money Order). Minimum Order Is \$15.00. CA residents add 6 1/2% sales tax. Prices valid through August 31, 1984. Pre-Paid Orders — Shipping and Insurance (48 States)



\$0 to \$500 \$ 4.50  
\$500 to 1000 \$10.00  
\$1000 and up \$15.00




Credit Card Orders Will Be Charged Appropriate Freight

**ORDER TOLL FREE (800) 423-5922 - CA, AK, HI CALL (818) 709-5111**

CIRCLE 20 ON FREE INFORMATION CARD

www.americanradiohistory.com

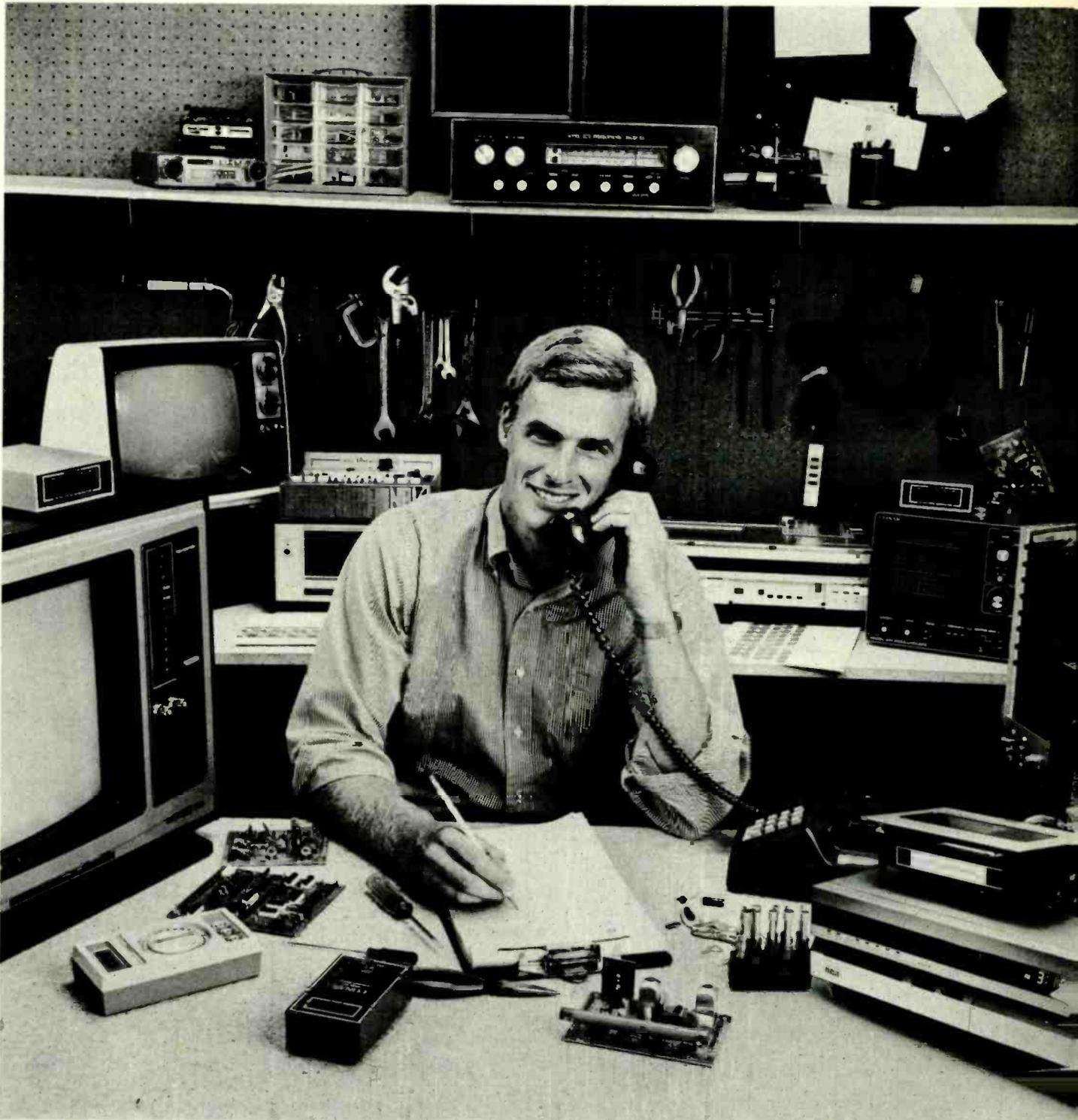**Wouldn't you like to have a  
new skill you could call your own?  
Learn TV, audio, and video servicing  
with at-home training from NRI.**



You can learn to service and repair TVs, stereos, electronic musical instruments and amplifiers, car and portable radios, record and tape decks, videocassette recorders and disc players, almost any kind of electronic equipment on the market. And you can learn to do it at home, in your spare time, without quitting your job or wasting time and gasoline on night school. NRI will train you, as it has over a million and a quarter others, with effective methods proven over 69 successful years.

## Hands-On Training

NRI training is practical training all the way. Throughout your course, you'll perform hands-on experience projects that make theory come to life and give you real understanding.

## Includes Both 25" TV And VCR, Plus DMM And More

As part of your training, you'll build your own 25" Heath/Zenith color TV, a state-of-the-art unit with infrared remote tuning, programmable channel selection, and the incredible space phone for remote calling. You also get a front-loading, remote-controlled videocassette recorder to play your videotaped lessons and learn about servicing this complex instrument.



Practical training on a real state-of-the-art TV, VCR or stereo, using professional equipment

You'll learn troubleshooting techniques using a professional 3½-digit digital multimeter. You'll use it when assembling your TV to check demonstration circuits you build on the NRI Discovery Lab, and in your professional work. It's the equipment and training you need for success.

## Exclusive NRI Training On Videotape

In addition to profusely illustrated lessons, you get NRI Action Videocassettes . . . videotaped lessons that show you graphic presentations of electronic systems, vivid closeups of servicing techniques and professional "shortcuts" to study and replay as often as you want.


## Training For Success

NRI not only prepares you to become a top technician, we get you ready for independence. NRI Video/Audio servicing gives you a great new way to earn

extra money doing part-time servicing for appliance and department stores—building a good-paying, new career with an electronics firm . . . or even starting your own business. You can start small, even part-time in your basement or garage, make the most of your opportunities to grow into a successful businessman.
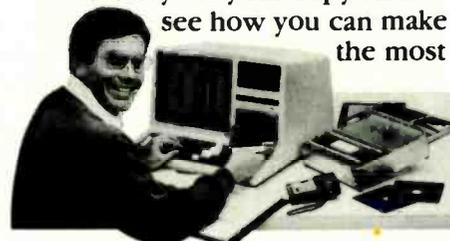
## Free Catalog . . . Mail Card Today


Send the postage-paid card for our free 104-page color catalog describing our courses in full, showing all equipment, lesson outlines, and career opportunities. It also shows other exciting courses like Microcomputers, Electronics Design, Industrial Electronics, Digital Electronics, and more. Mail the postage-paid card today for your copy. And



see how you can make the most of your talent. If card has been removed, please write to:

**NRI**  
McGraw-Hill  
NRI Schools of  
Electronics  
McGraw-Hill Continuing  
Education Center  
3939 Wisconsin Avenue  
Washington, DC 20016

We'll give you tomorrow.

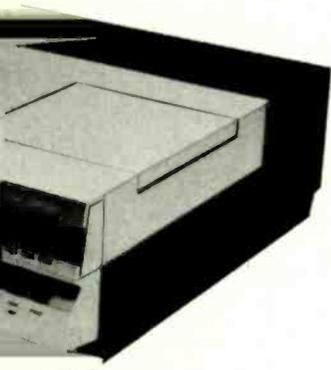

# WHAT'S NEWS

continued from page 6

## Remote-controlled VCR programs a year ahead

RCA has introduced a video cassette recorder that uses a remote-control unit to pre-program as many as eight programs up to a year in advance. The new VKP900's wireless infrared remote control also activates alphanumeric graphic displays on the TV screen to guide the user step-by-step through the programming sequence, with a screened request for each instruction as needed.

To start programming, the user pushes the PROGRAM button on his remote control and a "menu" appears on the TV screen: 1. Clock Set; 2. Normal Program; 3. Daily Program; 4. Weekly Program; 5. Program review.

Button 1 enables the viewer to set the clock and indicate AM or PM, day, month, and year, in response to requests for each piece of information. Button 2 is pressed to record a one-time program. The on-screen graphics ask first for the channel desired, and whether AM or PM, then for the time to start and to stop recording, and finally the date. Buttons 3 and 4 will bring forth the same queries, and the programs listed will then be recorded daily or weekly. The same steps can be repeated for seven more programs.

To review what has been programmed, press button 5, and the screen displays each program in

storage, pausing about ten seconds for each. Pressing the CLEAR button erases the program displayed at the moment.

Other features of the VKP900 include 133-channel capability, a five-head record/playback system with "field still" special effects, express recording (XPR), and stereo recording/playback with high-frequency noise reduction. The unit has a suggested list price of \$1,295.

## New device dissipates charges on spacecraft

Hughes Research Labs is building for the U.S. Air Force a system designed to overcome the problem of electrical buildup on a space vehicle. Called the Flight Model Control System, it uses a self-contained plasma source to dissipate charges on the spacecraft surface to the surrounding space plasma, eliminating destructive arcing from charged surfaces.

The system includes three types of charging sensors, a plasma source, and a microprocessor-based controller.

The sensors are a proton electrostatic analyzer, two side-by-side surface-potential monitors, and a transient pulse monitor. Those, respectively, detect absolute charging (relative to space), differential charging (relative to the spacecraft ground), and pulses generated as arcing begins.

The plasma source establishes a dilute plasma cloud of low-energy electrons and ions near the spacecraft surface. The ions in the plasma transport electrons through space to neutralize charge imbalance, thus preventing high-potential buildups.

The controller interprets the sensor outputs, determines if and when charging is occurring, and controls the discharge device. It will include software that can be altered from the ground in order to permit in-space refinement of the charge detection and neutralization operation.

## World's fastest IC's use gallium arsenide

Two new digital integrated circuits, a universal shift register, and a binary counter, have been introduced by Harris Microwave Semiconductor Co., of Melbourne, FL. Based on gallium arsenide (GaAs) technology, they operate at five times the speed of the fastest silicon-based integrated circuits available today.

The speed and miniaturization characteristics of the two new products are particularly applicable in very-high-speed signal processing, test instrumentation, computing, and telecommunications applications.

## 1,000 charge cycles in carbon-lithium cell

Matsushita Electric of Osaka, Japan, has developed a new 3-volt carbon-lithium battery which assures at least 1,000 charge-discharge cycles. Mass production is scheduled for late 1984.

The new battery uses activated charcoal for its positive electrode and lithium for the negative one. It uses a non-aqueous organic electrolytic solution. A special metal material, coupled with lithium, forms the negative electrode. The new metal absorbs lithium when charging, to form an alloy, and ionizes lithium when discharging.

The new coin-type battery, R2020, is 20-mm in diameter and 2.0-mm thick. Output voltage is 3, in contrast to lead or nickel-cadmium types, whose output has been limited to 2 volts. R-E



THE RCA VKP900 REMOTE-CONTROLLED VCR. The viewer is using her unit to review the programs stored in the memory. The alphanumeric display also assists the viewer in setting the equipment to record one-time daily, or weekly programs.

# Radio-Electronics

A  
GERNSBACK  
PUBLICATION

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, CET, publisher

Arthur Kleiman, editor

Carl Laron, WB2SLR, associate editor

Brian C. Fehton, assistant technical editor

Robert A. Young, assistant editor

Jack Darr, CET, service editor

Robert F. Scott, semiconductor editor

Herb Friedman, communications editor

Earl "Doc" Savage, K4SDS, hobby editor

Gary H. Arlen, contributing editor

David Lachenbruch, contributing editor

Lou Frenzel, contributing editor

Ruby M. Yee, production manager

Robert A. W. Lowndes, production associate

Dianne Osias, production assistant

Karen Tucker, production assistant

Jacqueline Weaver, circulation director

Arline R. Fishman, advertising coordinator

Cover photo by Robert Lewis

Radio-Electronics is Indexed In Applied Science & Technology Index and Readers Guide to Periodical Literature.

Gernsback Publications, Inc.  
200 Park Ave. South  
New York, NY 10003  
Chairman of the Board  
M. Harvey Gernsback  
President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler  
Publisher

### EAST/SOUTHEAST


Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
212-777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
Radio-Electronics  
540 Frontage Road—Suite 325  
Northfield, Illinois 60093  
312-446-1444
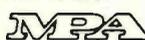
### PACIFIC COAST Mountain States

Marvin Green  
Radio-Electronics  
15335 Morrison St., Suite 227,  
Sherman Oaks, CA 91403  
818-986-2001



# Electronics Paperback Books

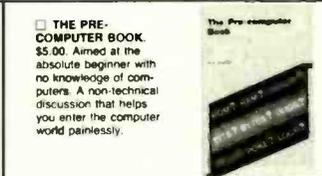
## Quality Paperbacks at Affordable Prices



- 30 SOLDERLESS BREADBOARD PROJECTS BOOK 1.** \$5.75. Whenever possible the same parts are used in several projects. Even a first-time builder can complete these circuits.
- HOW TO GET YOUR ELECTRONIC PROJECTS WORKING.** \$5.00. Helps you troubleshoot and repair home-built projects of every description.
- MINI-MATRIX BOARD PROJECTS.** \$5.00. A variety of projects that can all be built upon a mini-matrix board that has 10 strips and is 24 holes long.
- MODERN OP-AMP PROJECTS.** \$5.00. Wide range of specialized op-amp circuits including low-noise, no-distortion, ultra-hi input impedance, etc.
- MULTI-CIRCUIT BOARD PROJECTS.** \$5.00. 21 fairly simple projects that can all be built on a single printed-circuit board. All are powered by a 9V battery.
- IC PROJECTS FOR BEGINNERS.** \$5.00. Inexpensive digital and linear IC's are used to assemble this selection of circuits intended for the beginner.




- ART OF PROGRAMMING THE 1K ZX81.** \$6.25. Topics include full screen, scrolling, PEEK & POKE, plus actual working programs.
- ART OF PROGRAMMING THE 1K ZX81.** \$5.00. How to use the features of the ZX81 in programs that fit the 1K machine and are still fun to use.
- INTRODUCTION TO BASIC PROGRAMMING TECHNIQUES.** \$5.00. Based on author's own experience in learning BASIC and helping others to learn to program.
- A MICROPROCESSOR PRIMER.** \$4.50. Painless approach to computing for the beginner. Step-by-step explains computer operations and assembly.
- THE 6809 COMPANION.** \$5.00. Written for the average assembly language programmer. A discussion of 6809 features & reference work for the 6809 programmer.
- PRACTICAL COMPUTER EXPERIMENTS.** \$4.50. Fills in background for microprocessor by constructing typical computer circuits using discrete logic components.



**THE PRE-COMPUTER BOOK.** \$5.00. Aimed at the absolute beginner with no knowledge of computers. A non-technical discussion that helps you enter the computer world painlessly.



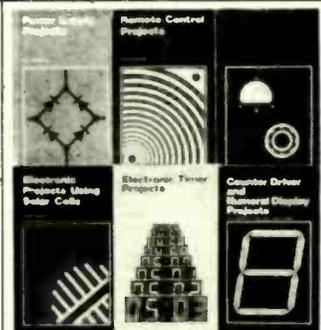
**AN INTRODUCTION TO VIDEO.** \$5.00. Perfect for the person just about to buy a VCR. Discusses pros & cons of the various formats: video discs, videotape, tape copying and more.




- POWER SUPPLY PROJECTS.** \$4.50. Contains designs and construction details for almost any power supply the experimenter is likely to need.
- ELECTRONIC PROJECTS USING SOLAR CELLS.** \$5.00. Simple circuits that have numerous applications around the home.
- REMOTE CONTROL PROJECTS.** \$5.00. Radio-control, infra-red, visible light, & ultrasonic systems are all included, along with methods of applying them.
- ELECTRONIC TEST EQUIPMENT CONSTRUCTION.** \$4.50. Construction details of a wide range of test equipment the experimenter can build at home.
- COUNTER DRIVER & NUMERICAL DISPLAY PROJECTS.** \$4.50. Features applications & projects using various types of numerical-display devices.
- ELECTRONIC HOUSEHOLD PROJECTS.** \$4.50.




- PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1.** \$5.00. All electronics circuits consist of simple building blocks. When you know how to make the blocks you can easily create your own projects.
- HOW TO MAKE WALKIE TALKIES.** \$5.00. Describes equipment for low-power handheld operation. 112 pages of must reading for the dedicated experimenter.
- ELECTRONIC CALCULATOR USERS HANDBOOK.** \$3.95. Presents formulae, data, methods of calculation, conversion factors & more from the view of the calculator user.
- INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE.** \$7.50. Products of more than 100 manufacturers are listed & cross-referenced with possible replacements.
- INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE.** \$7.50. Products of more than 100 manufacturers are listed & cross-referenced with possible replacements.
- LINEAR IC EQUIVALENTS AND PIN CONNECTIONS.** \$8.25. Shows equivalents & pin connections of a popular user-oriented selection of linear IC's.

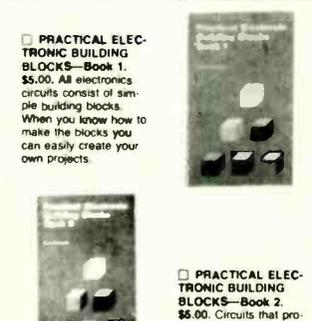

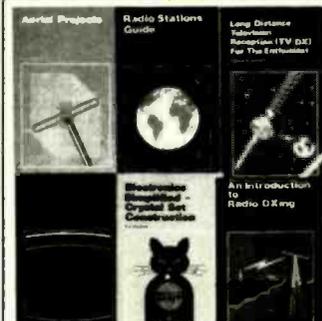- PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 2.** \$5.00. Circuits that process signals. Combines with those in Book 1.
- RADIO CONTROL FOR BEGINNERS.** \$4.50.
- ELECTRONIC MUSIC PROJECTS.** \$4.50.
- HOUSEHOLD PROJECTS.** \$4.50.
- ELECTRONIC MUSIC PROJECTS.** \$4.50.
- POPULAR ELECTRONIC PROJECTS.** \$3.75.
- PROJECTS IN OPTO-ELECTRONICS.** \$5.00.
- RADIO CIRCUITS USING IC'S.** \$4.50.



- ANTENNA PROJECTS.** \$5.00. Covers practical antenna designs including active, loop & ferrite types that are easy & inexpensive to build.
- RADIO STATIONS GUIDE.** \$4.75. Comprehensive listing of transmitters around the world. Presents location, frequency, power.
- LONG DISTANCE TV RECEPTION (TVDX) FOR THE ENTHUSIAST.** \$5.00. Practical & authoritative introduction to this unusual aspect of electronics.
- CB PROJECTS.** \$5.00. A number of useful and interesting designs for CB accessories. Speech processor, interference filter & more.
- CRYSTAL SET CONSTRUCTION.** \$4.50. Packed full of easy to duplicate designs for crystal radio receivers.
- AN INTRODUCTION TO RADIO DXING.** \$5.00. Listen, in your home, to broadcasts originating thousands of miles away. Tells how you can do it.

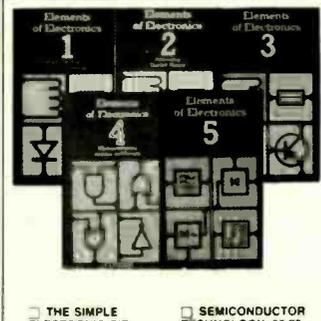

- THE SIMPLE ELECTRONIC CIRCUIT & COMPONENTS.** \$5.75. All the fundamental theory needed to lead to a full understanding of the simple electronic circuit and its components.
- SEMICONDUCTOR TECHNOLOGY.** \$5.75. Everything you always needed to know about solid-state devices in one volume.
- COMMUNICATIONS.** \$7.50. Covers most modern communication systems. Line, microwave, submarine, satellite, digital multiplex, radio & telegraphy.
- FIRST BOOK OF HI-FI SPEAKER ENCLOSURES.** \$4.50.
- SOLID STATE NOVELTY CIRCUITS.** \$3.50.
- 28 TESTED TRANSISTOR PROJECTS.** \$4.25.

**ELECTRONIC TECHNOLOGY TODAY INC.**  
P.O. Box 240, Massapequa Park, NY 11762

RE 8/84

Number of books ordered

Total Price of Books ..... \$ .....

Sales Tax (NY State Residents) .....

Shipping (75¢ 1st two books, 30¢ ea additional) .....

TOTAL ENCLOSED ..... \$ .....

Name .....  
Address .....  
City ..... State ..... ZIP .....

# DESIGNER'S NOTEBOOK

## Single-gate circuits

ROBERT GROSSBLATT

WHENEVER MOST OF US THINK ABOUT CIRCUIT-design shortcuts or tricks to make life easier, it usually involves taking a handful of familiar circuit elements and using them in a way *not* mentioned in the data books. Plenty of brainwork goes into saving time and energy and, of course, component cost. In general, the slicker the trick, the simpler the design and the greater the savings. This month we're going to look at the simplest design you can possibly have—one gate!

For the purpose of this discussion we'll be looking at an exclusive-OR (XOR) gate. You can use the 4070 CMOS version or, if you're into TTL design, you can pick any of the 7486 family. The XOR gate is a really useful device when you're thinking about a one-gate design. But, just how much can you do with a single gate? Well, let's see.

with its out being fed to an LED and resistor in series.

The LED's cathode is tied to ground through the resistor. When the two inputs are equal (both high or both low), the output of the gate is low. On the other hand, when the inputs are out of phase (one high and one low), the gate outputs a high. That forward-biases the LED, thus causing it to light. Now, if we turn LED around and connect its cathode to +V, as shown in Fig. 3, it will light when the inputs are in phase. What could simpler?

Another possibility is shown in Fig. 4. Here we see that if we replace LED 1 with a tri-color LED and tie it to a point halfway up the supply rail, it will be one color when the inputs are in phase and another color when they're not. Let's see why that happens. To understand how the circuit operates, we must first look into the mat-

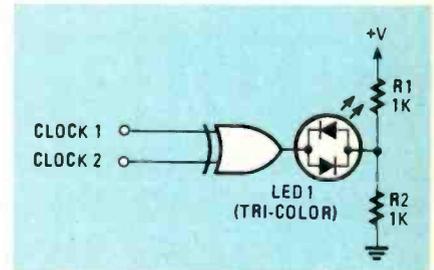


FIG. 4

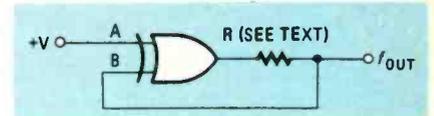


FIG. 5

is *not* as stable as an oscillator built from two inverters. However, if all you need is a clock, try that circuit.


So that you can understand why it works, let's see what is actually going on in that circuit. First, let's assume that the output of the circuit in Fig. 5 is high. Since the B input is tracking the output, it will be high as well. If we apply a high to input A (making both inputs high), the output will go low. That makes input B low, thus driving the output high again, and the whole cycle starts all over.

What you can expect to get from that circuit will depend on the level of voltage (+V) and the resistor value you use. If you're using a CMOS gate you will find that the output swing is less than you would get with a more traditional design. The output will only have an amplitude of about 80% of the supply. The frequency you get will depend on the supply because you have a resistor in line and a certain amount of time has to go by before input B "sees" enough voltage to make the gate change states.

Obviously the value of the resistor is going to come into play as well. Experiment with different values, but make sure you stay above 10,000 ohms or so. If you use a supply of about 7 volts (a 9-volt battery) and the resistor value is around 50,000 ohms, you should be able to get about 5 MHz out of the gate.

The actual frequency is also somewhat dependent on the IC itself. The propagation delay of the gate (the time it takes to

*continued on page 83*

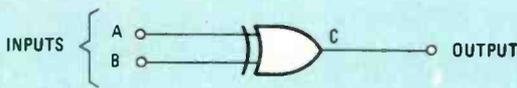

INPUTS		OUTPUT
A	B	C
H	H	L
H	L	H
L	H	H
L	L	L

FIG. 1

ter of how a tri-color LED works.

The tri-color LED can be thought of as two LED's connected anode to cathode in parallel. (It's not quite that simple, but, for discussion's sake, we'll use that illustration.) Anyway, when the voltage is negative, one LED will be forward-biased and will therefore light (let's say red). But, when the voltage is positive (or reversed) the other LED will light—this time green. The third color (yellow) lights when an AC voltage is applied, but we won't get into that this time. Now, let's get back to our circuit.

Let's say that the two inputs to our gate are in phase (both high). That drives the gate output low; that low is then applied to the tri-color LED, causing one color to light (let's say red). But why not both? Remember, only one LED is forward-biased at a time, therefore only one will light—it's just that simple. Now, we've all built "cheapo" oscillators using a pair of inverters; but, as you will see, the XOR lets us cut the gate count in half!

Figure 5 shows a clock circuit that we can build using just one gate and a resistor. Although its operation is reliable, it

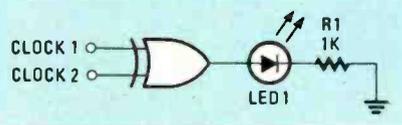


FIG. 2

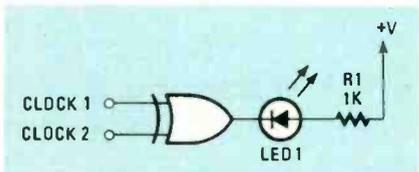


FIG. 3

### Exclusive-OR circuits


Figure 1 shows the symbol for the XOR gate along with its truth table. The truth table shows that its output is low whenever both inputs are the same, and high if the inputs are different. (That's an important characteristic, as we shall soon see.) The most immediate use for that truth table is to build the world's cheapest phase detector. All we have to do is route the two signals in question to the inputs of the gate and hang an LED on the output. Two possible layouts are shown in Figs. 2 and 3. The Fig. 2 circuit shows an XOR gate

# LETTERS

Address your comments to: Letters, **Radio-Electronics**,  
200 Park Avenue South, New York, NY 10003
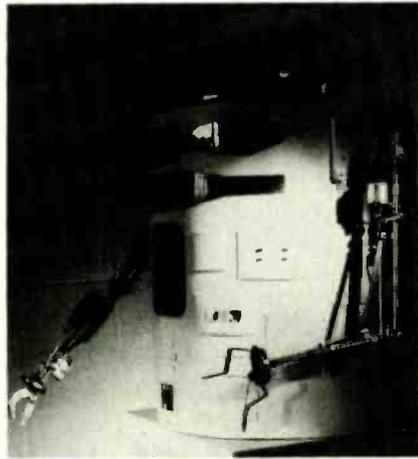
## ROBOT PARTS!

A note for those of you who have purchased the "Build Your Own Robot" reprint and have had trouble finding the various motors required: I have found a new source for all kinds of DC motors (including the all-important gearmotor for wheels and shoulders) at a very reasonable price (\$24.75). In addition, the company carries a host of relays, casters, motorized wheel assemblies, and a screw jack that extends from 1 1/2 to 20 inches (for those wanting the extendable type manipulator). For more information, contact: H&R Corporation, 401 East Erie Avenue, Philadelphia, PA 19134. Catalog sales: 215-426-1708.  
**JAMES A. GUPTON JR.**  
Charlotte, NC



## REPAIR MANUAL NEEDED

I am repairing an Accuphase C-200 stereo preamplifier and am in need of a schematic and service manual for it. The preamp was distributed in the United States around 1975-1980 by the Teac Corporation of Montebello, California. Can anyone help me with that? I would be willing to pay a fair sum for a repair manual if necessary. Thank you.  
**RONALD F. MORRIS**  
4823 Canehill Ave.  
Lakewood, CA 90713

## POWER SUPPLIES

I've just finished reading Mr. Horowitz's article, "How to Design Power Supplies", in the March 1984 edition. While I found it to be very  
*continued on page 18*

## QUALITY COMPONENTS NOT MAIL ORDER "SECONDS"

Send \$1.00 postage and handling for FREE COMPLETE CATALOG which includes coupon for \$1.00 OFF purchase

### ARIES ZERO INSERTION FORCE SOCKETS -

cam actuated, true zero insertion - tin plated solder tail pins - capable of being plugged into dip sockets, including wire wrap.

Stock No.	No. Pins	1-9	10-49	50
11055	24	4.98	\$4.35	\$3.90
11056	28	5.15	4.50	4.05
11057	40	8.81	5.95	5.35
11058	84	12.02	10.50	9.45

### IC-COOLERS from UMITRACK

dissipate over 2 watts of heat from IC's producing longer life and better performance. Just push IC-cooler on heat; is collected from top and bottom of IC and dissipated. Won't shake loose!

### WILD ROVER

Touch switch capsule. Operating motion is .005" without the use of a levered arm. Extremely fast on and off with low noise. Normally open - rated 115 VAC, 1.6 amp-30 milliohm resistance - 61.5 radius by .160 thick.

Stock No.	1-9	10 & Up
12098	\$1.42	\$1.28

### SCREW MACHINED SOCKET PINS, loose, packaged in bags of 100. Stock No. 11310 is solder tail with gold collet tin shell. Stock No. 11311 is wire wrap with gold collet gold shell.

Stock No.	Description	1 Bag	5 Bags	10 Bags
11310	Bag of 100 solder tail pins	4.95	4.45	\$3.95
11311	Bag of 100 wire wrap pins	11.95	10.75	9.50

### 60/40 ROSIN CORE SOLDER

Stock No.	Dia.	Length	Weight	Price
50075	062	9	1.5	\$1.16
50076	062	25	4	2.39
50077	062	50	8	4.25
50078	032	33	1.5	1.31
50079	032	88	4	2.47
50080	032	175	8	4.57

### WIRE WRAP SOCKETS

Tin plated phosphor bronze contact - 3 wrap

Stock No.	No. Pins	1-99	100-499	500-999
11301	8	\$4.40	\$3.36	\$3.30
11302	14	.59	.54	.45
11303	16	.64	.58	.48
11304	18	.73	.66	.55
11305	20	.99	.90	.75
11306	22	1.12	1.02	.85
11307	24	1.25	1.14	.95
11308	28	1.52	1.38	1.15
11309	40	2.05	1.86	1.55

### TIN LOW PROFILE SOCKETS

Tin plated copper alloy 688 contact pins with gas tight seal

Stock No.	No. Pins	1-24	25-99	100-999
11201	8	\$1.10	\$0.99	\$0.88
11202	14	.14	.13	.12
11203	16	.16	.15	.14
11204	18	.18	.17	.15
11205	20	.20	.18	.16
11206	22	.22	.20	.18
11207	24	.24	.22	.20
11208	28	.28	.26	.25
11209	40	.40	.37	.33

### EKI KITS

come with all parts necessary to assemble!  
Stock No. 88844 TV Jammer Kit "wipes out" your TV screen... \$ 7.71  
Stock No. 88850 Whooper Alarm Kit makes a great alarm or siren... \$11.33  
MANY, MANY MORE KITS AVAILABLE IN FULL LINE CATALOG



Low profile - .050 inch centers - can be bent or folded or "zipper" to separate individual connectors. Inter-faces with all interlocking displacement connectors!

### 3M ScotchFlex INSULATION DISPLACEMENT CABLES

Stock No.	Conductors	ROLL	ROLLS	ROLLS
03302	14	\$25.25	821.42	\$17.64
03303	18	28.90	24.45	20.18
03304	24	43.24	36.72	30.24
03306	40	71.88	61.18	50.34
03308	60	89.80	76.48	63.88
03310	80	107.42	87.00	71.69
03312	14	43.84	37.35	30.78
03314	18	50.24	42.70	35.17
03316	24	61.84	52.65	43.36
03318	30	70.42	59.50	49.19
03320	36	78.32	64.02	52.72
03322	42	87.00	71.68	58.88
03324	48	95.80	78.80	64.48

### Special of the Month!

**ANTI-STATIC BUG BOX** - has 30 compartments measuring 1" x 3 7/8" x 5" deep. Each Bug Box will store 60 eight-pin DIPs, 30 fourteen-pin DIPs, 30 sixteen-pin DIPs or 30 other small components such as transistors, diodes, resistor networks, etc. The transparent cover has a slipstep design that allows the user to empty one compartment at a time. A numbering system on the cover gives an instant count of remaining ICs.  
Stock No. 12803AB Package of 10 anti-static bug boxes \$18.95



### OPCOA

Single Digit Displays - Common Cathode  
Stock No. Color Price  
12082 Red \$1.12 \$ .99  
12085 Green 1.84 \$ 1.83  
12087 Yellow 1.92 \$ 1.70  
12089 Orange 2.08 \$ 1.84  
Right Angle Socket for Above Displays  
Stock No. Price  
11010 \$1.24 \$ .99



### OPTEL LCD's with pins

Stock No.	Description	1	10
47005	3 1/2 dig. 5"	\$ 5.95	5.50
47006	4 dig. 5"	5.95	5.50
47007	4 dig. 7"	11.90	11.00

Stock No. 47006 \$88.88

### The Battery Just Wrap Tool


New battery covered tool wraps insulated wires around .025" square posts without need for pre-cutting and pre-stripping. Completes with bit and 100 ft. 30 AWG wire.  
Stock No. Price  
13340 Battery just-wrap tool with bit and 100 ft. 30 AWG wire... \$58.95  
13341 Replacement bit... 10.35  
13342 100 ft. blue replacement wire... 7.54  
13343 100 ft. white replacement wire... 7.54  
13344 100 ft. yellow replacement wire... 7.54  
13345 100 ft. red replacement wire... 7.54

### MICRO Charts - colorful 8 1/2" x 11"

charts eliminate the need to stumble through manuals and summaries. Fully decoded - instant access - totally comprehensive - gives pin outs, cycle times, buy notes, etc. etc.  
Price  
23010 Z80 CPU... \$5.95  
23011 8086/8088... 5.95  
23012 8052 (8533)... 5.95  
23013 8048 and relatives... 5.95  
23014 54/7400 TTL Pinouts... 5.95  
23015 Basic Algorithms... 5.95
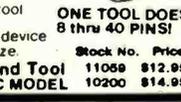
### PIN FORMING TOOL

puts IC's on their true row to row spacing. One side is for .300 centers. Flip tool over for devices .600 centers. Put device in tool and squeeze.  
Hand Tool 11058 \$12.95  
NEW! ANTI-STATIC MODEL 10200 \$14.95



### Scotchflex Breadboard System

Basic kit comes with 24 various Dual Sockets, 40 various Plug Strips, wire and locks. Kit can be used with any of the six boards.  
Stock No. Description Price  
03500 Basic Kit \$79.95  
03511 Basic board, 4.5 x 5.5 19.50  
03508 Intel 80C 8010 Board, 12 x 6.75 64.95  
03507 Motorola M-6800 Board, 9.75 x 6 42.95  
03506 S-100 Board, 10 x 5.3 38.95  
03509 Z-80 Board, 7.7 x 7.5 39.95  
03510 Eurocard Board, 6.3 x 3.9 21.95

### OK MACHINE AND TOOL

IC INSERTION/EXTRACTION KIT includes VUP IC extractors and inserters to accommodate all ICs from 14 to 40 pins. Tools that engage conductive surfaces are CMOS safe and include grounding lugs.  
Stock No. 13306 \$41.34

### SOCKET WRAP ID

Dip socket-sized plastic panels with numbered holes in pin locations. Slip onto socket before wire wrapping to identify pins. Also write on them for location, IC part number, function, etc. Simplifies initial wire wrapping.  
Price  
13295 14 pin 13.95  
13296 16 pin 16.95  
13297 18 pin 19.95  
13298 20 pin 22.95  
13299 22 pin 25.95  
13300 24 pin 28.95  
13301 28 pin 35.95  
13302 40 pin 49.95  
13303 96 pin 119.95  
Troubleshooting and repair \$1.95 per deck

### LOW PROFILE DIP SWITCHES

Stock No.	No. Poles	Price
10251	1	1.24
10252	2	1.35
10253	3	1.45
10254	4	1.50
10255	5	1.60
10256	6	1.70
10257	7	1.80
10258	8	1.90
10259	9	2.00
10260	10	2.10

**SINTEC** 28 8th St. Box 410 Frenchtown, NJ 08825 TOLL 800-526-5960 FREE in NJ (201) 996-4093




We accept VISA, MC, C.O.D., CHECK, M.O. INCLUDE SHIPPING CHARGES. DTG \$100 \$1.00 \$100 to \$250 \$3.00 over \$250 \$5.00

CIRCLE 71 ON FREE INFORMATION CARD  
[www.americanradiohistory.com](http://www.americanradiohistory.com)
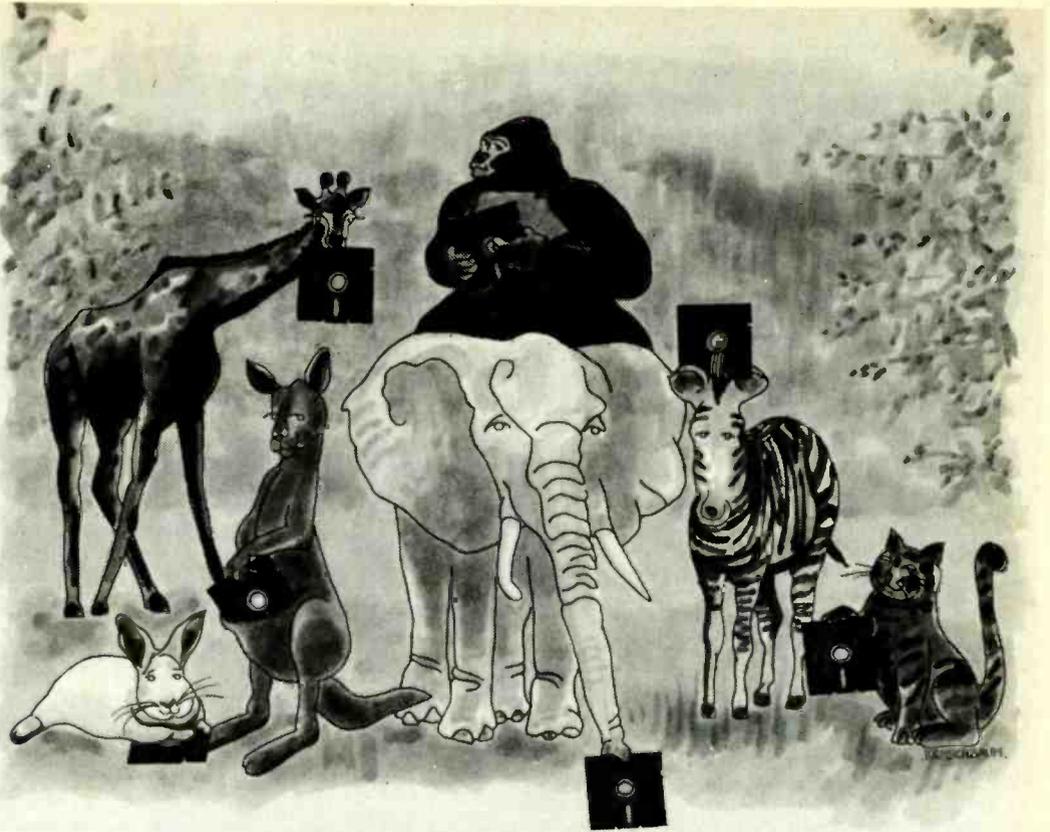
# Diskette Users...

When you've heard from all the animals in the diskette zoo, but you need fast delivery and high quality diskettes...



## Call Communications Electronics

Diskette order desk  
**800-USA-DISK**

In Canada 800-CA1-DISK

Choose your brand  
Choose your price



**Super Disk**  
diskettes  $\frac{5}{8}$ "  
\$0.99 each



**Wabash**  
diskettes  $\frac{5}{8}$ "  
\$1.14 each



**BASF**  
diskettes  $\frac{5}{8}$ "  
\$1.54 each



**3M**  
diskettes  $\frac{5}{8}$ "  
\$1.59 each

Product Description	Super Disk Part #	CE quot. 100 price per disk (\$)	Wabash Part #	CE quot. 100 price per disk (\$)	BASF Part #	CE quot. 100 price per disk (\$)	3M Part #	CE quot. 100 price per disk (\$)
8" SSSD IBM Compatible 128B/S, 26 Sector	_____	_____	F111-J	1.89	_____	_____	8SS80-J	1.94
8" SSSD Shugart Compatible, 32 Hard Sector	_____	_____	F31A-J	1.89	_____	_____	_____	_____
8" SSSD IBM Compatible (128 B/S, 26 Sectors)	_____	_____	F131-J	2.29	_____	_____	8SS80-J	2.39
8" DSDD Soft Sector (Unformatted)	_____	_____	F14A-J	2.69	_____	_____	8DS80-J	2.89
8" DSDD Soft Sector (256 B/S, 26 Sectors)	_____	_____	F144-J	2.69	_____	_____	_____	_____
8" DSDD Soft Sector (512 B/S, 15 Sectors)	_____	_____	F145-J	2.69	_____	_____	_____	_____
8" DSDD Soft Sector (1024 B/S, 8 Sectors)	_____	_____	F147-J	2.69	_____	_____	_____	_____
5 1/4" SSSD Soft Sector w/Hub Ring	6431-J	1.19	M11A-J	1.34	_____	_____	8DSDD-1024-J	2.89
5 1/4" SSSD Same as above but bulk product	6437-J	0.99	M11AB-J	1.14	_____	_____	_____	_____
5 1/4" SSSD 10 Hard Sector w/Hub Ring	_____	_____	M41A-J	1.34	_____	_____	_____	_____
5 1/4" SSDD Soft Sector w/Hub Ring	6481-J	1.44	M13A-J	1.59	54974-J	1.54	5SSDD-RH-J	1.79
5 1/4" SSDD Same as above, but bulk product	6487-J	1.24	M13AB-J	1.39	_____	_____	5SSDD-BL-J	1.59
5 1/4" SSDD Soft Sector Flippy (use both sides)	_____	_____	M18A-J	2.59	_____	_____	_____	_____
5 1/4" SSDD 10 Hard Sector w/Hub Ring	_____	_____	M43A-J	1.59	_____	_____	_____	_____
5 1/4" DSDD Soft Sector w/Hub Ring	6491-J	1.94	M14A-J	2.09	54980-J	2.04	5DSDD-RH-J	2.24
5 1/4" DSDD Same as above, but bulk product	6497-J	1.74	M14AB-J	1.89	_____	_____	_____	_____
5 1/4" DSDD 10 Hard Sector w/Hub Ring	_____	_____	M44A-J	2.09	_____	_____	_____	_____
5 1/4" DSDD 16 Hard Sector w/Hub Ring	_____	_____	M54A-J	2.09	_____	_____	_____	_____
5 1/4" DSDD Soft Sector w/Hub Ring (96 TPI)	6501-J	2.84	M16A-J	2.99	54992-J	3.14	5DSDD-96RH-J	3.14
3 1/2" SSSD Soft Sector micro-floppy	_____	_____	_____	_____	54112-J	2.74	3SSMD-J	3.74

For more information about this brand call:

**Lifetime warranty**  
For more info on Super Disk call  
**800-USA-DISK**  
In Michigan 313-973-1111

**6 year warranty**  
For more info on Wabash call  
**800-323-9868**  
In Illinois 312-593-6363

**Lifetime warranty**  
For more info on BASF call  
**800-343-4600**  
In Massachusetts 617-271-4000

**Lifetime warranty**  
For more info on 3M call  
**800-328-9438**  
In Minnesota 612-736-9524

CIRCLE 35 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

## CE...your best source for diskettes

For you the diskette buyer, it's a jungle out there. There are so many different brands to choose from, you need to go on a safari to find a good brand at a reasonable cost. Fortunately, CE has already hunted for the best diskettes and offers you an excellent choice at a CE price. To save you even more, CE also offers bulk product where 100 diskettes are packed in the same box without envelopes or labels. Since we save packaging costs, these savings are passed on to you. Diskette envelopes are also available from CE. These super strong and tear resistant Tyvek® envelopes are only \$15.00 per 100 pack. Use order # TE-5 for a 100 pack of 5¼" diskette envelopes.

## Quantity Discounts Available

Our diskettes are packed 10 disks to a carton and 5 or 10 cartons to a case. The economy bulk pack is packaged 100 disks to a case without envelopes or labels. Please order only in increments of 100 units for quantity 100 pricing. With the exception of bulk pack, we are also willing to accommodate your smaller orders. Quantities less than 100 units are available in increments of 10 units at a 20% surcharge above our 100 unit price. **Quantity discounts** are also available. Order 300 or more disks at the same time and deduct 1%; 500 or more saves you 2%; 1,000 or more saves 3%; 2,000 or more saves 4%; 5,000 or more saves 5%; 10,000 or more saves 6%; 50,000 or more saves 7%; 100,000 or more saves 8%; 500,000 or more saves 9% and 1,000,000 or more disks earns you a 10% discount off our super low quantity 100 price. Almost all our diskettes are immediately available from CE. Our efficient warehouse facilities are equipped to help us get you the quality product you need, when you need it. If you need further assistance to find the flexible diskette that's right for you, call the appropriate manufacturers compatibility hotline telephone number listed at the bottom of this ad. Dealer inquiries invited.

## Buy your diskettes from CE with confidence

To get the fastest delivery of your diskettes, phone your order directly to our order desk and charge it to your credit card. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. For maximum savings, your order should be prepaid. All sales are subject to availability, acceptance and verification. All sales are final. All prices are in U.S. dollars. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder or substituted for equivalent product at no extra cost to you unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. All shipments are F.O.B. CE warehouse in Ann Arbor, Michigan. COD terms are available, in U.S. UPS areas for \$5.00 extra, and are payable with cash or certified check.

For shipping charges add \$8.00 per 100 diskettes and/or any fraction of 100 8-inch diskettes, or \$6.00 per 100 diskettes and/or any fraction of 100 5¼-inch or 3½-inch diskettes for U.P.S. ground shipping and handling in the continental U.S. UPS 2nd day air rates are three times continental U.S. rates. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping is three times the continental U.S. rate.

**Mail orders to:** Communications Electronics, Box 1045, Ann Arbor, Michigan 48106 U.S.A. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-USA-DISK. In Canada, order toll-free by calling 800-CA1-DISK. If you are outside the U.S. or in Michigan dial 313-973-8888. WUI telex anytime 671-0155. Order today.

Copyright © 1984 Communications Electronics Inc.

Ad #062184



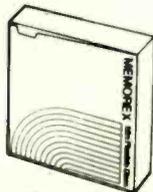
## Computer Products Division

Box 1045 □ Ann Arbor, Michigan 48106-1045 U.S.A.  
Call toll-free 800-USA-DISK or outside U.S.A. 313-973-8888



**Verbatim diskettes** low price  
**\$1.79 each**



**Memorex diskettes** low price  
**\$1.84 each**



**Ultra diskettes** low price  
**\$1.89 each**



**TDK diskettes** low price  
**\$2.09 each**



**Fuji diskettes** low price  
**\$2.14 each**



**Dysan diskettes** low price  
**\$2.49 each**

Verbatim Part #	CE quant. 100 price per disk (\$)	Memorex Part #	CE quant. 100 price per disk (\$)	Ultra Part #	CE quant. 100 price per disk (\$)	TDK Part #	CE quant. 100 price per disk (\$)	Fuji Part #	CE quant. 100 price per disk (\$)	Dysan Part #	CE quant. 100 price per disk (\$)
_____	_____	3062-J	1.94	81726-J	1.99	F1-S-J	2.69	F01S-128N-J	2.79	800501-J	2.79
_____	_____	3015-J	1.94	_____	_____	_____	_____	_____	_____	800605-J	3.19
_____	_____	3090-J	2.39	_____	_____	F2D-S-J	3.29	FD2D-J	3.59	800803-J	3.59
_____	_____	3102-J	2.89	82701-J	2.94	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	F2D-S1024-J	3.29	FD2D-1024-J	3.59	800839-J	3.59
_____	_____	3104-J	2.89	82708-J	2.94	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	M1D-S-J	2.09	M01D-J	2.14	801187-J	2.49
28820-J	1.79	3481-J	1.84	51401-J	1.89	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	52402-J	2.69	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	52401-J	2.64	M2D-S-J	2.84	M02D-J	2.89	802060-J	3.49
28821-J	2.54	3481-J	2.59	_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	_____	_____	_____	_____	M2D-S-J	3.89	M02D-96TPI-J	3.94	802067-J	4.29
_____	_____	_____	_____	52801-J	3.54	_____	_____	_____	_____	_____	_____
28823-J	3.44	3501-J	3.49	_____	_____	_____	_____	_____	_____	_____	_____
_____	_____	6100-J	3.74	_____	_____	_____	_____	_____	_____	_____	_____

**Lifetime warranty**  
For more info on Verbatim call  
**800-538-8589**  
In California 408-245-4400

**5 year warranty**  
For more info on Memorex call  
**800-448-1422**  
Monday-Friday 9am-4pm ET

**Lifetime warranty**  
For more info on Ultra call  
**408-728-7777**  
Monday-Friday 9 am-4 pm PT

**Lifetime warranty**  
For more info on TDK call  
**800-645-6571**  
In New York 516-625-0100

**Lifetime warranty**  
For more info on Fuji call  
**800-223-6535**  
In New York 212-736-3335

**1 year warranty**  
For more info on Dysan call  
**800-552-2211**  
In California 408-970-6086

CIRCLE 35 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

## LETTERS

continued from page 15

informative, I did notice several errors/omissions. I admit to some nitpicking, but there were enough bonafide errors to warrant the time to write this note. When Mannie talked about selecting a diode, he suggested that fullwave rectifier diodes would "see twice the secondary voltage across it when not conducting. It will actually "see" twice the center-tap voltage, or the full secondary across it when turned off. In explaining the choice of a proper transformer, he said, "Add the value

you get for  $\Delta T$  to  $R_C$ ." I'm not sure how to add  $^{\circ}C$  to ohms.

For Fig. 7-b and the equation for the voltage across  $Q_1$ :

$$V_2 \left( \frac{R_2 + R_3}{R_3} \right),$$

$V_2$  is not identified.

"In Fig. 8 we've added," should be Fig. 9.

Under Crowbar circuits: "A crowbar circuit is used to prevent damage to a regulated power supply..." A Crowbar circuit is used to protect the load, not the supply. When a high voltage appears across the load, for whatever reason, the SCR shorts the supply, thereby protecting the load from a possible damaging

voltage. The supply could be damaged but, one hopes, not the load. Quite often a fuse is placed in the power supply to protect it from excessive current.

Thank you for your time. I hope my observations are of some help.

ALFRED L. IZATT  
Aberdeen, Washington

*Yes, your observations are of some help—not only to turn our faces red but to give us the opportunity to correct ourselves. You cannot, of course, add  $^{\circ}C$  to ohms. You should add the temperature at which  $R_C$  was measured to  $\Delta T$ . The voltage  $V_2$  is actually  $V_Z$ , the Zener voltage. If a high voltage is applied across the load, both the supply and the load could be damaged. A crowbar circuit can protect both. (Of course, if the supply is the source of the high voltage, all you're concerned about is protecting the load.)—Editor*

### THANKS

Since you published my "Suggestions Needed" letter in the February 1984 issue of *Radio-Electronics*, I have received a phenomenal number of responses from readers all over. Thanks to them, my dream is a reality—I now have a 70-MHz IF amplifier and detector made from discrete parts. I would like to extend a most heartfelt thanks to all those who made it that way for me.

The response was really great and I have *Radio-Electronics* to thank also. By the way, I renewed my subscription for yet another year of fantastic articles of electronics innovation that has become a standard for your magazine. Keep up the good work.

LeROY SMITH  
Wetumpka, AL

### PLEASED WITH COMPUTER DIGEST

I was extremely pleased with your feature section *ComputerDigest*, especially because it didn't take any "editorial space" from *Radio-Electronics*.

With the death of *Popular Electronics* (I know they are now *Computers & Electronics*), you are the last decent electronics magazine left on the market.

I enjoy computers as much as the next person, but I also enjoy electronics and as far as I'm concerned I have my choice of computer magazines I can read.

Thank you for preserving my sanity.  
BOB BROADWAY  
Canoga Park, CA

### CORRECTION: C-QUAM STEREO CONVERTER

I've noticed an error in the parts-placement diagram that appeared in the January, 1984 article, "Build This C-Quam AM Stereo Converter." In all three parts-placement diagrams C17 and C18 listed as 2.2  $\mu F$  and 4.7  $\mu F$  respectively are interchanged from that of the schematic diagram. I assume the schematic has them listed correctly.

DOUGLAS FINK  
Dearfield, MI

*You are correct. Also note that, as we've mentioned before, IC2 is incorrectly labeled Q1, although the package outline is correct. We're sorry for any inconvenience we've caused.—Editor*

# A QUALITY TRIPLE-REGULATED POWER SUPPLY AT A LOW, LOW PRICE!!

NOT A KIT!



MODEL PS101  
FULLY ASSEMBLED & TESTED!

\$ 119.88

FULL 1 YEAR REPLACEMENT WARRANTY

— Made In The United States —

This DC triple regulated variable power supply has all the features you could ask for plus a full 1 year guarantee. Fully adjustable from 1 1/2 VDC to 35 VDC! Three completely independent supplies that offer many advantages! They can be either a pos. supply or a neg. supply...they can also be stacked in series so that a 5V and two 15V supplies can total a 35 VDC supply or any combination of the three...(after one of the terminals is grounded to give it a reference)...for the first time you can now purchase this American made fully adjustable power supply at a price that is one-half of what you'd expect to pay!

#### SPECIFICATIONS

3 outputs:

Fixed 5 VDC  $\pm 0.2V$

2 variable  $\leq 1\frac{1}{2}V$  to  $\geq 15V$  VDC

Polarity—floating; can be used as pos. or neg.

Ripple less than 10mV at full load,

Regulation  $\leq 1\%$  no load to full load,

Line Regulation  $< 0.2\%$  108 VAC to 135 VAC.

Current:

Fixed supply 1.0 amp max.

Variable supplies 0.5 amp max.

Protection built in, current limiting, with thermal shutdown.

Power: 108-135 VAC.

Dimensions: 8 1/4" x 3 3/4" x 7 1/4" (WxHxD)

Wood grain finished metal case.

Weight: 4 lbs., 9 ozs.

Lighted on/off power switch, easy-to-read

Voltmeter and large binding posts.

Warranty: one year full replacement

warranty from date of purchase.

DISTRIBUTOR AND REPRESENTATIVE INQUIRIES INVITED

**EWE**  
E.W. ENGINEERING, INC.

VISA, MASTERCARD, AMEX TELEPHONE ORDERS ACCEPTED!  
6 Herman Drive, E. Granby, CT 06026 □ 203/651-0285

CIRCLE 81 ON FREE INFORMATION CARD

## USEFUL ELECTRONICS FOR THE HANDICAPPED

I read with interest your "Communications Corner" column in the July 1983 issue of **Radio-Electronics** concerning electronics aids for the handicapped. However, I think that the article missed one of the most useful and obvious of those aids, namely the closed-caption device used by the hearing-impaired for watching television.

Perhaps you could devote a column and a construction article for such a device. I can't believe it would be that difficult to extract and save these characters from horizontal lines 10 through 13 and display them at the bottom of the screen. I would do this myself if I could find any literature on the format transmitted, exactly which lines carry the information, etc. Is it ASCII data? I have looked through all the reference guides at my library and can find no information. If this is a public service for the deaf, why isn't any information available? I know Sears Roebuck sells a decoder for about \$300.00, but couldn't a few dollars worth of chips do the same thing?

Two Teletext standards used in the United States are NAPLPS and Prestel. Is it possible that one of those two standards is being used, or is closed-captioning completely different? I know closed-captioning doesn't seem to work on my NAPLPS decoder (Zenith CV-550).

Please perform a public service and provide the technical details if not a complete construction project.  
JOHN BUNTING

## INPUT HELP NEEDED

I have a 9-inch Sanyo monitor and a Ball monitor, each with separate horizontal and vertical sync inputs. Can one of your readers help me with the circuit that will allow me to input composite video so I can use them with my home computer. Thank you.

WALTER MOORE  
551 Elmwood Drive  
Brandon, MS

## COMPUTERS & RADIO-ELECTRONICS

I thoroughly agree with the opinion expressed by Richard Taylor in his letter published in the May 1984 issue of **Radio-Electronics**. I had subscribed to *Popular Electronics* almost since its inception, and before that, its parent, *Radio News*, for more years than I can remember. However, when *Popular Electronics* switched to its almost completely computer-oriented format, I allowed my subscription to expire. I don't feel I left them—they left me!

Although I do own a Commodore 64, my first love is still general electronics and ham radio. I am now retired, after about 42 years with the Bell System. I would expect to continue subscribing to **Radio-Electronics** as long as you see fit to continue the present mix of general electronics and computers. I've been through a long career in electronics with Gernsback publications—*Radio-Craft*, *Short-Wave Craft*, and *Radio-Electronics*. There are more than enough computer magazines out there already. Stay as you are—I'll stay with you!

ALLEN L. BARNETT WB2QPM  
Jersey City, NJ

R-E

Now we can detect a breast cancer smaller than this dot.

At such an early stage, your chances of living a long, healthy life are excellent. But we need your help. The only proven way to detect a cancer this small is with a mammogram. A mammogram is a low-radiation x-ray of the breast capable of detecting a cancer long before a lump can be felt. If you're over 50, a mammogram is recommended every year. If you're between 40 and 50, or have a family history of breast cancer, consult your doctor. In addition, of course, continue your regular self-examinations.

 American Cancer Society



# THE RIGHT STUFF

The growth of NTE quality replacement parts has been nothing short of astronomical. And the proof is in our new 1984 Replacement Master Guide, destined to be the standard directory for technicians across the country. In excess of 3,000 quality NTE types are cross-referenced to more than 220,000 industry part numbers.

### YOU'LL FIND ALL THE RIGHT STUFF FOR REPLACEMENT, MAINTENANCE AND REPAIR:

- Transistors
- Thyristors
- Integrated Circuits
- Rectifiers and Diodes
- High Voltage Multipliers and Dividers
- Optoelectronic Devices
- Zeners
- Microprocessors and Support Chips
- Memory IC's
- Thermal Cut-Offs
- Bridge Rectifiers
- Unijunctions
- RF Transistors
- Microwave Oven Rectifiers
- Selenium Rectifiers
- NEW! The Protector 6000™ Transient Voltage Protection Strip

Look for our Replacement semiconductor in the bright green polybags and cartons that list rating limits, device type, diagrams and competitive replacement right on the package. NTE quality parts are available from your local NTE distributor and come backed by our exclusive two-year warranty. Ask for your FREE NTE Replacement Master Guide and take off with NTE!



NEW-TONE ELECTRONICS, INC.

44 FARRAND STREET • BLOOMFIELD, NEW JERSEY 07003

# NEW IDEAS

## Energy-use monitor

ENERGY CONSERVATION IS BECOMING increasingly more important, particularly when your trying to save a couple of bucks—and who isn't? In fact, it is often with thoughts of energy conservation that we decide to get rid of an appliance and replace it with a new one. But replacing old appliances is not always worth the expense. The circuit described this month will allow you to monitor the time that an appliance—such as an old refrigerator with worn out insulation—runs. Then, with some simple arithmetic you can figure the kilowatthours used.

Multiplying the run-time in hours by the appliance load in watts (as printed on the appliance) will let you know the kilowatthours used. Armed with that information, it is a simple matter to figure your total cost (by multiplying the kilowatthours by the cost of electricity in your area. Now, let's take a look at the circuit.

### How it works

Figure 1 shows the schematic of the energy monitor. Besides having a low parts count, most of the components are commonly available. Power for the circuit is provided by T1 (a 33-volt transformer) and diodes D4-D7 (1N4004), which form a full-wave bridge rectifier. The rectified AC voltage is filtered by capacitor C3. The LOAD and CLOCK sockets (SO1 and SO2 respectively) are connected to the primary of the transformer. One side of the line cord to socket SO1 is passed

through the center of (handwound) coil L1 so that they are inductively coupled. (More about that coil in a moment.)

When an appliance is plugged into socket SO1 and power is turned on, a current is induced in L1. That creates a potential difference that is then applied to the input of the op-amp, IC1, causing its output to saturate. Because of the high open-loop gain of the op-amp, a few millivolts is all that is needed. Capacitor C1 and diodes D1 and D2 are used to protect the input of IC1.

The output of IC1 is then fed through resistor R1 to the base of NPN transistor Q1, turning Q1 on. Transistor Q1 provides the necessary drive current for relay RY1, while capacitor C2 filters the 60-Hz pulses to prevent erratic relay operation. When Q1 is turned on, a signal path to ground is provided for RY1, causing its contacts to close. With the relay contacts closed, current flows to SO2, causing the clock plugged into that socket to begin operation.


With the components shown, a load current of from 6-8 amps can be monitored. Here the limiting factor is the size of the line cord and hook-up wire to the load socket. None of the components are critical, therefore, junkbox parts may be used. For instance, coil L1 was salvaged from an industrial power supply acquired from a junk dealer. The coil, one-inch in diameter, was rewound using 34 turns of No. 24 stranded hook-up wire.

The supply voltage can be varied to match the requirement of the components used. An ordinary household clock was used along with the circuit to find out how much the old refrigerator cost to keep running. —Sharon Christy
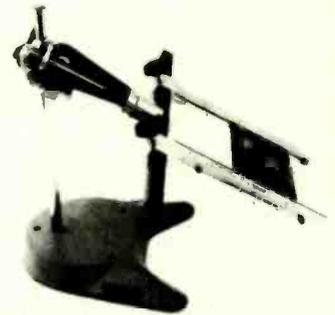
### NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, for U.S. residents only, Panavise will donate their model 333—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working.



I agree to the above terms, and grant Radio-Electronics Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material has not been previously published.

Title of Idea \_\_\_\_\_

Signature \_\_\_\_\_

Print Name \_\_\_\_\_

Date \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Mail your idea along with this coupon to: **New Ideas Radio-Electronics**,  
200 Park Ave. South,  
New York, NY 10003

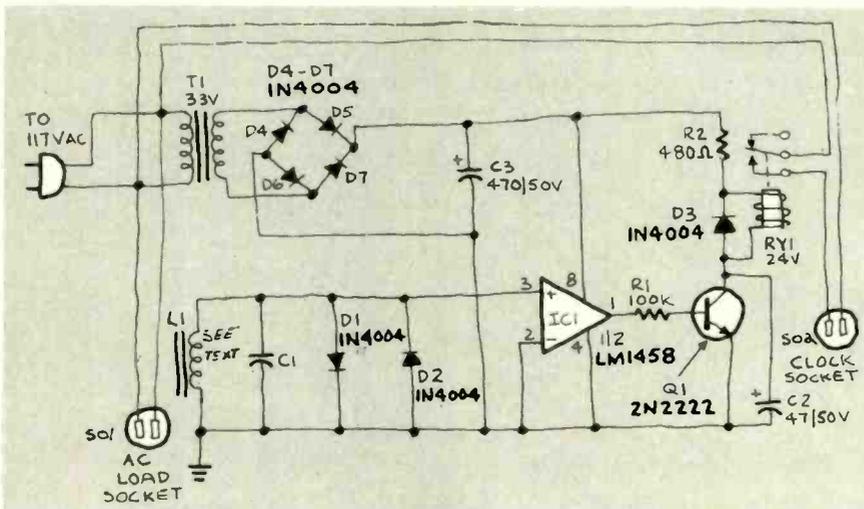



FIG. 1

# EQUIPMENT REPORTS

## Iwatsu SS-5702 Dual-Trace Oscilloscope

A 20-MHz, dual-trace model at an attractive price

CIRCLE 101 ON FREE INFORMATION CARD

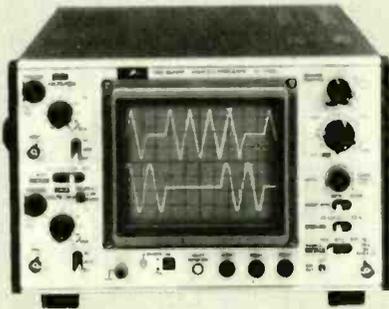

THERE ARE MANY DIFFERENT MODELS OF oscilloscopes available today—literally hundreds. They include low-cost, single-channel, narrow-bandwidth scopes; dual-beam, quad-trace scopes with 100-MHz

bandwidths, and flat panel, LCD-screen, storage oscilloscopes. But what type of scope are you looking for?

If you're in the market for an oscilloscope—and a 20-MHz, dual-trace

model will fill your needs—then you may want to start your shopping by checking out the SS-5702 from Iwatsu Electric Co. Inc. (1200 Commerce Road, Carlstadt, NJ 07072). We'll look at its capabilities shortly—after a look at its physical characteristics.

The SS-5702 weighs about 14 pounds. So although it's not a portable scope (in the sense that you need an AC power outlet), it is easy to move around. Its maximum dimensions are less than 11 x 7 x 18 inches. A comfortable carrying handle is included at the side of the scope, and three sets of feet (side, back, and bottom) let you store the unit in any position.

The front panel of the scope is dominated by a 8 x 10 cm display. The graticule, with 1-cm divisions, is internal (to

## SURPLUS BARGAINS

### Dataproducts D-50 Daisy Wheel Terminal:

- "35" Character per second print rate.
- RS-232 Input ("Receive-only" configured).
- 300-9600 Baud rate for fast print speed.
- Takes standard Diablo Daisywheels.
- Offers 10 pitch and 12 pitch.
- Full 13 1/2" carriage width.
- 6 & 8 lines per inch.

BUY NOW

These off-lease Daisy Wheel terminals are cleaned and adjusted and ready to use. Built in the U.S. by master printer manufacturer: DATAPRODUCTS. Ideal for use as a high speed Word Processor Printer. With data and info

SUPPLY LIMITED



NOW ONLY \$695<sup>00</sup> ea. Only!!

### CRT Terminals

Built by a major OEM, these terminals include 3 microprocessor boards (Interface, CPU & CRT) plus composite video & switching power supply 48K or roms, "Ergonomic" design and more. Experimenter special, includes Data, Keyboard, RS-232 I/O plus much more. Seems to be quite powerful.



NOW ONLY \$289<sup>00</sup> ea. Only!!

### Parallel, TTL Input I/O "Selectric"

TYPEWRITER/PRINTER These machines have built-in driver and decoder circuitry and take TTL level, 6-bit character, plus a 4-bit function input signals. Easily driven by most any micro. Use as a typewriter (with add'l "repeat" circuitry) or as a KSR I/O printer or both. "Table Top" style case.



NOW ONLY \$299<sup>00</sup> ea. Only!!

TESTED AND OPERATIONAL

### 9" Composite Video Input CRT Monitor

Requires approx. 12 VDC @ 1-2A VDC in attractive case. With schematics.



NOW ONLY \$89<sup>00</sup> ea. Only!!

### Shugart SA-400 "Mini-Floppy" Drives

Model SA-400, used, whole, untested, less power supply & case. Data and schematics included. Removed from Equipment.



NOW ONLY \$119<sup>00</sup> ea. Only!!

Prices do not include packaging and shipping

Write or Call for Our Latest Flyer NOW!!! "Selectric" is a registered trademark of IBM Corporation

Computer Products & Peripherals Unlimited

WAREHOUSE: 18 Granite St., Haverhill, Mass. 01830  
MAIL ORDERS: Box 204, Newton, New Hampshire 03858

617/372-8637

Sorry No Collect Calls  
MasterCard & VISA Accepted



CIRCLE 68 ON FREE INFORMATION CARD

## MULTIVISION

ELECTRONIC EQUIPMENT WHOLESALERS AND EXPORTS



JERROLD 60 CHANNEL WIRELESS REMOTE CONTROL CONVERTER LCC 58-3 \$99<sup>95</sup> EXTRA HAND REMOTES \$19<sup>95</sup>

PHILIPS 67 CHANNEL WIRELESS REMOTE CONVERTER with VOLUME CONTROL and MUTEING. FINE TUNING CENTERING. \$189<sup>00</sup>

PIONEER 57 CHANNEL WIRELESS REMOTE CONTROL with PARENTAL LOCKOUT and 10 CHANNEL FAVORITE MEMORY RECALL. DEALERS WE HAVE VIDEO RECORDERS, ENHANCERS, STABILIZERS AND ACCESS.

12' GALVINIZED RADAR MESH SATILITE DISH \$1075<sup>00</sup>  
Dealers call for pricing!



SATILITE RECEIVERS WIRELESS REMOTE CONTROL - HIGHEST QUALITY \$599<sup>00</sup>

RETAIL - WHOLESALE  
305-981-1112 • 305-981-1113

CIRCLE 17 ON FREE INFORMATION CARD

eliminate parallax error) and it is lighted. A front-panel control lets you continuously vary the graticule brightness.

**Controls and features**

Now that you have an idea of what the SS-5702 looks like, let's look at some of its capabilities. Perhaps the best way to do that is to go through some of the front-panel controls. To the left of the CRT are the vertical-amplifier controls. Each channel has a BNC INPUT jack and a coupling switch (with AC, DC and GND positions) as well as a VOLTS/DIV control that allows you to vary the vertical-deflection

factor from 5 millivolts per division to 10 volts per division in the familiar 1-2-5 sequence.

An inner, concentrically mounted control can be used to continuously vary the deflection factor. When that control is set in its CALIBRATED position, measurements can be made within  $\pm 4\%$ .

A display-position control is also included for each vertical channel. Incorporated in that rotary control is a push-pull switch that can be used to magnify the vertical sensitivity by a factor of five. The vertical-deflection factor can then be varied from 1 millivolt per division to 2 volts

Iwatsu										SS-5702										
OVERALL PRICE																				
EASE OF USE																				
INSTRUCTION MANUAL																				
PRICE/VALUE																				
	1	2	3	4	5	6	7	8	9	10	1	2	3	4	5	6	7	8	9	10
	Poor			Fair			Good			Excellent										

per division by using the VOLTS/DIV control. However, the accuracy of your measurements decreases to  $\pm 5\%$  in the  $\times 5$  mode.


Channel 1 and Channel 2 share a four-position V-MODE switch that is used to select the vertical operating mode (Channel 1, Channel 2, dual, and add). In the CH 1 (or CH 2) position, only the signal input to Channel 1's (or Channel 2's) BNC jack is displayed. In the DUAL mode, the signals that are input to both channels are displayed. (Chopped or alternate display is selected automatically: Below a sweep rate of 0.5 ms/division, the chopped mode is automatically chosen, while above that rate, the alternate mode is chosen.) The fourth position selects the ADD mode. In that mode, the signals that are input to both channels are algebraically added together. You can also determine the algebraic difference of two input signals because Channel 2 has a POLARITY switch that inverts the polarity of the Channel 2 display. Then, when the ADD vertical mode is chosen, the difference of the input signals (A - B) is displayed. Other controls include trace-intensity (INTEN), TRACE ROTATION and FOCUS.

Moving to the horizontal-deflection system, we see a POSITION control, a TIME/DIV, and a continuously variable time-per-division control. The sweep rate can be adjusted from .5 microseconds to .25 seconds-per-division in 18 steps (arranged in a 1-2-5 sequence on the control). Measurements made over the 8 center divisions are accurate within  $\pm 5\%$ . A rotary SWEEP LENGTH control doubles as a push-pull switch that increases the displayed sweep rate by a factor of five. However, measurement accuracy in that mode (again over 8 divisions) decreases to  $\pm 15\%$ .

Another group of controls are those for the trigger circuit. It includes the LEVEL/SLOPE control that is used to set the trigger level—that is, the level of the input signal that will cause the sweep to begin, and the slope of the input signal that will cause triggering.

The next trigger control is the SOURCE switch that is used to select internal trigger signals (from Channel 1 or Channel 2) or an external signal. (A BNC connector
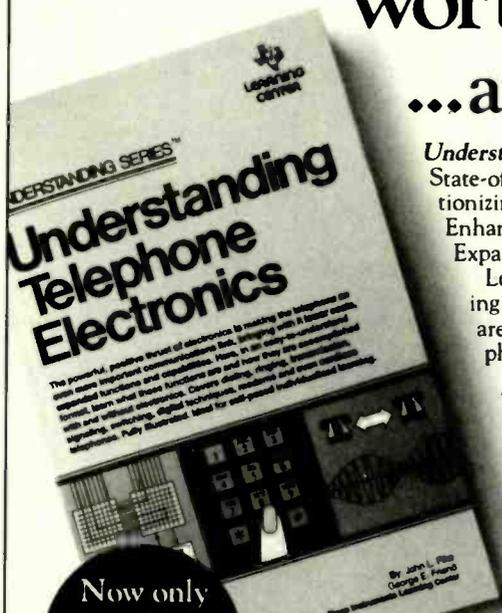
# Here's one phone book worth buying ...and reading.



**Understanding Telephone Electronics.**

State-of-the-art technology is revolutionizing telephone communications. Enhancing capabilities. Lowering costs. Expanding functions.

Learn why digital systems are replacing analog. Why cordless phones are practical. How cellular mobile phones work.

Fully illustrated, *Understanding Telephone Electronics* is written in concise, nontechnical language, ideal for self-paced learning.

To order *Telephone Electronics*, or any other book in the *Understanding Series*,™ use the coupon below.

Now only  
**\$6.95**

## TEXAS INSTRUMENTS

Creating useful products and services for you.

™ Trademark of Texas Instruments Incorporated

- |   |          |           |
|---|----------|-----------|
| Please send me:   | Quantity | Price     |
| <input type="checkbox"/> <b>Understanding Series Titles:</b>                              |          |           |
| <input type="checkbox"/> Understanding Telephone Electronics—(LCB7141)                    | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Solid-State Electronics—3rd edition (LCB3361)      | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Digital Electronics—(LCB3311)                      | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Microprocessors—(LCB4023)                          | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Calculator Math—(LCB3321)                          | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Communications Systems—(LCB4521)                   | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Computer Science—(LCB5471)                         | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Optronics—(LCB5472)                                | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Automotive Electronics—(LCB5771)                   | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Electronic Security Systems—(LCB7201)              | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Electronic Control of Energy Systems—(LCB6642)     | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Electronic Control of Automation Systems—(LCB6641) | _____    | @ \$6.95  |
| <input type="checkbox"/> Understanding Data Communications—(LCB7981)                      | _____    | @ \$6.95  |
| <b>Self Study Courses:</b>  |          |           |
| <input type="checkbox"/> AC Audio (LCB6651)/AC Text (LCW8168)                             | _____    | @ \$24.95 |
| <input type="checkbox"/> DC Audio (LCB5922)/DC Text (LCW8161)                             | _____    | @ \$24.95 |

Mail to:

Texas Instruments  
P.O. Box 3640, M/S 54  
Dallas, Texas 75285

Add \$1.25 per book for postage and handling. Prices subject to change without notice.

Enclose check or money order with sales tax (except AK, DE, NH, OR). Foreign orders must be in U.S. dollars and include shipping charges. No phone orders, please.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

27-2116 ©1984 TI RE884

is used as the external-signal input.)

The COUPLING switch selects either TV-V or AC (external DC) coupling. TV-V coupling is used mainly to view composite-video signals. The other position allows AC coupling (if internal triggering is chosen) or DC coupling (if the EXT trigger source is chosen).

The SWEEP MODE toggle switch is used to choose between the unit's AUTO and NORM sweep modes. In the AUTO position, the sweep can be triggered by signals with repetition rates greater than 50 Hz. In the NORM position, the sweep can be triggered by signals that are within the frequency range selected by the COUPLING switch, including DC.

The front panel also contains a CAL OUT terminal that is the source of a 0.3-volt P-P squarewave at 1 kHz. While the voltage is accurate within 3%, the signal cannot be used for frequency measurements—the frequency of the calibration signal is accurate only within 50%. It can, however, be used for probe compensation.

On the rear panel of the SS-5702 are several connectors. There is a four-position plug that is used to select the line voltage (90–110, 104–128, 194–238, and 207–257 volts P-P). A ground connector and an AC line input connector (a cable is supplied with the unit) are also on the rear panel, as is the Z-AXIS INPUT BNC connector. That Z-axis input is used to modulate the intensity of the trace. That is very useful for frequency measurements: You can compare a signal of unknown frequency (applied to the Z-AXIS INPUT jack) to an adjustable signal of a known frequency (applied to the horizontal amplifier). The unknown frequency can be determined by the number of segments (or blanks) on the trace and the frequency of the known signal.

An X-Y mode is also available on the SS-5702. Applications of the X-Y mode include comparing the phase of two signals by displaying a *Lissajou* pattern.

### Usability

The front panel's neat layout makes finding the right control easy—even if you've never used the scope before. Not only are the controls grouped according to function—for example, the TRACE ROTATION, INTEN, FOCUS, and SCALE-illumination controls are all located under the CRT—but a two-tone panel helps make

the groupings even more evident.


Two probes are included with the SS-5702. Each has a slide switch that selects attenuation factors of 1 or 10. A convenient ground lead is located at the tip end of the probe. An "arrow tip" (what we would call a mini-hook clip) is included as a probe accessory. An adjustable capacitor for probe compensation is located in the BNC-connector assembly.

A tilt bail, included at the oscilloscope's base, makes using the unit on a work bench easier.

The instruction manual, although better than some we've come across, is the

weak point of the SS-5702. It includes the usual specifications and operating instructions. Sections on maintenance (including a troubleshooting guide, performance check, and parts-placement diagrams) are also included, as are calibration instructions, schematics, and a parts list. Our complaint about the manual is that it is obvious that it is translated from the Japanese language. There are numerous misspellings, and "sentences" with bad grammar. (Magazine editors are sensitive to those things.) But the manual is usable and shouldn't cause too much  
*continued on page 30*
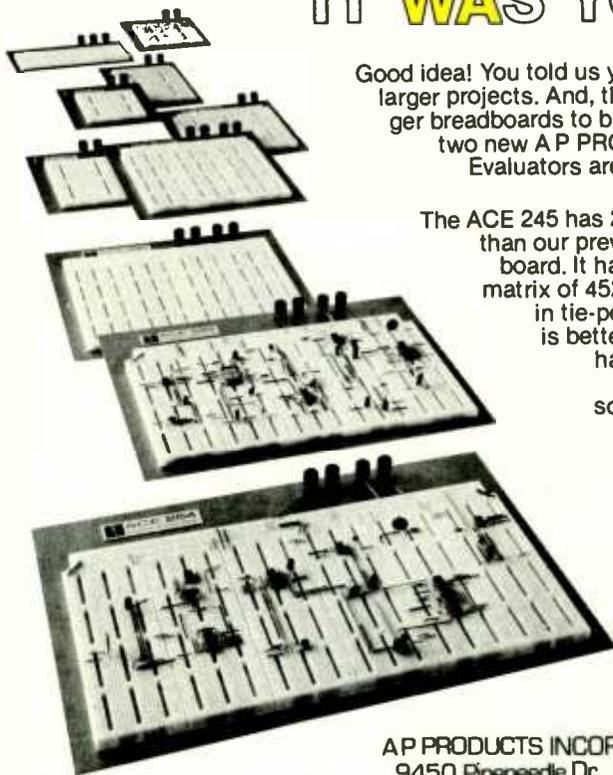
## IT WASN'T OUR IDEA TO ADD TWO NEW SIZES TO OUR LINE OF ACE BREADBOARDS. IT WAS YOURS.



Good idea! You told us you wanted to build larger projects. And, that you needed bigger breadboards to build them. Well, our two new A P PRODUCTS All Circuit Evaluators are just what you had in mind.

The ACE 245 has 25% more capacity than our previous largest breadboard. It has a circuit building matrix of 4520 solderless, plug-in tie-points. And, if bigger is better our new ACE 254 has a circuit building matrix of 5424 solderless tie-points.

For the  
A P PRODUCTS  
dealer near you  
call TOLL FREE  
800-321-9668.  
(In Ohio, call  
collect  
(216) 354-2101.)

A P PRODUCTS INCORPORATED  
9450 Pineneedle Dr. • Box 540  
Mentor, Ohio 44060  
(216) 354-2101  
TWX: 810-425-2250



In Europe, contact A P PRODUCTS • GmbH  
Bäumlesweg 21 • D-7031 Weil 1 • West Germany

CIRCLE 87 ON FREE INFORMATION CARD



# Heathkit instruments. Some buy



## Professional specs for serious users

- 1 IG-4244 Scope Calibrator. <math>< 1\text{ ns}</math> rise time. 0.015% tolerance.
- 2 IO-4205 Dual-Trace 5 MHz Scope. Low cost, 10mV/cm sensitivity
- 3 IT-2232 Component Tracer. Checks parts and circuits without energizing them.
- 4 IP-2718 Power Supply. One fixed 5 VDC and two adjustable 20 VDC supplies.
- 5 IG-1271 Function Generator. Sine, square, triangle waveforms. 0.1 Hz to 1 MHz.
- 6 IG-1277 Pulse Generator. Pulses from 100 ns to 1 sec width.
- 7 IT-5230 CRT Tester. Tests, cleans, restores CRT's.
- 8 IM-2264 DMM. True RMS readings of AC voltages. Analog metering, too.
- 9 IM-2420 Frequency Counter. 5 Hz to 512 MHz. 25 mV RMS guaranteed, 4 to 15 mV typical. Ovenized oscillator. Has period and frequency modes, too.
- 10 IM-2215 Hand-held CMM. Five DC V ranges. Accuracy:  $\pm 0.25\%$  of reading + 1 count.
- 11 IT-2250 Capacitance Meter. 199.9 pF to 199.9 mF. 0.2% basic accuracy. Auto ranging.
- 12 IO-4360 Scope and IOA-4200 Time/Voltage Module. Our finest. Triple trace, 60 MHz,  $< 7\text{ ns}</math> rise time. Revolutionary IOA-4200 controls CRT cursor and multi-function display.$

**them for pride...some, to save money.**



The time you spend at your test bench makes you a professional, whether you're pursuing a proud hobby...or earning a living.

So don't trust the accuracy of your measurements to anything less than the instruments that are built and used by professionals. Heathkit instruments.

Our products are designed, from the handles up, as kits. The parts and chassis are a little bigger, more rugged, more accessible. Most have calibration standards built in so you can do that job yourself – accurately, conveniently, at no charge. This makes our instruments superior to smaller, “disposable” varieties that discourage self-servicing.

Performance is superior, too. Check the specs on our new IO-4360 Scope and IOA-4200 Time-Voltage Module. View  $\geq 90$  MHz waveforms and get simultaneous cursor-controlled readout of Hz, period, pulse width and  $\pm$  DC voltage!

Get reacquainted with our full line. Bench, portable and hand-held instruments, from lab grade to hard working economy models.

These instruments are built by experienced hands. Your hands. So they'll save you money, give you confidence and help you do a better job. Heathkit instruments. Don't trust your pride or money to anything less.



**Heathkit instruments.  
The professional  
instruments.**

**more  
measurement  
for your  
money**

**Heathkit<sup>®</sup>**  
Heath  
Company



Take another look at the instruments you should be building.

**FREE**  
**COLOR HEATHKIT CATALOG**

Mail this coupon to:  
Heath Company, Dept. 020-204  
Benton Harbor, MI 49022

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

GX-394

# At CIE, you get electronics career training from specialists.



**If you're interested in learning how to fix air conditioning, service cars or install heating systems— talk to some other school. But if you're serious about electronics... even earning an Associate Degree... come to CIE —The Electronics Specialists.**

## Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

Be sure to shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type—with serious career goals in electronics—take a close look at what we've planned for you at CIE. **What you should look for first.**

Part of what makes electronics so interesting is it's based on scientific discoveries—on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them—before you start using them!

### How practical is the training?

This is the next big important question. After all, your career will be built on what you can do—and on how well you do it.

Here are ways some of CIE's career courses help you get your "hands-on" training...

### With CIE's Personal Training Laboratory...

you learn and review the basics—perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!

**When you get your own 5MHz, solid-state oscilloscope**, you take some real professional steps. You use it as a doctor uses an X-ray machine—to "read" waveform patterns...lock them in...study, understand and interpret them!

**When you get your Digital Learning Laboratory**, you'll

be into digital theory—essential training today for anyone who wants to keep pace with the state of the art of electronics. With CIE's Digital Lab, you'll be applying in dozens of fascinating ways the theory you've learned. For example, you'll compare analog and digital devices. You'll learn to make binary to decimal conversions and to work with semiconductor devices and circuits. You'll see how digital equipment is vital to today's exciting, growing fields such as security... where digital theory provides the brains for space-age alarm and protective devices. **You'll build your Microprocessor Training Laboratory**, a working microcomputer—from "scratch." You'll also learn how to program and interface it with displays, memories, switches, and more.

### Earn An Associate Degree from CIE.

One of the best credentials you can have in electronics—or any other career field—is a college degree. That's why CIE gives you the opportunity to earn an Associate in Applied Science


in Electronics Engineering Technology. Any CIE career course can offer you credit toward the degree...more than half of the number needed in some cases.

You can also prepare for the government-administered FCC (Federal Communications Commission) Radiotelephone License, General Class. It can be a real mark in your favor... government-certified proof of your specific knowledge and skills.
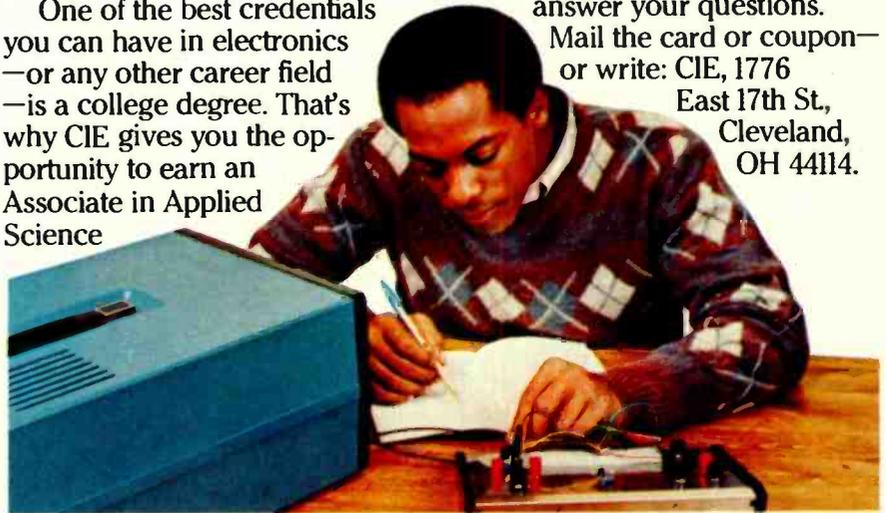
### Shop around...but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog—plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions.

Mail the card or coupon—or write: CIE, 1776 East 17th St., Cleveland, OH 44114.



## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

YES... I'm shopping around for the right kind of career training in electronics—and CIE sounds well worth looking into. Please send me my FREE CIE school catalog—including details about the Associate Degree program—plus my FREE package of home study information!

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_

Check box for G.I. Bill information:  Veteran  Active Duty

**MAIL TODAY!**

RE 90

## EQUIPMENT REPORTS

continued from page 23

confusion.

Some people might complain that the scope should have a polarity switch for both vertical channels; or that the calibration frequency should be more accurate, or that the scope should have provision for being powered by, say, 12 volts DC. (That is, incidently, an option). But with the SS-5702's list price of \$535, we're not complaining. R-E

## Regency Scanner Model Z30 Programmable Scanner

Listen in on the  
excitement of the  
public-service bands

CIRCLE 102 ON FREE INFORMATION CARD



# CEI DELIVERS ET NOTHING BUT THE BEST- AND FOR LESS!

CALL  
for your  
FREE CATALOG!



ET REPLACEMENT SEMICONDUCTORS  
ONLY AT CEI  
YOUR COMPLETE ELECTRONIC PARTS  
SOURCE

1-800-543-3568

NATIONAL WATS



1-800-762-3412

OHIO WATS

CONSOLIDATED ELECTRONICS INC.

705 WATERVLIT AVE. DAYTON, OHIO 45420 [513] 252-5602

TELEX: 288-229

CIRCLE 18 ON FREE INFORMATION CARD

THERE'S A LOT OF ACTIVITY AND EXCITEMENT to be found on the VHF and UHF bands. Police, fire, government, mobile telephone, amateur radio, and many other services use that portion of the spectrum for communications, and listening in on those communications has become a popular pastime.

Because of the wide range of frequencies we are dealing with, and because some exciting activity can be taking place on any one or more of those frequencies at any time, the most effective way to listen in is with a scanning radio. One such radio that we recently had a chance to examine is the Regency Electronics (7707 Records St., Indianapolis, IN 46226) model Z30 programmable scanner.

That unit is a programmable 30-channel, three-band, FM scanner receiver. It also incorporates a digital alarm clock. It can be powered from either the 117-volt line or from a 12-volt negative-ground DC supply such as found in a car, truck, or boat. To simplify mobile installation, a DC power cord is included. Also included is a detachable telescopic antenna.

The unit is compact, measuring  $10\frac{3}{4} \times 2\frac{7}{8} \times 8\frac{3}{8}$  inches, and weighs  $2\frac{3}{4}$  pounds. It is housed in a brown plastic case, with a simulated wood-grain finish.

Turning to the receiver itself, it is a double-conversion, superheterodyne circuit. It receives narrow-band FM communications over three bands: 30-50, 144-174, and 440-512 MHz. The unit boasts a sensitivity that varies by frequency from 0.7 to 1.5  $\mu\text{V}$  (12 dB Sinad, maximum), and a selectivity of  $\pm 7.5$  kHz at 6 dB and  $\pm 18$  kHz at 50 dB.

### Use

Aside from an ON/OFF switch and VOLUME and SQUELCH slide controls, all functions and frequencies are entered using a front-panel keypad called the Program Panel. (As you would expect in a unit of this type, except for the one used as a reference, there are no crystals. Instead, a microprocessor-controlled frequency synthesizer is used.)

The keys on the Program Panel are grouped into two types: the mode keys and the program keys. The mode keys are

used to place the unit in one of its various modes. They are also used to activate or deactivate the unit's special features and to control the built-in alarm clock. The program keys are used for entering frequencies and for selecting the channel number during programming.

Frequencies, channel numbers, and the time of day during periods that the unit is turned off, are displayed on a blue vacuum-fluorescent readout. In addition, the

Regency	Z30									
OVERALL PRICE	1	2	3	4	5	6	7	8	9	10
EASE OF USE	1	2	3	4	5	6	7	8	9	10
INSTRUCTION MANUAL	1	2	3	4	5	6	7	8	9	10
PRICE/VALUE	1	2	3	4	5	6	7	8	9	10
	1	2	3	4	5	6	7	8	9	10
	Poor	Fair	Good	Excellent						

readout can display a variety of prompting messages to alert the user to a particular condition. For instance, if the frequency entered is not within one of the bands that the unit covers, a FR ERR message is displayed. Also, a variety of annunciators are used to alert the user to which special functions and features are active. Finally, the brightness of the display can be controlled using the DISPLAY DIM key.

The unit has three primary modes of operation: search, scan, and manual. The search mode is used to find new frequencies. To use that mode, the PROGRAM key is pressed and upper and lower search limits are entered. Once that is done, the search is initiated by pressing the SEARCH key. The band of frequencies selected is then searched continuously in 5-kHz (VHF) or 12-kHz (UHF) increments.

Once you have found a frequency of interest, it can be entered into the unit by placing it into the manual mode. Entering frequencies is a very simple operation. It involves merely pressing the MANUAL key, entering the frequency using the program keys, pressing the ENTER key, and finally entering the channel (from 1 to 30) that you want the frequency stored in.

After you have programmed the frequencies of your choice, they can be scanned automatically by using the scan mode. That mode is entered by pressing the SCAN key.

The Z30 has several special functions that are designed to give the unit maximum flexibility. In the scan mode, you may want to delay the resumption of scanning after activity on a channel has ended so that you might hear a reply that might otherwise be missed. Pressing the DELAY key causes the unit to pause for about 2 seconds before resuming the scan. In the

search mode, the DELAY key is used to select between a 4-second delay and a hold function. If the hold function is selected, the unit will remain on a previously active frequency until either the SEARCH or DELAY key is pressed. (Note that pressing the DELAY deactivates the hold function.)

Other special functions include a priority mode that lets you sample a favorite frequency every two seconds during the scanning process. Channel 1 has been set aside for that function. A channel-lock-out feature lets you force the scanner to skip over any channel that you select.

The manual that accompanies the unit is, as you would expect, pretty much just an instruction manual. It covers the operation of the unit in step-by-step fashion, but has little in the way of technical details such as theory of operation, schematics, parts lists, or parts-placement diagrams. In fact, the company discourages any user adjustments by stating that such unauthorized adjustments will invalidate the unit's one-year warranty. One bit of useful information that is provided is a list of national frequency allocations. The model Z30 sells for \$269.95. **R-E**

*continued on page 32*

# Introducing the analog/digital handheld multimeter.



**Fluke 73**  
**\$85**

Analog/digital display  
Volts, ohms, 10A, diode test  
Autorange  
0.7% basic dc accuracy  
2000+ hour battery life  
3-year warranty

**Fluke 75**  
**\$99**

Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
Autorange/range hold  
0.5% basic dc accuracy  
2000+ hour battery life  
3-year warranty

**Fluke 77**  
**\$129**

Analog/digital display  
Volts, ohms, 10A, mA, diode test  
Audible continuity  
"Touch Hold" function  
Autorange/range hold  
0.3% basic dc accuracy  
2000+ hour battery life  
3-year warranty  
Multipurpose holster

FROM THE WORLD LEADER  
IN DIGITAL MULTIMETERS



The Professional Test Equipment Source



**The Instrument Mart**

295 Community Drive, Great Neck, New York 11021  
(516) 487-7430 Outside N.Y. (800) 645-6535

Sales, Service, Rental/Leasing Programs  
... and Pre-Owned Test Equipment also Available



CIRCLE 28 ON FREE INFORMATION CARD



# THE DRAWING BOARD

## Finishing the sinewave generator!

ROBERT GROSSBLATT

THIS MAY SEEM HARD TO BELIEVE, BUT we've just about reached the end of our discussion on digital sinewave generators. This month we're going to put a lid on the whole thing and take a look at the bits and pieces that have to be added to make a working unit. If you have been following along the last couple of months, you know that all that's left to do is to select an oscillator for the front end and a filter for the back end. Let's take care of the rest of the design and then talk a little bit about the advantages that come your way by generating sinewaves with digital, rather than analog circuitry.

If you were to single out the most often designed (or redesigned) circuit in the history of electronics, the oscillator would win hands down. The reason for mentioning that is to point out that it would be a waste of brain power to sit down and design a special one for our application.

Our requirements are sufficiently simple to make use of most existing general-purpose oscillator circuits. All we need is something that is easily tunable over a 1000:1 range, has good stability, is foolproof, and has a garbage-free output. The bells and whistles would include an adjustable pulse-width, minimum parts count, low power consumption, and so on. But first we must select an oscillator!

### Oscillator circuit

Obviously, the first thing that should come to mind is the venerable 555 timer. Not only is it easy to use, but the design equations are simple to apply. And if power requirements are really a problem, we can use the CMOS version (7555). Both parts also satisfy another unspoken design criteria. That is, they are common enough to be found almost everywhere except in a box of *Cracker Jacks*.

Figure 1 shows the basic circuit layout for an oscillator using a 555 timer. We are looking at one IC and four components—not a whole lot of parts. Now, there is absolutely no doubt (in my mind) that all of you out there know everything there is to know about the 555; but just to make sure, let's go through the circuit, equations, and the math.

The first thing that must be realized is that the output duty-cycle will not be exactly 50%. With the circuit in Fig. 1, we

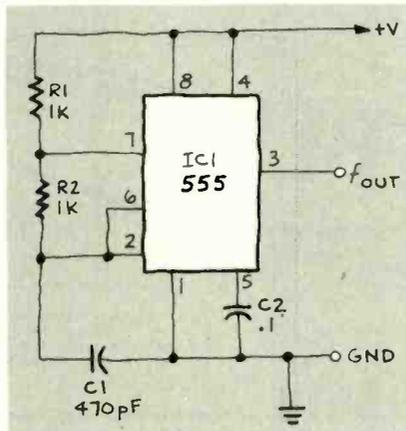


FIG. 1

capacitor C1 charges up until the voltage across it reaches about  $\frac{2}{3}$  of the supply. At that point the internal transistor turns on providing a discharge path for capacitor C1 through resistor R2, while the flip-flop changes states and the IC's output goes low. When the capacitor voltage gets down to about  $\frac{1}{3}$  of the supply, the flip-flop again changes states and the transistor turns off. Capacitor C1 starts to charge up again through both R1 and R2.

Now that we understand what determines the duty cycle of the basic 555 oscillator, a quick look at some of the design equations for the IC will show you what has to be done to square up the duty

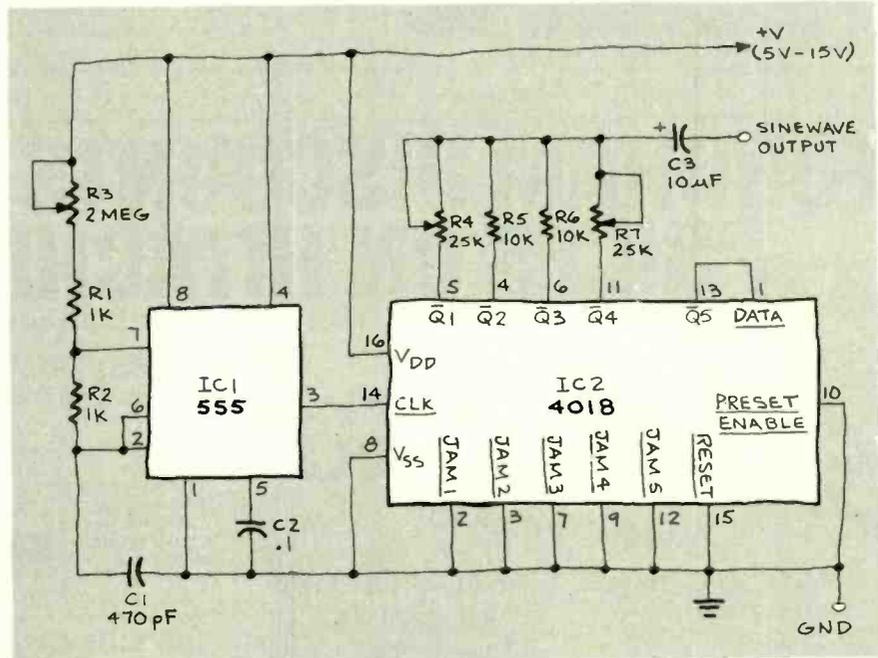


FIG. 2

can get extremely close to 50%, but never quite reach it. The reason for that is capacitor C1 charges up through resistors R1 and R2, but discharges only through R2. If you were to look inside a 555, you would see that there's a transistor handling the discharge half of the cycle and that its collector is connected to pin 7 of the IC. Its emitter is connected to ground and the base sits on the output of an internal flip-flop.

When the output of the 555 is high,

cycle. Because we're looking at a series R-C timing circuit, the equations related to the duty cycle will be as follows:

$$\begin{aligned} \text{high time} &= K(R1 + R2)C1 \\ \text{low time} &= K(R2)C1 \end{aligned}$$

The "K" in the formula is a constant, which we'll get to in a minute. But for now, we can ignore it because when we calculate the duty cycle, we'll see that

*continued on page 36*

# UNGAR DESOLDERING & SOLDERING

## Special Pricing... Special Free Offer

### Hot VAC Desoldering System



Model 4000

Built-in vacuum pump eliminates the need for shop air. Compact design and portability make it ideal for use at any location where there is an AC electrical plug-in outlet.  
**Self-Contained, Super-Quiet Air Pump:** The vacuum pump is not only virtually maintenance free, it is remarkably quiet. The pump operates only when the handle switch is actuated.  
**Temperature Control:** Variable solid-state control that adjusts the tip temperature from 500° - 1000°F. An electric circuit assures that transient spikes are fully suppressed thereby making the system safe for desoldering voltage-sensitive components.

Reg \$599.95  
**OUR SPECIAL PRICE**

**\$379<sup>95</sup>**

### Electronic Temperature Controlled Soldering System with Built-in Controller

**OUR SPECIAL PRICE \$89<sup>95</sup>**



Model 9100

Includes: base unit with built-in controller, micro-size handle with THERMO-DURIC heater, 1/16" #9012 screwdriver tip, sponge and tip tray, sponge, and Iron Holder. A low cost alternative in an operator-adjustable, temperature controlled soldering system.  
 • Electronic, closed-loop temperature control for maximum precision • Temperature is operator-adjustable from 400 F to 800 F • Continuous, variable control so you can select the exact temperature you need • Neon "on-off" light • Iron Holder can be right- or left-hand mounted to accommodate all operators.

**FREE UNGAR 9100**  
 with purchase of  
 Ungar 4000

TOLL FREE (800) 645-9518

**FORDHAM**  

260 Motor Parkway, Hauppauge, N.Y. 11788

in N.Y. State 800-832-1446  
 ■ VISA ■ COD ■ Master Charge  
 ■ Money Order N.Y. State residents add appropriate sales tax.  
 ■ Check  
 COD's extra (required 25% deposit)

**ADD FOR SHIPPING AND INSURANCE**  
 \$250.00 ..... \$4.50  
 \$251.00 to 500.00 ..... 6.50  
 501.00 to 750.00 ..... 8.50  
 751.00 to 1000.00 ..... 12.50  
 over 1000.00 ..... 15.00

# FORDHAM DISCOUNTS DISCOUNT PRICES ON HITACHI SCOPES

We will beat any advertised price

**SPECIAL OFFER!**  
*For a limited time only*

### 35 MHz DUAL TRACE SIGNAL DELAY LINE

Vertical sensitivity 5m V/div to 5V/div and 1m V/div to 1 V/div with 5X amplifier • Trigger modes Auto-matic, Normal, TV (+), TV(-).



V-355F

REG \$895  
**OUR PRICE**  
**\$599<sup>95</sup>**  
 WITH PROBES

### 60 MHz DUAL TRACE DELAYED SWEEP

High sensitivity • 1 mV/div (10 MHz) • 5 ns/div sweep rate  
 • 3rd channel display (trigger view) • Variable trigger hold-off  
 • Full TV triggering • Single sweep • Auto-matic focus correction.

**OUR PRICE**  
**\$995**  
 WITH PROBES




Model 650F

### 100 MHz QUAD TRACE DELAYED SWEEP

Large, bright 8x10 cm screen  
 • Quad trace operation/Ch1, Ch2, A trigger and B trigger • High sensitivity 500 μ V/div (5 MHz)  
 • Full TV triggering.

**OUR PRICE**  
**\$1299<sup>95</sup>**  
 WITH PROBES

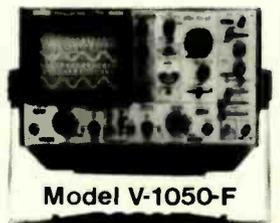

Model V-1050-F

TOLL FREE (800) 645-9518

**FORDHAM**  

260 Motor Parkway, Hauppauge, N.Y. 11788

in N.Y. State 800-832-1446  
 ■ VISA ■ COD ■ Master Charge  
 ■ Money Order N.Y. State residents add appropriate sales tax.  
 ■ Check  
 COD's extra (required 25% deposit)

**ADD FOR SHIPPING AND INSURANCE**  
 \$250.00 ..... \$4.50  
 \$251.00 to 500.00 ..... 6.50  
 501.00 to 750.00 ..... 8.50  
 751.00 to 1000.00 ..... 12.50  
 over 1000.00 ..... 15.00

# SUPERSALE

We will beat any advertised price

## BECKMAN Circuitmate® DMM

MODEL DM73  
**\$63<sup>95</sup>**

• Smallest digital multimeter on the market • Probe-style design makes it ideal for taking measurements in hard-to-reach test areas.



**\$64<sup>95</sup>**

• 3½-digit, pocket-size multimeter • 0.8% Vdc accuracy • diode test • hFE test • conductance • 10 amps AC and DC ranges • Autopolarity • Auto-Zero • Auto-decimal.



**\$79<sup>95</sup>** MODEL DM25

• 3½-digit, pocket-size multimeter • 0.5% Vdc accuracy • diode test • capacitance • continuity beeper • conductance • 10 amps AC and DC ranges • auto-polarity • auto-zero • auto-decimal.



## B&K PRECISION

### 100 MHz FREQUENCY COUNTER



MODEL 1803  
REG. \$169.95 **OUR PRICE \$144<sup>50</sup>**

• 5 Hz to 100 MHz range • 8 digit LED display • Leading zero blanking • Low pass filter • BNC Connector Input • Overflow indicator • Battery or AC powered • Charger/AC Adaptor included with Model 1803.

### NTSC COLOR BAR GENERATOR

MODEL 1251  
REG. \$995.00

**OUR PRICE \$849<sup>95</sup>**



• Generates a wide variety of test signals and patterns for comprehensive testing, servicing and adjustment of virtually all types of television and video equipment • Video patterns include standard NTSC color bars, -1W0, and staircase at two levels of burst phase chrominance • A full assortment of convergence patterns, raster colors gated or full field multiburst.

## HITACHI PORTABLE OSCILLOSCOPES

MODEL V-222 (20 MHz)  
REG. \$695.00



MODEL V-422 (40 MHz)  
REG. \$895.00



## CALL FOR SPECIAL PRICING

• New series of scopes provides high performance and light weight • Large 6-inch rectangular, internal graticule CRT • Autolocus circuit and scale illumination • DC offset function • Voltage and frequency reading outputs • High accuracy - ±3% • High sensitivity - 1 mV/div.

## BP DIGITAL CAPACITANCE METER



MODEL DCM-601  
REG. \$149.95

**OUR PRICE \$79<sup>95</sup>**

• Digital display easy and correct readout • High accuracy, 100 PPM 0.5% • LS-circuit provides high reliability and durability • LCD display provides low power consumption.

## FORDHAM 550 MHZ FREQUENCY COUNTER



MODEL FM-8  
REG. \$199.95 **OUR PRICE \$149<sup>95</sup>**

• 8-digit high frequency counter with a switch selectable input using single BNC • Completely assembled • Pre-Calibrated, Pre-tested.

## LEADER NTSC WAVEFORM MONITOR



MODEL LBO-5860 **OUR PRICE \$1850**  
REG. \$2050.00

Permits displaying vertical interval test and reference signals by front panel line selector.



NTSC VECTORSCOPE  
MODEL LVS-5850 **OUR PRICE \$1850**  
REG. \$2050.00

Convenient method for observing and measuring the relative phase and amplitude of chrominance signal components.

## FLUKE 70

• Analog Display • Rotary Knob • Volts AC & DC • Resistance to 32 MΩ • 10 Amps • Diode Test • 3200 Counts • Fast Autoranging • Function Annunciators in Display • Power-Up Self Test • 2000+ Hour Battery Life w/Power Down "Sleep Mode" • New Test Leads • VDE & UL Approval

75 **\$95<sup>00</sup>**

• 0.5% Accuracy • Manual or Autorange • 10A + 300 mA Range • Beeper



73

**\$74<sup>95</sup>**

• 0.7% Accuracy • Autorange Only • 10 Amp Only



77 **\$125<sup>00</sup>**

• 0.3% Accuracy • Manual or Autorange • 10A + 300mA Range • Beeper • "Touch-Hold" Function



## VIZ DC TRIPLE POWER SUPPLY

MODEL WP-708  
REG. \$489.00

**OUR PRICE \$399<sup>95</sup>**

• Dual DC Voltmeter • Triple DC Power Supply • Three separate completely isolated DC power supplies, two 0-20V at 0-2A, one fixed 5V at 4A



## WELLER SOLDERING STATION

MODEL EC1000  
OUR PRICE **\$109<sup>95</sup>**

• Identical to the EC2000 except LED Digital temperature readout • The EC1000 is dial controlled.

## SOLDERING STATION

MODEL EC2000  
OUR PRICE **\$139<sup>95</sup>**

• Continuously variable tip temperature from 350 to 850 F • Positive temperature coefficient sensor inside the tip provides temperature feedback to maintain tip temperature at a set point.



# FORDHAM

260 Motor Parkway, Hauppauge, N.Y. 11788

Master Charge  
VISA  
Money Order  
Check

N.Y. State residents add appropriate sales tax.

ADD FOR SHIPPING AND INSURANCE:  
\$0-\$250.00 ..... \$ 4.50  
\$251.00 to \$ 500.00 ..... \$ 6.50  
\$501.00 to \$ 750.00 ..... \$ 8.50  
\$751.00 to \$1000.00 ..... \$12.50  
over \$1000.00 ..... \$15.00

TOLL FREE  
**(800) 645-9518**  
in N.Y. State call 800-832-1446

Free Catalog on Request

# cable tv

## DESCRAMBLER PARTS

We stock the exact parts and PC Board for Radio Electronic's February Article on building your own Cable TV Descrambler.

**#701 PARTS PACKAGE ..... \$29.95**

Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, coils and IF transformers (BKAN-K5552AXX).

**#702 PC BOARD ..... \$12.95**

Original etched & drilled silk-screened PC Board used in the article.

**#704 AC ADAPTOR ..... \$12.95**

(14 volts DC @ 285MA)

**Both #701 & #702 ..... \$39.00**

**FREE!!** Reprint of Radio Electronics Article on Building Your Own Cable TV Descrambler with any purchase.

Add \$4.00 Postage & Handling

**TOLL FREE (24 HRS.)**

**1-800-522-1500 Ext. 708 (Orders Only)**

(9am to 5pm) 1/617-339-5372 (Information)

# J & W ELECTRONICS, INC.


P.O. Box 52  
Cumberland, RI 02864

CIRCLE 45 ON FREE INFORMATION CARD
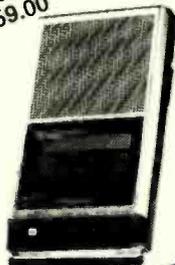
## SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00\*  
14 Hour Model — \$159.00\*

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 5 or 7 continuous hours of quality recording & playback on each side of cassette for a total of 10 or 14 hours depending on model. Built-in features include: Voice level control, Digital counter, etc. TDK DC 180 Cassette Furnished.



### PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. **\$24.50\***



### VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. **\$24.95\***



\*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA, M/C, COD's OK. Money Back Guarantee. Qty. disc. avail. Dealer Inquiries invited. Free data.  
**AMC SALES INC.** Dept A 9335 Lubec St., Box 928, Downey, CA 90421 (213) 868-8519

CIRCLE 67 ON FREE INFORMATION CARD

## DRAWING BOARD

continued from page 33

"K" takes care of itself and disappears.

$$\begin{aligned} \text{duty cycle} &= \text{high time/low time} \\ &= K(R1 + R2)C1 / K(R2)C1 \\ &= (R1 + R2) / R2 \end{aligned}$$

The duty cycle is controlled by the value of the two resistors (R1 and R2), so we can approximate 50% by making R1 really small when compared to R2. A ratio of up to two or three thousand to one is perfectly workable. The frequency of the oscillator, as we all know, is just the reciprocal of the period (or one divided by the period). Rather than just throw formulas at you, let's briefly reason the whole thing out.

$$\begin{aligned} \text{period} &= \text{high time} + \text{low time} \\ &= K(R1 + 2R2)C1 \end{aligned}$$

The frequency (f) is therefore:

$$f = 1 / K(R1 + 2R2)C1$$

For the circuit shown in Fig. 1, the value of "K" is about .695. That value comes about because the 555's internal comparator is set to trigger at 2/3 of the supply voltage. The actual math to derive that value is far from being interesting but, if you want to, you can check it out in any good data book that includes the 555 timer. You can set the trigger level higher by applying a DC voltage to pin 5, but for our application it's not needed. Besides, we can bypass it with C2 to help make the circuit a bit more immune to noise. Now, let's move on to the sinewave generator.

### Generator circuit

The original design criteria we set up for the sinewave generator called for an output range of 100 Hz to 100 kHz. Since the 4018 is dividing by ten, the range of the oscillator must be 1 kHz to 1 MHz. Because the upper limit of the 555 is just around 1 MHz, we should be all right.

Figure 2 is the layout for the complete sinewave generator with all the values shown. You can plug your own numbers into the formulas we've just described and change anything you want. Nothing is engraved in stone and, to tell the truth, you'll learn much more if you experiment with different value components.

Potentiometer R3 serves as the frequency selector, making the 555 tunable from about 1 kHz to 1 MHz. I say "about" because it's impossible to find standard value parts that will plug into a formula and give you exactly the results you want.

Resistors R4 through R7 are the famous ones we spent so much time examining. They determine the shape of the wave

you're going to get from the 4018. As shown, the fixed resistors are set at 10,000 ohms; and trimmers were used for the Q1 and Q4 outputs, because the value we want for each of them is calculated to be 1.617K—not exactly a standard value!

Not only that, but the strange resistor value is correct only if the fixed resistors are exactly 10,000 ohms. Since we all routinely use 5%- or 10%-tolerance resistors, the best thing to do is take two 10,000-ohms units, measure them (out of circuit), and then do the arithmetic necessary to find the value for the two trimmers. After you set the trimmers, it might be a good idea to put a drop of lacquer (or nail polish) on the turn screws to hold them in place.

The output filter is just a 10-μF capacitor. It should work well enough to smooth the wave out for most applications. However, if you feel that it does not fulfill your needs, by all means substitute some other type filter. Harmonics are not going to be much of a problem because they're quite a bit above the fundamental frequency and they are a good deal smaller in amplitude.

You may wonder what's so great about generating sinewaves digitally. Well, there are several advantages: good stability, low-power requirements, no complicated R-C setups, and so on. As far as I'm concerned though, the biggest advantage is that you can easily and reliably generate frequencies (of any precision) even well below 1 Hz. Since the input clock is running ten times higher than the output of the 4018, you can produce frequencies down around .0001 Hz. Try doing that with capacitors!

The output of the whole generator can be fed into anything you want from a simple buffer to an amplifier: What you use depends on what you want to do. An op-amp would be great to use as a buffer/amplifier here. Also, we could make the gain adjustable, and so on. But wait a minute: Op-amps need a bipolar supply and all that is available in our circuit is a single-sided one!

That's quite a problem—or is it? R-E




"John and I had a big row, so all last night he played this videotape of our wedding ceremony in reverse."

# NEW PRODUCTS

For more details use the free information card inside the back cover

**TOOL KIT**, model *JTK-87*, is a deep polyethylene case with a removable document portfolio. A recess in the outside of the lid accommodates a locking, black, vinyl portfolio for documents and schematics. It is se-

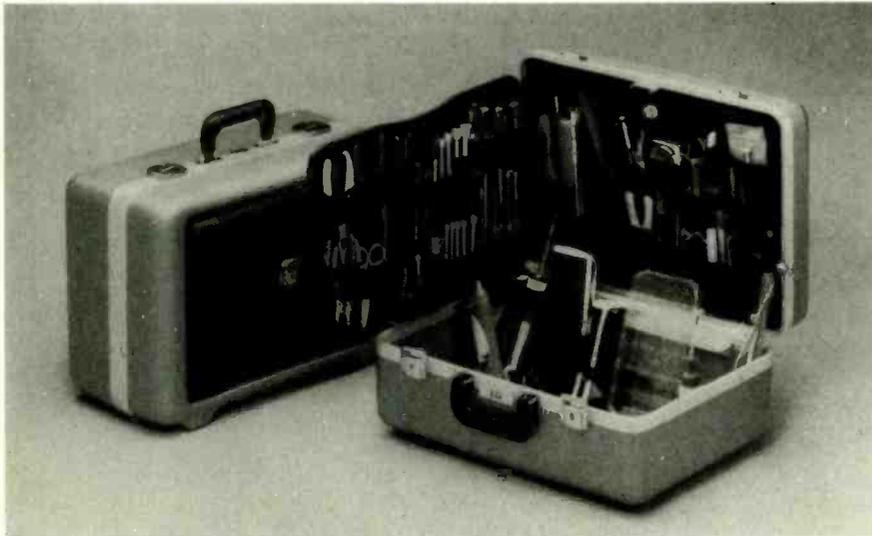The case measures 17¼ × 12¾ × 6½ inches and also features two removable gate-swung pallets. That permits easy access to tools, parts, and equipment carried in the case bottom. The model *JTK-87* is available




CIRCLE 111 ON FREE INFORMATION CARD

cured to the lid with velcro fasteners, and can be detached when necessary to do paperwork while traveling, or slipped into the case for shipping.

with a selection of over 100 tools, and is priced at \$509.00. The portfolio case only is priced at \$189.00—**Jensen Tools, Inc.**, 7815 South 46th St., Phoenix, AZ 85040.

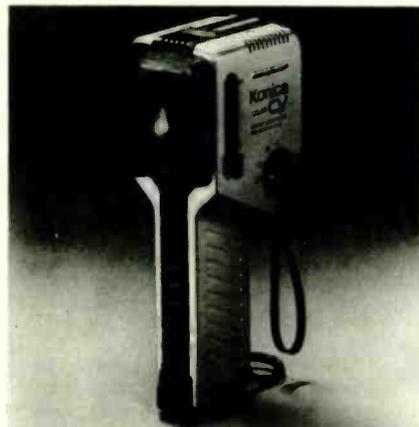**COLOR-VIDEO CAMERA**, model *CV-301*, weighs 1.6 lbs and is compatible with all VHS-format video-cassette recorders. It is adaptable to Beta-format video-cassette recorders with a standard adapter cable.



CIRCLE 112 ON FREE INFORMATION CARD

The unit delivers horizontal resolution of 270 lines; a minimum required luminance of 35 Lux; image signal-to-noise ratio of 45 dB; video-output signal of 1.0-volt p-p/75 ohms, and an audio-output level of -20 dB (1000 ohms).

Other features of the model *CV-301* include a unidirectional electret condenser microphone, and f/1.5 manual 3-to-1 zoom lens with 10 - 30mm focal length, a through-the-lens optical viewfinder with in-finder LED to indicate recording low-light and power warnings, and a light balance control to match four separate color temperatures.

The model *CV-301* has a suggested retail price of \$795.00.—**Konica, Konishiroku Photo Inc. USA Inc.**, 440 Sylvan Avenue, Englewood, Cliffs, NJ 07632.

**POWER SUPPLIES**, the *PAB-A* series, featuring 3½-digit LED readouts that are green in the voltage mode and red in the current mode. They are available in five models, with outputs ranging from 350 volts at 0.2 amperes to 5.0 amperes at 8 volts, with 0.02% regulation.

TRAIN AT HOME IN SPARE TIME!  
NO PREVIOUS EXPERIENCE NEEDED!

## FOR HOME OR BUSINESS! WHAT...WHEN...HOW



### LEARN HOW TO USE A COMPUTER

Learn how and why a computer can help you. Learn to write your own computer programs. See how easy it is to use different programs already available. See how they fit into your home or business operations...budgeting, real estate, bookkeeping, inventories, expenses, pricing, profit margins, investments, interest, taxes, shopping lists, vacation planning, addresses, phone numbers, routing...hundreds more including foreign languages, computer games and graphics. Never again be at the mercy of a so-called "computer expert." Know what really happens when you get a computer problem from a bank, store, loan company, oil company, utility or anyone else. You'll be able to talk their language...understand why and how things happen...be able to take the offensive when you're the victim of a computer error.

#### EXPERTS SHOW YOU WHAT TO DO, HOW TO DO IT...TO MAKE YOUR LIFE EASIER

Everything is explained in easy-to-understand language with plenty of examples. Step-by-step directions take you through basic computer programming. You learn everything you need to know to use the computer. You'll be able to understand computer experts and talk their language...storage, systems, terminals...you'll learn it all and much, much more.

#### NOW...ALL THIS IN ONE COURSE!

- Computer Training • Computer Programming
- Computer Applications • Computer Games

Find out what you need to know about computer operations



TIMEX COMPUTER INCLUDED WITH YOUR TRAINING  
Plugs into any TV!


SEND FOR FREE FACTS!

**ICS** COMPUTER TRAINING, Dept. DE 073  
SINCE 1891 Scranton, Pennsylvania 18515

Please rush me free facts and color brochure that tells how I can learn computer applications, programming and operation at home in spare time. NO SALESMAN WILL CALL.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City/State/Zip \_\_\_\_\_

# Radio-Electronics mini-ADS

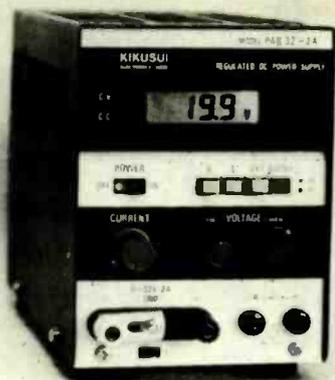

CIRCLE 113 ON FREE INFORMATION CARD

The features include constant-voltage or constant-current operation; remote-voltage programming; overcurrent protection; series or parallel operation; auto-ranging in voltage mode, and independent external-voltage readout using the supply's digital meter.

The PAB-A series has a design MTBF of over 10,000 hours, and prices range from \$175.00 to \$350.00.—Kikusui International Corporation, 17819 South Figuerola St., Gardena, CA 90248.

**DIRECT-DRIVE TURNTABLE**, model DP-15F, is a complete non-contact system that senses and corrects for record imperfections such as warps. The tonearm provides for improved tonearm/cartridge matching, because it responds to the combined tonearm/cartridge mass.



CIRCLE 114 ON FREE INFORMATION CARD

The DP-15F has a flat-twin direct-drive motor, microprocessor-controlled automatic operation with front-panel soft-touch controls, and magnetic head-speed detection.

The model DP-15F has a suggested list price of \$199.00.—Denon America, Inc., 27 Law Drive, Fairfield, NJ 07006.

**SIGNAL GENERATOR**, the model LSG-215A, is a programmable synthesized AM FM RF signal generator featuring convenient keyboard control of frequency and output level. Semi-automatic operation is available by pre-programming up to 100 different test conditions. Two kilobytes of memory stores frequency, output level, and modulation data for each test condition.

The model LSG-215A offers an output-frequency range of 0.1 to 120 MHz in two bands: 0.1 to 30 MHz in 100-Hz steps, and 30 to 120

continued on page 40



**DIGITAL BOARD TESTING COURSE**—This 18 lesson course, including lesson books, cassette tapes, and workbooks, will give you the information you need to enter the field of test engineering and to learn the latest techniques used in automatic test equipment. Earn your certificate from the Test Engineering Institute. Check/M.O./Mastercard/Visa. \$450 plus shipping. 10 DAY NO.RISK TRIAL. **Logical Solutions, Inc., 1799 S. Winchester, Suite 201, Campbell, CA 95008. (408) 374-3650.**

CIRCLE 46 ON FREE INFORMATION CARD




**SUBSCRIPTION TV MANUAL.** This information packed book details the methods used by subscription TV companies to scramble and descramble video signals. Covers the Sinewave, Gated Pulse, SSAVI system, and the methods used by most cable companies. Includes circuit schematics, theory, and trouble shooting hints. **Only \$12.95 plus \$1.50 first class P&H. Info \$2.00, refundable. RANDOM ACCESS, Box 41770-R, Phoenix, AZ 85080.**

CIRCLE 31 ON FREE INFORMATION CARD



**TELTONE'S TRK-957 KIT** makes breadboarding a low-power, central office quality DTMF detection system easy and inexpensive. The included M-957 receiver decodes 12 or 16 digits and operates from 5 to 12V dc. Its sensitivity, wide dynamic range, noise immunity, and low power consumption are ideal for telephone switching, computer and remote control applications. **Only \$24.75. To order, call: TELTONE, 1-800-227-3800, ext. 1130.**


CIRCLE 73 ON FREE INFORMATION CARD

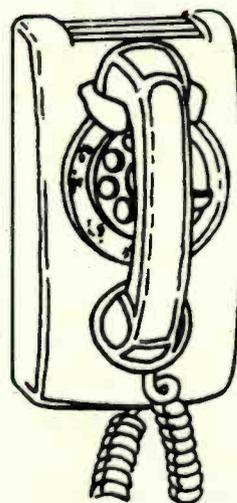
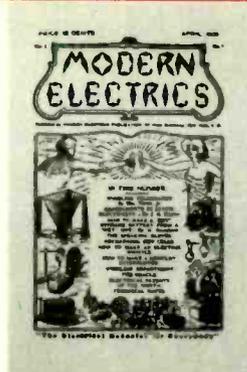
## CALL NOW AND RESERVE YOUR SPACE


- 6 x rate \$605 per each insertion.
- Reaches 215,460 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call 212-777-6400 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.



**MODERN ELECTRICS.** Miniature souvenir of the first publication ever produced by Gernsback Publications. This issue appeared in April 1908—just 75 years ago. You can own your own reprint of this unique first edition for just \$2.50 plus 75c P&H. It's available from **R-E BOOKSTORE, Radio-Electronics, 200 Park Avenue South, New York, NY 10003**

# Radio-Electronics mini-ADS

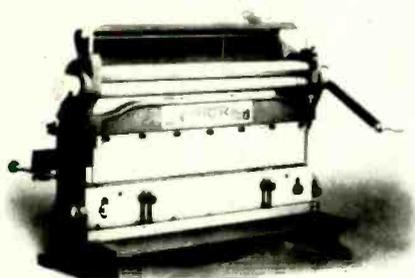

**SHEET METAL WORKER**—The 24" TRIOK is a Press Brake, Shear and Slip-roll machine—perfect for research and development or maintenance shops. Over a thousand machines world wide in little to the largest companies. For free literature on this and our other sheet metal working machines contact: **PACIFIC ONE CORPORATION, 513 Superior Ave. Suite K-410, Newport Beach, CA 92663, (714) 645-5962.**

**CIRCLE 55 ON FREE INFORMATION CARD**




**THE ULTIMATE IN VIDEO SWITCHING.** Finally a Video Switch with precision solid state electronic switching and a touch of class. "The Beta Bunny" features "one touch" control membrane panel; excellent video clarity; bright LED true position indicators; luxurious solid oak or simulated dark walnut wood enclosure; 6 inputs and 3 outputs. Kit form \$99.95, Assembled \$129.95. Add \$4.95 shipping/handling. **BETA ELECTRONICS, 2081-A 3RD ST., RIVERSIDE, CA. 92507 (714) 788-2701.**

**CIRCLE 22 ON FREE INFORMATION CARD**



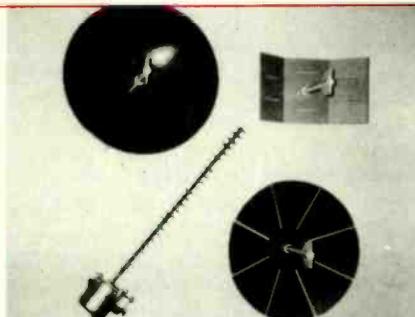**ZENITH Z-TAE CABLE T.V. Descrambler.** Brand new tag along. For Complete information and our Catalog SEND 5.00 to **R&M Distributors, P.O. Box 266-R15, Boston, MASS. 02190.**



Bring in those hard to get channels with these low priced amateur microwave T.V. receivers. **HMR Mini—\$64.95; HMR Daisy Dish—\$69.95; Spectra Dish—\$89.95; MDS 52 ROD—\$89.95.** All systems complete and fully guaranteed. Free Shipping. Cable converters call or write for quantity pricing. Add \$4.00 for COD orders. Call today. **H.M.R. Sales, 221 East Camelback, Suite 1, Phoenix, Arizona 85012, Phone 602-993-0398.**

**CIRCLE 38 ON FREE INFORMATION CARD**

## CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$605 per each insertion.
- Reaches 215,460 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call 212-777-6400 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: **mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.**




**SUPERMINI DIGITAL MULTIMETER**—8 Functions: 23 ranges; 0.5%- 0.8%; Slim Body. 22mm /0,87". DC Voltage 100uV to 1000V. AC Voltage 100mV to 750V. DC Current 100 nA to 10 A. Resistance 100 mΩ to 20 MΩ. Diode test 1mA junction voltage. hfe from 0 to 1000. 3½ digits LCD 0.5"H, AUTO ZERO POLARITY, Low Bat. INDICATOR, DIODE TEST, Transistor Hfe TEST, and CONDUCTANCE. INCL. BATTERY, Vinyl carrying case and test leads. MODEL - 108: 0.8%, \$44.95. MODEL - 105: 0.5%, \$54.95. **RENAU ELECTRONIC LABRATORY, 8465 Canoga Avenue, Canoga Park, Calif. 91304, 818-341-1994 - Telex 888 277.**

**CIRCLE 62 ON FREE INFORMATION CARD**




**FREE 1984 ELECTRONIC TOOL & INSTRUMENT CATALOG** is packed with over 5,000 quality technical products for assembling, testing and repairing electronic equipment. All products fully illustrated with photographs, detailed descriptions and pricing to allow for easy ordering by phone or mail. Most orders are shipped within 24 hours. 100% satisfaction guarantee. **CONTACT EAST, 7 Cypress Drive, Burlington, MA 01803. (617)272-5051.**

**CIRCLE 50 ON FREE INFORMATION CARD**

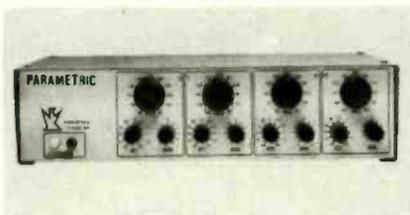

**FIX YOUR FREQUENCY RESPONSE!** The P-94-S Parametric Eq lets you dial up any center frequency from 40 Hz to 16 kHz and boost or cut anywhere from 1/10th to 2 full octaves up to 15 dB. Boost/Cut, Bandwidth (Q), and Frequency are continuously variable for perfect correction of amplitude errors. P-94-S (kit) \$129, P-94-SA (assembled and tested) \$179. M/C & Visa—Call or write **PHOENIX SYSTEMS INC-re3, P.O. Box 628, Manchester, Ct. 06040 (203) 643-4484.**

**CIRCLE 86 ON FREE INFORMATION CARD**

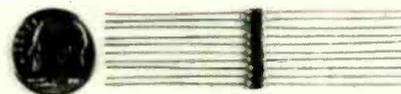

**MINIATURE 1/8W 5% CARBON FILM RESISTORS** offer superior overall performance characteristics compared to carbon composition resistors - at significant cost savings! EIA color coding. 1 ohm thru 10 megohm. \$3.75 per hundred per value. Mastercard, Visa, American Express, accepted. Please add \$2.00 for shipping. California residents add 6% Sales Tax. No C.O.D. **ACORN INDUSTRIAL ELECTRONICS P.O. Box 10846, SANTA ANA Ca. 92711. 1300-D E. Edinger Ave., Santa Ana, Ca. 92705. (714) 547-8424.**

**CIRCLE 59 ON FREE INFORMATION CARD**



CIRCLE 117 ON FREE INFORMATION CARD

MHz in 1-kHz steps. Output-level range is -10 to 120 dBμvolt in 1-dB steps.

The model LSG-215A is designed particularly for use in the communications industry, but is a general-purpose signal generator as well. It is priced at \$2,795.00.—Leader Instruments Corporation, 386 Oser Avenue, Hauppauge, LI, NY 11788. R-E

## EQUIPMENT REPORTS

*continued from page 32*

are used to indicate whether the reading is in kHz or MHz. Annunciators are also used to indicate when a measurement (GATE) is being taken and if an overflow (OVER) condition exists. The OVER annunciator lights whenever the range of the display is exceeded and one or more significant digits are not displayed.

The resolution of the display depends

upon the frequency of the input signal. For signals up to 10 MHz, the maximum resolution is 0.1 Hz. For signals from 10 MHz to 80 MHz the maximum resolution is 1 Hz. For signals higher than 80 MHz, the maximum resolution is 10 Hz. Lesser resolutions can be switch-selected in four decades from the front panel. For instance, for signals up to 10 MHz, the four selectable resolutions are 0.1, 1, 10, and 100 Hz. All available resolutions are shown on a handy front-panel chart.

All functions and measurements are selected using front-panel pushbuttons. In addition to the connectors and controls we've already touched upon, a RESET button is provided that can be used to clear the counter back to zero. When the button is released, a new measurement is taken. Also switch-selectable from the front panel are a  $\times 10$  attenuator and a 100-kHz lowpass filter. Those features are available whenever a signal is input through the CHANNEL A BNC connector. The attenuator is used to help prevent miscounting that might be caused by noisy or improperly terminated high-amplitude signals. The lowpass filter is used to prevent the miscounting of low-frequency signals due to the presence of high-frequency noise at the input.

The counter uses a 10-MHz time base. That time base is generated by a temperature-compensated crystal oscillator for excellent temperature and line-voltage stability. The specifications for the unit claim a temperature stability of  $\pm 1$  part-per-million over a range of 0°C to +50°C. Line voltage stability is about  $\pm 0.1$  part-per-million for a line-voltage variation of  $\pm 10$  percent.

The unit is housed in a rugged steel case that measures 3.75  $\times$  9.5  $\times$  12.6 inches; the unit weighs 5.31 pounds. In addition to making the unit more durable, the use of a steel case provides excellent RF shielding.

The manufacturer did a nice job with the instruction manual: It covers almost everything you need to know to use and maintain the unit. Included are sections dealing with specifications, operating instructions, circuit descriptions, maintenance and calibration, parts-placement diagrams, available accessories, and warranty information. You may have noticed that we did not list a parts-list or schematic diagram. That's because those are provided in a separate booklet that comes with the instrument.

Note that although there is a handle that doubles as a tilt stand, since there is no provision for battery power the instrument is not really suitable for most field work. Our only complaint, and it's a minor one, is that no probes were supplied with the unit. Those must be purchased separately and are available from B + K as outlined in the manual. The model 1851 carries a suggested retail price of \$575.00. R-E

The Professionals' Choice

# PTS

*"VCR service just got faster and better with new PTS VCR replacement boards..."*

Like thousands of professionals nationwide I've depended on PTS rebuilt tuners and modules for years. Now you can get the same fast quality rebuilding service for VCR boards!

- Most Popular Makes & Models
- Fast Turnaround
- Automatic Updates
- Meets or Exceeds Manufacturer's Specifications
- Six Month Limited Warranty



Ask for your

## FREE

PTS Price and Tech Guide with

### NEW VCR

replacement boards  
at over 1,500  
PTS distributors  
nationwide.

The Professionals' Choice

**PTS CORPORATION**

P.O. Box 272  
Boomington, N.J. 07002  
(612) 824-9331

BUILD THIS

# COLOR-BAR GENERATOR

JERRY LAWSON and DAN McELROY

PROBABLY THE LEAST APPRECIATED PIECE of test equipment is the color-bar generator. It is one of those pieces of equipment that there is no substitute for when needed. But since that is so infrequent, the price tags on those units would make most of us squirm.

But there is an alternative. In this article we will show you a color-bar generator that will produce color bars, dots, cross-hatch patterns and lines. And it can be built for less than \$25.00.


What makes that possible is a device that is found in over 15 million households: the Atari 2600. That color-graphics generator, which most people call a videogame computer, along with others that are available, can be programmed to produce graphics of almost any shape. For the sake of this project, it can be programmed to produce the same graphics pattern as a conventional color-bar generator, but at only a fraction of the cost.

## The 2600


What makes this device practical is the popularity of the 2600. Considering the number of those units that have been sold, the odds are excellent that either you or your children own one of those machines. If not, perhaps a friend would be willing to lend you his for a while. If all else fails, those units can often be bought at a substantial discount or even second hand.

Let's look a little more closely at the 2600. That unit (see Fig. 1) consists of three LSI IC's—A 6507 microprocessor (28-pin version of the popular 6502 CPU), a 6532 RAM-I/O-timer array, and a custom graphics IC known as a VIC. There is some other circuitry, but those three IC's are the heart of the 2600 game console.

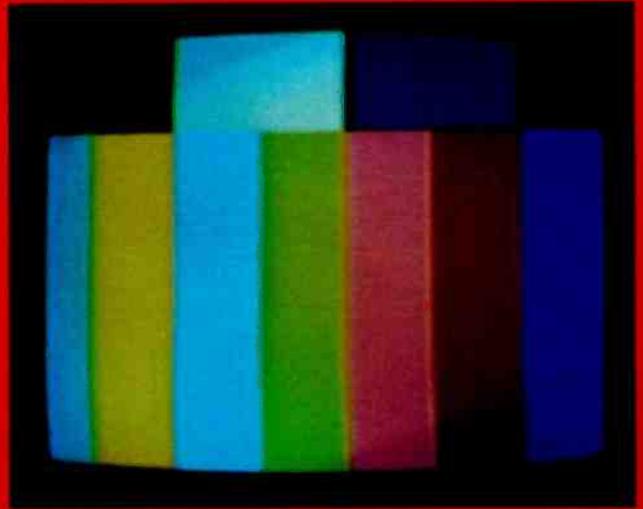The VIC IC and the 6532 act as the peripherals to the 6507 CPU. Since the



*This novel cartridge for the Atari 2600 lets you use that videogame computer as a color-bar generator.*

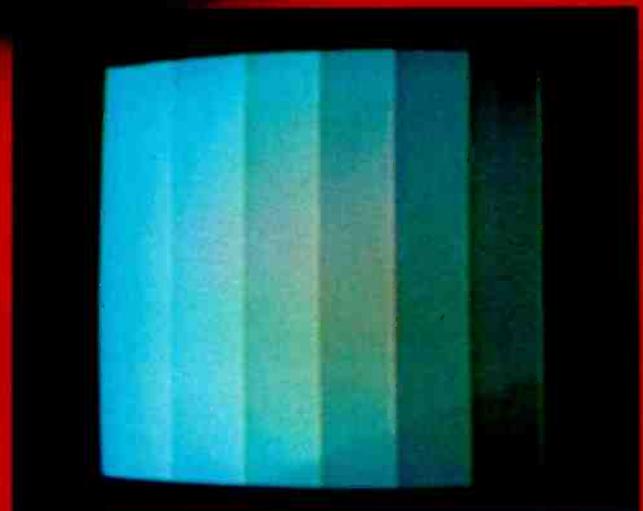

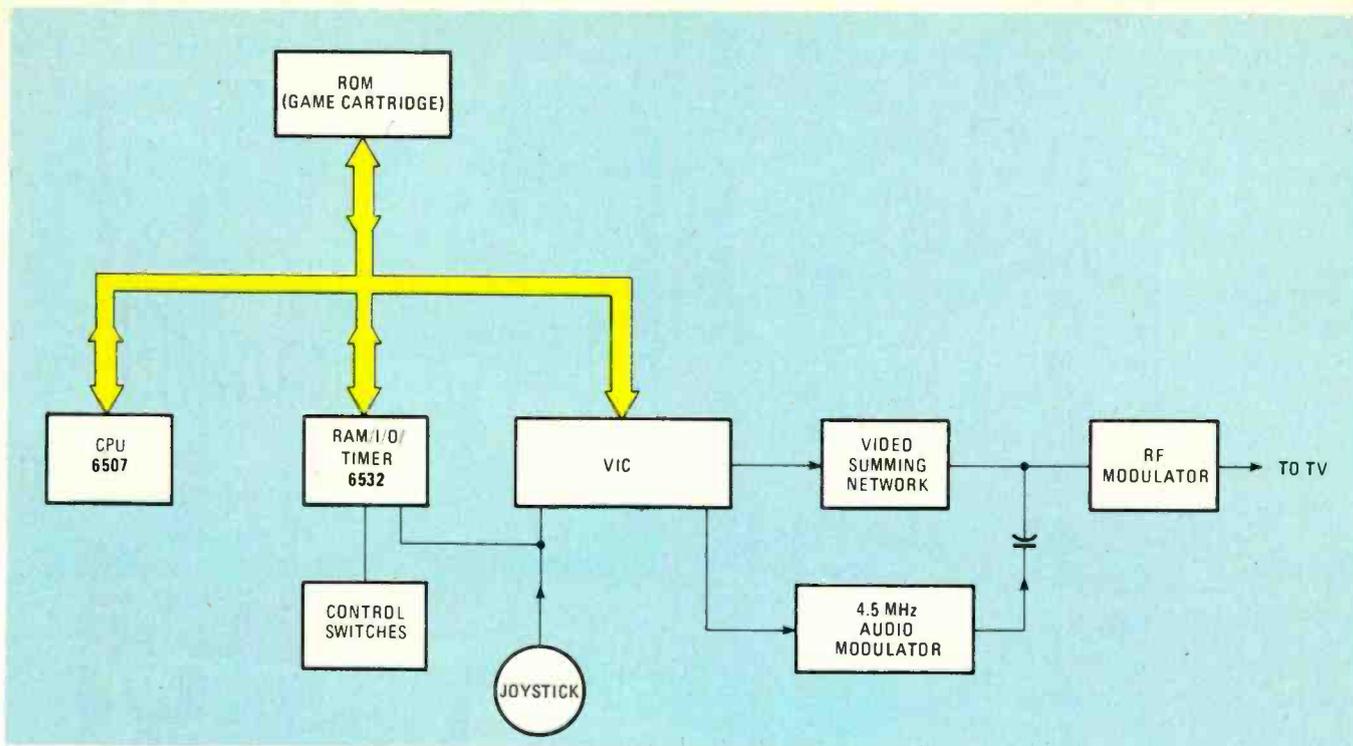


FIG. 1—BLOCK DIAGRAM OF THE 2600. Three IC's, a 6507 microprocessor, a 6532 RAM-I/O-timer array, and the VIC graphics IC form the heart of the unit.

6507 has only thirteen address lines, designated A0–A12, it can address only 8K bytes of memory.

The 2600 uses address line A12 to select whether the peripherals or the ROM, which is inside the external cartridge (more on that shortly), will be addressed. When address line A12 is high (logic 1), the ROM in the cartridge is selected; when address line A12 is low (logic 0), the peripherals inside the 2600 are selected.

Let's see how the memory of the 2600 is organized. The VIC is memory mapped at addresses 0000H to 002FH (the H at the end indicates that a number is in hexadecimal). Loading in the right data to the right address at the correct instant will produce the desired pattern or sound.

The RAM occupies the addresses from 0080H to 00FFH. The RAM is used by the 2600 for temporary data storage during program execution. The hand controllers and the unit's console switches are memory mapped at locations 0280H to 02FFH. The 6532's internal timer is also memory mapped within that range.

### Color-bar cartridge

The plug-in cartridges used by the 2600 consists of a printed-circuit board and a ROM that contains the instructions, or programs, to produce patterns or sounds from the game console. The contents of the ROM is memory mapped at locations 1000 to 1FFF. When a memory location within the ROM is selected by the address bus, the contents of that location is placed on the data bus and passed on to the 6507 CPU.

The program, which is contained in a 2732 EPROM, causes the 2600 to ack like a test-pattern generator. A TTL inverter (74LS04) is used to transform the OE signal from the 2600 to the OE signal required by the EPROM. A schematic diagram of the color-bar cartridge is shown in Fig. 2. The pinout of the device is shown in Fig. 3.

### Construction

The task of building the color-bar generator cartridge is very simple and straightforward: after all, there are only two components in the circuit. A double-sided PC board is required, however. The patterns for that board are shown in Figs. 4 and 5. The parts-placement diagram is shown in Fig. 6. Note that there is a metal shield over IC1. That shield is formed from copper foil and simply tack soldered to the board.

### Use

Connect The 2600 as you would normally to play a game. Insert the color-bar generator cartridge as you would an ordinary game cartridge, turn the power on, and the screen will display a title page. If you made your own board and do not have a cartridge case, be sure to insert the board with the component side up.

Table 1 is a listing of the display functions of the color-bar generator. By depressing the GAME-SELECT switch you move forward through the functions in the order they are listed in the table. By depressing the RESET switch you move backward through the functions.

### PARTS LIST

IC1—2732 EPROM (see text)

IC2—74LS04 inverter

Miscellaneous: PC board, metal shield, plastic case

The following are available from Video Soft, Inc., PO Box 4242, Santa Clara, CA 95050: Color-bar generator cartridge kit, \$23.95, plus \$1.70 postage and handling; assembled unit, \$29.95, plus \$1.70 postage and handling; Source-code listing for the EPROM, \$10.00, plus \$1.70 postage and handling. California residents add 6% sales tax. VISA and MasterCard accepted.

The color-bar display is a close approximation to the NTSC standard color bar. The top colors are grey, yellow, cyan, green, magenta, red, blue, and black. The bottom colors are a very dark green, white, blue, and black.

The gray-scale pattern produces eight shades across the screen, going from white to black. That pattern is used to check that the television can reproduce uniform changes in the luminance amplitude. The brightness and contrast can be adjusted so that all bars are showing across the screen. Note: It is not possible to turn off the color-burst signal on the game console, even with the COLOR/BLACK-WHITE switch.

The cross-hatch, dot, vertical lines, horizontal lines, and center-cross patterns are very useful for checking vertical and horizontal linearity on any television, and are also useful for checking and aligning

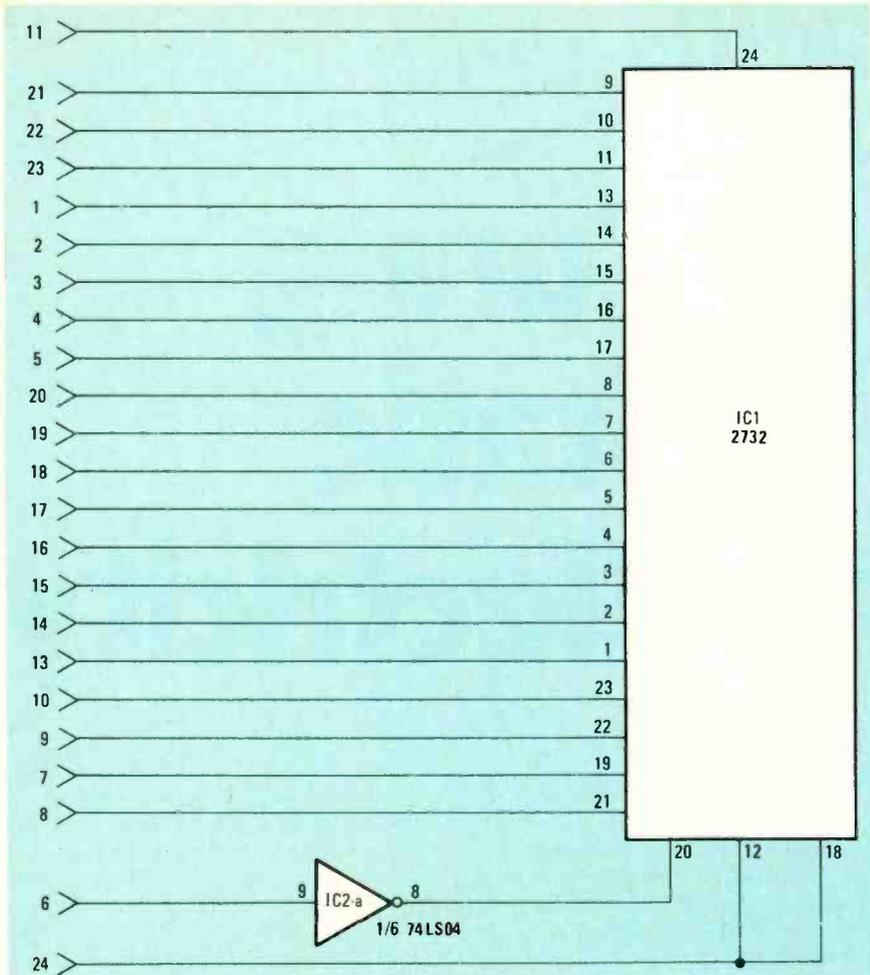


FIG. 2—THE COLOR-BAR CARTRIDGE. This simple circuit allows you to use the 2600 as a color-bar generator.

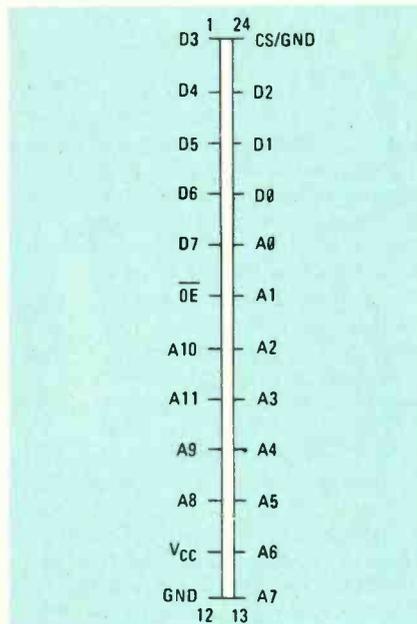


FIG. 3—THE PINOUT of the color-bar generator cartridge's card-edge connector.

convergence on a color television.

The circle pattern is used to adjust the vertical size and linearity. If the vertical

#### TABLE 1—FUNCTIONS

Title Page
Green Screen
Red Screen
Blue Screen
Low-Level White Screen
Window
Wide Vertical Bars
Circle
Cross Hairs
Horizontal Lines
Vertical Lines
Dots
Cross Hatch
Stair Step (Gray Scale)
Color Bars

size and/or linearity are out of adjustment, the circle will look like an oval or an egg.

Wide vertical bars are provided to test for smearing or fading of the video signal. If all is in order, the bars should appear as completely white and black bars.

If all is normal, the window pattern will appear as a white window in a completely black background. If the black background changes between black and grey at the top or bottom of the window, the DC coupling or DC restoration between the video amplifier and the picture tube is not

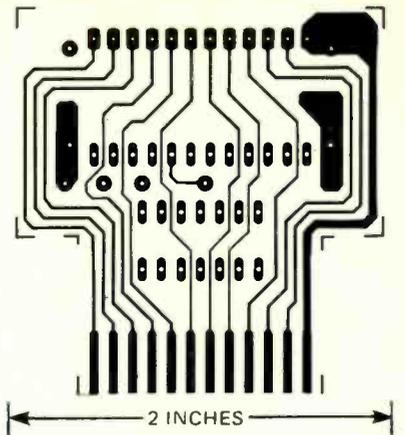


FIG. 4—THE COMPONENT SIDE of the double-sided PC board is shown here.

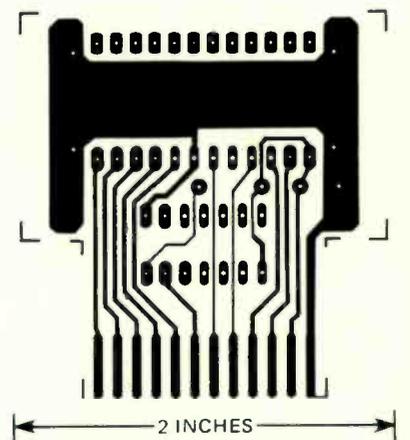


FIG. 5—THE FOIL SIDE of the double-sided board is shown here..

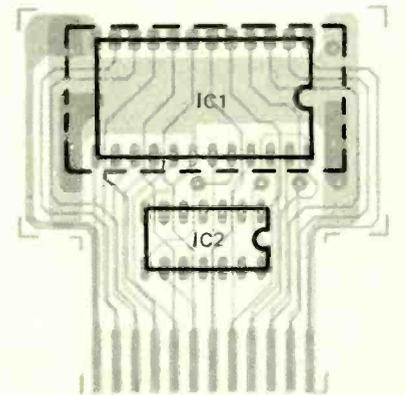


FIG. 6—PARTS-PLACEMENT DIAGRAM. The dashed box around IC1 is a shield made of copper foil. That shield is tack soldered to the PC board.

functioning correctly.

The white screen is used to adjust the color circuits to produce a white screen on a color television. The red screen is most useful in adjusting color purity. If the screen is not completely red (that is, if it shows other colors around the edges), the television should be degaussed (or the color-purity magnets will need adjustment).

R-E

# Curing Static Electricity

ELLIOTT S. KANTER

*Learn the "shocking" facts about static electricity, the damage it can do, and how it can be controlled.*

HIDDEN IN YOUR HOUSE, OFFICE, OR GAME room is a sinister and silent enemy. It sits quietly waiting for the proper moment to "zap" either your computer, disks, or videogame into oblivion. It has no smell, taste, leaves no odor, and can strike in the best of homes or offices. That silent killer of things electronic is static electricity. It strikes without warning, and in the blink of an eye can send over 50,000 volts of electricity coursing through the sensitive electronics of your computer, videogame, or data-filled floppy disk.

None of us would knowingly connect sensitive electronics equipment to such a large potential surge, but in fact, that potential is present all over your house, shop, office, or den. The problem, while not exactly the topic of conversation in polite circles, has found its way more than once to the pages of a national financial daily paper. There, a videogame company was quoted as acknowledging the hazard, its potential destruction of equipment, and then, perhaps in a tongue-in-cheek manner, suggested that game owners get themselves a large, hairy dog and touch it before operating their videogame, or handling a game cartridge.

While the suggestion does have some basic merit, it clearly would be inconvenient to use in an office situation, not to mention the obvious requirement to feed, water, and walk such an acquisition. However, there is hope; and in fact, the principles of dealing with this hazard are well known, documented, and even simple to implement in your office or home with little or no extra cost. You need not resort to sophisticated devices, or even hairy animals.

For years, hospitals throughout the country, and the world for that matter, have been forced to deal with static electricity and more important, to develop techniques to keep it in its place.

Static electricity is usually produced by differing potentials, friction, or the flow of gases through tubing at high flow-rates. What makes that static-electric formation dangerous in the hospital is the effect of a discharge of static electricity in the form of a seemingly harmless spark in the presence of either flammable anesthetic-agents or in oxygen-enriched areas. Obviously, if you were to apply a spark in an area rich in fumes or oxygen, a fire or explosion would result.

In order to safeguard the lives of patients and health-care personnel, hospitals embarked on an aggressive program of static-electric control that resulted in a number of simple cures and a better understanding of the problem. Readers desiring more information on that program are referred to *Document 56A*, a complete "course" on static-electricity control available from the National Fire Protection Association, Boston, Mass., for about \$3.00.

Static electricity can also cause serious problems in a number of other special situations. In the munitions industry, for instance, electrically ignited devices such as blasting caps and primers can be set off by static electricity.

A little closer to home, a variety of electronics components, such as MOS semiconductor devices (see Fig. 1), are extremely static sensitive. Because of that, special handling is generally required. When working with MOSFET's,

for example, both the user and the device case should be grounded at the same potential during any handling. During transit, all device leads should be shorted together. When soldering a device into a circuit, the soldering-iron tips should be grounded. Finally, the chassis and cabinet of any unit using MOSFET devices should be grounded.

In the balance of this article, we shall examine the basic principles and rules for keeping static electricity in its place, not in your sensitive equipment.

## Terms

To fully understand static electricity and how to control it, we have to change some of the ways we think about or define terms. Normally, when we refer to a conductor, we would assume that it has a very low resistance. An insulator, on the other hand, could be thought of as something that has a high resistance. Copper wire is a good example of a conductor, and rubber immediately comes to mind as a typical insulator. There are other examples, but for the purpose of this article, let's accept them as is.

In things of a static-electric nature, a good conductor will have a resistance of between 25,000 and 500,000 ohms; insulators a resistance of over 500,000 ohms. Typically, the resistance as measured from chassis ground to the ground pin of the power cord, would be less than 2 ohms, so we can see the disparity in terms and definitions. Another term we might want to examine is "isoelectric." Speaking in terms of static-electricity control, that term is defined as a condition wherein all objects are at the same potential.

# The Heathkit Catalog & American Technology... Inseparable!



Ever since radio grew into electronics, the illustrated Heathkit Catalog has been a guide to new and exciting electronic kit products for people like you to build. Enjoy. Learn from. And save money.

The Heathkit Catalog is now even better. The ALL NEW full-color catalog features more than 450 different products in electronics, computers and other state-of-art technology. Page after page is devoted to new and exciting products for your home, hobby and business.

If you don't have the latest Heathkit Catalog, you're missing something great! Now's your chance to get involved in American Technology first hand. Your free ALL NEW Heathkit Catalog is waiting for you.

**Fill out and return the attached Catalog request card today! Or use reader service number below.**

CIRCLE 15 ON FREE INFORMATION CARD.

# Discover the Challenge



Great innovations in electronics are at your fingertips in each quarterly issue of the Heathkit Catalog. From computers to test instruments to the latest in personal robotics. Act now and send this card for the **ALL NEW Heathkit Catalog**.

**CATALOG OFFER**  
Heath Company  
Dept. 020-209  
Benton Harbor, MI 49022

Yes I want to see the latest in electronics from Heathkit. Please send my free copy of the ALL NEW Heathkit Catalog to:

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

PC-148

# Discover the Pride



With Heathkit, you'll discover the pride of accomplishment only a hand-built quality product can provide. From Stereos and TVs to Ham Gear and the latest in education. Act now and send this card for the **ALL NEW Heathkit Catalog**.

**CATALOG OFFER**  
Heath Company  
Dept. 020-209  
Benton Harbor, MI 49022

Yes I want to see the latest in electronics from Heathkit. Please send my free copy of the ALL NEW Heathkit Catalog to:

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

PC-148

Post Office  
will not  
deliver mail  
without stamp.


**CATALOG OFFER**

Heath Company  
Dept. 020-209  
Benton Harbor, MI 49022

Post Office  
will not  
deliver mail  
without stamp.


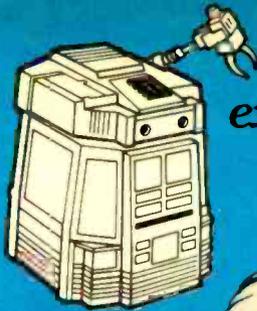
**CATALOG OFFER**

Heath Company  
Dept. 020-209  
Benton Harbor, MI 49022



*Be a part of today's  
exciting world of high  
technology.*

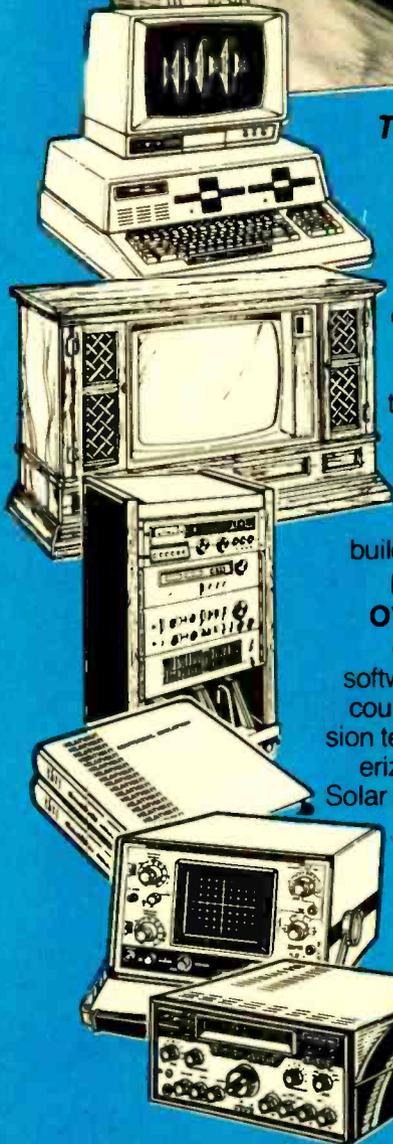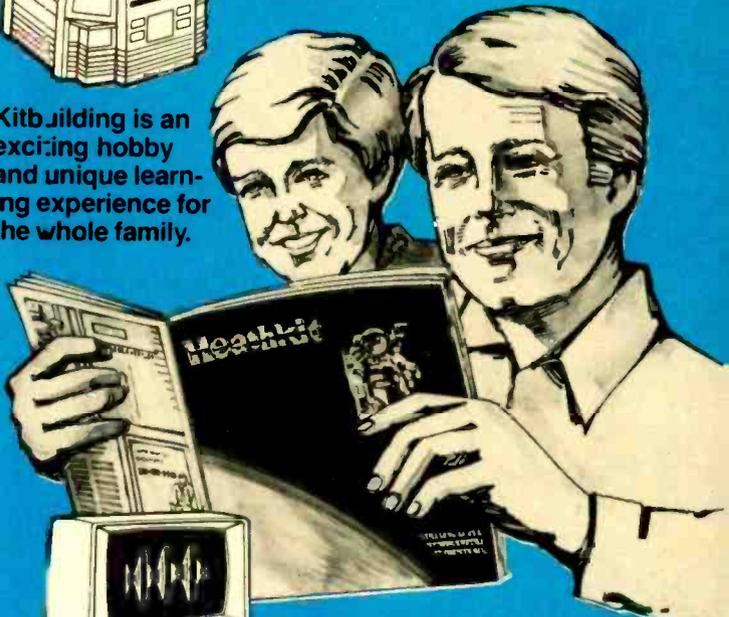Kitbuilding is an  
exciting hobby  
and unique learn-  
ing experience for  
the whole family.



*The best in electronics  
is hand-built by you.*

Building advanced computers and electronic products from kits is a great hands-on way to develop skills and ability in many technologies. Easy step-by-step directions take you through the building process. And we back our products and you with the simple promise: "We won't let you fail." Heathkit builders create more than fine products. They build pride.

**OVER 450 KITS TO BUILD**


- Computer hardware and software
- Robots
- Self-study courses in electronics
- Precision test instruments
- Computerized weather instruments
- Solar hot water systems
- Automotive and home energy products
- Security devices
- Color TVs and video accessories
- Quality Stereo components
- Amateur radio gear

PC-148

**Start by ordering your FREE  
Heathkit Catalog today. Or use  
Reader Service Number**

**CIRCLE 15 ON FREE INFORMATION CARD.**



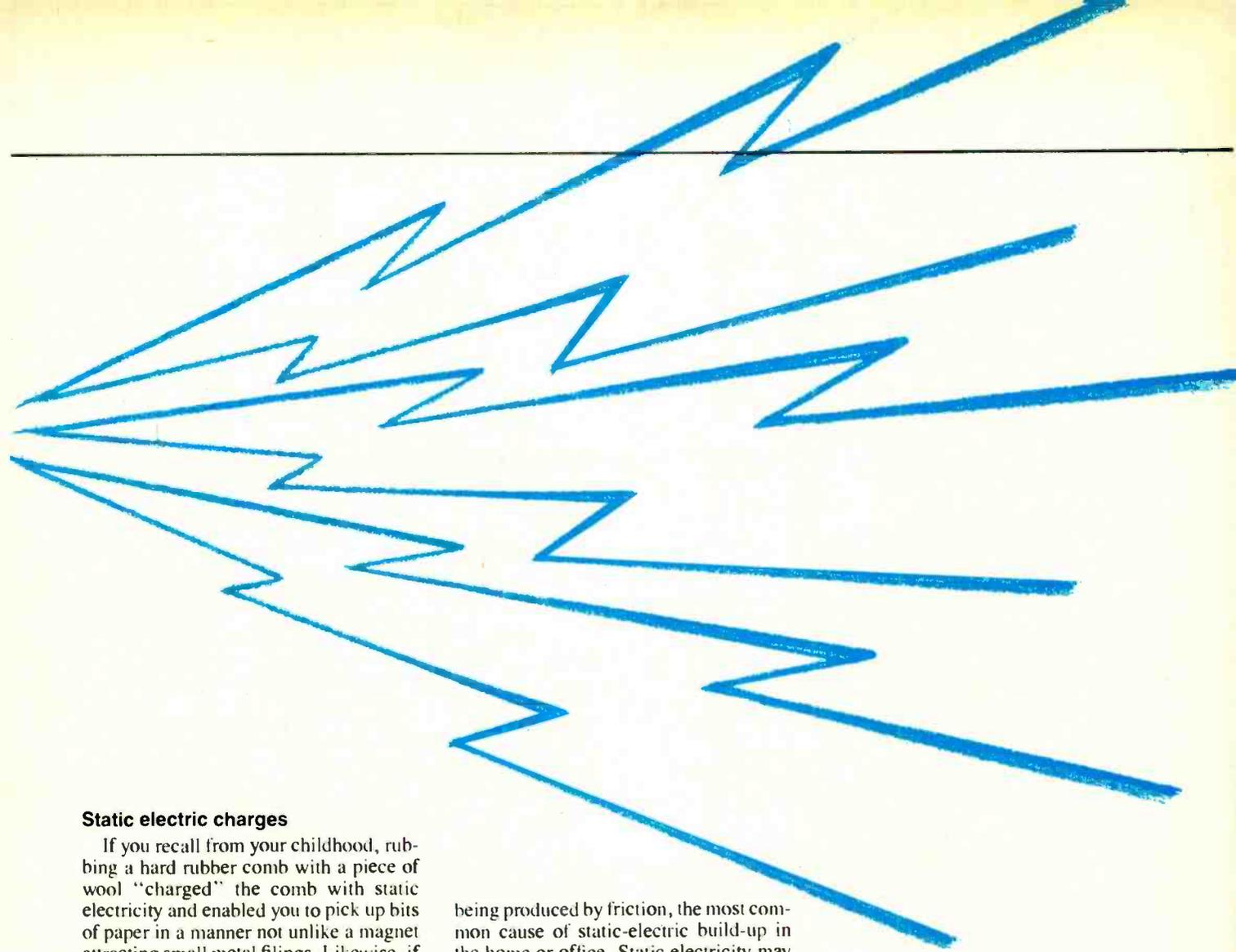

### Static electric charges

If you recall from your childhood, rubbing a hard rubber comb with a piece of wool "charged" the comb with static electricity and enabled you to pick up bits of paper in a manner not unlike a magnet attracting small metal filings. Likewise, if you have carpeting and shuffle your feet as you walk, you will have a visual and startling example of static electricity when you touch a metal object such as a door knob.

Those are examples of static electricity

being produced by friction, the most common cause of static-electric build-up in the home or office. Static electricity may be generated anytime that two objects rub against each other, especially if the objects are made of dissimilar materials. While the objects are in contact, the electrons move from one to the other. But if

either (or both) of the objects are non-conducting, when they separate, the built-up charge remains on the non-conducting object as it has nowhere to go. An object is considered to be strongly charged if it has an excess or deficiency of only one electron in 100,000 atoms.

The more perfect an insulator, the longer an object will retain its built-up charge. If the charge leaks off rapidly, there is no problem. If it continues to accumulate, the accumulation will become sufficient at some point to jump to some nearby object. That is what causes a spark (see Fig. 2).

A spark may be as long as eight inches, or may be too small to see. The energy in the spark is given by  $E = \frac{1}{2}CV^2$ , where E is the energy in joules, C is the capacitance in farads, and V is the voltage in volts. The capacitance for a person is considered to be 100 pF. The human body can build up some considerable static voltages under commonplace situations. For instance, sitting on a varnished wooden stool can generate up to 20,000 volts; a walk across the floor can generate up to 50,000 volts (see Fig. 3). Thus, since voltages of 50,000 are possible, a person can

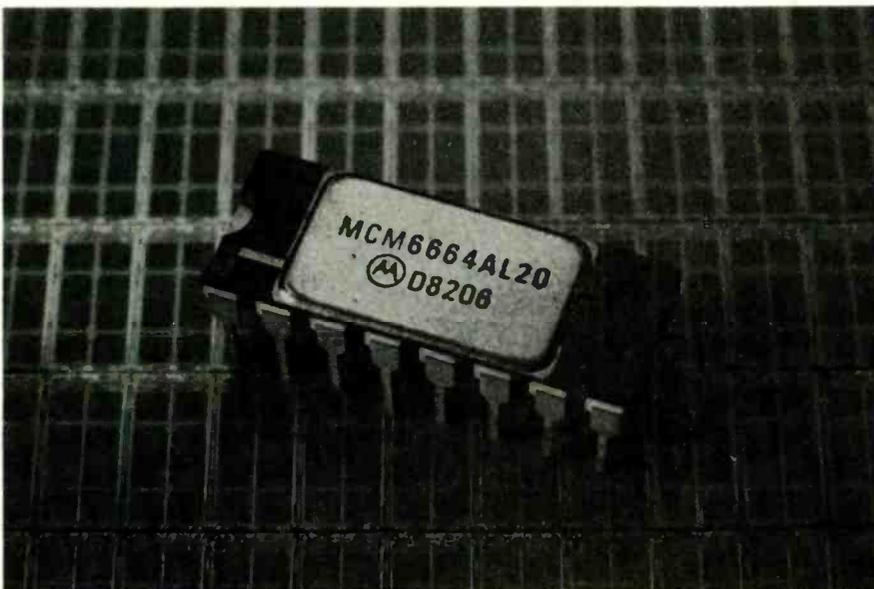


FIG. 1—BECAUSE THEY USE a variety of static-sensitive semiconductor devices, such as this MOS RAM IC, computers are especially prone to damage from static discharges.

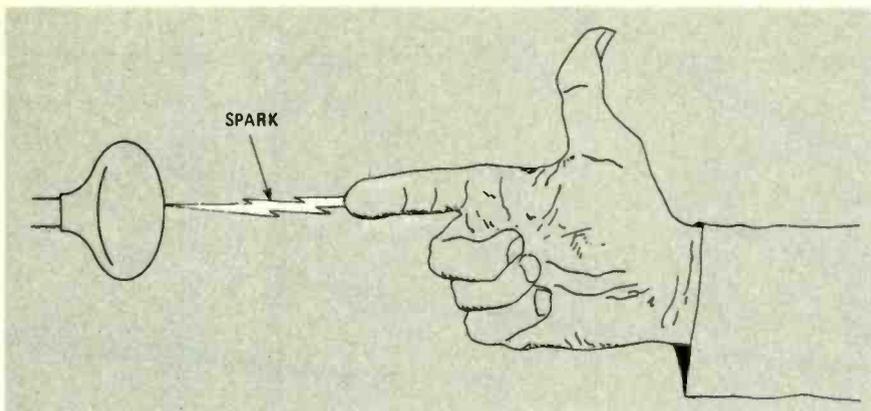


FIG. 2—IF A CHARGE DOES NOT LEAK OFF, the accumulation of charge will at some point be sufficient to jump to a nearby object. That is what causes a spark.

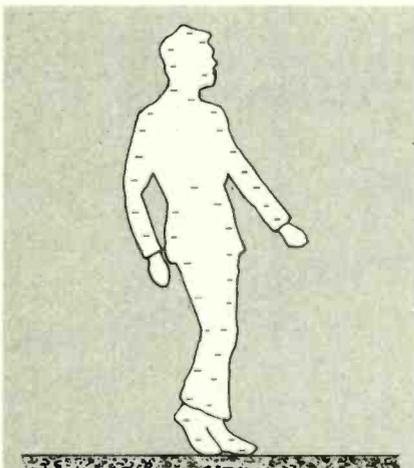


FIG. 3—THE ACT OF WALKING across a wood floor is sufficient to build up a charge of up to 50,000 volts.

cause a spark with an energy of 0.01 joule. A spark with that energy level is quite hazardous in many situations, as it is enough to ignite such chemicals as acetone, benzene, alcohol, and propane gas under certain circumstances. All of those are commonly used in industry, and also might be found in the home or workshop. To further complicate matters, if a drum of acetone, for instance, is left to sit for some time, it too will pick up some charge (see Fig. 4).

The spark caused by a static build-up can also cause some less spectacular, but quite harmful effects when dealing with sensitive electronics or computer equipment. A static discharge can be quite fatal to that data disk you are reaching for to load into the computer, or for that CMOS IC or a videogame cartridge.

Besides friction, we do need an atmosphere conducive to static-electric build-ups. That atmosphere or environment usually consists of a dry, (low-level humidity) room. For various reasons, low levels of humidity tend to amplify the effects of static-electric charge build-ups. Keeping that environment in mind, it would seem that if we had a controlled and

humidified atmosphere or environment, then we would have taken one important step in keeping static electricity in its place.

### Think humidity

Tests have shown that humidity levels of fifty percent (50%) or more tend to discourage the formation of static-electric build-ups. Hospitals condition their static electric critical areas to ensure that the humidity does not fall below that level. In the home or office, it is essential to first determine what the present humidity level is before taking any action. Humidity indicators are available at most discount stores and hardware dealers. Frequently they are available with thermometers so that you can keep track of temperature as well as humidity.

The NFPA suggests that the temperature be around 72°F, with a minimum humidity level of 50%. The normal change in seasons affects the natural humidity found in a room. During the summer or warm months, the humidity level in a room could conceivably be considerably higher than the suggested 50%. Con-

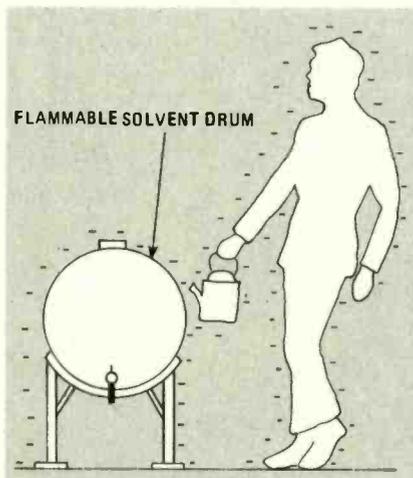


FIG. 4—SINCE BOTH a drum of solvent and a person moving about can accumulate a charge, the potential for disaster in an industrial situation is great.

versely, warm heated air present during the winter months tends to dry out the room. Knowing exactly where you stand is quite important in combatting static-electric charge build-ups. If your room or work area has a humidity level of 60%, it is not necessary to reduce it to the level suggested by the NFPA. Remember, that level is a minimum one where tests have shown that static-electric charge build-ups are discouraged. Too high a humidity level is uncomfortable for both people and equipment.

If the humidity level is too low, we would want to add moisture to the air. That can be done by using a humidifier to add precise amounts of water to the air until an acceptable level is reached. Those devices vary in size and cost; and if more than one area is affected, it might be wise to consider a central humidifier that would work with the centralized heating and cooling system. Conversely, if a room is too wet or overly humid (and we would define that as being at a level perceived as uncomfortable by the occupants of an area), then a dehumidifier, a device designed to remove moisture from the air is indicated. Again, we are looking to establish an environment that contains at least enough humidity (50%) to discourage the formation of static-electric build-ups but low enough to provide comfortable working conditions.

Typically, we will be removing moisture during the warm summer months and adding moisture during the dry winter months. However, if you live in a climate which is excessively dry or wet, you should make the needed adjustments accordingly.

### In search of a common potential

Building on our previous definition of isoelectric, we can see that we must attempt to bring all objects to a common potential. In pure electrical terms, that common potential would be ground; but unlike the pure electrical potential, we do not want the degree of conductivity that an electrical ground would produce. That is to say, our definition of conductive must follow the requirements for static-electric control and be somewhere between 25,000 and 500,000 ohms. The reason for those levels, rather than the traditional 2 ohms or less, is that the higher-resistance conductor will permit the static-electric charge to bleed harmlessly to ground. That bleeding off of the charge avoids the obvious differing potentials that would not be of any concern if we were dealing exclusively with conventional electrical energy.


Simplistically, if a stranded wire of perhaps 18-gauge were attached to the case (metallic only) of each item and then routed to a central ground through an individual 27,000-ohm, 1/2-watt resistor, then all

*continued on page 89*

# ALL ABOUT

# Electronics and Your Heart

RAY FISH, Ph.D., M.D.

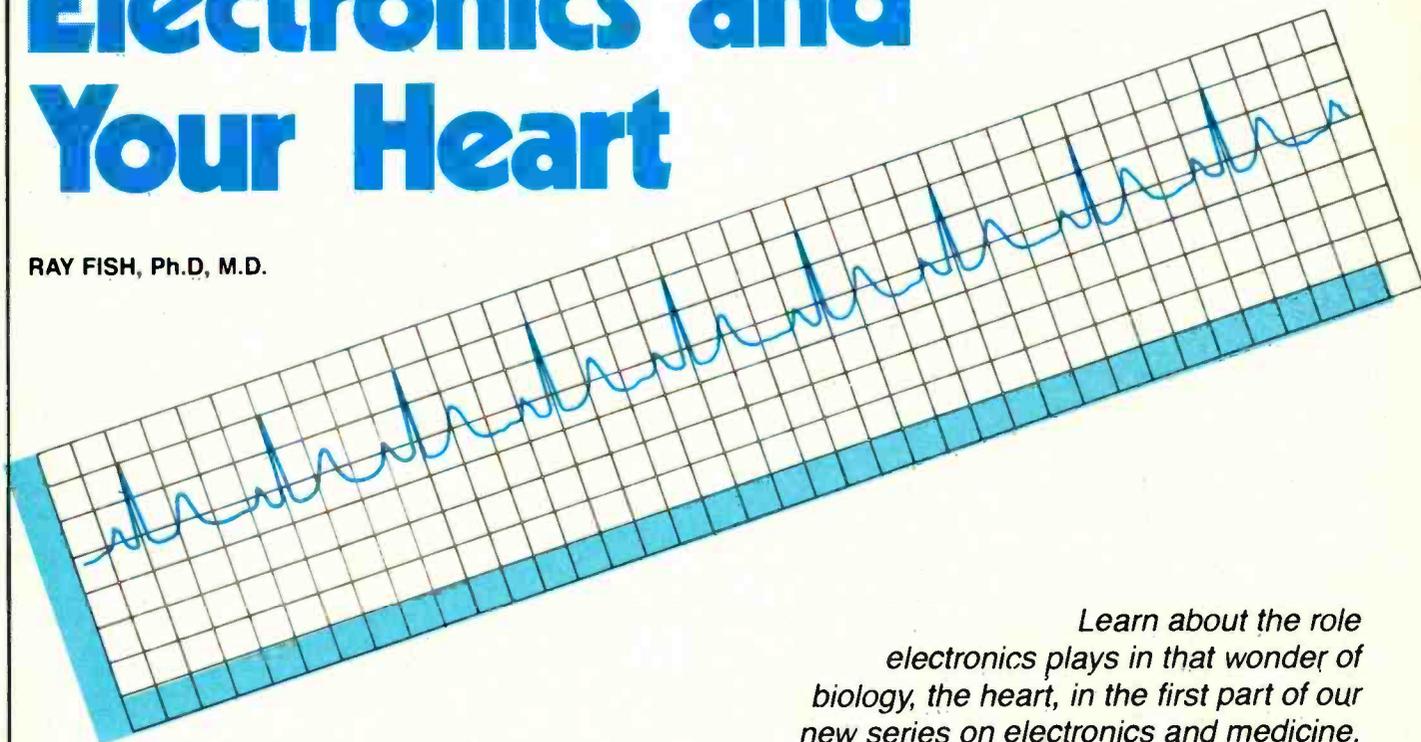

*Learn about the role electronics plays in that wonder of biology, the heart, in the first part of our new series on electronics and medicine.*

WE OFTEN HEAR THE WORDS BLOOD PRESSURE, electrocardiogram, cardiac arrest, heart attack, and myocardial infarction. But, what do those terms really mean? This article is the first of a series of articles which will explain those terms. Other topics to be discussed will include electrical rhythms of the heart, the causes of cardiac arrest, means of resuscitation (reversing cardiac arrest), electronic pacemakers, and the electronic monitoring of critically ill patients.

As we will see, there are many different causes and types of cardiac arrest (cessation of heartbeat). The most common cause of sudden, unexpected cardiac arrest is a myocardial infarction, or heart attack. In a myocardial infarction, a part of the heart loses its blood supply and dies. In the USA there are about 1,500,000 myocardial infarctions with 650,000 deaths resulting each year.

## Structure and function of the heart

The heart is the muscular pump that moves blood throughout the body. As shown in Fig. 1, the heart receives blood from the veins of the body. The blood first goes into the right atrium. The right atrium is the first of the four compartments, or "chambers" of the heart through which the blood will pass. Blood goes from the right atrium to the right ventricle. The tricuspid valve (see Fig. 2)

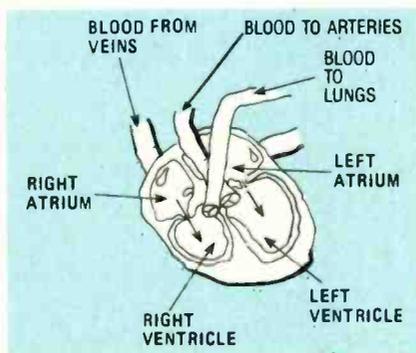


FIG 1—THE FOUR CHAMBERS of the heart. The arrows show the direction of blood flow.

keeps the blood from flowing backward into the right atrium. After leaving the right ventricle, blood goes to the lungs.

The lungs add oxygen to the blood and get rid of the waste gas (carbon dioxide) that the blood has accumulated while going through the body. The blood returns to the left side of the heart.

Blood passes from the left atrium to the left ventricle through the mitral valve. The left ventricle can then pump blood to the body through the aortic valve. The aorta is the largest artery in the body.

The aorta branches and divides into smaller arteries, as shown in Fig. 3. Those smaller arteries divide repeatedly into smaller and smaller arteries. Finally the dividing of arteries leads to the very small

capillaries. Capillaries join to form small veins. The small veins join together to form larger veins. The larger veins come together to form the great veins that return blood directly to the right atrium. The actual giving of oxygen to the body occurs at the capillary level.

Although the heart is full of blood, the heart's thick muscular walls must receive oxygen and nutrients through a separate system of arteries. The arteries that bring oxygen and nutrients to the heart muscle are called coronary arteries. If a coronary artery is blocked, or "occluded," the heart muscle supplied by the artery will die (infarct). Thus, a coronary artery occlusion is a blockage of an artery that leads to the death (infarction) of a part of the heart muscle. That muscle death is termed a myocardial infarction or heart attack.

The heart is an electrically controlled pump. Electrical signals cause a sequence of events to occur. First, the heart rests between heartbeats. Then the left and right atria, the top half of the heart, contract. Then the left and right ventricles, the bottom half of the heart, contract.

Between heartbeats, the heart rests and blood flows into the right and left atria from the body and lungs, respectively. Blood also flows into the ventricles at that time. Then the atria contract and force even more blood into the ventricles. There

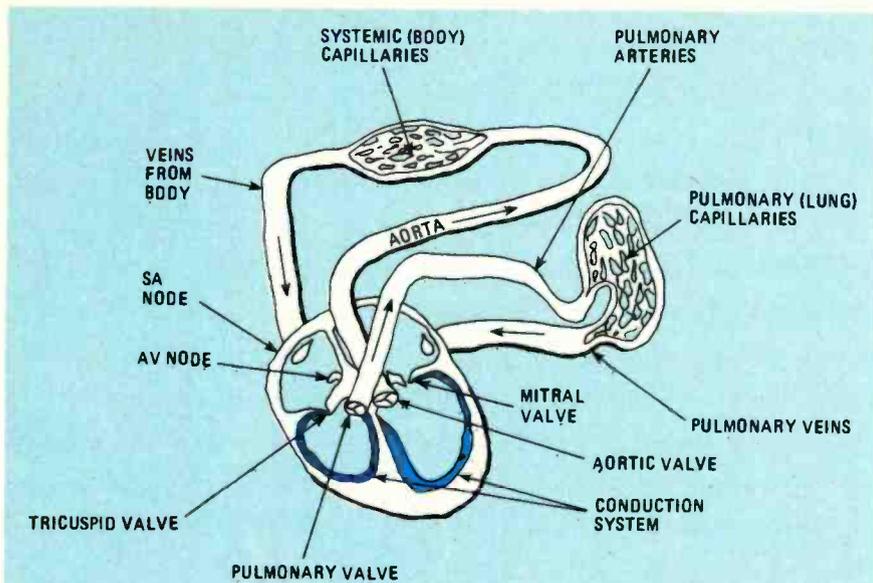


FIG. 2.—THE MAJOR PATHWAYS of blood flow are shown here. Also shown is the heart's electrical conduction system.

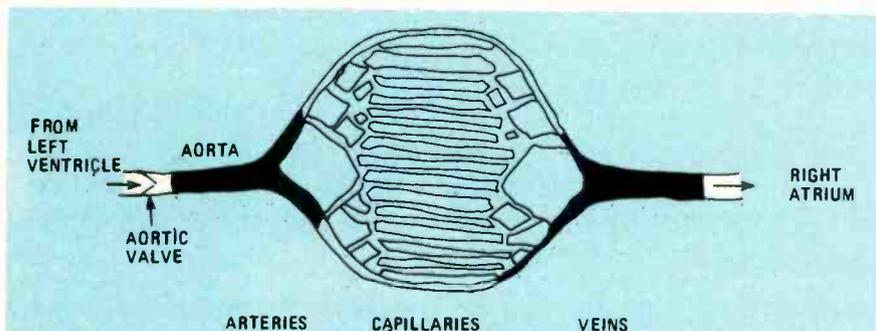


FIG. 3—BRANCHING in the vascular system. Nutrients and waste are exchanged between the blood and the cells of the body through the walls of the capillaries.

is a pause to allow time for the blood to flow, then the ventricles contract. That ventricular contraction forces blood into the lungs from the right ventricle and into the body (via the aorta) from the left ventricle.

### Electrical character of the heart

A heart muscle cell normally has a voltage on the inside of the cell membrane that is about 90 millivolts more negative than the voltage outside of the cell. (See Fig. 4.) That voltage is called the resting potential. If the resting potential is raised to a threshold voltage, the cell will suddenly discharge (or "depolarize"). When discharge occurs, the potential inside the cell becomes about +30 millivolts, and the cell contracts (the muscle cell becomes physically shorter in length). After about 200 milliseconds, the potential inside the cell returns to the resting potential, and the cell relaxes mechanically until the cycle repeats (when the resting potential is again raised).

The cells of the atria are connected to adjacent atrial cells electrically. Therefore when a cell discharges, nearby cells will receive the stimulus to discharge. A wave

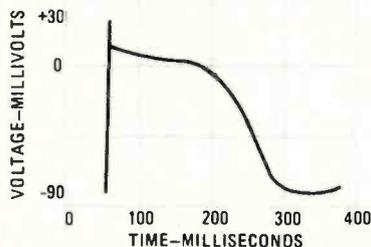


FIG. 4—THE VOLTAGE inside a heart-muscle cell. When caused to depolarize, the voltage becomes briefly positive, drops to 0 for about 200 milliseconds, and then goes negative.

of depolarization spreads through the atria. Eventually all the cells of the atria will have discharged. The atria will have contracted. Waves of depolarization involving large numbers of cells cause a voltage that can be detected by electrodes placed on the body surface. The voltage detected in that manner is the electrocardiogram (ECG or EKG).

Similar to the arrangement in the atria, all cells of both ventricles are connected electrically to adjacent ventricular cells. Therefore, discharge of any ventricular cell will spread and eventually cause dis-

charge (and contraction) of all ventricular cells.

However, the atria and the ventricles are not directly connected together. The atria are connected electrically to the ventricles by a small area called the AV (Atrio-Ventricular) node. That conduction path between the atria and the ventricles delays the signal about 0.04 second. That delay gives the atria time to eject blood into the ventricles. That delay also limits the number of beats per minute that can reach the ventricles. In conditions in which the atria are beating much too fast, this limiting of the ventricular rate is often life saving. That is because it is mostly the pumping of the ventricles that causes blood to flow to the brain and other vital organs. If the ventricles are made to beat too rapidly, the flow of blood is decreased because there is insufficient time for the ventricles to fill with blood between contractions.

Refer back to Fig. 2. A "schematic diagram" of the "circuitry" used to control organized sequential depolarization of heart muscle cells is shown there. If not caused to depolarize from some outside stimulus, most cells of the heart slowly depolarize from their resting potential and discharge a characteristic number of times per minute. The cells that discharge most quickly are the "pacemaker cells" in the SA node. The depolarization signal from the pacemaker cells spreads through the atria first. Then the AV node conducts the signal to the rapid conduction fibers that line the inside of the ventricles. The stimulus to depolarize then spreads from the inside to the outside of both ventricular walls simultaneously. Cells in the atria tend to depolarize at the rate of around 60 to 100 times per minute. The cells in the AV node tend to depolarize at a rate of about 60 times a minute. The cells in the ventricle tend to depolarize at a rate of about 30 times a minute.

Thus, the atria contract, first, then, following a delay, the ventricles contract. There will then be a pause before the next heartbeat or "cardiac cycle." All of the heart muscle cells become depolarized and contract in an orderly, timely fashion. Before any heart muscle cells outside of the SA node have time to depolarize and contract at their characteristic rate, another signal from the SA node will come along and cause depolarization again. Thus, the SA node is the normal pacemaker of the heart. If the SA node fails, or if signals are blocked in a diseased AV node, the ventricles will sometimes be able to effectively beat because some ventricular cells spontaneously depolarize and act as a pacemaker for the ventricles. The rate is often slow (around 30 beats-per-minute), but that "escape rhythm" will often be sufficient to sustain life until something can be done to help the patient.

## The electrocardiogram

The electrocardiogram is a signal that one can obtain by connecting electrodes to a person's chest, arms, and legs. Figure 5 shows a typical electrocardiogram. The signal is about 1 millivolt in amplitude, so low-noise differential amplifiers are usually used to obtain that signal. The chart recorder paper moves at 25 millimeters-per-second. The signal can also be displayed on an oscilloscope screen.

Several key points in a cardiac cycle are shown in Fig. 5. The P wave occurs due to atrial depolarization. The QRS complexes arise as a result of ventricular de-

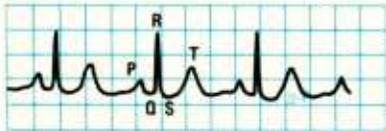


FIG. 5—A NORMAL ELECTROCARDIOGRAM tracing. The P waves cause by the atria are followed by the QRS complexes from the ventricles, which are followed by the T wave.

polarization. The T wave comes as a result of ventricular relaxation (repolarization). The wave associated with atrial repolarization is usually hidden by the QRS complex.

### Electrical problems in the heart

What problems might occur with this system? Just about anything you could imagine, and more! Some of those problems will be discussed in this series of articles.

With myocardial infarction, one of the arteries that supply blood throughout the thickness of the heart muscle becomes blocked. That blockage causes a lack of oxygen and nutrients to a portion of the heart muscle. The injured cells may not conduct electrical signals (may not depolarize) as they should. At other times the injured cells become irritable and depolarize more frequently than they should.

Thus, a signal to depolarize may be blocked by an injured or dead cell. Or, extra depolarizations from an injured cell may cause inappropriate contractions. In that case the result may be further harmful signals that propagate throughout the heart muscle.

Similar problems can occur with any condition that interferes with oxygen or blood supply to the heart. Thus the heart will often develop unusual rhythms (dysrhythmias or arrhythmias) or stop when there is lack of oxygen. Lack of oxygen may occur due to inadequate breathing, drugs, head injury, chest injury, drowning, or lung trouble. Arrhythmias can also occur as a result of blood loss or dehydration (depletion of body water). The heart's electrical function is also predictably affected by imbalance of salts and other substances in the blood such as calcium and

potassium and certain drugs.

### Electronic monitoring

The electrocardiogram is the first means of electronically monitoring the patient with a myocardial infarction or other heart problem. The electrocardiogram does not tell the whole story, however. Sometimes the electrocardiogram will look normal but the person will be having significant problems. Other measurements of heart (cardiac) function must be made. Electronic instrumentation plays an extremely important role in many of those measurements and will be discussed in future articles in this series.

In order to obtain vital information about cardiac function in an acutely ill patient, the blood pressure is often measured in the arteries, the veins near the heart, and in the pulmonary artery. Electronic pressure transducers are used to measure pressures in those locations. Sometimes the transducer itself is put in the area of interest. More often, however, a plastic tube filled with fluid goes from the transducer to the area of interest. The tubing transmits the pressure to the transducer.

The actual function of the heart can be determined by measuring the cardiac output, the blood flow coming from the heart as measured in liters-per-minute. Future articles in this series will discuss those measurements in detail.

### What happens in cardiac arrest

In cardiac arrest, the heart stops pumping blood. In the first type of cardiac arrest, the electrocardiogram may show a flat line representing no electrical activity (see Fig. 6-a). In the second type of cardiac arrest, the electrocardiogram may show ventricular fibrillation (see Fig 6-c) or ventricular tachycardia (see Fig. 6-d). Those tracings show that an electrical signal is present in the ventricles. However, the three dimensional sequence of depolarization and muscle contraction in ventricular fibrillation is irregular, non-repeating, and chaotic. Because there is no coordinated contraction of the ventricle, blood is not pumped into the lungs or body. Instead, the heart simply quivers or vibrates irregularly.

In ventricular tachycardia (tachycardia means fast heart) the same situation often holds. However, if the patient is lucky, ventricular tachycardia may produce a sequence of contractions that are effective in pumping blood. Such a patient would have ventricular tachycardia, but would not be in cardiac arrest.

In the third type of cardiac arrest, termed "electromechanical dissociation," the electrocardiogram looks normal. Yet, no blood is being pumped. How can that be? There are several ways. A large coronary artery occlusion (heart at-

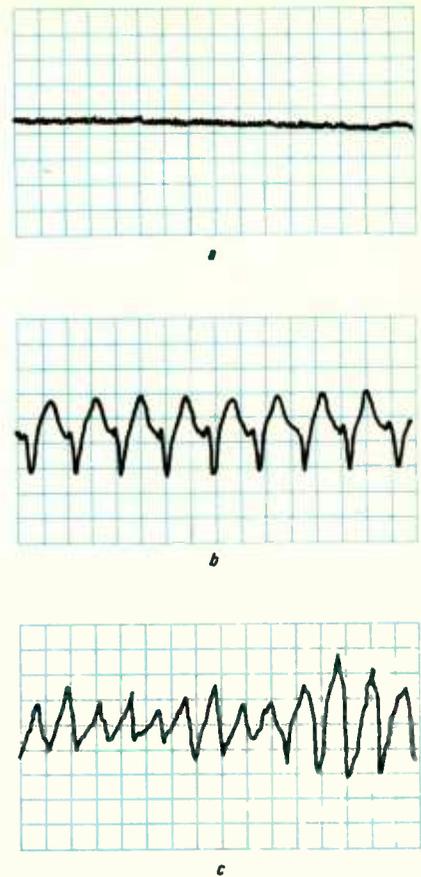


FIG. 6—THREE ELECTROCARDIOGRAM TRACINGS. The one in *a* shows only electrical noise; either a connection is loose or the patient's heart has stopped. The tracing in *b* shows ventricular tachycardia. The tracing in *c* shows ventricular fibrillation.

tack) may cause such a large part of the heart muscle to lack oxygen so that effective pumping does not occur. The electrical signals go through most of the heart normally, but pumping is undetectable. Another type of electromechanical dissociation occurs if blood is prevented from entering the heart. The heart puts out a normal electrocardiogram and goes through the motions of pumping, but no blood flows. That may occur when there is massive bleeding, when major blood vessels are plugged up (as with blood clots), or when the heart is compressed by outside mechanical forces.

A fourth general category of cardiac insufficiency may be defined. In that fourth category would be included various ineffective cardiac situations. For example, the heart may beat too slowly or the heart may beat too weakly.

### The causes of cardiac arrest

Cardiac arrest in children most often occurs due to obstruction of breathing. A child may have his or her airway obstructed, as by an ingested toy. Without oxygen, the heart muscle cannot function and eventually will die. Adults similarly sometimes choke on food and have a later cardiac arrest because the heart muscle

## A GLOSSARY OF TERMS

**Aorta**—The largest artery in the body. That artery branches off into smaller arteries and finally into small capillaries. It is at the capillary level that nutrients and oxygen are passed on to the individual cells.

**Arrhythmias (or dysrhythmias)**—An unusual heart rhythm.

**Atrium**—A chamber of the heart that receives blood from the veins. The right atrium receives blood from the body; the left atrium receives oxygenated blood from the lungs.

**AV Node**—The conduction path between the atria and the ventricles.

**Cardiac Arrest**—The stopping of the heart.

**Cardiac Cycle**—The series of contractions that form the heartbeat.

**Coronary Arteries**—The arteries that supply blood to the thick walls of the heart.

**Coronary Artery Occlusion**—The blockage of a coronary artery; that condition usually leads to the death of a part of the heart muscle and a heart attack.

**ECG (or EKG)**—Electrocardiogram. When large numbers of heart cells discharge, a voltage that can be detected by electrodes placed on the body is generated. The record of that voltage is called an electrocardiogram. (An ECG is shown in Fig. 6.)

**Electromechanical Dissociation**—A condition where the electrocardiogram looks normal but no blood is being pumped.

**Myocardial Infarction**—The death of part of the heart muscle; otherwise known as a heart attack.

**SA Node**—SinoArterial node; the group of cells responsible for beginning the cardiac cycle. The natural pacemaker of the heart.

**Ventricle**—One of the chambers of the heart. The ventricles force blood into the arteries. The right ventricle sends blood to the lungs while the left ventricle sends blood into the body via the aorta. (See Fig. 1 and 2.)

**Ventricular Fibrillation**—Irregular, non-repeating, and chaotic contraction of the ventricular muscle. (See electrocardiogram in Fig. 6-c.)

**Ventricular Tachycardia**—A very rapid heartbeat. (See electrocardiogram in Fig. 6-b.)

dies due to the lack of oxygen. Other causes of cardiac arrest include chest trauma, drugs, salt and fluid balance problems, and bleeding.

The most common cause of cardiac arrest, however, is acute coronary artery occlusion. In that situation, an artery supplying blood to part of the heart muscle is blocked. The blockage may be caused by a blood clot or by a muscular spasm of the wall of a coronary artery. Cardiac arrest may result because a large area of muscle was made incapable of pumping. Alternatively, cardiac arrest may follow coronary artery occlusion because the electrical signals telling the ventricles to pump were blocked (and the ventricles did not have an effective escape rhythm). More often than not cardiac arrest follows coronary artery occlusion because an area of ventricular muscle puts out extra signals and causes ventricular fibrillation.

### How cardiac arrest is treated

Quite often, a small area of heart muscle dies and causes ventricular fibrillation because of electrical impulses generated by the dying heart muscle. In those cases, ventricular fibrillation comes early during the myocardial infarction. In fact, over half the people who die of myocardial infarctions do so before they reach a hospital. That is often within the first two hours of the myocardial infarction. If the ventricular fibrillation could be stopped, many of those people could be saved because frequently only a small percentage of the heart muscle has lost its blood supply. Those patients are said to have "hearts that are too good to die." When they die it is because the electrical activity of the heart is disorganized.

Ventricular fibrillation is commonly the rhythm found in a person who has had a cardiac arrest following a coronary artery occlusion (heart attack). In ventricular fibrillation electrical signals are going every which way through both ventricles. Because of that, the heart muscle is quivering, not contracting in an organized manner.

Ventricular fibrillation can be stopped by applying a large electrical shock to the chest. The shock is created by an instrument called a defibrillator, which causes a current to flow through the heart. The voltage applied comes from a capacitor that is charged to several thousand volts. An inductor limits the peak current. The shock lasts 4 to 12 milliseconds.

That shock causes depolarization of all the muscle cells of the heart. The chaotic pattern of depolarizations is stopped because all the cells are depolarized simultaneously. The first cells to recover are those that naturally depolarize the fastest—the SA-node pacemaker cells. Thus, in ventricular fibrillation, a normal heartbeat can often be restored by means of

electrical shock.

Drugs can suppress unwanted spontaneous depolarizations occurring in dying or irritable areas of heart muscle. Suppressing those depolarizations with drugs will tend to prevent the reoccurrence of ventricular fibrillation.

In cardiac arrest caused by absence or blockage of the normal pacemaker signal from the SA node, an artificial electronic pacemaker can be connected to the heart muscle by means of wires. Small electrical shocks carried from the pacemaker to the heart muscle will then initiate waves of depolarization. That electrical activity caused by the pacemaker will cause the ventricles to contract.

So, in our simplified discussion of the cardiac arrest situation, rhythm problems can be treated with shocks, drugs, and pacemakers. Assuming there are no other major problems such as blood clots or bleeding, will restoration of the normal cardiac rhythm save the patient? Not usually. In addition to the original cause of the cardiac arrest, there are other problems that come up when a person has a cardiac arrest.


When a person's heart stops beating a number of things happen. Actually a person may remain awake and continue to talk for about 10 seconds after his or her heart stops. Relatively ineffective breathing may continue for about 30 seconds. No permanent damage occurs until about 4 minutes after the heart has stopped. At that time permanent brain-damage begins (though that time is less if the person was not functioning fairly normally before the cardiac arrest). Future developments in medicine may extend that 4-minute period.

Does that mean that if one cannot restore normal heart function and breathing within 4 minutes, the person will suffer brain damage? Fortunately not. There are ways to replace the functions of the heart and chest muscles with external forces applied to the body. Specifically, one can press on the chest about once a second to replace the heartbeat and breathe into the person's mouth to cause breathing to occur. Millions of Americans have learned the technique that was outlined above, which is called CPR, or CardioPulmonary Resuscitation."

While CPR is being done, additional procedures are prepared and performed. Those procedures include giving oxygen, intravenous fluids, drugs, electrical shocks, and pacemakers. Those additional procedures are termed ACLS, or Advanced Cardiac Life Support. The procedures used in CPR and ACLS have been widely taught in programs organized by the American Heart Association.

We've already covered a bit of ground, though not in too much detail. That detail will be supplied in future articles in this series.

R-E

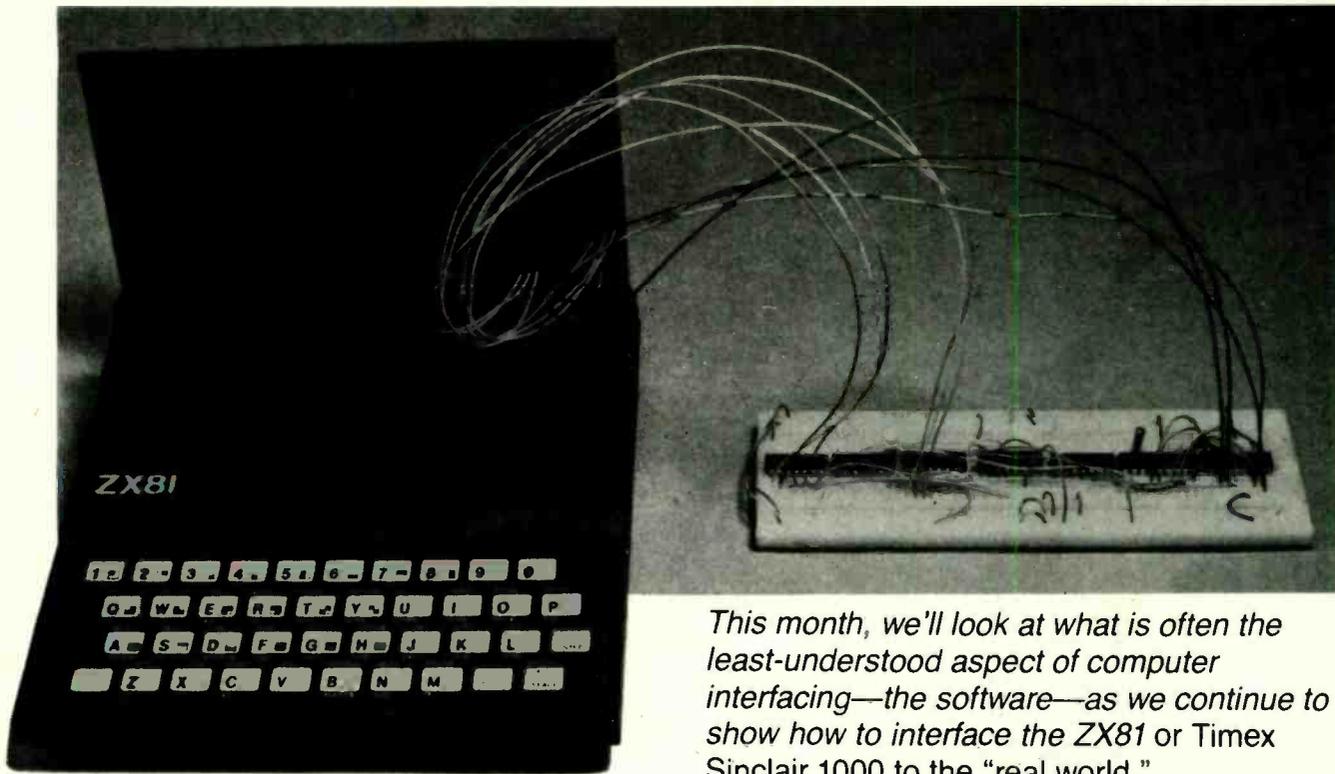

*This month, we'll look at what is often the least-understood aspect of computer interfacing—the software—as we continue to show how to interface the ZX81 or Timex Sinclair 1000 to the “real world.”*

## Interfacing the ZX81

NEIL BUNGARD

**Part 2** LAST MONTH, IN THE first part of this article, we took a look at hardware that allows us to connect external devices to the Sinclair ZX81 (or Timex-Sinclair 1000). We also looked at some basic principles of computer interfacing and described some of the ZX81's interfacing idiosyncrasies.

We used the interface circuit to connect a clock/calendar IC (OKI's MSM5382) to the ZX81. But we couldn't do anything with the resulting circuit—we never discussed the software that is required to operate the it. This month, we'll start with a review of some general software principles and take a look at machine-language programming.

### Machine language vs. BASIC

Why do we have to discuss machine-language programming? You might wonder why you can't use BASIC—a language that you're so familiar with and that is so easy to use—to control the interface. (If you're not familiar with BASIC and need more information, your ZX81 user's manual has a good explanation of most instructions, and many examples of how

to use them.) Actually, you *will* use BASIC to control the interface. But, because the Sinclair BASIC has no IN or OUT commands, you have to use machine language as well.

When you program in machine language, you are programming in the language that the Z80 microprocessor understands. BASIC simplifies programming by allowing many machine-language instructions to be represented by a single command. (When you program in BASIC, the ZX81 must break each command into machine-language instructions before can execute it.) In addition, BASIC was written to be more understandable and easier to learn by the inexperienced programmer. Its word structure is similar to the English language, and the command-words more explicitly describe the operation that the command represents.

If you program in BASIC, you do not have to be familiar with the architecture of the microprocessor (CPU). However, when programming in machine-language the architecture of the CPU becomes increasingly more important: You must be more aware of how the microcomputer system is configured. That's because you

become responsible for all of the “house-keeping” that BASIC takes care of automatically. If you don't completely understand that, don't worry—it will become clear as we study the machine-language mode of programming.

As mentioned earlier, the reason we must program in machine language is because no provisions were made in Sinclair's BASIC that allow us to output data to (or input data from) any external devices. There's another reason: Machine language executes many times faster than BASIC. That speed advantage, as you'll soon see, is a necessity in many interface applications.

### Machine language and the ZX81

To begin programming in machine language, we must first consider the ZX81 memory configuration. The ZX81 system-control software, and a number of stacks and registers occupy the first 16,512 memory locations of the computer's memory space. (Actually, it only occupies the first 8K, but “repeats itself” in the next 8K.) That means that when you enter a program into the ZX81 it begins storing your program at memory location 16513. For ZX81 owners with 1K of memory, your user

memory extends to 17408, giving you only 895 memory locations into which you can store program instructions.

When you program in BASIC, the ZX81 takes care of storing the instructions for you, and only bothers you with memory information (error-message 4) if you run out of space. But when programming in machine language, you are responsible for reserving memory locations for your program. Each instruction must be placed into a specific memory location within the reserved space.

### Reserving space for machine code

One way to reserve space for the machine-language instructions or machine code is to set up a REM (REMark) statement. The REM statement takes the following form:

```
1 REM 0123456789
```

Anything after the REM is not acted on by the computer—it is treated simply as a remark. However, the remark *does* occupy space in memory. For example, for the statement just listed, ten memory locations are occupied by the numbers from 0 to 9. Those ten locations are a good place to put the machine code. (Of course, the numbers 0 to 9 are not the machine code—they simply act as place holders until you enter the code.)

The reason we want to reserve the space in line number 1 is because we know the address where the first line of the program starts: The first character after the REM occupies location 16514. So the 0 in the REM statement is at location 16514, and the number 9 resides in memory location 16523. If your machine-code subroutine is longer than 10 bytes and you need more space, you can simply place more characters in the REM statement. If you want to know the ending address of your reserved space just add the number of characters after the REM statement to 16513. Once you have reserved sufficient space for the machine code you must then place the desired machine code into the reserved space.

We should point out that there are alternate ways to store machine code in the ZX81. One of the most convenient we've seen is to store it in RAM that occupies the addresses from 8K–16K. (That area is transparent to the ZX81's operating system and is not affected by NEW or LOAD commands.) A circuit that allows you to do that was described in the July and August 1983 issues of **Radio-Electronics**.

### Binary, decimal, and hexadecimal

If you're going to do any machine-language programming, you're going to have to get used to working in different number bases. The ZX81 understands numbers only if you enter them in decimal (base 10) form. In other words, when you POKE anything into the ZX81's memory, the address and data must be decimal numbers.

If you've never done any machine-language programming, you might think that using decimal numbers is convenient. It isn't. Usually, machine code is listed in hexadecimal (base 16) form. That's because it lets us represent one byte using just two symbols.

However, because everyone does not follow the same conventions, it is necessary to be able to convert from one number base to another. We will want to be able to convert to and from binary, decimal, and hexadecimal.

In this article, binary numbers will be listed with a capital "B" following the number while hexadecimal numbers will be followed by a capital "H." Decimal numbers will be written without any indication.

Before we can explain how to convert from one base to another, let's look at our decimal (base 10) system to see how it works. We all remember learning about the "ones' place," the "tens' place," the "hundreds' place," and so on. Each place is worth ten times the place to its right—as you move to the left, the value of each place increases by a factor of ten.

It's essentially the same when you work in other number bases—just the numbers change. For example, in the binary system, the value of each place increases by a factor of 2 as you move to the left. In the hexadecimal system, the value of each place increases by a factor of 16 as you move to the left. A look at Fig. 5 should clear up any questions you have—except, perhaps, one. Since the value of the "ones place" in hexadecimal doesn't change until after it reaches 15, you might wonder how you represent the numbers from 10–15 in hex while still using only one digit. It's rather simple: The numbers 10–15 are represented by the letters A–F. Here's a problem to see if you're following what we're talking about: What is D3H in decimal form?  $D3H = (D \times 16) + (3 \times 1) = (13 \times 16) + (3) = 208 + 3 = 211$ .

If you want to convert a hexadecimal formatted instruction to a decimal form, you have a few choices. First, you can follow Fig. 5 and the example above and multiply each number by its place value. But if you don't like multiplying things by 16, there's another way: Convert the hexadecimal form to binary and then convert

the binary to decimal. It's very easy to convert hex to binary—it's a special case where you can simply take each number (or place) in hex and replace it with the corresponding number in binary. (See Table 4). For example,  $D = 1101B$  and  $3 = 0011B$ . Therefore,  $D3H = 11010011B$ .

TABLE 4

Binary	Hexadecimal
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	B
1100	C
1101	D
1110	E
1111	F

You can convert the binary number to decimal by multiplying each digit by its place value. For example, the decimal value for 11010011B is  $(1 \times 1) + (1 \times 2) + (1 \times 16) + (1 \times 64) + (1 \times 128) = 211$ .

Which of the two methods is easier? It all depends on your point of view. However, we're sure that you'll agree that the following is the easiest method of all: Use the table shown in Fig. 6. You can use it to convert from hex to decimal and from decimal to hex. Unfortunately, it works only for numbers between 0 and 255.

Whatever method you choose, we would advise you to become comfortable with base conversions—when you do a lot of machine-code programming, you'll do a lot of base conversions.

### Entering machine code

We are now ready to begin storing machine-language instructions into the memory space you have previously reserved with the REM statement. How do you replace the contents of the REM statement with the machine code? You use BASIC! Specifically, the POKE instruction, which takes the form:

POKE *address, data*  
where the *address* is the memory location

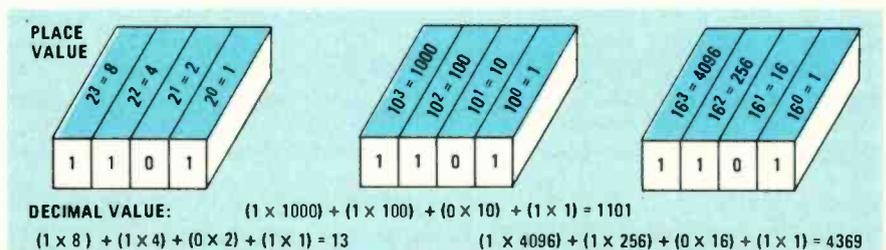


FIG. 5—CONVERTING FROM ONE BASE TO ANOTHER does not have to be difficult or confusing. Just remember that all number bases operate the same as the decimal system you're used to.

	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
1	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31
2	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47
3	48	49	50	51	52	53	54	55	56	57	58	59	60	61	62	63
4	64	65	66	67	68	69	70	71	72	73	74	75	76	77	78	79
5	80	81	82	83	84	85	86	87	88	89	90	91	92	93	94	95
6	96	97	98	99	100	101	102	103	104	105	106	107	108	109	110	111
7	112	113	114	115	116	117	118	119	120	121	122	123	124	125	126	127
8	128	129	130	131	132	133	134	135	136	137	138	139	140	141	142	143
9	144	145	146	147	148	149	150	151	152	153	154	155	156	157	158	159
A	160	161	162	163	164	165	166	167	168	169	170	171	172	173	174	175
B	176	177	178	179	180	181	182	183	184	185	186	187	188	189	190	191
C	192	193	194	195	196	197	198	199	200	201	202	203	204	205	206	207
D	208	209	210	211	212	213	214	215	216	217	218	219	220	221	222	223
E	224	225	226	227	228	229	230	231	232	233	234	235	236	237	238	239
F	240	241	242	243	244	245	246	247	248	249	250	251	252	253	254	255

FIG. 6—THE EASY WAY TO CONVERT FROM HEX TO DECIMAL. All decimal values from 0–255 can be represented by a two-digit hex number.

where the instruction is to be placed and the data is the machine-language instruction. In order for the ZX81 to understand the POKE command, both the address and the instruction must (unfortunately) be in decimal form. If you want to place an instruction into a single memory location, a POKE instruction is probably the easiest way to do it. But in a situation where you want to store many instructions (the usual case), POKE-ing each value can be a tiresome (and error-prone) process.

One way to get around some of the tedium is to write a small loader program that sets the starting address of the machine code, POKES the first instruction, and advances to the next memory storage location automatically. While we're at it, we'll include a couple of lines in the program to convert hex to decimal so that we can enter instructions in a hexadecimal format.

For the following programs, we'll assume that your ZX81 has only 1K of memory, which is standard with the ZX81. (The Timex-Sinclair 1000 came equipped with 2K.) Unfortunately, all the programs we'll need to operate the clock/calendar interface cannot be stored in 1K of memory at the same time. Therefore, we'll have to write individual programs to perform specific tasks and then erase the programs when we have finished to make room for the next program needed. As you can see, cassette-tape storage is almost essential: Once the programs are written, they can be stored on tape and loaded into the ZX81 via the tape player as they are needed. (Of course, if you have more memory than the standard 1K, you'll be able to write and save all of the programs in one shot. What? You can't plug in your RAM-pack when you have the interface board connected? We'll show you how to get around that problem next month.

Clear the ZX81 with the NEW command and enter the program shown in Table 5. If you have a cassette recorder,

SAVE the program.

The first line of the program reserves 17 memory addresses for storing a machine-language program. Line 10 sets the variable "X" to the value of the first address of the machine code storage area (16514) which is now occupied by the first number "1" in the REM statement. Line 40 converts your hexadecimal input to decimal and pokes it into memory.

The program takes your first input and POKES it into location 16514. Your following inputs are POKEd into successive memory addresses until an "S" is entered. When the machine-language program has been completely entered, input an S, and the program will end. Now you're ready to give the program a try. RUN it, and enter the machine code shown in Table 6.

#### Loading the registers

The left column is the machine code that is to be entered. The order of entering the code is: 06, 40, 0E, 91, 0A, etc. (When prompted, enter one number—two digits—at a time, followed by hitting the ENTER key. Don't, of course, enter the commas.) The right-hand column contains the mnemonics that represents the Z80 machine-language instructions. Unfortunately, we cannot go into a detailed description of the mnemonics at this time. (A full explanation of the Z80 instruction set is contained in the *Z80 Software Manual* from Zilog Corporation, and in a number of Z80-programming books on

TABLE 5—MACHINE-CODE ENTRY

```

1 REM 12345678901234567
10 LET X = 16514
15 PRINT "INPUT DATA"
20 INPUT A$
30 IF A$ = "S" THEN STOP
40 POKE X,16*CODE A$ + CODE
   A$(2) - 476
50 LET X = X + 1
60 GOTO 30

```

TABLE 6—REGISTER LOADING

06 40	LD B, 40
0E 91	LD C, 91
0A	LD A, (BC)
D3 00	OUT 00, A
0E 92	LD C, 92
0A	LD A, (BC)
D3 08	OUT 08, A
D3 04	OUT 04, A
C9	RET

the market.)

After all of the machine code has been entered, enter an "S." Look at a LISTING of the BASIC program. In the REM statement, you'll notice that the first 15 numbers have been replaced with strange looking characters. Those characters represent the machine-language program that has just been entered. The reason that you do not see the machine code as it was entered is because the ZX81 stores its "character set representation" of the hexadecimal numbers that were entered, and not the numbers themselves. A complete listing of the ZX81 character set and the associated codes can be found in "Appendix A" of the ZX81 User's Manual.

Now that you have the machine-language program in memory, you will no longer need the machine-code-entry program. Erase everything but the REM statement that contains the machine code (line 1) and enter the BASIC program in Table 7.

TABLE 7—REGISTER LOADING

```

10 FOR I=0 TO 12
20 PRINT I
25 PRINT "INPUT VALUE FOR REGISTER";I
30 INPUT A
40 POKE 16529,I
50 POKE 16530,A
60 LET C =USR 16514
70 NEXT I
80 PRINT "END OF LOAD"
90 STOP

```

That BASIC program, along with the machine-language program previously entered, work together to load the MSM5832 clock/calendar IC with its initial settings. The BASIC program asks for an input of the value to be stored in each of the 12 registers of the MSM5832. (Table 8 defines the registers and their allowable data ranges.) The BASIC program then calls the machine-language routine (line 60) which does the actual loading of the values.

Let us follow the operation of these programs line-by-line as they load a register in the MSM5832: Line 10 sets the first register to be loaded to register 0 (seconds register). Line 20 will print the register number and line prompt you to enter the value you want stored there.

After you enter a value, the ZX81 stores the register code in memory location 16529 (4091H) and stores the register val-

**TABLE 8—MSM5832 REGISTERS**

Register	Contents	DATA I/O				Allowable output range (decimal)
		D3	D2	D1	0	
0	SECONDS	x	x	x	x	0-9
1	TENS OF SECONDS	—	x	x	x	0-5
2	MINUTES	x	x	x	x	0-9
3	TENS OF MINUTES	—	x	x	x	0-5
4	HOURS	x	x	x	x	0-9
5	TENS OF HOURS	*	**	x	x	0-1/0-2†
6	DAY OF WEEK	—	x	x	x	0-6
7	DAYS	x	x	x	x	0-9
8	TENS OF DAYS	—	††	x	x	0-3
9	MONTHS	x	x	x	x	0-9
10	TENS OF MONTHS	—	—	—	x	0-1
11	YEARS	x	x	x	x	0-9
12	TENS OF YEARS	x	x	x	x	0-9

**Notes:**

- x Indicates that data can be either 1 or 0
- \* D3 = 1 for 24-hour format. D3 = 0 for 12-hour format
- \*\* D2 = 1 for PM. D2 = 0 for AM
- † Depends on D3
- †† D2 = 1 for 29 days in Feb. D2 = 0 for 28 days in Feb.

ue in location 16530 (4092H). Line 60 calls the machine-language subroutine.

The first thing the subroutine does is take the register code out of memory location 16529 (4091H) and send it to the MSM5832 via OUT device-code pulse 00H. (Recall from Part I of this series that that device code selects the MSM5832 for inputting and stores the register code in the 74LS75.) The machine-language routine then retrieves the value to be placed into the selected register from memory location 16530 (4092H). The ZX81 then sends the register value to the MSM5832 via the OUT device-code 08H. An OUT device-code 04H is then generated to de-select the MSM5832 so that it can resume normal timing operation. Program execution returns to the BASIC program and the remaining function registers are filled. When the last register is set, the ZX81 prints "end of load" and the program execution stops.

Table 9 is an example of the values that must be loaded to initially set the MSM5832 to: Sunday, April 18, 1983, 1:25:00 PM. At completion of the above program, the MSM5832 clock/calendar

**TABLE 9  
INITIAL REGISTER VALUES FOR  
SUNDAY, AUGUST 19, 1984**

Register code	Register value
0	0
1	0
2	5
3	2
4	1
5	4
6	6
7	9
8	1
9	8
10	0
11	4
12	8

IC will be loaded with initial values for time (\*hours, minutes, seconds), date (year, month, day), and day of the week.

**Reading the register contents**

Great—the MSM5832 knows the time and date, but we don't. A short program, however, will allow us to retrieve the time and date information from the MSM5832. To make room for the new retrieval program, clear the ZX81 with the NEW command. That will erase both the machine-language and the BASIC programs used to load the MSM5839 with initial values. Since a new machine-language routine is to be used, the BASIC program which loads hexadecimal machine code must be re-entered. If you SAVED the machine code entry program on cassette tape the first time you used it, it can be LOADED from tape. If not, you will have to type it again. (You can waste a lot of time that way, can't you?) After the hexadecimal machine-code entry program has been entered, you will need to reserve 39 memory locations for the machine-language program which retrieves the date and time values from the MSM5832. That is done via the REM statement:

1 REM (40 characters).

Type in the REM statement and load the machine-language program in Table 10, using the same method as you did earlier.

With the machine-language program in place, erase the entry program (lines 10 through 80) and enter the BASIC program in Table 11.

The BASIC program and machine-language routines work together to retrieve time and date information from the MSM5832. As the values of the 13 registers in the MSM5832 are retrieved, they are placed in memory locations 16540 through 16552. Table 6 lists the addresses and contents. (Those memory locations were reserved earlier by the REM state-

**TABLE 10—REGISTER RETRIEVAL**

06 40	LD B,40
0E 99	LD C,99
0A	LD A,(BC)
D3 00	OUT 00,A
3A 9A 40	LD A,(409A)
47	LD B,A
3A 9B 40	LD A,(409B)
4F	LD C,A
DB 00	IN A,00
E6 0F	AND 0F
02	LD (BC),A
D3 04	OUT 04,A
C9	RET

**TABLE 11—REGISTER RETRIEVAL**

```

800 LET C=0
810 LET D=156
820 FOR I=0 TO 12
830 POKE 16537,C
840 POKE 16538,64
850 POKE 16539,D
860 LET A=USR 16514
870 LET C=C+1
880 LET D=D+1
890 NEXT I
900 STOP
    
```

ment with 40 characters.) Let's follow the program through one complete register retrieval.

In lines 800 and 810, the initial register code (0 for seconds) and initial register content storage location are defined. In line 830, the initial register code is stored in location 16537 (409AH). In lines 840 and 850, the address of the initial register-content storage-location is placed into memory locations 16538 and 16539. Note that the address 16540 (409CH) has to be entered in two commands. Line 840 enters 64 (40H) and line 850 enters 156 (9CH). Line 860 calls the machine-language routine.

The first three instructions of the machine-language program place the contents of memory location 4099H (16537) into the Z80's accumulator. That value is the code that defines the MSM5832 register that will be accessed. (That location was previously loaded by line 830 before branching to the machine-language routine.) The OUT 00H.A instruction loads the 7475 (IC7 of the interface circuit) with the register code, and selects the MSM5832 for inputting. The next 4 instructions retrieve the address of where the MSM5832 register contents will be stored in the ZX81's memory. (That was also previously defined in the BASIC program, lines 840 and 850, before branching to the machine-language program.)

The instruction IN A, 00H inputs the MSM5832 register contents. AND 0FH masks the four higher-order bits to logic zeros, and LD (BC), A stores the MSM5832 register contents in the ZX81's memory.

The OUT 04H.A instruction deselects

*continued on page 98*

# BUILD THIS

## Infrared Transmitter and Receiver

STEVEN M. MARGOLIN



*You can add remote-control features to just about anything with an easy-to-build infrared transmitter/receiver pair.*

COMMUNICATION BY INFRARED LIGHT has found numerous applications in remotely controlling the operation of electronic equipment. If you don't believe that, just walk into any video store today. You'll find that many TV's and VCR's use infrared transmitters and receivers to change channels, set the volume level, or control videotape speed and direction.

That technology can be made practical for the electronics hobbyist. It is easier than you think to control some device, say a computer game, from a distance—without running wires around the room. Perhaps the best thing is that you don't have to spend a fortune to get started. We'll show you how to build an infrared (sometimes called IR) receiver/transmitter combination that you can experiment with and put to practical use. We'll show you one particular application example—a remote TV-channel selector (for TV's in which channels are selected by pushbuttons.) But we're sure that you'll discover practical applications for infrared communication on your own—you probably have a million going through your head right now.

When the infrared receiver and transmitter was designed, every effort was made to use as simple a circuit as possible and to use parts that are relatively easily available and inexpensive. That's because our goal is to bring infrared-communication

technology within easy reach of the hobbyist. If the price is kept low, the project becomes practical for many more hobby applications. But the circuits are not limited in potential applications just because they are simple to build. As we will see, the versatility of the receiver/transmitter design is limited only by your imagination.

The receiver/transmitter circuits contain CMOS IC's and few other components. That makes battery operation very feasible. However, we should point out that you can use TTL IC's instead of their CMOS equivalents. That would make battery operation impractical, however.

### Why infrared?

You may wonder why we would want to use infrared light for a remote-control project when any number of radio-frequency (RF) designs would do the job as well. One reason is that infrared light offers distinct advantages that, for the applications to be discussed, far outweigh those of RF circuits. For example, no tunable circuits are required—the circuitry simply pulses an infrared LED on and off. In addition, infrared light does not interfere with RF reception.

The problem with radio-frequency designs is that they require accurate tuning of both receiver and transmitter circuits. Also, RF circuits can be noisy and may

interfere with a neighbor's TV or radio reception. But more important, they are prohibited by the FCC's regulations regarding the use of unlicensed transmitters. Finally, RF circuits typically contain more devices not only to transmit carrier and information signals, but also to detect them and separate the transmitted data. Those characteristics not only add to the cost of the project, it means that the power requirement is greater, and battery use, if possible, will be limited.

We will admit, though, that RF does have at least one advantage over infrared light—transmission range: An RF design transmits its signal longer distances (even if the path is obstructed) than an infrared transmitter (whose beam path must be unobstructed) can. But if you think about it for a while, the range restriction is not necessarily a disadvantage: Most in-home remote-control applications are really in-room applications (such as controlling a TV). And the restriction on the unobstructed path for the infrared beam between the transmitter and receiver is not necessarily a disadvantage either: We can use another infrared transmitter/receiver pair in the room next door without any interference between units.

### The infrared transmitter

Let's begin our look at the remote control system with the infrared transmitter.

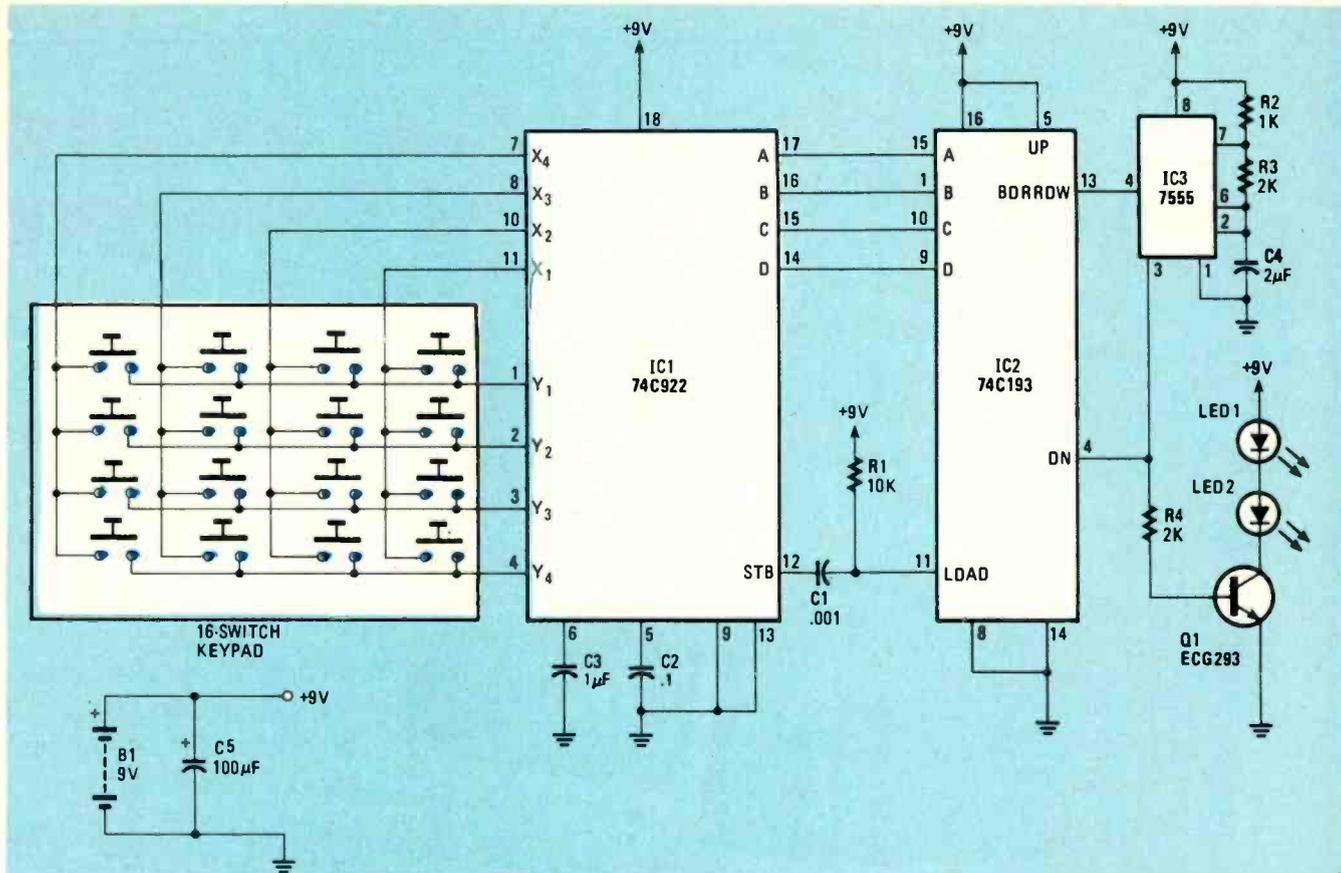


FIG. 1—INFRARED TRANSMITTER. To prolong the life of the battery, you might want to add a power switch.

Figure 1 shows its schematic. A 16-switch keypad, an X-Y matrix type, is connected to IC1, a 74C922 16-key keyboard encoder. That IC passes a 4-bit binary representation of the key number pressed to its outputs, A through D. Those outputs are applied to the DATA inputs of IC2, a 74C193 up/down counter.

Whenever a key is pressed, IC1 generates a data-available strobe signal at pin 12, which is differentiated by C1 and R1 to produce a low-going spike at pin 11, the LOAD input of IC2. When the 4-bit data is loaded into IC2, the BORROW output (pin 13) goes high to enable the clock. IC3, a 7555 timer. The clock signal is sent to the COUNT DOWN input of IC2, causing it to count down from the value that was first loaded into its registers. When the count reaches zero, the BORROW pin returns low, shutting off IC3. The pulses that clock IC2 also turn transistor Q1 on and off, which "fires" the infrared-emitting diodes, LED1 and LED2.

The LED's therefore pulse the exact number of times it takes IC2 to count down to zero—we have a circuit that generates a number of infrared pulses that corresponds to the key that was pressed. Actually, only 15 of the 16 keys, 1 through 15, generate pulses—the "0" key does not produce an output which can be pulsed.

Note that the clock speed could be varied to yield a faster pulse or transmission

rate. For the component values shown, IC3 operates at about 150 Hz; however, too fast a rate diminishes the pulse current through the LED's, thus reducing the transmission range. At a rate of 150 Hz, the transmitter range is about 15 feet.

Since the transmitter uses CMOS IC's, the current requirement from a 9-volt battery is minimal—about 7 milliamps when no key is pressed. The current increases to about 60 mA when the maximum number of pulses (15) is sent.

### The receiver

The receiver circuit is somewhat more complex than the transmitter because it must not only detect the transmitted pulses, but count and decode them as well. We'll start our description with a look at the basic circuit; we'll then add features to it.

Figure 2 shows the basic receiver circuit. The infrared pulses are detected by phototransistor Q2 and amplified by IC4, which is configured for very high gain. The output of IC4 is fed to a Schmitt trigger, IC5, which conditions ("squares up") the pulses to be counted by IC6, a 74C193 up/down counter. The output of IC6 (at pins 3, 2, 6, and 7) is the binary equivalent of the number of pulses received, 0001 to 1111.

The receiver circuit described thus far yields some interesting applications. For

example, the binary outputs of IC6 could be tied to an input port of a computer programmed to respond in some way to the received commands. A videogame remote control could be one application. Note, however, in this circuit configuration IC6 continually adds successive pulses as they are counted. So, if "0001" is present on IC6's outputs, and the next pulse train counted consists of two pulses, IC6's outputs will become "0011," the binary equivalent of three. That can be modified by allowing the computer to clear the 74C193 after the input port data is read. Figure 3 shows a possible application of that kind. Note that a buffer with three-state outputs is used to effectively disconnect the 74C193 from the data bus when not in use.

To expand the receiver's capability even more, we could add timing circuits that would freeze the outputs of IC6 for each pulse stream it counts. The outputs would remain stable until a new value is received. The addition to the circuit, IC7, a 4098 dual one-shot, is shown in Figure 4. The new circuit operates as follows: One half of IC7 triggers on the leading edge of the first pulse sent and immediately triggers its second half, which sends a CLEAR pulse to IC6. So, before IC6 can count the first transmitted pulse, the counter is cleared and allowed to count only the remaining pulses. The result is that the number of pulses detected is one less than what is transmitted. We can use that fea-

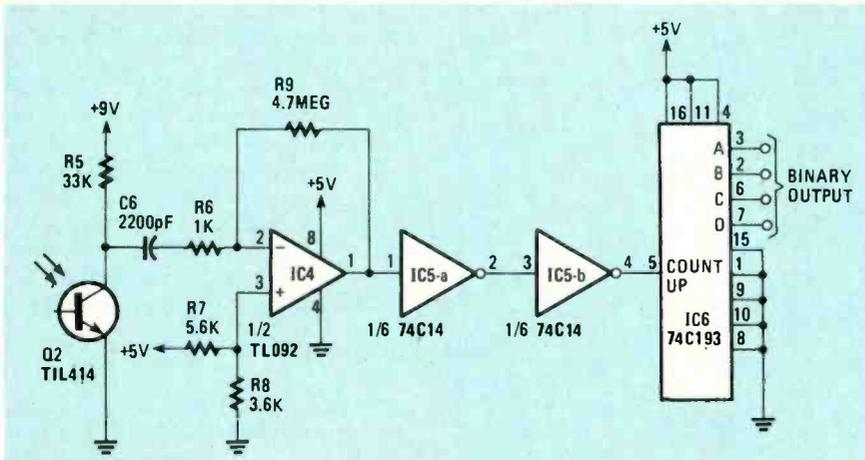


FIG. 2—THE BASIC INFRARED RECEIVER counts the pulses sent from the transmitter. The number it counts is output from IC6.

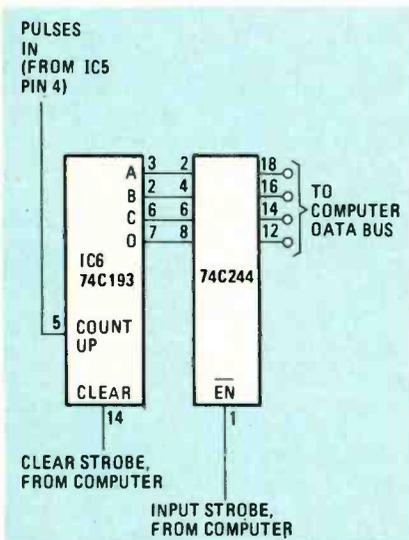


FIG. 3—AS MORE PULSES ARE COUNTED, they are merely added to the output already on IC6. You could use strobes from a computer to clear the output and enable a 3-state buffer.

ture to our advantage: By transmitting one pulse, we can clear all outputs to 0000. The pulse that is sent is effectively ignored by IC6, due to IC7's clear-before-count action. Alternately, the maximum number of pulses this circuit may count is 14, yielding a "1110" output.

Simply by adding another CMOS one-shot, IC8, shown in Fig. 5, we enable IC6 to momentarily hold its 4-bit outputs, then be reset and readied for the next value. Now, when IC7 reacts to the first pulse it received, it triggers IC8 to remove the high state on IC6's CLEAR input. That enables IC6 to count all the pulses and display the number on its outputs. But, IC5 times out after about .5 second, its  $\bar{Q}$  output, pin 11, returns high and clears IC6 to zero. IC6 may now count the next pulse stream, output the value briefly, and be reset.

But what if we can't use a binary output and want the receiver's outputs in a different form? This is easily done with the

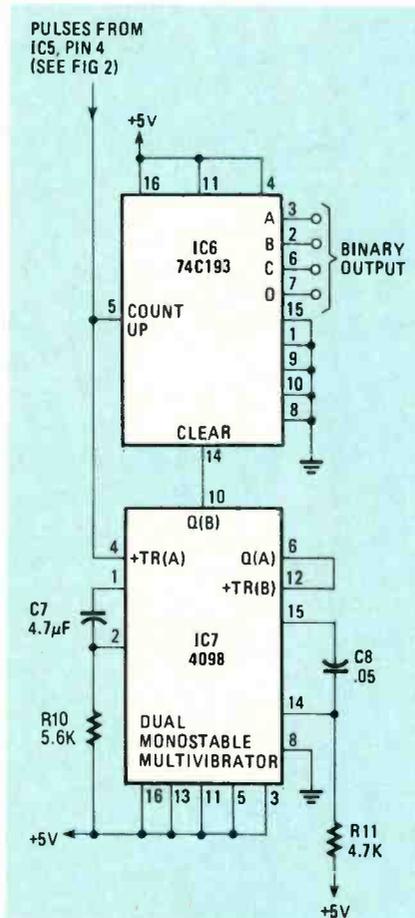


FIG. 4—A DUAL ONE-SHOT, IC7, sends a CLEAR pulse to IC6 upon receipt of an initial pulse.

circuit shown in Fig. 6. That circuit uses a one-of-sixteen decoder, IC9, to supply 15 unique output signals for a variety of control applications, such as a channel selector for a TV with push-button channel switches. By using one of the two timing circuit designs just mentioned, we allow each selected output to be held momentarily, or be frozen until a different output is selected.

The new circuit operates in the same

## PARTS LIST

All resistors 1/4-watt, 10% unless otherwise noted.

- R1,R12,R14,R16—10,000 ohms
- R2,R6—1000 ohms
- R3,R4—2000 ohms
- R5—33,000 ohms
- R7,R10—5600 ohms
- R8—3600 ohms
- R9—4.7 megohms
- R11,R13,R15—4700 ohms

### Capacitors

- C1—.001  $\mu$ F, ceramic disc
- C2—.1  $\mu$ F, ceramic disc
- C3—1  $\mu$ F, 16 volts, electrolytic
- C4—2  $\mu$ F,
- C5—100  $\mu$ F,
- C6—2200 pF, ceramic disc
- C7—4.7  $\mu$ F, 16 volts, electrolytic
- C8—0.05  $\mu$ F
- C9—10  $\mu$ F, 16 volts, electrolytic

### Semiconductors

- IC1—74C922 16-key keyboard encoder
  - IC2, IC6—74C193 synchronous up/down dual clock counter
  - IC3—7555 timer
  - IC4—TL092 op-amp
  - IC5—74C14 hex inverter
  - IC7—4098 dual monostable multivibrator
  - IC8—4047 monostable/astable multivibrator
  - IC9—4514 4-to-16 line decoder (or 4545—see text)
  - IC10—74C74 dual D-type flip-flop
  - Q1—ECG293
  - Q2—TIL414
  - Q3,Q4—2N4401
  - LED1,LED2—XC880-A infrared LED (Radio Shack 276-143 or similar)
- Other components**
- RY1—SPDT miniature relay (Radio Shack 275-240 or similar)
  - RY2—DPDT relay (Radio Shack 275-215 or similar)
  - B1—9-volts, transistor type

way, except that when the first pulse is detected, IC9 is disabled by the high-going trigger pulse from pin 6 of IC7. (That's done to prevent IC9's outputs from cycling as IC6's outputs change states during counting.) After the last pulse is counted, IC7 times out and enables IC9. By that time, the inputs to IC9 are stable and are decoded to select the appropriate output. IC9 may either be a 4514 (as shown) or a 4515 CMOS IC. If an application requires active-high signals, use a 4514. If the application requires active-low signals, use a 4515.

The receiver may be powered by a 9-volt battery and regulated by a voltage regulator to +5 volts. Current drain is between 7 and 15 milliamps, depending on how many of the additional IC's are used. Of course, the receiver could be powered by the circuit in which it is used; in this case, the receiver's voltage regulator might not be necessary.

Although not shown in the schematic, it's a good idea to add bypass capacitors (about .01–.1  $\mu$ F) between the positive supply pin and ground at each IC. (They

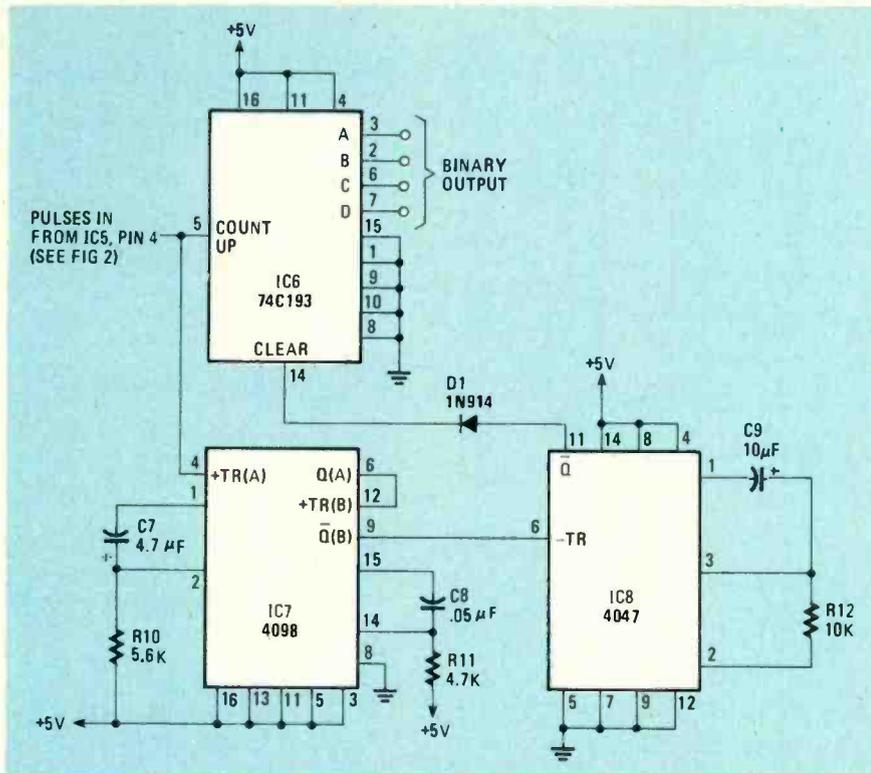


FIG. 5—THE ADDITION OF IC8 causes the output of IC6 to be automatically reset to zero after about ½ second.

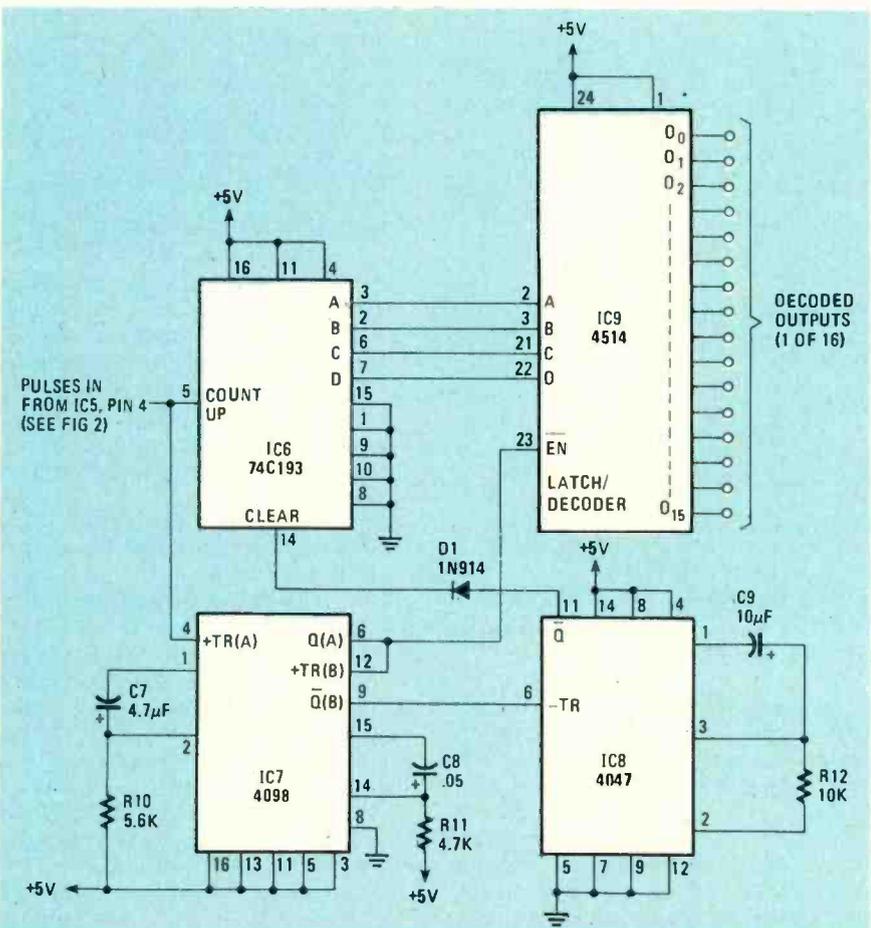


FIG. 6—THE 4-BIT OUTPUT of IC6 can be converted to a one-of-sixteen output with the addition of IC9, a 4514 latch/decoder.

should be mounted close to the IC.) Those bypass capacitors are especially important if the receiver is mounted in a "noisy" environment, such as inside a TV. Another step you should take to decrease on-board noise is to add a 100-μF capacitor between power and ground where the power cable is connected to the board. You might also find it necessary to add a .1μF bypass capacitor across the phototransistor (where the leads are connected to the board).

### Remote control TV

Using the circuitry shown in Fig. 6, we'll take a look at one particular application in more detail—a wireless TV-channel selector for a TV that uses a row of push-button channel switches. First, though, a word of caution: Adding remote control to a TV requires connecting wires to the circuitry inside a TV set. Extreme care must be taken when making connections to the switch board inside the TV. Obtain a copy of the set's schematic and be familiar with it before opening the set. Keep in mind that in making such connections, you may be voiding the manufacturer's warranty on the set. More important, remember **there are potentially dangerous voltages present in the set, even when it is unplugged from the AC line.**

The most critical design consideration in this receiver is to make the unit completely isolated from the TV's circuitry. We can use small relays to act as the channel selector switches (so that there are no electrical connections between the relay's contacts and the infrared-receiver circuitry). Do not attempt to bypass that safety function (unless other electrically isolated devices, such as opto-isolators, are used). The infrared receiver could be battery powered. But because it's likely that you don't need a portable receiver, you can use a small power supply, such as a "battery-eliminator" unit.

Figure 7-a shows one relay circuit that could be activated by one of the outputs of IC9. You may want to reserve one switch for muting the TV's sound, as is shown in Figure 7-b. For that feature, a 74C74 D-type flip-flop is added to hold the relay on for as long as the mute command is transmitted again. Note that a speaker-substitution resistor is connected to one set of relay contacts. The resistor's value must match the impedance and power rating of your set's speaker.

The original design of the receiver/transmitter was laid out on perforated construction board and hard-wired together as shown in Fig. 8—the wiring of the circuits is not very critical. Of course, you could use a printed-circuit board or another construction method. Enclose the phototransistor in a small black tube, with a diameter of about ½ inch; that reduces

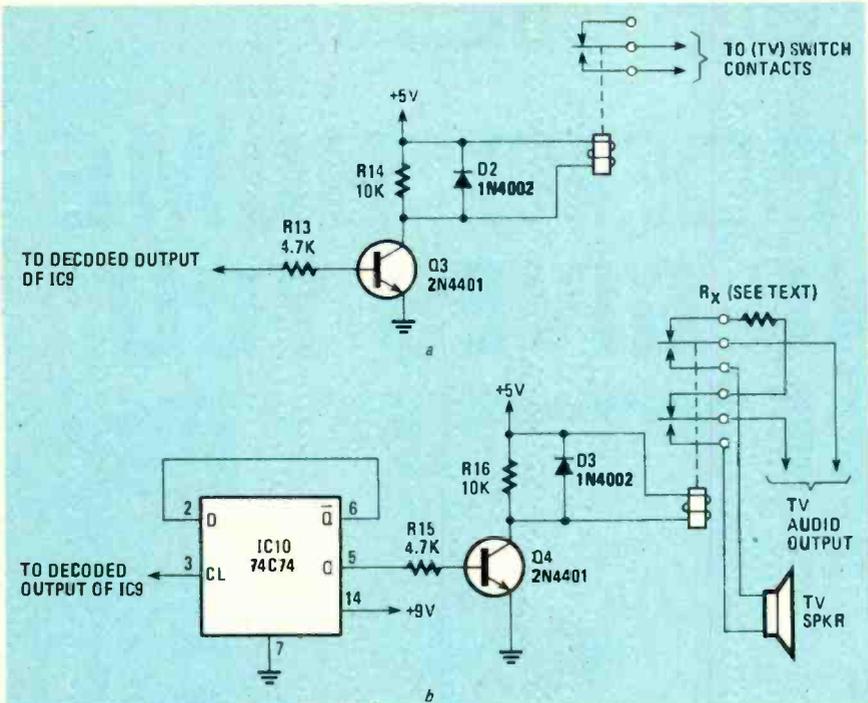


FIG. 7—THE OUTPUTS FROM IC9 can be used to turn on relays. In a, relay RY1 is set up to close switch contacts on a TV. In b, relay RY2 is set up to act as a remote muting switch.

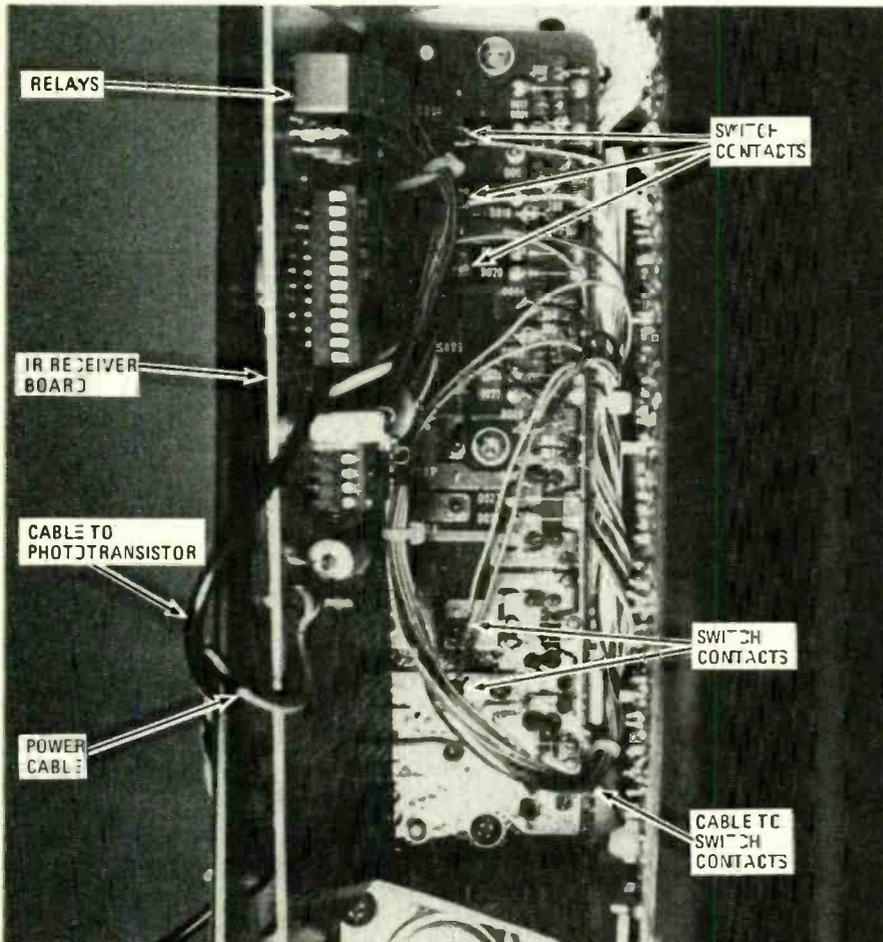


FIG. 9—THE RECEIVER BOARD installed in TV receiver. Note the connections to the TV switch-board.

the amount of ambient light falling on the photo device and improves reception.

The receiver can be built into a plastic

box that can be mounted to the rear of the set. If space permits, you can mount the receiver board inside the TV, as shown in

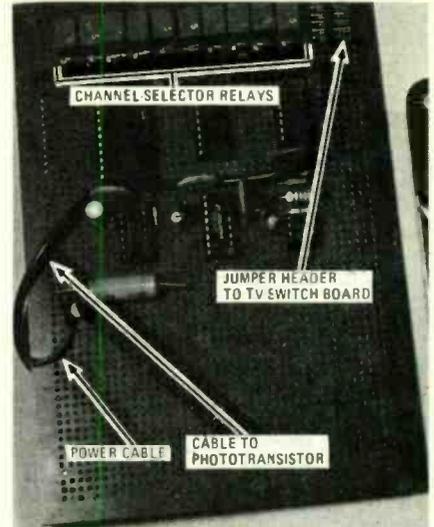


FIG. 8—THE INFRARED RECEIVER BOARD. Note that construction is not critical.

Fig. 9. The phototransistor and housing should be attached to a length of shielded cable, and the sensor should be mounted on the top or side of the TV, toward the front of the set.

The transmitter can be enclosed in a small plastic box and the keys labeled to correspond to the channel numbers and mute feature. The author's prototype used a membrane keyboard salvaged from a calculator. That, of course, is not a requirement; you can use any matrix arrangement of 16 keys.

### Troubleshooting

If you double check the wiring of all circuits before powering up the project, you shouldn't have any trouble. Even if you do, troubleshooting a faulty circuit should not present too many problems because the receiver and transmitter designs are fairly simple. Checking the transmitter can be done quickly by connecting an oscilloscope probe to the collector of Q1. Press one of the keys and watch for the corresponding number of pulses at this point. Look for the pulses at the base of Q1, also. Q1 may be faulty if no pulses appear at the collector, but are present at the base.


The receiver should be checked in stages. Using an oscilloscope, observe the output of phototransistor Q2 for a series of pulses from the transmitter. Trace through the circuit to locate the point where the pulses are no longer present. Check the output of IC4 and both sections of IC5. If the pulses are present, verify the operation of the timing circuits, IC7 and IC8, by looking for the various output pulses at their Q outputs while transmitting a number.

By now, you must certainly have a sense of how versatile this infrared communication project is and how you can enhance other projects by providing this wireless communication link. R-E

# In Computer Electronics...

# NTS INTRONIC™ HOME TRAINING GIVES YOU THE EDGE

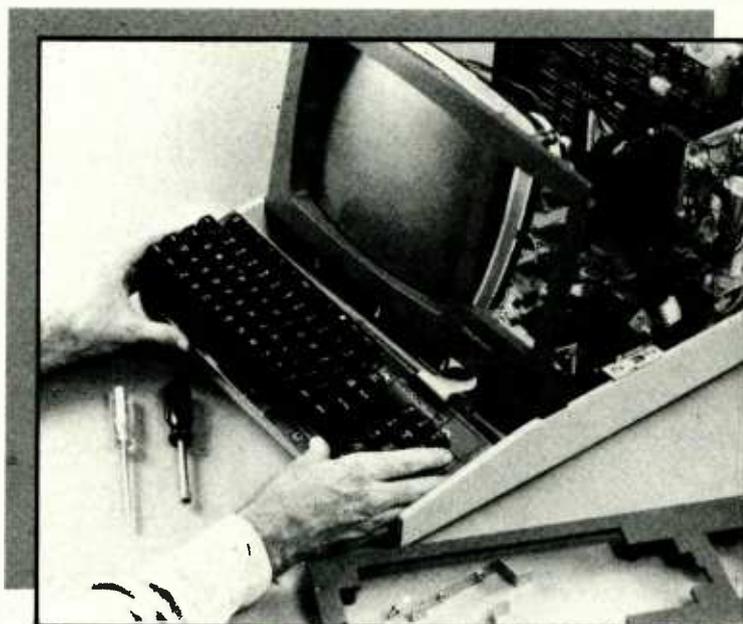**The competition for High-Technology careers is strong, and the rewards are great. Give yourself the edge you need by training with NTS.**



NTS INTRONIC home training provides you with a special kind of "Hands-On" experience that prepares you better, develops your skills faster. You advance as quickly as you wish, working with actual circuits, diagrams, schematics, and state-of-the-art hardware. There are a dozen different NTS programs in electronics to help you develop and reach your potential. They range from basics to advanced areas in several fields. And the ALL-NEW NTS course catalog spells it all out. It's free, and does not obligate you in any way. Send for it today.

## **A GROWTH INDUSTRY**

High-Technology is a growth industry. The evidence is clear, and most observers predict a steady expansion due to a relatively strong flow of investment capital into computers, electronics and precision instruments. Sales of computers alone will reach an estimated ten million units this year. This means challenges and new

employment opportunities, especially in servicing and maintenance. Computer servicing skills can best be learned by working directly on field-type equipment. NTS electronic hardware is selected and developed especially for the training program with which it is associated. You learn by doing, by assembling, by performing tests and experiments, covering principles of computer electronics, microprocessor troubleshooting, and circuitry.

## **MICROCOMPUTERS**

NTS offers three programs in computer electronics. You will receive training covering solid-state devices, digital logic circuitry, and the fundamentals of the computer itself. Instruction includes micro-control technology and detailed operation of microcomputers. These courses will prepare you for entry-level in many facets of the computer industry such as field service and customer engineering as well as programming. In addition to written texts your course includes the NTS/HEATH disc-drive computer which you assemble as part of the training process. The assembly and use of the computer will serve to reinforce practical application of principles.

## MICROPROCESSOR TECHNOLOGY


The field of industrial and microprocessor technology encompasses the application of electronic microprocessor control principles. Your course takes you from fundamentals of digital electronics and associated circuitry through the application of the microprocessor as a control device. You will learn how to move and manipulate instructions and information. The microprocessor trainer included in your course is a microcomputer system designed as a practical tool for learning the use of software and hardware techniques utilized in the linking of microprocessors to various systems.

## DIGITAL ELECTRONICS

The NTS Compu-Trainer is a fascinating solid-state device which you will build in order to perform over ninety logic circuit experiments. These experiments serve to emphasize an area of electronics which is essential to the understanding of state-of-the-art control equipment; they are also extremely important to those wanting to pursue a career in computer servicing. Separate courses involving the Compu-Trainer are also available in Microcomputer Servicing and Digital/Analog Electronics.
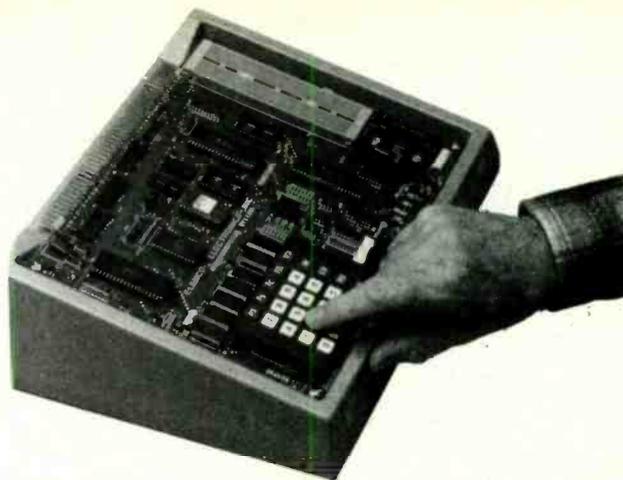
## ROBOTICS & VIDEO TECHNOLOGY

Other NTS courses cover a wide range of specialization. In Robotics, the NTS/Heath Hero I is included to train you in robotic applications in




manufacturing processes. In Video technology, a new course features the advanced NTS/Heath Z Chassis "Smart Set" color TV with computer space command remote control and space phone. This is an excellent program for those interested in a career in video servicing with microcomputer basics.
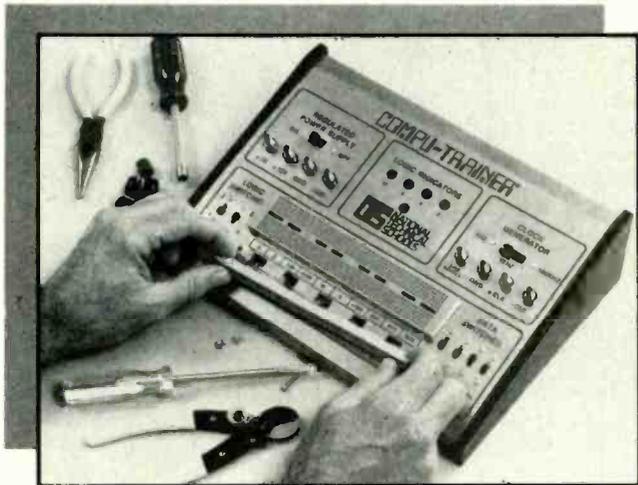
## EARN CEU CREDITS

America's industrial giants are turning more and more frequently to home study as an effective way to upgrade employee skills. You benefit from the experience NTS has gained in its 79 years as a leader in technical training. The skills and experience gained in the building of kits and test equipment provide you with training that cannot be duplicated. And, depending on the program you select, you can earn up to 30 CEU credits for successful completion. Complete details included in the catalog.



Use the mail-in card or fill out and mail the coupon. Indicate the field of your choice. (One, only please.) FREE full color catalog will be sent to you by return mail.



NO OBLIGATION NO SALESMAN WILL CALL

**NTS NATIONAL TECHNICAL SCHOOLS**

TECHNICAL TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 Sp. Figueroa St., Los Angeles, CA 90037

**NATIONAL TECHNICAL SCHOOLS** Dept 206-084  
4000 South Figueroa Street, Los Angeles, CA 90037

Please send FREE color catalog on course checked below:

- |   |   |
|---|---|
| <input type="checkbox"/> Robotics                       | <input type="checkbox"/> Computer Electronics |
| <input type="checkbox"/> Digital Electronics            | <input type="checkbox"/> Video Technology     |
| <input type="checkbox"/> Auto Mechanics                 | <input type="checkbox"/> Home Appliances      |
| <input type="checkbox"/> Air Conditioning/Solar Heating |   |

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Apt. \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
Zip \_\_\_\_\_ Phone ( ) \_\_\_\_\_

- Check if interested ONLY in classroom training in Los Angeles  
 Check if interested in G.I. Bill Information.

# DESIGNING WITH LINEAR IC'S

A look at differential and instrumentation amplifiers, and how to use them.

JOSEPH J. CARR

**Part 4** THE AMPLIFIERS DISCUSSED thus far in this series have all been single-ended; that is, they have a single input that is referenced to either ground or the power-supply common. In this part of the series, we are going to discuss the differential-input amplifier. A differential amplifier uses two ground-referenced inputs; one inverting, the other noninverting. Those inputs have an equal but opposite effect on the output voltage. As a result, applying equal voltages to the two inputs will cause cancellation; that is, zero output voltage. That phenomenon is called *Common Mode Rejection (CMR)*, and is expressed by the *Common Mode Rejection Ratio (CMRR)* specification. Devices are available with CMRR ratings of 60 dB to 120 dB; the higher the rating the better.

Differential amplifiers find extensive use in scientific and medical instrumentation. The electrocardiograph (ECG) amplifier is an example. The ECG amplifier must acquire a 1-millivolt signal generated by the heart, and amplify it to the 1 volt or so needed to drive an oscilloscope or strip-chart recorder. Thus, the ECG amplifier needs a gain of 1000 or so. The signals for the ECG amplifier are taken from the patient's limbs, with the right leg (RL) being common. For example, the "lead I" ECG signal uses the right arm (RA), left arm (LA), and RL signals. Since the bioelectrodes used to acquire the signal are high impedance, and the system is used in the presence of 60-Hz electric fields from local power lines, a substantial amount of 60-Hz signal pickup can be expected. If it were not for the CMRR of the differential ECG amplifier, the 60-Hz interference would be several

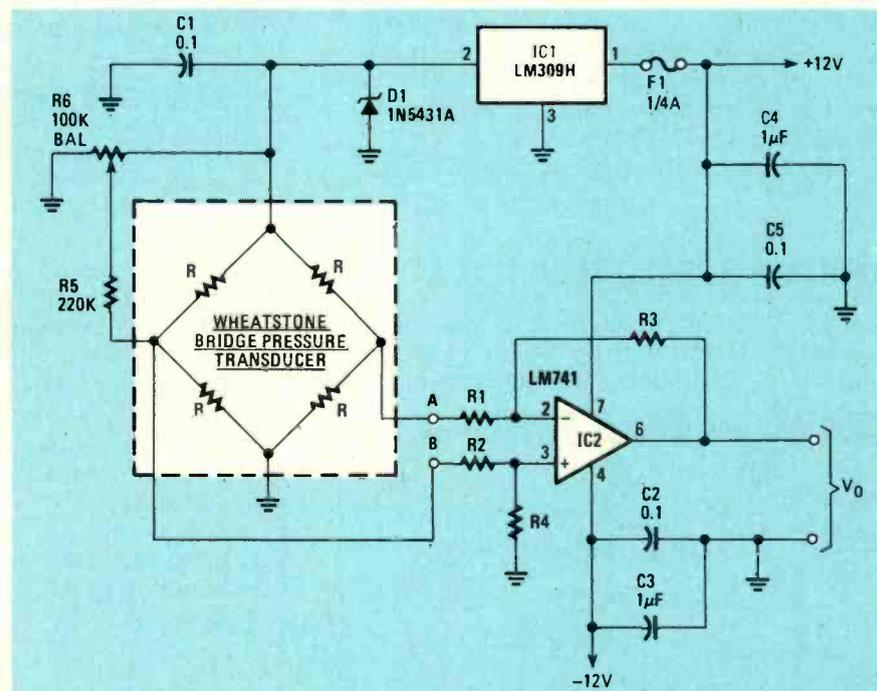


FIG. 2—DIFFERENTIAL AMPLIFIERS are used in a wide variety of medical applications. Here, one is used in a circuit that uses a Wheatstone-bridge transducer to measure arterial blood pressure.

hundred times higher than the desired signal. But, since the 60-Hz fields affect both leads equally, the 60-Hz signal is common mode, so it will be nulled to zero.

Ordinary operational amplifiers have differential inputs, so they can be used to form differential amplifiers. Figure 1 shows the simplest form of DC differential amplifier using an op-amp. The differential voltage gain is given by:

$$A_{VD} = R3/R1 \quad (1)$$

provided that  $R1 = R2$ , and  $R3 = R4$ . The value of  $R1$  and  $R2$  must be high enough to not load the signal source. A Wheatstone-bridge transducer might have

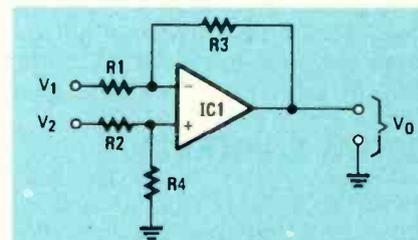


FIG. 1—THE SIMPLEST form of DC differential amplifier using an op-amp.

a source resistance of, say, 200 ohms. By the "rule-of-ten," then, the minimum value of  $R1$  and  $R2$  should be 2000 ohms.

In order to illustrate the design method, let's consider a practical example. Suppose we have a Wheatstone-bridge transducer that measures arterial blood pressure. Assume a transducer sensitivity of  $40 \mu\text{V}/(\text{V})(\text{P})$  (where P is pressure, measured in units of torr). Design a simple pressure amplifier that has an output scale-factor of 10 mV-per-torr and a maximum range of 300 torr. Figure 2 shows the required circuit, while Table 1 shows details of the calculations and the specifications for our circuit.

The Wheatstone bridge requires a DC-

**TABLE 1**  
**Specifications**

Sensitivity of Transducer:

$$\phi = \frac{40 \mu\text{V}}{\text{V torr}}$$

Full scale pressure: 300 torr

Output scale factor (S): 10 mV/torr or 3000 mV/300 torr

Transducer excitation potential: 5 volts

**Calculations**

1. Output voltage from transducer at full scale:

$$V_o = \phi V_e P_{\text{max}}$$

$$V_o = \frac{40 \mu\text{V}}{\text{V torr}} \times 5\text{V} \times 300 \text{ torr}$$

$$V_o = (40 \mu\text{V}) (5) (300) = 60,000 \mu\text{V}$$

$$V_o = 60 \text{ mV @ } 300 \text{ torr}$$

2. Find the required gain by dividing the output scale factor by the transducer output. (Note: Use values taken at same pressure, e.g. 300 torr.)

$$A_{VD} = \frac{S}{V_o} = \frac{3\text{V}}{\frac{300 \text{ torr}}{60 \text{ mV}}} = \frac{3000}{60} = 50$$

excitation voltage, which is provided from a +5-volt regulator (IC1). The LM-309H selected for that delivers 100 mA at +5 volts DC, so it can handle transducers with equivalent resistances down to 50 ohms.

The Zener diode (D1) in Fig. 2 is not used to regulated voltage, but to protect the transducer from faults in IC1. The diode is a 1N5431A, or any equivalent 6.2-volt, 5-watt Zener. Most resistive transducers have a maximum excitation voltage limit of 7.5- to 10-volts DC. A shorted IC1 would place +12-volts DC across the transducer, causing it to burn out. If IC1 shorts out, however, the excessive voltage will turn on D1, which conducts heavily and thereby blows fuse F1.

Potentiometer R6 is used as a balance control, and in most cases will be panel-mounted for operator use. It works by injecting a current into one arm of the bridge to counter offsets. All transducers have some inherent unbalance. In addition, there is also the possibility of induced unbalance. In the arterial-blood-pressure transducer, for example, hydrostatic pressure-heads (which can be positive or negative) develop from differences in patient position and in the position of the interconnections between the patient and the transducer. Potentiometer R6 eliminates those problems.

Under most circumstances, potentiometer R6 is adjusted with the parameter it detects equal to zero. In our hypothetical

blood-pressure amplifier, the potentiometer is adjusted to zero the output of IC2 when the transducer is open to atmosphere. That establishes a baseline; when the system is closed again, the transducer will measure gage pressure—i.e. pressure above and below atmosphere.

To provide the required gain of 50, we must select resistor values that have the ratio R3/R1 = 50. Furthermore, since the transducer has a Thevenin-equivalent resistance of 200 ohms, we must select R1 greater than or equal to 2000 ohms.

The process of finding suitable resistors is a matter of trial and error using standard values. Equation 1 may have to be worked several times to find a combination in which both R3 and R1 are standard values. Here, however, it is simple because 2000 ohms (the minimum value permissible for R1) is a standard value; fifty times 2000 ohms is 100,000 ohms, also a standard value. We accomplish our goal, therefore, by setting R1 = R2 = 2000 ohms, and R3 = R4 = 100 kilohms.

Maintenance of an acceptable CMRR requires that we specify resistors R1 through R4 as 1% tolerance, low-drift types. We might also want to build in a CMRR control. An example of that would be to replace R4 in Fig. 1 with a series combination of a fixed resistor and a potentiometer. The potentiometer should have a value not more than 20 percent of the total value of the series combination, and the total value of the series combination must be capable of swinging above and below the nominal R4 value.

Adjusting the CMRR control is best done with the transducer disconnected. Short together the differential amplifier's inputs and then connect the inputs to an

AC sinewave source (100 to 1000 Hz). Adjust the CMRR control for minimum output (zero if attainable).

The principal problems facing the simple circuit presented thus far are similar to those that plague the inverting follower; input-impedance limitations and gain limitations. We can overcome those by using the instrumentation amplifier.

**Instrumentation amplifiers**

The basic instrumentation-amplifier (IA) circuit is shown in Fig. 3. That particular design requires three operational amplifiers. If possible, IC1 and IC2 should be a dual op-amp so that drift problems are minimized by keeping the two input devices in the same thermal environment.

Amplifiers IC1 and IC2 are operated as noninverting followers, so the overall input impedance of the IA is extremely high. Amplifier IC3 is the IA output stage, and is operated as a simple DC differential amplifier.


The differential voltage-gain is given by the following expression:

$$A_{VD} = \left[ \frac{2R2}{R1} + 1 \right] \left[ \frac{R6}{R4} \right] \quad (2)$$

provided that R1 = R2, R4 = R5, and R6 = R7. The term in the first set of brackets is the gain of IC1-IC2, while the term in the second set of brackets is the gain of IC3.

Having two stages gives us more flexibility when juggling resistance values to get precise gains. The overall gain is the product of the gain of the two stages, so we can increase one or decrease the other in order to force-fit the values into the standard values normally available.

The IA would be selected when either

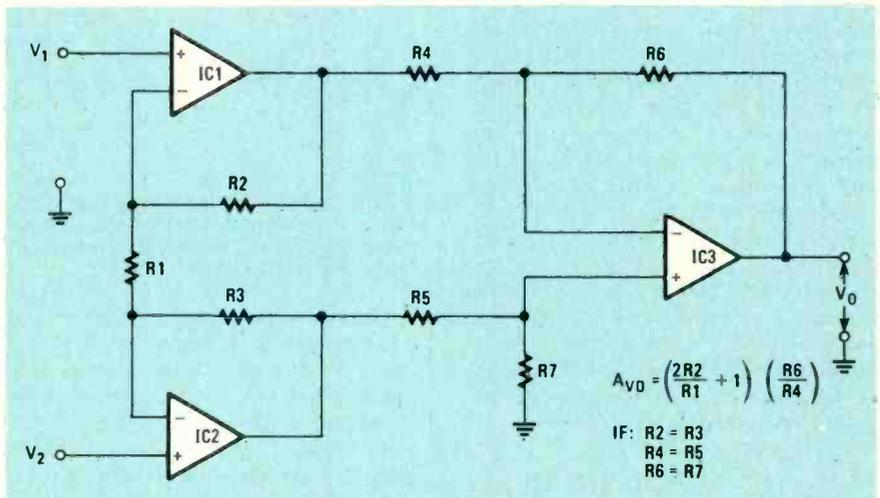

**FIG. 3—A BASIC INSTRUMENTATION AMPLIFIER.** Three op-amps are used: IC1 and IC2 are configured as non-inverting followers while IC3, the output stage, is a differential amplifier.

high gain or high input-impedance is needed. There are certain applications where those are required, for instance when certain chemical electrodes and most bioelectric amplifiers are used.

The circuit in Fig. 3 is a DC amplifier, so it can be used to amplify signal frequencies from DC to the upper limit of the amplifier bandwidth. Some applications, however, cannot tolerate a DC amplifier. The ECG amplifier, for example, has to contend with a half-cell potential formed when metallic electrodes are connected to skin through an electrolytic gel; in other words, a battery is formed. The half-cell potential is seen as an input offset by the amplifier, so that can produce problems. The solution is use AC-coupling.

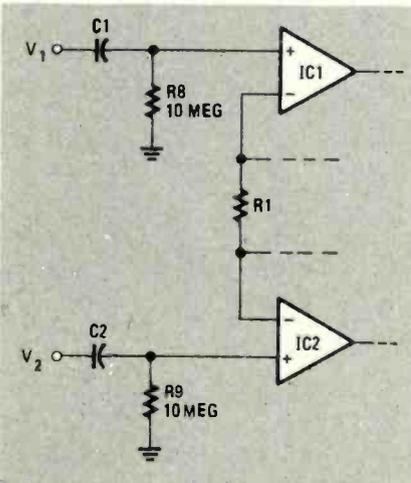


FIG. 4—WHEN THE INPUT to a circuit is AC-coupled, capacitors are used to block any DC.

Figure 4 shows the input circuit of the IA modified for AC-coupling. The capacitor in series with each input blocks the DC component. If the op-amp input is truly an infinite impedance, then the 10-megohm resistors are not needed. But real op-amps do have bias currents in the input circuits, so the capacitors will accumulate charge. The effect of that charge is to place a DC voltage in series with the input. The amplifier would see that voltage as a valid DC offset signal, which would eventually cause the amplifier to latch up. The solution is to ground the resistor so that the charge on the capacitor is drained off. In order to prevent degradation of the input impedance, the value of those resistors needs to be very high; 10 megohms, such as is used here, is usually selected.

Let's next see how to find the values for C1 and C2. Assuming that the input impedance is very much higher than 10 megohms (or whatever value is selected for the input resistor), the low-end frequency response is set by:

$$f_L = \frac{1}{2\pi RC} \quad (3)$$

Or, if 10 megohms is used, we can rearrange the "standard" formula to find what

we really want to know—what value capacitor will yield the specified frequency response. That is found from:

$$C = \frac{1.6 \times 10^{-2}}{f} \quad (4)$$

where C is capacitance in microfarads and f is the frequency in hertz.

Lets work an example. An ECG amplifier requires a frequency response of 0.05 Hz to 100 Hz. Select a capacitance value for C1 and C2 in Fig. 4 that will result in 0.05-Hz lower limit.  $C = (1.6 \times 10^{-2}) / (0.05 \text{ Hz}) = 0.32 \mu\text{F}$ . Since 0.33  $\mu\text{F}$  is the next lower standard value, specify 0.33  $\mu\text{F}$  for C1 and C2 in the final design.

### IC instrumentation amplifiers

The integrated circuit instrumentation amplifier (ICIA) combines in one package all of the components required to make an IA, with the possible exception of a single gain-setting resistor (R1 in Fig. 3).

The ICIA is not usually cheap, at least when compared with 741-family devices, yet it is often the most economical selection. Also, the IC packaging confers certain assembly advantages, and the ratings of the ICIA are often better than 741-family devices. The proper cost comparison would be between the ICIA and an ordinary discrete IA built from precision resistors and three premium-grade op-amps.

Figure 5 shows the National Semiconductor LM-363 device. Three versions of that device, with the difference between them being the gain, are available. Those are the LM-363-10, LM-363-100 and LM-363-500, which offer gains of 10, 100, and 500, respectively.

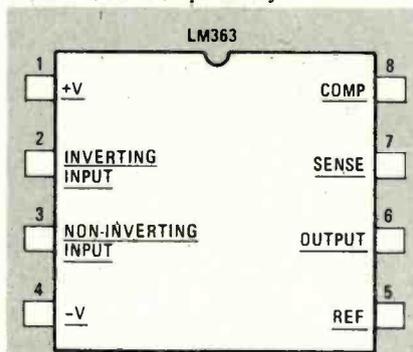


FIG. 5—THE INSTRUMENTATION AMPLIFIER is available in IC form. The pinout for one such IC, the LM-363, is shown here.

Ordinarily, the LM-363 is connected in a circuit such as the one shown in Fig. 6. The COMPENSATION terminal (pin 8) is connected to a series RC network for frequency-response tailoring. The REFERENCE terminal (pin 5) is connected to ground, and SENSE (pin 7) is connected to the output. No external components are needed to set gain as that is fixed. The IC comes in an eight-pin metal case.

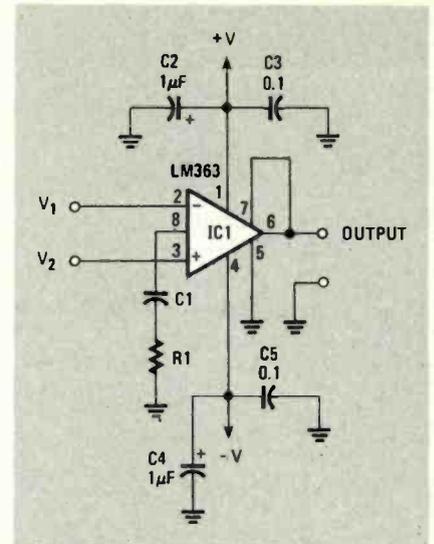


FIG. 6—THE SERIES R-C NETWORK is used to tailor the frequency response of the circuit, thus the values of C1 and R1 will vary according to the application.

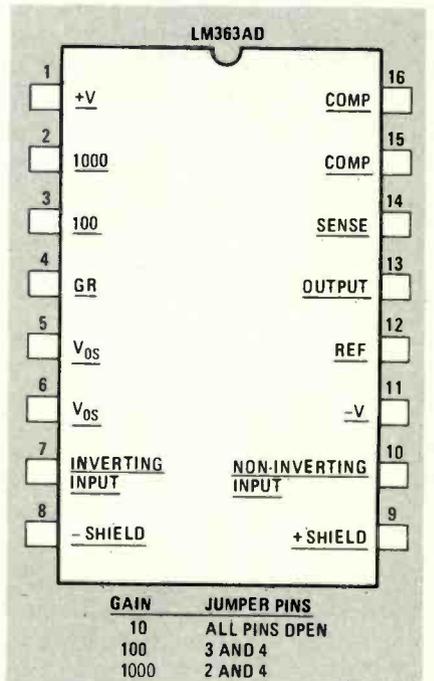


FIG. 7—PINOUT of the LM-363AD. The gain for that device is pin-selectable.

Another version of the LM-363, the LM-363-AD, is shown in Fig. 7. That 14-pin DIP also features fixed gain, but three selectable gain levels—10, 100, and 1000—are available in a single device. The gain is set by shorting the GR terminal (pin 4) and the gain terminals,  $\times 100$  (pin 3) and  $\times 1000$  (pin 2) as shown in Fig. 7.

The LM-363-AD has two terminals that may look a little strange; + SHIELD and - SHIELD. Those terminals are used to drive the input-wire shield (i.e. when shielded cable is used) with a sample of the signal. A shield treated in that manner is called a guard shield, and tends to im-

continued on page 88

## Cmos Analog


IN THE "OLD" DAYS—WHEN TTL (Transistor-Transistor Logic) was the only game in town—all sorts of hassles used to crop up when you designed circuitry that had both digital and analog elements. Not only were there different voltage requirements for each section, but transients generated by one section of the circuit were a problem for the other section. All sorts of design tricks had to be dreamed up if you expected the circuit to be reliable and glitch-free.

Designing the interface portion of the circuit also presented its own special problems. Schemes of incredibly complex circuitry had to be dumped in the middle of an otherwise sane and orderly design. The benefits you could enjoy by using digital logic to control analog signals were often outweighed by the problems inherent in the design.

Fortunately those days are gone forever. With the introduction of CMOS (Complementary Metal Oxide Semiconductor) technology a few years ago, most of the design problems we've been talking about went out the window. The construction techniques used in the design of the chips in that family opened up whole new worlds of possibilities. Because CMOS uses both P- and N-channel MOS transistors, (remember that the "C" in CMOS means Complementary), we aren't limited to having the current flow in only one direction. Everything depends on how we connect up the transistors on the chip. We can see some of the possibilities that appear if we connect the P- and N-channel transistors back to back as shown in Fig. 1.
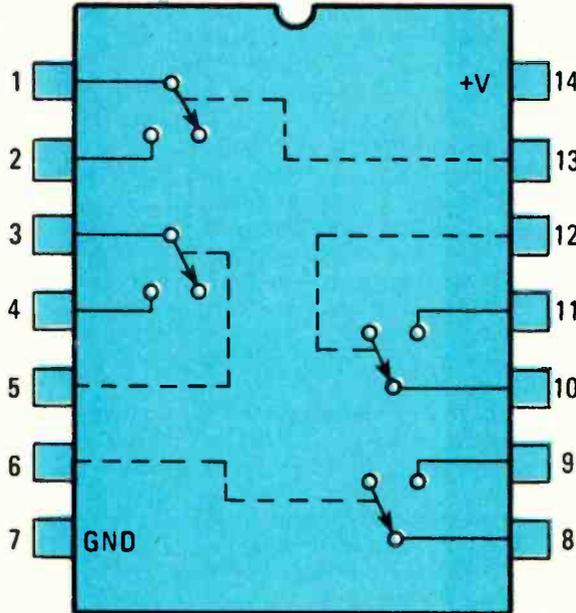
### The simple CMOS switch

When S1, the control switch, is connected to ground, the gate of the N-channel transistor is grounded and the gate of the P-channel (because of the inverter) is at +V volts. Since both transistors are turned off, points "A" and "B" are isolated from each other. (Well, that's not entirely true—because of the leakage cur-



## Switches

ROBERT GROSSBLATT

*With CMOS switches, you can use digital techniques to control analog signals.*

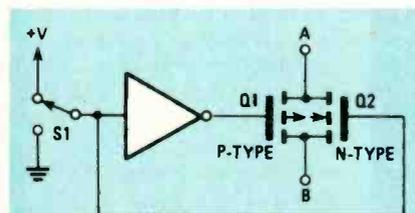


FIG. 1—SIMPLE CMOS ANALOG SWITCH. When S1 is switched to V, a signal path is created between points "A" and "B." When S1 is switched to ground, the path is opened.

rent of the transistors.) When we move the control switch to +V, a much more interesting thing happens. The P-channel gate is now grounded and the N channel gate is at +V. Both transistors are turned on and points "A" and "B" are connected to each other through the transistors. Since we're using two complementary transistors, the circuit of Fig. 1 can handle current flow in either direction. The P-channel transistor will conduct in the one direction and the N-channel transistor will conduct in the other. In other words, we can use the circuit to pass either digital or analog signals.

The OFF resistance of the circuit will be pretty high since we're essentially looking at a reverse-biased silicon diode. The ON resistance will be low; it's determined by the voltage across and the transistors and their physical characteristics. Although that looks wonderful, let's see what's wrong with it—and what can be done to make it better.

For starters, the ON resistance is going to be on the high side (about 500 ohms) for low-level analog signals. Running audio through that amount of resistance, especially low-voltage audio, can lead to possible termination problems and floating signals. A further problem with the circuit of Fig. 1 is that the resistance is going to change as the voltage changes across points A and B. That's because there's *always* a voltage drop across a transistor and the conductivity of even the world's most perfect transistor will vary somewhat with changes in voltage and frequency.

There's one more problem with the circuit of Fig. 1. Even though the transistors are a matched pair built on the same substrate, they are not *exact* complements of each other. That means that the signal path from point "A" to point "B" won't be exactly the same as the path from "B" to "A." In practical terms, that means that the resistances are going to be slightly different in each direction, and the switch

will run the risk of distortion and latch-up if the current flow gets up around the maximum limits of the transistors.

### The improved CMOS switch

It's for those and other reasons that the type of switch circuit shown in Fig. 1 was soon referred to as a "simple" switch and the semiconductor manufacturers introduced an "improved" version.

Figure 2 is the schematic of the improved version. At first glance it seems as if there has been quite a bit of change, but a second look will show you that we've simply made a few common-sense additions to the circuit of Fig. 1. Two inverters have been added to the control input of the switch to isolate the control voltage from the voltages being switched. That prevents the possibility of the control voltage being modulated by the voltages across the switch terminals. The high ON resistance of the simple switch has been reduced by adding two new transistors, Q4 and Q5, in parallel with Q1 and Q2. Since they're in parallel, the voltage drop across the two pairs will be less than it was in the simple switch—and a smaller voltage drop means a smaller resistance.

Because the controlling inverter is isolated from the control switch, we can add Q3 to make sure that the switching pairs of transistors stay off when the control switch is connected to ground. Since Q3 is an N-channel transistor, a logic-low at its gate will turn it on and help make sure that the other transistors are held in cutoff when the switch is opened. Remember that we added the extra switching pair, Q4 and Q5, to lower the voltage drop across the switch. Well, nothing is without a price. The cost of the lower resistance we achieved was the increased possibility of signal leakage through the switch when it's turned off. Even though Q3 goes a long way in helping to lock the other transistors in cutoff, the simple switch of Fig. 1 is still a better choice if your application demands the absolute lowest leakage current when the switch is turned off.

By using the basic principles we've just analyzed, chip designers have come up with an incredible variety of CMOS switches. By combining the switches with other digital circuits, MSI (Medium Scale Integration) IC's have been designed that can solve almost any circuit switching problem. On-chip binary counters and decoders allow the use of standard binary addressing to control the switching in a circuit. It doesn't take a great deal of imagination to realize the enormous advantage of being able to easily switch analog signals using digital control lines. Before you rush out and pick up some of those IC's, let's take a look at some of the rules you have to follow when you use them.

**1. CMOS technology is used to make analog switches.** That means that they are

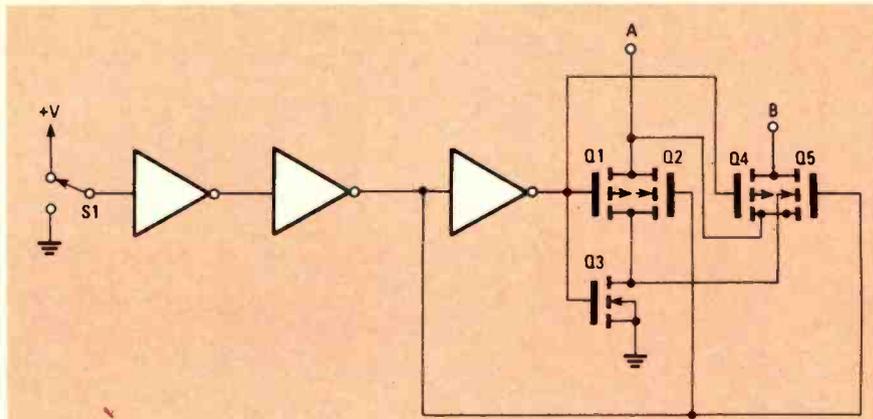


FIG. 2—IMPROVED SWITCH. The ON resistance has been decreased at the expense of a greater signal leakage when the switch is turned off.

subject to the same sort of damage from static electricity that you can expect with any other CMOS IC. The oxide layer between the gate and channel of a CMOS transistor is extremely thin and can be punctured by even a moderate amount of static discharge. Follow the same handling procedures you would with any MOS device and *never* insert or remove one of those IC's from a circuit that's powered up. It will ruin the chip—and your whole day.

**2. The amount of current** you can route through the switch changes somewhat with the supply voltage, but it should never be more than 25 mA for improved switches and 15 mA for simple ones. Trying to force more current through the switch will do things like degrading the internal transistors (if you're lucky) or blowing them up (if you're not).

**3. There are voltage limits** to your input signals. Never allow the voltage swing of the input to go above the supply rail or below ground. That isn't as much of a restriction as it would seem because CMOS IC's can operate over an astonishingly wide power-supply range. If you're sure that the voltage swing of the signals going through the switch in your circuit is going to exceed the range of the power supply, you're going to have to do some designing to meet that restriction. Since CMOS can operate safely at up to 15 volts however, you shouldn't have too much of a problem: It's a fairly simple matter to cut an input signal down to size ahead of the switch and boost it back up afterwards.

**4. Never let the control pins float.** That's especially true if you have signal voltages always present at the switch inputs. Don't forget that a general rule for all CMOS design is that all inputs have to go somewhere. Remember that the control pins are connected to inverters inside the IC. If the control inputs are floating, the state of the switches will be indeterminate at best and haywire at worst. More than likely, the inverters will bias themselves into linear operation and the whole circuit will

start oscillating. Since the inverters will have no clear path to either end of the supply rail, they'll draw a lot of power and you'll be running the risk of blowing up the IC and doing severe damage to the other parts of your circuit.

All those usage rules may make things seem a lot worse than they really are. But in practical terms, CMOS switch IC's are extremely easy to use and provide solutions to design problems by using methods that simply didn't exist before the introduction of CMOS technology.

Table 1 is a listing of some of the switch packages that are available. As you can see, some of the IC's are multiplexer/demultiplexers—switch configurations that are controlled by onboard binary decoders. They're a little bit slower than the plain switch packages, but they come in really handy when you're looking for an easy way to distribute analog data.

Before we examine some of the infinite amount of uses for these IC's, let's examine one consequence of usage rule 3—the input voltage can't exceed the IC's power supply. Although the voltages running around in a digital system are usually within those limits, analog signals are something else. It's perfectly normal for an analog signal to swing below system ground. That is especially possible if the analog signals are being generated by circuitry whose power supply is separate from the digital supply. Figure 3 is a graph that illustrates that problem perfectly. The digital voltage is between 0 and  $V+$  and the analog swing is between  $+(V/2)$  and  $-(V/2)$ . Although the voltage ranges are the same ( $V$  volts), it's evident that the difference in the values is going to present a special design problem—or at least one that has to be solved before the switches can be used to process analog data.


The solution is the same as it is with op-amps: The IC has to be powered by a bipolar supply. You're going to have to do something about generating a negative voltage for the IC. That means using center-tapped transformers or some other arrangement to produce the negative

**TABLE 1—ANALOG SWITCH IC TYPES**

IC type	Switch type	Quantity	ON resistance	Frequency response	Operating speed
4016	SPST	4	500 ohms	40 MHz	25 MHz @12 volts
4051	1 of 8	1	80 ohms	40 MHz	2 MHz @12 volts
4052	1 of 4	2	80 ohms	40 MHz	2 MHz @12 volts
4053	1 of 2	3	80 ohms	40 MHz	2 MHz @12 volts
4066	SPST	4	80 ohms	40 MHz	30 MHz @12 volts
4067	of 16	1	200 ohms	40 MHz	5 MHz @12 volts
4097	1 of 8	2	200 ohms	40 MHz	5 MHz @12 volts
4529	1 of 4 or 10 of 8	2 1	300 ohms 300 ohms	35 MHz 35 MHz	5 MHz @12 volts 5 MHz @12 volts

Pin 3 is the center pole of the switch and it will be connected to whatever pole is designated by the three-bit word presented to the weighted select pins (9, 10, and 11). Pin 6 is an enable or inhibit control for the IC—if it's made high the inputs will be disconnected from the output. That's a useful feature because there might very well be times when you want no channel to be connected. Pin 7 gives us an easy way to make the IC usable for both digital and analog applications.

If you're going to use the 4051 to han-

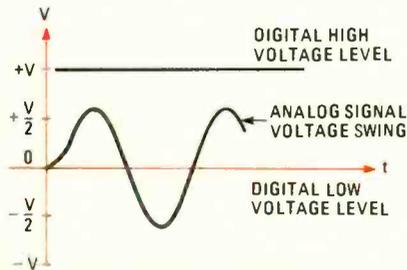

**FIG. 3—SITUATIONS WHERE THE ANALOG signal swings below the system ground require that a bipolar supply be used to power the IC.**

voltage level. The exact amount of power you'll need from a negative supply will depend on how you're using the switch, the frequency of the input voltage, the output load, and so on, but the current demand will never exceed about 5 to 10 milliamps. Since so little is needed, a center-tapped transformer is really overkill. A more realistic approach is to get below system ground by using some "Mickey-Moused" circuits or even one of the IC's specifically designed for the job, such as Intersil's ICL-7660 voltage converter.


**Some real devices**

Figures 4 and 5 show you two of the IC's in the family of analog switches. Since they're typical of the basic types of switches available, understanding them will make you familiar with the other IC's in the series.


The 4016 (in Fig. 4) is a package containing four simple switches exactly like the ones we analyzed. The 4066 is a pin-for-pin replacement containing four improved switches. The switches can be ganged together any way you want to satisfy whatever switching needs you have. A high signal on any control pin will close its associated switch and a low signal will open it.

Aside from the rules and limitations we've already discussed, there's nothing special you have to watch out for when you use this IC. The switches are all independent of each other and the crosstalk between them is very low—isolation is on the order of about 50 dB.

The 4051 (in Fig. 5) is one of the MSI rotary type switches we discussed before. It's a single-pole, eight-position switch

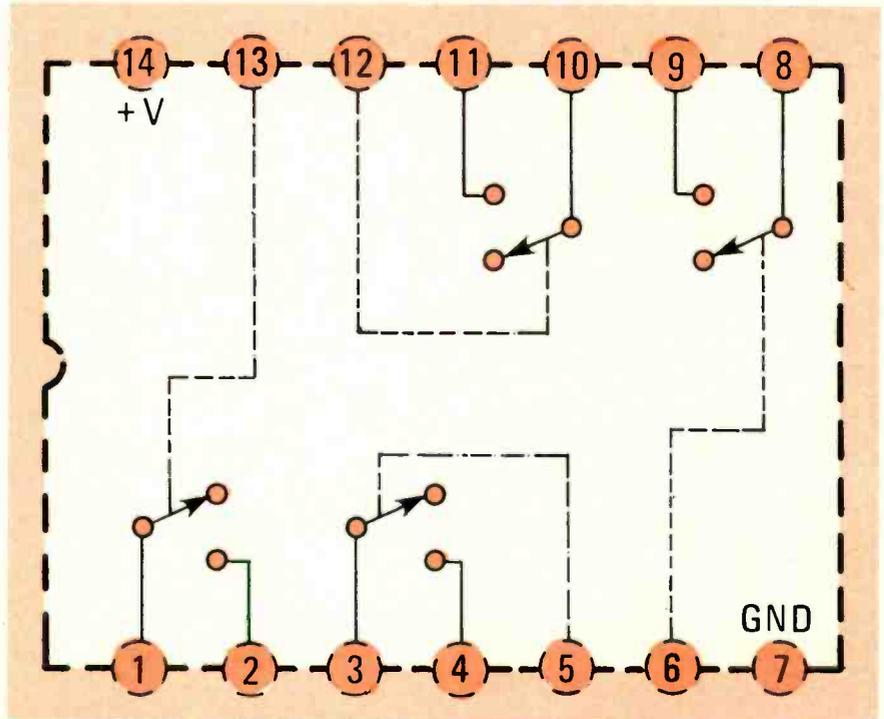

**FIG. 4—QUAD ANALOG SWITCH.** Functional diagram of the 4016 and 4066 switches.

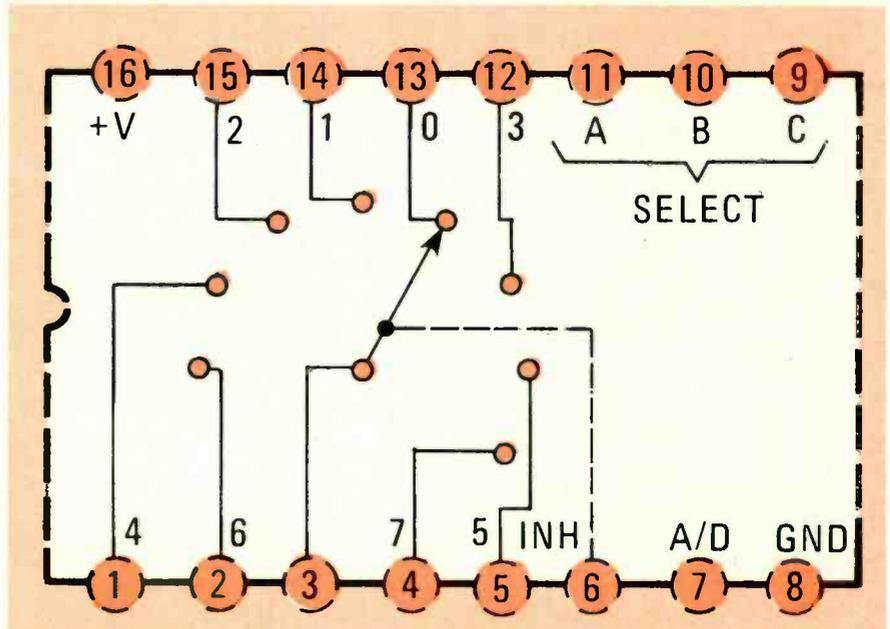

**FIG. 5—ROTARY ANALOG SWITCH, the 4051, is essentially the same as its mechanical counterpart.**

and can be used, like its mechanical counterpart, to either select or distribute data.

Only digital signals, you should tie pin 7 to ground. That pin is connected to cir-

cuitry inside the IC that takes care of the voltage translation needed to handle analog signals. When analog signals are going to be routed through the chip, you should connect it to the lowest voltage level in your system. That would be the lower limit of the analog voltage swing presented to the chip. In practice, that would probably be whatever negative voltage level you're generating in your system.

Remember that you can't ever let the input signals exceed the voltage range spanned by the supply levels on pin 8 and pin 16. If you connect pins 16 and 7 to +6 and -6 volts respectively, and connect pin 7 to ground, you can handle analog voltages of up to 12 volts and still use 6-volt digital-control signals to select the channel you want selected in the IC.

Even the slowest of the analog switches will operate at 2 MHz with a 12-volt supply. The frequency response of the switches is typically 40 MHz. That means that you can easily switch audio signals and even standard NTSC video signals. Since the propagation times are on the order of about 200 nanoseconds, you're probably thinking that these devices can be used for popless audio switching, remote control of analog signals, and so on.

### Digitally controlled gain

Well you're absolutely right. Let's look at two basic examples. Figure 6 shows how you could use a 4066 to digitally control the gain of an amplifier. The amplifier is an op-amp in a non-inverting configuration, and the gain is determined by the amount of resistance in the feedback path.

By putting a binary word on the control pins, we can have any one of 16 possible gain settings that are both precise and repeatable. Obviously that circuit is not the last word in this sort of thing, and we're not limited to using a 4066. We can gang as many switches as we want, use one of the "rotary" switches, or any combination at all. Microprocessor control of things is a real possibility and the range of control you have will be limited only by the width of your data bus.

The advantages of digital gain-control are obvious. Anyone who has fooled around with audio knows the insidious nature of 60-Hz hum from the power lines. As you run more and more lengths of shielded cable, your chances of maintaining a clean signal get less and less. That's in sharp contrast to digital signals: You can grind the digital control lines into the dirt and not upset anything. (Well, almost anything.)

Figure 7 shows you how you can use a 4051 to select the inputs to an amplifier. If you use that sort of arrangement with audio signals, the transition from one channel to another will be smooth, popless, and absolutely undetectable. Notice also

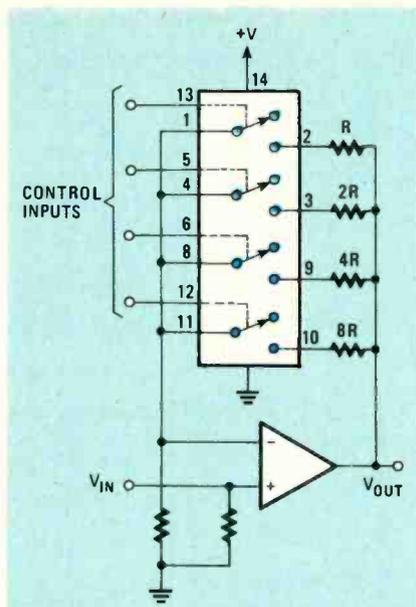


FIG. 6—SIMPLIFIED SCHEMATIC of a digitally controlled variable-gain control.

tially an open circuit, crosstalk is less than 50 dB, and because CMOS is an inherently noise immune logic-family, that sort of circuit is a real possibility.

The question of video switching is interesting. The analog switches have more than enough speed and bandwidth to handle it. Even the slowest devices can pass frequencies up to 40 MHz and premium IC's can go way past that. I've built video switchers using analog switches and, beyond the normal precautions you take when working with high frequencies, no particular problems showed up. Remember: I'm talking about NTSC video—not un-demodulated broadcast television signals. TV signals would be a bit of a problem because you'd be looking at VHF and UHF signals. You might be able to handle the extreme lower end of the VHF band, but that's about it. Since Channel 2 centers around 58 MHz, you're starting out at the upper limit of most analog switches. And since UHF begins somewhere around 440 MHz, it's out of

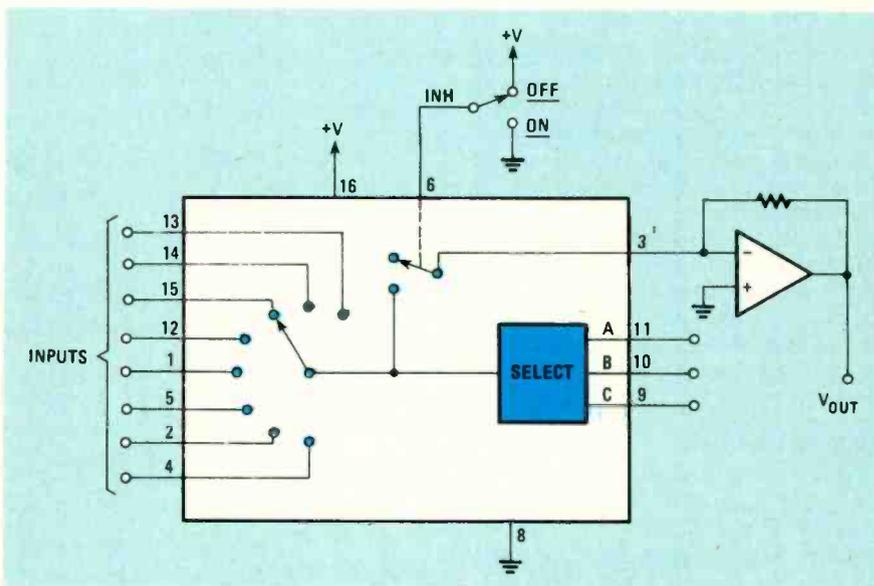


FIG. 7—INPUTS TO AN AMPLIFIER can be switched in any order using the select lines.

that you don't have to switch channels in any particular order as you do with mechanical switching. You might refer to that sort of circuit as a random-access selector. Since those are analog switches, you can turn the circuit upside down and use it to send a signal to a selected output—in other words, a distribution amplifier.

That isn't as trivial an observation as it may seem. Remember that the 4051 will scan outputs at greater than 2 MHz. That immediately brings to mind a unique sort of distribution amplifier. A little bit of design ingenuity will allow you to use one amplifier to feed eight outputs by scanning the outputs so quickly that there's no noticeable signal loss at any one of them. (That's similar to multiplexing LED displays.) Since the OFF resistance is essen-

the question. The best approach is to demodulate those signals before the analog-switch circuitry, and cut the frequencies down to a level more easily handled by the switches

CMOS switches are the digital windows to the analog world. No logic family has ever been able to directly process the signals those IC's were designed to handle. Although they can be used to deal with digital data, their real advantage comes in being able to deal internally with analog voltages. The next time you design circuitry for audio or video signals, using these specialized IC's can save you time at the bench. They'll also help reduce the number of problems with power supplies and provide you with an elegant solution to what used to be an impossibly complicated problem.

R-E



This August marks the 100th anniversary of the birth of Hugo Gernsback—author, publisher, and inventor. In this article, we'll look back at the life and achievements of that great man, the founder of **Radio-Electronics**.

## HUGO GERNSBACK: A MAN WITH VISION +

ROBERT A. W. LOWNDES

"IF HUGO GERNSBACK HAD STAYED HOME, everything would have been different." So begins *The Futurians*, by Damon Knight—a book about a famous science-fiction fan club of the late 30's and early 40's, many of whose members became prominent science-fiction writers and editors. That statement is even more true of the world of electronics and radio, and electronics periodicals.

Where was Gernsback's "home?" He was born in Luxembourg on August 16, 1884. That was the year that Grover Cleveland was first elected President of the United States; Harry S. Truman and August Piccard (Swiss physicist) were born, and the first practical steam turbine engine was invented.

As a boy, young Hugo was fascinated by the electrical workings of a doorbell he'd been given for his 8th birthday, and that concentrated interest in all aspects of electricity proved to be life-long. He studied that subject at the Bingen Technicum, one of the best technical institutes in Europe, from which he graduated. But his education was not a narrowly scientific one; he had a thorough classical education as well, and knew the literature of three languages in which he became fluent: German, French, and English.

His first venture toward a career was invention: He developed a greatly improved dry battery, and emigrated to the United States, at the age of 19, where he hoped to make his fortune as an inventor. His name had actually been Gernsbacher;

he changed it to "Gernsback," for the purposes of simplification.

The battery was, indeed, a superior one—but the cost of manufacturing it at the time proved to be too great. He got a job with a storage-battery manufacturer, and developed a cheaper, lighter, and stronger battery case than any other then available. Unfortunately, he neglected to test it fully and it proved all too vulnerable to corrosion. That ended his job and his career as an engineer.

His third venture would be successful and lead directly into his career as a publisher and writer. He formed the Electro Importing Co., to obtain equipment from Europe and sell it to electrical and wireless experimenters. His catalogs not only showed and described the products he was selling, but also contained short articles explaining how electrical equipment actually worked.

### Gernsback the publisher

In 1908, he decided to try publishing a magazine devoted to instructive articles on new and unfamiliar equipment, as well as background material on electrical fundamentals. The first issue of *Modern Electrics* was dated April, 1908, and from the start was concentrated on wireless theory and construction projects. The magazine was a success, and in 1911 Gernsback started to write what he would later term "scientifiction"—a charming story rooted in sound scientific principles, speculating upon the future (near or far) when as-

yet unheard of devices and inventions would be realities. Because of its combination of sound scientific background and vision, that first story, "Ralph 124C41+," contained a cornucopia of what proved to be accurate predictions: radar, television, tape recording, and night sports games, are just a few of them. The story ran serially for 12 issues in *Modern Electrics*, and it is very likely that Gernsback had no idea, when he started it as a space-filler, that it would wind up as a novel. It was rewritten for hardcover publication in 1925, and reprinted in the winter 1929 issue of *Amazing Stories Quarterly*.

*Modern Electrics* was sold in 1912; Gernsback had already started another publication with a broader base: *The Electrical Experimenter* was a large-size, roto magazine. (*Modern Electrics* had been something between pulp magazine and digest size.) The title was changed to *Science and Invention* in 1920. By then, he was already publishing *Radio Amateur News*; the word "amateur" was dropped from that title in 1920.

In 1925, Hugo Gernsback established radio station WRNY, the first broadcast station to devote regular time to broadcasting programs of interest to electrical experimenters and technicians. The editors of *Science and Invention* and *Radio News* were frequent speakers, and Gernsback himself talked on scientific subjects every Monday night at 9 PM.

In 1928, station WRNY began daily

television broadcasts, and those who had built themselves TV receivers saw tiny images comparable to halftones in the daily newspapers. There was no sound, however, and those without receivers who tuned into WRNY when TV broadcasts were going on heard only peculiar noises. In the same year, Station WRNY was broadcasting by shortwave all over the world.

He had already achieved considerable influence not only on inventors and researchers, but also on legislators. He founded the Wireless Association of America in 1909; its purpose was to advance the interests of both professionals and amateurs in the field. It went farther than that: it protected them. On two occasions when legislators would have eliminated the amateur and amateur radio itself, Gernsback's editorials (and undoubtedly much mail from his readers) prevented that from happening. The amateur section of the Wireless Act of 1912 reads like a paraphrase of one of his editorials. Gernsback also formed the first organization of radio repairmen, the Official Radio Service Men's Association.

Gernsback's humor came out, however, not only in stories, but in "April-Fool" type articles. For that purpose he adopted the pseudonym of Mohammed Ulysses Socrates Fips, office boy, who was also an immigrant from Mars. Fips' inventions, in the *Modern Electrics* days, included a device to obtain ham sandwiches through matter transmission.

Although his initial experience had convinced him that he wasn't going to make his living as an inventor, Hugo Gernsback didn't stop inventing. That aspect of his life continued and he obtained over 80 patents, few of which he made any attempt to commercialize. Among those that were developed was what he called the "hypnobioscope," described in "Ralph I24C41 +"—a device by which one can be instructed or educated while asleep. It was tried and used successfully in 1922 at the Pensacola, Florida, Naval Training School for teaching students Morse Code. Another was a bone-conduction hearing aid: he patented it in 1928 but never made or developed it, nor objected when someone else "reinvented" and manufactured it. His comment then was "I never intended to market it. Why should I bother someone else?"

One exception was the compression type "condenser," which was a prototype of the present-day trimmer capacitor. That was used as the "book condenser" in the Crosley radios. Patents were also obtained to protect devices he had developed for the Electro Importing Company.

However, he did not forsake developing some of his own ideas. In 1906, he brought forth the first radio set ever sold in the United States. It was a spark set that included both a transmitter and receiver,

and was portable. The price was \$7.50 and it included what would later be called receiving and transmitting antennas. While the range was limited (one mile), it operated in the UHF band and did not need tuning. There was no such thing as a commercial radio station at the time: the Telimco Wireless Outfit, as it was called, was used by experimenters and hobbyists who would later be known as radio hams.

Not all of Gernsback's periodicals were dedicated to radio or electricity. He also published *Your Body*, a magazine dedicated to sound medical instruction for the layman, as opposed to other, "health-fad", types of periodicals at the time. One of the publishers of that type of magazine was Bernarr MacFadden, who would play an important part in Hugo Gernsback's later fortunes.

While *Amazing Stories*, Gernsback's scientification magazine introduced in 1926, did not become a money-maker, it was popular; and the response to it was such that, after experimenting with one issue of *Amazing Stories Annual* in 1927, Gernsback started a second scientification title in 1928: *Amazing Stories Quarterly*, which featured a book-length novel, a novella, and short stories, all complete in each issue.

It was at this time that MacFadden tried to buy *Amazing Stories* and *Your Body* from Gernsback. MacFadden was a sincere scientification enthusiast, and it was more practical to obtain an already-established title than take the risks of starting a new one. (He wanted *Your Body*, however, in order to bury it.) Gernsback declined the offer, and assumed that that had ended the matter.

It hadn't. Early in 1929, Hugo Gernsback suddenly learned that bankruptcy proceedings had been set up against his Experimenter Publications. A sizeable debt to one of his suppliers (who also did much business with MacFadden) had been manipulated so that bankruptcy petitions could be presented to the court.

Such a ploy would be prosecuted as criminal conspiracy today, but in 1929, the steps taken by the "conspirators" were entirely within the law. The bankruptcy laws in New York were changed thereafter, to prevent further such incidents, but that could not restore Gernsback's ownership of his publishing company.

A few months later, proof appeared that Hugo Gernsback was not broke and finished. On May 3, 1929 the first issue of *Science Wonder Stories* came out, with the familiar "Hugo Gernsback, Editor" line on its cover. That cover was by Frank R. Paul, who had done all the previous covers for the monthly and quarterly *Amazing Stories*. The term Scientification had been dropped and "Science Fiction" substituted. Inside was a full-page announcement of another science-fiction title, *Air Wonder Stories*, which would start the following month. And that same month, June 1929, the first issue of *Radio-Craft* went on sale. Hugo Gernsback had made the fastest comeback in magazine-publishing history!

From its first issue, *Radio-Craft* gave close attention to not only hobbyists and experimenters, but also service technicians. (The editorial in that initial issue was titled: "How to Become a Service Man.") At that time it was extremely difficult to obtain needed technical information, or even parts, from radio set manufacturers; Gernsback's influence would gradually change that situation to the point where any layman could obtain information needed to repair his equipment or use components in his projects.

The year 1933 saw the inauguration of Hugo Gernsback's most important non-technological magazine: *Sexology*, the first periodical devoted to sound, scientific, and absolutely non-sensational articles on the entire range of sex, medical and psychological, including marital counseling.

The same year, one of Gernsback's choicest bits of humor backfired upon



HUGO GERNSBACK at the key of the Telimco wireless transmitter. The receiver is at the left.

him: The May 1933 issue of *Radio-Craft*, on sale in April, contained a description of a "super-hetero-ultradyné" radio so small that it could almost fit into the owner's pocket. It was called the "Westingmouse." Although the words "APRIL FOOL," in capitals, appeared at the end of the article, readers refused to believe it was all a joke. The manufacturer whose name was suggested received innumerable orders for the "Westingmouse," as did *Radio-Craft*. As steady readers know, **Radio-Electronics** now has "April Fool" material each year, but that was not the case for a number of years after 1933.

In 1934, readers saw the first article in *Radio-Craft* to use the term "high fidelity." (As with the word "television," high fidelity was not a Gernsback coinage, but he was prominent in bringing attention to the latter, while he introduced the former into English.) There were construction articles in 1933 issues on how to add high-fidelity to old sets, and the May issue of that year had five articles on the subject of hi-fi.

Also in 1935, the first mention of FM came up in discussion of an invention by Major Edwin H. Armstrong that would eliminate static; at the beginning that was its principal use. Earlier, Hugo Gernsback had championed de Forest in his claims to have developed an entirely new device in the Audion (rather than just an improvement on the Fleming diode valve), and the Supreme Court recognized de Forest as the inventor of the regenerative circuit.

In 1937, there was a serial: "How to Build Your *Radio-Craft* Television Receiver."

Nikola Tesla, now recognized as one of the world's greatest electrical inventors and engineers, died in 1943. Gernsback had been an admirer and personal friend of Tesla from the very beginning. It was through Gernsback's influence that Westinghouse arranged for Tesla to receive the pension as "consulting retainer" that kept him from poverty in his last years. The February 1943 issue of *Radio-Craft* was a special Tesla issue.

Today, the electret, which is a dielectric disc with a permanent positive charge on one face and a negative charge on the other, is widely used in microphones. The public first heard about it, however, in an article, "Electret—Frozen Electricity," appearing in the November 1945 issue of *Radio-Craft*. Few scientists and technicians paid any attention, but Gernsback kept pushing the idea and finally persuaded Edward Padgett to make some. Padgett described his experiments in a series of articles, and another author showed readers how to make their own.

### The birth of *Radio-Electronics*

By now, the magazine had a new title. Gernsback repeated a procedure he had used when he started his new company in

1929: he asked readers to choose a title—in this case a more appropriate name for *Radio-Craft*, whose coverage now had expanded far beyond the limits of radio. He specified that he wanted the word "television" in the new title—but the voters didn't. Starting with the September 1948 issue, the magazine became **Radio-Electronics**. (The old title was phased out on the cover after several months.)

Gernsback wrote all the editorials for the magazine, but began to confine his long, highly speculative and predictional material to his annual Christmas card. It was far from a card; each year, it appeared as a take-off on some other well-known national-circulation magazine, following that publication's general format. (*Time* was burlesqued as *Tame*.) The articles on scientific subjects, sound as they were in principle, read like science fiction, and many of them were illustrated by Frank R. Paul. A number of them were reprinted in Gernsback's last attempt to launch a successful science-fiction magazine in 1953. (*Wonder Stories* had folded in 1936.) There was a boom in science-fiction magazines at the time, although by the time the first issue of *Science-Fiction +* appeared, it had started to die down. The magazine was edited by Sara Moskowitz, and printed on coated paper, large size, but it only lasted for eight issues.

Some of the material from Christmas cards and *Science Fiction +* found its way into the original manuscript of Hugo Gernsback's final novel, *The Ultimate World*, which he wrote in 1958 and 1959. No publisher would take it because of the intermingling of narrative fiction and prophetic articles. It was finally published in 1971, as edited by Sara Moskowitz, without any of the non-fiction.

Gernsback had seen a number of his dreams come true, but one of them was proving to be a nightmare by the end of the 50's. FCC Commissioner Minnow had summed it up when he described commercial television (and that was the only variety then available) as a "wasteland." Gernsback noted in the February 1962 **Radio-Electronics** that TV programs had "shrunk to an incredible low." But what could be done about it? Gernsback suggested canned TV recordings, either in tape or disc format; such recordings existed at the time in experimental form. Educational material and entertainment on a high-quality level could thus be produced and sold profitably. Those who owned TV sets could buy such discs and view them whenever they wanted to.

The early 60's saw the first active communications satellite, Telestar, launched; the discovery of voiceprinting, the electret microphone and earphone, microwave ovens, and the first weather satellite. More and more electronics devices and procedures that Hugo Gernsback had either predicted, or championed when no

one considered them commercially viable, had come into being.

One of his last predictions was a voice-operated typewriter; he based that prophecy on work in progress. One experimenter, Count Dreyfus-Graf, had reached the point where he could dictate readable Christmas cards. Gernsback's powers were failing by 1965, and many of the editorials in **Radio-Electronics** that year were written by guest writers, such as John R. Pierce of Bell Labs (who had been a winner in a *Science Wonder Stories* cover contest); David Lachenbruch, one-time associate editor, and managing editor, Fred Shunaman. Gernsback had not stopped writing, but he was saving his material for his Christmas card, *Forecast—1966*. That would be the final one he would write.

He lived to see the opening of the computer age, and one of his most serious proposals was that of a computerized National Facts Center. While that has not come about, and may not because of the danger of massive government intrusions into citizen's privacy, privately-owned data files, accessible at reasonable prices, constitute the essence of his idea. Back in 1930, in ads for his science-fiction magazines, he had predicted that we would reach the Moon by 1950; he had predicted in 1929 that the first Moon-shots would be unmanned. His later prediction that the event would occur before 1970 hit the mark. He added that he wouldn't be around to see it happen—but in a sense he was there at the famous moon-landing in 1969: a crater on the Moon had been named after him.

Hugo Gernsback died on August 19, 1967—shortly after his 83rd birthday. His son, M. Harvey Gernsback, who had been working with his father in Gernsback Publications for many years, and had contributed articles to **Radio-Electronics**, continued the magazine.

Although his interest in invention remained throughout his life, the key element of Hugo Gernsback's personal faith was that the world would be greatly improved if the common man had a basic comprehension of science and its meaning in society in all aspects, and at all levels. With a very few exceptions, all his publications were directed to that end.

A collection of tributes to Hugo Gernsback's effectiveness in pursuing his chief goal from those who knew him, from close friends to acquaintances and working scientists and technicians, would fill a good-sized book. Testimonials from those who never met him, but whose lives had been significantly changed by following Gernsback publications, would fill a many-volume set.

Damon Knight, a prominent member of the larger group, was right: Had Hugo Gernsback stayed in Luxembourg, everything would have been different. R-E

# HOBBY CORNER

## Component specifications

EARL "DOC" SAVAGE, HOBBY EDITOR

DESIGNING AN ELECTRONIC CIRCUIT IS A difficult job in itself; nowhere is that better illustrated than in circuits that are to contain IC's. Without knowing something about the components that you intend to use, it's next to impossible.

Several of you out there have written recently about the troubles you've had in designing circuits using IC's. I have probably been of little help because troubleshooting by mail is a difficult, if not impossible, undertaking. However, I can offer this bit of advice to Pat Rube (SD), Walter Bumgarner (NE), William Stamile (NY) and others who may be having similar problems.

For general design information and IC requirements, go first to two books by Don Lancaster (published by Howard W. Sams): *The TTL* and the *CMOS Cookbooks*. They're getting a bit old now, but they still contain valuable information that is clearly presented. The next place to look is in the manufacturer's data sheets or databooks to get information on the specific IC's involved. (Your local library is a good place to look for databooks.)

The databooks will give you necessary information about such things as debouncing input lines, stabilizing power supplies, current requirements, what must be done with unused input pins,

### AN INVITATION

To better meet your needs, "Hobby Corner" has undergone a change in direction. It has been changed to a question-and-answer form. You are invited to send us questions about general electronics and its applications. We'll do what we can to come up with an answer or, at least, suggest where you might find one.

If you need a basic circuit for some purpose, or want to know how or why one works, let us know. We'll print those of greatest interest here in "Hobby Corner." Please keep in mind that we cannot become a circuit-design service for esoteric applications; circuits must be as general and as simple as possible. Please address your correspondence to:

Hobby Corner  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003

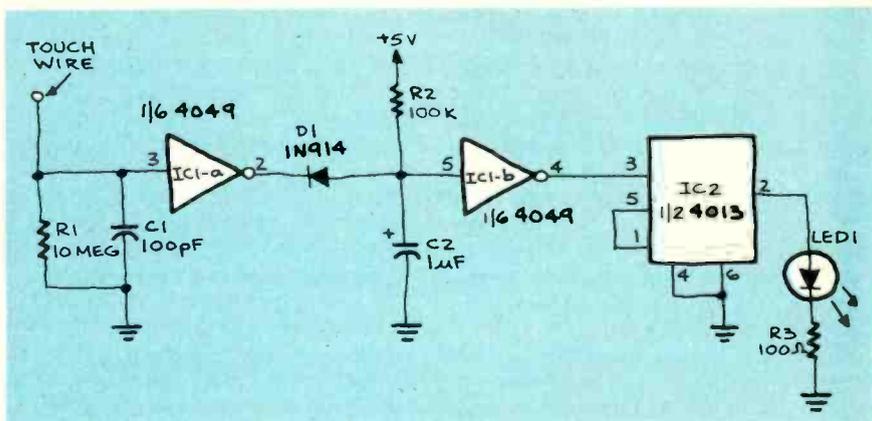


FIG. 1

needed "pull-up" resistors, fan-out limitations, current-sink limits, maximum frequencies, and the like. Those are the kinds of things you should know before you start designing a circuit.

There are many instances where two (or more) IC's have identical pinouts, yet are not interchangeable in most applications. Without both general and specific data, you are likely to go astray.

If you build a device based on an article, or other set of instructions, the author should have done all the ground work. On the other hand, if you are going from "scratch," you will need some references like those mentioned earlier.

Another question related to this subject comes from Roger Secura (OH), who inquired about the use of the phrase "designing for the worst case." You, no doubt, have heard of Murphy's Law—Anything that can go wrong, will. That certainly applies to electronic circuits! For example, someone is sure to put a book over the ventilation holes of a piece of equipment and cause it to run hotter than the designer intended, thus causing it to malfunction. Another instance where it is a good idea to consider the worst case is in dealing with the AC powerline. That is because the voltage on the line does not remain constant, but often varies over a range of ten volts or more and therefore, can affect the power input to a circuit.

In your designs, it's a good idea not to run components at or near their limits. That's because those limits are likely to be exceeded even during the normal operation of the circuit. In other words, *do not*

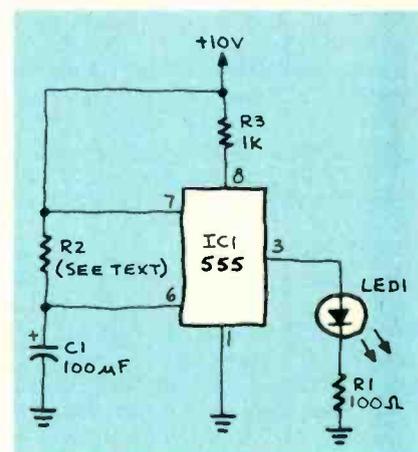


FIG. 2

use capacitors rated at 15 volts in 15-volt circuits. Likewise, don't use a 20 MHz IC in a circuit that you expect to run at 20 MHz. Also, do not use a 1/4 watt resistor when you expect it to dissipate 0.25 watts.

Though you may get away with doing such things now and again, your circuits will be more likely to fail or operate erratically. Allow your components and yourself some room to breathe (so to speak). Over-design enough to take care of the worst case the circuit is likely to meet during normal operation. That way your designs are bound to survive a little longer. And now, let's see what else is in the ol' mailbag.

### Touch switch

Dave Hipp (IL) sent a neat circuit for a touch (plate) switch using 4049 and 4013

integrated circuits: That circuit is shown in Fig. 1. He plans to rebuild the circuit and incorporate it into a table lamp, so that the lamp can be operated by simply touching it. His problem is that the circuit works fine when just a touch wire is attached as shown, but it turns on and stays on whenever he attaches a large piece of metal.

Well, Dave, you must first consider the principle on which that type of device operates. Remember, when you touch the end of the wire, the capacitance between your body and ground change the potential on the wire. That, of course, changes the potential on the IC's input pin, which then turns the device on. If you attach a big piece of metal, it forms a significant capacitor with ground, and that keeps the relay on.

You can still use that piece of metal for the touch plate, but you must first decrease the sensitivity of the input. There are two approaches that you can take to reduce circuit sensitivity, depending on the circuit involved. First, you can apply a small voltage to the input; in that way, the applied potential caused by body capacitance must first overcome that voltage to be effective. Second, you can use a voltage divider at the input so that only a portion of potential affects the input. (That's easily done in your circuit by adding a series input resistor).

Another circuit related to your project, one that I am sure will interest you and other readers, was sent in by Dan Napolitan (PA). In his circuit (shown in Fig. 2) he uses only the familiar 555 timer. If you vary the value of resistor R2 you can change the length of on time. (The value of R2 should be somewhere between 22 kilohms and 1 megohm.) You can combine the two circuits by taking the output of the first and feeding it to the trigger input (pin 2, not shown) of the 555 timer.

Note that both diagrams show LED's in the output. That is done for testing and adjustment purposes. To operate a lamp, or other high voltage/current device, just substitute a relay for the LED.

#### Wireless doorbell

Pat LoSquadro (NY) has written to ask for help in finding some kind of "wireless" doorbell. It seems that Pat has an apartment with cement-block walls and does not want to have wires strung around in plain view.

Well, Pat, two approaches to your problem occur to me. The first involves a carrier-current transmitter and receiver that sends RF (Radio Frequency) energy through the AC lines. Of course, you could build the equipment yourself, but the cost of the commercially available units is reasonably low. You have probably seen them advertised as wireless intercoms, monitors, or baby sitters.

My thought is to place a small bell or



# FREE

## McIntosh

### STEREO CATALOG and FM DIRECTORY







Get all the newest and latest information on the new McIntosh stereo equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.

SEND TODAY!

McIntosh Laboratory Inc. RE  
 East Side Station P.O. Box 96  
 Binghamton, N.Y. 13904-0096

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

If you are in a hurry for your catalog please send the coupon to McIntosh. For non rush service send the Reader Service Card to the magazine.

CIRCLE 93 ON FREE INFORMATION CARD

buzzer at or near the door in a small box with the transmitter. Then, you can plug the receiver into any convenient AC receptacle in the house. Obviously, you will not need a two-way intercom, though one could be used. Radio Shack has a wireless FM-monitor for about \$30 that could be used in this application.

Another approach would be to use an infrared transmitter and receiver. One circuit that could be easily adapted to your application is described in this issue of **Radio-Electronics**.

#### Walkie-talkie power modifications

A young man, who shall remain nameless, has written to ask advice on increasing the output power of walkie-talkies. That question raises several concerns. First, you should be aware that fooling around with the circuitry of a transmitter of any kind can change characteristics of the signal it produces. That can result in the radiation of spurious signals that could interfere with other equipment. That is illegal.

Second, there are precise legal limits on the power that can be used by certain types of devices. For those reasons, my young friend, I cannot give you the information you seek. In addition, I strongly advise that you operate the equipment as it was intended. R-E

## CABLE TV

### CONVERTERS DESCRAMBLERS

Largest Selection  
of Equipment Available

\$ Buy Warehouse Direct & Save \$



**36 channel  
converter  
\$45<sup>95</sup>**




**36 channel  
wired remote  
converter  
only  
\$88<sup>95</sup>**

Send \$2 for complete catalog  
of converters and unscramblers

Quantity Discounts • Visa • Master Charge  
Add 5% shipping—Mich. residents add 4% sales tax

C&D Electronics, Inc.  
 P.O. Box 21, Jenison, MI 49428  
 (616) 669-2440

# 1946. Sams Introduces PHOTOFACT.®

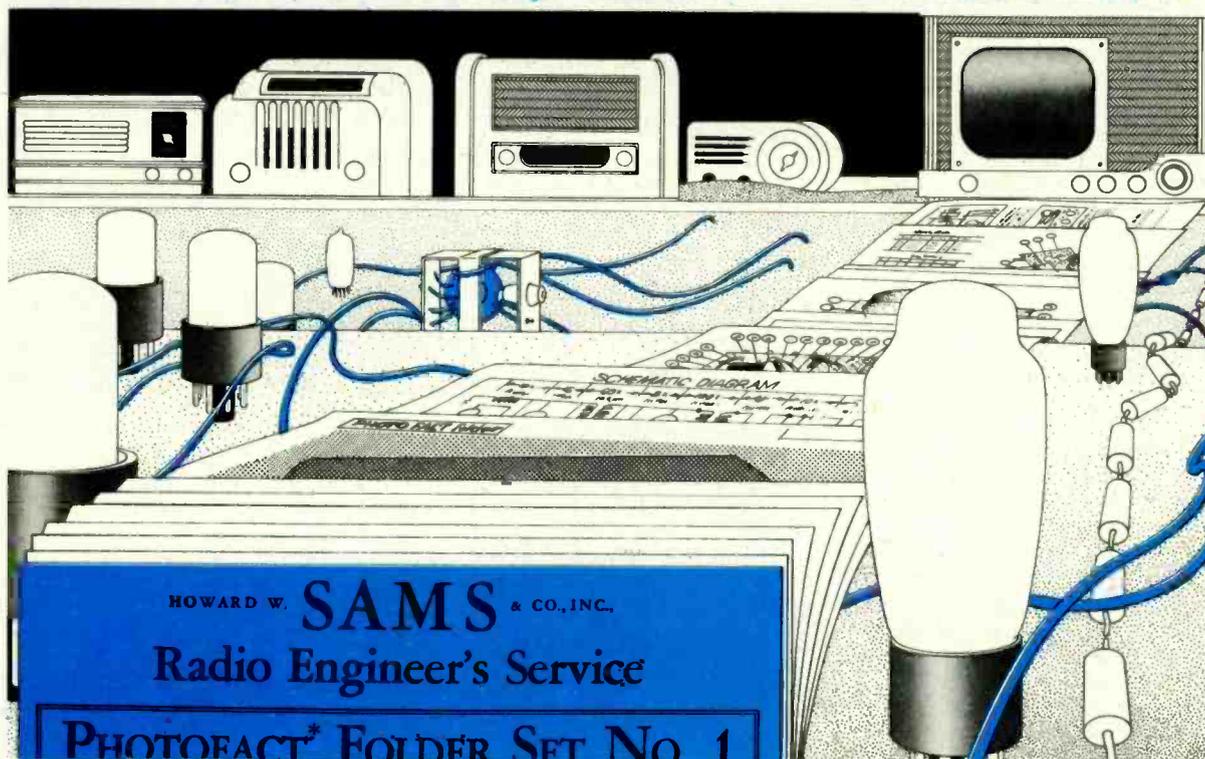

## The Inside Track To Servicing Your Microcomputer

### The Inside Track To Servicing Your Microcomputer.


It started in the early days of television. Sams began reconstructing and documenting how fechnology works and published its first PHOTOFACT TV service manual.

But Sams didn't stop there. Sams continued to apply its technical expertise in new areas. And in 1967, released the first computer book.

Now Sams has combined its knowledge of computers and technical servicing to bring you **COMPUTERFACTS**—the first and only technical manual series for servicing today's microcomputers and peripherals.
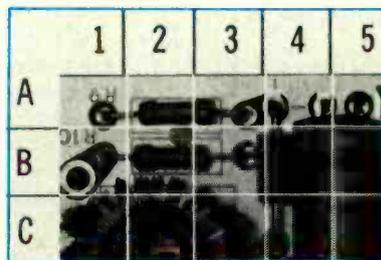
### The Facts Remain Clear.

Buy Sams **COMPUTERFACTS** and you've got the inside track to servicing and maintaining your computer yourself. Because with **COMPUTERFACTS**, you have everything you need to understand how your computer is put together and how you can make it work better.



Offer good in USA only. Prices and availability subject to change without notice.



In Canada, contact Lenbrook Electronics, Markham, Ontario L3R 1H2.

Apple is a registered trademark of Apple Computer, Inc. Commodore is a registered trademark of Commodore Business Machines, Inc. Atari is a registered trademark of Atari, Inc. Osborne is a registered trademark of Osborne Computer Corporation. Diablo is a registered trademark of XEROX CORPORATION. TI 99/4A is a registered trademark of Texas Instruments, Inc. PHOTOFACT is a registered trademark of Howard W. Sams & Co., Inc. COMPUTERFACTS is a trademark of Howard W. Sams & Co., Inc.

CIRCLE 25 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)
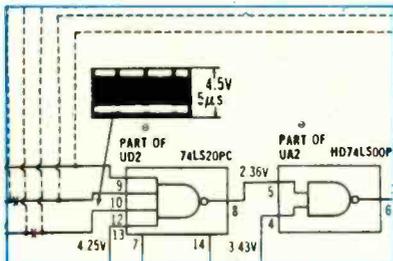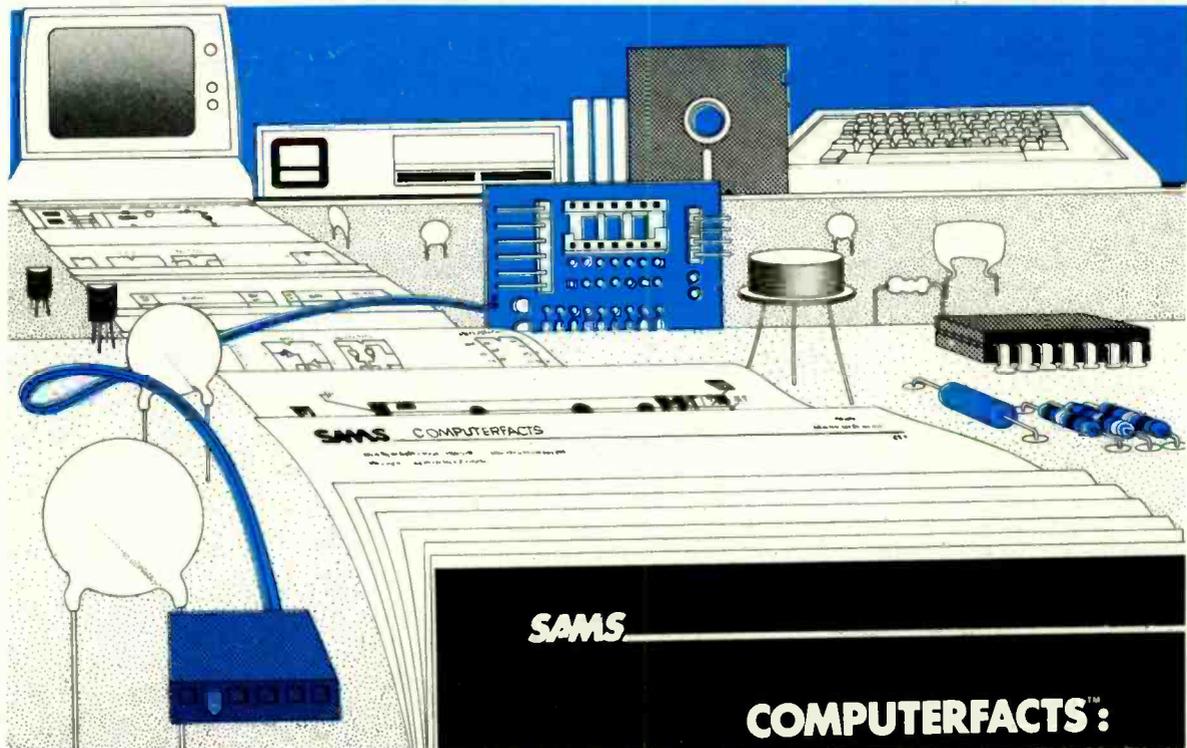
# 1984. Sams Introduces **COMPUTERFACTS™**



COMPUTERFACTS are available for every major computer and component made including data storage devices, modems, and printers by Apple®, Osborne®, Commodore®, Atari®, Diablo®, TI 99/4A®, and others.

And like PHOTOFACT, COMPUTERFACTS cover every circuit, chip and control thoroughly and accurately with pages of:

- Fully-diagrammed schematics
- Disassembly instructions
- Logic charts
- Parts descriptions

- Terminal guides
- Troubleshooting hints

So you can spot and service problem areas in minutes.

**COMPUTERFACTS Give You More.** If you want more out of your computer, get more into it with **COMPUTERFACTS**. Only **COMPUTERFACTS** can be used alone or with your favorite computer guide to improve operation, change configuration, replace defective parts, and more.

**So get Sams COMPUTERFACTS and get on the fast track to better computing. To order, visit your local Sams dealer. Or call OPERATOR 164 at 317-298-5566 or 800-428-SAMS.**

## **SAMS™**

**What Technology Is All About.**

HOWARD W. SAMS & CO., INC.  
4300 West 62nd Street, P.O. Box 674  
Indianapolis, IN 46268

CIRCLE 25 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# COMPUTER CORNER

## A look at a lesser-known computer

LOU FRENZEL

WHAT MANUFACTURERS COME TO MIND when you think of personal computers? If you're talking about conventional desktop computers, you probably think of Apple, IBM, or Radio Shack without hesitation. If you are talking about low-cost home computers, then Atari, Commodore, Timex/Sinclair, and Texas Instruments probably come to mind. Those are certainly the most popular machines—even though the last two have recently dropped out of the home-computer market. After all, there are more of them than any others in the field. Further, those manufacturers are all large companies that advertise regularly. Therefore, it's difficult not to know about their machines.

On the other hand, there are over 100 other manufacturers of personal computers. Their machines are not as well known and the manufacturers are certainly not as visible. For example, have you heard of Columbia, Corona, Eagle, Franklin, Memotech, Morrow, Seequa, Spectravideo, and TeleVideo? They're just a few of what we might call the second string of personal-computer products. Those manufacturers each sell hundreds of thousands of computers to satisfied customers. Yet most of us tend to forget the off-brand machines, and focus our attention and interest on the more popular mainstream units. Still those lesser-known companies offer excellent products—usually with prices, performance characteristics, or unique features worth considering.

Recently we had the opportunity to take an in-depth look at an offering from one of the smaller and newer manufacturers of personal computers; and what we found was astonishing. No longer will we ignore that second tier of products and neither should you. You could be overlooking the best machine for your needs.

### Memotech's MTX512

Recently, Memotech decided to take the plunge and offer a "full-blown" microcomputer; The result of their effort was the MTX512. While Memotech isn't exactly your basic household word in computers, they are known for their numerous add-on computer products. Their most popular products are memory-expansion modules and plug-in I/O interface adapt-



FIG. 1

ers for the Sinclair ZX81 and Timex/Sinclair 1000. The MTX512 (known in Europe as the MTX500) is manufactured in a small town in England called Whitney and is an excellent example of the powerful new machines being offered today. The U.S. version went on sale in July, 1983.

The MTX512 is packaged in an unusual but attractive black anodized aluminum cabinet (see Fig. 1). The cabinet itself is really an extrusion especially designed for this application. Very few personal computers have metallic housings; most use inexpensive foam or plastic cabinets. The unit has a 79-key keyboard that includes a numerical keypad and eight special-function keys. The MTX512 features a Z80 microprocessor running at 4 MHz. It comes with 64K of user RAM, plus an additional 16K of RAM dedicated to video graphics. The user RAM can be extended to 512K using bank switching. In addition, there two disk-drive options available: One is a floppy-disk unit that features a 500K byte double-sided double-density 5¼-inch disk drives, and the other a 10-megabyte hard-disk drive. The unit also comes with 16K of ROM that contains its own version of BASIC (more on that later), the operating system, and other programs.

As for the display, a standard color-TV set or video monitor can be used. The display uses the standard 24 × 40 format for text and graphics. The machine has excellent color and graphics capabilities. And thanks to a TI9918 graphic IC, the MTX512 can accommodate up to eight virtual screens. Its graphic resolution is 256 by 192 pixels with a full 16 colors

available in the high resolution mode. Up to 32 sprites can also be created and used. (A sprite is a special type of user-definable character. By user-definable we mean that the user decides what the character will look like, what color it will be, and where the character will appear on the screen.) An 80-column adapter and an RGB color-output interface are also available.

The unit also comes with several I/O interface ports, which include a standard Centronics-compatible parallel I/O port for a printer, two game-controller ports for joysticks, and a sound output. A built-in 2400-baud audio-cassette interface lets you use an external cassette player/recorder for mass storage. There is also an RS-232 serial-port board (2 ports-per-board) available as an option. Another interesting I/O feature of this unit is the Oxford Ring. The Oxford Ring is a built-in communications system using ring nodes that allow up to eight MTX512's to be interconnected for office, school, or lab applications. That is accomplished using the RS-232 ports and the optional disk system. The MTX512 has a slot on the side for plugging in ROM cartridges, which also accepts Memotech's game programs such as Toado, Blobbo, Kilopede, Super Minefield, Continental Invaders, Chess, and several others. Additional games, and program cartridges such as the Pascal and Forth languages will be available in the future.

### Firmware

The special version of BASIC mentioned earlier is known as Oxford BASIC. Oxford BASIC is pretty much the stan-

# COMPUTER DIGEST

VOL. 1 No. 4 August 1984

NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

## IBM COMPATIBILITY...

It's a claim many computer manufacturers make. But just **HOW** compatible IS your computer?

### SOFTWARE DIAGNOSTICS

New software will analyze your disk drives and pinpoint problems before they start.

### MAKE YOUR COMPUTER'S MEMORY SAFE

When power fails, you could lose the entire memory. Here's how to keep that from happening.



A  
**GERNSBACK**  
PUBLICATION

# EDITORIAL

## Let's set the record straight.

■ I was having dinner with a friend last night, and he commented that I've probably got—to use his words—a very “cushy” life. “You sit around in a big, walnut-panelled office all day, giving orders, pretty secretaries running in and out, three-hour lunches...You've really got it made!”

'Taint so. Much of my work is done in my bedroom at home, working at my typewriter, wearing only a pair of shorts. When I can spend time at my “office,” where I just happen to be right now, I'm in a room perhaps ten feet wide by about fourteen feet long. The computer terminal at which I'm working sits on a Formica-topped table, perhaps four-by-six feet in size, and the room is filled with a bunch of mysterious cartons, an old copying machine, a green metal cabinet or two, and a bank of file cabinets. Glamorous? Hardly.

I'm certain that someplace this side of Hollywood, there may be an editor or two that lives the kind of life my friend's fantasy called up, but I've never seen it, and frankly, I hope I never do.

Editing a magazine is simply hard work. It's exceedingly rewarding work, but it's also hard work. What makes it rewarding is getting mail from people like you, who read the magazine, who tell us that they appreciate what we're trying to do. That makes it all worthwhile. Ask any editor worth his salt what he does for a living, and before long, you're going to hear him talk about his readers. You, the reader, are what it's all about. For example an editor might be personally interested in a subject covered by a manuscript that comes in from an author, but the acid test of whether or not the manuscript is purchased, is “How much reader appeal will it have?” Each and every decision that an editor makes is based on the reader's point of view.

That's why we want to hear from you. We're starting a “letters” column with this issue of **ComputerDigest**, and we'd like some feedback from you. If you like what we're doing, please tell us. If you don't like it, tell us that, too. Got some suggestions on how we can improve things? You'll be amazed at how we listen!

Of course, editors *do* make certain decisions on their own. For example, I just decided—on my own—I'm going to get a cup of coffee.

BYRON G. WELS  
EDITOR

# COMPUTER DIGEST

**Hugo Gernsback** (1884-1967)  
founder

**M. Harvey Gernsback**, editor-in-chief

**Larry Steckler**, CET, publisher

**Art Kleiman**, editorial director

**Byron G. Wels**, editor

**Brian C. Fenton**, technical editor

**Carl Laron**, associate editor

**Robert A. Young**, assistant editor

**Ruby M. Yee**, production manager

**Robert A. W. Lowndes**, production associate

**Dianne Osias**, production assistant

**Karen Tucker**, production assistant

**Jacqueline Weaver**, circulation director

**Arline R. Fishman**,  
advertising coordinator

Gernsback Publications, Inc.  
200 Park Ave. South  
New York, NY 10003  
Chairman of the Board:  
M. Harvey Gernsback  
President: Larry Steckler

## ADVERTISING SALES 212-777-6400

Larry Steckler  
Publisher

### EAST/SOUTHEAST

Stanley Levitan  
Radio-Electronics  
200 Park Ave. South  
New York, NY 10003  
212-777-6400

### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen  
Radio-Electronics  
540 Frontage Road—Suite 325  
Northfield, Illinois 60093  
312-446-1444

### PACIFIC COAST

**Mountain States**  
Marvin Green  
Radio-Electronics  
15335 Morrison St., Suite 227,  
Sherman Oaks, CA 91403  
818-986-2001

# IBM

# COMPATIBILITY

*IBM compatible? Sure! But just how compatible?*

MARC STERN

■ In the world of personal computers, there's probably no more controversial a topic than compatibility. There are so many stories about it because so many manufacturers want to make their systems just a bit different from others on the market.

Why? Most likely, it's the result of an effort by computer manufacturers to marry users to one company for all their peripheral and software needs. And who can blame them? It seems to make eminently good business sense (at least to the manufacturers—not necessarily to the consumers). But it has led to an abundance of incompatible operating systems, incompatible disk formats and sizes, and incompatible programming languages.

Frankly, it's a confusing, aggravating situation for the average computer user. It's a situation about which many computer users complain, but also about which they have very little control. The various manufacturers have control of the situation—and, for competitive reasons, it's unlikely they will agree on standards in the near future.

## Halting steps forward.

By and large, that situation is likely to exist in the personal-computer world for some years to come as droves of computer manufacturers enter, compete and leave the industry and new competitors take their places.

There have been some halting steps toward standardization. It's not due to any cooperation between the manufacturers. It's because of the dominant presence of certain disk-operating and

personal-computer systems in the marketplace. For example, the CP/M operating system has brought a measure of standardization to the 8-bit computer world, while the IBM *Personal Computer* and its operating system, PC-DOS, have brought some standardization to the 16-bit world.


Why have these two forces been so dominant? With CP/M, quite simply, it has been a matter of longevity and ubiquity. It was one of the earliest disk operating systems in the microcomputer world and, as such, many programs were naturally written to run under it.

For the IBM *Personal Computer*, the story is much the same. Because IBM is so dominant in the world of computers and because its *PC* has become a major force in the market, it was inevitable that it would become the standard in the 16-bit world. Even the 16-bit version of the venerable CP/M system couldn't compete with it (apparently because of poor marketing decisions).

## Limited standards.

Since CP/M has become the *de facto* standard in the 8-bit world and since it has been covered in the pages of **ComputerDigest** (May and June 1984), we will concentrate on what is becoming the standard in the 16-bit world, MS-DOS, or, as it is also called, PC-DOS, the operating system of the IBM *Personal Computer* and "compatibles."

At the start, let's understand that even though advertising hype may say a computer is "PC-compatible," the range of that compatibility can vary greatly. There are computer systems on the market—

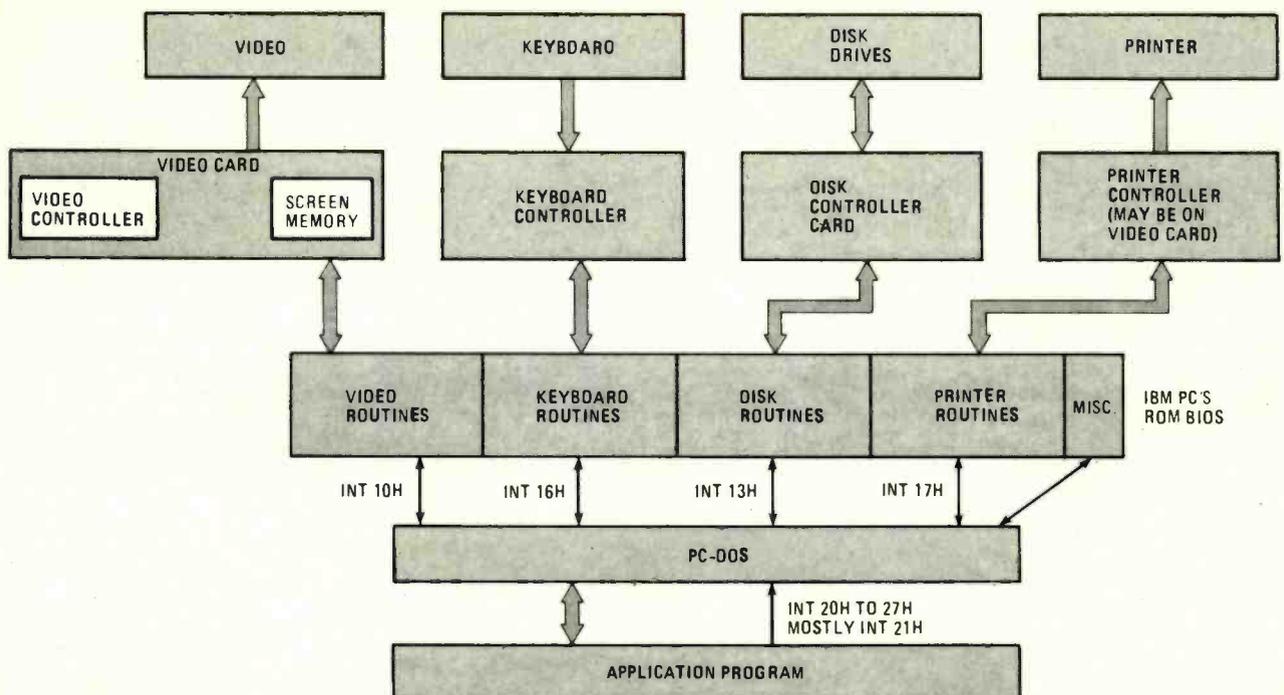

**FIG. 1—AN APPLICATIONS PROGRAM can access IBM PC hardware through PC-DOS. However, a program can also access the PC's ROM directly, causing incompatibility.**

such as the Leading Edge PC, Sperry PC, Corona, and Compaq—that can run just about any program available for the IBM PC. But there are others on the market, such as the Heath/Zenith H/Z 100 series that can only read IBM data disks. And there are still others that are only “DOS-compatible,” meaning they run MS-DOS but really can't handle program or data disks for the IBM PC.

*Theoretically*, any computer capable of running MS-DOS (MicroSoft-Disk Operating System) is capable of handling any program or data disk created or used by another MS-DOS computer system. In *reality*, it just isn't true. But it's not due to any fault of the operating system. Programmers can develop applications programs that will run under MS-DOS and that won't be difficult to move from machine to machine. But because of the way in which the IBM-PC—and those who write programs for the PC—handle things, programs that are developed for the PC may or may not run on a machine that is supposed to be compatible. On some “compatible” machines, however, the developers consciously tried to give users access to the wide base of IBM-backed programs. They succeeded in that 95 percent or even more of the programs available for the PC will run directly on those machines. But, on others, the developers were only striving for operating-system compatibility—meaning that they wanted a machine that could run MS-DOS. On such machines, few, if any, IBM-PC programs will run directly. Of course that doesn't mean that the programs cannot be rewritten so that they will run under MS-DOS. But let's see why they are not written that way for the IBM PC which, after all, is an MS-DOS machine.

### How IBM does it.

For a better explanation of why all “PC-compatible” machines aren't equal, let's take a look at how IBM does things.

When an applications program interacts with the PC hardware, it does so through PC-DOS. Keyboard I/O, video I/O, disk I/O, printer I/O, etc. are all handled by PC-DOS through software interrupts (which is something like calling a subroutine). But there is another way to access the PC hardware: through the PC's extensive ROM.

The advantage of using the PC's ROM instead of PC-DOS is that, in many instances, the ROM software lets you do more. For example, PC-DOS' video control is rather limited—its functions are much like those of a teletypewriter. You can send characters to the screen, but not much more. For example, you cannot directly position the cursor through PC-DOS. So word-processing programs, for example, go to the ROM, which contains extensive text- and screen-handling routines.

The routines in the PC's ROM are also accessed by interrupts. They can be accessed through PC-DOS (as shown in Fig. 1). But an applications program can “go around” PC-DOS and directly access the ROM-based routines. That (not shown in Fig. 1) is the real reason for the incompatibility problem.

The PC uses interrupt 10H (the H indicates a hexadecimal number) for video control, while interrupt 16H handles input from the keyboard. The system uses interrupt 17H to handle output to the printer, while disk input and output is handled via interrupt 13H (See Fig. 1). Those and other interrupts provide for most

programmers a chance to control the PC more completely than PC-DOS does. They write their applications programs accordingly.

For instance, when a programmer implements interrupt 10H to have direct access to the PC's video capabilities, he is given access to a set of powerful, proprietary, ROM-based routines; with those powerful routines he can make the screen do just about anything he wishes.

Interrupt 16H is used to access keyboard routines. PC-DOS can be used to get information on the keyboard. But programmers prefer to use interrupt 16H directly. You see, the PC's keyboard not only has the usual range of keys, but it also has 10 special function keys, and it is capable of generating an alternate set of characters. Some of the key codes are non-ASCII. PC-DOS can pass their values back to the program, but the ROM routine can do it in a more convenient form. So programmers use it.

The fact that so many programmers make use of the PC's ROM routines directly makes it hard for users of non-IBM machines. If you try to run a PC-DOS program on your IBM "compatible," you may find that the program makes many calls directly to the PC's ROM that may or may not be matched in your MS-DOS machines.

Of course, some developers have purposely opted to build their machines following IBM's blueprint as closely as possible, and some machines are more compatible than others. But on many machines, programs that use the proprietary capabilities of the PC will either fail to run or will run erratically, causing strange results or screen messages.

### Levels of compatibility.

If all things were equal in the world of microcomputers, then any program written to run under MS-DOS (PC-DOS) would be able to work on any MS-DOS machine. But, as we have seen, that just isn't the case. If you want a machine with 100% compatibility, a machine that will run all programs written for the PC without any surprises, then your only choice is to buy an IBM PC.

However, there are manufacturers who have chosen to implement IBM-like functionality in their machines and have made them nearly identical in capability with the PC. But don't forget that there are others who have only given their machines data-level compatibility, and still others who have chosen only to use MS-DOS without attempting to emulate the IBM PC. In a moment we will see the differences between those levels of compatibility.

In all honesty, there are limits to what the manufacturers can do because the routines contained within the PC's ROM are proprietary and copyrighted. So those companies that have chosen to implement a nearly IBM-like system have been forced to do massive amounts of engineering in order to achieve IBM-like capability, without violating any copyrights. An almost-fully-compatible machine must provide ROM calls like those in the PC (but they don't have to be in ROM). For close compatibility to be achieved, the video memory

must also be like the PC's.

With that said, you can now see that there are levels of PC-compatibility. The first level is nearly total compatibility, with the machine capable of using IBM programming and data disks and having the ability to create disks which can be read and used by the PC. The programming for those machines will also usually run without modification on the PC. (Although there will likely be some problems with BASIC unless each machine converts the BASIC instructions into the same single-byte tokens.) Near-total compatible machines can use PC programming and data disks, but their BASIC implementation will probably be different.

The next level can be considered system level or data compatibility. An example of such a machine is the Heath/Zenith H/Z-100. That microcomputer is capable of using IBM-generated data disks, but will run few, if any, PC-DOS programs. Instead, the user must employ a program ported over to the specific machine, but written under MS-DOS.

In this category of machine, the subtleties of the programmers become apparent. Because PC-DOS programmers make use of calls directly to IBM hardware, those calls usually don't work correctly on the data-compatible machines. The result is that programs that work correctly on the PC either won't run on the data-compatible computers or will run poorly, at best. If you can get them to boot and run, the chances are good that at some point in the program, your computer will head off into never-never land with the disk drive spinning.

The final category of machine is the DOS-compatible machine. That is, a computer that only uses the MS-DOS system and heads its own way as far as implementation and programs are concerned. It usually won't run any PC program and it usually can't use a PC's data disk. About the only apparent justification for calling it "PC-DOS-compatible" is from a marketing standpoint. It is apparently an effort on the part of the manufacturer to climb on the IBM bandwagon and gain from the popularity of the machine.

### Two good tests.

So how can you determine if a machine is a true compatible, a data compatible, or a DOS-compatible? There is an easy test, involving the programs *Microsoft Flight Simulator* and *Lotus 1-2-3*.

Those programs make heavy demands on screen and keyboard interrupts and machine calls. If they will run on a system being considered, then it is a good bet that it is a (nearly) true compatible. But if the computer just sits there with no reaction, then the machine is either only data compatible or DOS-compatible. If you are looking for a true compatible then that system isn't for you.

However, if you all you want is MS-DOS software and the ability to have 16-bit IBM-like power at your fingertips, as well as the broad variety of software available, then a data-compatible or DOS-compatible machine is the ticket because you can take advantage of familiar software names that have been ported to these machines. ◀▶

# DIAGNOSTIC SOFTWARE FOR DISK DRIVES

*Diagnose sick disk drives  
before they give you trouble.*

**HERB FRIEDMAN**

■Of all the various devices that go into a personal computer system, more often than not it's the disk drives that cause the most problems. If a computer fails, it fails: the screen fills with garbage and you know to press the reset key or recycle the power. If the printer fails it also fails: it stops printing, or feeding paper, or a good percentage of the printing is the wrong characters.

But a disk drive...it fails with finesse. It will work fine for 15 minutes, then fail to read data, and when you go to check it out it's back to reading data properly. Or it stores data on Monday, then won't feed it out on Tuesday. Or disk A: won't read data recorded on disk B.; while disk C: won't read data recorded on the computer in the next office.

Disk drives are very fussy, and rightly so. Consider, for a moment, the precision that we expect from something that sells for something like \$200 (the cost of a "bare" drive—meaning without power supply or case). We expect it to put down, in the space of 0.8 inch, at least 40 magnetic tracks that are so precisely positioned they can be sensed by any other disk drive (for the same computer) any where, any place, in any environment, anywhere in the world. We expect the polarization of the magnetic fields (the "alignment") to be so precise that data can be recorded on any disk drive and read by any drive. We expect the mechanism itself to be so precise that if we cycle the drive hundreds of thousands of times, the read/write head

will always be positioned right where it belongs.

Yes, we ask a lot from disk drives. That they work so well is almost magical. But disk drives work within such narrow tolerances that if wear or aging affects anything concerning the mechanical system the whole system "crashes."

Though a disk drive has many critical areas, for many years the only test commonly available to the average user was the "speed test." The speed of the 5¼-inch floppy disk is standardized at 300-RPM  $\pm 2\%$ . Actually, we strive for  $\pm 1\%$  because  $\pm 2\%$  is really 4% "worse case." (Figure it out: If disk A: is 2% high and disk B: is 2% low, though both are within tolerance, the disparity is 4%—and that's looking for big problems if any other adjustment isn't right "on the money.")

The typical speed test is done with software that provides a screen display of the disk speed, either through direct numerical values or through a graphic display. There are speed-test disks available for just about every major computer. Prosoft's (Box 560, North Hollywood, CA 91603) speed-test program called *RPM*, whose screen display is shown in Fig. 1, is representative of the better speed-test software. It continuously updates the data display, while the range of variation is stored by the graphic display—providing a visual indication of the speed range.

Most of the speed-test software available for personal computers is "memory resident," meaning the program loads into memory so the disk itself can be removed. The software disk must be removed because the software records test signals on a "blank" disk. (The speed test(s) will destroy any data on the disk.)

If you have ever examined a disk drive you will wonder why in heck you need test software when the

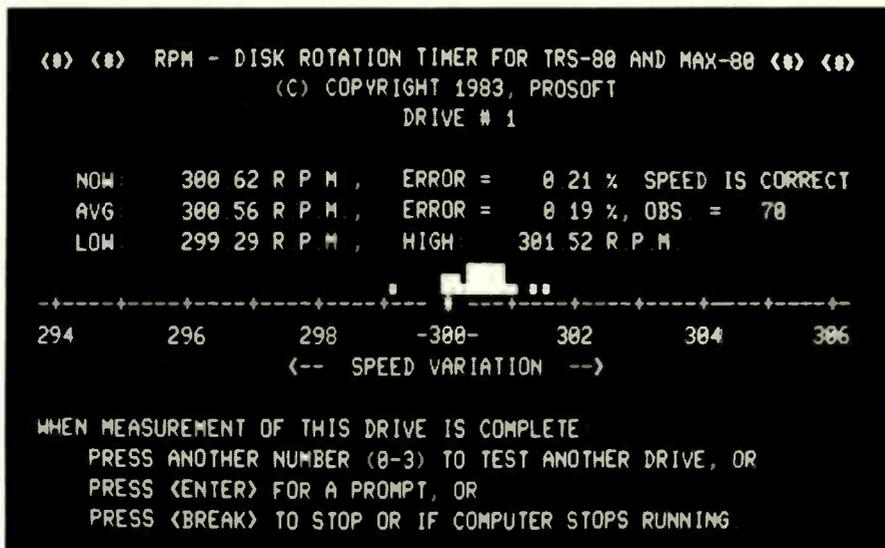


FIG. 1—THE DISK-DRIVE PROGRAM *RPM* displays the speed drift in both direct quantities and on a bar graph. Note the frequent read errors displayed on the graph.

disk drive mechanism has a "strobe" pattern on the flywheel or stabilizer (the metal weight attached to the back of the spindle that rotates the disk). Examined under the "pulsating" light from a fluorescent or neon lamp, the strobe pattern will appear frozen when the drive is running precisely at 300 RPM. So why use software when we can observe a strobe?

There are several reasons why software is preferable to "reading the strobe." First, you don't want to disassemble the drive's cabinet in order to view the strobe every time you feel it necessary to test the disk speed: it's a lot easier just to run software from a disk. Second, unless you're very skilled, it's almost impossible to determine if the speed is within tolerance, if the pattern is "drifting." Third, the strobe pattern doesn't easily disclose "crossover drift." By the time you notice the strobe pattern indicates a "low speed," the drive is running at a "high speed;" a real problem if you're attempting to adjust the disk drive's speed yourself.

Until recently, virtually all 5¼-inch drives in common use had a user-accessible speed adjustment. Generally, it was some form of trimmer potentiometer that could be adjusted using a small screwdriver or a TV-alignment tool. If a test disk disclosed that the disk speed was incorrect, the user could bring it "on the mark" by simply running the software and adjusting the potentiometer until the screen presentation was as close as possible to 300 RPM.

But technology eventually outruns the consumer. Some (and soon all) of the modern disk drives have electronic servo speed control that is often referenced to a crystal-controlled oscillator; hence, there is no user adjustment. The most the speed test disk can do is

indicate whether the servo circuit has failed: the actual repair or adjustment must be made by a service shop.

### Speed checks aren't enough

Poor speed adjustment is just one of the many things that cause disk read errors. Unfortunately, until recently the only software available to the average user tested only the disk speed, nothing else. The specialized software that tests all the disk drive adjustments, such as clamping (hub eccentricity), head alignment and sensitivity, mechanism hysteresis, and head azimuth was available only to the disk manufacturers.

Actually, all the required tests are on a single special diagnostic test disk manufactured by Dysan (5201 Patrick Henry Drive, Santa Clara, CA 95050), the same people who produce high-performance blank disks. The problem is that the Dysan diagnostic requires a


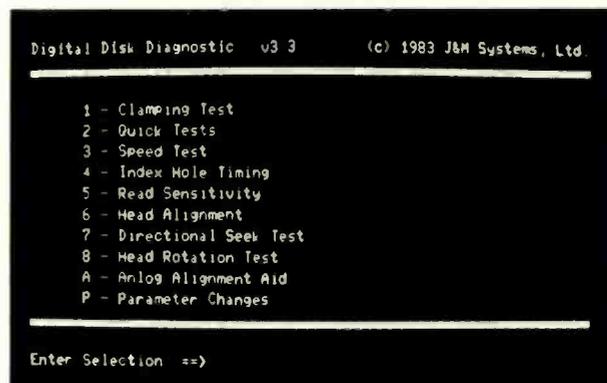


FIG. 2—THE MENU FOR J&M's DDD test disk. Other software well might have a different menu for the same functions.

separate in-memory runtime program written for a specific computer, so until recently the diagnostic disk wasn't available to the average user.

But create a need and someone will write the necessary program. Presently, J&M Systems (137 Utah NE, Albuquerque, NM 87108) markets a complete diagnostic kit consisting of the Dysan Diagnostic Disk and a separate disk with runtime software written specifically for the Radio Shack Models III and 4. By the time you read this article, Dysan themselves will have introduced a disk-drive diagnostic package for the IBM PC (and expects to have diagnostic packages available for other computers in the near future).


The Dysan Diagnostic Disk—which they and everyone else refers to as the DDD—is read-only and contains many different standardized tests and checks recorded in precisely-positioned tracks. When you run

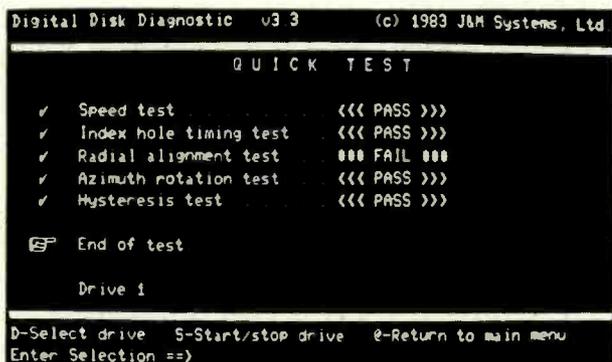

**FIG. 3—THE QUICK TEST does just what it claims: It tests the drive and compares the results against built-in standards. Note that the drive failed the radial-alignment test.**

the DDD you are actually comparing the performance characteristics of your disk drive against recognized standards.

While the visual displays will depend somewhat on the specific diagnostic package you use for your computer, the J&M screen displays are representative of what you can expect. While no one suggests that you muck around inside the drive and try to make adjustments using the screen display, it's really possible for a skilled technician to calibrate a drive using the

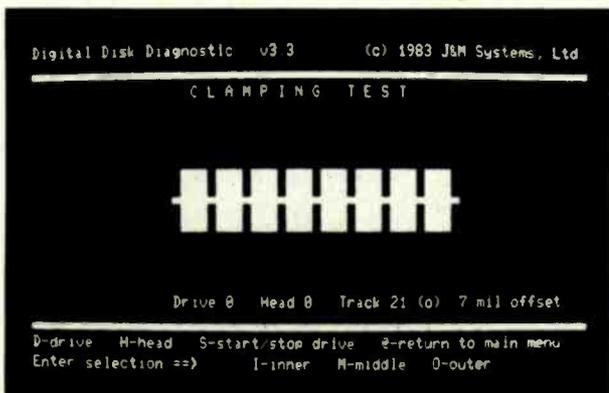

**FIG. 4—THE CLAMPING TEST checks the condition of the disk's hub, and also the drive's clamping mechanism. The eight rectangles indicate that the disk is properly centered.**

DDD. In fact, some of the tests are specifically intended for aligning the drive.

All tests are selected from the main menu shown in Figure 2. The DDD provides several individual tests, but if you're in a hurry and want to do quick-and-dirty periodic checks, the DDD contains a "Quick Test" for speed, index-hole timing (you've never heard of that test?), radial alignment (or that one?), Azimuth rotation, and hysteresis. (See Fig. 3.)


The quick test has its own *pass-fail* limits that are compared against the results of the other tests which are run automatically by the resident software. Unlike the individual tests which provide reference values, the quick-test screen display is pass-fail. If you want more specific information, you can run the individual tests.

The first specific test to run is for *clamping*, as shown in Fig. 4. Clamping is a function of the condition of the diskette's hub. The purpose of the clamping test is to insure that the test disk is properly centered around the drive spindle. Also, the clamping test checks the alignment of the read/write head. If the screen doesn't display a perfect set of eight rectangles, as they say, "You got big trouble!" It's probably the reason that disks written in drive A: gives read errors when read in drive B: (and vice-versa).

The clamping test proved to be an accurate guide to the overall performance of disk drives. We had one computer with three drives (Nos. :0, :1, and :2) that was producing sporadic read errors on drive :1. The first time we ran the clamping test we got nowhere near the eight rectangles on drive :1. Further tests indicated just about every conceivable problem with the drive. While no problem was extreme, they combined to produce a worst-case condition—having errors at the limits of the tolerance ranges—that resulted in sporadic read errors.

For example, the speed test, which is indicated on a bar-graph screen display calibrated from 294 to 306 RPM with 300 RPM at the center. (The maximum limits of  $\pm 2\%$  are represented by 294 and 306 RPM.) Drives :0 and :2 produced readings which—more or less—remained where they started out. Drive :1 produced a reading that wandered back and forth, always within tolerance but continuously drifting—an obvious harbinger of doom to come.

For soft-sectored disks—the kind with only one

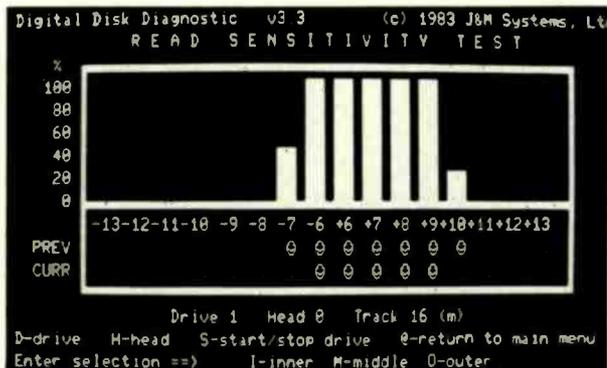


**FIG. 5—READ SENSITIVITY is a good indicator of the ability of a drive to read disks recorded on other drives. The display shown indicates that drive 1 passes, but barely.**

sector hole—between 100 and 30 microseconds should elapse from the leading edge of the index hole to the beginning of the sector mark. The measured timing is indicated by a bar graph with 200 microseconds—the optimum value—at the center. Actually, unless the drive literally falls apart or the LED that shines through the hole or its photodetector fails, you should never find the screen display in error. If you must align the index hole timing simply move the photodetector while observing the display. (*Don't do it unless it A) needs it, and B) you know what you're doing.*)

*Read sensitivity* is the ability of the drive to read low-level signals from the DDD. The signals that test for sensitivity are recorded progressively offset from the centerline of the track. The more sensitive the head the greater the offset that can be read.

As shown in Fig. 5, sensitivity is indicated by a special bar graph that indicates how many times out of five tries the offset is read. The results are expressed in percent. (As the drive mechanism ages, the upper and lower limits of the display are reduced.)

The same bar graph is used to indicate head alignment. If the bars are displaced, the head is out of alignment. As we've discovered, if all heads are similarly out of alignment, they cancel the error and disks from drives having the same misalignment can be read (within limits). But read errors can occur when a

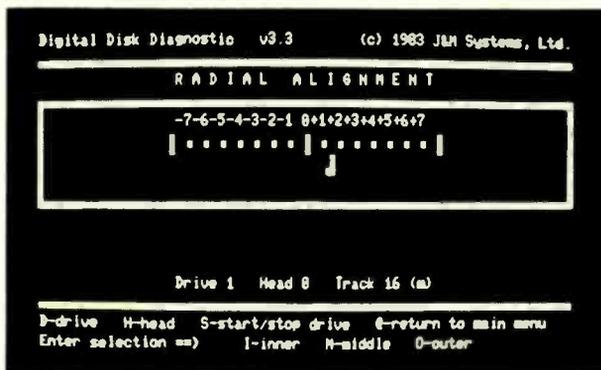


**FIG. 6—THE RADIAL-ALIGNMENT TEST must be interpreted in terms of the other tests. Here, drive 1 is shown in alignment, yet all other tests, including the Quick Test, indicated a problem with drive 1. The reason the Quick Test failed is because it combines both read sensitivity and head alignment into the "radial-alignment" quick test.**

misaligned head tries to read data recorded on a properly aligned head, or one misaligned on the opposite side of the center mark.

The radial-alignment test is similar to the read-sensitivity test except only the center of the total good sectors is displayed, thereby making for a much more sensitive display when aligning a drive. As shown in Fig. 6, a special zero-center radial-alignment bar graph is displayed, and the object is to adjust the head alignment so that the display is as close as possible to the center of the scale—the "0" mark.

The directional-seek test is the one that exposes really worn mechanisms because it tests the

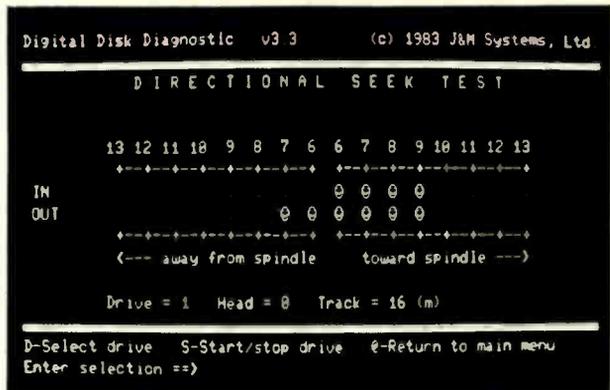

**FIG. 7—THE DIRECTIONAL-SEEK TEST indicates either excessive wear or a poorly manufactured drive. Note the results from drive 1, our problem drive.**

mechanical parts that move the head back and forth, the parts that get the most wear. This test uses "happy faces" to indicate both proper operation and misalignment. (See Fig. 7.) If the two rows of happy faces aren't in alignment it's likely the head-positioning hysteresis is defective. It works this way: The head is moved *inwards* to the test track and then *outwards* to the test track. If the mechanism isn't worn, it will center on the test tracks regardless of which direction it is moved. If the head positioning mechanism is worn, the head takes different positions on the inward and outward positioning. Each direction is represented by its own row of happy faces; if they are stacked one above the other the alignment is perfect. The greater the radial misalignment of the head the greater the misalignment of the happy faces.

The head-rotation test or azimuth test is analogous to the alignment test for conventional audio tape recorders. It provides an indication of the angle at which the head intercepts the track's center-line. It uses a special bar-graph display that indicates centering of the pattern. The better the centering, the more precise the head's alignment with the track.

To assist the technician in adjusting the disk drive, the J&M package contains a special *Analog Alignment Aid* program that provides such functions as disk-drive start and stop, select drive, step head in and out, seek track, restore to track 0, etc. All those are procedures for a *qualified* service technician. In no way should the casual user, or even a computer hobbyist, attempt a drive alignment with the program. It requires special knowledge and test equipment, and the service manual for the specific drive.

### Summing up

Though diagnostic disks were originally intended for the service technician, they are an invaluable aid to even the applications-oriented user when disk drives start to do peculiar things: when they read properly on even days of the week, but not on the odd days; when they read only when the disks are warm; when disks from drive C: will read in drive B: but not in drive A:. At the very least, they give you an insight into whether the trouble is in the drive or the computer. ◀▶

# HOW TO MAKE YOUR COMPUTER'S MEMORY NON-VOLATILE

TJ BYERS

*Don't let power failures wipe out that valuable data forever!*

■Ask any computer enthusiast a question about his system—*any question*—and his answer will likely ring with sounds of 64K, 128K, and so forth. Memory has become a buzzword within the computer community. Usually, the larger the memory cache, the more powerful the machine is considered to be.

In large part, most computers use static or dynamic RAM IC's for their memory. Unfortunately, semiconductor memory is volatile. Once power is removed from the device, whether it is accidental or intentional, everything is "forgotten." The sudden loss of power can be most frustrating when you're running a long program or doing word processing. Hours of work can be wiped out in a split second.

Unquestionably, there is a need for a memory that can retain its contents even in the wake of a disaster.

## Battery support

The most obvious solution is to place a battery within the memory circuit. Basically, the battery is paralleled with the main power supply and maintained in a standby state until it is needed.


Under normal operating conditions, the computer's main power supply is operating and furnishing power to the RAM. In the event of a power failure, however, the power supply drops out of commission and the battery takes over the task of supplying power for the memory so that the data is not lost.

It is fortunate, indeed, that most memory IC's don't require a full 5 volts in order to retain their stored bits. You'll find that the IC's will maintain their memory with voltages as low as 3 volts. That means that a 5-volt power source is not essential for memory support. Lower voltages can be used, thus relaxing the battery requirements.

## Battery isolation

To prevent damage to the battery by the power supply during normal operation, a switching circuit is employed to remove the battery from the circuit unless it is needed. A simple diode switch, like the one shown in Fig. 1, does an excellent job of isolating the battery from the power supply.

The switching circuit uses two diodes to steer currents in the proper direction at the right time. Remember, the battery voltage is normally lower than the 5-volt power supply; it is usually in the neighborhood of 3 to 4 volts. Because the power

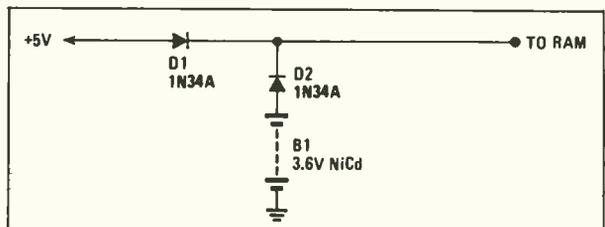

**FIG. 1. DIODES WITH LOW forward voltage drops work best in this circuit. Although Schottky diodes usually come to mind first, the trend has been to germanium diodes such as the 1N34A.**

supply voltage is higher than the battery voltage, diode D2 becomes reverse biased. Hence no current can flow either to or from the battery, thus isolating it from the rest of the circuit.

When the 5-volt source is removed, though, D2 is no longer reverse biased, and current can flow from the battery and provide power for the RAM IC's. Diode D1 now acts as a blocking diode which prevents the battery current from backing up into the power supply and other computer circuits.

A common choice for the auxiliary battery is the NiCd or nickel-cadmium cell, (commonly known as a "NiCad").

## Battery monitor

The voltage across a fully-charged NiCd cell is about 1.2 volts. By stacking three NiCd cells in series, we can make a battery with an output of 3.6 volts—well within the range needed for memory protection.

NiCd batteries have virtually flat discharge curves, which makes them very attractive for computer applications. However, leakage current inside the battery causes the cells to self discharge. The amount of self discharge is dependent upon the type of battery you use and its surrounding temperature. Regardless of the battery though, the entire charge will eventually bleed itself off.

Now this battery death could occur at a most inopportune moment—usually when you least expect it. A quick check of the batteries from time to time will eliminate the problem. But that simple chore often goes undone until it's too late.

Fortunately, Intersil (10710 N. Tantau Ave., Cupertino, CA 95014) makes an inexpensive battery monitor, the ICM7201, that can solve this problem. (That IC is sold through most Radio Shack stores.) Figure 2 shows a simple circuit that lets you monitor the battery voltage.

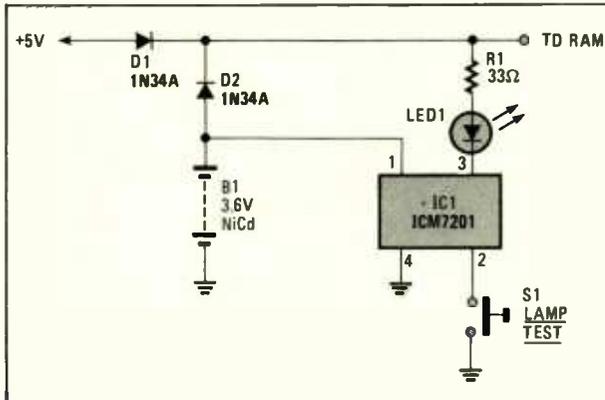


FIG. 2. GROUNDING PIN 2 will light the LED, thus providing a lamp-test feature.

The ICM7201 is a four-lead device that measures the voltage of your battery pack and can be used to give a visual indication of the battery's condition. As long as the battery voltage remains above 3.1 volts, the LED does not light. But if the voltage dips below 2.9 volts, the LED will light, indicating that only 5% of the battery's charge is left. That means that it's time you

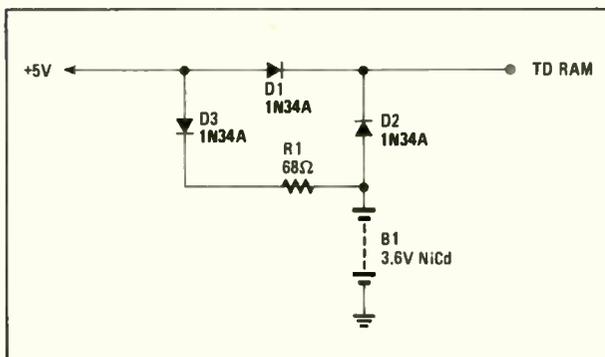


FIG. 3. A 68-OHM RESISTOR limits the charging current to 10 mA.

recharged your NiCd cells before they die altogether.

## Battery charging

In most cases the NiCd's can be charged right from the 5-volt line. The charging current, however, must be limited. That's easily accomplished by inserting a resistor between the 5-volt source and the battery, as shown in Fig. 3. The value of the resistor is selected so that the charging current satisfies the charging requirements of the battery, while staying within the limits of the power supply.

Depending upon the cell you use and your particular system, the value of the current-limiting resistor will vary from one application to the next. Calculating the value of that resistor is easier if you realize that the battery is actually placed in a float application. That is, the battery doesn't ordinarily have to supply power and it simply "floats." That means it has plenty of time for recharging between uses. Therefore, the charging rate can be rather small in comparison to other charging schemes.

Normally, a trickle current is all that's needed to keep the battery alive. As a rule of thumb, the trickle current is numerically equal to or less than 10% of the battery's rated capacity. For example, a standard "C" size NiCd cell, which has a capacity of 1200 mA, should be charged with 120 mA, no more. Otherwise you run the risk of overcharging the cell, and quickly destroying it.

Notice that another blocking diode, D3, has been added to the circuit. Its function is to prevent the discharge of the battery through the power supply via the charging resistor in the event of a power failure.

## What battery size?

How long will a fully-charged battery last? That all depends upon the battery itself and the number and type of RAM IC's it has to support. Bipolar RAM's, like the 2101, are pretty power hungry, drawing as much as 5 mA each in the standby mode. CMOS memory IC's, on the other hand, draw very little current, and the battery can be expected to last considerably longer.

Size the battery to your memory power requirements and the time you need it serviced. Let's say, for example, that your memory demands 5 mA. If you select an "AA" cell, which has a capacity of 500 mA, the battery can maintain the memory for about 100 hours. Remember, you will need three cells in series.

## Lithium batteries

One of the problems facing the user of batteries for backup power has always been shelf life. The longer a battery sits, the more charge it loses, even if it's not being used. The NiCd overcomes that problem by constant recharging.

Unfortunately, charging circuits are bulky and expensive. They add to the cost of providing memory protection and require considerable board space.

Recently, a new battery has come into the picture which eliminates the shelf-life problem: the lithium battery. Lithium batteries have a shelf life that exceeds

ten years!

Lithium cells also have another characteristic that makes them particularly attractive for computer use. Most batteries, as you know, generate less than 2 volts. The carbon cell produces 1.5 volts and the NiCd stores 1.2 volts. A lithium cell, on the other hand, develops 3 volts. That means one lithium cell can do the work of two flashlight batteries or three NiCds.

That results in a considerable savings of space—a commodity so precious in cramped computer cabinets. And because lithium batteries are primary cells, they require no charging circuits.

When the lithium battery is teamed up with the CMOS memory IC, a natural match up occurs. (See for example, the non-volatile memory add-on for the Sinclair ZX81 in the July and August 1983 **Radio-Electronics**.) The newer static-RAM designs consume almost no power in the standby mode, and the lithium cell will last as long as its shelf life when used in this application *even with constant use!*

Consequently, many lithium cells come with solder tabs rather than button contacts. The battery is simply soldered in place right on the memory board. The chances of the battery going dead before you service the board are very slim.

A more recent development is the introduction of a RAM IC that contains its own battery source. That IC, manufactured by Mostek (1251 W. Crosby Road, Carrollton, TX 75006), plugs right into the same socket as a conventional memory IC and provides its own standby power in the event of a power failure.

### Write protection

In most cases, it is not advisable to alter the data within the RAM after the operating voltage has dropped below 4 volts. That precaution is especially critical once the backup battery has taken over control of the IC. First, it requires more power to keep a RAM in its operating mode than it does to keep it in its standby mode. Since the battery already has a limited supply of power, that's important.


Second, and more important, the data bytes don't always write properly when they are entered under low-voltage conditions—the probability of an erroneous entry is quite high.

To protect against accidental data changes therefore, the write function must be disabled while the RAM is in the standby mode. That can't be done with our simple circuit of Fig. 1. We must instead go to a more sophisticated design, which senses the difference between the proper 5-volt input and a low-voltage condition. An example can be seen in Fig. 4.

Monitoring the supply voltage is a low-voltage sensor. That sensor can be built from a comparator. The output of the sensor drives switching transistors Q1 and Q2. When the 5-volt input is present, Q1 is switched on and Q2 is off. Current flows from the power supply, but not from the battery.

When the 5-volt line falls below the preset limit (usually 4.5 volts), the output of the low-voltage sensor toggles: Transistor Q1 drops out, and Q2 is activated.

Battery power now supports the RAM. At the same time, the low-voltage sensor inverts the input logic to the NAND gate, which prevents the chip-enable signal from reaching the RAM. Essentially, the write operation is locked out.

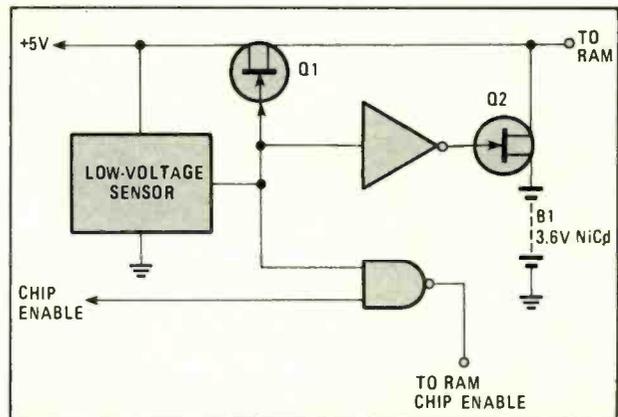

**FIG. 4. IT IS NOT ADVISABLE to alter the data within the RAM after the operating voltage has dropped below 4 volts. The low-voltage sensor essentially locks out the write function when the +5-volt line disappears.**

### Installation

Unfortunately, we cannot instruct you on installing battery protection for your particular computer—computers vary considerably from one model to the next. However, the following guide should help you along. But remember that each conversion is unique. Also remember that this modification might void your computer's warranty.

Your first task is to remove the cover and locate the memory IC's and the power leads.


You want to isolate the memory IC's from the main power supply, but not the other circuits. You can do that by cutting the power-supply traces on the board in the proper place using an *Exacto* knife. You may need to make two cuts: One at the input and one in the outgoing line(s). You can then use a jumper to bridge the gap and supply power to the other computer circuits.

Once that is done, all you have to do is to add one of the circuits—such as the ones in Figs. 1, 2, and 3. The hard part is making sure that the components fit on the computer board. If they don't, place them on a separate board and run wires to the memory section.
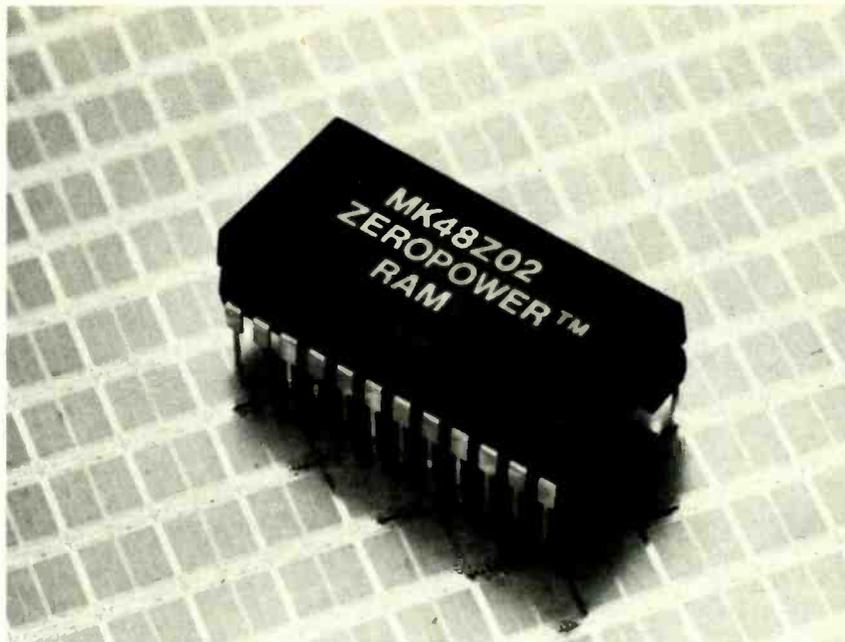
### Standby regulators

Sometimes though, you don't need full-time memory protection. For example, there may be times when you want to temporarily shut down the console without having to dump the memory. Removing the power source to the regulator will, of course, shut everything down and reset the memory. For such applications, a special voltage regulator has been developed. The LT1005 from Linear Technology (1630 McCarthy B'ld., Milpitas, CA 95035) is a dual-output regulator that contains two regulated 5-volt outputs instead of the usual one. (See Fig. 5.) The main power line is controlled by an enable pin on the regulator. A logic

THE MOSTEK MK48Z02 contains its backup batteries within the IC package.



high to that input enables the main 5-volt output. Pulling the input low kills the output.

The second output is a low-current 5-volt source that supplies power to the memory portion of the computer. It too, is regulated. That output remains on, even if the main output is turned off or shorted.

In other words, the memory will be preserved while the bulk of the system is shut down.

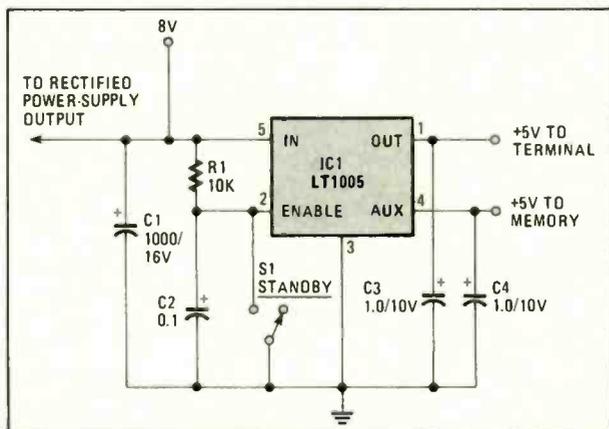


FIG. 5. A DUAL-OUTPUT REGULATOR can provide standby power for the memory while the main systems are shut down.

### Mostek's MK48Z02

We mentioned earlier an IC that contains a static RAM and lithium battery in one DIP (Dual In-line Package). The MK48Z02 combines the low power requirements of CMOS technology with the long lived energy of the lithium battery. But unlike other designs that use external lithium batteries attached to the memory board, the MK48Z02 contains its backup batteries right inside the IC package!

The memory portion of the IC contains a 2K by 8-bit CMOS static RAM. The unique thing about this RAM is its low power requirements. By using advanced CMOS

technology, Mostek has been able to reduce the power consumption of the static RAM to an ultra-low 5 nanoamperes. That's about as close to nothing as you can get. In normal operation, the IC functions identically to any other static RAM and has an access time of less than 200 nanoseconds.

Also contained on the chip is an analog voltage sensing circuit that consumes very little power. The precision voltage sensor continuously monitors the +5-volt line. When the voltage falls below 4.5 volts, control logic within the sensor disables the RAM's write circuits and prevents the write-enable signal to the array from becoming active. That play locks the memory into the IC and prevents accidental data changes.

After the 5-volt line falls below 3 volts, a switching circuit connects one of the two lithium batteries to the RAM's power distribution bus and disconnects the external power supply. The sensor circuit monitors the voltage of the two batteries contained in the IC. Whichever battery has the highest voltage is the one selected to power the IC. The lithium batteries are removed from service once power is restored.

The batteries are actually welded into the case of the MK48Z02. In other words, they are not replaceable. Just how long, you might wonder, will the batteries last? Well, with the combination of low-power consumption and high-battery power, the estimated life of the batteries is ten years.

What happens after the batteries are finally used up? Do they have to be replaced, or will the IC still function? According to Mostek, the IC simply reverts to a standard RAM. It will now use the 5-volt line to power its internal circuits, and completely disregard the internal batteries. Unfortunately, that leaves the memory vulnerable.

It appears that Mostek has succeeded in developing the perfect memory IC. They have avoided the pitfalls of EPROM's while maintaining nonvolatility.



# LETTERS

## PRO...

Dear Editor:

**ComputerDigest** is what I've been waiting for. Most computer magazines have no meat in their articles. They seem to be sales pitches for their advertisers.

**Radio-Electronics** had a good idea in keeping **ComputerDigest** as a separate section instead of scattering it throughout the magazine. Your thoughtfulness is appreciated.  
*Albert Shugzdis, Arkadelphia, AR*

Dear Editor:

Congratulations! I think **ComputerDigest** is heading in the right direction. I cast my vote for its survival and perpetuation!

I pray the "old pros" and electronics purists will be unable to gang up and force you to abandon your new and most promising effort. I think it makes **R-E** all the more valuable.

I also happen to be a fan of Herb Friedman. His piece on CP/M was superb. Wish I had something like that a couple of years ago. Mr. Friedman does a terrific job of boiling the best out of his subject. Please tell him to keep up the good work.  
*William H. Raden, Toledo, OH*

Dear Editor: I welcome the appearance of **ComputerDigest**. As you point out, no one can afford to buy all the computer magazines.

I hope you won't fall into the snare which has captured too many computer magazines. The world does not begin with IBM nor does it end with Apple.

I'll be looking forward to the next insert in **Radio-Electronics**. I've been a Gernsback fan since my youth.  
*Robert J. McGarvey, Kendall Park, NJ*

## ...AND CON.

Dear Editor:  
Regarding **ComputerDigest**:

Although it hasn't taken any space away from the regular **Radio-Electronics** editorial features, it must cost a lot of money that could better be spent on developing a series, or several series of articles for the home experimenter. It looks like just another computer magazine, even though it claims otherwise. My subscription is to **Radio-Electronics** and I expect my subscription dollars to be spent keeping it the best electronics publication possible. I do not want its precious resources diverted to another computer magazine.  
*W. M. Tuleja, Boilingbrook, IL*

Dear Editor: Regarding your new computer magazine, my advice is "Don't do it!" I want a magazine that covers the entire field of electronics. Sure, an occasional computer article is fine, but don't dwell on them. There is so much more in electronics that is equally, if not more fascinating.  
*Gary Gordon, Cincinnati, OH*

# COMPUTER PRODUCTS

For more details use the free information card inside the back cover


**CARTRIDGE WORD PROCESSOR**, "Write Now", catalog number C02 is designed for the Commodore-64 personal computer. It has a built-in 80-column display, and the user sees exactly what will print. Its features include: easy full-screen editing; compatibility with any printer; special codes



CIRCLE 121 ON FREE INFORMATION CARD

that can be transmitted to printers maintaining justification, and unlimited recall. Finding or replacing any copy is easy, and full-block command enables moving or deleting entire blocks of copy. The "Write Now" cartridge word processor is priced at \$49.95.—**Cardco, Inc.**, 313 Mathewson, Wichita, KS 67214.

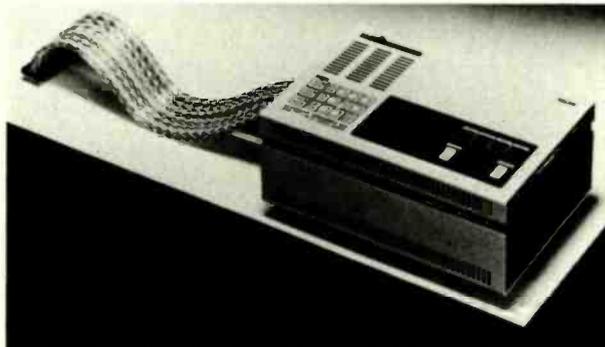**IN-CIRCUIT EMULATOR**, the model ICD-178 68000, has the following features as standard: It emulates the 68000, 68008, and 68010 in one unit to 10 MHz. There is 128K of emulation memory (expandable to 256K), a 4K x 48 bit realtime trace buffer, and 3 hardware and 8 software breakpoints.



CIRCLE 122 ON FREE INFORMATION CARD

The unit can also be connected to the IBM PC with optional software package that turns the PC into a complete development system for the 68000. The model ICD-178 68000 is priced at \$7,995.00.—**Zax Corporation**, 2572 White Road, Irvine, CA 92714.

dard BASIC, with statements and commands similar to those used by Microsoft and other popular BASIC language interpreters. However, one uncommon feature of this BASIC is that it contains LOGO-like commands that can be used in creating special graphics effects. Those include: MOVE, ADVANCE, ROTATE LEFT, ROTATE RIGHT, and SPRITE commands.

In addition to BASIC, the on-board ROM includes an assembler/disassembler. Name another machine that gives you an assembler/disassembler as standard equipment. There is also a special program called "Front Panel" that provides you with the full capabilities of a standard machine-language monitor. That program is one of the best ones that we've seen; it not only allows you to display and change all register and memory contents, but it also automatically disassembles a portion of the memory content shown on the screen. Three virtual screens show the full-register contents simultaneously along with a 256-byte block of memory in a hex format and a completely disassembled portion of that hex code complete with mnemonics.

You can also single-step the machine and assembler programs one instruction at a time—that feature should prove to be invaluable for such applications as debugging. While the machine/assembly language capability is not often used by the average personal-computer user, it is ideal for learning computer operation and programming, or such things as developing your own special routines.

One exciting bit of firmware included in ROM is a special language called *NODDY*. Its primary application is in developing programs that display sequential blocks or frames of information where the next block shown depends on the response to the previous frame. With that capability, *NODDY* should be great in creating question-and-answer sequences, exams, and computer-aided instruction (CAI) programs.

The *MTX512* uses the standard CP/M operating system, which puts the entire CP/M applications program library at your disposal. The latest version of CP/M, CP/M Plus (Version 3.0), is included with the disk-drive option.

Overall, the Memotech *MTX512* is an interesting machine; although there is nothing particularly new about a unit with a Z80 microprocessor and the CP/M operating system. What is different here, however, is that few, if any, Z80-CP/M machines feature full-color graphics. Also, most do not contain anything like the *Front Panel* program, assembler/disassembler, or the terminal-emulator program built into this one.

With its color graphics and joystick, the unit would be a good home computer to play games and learn to program on. In

addition, the *MTX512* can also be a serious business machine because of its CP/M operating system and software base. Wait 'til you see some of the more popular CP/M programs like WordStar in color: What other Z80-CP/M machine can do that?

In the United Kingdom, the European version (*MTX500*) has little competition. Its main competitor is the popular BBC *Acorn* microcomputer. The U.S. version has already been well received and is obviously on its way to being a best seller, although the competition here is much tougher. Its most direct competition will

probably be from the Franklin Ace (an Apple clone), the Commodore 64, the Apple IIe, and the IBM PCjr. Yet the *MTX512* has some uncommon features and benefits that make it worth considering. It's a great machine for the hobbyist or experimenter and dynamite for educational applications.

Billed as a "world class computer," the basic *MTX512* is priced at \$595 and is available at many dealers throughout the U.S. For those who want more information, you can write Memotech at 7550 West Yale Avenue, Suite 200, Denver, Colorado 80227. **R-E**

## Where's Your **ELECTRONICS CAREER** Headed?

Put Professional Knowledge and a **COLLEGE DEGREE**

in your Electronics Career through

**HOME STUDY**



Earn Your **DEGREE**

No commuting to class. Study at your own pace, while you continue on your present job. Learn from easy-to-understand lessons, with help from your instructors when you need it.

Grantham has been training students for electronics degrees longer than any other home-study, independent-study, or correspondence institution. *Grantham is the only school in the United States offering an accredited B. S. Degree in electronics by home study, independent study, or correspondence.*

Our free bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for our free **Bulletin 8-84.**

Grantham College of Engineering is a specialized institution catering to mature individuals who are employed in electronics and allied fields such as computers. The field of electronics is so enormous that opportunity for advancement is always present. Promotions and natural turnover make desirable positions available to those who are *prepared to move up!*

Advancement in electronics is made easier and more certain by (1) superior knowledge, and (2) documentation of that knowledge. Grantham specializes in making both 1 and 2 as listed above available to you.

Grantham's home-study program leading to the

**B. S. DEGREE**

may fill an important need for you. This is a comprehensive correspondence program in which you first review some things you already know, in preparation for the studies that come later. Some previous knowledge in the field is presumed, but is thoroughly reviewed in depth, so as to give you a thorough foundation for the level of studies you have not previously undertaken. Even though some students hold associate degrees before enrolling, an A. S. Degree is awarded along the way toward the B. S. Degree.

For full information, write for **Bulletin 8-84**

**Grantham College of Engineering**

**2500 So. La Cienega Blvd.**

**P. O. Box 35499**

**Los Angeles, CA 90035**

# COMMUNICATIONS CORNER

## A new era of personal communication

HERB FRIEDMAN, COMMUNICATIONS EDITOR

IN A RECENT ANNOUNCEMENT CONCERNING FM stations, which went unnoticed by most of the general public, the FCC opened up a whole new era in personal communications. In fact, many FM stations are already spending money that they have yet to earn. And the Public Broadcasting System (PBS) envisions a national personal-communications network that will bring in millions of dollars for the always financially-strapped public service and educational television systems.

The key to that somewhat grandiose, but not impossible, dream is the recent decision by the FCC to lift virtually all restrictions governing SCA (Subsidiary Communications Authorization) subcarriers, which are "piggybacked" on the main channel of FM-broadcast stations. To give you some idea of what we're talking about: A "subcarrier" is impressed or multiplexed on an FM-broadcast signal. That signal, transmitted along with normal programming, passes through standard FM receivers undetected—the general listening audience hears only the "main channel." But a special attachment added to the receiver detects the SCA subcarrier, thus providing SCA programming without interference from the main channel.

The SCA service was part and parcel of the restructuring of the FM service in 1945, which moved FM broadcasts to the present 88–108-MHz band. Initially, the SCA service was simply background music (such as Musak) for restaurants and offices, etc. It was originally intended to provide FM stations with a dependable alternate income, while building up a listening audience on a band for which there were few (if any) receivers. Eventually, SCA service grew to accommodate services for specialized audiences, such as talking books for the blind and foreign-language programming. There were even experimental digital-data transmissions of stock-market quotes and news reports. They represented the bulk of SCA-service transmissions with few exceptions.

But the FCC, with its February 1983 decision to deregulate SCA service, has opened up a whole new era in personal communications through common-carrier services. No longer will radio paging be available only through the VHF paging

and telephone services. With the new ruling, any group can have their own paging system, if they can find an FM station that will rent them a subcarrier.

As for the national radio-paging service envisioned by PBS, all the user would need to receive radio paging in any major city, and most minor cities, in the U.S. is a pocket pager that can be tuned to the local PBS station. For example, assume that you travel from Boston to Chicago; when you reach your destination, you'd simply tune your pocket-pager to the local PBS station. Now, when your office back in Boston wants you to call them, they call the PBS station in Boston and give them your code and location (Chicago). PBS would then relay the message to its Chicago affiliate, who would then transmit the signal to activate your pager. Then again, perhaps a national directory will be made available, thus allowing your Boston office to directly contact the Chicago service.

Another advantage of the service would be when you're on the road and your office needs to contact you. All they would have to do is simply arrange to have your pocket-pager code broadcast by several stations along the route that you're travelling.

In addition to that, suppose you're travelling cross-country, crossing vast stretches of the nation where it's likely that there would not be an FM station for several hundred miles. Well, that's when satellite paging could come into play. The satellite transmission could close up the void created by the lack of FM broadcasting in any area.

There are also several other possibilities for communications via an SCA service. For example, providing selected stock quotes through digitized SCA-transmissions would likely be a popular one.

Further, how about a receiver with a built-in alpha-numeric keypad for program selection and a display? Imagine the possibilities! A subscriber could then choose the transmission desired (news headlines, stock quotes, etc.) by way of the keypad on his/her receiver. For example, suppose you want to receive the latest stock-market quotes, you could "punch-up" the symbol for that program and receive a plaintext display of the information. At what cost? you may ask. Well, all

it will cost you is the price of the pocket receiver/display unit, and a \$20 monthly service charge.

Meanwhile, the FM station will incur little additional expense, because the signal is broadcast through the FM transmitter via telephone line or microwave transmission, and is paid for by the service operator. A considerable income can be realized by the FM station, particularly in view of the fact that little is required of it in the way of additional equipment or technical services.

### SCA subcarriers

The sidebands of an FM station can extend to 75 kHz as shown in Fig. 1-a. Technically, any number of subcarriers can be placed within that sideband as long as no part of the subcarrier modulation or the main-channel sideband extends

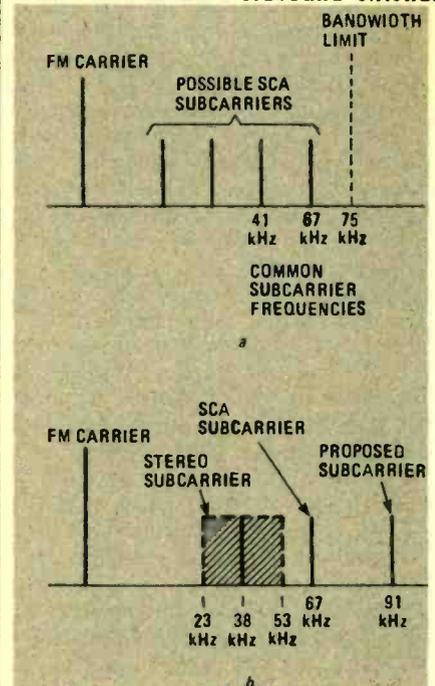


FIG. 1

beyond 75 kHz. One of the popular subcarrier frequencies is 67 kHz; because with 8 kHz SCA-sidebands, the total main-channel bandwidth would not exceed 75 kHz (67 kHz + 8 kHz = 75 kHz).

Back in the days when most FM transmissions were monophonic, the principle

# Give Blood. Give Life.

Company blood drives are a vital part of our nation's blood supply. So please have your firm start planning for a blood drive, today. And you can help save many lives tomorrow.

American Red Cross



We'll Help. Will You?

 A Public Service of This Magazine & The Advertising Council

limitation on the number of subcarriers was the 30% total-modulation ceiling on the amount of subcarrier modulation applied to the main channel. Since 8% is about the lowest degree of SCA modulation that can be used and still maintain decent reception, the practical limit was therefore three subcarriers, and preferably two. Also, to avoid interaction between the subcarriers due to poor receiver selectivity, the second subcarrier was placed at 41 kHz. But then, along came stereo.

As shown in Fig. 1-b, stereo has its own subcarrier frequency centered around 38 kHz, with its sidebands limited to  $\pm 15$  kHz. That means that the upper frequency-limit for the stereo signal is 53 kHz and the instantaneous frequency of the SCA is now limited to a range of between 53-75 kHz with no more than 10% modulation. That leaves only enough room for one SCA sideband, which must remain for "Talking Books for the Blind," if that's what the station was providing at the time of deregulation.

Since most FM stations transmit stereo signals, there obviously isn't much room available for a national paging service, or any of the other unusual personal communication for that matter. Because of that, it has been proposed that a subcarrier frequency of 91 kHz be permitted for such services as stock-quotes or personal messages, and 67 kHz be reserved for a national paging-service. **R-E**

## DESIGNER'S NOTEBOOK

*continued from page 14*

change state) is about 100 nanoseconds at 7 volts; which translates, theoretically speaking, into a maximum frequency of 10 MHz. The delay caused by the resistor will cut that amount by about half, and individual gates behave differently. Play with the circuit and see what you come up with. You will find, however, that the supply voltage, and not the individual gate, is the most important variable.

There are many other useful things you can do with only one gate. The XOR is a versatile gate and there are lots of other handy-dandy things you can do with it. But don't overlook the rest of the logic gates.

Let us know what unusual uses you've found for one gate and we'll pass them along in a future column. In fact, let's go one step farther and make an official contest out of it. The best and most imaginative circuit will win a one-year subscription to **Radio-Electronics**. What we will be looking for is originality and imagination. You can have as many passive components and diodes as you want, but the only silicon you may use is one gate. That means no transistors and no other IC's. **R-E**

SEE YOUR DEALER TODAY

FROM



HERE'S A TIP THAT'S PERFECT!  
AM/FM AUTO RADIO AND CB

**'Firestik' II**  
GOLDEN SERIES

BARE-HANDS TUNABLE  
"NO TOOLS NEEDED"  
HIGH PERFORMANCE ANTENNAS

ALSO ANTENNAS FOR  
CORDLESS TELEPHONES  
MONITOR SCANNERS

Dealer & Distributor Inquiries Invited  
SEND FOR FREE CATALOG


'Firestik' Antenna Company  
2614 East Adams/Phoenix, AZ 85034

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_  
Serving the CB and  
Communications Market Since 1962.

**5-YEAR REPLACEMENT WARRANTY**

CIRCLE 40 ON FREE INFORMATION CARD

## Vital protection for PC Boards

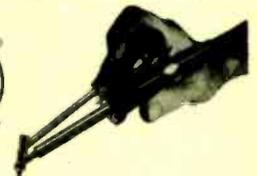

Be safe. Desolder PC components with Endeco irons. Get *proper* HEAT TO MELT and *strong* VACUUM ACTION TO LIFT solder and *cool* both PC board and component without damage.

These PC components replaced fast with Endeco desoldering or soldering tools.



Endeco professional features include safety light that denotes *high*, *low* and *off* on switch models. SS construction for long life, light weight and balance for easy use.

Contact your distributor for Endeco desoldering and soldering irons, kits and equipment—or write us today.

**Enterprise Development Corp.**

5127 East 65th Street  
Indianapolis, IN 46220  
Phone: (317) 251-1231

CIRCLE 42 ON FREE INFORMATION CARD

# STATE OF SOLID STATE

## Power supply over/under voltage monitor

ROBERT F. SCOTT, SEMICONDUCTOR EDITOR

MOST IC'S AND TRANSISTORS HAVE SPECIFIED "absolute maximum voltages" that, when exceeded, can destroy the device. Likewise, electronic circuits that use such devices have maximum supply-voltage limits. In addition, many solid-state devices also have voltage minimums that, when exceeded, can cause the device to malfunction.

Motorola recently announced the MC3425 and MC3525 monolithic power-supply supervisory circuits, which contain dedicated over- and under-voltage sensing channels. Figure 1 shows a block diagram of the MC3425/MC3525. Here we see that the over-voltage and under-voltage detector inputs feed two voltage comparators that are referenced to an internal 2.5-volt bandgap reference.

Separate delay pins (2 and 5) are provided for each channel to independently delay the drive and indicator out-

puts. That provides greater noise immunity and freedom from false triggering. The two delay pins are really the outputs of their respective input comparators and provide a constant-current source,  $I_{DLY(source)}$ . The delay pins are pulled low when their respective input comparator's non-inverting input signal level is brought lower than the inverting input. The delay is based on the time it takes for the 200- $\mu$ A current source to charge an external delay capacitor ( $C_{DLY}$ ) to the reference voltage.

The delay pins can sink more than 1.8 mA, so the delay capacitors can discharge much faster than they can charge from the 200- $\mu$ A source. When  $V_{CC}$  is 15 volts, the delay-time ranges linearly from .001 to 100 milliseconds as  $C_{DLY}$  is changed in decade values from .0001 to 10  $\mu$ F.

The delay pins are also directly coupled to the non-inverting inputs of the output

comparators, which are also referenced to 2.5 volts. The output time-delay ( $t_{DLY}$ ), in milliseconds, is determined by the value of the delay capacitor and is equal to  $2.5 \times C_{DLY}/200$  or  $12,500 C_{DLY}$ .

The over-voltage channel can source 300-mA with a turn-on slew rate of 2.0 A/microsecond; therefore, it is ideal for driving the gate of an SCR used to "crowbar" the power-supply line leading to a voltage-sensitive device. A current-limited emitter follower drives the over-voltage output at pin 1.

In the under-voltage channel, an open-collector NPN transistor can sink up to 30 mA to drive an LED, small relay, or shutdown circuitry. A fault must be sustained for a predetermined time before there is an output. The under-voltage input comparator has a feedback-activated 12.5  $\mu$ A current sink ( $I_H$ ) that is used when programming the input hysteresis voltage,  $V_H$ . That helps to assure positive shutdown during marginal undervoltage conditions. The source resistance ( $R_H$ ), feeding that input, determines the hysteresis voltage:  $V_H = I_H R_H = 12.5 \times 10^{-6} R_H$ .

There are several versions of the MC3525 and MC3525-U. The MC3525-U and -AU versions come in ceramic DIP packages and have a  $-55$  to  $+125^\circ\text{C}$  temperature range. The MC3425-PI and -API versions are packaged in plastic DIP's, while the MC3425-U and MC3425-AU are housed in ceramic packages. All the last four versions operate in the  $0$  to  $75^\circ\text{C}$  temperature range. The 2.5-volt band-gap reference regulator is rated at  $\pm 4\%$  accuracy in the basic devices. Accuracy for the "A" suffix devices is  $\pm 1\%$ . Each of the six versions operate on a supply voltages ranging between 4.5 and 40.

Figure 2 shows how the MC3525 is used for over-voltage protection and under-voltage indication with a programmable delay. The fuse is necessary when the power supply is not current-limited. That is because the crowbar SCR acts as a short circuit directly across the power-supply output. The fuse must be extremely fast acting with an  $I^2t$  rating less than that of the SCR, while having a continuous current rating that can handle normal supply

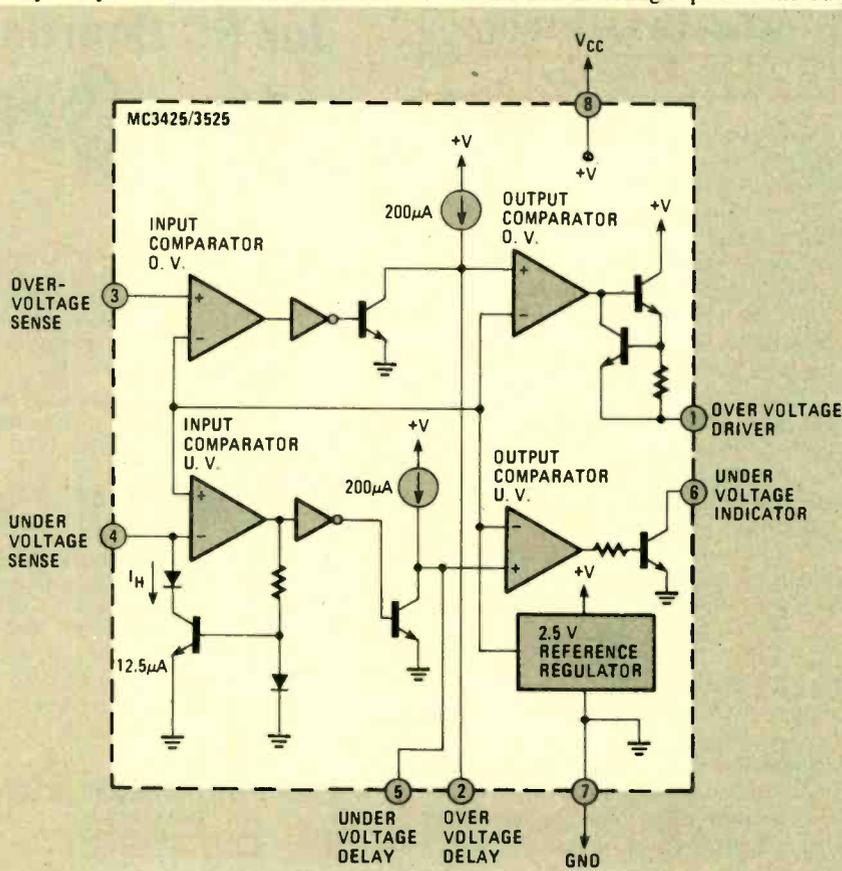


FIG. 1

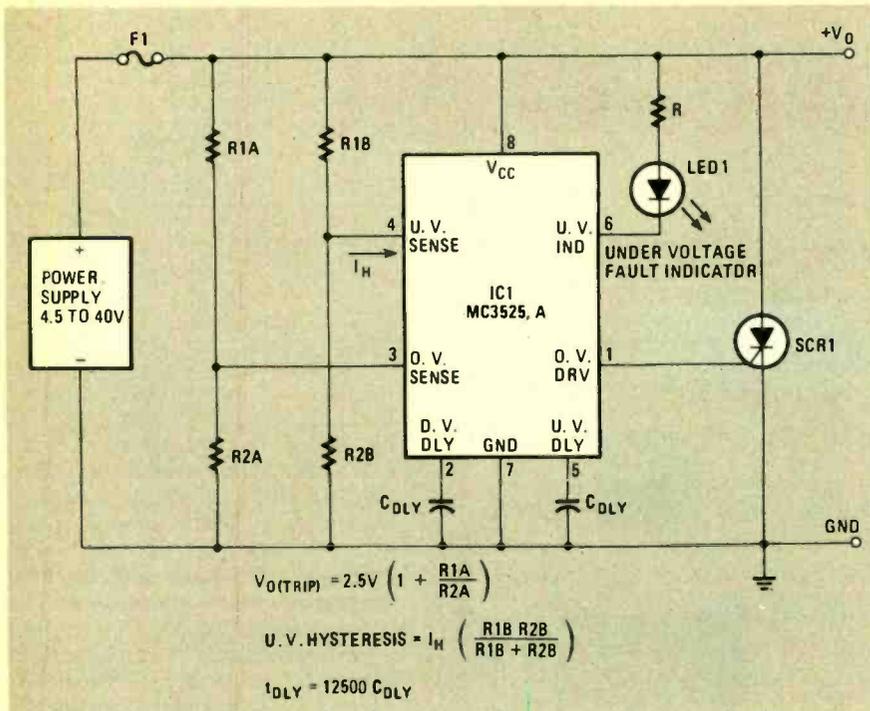


FIG. 2

currents. That type of fuse will be expensive—that is, if one is available. Therefore, we suggest that the protected supply include current limiting in its design. An

advance-information data sheet is available from **Motorola Semiconductor Products**, PO Box 20912, Phoenix, AZ 85036

### Bi-FET op-amp

Analog Devices has introduced a low-cost Bi-FET op-amp (the AD611KH) that offers premium-grade specifications for as low as \$1.00 in 100-piece lots. The AD611KH delivers a maximum offset voltage of 0.5 mV with an offset-voltage drift of 10  $\mu\text{V}/^\circ\text{C}$ . and a guaranteed maximum input bias current of 50 pA.

The lower cost AD611JH version guarantees the maximum offset voltage to be 2.0 mV, with an offset-voltage drift of 20  $\mu\text{V}/^\circ\text{C}$ , and an input bias current of 100 pA. The exceptionally low bias current makes the AD611 useful in current-to-voltage conversion applications.

Dynamic specifications for the AD611 include a minimum slew rate of 8 volts/microsecond, a unity-gain bandwidth of 2 MHz, and settling to 0.01% in 3 microseconds. Other specifications include a noise voltage of 2  $\mu\text{V}$  peak-to-peak at 0.1 to 10 Hz, and 0.0025% harmonic distortion. The K versions have a minimum open-loop gain of 94 dB and the J grade has a gain of 90 dB. The devices operate on supply voltages ranging from  $\pm 5$  to  $\pm 18$  with a maximum of 2.5 mA quiescent current. They are specified over the  $0^\circ\text{C}$  to  $+70^\circ\text{C}$  temperature range, and are housed in 8-pin TO-99 metal packages.—**Analog Devices**, 804 Woburn St., Wilmington, MA 01887. R-E

**DON'T FORGET**



USE YOUR READER SERVICE CARD

**Call or Write Us for Your Crystals**

- just one or hundreds -  
for Communications  
for Industrial Use  
for Your Technology



- You will get
- Cost Savings
  - Prompt Service
  - High Stability

Serving Crystal Users Since 1958

**JAN CRYSTALS**

P.O. Box 16017, Fort Myers,  
Florida 33906 All Phones  
(813) 936-2397



CIRCLE 30 ON FREE INFORMATION CARD

## Battery Powered Wire-Wrapping Tool



This revolutionary new battery powered tool will wrap insulated wire around .025" (0.63mm) square terminal posts without the need for pre-cutting and pre-stripping. Allows daisy chain, one-level wire-wrapping strings. Tool has built-in cut-off mechanism to end string at any time. Supplied complete with bit and 100ft. (30.4m) 30 AWG (0.25mm) wire.

- Fast and simple operation
- Daisy chain or point-to-point wiring
- Complete with bit and sleeve
- Automatic feed mechanism
- Cuts off wire at end of string
- Convenient wire refill spools

Uses two C size Nickel Cadmium batteries (not included).



**DAVLE TECH INC.**  
ELECTRONIC TOOLS & ACCESSORIES

78 2-05 Banta Place Fair Lawn NJ 07410-USA Tel: 201-796-1720

CIRCLE 54 ON FREE INFORMATION CARD

# SERVICE CLINIC

## Unusual repair problems

JACK DARR, SERVICE EDITOR

INTERMITTENT TV SETS HAVE LONG BEEN the bane of the TV service technicians—they've made many of us totally miserable. Like everyone else, I've come across my share of intermittent sets over the years. And at times, I've felt as though I was getting someone else's share as well! While there are some products that make troubleshooting such sets a little easier, they simply can't handle every situation that comes along. Even that can of freeze spray on your workbench (see Fig. 1) won't *always* help you find the problem. To illustrate, let's look at some real jewels that took up a great deal of my time.

### TV repair headaches!

The first case that we'll look at involves a Westinghouse table-model TV, that belonged to a little old lady who lived in a small house all by herself. Her complaint was that it "fell all to pieces" (no joke—that's what she said). Anyway, I hauled it off to the shop, set it up on the old workbench and turned it on. As I more than half expected, the picture came in perfectly. (Many sets will do that.) That's when I decided to let it "cook" for a couple hours; but I still saw no sign of trouble. Finally, I took the set back to the customer and turned it on. Again it played perfectly; so, I left it there and went away. The next day, a call came in and—wouldn't you know it—the problem was back again.

Well, I returned to the lady's apartment and hauled the set off to the shop once more. (Before I took the set away, I carefully checked her antenna and everything thing else, for that matter. But still nothing.) I checked and rechecked, and rechecked everything again—that went on for quite a while. Eventually, I took the set out of the cabinet and sat it on the bench close to me. (The PC board in this model was upright.) I sat there watching the screen in a mirror on the wall, while I "monkeyed around" in the back of the set. The picture was perfect as usual.

Finally, having run out of ideas, I drew a deep breath and heaved a huge sigh. That's when I noticed that the picture fell out of horizontal sync—very badly, I might add. I sat there, with my jaw hanging open, trying to figure out what was wrong. It was the first time that I had seen the set act up: But why? Finally it



FIG. 1

dawned on me; I had blown my damp breath on the PC board! By the time I had figured it out, the picture had straightened up. So I blew on it again and, sure enough, out it went.

A little while later, experiments and scope checks revealed that quite a bit of AC was showing up on the horizontal sync when I blew on it. Further examination showed that there was single point in the PC-board wiring that was being used as a tie point; it carried 110 volts AC. It was right smack in the middle of several others points that had the horizontal AFC on them. Needless to say, I soon removed the AC from that point (making a well taped "flying joint"). After that, you could sigh on it all you wanted and have no problem. But what caused it to act up to begin with, and why in her home and not at the shop?

Finally I found the answer: Her apartment was heated by a "wooly-backed" gas heater with asbestos padding behind the flame, but it had no vent. When an open flame burns in a small room, it can liberate an amazing amount of water vapor! That vapor had condensed on the cold PC board throwing the set "out of wack." Removing that AC connection from among all those AFC contacts cleared up the trouble.

Another dandy that that came my way (one that took me most of the summer to figure out) was another table model, made by DuMont this time. It too, would fall out of sync, but would later quit altogether. That is, it would quit at the customer's home—not my shop. To make an extremely long story a little shorter, I played the set on the end of my bench, where I could see it, for an estimated total of 200 hours and never saw any sign of trouble.

On several occasions I took the set back to the customer's home, where I'd sit watching it—what fun! (His home, naturally, was 5 miles out of town!) Anyhow, autumn rolled around and I was still trying to catch that thing acting up. The customer had said that it would cut out after about two hours—not so, at least not while I was there. Well, I sat there watching the screen for hours (while being supplied with cold beer by the customer!).

Anyway, one day it did jump a little, so I took the back off it and looked inside. As soon as I did, the customer yelled "Hey, there it goes!" At the time, I was looking at the neck of the picture tube and saw a tiny arc in there! After some tracing around, I finally located the real cause; the CRT screen-grid was intermittently arcing to the cathode. When it did, it shorted out the B+ voltage to the horizontal oscillator. All it took for a permanent repair was an isolation-type brightener, set to isolate, but not brighten. That was the result of all summer's checking of everything (except the picture tube, of course!). I filed that one away for future reference. But to this day, I haven't seen another problem like it.

All that just goes to show you that repair jobs are not always easy, even with all the tools at your disposal; but just hang in there and fortune will smile on you, too. Good luck and happy repairs! R-E

## SERVICE QUESTIONS

### LOST: VERTICAL DEFLECTION

*A Panasonic CT-914 has me climbing the walls. The vertical deflection is lost*

sometimes after a half hour, sometimes after a half day. I've changed a number of capacitors and resistors without success. Any ideas?—G.S., Red Bank, NJ

Of all the voltage measurements you gave me, the most significant is that of the collector of TR455, the bottom output transistor. It drops to 0 volts when deflection is lost. That tells me that one of the output transistors opens up. Spray them with component cooler.

With intermittents of this nature, the first suspect should be transistors, and unless you can pin it down with the spray technique, you should replace them, one by one, until you hit it. Slow, but certain.

### SHRINKING PICTURE

A Sears' hybrid, with tube outputs, has bad shrinking on the sides; the grid voltage on the horizontal output tube is too high, reading -128V where it should read -85V. I found that when I cut out the regulator diode the picture filled out nicely, but the brightness does not look right.—D.A., Babbitt, MN

High-voltage regulation in this set is achieved by tying the output-tube grid into the 6EL4 cathode, which itself is biased in part through the regulator diode, which goes to B-, and D120, the bias diode, which goes to B+. If you have not already tried a new 6EL4, do so at once. Then measure the voltages around that tube and see what turns up. An irregularity in the 6EL4 operating voltages must be upsetting the output tube bias.

### HORIZONTAL OUTPUT TRANSISTOR BLOWING

A Sears 528-41950316 blows the 3.25-amp fuse and the horizontal output transistor. Can you give me some assistance with some type of troubleshooting procedure?—S.K., Hamden, CT

Think of it as something loading down the output side of the transistor. If an ohmmeter check from collector to ground shows a low reading, it becomes a simple process to find the source of the low reading. If that is not the case, suspect something that breaks down when power is applied. A variable transformer is very useful for that: While starting at a low voltage and coming up to 70, 80, then 90 volts AC, keep your eyes, ears and nose open for an arc, a smell or anything else to catch your attention. If you don't get lucky, you'll have to lift the scan rectifiers from the circuit, or the high-voltage regulator, or anything else that you feel could be responsible. Keep the AC voltage as low as you can, while still getting results, to avoid blowing the transistor.

### REGULATOR PROBLEMS?

I have a Sanyo 91C90 that works on 85 volts AC, but will not work above 93 volts AC. I checked several parts around the

regulator, but don't know if the trouble is there or in the hold-down circuits. How would you approach this?—D.A., Babbitt, MN

As I interpret the diagram, the twin-transistor hold-down circuit monitors the 120-volt DC B+ voltage through Zener diode D403. If D403 is lifted, the hold-down would then be disabled, no longer killing the horizontal oscillator. Before lifting that, however, I would measure B+ while coming up with the variable transformer. If it goes beyond 120 volts, I would concentrate on the regulator system, whose function is to hold it at 120 volts. If the regulator is OK, check the components in the hold-down that might be causing premature tripping.

### TUNER PROBLEMS

The problem in an Admiral 9M50 seems to be in the tuning control. The picture and sound stay on for 3 or 4 seconds and then go out as if the tuner isn't on-station. I need help in repairing the ET200 or ET300 modules as they are very expensive to replace.—C.B., Bernie, MO

Your first job is to determine whether the loss of signal is in the ET boards, the tuner, or the IF section. A tuner subber would eliminate the IF as a possibility. Monitoring the voltages coming out of J306 would tell you whether the tuner is failing or the tuner supply-voltages, coming out of the synthesizer, are going awry. If the elimination process brings you there, you must rely on voltage measurements and perhaps the use of component cooler to pinpoint the transistor or IC at fault.

### FINDING THE RASTER

I wrote you about a Magnavox T991 that had no raster, and you suggested that instead of changing modules randomly, I should measure the kine-socket voltages to find out what was missing. I did, and traced my problem back to a bad demodulator IC. It is much easier when you know where to look for trouble rather than just using guesswork.—R.K.

### BRIGHT VERTICAL LINE

I have a bright vertical line approximately in the center of screen on this RCA CTC39X that I'm working on. I've changed tubes and the efficiency coil, and tried a new yoke with no luck.—T.C., Lime Ridge, WI

Something is wrong in the control-grid circuit of the output tube causing (what we used to call back in the old days) a drive line. Check C279, the coupling capacitor. For leakage, check all the components in the grid circuit, including the resistor that ties into the 6BK4 regulator. (I hope you tried a new regulator, just for the heck of it.) Also see that the peak-to-peak output of the 6FQ7 is OK. If not, check voltages around that tube. R-E

## New from B&K-PRECISION Autoranging and manual control in one DMM



### Model 2816 \$150

- Full manual or full autoranging on volts and ohms
- Single rotary selector switch control
- 0.25% DC accuracy
- 500 hour battery life
- Continuity test beeper
- Diode check
- Transient and overload protected
- High energy fuse

### Model 2807 \$115

Same features as Model 2816 with 0.5% DC accuracy

### Model 2806 \$75

Autoranging only on volts and ohms, manual amps. 0.7% DC accuracy

For more information contact your  
B&K-PRECISION  
distributor or write for specifications.

**BK PRECISION**

**DYNASCAN CORPORATION**

6460 West Cortland Street  
Chicago, Illinois 60635 • 312/889-9087  
International Sales: 6460 W. Cortland St., Chicago, IL 60635  
Canadian Sales: Atlas Electronics, Ontario  
South and Central American Sales:  
Empire Exporters, Plainville, NY 11803

CIRCLE 16 ON FREE INFORMATION CARD

# Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to \$600 a week and more!

Learn at home in spare time. No previous experience needed.

No costly School. No commuting to class. The Original Home-Study course that prepares you for the FCC Radiotelephone license exam in your spare time! An FCC Government license is your "ticket" to thousands of exciting jobs in Communications, Radio & TV, Mobile two-way, Microwave, Computers, Radar, Aerospace and more. You don't need a college degree to qualify, but you do need an FCC License. **No need to quit your job or go to school!** You learn how to pass the FCC License exam at home at your own pace with this easy-to-understand, proven course. It's easy, fast and low cost! **GUARANTEED PASS** You get your FCC License or money refunded. Write for free details. Soon you could be on your way to being one of the highest workers in the electronics field. **Send for FREE facts now. MAIL COUPON TODAY!**

## COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90  
P.O. Box 2223, San Francisco, CA 94126

Rush FREE facts on how I can get my FCC License in spare time. No obligation. No salesman will call.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

# ACTIVE RECEIVING ANTENNA

Gives excellent reception, 50 KHz to 30 MHz.

New MFJ-1024 Active Receiving Antenna mounts outdoors away from electrical noise for maximum signal.

Gives excellent reception of 50 KHz to 30 MHz signals. Equivalent to wire hundreds of feet long. Use any SWL, MW, BCB, VLF or Ham receiver.

High dynamic range RF amplifier. 54 in. whip. 50 foot coax. 20 dB attenuator prevents receiver overload. Switch between two receivers. Select auxiliary or active antenna. Gain control. "ON" LED. Remote unit, 3x2x4 in. Control, 6x2x5 in. 12 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

**\$129.95**  
+ \$4.00 shipping

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping). One year unconditional guarantee.

Order today. Call TOLL FREE 800-647-1800. Charge VISA, MC. Or mail check, money order. Write for free catalog. Over 100 products.

**CALL TOLL FREE 800-647-1800**

Call 601-323-5869 in Miss., outside continental USA, tech/order/repair info. TELEX 53-4590.

**MFJ ENTERPRISES, INCORPORATED**

Box 494, Mississippi State, MS 39762

CIRCLE 66 ON FREE INFORMATION CARD

## LINEAR IC'S

continued from page 68

prove the CMRR. Because of that feature, the LM-363-AD is useful for applications in difficult environments or unusual signal-acquisition situations.

Figure 8 shows a practical amplifier based on the LM-363-AD. Switch S1 is used to select the gains (10, 100, and 1000) and should be mounted on the front panel, in most cases, so that the operator can select the level desired.

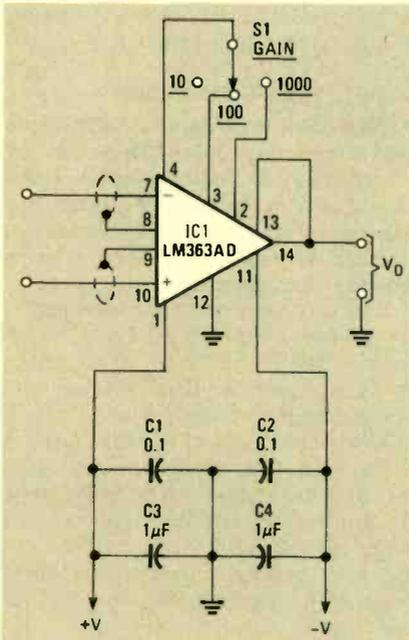


FIG. 8—BY ADDING A SWITCH, a variable-gain instrumentation amplifier can be formed.

If you want to make the circuit shown in Fig. 8 AC-coupled, it can be adapted as per Fig. 4.

It would be wise to configure the circuit such that the leads from gain-selector switch S1 and the IC package are as short as possible. Some lead length is permissible, but do not let it be excessive.

The capacitors used to bypass the -V and +V power-supply lines should also be mounted as close as possible to the body of the IC. The 0.1-μF units are the most critical in that respect because they take care of high frequencies. The reason why the 0.1-μF and 1-μF units are connected in parallel is that the 1-μF units are electrolytics and as such are not very effective at high frequencies.

Another ICIA device is shown in Fig. 9. That device is the Burr-Brown INA-101. The voltage gain of that device is set by resistor R<sub>G</sub>, which corresponds to R1 in Fig. 3. The gain equation is:

$$A_{VD} = \frac{40,000}{R_G} + 1 \quad (5)$$

If you compare Equation 5 with Equation

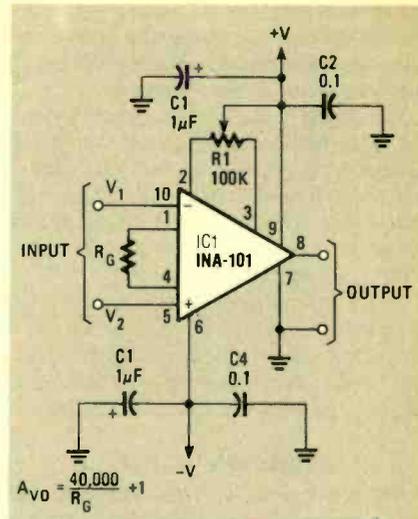


FIG. 9—THE GAIN OF IC1, an INA-101 instrumentation amplifier, is set by R<sub>G</sub>.

2, the gain equation for the IA in Fig. 3, you will note that they are similar. In terms of Fig. 3, if R4 = R5 = R6 = R7, and if R2 = R3 = 20 kilohms, then Equations 2 and 5 are identical.

As in most textbook equations, Equation 5 is not in its most useful form. In most practical situations, we know the gain we want to achieve. What we really need, then, is the value of R<sub>G</sub> that will produce that gain! Rewriting Equation 5 into a more practical form yields:

$$R_G = \frac{40,000}{A_{VD} - 1} \quad (6)$$

Equation 6 is somewhat more useful than Equation 5—at least outside of classrooms!

As an example, find the value of R<sub>G</sub> that will yield a gain of 1000. Substituting into Equation 6 gives us:  
R<sub>G</sub> = (40K/(1000 - 1)) = 40K/999 = 0.04 kilohms = 40 ohms.

It is permissible to make R<sub>G</sub> variable in order to provide gain control. You are cautioned, however, to place a series resistor in the circuit with the potentiometer to prevent the gain from going out of sight. As R<sub>G</sub> approaches zero, the gain climbs to infinite (not really, of course, but it will not take much at all to make the amplifier saturate). The value of the series resistor is one that satisfies Equation 6 at the highest gain you want to achieve.

## Next month

In Part 5 of this series we will discuss non-op-amp linear IC amplifiers, namely the current-difference amplifier (also called CDA or Norton amplifier) and the operational transconductance amplifier.

Looking ahead to the coming months, we will deal with such topics as logarithmic amplifiers, integrator and differentiator design, using isolation amplifiers, and the design of oscillators and multivibrators using op-amps. **R-E**

## STATIC ELECTRICITY

continued from page 48

equipment in the area could be considered to have a common potential and we would have achieved an isoelectric environment. However, it would not be practical to connect wires to each and every metal object (including your chair) in, say, a five-foot radius of your workbench or computer or other static-sensitive device. Some more rational approach must be followed.

We have already learned that friction is

harmful charges. Another approach would be to have the equipment operator wear a conductive wrist-strap that would provide that same controlled bleed-off of any charges before any sensitive equipment is damaged. (see Fig. 5)

### Ionization

Another method of controlling static build-up is ionization. Although generally impractical for use in the home or office, it is often used in industry. In ionization, the air is ionized so that a conductive path is formed between any charged objects and ground. That allows

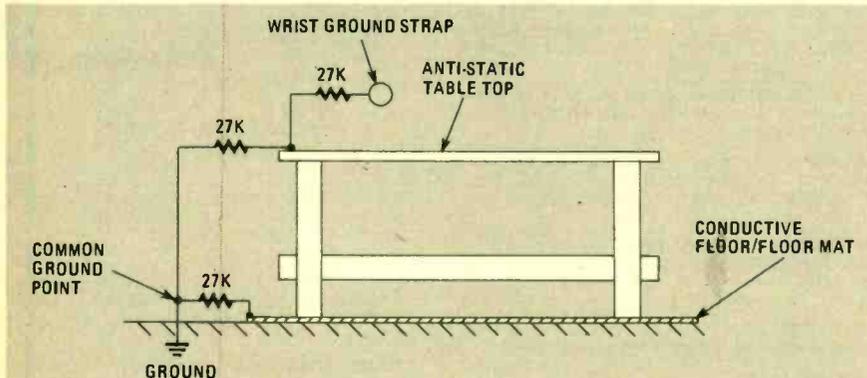


FIG. 5—MINIMIZING THE RISKS of a static discharge in a home workshop. Note the use of an anti-static table-top and a conductive floor or mat.

a chief cause of static-electric build-ups, so it should be apparent that if we eliminate potential sources of friction, especially between dissimilar objects, we would be well on our way to a practical solution to the static-electric problem. Carpets belong in plush homes, dens, cars, private planes, but not in computer rooms or workshops. If finances permit, a tile similar to the type used in hospitals with electrically conductive properties (per our static-electric definition) might be installed. Other approaches include floor covers of a conductive material for the under-desk and chair area. In lieu of those tiles or floor covers, and especially if the room must serve other purposes such as the living room of a home, a commercial "anti-static" carpet treatment may be effective.

Some installations have taken control of static to the level of restricting the type of clothing (material) that one can wear to avoid those fabrics that can produce harmful charges. Such steps are only necessary in ultra-sensitive areas, although personnel in sensitive hospital areas may be required to wear "scrub-clothes" with tiny metal fibers present in the fabric, and also special shoes.

In most situations, an anti-static table-top or discharge plate (a small square of metal) connected through a resistor of 27,000 ohms to ground, located near, say, a disk-storage area, would provide a convenient pathway to bleed-off potentially

the charges to dissipate safely.

It is obvious that control of static electricity can be carried to extremes (restrictive apparel, etc.) but it would be safe to assume that if you achieve at least 50% relative humidity, take normal care in removing potential sources of static build-ups (carpets, etc.), and further link the major metal surfaces in a reasonable radius to a common ground through appropriate resistors, you will have done much to control and perhaps even eliminate that source of damage to your equipment. R-E



"Then she said, 'Which is more important to you—the computer or me?'"

# EKI

**ELECTRONIC KITS INTERNATIONAL, INC.**  
(Formerly PPG Electronics)

**NEW!**

**AM RADIO  
6 TRANSISTOR  
#854/754**

A "Fun to Build" super sensitive 6-transistor AM radio. Exciting hands-on experience. Learn the how and why of a radio by building it yourself. All parts necessary are included, so tune in and discover the fun of building your own! Features: Low power consumption, low cost, easy step-by-step instructions with each kit, alignment procedure and troubleshooting instructions included. Circuit operations explained, wrist strap and cabinet included.



**NEW!**

### FROG PHONE W/CB & CASE

This kit has over 76 electronic parts including: speaker, microphone, microswitch, 12 button keypad, two circuit boards, transformer, two LED's eight transistors, one integrated circuit, twelve diodes, five electrolytic capacitors and sixteen resistors. Comes with step-by-step instruction and learning manual.

#815/715  
**NEW!**



- Large scale integration pulse generator IC's
- Matrix keyboards and decoders
- Dial tone generation
- Busy tone generation
- Ring pulse generation
- How to repair electronic telephones

### OVER 50 KITS AVAILABLE

#### KIT #

- |                                      |   |
|--------------------------------------|---|
| 801 Pocket Dice                      | 847 12-volt Color Organ                   |
| 802 Signal Inspector                 | 844 T.V. Jammor                           |
| 803 Space War Gun                    | 846 12-volt Strobo Disk                   |
| 804 Motor Detector                   | 850 Whistle Alarm                         |
| 805 Logic Probe                      | 857 Combination Lock/Alarm Control        |
| 806 Burglar Alarm                    | 858 Electronic Tammor                     |
| 808 Decision Maker                   | 859 Digital Rotator                       |
| 809 LED Flashlight Metronome         | 860 5-24 Volt Regulated Power Supply      |
| 811 Double Decision Maker            | 861 Big Sound Portable Organ              |
| 812 Simon Oscillator                 | 862 Full-wave Moser Speed Control         |
| 814 Robot Breaker                    | 866 Digital Saw Machine                   |
| 816 Mini-robot                       | 868 Digital Dice                          |
| 818 Fish Caller                      | 870 Morse Tester                          |
| 820 Strobe Lights                    | 876 5-amp Digital Clock                   |
| 821 Christmas Tree                   | 878 Digital Bird                          |
| 827 One Channel Color Organ          | 880 12-volt 7-amp Regulated Power Supply  |
| 824 Automatic Siren                  | 881 Musical Hars                          |
| 826 Fuzz Box                         | 884 Sound Activated Color Organ 1-channel |
| 828 9-Volt Power Supply              | 885 Audio Amp/Intercam                    |
| 830 Multi-purpose Power Supply       | 886 Librarian Terminator                  |
| 834 Color Organ 3-channel, 1-control | 890 Step-action Timing Tester             |
| 838 3-channel 6-control Color Organ  | 892 Telephone Hold Button                 |
| 840 Variable Strobo Light            | 894 Phase Gait/Sound Generator            |
|                                      | 898 Binary Clock                          |

**FREE**  
**CATALOG OF ALL KITS**

Available nationwide at your local electronics store.

(Or send \$1.00 shipping & handling to address below.)

**EKI ELECTRONIC KITS INTERNATIONAL, INC.**

791 RED ROCK ROAD  
ST. GEORGE, UTAH 84770

**Call TOLL FREE**  
**1-800-453-1708**

For store nearest you.

**Special Prices for Educators**

CIRCLE 58 ON FREE INFORMATION CARD

# MARKET CENTER

## FOR SALE

**CABLE-TV SECRETS**—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. Send \$8.95 to **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

**RESISTORS** 1/4W & 1/2W 5% 3 cents. 1% Metal-films, precision custom wirewounds, \$1.00 refundable to: **JR INDUSTRIES**, 5834-B Swancreek, Toledo, OH 43614.

**FREE** catalog featuring scanner accessories, carrier/subcarrier detectors, voice scramblers, unusual kits. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520.

**DESCRAMBLERS** for downconverters, high gain. Send \$1.00. **RB ELECTRONICS**, PO Box 643, Kalamazoo, MI 49005.

**THE Intelligence Library**— Restricted technical information & books on electronic surveillance, surveillance-device schematics, lock-picking, investigation, weapons, identification documents, covert sciences, etc. The best selection available. Free brochures. **MENTOR**, (Dept. Z), 135-53 No. Blvd., Flushing, NY 11354.

**CABLE TV** equipment, notch filters for "beeping" channels. Information: \$1.00. **GOLDCOAST**, PO Box 63/6025 RE, Margate, FL 33063.

**RF parts/Motorola transistors**. MRF454 \$16.00, MRF455 \$12.00. Catalog available. **RF PARTS CO.**, 1320-4 Grand, San Marcos, CA 92069. (619) 744-0720.

**UP** to \$500.00 per month. Sell computer software in your home. Write to: **COMPUTER SERVICES**, PO Box 7748, Tucson, AZ 85725.

**CABLE-TV** products. Jerrold, Hamlin, and Oak converters. Send \$3.00 for information. **ADDITIONAL OUTLET CORP.**, 111 E. Commercial Blvd., Ft. Lauderdale, FL 33334.

**RECONDITIONED test equipment**. \$1.00 for catalog. **JAMES WALTER TEST EQUIPMENT**, 2697 Nickel, San Pablo, CA 94806.

**POLICE** code unscramblers, other scanner accessories, telephone recording device, **DNE, Inc.**, Rt. 7, Box 257E, Hot Springs, AR 71901, (501) 623-6027.

**NEW!**... repair any TV... easy. Anyone can do it. Write, **RESEARCH**, RR No. 3, Box 601BR, Colville, WA 99114.

## MICROWAVE TV



Don't be misled  
Full parabolic dish  
Highest gain probe  
**Complete System \$69.95**  
**Satellite TV from \$99.00**

**Eprom & Gate**  
Cartridge Duplicator  
**EPRO 2000 - \$99.95**  
Blank Cartridges \$8.95

Visa & Mastercard accepted  
**S.R.S.** P. O. Box 331  
Isle of Palms, SC 29451  
(803) 886-6133

**PCB and TOKO** coils for TV project in February, 1984 article only \$17.00 **JIM RHODES**, 1025 Ransome Lane, Kingsport, TN 37660.

**OVER 1200** electronics parts, kits, and computer products. Lowest prices. Send \$1.00 (redeemable) for catalog. Stamp brings flyer. **DAYTAPRO ELECTRONICS**, 3029 N. Wilshire, Arlington Hts., IL 60004.

**CONNECTORS**—audio, co-axial, aviation, computer, industrial, and many other types. Send \$2.00 for complete price list and ordering information. Largest inventory in country. **CONNECTOR TECHNOLOGY INC.**, 5A Veronica Ave., Somerset, NJ 08873.

**DELUXE cable/UHF converters**. All systems. Zenith SSAVI-1 \$225.00, SB-3 \$89.95, N-12 \$79.95. \$2.00 catalog. **PRECISION VIDEO**, PO Box 1323, Elgin, IL 60121, (312) 683-4042.

**WHOLESALE** indoor antenna \$14.00. Master video control center \$30.00. (212) 897-0509. **D&WR**, 68-12 110 St., Flushing, NY 11375.

**CHANNEL 3**—60dB notch filter. 63.5MHz. \$32.00. **CROSLEY**, Dept. 763, Box 840, Champlain, NY 12919.

**LATEST** bug-detection equipment for home or office. Literature, \$1.00. **CLIFTON**, Box 220-X, Miami, FL 33168.

**RESISTOR** assortment. 2200pcs. 1/4W 5% C-film. 110 std. values, 20pcs. each individually packed. \$29.95 postpaid. Check/MO accepted. COD add \$2.00. **BENNETT CO.** 1271 Merchandise Mart, Chicago, IL 60654.

## Worlds Most Remarkable Radar Jammer!



Causes speed radar guns and devices to read out your choice of either a percentage of your true speed when in automatic mode (example: Your speed: 70 mph, auto mode set for 75%, speed displayed — 57 mph), or the speed that you dial in when in manual mode. Transmits only in the presence of speed radar, or by manual override. Operates on both X and K bands. **WARNING:** The device described in this literature is not legal for use against police radar, and is not FCC approved.

For complete literature and plan package, send \$14.95 to:  
**Phillips Instrument Design Co. Inc.**  
9560 S.W. Barbur Blvd., Suite #109 S  
Portland, Oregon 97219

**L.E.D. display** 10 L.E.D.'s light in sequence from output of any speaker. Unique visual display battery operated, handsome wood cabinet, \$39.99 + \$2.00 shipping. **L.S.E. ELECTRONICS**, Box 8402 Madison, WI 53708.

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$2.15 per word (minimum 15 words) to:

**Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003**

### ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$20.00.

{ } Plans/Kits ( ) Business Opportunities ( ) For Sale  
{ } Education/Instruction ( ) Wanted ( ) Satellite Television

Special Category: \$20.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PLEASE INCLUDE FOR OUR FILES YOUR PERMANENT ADDRESS AND PHONE NUMBER.

**CLASSIFIED COMMERCIAL RATE** for firms or individuals offering commercial products or services. \$2.15 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS**. 5% discount for 6 issues, 10% for 12 issues within one year, if prepaid.

**NON-COMMERCIAL RATE** (for individuals who want to buy or sell a personal item) \$1.50 per word prepaid...no minimum.

**ONLY FIRST WORD AND NAME** set in bold caps. Additional bold face (not available as all caps) at 20¢ per word. All copy subject to publisher's approval. **ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 20th of the third month preceding the date of the issue (i.e., August issue closes May 20th). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

**NOTEBOOK** of subscription TV descrambler technique (sinewave system). TV companies' descramblers technique. 38 pages full of things. NE 564 substitute, video improvement, Mitsumi, Amnec tuner modification, waveforms, troubleshooting and more. \$21.50. **ADVANCE ELECTRONICS**, PO Box 3298, Culver City, CA 90231.

**NEWEST cable-TV facts.** Manual includes: scrambling and descrambling theory, schematics of popular descramblers and converters, secret techniques and more. \$9.95 plus \$1.50 shipping. Free catalog. **ELECTRON**, Box 169, 17 N. State St., Room 1222, Chicago, IL 60602.

**BRADFORD parts 50% off—"JOE" TROY TV PARTS**, 76 Second Ave., Troy, NY 12180

**MICROWAVE antennas**, new burn-out proof type, hi-gain, \$75.00. Free info. **JCR SERVICE**, Box 20607, Denver, CO 80220

**TI-99/4A owners.** Get your free catalog of new, exciting, low cost software. **DYNA**, Box 690, Hicksville, NY 11801.

**WANTED:** Old RCA, Cunningham, Western Electric tubes, amplifier, speakers. McIntosh, Marantz, Tannoy, Altec, JBL. (713) 728-4343, **MAURY CORB**, 11122 Atwell, Houston, TX 77096.

## NEW! MULTI-CHANNEL MICROWAVE

Complete Antenna Systems from \$69<sup>95</sup>


Full 800 Mhz Range  
Tune 1.9-2.7 Ghz  
Includes all  
ITFS Channels

DEALERS WANTED

COD's and Credit Card  
Orders call TOLL FREE

1-800-247-1151

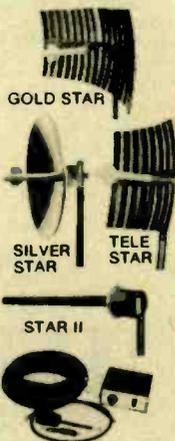**GALAXY ELECTRONICS**  
5644 N. 53rd Avenue  
Glendale, AZ 85301  
1-602-247-1151



**DESCRAMBLERS—sinewave, gated, Zenith.** Low as \$100.00. Free information. Dealers wanted—**STV**, Box 1226, Dublin, PA 18917. (215) 822-0558.

**TOP-quality** imported, domestic kits, surplus, discount electronics, computer components. Free catalog. **TEKTRASONIX**, 175 Fifth Ave., Suite 3194, N.Y., NY 10010.

**TI-99/4A—P-Box \$199.00—P-Box system \$500.00.** Extended BASIC \$93.05—cassette cables \$19.91. PHP-1250 \$299.00. Hard to get items, specify to: **CSC**, P.O. Box 1361, Bloomington, IL 61702-1361.

**BEST prices:** CB equipment, telephones, radar detectors, scanners. Free list. **CRS**, 1587 Central Ave., Yonkers, NY 10710.

**CABLE-television facts and secrets.** Now you can get the informative publication that CATV companies have been unsuccessfully trying to get banned for 15 years. Movie Channel, HBO, and Showtime converters, etc. Send \$8.75 to: **CABFAX**, P.O. Box 091196, Bexley, OH 43209.

**RESISTOR assortments 1/4W5%, 50pc.—\$2.00. 100pc.—\$3.00, 1000pc.—\$20.00, w/plastic container.** Add \$1.00 postage. **WADE ELECTRONIX**, P.O. Box 1473, Palmbay, FL 32905.

**EXACT** same PCB for descrambler in February article only \$17.00. **JIM RHODES**, 1025 Ransome Lane, Kingsport, TN 37660.

## AMAZING NEW PRODUCTS

**TONE Talking Memory Dialer**—This credit card size tone dialer can memorize and recall one hundred-32 digit phone numbers and is ideal for MCI and Sprint customers. A few features include special access entry code, alarm, stopwatch and calculator functions for only \$79.95. The **Listener**—represents the latest technology in the area of monitoring devices. Plugs into any modular phone jack. Its remote activation feature and ultra-sensitive microphone allows the user to telephone from anywhere in the world and listen into what is happening at another location for only \$99.95. **UHF Preamp Kit**—unit will drastically improve the picture quality of all UHF-TV stations and even find stations you never thought existed! Price \$29.95. Free shipping, MD residents add 5%. **HOWARD RESEARCH AND DESIGN**, P.O. Box 204, Ellicott City, MD 21043, (301) 465-8116.

## Govt. SURPLUS ELECTRONIC EQUIPMENT CATALOG

New ITEMS . . . New BARGAINS!  
**FREE UPON REQUEST!**

Send today for FREE Copy of  
**NEW CATALOG WS-841 • Address: Dept. RE**

**FAIR RADIO SALES**  
1016 E EUREKA • Box 1105 • LIMA, OHIO • 45802



# Active



1984 Mail Order Catalog

The One Stop Electronic Shop!

Call Toll FREE 1-800-343-0874

In the United States:

**Mail Orders**

P.O. Box 8000  
Westborough, Mass.  
01581  
(Mass) (617) 366-0500

**Boston**

133 Flanders Road  
Westborough, Mass.  
01581  
(617) 366-9684

**Seattle**

13107 Northup Way  
Bellevue, Wash.  
98004  
(206) 881-8191

In Canada:

**Montréal**

5651 Rue Ferrier  
Montréal, Québec  
H4P 1N1  
(514) 731-7441

**Ottawa**

1023 Merivale Road  
Ottawa, Ontario  
K1Z 6A6  
(613) 728-7900

**Toronto**

14 Carlton Street  
Toronto, Ontario  
M5B 1K5  
(416) 977-7692

**Calgary**

3220-5th Ave. N.E.  
Bay 2  
Calgary, Alberta  
T2A 5N1  
(403) 235-5300

**Downsview**

86 St. Regis Cr. N.  
Downsview, Ontario  
M3J 1Y8  
(416) 630-0400


**Vancouver**

3070 Kingsway  
Vancouver, B.C.  
V5R 5J7  
(604) 438-3321

Visit your nearest Active store, call, write or circle  
the Reader Service Card for your copy of Active's new catalog.

CIRCLE 77 ON FREE INFORMATION CARD

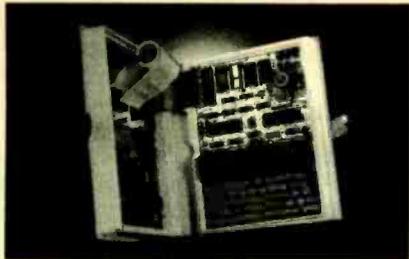Learn micro-processing with the new  
**MICRO-PROFESSOR 1P**



Students, engineers or technicians—  
upgrade your micro-processing skills  
with the new Micro-Professor 1P.

The MPF-1P features:

- extensive software support
- more built-in memory
- improved keyboard
- larger display

Three tutorial guides help cover all  
capabilities. The ideal training tool!  
MPF-1P will deliver you into the growing  
world of micro-processing. Invest now!

Plus—FREE GIFT Only \$179.95

☐ Check this box for FREE  
Z-80 Microprocessor  
Programming and  
Interfacing textbook when  
you order within 7 days.  
\$12.95 value.

**ETRONIX**

Dept. RE084,  
14803 N.E. 40th  
Redmond, WA 98052

For immediate action call TOLL FREE:

**1-800-426-1044**

Full money back guarantee.



CIRCLE 39 ON FREE INFORMATION CARD

**HIGH QUALITY up to 75dB GAIN**

**MICROWAVE  
TV SYSTEM**

Variable from 1.9 to 2.5 GHz



The latest advance  
in microwave  
technology with a  
**SNOW-FREE  
PICTURE.**

Two Models to choose from.

Both Models Include:

- 20" Parabolic Dish
- Pre-assembled Probe  
with Down Converter

- Power Supply and Coax Switch
- 60' of RG-59/U Coax with Connector
- Transformer for 75 to 300 Ohms
- All Mounting Hardware for Fast and  
Easy Installation

20" Fiberglass Dish  
Up to 55dB Gain  
Special **\$98<sup>95</sup>**

20" Aluminum Dish  
Up to 55dB Gain  
Low Priced **\$98<sup>95</sup>**

Add 10% for Foreign orders or U.S. Parcel Post

High Gain Yagi Antenna with Down Converter and  
Power Supply. Complete System. Ready to Use. **\$89<sup>95</sup>**

Send \$2.00 for Catalog. Refundable with first purchase.  
Available thru Mail and Phone Orders Only  
20% deposit for C.O.D. CA Res add 6 1/2% Tax.  
Send Cashiers Check or Money Order to:  
(Persons: Checks, allow 2-5 weeks to clear)

**PROFESSIONAL VIDEO, Inc.**  
4670 Hollywood Blvd., Hollywood, Calif. 90027

For C.O.D. Orders Call (213) 219-0227

CIRCLE 21 ON FREE INFORMATION CARD

**ELECTRONIC  
COMPONENTS**



**FREE CATALOG**

**MANUFACTURERS OF QUALITY  
ELECTRONIC COMPONENTS**

- BATTERY CLIPS & HOLDERS
- CABLE SETS • CONNECTORS • CAPACITORS
- DISPLAYS • LEDs • FUSES • JACKS & PLUGS
- KNOBS • LAMPS • POTENTIOMETERS
- RF COILS • RELAYS • RESISTORS
- SWITCHES • SEMICONDUCTORS • SPEAKERS
- TEST EQUIPMENT • TRANSFORMERS • TOOLS
- WIRE & CABLE

OVER 15,000 DIFFERENT ITEMS IN STOCK!

- Sales and Order Desk  
Open from 8:00 a.m. (PST)
- TERMS: C.O.D. Visa,  
MasterCharge  
(Open Accounts Available)
- Phone and Mail  
Orders Welcome
- Catalogs Mailed  
Outside USA  
Send \$2.00

**MOUSER ELECTRONICS**

11433 WOODSIDE AVE SANTEE CA 92071  
PHONE (619) 449-2222 TWX 910 331-1175

CIRCLE 94 ON FREE INFORMATION CARD

**BUSINESS OPPORTUNITIES**

VIDEO game repair business. Start your own. Infor-  
mation/parts list \$5.00. **BEST ELECTRONICS**,  
4440 Sheena, Phoenix, AZ 85032.

64K 6502/Z80 dual processor computer  
US\$420.00. Hundreds Apple-compatible softwares.  
Details US\$1.00. **RELIANT**, PO Box 33610,  
Sheungwan, Hongkong.

YOUR own radio station! AM, FM, cable, licensed,  
unlicensed, transmitter kits! Write: **BROADCAST-  
ING**, Box 130-F8, Paradise, CA 95969.

**BIG PROFITS  
ELECTRONIC  
ASSEMBLY BUSINESS**

Start home, spare time. Investment knowledge or  
experience unnecessary. **BIG DEMAND** assem-  
bling electronic devices. Sales handled by profes-  
sionals. Unusual business opportunity.

FREE: Complete Illustrated literature  
BARTA, RE-O Box 248  
Walnut Creek, Calif. 94597

BUY direct from Taiwan Hong Kong. Details \$1.00.  
Refundable. **TONY COLUCCI**, 56 Central Blvd.,  
Merrick, NY 11566.

DEALERS: Sell solderless breadboards IC DIP  
sockets. Very competitive prices. **LICATEK**, 26051  
Vermont Ave. 203C, Harbor City, CA 90710, (213)  
539-8997.

MONEY from your microcomputer. Send LSASE for  
details. **FRONT ROOM**, RE1, Box 1541, Clifton, NJ  
07013.

**SATELLITE TELEVISION**

UNSCRAMBLE secret satellite channels watch all  
the good stuff. Plans \$19.95—kits \$169.95—com-  
plete units \$395.00—Details and order forms \$3.00.  
**SCRAMCO**, 8688 Royal Dr., Noblesville, IN 46060.

SATELLITE-TV recelver breakthrough! Build  
your own system and save! Instruction manu-  
als, schematics, circuit boards! Send stamped  
envelope: **XANDI**, Box 25647, Dept. 21B, Tempe,  
AZ 85282.

**DESCRAMBLERS**

**AMERICAN—CANADIAN**

New Satellite Descramblers

**C-1000 / ZENITH TYPE**

Descrambles "over the air" and  
"cable" sync suppressed active  
video inversion signals

Ready to go C-1000 ..... **379.95**  
Complete Kit C-1000K ..... **274.95**  
Printed Circuit & Manual ..... **24.95**

**C-100 / JERROLD TYPE**

Cable Descrambler for in-band gated  
suppressed systems

Ready to go C-100 ..... **119.95**  
Complete Kit C-100K ..... **54.95**

SEND \$2 FOR COMPLETE INFORMATIVE CATALOG TO  
DETERMINE WHAT TYPE YOU NEED.

**J & D ENGINEERING**  
P.O. Box 6099

Falmouth, Maine 04105

Dealers Wanted  
Special Quantity Pricing  
COD'S—OK

Buy 1 kit  
Get 2nd kit  
at 1/2 price

All J & D products are engineered, not copied, all are guaranteed  
90 days & we stand behind our products where others fail to

ENJOY Satellite Television. Save money with  
easy, guaranteed, do-it-yourself antenna plans/kits.  
Electronics knowledge not necessary. Send \$1.00  
for catalog. **GFI-22**, Box 9108, Missoula, MT 59807.

SATELLITE-TV!—Lowest prices on complete  
systems! All popular brands available. Free in-  
formation. Complete installation instructions  
and programming guide \$2.00. Dealers want-  
ed—**ANTENNA INSTALLATION SERVICE**, P.O.  
Box 1226, Dublin, PA 18917, (215) 822-0558.

SATELLITE systems, build, save. For details send  
stamps, **MATCO ELECTRONICS**, Box 316RS, Ca-  
dillac, MI 49601.

SATELLITE-TV—Complete systems or compo-  
nents to upgrade your present one. Send \$1.00 for  
price list. **SAT-TELE**, P.O. Box 46057, Cleveland,  
OH 44146.

**SATELLITE TV VIEWERS**

Get the most complete weekly listings.  
Send \$1 for sample copy.

**Satellite TV Week**

P.O. Box 308E, Fortuna, California 95540  
**800-358-9977 (U.S.) • 800-356-8787 (Calif.)**  
**707-783-2476 (all others)**

**PLANS & KITS**

PRINTED-circuit boards. Quick prototypes, pro-  
duction, design, reflow solder send print or  
description for quote to **KIT CIRCUITS**, Box 235,  
Clawson, MI 48017.

HI-FI speaker kits, auto speaker systems and raw  
drivers from the world's finest manufacturers. For  
beginners and experts. Free literature. **A&S  
SPEAKERS**, Box 7462R, Denver, CO 80207 (303)  
399-8609.

NEW!... repair any TV... easy. Anyone can do it.  
Write **RESEARCH**, RR No.3, Box 601BR, Colville,  
WA 99114.

REPAIRS of all converters and cable boxes with  
prompt service. Deluxe sinewave kits \$95.00. 90%  
complete also available (quantity discounts) UHF  
converters of all types available. Send SASE (54  
cents postage) for information. I-(312) 637-4408.  
**HIGGINS ELECTRONICS**, 6014 W. Nelson, Chi-  
cago, IL 60641.

CATALOG: Hobby, CB, broadcasting! Linears,  
transmitters, bugs, scramblers, downconverters,  
antennas, modifications, more! **PANAXIS**, Box 130-  
F8, Paradise, CA 95969.

QUALITY light chaser/color organ kits. Refundable  
\$1.00 for flyer. **DESIGN SPECIALTY**, Box 1995,  
Huntington Beach, CA 92647.

HUNDRED exciting electronics kits with real life  
applications catalog, \$2.00. **MOSTKIT**, PO Box  
-4939, Berkeley, CA 94704



# FORMULA INTERNATIONAL INC.

12603 Crenshaw Blvd., Dept. B, Hawthorne, CA 90250

For information (213) 973-1921 • Orders Only (outside Calif.) (800) 672-8758



## MARK IV — 15 STEP LED POWER LEVEL INDICATOR KIT

This new stereo indicator kit consists of 36 4-color LED's (15 per channel) to indicate the sound level output of your amplifier from -36dB to +3dB. Comes with a well designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6-12VDC with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W. Kit includes 70 pcs driver transistors, 38 pcs matched 4-color LED's, all electronic components, PC Board and front panel. **MARK IV KIT \$31.50**



No FCC License Required  
**OUR PRICE \$49.50**  
Additional Microphone (Transmitter) Available at \$28.00 ea.  
**MURA WMS-49**

## CRYSTAL CONTROLLED WIRELESS MICROPHONE SYSTEM

Transmitter: FET mic for flat 30Hz-18KHz response. X'tal controlled 49MHz AM Band for drift-free performance. 100mW output (range approx. 1/4 mile) for reliable long range transmission. Powered by a 9V radio battery. Receiver: X'tal controlled locks on 49MHz transmitter signal. On panel VU meter, monitors the signal strength from the microphone. Standard phone jack outlet connection to a P.A. or other phone input. 9V battery included. This professional set is ideal for on stage, in field, church, in house or outdoor use.



## pinecom™ DP-64




- Dual Processor (6502 and Z80A)
- Detached Keyboard
- 64K RAM Expandable to 192K
- 25 Function Key Keyboard
- Auto Repeat Keys w/Upper/lower Case
- 2 Slim Disk Drives (optional)
- 100% Apple II Compatible
- 40/80 Column Display (optional)
- Runs Both Apple Soft and CP/M Software

Model DP-64

Fully Assembled ...

# \$650<sup>00</sup>
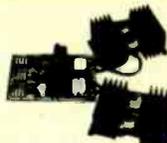
## TA-1000 KIT \$51.95 Power Transformer \$24.00 ea. 100W CLASS A POWER AMP KIT



Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low TIM stereo pre-amp.

Specifications - Output power 100W RMS into 8Ω. 125W RMS into 4Ω. Frequency response 10Hz-100KHz. THD less than 0.01%. S/N ratio better than 80dB. Input sensitivity 1V max. Power supply ±40V at 5A.

## LOW TIM DC STEREO PRE-AMP KIT TA-1020

Incorporates brand-new DC design that gives a frequency response from 0-100KHz ±0.5dB. Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuations!

Specifications: • THD TIM less than .005% • Frequency response DC to 100KHz ±0.5dB • RIAA deviation ±0.2dB • S/N ratio better than 70dB • Sensitivity: Phone 2mV 47KΩ, Aux 100mV 100KΩ • Output level 1.3V @ 50Hz, Treble ±10dB @ 15Hz • Bass ±10dB @ 50Hz, Treble ±10dB @ 15Hz • Power supply ±24VDC @ 0.5A. Kit comes with regulated power supply. All you need is a 48VCT transformer @ 0.5A.

Only \$44.50  
Transformer  
\$4.50 ea.



## pinecom™

# Pioneer of Low Cost Apple\* Compatible Computer



## Now with New Improved Keyboard and 64K RAM

No Copyright Problems!

Compare These Features with Our Competitors:

- Powerful Utility Program (100% Apple Compatible)
- 68-Key Upper & Lower Case Keyboard with Numeric Keypad
- 25 Pre-programmed Function Keys
- 2 Speed Auto Repeat Function
- 64K User Memory—expandable to 192K
- 5A Switching Power Supply (110/220VAC)
- All ICs Are Socketed for Easy Service
- Nation-wide Dealer Network for Convenient Technical Support

And best of all, the price  
Assembled and Tested is just. ....

# \$499<sup>00</sup>



★ SPECIAL ★  
Excellent Price!  
Model 001-0034  
\$29.50 per Kit  
Transformer  
\$10.50 ea.

## TA-322 30 WATTS TOTAL 15W + 15W STEREO AMP KIT

This is a solid state all transistor circuitry with on board stereo pre-amp for most microphone or phone input. Power output employs a heavy duty Power Hybrid IC. Four built on board controls for volume, balance, treble and bass. Power supply requires 48VCT 2.5A transformer. THD of less than 0.1% between 100Hz-10KHz at full power (15 Watts + 15 Watts loaded into 8Ω).

## MAGNETIC HEAD EQUALIZER

• Standard RIAA curve for all kinds of magnetic heads • 3 stages crossover circuit for best results • Output voltage guaranteed to be stable without any oscillation • Power Supply 24 V.D.C.



MODEL: MA-142  
Part #370-370 ..... \$6.95 ea.

## 60W + 60W O.T.L. AMP

Stereo pre-amp + tone control + power amp. All in one unit, fully assembled! Compact in size: 7"x4"x2 1/2". Can be fitted into most cabinets. Power transistors using 2SC1667 X 4 to give a max output of 60W + 60W (8Ω).

• Frequency response: 20Hz-85KHz (-1dB) • Total harmonic distortion: 0.02% (1KHz) • Signal/Noise Ratio: 88 dB (open loop) • Tone control: 100 Hz ± 16 dB 10 KHz ± 14dB • Dynamic range: 60 dB • Power Supply 48V-70V 5 Amp. • Filter Capacitor: 4700µF 75V or better.

MODEL:  
SA-4520



Part #370-0350 ..... \$39.95 ea.  
1 Transformer Part #670-0230 ... \$22.50 ea.  
2 Filter Capacitor 4700µF 70V \$6.50 ea.

## STEREO MIC. AND ECHO MIXER FOR STEREO AMPLIFIER SYSTEM

The circuitry employs all integrated circuits, BBD type echo circuit, echo time can be adjusted (max. 30 Msec.) Also with a microphone preamp on the board. Fully assembled.



MODEL: MX205  
Part #370-0360 ..... \$29.95 ea.

## PROFESSIONAL REGULATED VARIABLE DC POWER SUPPLY KIT

All solid state circuitry with high efficiency power transistor 2SD388 and IC voltage regulator MC1733. Output voltage can be adjusted from 0-30V at 1A current limited or 0-15V at 2A current limited. Internal resistance is less than 0.005Ω, ripple and noise less than 1mV, dual on panel meters for voltage and current reading, also with on board LED and audible over load indicator. Kit comes with pre-drilled PC Board, instructions, all necessary electronic components, transformer and a professional looking metal cabinet. The best project for school and the most useful instrument for repairmen. Build one today!



Model TR88A  
0-15VDC @ 2A

Model TR88B  
0-30VDC @ 1A

\$59.50 per Kit

## LOW T.I.M. TRANSISTORS 100W + 100W

• Employs Hitachi low noise I.C. for pre-amp • Max output 16 V P-P (non distortion) • With hi-low filter, and tone defeat circuit • Rear power amp with short circuit protection • Giant heat sink for maximum results • Tone controls ± 14dB • All components (except pots for volume, and tone controls) are pre-assembled, the quality is guaranteed. • Power supply DC ± 35V-50V



MODEL: SA802C  
Part #370-0340 ..... \$85.00  
POWER TRANSFORMER  
(68V-80V CT 6 AMP)  
Part #670-0220 ..... \$24.50

SEND ONE DOLLAR  
FOR OUR DETAIL CATALOG

Shipping & Handling Charges	
Under \$50.00 Purchase	Over \$50.00 Purchase
10%	5%
15%	10%
25%	20%

Minimum Order \$10.00/Calif. Residents add 6.5% Sales Tax. Phone Orders Accepted on VISA or MC ONLY. NO C.O.D.'s. Prices subject to change without notice.



**STORE HOURS**  
MON-FRI-10-7  
SAT-10-6

Inside California  
Outside Calif. (Incl. Mexico & Canada)  
Overseas

\*Apple and Apple II are the trademark of APPLE COMPUTERS, INC.

CIRCLE 76 ON FREE INFORMATION CARD

www.americanradiohistory.com

# FREE KIT Catalog

FUNCTION GENERATOR KIT \$59.95 contains TEST & EXPERIMENTER'S EQUIP  
Auto-Ranging Cap-meter kit \$79.95  
Phone 209-772-2076  
Write or Phone for FREE CATALOG  
**DAGE** SCIENTIFIC INSTRUMENTS  
BOX 144 VALLEY SPRINGS CA 95252

**FREE information.** Increase the vertical bandwidth of your 5Mhz oscilloscope to 200Mhz! **WHITE KNIGHT IND.** 3928 Iowa, No.102, San Diego, CA 92104.

**DIGITAL** clock kit plays 1-of-12 different melodies on the quarter hour. Displays time, date, and other features. Send \$2.00 for complete assembly plans and pricing to **KERBER KLOCK KO.**, 36117 Hillcrest, Eastlake, OH 44094.

**PCB and TOKO** colls for TV project in February 1984 article only \$17.00. **JIM RHODES**, 1025 Ransome Lane, Kingsport, TN 37660.

**CHLORIME** generator plans, pool owners save 90% easy to make, \$3.00. **MRH**, 1005 South Fromtace, Plant City, FL 33566.

**CONVERT** pocket AM radios to receive shortwave. Plans, kits. For more information send SASE to **HOWARD BAILEY**, 115 Manor Place, Santa Cruz, CA 95060.


# CB MODIFICATIONS

Increase channels, range, privacy! We specialize in frequency expanders, speech processors, FM converters, PLL & slider tricks, how-to books, plans, kits. Expert mail-in repairs & conversions. 16-page catalog \$2.

CBC INTERNATIONAL, P.O. BOX 31500RE, PHOENIX, AZ 85046 (602) 996-8700
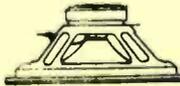
## CB EQUIPMENT

**PALOMAR/Pride** electronics—exclusive repair facility. Service—update—improvements on these and similar equipment. **PALOMAR-PRIDE REPAIR**, 1320-4 Grand, San Marcos, CA 92069 (619) 744-0720.



WRITE FOR **McGEE'S**  
**SPEAKER & ELECTRONICS CATALOG**  
1001 BARGAINS IN SPEAKERS

Tel.: 1 (816) 842 5092  
1901 MCGEE STREET KANSAS CITY, MO. 64108

## WANTED

**INVENTIONS**, ideas, new products wanted for presentation to industry and exhibition at national technology exposition. Call 1-800-528-6050. Arizona 1-800-352-0458. X831.

**HALLCRAFTERS** S-40, S-52, S-77. Any condition. Paying \$20.00-\$40.00 each. **FALA ELECTRONICS**, Box 04134-2, Milwaukee, WI 53204.

**RF MODULATORS**  
for the video industry

Satellite modulators from channels 1 thru UHF!  
Kits & assembled models for all intermediate... including our new Apple-verter designed to mount inside computer. Also an extensive line of modulators, cameras and kits. FREE CATALOG

PHONE (402) 857-9771  
**ATV Research**  
13-RE BROADWAY  
DAKOTA CITY, NE 68021

# TECHNICIANS, Get serious about your profession;



Now you can order the "Study Guide for the Associate—Level CET Test" from the International Society of Certified Electronics Technicians. It includes material covering the most often missed questions on the Associate CET Exam. 8 1/2" x 11", paperback, 80 pages.

## GET CERTIFIED!

Send check to **ISCET**, 2708 W. Berry St., Ft. Worth, TX 76109.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

\_\_\_\_\_ copies @ \$5.00 ea.,  
Send material about **ISCET** and becoming certified.

REPLACEMENT FOR

## ECG®/TRIPLERS/MULTIPLIERS

(MIN. 50 PC. PER TYPE)

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
500A	7.65	530	10.65	537	11.73
521	10.98	531	10.45	538	9.84
522	9.50	532	12.40	539	9.84
523	7.75	533	9.90	549	14.55
526A	7.75	534	10.48	550	10.05
528	9.40	535	11.48	556	11.90
529	8.90	536A	13.85	557	11.75
				564	11.55

## REPLACEMENT FOR ECG® TYPES

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
85	FOUR for .99	125	SEVEN for .99
102A	THREE for .99	159AP	FOUR for .99
123A	FIVE for .99	177	EIGHT for .99
123AP	SIX for .99	199	FIVE for .99

## SUPER SPECIAL (MIN. 5 PC. EACH)

TYPE NO.	YOUR COST	TYPE NO.	YOUR COST	TYPE NO.	YOUR COST
124	.85	185	2.25	375	.90
128	.45	171	.65	506	.55
129	.45	184	.45	500A	8.95
130	.80	185	.45	523	9.95
152	.40	238	2.25	526A	10.20
153	.40	276	6.95	529	13.75
154	.60	291	.95	712	1.25

## JAPANESE TYPES (MIN. 5 PC. EACH)

2SC867A	2.75	HA1366W	1.85	STK0029	3.80
2SC1114	3.25	HA1377A	2.90	STK0080	9.99
2SC1308K	1.95	LA4102	1.25	TA7205AP	1.50
AN214Q	1.45	M51515BL	2.95	TA7208P	1.85
AN239A	4.60	STK433	3.95	TA7222AP	1.95
BH532	1.80	STK435	3.95	UPC1181H	1.25
GH3F	.89	STK437	6.25	UPC1182H	1.25
HA1342A	2.30	STK439	6.50	UPC1185H	2.99

COD ORDERS WELCOME (\$25 MIN. ORDER)

For Complete Component Catalog Call or Write

## DIGITRON ELECTRONIC

110 HILLSIDE AVENUE, SPRINGFIELD, N.J. 07081

TOLL FREE: 800-526-4928

In N.J.: 201-379-9016

\*ECG IS A TRADE MARK OF PHILIPS ECG.  
DIGITRON ELECTRONIC IS NOT ASSOCIATED IN ANY WAY WITH PHILIPS ECG.

CIRCLE 11 ON FREE INFORMATION CARD

## MICROWAVE RECEIVER 1.9-2.5 GHz



- 50 dB gain
- 50 mile line of sight
- Complete power supply, cable antenna and probe.

RK-1 Assembled ... \$114.95  
RK-1 Kit Form ... \$ 84.95

## MICROWAVE RECEIVER 1.9-2.5 GHz

- Rod style
- 30 mile reception
- Complete system
- 32 element antenna
- Kit or assembled

RK-3 Assembled ... \$79.95  
RK-3 Kit ... \$64.95

## MICROWAVE PREAMP KIT!!!

- Use with RK-3 Kit. Add's 20-25 dB gain.
- Increase reception
  - Low noise
  - Use with all existing stop sign board receivers


MP-4 Kit ... \$38.95

**AD-1 PULSEWAVE**  
Pulsewave Kit  
and Enclosure ... \$119.95  
AD-1 Board Only ... \$19.95
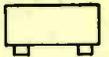
## UHF TV PREAMP

A very popular UHF Preamp Kit. Astounding signal amplification.

- Features:
- 27 dB gain
  - 2 dB noise factor
  - 75 ohm input/output
  - Enclosure & power supply included



CD-1 Preamp Kit ... \$34.95

## DIGITAL METER MIC-3300A

- Assembled • 3 1/2 digits • DC .5% accuracy • DCA up to 10 amps • Ohm up to 20 M ohm • hFE measurement • Floating decimal point • Leads • battery included

A high quality Digital Meter at an affordable price, the MIC 3300A is a high quality meter for all hobbyists and maintenance work.

MIC-3300A ... \$59.95  
Carrying Case ... \$ 9.95

## LOGIC PROBE



- Troubleshoot TTL-CMOS
- 4 LED states
- High input impedance
- Flexible clip on power leads
- Assembled & tested

L101A Logic Probe . \$34.95

TO ORDER CALL:  
1-617-641-0778

**GAMMA ELECTRONICS**  
455 Massachusetts Ave.  
Arlington, MA 02174



CIRCLE 60 ON FREE INFORMATION CARD

# Do Kay

COMPUTER  
PRODUCTS,  
Inc.

ORDER TOLL FREE

(800)  
538-8800

(CALIFORNIA RESIDENTS)

(800)  
848-8008



**TERMS:** Minimum order \$10.00. For shipping and handling, include \$2.50 for UPS ground or \$3.50 for UPS Blue (air). For each additional air pound, add \$1 for UPS Blue shipping and handling. California residents must include 6% sales tax; Bay area and LA residents include 6 1/2% sales tax. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturers. All merchandise subject to prior sale.

**HOURS:** Mon. - Fri. 7:30 to 5:00  
Saturdays 10:00 to 3:00

VISIT OUR RETAIL STORE

2100 De La Cruz Blvd.  
Santa Clara, CA 95050  
(408) 988-0697

ALL MERCHANDISE IS  
100% GUARANTEED

# Do Kay

## STATIC RAMS

2101	256 x 4 (450ns)	1.90
5101	256 x 4 (450ns) (cmos)	3.90
2102-1	1024 x 1 (450ns)	.88
2102L-4	1024 x 1 (450ns) (LP)	.88
2102L-2	1024 x 1 (250ns) (LP)	1.45
2111	256 x 4 (450ns)	2.45
2112	256 x 4 (450ns)	2.95
2114	1024 x 4 (450ns)	0/7.95
2114-25	1024 x 4 (250ns)	0/8.95
2114L-4	1024 x 4 (450ns) (LP)	0/8.95
2114L-3	1024 x 4 (300ns) (LP)	0/10.95
2114L-2	1024 x 4 (200ns) (LP)	0/11.95
2147	4096 x 1 (55ns)	4.90
TMS4044-4	4096 x 1 (450ns)	3.45
TMS4044-3	4096 x 1 (300ns)	3.95
TMS4044-2	4096 x 1 (200ns)	4.45
MX4118	1024 x 8 (250ns)	9.90
TMM2015-200	2048 x 8 (200ns)	4.10
TMM2015-150	2048 x 8 (150ns)	4.90
TMM2015-100	2048 x 8 (100ns)	6.10
HM6116-4	2048 x 8 (200ns) (cmos)	4.70
HM6116-3	2048 x 8 (150ns) (cmos)	4.90
HM6116-2	2048 x 8 (120ns) (cmos)	8.90
HM6116LP-4	2048 x 8 (200ns) (cmos)(LP)	5.90
HM6116LP-3	2048 x 8 (150ns) (cmos)(LP)	6.90
HM6116LP-2	2048 x 8 (120ns) (cmos)(LP)	8.95
Z-6132	4096 x 8 (300ns) (Quate)	33.95

LP = Low Power    Qdate = Quasi-Static

## DYNAMIC RAMS

TMS4027	4096 x 1 (250ns)	1.95
UPD411	4096 x 1 (300ns)	2.95
HM5280	4096 x 1 (300ns)	2.95
MX4108	8192 x 1 (200ns)	1.90
HM5298	8192 x 1 (250ns)	1.80
4118-250	16384 x 1 (250ns)	.48
4118-200	16384 x 1 (200ns)	.89
4118-150	16384 x 1 (150ns)	1.20
2118	16384 x 1 (150ns) (5v)	4.90
4184-250	65536 x 1 (250ns)	4.45
4184-200	65536 x 1 (200ns) (5v)	5.45
4184-150	65536 x 1 (150ns) (5v)	6.45

5V = Single 5 Volt Supply

## EPROMS

1702	256 x 8 (1us)	4.45
2708	1024 x 8 (450ns)	2.48
2758	1024 x 8 (450ns)	2.48
2758	1024 x 8 (450ns) (5v)	5.90
2716	2048 x 8 (450ns) (5v)	2.85
2716-1	2048 x 8 (350ns) (5v)	5.90
TMS2518	2048 x 8 (450ns) (5v)	5.45
TMS2716	2048 x 8 (450ns)	7.90
TMS2532	4096 x 8 (450ns) (5v)	5.90
2732	4096 x 8 (450ns) (5v)	3.95
2732-250	4096 x 8 (250ns) (5v)	8.90
2732-200	4096 x 8 (200ns) (5v)	10.95
2784	8192 x 8 (450ns) (5v)	5.95
2784-250	8192 x 8 (250ns) (5v)	13.95
2784-200	8192 x 8 (200ns) (5v)	23.95
TMS2564	8192 x 8 (450ns) (5v)	18.85
MC68764	8192 x 8 (450ns) (5v) (24 pin)	38.95
27128	16384 x 8 (5v)	19.95

5v = Single 5 Volt Supply

## 74LS00

74LS00	.23	74LS92	.54
74LS01	.24	74LS93	.54
74LS02	.24	74LS95	.74
74LS03	.24	74LS96	.88
74LS04	.23	74LS107	.38
74LS05	.24	74LS109	.38
74LS08	.27	74LS112	.38
74LS09	.28	74LS113	.38
74LS10	.24	74LS114	.38
74LS11	.34	74LS122	.44
74LS12	.34	74LS123	.78
74LS13	.44	74LS124	2.85
74LS14	.58	74LS125	.48
74LS15	.34	74LS126	.48
74LS20	.24	74LS132	.58
74LS21	.28	74LS133	.58
74LS22	.24	74LS138	.38
74LS26	.28	74LS137	.98
74LS27	.28	74LS138	.54
74LS28	.34	74LS139	.54
74LS30	.24	74LS145	1.15
74LS32	.28	74LS147	2.45
74LS33	.54	74LS148	1.30
74LS37	.34	74LS151	.54
74LS38	.34	74LS153	.54
74LS40	.24	74LS154	1.85
74LS42	.48	74LS155	.68
74LS47	.74	74LS156	.68
74LS48	.74	74LS157	.64
74LS49	.74	74LS158	.58
74LS51	.24	74LS160	.68
74LS54	.28	74LS161	.84
74LS55	.28	74LS162	.68
74LS63	1.20	74LS163	.64
74LS73	.38	74LS164	.68
74LS74	.34	74LS165	.94
74LS75	.38	74LS168	1.90
74LS76	.38	74LS168	1.70
74LS78	.48	74LS169	1.70
74LS83	.59	74LS170	1.45
74LS85	.68	74LS173	.68
74LS86	.38	74LS174	.54
74LS90	.54	74LS175	.54
74LS91	.88	74LS181	2.10

74LS189	8.90	74LS363	1.30
74LS190	.88	74LS364	1.90
74LS191	.88	74LS365	.48
74LS192	.78	74LS366	.48
74LS193	.78	74LS367	.44
74LS194	.68	74LS368	.44
74LS195	.68	74LS373	1.35
74LS196	.78	74LS374	1.35
74LS197	.78	74LS377	1.35
74LS221	.88	74LS378	1.13
74LS240	.94	74LS379	1.30
74LS241	.98	74LS385	1.85
74LS242	.98	74LS386	.44
74LS243	.98	74LS390	1.15
74LS244	1.25	74LS393	1.15
74LS245	1.45	74LS395	1.15
74LS247	.74	74LS399	1.45
74LS248	.98	74LS424	2.90
74LS249	.98	74LS447	.36
74LS251	.58	74LS490	1.90
74LS253	.58	74LS624	3.95
74LS257	.58	74LS640	2.15
74LS258	.58	74LS645	2.15
74LS259	2.70	74LS668	1.65
74LS260	.58	74LS669	1.85
74LS266	.54	74LS670	1.45
74LS273	1.45	74LS674	9.60
74LS275	3.30	74LS682	3.15
74LS279	.48	74LS683	3.15
74LS280	1.95	74LS684	3.15
74LS283	.68	74LS685	3.15
74LS290	.88	74LS688	2.35
74LS293	.88	74LS689	3.15
74LS295	.98	74LS783	23.95
74LS298	.88	81LS95	1.45
74LS299	1.70	81LS96	1.45
74LS323	3.45	81LS97	1.45
74LS324	1.70	81LS98	1.45
74LS352	1.25	25LS2521	2.75
74LS353	1.25	25LS2569	4.20

## SPECIALS

4116	250ns	49¢/ea
4116	200ns	89¢/ea
2708	8K EPROMS	2.49
2716	16K EPROMS	2.95
2732	32K EPROMS	3.95
2764	64K EPROMS	6.45
27128	128K EPROMS	19.95
4164	64K DYNAMIC 250ns	4.45
4164	64K DYNAMIC 200ns	5.45
4164	64K DYNAMIC 150ns	6.45
2114	450ns	8/7.95

## 5 1/4" DISKETTES ATHANA

SSDD	18.95
SSDD	22.95
DSDD	27.95

## BULK DISKETTES 5 1/4" DISKETTES NO LABEL

SINGLE SIDED DOUBLE DENSITY (WITH JACKETS AND HUB RING)	
Pack of Ten	\$ 16.95
Pack of 100	\$149.00

**CPU'S & SUPPORT CHIPS**

8035	8.95	8275	74.50
8080A	2.75	8279-5	6.95
8085A	10.00	8355	12.35
8086	22.50	280A CPU	4.75
AMD 2901	8.95	280B CPU	12.95
8202	19.95	280A CTC	8.75
8205	6.50	280A DART	9.00
8212	5.00	280A P10	4.95
8214	4.50	280A S10	10.95
8216	3.50	TMS 9927 NL	9.95
8224	3.50	4M502	5.75
8225	3.50	6809	8.95
8227	22.00	6810	12.25
8238	3.95	6810	4.00
8250	10.95	6821	4.50
8251	9.00	6845	13.95
8253	9.00	6850	3.95
8257	9.00	6875	4.50
8259	9.00	68000L8	39.50

**INTER FACE & DRIVERS**

1488	1.50
1489	1.50
3341A	2.95
8130	2.50
8830	2.50
8833	2.50
8834	2.00
8837	2.00
1602B	3.95
BR1041L	8.95
CRT5037	18.95
MM5307	7.95
MM5369	2.50
AY3-1015D	8.75
AY5-1013A	3.75
AY5300PRO	9.95

**SHIFT REGISTERS**

MM1402	1.75
MM1403	1.75
MM1404	1.75
MM5013	2.50
MM5055	2.50
MM5056	2.50
MM5057	2.50
MM5058	2.50
MM5060	2.50

**DISC CONTROLLERS**

1771	16.50
1791	25.00
1797	45.00
1797	45.00

**WIRE WRAP STRAND SINGLE**

2532	7.95
2708	3.50
2718	22.50
2718 - 5V	4.95
2722	7.95
3628A-3	3.00
6331	1.95
TP188542	3.50
TP1925166	9.50
745474	3.95
7463-5	3.95
8256-5	1.25
825130	1.95
825130	1.95
825181	8.95
AM9214C	2.95
8118-12	4.95

**EPOXY GLASS VECTOR BOARD**

1/16" thick with 1/10" spacing  
4 1/2" x 6 1/2" ..... \$1.95

SCR's				TRIAC's			
1.5A	6A	35A		PRV 1A	10A	25A	
100	35	40	1.40	100	35	60	1.40
200	40	50	1.80	200	50	80	1.90
400	50	70	2.40	400	70	100	2.80
600	80	100	3.60	600	100	120	3.60

**C/MOS**

4001	50	4028	80	4077	50	74C14	90
4002	50	4029	1.00	4081	40	74C20	50
4006	80	4030	.60	4082	40	74C23	80
4007	340	4034	1.75	4093	80	74C42	1.00
4008	70	4035	1.00	4099	175	74C75	1.00
4009	60	4040	1.00	4501	95	74C83	1.25
4010	60	4042	90	4503	150	74C86	70
4011	50	4043	90	4506	75	74C154	2.50
4012	50	4044	.90	4511	1.25	74C157	1.75
4013	.60	4046	1.20	4514	1.00	74C161	1.15
4014	70	4047	1.50	4515	1.50	74C174	1.18
4015	.60	4049	.60	4516	1.40	74C175	1.19
4016	.60	4050	.60	4518	1.00	74C192	1.30
4017	75	4051	1.00	4520	1.20	74C193	1.75
4018	70	4053	1.00	4528	1.00	74C901	60
4019	70	4053	1.00	4529	1.40	74C902	1.00
4020	80	4066	70	4539	1.25	74C903	75
4021	80	4068	50	4583	90	74C907	75
4022	50	4069	50	4585	75	74C914	1.75
4023	50	4070	50	4587	90	74C915	1.75
4024	70	4071	50	74C02	50	74C915	1.00
4025	50	4072	.60	74C08	70	74C921	3.95
4026	95	4074	1.75	74C10	50		
4027	.60	4076	.85	74C10	50		

**74S SERIES**

74S00	.50	74S174	1.40
74S02	.50	74S175	1.40
74S03	.50	74S181	2.20
74S04	1.00	74S182	1.75
74S05	1.00	74S184	1.10
74S08	1.00	74S185	1.50
74S10	1.00	74S186	1.50
74S11	.50	74S187	1.50
74S15	.50	74S189	1.10
74S20	.50	74S190	1.50
74S21	.50	74S191	1.50
74S22	.50	74S192	1.50
74S23	.50	74S193	1.50
74S24	.50	74S194	1.50
74S25	.50	74S195	1.50
74S26	.50	74S196	1.50
74S27	.50	74S197	1.50
74S28	.50	74S198	1.50
74S29	.50	74S199	1.50
74S30	.50	74S200	1.50

**4164-2 - \$6.25**

**4116-3 - \$1.00**

**2114-4 - \$1.00**

**4164-15 - \$7.00**

2N3820 P FET	\$ .45
TIS 73 N FET	\$ .45
2N2646 UJT	\$ .45
ER 900 TRIGGER DIODES	4/51.00
2N 6028 PROG. UJT	\$ .65

**DISC CAPACITORS**

1UF 16V	10/51.00	100/58.00
1UF 35V	16/51.00	100/55.00

**PRINTED CIRCUIT BOARD**

4" x 6" DOUBLE SIDED EPOXY BOARD 1/16" THICK \$5/2.60

**FULL WAVE BRIDGE**

PRV	2A	6A	25A
100	1.40		
200	80	1.30	2.20
400	100	1.65	3.30
600	130	1.90	4.40

**SILICON POWER RECTIFIERS**

PRV	1A	3A	12A	50A	125A	240A
100	.06	.14	.36	.90	5.00	6.00
200	.06	.17	.50	1.30	7.00	9.00
400	.09	.25	.66	1.50	10.00	12.00
600	.11	.30	.80	2.00	13.00	15.00
800	.13	.36	1.00	2.50	16.00	18.00
1000	.20	.45	1.25	3.00	20.00	26.00

**REGULATORS**

LM338K	45.75	323K (LA14051)	41.75
LM317T	41.36	LM309G	41.75
78L12	41.40	340T-5, 6, 8, 9, 12	
723	41.50	15, 18 or 24V	41.75
320T-5, 12, 15 or 24	41.85	LA51412 + 12V	
LM337T	41.86	3A	43.35

**TANTALUM CAPACITORS**

22UF 35V	5/51.00	15UF 16V	3/51.00
47UF 35V	5/51.00	30UF 6V	5/51.00
68UF 35V	5/51.00	33UF 15V	\$ .50
1UF 20V	5/51.00	47UF 20V	\$ .85
2.2UF 20V	5/51.00	68UF 16V	\$ 1.00
3.3UF 20V	4/51.00	200UF 20V	\$ 1.75
4.7UF 35V	4/51.00	150UF 16V	\$ 1.30
6.8UF 20V	4/51.00	330UF 10V	\$ 1.75
10UF 20V	— \$ .40		
22UF 10V	— \$ .30		

50 PIN EDGEBOARD CONN.	3.95
40 PIN EDGEBOARD CONN.	3.00
34 PIN EDGEBOARD CONN.	3.00
26 PIN EDGEBOARD CONN.	2.50
60 PIN RIBBON CABLE CONN.	4.00
50 PIN RIBBON CABLE CONN.	3.50
40 PIN RIBBON CABLE CONN.	3.00
34 PIN RIBBON CABLE CONN.	2.75
26 PIN RIBBON CABLE CONN.	2.50
20 PIN RIBBON CABLE CONN.	2.00

**TRANSISTOR SPECIALS**

2N1307 PNP GE TO-18	\$ .40
2N1404A PNP GE TO-18	3/91.00
HEP 68014 - PNP GE TO-18	\$ .85
TP 111 - PNP GE TO-18	\$ 1.35
2N2623 PNP SWITCHING POWER	\$ 1.95
MAF 8004 CM RF TRANSISTOR PNP	\$ .75
2N4808 PNP SI TO-18	\$ 1.00
TP 2555 PNP SI	\$ .70
2N2022 PNP SI TO-18	7/81.00
2N2027 PNP SI TO-18	7/81.00
2N3005 PNP SI TO-18	\$ .80
2N3004 PNP SI TO-18	7/81.00
2N3006 PNP SI TO-18	7/81.00
2N6108 PNP SI TO-220	\$ .56
TP 318 PNP SI TO-220	\$ .40
TP 328 PNP SI TO-220	\$ .40
TP 34 PNP SI	\$ .95
TP 121 PNP SI UHM	\$ 1.00
TP 141 PNP SI UHM	\$ 1.00
BU208	\$ 1.75
DP5200 - DUAL POWER DARL	\$ 3.95
MA3506T	\$ .80

**TTL IC SERIES**

7400	50	7475	60	74164	80
7401	40	7476	60	74165	80
7402	50	7478	60	74170	1.60
7403	40	7483	50	74170	1.60
7404	60	7485	70	74173	.75
7405	60	7486	60	74174	.80
7406	150	7489	2.00	74175	.70
7408	50	7491	55	74176	.75
7409	30	7492	55	74180	1.90
7410	40	7493	55	74181	1.90
7411	40	7494	60	74182	.90
7412	40	7495	55	74190	.80
7413	45	7496	60	8191	.80
7414	75	7497	50	74192	.80
7420	40	74116	1.80	74193	.80
7425	40	74121	45	74194	.85
7426	75	74122	50	74195	.45
7427	75	74123	55	74196	.75
7430	75	74125	60	74199	1.25
7432	100	74126	45	74221	1.00
7437	50	74145	60	74273	.85
7438	1.75	74146	1.10	74279	.60
7440	30	74150	1.10	74285	.80
7442	50	74151	70	74287	.80
7445	100	74153	70	74390	.90
7446	80	74154	1.60	75325	1.50
7447	1.10	74155	70	75492	1.05
7448	80	74157	70	9601	1.10
7449	30	74159	70	8176	1.40
7472	50	74161	65	8728	1.40
7473	50	74162	70	8178	1.10
7474	60	74163	70		

**74LS SERIES**

74LS00	70	74LS109	70	74LS241	1.50
74LS01	50	74LS112	60	74LS242	2.00
74LS02	70	74LS113	60	74LS243	2.00
74LS03	50	74LS114	65	74LS244	2.25
74LS04	100	74LS121	60	74LS245	2.25
74LS05	100	74LS125	1.60	74LS246	2.50
74LS08	50	74LS126	90	74LS247	1.50
74LS09	50	74LS132	90	74LS248	1.50
74LS10	50	74LS136	1.00	74LS251	90
74LS11	60	74LS137	1.00	74LS252	90
74LS12	50	74LS138	25	74LS253	90
74LS13	55	74LS139	1.30	74LS258	90
74LS14	90	74LS147	1.95	74LS259	2.00
74LS15	90	74LS148	1.95	74LS260	1.75
74LS16	90	74LS153	1.00	74LS266	1.00
74LS17	90	74LS155	1.00	74LS273	1.60
74LS22	60	74LS156	1.00	74LS278	1.00
74LS26	55	74LS157	1.00	74LS280	1.00
74LS27	60	74LS158	1.00	74LS283	1.00
74LS28	90	74LS160	1.20	74LS290	1.20

# ADVANCED COMPUTER PRODUCTS



## RAM UP-GRADES

64K D RAM (4164-200nS)

9 pcs for \$50.00

16K D RAM (4116-200nS)

8 pcs for \$12.95

### REPEAT OF BUY-OUT

58 Key Unencoded Keyboard



\$19.95 ea.

This is a new 58 key terminal Keyboard manufactured by a major manufacturer. It is unencoded with SPST keys unswitched to any PC board. Solid molded plastic base measures 11" x 4"

### Unencoded Key Pad

15 key keypad with 1-10 keys and tab, return, (.), (:) and (,).



Only \$9.95 ea.

### UV "EPROM" ERASER



Model DE-4  
\$89.95

Model S-52T \$325.00

### CORCOM FILTER

Popular CORCOM Filter  
\$4.95  
Compatible Line Cord Add. \$3.50

### SWITCHER SPECIAL

by ASTEC  
Originally designed for the Apple II  
+5 @ 4.0A  
-5 @ 25A  
+12 @ 2.5A  
-12 @ .30A  
only \$49.95

### MISC. HI-TECH

MM5740AAC 9.95 3341FIFO 54.75  
AY5 2376 13.75 2513-001UC 9.50  
AY5 3600 13.75 2513-002LC 9.50  
UPD7201 29.95 7107CPL 11.50  
ULN2003 2.25

WE STOCK 74HC & 74C CMOS

### PALS

PAL10H8 \$3.75 PAL14L4 \$3.95  
PAL12H6 3.95 PAL16L8 9.95  
PAL14H4 3.95 PAL16R8 7.75  
PAL10L8 3.95 PAL16R6 7.75  
PAL12L6 3.95 PAL16R4 7.75

### FUNCTION GEN.

MC4024 \$3.75 LM566 \$1.95  
8038 3.75 XR2206 3.75

### UARTS/USRTS

AY5-1013A \$3.95 2350 39.75  
AY5-1014A 6.75 8250 12.50  
AY5-1015 6.75 IM6402 7.75  
TR1802A 3.75 IM6403 6.75

### BAUD RATE GEN.

MC14411 \$11.50 COM5016 \$15.95  
BR1941 10.50 COM1118 11.95  
34702 12.75 MMS507 11.95

### SOUND CHIPS

76477 \$3.50 MC3340 \$1.95  
76488 5.90 SC01Votax 39.95  
76489 8.50 DT1050 10.95  
AY38910 8.95 DigiStar 34.95  
AY38912 12.50 MMS5104 14.95

### STEPPER MOTOR

Operates by applying 12VDC in one direction and then reversing polarity (or square wave). Uses 12VDC. Clock Wise Rotation. Rated 3 RPM at 4 P.P.S. with a 5 degree stepping angle.



ACP Price \$3.95

10 for \$34.95

### RS232 SIGNAL TESTER

COEX RS232 LINE TESTER (7) LED Indicators  
Other Styles Also Available  
Only \$24.95



### CONNECTORS



### DB25F (RS232) DB25S Female Hood

DB25F (RS232) \$2.95  
DB25S Female 3.25  
Hood 1.49  
Set with Hood, Sale 6.95  
25-50 ST, Apple 3.95  
25-50 W/W, Apple 4.95  
3162 ST, IBM 4.95  
3162 W/W, IBM 5.95  
50-100 W/W, S-100 Connector 3.95  
50-100 S/T, S-100 Connector 3.95

### CRT CONTROLLERS

6845 \$14.75 8275 \$34.95  
6845 11.50 7220 89.50  
6847 11.50 COM5027 17.95  
HD4650SP 15.75 COM5037 22.00  
MC1372 6.75 8350 39.95  
TMS9918 39.95 8545 21.50

### DATA ACQUISITION

DAC01 \$5.95 ADC0800 \$15.25  
DAC08 7.50 ADC0809 3.95  
DAC100 7.50 ADC0809 9.95  
DAC0800 4.95 ADC0817 9.95  
DAC0808 2.95 MC3470 4.95  
DAC1020 8.95 1408L6 1.50  
DAC1022 5.95 1408L8 2.95  
F979 4.95 DAC08EX 9.95

### DISK SUPPORT

1691 \$16.95 2791 \$49.50  
1771 18.00 2793 49.50  
1791 22.95 2795 55.50  
1793 25.95 2797 55.50  
1795 27.95 6843 31.50  
1797 44.50 8272 36.00  
2143 18.95 UPD765A 36.00

### INTERFACE

75188 \$11.19 8795 \$ 8.5  
75189 1.19 8796 .85  
8726 1.75 8797 .85  
8728 1.85 8798 .85  
8731 2.75 75150 1.50  
95636 3.75 75154 1.50  
9537 3.75

### CLOCK CHIPS

MM5369 \$3.50 MM58174 \$10.95  
MM58187 11.95 MMS5832 3.95

### OSCILLATORS

1.000 \$10.95 8.000 \$10.95  
1.8432 10.95 10.000 10.95  
1.000 10.95 12.000 10.95  
4.000 10.95 16.000 10.95  
5.000 10.95 18.432 10.95  
1.842MHz 10.95 19.608 10.95  
6.000 10.95 20.000 10.95  
6.144 10.95 22.184 10.95

### ZERO INSERT SOCKETS

14PIN21F \$5.75 24PIN21F \$7.95  
16PIN21F 5.95 28PIN21F 9.95  
18PIN21F 7.95 40PIN21F 10.95  
20PIN21F 7.75 60PIN21F 19.75

### MICROPROCESSORS

68000 \$47.95 6504 \$6.75 8749 \$49.95  
6800 3.95 8505 8.95 8755 39.95  
68000 10.50 6507 9.95 2.80 3.75  
6802 7.85 8025 8.95 2.80A 4.30  
68020 20.85 8039 11.95 2.80B 9.50  
6803 18.50 8080 3.50 28001 44.95  
6808 13.50 8085 4.75 28002 49.95  
6809E 12.95 8085A-2 11.00 F-83650 19.95  
68809E 27.95 8086 29.95 2650 18.95  
6809 11.50 8087 19.00 1802 5.95  
68809 27.95 8088 29.95 8208-1 16.95  
6502 4.75 8089 64.95 2901 6.95  
6502A 6.50 8741 34.95 2801A 8.95  
6502B 9.75 8748 29.95 2807-1 37.95

### WE STOCK IN DEPTH CALL FOR VOLUME PRICING

### EPROMS

1702 \$4.25 2732 \$4.75 2784-250 \$7.75  
2708 3.85 2732-250 8.25 2784-250 16.50  
2726 4.95 2732-250 9.95 2804 39.95  
2716 3.85 2732A 8.75 68786 41.95  
2716-1 5.75 2732A 9.75 27128 27.95  
TMS2716 7.50 2732A2 13.00 520A0 14.90  
TMS2516 8.25 2784 8.75 520A0 13.50  
TMS2932 8.75

### STATIC RAMS

2101 \$2.75 2147 \$4.75 5516 \$11.95  
2102-1 99 2016-200 4.95 6116-4 4.95  
2102L-4 1.29 2016-150 5.95 6116-2 8.75  
2102L-2 1.49 2016-100 6.95 6116L-2 5.90  
2111 2.75 4044-4 2.95 6116L2 10.95  
2112 2.99 4044-2 6.50 2B132 32.50  
2114 1.49 4118 9.75 27128 27.95  
2114L-2 1.89 5514 3.50 6167 9.95

### DYNAMIC RAMS

MM4027 \$11.85 4116-200 \$1.49  
UPD410 8.95 4164-200 5.95  
UPD411 4.95 4164-150 6.75  
MM5280 2.95 MC6805 8.50  
MM5290 1.49 TMS4164-15 8.50  
MM5298 1.49 1256 79.95

### WE STOCK MOST OBSOLETE RAMS. CALL FOR YOUR HARD TO FIND PARTS.

### 8000 SUPPORT

8155 \$9.95 8238 \$4.75 8271 \$74.95  
8156 9.95 8243 5.50 8272 37.50  
8202 23.50 8250 10.50 8273 34.95  
8203 38.50 8251 5.95 8275 8.95  
8205 3.25 8251A 9.95 8275A 8.95  
8212 1.95 8253 6.50 8282 7.95  
8214 4.50 8253-5 9.95 8283 7.95  
8218 1.95 8255 5.95 8284 7.95  
8224 2.20 8255A 9.95 8286 7.95  
8226 2.75 8257 7.25 8287 7.95  
8228 3.35 8257-5 9.95 8288 24.95  
8237 18.50 8259 7.25 8289 48.50  
8237-5 21.50 8259-5 37.50

### 6500 SUPPORT

8520 \$4.25 6532 59.75 6545A \$26.50  
8522 6.75 6532A 11.75 6551 11.50  
8522A 1.50 6545 21.50 6551A 12.95

### 6800 SUPPORT

6810 \$2.75 68840 \$17.95 68850 \$5.75  
68B10 6.75 6843 31.50 6852 5.50  
6820 4.25 6844 25.00 6860 7.75  
6821 3.75 6845 14.75 6875 6.25  
68B21 6.75 6845A 17.50 6880 2.50  
6828 12.50 6847 11.75 6840 22.95  
6840 12.50 6850 3.50 68488 19.50

### Z-80 SUPPORT

Z80CTC \$3.95 Z80DART \$10.75 Z80ASO1 \$12.80  
Z80ACTC 4.75 Z80ADART 10.95 Z80ASO2 11.80  
Z80BCTC 6.75 Z80BODART 18.95 Z80ASO2 12.50  
Z80PIO 3.95 Z80SIO0 11.50 Z80SIO2 36.00  
Z80APO 4.75 Z80ASO10 12.50 Z80SIO9 11.50  
Z80BPIO 12.50 Z80SIO1 11.50 Z80SIO9 12.50

### SOCKETS

#### LOW PROFILE SOCKETS (TIN)

8 pin LP .16 .15 .14  
14 pin LP .22 .21 .20  
16 pin LP .22 .21 .20  
18 pin LP .22 .21 .20  
20 pin LP .34 .32 .30  
22 pin LP .29 .27 .26  
24 pin LP .38 .37 .36  
28 pin LP .45 .44 .43  
40 pin LP .60 .59 .58

#### 3L WIREWRAP SOCKETS (GOLD)

8 pin WW .55 .54 .49  
10 pin WW (Tin) .65 .63 .58  
14 pin WW .75 .73 .67  
16 pin WW .85 .80 .81  
18 pin WW .95 .89 .81  
20 pin WW 1.15 1.08 .99  
22 pin WW 1.45 1.35 1.23  
24 pin WW 1.35 1.26 1.14  
28 pin WW 1.60 1.53 1.38  
40 pin WW 2.20 2.09 1.89

### CRYSTALS

32.768KHz \$1.95 2.4575 \$2.95 5.7143 \$2.95 14.318MHz \$2.95  
1.000MHz 3.75 3.2768MHz 2.95 6.000MHz 2.95  
1.842MHz 3.75 3.5795MHz 1.95 6.144MHz 2.95  
2.000MHz 2.95 4.000MHz 2.95 8.5363MHz 2.95  
2.010MHz 2.95 5.000MHz 2.95 8.800MHz 2.95  
2.097152MHz 2.95 6.0685MHz 2.95 10.000MHz 2.95

### TOLL FREE

800-854-8230  
910-595-1565

## LINEAR

78H05K \$5.95 LM1414N \$1.90  
78M05 1.49 LM1458CN \$1.49  
78L05 1.49 MC1469N 99.99  
LM1084H 2.95 MC1489N 99.99  
LM300H 99 LM1496M 89.99  
LM301CN 35 LM1556N 1.50  
LM304H 1.98 LM1820N 95.95  
LM305H 1.98 LM1850N 95.95  
LM306H 3.25 LM1899N 3.19  
LM307CN 29 LM2111N 1.75  
LM308CN 98 LM2900N 99.99  
LM309K 1.49 LM2901N 2.50  
LM310CN 1.25 LM2917N 2.95  
LM311D-CN 85 CA3013T 2.19  
LM312H 1.75 CA3018T 1.99  
LM317T 1.70 CA3021T 3.49  
LM318CN 1.49 CA3023T 2.95  
LM319CN 1.25 CA3035T 2.75  
LM320K-XX 1.25 CA3039T 1.29  
LM320T-XX 1.39 CA3048N 1.29  
LM320H-XX 1.35 LM3053N 1.49  
LM323K 4.95 CA3059N 3.19  
LM324N 95 CA3060N 3.19  
LM337K 6.95 CA3062N 1.49  
LM338K 9.95 LM3065N 1.95  
LM339N 1.95 CA3080T 1.29  
LM340K-XX 1.75 CA3081N 1.69  
LM340T-XX 1.25 CA3082N 1.69  
LM340H-XX 1.25 CA3083N 1.55  
LM344H 1.95 CA3086N 8.50  
LM348N 1.20 CA3089N 2.99  
LM350K 5.60 CA3096N 3.49  
LM358CN 98 CA3097N 1.99  
LM360N 1.49 CA3130T 2.30  
LM372N 1.95 CA3140T 1.19  
LM375N 3.75 CA3151N 1.49  
LM377N 1.25 CA3150T 1.19  
LM380CN 1.25 CA3190N 1.95  
LM381N 1.79 CA3410N 5.99  
LM383T 1.95 MC3423N 1.49  
LM386N 1.25 MC3460N 3.95  
LM387N 1.49 MC3524N 3.95  
LM390N 1.95 CA3600N 3.39  
NE531VT 3.75 LM3900N 5.99  
NE555V 39 LM3905N 1.19  
NE556N 98 LM3909N 5.99  
NE561T 19.95 LM3914N 3.75  
NE568N 1.25 LM3915N 3.95  
NE568VH 1.75 LM3916N 3.95  
NE567VH 1.50 RC4131N 2.75  
NE592N 2.75 RC4136N 1.10  
LM702H 1.99 RC4151N 4.95  
LM704H 2.99 RC41045H 4.95  
LM710N 75 RC4195TK 5.40  
LM711NH 39 ULN2001 1.25  
LM715N 95 ULN2003 1.50  
LM723NH 65 SN75450N 59.99  
LM737NH 98 SN75451N 35.99  
LM739N 1.15 SN75452N 1.69  
LM741CN/H 33 SN75453N 49.99  
LM741CN-14 19 SN75454N 49.99  
LM747NH 75 SN75491N 89.99  
LM748NH 39 SN75492N 89.99  
LM760CN 2.99 SN75493N 89.99  
LM71310N 1.90 SN75494N 89.99  
MC1330 1.95 TL494CN 1.85  
MC1350 1.95 TL496CP 4.20  
MC1358 -1.75 TL497 4.95

## 7400

7400 \$ 19 7475 \$ .38 74161 \$ .69  
7401 \$ 19 7476 \$ .34 74162 \$ .69  
7402 \$ 19 7479 \$ 4.60 74163 \$ .69  
7403 \$ 19 7480 \$ 49 74164 \$ .69  
7404 \$ 19 7482 \$ 95 74165 \$ .69  
7405 \$ 23 7483 \$ 74166 \$ 12.00  
7406 Call 7485 \$ 74167 \$ 2.95  
7407 Call 7486 \$ 74170 \$ 1.49  
7408 \$ 24 7489 \$ 1.75 74172 \$ 4.75  
7409 \$ 19 7490 \$ 35 74173 \$ .69  
7410 \$ 19 7491 \$ 45 74174 \$ .69  
7411 \$ 24 7492 \$ 45 74175 \$ .69  
7412 \$ 24 7493 \$ 35 74176 \$ .69  
7413 \$ 29 7494 \$ 69 74177 \$ .69  
7414 \$ 49 7495 \$ 50 74179 \$ 1.34  
7415 Call 7496 \$ 74180 \$ .69  
7416 Call 7497 \$ 50 74181 \$ 1.75  
7417 \$ 19 74190 \$ 2.90 74182 \$ 75  
7421 \$ 35 74197 \$ 24 74184 \$ 2.25  
7422 \$ 29 74199 \$ 37 74185 \$ 2.25  
7423 \$ 1.19 74118 1.25  
7425 \$ 29 74121 29  
7426 \$ 29 74122 39 74190 1.15  
7427 \$ 25 74123 45 74191 1.15  
7429 \$ 45 74125 39 74192 75  
7430 \$ 18 74126 44 74193 75  
7432 \$ 29 74128 59 74194 75  
7437 \$ 29 74131 59 74195 68  
7438 \$ 29 74136 75 74196 75  
7439 \$ 1.19 74141 85 74198 1.25  
7441 \$ 75 74142 2.95 74199 1.29  
7442 \$ 45 74143 50 74201 1.19  
7443 \$ 95 74144 2.95 74251 69  
7444 \$ 65 74145 59 74273 1.05  
7445 \$ 79 74147 1.69 74276 1.89  
7446 \$ 79 74148 1.19 74279 75  
7447 \$ 65 74150 1.09 74283 1.40  
7448 \$ 79 74151 4.75 74284 3.69  
7449 \$ 19 74152 67 74285 3.69  
7451 \$ 19 74153 49 74290 9.95  
7452 \$ 19 74154 1.19 74296 95  
7453 \$ 19 74155 69 74365 65  
7454 \$ 25 74156 25 74366 65  
7460 \$ 23 74157 49 74367 65  
7470 \$ 29 74158 1.65 74368 65  
7471 \$ 19 74159 24.99 74390 1.45  
7472 \$ 24 74160 79 74390 1.90

## 74LS00

74LS00 \$ 26 74LS113 \$ 39 74LS245 \$2.99  
74LS01 25 74LS114 39 74LS247 1.10  
74LS02 25 74LS122 49 74LS248 1.10  
74LS03 25 74LS123 1.19 74LS249 1.19  
74LS04 69 74LS124 2.75 74LS251 1.40  
74LS05 25 74LS125 1.19 74LS253 1.40  
74LS06 25 74LS126 49 74LS257 85  
74LS09 25 74LS132 59 74LS258 98  
74LS10 25 74LS136 49 74LS259 2.95  
74LS11 39 74LS138 59 74LS260 65  
74LS12 33 74LS139 59 74LS261 2.49  
74LS13 33 74LS145 1.25 74LS266 59  
74LS14 59 74LS148 1.49 74LS273 1.75  
74LS15 33 74LS151 99 74LS275 4.00  
74LS20 26 74LS153 99 74LS279 59  
74LS21 29 74LS154 1.19 74LS281 59  
74LS22 29 74LS155 1.19 74LS290 99  
74LS26 29 74LS156 1.49 74LS293 99  
74LS27 29 74LS157 1.49 74LS295 1.10  
74LS28 29 74LS158 1.49 74LS298 1.15  
74LS30 25 74LS160 1.49 74LS299 1.75  
74LS32 33 74LS162 1.49 74LS347 1.95  
74LS33 55 74LS162 1.49 74LS348 1.95  
74LS37 35 74LS163 1.49 74LS352 1.19  
74LS38 39 74LS164 1.49 74LS

# AMAZING DEVICES

**PERSONAL DEFENSE AND PROPERTY PROTECTION UTILIZE SPACE AGE TECHNOLOGY. CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL.**

**PHASORS**

**POCKET PAIN FIELD GENERATOR — IPG50**  
 Assembled..... \$59.50  
 IPG5 Plans \$7.00 IPG5K Kit/Plans..... \$39.50

**PHASOR PAIN FIELD CROWD CONTROLLER — PPF10**  
 Assembled..... \$250.00  
 PPF1 Plans \$15.00 PPF1K Kit/Plans..... \$175.00

**BLASTER** — Provides a plasma discharge capable of puncturing a can.  
 Assembled..... \$79.50  
 BLS1 Plans \$10.00 BLS1K Kit/Plans..... \$59.50

**SHOCKER/PARALYZING DEVICE** — Very intimidating and effective.  
 SHG60 Assembled..... \$99.50  
 SHG6 Plans \$10.00 SHG6 Kit/Plans..... \$79.50

**LASERS**

**RUBY LASER RAY GUN** — Intense visible red beam burns and welds hardest of metals. **MAY BE HAZARDOUS.**

**RUB3 All Parts Available for Completing Device \$15.00**

**CARBON DIOXIDE BURNING, CUTTING LASER** — Produces a continuous beam of high energy. **MAY BE HAZARDOUS.**

**LC5 All Parts Available for Completing Device \$15.00**

**VISIBLE LASER LIGHT GUN** — produces intense red beam for sighting, spotting, etc. Hand held complete.  
 LGU3 Plans \$10.00 (Kit & Assembled Units Available)

**IR PULSED LASER RIFLE** — Produces 15-30 watt infra-red pulses at 200-2000 per sec.  
 LRC3 All Parts & Diodes Available..... \$10.00

**BEGINNERS LOW POWER VISIBLE LASER** — Choice of red, yellow, green — provides an excellent source of monochromatic light.  
 LHC2 Plans \$5.00 LHC2K Kit..... \$29.50

**SECURITY**

**SNOOPER PHONE** — Allows user to call his premises and listen in without phone ever ringing.  
 SNP20 Assembled..... \$89.50  
 SNP2 Plans \$9.00 SNP2K Plans/Kit..... \$59.50

**LONG RANGE WIRELESS MIKE** — Miniature device clearly transmits well over one mile. Super sensitive, powerful.  
 MFT1 Plans \$7.00 MFT1K Plans/Kit..... \$39.50


**WIRELESS TELEPHONE TRANSMITTER** — Transmits both sides of phone conversation over one mile, shuts off automatically.  
 VWPM5 Plans \$8.00 VWPM5K Plans/Kit..... \$34.50

**TALK & TELL AUTOMATIC TELEPHONE RECORDING DEVICE** — Great for monitoring telephone use.  
 TAT20 Assembled..... \$24.50  
 TAT2 Plans \$5.00 TAT2K Plans/Kit..... \$14.50

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send for free catalog of hundreds more similar devices. Send check, cash, MO, Visa, MC, COD to: **INFORMATION UNLIMITED**  
 DEPT RB, P.O. Box 716, Amherst, N. H. 03031 Tel: 603-673-4730

CIRCLE 88 ON FREE INFORMATION CARD

## STATE OF THE ART KITS

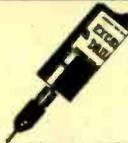

**EXCEL DRILL**

TITAN MINI DRILL \$29.95  
 RELIANT MINI DRILL KIT \$29.95

EXCEL MINI-DRILLS ARE HIGH PERFORMANCE, COMPACT AND LIGHTWEIGHT FOR ALL THE DELICATE AND MINUTE WORK INVOLVED WITH ELECTRONICS, ENGRAVING, MODEL MAKING AND OTHER CRAFTS. THE PRECISION DESIGN MAKES THEM AS EFFICIENT AS DRILLS MANY TIMES THEIR SIZE.

EACH DRILL KIT COMES COMPLETE WITH CASE AND 20 PIECE ACCESSORY MINI TOOLS SUCH AS DRILLS, BURS, BURCHES AND DISCS. NOTE: RUNS ON 12 VOLTS D.C.

DRILL STAND FOR ABOVE..... \$19.95

**EXCEL PRINTED CIRCUIT BOARD KITS**

CIRCUIT BOARD KITS..... \$24.95  
 COMPLETE KIT WITH POSITIVE RESIST PC BOARDS, ETCHANT, DEVELOPER, GRAPHICS & TRAY.

**CARBIDE P.C. DRILLS**

A SPECIAL PURCHASE MADE IT POSSIBLE TO PASS A SAVINGS ONTO YOU. THESE DRILLS NORMALLY SELL FOR AS MUCH AS \$3.95. ALL DRILLS HAVE A STANDARD 1/8 INCH SHANK.

033 DEC. SIZE..... \$1.90 EA. OR \$45.00  
 043 DEC. SIZE..... \$1.90 EA. OR \$45.00  
 062 DEC. SIZE..... \$1.50 EA. OR \$45.00

LOGIC PROBE KIT..... ONLY \$5.95  
 NEEDED BY ANYONE WORKING WITH LOGIC IN THEIR PROJECTS. HAS A RANGE CONSISTS OF: SMALL 0-10 P.C. BOARD MEASURING 2 7/8" x 3 3/4" AND PRE-DRILLED ONE SEVEN SEGMENT READOUT, ONE LC, TWO DIODES, THREE RESISTORS AND ONE TRANSISTOR. WORKS OFF 5 VOLTS AND MAY BE TAKEN FROM THE CIRCUIT BEING TESTED. INDICATES (H) HIGH, (L) LOW, NORMAL AND (P) PULSING. EXCELLENT STUDENT PROJECT.

**PRE-SCALER KITS**

HAL 300 PRE..... \$14.95  
 PC BOARD AND ALL COMPONENTS

HAL 300 APRE..... \$24.95  
 PC BOARD AND ALL COMPONENTS WITH PRE-AMP ONBOARD

HAL 800 PRE..... \$29.95  
 PC BOARD AND ALL COMPONENTS

HAL 800 APRE..... \$39.95  
 PC BOARD AND ALL COMPONENTS WITH PRE-AMP ONBOARD

HAL 1.2 GHZ PRE-SCALER..... \$66.95  
 BUILT AND TESTED - REQUIRES 5 VOLTS D.C.

SHIPPING INFORMATION: ORDERS OVER \$25 WILL BE SHIPPED POST-PAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUESTED. ON ORDERS LESS THAN \$25, PLEASE INCLUDE ADDITIONAL \$2.50 FOR HANDLING AND MAILING CHARGES. MICHIGAN RESIDENTS ADD 4% SALES TAX SEND 20 STAMPS OR \$ASE FOR FREE FLYER.

COMPLETE SETS OF P.C. BOARDS AVAILABLE FOR UNICORN ROBOT PROJECT, HEART & MATE PROJECT, PIANO MATE PROJECT, AND MANY MANY OTHER KITS AVAILABLE.

**HAL-TRONIX, INC.**  
 P.O. BOX 1101, DEPT. R  
 SOUTHWAY, MICH. 49783  
 PHONE (313) 285-1782



CIRCLE 75 ON FREE INFORMATION CARD

## INTERFACING

*continued from page 56*

the MSM5832, which resumes normal timing operations. Program execution then returns to the BASIC language routine. Line 870 defines the next MSM5832 register which is to be input. Line 880 defines the next storage location for that register's contents, and if all 13 registers in the MSM5832 have not been accessed, the machine-language program is called again. If all 13 registers of the MSM5832 have been accessed, program execution stops.

After program execution stops, the contents of all 13 registers of the MSM5832 will reside in memory, in the addresses listed in Table 12. Once the date and time information reside in memory, it is a simple matter to retrieve it and display it using the PEEK instruction. For instance, if you wish to retrieve the day of the week, write this simple program, you can enter the direct command:

```
PRINT PEEK 16546.
```

The number retrieved represents a day of the week as defined in Table 13. (Of course you could write a simple program to give you back the actual day instead of

**TABLE 14—TIME RETRIEVAL**

```

10 DIM A(6)
20 LET X = 16540
30 FOR J = 1 TO 6
40 LET A(J) = PEEK X
50 LET X = X + 1
60 NEXT J
70 LET B$ = "AM"
75 IF A(6) > 2 THEN LET B$ = "PM"
80 IF A(6) > 2 THEN LET
  A(6) = A(6) - 4
85 CLS
90 PRINT A(6);A(5);";";A(4);
  A(3);";";A(2);A(1);";"B$
100 STOP
  
```

**TABLE 15—DATE RETRIEVAL**

```

10 DIM A(6)
20 LET X = 16547
30 FOR J = 1 TO 6
40 LET A(J) = PEEK X
50 LET X = X + 1
60 NEXT J
70 LET B = 19
80 PRINT
  A(4);A(3);";";A(2);A(1);";";
  B;A(6);A(5)
90 STOP
  
```

• Delete line 90 in the time-display program (Table 14).

**TABLE 12—MEMORY LOCATIONS OF MSM5832 REGISTER VALUES**

Hexadecimal	Decimal	Register
409C	16540	0—SECONDS
409D	16541	1—TENS OF SECONDS
409E	16542	2—MINUTES
409F	16543	3—TENS OF MINUTES
40A0	16544	4—HOURS
40A1	16545	5—TENS OF HOURS
40A2	16546	6—DAY OF WEEK
40A3	16547	7—DAYS
40A4	16548	8—TENS OF DAYS
40A5	16549	9—MONTHS
40A6	16550	10—TENS OF MONTHS
40A7	16551	11—YEARS
40A8	16552	12—TENS OF YEARS

**TABLE 13—DAY-OF-WEEK VALUES**

0	Monday
1	Tuesday
2	Wednesday
3	Thursday
4	Friday
5	Saturday
6	Sunday

the number.)  
 If you want the time to be retrieved and displayed try the program in Table 14. And if you want to retrieve and display the entire date, try the program in Table 15.

Of course, using separate programs is not the most elegant way to use the clock/calendar circuit. You could put all of the simple BASIC routines in a loop and have the time information updated periodically. To demonstrate updating, make the following changes:

• Change line 900 in the retrieval routine (Table 8) to: 900 GOTO 20.  
 Those changes allow the time-display routine to print the time values (lines 10 through 80); go and get updated values from the MSM5832 (lines 800 through 900); and return to the time display routine. The program does that until a BREAK is entered.

We now have a good idea of how to control the clock/calendar IC. Controlling other external circuits and devices is not too much different. Next month, when we continue, we'll look at how to do that. When we're finished, you'll see how we can add an alarm function to the clock/calendar circuit. In addition to an alarm function you can use the MSM5832 in conjunction with the ZX81 as a nighttime light controller and a date/time home security system.

**R-E**

# WE HAVE QUALITY PARTS, DISCOUNT PRICES AND FAST SHIPPING!

## TRANSFORMERS

**120 volt primaries**

5.6 VOLTS @ 750 MA \$3.00  
 6 VOLTS @ 150 MA \$1.25  
 12 VCT @ 200 MA \$2.00  
 16.5 V. @ 3 AMPS \$6.50  
 18 V. @ 650 MA \$3.50  
 18 VOLTS @ 1 AMP \$4.50  
 24 VOLTS @ 250 MA \$2.50  
 24 VCT @ 1 AMP \$4.50  
 42 VCT @ 1.2 AMP \$4.50

## WALL TRANSFORMER

ALL ARE 115 VAC PLUG IN

4 VDC @ 70 MA \$2.00  
 6 VDC @ 100 MA \$2.50  
 6 VDC @ 500 MA \$5.00  
 9 VDC @ 225 MA \$3.00  
 14 VDC @ 300 MA \$3.50  
 15 VAC @ 300 MA \$3.00  
 16.5 VAC @ 10 VA \$3.50  
 17 VAC @ 500 MA \$4.00

## SPRING LEVER TERMINALS

TWO COLOR CODED TERMINALS ON A STURDY 2 3/4" x 3 3/4" BAKELITE PLATE GREAT FOR SPEAKER ENCLOSURES OR POWER SUPPLIES

\$1.00 EACH 10 FOR \$9.00

## 2 CHANNEL LIGHT ORGAN

EASILY HOOKS INTO STEREO SPEAKERS AND ALLOWS 110 VAC LIGHTS TO DANCE WITH MUSIC. TWO SEPARATE 110 VAC OUTPUTS FOR HIGH AND LOW FREQUENCY AUDIO SIGNALS. USE TWO ORGANS FOR STEREO

\$6.50 PER UNIT  
 COLOR LIGHT STRING AVAILABLE \$1.75 EA

## HELPING HAND

WILL HOLD P.C. BOARD OR OTHER SMALL ITEMS AND ALLOW BOTH YOUR HANDS FREEDOM TO WORK

\$6.50 EACH

## MIKE CONNECTOR

5 CONDUCTOR IN-LINE PLUG AND CHASSIS MOUNT YACK. TWIST LOCK STYLE. SAME AS SWITCHCRAFT 12CL5M.

\$2.50 PER SET

## METER

0 - 15 V.D.C.  
 THIS 2-1/4" SQUARE METER MEASURES 0-15 VDC.

\$4.50 EACH

## SUB-MINIATURE D TYPE CONNECTOR

SOLDER STYLE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.

DB-15 PLUG \$2.75  
 DB-15 SOCKET \$4.00  
 DB-15 HOOD \$1.50  
 DB-25 PLUG \$2.75  
 DB-25 SOCKET \$3.50  
 DB-25 HOOD \$1.25

## "PARALLEL" PRINTER CONNECTOR

SOLDER STYLE 36 PIN MALE USED ON "PARALLEL" DATA CABLES

\$5.50 EACH

## LIGHTS

**GRAIN OF WHEAT T1 SIZE**  
 125" DIA. (3.15mm)

3 to 6 VOLTS 3 for \$1.00  
 Rated: 55ma @ 5 VOLTS  
 6 to 12 VOLTS 3 for \$1.00  
 Rated: 55ma @ 8 VOLTS  
 12 to 24 VOLTS 3 for \$1.00  
 Rated: 45ma @ 14 VOLTS

**T1 SIZE WITH WIRE LEADS**

3 to 6 VOLTS 2 for \$1.00  
 Rated: 55ma @ 5 VOLTS  
 6 to 12 VOLTS 2 for \$1.00  
 Rated: 55ma @ 8 VOLTS  
 12 to 24 VOLTS 2 for \$1.00  
 Rated: 45ma @ 14 VOLTS

**T1 - 3/4 SIZE WITH WIRE LEADS**

163" DIA. (4.14mm)

3 to 6 VOLTS 2 for \$1.00  
 Rated: 45ma @ 6 VOLTS  
 6 to 12 VOLTS 2 for \$1.00  
 Rated: 55ma @ 8 VOLTS  
 12 to 24 VOLTS 2 for \$1.00  
 Rated: 45ma @ 14 VOLTS

**NEON W/ RESISTOR DIRECT OPERATION**

7 for \$1.00 FROM 120 VOLT

**120V INDICATOR**

NEON INDICATOR RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE - RED LENS.

75c EACH  
 10 FOR \$7.00  
 100 FOR \$65.00

## 8 TRACK RECORD/PLAY TAPE DECK

MORSE MODEL 94-A

8 TRACK RECORD WITH AUTO STOP. NOT FULLY FUNCTIONAL. REMOVED FROM ASSEMBLY LINE FOR MINOR PROBLEMS. IDEAL FOR PARTS. EACH UNIT CONTAINS SWITCHES, LIGHTS, TAPE MOTOR, BELT, WHEELS, PULLEYS, PRE AMPS, TAPE HEADS, ETC.

\*SPECIAL PRICE\* \$4.00 EACH  
 10 for \$35.00

**2K 10 TURN MULTI-TURN POT**

SPECTROL MOD 534-7161

\$5.00 EACH

## SWITCHES

**MINI-PUSH BUTTON**

S.P.S.T. MOMENTARY NORMALLY OPEN 1/4" BUSHING

35c EACH  
 10 FOR \$3.25  
 100 FOR \$30.00

SPECIFY COLOR: RED, BLACK, WHITE, GREEN, YELLOW.

## EDGE CONNECTORS

ALL ARE 156" SPACING

**18/36 GOLD**  
 SOLDER EYELET \$2.00 EACH

**22/44 TIN**  
 P.C. STYLE NO MOUNTING EARS \$1.50 EACH 10 FOR \$14.00

**22/44 GOLD**  
 P.C. STYLE \$2.00 EACH 10 FOR \$18.00

**28/56 GOLD**  
 28/56 GOLD PLATED CONTACTS 156 CONTACT SPACING.

\$2.50 EACH 10 FOR \$22.00

**50/100 GOLD**  
 STANDARD S-100 CONNECTOR 125" SPACING GOLD PLATED P.C. MOUNT.

\$3.75 EACH 10 FOR \$35.00

**LIGHTED PUSH BUTTON**

RED LIGHTED 120 VAC 10 AMP. S.P.S.T.

"POWER" PRINTED ON FACE MOUNTS IN 7/8" SQUARE HOLE

\$1.50 EA 10 FOR \$13.50

# FREE! FREE! FREE! SEND FOR NEW LARGER! 48 PAGE CATALOG FREE! FREE! FREE!

## LINE CORDS

**TWO WIRE**  
 6' 18ga TWO WIRE 3 FOR \$1.00

**THREE WIRE**  
 18 INCH 18ga THREE WIRE 2 for \$1.00  
 8 FOOT 18ga THREE WIRE \$2.00 EACH

## SOLDERING IRON STAND

SPRING STEEL IRON HOLDER ON WEIGHTED BASE

\$5.00 EACH

## TRANSISTORS

2N705 5 for \$1.00  
 2N2222A 4 for \$1.00  
 PN2222 8 for \$1.00  
 2N2904 4 for \$1.00  
 2N2905 4 for \$1.00  
 2N2907 4 for \$1.00

## POWER SUPPLY W/ PRE-AMP

THIS SUPPLY WAS USED TO POWER AN 8 TRACK/CASSETTE UNIT. IT WILL SUPPLY APPROX. 18 VDC AND INCLUDES A SMALL PRE-AMP TO BOOST SIGNAL LEVEL. RCA PLUGS FOR LINE IN/OUT.

\$4.50 EACH

## KEY ASSEMBLY

**5 KEY** \$1.00 EACH

CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 3 3/4" LONG

**6 KEY** \$1.25 EACH

CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 4 1/4" LONG.

## BATTERY OPERATED SMOKE DETECTOR

BRK MODEL #79R UL APPROVED 9 VOLT BATTERY OPERATION FOR CEILING OR WALL MOUNT.

\$8.00 EACH 2 FOR \$15.00

## ROTARY SWITCH

**1 POLE 6 POSITION**  
 1 1/4" DIA x 1 1/2" HIGH  
 75c EACH 10 for \$6.00

## RELAYS

**MINIATURE 6 VDC RELAY**

SUPER SMALL SPDT RELAY. GOLD COBALT CONTACTS

RATED 1 AMP AT 30 VDC. HIGHLY SENSITIVE. TTL DIRECT DRIVE POSSIBLE. OPERATES FROM 43 TO 6 V. COIL RES. 220 OHM.

1 3/16" x 13/32" x 7/16" AROMAT # RSD-6V

\$1.50 EACH 10 FOR \$13.50

## 13 VDC RELAY

CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT

COIL: 13 VDC 650 OHMS

SPECIAL PRICE \$1.00 EACH

## 4 PDT RELAY

14 pin style

- 3 amp contacts
- 24 volt d.c. or 120 volt a.c. coil
- Used but fully tested

\$1.70 EACH

Specify coil voltage

LARGE QUANTITIES AVAILABLE

SOCKETS FOR RELAY 50c each

## COMPUTER GRADE CAPACITORS

2,000 mfd. 200 VDC 1 3/4" DIA. - 5" HIGH \$2.00  
 3,600 mfd. 40 VDC 1 3/8" DIA. - 3 3/4" HIGH \$1.00  
 6,400 mfd. 60 VDC 1 3/8" DIA. - 4 1/4" HIGH \$2.50  
 21,000 mfd. 50 VDC 2 1/2" DIA. - 5" HIGH \$4.00  
 22,000 mfd. 40 VDC 2" DIA. - 6" HIGH \$3.00  
 31,000 mfd. 15 VDC 1 3/4" DIA. - 4" HIGH \$2.50  
 44,000 mfd. 35 VDC 2" DIA. - 5" HIGH \$4.00  
 72,000 mfd. 15 VDC 2" DIA. - 4 3/8" HIGH \$3.50  
 185,000 mfd. 6 VDC 2 1/2" DIA. - 4 1/2" HIGH \$1.50

CLAMPS TO FIT CAPACITORS 50c ea.

## MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

**S.P.D.T. (on-on)**  
 P.C. STYLE. NON-THREADED BUSHING. 75c EACH 10 FOR \$7.00

**S.P.D.T. (on-off)**  
 NON-THREADED BUSHING. P.C. STYLE 75c EACH 10 FOR \$7.00

**S.P.D.T. (on-on)**  
 SOLDER LUG TERMINALS \$1.00 EACH 10 FOR \$9.00  
 100 FOR \$80.00

**S.P.D.T. (on-off)**  
 P.C. LUGS. THREADED BUSHING \$1.00 EACH 10 FOR \$9.00  
 100 FOR \$80.00

**D.P.D.T. (on-on)**  
 SOLDER LUG TERMINALS \$2.00 EACH 10 FOR \$19.00  
 100 FOR \$180.00

## SLIDE POTS

**100K linear taper**  
 2" LONG  
 1 5/8" TRAVEL 75c EACH

**500K linear taper**  
 2 7/8" LONG  
 1 3/4" TRAVEL 75c EACH

**DUAL 100K audio taper**  
 3 1/2" LONG  
 2 1/2" TRAVEL. \$1.50 EACH

## CRYSTALS

CASE STYLE HC33/U

2 MHZ COLORBURST 3579.545 KC

\$3.50 EACH \$1.00 EACH

## METAL OXIDE VARISTOR

G.E. # V82A12 50 VOLTS. NOMINAL D.C. VOLTAGE. 5/8" DIAMETER

2 FOR \$1.50

## L.E.D.'S

**STANDARD JUMBO DIFFUSED**

RED 10 FOR \$1.50  
 GREEN 10 FOR \$2.00  
 YELLOW 10 FOR \$2.00

**FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE \$1.00 EACH**

**BI POLAR LED 2 FOR \$1.70**

**SUB MINI LED**

079 - .098

RED 10 FOR \$1.00  
 200 FOR \$18.00  
 GREEN 10 FOR \$1.50

**LED HOLDERS**

TWO PIECE HOLDER FOR JUMBO LED  
 10 FOR 65c 200 FOR \$10.00

## PHOTO-FLASH CAPACITORS

**35 MFD 330 VOLT**

1" x 5/8" DIA. 45c EACH 10 FOR \$4.00

**170 MFD 330 VOLT**

1 1/8" x 7/8" 2 FOR \$1.50 10 FOR \$7.00

**750 MFD 330 VOLT**

2" HIGH x 1 1/4" DIA. \$1.25 EACH 10 FOR \$11.00

TOLL FREE ORDERS ONLY  
 1-800-826-5432 (ORDER ONLY)  
 (IN CALIFORNIA: 1-800-258-6666)  
 ALASKA, HAWAII, OR INFORMATION  
 (213) 380-8000

# ALL ELECTRONICS CORP.

905 S. Vermont Ave. P.O. BOX 20406 Los Angeles, Calif. 90006

QUANTITIES LIMITED  
 MINIMUM ORDER \$10.00  
 USA: \$2.50 SHIPPING  
 FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING  
 CALIF. RES. ADD 6 1/2%  
 NO C.O.D.

CIRCLE 12 ON FREE INFORMATION CARD

# 4164

64K DYNAMIC  
200 ns

# \$595

# 4116

16K DYNAMIC  
250 ns

# 8/\$795

### STATIC RAMS

2101	356 x 4	(450ns)	1.95
5101	256 x 4	(450ns) (cmos)	3.95
2101-1	1024 x 1	(450ns)	.89
2102L-4	1024 x 1	(450ns) (LP)	.99
2102L-2	1024 x 1	(250ns) (LP)	1.49
2125	1024 x 1	(45ns)	2.95
2111	256 x 4	(450ns)	2.49
2111L	256 x 4	(250ns) (LP)	2.95
2112	256 x 4	(450ns)	2.99
2114	1024 x 4	(450ns)	8/9.95
2114-25	1024 x 4	(250ns)	8/10.95
2114L-4	1024 x 4	(450ns) (LP)	8/12.95
2114L-3	1024 x 4	(300ns) (LP)	8/13.45
2114L-2	1024 x 4	(200ns) (LP)	8/13.95
TC5514	1024 x 4	(650ns) (cmos)	2.49
TC5516	2048 x 4	(250ns) (cmos)	9.95
2147	4096 x 1	(55ns)	4.95
TMS4044-4	4096 x 1	(450ns)	3.49
TMS4044-3	4096 x 1	(300ns)	3.99
TMS4044-2	4096 x 1	(200ns)	4.49
UPD410	4096 x 1	(100ns)	3.95
MK4118	1024 x 8	(100ns)	9.95
TMM2016-200	2048 x 8	(200ns)	4.15
TMM2016-150	2048 x 8	(150ns)	4.95
TMM2016-100	2048 x 8	(100ns)	6.15
HM6116-4	2048 x 8	(200ns) (cmos)	4.75
HM6116-3	2048 x 8	(150ns) (cmos)	4.95
HM6116-2	2048 x 8	(120ns) (cmos)	8.95
HM6116L-P-4	2048 x 8	(200ns) (cmos) (LP)	5.95
HM6116L-P-3	2048 x 8	(150ns) (cmos) (LP)	6.95
HM6116L-P-2	2048 x 8	(120ns) (cmos) (LP)	10.95
TMS4016	2048 x 8	(200ns) (cmos)	6.95
Z-8132	4096 x 8	(300ns) (Qatst)	34.95
HM6264P-15	8192 x 8	(150ns) (cmos)	39.95
HM6264P-15	8192 x 8	(1192) (cmos)	49.95

LP = Low Power Qatst = Quasi-Static

### DYNAMIC RAMS

TMS4027	4096 x 1	(250ns)	1.99
2107	4096 x 1	(200ns)	1.95
MM5280	4096 x 1	(300ns)	1.95
TMS4080	4096 x 1	(300ns)	1.95
UPD411	4096 x 1	(300ns)	1.95
TMS4050	4096 x 1	(300ns)	1.95
MK4108	8192 x 1	(200ns)	1.95
MM5298	8192 x 1	(250ns)	1.85
4116-300	16384 x 1	(300ns)	8/11.75
4116-250	16384 x 1	(250ns)	8/7.95
4116-200	16384 x 1	(200ns)	8/12.95
4116-150	16384 x 1	(150ns)	8/14.95
4116-120	16384 x 1	(120ns)	8/20.95
2118	16384 x 1	(150ns) (5v)	4.95
MK4332	32768 x 1	(200ns)	9.95
4164-200	65536 x 1	(200ns) (5v)	5.95
4164-150	65536 x 1	(150ns) (5v)	6.95
4164-120	65536 x 1	(120ns) (5v)	8.95
MCM6665	65536 x 1	(200ns) (5v)	8.95
TMS4164-15	65536 x 1	(150ns) (5v)	8.95
TMS4416	16384 x 4	(150ns) (5v)	9.95
41256	262144 x 1	(200ns) (5v)	CALL

5v = Single 5 volt supply

### EPROMS

1702	256 x 8	(1us)	4.50
2708	1024 x 8	(450ns)	3.95
2758	1024 x 8	(450ns) (5v)	5.95
2716-6	2048 x 8	(650ns)	2.95
2716	2048 x 8	(450ns) (5v)	3.95
2716-1	2048 x 8	(350ns) (5v)	5.95
TMS2516	2048 x 8	(450ns) (5v)	5.50
TMS2716	2048 x 8	(450ns)	7.95
TMS2532	4096 x 8	(450ns) (5v)	5.95
2732	4096 x 8	(450ns) (5v)	4.95
2732-250	4096 x 8	(250ns) (5v)	8.95
2732-200	4096 x 8	(200ns) (5v)	11.95
2732-4	4096 x 8	(450ns) (5v) (21vPGM)	6.95
2732A	4096 x 8	(250ns) (5v) (21vPGM)	9.95
2732A-2	4096 x 8	(200ns) (5v) (21vPGM)	13.95
2764	8192 x 8	(450ns) (5v)	6.95
2764-250	8192 x 8	(250ns) (5v)	7.95
2764-200	8192 x 8	(200ns) (5v)	19.95
TMS2564	8192 x 8	(450ns) (5v)	14.95
MCM68764	8192 x 8	(450ns) (5v) (24pin)	39.95
MCM68766	8192 x 8	(350ns) (5v) (24pin)	42.95
27128-30	16384 x 8	(300ns) (5v)	29.95
27126	16384 x 8	(250ns) (5v)	34.95

5v = Single 5 Volt Supply 21vPGM = Programat 21 Volts

### ★ ★ ★ HIGH-TECH ★ ★ ★

## SSI 263 SPEECH SYNTHESIZER

- ★ MICROPROCESSOR COMPATIBLE
- ★ 5 8-BIT CONTROL REGISTERS
- ★ ENHANCE YOUR MOCKINGBOARD OR BUILD STEVE CIARCIA'S SWEET TALKER II (BYTE MARCH '84) **39.95**

### ★ ★ ★ SPOTLIGHT ★ ★ ★

- ★ Computer managed inventory — virtually no back orders!
- ★ Very competitive prices!
- ★ Friendly staff!
- ★ Fast service — most orders shipped within 24 hours!

### CRYSTALS

32.768 khz	1.95
1.0 mhz	3.95
1.8432	3.95
2.0	2.95
2.097152	2.95
2.4576	2.95
3.2768	2.95
3.579545	2.95
4.0	2.95
5.0	2.95
5.0688	2.95
5.185	2.95
5.7143	2.95
6.0	2.95
6.144	2.95
6.5536	2.95
8.0	2.95
10.0	2.95
10.738635	2.95
14.31818	2.95
15.0	2.95
16.0	2.95
17.430	2.95
18.0	2.95
18.432	2.95
20.0	2.95
22.1184	2.95
32.0	2.95

### CMOS

4000	29	4528	1.19
4001	25	4531	.95
4002	25	4532	1.95
4006	89	4538	1.95
4007	29	4539	1.95
4008	95	4541	2.64
4009	39	4543	1.19
4010	45	4553	5.79
4011	25	4555	.95
4012	25	4556	.95
4013	38	4581	1.95
4014	79	4582	1.95
4015	39	4584	.75
4016	39	4585	.75
4017	69	4702	12.95
4018	79	74C00	.35
4019	39	74C02	.35
4020	75	74C04	.35
4021	79	74C08	.35
4022	79	74C10	.35
4023	29	74C14	.59
4024	65	74C20	.35
4025	29	74C30	.35
4026	1.65	74C32	.39
4027	45	74C42	1.29
4028	69	74C48	1.99
4029	79	74C73	.65
4030	39	74C74	.65
4034	1.95	74C76	.80
4035	85	74C83	1.95
4040	75	74C85	1.95
4041	75	74C86	.39
4042	69	74C89	4.50
4043	85	74C90	1.19
4044	79	74C93	1.75
4046	85	74C95	.99
4047	95	74C107	.89
4049	35	74C150	5.75
4050	35	74C151	2.25
4051	79	74C154	3.25
4052	79	74C157	1.75
4060	89	74C160	1.19
4066	39	74C161	1.19
4068	39	74C162	1.19
4069	29	74C163	1.19
4070	35	74C164	1.39
4071	29	74C165	2.00
4072	29	74C173	.79
4073	29	74C174	1.19
4075	29	74C175	1.19
4076	79	74C192	1.49
4078	29	74C193	1.49
4081	29	74C195	1.39
4082	29	74C200	5.75
4085	95	74C221	1.75
4086	95	74C244	2.25
4093	49	74C373	2.45
4098	2.49	74C374	2.45
4099	9.00	74C901	.39
11C90	13.95	14409	12.95
95H90	7.95	14410	12.95
2513-001 UP	9.95	14411	11.95
2513-002 LOW	9.95	14412	12.95
		14419	7.95
		14433	14.95
		4502	95
		4503	65
		4508	1.95
		4510	85
		4511	.85
		4512	.85
		4514	1.25
		4515	1.79
		4516	1.55
		4518	.89
		4519	.39
		4520	.79
		4522	1.25
		4526	1.25
		4527	1.95

### UARTS

AY5-1013	3.95
AY3-1015	6.95
PT1472	9.95
TR1602	3.95
2350	9.95
2651	8.95
IM6402	7.95
IM6403	8.95
INS8250	10.95

### GENERATORS

MC14411	11.95
BR1941	11.95
4702	12.95
COM5016	16.95
COM8116	10.95
MM5307	10.95

### FUNCTION

MC4024	3.95
LM566	1.49
XR2206	3.75
8038	3.95

### MISC.

UPD7201	29.95
TMS99532	29.95
ULN2003	2.49
3242	7.95
3341	4.95
MC3470	4.95
MC3480	9.00
11C90	13.95
95H90	7.95
2513-001 UP	9.95
2513-002 LOW	9.95

### CLOCK CIRCUITS

MM5314	4.95
MM5369	3.95
MM5369-EST	4.25
MM5375	4.95
MM58167	12.95
MM58174	11.95
MSM5832	3.95

### KEYBOARD CHIPS

AY5-2376	11.95
AY5-3600	11.95
AY5-3600 PRO	11.95

### 6800

68000	49.95
6800	2.95
6802	7.95
6803	19.95
6808	13.90
6809E	14.95
6809	11.95
6810	2.95
6820	4.35
6821	2.95
6828	14.95
6840	12.95
6843	34.95
6844	25.95
6845	14.95
6847	11.95
6850	3.25
6852	5.75
6860	7.95
6875	6.95
6880	2.25
6883	22.95
68047	24.95
68488	19.95

### 6800 = 1MHZ

68B00	10.95
68B02	22.25
68B09E	29.95
68B09	29.95
68B10	6.95
68B21	6.95
68B40	19.95
68B45	19.95
68B50	5.95
68B00 = 2 MHZ	

### 6500

6502	4.95
6504	6.95
6505	8.95
6507	9.95
6520	4.35
6522	6.95
6532	9.95
6545	22.50
6551	11.85
6502A	6.95
6522A	9.95
6532A	11.95
6545A	27.95
6551A	11.95

### 2 MHZ

### 3 MHZ

### 6502B

1771	16.95
1791	24.95
1793	26.95
1795	29.95
1797	49.95
2225	54.95
2793	54.95
2795	59.95
2797	59.95
2843	34.95
8272	39.95
UPD765	39.95
MB8876	29.95
MB8877	34.95
1691	17.95
2143	18.95

### 8000

8035	5.95
8039	5.95
INS-8060	17.

# TMM2016

## 2K x 8 STATIC \$4<sup>15</sup>

# HM6264

## 8K x 8 STATIC \$39<sup>95</sup>

200 ns

150 ns

### 74LS00

74LS00	.24	74LS173	.69
74LS01	.25	74LS174	.55
74LS02	.25	74LS175	.55
74LS03	.25	74LS181	2.15
74LS04	.24	74LS189	8.95
74LS05	.25	74LS190	.89
74LS08	.28	74LS191	.89
74LS09	.29	74LS192	.79
74LS10	.25	74LS193	.79
74LS11	.35	74LS194	.69
74LS12	.35	74LS195	.69
74LS13	.45	74LS196	.79
74LS14	.59	74LS197	.79
74LS15	.35	74LS221	.89
74LS20	.25	74LS240	.95
74LS21	.29	74LS241	.99
74LS22	.25	74LS242	.99
74LS26	.29	74LS243	.99
74LS27	.29	74LS244	1.29
74LS28	.35	74LS245	1.49
74LS30	.25	74LS247	.75
74LS32	.29	74LS248	.99
74LS33	.55	74LS249	.99
74LS37	.35	74LS251	.59
74LS38	.35	74LS253	.59
74LS40	.25	74LS257	.59
74LS42	.49	74LS258	.59
74LS47	.75	74LS259	2.75
74LS48	.75	74LS260	.59
74LS49	.75	74LS266	.55
74LS51	.25	74LS273	1.49
74LS54	.29	74LS275	3.35
74LS55	.29	74LS279	.49
74LS63	1.25	74LS280	1.98
74LS73	.39	74LS283	.69
74LS74	.35	74LS290	.89
74LS75	.39	74LS293	.89
74LS76	.39	74LS295	.99
74LS78	.49	74LS298	.89
74LS83	.60	74LS299	1.75
74LS85	.69	74LS323	3.50
74LS86	.39	74LS324	1.75
74LS90	.55	74LS352	1.29
74LS91	.89	74LS353	1.29
74LS92	.55	74LS363	1.35
74LS93	.55	74LS364	1.95
74LS95	.75	74LS365	.49
74LS96	.89	74LS366	.49
74LS107	.39	74LS367	.45
74LS109	.39	74LS368	.45
74LS112	.39	74LS373	1.39
74LS113	.39	74LS374	1.39
74LS114	.39	74LS375	.95
74LS122	.45	74LS377	1.39
74LS123	.79	74LS378	1.18
74LS124	2.90	74LS379	1.35
74LS125	.49	74LS385	3.90
74LS126	.49	74LS386	.45
74LS132	.59	74LS390	1.19
74LS133	.59	74LS393	1.19
74LS136	.39	74LS395	1.19
74LS137	.99	74LS399	1.49
74LS138	.55	74LS424	2.95
74LS139	.55	74LS447	.95
74LS145	1.20	74LS490	1.95
74LS147	2.49	74LS624	3.99
74LS148	1.35	74LS640	2.20
74LS151	.55	74LS645	2.20
74LS153	.55	74LS668	1.69
74LS154	1.90	74LS669	1.89
74LS155	.69	74LS670	1.49
74LS156	.69	74LS674	14.95
74LS157	.65	74LS682	3.20
74LS158	.59	74LS683	3.20
74LS160	.69	74LS684	3.20
74LS161	.65	74LS685	3.20
74LS162	.69	74LS688	2.40
74LS163	.65	74LS689	3.20
74LS164	.69	81LS95	1.49
74LS165	.95	81LS96	1.49
74LS166	1.95	81LS97	1.49
74LS168	1.75	81LS98	1.49
74LS169	1.75	25LS2521	2.80
74LS170	1.49	25LS2569	4.25

### 74S00

74S00	.32	74S124	2.75	74S197	1.49
74S02	.35	74S122	1.24	74S201	6.95
74S03	.35	74S133	.45	74S225	7.95
74S04	.35	74S134	.50	74S240	2.20
74S05	.35	74S135	.89	74S241	2.20
74S08	.35	74S138	.85	74S244	2.20
74S09	.40	74S139	.85	74S251	.95
74S10	.35	74S140	.55	74S253	.95
74S11	.35	74S151	.95	74S257	.95
74S15	.35	74S153	.95	74S258	.95
74S20	.35	74S157	.95	74S260	.79
74S22	.35	74S158	.95	74S273	2.45
74S30	.35	74S161	1.95	74S280	1.95
74S32	.40	74S162	1.95	74S287	1.90
74S37	.88	74S163	1.95	74S288	1.90
74S38	.85	74S168	3.95	74S289	6.89
74S40	.35	74S169	3.95	74S301	6.95
74S51	.35	74S174	.95	74S373	2.45
74S64	.40	74S175	.95	74S374	2.45
74S65	.40	74S181	3.95	74S387	1.95
74S74	.50	74S182	2.95	74S412	2.98
74S85	1.99	74S188	1.95	74S471	4.95
74S86	.50	74S189	6.95	74S472	4.95
74S112	.50	74S194	1.49	74S474	4.95
74S113	.50	74S195	1.49	74S570	2.95
74S114	.55	74S196	1.49	74S571	2.95

### VOLTAGE REGULATORS

7805T	.75	7905T	.85
78M05C	.35	7908T	.85
7808T	.75	7912T	.85
7812T	.75	7915T	.85
7815T	.75	7924T	.85
7824T	.75	7905K	1.49
7805K	1.39	7912K	1.49
7812K	1.39	7915K	1.49
7815K	1.39	7924K	1.49
7824K	1.39	79L05	.79
78L05	.69	79L12	.79
78L12	.69	79L15	.79
78L15	.69	LM323K	4.95
78H05K	9.95	UA78540	1.95
78H12K	9.95		

C, T = TO-220 K = TO-3  
L = TO-92

### SOUND CHIPS

76477	3.95	AY3-8910	12.95
76488	5.95	AY3-8912	12.95
76489	8.95	MC3340	1.49
		SSI-263	39.95

### 7400

7400	.19	74123	.49
7401	.19	74125	.45
7402	.19	74126	.45
7403	.19	74132	.45
7404	.19	74136	.50
7405	.25	74143	4.95
7406	.29	74145	.60
7407	.29	74147	1.75
7408	.24	74148	1.20
7409	.19	74150	1.35
7410	.19	74151	.55
7411	.25	74153	.55
7413	.35	74154	1.25
7414	.49	74155	.75
7416	.25	74157	.55
7417	.25	74159	1.65
7420	.19	74160	.85
7421	.35	74161	.69
7425	.29	74163	.69
7427	.29	74164	.85
7430	.19	74165	.85
7432	.29	74166	1.00
7437	.29	74167	2.95
7438	.29	74170	1.65
7442	.49	74173	.75
7445	.69	74174	.89
7446	.69	74175	.89
7447	.69	74177	.75
7448	.69	74181	2.25
7451	.23	74184	2.00
7473	.34	74185	2.00
7474	.33	74191	1.15
7475	.45	74192	.79
7476	.35	74193	.79
7482	.95	74194	.85
7483	.50	74195	.85
7485	.59	74197	.75
7486	.35	74198	1.35
7489	2.15	74221	1.35
7490	.35	74246	1.35
7492	.50	74247	1.25
7493	.35	74259	2.25
7495	.55	74273	1.95
7497	2.75	74276	1.25
74100	1.75	74279	.75
74107	.30	74366	.65
74109	.45	74367	.65
74116	1.55	74368	.65
74121	.29	74393	1.35
74122	.45		

### BYPASS CAPS

.01 UF DISC	100/6.00
.01 UF MONOL	100/12.00
.1 UF DISC	100/8.00
.1 UF MONOL	100/15.00

### INTERFACE

8T26	1.59
8T28	1.89
8T95	.89
8T96	.89
8T97	.89
8T98	.89
DM8131	2.95
DP8304	2.29
DS8833	2.25
DS8835	1.99
DS8836	.99
DS8837	1.65
DS8838	1.30

### CONNECTORS

RS232 Male	2.50
RS232 Female	3.25
RS232 Hood	1.25
S-100 ST	3.95

### EXAR

XR 2206	3.75
XR 2207	3.75
XR 2208	3.75
XR 2211	5.25
XR 2240	3.25

### INTERSIL

ICL7106	9.95
ICL7107	12.95
ICL7660	2.95
ICL8038	3.95
ICM7207A	5.99
ICM7208	15.95

### IC SOCKETS

8 pin ST	1.99	100
14 pin ST	.13	.11
16 pin ST	.17	.13
18 pin ST	.20	.18
20 pin ST	.29	.27
22 pin ST	.30	.27
24 pin ST	.30	.27
28 pin ST	.40	.32
40 pin ST	.49	.39
64 pin ST	4.25	call
ST = SOLDER TAIL		
8 pin WW	.59	.49
14 pin WW	.69	.52
16 pin WW	.69	.52
18 pin WW	.99	.90
20 pin WW	1.09	.98
22 pin WW	1.39	1.28
24 pin WW	1.49	1.35
28 pin WW	1.69	1.49
40 pin WW	2.91	.80
WW = WIREWRAP		
18 pin ZIF	8.95	call
24 pin ZIF	7.95	call
28 pin ZIF	8.95	call
ZIF = TEXTLOK (Zero Insertion Force)		

### EPROM ERASERS SPECTRONICS CORPORATION

PE-14	Timer	Capacity	Intensity	
		Chip	(uW/Cm <sup>2</sup> )	
PE-14		9	8,000	83.00
PE-14T	X	9	8,000	119.00
PE-24T	X	12	9,600	175.00
PL-265T	X	30	9,600	255.00
PR-125T	X	25	17,000	349.00
PR-320T	X	42	17,000	595.00

### DATA ACQUISITION

ADC0800	15.55	DAC0800	4.95
ADC0804	3.49	DAC0808	2.95
DAC0806	1.95	DAC1020	8.25
ADC0809	4.49	DAC1022	5.95
ADC0816	14.95	MC1408L6	1.95
ADC0817	9.95	MC1408L8	2.95

### LINEAR

LM301	.34	LM348	.99	LM567	.89	LM1812	8.25
LM301H	.79	LM350K	4.95	NE570	3.95	LM1830	3.50
LM307	.45	LM350T	4.60	NE571	2.95	LM1871	5.49
LM308	.69	LM358	.69	NE590	2.50	LM1872	5.49
LM308H	1.15	LM359	1.79	NE592	2.75	LM1877	3.25
LM309H	1.95	LM376	3.75	LM709	.59	LM1889	1.95
LM309K	1.25	LM377	1.95	LM710	.75	LM1896	1.75
LM310	1.75	LM378	2.50	LM711	.79	ULN2003	2.49
LM311	.64	LM379	4.50	LM723	.49	LM2877	2.05
LM311H	.69	LM380	.89	LM723H	.55	LM2878	2.25
LM312H	1.75	LM380B-8	1.10	LM733	.98	LM2900	.85
LM317K	3.95	LM381	1.60	LM741	.35	LM2901	1.00
LM317T	1.19	LM382	1.60	LM741N-14	.35	LM2917	

### TUSA

A WHOLE NEW WORLD OF TV VIEWING WITH TUSA'S NEW MODEL CVU-40, 40 CHANNEL CABLE TV CONVERTER. Receives all the EXTRA CABLE TV "MOBAND" & SUPERBAND CHANNELS on your UHF DIAL. Eliminates the need for renting or leasing. This system takes the "moband" and "superband" channels your TV, VCR or projector can't receive and converts them to standard UHF channels that any set can tune in.

**A MUST FOR VIDEO-TAPING FROM CABLE TV!** The system allows you to program both pay day TV decoder required and standard cable channels for taping on any VCR — while you are watching a different channel on your TV.

Now **\$24.95 ea.** PLUS POSTAGE

**NOW AVAILABLE**  
NEW TUNABLE DELUXE MODEL CVU-1000 **\$29.95 ea.**

### UHF TUNERS

45 MHz Output

Click Stop Detent Tuna model. Excellent for replacement use or experimental work building UHF receivers for ham or TV.

**WHILE THEY LAST**  
**\$3.95 ea.**  
10 or more **\$2.99 ea.**

### POPULAR IC's

TOP QUALITY NO SECONDS

TYPE	DESCRIPTION	1-9	10-UP
LM-300N	2 watt Audio Power Amp	\$1.08	\$ .88
LM-300N-3	Low Voltage Audio Amp	1.08	1.10
LM-505A	Phase Locked Loop	1.49	.99
LM-725A	Video Amp	1.89	.98
MC-1330	Video Detector	2.29	1.80
MC-1349	Video II Amp	2.08	1.56
MC-1350	Video III Amp	1.75	1.19
MC-1352	Video II Amp AGC	2.89	2.09
MC-1358	Audio II Amp	1.75	1.64
MC-1374P	R.F. Modulator	3.19	2.39
MC-1458	Dual Com. Op Amp	.88	.59
LM-1458A	Balanced Mod. Com. Modulator	1.79	1.34
LM-1806	Video Modulator	2.79	1.95

LINEAR VOLTAGE REGULATORS

LM-7805	5 Volt Positive Volt. Reg.	1.19	.89
LM-7808	8 Volt Positive Volt. Reg.	1.19	.89
LM-7812	12 Volt Positive Volt. Reg.	1.19	.89
LM-7815	15 Volt Positive Volt. Reg.	1.19	.89
LM-7818	18 Volt Positive Volt. Reg.	1.19	.89
LM-7824	24 Volt Positive Volt. Reg.	1.19	.89

THE ORIGINAL NE-564 IS NOW BACK IN STOCK!  
**\$3.50 Each** (No minimum order)

---

### WINDWARD 7-ELEMENT 75 OHM UHF YAGI ANTENNAS

12 db GAIN

Specify Channel

18db Gain **\$8.95 ea.**

24db Gain **\$12.95 ea.**

30 or more **\$7.95 ea.**

### SANYO UHF VARACTOR TUNERS

75 Ohm Input - 45 MHz Output

For Channels 14 - 83

Now! **\$16.95 EACH**

All units are brand new from Sanyo. Call for Quantity Price.

### POPULAR MICROWAVE PARTS

MRF-801	\$2.30
9-Up	\$1.89
MRF-811	3.45
9-Up	3.12
MBO-101	.58
25 Up	.50
CHIP CAPS - .001 mfd.	.30
250K50 (Common) MRF-802	11.90

---

### CABLE CONNECTOR

F-50 Male connector for RG-59/U cable. Complete with ferrule. Males with female "F" connectors.

100 for **\$10.50**  
206 ea.

### B&K AUTO/MANUAL RANGING MULTIMETER

MODEL 2807

**SPECIAL PRICE! \$94.00 ea.**

### Wahl Soldering Irons

MODEL 7470 Temperature-Adjustable Micro Soldering Station Compact 500° to 700°.

Perfect for micro circuits and fine tip. Grounded tip. Comes with 3/32" 3 Type 98 tip, winding sponge & stand.

3-year grounded power safety cord.

**\$39.95 ea.**

---

### QUALITY POWER TRANSFORMERS

24V CT, 500 mA.

\$3.19 ea. 10-48 **\$2.75 ea.**

50 or more **\$2.25 ea.**

For Larger Quantities Call

### COLORMAX 36 CHANNEL REMOTE CATV CONVERTER

MODEL CM352P

2 pc. REMOTE CONTROL

Now you can change channels or fine-tune your TV set by remote control up to 20 ft. away. This unit receives channels 2-13 plus mid & superband cable channels then outputs them on Channel 3.

100 for **\$10.50**  
206 ea.

### GEN. INSTRUMENT LC558 58 CHAN. CATV CONVERTER

Receive all the standard VHF, Mid and Superband cable TV channels. Provides excellent reception on any channels that are not being scrambled by your local cable company. Converts all cable channels to channel 3 for viewing on your regular TV set. Hand held wireless remote control allows remote channel change and TV set on/off control. Includes all manuals on any set. To receive the cable frequencies you must subscribe to your local cable company.

**\$99.95 \$84.00**  
100 for \$8.00

114001 DIODES  
15 for \$1.00. . . 100 for \$5.00

---

### ISO-TIP

Wahl Soldering Irons

MODEL 7800 Iso-Tip "80" Constant Soldering Iron Fastest recharging cordless soldering iron on the market. Same as above but recharges in ONE HOUR.

**\$39.95 ea.**

### PROJECT BOXES

Woodgrain

This box is 11 1/4" W, 4 1/4" H, 8 1/4" D with a removable aluminum Unishaded chassis. 11" W, 3 1/4" H, 8" D inside.

4 or more **\$12.50 ea.**

Pre-punched & Soldered **\$10.95 ea.**

For Larger Quantities Call

### Phone-A-Tenna

EXTENSIVE CORDLESS TELEPHONE RANGE UP TO 3 TIMES!

Here's the best quality, best working phone antenna on the market. Simple installation. Mounts outdoors. Does not need telephone warranty.

Introductory Special **\$37.95**

---

### ORDER NOW TOLL FREE

800-854-4655  
OUTSIDE CALIFORNIA  
714-635-5090  
INSIDE CALIFORNIA

## R.F. ELECTRONICS

1086-C N. STATE COLLEGE BLVD., DEPT. R  
ANAHEIM, CALIFORNIA 92806

OPEN TUES - FRI 10 to 6  
SAT 10 to 5  
CLOSED SUN & MON

PERSONAL CHECKS HELD FOR CLEARANCE — NO MINIMUM ORDER  
ALL PREPAID ORDERS 2 LBS OR LESS MUST INCLUDE \$2.50 SHIPPING & HANDLING — SHIPPED SAME DAY RECEIVED

## EDUCATION & INSTRUCTION

**EARN your university degree** through evaluation assessment, of existing education, experience, achievements. Call, (614) 863-1791, or write, **ASSESSMENT**, Box 13130F, Columbus, OH 43213.

**F.C.C. General Radiotelephone License.** Home study. Fast, Inexpensive! "Free" details. **COM-MAND**, D-91, Box 2223, San Francisco, CA 94126.

**PIEZOCERAMICS**—Basic motor/generator theory and applications \$12.00. **EARL R. HANSON**, 2305 Hudson St., Piscataway, NJ 08854.

## LEARN COMPUTER REPAIR

Train at home in spare time. No previous experience needed. Experts show you what to do, how to do it! Even beginners can learn how to repair small computers. Everything explained in easy-to-understand language. You learn by doing with tools and materials included in your course. Easy home-study plan shows how you can get in on ground floor of this fast-growing business. Send for free facts. No obligation. No salesman will call.

**ICS School of Computer Repair, Dept. DE074**  
Scranton, Pennsylvania 18515

Yes! I want to get into computer repair. Rush me free facts and color brochure.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City/State/Zip \_\_\_\_\_

## TS 1000/ZX81 INTERFACE

**UNLEASH** a powerful controller tailored to your needs! 16 analog inputs, 8 digital input/outputs. For schematics, software and detailed explanations, send \$9.95 to **R. DEVRIES**, 215 N. Pleasant St., Jackson, MI 49202.

## INVENTORS! IDEAS HAVE VALUE!

EVER think of an idea, forget it, and see it later on the market? Many people don't forget, act quickly, and are rewarded by American industry. Write down your idea! We offer free disclosure registration and initial consultation regarding your idea's potential value. Call or write without delay for your free information package. **AMERICAN INVENTORS CORPORATION**, 82 Broad Street, Dept. RE, Westfield, MA 01086, (413) 568-3753.

## DESCRAMBLERS-CABLE-UHF-TVRO

"SINEWAVE" TV descrambler, video and sound in TV or VCR. Complete kit and instruction manual ready to go \$114.95 plus \$6.10 S & H. Free flyer information. **CABLE SEARCHER**, P.O. Box 182, Carle Place Station, NY 11514.

## Satellite Descramblers

For West Star 5  
COMSTAR D4  
Movies Movies Movies

Send \$5.00 for information  
Modern Technology  
P.O. Box 419 D1  
Boston, Ma. 02186  
(617) 871-5838



# SKYFOX

State-of-the-Art Excellence

**SKYFOX DESIGN PERFORMANCE FEATURES:**

- Gain 55 db • Frequency 1.9-2.5 GHz
- Range 55 miles maximum • Tuning channels 2-6
- 20 inch Parabolic dish antenna • 60 ft. cable
- Cable adapters, mounting brackets and hardware included
- Illustrated instructions

Receive movies, special presentations and educational broadcasts—**ALL FREE**—with the SKYFOX deep fringe microwave receiver for homeowners outside the service area of microwave TV stations. SKYFOX receives up to a distance of 55 miles. From microwave transmitters located on buildings or towers in almost all medium and large size cities. SKYFOX does not receive Cable TV or satellite transmissions.

SKYFOX I \$ **79.95** (not pictured. 25 mile line of site)  
SKYFOX II \$ **109.95** (as shown. 55 mile line of site)

**ORDERS ONLY: Toll Free 1-800-323/1327**  
For Information Call: 1-312/564-0104

Visa, MasterCard accepted. COD, cash or Money Order only. When ordering by mail, Money Orders or Cashiers Checks only. Personal checks, wait 4 weeks for check clearance.

90 day warranty • Conditional money back guarantee

**S.E.I. Inc.** Available by Mail Order Only  
641 Academy Drive  
Northbrook, Illinois 60062

**CIRCLE 84 ON FREE INFORMATION CARD**

# DON'T BLAME THE SOFTWARE!

Our Isolators eliminate equipment interaction, clean up interference, curb damaging power line spikes and lightning bursts.



**ISO-1 ISOLATOR**  
3 isolated sockets; quality spike suppression; basic protection. . **\$81.95**

**ISO-3 SUPER-ISOLATOR**  
3 dual isolated sockets; suppressor; commercial protection. . . . **\$122.95**


**ISO-17 MAGNUM ISOLATOR**  
4 quad isolated sockets; suppressor; laboratory grade protection. . **\$213.95**

**ESP. Electronic Specialists, Inc.**  
171 S. Main, Natick, MA 01780 (617) 655-1532  
Toll Free Order Desk 1-800-225-4876  
MasterCard, VISA, American Express

**CIRCLE 6 ON FREE INFORMATION CARD**

# RAMSEY

# THE FIRST NAME IN ELECTRONIC TEST GEAR

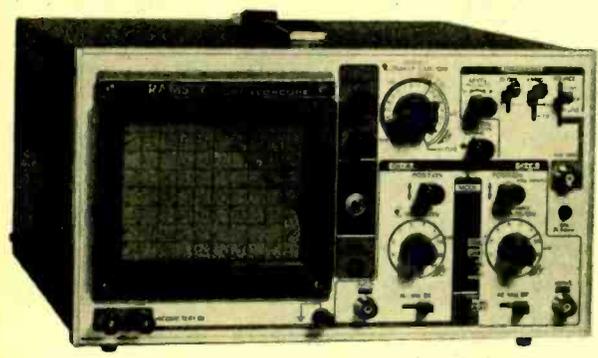

## NEW FROM RAMSEY-20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit that will allow you to easily test resistors, capacitors, digital circuits and diodes • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • high quality rectangular CRT • front panel trace rotator • Z axis • high sensitivity x-y mode • very low power consumption • regulated power supply • built-in calibrator • rock solid triggering • high quality hook-on probes

**\$399.95** high quality hook-on probes included



### RAMSEY D-1100 VOM-MULTITESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.


**\$19.95**  
test leads and battery included


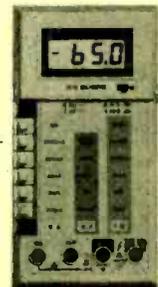
### RAMSEY D-2100 DIGITAL MULTITESTER

A compact easy to use unit designed to operate like a pro. Featuring • 3 1/2 digit LCD • low BAT. indicator • all range overload protection • overrange indication • auto-polarity • Transistor tester • dual-slope integration • vinyl carrying case

**\$54.95**  
hFE test leads, battery & vinyl carrying case included



### RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • In-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT. indicator

**\$59.95**  
test leads and battery included



### CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy

**\$119.95**  
wired includes AC adapter  
CT-70 kit ..... \$99.95  
BP-4 nicad pack ..... 8.95



### CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy

**\$149.95**  
wired includes AC adapter  
CT-90 kit ..... \$129.95  
OV-1 0.1 PPM oven timebase ..... 59.95  
BP-4 nicad pack ..... 8.95



### CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps

**\$169.95**  
wired includes AC adapter  
BP-4 nicad pack ..... 8.95



### CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy

**\$169.95**  
wired  
CT-50 kit ..... \$139.95  
RA-1 receiver adapter kit ..... 14.95



### DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity

**\$119.95**  
wired includes AC adapter  
DM-700 kit ..... \$99.95  
MP-1 probe set ..... 4.95



### PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01Hz resolution & built-in signal preamp/conditioner

**\$49.95**  
wired  
PS-2 kit ..... \$39.95



### PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for sniffing RF • ideal receiver/TV preamp

**\$44.95**  
wired includes AC adapter  
PR-2 kit ..... \$34.95



### PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity: 25mV @ 150 MHz • BNC connectors • drives any counter

**\$59.95**  
wired includes AC adapter  
PS-1B kit ..... \$49.95

- ACCESSORIES FOR RAMSEY COUNTERS**
- Telescopic whip antenna—BNC plug ..... \$ 8.95
  - High impedance probe, light loading ..... 16.95
  - Low pass probe, audio use ..... 16.95
  - Direct probe, general purpose use ..... 13.95
  - Tilt bail, for CT-70, 90, 125 ..... 3.95



**PHONE ORDERS CALL 716-586-3950**  
TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units



**RAMSEY ELECTRONICS, INC.**  
2575 Baird Rd.  
Penfield, N.Y. 14626

CIRCLE 79 ON FREE INFORMATION CARD

DT1050 Applications: Teaching aids, appliances, clocks, automotive, telecommunications, language translators, etc. The DT1050 is a standard DIGITALK™ chip encoded with 137 separate and useful words, 2 to 4 different sentence durations. The words and tones have been assigned discrete addresses, making it possible to output single words or words concatenated into phrases or even sentences. The "voice" output of the DT1050 is a highly intelligible male voice. Female children's voices can be synthesized also. The vocabulary is chosen so that it is applicable to many products and markets. The DT1050 consists of a Speech Processor Chip, MM54514 (40-pin) and two 2K Static ROMs MM52164S51R1 and MM52164S51R2 (24-pin) along with a Master Word List and a recommended schematic diagram on the application sheet.

DT1050 Digitalker™ Processor Chip \$34.95 ea. MM54514 Processor Chip \$14.95 ea.

DT1057 Expands the DT1050 vocabulary from 137 to over 260 words. Includes 2 ROMs and specs. Part No. DT1057 \$24.95 ea.



Table with columns: Part No., Pins, Function, Price. Lists various CMOS precision timer, stopwatch, and display chips.

3009 1983 Intersil Chip (1356p) \$9.95

74HC High Speed CMOS

Table with columns: Part No., Pins, Price. Lists various 74HC CMOS logic chips like inverters, buffers, and gates.

74C-C/MOS

Table with columns: Part No., Pins, Price. Lists various 74C-C/MOS logic chips.

DATA ACQUISITION

Table with columns: Part No., Pins, Price. Lists data acquisition chips like ADCs and DACs.

LINEAR

Table with columns: Part No., Pins, Price. Lists various linear ICs like op-amps and comparators.

WIRE WRAP SOCKETS (GOLD) LEVEL #3

Table with columns: Part No., Pins, Price. Lists wire wrap sockets in various configurations.

SOLDERTAL (GOLD) STANDARD

Table with columns: Part No., Pins, Price. Lists soldertal components like resistors and capacitors.

\$10.00 Minimum Order - U.S. Funds Only. California Residents Add 6% Sales Tax. Shipping - Add 5% plus \$1.50 Insurance. Send S.A.S.E. for Monthly Sales Flyer.

MICROPROCESSOR CHIPS

Table with columns: Part No., Pins, Price. Lists various microprocessor chips like the 8080, 8085, and 8088.

8080 SERIES

Table with columns: Part No., Pins, Price. Lists various 8080 series chips including ROMs and RAMs.

6500/6800/68000 SERIES

Table with columns: Part No., Pins, Price. Lists various 6500, 6800, and 68000 series chips.

8080 SERIES

Table with columns: Part No., Pins, Price. Lists various 8080 series chips including ROMs and RAMs.

DISK CONTROLLERS

Table with columns: Part No., Pins, Price. Lists disk controller chips.

SPECIAL FUNCTION

Table with columns: Part No., Pins, Price. Lists various special function chips.

LOW PROFILE (TIN) SOCKETS

Table with columns: Part No., Pins, Price. Lists low profile sockets in various configurations.

SOLDERTAL (GOLD) STANDARD

Table with columns: Part No., Pins, Price. Lists soldertal components like resistors and capacitors.

\$10.00 Minimum Order - U.S. Funds Only. California Residents Add 6% Sales Tax. Shipping - Add 5% plus \$1.50 Insurance. Send S.A.S.E. for Monthly Sales Flyer.



1355 SHOREWAY ROAD, BELMONT, CA 94002. 8/84 PHONE ORDERS WELCOME - (415) 592-8097 Telex: 1760-03

Table with columns: Part No., Pins, Price. Lists various 7400 series logic chips like inverters, buffers, and gates.

74LS

Table with columns: Part No., Pins, Price. Lists various 74LS series logic chips.

74S/PROMS\*

Table with columns: Part No., Pins, Price. Lists various 74S and PROM chips.

CA-LINEAR

Table with columns: Part No., Pins, Price. Lists various CA linear chips.

CD-CMOS

Table with columns: Part No., Pins, Price. Lists various CD-CMOS chips.

SOLDERTAL (GOLD) STANDARD


Table with columns: Part No., Pins, Price. Lists soldertal components like resistors and capacitors.

(More in Catalog)


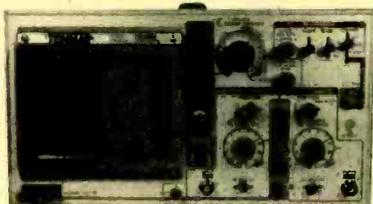
# TECHNICIANS!

We Have What You Need At  
The Prices You Want!



**TENMA**  
20MHz DUAL TRACE  
OSCILLOSCOPE **\$389.95**

Backed By Our 2 Year Warranty  
High Quality Hook-On Probes Included **#72-320**



**TENMA**  
DIGITAL  
MULTIMETER  
HFE TEST  
0.5" LCD display  
DC input impedance  
10MΩ

**\$39.80**  
**#72-050**

AGC FUSES  
STANDARD  
1 1/4x1/4

.25A	4A
.5A	5A
.75A	6A
1A	7A
1.5A	8A
2A	10A
2.5A	15A
3A	20A

**3.5¢**  
each  
(100-up pcs.)  
(NO MIXED QTY'S.)

36 PIN PARALLEL  
CONNECTOR



**\$3.95**  
**#83-310**

PANASONIC 2-4 HOUR  
VIDEO HEAD REPLACES  
PANASONIC PART #VEH-0070



**#32-160**  
**\$39.95**

## JAPANESE SEMICONDUCTORS

• D1341	1.92	• M515158L	2.49
• BUY69A	2.99	• STK0050	3.95
• HA1377	2.49	• 4116-200NS	1.38

(min. 10 pcs.)



**We Also Have...** a full line of: test equipment, computer accessories, telephone accessories, speakers, television parts, flybacks, yokes, switches, fuses, lamps, capacitors, resistors, cartridges, styli, wire, CATV equipment, and many more. **Over 4,500 items AT THE LOWEST PRICES AROUND!**

### Terms:

- \$10 minimum order. \$1.00 charge for orders under \$10.
- \$20 minimum charge card order.
- Orders shipped UPS C.O.D.
- Most orders shipped within 24 hours.
- Sales office open 8:30am to 6:00pm. Saturdays 10:00am to 3pm, EST.



**CALL TOLL FREE**  
**1-800-543-4330**

(in Ohio, 1-800-762-4315)

**mcm**  
ELECTRONICS  
THE ONLY  
ELECTRONICS  
PARTS COMPANY  
YOU'LL EVER  
NEED

858 East Congress Park Drive  
Centerville, Ohio 45459  
513-434-0031

**CALL OR WRITE TODAY**  
**FOR YOUR FREE 120 PAGE**  
**CATALOG! OVER 4500 ITEMS!**

PRICES SUBJECT TO CHANGE WITHOUT NOTICE



SOURCE NO. RE-1

CIRCLE 19 ON FREE INFORMATION CARD



DC TO OVER 1000MHz  
with any  
OSCILLOSCOPE

**HIGH PERFORMANCE SAMPLING SCOPE.** Litco GS-1 will convert, with a simple external connection, any DC scope to a high performance sampling scope. It will outperform for repetitive waveforms, any conventional scope regardless of price. Rise time 150ps max. Bandwidth DC to well over 1000 MHz. Useful to several gigahertz. Time base - 12 steps from 200ps to 1us/div. Noise or signal aberrations 10 mV max. Input signal range 10 Vp-p. 100 Vp-p with X10 probe attenuator sold below. Remote active sampling probe with 10 Meg, 1pF input. Stable trigger with slope and level controls. Manual scan for X-Y plotter operation. Quality construction with all BNC connectors. Internal fused power supplies.

**TIME DOMAIN REFLECTOMETER (TDR).** GS-1 can be combined with Litco ST-1 100ps, 2 Vp-p step generator to form a TDR - a powerful tool for analysis of UHF, VHF & microwave str-plines, coax cables, antennas & networks. **MICROPROCESSOR INTERFACE.** If X voltage is impressed on "SCAN IN" terminal of GS-1 (DC 1000KHz rate), Y voltage will appear on "VERT OUT" terminal if any waveform observed. ideal for digitizing of voltage, frequency, delay & risetime in microprocessor based test systems.

GS-1 Gigahertz sampler	\$349.00
PA-10 X10 probe tip attenuator	29.00
ST-1 100 ps 2 Vp-p step generator	195.00
IN-12 Booklet - Sampling, TDR, GS-1 & ST-1 theory & applications.	9.00

Shipping, handling & insurance 4.00  
Check or CDD NJ res. add 6% sales tax

LITCO SYSTEMS, INC. Box 90, E. Hanover, NJ 07936  
(717) 689-7835

**DON'T  
FORGET**



**USE  
YOUR  
READER  
SERVICE  
CARD**

### VIDEO REVERSER FOR THE TI-99

The picture fixer will invert the direct video signal from your computer. Allows you to use your TI-99 and other computers with a green phosphor monitor. Provides lit-up characters on a black background. Accepts standard polarity video- 5 volts to 5.0 volts P-P. Outputs normal or reverse video at 1.0 volt P-P into 75 ohms. **Complete kit \$19.95**



### BAR-GRAPH TACHOMETER

Add this sleek 40 segment tach to your dashboard instrument set. Measurement range is user adjustable (1K to 6K, 0 to 8K, etc.). Only 1.5 inches thick. can be mounted on the steering column without blocking view of the speedometer. Advanced circuitry provides fast, stable, and accurate readout. **Complete kit \$59.95.**



### AUTOMOTIVE VOLTMETER

Don't get stranded in the middle of no-where because of a dead battery. Build this expanded scale bar-graph voltmeter and keep an eye on the condition of your car or boats electrical system. Ten L.E.D.'s indicate battery voltage in .5 volt steps between 10.5 and 15 volts. Easy to build and very accurate. **Complete kit \$24.95.**



### OSCILLOSCOPE DELAYED SWEEP KIT

Upgrade your scope to lab quality. Contains a high quality video sync separator and trigger delay. Lock onto and expand any portion of a video waveform. Examine in detail the VITS waveforms. A must for all TV repair shops and scrambled video experimenters. Works with any triggered sweep scope that has external trigger input. **Complete kit \$54.95.**



### BROWNOUT ALARM


Save your voltage sensitive appliances (refrigerators, air-conditioners, etc.) from deadly brownouts. Sounds an alarm when the power line voltage drops to low or rises to high. Alarm trip points are adjustable. **Kit \$29.95.** With 10 amp power outlet for auto shut-off and four minute timeout delay (pictured) **\$39.95.**



**ELEPHANT ELECTRONICS INC**  
BOX 41770-R  
PHOENIX, AZ 85080

Arizona residents only must add 6% sales tax. Please add \$1.50 shipping and handling for each kit ordered. Overseas orders must add \$5.50 per kit for shipping, with payment made

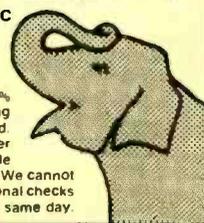in U.S. funds drawn on an American bank. We cannot accept charge card or C.O.D. orders. Personal checks held for clearance, money orders shipped same day.



CIRCLE 70 ON FREE INFORMATION CARD

# IT'S SMART TO BUILD WITH SHACK® PARTS

No Minimum Order!

Low Prices!

No Mail Order Delays!

## Power Transformers

120 VAC Primaries

Type	Volts	Current	Cat. No.	Each
Mini	6.3	300 mA	273-1384	2.59
Mini	12.6	300 mA	273-1385	2.79
Mini	25.2	300 mA	273-1386	3.49
Mini	12.6 CT	450 mA	273-1365	3.59
Mini	25.2 CT	450 mA	273-1366	3.99
Std.	6.3	1.2 A	273-050	3.79
Std.	12.6 CT	1.2 A	273-1505	3.99
Std.	25.2	1.2 A	273-1480	4.39
H-D	12.6 CT	3.0 A	273-1511	5.99
H-D	25.2 CT	2.0 A	273-1512	6.29
H-D	18.0 CT	2.0 A	273-1515	6.99

## Tantalum Capacitors

- 20% Tolerance
- Standard IC Pin Spacing




µF	WVDC	Cat. No.	Each
0.1	35	272-1432	.49
0.47	35	272-1433	.49
1.0	35	272-1434	.49
2.2	35	272-1435	.59
10	16	272-1436	.69
22	16	272-1437	.79

## Ceramic Disc Capacitors

Low As

**39¢** Pkg. of 2

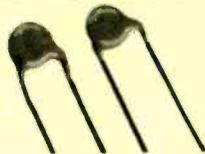

For RF, bypass and coupling. Hi-Q. Moistureproof coating. 50 WVDC.

pF	Cat. No.	Pkg. of 2	µF	Cat. No.	Pkg. of 2
4.7	272-120	.39	.001	272-126	.39
47	272-121	.39	.005	272-130	.39
100	272-123	.39	.01	272-131	.39
220	272-124	.39	.05	272-134	.49
470	272-125	.39	.1	272-135	.49

## Ultra-Compact SPST Reed Relays

**149** Each




Approximately 1" x 5/16". Pins for PC mounting. Contacts rated 1 amp at 125 VAC. Low-current coils.

5 VDC Coil. 275-232 ..... 1.49  
12 VDC Coil. 275-233 ..... 1.49

## Understanding Automation

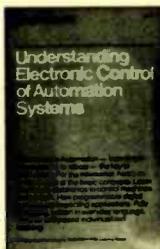**295**

Understanding Electronic Control of Automation Systems. This illustrated, 256-page book explains how electronics is being applied to industrial automation to increase productivity. 62-1387 ..... 2.95



## Low-Profile DIP Sockets

Quality non-wicking sockets for PC use. Low-resistance contacts.

Type	Cat. No.	Price
8-Pin	276-1995	2/.59
14-Pin	276-1999	2/.89
16-Pin	276-1998	2/.89

Type	Cat. No.	Each
18-Pin	276-1992	.49
20-Pin	276-1991	.59
24-Pin	276-1989	.79
28-Pin	276-1997	.89
40-Pin	276-1996	.99

## Computer/Game Connectors

Repair or make your own RS-232 cables and joystick extension cords and save!

Type	Positions	Cat. No.	Each
ID Card Edge	34	276-1564	4.95
Card Edge Socket	44	276-1551	2.99
No-Solder Sub-D Male	25	276-1559	4.99
No-Solder Sub-D Fern.	25	276-1565	4.99
Solder Sub-D Male	9	276-1537	1.99
Solder Sub-D Female	9	276-1538	2.49
Hood for Above	9	276-1539	1.99
Solder Sub-D Male	15	276-1527	2.49
Solder Sub-D Female	15	276-1528	3.49
Hood for Above	15	276-1529	1.99
Solder Sub-D Male	25	276-1547	2.99
Solder Sub-D Female	25	276-1548	3.99
Hood for Above	25	276-1549	1.99

## Communications ICs

Type	Cat. No.	Each
XR 2206 AFSK Generator	276-2336	5.95
XR 2211 Decoder/PLL	276-2337	5.95
MC1320 Video Detector	276-1757	1.99
MC1350 IF Amp With AGC	276-1758	1.99
MC1358/CA3065 FM Detector	276-1759	1.79

## 1/4-Watt, 5% Resistors

**39¢** Pkg. of 5

Ohms	Cat. No.	Ohms	Cat. No.
10	271-1301	10k	271-1335
100	271-1311	15k	271-1337
150	271-1312	22k	271-1339
220	271-1313	27k	271-1340
270	271-1314	33k	271-1341
330	271-1315	47k	271-1342
470	271-1317	68k	271-1345
1k	271-1321	100k	271-1347
1.8k	271-1324	220k	271-1350
2.2k	271-1325	470k	271-1354
3.3k	271-1328	1 meg	271-1356
4.7k	271-1330	10 meg	271-1365
6.8k	271-1333		

## Getting Started in Electronics

**249** By Forrest Mims III

Teaches the basics of modern electronics with an emphasis on integrated circuits. Easy-to-read text and diagrams. 128 pages. Already a "classic". 276-5003 ..... 2.49



## Replacement Transistors



Type	Cat. No.	Each	
2N1305	PNP	276-2007	1.19
MPS222A	NPN	276-2009	.79
PN2484	NPN	276-2010	.89
MPS3904	NPN	276-2016	.69
TIP31	NPN	276-2017	.99
TIP3055	NPN	276-2020	1.59
MPS2907	PNP	276-2023	.79
MJE34	PNP	276-2027	1.49
2N3053	NPN	276-2030	.99
MPS3638	PNP	276-2032	.79
TIP120	NPN	276-2068	1.29
2N3055	NPN	276-2041	1.99
2N4401	NPN	276-2058	.59
MPSA06	NPN	276-2059	.59
MPSA13	NPN	276-2060	.59
MPSA42	NPN	276-2061	.69
2SC945	NPN	276-2051	.79
2SC1308	NPN	276-2055	7.95
2N3819	N-FET	276-2035	.99
MPF102	N-FET	276-2062	.99

## 4000-Series CMOS ICs



With Pin-Out and Specs

Type	Cat. No.	Each
4001	276-2401	.99
4011	276-2411	.99
4013	276-2413	1.19
4017	276-2417	1.49
4049	276-2449	1.19
4066	276-2466	1.19

## TTL Digital ICs

In Stock at Low Prices!

Type	Cat. No.	Each
7400	276-1801	.89
7404	276-1802	.99
7408	276-1822	1.29
7447	276-1805	1.59
7490	276-1808	1.09

## Operational Amplifiers



Type	Cat. No.	Each
741 (Single)	276-007	.89
MC1458 (Dual)	276-038	.99
LM324 (Quad)	276-1711	1.29
TL082 (Dual)	276-1715	1.89
TL084 (Quad)	276-1714	2.99
LM3900 (Quad)	276-1713	1.39
LM339 (Quad)	276-1712	1.49

## Voltage Regulator ICs



Type	Adjustable	Cat. No.	Each
LM723	0 to 40 VDC	276-1740	.99
LM317T	1.2 to 37 VDC	276-1778	2.79

Type	Fixed Output	Cat. No.	Each
7805	+5 VDC	276-1770	1.59
7812	+12 VDC	276-1771	1.59
7815	+15 VDC	276-1772	1.59
7905	-5 VDC	276-1773	1.59
7912	-12 VDC	276-1774	1.59

A DIVISION OF TANDY CORPORATION

# Radio Shack®

Prices apply at participating Radio Shack stores and dealers

CIRCLE 51 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

OVER 8800 LOCATIONS WORLDWIDE

AUGUST 1984

107

**THE WM. B. ALLEN**

**WINNER'S DEAL**

**UP TO 25% OFF**



ON  
LARGEST FULL-LINE INVENTORY OF  
**HAND HELD METERS**

FROM THE LEADING MANUFACTURERS OF TEST EQUIPMENT

PLUS SPECIAL DISCOUNT PRICES ON SCOPES, INCLUDING HITACHI

SOAR SX220.....\$ 22	FLUKE 73.....\$ 75	BBC MA1M.....\$ 46
SOAR ME540.....\$ 44	FLUKE 75.....\$ 88	BBC M2031.....\$199
HICKOK LX304X.....\$ 94	FLUKE 77.....\$115	B&K 2806.....\$ 64
HITACHI 3510.....\$136	FLUKE 8022B.....\$125	KEITHLEY 128.....\$137

IN STOCK AND AVAILABLE NOW!

**WM. B. ALLEN SUPPLY**  
**ALLEN SQUARE**

300 BLOCK NORTH RAMPART, NEW ORLEANS, LA 70112  
LOUISIANA TOLL FREE 800 462-9520

CALL TOLL FREE FOR  
SAME DAY SHIPMENT

MANY MORE!



CIRCLE 56 ON FREE INFORMATION CARD

**MICROWAVE TV ANTENNA SYSTEMS**

Freq. 2.1 to 2.6 GHz · 34 db Gain +



- COMPLETE SYSTEMS  
(as Pictured)
- Commercial 40"  
Rod Style \$ 89.95
- Parabolic 20"  
Dish Style \$ 79.95

- COMPONENTS
- Down Converters  
(both types) \$ 34.95
- Power Supplies  
(12V to 16V) \$ 24.95
- Data Info (Plans) \$ 9.95

TWO YEAR WARRANTY  
PARTS & LABOR

CALL OR WRITE FOR  
KITS, PARTS, INDIVIDUAL  
COMPONENTS

We Repair All Types Down  
Converters & Power Supplies

**Phillips-Tech  
Electronics**  
1043 N. STADEM DR.  
TEMPE AZ. 85281  
(602) 967-6972

Special Quantity Pricing  
Dealers Wanted



CIRCLE 29 ON FREE INFORMATION CARD

**NORTH AMERICAN SOAR corporation**  
**PEN-STYLE DIGITAL MULTIMETER**

MODEL 3100  
GREAT PRICE **\$49.00**



**NEW!**

**Hand Held LCD Display - Fast One Hand Operation**

- SPECIFICATIONS:**  
 Display: LCD 3½ digits maximum reading of 1999/continuity beeper built-in  
 Range: Auto ranging  
 Polarity: Automatic no indication for positive polarity, minus sign for negative polarity  
 Overrange Indication: MBS 1 or -1 indication  
 Data Hold: Data hold in all ranges with hold switch on  
 Low Battery Indication: 'B' mark displayed when battery drops below operating voltage  
 Sampling: 2 Times/second  
 Power Supply: SR-44 battery (1.55V) X2  
 Power Consumption: 5.5mW  
 Size: 6" x 1½" LWH (less probe tips) Includes ½" and 2" probes

Add \$2.50 For Shipping  
STOCKING DISTRIBUTOR



**KCS ELECTRONICS CORPORATION**  
SEMICONDUCTOR PARTS AND PRODUCTS

1043 N. STADEM DR. (602) 967-6945  
TEMPE, AZ 85281

Call or Write for **FREE**  
Semiconductor Parts & Products Catalog

CIRCLE 83 ON FREE INFORMATION CARD



**NEW!**

**The complete  
BREADBOARDING  
SOURCE at the  
lowest prices  
ANYWHERE!**

### HB-0100 Buss Strip

Each buss strip contains four groups of labeled contact points (25 per group) providing multipoint distribution for Vcc, ground and signal paths. When interconnected, HB-0100's can simulate Micro-Processor's data or address busses simplifying ROM, RAM, UART, etc. to processor interconnects.

Competition Price: \$3.00!

**\$2.25**

HB-0100

### HB-1000 Socket

With HANDY sockets, breadboarding is easy because you always know where you're at. Each group of 5 contacts is labeled from 1-64 and each position within a group is labeled from a-j. With 64 groups of 5 contacts each you have more than enough room for infield and lab mock-ups that always come up when you least expect them.

Competition Price: \$12.50!

**\$9.95**

HB-1000

### HB-1210

One socket and one buss strip with self-adhesive backing and metal ground plate. Big nine 14-pin DIP capacity.

Competition Price: \$18.50!

**\$13.95**

HB-1210

### HB-1110

One socket and two buss strips with self-adhesive backing and metal ground plate. Big nine 14-pin DIP capacity.

Competition Price: \$15.49!

**\$11.95**

HB-1110



### HB-2112

A compact breadboard ideal for beginners, students, professionals and hobbyists. It's quick and easy to use and immediately becomes the most useful tool on your workbench. Includes: • 2 sockets • 1 buss strip • 2 binding posts and is mounted on an 8.7"x5.4" aluminum ground plate. 18 14-Pin DIP capacity.

**\$24.95**

HB-2112

**ORDER NOW!**

### HB-2313

Holds enough IC's to meet any quick-fix situation. Includes: • 2 sockets • 3 buss strips • 3 binding posts and is mounted on an 8.7"x5.9" aluminum ground plate. 18 14-Pin DIP capacity.

Competition Price: \$51.50!

**\$31.00**

HB-2313

### HB-3514

Ideal for light industrial as well as secondary level educational and hobbyist experimentation. Includes: • 3 sockets • 5 buss strips • 4 binding posts and is mounted on a 9.4"x7.7" aluminum ground plate. 27 14-Pin DIP capacity.

Competition Price: \$66.00!

**\$47.95**

HB-3514




### HB-4714

Largest HANDY breadboard available today. Complete PCB or even system mock-ups can easily fit on this breadboard. This high capacity, heavy duty board is a must for industrial users where time is money ... Great for advanced educational and hobbyist applications. Includes: • 4 sockets • 7 buss strips • 4 binding posts and is mounted on a 10.3"x9.5" aluminum ground plate. Giant 36 14-Pin DIP capacity.

Competition Price: \$89.00!

**\$63.95**

HB-4714

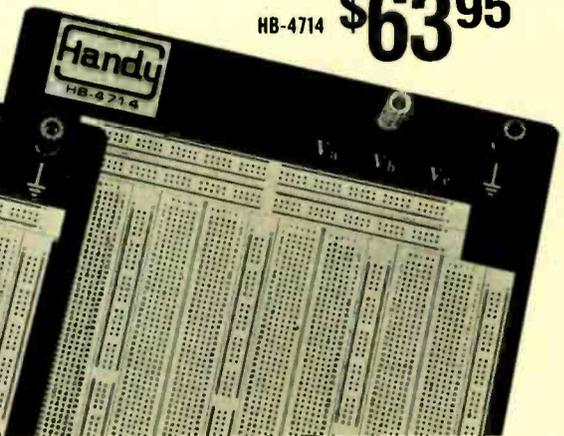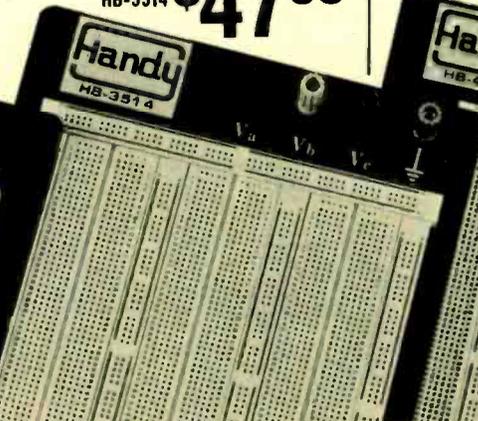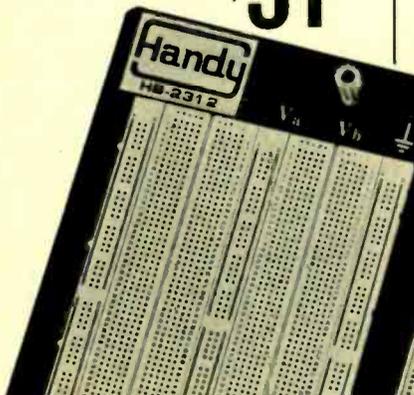

Mail Orders: Please add \$3 (Canada & Int'l add \$5) to cover cost of shipping/handling.  
Charge Cards: (Min. \$15). Please include Acct. No., Exp. Date, Bank No. (M/C only) and your signature.  
Checks: Drawn in U.S. Dollars on U.S. banks only.  
Conn Residents: Add 7% Sales Tax. Sorry! No C.O.D. orders.



To order... call 1-800-34-HANDY  
... charge with VISA, MasterCard or American Express.  
All items off-the-shelf for immediate shipment!

a division of RSP Electronics Corp.

7 Business Park Drive • P.O. Box 699 • Branford, CT 06405 • (203) 488-6603 • TWX: (910) 997-0684  
Easy Link Mail Box: 62537580 • CompuServe: 71346, 1070  
U.S. and Canadian Distributor inquiries welcomed.

CIRCLE 95 ON FREE INFORMATION CARD


[www.americanradiohistory.com](http://www.americanradiohistory.com)

# RADIO SHACK CORPORATION

In Me., N.H., Conn. Call 218-881-6074

**QUALITY** - Name brand products from nationally recognized manufacturers.  
**SERVICE** - Computerized order processing and inventory control.  
**SAVINGS** - Volume Discounts • OEM Quantity Pricing • Toll Free 800 Number

## SILICON RECTIFIERS ZENER DIODES

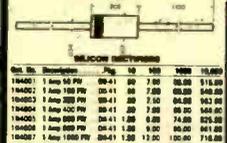


**1 AMP SILICON RECTIFIER**  
Part No. Description Price  
1A001 1 amp 50V Plastic 2.38 22.00 11.00  
1A002 1 amp 100V Plastic 2.38 22.00 11.00  
1A003 1 amp 200V Plastic 2.38 22.00 11.00  
1A004 1 amp 400V Plastic 2.38 22.00 11.00  
1A005 1 amp 600V Plastic 2.38 22.00 11.00  
1A006 1 amp 800V Plastic 2.38 22.00 11.00  
1A007 1 amp 1000V Plastic 2.38 22.00 11.00

## SILICON ZENER DIODES

Part No.	Description	Price
1Z001	3.3V 1/2W Zener	1.10
1Z002	4.7V 1/2W Zener	1.10
1Z003	6.2V 1/2W Zener	1.10
1Z004	8.2V 1/2W Zener	1.10
1Z005	10V 1/2W Zener	1.10
1Z006	15V 1/2W Zener	1.10
1Z007	20V 1/2W Zener	1.10
1Z008	30V 1/2W Zener	1.10
1Z009	40V 1/2W Zener	1.10
1Z010	50V 1/2W Zener	1.10
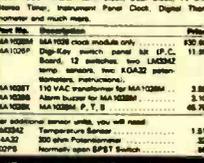
## National Semiconductor

**MA1026 Time Temp. Clock Module**  
Clock 7 Inch 4-Digit LED Display  
• 60/90/120 Hz Frequency Indicator  
• 12 or 24 Hour Display




**MA1026 Time Temp. Clock Module**  
Part No. Description Price  
MA1026 7" 4-Digit LED Display 11.95  
MA1027 7" 4-Digit LED Display 11.95  
MA1028 7" 4-Digit LED Display 11.95  
MA1029 7" 4-Digit LED Display 11.95  
MA1030 7" 4-Digit LED Display 11.95  
MA1031 7" 4-Digit LED Display 11.95  
MA1032 7" 4-Digit LED Display 11.95  
MA1033 7" 4-Digit LED Display 11.95  
MA1034 7" 4-Digit LED Display 11.95  
MA1035 7" 4-Digit LED Display 11.95

## Silicon Transistors

Part No.	Description	Price
2N2222	1.5W NPN Silicon	1.00
2N2904	1.5W PNP Silicon	1.00
2N3055	1.5W NPN Silicon	1.00
2N3638	1.5W PNP Silicon	1.00
2N4349	1.5W NPN Silicon	1.00
2N4350	1.5W PNP Silicon	1.00
2N4351	1.5W NPN Silicon	1.00
2N4352	1.5W PNP Silicon	1.00
2N4353	1.5W NPN Silicon	1.00
2N4354	1.5W PNP Silicon	1.00

## PR ROBINSON ENGINEERING

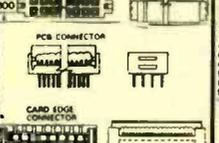

**PCB CONNECTOR**  
Part No. Description Price  
PCB101 10 Pin PCB Connector 1.00  
PCB102 15 Pin PCB Connector 1.00  
PCB103 20 Pin PCB Connector 1.00  
PCB104 25 Pin PCB Connector 1.00  
PCB105 30 Pin PCB Connector 1.00  
PCB106 35 Pin PCB Connector 1.00  
PCB107 40 Pin PCB Connector 1.00  
PCB108 45 Pin PCB Connector 1.00  
PCB109 50 Pin PCB Connector 1.00  
PCB110 55 Pin PCB Connector 1.00

## alpha wire cable tubing

Part No.	Description	Price
AL101	1/8" Dia. 100' Length	1.00
AL102	1/4" Dia. 100' Length	1.00
AL103	3/8" Dia. 100' Length	1.00
AL104	1/2" Dia. 100' Length	1.00
AL105	5/8" Dia. 100' Length	1.00
AL106	3/4" Dia. 100' Length	1.00
AL107	7/8" Dia. 100' Length	1.00
AL108	1" Dia. 100' Length	1.00
AL109	1 1/8" Dia. 100' Length	1.00
AL110	1 1/4" Dia. 100' Length	1.00

## Standard Assembly Styles

Part No.	Description	Price
AS101	1/2" Dia. 100' Length	1.00
AS102	3/4" Dia. 100' Length	1.00
AS103	1" Dia. 100' Length	1.00
AS104	1 1/4" Dia. 100' Length	1.00
AS105	1 1/2" Dia. 100' Length	1.00
AS106	1 3/4" Dia. 100' Length	1.00
AS107	2" Dia. 100' Length	1.00
AS108	2 1/2" Dia. 100' Length	1.00
AS109	3" Dia. 100' Length	1.00
AS110	3 1/2" Dia. 100' Length	1.00

## Bridge Rectifiers

Part No.	Description	Price
BR101	1A 50V 100mA	1.00
BR102	1A 100V 100mA	1.00
BR103	1A 200V 100mA	1.00
BR104	1A 400V 100mA	1.00
BR105	1A 600V 100mA	1.00
BR106	1A 800V 100mA	1.00
BR107	1A 1000V 100mA	1.00

## DIGI-KEY



**DIGI-KEY**  
Part No. Description Price  
DK101 10 Pin Connector 1.00  
DK102 15 Pin Connector 1.00  
DK103 20 Pin Connector 1.00  
DK104 25 Pin Connector 1.00  
DK105 30 Pin Connector 1.00  
DK106 35 Pin Connector 1.00  
DK107 40 Pin Connector 1.00  
DK108 45 Pin Connector 1.00  
DK109 50 Pin Connector 1.00  
DK110 55 Pin Connector 1.00

## Carbon Film Resistors

Part No.	Description	Price
CR101	100 Ohm 1/4W	1.00
CR102	200 Ohm 1/4W	1.00
CR103	500 Ohm 1/4W	1.00
CR104	1K Ohm 1/4W	1.00
CR105	2K Ohm 1/4W	1.00
CR106	5K Ohm 1/4W	1.00
CR107	10K Ohm 1/4W	1.00
CR108	20K Ohm 1/4W	1.00
CR109	50K Ohm 1/4W	1.00
CR110	100K Ohm 1/4W	1.00

## IC Chips

Part No.	Description	Price
IC101	74181 Hex Inverter	1.00
IC102	74182 Hex Buffer	1.00
IC103	74183 Hex Inverter	1.00
IC104	74184 Hex Buffer	1.00
IC105	74185 Hex Inverter	1.00
IC106	74186 Hex Buffer	1.00
IC107	74187 Hex Inverter	1.00
IC108	74188 Hex Buffer	1.00
IC109	74189 Hex Inverter	1.00
IC110	74190 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC201	74191 Hex Inverter	1.00
IC202	74192 Hex Buffer	1.00
IC203	74193 Hex Inverter	1.00
IC204	74194 Hex Buffer	1.00
IC205	74195 Hex Inverter	1.00
IC206	74196 Hex Buffer	1.00
IC207	74197 Hex Inverter	1.00
IC208	74198 Hex Buffer	1.00
IC209	74199 Hex Inverter	1.00
IC210	74200 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC301	74201 Hex Inverter	1.00
IC302	74202 Hex Buffer	1.00
IC303	74203 Hex Inverter	1.00
IC304	74204 Hex Buffer	1.00
IC305	74205 Hex Inverter	1.00
IC306	74206 Hex Buffer	1.00
IC307	74207 Hex Inverter	1.00
IC308	74208 Hex Buffer	1.00
IC309	74209 Hex Inverter	1.00
IC310	74210 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC401	74211 Hex Inverter	1.00
IC402	74212 Hex Buffer	1.00
IC403	74213 Hex Inverter	1.00
IC404	74214 Hex Buffer	1.00
IC405	74215 Hex Inverter	1.00
IC406	74216 Hex Buffer	1.00
IC407	74217 Hex Inverter	1.00
IC408	74218 Hex Buffer	1.00
IC409	74219 Hex Inverter	1.00
IC410	74220 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC501	74221 Hex Inverter	1.00
IC502	74222 Hex Buffer	1.00
IC503	74223 Hex Inverter	1.00
IC504	74224 Hex Buffer	1.00
IC505	74225 Hex Inverter	1.00
IC506	74226 Hex Buffer	1.00
IC507	74227 Hex Inverter	1.00
IC508	74228 Hex Buffer	1.00
IC509	74229 Hex Inverter	1.00
IC510	74230 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC601	74231 Hex Inverter	1.00
IC602	74232 Hex Buffer	1.00
IC603	74233 Hex Inverter	1.00
IC604	74234 Hex Buffer	1.00
IC605	74235 Hex Inverter	1.00
IC606	74236 Hex Buffer	1.00
IC607	74237 Hex Inverter	1.00
IC608	74238 Hex Buffer	1.00
IC609	74239 Hex Inverter	1.00
IC610	74240 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC701	74241 Hex Inverter	1.00
IC702	74242 Hex Buffer	1.00
IC703	74243 Hex Inverter	1.00
IC704	74244 Hex Buffer	1.00
IC705	74245 Hex Inverter	1.00
IC706	74246 Hex Buffer	1.00
IC707	74247 Hex Inverter	1.00
IC708	74248 Hex Buffer	1.00
IC709	74249 Hex Inverter	1.00
IC710	74250 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC801	74251 Hex Inverter	1.00
IC802	74252 Hex Buffer	1.00
IC803	74253 Hex Inverter	1.00
IC804	74254 Hex Buffer	1.00
IC805	74255 Hex Inverter	1.00
IC806	74256 Hex Buffer	1.00
IC807	74257 Hex Inverter	1.00
IC808	74258 Hex Buffer	1.00
IC809	74259 Hex Inverter	1.00
IC810	74260 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC901	74261 Hex Inverter	1.00
IC902	74262 Hex Buffer	1.00
IC903	74263 Hex Inverter	1.00
IC904	74264 Hex Buffer	1.00
IC905	74265 Hex Inverter	1.00
IC906	74266 Hex Buffer	1.00
IC907	74267 Hex Inverter	1.00
IC908	74268 Hex Buffer	1.00
IC909	74269 Hex Inverter	1.00
IC910	74270 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1001	74271 Hex Inverter	1.00
IC1002	74272 Hex Buffer	1.00
IC1003	74273 Hex Inverter	1.00
IC1004	74274 Hex Buffer	1.00
IC1005	74275 Hex Inverter	1.00
IC1006	74276 Hex Buffer	1.00
IC1007	74277 Hex Inverter	1.00
IC1008	74278 Hex Buffer	1.00
IC1009	74279 Hex Inverter	1.00
IC1010	74280 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1011	74281 Hex Inverter	1.00
IC1012	74282 Hex Buffer	1.00
IC1013	74283 Hex Inverter	1.00
IC1014	74284 Hex Buffer	1.00
IC1015	74285 Hex Inverter	1.00
IC1016	74286 Hex Buffer	1.00
IC1017	74287 Hex Inverter	1.00
IC1018	74288 Hex Buffer	1.00
IC1019	74289 Hex Inverter	1.00
IC1020	74290 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1021	74291 Hex Inverter	1.00
IC1022	74292 Hex Buffer	1.00
IC1023	74293 Hex Inverter	1.00
IC1024	74294 Hex Buffer	1.00
IC1025	74295 Hex Inverter	1.00
IC1026	74296 Hex Buffer	1.00
IC1027	74297 Hex Inverter	1.00
IC1028	74298 Hex Buffer	1.00
IC1029	74299 Hex Inverter	1.00
IC1030	74300 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1031	74301 Hex Inverter	1.00
IC1032	74302 Hex Buffer	1.00
IC1033	74303 Hex Inverter	1.00
IC1034	74304 Hex Buffer	1.00
IC1035	74305 Hex Inverter	1.00
IC1036	74306 Hex Buffer	1.00
IC1037	74307 Hex Inverter	1.00
IC1038	74308 Hex Buffer	1.00
IC1039	74309 Hex Inverter	1.00
IC1040	74310 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1041	74311 Hex Inverter	1.00
IC1042	74312 Hex Buffer	1.00
IC1043	74313 Hex Inverter	1.00
IC1044	74314 Hex Buffer	1.00
IC1045	74315 Hex Inverter	1.00
IC1046	74316 Hex Buffer	1.00
IC1047	74317 Hex Inverter	1.00
IC1048	74318 Hex Buffer	1.00
IC1049	74319 Hex Inverter	1.00
IC1050	74320 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1051	74321 Hex Inverter	1.00
IC1052	74322 Hex Buffer	1.00
IC1053	74323 Hex Inverter	1.00
IC1054	74324 Hex Buffer	1.00
IC1055	74325 Hex Inverter	1.00
IC1056	74326 Hex Buffer	1.00
IC1057	74327 Hex Inverter	1.00
IC1058	74328 Hex Buffer	1.00
IC1059	74329 Hex Inverter	1.00
IC1060	74330 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1061	74331 Hex Inverter	1.00
IC1062	74332 Hex Buffer	1.00
IC1063	74333 Hex Inverter	1.00
IC1064	74334 Hex Buffer	1.00
IC1065	74335 Hex Inverter	1.00
IC1066	74336 Hex Buffer	1.00
IC1067	74337 Hex Inverter	1.00
IC1068	74338 Hex Buffer	1.00
IC1069	74339 Hex Inverter	1.00
IC1070	74340 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1071	74341 Hex Inverter	1.00
IC1072	74342 Hex Buffer	1.00
IC1073	74343 Hex Inverter	1.00
IC1074	74344 Hex Buffer	1.00
IC1075	74345 Hex Inverter	1.00
IC1076	74346 Hex Buffer	1.00
IC1077	74347 Hex Inverter	1.00
IC1078	74348 Hex Buffer	1.00
IC1079	74349 Hex Inverter	1.00
IC1080	74350 Hex Buffer	1.00

## IC Chips

Part No.	Description	Price
IC1081	74351 Hex Inverter	1.00
IC1082	74352 Hex Buffer	1.00
IC1083	74353 Hex Inverter	1.00
IC10		

# DIGI-KEY: 800-346-5144

IN Mo., Ar., HI, Call 218-881-6674

**NATIONAL SEMICONDUCTOR • PANASONIC • QUALITY - Name brand products from nationally recognized manufacturers.**  
**DAVID • CHEMVAR • ATLANTIC DIODES • N. RIVERS • MOLEX • AVIAD • E. T. J. OX MACHINE • UNGAR • GC CHEMICALS • A. NATIONAL SEMICONDUCTOR • PANASONIC • SAVINGS - Volume Discounts • OEM Quantity Pricing • Toll Free 800 Number**  
**SERVICE - Computerized order processing and inventory control.**  
**CHEMICALS • ARIES • FLESSEY • MOLEX • E. MACHINE • DIAMOND TOOL • UNGAR • GC CHEMICALS • ARIES • INSTRUMENTS • DAG • A. PRODUCTS • A. DIAMOND TOOL • UNGAR • GC CHEMICALS • ARIES • CHEMICALS • ARIES • FLESSEY • MOLEX • E.**

**DISCOUNT COMPARE PRICES** **DISCOUNT COMPARE PRICES**

## INTEGRATED CIRCUITS

Part No.	Pin						
7400	14	7400	14	7400	14	7400	14
7401	14	7401	14	7401	14	7401	14
7402	14	7402	14	7402	14	7402	14
7500	14	7500	14	7500	14	7500	14

## TEXAS INSTRUMENTS I.C. SOCKETS

Body - 84 V-Molded polymer with Copper Alloy contacts.  
 All components standard IC leads up to 0.04" dia. This is the only socket which is designed and oriented to the IC lead to grasp the broad "T" of the lead, allowing the lead to slide in and "lock" tight. No crimping. Sockets are available in 14, 16, 18, 20, 22, 24, 26, 28, 30, 32, 34, 36, 38, 40, 42, 44, 46, 48, 50, 52, 54, 56, 58, 60, 62, 64, 66, 68, 70, 72, 74, 76, 78, 80, 82, 84, 86, 88, 90, 92, 94, 96, 98, 100 pins.

## SOLDER TAIL DIP SOCKETS

• Single leads  
 • Low profile  
 • YOUR CHOICE TYP OR GOLD  
 • 100% guaranteed with your purchase

**14 PIN PLATED SOLDER TAIL** (Pin 1 - 14)  
 Part No. Description Price  
 CS14 14 pin solder tail, tin 1.15 1.00  
 CS14 14 pin solder tail, gold 1.15 1.00  
 CS18 18 pin solder tail, tin 1.15 1.00  
 CS18 18 pin solder tail, gold 1.15 1.00  
 CS22 22 pin solder tail, tin 1.15 1.00  
 CS22 22 pin solder tail, gold 1.15 1.00  
 CS26 26 pin solder tail, tin 1.15 1.00  
 CS26 26 pin solder tail, gold 1.15 1.00  
 CS30 30 pin solder tail, tin 1.15 1.00  
 CS30 30 pin solder tail, gold 1.15 1.00

**GOLD LEAD SOLDER TAIL** (Pin 1 - 14)  
 Part No. Description Price  
 CS14 14 pin solder tail, gold 1.15 1.00  
 CS18 18 pin solder tail, gold 1.15 1.00  
 CS22 22 pin solder tail, gold 1.15 1.00  
 CS26 26 pin solder tail, gold 1.15 1.00  
 CS30 30 pin solder tail, gold 1.15 1.00

**WIRE WRAP DIP SOCKETS**  
 • Standard profiting and processing capabilities  
 • Underneath lead length  
 • Wire-wrap pins lead to wire position of IC pins  
 • 100% guaranteed with your purchase

**14 PIN PLATED WIRE WRAP** (Pin 1 - 14)  
 Part No. Description Price  
 CW14 14 pin wire wrap, tin 1.15 1.00  
 CW14 14 pin wire wrap, gold 1.15 1.00  
 CW18 18 pin wire wrap, tin 1.15 1.00  
 CW18 18 pin wire wrap, gold 1.15 1.00  
 CW22 22 pin wire wrap, tin 1.15 1.00  
 CW22 22 pin wire wrap, gold 1.15 1.00  
 CW26 26 pin wire wrap, tin 1.15 1.00  
 CW26 26 pin wire wrap, gold 1.15 1.00  
 CW30 30 pin wire wrap, tin 1.15 1.00  
 CW30 30 pin wire wrap, gold 1.15 1.00

**GOLD LEAD WIRE WRAP** (Pin 1 - 14)  
 Part No. Description Price  
 CW14 14 pin wire wrap, gold 1.15 1.00  
 CW18 18 pin wire wrap, gold 1.15 1.00  
 CW22 22 pin wire wrap, gold 1.15 1.00  
 CW26 26 pin wire wrap, gold 1.15 1.00  
 CW30 30 pin wire wrap, gold 1.15 1.00

## TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS

Part No. Description Price  
 CE14 14 pin edge board, tin 1.15 1.00  
 CE14 14 pin edge board, gold 1.15 1.00  
 CE18 18 pin edge board, tin 1.15 1.00  
 CE18 18 pin edge board, gold 1.15 1.00  
 CE22 22 pin edge board, tin 1.15 1.00  
 CE22 22 pin edge board, gold 1.15 1.00  
 CE26 26 pin edge board, tin 1.15 1.00  
 CE26 26 pin edge board, gold 1.15 1.00  
 CE30 30 pin edge board, tin 1.15 1.00  
 CE30 30 pin edge board, gold 1.15 1.00

## DISC CAPACITORS

**NEW KIT 2W KIT**  
 CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NEW KIT 2W KIT

CAT. NO. 24  
 Price \$54.95

## NSC Data Books

Part No. Description Price  
 NSC1 14 pin edge board, tin 1.15 1.00  
 NSC1 14 pin edge board, gold 1.15 1.00  
 NSC18 18 pin edge board, tin 1.15 1.00  
 NSC18 18 pin edge board, gold 1.15 1.00  
 NSC22 22 pin edge board, tin 1.15 1.00  
 NSC22 22 pin edge board, gold 1.15 1.00  
 NSC26 26 pin edge board, tin 1.15 1.00  
 NSC26 26 pin edge board, gold 1.15 1.00  
 NSC30 30 pin edge board, tin 1.15 1.00  
 NSC30 30 pin edge board, gold 1.15 1.00

## MOLEX I.C. SOCKET PINS

Part No. Description Price  
 M1 14 pin edge board, tin 1.15 1.00  
 M1 14 pin edge board, gold 1.15 1.00  
 M18 18 pin edge board, tin 1.15 1.00  
 M18 18 pin edge board, gold 1.15 1.00  
 M22 22 pin edge board, tin 1.15 1.00  
 M22 22 pin edge board, gold 1.15 1.00  
 M26 26 pin edge board, tin 1.15 1.00  
 M26 26 pin edge board, gold 1.15 1.00  
 M30 30 pin edge board, tin 1.15 1.00  
 M30 30 pin edge board, gold 1.15 1.00

## SUPER STRIPS

Part No. Description Price  
 SS1 14 pin edge board, tin 1.15 1.00  
 SS1 14 pin edge board, gold 1.15 1.00  
 SS18 18 pin edge board, tin 1.15 1.00  
 SS18 18 pin edge board, gold 1.15 1.00  
 SS22 22 pin edge board, tin 1.15 1.00  
 SS22 22 pin edge board, gold 1.15 1.00  
 SS26 26 pin edge board, tin 1.15 1.00  
 SS26 26 pin edge board, gold 1.15 1.00  
 SS30 30 pin edge board, tin 1.15 1.00  
 SS30 30 pin edge board, gold 1.15 1.00

## POWERACE

Part No. Description Price  
 P1 14 pin edge board, tin 1.15 1.00  
 P1 14 pin edge board, gold 1.15 1.00  
 P18 18 pin edge board, tin 1.15 1.00  
 P18 18 pin edge board, gold 1.15 1.00  
 P22 22 pin edge board, tin 1.15 1.00  
 P22 22 pin edge board, gold 1.15 1.00  
 P26 26 pin edge board, tin 1.15 1.00  
 P26 26 pin edge board, gold 1.15 1.00  
 P30 30 pin edge board, tin 1.15 1.00  
 P30 30 pin edge board, gold 1.15 1.00

## DIGI-KEY



# FOR FREE INFORMATION USE THESE POST-PAID CARDS


1 Print your name, address and Zip Code on one of the attached postage-paid cards.

2 Circle the number (or numbers) on the card that matches the number at the bottom of each ad or editorial item that you want information on. Advertisers' free information numbers also appear in the ad index on the facing page.

3 Mail the card. It's Postage-Paid.

The bottom free-information card is a BUSINESS/PROFESSIONAL CARD. If you use this card you MUST complete the spaces for Company Name, Title, and Phone Number. If these are not filled in, the card will not be processed.

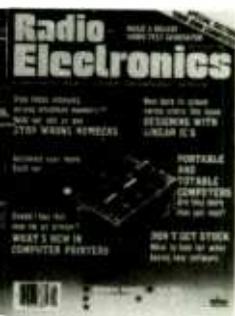**NOTE:** Use the postcard address or Free Product Information only. Address all editorial inquiries to Editor, Radio-Electronics, 200 Park Ave. South, New York, NY 10003.



**Radio-Electronics**  
Your favorite electronics magazine and still getting better

## POSTAGE-PAID FREE INFORMATION CARD



3-884

Name (please print) \_\_\_\_\_ Title \_\_\_\_\_  
 Company Name (if applicable) \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Unclear or incomplete mailing info will prevent our processing this request.

- 2  Please send me 12 issues of RADIO-ELECTRONICS for \$14.97 and bill me. (Canada \$17.97—US Funds only)
- 4  Please send me 4 issues of HANDS-ON-ELECTRONICS for \$10.00 and bill me. (Canada \$13.00—US Funds only)

25	49	73	97	121	145	169	193	217	241	265	289	313	337	361	
26	50	74	98	122	146	170	194	218	242	266	290	314	338	362	
27	51	75	99	123	147	171	195	219	243	267	291	315	339	363	
28	52	76	100	124	148	172	196	220	244	268	292	316	340	364	
5	29	53	77	101	125	149	173	197	221	245	269	293	317	341	365
6	30	54	78	102	126	150	174	198	222	246	270	294	318	342	366
7	31	55	79	103	127	151	175	199	223	247	271	295	319	343	367
8	32	56	80	104	128	152	176	200	224	248	272	296	320	344	368
9	33	57	81	105	129	153	177	201	225	249	273	297	321	345	369
10	34	58	82	106	130	154	178	202	226	250	274	298	322	346	370
11	35	59	83	107	131	155	179	203	227	251	275	299	323	347	371
12	36	60	84	108	132	156	180	204	228	252	276	300	324	348	372
13	37	61	85	109	133	157	181	205	229	253	277	301	325	349	373
14	38	62	86	110	134	158	182	206	230	254	278	302	326	350	374
15	39	63	87	111	135	159	183	207	231	255	279	303	327	351	375
16	40	64	88	112	136	160	184	208	232	256	280	304	328	352	376
17	41	65	89	113	137	161	185	209	233	257	281	305	329	353	377
18	42	66	90	114	138	162	186	210	234	258	282	306	330	354	378
19	43	67	91	115	139	163	187	211	235	259	283	307	331	355	379
20	44	68	92	116	140	164	188	212	236	260	284	308	332	356	380
21	45	69	93	117	141	165	189	213	237	261	285	309	333	357	381
22	46	70	94	118	142	166	190	214	238	262	286	310	334	358	382
23	47	71	95	119	143	167	191	215	239	263	287	311	335	359	383
24	48	72	96	120	144	168	192	216	240	264	288	312	336	360	384

## FREE INFORMATION CARD

VOID after October 31, 1984  
Allow 6-8 weeks for delivery of first issue

## BUSINESS REPLY CARD

FIRST CLASS PERMIT NO. 597 BOULDER, COLORADO

**Radio-Electronics**  
 SUBSCRIPTION SERVICE  
 P.O. Box 2520  
 BOULDER, COLORADO 80321

NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

## BUSINESS/PROFESSIONAL FREE INFO CARD



4-884

Name \_\_\_\_\_ Title \_\_\_\_\_  
 Company \_\_\_\_\_ Phone ( ) \_\_\_\_\_  
 Dept./MS \_\_\_\_\_  
 Company Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


Unclear or incomplete mailing info will prevent our processing this request.

- 2  Please send me 12 issues of RADIO-ELECTRONICS for \$14.97 and bill me. (Canada \$17.97—US Funds only)
- 4  Please send me 4 issues of HANDS-ON-ELECTRONICS for \$10.00 and bill me. (Canada \$13.00—US Funds only)

25	49	73	97	121	145	169	193	217	241	265	289	313	337	361	
26	50	74	98	122	146	170	194	218	242	266	290	314	338	362	
27	51	75	99	123	147	171	195	219	243	267	291	315	339	363	
28	52	76	100	124	148	172	196	220	244	268	292	316	340	364	
5	29	53	77	101	125	149	173	197	221	245	269	293	317	341	365
6	30	54	78	102	126	150	174	198	222	246	270	294	318	342	366
7	31	55	79	103	127	151	175	199	223	247	271	295	319	343	367
8	32	56	80	104	128	152	176	200	224	248	272	296	320	344	368
9	33	57	81	105	129	153	177	201	225	249	273	297	321	345	369
10	34	58	82	106	130	154	178	202	226	250	274	298	322	346	370
11	35	59	83	107	131	155	179	203	227	251	275	299	323	347	371
12	36	60	84	108	132	156	180	204	228	252	276	300	324	348	372
13	37	61	85	109	133	157	181	205	229	253	277	301	325	349	373
14	38	62	86	110	134	158	182	206	230	254	278	302	326	350	374
15	39	63	87	111	135	159	183	207	231	255	279	303	327	351	375
16	40	64	88	112	136	160	184	208	232	256	280	304	328	352	376
17	41	65	89	113	137	161	185	209	233	257	281	305	329	353	377
18	42	66	90	114	138	162	186	210	234	258	282	306	330	354	378
19	43	67	91	115	139	163	187	211	235	259	283	307	331	355	379
20	44	68	92	116	140	164	188	212	236	260	284	308	332	356	380
21	45	69	93	117	141	165	189	213	237	261	285	309	333	357	381
22	46	70	94	118	142	166	190	214	238	262	286	310	334	358	382
23	47	71	95	119	143	167	191	215	239	263	287	311	335	359	383
24	48	72	96	120	144	168	192	216	240	264	288	312	336	360	384
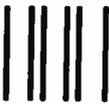
## FREE INFORMATION CARD

VOID after October 31, 1984  
Allow 6-8 weeks for delivery of first issue



NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY CARD**  
FIRST CLASS PERMIT NO. 27346 PHILADELPHIA, PA.

POSTAGE WILL BE PAID BY ADDRESSEE

# Radio-Electronics

FREE PRODUCT INFORMATION  
P.O. Box 13775  
PHILADELPHIA, PA. 19101



# For New Ideas In Electronics read Radio- Electronics every month.

## During the next 12 months

- Radio-Electronics will carry up to the minute articles on:
- Computers • Video
  - Solid-state technology
  - Outstanding construction project
  - Satellite TV • Telephones
  - Radio • Stereo • Equipment reports
  - Test equipment • VCR's
  - Servicing • Industrial electronic



**NEW IDEAS AND INNOVATIONS  
IN ELECTRONICS APPEAR IN EVERY  
ISSUE OF RADIO-ELECTRONICS**

**KEEP UP TO DATE! DON'T MISS  
ANY ISSUES!**

**SUBSCRIBE TODAY!**

**USE THE ORDER CARD ON YOUR LEFT**



Delivers construction article after construction article.....Exciting columns including Jensen on DXing, Friedman on computers, Test bench tips, Noll with Calling All Hams, New Products and more.



**SUBSCRIBE TODAY!**

**USE THE REPLY CARDS ON YOUR LEFT!**

## Radio-Electronics

4SH46

Subscribe today to the magazine that keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

### check offer preferred

- |  |   |
|--|---|
| <input type="checkbox"/> 1 Year—12 issues <b>ONLY \$14.97</b><br>(You save <b>\$6.03</b> over newsstand) | <input type="checkbox"/> 2 Years ( <b>SAVE MORE</b> )—24 issues \$28.97<br>(You save <b>\$13.03</b> over newsstand) |
| <input type="checkbox"/> Canada—12 issues \$17.97  | <input type="checkbox"/> Canada—24 issues \$34.97   |
| <input type="checkbox"/> All other countries—12 issues \$22.47   | <input type="checkbox"/> All other countries—24 issues \$43.97  |

- Payment enclosed     Bill Me     Check here if you are extending or renewing your subscription

Name (Please Print) \_\_\_\_\_


Company Name (If applicable) \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Allow 6-8 weeks for delivery of first issue

Offer valid in US \$ Only.

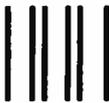


NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES


**BUSINESS REPLY CARD**  
FIRST CLASS PERMIT NO. 27346 PHILADELPHIA, PA.

POSTAGE WILL BE PAID BY ADDRESSEE

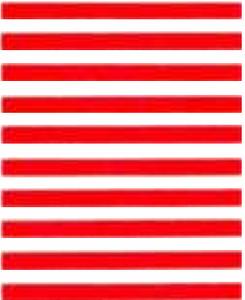
# Radio-Electronics

FREE PRODUCT INFORMATION  
P.O. BOX 13775  
PHILADELPHIA PA. 19101




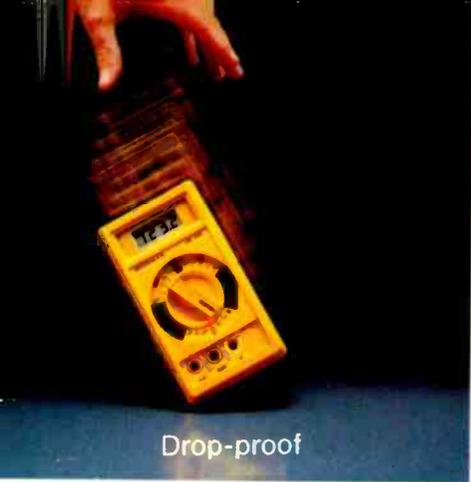

Drop-proof

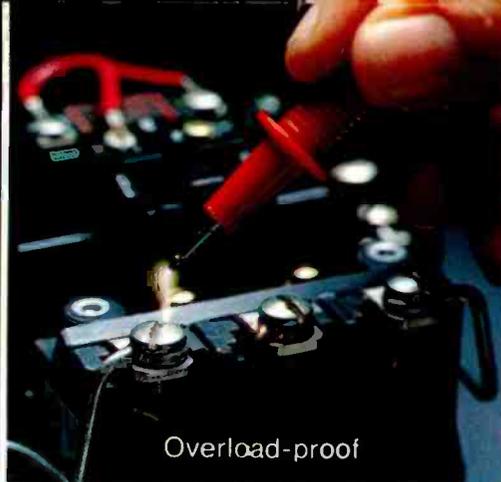

Overload-proof

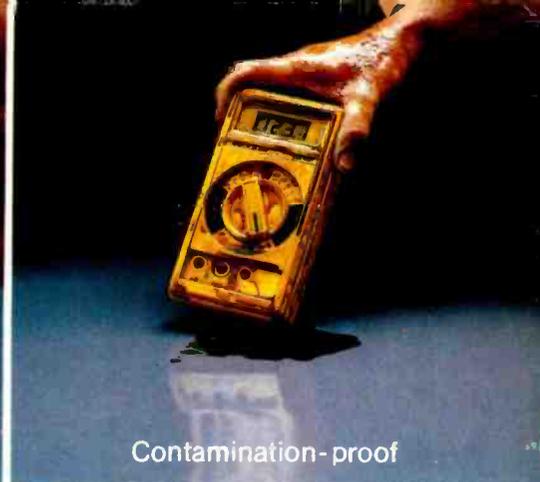

Contamination-proof

# Ooops proof.

Now there's a new breed of Beckman Industrial Corporation hand-held DMMs tough enough to withstand accidental drops, input overloads and destructive environments.

The new HD100 and HD110 DMMs are drop-proof, packed with overload protection and sealed against contamination. You won't find a more rugged meter than our HDs.

## Drop Proof

Constructed of double-thick thermoplastics, the HD100 series DMMs resist damage even after repeated falls. All components are heavy-duty and shock mounted.

## Contamination Proof

The HD series meters are designed to keep working even around dirt, heavy grime, water and oil. The special o-ring seals, ultrasonically-welded display window and sealed input jacks protect the internal electronics of the HD meters. The oops-proof meters are sealed so tightly, they even float in water.

## Accidental Overload Protection

All DC voltage inputs are protected up to 1500 Vdc or 1000 Vrms. Current ranges are protected to 2A/600V with resistance ranges protected to 600 Vdc. Transient protection extends up to 6KV for 10 microseconds.

## More Meter for Your Money

For starters you can get 2000 hours of continuous use

CIRCLE 100 ON FREE INFORMATION CARD

from a common 9V transistor battery. You can run in-circuit diode tests and check continuity. You even

get a one year warranty.

The 0.25% basic dc volt accuracy HD meters serve you with 7 functions and 27 ranges. The HD 110 also gives you 10 AMPS ac and dc. With one simple turn of the single selector switch, you can go directly to the function and range you need. There's less chance of error.

Also available is the electrical service kit. It includes the meter of your choice, a current clamp, deluxe test leads and a heavy-duty case designed to carry both meter and accessories, conveniently.

Feature for feature you can't find a more dependable meter with prices starting at just \$169 (U.S. only).

To locate your nearest distributor, write Instrumentation Products Division, Beckman Industrial Corp. A Subsidiary of Emerson Electric Company, 630 Puente Street, Brea, CA 92621 (714) 773-8111.



**Beckman Industrial™**



# Take home a world champion.

**\$85\*** gets you a technical knockout.  
**The Fluke 70 Series.**

## Winners of the digital vs. analog battle.

Since their debut, they've become the worldwide champions of the industry.

Never before have such tough, American-made meters offered so many professional features at such unbeatable prices.

Each comes with a 3-year warranty, 2,000+ hour battery life, and instant autoranging.

You also get the extra resolution of a 3200-count LCD display, plus a responsive analog bar graph for quick visual checks of continuity, peaking, nulling and trends.


Choose from the Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own protective holster and unique "Touch Hold" function\*\* that captures and holds readings, then beeps to alert you.

So don't settle for just a contender. Take home a world champion.

For your nearest distributor or a free brochure, call toll-free anytime

**1-800-227-3800, Ext. 229.** From outside the U.S., call 1-402-496-1350, Ext. 229.
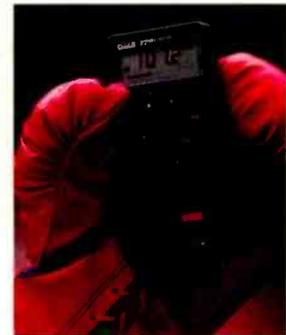
## FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.



FLUKE 73	FLUKE 75	FLUKE 77
\$85*	\$99*	\$129*
Analog/digital display	Analog/digital display	Analog/digital display
Volts, ohms, 10A, diode test	Volts, ohms, 10A, mA, diode test	Volts, ohms, 10A, mA, diode test
Autorange	Audible continuity	Audible continuity
0.7% basic dc accuracy	Autorange/range hold	"Touch Hold" function
2000+ hour battery life	0.5% basic dc accuracy	Autorange/range hold
3-year warranty	2000+ hour battery life	0.3% basic dc accuracy
	3-year warranty	2000+ hour battery life
		3-year warranty
		Multipurpose holster

\* Suggested U.S. list price, effective July 1, 1984.

\*\* Patent pending.