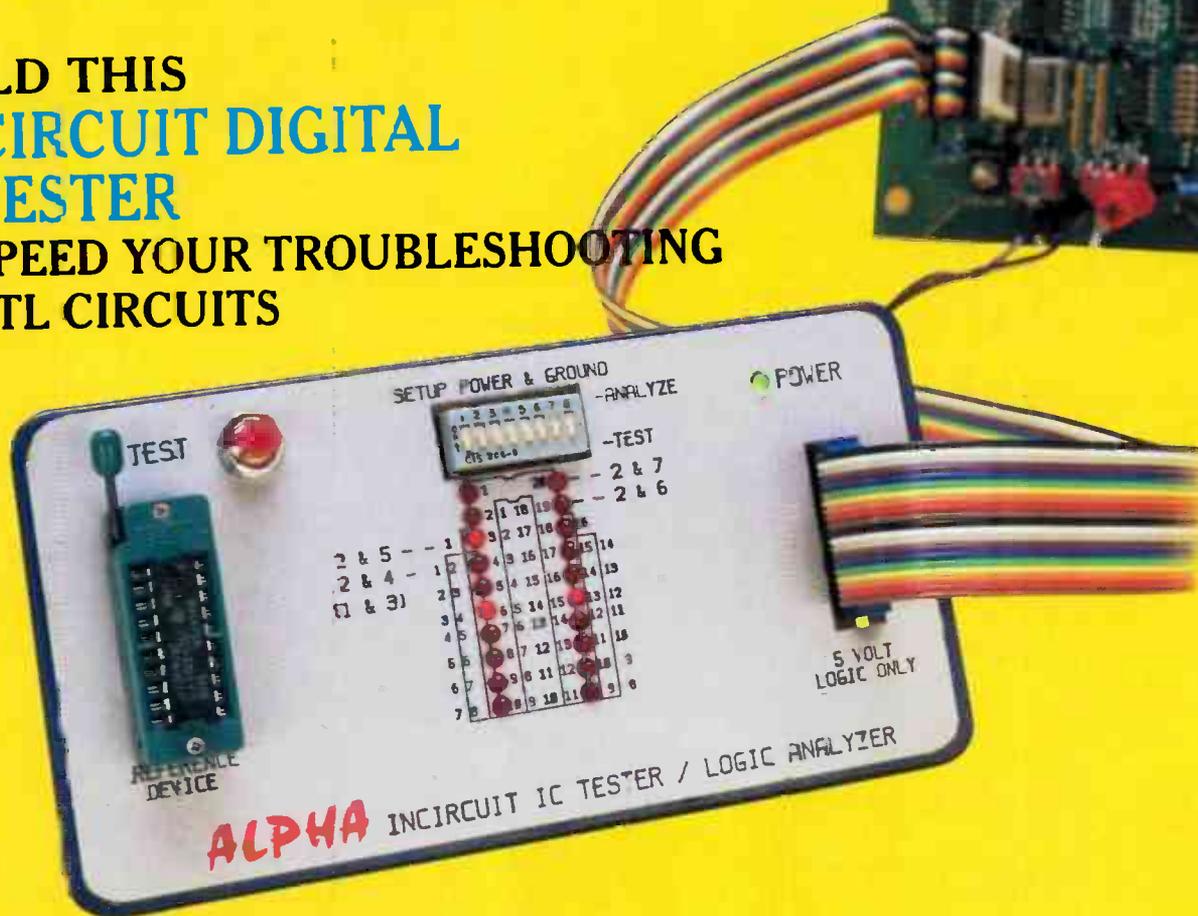


Electronics

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

**BUILD THIS
IN-CIRCUIT DIGITAL
IC TESTER
TO SPEED YOUR TROUBLESHOOTING
OF TTL CIRCUITS**



**BUILD AN AUDIO
UTILITY AMPLIFIER
FOR YOUR TESTBENCH—
OR YOUR WALKMAN!**


**LEARN HOW TO DESIGN
SWITCHING CIRCUITS**

**BUILD THE
COMPUTER DIGEST
SYNERGY CARD
TO INCREASE YOUR
BRAIN POWER**




\$2.25
IN CANADA \$2.75

A
GERNSBACK
PUBLICATION

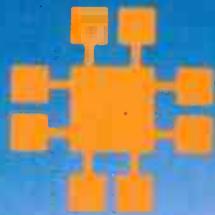

JDR INSTRUMENTS™

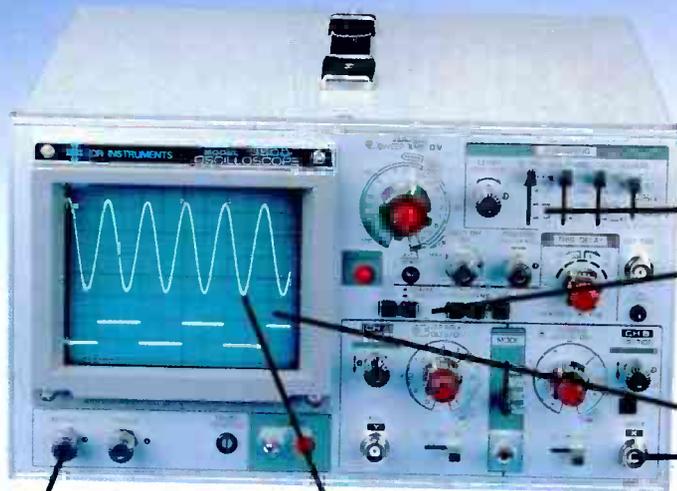Complete customer satisfaction... superior service... friendly, knowledgeable personnel... quality merchandise... providing the best values in leading edge technology.



35 MHz OSCILLOSCOPE

A remarkable value

\$499⁹⁵

Wide bandwidth and exceptional 1mV/DIV sensitivity make the Model 3500 a powerful diagnostic tool for engineers or technicians at a remarkable price. Delayed triggering allows any portion of a waveform to be isolated and expanded for closer inspection. Variable Holdoff allows stable viewing of complex waveforms.

TV SYNC FILTER

DELAYED AND SINGLE SWEEP MODES

EXCEPTIONALLY BRIGHT 5" CRT

X-Y OPERATION

Z AXIS INTENSITY MODULATION FAST 10NS RISE TIME


DMM-300

\$79.95

3.5 DIGIT DMM/MULTITESTER

This full function 3.5 digit DMM offers highly accurate performance and a host of added features like audible continuity, capacitance, transistor, temperature, and conductance to help you do the job—fast. Temperature probe, test leads and battery included.

- Basic DC accuracy: plus/minus 0.25%
- DC voltage: 200mV–1000V, 5 ranges
- AC voltage: 200mV–750V, 5 ranges
- Resistance: 200 ohms–20M ohms, 6 ranges
- Capacitance: 2000pF–20 μF, 3 ranges
- Transistor Tester: 0–2000°F
- Conductance: 200ns
- Fully overload protected
- Input impedance: 10M ohm.

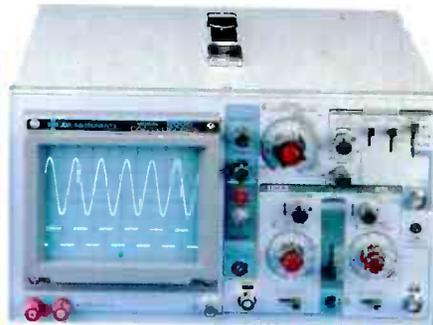

MODEL 2000

\$389.95

20 MHz DUAL TRACE OSCILLOSCOPE

Model 2000 makes frequency calculation and phase measurement quick and easy. The component tester aids in fast troubleshooting. Service technicians appreciate the TV Sync circuits for viewing TV-V and TV-H and accurate synchronization of the video signal, Blanking, VITS, and V/H sync pulses.

- Exceptionally bright 5" CRT
- Built-in component tester
- TV Sync filter
- X-Y operation 110/220 volts


DMM-100

\$29.95

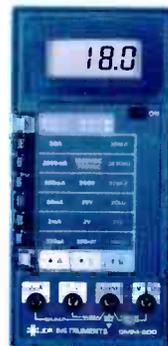3.5 DIGIT POCKET SIZE DMM

Perfect for the field service technician. Slim, pocket size without compromising features or accuracy. Large, easy to read 1 1/2" LCD display. Fully overload protected for safety. 2800 hour battery life with standard 9v cell. Probes and battery included.

- Basic DC accuracy: plus/minus 0.5%
- DC voltage: 2v–1000v, 4 ranges
- AC voltage: 200v–750v, 2 ranges
- Resistance: 2k ohms–2M ohms, 4 ranges
- DC current: 2mA–2A, 4 ranges
- Input impedance: 10M ohm
- Fully overload protected
- Approx. 5" x 3" x 1". Under 7 ozs.



DMM-200

\$49.95

3.5 DIGIT FULL FUNCTION DMM

Get highly accurate performance at a very affordable price. Rugged construction, 20 amp current capability and 22 ranges make it a perfect choice for serious field or bench work. Low battery indicator and tilt-stand. Probes and 2000 hour battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mV–1000V, 5 ranges
- AC voltage: 200mV–750V, 5 ranges
- Resistance: 200 ohms–20M ohms, 6 ranges
- AC/DC current: 200 μA–20A, 6 ranges
- Input impedance: 10M ohm
- Fully overload protected
- Approx. 7" x 3 1/2" x 1 1/2". Wt. 11 ozs.

DPM-1000

\$54.95

3.5 DIGIT PROBE TYPE DMM

Custom 80 pin LSI chip provides accuracy and reliability in such a compact size. Autoranging, audible continuity and data hold feature help you pinpoint the problem quickly. Case and batteries included.

- Basic DC accuracy: plus/minus 1%
- DC voltage: 2v–500v, autoranging
- AC voltage: 2v–500v, autoranging
- Resistance: 2k ohms–2M ohms, autoranging
- Fully overload protected
- Input impedance: 11M ohm
- Approx. 6 1/2" x 1" x 9/16". Under 3 ozs.



- ★ 2 YEAR REPLACEMENT WARRANTY
- ★ 30 DAY MONEY BACK GUARANTEE
- ★ TOLL FREE TECHNICAL SUPPORT
- ★ NEXT DAY AIR SHIP AVAILABLE

COPYRIGHT 1987 JDR MICRODEVICES



JDR INSTRUMENTS, 110 KNOWLES DRIVE, LOS GATOS, CA 95030
RETAIL STORE: 1256 SOUTH BASCOM AVE, SAN JOSE, CA (408) 947-8881

ORDER TOLL FREE 800-538-5000

CIRCLE 59 ON FREE INFORMATION CARD

September 1988 VOL. 59 NO. 9 Radio Electronics

Vol. 59 No. 9

BUILD THIS

- 37 IN-CIRCUIT IC TESTER**
An inexpensive way to speed your troubleshooting.
Bill Green
- 41 AMPLIFIED SPEAKER**
A low-cost, wide-range amplifier system, complete with loudness, bass, and treble controls.
Gary McClellan
- 45 Radio Electronics ADVANCED CONTROL SYSTEM**
Part 8. Building and programming the terminal interface.
Michael A. Tucker

TECHNOLOGY


- 49 NANOELECTRONICS: THE NEW SCIENCE OF MINIATURIZATION**
A quantum leap that may change integrated circuits forever!
Josef Bernard

CIRCUITS

- 53 VCR SERVICING BASICS**
A step-by-step approach to troubleshooting VCR problems.
Brian Phelps
- 57 LOGIC CIRCUIT DESIGN BASICS**
The ABC's of designing logic-switching circuits.
R.F. Sharp

DEPARTMENTS

- 6 VIDEO NEWS**
What's new in this fast changing field.
David Lachenbruch
- 24 EQUIPMENT REPORTS**
Psion's Organizer hand-held computer.
- 68 HARDWARE HACKER**
A/D and D/A conversions.
Don Lancaster
- 79 AUDIO UPDATE**
Can you hear the difference?—Pt. II
Larry Klein
- 82 DRAWING BOARD**
Copy protection and a Z-80 reset.
Robert Grossblatt
- 84 COMMUNICATIONS CORNER**
A new way to communicate!
Herb Friedman

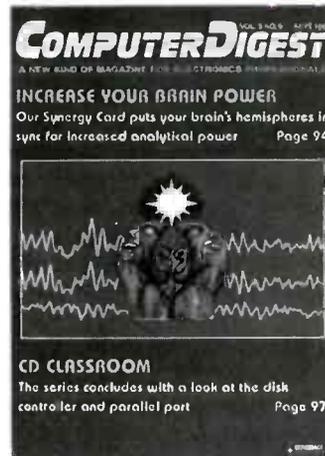

PAGE 89

TECHNOLOGY

ELECTRONICS NANOELECTRONICS

THE NEW SCIENCE OF MINIATURIZATION

Every year, improvements in manufacturing technology allow us to produce more and more complex, more efficient, more powerful, and more reliable integrated circuits. The result is a quantum leap in the performance of our electronic systems. The result is a quantum leap in the performance of our electronic systems. The result is a quantum leap in the performance of our electronic systems.

JOSEF BERNARD
The result is a quantum leap in the performance of our electronic systems. The result is a quantum leap in the performance of our electronic systems. The result is a quantum leap in the performance of our electronic systems. The result is a quantum leap in the performance of our electronic systems. The result is a quantum leap in the performance of our electronic systems.

PAGE 49

AND MORE

- 122 Advertising and Sales Offices**
- 122 Advertising Index**
- 12 Ask R-E**
- 123 Free Information Card**
- 16 Letters**
- 105 Market Center**
- 32 New Products**
- 88 PC Service**
- 4 What's News**

SEPTEMBER 1988

ON THE COVER



One of the advantages of integrated circuits is that they are much more reliable than the discrete components that they replace. Unfortunately, however, when an IC fails, the problem can be rather difficult—or very expensive—to trace.

Our digital IC tester makes it easy to find problem IC's, and it can be built for around \$100. It lets you compare a known-good IC to a questionable one. You can even test IC's as they're operating in a circuit! The IC tester can also be used as a 19-channel logic probe. The story begins on page 37.

COMING NEXT MONTH

THE OCTOBER ISSUE IS ON SALE SEPTEMBER 1

BUILD A BREATHALIZER

Learn how easy it is to go over the legal limit.

LED THERMOMETER

A great beginner's project!

ISDN

Find out what Integrated Systems Digital Network means to you now, and in the future.

COMPUTER DIGEST

Part 2 of the Hemi-Sync Generator lets you synchronize both hemispheres of your brain, for maximum concentration and efficiency.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

RADIO-ELECTRONICS, (ISSN 0033-7862) September 1988. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$17.97, Canada \$23.97, all other countries \$26.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$2.25. © 1988 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

Radio Electronics

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback,
editor-in-chief, emeritus

Larry Steckler, EHF, CET,
editor-in-chief and publisher

EDITORIAL DEPARTMENT

Art Kleiman, editorial director

Brian C. Fenton, editor

Carl Laron, WB2SLR,
editorial associate

Marc Spiwak, associate editor

Jonathan A. Gordon,
assistant technical editor

Teri Scaduto, assistant editor

Jeffrey K. Holtzman,
computer editor

Robert A. Young, assistant editor

Byron G. Wels, editorial associate

Jack Darr, CET, service editor

Robert F. Scott,
semiconductor editor

Herb Friedman,
communications editor

Robert Grossblatt, circuits editor

Larry Klein, audio editor

David Lachenbruch,
contributing editor

Don Lancaster,
contributing editor

Richard D. Fitch,
contributing editor

Kathy Campbell, editorial assistant

Andre Duzant, technical illustrator

Injae Lee, assistant illustrator

PRODUCTION DEPARTMENT

Ruby M. Yee, production director

Robert A. W. Lowndes,
editorial production

Karen Tucker, advertising production

Marcella Amoroso, production traffic

CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro,
circulation director

Wendy Aianko,
circulation analyst

Theresa Lombardo,
circulation assistant

Nancy Estrada, manager,
R-E Bookstore

Typography by Mates Graphics

Cover photo by Diversified

Radio-Electronics is indexed in
Applied Science & Technology Index
and *Readers Guide to Periodical Literature*.

Microfilm & Microfiche editions are
available. Contact circulation department
for details.

Advertising Sales Offices listed
on page 122.




SIMPSON Professional Series

★ Quality and Reliability ★

MENU-DRIVEN MULTIMETER — MODEL 560

The newest addition to the **PROFESSIONAL SERIES** the MODEL 560, incorporates measurement capabilities usually provided through the use of separate instruments. The 560 is a microprocessor based, 52 000 count, menu-driven multimeter designed and built with the requirements of the serious engineer in mind. The 560 provides the accuracy and stability necessary for exacting testing applications.

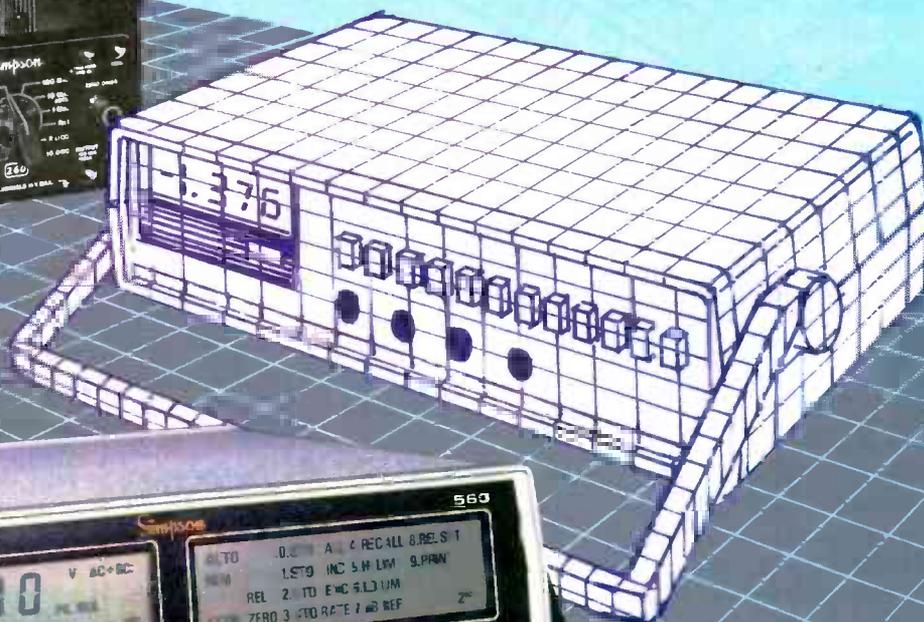COMPUTER-AGE SOPHISTICATION IN A BENCH TOP DMM



MENU-DRIVEN MULTIMETER

- Model 560 **\$2,195.00**
- Model 560 w/BUS Interface **\$2,395.00**



SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, Illinois 60120-3090
(312) 697-2260 • Telex 72-2416 • FAX (312) 697-2272

A CHIPPEWA NATION TRIBAL ENTERPRISE


Features

- Ultra Fast Autoranging
- Front Panel Programming
- Data Logging to 2150 Readings on any Selected Range
- 52 Segment Bar Graph
- 500kHz Frequency Counter
- Battery Backed Data Storage Buffer
- RS232C Capable
- Centronics Printer Capable
- REL and Continuity

For information on:

Model 560 circle 187 ON FREE INFORMATION CARD

WHAT'S NEWS

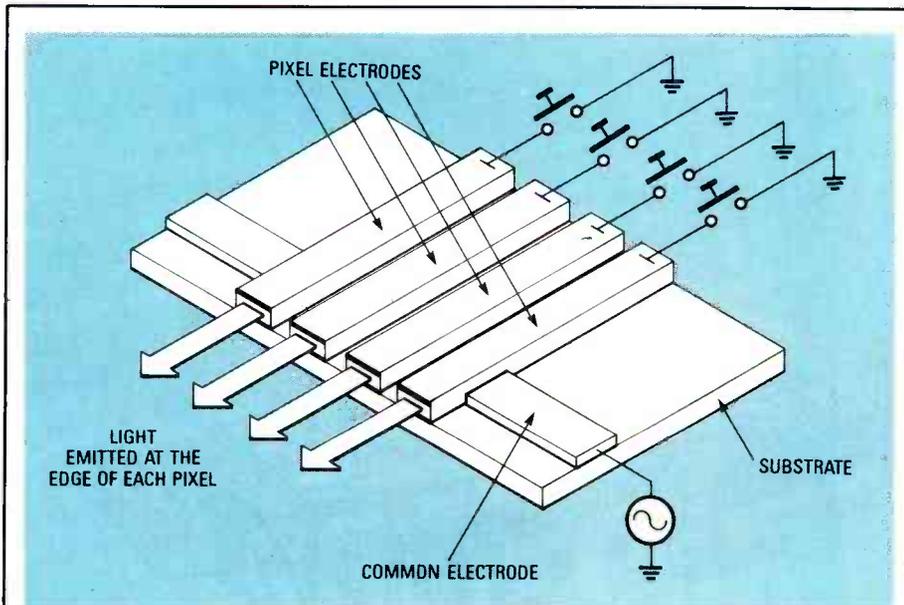

AN ELECTROLUMINESCENT ARRAY is a new economical light source for laser printers, according to scientists at Westinghouse.

Edge-emitter light source improves laser printers

Westinghouse scientists have demonstrated a light source which they believe may be a "low-cost alternative to laser printers." Unlike the laser-light sources in most of today's non-impact printers, the new source has no scanning mirrors or other moving parts, and it is smaller and more rugged.

Called a Thin-Film ElectroLuminescent (TFEL) edge emitter, the new light source is based on a discovery that light emitted from the edge of a thin film of zinc sulfide is up to 100 times brighter than light from the face of the film.

The new edge emitter was demonstrated with a specially built test station—a 10 page-per-minute laser printer with a 300 dots-per-inch printing capability was operated with a 400 dots-per-inch TFEL



A CHARACTER GENERATED BY THE TFEL EDGE EMITTER (left), is clearer than that from a laser-light source (right). Both images are magnified 50 times.

edge emitter replacing the laser. Even though not all parts were properly matched in the temporary setup, the edge emitter produced superior letters. By simply replacing the laser-matched photoreceptor of the laser printer with one matched to the TFEL edge-emitter wavelength, the printing speed could be doubled to 20 pages per minute, Westinghouse scientists said. R-E

Ion damage improves semiconductor quality

A new technique, known as *ion-damage-controlled photochemical dry etching*, may im-

prove the quality of computer chips and similar items, and save processing time and money.

In conventional semiconductors, complex circuits are etched

out by covering parts of the surface with photoresist and etching out the parts that are not covered by that protective material. Complex integrated circuits require multiple masks and etchings. It is difficult to align the masks perfectly with the structures already etched in the wafer, and where misalignment occurs, performance is degraded.

Scientists at Sandia National Laboratories (Albuquerque, NM) have developed the new technique that reduces the need for multiple masks. The semiconductor surfaces that would have surviving masks are bombarded with ions, damaging the exposed areas. That damage makes those areas relatively inert.

The masks that protected the other areas is then stripped away, and the surface is etched with a reactive chemical under strong light. The ion-damage forms an unshiftable mask for subsequent etching processes—the material will not be etched where the surface has been ion-damaged.

Wallet-sized cards hold a library of information.

The Optical Recording Corporation of Toronto, Canada has developed a wallet-sized optical-storage card capable of storing up to 200 megabytes. That is the equivalent of an optical memory disc, but the card costs as little as \$1.00 when purchased in quantities of 100,000. One of the first applications for the card will be to store personal-health records.

Information is placed on the cards in arc-shaped tracks on 2-micron centers. Data is stored on 1-micron diameter spots on 1-micron centers along the line of the tracks. A rotating multi-lens laser scanner is used to write or read four tracks per revolution. The card itself is held stationary during writes and reads. R-E

NEW! Measure to the MAX with the first Test Bench™ you can hold in your hand

For \$139.00 you can replace a bench full of instruments



Micro-miniaturization strikes again! B&K-PRECISION has combined the capabilities of five popular instruments into one hand-held Test Bench™ unit. This 41 range voltmeter, ammeter, ohmmeter, frequency counter, capacitance meter, logic probe, transistor and diode tester features an extra-large LCD display, ruggedized case and B&K-PRECISION quality.

You don't need a trunk full of instruments to get the job done. See your local B&K-PRECISION distributor for immediate delivery on the new 388-HD Test Bench.™

Large 3½ Digit LCD Readout. High-contrast display, slanted for easy viewing

Diode Test. Quick check of diode junctions

DC and AC Volts. 0.5% DCV accuracy

Integral Tilt Stand. Can be detached and used to hang DMM on vertical surface

Single Rotary Switch. Convenient range and function selection

Resistance. 0.1Ω to 2000 MΩ

hFE Measurement. Measures transistor gain

Audible Continuity Beep indicates a complete circuit

Logic Level Measurement. Checks TTL levels

Frequency Measurement. 20Hz-200kHz

DC and AC Current

Capacitance Measurement. Up to 20μF

20 Amp Range

ZAP Proofed. High-Energy Fused




Four-foot Drop Resistant Heavy Duty Case. Bright yellow safety color



6470 W. Cortland St. • Chicago, IL 60635 • 312-889-1448
International Sales, 6470 W. Cortland St., Chicago, IL 60635

Canadian Sales, Atlas Electronics, Ontario
South and Central American Sales, Empire Exporters, Plainview, NY 11803

CIRCLE 77 ON FREE INFORMATION CARD

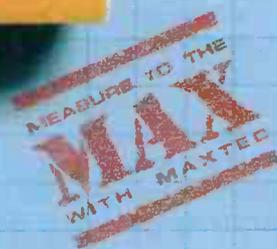

VIDEO NEWS



DAVID LACHENBRUCH,
CONTRIBUTING EDITOR

● **Sony Adds VHS.** Fourteen years after introducing the first successful home videotape recorder, Sony has finally conceded to the popular taste and added VHS recorders in the United States and Japan. Sony's VHS recorders, the first made in its own factories, are deluxe in every way. A mono recorder listing at \$600 and a stereo hi-fi version at \$1,100, have such features as "Digital Edit Monitor," which puts two small pictures on the screen for editing—one showing the edit source and the other the tape to be edited and the actual result. The recorders also have front-mounted input jacks for easy attachment of camcorders for editing, LCD remote controls for simple programming, flying erase heads, digital special effects such as picture-in-picture and other top-of-the-line features. In addition to the two recorders, Sony introduced a VHS Video Cassette Player (VCP), the first such major-brand play-only unit with hi-fi stereo—designed, presumably, for Beta owners who need a VHS machine to play rented tapes.

● **Video Walkman.** That's the name Sony has given its book-sized combination VCR and TV, obviously in hope of repeating the success of the audio Walkman. The little tote-along combines a complete color-TV set with 3-inch backlit LCD with a complete 8mm videocassette recorder in a neat package weighing just 2.4 pounds. List-priced at \$1,300, the Video Walkman is designed for viewing in almost any situation—it can be powered by rechargeable battery, dry cell, car battery, or AC adaptor, and has a loudspeaker as well as earphones for its PCM audio track. It can be used for watching TV, of course, as well as viewing tapes, which can play up to four hours.

● **Fancy New Brandnames.** What do Dimensia, Prism, Optonica, and HPX have in common? No they're not diseases; they're new lines being fielded by major color-TV brands in order to emphasize top-of-the-line features. Dimensia is the tippy-top line of the RCA brand; Prism belongs to Panasonic, Optonica is Sharp's dress-up label, and HPX is Hitachi's high end.

● **Introducing IDTV.** IDTV stands for "Improved Definition TV," and Philips and Toshiba share the honors of introducing the new initials to these shores. The first two IDTV sets vary in their features, so there's no real definition of what IDTV actually is. But what the Philips and Toshiba IDTV's share is digital memory—systems that double the number of horizontal lines and motion compensation to avoid blurring.


The Philips IDTV sets, available in either 27- or 31-inch sizes, derive new scanning lines to insert between the existing lines, resulting in 525 lines in each field. The derived lines constitute the median of the line above, the line below and the corresponding line from the preceding field. In addition, the sets have a noise-reduction circuit that remarkably improves snowy pictures. They have two tuners to make it possible to watch two different stations using the picture-in-picture feature. They also let you freeze and store either the main or the subsidiary picture, among other features. Toshiba's IDTV has a 28-inch picture and claims "advance double scanning." It also has picture-in-picture and a full-field memory, as opposed to the Philips' frame memory.

● **"Digital Paper."** Billed as the world's cheapest recording medium—so disposable that its developers call it "digital paper"—a new type of recording tape has been demonstrated by ICI, Britain's largest chemical company. It could make an excellent storage medium for digital-video recording as well as for computer data. The system uses low-cost polyester film with a layer of polymer dye. Recording is done by burning the dye layer with an infrared laser.

The medium can store one terabyte (one thousand billion bytes) on a strip of tape 35mm wide by 1,640 feet long, at a cost of about 5 cents per megabyte, according to ICI. It's a record-once system because it can't be erased. The "digital paper" can be used in several forms—tape, disc, sheet, and so forth. Several companies are working to commercialize it for various uses, and hardware for the system could be shown as early as next year.

R-E

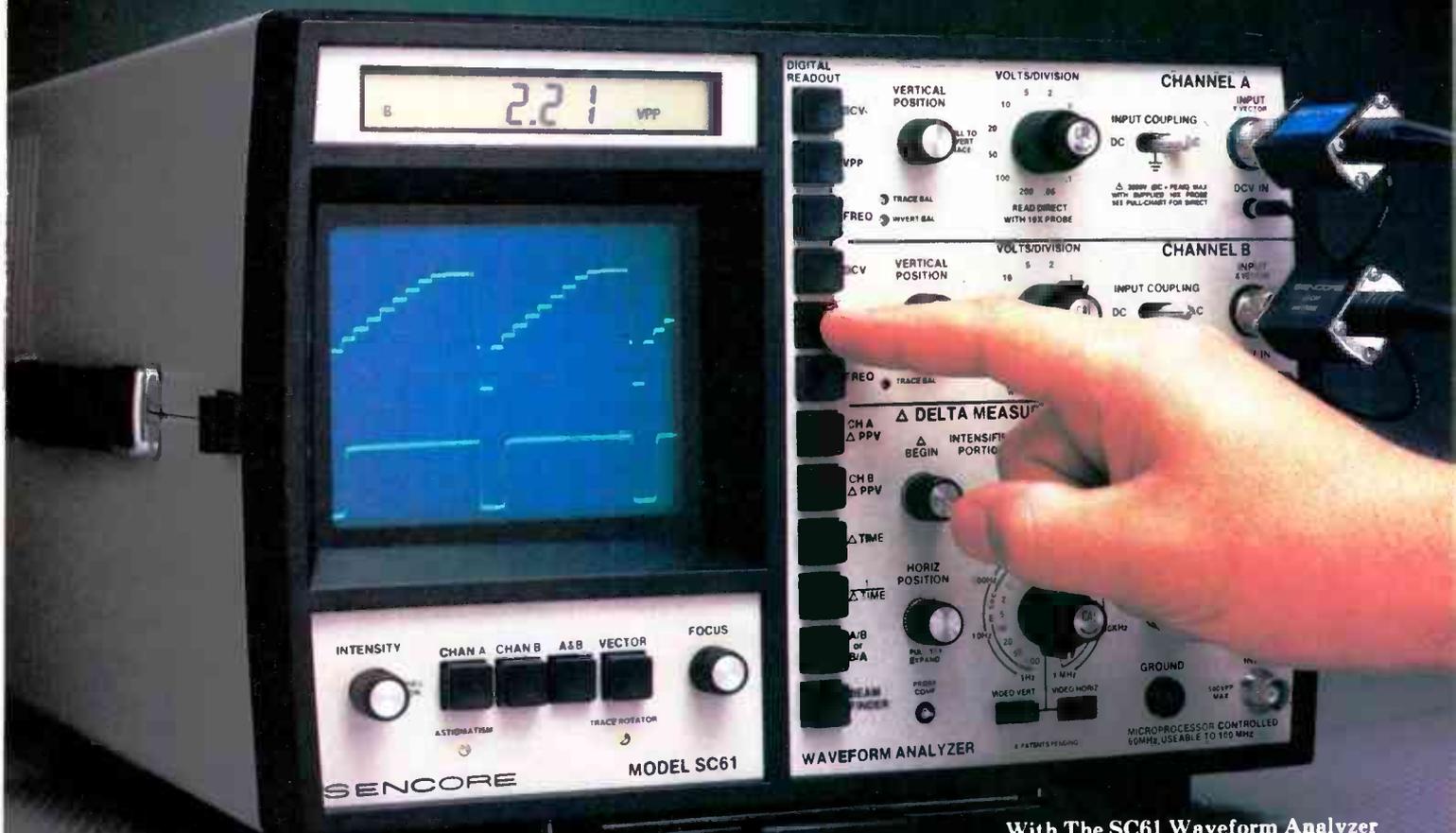With Just One Probe Hookup You Can Confidently Analyze Any Waveform To 100 MHz, 10 Times Faster, 10 Times More Accurately, Absolutely Error Free, Guaranteed Or Your Money Back . . .



With The SC61 Waveform Analyzer
~~\$3,295.00~~ **PATENTED**

\$2,895.00 — Limited Time Offer

Promises of increased productivity from other oscilloscopes fade fast when compared to the speed and accuracy of the SC61. Eliminate the confusing menus, cursors and complexity of regular oscilloscopes at the push of a button. Here's what the SC61 does for you:

Analyze Waveforms Easily

- Accurate Waveform Display - 60 MHz Bandwidth (usable To 100 MHz) To Test The Latest Digital Circuits.
- Rock-Solid Sync - ECL Logic Circuits And Differential Amplifiers Give Fiddle Free Operation.
- Four Times The Measuring Range - Measure From 5 mV To 2000 Volts (3000 Volts Protection) For Expanded Signal Handling.

Autotracking™ Digital Readings Analyze The Whole Signal

- Autoranging DC Volts Through Single Probe, Even With AC Coupled.
 - Automatic Peak-To-Peak Volts - Even If Variable Control Is "Out Of Cal".
 - Automatic Frequency Measurements Without Sensitivity Adjustment Or Range Switching.
- CIRCLE 189 ON FREE INFORMATION CARD

Digital Delta Tests Analyze Any Part Of The Signal.

- Delta Peak-To-Peak Volts - Peak-To-Peak Volts Of Any Part Of The Signal.
- Delta Time For Any Time Reading - Including Delay Between Traces
- 1/Delta Time - Frequency Of Part Of The Signal - Finds Sources Of Interference Or Ringing.

Frequency Ratio Test - Tests Multiplier And Divider Circuits

Easy To Use - Human Engineered Controls And Virtually No Graticule Counting Or Calculations

The SC61 is designed to give you the measurements you need fast. We make one claim:

"Try the SC61 on your bench for 30 days. If it doesn't cut your present scope time in half, send it back for a complete refund, no questions asked."

Try the SC61 for 30 days, and discover true troubleshooting speed.

Call 1-800-843-3338
In Canada Call 1-800-851-8866

SENCORE

REASONS FOR SELECTING CIE

- Approved for educational benefits under the G.I. Bill for Veterans and other eligible persons.
- CIE provides printed job resumes, letters of recommendation, and lifetime Employment Service for all graduates at no extra charge.
- State-of-the-Art laboratory equipment is yours to keep and it comes assembled, ready for hands-on-experiments.
- Only CIE offers an Associate Degree program based on actual study time used. The faster you complete your degree, the less your overall tuition.
- Upon graduation, CIE offers you free preparation to pass the Certified Electronics Technician Exam.



CIE

CLEVELAND INSTITUTE OF ELECTRONICS 1776 East 17th Street • Cleveland Ohio 44114
PHONE TOLL FREE 1-800-321-2155 / In Ohio 1-800-523-9109


LEARNING... THE KEY TO SUCCESS

A CAREER IN ELECTRONICS STARTS WITH CIE.

For the last few years, the electronics field and related industries have been growing at an incredible pace. And today, a career in electronics offers more opportunities and greater rewards than ever before.

Just ask any of the many graduates of the Cleveland Institute of Electronics who have landed high-paying positions with aerospace, computer, medical and communications firms. They'll tell you success didn't come easy... but that CIE made it all worthwhile.

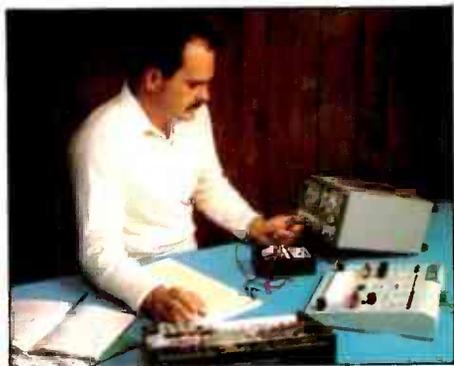SPECIALIZED TRAINING CIE isn't just another be-everything-to-everybody correspondence school. We're accredited by the National Home Study Council. And with more than 1100 graduates each year, we're the largest independent home study school specializing exclusively in electronics. CIE has been training career-minded students like yourself for over 50 years and we know the business inside and out.




Some of the training you will receive at CIE. The CIE Microprocessor Laboratory, an integral part of our program, provides you with all the practical experience you need to succeed in the field. We have the state-of-the-art equipment you need for tomorrow.

PRACTICAL TRAINING CIE students learn by doing, using sophisticated electronic learning tools that we've designed and developed. One such tool, our 4K RAM Microprocessor Training Laboratory, teaches programming, interfacing and lets you work with a broad range of computers in a way that working with a single, stock computer simply can't.

We combine that valuable hands-on training with our unique Auto Programmed® lessons, designed to teach you step-by-step and principle-by-principle. The result is practical training... the kind of experience you can put to work in the marketplace.

PERSONALIZED TRAINING While some of our students have a working knowledge of electronics others are just getting started. That's why we have 10 career course levels from Basic to Advanced. They let you start where you want. Learn at your own pace. And learn as much as you like. You can even earn an Associate in Applied Science Degree in Electronics. And when you need help, our trained professionals are on hand to assist you by phone or mail.

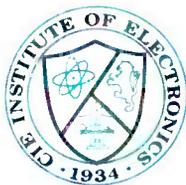Learning electronics isn't easy, but getting started is. For a CIE catalog and enrollment information, just mail the coupon below. Or call toll-free 1-800-321-2155. In Ohio, call 1-800-523-9109.



Accredited by the Accrediting Commission of the National Home Study Council, Washington, D.C.

CIRCLE 60 ON FREE INFORMATION CARD



YES! I want to get started. Send me my CIE school catalog including details about the Associate Degree program.

Print Name _____

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____/_____

Check box for G.I. Bulletin on Educational Benefits
 Veteran Active Duty

MAIL TODAY!

CIE CLEVELAND INSTITUTE OF ELECTRONICS
 1776 East 17th Street, Cleveland, Ohio 44114

ARE-95

ASK R-E

WRITE TO:

ASK R-E
Radio-Electronics
500-B Bi-County Blvd.
Farmingdale, NY 11735

WHERE IS TRUE NORTH?

Some months ago (Radio Electronics, October 1986) you showed us how to use the stars to locate True North to use as an aid in setting up a satellite dish. In my area, smog and bright lights on the northern horizon make locating and identifying stars almost impossible. Is there any way that I can use the sun to locate True North?—G.S.R., Duluth, MN.

There are several ways to use the sun to establish a true North-South reference line. All are based on the fact that the sun is exactly due south at high noon and the shadow of a vertical pole lies along a true North-South line. The drawing in Fig. 1 shows a method learned in the Boy Scouts.

All that you need is some string, sticks and pegs, and a plumb bob or Scout's knife. Place the crossed sticks as shown in Fig. 1 so that the longer one points in a general northerly direction. Anchor the lower end with a large stone or tie it to a stake driven into the ground. Tie the plumb line to the tip of the pole so that the weight is almost touching the ground. Drive a small stake directly beneath the plumb bob or the point of the knife at point A. About an hour before noon (local time), drive a stake at point B, the exact end of the leaning pole's shadow.

Tie a string to the stake at point A and extend it so its length is AB. Tie a sharpened stick to the string at point B and use it to scribe the arc BCD on the ground.

At about an hour and fifteen minutes after noontime, the pole's shadow will cross the scribed arc at point D. Mark that point with a stake and tie a string from B to D. A

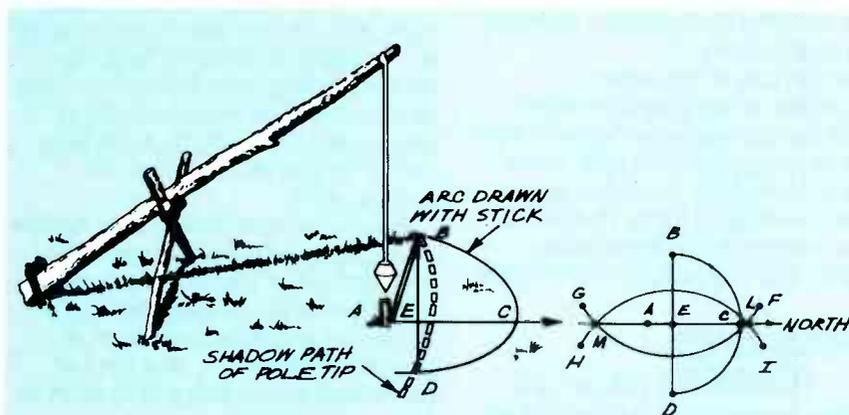


FIG. 1

perpendicular bisector of line BD actually lies in a true North-South direction.

To find the perpendicular bisector, either drive a stake at point E, the mid-point of line BD, or at point C, the mid-point of arc BCD. Line AE or AEC indicates the direction of true north.

If you don't have a tape measure or ruler for locating either E or C, use the scheme, derived from geometric principles, illustrated in Fig. 1. Cut a piece of string to about three-fourths the length of BD. At one end, make a loop that will fit loosely around the stakes at B and D. Tie the other end to a pointed stick that you will use as a scribe. Use the string and stick as a compass to draw arc FG from point B and HI from point D. The straight line passing through points L and M also passes through A, and lies in a true North-South direction.

TELEPHONE BELL SUBSTITUTE

I'm looking for the circuit of an electronic warbling telephone ringer that I can substitute for the con-

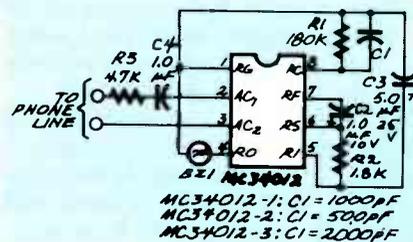


FIG. 2

ventional bell. I can't seem to find one. Can You help?—R.W.K., Kenilworth, NJ.

The circuit in Fig. 2 shows how the Motorola MC34012-series telephone ringers are used. The IC is powered by the ring voltage from the phone line. The ring voltage is nominally 60–80 volts at 20 Hz, but may be anywhere in the range of 40V/16Hz to 150V/68Hz depending on the TELCO system. That voltage is rectified by an internal bridge rectifier and it is then used to power the tone generators and also drive the ceramic piezo-electric buzzer (BZ1).

The base frequency of the relaxation oscillator controlling the high- and low-frequency notes

Heathkit®

NEW! HWS-24-HT Deluxe Twin Band Handie Talkie

Discover the fun and excitement of mobile communications with this highly versatile VHF/UHF FM handie talkie. Powerful, compact and easy to use, this deluxe twin band transceiver offers outstanding performance based on the most stringent specifications.

Features:

- Two internal VFOs • 20 available memory channels • Frequency entry via keyboard or rotary channel switch • Vacant channel search • Auto power off, and much more.

See it in the latest Heathkit catalog, along with our full line of handie talkies, including:

- The HWS-2 2 Meter • The HWS-4 450 MHz • The HWS-2-XL Deluxe 2 Meter • The HWS-4-XL Deluxe 450 MHz

To get your FREE Heathkit catalog, write:

**Heath Company
Dept. 020-694
Benton Harbor, MI 49022**

Send for your
**FREE
Catalog**

Easy-to-read display



Full-function keypad

Heath Company

Philips ECG's Master Guide gives you all the replacement semiconductor information you'll ever need.



For speed, accuracy and ease-of-use, nothing beats the Philips ECG® Master Guide!

- Contains technical data for 4000 Philips ECG semiconductors that replace over 240,000 industry part numbers
- Contains the most accurate cross-references available.
- New edition has 13,000 additional cross-references

and 230 new devices

All this, all in one book.

Contact your Philips ECG distributor or call 1-800-225-8326. It just might be the smartest call you make all week.

The Smart Choice.

PhilipsECG

A North American Philips Company

ECG® DM-76 Auto-Ranging Digital Multimeter: The smart choice for value!

ECG DM-76 Multimeter is accurate, priced right and packed full of features. Here's what you get:

- Auto or manual range selection
- 0.5% basic accuracy
- 3½ digit LCD with range indicator
- Data hold
- 20 megohm full scale
- Transistor hFE
- Diode V_F
- Audible continuity test

Accuracy! Value! All the features you need! Contact your ECG products distributor or call 1-800-225-8326. It just might be the smartest call you make all week.



The Smart Choice.

PhilipsECG

A North American Philips Company

Keep equipment in top shape with Philips ECG's top of the line Audio/Video products.



The best performance from any piece of equipment. The line-up that delivers it looks like this:

- To measure and adjust frequency response of audio tape decks, the AR20 frequency response cassette
- To accurately adjust audio tape running speed and record/playback head alignment, the AR30 speed and adjustment cassette
- To observe tape travel path in the VCR, the Video tape path view cassette
- To measure torque in play or fast forward/rewind modes, the Video torque meter cassettes

Contact your Philips ECG distributor or call 1-800-225-8326. It just might be the smartest call you make all week.

The Smart Choice.

PhilipsECG

A North American Philips Company

along with the warble rate is set by resistor R1 and capacitor C1 connected to pin 8. The base frequency can range between 1 kHz and 10 kHz when R1 is between 150K and 330K, and C1 is between 400 pF and 2000 pF. The tone that is fed to the buzzer at pin 4 switches between the two frequencies at a 12.5-Hz warble rate.

The MC34012-series device is available in three frequency ranges, and they can easily be identified by suffixes 1, 2, and 3. The tone frequencies in Hz are 822/1040 for the MC34012-1, 1664/2080 for the MC34012-2 and 416/520 for the MC34012-3.

Check with Motorola Semiconductor Products, PO Box 52073, Phoenix, AZ for sources and availability of the MC34012. The buzzer can be a Mallory PT-7, PT-8, or other similar ceramic piezoelectric device.

SOLID-STATE REPLACEMENT FOR AN OLD TUBE

I would like to have an oscillator circuit using some type of power transistor to replace the oscillator in a Boonton 160-A Q meter. The oscillator has a type-45 tube in an Armstrong circuit with a grid, plate, and output coils. The output coil delivers 0.5 volt at 500 mA along with the RF signal that heats the thermocouple element. I need help! Otherwise, it's back to the ancient 45.—J.C.M., Baldwin, NY.

You didn't say why you want to replace the original oscillator. If the instrument is operating properly, you should definitely leave it alone. It is a high-quality instrument and I doubt that you can improve it by simply replacing the oscillator circuit. "If it ain't broke, don't fix it." You'll only be creating unnecessary work for yourself.

If the 45 is weak, you may be able to purchase a replacement through Radio Shack or one of the tube suppliers that advertise in the Market Center. If you can't find a 45, try a 2A3; that tube is a plug-in replacement with somewhat similar characteristics. You may have to "juggle" the grid bias in order to adjust the output voltage and current to "specs." For the 2A3, one place that you can try is Edlie Electronics, 2700 Hempstead Turnpike, Levittown, NY 11756.

DAMARK

INTERNATIONAL, INC.

MUST LIQUIDATE AT FAR BELOW DEALER COST!

PUBLIC NOTICE:

Due to a variety of reasons, (overproductions, discontinued lines, Etc...) manufacturers & distributors get **STUCK** with inventories that must be liquidated. **DAMARK** walks in, lays down cash, and takes the entire inventory. This is how we can offer you products at **BELOW DEALER COST!** Just **LOOK** at the values below and order today - **QUANTITIES ARE LIMITED!**

Command VOICE RECOGNITION DIALER TELEPHONE

The Phone That Responds to Your Spoken Command! Say "Jim...Dial" and it dials Jim! It's that simple! No phone numbers to look up or remember. Command Dialer is the phone of the future. But it's here now!



- **Dial by Voice** - "Pat...Dial" Command Dialer dials: if Pat's line is busy, touch the REDIAL BUTTON.
- **Hands Free Speaker Phone** - For family or business conferences.
- **16 Number Memory** - By voice or touch.
- **Long Distance Lock-Out** - Prevents dialing long distance calls.
- Meets the needs of business people, families, elderly, handicapped, and even kids.
- Automatic re-dial of busy numbers.
- Digital Alarm Clock with snooze button.
- Electronic "Scratch Pad" ("write down" a phone number during a conversation).
- **One Year Warranty!**

Manufacturer's Suggested Retail \$299.00

DAMARK PRICE:

\$88

Order No. B-843-105809 Insured Ship/Hand.: \$6.00

maxon Radar Detector

This mini-size Maxon radar detector is one of the most sensitive, sophisticated, reliable radar detectors available today! Long range reception with early audio and visual warning signals are just some of the valuable features found in this most appreciative radar detector.



- Pocket-size-2-7/8"W x 4-1/2"D x 1"H.
- Superheterodyne receiver detects X band & K band radar signals, reacts in 1/8-second.
- Anti-false alarm circuit blocks signals from other vehicles' detectors.
- City & highway operating modes. •Synchronized audio alert, flashing visual display indicates radar signal strength.
- Includes spring visor clip, suction cup mount for windshield attachment, hook and loop fasteners, cord clips, straight and coiled power cords, earphone, and carrying case.
- **90 Day Warranty!**

Compare At: \$299.95

DAMARK PRICE:

\$79

Order No. B-843-106468 Insured Ship/Hand.: \$6.00

PAYER Rechargeable Razor

Having problems getting a close, smooth shave with an electric razor? Well, with the European made Payer cordless razor you can have it all! Close, smooth, shaves without fighting a cord.



- Single foil rechargeable razor with trimmer.
- Cordless • Small enough to fit in your shirt pocket or travel bag. • Made in Austria.
- Model #: 1001. • **Full Factory Warranty!**
- **Factory New! Factory Perfect!**

Compare At: \$129.95

DAMARK PRICE:

\$39

Established over 40 years ago in Graz, Austria, Payer has a long history of innovation, including the first foil razor and commissioning F.A. Porsche to design the now famous Porsche Design razor.

Order No. B-843-106237 Insured Ship/Hand.: \$4.00

AMBICO MTS STEREO DECODER



Add stereo excitement to your TV viewing with this state-of-the-art Ambico MTS Stereo Decoder. Creates TRUE stereo for most TV's! All cables included.

- Works with any tuner for TV (CATV cable converter, VCR, remote TV tuner, TV with MPX output).
- Automatically decodes stereo signals broadcast through antenna or cable.
- Slim, compact size: 9.75"Wx 7"Dx1.5"H.
- All necessary cables included.
- **FULL 90-DAY WARRANTY!**

Manufacturer's Suggested Retail: \$129.00

DAMARK PRICE:

\$58

Order No. B-843-102624 Insured Ship/Hand.: \$6.00

ZENITH PERSONAL REMOTE CONTROL CENTER

Operate your TV, VCR & Cable TV Decoder with one remote control. Consolidate all those remotes into one easy to use remote control center! It's simple to use! There's no need for the remote to "learn" anything...there's a simple, one-time set up of switches.



- Uses 3 AAA batteries (included).
- Dimensions: 8-1/10"H x 13-1/16"D x 2-1/2"W.
- The PCC may not operate every model listed.
- Made in U.S.A.
- **90 DAY WARRANTY!**

Compare At: \$99.95

DAMARK PRICE:

\$49

Order No. B-843-104323 Insured Ship/Hand.: \$4.00

FOR FASTEST SERVICE CALL TOLL FREE 1-800-832-5555



NAME _____
 ADDRESS _____
 CITY _____ ST _____ ZIP _____
 PHONE _____

Check/Money Order VISA
 MasterCard Discover CARD NO. _____ EXP. DATE _____

Send To: **DAMARK INTERNATIONAL, INC., 6707 Shingle Creek Parkway, Minneapolis, MN 55430**

PRODUCT	ITEM NO.	QTY.	PRICE	S/H/I	TOTAL
COMMAND DIALER	B-843-105809		\$88	\$6.00	
MAXON Radar Detector	B-843-106468		\$79	\$6.00	
PAYER Cordless Razor	B-843-106237		\$39	\$4.00	
AMBICO Stereo Decoder	B-843-102624		\$58	\$6.00	
ZENITH Unified Remote	B-843-104323		\$49	\$4.00	
SUB TOTAL					
DELIVERY TO 48 U.S. CONTINENTAL STATES ONLY					
in MN add 6% Sales Tax					
Total S/H/I					
TOTAL					

LETTERS

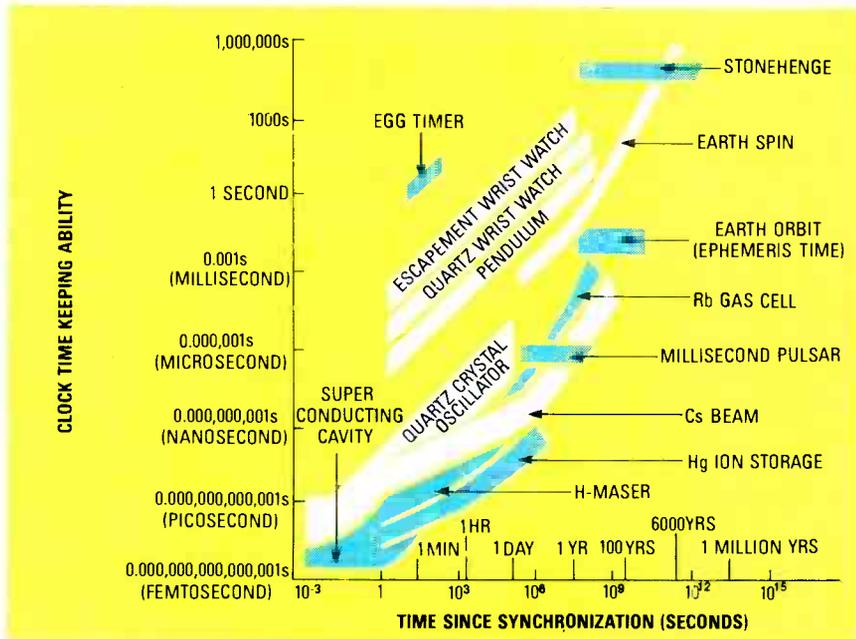
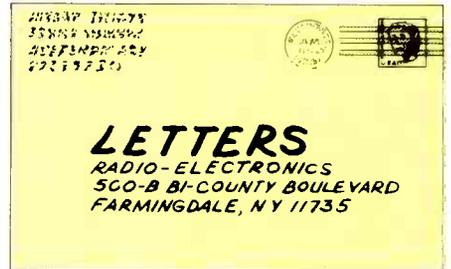


FIG. 1

KEEPING TIME

"All About Calibration" (*Radio-Electronics*, June 1988) contains some errors in relation to time standards. The article states, as a general rule, that "universal time (UTO, UT1, UT2) is accurate to within 3 ms in 1 day." That yields a factor of about 3.5×10^{-8} accuracy. The Ephemeris time value of 50 ms in 9 years yields a factor of about 1.8×10^{-10} accuracy. That is OK too. However, the atomic time of 0.1 μ s in 1 minute only yields a factor of 16.7×10^{-10} . That is less than what is stated for Ephemeris time. I believe that what you wanted was something like 0.1 μ s in 1 day, which yields a factor of 1.16×10^{-12} .

STEPHEN L. COAN
Beaverton, OR

Mr. Coan, you are absolutely correct. As the Time Chart shows, some Cesium-beam atomic clocks

are accurate to 1 ns in 1 day, or an accuracy factor of 1.16×10^{-14} . See Fig. 1.—Editor

RS-232 CORRECTION

It has come to our attention that there were a couple of errors in the article "RS-232 Monitor/Control System" (*Computer Digest*, August 1988). The voltage supplied to IC3 can range from 4.5–18.0 volts, not 4.5–8.0 volts, as the article indicated. The equation for the time it takes to transmit data from the same node twice should read: $(1/4800) \times 11 \text{ bits/byte} \times 8 \text{ bytes}$. We apologize for any inconvenience caused by those mistakes.—Editor.

VERSATILE FUNCTION GENERATOR

If you are building the "Versatile Function Generator" (*Radio-Electronics*, May 1988), please note that

the timing IC (IC6) must have an "A" suffix. Do not try to use an ICM7207IPD in place of an ICM7207AIPD. Someone has been advertising the IC with the "A" suffix, but sending the wrong one, so check carefully before using it.

A few minor errors appeared in the article. On the Parts Placement diagram, IC9, the negative regulator, is oriented backward. The tab side should face the middle of the board—just the opposite of the two positive regulators. The ramp output and the pulse output are reversed. In the schematics, R23 should be a 2K linear potentiometer, C8 should be 100 pF, and C9 should be 10 μ F, 25 volts. The two rectifier diodes, D4 and D5, should have been labeled 1N4001, not 1N4401. Any diode with at least 1-amp/50-volt rating will do. In the Parts List, R36 should be 2.7K, and R13 and R43–R47 should be 4.7K.

JOHN WANNAMAHER
Orangeburg, SC

AMATEUR COMPUTERISTS CLUB

In May 1966, Stephen B. Gray formed the Amateur Computer Society for people who were interested in building their own computers. By sharing their experiences and problems, Gray believed that hobbyists could reduce the frustration and isolation of working on their own to build a computer. Ned Wadsworth's *Scelbi-8H*, Jonathan Titus' *Mark-8*, and Ed Roberts' *Altair 8800* were the practical results of many years of effort to develop a personal computer.

While personal computers are now readily available, there is an increasing emphasis on business uses and software appropriate for

NEW

OPTOELECTRONICS INC.

FREQUENCY COUNTERS TO 2.4 GHZ

POCKET SIZE
SIZE: 4" H x 3.5" W x 1" D
MADE IN USA

#TA-1005

8 LED DIGITS • 2 GATE TIMES
ALUMINUM CABINET
INTERNAL NI-CAD BATTERIES INCLUDED
AC ADAPTER/CHARGER INCLUDED

EXCELLENT SENSITIVITY & ACCURACY

AC-DC • PORTABLE OPERATION



Small enough to fit into a shirt pocket, our new 1.3 GHz and 2.4 GHz, 8 digit frequency counters are not toys! They can actually out perform units many times their size and price! Included are rechargeable Ni-Cad batteries installed inside the unit for hours of portable, cordless operation. The batteries are easily recharged using the AC adapter/charger supplied with the unit.

The excellent sensitivity of the 1300H/A makes it ideal for use with the telescoping RF pick-up antenna; accurately and easily measure transmit frequencies from handheld, fixed, or mobile radios such as: Police, firefighters, Ham, taxi, car telephone, aircraft, marine, etc. May be used for counter surveillance, locating hidden "bug" transmitters. Use with grid dip oscillator when designing and tuning antennas. May be used with a probe for measuring clock frequencies in computers, various digital circuitry or oscillators. Can be built into transmitters, signal generators and other devices to accurately monitor frequency.

The size, price and performance of these new instruments make them indispensable for technicians, engineers, schools, Hams, CBers, electronic hobbyists, short wave listeners, law enforcement personnel and many others.

STOCK NO:

- #1300H/A Model 1300H/A 1-1300 MHz counter with preamp, sensitivity, < 1mV, 27MHz to 450MHz includes Ni-Cad batteries and AC adapter **\$169.95**
- #2400H Model 2400H 10-2400 MHz microwave counter includes Ni-Cad batteries and AC adapter **\$299.95**
- #CCA Model CCA counter/counter, for debugging, ultra sensitive, < 50 micro volts at 150MHz! 1-600 MHz with adjustable threshold, RF indicator LED. Includes Ni-Cad batteries and AC adapter **\$299.95**

ACCESSORIES:

- #TA-1005 Telescoping RF pick-up antenna with BNC connector **\$12.00**
- #P-100 Probe, direct connection 50 ohm, BNC connector **\$20.00**
- #CC-12 Carrying case, gray vinyl with zipper opening. Will hold a counter and #TA-10005 antenna. **\$10.00**



AVAILABLE NOW!

ORDER FACTORY DIRECT
FLA (305) 771-2050 **1-800-327-5912**



OPTOELECTRONICS INC.

5821 N.E. 14th Avenue
Ft. Lauderdale, Florida 33334

Orders to US and Canada add 5% of total (\$2 min, \$10 max)
Florida residents add 6% sales tax. COD fee \$2.
Foreign orders add 15%

CIRCLE 198 ON FREE INFORMATION CARD

www.americanradiohistory.com

RIP US OFF OUR NEW ELECTRONIC TOOL CATALOG IS A STEAL... IT'S FREE.

Paladin's new 1988 Electronic Tool Catalog shows you the latest selection of Paladin's top quality wire strippers, crimping tools, cutting tools and production aid equipment. 24 pages of the best specialty wire handling tools you can buy, and loaded with new products *on every page*. Chock so full of valuable productivity enhancing tools that it's hard to believe it's free. Be a thief and rip out this ad. Your new Paladin tool catalog will be on its way even before guilt sets in.



Name _____
 Title _____
 Company _____
 Address _____
 City _____
 State _____ Zip _____
PALADIN CORPORATION
 The Wire Handlers
 3543 Old Conejo Road, #102, Newbury Park, CA 91320 (805) 499-0318
 RE 9/88

CIRCLE 182 ON FREE INFORMATION CARD

businesses. There is a need for support and exchange among non-business users. To that end, we are announcing the publication of the first issue of the *Amateur Computerist Newsletter*, named in honor of Stephen Gray's pioneering interchange.

We want to encourage amateur computer users to write and share what they are doing with their computers—their successes and achievements, and their problems. We will try to support and encourage amateur use of computers, and to facilitate communication between users.

We recognize the important role **Radio-Electronics** has played in the history of the personal computer, by publishing Jonathan Titus' Mark-8 in July 1974. (*Editor's Note: H. Edward Roberts, M.D., author of the "Radio-Electronics Advanced Control System" series, is the same Ed Roberts of Altair 8800 fame.*) We're sure that many **Radio-Electronics** readers will be interested in the *Amateur Computerist Newsletter*, and we hope they will write to us giving details of how they are using their computers; what uses they are most proud of, which programs are most useful, problems they've encountered, and programs they've created.
RONDA HAUBEN
Amateur Computerist Newsletter
 P. O. Box 4344
 Dearborn, MI 48126

NON-CLONE COVERAGE
 "Do it yourself"—I can't believe I read that in **Radio-Electronics**! Although you have some very valid points about budgeting your efforts to cover computers for the greatest return, you may have really frosted some of your readers with your response to Carl Kona. ("Letters," July 1988.)

I, too, own a non-clone home-computer system, and I, too, get miffed at seeing virtually all the technical journals ignoring any system that is not IBM-PC compatible. It is heartwarming to see Apple's MAC's making serious inroads into the PC jungle, and frightening to see that **Radio-Electronics** is not.

It is especially frustrating to see that tunnel-vision attitude in a journal such as **Radio-Electronics**. I

DOES YOUR DIGITAL CAPACITANCE METER DO THIS?

FULL 4 DIGIT 0.5 INCH LCD DISPLAY COMPLETELY AUTORANGING WITH 10 RANGE MANUAL CAPABILITY

- AND THIS**
RANGE OF 0.0 pF to 1 FARAD (999.9 mF)
0.5% BASIC ACCURACY UP TO 100 uF
- AND THIS**
READS DIELECTRIC ABSORPTION
- AND THIS**
EXTENDED PSEUDO 5 DIGIT
RESOLUTION ON SOME RANGES ONLY
- AND THIS**
ABILITY TO ZERO LARGE CAPACITANCE
VALUES UP TO 99.99 uF
- AND THIS**
CALCULATES TRUE CAPACITANCE
IF CAPACITOR IS LEAKY
- AND THIS**
DIODE CLAMP AND FUSED
PROTECTED INPUT,
DISCHARGE RESISTOR IN OFF
POSITION AT TERMINAL INPUTS.
POWERED BY 9V BATTERY
- ONE YEAR PARTS &
LABOUR WARRANTY**
- FOR ONLY THIS**



- AND THIS**
IDENTIFIES TRANSISTORS (NPN, PNP)
AND THEIR LEADS (E, B, C, ETC.)
- AND THIS**
TESTS ZENER DIODES AND RECTIFIERS.
UP TO 20V ZENER WITH AC ADAPTOR.
ZENER VOLTAGE WITH 9V BATTERY
DEPENDS ON ITS CONDITION
- AND THIS**
AUTOMATICALLY CALCULATES LENGTHS
OF CABLES IN FEET, METRES, MILES,
KILOMETRES (THEORETICAL RANGE
OF 9,999 MILES)
- AND THIS**
ABILITY TO SORT CAPACITORS IN
MANY DIFFERENT MODES
- AND THIS**
ABILITY TO READ LEAKY CAPACITANCE
(INSULATION RESISTANCE OR CURRENT)
- AND THIS**
CALCULATES TIME CONSTANTS WITH
USER DEFINED RESISTANCE VALUES
- AND THIS**
HOLD FUNCTION FREEZES DISPLAY

SHIPPING INSTRUCTIONS:

All units shipped out F.O.B. Buffalo NY via United Parcel Service (except Hawaii & Alaska) unless otherwise indicated (in which case shipments will be F.O.B. Canada)

\$189.95

MODEL
MC300 Approx. Size
 7" x 4" x 1 3/4"
DAETRON
 a division of Bergeron Technologies Inc.
 935 THE QUEENSWAY, BOX 641
 TORONTO, ONTARIO M8Z 5Y9
 CANADA (416) 676-1600


PLEASE SEND ME		U.S. FUNDS
(QUANTITY) MC300(S) @	\$189.95	\$ _____
CARRYING CASE	\$ 16.95	\$ _____
AC ADAPTOR	\$ 9.95	\$ _____
SHIPPING AND HANDLING @ \$5.00 PER INSTRUMENT		\$ _____
<input type="checkbox"/> CHECK <input type="checkbox"/> MONEY ORDER		\$ _____
<input type="checkbox"/> VISA <input type="checkbox"/> MASTERCARD	TOTAL	\$ _____
<input type="checkbox"/> CARD NO _____		
EXPIRY DATE _____	SIGNATURE _____	
NAME _____	TELEPHONE _____	
ADDRESS _____		
CITY _____ STATE _____	ZIP CODE _____	

DEALER ENQUIRIES INVITED

CIRCLE 192 ON FREE INFORMATION CARD

Now from NRI comes the first course of its kind . . . anywhere!

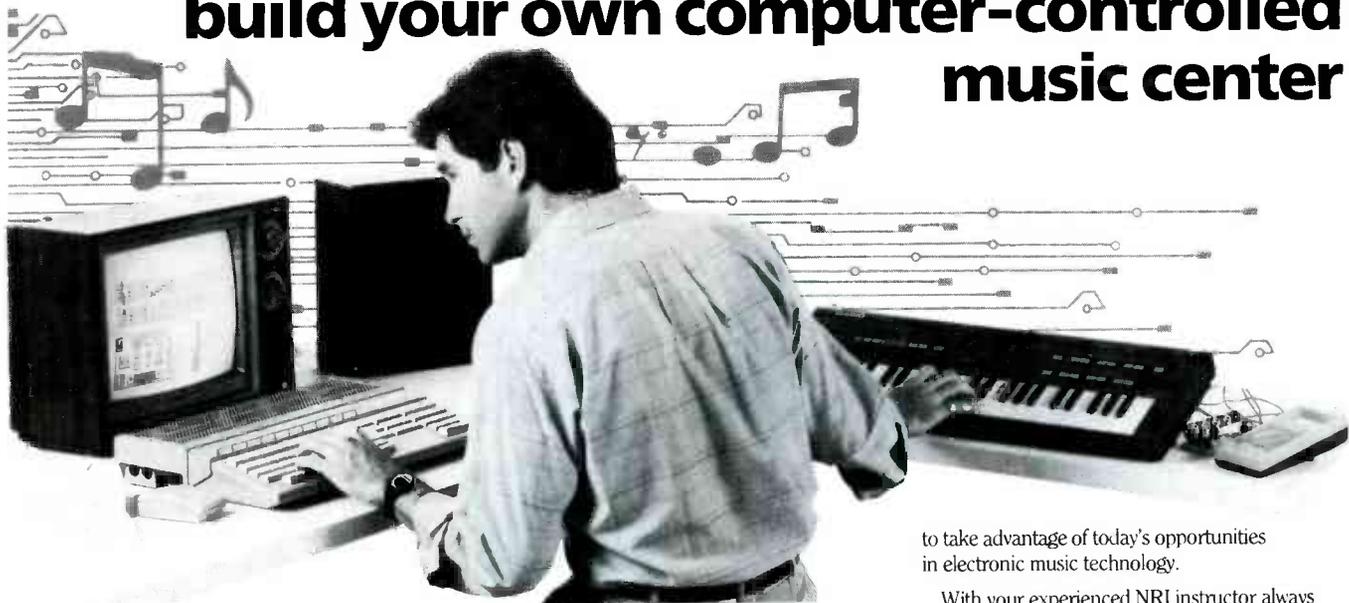Learn to use, program, and service today's digital electronic music equipment as you build your own computer-controlled music center



Now NRI puts you at the heart of the most exciting application of digital technology to date! With NRI's new at-home training in Electronic Music Technology, you get hands-on experience with the equipment that's revolutionizing the music industry—Atari ST Series computer with built-in MIDI ports, Casio CZ101 digital synthesizer with advanced MIDI capabilities, and ingenious MIDI software that links computer keyboard to synthesizer keyboard—all yours to train with and keep.

This year, over \$1.5 billion worth of digital electronic music instruments—keyboards, guitars, drum machines, and related equipment—will be sold in the U.S. alone. Who's buying this new-tech equipment? Not just progressive musicians and professional recording technicians, but also thousands of people who have never touched a musical instrument before. And there's good reason why.

Something called MIDI (Musical Instrument Digital Interface) has suddenly transformed musical instruments into the ultimate computer peripherals . . . and opened up a whole new world of opportunity for the person who knows how to use, program, and service this extraordinary new digital equipment.

Now NRI's breakthrough Electronic Music Technology course puts you at the forefront of this booming new technology with exclusive hands-on training built around a MIDI-equipped computer, MIDI synthesizer, and MIDI software you keep.

Dynamic New Technology Opens Up New Career Opportunities for You

The opportunities are unlimited for the person who's trained to take advantage of today's electronic music phenomenon. Now you can prepare for a high-paying career as a studio technician,

sound engineer, recording engineer, or road technician . . . even start your own new-age business providing one-stop sales and service for musicians, technicians, and general consumers alike. Or simply unleash your own musical creativity with the breakthrough training and equipment only NRI gives you.

Only NRI Gives You an Atari ST Computer, Casio Synthesizer, and Innovative MIDI Software You Train With and Keep

The Atari ST Series computer included in your course becomes the heart of your own computer-controlled music center. With its tremendous power, superior graphics capabilities, and built-in MIDI interface, the 16/32-bit Atari ST has almost overnight become the computer of choice for today's most knowledgeable electronic musicians.

The Casio CZ101 digital synthesizer, also included in your training, is the perfect complement to your Atari ST. The polyphonic, multitimbral CZ101—which stores up to 32 voices internally—"communicates" with your ST computer through MIDI, bringing life to virtually any sound you can imagine.

Plus, you get ingeniously designed MIDI software that opens up amazing new creative and technical possibilities . . . you actually build your own 4-input audio mixer/amplifier . . . and you test the electronic circuits at the core of today's new-tech equipment with the hand-held digital multimeter included in your course.

No previous experience necessary—in electronics or music!

No matter what your background, NRI gives you the skills you need

to take advantage of today's opportunities in electronic music technology.

With your experienced NRI instructor always available to help, you master the basics of electronic theory step by step, gaining the full understanding of electronics that's now so essential for technicians and musicians alike. You move on to analyze sound generation techniques, digital logic, microprocessor fundamentals, and sampling and recording techniques . . . ultimately getting first-hand experience with today's explosive new technology as you explore MIDI, waveshaping, patching, sequencing, mixing, special effects, and much more.

Plus, even if you've never been involved with music before, NRI gives you enough basic training in music theory and musical notation to appreciate the creative potential and far-reaching applications of today's electronic music equipment.

Send Today for Your FREE Catalog

For all the details about NRI's innovative new training, send the coupon today. You'll receive a complete catalog describing NRI's Electronic Music Technology course plus NRI courses in other high-tech, in-demand electronics fields.

If the coupon is missing, write to NRI School of Electronics, McGraw-Hill Continuing Education Center, 3939 Wisconsin Avenue, Washington, DC 20016.

NRI School of Electronics		
McGraw-Hill Continuing Education Center 3939 Wisconsin Avenue Washington, DC 20016		
<input checked="" type="checkbox"/> CHECK ONE FREE CATALOG ONLY		
<input type="checkbox"/> Electronic Music Technology	<input type="checkbox"/> Computers and Microprocessors	
<input type="checkbox"/> TV/Video/Audio Servicing	<input type="checkbox"/> Basic Electronics	
Name _____	(Please Print)	Age _____
Street _____		
City _____	State _____	Zip _____
NRI is accredited by the Accrediting Commission of the National Home Study Council 10-098		

always thought that "diversity" and "ingenuity" were two of the buzzwords in your editors' vocabularies. I guess not, if their excuse for not investigating Atari's and CoCo's is that they "grew up on CP/M and later moved to MS-DOS systems" and that's all they know. Thank goodness the computer/electronics industry as a whole does not operate on that same kind of philosophy! We'd still be using tubes and analog computers if it did.

I fully respect the amount of time, effort, and money that goes into just keeping up, never mind diversifying into low-popularity areas. However, as a leading reference journal for so many novice (and expert) computer users and technicians, shouldn't **Radio-Electronics** give space to some of the "other guys" in the world of non-compatible systems? I was shocked at the strength of your rejection in your reply to Mr. Kona. Go away, kid, you bother me! I

honestly cannot believe that that is really your policy.

After all, does a good tech know only one class of electronics? No, a good tech diversifies to learn analog, digital, radio, and computer (not just MS-DOS).

It would benefit us all—editors and readers alike—if you could diversify a little. Your surveys show that 80% of your readers use clones. Too bad the other 20% can't get equal time, proportionally. How much of your resources would it take to publish an article or series on non-clones once a quarter?

Come on guys, let's get with it!
RAY LaBRECQUE JR.
Huntington, MA

MORE ON NON-CLONES

I wish to express my disappointment with the editorial policy of the *ComputerDigest* section of **Radio-Electronics**. It seems locked in with the IBM and the Commodore. Out here in the West, quite a number of Apples are being used, especially in the schools.

I hope you will abandon that myopic approach.
ED GILLIS
Central Valley, CA

ANTIQUÉ-RADIO REPAIR

In the July 1988 issue of **Radio-Electronics**, Mr. Fitch gave some pointers on the repair of antique automobile radios in his "Antique Radio" column. Regarding the repair of vibrators, that service is advertised regularly in the publication *Hemmings Motor News* (P. O. Box 100, Bennington, VT 05201.) Other services advertised are speaker rebuilding, transistorized vibrator substitutes, complete radio rebuilding, and FM conversion is also available.

I have no experience with any of those advertisers, so I cannot vouch for their workmanship. I hope this information will be of some help to the readers of **Radio-Electronics**.

ROGER RAVENSBORG
St. Paul, MN

RADIATION SCARE TACTICS

As a subscriber to **Radio-Electronics** since 1949, I have appreciated the technical quality of the



SEEK PROFESSIONAL HELP

Servicing electronic equipment isn't always easy, especially if you're doing it in the field. At Chemtronics we can help with over 200 specially engineered products for the maintenance, repair and production of high technology equipment. Call today for our latest problem solving catalog.

Chemtronics
 Keeping pace with advanced technology

Chemtronics Inc. 681 Old Willets Path Hauppauge, NY 11788 516-582-3322 Telex 968567

articles. I am writing now because of the articles on the radiation monitor (June and July 1988).

While I could not fault the electronics aspects, the discussion of health effects smacks of yellow journalism. For those readers unfamiliar with the biological effects of radiation, such comments could be alarming—and I suspect that that is why they were made.

You are probably unaware that there is a negative correlation between the presence of radon and lung cancer. In other words, those areas with the highest concentration of radon have a lower incidence of lung cancer. The EPA set the radon standard by measuring the radon content in uranium mines without regard for the dust particles containing radioisotopes that are deposited in the lungs. The guideline of 4 picocuries per liter of air is a number that the EPA pulled out of thin air. There is nothing to support that.

It is unfortunate that John Gofman was chosen as an authority on the hazards of radiation, as he is at odds with most authorities on the effects of radiation. After Gofman testified at one hearing, the judge commented, "This court does find that Dr. Gofman's dramatic conflict with all the world's radiation experts creates a bias in him which destroys his credibility as an objective witness in radiation cases. His obsession blinds his objectivity."

The July article states that there are "differences of opinion on the ability of Geiger counters to detect radon." I don't know what the window of the GM1 tube is made of, but I can guess that alpha particles do not penetrate it. A Geiger counter can measure some of the radon daughters, but I doubt that it measures radon.

In the future, I would suggest that you stay with what is technically correct, and stay away from scare tactics. The *Journal of Health Physics* can handle the biological effect of radiation considerably better than you can.

LESLIE P. McCARTY, Ph.D., DABT
Midland, MI 48640

THE MUSIC LIBRARY

I'm sure that *Radio-Electronics'* readers will be interested in the

National Music Library, a nonprofit organization established in February 1988. High-quality compact discs, cassette tapes, sheet music, and other musical items can be taken out free of charge, by mail, through the National Music Library organization.

The library's circulation contains a large selection of compact discs and tapes of all types of music, including rock, classical, country, and jazz.

For library card-information, write to the National Music Library, 1994-A202 Woodward Ave., Bloomfield Hills, MI 48013.

ALAN FOXX

Chairman, National Music Library

LEGAL LISTENING

Regarding Forrest Mims III's letter in the May 1988 issue of *Radio-Electronics*: If Mr. Mims had his way, possessing an ordinary pencil would be against federal law as it could be used as a weapon to kill. It would be "assuming a fact not yet in evidence" to prohibit a device simply because it *could* be used in the commission of a violation of the law.

Section 2511 2 (d) of the U.S. Federal Title 18 states "It shall not be unlawful under this chapter for a person not acting under the color of law to intercept a wire or oral communication where such person is a party to the communication or where one of the parties to the communication has given prior consent to such interception unless such communication is intercepted for the purpose of committing any criminal or tortuous act in violation of the Constitution or laws of the United States or of any State or for the purpose of committing any other injurious act."

The word "intercept" is defined in section 2510 (4) as "the aural acquisition of the contents of any wire or oral communication through the use of any electronic, mechanical, or other device."

Just for the record, there are many devices on the market that are specifically designed for "listening and/or recording purposes" that are legally sold and registered with the FCC.

RICHARD A. BOWEN
Hudson, NH

R-E

Put a
test lab in
your tool pouch.



The Fluke 8060A 4½-digit handheld multimeter.

It's the best tool you could add to your tool pouch, because it lets you troubleshoot more ... with less.

This portable, powerful instrument has a unique combination of features not available in any other handheld DMM.

A simple push of a button on the Fluke 8060A lets you measure frequencies to 200 kHz, make relative offset measurements, convert voltages to direct reading decibels, or conduct audible continuity tests. Plus the 8060A offers wideband True RMS ac measurement capability to 100 kHz.

So say goodbye to your part-time counters, oscilloscopes, continuity testers, calculators and power supplies. And welcome a full-time professional that'll be there when you need it.

You'll find that for troubleshooting everything from motor controls to data communications equipment, the Fluke 8060A is the best multimeter value going.

Find out more by calling our toll-free hotline 1-800-44-FLUKE, ext. 33, day or night.

FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.

FLUKE[®]

©1988 Fluke

Ad No 0183-F8060

CIRCLE 121 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

Psion Organiser II Handheld Computer

A "lifestyle compatible"
pocket computer



CIRCLE 48 ON FREE INFORMATION CARD
ONE OF THE MOST INTERESTING PRODUCTS displayed at this summer's CES (Consumer Electronics Show) was a handheld computer called the *Organiser II* from Psion Incorporated (320 Sylvan Lake Road, Watertown, CT 06779).

The computer, which its manufacturer likes to call "lifestyle compatible," is designed to replace address books, phone books, appointment books, diaries, Rolodexes, calculators, expense logs, message pads, and so on. But emphasizing those capabilities is selling the computer short. The *Organiser* can become

a versatile and powerful tool if it is so programmed. In fact, prior to this year, the *Organiser* was available in the U.S. only to OEM's and VAR's, who custom-programmed the powerful computer for their clients. (The *Organiser* was introduced in Europe in mid-1986, where it has since been the best-selling new consumer-electronics product.)

Before we look at any applications for which the computer can be programmed by the user, we should point out that right out of the box, the computer's built-in functions are impressive. Also, several applications programs are now available from Psion and others.

Technical specifications

The *Organiser's* microprocessor is an 8-bit CMOS 6303 running at a speed of 1 MHz. (The 6303 is in the 6800 family.) The computer's internal RAM is 16K on the model *XP*, which we evaluated, and 8K on the less-powerful model *CM*. The built-in ROM, which contains the operating system and programming language, is 32K on both models. Two "solid-state drives" are built in to the computer.

The drives accept up to two special "solid-state disks"—up to a total of 128K on the *XP*, or up to 64K on the *CM*. Those solid-state disks are either special EPROM's, or battery-backed RAM modules. Software for the *Organiser* is distributed in pre-programmed PROM's. Blank EPROM's are also available for data storage. As shown in Fig. 1, the EPROM modules plug into the side of the computer. They are flush with the case when fully installed, and are protected by the slide-up protective case when the cover is closed.

The computer includes an interface port. While the port isn't stan-

dard, it can be made so with the addition of the *Comms Link*, an optional RS-232 interface that allows the *Organiser* to communicate with other computers, printers, modems, etc. Other peripherals, including a bar-code reader and a magnetic card reader, are available.

The *Organiser* is powered by a standard 9-volt alkaline battery, and an optional AC adapter is available. The computer consumes from 50 microamps to 100 milliamps depending on its operating mode. Expected battery life is from 2 to 6 months. When the battery is removed for replacement (the computer tells you when it's time), RAM-stored data are protected for more than half a minute.

The computer has some limited audio capabilities. Under software control, it can output tones from 11 Hz to 10 kHz with durations from 1 millisecond to 30 seconds.

The *Organiser*, including its protective case is about 6×3×1 inches and weighs about half a pound. Its display is a 2-line by 16-character dot-matrix LCD, and its keyboard had 36 keys arranged in an ABC sequence.

Using the Organiser

Right out of the box, the *Organiser* is ready to help you get organized. Its menu at power up is: FIND, SAVE, DIARY, CALC, PROG, and ERASE. Scrolling down through the menu yields the further choices: TIME, INFO, ALARM, COPY, RESET, and OFF. All menu choices can be run by moving the cursor over the appropriate word and pressing the EXE key. When you become familiar with the system, you can take shortcuts by simply entering the first letter of any menu choice whether or not it is displayed.

While many of the functions are

more-or-less self explanatory, some require a bit of explanation. FIND retrieves records that have been previously saved; SAVE writes a record to memory—either internal RAM or to a Datapak. DIARY is a sort of appointment book with alarms. CALC turns the *Organiser* into a full-function calculator. PROG puts the *Organiser* into the programming mode. Programs are written in a specialized procedure-based language called OPL (*Organizer Programming Language*). ALARM allows you to set up to eight alarms, each of which can be set to ring once, hourly, daily, or weekly. INFO gives memory-status information.

With those basic built-in functions, the *Organiser* can become a replacement for appointment books, address books, and the like. With plug-in *Software Paks* (pre-programmed ROM's) it can become much more. Currently available *Paks* include *Pocket Spreadsheet* (which allows up to 26 columns by 99 rows and accepts Lotus worksheets) a bank-account program, a spelling checker,



FIG. 1

Maths Pak (which can solve Bessel functions, polynomial equations, matrices, and the like), and *Travel-Pak* (which does some language translation, provides international dialing assistance, metric conversions, etc.). We're sure that many additional program packs will become available as well.

Of course, since the *Organiser*

contains its own programming language, OPL you its potential applications are almost endless. For example, an Alabama company created a program that calculates the impact of the sugar in various foods on a diabetic's blood system. The diabetic patient need only punch in the type of food he plans to eat, and the *Organiser* will then calculate the amount of insulin the diabetic should take. Other real-world dedicated programming examples include programs that calculate—based on input measurements—the amount of material needed for the flooring and wall-covering of a room. With the addition of a bar-code reader, the *Organiser* can become a portable inventory logger.

In Britain, a drug smuggler used the *Organiser* to record his transactions, and the names of his associates. He was tipped off that the police were set to grab him, and was erasing the last *Datapak* as he was seized. (Unfortunately for him, he didn't realize when data is erased from the *Datapak* EPROM, it's only removed from the display

GUARANTEED PERFORMANCE!!

METERS	SCOPES	POWER SUPPLIES	IC TESTER
FLUKE 73 3 1/2" digit, DMM \$67 75 3 1/2" digit, DMM 99. 77 3 1/2" digit, DMM 128. 8060A 4 1/2" digit-true RMS 323. 8062A 4 1/2" digit-true RMS 260. 37 Bench portable DMM 217. 8010A Bench portable true RMS 255. 8012A Bench portable true RMS 318. 8050A Bench portable true RMS 349. FULL LINE AVAIL BECKMAN <i>Beckman Industrial</i> DM15B 3 1/2" digit, 26 ranges, beeper \$51.98 DM25L 3 1/2" digit, 29 ranges, logic probe, cap measure 94.50 DM850 4 1/2" digit, frequency counter, data hold 207.83 Tech300 Diode Test 113.00 Tech330 True RMS, Diode Test 206.00 DM73 Probe-Auto-ranging, beeper, data hold 55.00 CC6 Clamp-on meters (measure up to 600 amps) 68.18 DM10 3 1/2" digit 38.	HITACHI <i>Special</i> 3 Years Manufacturers Warranty parts & labor V-212 20 MHZ dual trace scope \$385. V-222 20 MHZ dual trace scope 550. V-423 40 MHZ dual trace, delayed sweep scope 795. V-660 60 MHZ dual trace scope V-665 60 MHZ dual trace cursor readout scope V-1060 100 MHZ dual trace scope V-1065 100 MHZ/cursor readout scope V-6020 20 MHZ digital storage scope Beckman 9020 20 MHZ dual trace scope, component tester, delay sweep B&K 2120 20 MHZ dual trace scope \$455.	Viz WP-702A Dual 0-20VDC (or 0-200MA, dual meter) \$190. WP-703A Single 0-20VDC (or 0-500MA, single meter) 146. WP-704A Single 0-40VDC (or 0-250MA, single meter) 146. WP-705A Single 0-50VDC (or 0-2A, digital meter) 349. WP-706A Single 0-25VDC (or 0-4A, digital meter) 370. WP-707A Dual 0-25VDC (or 0-2A, digital meter) 465. WP-31A Isolation transformer 1.5KVA, 3 fixed 350VA outputs 223.78 B&K 1610 Power supply 0-30VDC, 0-1A \$ 147. 1630 Power supply 0-30VDC, 0-3A 228.80 3011 Function generator 0.2 HZ - 2MHZ 217.	B&K 560 Programmable IC tester \$2970. 541 Component tester 354. 550 T.T.L. IC comparator 364. 552 CMOS I.C. comparator 364. SOLDERING SUPPLIES Ungar UTC 100 Temperature controlled soldering system \$67 4024 De-soldering service station 414. 9000 Temperature controlled soldering station 208. 6970 HD Heat gun (gives 1000 watts) 72. 1095 Heat gun (gives 1000 watts) 35. 1100 Soldering gun 100/140 watts 20. WELLER WTCPR Control output soldering station \$119. 8200 All purpose soldering gun 21. D550 28.58 <i>Kester solder and multicore solder available CALL!</i>

Tool Kits Our Specialty — Call

KELVIN **FREE CATALOG** **1-800-645-9212**

ELECTRONICS 7 FAIRCHILD AVE., PLAINVIEW, N.Y. 11803 (516)349-7620 FAX:516-349-7830

"I GUARANTEE YOUR SATISFACTION!"
 For 43 years professionals have counted on KELVIN, for the lowest prices and immediate delivery, from our huge inventory. Count on KELVIN!
 Lisa S. Hadar
 Executive V.P., C.P.A.
WE CARRY
 Panavise, Xcelite Tools, Vaco Tools, X-Acto, Kester Solder, Sellstrom Safety Equipment
 • Electronic Parts
 • Electrical Parts
 • Large Selection of State of the Art Educational Kits.
 Not Responsible For Typographical Errors.

CIRCLE 185 ON FREE INFORMATION CARD

Radio-Electronics mini-ADS

as a housekeeping chore. It's still programmed into the EPROM.) Now, RAM *Datapaks*—backed up by an internal battery—are also available.

We've had a lot of fun putting the *Organiser* through its paces. For the most part, the *Organiser*, although powerful, is easy to use, and its manuals are well written, although we did find the *Comms Link* manual to be a bit convoluted.

The *Organiser* model *XP* is priced at \$249.99, while the less powerful model *CM* is priced at \$179.99. The RS-232 link costs \$99, and program paks range from \$49.99 to \$129.99. **R-E**

READER-HELP-READER

● SAMUEL DA ROCHA FONSECA FILHO was happy with his Marantz 4400 receiver, until the filament of the cathode ray tube broke down. He needs a new one, but can't locate the 50TB1, 3-inch, 14-pin cathode ray oscilloscope tube anywhere. Send any information to *Rua Dias da Cruz, 417; 20720 - Rio de Janeiro, Brazil.*


● IVAN RODRIGUEZ has a single-trace, 5-MHz triggering oscilloscope. He wants a schematic with components and values for converting it into a dual-trace scope. Can you help? He's at *325 East 106th St., #13-F, New York, NY 10029-4808.*

● Any assistance you can give RAY MARTIN would be greatly appreciated. He's looking for a vibrator/chopper for a 1956 Plymouth car radio, MOPAR model *916-HR*. He doesn't have any specs on it (no schematic), and the part number on the old one is no longer readable. The radio is an original and works otherwise. It has three vacuum tubes (a 12AX4 and two 12AB5's) that must draw some power. If you can help him locate the vibrator/chopper—or a solid-state replacement for it—write to Ray at *2531 Melrose Dr., Wooster, OH 44691.*




FREE CATALOG OF HARD-TO-FIND TOOLS is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85044. (602) 968-6231.**

CIRCLE 115 ON FREE INFORMATION CARD

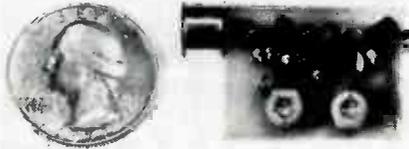


SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHz. Use with any FM radio. Complete kit **\$29.95 + \$1.50 S + H.** Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD

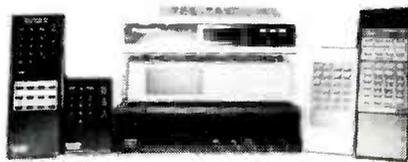

PANASONIC CABLE CONVERTERS, Wholesale and Retail. Scientific Atlanta and Pioneer Cable Converters in stock. Panasonic model 140N 68 channel converter **\$79.95**, Panasonic Amplified Video Control Switch Model VCS-1 **\$59.95**. Scientific Atlanta Brand new Model #8528 550MHZ 80 Channels Converter **\$89.95**. Video Corrector (MACRO, COPYGUARD, DIGITAL) ENHANCER **\$89.95**. We ship to Puerto Rico, Caribbean countries, & So. Amer. Write or call **BLUE STAR IND., 4712 AVE. N, Dept 105, Brooklyn, NY 11234. Phone (718) 258-9495.**


CIRCLE 85 ON FREE INFORMATION CARD

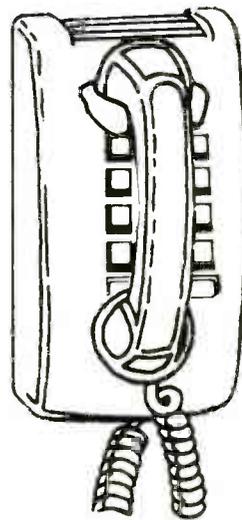

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$815.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

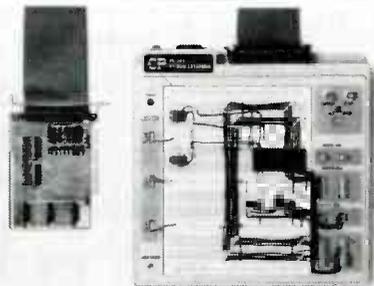Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.




PC-601 XT BUS EXTENDER BREADBOARD LAB connects to any IBM PC compatible computer and extends all PC electrical bus connections out to the PC-601 for easy circuit prototype connection, testing and trouble-shooting. Includes large 3060 tie-point breadboard, ±5V and ±12Vdc AC line powered power supplies. Includes buffer card, 2' ribbon cable & 1-Year warranty. Price: **\$369.95 CHENESKO PRODUCTS, 21 Maple St., Centereach, NY 11720. 516-736-7977, Fax: 516-732-4650**

CIRCLE 200 ON FREE INFORMATION CARD



2645T—117 PRACTICAL IC PROJECTS YOU CAN BUILD.....\$10.95. Dozens of fully-tested, ready-to-build circuits you can put together from readily-available, low cost IC's! There are a total of 117 IC circuits ranging from an audio mixer and a signal splitter to a tape-deck amplifier and a top-octave generator organ! From TAB Books. **To order your copy send \$10.95 plus \$2.75 shipping to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240**

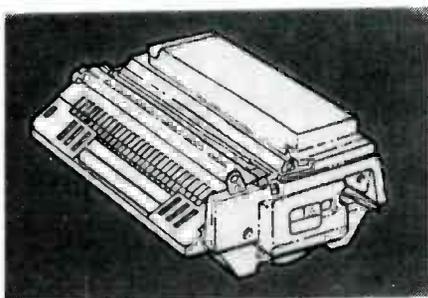

RECHARGE LASER PRINTER TONER CARTRIDGES—Earn big \$\$ in your spare time—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from **\$10.95** in qty and you can sell recharged toner cartridges for **\$40.00 to \$55.00** each. Printers include HP LaserJet and Series II, Apple LaserWriter, QMS, etc. Canon PC-25 Copier also. **CHENESKO PRODUCTS, 21 Maple St., Centereach, NY 11720, 516-736-7977, Fax: 516-732-4650**

CIRCLE 199 ON FREE INFORMATION CARD



APPLIANCE REPAIR HANDBOOKS—13 volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. **\$2.65 to \$7.90 each.** Free brochure. **APPLIANCE SERVICE, P.O. Box 789, Lombard, IL 60148. (312) 932-9550.**

CIRCLE 84 ON FREE INFORMATION CARD

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$815.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.




ZENITH SSAVI UHF input from **\$169**; ch.3 input **\$229**, reconditioned. UHF SSAVI project handbook **\$6.50** ppd. Used Sylvania 4040 w/remote **\$169**. N-12s **\$99**. Converters, amplifiers & accessories. Radar speed guns for car/boat racing, baseball, skiing, etc. Professional X and K band police models, from **\$275** used. Panasonic multi-line business telephone systems from **\$675**. Catalog **\$1**. **AIS SATELLITE, INC., 106 N. 7th St./S, Perkasie, PA 18944. 215-453-1400.**

CIRCLE 81 ON FREE INFORMATION CARD



THE DIGITAL TACHOMETER MONITORS engine speed with a fast, easy to read bar/graph along with an accurate digital readout. The Digital Speedometer's dual display delivers vehicle speed with a 3-digit readout and a rapid-read analog display. Adjustable redline on both units. Complete kits only **\$75.00 ea.** Assembled & tested **\$99.95 ea.** Add 4% S/H. 90 day warranty. Contact: **DAKOTA DIGITAL, 11301 Kuhle Drive, Sioux Falls, SD 57107. (605) 332-6513.** Visa/MC accepted. Dealer inquiries welcome.

CIRCLE 191 ON FREE INFORMATION CARD

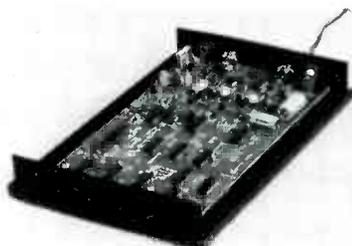

TRI-MODE DESCRAMBLER PARTS Original parts as called up in Radio Electronics Feb 1987 article on tri-mode descrambling. Includes pc board, ac adaptor, resistors, capacitors, diodes, pots, transistors, IC's, LED's, toko coil and Plessey SAW filter. Article included. **\$59** plus **\$2.50** shipping. **ELECTRONIC PARTS, Box 276, Alburg, VT 05440 (514) 739-9328.**

CIRCLE 80 ON FREE INFORMATION CARD



CHAPMAN MFG. CO. KIT #6320 IS THE most popular tool set in the Chapman line. This kit contains twelve allen hex type adaptors, two slotted, two phillips, one 1/4" square drive adapter plus a midget ratchet, screwdriver handle and extension. Packaged in a pocket sized (4" x 6") vinyl covered steel case. Only **\$22.94** plus **\$2.00** for shipping. Other kits available. Write for free brochures. **THE CHAPMAN MFG. CO., P.O. Box 250, Dept. RE-9, Durham, CT 06422. (203) 349-9228.**

CIRCLE 183 ON FREE INFORMATION CARD




THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to 1/4 mile range. Adjustable from 70-130 MHz. Complete kit **\$29.95 + \$1.50 S+H.** Free Shipping on 2 or more! COD add **\$4**. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD

Take any one of these HANDBOOKS ELECTRONICS and CONTROL

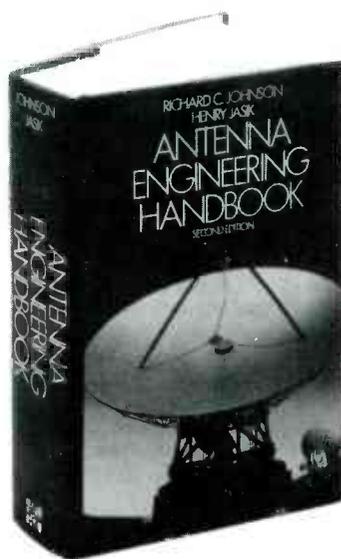- your one source for engineering books from over 100 different publishers
- the latest and best information in your field
- discounts of up to 40% off publishers' list prices



322/910

Publisher's Price \$110.00

ANTENNA ENGINEERING HANDBOOK, Second Edition

Edited by R. C. Johnson and H. Jasik


- 1,408 pages, 946 illustrations
- covers all types of antennas currently in use with a separate chapter devoted to each
- provides detailed data on physical fundamentals, operating principles, design techniques, and performance data
- up-to-the-minute information on antenna applications
- a must for those involved in any phase of antenna engineering

Publisher's Price \$64.50

STANDARD HANDBOOK OF ENGINEERING CALCULATIONS, Second Edition

By T. G. Hicks

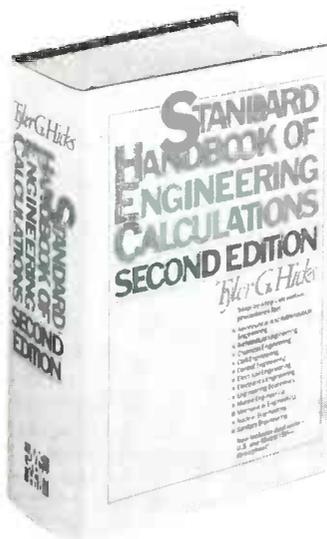- 1,468 pages, 793 illustrations, 499 tables
- puts more than 1,100 specific calculation procedures at your fingertips
- every calculation procedure gives the exact, numbered steps to follow for a quick, accurate solution
- virtually all procedures can be easily programmed on your PC or calculator
- uses USCS and SI units in all calculation procedures



287/35X



047/790

Publisher's Price \$89.50


TELEVISION ENGINEERING HANDBOOK

Edited by K. B. Benson

- 1,478 pages, 1,091 illustrations
- packed with all the technical information today's engineer needs to design, operate, and maintain every type of television equipment
- extensive coverage of receivers, broadcast equipment, video tape recording, video disc recording, and the latest technological advances
- provides television system and industry standards for the U.S. and other countries
- the most comprehensive book on the subject of television engineering

for only \$14.95 – when you join the ENGINEERS' BOOK CLUB®

values up to \$110.00

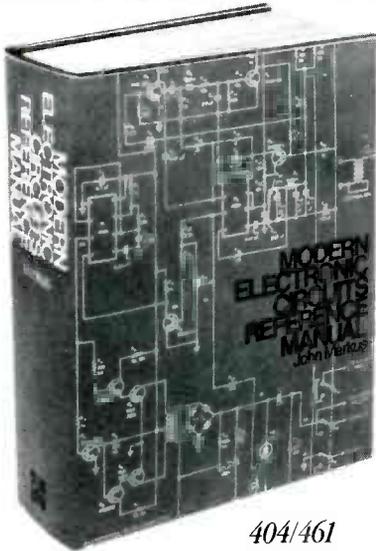

404/461

Publisher's Price \$82.50

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL

By J. T. Markus

- 1,264 pages, 3,666 circuit diagrams
- a handy, desktop reference with 103 chapters organized by "family" grouping
- filled with predesigned and use-tested circuits to save you production time and money
- includes concise summaries of all the recent applications notes, journal articles, and reports on each circuit, efficiently organized and indexed for the practicing engineer



4 reasons to join today!

1. Best and newest books from ALL publishers! Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

2. Big savings! Build your library and save money, too! Savings range up to 40% off publishers' list prices.

3. Bonus books! You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

4. Convenience! 14-16 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and alternate selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an alternate selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.


As a Club member you agree only to the purchase of three additional books during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the three additional books.

Publisher's Price \$86.50

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, Twelfth Edition

Edited by D.G. Fink and H.W. Beaty

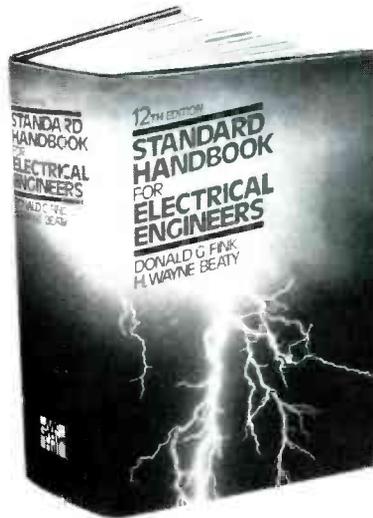- 2,416 pages, 1,388 illustrations, 430 tables
- the essential reference for all electrical engineers
- ranges from basic circuits and measurements to advanced topics, such as power distribution and telecommunications
- fully updated to cover all recent advances and developments
- written and compiled by 115 contributors — all experts in their fields



209/758

FOR FASTER SERVICE IN ENROLLING CALL TOLL FREE 1-800-2-MCGRAW

McGraw-Hill Book Clubs
Electronics and Control Engineers' Book Club®
 P.O. Box 582
 Hightstown, NJ 08520-9959

Please enroll me as a member of the Electronics and Control Engineers' Book Club® and send me the book I have chosen for only \$14.95, plus local tax, postage, and handling. I agree to purchase a minimum of three additional books during my first year as outlined under the Club plan described in this ad. Membership in the club is cancellable by me or McGraw-Hill any time after the three book purchase requirement has been fulfilled. A shipping and handling charge is added to all shipments.

I wish to order the following book:

- ANTENNA ENGINEERING HANDBOOK (322/910)
- MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL (404/461)
- STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 12/e (209/758)
- TELEVISION ENGINEERING HANDBOOK (047/790)
- STANDARD HANDBOOK OF ENGINEERING CALCULATIONS (287/35X)

Signature _____

Name _____

Address/Apt. # _____

City/State/Zip _____

This order subject to acceptance by McGraw-Hill. Offer good only to new members. Foreign member acceptance subject to special conditions.

E33996

NEW PRODUCTS



CIRCLE 10 ON FREE INFORMATION CARD

PERSONAL VIDEO. Sony introduces the concept of "Personal Video" with the *GV-8 Video Walkman TV/VCR-combination*. A portable hand-held unit, about the size of a paperback book, the *GV-8* contains a 3-inch diagonal color-TV screen and a complete VCR. With it, viewers can use and enjoy video virtually anywhere—while waiting for appointments, riding in the car, cooking in the kitchen, or at the beach or park.

Sony predicts that the *Video Walkman* will have the same affect on the video market as personal stereo had on the audio market, and expects consumer demand to

precipitate a boom in prerecorded 8mm-tape production. Other companies have already announced production plans for do-it-yourself instructional tapes, children's videos, full-length feature films, and video magazines called "videodicals"—all compatible with the *GV-8*. Sony's ultra-miniature *CCD-G1* color-video camera can also be used with the *Video Walkman*.

The *Video Walkman* measures 5 × 2½ × 8 inches and weighs about 2½ pounds. The color-LCD screen has an active-matrix system for superior sharpness, contrast, and color purity. A back-light built in

behind the screen provides a brighter picture and easier viewing in sunlight. The VCR has playback and recording capabilities of up to four hours on a single high-performance 8mm videocassette, in the extended-play mode.

The *GV-8's* VCR component features a high-speed picture search to scan recordings quickly, a one-day/one-event timer, a sleep timer, and a built-in TV tuner with full VHF and UHF channel reception. A linear time counter displays the tape position in hours, minutes, and seconds. Despite its compact size, the 8mm format yields a high-quality video image and high-fidelity sound. The *Video Walkman* has a built-in high-performance speaker for clear audio reproduction.

Although designed for personal use, the *GV-8* can be connected to a monitor for viewing by groups. Audio/video-input and output connectors allow for connection to another VCR—of any format.

The *Video Walkman's* telescoping antenna allows TV viewing in many locations. There is also an external-antenna connector for improved reception outdoors, or while travelling in a car. For indoor/outdoor flexibility, the *Video Walkman* unit operates on AC or DC current, rechargeable nickel-cadmium batteries, or alkaline batteries, when used with an optional external battery case.

The *GV-8*, complete with soft carrying case, will be available in late 1988 at a suggested retail price of \$1300.00.—**Sony Corporation of America**, Corporate Communications Department, 9 West 57th Street, New York, NY 10019.

UNIVERSAL REMOTE CONTROL. Onkyo has introduced a second-generation, lower-cost model of

the *Unifier* universal programmable remote control. The *RC-AV10* has enough memory functions to

control at least one of each unit found in a typical audio/video entertainment system.



CIRCLE 11 ON FREE INFORMATION CARD

The RC-AV10 has 55 programmable keys, clearly marked to control a television or cable box, two VCR's, two cassette decks, a compact disc player, and a full array of amplifier or receiver functions. Function keys for each component are in separate, clearly marked areas on the keypad. Programming is simplified by lighted displays that indicate the necessary procedures, step-by-step.

The suggested retail price for the RC-AV10 universal remote control is \$79.95.—Onkyo, 200 Williams Drive, Ramsey, NJ 07446.

DIGITAL-STORAGE SCOPE. Heath/Zenith's model SDS-5000 comes complete with menu-driven software. It plugs directly into a PC, or can be mounted in an instrument chassis, so it can be working within a few minutes after its arrival.

Dual analog-to-digital converters capture two channels simultaneously, without reducing the digitizing rate. The SDS-5000 has a real-time mode which samples data at up to 20 MHz with 4K memory depth, and 16K memory is available with the optional SDS-5000-16 Memory Upgrade. The digital-storage scope also has software-controlled 10-step attenuators for scaling input voltages from 40-mV to 40-volts full scale.

Users can examine both pre- and post-trigger events, zoom in

on trouble spots, and make cursor movements. Signal averaging, delayed sweep, infinite persistence, signal addition and subtraction, and file-saving retrieval can also be performed. The SDS-5000 Digital Storage Oscilloscope is priced at \$1995.00.—Heath/Zenith Computer-Based Instruments Group, Hilltop Road, St. Joseph, MI 49085.


IN-FLIGHT HEADPHONES. Air travelers can now enjoy music, movies, and other in-flight enter-

tainment on lightweight stereo headphones with premium-quality stereo sound. Lotus Developments Ltd.'s Jetset portable audio system provides an alternative—with increased comfort and better sound quality—to the standard airline headsets.

The Jetset system consists of a patented Airdapter amplifier which plugs into the plane's seat jack, and a set of lightweight headphones. The Airdapter features a pair of sensitive condenser micro-

Special INSTRUMENT SALE!

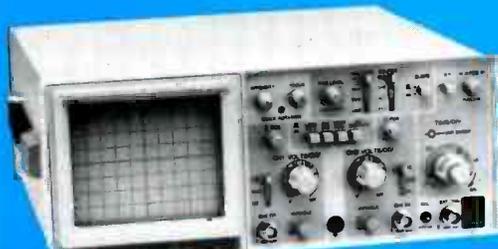Joseph Electronics' 40th Anniversary Specials!



Model 2120 Oscilloscope
DC to 20 MHz. Dual Trace, 6" CRT, 1mv Sensitivity.

Reg. \$520 **\$379.40**
40TH ANNIVERSARY PRICE

Model 2125 Oscilloscope

Same great features as 2120, except with delayed sweep
Reg. \$620 **\$519.40**
40TH ANNIVERSARY PRICE

Model 1541A Oscilloscope DC to 40 MHz, Dual Trace, 6" CRT 1mv Sensitivity
Reg. \$845 **\$739.40**
40TH ANNIVERSARY PRICE

Model 2160 Oscilloscope DC-60MHz, Dual Trace, delay sweep, 6" CRT, 1mv. sensitivity
Reg. \$995 **\$839.40**
40TH ANNIVERSARY PRICE

Model 2520 Digital Storage 20MHz, Dual Trace, 2mv Sens
Reg. \$1990 **\$1795.40**
40TH ANNIVERSARY PRICE

Model 2521 Digital Storage 20MHz, Dual Trace CRT Readout, Cursors, RS232 interface
Reg. \$3050 **\$2745.40**
40TH ANNIVERSARY PRICE

Model 1249 NTSC/RGB Color Bar Generator. Composite Video Output, RF Output
Reg. \$499 **\$419.40**
40TH ANNIVERSARY PRICE

Model 2009 MTS TV Stereo Generator Ideal for Stereo TV Receivers, VCR's and Stereo Adapter Service
Reg. \$499 **\$419.40**
40TH ANNIVERSARY PRICE

Model 2830 3 1/2 DIGIT LED BENCH Multimeter .5 DCV Accuracy, ALL 33 Ranges and Functions are Push Button Selectable
Reg. \$243 **\$209.40**
40TH ANNIVERSARY PRICE

Model 1045 Telephone Product Tester Provides Basic Operation Tests for Corded and Cordless Telephones, Answering Machines and Automatic Dialers
Reg. \$495 **\$415.40**
40TH ANNIVERSARY PRICE

Model 1803 Frequency Counter 100 MHz, 8 digit display, zero blanking AC or Battery
Reg. \$199 **\$169.40**
40TH ANNIVERSARY PRICE

Model 2005 RF Signal Generator 100 KHz to 150 MHz, in 6 fundamental bands and 450 MHz in harmonics
Reg. \$195 **\$165.40**
40TH ANNIVERSARY PRICE

Model 3011 Function Generator 2 MHz, 4 digit display, TTL & CMOS pulse outputs
Reg. \$239 **\$199.40**
40TH ANNIVERSARY PRICE

Model 1630 DC Power Supply 0-30V, 0-3A, high-low current range, Low ripple
Reg. \$251 **\$209.40**
40TH ANNIVERSARY PRICE

Model 1601 DC Power Supply isolated 0-50V, 0-2A in ranges, fully automatic shutdown, Adj. current limit
Reg. \$463 **\$389.40**
40TH ANNIVERSARY PRICE


Model 1650 Triple Output Power Supply two 0-25 VDC @ .5A and 5VDC @ 5A, fully automatic shutdown
Reg. \$489 **\$409.40**
40TH ANNIVERSARY PRICE

Model 1653 AC Power Supply variable isolated 0-150 VAC @ 2A, built-in isolation transformer
Reg. \$200 **\$169.40**
40TH ANNIVERSARY PRICE

NEW! Model 388-HD Hand-held 3 1/2 Digit LCD TEST BENCH

41 voltage ranges, frequency counter, capacitance meter, logic probe, transistor and diode tester. All packed into a drop-resistant case. **SPECIAL PRICE!**

Reg. \$139 **\$119.40**

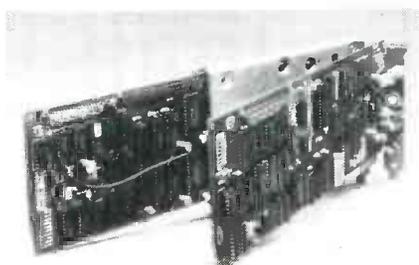

CIRCLE 12 ON FREE INFORMATION CARD

Send for FREE 480 page "Industrial Products Catalog." I understand it is FREE with any order or if requested on company letterhead. (Otherwise, \$4.95 to cover catalog and shipping costs.)

ORDER TOLL FREE
1-800-323-5925
IN ILLINOIS
312-297-4200
FAX: 312-297-6923



JOSEPH ELECTRONICS, INC. Dept. R
8830 N. Milwaukee Ave., Niles, IL 60648

Rush merchandise per attached order.
I understand rated accounts are shipped open account; otherwise send per credit card.

Include \$5.00 per item for shipping and handling.

Visa Master Card Discover
 Check Money Order Rush Catalog

Card No. _____ Exp. Date _____

Name _____

Company _____

Street Address _____

City _____ State _____ Zip _____

IL Res. 7% Tax

phones mounted in a specially designed seat connector, and acoustic "correction baffles" to filter excess hiss and sibilance from the sound source. Those microphones convert the airline's piped sounds to stereo electronic signals, which are amplified and then reconverted to sound by the stereo headphones. The stereo amplifier has a 30-20,000-Hz response and is protected from short circuits and reverse polarity.

Measuring only $3 \times 2\frac{3}{8} \times \frac{1}{2}$



CIRCLE 13 ON FREE INFORMATION CARD

inches, the *Airdapter* module is small enough to fit into a shirt pocket. It can be used on any plane fitted with the standard air-pipe audio connector, in any seating class, when in-flight entertainment is provided. The headphones can also be used with *Walkman*-style tape players.

The *Jetset* is powered by two AAA batteries. Power is automatically switched off when the headset is disconnected. It is priced at \$19.95, plus \$3.00 shipping and handling. (Illinois residents must add 8% sales tax.)—**Executive Travelware**, P. O. Box 59387, Chicago, IL 60659.

SOUND-MIXING SYSTEM. Designed for all "would-be" disc jockeys, the *Studio 4* sound-mixing system from Bondwell combines an audio console, sound mixer, and computerized-effect generator in one package.

The system features a built-in four-channel mixer, 6-function control cassette-deck recorder, microphone, and 3-inch speaker.



CIRCLE 14 ON FREE INFORMATION CARD

Studio 4 can be used to record music; to create sound effects, voice-overs, and dialogue; and to mix all the recorded elements together into a customized track.

The sound-mixing system also has plug-ins for a second cassette deck, status lights and record-level indicators, an AC/DC power transformer, and a headset.

Studio 4 retails for \$59.95; a stereo version is available for \$79.95.—



Prototyping Made Easy. In The Quantities You Require.

Your Electronic Specialty Products distributor has a wide selection of 3M breadboards and prototyping labs in the quantities and styles you desire.

We invented solderless breadboarding with one thought in mind: "make it fast and easy!" And we build these products with American made reliability.

Whether your requirements demand 3M's A·C·E 100 Series solderless breadboards or Powerace prototyping labs with self-contained power supplies, or our newest Powerace labs

with removable boards, you'll find what you need at your authorized 3M Electronic Specialty Products distributor.

For educators, students, hobbyists and even professional designers, 3M prototyping products make circuit building and testing fun and easy. And whether you need one breadboard or a hundred, we've got them packaged as you need them.

Your Electronic Specialty Products distributor also has all the prototyping tools you'll need. Tools such as jumper wires, adaptor pins and patch cords.

For the name of your nearest 3M A·C·E Board and Powerace distributor, call toll free 800-321-9668 or (216) 354-2101 in Ohio.

**Electronic Specialty Products
3M Electronic Products Division**

9325 Progress Parkway
Mentor, Ohio 44060

We've Packaged Our Solutions.




CIRCLE 76 ON FREE INFORMATION CARD

Bondwell, 47358 Fremont Blvd., Fremont, CA 94538.

A-D SCOPE CONVERTER. The *Model 2501 Digital Storage Adapter* adds the features of a true digital-storage oscilloscope to almost any analog oscilloscope. It provides dual-channel operation, an output connector for a hard-copy plotter, and 10-MHz per second sampling rate.

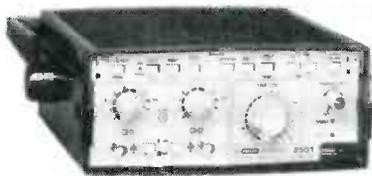The *Model 2501* connects to the oscilloscope with a simple three-lead hook-up. It is easy to operate, even for those who have never used a digital-storage oscilloscope before. By adding the adapter, even a simple analog scope can be used to capture single-shot events, to store and magnify waveforms for analysis, and to view pre-trigger information at either zero, 50%, or 100%.



CIRCLE 15 ON FREE INFORMATION CARD

The digital-storage memory is 2048 × 8; vertical resolution is 8-bits; and sampling rate is from 10-MHz per second to 2.5-MHz per second. The *Model 2501* has a suggested retail price of \$795.00.—**B&K Precision**, Division of Maxtec International Corp., 6470 West Cortland St., Chicago, IL 60635.

HOME-OFFICE FAX MACHINE. Sharp has introduced a "no-frills" facsimile, designed for use in



CIRCLE 16 ON FREE INFORMATION CARD

home offices by those who need fax capabilities but don't want to

pay for extra features that they don't really need. The compact unit, *Model UX-50*, has an integrated telephone handset and also has the ability to transmit and receive standard-size documents.

The *UX-50* measures 13.7 × 9.9 × 3.3 inches, and weighs 9 pounds, so it won't take up too much space. Its features include automatic reduction, on-hook dialing, contrast control, manual/automatic receiving selection, and redialing/pause function. The user

can also signal the receiving party and instruct them to pick up the phone to talk after the transmission is complete. The *UX-50* facsimile is equipped with a 50-second transmission speed, and it also has a fine mode to increase the resolution of transmissions, for documents that require it.


The *UX-50* is priced at \$1399.00.—**Sharp Electronics Corporation**, Personal Home Office Electronics Division, Sharp Plaza, Mahwah, NJ 07430. R-E



Celebrating our 10th Year in U.S.A. . . .

Proven Quality . . .

Factory Direct Prices!

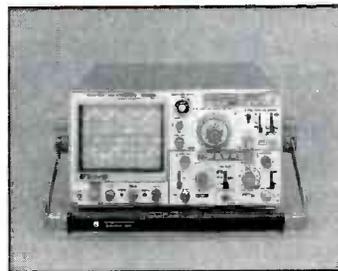


COS 5100: 100 MHz

- 3 Channel, 8 Trace
- P-P level-lock auto-trigger
- Delayed Sweep

Now Only
\$999.00

COS 5042TM, 40 MHz \$779.00

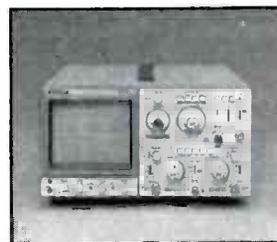

COS 5041TM

- 40 MHz, Delayed Sweep
- 2 Channel
- Ch 1 Signal Output

\$669.00

COS 5021TM

- 20 MHz, Delayed Sweep
- 2 Channel
- Ch 1 Signal Output

\$489.00



COS 5060TM

- 3 Channel, 8 Trace
- P-P level-lock auto-trigger
- Delayed Sweep

\$889.00

255 Frequency Counter:
150 MHz **\$299.00**

FCO1130 Frequency
Counter: 1GHz **\$739.00**

677D Wow and Flutter
Meter **\$949.00**

6701 Wow and Flutter
Meter **\$999.00**

COS 5040TM


- 40 MHz
- 2 Channel
- CH 1 Signal Output

\$639.00

COS 5020TM

- 20 MHz
- 2 Channel
- CH 1 Signal Output

\$449.00

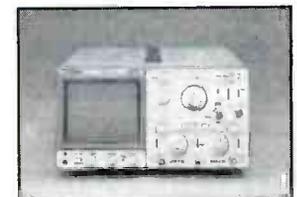

Add \$15 per unit shipping and handling.

(800) 545-8784

(213) 371-4662
Collect CA & AK

Local Service Centers
Nationwide



Kikusui International Corp.
19601 Mariner Avenue
Torrance, CA 90503

©Copyright Kikusui International Corp. 1988

CIRCLE 180 ON FREE INFORMATION CARD

Your Career in *ELECTRONICS* or *COMPUTERS*

Add *prestige and earning power* to your technical career by earning your Associate or Bachelor's Degree in electronics or computers—through independent home study.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand lessons, with help from your Grantham instructors when you need it.


Grantham College of Engineering is a specialized institution catering to adults who are employed in electronics and allied fields such as computers. These fields are so enormous that opportunity for advancement is always present. Promotions and natural turn-over make desirable positions available to those who are *prepared to move up!*

An important part of being prepared to *move up* is holding the proper college degree, but the absolutely essential part is *really knowing your field*. In electronics or computers, Grantham can prepare you in both ways. But don't expect to really know your field *or* earn that college degree without hard work. Any degree that's worth your while can't be had without giving effort to the task. Of course it's what you learn in the process, as much or more than the degree itself, that makes you stand out above the crowd — that places you and your career in an enviable position, prestige-wise and financially.

Why not "go for it"? Go for the knowledge, and the degree will follow naturally. Be a "can do" person, with the right credential to put your best "moving-up" foot forward!

Put Professional Knowledge and a
COLLEGE DEGREE

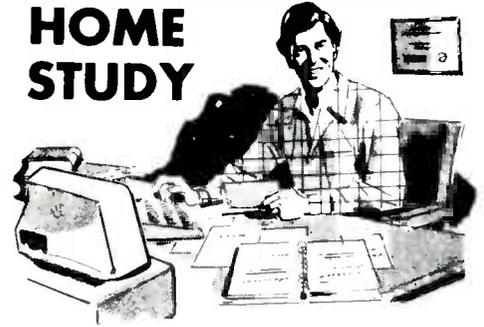in your Technical Career through
HOME STUDY




Accredited by the
Accrediting Commission of the National Home Study Council

Grantham College of Engineering
10570 Humbolt Street
Los Alamitos, California 90720

Write for our free catalog
(see coupon below) or phone
(213) 493-4421 (no collect calls)
and ask for our "degree catalog."

Grantham offers two B.S. degree programs — one with major emphasis in *ELECTRONICS* and the other with major emphasis in *COMPUTERS*. Either program can be completed by correspondence (also known as "distance education.") An A.S. degree is awarded along the way in each B.S. program, but the B.S. program is not complete without the A.S. part. Our catalog gives complete details.

Now in Our 38th Year

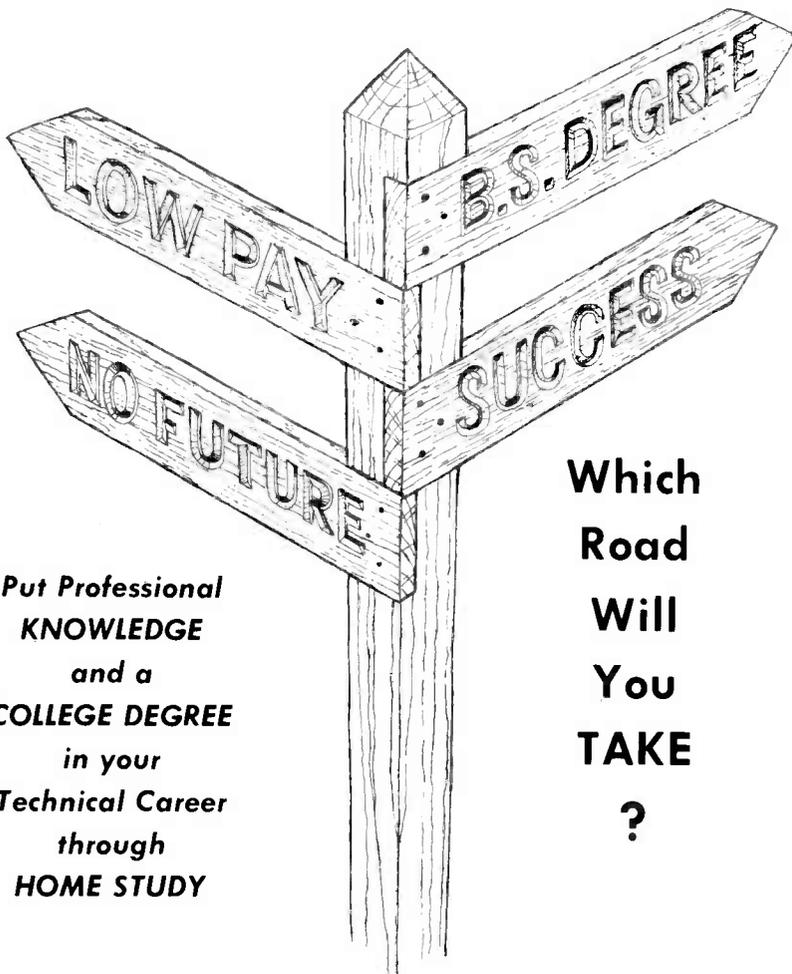

**Which
Road
Will
You
TAKE
?**

Put Professional
KNOWLEDGE
and a
COLLEGE DEGREE
in your
Technical Career
through
HOME STUDY

Grantham College of Engineering
P.O. Box 539, Los Alamitos, CA 90720

Please mail me your free catalog which explains your distance-education (home study) degree programs.

NAME _____

ADDRESS _____

CITY _____

STATE _____


ZIP _____

R-09-88

BUILD THIS

IN-CIRCUIT DIGITAL IC TESTER

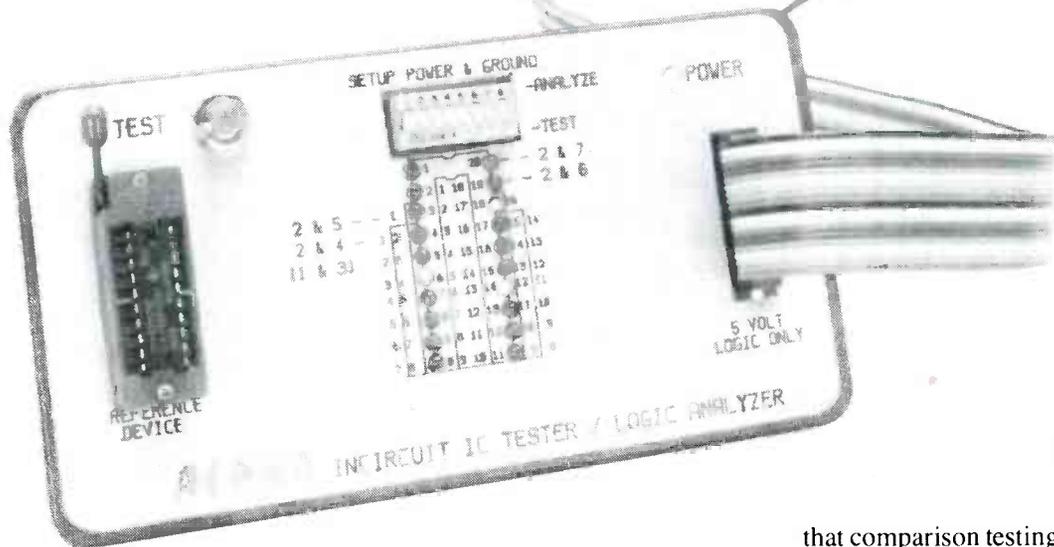Now you can test digital IC's without lifting a pin—or a probe!



BILL GREEN

ARE YOU TIRED OF HAVING TO CHECK EACH pin of a digital IC using some kind of probe? Do you hate having to look up truth tables in order to compare the inputs and outputs of IC's? Well, now you can stop wasting time troubleshooting IC's that are working in the first place. By using our in-circuit tester, you can check out the whole IC—while it's still on the board and operating—without having to investigate each pin separately. And our tester can do more than check IC's. It can also function as a 19-channel logic monitor.

There are several types of in-circuit IC testers that are now available. Some come equipped with a library of IC parameters stored in their memories, while others require the user to enter the testing parameters. Still others merely compare a known-good IC with an identical one that is operating in a circuit.

The first two types, although expensive and complex, do a superior job. The comparator-type tester, has the important advantage of being less

expensive—ours can be built for under \$100! But it also has a disadvantage: Because it is passive, it does not provide any stimulation to the IC being tested. As a result, a defective IC may appear to be good. An inverter with an output stuck low will appear bad only when its input is low.

While our tester is of the comparator type, it has both monitoring and testing capabilities. By selectively using its compare and monitor functions, we can determine whether the inputs of an IC are being exercised sufficiently—that is, in a way such

that comparison testing can be used to determine its quality. If not, we can move through the circuit using the tried-and-true methods of circuit tracing, along with comparison testing, until we can sort the good IC's from the questionable and obviously bad ones.

Circuit description

The in-circuit IC tester is based on four custom AE013 IC's. Custom IC's were used to make the tester as easy to build as possible. When you consider that each AE013 contains 5 independent comparator/latch/LED-driver


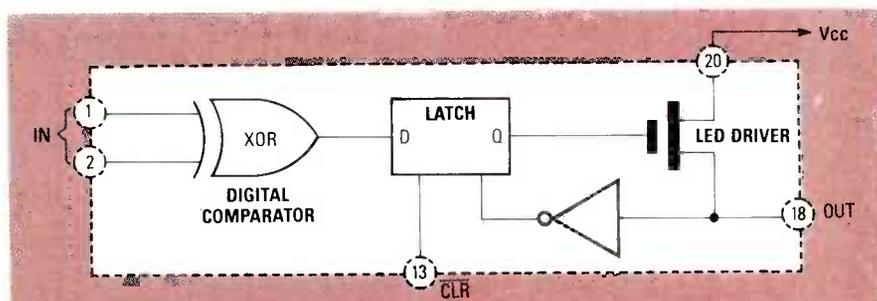


FIG. 1—ONE OF THE DIGITAL-COMPARATOR/LATCH/LED-DRIVER sections in the AE013 custom logic IC. Each IC contains four of these circuits.

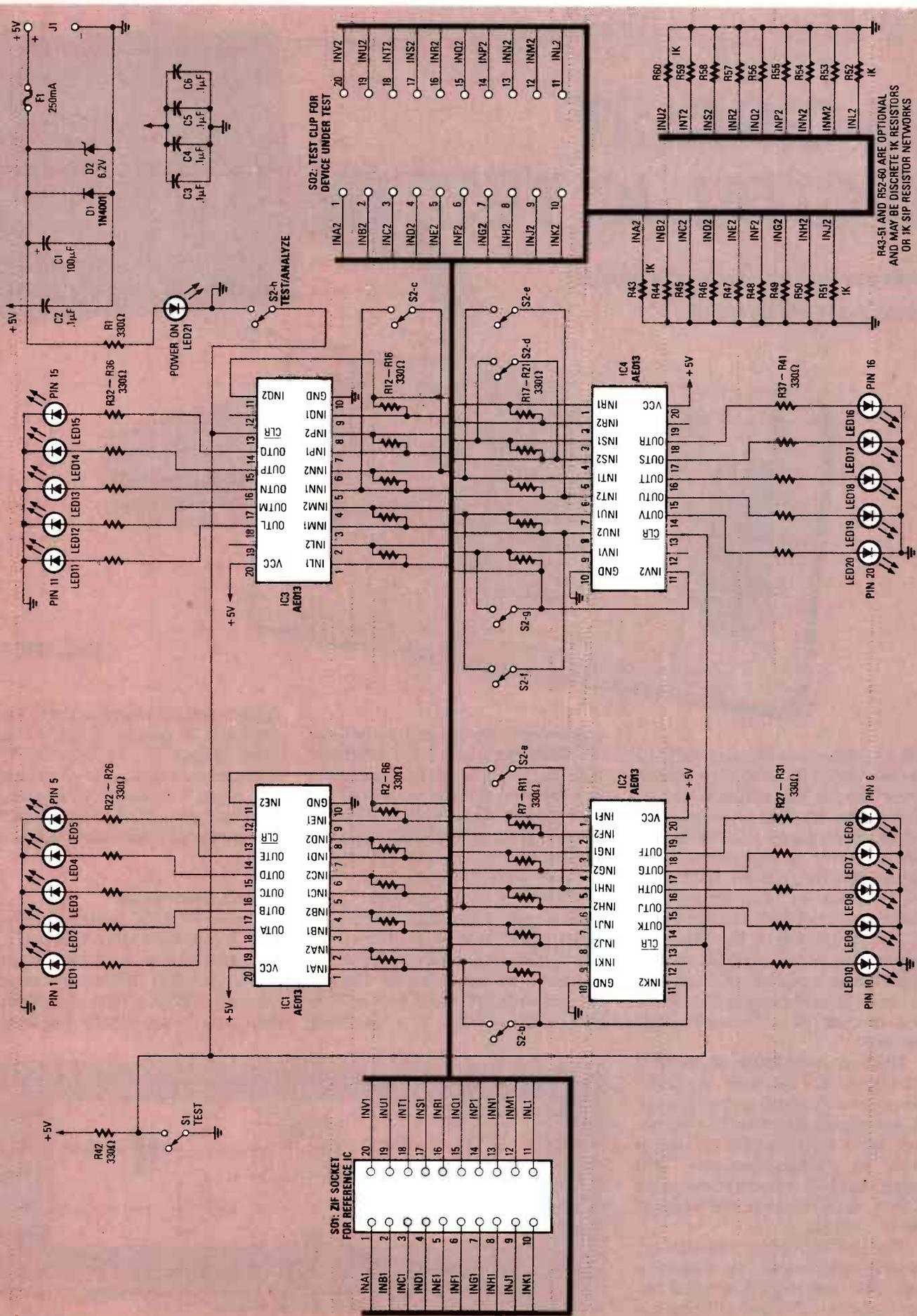

R43-51 AND R52-60 ARE OPTIONAL AND MAY BE DISCRETE 1K RESISTORS OR 1K SIP RESISTOR NETWORKS

FIG. 2—THE COMPLETE IC TESTER. The reference IC is plugged into the ZIF (Zero Insertion Force) socket, SO1, while the test clip, SO2, is attached to the device under test.

PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise noted.

R1-R42—330 ohms, carbon film
R43-R60—1000 ohms, or 9-pack SIP network

Capacitors

C1—100 μ F, 10 volts, electrolytic
C2-C6—1 μ F, 10 volts, ceramic monolithic

Semiconductors

IC1-IC4—AE013 Custom Comparator/Latch/LED Driver

D1—1N4001 rectifier diode

D2—6.2 volt, 1-watt Zener diode

LED1-20—T-1 size, red

LED21—T-1 size, green

Other Components

F1—250 mA, pigtail fuse

SO2—20-pin straight male header

SO1—20-pin wire wrap socket

P1—20-pin DIP header

S1—Normally-open pushbutton

S2—8-section DIP switch

Miscellaneous: PC board, test cables and clips, power cord and clips, IC sockets, 20-pin ZIF socket, and any kind of suitable cabinet and front panel.

Note: The following items are available from W.L. Green, ALPHA Electronics, P.O. Box 541005, Merritt Island, FL 32954-1005, (407) 453-3534. **In-Circuit IC Tester kit (does not include DIP header, cables, test clips and ZIF socket): \$100.00 plus \$5.00 postage and handling. Fully assembled IC Tester with IC test cable, 20-pin and 16-pin DIP clips included, (does not include DIP header, ZIF socket, monitor cable and clips): \$169.00 plus \$5.00 postage and handling. AE013 custom IC: \$18.00 each plus \$1.00 postage and handling. PC board and four AE013 IC's: \$80.00 plus \$4.00 postage and handling. Florida residents must add state sales tax. Canadian sales must add \$2.00 additional postage and handling to each order. Foreign sales add appropriate amount for air shipping and insurance.**

on a given pin of the DUT (Device Under Test) doesn't match the level on the RIC (Reference IC).

Figure 2 shows the complete schematic for the tester. As we describe the operation of the tester in the test mode, we will assume that the DUT has 20 pins. Since all twenty of the sections are used in essentially the same manner, we will describe only one and point out any exceptions.

Resistor R2 is connected across the input of one of the comparators of IC1. If pin 1 of the RIC is an input, then R2 provides a path for an input signal to flow from pin 1 of the DUT to pin 1 of the RIC. On the other hand, if pin 1 of the RIC is an output, then R2 is unnecessary. When both inputs of the comparator are at the same logic level, a low will be on the driver output and the LED will be off. When a logical difference is present at the inputs, the output and the LED will be on. As explained previously, a lit LED is an indication of a defective IC. The LED indicates at which pin the problem exists.

The $\overline{\text{CLR}}$ pin of IC1 is common to all sections of the IC. When it is high, the latch between the comparator's output and the LED driver's input is active; any disparity at the comparator's inputs will be latched. When low, the latch will be cleared and will appear transparent, meaning that the logic

sections, you can appreciate how much the custom IC's simplify the unit's construction.

A single section of an AE013 is shown in Fig. 1. When both inputs of the comparator are at the same logic

level, the driver output will be low, and the LED will be off. When there is a logical difference at the inputs, the driver output will be high, and the connected LED will be on. Therefore, an LED will light when the logic level

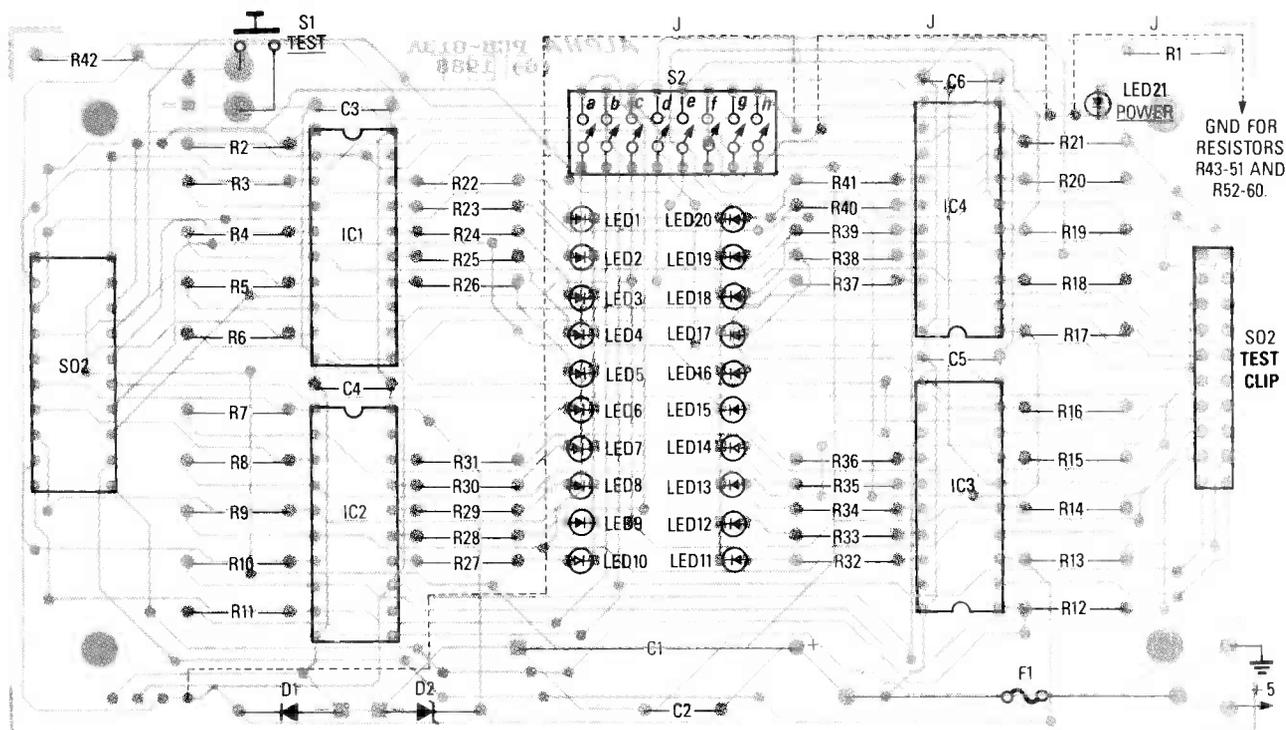


FIG. 3—PARTS-PLACEMENT DIAGRAM. Notice how IC1 and IC2 are facing in the opposite direction of IC3 and IC4.

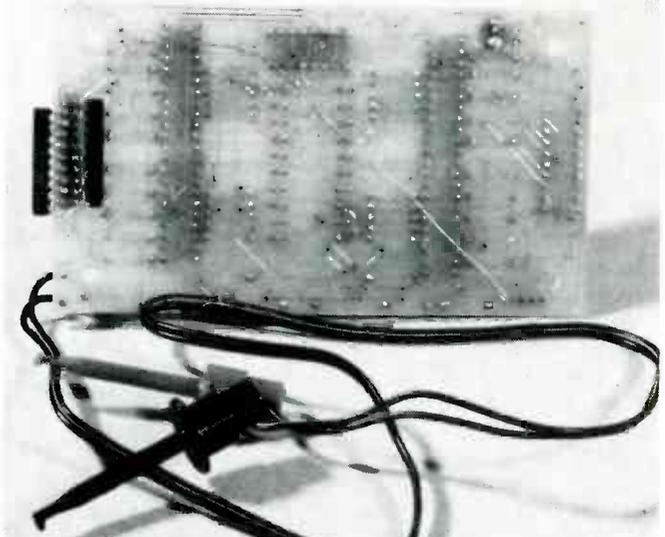
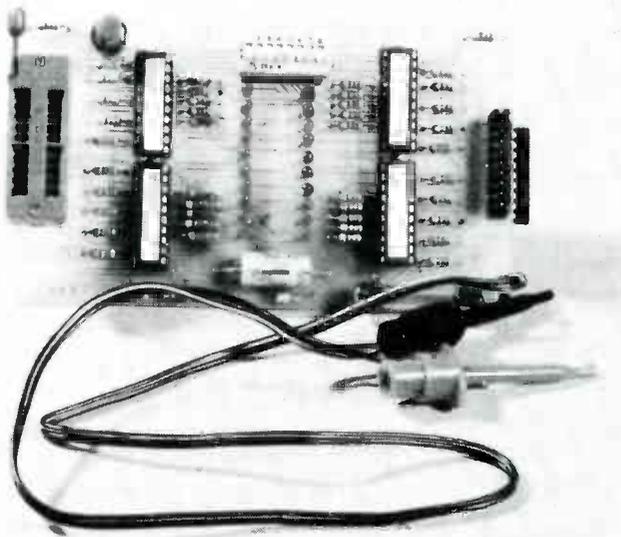


FIG. 4—FINAL ASSEMBLY should look like this. Notice the E-Z hook power-supply clips and the ZIF socket on the left.

level at the latch's input will appear at its output. When test-button S1 is pressed, the $\overline{\text{CLR}}$ input of each AE013 is grounded; that clears all latches in preparation for a new test.

IC's can have 14, 16, 18, or 20 pins. Notice that each switch contained in S2 (DIP switch) is connected in parallel with an input resistor. Depending on how many pins the DUT has, and which pins are power and ground, the appropriate switches should be closed. In other words, we will short out two of the resistors to provide a direct path for power and ground from the DUT to the RIC.

Resistors R1, and R22–R41 limit the current through the LED's to less than 10 mA. LED's 1–20 indicate the level at the output of the drivers, and the green LED (LED21) is the power indicator. All capacitors are used to filter the power bus. Rectifier-diode D1, Zener-diode D2, and fuse F1, provide power-supply polarity and short-circuit protection. Because power for the tester is supplied from an external source—usually the circuit board under test—you must protect it against overvoltage and reverse voltage. Rectifier-diode D1 will conduct with re-

verse polarity and blow the fuse because there's no current limiter. Also, Zener-diode D2 will conduct at greater than +6.2 volts and also cause the fuse to blow.

When the tester is used as an analyzer/monitor, one side of all of the comparators are connected to ground. The other side of the comparators are connected through the test cable to various points in the circuit that we wish to analyze. When any one of those points is high, the corresponding LED will light. Whether S1 is open or closed will determine if those LED's will be latched or non-latched, respectively.

Assembly

Refer to the parts-placement diagram in Fig. 3 for correct orientation of all components on the PC board. (Space does not allow us to print the board pattern in this month's issue. It will appear in next month's PC Service section. We apologize for the inconvenience.)

Begin by installing resistors R1–R42 on the board. Next, install the two diodes D1 and D2, and filter-capacitors C2–C6. Install the sockets

for the IC's and switch S2, noting that IC1 and IC2 face one direction while IC3 and IC4 face in the other direction. Install C1 with its negative lead in the hole marked by a “–,” and then install the fuse F1.

In the author's model, the LED's are installed with their bottom edges spaced $\frac{3}{8}$ -inches from the board; that way each LED will protrude through the front panel when the PC board is installed. Of course, the amount that the LED's will protrude above the front panel depends on the length of the stand-offs that you use to mount the PC board. As with most LED's, the cathode lead is shorter than the anode lead, however, our experience tells us that it's a good idea to check each LED before installing it—especially if you're using “grab-bag” parts. Each LED is installed so that the cathode lead is soldered to the square pads, which are the ground points.

Use a 20-pin wire-wrap socket for SO1 so that the socket will be flush with the top of the case when the board is installed. If you fail to do that, you will never be able to plug the ZIF socket into SO1. Seat a socket for DIP-switch S2 against the board and solder it in. (Use a wire-wrap socket as a pin extender if necessary.) Next, install connector SO2, a 20-pin double-row straight male header strip.

For the power cord, use a piece of zip-cord, about 18–24 inches long. On the free end of that cord, attach a red and a black hook clip. The black clip goes to the ground side of J1,

continued on page 86

TABLE 1—IN-CIRCUIT IC TESTER

Number of IC Pins	DIP-Switch S2 Sections Turned-On
20 pins	a and g
18 pins	b and f
16 pins	b and e
14 pins (pin-7 ground, pin-14 power)	b and d
14 pins (pin-10 ground, pin-5 power)	a and c

IF YOU WORK WITH AUDIO, THERE MUST BE times when you wish you had an amplifier and speaker system handy. If so, the amplified speaker described in this article is the answer to your needs. It is a low-cost, wide-range amplified-sound system complete with loudness, bass, and treble controls. Just connect power, and a line-level audio source and you're in business! Here are some common uses for the project:

If you would like to share the sound of your headphone stereo with your friends, all you have to do is connect the amplified speaker system. The project provides over 5 watts into an internal speaker, and the sound quality is great.

The amplified speaker system is also a great addition to your workshop because you'll no longer have to drag out your stereo and speakers just to check a tuner, tape deck, or other audio component. You'll be able to troubleshoot an audio component on your workbench rather than where your stereo is located.

Another possible use for the amplified speaker system is as an amplifier for an electric guitar or other musical instrument. And, because the project can be powered from a 12-volt car battery (we'll explain how later), you can even use it outdoors.


You should enjoy building the project almost as much as you'll enjoy using it. And, perhaps best of all, it's not going to break your bank account; ours only cost \$17.00 to build. Of course, your cost will be determined by the state of your junkbox, and your ability to track down bargains.

How it works

The amplifier is based on a high-quality audio-amplifier IC made by Sanyo. That particular part was chosen because of its low distortion, high power output, and relatively low noise. Additional circuitry is included for loudness, bass, and treble controls, which are always included in a high-quality audio amplifier.

The schematic of the amplified-speaker project is shown in Fig. 1. Input signals to the audio-input terminals drive volume-control R2. Capacitor C2, resistor R1, and a tap on R2

AMPLIFIED SPEAKER

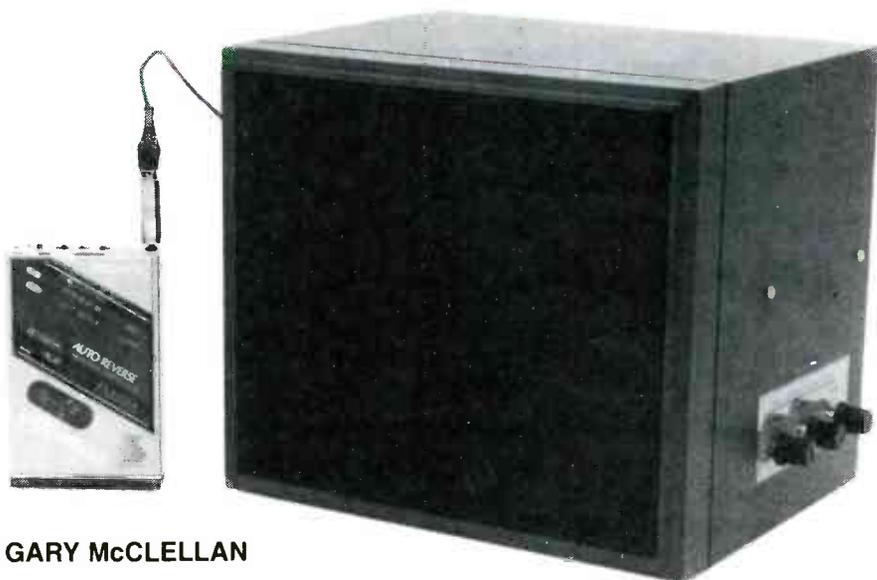

GARY McCLELLAN

You can build this low-cost amplified speaker system that is useful for testing audio components, or to amplify a walkman-type stereo for "ears-free" listening pleasure.

are a loudness-compensation network, which boosts bass tones at low-volume levels. That circuitry corrects for human hearing deficiencies at low volume.

From R2, the audio signal is amplified by transistor Q1, which is a high-gain, low-noise device. That stage compensates for losses in the tone-control circuitry. Bias-resistor R3 further reduces noise by providing negative feedback. Capacitor C4 is included to prevent RF pickup and to roll off high-frequency noise.

Basically, the circuit connected between capacitor C6 and resistor R12 is a 20-dB resistive attenuator network combined with adjustable low-pass (bass) and high-pass (treble) filters. The potentiometers increase or decrease the capacitive reactance across various resistors, boosting or cutting

bass and treble tones. Bass-control R7 is part of a voltage divider consisting of R6 and R8. Turning the potentiometer clockwise puts more of the reactance of capacitor C8 across the potentiometer and R8, shunting most of the high frequencies to ground, and boosting the lows. Turning the potentiometer counterclockwise puts more reactance of C7 across the potentiometer and R6, boosting most of the high frequencies and cutting the lows.

The output from the bass potentiometer (R7) goes to resistor R10, which reduces control interaction, and then it goes to treble-control R11. That potentiometer is in a series voltage divider with capacitors C9 and C10. Turning R11 clockwise puts more of the reactance of C9 in the circuit, shunting high frequencies around the bass control, boosting tre-

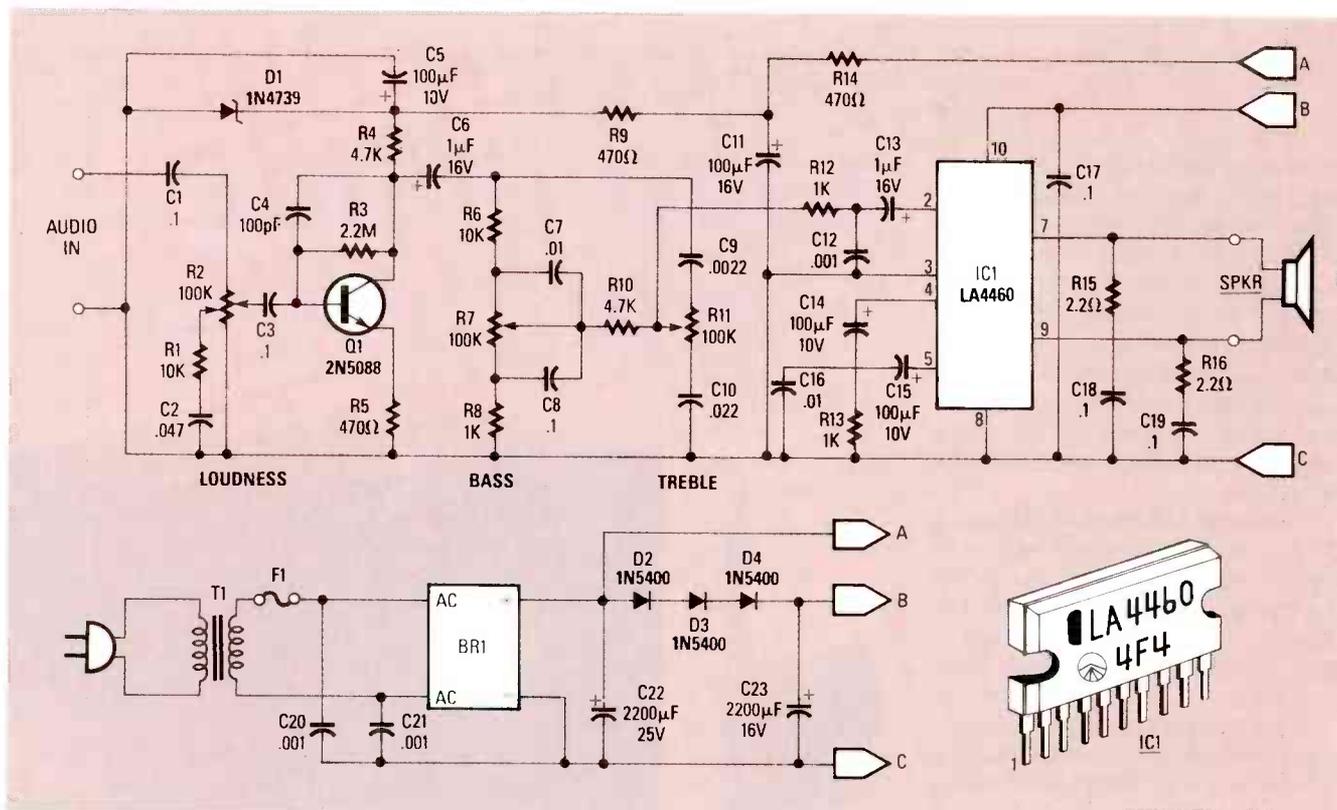


FIG. 1—SCHEMATIC DIAGRAM of the amplifier board and its power supply.

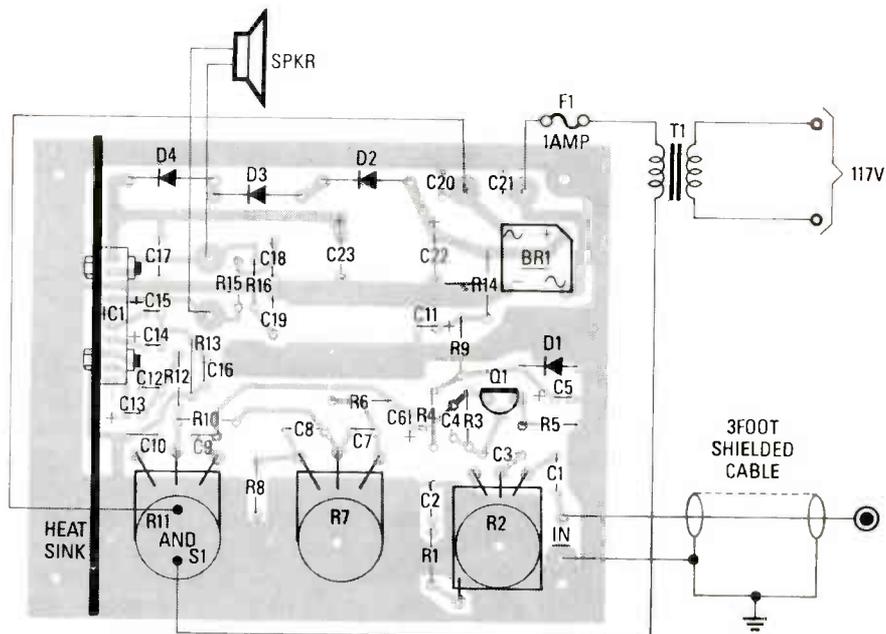


FIG. 2—PARTS PLACEMENT DIAGRAM for the PC board. Close attention should be paid to the polarities of the electrolytic capacitors.

ble. Likewise, turning R11 counterclockwise shunts high frequencies away from the bass control to ground, cutting treble tones. The tone-control output drives resistor R12 and capacitor C12, which serve as a low-pass filter. That circuitry is included to prevent oscillation in power-amplifier IC1.

Power-amplifier IC1 is a bridging-type amplifier. That means that there are two power amplifiers inside the package that drive the speaker in a push-pull configuration for double the power output. The input signal to pin 2 is amplified and then drives the speaker from the pin-7 output. A phase-inverted output appears at pin 4

and is coupled through capacitors C14 and C13 to the second amplifier in IC1. After being amplified, the phase-inverted output drives the speaker from pin 9. Resistors R15 and R16, and capacitors C18 and C19, are included at the output of IC1 to prevent high-frequency oscillation. Note that if you can't find the 2.2-ohm resistors specified for R15 and R16, 10-ohm units may be substituted. The exact value isn't critical, although 2.2 ohms is preferred.

Rounding out the circuitry is a fairly conventional power supply, consisting of bridge rectifier BR1; capacitors C22 and C23; and diodes D2, D3, and D4. Since the supply voltage, after being rectified, is at about 17 volts, D2, D3, and D4 are required in order to drop it down to about 15 volts. Note that power is also tapped off capacitor C22 for Q1. That extra

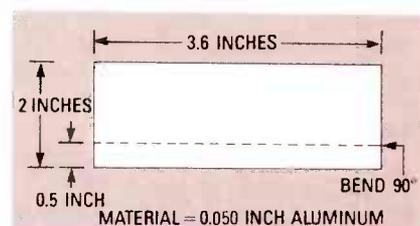


FIG. 3—YOU CAN MAKE A HEAT SINK for IC1 from a piece of scrap aluminum.

All resistors are 1/4-watt, 5% unless noted

R1, R6—10,000 ohms
R2—100,000 ohms, potentiometer, 40% loudness contour tap (Radio Shack 271-1732)
R3—2.2 megohms
R4, R10—4700 ohms
R5, R9, R14—470 ohms
R7, R11—100,000 ohms, potentiometer, audio taper (Radio Shack 271-1722)
R8, R12, R13—1000 ohms
R15, R16—2.2 ohms

Capacitors

C1, C3, C8, C17, C18, C19—0.1 μ F, 50 volts, radial-lead polyester
C2—0.047 μ F, 50 volts, radial-lead polyester
C4—100-pF, 500 volts, ceramic disc
C5, C14, C15—100 μ F, 10 volts, radial-electrolytic
C6, C13—1 μ F, 16 volts, radial-electrolytic
C7, C16—0.01 μ F, 50 volts, radial-lead polyester
C9—0.0022 μ F, 50 volts, radial-lead polyester
C10—0.022 μ F, 50 volts, radial-lead polyester
C11—100 μ F, 16 volts, radial-electrolytic
C12, C20, C21—0.001 μ F, 50 volts, ceramic disc
C22—2200 μ F, 25 volts, radial-electrolytic
C23—2200 μ F, 16 volts, radial-electrolytic

Semiconductors

IC1—LA4460 linear power amplifier (Sanyo)
Q1—2N5088 NPN transistor
D1—1N4739 9.1-volt, 1-watt, Zener diode
D2—D4—1N5400 3 amp, 50 PIV, silicon diode

BR1—6 amp, 50 PIV, bridge rectifier

Other components

S1—SPST potentiometer switch for R11 (Radio Shack 271-1740)
T1—Plug in transformer, 12 volts AC, 1 amp (Jamenco AC1000 or equivalent)

PL1—RCA plug

F1—1 amp, slow-blow, 3AG fuse and holder

Miscellaneous—speaker, PC board, 3 knobs, 3 feet of shielded wire, scrap aluminum for heatsink, hardware. **Note: A PC board is available from E²VSI, P.O. Box 72100, Roselle, IL 60172, for \$9.95 plus \$0.50 shipping.**

self-oscillation). Resistors R14 and R9 provide current limiting, while capacitors C11 and C5 provide extra filtering. Zener diode D1 ensures that the supply voltage is stabilized at 9.1 volts, as required by transistor Q1.

Part selection

Now that we have covered the circuit details, let's discuss the parts.

The speaker system may be any decent-sounding unit you can find. Chances are you will want to build two amplified-speaker systems, so it would be wise to get two identical units for balanced sound. The Panasonic two-way unit used for our prototype was purchased at a flea market for \$1.50; perhaps you can do better. If possible, test out the speaker system you are considering, as you don't want to waste time on a unit that is defective, or has poor sound quality.

You may have some trouble finding a tapped potentiometer that is required for R2. One alternative is the

ganged unit mentioned in the Parts List. That unit consists of two ganged potentiometers, but only one of them is used. Of course, if you can find a single-unit substitute with same specifications, you should use that.

The semiconductors are available from a wide variety of sources. Many Japanese TV/stereo replacement-parts suppliers carry the Sanyo LA4460 for IC1. And any 3-amp diodes can be used for D2, D3, and D4. The bridge rectifier specified is a standard 6-amp, 0.6-inch square-cube unit. You can also cross-reference those semiconductors with the Phillips-ECG replacement line, as well as many others.

Finally, transformer T1 is a plug-in 12-volt AC 1-amp unit. It is available from several sources. If you prefer, a standard 12.6-volt AC, 1-amp or better, filament transformer may be used. If you go with a standard filament transformer, remember to pick up a line cord and a 1/4-amp fuse for F1.

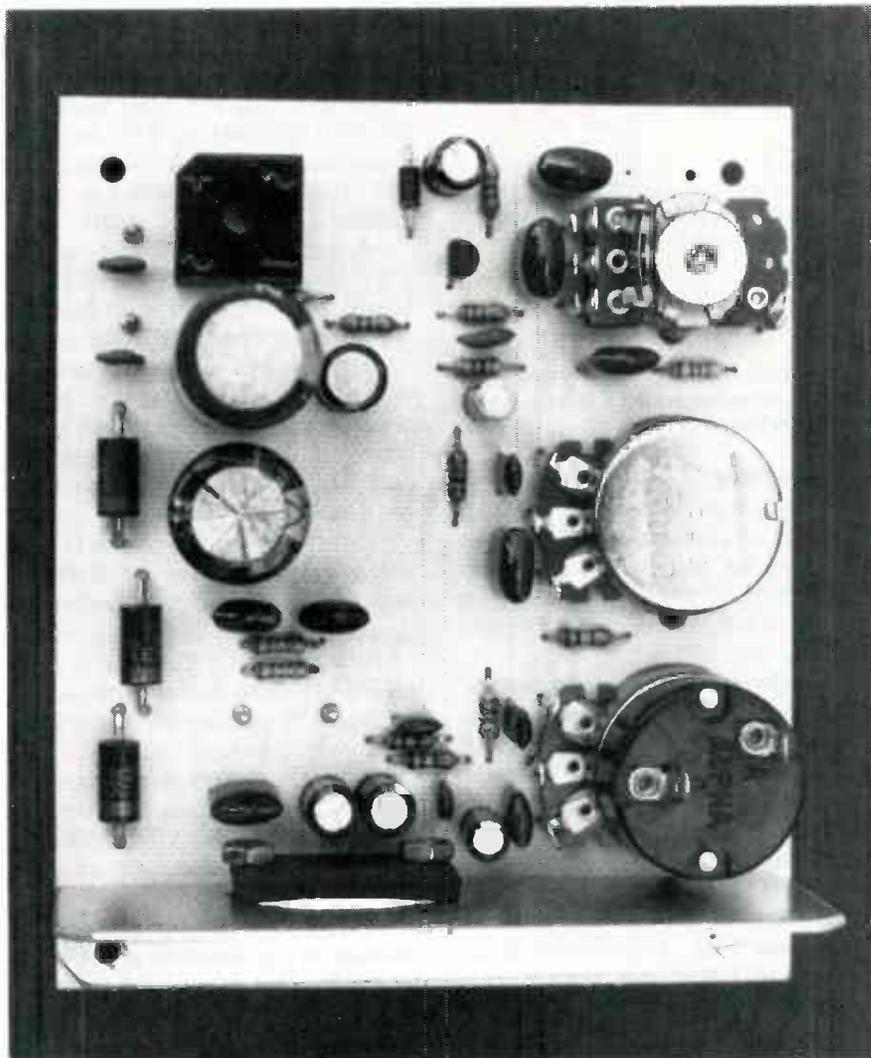


FIG. 4—YOUR BOARD SHOULD look similar to this one when it is completed.

power-supply circuitry is required to ensure amplifier stability, as it would otherwise *motorboat* (low-frequency

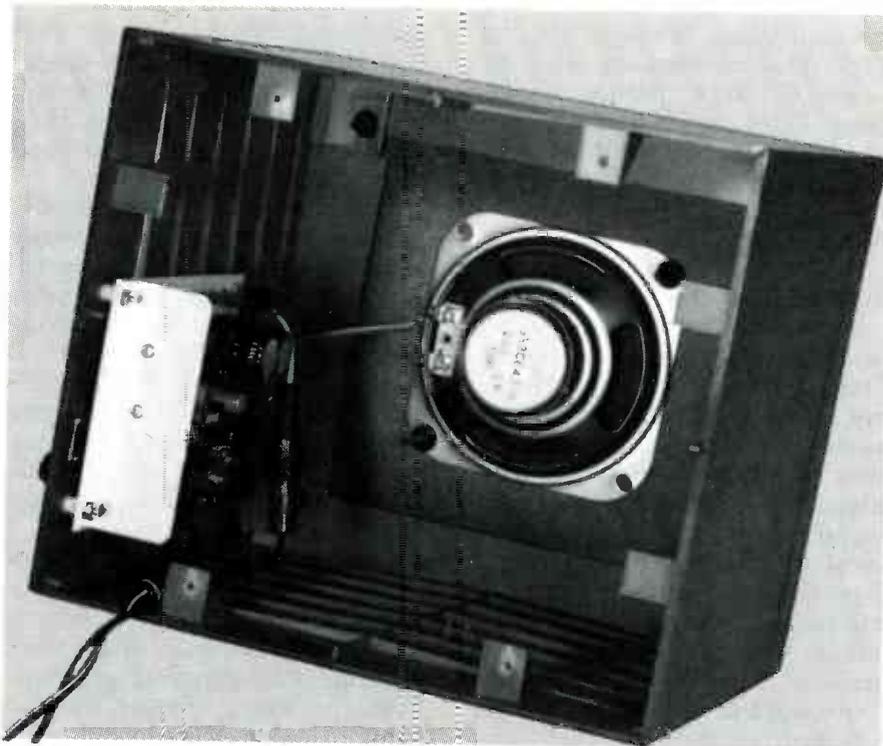


FIG. 5—A GOOD PLACE TO MOUNT the board is on the side of the cabinet, near the rear. Note the spacers that are used between the board and the cabinet

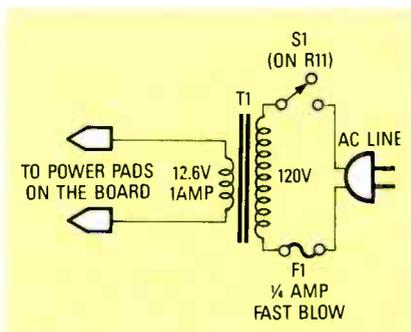


FIG. 6—ALTERNATE TRANSFORMER details should be followed if a standard filament transformer is used.

Construction

The amplifier should be built on a PC board for best results. Either make one using the pattern in the PC Service section of this magazine or you can buy one from the source given in the Parts List.

Start the assembly by stuffing the amplifier PC board. Refer to Fig. 2 for component locations and the Parts List for values. Starting with the diodes, install bridge-rectifier BR1 with the case, notch, or positive terminal as shown. Then install 3-amp diodes at D2, D3, and D4 as indicated. Finally, install the 1N4739 Zener diode at D1 near BR1. Double-check all parts before continuing.

Next comes the resistors. Install 470-ohm resistors at R14, R9, and R5 as indicated. Then install a 2.2-

megohm resistor at R3 and a 4.7K resistor at R4. Next, install 10K resistors at R1 and R6. After that install 2.2-ohm resistors at R15 and R16. Continue by installing 1K resistors at R12, R13, and R8. Finish up by installing a 4.7K resistor at R10.

Modify the three potentiometers next. If necessary cut the shafts to length. Measure 1 inch from the bushing, mark it, and cut it off with a hacksaw, and then smooth the edges with a file. We suggest using a potentiometer switch for S1, and an appropriate unit is listed in the Parts List. The switch, by the way, should be installed on R11.

Install the potentiometer and switch combination at the R11 location, and the tapped potentiometer in the R2 location. Then install the last potentiometer in location R7. Connect the potentiometer terminals to the board by passing short lengths of solid wire through the board and through each potentiometer terminal. Leftover resistor leads are good for that. Make sure that all connections are soldered, and check for mistakes before continuing.

Next comes the capacitors. Remember to pay attention to the polarities of the electrolytics as you install them. Start by installing the 2200- μ F, 25-volt capacitor at C22. Then install the 2200- μ F, 16-volt capacitor at

C23. Continue by installing 0.1- μ F capacitors at C17, C18 and C19. Now move over to the righthand side of the board and install 0.1- μ F capacitors at C1 and C3. Next, install a 0.047- μ F capacitor at C2 and install a 100-pF disc at C4. Now install 1- μ F capacitors at C6 and C13, and a 0.01- μ F capacitor at C7. Next to that, install a 0.1- μ F capacitor at C8. Now install a 0.0022- μ F capacitor at C9, and install a 0.022- μ F capacitor next to it at C10. Finish up by installing 100 μ F capacitors at C14 and C15, and check everything before continuing.

Next, Q1 and IC1 are installed. Place the 2N5088 as shown at Q1, and then install the LA4460 at IC1. Insert the part with the metal side to your left. Also, note that the pin-1 marking on the board matches the pin-1 stripe on the IC package. Double check before soldering the connections.

Continue by fabricating a heat sink for IC1. Details are shown in Fig. 3. We used a piece of aluminum salvaged from an old chassis for the heat sink, as it conveniently already had a 1/2-inch lip on it.

Install the heat sink. Place it against IC1 with the lip over the board's mounting holes. Then mark and drill the two mounting holes for IC1. Also, mark and drill the board's mounting holes. Put a dab of silicon grease on the metal surface of IC1 and secure the heat sink to IC1 with 4-40 \times 1/2-inch screws. Tighten the screws just enough to hold IC1 in place, as overtightening may damage it. The board is now complete, and it should look like the one shown in Fig. 4.

Set the assembled board aside for a moment and work on the speaker cabinet. Determine a suitable location to mount the board. A good location is on the side of the cabinet, toward the rear, as shown in Fig. 5. Using the board as a guide, measure, and mark the holes for the four mounting screws, and the three knob shafts. Do that carefully, as mistakes will be hard to fix later on. Note that the holes for the screws must be smaller than the holes for the knob shafts. Drill all holes and make sure the board fits. You can, if you like, use rub-on lettering to label the controls for a professional appearance.

Return to the assembled board and refer back to Fig. 2 for final assembly details. Start by wiring a shielded cable to the IN pads on the board as

continued on page 104

Build REACTS: THE RADIO-ELECTRONICS ADVANCED CONTROL SYSTEM

This month we're going to show you how to build and program the terminal interface for your REACTS system.

Part 8 LAST MONTH we didn't get a chance to discuss the data registers. So, we'll start with that, and then build the interface.

By writing an eight (00001000) to the address register, the top-of-screen register is selected. That register contains the RAM address of the first character displayed at the top of the video screen.

The cursor-low register is addressed by writing a nine (00001001) to the address register. The cursor-low register holds the lower eight bits of the 11-bit RAM-cursor address, and the upper three bits of the cursor address are in the cursor high register.

As was mentioned, the upper three bits of the RAM-cursor address are located in the cursor-high register. The other five bits of the cursor-high register select the smooth-scroll offset value and disable/enable the non-scrolling 25th status line. That register is located at address ten (00001010).

The fill-address register is selected by writing an eleven (00001011) to the address register. That register is used to obtain the fill-screen feature. The fill-address register contains the memory-RAM address of the character following the last address to be filled. After writing to the fill-address register, the next character



MICHAEL A. TUCKER

placed into the character register will be placed in each display-memory-RAM location between the address specified by the cursor-low and cursor-high register (the cursor address), and the address preceding the one in the fill-address register.

The screen attribute data register is at address twelve (00001100). The most-significant bit (bit 7) of the register determines whether the EVTLC is in the 9×28-graphics or 9×28-alphanumerics mode. If the alphanumerics mode is enabled, the other seven bits of the register will select the type of attribute to be exhibited by the "tagged" screen characters. Remember that in the 9×28 mode, only one attribute per screen is possible. If the EVTLC is in the graphics mode, no attributes are permitted; however, a combination of graphics and alphanumeric characters can be displayed on a single screen. In the graphics

mode, a character is determined to be a graphics or alphanumeric character by the most-significant bit of the character byte. That is the same bit that determines whether or not an alphanumeric character is "tagged" in the 9×28 alphanumeric mode.

Only the most-significant bit (bit 7) of the mode-1 register is used. It is called the auto-increment bit and it determines whether or not the display-memory character address is automatically incremented by the EVTLC after every read/write of the character register. The mode-1 register is at address fourteen (0001110).

A fifteen (00001111) output to the address register will select the EVTLC's mode-2 register. Bit 0 places the EVTLC in either the 9×28 or 9×53 mode. Bit 1 enables or disables the cursor blink, and the other bits are not used.

The last register to be discussed is at register-address thirteen (00001101), and it is called the character register. All screen characters are written to and read from the display memory via that register. It should be noted that the register is accessible when the done-bit (bit 7 of the status register) is high. Tables 1, 2, and 3 show the assignments of each bit of the character register in the various programmable modes.

Control software

If you purchase the CRT-controller kit from the source listed in this article, you will receive a PROM with a CRT-controller program already loaded. We strongly recommend that you

TABLE 1—9 × 28 GRAPHICS MODE

Character-register bit	7	6	5	4	3	2	1	0
Character	1	----- Character Data -----						
Thin Graphics	0	0	X	X	SEG4	SEG3	SEG2	SEG1
Wide Graphics	0	1	SEG6	SEG5	SEG4	SEG3	SEG2	SEG1

TABLE 2—9 × 28 ALPHANUMERIC MODE

Character-register bit	7	6	5	4	3	2	1	0
Character (Attr. enabled)	1	----- Character Data -----						
Character (No attribute)	0	----- Character Data -----						

TABLE 3—9 × 53 OPERATION MODE

Character-register bit	7	6	5	4	3	2	1	0
Character	0	----- Character Data -----						
Attribute Character	1	0	0	Blank	Blink	Int	UL	RV
Thin Graphics	1	0	1	X	SEG4	SEG3	SEG2	SEG1
Wide Graphics	1	1	SEG6	SEG5	SEG4	SEG3	SEG2	SEG1

UI = Underline Attribute
RV = Reverse Video Attribute

start with the preprogrammed PROM even if you decide to develop your own.

The software that you can purchase works in the following manner: When a key is pressed the DR (Data-Ready) output of the 82C52 UART, which is connected to the maskable interrupt (INT) of the Z80, goes high notifying the CRT microprocessor that it has received a character. The Z80 will read that character from the UART and determine whether the character is alphanumeric or a special function. If the character is alphanumeric, the CRT's CPU will send it to the system CPU. The system CPU, after placing the character in the file or program currently called up, will then send it back to the CRT controller to be displayed. A special function can be one that is performed by the system's CPU such as CTRL-C, ESC, and CTRL-S, or one sent to the EVTLC to disable or enable a screen attribute such as reverse video, character blink, or move the screen cursor.

Programming the CRT controller

Before programming the CRT controller, various registers of the controller's IC's must first be initialized. All but one of the IC's of the CRT controller are hardwired to the I/O ports of the onboard Z80. The only one that is not addressed by the onboard Z80 is one of the 82C55 PPI's; it is addressed by four of the I/O ports of the CPU's Z80. The following list

shows the addressable CRT controller IC's and their assigned I/O ports. All addresses are in decimal form:

- 82C52 UART—Ports 64–67
- Page register—Port 68
- 82C55 PPI (addressed by the on-board Z80)—Ports 72–75
- EVTLC—Ports 76 and 77
- 82C55 PPI (addressed by the CPU's Z80)—User selectable (uses 4 ports)

Those ports are selected by the on-board CRT-controller address switches. If the operating system is used, the switches should be set to 252. The address set by the switches will be the first of four, with the others following in consecutive, incrementing order. For example, if the switches are set to address 252, the first address used by the 82C55 will be 252 and then 253, 254, and 255.

The 82C52 UART is initialized by the on-board Z80 sending a 62 to I/O-port 65, a 34 to I/O-port 67, and a 35 to I/O-port 66, in that order. I/O-port 64 is the data port, and the control program should read the byte from there when the INT (maskable interrupt) input of the Z80 goes active (high), such as when a keyboard character has been received.

The CRT controller can display a maximum of two thousand characters on the monitor at one time. Each character being displayed uses one byte of the display RAM's memory. You will notice that the display memory is an 8K × 8 RAM IC. That is four

times the amount of RAM needed to display one screen. Therefore the memory-page register allows the storing of four different screens within the display RAM. That is, the display

PARTS LIST

All resistors ¼-watt, 5%, unless otherwise noted.

- R1—1 megohm
- R2—68 ohms
- R3—330 ohms
- R5—70 ohms
- R6, R7—9-into-1, 10,000 ohms, SIP resistor pack

Capacitors

- C1—C20—0.47 µF, 25 volts, ceramic disc
- C21, C22—22 µF, 25 volts, ceramic disc
- C23—47 µF, 16 volts, electrolytic

Semiconductors

- IC1, IC17—8K × 8-bit CMOS static RAM
- IC2—74HC573 tri-state D-Type latch
- IC3, IC18—74HC245 octal tri-state transceiver
- IC4—IC6—74HC04 hex inverter
- IC7—9053 enhanced video terminal logic controller
- IC8, IC11—82C55 programmable peripheral interface
- IC9—74HC02 quad 2-input NOR gate
- IC10—Z80 8-megahertz CMOS IC microprocessor
- *IC12—32K × 8-bit CMOS PROM with controller software
- IC13—82C52 UART
- IC14, IC15—74HC688 8-bit magnitude comparator
- *IC16—CRT32—16 programmable array logic (PAL)
- IC19—74HC273 octal D-type flip-flops
- *IC20—CRT32—20 programmable array logic (PAL)
- LED1—right angle PC-mount red LED

NOTE: Components that are marked with a * are customized parts that can be obtained from the source listed in last month's article.

Other components

- SO1, SO2—60-pin male and female bus-conductor set
- SO3—6-circuit telephone jack
- SO4—9-pin female D-sub printer connector
- SO5—25-pin female D-sub connector
- X1—16.4 MHz crystal
- SW1, SW2—6-position DIP switch

Miscellaneous: 1 PC board, extruded aluminum case, 4 14-pin IC sockets, 8 20-pin IC sockets, 4 28-pin IC sockets, 4 40-pin IC sockets

Macrovision . . . now you see it, now you don't.

Remove copy-protection from video cassettes.



- Digital Filter Type, removes only Macrovision pulses
- No adjustments, crystal controlled
- Compatible with all VCR's, uses automatic vertical blanking level

Macro-Scrubber — We stock the exact parts, PC board, and AC adaptor for an article on Building a Macro-Scrubber appearing in *Radio-Electronics* December 1987 issue.

JMAK-1 Parts Package \$19.00

Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, and crystal.

JMAK-2 PC Board \$9.95

Original etched and drilled silk-screened PC board used in article

JMAK-3 AC Adaptor \$7.95

Original (14 to 18 volt DC @ 285 ma) AC adaptor used in article.


Free reprint of article on building a Macro-Scrubber with any purchase above. Add \$2.50 shipping & handling; \$4.50 Canadian orders.

Note: Unauthorized duplication of copyrighted material is illegal. Use Macro-Scrubber for viewing only.

72-CHANNEL

CABLE CONVERTER

WITH INFRA-RED REMOTE CONTROL

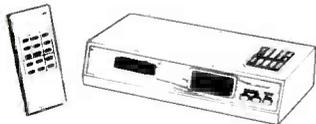

Add \$3.50 shipping & handling
\$9.50 Canadian orders.

MC-702 CONVERTER

\$79.95

- 72-channel capability
- Wireless, Infra-Red remote control
- Channel output 2 or 3 switchable
- Microprocessor controlled PLL operation
- Skip channel memory eliminates unused channels
- Parental control for all channels
- Last channel recall
- Fine tune memory
- UL listed/FCC approved
- Simple installation with any TV
- Includes battery and 3 foot coax cable

CABLEMASTER \$19.95 Cable/VCR Timer

- Record multiple premium play channels
 - Turns cable box on and off
 - Selects channel for unattended recording
 - Thousands sold nationally for \$99.95
- Add \$3.50 shipping & handling
\$4.50 Canadian orders

ORDER TOLL FREE ANYTIME
1-800-227-8529

Ask for **FREE**
Color Catalog

Inside MA: 617-695-8699

VISA, MASTERCARD,
or C.O.D.



J & W
ELECTRONICS, INC.

P.O. BOX 800 • MANSFIELD, MA 02048

©Copyright 1988 by J&W Electronics Inc.

that you use sockets for all the IC's. First Solder in all the components, then check all of the connections. Then double-check them.

Checkout

Before installing the CRT controller/printer module onto the REACTS CPU, make sure the system is off. If you are using the REACTS operating system, set the CRT controller's I/O-addressing switches to I/O-port 252 (all switches up). Also, set the printer-interface addressing switches to I/O-port address 248 (the rightmost switch down and the rest up). The fourth switch from the right on the row of CPU switches should be placed in the down position; that switch should be up if a terminal is being used as the console and is connected to the CPU's serial port.

Make sure that none of the pins of the CPU connectors are obstructed or bent. To install the module, align the female connectors on the bottom of the CRT/printer module with the male connectors on the top module of your system, making sure the modules are parallel to each other. Press the CRT/printer module onto the system (extreme force is not necessary). Using common sense and following proper procedures, the connectors will last indefinitely.

After the CRT/printer module has been properly installed, connect the monitor to the 9-pin D-type port on the rear of the module and the keyboard to the connector on the front. Turn on the power, and if everything is in order, the opening menu should be displayed.

If that does not occur, check your switch settings. Also, make sure the correct switches for the CRT controller were set and not confused with the ones for the printer-interface I/O-address selection. Connect a parallel printer to the printer port to check out the printer interface. If you are using the REACTS operating system you can enter a CTRL-P, and any data entered afterwards will be printed. To get out of that mode, simply re-type CTRL-P.

In the next REACTS installment we will discuss the operation and construction of a module that will allow REACTS to remotely-control appliances, lights, etc., using the existing AC-power lines in your home, and inexpensive, easy-to-get control modules.

R-E

CIRCLE 65 ON FREE INFORMATION CARD

ELECTRONICS

ELECTRONICS

ELECTRONICS

NANOELECTRONICS

THE NEW SCIENCE OF MINIATURIZATION

Every year, improvements in manufacturing technology allow us to squeeze more and more circuitry onto a silicon wafer. However, it is physics, not manufacturing technology, that ultimately determines how small the features of an integrated circuit can be made before the circuit will no longer function—and technology is rapidly approaching that limit. Therefore, if our quest for the miniaturization of integrated-circuits is to continue beyond that limit, a whole new breed of semiconductors must be developed.

JOSEF BERNARD*

AS MORE AND MORE COMPONENTS ARE crammed on the small chip of silicon that is the basis for an integrated circuit, it becomes necessary to make those components, and the paths that connect them and carry electrical signals between them, smaller and smaller. As feature sizes decrease, some interesting things begin to happen. Some of those effects are useful, others less so.

Miniaturization certainly makes for compactness, that much is evident to the eye. Smaller features on an IC, and an increase in their proximity to one another also means that switching operations can take place more rapidly due to the fact that the electrons do not have so far to travel—the shorter the distance they have to travel, the faster an IC will operate. The small feature size and dense architecture of today's LSI and VLSI integrated circuits is what make possible their high speed and throughput.

Small size brings with it another benefit—fewer electrons to be moved shorter distances means that less power is required. In an IC with several hundred thousand active elements that is important. Even so, with that large number of components, a lot of energy is used (and lost) in getting electrons from one point to another. Just try to keep your finger on top of a 80386 microprocessor running at full tilt. A lot of energy is dissipated as heat and wasted just in pushing those electrons through the equivalent of microscopic wires.

Small feature size brings with it another problem, too. While tiny features mean that power consumption is lower, there is a phenomenon in transistors known as leakage current. A transistor is never fully, one-hundred-percent, off. There is always some current passing through it. At the discrete component level, and even in most integrated circuits, that leakage current is so small compared with that used to differentiate “on” from “off,” that it can be ignored. As

switching currents become lower, however (something that goes hand-in-hand with small size and is, in fact, something to be desired—up to a point) they come to approach the value of the leakage current, and the point at which a device can be said to be on or off starts to become vague. As you might imagine, vagueness is not a desirable quality in digital logic circuits.

And, on really *small* small-scale devices, another, and much more disturbing, phenomenon occurs. Present-day technology allows us to manufacture integrated circuits with features as small as .3 micron—three hundred-millionths of a meter. And technologies are under development that will allow even smaller feature sizes—perhaps as small as .05 micron by the mid 1990's (see Fig. 1).

On that submicroscopic scale, strange things begin to happen. As we enter the realm of dimensions approaching billionths of a meter (10^{-9} meter) we begin to encounter a world unlike any that we have experienced

*Thanks to everyone at Texas Instruments, especially Robert Bate for their help in preparing this article.

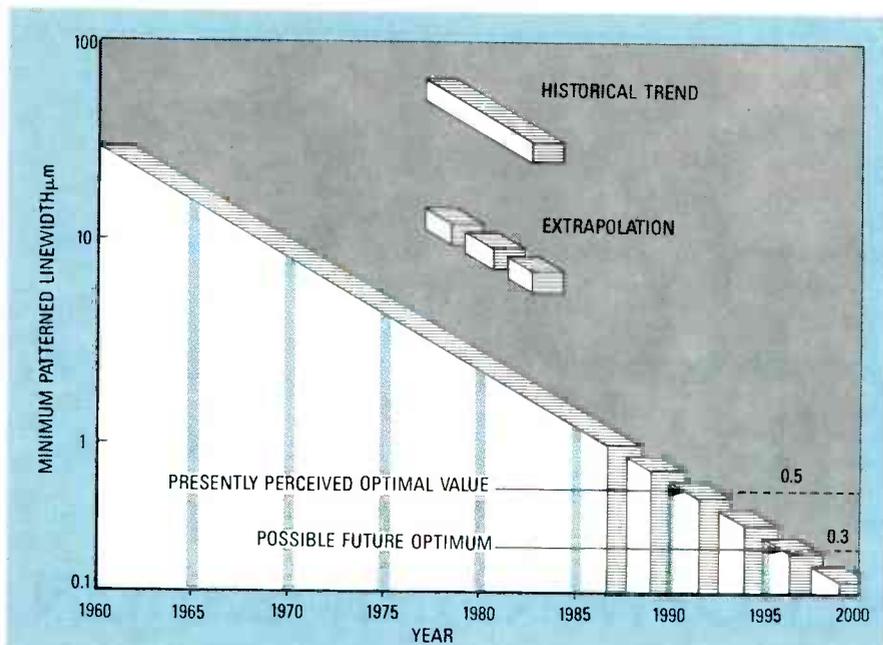


FIG. 1—EVERY YEAR INTEGRATED-CIRCUIT feature sizes shrink. Shortly they'll reach physical limits.

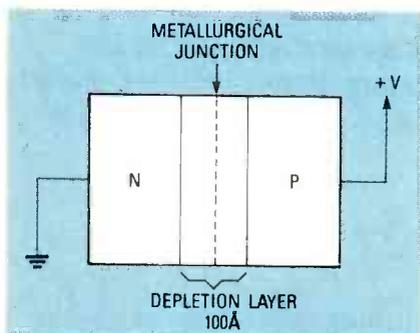


FIG. 2—IN A TUNNEL DIODE electrons burrow through a barrier layer only about 100 angstroms thick.

in our lives. On that scale the nature of matter becomes completely different.

Particles and waves

Way before the time of Isaac Newton (as far back as ancient Greece) there was argument as to the nature of light. Some said it was made up of particles, and some said it was a series of waves in the *luminiferous aether* (the ether, as it later was called). One theory worked better for some of the observed characteristics of light, the other better for others. Eventually the concept of a *wavicle*—a wave that acted like a particle (or a particle that acted like a wave) evolved. And it is still with us today.

Up to a point, the behavior of matter can be explained by treating it as solid particles. That extends down even to electrons and below, hence the concept of electron shells and orbits.

At a certain point, though, we have to begin to think of electrons and other subatomic particles as exhibiting the type of behavior we associate with waves. That becomes more and more the case as we approach dimensions close to those of the electron itself.

When we do approach those dimensions, a curious thing happens. The minimum feature size of the integrated circuit begins to approach the size of the electron. Using present-day optical manufacturing techniques, the feature size of an integrated circuit can be made as small as 0.3 micron, or 3×10^{-7} meter (feature sizes as small as 0.1 micron have been achieved in the laboratory). The size of an electron is about 200 billionths of a meter, or 2×10^{-7} meter. The electron and its environment are almost the same size!

Now what happens?

To explain the behavior of things at that level, a science called quantum mechanics has evolved (actually, the quantum theory was expounded by Max Planck in 1900). You're probably familiar with the expression "quantum leap," as in "a quantum leap forward." Many people think that that means a huge leap, but it doesn't (especially if you're talking about things as minuscule as electrons). It refers to the behavior of things at the level where they lose their "particle" characteristics and start behaving more like waves.

At the quantum scale, energy travels in packets or bunches. Depending on their nature and wavelength, those packets of energy may be photons, electrons, or other types of particles. Furthermore, they seem to go from here to there, or from one state to another, without entering or passing through the space, or states, in between.

In a semiconductor, that "passing through states" takes the form of an effect known as tunneling. If two adjacent layers of a semiconductor device are separated by an extremely thin (about the wavelength of an electron) depletion layer containing neither electrons nor holes, under the right conditions electrons can "tunnel" through that depletion layer as if it presented no barrier (see Fig. 2).

(While the idea of quantum-effect semiconductors is just now getting under way, tunneling devices have been known for some time. In the late 1950s and early 1960s a device known as a tunnel diode gained some degree of popularity. It even showed up in a Heathkit grid-dip meter, used for measuring antenna performance.)

Quantum dots, wires, and wells

In an ordinary semiconductor, electrons, that act like particles rather than waves, are confined in a material such as one of the layers of doped silicon making up the device. In a quantum-effect device, however, the barriers that confine the electrons are made of energy.

Electrons occupy what are known in quantum physics as energy levels or energy bands. That is the quantum-theory equivalent of electron orbits in the more conventional model of atomic theory. A higher orbit represents a higher energy band. Under certain conditions, some materials, such as the doped gallium arsenide (GaAs) and aluminum gallium arsenide (AlGaAs) that have been contemplated for use in quantum-effect devices, have energy bands that are different. And unless the two different materials have energy bands that overlap, electrons cannot be transferred from one to the other. That discontinuity prevents electron movement from one material to the other.

In order to overcome that barrier, a semiconductor "sandwich" is made, consisting of a very thin layer (200 angstroms—about the same size as an electron's wavelength) of AlGaAs be-

tween two layers of GaAs. Then, under certain conditions, the wave nature of electrons make it possible for them to tunnel through the middle barrier layer as if it were not there.

If we take advantage of the barrier effects of differing materials, we can construct several types of quantum-effect devices. There are quantum dots, quantum wires, and quantum wells, depending on whether confinement is to zero, one, or two dimensions (see Fig. 3). The energy bands in one- and two-dimensional

quantum structures are somewhat continuous, meaning that there can be some degree of electron transfer between them by conventional means. In a quantum dot, though, the energy bands become discrete and electron transfer, in a physical sense, is effectively blocked.

Another aspect of the wave nature of electrons becomes apparent in confinement. Standing waves, like those in systems involving sound (the way your voice sounds so great when you sing in the shower) or radio-frequency (affecting an antenna's efficiency) can occur. The quantum structure becomes resonant at a certain frequency.

At resonance, where the standing waves reinforce rather than cancel each other, a small amount of energy has a great effect. A specific voltage will easily cause tunneling; other voltage levels, both higher and lower, will not. That, in effect, enables us to turn a quantum-device switch on or off.

Thus, the quantum effect, which at first appeared to be rather disconcerting, and perhaps to present a barrier to the further miniaturization of electronic components and circuits, now appears to present a way out of the situation. It may eventually allow us to produce complex semiconductor devices that will be perhaps one one-

EXPONENTIAL NOTATION

To express extremely large or extremely small numbers, a method known as exponential notation is frequently used. For example, the number 10^6 represents one million—a one followed by six zeros. The exponent, 6, tells us how many times ten must be multiplied by itself to reach that magnitude, and indicates how many zeros to put after the one if the number is written out.

For numbers smaller than one, a negative exponent is used: 10^{-6} represents one millionth ($1/1,000,000$), or ten divided by itself six times.

Numbers that are not exact multiples of ten can be represented as follows:

$6 \times 10^6 = 6,000,000$ (six times one million)

$4.5 \times 10^6 = 4,500,000$ (four-and-a-half times one million)

$3.14 \times 10^{-4} = 0.000314$ (3.14 times one ten-thousandth)

The table below is a guide to the exponential system for representing values. Each time the exponent changes by one, the value of the number changes by an order of ten.

TABLE 1

10^{12}	1,000,000,000,000	trillion	tera-
10^9	1,000,000,000	billion	giga-
10^6	1,000,000	million	mega-
10^3	1,000	thousand	kilo-
10^2	100	hundred	hecto-
10^1	10	ten	deca-
10^0	1	unit	-
10^{-1}	1/10	tenth	deci-
10^{-2}	1/100	hundredth	centi-
10^{-3}	1/1,000	thousandth	milli-
10^{-6}	1/1,000,000	millionth	micro-
10^{-9}	1/1,000,000,000	billionth	nano-
10^{-12}	1/1,000,000,000,000	trillionth	pico-
10^{-15}	1/1,000,000,000,000,000	quadrillionth	femto-

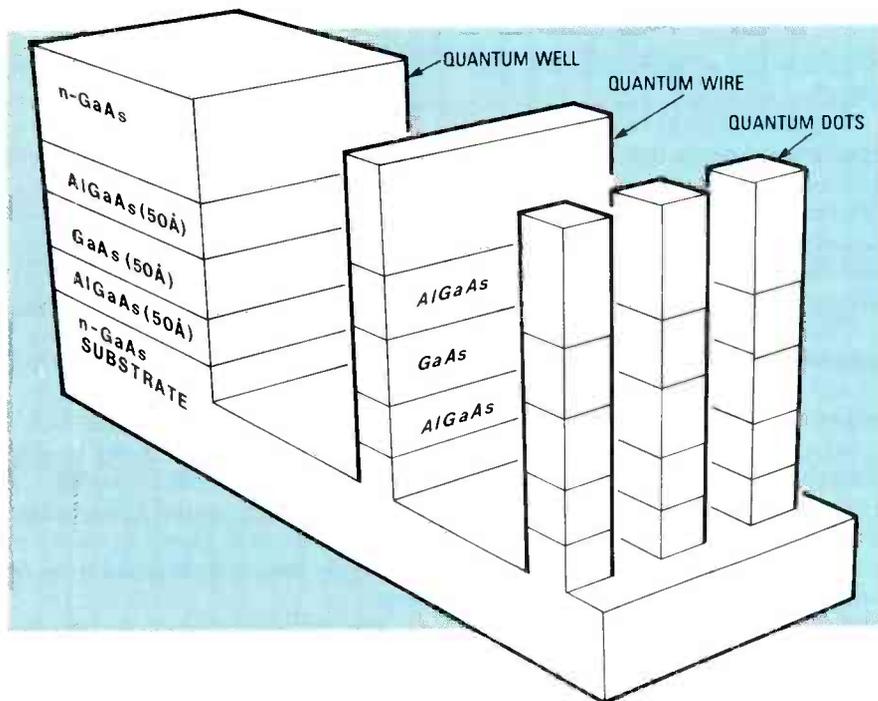


FIG. 3—DEPENDING ON THE DEGREE of confinement of electron travel, a quantum device may be defined as a quantum well, wire, or dot.

hundredth the size of current devices.

Furthermore, while current semiconductor devices have a theoretical switching-speed limit in the picosecond (10^{-12} second) range, quantum-effect devices can have switching speeds up to 100 femtoseconds (10^{-13} second)—ten times faster. The way in which such a device might be constructed is shown in Fig. 4, and an experimental array of quantum-dot diodes is shown in Fig. 5.

Getting things down to size

It is unfortunate that this new science of nanoelectronics (from the Greek nanos, meaning "dwarf") is not yet a reality. There are still many difficulties to overcome before you'll

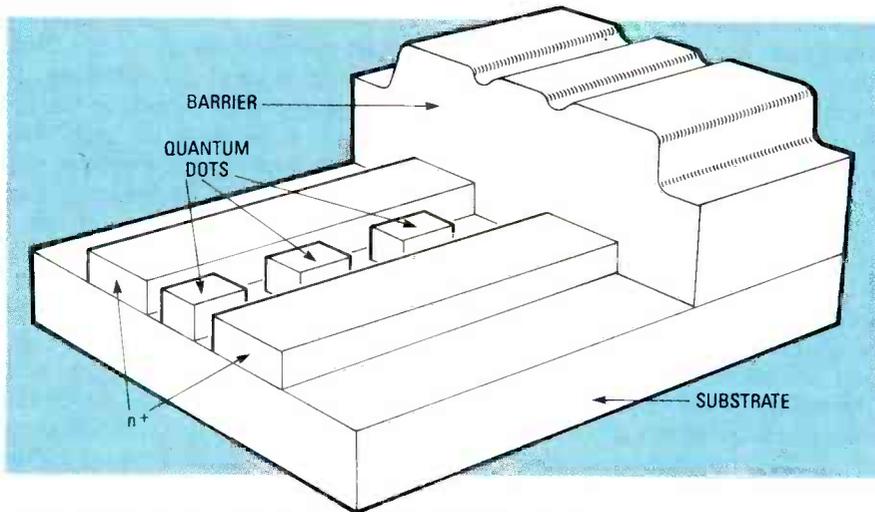


FIG. 4—CROSS SECTION of a theoretical quantum-dot device.

be able to buy a “supercomputer on a chip.”

The first difficulty in making semiconductor devices that small lies in getting the pattern for the IC from its original size (perhaps several dozen square feet) down to a quarter-inch or so—the size of the square piece of silicon for which it is intended.

Conventional integrated circuits are produced in much the same way as an enlargement from a photographic negative, only in reverse. Simply speaking, a large negative of the IC pattern is projected onto the sensitized surface of the small silicon wafer that will eventually become the integrated circuit. It is an optical process, where a beam of light does the work. The main difference is that the image is reduced in size rather than blown up.

In quantum-effect IC's, though, we are dealing with extremely small dimensions. So small, in fact, that light

is too crude a medium to achieve the precision required. The wavelength of light is measured in angstroms, one angstrom being one ten-thousandth of a micron, or 10^{-10} meter. Blue light has a wavelength of approximately 4500 angstroms, or 4.5×10^{-7} meters. The feature size of our intended quantum-effect IC, however, is less than 3×10^{-7} meters, which is smaller than the wavelength of the light that we would use to project the image.

Obviously, that method won't work. It would be like trying to slice an olive with a sledgehammer! To achieve smaller feature sizes, something smaller than photons (with their relatively long wavelengths) must be used.

The current solution to the size problem is a technique called electron-beam lithography, where electrons, rather than photons, are used. With their smaller wavelengths, electrons afford a much greater definition

than photons. (That is why electron microscopes can enable us to see things that are much smaller than we can see using conventional optical microscopes.)

Electron-beam lithography, however, is an impractical method for mass-production. At present, the most promising answer lies in Masked Ion-Beam Lithography (MIBL), a technique now under investigation at the University of Houston. Instead of using photons or electrons to project the IC pattern onto the surface of a silicon wafer, MIBL uses ions of hydrogen. The wavelength of those ions is even smaller than that of electrons, making it possible to achieve the feature size required by quantum-effect devices.

The next problem comes in the interconnection of the components on the surface of the integrated circuit. In ordinary-scale IC's, the components are connected by thin strips of conductive material deposited on the silicon surface. At the quantum-effect scale, however, such a method is impractical. Not only does electrical resistance and current leakage cause problems, but we also run into the problem of how to contain the electrons in the microscopic conductors that would have to be used.

One solution is to make the interconnects as large as, if not larger than, the components they join—not a very practical answer. A more elegant solution involves what is called limited-interconnect architecture. Using computer assistance, the IC pattern is laid out so that parts of the circuit that are electrically adjacent to one another are physically adjacent as well. Where one ends, the next begins, and electrons move from one to the other directly. Using that approach, at least a good deal of the interconnections can be eliminated.

Other difficulties arise from the extremely small feature size of quantum-effect devices. A quantum dot can contain only a few electrons—not enough to make it possible to discriminate between a legitimate signal and random noise. Several quantum dots have to be ganged together to overcome the noise threshold.

Also, getting signals out of a quantum-effect integrated circuit and into the real world is not a simple matter. The voltages and currents present in quantum-effect devices are much

continued on page 104

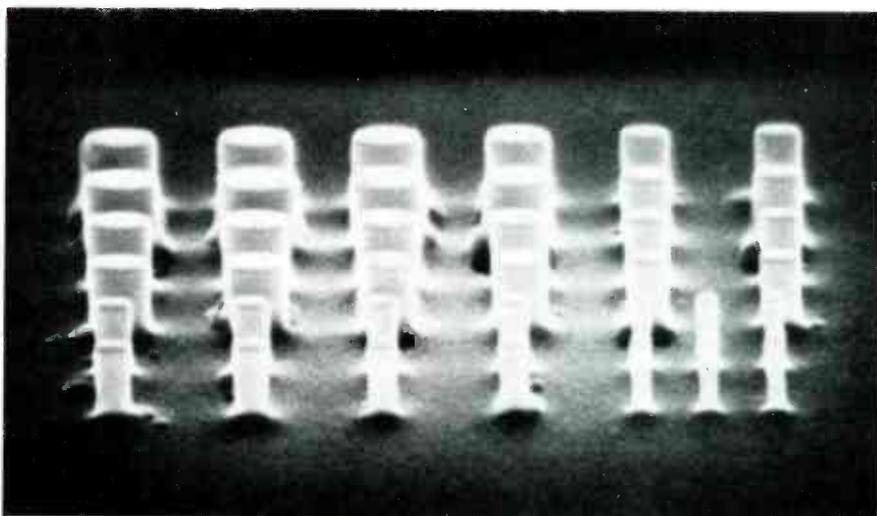


FIG. 5—MICROGRAPH of an experimental array of quantum-dot diodes. The smallest feature here is just 1000 angstroms, or 10^{-7} meters. (Photo courtesy of Texas Instruments)



VCR SERVICING BASICS

This quick six-step approach can help you to isolate VCR failures.

BRIAN PHELPS

PEOPLE OFTEN HAVE QUESTIONS DEALING with VCR problems. One of the most frequent is: "How can I tell which circuit in my VCR is causing the symptoms I see on my TV or monitor?" This article will provide some of the answers to that question, and also discuss some valuable servicing tips.

One reason why it's sometimes so difficult to isolate a VCR failure is that almost any circuit can cause many different problems, and, quite often, the symptoms are misleading. Sometimes something unusual, such as a shorted switching transistor or a capstan- or cylinder-servo problem, may confuse a servicer into replacing a good component. Therefore, to avoid any unnecessary procedures, some kind of step-by-step process is required.

A step-by-step method

One way to isolate problems is by checking out the unit in the following order:

1—Visual inspection

- 2—Check microprocessor
- 3—Servos (cylinder and capstan)
- 4—Luminance
- 5—Chrominance
- 6—Audio

Visual inspection

Looking for the obvious includes things such as foreign objects that may be jammed inside the VCR. (You would be surprised what children might manage to stick inside an appliance). The tracking control may be out of the center-detent position, or the consumer may have locked-up their VCR in a program mode. At any rate, failure to check for the obvious problems first can send you on a wild goose chase.

Microprocessor analysis

There are some very basic things to check that concern the microprocessor.

- The B+ supply for DC level, ripple, and any high-frequency glitches.
- The clock input for any DC voltage that should be there, the amplitude of

the clock signal, and the frequency.

- The data inputs and outputs. We're mostly concerned that there is activity on those lines, and that the activity changes when different functions of the VCR are selected, rather than how the actual signals look.

- The reset pulse; it usually occurs between 0.5 and 1 second after B+ is applied to the microprocessor. If the reset pulse is absent, the microprocessor may start its routine at any point, yielding some strange symptoms—if anything at all.

Servos

When troubleshooting servos, it is often helpful to use a block diagram (see Fig. 1). Before you start, however, you must decide which servo or servos you should be looking at.

You can determine if the problem is caused from the capstan or the cylinder servos by listening to the audio. The audio quality is dependent upon the rate at which the tape is being pulled by the capstan across the audio head. If the speed is incorrect, the

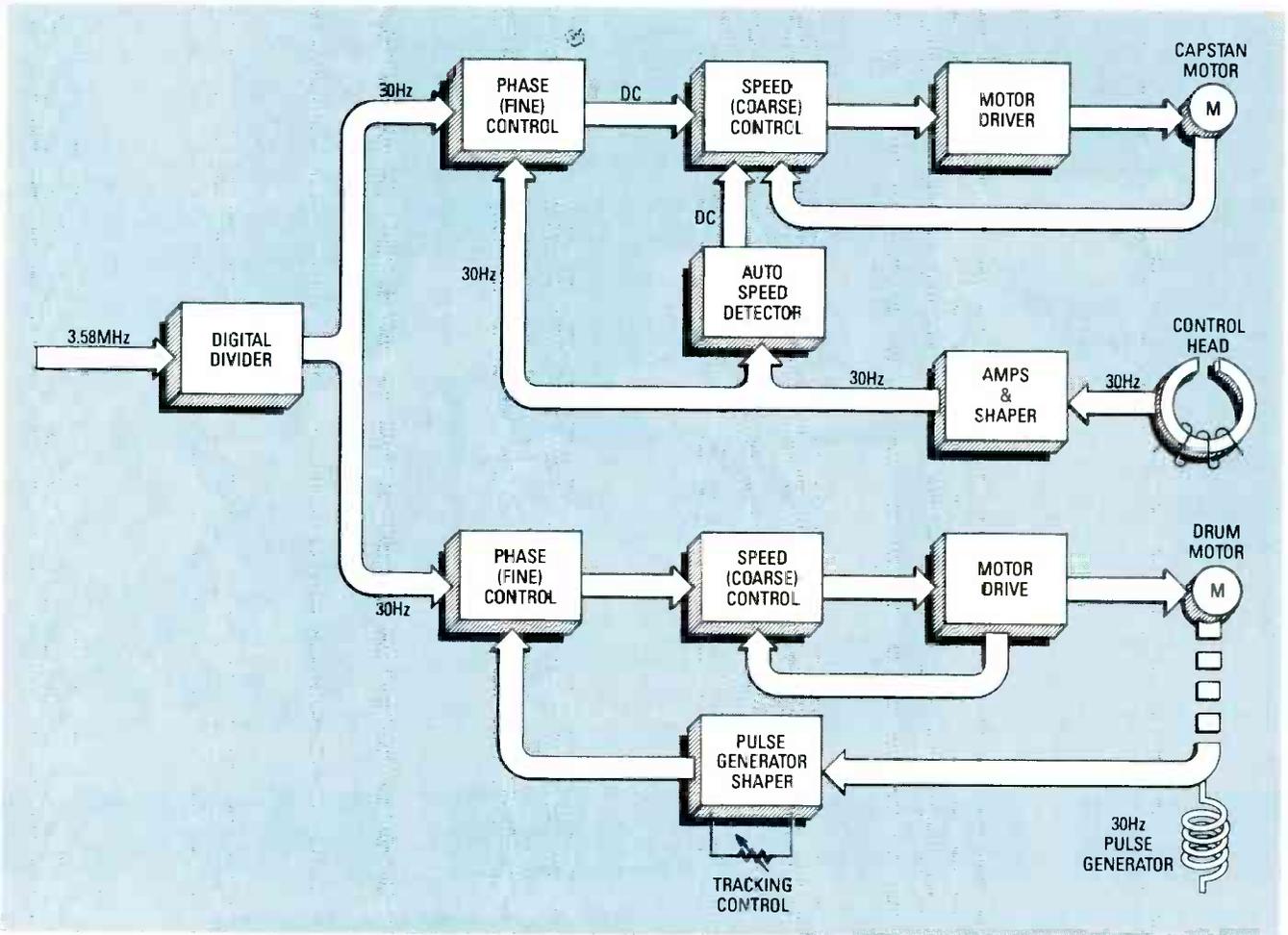


FIG. 1—THE BLOCK DIAGRAM of the servo circuits inside a VCR. A block diagram is often very helpful in troubleshooting because it shows you how the different sections of a circuit are interconnected.

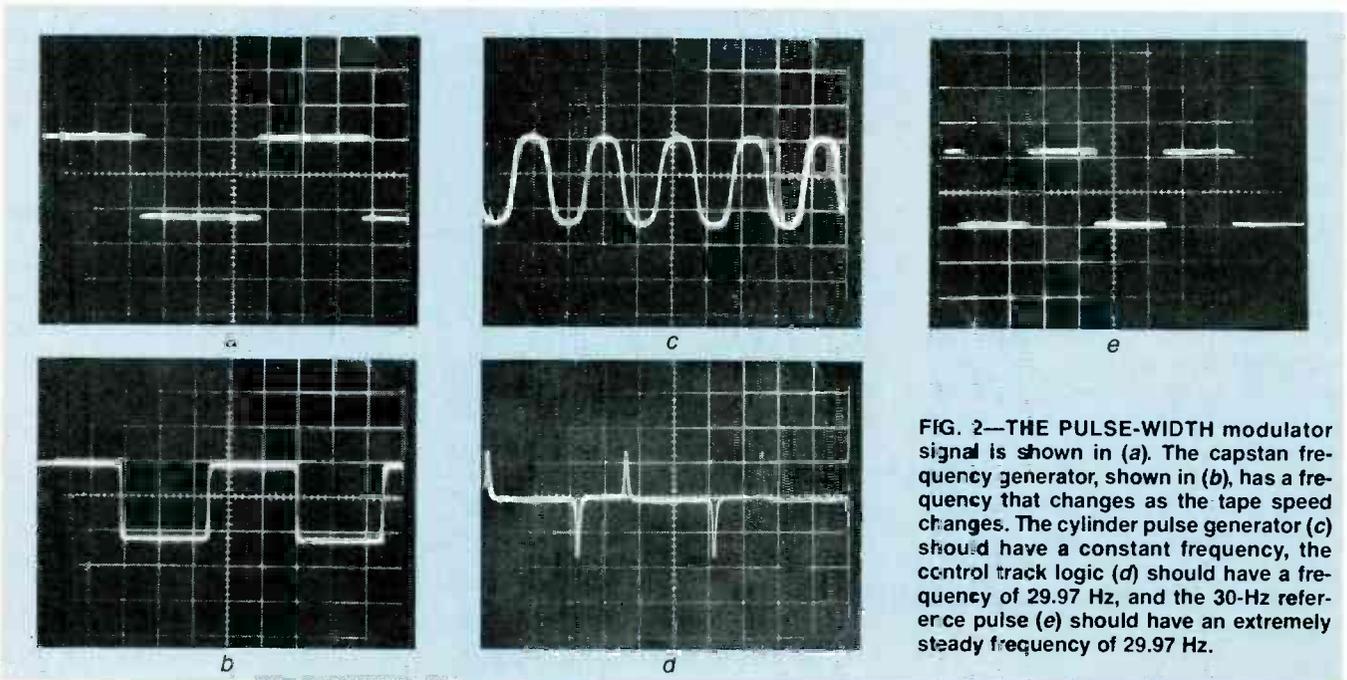


FIG. 2—THE PULSE-WIDTH modulator signal is shown in (a). The capstan frequency generator, shown in (b), has a frequency that changes as the tape speed changes. The cylinder pulse generator (c) should have a constant frequency, the control track logic (d) should have a frequency of 29.97 Hz, and the 30-Hz reference pulse (e) should have an extremely steady frequency of 29.97 Hz.

audio will sound distorted. But, if the audio sounds good, you should lock at the cylinder servo circuitry.

When analyzing the servo circuits, there are some key signals to check. Those include the pulse-width modu-

lator signal (PWM), the capstan frequency-generator signal (FG), the cylinder pulse-generator signal (PG),

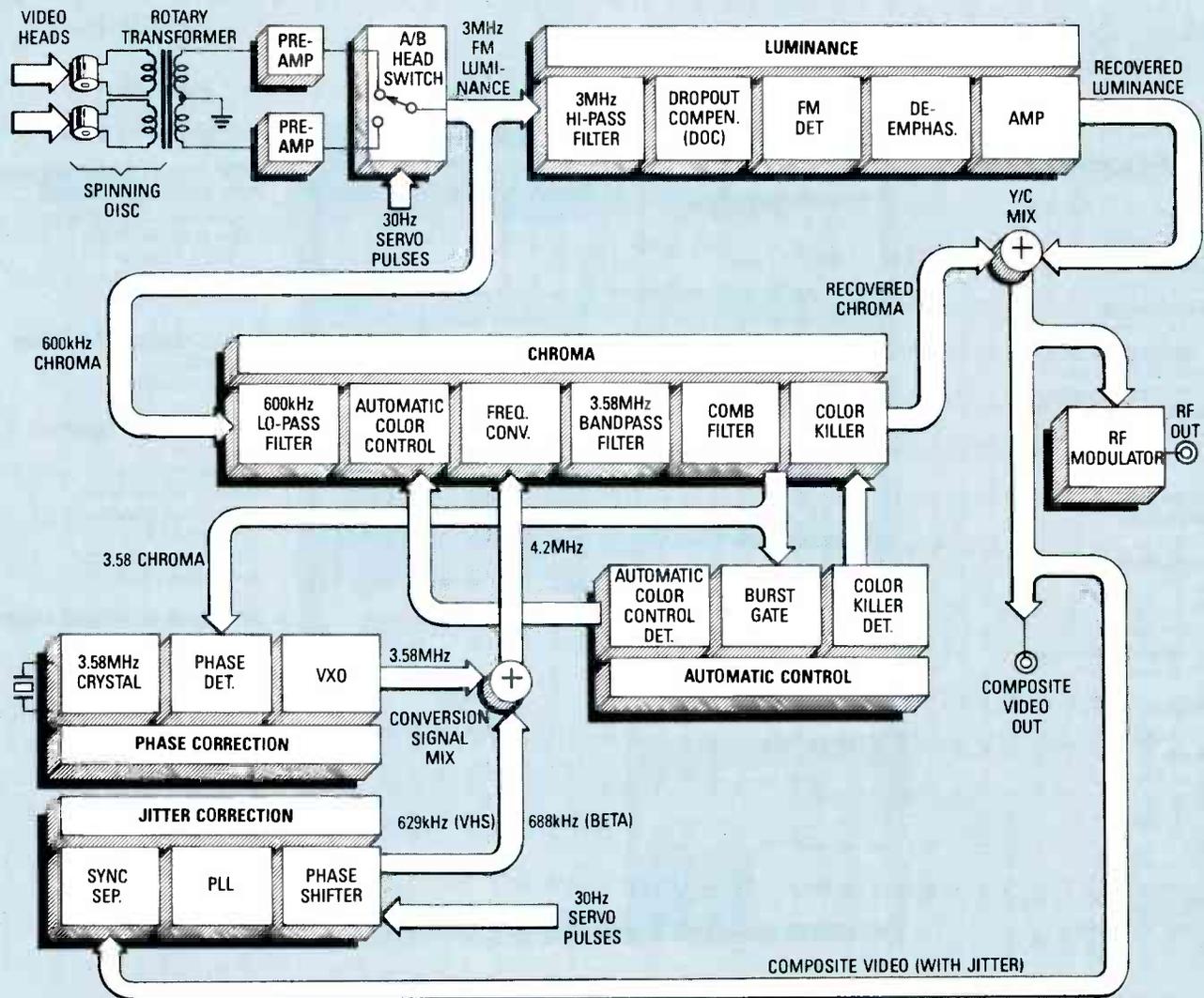


FIG. 3—THIS BLOCK DIAGRAM shows the video-processing circuitry inside a VCR. The circuitry inside all VCR's is similar.

the control-track logic pulse (CTL), and the 30-Hz reference signal. Figure 2 shows how those signals should look for proper servo operation.

Luminance circuitry

The luminance circuits typically produce failures ranging from noisy video to a lack of video. However, failures such as those can also be caused by anything from the video-head circuitry to the RF modulator.

A good approach to troubleshooting luminance circuits is to inject a signal that would be present at various test points if the VCR were operating properly. That way you can determine which circuits are and aren't working by checking every point where the signal is supposed to appear.

One example of troubleshooting by using signal injection is substituting a known good signal in place of the one coming from the video heads (see Fig.

3). Sencore's VC63 VCR test accessory provides a signal to inject into the video preamps. (You should use equal levels for both preamp inputs and if one of the inputs needs a greater signal level, that's the path to follow.) That simple procedure tells you whether or not the preamps were receiving a good signal from the video heads. If everything checks out after the signal is injected, that would probably indicate a bad video head.

If, after injecting a signal into the preamps, there is still a problem, the chances are good that the video heads are all right. For example, suppose that one of the playback/record switching transistors has a short. That would put 10 ohms between the playback path for one of the heads and ground. The resulting picture on the monitor is similar to that of a bad video head, and many repairmen would prematurely clean and/or re-

place the video heads—a procedure that is costly and time-consuming.

Chrominance

Defects in the chrominance and audio circuits can be detected by looking at the color or listening to the audio. Quick checks for the chrominance include testing the 3.58-MHz oscillator, the 4.2-MHz conversion signal, the 30-Hz and 15-kHz reference signals, and the 629-kHz VHS color subcarrier.

If you troubleshoot a VCR following the procedures in the correct order, you can quickly and accurately isolate defective stages in the circuitry. After a couple of trial runs on known-good VCR's, you should be able to tackle the "Tough Dog" problems that you may come across. Just be sure that you learn any new techniques and procedures on a known good unit, so that you are not led astray by erroneous readings and strange results.

R-E

This will be coming to you when you subscribe to **Radio-Electronics**

• **HELPFUL CONSTRUCTION ARTICLES...**


- Test Equipment
- Hi-Fi Accessories
- Telephone Accessories
- Music Synthesizers
- Computer Equipment
- Automotive Equipment
- Intruder Alarms- Home & Car
- Video Accessories

• **NEWS ON NEW TECHNOLOGY**

- Computers
- Microprocessors
- Satellite TV
- Teletext
- Automotive Electronics
- Speech Synthesizers
- IC Applications

• **FASCINATING "HOW TO DO IT" ARTICLES...**

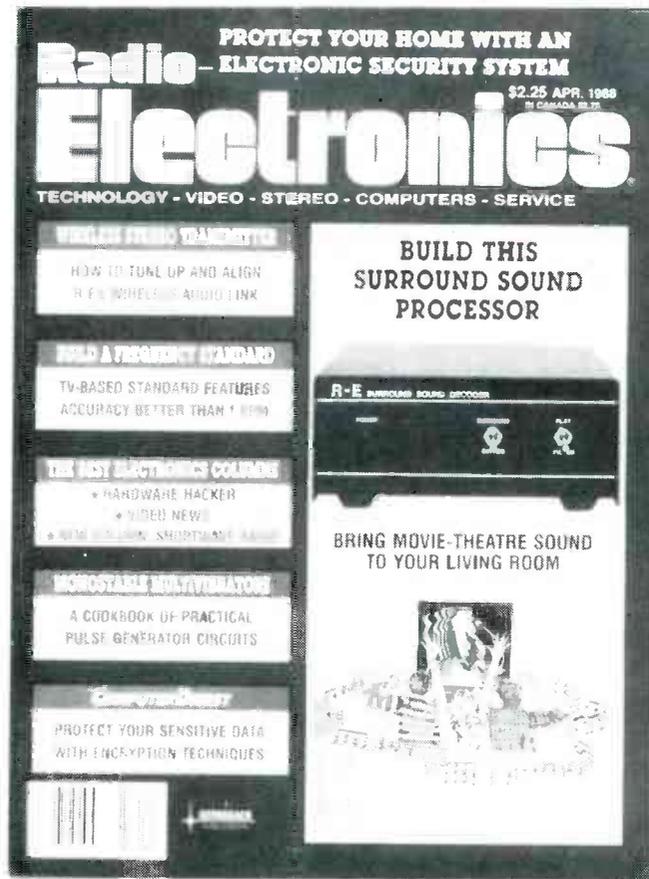- Build Your Own Projects
- Make Your Own PC Boards
- Wiring Techniques
- Soldering and Desoldering
- Design and Prototyping



• **HOW YOU AND THE COMPUTER CAN BE FRIENDS...**

- Getting Started
- Programs, Circuit Design, Games
- A/D-D/A Interfacing
- Peripheral Equipment

• **NEW AUDIO DIMENSIONS FOR YOUR PLEASURE...**

- Noise-Reduction Devices
- How to Connect that Extra Add-On
- Hi-Fi Accessories
- New Technology

• **TV WONDERS FOR YOUR FUTURE...**

- Latest Receivers and Circuits
- The Home Entertainment Center
- Projection TV
- Satellite TV Receivers
- Jack Darr's Monthly Service Clinic
- Service Problems and Solutions

• **REGULAR MONTHLY FEATURES**


- DESIGNERS NOTEBOOK by Robert Grossblatt
- HOBBY CORNER by "Doc" Savage, K4SDS
- STATE-OF-SOLID-STATE by Bob Scott
- WHAT'S NEWS, new products, stereo news and NEW IDEAS, STEREO PRODUCTS, NEW COMPUTER PRODUCTS FOR HOME/JOB and MUCH MORE!

Radio-Electronics covers all aspects of the fast moving electronics field...featuring **COMPUTERS • VIDEO • STEREO TECHNOLOGY • SERVICE COMMUNICATIONS • PROJECTS**

Get it all!

Subscribe today to **Radio-Electronics**! Don't miss a single issue and...see subscription card in this issue for big savings.

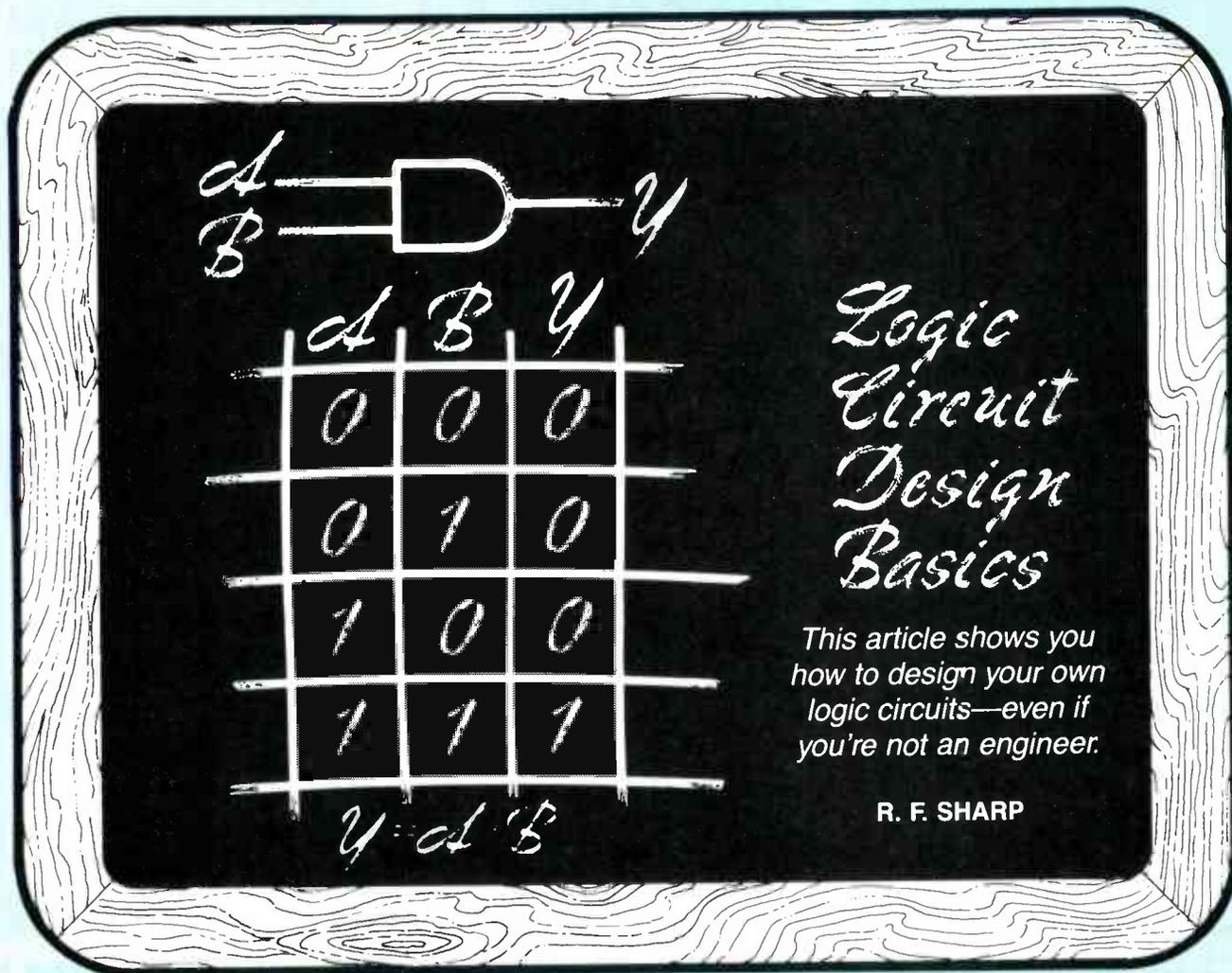When you select one of the subscription offers listed on the handy coupon—you'll be assured of having your copy reserved, even if it sells out on the newsstand. Make sure you get all the excitement in every issue of **Radio-Electronics**, every month, by filling in and mailing your subscription card today.



NOT LONG AGO, PEOPLE WHO WERE INVOLVED in electronics as a hobby more than likely worked in the electronics field as well. As a result, those people quite often had a strong background in circuit design. Nowadays, however, many people dabble with all sorts of do-it-yourself electronic gadgets. Unfortunately, when you build a ready-to-assemble kit, or if you assemble a circuit according to someone else's schematic, you learn very little in the way of actual circuit-design and engineering techniques.

In this article we will show you a systematic approach that is used by circuit designers to create switching circuits. And although circuit design is a broad topic, and cannot be covered in detail in the space we have available, you should still be able to acquire enough knowledge from reading this article to get a good head start when you set out to design a logic circuit of your own.

We will begin with the fundamentals and, although the subject of circuit design requires some familiarity with algebra, we will try to avoid mathematics as much as possible. Those of you who are already familiar with digital circuitry may find some parts of this article too elementary and will want to skip over them. Even so, it might be a good idea to read along just as a refresher.

Number bases

The most elemental language of computers or digital circuits is the base-2 (or binary) number system. The reason for that is because all digital circuitry is basically a collection of on/off switches, electronic or mechanical. And since a switch has only two states it can therefore be represented using the digits 0 or 1 in the binary number system. Other number systems, such as *Binary Coded Decimal* (BCD) and hexadecimal (base 16)

are natural outgrowths of base 2. Our everyday number system, decimal, was originally chosen as base 10 to correspond to the number of fingers (digits) we have. Perhaps there are some computer scientists who at one time or another have wished that humans had eight fingers on each hand so that we would be more familiar with hexadecimal!

To help explain how the binary number system works, let us first analyze the decimal number system. The base-10 number system works like this: The number 1234 means $4 \times 1 + 3 \times 10 + 2 \times 100 + 1 \times 1000$. Each successive position to the left of the decimal point represents the next highest power of 10. So, the number 1234 could also be represented as $4 \times 10^0 + 3 \times 10^1 + 2 \times 10^2 + 1 \times 10^3$. (Note that any number raised to the power of 0 is equal to 1 and any number raised to the power of 1 is equal to the number itself.)

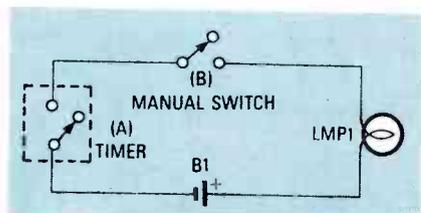


FIG. 1—IN THIS CIRCUIT, the lamp will turn on if both the timer AND the switch are closed.

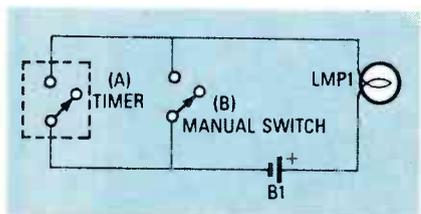


FIG. 2—THIS CIRCUIT REQUIRES that either the timer OR the switch must be closed for the lamp to be on.

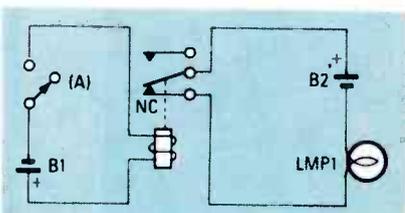


FIG. 3—IF THE SWITCH (A) is open, the lamp is on, and if the switch is closed, the lamp is off. The relay inverts the switch's action.

Base-2 numbers use powers of 2 instead of 10. For example, the number 111011 in base 2 translates as $1 \times 1 + 1 \times 2 + 0 \times 4 + 1 \times 8 + 1 \times 16 + 1 \times 32$. It could also be written as $1 \times 2^0 + 1 \times 2^1 + 0 \times 2^2 + 1 \times 2^3 + 1 \times 2^4 + 1 \times 2^5$. Notice that the base number of any given number system never appears as a single character. For example, base 10 only has the characters 0-9, while base 2 only has the characters, 0 and 1. Counting in binary is actually very easy, for example, 000, 001, 010, 011, 100, 101, 110, 111, 1000, 1001, etc.

Logic

When it comes to switching circuits, there are two types of logic: positive and negative. Positive logic assigns the digit "1" to represent a high output and "0" to represent a low output. Negative Logic is much less common and works just the opposite (1 = low output and 0 = high output). For our purposes we'll say that a high output is 5 volts and a low output is 0 volt. We can also say that a "1" means true and that a "0" means false.

So why, you wonder, is all that of interest? As an example, suppose we want to design a circuit that will turn on a lamp at 7:00 pm. We would also like to have an override switch so that we can manually turn the lamp off regardless of the time.

The circuit in Fig. 1 turns on the lamp if both the timer AND the manual switch is closed. Using positive logic we can say that LMP1 is true only if A AND B are closed. Alternately, we might want to turn the lamp on even if the timer has not reached its set time. The circuit in Fig. 2 will light the bulb if either the timer OR the manual switch is closed. Again, using positive logic we can say that LMP1 is true if either A OR B is closed.

While those two circuits are trivial, and are very easy to design, we have nonetheless introduced some concepts that will eventually allow us to create much more complicated circuits. The two key words that we used were AND and OR, our basic tools. When we talk about AND and OR in electronics, we are referring to devices called logic gates (switches that control electron flow).

Our last basic building block is the NOT gate, better known as an inverter. Figure 3 shows a way of implementing the NOT function by using a normally closed relay to invert the switch's action. Logically, LMP1 is true only when switch A is open.

Logic gates can be made using diodes and resistors, known as Diode Resistor Logic (DRL). Figure 4-a is a DRL OR gate and it works as follows: If both inputs (A and B) are low, the output (V_{OUT}) is low. However, if either input is high, the diode that corresponds to the high input conducts, providing a path for current to flow to ground. As the current flows, most of

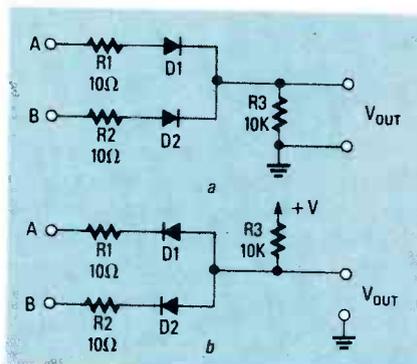


FIG. 4—THESE TWO CIRCUITS use diode-resistor logic (DRL). The one in a is an OR gate, and the one in b is an AND gate.

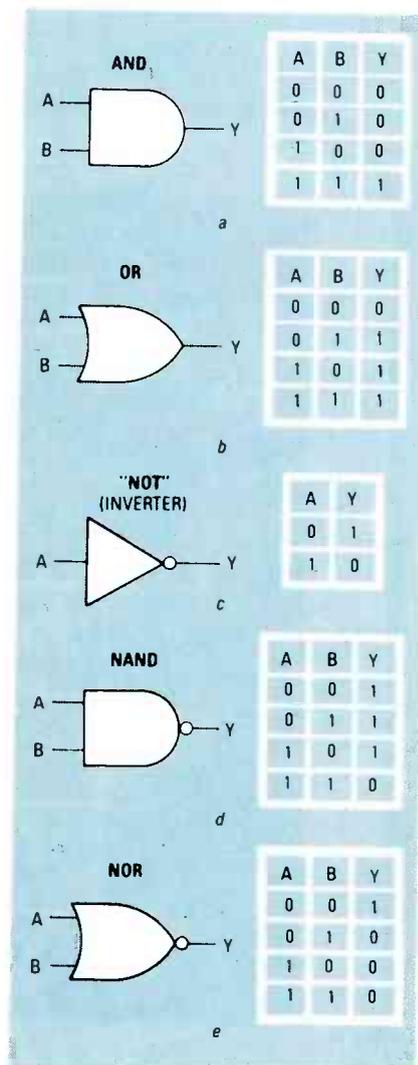


FIG. 5—SHOWN HERE ARE the truth tables and schematic symbols for the five basic logic gates.

the voltage is dropped across R3, and a high is measured at V_{OUT} . The output is the same if both inputs are high.

Figure 4-b is a DRL AND gate and it works as follows: If both inputs are low, both diodes are conducting and V_{OUT} will be low. If only one input is high, the other input is still conducting and there is still a low at the output. It is only when both inputs are high, that neither diode is conducting and a high is measured at the output.

Two other useful gates can be made by adding an inverter at the output of an AND gate and an OR gate. An AND gate becomes a NAND gate (meaning NOT AND) and an OR gate becomes a NOR gate (meaning NOT OR).

Truth tables

A truth table is a method of summarizing the operation of a gate or

combination of gates. Circuits are said to have equal functions if their truth tables are the same. In general, the inputs to a logic gate are labeled "A", "B", "C", etc., and the output is labeled "Y." A truth table usually has those designations, uses positive logic, and 1's and 0's to represent highs and lows. You may also come across a truth table using "T" and "F"(true and false), or "H" and "L" (high and low).

A truth table lists all possible combinations of inputs and their corresponding outputs. Figure 5 shows the truth tables for the gates that we have discussed, along with the schematic symbols for each one. Note that although we have shown only two inputs for the AND, OR, NAND, and NOR gates, they often have several inputs.

Listing all possible combinations of inputs can be a very painstaking process, especially for a circuit having ten inputs. That would require that you recognize 1024 different combinations. The simplest way to figure out how many possible combinations of inputs there are is to count the number of inputs to the device or circuit, and then raise 2 to that power. For example, a circuit having ten inputs would have 2^{10} , or 1024 possible combinations of inputs.

Figure 6 shows a partial truth table for a 5-input AND gate. Although the table is incomplete, you should see a pattern there. Notice that the five inputs (A-E) are actually counting in binary from zero to thirty one (there are a total of 32 possible combinations of inputs). For example, input number 4 corresponds to the binary number 4 (00100). Notice that the

	INPUTS					OUTPUT
	16's	8's	4's	2's	1's	
	A	B	C	D	E	
0	0	0	0	0	0	0
1	0	0	0	0	1	0
2	0	0	0	1	0	0
3	0	0	0	1	1	0
4	0	0	1	0	0	0
5	0	0	1	0	1	0
6	0	0	1	1	0	0
7	0	0	1	1	1	0
8	0	1	0	0	0	0
9	0	1	0	0	1	0
10	0	1	0	1	0	0
.
.
.
31	1	1	1	1	1	1

FIG. 6—THIS IS A PARTIAL truth table for a five-input AND gate.

only time the output of the 5-input AND gate is a "1" is when all the inputs are 1.

Suppose you had a device with seven inputs and you had to list all the possible combinations of inputs. To make a truth table you would first have to calculate: $2^7=128$. That means that there are 128 possible combinations of inputs. Then you would have to count in binary from 0 to 127, and that would be the list of all the different inputs. Data sheets supplied with logic components usually list truth tables.

Boolean algebra

So far we have developed most of the tools we will need for circuit design. However, the last subject that you must become familiar with, Boolean algebra, is at the very heart of circuit design.

Boolean algebra is named in honor of George Boole, an English mathematician, who was underappreciated during his own times. His developments of the "algebra of logic" had little practical use in 1847 when it was introduced. However in 1938, Claude E. Shannon of M. I. T. presented a paper outlining how Boolean algebra could be adapted to represent switching circuits.

If you are familiar with ordinary algebra you'll notice some similarities between that and Boolean algebra. The main difference is that the variables (the unknown quantities) of algebra can represent any value, while the constraints of logic (that a statement is either true or false) insist that variables of Boolean algebra have only one of two values.

Rules

Certain rules must be followed in Boolean algebra. We will not offer any proof of these rules, we will simply list them for later use. **In Boolean algebra you must be aware that:** the symbol "." means AND (the "." can be dropped: $A \cdot B$ can also be written as AB), the symbol "+" means OR, and when something has a bar over it, the term is negated; for example, "A" means "A NOT."

- 1—A, B, C, etc., can either be 1 or 0 (true or false)
- 2— $0 \cdot 0 = 0$
- 3— $0 \cdot 1 = 0$
- 4— $1 \cdot 0 = 0$
- 5— $1 \cdot 1 = 1$
- 5— $0 + 0 = 0$

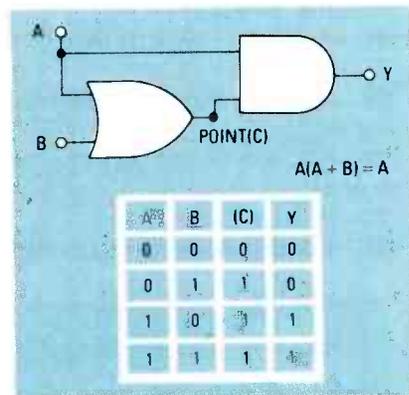


FIG. 7—THIS CIRCUIT PROVES that $A(A+B)=A$ because the columns for A and Y in the truth table are the same.

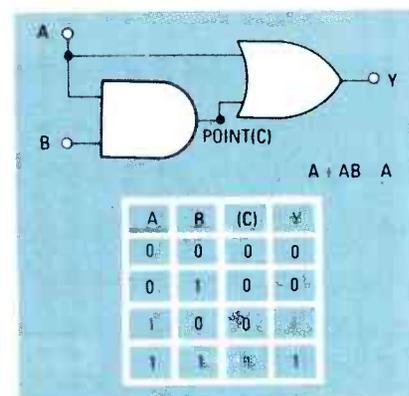


FIG. 8— $A + AB = A$. That can be proven by comparing columns A and Y.

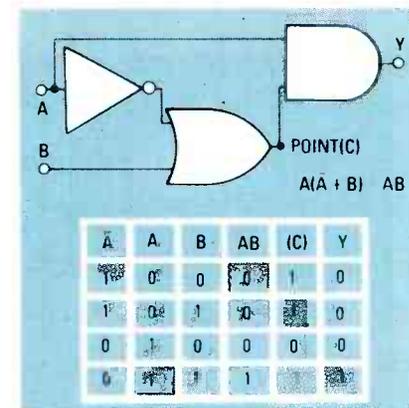


FIG. 9—THE TRUTH TABLE has been expanded to include other points in the circuit. It proves that $A(A+B)=AB$.

- 6— $0 + 1 = 1$
- 7— $1 + 0 = 1$
- 8— $1 + 1 = 1$
- 9— $\bar{1} = 0$
- 10— $\bar{0} = 1$
- 11— $AB = BA$ (the commutative property)
- 12— $A + B = B + A$
- 13— $A(BC) = AB(C)$ (grouping is also commutative)
- 14— $A + (B + C) = (A + B) + C$

- 15— $A(B+C) = AB+AC$ (the distributive property)
- 16— $A+BC = (A+B)(A+C)$
- 17— $A \cdot 0 = 0$
- 18— $A \cdot 1 = A$ (depends solely on A's value)
- 19— $AA = A$ (A can only be equal to 0 or 1)
- 20— $A \cdot \bar{A} = 0$
- 21—a double negative equals itself

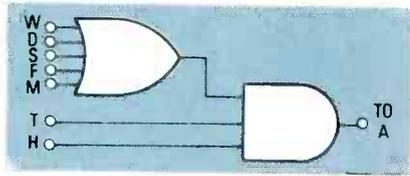


FIG. 10—OUR BURGLAR-ALARM system can be represented using logic gates.

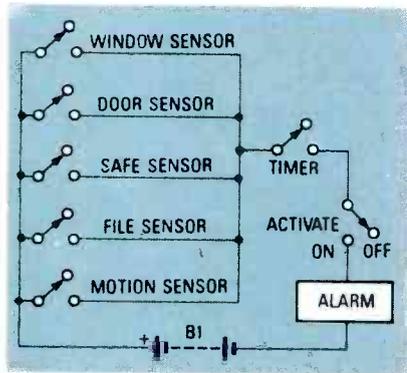


FIG. 11—HERE IS THE ACTUAL CIRCUITRY for our office burglar-alarm system.

- 22— $A+0 = A$
- 23— $A+1 = 1$ (1 is always true)
- 24— $A+\bar{A} = 1$
- 25— $A+\bar{A} = 1$

DeMorgan's theorems can often be used to simplify a Boolean expression. The theorems are as follows:

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

and

$$\overline{A + B + C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

We will not prove the validity of those equations; however, the three steps for using them are:

- 1—Change all the “ \cdot ” to “ $+$ ” and vice versa
- 2—Replace all variables with their complements. (A would become \bar{A} , B would become \bar{B} , etc.)
- 3—Negate the entire expression.

Figures 7–9 show some interesting ways of simplifying Boolean expressions. The relationships can be derived from DeMorgan's theorems, however, there is no need to go into those derivations.

The circuit in Fig. 7 proves that: $A(A+B) = A$. In that circuit Y is true if A is true AND A OR B is true. Obviously Y is equal to A. The truth table demonstrates that equivalence. The circuit in Fig. 8 proves that $A+AB = A$. You can see that by looking at the truth table and compar-

ing A to Y. That whole circuit can therefore be replaced by A alone. The circuit in Fig. 9 is a bit more tricky, proving that $A(\bar{A}+B) = AB$. The truth table has been extended to include \bar{A} and AB. Since the truth table shows that AB and Y are equal, the expression is true.

In the beginning of this article we agreed to go lightly on mathematics, and by now you probably suspect that we have strayed from that promise. Take heart, you now have all the equipment you need to design a workable switching circuit. Of course you must observe the parameters given in the data that is included with the components you plan to use in your designs. Those include power-consumption, loading, and timing constraints, that we are not going to get into.

Circuits

Before we apply the techniques we have learned to designing an actual circuit, let us first list the steps we must follow when designing a circuit from scratch:

- 1—State the problem in logical and concise sentences, using the logical operators OR, AND, and NOT.
- 2—List the input variables and assign a letter to each.
- 3—Determine the desired output for the circuit.
- 4—Translate the words into a Boolean equation.
- 5—Represent the Boolean expression using gate symbols.
- 6—Redraw the schematic using real components.

As our first test of that approach we will design a security system for an office.

Let's suppose that the office has a window and a door that are potential entrances for a burglar. We also want to guard the contents of a safe and a file cabinet. As an added measure of security we will add a motion sensor to cover the entire room. Since no one is authorized to enter the room except during working hours, we can power the alarm system from a timer that activates the system from 5:30 pm until 8:30 am. We will also need some sort of disable switch in case an authorized person must enter during non-working hours.

Step one:

The alarm will sound if the timer is on AND the on/off switch is on AND the window sensor OR the door sensor OR

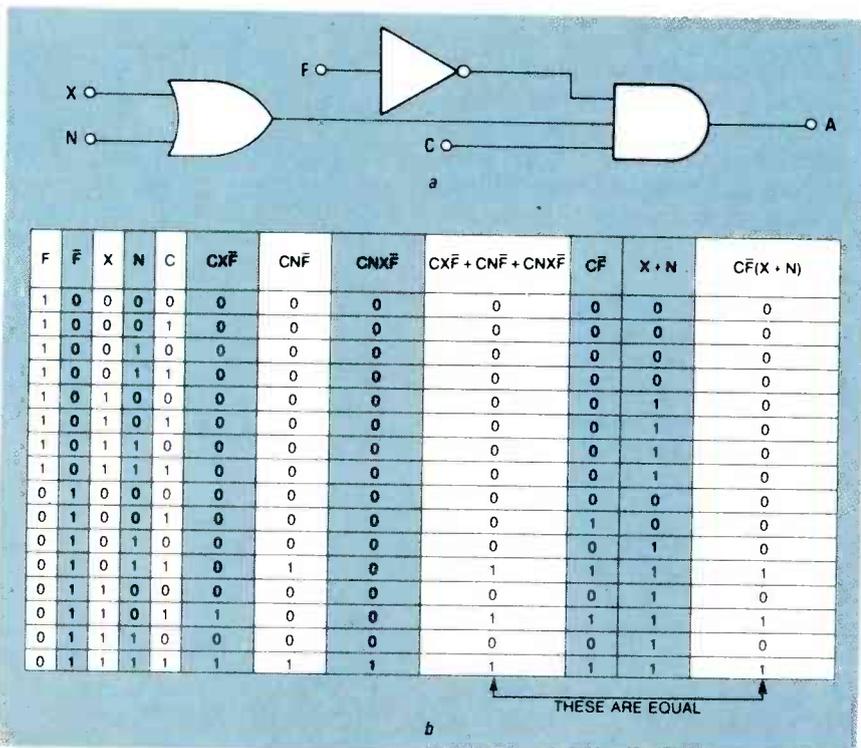


FIG. 12—THIS CIRCUIT WILL PREVENT our farmer from loosing any of his goods.

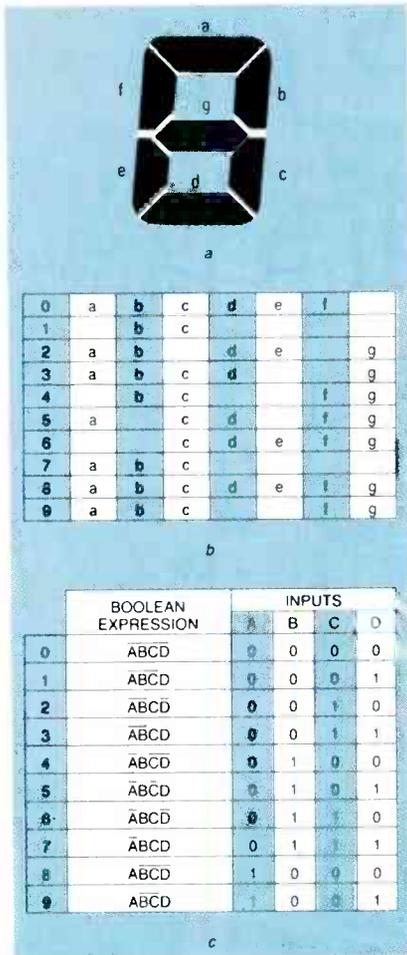


FIG. 13—A 7-SEGMENT DISPLAY (a) is labeled as shown. In order for it to display a number correctly, the segments shown in b must be lit. The table in c shows the Boolean expressions that must be decoded in order to display the corresponding decimal number.

the safe sensor OR the file sensor OR the motion sensor are on (or triggered by an intruder).

Step two:

We will represent our variables with the following letters:

- Window sensor—W
- Door sensor—D
- Safe sensor—S
- File sensor—F
- Motion sensor—M
- Timer—T
- On/off switch—H

Step three:

Our output will be something like a bell or siren and we will represent it with the letter “A”

Step four:

Our Boolean expression is:
 $A = TH(W + D + S + F + M)$

Step five:

Figure 10 shows our Boolean expression being implemented with gate symbols.

Step six:

The easiest way to implement our alarm system is to use switches to detect an open or closed window, door, safe, or file cabinet. The motion sensor can be considered as a switch that closes when motion is detected in the room. The circuit in Fig. 11 illustrates our alarm system.

The chicken and the fox

Our first circuit was fairly simple. Let us now turn to a classic example, a variation on what appears in nearly all logic texts. This time we will design an electronic version of an old word puzzle:

There was once a farmer who was taking to market a fox, a chicken, and a basket of corn. To get to market the farmer had to cross a stream. His boat could carry only the farmer and one other item. The farmer found himself in a dilemma. If he left the chicken and the corn together while he took the fox across the stream, the chicken would feast on the corn. Alternately, if the chicken and the fox were left alone, that would cost the farmer a hen. Short of wringing a few necks, what was the farmer to do? We’re sure everyone has heard this one, but as a refresher, first the chicken is taken across and left alone on the market side of the stream. The farmer returns across the stream and picks up the fox which he then carries across. The farmer returns the chicken to the original side where he exchanges it for the corn. The corn is taken across and left with its safe companion, the fox. The

farmer returns for the chicken and, on recrossing, is on his way to market; all products intact and healthy, though a bit confused.

Now we want to construct an electronic game around that old scenario.

Step 1:

We want to sound an alarm if the fox AND chicken are together but NOT the farmer, OR if the corn AND chicken are together but NOT the farmer, OR if the corn AND the chicken AND the fox are together but NOT the farmer (that last situation could leave the farmer with only a very fat fox!).

Step 2:

We’ll use the following letters:

- Farmer—F
- Fox—X
- Corn—N
- Chicken—C

Step 3:

Our output will be a buzzer or light represented by the letter “A”

Step 4:

Our Boolean expression is: $A = CX\overline{F} + CN\overline{F} + CNX\overline{F}$

We will now attempt to simplify that expression using Boolean algebra, and then we will check our results with a truth table.

$A = CX\overline{F} + CN\overline{F} + CNX\overline{F}$ (original expression)

$A = C\overline{F}(X + N + NX)$ (rule 15)

$A = C\overline{F}(X + N(1 + X))$ (rules 15 and 18)

$A = C\overline{F}(X + N)$ (rule 23)

Step 5:

Figure 12 shows our circuit and also the truth table confirming that our simplification was correct.


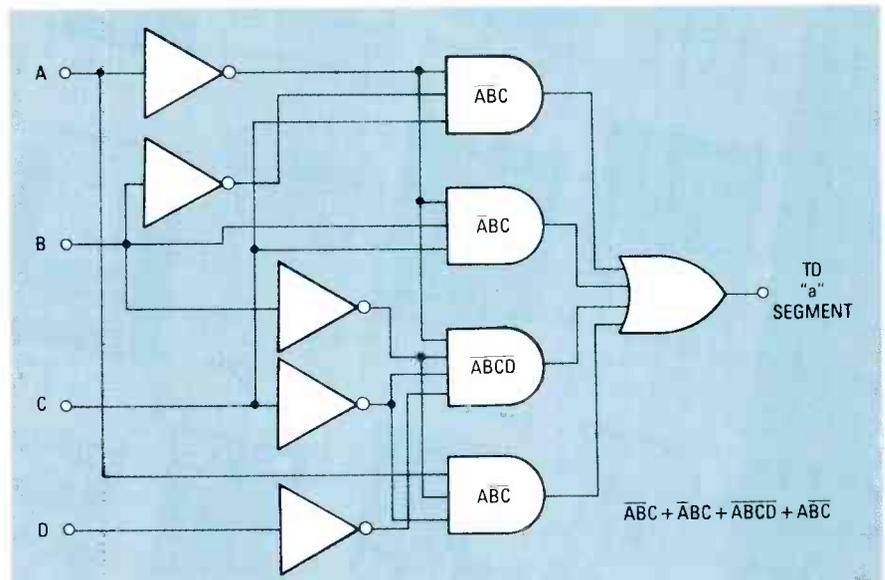


FIG. 14—HERE IS OUR FINAL CIRCUIT. It will decode the BCD information for the “a” segment.


SELECT 5 BOOKS

for only \$3⁹⁵

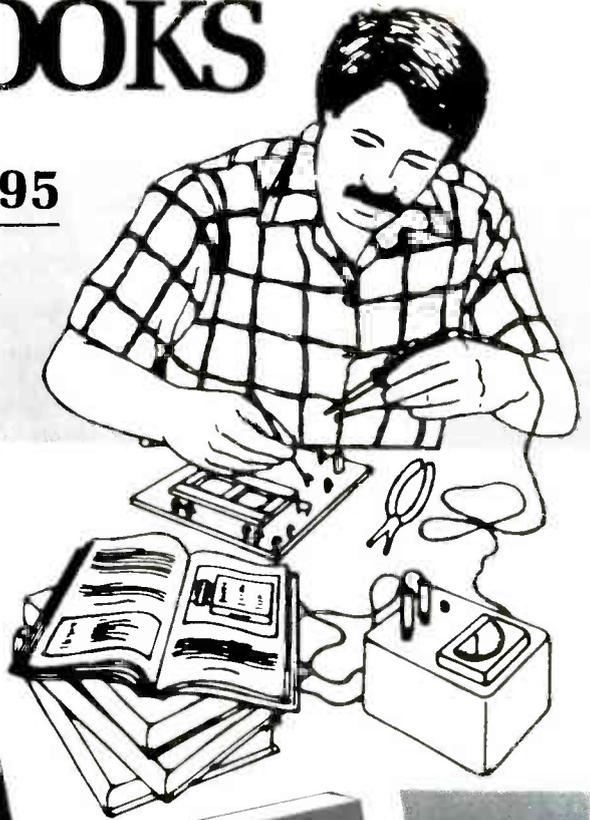(values to \$132.70)
and get a Free Gift!



2912 \$23.95

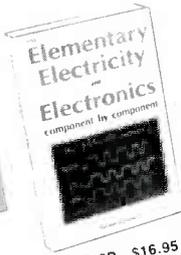


2753P \$16.95



2905 \$19.95



2831 \$22.95

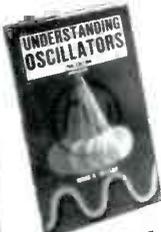


2715 \$16.95




1925P \$16.95



2724 \$24.95

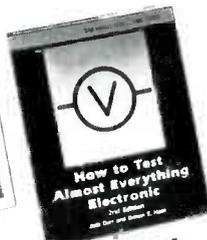

2925 \$15.95

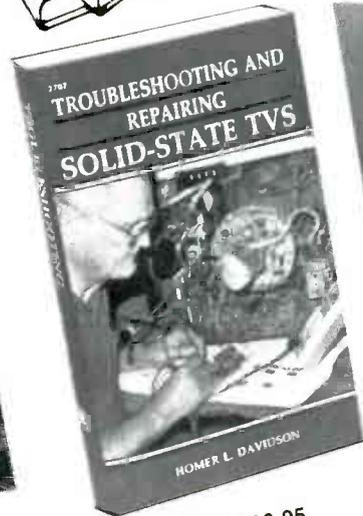

2707 \$26.95
Counts as 2




1367P \$17.95



2790 \$18.95



1957P \$14.95

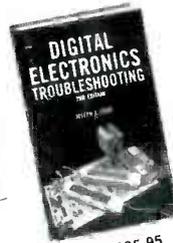


2750 \$25.95



2839P \$7.95



1977 \$26.95
Counts as 2

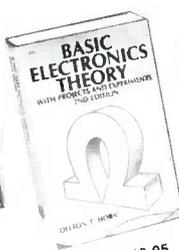

1775P \$18.95



2887 \$16.95



1777P \$18.95




2731 \$21.95




1199P \$18.95



1341P \$14.95

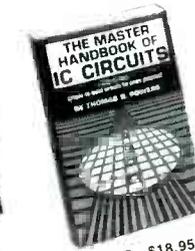

1370P \$18.95

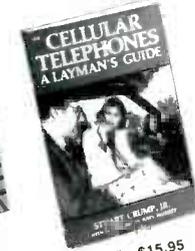

1965 \$15.95



728P \$11.95



1599P \$17.95

Compare this offer with any other book club for Price • Quality • Benefits • Selection!


An Absolute No-Risk Guarantee



2861 \$14.95



2613 \$23.95

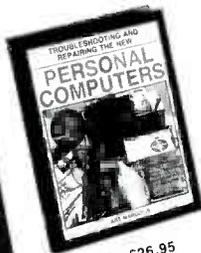


2809 \$26.95
Counts as 2



2883 \$25.95



1897P \$13.95

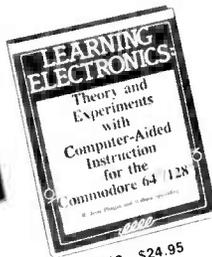

2882 \$24.95



1532P \$14.95



2832 \$23.95




2733 \$14.95



1536P \$8.95



1793P \$9.95

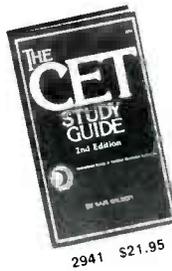


2941 \$21.95



2617 \$17.95



1604P \$16.95

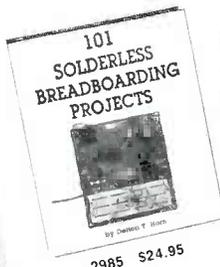

2985 \$24.95



2705P \$14.95

FREE when you join!

Here's 15 Best Electronic Projects From Delton T. Horn

Projects you can build—some unique, some old favorites—from the author's vast treasury of electronics know-how. (a \$7.95 value!)

Delton T. Horn's
All-Time Favorite
Electronic Projects



Membership Benefits • Big Savings. In addition to this introductory offer, you keep saving substantially with members' prices of up to 50% off the publishers' price. • **Bonus Books.** Starting immediately, you will be eligible for our Bonus Book Plan, with savings of up to 80% off publishers' prices. • **Club News Bulletins.** 14 times per year you will receive the Book Club News, describing all the current selections—mains, alternates, extras—plus bonus offers and special sales, with hundreds of titles to choose from. • **Automatic Order.** If you want the Main Selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no book at all, simply indicate your choice on the reply form provided. As a member, you agree to purchase at least 3 books within the next 12 months and may resign at any time thereafter. • **Ironclad No-Risk Guarantee.** If not satisfied with your books, return them within 10 days without obligation! • **Exceptional Quality.** All books are quality publishers' editions especially selected by our Editorial Board.



ELECTRONICS BOOK CLUB

Blue Ridge Summit, PA 17294-0810

Please accept my membership in the Electronics Book Club® and send the 5 volumes listed below, plus my FREE copy of Delton T. Horn's All-Time Favorite Electronics Projects (3105P), billing me \$3.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership canceled. I agree to purchase at least 3 books at regular Club prices (plus shipping and handling) during the next 12 months and may resign any time thereafter.

Name _____
 Address _____
 City _____
 State/Zip _____ Phone _____
 Signature _____

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club®. Signature of parent or guardian required for all new members under 18 years of age. RE-988

7-segment decoder

By now you should be able to see how Boolean algebra allows for an orderly design procedure. As a final example we will construct part of a 7-segment decoder. Such a device is used to translate BCD (*Binary Coded Decimal*) information into a familiar base-10 digit to be displayed on an LED or LCD 7-segment display. Figure 13-a outlines the segment designations for that type of display. For

example, to display the numeral 3 we would light segments a, b, c, d and g.

Step 1:

We want to be able to display the digits 0-9 so we'll need at least ten different combinations of inputs. That's because in binary, if we have three inputs (A,B,C), we would only have eight possible combinations ($2^3 = 8$). Therefore we need four inputs (A,B,C,D). Let A represent the most-significant digit, B the next, and

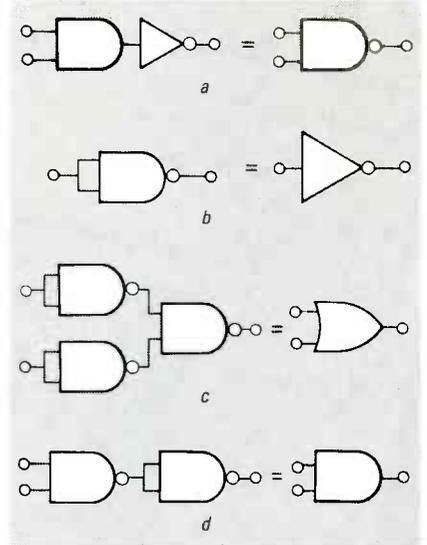


FIG. 16—THE CIRCUITS ON THE LEFT are functionally equivalent to the ones on the right.

so on. For example, if the BCD number is 0011, $D=1$, $C=1$, $B=0$, and $A=0$. That is the code for the number "3" in base-10. We want our display to show a:

- "0" if NOT D AND NOT C AND NOT B AND NOT A
- "1" if D AND NOT C AND NOT B AND NOT A
- "2" if NOT D AND C AND NOT B AND NOT A
- "3" if D AND C AND NOT B AND NOT A
- "4" if NOT D AND NOT C AND B AND NOT A
- "5" if D AND NOT C AND B AND NOT A
- "6" if NOT D AND C AND B AND NOT A
- "7" if D AND C AND B AND NOT A
- "8" if NOT D AND NOT C AND NOT B AND A
- "9" if D AND NOT C AND NOT B AND A

Step 2:

Input variables are A, B, C and D.

Step 3:


Figure 13-b shows which segments must be lit according to the number to be displayed.

Step 4:

Figure 13-c shows what the Boolean expressions for our inputs look like, and also the corresponding hi/low (1/0) input values.

Step 5:

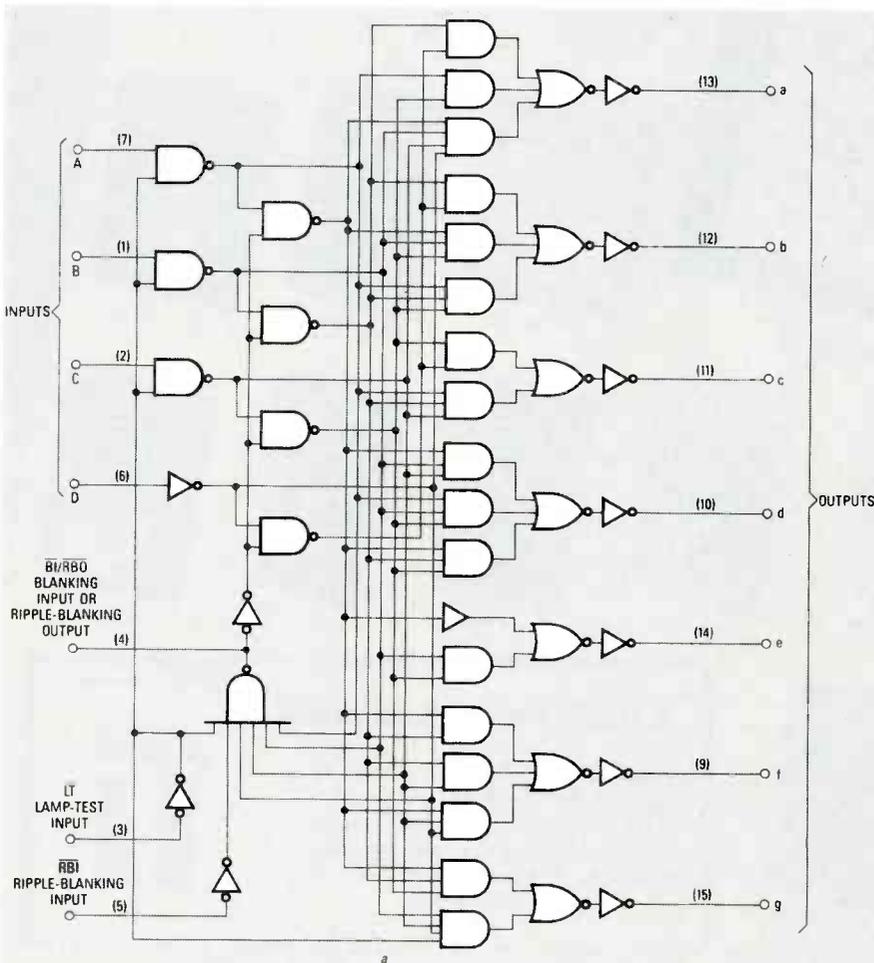We now have to do some thinking. Each segment of our display needs a circuit that can decode the BCD information so that the segment will light *only* when it is supposed to. Let's work on the "a" segment. Figure 13-b shows that segment "a" is supposed to light when displaying 0, 2, 3, 5, 7, 8, and 9. From the information in Fig.



DECIMAL OR FUNCTION	INPUTS				OUTPUTS						
	D	C	B	A	a	b	c	d	e	f	g
0	L	L	L	L	ON	ON	ON	ON	ON	ON	OFF
1	L	L	L	H	OFF	ON	ON	OFF	OFF	OFF	OFF
2	L	L	H	L	ON	ON	OFF	ON	ON	OFF	ON
3	L	L	H	H	ON	ON	ON	ON	OFF	OFF	ON
4	L	H	L	L	OFF	ON	ON	OFF	OFF	ON	ON
5	L	H	L	H	ON	OFF	ON	ON	OFF	ON	ON
6	L	H	H	L	OFF	OFF	ON	ON	ON	ON	ON
7	L	H	H	H	ON	ON	ON	OFF	OFF	OFF	OFF
8	H	L	L	L	ON	ON	ON	ON	ON	ON	ON
9	H	L	L	H	ON	ON	ON	OFF	OFF	ON	ON
10	H	L	H	L	OFF	OFF	OFF	ON	ON	OFF	ON
11	H	L	H	H	OFF	OFF	ON	ON	OFF	OFF	ON
12	H	H	L	L	OFF	ON	OFF	OFF	OFF	ON	ON
13	H	H	L	H	ON	OFF	OFF	ON	OFF	ON	ON
14	H	H	H	L	OFF	OFF	OFF	ON	ON	ON	ON
15	H	H	H	H	OFF	OFF	OFF	OFF	OFF	OFF	OFF

FIG. 15—THIS IS A COMPLETE 7-SEGMENT decoder. The device is made by Texas Instruments.

13-c we can come up with the following expression:

$$a = \overline{ABCD} + \overline{ABCD}$$

Using the rules we have learned we will simplify that expression.

$$a = (\overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD}) + (\overline{ABCD} + \overline{ABCD} + \overline{ABCD} + \overline{ABCD}) \text{ (rule 12)}$$

We will work it out in two halves:

$$= \overline{ABC(D + \overline{D})} + \overline{ABD(C + \overline{C})} \text{ (rule 15)}$$

$$= \overline{ABC} + \overline{ABD} \text{ (rule 25)}$$

Now the second half:

$$\overline{ABCD} + \overline{ABCD} + \overline{ABCD} = \overline{ABCD} + \overline{ABC(D + \overline{D})} = \overline{ABCD} + \overline{ABC}$$

Now we recombine the two halves to form our final expression:

$$\overline{ABC} + \overline{ABD} + \overline{ABCD} + \overline{ABC}$$


Figure 14 shows our final circuit. That circuitry will turn on the "a" segment whenever a BCD input requires it. By now, you should be able to design the circuitry to decode BCD for all the other segments.

Figure 15 shows a complete BCD-to-7-segment decoder, Texas Instruments' 74LS47. Right away you should notice that the circuitry for the "a" segment is different from what we came up with. One of the reasons for that is because ours only decoded digits 0-9. The one made by Texas Instruments will display six additional characters that we made no provisions for. However, the techniques that were used in designing Texas Instruments' decoder are similar to ours. Texas Instruments also added some extra features to their decoder, such as a means to test of all of the segments of the display simultaneously.

So far we haven't said anything about reducing the number of components in your circuit design. However, by properly applying the rules of Boolean algebra, many unnecessary components can be eliminated. We can, if necessary, change an expression so that we can use components that we have on hand. Also, most logic components contain several of the same gates in a single package, so you should make full use of all gates available whenever possible. For example, notice the substitutions you can make shown in Fig. 16. Those substitutions are quite often very useful, should you have any unused gates in your circuit.

R-E

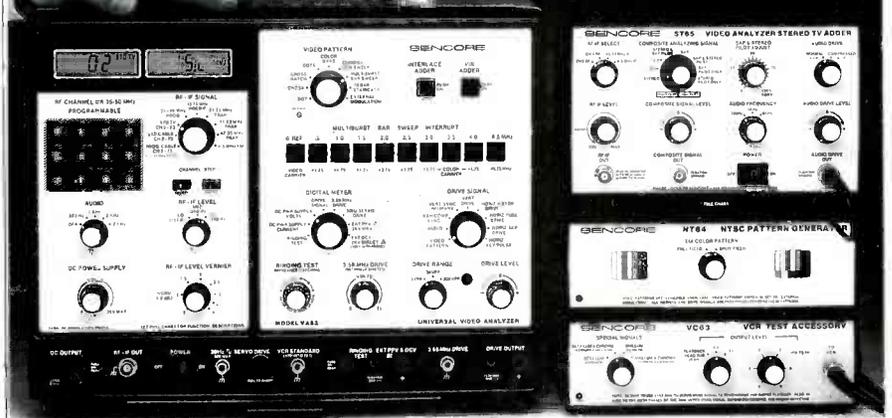Ten Things You Can Do With The VA62 Universal Video Analyzing System — That You Can't Do With The Others.



\$3,495 Patented

1. Quickly locate defective circuits by injecting signals without disconnecting components.
2. Replace video heads with confidence; a simple good/bad head test removes all doubt.
3. Align IF traps simply by just the pattern on the CRT — have the picture "looking like it did when they bought it."
4. Quickly align VCRs with special video patterns, or NTSC color bars. Meets all manufacturers' warranty requirements.
5. Performance test and troubleshoot any MTS stereo TV or VCR system, so you can cash in on new technology.
6. Confidently test deflection yokes, IHVTs, and flyback transformers, in-or out-of-circuit, before you replace them.
7. Add on phase-locked accessories into your video analyzing system to increase service potential as technology changes.
8. Performance test and troubleshoot digital/analog RGB video monitors, so you can test all of today's video systems.
9. Conquer tricky servo circuits in VCRs by injecting a reference 30 Hz servo pulse.
10. Cut your video servicing time in half . . . or your money back.

Discover what the Universal Video Analyzing System can do for you! Call Today 1-800-843-3338.

In Canada Call 1-800-851-8866.

100% American Made

SENCORE

3200 Sencore Drive, Sioux Falls, SD 57107 605-339-0100 In SD Only

CIRCLE 190 ON FREE INFORMATION CARD

HARDWARE HACKER

Electronic references
16-bit converter chips
Synchronous inverters
A/D conversion secrets
Apple computing books

A/D and D/A conversion

DON LANCASTER

CONGRATULATIONS TO RICK STANLEY of Bloomsburg, Pennsylvania for his winning of our grand prize tinaja quest in the pneumatic-valve-hacker applications contest. Rick's Air-Dale automatic dog-watering mechanism won paws down, while his Air-O-Smith guitar-playing machine was in a special class by itself.

As per usual, this is your column and you can get both tech help and off-the-wall networking by calling up the Guru himself per the "Need Help?" box. The best calling times are weekdays, 8-5, mountain-standard time.

Also as per usual, we've again gathered all of those names and numbers together for you into one single table. That's where you go for further tech info on any and all of the items mentioned.

One correction. The real phone number is (812) 339-7305 to reach Speleonics. You might call Frank Reid there on most any weekday evening. Many thanks to the Indiana University Chem Department Machine Shop (the wrong number previously listed) for forwarding the zillions of calls they got.

A bunch of positively ridiculous breakthroughs in the hacker A/D converter pricing, availability, and performance have happened in the last few weeks. The rule seems to be this: If the ink on your A/D data sheet is not still wet, then you are dealing with a very overpriced and obsolete part.

The best place to start on all this is with some....

A/D conversion fundamentals

An A/D Converter (ADC) is most

any electronic device for changing varying or analog inputs into digital pulses or numbers. The two most important specifications of an ADC are its resolution and its conversion speed.

The resolution will determine the best possible output accuracy and is usually expressed in bits. An 8-bit ADC can resolve up to one part in 256. A 10-bit ADC can resolve one part in 1024. 12-, 14-, and 16-bit ADC's can resolve 4096, 16384, and 65514 separate analog levels.

But note that a 16-bit ADC will only give you a 16-bit result for a full-scale input, and then only if the input signal has not been corrupted by noise or any kind of frequency limitations.

For instance, a 16-bit ADC with a four-volt reference will give sixteen bits of resolution for a four-volt input, twelve bits of resolution for a one-volt input, only eight bits of resolution for a quarter-volt input, and so on. The minimum input signal that can be converted is often set by the quantization noise of the A/D process itself.

The conversion speed is simply how many conversions per second the ADC is capable of. Examples include instrument circuits that

can very accurately handle only a few to a few hundred conversions per second, telephone chips that work in the three- to six-kHz range, CD audio converters that run near 40 kHz, video A/D circuits that operate at 15-25 MHz, and the pricey radar A/D converters that extend beyond 200 MHz.

There are a number of different ways of doing an A/D conversion. The fastest is called a brute-force or flash-converter type, in which a pile of comparators is put to use, having one for each input level. A variation on flash converters uses the new feedforward conversion process, where one-half of the bits are flash converted, and the remainder error is calculated. The remaining half of the bits are then flash converted and combined with the previous conversion. Feedforward converters run at one-half or less of flash-converter speeds, but will use far fewer comparators to do the job.


Most video converters are either the flash or the feedforward type. Radar converters of necessity must use flash conversion. They can be insanely expensive.

One of the very common older conversion methods is known as successive approximation. In that, one-half of the reference is subtracted from the input so long as a positive result remains. Then one-quarter of the reference is subtracted, which is followed by one-eighth, one-sixteenth, and so on down the bits. Those successive-approximation converters are fairly simple and fairly cheap. Uses are typically in the medium-speed and medium-resolution areas.

NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:
Don Lancaster
Synergetics
Box 809
Thatcher, AZ 85552
(602) 428-4073.

DO IT BY THE BOOK!

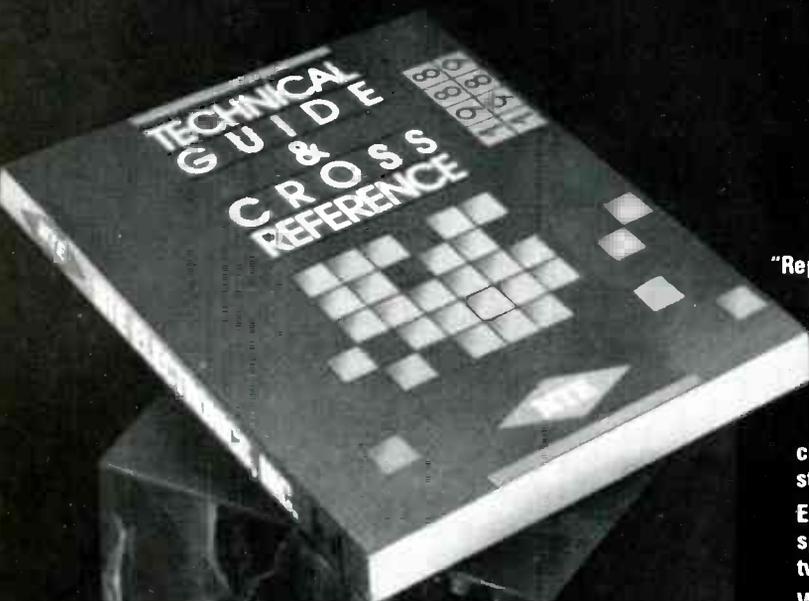

"Replacitivity" is the science of getting things up and running again. And nothing helps accomplish it faster, easier and with more confidence than the new 1988-1989 NTE Technical Guide and Cross Reference — now the standard directory for technicians everywhere! It lists more than 230,000 original devices cross-referenced to 3,400 top of the line NTE universal replacement parts. Semi-conductors, flameproof resistors, capacitors, wire ties, and static control products.

Each is quality tested to assure it meets or exceeds OEM specifications. And all NTE parts are backed by an exclusive two-year warranty.

Whether you order 1 or 100 NTE parts you'll discover they are readily available, limiting downtime to a minimum.

For your copy of the 1988-89 NTE Technical Guide contact your local NTE distributor, or simply fill in the coupon below and send it to us today with a check or money order for \$3.25 each.



NTE ELECTRONICS, INC.

A WORLDWIDE REPUTATION FOR QUALITY, SERVICE AND VALUE

For the name of your nearest NTE distributor, call NTE toll free:
Outside NJ 1-800-631-1258 • Inside NJ 1-800-624-2624

Please rush me _____ copies of the 1988-89 NTE Technical Guide and Cross Reference manual at \$3.25 each. I have enclosed my check or money order for a total of \$ _____

Name _____

Company _____

Address _____

City _____

State _____ Zip _____

Mail to: NTE, 44 Farrand Street, Bloomfield, NJ 07003

CIRCLE 71 ON FREE INFORMATION CARD

Telephone A/D converters are sometimes also called comparators. They do a non-linear conversion where the small signal levels are sliced finer than larger ones. That way, you can digitally represent a 12-bit range with only an 8-bit non-linear output.

Those instrument A/D converters normally run much slower than the others while providing a considerably higher accuracy. The classic conversion schemes here include the dual-slope and multiple-slope conversions, where the input will linearly charge up an integrating capacitor and a precision reference then discharges it. By measurement of the discharge time, you end up with a number equal to the input analog voltage or current.

One very important feature of most instrument converters lies in their ability to reject power-line frequency noise or hum. That is done by converting exactly at the power-line rate or a submultiple.

Other A/D conversion schemes do include the voltage-to-frequen-

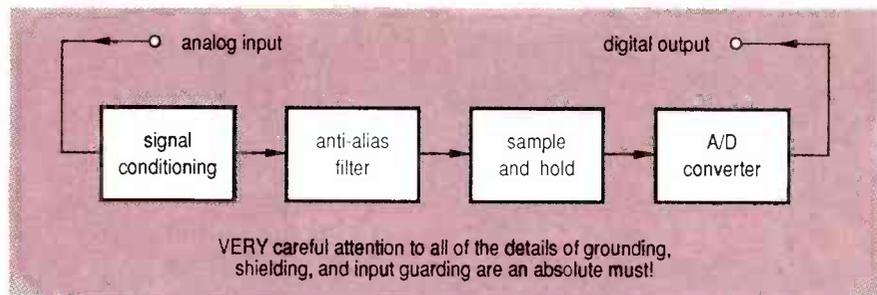


FIG. 1—AN ANALOG-TO-DIGITAL conversion system normally will need all of the areas shown here. Often, the A/D converter chip itself will be the least of your worries.

cy converters and charge balancers. In a charge balancer, the input will continually add charge to an integrating capacitor, while the output will remove the charge in discrete current-line packets. The number of packets removed is proportional to the input voltage or current.

But the latest, and certainly the most bizarre, of A/D converters are called oversampling converters that use an elaborate decimation and digital filtering process. An oversampling converter makes all of its measurements at an extremely high sampling frequency.

They're also known as delta-sigma A/D converters. They are new and they are hot.

The theory here is that the only "little thing" wrong with one-bit A/D is that its quantization noise is totally gruesome. By taking that quantization noise and spreading it out over a much wider bandwidth than the input signal and by then rejecting most of the noise with a filtering process, you can actually reduce the noise to below that of a 16-bit converter!

The Crystal Semiconductor folks are a leading developer of those exciting new low-cost oversampling converters.

A fairly good background book on A/D conversion in general is *Analog to Digital Conversion*, now available from Analog Devices for \$32. Some of the fundamentals of computer A/D interface appear in my *Micro Cookbooks*, both volumes I and II.

The rest of the story

Unfortunately, though, your A/D converter chip is only a tiny part of the hardware that you will really need to do an A/D conversion. Figure 1 shows you some of the rude surprises that you are

going to have to work around to get a complete analog-to-digital conversion system.

You first need some input-signal conditioning. That will accept your input signal and amplify it enough so that its maximum value equals the converter's reference voltage.

Signal conditioning can also do such things as subtracting out an offset value, filtering, rejection of noise, temperature compensation, or calibration.

The latest of A/D converter chips allow you to use lower or floating-point reference voltages or else can have enough bits that you might work at reduced resolution and are able to end up with useful results. Nonetheless, signal conditioning is always a very sticky design area.

After all of your initial signal conditioning, you must provide an anti-aliasing filter, and a darn good one. There is a fundamental rule that says that any A/D converter must never be fed any signal that is greater than one-half of its sampling frequency.

Figure 2 shows you what an alias is and how it is created. Say you were on a long commuter airline flight and you are very sleepy. You briefly open your eyes and see a green service truck on the runway. You fall asleep, and wake up an hour later at a new airport. This time the green service truck is ten feet further along. You repeat the process a third time, and now, the green truck is yet another ten feet further away. You then wrongly conclude that the green truck is traveling at ten feet per hour.

In exactly the same manner, an alias gets created if you sample any frequency near the sample rate of an A/D converter. For instance, if you employ a 40,000-Hz sample rate, and then sample a 40,100-Hz

NEW FROM DON LANCASTER

HANDS-ON BOOKS

Ask the Guru Reprints	24.50
CMOS Cookbook	16.50
TTL Cookbook	16.50
Active Filter Cookbook	15.50
Micro Cookbook vol I or II	16.50
Enhancing your Apple v. I or II	15.50
Applewriter Cookbook	19.50
Apple Assembly Cookbook	21.50
Incredible Secret Money Machine	9.50
PostScript Cookbook (Adobe)	16.50
PostScript Ref. Man. (Adobe)	22.50
PostScript Prog. Man (Adobe)	22.50

UNLOCKED SOFTWARE

Absolute Reset IIe & IIc	19.50
Applewriter/Laserwriter Utilities	49.50
PostScript Show & Tell (IIe/Mac/PC)	39.50
Intro to Postscript VHS Video	39.50
PostScript Perspective Draw	39.50
PostScript Printed Circuits	39.50
PostScript Technical Illustrations	39.50
Postscript BBS stuff	19.50
Apple Ram Card Disassembly Script	24.50
Enhance I or II Companion Disk	19.50
Applewriter CB or Assy CB Disk	24.50

FREE VOICE HELPLINE

VISA/MC

SYNERGETICS

Box 809-RE
Thatcher, AZ 85552
(602) 428-4073

CIRCLE 83 ON FREE INFORMATION CARD

NAMES AND NUMBERS

Analog Devices
One Technology Way
Norwood, MA 02062
(617) 329-4700

Burr-Brown
P.O. Box 11400
Tucson, AZ 85734
(602) 746-1111

C & H Sales
2176 East Colorado Blvd.
Pasadena, CA 91107
(800) 325-9465

Crystal Semiconductor
4210 South Industrial Drive
Austin, TX 78744
(512) 445-7222

Exar Corp./Literature
2222 Qume Drive
San Jose, CA 95161
(408) 732-7970

Harris Publishing Co.
2057-2 Aurora Rd.
Twinsburg, OH 44087
(216) 425-9000

Interlink Electronics
535 E. Montecito
Santa Barbara, CA 93103
(805) 965-5155

ISL Corp.
4354 Olive St.
St. Louis, MO 63108
(314) 535-5760

Linear Technology
1630 McCarthy Blvd.
Milpitas, CA 95035
(408) 432-1900

Motorola
PO Box 20912
Phoenix, AZ 85036
(602) 244-6900

National Semiconductor
2900 Semiconductor Dr.
Santa Clara, CA 95052
(408) 721-5000

Plessey Semiconductors
9 Parker
Irvine, CA 92719
(714) 472-0303

Samsung Semiconductor
3725 North First St.
San Jose, CA 95134
(408) 434-5400

Solar Age
Church Hill
Harrisville, NH 03450
(603) 924-9641

Solar and Wind Technology
Fairview Park
Elmsford, NY 01523
(914) 592-7700

Solar Energy
Fairview Park
Elmsford, NY 01523
(914) 592-7700

Solar Engineering
Box 3600
Troy, MI 48007
(313) 362-3700

Standard Microsystems
35 Marcus Blvd.
Hauppauge, NY 11788
(516) 273-3100

Speleonics
PO Box 5283
Bloomington, IN 47407
(812) 339-7305

Texas Instruments
Box 655303
Dallas, TX 75265
(214) 995-3821

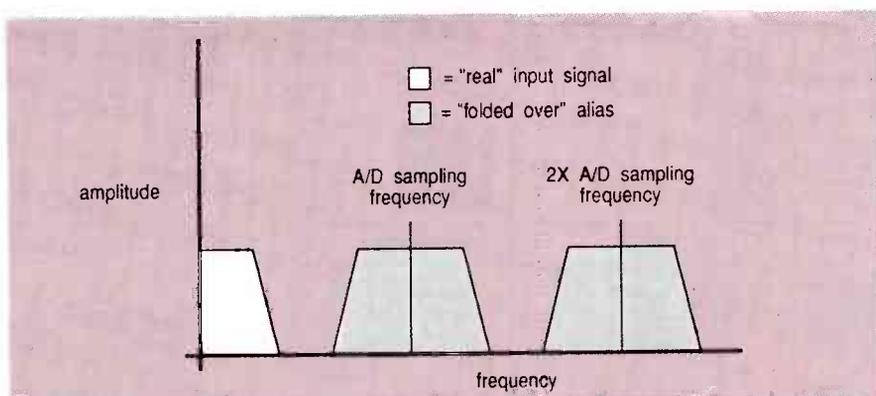


FIG. 2—A ANTI-ALIASING filter absolutely must be used with any A/D converter so as to sharply reject any and all frequencies above one-half of the sampling frequency. Should any higher frequencies remain present, they will "fold over" and form aliases that end up looking just like "real" input signals.

signal, you will apparently get a 100-Hz signal digitized that you simply cannot tell from a "real" 100-Hz signal. That's an alias, and you absolutely must not ever let that happen.

One big advantage of the new oversampling converters is that the anti-aliasing filter is both simpler and cheaper to build.

After filtering, you normally must do a sample and hold, as shown in Fig. 3. If your input signal is allowed to change during the measurement interval, you can get

wild inaccuracies since you are now measuring a different amplitude at the end than you were at the beginning.

A sample and hold is normally done with an electronic switch that charges up a capacitor during the sampling, or the aperture time. The charge is kept during the time a conversion gets completed.

At high resolutions, the penalty for leaving off a sample and hold is severe. Figure 4 shows you the differences in the full accuracy input frequency response you will get

with or without using a sample-and-hold circuit.

Fortunately, most of the newer chips do have their own internal sample-and-hold circuits on board. But you have to be absolutely certain that you understand how the sampling process works.

Your actual A/D converter will follow the input conditioning, the anti-aliasing, and the sample and hold. That final circuit area is often the least of your problems.

Along the bottom, we also have shown you some guarding and shielding. It is trivially easy to let digital noise and even power-line hum totally trash out any accuracy from your A/D system. Ferins-tance, a typical hacker digital circuit will be very lucky to hold the digital-logic ground noise down below 300,000 microvolts.

On a typical 16-bit A/D converter circuit, any input noise greater than 15 microvolts or so might bobble the bits and give you all sorts of nasty jitter and errors.

If so much as a hint of a whiff of a few of the fumes of your ground noise ends up referenced to the input of your high-resolution A/D, then all is lost.

HITACHI SCOPES AT DISCOUNT PRICES!

\$100 Price Reduction



V-212
NOW \$379
was \$475
List \$560

Plus 'Free' 9600 Function Generator

All Hitachi scopes include two 50 MHz probes and have a 3 year warranty on parts and labor



40MHz **V-425** List 995
CRT readout **\$835**




60MHz **V-660** List 1,195
Delayed sweep **\$949**



100MHz **V-1060** List 1,595
Delayed sweep **\$1,285**

	List	Our Price	Save
V-223 20MHz D.T. 2mV Sens. Delayed Sweep	770	695	75
V-422 40MHz D.T. 1mV Sens. DC offset	875	695	180
V-423 40MHz D.T. 1mV Sens. Delayed Sweep DC offset	955	795	160
V-1065 100MHz D.T. 2mV Sens. Delayed Sweep	1,895	1,575	320
V-1100 100MHz Q.T. 1mV Sens. Cursor meas. DVM counter	2,295	1,995	300
V-1150 150MHz Q.T. 1mV Sens. Cursor meas. DVM counter	3,100	2,565	535

ELENCO PRODUCTS AT DISCOUNT PRICES!

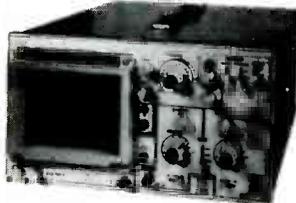

\$349
MO-1251

- 6" CRT
- Built in component tester
- TV Sync
- Much More

20MHz Dual Trace Oscilloscope

Scope Probes

P-1 65MHz, 1x, 10x **\$19.95**
P-2 100MHz, 1x, 10x **\$23.95**
with 5 accessories
10 Meg ohms input impedance
Fits all scopes with
BNC connector
TL-3 BNC to Minigrabber **\$3.49**



\$498
MO-1252

- High Luminance 6" CRT
- 1mV Sensitivity
- 6KV Acceleration Voltage
- 10ns Rise Time
- X-Y Operation • Z Axis
- Delayed Triggering Sweep
- Much More

35MHz Dual Trace Oscilloscope

Top quality scopes at a very reasonable price. Contains all desired features. Two 1x, 10x probes, diagrams and manual.



True RMS 4 1/2 Digit Multimeter
\$135 M-7000

.05% DC Accuracy
1% Resistance with Freq. Counter & Deluxe Case

10MHz Oscilloscope
S-3000
\$239

10MHz DC or AC Triggered Sweep
Calibrated Vert & Hor
Reads Volts & Freq

Decade Blox
9610 or 9620
\$14.95

#9610 Resistor Blox
47 ohm to 1M & 100K pot
#9620 Capacitor Blox
47pf to 10MFD

Low Cost Multimeter
M-1600
\$25

3 1/2 Digit LCD
1% DC Accuracy
10A Scale
Auto zero/polarity

Digital LCR Meter
LC-1800
\$138

Measures
Coils (1uH-200H)
Caps (.1pf-200uf)
Resistors
(.1 ohm-20M ohms)

Breadboard
9436 Shown

9430 1,100 pins \$15
9434 2,170 pins \$25
9436 2,860 pins \$35

Multimeter with Capacitance and Transistor Tester
\$55 CM-1500A

Reads Volts, Ohms
Current, Capacitors,
Transistors and
Diodes w/case

Digital Capacitance Meter
CM-1550
\$58.95

9 Ranges
.1pf-20,000ufd
.5% basic accuracy
Zero control
w/case

Analog Multimeter
M-1100
\$19.95

19 ranges
High Accuracy
10A reading
Mirrored scale
Kit 17.50

3 1/2 Digit Meter Auto and Manual Ranging
28 Functions Fully Protected

M-1180 .7% Ac \$36.95
M-1181 .1% Ac \$42.95
M-1182 .25% Ac \$39.95

Function Generator Blox
#9600
\$24.95

Provides sine, tri, squ wave
From 1Hz to 1MHz
AM or FM capability

Solderless Breadblox
#9550
\$7.50

550 tie pts
including 2 power
bus lines

IC Test Clips
16 pin \$5.95
20 pin \$8.25
24 pin \$10.75
28 pin \$11.75
40 pin \$18.50

All are gold plated to
assure trouble free contact

Temperature Probe
M-110CF
\$29.95

Semiconductor type
Range
-58F-302F
Fits most digital multimeters

50MHz Logic Probe
LP-700
\$23

Logic Pulsar LP-600 \$23

Digital 3 Amp Power Supply



XP-750
\$175

0-40V @ 1.5A
0-2V @ 3A

XP-650 with Analog Meters \$129.50

Regulated P.S. Breadboard



\$99.95 XK-400

- Fully regulated
- Short circuit protection
- 3550 test points
- 3 power supplies

• 5V @ 2A, 12V @ .3A, -12V @ .3A

GF-8016 Function Generator with Freq. Counter
\$239



- Sine, Square, Triangle
- Pulse, Ramp, .2 to 2MHz
- Frequency .1 thru 10MHz

GF-8015 without Freq. Meter \$179

Digital Triple Power Supply



XP-765
\$239

0-20V @ 1A
0-20V @ 1A
5V @ 5A

Fully Regulated, Short Circuit Protected with 2 Limit Cont. 3 Separate Supplies

XP-660 with Analog Meters \$169.50

Quad Power Supply



XP-580
\$59.95

Fully regulated and short circuit protected

XP-575 without meters \$44.95

Four-Function Frequency Counters



F-1000 \$259
1.2GH

F-100 \$179
120MH

Frequency, Period, Totalize, Self Check with High-Stabilized Crystal Oven Oscillator, 8 Digit LED Display

WE WILL NOT BE UNDERSOLD!



C & S SALES INC.
1245 Rosewood, Deerfield, IL 60015
Add 5% for Postage (\$10 Max) IL Res., 7% Tax

(800) 292-7711 15 Day Money Back Guarantee
(312) 541-0710 2 Year Warranty

ASK FOR FREE CATALOG

MASTER THE NEW ELECTRONICS WITH MCGRAW-HILL'S

Contemporary Electronics Series

The fast, easy and low cost way to meet the challenges of today's electronic innovations. A unique learning series that's as innovative as the circuitry it explains, as fascinating as the experiments you build and explore.


From digital logic to the latest 32-bit microprocessor, the McGraw-Hill Contemporary Electronics Series puts you into the electronic picture one easy step at a time. Fifteen unique Concept Modules, sent to you one every 4-6 weeks, give you a handle on subjects like optoelectronics, robotics, integrated circuits, lasers, fiber optics and more.

Each Concept Module goes right to the heart of the matter. You waste no time on extraneous material or outdated history. It's a fast, efficient, and lively learning experience...a non-traditional approach to the most modern of subject matter.


Unique Interactive Instruction

With each module, you receive a McGraw-Hill Action Audio Cassette. Each tape is a dynamic discussion that drives home the key facts about the subject. Your learning

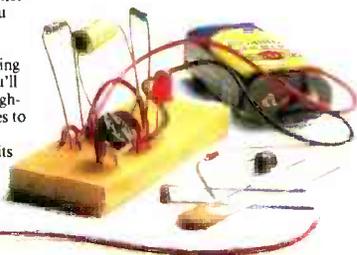With your first module, you get this solderless breadboarding system. You'll use it throughout the series to build electronic circuits and bring concepts to life.



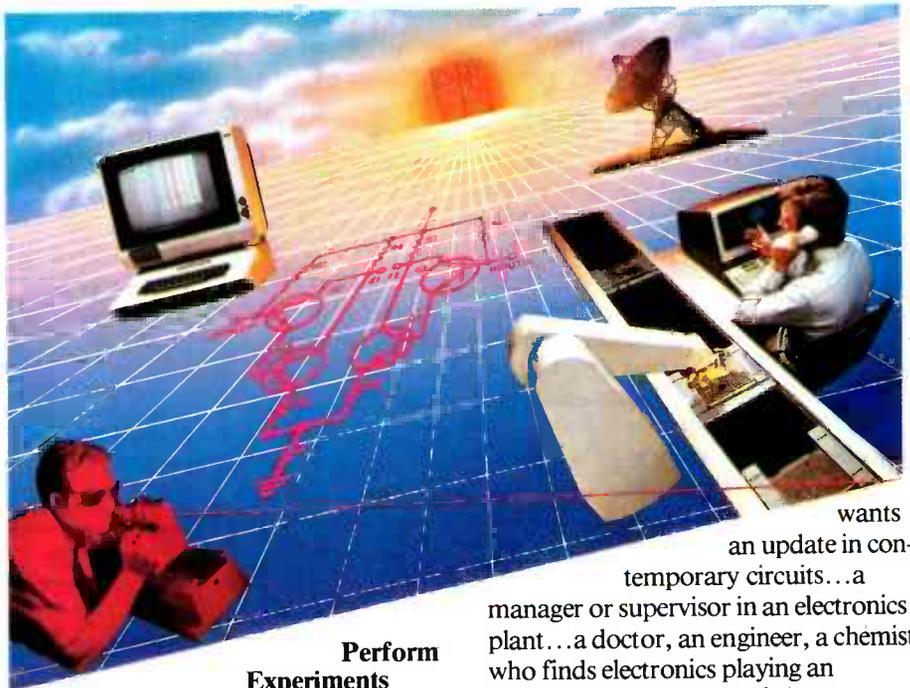experience is reinforced through interaction with vividly illustrated text, audio cassettes, and actual electronic experiments. Indexed binders preserve backup material, notes, and tapes for convenient referral.



Perform Experiments in Contemporary Electronics

Throughout your series, laboratory experiments reinforce every significant point. This essential experience...dynamic, hands-on demonstrations of theory in practice... will help you master principles that apply all the way up to tomorrow's latest VLSI (Very Large Scale Integrated) circuitry.

In your very first module, you'll use integrated circuits to build a digital oscillator, verifying its operation with a light emitting diode (LED). You'll learn to identify passive and active components, understand concepts common to all electronic circuits.


For Anyone Interested in Electronics

The Contemporary Electronics Series is designed for anyone from hobbyist to professional. It's for you if you're looking for new fields of interest...if you're a teacher who

wants an update in contemporary circuits...a manager or supervisor in an electronics plant...a doctor, an engineer, a chemist who finds electronics playing an increasingly important role in your work. It's even for electronics engineers or technicians who feel their training needs freshening up. It's the quickest, most convenient, probably least expensive way to do it. And the only one that gives you hands-on experience.

15-Day No-Risk Trial

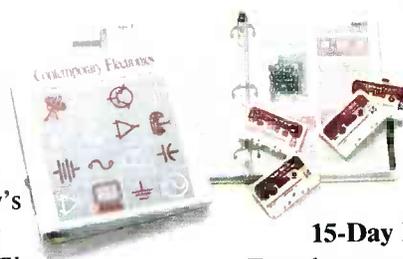To order your first module without risk, send the card today. Examine it for 15 days under the terms of the order form and see how the Contemporary Electronics Series gets you into today's electronics. If card has been used, write us for ordering information.



McGraw-Hill
Continuing Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016

number of bits	max frequency WITH a S/H	max frequency WITHOUT a S/H	speed penalty WITHOUT a S/H
2	20,000	3120	13
4	20,000	795	50
6	20,000	199	201
8	20,000	50	804
10	20,000	12	3216
12	20,000	3.1	12,868
14	20,000	0.8	57,472
16	20,000	0.2	205,887

FIG. 4—A RIDICULOUSLY SEVERE speed penalty must be paid if you omit the sample and hold from your A/D converter. The examples here are for a 40-kHz conversion rate.

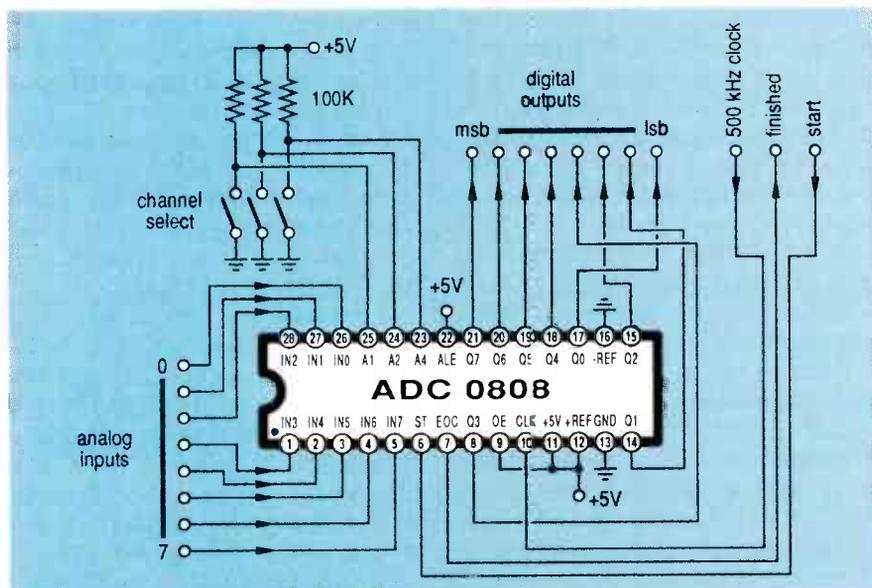


FIG. 5—THIS OLDER 8-BIT, 8-CHANNEL A/D converter is very easy to interface to any parallel input port on most any personal computer

As an interesting entry in video-rate A/D conversions, do check out Samsung. They now have a dozen different combined 8-bit A/D and 10-bit D/A chips. Their KVS3110N-7 should be a good starting point.

For the contest this month, just dream up an unusual use for A/D or D/A converters. A paper design is just fine. There will be the usual Incredible Secret Money Machine prizes for the best twenty entries, and a great all-expense-paid (FOB Thatcher, AZ) tinaja quest for the best entry of all.

Finding names and numbers

How do you find out where to buy a Maxim integrated circuit? Or how do you get a National Semiconductor data sheet? Who makes solid-state gyroscopes? Electronic inclinometers?

Finding sane answers to those and other similar questions is what hardware hacking is all about.

Naturally, you start with our own Names and Numbers section, and by reading all of our great **Radio-Electronics** ads. And, yes, a master names and numbers directory will soon be available. Call or write for full details.

But where to from there?


Let us start out with the only electronics directory that I actually pay cash for out of my own pocket. That is the *Electronic Industry Telephone Directory*, and costs \$40 per year from Harris Publishing.

An excellent list of many local distributors for electronic goodies appears monthly in the *E.E. Times* magazine. But for some strange reason, that otherwise great list seems to be strictly limited to their current advertisers.

CRYSTEK

The pulse of dependable communications

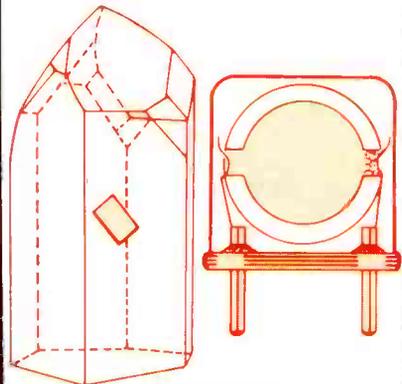Reliability & Quality
From Start To Finished Product



QUARTZ CRYSTALS/OSCILLATORS

FOR ELECTRONIC — INDUSTRIAL

- Micro-Processor Control
- Computers/Modems
- Test/Measurement
- Medical

COMMUNICATIONS—REPLACEMENT

- Mobile/2-way/Channel Elements
- Pagers
- Marine
- Aircraft
- Telemetry
- Monitors/Scanners

AMATEURS

- CB
- Hobbyist
- Experimenter

- COST EFFECTIVE
- MODERATE PRICING
- FAST DELIVERY



NEW

The Pulse of Dependable Communications

Crystek Crystals offers their new 16 page FREE catalog of crystals and oscillators. Offering state-of-the-art crystal components manufactured by the latest automated technology. Custom designed or "off the shelf," Crystek meets the need, worldwide. Write or call today!

CRYSTEK CRYSTALS

2351/2371 Crystal Dr. • Ft. Myers, FL 33907
P.O. Box 06135 • Ft. Myers, FL 33906-6135

TOLL FREE 1-800-237-3061
(813) 936-2109 - TWX 510-951-7448

CIRCLE 184 ON FREE INFORMATION CARD

NEW SUPER LONG PLAY TAPE RECORDERS

12 Hour Model — \$105.00*

USES D-120 TAPE

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 6 continuous hours of quality recording & playback on each side of cassette for a total of 12 hours.

Built-in features include • Voice level control. • Digital counter, etc. TDK DC 120 Cassette Furnished.



PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. \$24.50*



VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. \$24.95*



*Add for ship & hdg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA, M/C, COD's OK. Money Back Guarantee. Qty. disc. avail., Dealer Inquiries invited, Free data. © AMC SALES INC. Dept. 9335 Lubec St., Box 928, Downey, CA 90241 Phone (213) 869-8519

CIRCLE 108 ON FREE INFORMATION CARD

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to \$30 an hour and more!

Learn at home in spare time. No previous experience needed!

No costly School. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School

This proven course is easy, fast and low cost! **GUARANTEED PASS** — You get your FCC License or money refunded. Send for **FREE** facts now. **MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

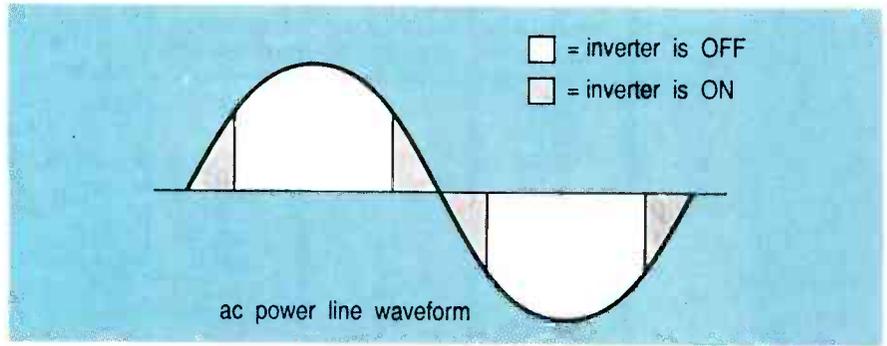


FIG. 6—A SYNCHRONOUS INVERTER can be used to feed surplus energy from a solar panel or other alternate energy source back into the power line. Here is one possible waveform.

Most of those electronics trade journals publish yearly directories that are extremely useful for pinning down names and numbers. I especially like the *Gold Book* from Electronic Design, the *Electronics Buyers Guide* from Electronics, and the *EEM Master* from the Electronic Products people.

Various "focus" tech stories in EDN are also quite handy reference sources for needed names and numbers.

You can get a list of all of the trade journals from that *Uhlricht's Periodicals Dictionary* over on the reference shelf at your local library. Also at your favorite library will be the *Thomas Registry of Manufacturers*, and possibly the *Electronic Representatives Association* (ERA) Directory.

Asking for help from an engineer or a technician working for a larger electronics company will sometimes work, as might a ham-radio operator, our technical help-line, the editor of a trade journal, or an electronic bulletin board.

Naturally, it is best to build up your library of useful names and numbers ahead of time, rather than waiting until you desperately need some hard-to-get part. Your own resource library should always be the first place to check.

As a second contest this month to test your source-finding abilities, just tell me the cheapest source of 64 pin, 70 mil shrink dip IC sockets that you know of. That component is desperately needed for an upcoming Radio-Electronics project or two.

Synchronous inverters

I've been getting a lot of calls and letters from hardware hackers who have heard somewhere that,

if you have a few solar panels or other alternate energy source up, then your local power company is required by law to buy all of your surplus power from you.

Well, in this day and age, most of the power companies are fairly enlightened and would be most happy to buy power from most any alternate energy source that is both local and reliable.

But there are several very big gotchas here.

First, a power company will sell power to you at retail and buy it back from you at their wholesale avoided cost. Avoided cost is the price of the most expensive power they are currently buying or generating. Thus, you do not simply swap energy, since one of their kilowatt hours may be worth five or more of yours.

Secondly, a very special device called a synchronous inverter is needed to meter your energy back into the power line. As Fig. 6 shows us, a waveform is carefully crafted that feeds your power back in phase with the existing AC-line waveforms.

Synchronous inverters and all of the metering that goes with them are not cheap. The bottom line is an economic one. The time value of the money used to pay for the synchronous inverter and all of its metering will often insanely exceed the total value of all the power you are able to generate.

Thus, many smaller solar-power installations are never able to reach cost breakeven, let alone show a profit. But I certainly encourage all of you dedicated hackers out there to keep on trying. The situation is certain to improve in the future.

continued on page 87

AUDIO UPDATE



LARRY KLEIN,
AUDIO EDITOR

Can You Hear the Difference?—Pt. II

LAST MONTH I PROBABLY ALIENATED some readers and invalidated my ears by maintaining that amplifiers that measure well and are operated within their power ratings almost always sound alike. Note that I'm *not* saying flatly that all amplifiers sound alike—they don't—but I do believe that there are no mysterious forces, factors, or formulas, that cause one amplifier to sound better or worse than another. The use of gold-plated linear-crystal AC line cords, special capacitors, vacuum tubes, a bandwidth extending from DC to light, plus the ear of a bat and the eye of a newt, may or may not have audible consequences—but when they do, their influence is readily measurable by conventional methods.

The "readily measurable" performance parameters I'm referring to go far beyond the FTC-mandated specifications on power, bandwidth, and distortion, that you see in every amplifier or receiver advertisement. Nobody believes that the FTC power statements come close to totally defining the comparative performance and sound of any two amplifiers. For example, the dynamic headroom and current capabilities of an amplifier, although they are ignored by the required FTC statement, can still significantly affect its sonic performance.

I'm aware that *my* beliefs about what is audible, inaudible, or measurable don't carry much weight with those who believe in the special sonic wonders produced by the designs and designers of their

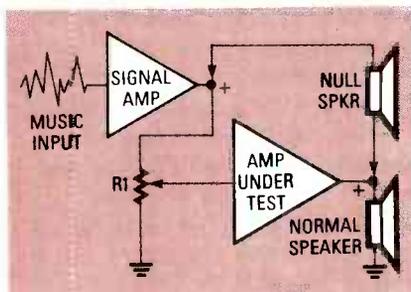


FIG. 1

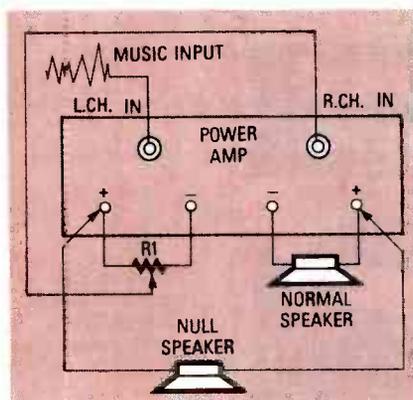


FIG. 2

chosen and usually costly amplifiers. My claim that scientifically constructed double-blind listening tests regularly fail to confirm the existence of mysterious differences is pooh-poohed by those who hear such differences every time they switch on their equipment. Is there any way out of the impasse?

Listening tests

There are two popular types of listening-comparison tests: 1—"Do you prefer A or B?" and 2—"Can you hear a difference between A and B?" Obviously, question 1 includes question 2, but they

are really quite different in several ways. Question 1 is appropriate when comparing components in a showroom and is likely to reveal as much about the taste of a listener as it will about the performance of a component. Laboratory listening tests, on the other hand, usually ask a type-2 question because it leaves out the confusing "better or worse" element—which can be addressed later if desired.

But the type-2 question has its own problems. Because of psychoacoustic masking and other reasons it is not always easy to *hear* distortion in program material even when the amplifier aberration producing it can be easily measured. (It is well-documented that impedance-matching problems and harmonic distortions in complex wide-band program material have to reach the 6-percent level before becoming perceptible. Musical energy at the frequencies of the distortion products tends to have a masking effect.) If we could convert the type-2 question from "Do you hear a difference?" to "Do you hear something—or nothing?" many of the psychoacoustic and other subjectivity problems would be avoided. David Hafler of The Hafler Company has long been concerned with such matters and has recently come up with a very clever type-3 test configuration that should help resolve many of those questions.

The Hafler differential test

Many years ago Hafler invented a sort of poor man's quadraphonic

ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR
**B.S.E.E.
DEGREE**

THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

**COOK'S INSTITUTE
OF ELECTRONICS ENGINEERING**



4251 CYPRESS DRIVE
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD



system. It consisted essentially of an additional speaker (or a pair of series-connected speakers) connected directly across the two *hot* (positive) terminals of the amplifier in use. Connecting a speaker in such a fashion feeds it a signal which contains *only* the differences (including those of amplitude and phase) between the two stereo channels. Because on many recordings, out-of-phase "hall-ambience" sound is a good part of that difference, feeding it to separate speakers located toward the rear of the listening room provides a worthwhile listening enhancement at a very low cost. For our present discussion, keep in mind that the additional "ambience" speakers are silent when there is no difference between the channels—such as would occur if a mono signal were fed simultaneously to the two channels of a perfectly balanced amplifier.

At some point it occurred to Hafler that the ability to nullify identical signals by a "hot-to-hot" speaker connection could be

useful in amplifier testing. A circuit (see Fig. 1) was devised that, in effect, *electrically* subtracts the original signal (from a signal-source amplifier) fed into an amplifier under test from the signal coming out of it. After adjustment for level differences and phase shift (using R1), any residual sound that's heard in the *null* speaker represents the difference between the input and output signals. By definition, such a difference is considered to be distortion. Because the distortion-signal level at the null speaker is always much lower than the normal program sound—even if the distortion is severe—the normal speaker has to be moved out of listening range to keep it from overwhelming the null speaker.

Figure 2 shows a practical connection of the Hafler test circuit (which he refers to as the "straight-wire differential test" or SWDT). The left channel of a stereo power amp serves as the low-impedance/power signal source and the right channel is the amplification section under test. Potentiometer R1 is used to adjust the signal level fed to the right-channel input so that the signal voltages appearing at the right and left channels' hot speaker terminals are as close as possible.

All that technical work has not been done in the cause of pure science. Hafler's new power amplifier, the XL-280, has been developed using the SWDT test technique. The new amplifier also includes trimmer adjustments on each channel to compensate for speaker impedance characteristics and thereby enhance the amp's performance on the SWDT test. SWDT testing of the Hafler—and most other amplifier brands—is facilitated by a switching/adjustment test box available from The Hafler Company. Note that amplifiers with bridged and polarity-inverting output circuits are not suitable for SWDT testing.

Final thoughts

The Hafler difference-signal test is sensitive enough so that it will easily show up any conceivably audible difference between an amplifier's input and output signals. As a matter of fact, I would guess

The Only Universal Back Tension Gauge

Tension cassettes work on less than half the VHS machines now in the field.

The Tentel® T2-H7-UM Tentelometer® is so universal, it will work on all brands and models of VHS recorders and allows the accuracy to be easily verified in the field. Tension measurements are made out in the tape path near the heads where tension is important. Tape tension can cause a number of problems difficult to correct when you're only guessing. Stop guessing, do it right!



Ask about Tentel's **NEW T.E.S.T. Cassette** for use with the Tentelometer. This **NEW T.E.S.T. Cassette** (Patent Pending) offers a fast, complete performance evaluation of holdback tension and the entire tension servo system; to determine if it is maintained in the 23 to 35 gram specification.

T2-H7-UM - \$325

T.E.S.T. Cassette/VHS - \$29

Call our toll free number or send for complete details on these and Tentel's other VCR test gauges. We make the difficult easy...to help you!

TENTEL® Corp. (800) 538-6894

1506 Dell Avenue
Campbell, CA 95008

In Calif. - (408) 379-1881

CIRCLE 196 ON FREE INFORMATION CARD

How to live with someone who's living with cancer.

When one person gets cancer, everyone in the family suffers.

Nobody knows better than we do how much help and understanding is needed. That's why our service and rehabilitation programs emphasize the whole family, not just the cancer patient.

Among our regular services we provide information and guidance to patients and families, transport patients to and from treatment, supply home care items and assist patients in their return to everyday life.

Life is what concerns us. The life of cancer patients. The lives of their families. So you can see we are even more than the research organization we are so well known to be.

No one faces cancer alone
AMERICAN CANCER SOCIETY

that the test is so sensitive that the null speaker will reproduce "distortion" that under normal stereo music playback conditions would never be heard—no matter how golden the listener's ears. I certainly do not fault the Hafler test for excessive sensitivity, but I could see it sending some engineering-type audiophiles in pursuit of ever deeper nulls—a pursuit which would have no audible benefit.

Incidentally, a variation on the null test can easily be used to test the alleged benefits of special capacitors, wires, and so forth. All that is necessary, is to install the special parts in one channel, leaving the other unaltered. If a speaker connected across the two hot terminals indicates a difference between the channels, the SWDT test can then be used to determine which channel has less distortion.

I don't really expect that this new test will end the debates among the audio critics. The problem is that you can't really argue convincingly with those who state

calmly that their ears consistently reveal things that your tests don't, despite all the science and logic you bring to bear. Or worse, that the very quality that your test reveals as distortion is really the magic ingredient that makes the equipment sound so good. One would hope that the inner realities of all audio critics would be in accord with objective reality; but when it isn't, there is no way that I know of to force them to agree. **R-E**



NEXT MONTH watch for a feature article that will show you how to build a Hafler differential test box.

**Technicians,
Get Serious
About Your
Profession**



Being a certified electronics technician lets people know that you are a professional in your field. It tells them that you are serious about your work and can perform up to CET standards.


Now you can order the "Study Guide for the Associate-Level CET Test" from the International Society of Certified Electronics Technicians. It includes material covering the most often missed questions on the Associate CET exam. 8½" x 11", paperback, 60 pages.

For More Information Contact:

IS CET, 2708 W. Berry, Fort Worth, TX 76109; (817) 921-9101

NAME _____
ADDRESS _____
CITY _____ STATE _____
ZIP _____
_____ copies @ \$5 (+ \$1 postage.)
_____ send material about IS CET and becoming certified.

FACTCARDS

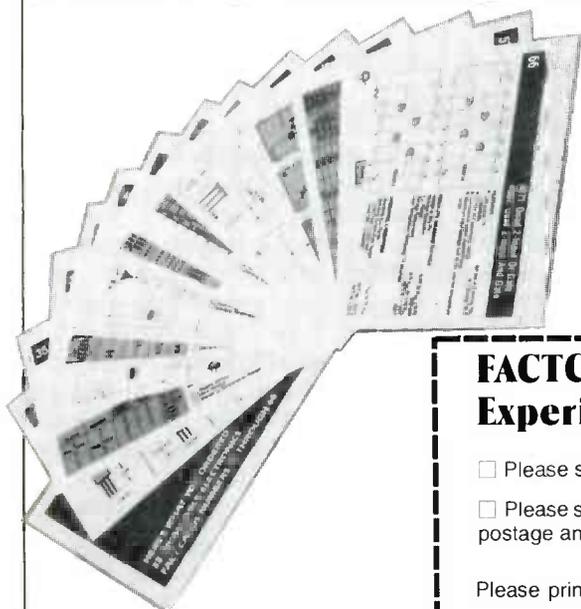

**Jampacked with
information at your
fingertips**

■ ALL YOU NEED to know about electronics from transistor packaging to substitution and replacement guides. FACTCARDS numbers 34 through 66 are now available. These beautifully-printed cards measure a full three-by-five inches and are printed in two colors. They cover a wide range of subjects from Triac circuit/replacement guides to flip-flops, Schmitt triggers, Thyristor circuits, Opto-Isolator/Coupler selection and replacement. All are clearly explained with typical circuit applications.

■ WANT TO EXPAND your knowledge of electronics? Do it the easy way

by studying the Electronics Fact Cards. Do you travel to and from your job each day? Drop a handful of cards in your pocket before you leave, and the bus becomes a schoolroom! At home, you can build some of the projects and not only have fun building and using them, but learn how they work at the same time.

■ YOU'LL BE AMAZED both at how rapidly you learn with these cards, and how easy it is to understand. These new cards are available right now. Don't miss out. Send your check or money order today.

FACTCARDS—Facts at your fingertips for Experimenters and Project Builders!

- Please send one copy of FACTCARDS at \$3.50. Shipping \$1.00 (U.S. and Canada only).
 Please send _____ copies of FACTCARDS. Total cost is sum of copy price and First Class postage and handling cost multiplied by number of card sets ordered.
Allow 6-8 weeks for the material to arrive.

Please print

(Name)

(Street Address)

(City)

(State)

(Zip)

Detach and mail today:
HANDS-ON BOOKSTORE
P.O. Box 4079
Farmingdale, NY 11735

All Payment must be in U.S. Funds!

R9-88

DRAWING BOARD



ROBERT GROSSBLATT,
CIRCUITS EDITOR

Copy protection and a Z-80 reset

A FEW MONTHS AGO I WROTE SOME articles on disk storage and copy protection—what it is, how it's done, and why it works. At the end of the series, I decided to see how many of you found the subject as interesting as I did. In order to make things a bit juicier, I threw in a short listing I found in a protected Apple game a few years ago and figured that only a few of you would be able to work it out.

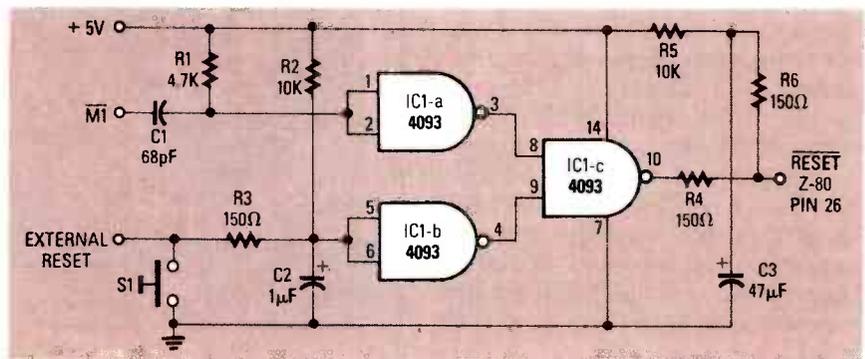


FIG. 1

LISTING 1

```

59E4 CE E7 59 DEC $59E7
59E7 CF ???
59E8 EA NOP
59E9 59 EF EA EOR $EAEF,Y
59EC 59 AD 51 EOR, $51AD,Y
59EF C0 AD CPY #$AD
59F1 54 ???
59F2 C0 AD CPY #$AD
59F4 57 ???
59F5 C0 AD CPY #$AD
59F7 52 ???
59F8 C0 20 CPY#$20
59FA 60 RTS
59FB 5B ???
59FC 20 C5 5B JSR $5BC5
59FF 20 4E 5B JSR $5B4E
5A02 A9 04 LDA #$04
5A04 8D EC B7 STA $B7EC
5A07 A9 00 LDA #$00
5A09 8D EB B7 STA $B7EB
5A0C A9 00 LDA #$00
5A0E 8D F0 B7 STA $B7F0
5A11 A9 60 LDA #$60
5A13 8D F1 B7 STA $B7F1
5A16 A9 40 LDA #$40
5A18 20 45 5A JSR $5A45
5A1B 10 01 BPL $5A1E
5A1D A9 20 LDA #$20
5A1F 91 5A STA ($5A),Y
5A21 AD 50 C0 LDA $C050
5A24 A9 09 LDA #$09
Etc., etc., etc.
    
```

Boy, was I wrong!

It seems that not only are there loads of Apple freaks out there but a lot of you have spent some time code-snooping. However difficult it is to follow uncommented machine code, protected code is twice as hard to understand. The listing in the article was an example of a self-modifying code—a particularly nasty piece of business that shows up every once in a while in low-end software, like games. The original and commented disassembly are shown in listings 1 and 2 respectively. As you can see, once you figure out what's going on, the correct code stares you right in the face.

The only interesting part of the listing is the first three lines of the original code. If you don't catch that, there's absolutely no way you'll be able to make sense out of the rest of it. I'm not going to talk about all of the code, but it's worth some time to go through the protection scheme. Like many other things, it's really simple when you see it.

The first three lines of the original code disassembled like:

```

----> 59E4 CE E7 59 DEC $59E7
59E7 CF ???
59E8 EA NOP
59E9 59 EF EA EOR $EAEF,Y
59EC 59 AD 51 EOR $51AD,Y
59EF etc., etc.
    
```

That looks exactly like the kind of junk you usually see when you try to disassemble data, graphics, or look-up tables. In actual fact, that is the kernel of the method used by the programmer—more than once, I might add—to keep people from following his code. All you have to do to figure it out is exactly what's shown in the first instruction. After decrementing the \$CF at \$59E7, the code changes and looks like this:

```

----> 59E4 CE E7 59 DEC $59E7
59E7 CF EA 59 DEC $59EA
59EA EF ???
59EB EA NOP
59EC 59 AD 51 EOR $51AD,Y
59EF etc., etc.
    
```

By now, a bit of light should be peeking through the window. And as soon as you execute the second instruction at \$59E7, the whole

LISTING 2

```

1 *****
2 *
3 * COMMENTED LISTING OF THE SELF MODIFYING *
4 * CODE FROM THE COPY PROTECTION ARTICLE *
5 *
6 *****
7 *
8 *      ORG  $59ED
9 *
10 *
11 *      Set the screen display switches
12 *
59ED: AD 51 C0 13  SETUP  LDA  $C051  ;Set screen to text
59F0: AD 54 C0 14          LDA  $C054  ;Set Page 1
59F3: AD 57 C0 15          LDA  $C057  ;Set HIRES graphics
59F6: AD 52 C0 16          LDA  $C052  ;Set full screen
17 *
18 *
19 *      Run several subroutines
20 *
59F9: 20 60 5B 21          JSR  $5B60  ;Jump to subroutine #1
59FC: 20 C5 5B 22          JSR  $5BC5  ;Jump to subroutine #2
59FF: 20 4E 5B 23          JSR  $5B4E  ;Jump to subroutine #3
24 *
25 *
26 *      Set several DOS parameters
27 *
5A02: A9 04 28          LDA  #$04  ;Make track #4 the
5A04: 8D EC B7 29          STA  $B7EC  ;current disk track
5A07: A9 00 30          LDA  #$00  ;Make 00 the current
5A09: 8D EB B7 31          STA  $B7EB  ;disk volume number
5A0C: A9 00 32          LDA  #$00  ;Set the active DOS
5A0E: 8D F0 B7 33          STA  $B7F0  ;buffer to the one
5A11: A9 60 34          LDA  #$60  ;that's located at
5A13: 8D F1 B7 35          STA  $B7F1  ;address $6000
36 *
37 *
38 *      Run another subroutine
39 *
5A16: A9 40 40          LDA  #$40  ;Set up accumulator
5A18: 20 45 5A 41          JSR  $5A45  ;jump to subroutine #4
42 *
43 *
44 *      The next instruction makes the program
45 *      bypass the byte at $5A1D, (an $A9). The
46 *      A9 is put there only to confuse the
47 *      disassembly since there's absolutely no
48 *      way it can be reached and executed. This
49 *      is an example of another protection method
50 *      called 'FALSE DISASSEMBLY' and is used by
51 *      some programmers to hide sensitive code.
52 *
53 *      It can be VERY hard to detect!!
54 *
55          BPL  $5A1E  ;Skip over next byte
56          A9          ;False disassembly
57 *
58 *
59 *      Run another subroutine
60 *
5A1E: 20 91 5A 61          JSR  $5A91  ;Jump to subroutine #5
62 *
63 *
64 *      Switch the screer to graphics
65 *
5A21: AD 50 C0 66  START  LDA  $C050  ;Set graphics screen
67 *
68 *
69 *      Continue with the rest of the program
70 *
5A24: A9 09 71          LDA  #$09  ;etc., etc.....

```

thing becomes clear since what you get is:

```

59E4 CE E7 59 DEC $59E7
59E7 CE EA 59 DEC $59EA
----> 59EA EE EA 59 INC $59EA
59ED AD 51 etc.LDA $??51

```

The final instruction at \$59EA

changes the \$EE back to \$EF—but not until after the instruction executes! That means the instruction at \$59EA modifies itself and location \$59EA only contains an \$EE for as long as it takes the instruction to execute. Unless you work it out you'll never get it.

continued on page 86

For 25 years,
our people have
endured long hours
and tough
working conditions
for no pay.



And 9 out of 10 would
do it again.

TO FIND OUT WHY

call
(316) 263-2100
or write

REACT INTERNATIONAL, INC.
242 Cleveland
Wichita, KS 67214

Get A Complete Course In

ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. \$99.95, Postage Included. Satisfaction guaranteed or money refunded.



**Banner
Technical
Books, Inc.**
1203 Grant Ave.
Rockford, IL 61103

CIRCLE 188 ON FREE INFORMATION CARD

COMMUNICATIONS CORNER



HERB FRIEDMAN,
COMMUNICATIONS EDITOR

A new way to communicate!

THE ENCODING OF NON-MILITARY communications originated as a need to conceal commercial transactions from accidental discovery. Almost anyone could eavesdrop on short-wave Morse-code cable traffic, and so the five-group commercial code was developed as a way to pass international traffic without a casual listener discovering that a boatload of bananas had just left Central America, or that a rust-bucket pulling into Pago-Pago had gold bars concealed in the salted fish.

Those who required maximum secrecy—spies, international bankers, merchants of death, and other nefarious schemers—used encoding that might take hours to decode by those having the key; weeks, months, years, or never by those not having a key, or a spy or a mole with the opposition.

Non-military encoding was also used to reduce the amount of time and effort needed to send a commercial message, and there were various national and international message codes for that purpose. The familiar 73's (goodbye, or best regards) and 88's (love and kisses) used by the amateur radio operators are from an old international message code in which two-digit numbers represented complete sentences. Radio operators also had the international Q-signal code, in which 3-letter groups starting with the letter Q represented a thought, a sentence, or a particular situation.

Digitize

In the context of using encoding to save time—not for conceal-

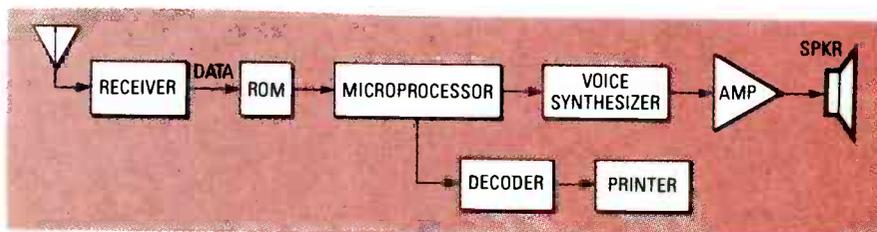


FIG. 1

ment, espionage, nor military use, although it provides security even superior to the famed enigma code machine—we have combined the modern microprocessor with the old concept of an alpha or a numeric commercial code to create the fastest, most secure means of sending a message from one place to another.

For example, assume we have a data-exchange system running at 1200 baud. The transmission of the digitized message 22 96 16—which at 1200 baud would sound exactly like a blip of static—would produce a printout at the receiver of "CONGRATULATIONS ON YOUR WINNING THE LOTTERY FROM YOUR LONG LOST FAMILY IN CALIFORNIA." Or perhaps a digitized blip of 13 87 23 POLE 15 MALAMUTE 17 would result in a telegram reading "SORRY WE CAN'T BE WITH YOU ON YOUR MOST JOYOUS OCCASION. CONGRATULATIONS ON YOUR REACHING THE POLE. THE BOYS AT THE MALAMUTE SALOON."

Not only would the blips of what sounds like static to the human ear result in complex messages; they would also be automatically translated into the language and grammar of the people at the receiving facility.

Done in memory

Sound farfetched? Not so! Just such a system is being introduced in Europe for—would you believe?—the common automobile radio, and **Radio-Electronics** will have a feature article on the European system in a future issue. Meanwhile, let's take a quick-and-dirty look at how it's done.


The key to the system is the same idea used in the *Digital L/C Meter* project in the July '88 issue of **Radio-Electronics**. If you recall, the results of thousands of calculations were stored in a ROM. A capacitor or inductor connected to the meter's input terminals created a specific voltage condition. Instead of going through all the calculations and interpretations needed to determine the L or C value represented by the condition, the meter simply compared the condition to the calculated results stored in the ROM. Almost instantly, a match was found; and the meter displayed the L or C value that corresponded to the stored ROM data. (Yes, that's a gross oversimplification. Read the original article if you want an in-depth explanation.)

Using the functional block diagram shown in Fig. 1 as the reference, let's apply the L/C meter's

R-E Engineering Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775 each. Closing date same as regular rate card. Send order with remittance to **Engineering Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Engineering ads are accepted for this Admart.**

MIDI PROJECTS

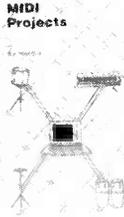

BP182—MIDI interfacing enables any so equipped instruments, regardless of the manufacturer, to be easily connected together and used as a system with easy computer control of these music systems. Combine a computer and some MIDI instruments and you can have what is virtually a programmable orchestra. To get your copy send **\$6.95 plus \$1.25 for shipping** in the U.S. to **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.

FCC LICENSE PREPARATION

The FCC has revised and updated the commercial license exam. The **NEW EXAM** covers updated marine and aviation rules and regulations, transistor and digital circuitry. **THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE** contains the necessary preparation for **ONLY \$25.00.**

WPT PUBLICATIONS
979 Young Street, Suite A
Woodburn, Oregon 97071
Phone (503) 981-6122

CIRCLE 181 ON FREE INFORMATION CARD

NO WAITING FOR COMPLETE, LOW PRICED, CHIP COMPONENT KITS

CC-1 Capacitor Kit contains 365 pieces, 5 ea. of every 10% value from 1pf to .33µf. CR-1 Resistor Kit contains 1540 pieces; 10 ea. of every 5% value from 100 to 10 megΩ. Sizes are 0805 and 1206. Each kit is **ONLY \$49.95** and available for immediate One Day Delivery!

Order by toll-free phone, FAX, or mail. We accept VISA, MC, AMEX, COD orders, or company PO's with approved credit. Call for free detailed brochure.



COMMUNICATIONS SPECIALISTS, INC.
426 West Telford Avenue - Orange, CA 92665-4296
Local (714) 998-3021 • FAX (714) 974-3420
Entire U.S.A. 1-800-854-8547

CIRCLE 186 ON FREE INFORMATION CARD

use of ROM memory to communications. Notice that we have a receiver feeding a data output to a ROM, which, in turn, feeds a microprocessor, a voice synthesizer, an audio amplifier, and a speaker. A second output channel from the microprocessor feeds a decoder and a printer.

The ROM is like a giant CD-ROM, or even a Compact Disc, in that it contains a digitized representation of thousands of words and phrases; much like the "human" voice the telephone company uses for its information service to give telephone numbers. Each word or phrase can be keyed only by a specific input data code. For the sake of discussion, let's assume that a number represented by binary data represents a digitized word, or a string of digital data represents a phrase.

Assume that the receiver outputs data representing the number 13. The 13 is the ROM-address key for digitization of "SORRY WE CAN'T BE WITH YOU ON YOUR MOST JOYOUS OCCASION." That digitized message is fed to the voice synthesizer, which outputs the complete phrase in a "human voice." Alternately, the digitized data from the ROM could also feed the decoder and printer, thereby printing the message.

Now I have the message represented by a 13 written in English. In actual use, the equipment used in each country would have a ROM whose messages are digitized in its own language. In that way, an international communications code of 13 could produce the same message in any language.

What's that? You claim that the system would provide unbreakable encryption. You betcha! If the ROM data were uncovered by a spy, it would only be necessary for the user(s) to plug a different ROM into each receiver. If the ROM exchange was time-coordinated, a communications service, country, or whomever could change all their encoding equipment in a matter of minutes. It would even be possible to bank-switch various ROM's in order to accommodate specific services.

Rolling code

In the event that the ROM could not contain certain data, such as the name of a city, state, or person, that information for ordinary communication traffic could be sent in clear text—as we showed with *POLE* and *MALAMUTE*, or digital data could be used to represent individual characters. Were full secrecy necessary, the character encoding could be done on a rolling

basis, in the same manner as used for the enigma machine. That is, the first time a 12 might represent the letter P, while the second time a 12 would represent a Z while a 26 represented E, etc., etc., etc. A 4-bit microprocessor is really all that's required to accommodate a rolling code.

The only real limitations for ROM'ized communications are the practical limitations on the size of the ROM and the kind of messages we intend to exchange. But the way that technology is going, in a couple of years a \$2 ROM might well contain the digitized data for every word and phrase known both on Earth and in the nearest inhabitable galaxy.

The applications for such a system are endless. For example, imagine that you're driving in your car somewhere out of state, and you don't know what stations are broadcasting classical music, which you enjoy. All you would have to do is program your car radio to tune in to any station that happens to be broadcasting classical music, and your car radio would then tune in to only those stations. In fact, there is just such a system in use today. You should keep an eye out for a feature article on that system in an upcoming issue.

R-E

DRAWING BOARD

continued from page 83

In actual fact, that is really sloppy programming. The game it was protecting (no names) is a really slick piece of work and is obviously that of a gifted programmer. Finding that kind of garbage in the middle of it is evidence that someone else modified the source code in order to make it difficult for people like us to examine and understand.

If you go through the corrected listing carefully, you'll realize that the second programmer forgot to put everything back the way it was in the beginning, because executing the instruction at \$59EA will leave the listing looking like:

```
59E4 CE E7 59 DEC $59E7
59E7 CE EA 59 DEC $59EA
59EA EF     ???
59EB EA     NOP
59EC 59 AD 51 EOR $51AD,Y
----> 59EF etc., etc.
```

That's not the same as the original listing. In order to do the job properly, the code should have looked like:

```
59E4 CE E7 59 DEC $59E7
59E7 CE EA 59 DEC $59EA
59EA EE EA 59 INC $59EA
----> 59ED EE E7 59 INC $59E7
59F0 AD 51 etc. LDA $??51
```

The instruction I added at \$59ED would make the code go back to its original garbage appearance as soon as it was finished.

Hey, if you want to throw people off the scent at least do the job properly!

Several people who worked out the listing also picked up the fact that there was some unnecessary code as well. It showed up as:

```
5A07 A9 00 LDA #$00
5A09 8D EB B7 STA $B7EB
----> 5A0C A9 00 LDA #$00
5A0E 8D F0 B7 STA $B7F0
```

You can see that the instruction at \$5A0C is a waste of space since the accumulator was already loaded with \$00 at \$5A07 and hasn't been changed. It's only a couple of bytes and doesn't really mean

much in the great scheme of things, but it's surprising to see it there since the game was such a neat bit of programming.

A special thanks to D. H. Evett, Steve Z, James Swindell, Raymond Zapp Jr., Philip Albro, Alan Wilson, Isaac Molho, Michel Kronowit, and David Andrus, for sending in the correct listing. You've all earned 17 cracking points and a gold star.

I was happy to see that a lot of you share my interest in working out puzzles in general and snooping around software in particular. If you'd like to see more of that kind of thing, drop me a note and let me know. The next time I do it, however, I'm going to make it *really tough!*

There isn't really enough room in this column to go into a heavy discussion of copy protection, but I can certainly pass along any tips and suggestions that look interesting. One thing though: Software is machine-specific—an elegant code on an Apple is just garbage to an IBM. If you want to see more on that subject, let me know what kind of computer you have and what peripherals you have connected to it.

In order to deal with copy protection you have to have a working understanding of assembly-language programming. There's no easy way to get into it—you just have to make up your mind and do it.

The more experience you have with dealing with the CPU on a gut machine-code level, the more success you'll have in dealing with the ins and outs of copy protection. When I get a better idea of what kind of computers you own, I'll be able to make some recommendations of programming books and tutorials. If you know of any good ones for your hardware, put them on the note and I'll be sure to pass them along.

Z-80 Reset

On a completely different subject, John Gruszynski dropped me a note with a question about the Z-80 series we did a few months ago. He wants to know what happens to the registers when the Z-80 is reset. Here it is:

IC TESTER

continued from page 40

while the red clip goes to the positive side. Make or purchase an IC test cable and test clips (one 20-pin and one 16-pin test clip should be adequate), and use a 20-pin cable with multi-colored micro-hook probes for the analyzer cable.

After checking for good solder joints and proper component location, install the four AE013 IC's observing proper handling precautions for CMOS devices. As shown in Fig. 3, pin 1 of IC3 and IC4 is oriented 180 degrees from pin 1 of IC1 and IC2. If the IC's are installed backwards, they will be damaged. Put an 8-section DIP switch in the S2 socket; the switch marked "1" goes toward the pin-1 end of the socket.

Checkout and final assembly

For the preliminary checkout you will need a +5-volt supply, capable of outputting at least 250 mA. (DO NOT connect the tester to anything greater than +5.5 volts.) Plug the 20-pin header, P1, to SO1, and connect a jumper from any pin of the header to ground. Now wrap a thin piece of bare wire around each pin of the header, so that all of the pins are connected together. Wrap a thin piece of bare wire around each pin of DIP-clip S02, so that all the pins are connected together. Now connect a jumper from any pin to ground. Turn off all sections of S2, and then connect the power leads to the +5-volt supply and then press and release S1. If the tester is working properly, all of the LED's should be off except LED21.

With S2-h open, connect the P1 header jumper to +5 volts, and then remove it and connect it to ground. All of the LED's should turn on and stay on. Now, with S2-h closed, connect the jumper to +5 volts, and then to ground. All the LED's should turn on when 5 volts is applied, and then go off when the jumper is grounded (holding S1 will have the same effect). Now remove the power, the P1 header from SO1, and the SO2 test clip.

Now get your enclosure, and label the front panel using the photographs as a guide. Drill and/or punch holes as necessary, and be sure to make a hole in the bottom of the case for the power

continued on page 104

1—Output control lines become inactive.

2—Data and address buses go tristate.

3—Interrupt mode is set to zero.

4—Interrupt and refresh registers are set to zero.

5—All interrupts, except NMI, are disabled.

6—Program counter is set to zero (execution starts at 0000h).

As you can see, it pretty much starts everything from scratch. A hardware reset is usually generated when you first power-up the system to make sure things start off in a known state.

To answer specifically: The program counter resets to zero as a result of a reset, and program execution starts at location 0000h. If you do a reset at startup, (and you should), it doesn't really matter what else is going on in your circuit because you're just starting out. If, however, you do a reset while your circuit is powered up, there is one circumstance that can cause you some problems.

If you're using dynamic RAM in your circuit and the R register in the Z-80 to handle the refresh, a hardware reset can cause the contents of the RAM to get trashed because the reset signal takes precedence over everything else.

When RESET is brought low, it takes effect irrespective which part of the instruction is being executed. One way around that is to synchronize a reset with the appearance of the M1 signal. The circuit in Fig. 1 will do that for you and also give you a way of having a reset done by either a manual switch or some other kind of logic circuitry.

By synchronizing reset with M1, a reset can never happen while the CPU is talking to memory so there's no chance of a memory glitch due to an erroneous write. Of course, since the R register is reset to zero as well, you'll have to make sure your refresh timing is fast enough to save the data you've already stored—but that is a different problem.

The Z-80 can take the strain out of a lot of design problems. A good designer can mix some hardware with a bit of software and cut the size of the board down to a minimum. But the price you pay for that convenience is that the Z-80 is a complex IC and dealing with software is a whole new can of worms. There's no way you can use the IC successfully without doing your paperwork first.

There are lots of books on the Z-80 that can tell you everything you want to know about the IC. The first place to look is in your local library; if you don't find what you want there, write to the electronics book publishers. And don't forget the people who make the Z-80 (Zilog, 210 Hacienda Ave., Campbell, CA 95008). They all have data books and application notes that are crammed with lots of good information.

We seem to have gotten off the subject of display multiplexing but don't worry, we'll pick it up again next month. I promise. R-E

HARDWARE HACKER

continued from page 75

The best sources of design and supplier information on synchronous inverters seem to be several rather expensive trade journals. Visit a large technical library and see if they have *Solar Age*, *Solar Energy*, *Solar and Wind Technology*, or, on the more practical side, *Solar Engineering and Contracting*.

New tech info


Let's see. There's a free *Thyristor selector guide and cross reference* from Motorola, a *Modem Design Booklet* from Exar, a new *Linear IC Handbook* from Plessey, and the *Standard Products data book* from Standard Microsystems that does include such chips as CRT display circuits and keyboard encoders.

And C & H Sales now has a new surplus catalog full of robotics and other goodies. A free sample force-sensing resistor is obtainable from Interlink Electronics. And, at long last, sanely priced current transformers for energy

management and such as described in the *Current Ring* data sheets from ISL.

If you are at all interested in any Apple computing, be sure to check into my *Enhancing your Apple IIe*, volumes I and II, my *AppleWriter Cookbook*, and my *Apple Assembly Cookbook*. By one of those absolutely astounding coincidences, I do appear to have several autographed copies on hand here.

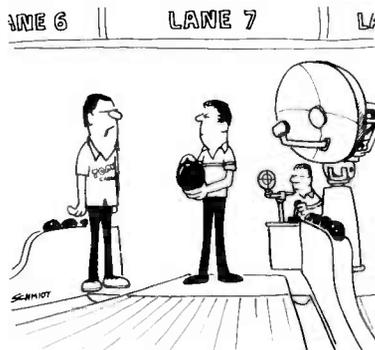Write or call if you are at all interested. Let's hear from you. R-E



"There's a rumor around that some of your guys are using an electronically controlled ball..."

CONVERTERS & CABLE DECODERS

INFORMATION

402-554-0417

Orders & Free Catalog

1-800-624-1150

ALL PRODUCTS GUARANTEED

New Stargate 2000	\$99.00
SB-3/2.....	\$89.00
Tri-Bi Mode.....	\$99.00
Hamlin MLD-1200.....	\$100.00
Oak N-12 W/V.S.....	\$99.00
Panasonic.....	\$99.00
Oak-M-35-B W/V.S.....	\$100.00
Zenith SSAVI.....	\$185.00
Eagle PD-3.....	\$110.00
Scientific Atlanta.....	\$120.00
Pioneer W/ Parental.....	\$105.00
Tocom.....	Call
Oak N-12 W/ Auto.....	\$140.00
Evaluator Tap Detector..	\$495.00
ViewStar Volume+.....	\$129.95
Jerrold Starcom CSV....	\$139.95


M.D. ELECTRONICS
5078 SO. 108th
SUITE 115MD
OMAHA, NE. 68137

CIRCLE 53 ON FREE INFORMATION CARD

SEPTEMBER 1988


87

PC SERVICE

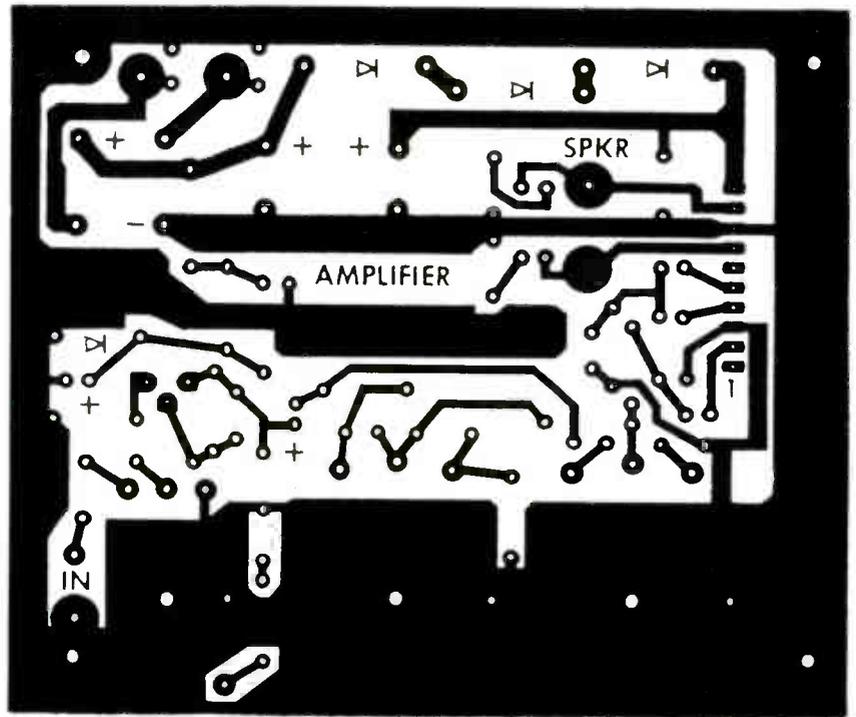


4 5/16 INCHES

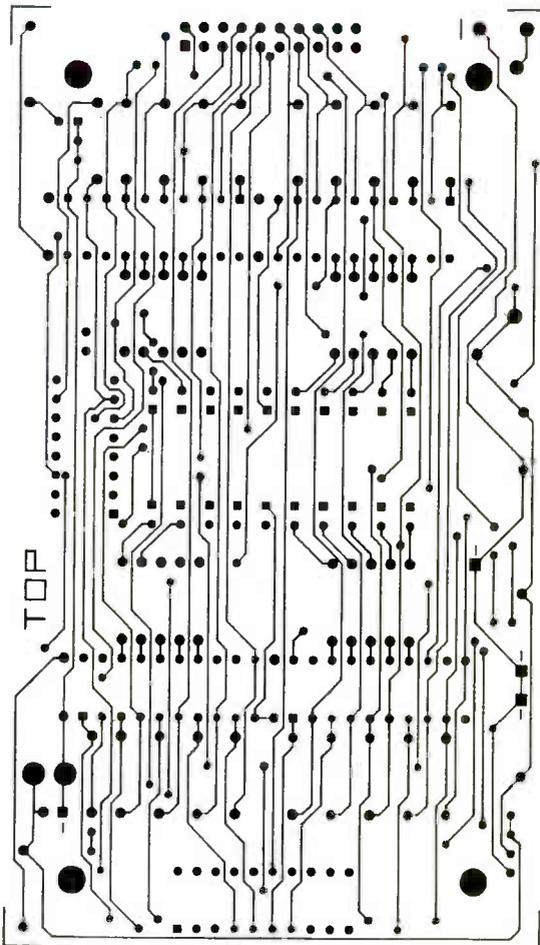BUILD THE AMPLIFIED SPEAKER SYSTEM using this pattern.



4 7/8 INCHES

COMPONENT SIDE of the IC tester.

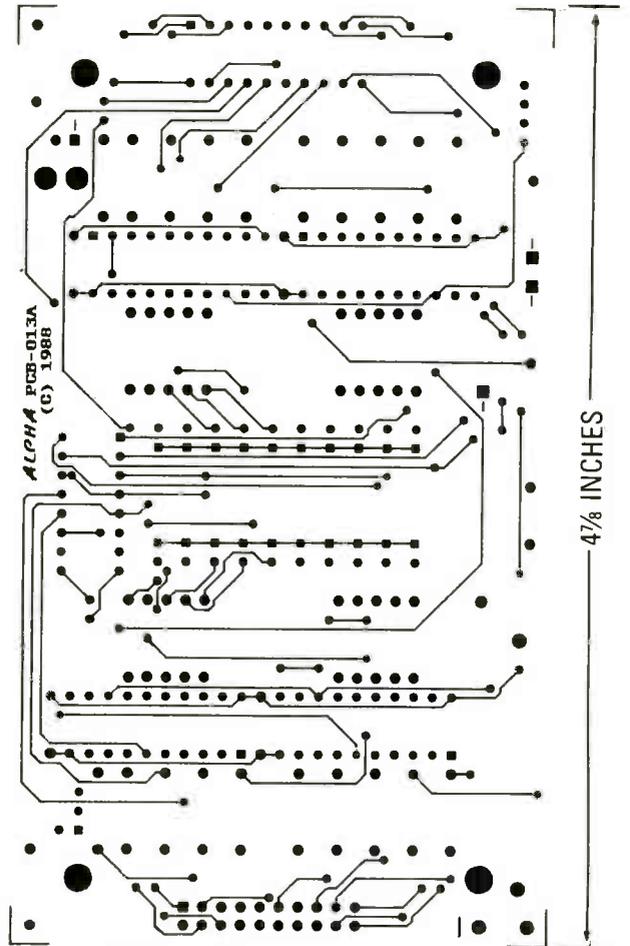

4 7/8 INCHES


SOLDER SIDE of the IC tester.

COMPUTER DIGEST

A NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

INCREASE YOUR BRAIN POWER

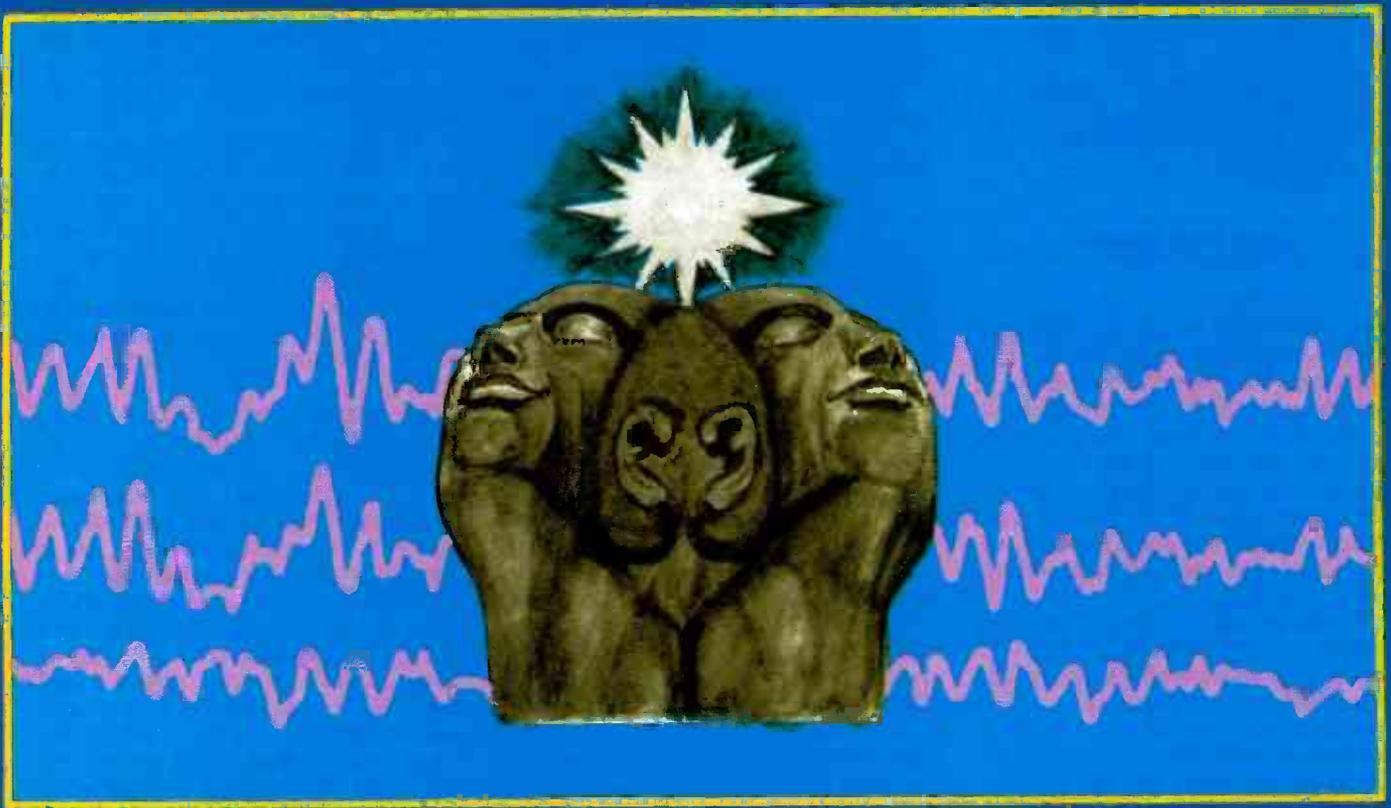
Our Synergy Card puts your brain's hemispheres in sync for increased analytical power **Page 94**



CD CLASSROOM

The series concludes with a look at the disk controller and parallel port **Page 97**

EDITOR'S WORK- BENCH

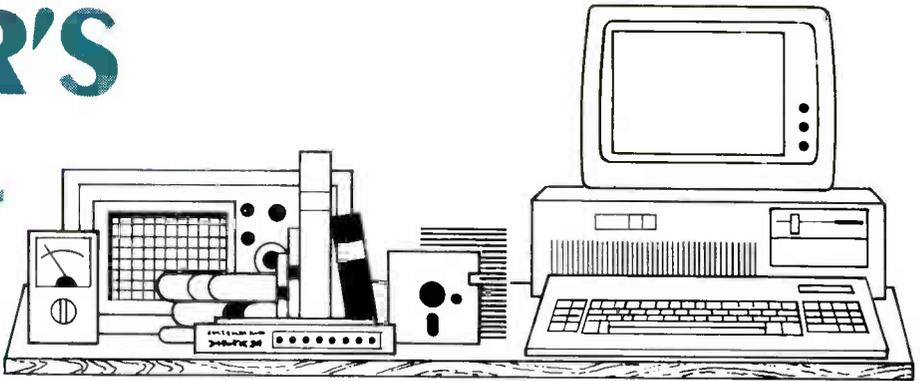

A Pair From Paradise

Resolution of video adapters and monitors is increasing. For those in fields requiring high resolution (CAD and desktop publishing), that's good news. For the rest of us—those who want it but can't afford it—it's bad news. In fact, a quality EGA adapter and monitor still costs three times or more what a Hercules mono system costs—and a Hercules system actually provides 12% better resolution than an EGA!

To help users at both ends of the scale, Paradise Systems recently introduced a pair of half-length video adapters. The low-cost AutoSwitch Monochrome EGA allows the user to run both CGA and EGA programs on a TTL monochrome monitor. Of course the board can also run standard Hercules monochrome graphics. The VGA Plus Card, on the other hand, requires an analog monitor or a NEC MultiSync (or equivalent), and provides displays of up to 800 × 600 with 16 simultaneous colors.

The AutoSwitch Monochrome EGA

Many programs are written to support both Hercules and EGA graphics systems—but some aren't. OS/2, for example, requires EGA (or VGA) graphics. However, it's hard to scrap a perfectly good video system, especially when you consider that a standard TTL monochrome monitor has the bandwidth to display images at EGA resolution easily.

Paradise did consider that fact, and decided to build an adapter that takes

advantage of it. The AutoSwitch Monochrome EGA Card can run any software designed for CGA, EGA, and Hercules graphics—all on a standard TTL monochrome monitor.

The board works in two modes: True Monochrome Mode (TMM) and Color Simulation Mode (CSM). In TMM, you run software set up for standard text, Hercules text and graphics, and monochrome EGA text and graphics. In CSM, you run software set up for color CGA and EGA text and graphics. In this mode, colors are represented as different intensity levels. White is bright, black is dark, and the other colors are somewhere in between.

DIP-switch settings allow you to boot the card in either TMM or CSM. You can also change modes at the DOS command line using a utility program (MEGA.EXE). You can even "lock" a mode, so that even if you normally run in TMM, you can lock CSM, reboot, and then run Flight Simulator and other self-booting programs.

In addition to the two modes, the board has a feature called AutoSwitch which is also enabled and disabled by a DIP switch and MEGA.EXE. With AutoSwitch enabled, in TMM, you can run any monochrome software (MDA, Hercules, or mono EGA), and the card will switch into the correct mode automatically without changing switch settings, software drivers, or anything else. Likewise, in CSM, you can run CGA and EGA software at will.

The board's last major feature allows you to run text-mode applications in 132-column width, with either 25 or 43 lines. Paradise supplies software drivers and patches that allow you to do so using Lotus 1-2-3 and Symphony, Framework II, WordPerfect 4.2, and WordStar versions 3.3 and 4.0.

One potential problem with a board of this nature is lack of contrast. Color combinations that are perfectly legible on a color monitor may be illegible on a monochrome monitor. So Paradise supplies an additional utility that allows you

to modify, save, and load "palettes"; maps that show how various colors are translated into different levels of intensity. You can have different palettes for different applications, loading them as required at the DOS command line or by batch file.

As for compatibility, the board worked fine in both modes with all software tested, including tough graphics programs such as Windows 2.0, Dr. Halo III, and Broderbund's PrintShop. (By the way, in the past we had run the latter on a Hercules mono card using a public-domain utility called SIMCGA, which is available on the RE-BBS. It looks *much* better on the Paradise card.)

We tested the card in two machines: a new-model IBM PC XT (with a 640K motherboard), and an AST Premium/286 (a 10-MHz AT compatible). The AutoSwitch Monochrome EGA card ran with no problems whatsoever in the AST, but in the IBM, a slight shimmering effect was observable with some color combinations. For example, the bright blue that is used as a background color in PC Outline shows up as a shimmering grey on the AutoSwitch Monochrome EGA. Careful adjustment of the monitor's contrast and brightness controls could reduce the effect, but not eliminate it. Because we've had compatibility problems with that XT before, we suspect it is at fault. Paradise is looking into the problem.

Enhanced VGA

At the other end of the scale, the VGA Plus is an analog-only card, which means you'll need a NEC MultiSync or compatible, or one of the new IBM analog monitors.

The VGA Plus is compatible with all IBM standard video modes (CGA, EGA, MCGA, and VGA), Hercules monochrome, and three proprietary modes. Like the monochrome EGA card, the VGA Plus supports 132 columns by 25 or 43 lines in text modes. It also supports an 800 × 600 graphics mode. (The latter mode won't run on IBM analog monitors.)

Special drivers are supplied that allow you to run Windows 2.0 (including any program that runs under Windows—PageMaker, Excel, etc.), GEM, AutoCAD, Ventura Publisher, Cadvance, and Framework II in the 800 × 600 graphics mode. Other drivers and patches are available for running Framework II, WordStar 3.3 and 4.0, and WordPerfect 4.2 in 132-column text modes.

Unlike some VGA-compatible boards, the VGA Plus has the "Feature Connector" that is part of the IBM VGA standard. The Feature Connector is designed to allow add-on hardware to provide enhanced video features, but so far there are no commercial products that utilize the Feature Connector.

Like the AutoSwitch Monochrome EGA adapter, the VGA Plus ran all the software we tested it with, without any problems, including Windows 2.0 and AutoCAD Release 9.0.

Whether you're looking for an enhanced VGA card for advanced graphics applications, or for an inexpensive way to obtain EGA graphics, Paradise has a solution for you.

OS/2 on an XT?

If you know anything about OS/2 at all, you know that it requires an 80286 or 80386 microprocessor and at least 1.5MB of extended memory. Therefore, the new operating system can't run on an XT—right? Wrong. SOTA Technology's Mothercard 5.0 (reviewed in the November 1987 issue of *Computer Digest*) is an accelerator card that provides a complete operating environment for its 80286: it has its own AT-compatible BIOS, its own on-board RAM, its own math coprocessor, etc. Except for I/O circuitry, the Mothercard amounts to an entire AT machine on a card.

The wizards at SOTA have devised a set of drivers that allow IBM's version of OS/2 to run on the card. It works nicely: We tried it.

You'll need a high-density disk drive (1.2M or 1.44M) to install OS/2; because most XT's don't have the proper adapter, SOTA has designed one of their own. We saw an early version of The Floppy I/O Plus, which should be ready by the time you read this. The board will support as many as four internal and external floppy-disk drives in any format (3½ and 5¼, 720K and 1.44M, and 360K and 1.2M, respectively), and also contains a parallel port and one or two serial ports. The company will throw in a free copy of OS/2 and a Floppy I/O Plus to anyone who purchases the 12.5-MHz version of the Mothercard and the two-megabyte daughtercard.



GrandView

Organization is the key to working efficiently; a new category of software purports to help us get organized. Some programs in that category provide brand-new interfaces and techniques; others build on past types of software (outliners, project managers, free-form databases) to provide capabilities far beyond those of the software type on which they're based. Because of the potential and versatility of these organizers, we'll examine several of the more interesting ones during the next few months.

Living VideoText (a division of Symantec) recently introduced GrandView, a program that comes from the outline tradition. In fact, the program was written by the same person who wrote our favorite (till now) outliner, PC Outline. As you might expect, GrandView resembles PC Outline in many respects, but the program was also influenced by Living VideoText's own ThinkTank. (PC Outline and ThinkTank were examined briefly in the March 1987 and May 1988 editions of *Computer Digest* respectively.)

The basic user interface strongly resembles that of PC Outline. A series of drop-down menus allows you to load and save files, perform editing functions, change the screen view, reorganize your outline, etc. You can access the menus by pressing F10 or the slash key ("/"), or by using a mouse. Many common menu commands are also accessible through Ctrl- and Alt-key combinations. Alt-S, for example, saves the current outline to disk. A built-in keyboard macro processor allows you to define your own keystrokes to accomplish the tasks you perform most often.

Like PC Outline, you can have as many as nine outlines open on-screen simultaneously. But GrandView gives you quite a bit more flexibility in their on-screen arrangement. They can be tiled (arranged in adjacent, non-overlapping windows) in several ways, overlapping, or in a custom arrangement designed by you. When you hit on the correct format, you can save it to disk and reload it later. And using the Autostart macro, you can even force that window setup to be loaded every time you start GrandView. Those are great improvements over PC Outline.

If you've never used an outliner, nearly all allow you to create headlines, sub-headlines, sub-subheadlines, and so forth. Each headline (or subhead) may be just a single line of text, or it may contain several paragraphs of text. To rearrange an outline, you can move a headline (or subhead); all subheads and associated text will move with it. Display options allow you to hide and show various levels of detail—headlines only, headlines and first-level subheads, etc. The ability to "zoom" in and out using the various display options allows you, at different times, to see the overall structure and to zero in on the details.

Of course, GrandView includes the usual complement of editing and outlining functions, as well as advanced features like the ability to mark a disparate group of headlines throughout the outline and gather them together in a new place. Other commands allow you to move and copy a headline or group thereof, join and divide headlines, clone headlines (in which all changes made to one copy of a headline or group are reflected in the other), sort and prioritize headlines. Hoisting a headline hides all of the outline except the current headline, its subheads, and all associated text. That allows you to focus on the subset. Hoisting and cloning are borrowed from ThinkTank.

GrandView also allows extensive print formatting, including headers and footers, specification of fonts and typestyles by outline level, etc. No longer do you have to transfer an outline from an outliner to a word processor for final printing.

What's new

So far, GrandView sounds like a beefed-up outliner. What gives it the increased organizational abilities mentioned above? Two things: the automation provided by the automatic keyboard macros, and the new ability to view outline entries by category.

In fact, GrandView allows three views of a given document: outline, document, and category. Outline view is the traditional indented hierarchy of headlines and subheads.

Document view shows (and allows you to edit) just the text of a particular headline or subhead.

Category view is more complex. When creating your outline, you can associate each headline and subhead with one or more different categories. You can then use category view to view your outline by category entries.

For example, suppose you're managing the research, engineering, and manufacturing departments of an engineering firm. Suppose further that some people work in more than one department. You

might create an outline with research, engineering, and manufacturing as the major headlines. Under each headline you would create a list of current projects. Each project would be categorized according to project leader, monthly expenses, and critical parts.

Then, when Bill comes in and complains that he has too much to do, you could call up your outline, go into category view, and instantly display all the projects he's working on. Once a week you would examine your outline from the critical parts perspective, thereby making sure that a project isn't being delayed because parts aren't available. Once a month, you could update (and justify to your boss!) the expenses category.

GrandView also has numerous small features that make it a joy to use. It is, for example, one of the growing class of text-mode programs that make impeccable use of a mouse to initiate menus and select items from them, mark blocks of text, etc. The program also has an enviable on-line help system, and numerous configuration options that allow you to customize behavior to your tastes.

Conclusion

Even without the ability to categorize information, GrandView represents a significant improvement in outlining software. In fact, GrandView currently represents the state of the art. So whether you've been considering using an outliner or you're already experienced with another outliner, check out GrandView—you won't be disappointed. Just remember that, like any tool, GrandView is only as effective as the person using it. If you're new to PC-based outlining, you'll probably have to spend some time getting acquainted before you can become productive.

Excel

Lotus 1-2-3 has reigned as king of the spreadsheet hill (which is rapidly becoming a mountain) for many years now, but several contenders to the throne have arisen recently. Borland's Quattro attempts to out-Lotus Lotus, but Microsoft's Excel takes the spreadsheet metaphor to new heights.

The program runs under Windows 2.0. Excel comes with a run-time version of Windows, but to pass data among Windows applications, you need a regular copy of Windows 2.0. You also need a big, fast machine with a lot of RAM to run Excel. At a minimum, a fast AT with a fast hard disk, 640K of conventional memory, and at least a few hundred K of expanded or extended memory are required. You'll also want a mouse.

Whereas Quattro provides an optional clone of the Lotus interface, Excel has its own user interface. However, in what is without question the best on-line help system we've ever seen, an experienced Lotus user can easily find the equivalent Excel command. A similar capability is provided for Multiplan users. In addition, the help system contains an excellent tutorial and an encyclopedic multi-level indexed and cross-referenced listing of all commands. There is also a separate guide to keyboard commands, and a Feature Guide that functions as a tutorial for intermediate users. The combination of all the help functions makes it possible to learn (or relearn) most of what you need to know about that complex product without ever opening the well-done manual.

Because Excel runs under Windows, you get all of the advantages and disadvantages of that environment. On the plus side, the graphic environment is easy to work with, and provides, with the proper printer, the possibility of high-quality output in a multitude of type faces, as well as high-quality graphics. On the other hand, with anything less than a fast 286, operation is *slow*.

Excel provides three basic kinds of structures: spreadsheets, macros, and charts. Unlike Lotus, each type of structure is stored in a separate file, which helps keep your spreadsheets free of clutter. All three structures provide capabilities that Lotus is only now beginning to incorporate into the latest version of the program (3.0), which is due out about the time you read this. For example, Excel provides more than 40 pre-defined charts, including various types of bar, line, and scatter charts. You can define multiple charts for a single spreadsheet; each chart appears in a separate window. Unfortunately, 3D charting is not implemented. Unlike Lotus, Macros can be recorded as you enter the actual keystrokes; later you can edit your macros in a macro editing window. As for spreadsheets, you can have more than one open at once (limited by the amount of memory you have), and separate spreadsheets can be linked, so that changing data on one spreadsheet is automatically updated on any linked spreadsheet. The list goes on and on.

Excel is a big, powerful program, and it requires a big, powerful machine to run it. But working with it is both fun and productive. And it's also a harbinger of the type of program we'll start seeing soon that run under OS/2.

Graphics Conversion with Hijaak

Graphics on PC's were once limited to games, but more and more serious uses are cropping up all the time. The

problem is that there is no standard file format, so you can't, for example, read images created by Microsoft Paint into Dr. Halo for further editing. And forget about transferring an image from an Amiga or a Macintosh to a PC (or vice versa).

Inset Systems recognized the problem and has started building a solution to it. (The company's first product, Inset, allows you to do desktop publishing within the confines of your own word processor; see the February 1988 issue for a review.)

Hijaak allows you to capture the screen of just about any IBM PC program and then convert it to one of the supported formats, which presently include: Amiga ILBM, Compuserve GIF, Halo CUT, Hewlett-Packard PCL, Inset PIX, Lotus PIC, Macintosh MacPaint, Microsoft Paint, NewsMaster, PC Paintbrush, PrintMaster, Text, TIFF, and PostScript. Or you can convert a disk file created in one format to another. Exceptions presently include the ability to transfer only from (not to) the Lotus PIC format, and only to (not from) PostScript format.

Conversion can be accomplished from a fill-in-the-blanks program or via the DOS command line (or in batch files). In either case, the process is quick and painless.

Supported formats for capturing images directly from screen include C/GA, EGA, VGA, Hercules, AT&T, and Toshiba (T3100).

Hijaak's manual is very well written and laid out, which makes learning and using the program simplicity itself. All software manufacturers should buy a copy of Hijaak just to see the right way to do a manual.

Optimize Disk Performance with VOPT

It's a fact of PC life that disk files become fragmented over time. By un-fragmenting them, they load faster because the read/write head needn't shuttle back and forth across the surface of the disk. Rather it laps up each sector as it passes beneath the head.

Several un-fragment programs are sold commercially; one of the better is VOPT, by Golden Bow Systems. VOPT is both safer and faster than most comparable programs, because it does not try to account for every single sector. For example, if there is a single unused sector in one of the lower numbered tracks, other programs will shift the entire sector chain—which could comprise many megabytes—down just to reclaim a few K of space. Doing so takes a long time and is dangerous, because if a power line glitch occurred in the middle of the pro-

cess, one or more files could be hopelessly scrambled.

VOPT, on the other hand, adopts an intelligent approach to reclaiming unused space. Rather than shifting an entire disk down to fill a small space, it will move a small file there, or simply leave it unused. Doing so greatly increases safety and greatly decreases the amount of time required to optimize the disk.

In addition to VOPT, the disk comes with several utility programs, including one (VMAP) that provides a graphic display of your hard disk's sector usage. Figures 1 and 2 show the displays provided before and after running VOPT on a 20-megabyte hard disk (a Seagate ST-225) installed in an IBM PC XT, a process that took about 2.5 minutes, rather than the 25-40 minutes required by other similar programs.

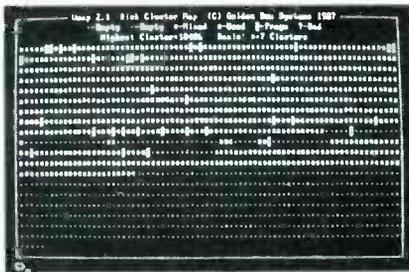


FIG. 1

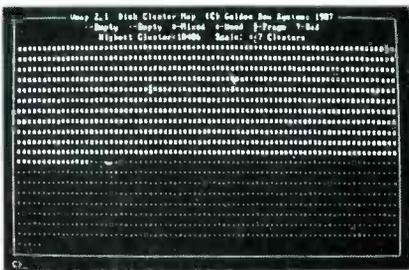


FIG. 2

Golden Bow also markets a quality disk-caching program, VCACHE, and a hard-disk partitioning program called VFEATURE that allows you to create bootable partitions larger than the 32-megabyte limit imposed by DOS.

BASIC 6.0

Microsoft just released a slew of languages (BASIC, assembler, Pascal, FORTRAN, and C) that allow you to develop programs for both DOS and OS/2. BASIC 6.0 is a complex hybrid product that includes the QuickBASIC 4.0 environment for developing DOS programs interactively, as well as a command-line compiler that both runs under and produces code for both DOS and OS/2 environments. The only problem is that the compiler cannot take full advantage of some of the advanced features of OS/2, such as multiple processes in the same program.

Fortunately, versions of CodeView, Microsoft's windowing debugger, are in-

cluded for both environments. Unfortunately, however, QuickBASIC doesn't run under OS/2 (yet).

The programs are supplied on nine 360K diskettes, and are accompanied by about six inches of spiral-bound documentation. It's possible to run various portions of the package from a floppy-only system, but you'll really want a hard disk for convenience. To store everything you'll need almost three megabytes of space; you won't need all files if you're just going to use QuickBASIC, for example, or just the OS/2 development tools.


This author gave up on BASIC as a serious programming tool long ago, but QuickBASIC could change his mind. There are several reasons for that. For one, the language doesn't require line numbers, and it allows named procedures (subroutines). In addition, it contains a built-in debugger that allows you, for example, to keep a watch on one or more variables while a program is running. Further, its built-in editor is infinitely better than that supplied with GW-BASIC. An especially nice feature is that, many times, you can modify a program (not just a variable, as in GW-BASIC) and continue running it without recompiling. Last, file facilities that allow for binary records allow you to create Pascal-like records. No more FIELD, LSET, etc!

For use with the command-line compiler (BC.EXE), BASIC 6.0 also includes a configurable text editor (M.EXE) from which other programs—including BC, of course—can be run. That ability is no replacement for the integrated Quick environment, but it helps.

You can buy QuickBASIC separately for considerably less money, but with BASIC 6.0 you also get the command-line compiler and editor, and versions of CodeView for both DOS and OS/2. So you could use QB to develop, say, the interactive portions of programs, and BC to compile (and CodeView to debug) the "meat." Also, don't forget that under OS/2, you can run multiple programs simultaneously, so you could run BC—even several copies of it—in the background, while at the same time editing another file in the foreground.

If you're looking for a simple way (i.e.,

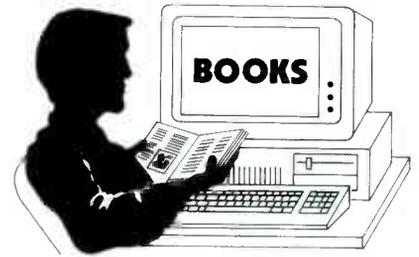not with C or assembler) of easing into OS/2 programming, BASIC 6.0 is what you need. It combines a wealth of programming tools for both old and new environments, all at a reasonable price.



Customizing AutoCAD

AutoCAD has developed a cult following for a number of reasons, not the least of which is its ability to be thoroughly customized. (See the April 1988 issue for a review of the current version.) You can customize the program's on-screen menus to provide you with a subset of commands that fit your particular application. In addition, using AutoCAD's built-in LISP-like language, you can program special functions to do just about anything you like.

The problem is that Autodesk's documentation on customization is sparse. So New Riders Publishing decided to show us how to do it. The result is a big (8½ x 11), thick (600 pages) book written by Joseph Smith and Rusty Gesner that covers just about every imaginable (and several unimaginable) aspect of customizing AutoCAD. The book teaches you all about menu customization and working with LISP. The book does not, however, inundate you with much detail all at once; rather, it presents information to you in well-chosen and easily manageable chunks, gradually building on earlier concepts.

Along the way, it teaches how to best use DOS (subdirectories, etc.), interfacing with Lotus 1-2-3 and dBASE, and more.

In short, if you're seriously into AutoCAD, you need a copy of *Customizing AutoCAD*, to help you get the absolute most from your system.

PRODUCTS REVIEWED

- AutoSwitch Monochrome EGA (\$249) and VGA Plus Card (\$399), Paradise Systems, Inc., 99 South Hill Drive, Brisbane, CA 94005. (415) 468-7300.
- Mothercard 5.0 (12.5 MHz, \$995; 10 MHz, \$895), SOTA Technology, 657 N. Pastoria Ave., Sunnyvale, CA 94086. (403) 245-3366.
- GrandView (\$295), Symantec Corp., Living VideoText Division, 117 Easy Street, Mountain View, CA 94043. (415) 964-6300.
- Excel (\$495), Microsoft 16011 NE 36th Way, Redmond, WA 98073. (206) 882-8080.
- Hijaak (\$89), Inset Systems 12 Mill Plain Road, Danbury, CT 06811. (800) 828-8088, (203) 794-0396 (CT).
- VOPT (\$49.95), Golden Bow Systems, 2870 Fifth Ave., Suite 201, San Diego, CA 92103. (619) 298-9349.
- BASIC 6.0 (\$295), Microsoft Corp., 16011 NE 36th Way, Redmond, WA 98073. (206) 882-8080.
- Customizing AutoCAD (\$34.95, disk with AutoLISP routines, \$29.90), New Riders Publishing, P.O. Box 4846, Thousand Oaks, CA 91360. (818) 991-5392.

BUILD A SYNERGY CARD FOR YOUR PC

Tap your hidden potential!

Jeff Wiley & R. D. Warner

In our society, we tend to over-emphasize analytical, linear thinking, and under-emphasize intuitive, symbolic approaches. However, we short-change ourselves when we do. The best scientific achievements have something "artistic" about them, and the best artistic achievements have something "scientific" (organized or structured) about them. Systems design and analysis, for example, requires one to retain an image of the overall system while simultaneously being able to break that system down into its component parts.

To help you learn to maximize both analytical and intuitive types of skills, we're going to describe the construction of a device, called the Synergy Card, that plugs into any IBM PC or compatible with an eight-bit slot. The Synergy Card works by generating computer-controlled sound waves that put your brain into a state that is more conducive to both learning and creating. The Synergy Card can also be used to create various sound effects. The card can be built for under \$100; assembled and tested versions are also available. See the sidebar for more information.

Because of the controversial nature of the technique, we'll spend most of this first article describing basic terms, background research, and philosophy. Next time we'll build the card itself and show you how to use it.



Background

Research has taught us much about how the human brain works. Using machines such as the *Electro-EncephaloGraph* (EEG) and the *Superconducting Quantum Interference Device* (SQUID), researchers have discovered that there is a division of labor between the sides of the brain. The left hemisphere is predominantly analytical, linear, and verbal. By contrast, the right hemisphere is intuitive, creative, visual, and symbolic. Throughout the course of the day, we shift from one hemisphere to the other, depending on the task at hand. When speaking or balancing a checkbook, the highest brainwave amplitudes are in the left side. When painting or listening to music, the right side becomes most active.

Another discovery revealed that certain psychological and physiological states were associated with certain ranges of brain waves. That discovery led to the development of bio-feedback techniques. With the proper techniques, a person could learn to produce alpha or theta brainwaves, and thereby experience the physical and mental states associated with them.

A technique that, unlike biofeedback, requires no learning by the subject has been developed by Robert Monroe, presently of *The Monroe Institute* (TMI) in Faber, Virginia. In the late 1950's, Monroe began investigating methods of accelerated learning, which led to remarkable discoveries about the nature of human consciousness. For example, Monroe found that regular sound waves at brainwave frequencies could induce the brain to produce brainwaves of a similar frequency. That phenomenon is called a *Frequency-Following Response* (FFR). The important thing about FFR is that, given the correct frequencies, one could enjoy the physical and mental states associated with those frequencies.

Because most brainwave frequencies are quite low, "beat" frequencies are used to generate them. The way they're generated is unusual, though, because the actual beat frequencies are synthesized by the brain instead of being heard normally. To understand how it works, imagine listening through headphones to two distinct signals. A 200-Hz signal is fed to one side, and a 205-Hz signal to the other. Those signals are not being mixed electrically, nor are they mixing in the air. Nevertheless, you will hear a distinct 5-Hz beat frequency, which is created in your brain. The way it works is that the two brain hemispheres synchronize to synthesize the beat signal. That process was dubbed *Hemi-Sync* (for hemisphere synchronization) by Monroe. We'll call it HS.

In that example, if you were being monitored with an EEG, it would trace a 5-Hz brainwave, and the amplitudes of the signals from both hemispheres would gradually become equal.

Which signals produce desirable physiological and

psychological responses? TMI was founded in 1971 to answer just that question. Thousands of experiments with volunteers led to the development of certain combinations to produce specific responses. For example, a frequency of about 4 Hz can produce theta waves, which are associated with deep relaxation and high receptivity. By itself, theta waves may produce drowsiness, but when combined with beta waves (which are associated with concentration and alert problem solving), you have an excellent mental state for learning, retention, and problem solving.

Case studies

A philosophy professor at the Tacoma Community College in Washington has been using HS signals combined with music in his classes since 1978. The professor spends less time on housekeeping and department tasks; students are more relaxed, cooperative, and interested in learning; and student performance is enhanced.

In another study, HS (delta, theta, and beta) was mixed with music and played in 24 second- through fifth-grade classrooms. Teachers reported that students had more highly focused attention, were more interested in learning, and were able to learn more material in a given period of time. The general classroom atmosphere was one of relaxed attentiveness.

Dream research

HS also looks useful for dream research. In fact, HS was developed mainly as a way to maintain a state conducive to lucid dreaming, so that dreaming could be studied in a more consistent manner. That fascinating phenomenon has potential as a psychological and creativity tool, and as entertainment. In fact, HS has been used to develop techniques that can teach you how to increase dream awareness, and how to dream with finesse.

Sleep research has shown that in REM sleep (the period when most dreams occur) the right hemisphere is much more active than the left. That's understandable based on what we said before, because dreams are usually pictorial, emotional, and illogical, and the right side of the brain is the home of such states.

In order to become lucid in a dream, it is necessary to increase activity in the left hemisphere. The effect of hemisphere synchronization seems to be that it allows one to carry more left-brain critical-analysis functions into dreaming. Much of what we've said about HS and dreaming is speculative, but the authors can personally attest that HS helps induce lucid dreaming.

Hardware introduction

The Synergy Card is built around two 8255A parallel interfaces, three AY-3-8910 Programmable Sound Generators (PSG's), and a stereo amplifier suitable for driving headphones or the line-level inputs of your stereo system.

Because sound generation is done with hardware rather than software, the control software is easy to write. The hardware approach also provides much greater control over the sound envelope generated by the Synergy Card. In addition, it also frees the CPU for other tasks. For example, the CPU can give the card the necessary parameters, and then go off and monitor biofeedback equipment, altering the signal mix based on the information provided by that equipment.

ORDERING INFORMATION

The following are available from Perceptual Research Ventures, P.O. Box 201516, Missoula, MT 59801: Etched, drilled, tin-plated, and silk-screened PC board (PR-10), \$36.00; assembled, tested, and conformal-coated card (PR-48), \$319.95 (for research organizations only); custom cabling (PR-8), \$28.95; Sleep Lab software, compiled, runs card as a background task, leaving CPU free for other work, (PR-100), \$29.95. Add \$5 for postage and handling.

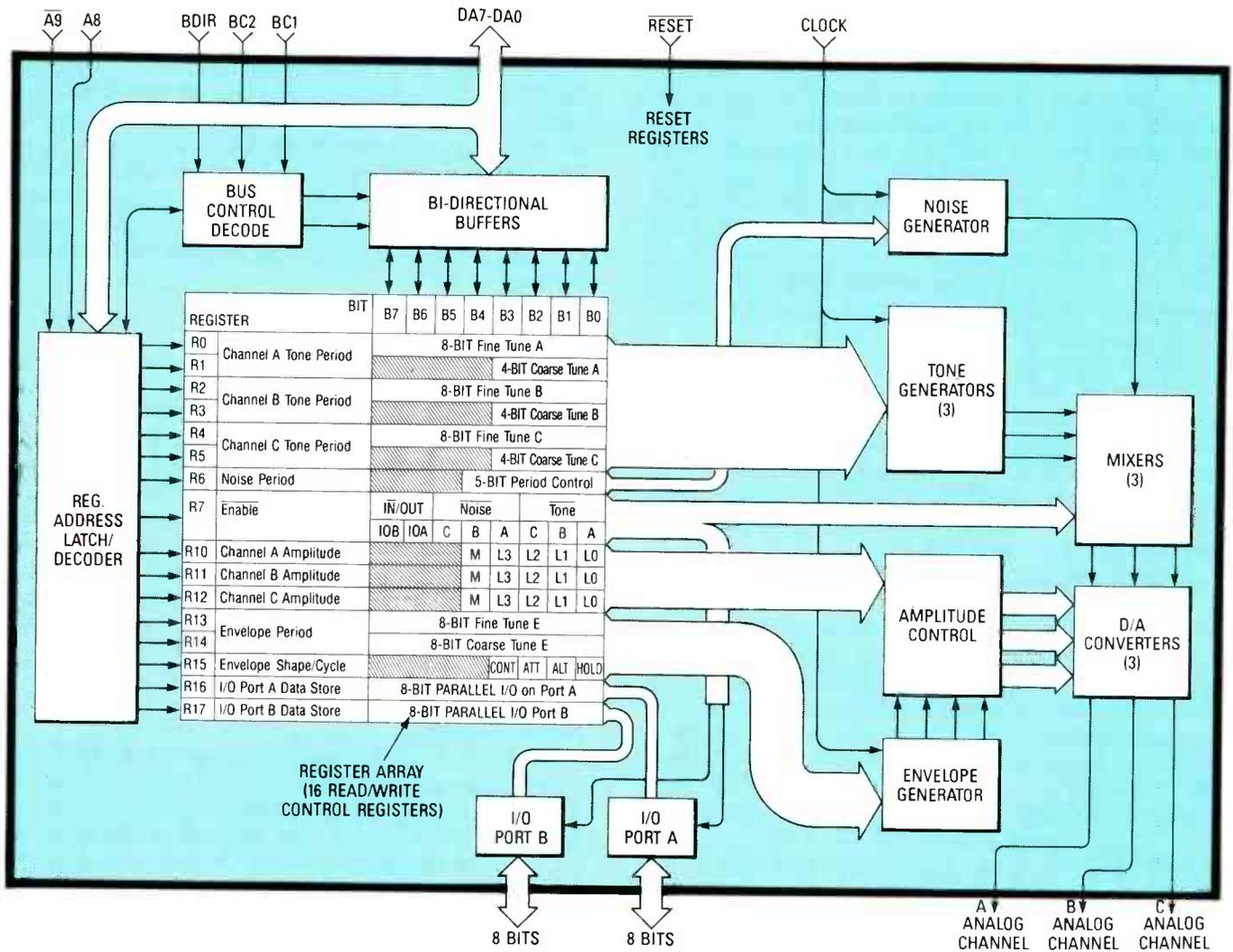


FIG. 1—THE PROGRAMMABLE SOUND GENERATOR has sixteen registers that control the operation of a noise generator, tone generators, and the frequency and amplitude of the resulting waveforms.

Figure 1 shows a block diagram of the PSG. As you can see, each PSG has three analog outputs and 16 digital I/O lines. Each of the three analog outputs has its own tone generator; the output of a single noise generator (if enabled) may be mixed with one or more outputs. The amplitude of each output may be fixed or variable, depending on the state of the envelope generator. The output of each mixer is fed through its own four-bit (sixteen-level) D/A convertor. The analog outputs of the IC have maximum amplitudes of 1 volt pk-pk.

All operational parameters are specified by a set of sixteen registers. Output frequency, for example, is determined by the contents of registers R13 and R14, which are the fine and coarse envelope period control registers. Here is the formula for determining output frequency:

$$F_O = F_C [16 \times (256 \times C_T + F_T)]$$

F_O is the desired frequency, F_C is the clock frequency, C_T is the contents of the coarse-tune register, and F_T is the contents of the fine-tune register.

Control software must be able to calculate C_T and F_T ,

given a desired output frequency (F_O). (Clock frequency F_C is set at 1.8432 MHz.) For example, to obtain a 200-Hz tone, plug in the known values and re-arrange the equation as follows:

$$200 \text{ Hz} = 1843200 \text{ Hz} / [16 \times (256 \times C_T + F_T)]$$

$$200 \text{ Hz} = 1843200 \text{ Hz} / (4096C_T + 16F_T)$$

$$4096C_T + 16F_T = 1843200 \text{ Hz} / 200 \text{ Hz}$$

$$4096C_T + 16F_T = 9216$$

$$C_T = 9216 / 4096 = 2$$

$$F_T = 1024 / 16 = 64$$

C_T is calculated first, and then F_T is determined from the remainder. The reason is that the PSG views the eight-bit fine-tune register and the four-bit coarse-tune register as representing one twelve-bit number. So you really aren't solving the equation for two unknowns, but one that is broken down into most-significant and least-significant parts that fit into the two registers.

Next time we'll present the complete circuit, discuss how it works and how to build it. \blacklozenge

BUILD THE PT-68K

This time we install hard- and floppy-disk controllers, and a parallel port.



Copyright (C) 1988 by Peter A. Stark

PETER A. STARK

We tend to look in awe at the floppy-disk circuitry of a computer, but actually it is very simple, mainly because the most complex parts are hidden in a dedicated IC known as the *Floppy Disk Controller* (FDC).

Step 21: Floppy-disk controller

Figure 1 shows the floppy-disk circuit used in the PT-68K. The heart of the circuit is the WD1772 FDC, which connects to the lower eight bits of the data bus, to address bits A1 and A2, to the \overline{RW} line, to the \overline{RESET} line, to the $\overline{I/O4}$ select line from the address decoder, and to the 8-MHz clock signal ($CLK8$).

The $\overline{I/O4}$ line comes from IC34 in the address decoder (shown in Fig. 3 in the January 1988 installment). It goes low whenever the 68000 accesses any location \$FE0100–\$FE013F, and thus selects the FDC whenever the 68000 reads or writes any address in that range. However, because only the lower eight bits of the data bus go to the FDC, only odd addresses in that range actually are used to transfer data.

Internally, the CPU-side of the FDC is organized into six byte-size registers, two of which the 68000 can either read or write. Two others can be read but not written, and the remaining two can be written but not read. The 68000 selects which register it is reading or writing by (a) making the \overline{RW} line high for reading or low for writing, and (b) putting the appropriate bit pattern on address lines A1 and A2.

The values of those two bits depend on the address (in the range from \$FE0100 through \$FE013F) that the program accesses. For example, writing to location \$FE0103 makes \overline{RW} low and puts the bits 01 on A2 and A1 respectively. (Remember that the 3 at the end of \$FE0103 is the bit pattern 0011; the middle two bits of this pattern correspond to A2 and A1, respectively.) The six registers appear at the addresses shown in Table 1.

Each register has a specific job. The Control register, for example, tells the floppy-disk drive to move the read/write head to a specific track, to read or write a specific sector, or to format a track. (See the December 1987 and January 1988 issues for more on tracks and sectors, and the sidebar here entitled “SK*DOS Disk Organization” for information on how SK*DOS stores information on disk.)

The FDC presents the results of various operations in the Status register, where each bit has a function: indicating that the FDC is busy, that it is waiting for data, that the disk is write-protected, or that an error has occurred.

The 68000 tells the FDC where to read or write by placing the track and sector number into the Track and Sector registers.

Last, the 68000 places data to be written on the disk into the Write data register, or reads data from the disk in the Read data register.

Although the FDC handles most of the housekeeping involved with reading and writing floppy disks, there are several tasks it does not handle: choosing one of several drives, choosing a specific side of a double-sided disk, and choosing single- or double- density format. All three tasks are handled by IC11, a quad latch.

As shown in Fig. 1, the four data inputs of IC11 connect to bits 0, 1, 5, and 6 of the data bus, and the IC's CLK input connects to $\overline{I/O3}$. Like $\overline{I/O4}$, $\overline{I/O3}$ comes from IC34 in the address decoder, but $\overline{I/O3}$ is pulsed whenever the 68000 reads or writes locations \$FE00C0—\$FE00FF. Specifically, any time the 68000 stores a byte into location \$FE00C1, IC11 is clocked and the data present on bits 0, 1, 5, and 6 of the data bus is stored in IC11.

The outputs of IC11 are used as follows: bits 0 and 1 go to IC12, a decoder that selects one of four drives; bit 5 goes to the \overline{DDEN} input (pin 26) of the FDC to choose single or double density; bit 6 is buffered by IC22-a and is used to select the side.

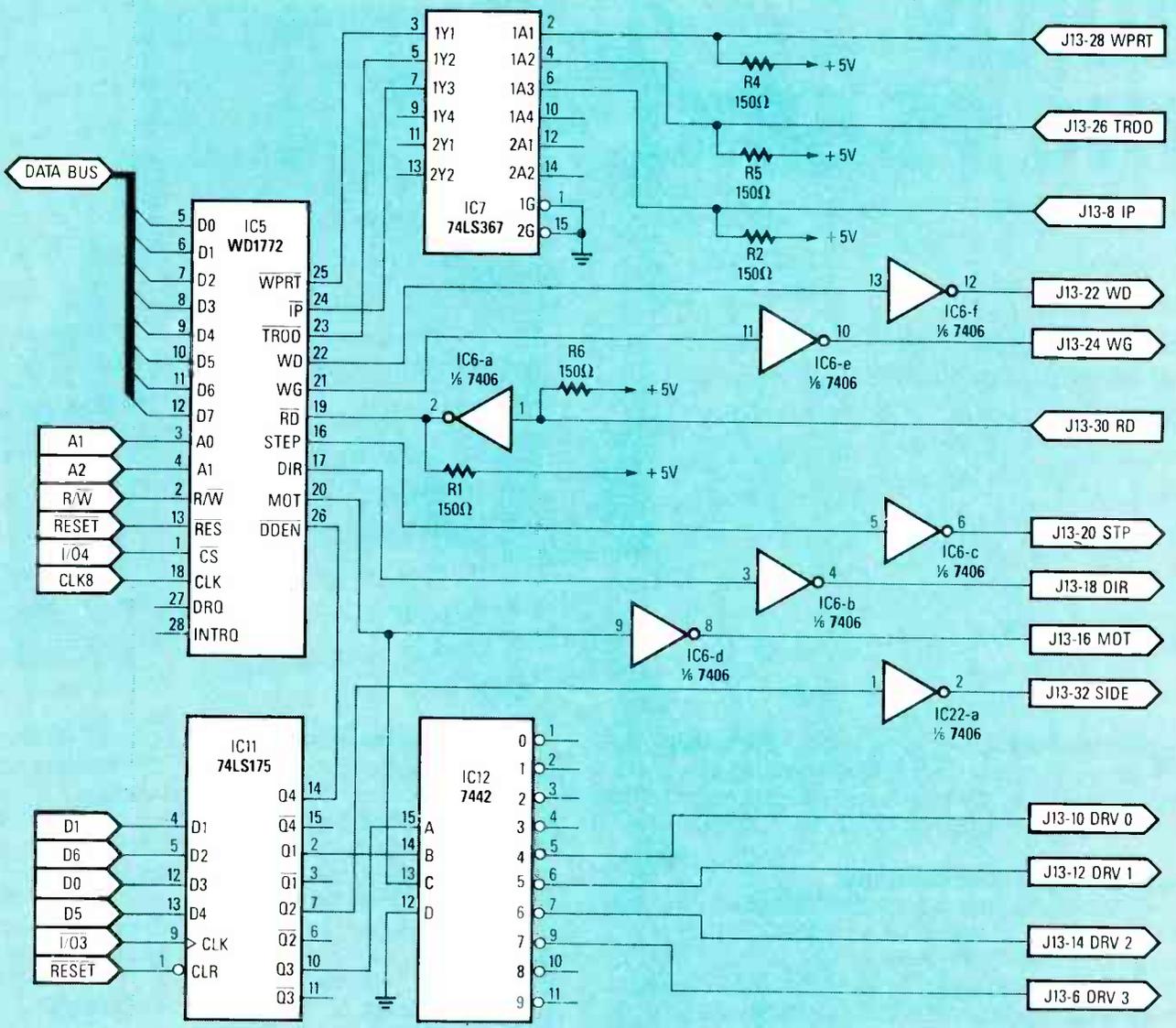


FIG. 1—FLOPPY-DISK CONTROLLER: IC5 does the real work; IC11 and IC12 select drive, disk side, and disk density.

TABLE 1—FDC REGISTERS

\$FE0101	Write only Control register
\$FE0101	Read only Status register
\$FE0103	Read/Write Track register
\$FE0105	Read/Write Sector register
\$FE0107	Write only Write data register
\$FE0107	Read only Read data register

Last, let's look at the connections to the disk drives themselves. Disk drives connect to the PT-68K through a 34-wire flat cable that plugs into J13. All odd-numbered pins of the cable are grounded; the even-numbered pins carry signals to and from the drives. Physically, all the odd pins are on one side of the connector, but in the cable, the odd-numbered wires, alternate with the even-numbered wires. Therefore there is a ground between each adjacent pair of signal-carrying wires, reducing noise pickup.

There is only one 34-conductor cable, even when there is more than one disk drive. So each drive receives all signals from the computer. A specific drive is selected through use of the DRV0-DRV3 signals. For example, to access drive 0, the PT-68K places a low on DRV0, meanwhile keeping the other three lines high. In that way, when a command or data is sent down the cable, only the selected drive actually obeys.

The signal wires themselves can be divided into three types: data, control, and status signals. The data lines carry serial data to and from the drives. The computer uses the control lines to tell the drive what to do. And, the status lines tell the computer the results of various operations.

The two data lines are RD for Read Data, and WD for Write Data. Although data on the data bus travels in parallel, the FDC contains shift registers that convert parallel data (that comes from the bus) to serial form (that goes to the drive), and vice versa. The FDC also adds clock pulses to ensure that the data on the disk is properly timed and can be read back correctly. In single density, a clock bit follows every data bit; in double density, clock bits are inserted

only between consecutive zero bits. Reducing the number of clock bits is what allows double-density operation to store more bits per track.

Several signals control the operation of the drive. We already discussed the four *DRV* signals, which select a particular drive; and the *SIDE* signal, which selects a particular side of the disk. Other control signals include Write Gate (*WG*), which goes low to tell the drive to switch from reading to writing; (Step *STP*), which tells it to move the read/write head to the next track; Direction (*DIR*), which tells it which direction to move the head; and Motor (*MOT*), which tells it to turn the motor on.

Actually, *MOT* controls all drives, so even unselected drives turn their motors on and rotate the disk when *MOT* is asserted.

The *STP* signal is so named because floppy drives use a *stepper motor* to move the head from track to track. A stepper motor has a ratchet-like motion, whereby the head aligns itself over a track correctly each time the motor clicks into position. In that way, the head is positioned precisely by the motor with no help from other potentially problematic mechanical devices.

Last, there are three status signals, all of which are usually derived from photo-electric sensors in the drive. A drive sends back a low on the Write Protect (*WPRT*) line when the write-protect notch on the disk is covered. The drive sends back a low on the Track 0 (*TR00*) line when the head is positioned over Track 0, which is the outermost track on the floppy disk. Note that the FDC has no easy way of knowing which track the head is positioned over—it keeps track of head position by sensing track 0 and then keeping a count of the *STP* step pulses as the head moves in and out.

The drive senses the beginning of the track by sending a beam of light through a small hole in the disk called the *index hole*. That light is sensed once per revolution. When a disk is rotating, the Index Pulse (*IP*) goes low every time the beginning of a track comes under the read/write disk-drive head.

The FDC uses the index pulse in several ways. In normal operation, the presence of the signal tells the FDC that there is a disk in the drive and that the door is closed (otherwise the disk would not turn). In addition, when a disk is being formatted, the index hole tells the FDC where to begin and end each track. Also, when the FDC encounters a disk error, it uses *IP* to count the number of times it retries the failed operation before giving up.

A word or two about 40- and 80-track drives. An 80-track drive can read 40-track disks by a process called double-stepping, in which the drive takes two steps of $\frac{1}{8}$ " to traverse the $\frac{1}{4}$ " spacing between tracks on a normal 40-track disk. In fact, SK*DOS automatically tries double-stepping when it encounters a disk error, so reading a 40-track disk in an 80-track drive is totally invisible to the user.

However, the reverse is not true—although SK*DOS can write a 40-track disk in an 80-track drive, it often happens that the disk is unreadable in a 40-track drive. The reason is that the tracks on an 80-track disk are not just closer together, they are also narrower. So when an 80-track drive writes on a 40-track disk, it does not write over the full track width, and some of the original 40-track data may remain around the edges of the track. Then, when a 40-track drive tries to read the disk, it reads the new data

SK*DOS DISK ORGANIZATION

Although a double-density track can theoretically hold almost 6000 bytes, in practice only 4608 bytes are used for actual data storage; the remaining bytes are wasted. On an IBM disk running MS-DOS, those 4608 bytes are divided into 9 sectors of 512 bytes each; on the PT-68K running SK*DOS, they are divided into 18 sectors of 256 bytes each. Sectors are numbered beginning with 1.

On an SK*DOS disk, track 0 holds system information; the remaining tracks hold program and data files. Sectors 1 and 2 of track 0 hold the superboot program, which is used when starting (booting) the system. Sector 3 is called the System Information Sector (*SIS*) because it stores system information such as how much of the disk is free. Sector 4 is used for testing purposes, and the disk directory begins with sector 5. If more space is needed for the directory, then it may be continued in other sectors of track 0.

Each file on the disk has an entry in the directory that contains the file's name, size, time and date of creation or last update, location on the disk, and a one-byte attribute that provides further file information. The location of the file is specified by the track and sector where the file begins, and the track and sector where the file ends.

Because only the beginning and ending locations are specified in the directory, additional information indicating where to find the rest of the file is contained within the file itself. The first two bytes of every sector in the file contain a pointer to the next sector of the file, in the form of another track and sector number. The linked sectors form a chain-like structure, so this type of disk organization is called a linked chain system.

The free space on the disk is treated like a file (i.e., as another linked chain of sectors), whose beginning and ending locations, as well as size, are stored in the *SIS*, sector 3 of track 0.

As SK*DOS creates or deletes files, it simply moves sectors between chains. For example, when a file is deleted, its name is removed from the directory, and its sectors are added to the end of the chain of free sectors. One neat side-effect of this system is that, if there is enough free space on the disk, these sectors may not be overwritten for some time. It is therefore possible to recover a deleted file, sometimes days or weeks later, depending on how the disk has been used. SK*DOS is supplied with such an *UNDELETE* program.

as well as some of the old. Depending on the exact track positioning and other factors, it may then misread the disk and fail.

Build the floppy controller

Enough theory; let's warm up our soldering irons. Install the following components, using sockets for all IC's: IC5 (WD1772), IC11 (74LS175), IC12 (7442), IC7 (74LS367), IC6 (7406). Then install 150-ohm, $\frac{1}{4}$ -watt resistors at R1, R2, R4, R5, and R6, and a 0.1- μ F ceramic disk at C6 (if it's not already installed). Last, install J13, a 34-pin dual-row header strip.

Just about any $\frac{5}{4}$ " disk drive will work with the PT-68K, but a double-sided, 80-track drive is preferable, because it holds more data. Note that the SK*DOS disk operating system is normally supplied on 80-track double-sided disks unless you specify otherwise.

The next task is to make sure that the jumpers on the drive are properly set. As described above, selecting one of four possible drives is done by the four *DRV* lines.

Although all four lines go to each drive, only one DRV signal is actually used by any single drive.

Figure 2 shows a simplified diagram of the jumpers that control drive selection on a typical floppy drive. As you can see, the four DRV signals appear on pins 6, 10, 12, and 14 of the 34-pin connector, and go to a set of jumpers usually called DS0–DS3, although sometimes they are labeled DS1–DS4. When one of those jumpers is installed, the corresponding DRV signal goes to the Drive Select line of the drive itself.

To use a drive with the PT-68K, you must make sure that it has only one Drive Select jumper installed. In some drives, the connections are made through a shorting plug installed in an IC socket; in that case, you may have to break three of the four connections on the shorting plug (or install a small DIP switch instead of the shorting plug). In other cases, you may have to move a jumper from one of the other positions into DS0. Many floppy drives currently sold for use in IBM PC's and compatibles have the DS1 jumper installed, because drive selection in IBM's is done by flipping wires in the 34-pin cable, rather than by moving jumpers on the drive.

In a single-drive system, the jumper would be installed on DS0 (or DS1 if your drive's numbering scheme starts with 1). If you install more than one drive, place each DS jumper in a successively higher position.

In addition to moving the DS jumpers, you should also remove the MUX (or MX) and HM jumpers if installed, and install a jumper in the HS position. MUX is used to select a drive permanently for those computers that don't provide DRV signals. HM and HS jumpers control the Head Load signal in those drives that use a solenoid to move the read/write head against the disk. Installing the HM (Head with Motor) jumper would bring the head against the disk as soon as the motor turned on, whereas installing the HS (Head with Select) jumper only brings the head against the disk if the drive is selected.

A word about terminating resistors. In order to minimize noise, each signal-carrying wire must be terminated at the drive with a resistor. A drive usually has a small

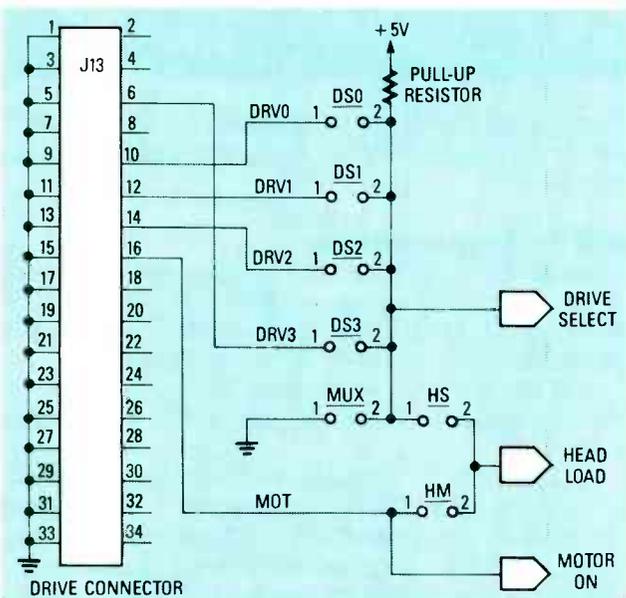


FIG. 2—DRIVE-SELECT CIRCUITRY: Typical floppy-disk drives have a header block for selecting the disk-drive number that the drive will respond to.

FURTHER HELP

For further help, contact us through our BBS at (914) 241-3307. Hardware questions can be answered by Peripheral Technology, 1480 Terrell Mill Rd. #870, Marietta GA 30067, (404) 984-0742. Software questions dealing with HUMBUG and SK*DOS can be answered by Star-K Software Systems Corp., P. O. Box 209, Mt. Kisco NY 10549, (914) 241-0287.

Ordering Information

Complete details were given in Part One (in the October 1987 issue). To summarize: the basic kit (PT1, \$200) contains all parts except power supply, case, and video terminal or personal computer to get a small system (ROM monitor, 2K RAM) up and running. The full basic system (PT-68K, currently \$530 but the price may vary as DRAM prices change) includes 512K of dynamic RAM, floppy-disk controller, parallel port, battery-backed clock/calendar, three PC-compatible expansion slots, SK*DOS, editor, assembler, and system utilities. To order, or for more information, contact Peripheral Technology, 1480 Terrell Mill Road #870, Marietta GA 30067, (404) 984-0742.

resistor pack that provides termination. To avoid overloading when more than one drive is installed in a system, only the drive at the end of the cable should have its resistor pack installed. If there is no terminating resistor pack, or if there are two or more, the disk system may be unreliable, so check each drive in your system.

Then connect the four-pin power plug to the power supply, and connect the 34-pin data cable between the computer and disk drive. Pin 1 of J13 is toward the back of the board, and the pin 1 end of the connector is marked on most disk drives with a small notch between pins.

Now insert a blank disk into drive 0 and turn on the power. When HUMBUG is running, examine the disk drive to check that the motor is off and the drive select LED on the face of the drive is off. If either of those is on, the 34-pin cable may be reversed at one end.

Now type the HUMBUG command *FD* (Floppy Disk). The drive still contains a blank disk, so it cannot boot SK*DOS; even so, the drive motor should start and the drive-select LED should light. If the motor comes on but the LED does not, the DS jumpers may not be properly placed. Don't continue on until the motor and the LED behave properly.

When all seems well, reset the computer, remove the blank disk, place a write-protect strip on your SK*DOS system disk, and place it in the drive. Then type *FD* again.

If all goes well, the disk drive should start, the drive select LED should go on, the head should go back and forth a few times, and in a few seconds the SK*DOS sign-on message should appear. Congratulations—your system is working and almost finished!

Drive debugging

If not, then a bit of debugging is in order. First check the type of disk drive—a single-sided drive cannot read a double-sided disk, a 40-track drive cannot read an 80-track disk. If you are really quick, try to count the disk revolutions per second (rps). The disk should be turning at 5 rps, not 6. If it turns at 6 rps, it may be a 360-rpm 1.2-megabyte drive intended for an AT-type system; if so, you may be able to boot by switching jumpers, because

some drives of that type have a jumper to select either 300 or 360 rpm.

If the drive seems correct, use HUMBUG's FM command to fill all of memory from address \$0800-\$8000 with zeros, and then try the FD command again. After about 15 seconds, reset the system and use the HA command to look at locations \$0800-\$0900. If those locations still contain zeros, the disk system failed to read the disk. If an oscilloscope or logic probe is available, check that the *IP* and *RD* lines are normally high, but have negative-going pulses just after you type *FD*. If not, the disk may be in the drive backward, the disk drive may still not be properly selected, or it may be defective.

An easy way to check the drive is to remove the disk, turn off the power, then manually (and very carefully—it might be wise to ask a knowledgeable person for help!) move the drive's head carriage a half-inch toward the center of the disk, and then try again. As soon as you type the *FD* command, the FDC should step the head carriage outward toward track 0. If it doesn't, then either some of the control signals are not getting to the drive, or else they are being ignored.

If locations \$0800 and up are now non-zero, then *something* was read from the disk. Check whether the first few bytes at \$0800 are:

60 08 50 54 32

Those are the very first bytes read from track 0, sector 1 of the disk. If that data is correct, then the disk system is almost OK. The data read from this very first sector contains the first half of a program we call the *superboot*, which loads into locations \$0800-\$08FF. Once loaded via HUMBUG's *FD* command, *FD* then begins execution at location \$0800. The program loaded there then loads the next sector (track 0 sector 2) into memory beginning at location \$0900, so check whether the area from \$0900-\$09FF still contains zeros. If so, the second sector wasn't loaded.

The combination of those two sectors is supposed to load the *SK*DOS.SYS* system file into memory at location \$1000, and then start execution there. Look at locations \$0805 and \$0806; those two bytes should contain two non-zero numbers, which tell the program where to find *SK*DOS.SYS* on the disk.

Next, look at locations \$1000-\$1100. If those locations still contain zeros, then *SK*DOS.SYS* was not loaded. If the drive seems able to read the *superboot* program but fails to read *SK*DOS.SYS*, there may be a problem with the *STP* or *DIR* lines or circuitry such that the drive can read track 0 but not other tracks. The same symptom would also appear if you were using a 40-track drive to read an 80-track disk, or a single-sided drive to read a double-sided disk.

Last, look at locations \$4000-\$5000 or so. If that area still contains zeros, then an error may have occurred while reading the disk. A common problem is head alignment: The disk head may not be centered over a track. If you suspect that's the case, try a different drive or copy your *SK*DOS* system disk on another system and try the copy. (You can also copy *SK*DOS* disks with the Copy II PC Option Board on IBM hardware.) Alternatively, return your *SK*DOS* disk for exchange to either Peripheral Technology or Star-K Software.

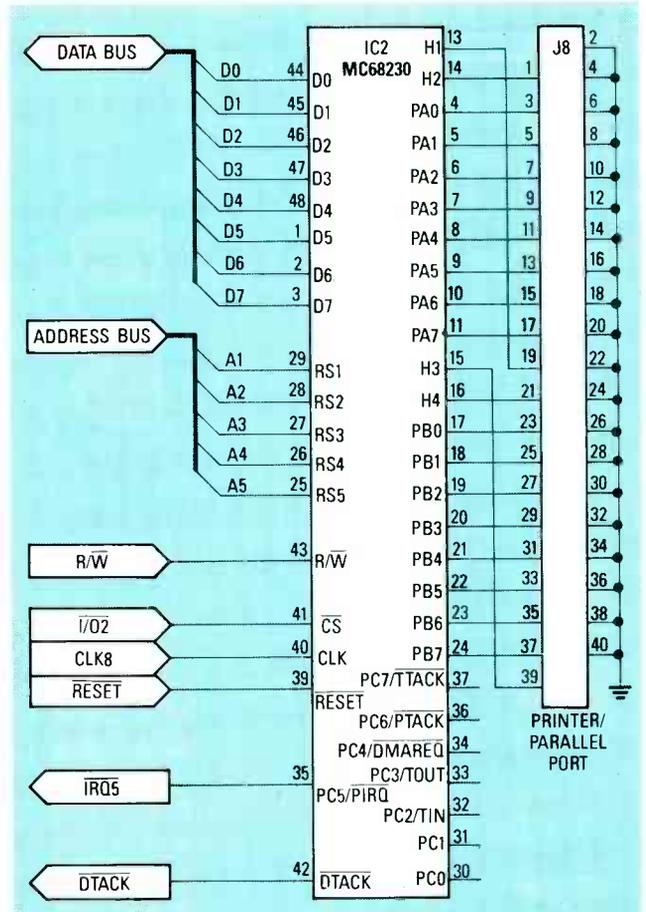


FIG. 3—PARALLEL PORT: IC2 has two full eight-bit ports and a counter/timer. Port A can drive a printer with standard Centronics parallel interface.

Step 22: The parallel printer port

There are several ways to connect a printer to the PT-68K. A serial printer can be connected to the serial port at J21. A parallel printer can be connected to either the printer port on an IBM-type monochrome video card, or directly to J8 on the PT-68K system board. All three are supported by *SK*DOS* drivers, and it is even possible to connect all three printers at once. Here we'll discuss installing the parallel printer port at J8.

As shown in Fig. 3, there isn't much to the port. In fact, the entire port consists of just IC2, an MC68230 Parallel Interface/Timer (PI/T), which is part of the Motorola 68000 family.

The 68230 consists of three main sections. Port A is an eight-bit input/output port consisting of the eight pins labeled PA0-PA7, along with two handshaking pins, labeled H1 and H2, that are used for sending control information. When used with a printer, pins 1-20 of J8 connect to a Centronics-compatible parallel-printer connector. The PA lines deliver characters to the printer, H2 tells the printer that a character is ready, and H1 lets the printer tell the PT-68K when it is busy.

Port B is a second eight-bit port that is similar to port A. Its control lines are H3 and H4. Port B is uncommitted, so you are free to use it for whatever you wish. When using port A to drive a parallel printer, don't connect anything to pins 21-40 of J8.

The third part of the 68230 PI/T is a timer consisting of a 24-bit counter that can count either CLK8 clock pulses or

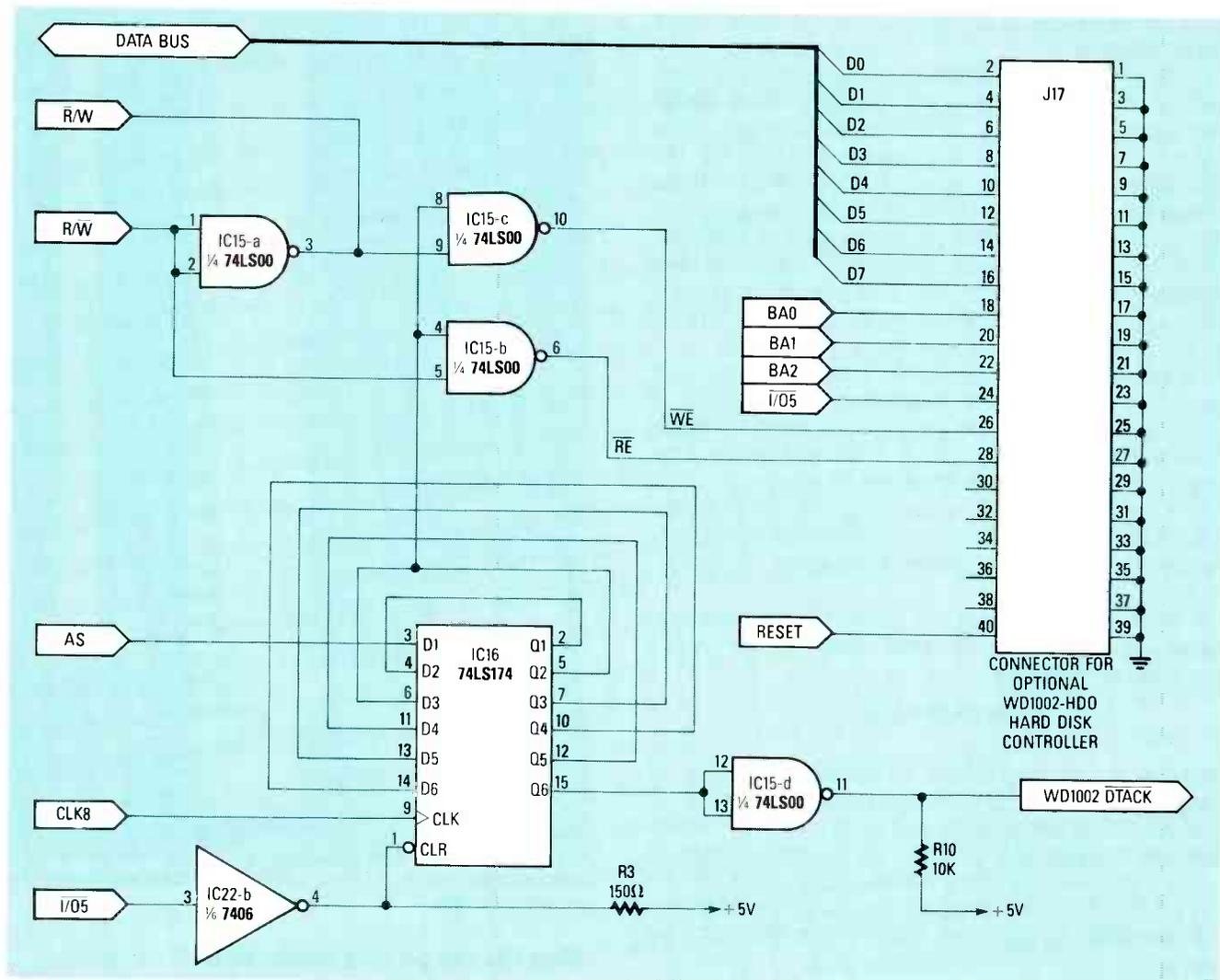


FIG. 4—HARD DISK INTERFACE: Use this circuit only if you're not using a hard-disk controller in one of the IBM expansion slots.

external pulses, generate square waves, generate interrupt signals to the computer at fixed time intervals, and various other functions. It is not used by PT-68K software, but it is available for custom applications.

The 68230 connections to the computer are similar to those of the floppy-disk controller. The 68230 receives the $\overline{IO2}$ signal from the address decoder, so it is selected whenever an address in the range \$FE0080—\$FE00BF appears on the address bus. Like the FDC, it contains a number of internal registers that are accessed at specific addresses, depending on the states of address lines A1–A5. However, there are too many registers and operating modes to describe here—Motorola publishes a 75-page manual on that IC alone!

Construction is simple; install the following components: IC2 (MC68230) with socket, J8 (40-pin header), and C2 (0.1 μ F ceramic disk).

Build the printer cable with 20-conductor flat cable; you may use a 20-pin connector at the computer end if you install it only in the pin 1 end of J8; otherwise, use a 40-pin connector. Place a standard Centronics printer connector at the other end, making sure that pin 1 of the Centronics connector connects to pin 1 of the other connector.

Step 23: Optional HDO hard disk controller port

The cheapest way to add a hard disk to your PT-68K is with a Western Digital WD1002-WX1 or -WX2 hard-disk controller (used in IBM XT's and compatibles). The controller generally costs about \$90, or can be obtained complete with a 20-megabyte disk and cables for under \$300.

However, to keep all their XT-type slots open for other purposes, some users may wish to use the Western Digital WD1002-HDO controller, which costs about \$250 (without a drive). The HDO hard-disk port is shown in Fig. 4; all others can simply skip this part since the HDO controller has no other advantages. (While both hard disk controllers can be installed at the same time, they require slightly different versions of SK*DOS and therefore cannot be used simultaneously.)

The HDO controller connects to the PT-68K with a 40-pin flat cable connected to J17. The controller needs the data bus and three bits from the address bus to select internal registers. Buffered address lines BA0–BA2, obtained from the XT-type interface connectors, are used. In addition, the controller needs $\overline{IO5}$, which selects the port at locations \$FE0140—\$FE017F, \overline{RESET} , and a pair of signals called \overline{WE} and \overline{RE} for write enable and read enable. \overline{WE} and

R-E Computer Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775. each. Closing date same as regular rate card. Send order with remittance to Computer Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Computer ads are accepted for this Admart.

Dynamic Electronics

23552
Commerce
Center Dr.
Suite L
Laguna Hills
CA 92653

Stocking Distributor of Semiconductors

8087 • 5 • 8 • 10 MEG
80287 • 6 • 8 • 10 MEG
80387 • 16 • 20 MEG
256K • 64K • 128K • V20 • V30

Fast • Reliable • Everytime

Phone: 714-855-0411
Fax: 714-855-8504

No refund - exchange only - Exchange good for 30 days
unless manufacturer warranties merchandise longer.

CIRCLE 194 ON FREE INFORMATION CARD

ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)
QUANTITY ONE PRICES SHOWN FOR JUNE 14, 1988

OUTSIDE OKLAHOMA: NO SALES TAX

DYNAMIC RAM			
1Mbit	1048Kx9	100 ns	\$600.00
41256	1048Kx1	100 ns	36.25
41256	256Kx1	60 ns	16.00
41256	256Kx1	80 ns	15.30
41256	256Kx1	100 ns	14.50
51258	* 256Kx1	100 ns	15.50
41256	256Kx1	120 ns	13.25
41256	256Kx1	150 ns	11.75
41264	+ 64Kx4	120 ns	16.95
EPROM			
27C1000	128Kx8	200 ns	\$37.50
27C512	64Kx8	200 ns	14.95
27256	32Kx8	250 ns	7.50
27128	16Kx8	250 ns	6.95
STATIC RAM			
43256L-12	32Kx8	120 ns	\$16.50
6264P-12	8Kx8	120 ns	13.75

OPEN 6 1/2 DAYS, 7:30 AM-10 PM. SHIP VIA FED-EX ON SAT.

WE EXPORT ONLY TO CANADA, GUAM, PUERTO RICO & VIRGIN ISLANDS

SAT DELIVERY INCLUDED ON FED-EX ORDERS RECEIVED BY: THE SW AIR 5:13 PM FR: P:1 \$20.25 (1 lb)

MasterCard/VISA or UPS CASH CDD
Factory New, Prime Parts μ P80
MICROPROCESSORS UNLIMITED, INC.
24,000 S. Peoria Ave.
BEGON, OK 74421 (918) 267-4961

No minimum order. Please note that prices are subject to change. Shipping & insurance extra. \$ up to \$1 for packing materials. Orders received by 9 PM CST can usually be delivered the next morning, via Federal Express Standard Air at \$6.30, or guaranteed next day Priority One at \$10.25

CIRCLE 61 ON FREE INFORMATION CARD

WORDFORWARD PROFESSIONAL

The Industry Standard in document conversion.

- Two way conversions
- Preserves all formatting
- Fast and menu-driven
- Special "Smart" ASCII retains page formatting

\$149.00

Supports conversions between:

WordStar	WordPerfect	MultiMate
PFS: WRITE	PFS: First Choice	PFS: Pro Write
OfficeWriter	IBM Writing Asst.	Microsoft Word
Volkswriter	DCA/RFT	ASCII
XyWrite	EBCDIC	"Smart" ASCII
DisplayWrite	Navy DIF	

LAN Version \$299

Call 800-624-6107, Dept. R

MASTERSOFT, INC.
4621 N. 16th ST.
PHOENIX, AZ 85016

CIRCLE 195 ON FREE INFORMATION CARD

\overline{RE} are generated by IC15-b and IC15-c from the \overline{RW} signal and a port-select signal derived from IC16.

IC16 is a digital delay that is used to generate \overline{DTACK} . Each time the HDO port is selected by $\overline{IO\overline{S}}$ and \overline{AS} (Address Strobe) arrives, IC16 starts to shift \overline{AS} from stage to stage. After two $\overline{CLK8}$ clock pulses, it clocks IC15-b and IC15-c to generate either \overline{WE} or \overline{RE} , depending on the state of \overline{RW} . After six clock pulses, IC16 sends a pulse to IC15-d, which generates \overline{DTACK} .

If you're going to build this portion of the PT-68K, start by removing the jumper between pins 7 and 12 of IC15. When we installed IC15 (in Step 16, as part of the XT-bus connector circuitry), we connected the jumper to prevent IC15-d from generating a continual \overline{DTACK} , which would prevent the rest of the computer from working properly.

Then install the following parts: IC16 (74LS174) with socket, R3 (150 ohms, 1/4 watt), J17 (40-pin header). The other components (R10, IC15, and IC22) were installed in previous steps, so installation is complete.

Unless you have the HDO controller, there is no easy way for you to test this circuit, so we will leave it as is, and hope for the best.

Step 24: Loose ends

If you still have a test wire connected to pin 1 of J14, cut it very short and use it to jumper pin 1 to pin 2. We won't need the LED logic probe any longer; cutting that jumper restores the circuitry feeding the LED, thereby restoring the LED's operation.

Way back in Step 4, we installed three LED's at J15, J16, and J17. If you're planning to install the PT-68K in a cabinet with cutouts for LED's on the front panel, you may wish to

replace the board-mounted LED's with those on the front panel. Since the DISK LED at J16 is only used with the HDO hard disk controller, you will probably choose to leave it on the motherboard, but the POWER LED at J15 and the HALT LED at J17 might be useful on the front panel. If so, cut off the two LED's, leaving about 1/2" of each lead sticking up above the board. The two-pin connectors that most cabinets are supplied with for the LED connections will slip right over the LED stubs. If the LED's do not light, all you have to do is reverse the connectors.

Before mounting the motherboard in the case, examine it carefully to make sure that all solder joints are good, and that there are no suspicious joints that might cause problems a few months from now. Also make sure that all components are installed; look especially for capacitors or resistors you may have missed. The computer might work without a particular resistor or capacitor, but it might not be as reliable as it should be.

Conclusion

That brings us to the end of this series. Keep in mind that hundreds of other readers have built this project, and that they're all interested in learning more about the 68000 microprocessor and the PT-68K computer. If you come up with an unusual application for the computer, or with an interesting add-on to make it more useful or more powerful, let the editors know. They may ask you to write an article based on your idea.

If you built a PT-68K, send your name and address to Star-K Software Systems to be placed on their mailing list. A newsletter is mailed occasionally with information about improvements and updates.

Above all, enjoy using your 68000 system. \blacklozenge

AMPLIFIER

continued from page 44

shown. After that, install an RCA plug on the other end for PL1. Then install two short wires at the pads marked SPKR for the speaker. Continue by connecting a 6-inch wire between S1 and the power pads (unmarked). Finish up by connecting transformer T1 and fuseholder between S1 and the other unmarked pad. Snap a 1-amp slow-blow fuse into the holder when you are finished.

Note that if you substitute a standard filament transformer for T1, the wiring is a somewhat different, as shown in Fig. 6. Wire the transformer's secondary directly to the unmarked pads, then wire the primary to S1 and F1 as shown. Also, be sure to use a ¼-amp fast-blow fuse for F1.

All that is left to do now is to install the board in the cabinet with 4-40 hardware, using spacers between the cabinet and the board, as shown in Fig. 5. Now connect the speaker wires, attach the knobs.

Operation

Now set all controls fully counterclockwise. Plug the unit into a nearby AC outlet, then turn it on by advancing the treble control. You will hear a brief "pop" from the speaker, then silence if all is well. Turn up the volume and touch the center terminal of PL1. You should hear a hum. If you are successful so far, you should connect a signal source, such as a tuner, and adjust the controls.

If you have any problems, check some voltages. From ground, you should read about 17 volts on C22, 15 volts on C23, and 9.1 volts on D1. The collector of Q1 should read about 4.9 volts. Start troubleshooting where the voltages are seriously off. Integrated circuit IC1 is more difficult to check, but start by measuring the voltages on the SPKR pads with the speaker disconnected; expect 7.5 volts on each pad, and if that voltage is not present, try replacing IC1.

The project also works well from a 12-volt battery. Simply short out diodes D2, D3, and D4 with a jumper wire, and then connect the +12 volts through fuse F1 and switch S1 directly to the positive terminal of BR1. Wire the negative side of the battery to the negative terminal of BR1. **R-E**

NANOELECTRONICS

continued from page 52

lower than those used in conventional logic circuits. Therefore, quantum-effect devices will have to have current- and voltage-translation devices built into them to make the signal levels compatible with more conventional devices. Similarly, signals input to a quantum-effect device will have to be reduced to levels compatible with its operation. And, presumably, signals routed from one quantum-effect device through a PC trace to another quantum-effect device on the same board will also have to go through a translation process to push them along.

Tooling up for a new generation of quantum-effect devices will not be easy or cheap. However, in the end, the benefits will outweigh whatever obstacles may presently stand in the way. Future integrated circuits will permit us to place as many as a hundred switching devices in the space that is now required for just one. Power requirements will be reduced significantly, and switching speeds will increase. Indeed, sometime in the next decade, we may truly see the advent of the "supercomputer on a chip." **R-E**

IC TESTER

continued from page 86

cord. Install the completed board in the case, and make sure that the wire with the black clip goes to the "-" pad of J1.

Tester operation

Table 1 shows the settings of S2a-h. The settings depend on the pinout of the IC being tested, and whether the in-circuit tester is in the testing or analyzing mode.

Connect the power leads to the power supply of the board to be tested. Set the DIP switches to the in-circuit test position, as shown in Table 1. Install a known-good reference IC in SO1, and connect the IC test clip to the DUT. Now, press and release S1; if any LED's light, the IC is bad. Remove and replace any bad IC's that you find, and then observe the board's

operation. If the board works properly, we are now finished, and if not, we will need to use the monitor/analyzer feature to check the circuit.

To set the tester for analyzing, set S2-b on, and S2-h either on or off as your experience dictates. Also, install the 20-pin header in SO1 (with all pins shorted together). Closing S2-b provides a ground to the header in most cases. If, however, you are analyzing an IC with pin 10 grounded, open S2-b, and close S2-c.

Let's call upon your experience and knowledge of logic circuits to determine which IC's would be most likely to cause the symptoms that the circuit exhibits. A schematic and IC data sheets would, at this time, be helpful. The in-circuit tester is an instrument that can separate IC's that are definitely good from those that might not be. Remove and replace suspected IC's as necessary, but keep in mind, that it may be something other than an IC that's causing the problem.

As mentioned earlier, resistors R43-R60 may or may not be necessary. It depends on the type of circuit that is being tested. They may be needed when testing circuits with three-state outputs connected to a common bus, such as the data bus of a microprocessor, but not always. In fact, those resistors are so rarely required, that they are optional. LED's on the tester corresponding to these outputs may turn on during the time when the bus is floating. If that occurs, it can be overcome by using the resistors, or by holding S1 down during testing. If needed, they can be discrete resistors or resistor networks. Mount them on the pins of SO2 on the bottom side of the PC board. The ground for those resistors is provided by the jumpers through S2-h.

To use the tester as a logic monitor/analyzer, plug the 20-pin DIP header into SO1, and close S2-b. Connect the cable with the hook probes to SO2. The hook probe connected to pin 10 of SO1 is to be connected to a ground point on the board we are monitoring. That connects one side of all the comparators to ground. Now, connect the other probes to the points in the circuit that you wish to examine.

As mentioned earlier, S2-h will select the latched or non-latched mode. Generally, use the non-latched (S2-b closed) mode because the latched mode is used mostly to capture very short pulses. **R-E**

MARKET CENTER

FOR SALE

TUBES, name brands, new, 80% off list. **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

IS it true...jeeps for \$44 through the government? Call for facts! 1-(312) 742-1142, ext. 4673.

TUBES. "Oldest," "latest." Parts and schematics. SASE for list. **STEINMETZ**, 7519 Maplewood Ave., R.E., Hammond, IN 46324.

SOLAR battery chargers. Homes, RVs, boats. From \$30.00. Brochure. **SUN POWER**, Texas, Dept. 01B, P.O.B. 2788A, Freeport, TX 77544.

TESLA coils—Kirlian electrophotography—plasma bulbs...Free 1988 science plan catalog! **SCIENTIFIC**, Box 1054HRH, Duval, WA 98019.

GREAT buys! Surplus prices, ICs, linears, transformers, PS, stepping motors, vacuum pump, phototransistor, meters, Isase, **FERTIK'S**, 5400 Ella, Phila., PA 19120.

TWO-Way-Radio, PC computers, **Uniden** service. General Radiotelephone licensed technician. Catalog-**RAYS**, 2025 Moline, Ft. Worth, TX 76117 (817) 831-7717.

AIDS? Yes we have! Cable aids to help you. Zenith, Jerrold, Scientific Atlanta, Oak, Hamlins, much more. No Michigan sales! **HOTRONICS**, (313) 675-5834.

ATTENTION, are you looking for surplus test equipment volt meters, oscilloscope, etc. **J.B. ELECTRONICS**, 9518 W. Grand, Franklin Park, IL 60131, (312) 451-1750.

Multi-Channel Microwave T.V. Receivers



1.9-2.7 GHz Parabolic Dish 40+ dB Gain
LIFETIME WARRANTY
 Complete System \$99.95 (Shipping Incl.)
 Replacement Components
 & Expert Repairs Available
K & S ELECTRONICS Call now for same
 P.O. Box 34522 day shipping!
 PHOENIX, AZ 85067 (602) 230-0640
 VISA/MC/COD \$2 CREDIT ON PHONE ORDERS

RESTRICTED technical information: Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochures.** **MENTOR-Z**, Drawer 1549, Asbury Park, NJ 07712.

FREE power supply, connectors (\$8.95 value) with assortment #103 (February 1984 article) contains PCB, Toko coils, transistors, IC's, diodes. \$25.00. Five/\$112.50. Assortment #104 contains all other parts. \$10. Shipping \$2.00. **JIM RHODES, INC.**, PO Box 3421, Bristol, TN 37625.

COPYGUARD corrector restores rental movies. Connects between VCRs. Satisfaction guaranteed. \$59.95 plus \$4 handling. 1 (800) 338-8751.

SAVE/make \$1000's high technology insider secrets catalog \$2.00. Exotic parts, **LEEWARE**, Box 5636, Greensboro, NC 27435.

TUBES 59¢. Year guarantee. Free catalog. Tube checker \$8.95. **CORNELL**, 4215 University, San Diego, CA 92105.




TUBES - 2000 TYPES DISCOUNT PRICES!

Early, hard-to-find, and modern tubes. Also transformers, capacitors and parts for tube equipment. Send \$2.00 for 20 page wholesale catalog.

ANTIQUE ELECTRONIC SUPPLY
 688 W. First St. • Tempe, AZ 85281 • 602/894-9503

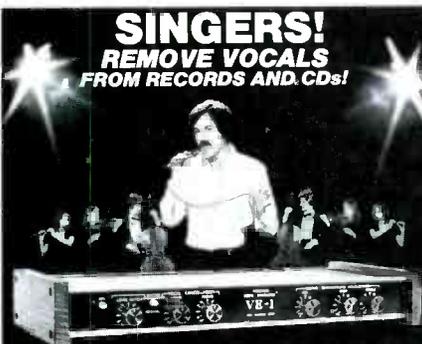CABLE TV decoders Jerrold, Scientific Atlanta, Zenith, most major brands. Dealer inquiries welcome. Visa-M/C accepted **E & O VIDEO**, 9691 E. 265th Street, Elko, MN 55020, 1-(800) 638-6898.



SING WITH THE WORLD'S BEST BANDS!
 An Unlimited supply of Backgrounds from standard stereo records! Record with your voice or perform live with the backgrounds. Used in Professional Performance yet connects easily to a home component stereo. This unique product is manufactured and sold Exclusively by LT Sound! Not sold through dealers. Call or write for a Free Brochure and Demo Record.
LT Sound, Dept. RL-3, 7980 LT Parkway
 Lithonia, GA 30058 (404) 482-4724
 Manufactured and Sold Exclusively by LT Sound
24 HOUR PHONE DEMO LINE: (404) 482-2485

COMMODORE-Amiga chips, diagnostics, parts or low cost repair. Send for complete catalog, (dealer pricing available). **VISA/MC. KASARA, INC.**, 31 Murray Hill Drive, Spring Valley, NY 10977, 1-(800) 248-2983 or (914) 356-3131.

CABLE TV converter/descramblers—original factory equipment—Zenith, TOCOM, Scientific Atlanta, Oak, Jerrold, Panasonic—remotes, video accessories. Best buys/warranties, quantity discounts—Free catalog. **ARIZONA VIDEO**, 7739 East Broadway, #108, Tucson, AZ 85710. (602) 323-3330.

PLASTIC BAGS many sizes, types. Samples \$2 list **LSASE. BAGMAN**, E2 Box 466, Georgetown, TX 78627.

CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Over 12 years of satisfied customers! Catalog \$2.

CBC INTERNATIONAL

P.O. Box 31500RE, PHOENIX, AZ 85046

DESCRAMBLERS! for all systems. Individually packaged, warranties, instructions. C.O.D. same day. (In stock! SA8580-338's) 1-(800) 288-7333.

DESCRAMBLERS. All brands. Special combo Jerrold 400 and SB3 \$165. Complete cable descrambler kit \$39. Complete satellite descrambler kit \$45.00. Free catalog. **MJM INDUSTRIES**, Box 531, Bronx, NY 10461-0531.

DESCRAMBLERS. Jerrold 400 combo remote, factory built-in decoder, \$149.95, 90 day warranty. S.A.C. (702) 647-3799.

FAIR prices SB-3, SX3, SA3, TRI-BI, MLD-1200-3. Some Oak, any notch filters. Small dealer only. No Michigan sales (313) 979-8356.

3-D HOLOGRAMS with any camera. \$2.00 info. **STELLAR TECHNOLOGIES**, 4710 University Way N.E., #1003, Seattle, WA 98105 (206) 783-3548.

TUBES. new, unused. Send self-addressed, stamped envelope for list. **FALA ELECTRONICS**, Box 1376-2, Milwaukee, WI 53201.

PHOTOFACT folders, under #1400 \$3.00. Others \$5.00. Postpaid. **LOEB**, 414 Chestnut Lane, East Meadow, NY 11554.

TRANSISTORS-tubes: MRF421 \$24.00, MRF454 \$14.50, MRF455-MRF477 \$11.75, MRF492 \$16.00, SRF2072 \$12.75, SRF3800 \$17.50, 2SC2290 \$16.75, 2SC2879 \$22.00, 6LF6, 6LQ6, 6JS6, 8950, etc-call. New **Ranger AR3500** all mode 10 Meter transceiver \$319.00. Quantity discounts! Best prices on hard-to-find parts, antennas, mics, power supplies, & equipment! Catalog \$1.00 (refundable), or free with order. **RFPC**, Box 700, San Marcos, CA 92069. For information or same day shipment—call (619) 744-0728. Visa/MC/C.O.D.

FREE CATALOG

FAMOUS "FIRESITK" BRAND CB ANTENNAS AND ACCESSORIES. QUALITY PRODUCTS FOR THE SERIOUS CB'er. SINCE 1962
FIRESITK ANTENNA COMPANY
 2614 EAST ADAMS
 PHOENIX, ARIZONA 85034

SAM'S photofact folder sets new above #1300 \$9.95 used under #1300 \$5.95 add \$1.00 **SHIPPING ELECTRONICS**, P.O. 219, Edgewood, NM 87015.

DESCRAMBLERS, Zenith, combo remote, Z-TAC, \$199.95, 90 day warranty anti flash \$35.00 extra. S.A.C. (702) 647-3799.

CABLE descrambler liquidation. Major makes and models available. Industry pricing! (Example: Hamlin combo's, \$44 each...minimum 10 orders) **DEALERS ONLY!**, Call West Coast Electronics, (818) 989-0890.

Quality Microwave TV Antennas



Multi-Channel 1.9 to 2.7 GHz. 40dB Gain
 30-Channel System complete \$149.95
 12-Channel System complete \$104.95
 2-Channel System complete \$79.95
Phillips-Tech Electronics
 P.O. Box 8533 • Scottsdale, AZ 85252
 (602) 947-7700 (\$3.00 Credit all phone orders!)
LIFETIME WARRANTY MasterCard • Visa • COD's Quantity Pricing

LASERS, components and accessories. Free catalog. **M.J. NEAL COMPANY**, 6672 Mallard Court, Orient, OH 43146.

PICTURE flyer lists quality surplus electronics at low prices. Since 1970. Send for the last 3 issues. **STAR-TRONICS**, Box 683, McMinnville, OR 97128.

SATELLITE & cable equipment. We have those hard-to-find units ready to go. Tired of junk that doesn't work properly? Try our 10 day satisfaction guarantee & 90 day warranty (wholesale only). **HI TECH ELECTRONICS**, PO Box 42423, Detroit, MI 48242, (313) 722-9381.

FEDERAL law and descrambling. Statutes and court cases. \$6.95 **G.H. PUBLICATIONS**, RR1 Box 121, Hartland, MN 56042.

SONY, Trinitron rebuilt picture tubes are now available. All tubes shipped U.P.S. No charge. We buy all Sony tubes. **ROCHESTER KINESCOPE**, (716) 235-0750.

OLD radio TV schematics. Send \$3.00, make, model. **RADIO MAPS**, P.O. Box 791, Union City, CA 94587

CONVERTER sales and repairs on all types S.A., Jerrold, Panasonic, Pioneer. **REDCOAT ELECTRONICS**, (718) 459-5088.

SCRAMBLING NEWS

Twenty plus pages of information per issue, covering cable, satellite and wireless cable. News, product reviews, mailbag, features, patents, circuits, turn-ons etc. Current articles Cable TV, SSAVI-SAVVY Part 5, VC and the Self Sufficient Pirate. \$24.95/yr. May backdate to Oct. 87. Sample \$3. New... ST-1085 decoder schematic \$14.95. Z-TRAP III eliminates flashing \$15.95. Z-BAG Bogus Address Generator \$19.95. Both \$29.95. Pay TV and Satellite Descrambling Vol. 1 or Vol. 2. \$13.95 each. Cable TV Security \$12.95. Wireless Cable Hacking \$9.95. Satellite Systems Under \$600. \$12.95. Experiments with Videocipher \$14.95. Any 3/\$28 or 6/\$40. New Fall Catalog \$1.

Shojiki Electronics Corp., 1327A Niagara St.,
Niagara Falls, NY 14303 CODs 716-284-2163

SATELLITE TV

CABLE TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Supplier's list included \$8.95. CABLE FACTS, Box 711-R, Pataskala, OH 43062.

FREE catalog systems, Upgrades, Houston, Uinden, Chaparral, etc. Save, \$\$\$ SKYVISION, 2009 Collegeway, Fergus Falls, MN 56537, (218) 739-5231.

SCRAMBLE FACTS 718-343-0130

PHONE TODAY for 3 minutes of satellite TV industry news, technical tips, and new product information.

SATELLITE TV receiver kits! Instruction manual, boards, semiconductor parts! 59° LNAs! LNB's! Ku-Band LNB's! Catalog \$1.00 (refundable): XANDI ELECTRONICS, Box 25647, Dept. 21JJ, Tempe, AZ 85282.

DESCRAMBLERS for movies, networks, \$175. video only. \$450 complete. Visa, MC accepted. Catalog \$4 SKYWATCH, 238 Davenport Road, Toronto, Ontario, Canada, M5R-1J6.

VIDEOCYPHER II descrambling manual, schematics, both video and audio encoding, DES, cloning, muskateering, EPROM codes. (HBO, Cinemax, adult channels.) \$13.95, \$2 postage. CABLETRONICS, Box 30502R, Bethesda, MD 20814.

CABLE TV. "BOXES"

Converters—Descramblers
Remote Controls—Accessories

- ★ Guaranteed Best Prices ★
- ★ 1 Year Warranty—C.O.D.'s ★
- ★ Immediate Shipping ★
- ★ FREE CATALOG ★

Call or Write
TRANS-WORLD CABLE CO.
12062 Southwest 117th Court, Suite 126
Miami, Florida 33186
800-442-9333

ROBOTIC SENSORS

TACTILE and pressure sensors, \$5/element, singles and arrays available. For info, send address to: RECEPTOR TECHNOLOGY INC., 2 Kenwood Street, Somerville, MA 02144.

BIG PROFITS

ELECTRONIC ASSEMBLY BUSINESS

Start home spare time. Investment knowledge or experience unnecessary. BIG DEMAND assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

FREE: Complete illustrated literature
BARTA, RE-O Box 248
Walnut Creek, Calif. 94597

BUSINESS OPPORTUNITIES

EARN thousands with your own part time electronics business. I do. Free prof. information. INDUSTRY, Box 531, Bronx, NY 10461.

EASY, lucrative. One man CRT rebuilding machinery. Free info: (815) 459-0666 CRT, 1909 Louise, Crystalake, IL 60014.

PROJECTION TV...easy...results comparable to \$2,500 projectors...Plans, 8" lens & dealers information \$22.50...Professional systems available... Illustrated catalog free. MACROCOMA 15GAX Main Street, Washington Crossing, PA 18977. Creditcard orders 24hrs. (215) 736-2880.

YOUR own radio station! AM, FM, TV, cable. Licensed/unlicensed. BROADCASTING, Box 130-F9, Paradise, CA 95967.

Big Profits!

LEARN VCR CLEANING-REPAIR. Prior Experience UNNECESSARY. Need only small hand tools & average mechanical abilities. BIG DEMAND performing VCR cleaning and repairs. REAL EXAMPLES of VCR malfunctions and their solutions. Photos and illustrations. ALSO: Information on starting your own business.

Free information: Write
Vicjo VCR Repair
23010 Lake Forest Dr #155
Laguna Hills, CA 92653
(714) 68-1925

PIONEER



10" WOOFER

Heavy duty paper cone with 20 oz magnet. 60 watts RMS, 90 watts max. Response: 35-3500 Hz. 1 1/2" v.c.

#290-083 \$1880 (1-3) ~~\$1690~~ (4-up)



8" WOOFER

Ribbed paper cone with poly foam roll edge. 20 oz. magnet. 4 ohm. 50 watts RMS, 75 watts max. 1 1/2" v.c.

#290-053 \$2150 (1-3) ~~\$1995~~ (4 up)

WOODGRAIN GRILL CLOTH

Authentic woodgrain print design cloth. 36" x 60".

#260-340 \$595 Per Yard

SPEAKERS AND COMPONENTS

PIONEER

MOTOROLA

MOTOROLA

3 1/2" PIEZO TWEETER

Super horn tweeter. Mfg. #KSN1005A. 3K-30KHz.

#270-010 \$530 (1-9) ~~\$450~~ (10-up)

12" 3-WAY, 100 WATT SYSTEM

Pioneer design engineers carefully evaluated the performance characteristics of this speaker system to ensure the best full range frequency response.

System Includes: (1) #290-125 poly woofer, (1) #280-045 heavy duty 5 1/4" midrange, (1) #270-035 4" soft dome tweeter, (1) #260-210 3-way 100 watt crossover, (2) #260-255 50 watt L-pads, (1) #260-300 terminal, and (1) #260-340 woodgrain grill cloth. Recommended cabinet volume: 3.1 cu ft.

#12-100

Save Over \$1000

EMPIRE ELECTRONICS


EMPIRE



12" POLY WOOFER

Super duty, 40 oz. magnet. Polypropylene cone. 100 watts RMS, 145 watts max. 4-8 ohm compatible (6 ohm). 2" voice coil.

#290-125 \$3680 (1-3) ~~\$3450~~ (4-up)

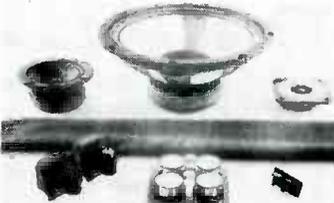

\$7395 each

* 15 day money back guarantee. * \$10.00 minimum order. * We accept Mastercard, Visa, Discover, and C.O.D. orders. * 24 hour shipping. * Shipping charge = UPS chart rate (\$2.50 minimum charge). * Hours: 8:30 am - 6:00 pm EST, Monday - Friday. * Mail order customers, please call for shipping estimate on orders exceeding 5 lbs.

THUNDER by EMINENCE



15" WOOFER

56 oz. magnet. 2 1/2" voice coil. 150 watts RMS, 200 watts max. Paper cone with poly foam roll edge. 4 ohm.

#290-180 \$4350 (1-3) ~~\$3980~~ (4-up)

PIONEER

HORN TWEETER

Exponential horn design. Mylar dome. 3 1/2" x 3 1/2". 1800-20,000Hz response. 35 watts RMS, 50 watts max.

#270-050 \$650 (1-9) ~~\$590~~ (10-up)

150 WATT 3-WAY CROSSOVER

12 dB/octave 3-way crossover network. 800-5000Hz. Automatic resetting over-power protection.

#260-212 \$2180 each

Parts Express International, Inc.

340 E. First St., Dayton, OH 45402
Local 1-513-222-0173
FAX 1-513-461-3391

CALL TOLL FREE
1-800-338-0531

FREE CATALOG

DO YOU OFTEN WISH THAT THE SMITH COMPANY WAS THE SMITH & SMITH & SMITH & SMITH COMPANY?

Business people often find themselves doing so many things that just one of them isn't enough. So hire some of the needy and disadvantaged young people of America this summer to help you. Hiring them can also help you in another very important way. Because a business that hires economically disadvantaged youth during the summer may get as much as an 85% tax credit on the first \$3,000 of wages you pay them. Write the National Alliance of Business at P.O. Box 7207, Washington D.C. 20044. And support your local summer-jobs-for-youth programs. You'll be doing something for yourself, for your business, for your community, and for the needy youth of America, too.

LET'S GET ALL OF AMERICA WORKING AGAIN.

Ad A PUBLIC SERVICE OF THIS PUBLICATION & COUNCIL THE ADVERTISING COUNCIL

ENGINEERING core course everybody can understand with programming **Practical circuit theory simplified.** \$12 BAY SHORE PRESS, 981 Indian Beach Drive, Sarasota, FL 34234. Money-back guaranteed.

CABLE TV CONVERTERS

CABLE TV converters. Scientific Atlanta, Jerrold, Oak, Zenith, Hamlin. Many others. "New" Video Hopper "The Copy Killer." Visa, M/C & Amex. 1-(800) 826-7623. B&B INC., 10517 Upton Circle, Bloomington, MN 55431.

This publication is available in microform.

University Microfilms International

Please send additional information

Name _____
Institution _____
Street _____
City _____
State _____ Zip _____

300 North Zeeb Road
Dept. P.R.
Ann Arbor, MI 48106
U.S.A.

30-32 Mortimer Street
Dept. P.R.
London WIN 7RA
England

CABLE-TV AT IT'S BEST

SCIENTIFIC Atlanta models 8500-8550 remote included...\$240.00. SB-3's...\$74.00. TRI-B's...\$95.00. SA-3's...\$99.00. Zenith (Z-Tac) descramblers...\$169.00. N-12 (Vari-sync)...\$89.00. M-35 B (Vari-sync)...\$99.00. Hamlin MLD-1200's...\$89.00. 80-Channel converters...\$95.00. Dealer discount on (5) units. Call N.A.S. INTERNATIONAL, (213) 631-3552. FAX: (213) 925-3542.

NEURAL NETWORKS

AMAZING circuits simulate thought & sensory processing. Plans \$25. Brochure \$2 purchase deductible. Author MSEE. LP WEBER, Box 621, Dept. RE-0902, Allenwood, NJ 08720.

CAR-STEREO EQUIPMENT

BOOM boom subwoofer speaker systems, electronic crossovers, power amplifiers, equalizer stereos, CB's etc. Wholesale prices, free catalog, information. BOOM BOOM ELECTRONICS, 2905 Las Vegas Blvd. North, #53RE, North Las Vegas, NV 89030.

EDUCATION & INSTRUCTION

F.C.C. Commercial General Radiotelephone license. Electronics home study. Fast, inexpensive! "Free" details. COMMAND, D-176, Box 2223, San Francisco, CA 94126.

ENGINEERING software for IBM-PC. CompDes... circuit design. CompMath... math tutor. CompView... digital signal analysis. \$49 each. (614) 491-0832. BSOFT SOFTWARE, 444 Colton Road, Columbus, OH 43207.

300W HQ HI-FI POWER AMPLIFIER (MONO) TA-3600

QUASI-COMPLEMENTARY SYMMETRY WITH PARALLEL HIGH OUTPUT TRANSISTORS SPECIFICATIONS:

- *POWER OUTPUT: 300W IRMS INTO 8 OHMS - 2450W (P.M.P.O.) INTO 8 OHMS
- *450W (MUSIC POWER) INTO 8 OHMS
- *LOAD IMPEDANCE: 4 OHMS OR 8 OHMS
- *FREQUENCY RESPONSE: 10Hz-200,000Hz
- *TOTAL HARMONIC DISTORTION LESS THAN 0.05%
- *INPUT SENSITIVITY AND IMPEDANCE AT 1KHz: 1V-1.4V 47K OHMS
- *SUPPLY VOLTAGE: DC: 75V OR AC 53V x 2BA
- KIT/ASSM WITH TESTED \$86/110
- X FORMER \$38 00

Build up your supreme Power Amp!

120W VERSATILE STEREO POWER BOOSTER TA-302

MATCH WITH OUR SURROUND SOUND PROCESSOR

- * OTL full transistorize and low distortion of SEPP circuit design, high output power and sound fidelity.
- * With high and low input impedance for selection, so it can match with all preamplifiers, low power of portable sound equipment, and all types of stereo recorder deck to use. It can boost "walkman" type of radio and tape player, 100.
- * With 10 band color LED power meter, output power can be easily defined. TA-302 is a versatile amplifier for both visual and listening enjoyment. 60Wx2 P.M.P.O.

KIT/ASSM WITH TESTED \$50/70

ELECTRONIC LOTTO

TY-8



NEW FOR '88

- * 0-49 DIGITS DISPLAY, SUITABLE FOR LOTTERY GAME.
- * AUTO-SHUT OFF POWER, SO POWER CONSUMPTION IS VERY LOW.
- * 05" GREEN LED DISPLAY WITH FANCY PLASTIC PANEL
- * OPERATION VOLTAGE: 9V DC (BATTERY NOT INCLUDED)
- * DIMENSIONS: 3.1" x 2" x 0.5"

KIT \$15 00

100W+100W NEW CLASS 'A' DC STEREO PRE-MAIN AMPLIFIER



TA-1500
200W POWERFUL AMP W/MIC MIXER!
KIT \$73 70
METAL CABINET/XFORMER \$26/\$16 80

MARK V ELECTRONICS INC.,

8019 E. SLAUSON AVE.
MONTEBELLO CA90640
FAX: (213) 888-1029

INFORMATION: (213) 888-8988

TOLL FREE 1-800-423-3483 FOR ORDERS ONLY

Only for orders paid by Master or VisaCard
IN CAL.: 1-800-521-MARK

TERMS: \$10 min order • \$20 min charge card order • Check, money order or phone order accepted • We ship UPS Ground • Add 10% of total order (min \$25) for shipping, outside USA add \$20 • Transit insurance: add 5% of total (outside USA only) • CA residents add sales tax • All merchandise subject to prior sale • Prices are subject to change without notice • Any goods proved to be defective MUST BE RETURNED IN ORIGINAL FORM WITH A COPY OF YOUR INVOICE WITHIN 30 DAYS FOR REPLACEMENT

150MC Digital SM-100 Frequency Counter

Frequency Range: 10Hz - 150MHz
Event Counter: 0 to 99999999 counts (8 Digit)
Input sensitivity: KHz range 10Hz - 10MHz 50mVrms
MHz range 1MHz - 150MHz 40mVrms
Response time: 0.2 second
Hold Function: Hold the last input signal
Power Supply: DGBV Battery or DCGV Adaptor
Dimensions: 9 7/8" x 6 11/16" x 2 3/4"
Assembled with tested \$99 00

PROFESSIONAL COLOR LIGHT CONTROLLER SM-328

FEATURES:
1. FOUR GROUPS OF INDEPENDENT OUTPUT SYSTEM 1000W/CH. MAX. 4680W (1100-117V)
2. PROFESSIONAL COLOR CONTROL SYSTEM (KEYBOARD TYPE) 3. INDEPENDENT INPUT SIGNAL ADJUSTMENT 4. FOUR GROUPS OF INDEPENDENT DIMMER CONTROL 5. SPEED CONTROL CHASER 6. AUTOMATIC CHASING CONTROL SYSTEM 7. FOUR KINDS OF SPECIAL CHASING PROGRAM 8. COMBINATION OF PROGRAM AND MUSIC CHASING EFFECT 9. FORWARD/BACKWARD CHASING CONTROL
SM-328 color light controller is specialized for ballroom, night club disco and advertisement lighting. It consists with several color control characteristics, which employ professional color control system and keyboard program selection. Therefore, it is capable of producing lighting effects by using chasing program and fluctuating music signal. There are two kinds of lighting effects. The first type is controlled by "music" signal. In order to adjust the brightness of four groups of lightings, each music signal will be separated into high, medium low A, and low B frequency range. Furthermore, each group of lightings is incorporated with an independent signal adjustment. The second kind is composed of electrical circuits and this is the main part for creating a special lighting effect. It has four chasing programme.
Dimensions: 14 5/16" x 8 15/16" x 3 3/16"
Ass. with tested \$150.00

STORE HOURS: (PACIFIC TIME)
MON.-FRI. 9:30 to 5:00 SAT. 10:00 to 5:00

SURROUND SOUND PROCESSOR

SM-333



Enjoy Surround sound with our SM-333

This processor employs the most updated IC at its heart. It is also equipped with a "DNR" DYNAMIC NOISE REDUCTION SYSTEM IC made by NATIONAL SEMICONDUCTOR to particularly filter out the annoying noise that is commonly found on tapes or CD disk. In addition, there is six LOW NOISE OP-AMPS and all in one board design, no other external connections connect to the main board.

SPECIFICATIONS:
Frequency Response: 20Hz-20KHz (± 5dB) Total Harmonic Distortion: 0.06% 20Hz-20KHz (front channel), < 0.25% (surround channel). Input Voltage: 0.1V-3.5V, Output Voltage: 0.1V-3.5V (front channel), 8.6V Max. (surround channel). Delay Time: 5ms-50ms. Input Impedance: 47K Ohms. Power: AC 110V 50Hz. Dimensions: 4 3/16" (W) x 4 13/16" (D) x 2 1/16" (H)
KIT/ASSM WITH TESTED \$72/93

0-15V 2A REGULATED DC POWER SUPPLY



TR-100A
ESSENTIAL FOR FACTORIES, PROFESSIONALS & ENTHUSIASTIC AMATEURS!

Kit \$59 50
Ass. with tested \$69 50

- * Output voltage is adjustable from 0-15V DC, two current limit. range are available for selection: 200mA or 2A.
- * An elaborated protection system is specially designed, a "BB" sound and a sparkling light will appear when the output is overloaded.
- * High stability and reliability is resulted by employing high quality voltage regulated IC.
- * King-size meter makes the reading of voltage and current more clearly and accurately.
- * A refined case, meter and all accessory are enclosed for both kit and assembled form. It is most suitable for professional or amateur use.

8 Digit 1GHz Multifunctional Counter FC-1000A

A versatile laboratory bench digital counter with 1111111111 performance. FREQUENCY PERIOD UNIT TOTALIZE/ DATA HOLD & SELF CHECK. The period function makes the instrument outstanding for video base recorder service applications. D5: Bright LED display assure easy readability of values. High stabilized dual crystal oscillators are used to ensure the accuracy in measurement. Durable alloy cabinet with a fancy looking panel. Comes complete with test lead and owners manual.
FEATURES:
Frequency range: 10Hz - 1GHz GUARANTEED, 5Hz - 120Hz typical
Input sensitivity: 10Hz - 100MHz 10mV - 20mV
100MHz - 1.2GHz 15mV - 20mV
Pulse range: 0.5us - 10us
Unit counting mode: 99999999
Accuracy: ± 0.001% time base accuracy
Hold function: Hold the last input signal (Max 8 digits)
Power source: 1.5V AC 120V 60Hz
Dimensions: 8 5/8" (W) x 7 7/8" (D) x 3" (H)
ASSM WITH TESTED & CAL. \$192.00



LAB QUALITY AT A BREAKTHROUGH PRICE!

CIRCLE 93 ON FREE INFORMATION CARD

Weller, Xcelite, and EV....



Three of the industry leaders, have joined an already comprehensive list of name brands at MCM. Whether you're looking for soldering equipment, tools, audio accessories or high quality semiconductors... you'll find them in our Free 172 page "power house" catalog. Get your free copy today!



Weller has become the world's leading supplier of professional quality soldering equipment, including the famous Weller temperature controlled irons and soldering guns. Weller also makes advanced desoldering stations and SMT equipment for all your sophisticated industrial and service requirements.

Xcelite sets the standard for tools in the electronics, electrical and telecommunication industries around the world. With their extensive line of high quality screwdrivers, nutdrivers, cutters and service kits, they are sure to have the right tool for all your service needs.

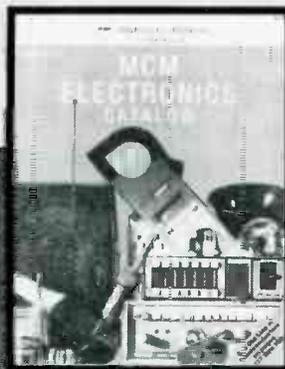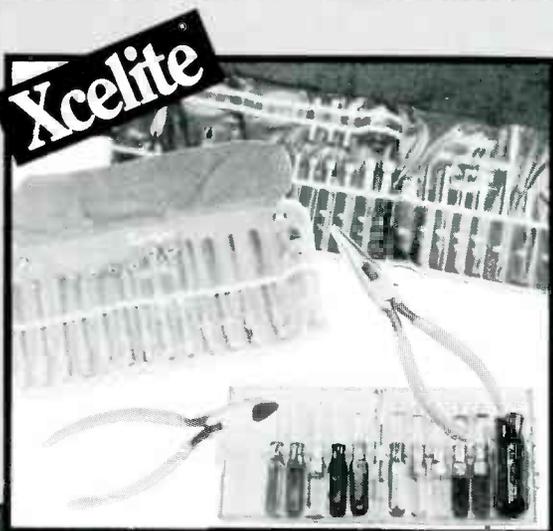Electro-Voice loudspeakers represent the ultimate in maximum efficiency, low frequency speaker design. Years of experience, testing, and design refinement have resulted in a series of loudspeakers that are universally accepted by sound consultants, contractors, musicians, and touring sound companies.



For your **FREE** copy, call **TOLL-FREE!**

1-800-543-4330

In Ohio, call **1-800-762-4315**

In Alaska or Hawaii, call **1-800-858-1849**




MCM ELECTRONICS

858 E. CONGRESS PARK DR.
CENTERVILLE, OH 45459-4072

A *PREMIER* Company

SOURCE NO. RE-48

CIRCLE 87 ON FREE INFORMATION CARD

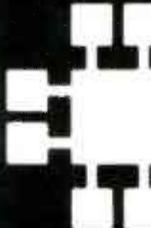

JDR Microdevices®

Complete customer satisfaction... superior service... friendly, knowledgeable personnel
quality merchandise... providing the best values in leading edge technology.

STATIC RAMS

2112	256x4 (450ns)	2.99
2114	1024x4 (450ns)	.99
2114L-2	1024x4 (200ns)(LOW POWER)	1.49
TMM2016-100	2048x8 (100ns)	1.95
HM6116-4	2048x8 (200ns)(CMOS)	3.29
HM6116LP-3	2048x8 (150ns)(CMOS)	3.95
HM6116LP-4	2048x8 (200ns)(CMOS)(LP)	4.29
HM6116LP-3	2048x8 (150ns)(CMOS)(LP)	4.95
HM6116LP-2	2048x8 (120ns)(CMOS)(LP)	5.49
HM6264LP-15	8192x8 (150ns)(CMOS)(LP)	6.49
HM6264LP-12	8192x8 (120ns)(CMOS)(LP)	6.99
HM43256LP-15	32768x8 (150ns)(CMOS)(LP)	12.95
HM43256LP-12	32768x8 (120ns)(CMOS)(LP)	14.95
HM43256LP-10	32768x8 (100ns)(CMOS)(LP)	19.95

DYNAMIC RAMS

4116-250	16384x1 (250ns)	.49
4116-200	16384x1 (200ns)	.89
4116-150	16384x1 (150ns)	.89
4116-120	16384x1 (120ns)	1.49
MK4332	32768x1 (200ns)	6.95
4164-150	65536x1 (150ns)	2.89
4164-120	65536x1 (120ns)	3.19
MCM6665	65536x1 (200ns)	1.95
TMS4164	65536x1 (150ns)	1.95
4164-REFRESH	65536x1 (150ns)(PIN 1 REFRESH)	2.95
TMS4416	16384x4 (150ns)	3.75
41128-150	131072x1 (150ns)	5.95
TMS4464-15	65536x4 (150ns)	7.95
41256-150	262144x1 (150ns)	12.45
41256-120	262144x1 (120ns)	12.95
41256-100	262144x1 (100ns)	13.45
HM51258-100	262144x1 (100ns)(CMOS)	6.95
1 MB-120	1048576x1 (120ns)	34.95
1 MB-100	1048576x1 (100ns)	37.95

EPROMS

2708	1024x8 (450ns)(25V)	4.95
2716	2048x8 (450ns)(25V)	3.49
2716-1	2048x8 (350ns)(25V)	3.95
TMS2532	4096x8 (450ns)(25V)	5.95
2732	4096x8 (450ns)(25V)	3.95
2732A	4096x8 (250ns)(21V)	3.95
2732A-2	4096x8 (200ns)(21V)	4.25
27C64	8192x8 (250ns)(12.5V CMOS)	4.45
2764	8192x8 (450ns)(12.5V)	3.49
2764-250	8192x8 (250ns)(12.5V)	3.49
2764-200	8192x8 (200ns)(12.5V)	4.25
MCM68766	8192x8 (350ns)(21V)(24 PIN)	15.95
27128	16384x8 (250ns)(12.5V)	4.25
27C256	32768x8 (250ns)(12.5V CMOS)	7.95
27256	32768x8 (250ns)(12.5V)	5.95
27512	65536x8 (250ns)(12.5V)	11.95
27C512	65536x8 (250ns)(12.5V CMOS)	12.95

MEMORY PRICES SUBJECT TO CHANGE DUE TO MARKET CONDITIONS. PLEASE CALL TO CONFIRM PRICES.

HIGH-TECH SPOTLIGHT 1 MB EPROMS

■ 128K x 8 ORGANIZATION ■ 200 NS
■ CMOS DESIGN FOR LOW POWER

\$34.95

8000

8031	3.95
8035	1.49
8039	1.95
8052AH BASIC	34.95
8080	2.49
8085	1.95
8086	6.49
8088	5.99
8088-2	7.95
8155	2.49
8155-2	3.95
8741	9.95
8748	7.95
8749	9.95
8755	14.95

8200

8203	14.95
8205	3.29
8212	1.49
8216	1.49
8225	2.25
8228	2.25
8237	3.95
8237-5	7.95
8243	1.95
8250	6.95
8251	1.29
8251A	1.69
8253	1.59
8253-5	1.95
8255	1.49
8255-5	1.59
8259	1.95
8259-5	2.29
8259-5	2.25
8272	4.39
8274	4.95
8275	16.95
8279	2.49
8279-5	2.95
8282	3.95
8283	3.95
8284	2.25
8286	3.95
8287	3.95
8288	4.95

MATH COPROCESSORS

8087 5 MHz \$99.95
8087-2 8 MHz \$159.95
8087-1 10 MHz \$229.95
80287 6 MHz \$179.95
80287-8 8 MHz \$249.95
80287-10 10 MHz \$309.95
80387-16 16 MHz \$499.95
80387-20 20 MHz \$799.95

74LS00

74LS00	16	74LS112	29	74LS241	.69
74LS01	18	74LS122	45	74LS242	.69
74LS02	17	74LS123	49	74LS243	.69
74LS03	18	74LS124	2.75	74LS244	.69
74LS04	16	74LS125	39	74LS245	.79
74LS05	18	74LS126	39	74LS249	.49
74LS08	18	74LS132	39	74LS253	.49
74LS09	18	74LS133	49	74LS257	.49
74LS10	16	74LS136	39	74LS258	.49
74LS11	22	74LS138	39	74LS259	1.29
74LS12	22	74LS139	39	74LS260	.49
74LS13	26	74LS145	99	74LS266	.39
74LS14	39	74LS147	99	74LS273	.79
74LS15	26	74LS148	99	74LS279	.39
74LS20	17	74LS151	39	74LS280	1.98
74LS21	22	74LS153	39	74LS283	.59
74LS22	22	74LS154	1.49	74LS290	.89
74LS27	23	74LS155	59	74LS293	.89
74LS28	26	74LS156	49	74LS299	1.49
74LS30	17	74LS157	35	74LS322	3.95
74LS32	18	74LS158	29	74LS323	2.49
74LS37	26	74LS160	29	74LS365	.39
74LS38	26	74LS161	39	74LS367	.39
74LS43	26	74LS162	49	74LS368	.39
74LS47	75	74LS163	39	74LS373	.79
74LS48	85	74LS164	49	74LS374	.79
74LS51	17	74LS166	65	74LS375	.95
74LS73	29	74LS169	95	74LS390	1.19
74LS74	24	74LS173	49	74LS393	.79
74LS75	29	74LS174	39	74LS397	1.49
74LS76	29	74LS175	39	74LS624	1.95
74LS83	49	74LS191	49	74LS640	.99
74LS85	49	74LS192	69	74LS645	.99
74LS86	22	74LS193	69	74LS670	.89
74LS90	39	74LS194	69	74LS682	3.20
74LS92	49	74LS195	69	74LS688	2.40
74LS93	39	74LS196	59	74LS783	22.95
74LS95	49	74LS197	59	25LS2521	2.80
74LS107	34	74LS221	59	26LS31	1.95
74LS109	36	74LS240	69	26LS32	1.95

7400

7400	19
7402	19
7404	19
7406	29
7407	29
7408	24
7410	19
7411	25
7414	49
7416	25
7417	25
7420	19
7430	19
7432	29
7438	29
7442	49
7445	69
7447	89
7473	34
7474	33
7475	45
7476	35
7483	50
7485	59
7486	35
7489	2.15
7490	39
7493	35
74121	29
74123	49
74125	45
74150	1.35
74151	55
74153	55
74154	1.49
74157	55
74159	1.65
74161	69
74164	85
74166	1.00
74175	89
74367	65

LINEAR

LM071	69	LM567	79
LM072	1.09	NE570	2.95
LM074	1.95	NE592	.98
LM083	39	LM723	.39
LM084	4.49	LM733	.99
LM301	34	LM741	29
LM309K	1.25	LM742	.69
LM311	5.95	MC1330	1.69
LM311H	89	MC1350	1.19
LM317K	3.49	LM1458	3.95
LM317T	69	LM1488	.49
LM318	1.49	LM1489	.49
LM319	1.25	LM1496	.85
LM331	see 7900	ULN2003	.79
LM332	29	XR2206	3.95
LM333	34	XR2211	2.95
LM334	3.95	LM2917	1.95
LM339	1.19	CA3046	.89
LM335	1.29	CA3146	1.29
LM336	1.75	CA3308	1.29
LM338K	4.49	MC3470	1.95
LM339	5.95	MC3480	8.95
LM340	see 7800	MC3487	2.95
LM353	59	LM3909	2.95
LM359	99	LM3911	4.95
LM359	99	LM3909	.98
LM358	59	LM3914	1.89
LM380	89	MC4024	3.49
LM393	49	74HC123	3.99
LM386	89	RC1436	1.15
LM393	45	RC4558	.69
LM394H	5.95	LM13600	1.49
LM494	4.20	75107	1.49
LM497	3.25	75110	1.95
NE555	99	75150	1.95
NE556	49	75154	1.95
NE558	79	75188	1.25
NE564	1.95	75189	1.25
LM565	95	75451	.39
LM566	1.49	75452	.39
NE590	2.50	75477	1.29

H-TO-5 CAN. K-TO-3. T-TO-220

6500 1.0 MHz

6502	2.25
65C02 (CMOS)	7.95
6520	1.65
6522	2.95
6526	13.95
6532	5.95
6545	2.95
6551	2.95

2.0 MHz

6502A	2.69
6520A	5.95
6522A	2.95
6532A	11.95
6545A	3.95
6551A	6.95

3.0 MHz

6502B	4.25
-------	------

Z-80 2.5 MHz

Z80-CPU	1.25
---------	------

4.0 MHz

Z80A-CPU	1.29
Z80A-CTC	1.69
Z80A-DART	5.95
Z80A-DMA	5.95
Z80A-PIO	1.89
Z80A-SIO 0	5.95
Z80A-SIO 1	5.95
Z80A-SIO 2	5.95

6.0 MHz

Z80B-CPU	2.75
Z80B-CTC	4.25
Z80B-PIO	4.25
Z80B-DART	6.95
Z80B-SIO 0	12.95
Z80B-SIO 2	12.95
Z8671 ZILOG	9.95

DISK CONTROLLERS

1771	4.95
1791	9.95
1793	9.95
1795	12.95
1797	12.95
2791	19.95
2793	19.95
2797	29.95
2872	4.39
UPD765	4.39
MB8876	12.95
MB8877	12.95
1691	6.95
2143	6.95
9216	6.29

V20 SERIES

V20* 5 MHz	8.95
V20* 8 MHz	10.95
V20* 10 MHz	12.95
V30 8 MHz	13.95

*Replaces 8088 to speed up PC 10.40%

CRYSTALS

32.768 KHz	95
1.0 MHz	2.95
1.8432	2.95
2.0	1.95
2.4576	1.95
3.579545	1.95
4.0	1.95
5.0	1.95
5.0688	1.95
6.0	1.95
6.144	1.95
8.0	1.95
10.0	1.95
10.738635	1.95
12.0	1.95
14.31818	1.95
16.0	1.95
18.0	1.95
18.432	1.95
20.0	1.95
22.1184	1.95
24.0	1.95
32.0	1.95
74F00	35
74F02	35
74F04	35
74F08	35
74F10	35
74F32	35
74F64	55
74F74	39
74F86	35
74F138	79
74F139	79
74F253	89
74F157	89
74	

CAPACITORS

TANTALUM			
10	15V	12	1.0µF 35V 45
6.8	15V	42	2.2 35V 19
10	15V	45	4.7 35V 39
22	15V	99	10 35V 69
DISC			
10	50V	05	001µF 50V 05
22	50V	05	005 50V 05
33	50V	05	01 50V 07
47	50V	05	05 50V 07
100	50V	05	1 12V 10
220	50V	05	1 50V 12

MONOLITHIC

.01µF	50V	14	1µF 50V 18
.047µF	50V	15	47µF 50V 25

ELECTROLYTIC

RADIAL		AXIAL	
1/4	25V	14	1/4 50V 14
4.7	50V	11	10 50V 16
10	50V	11	22 16V 14
47	35V	13	47 50V 19
100	16V	15	100 35V 19
220	35V	20	470 50V 29
470	25V	30	1000 16V 29
2200	16V	70	2200 16V 70
4700	25V	145	4700 16V 1.25

BYPASS CAPACITORS

01	µA CERAMIC DISC	100	\$5.00
01	µA MONOLITHIC	100	\$10.00
1	µA CERAMIC DISC	100	\$6.50
1	µA MONOLITHIC	100	\$12.50

"SNAPABLE" HEADERS

CAN BE SNAPPED APART TO MAKE ANY SIZE HEADER, ALL WITH .1" CENTERS

1x40	STRAIGHT LEAD	99
1x40	RIGHT ANGLE LEAD	49
2x40	2 STRAIGHT LEADS	2.49
2x40	2 RIGHT ANGLE LEADS	2.99



VOLTAGE REGULATORS

7805T	49	7812K	1.39
7808T	49	7905K	1.69
7812T	49	7912K	1.49
7815T	49	78L05	4.9
7905T	59	78L12	4.9
7908T	59	79L05	6.9
7912T	59	79L12	1.49
7915T	59	LM323K	4.79
7805K	1.59	LM338K	6.95

DISCRETE

1N751	15	4N28	6.9
1N414825	11.00	4N33	.89
1N400410	11.00	4N37	1.19
1N5402	25	MCT-2	5.9
KBPO2	55	MCT-6	1.29
2N2222	25	TIL-111	.99
PN2222	10	2N3906	10
2N2907	25	2N4401	25
2N3055	79	2N4402	25
2N3904	10	2N4403	25
4N26	6.9	2N6045	1.75
4N27	6.9	TIP31	4.9

SOLDER STATION

- UL APPROVED
- ADJUSTABLE HEAT SETTING WITH TIP TEMPERATURE READOUT
- REPLACEMENT TIPS AVAILABLE \$2.95

\$49.95



WIREWRAP PROTOTYPE CARDS

FR-4 EPOXY GLASS LAMINATE WITH GOLD PLATED EDGE-CARD FINGERS SILK SCREENED LEGENDS, MOUNTING BRACKETS INCLUDED



FOR PS/2

JDR-PR32	32 BIT PROTOTYPE CARD	69.95
JDR-PR16	16 BIT CARD WITH I/O DECODING LAYOUT	49.95
JDR-PR16PK	PARTS KIT FOR JDR-PR16 ABOVE	15.95
JDR-PR16V	16 BIT CARD FOR VIDEO APPLICATIONS	39.95

FOR AT

JDR-PR10	16 BIT CARD WITH I/O DECODING LAYOUT	34.95
JDR-PR10PK	PARTS KIT FOR JDR-PR10 ABOVE	12.95

FOR XT

IBM-PR1	WITH +5V AND GROUND PLANE	27.95
IBM-PR2	AS ABOVE WITH I/O DECODING LAYOUT	29.95

RESISTOR NETWORKS

SIP	10 PIN	9 RESISTOR	6.9
SIP	8 PIN	7 RESISTOR	5.9
SIP	16 PIN	8 RESISTOR	1.09
DIP	16 PIN	15 RESISTOR	1.09
DIP	14 PIN	7 RESISTOR	.99
DIP	14 PIN	13 RESISTOR	.99

SHORTING BLOCKS
5/\$1.00



EXTENDER CARDS

FOR PROTOTYPE DEBUGGING AND TROUBLESHOOTING



EXT-8088	FOR XT SYSTEM	29.95
EXT-80286	FOR AT SYSTEM	39.95
EXT-16	MICROCHANNEL 16-BIT	69.95
EXT-32	MICROCHANNEL 32-BIT	99.95

WHY THOUSANDS CHOOSE JDR

- ★ QUALITY MERCHANDISE
- ★ COMPETITIVE PRICES
- ★ MOST ORDERS SHIPPED IN 24 HOURS
- ★ FRIENDLY, KNOWLEDGEABLE STAFF
- ★ 30-DAY MONEY BACK GUARANTEE
- ★ TOLL FREE TECHNICAL SUPPORT
- ★ EXCELLENT CUSTOMER SERVICE

CALL FOR VOLUME QUOTES

SOLDERLESS BREADBOARDS

WBU-D	100 TIE PTS.	2.95	WBU-204	1660 TIE PTS.	24.95
WBU-T	630 TIE PTS.	6.95	WBU-206	2390 TIE PTS.	29.95
WBU-204-3	1360 TIE PTS.	17.95	WBU-208	3220 TIE PTS.	39.95



IDC CONNECTORS/RIBBON CABLE

DESCRIPTION	ORDER BY	CONTACTS					
		10	20	26	34	40	50
SOLDER HEADER	IDHxxS	.82	1.29	1.68	2.20	2.58	3.24
RIGHT ANGLE SOLDER HEADER	IDHxxSR	.85	1.35	1.76	2.31	2.72	3.39
WIREWRAP HEADER	IDHxxW	1.86	2.98	3.84	4.50	5.28	6.63
RIGHT ANGLE WIREWRAP HEADER	IDHxxWR	2.05	3.28	4.22	4.45	4.80	7.30
RIBBON HEADER SOCKET	IDSxx	.63	.89	.95	1.29	1.49	1.69
RIBBON HEADER	IDMxx	...	5.50	6.25	7.00	7.50	8.50
RIBBON EDGE CARD	IDExx	.85	1.25	1.35	1.75	2.05	2.45
10' GREY RIBBON CABLE	RCxx	1.60	3.20	4.10	5.40	6.40	7.50

FOR ORDERING INSTRUCTIONS SEE D-SUBMINIATURE CONNECTORS BELOW

D-SUBMINIATURE CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS						
		9	15	19	25	37	50	
SOLDER CUP	MALE	DBxxP	.45	.59	.69	.69	1.35	1.85
	FEMALE	DBxxS	.49	.69	.75	.75	1.39	2.29
RIGHT ANGLE PC SOLDER	MALE	DBxxPR	.49	.6979	2.27	...
	FEMALE	DBxxSR	.55	.7585	2.49	...
WIREWRAP	MALE	DBxxPWW	1.69	2.56	...	3.89	5.60	...
	FEMALE	DBxxSww	2.76	4.27	...	6.84	9.95	...
IDC RIBBON CABLE	MALE	IDBxxP	1.39	1.99	...	2.25	4.25	...
	FEMALE	IDBxxS	1.45	2.05	...	2.35	4.49	...
HOODS	METAL	MHOODxx	1.05	1.15	1.25	1.25
	GREY	HOODxx	.39	.3939	.69	.75

ORDERING INSTRUCTIONS: INSERT THE NUMBER OF CONTACTS IN THE POSITION MARKED xx OF THE ORDER BY PART NUMBER LISTED. EXAMPLE: A 15 PIN RIGHT ANGLE MALE PC SOLDER WOULD BE DB15PR

MOUNTING HARDWARE 59¢

IC SOCKETS/DIP CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS								
		8	14	16	18	20	22	24	28	40
SOLDER TAIL SOCKETS	xxST	1.1	1.1	1.12	1.5	1.8	1.5	2.0	2.2	3.0
WIREWRAP SOCKETS	xxWW	.59	.69	.69	.99	1.09	1.39	1.49	1.69	1.99
ZIF SOCKETS	ZIFxx	...	4.95	4.95	...	5.95	...	5.95	6.95	9.95
TOOLED SOCKETS	AUGATxxST	.62	.79	.89	1.09	1.29	1.39	1.49	1.69	2.49
TOOLED WW SOCKETS	AUGATxxWW	1.30	1.80	2.10	2.40	2.50	2.90	3.15	3.70	5.40
COMPONENT CARRIERS	ICCx	.49	.59	.69	.99	.99	.99	.99	1.09	1.49
DIP PLUGS (IDC)	IDPxx	.95	.49	.59	1.29	1.4985	1.49	1.59

FOR ORDERING INSTRUCTIONS SEE D-SUBMINIATURE CONNECTORS ABOVE

3 VOLT LITHIUM BATTERY
\$1.95
HOLDER \$1.49



SPECTRONICS CORPORATION EPROM ERASERS

Model	Timer	Chp Capacity	Intensity (uW Cm ²)	Unit Cost
PE-140	NO	9	8,000	\$89
PE-140T	YES	9	8,000	\$139
PE-240T	YES	12	9,600	\$189



DATARASE

- ERASES 2 EPROMS IN 10 MINUTES
- VERY COMPACT, NO DRAWER
- THIN METAL SHUTTER PREVENTS UV LIGHT FROM ESCAPING

\$34.95



RS-232 BREAKOUT BOX

FOR TROUBLESHOOTING SERIAL COMMUNICATIONS


- OPEN CLOSE INDIVIDUAL CIRCUITS
- 20 JUMPER CROSS-CONNECT ANY TWO CIRCUITS
- 10 LEDS SHOW CIRCUIT ACTIVITY
- GENDER-BO \$34.95



GENDER CHANGERS

FOR 25 PIN D-SUBMINIATURE CONNECTORS


GENDER-FF	FEMALE-MALE	7.95
GENDER-MM	MALE-MALE	7.95
GENDER-MF	MALE-FEMALE	7.95
GENDER-NM	NULL MODEM	8.95
GENDER-JB	JUMPER BOX	8.95
GENDER-MT	MINITESTER	14.95

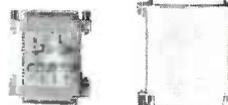

JOYSTICK

- SET X-Y AXIS FOR AUTO CENTER OR FREE MOVEMENT
- FIRE BUTTON FOR USE WITH GAME SOFTWARE
- ADAPTOR CABLE FOR IBM, APPLE II

\$19.95

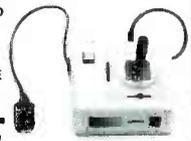

JDR MICRODEVICES, 110 KNOWLES DRIVE, LOS GATOS, CA 95030
LOCAL (408) 866-6200 FAX (408) 378-8927 TELEX 171-110




RETAIL STORE: 1256 SOUTH BASCOM AVE., SAN JOSE, CA (408) 947-8881
HOURS: M-F 10-7 SAT. 9-5 SUN. 12-4



ORDER TOLL FREE 800-538-5000

COPYRIGHT 1988 JDR MICRODEVICES

CONTINENTAL U.S. AND CANADA

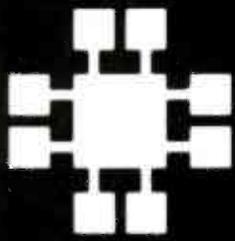

JDR Microdevices®

Complete customer satisfaction...superior service...friendly, knowledgeable personnel
quality merchandise...providing the best values in leading edge technology.

PROMETHEUS 2400 BAUD MODEM

\$129⁹⁵

NEW LOW PRICE!



IT'S TIME TO TRADE UP NOW THAT JDR BREAKS THE PRICE BARRIER ON 2400 BAUD MODEMS

- AUTO DIAL ANSWER
- SELF TEST ON POWER-UP
- TOUCHTONE OR PULSE DIALING
- HAYES & BELL SYSTEMS COMPATIBLE
- FULL OR HALF DUPLEX
- MIRROR II COMMUNICATIONS SOFTWARE INCLUDED

MCT-241

MCT-121 1200 BAUD 1/2 CARD \$ 69.95

EXTERNAL MODEMS

MCT-12E 1200 BAUD \$ 99.95

MCT-24E 2400 BAUD \$169.95

COMPUTER CASES

ATTRACTIVE, STURDY STEEL CASES FIT THE POPULAR SIZED MOTHERBOARDS AND INCLUDE SPEAKERS, FACEPLATES, EXPANSION SLOTS, FRONT PANEL KEYLOCKS, LED INDICATORS AND ALL NECESSARY HARDWARE



XT STYLE FLIP-TOP \$34.95

XT STYLE SLIDE-TOP \$39.95

AT STYLE SLIDE-TOP \$89.95

JR. AT STYLE FLIP-TOP \$149.95

- INCLUDES 150 WATT POWER SUPPLY

POWER SUPPLIES

FOR IBM XT COMPATIBLE \$59.95

- UL APP. 135 WATTS
- +5V 15A, +12V 4.2A
- -5V .5A, -12V .5A

PS-135

PS-150 150W MODEL \$69.95



FOR IBM AT COMPATIBLE \$89.95

- 200 WATTS
- +5V 22A, +12V 8A
- -5V .5A, -12V .5A

PS-200



DIABLO PRINTER \$279⁹⁵

- LETTER QUALITY AT 20 CPS, 132 COLS
- 10, 12, 15 PITCH & PROPORTIONAL SPACING
- SERIAL & PARALLEL INTERFACE
- AUTO PAPER LOAD, FRICTION FEED
- FULL XEROX WARRANTY



CENTRONICS LASER \$1195 PRINTER

NEAR TYPESET QUALITY
AFFORDABLE AT LAST

- 8 PAGES PER MINUTE ■ 300 DPI RESOLUTION
- 1 YEAR WARRANTY ■ CHOICE OF EMULATION BOARDS

MULTI-PRINTER EMULATION BOARD:

- EPSON FX-80 EMULATION—NOTHING ELSE REQUIRED
- IBM PC GRAPHICS, PROPRINTER & DIABLO 630
- EMULATION REQUIRES ADDITIONAL FONT CARD

HP LJ+ EMULATION BOARD:


- HP LASERJET EMULATION—3 RESIDENT FONTS & 2 PITCHES ADDITIONAL FONT CARD AVAILABLE

1.5MB RAM CARD \$139.95

EXTRA FONT CARDS \$199.95

TONER CARTRIDGES \$59.95

PFS FIRST PUBLISHER \$99.95

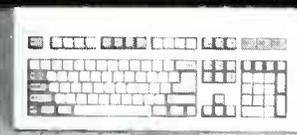

IBM COMPATIBLE KEYBOARDS

FULL ONE YEAR WARRANTY

IBM ENHANCED STYLE LAYOUT \$79.95

- AUTONSENSE FOR XT OR AT COMPATIBLES
- LED INDICATORS ■ AUTO REPEAT FEATURE
- SEPARATE CURSOR PAD

MCT-5339

IBM AT STYLE LAYOUT \$59.95

- SOFTWARE AUTONSENSE FOR XT OR AT COMPATIBLES
- LED INDICATORS ■ AUTO REPEAT FEATURE

MCT-5060

MAXI-SWITCH KEYBOARDS

ENHANCED STYLE LAYOUT \$84.95

- STANDARD ENHANCED KEYBOARD LAYOUT
- TACTILE FEEDBACK
- LIGHTED NUM, CAPS, AND SCROLL LOCK
- NUMERIC & CURSOR KEYPADS, 12" F" KEYS

MAX-5339

MAX-5060 MAXI-SWITCH, AT STYLE \$64.95

VGA COMPATIBLE PACKAGE

\$649⁰⁰

MONITOR & CARD TOGETHER



- 800 X 560 MAXIMUM RESOLUTION
- 640 X 480 IN 16 COLORS
- 320 X 200 IN 256 COLORS
- IBM STYLE ANALOG MONITOR
- FULLY VGA, EGA, CGA, HERCULES & MONOCHROME COMPATIBLE



NEC MULTISYNC \$599.95

- ORIGINAL CGA EGA VGA COMPATIBLE MONITOR
- AUTO FREQUENCY ADJUSTMENT
- RESOLUTION AS HIGH AS 800 X 560

CASPER EGA \$399.95

- 15.75 21 85 KHz SCANNING FREQUENCIES
- 640 X 200 350 RESOLUTION ■ 31 MM DOT PITCH
- 14" BLACK MATRIX SCREEN ■ 16 COLORS

CASPER RGB \$279.95

- COLOR GREEN AMBER SWITCH ■ 39MM DOT PITCH
- 640 X 240 RESOLUTION ■ 14" NON-GLARE SCREEN
- RGB IBM COMPATIBLE ■ CABLE INCLUDED

SAKATA MONOCHROME \$69.95

- IBM COMPATIBLE TTL INPUT
- 12" NON-GLARE SCREEN
- CABLE FOR IBM PC INCLUDED

SAMSUNG MONOCHROME MONITOR \$129.95

MONITOR STANDS

MODEL MS-100 \$12.95

- TILTS AND SWIVELS
- STURDY PLASTIC CONSTRUCTION

MODEL MS-200 \$39.95

- TILTS AND SWIVELS ■ BUILT-IN SURGE SUPPRESSOR
- INDEPENDENTLY CONTROLS UP TO 5 AC OUTLETS

LOGITECH MOUSE \$79⁹⁵



PC MAGAZINE'S EDITORS CHOICE
ALL MODELS HAVE SERIAL SUPPORT (COM1, COM2), 200 D.P.I. RESOLUTION, LOTUS 1-2-3 SHELL, SELF-INSTALLING SOFTWARE AND "POINT EDITOR"

SERIAL MOUSE W/PC PAINTBRUSH \$99.95

BUS MOUSE W/PC PAINTBRUSH \$99.95

BUS MOUSE W/PC PAINTBRUSH/CAD \$149.95

3.5" FLOPPY DISK DRIVE \$149⁹⁵



1.44 MB 3 1/2" DRIVE

- ULTRA HIGH DENSITY
- ALSO WORKS WITH 720K DISKS

FDD-1.44 x BLACK FACEPLATE \$149.95

FDD-1.44 x BEIGE FACEPLATE \$149.95

720K 3 1/2" FLOPPY DRIVE \$129.95

FDD-3.5 x (FORXT)

FDD-3.5 x (FORAT)

Seagate

NEW!
FAST 40MB DRIVE
\$529⁰⁰

THE NEW ST-251-1 DRIVE IS 30% FASTER WITH AN AVERAGE ACCESS TIME OF 28 MS. EASY TO INSTALL HALF-HEIGHT DRIVE.
ST-251-1

WITH MCT-HDC CONTROLLER \$569.00
WITH MCT-ATFH CONTROLLER \$639.00

1/2 HEIGHT DRIVES

- 20 MB, 65 MS, ST-225** \$225.00
WITH MCT-HDC CONTROLLER \$269.00
WITH MCT-ATFH CONTROLLER \$339.00
- 30 MB RLL, 65 MS, ST-238** \$249.00
WITH MCT-RLL CONTROLLER \$299.00
WITH MCT-ATFH-RLL CONTROLLER \$389.00
- 40 MB, 40 MS, ST-251** \$429.00
WITH MCT-HDC CONTROLLER \$469.00
WITH MCT-ATFH CONTROLLER \$539.00
- 60 MB RLL, 40 MS, ST-277** \$499.00
WITH MCT-RLL CONTROLLER \$549.00
WITH MCT-ATFH CONTROLLER \$639.00

FULL HEIGHT DRIVES

- 30 MB, 40 MS, ST-4038 \$559.00
- 80 MB, 28 MS, ST-4096 \$895.00

TEAC DISK DRIVE

360K 5 1/4 DRIVE
RELIABLE DIRECT DRIVE MOTOR
DOUBLE-SIDED/DOUBLE-DENSITY FD-55B

\$99⁹⁵

1/2 HEIGHT FLOPPY DISK DRIVES

- 5 1/4 TEAC FD-55G DS/HD 1.2M \$129.95
- 5 1/4 FUJITSU M2551A DS/DD 360K \$89.95
- 5 1/4 FUJITSU M2553K DS/HD 1.2M \$119.95
- 5 1/4 DS/DD 360K \$69.95
- 5 1/4 DS/HD 1.2M \$109.95
- 3 1/2 MITSUBISHI DS/DD (AT OR XT) \$129.95



INTERFACE CARDS FROM MODULAR CIRCUIT TECHNOLOGY DISPLAY ADAPTORS

MONOCHROME GRAPHICS CARD \$59.95
TRUE HERCULES COMPATIBILITY. SUPPORTS LOTUS 123
PARALLEL PRINTER PORT CONFIGURES AS CPT1 OR LPT2. USES VLSI CHIPS TO ENSURE RELIABILITY
MCT-MGP

ENHANCED GRAPHICS ADAPTOR \$149.95
100% IBM COMPATIBLE. PASSES IBM EGA DIAGNOSTICS
256K OF VIDEO RAM ALLOWS 640 X 350 IN 16 OF 64 COLORS. COMPATIBLE WITH COLOR AND MONOCHROME ADAPTORS
MCT-EGA

COLOR GRAPHICS ADAPTOR \$49.95
COMPATIBLE WITH IBM GRAPHICS STANDARDS
SUPPORTS RGB, COLOR & COMPOSITE MONOCHROME
840 320 X 200 RESOLUTION. LIGHT PEN INTERFACE
MCT-CG

MULTIFUNCTION CARDS

MONOGRAPHS MULTI I/O \$119.75
TOTAL SYSTEM CONTROL FROM A SINGLE SLOT!
CTRL 2 FLOPPY S, SERIAL, PARALLEL, GAME PORT, CLOCK CAL. RUN COLOR GRAPHICS SOFTWARE ON A MONOCHROME MONITOR
MCT-MGMIO

MULTI I/O FLOPPY CONTROLLER \$79.95
A PERFECT COMPANION FOR OUR MOTHERBOARDS
SUPPORTS UP TO 2 360K FLOPPIES, 720K WITH DOS 3.2
SERIAL, PARALLEL, GAME PORT, CLOCK CALENDAR
MCT-MIO
MIO-SERIAL—2ND SERIAL PORT \$15.95

MULTI I/O CARD \$59.95
USE WITH MCT-FH FOR A MINIMUM OF SLOTS USED
SERIAL PORT, CLOCK CALENDAR WITH BATTERY BACK-UP. PARALLEL PRINTER PORT ADDRESSABLE AS LPT1 OR LPT2
MCT-IO

AT MULTIFUNCTION CARD \$139.95
ADDS UP TO 3 MB OF RAM TO YOUR AT
USER EXPANDABLE TO 1.5 MB, OR 3 MB WITH OPTIONAL PIGGYBACK BOARD (0 K INSTALLED). INCLUDES SERIAL AND PARALLEL PORT
MCT-ATMF-MC PIGGYBACK BOARD \$29.95
ATMF SERIAL-2ND SERIAL PORT \$24.95

AT MULTI I/O CARD \$59.95
USE WITH MCT-ATFH FOR MINIMUM OF SLOTS USED
SERIAL, PARALLEL AND GAME PORTS. USES 16450 SERIAL SUPPORT CHIPS FOR HIGH SPEED OPS
MCT-ATIO
ATIO-SERIAL—2ND SERIAL PORT \$24.95

MEMORY CARDS

576K RAM CARD \$59.95
A CONTIGUOUS MEMORY SOLUTION IN A SHORT SLOT
USER SELECTABLE CONFIGURATION UP TO 576K
USES 64K & 256K RAM CHIPS (ZERO K INSTALLED)
MCT-RAM

EXPANDED MEMORY CARD \$129.95
2 MB OF LOTUS INTEL MICROSOFT COMPATIBLE MEMORY FOR AN XT. CONFORMS TO LOTUS INTEL EMS. USER EXPANDABLE TO 2 MB. CAN BE USED AS EXPANDED OR CONVENTIONAL MEMORY, RAMDISK AND SPOOLER
MCT-EMS
MCT-ATEMS AT COMPATIBLE VERSION \$139.95

DRIVE CONTROLLERS

FLOPPY DISK CONTROLLER \$29.95
QUALITY DESIGN FOR SINGLE SLOT CONTROL OF 4 FLOPPY'S. INTERFACES UP TO 4 FDD'S TO AN IBM PC OR COMPATIBLE. SUPPORTS BOTH DS DD AND DS QD WITH DOS 3.2
MCT-FDC

1.2 MB FLOPPY CONTROLLER \$69.95
ADD VERSATILITY AND CAPACITY TO YOUR XT
SUPPORTS 2 DRIVES, BOTH MAY BE 360K OR 1.2 MB
ALLOWS DATA TO FLOW FREELY FROM XT'S TO AT'S
MCT-FDC-1.2

FLOPPY/HARD CONTROLLER \$139.95
XT SYSTEM STRIVED FOR SLOTS? THIS CARD FREES ONE UP. INTERFACES UP TO 2 FDD'S & 2 HDD'S. CABLING FOR 2 FDD 1 HDD. SUPPORTS BOTH DS DD & DS QD WITH DOS 3.2
MCT-FH

AT/IFH CONTROLLER \$149.95
FLOPPY HARD DISK CONTROL IN A TRUE AT DESIGN
SUPPORTS UP TO 2 360K 720K 1.2MB FDD'S AS WELL AS 2 HDD'S USING STANDARD CONTROL TABLES
MCT-ATFH

RLL DISK CONTROLLER \$199.95
IMPROVE SPEED AND STORAGE OF YOUR AT COMPATIBLE. SUPPORTS UP TO 2 RLL HARD DISCS AND 2 FLOPPY DRIVES. SUPPORTS 360 720 1.2 MB FLOPPIES IN 5 1/4 & 3 1/2".
MCT-ATFH-RLL

ARCHIVE XL TAPE BACK-UP
\$369⁹⁵

- BACK UP 40 MB IN 40 MINUTES!
- EASY-TO-USE MENU DRIVEN SOFTWARE
- USES STANDARD QIC DATA FORMAT
- FULL & INCREMENTAL BACK-UP
- PARTIAL & FULL RESTORE

AR 5240 XT —FOR XT'S & AT S
AR 5540 AT — AT S ONLY, 2X FASTER
TAPE NOT INCLUDED
TAPE CARTRIDGE—40 MB \$24.95



20MB HARD DISK ON A CARD
\$349

- SAVES SPACE AND REDUCES POWER CONSUMPTION
- IDEAL FOR PC'S WITH FULL HEIGHT FLOPPIES
- LEAVES ROOM FOR A HALF-LENGTH CARD IN ADJACENT SLOT



“ JUST A NOTE TO LET YOU KNOW THAT MY SALESPERSON, HELEN MORSE, AT YOUR COMPANY HAS BEEN VERY HELPFUL AND COURTEOUS. THIS IS A PLEASANT CHANGE FROM MOST TELEPHONE SALESPeOPLE I DEAL WITH. PLEASE PASS MY THANKS TO HELEN. I PLAN ON DOING FREQUENT BUSINESS WITH JDR AS MY NEW COMPANY, ODEM INC. GETS GOING, AND HELEN'S ATTITUDE AND HELPFULNESS ARE A MAJOR REASON WHY I LIKE DOING BUSINESS WITH YOU. ”

R.C.K.
BENSALEM, PA

BARGAIN HUNTER'S CORNER
720K FLOPPY DISK DRIVE
BY MITSUBISHI

- 5 1/4" HALF-HEIGHT
- 96 T.P.I.
- 100% IBM COMPATIBLE
- DOUBLE-SIDED/QUAD DENSITY

ONLY \$69⁹⁵
SPECIAL ENDS 8/31/88

intel



INBOARD 386/PC
\$895.00

UPGRADE YOUR XT TO A 386 FOR LESS THAN \$1000
16 MHZ PROCESSOR REPLACES 8088. 1 MB INSTALLED. EXPAND TO 3MB WITH PIGGYBACK CARD
5 YR WARRANTY

INBOARD 386/AT \$1199.95
ABOVE BOARD PS 286 \$399.95
ABOVE BOARD 286 \$369.95

JDR MICRODEVICES, 110 KNOWLES DRIVE, LOS GATOS, CA 95030
LOCAL (408) 866-6200 FAX (408) 378-8927 TELEX 171-110

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1988 JDR MICRODEVICES

CONTINENTAL U.S. AND CANADA

CIRCLE 178 ON FREE INFORMATION CARD
www.americanradiohistory.com



BUILD YOUR OWN SYSTEM



**OVER 20,000 JDR SYSTEMS
HAVE ALREADY BEEN BUILT.
EASY TO ASSEMBLE IN JUST 2
HOURS WITH A SCREWDRIVER.
SAVE MONEY AND LEARN
ABOUT YOUR COMPUTER AT
THE SAME TIME.**

**12 MHZ AT
COMPATIBLE
\$1101⁷⁰**

- 12 MHZ BABY AT MOTHERBOARD
- 256K RAM MEMORY
- MINI-AT CASE W POWER SUPPLY
- AT STYLE KEYBOARD
- 1.2 MB FLOPPY DRIVE
- FLOPPY HARD DRIVE CONTROLLER
- MONOCHROME MONITOR
- GRAPHICS ADAPTOR

**10 MHZ XT
COMPATIBLE
\$656⁵⁰**

- INCLUDES SERIAL PORT, 2 PARALLEL PORTS, CLOCK CALENDAR AND GAME ADAPTOR. RUNS COLOR GRAPHICS ON A MONOCHROME MONITOR
- MOTHERBOARD
 - 256K RAM MEMORY
 - 135 WATT POWER SUPPLY
 - FLIP-TOP CASE
 - AT STYLE KEYBOARD
 - 360K FLOPPY DRIVE
 - MONOGRAPHS I/O CARD
 - MONOCHROME MONITOR

**16 MHZ
1 MB 386
\$2298⁶⁵**

- MYLEX 386 MOTHERBOARD
- 1 MB RAM ON BOARD
- 200 WATT POWER SUPPLY
- AT STYLE CASE
- ENHANCED AT STYLE KEYBOARD
- 1.2 MB FLOPPY DRIVE
- AT FLOPPY HARD CONTROLLER
- MONOCHROME MONITOR
- MONOGRAPHS CARD

**VIDEO
INSTRUCTIONS
\$4⁹⁵
WITH KIT PURCHASE**

**IT'S A JDR
EXCLUSIVE!
EASY TO FOLLOW
20 MINUTE VHS
TAPE SHOWS YOU
STEP-BY-STEP
HOW TO BUILD
AN XT COMPATIBLE
SYSTEM.
WITHOUT KIT
\$19.95**

MOTHERBOARDS

TURBO 4.77/8 MHZ \$99.95 12 MHZ MINI 80286 \$399.95

- 4.77 OR 8 MHZ OPERATION WITH 8088-2 & OPTIONAL 8087-2 CO-PROCESSOR
- FRONT PANEL LED SPEED INDICATOR AND RESET SWITCH SET SUPPORTED
- CHOICE OF NORMAL TURBO MODE OR SOFTWARE SELECT PROCESSOR SPEED

MCT-TURBO

MCT-XTMB STANDARD MOTHERBOARD \$87.95

- 6 MHZ, 10 MHZ (0.1 WAIT STATE), 12 MHZ (1 WAIT STATE)
- USES ZYMOS ASIC'S FOR LESS CHIPS. GREATER RELIABILITY
- SUPPORTS 256K-1024K MEMORY
- RE-CHARGEABLE HIGH CAPACITY NI-CAD BATTERY
- 6 16-BIT SLOTS, 2 8-BIT SLOTS
- MOUNTS IN STANDARD XT CASE

MCT-BATMB-12

MCT-BATMB 6/10 MHZ MINI 80286 BOARD \$389.95

80286 6/8 MHZ \$379.95 16 MHZ MYLEX 386 \$1649.00


- 8 SLOT (2 EIGHT BIT, 6 SIXTEEN BIT) AT MOTHERBOARD
- HARDWARE SELECTION OF 6 OR 8 MHZ
- 1 WAIT STATE
- KEYLOCK SUPPORTED. RESET SWITCH, FRONT PANEL LED INDICATOR
- SOCKETS FOR 1 MB OF RAM AND 80287
- BATTERY BACKED CLOCK

MCT-ATMB

- 1 MB RAM ON BOARD
- 8 SLOTS, 2 8-BIT, 6 16-BIT
- SUPPORTS 80287 MATH CO-PROCESSOR
- SUPPORTS 80387 W ADAPTOR
- 64 KB CACHE FOR NEAR 0 WAIT STATE
- USES AMI BIOS

MCT-386 MB

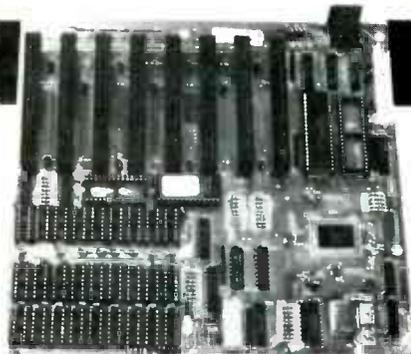MCT-386 MB-4 4 MB MEMORY INSTALLED \$2649.00
MCT-386 MB-MCB MATH CO-PROCESSOR ADAPTOR BOARD \$149.00



**10 MHZ SINGLE CHIP XT
\$129⁹⁵**

- SINGLE CHIP USES LESS POWER - IMPROVES RELIABILITY
- KEY SELECTABLE SPEED 4.77 MHZ OR 10 MHZ
- 2-3 TIMES FASTER THAN A STANDARD
- RESET SWITCH, KEYLOCK AND SPEED POWER INDICATORS SUPPORTED

MCT-TURBO-10

DEVELOPMENT TOOLS

**EPROM
PROGRAMMER
\$129⁹⁵**

- PROGRAMS 27XX & 27XXX EPROMS UP TO 27512
- SUPPORTS VARIOUS PROGRAMMING FORMATS AND VOLTAGES
 - SPLIT OR COMBINE CONTENTS OF SEVERAL EPROMS OF DIFFERENT SIZES
 - READ, WRITE, COPY, ERASE CHECK AND VERIFY
 - SOFTWARE FOR HEX AND INTEL HEX FORMATS

MCT-EPROM

MCT-EPROM-4 4 GANG PROGRAMMER \$189.00
MCT-EPROM-10 10 GANG PROGRAMMER \$299.95
MCT-PAL PAL PROGRAMMER \$269.95
MCT-MP PROCESSOR PROG. \$199.95



- 1 YEAR WARRANTY ON MCT PRODUCTS
- 30 DAY MONEY BACK GUARANTEE
- TOLL-FREE TECHNICAL SUPPORT
- NEXT DAY AIR SHIP AVAILABLE

JDR Microdevices®

JDR MICRODEVICES, 110 KNOWLES DRIVE, LOS GATOS, CA 95030

LOCAL (408) 866-6200 FAX (408) 378-8927 TELEX 171-110

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1988 JDR MICRODEVICES




CONTINENTAL U.S. AND CANADA

CIRCLE 177 ON FREE INFORMATION CARD
www.americanradiohistory.com

Radio Shack Parts Place™

EXCLUSIVE VALUES AT THE SHACK® NEAR YOU

"Hotline" Service for Rare Parts

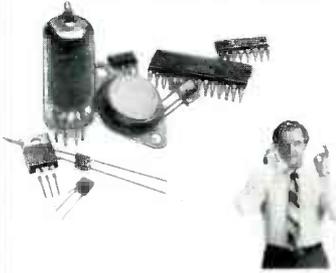

If the part you need is not in our regular stock, we'll check our substitution guide and special order it for you. Over 200,000 substitutions available, including ICs, microprocessors and support chips, tubes, crystals, phono cartridges, transistors, hybrid modules, and Sams Photo-facts. The order will be sent to your local Radio Shack in about a week. No minimum and no shipping charges!

Enhanced-Novice Exam "Prep" Kit

Everything You Need to Quickly And Painlessly Prepare for The New FCC Exam

Take advantage of the new enhanced Novice privileges on Amateur radio! This package quickly prepares you for the voice-class license. You get two audio cassettes for self-paced Morse code learning plus practice exam questions and answers to help you get ready for the test. #62-2402 19.95



Voice Synthesis Pair—23%-30% Off



9⁹⁵ Reg. 12.95 **11⁸⁸** Reg. 16.95

SPO256-AL2 Speech Synthesizer IC. Cut 23%. Built-in program makes it easy to interface with most computers. Requires 3.12 MHz crystal. With data and circuit examples. 28-pin DIP. #276-1784 Sale 9.95

CTS256-AL2 Text-to-Speech IC. 30% Off. Preprogrammed to translate ASCII characters into control data for synthesizer chip (above) for RS-232 hookup. Requires 10 MHz crystal. 40-pin DIP. #276-1786 Sale 11.88

Advanced ICs—Slashed 21% to 43%




3⁹⁹ Reg. 6.95 **7⁸⁸** Reg. 9.95

TLC548 8-Bit A/D Converter IC. 43% Off. Complete data acquisition system in one IC. High-speed data transfer with few external components. Single 5VDC supply, internal clock. #276-1796 Sale 3.99


AY-3-8910A Sound Generator IC. Cut 21%. Use with a computer to provide a spectacular variety and range of sounds! Three independent analog outputs. Single 5 VDC supply. 40-pin DIP. With data. #276-1787 Sale 7.88

Computer Helpers

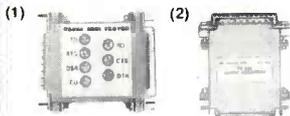

- (1) RS-232 Tester. LEDs indicate status of TD, RTS, DSR, CD, RD, CTS, DTR lines. #276-1401 . . . 14.95
- (2) RS-232 Spike Protector. Stops transients dead in their tracks. #276-1402 16.95

Builder Bargains

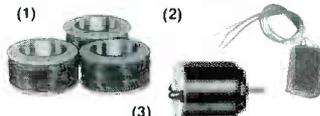


- (1) Magnet Wire. Three-spool set—22, 26, 30 gauge. #278-1345 . . . 4.79
- (2) 1:1 Audio Transformer. #273-1374 3.49
- (3) 1.5-3 VDC Motor. #273-223 89¢

Parts-Pourri



- (1) Fuse Holder Clips. #270-739 . . . 2/99¢
- (2) 8-"AA" Bat. Holder. #270-387 . . . 1.29
- 4-"AA" Battery Holder. #270-383 . . . 99¢
- 2-"AA" Battery Holder. #270-382 . . . 99¢
- (3) 9-Volt Battery Clips. #270-325 . . . 5/99¢
- (4) Thermal Fuse. 139° C. #270-1320 . . 1.19
- Thermal Fuse. 226° C. #270-1321 . . . 1.19

Sight 'n Sound

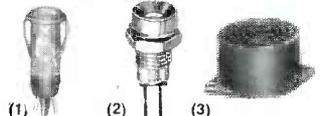

- (1) Super-Bright Panel LED. Brilliant 500 mcd ruby light. #276-088 1.79
- (2) LEDs in Chrome Holders. Red LED. #276-068 1.89
- Green LED. #276-069 1.89
- (3) Melodic IC Chime. #273-071 8.69

4000-Series CMOS

Low As

99¢

With Specs




Description	Type	Cat. No.	Each
Quad NOR GATE	4001	276-2401	99
Quad NAND Gate	4011	276-2411	99
Dual Type-D	4013	276-2413	1.19
Flip Flop	4049	276-2449	1.19
Hex Inverter	4049	276-2449	1.19
Decade Counter/Divider	4017	276-2417	1.49

Hard-to-Find Parts




- (1) 335 pF Variable Cap. Two-section, PC-mount. #272-1337 4.95
- (2) 6-50 pF Trimmer Caps. #272-1340 2/1.59
- (3) TV Colorburst Crystal. 3.579545 MHz. #272-1310 1.69

Irresistibles

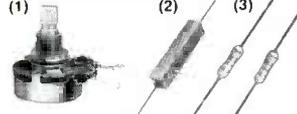

- (1) 25-Ohm, 5W Rheostat. #271-265, 2.99
- (2) 8-Ohm, 20W Resistor. #271-120 1.39
- (3) Metal-Oxide Resistors. 10 Ohms. #271-151 Pkg. 2/29¢
- 100 Ohms. #271-152 Pkg. 2/29¢
- 1000 Ohms. #271-153 Pkg. 2/29¢


Relays & Switches

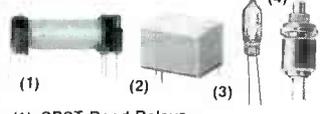

- (1) SPST Reed Relays. Contacts. 1A, 125VAC.

Coil	Cat. No.	Each
5VDC, 20 mA, 250 Ω	275-232	1.89
12VDC, 11 mA, 1050 Ω	275-233	1.89
- (2) Mini SPDT Relay. #275-248 . . . 2.99
- (3) Mercury Switch. #275-027 1.29
- (4) Momentary Switch. #275-1571 . . . 2/2.39

Builders Bargain Corner

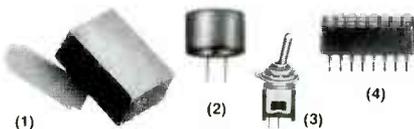

- (1) Box With PCB. 2 1/8 x 3 9/16 x 1 3/8". #270-283 3.99
- As Above. 2 3/4 x 4 3/16 x 1 1/4". #270-284 4.99
- (2) Electret Mike Element. PC mount. #270-090 . . . 1.49
- (3) Mini SPST Toggle Switch. #275-645 1.99
- (4) 8-Position DIP Switch. #275-1301 1.79

Solderless Breadboard

Popular Choice Of "Pros" and Students



The 2 1/4 x 6 1/2" universal board is mounted on a 4 x 7" "stay-put" steel base. Accepts DIPs, discrete components and up to 22-gauge wire. Has 640 plug-in tie points and three binding posts for external power. #276-169 19.95

Pocket Autoranging DVM

24⁹⁵

- Autopolarity
- Diode-Checker



A lot of meter in a little package! "Beep" continuity, low-battery indicator. Measures to 400 volts AC/DC, resistance to 2 megohms 4 1/2 x 2 1/8 x 5/16". With batteries, miniprobes and folding case. #22-171 24.95

Over 1000 items in stock: Binding Posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Coax, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multitesters, PC Boards, Plugs, Rectifiers, Resistors, Switches, Tools, Transformers, Wire, Zeners, More!

Prices apply at participating Radio Shack stores and dealers

Radio Shack®
The Technology Store™


A DIVISION OF TANDY CORPORATION

Now Available...Jameco's NEW Summer Flyer #137 with 48 pages of Computer Peripherals, Components & More!

MEMBER
MMC
MICROCOMPUTER
MARKETING COUNCIL
of the Direct Marketing Association, Inc.

PROTOTYPING PRODUCTS

Jameco Solderless Breadboard Sockets

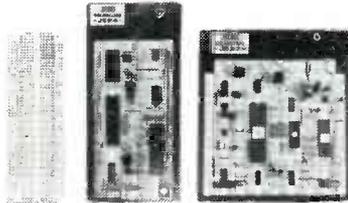

Part No.	Dim. L x W	Contact Points	Binding Posts	Price
JE20	6 1/2 x 3/4	200	0	\$ 2.29
JE21	3 1/4 x 2 1/8	400	0	\$ 4.49
JE22	6 1/2 x 1 3/8	630	0	\$ 5.95
JE23	6 1/2 x 2 1/8	830	0	\$ 7.49
JE24	6 1/2 x 3 1/8	1,360	2	\$14.95
JE25	6 1/2 x 4 1/8	1,660	3	\$22.95
JE26	6 1/2 x 5 1/8	2,390	4	\$27.95
JE27	7 1/4 x 7 1/8	3,220	4	\$37.95

Jameco's IBM PC/XT/AT Compatible Motherboards



Award BIOS ROMs included

Part No.	Speed	Price
JE1001	4.77/8MHz (PC/XT)	\$ 99.95
JE1002	4.77/10MHz (PC/XT)	\$119.95
JE1007	6/8/10/12MHz (AT)	\$349.95

2 & 3MB Memory Expansion Cards for IBM AT and Compatibles




Part No.	Description	Price
JE1081	2MB of expanded or extended memory (zero-K on-board) (AT)	\$119.95
JE1082	3MB of expanded or extended memory, parallel printer port, serial port and game port (zero-K on-board) (AT)	\$169.95

Jameco Computer Power Protection



Part No.	Description	Price
JE1190	Power Base	\$29.95
JE1191	6-Outlet Power Strip	\$11.95

IBM PC/XT/AT Compatible Keyboards

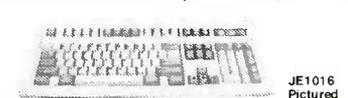

• Tactile touch keyswitches • Switch selectable between PC/XT or AT • Illuminated Caps Lock, Num Lock and Scroll Lock

JE1015... \$59.95

• Enhanced keyboard layout • Illuminated Num Lock, Caps Lock and Scroll Lock • Automatically switches between PC/XT or AT

JE1016... \$79.95

DATA BOOKS

400041	NSC Linear Data Book-Vol. I (87)	\$14.95
400042	NSC Linear Data Book-Vol. II (87)	\$ 9.95
400043	NSC Linear Data Book-Vol. III (87)	\$ 9.95
210830	Intel Memory Handbook (87)	\$17.95
230843	Intel Microsystem Hndbk. Set (87)	\$24.95

IBM AT COMPATIBLE KIT Mini-286 6/8/10/12MHz Kit

JE1007	Baby AT Motherboard (Zero-K RAM - includes Award BIOS ROMs)	\$349.95
JE1015	XT/AT Style Keyboard	\$ 59.95
JE1017	Baby AT Flip-Top Case	\$ 69.95
JE1022	5 1/4" Hi-Density Disk Drive	\$109.95
JE1032	200 Watt Power Supply	\$ 89.95
JE1043	360K/720K/1.2M Floppy Controller Card	\$ 49.95
JE1065	Input/Output Card	\$59.95

Regular List \$789.65

SAVE \$99.70!

JE1059 \$519.95 (EGA Monitor and Card not included)

JE2009*	IBM AT Compatible Kit	\$689.95
JE286M	JE2009 Technical Manual	\$29.95

*RAM not included - Minimum RAM configuration 512K (18 Chips 41256-120, see left)

IBM COMPATIBLE DISPLAY MONITORS

12" Amber Monochrome - TTL Input, High Resolution (PC/XT/AT) AMBER... \$99.95

14" RGB Color - CGA Compatible Amber/Green/Color Switchable, 640 x 200 Resolution (PC/XT/AT) TTX1410... \$279.95

14" EGA Color - EGA/CGA Compat., 720 x 350 Max. Resolution (PC/XT/AT) TE5154... \$399.95

14" Multiscan Color - VGA/PGA/EGA compatible, 800 x 600 Max. Resolution (PC/XT/AT) CTX1435... \$549.95

EGA/VGA MONITOR AND CARD SPECIALS

14" EGA Monitor and EGA Card - EGA compatible, 720 x 350 Max. Resolution - displays up to 16 colors (PC/XT/AT) JE1059... \$519.95

13" VGA Monitor and VGA Card - VGA compatible, 800 x 560 Max. Resolution - displays up to 256 colors (PC/XT/AT) JE1059... \$649.95

IBM PC/XT/AT COMPATIBLE CARDS

Graphic Display Cards **MGA, CGA or EGA!** JE1050

JE1050	Mono Graphics Card w/Printer Port (PC/XT/AT)	\$59.95
JE1052	Color Graphics Card w/Printer Port (PC/XT/AT)	\$49.95
JE1055	EGA Card with 256K Video RAM (PC/XT/AT)	\$169.95
JE1071	Multi I/O with Drive Controller and Mono Graphics (PC/XT)	\$119.95

Multifunction, I/O and Expansion Cards

JE1060	I/O Card with Serial, Game, Parallel Printer Port and Real Time Clock (PC/XT)	\$59.95
JE1061	RS232 Serial Half Card (PC/XT/AT)	\$29.95
JE1065	I/O Card with Serial, Game and Parallel Printer Port (AT)	\$59.95
JE1078	Expand to 384K (zero-K on-board) Multifunc. w/Serial, Game, Parallel Printer Port & Real Time Clock (PC/XT)	\$69.95

Floppy and Hard Disk Controller Cards

JE1040	360KB Floppy Disk Drive Controller Card (PC/XT)	\$29.95
JE1041	20/40MB Hard Disk Controller Card (PC/XT)	\$79.95
JE1043	360K/720K/1.2MB Floppy Disk Cont. Card (PC/XT/AT)	\$49.95
JE1045	360K/720K/1.2MB Floppy/Hard Disk Controller Card (AT)	\$149.95

COMPUTER PERIPHERALS



Seagate 20,30 40 and 60MB Half Height Hard Disk Drives

Part No.	Description	Price
ST225	20MB Drive only (PC/XT/AT)	\$224.95
ST225XT	20MB w/Controller (PC/XT)	\$269.95
ST238	30MB Drive only (PC/XT/AT)	\$249.95
ST238XT	30MB w/Controller (PC/XT)	\$299.95
ST238AT	30MB w/Controller (AT)	\$389.95
ST251	40MB Drive only (PC/XT/AT)	\$429.95
ST251XT	40MB w/Cont. Card (PC/XT)	\$469.95
ST251AT	40MB w/Controller Card (AT)	\$539.95
ST277	60MB Drive only (PC/XT/AT)	\$499.95
ST277AT	60MB w/Controller Card (AT)	\$639.95



Jameco 5.25" PC/XT & AT Compatible Disk Drives

Part No.	Description	Price
JE1020	360K Black Bzl. (PC/XT/AT)	\$ 89.95
JE1021	360K Beige Bzl. (PC/XT/AT)	\$ 89.95
JE1022	1.2MB Beige Bzl. (PC/XT/AT)	\$109.95



Toshiba 3.5" PC/XT/AT Compatible Disk Drive

352KU	3.5" 720KB (Bezels and Installation Kit incl.) (PC/XT/AT)	\$129.95
-------	---	----------

2400/1200/300 Modems



Datatronics • Hayes command compatible • Bell 103/212A compatible • Auto-dial/auto-answer • FCC approved 1-year warranty • Includes MaxiVite Communication Software

1200H	1200/300 Baud Internal Modem	\$ 69.95
2400S	2400/1200/300 Internal Modem	\$139.95
1200C	1200/300 Baud External Modem	\$119.95
2400E	2400/1200/300 External Modem	\$179.95

Jameco Extended 80-Column Card for Apple IIe




• 80 Col./64K RAM • Doubles amount of data your Apple IIe can display as well as its memory capacity • Ideal for word processing • Complete with instructions

JE864	\$39.95
-------	---------


ADD12 (Disk Drive II, II+, IIe) \$99.95

TEST EQUIPMENT

Digital Multimeters

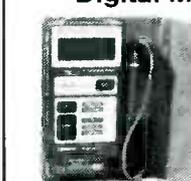

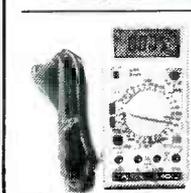Kingdome KD302: • Pocket Size in handy carry case • 3 1/2 Digit LCD • Auto or manual ranging • Audible continuity tester • Tests: AC/DC Voltage, Resistance and Continuity • One Year Warranty • Size: 4 1/4" x 2 1/4" x 1 1/4"




Metex M4650: • Handheld high accuracy • 4 1/2 Digit LCD • Manual ranging with Overload Protection • Audible continuity tester • Tests: AC/DC Voltage, Resistance, Continuity Capacitance, Frequency • One Year Warranty • Size: 7 1/2" x 3 1/2" x 1 1/4"

M4650	\$89.95
-------	---------

U.S. Funds Only
Shipping: Add 5% plus \$1.50 Insurance
(May vary according to weight)

California Residents:
Add 6%, 6 1/2% or 7%
Sales Tax
FAX: 415-592-2503

9/88

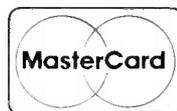

Data Sheets - 50¢ each
Prices Subject to Change

Send \$1.00 Postage for a
FREE 1988 CATALOG

Telex: 176043

©1988 Jameco Electronics

1355 Shoreway Rd., Belmont, CA 94002 • 24 HR. ORDER HOTLINE 415-592-8097 • All Other Inquiries (7am-5pm PST) 415-592-8121

CIRCLE 114 ON FREE INFORMATION CARD

www.americanradiohistory.com



AK, Puerto Rico - 218 881-6674 Telux - 6287914 FAX - 218-881-3380 TWX - 913050882 DIGI KEY CORP

-80-344-4539-

INTEGRATED CIRCUITS

Table with columns: Part, Price, Description. Includes 7400 TTL and 74500 TTL series.

Micro.

Table with columns: Part, Price, Description. Includes various microprocessors and controllers.

Interface

Table with columns: Part, Price, Description. Includes interface ICs for various protocols.

A/D & D/A

Table with columns: Part, Price, Description. Includes analog-to-digital and digital-to-analog converters.

Memory

Table with columns: Part, Price, Description. Includes various types of memory chips.

NEC MEMORY CHIPS

Table with columns: Part, Price, Description. Includes NEC brand memory chips.

NEC MICROPROCESSOR CHIPS

Table with columns: Part, Price, Description. Includes NEC brand microprocessors.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

4000 CMOS

Table with columns: Part, Price, Description. Includes 4000 series CMOS ICs.

74150 TTL

Table with columns: Part, Price, Description. Includes 74150 series TTL ICs.

74150 TTL

Table with columns: Part, Price, Description. Includes 74150 series TTL ICs.

74150 TTL

Table with columns: Part, Price, Description. Includes 74150 series TTL ICs.

74150 TTL

Table with columns: Part, Price, Description. Includes 74150 series TTL ICs.

74150 TTL

Table with columns: Part, Price, Description. Includes 74150 series TTL ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

7400 CMOS

Table with columns: Part, Price, Description. Includes CMOS versions of 7400 series ICs.

1% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 1% metal oxide film resistors.

5% WIREWOUND REC. RESISTORS

Table with columns: Part, Price, Description. Includes 5% wirewound resistor assemblies.

DISC CAPACITORS

Table with columns: Part, Price, Description. Includes disc capacitors.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC V SERIES

Table with columns: Part, Price, Description. Includes Panasonic V series components.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC B-SERIES

Table with columns: Part, Price, Description. Includes Panasonic B-series components.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC B-SERIES

Table with columns: Part, Price, Description. Includes Panasonic B-series components.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC B-SERIES

Table with columns: Part, Price, Description. Includes Panasonic B-series components.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC B-SERIES

Table with columns: Part, Price, Description. Includes Panasonic B-series components.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC B-SERIES

Table with columns: Part, Price, Description. Includes Panasonic B-series components.

5% METAL OXIDE FILM RESISTORS

Table with columns: Part, Price, Description. Includes 5% metal oxide film resistors.

TRANSFORMERS

Table with columns: Part, Price, Description. Includes various types of transformers.

PANASONIC B-SERIES

Table with columns: Part, Price, Description. Includes Panasonic B-series components.

The Dig Key volume discount and service charges are subject to apply. Most items sold by Dig Key may be compared to a volume discount. Items that are not discountable are identified by the suffix 'ND'. No pricing the part number. After writing your order, attach a copy of this information and apply the appropriate discount. To this information, add the non-discountable items. There are other discounts available. We will ship and process your order to the address in the U.S.A., Canada and Mexico when check or money order accompanies order. Dig Key only ships orders within the continental U.S., Alaska, Hawaii, Canada and Mexico.

WHEAT ORDER BY PHONE. Call 1-800-344-4539. FAX. MAIL SEND YOUR ORDER TO: DIGI KEY, P.O. Box 877, Thayer River Falls, MN 56701. You may pay by check, money order, MasterCard, VISA or C.O.D. DIGI KEY GUARANTEE. Any parts or products purchased from Dig Key that prove to be defective will be replaced or refunded if returned within 90 days from receipt with a copy of your invoice. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

CIRCLE 82 ON FREE INFORMATION CARD

www.americanradiohistory.com

SEND FOR
FREE
1988 CATALOG...
56 PAGES

★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING

ALL ELECTRONICS CORP.

WE STOCK OVER
4,000 ITEMS...
CALL OR WRITE FOR OUR
FREE
CATALOG OF PARTS!



RESISTORS • CAPACITORS • DIODES • CABLES •
BRIDGE RECTIFIERS • CHOKE COILS • CRYSTALS •
CRIMP CONNECTORS • LAMPS • HEAT SINKS • MO-
TORS • SUB MINIATURE D CONNECTORS • TRANSIS-
TORS • I.C.'S • PROTO BOARDS • POTENTIOMETERS •
POWER SUPPLIES • JACKS • PLUGS • SWITCHES •
PERF BOARDS • FANS • FUSES • SHRINK TUBING • TIE
WRAPS • TOOLS • KEYPADS • VIDEO ACCESSORIES •
RELAYS • S.C.R.'S • TRANSFORMERS • TELEPHONE
ACCESSORIES • RIBBON CABLE • CIRCUIT
BREAKERS • VOLTAGE REGULATORS •
AND MANY OTHER ITEMS...

TRANSISTORS

CAT#	TYPE	CASE	PRICE
PN2222	NPN	TO-92	5 for .75
2N2904	PNP	TO-5	3 for \$1.00
2N2906	PNP	TO-18	3 for \$1.00
PN2907	PNP	TO-92	5 for .75
2N3055	NPN	TO-3	\$1.00 each
PN3569	NPN	TO-92	5 for .50
2N3904	NPN	TO-92	5 for .75
2N3906	PNP	TO-92	5 for .75
2N4400	NPN	TO-92	5 for .75
2N4402	PNP	TO-92	5 for .75
2N5400	PNP	TO-92	4 for \$1.00
2N5880	PNP	TO-3	\$2.00 each
2N5882	NPN	TO-3	\$2.00 each
MJ2955	PNP	TO-3	1.50 each
MJE2955T	PNP	TO-220	.75 each
MJE3055T	NPN	TO-220	.75 each
TIP30	NPN	TO-220	.75 each
TIP31	NPN	TO-220	.75 each
TIP32	PNP	TO-220	.75 each
TIP41	NPN	TO-220	.75 each
TIP42	PNP	TO-220	.75 each
TIP121	NPN	TO-220	.75 each
TIP126	PNP	TO-220	.75 each

10 AMP SOLID STATE RELAYS



ELECTROL# S2181
CONTROL:
Rated 5.5 to 10 Vdc
(will operate on 3-32 Vdc)
LOAD:
10 Amp @ 240 Vac
2 1/4" X 1 3/4" X 7/8"
CAT# SSRLY-10B
\$9.50 each
QUANTITY DISCOUNT!
10 for \$85.00
25 for \$175.00
50 for \$300.00
100 for \$500.00

SWITCHES

MINIATURE TOGGLE SWITCHES
all rated 5 Amps

S.P.D.T. (on-on)
Solder lug terminals.
CAT# MTS-4
\$1.00 each
10 for \$9.00



S.P.D.T. (on-on)
Non threaded bushing.
P.C. mount.
CAT# MTS-40PC
75c each
10 for \$7.00



D.P.D.T. (on-on)
Solder lug terminals.
CAT# MTS-8
\$2.00 each
10 for \$19.00



PIEZO WARNING DEVICE

Murata Erie #
PKB8-4A0
High pitched
audible alarm.
Operates on
3 - 20 Vdc @ 20 ma. 1" high
X 7/8" dia. P.C. board mount.
CAT# PBZ-84 \$1.75 each



SOUND ACTIVATED BOARD

Designed to react to high pitched sounds. Each board contains many useful parts including a condenser mike. Operates on 6 Vdc. Instructions included.
CAT# SAB \$2.50 each



24 VOLT D.C. SOLENOID

Intermittent duty cycle. 240 ohm coil.
Mounting flange is 1 1/8" wide.
Solenoid body 1 1/2" X 1/2" X 1/2".
CAT# SOL-34 \$1.00 each • 10 for \$8.50
100 for \$75.00 Large Quantity Available



MINI PUSH BUTTON

S. P. S. T. momentary.
Push to make. 1/4" threaded bushing.
Red button.
CAT# MPB-1
35c each • 10 for \$3.25



SOUND & VIDEO MODULATOR

TI# UM1381-1.
Designed for use with T.I. computers. Can be used with video cameras, games, or other audio/video sources. Built in A/B switch enables user to switch from T.V. antenna without disconnection. Operates on channel 3 or 4. Requires 12 Vdc. Hook up diagram included.
CAT# AVMOD \$5.00 each



GRAB BAGS \$1.00 EACH

50 ASSORTED DISC CAPS. Cut leads. Many common values. Some are 500 volts.
CAT# GRABDC

ASSORTED 1/4 WATT RESISTORS
Approximately 200 pieces of assorted values, some cut leads.
CAT# GRES

ASSORTED PARTS
Strips of 100 assorted parts. Each strip contains an assortment of resistors, capacitors, diodes, coils, etc. 100 pieces.
CAT# GRABTR

15 VALUES OF ELECTROLYTICS
Assortment contains 15 values of 1 mfd and up. Some cut leads.
CAT# GRABCP

N-CHANNEL MOSFET

IRF-511 TO-220 case
CAT# IRF 511
\$1.00 each
10 for \$9.00
LARGE QUANTITY AVAILABLE...



ITT PUSH BUTTON

ITT MDPL series. 3/4" X 1/2" gray rectangular key cap. S.P.S.T. N.O. Push to close.
RATED:
0.1 amp switching,
0.25 amp carry current. P.C. mount
CAT# PB-8 65c each
10 for \$6.00 • 100 for \$50.00



HALL EFFECT SWITCH

MICROSWITCH #4BE3
Slanted keyboard switch with hall effect sensor.
Snaps into 5/8" square chassis hole. Hall effect sensor slides easily from switch and can be used in other applications.
CAT# HESW 4 for \$1.00
10 for \$2.00
100 for \$15.00




XENON TUBE

1" long flashtube prepped with 3 1/2" red and black leads. Ideal for electronic flash or strobe projects.
CAT# FLT-3 2 for \$1.00



NEW! STROBE KIT

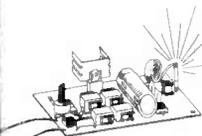
Variable rate strobe kit, flashes between 60 to 120 times per minute. Will operate on either 6 or 12 Vdc depending upon how you wire the circuit. Comes complete with P.C. board and instructions for easy assembly.
CAT# STROBE-1 \$7.50 each



NICKEL-CAD (RECHARGEABLE) BATTERIES

SPECIAL AAA SIZE

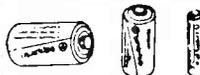Panasonic # P-18AAA
1.2 volt @ 180 mAh
CAT# NCB-AAAX
\$1.50 each
10 for \$13.50
100 for \$125.00
LARGE QUANTITIES



AA SIZE \$2.00 each
1.25 Volts 500 mAh
CAT# NCB-AA

AA SIZE \$2.20 each
WITH SOLDER TABS
CAT# NCB-SAA

C SIZE \$4.25 each
1.2 Volts 1200 mAh
CAT# NCB-C

D SIZE \$4.50 each
1.2 Volts 1200 mAh
CAT# NCB-D

WALL TRANSFORMERS

ALL PLUG DIRECTLY INTO 120 VAC OUTLET



6 Vdc @ 200 ma. \$2.25
CAT# DCTX-620

6 Vdc @ 750 ma. \$3.50
CAT# DCTX-675

9 Vdc @ 250 ma. \$2.50
CAT# DCTX-925

12 Vac @ 930 ma. \$3.50
CAT# ACTX-1293

18 Vac @ 1 Amp. \$3.50
CAT# ACTX-1885

PROTO BOARD



Large enough to design most experimental circuits. This proto board measures 6 3/4" X 2 1/2". Contains main board and two power buss strips.
CAT# PB-101 \$9.00 each

WATER TIGHT ENCLOSURE

ROSE# 02081905
Molded fiberglass enclosure with neoprene gasket.
2" X 3" X 7 1/2". Light blue.
CAT# WP-905 \$7.50 each



FULL WAVE BRIDGE RECTIFIERS

10 AMP 200 P.I.V.
5/8" SQUARE

CAT# FWB-1020
\$1.00 each • 10 for \$9.00

25 AMP RATING
1 1/8" SQUARE
metal epoxy filled case

200 P.I.V. \$2.50 each
CAT# FWB-252
400 P.I.V. \$3.00 each
CAT# FWB-254
600 P.I.V. \$3.50 each
CAT# FWB-256



MAIL ORDERS TO:
ALL ELECTRONICS
P.O. BOX 567
VAN NUYS, CA 91408

TWX-5101010163
(ALL ELECTRONIC)

OUTSIDE THE U.S.A.
SEND \$1.50 POSTAGE
FOR A CATALOG!!

TOLL FREE
800-826-5432

INFO: (818)904-0524
FAX: (818)781-2653
MINIMUM ORDER \$10.00
QUANTITIES LIMITED

CALIF. ADD SALES TAX
USA: \$3.00 SHIPPING
FOREIGN ORDERS
INCLUDE SUFFICIENT
SHIPPING.
NO C.O.D.



STORES:

LOS ANGELES
905 S. VERMONT AVE.
LOS ANGELES, CA 90006
(213)380-8000

VAN NUYS
6228 SEPULVEDA BLVD.
VAN NUYS, CA 91411
(818)997-1806

LIGHT EMITTING DIODES (L.E.D.)

STANDARD JUMBO LED
DIFFUSED
T 1-3/4 size

RED 10 for \$1.50
CAT# LED-1 100 for \$13.00
1000 for \$110.00

GREEN 10 for \$2.00
CAT# LED-2 100 for \$17.00
1000 for \$150.00

YELLOW 10 for \$2.00
CAT# LED-3 100 for \$17.00
1000 for \$150.00

FLASHING LED

with built in flashing circuit operates on 5 volts...

RED \$1.00 each
CAT# LED-4 10 for \$9.50

GREEN \$1.00 each
CAT# LED-4G 10 for \$9.50

BI-POLAR LED

Lights RED one direction, GREEN the other. Two leads.
CAT# LED-6 2 for \$1.70

LED HOLDER

Two piece holder.
CAT# HLED 10 for 65c

CLIPLITE LED HOLDER

Makes a L.E.D. look like a fancy indicator. Fits T 1-3/4 size LED.
CLEAR CAT# HLDCL-C
RED CAT# HLDCL-R
GREEN CAT# HLDCL-G
YELLOW CAT# HLDCL-Y



ADVERTISING INDEX


RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

NEW ACCESSORIES FOR THE MOTION CONTROL SYSTEM

SCANNER CONNECTS TO THE VIDEO LOGIC BOARD AND ALLOWS THE SYSTEM TO MONITOR 92 SWITCH/RELAY CONTACTS. ASSEMBLED & TESTED. ORDER NUMBER 50/04. ADD \$4 FOR SHIPPING & HANDLING. **\$35.00**

SPIN CONNECTS TO THE SERIAL PORTS AND ALLOWS PULSE WIDTH MODULATION OF TWO DC SERVO MOTORS. TRANSPARENT TO NORMAL USE OF SERIAL PORTS. OPTICAL ENCODER FEED BACK KEEPS THE MOTORS UNDER CONTROL! INCLUDES REFLECTIVE LEDS, ENCODER DISKS, DRIVER KIT, AND SOFTWARE. H PATTERN DRIVERS ALLOW FORWARD & REVERSE FROM ONE 12 VOLT POWER SUPPLY. FOR USE WITH MOTORS UP TO .6 AMPS AT 12 VDC. ORDER NUMBER 50/05. ADD \$4 FOR SHIPPING & HANDLING. **\$59.00**

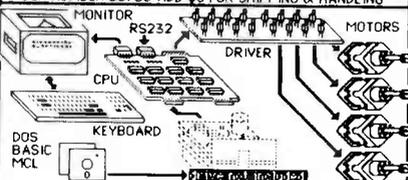POWER 8 AMPS OF POWER FOR LARGER MOTORS. OUTPUT MAY BE SPLIT TO DRIVE 2 4AMP MOTORS. OR USE 2 TO DRIVE ONE 16 AMP MOTOR. ORDER NUMBER 50/06. ADD \$3 FOR SHIPPING & HANDLING. **\$19.99**



- GENERAL PURPOSE 64K SINGLE BOARD COMPUTER
- AMBER MONITOR WITH 80 BY 24 LINES DISPLAY
- QUALITY KEYBOARD WITH KEYPAD & FUNCTION KEYS
- 4 "EASY STEPPER" MOTORS AND DRIVER KIT
- PDS/DOS MICROSOFT BASIC AND PILOT LANGUAGE
- MOTOR CONTROL PROGRAM WITH SOURCE LISTING
- POWER SUPPLIES INCLUDED OR USE YOUR BATTERIES
- FULLY DOCUMENTED INCLUDING SCHEMATICS
- ALL BOARDS EXCEPT THE DRIVER ARE PREASSEMBLED
- DISK STORAGE (not included) EXPANDABLE TO 3.2 MEG
- ORDER NUMBER 50/03. PLEASE ADD \$14 FOR S&H

MOTION CONTROL SYSTEM \$149.00

Call for a copy of 15 day trial agreement. Tax & freight extra. COD to cont USA ok add \$3 to S&H. Price may change. Store Price may differ. While supplies last. No PO's, terms, or credit cards.

Silicon Valley Surplus
415-261-4506
4401 OAKPORT OAKLAND CA. 94601

OPEN 10am-6pm
CLOSED SUN & MON

CIRCLE 51 ON FREE INFORMATION CARD

Free Information Number	Page	195	Mastersoft	103	
81	A.I.S. Satellite	27	—	McGraw Hill Book Club	28
108	AMC Sales	78	—	McGraw Hill (CED)	75
—	AMCOM	106	61	Microprocessors Unltd.	103
107	All Electronics	121	—	NRI	21
—	Amazing Devices	106, 122	71	New-Tone Electronics	69
106	American Design Components	111	80	OCTE Electronics	27
84	Appliance Service	27	198	Optoelectronics	17
76	Associated Electronics/3M	34	—	Pacific Cable	107
76	Atlantic Cable Distribution	76	182	Paladin	18
77	B&K Precision	5	56	Parts Express	108
188	Banner Technical Books	83	68	Philips ECG	14
85	Blue Star Industries	26	78	Radio Shack	117
109	C & S Sales	72	—	React	83
60	CIE	8	189, 190	Scencore	7, 67
50	Caig Laboratories	76	51	Silicon Valley Surplus	122
183	Chapman Tools	27	187	Simpson	3
54	Chemtronics	22	83	Synergetics	70
199, 200	Chenesko Products	26, 27	196	Tentel	80
—	Command Productions	78	181	WPT Publications	85
186	Communications Specialists	85	Gernsback Publications, Inc. 500-B Bi-County Blvd. Farmingdale, NY 11735 (516) 293-3000 President: Larry Steckler Vice President: Cathy Steckler		
58	Cook's Institute	80	For Advertising ONLY 516-293-3000 Larry Steckler publisher Arline Fishman advertising director Shelli Weinman advertising associate Lisa Strassman credit manager Christina Estrada advertising assistant		
184	Crystek	77	SALES OFFICES		
192	Daetron	18	EAST/SOUTHEAST Stanley Levitan Eastern Sales Manager Radio-Electronics 259-23 57th Avenue Little Neck, NY 11362 718-428-6037, 516-293-3000		
191	Dakota Digital	27	MIDWEST/Texas/Arkansas/Okla. Ralph Bergen Midwest Sales Manager Radio-Electronics 540 Frontage Road—Suite 339 Northfield, IL 60093 312-446-1444		
—	Damark International	15	PACIFIC COAST/ Mountain States Marvin Green Pacific Sales Manager Radio-Electronics 5430 Van Nuys Blvd. Suite 316 Van Nuys, CA 91401 1-818-986-2001		
127	Deco Industries	26, 27			
82	Digi-Key	120			
194	Dynamic Electronics	103			
—	Electronic Technology Today	CV3			
—	Electronics Book Club	62			
—	Firestik II	105			
121	Fluke Manufacturing	23			
—	Fordham Radio	CV4			
—	Grantham College of Engineering	36			
—	Heath	13			
—	ISCET	81			
65	J & W	48			
59	JDR Instruments	CV2			
113, 176	JDR Microdevices	112, 113			
177, 178	JDR Microdevices	114, 115			
179	JDR Microdevices	116			
114	Jameco	118, 119			
115	Jensen Tools	26			
—	Joseph Electronics	33			
185	Kelvin	25			
180	Kikusui	35			
87	MCM Electronics	110			
53	MD Electronics	87			
93	Mark V. Electronics	109			

SUPER CONDUCTIVITY

LEVITATING OBJECT

PIONEERING RESEARCH IN NEW FIELDS AS:

- MAGNETIC WEAPONS
- VEHICLE LAUNCHING
- LEVIATION-MEISSNER EFFECT
- FORCE SHIELDS
- MAGNETIC SUSPENSION
- ENERGY STORAGE
- PARTICLE BEAMS
- HI POWERED COMPUTERS
- ULTRA SENSITIVE DETECTION

SCON1-STARTER KIT — \$2750
SCON2-INTERMEDIATE KIT — \$6950
SCON3-LABORATORY KIT — \$16500


FREE CATALOG WITH ALL ORDERS
 ORDER BY NAME AND INCLUDE \$3.00 FOR P&H. SEND CHECK, MO VISA MC TO:

AMAZING CONCEPTS
 PO BOX 716 AMHERST
 N.H. USA 03031

RADIO-ELECTRONICS

Electronics Paperback Books

GREAT PAPERBACKS AT SPECIAL PRICES

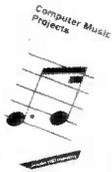

BP173—COMPUTER MUSIC PROJECTS \$6.95. Shows how to use your home computer to produce electronic music. Many circuits. Mostly jargon free.



BP176—TV DXING FOR THE ENTHUSIAST.... \$6.95. Practical, authoritative info to this unusual aspect of electronics. 812 p. 11 in. 144 pp.



PCP103—PRACTICAL MIDI HANDBOOK \$3.95. Explains what MIDI (the Musical Digital Interface) can do and how you can put it to work. Covers Keyboards, drum machines, sequencers, mixers, guitars and computer music.



RFTD—RADIO'S FIRST TWO DECADES \$3.50. This story of radio's early days makes for fascinating reading. Spark-gap transmitters, KDKA's beginnings, and much more.



PCP102—INTRODUCING DIGITAL AUDIO.... \$9.95. CD, DAT, and sampling. What is involved in the digital part of audio signals. Principles and practices of digital audio techniques.



BP195—INTRODUCTION TO SATELLITE TV.... \$8.00. A definitive introduction to the subject written for the professional engineer, electronics enthusiast, or others who want to know more before they buy 8-10 in.



BP239—GETTING THE MOST FROM YOUR MULTIMETER.... \$5.00. Covers basics of analog and digital meters. Methods of component testing (includes transistors, thyristors, resistors, capacitors and other active and passive devices).

BP146—THE PRE-BASIC BOOK \$6.95. A book on the BASIC programming for those who have not yet bought a computer as well as those who have trouble learning how to program.



BP135—SECRETS OF THE COMMODORE 64 \$5.00. Masses of useful info and programming tips not found in any user's manual.



BP143—INTRO TO PROGRAMMING THE ATARI 600/800 XL \$5.00. Perfect complement to the Atari user's manual. Even shows how to use animated graphics.



BP131—MICRO INTERFACING CIRCUITS—BOOK 1 \$5.75. Practical add-ons transform your computer into control or measurement equipment.



BP148—COMPUTER TECHNOLOGY EXPLAINED \$5.00. Explanations for computer terms often encountered. A dictionary for computer lingo.



BP152—INTRO TO Z-80 MACHINE CODE \$5.95. Speed up your programs. They may be harder to write, but it's worth learning how. Some demo programs are included.




BP105—ANTENNA PROJECTS \$5.00. Practical radio antenna designs that deliver good performance and are relatively simple and inexpensive to build.



BP198—AN INTRODUCTION TO ANTENNA THEORY \$6.95. Basic concepts relevant to receiving and transmitting antennas.



BP144—FURTHER PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE.... \$9.00. Companion volume to BP53. Book carries on with new data not found in earlier edition. 450 pages.

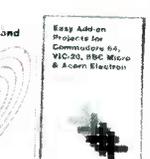

BP170—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS \$5.00. Data and circuits for interfacing the computer to the robot's motors and sensors.

Quality Paperbacks




BP128—20 PROGRAMS FOR THE ZX SPECTRUM & 16K ZX81 \$5.75. All programs run on both machines. Include flow charts and info on how to modify to run on other computers.



BP127—HOW TO DESIGN ELECTRONIC PROJECTS \$5.75. How to use standard circuit elements to make custom electronic projects.



BP110—HOW TO GET YOUR ELECTRONIC PROJECTS WORKING \$5.00. How to find the faults in your projects, repair them and get them working.

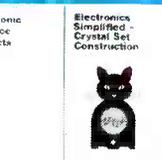

BP121—DESIGN & MAKE YOUR OWN PC BOARDS \$5.75. Everything you need to know before you make printed-circuit boards for your projects.



BP85—INTERNATIONAL TRANSISTOR EQUIVALENTS \$7.50. Locates possible substitutes for a popular user-oriented selection of modern transistors Japanese, European and American types.



BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS, Book 1 \$5.75. Build the blocks and then combine them to form almost any custom project of your choice.



BP118—PRACTICAL ELECTRONIC BUILDING BLOCKS, Book 2 \$5.75. Amplifiers for all kinds to add to the circuits from Book 1 of this series.



BP169—HOW TO GET YOUR COMPUTER PROGRAMS RUNNING \$5.95. Have you ever written your own programs only to find that they do not work? This book shows you how to find errors.

Affordable Prices



BP128—20 PROGRAMS FOR THE ZX SPECTRUM & 16K ZX81 \$5.75. All programs run on both machines. Include flow charts and info on how to modify to run on other computers.



BP106—MODERN OP-AMP PROJECTS \$5.00. Includes a Slide Timer, AF Signal Gen, Mike Pre-amp, Scratch Filter, and much more.



BP59—SECOND BOOK FOR CMOS IC PROJECTS \$5.00. Multivibrators, amplifiers, triggers & gates; special devices including reaction timer, simple electronic organ, and more.




BP182—MIDI PROJECTS \$6.95. Details of how to interface many popular home computers with MIDI music systems.



BP65—SINGLE IC PROJECTS \$4.95. All projects in this book are based on one IC and are simple to construct. Great way to get started with IC's.




BP49—POPULAR ELECTRONIC PROJECTS \$5.50. A collection of a wide range of electronic projects and circuits for the experimenter.

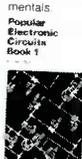

BP97—IC PROJECTS FOR BEGINNERS \$5.00. Written especially for the less experienced experimenter. Complete parts layouts and wiring diagrams.




BP161—INTO THE QL ARCHIVE \$5.95. Presents the powerful database for the Sinclair QL. Step-by-step approach includes practical examples.

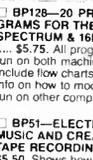

BP51—ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING \$5.50. Shows how you can make electronic music at home with simple and inexpensive equip.



BP185—ELECTRONIC SYNTHESISER CONSTRUCTION \$5.95. Shows how to build a monophonic synthesizer, section by section. Replaces BP81.

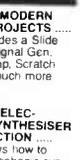

BP80—POPULAR ELECTRONIC CIRCUITS, Book 2 \$5.00. More circuits for hobbyists. Audio, radio, test music, household and more.



BP98—POPULAR ELECTRONIC CIRCUITS, Book 1 \$5.75. More useful circuits. None of these projects duplicate those in Book 1 of this series.

CHECK OFF THE BOOKS YOU WANT

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 240, Massapequa Park, NY 11762-0240

SHIPPING CHARGES IN USA AND CANADA

SORRY, No orders accepted outside of USA and Canada

Number of books ordered

Name _____
Address _____
City _____ State _____ Zip _____

\$0.01 to \$5.00 \$1.25
\$5.01 to 10.00 \$2.00
\$10.01 to \$20.00 \$3.00
\$20.01 to \$30.00 \$4.00
\$30.01 to \$40.00 \$5.00
\$40.01 to \$50.00 \$6.00
\$50.01 and above \$7.50

Total price of merchandise \$ _____
Sales Tax (New York State Residents only) \$ _____
Shipping (see chart) \$ _____

All payments must be in U.S. funds
Total Enclosed \$ _____

R9-88

Fordham measures up

Quality • Price • Delivery

Mini-Meters with Maxi-Specs



SCOPE 3½ Digit LCD Meter

- 0.5% Accuracy • DC Voltage • AC Voltage • DC Current • Resistance • Diode Test • Battery Life 300 Hrs. • Overload Protection: DC 500V, AC 350V, ohms 250V DC/AC.

Model DVM-630
Our Price **\$2995**

Zippered carrying case CC-30 \$4.50

NEW! SCOPE 3½ Digit, LCD 8 Function with Transistor Tester

- 0.5% Accuracy • Audible continuity and diode test • 10 Amp measurement • Resistance • DC/AC Voltage.

Model DVM-632
Reg. \$60.00
Our Price **\$4495**

Zippered carrying case CC-30 \$4.50

SCOPE 3½ Digit LCD with Autoranging

- 0.5% Accuracy • Auto/Manual range selection • DC Voltage • AC Voltage • AC Current • DC Current • Resistance.

Model DVM-631
Our Price **\$4995**

Special

Deluxe carrying case CA-92 \$9.95

SCOPE Hand-Held Digital Multimeters

- Overload protection • Auto-decimal LCD readout • Polarity indication • 300 hr. 9V battery life • Low battery indicator.

- 8 Function, 37 ranges including Transistor and Capacitance measurements


Model DVM-636
\$6750
Our Price



CA-92 Deluxe Padded Case for DVM meters. \$9.95
TL-216 Transistor and Capacitance Test Leads \$9.90

- 11 Function, 38 ranges including Logic Level Detector, Audible and Visual Continuity, Capacitance and Conductance measurements

Model DVM-638
\$8750
Our Price

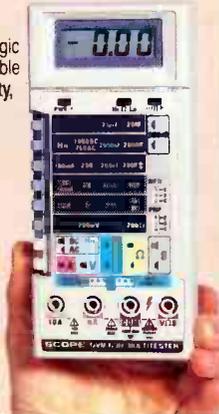

NEW!
SCOPE Frequency Counters
• 8-digit LED • Compact • lightweight • High performance • Automatic range and Hold function • High stability in reference oscillator.

Model FC-7011
100 MHz Our Price **\$14995**

Model FC-7051
550 MHz Our Price **\$19995**



FORDHAM Frequency Counter

- 10 Hz - 150 MHz Range • 7-digit LED display • VHF/HF selection • Gate time 1 sec., 5 sec. • ±1 count accuracy.

Model FC-150
Our Price **\$13990**



NEW FORDHAM Function Generator

- 0.5 Hz - 500 KHz in 6 ranges • Sine, square & triangle wave forms • VCA and VCF inputs • Accuracy ±5% of full scale.

Model FG-202
Our Price **\$14990**



FORDHAM Signal Tracer/Injector

- Easy to operate • VU meter • Two LED mode indicators • 1 KHz test tone • 8 ohm speaker • Test leads.

Model SE-610
Our Price **\$11990**



FORDHAM LCR Bridge Meter

- Fully transistorized • 1 KHz signal generator • Measures resistance • Inductance • High mechanical and electrical stability • Battery operated.

Model LC-340
Our Price **\$14995**



SCOPE Digital Capacitance Meter

- Digital LCD display • LSI-circuit • High accuracy: 100 ppm 0.5% • Broad test range • Fast sampling time • Capacitor discharge protection • Compact, lightweight design • One-hand operation.

Model DCM-602
Our Price **\$5995**

Telephone Orders Now! EVERYDAY INCLUDING SATURDAY
Mon. - Fri. 8 a.m. - 6:30 p.m. EST. Sat. & Sun. 9 a.m. - 3 p.m. EST

ASK FOR FREE CATALOG. Money orders, checks accepted. C.O.D.'s require 25% deposit



Fordham

Toll Free **800-645-9518**

260 Motor Parkway, Hauppauge, NY 11788

In NY State 800-832-1446

Service & Shipping Charge Schedule Continental U.S.A.

FOR ORDERS	ADD
\$25-50	\$4.50
\$51-100	\$5.50
\$101-200	\$7.00
\$201-300	\$8.00
\$301-400	\$9.00
\$401-500	\$10.00
\$501-750	\$12.50
\$751-1000	\$15.00
\$1001-1250	\$17.50
\$1251-1500	\$20.00
\$1501-2000	\$25.00
\$2001 and up	\$30.00