

# Radio and Model Engineering

10 cents a Copy - 570 West 184th Street, New York City - \$1.00 Per Year

Vol. I

JULY, 1921

No. 3

## Editorial

N the June issue of R and M you may have noticed the statement that your combination square, dividers, scribe, and center punch are your best friends in laying out your panels. That this is true I have seen demonstrated many times by Experimenters who say they can't lay out a panel neatly and accurately, but when they locate their holes by cross lines made with the square and scribe or the dividers, and carefully start the holes by center punch marks, they do as good work as the best. The use of these small tools is a habit, and one that every Experimenter should acquire.

Of great assistance is the use of L. P. F. panels because they are ground on the edges to be perfectly square and accurate as to dimensions. Therefore a line at right angles to one side is at right angles to the opposite side. This material is also agreeable to drill and tap, for the holes are clean, with no broken under-sides. It can be filed nicely, too.

The added time required to make things right and accurate is both time and money saved, for it guards against spoiled materials and the necessity of "making it over." Most important of all, however, is the feeling of pride and confidence in a well made instrument, against the untidy work of a man who has to hurry to try it out, for he has little pleasure for his pains.

Look over your own apparatus and see which kind of a man you are. On the next instrument make a real job of it.

M. B. SLEEPER, *Editor.*

# A Real Receiving Equipment

*This set probably introduces a new era in experimental instruments; it is a regeneration tuner of astonishing sensitivity for 150 to 2,600 meters.*

By W. H. BULLOCK

The  
Tuning  
Circuit.

**R**EGENERATIVE receivers, as many an experimenter knows, are not only difficult to handle but are quite expensive. Some of the variometer type sets have as many as nine control knobs, the minimum being five, exclusive of the audion circuits.

The time required to tune such sets multiplies rapidly with the number of controls, because of the extremely sharp tuning and the frequency variations due to the hands, with the result that short calls are often lost before they can be tuned in. Moreover, the wavelength range at best is 150 to 300 meters unless an air or mica condenser is added in the secondary.

When properly constructed, this set brings in signals louder than the very best variometer set, regenerates splendidly on the first half of the feed-back coil scale, and oscillates freely on the second half. In addition, it is excellent for receiving long waves to which a variometer outfit will not respond.

Both in operating qualities and cost it is a logical successor to the older receivers, which have so long held the interest of experimenters.

New  
Type of  
Construction.

**A**NOTHER new feature is introduced in this article, namely, the panel supporting methods. At the G. A. Company we have actually built dozens of boxes and tried out many and varied schemes for supporting instrument panels, for the purpose of finding an inexpensive and at the same time good-looking method. The angle brass supports, shown in Fig. 1, is the outcome. These are easily made, furnish excellent bracing for the panel, permit instruments to be attached on top or at the sides, and carry the rear connection panel conveniently. All around, it is the best system for the man who does not want to put four or five dollars into a cabinet for each instrument.

Panels  
and  
Supports.

**F**IG. 2 gives the layout of the front and rear panels and of the angle brass supports. These can be cut and drilled from regular stock. They are also sold completely made up, in which case the brass is nicked. Since all dimensions are one-half size, they can be readily scaled off from the drawings. If a sharply pointed scriber is used, light lines can be made on the front of the panel and later sanded off, when the holes have been drilled, with No. 0 sandpaper and oil. Do not rub dry sandpaper on L.P.F., for it quickly fills up. Plenty of oil, however, keeps the particles floating, and they do not coat over the sandpaper.

First  
Ass mblly  
Job.

**A**S soon as the front panel has been drilled, the three coil mounting pillars, the switch, and switch points should be put on. An extra switch point is allowed at each end of the row. The condenser may be mounted also, but none of the other parts, for they will be in the way.

Winding  
the  
Coil.

**B**ANKED windings, hold a terror for many experimenters who have had experience with them, in almost every case because they did not go about it in the right way. A simple winding rig is needed, consisting of two round pieces to fit in the tubing, fastened to a 1/4-in. shaft fitted with a handle and supported on two sturdy uprights. It is difficult to tell an Experimenter how to wind the coil; he must learn by practice. For a three-bank coil, the process, briefly, is this:

Wind three complete turns around the tube, keeping the wire just as tight as possible. At the end of the third turn, bring the wire up between the second and third turns and wind once around. Then another turn between the first and second. At the end of the fifth turn,

jump up between the fourth and fifth and wind one turn. The result should be a pyramid of three layers of three turns, then two, then one.

When the sixth turn has been completed, bring the wire down onto the

take off the taps. This method keeps the winding tight and the taps out of the way.

A G-A-Lite tube,  $3\frac{1}{2}$  ins. in diameter and  $4\frac{1}{2}$  ins. long, carries the winding of No. 24 S.S.C. wire in three banks. Taps

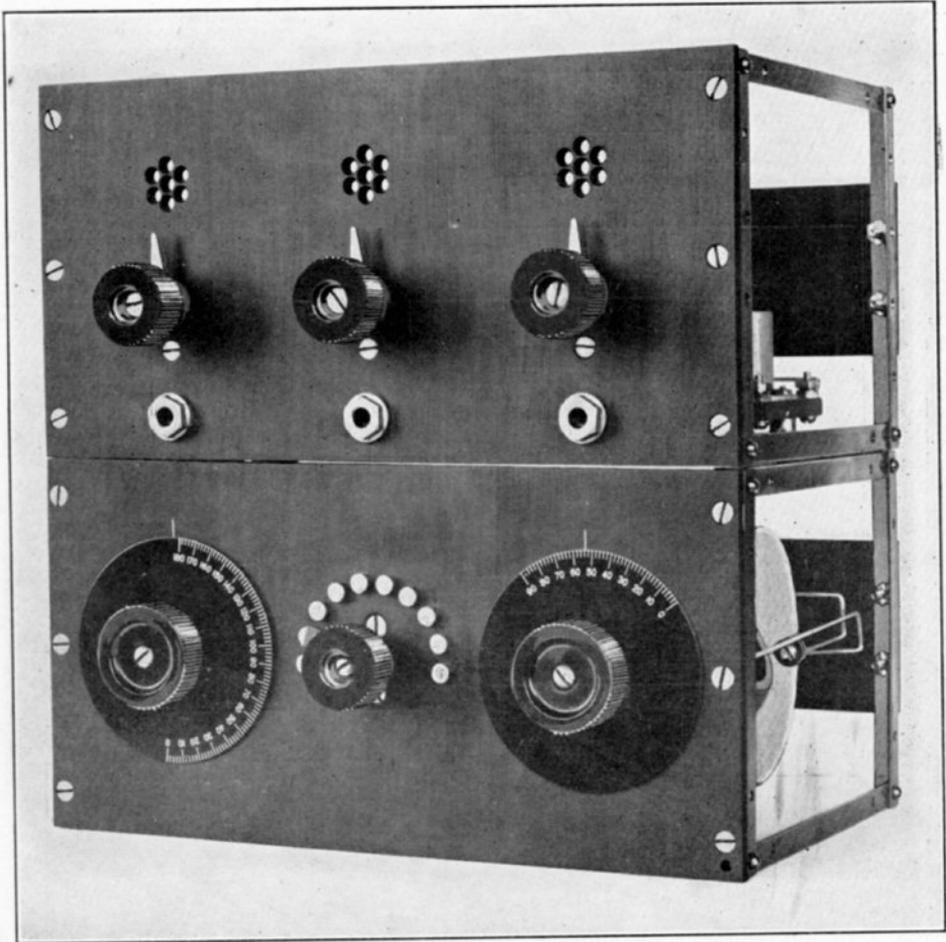


Fig. 1. The 150 to 2,600 meter regenerative set with a detector and two-step amplifier. The latter will be described in the August issue.

tube and put on the seventh turn, the eighth turn on the seventh, and the ninth turn on the eighth. Jump to the tube again, and repeat the process. To take off taps, when the tapping point is reached, bend the wire sharply to one side and wind a single turn around the part of the coil already wound. Bring the end of that turn back to where it was started and continue with the winding. After the coil has been completed and varnished, cut the tapping turns and

for this 150-to 2600-meter coil are taken off, as shown in Fig. 2. Remember that a  $\frac{3}{8}$ -in. space is allowed after the fifth tap. The inductances and wavelength ranges with a 0.0008 mfd. series condenser and a 0.0003 mfd. antenna are:

- Tap 1—0.09 millihenry  
150 to 253 meters.
- Tap 2—0.16 millihenry  
200 to 337 meters.
- Tap 3—0.30 millihenry  
270 to 462 meters.

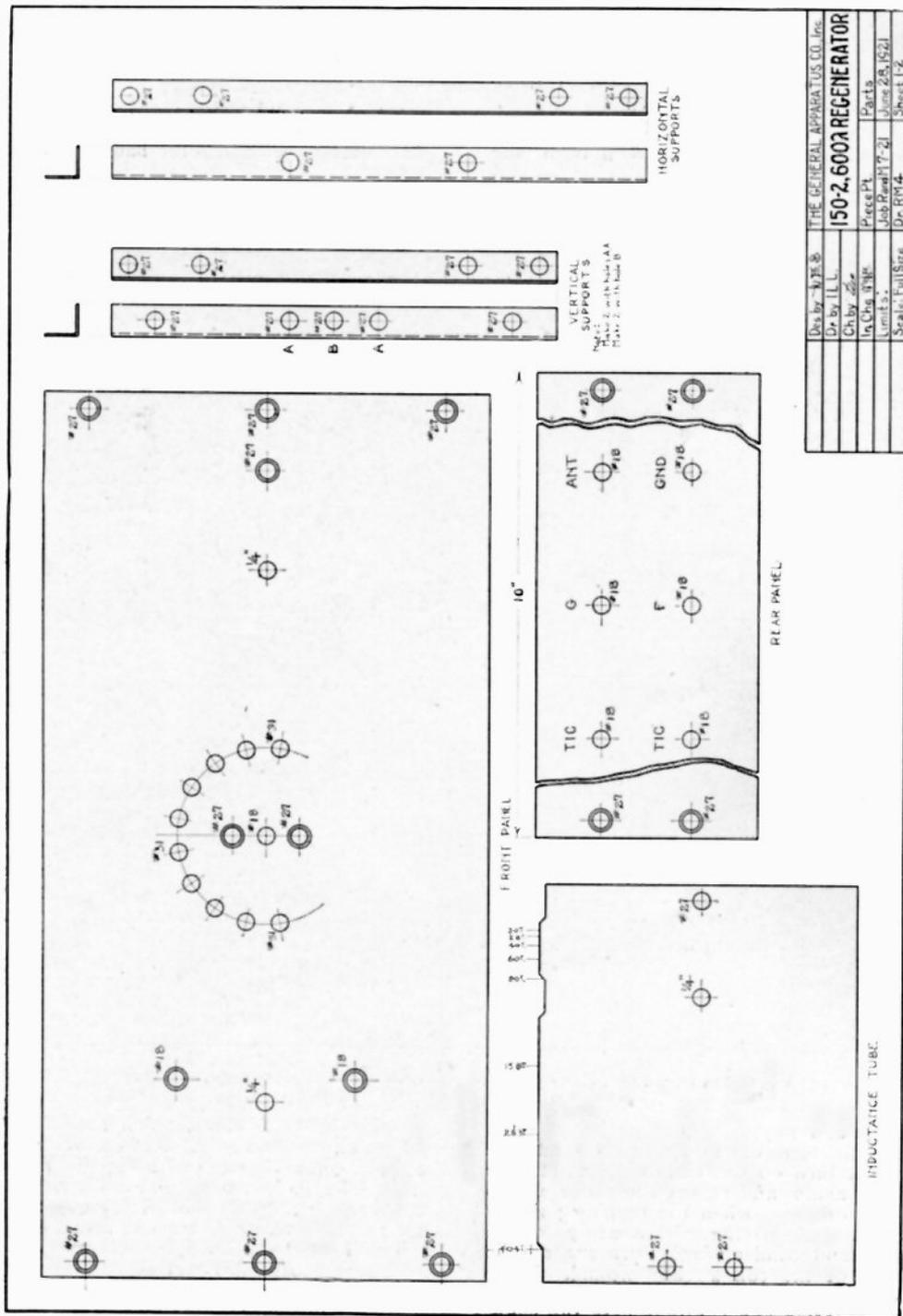


Fig. 2 Mechanical details of the receiver.

Designed by	W. J. B.	THE GENERAL APPARATUS CO. INC.
Drawn by	W. L. L.	<b>150-2, 6000 REGENERATOR</b>
Checked by	W. J. B.	Price \$1
In Charge	W. J. B.	Job No. 117-21
Units		June 28, 1921
Scale	Full Size	Dr. 117-21
		Sheet 1-2

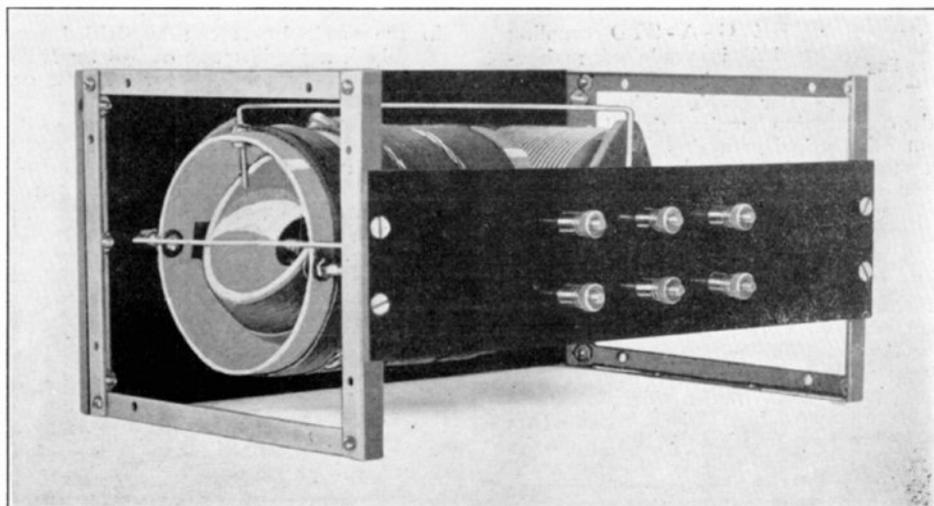


Fig. 3. End view, showing the tickler details and the connection panel.

Tap 4—0.60 millihenry  
383 to 653 meters.

Tap 5—1.20 millihenries  
546 to 923 meters.

Tap 6—2.50 millihenries  
789 to 1,333 meters.

Tap 7—5.00 millihenries  
1,066 to 1,885 meters.

Tap 8—10.00 millihenries  
1,577 to 2,665 meters.

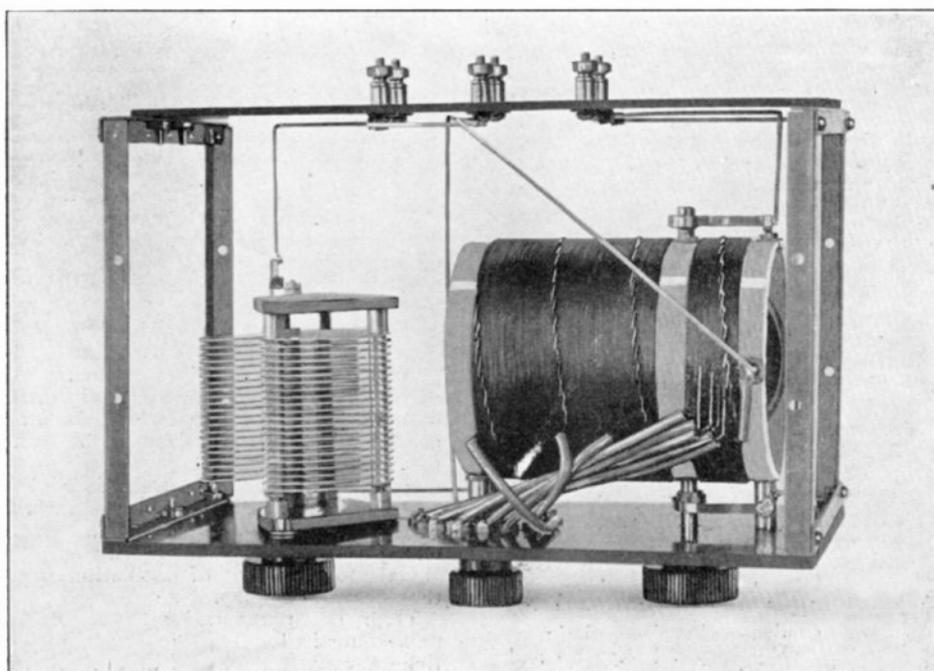


Fig. 4. Looking down on the condenser and inductance.



# Inductance, Capacity and Wavelength

By M. B. SLEEPER

*Showing that wavelength is not a cause but an effect—a result and not a factor.*

**T**HE beginner usually comes to realize in a short time that wavelength has nothing to do with transmitting or receiving range, but of those who have been in radio work for years not one in a hundred really understands the meaning and application of the term.

Did you ever hear of the area of length, or the area of a width? You know that there can be area only as a result of width and length. In radio work, inductance can be compared with the length of a piece of paper, capacity with the width, and wavelength, the area. A circuit made up of inductance alone has no wavelength, nor has a circuit of capacity only. When, however, an inductance and a capacity are connected together, they give a resulting wavelength.

For this reason, Experimenters who wish to speak intelligently should no more talk about the wavelength of a coil than about the area of a width. There is, of course, a natural period for every coil, just as there is area in a ten-inch pencil mark, but this value is of no use except in very special cases.

Here is another important point. A given coil which, added to one circuit, increases the wavelength from 1,000 to 1,500 meters will not increase the wavelength of a 3,000-meter circuit to 3,500 meters. Carrying out the comparison given above: Suppose a panel measuring 5 by 10 inches, giving an area of 50 square ins., is increased in length to 15 ins. The area then becomes 75 sq.

ins., increasing the area by 25 sq. ins. Another panel 10 by 10 ins., 100 sq. ins., is increased by 5 ins. in length, giving an area of 150 sq. ins. or an increase of 50 sq. ins. However, 5 ins. was added to the length in both cases.

In a radio circuit a coil of 1,000,000 cms. and a 0.0005 mfd. condenser are connected. The wavelength resulting is 1,333 meters. Adding a coil of 500,000 cms. brings the wavelength up to 1621 meters, an increase of 288 meters. On the other hand, a circuit of 2,500,000 cms. and 0.0002 mfd. also gives a wavelength of 1,333 meters, but when the inductance is increased to 3,000,000 ins. the wavelength only goes up to 1,460 meters, or an increase of 127 meters.

Consequently the man who thinks and designs his apparatus intelligently must learn to figure the actual inductance of his coils and, knowing the capacity ranges of his condensers and the capacity of his antenna, determine the wavelengths to which these values will respond. The former can be worked out by simple arithmetic with the aid of Inductance Tables<sup>1</sup>, and the latter read directly from tables given in Design Data for Radio Transmitters and Receivers.<sup>2</sup>

You owe it to yourself and to those who are learning from you to clear up this very fundamental subject, for wavelength is to radio work what vibration is to the study of sound.

(1) Inductance Tables, Published by The General Apparatus Co., Inc. Price \$25.

(2) Design Data, Sold by The General Apparatus Co., Inc. Price \$75.

## STANDARDIZED PARTS FOR THE 150 to 2,600 METER REGENERATOR

1—L.P.F. panel 5x10x $\frac{3}{8}$ in. (12 oz.)	\$1.31
1—L.P.F. rear panel 2 $\frac{1}{2}$ x10x $\frac{1}{4}$ in. (4 oz.)	.45
4—Lengths $\frac{3}{8}$ in. angle brass. (3 oz.)	.80
1—G.A.-STD. variable condenser, 0.0008 mfd. (1 lb.)	4.30
1—180° dial and knob, $\frac{1}{4}$ in. hole. (2 oz.)	.80
1—90° dial and knob, $\frac{1}{4}$ in. hole. (2 oz.)	.80
1—Complete switch, 1 in. radius (2 oz.)	.40
10—Switch points, $\frac{1}{4}$ in. diam., 4-36 shank (1 oz.)	.40
1—G-A-Lite tube, 3 $\frac{1}{2}$ in. diam., $\frac{3}{8}$ in. wall (5 oz.)	.32
1— $\frac{1}{2}$ lb. spool No. 24 S.S.C. wire. (8 oz.)	1.25
3—Coil supporting pillars, 6-32 thread. (2 oz.)	.24
1—Length $\frac{1}{4}$ in. brass rod (7 oz.)	.15
2—Ft. Empire tubing (2 oz.)	.40
1—Pkg. 6-32 washers (1 oz.)	.04
2—Pkgs. $\frac{1}{2}$ in. 6-32 R.H. nicked screws (1 oz.)	.12
2—Pkgs. $\frac{1}{2}$ in. 6-32 F.H. nicked screws (1 oz.)	.12
2—Pkgs. 6-32 nicked nuts (1 oz.)	.16
1—Pkg. $\frac{1}{4}$ -in. 4-36 R.H. nicked screws (1 oz.)	.11
1—Pkg. 4-36 nicked nuts (1 oz.)	.08

6—G.A.-STD. nicked binding posts (3 oz.)	.60
2—Lengths square tinned copper connection wire (2 oz.)	.12
1—G.A.-STD. mahogany variometer ball, shaft hole drilled (3 oz.)	.90

## COMPLETE SET OF PARTS TO BUILD THE 150-TO-2,600 METER REGENERATOR (7 lbs.) \$13.49

NOTE: This set, giving extremely loud signals over the entire wavelength range, costs less than two variometers alone.

### AUXILIARY PARTS:

Front panel fully engraved, extra	\$2.70
Rear panel fully engraved, extra	1.30
Complete supporting frames, nicked, pair	1.00
Inductance coil, wound and tapped	4.00
Coil and Tickler, mounted on 5x10x $\frac{3}{8}$ in. L.P.F. panel, with all holes drilled in panel, ready to complete	9.90
Front panel with condenser, coil, and tickler mounted, fitted with dials, switch, and switch points, practically finished except for supports, connection panel and wiring	17.25
<b>SPECIAL SALE UNTIL AUG. 15th ONLY</b>	
New Federal amplifying transformers, fully mounted	\$6.00
Paragon Rheostats complete	1.30

# FIXED CONDENSERS



GA-STD-A2 GA-STD-A3 GA-STD-A4


THE Grid Condenser, 0.0005 mfd., is the correct size for the new receiving tubes. This also applies to the Grid-Leak Condenser, which combines a capacity of 0.0005 mfd. with a leak of 1 megohm. The Phone Condenser, 0.001 mfd., is to shunt around the telephones in a crystal detector circuit, or to put across the phones—and transformer if an amplifier is used, in a regenerative set.

The G. A. mark on a condenser means that the capacity is accurate within 5% and the resistance within 10%.


PRICE: GA-STD—A2 Grid Condenser, postage 5c.....\$.35  
 GA-STD—A3 Phone Condenser, postage 5c......35  
 GA-STD—A4 Grid-Leak Condenser, postage 5c......50

CLASS F

# DETECTOR AMPLIFIER

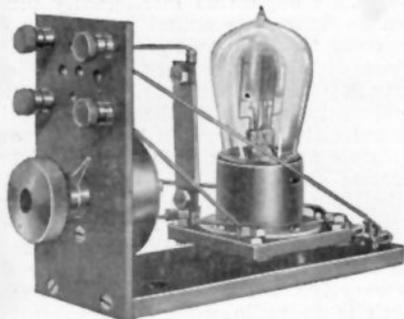

GA-STD-A5

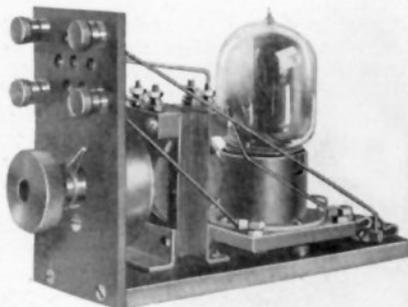

GA-STD-A6

NO matter what you pay, you can't buy better stuff than is in the Laboratory Type Detector and Amplifier. This combination of the finest parts and the simplest circuits can't be surpassed at any price in the final test for loud signals. Wooden base 2 1/2 x 6 ins. L. P. F. panel 2 1/2 x 5 ins. Input and output posts on panel, battery connections at rear of base. Wired with

square tinned copper, all joints soldered. The workmanship is perfect. A detector and three amplifiers set side by side will not howl. Diagrams on bottom of the base. The handiest instruments you ever used for laboratory work.

PRICE: GA-STD—A5 Detector, without tube, 1 lb. ....\$5.95  
 GA-STD—A6 Amplifier, without tube, 2 lbs. .... 13.95

CLASS 20-C

# GA-STD

G.A. STANDARDIZED EXPERIMENTAL SUPPLIES

THE GENERAL APPARATUS COMPANY, Inc.  
 570 West 184th Street, New York City

John Barber Art Printing, 153 West 31st Street, New York City