

JUNE, 1950

Radio
**SERVICE
DEALER**



The Professional Radio-TVman's Magazine


IN THIS ISSUE:

Short Cuts In Audio Servicing
Conversion of 630 TS Type Chassis to
3 Ft. x 4 Ft. Projection
Combination Inductance Bridge
TV Front Ends — Part I
U. H. F. Tuning Elements

AM-FM-TV-SOUND

Paid Circulation Of This Issue: Over: 23,500
Total Distribution Of This Issue: Over: 25,000

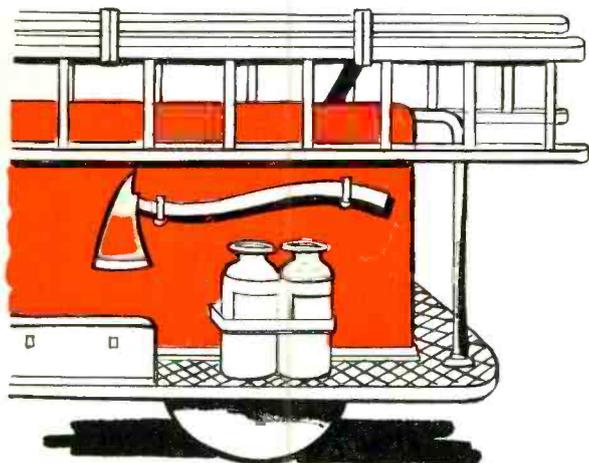Because
**They're Dependable
Starters . . .**



MALLORY Vibrators Give Better Service !

An exclusive combination of Mallory-engineered and Mallory-made contacts retard oxide formations...on the shelf. A unique "self-cleaning" action prevents oxidation in service. Therefore, Mallory Vibrators are dependable starters and dependable performers.

And the patented tuned mechanism of the Mallory Vibrator provides low contact wear, low resistance and reduced arcing and pitting.

That's why more Mallory Vibrators are used in original equipment than all other makes combined. When you use Mallory Vibrators for replacement, you can be sure of dependable starting, long life and high output efficiency. See your Mallory distributor now!

More Mallory Vibrators Are Used In Original Equipment Than All Other Makes Combined



P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U. S. Pat. Off.

APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

The Greatest TV Servicing Manual Ever Published!

more data than ever before! ...at the same low price!

NEW


RIDER TV MANUAL VOL. 4

Complete Coverage From October, 1949
through February, 1950

- Authentic, Accurate, **FACTORY-AUTHORIZED** TV Servicing Information Direct From 73 Manufacturers
- New, Larger Page Size, 12" x 15", Equivalent of 2296 Pages (8½ x 11)
- All Pages Filed in Proper Place, For Quick, Easy, Efficient Reference.
- 494 Models. 235 Chassis. The Greatest Collection Ever Assembled In One Handy Volume
- Test Patterns, Wave Forms, Schematics, Voltages, Adjustment Of Traps, Alignment Tables, Etc.
- Giant Pages Have Only One Fold For Extra Convenience And Greater Durability
- Nobody Else But RIDER Brings You All This Information At Such An Amazingly Low Price
- Get Yours Right Now Without Delay. Volume 3 Sold Out in A Few Weeks. Volume 4 should Do the Same

ONLY \$ **21⁰⁰**

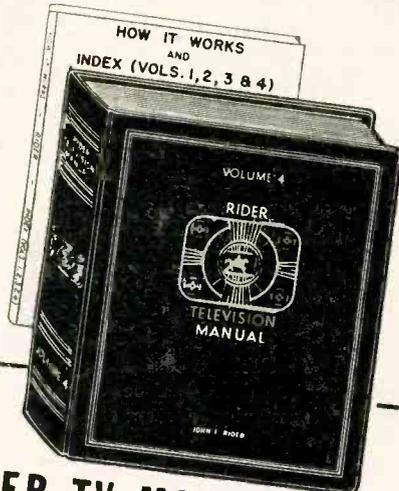Including Cumulative Index Volumes 1, 2, 3 and 4... PLUS the One and Only RIDER "How It Works" Book.



RIDER TV MANUAL VOL. 3
74 Television manufacturers. 441 models. 243 chassis. Larger page size, 12" x 15". All pages filed in their proper place.
Equivalent of 2032 Pages (8½" x 11") Plus Cumulative Index Volumes 1, 2 and 3, plus the famous RIDER "HOW IT WORKS" Book..... **\$21.00**

RIDER TV MANUAL VOL. 2
Complete factory-authorized coverage up to January 1949. 67 manufacturers. June delivery—in new, larger page size, 12" x 15". Contains all of the data formerly presented in the 8½" x 11" page size manual. PLUS the RIDER "HOW IT WORKS" Book, and Cumulative Index Volumes 1 and 2 **\$21.00**

RIDER TV MANUAL VOL. 1
Complete factory-authorized coverage up to early 1948. 34 manufacturers.
Equivalent of 2000 pages. (8½" x 11") PLUS Index and the RIDER "HOW IT WORKS" Book..... **\$18.00**

RIDER MANUALS

Television Manual Volume 4 (Plus "How It Works" Book and Index).....	\$21.00	Volume XX.....	\$18.00
Television Manual Volume 3 (Plus "How It Works" Book and Index).....	\$21.00	Volume XIX.....	\$19.80
Television Manual Volume 2 June delivery—in new, larger page size, 12" x 15". (Plus "How It Works" Book and Index).....	\$21.00	Volume XVIII.....	\$19.80
Television Manual Volume 1 (Plus "How It Works" Book and Index).....	\$18.00	Volume XVII.....	\$16.50
PA Equipment Manual, Vol. 1.....	\$18.00	Volume XVI.....	\$ 8.40
		Volume XV.....	\$19.80
		Volume XIV to VII (each vol.)	\$16.50
		Volume VI.....	\$12.50
		Abridged Manuals I to V (one volume).....	\$19.80
		Master Index, Covering Manuals, Vols. I to XV.....	\$ 1.50

NOTE: Are you receiving your copy of "Successful Servicing"? It's Rider's own publication of interest to every Serviceman. Write for it...it's FREE!

NOTE: The Mallory TV Service Encyclopedia, 1st TV Edition, makes reference to only one source of TV receiver schematics—Rider TV Manuals.

NOTE: The Mallory Radio Service Encyclopedia, 6th Edition, makes reference to only one source of radio receiver schematics—Rider Manuals.

NOTE: The C-D Capacitor Manual for Radio Servicing, 1948 Edition No. 4, makes reference to only one source of receiver schematics—Rider Manuals.

JOHN F. RIDER PUBLISHER, Inc., 480 Canal Street, New York 13, N. Y. • Export Agent: Rocke International Corp., 13 East 40th St., N. Y. C., Cable, ARLAB.

Another Great RIDER Servicing "Must!"

RIDER MANUAL Vol. XX



Do a better, more satisfactory job... insure repeat business... make a larger net profit. Get RIDER MANUAL Volume XX. Complete coverage up to November, 1949—AM-FM, Radio, Auto Receivers, Record Changers. Products of 74 manufacturers. All pages and double spreads filed in proper positions.

1776 Pages... Plus Separate "How It Works" Book, and Cumulative Index, **\$18⁰⁰**
Volumes XVI to XX. ONLY.....

RIDER MANUALS mean **SUCCESSFUL SERVICING**

EDITORIAL

by S. R. COWAN

Ten years ago we editorially opined that the Radio Industry should emulate Baseball by appointing a "czar" who could and would establish and then enforce the maintenance of certain standards and policies that would benefit all branches of this complex industry. Said "czar", we proposed, would protect the "high" and "low" groups and the parts maker particularly, for because he supplies both set maker and the replacement trade his position is often that of the guy squeezed between two extremes.

Our original editorial caused a furore which died of inertia because then, as now, only the "big boys" had any say in industry developments. But now such chaos is rampant in the radio-television field that the "big-boys", meaning RMA members, are on the verge of assigning a man of world-wide reputation to become, in effect, the industry "czar", although actually he would have a more proper title, such as Industry Co-ordinator.

We reiterate our opinion of ten years ago: This industry needs a "czar" or "co-ordinator", and it needs one immediately. The industry needs Standards and a force to police them once they are established. For example, we need standards of pricing and discount methods. Why are some set manufacturers permitted to offer under their private labels volume controls and other components at lower list prices than the list prices established by the original parts manufacturers for the identical items packaged at their own factories? Why are some glorified servicemen recognized as jobbers, and given jobber discounts, by some parts makers who can't get legitimate jobbers in that section to stock their lines? Why do some "legitimate" jobbers sell items at trade discounts over-the-counter to any Tom, Dick and Harry who walks into their stores when business ethics require that wholesalers should only give established trade discounts to servicemen and dealers who have legitimately established themselves as such? Why do some Jobbers (sic) operate their own retail radio service departments in direct and unethical competition with their own service organization customers?

The industry needs a man who can also co-ordinate and control unethical trade practices on the part of manufacturers, too. Many of them, for example, are advertising ridiculous, false and improper claims for TV sets with built-in antennas. The ex-general of the U. S. Armed Forces currently being considered for the job under discussion, Industry Co-ordinator, deserves the support and best wishes of us all, but the servicing fraternity in particular had better get itself organized quickly so that its properly elected delegates can be appointed at the right time to present our case and win justified recognition from the man who may become radio-TV's "Mr. Big".



Sanford R. Cowan
EDITOR & PUBLISHER

Samuel L. Marshall
MANAGING EDITOR

COWAN PUBLISHING Corp.
342 MADISON AVENUE
NEW YORK 17, N. Y.

Vol. 11 No. 6

June, 1950

Editorial	2
Field Findings	6
Trade Flashes	10
Short Cuts in Audio Servicing, by Matthew Mandl	13
Methods of trouble-shooting audio circuits	
Conversion of 630 TS Chassis to 3 ft. x 4 ft. Projection, by V. R. Parker	16
Describing a new kit which enables the service dealer to go after additional business of wide potential.	
Combination Inductance Bridge, by Rufus P. Turner	18
Constructional details of an instrument many servicemen would like to own.	
Front Ends, Part I, by Samuel L. Marshall	19
Discussion of Front End requirements and input circuits.	
U.H.F. Tuning Elements, by Allan Lytel	21
Introduction to various types of tuning circuits used in the ultra high frequencies.	
Shop Notes	22
Crosley (Models 10-412, 10-418, 10-404MU, 10-MIU)—increase vertical size. Philco (Models 49-1040 code 123, 49-1240 code 124, 49-1278 code 123, 49-1280 code 121)—changes in rating of B+ protective fuse. Checking flyback transformer. Dial cord stringing hook. Discarded pen light carries speaker shims. Difficult bolt and nut replacement.	
Circuit Court	23
Kappler Model 102T	
New Products	24

SANFORD L. CAHN
National Advertising Sales Manager

HARRY N. REIZES
Advertising Manager

NATHAN BOYCE, Circulation Manager

BRANCH: J. C. GALLOWAY 816 W. 5th St., Los Angeles 13, Calif., Mutual 8335

RADIO SERVICE DEALER is published monthly by Cowan Publishing Corp., 342 Madison Ave., N. Y. 17, N. Y. Subscription price: \$2 per year in the United States, U.S. Possessions & Canada: elsewhere \$3. Single copies: 25c. Entered as second class matter Dec. 13, 1948 at the Post Office at New York, N. Y. under the Act of Mar. 3, 1879. Copyright 1950 by Cowan Pub. Corp.

It Sells Itself

Because It Has Everything!

THE RADIART TELE-ROTOR



MAKES ORDINARY TELEVISION GOOD-
AND . . . GOOD TELEVISION BETTER

- ✓ **MOST POWERFUL** . . . of all TV rotators! It's heavy duty motor turns a 150-lb. load with ease!
- ✓ **MOST STURDY** . . . Rugged, thick wall aluminum alloy castings, steel gears PLUS a full 12 ball bearing movement!
- ✓ **QUICK, TROUBLE-FREE INSTALLATIONS** . . . TELE-ROTOR goes up quickly. Stays up trouble-free without call backs!
- ✓ **DEPENDABLE PERFORMANCE** . . . when you install a TELE-ROTOR, you know it will perform under any and all conditions!



Available in the following models:

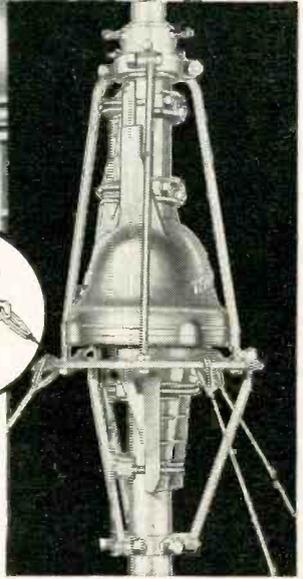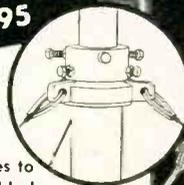- **TR-1** . . . rotator and Control Unit with
erd of rotation light (uses 4 wire Cable) **\$37.45**
- **TR-2** . . . Compass Control Rotator with
illuminated "Perfect Pattern" dial (uses
3 wire Cable) **\$44.95**



**WATCH RADIART
FOR TWO SENSATIONAL
NEW TV ANTENNAS**

Here are two NEW accessories to the TELE-ROTOR to give it added versatility for extraordinary installations. The "Super-Structure" will "support a ton" . . . and the "Floating Guy Collar" is adequate for most guyed installations.

You Can't Beat a RADIART ANTENNA on a TELE-ROTOR . . . It's TOPS!



THE **RADIART** CORPORATION
CLEVELAND 2, OHIO




- ROTATORS
- VIBRATORS
- TV ANTENNAS
- AUTO AERIALS
- POWER SUPPLIES


SERVICE TECHNICIANS ACCLAIM SENSATIONAL

IRC control development

Concentrikit

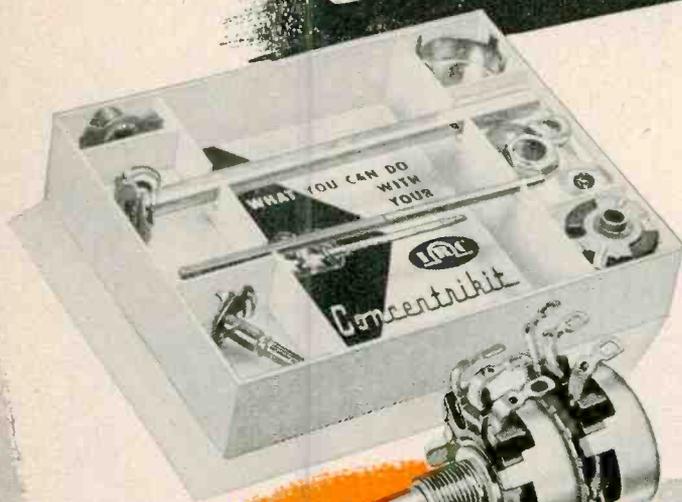

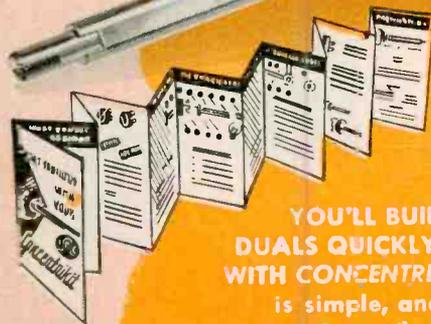Amazing new IRC Concentrikit is the practical answer to your concentric dual replacement problems. With this set of specially designed parts you can assemble over 90% of all concentric dual types . . . no more long searches and waits for exact duplicates. You save time, worry *and* inventory investment.



**YOU'LL BUILD CONCENTRIC
DUALS QUICKLY AND EASILY
WITH CONCENTRIKIT.** Assembly
is simple, and can be completed
in a few minutes. Step-by-step
Instructions are furnished with every kit.

REPLACEMENT MANUAL AVAILABLE
Full replacement data on concentrics
for all applications, from the earliest
home and auto radios to television,
are contained in a new IRC CON-
CENTRIC DUAL REPLACEMENT
MANUAL. Be sure to get a copy
from your IRC Distributor.





STOCK ASSORTMENT

Television has greatly increased your concentric dual requirements . . . be ready with this CONCENTRIKIT Stock Assortment on your bench. Handsome metal cabinet contains all you need to assemble quickly any of 144 different concentric duals. It covers over 500 models . . . RCA, Admiral, Air King, Belmont, Emerson, General Electric, Motorola, Philco, Westinghouse, Zenith and many others. Order from your IRC Distributor now, or send coupon for more information. International Resistance Company, 413 N. Broad St., Philadelphia 8, Pa.

HERE'S WHAT YOU GET

In Concentrikit Stock Assortment #13

	Quantity		Quantity
Complete Concentrikits	4	B19-133X	1
Base Elements		B11-137	3
B11-108	1	B13-137	2
B11-114	1	B13-137X	1
B11-115	1	B18-137XX	1
B11-116	1	B19-137X	1
B17-116	1	B11-139	2
B11-119	1	B13-139	1
B11-120	1	B13-139X	1
B11-121	1		
B11-123	2	Inner Shaft Ends	
B11-128	2	E-187	3
B11-130	1	E-190	1
B13-130	2	E-202	2
B13-130X	1		
B18-J30X	1	Sleeve Bushings	
B18-132X	1	S-4	1
B11-133	2	S-5	1
B13-133	2		
B13-133X	1	Resilient Retainer Rings	10
B18-133X	1	Switches	
		76-1	3

Concentrikit Stock Assortment comes in a sturdy all-metal cabinet. Four drawers and individual compartments assure efficient stocking . . . and cabinets may be stacked with IRC Resist-O-Cabinets to make a convenient and good-looking shop arrangement. METAL CABINET IS SUPPLIED AT NO EXTRA CHARGE, you pay only the regular price of the parts.

and
the
price
is—

ONLY
\$24.78
dealer net cost

ORDER YOURS TODAY!



**INTERNATIONAL
RESISTANCE COMPANY**

Wherever the Conduit Says

In Canada: International Resistance Co., Ltd., Toronto, Licensee

INTERNATIONAL RESISTANCE COMPANY
413 N. Broad Street, Phila. 8, Pa.

- I'm interested. Send Catalogs DC1A and DC2S with details on CONCENTRIKIT and Dealer Stock Assortment.
- Enclosed find 25c in stamps or coin for my copy of IRC Concentric Dual Replacement Manual.

Name.....

Company.....

Address.....

Field Findings

A resume of Industry happenings here, there and everywhere

TV Service Advertising

Newspapers and TV stations have been getting more and more advertising from service organizations who feature the advantages of buying a "policy" from them. Some of this advertising is first class, but most of it is very bad indeed. The good advertising simply states that for certain stipulated sums the TV set owner gets certain services for a period of time. The bad advertising contains either willful misrepresentation or, much worse, by deliberate omission deceives the prospective buyer into believing he is going to get much more than actually is the case. We are not going to publish examples of "bad" advertising for that would serve no useful purpose. However, here are illustrations of what can be considered good sales promotional effort.

Summertime TV Slack

All TV set makers have come to believe that the sales potential drops off sharply during the summer months, July and August. They are justified in that conclusion. But, such is not true of TV service potentials, for TV sets are more apt to require repairs during hot and humid summer weather than during more temperate periods. So, during the two Summer months ahead, while the volume of initial TV installation work drops off, it would be advisable for Service Dealers to spend any spare time rechecking the installations they have already made. Without doubt they will find that guy wires have gotten too much play, or have broken off. Or they'll find installations which were made improperly in the first place, and which should be corrected now. Even though the set owner may not have called for service, TV service contractors can render themselves a great money-making service by checking their jobs rather than by merely resting during the slack period ahead.

While on the subject of busy and slack periods, certainly April and May were bad months for TVmen because the plague of windstorms in all parts of the country required countless thousands of call-backs to reset antennas that had blown down or out of orientation.

by S. R. Cowan

More TV Statistics

According to RMA reports during the first quarter of 1950 over 1½ million cathode-ray picture tubes were made and of that total 98% were 12" or larger, 37% being 14" or larger. At the same time, it is interesting to note that the production and sale of conventional radio receiving type

Chicago to Omaha by this Fall. The extension from Omaha to San Francisco, routed via Denver and Salt Lake City, may be completed by the end of 1951. Let's hope so. Television, while still in its infancy, with only 108 stations in operation and less than 6 million TV sets in use, has already become one of this nation's 3 largest industries, having passed the \$2 billion mark already. Imagine what it will be like in 10 years if no untoward event, like a war, stymies its progress.

Phonograph Drive Planned

A committee of RMA, appointed for the purpose, has approved a plan to promote a national campaign designed to increase the sale of TVsets and conventional radios having built-in phonograph record players, and a joint campaign stressing the modernization of sets in use either by urging the set owner to add phono-players to those that are not so equipped, or by the conversion to 3-speed models if their sets are of the now obsolete single or double-speed player type. We are 100% behind such a campaign, particularly the phase that bears upon modernization of in-use equipment, for this is a purely service-technician type of business.

Only a small fraction of the millions of radios and TV sets now in use are phono-radio combinations. Likewise, in proportion to the total, there are hardly any 3-speed record-player combinations in use as yet. It's up to Service Dealers to try to change this picture for several reasons. To begin with, it is a known fact that the public wants to play records and have record-players. The fact that there are 3 types of records (referring to speeds) available and each having merit justifying its preference, thus simply means that we, as technician-installers, must do the sales promoting job which will result in the prospective customer saying "Okay, go ahead and install one of the new 3-speed units". Once again we must urge radio-TV technicians to overcome their inherent reluctance to be sales-minded. You've got to sell to survive—and in this instance you are basically selling your service as well as a product. No other

TELEVISION OWNERS!
AMAZING CASH DIVIDEND AND MONEY REFUND IN CASH ON 1st and 2nd Year Television Service Contracts

You can receive an actual CASH refund on your TV service contract with Video Labs. Any questions? Call Miss Scott.

- Service and maintenance on set and antenna
- Six-day work, 8:30 A. M. to 10 P. M.
- Free inspection
- Take 5 months to pay

Compare!
VIDEO LAB. Prices With Any In Town

7"	\$35	10"	\$45
12"	\$55	16"	\$65

Prices INCLUDE Picture Tube

NOW! Convert your present 10" to

12½" Large Screen	\$80
16" "Black Magic" Square Tube (Non-Glare)	\$99
19" "Super-Screen"	\$124

(Cabinet Optional)

VIDEO LABORATORIES, INC.
 1851 BROADWAY JUDSON 6-0180

TV FIXED FREE!
 If your set now needs repair, we'll fix it free with your **SERVIEO 2nd YEAR SERVICE & MAINTENANCE CONTRACT**

FOR COMPLETE DETAILS CALL

Far Green and Manhattan WA 6-4100	•	For Brooklyn and Queens NE 8-8308
33 W. 125th St., N. Y. C.		100 Bedford Ave., Brooklyn

FIRST WE FIX IT FREE—THEN WE KEEP IT FIXED!

This contract covers complete service. Day Time Payment. See store chart.

• 24 hour service	• 5 consecutive phone calls	• Complete equipment shop and 1000 parts	• Trained technicians
74 hour service	• 10" - \$45	15" - \$55	16" - \$65

Add \$5 each for radio and phono

SERVIEO, INC., 1261 Bedford Ave., Brooklyn 16, N.Y.

Examples of good sales effort

tubes during the first quarter of this year also broke all previous records. For example, in the first quarter of this year over 80 million radio tubes were made as compared to 40 million for the same period of 1949. In March 1950 over 40½ million radio tubes were produced, of which more than 6 million were for replacement use. Therein lies the reason why radio service dealers are doing so well. The more sets in use the greater potential for servicing and replacement sales. Actually, though, as the average TV set is equivalent to 7 conventional AM models, the service volume is still overwhelmingly concentrated in sections of the country having TV.

TV Wire Links

A. T. & T. has gotten its cable through from St. Louis to Memphis and plans to complete the link from

"This book might easily be worth \$100.00 to you!"




SERVICING TV RECEIVERS

• SYLVANIA ELECTRIC PRODUCTS INC.

\$2.

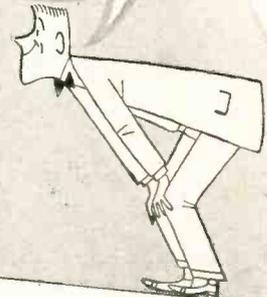"The most complete TV servicing book ever printed"



JUMPING PICTURE—NOISY SOUND



Characteristics
 1. Picture is unsteady, jumps and is erratic
 2. Thin white horizontal lines through picture
 3. Sound is distorted by noise

Cause
 A lost focus

Lead shorts the & frayed
 Exceed coil and receiver

SPLIT PICTURE (VERTICALLY)



Characteristics
 1. Horizontal bar in center of screen
 2. Half of picture on each side of bar
 3. Picture wobbles up and down
 4. Two pictures vertically in a single frame
 5. Vertical frequency too high or too low

Cause

Vertical hold control not properly set (R164)
 Resistor in vertical oscillator amplifier section is changed in value (R163)
 Shorted or leaking condenser (C167) in vertical oscillator amplifier circuit
 Shorted turns in vertical holding oscillator transformer (T58)

Remedy
 Manually reset vertical hold control

Check for resistance value with ohmmeter; refer to manufacturer's service guide
 Check for shorts in circuit with ohmmeter. Replace defective component
 Check transformer for continuity or a short with ohmmeter. Replace if defective

FREE NOW!...

with your order for 100 Sylvania Receiving Tubes or 3 Sylvania Picture Tubes

Could be this book'll be worth its weight in dollar bills. For it explains in clear, plain language and illustrations how to identify TV set trouble . . . and what to do about it.

Contains more than 100 pages . . . filled with diagrams and photos to help you more quickly locate trouble . . . solve problems . . . improve your TV set repair business.

FREE only until August 31st

Remember, you can't buy this book. It's yours free from your regular Sylvania distributor during June, July, and August, with the purchase of 100 Sylvania Receiving Tubes or 3 Sylvania Picture Tubes.

So call your distributor today . . . while his supply lasts. Ask him for the book that will improve your television service, and the tubes to improve your profits . . . SYLVANIA.

HERE'S WHY YOU NEED THIS BOOK

- Shows more than 80 actual photos of screen test patterns. Shows how to identify trouble by pattern behavior.
- Gives simple, concise instructions for making repairs, proper adjustments.
- Contains complete circuit diagrams of typical television receiver.
- Explains latest television developments.
- Tells about television test equipment and what each instrument will do.
- Provides a practical dictionary of television set trouble.

SYLVANIA ELECTRIC



RADIO TUBES; TELEVISION PICTURE TUBES; ELECTRONIC PRODUCTS; ELECTRONIC TEST EQUIPMENT; FLUORESCENT LAMPS, FIXTURES, SIGN TUBING, WIRING DEVICES; LIGHT BULBS; PHOTOLAMPS; TELEVISION SETS

RADIO SERVICE DEALER • JUNE, 1950

**TOP SALES PROVE TV
SET OWNERS WANT THE
QUALITY PERFORMANCE
AND QUALITY APPEARANCE
OF**



*. . . The
Astatic
MODEL AT-1
Television Booster*

YES, the proof is in! When TV set owners want improved reception, they want the best in boosters — as witness the soaring sales of Astatic's Model AT-1. This is the powerful booster with four tubes, and such exclusive features as dual tuning and variable gain control, the latter permitting pinpoint tuning for exact amount of boost required for best picture and sound. The Astatic AT-1 Booster not only outperforms any other on the market, but it looks the part — in handsome, furniture-finish mahogany or blond cabinet to complement the finest receivers and other costly furnishings. These are typical advantages which have made the Astatic Model AT-1 Television Booster the undisputed leader today. Why not write for complete details, technical data?

Astatic Crystal Devices manufactured under Brush Development Co. patents



class of radiomen, other than servicemen, enjoys such close personal contact with and entré to homes where there is potential business such as phonograph modernization work. So, let's get going! There's a bright, money-making promotional campaign being worked out now, and as soon as details are available from RMA's committee we'll give you the facts. Then it will be up to you to get your share of business, and it should be a cinch.

Higher Income Brackets

Twenty years ago a national survey was made to ascertain what the average radio serviceman's income was. Having ascertained that the average serviceman then earned approximately \$21 per week, a deplorably low figure, every effort was made to suppress the information. Ten years later it was learned that servicemen had improved their status to the point where they were averaging \$25 in gross weekly earnings. Remember, however, that in those days a man in the low income brackets kept for himself almost every cent he earned for the income tax rates did not affect him. Now-a-days we have a different situation.

Latest reports from reliable sources indicate that the average radio-TV technician is earning upwards of \$66.66 per week gross. He is a married man with 2 children. His average federal and S.S. tax deductions approximate \$3.09 weekly giving him a take-home pay check of \$62.97. Of course in most states he has to pay state, hidden and other sales taxes not known 10 years ago, and experts compute that these amount to almost \$2.05 more, weekly. So, in effect, today the average radio-TV technician is in the 10% tax brackets, but has a net income of \$60.95 as compared to \$25 a decade ago.

Other factors to consider are these: ten years ago the average radio technician worked 60 hours weekly while today the average is closer to 50 hours. So, summarized, the earnings status of radio-TV servicemen has improved to an impressive degree. Now-a-days we're not ashamed to call attention to our profession, for the status of "profession" is rapidly accruing to us.

Licensing Again Looms

Because various cities have had so many "serviceman complaint" problems recently, although the majority stem from complaints about dealers rather than technicians, the various civic fathers are again holding council hearings on the subject of licensing legislation. The hearings being held in New York City are typical. We

[Continued on page 27]

IF IT'S NEW...


KEN-RAD DEALERS HAVE IT!

THE way to get ahead, stay ahead, in radio-TV servicing, is stock and install Ken-Rad tubes! New types—because Ken-Rad designing sets the pace—come to you ahead of time. As 1950 home receivers appear in your neighborhood, G-E and Ken-Rad tube research enables you to service new sets with the ultra-modern types they require, whether TV-picture, metal, glass, or miniature. Ken-Rad tubes you receive today, fill tomorrow's needs!... 6AV5-GT is one of many advanced types you will find in modern TV circuits. Your Ken-Rad distributor has this new tube, and others, that will give you rail position in the race for more service business. Phone or write him at once!



6AV5-GT BEAM POWER TUBE

With its companion type the 25AV5-GT (heater requirement 25 v as against 6 v), this new tube serves as a horizontal-deflection amplifier in TV. Operating direct from a 125-v power supply, accessories such as a transformer and high-voltage filter capacitors can be done away with, which adds to circuit simplicity and economy. Design of the tube gives it the ability to withstand high surge plate voltages. ... By stocking the Ken-Rad brand, you will have the 6AV5-GT and 25AV5-GT—and other important new types—*now*, when required to service late-model receivers!

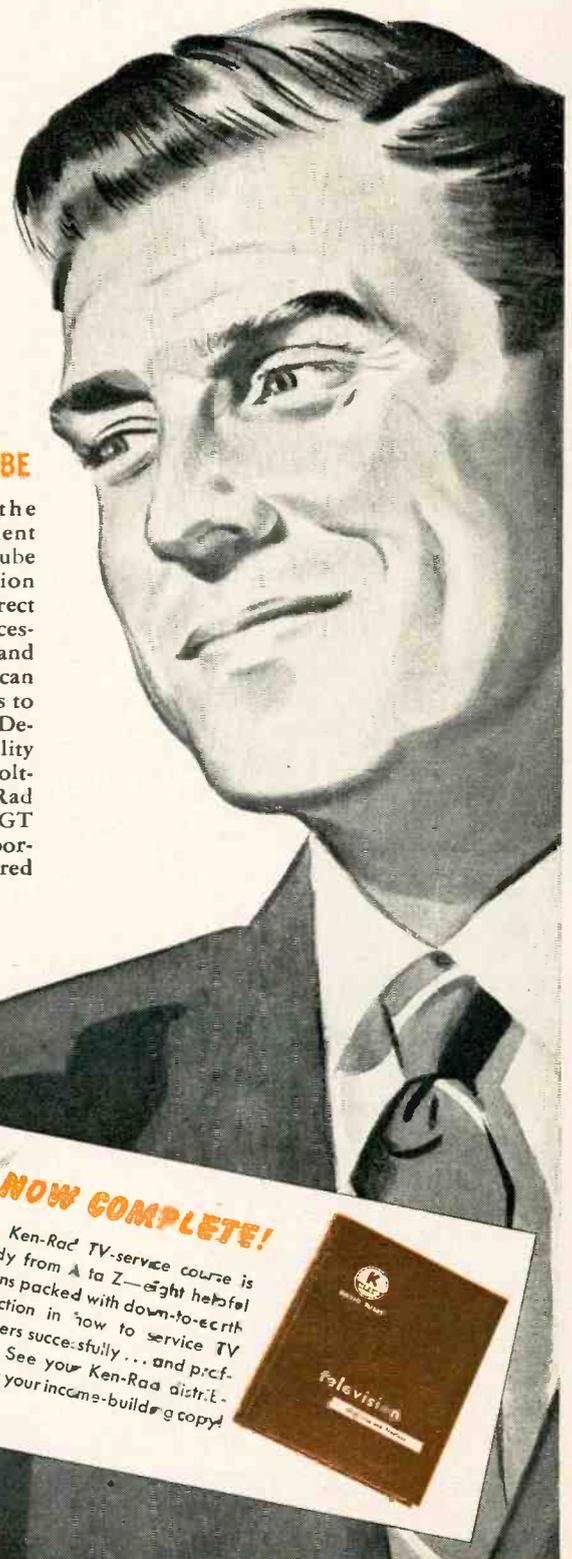

V NOW COMPLETE!

The Ken-Rad TV-service course is ready from A to Z—eight helpful lessons packed with down-to-earth instruction in how to service TV receivers successfully... and profitably. See your Ken-Rad distributor for your income-building copy!



KEN-RAD *Radio Tubes*

PRODUCT OF GENERAL ELECTRIC COMPANY

Schenectady 5, New York

182-JA4

PREMIUM QUALITY AT NO EXTRA COST

Sprague Black Beauty Telecap* Tubulars are different from and superior to every other molded paper capacitor because they are made by the same dry assembly process as large metal-encased oil capacitors. They cannot be contaminated by dust or moisture during manufacture.


Ask for Black Beauty Telecaps at your jobber's.

*Trade Mark

Non-flammable,
dense bakelite
phenolic-molded
housing

Hollow eyelid ter-
minal for oil im-
pregnation after
molding

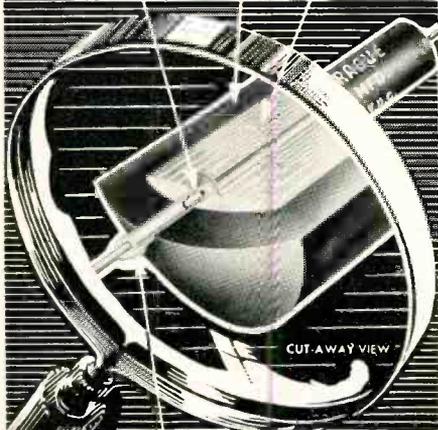Uniform wind-
ings of high
purity paper
and alumi-
num foil



Solder seal as in
large metal-encased
oil capacitors

SPRAGUE

SPRAGUE PRODUCTS COMPANY

(Distributors' Division of Sprague Electric Co.)

71 Marshall Street
NORTH ADAMS, MASS.

TRADE FLASHES

A "press-time" digest of production,
distribution & merchandising activities

	TV Sets	Home Sets	Auto Sets	All Sets
January	335,588	470,715	189,480	995,783
February	367,065	529,254	221,139	1,117,458
March (five weeks)	525,277	724,691	255,673	1,505,641
TOTAL	1,227,930	1,724,660	666,292	3,618,882

Receiver production figures first three months, 1950

TV Production

Television receiver production during the first quarter of 1950 was 21 percent higher than in the previous peak period, the last quarter of 1949, and was more than three times the output of TV sets in the first quarter of 1949, the Radio Manufacturers Association said today.

Following is a month-by-month breakdown of radio and television set production reported to RMA for the first three months of 1950:

RCA Service Clinic

Spurred by the response to its first television Service Clinic, which attracted more than 5,000 RCA Victor and independent television servicemen to more than 50 inaugural meetings conducted nationwide last month, RCA Victor announced that the second in the series of six scheduled lectures got under way during the week of May 1.

An essential part of the lecture will be the display and demonstration of television test equipment, provided by the RCA Service Company, which includes a sweep generator, oscilloscope, and a marker oscillator. In addition to film slides and printed lecture texts, the meetings will also feature a dynamic demonstrator which will be used to illustrate how servicemen can localize service troubles by analyzing the kinescope picture. Each serviceman attending the lecture will receive a booklet, complete with illustrations and diagrams, covering the information discussed. In effect, the complete set of six manuals, one for each of the six different lectures scheduled, will serve as an invaluable reference guide for the servicing of RCA Victor television receivers.

New Du Mont Color System

A patent for a three color direct view television tube has just been issued to Allen B. DuMont Laboratories, Inc.

In its construction, the new tube is similar in most ways to the familiar black-and-white picture tube except for a new form of fluorescent screen. Instead of having a coating of fluorescent material which produces black and white pictures when struck by an electron beam, this new color tube has a fluorescent screen composed of tiny fluorescent dots which give forth red, blue, and green colors respectively when struck by the electron beam. The tiny dots are arranged so that each dot of one color is adjacent to adjoining dots of another color.

In operation, as the electron beam of this new color television tube passes over the tiny color spots successively, it is turned on and off rapidly in accordance with both the brightness and color of the picture to be reproduced.

The new color television tube can be used in any one of the three color systems now proposed before the F.C.C.; namely, field sequential, dot sequential, or line sequential.

Tele-Clues Proving Popular

A series of pictorial "Tele-Clues" to aid servicemen in localizing circuit defects within television sets, are proving to be popular as evidenced by the large number of requests received by the editor. The "Tele-Clues", which are available free of charge through General Electric and Ken-Rad distributors, are inserted in the bi-monthly publication, "Techni-talk" which is published by the Tube Divisions of General Electric.



[Continued on page 28]

**ANOTHER TACO
REQUIREMENT-DESIGNED
TYPE ALL-CHANNEL
TACO**

TRI-X


● For 16 years Taco has been providing the serviceman with the antenna best suited to his particular needs. For each TV area with its own specific conditions as to channels operating, directivity and signal strength, Taco has provided the best design.

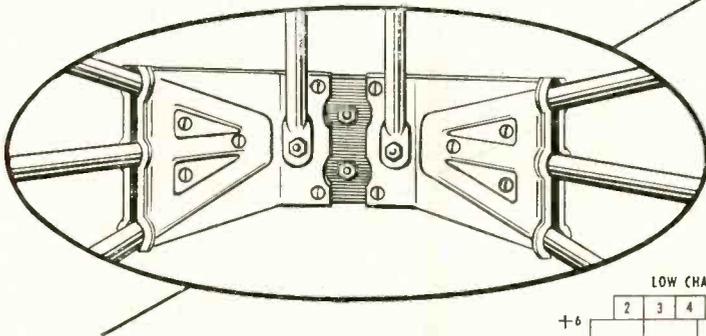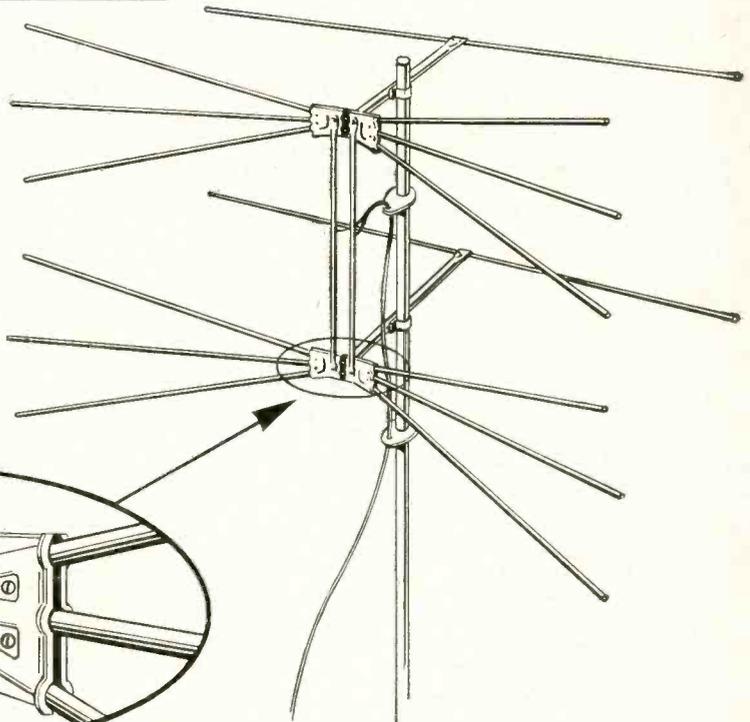For areas where additional gain is desired on channels 11, 12, and 13, the new Taco Tri-X is now offered. Designed as an alternate for the Lazy X, this new Taco antenna incorporates all the latest developments of the unparalleled Taco Engineering and Research facilities.



The new apex design used in the Taco Tri-X eliminates the inherent weak point of X type antennas. Heavy aluminum fans, ribbed for extra strength, are bell-mouthed on ends of grooves thus leaving no sharp edges in contact with element rods. Special Taco noise-snubber eliminates bothersome wind-whistle effect. Jiffy-Rig construction provides the fastest, most practical assembly.

SEE YOUR JOBBER FOR PRICE AND DETAIL

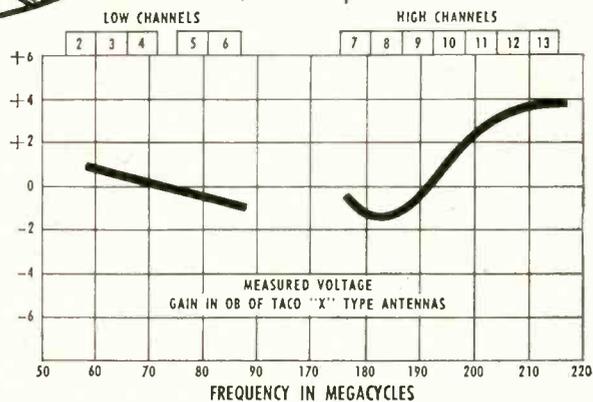

Graphic illustration showing gain of Tri-X compared to Lazy X. Through low-band difference is negligible. In high-band operation the Tri-X shows considerable gain over the Lazy X on channels 11, 12, and 13.

MR. TV SERVICEMAN:

Don't risk your reputation or lose TV receiver sales by gambling with unproven antenna equipment. Taco equipment has proven itself for the past 16 years. Avoid those costly call-backs due to electrical or mechanical failures in antennas.

RADIO AND ELECTRONIC EQUIPMENT

TACO

TECHNICAL APPLIANCE CORP.

SHERBURNE, N. Y. • IN CANADA: STROMBERG-CARLSON CO. LTD. TORONTO 4, ONTARIO

Are You KEEPING Your TV Installation PROFITS


... Or paying them back
in "FREE" Service Calls?

IT'S expensive... following up nuisance calls and "complaints" during guarantee periods... wasteful in truck operation, traveling time and labor. You can reduce your costs to a new low - with the high quality, all-around ruggedness and dependable performance of Federal lead-in cables!

Where noise level is low - Use Federal K-1046 ... with distinctive Federal-developed "silver" polyethylene insulation... providing 30 per cent more service life than ordinary polyethylene. K-1046 repels sunlight... fights heat... doesn't dry out, crack, buckle or leave conductors exposed. It holds its original characteristics longer... retains its impedance values. In Weatherometer tests, K-1046 surpassed all competitive types.

Where noise level is high - Use Federal K-111... shielded lead-in... another exclusive FTR development. K-111 is a top item in TV because it minimizes noise, snow and ghosts due to transmission line pick-up. Pictures are clearer, brighter and steadier... all the time. Actually, Federal's K-111 permits TV installations in many noisy areas where good, clear reception was impossible before!

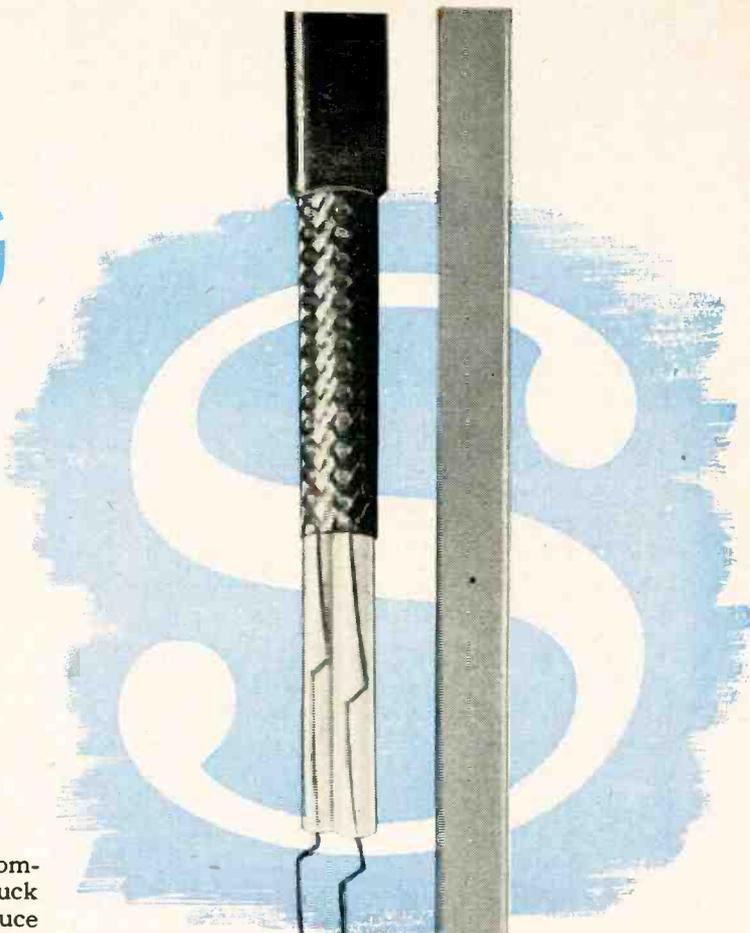See your distributor now for data and prices on Federal's K-1046 and K-111... for that next new installation or lead-in replacement. You can depend on these highly efficient 300-ohm lead-ins to keep service calls down... to keep profits UP. Insist on Federal... it pays to start with the best!



K-111
300-Ohm
Shielded
Lead-in for
HIGH
Noise Level
Areas

K-1046
300-Ohm
"Silver"
Polyethylene
Lead-in for
LOW
Noise Level
Areas

These **2**
Federal TV Lead-ins Protect
Your Profits in
HIGH and LOW
Noise Level Areas

America's largest producer of solid dielectric high-frequency cables



Federal Telephone and Radio Corporation



SELENIUM and INTELIN DIVISION, 100 Kingsland Road, Clifton, New Jersey

In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.

Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

The tube lifting procedure will not work with the a-c/d-c receivers, however, because of the series filament arrangement. Again, however, if all tubes are lit and with the chassis removed from the cabinet, each grid terminal of the tube socket can be touched with the end of a screwdriver. Inasmuch as the grids are the most sensitive, this method will again produce clicks if B voltages are present and the signal finds continuity from the disturbed grid to the loudspeaker. This procedure is, in reality, a rudimentary form of signal tracing and forms an excellent basis upon which to build the trouble shooting procedures.

If the set acts alive for all tubes but one, the stage in which the trouble exists will have been localized. From then on it will be a matter of checking the suspected tube with a tube checker or locating the defective resistor or condenser which is giving trouble in that particular stage.

If the set acts totally dead and it has a dynamic type of speaker, several quick means can be employed for finding out whether or not the field coil is open. One of these methods consists of bringing a screw-driver near the center bar of the speaker pot in order to see if the magnetic field is absent due to lack of B current flowing through the field coil. With most modern receivers, however, the front is sealed off by a felt disk to prevent metal filing or dust from entering the voice coil aperture. A better method is to get a pocket compass and have it handy on the work-

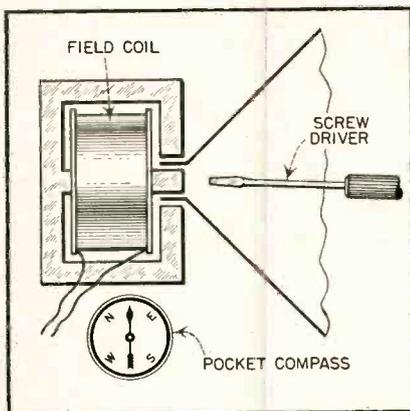


Fig. 2. Quick means for checking magnet field in speaker.

bench. Bringing the compass near the field coil will give a quick indication of B current flow through the field coil, and the presence of the magnetic field is a sure indication that the field coil is not open. (See Fig. 2)

Another cause for the set acting totally dead is a defective output

transformer. If the primary opens, the output tube (or tubes) will not receive B voltage and no sound will reach the voice coil. The latter, too, could be defective, as well as the secondary winding of the output transformer. An ohmmeter check of these sections will, of course, show up the trouble, as would B voltage check at the plates of the tubes. A handy device, however, which will give an immediate audible indication of the trouble, as well as show up any distortion or volume decrease which might arise by faulty output components, is indicated in Fig. 3. This consists of a small PM speaker mounted in an old receiver housing or attached to the most convenient place on the work bench.

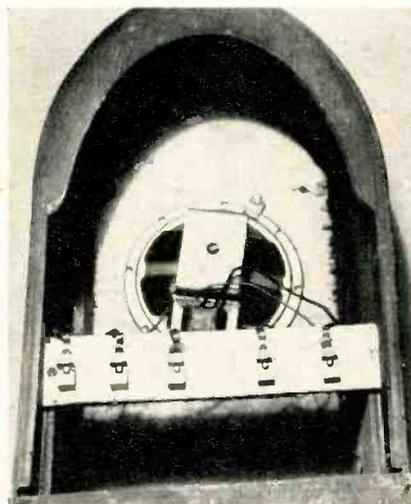


Fig. 3A. Physical appearance of test speaker illustrated schematically in Figure 3B.

This test speaker is wired in such a manner that it will check voice coils, secondaries and primaries with a minimum of bother, and some of the older shops have several set up along the bench. As shown in Fig. 3, a terminal strip is provided so that test prods can be attached as required. If the primary of a transformer is suspected, terminals 4 and 5 can be placed from the output tube plate to +B, placing a jumper across 1 and 2 to close the circuit. If this speaker produces the sounds from a station, the trouble will, of course, be in the transformer or speaker of the receiver. If the test speaker gives no sound, the earlier stages should be checked for open circuits or defective components. If the output transformer of the receiver is shorted, the test speaker will not function—but the usual trouble in transformers will be open circuits, and it is rare that a short is encountered.

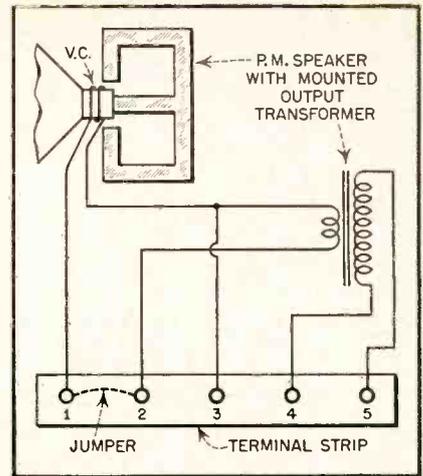


Fig. 3B. Wiring diagram of service bench test loud speaker.

If one of the tubes of a push-pull stage is defective, the test speaker will also indicate this, by placing terminal 4 at the plus B center of the transformer and alternately touching the terminal 5 test prod to the plate of one output and then the other. The lack of response for a particular test will indicate, of course, which push-pull tube is defective.

If the test speaker plays at the primary side of the output transformer, but the receiver is still dead, the trouble must lie in either the secondary winding or in the voice coil of the speaker itself. In this case a quick check can be made by removing the jumper from terminals 1 and 2 of the test speaker, and running test prods from terminals 1 and 3 to the secondary of the receiver's output transformer. This places the voice coil of the test speaker across the output and if no sound is forthcoming it indicates a defective secondary or shorted voice coil. If the test speaker does play, then the secondary winding is all right, but the voice coil of the receiver's speaker is at fault. Many other uses will be found by the servicing technician for this simple and inexpensive time-saver.

Checking Distortion

Distortion in audio amplifiers is usually due to faulty coupling capacitors, incorrect bias or defective tubes. In push-pull a decided unbalance between the tubes will also be a contributing factor, even though both tubes may check all right in a tube checker. A rapid method for ascertaining unbalance is to place a d-c voltmeter directly across the two plates of the output tubes as shown in Fig. 4. If both tubes are substantially matched and drawing equal currents, little voltage will appear across them. If they are decidedly mis-

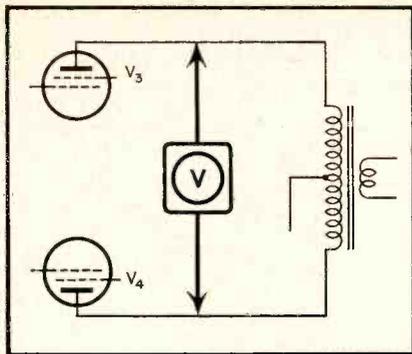


Fig. 4. Quick check for unbalance in push-pull stage.

matched, potentials of 5 volts or more will be encountered. If the meter reads backwards, change the meter leads. Zero voltage should not be expected across the plates, because there will always be slight differences between the d-c resistance of the two primary windings as well as small differences in tube emission. Voltages up to approximately five volts are normal, though voltages of 8, 10, or 15 volts indicates tube replacements are necessary.

For efficient push-pull operation, two tubes should be chosen which have similar emission characteristics. If, for instance, four tubes are checked on a tube tester and the readings are as indicated in Fig. 5, tubes 1 and 2 would work better in a push-pull arrangement than tubes 1 and 4 or 1 and 3. Tubes 3 and 4, however, will also be satisfactory, since these two have similar characteristics. Thus, even though all four tubes are good, certain combinations will not work out best for push-pull operation.

Another common cause of distortion are leaky coupling capacitors, because their lowered resistance will alter the grid voltage due to leakage from the +B side of the capacitor. The quickest way of checking this is to read grid voltage from grid to cathode, to make sure a minus bias still exists. A plus grid potential means either a bad coupling capacitor or a gassy tube, and both should be checked further. Bridging a coupling capacitor with another is no check for a leaky condition, since putting another across a leaky one does not remove the partial short. Bridging a along the bench. As shown in Fig. 3, capacitor (or resistor) is only a means for checking a suspected open circuit, not a leaky or shorted condition. If the coupling capacitors of a push-pull stage are suspected, both should be replaced for either one alone can introduce distortion.

In Fig. 1, a shorted $C1$ or $C4$ would also cause distortion because it would

remove the bias which is developed across these cathode resistors and cause excessive tube currents. A d-c voltage check across these resistors will indicate a shorted capacitor by the absence of a reading. If either of these capacitors open, there will be a decrease in volume due to degeneration, but distortion will not be produced. In case of a suspected open capacitor, another one can be temporarily placed across it as a rapid check. A pronounced increase in volume indicates an open cathode bypass.

Other causes of distortion may be loose speaker cones, improperly centered voice coils or insufficient magnetic fields in the speaker core. A substitution check with the test speaker as previously detailed will indicate whether the distortion exists in the speaker or originates within the circuit itself.

Checking Other Troubles

As will be noticed in Fig. 1, the screen grids of $V3$ and $V4$ are returned to plus B, a common practice

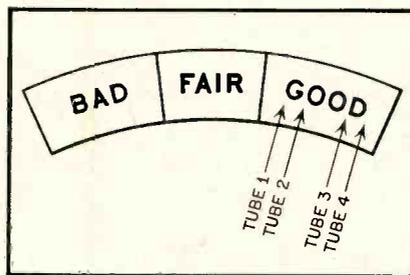


Fig. 5. Tubes which read closest to each other should be paired.

in both single and push-pull outputs. With pentodes and beam power amplifiers the slightly greater screen potential has no appreciable affect on performance, and this design eliminates the need for a screen dropping resistor and a by-pass condenser. In this position the second filter condenser of the power supply effectively acts as a by-pass for the screens and prevents signal variations and motorboating. If severe motorboating exists, therefore, a quick check can be made by placing an 8 or 16 μf electrolytic from one of the screen grids to ground. If this stops the motorboating, the second filter capacitor should be replaced. This check works in almost all instances, because the motorboating is usually due to an open second filter, or one in which the capacity has decreased to an appreciable degree. When the test establishes a defective filter, the old one should be removed, because a decrease in capacity is usually accompanied by a decrease in resistance, and the ca-

pacitor may be passing a considerable amount of current, thus loading the power supply and dropping B voltages. Any filter condenser which runs hot should be replaced, because it indicates excessive current drain.

Distortion in push-pull will also result if one of the push-pull tubes becomes defective, or if one side of the primary opens. If the defective tube does not short, the amplifier will still function, though with decreased efficiency. This does not always show up as distortion unless the volume is turned up, because the remaining tube is still capable of handling approximately half of the normal power output of the push-pull stage. Thus, if distortion is high when the volume is turned up, but virtually non-existent with low volume, it may mean one push-pull section is not functioning.

If glass tubes are used in the final stage they will provide for virtually an instant indication of an open transformer section. With the one side of the primary open, the tube plate will receive no voltage. The excessive current flowing through the screen grid circuit will cause the screen grid wires to glow brightly from the excessive current dissipation, and this indication is readily visible in the glass tube. With the metal tubes, lifting one tube out, replacing it and lifting the other of the push-pull tubes, will show which side is the dead side, because the receiver will not play when the good tube is pulled out and the defective one remains. This test will also be effective for indicating an open transformer section in the primary.

While the foregoing short cuts will not solve all the problems of trouble shooting audio amplifiers, particularly those of the intermittent type, they will in most cases enable the technician to save considerable time in localizing the stage or even the exact part which is defective.

Similar procedures can be applied to other stages of FM, AM or TV receivers with the same time-saving results. When these short cut methods have been applied several times, they will become an automatic routine which will greatly facilitate and expedite trouble shooting.

**TECHNICAL WRITERS
WANTED**
for articles on
AM - FM - TV - SOUND
Radio Service Dealer Magazine
342 Madison Avenue
New York 17, N. Y.

Conversion of 630 JS Chassis TO 3 ft. x 4 ft. PROJECTION

by V. R. PARKER

Chief Engineer, Hi-Par Products Co.



Fig. 1. Complete unit in operation.

Converting 630 chassis for Projection TV can prove highly profitable if the proper sales approach is made

CONVERSION of an RCA 630 TS type chassis to 3 ft. x 4 ft. Projection may readily be done by means of a kit manufactured by the Hi-Par Products Co. The projection unit used is the Norelec Protelgram Television Projection System (North American Philips Co., Inc.). The kit consists of a wired Picture Tube Protection and Power Supply for the H.V. Driver Unit chassis, plus a number of interconnecting cables and components, the purposes of which will be explained shortly.

Used in conjunction with the Protelgram System, which consists of a 3NP4 projection tube, a 3NP4 tube socket with cable, a tailpiece, an optical box, and a high voltage power supply; and housed in a suitable cabinet as shown in *Fig. 1*, excellent results will be obtained on a suitable screen. *Figure 2* illustrates all the parts and units necessary for the conversion. The circuit schematic of the Picture Tube Protection and Power Supply for the H.V. Driver Unit is shown in *Fig. 3*.

Circuit Changes

By referring to *Figs. 4* and *5* which are the original and modified circuit diagrams it will be seen that the principal changes to be made on an existing chassis are in the 2nd video amplifier stage. This is necessary because the 3NP4 projection triode requires considerable more grid drive than conventional 10" or 12" direct view type tubes. A peak to peak voltage of 90 to 100 volts is quite satisfactory. A 6V6 beam type tube is used in place of the 6K6 pentode. A lower value plate resistor (2200 ohms) is used to increase the band width and a B+ supply of 275 volts is used in place of the 135 volt connection. Other changes are in the grid circuit and cathode bias resistors.

The procedure in making the conversion is as follows:

1. Before attempting the conversion it is absolutely necessary that the TV chassis be in perfect normal operating condition with a direct view tube. A copy of the service notes on the 630TS receiver as published by RCA Victor should be available for reference purposes.
2. Remove the following parts:
Deflection coils and focus coil.
C. R. tube socket.
Focus control.
1B3 tube and connection to top cap.
H.V. lead to C.R. tube.
3. Detach Brightness control and Hor. and Vertical hold control from their bracket.

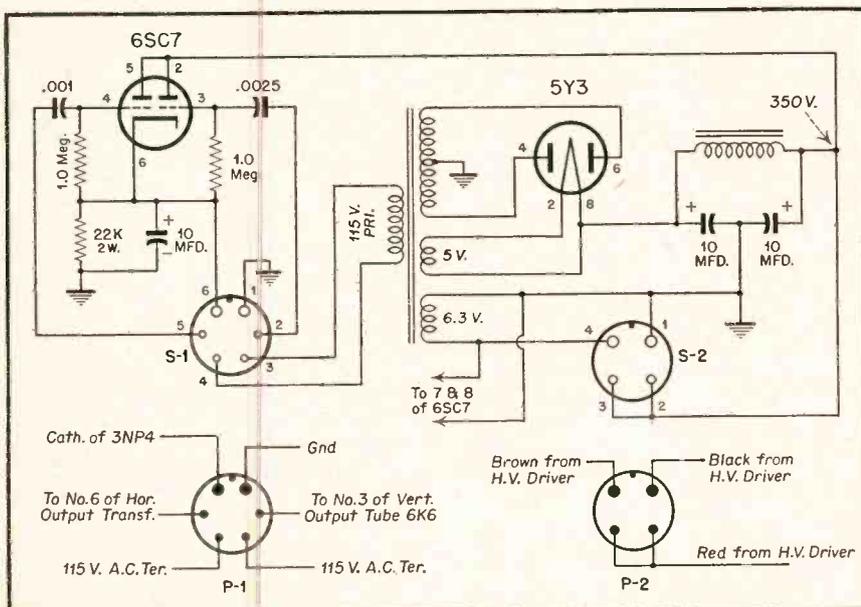


Fig. 3. Picture Tube Protection and Power Supply for H. V. Unit.

4. Remove bracket controls are mounted on.

5. Install new bracket for controls. One end is mounted under nut that holds the volume and contrast control to chassis. The other end is mounted to chassis using the same 3 self tapping screws previously used.

6. The controls are now mounted to the new bracket with the Brightness Control on the *inside* and the Horizontal and Vertical hold control on the *outside*.

7. The focus control is mounted in the center of the bracket. An extension shaft is provided to increase the shaft length to match the other controls.

8. Install one of the bakelite terminal strips with #6 screw and nut in the small hole next to the $\frac{3}{8}$ " hole that previously held the focus control.

9. Remove the 1800 ohm resistor R-183 in the focus coil circuit. One end of the 270 ohm 2 watt resistor R-182 is attached to one terminal of this strip and the connection that previously went to the arm of the focus control is attached to the remaining terminal. From these two terminal points connect the twisted black wire to the focus control, routing the wire through the wide slot in the front center of the chassis.

10. The remaining bakelite terminal strip is mounted close to the 6K6 2nd video amp. tube socket in one of the holes that previously held the focus coil bracket to the chassis. The original self tapping screw is used.

11. From terminal #4 of the 6K6 2nd video amplifier V-116 socket remove the 135 V. B+ connection and the short wire that is connected to

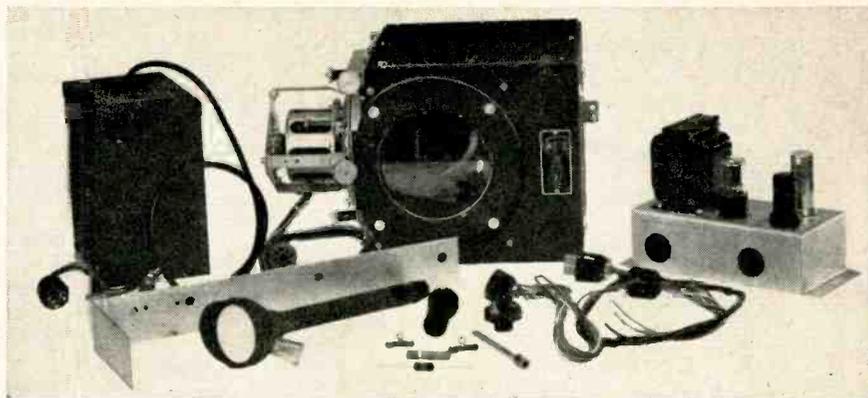


Fig. 2. Parts necessary for conversion.

terminal 6 of the 6AU6 1st video amp. V-115. These are now soldered to one terminal of the bakelite terminal strip. This is very important as this preserves the continuity of the 135 V. B+ through the entire chassis.

12. Next remove the 3300 ohm resistor R-147 and in its place install the new 2200 ohm 2-watt resistor. A connection is now made from terminal 4 of tube V-116 and the 2200 ohm resistor to a 275+ point. The end of the 6800 ohm resistor R-141 is a convenient point to make this connection.

13. Remove the video peaking link jumper bar on rear of chassis. Remove the 330 ohm resistor R-144 from cathode circuit and replace with the new 220 ohm resistor provided.

14. In the grid circuit of V-116 the 1.2 meg. resistor is removed. The grounded end of the 820 K ohm resistor E-142 is removed and attached to the remaining terminal on the bakelite terminal strip. A connection from this point to -2V. is made by running a wire to one side of the 470 K ohm resistor R-138 in the grid cir-

cuit of the 6AU6 1st video amplifier tube V-115.

15. Replace the 6K6 2nd video amplifier tube with the 6V6GT.

Final Assembly

This completes the actual circuit modifications and it is now only necessary to connect the 7-wire cable from the optical unit, the 6-wire cable from the picture tube protection and H.V. driver power supply chassis, and the 5-wire cable to the picture tube.

The 7-wire (octal) cable from the Norelco Optical Unit fits into a male octal socket supplied with the kit. The other end of this cable is connected to points on the receiver as explained shortly. The 6-wire cable plugs into the Picture Tube Protection Unit, and is also connected to various points in the receiver. The 5-wire cable is the picture tube cable supplied with the Norelco Unit, and connects to certain points in the receiver as explained shortly. Finally, the 4-prong cable, which is part of the Norelco

[Continued on page 35]

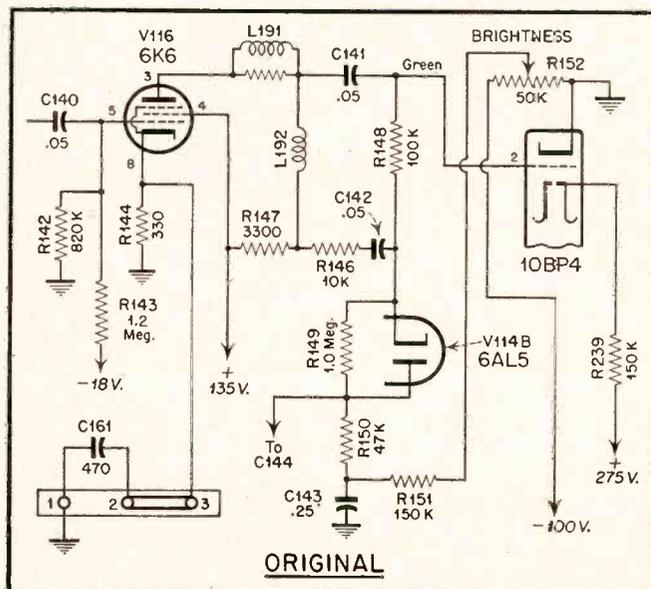


Fig. 4. Original 630 TS partial schematic.

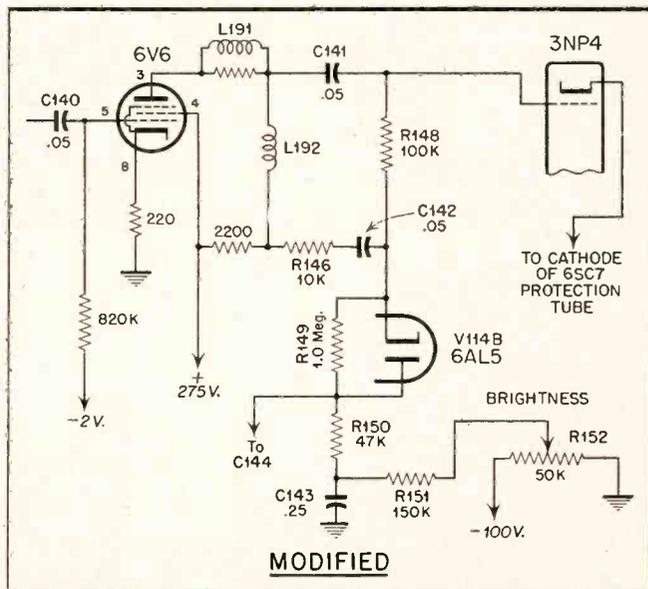


Fig. 5. Modified 630 TS partial schematic.

Combination Inductance Bridge

by Rufus P. Turner

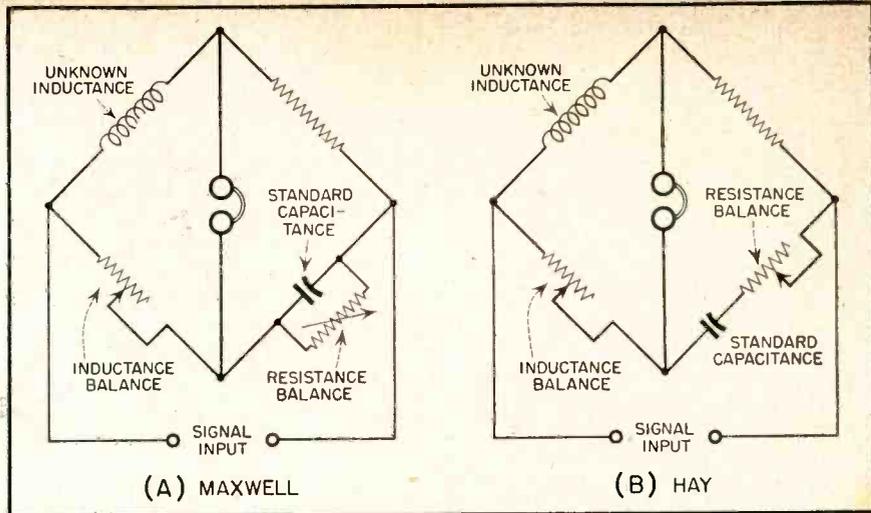


Fig. 1. Maxwell and Hay Bridge Circuits

Inexpensive arrangement which may be switched to either Maxwell or Hay circuit for close adjustments with all coils.

THE Maxwell bridge is very handy for coil checking because its circuit is simple and it requires no inductance standard. This bridge measures an unknown inductance in terms of a known capacitance, a desirable method since accurately-determined capacitors are more readily obtained by servicemen than inductance standards. A very useful bridge


may be assembled from ordinary radio parts and calibrated with an ohmmeter.

Many technicians who have built Maxwell bridges have had difficulty in securing a good resistance balance, especially when checking large iron-core choke coils. This is because the resistance balance rheostat is in parallel with the standard capacitor,

as shown in *Fig. 1(A)*. The Hay bridge (See *Fig. 1(B)*), on the other hand, is more satisfactory for checking such coils. In the latter circuit, the resistance balance rheostat is in series with the standard capacitor. It would appear that some scheme for changing the Maxwell bridge to a Hay bridge, and vice versa, would permit checking of all kinds of coils with little difficulty.

Figure 2 shows how the addition of a double-pole, double-throw switch (S_2) will permit the resistance balance rheostat to be connected at will either in series or in parallel with the standard capacitor. In position *M* of switch S_2 , the rheostat is in parallel with the capacitor and a Maxwell bridge circuit is obtained. In position *H*, the rheostat is in series with the capacitor, and we have a Hay bridge. Thus; if a satisfactory null setting is not obtained at one position of the change-over switch, simply throw the switch to the other position and repeat adjustments of the inductance balance rheostat (R_1) and resistance balance rheostat (R).

The circuit constants given in *Fig. 2* permit measurement of the inductance of all air-core, iron-core, and powdered-iron-core coils between 10 microhenries and 100 henries. Four ranges are provided. Rheostat R_1 is a linear-taper wirewound unit and may be of the volume control type. Its dial is graduated in as many steps as possible from 1 to 10. (1 corresponds to the 100-ohm setting of R_1 , and 10 to the 10,000-ohm setting). The calibration may be carried out with a resistance bridge or a good ohmmeter. The dial readings are in-

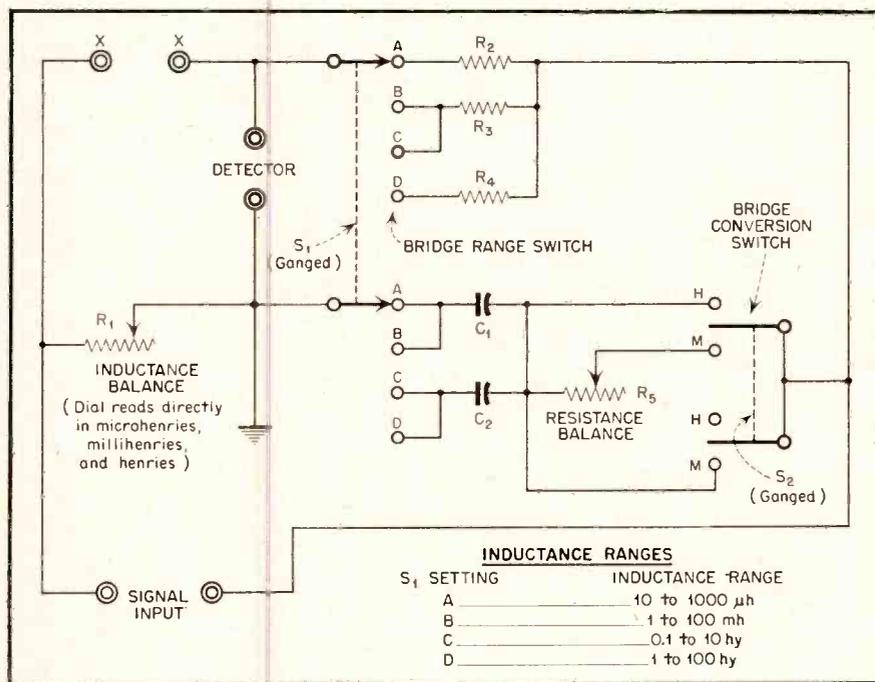

- C₁—0.01 ufd. mica
- C₂—1.0 ufd. oil-impregnated, oil-filled
- R₁—10,000-ohm linear-taper wirewound potentiometer
- R₂—10 ohms 1 watt
- R₃—1000 ohms 1 watt
- R₄—10,000 ohms 1 watt

- R₅—250,000-ohm potentiometer (See Text)
- S₁—2-pole, 4-position, non-shorting rotary selector switch
- S₂—2-pole, 2-position, non-shorting rotary selector switch
- S₂—2-pole, 2-position, non-shorting wafer-type switch

Fig. 2. Circuit of Combination Bridge

[Continued on page 35]

FRONT ENDS

by Samuel L. Marshall

(From a forthcoming book, "Television Service Techniques")

Part I

The purpose of the Front End, and its position in the overall receiver was discussed in the previous installment. We are now ready to analyze the circuits and components of various types of Front Ends used in television receivers. In this first installment we cover the ant. and r-f input sections.

BREAKING down the Front End into its basic circuits as indicated in the block diagram of Fig. 3-1, we find that the signal progresses through this section* in the following manner: First, coming from the antenna the signal enters the receiver through a suitably matched Antenna Input circuit. The output of this circuit is then fed into an r-f tube, from which it proceeds to an r-f transformer. After amplification and selection in these circuits the signal enters the mixer tube. There it combines with the signal from the local oscillator, and, by the familiar action of heterodyning, produces *sum* and *difference* frequencies in the output of the mixer. All signals except the *difference* frequencies are short circuited by the i-f transformer which is connected in the plate circuit of the mixer.

Front End Requirements

A properly operating Front End should provide the following:

1. Proper impedance match between downlead and receiver.
2. Proper electrical and mechanical selection of the desired Channels.
3. Proper conversion of the incoming r-f signal to the required sound and video intermediate frequencies.
4. Good signal to noise ratio.
5. Proper bandwidth characteristics.
6. Rejection of unwanted frequencies.
7. Amplitude and Frequency stability.
8. Ease of servicing.

The effectiveness of a Front End in meeting the above requirements is usually dependent on the care and ingenuity put into the electrical and mechanical design, the quality of its components, and the extent to which it has been put through actual tests in the field. In the early days of TV many manufacturers and servicemen engaged in contract work suffered great financial losses as a result of Front End trouble; Front Ends which

behaved well at first but which broke down in the Field. This could have been prevented by a little more time and effort spent by manufacturers in testing the durability of their products. The lesson learned by many servicemen as a result of this experience has been not to accept claims by any manufacturer regarding his products unless backed up by adequate field tests or authoritative testing agencies.

Effects of Line Mismatch

For optimum transfer of signal energy from the antenna to the receiver, and for minimum reflections in the antenna circuit, the characteristic impedance of the downlead should be equal to that of the input circuit of the receiver. Impedance mismatch between these two circuits may weaken the signal at the antenna terminals of the receiver. The reason for this is that line mismatch produces reflections and standing waves which in turn increases the *reactive*

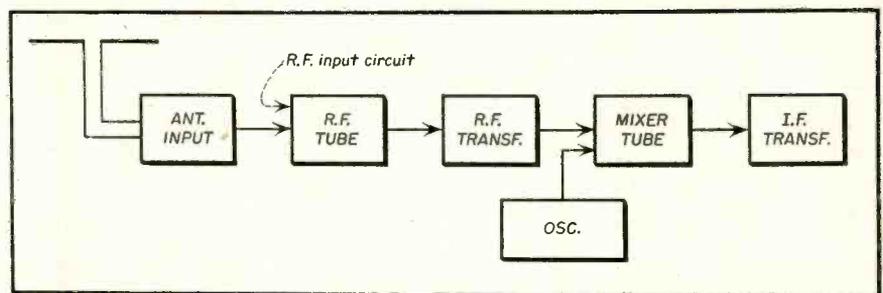


Fig. 3-1: Block diagram of typical Front End.

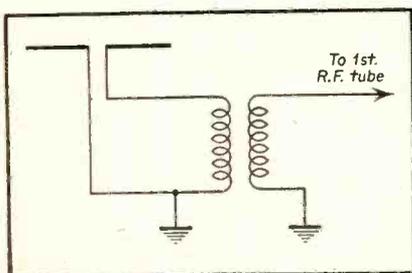


Fig. 3-2: Unbalanced input.

* RSD, May 1950, Elements of Signal Distribution, Part 1, Fig. 2-3

line current, thereby producing greater line losses. A line which is reactive is one in which an equivalent amount of inductance of capacitance exists.

For the same reason, a mismatched line may produce phase conditions or standing waves along the line. Thus, the signal strength may actually have maximum and minimum values all along the line, and if by chance the line is connected to the receiver antenna terminals at a point of zero potential, very poor reception will be had. Where such conditions exist, better results may be obtained, especially on weak stations, by trying different locations on the line as the points of connection to the receiver.

Another condition arising from an unmatched line is picture blurring caused by reflections set up in the line.

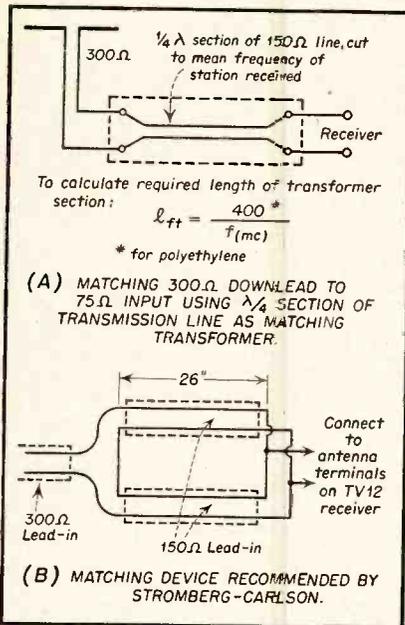


Fig. 3-3: Two methods of matching downloads to receivers.

These reflections produce multiple images on the picture tube screen which, though not as widely separated from each other as the familiar "ghosts" produced by building reflections, are separated just enough to produce a blurred picture.

Antenna Input Circuits

Antenna input circuits are broadly divided into two categories, balanced, and unbalanced. Referring to Fig. 3-2 we show a typical unbalanced circuit. Unbalanced circuits are generally designed for use with 75 ohm unbalanced coaxial cable. In some locations, particularly in Fringe Areas, it might be necessary to use 300 ohm line with a 75 ohm input receiver because of the

* For complete treatment see "Television Installation Techniques", by Samuel L. Marshall; John F. Rider, Publishers.

TYPE	CHARACTERISTIC IMPEDANCE (OHMS)	CAPACITANCE $\mu\text{mf}/\text{ft.}$	ATTENUATION db/100 ft. 200 mc.	VELOCITY OF PROPAGATION	
COAXIAL CABLE (LOW CAP)	71	13.5	4.4	65.9	Coax.
300 Ω	300	5.8	3.6	82.0	
150 Ω	150	10.0	4.7	77	
75 Ω	75	19.0	8.3	69	Unshielded Polyethylene twinlead
FEDERAL K111	300	4.2	4.6	82	
FEDERAL K117	185	6.8	6.0	84	Shielded twin-conductor cable
FEDERAL K200	200	7.8	.66*	—	
ANACONDA ATV225	225	6.4	4.7	84	

Fig. 3-4: Characteristics of coaxial cable, twinlead, and shielded twin conductor cable. Federal K200 is a very large diameter cable.

lower loss characteristics of 300 ohm line. In such cases a proper matching transformer, or system such as shown in either Fig. 3-3A or B, may be used. These systems make use of the properties of transmission lines whereby they behave as transformers when cut to one-quarter of their operating wavelength, and connected in the line at their open ends. It might be pointed out that there are many excellent grades of coaxial cable, single and balanced, which approach the low-loss characteristics of polyethylene twinlead, and which have the added advantage of being matched to the receiver without the use of impedance matching devices.

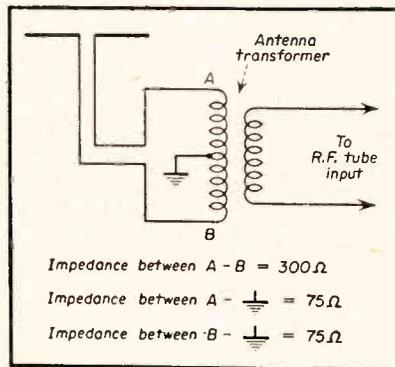


Fig. 3-5: Balanced input.

The following is an example illustrating the application of these principles to a typical problem.

Example 3-1:

Find the length and impedance of a section of quarter-wave line designed to match a 300 ohm download to a 75 ohm antenna input. The station being received is Channel 4 (66-72 mc).

Solution:

- Mean frequency equals $\sqrt{66} \times \sqrt{72} = 70 \text{ mc.}$
- Length (ft.) = $\frac{70}{400} = 5.71 \text{ ft.}$
- Impedance = $\sqrt{300 \times 75} = 150 \Omega$

For best results the transmission line should not be rolled up. Note also that the length of line was calculated for Channel 4, and does not hold for other frequencies.*

Comparative loss, propagation, and capacitance per foot characteristics of twinlead, coaxial cable, and low-loss shielded twin conductor cable are given in Fig. 3-4.

Most modern receivers use balanced 300 ohm input circuits with a 75 ohm center tap as shown in Fig. 3-5. Since the inductance, and hence the impedance, of a transformer varies roughly as the square of the number of turns, half a coil will have one-quarter the impedance of an entire coil. This explains why the center tap of a 300 ohm coil has an impedance of 75 ohms. It must be remembered that the d-c resistance has not been considered in this discussion since it is negligible.

The advantages of a balanced input over an unbalanced one is that any electrical noise or other signals picked up in the download will be cancelled in the primary of the transformer. In

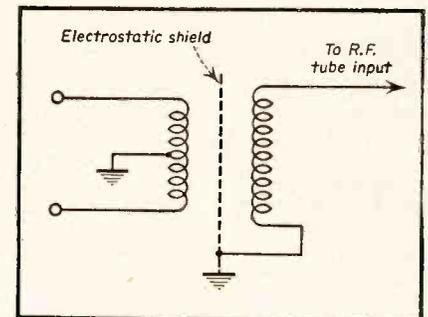


Fig. 3-6: Balanced input circuit with electrostatic shield; used in G.E. Model 820 receiver.

fact any signal striking the download causes two identical signals to pro-

[Continued on page 32]

U. H. F. TUNING ELEMENTS

by ALLAN LYTEL

Read this analysis of the behavior of condensers and resonant circuits at ultra high frequencies, and learn why certain components and circuits now employed in TV, and about to make their appearance on the market, behave as they do.

THE fundamental action of high frequency currents are quite different from those generally considered in low frequency broadcast band operation. These differences form an important basis for ultra high frequency techniques since ordinarily a coil or an inductance is composed of many turns of wire, in which the inductive reactance varies directly with frequency. A capacitance is defined as any two conductors separated by a dielectric and this no longer remains a pure capacitance for u.h.f. The paper capacitor with its rolled up construction actually has a small amount of inductance inherent in its design and construction which is ordinarily ignored for low frequency radio work. However, as the frequency is increased, the inductive effect of the capacitor construction becomes increasingly important.

The capacitor leads themselves have a small amount of inductance and taken together, the inductive effects of an ordinary capacitor become increasingly important as the frequency is increased until the capacitor becomes a self-resonant circuit. At this point, it can no longer effectively

act as a capacitance. The coil has capacitance between adjacent turns and this capacitive reactance causes the coil to act as a self-resonant circuit. Even in the present day television band, some tuned circuits use the distributed capacitance of the coil to resonate with the inductance of the coil.

As the frequency is increased, alternating current flow tends to travel on the surface of conducting materials, and this is known as the skin effect. The effective resistance of a wire is increased as the frequency is increased since the current flow is now entirely on the surface of the wire and the wire effectively has a smaller diameter per current flow. Eddy currents also contribute an undesirable additional loss at high frequencies. An eddy current is that current flow between any two points of potential difference on a given conductor caused by induction. There is no work done by these eddy currents hence they represent energy losses. An example of eddy current loss is the current flow induced in a nearby conductor in which this induced current flow represents a circuit loss. The eddy currents plus the skin effect are responsible for the increased losses of an ordinary circuit at the higher frequencies.

Taken together the effects of a capacitor and an inductor as the frequency is increased make the ordinary parallel resonant circuit unreliable for use as a tuning element. The distributed capacity (See Fig. 1) reduces the efficiency of a coil and the skin effect and eddy currents further reduce the effectiveness of a coil. Inductance present in the capacitor leads, reduces the capacitance hence the ordinary parallel resonant circuit with a fixed capacitor and inductor no longer can be used for tuning.

Another difficulty is involved with

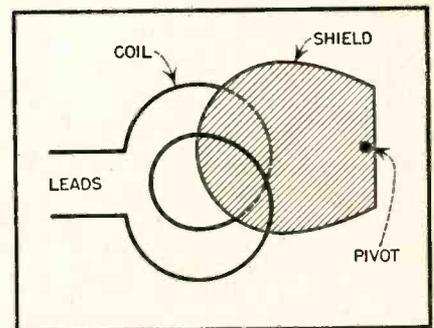


Fig. 2. Unique tuning system used at the ultra high frequencies.

the size of the elements. Less and less wire, that is fewer and fewer turns are needed for the coil to resonate at a high frequency. The capacitance necessarily, also must be very small, hence a high frequency tuning circuit would consist of perhaps half a turn of wire with a distributed capacitance existing in this half turn. Other methods than the ordinary variable capacitor are obviously needed to tune this circuit.

New Types of Tuned Circuits

A coil having a very few number of turns can be used as a self-resonant circuit as pointed out above by utilizing the distributed capacity of the coil. A unique tuning system shown in Fig. 2. uses a metallic conducting shield which effectively reduces both the inductance and capacitance of this coil and thus becomes the tuning element. The shield is rotated about the pivot point as shown and the maximum shielding effect which is minimum inductance is obtained when the shield is inserted the maximum distance in the coil. Minimum shielding and hence the greatest inductive effect

[Continued on page 31]

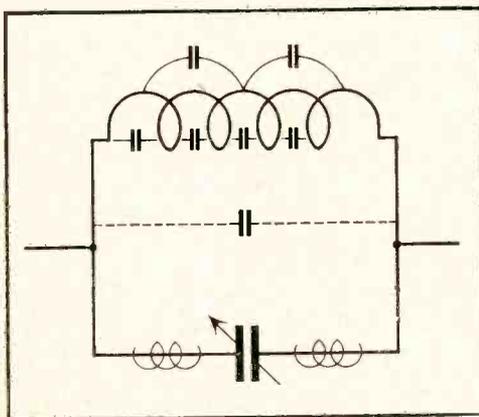


Fig. 1. Effect of distributed capacitance across a coil.

SHOP NOTES

Write up any "tricks-of-the-trade" in radio servicing that you have discovered. We pay from \$1 to \$5 for such previously unpublished "SHOP NOTES" found acceptable. Send your data to "Shop Notes Editor".

Crosley Models—10-412, 10-418, 10-404MU, 10-404M1U Increase Vertical Size

If trouble is experienced with the above models in being unable to obtain sufficient vertical height, the following changes can be made.

1. Change *R171* from a 5,600 ohm resistor to a 4,700 ohm, 10%, one watt resistor, Part No. (39374-121).

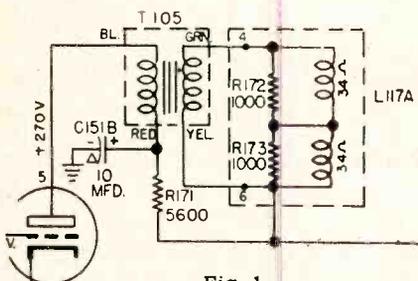


Fig. 1
Before Change

If this change does not provide enough height, the vertical height may be further increased as follows:

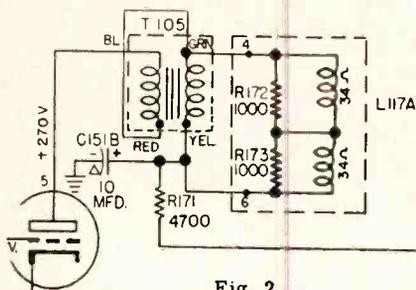


Fig. 2
After Change

2. Change *T105* to an Auto-transformer by connecting the secondary winding in series with primary, as is shown in Fig. 2.
 - a. Remove the red lead of the primary winding of *T105* at the terminal board where it is soldered beneath the chassis. There is another lead to this lug which is red with white tracer.
 - b. Move it to the adjacent lug to which two green leads (one from the transformer secondary and one from the deflection coil) are connected.

- c. Remove the yellow lead of the *T105* secondary winding and the yellow lead of the deflection yoke from the lug of the terminal board nearby where they are both soldered.
- d. Move these two leads to the lug where the red lead of *T105* was formerly connected.

Crosley Service Dept.

Philco-Models 49-1040 Etc. Changes In Rating Of B+ Protective Fuse

The value of the protective fuse in the first productions of the above models was $\frac{1}{4}$ ampere. It was found that under normal operating conditions the current surge encountered during the warm-up period may cause the fuse to melt. Therefore, its value was changed to $\frac{1}{2}$ ampere. The chassis using the $\frac{1}{2}$ -ampere fuse has " $\frac{1}{2}$ " stamped on the rear.

After extensive tests, it was found that a $\frac{3}{8}$ -ampere fuse withstands the normal current surge and also provides greater protection than the $\frac{1}{2}$ -ampere fuse. The $\frac{3}{8}$ -ampere fuse is used in all later productions of these models.

Whenever fuse replacements are made in the field, a $\frac{3}{8}$ -ampere fuse should be used regardless of the value originally in the receiver. Orders should be placed with the Accessory Division under Philco Part No. 45-2656-10.

Philco Service Dept.


Checking Flyback Transformer

Without a scope it is difficult to determine whether the high voltage flyback transformer is delivering the proper voltage to the 6BG6 and the 1B3GT. I overcame this by wiring a 1.5 volt flashlight bulb into a tube base to pins 2 and 7. Remove the 1B3GT and replace it with the flash-light bulb. The brilliance of the bulb will give a good indication as to the performance of the transformer.

Submitted by:
H. Ackerman
Brooklyn 4, N. Y.

Dial Cord Stringing Hook

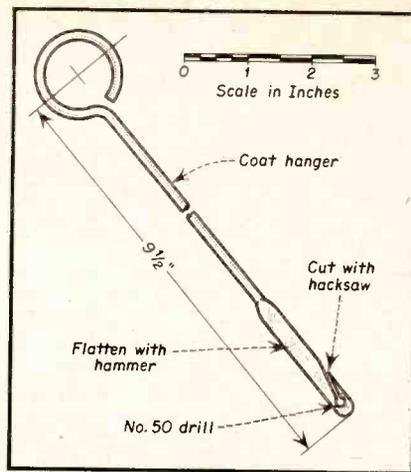This hook is very simple and inexpensive to make and requires only a few minutes of your time. You will




Dial Cord Stringing Hook

find it very handy and will save many headaches. It is made as follows: Take a piece of a coat hanger, about 10 inches long and make a loop at one end. The other end is flattened with an ordinary hammer and a hole drilled with No. 50 drill. This hook can be put to many other or special use by varying the shape and the length of it. Cut a slot with a hacksaw from the edge to the center of the hole.

Submitted by:
Donat A. Duquet
Waterville, Maine

Discarded Pen Light Carries Speaker Shims

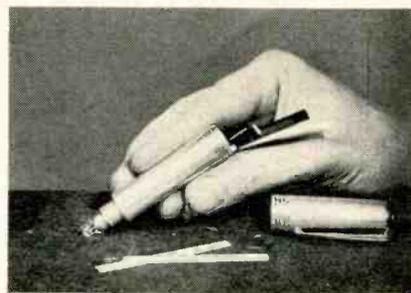A convenient method of carrying speaker centering shims is to place the shims in the battery section of a discarded pen light which has a clip for the pocket.



While the shims are mixed in the container, they are easily selected by their color.


Submitted by:
H. Leeper
Canton, Ohio

Difficult Bolt & Nut Replacement

To replace a nut on a bolt in a congested place is easy if you use a length of wire or small solder. Place the wire or solder on top of the bolt and allow the nut to slide down over the wire into place. Using a small screwdriver to start the nut will finish the job.

Submitted by:
Wayne E. Lemons
Buffalo, Mo.


CIRCUIT COURT

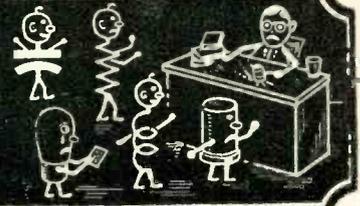


Kappler Model 102T

Almost everything about this rack-mounting, a-c operated broadcast band receiver is different from the conventional instrument. A total of six tubes, exclusive of the rectifier, are employed and it is interesting to note that only two types are employed. The layout is so interesting that a block diagram is shown. It will be noted that the mixer stage uses four crystal rectifier elements in a full wave circuit in place of a tube.

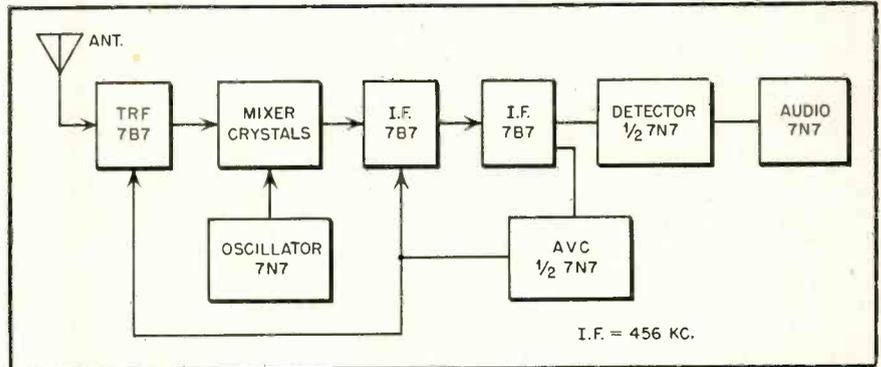Type 7B7 pentodes are used as r-f and i-f amplifiers, all the other stages employing 7N7 dual triodes. A partial schematic shows the mixer circuit and



Block diagram of Kappler Model 102T.

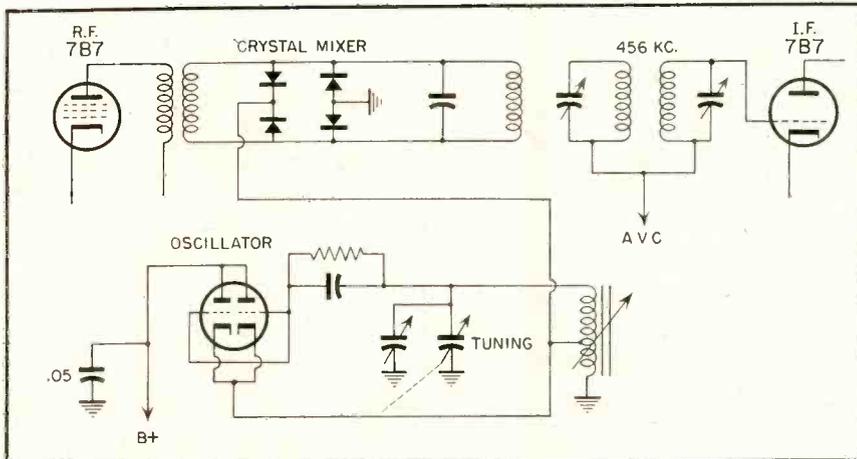

Partial schematic showing mixer circuit and coupling to first i-f stage.

coupling to the first of the two i-f stages. It is interesting to note that the i-f signal is coupled to the two tuned circuits by a low impedance link from the rectifiers. A large capacitor, .001 μ f, keeps any signal or oscillator voltage out of this circuit, permitting the 466 kc i-f to pass.

The oscillator circuit, using the two sets of triode elements in the 7N7 tube in parallel, uses a Hartley circuit with the plate at ground potential for r-f. Voltage is fed to the mixer stage from the cathode tap. A feature of the coupling to the mixer is that the point is balanced to ground and thus will not tend to pass oscillator voltage to the stage ahead or following. A frequent source of birdies is thus eliminated.


The i-f stages are overcoupled to provide exceptional bandpass with good gain and reasonable selectivity.

The second detector is of the so-called infinite impedance variety. Rectifica-

tion takes place between the grid and cathode and the output appears on the cathode. Amplification takes place as audio frequency in another 7N7 with parallel frequency sections, and as shown is connected as a cathode follower. Note the similarity of the detector and amplifier stages. These circuits are shown to the left and below in the partial schematics.

The output of this instrument is at transformer is parallel fed and has two paths, selected by a switch. One path feeds the transformer directly. The other connects a 10 kc filter in the primary circuit to eliminate cross-talk and heterodyne. The filter has both series and parallel sections.

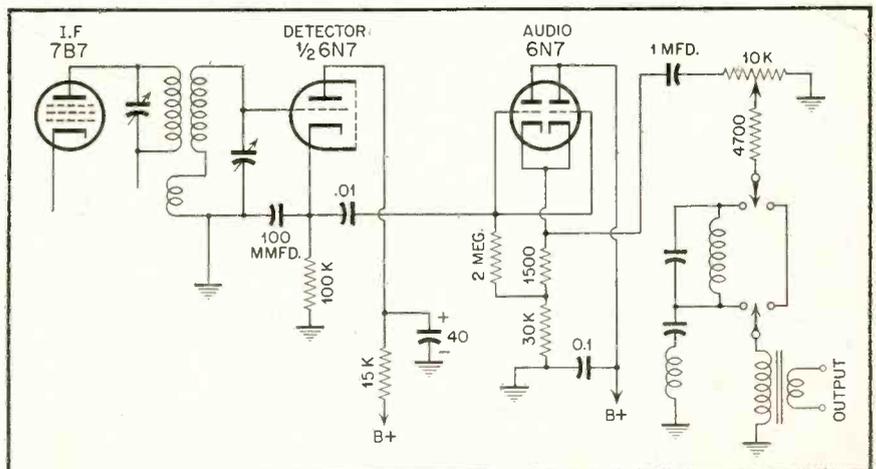The output of this instrument is at a low level and is designed to feed a low impedance amplifier for subsequent gain and power.



Partial schematic of detector and output circuits.

NEW PRODUCTS

NEW DU MONT TYPE 12LP4A

Allen B. Du Mont Laboratories, Inc., Tube Division, announces a new Telatron, the Type 12LP4A, in production at its Allwood, New



Jersey, plant. This new picture tube will provide leading manufacturers of initial equipment, for the first time, with a Type 12LP4 tube employing the Du Mont bent-gun ion-trap design, and featuring the new gray filter face plate.

The elimination of ion blemishes by use of the Du Mont bent-gun results in sharper spot resolution. Modification of the bent-gun design in the Type 12LP4A, permitting the use of either a single or double magnet beam-bender insures direct interchangeability with all Type 12LP4 tubes.

LOW NOISE PENTODE

Tube Department, Radio Corporation of America, Harrison, N. J. announces the new tube 5879 is a sharp-cutoff pentode of the 9-pin miniature type intended for use as an audio amplifier in applications requiring reduced audio noise.



Utilizing a single-ended structure which is relatively short and rigidly mounted to minimize microphonics, a controlled getter deposit to minimize internal leakage, and a double-helical-coil heater to minimize hum—all features contributing to reduced audio noise—the 5879 is especially recommended for service in the input stages of medium-gain public-address systems, home sound recorders, and general-purpose audio amplifiers.

NEW HYTRON TUBES


The Hytron 1X2A is a miniature filamentary-type rectifier (having higher ratings than the 1X2) designed for use in television sets as

high-voltage rectifier supplying power to the anode of the cathode-ray tube. It is designed and rated primarily for use in fly-back type of power supplies. In new equipment applications the 1X2A when used within its maximum ratings, is a replacement for type 1B3CT/8016 at d-c output potentials as high as 14 to 15 kilovolts.

Also announced is the new Hytron type 12BH7 a double triode, having semi-high permeance units. It is intended for use in television receivers and other applications where the use of two similar triode sections in a single envelope is desirable from the viewpoint of space saving and lower cost.

ALL-CHANNEL ANTENNA

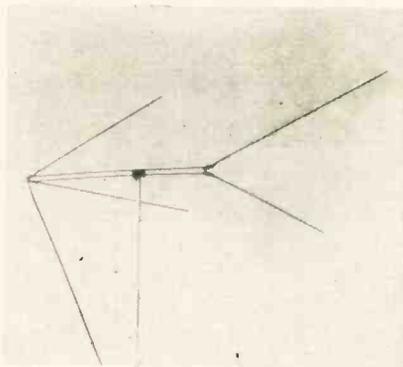The Workshop Associates, Inc. announces a new all-channel television antenna—the DUBL-VEE. Utilizing a principle new to television,




the DUBL-VEE features extremely high gain with a streamlined, rugged, easy-to-assemble construction.

Workshop has acquired a new factory to manufacture DUBL-VEE antennas where production is already in progress. First shipments were made to distributors in mid April and have continued regularly to date.

Free literature may be obtained by writing directly to Sales Department, the Workshop Associates, Inc., 135 Crescent Road, Needham Heights 94, Massachusetts.

NEW FUSE HOLDER

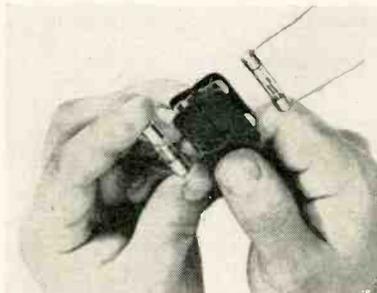Littelfuse Corporation of Chicago has perfected a new fuse holder which snaps onto inates the time wasting and costly servicing the blown pigtail within the set. This eliminates the problem which is the usual difficulty when replacing soldered-in pigtail fuses.



Called the "Snap-On TV Fuse Holder", this fibre attachment takes only 15 seconds for installation. The fuse holder and the pigtail be-

come permanent attachments within the set. Each time a new fuse is needed, it can be slipped into the holder. With this revolutionary improvement for servicing—soldering, cutting and the blowing of fuses with a hot iron become trials of the past.

CONCENTRIC CONTROL

ASSORTMENT

To meet Service Technicians' increasing need for replacement concentric dual controls, IRC has announced a new Concentrikit Stock Assortment. This assortment, an extension of IRC's revolutionary Concentrikit, contains 94 parts. With it the majority of concentric dual controls can be speedily assembled.




This stock assortment of standard IRC parts is supplied in a handsome all-metal cabinet. Cabinet has four drawers and individual compartments marked for efficient stocking. For an attractive and convenient shop arrangement, cabinets may be stacked with IRC Resist-O-Cabinets. Concentrikit Stock Assortments are available at all IRC Distributors, or write for Catalog DC2S: International Resistance, 401 N. Broad St., Phila. 8, Pa.

RECTANGULAR TUBES

Two new 16" and 14" rectangular tubes have been announced by National Union Radio Corporation of Orange, New Jersey.

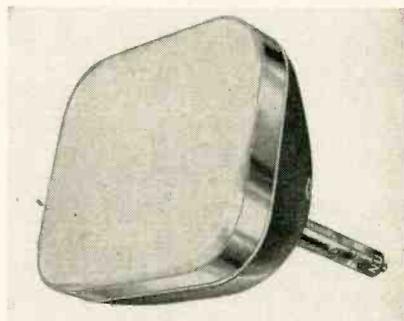The N. U. 16KP4 is a 65° direct-viewing picture tube providing a 10 1/8" x 13 1/2" rectangular picture having the standard 3 x 4 aspect ratio. It features a face plate having an integral neutral gray filter which increases the contrast ratio when viewing under ambient light conditions. The N. U. 16KP4 utilizes the



new tilted-beam type gun to obtain improved picture detail. It requires only a single-field ion trap. The N. U. 16KP4 is identical to the now-popular N. U. 16TP4 except for an increase in neck length to 7 1/2" which permits adaptability to a greater range of focus coil and deflection yoke designs.

The N. U. 16KP4, in addition, makes a suitable replacement for type 16PR4 in most applications.

The N. U. 14CP4 is a 65° direct-viewing picture tube providing an 8 3/8" x 11 1/2" rectangular picture. In other respects it is similar

to the 16KP4 described above, having the 7½" neck length for greater flexibility with respect to focus coil and deflection yoke designs.

NEW BLUE-CONE SPEAKER

A brand-new, dark-blue cone for which ideal response is claimed, now identifies the Permo-flux 8T8-1 "ROYAL EIGHT" 8" speaker. Manufacturer says that when this speaker is properly baffled, it compares with any 12"




speaker on the market. Literature is available showing how to baffle the "ROYAL EIGHT" in a cabinet occupying ½ the space and costing about ½ as much as equally effective baffling for a 12" speaker. Write the manufacturer: Permo-flux Corporation, 4900 W. Grand Ave., Chicago 39, Ill.

TUBE TESTER

A new laboratory type instrument built to test all the latest sub-miniature tubes, including television, with professional accuracy.

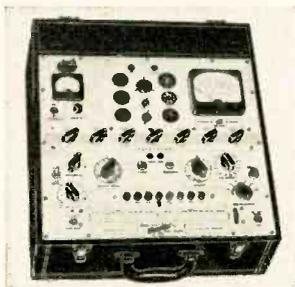Known as the Model 539, this tube tester is designed for maximum accuracy throughout. Scale reads directly in microhms. Has a separate meter to permit accurate adjustment of line voltage while tube is under test. Pro-



vision is made for inserting plate milliammeter to read plate current of the tube under test.

Built into strong, portable carrying case with leatherette covering. 17" x 18" x 18½"; 31 lbs.; 110-130 VAC.

Available at Hickok jobbers, or for additional information, write today to H. D. Johnson, The Hickok Electrical Instrument Company, 10533 Dupont Avenue, Cleveland 8, Ohio.



SLAVE PROJECTION UNIT

Joe Snaider, President of Snaider Television Corp. announced that his firm is now ready to


deliver a new projection slave receiver that is entirely new in the industry.

This new product, the result of many months of development, is remarkable in that it may be attached to any type of TV receiver on the market, regardless of the size of the CR tube and it will deliver a bright, clear projected picture up to 6 feet by 8 feet. It uses only the video signal and sound of the master set having its own, self-contained power supply.

This new unit is now being demonstrated at the factory at 540 Bushwick Avenue, Brooklyn, and is in production to fill the many advance orders on hand.

CONICAL ANTENNAS

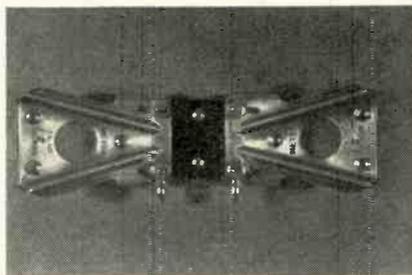Telrex, Inc., Asbury Park, N. J., manufacturers of the "Conical-V-Beam" has just in-




roduced its new "Metro" series, an economy line of "Conical-V-Beams" which supercedes the former "Special" series.

Designed to incorporate many of the exclusive features of their DeLuxe line, the "Metro" includes full 3-inch element clamping channels, reverse flanging of the "butterfly clamp" for greater rigidity and freedom from vibration, and other important electrical and mechanical improvements. The "Metro" features solid dural elements.

UNIQUE ARRESTER IDEA

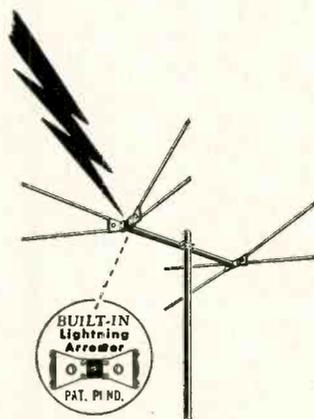
JFD Mfg. Co., B'klyn, N. Y. announced that its television antenna engineers have perfected a Lightning Arrester that is molded directly



in the dipole bakelite insulator of the "D-Xer" Conical antennas Nos. TA160, TA161 and TA162. Further information and literature is available from the manufacturer, its representatives and distributors.

JACK-UP TOWER & ROTATOR

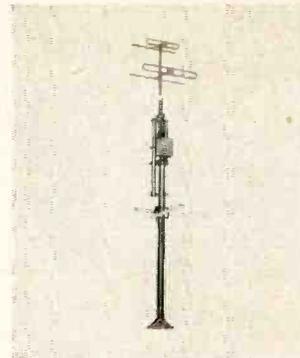Shown below is the Crown Antenna Rotator mounted on a "Camburn Jack-Up T.V. tower". The Camburn Sales and Manufacturing Company of Battle Creek, Michigan and Crown Controls Company, New Bremen, Ohio, work together in developing a mounting arrangement so that the Crown Antenna Rotator and the Jack-Up tower can be used together.



The Jack-Up tower has a variable height of 20' 8" to 47' and in this way the rotator is easily accessible. Further information on either product can be obtained from Crown Controls Company, New Bremen, Ohio.

ORE DETECTOR KIT

Allied Radio Corporation 833 W. Jackson Blvd. Chicago 7, Ill., announces the KNIGHT "Scout"—a new, low-priced, portable, radioactive ore detector in easy-to-build kit form. A great deal of interest in such units has been aroused by the big rewards offered by the Government for the finding of radioactive mineral deposits. An 8-page instruction manual contains step-by-step pictorial diagrams keyed to the instructions, plus a schematic diagram.

Compact and lightweight (only 2¼ pounds), the "Scout" is very easy to use. Operator merely carries it at his side; when a radio-



active source such as uranium is approached, the clicking sound in the headphones increases in frequency.


ANTENNA ROTATOR

The U. S. Devices Corp., of Oak Tree, South Plainfield, New Jersey, announces its entry into the antenna rotator field with the introduction of its new Antenna Rotator.

The new U. S. Devices Antenna Rotator has been fully tested by the largest independent testing laboratory in the world. From their very severe tests, it was definitely established that the new rotator is capable of rotating any antenna or stacked array of antennas manufactured. It is also sufficiently strong to rotate all "ham" equipment.

Full information may be obtained by writing direct to the manufacturer, U. S. Devices

NEW WORKSHOP

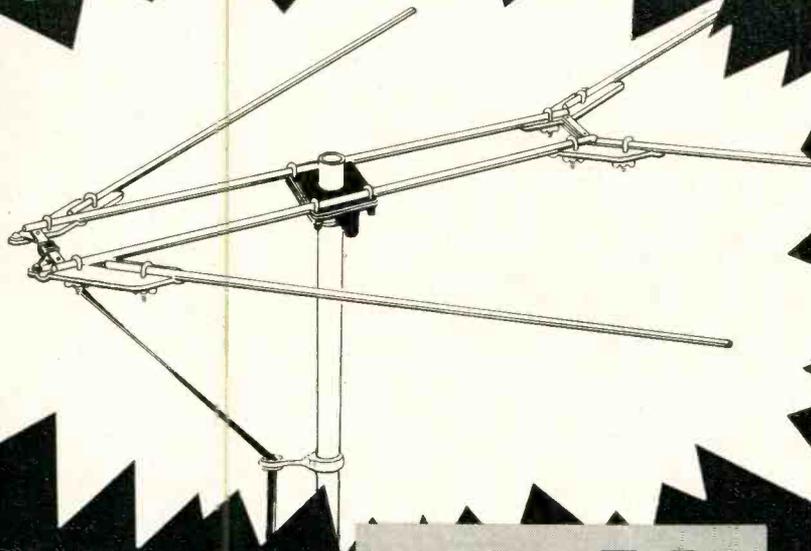

PATENT
PENDING

DUBL-VEE

TV ANTENNA

Outstanding ALL-CHANNEL Performance

THE "end-fire" DUBL-VEE sets a new standard in TV antenna performance. Higher gain, sharper directivity, and closer match assure superlative reception — clearer, steadier, sharper pictures. In fact, a single DUBL-VEE actually outperforms double-stacked models of most other types. Rugged — easy to assemble — economically priced. Your best buy at any price.

Clearer Pictures—higher gain brings in stronger signal — especially on higher channels

Clearer Pictures — narrow beam cuts down multi-path ghosts

Clearer Pictures—better impedance match on all channels maintains high signal strength

Clearer Pictures — true horizontal polarization—no out-of-phase ghosts

Clearer Pictures—no parasitic elements — all driven

Clearer Pictures—designed by the pioneers in the antenna industry

MODEL VV

Write for Bulletin ☐


THE WORKSHOP
ASSOCIATES, Inc.

135 CRESCENT ROAD,
NEEDHAM 94, MASS.

\$10.95 LIST

Model 2VV Double-Stack \$21.90 List

Specialists in High Frequency Antennas

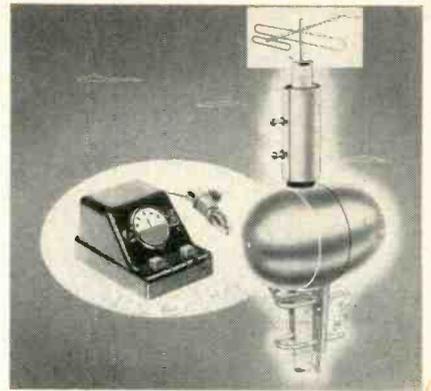

Corp., Antenna Rotator Division, Hillside Ave., Oak Tree, South Plainfield, New Jersey.

7-INCH SCOPE

A new high-gain, wide-band cathode ray oscilloscope designed particularly for television circuit, has been announced by the Radio Tube Division of Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y., according to C. W. Shaw, general sales manager.



The new type 400 oscilloscope, which is supplied with 7-inch Type 7JP1 green screen cathode ray tube, provides a vertical sensitivity of ten millivolts per inch and a vertical response which is useful up to four megacycles.

NEW CRYSTAL-CONTROLLED TV GENERATOR

The Dual Mega-Marker Sr., manufactured by Kay Electric Co., Pine Brook, N. J., is a crystal controlled generator of sound and picture RF carriers for use as markers in TV tuner and receiver work. Tone modulation on the sound carrier may be switched on or off. The sound carrier may also be switched on or off. A 4.5 mc crystal controlled signal is available at a separate output connector. At-



tenuators are provided for all out-put signals. This instrument may be used for marking picture carrier positions on TV RF curves,

for providing signal at 4.5 mc for intercarrier work, and for aligning the local oscillator of TV receivers.

TV TOWER

A new All-Aluminum home antenna tower is now in production by Thompson & Ruby, Inc., of Brownstown, Indiana.

Numerous desirable features are incorporated in this new product. Riveted tower sections are shipped completely cartoned, ready for the installer to easily join together.



Full information is available from the Company in Brownstown, Indiana.

MAGNETIC TAPE RECORDER

Allied Radio Corporation of Chicago announces the release of a new low-priced Magnetic Tape Recorder. Extremely light and compact, the new Knight Tape Recorder incorporates the latest engineering features for ease of operation—simplified tape threading which eliminates fumbling, and only one control for tape transport mechanism (with three positions: Record-Play, Off, Rewind). This unit records for a full hour on a 1200-ft. reel of tape with 30 minutes for each half of tape width. Recording speed is $7\frac{1}{2}$ " per second, rewind speed is 20 times as fast—another outstanding feature of this unit. Other features include a special speaker switch that permits muting speaker when recording from microphone and a constant speed capstan drive. Proper recording level at all times is assured by the neon bulb level indicator.

FIELD FINDINGS


[from page 8]

will report full details in our next issue provided such information qualifies for publication.

Philadelphia's 2nd

The Philadelphia Radio Service Men's Assn. will hold its second annual radio-TV service convention at the Broadwood Hotel Sept. 25-27, 1950. The technical lectures on the program last year were so fine that attendance passed the 4,000 mark; and even greater results are anticipated for the coming clinic. Outstanding au-

You're Right 3-Ways With BURGESS

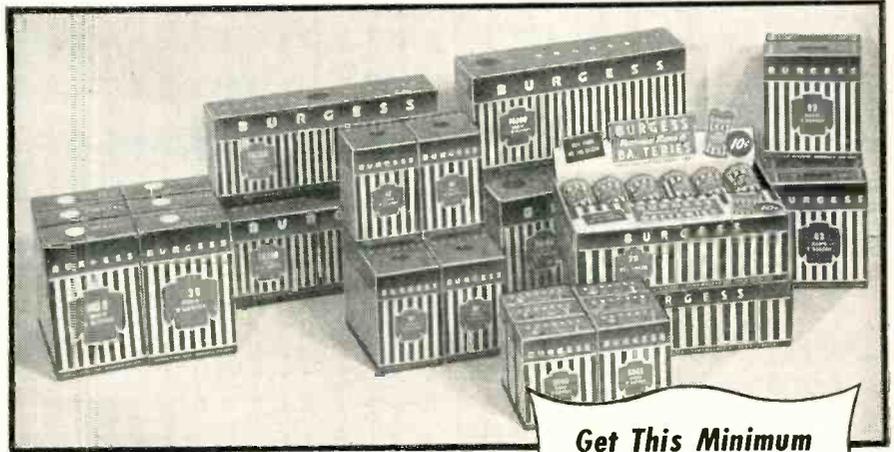

1st The RIGHT Line!

BURGESS is America's Best-Known Line of radio batteries. America's best-sellers, too! Cash in with sales on the tradition of quality that has made Burgess Batteries famous throughout the world. And remember BURGESS is the complete dry battery line—the line that helps you sell all portable radio battery customers!

2nd The RIGHT Promotion

FREE SALES-BUILDING KIT—Includes a sturdy floor display merchandiser that puts your minimum stock battery assortment out front where they sell themselves; a big, bold 9"x22" window streamer; a lively new counter-window card; new enclosures; ready-to-run ad mats; dummy display cartons; and the big, new 1950 Burgess Replacement Guide that answers all your replacement questions.

3rd The RIGHT Advertising

BURGESS is advertised in leading national magazines with a heavy concentration of male readers—your best battery customers. Eye-catching, colorful advertising all during the portable radio season will pre-sell millions of portable radio battery users—will pre-sell your customers on Burgess quality and long life.

Get This Minimum
Stock Assortment
that Serves Over

63%

of All

Portable Radios

6 No. XX45 67½ v. "B"

6 No. M30 45 v. "B"

6 No. G3 4½ v. "A"

6 No. 4F 1½ v. "A"

48 No. 2R 1½ v. "A"

3 No. F6A60 7½,

9 and 90 v. "A&B"

3 No. T6Z60 7½,

9 and 90 v. "A&B"

Ask Your
Distributor

about this
Burgess Portable
Battery Promotion and how
to get your FREE Sales-
Builder Kit of Promotional
Material.

BURGESS BATTERIES

America's Best-Known Line of Portable Radio Batteries


Here's *telrex* quality AT LOW COST— "THE **METRO**" CONICAL-V-BEAM*

This Antenna structure is built to give years of trouble-free service.

- No Fragile Castings
- No Plastic Moldings
- No Paper-thin Fittings

The "METRO" has that famous TELREX-QUALITY construction throughout.

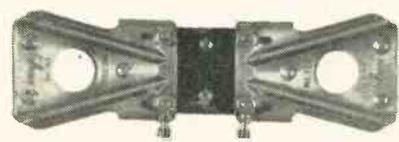NOW! EVERYONE CAN AFFORD TELREX PERFORMANCE & QUALITY!



The new "METRO" Element Clamp is second to none in mechanical and electrical structure.


- 1** Rugged, heavy gauge "Butterfly" of corrosion resistant, aluminum alloy.
- 2** Universal Clamp holds either solid or tubular elements.
- 3** Full 3 inch element clamping channel for permanent contact.
- 4** Laminated, high impact, low absorption, phenolic insulator for minimum loss and maximum strength.
- 5** Rust-proof, seamless aluminum crossarms for strength and light weight.
- 6** Maximum Sales and Profits — Abundant Sales Aids and Literature — Compelling National Advertising — Technical Assistance.

Uni-Directional Conical "V" Beam with Reflector.

Channels 2-13 plus FM.

Ideal for Distances up to 50 Miles.

Full Audio and Video Band Pass.

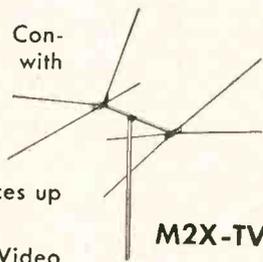

M2X-TV


★ ★

Uni-Directional Conical "V" Beam with Reflectors.

Channels 2-13 plus FM.

Hi-Gain 2 Bay for Distances up to 100 Miles.

Full Audio and Video Band Pass.

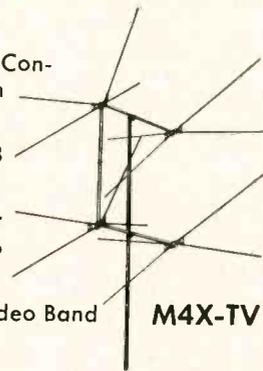

M4X-TV

Be sure it's a "CONICAL-V-BEAM"
—Look for the TELREX* Trademark

Patents Pending
Copyright 1950

telrex INC.
CONICAL-V-BEAMS*

* REGISTERED TRADEMARK

AMERICA'S
STANDARD OF
COMPARISON

ASBURY PARK 5, N. J.

FIELD FINDINGS

[from page 27]

thorities on many phases of radio and television servicing problems are scheduled to deliver lectures, none of which will exceed one hour. The moderator this year, as last, will be yours truly. More about this really worthwhile technical convention will be published in a forthcoming issue, especially when a complete listing of lecture titles and speakers is available. Other service associations would do well to have delegates attend the Philadelphia shindig to learn how to plan and carry on such conventions of their own, for it is our considered opinion that no technician situated within reasonable travel limits from such a technical clinic can afford to miss a single lecture on the program.

[Continued on page 36]

TRADE FLASHES

[from page 10]

By referring to the pictorial "TeleClues", the serviceman can identify the circuit and in many cases the component which is defective. For instance, one photograph may show the type of picture produced on the TV screen which results from a short in the deflection yoke, or another picture, which shows white trailing reflections, indicates phase shift and poor low-frequency response due to a particular resistor having changed value.

Thus the serviceman can "pin down" the source of his trouble and make the necessary repairs without testing or experimenting with each circuit.

Centralab Introduces New Line

Centralab unveiled for Distributors at the Chicago May Parts Show a new and greatly increased line, including new "Blue Shaft" Volume Controls, a new plan for handling TV control replacements with "exact duplicate" controls, an expanded line of ceramic capacitors, printed Electronic Circuits introduced to the Distributor trade, and various control, switch and capacitor kits offered as merchandising features.

A new television and radio service catalog, No. 27, had its first distribution at the Show.

Hytron Announces New Reference Guide


The new 4th Edition Hytron Reference Guide for Miniature Electron Tubes is just off the Press. Original—unique—lists all miniature tubes to date, regardless of make. 132 minia-

Subscribe to "RSD" -

Form A Group,

Service Dealers

SAVE Up to \$1.00 each.

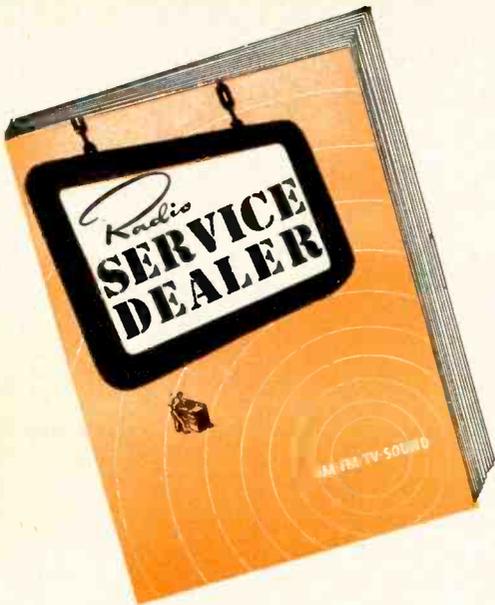

"The Professional Radioman's Magazine"—published monthly. All articles are exclusive and timely. Practically every issue is worth what an entire 1 year subscription costs.

★ The more in a group the bigger the savings. 6 men in a group save \$1.00 each; 4 men groups save \$.75 per man. Present "RSD" subscribers may participate in or form a group with co-workers, or even competitors. Still active subscriptions are automatically extended 1 year. Start a Group today! The timely and exclusive technical data appearing in future issues of "RSD" will make this the best investment you ever made. The special Group Rate offer may be withdrawn at any time—so hurry.

Use This Coupon For Convenience

(The coupon below can be used for from 1 to 6 subscription orders. Use it today!)



TEAR OUT—MAIL TODAY!

RADIO SERVICE-DEALER MAGAZINE 342 Madison Ave., New York 17, N. Y.		In U.S.A. & Canada	Foreign Rates
<input type="checkbox"/> One 1-year subscription		\$2.00	\$3.00
<input type="checkbox"/> Two 1-year subscriptions, each		1.75	2.75
<input type="checkbox"/> Three 1-year subscriptions, "		1.50	2.50
<input type="checkbox"/> Four 1-year subscriptions, "		1.25	2.25
<input type="checkbox"/> Five 1-year subscriptions, "		1.10	2.00
<input type="checkbox"/> Six 1-year subscriptions, "		1.00	1.50

Please enter 1 year subscription orders for the names given below. Our remittance is enclosed.


NOTE: If you do not wish to tear this order blank out, just print or type the information on a single sheet of paper, following the style given. Each subscriber's occupation must be clearly described.

Name..... Address..... Describe Title or Position and Type of Business..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Name..... Address..... Describe Title or Position and Type of Business..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>
Name..... Address..... Describe Title or Position and Type of Business..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Name..... Address..... Describe Title or Position and Type of Business..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>
Name..... Address..... Describe Title or Position and Type of Business..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>	Name..... Address..... Describe Title or Position and Type of Business..... State whether a New Subscriber <input type="checkbox"/> or Renewal Order <input type="checkbox"/>


Eliminates Messy Soldering Jobs!

**LYNN Lightning
SOLDERLESS WIRE
TERMINAL
REPAIR KIT**

NO. 2090
SERVICE KIT

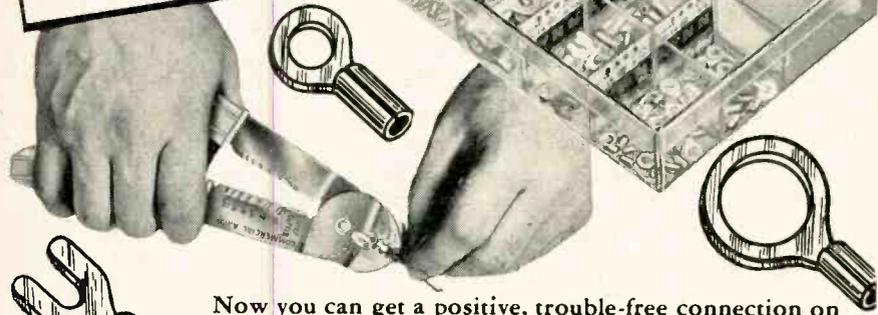

Now you can get a positive, trouble-free connection on every terminal... as fast as you can close your hand. No messy soldering or waiting for an iron to heat! With a Lynn *Lightning* service kit you just strip primary wire from 10 to 22 gauge with handy, combination stripping and crimping tool... select the proper terminal... then *crimp* it on. Every job quick, clean, professional-looking! Kit comes complete with crimping tool, 10 different types of terminals plus insulation tubing in 11-bin, clear plastic box. Only... **\$7.95**

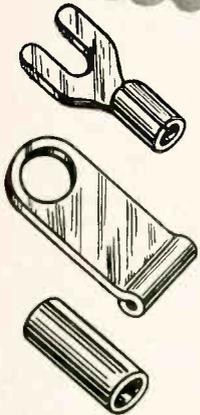


Two New Television Screw Drivers

Reach hard-to-get-at spots with the new Vaco AT 510 non-metallic, fiber shank driver for critical tuning and aligning work... the 10" blade gives you all the length you need. Adjust the new type focalizers with specially designed Vaco Beryllium-copper drivers... non-magnetic, yet nearly as hard as steel for adequate torque without interference with the Ion trap field. Full information on other aligning tools, nut setters and special radio tool kits on request. Write for FREE catalog.



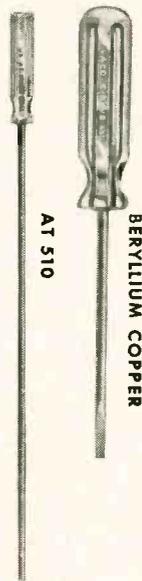317 E. Ontario St., Chicago 11, Ill.
In Canada: Vaco-Lynn Products Co., Ltd.
1212 Notre Dame St., W., Montreal 3, Que.



tures—41 new tubes. 70 Basing diagrams. Lists similar larger prototypes. This new 4th Edition may be had from the Hytron jobber; or write Hytron Radio & Electronics Corp., Salem, Mass. They are free for the asking.

Mrs. Jacob Mucher Passes On

The wife of Jacob Mucher, one of the founders and original owners of Clarostat Mfg. Co., Inc., passed away on May 17th at their Brooklyn, N. Y. home. She had been in poor health for some time past.

Mrs. Mucher was the mother of Vic, George and Bill Mucher of the Clarostat organization. Also the mother of Mrs. Fran Chamberlain, wife of Clarostat's jobber sales manager, and of another daughter.

Ulrich Joins National Union

Appointment of Vinton K. Ulrich as Manager of the Renewal Tubes Sales Division has been announced by Kenneth C. Meinken, President, National Union Radio Corporation of Orange, New Jersey.



Vin Ulrich is one of the few radio sales managers who is a qualified applications engineer. Plans for National Union's active promotion of renewal tubes to be announced shortly, include both radio and television receiving tubes as well as "Videotron" television picture tubes.

New Catalog


Walker-Jimieson, Inc. Chicago distributors, has announced release of its new 1950 television, radio, and electronics parts catalog, specially planned and designed for quick and easy use by Service Dealers.

Catalog will be sent free to those entitled to buy at wholesale prices. Write for Catalog No. 170, Walker-Jimieson, Inc., 311 S. Western Ave., Chicago 12, Ill.

New 1949 Electronic Index

John F. Rider, president of the Electronics Research Publishing Co., Inc., 480 Canal Street, New York 13, N. Y., announces that the Electronic Engineering Master Index for 1949 will be available in June.

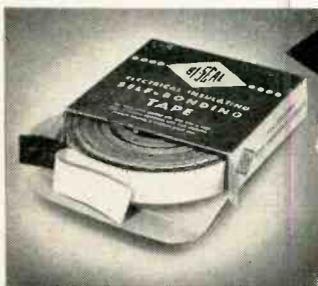SOLVE SERVICING INSTALLATION PROBLEMS WITH



SELF BONDING TAPE

for insulating and hermetic sealing

Radio • Television • UHF Components • Installations

- Fuses to solid mass
- For sealing moisture-proof ant. connections
- For taping ion trap magnets to CRT
- For splicing twin line and all co-ax AT & K cables
- For master antenna box connections
- Multiple and varied other applications

BISHOP MANUFACTURING CORP.

Established 1847

254 WEST 31st STREET NEW YORK 1, N. Y.

Available at your local jobber, or write

Designed to save
Servicemen
Time & Money

U. H. V. TUNING

[from page 21]

and lowest frequency, is obtained when the shield is rotated so that it is not inserted in the turns of the coil. The shield effectively reduces the inductance of the coil since it prevents the magnetic field from one turn from interacting with a magnetic field in another turn. The shield may be thought of as a metal chassis dividing the coil into two parts and such a coil would obviously have less inductance than if both parts of the coil were mounted on the same form so that they had a mutual inductance. Tuning by means of a shield is actually used in u.h.f. tuned circuits and it serves as an introduction to other types of tuned circuits.

The Butterfly Tuner

An extension of the idea that a shield reduces the magnetic effect in a coil and can be used for tuning evolves into the tuned circuit known

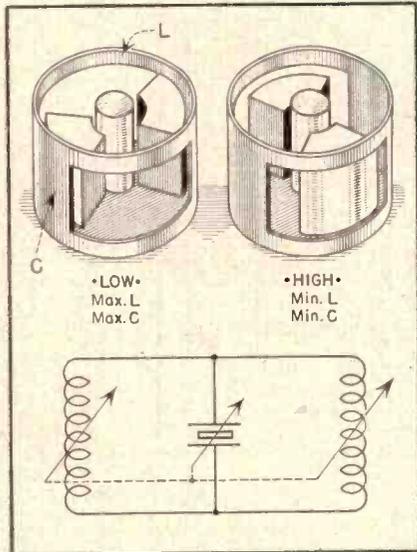


Fig. 3. Butterfly Tuner and its equivalent circuit.

as the "butterfly". This circuit actually contains inductance and capacitance which are integral parts of the mechanical arrangement which comprises the circuit. As shown in Figure 3, a butterfly consists of an outer cylinder and an inner rotor. This outer cylinder has two large rectangular holes cut from its surface. Because of this, the cylinder effectively acts as both an inductance and a capacitance as may be seen from the figure. Capacitance is obtained between the plates of the outer cylinder and the inner rotor. Inductance is obtained from the strips of metal which connect the capacitor plates. An equivalent circuit for the butterfly is shown in the figure

Anyone Can build a HEATHKIT

Heathkit SIGNAL TRACER KIT
\$19.50

Heathkit VACUUM TUBE VOLTMETER KIT
\$24.50

Heathkit TUBE CHECKER KIT
\$29.50

Heathkit BATTERY ELIMINATOR KIT
\$22.50

Heathkits are beautiful factory engineered quality service instruments supplied un assembled. The builder not only saves the assembly labor cost but learns a great deal about the construction and features of the instrument. This knowledge aids materially in the use and maintenance of the equipment. Heathkits are ideal for and used by leading universities and schools throughout the United States. Each kit is complete with cabinet, 110V 60 cycle transformer (except Handitester), all tubes, coils assembled and calibrated, panel already assembled and punched, formed and plated, every part supplied. Each kit is provided with detailed instruction manual for assembly and use. Heathkits provide the perfect solution to the problem of affording complete service equipment on a limited budget. The basic three instruments — an Oscilloscope, Vacuum Tube Voltmeter, and Signal Generator can be purchased in Heathkits for \$83.50, about the cost of a factory-built VTVM alone. Write for complete catalog.

Heathkit CONDENSER CHECKER KIT
\$19.50

Heathkit AUDIO GEN. KIT . . . \$34.50

Heathkit ELECTRONIC SWITCH KIT
\$34.50

Heathkit IMPEDANCE BRIDGE KIT
\$69.50

Heathkit 5" OSCILLOSCOPE KIT
\$39.50

Heathkit TELEVISION GEN. KIT . . . \$39.50

HEATH COMPANY
BENTON HARBOR 12,
MICHIGAN

EXPORT DEPT., 13 E. 40th ST., NEW YORK 16, N.Y. • CABLE ARLAB - N.Y.

as a parallel resonant circuit. Both the inductances and the capacitance are made variable by turning the rotor.

In the position of highest resonant frequency, the rotor is turned for the position of minimum capacity and

minimum inductance. A small value of capacity is obtained since there is the greatest possible separation between the rotor and the stator. At the same time, this position represents minimum inductance because the


rotor is effectively shielding the inductance. As we have seen, a shield placed in or near a coil reduces its inductance hence the rotor in this position acts as a shield.

The lowest resonant frequency is obtained when the rotor is in the opposite position. Here there is a maximum capacity since the rotor and stator are in the completely meshed position. There is also maximum inductance at the same time there is maximum capacity which results in the lower resonant frequency. Maximum inductance is obtained since there is a minimum shielding effect on the inductor by the rotor in this position.

Some types of butterfly circuits consist of several layers, that is, the rotor has a number of plates and the stator has a number of plates and this type of butterfly circuit which is stacked rather resembles a variable capacitor in which the stator plates are connected to a one-turn coil. Tuning is accomplished in the same manner by changing both the inductance and capacitance simultaneously. Various shapes of rotors and stators may be used to obtain different types of angular rotation. For a particular frequency band, a special type of rotor or stator shape is chosen to cover the band with a reasonably good degree of tracking.

This new book will help to SELL MORE TV SETS

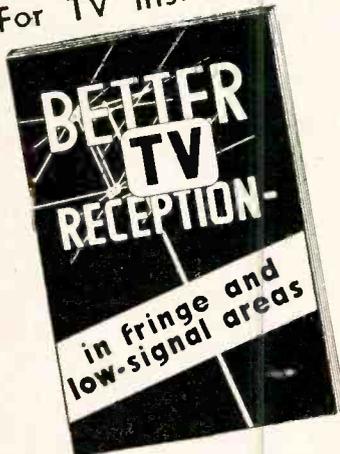For TV Installation Engineers • TV Experimenters
and TV Reception Enthusiasts



"BETTER TV RECEPTION in fringe and low-signal areas"

By W. W. SMITH, author of the "ANTENNA MANUAL" and R. L. Dawley, editor of the "RADIO HANDBOOK"

- Emphasis on concise, clear how-to-do-it information.
- Many tried-and-proved practical suggestions to improve that poor picture when standard set-ups fail.
- The only book of its kind, with much new information and a compilation of all the most useful data from many sources.

Practical, how-it-works data on TV signal propagation into the fringe areas. Evaluation of all common TV antennas in terms of their performance under low-signal conditions. Selecting the best transmission line. Making a rapid TV survey of an area, locating the "hot" radials and areas of high signal caused by focusing. Eliminating ghosts in difficult installations. Practical methods of minimizing fading.

Selection of boosters and receivers; practical suggestions for improving receiver performance in fringe areas. Full information on rhombics of all practical sizes. Using open-wire line when the antenna must be at a distance from the receiver.

Full treatment of masts and towers including data on installation and guying. Keeping the antenna from coming down in a high wind. One complete chapter on reducing TV interference.

\$2.50

AT YOUR FAVORITE DEALER—On mail orders from us, \$2.60 postpaid. Add sales tax in California.

Editors and Engineers 1317 KENWOOD ROAD Santa Barbara CALIFORNIA

Insure BETTER Television Service to Your Customers! . . . Exclusively Designed



HIGH VOLTAGE AND ELECTROLYTIC TUBULAR TELEVISION CAPACITORS

Especially Engineered for Television Circuits by INDUSTRIAL CONDENSER CORP.


The economical quality line for replacement. Industrial Condenser Corp., manufacturers of Capacitors exclusively brings you highest quality for the particular requirements of Television at exceptionally attractive prices! Special Capacitors are Pyroteen Impregnated for low power factor, high insulation resistance, high operating temperatures. Oil, Pyroteen, Wax and Electrolytic Capacitors. Finest materials throughout.

Ask Your Jobber for our Attractive Prices Today!

Or write for Bulletin 1095. Industrial makes quality Capacitors for Television, Radio, every electronic and industrial application—all types.

Send for Complete Catalog

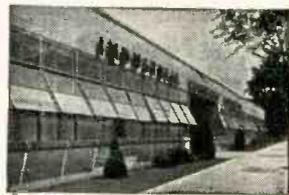INDUSTRIAL CONDENSER CORP.
3243 N. CALIFORNIA AVENUE CHICAGO 18, ILLINOIS
Sales offices in all principal cities.



Modern plant built by Industrial Condenser Corp., for manufacture of Capacitors only.

FRONT ENDS

[from page 20]

ceed down both conductors almost instantaneously. Since both signals entering each end of the antenna transformer primary are in phase they cancel each other in the coil. This does not happen to the antenna signal because the signals in both conductors of the downlead are 180° out of phase with each other.

Noise pickup in a balanced transformer may enter the secondary by virtue of the capacitive coupling between primary and secondary before the signal is cancelled in the primary. This condition may be minimized by employing an electrostatic shield between both windings as shown in Fig. 3-6.

Another type of antenna transformer, called an "Elevator Transformer", is illustrated in the partial schematic shown in Fig. 3-7 where a pair of transformers are shown as used in the RCA 206E3 printed-circuits tuner. These transformers are primarily designed to match the tuner to a balanced 300 ohm transmission line, and



OHMITE Little Devil

INSULATED COMPOSITION RESISTORS

In critical television applications, Little Devil Resistors can be depended on for longer, trouble-free service. These tiny, rugged units give quiet performance and are ideal for sensitive RF circuits. Moreover, they are available in $\pm 5\%$ as well as $\pm 10\%$ tolerances — in $\frac{1}{2}$, 1, and 2-watt sizes; standard RMA values.



"Little Devil" RESISTOR ASSORTMENT IN All-Plastic CABINET

Designed for the serviceman! Three assortments to choose from— $\frac{1}{2}$ -watt, 1-watt, 2-watt sizes. Each includes 125 most frequently used Little Devils, in 40 values, from 10 ohms to 10 megohms. Packed in rugged plastic cabinet—you pay only for the resistors! Prices: $\frac{1}{2}$ -watt, \$12.50; 1-watt, \$18.75; 2-watt, \$25.00.

SEND NOW for Catalog No. 21

OHMITE MFG. CO.
4845 Flournoy St., Chicago 44



Be Right with...



RADIO SERVICE DEALER • JUNE, 1950

to attenuate any noise which may be induced in the line.

The network of coils and condensers following this antenna transformer combination is designed to pass frequencies above 47 mc only, and as such is called a "high pass filter". It

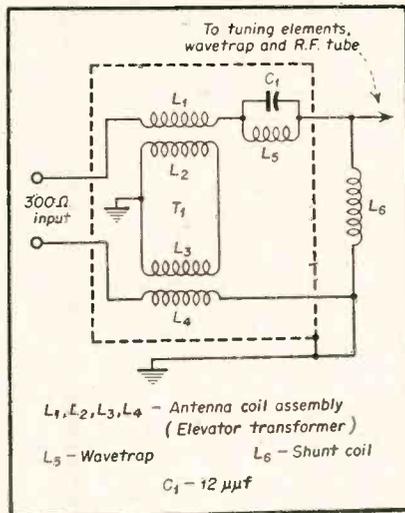


Fig. 3-7: Application of Elevator Transformer as an antenna input transformer. (RCA)

is also designed to provide maximum attenuation at 23.5 mc for rejection of i-f interference at the r-f grid.

Tube Input Circuits

Two basic types of tube input circuits are used in TV. The first is the conventional grid input circuit shown

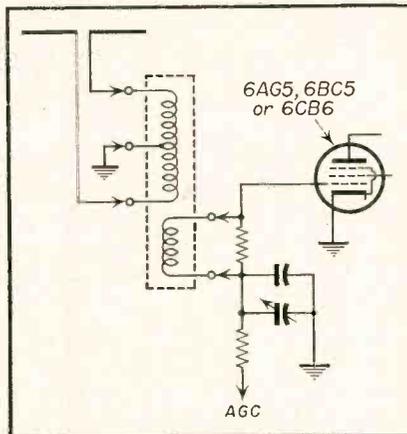


Fig. 3-8: Conventional grid input circuit as used in Standard Tuner.

in Fig. 3-8. The second is a grounded grid amplifier as shown in Fig. 3-9.

The use of grounded grid amplifiers arose from the use of triodes in the Front Ends of TV receivers because of their lower noise (internal tube noise) characteristics. As the number of elements in a tube is increased the internal noise effects also increase, especially at high frequencies. There-



You Don't Risk Your Neck

ERECTING THE ALL-ALUMINUM

MILNER MAST

patent applied for

Check These Points Before You Buy a Mast

- 50 ft. Mast complete weighs less than 50 lbs.
- Minimum wind resistance. No painting, no rusting, no corrosion
- Threaded section of Mast tubing stronger than the tubing itself
- No climbing—entire assembly is done from the bottom even on 100 ft. heights
- Can be erected from horizontal position up to 40 ft.
- Rotatable from the bottom
- Less space to stock
- All shipments prepaid


Get full details, write MILNER MANUFACTURING COMPANY

Jackson, Mississippi

All-aluminum fittings. Universal top adapts to any size antenna.



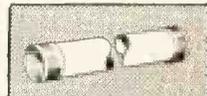Can be placed anywhere. Bases designed for any type installation.



Tubing in 10-ft. sections is joined by special rolled thread design (patent applied for).

**MORE CAPACITANCE
... LESS BULK...**

AEROVOX

**TWIST-PRONG
BASE
ELECTROLYTICS**



● It's the "new look!" See it right on the labels. Higher voltages and capacitances—without increase in sizes — in some numbers!

That makes these handy twist-prong base electrolytics handier than ever. Prongs extend through mounting surface and are twisted or bent to hold unit rigidly in place. May be mounted on fibre (insulated) or metal (grounded) socket-shaped washer riveted or eyeletted on chassis. Ideal for initial equipment. Indispensable for replacements.

● Our jobber stocks Aerovox twist-prong base Type AF electrolytics. See listings in latest catalog for your precise needs. Ask our jobber for your copy — or write us.



**FOR RADIO-ELECTRONIC AND
INDUSTRIAL APPLICATIONS**

AEROVOX CORP., NEW BEDFORD, MASS., U.S.A.
Export: 13 E. 40th St., New York 16, N.Y. • Cable: 'ARLAB'
In Canada: AEROVOX CANADA LTD., Hamilton, Can

fore, triodes are favored at tube types in TV Front Ends.

However, triodes cannot be used in very high frequency circuits without some form of neutralization, on account of feedback between plate and grid. The use of a grounded grid circuit permits the use of a triode without neutralization, since the grid now acts as a shield between plate and cathode. Because the potential between grid and cathode still varies with the input signal, as far as the output vol-

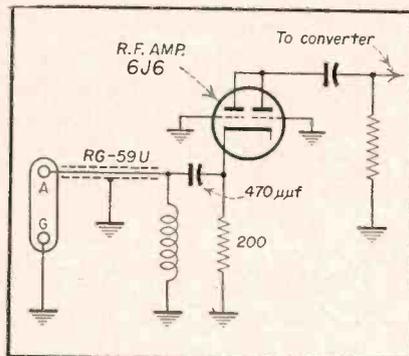


Fig. 3-9: Grounded grid amplifier used in Stromberg-Carlson Model TV-12LM receiver.

tage is concerned the tube acts as a conventional amplifier.

No discussion on antenna input circuits would be complete without mention of the push-pull input arrangement used in the RCA 630 TC chassis. Reference to Fig. 3-10 will reveal a simplified version of this section.

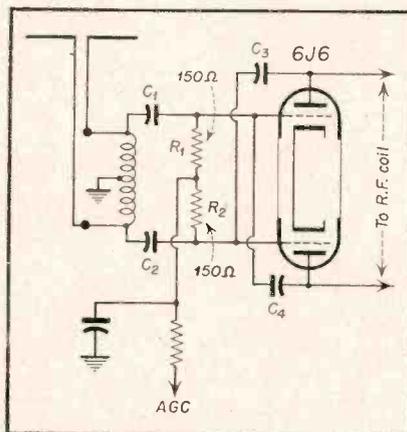


Fig. 3-10: Input circuit used in RCA 630 TS chassis.

The balanced input coil effectively short circuits the low-frequency signals which are picked up by the antenna. Condensers, C_1 and C_2 are antenna isolating capacitors. The re- of the twin triode 6J6 tube, and effect sisters R_1 and R_2 are the grid returns a 300 ohm circuit for the antenna input. Condensers, C_3 and C_4 are neutralizing capacitors.

The ORIGINAL and Still the BEST
LIGHTNING ARRESTER

for all
weather
conditions

will not
absorb
moisture

completely
waterproof



APPROVED
for OUTDOOR-
Indoor Use!
Protects Television Sets Against
Lightning and Static Charges

JFD SAFE TV GUARD

Fits Any Type of Twin Lead

No. AT102 for Regular Twin Lead
No. AT103 for Oval Jumbo Twin Lead
No. AT103 Also for Tubular Twin Lead
BOTH Models Conform With Fire
Underwriters and National Electrical
Code Requirements for OUTDOOR
installations.

\$2.25
EACH

SIMPLE TO INSTALL . . . For maximum efficiency, arrester should be mounted outside window nearest to TV receiver, with ground wire attached to nearest grounded point. No stripping, cutting or spreading of wires necessary. Supplied complete with 4 ft. length of Ductile Aluminum Ground Wire for Wall Mounting, and Strap for Mast or Grounded Pipe installation.

Look for the JFD Trademark

JFD MANUFACTURING CO., Inc.
6127 16th Avenue, Brooklyn 4, N. Y.
First in Television Antennas & Accessories

WALDOM
Replacement Cone Manual
Catalog No. 50

For
Finer
Tone
a Waldom
Cone

Write for your FREE
Copy of this handy catalog Today!

Waldom's Free 24-Page Replacement Cone Manual is a handy reference that Speeds up your repair jobs — which means more profit to you! This reference manual lists excellent replacement data for over 75 different TV, FM, and AM Sets. Write today for your Free copy. Just send your name and address to Dept. D.



Waldom Replacement Cone Assemblies are manufactured with the highest standards of precision workmanship and technique! Waldom Cone Assemblies feature:

- Hawley diaphragms — with the patented thin, tapering edge that assures maximum speaker efficiency and true low frequency response.
- The finest voice coils and spiders made with precision craftsmanship to exacting specifications.
- Unconditionally Guaranteed as to construction and performance.
- The full R.M.A. Warranty.

For Finer Tone a Waldom Cone

WALDOM ELECTRONICS, INC.
911 N. Larrabee St., Chicago 10, Ill.

INDUCTANCE BRIDGE

[from page 18]

terpreted directly in inductance units (microhenries, millihenries, or henries) according to the range table given in Fig. 2. The signal source may be an audio oscillator (400 or 1000 cycles) or a 60-cycle voltage obtained from the secondary of a filament transformer. The detector may be headphones, an a-c vacuum tube voltmeter, or magic eye tube. Provision should be made to plug in volume-control-type rheostats of different values at R_5 , since no single unit will reach all of the high- and low-resistance values required over the full range of the bridge.

The bridge is operated in the following manner: (1) Connect the coil of unknown inductance to terminals X-X. (2) Connect the detector and signal generator to the bridge. (3) Set switch S_2 to position M. (4) Rotate the dial of rheostat R_1 to obtain a null. (5) Adjust rheostat R_5 to sharpen the null, and readjust R_1

if necessary. (6) If the null is indistinct, or if no null is obtained at any setting of switch S_1 , throw switch S_2 to position H and readjust R_1 and R_5 .

The busy radio serviceman can build a handy inductance bridge of this type for five dollars or less, using all new components. It is very likely that he will be able to salvage most required parts from his spare parts box.

PROJECTION CONVERSION

[from page 17]

Unit, plugs into the Picture Tube Protection Unit directly.

Since the plug and socket ends of these cables are factory made and tested, it is only necessary that the remaining ends be properly connected to the chassis point indicated.

On the top side of the 630TS chassis, almost directly over the Vertical Linearity control are 3, 1/2" holes. The seven wire cable with octal plug is run through the rear hole. The 5-wire tube socket cable is run through the front hole. The 6-wire cable is run through

the hole in the rear of the chassis where the focus control was originally mounted.

The following color coding is used to identify each wire:

7-wire cable with octal plug.

1. Black — Ground
2. Orange with White Tracer — Arm of Horizontal Centering control.
3. Orange with Black Tracer — #4 and #6 of 5V4G tube V-128.
4. Blue with white tracer — Arm of Vertical Centering control.
5. Blue with Black tracer — Green Lead of Vertical Output transformer.
6. Red — To one side of terminal strip that focus control leads are connected to.
7. Yellow — To remaining terminal of above same strip.
8. No connection.

6-wire cable with plug.


1. Black — Ground
2. Orange — #3 of Vertical Output tube 6K6, V-122.
3. Rubber zip — (115 V. A.C. Connect to the two outside terminals of the 3-terminal strip located on the end of chassis directly behind the Horizontal Centering.



GUARDIAN CENTERING MAGNETS and FOCUS COILS Insure Better Positioning of the Pattern in Popular TV Sets . . .

GUARDIAN CENTERING MAGNETS

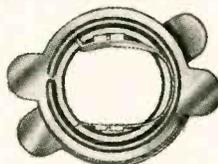The Guardian Centering Magnet compensates magnetically for any misalignment of the electronic beam of the focus coil assembly. Eliminates manual adjustment of the raster.



GUARDIAN FOCUS COILS

Over a million Focus Coils have rolled off Guardian's production lines into TV sets of leading manufacturers. With more than 75 types established as Guardian standard, speedy delivery to meet today's replacement needs is a matter of routine. Write.



GUARDIAN ELECTRIC
1606-G W. WALNUT STREET CHICAGO 12, ILLINOIS
A COMPLETE LINE OF RELAYS SERVING AMERICAN INDUSTRY


NEW Departure in Antenna Design!

PEAK RECEPTION

on ALL Channels

with the NEW

**Tricraft
P-38**

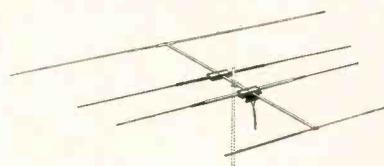

Uni-directional FM and TV ANTENNA!

- Good reception in every channel
- Receives ONLY from direction of station
- 7 separate and distinct radiating elements
- 23 degree beam rejects ghosts, interference and noise
- Designed for maximum strength — sturdy construction
- Can be stacked into two and four bay arrays
- Easily and quickly installed
- Available with or without masts
- Detailed, illustrated and technical literature available upon request

TRICRAFT ANTENNAS
are available from
leading jobbers!

New Our new catalog is
NOW available. Write
Catalog for your FREE copy.




Tricraft Products Co.

1535 North Ashland Ave., Chicago 22, Ill.

Manufacturers of complete line of Television, FM and AM antennas and accessories

DRAKE *insta-heat* SOLDERING GUN

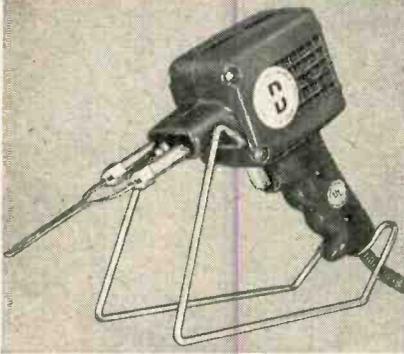

with the *New*

READY STAND

Designed and engineered for you, the perfectly balanced Drake "insta-heat" Soldering Gun features a full 135 watts, easy-removable tip and the ideally located *visa-lite*. Now with the new ready stand—to keep the Drake *insta-heat* Soldering Gun at hand for instant use — it's the gun with all the features you've wanted. See your distributor today.

DRAKE ELECTRIC WORKS, INC.
3656 LINCOLN AVENUE CHICAGO 13

1950 PROFIT GUIDE
WALKER-JIMIESON • ELECTRONIC SERVICE • CHICAGO
JUST OFF THE PRESS
W-J
THE TELEVISION AND RADIO SERVICE-DEALERS' SUPPLY HOUSE
WALKER-JIMIESON, INC.
211 SOUTH WESTERN AVE., CHICAGO 12, ILLINOIS • CHICAGO 12-2253

PACKED WITH NEW PROFIT ITEMS

Complete buying guide for service-men, dealers. New TV accessories, TV installation equipment, TV test instruments, tubes, radio accessories and other electronic supplies. Thousands of repair parts cross-indexed for quick, easy selection. Same-day shipment. Catalog sent only to those entitled to wholesale prices.

SEND For Your FREE Copy Now

WALKER-JIMIESON, INC. 102
311 S. Western Ave., Chicago 12, Illinois
 Please send your 1950 Free Profit Guide

Name _____
Address _____
City _____ Zone _____ State _____

4. Rubber zip — (control and just below the power transformer.
 5. White — #6 of Horizontal Output transformer.
 6. Green — Cathode of 3NP4 tube. Connect to green lead of 5-wire cable from tube socket.
- 5-wire cable with 3NP4 tube socket.
1. Red — Video, to junction of .05 mfd. condenser C141 and 100K ohm resistor R148.
 2. Yellow — #7 of 6K6GT Horizontal oscillator tube, V125.
 3. Blue — Ground.
 4. Black — Ground.
 5. Green — To Green lead of 6-wire cable and plug.

Separate instructions are enclosed for the North American Philips projection unit and reference is made to them for installing the projection tube and adjusting the optical unit.

It is advisable to set up the complete assembly "on the bench" and adjust the chassis and optical unit before installing it in the cabinet.

Before applying power to the chassis make sure all plugs are inserted in their proper sockets and that all tubes are firmly seated.

FIELD FINDINGS

[from page 28]

Pacific Electronic Exhibit

Plans continue for the 6th annual Pacific Electronic Exhibit that opens in the Long Beach, Cal., municipal auditorium Sept. 13 for a three-day run. This year, besides the exhibit booth displays, the event will also be a conference for electronic business leaders and engineers.

Golenpaul 20 yrs with Aerovox

Comes spring, 1950, and Charley Golenpaul rounds out twenty years with Aerovox Corporation, one of the world's largest manufacturers of capacitors for radio, electronic and industrial applications, located in New Bedford, Mass.

It was back in 1930 when Aerovox was still in Brooklyn, N. Y., that Charley joined the company.

Twenty years later finds Charley Golenpaul still at Aerovox, wearing the title of Sales Manager, Distributor Division.

Shure Bros. 25th Anniversary

Shure Brothers, Inc., Chicago, Ill., one of the largest independent makers of microphones and acoustic devices, celebrated its 25th anniversary on April 25 with a luncheon and afternoon party for all employees.

HAVE YOU A JOB FOR A TRAINED TECHNICIAN?

We have a number of alert young men who have completed intensive training in Radio and Television Repairing. They learned their trades thoroughly by working on actual equipment under personal, expert supervision. If you need a trained man, we invite you to write for an outline of our course, and for a prospectus of the graduate. No fees, of course. Address:

Placement Manager, Dept. P105-6
COMMERCIAL TRADES INSTITUTE
1400 Greenleaf Chicago 26

JOB CONDITIONED! ABLE, ALERT MEN— READY FOR WORK!

Thoroughly trained in TV Installation and Service by UNIVERSAL TV SCHOOL (Est. 1938), Pioneer TV Training School. Screened men, willing to work and eager to demonstrate their skill. Expertly guided on modern TV test equipment, these men have completed 9 months intensive training and are fully groomed for industry. When in need of TV installation or bench man please contact us. This service is FREE. Write or wire

UNIVERSAL TELEVISION SYSTEM
Wirthman Bldg. Kansas City 3, Mo.
G. I. APPROVED

TECHNICIANS AVAILABLE

Carefully selected group of trained men, graduates of reliable and well established trade school now available to fill positions in the Radio or Refrigeration field. Willing to travel anywhere. Why not fill that vacancy with an efficient and reliable man. Write Eastern Technical School, 888 Purchase Street, New Bedford, Mass.

AD INDEX

Aerovox Corporation	31
Astatic Corporation, The	8
Bishop Manufacturing Corp.	30
Burgess Battery Company	27
Commercial Trades Institute	36
Drake Electric Works, Inc.	36
Eastern Technical School	36
Editors & Engineers, Ltd.	32
Federal Tel. & Radio Corp.	12
Guardian Electric	35
KenRad Tube Div. of G-E Co.	9
Heath Company, The	31
Industrial Condenser Company	32
International Resistance Co.	4, 5
J. F. D. Manufacturing Co., Inc.	34
Mallory Co. Inc., P. R.	Cover 2
Milner Manufacturing Co.	33
Ohmite Manufacturing Co.	33
Radiart Corporation, The	3
RCA (Electron Tubes)	Cover 4
Rider Publisher, Inc., John F.	1
Sangamo Electric Company	Cover 3
Sprague Products Company	10
Sylvania Electric Products, Inc.	7
Technical Appliance Corp.	11
Telrex, Inc.	28
Tricraft Products Company	35
Universal Television System	36
Vaco Products Company	30
Waldom Electronics, Inc.	34
Walker-Jimieson, Inc.	36
Workshop Associates, Inc. The	26

Hiawatha was a PIKER!



"Go out into the world," said Pops* "and don't come back 'till you're proved tops!"



The water test he passed with ease. Earning a feather was just a breeze...



Heat was applied to test his worth. In "hot spots" he then won a berth...



The life test took a long, long time. Though others quit—he kept his prime...



His leads proved strong—his casing tough. It did no harm to treat him rough!


His Pops was pleased when he came through. We know you'll like the Redskin, too!

Sangamo's New Molded Paper Tubular Capacitor gives LONG LIFE under severe conditions!

The REDSKIN is easy to work with—on production line or on the bench—because the especially designed flexible leads resist breakage and can't pull out! It offers greater mechanical strength because of its plastic construction. It is molded under *low* pressure, assuring elements undamaged in fabrication, longer life and greater dependability. It is an 85° C tubular which offers assurance of long life under television and other severe operating conditions.

A trial of these *better* molded tubulars will convince you. See your jobber—if he can't supply you, write us.

*Big Chief Sangamo

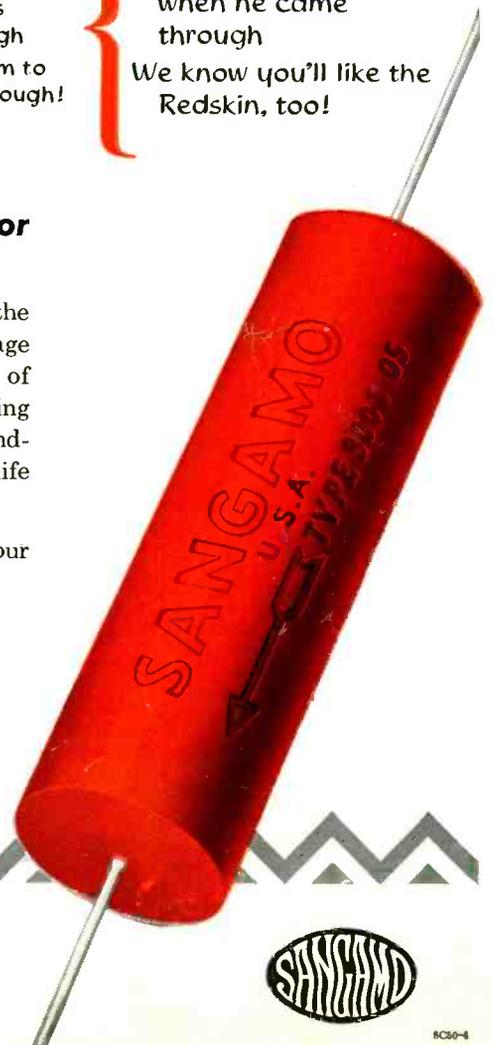


SANGAMO ELECTRIC COMPANY
SPRINGFIELD, ILLINOIS

In Canada: Sangamo Electric Company Limited, Leaside, Ont.



8C30-4

Encore!

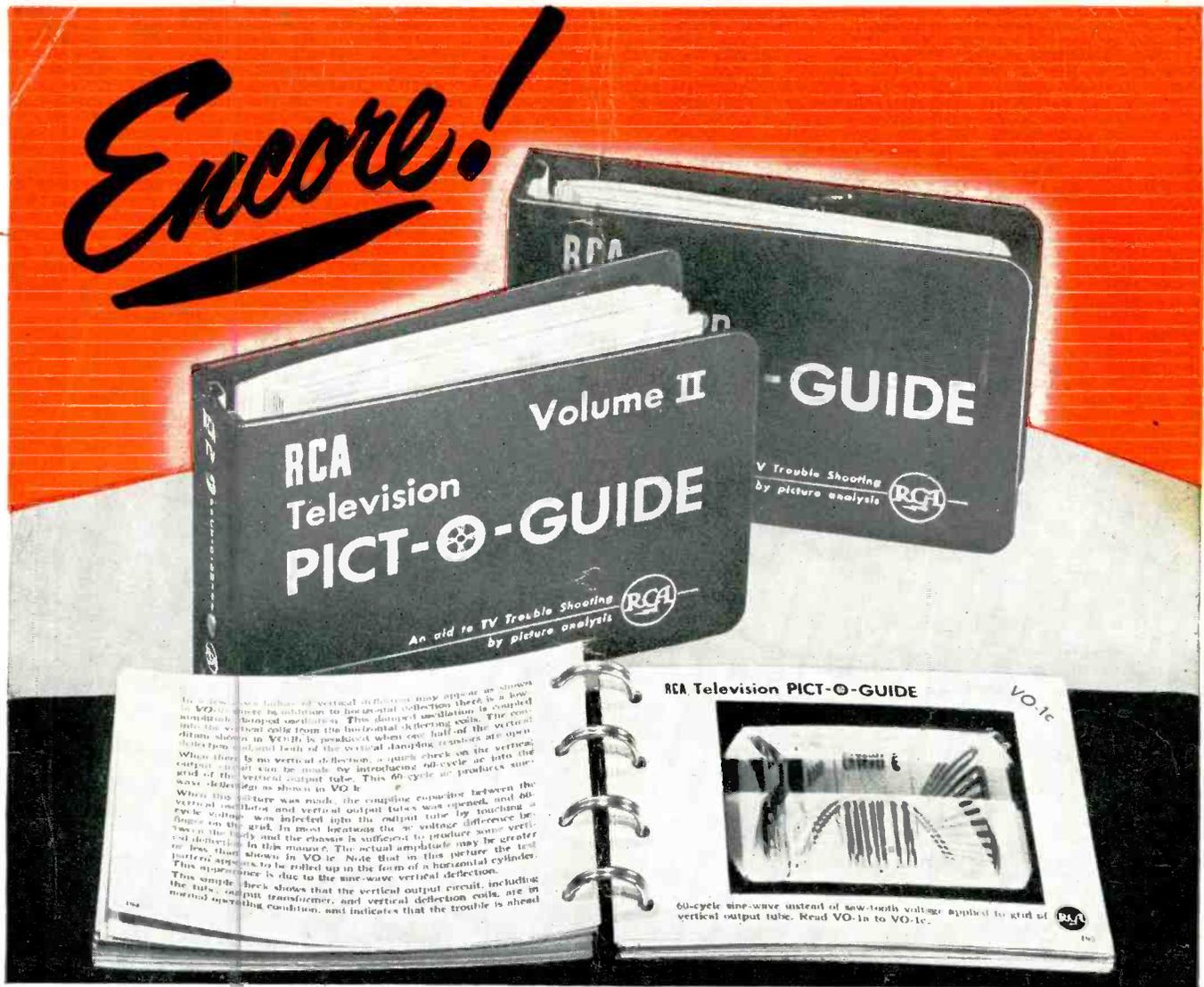

Again -
Yours -

by popular demand . . . the Famous RCA Pict-O-Guide Volume I or II with each order of 100 tubes or 3 kinescopes

NOW . . . another big opportunity for service technicians to get Volumes I and II of the famous, *original* RCA Television Pict-O-Guide edited by John R. Meagher, the renowned TV service authority. Place your order with your RCA Tube Distributor at once to insure delivery of your copies before the supply is again exhausted, or the offer expires.

Acclaimed as one of the greatest practical and instructive aids to TV receiver trouble shooting in

the field, the *original* RCA Pict-O-Guide provides eyewitness identification of many faults common to all TV receivers and gives basic, authoritative remedies—the kind of practical information that pays off on the job.

There's no substitute for the quality of service information in the RCA Television Pict-O-Guide . . . just as there's no substitute for the quality of RCA tubes. *Both* are yours at no additional cost!

Always keep in touch with your RCA Tube Distributor



RADIO CORPORATION of AMERICA

ELECTRON TUBES

HARRISON, N. J.