
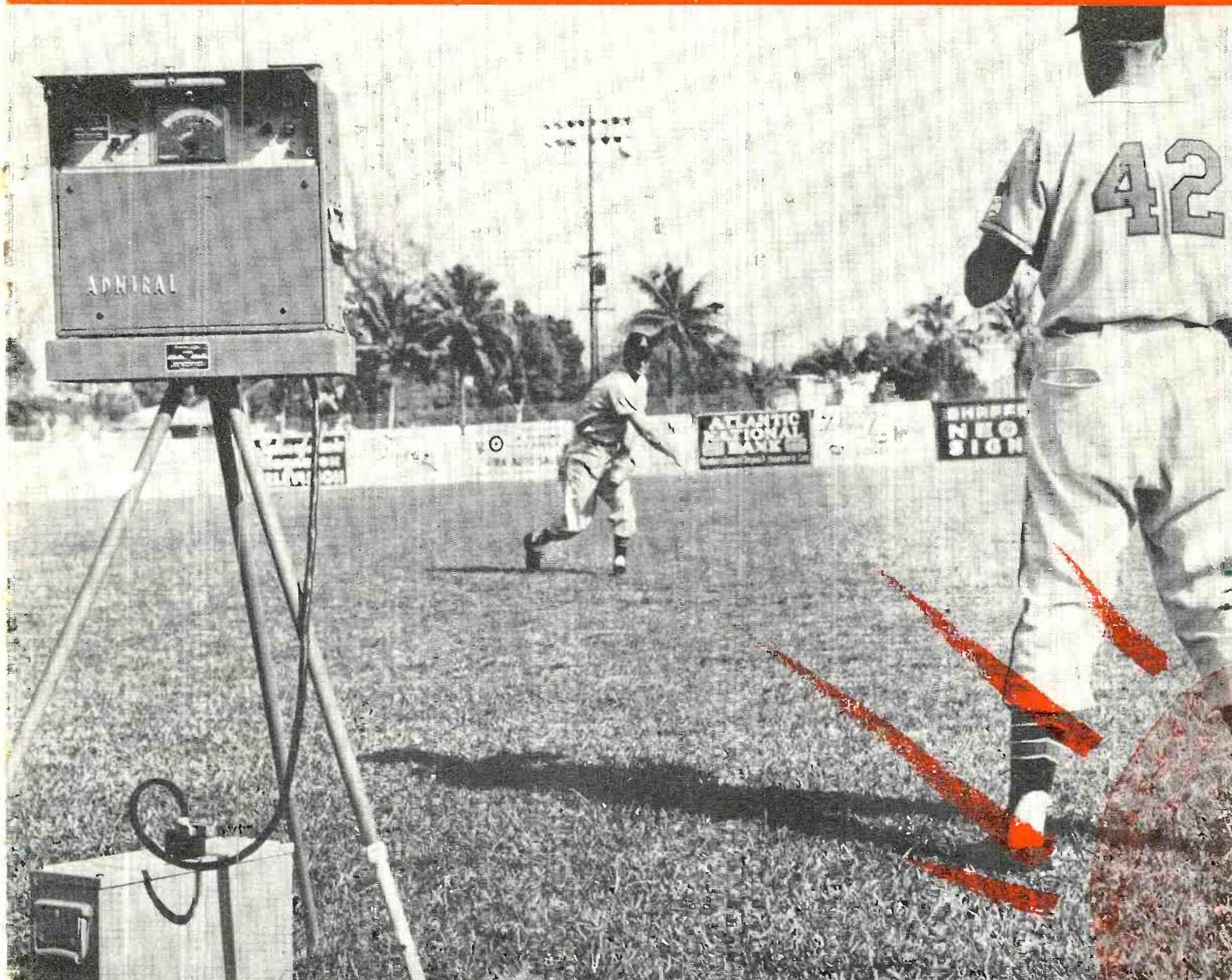


ELECTRONIC SERVICING

APRIL
1957
50¢

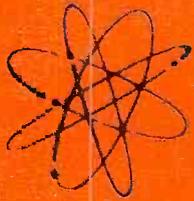

Electronic Level Controls

Color Bar Generator

Chrysler Auto Radio

New Transistor Schematics

New TV Schematics

depend on

RADIART VIBRATORS

... the COMPLETE replacement line

Men who know

THE RADIART CORP.
CLEVELAND 13, OHIO

A Subsidiary of  Cornell-Dubilier

Radiart vibrators are the Standard of Comparison for quality, performance and dependability in the industry! Men who know... management, jobbers... and servicemen... ALL agree that experience over the years has dictated that RADIART vibrators are the ones to buy and use.

AND... the complete line of COMMUNICATION vibrators offers the correct replacement for 6 volt and 12 volt applications.

Be sure you have the new vibrator replacement guide... write for your FREE copy...

EDITORIAL STAFF

Sanford R. Cowan	Publisher
Samuel L. Marshall	Editor
Oscar Fisch	Assistant Editor
Robert T. Dargan	Technical Editor
Charles W. Gardner, Jr.	Production Manager
San D'Arcy	Contributing Editor
Paul Goldberg	Contributing Editor
Elbert Robberson	Marine Communications Editor
Lawrence Fielding	HI-FI & PA Editor

BUSINESS STAFF

Advertising Sales

New York and East

Richard A. Cowan
Jack N. Schneider
300 West 43rd Street
New York 36, N. Y.
JUdson 2-4460

Chicago and Midwest

Jim Summers
Suite 55 C
Pure Oil Building
35 E. Wacker Drive
Chicago 1, Ill
ANdover 3-1154

West Coast

Ted E. Schell
2700 West 3rd Street
Los Angeles 57, Calif
DUnkirk 2-4889

Charles W. Hoefler
1664 Emerson Street
Palo Alto, Calif.
DAvenport 4-2661

David Saltman Advertising Production Mgr

CIRCULATION

Harold Weisner	Circulation Manager
Carol J. Binderman	Ass't Circulation Mgr.
Madeleine Sturmer	Circulation Processing

ELECTRONIC SERVICING (formerly Radio-TV Service Dealer) is published monthly by Cowan Publishing Corp., 300 West 43rd Street, New York 36, New York. JUdson 2-4460. Subscription Price: \$3.00 one year, \$5.00 two years in the United States, U. S. Possessions, Canada and Mexico. Elsewhere \$1.00 per year additional. Single copies 50c. Second Class Mail privileges authorized at New York, N. Y.

POSTMASTER: SEND FORM 3579 TO ELECTRONIC SERVICING, 300 WEST 43rd STREET, NEW YORK 36, N. Y.

ELECTRONIC SERVICING



VOL. 18, NO. 4

Member

APRIL, 1957

BPA



FEATURE ARTICLES

- Automatic Electronic Control**, by Murray Barlowe 2
Basic methods of measurements and control used in liquid level applications.
- Using the Color Bar Generator**, by Robert G. Middleton 4
How to set up and test color TV receivers using a color bar generator.
- Equalization In Hi-Fi Systems, Part 2**, by Lawrence Fielding 12
Presence controls, record scratch and turntable rumble filters, FM de-emphasis characteristics, and loudspeaker padding are some of the topics discussed in this installment.
- Test Equipment** 14
Kitronic Model TT-2 Transistor Checker, and Simpson Model 382 Horizontal System Analyzer described.
- Servicing Emerson 1957 Receivers, Part 2**, by Harold Bernstein 18
Noise inverter, pix stabilizer, and amplified pulsed age stages discussed.
- Auto Radios for 1957—Chrysler**, by Ralph A. Moss 39
Removal, installation and service problems.
- Selling Service, Part 1**, by M. E. Wirt 45
Helpful hints on merchandizing your servicing facilities.

CIRCUIT AND SERVICE FORUM

- Workbench** 6
- The Answerman** 10
- Complete Manufacturer's Schematics—TV** 21-36
Admiral 14UY series chassis RCA 14-S-7052 chassis
Motorola TS 423 chassis Philco 7L40 chassis, etc.
- Complete Manufacturer's Schematics—Radio** 37, 38
DuMont Transistar Portable RA-902 Model 1210
RCA Transistor Portable RC-1164A Model 9-BT-9 series
- Video Speed Servicing Systems** 41-44
Admiral Ch. 14YP3B Philco 7E10, 7E11

DEPARTMENTS

- S. R. Cowan Ad Libs** 8 **Trade Flashes** 46
- New Antennas** 17 **Contacts** 48
- Hi-Fi-P.A.-Audio** 20 **Rider Speaks** 49

Advertisers' Index Cover III

THIS MONTH'S FRONT COVER

Automation has entered the baseball picture now that the Kansas City Athletics are using a traffic radar set (portable Admiral Radarscope) at spring training camp to check the speed of their pitchers.

Entire Contents, Copyright 1957, Cowan Publishing Corp.

COWAN PUBLISHING CORP., 300 West 43rd Street, New York 36, N.Y.

HAVE SHORT MARK-UPS KILLED YOUR



PROFITS

Supplement "highly discounted" items with high profit sales of AMPHENOL TV Antennas, Accessories and Twin Lead!

High Profit installations using top quality components are the way to make up for short discounts on other items. Use the "tail to wag the dog" as the sure way to Profits in 1957!

1957 can be Your Profit Year!



AMPHENOL ELECTRONICS CORPORATION
chicago 50, illinois

AUTOMATIC ELECTRONIC CONTROL

IN LIQUID LEVEL MEASUREMENTS & CONTROL

by MURRAY BARLOWE

THE maintenance of electronic devices used in industry is definitely within the capabilities of the alert service technician who is well grounded in electronic fundamentals. The basic electronic building blocks such as resistors, capacitors, inductors, and vacuum tubes, operate in exactly the same way in an automatic electronic control, as they do in a radio or television receiver. As a matter of fact, the circuitry that the service technician tackles in his daily routine work are in most instances *much* more complex than what he would find in the average industrial electronic control unit. Since cost is not as great a factor in the industrial electronic field as it is in the highly competitive television business, you will find that industrial electronic equipment uses simple straightforward circuitry, rather than the complex circuits designed by cost-conscious engineers.

Automatic control as such, is not new. The very process of life is dependent upon many delicate and complicated automatic control systems. The process whereby the human body automatically maintains its temperature at approximately 98.6 degrees Fahrenheit is an excellent example of an automatic control system in nature.

One of man's early attempts at automatic control is probably best illustrated by James Watt's invention of the flyball governor back in 1788. He needed a method of controlling the speed of his steam engine. The principle of operation of the flyball governor clearly illustrates the basic elements of most modern control systems. Referring to *Fig. 1*, we notice that the vertical shaft of a governor is driven by an engine. As the entire assembly revolves, the flyball weights A and B are moved outward

from the shaft by centrifugal force. The higher the speed, the further out the weights move. In so doing, assembly C is moved down on the shaft. This downward motion which has a direct relationship to the speed of the engine, is mechanically coupled to lever D, which is connected to the steam valve, or throttle, of the engine. An increase in speed will then automatically operate the valve to slow down the engine. On the other hand, a decrease in speed will reduce the centrifugal force. The weights will then drop down toward the shaft assembly, C will move up, and lever D will open the valve to cause the engine to speed up again. Thus the steam engine becomes "self regulating" or automatically controlled.

Let's break down the elements of this simple control system in the manner shown in *Fig. 2*. In any control system we must have a "sensing" device, to sense or measure the "variable" which we are trying to control. In our mechanical flyball governor the weights "sense" the changes in speed and convert them into an up and down motion. The system of levers mechanically "amplifies" or modifies this motion and then activates the "correction" element, in this case the steam valve. And so we have completed our control loop.

A simple automatic electrical control system which we come in contact with daily is the control of the heating system in our homes. A temperature sensitive piece of metal constructed in the form of a switch (thermostat) serves as the sensing element. It converts changes in temperature into electrical information. The electrical impulse activates a relay, valve, or motor to increase or decrease the amount of heat in the house.

In industry it is often desirable to automatically control the level of materials in tanks, furnaces, etc. Before the level can be controlled it has to be detected, or "sensed." Quite often a simple mechanical float assembly can be used, such as the ball type float used to maintain the level of water in the tank of a toilet reservoir. When the level falls below a predetermined point the float drops, opening a valve until a desired water level is re-established.

In many cases, a purely mechanical system is not practical. Temperatures, pressures and contents of storage tanks may prevent or complicate the use of floats and mechanical linkages through the walls of the tanks.

One such problem encountered by the writer required that the level of molten glass be maintained in a furnace with burning gases moving across the surface of the molten glass at high pressures. The primary problem was to devise a sensing device to determine the actual level of the glass.

Obviously a simple float arrangement would not work. This was a problem that lent itself to electronic sensing. A system of probes was devised and a novel circuit developed whereby the level could be maintained within very close limits.

There are many ways that the level of liquids and other substances can be detected electronically. One of the simplest which would be suitable for conductive liquids (most liquids and molten solids are conductive) would be to mount a probe from the top of a tank (*Fig. 3a*). The bottom tip of the probe would be set at the level to be maintained. If the tank is metal, a second connection can be made directly to the tank. When a meter and a source

of voltage are then connected to these two points, a current will flow when the tip of the probe touches the liquid. If the tank is non-conductive, two probes (*Fig. 3b*) could be mounted side by side; or a metal plate as shown in the bottom figure, could be put into the tank.

To provide more than just an indication, a relay would be substituted for the meter. The relay in turn could actuate an electric valve to turn the flow of liquid on or off. If it is desired to sense the level of the liquid without actually coming in contact with its surface (as with highly corrosive acids) it is possible to use the capacity formed by a metal plate suspended above the liquid and the surface of the liquid itself (*Fig. 4*). The capacitance thus developed could be part of the tuned circuit of an oscillator and the plate current of the oscillator would then be a function of this capacitance.

As the level of the liquid rises, the capacitance between the metal plate and the surface of the liquid, increases. A relay in the plate circuit of the oscillator could be set so that it would pull in when the current reaches a pre-determined level.

A pair of parallel probes (*Fig. 5*) could be used in place of the metal plate. The probes would then form a capacitor in parallel with the tuned circuit of an oscillator. The capacitance of the condenser thus formed is determined by, (a) the area of the probes, (b) the space between the probes, and, (c) *the dielectric constant of the surrounding medium*.

The electrostatic field set up by the capacitor is concentrated between the probes, but it also extends out into the

[Continued on page 52]

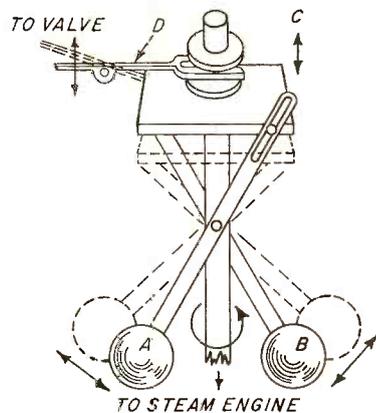


Fig. 1—Control of engine speed by governor action.

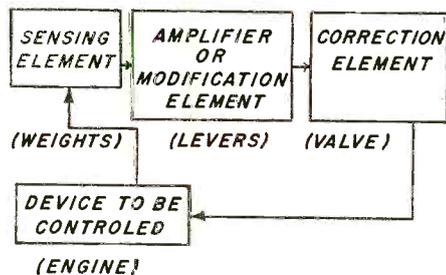


Fig. 2—Basic elements of an automatic control system.

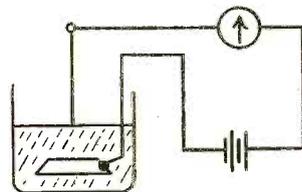
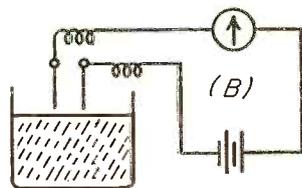
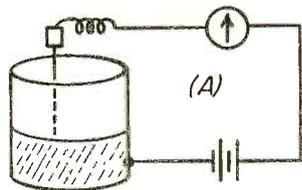


Fig. 3—Three probe arrangements for sensing liquid levels.

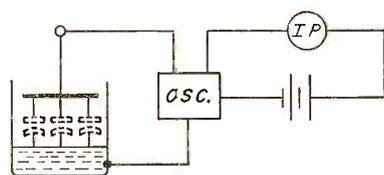


Fig. 4—Capacitance used to avoid contact with the liquid.

RAYTHEON

"ALL-SET" TUBES

designed with Independent Service Dealers in mind

When Raytheon engineers design tubes, they are not restricted to engineering the tubes to the limited specifications of a specific TV or radio receiver. On the contrary, Raytheon engineers must design tubes that combine top quality with all-around performance in all makes and models of receivers. Proof of their success lies in the fact that Raytheon tubes are sold to virtually all TV and radio set manufacturers on a competitive technical basis.

This ability to perform in many circuits makes Raytheon "All-Set" Tubes ideal for service dealer replacement work. Fill your Tube Carrying Cases and tube shelves with Raytheon "All-Set" TV and Radio Tubes and you'll be able to meet tube replacement needs of all sets.

TV-Radio service is your business . . . serving you is ours

THEY'RE RIGHT...
FOR SOUND AND SIGHT

RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations
 Newton, Mass. • Chicago, Ill. • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes } Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes,
 all these } Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.

Excellence in Electronics®

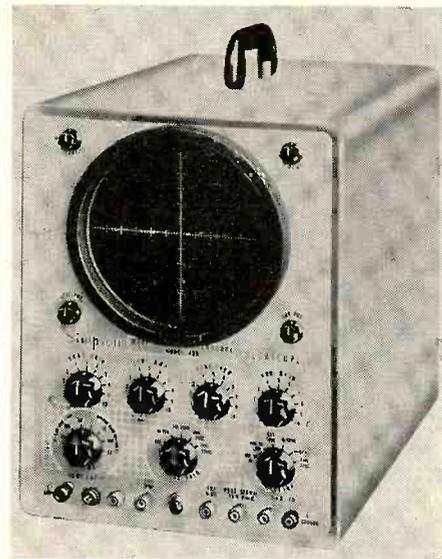


Fig. 1-A—Typical color bar generator and wide band oscilloscope are shown above.

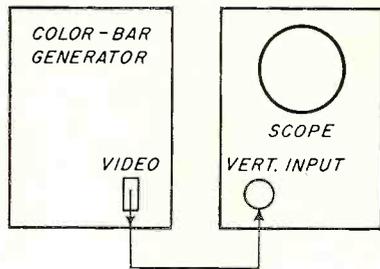


Fig. 1a—Block diagram illustrating how color bar pattern is applied directly to scope.

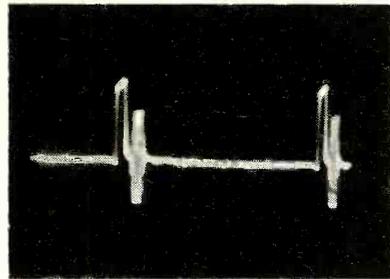


Fig. 2—Display of sync and burst signals with the appropriate setting of the selector switch.

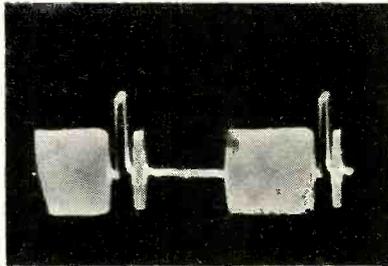


Fig. 3—The addition of the R-Y signal to the sync and burst signals produces above pattern.

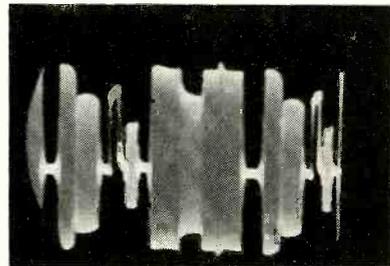


Fig. 4—Pattern produced by the simultaneous display of several color bars plus sync and burst.

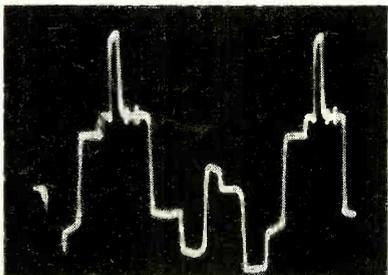


Fig. 5—Appearance of the Y signal in the absence of chroma.

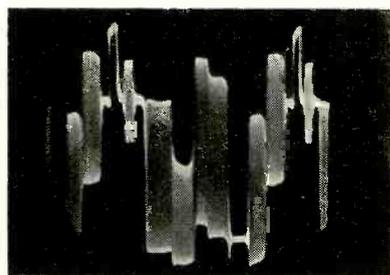


Fig. 6a—Chroma added to Y gives the complete color signal.

Using the Color Bar

The Color Bar Generator is an essential piece of test equipment in the servicing of color receivers. This article discusses some of the features of this instrument which will assist the serviceman in its use.

TELEVISION service technicians are confronted with the operation of several new instruments, with the advent of color television. Chief among these are the white-dot generator and the color-bar generator. The color-bar generator, (used with the wide-band scope) is little understood at the present time, and it is the purpose of this article to describe and illustrate its operation.

Fig. 1 shows the external appearance of an NTSC color-bar generator and a wide-band scope, used in color-TV service work. To start with, it is helpful to apply the output from the color-bar generator directly to the vertical-input terminals of the scope, as shown in Fig. 1A.

Components of the Complete Color Signal

Fig. 2 shows the display of sync and burst which is obtained when the selector switch is set to the appropriate position. Sync and burst are actually obtained in *all* chroma positions, although the accompanying chroma waveforms differ from one setting to the next. Fig.

3 shows the sync and burst with accompanying R-Y chroma when the selector switch is set to (R-Y).

The color burst (Fig. 2) consists of 8 or 9 cycles of a 3.579545-mc voltage, commonly referred to as 3.58 mc. The burst is located on the back porch of the horizontal blanking pulse. The (R-Y) bar signal seen in Fig. 3 also has a frequency of 3.58 mc, but its *phase* differs from that of burst. The chroma bar is a signal voltage, which is *phased* to correspond to the (R-Y) specification, namely 90° out of phase with the burst.

Several chroma bars can be switched in simultaneously from the generator, as shown in Fig. 4. Each of the bars differs in phase from the next, and represent signals such as the (R-Y), (B-Y), I, Q, etc. Note that all the chroma bars so far illustrated are centered on the black level. For this reason, they are *incomplete* color signals, but are provided because they serve extremely useful purposes in testing individual chroma circuits in color TV receivers.

The next step in building up the complete color signal is the addition of the Y (or brightness) signal, shown in Fig.

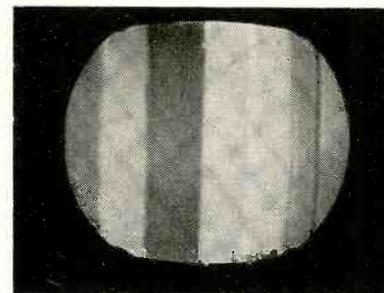


Fig. 6b—Bar pattern corresponding to color signal of Fig. 6a.

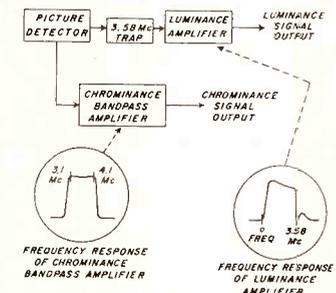


Fig. 7—Separation of luminance and chrominance signals.

Generator

by **ROBERT G. MIDDLETON**
Chief Field Engineer, Simpson Electric Co.

5. This is the component of a color signal to which a black-and-white TV receiver responds. Color reception is dependent upon reception of both the chroma signal and the Y signal. The Y signal fundamentally represents brightness levels of the video signal, and in the absence of the Y signal the matrices in the receiver do not respond normally, and true colors are not obtained.

When the chroma signals are added to the Y signal, a complete color signal is obtained, as illustrated in Fig. 6A. When this complete color signal is applied to the circuits of a color TV receiver, fully saturated true colors are obtained. The bar pattern displayed on the screen of the color picture tube is equivalent in all essential respects to that of a color test pattern transmitted by a color TV broadcast station. (See Fig. 6B.)

Separation of the luminance and chrominance signals proceeds in a color TV receiver as illustrated in Fig. 7. When individual Y chroma outputs are available from a color-bar generator, it is evident that the technician can make quick and decisive tests of the operation of the two principal receiver sections.

Vectorscope Analysis

Another very useful application of the color-bar generator and wide-band scope is the *vectorscope* application, for checking the phase relationships in the receiver circuits. To make this check, the output from the (R-Y) detector is applied to the vertical-input terminals of the scope, and the output from the

[Continued on page 53]

SHOW ANY PICTURE or PATTERN

at any time — ON ANY TV SET



For Both Black & White and Color TV

Provides standard Indian Head Test Pattern for proper TV set alignment, and stable White Dot and White Line Patterns for color convergence adjustments.

For Merchandising & Industrial Uses

Provides closed circuit TV system. Transmits pictures or messages for advertising, educational and commercial visual communication.

MODEL 1000

B&K DYNA-SCAN

PICTURE AND PATTERN VIDEO GENERATOR

Make the most of this *Complete Flying Spot Scanner*. It produces a composite video and sync signal that operates any standard black & white or color TV receiver. Can be used with one or more TV sets or fed into a master antenna system or community antenna system. Maximum resolution capability is well in excess of 450 lines; band width in excess of 5 mc. Projects and reproduces pattern or picture with high definition from any slide transparency. Transmits messages typed or written on clear acetate. Makes convenient stand-by and break-in for community distribution operation. Rugged, compact, portable, and ready to operate.


NET \$199.95

See your B&K Distributor, or Write for Bulletin No. 1000-D.

Available on Easy Time Payment Plan

B & K MANUFACTURING CO.

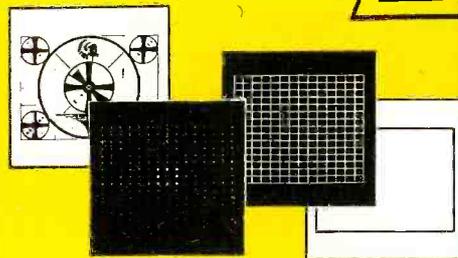
3726 N. SOUTHPORT AVENUE · CHICAGO 13, ILL.



3 TEST PATTERN TRANSPARENCIES AND ONE CLEAR ACETATE SUPPLIED

- 1 Indian Head Test Pattern
- 2 White Dot Pattern
- 3 White Line Crosshatch Pattern

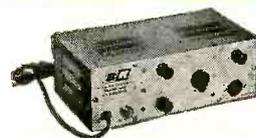These are broadcast-quality transparencies, and assure accurate, high-definition TV images. You can also transmit your own transparencies of any subject you wish. The clear acetate can be used for special messages. Extra transparencies and acetate available.



Model 950 Dyna-Scan Pickup and RF Generator only. Enables you to make your own picture and pattern video generator, at a saving. Supplied with three test pattern transparencies and one clear acetate. Net, \$69.95.



Model 500 DYNA-QUIK Dynamic mutual conductance tube tester. Accurately tests tubes faster. Net, \$109.95



Model 400 CRT Cathode Rejuvenator Tester. Tests and repairs TV picture tubes. Net, \$54.95



Model 750 CALIBRATOR Designed to check and adjust test instruments with laboratory accuracy. Net, \$54.95



Build today's profits with

MALLORY Mercury BATTERIES


— the batteries of tomorrow !

The amazing mercury battery, pioneered by Mallory, helped make practical the remarkable new pocket-size transistor radios. Tiny, powerful, long-lasting, Mallory Mercury Batteries are the fast-growing line that will bring you profitable sales today . . . even greater sales tomorrow.

Mallory Mercury Batteries excel in long shelf life . . . in service life and economy in transistor portables. To help spark your sales, you get the backing of year 'round promotion and strong advertising in magazines like The Saturday Evening Post, Time, Newsweek, Business Week and TV Guide.

See your Mallory distributor today, and get full facts on the full line of Mallory Mercury and Zinc-Carbon Batteries.

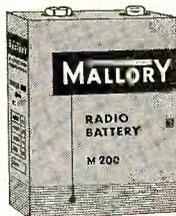For vacuum-tube portables,
sell Mallory Zinc-Carbon
Batteries . . . unsurpassed
for performance.



P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Mercury and Zinc-Carbon Batteries
- Controls
- Switches
- Rectifiers
- Filters

THE WORK BENCH

Unusual Service Problems And Their Solutions

by PAUL GOLDBERG
Service Manager

This Month's Problem:
Composite Sync Amplifiers

THIS installment is devoted to composite sync amplifier problems. Knowledge of the receiver circuitry, skill in utilizing the scope, manufacturer's service notes with waveforms in the proper places, are tremendous aids in solving problems of this type.

Dumont RA 340

The receiver was turned on and it was observed that the picture was rolling vertically and tearing horizontally. This was a composite sync problem. The picture did not overload on any channel. Thus we discounted an *agc* problem. V212B, the 1st sync clipper. V213B, the 2nd sync clipper, and V205A the noise inverter, were replaced individually but had no effect. At this point, the diagram was consulted. In order that V212B conduct only on sync information, the proper bias is automatically applied to the grid of V212B, pin 7, by the action of capacitor C269, and resistor R293. On the positive peaks of signal voltage, the grid of V212B will draw current, charging capacitor C269. This charge leaks off between pulses through

R293 making the average grid potential negative. With the proper design values in the plate, grid, and cathode of V212B, the bias will hold the tube at cut off until a signal at a higher level than the blanking pulse comes along. The output will then consist only of sync information. V213B performs the dual function of a 2nd sync clipper and a phase splitter. Negative going sync pulses are fed to the grid, pin 7, of V213B. The tube is operated at plate current saturation due to positive grid bias applied through R276. The negative sync pulse takes the tube out of saturation into reduced conduction and finally cut off. This achieves both positive and negative clipping with additional amplification. Horizontal sync pulses are fed to the horizontal phase detector from the plate and cathode. Vertical sync pulses also are fed to the vertical integrator from the plate of V213A. With these facts in mind, the scope was set up and a waveform check was made at pin 7 of V212B. The waveform was normal (see Fig. 1). Next a waveform check was made at pin 6 of V212B. It was noted

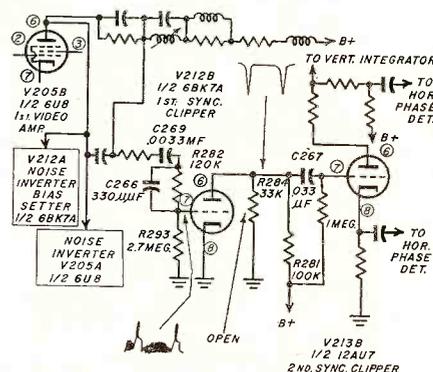


Fig. 1—Portion of DuMont RA-340 where defect caused loss of sync.

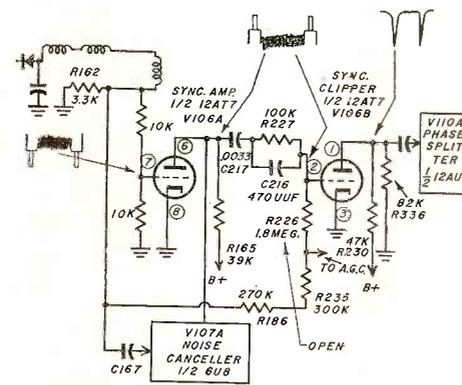


Fig. 2—Loss of sync caused by open grid resistor in GE 21C40.

that video information accompanied the sync pulses in this waveform. In other words, this tube was not completely separating the sync pulses from the video information. A voltage reading was next taken at pin 6 of V212B. Here, instead of +30 volts, the meter read approximately +60 volts. A resistance check was next made on R281 and R284. R281 checked satisfactorily, but R284, a 33K resistor, was found to be open. A new 33K resistor was installed and the receiver functioned properly.

With R284 open, the plate voltage went up causing the cut off point to move to a new and more negative location on the tube's characteristic curve. This allowed video information to come through to trigger the horizontal and vertical oscillators.

GE 21C40 "O" Line

The receiver was turned on and it was observed that there was no horizontal or vertical hold. There was a small *agc* problem involved here, since the receiver did overload on some channels. V106, a 12AT7 acting as a sync clipper and amplifier and V107A, a 6U8 used as a noise canceller were replaced individually, but had no effect. This therefore, was a composite sync problem where the receiver utilizes V106A as a sync amplifier, and composite sync trouble was suspected. The composite sync system functions in this manner. A portion of the detected signal from the video detector is directly coupled to the sync amplifier, V106A. After amplification, this signal is in turn fed to the sync clipper. Tied directly to the sync amplifier plate, is the noise canceller V107A. A negative signal is fed to the cathode of the noise canceller through C167 from the detector. Noise bursts exceeding the sync tip level, reduce the sync amplifier output (which is fed to the clipper) in such a way, that neither sync nor noise will be found in the output of the clipper. The inertia of the *afc* system maintains proper horizontal sweep synchronization. From the sync amplifier V106A, the amplified signal is fed to the grid of the sync clipper V106B. The composite video appearing on the grid of the clipper tube, V106B, causes this clipper to draw

[Continued on page 50]

Electro-Voice® POWER-POINT

HELP YOURSELF TO PROFITS BY HELPING YOUR CUSTOMERS!

HERE'S YOUR PROFITABLE OPPORTUNITY

to do your customers—and yourself—a favor! Stock and sell E-V POWER-POINT, the unique phonograph cartridge-and-needle combination that ends service and inventory headaches, insures customer satisfaction, assures repeat business!

ONE SERVICE CALL DOES THE JOB!


You install the mount and cartridge—there's a type for almost any phonograph. From there on it's repeat, repeat business for you! Because . . . come replacement time, your customer slips out the old, returns it to you for replacement, slips in the new faster than you can read this sentence!

POWER-POINT

is a nylon-encased FRESH ceramic cartridge PLUS two Jeweled (Superior synthetic sapphire or natural diamond) playing tips—ALL IN A SINGLE UNIT! There's a POWER-POINT for every record speed. List prices, \$3.95 (for two sapphire tips) to \$21.50 (for two diamond tips).

Plenty of sales-stimulating merchandising aids are available, backed up by national ads. Millions of POWER-POINTS are in use as original equipment, guaranteeing volume replacement sales.

3 MOUNTING MECHANISMS

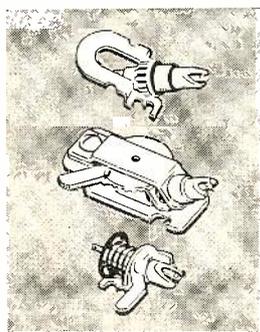

Model PFT-1, fixed mount, 50¢ List.

Model PT-1, turnover mount, \$1 List.

Model PT-2, turnunder mount, \$1 List.

HERE'S
POWER-POINT
ACTUAL SIZE



E-V POWER-POINTS

Model 51-1 (red) Two 1-mil sapphire tips List \$ 3.95	Model 56DS (orange) One 1-mil diamond, one 3-mil sapphire tip List \$21.50
Model 52-2 (green) Two 2-mil sapphire tips List 3.95	Model 76S (white) One 1-mil, one 3-mil sapphire tip. . List 4.25
Model 53-3 (black) Two 3-mil sapphire tips List 3.95	Model 76DS (pink) One 1-mil diamond, one 3-mil sapphire tip. List 21.50
Model 56 (blue) One 1-mil, one 3-mil sapphire tip. . List 3.95	



write FOR COMPLETE POWER-POINT
INFORMATION AND SPECIFICATION
SHEET SD-74

Electro-Voice®

ELECTRO-VOICE, INC. • BUCHANAN, MICHIGAN

Export: 13 East 40th Street, New York 16, U. S. A.
Cables: ARLAB



modern servicemen rely on RIDER books, manuals and S D O

... their future depends on electronic know-how

TV MANUFACTURERS' RECEIVER TROUBLE CURES

edited by Milton Snitzer

Fabulously successful, positive courses—a service library that has everlasting use in 8 volumes. Covers the specific TV receiver troubles, and the cures specified by the set manufacturer. Listings are by manufacturer, model and chassis number. Soft cover, illustrated. Each volume over 115 pp.

- VOL. 1: Covers complete details on sets produced by mfrs. (listed in alphabetical order) from Admiral to Dumont. #143.....\$1.80
- VOL. 2: Covers mfrs. from Emerson to Jackson. #143-2.....\$1.80
- VOL. 3: Covers mfrs. from Kaye-Halbert to Philco. #143-3.....\$1.80
- VOL. 4: Covers mfrs. from Philharmonic to Shaw. #143-4.....\$1.80
- VOL. 5: Covers mfrs. from Sparton to Zenith. #143-5.....\$1.80
- VOL. 6: All new coverage, through 1954, no duplications. Admiral to Firestone. #143-6.....\$1.80
- VOL. 7: New Coverage, from General Electric to Raytheon. #143-7.....\$1.80
- VOL. 8: New coverage, from RCA to Zenith. #143-8.....\$1.80

PICTURE BOOK OF TV TROUBLES

by Rider Lab. Staff

A fabulous series of definitive, practical books that teach recognition of faults in TV receivers.


- Vol. 1: Horizontal AFC-Oscillator Circuits. #168, 80 pp., \$1.35.
- Vol. 2: Vertical Sweep-Deflection Circuits. #168-2, 96 pp., \$1.80.
- Vol. 3: Video I-F & Video Amplifier Circuits. #168-3, 96 pp., \$1.80.
- Vol. 4: Automatic Gain Control Circuits. #168-4, 96 pp., \$1.80.
- Vol. 5: Horizontal Output & H-V Circuits. #168-5, 108 pp., \$1.80.
- Vol. 6: Horizontal & Vertical Sync Circuits. #168-6, 120 pp., \$1.80.
- Vol. 7: Sound Circuits & L-V Power Supplies. #168-7, 64 pp., \$1.50.

TV REPAIR QUESTIONS & ANSWERS

by Sidney Platt

A practical, extremely useful series of question and answer books on the troubles in, and the repair of, TV receivers.

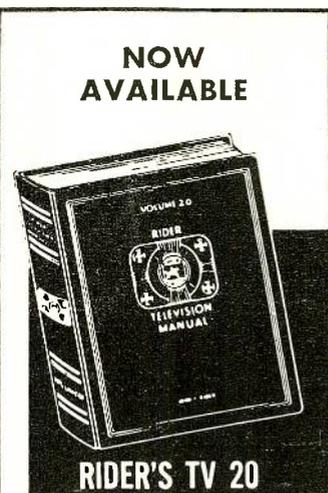- #173, Front Ends: 128 pp., \$2.10.
- #173-2, Video Circuits: 128 pp., \$2.10.
- #173-3, Sync & Sweep Circuits: 140 pp., \$2.10.
- #173-4, Deflection & H-V Circuits: 128 pp., \$2.10.
- #173-5, Sound & L-V Circuits: 120 pp., \$2.10.



NOW
AVAILABLE

RIDER'S TV 20

The only source of unabridged factory prepared and factory accurate TV receiver servicing information

LIMITED PRINTING

Reserve your copy at your jobber. If your jobber does not handle Rider Manuals, write direct.

NEW BOOKS

HOW TO INSTALL & SERVICE INTER-COMMUNICATION SYSTEMS by Jack Darr

The growth of the intercom as a modern tool of business presents an important service and installation opportunity. This book covers completely installation and maintenance of commercial intercommunication equipment. Soft Cover, 152 pp., 5 1/2 x 8 1/2", illus. #189.....Only \$3.00

REPAIRING TELEVISION RECEIVERS by Cyrus Glickstein

The most modern completely practical book, written by an expert with long experience in television receiver repair. Devoted to troubleshooting and repair techniques which are modern, yet down-to-earth. Covers the use of simple as well as elaborate test equipment of all kinds. Profusely illustrated. Soft Cover, 212 pp., 5 1/2 x 8 1/2", illus. #191.....Only \$4.40

SERVICING TV AFC SYSTEMS by John Russell, Jr.

This book discusses the trouble, location, and repair of the major types of AFC circuits used today... as well as some of the less common AFC systems the technicians may encounter. Waveforms, components, common faults, and their diagnosis are presented in a manner that affords the reader a thorough understanding of AFC circuits. Supplemented by more than 75 illustrations. Soft Cover, 128 pp., 5 1/2 x 8 1/2", illus. #192.....Only \$2.70

MUST READING FOR SERVICEMEN

TELEVISION—HOW IT WORKS (2nd Edition) by J. Richard Johnson

The most modern and authoritative text describing the theory of operation of all black-and-white television receivers. Each part of the receiver is explained in thorough detail and in a manner that makes the functioning of the components and the organization of the circuitry completely understandable. Fully illustrated. #101, MARCO cover, 352 pp., \$4.60; #101-H, cloth bound, \$5.50.

SERVICING TV VERTICAL AND HORIZONTAL OUTPUT SYSTEMS by Harry Thomas

Technicians and students will here find a complete discussion of vertical and horizontal output systems and their operation. #150, Soft cover, 176 pp., illus., \$2.40.

ALL WHO WANT THE BEST IN TV SERVICE INFORMATION

ON


RCA	EMERSON	SYLVANIA
PHILCO	MOTOROLA	HOFFMAN
ADMIRAL	CROSLLEY	WESTINGHOUSE
GE	ZENITH	PACKARD-BELL

Covers Production 1950-1956

...ASK YOUR JOBBER ABOUT
RIDER'S NEW
S D O
("single diagram only")

ONLY **50¢** PER CHASSIS!

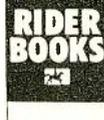RIDER books, manuals, S D O are available at your Parts Jobber. Look for the RIDER BOOK-SELLER. If these RIDER books are not available, order direct by checking books desired in this ad. **FREE! FREE!** Handsome genuine leather, gold stamped book-mark — lasts a lifetime — if you write today for **FREE** 1957 Spring-Summer Catalog SD-4 of all RIDER Books.



THE ANSWERMAN

Inquiries Sent To The Answerman Will Be Acknowledged Only
If Accompanied By Radio-TV Service Firm Letterheads.

BY ELECTRONIC SERVICING TECHNICAL STAFF

Answerman:

I have a Crosley chassis 484 which has not as good vertical linearity as I would like to see. I have checked everything and can't seem to find anything wrong. Can you suggest something that will improve the vertical linearity in this receiver. Although it is not objectionable to the customer I do know that it is not perfect and would like to make it better.

C. W.
Chicago, Ill.

chassis coded E or later and are shown in Fig. 1.

Dear Answerman:

I have a case of vertical stretching in the upper portion of a GE "S" model. I have tried such things as vertical output transformer, output tube, etc., and have not been able to correct it. What might be the least suspected cause of this type of condition?

E. G.
Philadelphia, Pa.

Crosley Television Service information has made available a circuit improvement for this receiver that will improve the vertical linearity in those receivers in which this is found to be desirable. The changes involve the removal of resistor R181, the addition of R186 and the changing of R180 from 5.6 K to 10 K ohms. These circuit changes have been incorporated in

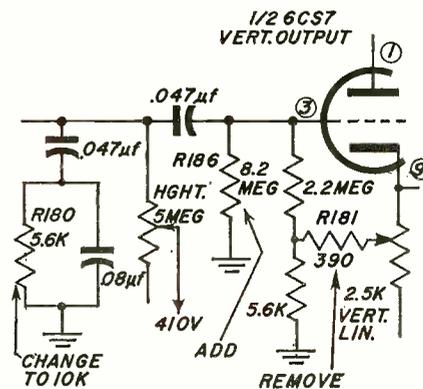


Fig. 1—Changes to improve vertical linearity in Crosley chassis.

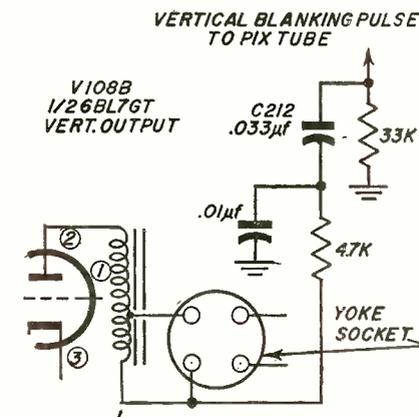


Fig. 2—Vertical stretching may be caused by defective C212.

JOHN F. RIDER PUBLISHER, INC. 116 West 14th Street, New York 11, N. Y.

Mr. Answerman:

I have a TV set that exhibits poor interlace. I doubt that the set ever had a normal presentation as far as interlace is concerned but since it otherwise works very well I would like to correct this condition. Pairing of the horizontal lines is common in about all positions of the vertical hold control. What is the best approach in overcoming this problem?

A. L.

Columbus, Ohio

Line pairing or poor interlace is usually due to the presence of a horizontal deflection pulse finding its way into the vertical oscillator grid circuit. What occurs is that some radiated or coupled pulse from the horizontal deflection system prematurely triggers the vertical oscillator and prevents the vertical sweep from starting the second field slightly below the first. The result is that the lines are paired instead of interleaved. To correct for this condition first investigate the integrating network for changes in capacitance or resistance. The addition of filtering into the circuit might be considered so as to remove the undesirable horizontal pulses if they exist there. Another possible cause is that the leads from the vertical hold control may have induced in them the horizontal deflection pulses which disturb the vertical oscillator circuit. The best approach to the problem is to determine the manner in which the horizontal pulses are reaching the vertical circuit. This is done experimentally. Some receivers, because of their component layout and the close proximity of the horizontal deflection circuitry to the vertical circuit, inherently exhibit poor interlace and might possibly require extensive redesign to be fully corrected. ■ ■



National Society
for
Crippled Children and Adults
11 So. LaSalle Chicago 3

Right from the carton...

Right for the set!



No guessing...
No fussing...
No wasting
precious time and effort.

CLAROSTAT

Right from the "RTV"* green carton, you get the right replacement control matched to original specifications.

Ask your Clarostat distributor
for "RTV"* Replacements!



* Reg. U. S. Pat. Off.

Controls and Resistors
CLAROSTAT MFG. CO., INC. • DOVER, NEW HAMPSHIRE

In Canada: CANADIAN MARCONI CO., LTD., Toronto 17, Ont.

IN THE previous issue, part one of this series discussed the record and tape playback preamplifier, the RIAA and older AES playback response curves, and delved into bass boost circuits. Part two will explain other conditions affecting hi-fi reproduction such as rumble, unbalance between woofer and tweeter speakers, etc.

Presence Controls

A presence control is something the "purists" resent, but which many hi-fi fans find quite interesting. It is nothing more than a low-Q resonant circuit inserted at some point in the preamplifier to give a gentle "bump" to the response curve of the system at frequencies between about 2000 and 4500 cps. This is nothing more than a little trick used by "pop" recording manufacturers for years to make singing vocalists seem to stand out from the accompanying orchestra. Since the circuit is usually passive, nothing much can go wrong with it. We mention it here simply so that you won't be surprised, when taking the response measurement of a preamplifier equipped with this gimmick, to find a 5 or 6 db rise at some mid-frequency for no apparent reason. The effect is usually adjustable by means of a potentiometer and can be cancelled out for program material that does not warrant this "refinement."

Record Scratch Filters

These circuits, sometimes built right into preamplifiers and sometimes sold

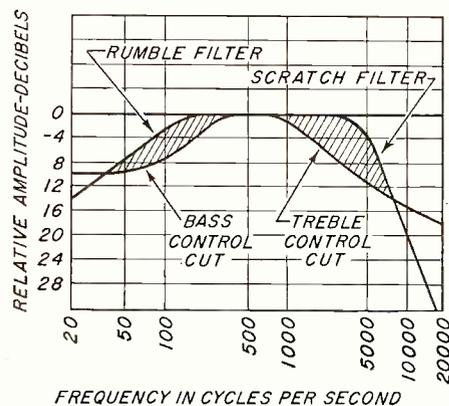


Fig. 7—Effect on audio response curve of filters and controls.

as separate equipment, are a worthwhile addition to a hi fi system, particularly if the proud possessor owns many older, 78 rpm recordings. The principle here is to retain as much of the music as possible while filtering out the maximum amount of surface noise. The problem is not as difficult as it would seem if you bear in mind the fact that most older, "scratchier" records had very little musical content above 5000 cps and that record scratch, as such, consists of frequencies above this point. The reason this filtering cannot be done with conventional tone controls is that their rate of cut (or slope) is too gradual, and for reasonable attenuation of scratch frequencies they would necessarily take a big bite out of the music portion of the spectrum as well. Scratch filters, on the other hand, are composed of both inductances and capacitors and can provide attenuation rates of as much as 18 db per octave, as shown in the comparison graph of Fig. 7. The shaded portion illustrates how much useful spectrum would have to be sacrificed to achieve equal attenuation at 10 kc using only tone controls. The biggest trouble encountered with scratch filters of this type involves hum. Because large inductances are usually present in the circuit, hum pick-up is apt to take place. Many users of such filters have them inserted in the chain at a point of too low a signal level. Thus the hum is particularly annoying. A quick cure involves nothing more than re-locating the filter electrically. For example, if a separate scratch filter is interposed between a preamplifier and an amplifier and the hum level seems

too high, the chances are that the amplifier has too much gain and the preamplifier not enough. By increasing the volume setting of the preamplifier and correspondingly decreasing the input level adjustment of the power amplifier you can, in effect, improve the signal-to-hum level to a satisfactory point. Remember, doubling the voltage level into the filter will improve its signal to hum ratio by two to one (6 db). Do not carry this procedure to extremes because many preamplifiers begin to show signs of distortion when driven to levels exceeding 1 or 2 volts.

FM De-Emphasis characteristics

If a customer complains that his FM reception has suddenly become shrill and "hissy" the chances are that the de-emphasis capacitor has opened up. Just as in record making, FM broadcasters deliberately introduce a substantial amount of pre-emphasis before transmission. The receiver, on the other hand, is designed to attenuate the highs and restore normal balance (at the same time suppressing unwanted hiss and noise, as in record playback). The amount of de-emphasis agreed upon by the industry is an attenuation of 11 db at 8200 cps. Of course, this cannot be readily checked without rf, FM generators, but the components used to accomplish this de-emphasis are easily found and measured. The network used consists of a series resistor and a shunt capacitor to ground, immediately following the FM discriminator or ratio detector. The product of the two values

Equalization in Hi Fi Systems

by LAWRENCE FIELDING

Frequency response equalization is further considered in relation to presence controls, de-emphasis circuitry, loudspeaker padding, and rumble and record scratch filters, showing their effects.

PART 2

(R in ohms times C in farads) is called the time constant and should equal about 75×10^{-6} (.000075). Thus, a 75 K resistor and a 1000 μfd shunt capacitor would comprise a proper combination for correct fm de-emphasis. In this instance, a shift in value of the 75K because of heat, or an open 1000 μfd capacitor would result in completely unbalanced and unnatural sounding FM reception.

Loudspeaker Padding

Many hi fi enthusiasts, in their quest for perfect sound, have assembled two-way and three-way loudspeaker systems which have anything but flat response. That is not to say that any one of their speaker selections was a poor choice. The fact is, the acoustic efficiency of loudspeakers varies greatly between units of different manufacture and occasionally, even between units bearing the same model number. It is not uncommon to find speaker efficiencies as low as 1% or as high as 15%.

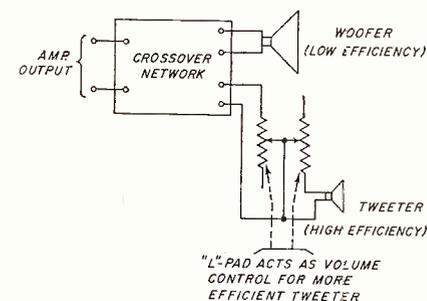



Fig. 8—An L pad for balancing the tweeter and woofer speaker outputs.

We will go into this subject in much more detail in the future. For the moment, however, it can be readily seen that if a "woofer" (low frequency speaker) having an efficiency of 1% is teamed up with a "tweeter" (high frequency speaker) having an efficiency of 5%, the result will be an overabundance of "highs." The easiest way to solve this one is to install a "pad" in the circuit of the overly efficient component as shown in *Fig. 8*. This device, technically termed an L pad, acts just like a volume control and enables the user to balance the output of the more efficient component against that of the less efficient one. The pad is usually mounted at the speaker to minimize extra stringing of wires around the room. Actual adjustment of the pad cannot, of course, be done with instruments and is a subjective matter between your customer and yourself. It is usually better to rely on your customer's judgment here, because he is the one who is most familiar with the sound of his system. Once adjusted, no further attention need be given to this control unless some major refurbishing or re-layout of the room furnishings takes place.

Turntable Rumble Filters

Like their "scratch filter" counterparts, rumble filters serve to reduce or eliminate this low frequency disturbance caused by somewhat inferior record changers or turntables. Rumble troubles usually lie in a band of frequencies between 10 and 60 *cps.* While it is true that the lower end of this band is inaudible anyway, the presence of such frequencies can, nevertheless, cause an annoying form of distortion. If the speaker cone is caused to move back and forth by a large amount at say, 10 *cps.*, it means that portions of the regular program content are superimposed upon the speaker cone when it is in a highly distended position. Under these circumstances, the stretched cone will reproduce even the mid frequencies with distortion and reduced efficiency. The overall effect is not immediately apparent, but becomes annoying after extended listening. The best way to check for rumble is to gently touch the speaker cone with your fingertips (either from

[Continued on page 56]

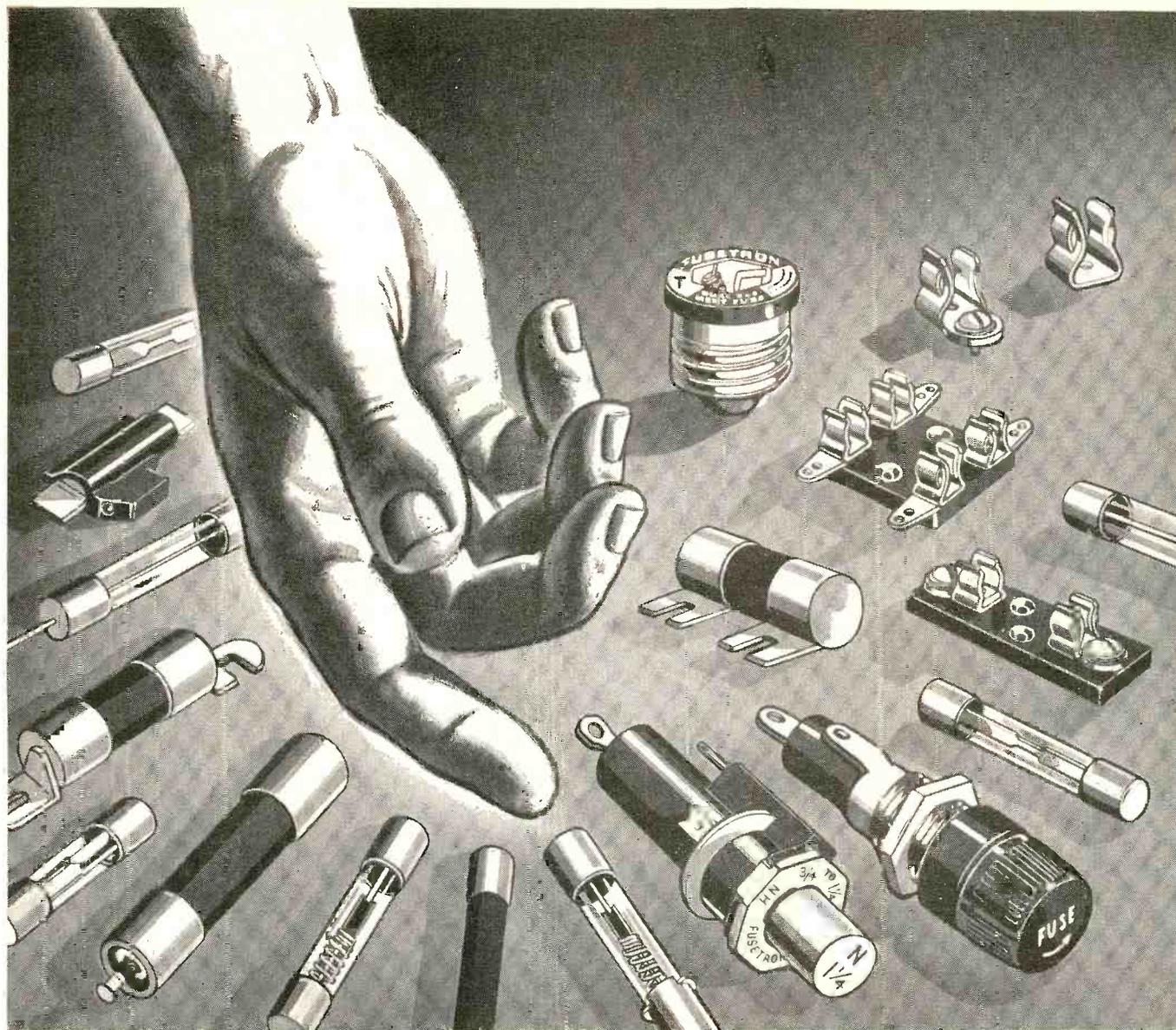

BUSS FUSES provide maximum protection against damage due to electrical faults

Protection against damage due to electrical faults can be no better than the device used to protect the equipment. The safest, most dependable protection you can get is with BUSS fuses.

To make sure BUSS fuses will clear the circuit should an electrical fault occur,—BUSS fuses are electronically

tested. A sensitive testing device automatically rejects any fuse not correctly calibrated, properly constructed and right in all physical dimensions.

This careful testing is also your assurance BUSS fuses won't give a false alarm by blowing needlessly. Shut-downs due to faulty fuses blowing without cause are eliminated.

By safeguarding users' equipment against damage—and by eliminating needless fuse blows—BUSS fuses give you double protection against loss of customer goodwill.

With a complete line of "trouble-free" BUSS fuses available in all sizes and types,—it is just good business to standardize on BUSS fuses.

For more information on BUSS and FUSETRON Small Dimension fuses and fuseholders . . . Write for bulletin SFB. Bussmann Mfg. Co. (Div. of McGraw-Edison Co.) University at Jefferson, St. Louis 7, Mo.

BUSS fuses are made to protect—not to blow, needlessly



Makers of a complete line of fuses for home, farm, commercial, electronic, automotive and industrial use.




Leave a trail of happy customers... replace with Sonotone Cartridges!

Every time you replace with a Sonotone 1P (single-needle) or 2T (turn-over) you're sure of another highly satisfied customer. Both Sonotone Ceramic Cartridges give sparkling, long-lasting and trouble-free performance—almost always *better than original equipment*.

And every time you replace with a Sonotone, you're better off, too. Both models mount the same easy way—take care of over 90% of your quality replacement calls! With only 2 models to work with, you can do the *same job the same way*, time after time, easier and faster.

New standard of the phono industry

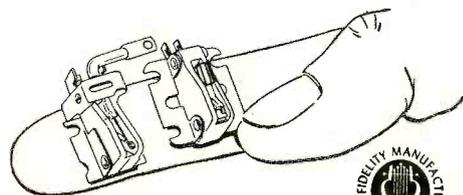In more than half the quality phonographs made today by leading manufacturers, you'll find one of these Sonotone cartridges. All the more reason why you should standardize on Sonotone.



Electronic Applications Division

SONOTONE® CORPORATION

ELMSFORD, N. Y.

IN CANADA, CONTACT ATLAS RADIO CORPORATION, LTD., 50 WINGOLD AVE., TORONTO

Test Equipment

TRANSISTOR TESTER KIT

by the Technical Staff
of KIT-TRONICS

THE KIT-TRONICS Model TT-2 Transistor Tester is a new high precision unit for testing PNP and NPN transistors and semi-conductors. It is available either in kit form or wired and tested. The TT-2 measures basic parameters of the transistor under test. As such, it corresponds to a mutual conductance tube tester as contrasted to the cheaper emission type of tube tester. It features a 4 $\frac{5}{8}$ " rectangular meter with a 2% movement and 1% precision components. It is housed in a molded phenolic case and is completely self contained and self calibrating.

It permits the serviceman to test a transistor without charts, and even without knowing in advance whether the transistor is NPN or PNP. The tester will determine the polarity of the transistor without damaging it.

The development laboratory and university laboratory will appreciate the quick and accurate tests provided by the tester. The audio fan will be especially well pleased with the feature which permits him to match like or unlike (i.e. NPN-NPN and PNP-PNP or NPN-PNP) pairs in push-pull applications, for both gain and leakage.

Ranges include current gain BETA 0-100 and 0-300, an expanded ALPHA scale 0.50 to 0.99 and Leakage I_{bo} .

Circuit Description

The tester operates the transistor under test as a *dc* amplifier in a common-emitter configuration.

The function is first set to switch select circuits for testing the transistor leakage I_{bo} between the emitter and the collector, as shown in *Fig. 1*. This position also provides for testing the transistor for short or open, and for measuring the front-to-back ratio of xtal diodes by using the TYPE switch to reverse polarity.

Next the selector switch is set to the CAL position and the calibration circuits are brought in to operation. A precise one microampere reference bias is placed on the base of the transistor under test, using 1% components. (see *Fig. 2*)

The selector switch is then turned to position BETA-300 and the base current is automatically increased by exactly 3.333 microamps, (*Fig. 3*). An increase of 1 *ma* in the collector current would correspond to a current gain of exactly 300. The function is linear and the meter BETA scale is calibrated from 0 to 300.

If the transistor under test is found to have a BETA of 100 or less, the selector switch is advanced to the BETA-100 position. Here the base current is automatically increased to a value exactly 10 microamps above the reference bias. A collector current of 1 *ma* would correspond to a current gain

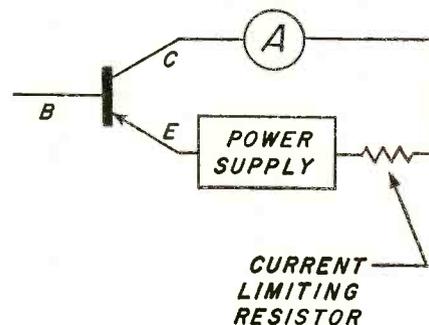


Fig. 1—Simplified circuit used for testing emitter to cathode leakage.

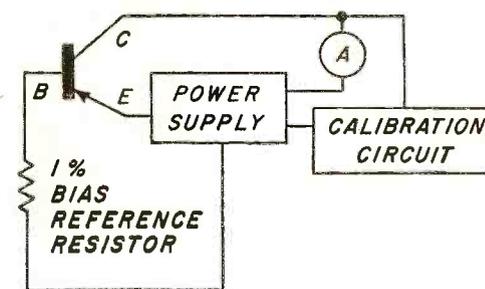


Fig. 2—Simplified circuit for calibrating the tester (CAL position).

WIN A WEEKEND AT THE WALDORF FOR 2

IN THE PYRAMID TWIST-MOUNT CAPACITOR CONTEST

TOTAL—147 WONDERFUL PRIZES—PLUS A PRIZE TO EVERY ENTRANT . . . SERVICEMEN, ENTER NOW! YOU CAN'T LOSE!

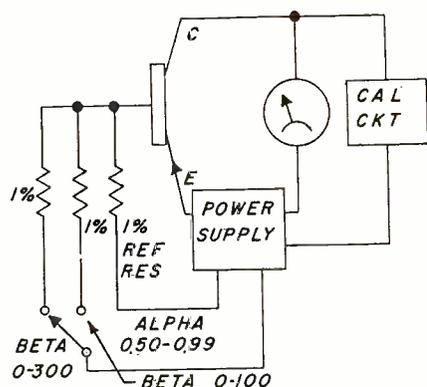


Fig. 3—Position BETA-300 for determining current gain of transistors.

of 100 and the BETA scale is therefore calibrated from 0 to 100.

The measurement of ALPHA, strictly speaking, requires operating the transistor in a common-base configuration. The direct measurement of ALPHA in such a circuit is not very practical since the range of interest (0.9 to 0.9999) is compressed into the upper ten percent of a linear meter scale. Fortunately ALPHA is equal to $BETA / (1 + BETA)$ and the ALPHA range of interest can be displayed on most of the meter scale, using a logarithmic calibration. Accordingly the meter is calibrated to indicate ALPHA from 0.5 to 0.99, corresponding approximately to the BETA range 0-100. Values of BETA greater than 100, i.e. 100 to 300 on the BETA-300 range, correspond to values of ALPHA greater than 0.99. For example, a BETA of 200 corresponds to an ALPHA of about 0.995, a BETA of 250 to an ALPHA

IT'S EASY TO WIN ANY ONE OF THESE WONDERFUL PRIZES:

GRAND PRIZE: Weekend at New York's fabulous Waldorf Astoria Hotel for 2, guest of Pyramid. Air transportation from your home to New York and return. Weekend of entertainment including a visit to the famous Gaslight Club, dinner at the Waldorf's Starlight Roof, and breakfast at the Waldorf. Air transportation by CAPITAL Airlines Viscount.

1st PRIZE: One 4-drawer steel file cabinet plus your choice of 50 sets of PHOTOFAC folders. Value: \$120.45.

FIVE 2nd PRIZES: 5 CR-30 PRECISION Cathode Ray Tube Testers. dlr. net \$109 ea.

TEN 3rd PRIZES: 10 CRA-2 PYRAMID Capacitor-Resistor Analyzers. dlr. net \$92.50 ea.

TWO 4th PRIZES: 2 SW-54 NATIONAL Short Wave Receivers. dlr. net \$59.95 ea.

TEN 5th PRIZES: 10 JENSEN professional speaker units consisting of a D-30 lifetime driver unit and RT-20 rectangular horn. dlr. net \$44.40 per set.

FIFTEEN 6th PRIZES: 15 TW CHANNEL MASTER 7 element "traveling wave" TV antennas, Model 350. dlr. net \$33 ea.

EIGHTEEN 7th PRIZES: 18 PYRAMID Pyra-Pak kits consisting of \$69.95 in Pyramid capacitors, metal tool box and tool kit. dlr. net \$29.95.

THIRTY-FIVE 8th PRIZES: 35 PYRAMID gift certificates entitling you to \$10. (dlr. net) of Pyramid capacitors at your distributor.

9th PRIZE: WALCO twin-point diamond phono needle. dlr. net \$30. For G.E. Var. Rel. Cartridge.

FIFTY 10th PRIZES: 50 WALCO needles for G.E. twin-point sapphires. \$3.50 dlr. net.

AND to all entrants a kit of 5 bypass and coupling capacitors featuring the Pyramid type IMP.

It's easy to win any one of 147 big prizes—just follow these simple rules: Identify the unnamed Pyramid T-M capacitor in the TV set schematic appearing on this page. Give the Pyramid stock number, name and model number of TV set. Then mail your entry to Pyramid. Use coupon on this page or obtain additional blanks from your distributor. A different schematic will appear in these servicemen's magazines for 4 months. Prizes will be awarded on a points-earned basis as follows: 5 points for Contest No. 1; 10 points for Contest No. 2; 15 points for Contest No. 3; 20 points for Contest No. 4; and 10 points each contest for neatness. Possible perfect score: 90 points. However it is not necessary to achieve a perfect score to be declared a prize winner.

So act quickly...send in your entries early each month...you can't lose.

JUDGES: M. Harvey Gernsbeck, editorial director, Radio-Electronics
Oliver Read, D.Sc., publisher, Radio & Television News
Howard W. Sams, chmn. board, Howard W. Sams & Co., Inc.



HELPFUL HINTS


The unidentified capacitor in each entry will be a Pyramid Twist-Mount. All schematics are of TV sets made in the U. S. by a known manufacturer within the past 2 years.

Schematics for reference may be those published by the TV set manufacturers, Howard-Sam's Photofacts, or by any other accepted publisher. You may enter as often as you like but be sure to include a box top (showing stock number) of any Pyramid Twist-Mount Capacitor, with your letterhead or business card with each entry.

WHO MAY ENTER

Any Radio-TV serviceman or employee of a Radio-TV service company may enter. Officers, employees, (members of their families) of Pyramid Electric Co. or its advertising agency are not eligible to enter the contest. All entries are limited to residents of the continental U. S. over 21 years of age.

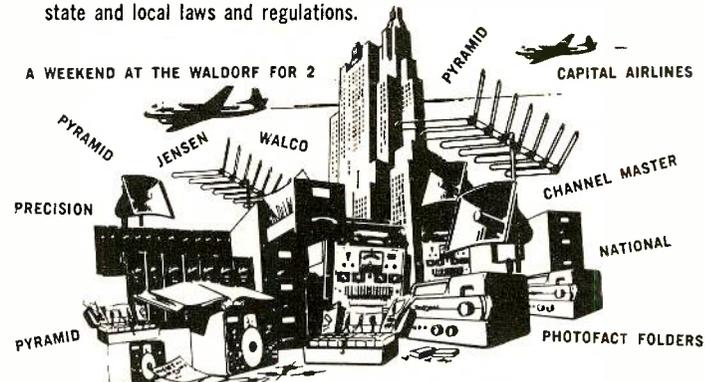All entries become the property of Pyramid Electric Co., none will be returned and the decisions of the judges are final. In case of ties, duplicate prizes will be awarded. This contest is subject to all federal, state and local laws and regulations.



MAIL THIS ENTRY BLANK NOW!

Pyramid Twist-Mount Contest, Dept J
Pyramid Electric Co.
P.O. Box 655, Tyler Park Station, North Bergen, New Jersey

Entry No. (1) (2) (3) (4)—(check one)—Is: Pyramid stock No. _____

Twist-Mount values _____

Set manufacturer's name _____ TV set model No. _____

I enclose a box top (indicating stock number) of any Pyramid Twist-Mount Capacitor together with my business card or letterhead or my employer's.

Contestant's name _____ Position _____

Contestant's address _____

City _____ Zone _____ State _____

Employer's Firm name _____

Employer's address _____

City _____ Zone _____ State _____

My jobber's name and address _____

ENTER AS OFTEN AS YOU LIKE—FOR ADDITIONAL ENTRY BLANKS
SEE YOUR JOBBER.

Capacitors, Selenium Rectifiers—for original equipment, for replacement
PYRAMID ELECTRIC COMPANY North Bergen, New Jersey


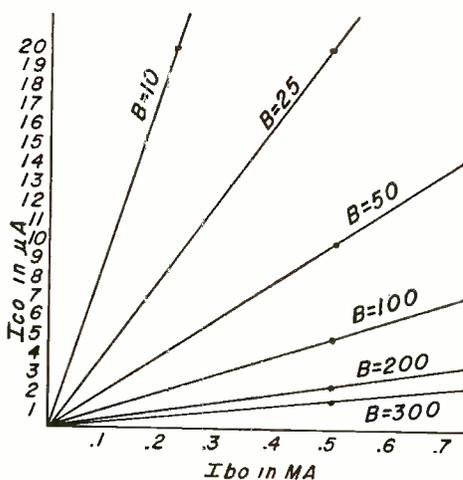


Fig. 4—Base collector leakage is read directly from above curves.

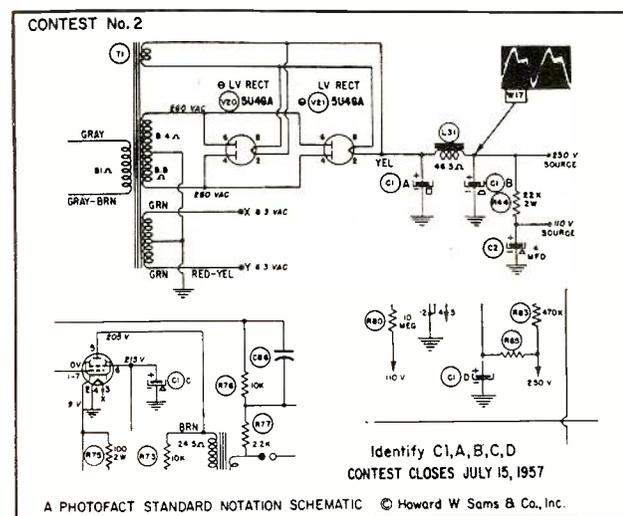

A PHOTOFAC STANDARD NOTATION SCHEMATIC © Howard W. Sams & Co., Inc.

MORE TV SIGNAL GAIN AT LOWER COST FOR ALL VHF INSTALLATIONS...



Automatic Broadband VHF BOOSTERS and AMPLIFIERS

Whether you need signal amplifiers for a 2000-set master TV system or a booster for a single TV receiver, there's a B-T unit that's designed for the job.

Most TV technicians and installers will say 'amen.' They have learned that they can rely on products bearing the B-T Labs symbol. Rigorous factory quality control of construction, gain and match assures dependable and uniform performance of each product that goes out into the field.

And for positive proof of superior engineering...

Exclusive patents: $\left\{ \begin{array}{l} 2,710,314 \\ 2,710,315 \\ 2,609,466 \end{array} \right\}$ covering automatic broadband circuits and relays have been granted to Blonder-Tongue.

Check to see which one of these units will clear up your specific signal gain problem.

VHF AMPLIFIER Model MLA

Powerful all-channel VHF cascode amplifier with more than 37 db gain. Has variable gain controls for equalizing high and low bands. Output on each band: 1.25 volts RMS, flat to within 2 db. Self-powered. Matched input. 75-ohm coax fittings at input and output. When used with MAGC maintains constant output level. **\$132.50 list**

COMMERCIAL ANTENSIFIER Model CA-1

A popular broad band VHF amplifier for antenna and line applications. Gain: 26 db on low band and 24 db on high band. Low noise circuit. Matched 75 ohm and 300 ohm input. Gain control. Self-powered. **\$84.50 list**


ANTENNA BOOSTER Model AB with Remote Control

More than 25 db gain. Most popular broadband antenna amplifier in weatherproof housing with mast-mounting bracket. Remote control power supply located near set. Furnishes either 24 or 110 volts to amplifier, as desired. Single line carries power 'up' and signal 'down.' 'On-off' is automatic with TV set. Swing down chassis for easy servicing. **\$99.50 list**

HOME BOOSTER Model HA-3

Provides more than 16 db gain. Automatic 'on-off' operated by TV set. No tuning. Features low-noise, push-pull, broadband circuits. Self-powered. **\$47.00 list**

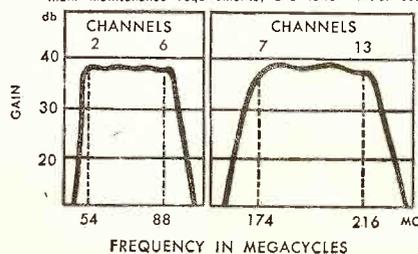This Typical Response Curve means superior performance—greater gain with lower noise, flatter response, minimum maintenance requirements, and lower initial cost.



Dept. SD-4



BLONDER-TONGUE LABS., INC.

9-25 Alling Street, Newark 2, N. J.

Industrial TV Cameras • TV Systems • VHF and UHF Amplifiers and Converters • TV Accessories

of about 0.996 and a BETA of 300 to an ALPHA of almost 0.996677.

The other important parameter of leakage I_{co} , the base collector leakage, can be read directly from the curves of Fig. 4 after I_{bo} and BETA have been measured.

General purpose consumer equipment such as hearing aids, portable radios and auto receivers are using transistors having BETA in the 20 to 100 range. A few types with BETA above 100 have been introduced. One Transitron unit has a design center BETA of 180. After a little experience the service engineer will know the approximate gain required for the several popular transistor circuits in radio receivers and industrial applications.

SIMPSON MODEL 382 HORIZONTAL SYSTEM ANALYZER

by R. Patejunas
and P. DePaolo

THE Model 382 contains two separate circuits to perform its functions as a Horizontal System Analyzer and Capacitor Tester. With the function switch in the "SHORTS" position, the circuits are arranged to test horizontal systems, flyback transformers and yokes for shorted turns. The other positions of this switch are for checking continuity and for measuring capacitance.

Short Tests

A 6K6 tube is used in a self rectifying oscillator circuit similar to that of a grid dip meter but used in a manner which causes the meter indication to be largely a function of the "Q" of the external device attached to the test leads. When a component or group of components (a horizontal system) is connected to the test leads, and either one or more of the components is shorted or contains shorted turns, power is drawn from the oscillator and feedback from the plate circuit to the grid circuit is reduced. This reduction in the energy fed to the grid reduces the grid current and the microammeter which is measuring the grid current drops down scale. This is only true if shorts are present in the component (yoke, or flyback transformer) or group of components being tested. (See Fig. 5).

It should be pointed out that there may be cases where very high "Q" components are tested. This applies in particular to a high efficiency deflection system and its component parts (yokes and flyback transformer). The Model 382 is adjusted so that the pointer is set to the ADJUST mark on the meter. The clip leads are then connected to the yoke or flyback transformer and the meter actually goes up scale or even "off" scale. This is completely normal

[Continued on page 54]


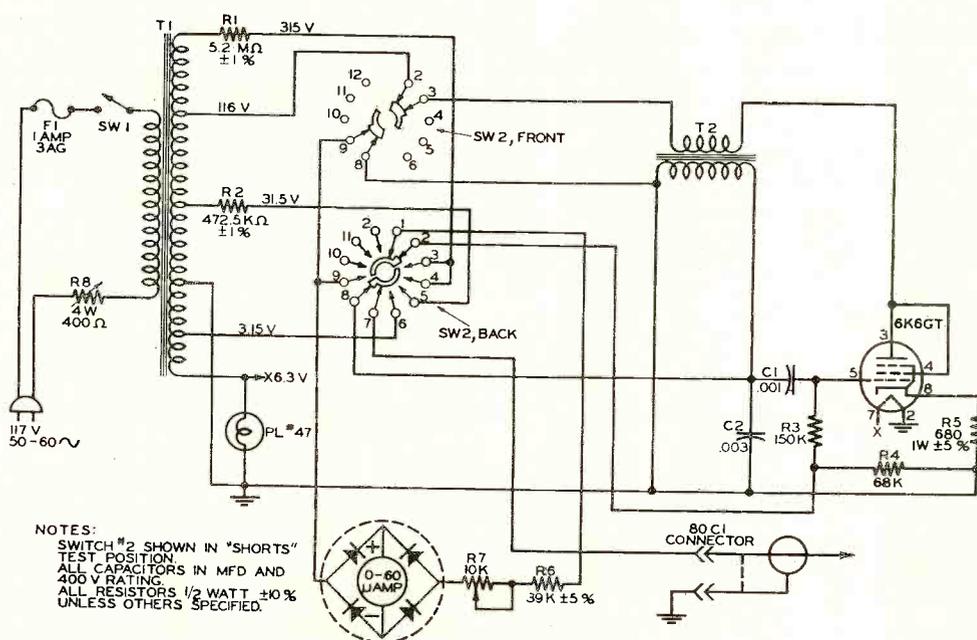


Fig. 5—Schematic diagram of Simpson Model 382 Horizontal System Analyzer.

CHANNEL MASTER "SHOWMAN"



Channel Master Corp. announced a radically new indoor antenna, the Showman. The Showman is specifically designed to overcome the principal consumer objections to "rabbit ear" antennas, which may be unsightly with clumsy maneuverability. It is smartly styled in the latest fashion mode. A wide range of elegant color combinations offers the consumer an opportunity to match the antenna with their specific decor.

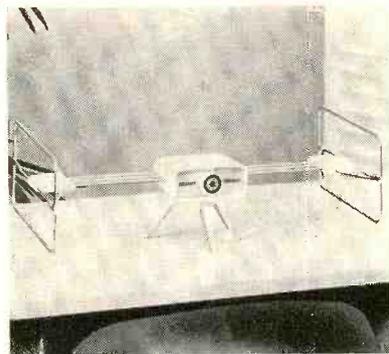

ELECTRONIC SERVICING NEW ANTENNAS

TELREX "QUICKIE"

Telrex Labs. announced its new high-performance "Conical-V-Beam" designed for the replacement-market as a low-priced, good-quality, durable, simple-to-install TV antenna. As its name implies "Quickie" is easy to assemble and quickly installed. This low-price, all-aluminum conical is rugged in design and has no plastic substitutes. Butterfly clamps are all-aluminum. The elements are doweled tubular, and position automatically.

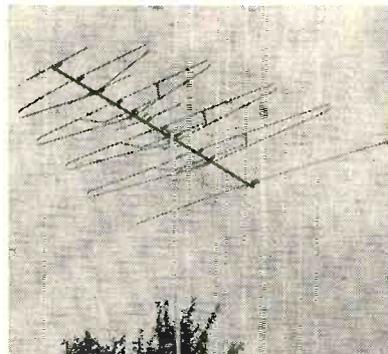
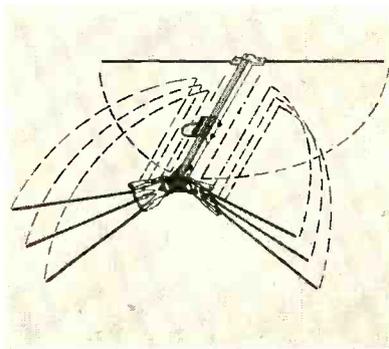


TV ANTENNA

The Trio Manufacturing Company announces the introduction of their new 1957 Zephyr Royal TV antenna which incorporates a new antenna development known as the "Wing" director. The "Wing" director is designed to enhance the power and sensitivity of the "Wing" dipole—a Trio innovation last year. The Zephyr Royal is manufactured by Trio Manufacturing Company, Griggsville, Illinois.

JERROLD "TRAP-EASE"

The Jerrold "Trap-Ease" is a tunable "deep-notch" antenna trap (greater than 50 db) that permits TV viewers to remove "beat" or "herringbone" patterns caused by strong adjacent channel sound or video carriers. Trap-ease works with any TV receiver and any 300-ohm antenna that would normally bring in pictures from the distant stations if the interfering adjacent channel were not on. Regular reception is not affected by the unit.

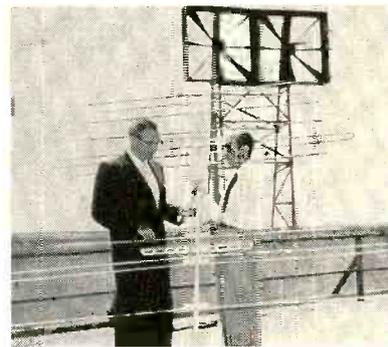
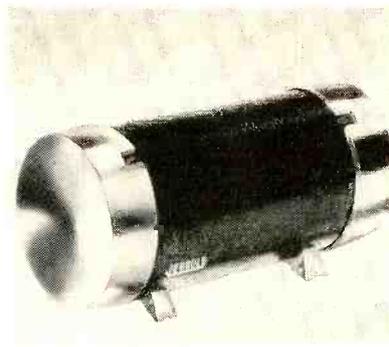


WALSCO FRINGE ANTENNA

Impressive performance reports from Walsco engineers are focusing attention on Walsco Electronics Corporation's latest entry in the super-fringe antenna field, the new "Super Wizard." Successfully completing a series of severe tests in extremely remote fringe areas, the developers claim it to be the first major antenna to overcome the reception problems of difficult locations once considered impossible for good reception.

SNYDER'S "ELDORADO"

A high-style advance-engineered auto radio antenna which can be easily adjusted to fit the lines of any automobile and which is designed either for fender mount or twin rear-deck installation, is on the market under the name of the "Eldorado," a product of Snyder Mfg. Co. The "Eldorado," a gleaming triple-chrome plated antenna with a die-cast base assembly and super-mount fits snugly either on a front fender or on rear decks.

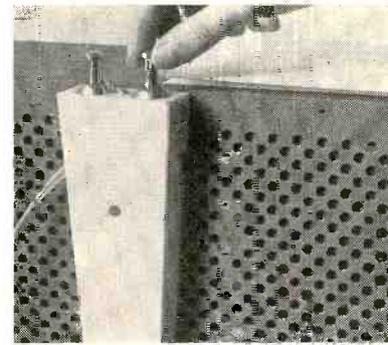
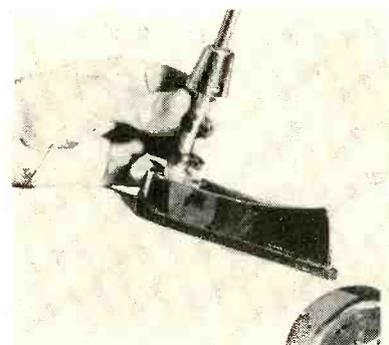


JFD SNORKEL-TENNA

A new miniature television antenna was announced by JFD Manufacturing for improving reception of portable, table and console television receivers. Featuring 4, 5 or 6 telescoping sections the Snorkel-Tenna measures as little as 7 $\frac{3}{4}$ " tip to tip when closed. Encased in a sturdy colorful injection-molded high-impact styrene housing, the Snorkel-Tenna mounts permanently to the back of any TV receiver in a matter of minutes.

TACO "EXTRA-GAIN" ANTENNAS

Taco distributors are introducing the new Top-liner antenna made by Technical Appliance Corporation. The antennas represent a complete departure from previous broad-band antennas, with resulting higher gain and better all-around electrical characteristics. One outstanding feature is the streamlined, compact design that not only looks better when installed, but also has a very definite mechanical advantage in minimizing wind resistance.

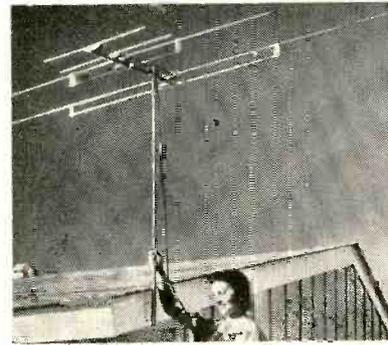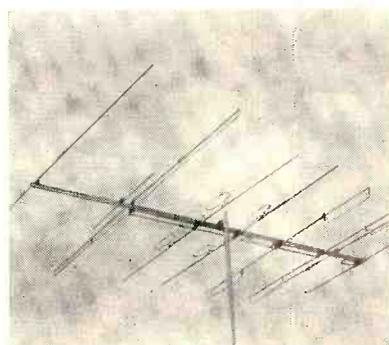

WINEGARD COLOR BEAM

A new "install-it-yourself" outdoor TV antenna manufactured by Winegard is completely assembled, attractively packaged, and ready for customer installation. The Color Beam comes with lead-in clip, insulators and all other necessary parts all attached—nothing to assemble—nothing to put together. Designed to meet the technical demands of color reception, the Winegard Color Beam is guaranteed to improve black and white pictures.

Radio Section of Port-O-Rama Models

Power for the radio is derived from the TV receiver's power supply when the function switch is turned to radio. The radio chassis consists of a 6BE6 converter, a 6BA6 as an *if* amplifier, a crystal detector, and uses the audio portion of the TV receiver. When in the radio position, the function switch removes the B supply from the sweep circuits and connects the *rf* radio antenna coil to one side of the self contained, telescopic, four section antenna. This arrangement not only provides adequate signal pick up but reduces power consumption and eliminates a possible source of internal interference.

Deluxe Series

All of the models in the Deluxe series are 21" receivers incorporating a full power transformer chassis (5U4GB rectifier tube and parallel connected filaments), and the new Standard Coil Neutrode type tuner for superior signal to noise ratio and trouble free operation.

Picture Stabilizer Control and I.F. Noise Inversion

A noise inverter is generally used to provide maximum sync protection in electrically noisy, weak signal areas. This is accomplished by cancelling out all noise pulses which are of greater amplitude and in the same polarity as sync pulses.

Figure 5 shows an *if* type noise inverter circuit used by Emerson. A

manually operated picture stabilizer control not only sets the proper level of noise inversion for various areas but also limits the peaks of the noise pulses as described earlier (Part one.) (Fig. 3 picture stabilizer control). The operation of the noise inverter circuit is as follows. The screen circuit of V-3 is not fully by-passed due to the relatively low value of capacitor C-2 (68 μ F). The screen circuit therefore, acts as a video detector. V-3 is neutralized by C-1 rather than by the choice of a proper screen by-pass condenser as used for the 1st two *if* stages. With approximately 150 volts applied to the screen, the curve of screen current versus grid voltage is such that very little video information is detected, but all noise pulses (which are of the same polarity and greater in amplitude than the sync pulses) are greatly amplified. This results in a noise pulse to video information ratio at the screen grid of approximately

SERVICING 1957 EMERSON

The second portion of this illuminating discussion on servicing Emerson TV receivers considers the circuitry of the noise inverter, picture stabilizer and amplified pulsed agc stages.

PART 2

seventeen to one. These detected noise pulses, which are of *negative* polarity, are fed through resistor R-1 to one side of the picture stabilizer control (R-2) while regularly detected video information containing noise pulses of positive polarity are fed through R-5 to the other side of the picture stabilizer control. These noise pulses subtract within the picture stabilizer control with the result that all noise pulses which originally were of the same polarity as the sync but of greater amplitude are now reduced, eliminated, or even made negative going depending on the setting of the picture stabilizer control. By reducing or eliminating these high level noise pulses, the sync separator tube will be able to function properly resulting in very stable sync performance. The wave shapes indicated in Fig. 5 are exaggerated for clarity and would not actually appear on an oscilloscope unless the output from the

video amplifier were disconnected when viewing the screen waveshape, and the output of the V-3 screen circuit were disconnected when looking at the video amplifier's contribution to the picture stabilizer control.

Eldorado Series

There are six models in the Eldorado series, three of which are UHF-VHF receivers. This series was designed for superior operation in all signal areas (very strong signal areas, extremely weak electrically noisy signal areas, and areas with adjacent channel interference problems). To accomplish this end, a great deal of emphasis was placed in the design of the pulsed amplified *agc* circuit, the automatic noise inverter, the sync amplifier and separator circuits, the horizontal *afc* system, and the *if* system. The Eldorado models incorporate a die cast front which not only acts as the mask but also as the picture tube and chassis support. Because of this self contained construction, these models can easily be used for all sorts of custom installation.

The complete chassis assembly (picture tube and die cast front) are easily removed from the cabinet as a single unit. When out of the cabinet, many more components are accessible for replacement purposes without having to remove the chassis section or the picture tube from the rest of the assembly.

Amplified Pulsed AGC Circuit

An effective *agc* circuit is one which automatically adjusts the gain of the receiver to maintain uniform contrast over wide variations in received signal strength. To do this, the *agc* voltage

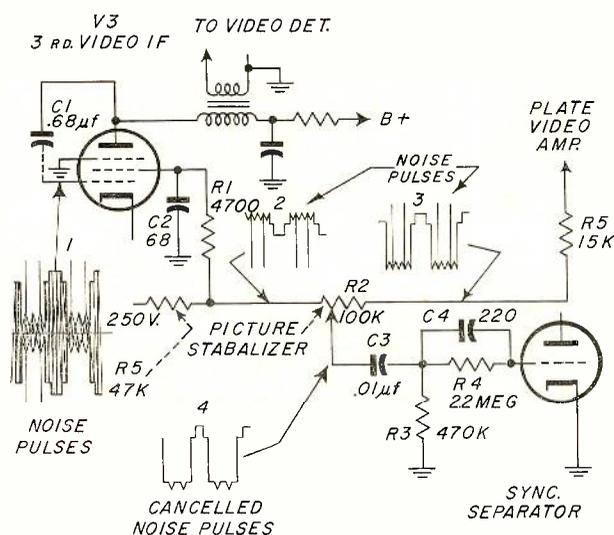


Fig. 5—Noise Inverter and picture stabilizer control circuitry.

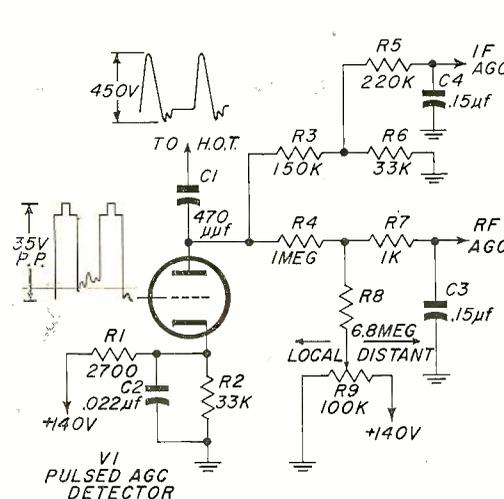


Fig. 6—Emerson Amplified, pulsed agc system with local-distance control.

RECEIVERS

by HAROLD BERNSTEIN
Service Manager,
Emerson Radio Phonograph Corp.

should be able to vary from a few tenths of a volt negative to about sixteen volts negative and be dependent only on the strength of the actual incoming signal and not noise. A straight amplified *agc* system can provide the necessary wide variation in voltage, but since a pulsed amplified system samples *only* the horizontal sync pulse amplitude, it is not as affected by noise or the type of picture information being transmitted and is therefore superior to the ordinary non-keyed *agc*. The pulsed amplified *agc* circuit used in these receivers is shown in Fig. 6. A horizontal fly-back pulse is fed from the horizontal output transformer to the plate of the pulsed *agc* detector through capacitor C-1. The cathode voltage, and therefore the grid to cathode bias, of V-1 is set by the ratio of resistors R-1 and R-2 and is designed to keep the tube cut off during the absence of the fly back pulse on the plate. The fly-back pulse at the plate and the sync pulse at the grid will be applied at the same time. During this time V-1 can conduct and C-1 will charge to a value depending on the amplitude of the sync pulse and that of the fly-back pulse. Since the amplitude of the fly-back pulse remains constant, the charge on C-1 will depend only on the amplitude of the sync pulse, which is directly related to the received *rf* signal strength. During video time there is no horizontal fly-back pulse present on the plate of the *agc* detector and therefore the tube will not conduct. Noise pulses during this time, or changes in picture content cannot affect the *agc* voltage. During tube cut off C-1 discharges through resistors R-3 and R-6, developing the *agc* voltage. Almost all

[Continued on page 55]

GUIDE

AUTRONIC-EYE[®]

TRAINING COURSES

MEAN MORE

BUSINESS FOR YOU!




Courses for experienced service technicians provide latest repair information—enable you to do the job faster and more efficiently.

Quick, accurate circuit diagnosis and repair to factory specifications boosts your profits. That's why so many qualified auto technicians attend these Guide training courses at no cost other than transportation and living expenses.

The Guide Lamp diploma, awarded only to those who successfully complete the course, is proof that you're equipped to give more and better service to more people—and that means business.

If you're an auto radio service dealer, come yourself, or send your technicians. There's one of 30 GM Training Centers near you. Apply through your local United Motors Service Division Distributor or write

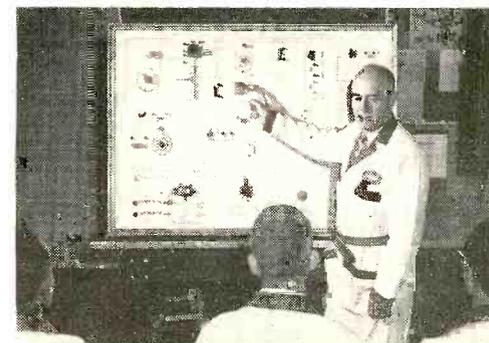GUIDE LAMP DIVISION • GENERAL MOTORS CORP. • ANDERSON, INDIANA



Jumbo-size operational panel of Guide's Autronic-Eye Circuit puts all parts out front for better, more efficient instruction.



Thirty modern GM Training Centers offer newest equipment and latest service techniques. There's one nearby... no matter where you live.




BLINKY MEANS BUSINESS!

ELECTRONIC SERVICING

Hi-Fi — P.A. — AUDIO


MAGNETIC TAPE PLASTIC LEADER

A new plastic leader and timing tape featuring a special anti-static coating and a 50% increase in strength has been introduced by Minnesota Mining and Manufacturing Co., St. Paul, Minn., for use with magnetic tape. To be spliced to the beginning and end of a reel of magnetic tape, the new non-magnetic tape provides a tough protective leader that makes for easier tape thread-up and prevents damage to the recorded material.

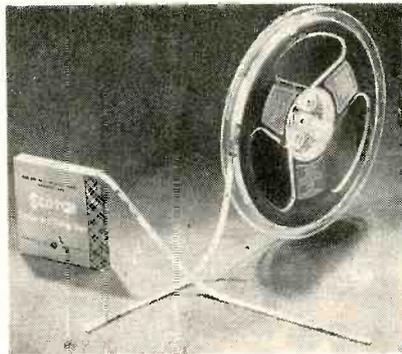


ELECTRIC MEGAPHONE SYSTEMS

University Loudspeakers, Inc., White Plains, New York, announces two new self-contained systems for soundcasting, embodying advanced design and exclusive features to produce compact, efficient and lightweight units. The two models, Portable Powerpage (PP-1) and Pistolgrip Powerpage (PP-2) fill practical applications of outdoor and indoor soundcasting for self-contained equipment. Both PP-1 and PP-2 are powered by flashlight cells.

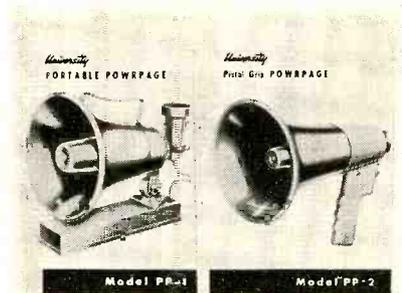



60 WATT HI-FI AMPLIFIER KIT

Featuring the ACRO TO-330 output transformer, the new HF60 power amplifier is the latest in the EICO line of 52 instruments and HI-FI in kit and wired form designed and manufactured by Electronic Instrument Co. of Brooklyn. The circuit comprises an EF86 low-noise voltage amplifier direct-coupled to a 6SN7GTB cathode-coupled phase inverter which drives a pair of ultra-linear connected push-pull EL34 output tubes.

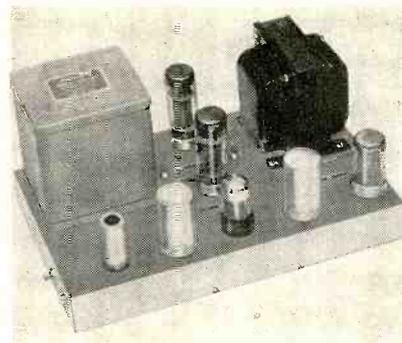


FM/AM TUNER-PREAMPLIFIER

Bogen FM/AM tuner-preamplifier Model R775 provides ease and accurate FM tuning through the Bogen Auto-Lock Tuning Circuit according to Bogen. This unit makes precise adjustments for accurate reception and then locks into position. No station "drift" is claimed, or the chance of a strong broadcast signal dominating the *a.f.* control because it does not operate until a station is selected. FM sensitivity is 2 microvolts for 30 db of quieting.

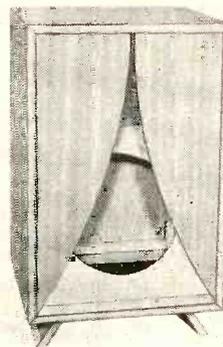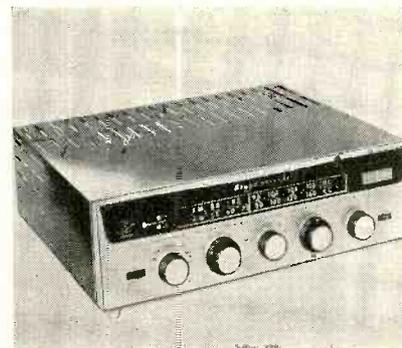


TRANSDUCER ENCLOSURES

A completely new '57 series of Karlson Transducer enclosures, including kits and assembled unfinished models with hardwood exteriors capable of fine furniture finish, has been announced by Karlson Associates, Inc., of Brooklyn, N. Y. All the enclosures in this new series offer improvements in performance based on the establishment of new testing techniques aided by an entirely new type of microphone which permits precision measurements.

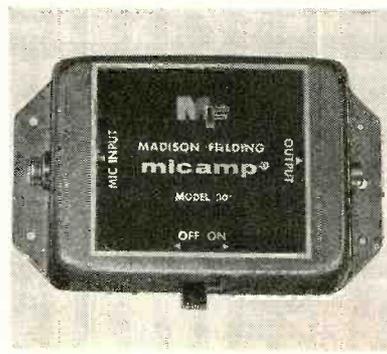


MICAMP MATCHING AMPLIFIER

The Micamp announced by Madison Fielding Corp., of Brooklyn, N. Y., will find application in Hi-Fi systems where the problem of matching a low-impedance output to a high impedance amplifier has hitherto been resolved by a transformer. In addition to providing a 30 db gain from input to output there is an absolute zero in hum. Micamp permits the use of high quality, low impedance mikes with tape recorders and high fidelity systems.

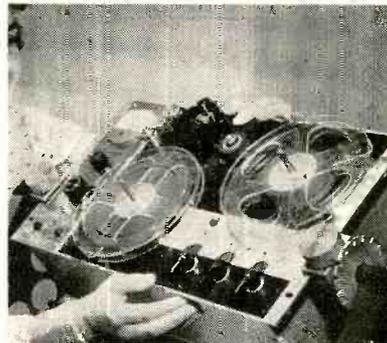

TRANSISTORIZED TAPE RECORDER

Transistorized hi-fi magnetic tape recorder for home-assembled music systems and industrial sound systems has been placed on the market by the Radio Corporation of America. RCA-developed instrument SRT-2 shown in the display rack is a tape recorder-reproducer chassis incorporating such design advances as transistors, printed circuitry, and electrodynamic operation which eliminates parts formerly required to change speed and direction.

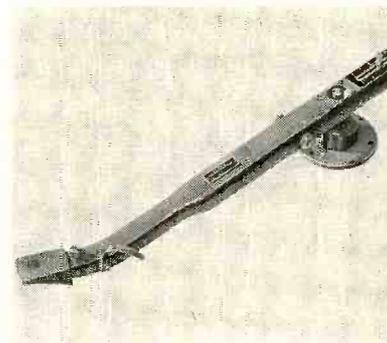

tone ARM KIT

The Audak Company announces that a tone-arm has been successfully engineered specially for a do-it-yourself kit. This new Audax kit consists of only 3 basic parts which anyone can assemble in about 10 minutes into a complete professional tone-arm which exactly duplicates the Audax transcription arm. Simplicity of design eliminates spurious responses. The arm weight is supported on a needle-point. Hence the name "compass-pivoted" arm.



NEW EQUIPMENT CONSOLE

Electro-Voice, Inc., Michigan announces a newly designed equipment console and bench. The Model 890 console enclosure measures 54" x 16" with a depth of 17 1/4". The center storage compartment will accommodate any size line amplifier. The front panel of the compartment can be removed for conversion to record storage or for installation of an 8" speaker enclosure. The record changer drawer slides forward at a convenient operating height.

There
is a
faster
way



to **SPEED SERVICING!**



Time is money to servicemen. Thousands of servicemen who have bought Vol. 1 VSSS report that it is a time-saver which helps them pinpoint their trouble-shooting so they can service sets more efficiently.

A compilation of specific receiver service repairs, "bugs," chronic troubles, field circuit changes, manufacturers' production revisions, etc. The compilation enables the service technician to pinpoint what is wrong with any given TV set and to correct the fault in the shortest possible time.

Video Speed Service Systems is guaranteed to simplify servicing all TV sets. Contains over 600 service items representing over 2500 of the most serviced TV models now in use. Over 25 different manufacturers' lines are covered.

CUT OUT AND MAIL

COWAN PUBLISHING CORP., 300 WEST 43rd STREET, NEW YORK 36, N. Y.

Please send me postpaid Video Speed Servicing Systems

- Vol. 1 in Paper Bound Edition for \$2.95
 Vol. 1 in Hard Cover Ring-Binder Edition for \$4.95
 Vol. 2 in Paper Bound Edition for \$2.95

My Check for \$..... is enclosed.

Name.....

Address.....

City..... Zone..... State.....

AUTO RADIOS [from preceding page]

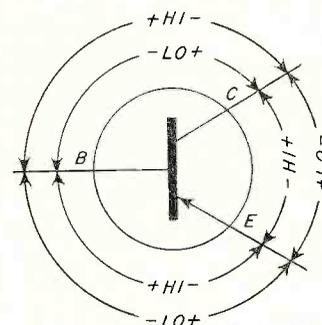


Fig. 1—Resistance check guide for PNP transistors.

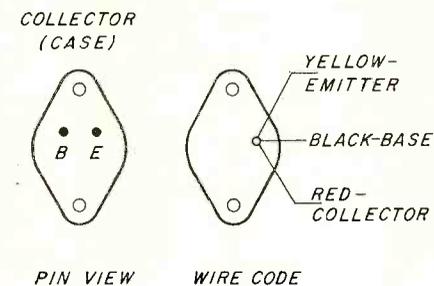


Fig. 2—Base and wire connections used in two types of Philco transistors.

tion is tuned in.

Power transistors can be rough-checked by battery operated ohmmeter resistance readings, as indicated in Fig. 1. It is of utmost importance that the polarity of the ohmmeter leads be known, and that the proper polarity be observed in applying these leads to the transistor. The resistance in the conduction direction is very low compared to the resistance in the nonconducting direction. Low readings are 10 to 100 ohms and high readings are 100,000 to 10 megohms. Checks which show lower readings than these indicate faulty, shorting transistors.

When making the bias adjustment after replacing the transistor, always use a fibre tool. Shorting the base of the transistor, which is connected to the control rotor, to ground, will destroy the transistor. Before applying power, center the control rotor and connect a *dc* voltmeter from the heat sink to chassis. With power on, adjust model C-5705 for 500 ma. or models C-5707 and 5709 for .75 volt bias. Another method is to connect a *dc* ammeter in the collector circuit and adjust model C-5705 for 500 ma. or models C-5707 and 5709 for 750 ma. current.

There are two types of transistors used, as indicated in Fig. 2, and either may be substituted for replacement. Philco numbers are AR5 and AR6, with either pin type connections or color coded wire leads. Where a wire lead unit is replacing a pin type simply follow the yellow and black color coding and solder the red lead to a convenient tie point riveted to the heat sink. In reverse, the pin type can be used with

terminal jacks from a miniature tube socket. When inserted, these jacks must be insulated by a fibre strip to prevent shorting to the heat sink. In every case, be absolutely sure that the transistor body or collector is securely fastened flush with the heat sink and both bolts tight with lock washers.


Important Note—Never use other than battery-operated meters and equipment in the transistor circuit. When soldering is necessary, power must be disconnected from the set. Care must be exercised when soldering both on printed circuit panels and transistor connections, since excessive heat may spoil internal contacts.

The tube circuits can be checked in the usual manner in all but the driver stage. Tubes can be clicked on the grid terminals or removed temporarily for checking. The driver stage, however, must not be disturbed with power on since changes of current will affect the transistor. Substitution of the tube or its associated parts must be done with the power off.

Microphonics in most instances is not due to a faulty driver tube. It has been found that the output required of this tube to drive the transistor, necessitates such close spacing between tube elements, that excessive vibration will cause microphonics. In view of this tapping of the chassis instead of the driver tube would be the better check.

Where the customer complaint is of excessive hum and distortion, it is best to check the bias adjustment and the filter condensers before condemning the transistor. Filters can be jumped across

[Continued on page 55]

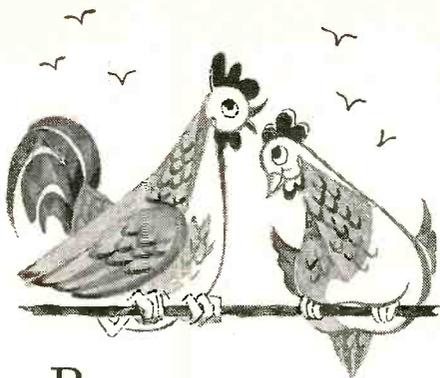


Birds of a feather
flock together,
And so will pigs
and swine;



Rats and mice
will have their choice,
And so will I
have mine.

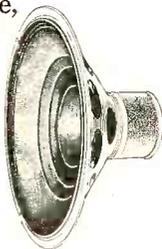My choice is Norelco,
Speakers, of course,
The reason I'm honored
to tell;
Few other speakers are
quite as true,
Or will please you
half as well.



Norelco *F.R.S. Speakers are available in 5", 8" or 12" sizes in standard impedances. Priced from \$6.75 to \$59.98. Blueprints are available for the do-it-yourself enclosure builder. Norelco Enclosures are available in three sizes, priced from \$33.75 to \$119.95.

ADD TO ...and improve any sound system with *Norelco*®
*FULL RESPONSE SPEAKERS

Write today to Dept. E4 for brochures and prices of these unique speakers.

NORTH AMERICAN PHILIPS CO., INC.
100 E. 42nd St., New York 17, N.Y.



Mfr.: Admiral Chassis No. 14YP3B

Card No.: AD-14Y-1


Section Affected: Pix.

Symptoms: Sync instability.

Reason for Change: To improve circuit operation under high contrast levels.

What To Do:

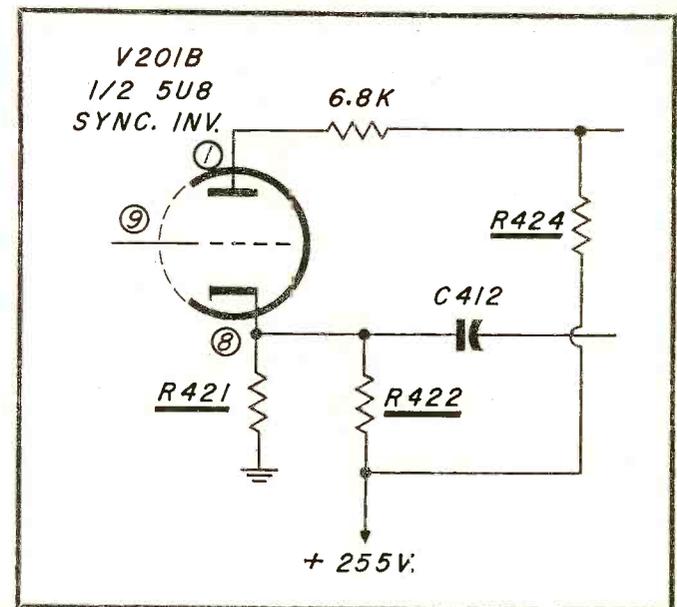Replace: R421 and R424 (4,700 ohms) with 3,300 ohms. R422 (39K ohms) with 47K ohms. This change was included in run 10 through run 12.



Mfr.: Admiral Chassis No. 14YP3B

Card No.: AD-14Y-2


Section Affected: Pix.

Symptoms: Audio distortion.

Cause: Drift, especially during warm-up time.

What To Do:

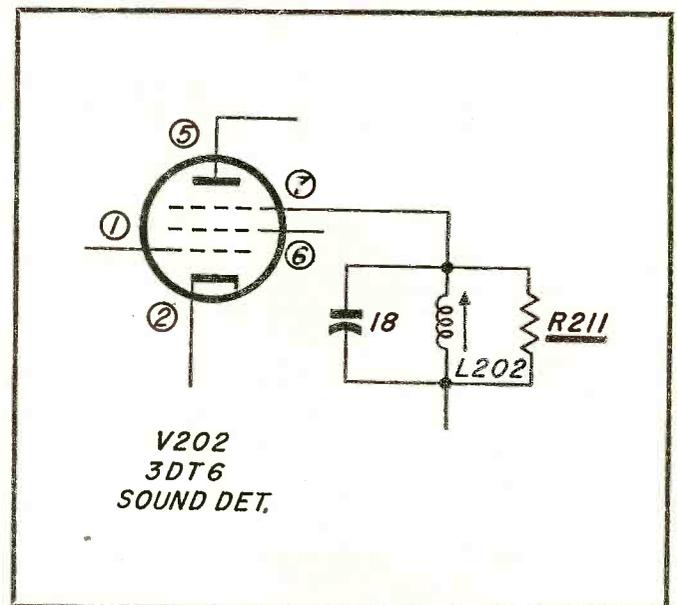Add: R211 (100K ohms) across quadrature coil L202. This change was included in run 10 through run 12.



Mfr.: Admiral Chassis No. 14YP3B

Card No.: AD-14Y-3


Section Affected: Pix.


Symptoms: Horizontal sync instability.

Reason for Change: To prevent frequency drift due to change in capacitance of circuit component.

What To Do:

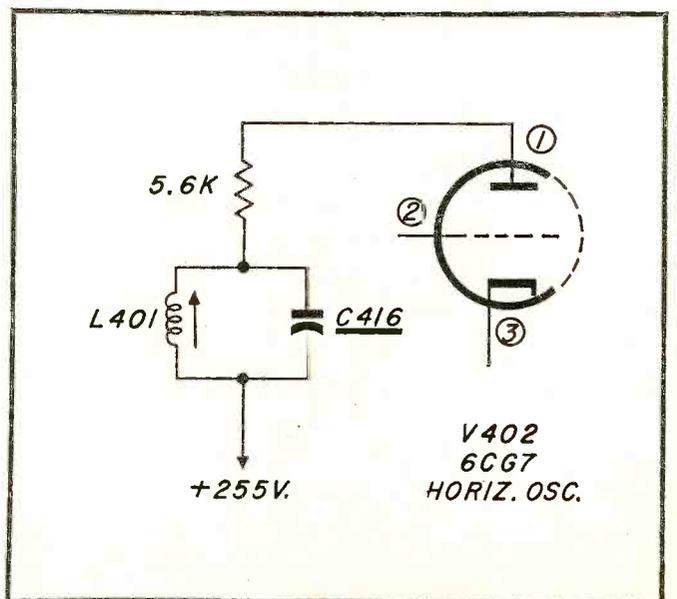Replace: C416 (.0039 μ f) paper tubular type with a mica type. Admiral part number 65B21-392. This change was included in run 10 through run 12.



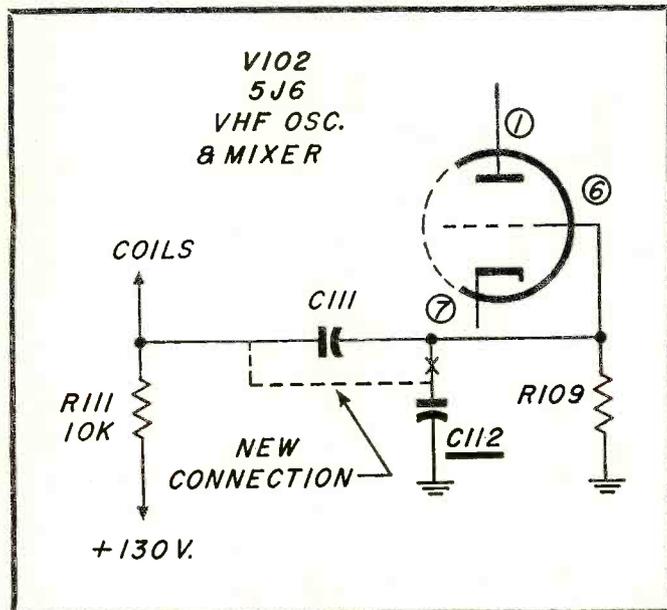

Mfr.: Admiral

Chassis No. 14YP3B

Card No.: AD-14Y-4


Section Affected: Pix and sound.

Symptoms: No picture and sound due to local oscillator not operating.

Cause: Under low line voltage conditions oscillator circuit may cease oscillating due to lowered transconductance.

What To Do:

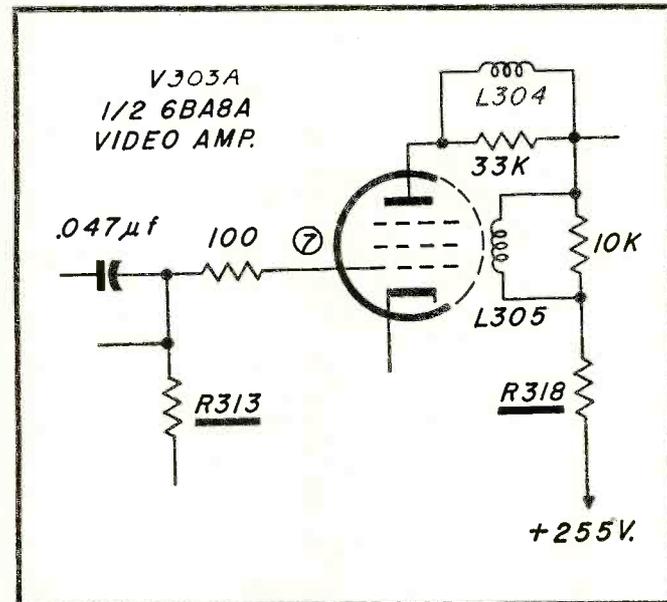Change: C112 (5 μ f) from junction of C111 and R109 to junction of C111 and R111. This change was included in run 10 through run 12.



Mfr.: Admiral

Chassis No. 14YP3B

Card No.: AD-14Y-5


Section Affected: Pix.

Symptoms: Picture turns negative or has silvery appearance at high contrast levels.

Cause: Video amplifier grid and plate resistors may have changed value.

What To Do:

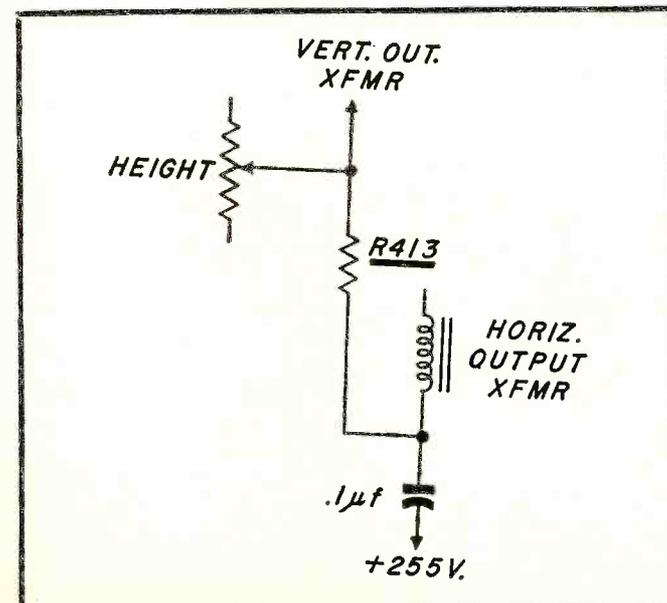Check: R313 (1.3 megohms), R318 (6.8K ohms, 2 watts).
Also picture tube.



Mfr.: Admiral

Chassis No. 14YP3B

Card No.: AD-14Y-6


Section Affected: Pix and raster.

Symptoms: Insufficient height.

Cause: Resistor increased in value.

What To Do:

Replace: R413 (6800 ohms, 1 watt).

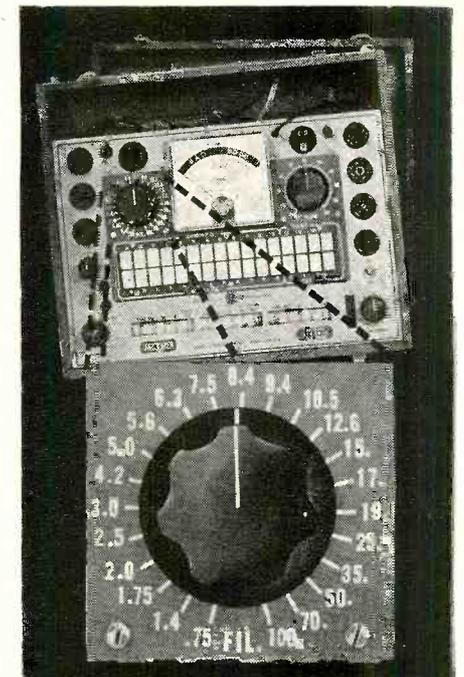

23 Separate
Heater Voltages
on the Dynamic®
JACKSON 648A
Assure Accurate
Tests for all
Series-String Tubes
...The Correct Voltage
for Every Known or
Presently Planned Type.

YOU CAN MODERNIZE YOUR PRESENT 648
New 648 FV Kit provides same heater
voltages as the new 648A Tester. Only
four wires to solder. Installs in minutes.
Available from your distributor now.

JACKSON
ELECTRICAL INSTRUMENT CO.

"Service Engineered"
Test Equipment

16-18 S. Patterson Boulevard • Dayton 2, Ohio
In Canada: The Canadian Marconi Company

NO
MATTER
WHAT
THE
WEATHER...



Hot-and-humid or cold-and-damp...Aerovox "DURAMIC" Capacitors give you "trouble-free" operation even under the most adverse weather conditions. You avoid costly call-backs when you specify-and-buy "DURAMIC" capacitors because the severe-service characteristics are built into each capacitor.

AEROVOX "DURAMICS"

...utilize a dense steatite case to provide exceptional protection against humidity. All terminal lead wires are firmly imbedded into the end seals so that they will not pull out or work loose even under the most severe operating conditions.

AEROVOX "DURAMICS"

...have that exclusive Aerovox end-fill which will not soften or flow nor separate from the case at any rated temperature.

AEROVOX "DURAMICS"

...have excellent power-factor, insulation resistance and temperature characteristics. Operating temperatures from -55°C. to $+85^{\circ}\text{C.}$ Available in 10 standard voltage ratings from 200 to 15,000 VDC.

Your local Aerovox Distributor always carries a stock of Aerovox "DURAMIC" Capacitors in a wide range of capacitance values and voltage ratings. While you're there ask for your free copy of the latest Aerovox Catalog with complete listings of all Aerovox components.



AEROVOX CORPORATION

Distributor Sales Division NEW BEDFORD, MASS.

In Canada: AEROVOX CANADA, LTD., Hamilton, Ont.
Exports: Ad. Autema, 89 Broad St., New York, N. Y. • Cable: Autema, N. Y.

Mfr.: Philco Chassis No. 7E10 and 7E11

Card No.: PH-7E-1


Section Affected: Pix.

Symptoms: Critical horizontal sync.

Reason for Change: To improve horizontal oscillator performance.

What To Do:

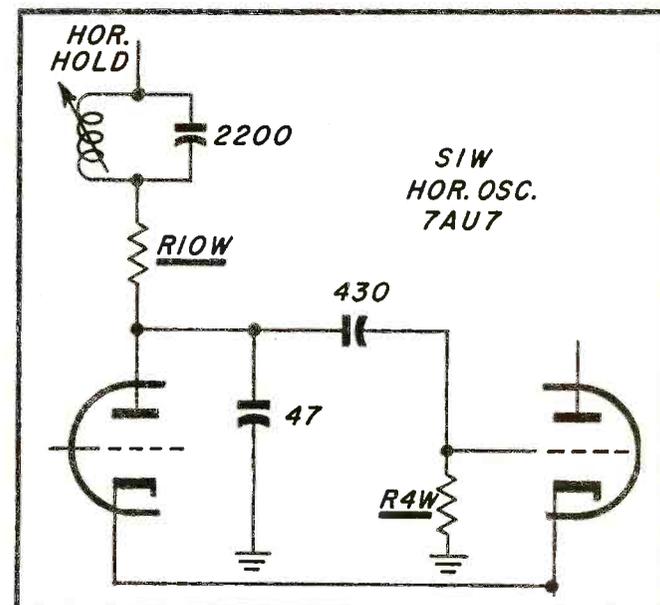Replace: R10W (15K) with 10K, $\frac{1}{2}$ W.
R4 (130K) with 150K, $\frac{1}{2}$ W.



Mfr.: Philco Chassis No. 7E10 and 7E11

Card No.: PH-7E-2


Section Affected: Pix and raster.

Symptoms: Insufficient width.

Cause: Low screen voltage under low line voltage conditions.

What To Do:

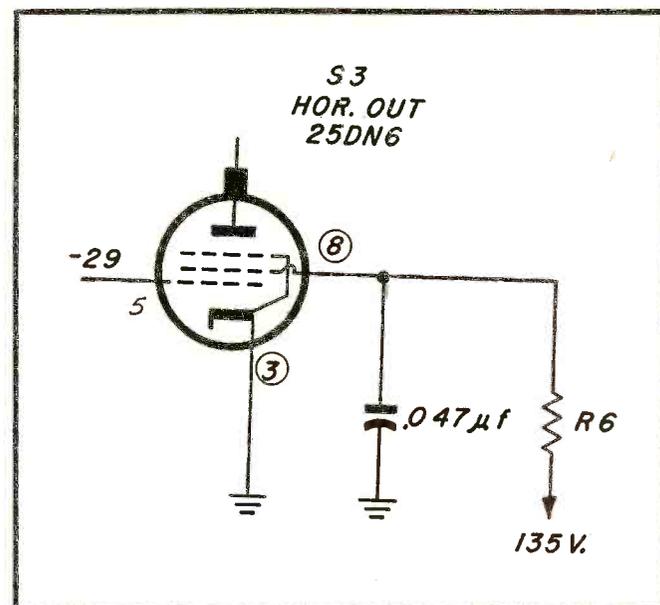Replace: R6 (1500 ohms) with 1200 ohm resistor.



Mfr.: Philco Chassis No. 7E10 and 7E11

Card No.: PH-7E-3


Section Affected: Nearby radios are interfered with.


Symptoms: Tunable whistle in audio output of radio.

Cause: Horizontal deflection voltages are not filtered and prevented from being present on power lines.

What To Do:

Change: C7 (.047 μf) to .1 μf .

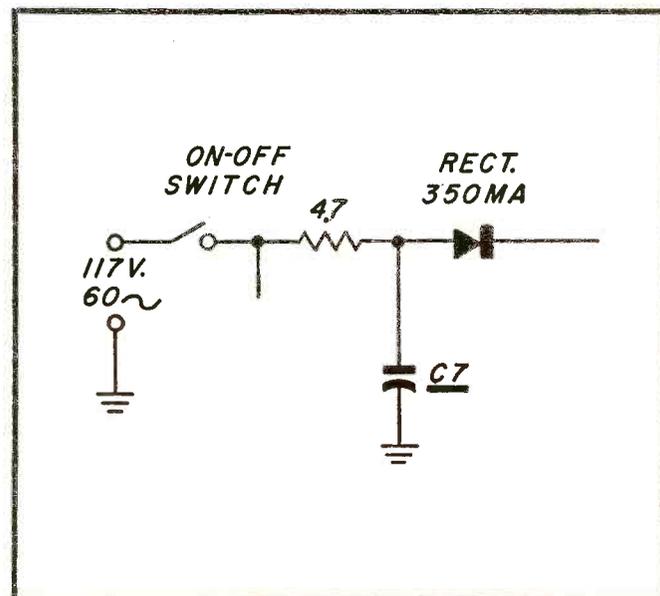

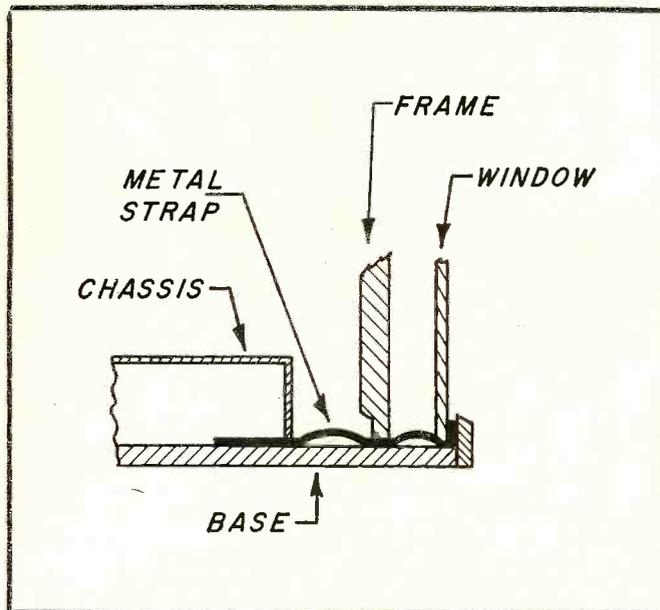

Mfr.: Philco Chassis No. 7E10 and 7E11

Card No.: PH-7E-4


Section Affected: "Popping" noise.

Symptoms: The most probable cause is a poor ground connection from the chassis to metal window frame.

Cause: When the metal ground strap makes a poor contact between chassis, frame and window a static charge is built up on the metal frame and window which causes the popping sound when it breaks across the air gap or poor connection.

What To Do:

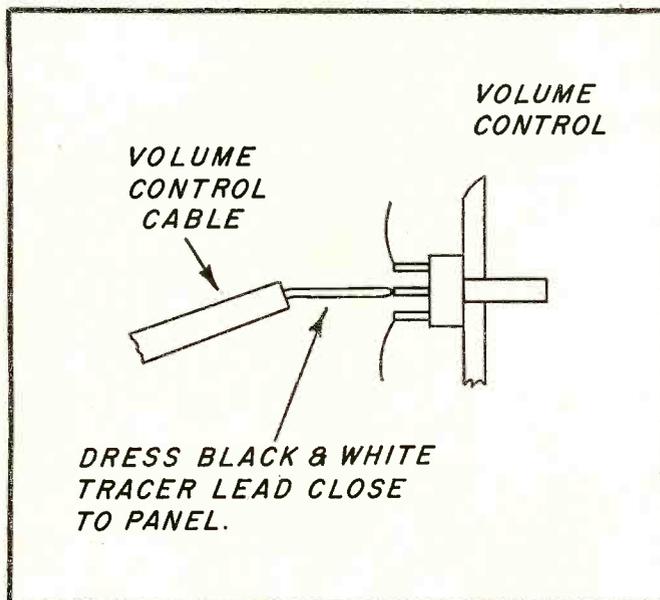Check: Grounding metal strap beneath the bottom rail of the metal frame and the window. The weight of the window will generally cause good connection and hold the strap in place. The other end of the strap should be connected to the chassis by its pressure as it rests on the end.



Mfr.: Philco Chassis No. 7E10 and 7E11

Card No.: PH-7E-5


Section Affected: Sound.

Symptoms: "Squeal."

Cause: Feedback in the audio amplifier grid circuit.

What To Do:

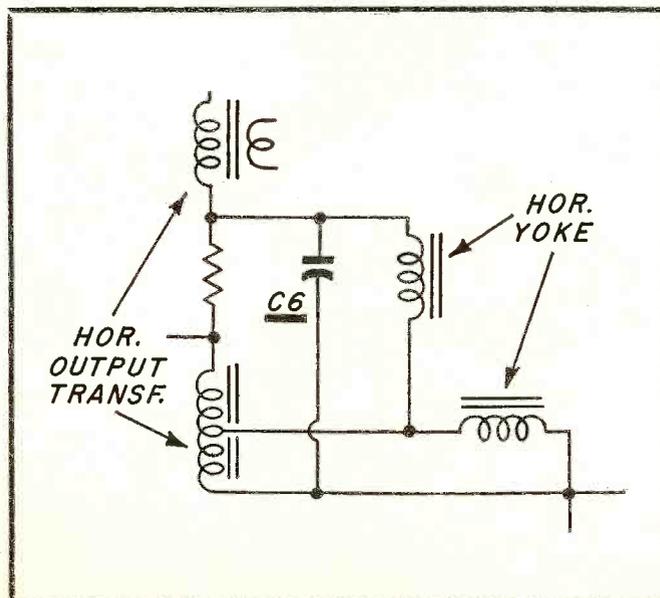Check: Lead dress of inner conductor of the volume control cable connecting the grid of the 5T8 audio amplifier tube to the volume control. Position inner conductor of the cable (black and white tracer) as close to the surface of the panel as possible. In addition to this, tilt the audio couplet, 30-6023, toward the 5T8 tube socket as far as possible.



Mfr.: Philco Chassis No. 7E10 and 7E11

Card No.: PH-7E-6

Section Affected: Pix and raster.

Symptoms: No raster or high voltage.

Cause: Shorted horizontal damping condenser across yoke.

What To Do:


Replace: C6 (82 μ f, 3KV ceramic disc type), Philco part number 30-1246-4.

FOR SOUND SATISFACTION



... use

RCA GOLD LABEL SPEAKERS!

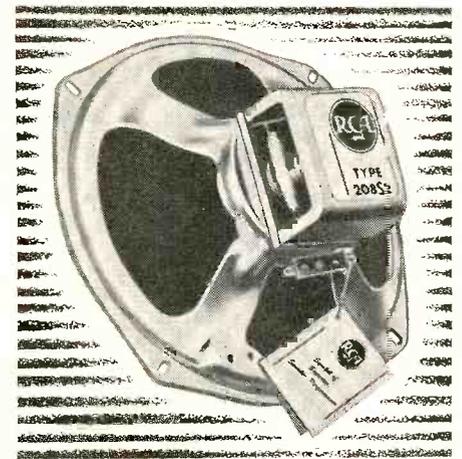

Replace dead speakers with *live* RCA Gold Label Speakers. They're *short* on installation time . . . *long* on customer satisfaction. All types built to RETMA size standards REC 148 . . . mounting hardware is included on most smaller sizes . . . For *all* your speaker requirements . . . play it smart and safe! Be sure you ask for RCA Gold Label Speakers . . . at your local distributor.



RADIO CORPORATION of AMERICA

COMPONENTS DIVISION

CAMDEN, N. J.

SELL SERVICE

WITH EFFECTIVE ADVERTISING

PART 1

By M. E. WIRT

You are a professional television technician. You probably spent some time in an accredited school learning your profession, have studied many hours on your own time to keep up with the almost daily advances made in television, and are equipped by knowledge, skill, and experience to repair any make or model of television receiver with a minimum of delay and "out of use" time.

Now—you know this, we know this, and probably a few of the customers whose sets you have repaired know this, but who else knows it? Probably darn few, if you don't advertise, or don't advertise properly. It is the purpose of this article to show you some of the more effective ways to sell your service through advertising, and every one of them has proven its merit in actual use. So don't just read them and forget them—apply them!

The first thing to bear in mind is that you must, in some way, "individualize" your advertisement. It is necessary to see that *your* particular advertisement stands out from the many who will be using the same basic style or format. Don't just head up your advertisement in the newspaper, for example, with something like "TELEVISION SERVICE" or "RADIO AND TV SERVICE." Look at the rest of the ads; they say substantially the same thing, and if a potential customer is searching for TELEVISION SERVICE, why repeat the original heading? The name of your concern might be something like UNITED TELEVISION SERVICE or BILL JONES TV SERVICE. But whatever it is, the thing to push is *your* name, the name of the man in charge of your service

department, or the name of the man who does the actual bench work.

The next thing to do is to make your advertisement **DIFFERENT**. The old saying that "brevity is the soul of wit" can also be applied to advertising, but remember that the **DIFFERENT** advertisement catches the eye. Don't let your ad follow the same lines as all the rest. Use a little imagination in not only the composition of your ad, but also in the way in which it is displayed or presented. Not only that, but don't tie yourself down to only one form of advertising. Many ways of advertising are available to you, among them being newspaper, (probably the most effective for service if used consistently), radio, television, direct mail, circulars, envelope stuffers, handbills, and the telephone directory "Yellow Pages." Last, and best of all, is word-of-mouth advertising, and this is entirely dependent on your service quality.

So now you've made your advertisement both *personal* and *different*. What's next? Let's try **TRUTH**. You wouldn't want to make a statement that wasn't true concerning some phase of your work or a repair job you have done; the same sense of ethics won't let your advertisement mislead anyone, even by implication. Don't use "half-truthful" statements that may be taken more than one way. It isn't fair to the customer to make them believe one thing when you mean another, and it isn't worthwhile "sales-wise." You may fool them once—but if they feel they've been "had," never again.

There is another facet of advertising which is sometimes used, sometimes unused, and sometimes mis-used, but

[Continued on page 51]



American


Now... look to **ELGIN** for research, design and manufacturing leadership

American's **FULL VISION**—**FULL SOUND** audio equipment now comes to you from Elgin! Warehouse and service facilities are being maintained in California, of course; but manufacturing and product development have been moved to Elgin to work hand-in-glove with Elgin's well known styling and electronics research experts. You can expect the best... in appearance and performance... from American Microphones.

Does your equipment require a specially designed microphone? American is now better equipped than ever to help you!



1.

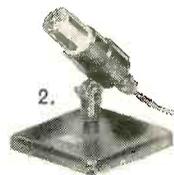

2.

an American Microphone
for every use!



3.



4.



5.



6.

FOR BROADCAST QUALITY

1. DR330 Cardioid Dynamic and Ribbon Microphone meets strictest requirements of tv-radio broadcasting and motion pictures.

2. Presidential Series Dynamic Omni-Directional Microphone is rugged, compact, quickly converts to 6 oz. hand microphone.

FOR RECORDING AND GENERAL P. A. USE

3. D22 Dynamic Omni-Directional Microphone is a beauty queen—and dependable too. Quickly converts to hand use.

FOR TAPE RECORDERS

4. Versatile microphone is designed for hand or desk use, weighs only 2 ounces, yet gives outstanding performance.

FOR SOUND-POWERED TELEPHONES

5. No external power source required for this lightweight, sensitive unit. Rugged and extremely versatile.

FOR RUGGED, DEPENDABLE OUTDOOR MICROPHONES


6. A mobile microphone that resists moisture. Ideal for ship-to-shore and aircraft installation. High output, shock resistance.

ELECTRONICS DIVISION

ELGIN NATIONAL WATCH COMPANY

107 National Street, Elgin, Illinois

FOR A
brighter

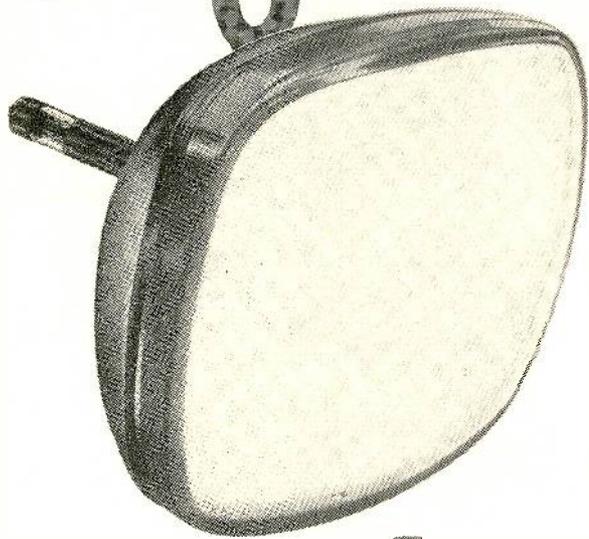

TV
picture

Rely on the tube that has always been specified by leading independent set makers.

Blue Chip Quality
TUNG-SOL®
Magic Mirror Aluminized
PICTURE TUBES

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Ga.; Columbus, Ohio; Culver City, Calif.; Dallas, Tex.; Denver, Colo.; Detroit, Mich.; Irvington, N. J.; Melrose Park, Ill.; Newark, N. J.; Seattle, Wash.

Over 8.4 million radios, excluding automobile receivers were shipped to dealers during 1956, RETMA reported—an increase of more than 1.3 million over the number of receivers shipped in 1955. During December, 1,544,987 radios went into the hands of dealers, compared with 797,011 radios sent to dealers in November and 1,273,181 units shipped in December 1955.

Nearly 7.1 million television receivers were shipped to dealers during 1956 to become the fourth highest year on record. During the last year, 7,028,456 TV set moved into the hands of dealers, RETMA reported, compared with the all-time high of 7,421,978 in 1955, and 7,161,362 and 7,078,000 in 1954 and 1950, respectively.

Bill Ashby, well-known expert and lecturer on TV servicing, is again on an extended tour of the country with his Radio-TV Clinic. Underwritten by the Cornell-Dubilier Electric Corporation and sponsored by local Parts Distributors, the Clinic is scheduled for most of the major cities in the U. S.

Servicemen who have already attended Clinic meetings have found them unusually helpful. The Clinic features Bill Ashby's famous "Chalk Talk"—a unique blackboard presentation, based on the use of cartoons and sketches that simplify complex problems. The "Chalk Talk" is followed by a question and answer period that gives every serviceman the opportunity of asking the questions that so often go unanswered at meetings of this sort.

Multi-Tron Laboratory, this week unveiled the first basic design change in Cathode Ray Tubes since the introduction of electrostatic focusing and deflection. The new tube, called the "Pure Signal" Tube, is of "multiple beam" design, and it is claimed, takes a signal directly from the crystal detector, completely eliminating the necessity for the video amplification circuitry section in any current TV chassis. According to a statement by Nicholas Glyptis, President and Research Director of Multi-tron, and his staff, this "Pure Signal" tube opens the way for full utilization of transistors, as this tube can be transistor driven.

A new line of electronic test instruments in kit form has been launched by the Paco Electronics Company, Inc., a newly formed division of the Pre-

t r a d e

cision Apparatus Company, now celebrating its 25th anniversary. The PACO kits were unveiled for the first time at the New York Radio Engineering Show. They are expected to find wide application in radio and TV servicing, hi-fi custom-building and service, electronic hobbies and amateur radio, science education and technical schools, as well as industrial testing and quality control.

David T. Siegel, 125 Beach Road, Glencoe, Illinois, died suddenly in Palm Beach, Florida, Friday, March 8. Mr. Siegel, prominent in the electrical and electronic industries, was the founder and president of the Ohmite Manufacturing Company, Skokie, Illinois. The firm manufactures resistance products and other electrical components.

Throughout the rapid growth of the firm, which was founded in 1925, Mr. Siegel was closely associated with all phases of the business. However, he never lost sight of the fact that people were important and he was always in the forefront with progressive employee relations and modern facilities.

The Delco Radio Division of General Motors announces the introduction of an all-transistor automobile radio in the Cadillac El Dorado Brougham, Cadillac's new luxury model.

The announcement was made in connection with the annual convention of the Institute of Radio Engineers (IRE) now being held in New York.

Using 13 transistors and three germanium diodes, the advanced set requires approximately 90 per cent less current to operate than a conventional car radio and has an improved reliability factor of at least 50 to 1, according to Delco Radio engineers.

Manual, push button and Wonder Bar tuning are provided as well as a two speaker fader system and an electric antenna which automatically extends when the radio is turned on and retracts completely when the radio is turned off.

The advanced design makes the best use of automatic gain control to provide reception almost completely free of fading problems.

Norman A. Triplett, Executive Vice President of Triplett Electrical Instrument Company, Bluffton, Ohio, announces effective immediately, Norm Edin-

flashes

ger will assume the responsibilities of marketing service manager for Triplett. Mr. Edinger is well qualified to fill this recently created position having spent fifteen years in various phases of the Triplett operation. In announcing the appointment, Mr. Triplett pointed out, "This is only one more step in our program to provide a more personalized liaison between our customers and our factory operation."

A testimonial dinner for Julius Finkel, president of JFD Electronics, Inc., in honor of his 70th birthday, was held at the Hotel Commodore in New York City on March 30, 1957. Proceeds from the dinner will be used for the establishment of the Julius Finkel Free Loan Fund in Israel. A highlight of the dinner was the presentation to Mr. Finkel of a scroll signed by all of his employees.

A unique program of advertising and promotion for the Snyder "Imperial" 10-D single-mast indoor TV antenna has been evolved in this area by Snyder Mfg. Co., Almo Radio Co., Snyder distributor and all the department stores. Tentatively, the plans revolve around initial exclusives to the department stores in the Philadelphia area for an unspecified limited period of time and guaranteed sales by the manufacturer. In addition, the initial announcement of the marketing of the antenna broke here on March 17th over the signatures of all the department stores for the first time in retail history in the Philadelphia area, Mr. Snyder disclosed. Heretofore, he said, the department stores have never joined in sponsoring any one product or line of products in joint advertising.

CBS-Hytron will continue and expand its aggressive support of independent radio-television service dealers across the nation in its 1957 sales promotion program, according to an announcement by John H. Hauser, Distributor Sales Manager, issued from the company's executive offices in Danvers, Mass.

At a recent sales conference with its national sales force, CBS-Hytron, the electron tube and semiconductor manufacturing division of Columbia Broadcasting System, Inc., set up a new approach to the problem of giving effective support to the independent radio-television service industry. The

1957 CBS-Hytron program calls for extensive national advertising augmented by concentrated local promotion aimed at attracting business into the shops of independent service dealers.

Military secrecy has been lifted from a new electron tube that adds might to radio's muscles, allowing these electronic devices to see targets more clearly and farther away. Developed by Raytheon Manufacturing Company under sponsorship of the Army Signal Corps Engineering Laboratories, Fort Monmouth, N. J., the new tube's peak power is equal to that needed to light a city of 200,000 people. Called an "amplitron," the new tube effectively "beefs up" the radar's performance by amplifying or boosting the energy output of the basic signal as much as 8 to 14 times. When added to the air traffic control radars now being built by Raytheon for the Civil Aeronautics Administration, the effective range of these sets will be increased from 200 miles to about 350.


The inclusion of a new permanent dealer aid, the Select-A-File, in RCA's 1957 Spring portable radio battery promotion kit, was announced by L. J. Battaglia, Manager, Marketing Department, RCA Components Division.

"Designed to support the RCA dealer in his biggest battery market year," said Mr. Battaglia, "the Select-a-File is a complete, illustrated, up-to-date source of battery replacement information for practically every portable radio currently in use. Contained in a sturdy steel file box, a data card carries a photograph of a portable together with the manufacturer's name and model, plus the recommended RCA battery complement.

P. R. Mallory & Co. Inc., of Indianapolis announced the unification of its battery activities into a single operation—the Mallory Battery Company. This Company is a division of P. R. Mallory & Co. Inc., with headquarters in Cleveland, Ohio. Officers of the new Company are Fielder Israel, President; Carl Rudiger, Vice President; Walter Onorato, chairman of the Management Committee, and Ray Stone, Comptroller.

The company produces unique mercury batteries, conventional zinc-carbon batteries and a new line of solid state batteries.

FOR A brighter

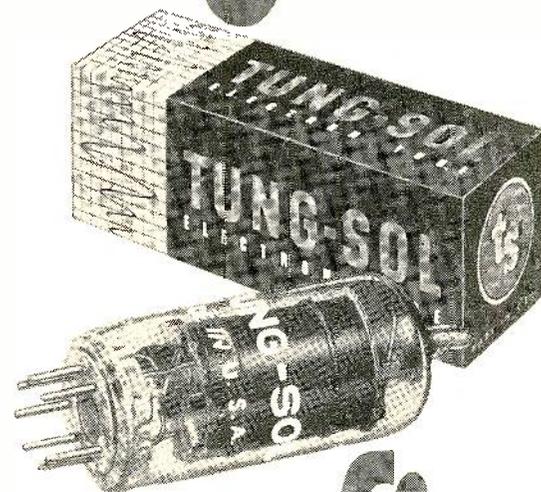

profit picture

Rely on the tube that has always been a favorite with leading independent service dealers.

Blue Chip Quality
TUNG-SOL[®]
RECEIVING TUBES

TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.

CONTACT

This section of **ELECTRONIC SERVICING** serves as liaison office between 1) Manufacturers of Electronic devices who seek qualified service firms capable of acting as their branch service depots, and 2) Technically qualified, financially sound Service Firms or Independent Radio-TV Servicemen who seek to be appointed as Factory-Trained Branch Service Agencies for Electronic Equipments Manufacturers in the areas where they are situated.

Advertising run in this section costs \$15.00 per column inch.

QUALIFIED STAFF OF TECHNICIANS AVAILABLE

All types of Television Service and parts depot including any electronic equipment. Presently doing factory service and parts depot. Indianapolis, Indiana firm.

BOX 1407, ELECTRONIC SERVICING

SHREVEPORT, LOUISIANA SERVICE FIRM SEEKS CONTRACT JOBS TO SERVICE:

Box 1301, ELECTRONIC SERVICING

Three competent technicians with many years' experience in electronics are prepared to accept service contracts and assembly work in light electronic equipment. We have 2400 feet of space available for immediate expansion of our operation.

Newburgh, N. Y. Firm

Box 1302, ELECTRONIC SERVICING

OFFICE, CHIEF SIGNAL OFFICER
CIVILIAN PERSONNEL BRANCH

Room 2C200, The Pentagon
Washington 25, D. C.

OPPORTUNITIES FOR OVERSEA ASSIGNMENT

Item No.	Position Title	Grade	Salary	Location	Allowances	Housing	Qualification Requirements
3	Electronic Engineer	GS-855 - 11	\$6390 p.a.	Verdun, France	10 per cent differential. \$2000 p.a. when with dependents, \$1500 p.a. when without dependents.	Gov't family quarters not available. Concurrent travel of dependents may be authorized depending upon size of family.	Male only. Degree in electrical engineering plus 2½ years of progressive professional experience which must include at least 1 year of specialized experience in the branch of engineering for which applicant is being considered.
5	Supervisory Electronic Engineer (Wire Comm)	GS-855 - 12	\$7570 p.a.	Japan	No differential authorized. Quarters allowance of \$2800 p.a. when with dependents, \$2100 p.a. without dependents.	Gov't housing authorized on a waiting time basis.	Degree in electrical engineering plus 3½ years of progressive professional experience which must include at least one year of specialized experience in the branch of engineering for which applicant is being considered.
6	Equipment Specialist	GS-1670- 12	\$7570 p.a.	Japan	Same as above.	Same as above.	Total of 7 years experience, 2½ years of which must include composing and organizing written info concerning maintenance and operation of radio, radar, electronic instruments, photographic equipment power units, public address and recording systems, etc.

NOTE:

Civil Service status not required for positions in Alaska.

KOREA—Family quarters unavailable. Dependent travel not authorized. Male only. Separation allowance authorized for eligible civilian employees.

OKINAWA—Requests for concurrent travel from Continental United States at GS-9 and above may be applied for on an individual basis.

Further information may be obtained by contacting Office, Chief Signal Office, Civilian Personnel Branch, Room 2C200, The Pentagon, Washington 25, D.C. You may call Mr. Albert G. Crosetto, telephone number LIberty 5-6700, Extension 52525 or Code 131, Extension 52525.

Dated
2-19-57

In addition to these vacancies, there are openings in Washington and in the vicinity of Winchester, Virginia, for teletype installers, repairers and operators, communication code clerks, relay equipment operators, micro-wave technicians, electronic engineers and electronic equipment installers and repairers.

RIDER SPEAKS



JOHN F. RIDER

WERE it NOT true that many publishers release books and magazines which can be beneficial to the home electronics equipment servicing industry, we would never dare write this piece. But since there *are* many, we feel that we can take the chance and not be accused of using these columns for personal gain.

There are many services available in this nation, but we doubt if any of them are as subject to continuous change in technology as is the servicing industry, which has been maintaining the public's electronic equipment. There just doesn't seem to be any limit to the rate at which new ideas appear on the scene and new brain children make these ideas practical realities.

To keep abreast of these technological advances imposes an added burden to those already being carried by the men engaged in this work. But there is nothing that can be done to circumvent it; it just happens to be the nature of the business. Experience is a very wonderful thing, but the skill accrued from experience in electronic technology alone does not appear to be the complete answer.

We recognize that the experienced TV technician would be more successful, generally, in the servicing of television receivers than the average electronics engineer with a formal degree, but without experience. Time is money in this business and it is doubtful whether the average engineer without extensive familiarity with a television receiver could make his theoretical background compensate for the tricks of the trade which the practiced technician has gathered.

Granting all this to be true, does it permit setting a limit on how much theoretical knowledge need be possessed by the service technician? Does the service technician gain anything by imposing a limitation on his theoretical background just because he has the practical experience? Or is it to his distinct advantage to possess the broadest possible theoretical base too? This doesn't necessarily imply engineering schooling. As we see it, it means recognition of the tremendous scope of the activity of which he is part; seeing the great expanse of the horizon of possibilities, and trying to do something about it.

It is said that only death and taxes are certain. No one knows what fate has in store, nor what twisting paths opportunity will present. To be ready for these opportunities cannot help but be important to every one. We hear and read of many forecasts. Each is more glowing than the other in what electronics will do for mankind. Everything within the province of the servicing industry is part of the electronics industry. Being the kind of activity in which there seems to be no leveling off point in the progress being made every days, it seems only natural to want to take a bigger bite of everything that is available and becomes available. Practical experience alone doesn't make this possible; knowledge of theory is needed also.


One of the baffling things we have heard for many years from many practicing service technicians is that they had *no time to read*. We acknowledge that servicing is a hard task master. The hours are long and many jobs can be irritating. But to go along with this

attitude means a self-imposed limitation on the future—on the potential of one's self. Whatever may be the direction a service technician would want to take in the electronics field — whether in or outside the servicing industry — a grounding in electronic theory will help to climb many of the rungs on the ladder upward.

This has become a scientific world with electronics in the forefront. The engineer has come into his own. Maybe everyone cannot be an engineer, but a strong mixture of theory and practice offers tremendous possibilities, even without a formal college degree. The engineer fresh out of school is shy experience. It takes years to get it. The service technician has had the years of experience. He already has that the-

oretical background which served as the base for the service activity. To solidify this, and to broaden it, is not only advantageous in the expansion of one's servicing effort as it may be dictated by the future, but it also makes possible changing the direction in which one wants to go, if it is to his advantage.

Let's summarize. Time for reading technical books and magazines should be found. We realize that servicing is almost a world of its own—but the barriers should be taken down. Admittedly, it isn't easy to acquire technical knowledge after a hard day's work, but the effort will pay off. The servicing industry is faced with immediate problems, but they should not be a deterrent to nourishing the mind. They should not be a block to progress. ■■

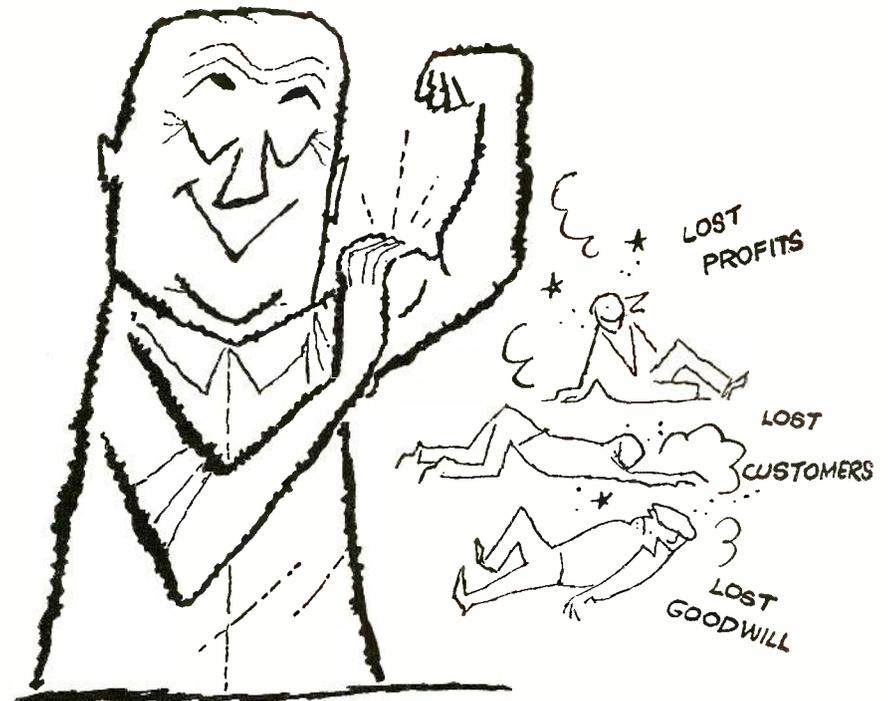

STOP CB* WITH C-D



*STOP SERVICE CALL BACKS with Cornell-Dubilier's popular "UP" Twist Prong Electrolytics—specified by leading manufacturers as original equipment, adopted by "profit-conscious" technicians and the top choice for wide-coverage replacement service. Call-back-free dependability is the big reason why more C-D Capacitors are in use today than any other make. Complete catalog available. Write to Dept. ST-47. Cornell-Dubilier Electric Corp., South Plainfield, New Jersey. SAVE TIME AND MONEY—INSIST on C-D Twist Prong ELECTROLYTICS.

stop call backs...insist on

CORNELL-DUBILIER CAPACITORS

SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER & CAMBRIDGE, MASS.; PROVIDENCE & HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD, FUQUAY SPRINGS & VARINA, N. C.; VENICE, CALIF.; SUB.: THE RADIART CORP., CLEVELAND, O.; CORNELL-DUBILIER ELECTRIC INTERNATIONAL, N. Y.

the BURGESS 1957 Portable Radio



BATTERY PROGRAM
STAY FRESH... LONGER!

**WILL INCREASE
YOUR SALES!**

Here's a four-barrelled portable battery promotion that's bound to boost your battery profits in 1957. Built around proved sales-getters, the Burgess program has everything . . . Be sure to see your Burgess distributor soon for complete details about this big new 1957 promotion.

**BURGESS BATTERIES FOR
QUICK SALES—EXTRA PROFITS**



**NEW SALES STIMULATING
PROMOTION IDEAS!**



A new dual-purpose wall chart or counter easel contains Portable Radio Picture Chart, Replacement Guide Index and Cross Reference Chart. Ask your jobber. It is FREE!

**POINT OF SALE
MERCHANDISING AIDS
THAT SELL BATTERIES**



Window card in full color at right is just like the one described above except it is not animated.



- BATTERY TESTERS
- OTHER MOTION DISPLAYS

CONTACT YOUR BURGESS DISTRIBUTOR FOR DETAILS TODAY!

BURGESS BATTERIES
BURGESS BATTERY COMPANY FREEPORT, ILLINOIS

IT'S ANIMATED!

New action display merchandiser at left has colorful animated action. Use in window or on counter. Will display assortment of most popular Burgess portable types or both batteries and a radio.



WINDOW STREAMER

A big, bright full-color window banner that's double-designed to stop the customer and tie in with the other Burgess sales aids for maximum impact in the store. FREE!

RETAIL PRICE CARD

Furnishes Burgess portable battery numbers, voltages and up-to-date retail prices in "easy to select" form. FREE!

REPLACEMENT BATTERY STICKER

Provides ample space for replacement battery number and dealer imprint — a sure repeat business getter! FREE!

WORKBENCH

[from page 7]

grid current which charges C217 and C216. This negative charge sets the operating bias in such a manner that the tube is beyond cut off and passes only the most positive portions (sync pulses). The charge on C217 and C216 leaks off through resistors R226, R235 and R186 towards a minimum reference voltage developed by the video detector, Y151. Thus, the clipper bias voltage which varies with changes in received signal strength is also used to control *rf* and *if* gain. From V106B the signal is fed to the phase splitter, V110A, and then to the oscillator circuit.

With these facts in mind, check was made at pin 7 of V106A. Here




"Watch, Ma, I'm going to wake Daddy up by remote control!"

the waveform checked normal (see Fig 2). A waveform check was next taken at pin 6 of V106A. The waveform here was also correct. At pin 2 of V106B, the waveform also checked correctly. However, at pin 1 of V106B, the waveform was abnormal. It was observed that video information accompanied the sync pulses in this waveform. V106B was therefore not separating the sync pulses from the video information. A voltage check was then made from the plate, pin 1, to ground and measured correctly at about 140 volts. The voltage was close enough to be satisfactory. Next, resistance checks were made across R227, R236, R228 and R226. All measured correctly except R226. This resistor which should

have measured 1.8 megs was found to have a value of 1.8K!! R226 was replaced with the proper value and the receiver then functioned properly.

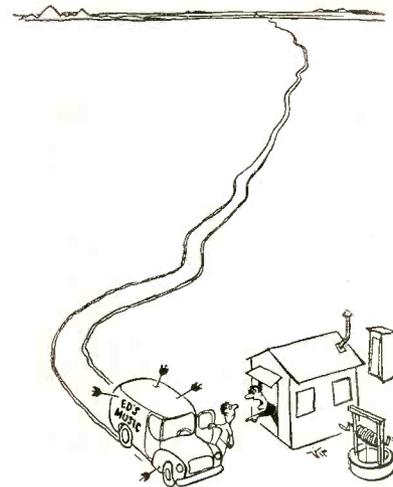The extremely low value of R226 caused too rapid a condenser discharge in the grid leak action. This in turn lowered the bias on the clipper tube to a point where the picture information rode through and incorrectly triggered the horizontal and vertical oscillators. This was apparently a manufacturing defect, since the complaint dated back to the original purchase. ■ ■



"Listen! If you don't have JENSEN NEEDLES, just forget I called!"


ZYTRON "QUALITY BRAND"
RADIO & TV RECEIVING
TUBES
BRAND NEW
INDIVIDUALLY BOXED
Terrifically LOW PRICED!
Send TODAY for Complete Catalog
ZYTRON TUBE CORPORATION
220 West 42nd Street - New York 36, N. Y.

SUCCESSFUL SERVICEMAN DOES BETTER JOB

Direct-from-the-factory product information is the key...

he finds it faster in **The MASTER!**

The MASTER describes, illustrates, lists specifications of over 125,000 items necessary to radio-TV servicing. What's more — it offers thousands of other products that can lead to extra income in Hi-Fi, sound and industrial servicing. You can buy, sell and bill direct from The MASTER. It shows list prices! 1546 pages of current, direct-from-the-factory product information, systematically arranged for quick, easy reference.

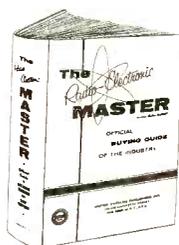

1546 Pages
World's Largest
Electronic Parts
Catalog

Today... Get The
NEW 1957—21st EDITION

Radio-Electronic MASTER
at Electronic Parts Distributors

ONLY \$2.95


THE RADIO-ELECTRONIC MASTER
60 Madison Ave., Hempstead, N. Y.

SENCORE

TRANSISTOR

CHECKER

Model TDC22

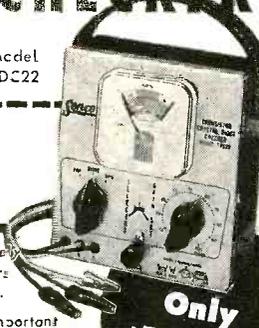

Only \$15.95
DEALER NET

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Voltage Regulator
- Bias Supply

Another Sencore Time-Saver

NOW WANTED and NEEDED by EVERY SERVICEMAN

Quickly and accurately checks all transistors and crystal diodes.

Provides these 4 important checks on transistors:
OPEN • SHORT • CURRENT GAIN • LEAKAGE
Checks forward to backward resistance of diodes.

★ Complete set-up chart and instruction booklet attached to back ★ Will never become obsolete, with test leads, replaceable up-to-date set-up chart and gain control to vary battery voltage ★ Accurate and simple to operate — takes less than 30 seconds to test either TRANSISTORS or crystal diodes ★ Uses test leads which eliminates need of completely removing transistor from circuit.

At Leading Distributors Everywhere

Mfg by **SENCORE SERVICE INSTRUMENTS CORP.**
171 OFFICIAL RD., ADDISON, ILL.

SELL SERVICE


[from page 45]

properly used it can pay off in advertising impact. It takes a deft hand and an honest-to-goodness feeling for it, but used sparingly and at appropriate intervals, HUMOR can reap rich dividends for you. Humor in advertising, without ruining the entire effect of the ad or cheapening it, is a little hard to achieve. But everyone can occasionally come up with a humorous twist on an old subject, and the time to use it in your advertising is while it is fresh and new. If your advertisement does nothing more than pay for itself within a reasonable length of time after use, it has more than done its job. Its long range effects are greatest; each customer attracted to your service is a potential future customer if your service is as good as your advertising.

The "reasonable length of time" mentioned in the previous paragraph is essentially dependent on how frequently you advertise, and this brings us to another point in making your service advertising pay—REPETITION. You may have a real honey of an advertisement; the display may be perfect or its presentation everything you could desire; but if it is used only once and then withdrawn, you have lost the value of the basic block upon which all forms of advertising rest. As applied to service advertising, it is this: If your name is displayed often enough, attractively enough, and effectively enough, the first thing that will pop up into the public's mind when something happens to its TV set will be *your* name.

We now have five points to remember in designing and using your service advertisements to secure the maximum in pulling power: first, PERSONALIZE it, second, make it DIFFERENT, third, be TRUTHFUL, fourth, use a little HUMOR occasionally, and fifth and just as important, REPEAT on a regular schedule. A small advertisement which includes the first four points listed, and which is used consistently, is a great deal more effective than one large ad used only once or twice, regardless how well designed the large ad may be. Save the "one-shot" to use with "leaders" and specials only.

PERFORMANCE

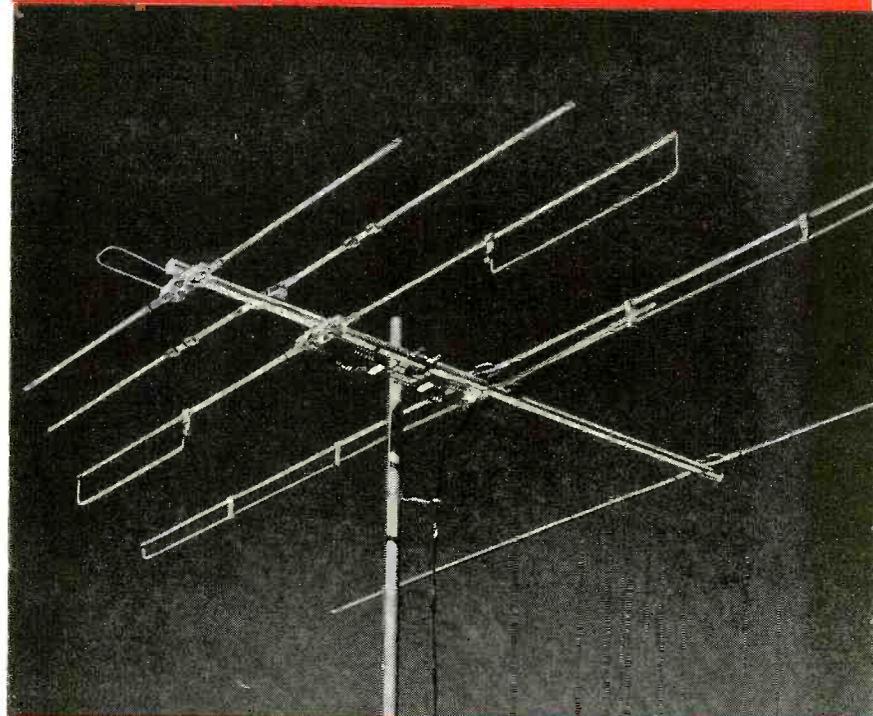

above all others

The TACO Topliner has been proved the finest performer—in side-by-side comparisons. In actual installations the Topliner provides the day-in, day-out performance so necessary to maintain your reputation with the customer.

Seeing is believing—use a Topliner on that next installation. See for yourself just how much better the Topliner works.

TACO *Topliners*
Trade mark

TECHNICAL APPLIANCE CORPORATION, SHERBURNE, N. Y.

IN CANADA: Hackbusch Electronics, Ltd., Toronto 4, Ont.

ELECTRONIC CONTROL

[from page 3]

area surrounding the probes. As the level of the liquid rises, it displaces the air immediately below the probes. The liquid has a different dielectric constant than the air it displaces. As a result the probes "sense" the change in level as a change in capacitance.

Another method of sensing the level of a liquid is through the use of a thermistor. A thermistor is a temperature sensitive semi-conductor. In other

words, it is a resistor, the resistance of which varies with temperature. A TV technician will recognize a similar device, the "Globar" used in many of the G.E. series string television sets.

If we were to connect a thermistor in series with a light bulb and a battery as shown in Fig. 6, the bulb would light for a certain low value of the thermistor determined by the temperature. As the battery current flows through the circuit, it heats the thermistor which drops in resistance and allows enough current to flow to light the bulb. When the

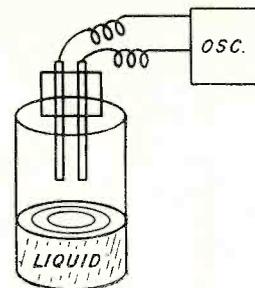


Fig. 5—Capacity as "senser."

level of the liquid rises to the point where the thermistor is submerged, its temperature drops to the reduced temperature of the liquid. As a result the resistance increases sharply and the light goes out. The light bulb then indicates when the liquid has reached a predetermined level. A relay could be substituted for the light bulb which in turn could operate a valve to control the level of the liquid.

There are other devices for sensing liquid levels, such as photo-electric cells

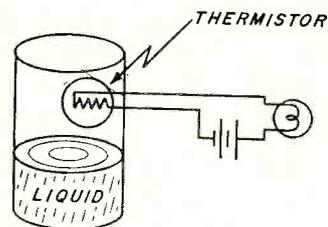


Fig. 6—Control by thermistor.

(Fig. 7) and float-operated switches and potentiometers. Many of these sensing devices can be adapted to operate either when a liquid reaches a predetermined level or to continuously indicate the level.

Half the task of maintaining these controls is accomplished if we understand their basic principles of operation.

The procedure in servicing these systems consists primarily of isolating the defective component; then either replacing or repairing it. The same techniques and instruments are used in measuring voltage, current, resistance, capacitance, inductance, etc., as are used in radio and TV.

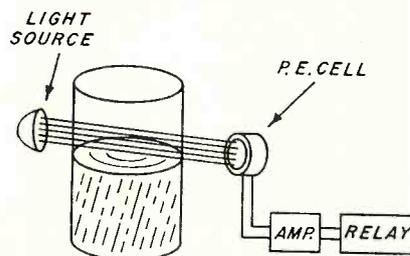


Fig. 7—Control by photo-cell.

BY YOUR REQUESTS WE REPEAT...

SPECIAL INTRODUCTORY OFFER

to acquaint servicemen with ROGERS Quality Components.

FREE \$1.25

75¢ Rogers Exact Replacement Manual listing over 11,000 sets and 7,000 parts and including the Rogers subscription service of up to date reference material to add to the manual.

50¢ DISCOUNT on any flyback or yoke.

EXPIRES

MAY 15 1957

ROGERS

Clip out this valuable coupon and bring it to your nearest ROGERS distributor for this sensational offer!

Write for your nearest ROGERS jobber.

ROGERS

ELECTRONIC CORP.

43-49 Bleeker Street New York 12, N. Y.

Note:
Estimated 13/4 million portable TV sets to be sold in '57!

Here's Your MARKET...

for the
MOSLEY Flush Mount TV Socket

LOW LOSS

NEAT

EFFICIENT



MODEL F-1PK

• The tremendous demand for portable TV sets opens another BIG market for good set-to-antenna plug-in outlets. MOSLEY Flush Sockets meet this need—supplying attractive, convenient, customer-approved wall outlets for every installation requirement.

Without MOSLEY TV Outlets, portable TV—in most areas—ceases to be portable!

Let MOSLEY TV Outlets spark YOUR Portable TV Sales!

For a complete line of up-to-date TV Accessories and Electronic Components send for our "57" catalog.

Mosley Electronics, Inc.

8622 ST. CHARLES ROCK ROAD
ST. LOUIS 14, MISSOURI

SERVICE TRANSISTOR RADIOS?



YES!! Then you need a Kit-Tronics TT-2 Transistor Tester. New Kit calibrated scales on full 4 1/2" 2% Meter. Current Gain: Alpha 0.50-0.99 Beta 0-100 Beta 0-300. Leakage: 100. Precision: 1%. Components: Self-Calibrating measures NPN and PNP Transistors & Crystal Diodes. 17-page step-by-step use and theory manual included. KIT ONLY \$39.95. Postpaid in USA. Factory Wired & Tested \$49.95.

ORDER DIRECT FROM FACTORY

KIT-TRONICS 2315 Hendola Drive, N.E., Albuquerque, New Mexico

COLOR BAR GENERATOR

[from page 5]

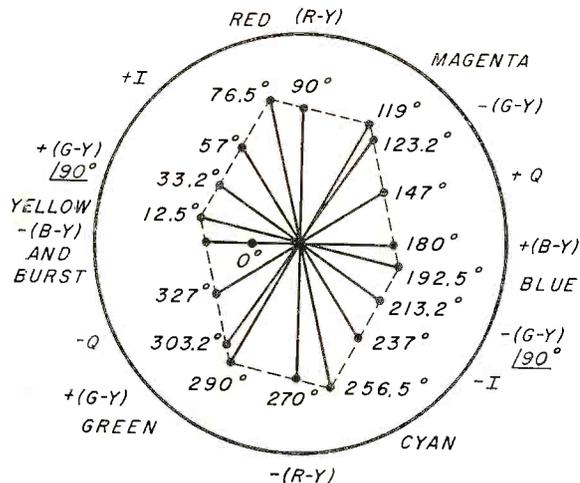


Fig. 8—Vectorscope pattern for normally operating receiver.

(B-Y) detector is applied to the horizontal-input terminals of the scope.

A color-bar signal is used to drive the color TV receiver, and the resulting scope pattern shows how the receiver is processing the various phases of the color signal, as depicted in Fig. 8. Misadjustment of the quadrature transformer, misalignment of the signal circuits, or faulty operation of a color detector shows up in the vectorscope pattern as a departure from the pattern shown in Fig. 8.

Checking the Delay Line

An essential component in the Y channel is the delay line, the operation of which is accurately checked with the aid of a color-bar signal. Fig. 9 shows the principle of operation of a delay line (which delays the Y signal by approximately 0.9 microsecond). The result of a short in the delay line is illustrated in Fig. 10.

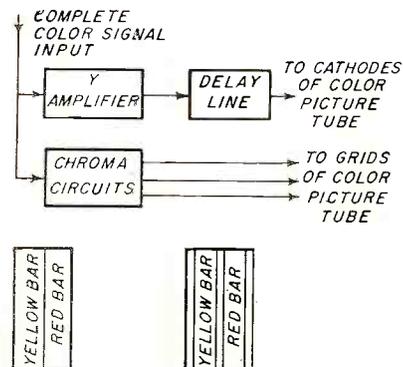


Fig. 9—Block diagram illustrating delay line functioning.

It is evident that the color-bar generator and wide-band scope are now essential equipment items on every color service bench. To these basic instruments, the technician may also wish to add others such as special purpose test probes, capacitance and inductance meters, color-filter cards, and a low-power microscope. However, the color-bar generator and wide-band scope are fundamental test instruments which are the foundation of color TV service work. ■ ■

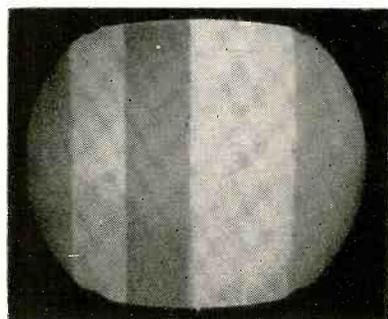


Fig. 10a—Color bar display for a normally operating delay line.


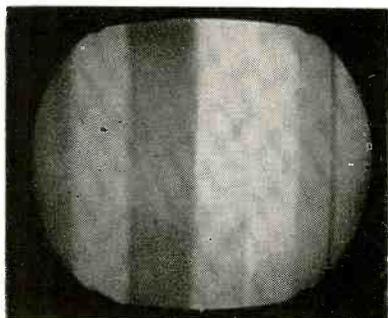


Fig. 10b—Color bar display when a short exists in the delay line.

for service and lab. work


Heathkit PRINTED CIRCUIT OSCILLOSCOPE KIT FOR COLOR TVI

① Check the outstanding engineering design of this modern *printed circuit* Scope. Designed for color TV work, ideal for critical Laboratory applications. Frequency response essentially flat from 5 cycles to 5 Mc down only 1½ db at 5.58 Mc (TV color burst sync frequency). Down only 5 db at 5 Mc. New sweep generator 20-500,000 cycles, 5 times the range usually offered. Will sync wave form display up to 5 Mc and better. Printed circuit board-stabilize performance specifications and cut assembly time in half. Formerly available only in costly Lab type Scope. Features horizontal trace expansion for observation of pulse detail — retrace blanking amplifier — voltage regulated power supply — 3 step frequency compensated vertical input — low capacity nylon bushings on panel terminals — plus a host of other fine features. Combines peak performance and fine engineering features with low kit cost!

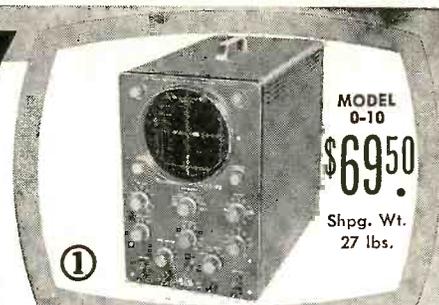


Heathkit TV SWEEP GENERATOR KIT ELECTRONIC SWEEP SYSTEM

② A new Heathkit sweep generator covering all frequencies encountered in TV service work (color or monochrome). FM frequencies too! 4 Mc — 220 Mc on fundamentals, harmonics up to 880 Mc. Smoothly controllable all-electronic sweep system. Nothing mechanical to vibrate or wear out. Crystal controlled 4.5 Mc fixed marker and separate variable marker 19-60 Mc on fundamentals and 57-180 Mc on calibrated harmonics. Plug-in crystal included. Blanking and phasing controls — automatic constant amplitude output circuit — efficient attenuation — maximum RF output well over .1 volt — vastly improved linearity. Easily your best buy in sweep generators.

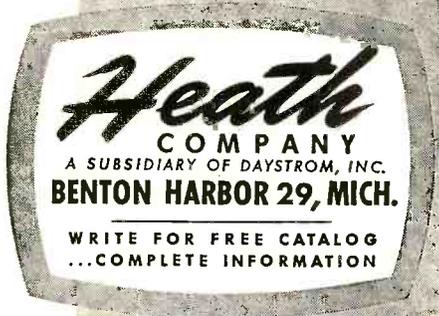

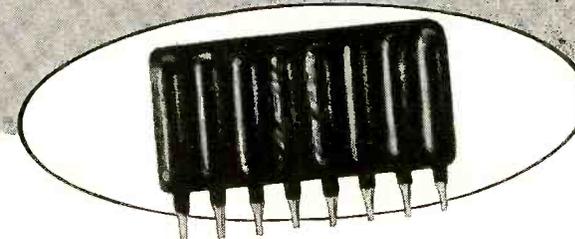Your ERIE Distributor Has "PAC" Replacement Modules




for Servicing 1957 Auto Radios

PAC is a group of interconnected capacitors and resistors, combined in a single-insertion unit. Several popular 1957 model automobile and truck radios employ this new concept in component packaging. When servicing these auto radios, a complete PAC (Pre Assembled Circuit) module can be quickly and easily replaced.

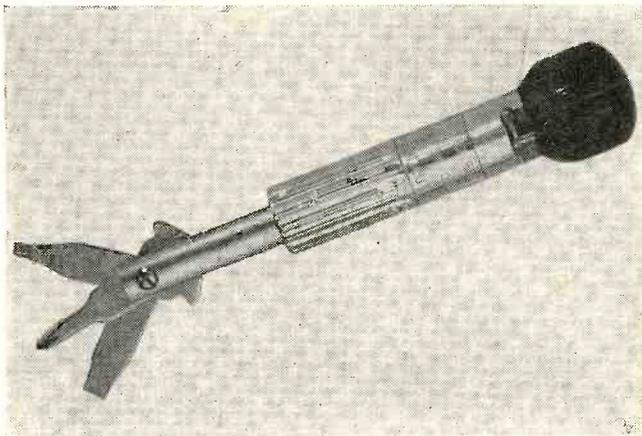Your ERIE Distributor has PAC Replacement Modules in stock. See him for complete information and prices.






WE MAKE CONDENSERS NOT SCREW DRIVERS!

But for a limited time you can get from your PLANET DISTRIBUTOR—FREE—this handy three-blade Versatool with the purchase of the thirty-five popular PLANET Condensers contained in the PLANET SD-35 Assortment.

See your Planet jobber now.

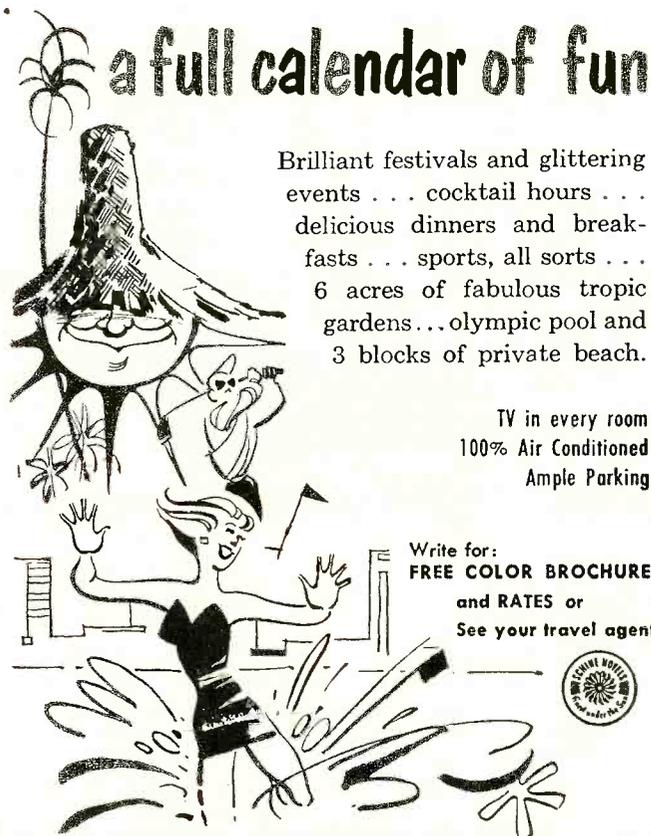PLANET SALES CORPORATION
225 BELLEVILLE AVENUE, BLOOMFIELD, N. J.



a full calendar of fun

Brilliant festivals and glittering events . . . cocktail hours . . . delicious dinners and breakfasts . . . sports, all sorts . . . 6 acres of fabulous tropic gardens . . . olympic pool and 3 blocks of private beach.

TV in every room
100% Air Conditioned
Ample Parking

Write for:
FREE COLOR BROCHURE
and RATES or
See your travel agent



RONEY PLAZA

(7 Acres on the Ocean) COLLINS AVE. AT 23rd ST. MIAMI BEACH

TEST EQUIPMENT

[from page 16]

and is due to the fact that not only is the power drawn from the circuit quite low, but the over-all conditions for oscillation are improved, the feedback ratio is increased, more rectified grid current is obtained and the meter goes up scale. However, if this same component is defective (shorted) it will cause the meter reading to drop into the REPLACE region.


Vertical windings may be tested for shorted turns in a manner similar to that used with the horizontal deflection coils. However, in this case it is imperative that any resistors or capacitors across or in series with the coils be removed.

Continuity Tests

When components in the horizontal system (except capacitors) are suspected as "open," the Model 382 is used in the "CONTINUITY" position. Switching to this position converts the instrument to a simple *ac* operated ohmmeter. The magnitude of the *ac* voltage is varied by means of the "METER ADJUST" control on the front panel.

Capacitance Measurement

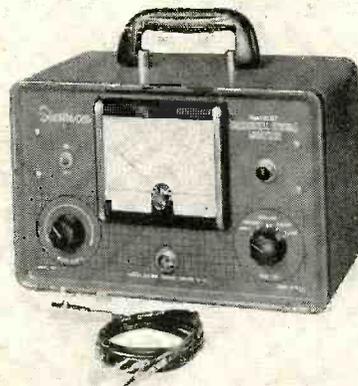The Model 382 may be used to measure capacitance values from 10 μf to 0.1 μf in three ranges, with an accuracy of ± 5 degrees of arc on the meter. In this application, the Model 382 once again becomes an *ac* ohmmeter. It utilizes a variable source of *ac* voltage, an *ac* micro-ammeter and a precision multiplier resistor. All of these com-



Simpson Model 382 Horizontal System Analyzer.

IF YOU MUST
SPEND
YOUR MONEY...
Why not get
Something
for it?

QUIETROLE

the Choice
of Better
Servicemen
Everywhere

Available in
2 oz., 4 oz., 8 oz.



QUIETROLE

TRADE MARK REG. U.S. PAT. OFF.

Costs little more than the
poorest substitutes. Why
take less than the BEST...

No Product can match its merit . . .
None can equal its quality . . .

It's the answer to noisy controls
and switches

QUIETROLE is the original product of its kind

MFG
BY **QUIETROLE Company**
SPARTANBURG, South Carolina



Sandy Says!
Has
USES GALORE

Anchor S-203
3-Way
Selecto-Switch



IDEAL for selecting Hi-Fi components;
operating speakers singly or in combination;
switching from UHF to VHF;
TV to FM, changing from one antenna
to another and many other varied
applications . . . Indicator rotates
positive acting switch. Solder-
less connections. Attractively
packaged.

AT YOUR DISTRIBUTOR
OR WRITE

anchor products co.
ELECTRONIC COMPONENTS
2712 W. Montrose • Chicago 18, Ill.

Perma-Power
**GOLDEN
 C-BRITE
 TV BRITENER**


**Series or Parallel
 Booster!**



At All
 Distributors

Manufactured by
Perma-Power COMPANY
 3100 N. ELSTON AVENUE
 CHICAGO 18, ILL
 Manufacturers of Electronic
 Equipment Since 1928

HICKOK
 Model 290X

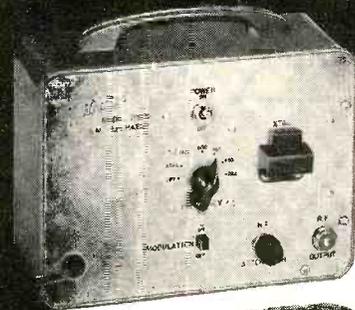

\$35.00 Net

**HIGHLY ACCURATE
 AM GENERATOR**

Specifically designed to meet the accuracy and high speed requirements of today's radio servicing. All output frequencies easily obtained by dialing the front panel selector switch. Crystal accuracy through addition of crystal in holder provided.

THE HICKOK ELECTRICAL INSTRUMENT CO.

10533 Dupont Ave. • Cleveland 8, Ohio

ponents are essentially in series with the test leads.

Features

Summarizing the Model 382 Horizontal System Analyzer can be used to test most of the individual components TV set, "in circuit." It can be used to test most of the individual components of the horizontal system, namely, the flyback transformer, the yoke, and the associated capacitors. It can also be used to measure other capacitors in the TV set, radio set, audio amplifier, etc. which fall within its capacitance range. ■ ■

AUTO RADIOS

[from page 39]

for checking, but remember, *do not use the heat sink as a ground.*

Push buttons are of the mechanical type, pull-push lockup. It is advisable to double-check these setups since a poor setting may sound hashy to the customer.

Dial or manual tuning slippage may occur sometimes when too much lubricant is used on the clutch assembly spindle. This may soften the clutch faces enough to become tacky and bind. Careful use of carbon-tet can remove the tackiness and allow a clean separation of the clutch faces. ■ ■

EMERSON


[from page 19]

of the *agc* voltage (providing no delay is applied) is applied to the tuner (*rf*) while only about one fifth of this voltage is applied to the *if*. The time constant of *C-1*, *R-3*, and *R-6* is relatively fast allowing the *agc* voltage to follow rapid variations in signal strength. This is most noticeable in the reduction of airplane flutter. Variable tuner *agc* delay is provided by the local-distant potentiometer (*R-9*). In most areas, this control is set for maximum tuner delay (distant) for best gain and signal to noise ratio. To eliminate tuner overload in very strong signal areas, the control should be set for maximum *agc* (local-minimum delay). The use of a potentiometer allows for optimum adjustment of delay. ■ ■

TELCO TV HARDWARE
 with Di-Chromate Finish



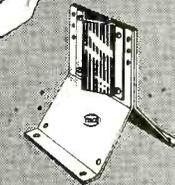**EVERYTHING YOU NEED... QUALITY MADE
 FOR PROFITABLE INSTALLATIONS!**



ROOF MOUNTS




STANDOFFS




ARRESTORS




TOWERS

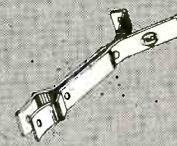

CHIMNEY
 MOUNTS

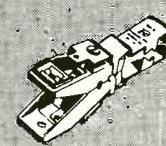

LINE CLIPS

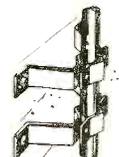

WALL
 MOUNTS

ALL ACCESSORIES




**Di-Chromate Finish
 Prevents Roof Streaks**

All Telco TV Hardware is built and finished to last regardless of the rigors of weather, climate or usage. Quality features at a price that makes your TV installations profitable. Insist on TELCO for all your hardware needs.

**YOUR JOBBER HAS COMPLETE TELCO
 HARDWARE STOCKS... SEE HIM AND SAVE!**

TELEVISION HARDWARE MFG. CO.

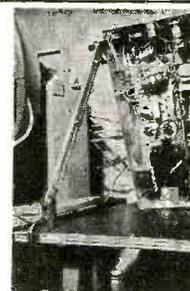Division of G-C • Textron Inc.
 400 South Wyman Street • Rockford, Illinois



**ADJUST-
 ABLE
 3rd ARM**

FOR HOLDING
 CHASSIS IN
 POSITION ON
 WORK BENCH

\$5.50
 each

SUPPORTS VERTICAL CHASSES.
 PREVENTS BREAKAGE OF
 PRINTED CIRCUITS AND
 OTHER COMPONENTS

Send checks or money orders only
TELESCOPIC PRODUCTS, INC.
 262 Sullivan Pl., • Bklyn 25, N. Y.

**LIGHT the TORCH
 OF HOPE**



**HELP YOUR
 HEART FUND**

sell

RECOTON

REPLACEMENT NEEDLES



on every job!

It's easy to sell famous Recoton Replacement Needles on every service call you make! Everyone buys phonograph needles — and Recoton's have 100% consumer acceptance. Easy to carry in Recoton's smart, professional #100 Kit, complete with eye loupe and tools, all Recoton Replacement Needles are easy to find, too, without guessing, and best of all, easy to install. That's why more service men recommend — and sell — RECOTON Replacement Needles on every job!


RECOTON CORPORATION

52-35 Barnett Avenue
Long Island City 4, N. Y.

IN CANADA: QUALITY RECORDS, LTD., TORONTO

Superior's New Model TV-12

TRANS-CONDUCTANCE TUBE TESTER

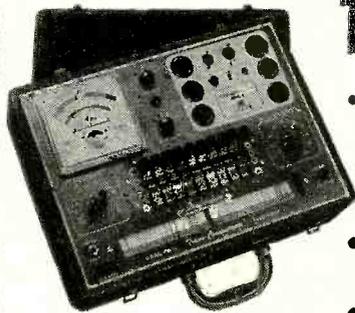

FEATURES

- Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio and TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.
- NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.
- SAFETY BUTTON — protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

- NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY. Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

EXTRA FEATURE: Model TV-12 also tests Transistors

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on special "transistor only" meter scale.

Model TV-12 housed in handsome rugged portable cabinet sells for only

\$72.50
NET

**SHIPPED ON APPROVAL
NO MONEY WITH ORDER — NO C. O. D.**

Try it for 10 days before you buy. If completely satisfied send \$22.50 and pay balance at rate of \$10.00 per month for 5 months. —No Interest or Finance Charges Added. If not completely satisfied, return to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC.
Dept. D-348, 3849 Tenth Ave., New York 34, N.Y.
Please rush one Model TV-12. I agree to pay \$22.50 within 10 days after receipt and \$10.00 per month thereafter.

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

All prices net, F.O.B., N.Y.C.

EQUALIZATION IN HI-FI

[from page 13]

the front or from the back). If a relatively slow back and forth vibration is felt, you can be sure that several watts of low frequency rumble are present, even though it cannot be heard because it is outside the human range of audibility. A rumble filter does to the low frequencies what a scratch filter does for the highs. It cuts sharply, at a predetermined frequency of, say 30 cps, so that anything below that frequency is sharply attenuated. Since very little music or program material goes down that low, virtually no difference in sound will be experienced by the insertion of such filtering action. A simple circuit for the elimination of rumble is shown in Fig. 9 and can be installed at the input of just about any power amplifier with good results. Because of the values chosen no insertion loss will take place with this circuit. Make all ground connections at the input jack, if possible, to prevent the possibility of any increase in hum. The values chosen will give a sharp cut-off below about 30 cps. For a higher frequency of cutoff choose lower values of C_1 and C_2 . For even lower cut-off points, choose larger values of C_1 and C_2 .

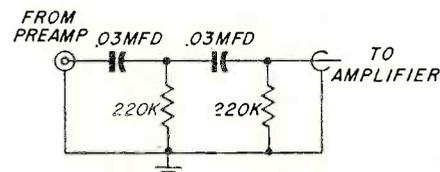


Fig. 9—Rumble filter for the elimination of frequencies below 30 cps.

In the next installment of this series, we shall begin outlining the layout and servicing procedures recommended for basic power amplifiers. We shall also touch upon the very controversial subject of "how much audio power is required in Hi-Fi amplifiers." In addition, we shall present some simple rules with which you can check the adequacy of a given system or make recommendations to customers planning to buy an amplifier.

Only the 5 TOP-QUALITY brands of

STANDARD BRAND TUBES AT SENSIBLE PRICES!

All tubes are brand new, 1st quality, 90 day RETMA guaranteed, individually boxed.

This month's

BARRY TUBE SPECIALS!

0A2	\$.70	6AG7	\$.120	6F6M	\$.90
0B2	.60	6AH6	1.20	6H6	.60
0B3	.60	6AK5	.80	6J6	.75
0C3	.60	6AK5W	1.20	6J7	.50
0D3	.60	6AN8	1.10	6K7	.80
0Z4	.56	6AQ5	.70	6L6M	1.35
1B3	.93	6AQ6	.60	6N7	1.00
1B4	.55	6AR6	1.35	6SQ7	.55
1LC5	.70	6AS6	1.00	6SH7	.65
1U4	.50	6AT6	.60	6SJ7	.70
1X2B	.97	6AT8	1.00	6SK7	.70
5R4GY	1.15	6AU6	.68	6SL7GT	.90
5U4G	.68	6B4G	1.50	6SN7GT	.70
5X4	.60	6BA6	.67	6SQ7GT	.65
5Y3	.55	6BE6	.73	6Y6G	.70
5Z3	.75	6B6	.85	6Z7	.80
6AB4	.66	6BQ6G	.85	12AT7	.80
6AB7	1.25	6BQ7	1.25	12AU7	.75
6AC7	.85	6BZ7	1.25	12SH7	.85
6AG5	.65	6CB6	.73	12SC7	.75

Orders over \$25 (with remittance) postpaid.

(Effective to midnite June 1, 1957)
In lots of 50 or more. May be ass'd.
May include other numbers at regular prices.
Write for latest tube sheet.

We stock over 1000 types including Diodes, Transistors, transmitting and Special Purpose types.
TERMS: 25% with order, balance C.O.D. All merchandise guaranteed. F.O.B., N.Y.C.

BARRY ELECTRONICS CORP.
Dept. 5D

512 Broadway, N. Y. 12, N. Y.


24-hour telephone service

Teletype: NY 1-3731

Walker 5-7000

ask the
"Man-on-the-Roof"
why he prefers

South River

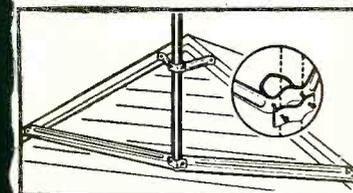

EAVE MOUNT Model EM-48

One piece construction of heavy gauge, embossed steel. Hot-Dip galvanized to prevent corrosion. Unique design of lower bracket gives extra strength and rigidity. Extended lip supports mast during installation. Spread permits generous spacing between brackets for excellent mechanical mast support. Both 3" embossed steel upper bracket and lower bracket have new "reversed" U-bolt and clamp feature for Spintite fastenings. Also available with 60" spread: EM-C0

WRITE FOR NEW 1957 CATALOG

SOUTH RIVER
METAL PRODUCTS CO., INC.
South River, New Jersey


pioneer & outstanding producer of finest line of antirna mounts

Advertisers Index

Aerovox Corporation	43
Amphenol Electronics Corp.	1
Anchor Products Company	54
B & K Manufacturing Co.	5
Barry Electronics Corp.	56
Belden Manufacturing Co.	Cover 3
Blonder-Tongue Laboratories, Inc.	16
Burgess Battery Company	50
Bussmann Manufacturing Co.	13
Clarostat Mfg. Co. Inc.	11
Cornell-Dubilier Elec. Corp.	49, Cover 2
Electro-Voice, Inc.	7
Elgin National Watch Co.	45
Erie Resistor Corp.	53
General Cement Mfg. Co.	55
Guide Lamp, Div. of General Motors Corp.	19
Heath Company	53
Hickok Electrical Instrument Co.	55
Jackson Elec. Instrument Co.	42
Kit-Tronics	52
Mallory, P. R. & Co. Inc.	6
Mosley Electronics, Inc.	52
Moss Electronic Dist. Co. Inc.	56
North American Philips Co. Inc.	41
Perma-Power Company	55
Philco Corporation	8, 9
Planet Sales Corp.	54
Pyramid Electric Company	15
Quietrole Company	54
RCA Batteries	Cover 4
RCA Components	44
Radiart Corporation	Cover 2
Raytheon Manufacturing Co.	3
Recoton Corporation	56
Rider, John F. Publisher Inc.	10
Rogers Electronic Corp.	52
Roney Plaza Hotel	54
Service Instruments Co.	53
Sonotone Corporation	14
South River Metal Products Co.	56
Taco	51
Tung-Sol Electric, Inc.	46, 47
United Catalog Publishers	53

If it's worth Engineer's time . . .

. . . it's worth Engineered Cable

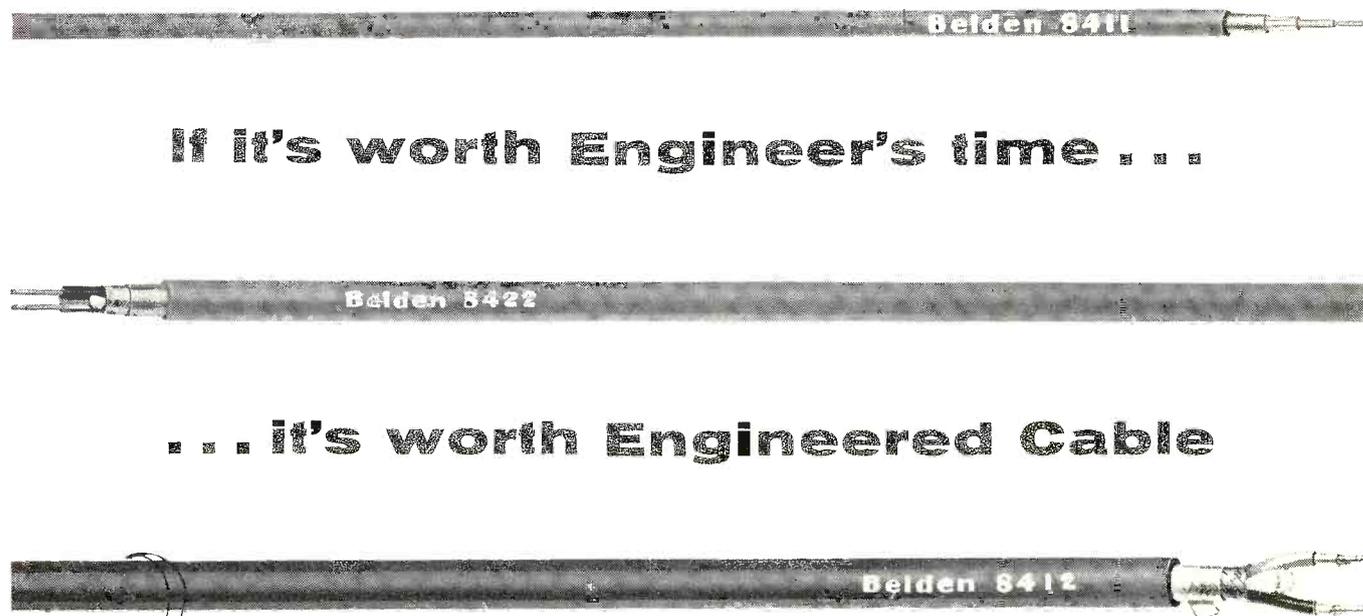

**Belden
microphone
cables**


Whatever the installation,
whatever the requirements,
there is an accurately
rated Belden Microphone
Cable built for the job.



1001 WIRES FOR EVERY ELECTRONIC NEED

RCA BATTERIES

... your nest egg

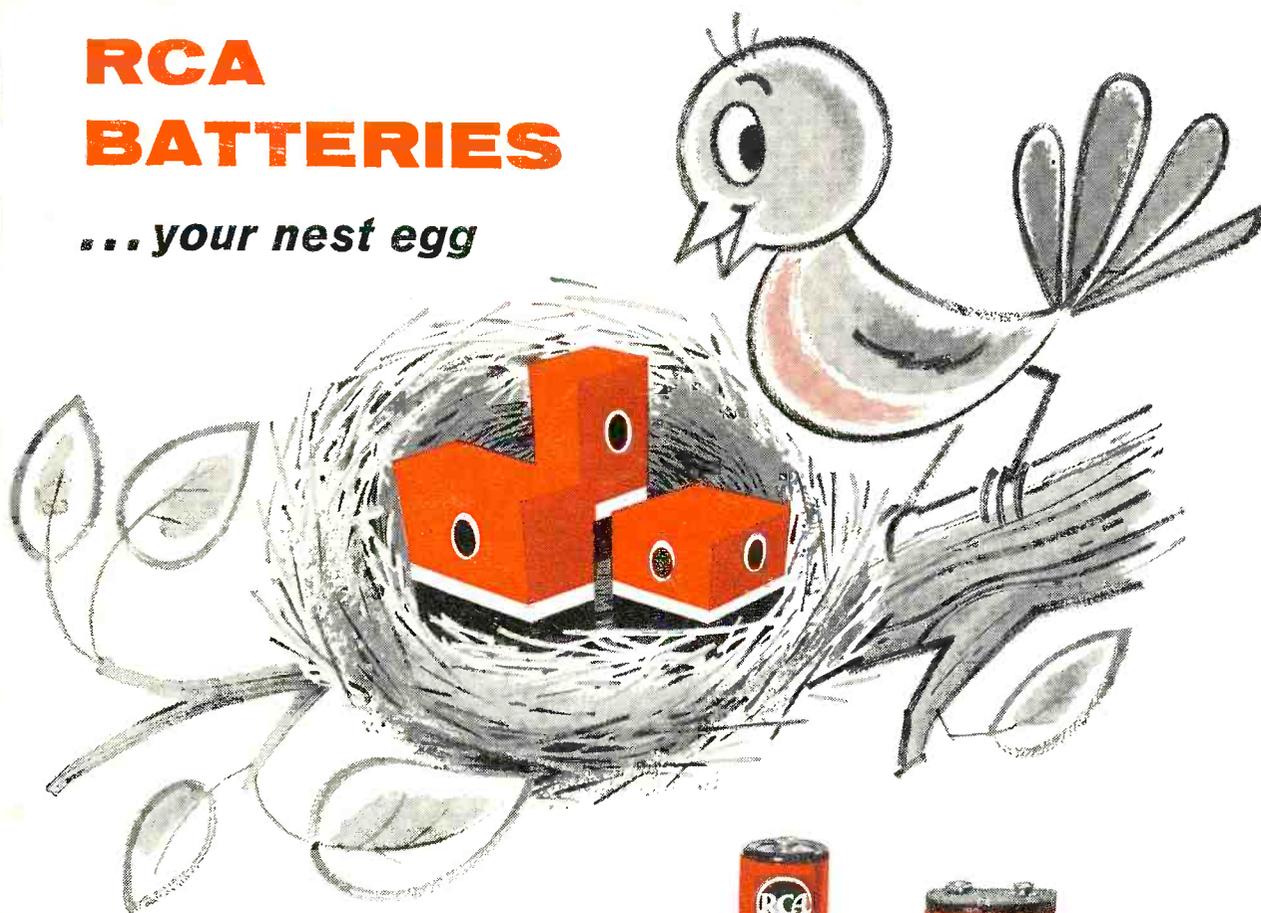

... for profits all year long!

Customer acceptance of RCA quality assures you of profit making battery sales all year long. And, there's an RCA Battery to serve virtually every customer's need. This includes batteries for the new transistor-powered portables as well as for industrial and general use. Order your nest egg of RCA batteries *TODAY* for profit making sales all year long!



RADIO CORPORATION of AMERICA

COMPONENTS DIVISION

CAMDEN, N. J.

CONSUMER • INDUSTRIAL • GENERAL • RCA IS YOUR BEST BATTERY BUY!

COWAN PUBLISHING CORP., 300 West 43rd Street, New York 36, N. Y.

ELECTRONIC SERVICING

JAN 6E 1716 16 SEP 57A
HINKO
Y TRAFALGAR
LAND 10 OHIO