

RADIO

REG. U.S. PAT. OFF.

WORLD

America's First and Only National Radio Weekly


Exponential Horn Explained

Victoreen Fans Form Club

Choke and Bypass Problems

Lucky Curves "Fall Flat"

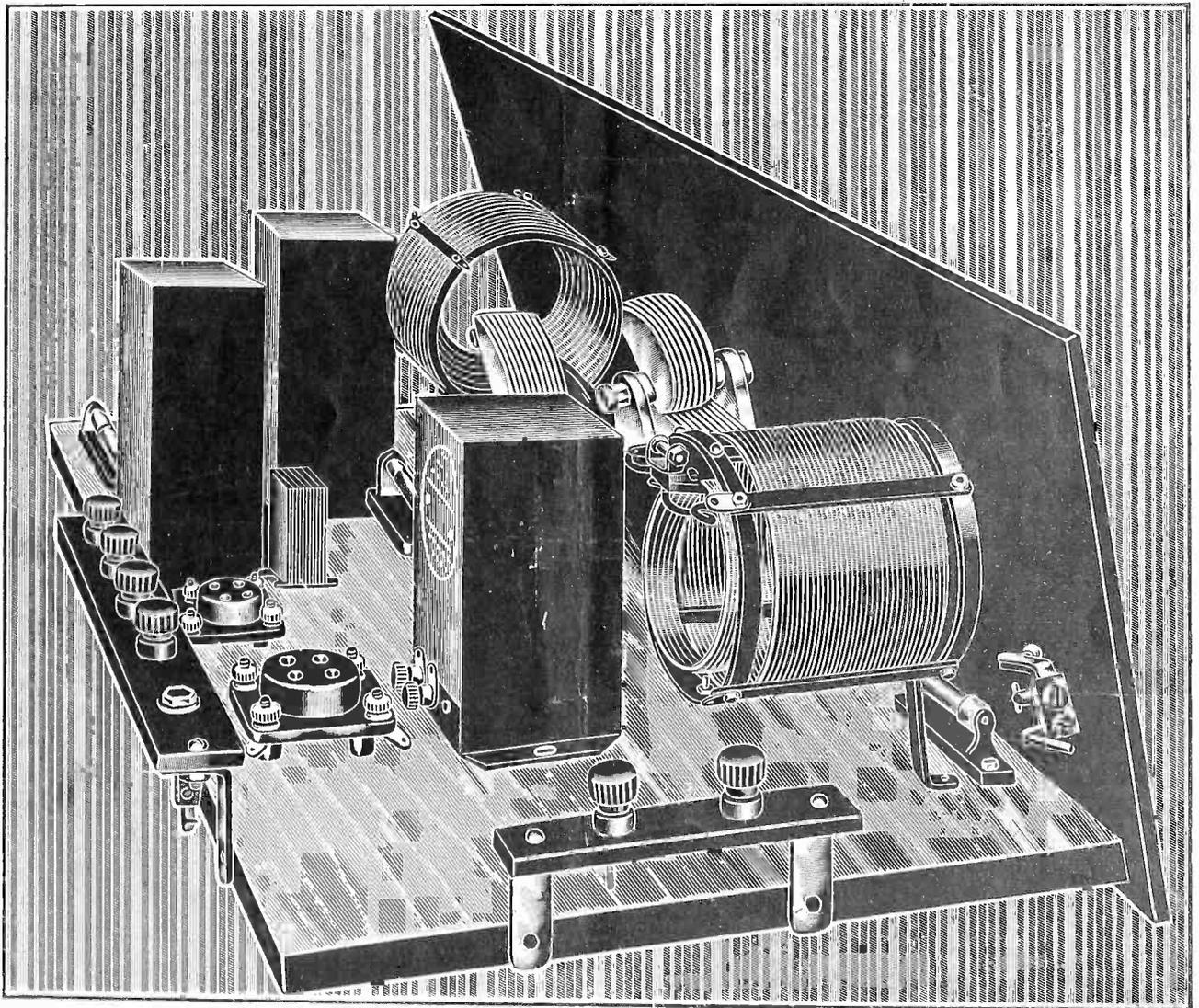The One-Dial Witz, With Double Impedance Audio



One Dial, One Switch, One Volume Control, but a Double Condenser and Double Impedance Audio Are Used in This Attractive Receiver. See page 3.

A Great Deal for a Very Little!

Ordinarily This Seems Too Good to Be True, But Here Is An Instance of Complete Verification



The New De Luxe Model Bretwood With Condenser Attached

WHEN you are deciding on what parts are to go into the receiver you are about to build, under no circumstances dismiss the grid leak with only casual consideration. Respect the grid leak as something well worthy of expert choice.

The best course is to select a variable grid leak with an ample resistance range, one that may be mounted on baseboard, sub-panel or front panel, as you prefer.

Such a leak is the BRETWOOD VARIABLE GRID LEAK, which is now on the market in new de luxe model, representing improvements in mechanical strength, electrical efficiency and utility.

Higher Efficiency

You should use a variable grid leak like the

North American Bretwood Co.,
145 West 45th Street, New York City.

Gentlemen: Enclosed find \$1.75. Send me at once one De Luxe Model Bretwood Variable Grid Leak on 5-day money-back guarantee. (Or \$2.25 for leak with grid condenser attached.)

NAME

ADDRESS

CITY STATE

Inquiries Solicited from the Trade

BRETWOOD VARIABLE GRID LEAK in a set you are about to build, or should put one in your present receiver, because it will enable you to get highest operating efficiency from the detector tube. As nearly all tubes used as detectors draw grid current, the resistance value of the leak is important for biasing and discharge purposes. Not only can exactly the right degree of flow be established to discard excess electrons, but the grid-to-filament impedance is so affected as to afford best selectivity under the circumstances. Only a variable leak gives this precision choice.

You prevent overloading of the detector tube by correct leak setting. This improves tone quality considerably. Often if your set sounds distorted, this is immediately and permanently remedied. Hence you reap greater volume, better selectivity and purer tone quality—all by the simple insertion of a BRETWOOD DE LUXE MODEL VARIABLE GRID LEAK.

Selected by Bernard

This efficient instrument so struck Herman Bernard that he prescribed it for his latest and most popular circuit, Radio World's Universal Four-Tube Receiver.


The BRETWOOD DE LUXE MODEL VARIABLE GRID LEAK costs \$1.75—a small enough price for so much efficiency. If desired, a .00025 mfd. BRETWOOD BULLET CONDENSER is supplied, mounted on the leak, at 50 cents extra.

Note: The Bretwood Leak's range is .25 to 10 meg.

Dealers: Send in your orders direct!

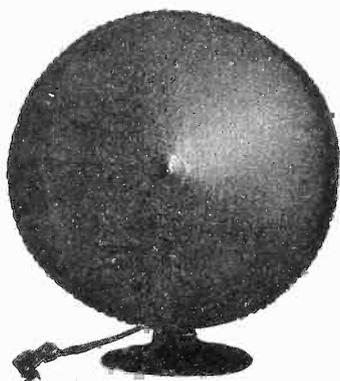B. S. T. CONE SPEAKER

Guaranteed to give Satisfaction in
Tone, Volume and Appearance
Adjustable to Volume Desired



18 inches in diameter edged in Gold Braid, Art Metal Base can be placed on highly polished surface without danger of scratching.

Immediate
Delivery

\$7.50

Shipped Direct
from Factory

Satisfaction Guaranteed or Money Back

GUARANTY RADIO GOODS CO.

145 West 45th St., New York

RADIO WORLD


A Weekly Paper Published by Hennessy Radio Publications Corporation from Publication Office, 145 W. 45th Street, New York, N. Y.

Phones: BRyant 0558 and 0559

[Entered as second-class matter, March, 1922, at the post office at New York, N. Y., under Act of March, 1897]

The One-Dial Witz

By A. Irving Witz

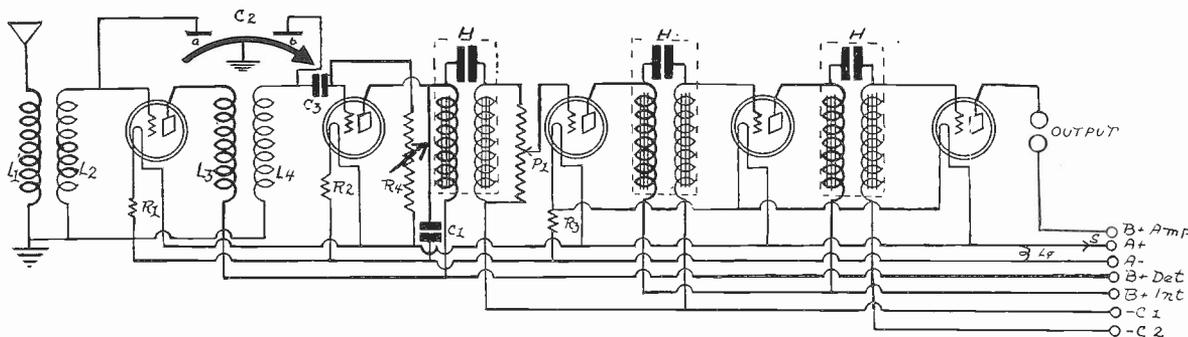

THE circuit diagram of the One-Dial Witz Receiver, employing the double impedance system of audio amplification. It also employs a double condenser for simplified tuning. The pilot light is a part of the National dial.

PART I

WHAT are some of the advantages of the double impedance system of audio amplification which in a comparatively short time has succeeded in capturing the interest of the engineers and the fans alike? Surely the advantages are real and not fancied, or the engineers would have discovered the flaw and the rapidly increasing number of fans would not continue to be satisfied with their double impedance receivers.

Let us attempt to answer the question before we take up the description of a receiver in which the system is incorporated.

One of the obvious advantages of the system is the high degree of amplification of which it is capable. The plate coupling coil has a very high inductance, which is equivalent to a high impedance at any one frequency. Since the tube works into a very high impedance, nearly the entire voltage available in the plate circuit of the tube is transferred to the next tube. If the amplification constant of the tube is 30, the step-up per stage at 1,000 cycles per second is about 29. With certain resistance coupled amplifiers this would not have been more than 20, or two-thirds the μ of the tube.

Hence the gain in amplification is considerable in a circuit having three double impedance couplers.

Works on Low Plate Voltage

Another advantage is the low voltage requirements for the plate circuits. The choke coil through which the plate current flows has a comparatively low resistance. Hence the voltage drop in the coil will be negligible. This makes it practicable to work the amplifier with applied voltages as low as 45 volts, whereas in a resistance coupled amplifier voltages as high as 180 volts are desirable.

The low voltage requirement is an advantage especially when dry cell batteries are used to activate the set.

Again it will be recalled that when the load impedance on a tube is very high the

amount of harmonic which is introduced into the signal is negligible. Thus in this system the wave form of the signal will remain pure.

These are considerable advantages yet they are of less importance than the advantages the system offers on the grid side of the couplers. One of the greatest of disadvantages of ordinary direct coupled circuits is the effect of the grid current which flows when the grid becomes positive. When the resistance of the device delivering voltage to the grid is high there will be a considerable voltage drop in it, and the effective voltage on the grid becomes less. Amplification drops. In fact there is practically no amplification while the grid is positive. If the input voltage swings positive during part of the cycle the positive peaks of the wave will be cut off. This represents harmonic or wave form distortion.

Effect of a Coil

When an inductance coil is used in place of a high resistance the voltage drop in the device is negligible even when considerable grid current flows, and there is no appreciable diminution in the amplification on the positive peaks. It is possible to leave the grid bias zero and let the voltage swing just as much positive as negative without introducing wave form distortion. Hence it is possible to put much higher signal voltages on the tube than would be possible with a resistance grid leak. The output also would be much greater.

With a low resistance in the grid circuit there is no tendency for the tube to choke due to the accumulation of a negative charge on the grid and stopping condenser. This trouble is one of the most exasperating in ordinary direct coupled circuits.

When hooking up a double receiver with a B eliminator one is at once struck by the absence of low frequency oscillation which is common in many other types of receivers. That is, the receiver does not motorboat. Naturally, that is a great advantage, because if a circuit motorboats it is of no value no matter how well it has been designed otherwise.

The reason for the absence of motorboat-

ing may be found partly in the phase relations in the circuit and partly in the amplification at the extremely low notes.

Amplification Analyzed

Each coil in the circuit introduces a certain change of phase in the signal. The condenser also introduces a change of phase. A complete coupler comprising the plate coil, the condenser and the grid coil, introduces a definite phase shift at any given frequency. This shift will throw the currents in the eliminator out of phase with each other so that they cannot produce motorboating. Particularly, the current through the loudspeaker is out of phase with the current through the first plate coupling impedance. When these two are opposite in phase, or if they are out of phase more than 90 degrees, the circuit is stable and will not oscillate.

The amplification at the sub-audible frequencies is low in this amplifier for two reasons. The first is that a finite stopping condenser is used and the second is that the various choke coils are not effective at these very low frequencies. This fact prevents the circuit from motorboating at the low frequencies, but it does not prevent the amplification of the audible frequencies. The capacity of the stopping condenser and the inductances of the two chokes in each coupler have been chosen so that the amplification is satisfactory down to the lower limit of audibility, while the amplification is very low below that limit. The low amplification at the sub-audible frequencies prevent very slow motorboating or fluttering.

The Inverse Proportion

An objection may be raised against the claim of sharp demarcation between the transmitted and the suppressed frequencies on the ground that the impedance of the stopping condenser is inversely proportional to the frequency and that the impedance of the choke coils is directly proportional. These facts would tend to make the transition from high to low amplification very gradual. And would, if either the chokes or the condenser alone were effective. When both inductance and capacity enter, the phenomenon



VIEW of the front panel of the one-dial set. The volume control, an Electrad type E Royalty, is at right, the switch at left. The National type C dial is used on the Lignole panel.

LIST OF PARTS

- C2—One double section, .00035 mfd. Continental die-cast condenser.
 C3—One Electrad .00025 mfd. grid condenser.
 C1—One Electrad .0005 mfd. condenser.
 R4—One Turnit grid leak, .5 to 12.5 megohms.
 R1, R2—Two No. 1A Amperites.
 R3—One No. 4A Amperite.
 P1—One Electrad .5 megohm potentiometer (Royalty, Type E).
 L1L2, L3L4—Two radio frequency transformers for .00035 mfd. condensers.
 HHH—Three F.M.C. double impedance couplers.
 Lg—One six-volt pilot light.
 S—One switch.
 Nine binding posts.
 One standard battery cable.
 Five UX sockets.
 One National Type C vernier dial.
 One 7x21 inch Lignole inlaid two-tone panel.
 One 7x20-inch wooden baseboard.

of resonance also enters, and where that occurs the amplification will be very high.

Now, it is possible to choose the values of the inductances and the capacity so that the resonance occurs rather low in the scale. This will keep up the amplification of all frequencies above the resonance frequency. The change in the amplification below the resonance point will be very rapid. This accounts for sharp cut-off. If it is desired to amplify all notes evenly down to 50 cycles per second the resonance point might be placed between 75 and 100 cycles. If it is desired to go down to 16, the resonance might be placed between 24 and 32 cycles. In this coupler the amplification is uniform

down to about 30 cycles per second.


Two identical radio frequency transformers L1L2 and L3L4 are used in the receiver. The two secondaries L2 and L4 of these are tuned with a double Continental Die Cast condenser C2 of .00035 mfd. capacity per section. Careful adjustment of the inductances and the distributed capacities in the two tuned circuits is necessary to get the greatest selectivity and sensitivity out of this arrangement. But it is only necessary to make this adjustment once. To facilitate the adjustment of the distributed capacity, the rotor plates of one of the sectional condensers are shifted, if necessary. Small adjustments of capacity can be effected when tubes are changed, as different tubes have different capacities. The capacity difference thus established for equalization varies at the same rate as the condenser in rotation, a good point.

Discussion of Constants

A grid condenser C3 of .00025 mfd. capacity is connected in the grid circuit of the detector tube. The grid leak resistance R1 is variable and it is connected between the grid and the positive side of the filament. It is variable so that the detector circuit can be adjusted for optimum sensitivity for any given signal strength. It is connected in parallel with the tuned circuit so that the positive grid return can be used when the tuning coil returns to the negative or ground. The coil is thus returned because the rotor side of the double condenser is grounded.

To provide a low impedance load on the detector for the radio frequencies, a by-pass condenser C1 is connected across the first plate coupling choke, or rather from the plate to ground. This also by-passes the batteries. The condenser should be of .0005 mfd. capacity.

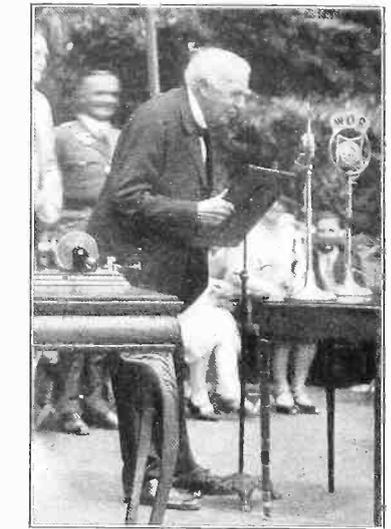For controlling the volume in the set a high resistance potentiometer P1 is con-



THOMAS A. EDISON RECITING

On the fiftieth anniversary of the invention of the phonograph a reception was given in honor of Thomas A. Edison, the inventor, by his friends and business associates. Mr. Edison was induced to make a speech. It was one of the few times that the inventor had ever made a public address, and had spoken into a broadcast microphone.

The subject of his address was "Mary Had A Little Lamb." He recited the well-known ditty because this was the first thing that came to the inventor's mind fifty years ago when he was about to record his first record in the laboratory.

The photograph shows Mr. Edison telling the radio listeners about the faithfulness of Mary's little lamb.

connected across the first grid choke coil. This instrument should have a resistance of 500,000 ohms. By means of this the volume can be varied from almost zero to the full output of the circuit.

There are three double impedance couplers H in the circuit. The symbols inside the dotted lines indicate just what is an integral part of each coupler.

Plate and Grid Voltages

The plate voltage on the detector and the radio frequency tube is 45 volts, obtained from the B plus Det. bus wire. The plate voltage applied to the intermediate audio amplifiers is 90 volt, obtained from the B plus Int. bus wire. The voltage applied to the last tube is 180 volts.


The grid voltage on the RF tube is obtained from the drop in the Amperite R1. The normal drop in this ballast is one volt.

While a grid bias is not necessary on the intermediate tubes with the double impedance coupling system, bias voltages can be used if desired. When a bias is used the value depends on the type of tube that is used. Since the load impedances in these tubes is very great, high mu tubes like the CX-340 can be used to advantage. Fine results are obtained with —01A tubes. The grid voltages for these tubes with 90 volts on the plates are as follows: CX340, 1½, and —01A, 4½ to 6 volts.

The last tube should be a —71 type power tube. Since the applied plate voltage on this tube is 180 the grid voltage should be 40½ volts. The small battery E gives this bias. By tapping suitably it will also give the bias for the other tubes if a bias is desired.

[Part II Mr. Witz's interesting article will be published next week, issue of September 3. Constructional data will be completed then. In the two succeeding issues other important aspects of the circuit will be discussed.]

"DON'T WRITE—"

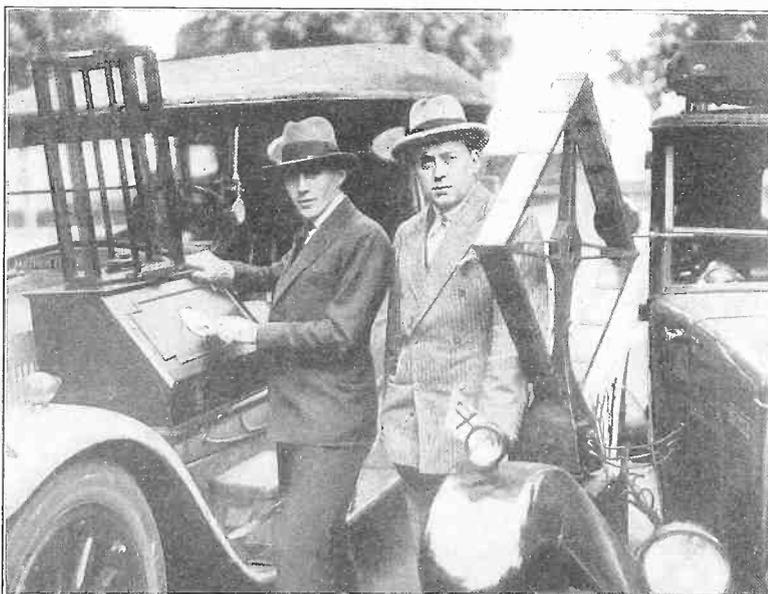


(Herbert Photos)

CAPTAIN L. F. PLUGGE (right) and Horace Connell (left) with their radio equipped cars. These well-known Europeans will attempt to keep in constant communication with each other while touring about 500 miles apart on a trip through southern Europe.

What Is the Exponential Horn?

By H. B. Herman
Acoustical Expert

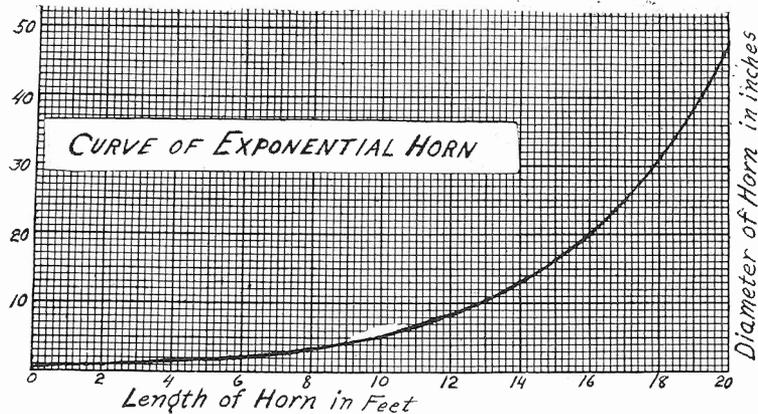

THE CURVE shows the diameter of a 20 foot exponential horn having a small end diameter of .625 inch and a large end diameter of four feet. The abscissas give the length of the horn in feet and the ordinates the diameter in inches.

In the constant quest for better reproduction of radio broadcasts many types of loudspeakers have been made and marketed. At first we had the horn in its devious forms. We had straight horns, bent horns, coiled horns, reflex horns. We had horns of circular cross-section, of elliptical cross-section, of square section, of hap-hazard cross-section. We had horns of pyramidal and conical lines and we had horns with graceful curved lines. We heard about exponential horns but we did not see any, not in the radio field. Following the era of horns we entered the era of cones, discs, and other large diaphragms. We also entered the era of better reproduction and of a greater demand for still better reproduction. Then in the midst of popular acclaim for the cone a couple of engineers had the audacity to bring out another horn, this time an exponential horn in fact. And they claimed for it uniform reproduction over the entire audible range of frequencies and great volume as well. One of these exponential horns was used at the Westinghouse plant in Pittsburgh for projecting the human voice over a distance of three-quarter of a mile. The voice was clear and easily intelligible. Again horns of the same type were used to inform the New York crowds of the progress of the welcoming ceremonies in honor of Com. Richard E. Byrd and his crew and Clarence Chamberlin. The voice of the announcer was clearly heard over the din of the street.

ACOUSTICAL engineers are agreed that the exponential horn is the most uniform sound radiator. They have proved mathematically that it is so, and they have corroborated their deductions by experimental evidence. What is meant by "the most uniform sound radiator" and of what practical interest is such a radiator?

The uniform sound radiator radiates sound energy at the same rate at all frequencies. It does not favor the very low notes, nor the very high, nor the medium, nor any other notes. It is as impartial as a judge is supposed to be. It has no resonance peaks.

Stated otherwise, it has a straight line output characteristic. The practical value of such a radiator is that it is capable of faithfully reproducing whatever is impressed on the driving unit. It is distortion free. By the "most uniform sound radiator" is meant the most nearly uniform radiator. The fidelity of the output of such a radiator depends directly on how "nearly" it is uniform.

Nearest to Perfection

The well-constructed exponential horn radiator is as close to the uniform as can be attained in practice, and hence it is capable of quality as near perfection as possible, provided that perfect quality is delivered to it by the receiver and driving unit.

There are certain practical limitations

which prevent the exponential horn from being a perfect radiator. The main one is the necessity of termination. The horn cannot be indefinitely long. Neither can it have an indefinitely wide flare. This limitation militates against the lower notes. But horns 20 feet in length will be uniform radiators down to a frequency of about 16 cycles per second; and lower it is never necessary to go since that is the lowest frequency that anyone can hear.

Now what characterizes an exponential horn? The rate at which the cross-sectional area increases as the distance from the end increases.

The Mathematical Side


Suppose that the area of the small end is one square inch, that at one inch from the end it is 2 square inches, at two inches the area is 4 square inches, at three inches it is 8 square inches, and so on to the end, the area of the cross-section increases exponentially. A horn constructed according to this law would be an exponential horn, but the shape would not be practical.

Mathematically the requirements of an exponential horn can be stated thus:


$$D = (D_0) B^L$$

in which D and D_0 are the diameters at the large and small ends respectively and L is the length of the horn. B is a number which determines the shape of the horn in between the two ends when the length and end conditions are known. While this formula gives a relation between the linear dimensions of the horn it is not inconsistent with the requirement stated in the preceding paragraph

(Continued on page 22)

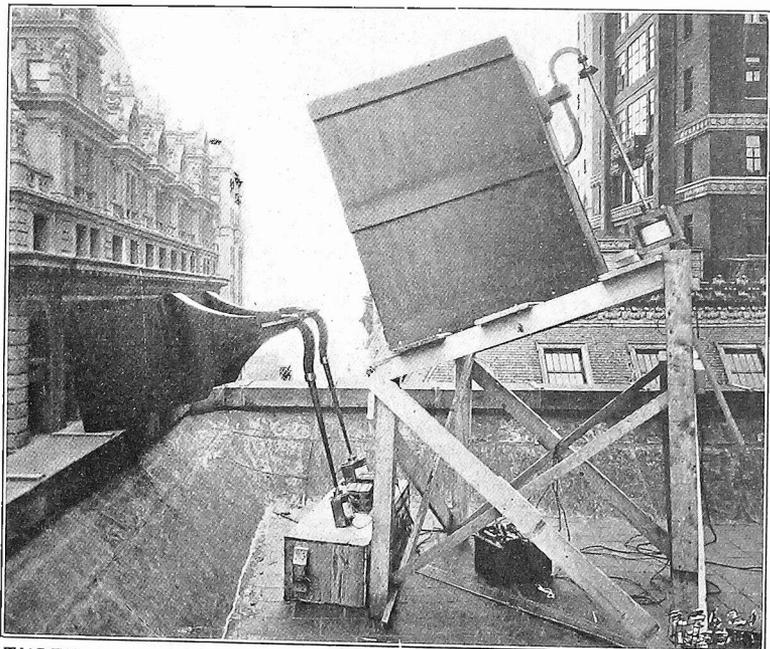

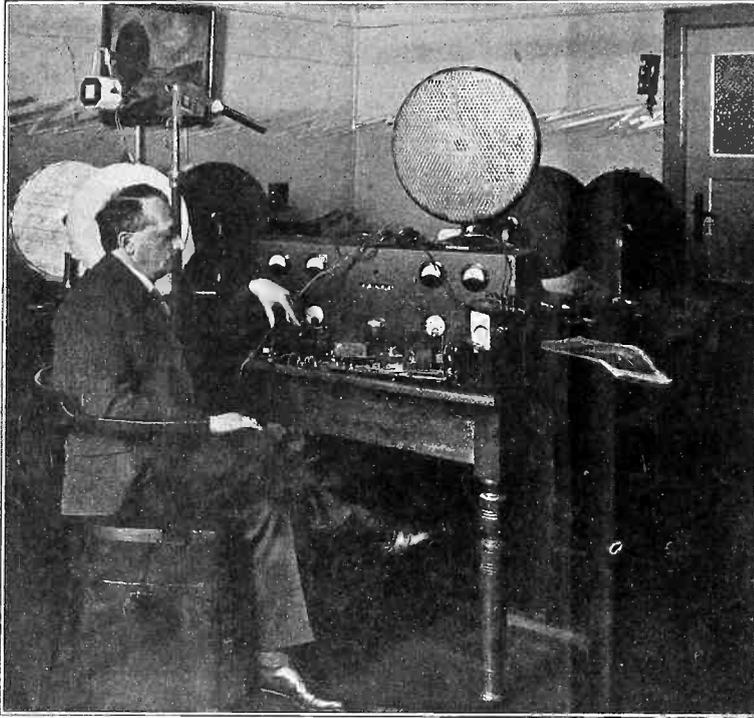THREE exponential horn speakers installed on top of Westinghouse building lower Broadway on the occasion of Commander Richard E. Byrd's return from France.



(Reinhold Lissner Photograph)

EUGEN REISZ, the inventor of the Marbleblock microphone and the electro-static loudspeaker, is seated in his laboratory among some of his inventions. Note the marbleblock microphone suspended just above the inventor's head. Also note electro-static loudspeakers in various stages of construction.

Something

Condenser Type Being
American Use—Original

By Eugen Reisz

MICROPHONE and telephone, these two elements of every electrical transmission of sound, have gone through a great many constructive improvements since the time of their invention. The principle of their mode of operation has, on the whole, remained the same up to the present time.

In the case of the microphone the sound is received by a diaphragm, the oscillations of which either cause changes of pressure in carbon particles, or alter the size of the capacity of a condenser. In the case of the telephone the sound is transmitted in the following way: the sound waves, which are produced by the microphone, alter the intensity of an electro-magnetic field, and these field-oscillations create the varying pressure on the diaphragm.

The sole improvements in the course of the last few years, regarding the construction of the transmission elements, microphone and telephone, consisted on the one hand in giving the microphone diaphragm a high self-oscillation, by means of a tight stretching of material, and on the other hand in changing the originally small metal diaphragm of the telephone into a large,

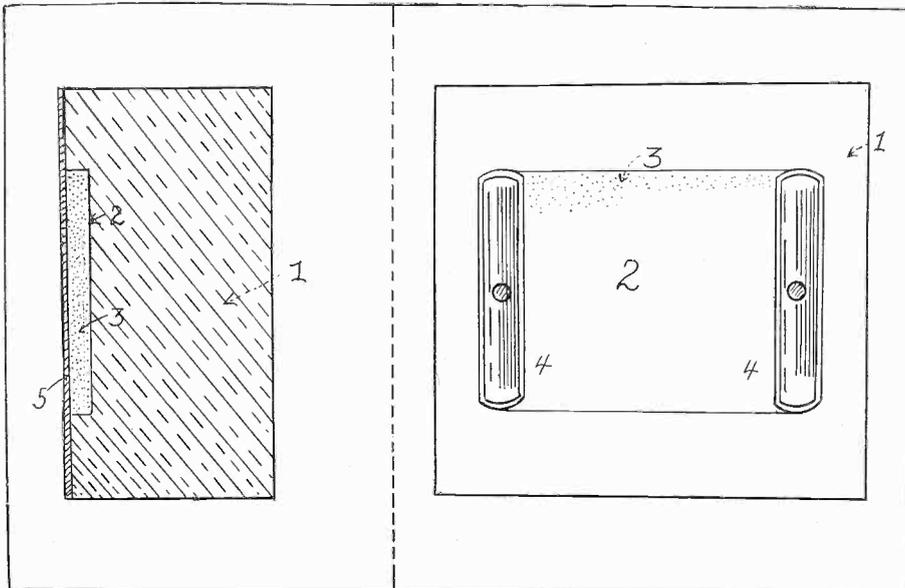


FIG. 1

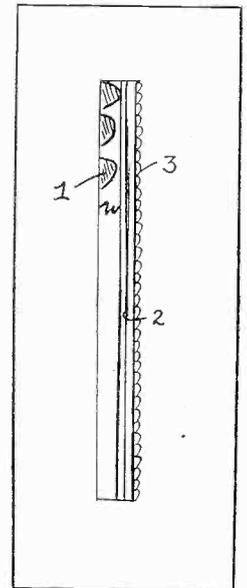


FIG. 2.

When Baron von Ardenne, the twenty-year-old German radio scientist, visited America a couple of months ago, he occupied a suite at the Hotel Commodore, New York City, while on the floor below Eugen Reisz, Berlin acoustical engineer and manufacturer, occupied a suite. The Baron insisted he was not here on business, but simply to learn, and to make arrangements for a free exchange of ideas between the two countries. But Mr. Reisz was here admittedly to arrange for the introduction into the United States of his microphone, earphone and speaker, all of which are most extraordinary. He was aided in his negotiations by Eric

Palmer, who was the official welcomer to both Germans, and who made all arrangements for their comfort and convenience while they were in this country.

One afternoon the Baron entertained some radio writers at luncheon in his suite and demonstrated a small receiver he had brought from Germany, which embodied a German three-in-one tube, the joint invention of the Baron and Siegmund Loewe. The set worked a pair of earphones, just ordinary ones. The Baron took keen delight in demonstrating the difference between mere earphones and Reisz phones, which were of the condenser type with a resistance as the impedance. The

Baron's guests were startled at the thrilling realism of the low-note reproduction, notes coming through that were utterly unheard in the ordinary phones, and the whole music of the orchestra becoming endowed with crispness and sparkle.

Mr. Reisz was interviewed a few days later, through the courtesy of Mr. Palmer, and arrangements were made for the publication of the first article on the theory and practice of the Reisz microphone, earphone and speaker. The article, written in English in Germany, is published in full herewith.

EDITOR.

New in Speakers

Perfected in Berlin for
One Comes to Radio World

Noted German Acoustical
Engineer and Inventor

in most cases conical shaped, diaphragm of cardboard or other material of this kind.

Tightness Invites Distortion

The tightly stretched diaphragm of the microphone had the disadvantage that the sensitiveness of such a microphone was very small, so that amplifiers with several amplifying tubes had to be used in order to obtain better results. Though there are no difficulties to-day in constructing suitable amplifying sets with several tubes, i.e., to obtain a distortionless amplifying by means of good amplifying valves and transformers, it is most advantageous for practical use if rather the sensitiveness of the microphone is increased. In the case of amplifiers with several tubes there will often be a reaction between the input and output of the amplifier, especially if the conductors to the microphone are extremely long, or the output conductors vary too much in their character. In the case of carbon microphones the increase of the sensitiveness is already advisable for reducing the self-resonance of the microphone.

The object of all improvements, as regards the microphone, must always be the increase of the sensitiveness, which is identical with the problem of a stretched diaphragm.

Diaphragmless Microphone

My microphone construction, which is known as Reisz Microphone or Marble-block Microphone, and used by all European broadcasting stations, has no diaphragm. The changes of pressure, caused by sound, can directly influence the carbon particles. In this construction there is no difficulty to increase the sensitiveness so much that the sensitiveness of the old carbon microphones is obtained. In this case it would suffice to use amplifiers with only two tubes in the broadcasting stations. The danger of a reaction between the input and output will be absolutely done away with. Distortion with good one-tube or two-tube amplifiers is almost impossible, and the whole microphone will become cheap and simple for practical use. Owing to the great sensitiveness all undue resonances are absolutely eliminated. The construction of this microphone is to be seen in Fig. 1.

In the marble block (1) a chamber (2) has been worked out, containing carbon particles (3) of various sizes, which are supplied with direct current by the two fixed carbon electrodes (4). The chamber (2) is covered with a very thin and non-stretched rubber sheet or with a mica plate (5). This rubber sheet is no diaphragm, but only serves the purpose to separate the inside of the chamber from without.

The described microphone consists only of elements which are free from oscillations, of a marble block and carbon powder. Thus it is quite different from the known carbon microphones, which work with oscillating elements. Owing to a special construction of the chamber and enlargement of the carbon surface the sensitiveness may be increased ad libitum.

Curve Called Ideal

In the near future microphones will be placed on the market which have the same sensitiveness as the old carbon microphones. Carefully executed measurements have shown that the Reisz Microphones have an ideal working curve, i.e. they possess the


same sensitiveness for sound waves of 30 to 10,000 cycles. As the making of these microphones is very simple and always shows a uniformity and as the effect cannot be influenced by climatic conditions, these microphones are superior to all other constructions.

Almost all constructed telephones are working with electro-magnetic fields, and have diaphragms of metal or paper. These diaphragms are conducted by the electro-magnetic field practically from one point, so that the oscillating elements are coupled loosely to each other. The result is that the whole surface of the diaphragm shows acoustic figures, and that the sound waves, when reproduced, do not correspond to the primary sound waves.


Again, Stiffness Means Distortion

The larger and more rigid the surface of the diaphragm, the more the distortion will grow in sound reproduction.

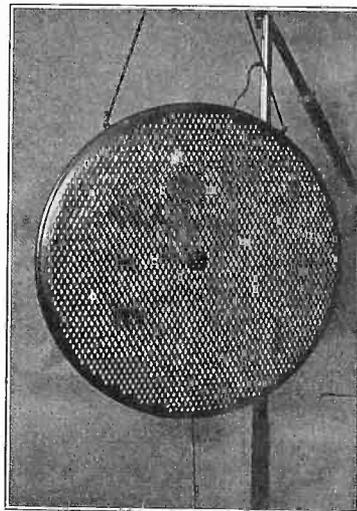The self-oscillations of the vibrating ele-



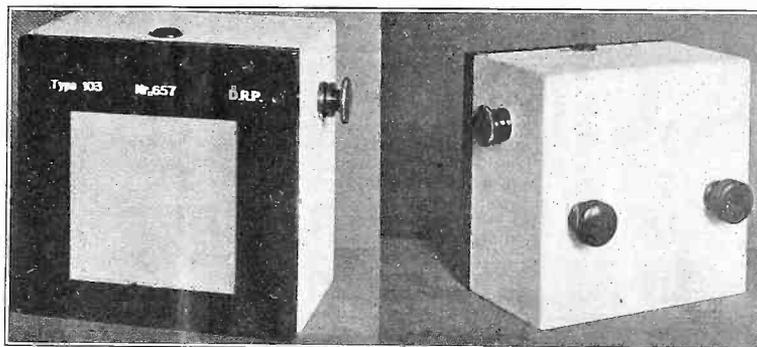THE front view of the Reisz condenser speaker.



THE front side of the marbleblock microphone (left). At right, the rear side of the marbleblock microphone, showing the marble and the terminal posts.

ments on the surface of the diaphragm can only be eliminated if the whole surface of the diaphragm is in the magnetic field, as in this case the self-oscillation is damped considerably.

However, it is not possible to extend magnetic fields on a large surface with simple means, so that it seems impossible, from a theoretical point of view, to operate an electro-magnetically conducted surface of a diaphragm without resonances. The more rigid the material used for the diaphragm, the stronger the disturbing acoustic figures. On the other hand, a rather great rigidity is necessary to reproduce the high notes, so that it seems impossible to attain a satisfactory result in this way.

The condenser telephone has, compared with the electro-magnetic telephone, the advantage that the electro-static field can be equally extended over a large surface, damping the self-oscillations of each element. A faithful reproduction, even with the electro-static telephone, can be expected only if the self-oscillations of the surface elements of the diaphragm are outside the musical frequency range.

Meets Conditions

This condition is fulfilled by my condenser telephone, the construction of which is indicated in Fig. 2. A very thin sheet of rubber (2), which is closely connected with a powdery conductor (3), lies on a perforated plate. This plate represents one electrode of a condenser, the metal powder the other.

In the case of varying electric pressure between these two electrodes, the thin rubber sheet will oscillate and transmit these oscillations to the surrounding air. As the rubber sheet lies loosely, i.e. almost with-

out any stretch, on the fixed electrode, thus its self-oscillation is outside the musical frequency range.

To attain a good working curve of the telephone it is necessary that the holes in the fixed metal plate be shaped conically, so as to facilitate, in the case of great amplitudes, a free oscillation of the elements of the diaphragm. Those earphones, which have already been constructed on this principle, have an ideal working curve, i.e., the sensitiveness is constant for a frequency range of 30 to 10,000 cycles. The loudspeaker, which is built with electrodes of 52 to 60 cm diameter, has an ideal working curve of 250 to 10,000 cycles. In the near future a model will be brought out in which the range will be extended to 30 cycles.


Judging from the results attained up to now, it seems most probable that it will soon be possible to give a perfectly faithful reproduction of speech and music with this electro-static loudspeaker.

Lowest Notes Are Heard On New Reisz Speaker

Berlin, Germany, August 15, 1927.
Mr. Herman Bernard,
c-o Radio World,
145 West 45th Street,
New York, N. Y.

In my laboratory a loudspeaker is now being made, based upon the electrostatic principle. This loudspeaker reproduces completely the lowest notes, and I will see that it is sent to you as soon as it is finished.

Yours faithfully,
EUGEN REISZ.

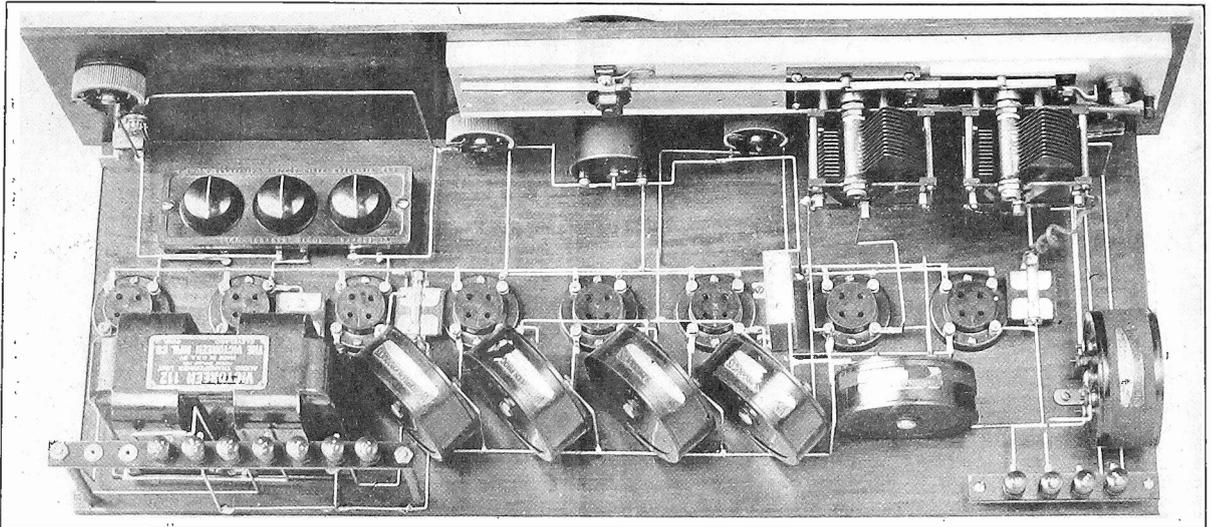

HERE is an advance showing of the 1928 Victoreen Universal Circuit, soon to be described in Radio World. Note the placement of the intermediate coils and also the position of the new Victoreen 112 Audio Unit. The Victoreen was subjected to months and months of testing and experimenting and the above was the choice.

A Club Based on a Circuit!

Victoreen Admirers Elect President— Hold Meetings and Weighty Discussions

By James H. Carroll

Contributing Editor; Associate, Institute of Radio Engineers

THAT a club has been built up around a radio circuit is a fact indeed. And the circuit is the famous Victoreen-eight tubes, but oh, what a kick! Eight tubes last year, eight tubes this year, and eight tubes next year.

The Victoreen Club, of which I am a member, meets at the office of its president, Paul R. Fernald, at 168 Washington Street, New York City. There members discuss the circuit, report on kinks they've tried in connection with it, tell of remote stations they picked up through the local barrage, and discuss radio topics in general. No doubt branches will spring up throughout the country.

It is the consensus of members of this club that the Victoreen is the simplest Super-Heterodyne to build and operate.

Some Efficiency Data

In spite of the Victoreen's ease of construction, tuning and operation, a small percentage of fans encounters what is called "trouble." In 99 per cent. of these cases, upon investigation, the fault is found to be their own. These fellows would encounter trouble in the most simple and fool-proof diagram or apparatus that could be devised, because they will insist on following their own ideas of what they think should be done regardless of what is specified or what they are advised to do.

Most of these chaps have a psychological reflex which causes them to go to the right when you say "left," or to rush onward when you cry "stop."

Others are preternaturally bright and believe they can improve the results of hard-fraught research and testing by the designer of the circuit—these experiments

being made entirely in their behalf to save them time, money and worry and to give them the best results.

Figures compiled from the card-index reports filed in the H. & F. Radio Laboratories, New York City, show that 75 per cent. of the Victoreen so-called troubles inspected were due to mistakes by fans in wiring, and deviations from the blueprint; 20 per cent. were due to the substitution of inferior parts for those specified, and the remaining 5 per cent. were due to what we might call natural causes. This record covers the past two years.

Our next pointer is on increasing efficiency in battery operation. With the regulation placement in line of block B batteries, two for 90 volts, three for 135 volts and four for 180 volts, it will be found that the intermediates are functioning on one battery of the series only, thus causing a higher resistance in that particular battery than in the rest, not evenly distributing the load throughout the circuit. This is liable to cause some noise and trouble in tuning for extreme distance, in some instances blocking the signal entirely.

Plate Voltages

Placing a variable resistance, such as the Clarostat, in the detector line and stepping the source voltage from 45 to 90 volts input we can control to almost a millivolt the current flow on to the intermediates and the oscillator. And still finer results may be accomplished with a separate control on the oscillator voltage.

This method also distributes the resistance more fully throughout the line and does not cause any one battery to bear

the burden. This results in longer battery life, fewer frying noises and absolute control of the set for DX tuning. In installing this system, use a 1 mfd. condenser to by-pass this resistance.

Another pointer for those who favor the use of by-pass condensers, we find that if the .001 condenser bypassing the plate of the second detector is taken to the negative of its own tube rather than directly to the negative battery lead clearer results will be obtained. If a milliammeter is used be sure to bypass it with a .001 between the poles.

The Audio Unit

As to pointers on the audio, exclusively, there are many audio ends in vogue and all popular with their owners. However, for the real Victoreen fan there is now ready the new Victoreen 112 Audio Transformer Unit, designed especially for them by John A. Victoreen and built into perfect form by the engineers of the Victoreen research laboratory. Its quality is wonderful.

Physically and mechanically it is a beautiful piece of work, and severely tested and charted it shows a fine curve and marvelous characteristics. There are many unusual features about this unit and many preconceived notions of some of our experts are upset but it looks mighty good to the seeker after perfection. Two power tubes are called for with its use 112s being recommended and the power prescribed to operate them is 250 volts or over so that ample volume with perfect tone quality, the best that a 36-inch cone can deliver, is the result.

The quality is a revelation to even the most experienced fan.

Push-Pull for Pep 'n' Power

80 Volts on Last Grids
BUT Let 'em Swing!

By J. E. Anderson

Contributing Editor; Associate, Institute
of Radio Engineers; Consulting Engineer

HUNDREDS of thousands of receivers are in use throughout the country in which there is no provision for high power amplification. In many of the sets the output tube is only a -99 type while in many others it is only an -01A type. Neither of these tubes can handle enough power to drive properly a good loudspeaker. Even such tubes as the -20 and the 112 cannot handle enough undistorted power to satisfy modern demand for quality and volume. To get really good results when using a first-rate loudspeaker it is necessary to use a -71 or a -10 tube in the output stage. To get the very best results two of either of these tubes should be used in a push-pull arrangement in the last stage.

It is not necessary to rebuild the old set nor to buy a new one in order to take advantage of modern power amplification. An inexpensive addition can be connected to the old set and make it handle all the power that will be required for the best loudspeaker.

Need of High Plate Voltage

An objection will be raised against this solution to the problem on the ground that those who have inadequate receivers are not provided with suitable voltages to operate the power tubes. That objection is met, if you have alternating current, by the installation of a battery eliminator in the addition. This eliminator will not only supply the high voltage necessary to feed the power amplifier tubes but also to supply the plate voltage to the tubes in the old receiver.

Fig. 1 is the diagram of a stage of push-pull power amplification with a B eliminator attached. The cost of construction of this circuit is not prohibitive and it will pay for itself in satisfaction many times a year.

The input transformer T1 may be any good coupling transformer, e. g., Karas, Amertran AF7, Silver Marshall 220, Pa-

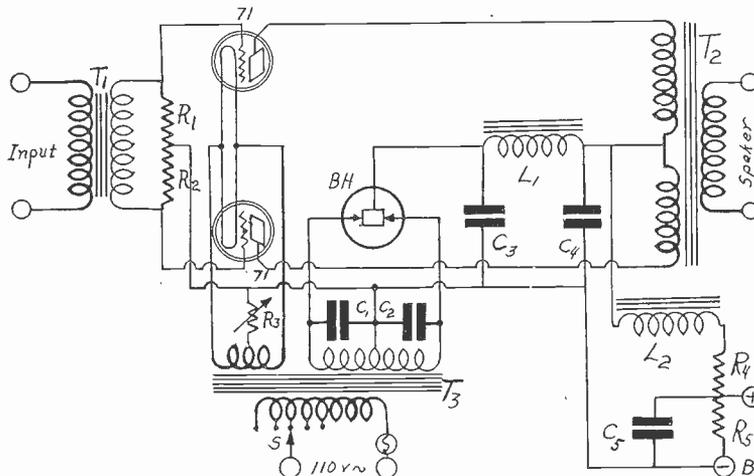


FIG. 1

The circuit diagram of a push-pull stage of power amplification using two -71 tubes, in conjunction with a B and C eliminator employing a Raytheon BH tube.

cent Super Audioformer, Samson AW3, etc. Its ratio is of little importance, but usually the better transformers stick to low or medium ratios. The secondary voltage of this transformer is divided equally between the two tubes of the push-pull amplifier by means of resistances R1 and R2. These resistances should be equal, and it will pay the constructor to take steps to insure that these resistances are closely the same. Each should be about 0.5 meg.

An Insight Into Overloading

Since the maximum input peak voltage to a -71 tube is forty volts, the circuit will not become overloaded until the total voltage across the secondary of the transformer exceeds 80 volts.

This will insure a high output power which will be sufficient for even the lowest audible notes. The 40-volt swing is the maximum allowable when a single -71 tube is used. When two of them are used in push-pull arrangement this may be exceeded without causing distortion. Hence there is considerable reserve power available to take care of unusual demands.

The question now arises as to whether an 80-volt input swing can be undistorted if the previous output of the existing set employs a -99 tube or an -01A tube, as the output (the tube preceding the Fig. 1 arrangement). This can be decided only when the ratio of the transformer T1 is known. Let us suppose that the ratio is 4-to-1. To get 80 volts across the secondary the primary voltage must be 20 volts, or a little more. Now the -99 type tube has an amplification constant of 6.5. If we assume that the impedance of the transformer primary is high enough so that the voltage across the primary at the lower audible frequencies is 2/3 of the total voltage in the plate circuit of the tube, the total voltage must be 30 volts. Dividing this by the amplification constant of the tube, or by 6.5, we get the voltage swing that must be 30 volts. Dividing this by the amplification constant of the tube, or by 6.5, we

get the voltage swing that must be put on the grid of the -99 type tube to give us a voltage of 80 across the secondary of the transformer T1. The division gives about 4.6 volts, which is not excessive to give undistorted output provided that the proper plate and grid voltages are used on the -99 tube. If the -99 type tube will work without overloading with the push-pull amplifier, the larger tubes will also work safely. This conclusion was based on a 4-to-1 transformer having a high impedance primary. The latest and best-known audio transformers meet the requirements.

AC Heats Power Tubes

The loudspeaker can be coupled to the push-pull tubes by means of an output transformer T2. The primary of this transformer should be center-tapped for connection to the plate voltage source.

The filaments of the two power tubes are heated with alternating current taken from a low voltage secondary of the power supply transformer T3. This low voltage winding is center tapped so that the grid and plate returns can be connected to the neutral point.


The grid bias for the power tubes is obtained in the usual manner by means of a resistance placed in the common return. This is R3 (lower left). When one tube is used the value of this resistance is 2,000 ohms, but when two tubes are used it should only be 1,000 ohms, since the plate current will be twice as great. This will give a bias of 40 volts to the grids when the plate voltage is 180 and the plate current in each tube is 20 milliamperes. R3 might well be a Ward Leonard variable wire-wound resistor with a maximum at 2,250.

The plate voltage is obtained from a high voltage winding on the power transformer with the aid of a Raytheon double wave rectifier and a filter system. The total voltage across the high winding should be about 700 volts. The buffer condensers C1 and C2 across either half of the high voltage winding are of .1 mfd. capacity of 1,000 working volts.

LIST OF PARTS

- R1, R2—Two .5 meg. Lynch resistors.
- R3—One Ward Leonard Adjustat, 2,250 ohms.
- R4, R5—Two Ward Leonard 5,000-ohm resistors.
- C1, C2—Two Tobe .1 mfd. condensers, 1,000-volt test.
- C3—One Tobe 2 mfd. condenser.
- C4—One Tobe 4 mfd. condenser.
- C5—One Tobe 4 mfd. condenser (up to 12 mfd., if possible).
- T1—One audio frequency transformer.
- T2—One output transformer, with center tapped primary (Silver Marshall 231).
- T3—One power transformer with one 700 volt or so winding, center tapped; one 5-volt winding center tapped (Thordarson; Acme 2 kw).
- S—One indicating snap switch.
- F—One fuse and receptacle.
- L1—One Acme BA2 choke.
- L2—One fine wire choke coil of about 100 henrys.
- Three standard tube sockets.
- Six binding posts.
- One baseboard 7x10 inches.
- One extension cord with plug.
- Two -71 tubes amplifiers.
- One Raytheon BH rectifier.

COURTNEY PLANE'S INSTALLATION

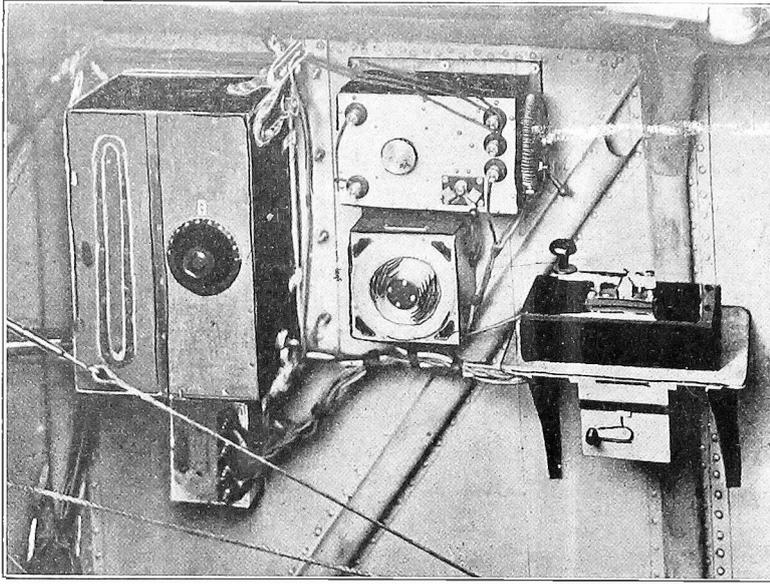

(Herbert Photos)

THE COCKPIT of the *Whale*, Captain Frank T. Courtney's Dornier-Napier Seaplane, in which he planned to fly from Ireland to New York. The neat arrangement of the radio installation is shown. The transmitting key is at the right and the receiver at the left, both within easy reach of the operator's hand. Electric power is obtained from a wind-driven generator atop the fuselage. The antenna system is built above the fuselage and supported by the wings. This is an improvement suggested by the radio troubles of Commander Richard E. Byrd and the Hawaiian fliers, obviating destruction of the aerial in case of a landing in the ocean or flying very close to the water.

Bellows Lists Board's Three Major Problems

Washington, Aug. 8.

Three major problems, according to Commissioner Henry F. Bellows, are now up for decision before the commission, all exemplified in as many applications.

The first is whether a station which is primarily cultural shall have priority over a station which is primarily engaged in advertising for profit.

The second is how far the Radio Commission may go in enforcing the location of a station over the protests of the inhabitants of the community.

The third relates to the claim that each state is entitled under the radio act to have at least one powerful "key" station.

The first involves the application of station KMA, operated by a seed distributing house, for division of time with the frequency of 710 kilocycle with station WSUM, which is maintained by the University of Iowa. Both stations are operating in Shenandoah, Iowa. Station WSUM objects to dividing time on the ground that it is an

educational institution and as such is entitled to preferential treatment over a station which is devoting part of its time to direct advertising of its wares to stimulate profitable sales.

In the second case the Commission is asked to prevent the transfer of station WICC from Bridgeport, Conn., to Easton, Conn., a town near Bridgeport. The spokesmen for Easton claim that the establishment of the station in Easton would prevent reception of outside service. The proposed removal of station WICC is a result of the order of the Commission to stations to locate in the country at a distance from large population centers.

The third case involves the request of Station WJBM for an assignment to the frequency, 1,330 kc with 1,000 watts power. The station claims that Indiana is entitled to at least one large broadcasting station. It also contends that it is unfair for the commission to give New York, Chicago or the other centres priority in high-power.

Sudden Distortion a Mystery

Distortion recently heard in receivers where real quality usually is emitted was traced to two particular stations, one of them the usually incomparable WJZ. There was no such misfortune on several other channels tested. As the complaint was widespread, the sets, blamed at first,

were eagerly exonerated. As the distortion lasted, though not steadily, for a few nights, much comment resulted. A fierce rainstorm preceded the first instance of distortion in transmission, so some surmised that damaged apparatus was temporarily replaced by others not so good, pending repairs.

New Engine House for Naval Station

WASHINGTON.

Sealed bids for alterations to buildings and appurtenances and construction of a new engine house at the Naval Radio Station at Otter Cliffs, Bar Harbor, Me., have been invited by the Bureau of Yards and Docks of the Department of the Navy.

The full text of the invitation for bids follows:

"Sealed bids, indorsed 'Bids for Alterations to Buildings, Specification No. 5416,' will be received at the Bureau of Yards and Docks, Navy Department, Washington, D. C., until 11 o'clock a. m., Sept. 7, 1927, and then and there publicly opened, for alterations to buildings and appurtenances and construction of a new engine house, at the Naval Radio Station, Otter Cliffs, Bar Harbor, Me. Specification No. 5406 and accompanying drawings may be obtained on application to the Bureau or to the Commandant, Navy Yard, Boston, Mass.

"Deposit of a check or postal money order for \$10, payable to the Chief of the Bureau of Yards and Docks, is required as security for the safe return of the drawings and specification. B. L. Reed, Acting Chief of Bureau, July 25, 1927."

Repair Station Ready In Canal

WASHINGTON.

A radio repair shop has been established by the Panama Canal, and it is now prepared to do radio repair work for any vessel requesting it, the office of the Panama Canal in Washington announced. Establishment of the shop, the statement said, is in line with the desire of the Canal to afford facilities for practically any class of repairs to vessels.

The statement set forth:

As a part of its provision of facilities for practically any class of repairs to vessels, the Panama Canal is prepared to do radio repair work for any vessel requesting it. The Electrical Division generally employs one mechanic qualified to make repairs on radio equipment and at present has two such in the organization. There are also in stock some supplies for this class of repair work. With these facilities the organization has been able to make such repairs as have been requested, and it is believed that if there should arise cases which could not be handled satisfactorily they would be exceptional.

How Radio Works for Train Talk

Successful tests of radio communication between the engine and the caboose of mile-long trains have been made by the New York Central Railroad. Short waves and low power are used to minimize interference with other radio services.

The caboose and the engine will carry identical apparatus—a transmitter and a receiver—and both will carry a transmitting and a receiving antenna. Communication can be started from either end by the mere act of lifting the receiver off the hook and pressing a button.

WNYC IS PRECAUTIOUS

WNYC has added a quartz piezo crystal to its equipment for keeping the station on its frequency. It cost \$200.

Higher Power Sought By Two

Washington.

Backed by affidavits from persons and organizations supporting their claims, WTAD, Quincy, Ill., and KOW, Denver, Colo., appealed to the Federal Radio Commission for higher power on their present wavelengths at hearing. The opposition came from stations now on the same respective frequencies and was in the form of affidavits and other papers, no personal appearances being made.

WTAD, owned by the Illinois Stock Medicine Company, asked for an increase from 250 to 500 watts on a frequency of 1,270 kilocycles, basing its request on its desire to broadcast its programs to the farmers of Illinois, Missouri, and parts of Iowa.

One of the owners of the station, which derives its funds from the concern whose name it bears, is W. Emory Lancaster, who presented a letter from the president of the American Farm Bureau Federation, Sam Thompson, endorsing the activities of the station. According to Mr. Lancaster, WTAD broadcasts farm programs and speakers and courses from the Gem City Business College which are all in the interests, he said, of its farm constituency.

The station does not now permit advertising, but expects to do so if it gets enough power to reach a wider audience. The advertising, however, will be indirect, the witness testified.

The application of KOW (formerly KFVR) was for an increase in power from 250 to 1,500 watts on a frequency of 630 kilocycles. The object of the station, which is owned by the Olinger Corporation, described as a group of associated industries with assets of \$4,000,000, is to broadcast to prospective home builders the advantages of living in the State of Colorado, according to the attorneys for the station, George S. Strong and John W. Price, both of Washington.

Objections to adding higher powers to the same wave were forwarded by WSB, Atlanta, Ga., because of possible interference. The objections were contained in affidavits. The Commission also had before it affidavits from other interests opposing the application of the Denver station.

License Given To Klan Weekly

Washington.

The issuance of a license to WFFF, owned by the Independent Publishing Company, of Washington, D. C., was announced by the Federal Radio Commission. The station will operate on a frequency of 1,470 kilocycles (204 meters), using 50 watts of power, according to the terms of the license.

Broadcasting programs are under the auspices of "Fellowship Forum" a pro-Klan weekly newspaper, from the title of which its call letters were drawn. WFFF, will be located at Mt. Vernon Heights, Va., where its manager has announced they will shortly begin experimental broadcasting on their assigned wave and using the designated power.

WHAT HERTZ DID

Heinrich Hertz, the famous German physicist, was the first to send and receive radio waves. He did this in the course of experiments designed to test Maxwell's electro-magnetic theory. Hertz used very short waves and simple apparatus. The distance between transmitter and receiver was only a few feet.

SET FITS VARIOUS CABINETS



A STANDARD SET, which may be removed from its metal cabinet and placed in any one of several more pretentious pieces of furniture he makes, is being marketed by a prominent manufacturer. This strikes a new idea in sets.

New Power Allotment Basis Being Worked Out

Washington.

Federal Radio Commissioner O. H. Caldwell has announced that a new system of determining the amount of power to be assigned to broadcasters is being investigated by the federal body in conjunction with leading engineers throughout the country. It has been found that radio transmitters, he said, are generally more effective in certain directions than others, and that they cause the greatest interference in the direction of greatest effectiveness.

To overcome this difficulty under the present system of allocating several transmitters to one channel, it has been found necessary to ascertain the area of effectiveness of each station for certain operating powers.

"Broadcasting engineers and radio experts are expected to meet with the commission within a few days in Washington," said Mr. Caldwell. "Extensive field tests will be made on wave and radiated energy of several stations throughout the country to determine the comparative amounts of power sent out

in various directions. Then the broadcasting system in the United States will be studied with regard to the field intensity of individual transmitters, and the whole fitted together.

"At present it is impossible to tell how effective a station will be, that is, just what 500 or 5,000 watts of power will mean in terms of field strength about the broadcaster in various directions.

"We are trying to correct just such a case of interfering waves at the present time," he said. "WDRG of New Haven, Conn., operating in the 1,090-kilocycle channel with 250 watts power, interferes with WPG of Atlantic City, N. J., operating on 1,100 kilocycles with 2,500 watts power. Ordinarily the distance between the two stations would be great enough to avoid any interference on the powers used. However, the waves seem to follow the Atlantic Ocean, and geographical separation counts for little."

Others debate this point.

Oh! How I Love to Listen to the Toot-Toot of the Tuba

By Tim Turkey

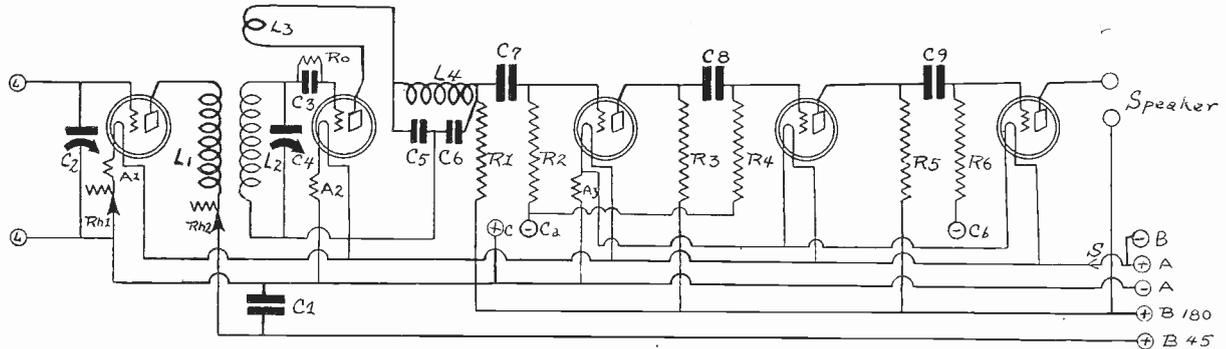


FIG. 1

The circuit diagram of the Tuba Special. A special type of low pass filter is used to stop the radio frequency currents at the detector. The detector and the three audio frequency amplifiers are all put on 180 volts as a means of preventing motorboating.

WHEN I listen to a musical program with the aid of my radio set I want to hear the low notes. I am partial to the sounds of the tuba, the bass drum, the bass viol, the bassoon, the lowest octave of the piano, and to the basso profundo voice. I am even fascinated by the sonorous boom of the savage tom-tom. It is because of my fondness for these base and lowly sounds that I built the Tuba Special receiver, and it is because this set has served me so profoundly that I now describe it so that others with equally base predilections may descend with me into the nether realms of musical sounds, there to enjoy such rare treats as a bass viol solo, a tuba solo, and a rendition of "Rocked in the Cradle of the Deep."

I am keenly interested in having other radio fans join me at the base of the musical scale in a thunderous demand

for more broadcasting of the profound elements of music.

Being partial to the bass notes is equivalent to being partial to a resistance coupled audio frequency amplifier. There is no other circuit, in my opinion, which will bring out the basses so strongly as the resistance coupled amplifier. But to make a resistance coupled amplifier a success it is necessary to take certain precautions, which will be pointed out in the progress of this article.

Two Conditions to Be Met

There are two conditions for the amplification of the lowest notes. One of these is that the stopping condensers in the grid circuits of the amplifier be large. The other is that the grid leak resistances be high. These conditions can be combined into one condition by stating that the product of the capacity of the stop-


ping condenser and the resistance of the leak be large.

The capacity of the stopping condenser cannot be increased indefinitely, because a large condenser will leak more than a small one, and when there is considerable leakage through the condenser the circuit will not behave properly. In this circuit a compromise of .1 mfd. has been effected. With this fixed value of the stopping condenser, the resistance can be made high to increase the product of the capacity and the resistance. Under certain conditions there is practically no limit to the resistance of the leak. I have used successfully 10 megohm resistors in all the grid circuits, that is, for R2, R4 and R6. Higher values can be used if the insulation of the grids is of a high order. The values for the grid leaks mentioned in the list of parts are conventional. They will give good results but it is not necessary to cling to these low values. The use of high grid leak resistances increases the amplification at all frequencies but more at the low.

Conventional and Otherwise

It is also conventional to use .1 megohm resistors in the plate circuits of the tubes, that is, for R1, R3 and R5. But in the interest of high amplification much greater values can be used. I am now using .5 megohm and get excellent results. The use of high values for coupling resistances helps to prevent motorboating by overwhelming the cause of it, and at the same time it increases the amplification. When unusually large plate coupling resistances are employed the applied plate voltage may be increased if desired, but it is not necessary to do so to get distortionless amplification. The question of applied plate voltage will be taken up later.

A point of utmost importance in a resistance coupled amplifier is to use adequate and correct grid bias on all the amplifier tubes. Clearly it is not necessary to do so to protect the tubes from excessive filament emission or to reduce the plate current, as the coupling resistors do that effectively. But it is necessary to use grid bias to get any real amplification and to prevent the tubes from choking up. The grid current will not maintain the grids negative. It will merely prevent the grid voltage from

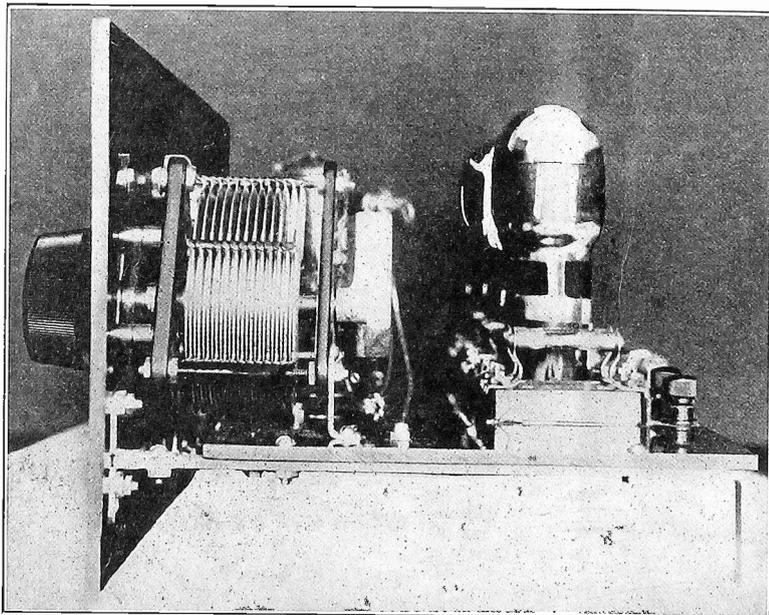

VIEW of right side of the receiver.

LIST OF PARTS

L1, L2, L3—One three-circuit No. 99 Bruno coil to go with .0005 mfd. condenser.

L4—One General Radio RF choke coil.

C1—One Dubilier .01 mfd. condenser.

C2, C4—Two General Radio .0005 mfd. tuning condensers.

C3—One Polymet grid condenser with resistance clips.

C5, C6—Two .0005 Polymet condensers.

C7, C8, C9—Three .1 mfd. Daven condensers (built into couplers).

Rh1—One Carter 10-ohm midget rheostat.

Rh2—One Carter midget 25,000-ohm variable resistance.

S—One Carter filament switch.

R0—One 2 megohm Daven glastor grid leak.

R1, R3, R5—Three Daven Glastor .1 megohm resistors.

R2—One Daven Glastor 1 megohm resistor.

R4—One Daven Glastor .5 megohm resistor.

R6—One Daven .25 megohm Glastor resistor.

A1, A2—Two No. 1A Amperites.

A3—One 1 ampere Amperite (No. 4).

Three Daven resistance couplers with resistor clips.

Five UX sockets.

Eight Eby binding posts.

Three small binding posts.


Two Carter phone tip jacks.

Two dials.

One tickler knob.

One hard rubber panel, 7 x 18 inches.

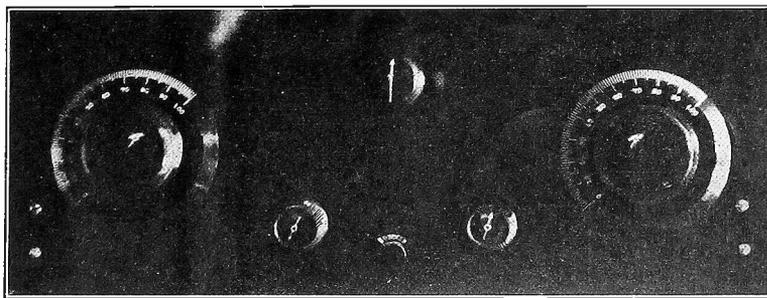One hard rubber baseboard, 7 x 17 inches.



THE FRONT PANEL

connected to 180 volts it does not mean that the effective plate voltage on the tube is 180 volts. It is considerably less, on account of the voltage drop in the resistor R1. But effective plate voltage on the detector is not the criterion of correct adjustment. Detection efficiency is. The detector is more efficient when the applied voltage is high than when it has the conventional value.

High Mu Detector Tube

As the coupling between the detector and the first audio tube is by means of resistance, it is desirable to use a high mu tube for detector. A mu 20 tube gives excellent results as detector under the conditions of operation in this circuit.

The loudspeaker is connected directly to the output of the last tube. This is permissible for the semi-power tube employed. If desired, an output transformer can be used, or the speaker can be coupled to the tube by means of a series

Phone tip jacks are used for the output.

It is necessary to employ some means of separating the radio from the audio frequency currents in the output of the detector. A special filter arrangement has been employed for this purpose. It consists of two equal condensers C5 and C6, of .00025 mfd. each, and a radio frequency choke coil, L4. It is customary to employ a filter composed of a choke coil and one condenser C5, but in such a filter the coil is useless on account of the high resistance R1 in series with. The second condenser C6 by-passes this resistance and gives the coil a chance to check.

Avoids Suppressing AF

While the radio frequency currents can be prevented from reaching the audio amplifier much more effectively by using larger condensers and a greater inductance in the choke, it is not advisable to do so because such a combination would also suppress the amplitude of the higher audio frequencies. The filter as described very effectively stops the radio frequencies as low as 500 kilocycles, yet it has no appreciable effect on any audio frequency as high as 10,000 cycles.


The detector is regenerative, thus adding enormously to the sensitivity of the receiver. A Bruno No. 99 three-circuit tuner L1L2L3 is used. The secondary L2 of this tuner is designed to work with a .0005 mfd. condenser C4.

The grid condenser and leak have the usual values of .00025 mfd. and 2 megohms, respectively.

The set is particularly intended for local reception and consequently a loop is used. This is tuned with a .0005 mfd. condenser, C2.

Three Volume Controls

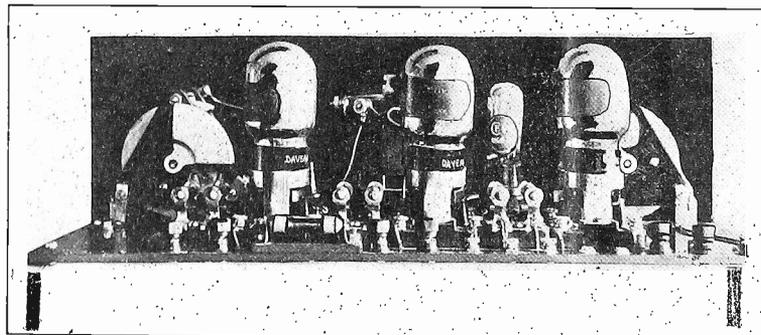There are three methods of controlling the volume in the set, and all three are necessary at times. The first is the rheostat Rh1 in the filament circuit of the RF amplifier. This rheostat is in series with a 1A Amperite, so that the filament current can be varied from normal down to zero. A 10-ohm rheostat is sufficient. [Theoretical data next week.]



REAR VIEW.

going very much positive. A grid bias of suitable value will prevent grid current and distortion and it will increase the amplification.


The correct bias to use will depend on the mu of the tubes and on the applied plate voltage. If the mu is 20 and the voltage is 180, the bias should be between 3 and 4½ volts. If the last tube is a mu 6 and the plate voltage is 180, the grid bias should be about 18 volts, or a little more.

180 Volt Line to Detector

Note that the plate returns of the detector and the three audio frequency tubes are connected to the common 180-volt bus. There is nothing unusual in connecting the resistance coupled tubes and the power tube to the same high voltage, but it is not often that the detector is thus connected. The reason for connecting the detector plate return to the 180-volt point is to prevent low frequency motorboating. As the circuit is connected, there are four tubes on the common impedance which causes motorboating, and such a circuit is stable on low frequencies. The plate return of the RF tube is connected to 45 volts.

Although the detector plate return is

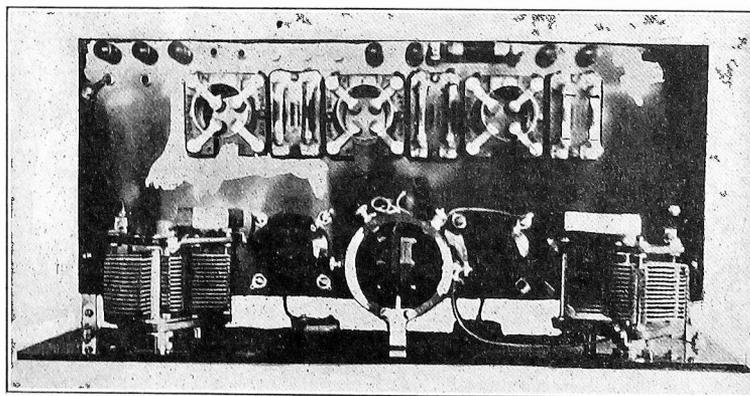condenser and a choke coil. The condenser in series with the speaker should be at least 8 mfd. and the choke coil should have an inductance of at least 100 henrys. In the interest of the low notes the speaker should be connected directly to the tube, since both of the other two methods depress the intensity of the lower notes.



LOOKING at the set from the top.

Rule Upset; 7 Licensed

Washington.

The granting of seven construction permits and licenses to new stations was announced by the Federal Radio Commission. Although it is the stated policy of the Commission not to allow new stations to go on the air, it was explained orally by Commissioner Eugene O. Sykes, in whose district the stations are located that all had been granted construction permits prior to the passage of the Radio Act of 1927.

To have refused to allow them to broadcast would be to deprive them of their facilities, it was explained. Moreover, Mr. Sykes added, the regions involved already have only a limited number of stations.

"These permits," he said in a formal statement, "were granted to stations which were constructed prior to the passage of the Radio Act of 1927.

"They were held up by the Federal Radio Commission pending action by stations already licensed and were assigned frequencies which in the judgment of the Federal Radio Commission will not be harmful to other broadcasters.

"The Commission feels that these stations will render a real public service in States which heretofore have had very limited broadcasting facilities, and with their low power will not create material new interference."

Following is the list of construction permits and licenses as announced by the Commission.

WKBJ, Toccoa Falls Institute, Toccoa, Ga., issued construction permit specifying 1,430 kilocycles—250 watts power.

KHMC, Harlingen, Tex., Harlingen Music Company, issued construction permit specifying 1,270 kilocycles—100 watts power.

WTHS, Atlanta Technological High School, Atlanta, Ga., issued construction permit specifying 1,320 kilocycles—200 watts power.


KFYO, Kirksey Bros., Battery & Elec. Co., Breckenridge, Tex., issued construction permit specifying 1,420 kilocycles—15 watts power.

KGGF, Dr. D. L. Connel, Picher, Okla., issued license to operate on 1,450 kilocycles—100 watts power.

KLCN, Daily Courier News, Edgar C. Harris, Publisher, Blytheville, Ark., issued license to operate on 1,050 kilocycles—50 watts power—6 a. m. to 6 p. m. only.

KGGH, Bates Radio & Electric Co., Cedar Grove, La., issued license to operate on 1,410 kilocycles—50 watts power—shares time with Station KDGX.

GOOD LOCATION FOR THE RESISTORS

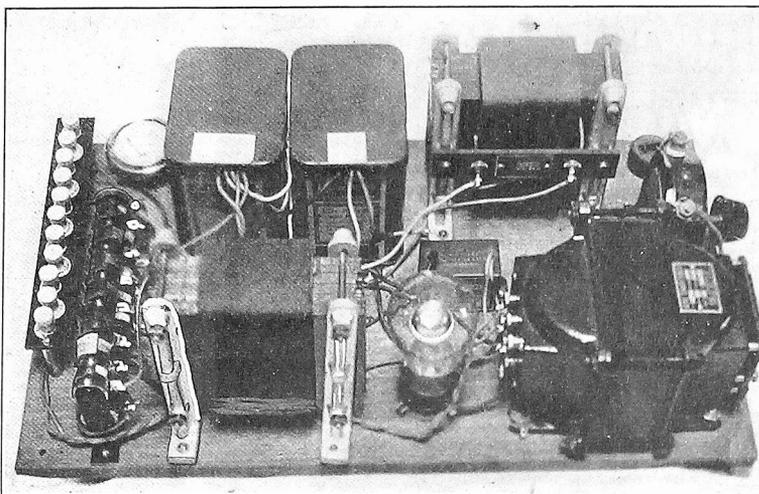

(Goodwin-Bruno)

IN an A B C eliminator the resistance bank for affording variety of output voltages should not be bottled up nor should it be placed very close to the filter condensers. The reason is that the resistance heats up—no matter what kind it is—and requires ventilation. The photograph shows an A B C eliminator, using the Raytheon BA tube, with the Ward-Leonard resistance bank at left. The rheostat at right is for control of the input voltage and is also of Ward-Leonard manufacture. It goes in series with the power transformer primary.

WGY's 100,000 Watts A Hit With Listeners

Test programs on WGY's 100-kilowatt transmitter have brought an unexpected volume of listener response. Especially interesting for the engineer is the fact that there is almost unanimous indorsement of the temporary power increase and enthusiastic applause for the quality and volume of the signal as well as the sharpness of tuning.

A survey of the letters received at the conclusion of the third early morning test indicates that:

Signal strength over the region east of the Mississippi river and north of North Carolina is equal to that of station operating within fifty miles of the receiver.

WGY was heard with good volume and clarity in parts of country not reached since early in the Spring.

The signal strength is so great that static, even during severe electrical storms, was completely overridden and the program could be appreciated for its musical quality.

Fading is not appreciably circumvented

by high power in areas within 300 miles where WGY's normal transmissions faded. But many of the distant listeners reported that fading was less frequent and less pronounced.

Modulation was excellent and quality of reproduced signal above the average.

100 kilowatt signal tuned sharply. Those with sensitive receivers were able, in many cases, to tune out WGY and tune in more distant stations whose frequency was separated but 20 kilocycles from WGY's frequency.

Tests on 100 kilowatts will be continued by the radio engineers of the General Electric Company every morning, from 12 to 1, eastern standard time, under the special license granted by the Federal Radio Commission for a period of thirty days. Reports of listeners are earnestly requested by the engineers as such letters will be of value to them to supplement the reports of field men who are making measurements and observations at many places in the United States.

N.B.C. Asks Permit for a Water Still

An application to the Bureau of Prohibition at Washington, D. C., has been made by the National Broadcasting Company for a permit to operate a still at the new transmitting station, now nearing completion, at Belmore, L. I. Distilled water is necessary to cool the giant tubes as any other water leaves deposits on the plates. Recently, in discussing apparatus for the new transmitter, it was suggested that a small still be installed to distill three gallons of water an hour. This is, probably, the first record received by the Bureau of Prohibition from a radio station for permission to operate a still, as necessary equipment for broadcasting.

Station Locates Her Missing Son

The directors of WGL, New York, were asked by a young woman to help find her son who had been missing for about four years. This poor mother had become seriously ill, owing to worry. WGL for several days broadcast a description of the missing boy as well as several other details about him.

Nothing further concerning this matter was heard for several weeks. Then a long distance telephone call was received from Baltimore by the mother of the missing boy. It was from none other than this missing person himself. To quote from the letter written to WGL by this now joyful mother: "Believe me, gentlemen, it certainly has given me a new grip on life, thanks to management of WGL, to have my son with me again."

Fairs Aplenty on Radio Day

Wednesday, September 21st will be National Radio Day.

On this date in addition to radio shows in Rochester and St. Louis the Radio World's Fair will be held in New York City in the New Madison Square Garden with more than 300 exhibitors and an attendance estimated at more than 150,000 people with more than 10,000 radio visitors from all parts of the country present in the form of exhibitors and dealer visitors.

Local banquets in conjunction with the Radio Industries Banquet in New York City are being planned in many of the fifty-odd cities where the radio banquet program will be broadcast.

At these local banquets the speeches from New York will be received.

SIXTH YEAR
RADIO WORLD
The First and Only National Radio Weekly

Member, Radio Publishers Association
 Radio World's Slogan: "A radio set for every home."

TELEPHONES: BRYANT 0558, 9559
 PUBLISHED EVERY WEDNESDAY
 (Dated Saturday of same week)
 FROM PUBLICATION OFFICE
HENNESSY RADIO PUBLICATIONS CORPORATION
 145 WEST 45TH STREET NEW YORK, N. Y.
 (Just East of Broadway)
 ROLAND BURKE HENNESSY, President
 M. B. HENNESSY, Vice-President
 HERMAN BERNARD, Secretary
 European Representatives The International News Co.
 Breams Bldg., Chancery Lane, London, Eng.
 Paris, France: Brentano's, 8 Avenue de l'Opera

EDITOR, Roland Burke Hennessy
 MANAGING EDITOR, Herman Bernard
 TECHNICAL EDITOR, Lewis Winner
 CONTRIBUTING EDITORS:
 J. E. Andersen, Capt. Peter V. O'Rourke, and
 James H. Carroll

SUBSCRIPTION RATES
 Fifteen cents a copy. \$6.00 a year. \$3.00 for six months. \$1.50 for three months. Add \$1.00 a year extra for foreign postage. Canada, 50 cents.
 Receipt by new subscribers of the first copy of RADIO WORLD mailed to them after sending in their order is automatic acknowledgment of their subscription order. Changes of address should be received at this office two weeks before date of publication. Always give old address; also state whether subscription is new or a renewal.

ADVERTISING RATES
 General Advertising

1 Page, 7 1/2"x11"	482 lines.....	\$300.00
1/2 Page, 7 1/2"x5 1/2"	231 lines.....	150.00
1/4 Page, 8 1/2" D. C.	231 lines.....	150.00
1/4 Page, 4 1/2" D. C.	115 lines.....	75.00
1 Column, 2 1/4"x11"	154 lines.....	100.00
1 Inch	10.00
Per Agate Line75

Time Discount

52 consecutive issues	20%
26 times consecutively or E. O. W. one year	15%
4 consecutive issues	10%

WEEKLY, dated each Tuesday, published Wednesday.
 Advertising forms close Saturday, eleven days in advance of date of issue.

CLASSIFIED ADVERTISEMENTS
 Ten cents per word. Minimum 10 words. Cash with order. Business Opportunities ten cents per word, \$1.00 minimum.

Entered as second-class matter March 23, 1923, at the Post Office at New York, N. Y., under the Act of March 3, 1879.

Interesting Fallacies

Motorboating is caused by residual ripple in the plate voltage supply.

Motorboating is caused by blocking of the grids in the amplifier.

Motorboating is non-oscillatory if the frequency is less than 16 cycles per second.

Radical reduction of the grid leak resistance stops motorboating without affecting the amplification of the low notes.

A high inductance choke coil is effective when it is connected in series with a grid leak or a plate coupling resistor.

Small stopping condensers and low value grid leaks can be used with no decrease in the amplification of the low notes.

Large by-pass condensers can be placed across the line without reducing the higher audio notes.

Volume can best be controlled by cutting down the filament current in the power tube, because there the volume is greatest.

Interesting Facts

The worst radio quality is heard in some radio stores. It is not fair to the radio industry nor to the individual himself to take this stuff as typical of what radio can do.

Complete radio installations in which all batteries have been replaced by AC operated substitutes are now available.

Over-selectivity cuts the higher frequencies from the output and renders the signal less pleasing and less intelligible.

There is too much dance music broadcast these days.

Marconi was the first man to erect an antenna for radio transmission and reception.

Benjamin Franklin was the first man to erect an antenna for receiving static.

A signal strength of 5 millivolts per meter is satisfactory for reception. If the signal strength is still more intense the reception is more reliable.

The field strength of a radio wave is measured in millivolts, or microvolts, per meter. If the potential difference between two points one meter apart, one above the other, is one millivolt, the intensity of the vertical component of the wave is 1 millivolt per meter. An antenna 10 meters high would pick up a voltage of 10 millivolts in such a field. If the field strength were 5 millivolts per meter, the antenna would pick up 50 millivolts.

A radio wave which leaves the transmitting station with the front vertical, or perpendicular to the ground, gradually topples over so that the wave front is parallel to the ground, provided that it travels faster in air than in ground. Compare the wave front with a reed which is lodged in the ground at one end and is free at the other. The wind bends it over. Also compare the wave front with water waves near shore and out at sea. No matter what the direction of the wave out at sea, near a sloping shore line, the wave front is always parallel to the shore. This is due to the fact that the velocity of the wave is slower in shallow water than it is in deep water.

The power output of a tube is measured by the current times the voltage. In the -71 type tube the current is heavy and the voltage moderate; in the -10 type the current is relatively low and the voltage is high. Although the current in the -10 tube is less the power is much greater than in the -71 due to the difference in plate voltage.

A high impedance speaker can be connected to a low impedance tube without great loss in output, but a low impedance speaker cannot be connected efficiently to a high impedance tube.

Resistors used in radio circuits will not always carry all the current which is sent through them. They burn out. To prevent burnout ascertain the safe wattage dissipation of the resistor and then use it only within the limits.

Stopping condensers can only withstand a certain voltage. When this is exceeded the insulation breaks down and

GOODSINGERS ARE SCARCE

Even a radio singer must know how to sing.

It seems almost impossible to convey this thought to the thousands of woefully deficient vocalists who weekly descend upon the broadcasting stations of the country say officials of KFI.

Students of a month's standing besiege radio stations sure that overnight fame and fortune await them. Many cannot read music. Few can produce a correct scale. None would dare to approach concert or theatrical managers, but all consider the microphone legitimate prey. Of one thousand applicants, less than ten are really acceptable, and perhaps only one is a valuable find.

"A good radio singer must have a flawless production," Earl C. Anthony, owner of KFI points out. "This perfection is not necessary in concert work for there facial expression, costume, personality and the distance of the singer from the listener mask even major defects. A radio singer stands within three feet of the microphone and the loud speaker is only a few feet from the auditor. Few artists can sing in your ear and make you like it.

"The concert artist may work with the vigor and broad strokes of a mural painter," Anthony continues, "while the radio singer must sing with the meticulous exactness of a painter of miniatures. The radio voice must not be 'breathy' as the impact of the breath column on the microphone may overload the tubes. Correct breathing from a well supported diaphragm is necessary for a firm free tone. Clean unexaggerated diction is imperative to prevent hisses and gurgling noises. Playing to what is really a blind audience, color and feeling are the soul of the radio voice. Great volume is not necessary, but the muscular ability to maintain a certain tone level and color is. Also the artist must have an innate sense of dramatic effect; must be able to pull down volume on forte passages and still achieve power. Tempo, so often disregarded, is one of the rarest and most valuable aids of the broadcast vocalist."

In the ruck of the three gold rushes—'49, movie and radio—have trailed thousands of incompetents. Time weeds them out, however, and in the next five years the supply of bad radio artists will have exhausted itself running from studio to studio. Then radio stations will be able to concern themselves with using the suitable material at hand rather than struggling to evade the inadequate.

Announcer Not Rattled; It's the Manuscript

When you hear an announcer speaking rhythmically and monotonously accompanied by a crackling noise, don't blame the noise on static. It may be the rattling of paper from which the announcer is reading. KFI, Los Angeles, has a rule which prevents its announcers from holding papers in their hand at the microphone. The sheets must be flat on a table.

the condenser is useless. It is better to buy a condenser with a large margin of safety in the first place than to do it after the cheaper condenser has broken down.

Condensers of the electrolytic type are self-healing after a breakdown. So are air condensers. Condensers with solid dielectric are not and after breakdown they are useless.

June Exports up; Kindred Lines Slow

While the value of exports of radio apparatus during June gained considerably, total exports of electrical equipment during the month declined from May and from June of last year, according to a statement issued by the Electrical Division of the Department of Commerce.

Exports of radio apparatus during June, 1927, recorded a gain over June of last year of \$138,221 to \$651,664. Shipments of batteries, including flashlight, other primary, and storage, also showed an increase of \$103,346 to \$673,721.

All classes of radio sets and parts showed increases with the exception of receiving set accessories, which class decreased \$16,058 to \$134,197.

The largest individual increase was for tubes, which registered a \$53,905 increase to \$112,756 as compared with June last year. Total shipments of radio apparatus for June this year amounted to \$45,431 more than for May, which were valued at \$606,233.

All items under the class of batteries showed a gain during June, flashlight batteries gaining \$69,104, other primary batteries, \$8,862, and storage batteries, \$25,380. The total for this class, \$673,721, is more than a \$100,000 gain over the \$570,375 of June, 1926.

Women Musicians Prefer the Piano

Baltimore.

The piano is the most popular instrument with women musicians, according to facts gleaned from the files of WBAL, Baltimore. The majority of pianists heard over WBAL have been women, and of all the many instruments now available for instruction, more women "take" to the piano than any other instrument. There are, of course, numerous women

organists, but these are not included in this survey.


There are four instruments which women musicians play, according to WBAL's artists' file. These are the piano, then the violin, cello and harp. Apparently, feminine musical fancy does not include flights to fields that have been occupied solely by men artists for generations, and, seemingly, women musicians are content to remain in the better known instrumental fields, and are leaving such instruments as the clarinet, oboe, cornet, flute, viola, horn, etc., entirely free for their masculine contemporaries.

Oscillation Bothers Him On the Low Waves

MY receiver oscillates too violently on the shorter wavelengths and I cannot stop the oscillations even by turning the tickler full on in reverse. What can I do about it? — FRANK EDMONDS, Bridgeport, Conn.

(1)—Put a rheostat of higher value in the filament circuit of the radio frequency tube so that the current in that tube can be cut down below normal.

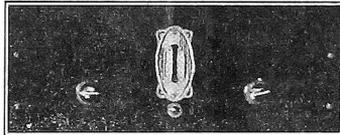(2)—Put a variable resistor of 0 to 25,000 ohms in the plate lead to the radio frequency tube. Use as much of this resistance as necessary to stop the oscillations.



Powertone Drum Control
Complete Kit, \$23.50 Built to Order, \$1.50 Extra
Diamond Kit..... \$37.50
Diamond Eng. Panel..... 1.95
Web Cone Unit..... 3.45
POWERTONE CONE KIT
18-inch\$9.00 24-inch\$10.00
Finest paper, beautiful metal stand, Powertone Unit, etc. Easily built, fully guaranteed.

Write and Get Our New and Low Price on Complete Bruno and Other Lines

B. C. L. RADIO SERVICE CO., Inc.
220 FULTON ST., N. Y. CITY

25 Cents Brings ALL THIS!

One Official Blueprint of the Five-Tube Diamond of the Air

One official booklet describing in detail how to build this famous set, wind coils, etc.

Act Now! Send That Quarter to
RADIO WORLD
145 West 45th Street, New York City

TELL YOUR NEWSDEALER

to save you a copy for each week you are away on your vacation, so that when you return you will have a complete file of Radio World. If you require any summer numbers of this paper, send 15c for each issue desired to Circulation Manager, Radio World, 145 West 45th St., N. Y. C.

Power Clarostat Sizes

The Power Clarostat is now available to builders of home-made radio power devices in three resistance ranges, namely: 0-10 ohm, intended for the control of standard tube filaments wired in parallel, or again for line voltage control and the group control of secondary voltages; 25-500 ohm, intended for the control of series-connected filaments especially when used in series with the B-voltage tap resistances; and the 200-100,000 ohm, especially intended for the control of series-connected filaments when controlled alone, or directly from the maximum voltage terminal of the A B C radio power unit.

FLECHTHEIM

Superior Condensers for Socket Power Circuits Are UNCONDITIONALLY GUARANTEED Not to Break Down In Use if Operated At or Below Their Rated Voltages. Flechtheim Quality Condensers, in compact aluminum cases, are designed for Socket Power Sets and Power Amplifiers, with a working voltage up to 600 volts D.C., and in Filter Circuits for plate supply. Accurate when made and remain accurate within 5% of their rated capacities. Inquiries from the Trade Solicited.

Manufacturers Supplied


A. M. Flechtheim & Co., Inc. 275 B'way New York

FLECHTHEIM CONDENSERS

BEST BY TEST
Dealers! Write for Attractive Proposition!
VENUS RADIO CORP.
142 LIBERTY STREET, NEW YORK CITY
Sole distributors of Flechtheim Condensers and Imperial "B" Cases for these states:
N. Y., N. J., Conn.

**RADIO WORLD'S
QUICK-ACTION
CLASSIFIED ADS**
10 CENTS A WORD
10 WORDS MINIMUM
CASH WITH ORDER

SELECTED FOR THE ONE DIAL WITZ

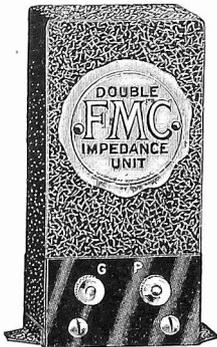

Three
FMC
Double
Impedance
Units

After exhaustive tests of all similar apparatus FMC Double Impedance Units were selected because of their superior tone quality, ease of mounting and general efficiency. Price, per unit

\$600

Ford Radio & Mica Corp.
111 Bleecker St. New York

"Licensed under Miller Patent No. 1589692" If your dealer cannot supply you, we will ship to you direct upon receipt of price.

Be sure to take RADIO WORLD along with you on your vacation, or read it while you are at your summer home so that you will not miss a copy; send \$1.50 for three months subscription and RADIO WORLD will be sent to you all summer. RADIO WORLD, 145 W. 45th St., N. Y. C.

SETS, ELIMINATORS, PARTS—Bargain literature FREE. Radio, R427 East 16th Street, New York.

USE AN OVERSIZE SPEAKER choke eight-pound 100H, 125MA—\$5.75. 550V Raytheon transformers—\$3.50. Write for lists. Radio Parts Sales Co., Orange, N. J.


HOW TO BUILD RADIO WORLD'S Four-Tube Universal Receiver fully described by Herman Bernard in the March 12, 19 and 26 issues of RADIO WORLD. Send 45c and get these three numbers. RADIO WORLD, 145 West 45th Street, New York City.

NEW DE LUXE BST RECEIVER—5-Tube Set, resistance coupled audio, built-in C eliminator, genuine mahogany cabinet. Price, \$60. Five-day money-back guarantee. GUARANTY RADIO, GOODS CO., 145 W. 45th St., N. Y. City.

VALET AUTOSTROP RAZOR—The only razor that sharpens its own blades. Highly polished, nickel-plated, self-stropping Valet AUTOSTROP Razor, with one blade, in velvet lined metal case. Leather strop especially prepared, and complete outfit in neat, lithographed carton. Mailed post-paid on receipt of 50c. SPECIAL: Send \$2 for one-third of a year subscription for Radio World (yearly price \$6) mention this particular ad, and complete "Pal" set will be sent as a premium. If already a subscriber, your subscription will be extended three months. THE COLUMBIA PRINT, 145 West 45th Street, New York City.

LINDBERGH PLANE SPEAKER. Pictures and explanatory article appeared in Radio World dated June 25, 1927. Sent on receipt of 15 cents or start your subscription with that number. Radio World, 145 W. 45th St., N. Y. C.

COMPLETE AND LATEST LIST OF STATIONS appeared in Radio World, dated Aug. 6. Sent on receipt of 15c., or start your subscription with that number. RADIO WORLD, 145 West 45th St., New York City.

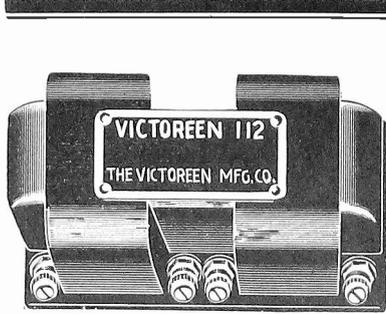

Victoreen 112

Audio Transformer Unit

New, because for the first time two scientifically developed audio transformers are successfully combined into one unit, giving utmost simplicity and efficiency.

Different, because of its radically different design and the recommended use of two "112" tubes, with high plate voltage.

Better, because for the first time, broadcast programs are reproduced with the same clarity and naturalness as is heard in the original.

Simple to install in either new or old sets.

PRICE \$22.00

Victoreen R.F. Transformers, Master Control Units, Rheostats, Potentiometers and Audio Control Units are the recognized standard of quality. Send for complete folder.

The Geo. W. Walker Co.

Merchandisers of Victoreen Radio Products

6528 Carnegie Avenue, Dept. RW
Cleveland, Ohio

Thoriated Filaments Are Called Critical

Three types of substances are used as the source of electrons in present-day vacuum tubes, according to S. Ruttenberg, chief engineer of the Radiall Company. These are the oxides of certain metals, such as calcium, barium, strontium, etc.; the pure metals themselves, such as tungsten or molybdenum; and these pure metals mixed with a small amount of thorium to produce the so-called thoriated or X-L filament.

The oxides are coated on a wire of platinum or nickel, and give off their electrons at temperatures below the melting points of these metals. The pure tungsten filaments are operated at about 2,400 or 2,500 degrees Centigrade, while those containing thorium are operated around 2,000. Operating at the same temperature, the emission from the thoriated tungsten filament is about five thousand times greater than from tungsten. A pure thorium filament, however, vaporizes and melts at too low a temperature to obtain sufficient emission from it to make a successful tube. It, however, evaporates much more slowly in the form of a thin film on a tungsten base, and so it is used in this condition.

The popular —01A as well as the —99 type of tube has a thoriated filament, with a tungsten base containing one or two per cent. of thorium. This thorium, at the proper operating temperature, slowly diffuses to the surface of the filament as thorium metal.

Quite Some Emission

The large emission of the thorium is thus obtained at the high operating temperature of the tungsten filament. Some idea of the quantity of electrons given off from the hot filament is gained from the fact that 6.28X10.19 electrons escape per second from one square centimeter of surface when the emission current is one ampere.

There is a critical temperature for the filament of any vacuum tube, according to Mr. Ruttenberg. Especially is this true in the case of thoriated tungsten tubes, wherein a delicate balance must be struck between the heat necessary to boil out the required quantity of thorium to coat the surface, and the excessive heat which results in burning off the thorium coating so that veritable bald spots are formed with the paralyzing of the tube in short order.

A tube may be deactivated or paralyzed, and still light. There is also the danger of altering the crystal structure of the tungsten filament, either by excessive or by insufficient temperature, in either event weakening the filament permanently.

Tests recently conducted in the Radiall laboratory indicate that the majority of radio enthusiasts do not burn their filaments at the proper temperature when using hand-operated rheostats.

Usually Excessive

In the usual case the filaments are operated at from 10 to 30 per cent. excessive voltage, reducing the tube life by hundreds of hours, not to mention the lowered efficiency of the receiver through serious deactivation. In cases where the radio enthusiasts are fretful of harming the tubes through excessive voltage, tests indicate that tubes are operated at as much as 40 per cent. below the proper temperature, again impairing the crystalline structure of the filament while at the same time introducing distortion due to the insufficient space current in the tubes.

Two methods are recommended for the proper operation of vacuum tubes: First, a high-grade voltmeter which, in conjunction with the manually-operated rheostat, permits of adjusting the filament current for the proper filament operation from time to time in compensating for fluctuations in the filament or A battery; secondly, the use of Amperites, the self-adjusting rheostats, which automatically hold the filament temperature of each tube at the correct value despite fluctuations in filament or A battery.

Powertone

36" Giant Cone Speaker \$12.00
Kit, including stand

using the new
Powertone Unit

List, \$6.50

Used in 18", 24" and 36" Speakers. Kit includes 1 front sheet (designed), 1 back sheet, 2 metal Baffle Rings, 1 mounting bracket, 1 set Apex fittings, 1 POWER-TONE UNIT, 1 stand, 1 tube cement, 1 set screws, nuts, etc.; full instructions. Can be assembled by anyone in half hour.

At Your Dealers or Direct on Receipt of Check or Money Order. Jobbers and Dealers, Write!



Powertone Electric Co.
220 Fulton Street, New York City

More than HUMAN

The only automatic self adjusting filament control, supplying at all times just the current your tubes require. Insures 100% tube performance. Safeguards against damage. Eliminates hand rheostats. Simplifies wiring. Insist on Amperite. Refuse substitutes claimed just as good. Price \$1.10 complete.

Radiall Co., 50 Franklin St., New York City



Write Dept. RW 18 for FREE Hook-Ups

AMPERITE
REG. U.S. PAT. OFF.
The "SELF-ADJUSTING" Rheostat

FILL OUT AND MAIL NOW
SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City
(Just East of Broadway)

Please send me RADIO WORLD for months, for which

please find enclosed


SUBSCRIPTION RATES:
Single Copy \$.13
Three Months 1.50
Six Months 3.00
One Year, 52 Issues 6.00
Add \$1.00 a Year for Foreign Postage; 50c for Canadian Postage.

New and Improved FRESHMAN MASTERPIECE

AT AUTHORIZED
FRESHMAN DEALERS ONLY

COMPLETE LIST OF STATIONS
appeared in Radio World, dated Aug. 8. Sent on receipt of 15c., or start your subscription with that number. RADIO WORLD, 145 West 45th St., New York City.

Choke Coil

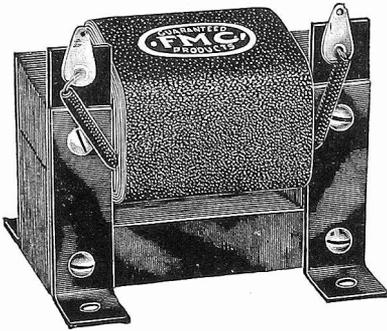

An impedance designed for use in connection with a B eliminator or as an output choke for use with a power tube in the last stage of the receiving set is made by Ford Mica Co. The core is of fine electrical steel, ample in size. The large wire used in the coils gives it a current capacity of 90 milliamperes which is ample for use in any eliminator and the resistance is low thus keeping losses at a minimum. Using the choke for a B eliminator it is preferable to use two chokes as recommended for the Raytheon tubes, although in some cases, where the output is low, one choke will be sufficient. This unit is but one of a large line of reliable radio parts made by the Ford Mica and Radio Corporation, 111 Bleecker Street, New York City.

Makers of Clarostat Double Their Space

The American Mechanical Laboratories, manufacturers of Clarostat, have moved their plant and offices from the top floor to the first and second floors of their own building at 285 North Sixth Street, Brooklyn, N. Y., thus doubling their former space. Additional equipment has been installed in the enlarged plant, so as to take care of the steadily increasing demand for the Standard type Clarostat as well as for the Power type and other types now coming into extensive use with the advent of the A B C radio power units.

CARTER

PARTS

as usual—specified
Rheostats
Resistors
Switches
in

TUBA SPECIAL

Ask your dealer to show you why.
In Canada: Carter Radio Co., Ltd., Toronto

MEMBER
RMA

Carter Radio Co.
CHICAGO

CONTINENTAL

DIE CAST CONDENSER Double Condenser
MADE IN CAPACITIES OF \$500
.0035 and .0005 Mfd.....

THE CONTINENTAL CONDENSERS are famous for their scientific design, sturdiness and precision workmanship. The new models will meet the most exacting requirements.

The Continental UNI-SWITCH

This automatic, double-throw relay switch is in great demand everywhere. It is easy to sell because it makes any set of three or more tubes automatic and helps the dealer to sell \$3.00 eliminators and trickle chargers.

We have taken over the manufacture and sale of the new, improved

"TURNIT" GRID LEAK

Patented by Chas. E. Bonine
Variable from .5 to 12.6 Megohms
NON-EVAPORATING

\$1.00

If your jobber cannot supply you write us direct
GARDINER & HEPBURN, INC.

611 Widener Building, Philadelphia

Why is the Karas Equamatic the Most Efficient Receiver Ever Designed?

Write Us for Full Information

KARAS ELECTRIC CO.

4039 HD, No. Rockwell St., Chicago, Ill.

Make any Good Receiver
BETTER

CEC TUBES
C.E.MFG.CO.
Providence
R.I.



WATCH EXPIRATION OF YOUR SUBSCRIPTION

Subscribers will note that the end of their subscriptions is indicated on the labels on wrappers. If your wrapper shows a date earlier than the current issue, please send payment for renewal. Changes in expiration dates on wrappers appear two weeks after receipt of renewal. PLEASE ALWAYS INDICATE WHEN SUBSCRIPTION IS A RENEWAL.

RADIO WORLD, 145 West 45th Street, New York City (Phones: Bryant 0558-0559)



There is a
Vitrohm
Radio Resistor
for EVERY circuit

MORE than 90 standard Vitrohm Resistors and Rheostats cover the entire resistance need of every socket power circuit now on the market.

As new circuits and new resistance needs arise, Ward Leonard will develop new resistor units scientifically correct for the work to be done.

Vitrohm Resistors and Rheostats are guaranteed unconditionally for continuous duty in any circuit where they operate within their watts dissipation rating—and Vitrohms have the highest continuous-duty watts dissipation rating without resistance change of any resistor.

Bulletin 507 covers Vitrohms for radio. Send for it. There is no charge.

Ward Leonard
ELECTRIC COMPANY
Mount Vernon
N. Y.



2100 intelligent questions

2100 correct answers

Ratings of 62 celebrities

and

THE SUPER-TEST

Ask Me Another

Series 2

The second question book

THE VIKING PRESS

Sent, postpaid, for \$1.00

THE COLUMBIA PRINT
145 West 45th St., New York

Good Back Numbers of RADIO WORLD

The following illustrated articles have appeared in back issues of RADIO WORLD, 1924-1927:

1926

- Oct. 9—A Practical "A" Eliminator, by Arthur H. Lynch. Building the Equamatic, by Capt. P. V. O'Rourke.
- Oct. 16—The Bernard, by Herman Bernard. How to Box an "A" Supply, by Herbert M. Hayden.
- Oct. 23—The 5-tube P. C. Samson, by Capt. P. V. O'Rourke. Getting DX on the Bernard by Lewis Winner.
- Oct. 30—The Singletrol Receiver, by Herbert M. Hayden. How to Get Rid of Squeals, by Herman Bernard.
- Nov. 6—Reduction of Interference, by A. N. Goldsmith. Variations of Impedances, by J. E. Anderson.
- Nov. 13—The 4-tube Hi-Power Set, by Herbert E. Hayden. A Study of Eliminators, by Herman Bernard.
- Nov. 20—Vital Pointers About Tubes, by Capt. P. V. O'Rourke. The 4-tube Diamond of the Air, by Herman Bernard.
- Dec. 4—The regenerative 5-tube Set, by Capt. P. V. O'Rourke. The 8-tube Lincoln Super, by Sidney Stack.
- Dec. 18—Selectivity on One Tube, by Edgar Speare. Eliminating Interference, by J. E. Anderson.
- Dec. 25—A New Coupling Device, by J. E. Anderson. Function of Eliminators, by Herman Bernard.
- Jan. 1, 1927—The 2 Tube DeLuxe Receiver, by Arthur H. Lynch. The Twin-Choke Amplifier, by Kenneth Harkness.
- Jan. 8—Tuning Out Powerful Locals, by J. E. Anderson. A Choice Superheterodyne, by Brunsten Bruun. The 2-Tube De Luxe Receiver, by Arthur H. Lynch (Part 2).
- Jan. 15—The P. DeLuxe Receiver, by Arthur H. Lynch (Part 3). The Simple Meter Test Circuit, by Herbert E. Hayden. The Superheterodyne Modulator Analyzed, by J. E. Anderson.
- Jan. 22—The Atlantic Radiophones feat. by Lewis Rand. An Insight Into Resistors, by J. E. Anderson. A Circuit for Great Power, by Sidney Stack.
- Jan. 29—The Harkness KH-27 Receiver (Part 1), by Kenneth Harkness. Use of Biasing Resistors, by J. E. Anderson.
- Feb. 5—5-Tube, 1 Dial Set, by Capt. P. V. O'Rourke. The Harkness KH-27 (Part 2), by Kenneth Harkness. What Produces Tone Quality, by J. E. Anderson.
- Feb. 12—Phone Talk Put on Speaker, by Herbert E. Hayden. All Batteries Eliminated, by Herman Bernard. The Harkness KH-27 Receiver, by Kenneth Harkness (Part 3). Conclusion.
- Feb. 19—The 6-Tube Victoreen, by Herman Bernard (Part 1). The Big Six Receiver, by Wentworth Wood. "B" Eliminator Problem, by Wm. P. DeLuxe. The Phasitrol Circuit, by Capt. P. V. O'Rourke. The 2-Tube Victoreen, by Herman Bernard (Part 2). Conclusion.
- Feb. 26—The 5-tube Diamond in a Phonograph, by Hood Astrakan. How to Read Curves, by John F. Rider. Proper Tubes for 5-Valve Receiver, by J. E. Anderson.
- Mar. 5—Introduction of 4-tube Universal, by Herman Bernard. Discussion on DX, by Capt. P. V. O'Rourke. Sensible Volume Control, by Chas. Gribben.
- Mar. 12—Ten Tell-Tale Points, by J. E. Anderson. How to Figure Resistors, by Frank Logan. The 4-tube Universal, by Herman Bernard. (Part 1)
- Mar. 19—Psycho-Analyzing Circuits by Thomas L. McKay. The Universal, by Herman Bernard (Part 2). How to Use a Wave Trap, by James H. Carroll.
- Mar. 26—The Universal, by Herman Bernard. (Part 3). Flow of Current in a Vacuum Tube, by Badeloffs Parker. Broadcasting Hypnotism.
- April 2—Facts Every Experimenter Should Know, by J. E. Anderson. The Ship Model Speaker, by Herbert E. Hayden. The 8-tube Compact, by Jasper Henry. The Nine-in-Line Receiver, by Lewis Rand (Part 1.)
- April 9—A 5-tube Shielded Set, by Herbert E. Hayden. The Power Control, by Lewis Winner. The Nine-in-Line Receiver, by Lewis Rand, (Part 2.)
- April 16—The Scholloy's Set, by Wally Frost. The Melo-Head 11-tube Set, by Herbert E. Hayden. The Nine-in-Line Circuit (Part 3), by Lewis Rand.
- April 23—The Melo-Head Set, by Herbert E. Hayden (Part 2). The Nine-in-Line, by Lewis Rand. (Conclusion). How Frequencies Are Cut-off, by J. E. Anderson.
- April 30—A 1-tube Portable, by Jasper Jelliffe. A Ship Model Receiver, by Smidley Farnsworth. A Double Three Foot Cone, by W. H. Sinclair.
- May 7—The Adams-Griffin 6-tube Set, by Dana Adams-Griffin (Part 1). A 2-tube Portable, by Hood Astrakan. How to Improve Super-Heterodyne Sets, by John L. Barrett.
- May 14—A 3-tube Portable, by Herbert E. Hayden. The Adams-Griffin Receiver, by Dana Adams-Griffin. (Conclusion).
- May 21—The Victoreen Portable Receiver, by Capt. P. V. O'Rourke. A Low-Pass Filter, by J. E. Anderson.
- May 28—The Console Cone, by Thorvald Larsen. The 3-tube Reflex by Edgar B. Francis. The Victoreen Portable Receiver, by Capt. P. V. O'Rourke. (Part 2).

Any copy, 15c. Any 7 copies, \$1.00. All these 32 copies for \$4.00, or start subscription with any issue. Any 7 of these numbers sent as premium with NEW yearly subscription. No other premiums allowed. RADIO WORLD, 148 West 45th Street, New York City.

How to Figure Out An Exponential Horn

(Continued from page 5)

that the exponential horn is determined by the rate of increase of cross-sectional area. If the linear dimensions increase exponentially, but at twice the rate.

The equation above presumes that the horn has a circular cross-section throughout. It can also be of square section, or any other type. No change is necessary in the formula to make it represent sections other than circular. D might be the side of a square, the diagonal of a square, or the major axis of an ellipse. (Do) would have a corresponding meaning.

Type Should Change Slowly

The section of the horn can even change from one type to another between the two ends. In that event the area of the square should be the same as the area of the circle would have been had the circular shape been continued. For example, if the circular horn requires a diameter of four feet at the large end, the area of that section is 12.57 square feet. If the section is to be square, its

side must be the square root of 12.57, or it must be 3 feet and 6 1/2 inches.

Suppose we wish to construct an exponential horn 20 feet long with a small end diameter of .625 inch and a large end diameter of 4 feet. We then have $D=48$ inches, $D_0=.625$ inches, and $L=20$ feet. We can substitute these values in the formula as it stands, but it is more convenient to convert the formula so that we can use common logarithms directly. Rewriting it we have $D=(D_0) \times 10^{.09427L}$, or $48=.625 \times 10^{.09427 \times 20}$. Taking the common logarithm of both members of the last formula and solving for b we have $b=.09427$.


Our design formula now takes the shape $D=.625 \times 10^{.09427L}$. We can also write this $\log D=.09427L—.2041$. This gives the value of D in inches for any value of L in feet.

The table gives D for every integral foot from the small end to the large of a 20 foot horn.

L feet	D inches	L feet	D inches
0	.625	11	6.81
1	.777	12	8.46
2	.965	13	10.50
3	1.200	14	13.05
4	1.49	15	16.20
5	1.85	16	20.04
6	2.298	17	25.00
7	2.854	18	31.10
8	3.55	19	38.60
9	4.41	20	48.00
10	5.475		

(Continued on next page.)

Dependable "B" Battery Power

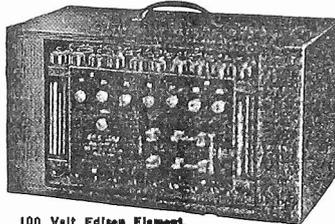

100 Volt Edison Element. Non-Destructive, Rechargeable "B" Battery with charger. Shipped dry with solution, \$12.00. 140 Volt with charger, \$17.00. SEND NO MONEY. PAY EXPRESSMAN Write for our Free illustrated 24-page Booklet SEE JAY BATTERY COMPANY 913 Brook Avenue New York City

World "A" Power Unit--\$12.75

Automatically provides even, unvarying "A" current from your light socket. Absolutely noiseless. Assures full tone quality from your set and wider D. X. range. Famous WORLD quality—at less than half of the cost of any similar equipment. Shipped complete, subject to inspection on receipt of price, or C.O.D., if you wish. 25 amp. unit for sets of 4 tubes or less, \$12.75. 60 amp. unit for sets of 5 tubes or more, \$15.75. 5% discount if cash in full is sent with order. Send order today. World Battery Co., 1219 So. Wabash Ave., Dept. 82, Chicago, Ill.

Take Your Choice of 7 Other Publications!

For NEW RADIO WORLD Subscribers Ordering NOW

Radio World has made arrangements

—To offer a year's subscription for any one of the following publications with one year's subscription for RADIO WORLD

RADIO NEWS or POPULAR RADIO or SCIENCE AND INVENTION or BOYS' LIFE or RADIO DEALER or RADIO (San Francisco) or RADIO AGE.

This is the way to get two publications

- for the price of one
- Add \$1.00 a year extra for
- Send \$6.00 today for RADIO WORLD
- Canadian or Foreign Postage.
- for one year (regular price
- Present RADIO WORLD subscribers
- for 52 numbers)
- can take advantage of this offer by
- and select any one of the other
- extending subscriptions one year
- nine publications for twelve months.
- if they send renewals NOW!

Radio World's Special Two-for-One Subscription Blank RADIO WORLD, 148 West 45th Street, New York City.

Enclosed find \$6.00, for which send me RADIO WORLD for twelve months (52 numbers), beginning..... and also without additional cost, Popular Radio, or Radio News, or Science and Invention, or Radio Dealer, or Radio (San Francisco), or Radio Age or Boys' Life (or \$10.00 for a two-year subscription to one address). No other premium with this offer.

Indicate if renewal. Name

Offer Good Until Street Address

Sept. 10, 1927 City and State

(Continued from preceding page)

It is interesting to note how slowly the horn increases at first and how rapidly as the length increases. In the first ten feet the diameter has increased less than 5 inches. In the second ten feet it has increased more than 40 inches. It is still more interesting to see what will happen to it the next 20 feet. When the length of the horn is 40 feet the large end diameter is 307 feet.

If a change is made from one type of

cross-section to another it should not be made abruptly. Any sudden changes in the lines of the horn will introduce reflection of sound waves, and that is just what the exponential horn prevents.

The length of the exponential horn should be at least half a wavelength of the lowest note it is desired to bring out with full volume. The lowest note on the piano is about 30 cycles per second. The wavelength of this note at room temperature 68 degrees F, is 37.6 feet.

Everybody *or* Nobody?

If It's a Product You Manufacture, the Answer Is "Everybody"—If It's the Extent of Your Personal Financial Resources, the Answer Is "Nobody."

Secrets Should Be Imparted to Nobody. You Would Not Spend Any Time, Much Less Any Money, Arousing Anybody's Interest in What Is Nobody's Business. For Instance, How Old Your Wife Is, or How Much Money You Have in the Bank.

If You Have Something to Sell You Want EVERYBODY to Know It. Perhaps you have a new product this season, and your first real problem is to ESTABLISH it as an entity. Or you may have the same excellent line this season as you had last. But you don't want the radio buying public to forget you, as it quickly will, unless you keep your name and product constantly in the foreground.

You Must Sell the Consumer—The Jobber Will Fill the Dealer's Orders When the Public Demand Makes the Dealer Send in the Orders, Therefore—

Create that public demand. Advertise your product in the

Fourth Annual Radio World's Fair Number

of Radio World, which will be published September 17, two days before the Fair opens, and will be circulated throughout the entire United States by that date, as well as being distributed to thousands upon thousands who attend the Fair, at Madison Square Garden, New York, September 19 to 26, inclusive.

Radio World is America's First and Only National Radio Weekly, dated every Saturday and Published every Wednesday, and circulating among home builders of sets, purchasers of factory-made sets, and also among the retail, jobbing and manufacturing trade.

Advertising forms for the Fourth Annual Radio World's Fair number—the predominant issue—dated September 17, close Tuesday, September 6, at noon. For rates, see editorial page.

"Tell It to Everybody"
Magnetize Your Dollar.
Give It a Pulling Power It Never Had Before.
Advertise in the Fourth Annual Radio World's Fair Number.

**RADIO WORLD (Advertising Manager), 145 West 45th Street
New York, N. Y.**

Write or Telegraph for Reservations—*or Telephone BRY ant 0558 or 0559*

BLUEPRINTS OF INEXPENSIVE DX RECEIVERS

THE FIVE-TUBE DIAMOND OF THE AIR, a very selective circuit of thrilling tone quality, that brings in distant stations to the great delight of the fans, is easily built, in fact can be constructed in a couple of hours. The authorized blueprints that make this speed and efficiency possible are just off the press and will be shipped at once, together with a booklet of full textual exposition of construction, including winding of coils, how to connect coil terminals, what values of condensers and resistors to use, etc. If you want a tone quality set that will give you great enjoyment, be sure to build this five-tube Diamond of the Air. The receiver consists of a stage of tuned radio frequency amplification, a specially sensitized detector, first stage of transformer audio and next two stages of resistance audio. It is easily adapted to playing phonograph records on your speaker. Get acquainted with this NEW delight.

THE FOUR-TUBE DIAMOND

represents the most that is obtainable from four tubes. A stage of tuned radio frequency amplification, a specially sensitized detector, and two stages of transformer coupled audio. Follow the diagrams as shown in the blueprint and you can't go wrong. You will be amazed at the results. Build the set from parts that you have. Full instructions cover utilization of such apparatus. Thousands are eager to build an economical set and this one is the most economical in cost of construction and upkeep, where one considers the surpassing results. Works splendidly from batteries, with either type 99 or type 01A tubes, and can be used with A and B eliminators, power packs, etc., with great success.

Look Over Both of These blueprints and read the text in both cases before choosing the receiver you are to build.

SEND NO MONEY!

Just fill out the coupon below, and note what you get FREE!

Guaranty Radio Goods Co.

145 West 45th Street, New York City

Please send me one newly-printed official blueprint of the 5-tube Diamond of the Air, one newly printed official blueprint of the 4-tube Diamond, and the textual data giving full directions for constructing these sets. I agree to pay the postman 75 cents on delivery. Also, you are to send me, without extra cost, one Auto Strop Safety Razor, one blade and one automatic razor strop.

Name
Address
CityState.....

TELEVISION

Picture Transmission—the Marvel of the Century

Newest and greatest authority, just published, gives History, facts and complete instruction to build a home television set

THE marvel of Radio Broadcasting, the transmission of the voice and music over the air is no longer the greatest achievement of this precocious 20th century.

We now have TELEVISION—the transmission of events over land wires or by radio. A tremendous step ahead of even Radio.

For many years experiments on television have been diligently made by many famous inventors and engineers. Step by step machines have been corrected, improved and simplified—until today—practical machines

are in constant operation, annihilating distances in picturing events to the eager public.

Here is the first and only book in print that gives you the complete story of television from earliest experiments to the present day machines.


The book is the most complete publication of its kind. It gives you *the history, the facts* and the full instructions on how to build, in your own home, an up-to-date model Television apparatus.

Great Future for practical Experimenters

Television will be as popular as Radio. Even now the public is showing great interest in telephoto pictures from Europe and elsewhere. Get your apparatus together. You are in for many days of fascinating experiments that beat anything you've ever tried. 4 special chapters in this book deal exclusively with how to construct an experimental set.

Like Radio in 1921

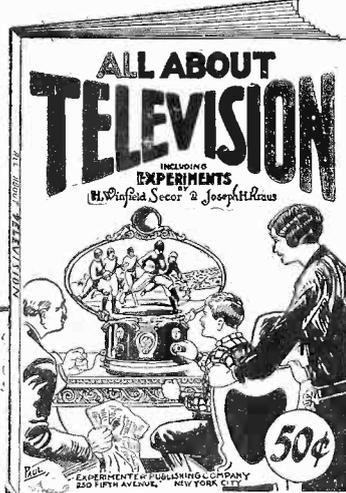Television is ready for the world. Like Radio in 1921, it waits only for you experimenters to invent, develop and perfect the apparatus. You may be fortunate enough to develop an idea that will be worth many dollars—start now with a copy of this book.



**COPIES 50¢ EACH
AT ALL
NEWSSTANDS**

If Your Newsdealer Cannot Supply You—Order Direct
EXPERIMENTER PUBLISHING CO., Inc.
230 Fifth Ave., New York, N.Y.

1000 Hours of Fun with SAM LOYD

THERE are more than one thousand hours of truly amazing fun and frolic—in Sam Loyd's "Tricks and Puzzles." There is only one Sam Loyd, the Puzzle King, the incomparable, a true master mind, and he has crowded in this new volume, "Tricks and Puzzles," the best work of his lifetime.

In this book are thousands of puzzles of every conceivable nature, games, tricks, conundrums. Hundreds of illustrations. Scores of real brain-teasing puzzle stories, dozens of humorous anecdotes.

With this inexhaustible gold mine of lively entertainment at hand you need never be at loss for an evening's party program or a rainy day's delight.


It's a book for young and old folks alike —Riddles for the youngsters—Brain teasers for the grown-ups.

The kind of a book every home should have in its book-rack. 116 pages, 100 or more illustrations, large size, 9 x 12 inches with beautiful 2-color cover.

50c THE COPY EVERYWHERE

or you can order direct

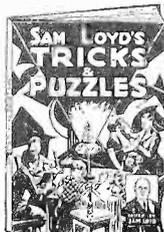EXPERIMENTER PUBLISHING CO., Inc.
230 Fifth Ave. New York, N. Y.



SECRETS of your HANDS

96 page Book on the revelation of character, fortune, etc.—in Hands

FINGERPRINTS are used throughout the world as a means of apprehending criminals—but fingerprints are but a small portion of the secrets of your character that your fingers, your palm, even your handshake reveals.

Every inch of your hand has been charted by the experts of this highly developed science, and so simply and accurately that anyone can learn the telltale signs by heart.

Here is a brand new book with all the latest information—written in such a way that you can quickly master "Palmistry."

Everything is simplified, easy to understand, the book contains 96 pages, hundreds of illustrations and is the large size 9x12 inches.

50c THE COPY EVERYWHERE

or you can order direct

EXPERIMENTER PUBLISHING CO., Inc.
230 Fifth Ave., New York, N. Y.