

DEC. 12  
1931

# HOLIDAY GIFTS NUMBER

PRICE  
**15c**  
Per Copy


NEW  
R-F  
PENTODE  
TUBE

# RADIO REG. U.S. PAT. OFF. WORLD

The First and Only National Radio Weekly  
**507th Consecutive Issue**  
TENTH YEAR

BIAS  
FROM  
UNTAPPED  
FIELD  
COIL

## INSTALLING A SET IN A CAR

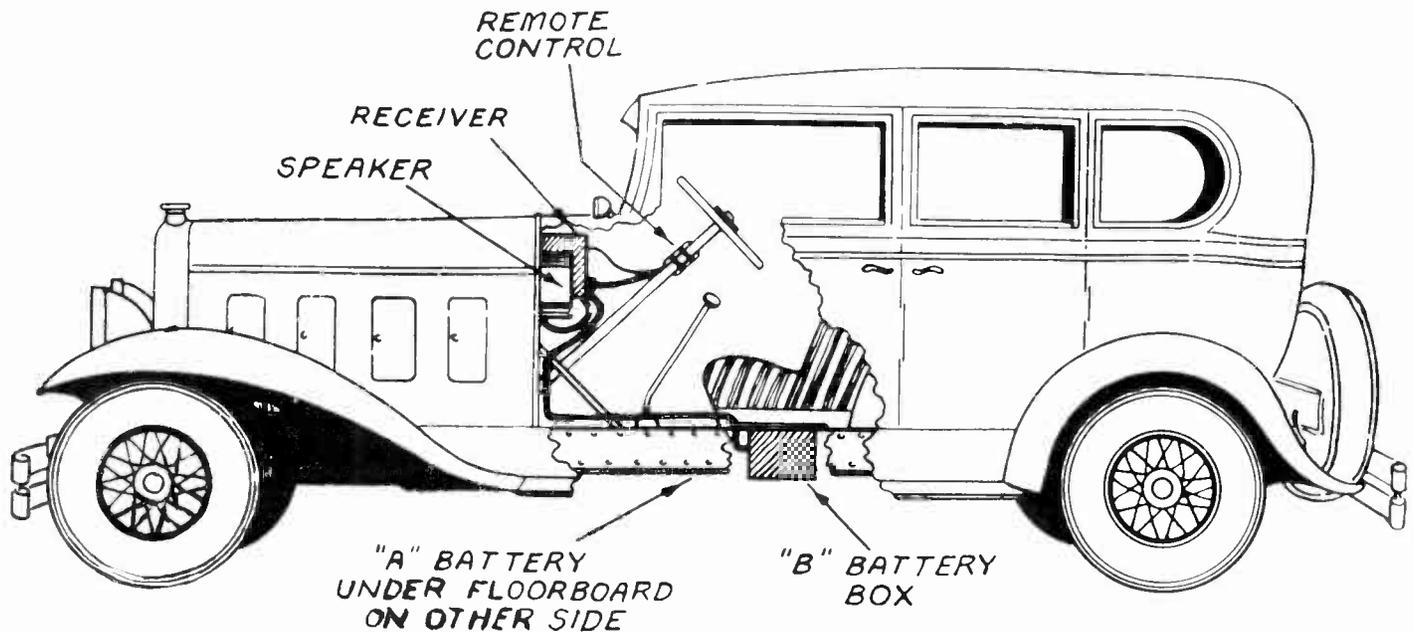

Behind the bulkhead, under the cowl, is a good place to put both auto set and speaker, with remote control on the steering post. See article on pages 6, 7 and 8.

**DIODE  
DETECTOR  
FOR  
BATTERY SETS**

*Simple  
Converter  
with  
Power Supply*

**LIST OF STATIONS  
IN U. S. AND  
CANADA BY  
CALL LETTERS**



Latest Midget Hand Type Mike can be worn on lapel.

No. 306. List \$5.00. Used for public address work as Callophone System when attached to your radio.

MILES REPRODUCER CO.  
26 E. 22nd St., New York

**\$6.00 Wilkens UNI-WAVE Converter \$6.00**  
A custom built screen grid SW converter covering 30-110 meters. A little wonder on DX. Housed in Alcoa aluminum cabinet and sent complete with tubes, ready to use. Wilkens Eng. Co., 241 S. 11th St., Reading, Pa.

## NATIONAL DRUM DIAL



National Velvet Vernier drum dial, type H, for 1/4" shaft. An automatic spring take-up assures positive drive at all times. Numbers are projected on a ground glass. Rainbow wheel changes colors in tuning. Modernistic es-cutcheon. Order Cat. ND-H @ \$3.13.

GUARANTY RADIO GOODS CO.  
143 West 45th Street, New York, N. Y.

### - SPECIALS -

Five-lead cable, 2 ft. long, with plug to fit a five-prong (UY) socket. The cable is connected at the factory so that following wires represent the respective prongs of the socket: Blue with white marker—G post of socket; Red—plate of socket; Green—cathode of socket; Yellow—heater adjoining cathode; Black with yellow marker—heater adjoining plate. Net 65c  
MARCO black bakelite vernier dials. Read 0-100 with a supplementary scale reading 0-10 between figures on large scale. Takes a 1/4" shaft. Net 50c  
Parts for "A" battery eliminator: Dry rectifier, \$2.10; 0-10 ammeter, 75c; 20-volt filament transformer, \$2.50. Will handle up to 2 amperes filament current.

GUARANTY RADIO GOODS CO.  
143 West 45th St. New York, N. Y.

## BLUEPRINTS

- 627.** Five-tube tuned radio frequency, A-C operated; covers 200 to 550 meters (broadcast band), with optional additional coverage from 80 to 204 meters, for police calls, television, airplane, amateurs, etc. Variable mu and pentode tubes. Order BP-627 @ .....25¢
- 628-B.** Six-tube short-wave set, A-C operated; 15 to 200 meters; no plug-in coils. Intermediate frequency, 1,600 kc. Variable mu and pentode tubes. Order BP-628-B @ .....25¢
- 629.** Six-tube auto set, using automotive tubes, with pentode push-pull output. Order BP-629 @ .....25¢

RADIO WORLD

145 WEST 45TH ST., NEW YORK, N. Y.

## A NEW BOOK

SERVICING SUPERHETERODYNES  
By John F. Rider

a NEW book offered to the radio service man. Here is the superheterodyne service information you have been awaiting for a long time. Everything you want to know and need to know about servicing superheterodynes at a profit.

Principles of operation—Explanation of the different commercial circuits—Breakdown of the superheterodyne receiver sections—Troubles in superheterodynes—Servicing superhets—Application of set analyzers—oscillators—adjustment of trimmer and tuning condensers—Peculiarities in superhets—Design of IF and RF oscillator. . . Sold with Money-Back Guarantee.


### COUPON

RADIO TREATISE CO., Inc. Dept. RW  
1440 Broadway, N. Y. City

Here is \$1.00. Send Rider's "Servicing Superheterodynes" postpaid. It is understood that if I am not satisfied with this book, and I return it in good condition within 10 days, you will refund my money.

Name.....  
Street.....  
City..... State.....
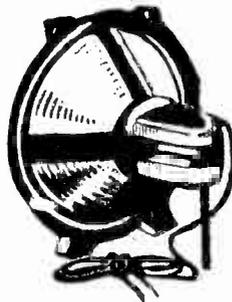
## Try - Mo Radio's Sensational Speaker Sale




FARRAND INDUCTOR DYNAMIC

The Farrand Inductor Dynamic is the only speaker of its kind that can be used equally well on battery, A.C. or D.C. sets. You will be amazed at the tone quality of this speaker. Matched for power tube. State type of power tube when ordering.

9" Speaker, \$5.95  
10" Speaker, \$6.95

ALL IN ORIGINAL FACTORY SEALED CARTONS

B. R. L. Magnetic Chassis.....	\$3.25
B. B. L. 12-inch Magnetic Chassis.....	5.75
Baldwin D. C. Midget Dynamic.....	2.95
Baldwin A. C.....	6.95
Farrand Magnetic Chassis.....	1.69
Jensen D. C. Midget Dynamic, 2500 ohms.....	3.95
Jensen A. C. Midget Dynamic.....	7.95
Oxford D. C. Midget Dynamic.....	3.25
Pearless 12-inch A. C. Super Dynamic.....	10.95
Rola A. C.....	7.95
R. C. A. 106 Dynamic.....	3.95
R. C. A. A. C. 106.....	9.50
Rola D. C. Midget Dynamic, All Types.....	4.25
R. C. A. Magnetic Chassis.....	2.25
R.C.A., 100-B Speaker.....	3.95
Victor A. C. Dynamic.....	8.95
Victor D. C. Dynamic.....	3.95

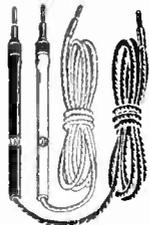

### Test Leads

A pair of test leads which are indispensable to the serviceman.

Your Price 35¢

A heavier type with needle pointed tips which list for \$2.50.

Your Price 59¢

TRY-MO RADIO CORPORATION  
177 Greenwich St. (near Cortlandt)  
New York City

## Fixed Condensers

Dubilier Micron fixed condensers, type 842, are available at following capacities and prices:

.0001 mfd. ....	10¢	.008 .....	20¢
.0002 mfd. ....	10¢	.0025 with caps. 210	
.0005 mfd. ....	10¢	All are guaranteed	
.0015 mfd. ....	12¢	electrically perfect and	
.001 .....	12¢	money back if not	
.002 .....	15¢	satisfied within 90	
		days.	

GUARANTY RADIO GOODS CO.  
143 West 45th St., New York, N. Y.

## Quick-Action Classified Advertisements

7c a Word — \$1.00 Minimum  
Cash With Order

SERVICEMEN, MAKE THIS A FAIRWAY CHRISTMAS! Co-operate with us; feature Fairway Silver Polish. Retail 50¢; price to you for the asking. Ryber Mfg. Co., Room 1114, 1700 Walnut St., Philadelphia, Pa.

PRINTING: 1000 BUSINESS CARDS, with Card Case, \$1.50 postpaid. Other printing reasonable. MILLER, Printer, Narberth, Pa.

SHORT WAVE BLUEPRINTS. Send 25c (coin) for five blueprints which give real D.X. results. Super Engineering Laboratories, 1313 - 40th St., Brooklyn, N. Y.

WORLD'S LARGEST HOUND KENNELS OFFERS: Quality Hunting Dogs, Sold Cheap, Trial Allowed; Literature Free. Dixie Kennels, Inc. B-69 Herrick, Illinois  
SONG POEM OR MELODY WRITERS! I offer you outstanding proposition. Hibbeler, D67A, 2104 Keystone, Chicago.

HANDY 4 FT. FLEXIBLE TEST-CORDS WITH UNIVERSAL CLIPS—25c postpaid. Five for \$1.00. Tele-Dyne Electrical Laboratory, 2935 Walnut Street, Chicago, Ill.

## 853 PAGES, 1,800 DIAGRAMS IN RIDER'S NEW 6-LB. MANUAL

THE most complete service man's manual is "The Perpetual Trouble Shooter's Manual," by John F. Rider, published during 1931, and full of real information. Wiring diagrams of ALL popular commercial receivers and kit sets from 1922 to 1931, inclusive. Also contains a course in trouble shooting. Loose leaf pages, 8 1/2 x 11", bound. 853 pages; index and advertisements on additional pages. Order Cat. RM-31, and remit \$4.50. We will then pay postage. (Shipping weight, 6 lbs.) Ten-day money-back guarantee.

RADIO WORLD

145 West 45th Street, New York, N. Y.

## FOR THAT BOY—OR MAN—AT CHRISTMAS TIME!

Why not have us send him RADIO WORLD for the coming year so that he can keep abreast of all that is going on in radio? Besides, every week RADIO WORLD will carry him a message that suggests your thoughtfulness.

Also, on receipt of your \$6, we shall take pleasure, if you wish, in sending him a special letter to the effect that you have requested us to put his name on our subscription list for 52 issues, as a holiday gift.

Subscription Dept., RADIO WORLD, 145 West 45th St., New York City

## Two for the price of One

Get a FREE one-year subscription for any ONE of these magazines:

- RADIO CALL BOOK MAGAZINE AND TECHNICAL REVIEW (monthly, 12 issues)
- POPULAR MECHANICS AND SCIENCE AND INVENTION (combined) (monthly, 12 issues).
- POPULAR SCIENCE MONTHLY
- RADIO INDEX (monthly, 12 issues), stations, programs, etc.
- RADIO (monthly, 12 issues; exclusively trade magazine).
- MODERN RADIO (monthly).
- EVERYDAY SCIENCE AND MECHANICS (monthly).
- RADIO LOG AND LORE. Monthly. Full station lists, cross indexed, etc.
- AMERICAN BOY—YOUTH'S COMPANION (monthly, 12 issues; popular magazine).
- BOYS' LIFE (monthly, 12 issues; popular magazine).

Select any one of these magazines and get it FREE for an entire year by sending in a year's subscription for RADIO WORLD at the regular price, \$6.00. Cash in now on this opportunity to get RADIO WORLD WEEKLY, 52 weeks at the standard price for such subscription, plus a full year's subscription for any ONE of the other enumerated magazines FREE! Put a cross in the square next to the magazine of your choice, in the above list, fill out the coupon below, and mail \$6 check, money order or stamps to RADIO WORLD, 145 West 45th Street, New York, N. Y. (Add \$2.00, making \$8.00 in all, for extra foreign or Canadian postage for both publications).

Your Name.....


Your Street Address.....

City..... State.....

- If renewing an existing or expiring subscription for RADIO WORLD, please put a cross in square at beginning of this sentence.
- If renewing an existing or expiring subscription for other magazine, please put a cross in square at the beginning of this sentence.

RADIO WORLD, 145 West 45th Street, New York. (Just East of Broadway)

DOUBLE VALUE!

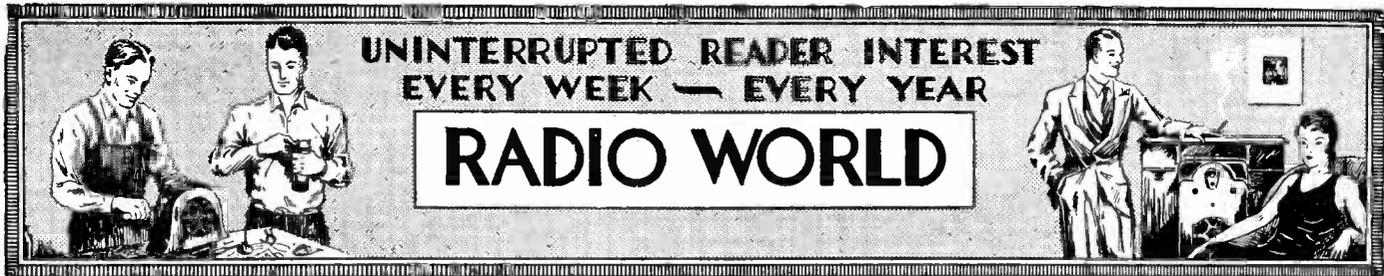

Vol. XX No. 13 Whole No. 507  
 December 12th, 1931  
 [Entered as second-class matter, March, 1922, at the Post Office at New York, N. Y., under act of March, 1879]  
 15c per Copy. \$6 per Year

TENTH YEAR  
 Technical Accuracy Second to None  
 Latest Circuits and News

A weekly Paper Published by Hennessy Radio Publications Corporation, from Publication Office, 145 West 45th Street, New York, N. Y.  
 (Just East of Broadway)  
 Telephone, BRyant 9-0558 and 9-0559

RADIO WORLD, owned and published by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y. Roland Burke Hennessy, president and treasurer, 145 West 45th Street, New York, N. Y.; M. B. Hennessy, vice-president, 145 West 45th Street, New York, N. Y.; Herman Bernard, secretary, 145 West 45th Street, New York, N. Y.; Roland Burke Hennessy, editor; Herman Bernard, managing editor; J. E. Anderson, technical editor; J. Murray Barron, Advertising Manager.

# New Tube Announced

## 239 Is R-F Pentode of Automotive Series

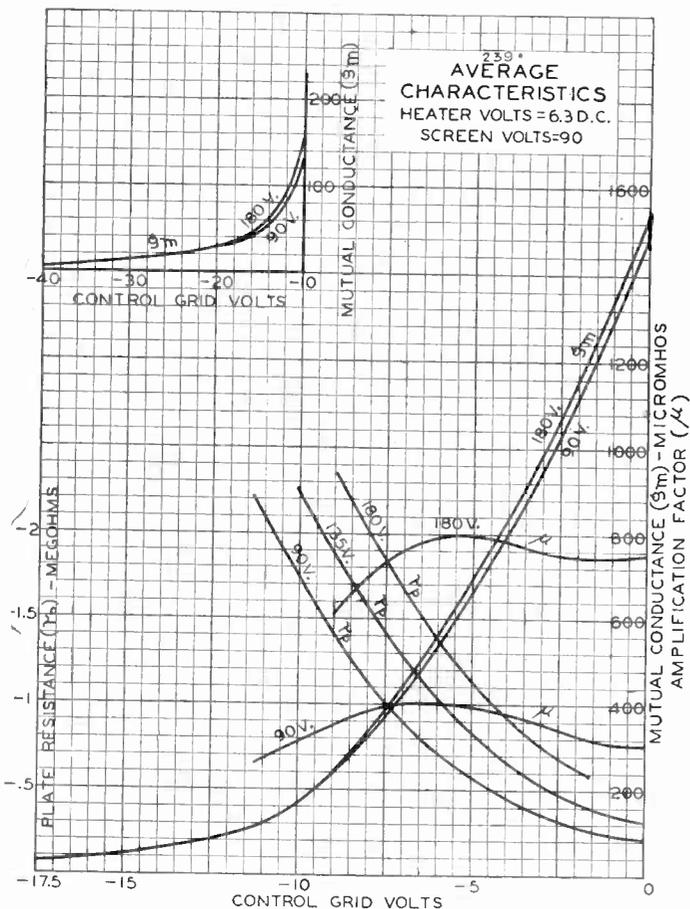


FIG. 1

Characteristic curves for the first standard pentode r-f amplifier tube to be placed on the American market, the 239. It is also a variable mu tube and even may be used as a first detector in superheterodynes.

THE first radio frequency pentode of standard type ever to come into the American market has just been announced. It is a variable mu tube of the automotive series, suitable also for operation from d-c electric lines. It is the 239.

This new tube incorporates a number of new design features which make it particularly suitable for use in future circuits.

The 239 is recommended for use as a radio frequency amplifier, intermediate frequency amplifier, and superheterodyne first detector. It is very effective in reducing cross modulation and modulation distortion over the usual range of received signals. Its design, like that of the 235, is such as to permit easy control of a large range

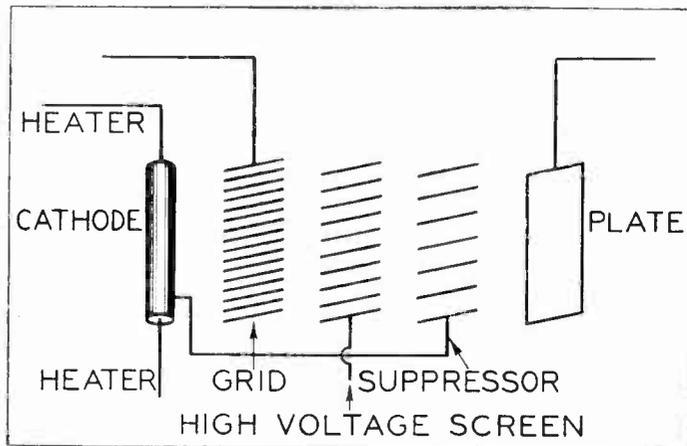


FIG. 2

Diagrammatic view of the element arrangement of the 239. The element marked "grid" is also known as the control grid.

of signal voltages without the use of special local-distance controls. This super-control characteristic makes the tube uniquely suitable for use in receivers designed for automatic volume control.

### Why It is a Pentode

This new tube is a five electrode design, hence the name pentode. In addition to the usual cathode, control grid, screen, and plate elements, a fifth element, called the suppressor, is placed between the screen and the plate. This suppressor is connected within the tube to the cathode and effectively eliminates the secondary emission effects which otherwise limit the voltage swing permissible in screen grid tubes if operated with a low plate voltage, that is, at a plate voltage approximately equal to the screen voltage. The suppressor in this new radio-frequency pentode therefore makes possible the operation of this new type of tube with excellent results where the plate voltage available is limited, as for example in sets designed for operation on 110 volt d-c.

The use of the suppressor makes possible further advantages tending toward better set performance, since the fifth element permits of greater flexibility in obtaining a high mutual conductance and a high plate resistance, even though the tube may be operated at a low supply voltage.

### Allows for Heater Voltage Variation

The 239 utilizes a coated cathode of the heater type designed for direct current operation. Owing to the special cathode construction, the heater voltage may vary during the charge and discharge cycles of the automobile storage battery without affecting seriously the performance or service of this tube.

No resistor in the heater circuit is required for operation from a six volt battery.

For operation in receivers designed for direct current power lines, the heaters of two or more of these tubes may be connected in series. Since the current rating of this tube is the same as the 236, 237, and 238, that is, 0.3 ampere, any heater combination of these tubes

(Continued on next page)

# Pentode R-F in A-C Set

## Series Heaters Enable Use of 20 Volt Transpower

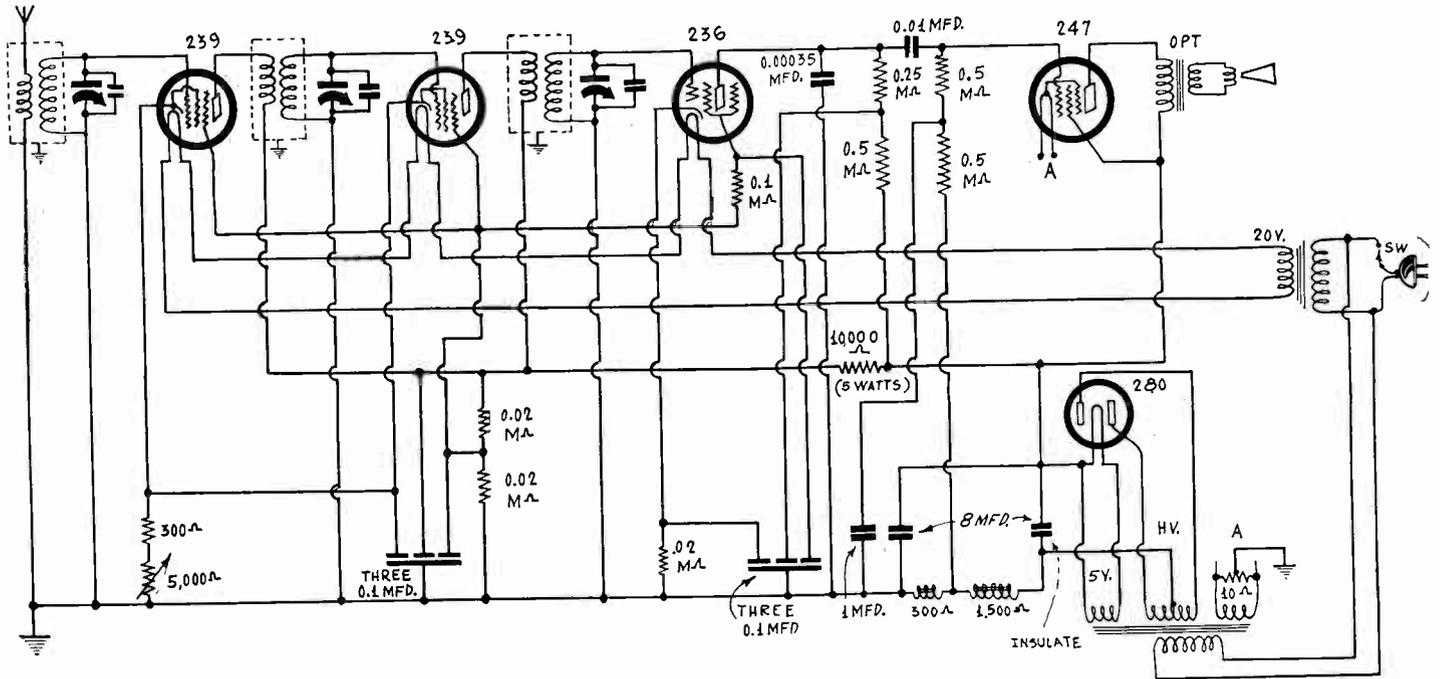


FIG. 1

Using the new pentode r-f tubes in an a-c operated circuit, one may develop greater gain, while the heater voltage is economically supplied from the secondary of a 20 volt transformer, the heaters of course being in series. Therefore the detector tube is also of the automotive series.

(Continued from preceding page)

in series is practical, provided that the current is adjusted to the proper value.

This new tube is not interchangeable with any other type of vacuum tube.

### Set for A-C Operation

The enticing thing about the tube, of course, is the fact that it is a pentode, and that it therefore has an accelerator grid. This is important as lifting the amplification factor, it being 750 at most, a value that may be at least approximated in practice, because of the prevention of secondary emission.

When the cathode emits electrons some of them strike the plate and bound back and therefore constitute a retarding influence on the new crop of electrons that is about to bombard the plate. The accelerator speeds on the electrons, or, to put

the same thing differently, the extra grid is a suppressor grid in that it suppresses the secondary emission.

The fact that the tube is a variable mu tube, while important, is secondary in point of interest, as we are familiar with variable mu tubes, but the pentode as an r-f amplifier of standard make is something new. An r-f pentode was put on the market nearly two years ago by a manufacturer then an independent, but the market was not ripe for it.

Although the tube is primarily intended for automotive use, or for d-c electric operation, it can be used in a-c sets as well, as Fig. 3 shows a diagram for this purpose.

### Heaters in Series

About the most economical method of supplying the heater voltages, in the absence of a 6.3 volt winding, would be to get a 20 volt transformer, such as it used for loudspeaker dynamic rectifier supply, and which can be bought for less than \$1. Then the heaters of the two 239 r-f tubes, as well as the heater of the 236 detector, are connected in series across the secondary, the voltage across each heater being 6.7 volts. This is all right, as when the automotive tubes were first announced it was said that up to 7.5 volts a-c could be put on the heaters, as they are not critical.

The circuit follows the design of standard midget five tube a-c sets and has the volume control as a voltage alterer in the cathode return of the two r-f tubes. The minimum bias requirement of 3 volts is afforded by the 300 ohm resistor, as the current will be 11.4 ma through it when the volume control is at zero, and 260 ohms would give that voltage.

The requirement that must be watched carefully is the plate voltage. This is not as high as for other tubes used in a-c sets. Therefore a resistor is used to drop the maximum B voltage to 180 volts. If the d-c output of the rectifier on load is 275 volts, then about 180 volts will result if the series resistor is 8,300 ohms, though 10,000 ohms is more easily obtainable and may be used as shown. The rating of this resistor should be 5 watts or more. The half watt and one watt resistors will burn out.

Except for the extra filament transformer and the 10,000 ohm resistor the circuit is substantially the same as that on which the Blueprint No. 627 is based, and therefore it is quite practical to use that blueprint, and the same layout, adding the transformer where there is room underneath, at the middle of the chassis, and making the slight wiring and parts changes necessary.

## Tentative Rating and Characteristics of the New 239 Valve

The preliminary rating and characteristics of the RCA-239 and the Cunningham C-239 are as follows, while the tubes of other manufacturers will have about the same characteristics:

Heater Voltage	6.3 Volts D-C		
Heater Current	0.3 Amperes		
Plate Voltage	180 Volts Maximum		
Screen Voltage, Maximum	90*	135	90 Volts
Grid Voltage, Variable	-3*	-3	-3 Volts Minimum
Plate Current	4.4	4.4	4.5 Milliamperes
Screen Current	1.3	1.2	1.2 Milliamperes
Plate Resistance	375000	540000	750000 Ohms
Amplification Factor	360	530	750
Mutual Conductance	960	980	1000 Micromhos
Mutual Conductance at { -30 volts bias	10	10	10 Micromhos
{ -40 volts bias	very small, but not zero		
Interelectrode Capacitances			
Effective Grid-Plate Capacitance	0.007 uuf. Maximum		
Input Capacitance	4 uuf.		
Output Capacitance	10 uuf.		
Overall Dimensions			
Length	4 3/16" - 4 11/16"		
Diameter	1 9/16"		
Cap	0.346" - 0.369"		
Bulb	S-12		
Base	Small 5 Prong		

\*Recommended values for use in receivers designed for 110-volt d-c operation.



# Car Set Installation

## Instrument Board Unmolested—Compactness Essential

By Edwin Stannard

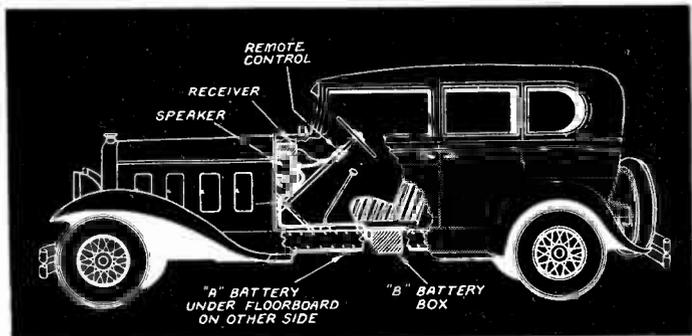


FIG. 1

A method of installing a radio set in an automobile without "cutting up the car" in any way. The set is mounted with four screws on the bulkhead under the cowl, the speaker is next to the set, while the remote control is on the steering post. A B battery box goes underneath the floorboard

MANY persons who have an automobile would like to have a radio receiver in it, but are deterred by the possibility that the instrument board will be cut up and possibly be ugly after the job is finished. While automobiles with radios built in do have instrument board access, this of course is done neatly and easily as part of the construction of the car. But when one has a radioless car, the problem of not doing any injury to the car has to be met.

The circuit has nothing to do with this problem. The consideration is purely mechanical. Therefore one has to decide where the set, the tuning control and the B batteries shall be. Of course, the storage A battery is on the car, and all one need to do is make connections thereto.

The first requirement is that the set itself be small, and as six tubes must be used for sensitivity, the mechanical problem is partly solved by compactness. A steel box shield 9 inches wide, 6 inches front to back, and  $7\frac{3}{4}$  inches high was found, on the basis of measurements taken in many cars, to constitute an excellent size, so that the set could be fastened to the bulkhead under the cowl, and elevated sufficiently not to interfere with the feet of the assistant driver at the chief's right.

### How About the Austin?

The box fits nicely in this manner even in the new and old Fords, in the Chevrolets, Pontiacs and other small cars, though no test was made on the Austin.

When the set is housed in so small a box shield the problem is essentially solved if remote control tuning is introduced. The attachment of the box to the bulkhead is easily done by using "self-starting" screws, four of which are required.

How high to elevate the set from the floorboard is a matter of choice. In virtually all cars there is a slant of the flooring behind the bulkhead, so any height should be measured from the highest floor point. However, between the back of the

instrument board and the bulkhead there is room in all the standard cars, small ones included, for the box of specified size, so Fig. 1 shows the set mounted almost as high up as it will go. To the left of the set is the speaker, a dynamic with its field excited by the 6 volt storage battery. The drain is about half an ampere. The push-pull output transformer is built into the speaker and is matched for pentode output.

Now, there is scarcely a handier place to put the tuning, switching and volume controlling mechanisms than on the steering post. Fortunately, a remote control device is obtainable that has the dial, dial light, volume control and on-off key switch for the set built into it compactly, with a clamp for attachment to the steering post, and a fuse holder and fuse at the side. Fig. 2 shows the chassis shield, B battery box and the remote control.

### Details on Three Cables

Two screws are tightened down and the clamping is completed. The B battery problem still has to be solved. It is most practical to make a box of just the right size to contain three 45 volt B batteries. Then the B battery box can be screwed underneath the left-hand side of the floorboard, about parallel with the position of the A battery, which is commonly located on the right-hand side, under the floorboard.

The cabling is as follows:

(1)—A four lead shielded battery cable with no plug at either end, used for connecting to the A minus, A plus, B plus 67.5 and B plus 135 volts. B minus and A minus are interconnected direct between batteries.

(2)—A five lead speaker cable, with a five prong plug at one end, the free leads at the other end soldered by the builder to the five posts on the terminal strip of the speaker. The plug goes into the UY socket marked "SPK." The connections establish contact for the plates of the push-pull tubes, B plus 135 volts and the 6 volts of the storage battery (through the set) for field coil excitation.

(3)—A five lead remote control cable, marked VC on Blueprint No. 629, which connects to the A voltages and to two points (extremes) of the volume control potentiometer. One extreme is the aerial connection also, which may be made at the control on the steering post. The fifth connection is a "spare" and is used for interconnecting A plus battery cable and A plus of the tube sockets.

### Circuit Shown in Fig. 3

A special auto aerial may be placed over the top, under the car chassis or under the running board.

As for the circuit, Fig. 3, this consists of two stages of tuned radio frequency amplification, using the new 239 variable mu pentode r-f tubes, 236 tuned detector (thus three screen grid tubes), 237 first audio and 238 (pentode) push-pull output. The r-f tubes may be 236 screen grid, if you have tubes already, otherwise use 239. The circuit was designed by J. E. Anderson and is covered by Blueprint No. 639, which is full scale and gives all constructional and dimensioned data, except coil winding. The coils may consist of 30 turn primaries (No. 32, enamel or silk) wound over 127 times (No. 32 enamel), on 1 inch diameter, encased in shields, or 300 turn r-f chokes may be used as primaries inside the secondaries. These shielded coils are T1, T2 and T3. *(Continued on page 8)*

# Speaker Plug Connections for A-C Sets

*(Continued from preceding page)*

former has a center tap. Probably the same 2.5 volt winding is used for pentode and all the heater tubes of the receiver. That is quite proper, as it merely gives the heaters a positive bias equal to the negative bias on the pentode, or 16.5 volts, which is well within the approved limits, as much as 50 volts having been common, when 245 tubes were in vogue.

The center tapped resistor should have a low value, total not exceeding 30 ohms, and may be as low as 10 ohms or so.

In the preceding part of the circuit (not shown), grid returns of r-f, detector and preliminary audio tubes would be made to ground, through biasing resistors in cathode legs, just the same as if the choke were in the positive leg.

The filter capacities of the B supply are shown as 8 mfd. each and are situated, one from B minus to B plus maximum, the other from ground to B plus maximum. Electrolytic condensers are commonly used.

Therefore the caps of these condensers are interconnected (anodes), but the cases have different potentials, 137.5 volts

apart in one instance, as we have found. The condenser on the grounded side of course has its case grounded, but the condenser next to the rectifier has its case insulated. For this purpose two insulating washers are furnished, the metal chassis (if such is used) being sandwiched between the insulators, and a special removable lug provided so as to pick up the otherwise unconnected case. This lug goes to B minus.

In building a set it is customary to use a tube socket as a receptacle for the so-called speaker plug. For the untapped choke coil a four spring socket (UX) may be used, as there are only four leads from the speaker: plate of pentode, B plus maximum, B minus and ground. For the tapped coil there are five connections, plate of pentode, B plus, B minus, tap and ground. A good method is to use the heaters of the receptacle socket interchangeably for plate and B plus; plate of socket as ground; cathode of socket as B minus; grid of socket as tap. For the UX socket condition, filaments would be used as plate of pentode and B plus maximum, plate as ground and grid as B minus.

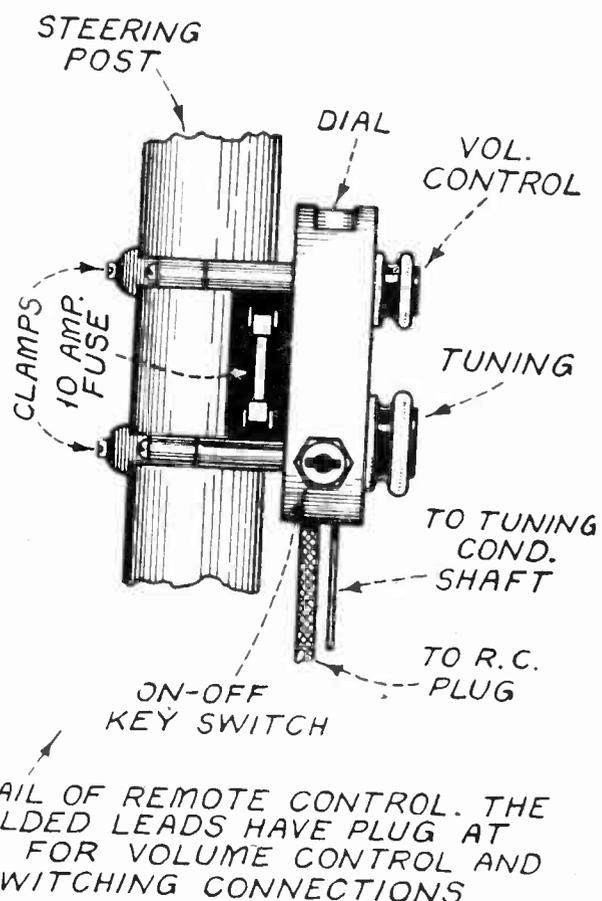
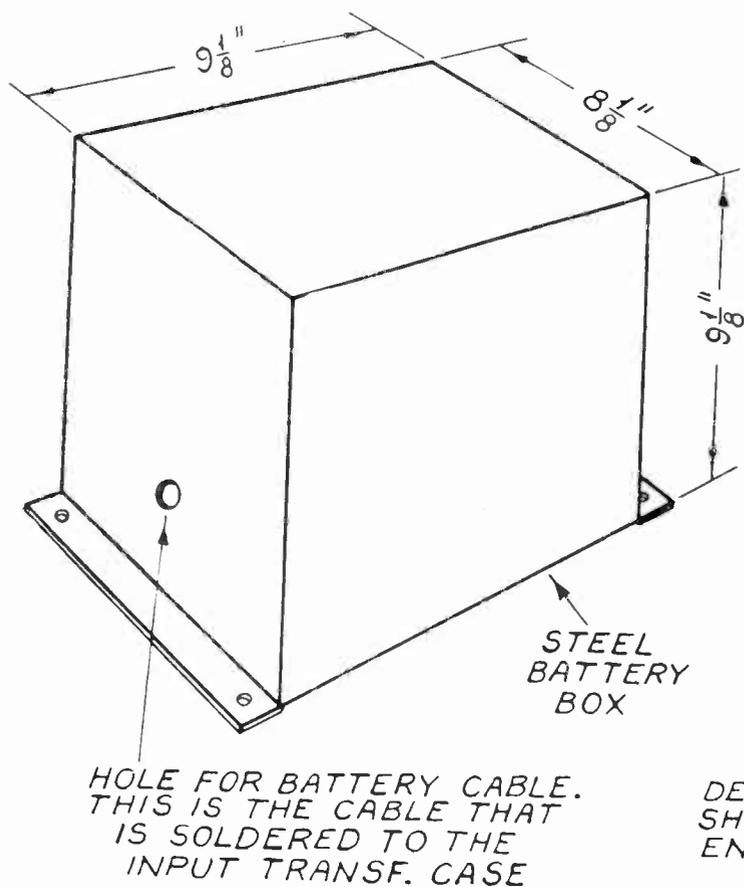
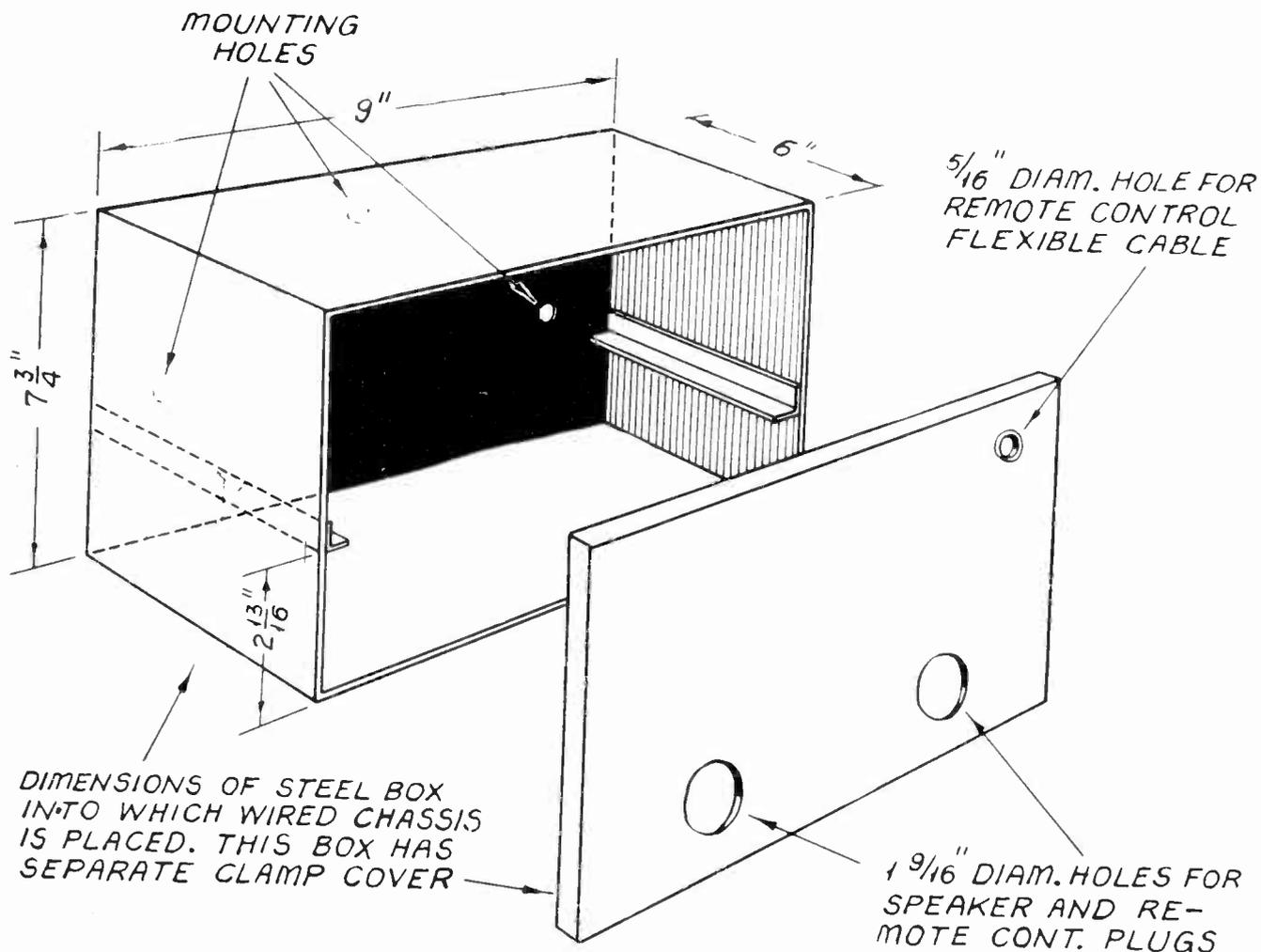


FIG. 2

Detail of the steel box shield into which the set chassis fits is shown at top. A clamp cover goes in front and passes two UY plugs (speaker and remote control cables) as well as the thin control cable for the tuning condenser shaft. The battery box and remote control are depicted at bottom.

# Aerial Problems in Auto Sets

(Continued from page 6)

Aerial facilities are at a premium in automobile installations. One desires as much pickup as possible, and it is not possible to get a great deal.

Undoubtedly the best solution is to string an aerial across the top, elevated 1 foot or more, and bring down the lead-in straight at the front. The car chassis will serve suitably as ground.

Some of course will object to this replacement of the aerial, because the appearance of the car is not improved, and the fact may be brought home by some skirted sharer of one's worldly possessions.

Lacking the aerial as described, one may use an upright wire at front, with lead-in taken from the top, giving the general appearance of an incompleting figure 4.

## Loop Effect

The reason for stressing the lead-in position and the horizontal aerial is to avoid any loop effect. Suppose one had a horizontal aerial over the top, brought the lead-in down at rear, under the floorboard, to the front, then up to the set. This would be a U-shaped aerial, really a loop. Then you would have the same effects as obtained when you are using a regular loop. Directional effects would be strong and when you turned a corner either the station would be tuned out or the volume would decline considerably.

This condition is generally called "fading," although of course it is not fading, but is due exclusively to the directional effect of the actual loop aerial. Fading concerns the difference in phase or time of arrival between the ground wave and the sky wave, due to the reflection of the sky wave back to earth by the Kennelly-Heaviside layer.

## Coil Suggestions

Large primaries should be used on automobile receivers, because the sensitivity of tuned radio frequency receivers is least at the higher wavelengths, and the short antenna also has least field strength at these waves.

Sometimes the primaries consist of radio frequency choke coils that fit inside the secondary form, and are honeycomb coils of about 300 turns. This opens the possibility also of tuning the primaries to some high wavelength, preferably just outside the broadcast band, which tends to compensate for the receiver's sensitivity characteristic that rises sharply with frequency.

The automobile set has been slow in gaining popularity, but since the improvement of receivers for this purpose, and the introduction of methods of installation that do not ruin the appearance or require cutting up the instrument board, interest has increased greatly.

It is estimated there are 50,000 auto sets in use, constituting a small percentage of the number of cars, but no doubt this will increase, especially now that receivers with 239 multi-mu pentode r-f amplifiers are possible. The sensitivity will be much greater than formerly, hence the results and enjoyment will be greater.

## LIST OF PARTS

### Coils

T1, T2, T3, one set of three-shielded automobile R-F transformers for 0.00035 mfd. tuning condenser.  
One push-pull input transformer.

### Condensers

One 3-gang 0.00035 mfd. tuning condenser, trimmers built-in.  
One 0.00035 mfd. fixed condenser.  
One 0.01 mfd. fixed condenser.  
One 0.25 mfd. fixed condenser.  
Three 0.1 mfd. fixed condenser in one shield case.

### Resistors

Five resistors, viz: One 150 ohms, one 300 ohms, one .03 meg (30,000 ohms), one 0.25 meg. and one 0.5 meg.  
[5,000 ohm potentiometer is in remote control]

### Miscellaneous Other Parts and Accessories

Eight UY sockets; six marked for tubes, two for plugs.  
Five grid clips.  
Dynamic speaker with 6 volt field and cable.  
One special auto aerial to go over top, under auto chassis or running board.  
One chassis, one chassis box with shelves, one box front and one battery box.  
Special remote control unit, containing potentiometer, tuning dial, pilot bracket, lamp and switch.  
One 4-wire shielded battery cable, 8 feet long.  
Seven spark suppressors and one mfd. condenser.  
One 5-prong plug for speaker.  
Four 6/44 Parker screws.

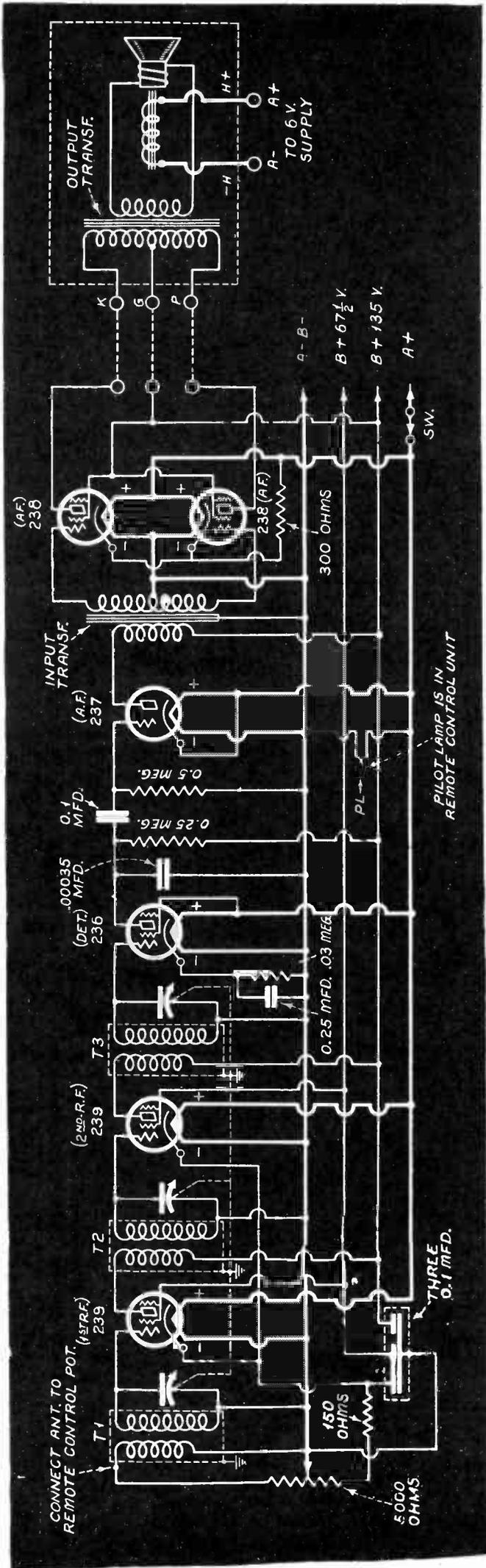


FIG. 3 The new variable mu pentode r-f tubes are used as amplifiers, while there are screen grid power detection and two stages of audio, the last push-pull pentode.

# The "Scotch" Converter

It Can Be Built for Less than \$10

By Ralph C. Cross

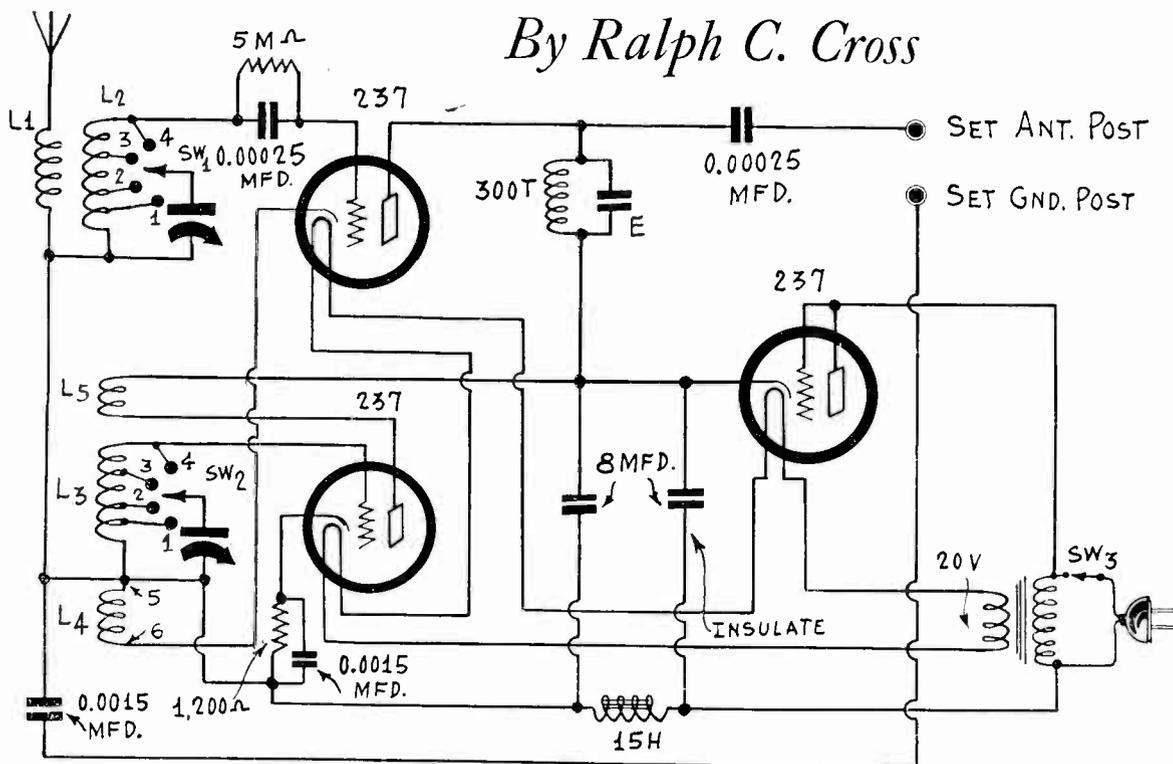


FIG. 1

THE 237 tube lends itself admirably to use in a short wave converter, since the general purpose tube is well adapted to modulation, serves well as B supply rectifier and moreover is a fine oscillator. In fact, for such a circuit there would be no advantage whatsoever in using screen grid tubes. Would a screen grid tube make a better oscillator, a better B supply rectifier, or a better modulator in view of the output coupling necessity? It would not. Therefore no advantage whatsoever would be served by using a screen grid tube in any one of these positions, and no purposes of economy prompted the selection of the tubes, despite my Scotch ancestry. Their functioning is at par, and moreover the current drain is so very low that the outfit does not cost more than one-tenth of a cent an hour to run, anywhere in the United States. That is at the rate of 10c per kilowatt hour, and the rate is less than that nearly everywhere, and in some sections of the country is being lowered from recent levels. So you can listen on short waves from far and near, all night long, if you desire, and still run up your juice bill less than one cent!

### Changes Made

The circuit is similar to one discussed before, but the changes introduced are as follows: the single output choke coil has an equalizing condenser across it, so that there may be some tuning in this circuit and there is no resistor in this circuit; there is no series condenser in the antenna circuit, but instead a larger capacity condenser is in series with the external ground; the grid continuation method is used in the coil system, instead of the shorting out turns for higher frequencies.

The circuit as previously presented, in the August 29th issue, has been very successful, and users report the reception of the most remote foreign countries and the smallest powered stations, all over the earth, and the shorting coil method was used. After 42 hours of laboratory testing and comparison it has been found that the present "edition" is a little more sensitive, due particularly to the tuning of the output, which also gets rid of direct reception of broadcast stations, to a large extent. The rest of the changes are of small but actual help, and the circuit as published now is recommended to be used, even though it is admitted that the improvement is not enormous.

### Works on All Types of Sets

The circuit offers an excellent opportunity for the construction of a converter that will work on all types of sets, including superheterodynes, because the output coupling is such that it feeds well into the antenna systems used in supers, providing for good results on any intermediate frequency, thus including tuned radio frequency sets as among those with which the converter well may be used.

It should be noted that there is no essential difference

between one type of set and another, so far as the signal is concerned, and that if the a converter will pick up a signal, even if there must be mixing in the converter, and again more mixing in the superheterodyne, the output of the converter still is subjected to whatever sensitivity the receiver has, and therefore results should be good. Poor coupling methods, particularly the use of screen grid output tubes, which do not present a suitable impedance to any type of antenna load found in sets, account for the failure of some converters to work well on some sets. Persons will report that a converter worked well on a set in a friend's home but in the owner's home (using a different set) the same converter did not work. The present design does not depend so much on the sensitivity of the receiver to solve the problem, but itself delivers a good voltage to the input of the set.

### Independently Tuned Circuits

This fact arises from the use of two tuned circuits, the  
(Continued on next page)

### LIST OF PARTS

#### Coils

- Two coils, one for modulator, one for oscillator; two windings on modulator coil, three windings on oscillator coil.
- One 300 turn honeycomb coil.
- One 20 volt transformer.
- One 15 henry B supply choke coil.

#### Condensers

- Two 0.00035 mfd. tuning condensers.
- Three 0.00025 mfd. fixed condensers (one with grid clips).
- Two 8 mfd. condensers, with mounting nut and lug for each.
- One Hammarlund equalizer, 20-100 mmfd.
- One 0.0015 mfd. fixed condenser.

#### Resistors

- One 5 meg. grid leak.
- One 1,200 ohm fixed resistor.

#### Miscellaneous Parts and Accessories

- One a-c cable and male plug.
- Three leads for external connection (ant., gnd., output).
- One 10x8x3 inch cabinet.
- One a-c toggle switch.
- Hardware: two dozen 6/32 machine screws, two dozen nuts, two dozen screws; one machine screw 2 inches long; two threaded bushings.
- Two flexible leads, tipped at both extremes.
- Two dials.

# High Sensitivity from Independent Tuning, Plus Output Tuning

(Continued from preceding page)

avoidance of use of an untuned stage in or ahead of modulator, and to the independence of the tuning. It is all right to put in a gang condenser when the intermediate frequency is fixed, as where a stage of i-f is built in (which is not done here) but any such system forecloses one from choice of an intermediate frequency. An i-f stage, of course, adds considerable gain, probably around 100, so even if a set is not very sensitive at the compulsory intermediate frequency, the i-f stage makes up for it. There are some very excellent converters of this built-in-stage type, and they are very good, particularly one of them (National's) but in the present instance the circuit is necessarily confined to greater simplicity of construction, and is offered as one that can be built of parts costing not in excess of \$10. Any intermediate frequency may be used—from 30 kc to 1,600 kc.

## Coil Method

The grid continuation method of coil switching simply consists of connecting the stator of a condenser to the moving arm of a switch and picking up the coil extreme, next first tap removed therefrom, next second tap removed therefrom, etc., and, depending on the capacity of the condenser, the number of taps will be chosen accordingly. So the diagram shows four taps, as some will use smaller capacity than 0.00035 mfd. for tuning, whereas if 0.00035 mfd. is used, only three taps are necessary.

Instead of regular switches, however, the condenser shifting to various taps is done as follows: two UY tube sockets are put on the cabinet top, their grid springs wired to the stators of the respective tuning condensers. Then the extreme and two (or three) taps are wired to the other springs. A flexible lead with tips that fit into socket springs is then used, one end going into the grid hole and staying there, while the other end is moved from one point to another, as desired, the only necessary precaution being that the progression (extreme, first tap, etc.) be in the same order for both tube sockets, to avoid confusion. Surely this is not the use of plug-in coils, but it is the use of plug-in leads, and of course it is a switching arrangement. Whatever definition may be attached to it, the system works very well, costs little, and helps to bring to the radio building public a converter for which the parts cost so very little that even in these times no one need be without the sheer fascination of listening to short waves.

## Balance Struck

The two coils used are oscillator and modulator. The oscillator coil, at left in the picture diagram (Fig. 2), has one more winding than the modulator coil, which has two. The modulator coil also may be referred to as the antenna coil. The aerial is connected directly to primary, and the series condenser previously present is not used. The pickup is a little stronger this way, and so, of course, the danger of direct interference from broadcast stations would be heightened, but the tuning of the output cuts down the direct interference, while the input is kept high.

The series condenser in the ground lead prevents putting the B supply choke across the line, not that it would do any harm, as the choke has as high an impedance as the primary of the filament transformer, but there is that much less current used, so the economy is worth while, besides there is a little added coupling between modulator and oscillator by this method, provided there is an r-f drop between B minus of the converter and actual external ground, which there usually is.

The main coupling, of course, is afforded by the coil system. The cathode of the modulator, instead of returning direct to ground, returns through a winding on the oscillator coil (second from bottom in Fig. 2, left), and this winding is in close inductive relationship to the oscillator secondary, so the coupling is effectuated. The oscillator plate winding is at bottom in the pictorial diagram, and must be connected as shown (provided windings are in the same direction), to insure oscillation. However, if oscillation fails, or if you suspect its absence, simply reverse the connections to the plate winding.

## Cabinet Size

The top panel size is 10x8 inches, and the converter may be built into a box cabinet that has the proper holes drilled. The sockets have to be accommodated, there being three for the converter tubes and two for the switching method, and provision must be made for the two 8 mfd. condensers. The inclusion of such high capacity in a modest converter is well considered, because it is a sure preventive of any hum trouble, when used with a B choke of even small inductance. The

B choke coil is specified at 15 henries, but that does not mean it is large, for the total current through it may be only around 10 ma, while the 30 henry chokes readers are more familiar with are usually rated for 100 ma, or so. The inductance increases as the current decreases, so the 15 henry choke is a small affair, though wholly adequate.

The same precautions obtaining in receivers must be taken here regarding the insulation of the case of one of the electrolytics, but if a wooden cabinet is used, including top panel or any other insulating material, then of course the panel itself takes care of the requirement. Some lug or looped wire must be used to establish an easy connection to the case, which may be aluminum, hence not solderable by you.

## Tuned Output

The same precautions obtaining in receivers must be taken to insure selection of the best intermediate frequency. If your set is sensitive at a high frequency, say, from 800 kc up, turn the setscrew of the equalizer to zero, for minimum capacity. If your set is more sensitive at lower frequencies, turn its dial to respond to some favorable frequency, where there is no broadcasting coming in directly, and then tune in a station on the converter, which already is connected to the set.

You can leave the modulator dial at the same position for this short wave station, and simply use a screwdriver to turn down the setscrew of the equalizer until the signal comes in loudest.

If you don't know just where sensitivity is best, as the power and distance of broadcast stations vary, and an open guess may away off, tune in a short wave station, leave the modulator dial as it is for this wave, and then keep changing the dial settings of your set and of the oscillator, first the set, then the oscillator to catch up with the changing intermediate frequency, and listen until the station is heard loudest. Of course some direct broadcasting—powerful locals—may be heard as you go over the set dial, but at least you can determine the region of the best sensitivity, and can then adjust the trimming condenser of the output coil to meet this situation.

## Layout of Parts

If the equalizing condenser is connected with its thick brass lug to the plate and the thin copper lug to B plus voltage (referring to the Hammarlund 20-100 mmfd. equalizer), then a metal screwdriver may be used for adjustment without any body capacity effects.

The layout is such that at left and right rear are the two 8 mfd. electrolytic condensers, the three tubes are in a line between them, the sockets for coil switching are just forward of the electrolytics, and the two dials are at front, with a-c switch between them. An a-c cable with plug emerges from the rear. This goes to the convenience outlet or lamp socket. The only other connections to make are: remove the aerial from your set (a long aerial is advisable) and connect it instead to the antenna wire of the converter; connect the ground wire of the converter to the ground post of the set but leave the ground at the set; connect the remaining converter wire (output) to the vacated antenna post of the receiver. The connections can be made in three minutes by any one who has read these directions.

## Coil Data

If you want to wind very small coils for this outfit, using 1½ inch diameter tubing, No. 28 enamel wire, you may put on, for the modulator coil's primary (antenna winding), 10 turns, for the secondary, 33 turns, tapped at the 22nd and 26th turns. The oscillator coil would consist of 25 turns secondary, tapped at the 13th and 18th turns. The taps are counted from the grid end. The plate winding consists of 20 turns, spaced close to the pickup winding of 10 turns that is between the plate and the grid windings. These data are for 0.00035 mfd.

## NEW BOOKS

"SERVICING SUPERHETERODYNES," by John F. Rider. Published by Radio Treatise Co., 1440 Broadway, New York, N. Y. Price \$1.00.

This book contains information of immediate and everyday value to the service man. What with the large number of superheterodyne receivers being sold daily and the meagre amount of service information available concerning superheterodynes, this book should be welcome.

The book is type set and bound in a flexible cover. The folio size is 5x7 inches.

# a Low-Cost Converter

ing, Afford Device That Works Well

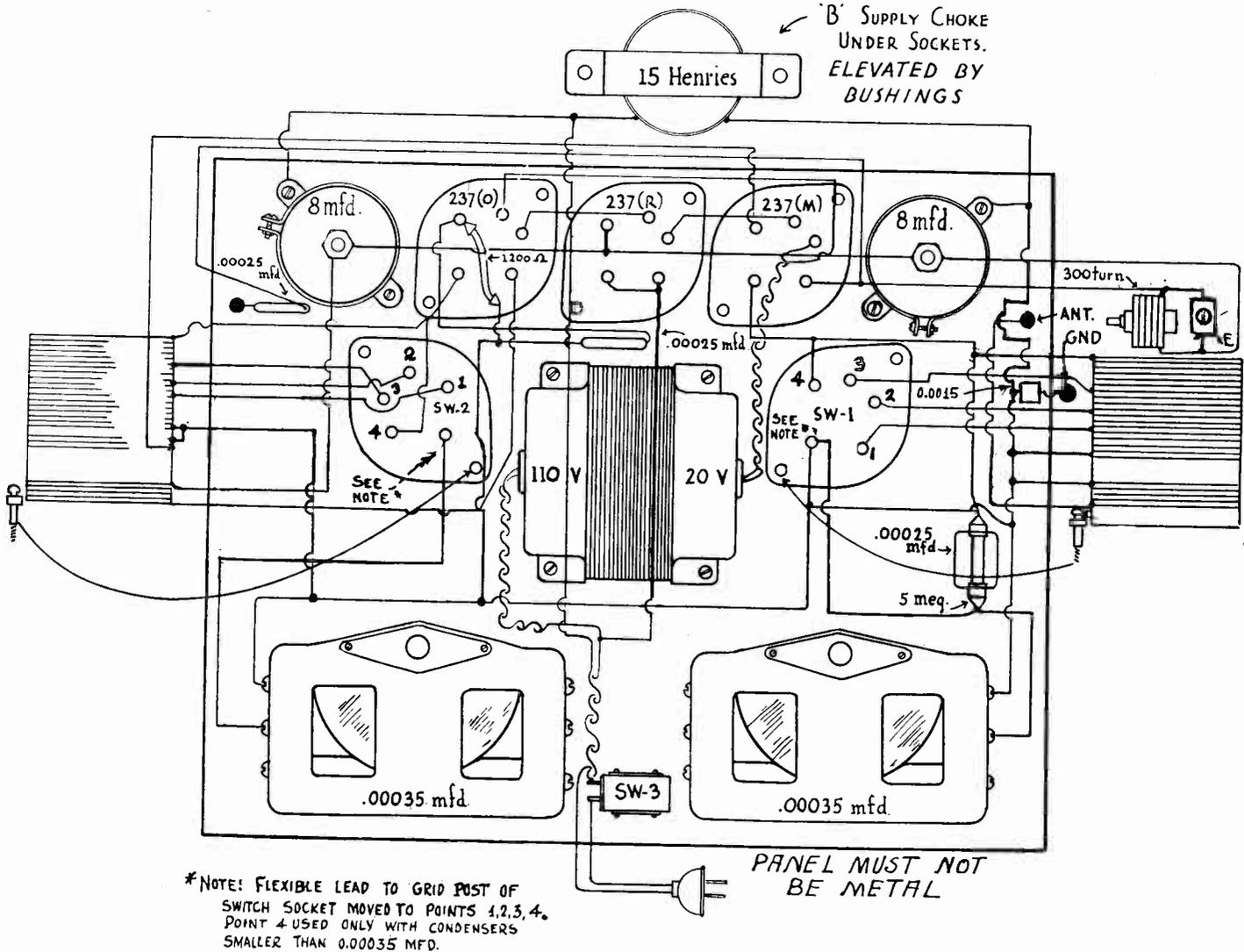


FIG. 2

Pictorial diagram of the converter.

- Raymond F. Brown, 101 Prospect Street, Gloucester, Mass.
- A. Davies, South Slocum, B. C., Canada.
- R. S. Gillam, Mart, Texas.
- Elwood S. Fauls, 325 Carpenter St., Oneida, N. Y.
- L. E. Parris, 515 Martin St., Greensboro, N. C.
- Edward McQuade, 9 Lincoln St., Marlboro, Mass.
- Tom Edwards, 420 Lantz Ave., Detroit, Mich.
- Y. Ewart, 5775 Victoria Drive, Victoria, B. C., Canada.
- Sr. Jose Garza Lopez, Calle Gral Tren No. 834, Monterey, N. L., Mex.
- C. B. Johnston, R. D. No. 1, Verona Rd., Verona, Pa.
- Kenneth Wood, Jr., Box 26, Leslie, Ga.
- C. C. Stalder, Route No. 19, Orlando, Fla.
- Vincent F. Edick, Mgr., Radio Service Co., 906 Jefferson Ave., Utica, N. Y.
- Kenneth Sargent, 3717-74th St., Jackson Heights, N. Y.
- Howard R. Taylor, 2925 Scarborough Rd., Cleveland, Ohio.
- Sam. Adams, Bennington, Nebr.
- Harold Sopanek, Hays Hall, Moscow, Idaho.
- P. R. Swan, 2801 Ohio Ave., Topeka, Kans.
- O. B. Sparks, No. 6 So. 80th St., Birmingham, Ala.
- S. J. Welch, Ellicottville, N. Y.
- Robin Matthew, 5 St. Michaels Pl., Charleston, So. Car.
- L. E. Parris, 515 Martin St., Greensboro, No. Car.
- Robert E. J. Tate, 25 Kingsbury St., Roxbury, Mass.
- Franklin O. Miller, 934 Allen St., Allentown, Pa.

### Literature Wanted

*Readers desiring radio literature from manufacturers and jobbers concerning standard parts and accessories, new products and new circuits, should send a request for publication of their name and address. Send request to Literature Editor, RADIO WORLD, 145 West 45th Street, New York, N. Y.*

- Charles E. Smith, 24 Upland St., Lyman, S. C.
- James Dunlop, Rt. 2, Box 85, Placerville, Calif.
- Allen H. Schooley, 282 Littleton St., West Lafayette, Ind.
- W. R. Newcomb (for short wave parts and accessories), 156 Enfield Cres., Norwood, Winnipeg, Man., Canada.
- John J. Clifford, 4924 Broad St., Pittsburgh, Pa.
- Bradley Overton, Box 765, Bartow, Fla.
- K. R. Zumhagen, 3609 No. 17th St., Milwaukee, Wis.
- John E. Adams, P. O. Box 2197, Atlanta, Ga.
- Daniel Johnston, R. F. D. No. 4, Vilonia, Ark.
- H. F. Williams, 109 Dresden St., Houston, Texas.
- Cadet Wm. A. Rank, Jr., N. M. M. I., Box 378, Roswell, New Mex.
- Lewis M. Scott, 1015 1st Ave., Columbus, Ga.
- W. E. Bishop, Bishop Radio Service, 706 Florida St., Amarillo, Texas.
- T. W. Mermel, 1900 D St., N. W., Washington, D. C.

- Reginald McCullough, La Grange, Mo.
- Adolph Lohner, 820 Holland Ave., Wilkinsburgh, Pa.
- Louis Bittay, 25 Brookline Ave., New Brunswick, N. J.
- F. Smarde, 4226 Ogden Ave., Chicago, Ill.
- Hubert F. Lange, R. F. D., No. 1, Fredonia, Pa.
- Frank Q. Norman, 2604 Wentworth Rd., Hanilton P. O., Baltimore, Md.
- Geo. A. Ashland, Douglas Steam Laundry, Douglas, Wyo.
- N. Leonard Wilson, 831 Lincoln Ave., Cincinnati, Ohio.

### List Prices of Tubes

*The following table gives the prevailing price lists of the various tubes:*

Tube	Price	Tube	Price	Tube	Price
227	@ \$1.00	551*	@ \$2.20	240	@ \$3.00
201A	@ .75	224	@ 1.00	WD-11	@ 3.00
215	@ 1.10	171A	@ .90	WX-12	@ 3.00
230	@ 1.00	112A	@ 1.50	200A	@ 4.00
230	@ 1.80	232	@ 2.30	222	@ 4.50
231	@ 1.60	199	@ 2.50	BH	@ 4.50
228	@ .80	100	@ 2.75	281	@ 5.00
237	@ 1.75	233	@ 2.75	250	@ 6.00
247	@ 1.55	236	@ 2.75	210	@ 7.00
235	@ 1.60	238	@ 2.75	BA	@ 7.50
		120	@ 3.00	KIno	@ 7.50

\*This tube comparable to the 235.


# Diode Detector in

## Provision for Automatic Volume Control Includ

By Herman

FIG. 1

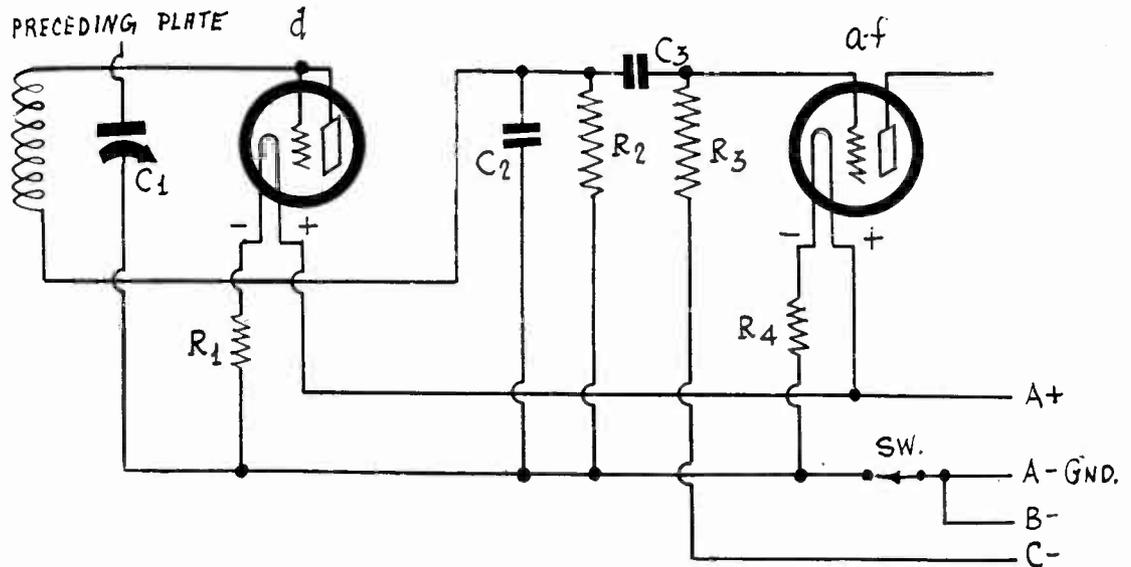The diode detector in a battery operated circuit, using filament type tubes. The tuning condenser is not put directly across the secondary that feeds the detector, but effectively across the primary.



THE diode as a detector is applicable to battery operated receivers, as well as to sets that are a-c operated, the single exception being that the filament type diode can not be used for feeding a push-pull resistance coupled stage, as can heater tubes. This is due to the grounding of the cathode circuit (filament) in battery type tubes.

Since the advent of the automotive series, which are classed as battery type tubes, although the heaters may be fed by a-c, it is no longer possible to distinguish tubes simply as battery operated or a-c, for some are both, but the present article deals with filament type tubes. The automotive series tubes may be treated as in the a-c class for the present purpose, and readers therefore are referred to the equivalent use of a-c tubes as diodes, pages 6 and 7 of the November 21st issue.

Fig. 1 shows the use of a battery type tube as a diode detector. A diode is simply a two element tube. But no such tubes are marketed to-day in this country, so a diode is constituted of a triode (three element tube) by joining grid and plate elements. A general purpose tube is used, e. g., 201A, 199, 237.

### Coil's Return Connections

In any rectifier the plate or anode is negative, and here the equivalent is the joined grid and plate elements. The radio frequency coil's secondary feeding the detector therefore may be included directly in the circuit, but instead of grounding the secondary directly, the secondary must be connected with its low potential end to a resistor (R2), and thus gets to ground. However, we desire to remove the radio frequency from the resistor, retaining a high impedance to audio frequencies while presenting a low one to radio frequencies. The fixed condenser C2 accomplishes this sufficiently. However, if the coil shown were tuned with a condenser, the C1 and C2 would be in series, and would upset gang tuning, hence the preceding plate circuit is tuned.

The values are as follows: C1, your tuning condenser; R1 and R4, the filament resistors in your set; C2, 0.00035 to 0.001 mfd.; C3, 0.01 mfd.; R2, 50,000 ohms; R3, from 0.5 meg. up, using as large a value here as is consistent with absence of motorboating.

There is no danger of motorboating, if only one stage of resistance audio is used, as there can be no feedback to the detector, because the detector is not an amplifier.

Stated broadly, therefore, the diode may be classed as not as sensitive a detector as the tubes normally used, but it will stand a greater load, it being virtually impossible to overload it with any radio signal obtainable from the run of receivers, even from the nearest local.

### Aspect of Sensitivity

However, since the tube does not amplify, it is removed from the chain that aids in producing r-f squealing when the amplification is lifted. So if you have two stages of t-r-f ahead of the diode, and if with some other type detector there was squealing and general instability until primaries were cut down,

with the diode the large primaries may be restored, for the amplification at r-f is confined to the r-f tubes alone. In other cases the detector adds to r-f gain by feedback.

So it is advisable not to regard a detector or any other tube in any circuit as something quite unto itself, but as a link in a chain, or, preferably to regard the chain as a unit, and design circuits according to that theory. Practice requires such procedure, anyway, whatever the mental attitude or the code of approach.

Thus with greater sensitivity easily developed by increasing the number of primary turns, the net effect may be as great a sensitivity as you had before, with better quality. The object of the diode detector is entirely one of quality, but of course it is desired to achieve this end with minimum sacrifice, particularly on the sensitivity score.

Fig. 1 shows the diode circuit, but it is suggested that two stages of resistance coupling be used.

It is assumed in the foregoing that shielded coils are used in r-f systems and that batteries are bypassed, as necessary aids to stability.

### Case of Transformer Coupling

If instead of resistance coupling you desire to use transformer coupling, this may be done simply by making the primary replace R2 and the secondary replace R3, omitting the stopping condenser, C3.

The diode may be the second detector of a superheterodyne or it may be the detector of a t-r-f set.

It was pointed out, in connection with a-c sets discussed in the November 21st issue, that automatic volume control can be achieved, without the use of an extra tube, by making the diode detector serve as the control tube as well. The way to do this is to connect the grid return of the controlled tube or tubes to a point on the diode load resistor, which is negative in respect to ground. This is shown in Fig. 2. It is usual and preferable to filter the return circuit, so C1 and R1 are used for that purpose. They are 0.1 mfd. and 0.25 meg. respectively.

It will be noticed that the filament resistor R2 is in the negative leg of the r-f amplifier, which may be any type tube, including screen grid, but is shown as a general purpose tube for convenience. Thus when there is no signal there is still current flowing through R1, and the potential difference between its terminals constitutes a negative bias on the tube.

### Bias Necessary When There's No Signal

This is important, because there must be always some provision for negative bias when there is no signal, that is, the bias can not depend exclusively on the control, for then there would be zero bias when tuning from one station to another, or when "fishing" for a station, or when an SOS puts all stations off the air, or when the aerial is disconnected. Especially uneconomical would zero bias be for battery operated systems, due to the heavy B current drain, not to mention the

# Battery Operated Sets

## Push-Pull Resistance Possibilities Discussed

Bernard

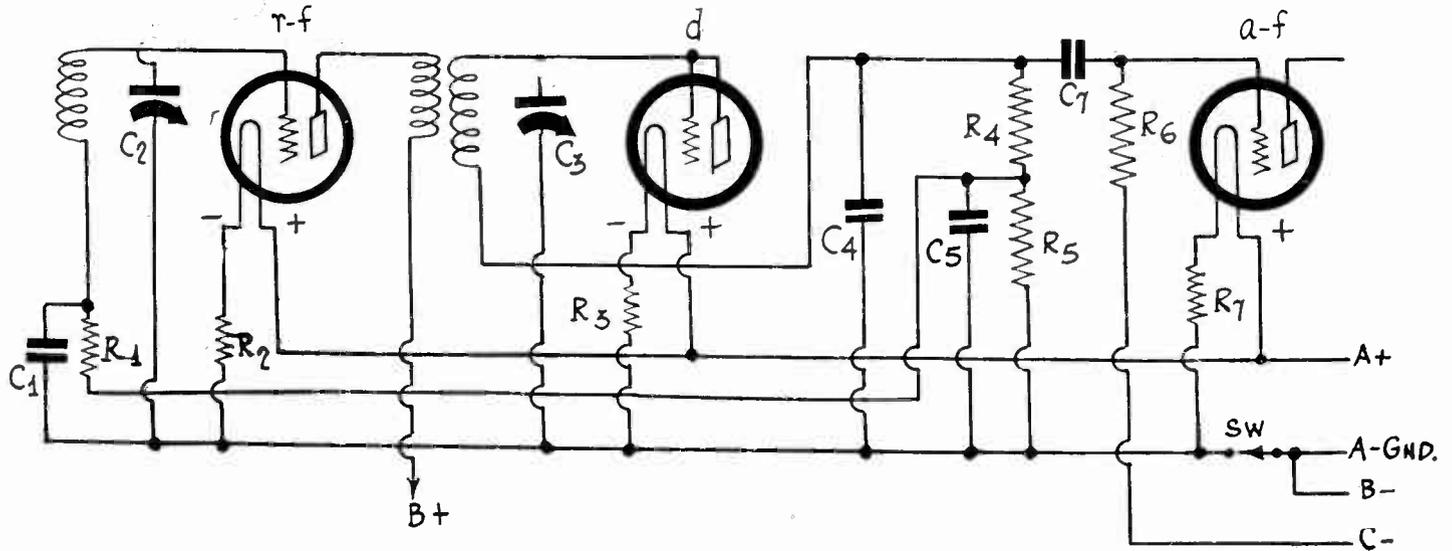


FIG. 2

Here the diode serves as detector and also as an automatic volume control tube. There must be regulation bias, or not very much less than the recommended value, when there is no signal, and this is provided by the grid return, through capitalizing the voltage drop in the filament resistor R2. R5 may be considered as the control element. The modulation is removed by C5, which is 1 m.f.d. C2 stator goes to grid, C3 stator to preceding plate.

reduction in tube life no matter what type tube is used or how powered.

The negative bias is retained, due to R2, even though the grid return is through a high resistance, because at no signal there is no current through this resistance (R5).

The second that there is a signal there is current through the rectifier (d) and while it is direct current, on account of the rectification that has taken place, there is still the signal in it, that is, the current is pulsating direct current. To avoid possibility of negative audio feedback, hence damping, it is necessary that the modulation component be removed from the control section.

### Modulation Removed from R5

The current flows through the untuned secondary feeding the detector, which secondary handles therefore both d-c and a-c, and from the subsequent circuit the a-c is sufficiently removed by C4. Now the current, pulsating d-c, flows through R4. There is another resistor, this one R5, in series, and across it is C5, a large capacity, one that will remove the modulation. It is 1 mfd.

Now, the current at the plate or anode of the detector is negative, hence it is negative even in respect to ground, for, as to this rectified current alone, grounded B minus is positive. So when the controlled tubes have their grid returns detoured to the juncture of the two series resistors, R4 and R5, the grids are negative in respect to what they would be were the returns made directly to ground. If the returns were made to ground the bias would be negative by the voltage drop in R2, whereas the control makes the return more negative than the drop in R2 provides, but only when there is a signal, and the greater the amplitude of the carrier at the detector point, the greater the drop in R5 and the greater the bias.

The automatic volume control system is applicable to tuned radio frequency sets as well as to superheterodynes, in fact, Fig. 2 contemplates a t-r-f set.

### Fixing the Steady Bias

If the tubes ahead of the diode are of the general purpose type, or are 222's, there is little danger of crossmodulation, but if the 236 is used there is a little danger that the bias increase due to the signal will introduce crossmodulation. The 222 and the general purpose tubes do not have detecting characteristics at negative bias increase within the values contemplated by this article, but the 236 has. The 236 is the screen grid tube of the 2 volt series. However, even that would have to be subjected to a three-fold rise in bias before attaining serious detection, and such a large increase is not to be expected from

t-r-f sets, except six circuit tuners or the like, few of which exist in battery models.

Another precaution is that, depending on the type of tube used, and the voltage of the supply to the filament, the steady bias should not be much more than that recommended in the characteristics chart. Such a chart, covering all receiver and some transmitter tubes, total, 34 tubes, was printed in full in last week's issue, dated December 5th. What voltages to apply, bias and otherwise, was given in that chart. The only tube not included was the new 239, the variable mu pentode r-f amplifier of the automotive series, data on which will be found elsewhere in this issue. The 239 was not ready for the market when the characteristics chart was prepared.

### Bias Solution

The solution where the bias is too high to start with—that is, the steady bias alone is beyond the recommended limit—would be to make the drop in the negative leg of the filament less. You could halve it, for instance, by putting half the value of R2 in the negative leg and half in the positive leg, or establish any other proportion the circumstances required. The drop in R2 always can be made what you want it to be, or what it should be, as to steady value, provided the departure is on the side of too high starting bias. If the bias is too low by a small amount, even by one-third, you may leave it thus and depend on the signal for the rest.

The value for Fig. 2 are: C1, 0.1 mfd.; R1, 0.25 meg.; R2, R3, R7, your filament resistors; C2, C3, your tuning condensers; C4, 0.00035 mfd. to 0.001 mfd.; R4, 50,000 ohms; R5, 50,000 ohms; R6, 0.5 meg. or larger value, as high as consistent with absence of motorboating, although no motorboating can arise in a single stage of resistance coupling following a diode, as there can be no feedback; C5, 1 mfd.; C7, 0.01 mfd.

### Diode Arouses Interest

Considerable attention has been attracted to diodes since the publication in these columns, pages 6 and 7 of the November 14th issue, of an article, "Diode Rectification for Push-Pull and Other Circuits." The use of automatic volume control in the diode, issue of November 21st, continued the same general discussion, while the present article constitutes an exposition of the diode applied to battery operated sets. It can be seen, aside from automatic volume control, the change is easily made, and many no doubt will desire to experiment with the results. For primary tuning, ordinary r-f transformers may be reversed. Also, other radio magazines are taking up the subject, and articles along the same lines as published herewith and previously in these columns will be found weeks or months later in other periodicals.

# Bringing Out the Low Nc

## High Current Voltage Divider and Choke

By Charles

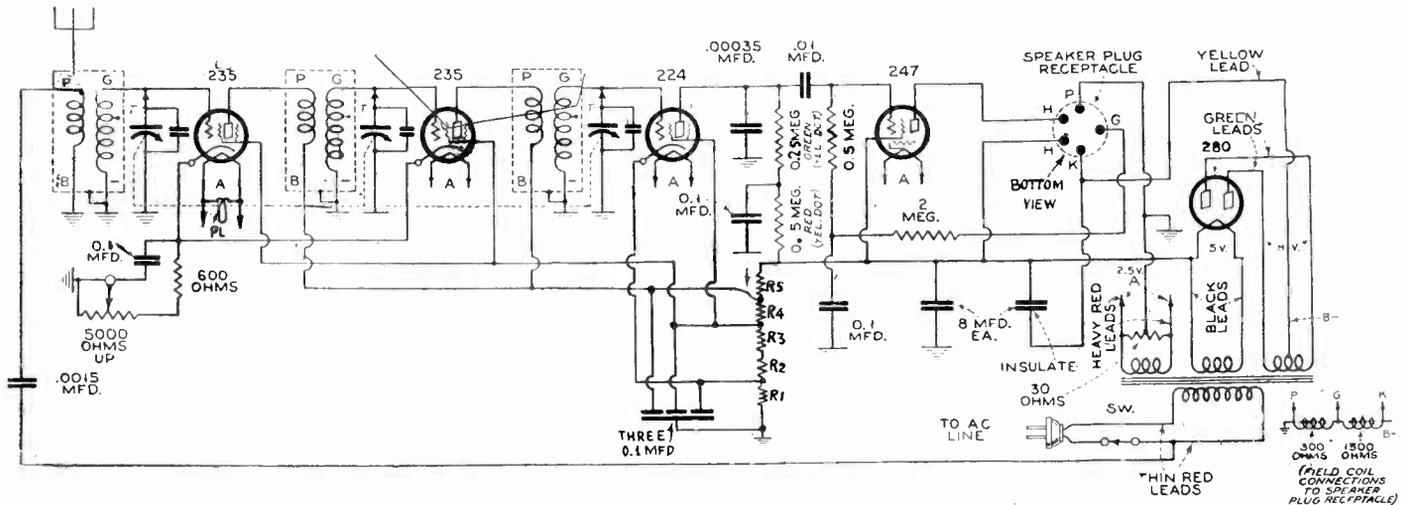


FIG. 1

A high current voltage divider is used in this circuit, intended for midget receiver, while the negative bias for the pentode nevertheless is obtained from the voltage drop in the dynamic field coil, an unusual combination. By this method grid leak values of the order of 2 meg. are practical in the pentode circuit without motorboating. Tonal response was excellent, with full rendition of low notes.

NEARLY all of the circuits for midget set construction, including factory-made receivers, call for grid leak type of resistors for voltage division. Some sets have the B supply choke coil, which is the dynamic speaker's field coil, in the negative leg, to enable pentode bias attainment from a choke, others have the choke in the positive leg and get the bias from an independent resistor, from 247 filament center to grounded B minus. However, an advantage of having the choke in the negative leg is that audio regeneration results.

The other type of voltage divider is known as the high current type, and its function, besides affording voltage distribution, is to permit a sufficiently large bleeder current to steady the actual voltages despite the changes introduced by the signal. As the signal amplitude increases, more plate current is drawn, so voltage drops in series resistors increase, where voltages otherwise governed will increase, and this introduces an unsteadiness. It is not a harmful one and there is no serious objection to these changes, nor is it true that the high current voltage divider completely eliminates them. Yet the high current type does tend to reduce the relative effect of the voltage changes.

### Combination of Uses

Constructors, used to wire wound voltage dividers that stand considerable current, may prefer to use them. Those who adhere to the grid leak type need have no qualms, however, for the only resistor that carries considerable current is the one that drops the maximum B voltage to the B plus plate voltage for the radio frequency tubes. This is marked R5 in Fig. 1, and it is usually recommended that the rating be 5 watts. Now, this is not a husky resistor, yet 5 watts would be ample for the purpose (more than twice the actual wattage). Resistors don't begin to look husky until they get into the 25 watt class.

The other resistors, even in Fig. 1, may be of the 1 watt type, the familiar 2-inch pigtail resistors of the grid leak style.

Fig. 1 shows what is intended to be a combination of uses. While the voltage division may be on the basis of 1 watt resistors, except for R5, for none of them carries more than 10 ma, while R5 will not carry more than 20 ma, if the resistance values of R4, R3, R2 and R1 are lowered, the device becomes a high current voltage divider. The total then need not much exceed 6,000 ohms.

The current through the various sections will differ, and in some instances there will be only a net current, due to the flow of a certain amount in one direction and another amount in the opposite direction. If a voltage divider of around 6,000 to 10,000 ohms total is used, that has sliders on it, the sliders may be moved until the desired voltages are obtained, and a voltmeter will measure

them. For instance, across the total voltage divided there would be around 230 volts, whereas the joint of R5 and R4 would be 180 volts, and that of R3 and R4 around 50 volts or more, that of R1 and R2 around 5 volts. The screen voltage as stated (50) is lower than the standard value, which is 90 volts, but any voltage between 50 and 90 may be used, as this variant is a check on oscillation.

### Speaker Leads

The diagram is partly pictorial, and therefore an explanation of the choke and bias is necessary. Taking the pentode output, this is connected to the primary of an impedance-matched transformer built into the dynamic speaker, and the connections are made to the heater springs of a UY socket used as speaker plug receptacle. The speaker has five leads emerging in a cable with UY plug at end, and the plate and maximum B plus connections are as stated. Then there are the three leads emerging from the field coil—two extremes and bias tap. The receptacle socket has its plate spring for ground connection, grid spring for the tap (G) on the field coil and cathode for B minus, as detailed at lower right of Fig. 1. So the field coil is actually connected between B minus and ground, and the grid return of the pentode is to the tap (G), not to ground. Center of the 2.5 volt filament is grounded.

There is a voltage difference of more than 100 volts between cans of the electrolytic condensers, hence the identified can must be insulated from a metal chassis.

The B current for the pentode, flowing to plate and to suppressor grid, has to get back to B minus, and finds that path wholly outside of the voltage divider. That is, the current flows from B plus maximum to plate and suppressor grid, through the tube to the filament and through the filament to its grounded center and then through the field coil to B minus. The 38 ma or so in the power tube therefore do not go through the voltage divider, but the 12 to 15 ma or so for the radio frequency and detector tubes do flow through at least part of the divider. Although the currents through various sections of the divider will be different, if the average is, say, around 20 ma, the variations are more than halved, except in the pentode, but that tube's variations are controlled largely by those in the preceding tubes.

### Divider Values

In designing a voltage divider, it is usual to ascribe first a certain amount of bleeder current. Suppose it was 20 ma. This would be the value of current without any augmentation by tube drain. Then the bleeder is added to the tube drain, say 15 ma for the radio frequency tubes, whereupon the resistance value of R5 might be (275 minus 180) divided by 0.035, or about 2,700 ohms. This is R5. The plate current that is thus diverted by the tubes

# tes in Midget Receivers

## Bias Combined—Grid Leak Value High

*J. Barrington*

never returns through the divider, but reaches B minus through the cathode circuit of the tubes. This is true also of the screen currents of the r-f tubes. However, the bias of the detector is obtained from the voltage divider, so its plate and screen currents flow through R1. Current that has never passed through R5 therefore passes through R1. The detector plate voltage is the maximum (275 volts nominally, but 230 actually, due to the divider's bleeder current pulling down the voltage).

The value of R5 and R1 will not change materially, whatever the values R2, R3 and R4, within reasonable limits for these three, so a rather wide choice remains for these three.

By using a voltmeter of 1,000 ohms per volt it is easier of course to work out the problem experimentally, and obtain the resistance values. Also, no computation errors will creep in. The experimental method was used in obtaining the resistance values for the chain as follows: R5, 1,200 ohms; R4, 3,000 ohms; R3, 2,000 ohms; R2, 1,000 ohms; R1, 200 ohms.

### High Value Pentode Leak

The method of obtaining the bias from the field coil, while apportioning the other voltages from the voltage divider, made possible the use of a high value of resistor in the resistor-capacity filter of the pentode stage.

The condenser used in this filter is marked 0.1 mfd., but may be larger, say, up to 0.5 mfd. for this circuit, and yet the effect of a large grid leak remains. The 0.5 meg. resistor in the upper part of the grid circuit is in series with the 2 meg. grid leak except as to the reduction effect of the condenser from 2 meg. to ground. This reduction is extremely low for the low frequencies, in fact, may be neglected, and yet the condenser is effective as preventing hum from backing into the pentode tube. Just why this should be so does not seem quite clear, for the circuit (2 meg. with 0.1 mfd. across) is a low pass filter, the condenser being effective therefore only on the high frequencies. Still the hum is of a low frequency, particularly 120 cycles, the second harmonic of the line frequency. Only a phase displacement, therefore, can account for the phenomenon.

### A Previous Experiment

Such a displacement renders the effect of small capacities quite considerable, as was brought out quite obviously in another circuit, where three resistance coupled audio stages were used, a resistor of 10,000 ohms between cathodes of the two preliminary 224 tubes, and a common 10,000 ohm resistor going to grounded B minus. A small capacity across the first 10,000 ohms had a strong tuning effect. As low as 0.0005 mfd. cut off the high notes abundantly. Of course that was in the opposite direction, for it was a low pass filter in theory that proved a real low pass filter in fact. The hum cutter is a low pass filter in theory that is a low pass filter in fact, except as to the hum. Since the result is hum elimination, possibly we had better not look a gift horse in the mouth, but accept the favor gracefully and without inquisitive comment.

The 2 meg. resistor therefore is, to all audio intent and purpose, in series with the 0.5 meg., so we have 2.5 meg. in the grid circuit, a respectable value of resistor. This makes the low note response much stronger. Since such methods may be used it seems idle to mention high audio frequency accentuation of the pentode tube, for the lows can be brought out much more strongly by devices such as the one mentioned.

### Raising Leak Values

It is sound advice to all who build sets, using resistance audio, whether a-c operated or not, to use as high a value of grid leak in the output stage as is practical. The limitation is motorboating. Once that appears, reduce the leak value only so much as necessary to get rid of the motorboating. Moreover, the grid leaks in any other audio stages have a similar effect, and the raising may be done in any audio grid circuit, for the audio channel is a unit, and it is without profit to theorize on the independence of the tube circuits. The audio channel is best regarded as a single impedance.

The detector tube must be included as an audio tube, since it handles audio frequencies. Its radio frequency output is sidetracked purposely, usually by a bypass condenser, except in regenerative sets, and even then the radio frequency is sidetracked finally, that is, after the tickler coil.

The circuit, Fig. 1, is markedly similar to that in Blueprint No. 627, and those desiring to follow Fig. 1 may use the blueprint for the layout and nearly all of the wiring.

### R-F Coil Taps

The taps T on the radio frequency coils represent points picked

up by a rotary selector switch, for coverage down to 80 meters. The coils used were in small aluminum cans (2.5 inches diameter), with screw bases, and the taps were represented by the ground symbol lugs protruding at bottom.

The ground connection was made in the coils to the can itself, except for the B lug representing ground of the antenna winding itself.

A short switch was tried, and the condenser stators connected to it, but running these leads from condenser to switch, back to coil, required such lengths of wire that the coupling was too strong, and there was oscillation on the broadcast band as well as on the short wave band. However, when a special switch was used, with sections so placed that they came right close to the condenser and coil leads, there was no trouble on broadcasts.

The coils consisted of 100 turns secondaries, No. 31 enamel wire, tapped at the 24th turn from the grid end. Therefore the coils evidently contemplate the shorting out of the 76 turns, and if you have only the shorting type of switch, this method has to be used. However, if you desire to follow Fig. 1 literally, and adhere to these coil data, then what is the ground end of the winding, soldered to a rivet in the shield, will have to go to the grid, and the other end of the secondary will be soldered to the rivet. Then instead of shorting out 76 turns, these turns are left in circuit as a continuation to grid, while the condenser stator is moved from the extreme of the winding to the tap 76 turns removed from the grid end.

The primaries for these coils consist of 25 turns of No. 42 silk wire wound over the secondary, with three layers of insulating fabric in between. The actual wire sizes stated need not be used, but any size somewhere near the specifications.

### Detector Screen Voltage

As sliders on a voltage divider were used, it was easy to experiment with different values of screen and plate bias voltages for the detector tube. A much lower screen voltage was used, whereupon the bias had to be lowered, and the rectified voltage output of the detector (using a vacuum tube output meter) was excellent. It merely showed that low screen voltages are quite all right, but bias must be accordingly. However, since one screen voltage for all is handier, and the results were good, with 5 volts negative grid bias, the circuit is shown with a single screen voltage for the r-f and detector tubes.

It will interest many to know that the tonal values were excellent indeed from this receiver, so excellent that some radio engineers specializing in acoustics actually enjoyed the reproduction of an orchestra broadcasting from a local station, and admitted that the quality was good. The set was in a typical midget cabinet, except oblong, rather than of the Gothic arch type. The speaker was 7-inch diameter Rola, series F. The Magnavox and Utah speakers of the same specifications may be used interchangeably. These specifications are: 1,800 ohm field coil, tapped at 300 ohms; output transformer built in, matched for the impedance of a single pentode tube. The cone diameter must be 7 inches for such a cabinet, but may be 10.5 or 12 inches for a console installation.

## Kit Enables Short Wave Sets to Reproduce Television

Short Wave Club members can now very inexpensively add television to their present equipment and enjoy the thrill of seeing as well as hearing their favorite programs. The See-All Telesvisor, manufactured by the Television Manufacturing Company of America, Inc., New York, can be purchased in kit form at a reasonable cost for use with a present short wave set.

The feature of this new scanner kit is the low price coupled with excellent engineering and workmanship. Actual demonstrations of the See-All kit prove the manufacturer's claim that it produces a brilliantly clear picture.

One of the reasons for this is that the holes in the special scanning disc are square, not round, thus providing greater illumination.

Another feature of the See-All scanning disc is that a double spiral of holes is provided, which greatly simplifies the framing of the picture.


Upon receipt of the call signal the See-All tunes is instantly in perfect synchronization with the broadcasting station. The kit comes with detailed simple instructions and blue prints for quick assembly. With over thirty important radio stations now broadcasting television, this new form of radio entertainment should be very gratifying to the club members.

# THE SECRET OF SUCCESS IN BR

# Apply Precision to the Short

## The Programs of Strange Lands

### 15 TO 200 METER CONVERTER

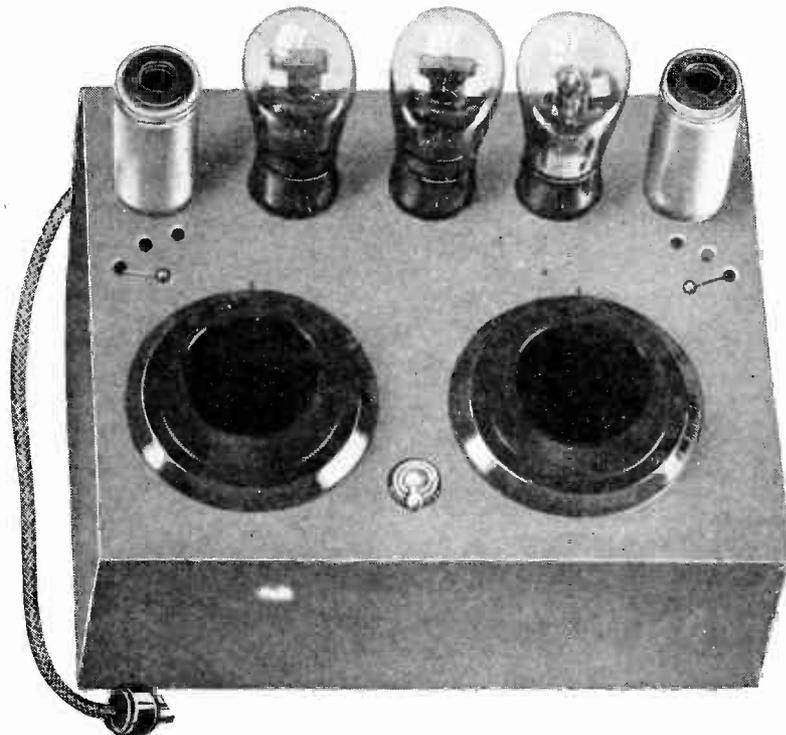

**H**ERE at last you have it—a highly sensitive short-wave converter, 15 to 200 meters, that works on *any* set and that has its own A, B and C supply built in and that does not use plug-in coils for band shifting. Two separate tuning condensers and two dials are used, so there *can not be any possibility of sensitivity loss* due to mistuning, as where ganging prevails. Also, any intermediate frequency may be used.

The little extra effort in tuning is well repaid by thousands of miles of extra reception. Stations all over the world have been tuned in, using this converter with a good broadcast set.

There are only three connections to make in teaming up the converter with a receiver.

Two coils are used, one for oscillator, the other for modulator, and two tube sockets are near these coils, and underneath the top panel, not for tubes but so that you can move the grid connecting wire of the two condensers to any one of four points for wave shifting. Simple, effective, inexpensive, infallible!

Three 237 tubes are used. These are of the automotive series and are most economical, the total consumption, A and B power being less than 10 watts. Hence costing no more than one-tenth of a cent per hour to operate!

This converter works on superheterodynes as well as on tuned radio frequency sets, because **IF ANY CONVERTER IS A GOOD ONE IT IS BOUND TO WORK ON ANY TYPE OF SET.**

There are 16 mfd. of filter capacity and a 15 henry B **Complete Parts, choke, in the B supply, as well as a husky line transformer. Less Tubes**

Do not suppose just because the price of parts is low that this converter does not perform efficiently, for it is a knockout! What sensitivity! What power! What results! Send for complete parts to-day. A clear diagram is furnished with each kit. Order Cat. R-CNV.....

**\$7.60**

TUBES USED: THREE 237.  
(SEE TUBES ADVERTISED AT BOTTOM OF OPPOSITE PAGE)

### INTERMEDIATE FREQUENCY TRANSFORMERS



**F**OR short wave superheterodyne work 1,600 kc. is the popular intermediate frequency, because you can tune to below 9 meters without interlocking of modulator and oscillator circuits, due to the high intermediate frequency. Our 1,600 kc. shielded transformers have large diameter wire, loose coupling for selectivity and stability, and Hammarlund's new superheterodyne condensers built in, accessible to a screwdriver. Both plate and grid circuits are tuned. Shield is 2 3/8 inch diameter, 2 3/8 inches high. For variable mu tubes. Order Cat. FF-1600 @ \$1.65

Doubly tuned fixed-frequency transformer, 1 to 1 ratio, 175 kilocycles. Band pass filter characteristic. Hammarlund 20-100 mfd. equalizers across primary and secondary accessible. Aluminum shield (must be grounded) 2 1/4 inches diameter, 2 1/2 inches high, removable bottom. For variable mu tubes. Order Cat. FF-175 @ \$1.50

Same as directly above, for 450 kc. Order Cat. FF-450 @ \$1.50

Please Remit 10% With All C.O.D. Orders. Roland Radio Co., 35-W Hooper Street, Brooklyn, N. Y.

### 15 TO 200 METER SET



**Y**OU can build a midget short wave set that will give you the acme of performance—six tubes, including variable mu radio frequency amplification, screen grid power detection, and **THREE STAGES OF REGENERATED AUDIO AMPLIFICATION.** Then you can bring in short waves with a wallop.

This set enables band shifting from the front panel without any further effort than turning a single knob. It is equipped also with on-and-off switch and volume control (one unit) and a rotary band selector switch of the anti-capacity and non-shorting, insulated type.

You know from your experience with short waves that you need plenty of audio amplification, and here you have it—two stages of screen grid audio and 247 pentode output! The audio amplifier is of the highest quality and is *perfectly suitable for television.*


The radio frequency end affords the simplest possible method of tuning in a wide band of frequencies, so that the radio circuits are all tuned to the same frequency, and no padding or other difficulties present themselves. The circuit is tuned radio frequency.

The cabinet into which the chassis fits is one of exquisite beauty, being a two-tone walnut effect, with decorative grille for a 7 inch dynamic speaker. All parts are of the highest class, including Rola full dynamic speaker (7 inch cone). Build this set and know real short wave reception. All parts and diagram are supplied at this price, exception tubes.

**\$24.25**

Order Cat. R-S.....  
(Tubes used: three 235, one 224, one 247 and one 280. See tube prices at bottom of opposite page.)

### SHORT WAVE SWITCHES

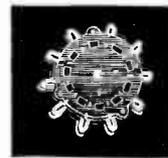

**S**WITCHES of special precision, positive contact, non-shorting, are needed for short waves. These rotary selector switches are suitable for moving the stator connections of tuning condensers

to taps or to separate coils. Single knob actuates multiple circuits. Knob can't slip on shaft and switch can't slip on panel.

Single circuit, 4 taps and index. Cat. 4-1-SW @ \$1.05

Two circuits, 4 taps and index for each. Cat. 4-2-SW @ \$1.87


Three circuits, 4 taps and index for each (fewer taps may be used). Cat. 4-3-SW @ \$2.28

*These switches may be used for any purpose where single, double or triple circuits are to be worked, up to four different positions, and are suitable for all wave switching because the shafts are totally insulated. These are anti-capacity switches of the precision type.*

# INGING IN UNCANNY DISTANCE Waves and Conquer the Earth! Made Familiar to You Nightly!
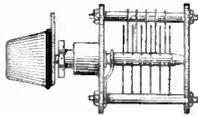
## MIDGET CONDENSER

The rotor has no end stop and therefore precision calibration of oscillators and tuners is not upset by dial-jarring.



A MIDGET condenser for high frequency work, equipped with knob and pointer, and including a milled bushing that can be attached for taking 1/4 inch dial hub. This condenser may be used either as a trimmer for a main condenser or alone for tuning in the high frequencies. Particularly valuable for amateur work reception, short wave converters and short wave sets generally, where wide dial spread is highly desired, and five coils are used for coverage of 200 to 15 meters. The capacity is 0.00045 mfd. (45 mmfd.). Cat. CHMG-45 @ \$0.69

The same model condenser also is obtainable in 0.00055 mfd. (55 mmfd.) capacity. Order Cat. CHMG-55 @ \$0.69

Oscillator coil for switching bands without plugging in, to cover 15 to 200 meters with 55 mmfd. Cat. M-55-C (coil only) \$2.15

## TAPPED COILS FOR BAND SHIFTING


TAPPED coils are proving very popular, as they make for economy of room and also afford good results. The Roland coils are obtained in two types, one for broadcast coverage, 200 to 600 meters, with tap for going down to 80 meters, so television, airplane talks, amateur and other interesting transmission may be heard, and the other for coverage from 200 to 15 meters only. (No broadcast band.) These coils are wound on 1 1/2 inch diameter and are attached at the factory to aluminum screw bases, with lugs protruding at bottom. An aluminum cover (not illustrated) screws over the base.

The primary is wound over the secondary, with insulating fabric between, and the inductance is kept exactly equal for all coils by keeping the axial length of the winding identical, as well as the number of turns. Therefore at top (what looks like a separate winding) a space is "spun," as well as at bottom, to insure such identical inductance.

For 80-600 meters, for use with 0.00035 mfd. three gang, order Cat. M-35-C (three coils, three shields at this price) @ \$2.45  
For 0.00046 mfd. order Cat. M-46-C MNSC @ \$2.45  
For 0.0005 mfd. order Cat. M-05-C @ \$2.45

The short wave coils, 15 to 200 meters, are listed herewith:

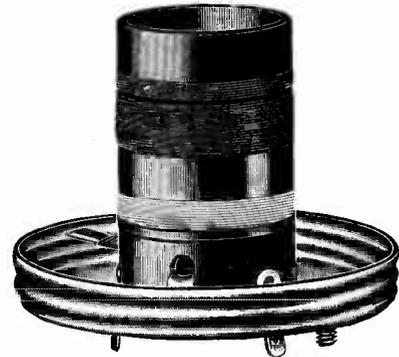For 0.00035 mfd., two shielded coils, one with two windings for antenna coupler, other with three windings for sensitized detector. Order Cat. OSW-35-L @ \$1.95  
For 0.00015 mfd., two shielded coils. Cat. SW-015-L @ \$2.05



## PRECISION PARTS AND ACCESSORIES

We carry a complete line of Rola dynamic speakers, all sizes, all purposes, as well as the exclusive Farrand inductor speaker for push-pull pentode output that requires no output transformer.

The Rola speakers are very popular in midget sets, both of the broadcast and short-wave type, as well as for all-wave coverage, and are used also to great advantage in automobiles.

The Rola speakers for home receivers are obtainable with field coils that may be used also as the B supply choke coil, and which field coil has a tap, so that bias for a pentode may be obtained from the field coil itself. This method introduces audio regeneration, which improves tone and sensitivity. The tapped coils have a total resistance of 1,800 ohms and the tap is at 300 ohms from the ground end. The grid return of the power stage is connected to the tap. This is the method used in all our a-c circuits.


Rola dynamic speaker, 1,800 ohm field coil, tapped at 300 ohms. Output transformer matched to single pentode is built in. Diameter of cone is 7 inches. Cat. RO-18 @ \$4.50

Same as above, except that cone diameter is 10.5 inches. Cat. RO-18-10 @ \$5.85

Same as above, except that cone diameter is 12 inches. Cat. RO-18-12 @ \$7.25

Rola dynamic 6 inch cone for automobile sets, 6 volt field to be connected to car's storage battery. Speaker fits on bulkhead under the instrument board. Shielded cable is supplied with each speaker. Cat. RO-AU @ \$4.95


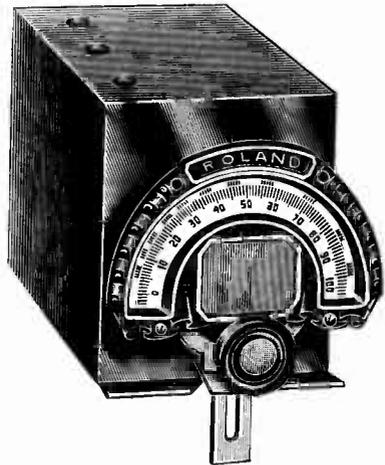
Notes: Send for our Blueprint No. 629, six tube auto set. See bottom of this page.  
Magnavox speakers can be supplied, if desired, at same prices, same specifications. Use code "MA" instead of "RO", same letters and numbers otherwise, when ordering Magnavox speakers.



**MATCHED COMBINATION TUNING UNIT.** to cover from 80 to 600 meters, using a coil system including a single tap on each secondary, and serving as the tuning adjunct in superheterodynes with an intermediate frequency of 175 kc. The tap need not be used if only the broadcast band is desired. The oscillator circuit is accurately padded for that in intermediate frequency. The matched tuning unit includes a three gang, brass-plate, steel-frame condenser, with stator shields built in, the entirely shielded again, with extra partitions built inside to serve as rotor shields. Low vibration factor to avoid grunting nuisance

FARRAND inductor dynamic, for pentode push-pull requiring no output transformer. Simply connect the two tipped leads to the plates of the pentodes and connect the untipped (yellow) lead to the maximum B plus voltage. By this method no plate current flows through the winding, only signal current so there is no danger of burnout or premature saturation, and the tone quality is superb.

This speaker has one of the best audio curves of any ever produced, but it is not quite so sensitive as other type dynamic speakers, and therefore should be used on high powered sets. It is suggested therefore that it be used on a-c sets having no fewer than six tubes or battery sets having fewer than seven tubes. It is strongly recommended, however, that the speaker be used on all high powered sets using push-pull pentode output. These pentode speakers are not generally obtainable. We're privileged to have a source of supply that enables us to fill the needs of those most discriminating as to tonal values. Order Cat. FAR-1EXT @ \$8.75

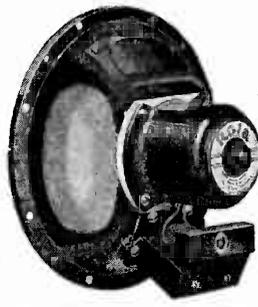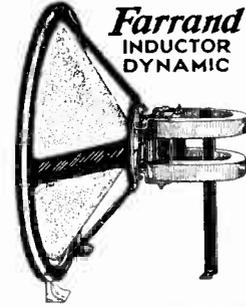

of some types of superheterodyne condenser construction. Three trimmers are built in. The three shielded coils, of the same general appearance as the one illustrated at upper right-hand position on this page, are supplied. The oscillator coil is already padded. Order Cat. CMFU @ \$6.65

Set of three shielded coils, padded for 0.00035 mfd. for use with 175 kc. intermediate amplifier. Tap is included. Cat. SUC-35 @ \$3.10

Same as above (set of coils) except for 0.00016 mfd. Cat. SUC-36 @ \$3.10

Same as above, except for 0.0005 mfd. Cat. SUC-5 @ \$3.10

800 TURN HONEYCOMB coil, total diameter 1 1/4 inches; will tune to 175 kc. with 0.0001 mfd. (or 20-100 mmfd. equalizer) Cat. HO-800 @ \$1.45

200 TURN HONEYCOMB coil, same style, tunes to 450 kc. with 0.0001 mfd. Also may be used without condenser as antenna input coil, screen and plate choking, or two used inductively coupled for evening the amplification of t-r-f sets, in untuned stage feeding detector. Cat. HT-500 (each) @ \$1.43

50 TURN HONEYCOMB coil, 1/2 millihenry for all short wave purposes. Cat. HC-50 @ \$0.25

1 WATT PIGTAIL RESISTORS, all resistance values. Mention Cat. PGTR and state resistance in ohms thereafter. Price \$0.15

5 WATT 2,000 OHM resistor to drop maximum B to B plus 180 volts for plates of r-f tubes in any t-r-f set. Cat. S-W-2 @ \$0.45

POTENTIOMETERS: 400 ohms at 27c; 5,000 ohms @ 35c; 25,000 ohms @ \$1.25; 50,000 ohms @ \$1.25; 100,000 ohms @ \$1.25; 500,000 ohms @ \$1.25.

POTENTIOMETER with a-c switch attached, 10,000 ohms, for variable mu grid bias as volume control. Cat. POT-5-SW @ \$1.55

WALNUT FINISH ROLAND (illustrated upper left) CABINET for midget sets, cut for 7-inch cone. Cat. MDCB @ \$4.90

TWO GANG 0.00035 MFD. straight frequency line condenser, brass plates; long 1/4 inch shaft; nickled frame. Shielded. Cat. DIA-45 @ \$1.95

**Eveready-Raytheon 4-Pillar Tubes**

237 @ \$0.80	215 @ \$0.60	210 @ \$1.80	236 @ \$1.65
224 @ .90	250 @ 3.00	112A @ .90	237 @ 1.95
235 @ .96	U-99 @ 1.50	222 @ 2.70	238 @ 1.65
247 @ .98	V-99 @ 1.68	231 @ .96	239 @ 2.05
236 @ .48	120 @ 1.80	231 @ .96	280 @ .60
171A @ .54	201A @ .45	232 @ 1.30	281 @ 3.00
210 @ 4.20	200A @ 2.40	233 @ 1.65	Neon @ 4.50

DYNATRON OSCILLATOR, a-c operated; plug-in coils; 15 to 550 meters; built-in filament transformer; requires 90 volts B supply extra, which may be battery. National vernier dial. Completely wired, with tube. Cat. DN-OS @ \$11.00

KELFORD 30 henry choke; stands up to 100 ma; in black shield case. Cat. KEL-30 @ \$1.75

KELFORD 15 henry B supply choke; 60 ma; unshielded. Cat. KEL-15 @ \$0.95

2.5 VOLT center tapped fil. trans., 8 amperes (will stand up to five heater tubes, when voltage is 2.25 v). Cat. FLT @ \$1.62

HAMMARLUND 0.0002 mfd. variable condenser, junior middle; rotation is within 2-inch diameter; for short waves. Cat. H-20 @ \$1.35

HAMMARLUND 60 mmfd. manual trimming condenser. Cat. H-60 @ \$0.79

HAMMARLUND 20-100 MMFD. EQUALIZERS; adjustable screw works in a threaded brass stud, so excess force cannot damage the unit. Cat. 3-EQ-100 (price is for three) @ \$0.60

CHASSIS for midget, fits in Roland cabinet; chassis is 1 1/2 inches wide, 7 1/2 inches front to back; flaps front and back 3 inches high; drilled for socket and speaker plug and for volume control and switch at front. Cat. 5-TCH @ \$1.75

CHASSIS for 6 tube midget. Cat. 6-TCH @ \$1.75

TWO GANG 0.00035 MFD. straight frequency line condenser, brass plates; long 1/4 inch shaft; nickled frame. Cat. DIA-35 @ \$1.95

THREE 0.1 MFD. condensers in one shield case; black lead is common; three red leads go interchangeably to destination; mounting screw built in. Cat. 31 @ \$0.57

MIDGET POWER TRANSFORMER, for five-tube set, to handle three heater tubes, one 247 and one 280. Cat. MPT-5 @ \$3.15

MIDGET POWER TRANSFORMER for six-tube set, to handle four heater tubes, one 217 and one 280. Cat. MPT-6 @ \$3.55

8 MFD. WET ELECTROLYTIC condenser, for inverted mounting; washer and extra lug provides insulation for chassis for circuits with B choke in negative leg. Cat. LCE-8 @ \$0.85

### BLUEPRINTS

Blueprint No. 627, five tube a-c midget, broadcast band. Uses two 235, one 224, one 217, one 280. There is no 5 tube midget to compare with it. 80 meter tap coverage optional. Order Cat. BP-627 @ \$0.25  
Blueprint No. 628, six tube a-c short wave set, no plug-in coils; 15 to 200 meters. Order Cat. BP-628 @ \$0.25  
Blueprint No. 629, six-tube auto set. Order Cat. BP-629 @ \$0.25

**Roland Radio Co**

35-W Hooper St., Brooklyn, N. Y.

ALL PRODUCTS ARE BRAND NEW. NO USED OR DISTRESS MERCHANDISE, DESPITE THE LOW PRICES.

**A Question and Answer Department conducted by Radio World's Technical Staff. Only Questions sent in by University Club Members are answered. Answers printed herewith have been mailed to University Members.**

# Radio University

To obtain a membership in Radio World's University Club for one year, send \$6 for one year's subscription (52 issues of Radio World) and you will get a University number. Put this number at top of letter (not envelope) containing questions. Address, Radio World, 145 West 45th Street, New York, N. Y.

**Annual subscriptions are accepted at \$6 for 52 numbers, with the privilege of obtaining answers to radio questions for the period of the subscription, but not if any other premium is obtained with the subscription.**

## Choice of a Circuit

HAVING 28x14 inches room in a console I intend to build a receiver and was wondering whether four stages of tuned radio frequency, detector, two stages of audio and rectifier would be better than an eight tube superheterodyne. Also, I desire to receive television and would like to know if transformer coupled audio will be satisfactory, as it is of the best and most expensive kind. If I build a super, is it all right to put a coil in the screen of the modulator to couple to the oscillator, or what do you suggest? Should I use the 235 or the 551 tubes for radio frequency?—H. G. D.

You will get high sensitivity from a tuned radio frequency set of the type that you describe, but the selectivity will not be comparable to that the super will afford. Moreover, four stages of t-r-f can not readily be stabilized, and you are almost certain to have oscillation trouble. We advise you to build a super instead. As for television, using audio transformers of the best type, it is practical to get a good picture, even though resistance coupling is more usually recommended. It is true that a better quality of amplification is obtainable from resistance coupling, but some of the resistance audio circuits in television receivers are not as good in that respect as the best audio transformers. The reason is inappropriate choice of constants. Evidently you have the transformers and there is no reason why you should not use them. Be sure, however, not to connect them with primaries as plate loads on screen grid tubes. Use a 227 as negative bias detector and another as first audio tube, with push pull output. It is all right to couple as you suggest, but take care not to make the coupling tight. The 235 tubes cost less and are very satisfactory.

\* \* \*

## Hum on Converter at 25 Cycles

ABOUT four months ago I bought a short wave converter, but it so happened it was for 50-60 cycles, while the frequency here (London, Alberta, Canada) is 25 cycles. As you may surmise, there was very considerable hum. I put in a 25 cycle transformer, but this did not cure the trouble. Then I suspected the filtration, and I believe that the choke coil in the B supply is not large enough, and that I need more than the two 8 mfd. electrolytic condensers, to get rid of hum.—C. H.

The 25 cycle transformer certainly was necessary, for while a transformer of a given frequency rating may be used at higher frequencies, it can not well be used at lower frequencies, because the impedance is too low at the lower frequencies. Likewise the filtration for 25 cycles has to be better. It is doubtful whether you need any more choking, even though the inductance of a choke intended for 60 cycles is less at 25 cycles. The common practice in receivers is to add more capacity next to the rectifier, so we suggest that you connect an 8 mfd. condenser in parallel with the present one next to the rectifier, and we believe this will be satisfactory. If, however, you desire also to add more inductance, simply put another choke in series with the one now there, arranging the condensers so there will be the two 8 mfd. in parallel (totaling 16 mfd.) from the B plus output of rectifier to ground, and the 8 mfd. single at the end of the newly constituted choke system. In other words, do not put capacity at the joint of the two chokes.

\* \* \*

## Phonograph Amplifier

A SPECIAL amplifier, for use with phonograph only, is desired. I have on hand one Polo power transformer, 100 ma rating, 700 volts d-c, 5 v and 2.5 volts, also an Amertran output transformer, primary 14,000 ohms for pentode tube, secondary, 15 ohms, to work into my dynamic speaker, also one Audak pickup of specially low impedance with special Ferranti matching transformer, matched primary for the pickup and secondary for the input to a 227 tube. What I want is no hum. I have read "New Audio Circuit," by Bernard, on page 4, Fig. 1, October 10th issue, also "Public Address System," by Brunn, September 5th, page 12. How about providing a push-pull output from 227 first audio? And is the Bernard (new audio) amplifier as quiet as Brunn's public address system? I have had hum trouble with pentodes. The amplifier is to be used in a living room, 30 x 40 feet.—L. T. G.

The public address system would be rather too much for the living room, as it is intended primarily for small halls and auditoriums. The Bernard audio amplifier, using audio regeneration, has been worked out entirely along the lines of resistance coupling and therefore does not fit into your parts supply. You will get all the volume you need, and more, from two stages of audio, the last stage in push-pull. The power

transformer will fit nicely into the requirements if you use 247's in push pull. The first audio tube may be a 227, with 90 volts applied to the plate through the primary of the push-pull input transformer, whereupon the bias should be 6 volts negative, through a potential drop in a cathode resistor, and the plate current will be 2.7 milliamperes. This current is low enough not to reduce substantially the inductance of the primary of the push-pull transformer. The maximum undistorted power output of the first stage will be 30 milliwatts and the ohms load required is 14,000. The biasing resistor should have a condenser of 8 mfd. across it. The push-pull stage is standard, but be certain not to put a condenser across the common resistor from filament center to ground biasing the push-pull tubes. Connect a resistor of 0.25 meg. from the joint of the secondary winding of the push-pull input transformer to ground, and put a 1 mfd. condenser across this resistor. Thereby you will have a resistor capacity filter that will stop hum from backing into the output tubes. The hum should be very low, particularly as push-pull gets rid of second harmonics, and the principal hum component is the second harmonic of the line frequency, that is, 120 cycles. The filtration need be no more than the usual B supply choke coil with 8 mfd. next to the rectifier and 8 mfd. at the other end of the choke. However, if your speaker field has a tap to permit pentode bias, then you may put the choke in the negative leg of the rectifier, connect the push-pull grid return through the 0.25 meg. resistor to the tap in the field coil, instead of to ground, but have the 1 mfd. bypass condenser go from the joint to ground nevertheless. The pentodes do not produce hum any more than do the 245's, only they amplify more. That is, the  $\mu$  of the 245 (single) is 3.5, whereas that of the pentode is 90, so the pentode enables a gain of almost 26 times that of the 245. Your hum trouble may have been due in part to inclusion of a bypass condenser across the biasing resistor of the push-pull tubes, for such a condenser upsets the dynamic symmetry of the push-pull circuit, to the extent that any overtaxing of tube by signal is not to be compensated. In a proper push-pull circuit there is no signal current in the biasing resistor, so the use of a bypass condenser could never work anything but injury.

\* \* \*

## Coils for 628-B

PLEASE give coil data for 0.00035 mfd. condenser, for use in the circuit covered by your Blueprint No. 628-B (short wave six tube receiver of the midget type).—B. A. J.

The impedance coil for broadcasts may consist of 127 turns of No. 34 wire or thereabouts, on 1 inch diameter tubing. For a series condenser of 100 mfd. in the oscillator circuit, for broadcast waves, the first secondary may have 47 turns, the secondary 20 turns, and the third secondary 9 turns, the fourth 4 turns on 1 inch diameter. Use 28 enamel wire. The plate winding is between the first and second largest secondaries and consists of 22 turns. The blueprint clears up the relative positions. While 628-B is a set primary for 15-200 meters, the data given cover the broadcast band as well, since this is easily done.

\* \* \*

## Speaker Impedance

I WONDER if you could tell me if the impedance of the Farrand inductor speaker, model G, is satisfactory for pentode push-pull output, and if not, what shall I do about obtaining a suitable output transformer?—J. M.

If you have the Farrand Model G with the center tap coming out as a free lead (as distinguished from the two tipped leads), then you do not need any output transformer. Simply connect the tipped leads to the plates of the output tubes, and the plain lead (yellow) to B plus maximum voltage. The impedance is satisfactory for such a circuit. However, the Farrand is not as sensitive as the other types of dynamics, therefore there will be less volume of sound, not due to impedance trouble, but to the constructional features of the speaker. The tone will be most excellent, as the Farrand inductor in that respect is one of the best speakers ever made. The Farrand company sold out to a set manufacturer that now uses the inductor dynamic in his own sets, and the speakers are not generally obtainable by experimenters for that reason. If you have a Farrand with single output (no yellow third lead) it would be handier to use it with an audio choke coil in the plate circuit of a single output tube, a 2 mfd. condenser connected one side to plate, other side to one of the speaker leads, the other speaker lead going to the center tap of the power tube filament winding (usually ground).

### Detector Short Wave Adapter

As a reader of your magazine I have become interested in short waves. I am particularly interested in a set that could be plugged into the detector of a broadcast receiver. Do you know of a good short wave device of this kind or can you give diagrams for its construction? Do you believe that such an arrangement is practical and that the results would be equal to those of a regular short wave set?—E. G. S.

An adapter such as you describe is not very reliable. It works on some sets, not on others, and at best does not do nearly as well as a good short wave set. The resort to plugging into the detector brings in too many uncertainties, such as type of detector is used, distribution of d-c voltages and nature of the plate load. As such a device must be regenerative, the trouble too often is that regeneration fails, as conditions are

FIG. 974

A regenerative detector and one stage of audio. This circuit was popular several years ago for broadcasting listening, on ear-phones, and short wave listening, but present conditions require greater selectivity, as obtained from the circuit shown in Fig. 973. Besides, the t-r-f stage (Fig. 973) provides about as much gain as does an audio stage.

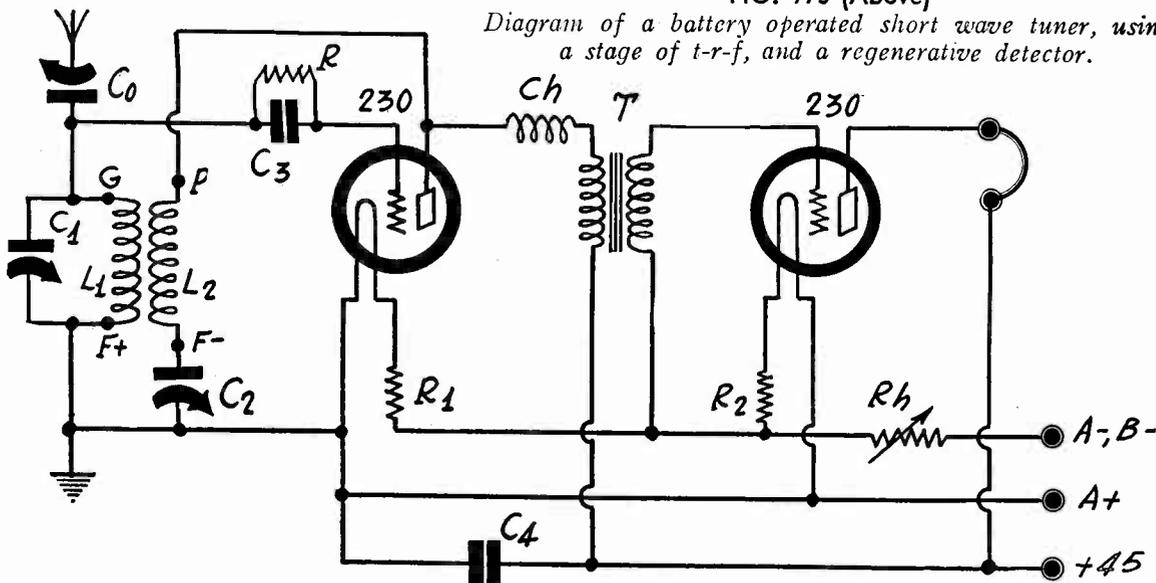


FIG. 973 (Above)

Diagram of a battery operated short wave tuner, using a stage of t-r-f, and a regenerative detector.

not right to produce it, and thereupon next to nothing is heard. We published some information on building such devices about a year ago, but pointed out the absence of general application, along the lines now laid down. We do not encourage the building or use of these detector socket adapters, as short wave converters can do ever so much more, and short wave sets outclass both. A good converter was described in last week's issue, dated December 5th, and another one is published this week.

### Short Wave Set

Will you please tell me where to get a blueprint of the circuit shown on page 8 of the September 5th issue, a short wave midget?—H. L. N.

That was a five tube a-c tuned radio frequency set. There is no blueprint on it. However, Blueprint No. 628-B is available, for 15 to 200 meter coverage (optional 200-550 meters easily exercised), using six tubes in an a-c superheterodyne circuit.

### From a Battery User

I HAVE built a compact resistance coupled circuit, one 222 r-f tube, one 240 detector, one 222 first audio and one 112 second audio, but have been unable to overcome slow motorboating, except at the expense of greatly reduced volume. You have shown methods of overcoming audio regeneration but I have not seen where you ever applied this to battery operated sets. Also, in regard to the diode detector, November 7th issue, you apply this to a-c sets, but not to battery sets. I would like to include this detector. Please take care of this in an early issue, as we battery users are many.—J. C. W.

The slow motorboating may be killed off by using a lower value of grid leak in either first or second audio circuits. Also a resistor-capacity filter will tend to isolate the last audio grid circuit from the variations that cause the trouble. Disconnect the power tube grid leak from its grid return, insert an 0.25 meg. resistor between this point and C minus, and connect a 1 mfd. from the resistors' juncture to ground. Overcoming regeneration in battery operated sets is more difficult than in a-c sets, because batteries are used for biasing, hence there are no biasing resistors in the plate-grid circuits. The set you built is not one of extreme sensitivity, and as the diode is best applicable to sensitive sets, because adding no gain of its own, you would not get enough volume of sound, unless you increased the primaries of the transformers considerably. You may retain the detector tube and circuit as you have them and by getting rid of the slow motorboating you will have good performance. Also, you may try a condenser of 8 mfd. from B plus maximum to ground, to lessen motorboating, although when motorboating is very slow of course a capacity of 8 mfd. would not be of much help. Data on battery tubes as diodes are published elsewhere in this issue.

### Two Circuits Compared

Will you kindly illustrate and compare these two circuits: each has two tubes and each is for short waves, but one has one stage of audio and the other has a stage of t-r-f and a detector. These circuits are for battery operation and to cover only one band (200 to 60 meters).—N. I. P.

Please see Figs. 973 and 974. Fig. 973 represents the stage of t-r-f and detector, while Fig. 974 shows the detector and one step. We prefer Fig. 973, because of the increased selectivity. The short waves are badly congested and high selectivity is needed in that region much as in the broadcast band. As most short wave listeners want some foreign reception, and about their only opportunity of getting it is through high selectivity and good sensitivity, we recommend the two tuned circuits. Using a tickler coil, of course plug-in coils or switching would not be very practical, however you desire to cover only about a 3-to-1 frequency ratio, and this can be done with 0.00035 mfd. tuning condensers. L1 and L2 are the antenna coupler. L1 is 10 turns, spect 1/8 inch, L2 is 50 turns, No. 28 enamel wire on 1-inch diameter. L3, L4, L5 are the three circuit coil. L3 has 6 turns, L4 has 50 turns, tapped at the 10th turn from the ground end. No. 28 enamel wire, 1 inch diameter. L5 is on a shaft. Secure the shaft to the front panel to actuate the coil, which clears the other form by 1/2 inch. The diameter is 1/2 inch dowel, and the number of turns is 16 of No. 32 wire on each side of where the shaft is fastened. Provide an end stop for the tickler and reverse tickler connections if regeneration fails. NC is an equalizing condenser of 15 mmfd. maximum, adjusted with a neutralizing rod to stop oscillation in the r-f tube. CT also are equalizers and may be of higher capacity. C1 and C2 are 0.00035 mfd., C3 is 1 mfd., C4 is 0.00025 mfd. with clips, C5 is 0.0001, 0.00025 or 0.00035 mfd. For 201A tubes, R1 is 20 ohms, but should also have a 4-ohm resistor in series with it (not shown), while R2 is 50,000 ohms and R3 is 4 ohms. These directions assume a 6-volt storage battery. The other circuit, Fig. 974, is adaptable to plug-in coils and the condensers and coils may be smaller.

### Diode in T-R-F Set

HAVING just finished reading Herman Bernard's article in the November 21st issue on the use of the diode as a combination detector and automatic volume control tube, while this applied to an a-c superheterodyne, could it not also be applied to a tuned radio frequency set? Would not a dual impedance transformer work as a coupler between a first audio tube (227) and a push-pull pentode output?—F. G. L.

The system of course can be applied to tuned radio frequency just as to superheterodyne sets. In fact, the circuit is identical in this respect. The dual impedance can be used, working out of a 227.



tells how to add automatic volume control to t-r-f sets, and could it be added to these that have regenerated audio?—W. B. M.

Another step of r-f amplification could be added, but it is not necessary to do so, as the set, as shown in Blueprint No. 627, has the r-f gain developed almost to the squealing point, and added t-r-f, while increasing selectivity, would not increase sensitivity, as primary turns would have to be removed in the plate circuits to avoid squealing. The blueprint itself contains all improvements to date. You can, if you desire, add regeneration to the detector, for improved sensitivity and selectivity, but that adds another control and besides introduces the usual critical tuning accompanying regeneration, which is generally not wanted in a broadcast set nowadays. It is better to build the set completely as shown, rather than to use only the tuner portion with an extra power pack, as the total parts, including cabinet cost something less than \$20, and a power pack alone, such as you have in mind, costs about as much. However, the voltage values are: for r-f plates, around 200 volts; for screens, around 90 volts; for detector bias, around 5 volts; for pentode bias, around 16.5 volts, and for volume control (235 tube adjustable bias) from about 1.5 volts to about 15 volts. If, in using a separate power pack, the field is independent, and thus not in the negative leg of the rectifier, the whole circuit is changed, and we have no prints to accommodate your needs. For a six tube set the total current drain (where the extra tube is for r-f) would be about 60 ma, the voltage rating being unchanged, that is, around 350 volts a-c on either side of B minus, or, after the filtration, 275 volts d-c. If another 247 pentode is added besides, add 40 ma, voltages the same. However, the power transformer must have a wattage rating to meet the need (100 ma, 350 v a-c either side of B minus, 700 v a-c total, of course). The Monitor Receiver's two stage system has audio regeneration. Automatic volume control can be added to t-r-f sets as well as to supers, but is found almost exclusively in supers, because so soon as these extra refinements are introduced, cost goes up, and it becomes cheaper to build a superheterodyne. The automatic volume control is introduced in the same way as in supers, by bringing the grid returns of the controlled r-f tubes to the volume control. The easiest way to do this is by using a diode detector. The method was described in the November 21st issue, pages 6 and 7. Automatic volume control can be added to sets having regenerated audio, as there is no real relationship between the audio channel and the control.

\* \* \*

Mixer Coil

WHAT are the coil data for a mixing coil on 1.75-inch diameter tubing, using, say No. 28 enamel wire, for short-wave work, from 200 meters down, using two separate variable condensers of 0.00015 mfd.?—E. S.


The data are shown on the diagram, Fig. 977. The space between the plate coil and the oscillator grid winding is 1 7/8 inches. All windings are in the same direction. The tapped coil method is used. There may be a switch to slide the stator of each tuning condenser from one extreme to next tap and so on. This is the grid continuation method and avoids dead end effects and short circuited turns.

\* \* \*

Experiences With Compact Set

SOMETIME ago I made one of your sets, published in RADIO WORLD, known as the H. B. Compact. It has been a very satisfactory receiver indeed, and recently I made another one in which I made some little changes as follows: I inserted an output transformer (S-M 221) and use a Western Electric speaker. I also put in an r-f choke in the plate outlet from the detector tube, which seems to have made an improvement, although I do not know the proper value of the by-pass condenser. I am using a 0.0005 mfd. The r-f choke is General Radio Co. m-h, Type 379. However, what I wanted you to straighten me out on was this: The third tube or first audio stage, is a screen grid tube, 222. I find that the only tube that will work in this position is one particular make. I have tried other makes and they all produce a sort of motorboat growl, and that is the best I can get out of them, although the one tube works nicely. Why is this, when the other tubes are supposed to be of a higher quality, and the particular one I use does not test very high, I don't know. The next point is that I cannot make the set work with the three volt C battery attached. If I connect the two ends of the intended three volt C leads together it works very nicely, but attach them to a battery and the set will not work at all satisfactorily. In fact, it will scarcely give any results. In view of the fact that the set gives such satisfactory results otherwise, I would be very much interested to have you explain the reason of the above mentioned peculiarities.—H. E. G.

The radio frequency choke coil is all right as located, but to make the filtration complete you should use two condensers. The fixed capacity, 0.0005 mfd. that you have may be from plate to ground, but at the other end of the r-f choke put another condenser of equal or somewhat smaller capacity, from choke to ground. The motorboating or growl is due to the higher amplification of the other tubes that you use. In other words, the one that works best has a lower mu than the others. You can retain higher mu tubes in the circuit if you will put a large capacity across the B battery,

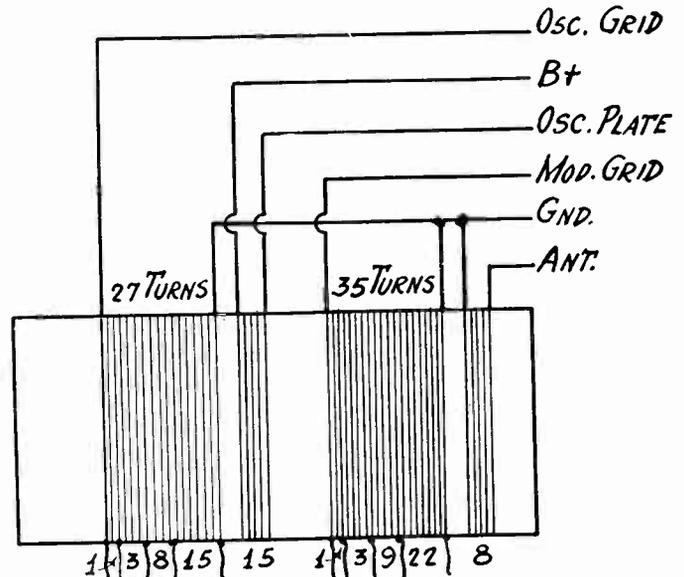

ALL WINDINGS IN THE SAME DIRECTION  
No 28 ENAMEL WIRE ON 1.75" DIAMETER

FIG. 977

Oscillator and modulator coils on 1.75 inch diameter tubing for 15-200 meter coverage, using 0.00015 mfd.

from maximum B plus to B minus. How large this condenser will have to be will depend on the frequency of motorboating, but less than 8 mfd. will have small effect. Absence of results when the C voltage is applied is due to incorrect bias for detection, but if you will connect a potentiometer across the C battery, with the grid return to the slider, you will find a detecting point. The potentiometer should have a switch attached, so as not to remain across the C battery when the set is not being operated, otherwise the battery life will be extremely short.

\* \* \*

B. P. Filter for Super

WILL it be necessary for me to use a band pass filter ahead of the modulator of a superheterodyne I intend to build? I have a three gang condenser.—S. F. F.

No, that isn't necessary. You may use 235 r-f, 224 negative bias modulator and 235 oscillator, if for broadcast band and a-c. The oscillator then may be a dynatron.

Join  
Radio World's

# University Club

And Get Free Question and Answer Service for the Coming 52 Weeks. This Service for University Subscribers Only. Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below or write on a separate sheet of paper, if preferred. Your name will be entered on our subscription and University Club lists by special number and you will be apprised of the number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your query. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

**NO OTHER PREMIUM GIVEN WITH THIS OFFER**

[In sending in your queries to the University Department please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City. Enclosed find \$6.00 for RADIO WORLD for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name .....

Street .....

City and State .....

### A THOUGHT FOR THE WEEK

**G**ERALDINE FARRAR, singer of many a delightful aria or simple song, in opera and on the concert stage, has forsaken the field of personal appearance before audiences. She is going to devote her time and talent to radio. Thus the world's newest and greatest unit of the amusement world is to have for its very own the lovely voice and fine artistry of a woman who has devoted her whole glamorous professional career to the best there is in music. Her friends are legion in all the countries in which she has given always the best she had to offer in musical culture and lovely womanhood.

# RADIO WORLD

The First and Only National Radio Weekly  
Tenth Year

Owned and published by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y. Roland Burke Hennessy, president and treasurer, 145 West 45th Street, New York, N. Y.; M. B. Hennessy, vice-president, 145 West 45th Street, New York, N. Y.; Herman Bernard, secretary, 145 West 45th Street, New York, N. Y. Roland Burke Hennessy, editor, Herman Bernard, managing editor and business manager; J. E. Anderson, technical editor.

## This Christmas

**C**HRISTMAS this year will find radio and radioists admittedly not in the best circumstances ever, and yet those who may be confronted with serious problems are none the less actuated by a desire to do all by the Christmas spirit that should be done. If anything, a little lull affecting the exuberance usually attending this season has the effect of making Christmas seem more serious, so that the gifts that will be made will be invested with an even greater measure of sincerity.

It has been notable that what provokes mirth has been most welcome, even if less effective than on more auspicious times. Magazines of silly humor recently started have developed large circulation. Comedy sketches and songs win unexpectedly big response. More persons read the newspaper comics. Jokes are most welcome. Even old ones will do, rather than the void of fun. The whole world probably needs humor as much now as it needs anything, for the tonic has its psychological effect, and we are told that much that faces us now is due to psychology.

Radio is playing its part in not only sending forth what are intended to be words and songs of good cheer, but is itself giving a striking lift to the acting profession that otherwise would be in a more serious plight. The microphone gives work to many artists, and pays quite a number of them enormously. Some gifted few are able, with vaudeville engagements and night club contracts, to make as much as \$10,000 to \$15,000 a week over a period of months, where radio alone contributes around \$5,000 to \$6,000 a week to the income. So something more tangible than psychology is helping along a few.

It must not be forgotten, too, that many

others in different callings are earning more than at any previous time in their lives, including persons associated with the manufacture and sale of inexpensive novelties, where there is small competition, or low-priced social commodities, where there is considerable competition, but the consumption is large.

Radio manufacturers have almost completely withdrawn from participation in sponsored broadcasting, and their answer is that they will return to the microphone so soon as business improves, in itself an admission that profit is at a low ebb in radio. However, those associated with the trade in any way will take heart in the fact that, with strictest economy, it has been possible to carry on without loss, or at a small setback, and that the public has showed, during the depression, that it keeps right on being radio-minded, and is buying in the radio field as strongly as the purse warrants. Manufacturers reduced their own costs, and the prices of their products, to meet the state of the public pocketbook, which was sane beyond praise. As it is there is considerable selling, though at little or no profit.

So the public should become aware that radio sets, parts and accessories are very low priced right now, and if the present low levels will not continue much longer, that is merely saying the return of profitable business is at hand. Prices are too low in nearly all lines. The man who produces the product does not have enough margin to permit him to do enough spending in fields that will eventually bring profitable business to you and me. There should be a wider margin all around.

With prices lower than they've ever been in radio, even though with some persons' pocketbooks very scantily attended, there will no doubt be considerable volume of Christmas gift shopping in the radio field. The economic status may change from time to time, but the human heart, if anything, grows more generous in an emergency, and it would be the sheerest affront to good nature for any one even to suggest a moratorium on Christmas giving. Those who are not riding high are at least not so low in spirit or purpose as to forego Christmas giving, and may many a deserving heart be warmed by a thoughtful radio gift.

## Continued in Our Next

**A** NEW method of advertising was instituted during the True Story Hour. Previously there had been a thrilling story enacted and completed before the microphone, supposedly an experience from real life, but at all hazards something that held the attention.

Then a prize contest was started, wherein manuscripts of stories told in plain words, were solicited—"just as you would speak"—and cash awards of high amounts were offered. Naturally, adding the expense of the contest to that of putting on the program on a chain required large returns. These must come from newsstand sales of the magazine, from increased advertising due to larger circulation, or other standard sources of revenue for a publishing company.

The use of the air to reveal the type of stories printed in the magazine on behalf of which broadcasts were made was not

only entirely proper, but constituted a contribution to radio, for the publishers of the magazine know the art of story presentation to a nicety.

After rendering such a good service to the radio listeners, and probably to themselves, the publishers suddenly changed front. The period of broadcasting was devoted to two stories. One was enacted and completed. The other was enacted up to a certain exasperating point, and the listener was recommended to the newsstands for copies of the magazine containing the next instalment. There was to be no appeal of curiosity over the air. One had to buy the magazine to find out what happened to whom.

As if from sheer malice of circumstances the story selected for the first of these experiments at incompleteness did not strike one as raising enough interest to warrant buying the magazine for the solution of the mystery of whether an unhappily married divorcee shot her husband's latest girl friend, but the shock felt at the abuse of the air as a mere come-on lure for magazine sale, instead of as a genuine builder of good will, was none the less keen. It is to be wondered that a chain, or any station, would encourage sending into persons' homes programs that referred listeners somewhere else for the completion of the story. One would expect that the National Broadcasting System (WEAF) would not stand for it, and probably won't after the public has made its feelings well known. Also a word might be said by the associated stations against the practice: KSD, WBEN, WCAE, WCSH, WENR, WGY, WLIT, WOC, WRC, WSAI, WTAM and WWJ, even those owned by the N.B.C! The publishers themselves will be the first to stop the practice if the public tells them so.

Listen in, if you can, to Mary and Bob on the True Story Hour, Monday, 10:00 to 10:45 P. M. Eastern Standard Time, and if the same method is repeated again, write to the station you heard, and give your frank opinion of the practice, one way or the other.

## KALEIDOSCOPE

Radio Station WELL, Battle Creek, Michigan, is ideal for reminding listeners to keep healthy. This admonishing station's symbol prophesies a renewed fad—longevity.

\* \* \*

Is there no way to preserve proper ether conditions for long distance reception? Radio set owners feel aggrieved when frustrated in capturing far-off programs. The ether is not an actor, nevertheless is temperamental.

\* \* \*

So much more comes out of the modulator than goes into the microphone that all radio singers become convinced they have powerful voices.—A. B.

\* \* \*

## RAY PERKINS ON NEW PROGRAM

Ray Perkins, jester, has retired as master of ceremonies of the Three Bakers hour on Sunday evening. A new contract calls for Perkins to broadcast for Jergens Hand Lotion at 6:30 p. m. on Tuesday and Saturday over WJZ and a chain instead of over WEAF on Wednesday and Friday at the same hour. As "The Prince of Pineapple," Perkins also broadcasts at 10 a. m. on Thursday and Friday.

**IMPORTANT NOTICE TO CANADIAN SUBSCRIBERS — RADIO WORLD will accept new subscriptions at the present rates of \$6 a year (52 issues); \$3 for six months; \$1.50 for three months; (net, without premium). Present Canadian subscribers may renew at these rates beyond expiration dates of their current subscriptions. Orders and remittance should be mailed not later than December 30, 1931. Subscription Dept., Radio World, 145 W. 45th St., New York, N. Y.**

# Station Sparks

By Alice Remsen

## The Song Thrush

(For Morton Downey, WABC, Daily  
Except Sunday, 7:45 P.M.)

Oh, hear the golden-throated thrush singing on the breeze!  
And harken to its liquid notes trembling through the trees!  
The tall trees, the green trees, the verdant trees of spring,  
The slender trees that listen to the thrush's caroling.

The thrush is not a lovely bird, feathers bright and gay,  
But oh, the lovely song it sings on a day in May,  
A May day, a gay day, a day so green and lush,  
A perfect day to listen to the singing of a thrush.

And in the early morning light, sounding clear and strong,  
A solitary lowly thrush sings a faultless song;  
And then again at eventide cascading o'er the dale,  
The thrush is only rivaled by the graceful nightingale.

Oh, hear the golden-throated thrush singing on the breeze!  
And harken to its liquid notes trembling through the trees!  
The tall trees, the green trees, the verdant trees of spring,  
The tall trees, the green trees, the verdant trees of spring,

—A. R.

\* \* \*  
Golden-Throated Morton Downey, the "Song Thrush" of the Camel program, is due back on the air this week, after a vacation which took him out to the Coast. The Roundtowners Quartet substituted for him on the program during his absence. Morton needed the rest. He has returned all ready for a strenuous season and his countless fans will welcome his reappearance, for the program did not seem the same without him.

\* \* \*  
That Sinister Character of Radio, "The Shadow," will return to the air in the early days of 1932, after an absence of six months. The identity of this mysterious person has never been discovered, even by the people working in the same studio, for he always wears a black gown, a hood and mask and in order to escape detection, he uses the freight elevator direct to the twenty-first floor of the Columbia building whenever he is due for a broadcast.

\* \* \*  
Have You Ever Caught the "Hunter and Hampton" daily broadcast over WAAT, Jersey City? The nuttiest program on the air, with no prepared continuity. Hampton's laugh is most infectious and he possesses a very quaint sense of humor.

\* \* \*  
Another Good Feature on WAAT is the Sunday "Stardust" program, featuring J. C. Ingram, New Jersey's most popular radio editor, interviewing radio stars. I heard him interview Raymond Knight of N. B. C., recently, and he did a very good job. I had the pleasure of appearing on his program two years ago. It was a very enjoyable experience. Among other artists brought to WAAT by J. C. Ingram at various times were Singin' Sam, Ray Perkins, The Two Trouters, Vaughn de Leath and the Street Singer.

\* \* \*  
Apologies Are Due to Howard Greene; in a recent issue I told you what lovely photographs Mr. Greene made for radio stars and then left the final "e" off his name and also put him "West" instead of "East." The right address is 24 East 58th St. Sorry for the mistake!

\* \* \*  
George Olsen and His Music is the latest program to be featured daily by WABC. This will be the most extensive night schedule ever allotted a remote ensemble. The orchestra will be heard over a nationwide network every evening

except Sunday at 11:45 p. m. Eastern Standard Time.

\* \* \*  
Joe Garrick, the Distinguished Star of talking pictures and musical comedy, was the guest artist on Footlight Echoes over WOR on November 29th. He sang three songs and proved to have an exceptionally beautiful high baritone voice, with perfect diction and fine dramatic restraint. By a strange coincidence we had as guest in the studio that evening the delightful little English dancer, Esme Gordon, who was born in the same town of Brighton, England, in the same year as Mr. Garrick. She also commenced her stage career the same year as he did, and in the same show, at the Queen's Theatre in London, with Lee White and Clay Smith's revue, "Come In."

Mr. Garrick is well known in this country for his good work in pictures, particularly in "The Sky Hawk," "Song of My Heart," "The Lottery Bride" and "Bad Company." Of course, like all moving picture stars, he has a beautiful home in California, and loves that state. He is married to a lovely brunette named Harriet, an American girl, who accompanies him everywhere. He is blond, of medium height, and has a charming smile. Likes sports of all kinds, particularly golfing, riding and swimming. Likes everything American but still wears English clothes and smokes Navy Cut cigarettes.

## SIDELIGHTS

EMERY DEUTSCH was the first to introduce gypsy music on the air... JACQUES RENARD was born in Kiev, Russia... BING CROSBY studied to be a lawyer... KATHRYN PARSONS may be a girl of yesterday on the air, but she is modern enough to personally make any and all repairs necessary upon her automobile... VINCENT LOPEZ once was a stenographer for the president of a milk company. His salary was eight dollars a week... JOE WHITE not only sings, but his broadcasts over the National Broad- also directs the string trio heard during his broadcasts over the N. B. C. . . . J. MAXWELL, N. B. C. tenor, was born in Maxwellton, Scotland... RAYMOND KNIGHT, N. B. C. humorist, stands six feet one and a half inches in height, and, like all humorists, he has a lugubrious look . . . RUSS COLUMBO is an athlete. plays handball, rides horseback, shoots accurate goals in basket-ball and swings

a wicket tennis racket... HARVEY FIRESTONE, JR., son of the rubber manufacturer, has a perfect radio speaking voice... PAUL DUMONT has shaved off that tricky little mustache... IRVING KAUFMAN is heard five times weekly over WABC—three times for Kolynos as "Salty Sam" and twice as "Charlie and Oscar"... FRANK PARKER has replaced tenor Leo O'Rourke in the Cavaliers Quartet. \* \* \*

## Biographical Brevities

About M. H. Aylesworth

Many people have asked me to tell them a few facts about the career of M. H. Aylesworth. Well, in the first place, everybody knows that he is president of the National Broadcasting Company. His full name is Merlin Hall Aylesworth. He was born in Cedar Rapids, Iowa, a son of the Rev. Barton O. Aylesworth. When he was one year old he was taken to Colorado and spent his childhood and youth in the Rocky Mountain region, which probably helped to develop his wide perspective, for early in life he displayed the great executive ability that was later to place him at the helm of the world's largest radio organization.

Fellow students at the University of Denver, Colorado Agricultural College, University of Colorado, University of Wisconsin and Columbia University, knew him as an organizer of glee clubs—his singing voice was considered good—and also as manager of athletic societies, director of debating societies, and a good student.

Upon completing his education—he holds an L.L.D. degree from the University of Denver—Mr. Aylesworth took up the practice of law in Fort Collins, Col., one of his first accounts being the collection of bad debts for the county medical society.

Later he went into politics and served as Republican chairman for Larimer County for some time. He abandoned his law practice in 1914 to become chairman of the Colorado Public Utilities Commission, a post he held until 1918. At that time he became head of the Utah Power and Light Company, with headquarters in Salt Lake City, where he remained until the National Electric Light Association lifted him into New York in 1919 to reorganize that organization.

In 1909 Mr. Aylesworth married Miss Blanche Parrett and the couple have two children, a son, Barton Jerome, and a daughter, Dorothy.

Mr. Aylesworth has been chief executive of the National Broadcasting Association since its inception, November 15th, 1926, coming to radio from the National Electric Light Association, where he held the position of Managing Director. Since he took the reins the N. B. C. has forged to the front ranks in the entire world of broadcasting, according to various foreign experts who have visited America in recent months.

A few months ago Mr. Aylesworth visited Europe to make an exhaustive study of broadcasting conditions there and to consider the possibility of an international exchange of programs.

He is a member of the Christian Church and belongs to several clubs and organizations, including Sigma, Chi (Wisconsin), the Lotus, and Engineers Clubs of New York, and the Pelham (N. Y.) Country Club.

Until a short time ago Mr. Aylesworth was an ardent tennis player and still swings his racquet upon occasion, but his chief outdoor interest at present is golf. His only other hobbies are his family, public service and radio—the latter two, he thinks, are synonymous.

He is a kindly gentleman, not given much to chatter; rather silent than otherwise; has a very observant eye; is unassuming and possessing the blessed faculty of minding his own business.

## SELF-SERVICE

One of the problems confronting service men is that next year is leap year and the tube replacement business is bound to be bad. This is because tube manufacturers have told the public to retube their sets at least once a year, and the public forgets the "at least" and goes to it once a year, if then. So with a shorter year ahead, the tube replacement market will fall off by 1/365, and as an offset, service men have decided to be more insistent on installation of new aerials. The P. M. business therefore will shift from unbranded tubes to polyglot aerials.

\* \* \*

Prices of parts are lower now than ever before, and money is scarcer, so service men are considering improving their economic status by going into other lines of business. A committee of the Profitless Service Men's Contamination has been appointed to discover if there is any other business besides radio, since once a fellow is in radio he gets quite the opposite idea.

\* \* \*

It is expected that the Japanese and Chinese markets will prove good outlets for manufacturers as soon as the military clashes become more serious. The advice about tube replacements being in order once a year does not apply to armies in the field, as various accidents attendant upon warfare makes more frequent replacement necessary. Not only tubes but portable transmitters and receivers can be sold to both armies, the only difficulty being in getting the credit department to O.K. the shipment. The demands may become "Sight Draft Bill of Lading."

\* \* \*

Remote control tuning is being featured by the Piffle Encouragement Company, Inc., for adaptation to homes not equipped with radio. The device fits nicely onto a neighbor's set, and permits the non-radio household to tune in and hear what programs it desires, leaving the real owner of the set to suffer in noise, instead of the usual silence.

\* \* \*

Short wave adapters and converters are becoming more numerous, and one of them that works has been manufactured by the National Company. This created such a furor that the company was accused of unethical conduct. The Worse Business Bureau has been notified. One of the newest adapters plugs into the detector socket and brings in police calls, if that is possible, without any other disturbance of the set or the user.

\* \* \*

Four-tube superheterodynes are promised for the coming market, but why only four tubes, when you can also get next to nothing on only three, has not yet been disclosed.

EVERYTHING ON THESE TWO PAGES IS ONLY A JOKE,  
BUT REMEMBER! ONLY THESE TWO PAGES!

INTERRUPTED CONTINUOUS WAVES  
EVERY DAY ——— EVERYWHERE

GOL. 2 Cu. Ft. No., Minus 2  
Whole No. 1/2  
December 12th, 1931  
(Entered as seventh rate matter  
while playing Office Boy despite  
Act 1, Scene 2, of the farce  
"Congress," at the Radio Play-  
house, New York, N. Y.)

RADIO WHIRL  
Nth YEAR


Two Lively Pages, Published  
once in a lifetime by Anybody  
Who Has the Nerve, from pub-  
lication office in editor's hat,  
Coatrack No. 2, Aisle 4, Suite  
1214, at 145 West 45th Street,  
New York, N. Y., next door to  
the Lyceum Theatre.

# Infinite Element Tube
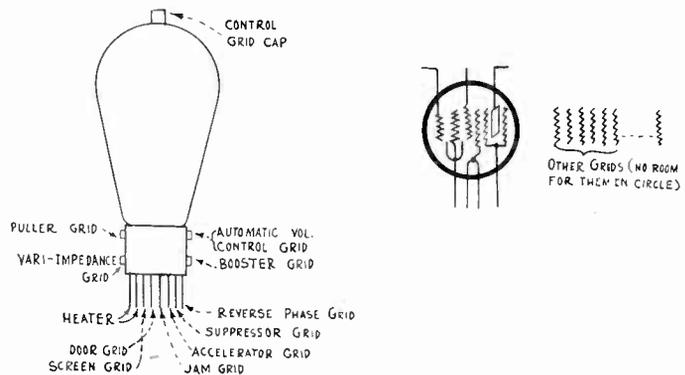
## Nth Screen in Vari-mu Valve—Price Reduced 40% Before Tube's Release

By Daniel Dopster

A pictorial view of the new nth-ode is shown at left, the various grids being illustrated as numerously as possible, with functions stated. At right is a schematic diagram of the tube, showing nearly all the grids, but it was impossible to get even half of them in the circle.



**B**USINESS being slow in tube factories, they have a lot of surplus grids around the plant, so a new tube has been brought out. It is called an nth-ode, not for poetic reasons, but because it has n-elements. It is the forerunner of the plus-infinity tube, which is now being perfected in the laboratories, and which will have n plus 1 elements.

The present new tube is the first nth-ode to be put on the world market, and requires special circuit design, as well as a socket that looks like a circular collander. Physical or mechanical limitations prevent the actual use of all the electrodes, because while engineers can dream up infinite purposes and variations, nature provides tangible and practical means of utilizing only some of them; that is, empirically one can not even approximate infinity, but let it go at that.

### New Tube Has Low Number

The new tube, known as the 2946896342987, can not be used as replacement for any other tube, but is a very special purpose valve. Besides the familiar heater, control grid, cathode and plate there are other grids that serve new and startling purposes.

The result is a stable tube that has a working mu factor of 10,000. One of the reasons why this high mu is attained is that the nth grid, which can not be used for want of practical means of attaining the value n, automatically brings the tube in resonance with a tuned circuit. Hence only one condenser is needed for tuning, and one coil, using the n minus 1 tube, 2946896342986. The nth-ode will be pulled by its resonating grid into the same frequency as the tuned tube. This is known as the puller grid. It makes a very effective display in radio stores.

Another remarkable feature of the nth-ode is that it has an automatic volume control grid, thus dispensing with another tube.

This grid is so placed, between the vari-impedance grid and the puller grid, that any rise in amplitude shows up as a corresponding decline in amplitude, and affects the vari-impedance grid in such manner that the output is held constant despite the input fluctuations.

In fact, the tube is so remarkable that even when there is no input there is a large output. This violates the law of conservation of energy, but the engineers who designed this

tube are scofflaws. An amendment to the Radio Law of 1927 is to be sought to make the use of this tube legal for amateur and experimental use, especially as the functioning of the tube is more completely experimental than anything hitherto developed in radio, which is saying a lot.

Blueprints of circuits using this tube will have to be built by underpinning and construction companies, in layers. They really will not be prints, but models. The tiers will have the set-back construction required by the building zone laws of most large cities.

The heater voltage is 2.5 volts, a-c or d-c, and the heater current is 0.05 ampere. Thus power conservation is practiced in these times when the electric companies need all the business they can get.

The plate voltage is 200 volts and the amplification bias is 9.99 volts negative. Only the bias, not the results, are negative, the engineers report on the basis of the Schick test. The tube can not be used as a detector, so it has a non-detecting characteristic and can not detect the difference in functions of its multi grids.

It will be noted that the grids are numerous, but there is only one plate. After the n-plus-1-ode is brought out there will be, it is expected, an n-plus-20 ode, in which nineteen extra plates will be used, as there is a surplus of plates around factories, too.

### Price Fixed and Reduced

The list of the nth-ode was given a pre-release price of \$3.50, but the price was reduced 40 per cent. before the tube was brought out, and it is expected that as soon as quantity production begins the list price will be reduced below the cost of manufacture, the tube makers figuring that by selling an enormous quantity of tubes they can finally make income meet expenses.

The usual trade discounts will be allowed, and dealers ordering 100 tubes will get five tubes free, the discount applying to the free tubes as well, so that the manufacturer will have to pay the jobbers and retailers for taking the five extra tubes. This is a move to accelerate business.

A counting machine is sold to dealers by the tube manufacturers at cost, less express charges, so that customers can tell the number of grids without having to get out pencil, paper and a book of Napier's logarithms.

## NEW "MIKE" IS SNOOPER

A sensitive microphone that has an opening front and back, like a double V evening dress, has been developed by engineers of the Impulse Registration Corporation. Also, the microphone can be focused on certain spots.

One of the outstanding advantages of this microphone is that, as to sound, it behaves as a searchlight does to light, except that the focusing is inverse, that is, sharper, the greater the distance.

The principal use to which the microphone will be put will be at large gatherings, like football, baseball, horse show, opera and other events, so that during periods of lull in the main event the microphone can be focused on the confidential conversation of celebrities, and the world will thus obtain their side comment on persons and events.

For instance, what does Mrs. Abernathy Dowager think of Mrs. Swell Mansion? The focusing microphone may pick up Mrs. Dowager's derogatory comments on Mrs. Mansion's table linen or evening dress (the latter was made from the former), or any other comment.

## Hoover Idea Is Rejected

Washington.

A permit to use radio frequency transmission, from a small modulated oscillator, for pointless to pointless service, was issued by the Federal Radio Commission to the N. G. Hunter Corporation, which seeks to develop mine areas in the Southwest.

The corporation has a radio adaptation of the divining rod, and by radio means not only can tell whether there is water underneath, but even if there is something stronger, besides being able to disclose the presence of mineral ores and oils.

The Commission gave long and due consideration to the application, nevertheless granted the request. It is said that President Hoover, who, it will be remembered, is after all a mining engineer, was greatly interested in the application, to the extent of expressing doubt as to the practicability of the device.

The Commission overruled the President with no less compunction than it did Examiner Pratt in another case.

It was said at the Commission's office that the Commission has a mind of its own. A search was started instantly.

## SECOND SIGHT AIDS BOARD

Washington.

The Federal Radio Commission has decided to require all stations to file daily reports, with full tabulated matter, stating what percentage of the programs is devoted to lotteries, fortune telling and other quack undertakings. It is understood the Commission has no direct power to rid the air of these, as a matter of censorial activity, so it is believed the statute has been construed to mean the Commission should give all possible assistance to wandering gypsies, Nabobs, second-sighters and miscellaneous other easy-money grabbers, provided not listed in the phone book.

One reason put forth for the attitude toward the necromancing ilk is that the Commission is at a loss to solve some of its most serious problems, and that one of the members got a big lift from a fortune teller, who solved two problems very nicely. This has engendered a deep respect for fortune tellers, although the prophesied dark man coming with a bundle turned out to be a colored letter carrier arriving with a bag of complaint mail.

## ZVX Ousted but Increases Power

Washington.

After a hearing before Examiner Ellis Pratt, the Federal Radio Commission ordered ZVX off the air, thus reversing the examiner's recommendation.

The ground was that the station did not carry any advertising programs, and therefore was not emitting blurbs of or so-called "credits" of a fulminating and goading nature. This was held to constitute failure to comply with the legal requirement of serving public interest, convenience and necessity.

The station, as soon as it received the illustrated post card announcing it had been ousted, increased its power to 50,000 watts.

## Worthless Accuracy

Statistics compiled by the Department of Commerce show that there are not as many sets in use as there should be, and that only 15,000,000 families have receivers. The total was arrived at by the simple process of counting noses during the 1930 census, and therefore is not as reliable as the estimates given out by the Department on other subjects. Statistics lose their significance when they represent actual values.

## LATE NEWS

A German by the name of Heinrich Hertz, pronounced Hairtz, with a decided roll of the r, has been monkeying around with some apparatus that he calls electrical, and it has been possible, for him, says he, to generate what he calls radio waves, and receive them at a short distance, say, across a room. The waves are of different frequencies, some of them very high. Hertz, who is a professor at a university there, gave a demonstration before domestic and imported scientific celebrities. After he had sent and received he was congratulated by the German scientists, all of them his own students, but the foreign scientists said: "After having seen the thing done, we come to the conclusion that the pretended performance is impossible." Hertz then refrained from passing pretzels among the foreigners.

\* \* \*

J. C. Maxwell, a British mathematician, has doped out some formulas that he says proves that radio waves are continuous and of the nature of light waves, differing only in frequency. His word for them is undulating. This is contrary to the accepted theory, as real scientists believe that Mr. Maxwell pulled a boner in some of his computations, but they can't say just where, because Maxwell's formulas are so complicated, and his sign language so original, that others cannot make head or tail of them. In fact, Maxwell, at a public meeting, could not read his own mathematical notes.

The oil in the kerosene lamp had given out.

\* \* \*

Michael Faraday has been doing some experimenting in a London garret, making most progress by ignoring the advice of a learned scientist for whom he had been working, and with whom he had travelled in Italy as sort of secretary. While on the great scientist's payroll the enterprising valet had to be polite. He drew the line, however, at polishing his master's shoes, as he said, that did not come within the civil service requirements of an assistant scientist. While protesting against shoe shining, and thus arousing the displeasure of his master's wife, Faraday disclosed confidentially that he had discovered a means of transferring current without wires, using what he calls electromagnetic induction. As the inductive school of reasoning is not in the ascendancy in England, Faraday has had trouble with his landlord about rent payments, and the theory of electromagnetic induction did not impress the unpaid landlord at all. Faraday said if he does not get a better break at home he'll go to America, as he has a season pass for the New York Aquarium.

## LATER NEWS

Guglielmo Marconi, an Italian as his name indicates, but who was educated in England, has succeeded in flashing the letter S across the Atlantic, explaining that the letter S stands for Science, and that the letter Z, being zig-zag, could not make the grade, due to the straight

(More of these serious discussions, alas, on next page)

path of the wave. His demonstration is regarded as a boyish prank of no useful significance.

\* \* \*

Oliver Lodge has a new idea. He says that as different radio frequencies can be generated some means must be used for receiving different frequencies. So he has two coils and changes the relationship of one to the other to accomplish what he calls tuning. As Lodge's dues in the Learned Scientific Society are paid up to date his demonstration and explanation have been given official approval, and he is on the road to knighthood.

\* \* \*

John Ambrose Fleming, being dissatisfied with devices called rectifiers, and wanting something more sensitive and more stable to afford the advantage of listening to radio transmissions, which are said to be utterly practical, has taken a piece of glass, removed the air with an air-remover, leaving inside two elements, one called the negative anode or plate, the other the cathode or positive. This device he calls a rectifier because it eliminates radio frequency and leaves something you can hear. Now that he is hearing things he may soon be expected to be seeing things. This business of seeing will be called television.

\* \* \*

An American named Lee De Forest has produced what he calls an audion, and which not only can be used as a detector, as was the case with Fleming's device, but can be used to magnify signals. This magnification takes place because the signal put into the audio comes out

larger. Besides, he can make the tube generate radio frequencies, which is regarded as important. This generation is all due to oscillation. The time between one generation and another is known as a cycle instead of as three score and ten.

## LATEST NEWS

What is called a radio broadcasting station and is known by letters only, instead of by name, has sent out Harding election returns by radio. The results were spoken into a disc called a microphone and the pulses amplified and sent out from one of De Forest's oscillating tubes.

The station, or sending plant, is known as KDKA, and is owned and operated by the Westinghouse Electric and Manufacturing Co. People who owned receivers and earphones could hear the result. In this way Harding became aware of his election before the results were counted.

\* \* \*

John McCormack and Geraldine Farrar were heard before the microphone of WEA, New York City, on New Year's Night. They sang well, as usual, and their voices came in excellently on broadcast receivers. Such sets as were equipped with audio frequency amplifier and loudspeaker brought in the fine music with volume enough to fill an empty room.

\* \* \*

The Television Thrilling Corp. has erected a station to send television around the world and is making receivers that get Mars and Hades.

# Station Caps Optician Discovers New Facts About Ultras

By Bernice Warbler

## GOOD COOKING

(Agnes Catsaunt, QWMZ household adviser, recipe hound; Sunday and holidays, 2 p.m.)

HOW telling is a pie that's aptly baked,  
Compared to stomachs that so sorely ached;  
What joy ecstatic swells the human breast,  
When mother's matchless pies have gone to rest.  
And, oh, the lusty purpose of the hatch  
Down which we crowd thrice daily quite a batch  
Of what we miscall food, and oh, the look  
Of joy on greeting one who is a cook!  
So swell with pride instead of stomach pain  
To greet the gorgeous oven-baked refrain,  
The sizzling roast, the cake or custard pie  
That thrills the spirit where the innards lie!

—B. W.

Oscar Impresario has been shifted from playing the breakfast music in the Pink Room of the Dewrop-Astoria, to playing the luncheon music in the Heliotrope Room. As only the Pink Room music is being broadcast, this leaves the maestro off the air temporarily. He is being congratulated by enemies on account of his advancement.

\* \* \*

"Nobody's Business," a playlet in one-half act, recently was put on by the Nationwide Broadcasting Company. In it played Helen Tippy, the wide-eyed girl of the Frozen North, who made such a hit twenty-seven years ago on the Pantages circuit, playing five a day as a middle aged lady. Helen has a voice that possesses the finest cracks imaginable, and the playlet was halted when half over only because of trouble in the control room. The studio director was in that room at the time.

\* \* \*

Historical episodes from the early American era are to be presented beginning Friday by the Country Service Company. The first episode will deal with the Neanderthal ascension of the present Rocky Mountains. The part of the dinosaur will be taken by Herman Stuffem, former taxi driver.

\* \* \*

Cissie Simplelocks, juvenile of the Down Home Air Opera Company, who sang "Manon" with great success, is a lover of Easter lilies. She married the first man who sent her a bunch, but later found out that the messenger had misdelivered the nosey spran. She is now his leading woman, and how she drives him. Her French is regarded as the most perfect specimen ever to be bred in an American high school. When she sings "Connais tu le Pays" what for the fine French and the adherence to tune, she perfects an artful doubling, also making it sound like "Coming Through the Rye," tune, words and all.

\* \* \*

Several brand new numbers are about to go on the air and some have very attractive tunes and

RECENTLY there has been considerable interest in the ultra frequencies, those that enjoy the effects of light waves, and are obstructed by buildings and other objects, and follow the earth's curvature, travelling as far as sight, or to the horizon, as you prefer.

Dr. Spinwell Truthless, noted optician, optometrist and eyeglass doctor, who has made a special study of the possibilities of the ultra frequencies improving the attendance in his at his glassware store, said:

"After painstaking efforts, and the use of a high-powered microscope, I have found that not only is the behavior of the ultra frequencies like that of light, but also that these waves, are, in a sense, true light, and the only reason we listen to the transmissions instead of seeing them is lack of sufficiently penetrating vision. I have developed a new lens that so improves the sight that the ultra-waves, like small boys, should be seen and not heard. I call it the Small Boy Lens and recommend it to radio engineers in particular, as judging by what I have observed, they do not see any too well."

Others have found interesting facts concerning the ultra frequencies. Jean Secondfiddle, the French-Canadian, assistant director of the Flop Laboratories, has invented an escutcheon that goes on any broadcast set and is used as an adapter for ultra frequencies. Thus, by putting this escutcheon on the broadcast set, and walking to or from the set, body capacity is made to change the frequency. It is the Theremin principle applied to an oscillating escutcheon.

words. One of them is "Tea for Two," sponsored by the Great Pacific and Mediterranean Tea Company, with special dispensation from Providence and the copyright owners. Another is "A Kiss in the Dark," which has been open to some criticism from the Censurious Society, due to the frequent matrimonial consequences of dark kissing.

\* \* \*

A most delicious luncheon was served the other evening at a radio star party by Uncle Donald Wan, who delights the hearts of the kiddies and is better known to them than their own daddies, what with the times driving daddies out nights to forget their troubles. When daddies return home from the office for supper they find it hard to get a greeting from their young sons and daughters, because Uncle Donald engrosses the children's attention. Uncle Donald really does not ride to and from the studio in an airplane but uses an automobile. He has a Lincoln. He gave his wife the Packard that needed new rubber.

## PERSONALITIES

EDITH ACRIMONY has blimp hair. After washing, it goes up and stays up and on occasion circumnavigates the world. . . . ROSS TURNOVER learned to croon before crooning was known, as his mother was a crooner before him. Only they called it crowning at that time and Ross became an orphan at an early age. . . . Sugar sandwich biscuits are manufactured by the father of JASMINE DRAGON-EILA. The charming daughter gives large quantities of these biscuits to the poor, who call her Marie Antoinette.

## COLLIDE-OSCOPE

Short waves, being very low waves as used in radio, have encircled the globe. Amateurs listen regularly to stations all over the world, receiving code. It is expected that voice soon will be used, as amateurs who know enough code to pass the examination sometimes get rusty on code, but can follow the English language all right, even as spoken in foreign lands.

\* \* \*

Alternating current tubes are announced, so that now it will be possible to operate sets without batteries or battery eliminators.

## See Things On Trip To Europe

Just back from a trip to Europe, made on behalf of his firm, all expenses paid, Ignatz Forsooth, consulting engineer of the Short and Long Selling Company, reports that Europe is making great advances in television.

He said that he attended a show in Berlin and that, to the best of his information and belief, it was possible actually to see the pictures. The neon lamp was used by some, the Kerr cell by others, mechanical scanning by most, a cathode tube by Von Ardenne, while all the men wore evening clothes, and the women had on slippers and fine dresses.

Speaking of the comparative quality of the television in Berlin, Mr. Forsooth said that the steins are a little shorter now, due to the reparations situa-

tion, but that the contents were just as enjoyable as during his visit two years previous, in fact, more so, since then he was strictly on his own, while this time the firm was paying all.

One of the scanning discs, that develops greatest speed, or was it the motor, was known as Sparkling Mozelle, and if anyone had ever seen a finer picture, it must have been a miracle, he said.

Besides, wherever he went, he received nothing but information on television, excepting of course a few concerns that had some worthwhile developments, and as to these there was only guarded information.

"Nothing to say," revealed these manufacturers, and Mr. Forsooth sailed for home, all expenses paid.

## Here, There and Nowhere

Bargain prices prevail on midget sets, and on large console sets, as well as consolettes. It is always the same set, in one or another picked-up cabinet, and there is a bonus (P.M., for pin money) to every store salesman who palms off one of these in preference to a standard receiver on which the profit is greater.

\* \* \*

The standard color designation code for resistors has caused considerable comment, as by having a little book in his pocket a service man can not mistake the value required for a replacement resistor. This takes much of the fun out of the work, since the tubes stay East and the set plays.

\* \* \*

After patient years of experimental improvement, the Hammarlund Manufacturing Company has brought out an all-wave superheterodyne. When a demonstration was given recently, a European station was tuned in loudly and clearly, and one of the prospects ordered a set without discount and paid for it in advance, thus setting a precedent that unnerved even Lewis Winner, the chin of the Hammarlund unit.

\* \* \*

The ability of radio waves to travel long distances has been established, as persons who listened to recent broadcasts at a

distance of 1,000 miles or more were asked to report by mail to stations, and forty-six letters were received by six stations. This proves the wide range and extensive interest. It is expected that within ten years hundreds of radio sets will be in use.

\* \* \*

Television isn't here commercially yet, so when Secretary Stimson takes a walk, or does anything equally vital, there is no camera to record the tremendous episode. For this he should be thankful, for his coat collar always rides far too high on his neck to make television safe for tailored democracy.

\* \* \*

If that man who has not written to the station complaining of overdose of advertising talks will please communicate with the Secretary of Incredibility, he will not be suitably rewarded.

\* \* \*

Over in China they have plenty of radio reception to keep their minds off the consequences of League of Nations assistance.

\* \* \*

Another sort of Gandhi, more full attired, and bewhiskered besides, is Dino Grandi, Italian Premier, recent visitor here, who was said to speak English fluently, Hoover needing no interpreter. Then Grandi broadcast in English and we needed one.

## AIR TO LINK 5 CONTINENTS IN MARCONI HONOR

Five continents will be linked in a radio roll call around the world arranged by the National Broadcasting Company to celebrate Marconi Day, December 12, thirtieth anniversary of the first successful attempt to span the Atlantic by wireless.

M. H. Aylesworth, president of N.C., characterized the celebration as the biggest international broadcast ever undertaken. Australia, Japan, Brazil, England, Argentina, France, Germany, Italy, Poland, Belgium, Holland, the Philippines, Hawaii, Canada, Hungary and the United States will participate in the program, hooked in a single network, the largest ever set up.

### Marconi to Speak

Guglielmo Marconi will speak over the world-wide span on this anniversary of the most important day of his life—a day on which was born a device that has saved thousands of lives, and now unites the world in a net of instantaneous communications.

On December 12, 1901, Marconi sat in Cabot Tower in St. John's, Newfoundland, and heard three faint clicks, the telegraphic code for the letter S, which had been originated a fraction of a second before by contacts of a key in Marconi's specially constructed station at Poldhu, South Cornwall, England.

Those three clicks, in a longer combination (. . . — — — . . .) form the SOS. They have brought rescuers to passengers and crews of innumerable ships in all the seen seas. That symbol still halts broadcasting everywhere with nits reach, so the the commerce and entertainment of the world may not interfere with the urgency of saving endangered lives.

### Other Scientists to Be Heard

The anniversary program will go on the air sometime during the afternoon of December 12. The exact hour has not been set, as a multitude of technical details must be arranged in order to tie together so many far-flung stations in a smoothly working unit. N.B.C. engineers and technical experts have been working for weeks in cooperation with officials of the various countries to perfect the network so it may uncton without a flaw.

Scientists and other personages of the cooperating nations will speak briefly during the program in honor of Marconi, and music will be heard from many points around the world.

## International Resistance Elects New Officers

The directors of the International Resistance Company have announced their reorganization plans necessitated by the death of their president, Francis R. Ehle, in a recent airplane crash.

Ernest Searing, former vice-president and director of the company, succeeds Mr. Ehle as president. William G. Porter has been elected vice-president and a director. Ruth N. Shires, formerly secretary of the company, has been elected secretary and treasurer.

## 45,000 Record for N. B. C. Missives

The daily incoming correspondence from radio listeners struck a new high at the National Broadcasting Company recently when more than 35,000 letters and telegrams were delivered to the company's headquarters in New York.

In addition some 10,000 letters, not included in this total, were opened and read at N.B.C. branch offices in Chicago and San Francisco.

The grand total for the day represents more pieces of mail than were received in a month when the N.B.C. was first organized five years ago, and better than half the total amount received during the entire year of 1923, the first year of chain broadcasting through station WEAF.

Many fans in New York delivered or sent their communications by hand, and the day's communications included nearly a thousand telegrams, as well as special delivery and air mail letters.

## WHY WILKINS CAME TO TOP

W2XAF, Schenectady, N. Y., demonstrated that it is possible for short wave radio signals to bring a submerged submarine to the surface. This unusual demonstration recently was reported to the engineers of WGY's short wave station by Ray Meyers, radio officer of Sir Hubert Wilkins' submarine, Nautilus.

According to Mr. Meyers, W2XAF was the only short wave station he could receive dependably while in the Arctic. The Nautilus, at its Arctic base, was made ready for under water and ice exploration by dismantling the transmitter antenna. With this antenna out of commission it was impossible for the submarine commander to communicate with the outside world, but it was possible, through the receiver, to get the signals of W2XAF during the time the Schenectady transmitter was on the air.

The Nautilus had been under for a long time. No word had been received back in the United States and as the silence continued, anxiety was felt for the safety of the crew. When ships at sea and land stations failed to get response, the news of this failure was carried by the newspapers. This news item was included in news service read over WGY and carried by W2XAF. Mr. Meyers heard the story which reported that the entire world was concerned over the silence. When Sir Hubert learned that relief expeditions were actually being planned to locate him he decided to come to the surface. The transmitter antenna was replaced an dthe news of the craft's safety was sent out.

## Grosswendt Named Pacent Plant Manager

The appointment of Carl Grosswendt as production manager of the Pacent Electric Co., Inc., is announced by Louis G. Pacent, president of the firm. Mr. Grosswendt assumed his new duties at the Pacent plant at 91 Seventh Avenue, New York.

Trained as a mechanical engineer, Mr. Grosswendt has specialized in scientific factory management in both Europe and the United States. His radio experience dates back to 1921, when he established a radio parts factory in Berlin. He has been connected with several large American radio firms.

## WORK IS BEGUN FOR N. Y. OPERA BROADCASTING

Metropolitan Opera on the air came nearer recently when National Broadcasting Company engineers began drafting plans for microphone locations and a control and observation booth in one of the upper tiers, to be submitted to Edward Ziegler, assistant general manager for the Metropolitan Opera Company, New York.

Installation and construction work will commence as soon as the plans are approved by the opera company, and within two weeks it is expected that actual acoustical tests will be under way.

As soon as possible thereafter portions of regular performances of the nation's leading opera company will be made available to listeners throughout the United States.

With the realization that a great part of the country cannot hear opera because it is available only in the largest cities, the National Broadcasting Company is bringing opera directly from the stage of the Metropolitan to the homes of music lovers.

### Deems Taylor to Be Narrator

Although it will be several weeks before the necessary arrangements for broadcasting can be completed, the services of Deems Taylor, music critic, whose own compositions have been heard from the Metropolitan stage, have already been obtained as narrator for the series of operatic programs which will follow Assistant General Manager Ziegler's approval of the N.B.C. plans.

According to these plans, no temporary or portable equipment will go into the opera house. Control booth, wires and microphones will be permanent, but inconspicuous. Technical facilities will be of the finest, but there will be nothing, save the control and observation booth in an out-of-the-way spot, to indicate to opera-goers that the performance is being broadcast to a far larger audience.

In the construction of this booth and the installation of equipment every effort will be made to share boxholders inconvenience or annoyance. The booth, from which the operating engineer and the production man coordinate the visual and auditory control of the broadcast, will be constructed outside the building and carried in section by section, in order that building operations will not conflict with scheduled performances.

### Announcer in Chamber

In addition to the control room, this structure will also contain a special sound-proof chamber, with a full view of the stage, from which Taylor and the announcer can speak to the radio audience without disturbing those seated in the vicinity.

Erection of the booth will be further complicated by the necessity for constructing it of fire-proof as well as sound-proof material. Ordinary soundproofing employs wood, but in order to eliminate every possible fire hazard in the opera house the booth will be built of steel. his, the engineers point out, will make the equally necessary sound-proofing more difficult, thereby delaying the time when actual broadcasts may begin.

Once completed, the entire control room structure will be painted old rose to harmonize with the color scheme at the Metropolitan. Plans for the installation of the microphones have not been completed.

## ULTRA WAVES' RANGE PUT AT FIFTY MILES

Tests made by the Shortwave and Television Corporation in Boston lead the corporation to state that the projection of signals from great heights on ultra short waves brings about good television results.

Marshall P. Wilder, member of the research staff of the organization, analyzes the experiments conducted by WIXZ which contributed much new data on ultra-frequency television.

"The 100-watt transmitter of WIXZ is the first to be modulated with television and voice and broadcasts regularly on 6.7 to 6.97 meters," he reports. "The character of these waves makes them almost ideal for television purposes.

"Absence of fading, negligible (if not entirely eliminated) background noises, 'plenty of room to move around in' for the emission of wide bands for spreading good pictures, are among the favorable aspects.

### Range About 50 Miles

"The main drawback, short range, is more than offset by the quality of received signals—and it must be borne in mind that few listeners in the eastern metropolitan districts regularly receive broadcasting from stations farther away than fifty miles. The quality of locals is undisputed and will be preferred to a distant station which have a hissing sound, perhaps a slight amount of crosstalk, or even a small amount of fading, no matter how good the program.

"Transmission on 43,000 to 45,000 kilocycles has approximately the same range, with no dead spots, provided the antenna is high enough at the station, at least 750 feet above the surrounding country, to attain this coverage.

"New York has a group of buildings suitable for such purpose and there are tall structures in other cities adaptable for television stations. With one-kilowatt power the high-up transmitter will be most effective. Shadows cast by large buildings do not seem to be such an obstacle; at least, I have not noticed any interference when receiving signals from the low powered station in and about Boston, although the present antenna is not advantageously placed. WIXZ's antenna is a full wave current fed outfit with tuned transmission line.

### Used Super-regenerator

"Voice reception was carried on through the use of a small super-regenerative receiver placed inside an automobile, with an aerial three feet long. Signals were strong with no fading over an irregular course from Boston to Newton Center, a distance of seven miles. At no time has the ignition system of the car been an annoyance. This form of interference, as well as that created by X-ray machines, power lines, etc., is negative. From Newton Center to Wellesley the signals sometimes dropped, fading behind hills and in valleys; sometimes a foot advance brought them in at full strength. This is understandable because according to the accepted formula our signals should be effective at only eight miles based on the fact that our antenna is only about 50 feet above ground.

### Results on Meters

"Yet there is evidence that these high frequencies sometimes cover great distances. A Hoyt Taylor, of the Naval

## "Goldbergs'" Party Gay Despite All

The second anniversary of "The Goldbergs" was celebrated recently. It was a happy occasion in the career of Gertrude Berg, author and principal actress of the National Broadcasting Company series.

"The Goldbergs" held open house in a studio at 711 Fifth Avenue, New York, home of the N. B. C., throughout the late afternoon and early evening.

For "Jake Goldberg," whose character in the sketch as that of the wife of Mollie Goldberg (played by Mrs. Berg), shook hands with the real life husband, Mr. Berg. The fictional husband of Mollie Goldberg and the real husband of Gertrude Berg chatted pleasantly together as they nibbled cakes and sipped coffee, and there never was greater serenity and less awkwardness or discomfort. They agreed they had, in their respective spheres, one professional, the other domestic, the finest helpmate in the world. Mrs. Berg beamed domestically on the one and professionally on the other—you can imagine which—and decided that they both meant a great deal to her.

## HOW CELEBRITIES WRITE NAMES

Three weeks after N.B.C. placed a guest register in its Fifth Avenue studios the first page was filled with signatures famous in the fields of adventure and music.

By coincidence, the first half of the opening page included such famous names as A. Whitten Brown, first to fly the Atlantic with John Alcock; Capt. Eddie Rickenbacker, war ace; Colonel Charles A. Lindbergh, and Roy Chapman Andrews, exploring scientist.

Below them were registered famous singers and composers, including Geraldine Farrar, Mary Garden, John Philip Sousa, Henry Hadley and Rudolf Friml.

The smallest signature was that of the bandmaster, who wrote in a thin hand. "John Phil. Sousa." Lindbergh signed himself "C. A. Lindbergh" in simple style, with a slight tilt to the right. Explorer Andrews stretched his name in a sweep almost across the page. The boldest signature was written by Miss Garden, beginning with a giant capital "M."

Miss Farrar signed with sharp, cryptic capital letters tapering off into almost illegible endings. Friml had a dashing flourish with lines that whipped across his name in the 1890 style.

The book is kept in the office of J. de Jara Almonte, night executive, who is host to all notables participating in or attending broadcasts.

Research Laboratories, told me that he had maintained 24-hour service from Washington to Panama using only 7 meters for six months. That was two years ago. Conditions are different and hazily comprehended. Dr. Taylor described successful communications on waves of 4.5 meters between Washington and California in only two out of two this cannot be done now, for reasons only hundred trials. The border for reflected waves is reached at about 8.5 meters.

"At Arlington, Mass., ten miles from WING, reception is excellent on the hills."

## CHINESE KEPT POSTED BY AIR ON MANCHURIA

Chinese are kept posted by radio about developments in Manchuria, Henry K. Chang, Consul General in New York, said in a recent broadcast over WOR, Newark, N. J. He also spoke, in substance, as follows:

The Chinese Signal Corps has acquired modern vacuum tube transmitters and receivers. The men are well trained in military communication practice both for point-to-point service and mobile operation in the field. These portable stations can be erected in a few minutes and put the troops in touch with headquarters at distances upward to a thousand miles. Power is supplied either by hand-driven or engine-driven generators.

### Trained in Three Languages

The Chinese Signal Corps men are put through a long period of training in government schools, both in engineering and telegraphy, being able to maintain and repair equipment and many being able to copy messages in English, Russian and Japanese.

Broadcasting stations in China are located at Shanghai, Peking, Mukden, Canton, Hangchow, Harbin, Nanking, and Tientsin, operating on wavelengths between 30 and 500 meters.

There are also more than twenty modern short-wave stations, some of which are used for broadcasting and others for telegraph purposes.

These are located at Shanghai, Nanking, Chungking, Wuhu, Ichang, Hankow, Tientsin, Pieping, Swatow, Canton, Taian and other points. Some of this equipment has been supplied by the RCA and some by the International Telegraph and Telephone Company.

### Hear Japanese Stations

The listener in China today finds a thrill in every turn of the dial, at one setting finding something coming out of Russia, at another from Japan, and again from the zone of hostilities. Some of the Japanese stations heard in China are JEZB, Tokyo, or 20 meters; JFAV, on 39.50 meters, and JHBB on 37.50 meters. Moscow is heard regularly on short waves.

An English program is broadcast daily (two p. m., Eastern Standard Time) from the 20 kilowatt short-wave station at Shanghai, XEL, on a wavelength of 37.64 meters.

## Asking Too Much, or Who Could Comply?

"I don't like the person who plays Clem in your sketch 'Jimmy and Dad.' Why don't you fire him and get somebody else?" So wrote a listener to Pat Barnes whose one-man radio comic strips are heard daily over an NBC-WJZ network. Pat replied he couldn't discharge Clem without discharging himself, for Pat takes all the parts in his sketches.

## Eight Tube Super

Further discussion of the eight tube superheterodyne treated in an instalment last week will be published next week, December 19th.

Another article will deal with voltage dividers.

# CONTROL KEEPS ULTRA WAVE ON ITS FREQUENCY

What constitutes the first practical employment of ultra-short radio waves, which for many years have remained one of the curiosities of radiotelegraph experimental work, has been accomplished with the establishment of the new inter-island radio telephone system of Hawaii.

The development is regarded as an important milestone of radio, as it taps an altogether new reservoir of wavelengths for commercial utilization. Such an ultra-short wave communications system lends itself to duplication in other archipelagos, and particularly in those of the tropical regions for this and similar short distance communication in reliable, continuous communication, although the efficiency of frequencies now employed for long range communication remains unchallenged.

## Attempts Begun 20 Years Ago

Attempts to establish inter-island telephone service for Hawaii were begun by the Mutual Telephone Company in 1912, when a survey disclosed that the channels between the islands were too deep to make the use of cables for voice communication practicable. The successful system eventually was established through the cooperation of Radio Corporation of America engineers with the Mutual Company, which called upon R.C.A. Communications, Inc., for assistance following extensive research and experimental work by R.C.A. in the ultra-short wave field.

At the time R.C.A. engineers were brought into consultation, in 1928, experiments had been conducted in Hawaii over a period of years on various frequency bands open for use by the telephone company. However, the spectrum of intermediate and the so-called "normal band" of short waves had been abandoned because of the selective fading and strong atmospheric experienced. It was quickly found that transmission on the ultra-short waves would convey telephone conversation with reliability over the required distances, but many problems remained for solution before a practical system could be developed.

## Behave Like Light Waves

Ultra-short waves have many of the properties of light waves, which do not tend to follow the curvature of the earth. In the Hawaiian system they are transmitted from point to point on the same plane, without there being mountains or other intervening obstacles. This condition was met by locating the Hawaiian stations on top of the mountains and in a direct air line with stations on the mountain peaks of other islands. Mathematically exact surveys were conducted so as to permit a perfect alignment of sending and receiving antennae at the different stations.

Although ultra-short waves provided, in this instance, the solution of transmission through the ether without static or interference, the apparatus which generated the waves was extremely critical of adjustment. A transmitter on so short a wavelength is subject to "frequency drift" or shifting of wavelength, from very slight causes. Even so small a factor as a change in atmospheric temperature would throw

it off the appointed wave. This had to be overcome, else the constant attention of trained engineers would be required to keep the stations "in tune" and even then interruptions to the service would be inevitable.

## New Control Introduced

The usual engineering method of maintaining a transmitter on its assigned wave is by means of electric crystal control. But this necessitates much associated apparatus and, in the case of ultra-short waves, so much additional equipment as to place the cost of operation beyond all reasonable limits. R.C.A. engineers solved this difficulty with a new development known as the Long Line Frequency Control.

This is an electrical circuit, with no tubes and no moving parts, connected to the five meter transmitting circuit. The action of the Long Line Frequency control is to correct automatically and entirely by electrical means any tendency of the transmitter to stray from its proper wavelength.

Through its employment, the apparatus is lifted out of the category of critical, laboratory equipment and made practical for commercial use. The Long Line Frequency Control makes possible installations which need only periodic attention and otherwise maintain telephone communication between islands as dependably as though they were connected by wires. Equipment for the new system was supplied by R.C.A.-Victor Company.

## Band from 5 Meters Down

The possibilities of ultra-short waves have for some years been a subject of speculation and investigation among radio engineers. Pioneering research in this field had been done by Marconi, both in his independent efforts and in cooperation with the Italian Government. R.C.A. began experiments several years ago.

The ultra-short wave band is generally listed in present day parlance as that part of the radio spectrum which extends from five meters downward. There appears to be little or no difference in the essential properties of these frequencies except that they present more problems in control as the wavelength shortens. Research among other frequencies in the realm of ultra-short waves has been and is being conducted at the R.C.A. Communications laboratories at Riverhead and Rocky Point, Long Island. It is believed that the principles of the Long Line Frequency Control will prove of great value in the taming of even the shorter of the ultra-short waves.

The Long Line Frequency Control is so named because the electrical circuit which constitutes this device comprises lines having a length many times the length of the wave on which the transmitter operates.

The Hawaiian radio-telephone system was due largely to the efforts of J. A. Balch, president of the Mutual Telephone Company, who pushed forward continuous experimental work on the islands. Of its operation, Mr. Balch reported that on the day the new system was opened for commercial traffic a total of 213 calls was handled without a single instance of a call having to be cancelled on account of unsuccessful transmission.

## Immune from Static

During the first week of commercial service the islands were visited by a severe static storm, described by Mr. Balch as one of the worst in his experience, with lightning flashing almost continually for the better part of two days and nights.

"No difficulty was experienced, however, in the operation of our ultra-fre-

# WAVES OF FIVE METERS OR LESS FOR MESSAGES

quency telephone circuits," said Mr. Balch, "and it was a weird experience to be watching the lightning flashing and at the same time talking to Hilo without difficulty, or without any particular annoyance being experienced from the very faint indications of static on the circuit."

The system links the islands of Hawaii, Kauai, Oahu and Maui. A radiotelephone service in which the Mutual Telephone Company is interested between Hawaii and the North American mainland will be opened probably before this Christmas. For the mainland service, transmitting and receiving stations in Hawaii will be owned and operated by the R.C.A. Communications, Inc. In trans-ocean work the transmitting and receiving stations in California will be owned and operated by the American Telephone and Telephone Company. Connection to the Hawaiian land telephone network as well as to the new, inter-island radiotelephone service, will be made through the Mutual Telephone Company.

## Forum

### Thank You; We Feel Better Now

I SHALL not attempt to praise your (or should I say "our") publication, as words are inadequate to express the pleasure I feel when I arrive home and find the latest edition waiting for me.

Five hundred and six consecutive issues and getting better all the time, if that be possible. Keep up the good work and believe me to be one of your best boosters.

WILLIAM WOOD,  
743 Willibrord Ave.,  
Verdun, P. Q., Canada.

### SUNDRY SUGGESTIONS FOR WEEK COMMENCING DECEMBER 13

- Sun., Dec. 13: N. Y. Philharmonic Orchestra; WABC—3:00 p. m.
- Sun., Dec. 13: Footlight Echoes; WOR—10:30 p. m.
- Mon., Dec. 14: Merrie-Men—Male Quartet; WJZ—12:00 noon.
- Mon., Dec. 14: Carl Fenton & Bing Crosby; WABC—7:15 p. m.
- Tues., Dec. 15: Marion Harriss; WEA—11:30 p. m.
- Wed., Dec. 16: Sherlock Holmes; WJZ—9:00 p. m.
- Thurs., Dec. 17: Weaver of Dreams; WOR—10:15 p. m.
- Fri., Dec. 18: March of Time; WABC—8:30 p. m.
- Sat., Dec. 19: Arthur Pryor and Revelers; WEA—9:00 p. m.

(If you would like to know something of your favorite radio artists and announcers, drop a card to the conductor of Station Sparks. Address her: Miss Alice Remsen, care RADIO WORLD, 145 W 45th St., New York.)

# Stations in United States and Canada, Corrected to Press Time

CANADA		Station	kc										
CFAC	690	WBBM	770	WFDW	1420	WKBO	1450	WODM	1370	KFII	1370	KJBS	1070
CFBO	890	WBBR	1300	WHEC	1430	WKBS	1310	WODX	1210	KFJM	1370	KIR	970
CFCA	1120	WBBZ	1200	WFI	560	WKBV	1500	WRAC	1370	KFJR	1300	KLCN	1290
CFCF	1030	WBCM	1410	WFIW	940	WKBW	1480	WPRO	1210	KFJY	1310	KLO	1400
CFCH	930	WBEN	900	WFLA	620	WKBZ	1500	WRAX	1310	KFJZ	1370	KLFM	1240
CFCL	960	WBEO	1310	WFOX	1400	WKIC	1200	WRAY	1020	KFKA	880	KLRA	1390
CFCN	985	WBGF	1370	WGAL	1310	WKRC	550	WRBJ	1370	WFKU	1220	KLX	1440
CFCO	1210	WBHS	1200	WGAR	1450	WKY	900	WRBL	1200	KFKX	1020	KLZ	880
CFCT	630	WBIG	1440	WGBC	1210	WKZO	590	WRBO	1210	KFLV	1410	KMA	930
CFCY	580	WBIS	1230	WGCB	1430	WLAC	1470	WRBX	1410	KFLX	1370	KMAC	1370
CFIC	1120	WBMS	1450	WGBF	630	WLAP	1010	WRC	950	KFMX	1250	KMBC	950
CFIL	915	WBNX	1350	WGBI	880	WLB	1250	WRDO	1370	KFNF	890	KMCS	1120
CFNB	1210	WBOQ	860	WGBS	1180	WLB	1319	WRDW	1500	KFOR	1210	KMED	1310
CFOC	690	WBOW	1310	WGCM	1210	WLB	1420	WREC	600	KFOX	1250	KM	1210
CFRB	930	WBRC	930	WGCP	1250	WLBG	1200	WREN	1220	KFPL	1310	KLMB	1200
CFRC	930	WBRE	1310	WGES	1360	WLBL	900	WRHM	1250	KFPM	1310	KMMJ	740
CHCK	960	WBRS	920	WGH	1310	WLBW	1260	WRJN	1370	KFPW	1340	KMO	860
CHCS	630	WBSO	1080	WGL	1370	WLBX	1500	WRNY	1010	KFQD	1340	KMOX	1090
CHGS	1120	WBT	1370	WGN	720	WLBZ	620	WROL	1010	KFOU	1420	KMP	710
CHLS	730	WBTM	990	WGR	550	WL	1210	WRR	1280	KFOW	1420	KMTR	570
CHMA	580	WBZA	990	WGST	890	WLCI	1370	WRUF	830	KFRU	1420	KNX	1050
CHML	880	WCAC	600	WGY	790	WLIT	560	WRVA	1110	KFRU	610	KOA	830
CHNS	910	WCAD	1220	WHA	940	WLOE	1500	WSAI	1330	KFSD	600	KOAC	550
CHRC	645	WCAE	1220	WHAD	1120	WLS	870	WSAN	1440	KFSG	1120	KOB	1180
CHWC	960	WCAH	1430	WHAM	1150	WLTH	1400	WSAN	1450	KFUL	1290	KOCW	1400
CHWK	665	WCAJ	590	WHAP	1300	WLVA	1370	WSAZ	580	KFUD	550	KOH	1380
CHYC	730	WCAK	1250	WHAS	820	WLW	700	WSB	740	KFUP	1310	KOIL	1260
CJBR	960	WCAM	1280	WHAT	1310	WLWL	1100	WSBC	1210	KFV	1000	KOIN	940
CJCA	930	WCAO	600	WHAZ	1300	WMAC	570	WSBT	1230	KFWB	1210	KOL	1270
CJCB	880	WCAP	1280	WHB	860	WMAK	1040	WSEN	1230	KFWF	1200	KOMO	920
CJCI	690	WCAT	1200	WHBC	1200	WMAL	630	WSEA	1410	KFWF	1200	KONO	1370
CJCC	910	WCAU	1170	WHBD	1370	WMAZ	670	WSFX	1210	KFXD	1420	KOOS	1370
CJCD	630	WCAZ	1200	WHBL	1410	WMB	1500	WSJS	1310	KFXD	1420	KORE	1420
CJCE	1120	WCB	1440	WHBQ	1370	WMB	1420	WSM	650	KFXE	920	KOY	1390
CJCF	1210	WCB	1080	WHBY	1200	WMBD	1440	WSMB	1320	KFXJ	1310	KPCB	650
CJCG	665	WCB	1210	WHBY	1370	WMBG	1210	WSMC	1380	KFXM	1210	KPJM	1500
CJCH	730	WCCO	810	WHDF	1370	WMBH	1420	WSOC	1210	KFXR	1210	KPO	680
CJCI	645	WCDA	1350	WHDH	830	WMBI	1080	WSPA	1420	KFXV	1420	KPOF	880
CJCK	960	WCFL	970	WHEC	1440	WMB	1310	WSPD	1340	KFY	1420	KPPC	1210
CJCL	960	WCGU	1400	WHFC	1420	WMB	1500	WSUI	880	KFYR	550	KPRC	1500
CJCM	890	WCHI	1490	WHIS	1410	WMBR	1370	WSUN	620	KGA	1470	KQV	1380
CJCN	645	WCKY	1490	WHK	1390	WMC	780	WSVS	1370	KGB	1370	KQW	1010
CJCO	880	WCLO	1200	WHN	1010	WMCA	570	WSYB	1500	KGB	1330	KRE	1370
CJCP	730	WCMA	1310	WHO	1000	WMIL	1500	WSYR	570	KGBU	900	KRGV	1260
CJCR	730	WCOA	1340	WHOM	1450	WMMN	890	WTAD	1440	KGBX	1310	KRLD	1040
CJCS	840	WCOC	880	WHP	1430	WMPC	1500	WTAG	580	KGBZ	930	KRMD	1310
CJCT	1010	WCOD	1200	WIAS	1420	WMRJ	1210	WTAM	1070	KGCA	1270	KROW	930
CJCC	840	WCOD	1200	WIBA	1280	WMSG	1350	WTAR	1330	KGCR	1210	KRSC	1120
CJCD	1210	WCOH	1210	WIBG	930	WMT	600	WTAR	780	KGCU	1240	KSAC	580
CJCE	730	WCRW	1210	WIBM	1370	WNAC	1230	WTAX	1120	KGDA	1370	KSCJ	1330
CJCF	960	WCSC	1360	WIBO	560	WNAD	1010	WTBO	1210	KGDE	1200	KSD	550
CJCG	630	WCSE	940	WIBR	1420	WNAX	570	WTBO	1420	KGDM	1100	KSEI	900
CJCH	1200	WDAE	1220	WIBU	1210	WNB	1500	WTFL	1310	KGDY	1200	KSL	1130
CJCI	880	WDAF	610	WIBW	580	WNBH	1310	WTFI	1450	KGEW	1200	KSMR	1200
CJCK	890	WDAG	1410	WIBX	1200	WNB	1200	WTIC	1060	KGEV	1300	KSO	1380
CJCL	580	WDAH	1310	WICC	600	WNB	1430	WTIS	1310	KGFK	1200	KSOO	1110
CJCM	730	WDAY	940	WIL	1200	WNBW	1200	WTMJ	620	KGEW	1360	KSTP	1460
CJCN	960	WDBJ	930	WILL	890	WNBX	1200	WTNT	1470	KGEW	1200	KTAB	560
CJCO	540	WDBO	1120	WILM	1420	WNBZ	1290	WTOT	1260	KGFF	1310	KTAR	620
CJCP	780	WDEL	1120	WIOD	1300	WNJ	1450	WTSL	1310	KGFG	1370	KTAT	1240
CJCR	630	WDEV	1420	WIP	610	WNOX	560	WWAE	1200	KGFI	1500	KTBR	1300
CJCS	840	WDGY	1180	WIS	1010	WNYC	570	WWJ	920	KGFI	1200	KTBS	1450
CJCT	910	WDIX	1500	WISN	1120	WOAI	1190	WWL	850	KGFK	1200	KTFI	1320
CJCC	730	WDOD	1280	WIAC	1310	WOAX	1280	WWNC	570	KGFL	1500	KTHS	1040
CJCD	600	WDRC	1330	WJAG	1060	WOBU	580	WWRL	1500	KGFV	1370	KTLC	1310
CJCE	880	WDSU	1250	WJAK	1310	WOC	1000	WWSW	1500	KGFV	1310	KTM	780
CJCF	960	WDZ	1070	WJAR	890	WOCL	1210	WWVA	1160	KGGC	580	KTRH	1120
CJCG	910	WEAF	660	WJAS	1290	WODA	1250	WXYZ	1420	KGGF	1010	KTSA	1290
CJCH	1120	WEAL	1270	WJAX	900	WODX	1410	KABC	1420	KGGM	1010	KTSL	1310
CJCI	1030	WEAN	780	WJAY	610	WOI	640	KBPS	1420	KGHF	1320	KTSM	1310
CJCM	780	WEAO	570	WJAZ	1490	WOKO	1430	KBTM	1200	KGHI	1200	KTWS	1220
CJCN	690	WEBC	1290	WJBC	1200	WOL	1370	KCRJ	1310	KGHL	950	KUJ	1370
CJCO	840	WEBO	1210	WJBI	1210	WOMT	1210	KDB	1500	KGI	1360	KUOA	1390
CJCP	840	WEBR	1310	WJBK	1370	WOOD	1270	KDKA	1210	KGIW	1420	KUSD	890
CJCR	630	WEDC	1420	WJBL	1200	WOPI	1500	KDLR	1210	KGIX	1420	KUT	1500
CJCS	840	WEDH	1210	WJBO	1420	WOQ	1300	KDYL	1290	KGIZ	1500	KVI	760
CJCT	910	WFFI	590	WJBT	770	WOR	710	KECA	1430	KGJF	890	KVL	1370
CJCC	730	WFEU	830	WJBU	1210	WORC	1200	KELW	780	KGKB	1500	KVOA	1260
CJCD	600	WEHC	1350	WJBW	1200	WOS	630	KEX	1180	KGKO	1370	KVOO	1140
CJCE	880	WEH	1420	WJBY	1210	WOV	1130	KFB	770	KGKY	1420	KVOR	1270
CJCF	960	WEHS	1370	WJDX	1270	WOW	590	KFAC	1300	KGMB	1320	KW	1210
CJCG	910	WEIK	1470	WJDK	1130	WOWO	1160	KFBI	1280	KGNF	1430	KWJ	1060
CJCH	1120	WELL	1420	WJJD	1130	WPAD	1420	KFBK	1310	KGNO	1210	KWK	1350
CJCI	1030	WENR	870	WJKS	1360	WPAP	1010	KFBL	1370	KGO	790	KWKC	1370
CJCM	780	WEPS	1200	WJMS	1420	WPAP	1010	KFDY	560	KGRS	1410	KWKH	850
CJCN	690	WEVD	1300	WJR	750	WPAP	1210	KFEL	920	KGU	940	KWLC	1270
CJCO	840	WEV	760	WJSV	1460	WPCH	810	KFEQ	680	KGVO	1420	KWSC	1220
CJCP	840	WEXL	1310	WJW	1210	WPEN	1500	KFG	1310	KGY	1200	KWWG	1260
CJCR	630	WFAA	800	WJTL	1370	WPG	1100	KFH	1300	KHI	900	KXA	570
CJCS	840	WFDV	1310	WJZ	760	WPOE	1370	KFI	640	KICK	1420	KXL	1420
CJCT	910	WFAN	610	WKAQ	890	WPOR	780	KFIO	1120	KID	1320	KXO	1500
CJCC	730	WFBC	1200	WKAR	1040	WRAM	1370	KFJB	1200	KIDO	1350	KY	1230
CJCD	600	WFBE	1200	WKAV	1310	WRPC	1230	KFJF	1485	KIT	1310	KYW	1020
CJCE	880	WFBG	1310	WKBB	1310	WPTF	680						
CJCF	960	WFBL	1360	WKBC	1310	WQAM	560						
CJCG	910	WFBM	1230	WKBF	1400	WQAN	880						
CJCH	1120	WFBR	1270	WKBI	1380	WQAO	1010						
CJCI	1030	WFDD	1310	WKBN	570	WQBC	1360						
CJCM	780	WFDV	1370										

H. E. Wehmler, 1312 Porter St., Dearborn, Mich.  
 Joseph Henderson, 547 83rd St., Brooklyn, N. Y.  
 W. B. Smith, 21 Regent St., Jamestown, N. Y.  
 Foster Fraleigh, Box 196, Lawndale, Ohio.  
 Arthur Smith, 1003 N. Poplar St., Ottawa, Kns.  
 Ralph G. Hoesly, 27 Ely Place, East Orange, N. J.  
 W. R. Newcomb, 156 Enfield Cres., Norwood, Winnipeg, Man., Canada.  
 Jerome Engelhart, 24 Tuitman St., Newark, N. J.  
 L. M. Jackman, E. Corinth, Vermont  
 Martin J. Lieberman, 731 Marshall Ave., St. Paul, Minn.  
 William Broadbent, 6022 Byron St., Chicago, Ill.  
 Peter Rossetti, 8 Beacham Ave., Cliftondale, Mass.  
 Charles Haefner, 1810 North Park Ave., Chicago, Ill.

## SHORT WAVE CLUB

Any reader may join without obligation by sending in name and address.


Cecil Johnston, 73 Langford Ave., Toronto, Ont., Canada.  
 Emil V. H. Weber (W6AEL), 5622 So. Harcourt Ave., Los Angeles, Calif  
 Vernon J. Larsen, Browning, Mont.  
 Everett Clark, Box 127, Marietta, Okla.  
 Louis Godovnick, 262 Barrett St., Brooklyn, N. Y.  
 Edward Eufemia, 1170 Gun Hill Road, New York, N. Y.  
 Milton Greene, 1621 St. Marks Ave., Brooklyn, N. Y.  
 Lewis Mitchell, Muhlenburg Hospital, Plainfield, N. J.

Andrew I. Gorka, Jr., 10548 Corliss Ave., Chicago, Ill.  
 H. M. Brickwedel, 264 Broad St., San Francisco, Calif.  
 Louis P. Urban, 530 Notre Dame Ave., Dayton, Ohio.  
 Charles E. Smith, 24 Upland St., Lyman, So. Car.  
 Kenneth McClure, 622 Thomas St., Elkhart, Ind.  
 John D. Mullane, 3750 102nd St., Corona, N. Y.  
 Arthur Anagnost, 21

# TELEVISION

*Now Ready for*

## Short Wave Club Members!

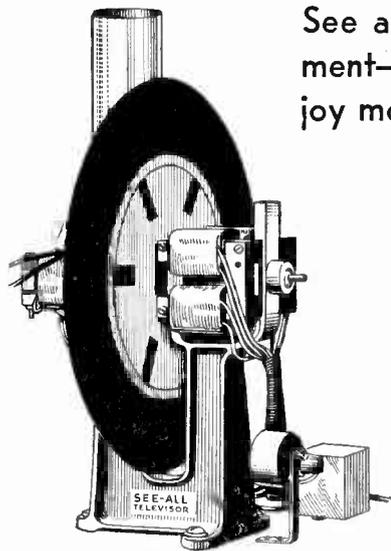

See as well as hear your radio entertainment—complete your equipment and enjoy modern television with the

## SEE-ALL TELEVISOR


only \$19.75

Unconditionally guaranteed against electrical and mechanical defects.

A complete practical kit outfit at less than the cost of a synchronous motor . . . easily assembled in less than 30 minutes.

You get all of this for \$19.75

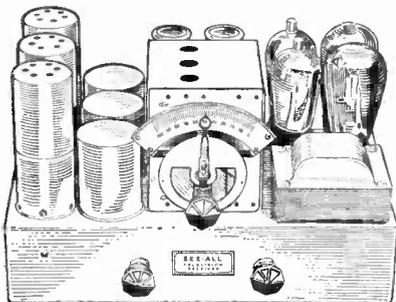Complete eddy current motor . . . 60 line square hole double spiral scanning disc, made of special alloy aluminum . . . Rheostat . . . Condenser . . . Adjustable lamp housing and bracket . . . Synchronizing wheel . . . All necessary wiring . . . Complete blueprints of televisor . . . Complete blueprints of short wave receiver . . . Detailed assembling instructions.



### The SEE-ALL Short Wave Set

For use with the SEE-ALL or any standard Televisor. Range 85-220 meters. Assures reproduction of television pictures with minute detail. Side band suppression causing loss of detail entirely eliminated. Tunes in as easily as a modern broadcast receiver.

Price \$39.50

Assembled but unwired and less tubes

Price for Scanning Disc alone—\$2.50. Any other parts can also be purchased separately. Write for price list.



TELEVISION MFG. CORP. OF AMERICA

5 Union Square, New York

Send me the SEE-ALL TELEVISOR KIT C.O.D. I will pay postman \$19.75 plus postage charges.

NOTE—If remittance accompanies order, we will prepay postage.

Name .....

Street .....

City ..... State .....

R. W. 12 12 31

## LYNCH Resistors



Write for details of new RMA Color Code Chart  
LYNCH MFG. CO., Inc., Dept. W, 1775 B'way, N. Y.

## Receiving Tube Chart

A receiving tube chart, 7 x 13 inches, with accompanying explanatory text, was published in the December 5th issue.

This chart contained the characteristics of 34 receiving and transmitting tubes, and covered all the tubes in general use. The type, purpose, rating, voltage requirements, current, mutual conductance, amplification factor, ohms load and power output were given. The tubes are classified as detectors and amplifiers, power amplifiers, rectifiers, regulators and types for amateur and experimental uses. Data on the new tubes are included. Send 15c for a copy of the December 5th issue and retain this table as a permanent record until the next one is published, which will not be for several months.


RADIO WORLD  
145 West 45th Street, New York, N. Y.

## RADIO WORLD and "RADIO NEWS"

BOTH FOR ONE YEAR \$7.00 Canadian and Foreign \$8.50

You can obtain the two leading radio technical magazines that cater to experimenters, service men and students, the first and only national radio weekly and the leading monthly for one year each, at a saving of \$1.50. The regular mail subscription rate for Radio World for one year, a new and fascinating copy each week for 52 weeks is \$6.00. Send in \$1.00 extra, get "Radio News" also for a year—a new issue each month for twelve months. Total, 64 issues for \$7.00.

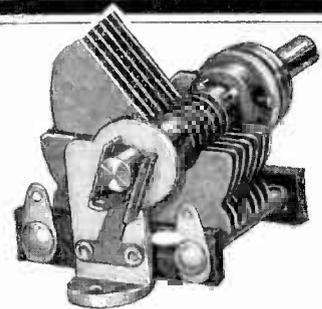RADIO WORLD, 145 West 45th Street, New York, N. Y.



## Ideal for Short-Wave RADIO

For quality reception on the short-waves, use equipment recommended by experts throughout the world.

HAMMARLUND Condensers, Chokes and Coils are backed by thirty years of engineering experience.

Write Dept. RW-12 for literature.

HAMMARLUND MFG. CO.  
424-438 W. 33rd St., New York



CHRISTMAS GIFTS FOR HIM

A Great Volume by Prof. Morecroft An Event in Radio Literature



PROF. JOHN H. MORECROFT, of the department of electrical engineering, Columbia University, is the outstanding writer of radio text books in the United States.

Now Prof. Morecroft has just brought out a new book, "Experimental Radio Engineering," just the volume for the radio experimenter, a valuable adjunct to the actual work performed by radio enthusiasts in their laboratories, whether at home or in shops or factories.

Also, the new volume marks the Professor's recognition of the great amount of experimental work and receiver and amplifier construction going on throughout the world. He has handled the experimental subject with the same deft skill and authority that marked his two previous volumes.

It behooves every radioist to possess all three books by Prof. Morecroft, but if he can choose only one at a time the experimenter of course wants to start with "Experimental Radio Engineering."

Prof. Morecroft's style is clear and definite and besides he writes with the authority of a scientist. Problems that have vexed you will be found solved and explained in as simple a manner as is consistent with accuracy.

The volume contains fifty-one experiments on the more important phenomena of radio. It is intended to be companion book to the author's "Principles of Radio Communication," but is in itself a text on practical radio measurements. Contains a vast fund of useful information for the beginner as well as for the advanced student of the principles of radio.

Measurements of resistance, self-inductance, mutual inductance, capacity, radio frequency voltages and currents, frequency, amplification; characteristics of antennas, tubes, loud-speakers, vacuum tube voltmeters, rectifiers, detectors; study of selectivity, sensitivity, fidelity, filters, modulation, and many other phases of radio are fully discussed.

The book has 345 pages, 250 illustrations, and is cloth-bound.

Order Cat. M-EXRE @ \$3.50

"ELEMENTS OF RADIO COMMUNICATION"

"ELEMENTS OF RADIO COMMUNICATION," written in plain language, requiring little foundation knowledge of radio, is a complete course on the elements of radio, and gives one an insight into radio phenomena in such a way as to clear them up. For instance, take tuning. A variable condenser commonly is connected across the secondary of a tuning coil. Just what processes take place to accomplish tuning? Obtaining full knowledge of the causes of resonance, and learning how to compute the resonant frequency of a circuit, contribute toward the enjoyment of radio construction. Resistance, impedance, reactance, inductance and capacity are explained with fitting analogies, and the whole theoretical story of radio laid bare in such a fascinating and compelling manner as to make the volume of inestimable value.

The book contains much material never before published, is up-to-date and contains 226 pages, 170 illustrations and a complete index. Cloth bound.

Order Cat. M-ELEM @ \$3.00

(Remit with order and we pay transportation. Five-day money-back guarantee attaches to the purchase of all books.)

"PRINCIPLES OF RADIO COMMUNICATION"

"PRINCIPLES OF RADIO COMMUNICATION," the larger and deeper volume by this outstanding authority and former president of the Institute of Radio Engineers, covers essentially the same ground as "Elements of Radio Communication," but does so more extensively and with a mathematical treatment that commends this book to radio engineers and college and university students in radio engineering.

"Principles of Radio Communication," which is in its second edition, contains 1,001 pages, 831 illustrations and is cloth-bound.

Order Cat. M-PRN @ \$7.50

[Remit with order and we pay transportation. Five-day money-back guarantee attaches to the purchase of all books.]

BOOKS BY MOYER AND WOSTREL

ANOTHER new volume is "The Radio Handbook," by James A. Moyer and John F. Wostrel, both of the Massachusetts Department of Education. This handbook meets the need for a complete digest of authoritative radio data, both theoretical and practical.

From the fundamentals of electricity, magnetism and the electron theory, right down to the latest commercial and industrial applications of radio, this book covers the field, with descriptions, definitions, design data, practical methods, tables and illustrations in profusion. It is a complete modern manual of practical and technical radio information.

Some of the subjects covered are: modern transmitters, piezo crystal control, percentage modulation, commercial and amateur short-wave receivers and transmitters, Kennelly-Heaviside layer effects and measurements, marine radio equipment, auto alarm, automobile receivers, latest tubes including photo-electric cells, television, sound motion pictures, etc.

If you want a book that quickly refers you to the correct information contained within its covers on any subject pertaining to radio, this is the volume. It has 886 pages, 650 illustrations. Flexible binding.

Order Cat. MW-RH @ \$5.00

The need for an up-to-date book on radio tubes that answers all the important questions has been filled by Moyer and Wostrel. This book is a complete discussion of tube principles, functions and uses. The essential principles underlying the operation of vacuum tubes are explained in as non-technical a manner as is consistent with accuracy. The book covers the construction, action, reactivation testing and use of vacuum tubes as well as specifications for vacuum tubes and applications for distant control of industrial processes and precision measurements. 297 pages, cloth bound. Order Cat. MWT. @ \$2.50

"Practical Radio," including the testing of radio receiving sets. 378 pages, 223 illustrations. Cloth bound. Order Cat. MWP. @ \$2.50

"Practical Radio Construction and Repairing," 319 pages, a companion volume to the above. New edition, new price. Order Cat. MWC. @ \$2.50

(Remit with order and we pay transportation. Five-day money-back guarantee attaches to the purchase of all books.)

THREE BOOKS BY ANDERSON AND BERNARD

AUDIO POWER AMPLIFIERS

The book begins with an elementary exposition of the historical development and circuit constitution of audio amplifiers and sources of powering them. From this simple start it quickly proceeds to a well-considered exposition of circuit laws, including Ohm's laws and Kirchhoff's laws. The determination of resistance values to produce required voltages is carefully expounded. All types of power amplifiers are used as examples: AC, DC, battery operated and composite. But the book treats of AC power amplifiers most generously, due to the superior importance of such power amplifiers commercially. Tube characteristic tables and curves profusely included. Cloth cover, 193 pages. Order Cat. APA @ \$1.50

THE SUPERHETERODYNE

This volume by Anderson and Bernard deals with the principles and practice of the Superheterodyne method of receiving and is particularly important now, because this is a superheterodyne year. It explains the function of the oscillator, the modulator, the pre-modulator selector, and the intermediate frequency amplifier. It explains the cause of repeat points and gives methods for avoiding them or minimizing their effect. It illustrates various forms of oscillators and tells of the advantages of each. Different types of modulators and pick-up systems are explained and their advantages stated. Different methods of coupling in the intermediate frequency amplifier are shown.


Order Cat. SEH @ \$2.50

FOOTHOLD ON RADIO

In simple English that any one can understand, the technical side of radio is presented by Anderson and Bernard in their book, "Foothold on Radio." Any one who can read English can understand this book. It is intended for the sheer novice. The treatment is non-mathematical.

Order Cat. FOR @ \$0.60

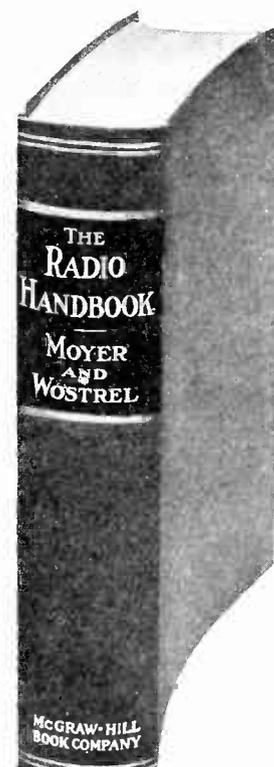(Remit with order and we pay transportation. Five-day money-back guarantee attaches to the purchase of all books.)



RADIO WORLD, 145 West 45th St., New York, N. Y.
Include please, in following books and prices:
Cat. M-EXRE @ \$3.50
Cat. M-ELEM @ \$3.00
Cat. M-PRN @ \$7.50
Cat. MW-RH @ \$5.00
Cat. MWT @ \$2.50
Cat. MWP @ \$2.50
Cat. MWC @ \$2.50
Cat. APA @ \$1.50
Cat. SEH @ \$2.50
Cat. FOR @ \$0.60
Name \_\_\_\_\_
Address \_\_\_\_\_
City \_\_\_\_\_
State \_\_\_\_\_
Remit with order and we pay transportation. Five-day money-back guarantee attaches to the purchase of all books.