

JUNE 10 1933 15¢ Per Copy

# RADIO

REG. U.S. PAT. OFF.

# WORLD

The First and Only National Radio Weekly  
*Twelfth Year 585th Consecutive Issue*

## PORTABLE UNIVERSAL

FOR


## SHORT WAVES



*See Article  
on Page 6*

Introducing For The First Time—The **POWERTONE PORTABLE AC-DC Short Wave Receiver**

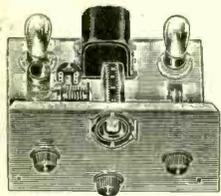
**Beginner's Twin S. W. Receiver with Hammarlund Parts**



Described in RADIO WORLD, April 15. Acclaimed by RADIO WORLD readers, who have purchased a "TWIN," as the finest short wave set to learn the mysteries of short waves. A letter to N. Y. Sun, May 20th, from one of our customers, states that he received stations in England, Germany, Italy, Africa, Geneva, and Spain. Economical—

Uses two 2-volt 230 low current tubes.  
KIT OF PARTS (blueprints, 4 coils, etc.) **7.95**  
Wired, with 4 coils (15-200 meters).....8.95

**"AMBASSADOR OF THE AIR" RELIABLE ONE**

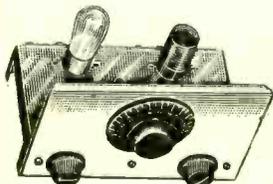


**Short Wave Receiver**  
As described in the RADIO WORLD on June 3rd. A peach of a set for the novice short wave fan. A simple layout yet with the facilities of a larger short wave set. The kit is complete in every detail, with a simple blueprint showing every

step how to assemble it. A 230 tube is used for low current consumption and a super smooth regeneration control for better and clearer results.

(Kit of parts, with coils 15-200 meters).....**3.95**  
Wired with coils.....4.95  
230 tube .....75

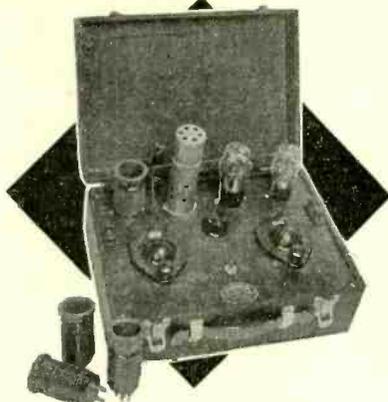Described in detail in this issue of the **RADIO WORLD**



TRY-MO is the exclusive distributor of this Universal Portable Short Wave Receiver. It is a splendid engineering achievement, and both its performance and price should make it one of the most popular S.W. sets this Summer.

Kit is complete down to the smallest nut. Panel and base already drilled. Blueprint very simple to follow. Beautiful black carrying case. Tunes from 15 to 550 meters.

KIT OF PARTS (blueprint, case, coils).....**8.95**  
Wired \$2.00 extra. Kit of tubes.....3.25  
Regular broadcast coil.....85c

**UNIVERSAL A.C. and D.C.**

**Short Wave Receiver with Hammarlund Parts**

Described in RADIO WORLD, May 13th. Get your share of the thrills of short wave reception! Here is a "beaut" of an all-round set that can be connected to any current without batteries. Stations received from all parts of the globe. Uses 1-'43, 1-'78 and 1-2525. Coils cover from 15 to 200 meters.




Complete kit of parts with cabinet, coils.. **7.95**  
Wired with coils .....\$2.00 extra

**POWERTONE**

**4-Tube S. W. Receiver (15-200 Meters)**

Described in July Issue of Short Wave Craft

A receiver that will log stations from all parts of the United States on your loudspeaker, and with the use of headphones will receive stations from all continents. Exceedingly easy to tune, and oscillation is always under full control of the operator.

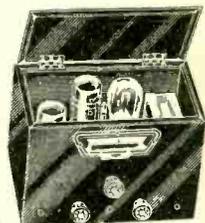

Uses 1-'56, 1-'58, 1-'80 and 1-'47 tubes. Kit complete with every necessary part.

Kit of parts with OCTO form coil, SYLVANIA coils.....**16.95**

Wired with OCTO form coils and SYLVANIA tubes .....19.75

**TRY-MO RADIO CO.**

(Dept. R. W.)  
85 CORTLANDT STREET N. Y. CITY  
Branches—178 Greenwich Street—179 Greenwich Street  
Send for new 108-page Catalog

"AMATEUR MOVIE CRAFT," by James R. Cameron. A book dealing with the making and showing of 16 m/m pictures and equipment necessary for same. Paper cover, \$1.00; Cloth, \$1.50. Radio World, 145 W. 45th St., New York, N. Y.

**PUSH-PULL DIAMOND**

**A** dual-range receiver, 1550—535 kc, 1525—4200 kc, using a perfected superheterodyne circuit, frequency-stabilized oscillator and electron coupling between modulator and oscillator. Ten tuned circuits, four variable. Two stages of t-r-f, tuned modulator, tuned oscillator, with switch for wave-changing. Output 15 watts from 2A3's in push-pull. Full-wave second detector, with 56 driver of output. 52 mfd. of B filter capacity. Automatic volume control of two i-f tubes. Automatic inter-channel noise suppression. Selectivity enough to blot out strong locals 10 kc removed from distant station. No squeals whatever.

Tubes used: Five 58's; two 55's; one 56; two 2A3's; one 5Z3.  
Wired Model of 12-Tube Push-Pull 8-Tube Model, 2A5 output, complete kit, speaker, tubes, \$24; wired, \$29.50.  
Super Diamond, including speaker, tubes and everything else, except cabinet. Lined up and padded by experts. Licensed. **\$41.27**

Complete parts, speaker, tubes, everything except cabinet. **\$37.77**

**Direct Radio Co.**

143 West 45th Street  
New York, N. Y.

1-WATT PIGTAIL RESISTORS @ 5c EACH in following ohmages: 350; 800; 1,200; 20,000; 50,000; 100,000; 250,000; 2,000,000; 5,000,000. Direct Radio Co., 145 W. 45 St., N. Y. City.

"HANDBOOK OF REFRIGERATING ENGINEERING," by Woolrich—Of great use to everybody dealing in refrigerators. \$4. Book Dept., Radio World, 145 W. 45th St., N. Y. City

NEW RADIO AMATEUR'S HANDBOOK, 180,000 words, 207 illustrations, 218 pages (10th edition, issued 1933). Price, \$1.00 per copy. Radio World, 145 West 45th Street, New York, N. Y.

**MAKE AN A & B RADIO BATTERY CHARGER**

Why pay \$8.00 to \$14.00 for a charger, when you can make one at home at a low cost? Charges all kinds of batteries, including automobile. Charges at the rate of 1/2 amp. per hour or more. One of the finest chargers there is. Plans mailed to anyone for seventy-five cents.

JOS. WOLK, 2683 Deacon St., Philadelphia, Pa.

**Mr. SERVICEMAN**

Take a tip! Get Rider's Volume II of the Perpetual Trouble Shooter's Manual. Buy it today. Don't wait until you cannot repair a receiver because you do not have the data.

**FREE.** If you are a Service Man, write for the color code chart of the resistors used in Atwater Kent receivers. Enclose 3c to cover postage.

RADIO TREATISE CO., Inc.  
1440 Broadway New York City


**SHIELDED SHORT WAVE BATTERY SET**

17 to 200 Meters  
As Described in RADIO WORLD May 20th Issue

USING

1-'30, 1-'32,  
1-'33, 1-'34

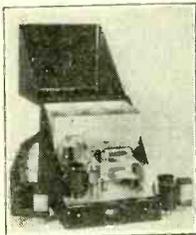LOW  
CURRENT  
DRAIN  
INEX-  
PENSIVE  
TUBES



COMPLETE KIT of parts with 2 sets of coils (8 coils) **\$8.95**

With Tubes ..... **\$10.95**

Completely Wired ..... **\$10.95**


With Tubes ..... **\$12.95**

Tubes Guaranteed 3 Months  
Foundation Kit, includes 1 Metal Case, 1 Chassis and 1 Shielded Compartment **\$2.45**

A REAL THRILL IN STORE FOR SHORT WAVE RECEPTION. Get Police reports, Ship-to-Ship and Amateur Conversations, also Short Wave Broadcast Stations.

**LEOTONE RADIO COMPANY**  
63 DEY STREET, NEW YORK CITY

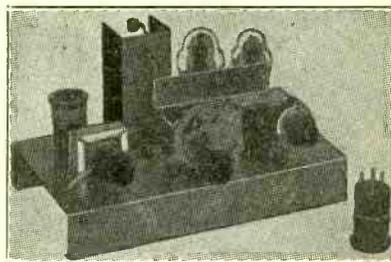**Get the ORIGINAL IMPROVED PRIZEWINNER**



THE PRIZEWINNER is complete. No extras, such as power supply, coils, etc., to buy. Power supply is built-in and will operate on EITHER AC OR DC! Four coils included, cover all bands, 20,000 KC to 1,500 KC.

Complete kit of PRIZEWINNER parts identical in every respect with those used in built-up models, complete in every detail, including hardware, hookup wire, solder, coils, etc., and also the cabinet and dial. Price..... **\$8.95**

Set of RCA tubes containing 1-77, 1-43, 1-25-25 for above..... **\$3.75**

Assembled, wired, tested and enclosed in beautiful crackle finish, or Cadmium Plated metal cabinet, ready to plug into your power line. Complete with four coils..... **\$10.95**

Mail Orders Promptly Filled  
Write for Free Literature

**ALAN RADIO CORP.**  
The House of Dependable Service  
83R CORTLANDT STREET  
N. Y. CITY

ROLAND BURKE HENNESSY  
Editor

HERMAN BERNARD  
Managing Editor

# RADIO WORLD

J. MURRAY BARRON  
Advertising Manager

The First and Only National Radio Weekly  
TWELFTH YEAR

Vol. XXIII

JUNE 10th, 1933

No. 13. Whole No. 585

Published Weekly by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y.

Editorial and Executive Offices: 145 West 45th Street, New York  
Telephone: BR-yant 9-0558

OFFICERS: Roland Burke Hennessy, President and Treasurer; M. B. Hennessy, Vice-President; Herman Bernard, Secretary.

Entered as second-class matter March, 1922, at the Post Office at New York, N. Y., under Act of March 3, 1879. Title registered in U. S. Patent Office. Printed in the United States of America. We do not assume any responsibility for unsolicited manuscripts, photographs, drawings, etc., although we are careful with them.

Price, 15c per Copy; \$6.00 per Year by mail \$1.00 extra per year in foreign countries. Subscribers' change of address becomes effective two weeks after receipt of notice.

## FREQUENCY MEASURED with Television Scanner

### Range is From About 20 to 12,000 Cycles

By J. E. Anderson

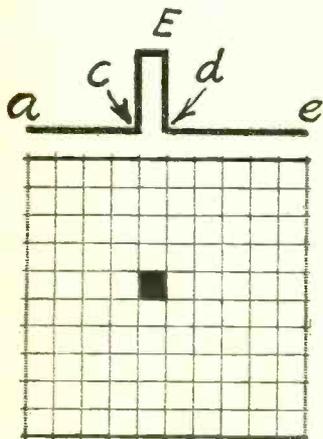


FIG. 1

A television screen and the kind of image that results when a dot appears once every frame.

AN INTERESTING application of the television scanner is to the measurement of frequencies. How this is done will be understood when the mechanism of scanning is understood. Let Fig. 1 represent the field of the television screen, and assume it to be square. In most scanning systems at present the field is covered by 60 lines, running from left to right and from top to bottom. That is, a spot of light moves over the screen in exactly the same way as one reads a printed page. The 60 lines are completed in  $1/20$  of a second, or the "frame frequency" is 20 per second. Of course, it could have some other value, but that is the principal rate of scanning at the present time.

At the top of the frame in Fig. 1 is a curve representing the signal. It is a dot of very short duration. From  $a$  to  $c$  the signal is zero, from  $c$  to  $d$  it has a constant value  $E$ , and from  $d$  to  $e$  it is again zero.

Let us first suppose that the time be-

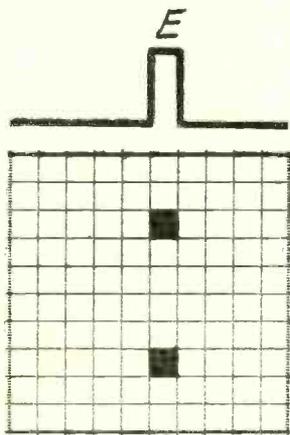


FIG. 2

When dot signal frequency is twice the frame frequency two dots appear, one above the other.

tween  $a$  and  $e$  is  $1/20$  second and that  $cd$  occupies a very small part of this, say  $1/3,600$  part. As the scanning proceeds this spot will appear on the screen either as a black dot on a white background or as a white dot on a black background, depending on whether the image is positive or negative. It will only occur on one line and at one spot in this line. Since this signal is repeated once every  $1/20$  of a second, or once for each frame, it will always appear at the same spot, at which it will remain stationary, provided that the frequency of the dot is the same as the frame frequency.

#### Frequencies Not Coincident

Suppose now that the signal frequency is a little greater than the frame frequency. The spot will no longer occur at the same place. It will always occur a little sooner than it did the previous time. Hence the spot will move in the direction opposite to the scanning direction. For example, if the

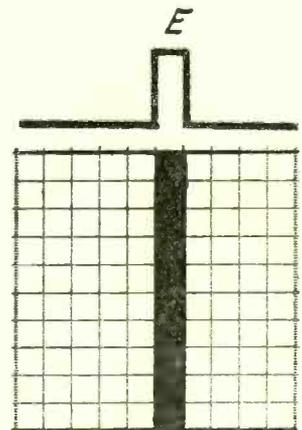



FIG. 3

When the dot signal frequency is equal to the line frequency of scanning a vertical line is stationary.

spot first appears at the right edge of a line, it will slowly move toward the left edge. There it disappears, but immediately reappears at the right edge in the line above. The spot will scan the entire field but in the opposite direction to the true scanning. If, on the other hand, the frequency of the signal is a little slower than the frame frequency, the spot will move in the same direction as the scanning beam, because each time it will appear a little later than it did before.

If it were possible to follow the spot as it moves, which it may not be, it would be possible to measure frequencies both higher and lower than the frame frequency, as well as the frame frequency, in terms of that frame frequency. It would be necessary only to measure the time the spot covers the field. It is possible to measure a frequency exactly equal to the frame frequency because then the spot will stand still and it will be visible. It is also possible

(Continued on next page)

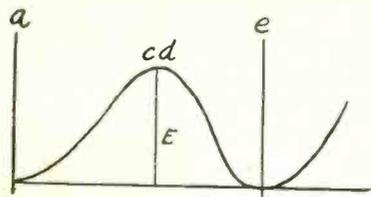

**FIG. 4**  
When the signal is a sine wave dots are drawn out into bands, with sine wave distribution of intensity.

(Continued from preceding page)  
to measure frequencies differing slightly in either direction from the frame frequency because the spot will move slowly and will be visible.

### Twice Frame Frequency

Now suppose that the signal frequency is twice as great as the frame frequency, that is, 40 per second, and that it otherwise is the same as before. The spot will now appear in two lines, one spot appearing directly over the other. If the frequency is exactly twice the frame frequency the two spots will stand still and they will be visible. This case is illustrated in Fig. 2. Wherever the spots appear, the sum of the blank lines between the dots and the edges will be the same as the number of blank lines between the two dots.

If the frequency of the signal is slightly greater than twice the frame frequency, the two dots will move to the left as in the case of a single dot, but the lower dot, that is, the one that occurs later, will be shifted more to the left. Hence the effect is that the line joining the two dots will have a positive slope. And if the frequency is slower than twice the frame frequency the dots will move toward the right, and the later dot will move farther. Hence the line joining the two dots will have a negative slope.

### Higher Frequencies

As the frequency becomes three times the frame frequency three dots will appear in a vertical line, and they will be visible because they will stand still. This may be continued until the frequency of the signal is 60 times the frame frequency, when a dot will appear in every scanning line. These dots will be so close together in the vertical direction that they will appear as a vertical line, which will be clearly visible. When the line stands still the frequency of the signal is exactly equal to 60 times the frame frequency, which in the case considered is 1,200 cycles per second. See Fig. 3.


If the frequency differs from 1,200 cycles the individual dots making up the line will not remain in one position but will move to the left or to the right depending on whether the frequency is less or greater than 1,200 cycles. The line, however, will not be vertical slant with positive or negative slope. If the frequency of the signal is less than 1,200 cycles, any dot will appear a little later, relatively, than its immediate predecessor, and the line will lean backward. Conversely, if the frequency is a little greater than 1,200 cycles, the line will lean forward.

The more the signal frequency differs from 1,200 cycles the greater will the slant be. By observing the slope of the line, it is possible to compute the amount by which the signal frequency differs from 1,200 cycles.

### Harmonics of 1,200

When the signal frequency has risen to twice 1,200 cycles, two vertical lines will appear, and they will stand still. Hence it is possible to tell exactly when the frequency is 2,400 cycles. These lines will have definite spacings, for there will be as much blank space between the two lines as the sum of the blank spaces at the sides.

When the frequency of the signal differs slightly from 2,400 cycles, the lines will

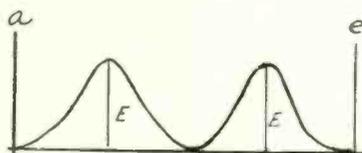

**FIG. 5**  
When the signal in Fig. 2 consists of sine waves like this the two dots are drawn out into bands.

slant in the same manner as in the case of a single line, and it is possible to estimate the frequency from its slope and the fact there are two lines.

As the frequency increases still further, more vertical lines will appear. Thus when the frequency is 3,600 cycles there will be three lines, when it is 4,800 cycles there will be four. In general, the number of stationary vertical lines multiplied by 1,200 cycles will give the frequency of the signal. Theoretically, this could be extended indefinitely, but it would be very difficult to count the number of lines when the frequency is very high.

In estimating the frequency requirements of a television circuit it is customary to assume that the lines will not be more than 60. This limit is purely arbitrary. When the scanner is used for measuring frequencies perhaps 10 lines would be the most that could be counted without much effort. That would place the frequency at 12,000 cycles.

Deviations of the signal frequency from the exact harmonics will be indicated in every case by rotation of the lines.

### Sine Wave Signal

We have assumed that the signal was a dot of very short duration. In most instances a signal to be measured is not of that type at all, but rather a sine wave. It may take the form of the curve in Fig. 4, in which the signal intensity varies from zero at *a* to a maximum *E* at *cd* and again to zero at *e*. Fig. 4 really corresponds to the case in Fig. 1, where the "dot" now has spread out over the entire field. The maximum intensity, either the darkest or the lightest area, now falls where the dot fell before.

If the sine wave signal has twice the frame frequency, the signal may be represented as in Fig. 5. This corresponds to the case in Fig. 2. The two dots now will spread out into two dark bands running horizontally across the field. Near the edges and half way between the bands there will be a minimum of "darkness." That is, the field will be practically white. That is for the case of a positive image. There will be hardly any change in intensity along the bands. Therefore the bands will be clearly visible.

When the sine wave signal has a value of 60 cycles per second, there will be three bands across the field, which are produced by stretching out the three dots. For higher harmonics of the frame frequency, there will be more bands across the field, running horizontally, one dark band and one light band for each harmonic.

Three dark and three light bands appear on the television screen when there is an appreciable 60-cycle hum in the television amplifier. These seriously interfere with the clarity of the image, and for that reason it is very important that the output of the amplifier be as free as possible from hum. If there is a 120-cycle hum in the output, there will be twice as many light and dark bands across the field, that is six of each.

### Fractional Ratios

What will happen when the impressed frequency bears some other simple ratio to the line frequency, for example, when it is 1.800? It is not easy to see directly just

what will happen, but we can analyze the case practically. Refer to Fig. 6. If we let *t* represent the time it takes the scanning beam to complete a line, then the time between two dots will be  $2t/3$ . If a dot occurs at zero time in the upper left hand corner, the next dot will occur when a time  $2t/3$  has elapsed. This will fall  $2/3$  of the way over on the first line. The second dot will occur after another  $2t/3$  has elapsed. This therefore will fall  $1/3$  of the way over on the second line. If this process is continued throughout the field, three vertical lines of dots will appear in the field, but these will not be continuous for there will be a dot in only every other horizontal line. These lines, therefore, will differ from the case when the frequency is 3,600 in that the rows of dots will be only half as intense.

It is easy to extend this case to the sine wave signal by imagining the dots to be spread out horizontally.

The case for any other simple frequency ratio can be obtained by analogy. Suppose the frequency is  $nF$ , in which *F* is the line frequency. When  $n=1$ , there is one solid line; when  $n=3/2$ , there are three half-solid lines; when  $n=2$ , there are two solid lines; when  $n=5/2$ , there are five half-solid lines; when  $n=3$ , there are three solid lines; when  $n=7/2$ , there are seven half-solid lines; when  $n=4/3$ , there are four  $1/3$ -solid lines, and so on. These various patterns that appear on the screen correspond to the beats between harmonics in a circuit in which there are two beating oscillators.

It is no more difficult to identify the ratios on the screen than in a beat generator. It is a matter of experience to judge the value of the light, or shade, in a line, and thus tell whether it is solid, one-half, one-third, and so on. As in the case of beating oscillators it is possible to identify them by observing the order in which they appear as the frequency is varied. It will be noticed that in the television scanner one frequency is always known, and it is the frequency of line repetition.

### Skew Patterns


We found that when the frequency of the signal differed somewhat from a harmonic of the frame frequency that the line joining the dots slanted one way or the other. This will also occur when the frequency differs somewhat from the line frequency or from one of its harmonics. Refer to Fig. 7. Here it is assumed that the signal frequency is to the line frequency as 60 is to 59. In the figure are sixty small squares in each line. If the first dot occurs at square (1) in the first line, the next dot will occur in the 60th square in the same line. This dot is equivalent in point of time to the zeroth square in the second line. The next dot will appear at the 59th square from this. Hence it will appear one square to the left of the last dot in the first line and one line below it. Following this out by placing a dot in each 59th square we obtain a diagonal of dots. Dots are placed at the two corners not including the diagonal for reference. Two of these dots will appear in the pattern if the field is square and if the diagonal divides the field. Of course, the diagonal might appear in another position, and then there would be two of them, the sum of the two being equal in length of the principal diagonal as shown.

Had the frequency ratio been the reciprocal of the ratio assumed, that is, 59 to 60, the diagonal would have had the opposite slope.


### Sine Wave Pattern

If the signal frequency is higher than that assumed in Fig. 7 there will be more diagonals. A case of this is illustrated in Fig. 8. Here the signal frequency is assumed to be such that a dot occurs in every 31st square. There are no less than five diagonal lines. In this case the slope of the lines is negative, the opposite of the slope in Fig. 7. Had the dots been placed so that one occurred every 29th square the slope would have been positive.


It is understood that the pattern will not

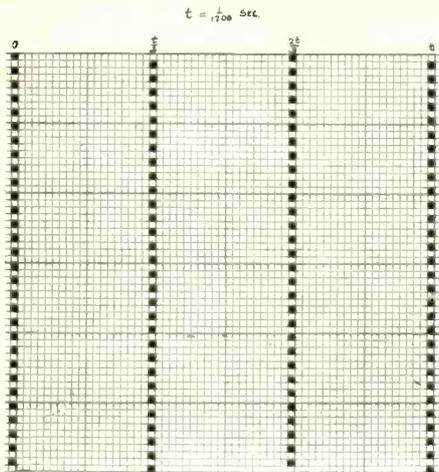

**FIG. 6**  
If the signal frequency is 3/2 times the line frequency, the pattern appears like this, three vertical half-solid lines.

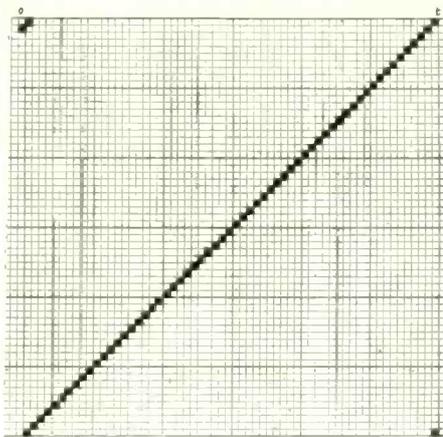

**FIG. 7**  
In this case the signal frequency is 60/59 times the line frequency. One solid diagonal line appears, or two broken diagonals.

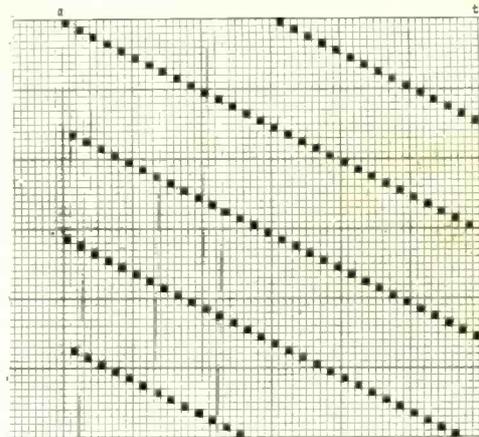

**FIG. 8**  
In this case the signal frequency is 60/31 times the line frequency. Five half-solid diagonals appear, the negative slope being 1/2.

be diagonal rows of squares when the signal consists of sine waves but rather that they will be bands in which the diagonals are maxima. The field will appear as alternate light and dark bands in which the values are so distributed that if a line is drawn at right angles to them the intensity will be a sine function.

In connection with the half-solid lines in Fig. 6 it should be pointed out that the maximum intensity in one line will be opposite to a minimum in the next. This fact may make the apparent distribution over the field uniform due to the fact that the eye does have sufficient resolving power.

When the relative values of the signal and line frequencies vary continuously, the lines, whether they be vertical, horizontal, or diagonal, will rotate either in the clockwise or counter clockwise direction. This occurs when the motor driving the scanner varies in speed, the signal frequency remaining constant, and it will also occur when the signal frequency varies, the scanning motor remaining at constant speed. When the motor is hunting, as it usually does just before it falls into synchronism, the rotation of the pattern is first in one direction and then in the other. A similar effect is often observed in the movies when a moving vehicle is shown. It frequently happens that the wheels of an automobile will appear to turn backward. As the car is retarded the wheels appear to stand still for a moment, and then to turn in the proper direction. This effect is due to the fact that wheels are seen 24 times a second. The appearance is, of course, an optical illusion and is stroboscopic in nature.

When the scanner is used for measuring frequencies, the standard is the frequency driving the motor. For example, if the motor is synchronous and is driven by a 60-cycle line, the standard frequency is really 60 cycles per second. It is possible to arrange the motor so that it revolves at different rates, all of which bear a simple ratio to the driving frequency. The rate can be determined very easily by examining the motor, that is, the lowest rate. The scanning line frequency is determined by the number of elements in the scanner, such as holes or mirrors or lenses. The scanning line frequency is also known and can be used as a reference or standard frequency.

If a variable speed motor were used it would be possible to get simple patterns for almost any signal frequency. This would be a decided advantage in measuring frequencies as it would only be necessary to adjust the speed of the motor until a simple pattern appears, from which the frequency could be determined quickly in terms of the rate of the motor. However, this method vitiates the standard frequency and it would be necessary to measure the speed of the motor. This might be done with a tachometer if no great accuracy were required.

A sensitive and reliable tachometer might possibly be constructed on the generator principle, in which the speed would be

measured with a voltmeter calibrated to read revolutions per second. This is possible because the voltage generated is directly proportional to the speed.

### SET BUILT INTO ARMCHAIR



(Acme)

**Though there's nothing sinister about a radio set, various methods are constantly devised for secreting it. Here you have the armchair as the cache. The contraption was exhibited at the Los Angeles show.**

# PORTABLE UNIVERSAL for the Reception of Short Waves

By Frank Grimes and Herman Cosman  
Try-Mo Radio Corporation

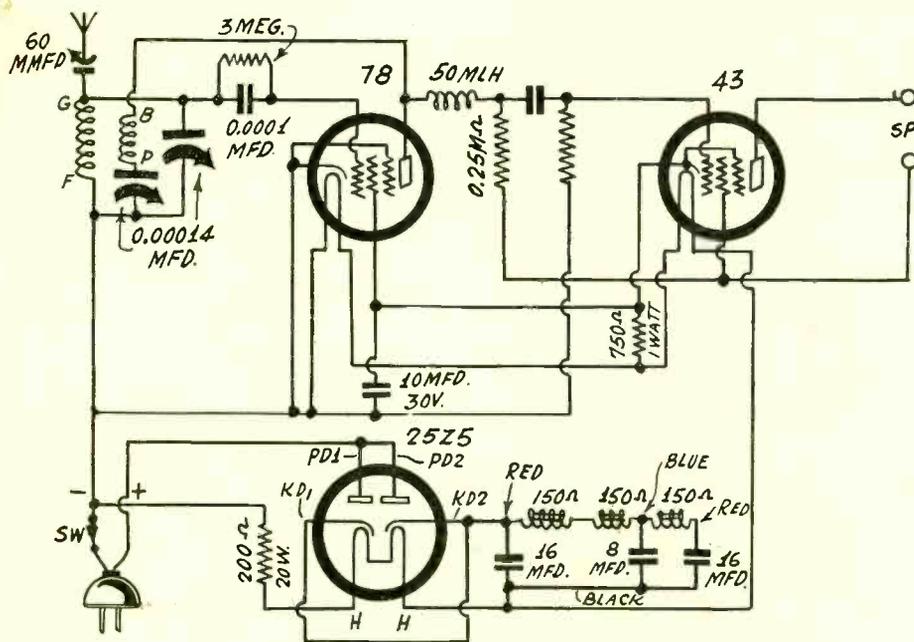


Diagram of a universal short-wave receiver, using plug-in coils. This set works on a. c. or d. c. and gives good performance in either instance. The choke coils in the B leg should be of low resistance, to hold up the voltage at the output, and in line with this voltage consideration the condenser next to the rectifier is 16 mfd.

**A**N earphone portable for short-wave reception, on a.c. or line d.c., requiring few parts, being simple to construct, and assuring good performance, is especially attractive at this time of the year, when week-end travelling is popular. Then as vacation time comes along, the short-wave enthusiast will like to take his set with him under the assurance that no matter if the places where he stays have a.c. or d.c. he still can tune in with delight. So the little receiver has several attractions.

The universality is of course due to the use of the 25Z5 as rectifier when a.c. is the supply, the tube being floated otherwise on the d.c. line. For d.c. the only use of the tube is for the d.c. resistance of its heater, as it can be seen that the line voltage in any case is reduced due to the drop in the 200-ohm, 20-watt series resistor, the resistance of the rectifier heater, and the resistances of the heaters of the two other tubes.

### The 78 as Detector

Of these two others, one, the 78, is the detector. In general this tube is classed as a remote cutoff radio-frequency amplifier, but it lends itself well to the grid leak type of detection, with cathode connected, as is suppressor, to ground. The plate load remains the same as in the instances of more formal uses, 250,000 ohms, and the voltage applied to the plate is the maximum obtainable, around 110 volts.

Since the total B current is only around 16 milliamperes, the three separate chokes in the positive B leg drop only 7.2 volts, and if 115 volts exist under a-c conditions, the d-c voltage may be even higher

than that, despite the small drop in the chokes, because of the voltage-lifting effect of the filter condensers. However, on line d-c the output voltage would be the difference, or 112.8 volts.

The 43 is the output tube, as it is one that possesses quite a kick. Remembering that the circuit is for earphone operation, the theoretical power output will be greater than that any normal earphones would stand. That is, the output tube can deliver 1 watt, or much more than what is at hand, a more acceptable condition.

### Foreign Reception

An output of 1 watt will give satisfactory speaker volume for a small room, and as some local short-wave stations will come in strong enough to be heard on a speaker, those who desire to hook up a magnetic speaker may do so for special reception purposes, although for the general run of reception, including foreign stations, earphone use is imperative.

The circuit is an improvement on one discussed recently, in that portability has been encompassed, and that the sensitivity has been increased by making the antenna series condenser variable from the front panel, instead of merely adjustable to one particular capacity setting at the rear.

The variation thus introduced is such that the effective capacity of the aerial is reduced as the series condenser is set to smaller capacity positions, and this often affords unconscious selection of half-wave and quarter-wave antenna conditions. Whatever may be the merits of the respective "measured" aeri-als, at least it is true that the regenerative effect is height-

## LIST OF PARTS

### Coils

One set of four two-winding short-wave plug-in coils  
One 50-millihenry radio frequency choke coil  
Three high-inductance filter chokes (about 30 henries each)

### Condensers

Two 140 mmfd. variable condensers (Hammarlund)  
One 60 mmfd. variable condenser (Hammarlund)  
One 0.0001 mfd. grid condenser  
One 0.01 mfd. stopping condenser  
One 10 mfd. by-pass condenser  
Three electrolytic condensers, two 16 mfd. and one 8 mfd., in one unit

### Resistors

One 3-megohm grid leak  
One 250,000-ohm coupling resistor  
One 0.5-megohm grid leak  
One 750-ohm bias resistor (one watt)  
One 200-ohm, 20-watt ballast resistor

### Other Requirements

Three six-contact sockets  
One four-contact socket  
One grid clip  
Two pairs of binding posts  
One line switch  
One slow motion dial  
Three knobs  
One Powertone metal chassis  
One six-foot chord with plug  
Two tube shields, large for 43 and one small for 78.  
One metal panel  
One wooden carrying case.

ened by decreasing the antenna coupling (using less series capacity), and thus regeneration is as assured even on the smallest coils for the highest frequencies.

So that there shall be regeneration it is necessary to hook up most standard coils so that the so-called B plus connection goes to plate and the P connection to the stator of the feedback condenser. The feedback winding is the one connected from plate to the stator of the left-hand 0.00014 mfd. condenser.

### Phase Reversal

The reason for this polarity is due to the phase reversal in the tube, and the normal construction of coils for inter-stage coupling rather than for regeneration. At all hazards, whatever coil you use, if oscillation can not be introduced one way it can the other, so reverse the connections either to the grid or the plate coil, but not to both. "Reversal" here means transposition of P and B or transposition of G and F.

Experiments were performed with various values of grid condenser and leak, and the final selection was for a combination of 0.0001 mfd. and 3 meg. The condenser is lower in capacity than ordinarily used for broadcast reception, because of the higher frequencies, and the consequent improved assistance to regeneration. Failure of regeneration always is accompanied by almost total collapse of performance, and therefore every precaution has been taken to insure regeneration

no matter which coil is plugged in, and also no matter what the frequency. So even if regeneration would tend to fail because of the trapping effect due to the natural period of the aerial in relationship to the frequency being received, again an adjustment of the series condenser (60 mmfd.) will correct for this.

The radio frequency choke coil should have a high inductance, and a value of 50 millihenries is specified, although higher inductance values may be used, particularly if the coil is of the honeycomb type of construction, or for any other reason has a low distributed capacity. If that distributed capacity is high, the choke will act as a condenser at the higher frequencies.

### Inductance Becomes Capacity

That gives rise to the point, raised occasionally before, that one has to regard a part as a condenser, inductor or resistor depending on its action at the frequency under consideration. Thus a coil may be a choke at a broadcast frequency, because of the relatively low frequency, yet the distributed capacity of the coil may be so high that as soon as one dips a bit into the short-wave band the capacity is large enough to bypass the otherwise inductance of the coil. And again, if d.c. were considered alone, the coil could be treated as a resistance only.

The 43 tube, used in the output, has an apparent bias of 12 volts negative, actually more. Since the cathode is elevated from ground by the sum of the voltages in this resistor and in the heater of the 78 tube, the total negative bias is 18.3 volts, approximately. Since the cathode of the 78 is grounded, and the screen voltage is tied to the cathode of the output tube, the screen actually gets 12 volts, which is sufficient, particularly so with detection.

Although only 750 ohms are placed between the 78 screen and ground, or cathode of the 43 and ground, so far as audio frequencies are concerned, this constitutes an imposing obstructive impedance to low frequencies, hence a large condenser bypasses this resistance. A capacity of 10 mfd. is obtainable in dry electrolytic form.

The filter condensers in the B supply also are electrolytics, in fact, are three condensers in one block, of which the two 16 mfd. elements have red outleads and the 8 mfd. unit has a blue outlead. The common black lead goes to negative. These condensers are dry.

In any use of the 25Z5 and its universal circuits, due regard must be paid to the polarity of the d.c. line voltage, though no precaution is necessary for a.c. In the diagram the positive and the negative are clearly marked. The connection of

the plug to the line should be in strict accordance with this designation, because the electrolytic condensers are endangered, and may be permanently ruined, if the line is connected the wrong way.

Perhaps the best method is to take a voltmeter or other indicator and determine the polarity at the convenience or wall outlet. Then mark the positive connection, either with a plus sign, or with a red dot. Then the plug should be similarly marked, and therefore when the plug is connected into the line, and the markings respected, there can not be that costly mistake. So, if the set is taken on outings, it is well to bring a voltmeter or other polarity indicator along, so that the wall outlets can be gauged.

It is noted that the negative is shown as the grounded side, and this normally obtains, but if positive is grounded, no change in the circuit need be made, so far as radio frequency returns are concerned, for the points along the filament circuits are at ground potential, to radio frequencies.

The coils used are those manufactured by the concern for which the designers work, and these coils follow the general pattern, except that the tickler windings are a little larger than ordinarily met, as proved necessary for the retention of regeneration at all frequencies.

### Regenerative System

The regeneration system consists of the parallel or shunt feed. The d. c. is fed to the plate through the resistor, while the choke differentiates the potentials, or enables the plate to be at a high r-f potential. Thus the high side may be fed back, as it is, through the throttle condenser. The operation depends in general on oscillation progressively damped by the throttle condenser to the degree of feedback just below oscillation, which is the most sensitive point of operation, the one meant by "regeneration."

Of course there should be no hum in a set like this, and that is the reason for including three separate chokes. The midsection has no bypass capacity across it, as when one was placed there it was found to constitute no advantage whatever.

The front cover illustration shows the appearance of the receiver, the diagram herewith shows the connections, and the list of parts sets forth the material necessary for construction.

In the diagram the designations in the rectifier tube have the following significance: PD1 is the plate of diode 1; PD2 is the plate of diode 2; KD1 is the cathode of diode 1, and KD2 is the cathode of diode 2.

Since not all readers will be familiar with the tubes used, particularly as all

three of them are rather new, the following note on the characteristics is given: **Seventy eight**—This is a super-control radio frequency amplifier, also useful as a detector with grid leak. The base is the small six-pin. Heater, 6.3 volts, at 0.3 ampere. The socket connections, bottom view, are right to left: heater, heater, plate, screen, suppressor, cathode. Grid is overhead cap.

**Forty three**.—This is a power amplifier, medium six-pin base, heater volts 25 at 0.3 ampere. The plate current is only around 20 ma, the negative bias not vertical, 12 to 20 volts. The mutual conductance is 2,300 micromhos, which is extremely high. The voltage amplification is 90, the ohms load 4,500 and the power output at voltages used is 1 watt. The socket connections, bottom view, beginning with right-hand heater, are right to left: heater, heater, plate, screen, grid, cathode.

**Twenty-five Z five**—This is a rectifier, used here in half-wave fashion, two plates paralleled. The socket connections are, bottom view, right to left: heater, heater, plate of diode 1, cathode of diode 1, cathode of diode 2, plate of diode 2.

## OUTPUT METER

In attempting to make some measurements of a set a man tried an a-c meter across the voice coil of a dynamic speaker, but did not get any deflection, although a strong signal had been coming through. However, he got some deflection across the primary of the output transformer (the voice coil is across the secondary of this transformer).

This is not unusual. The voltage is low at the voice coil, because of the large step-down ratio, primary to secondary. Besides, if you just put an a-c meter across the voice coil it is more than likely that it was one of those meters that draw immense current, a usual condition of the run of a-c meters, and therefore the voice coil was practically shorted when the attempted test was made. If you desire to make an output measurement it is essential that the d.c. be filtered out, leaving only a.c., to be measured by a sensitive a.c. meter, say, of the rectifier type. A paper condenser or paralleled paper condensers of a total of 10 mfd. may be connected, one side to plate, other side to meter, remaining meter terminal to cathode of the output tube. This method is best used when a non-inductive resistor is in the plate circuit, of a value equal to the recommended ohms load for the tube, as derived from tube characteristics charts. When these conditions are imposed, the circumstances are favorable to an expert measurement, as there would be negligible shunt admittance and negligible series impedance.

# Short Waves to Originate in Stratosphere

Plans for the first American flight into the stratosphere, which will carry National Broadcasting Company microphones into new territory, are progressing rapidly following a meeting in Chicago of the principals in the venture.

Some of the most noted figures in science and aviation conferred on the proposed ascent, which is scheduled to be made from the Century of Progress on or about July 1st, under the supervision of the Piccard brothers, Auguste and Jean, one of whom will be official observer in the balloon. Auguste now holds the altitude record of more than ten miles, made in Switzerland last year.

### Conferees Listed

Among the men who attended the meeting in Chicago, the first in which all the chief figures in the undertaking were gathered together, were the following:

Lieutenant Commander T. G. W. Settle,

U. S. N., who will pilot the balloon; Dr. Arthur Compton, professor of physics at the University of Chicago; Jean Piccard; Dr. Irving Muskat, representing the Century of Progress; W. C. Young, manager of the aeronautics department of the Goodyear Tire and Rubber Company, builders of the balloon; E. H. Perkins of the Dow Chemical Company, makers of the Gondola; R. M. Morris, research engineer of the National Broadcasting Company; J. I. Banish, president of the National Safety Council and consulting engineer of the Union Carbide and Carbon Company which will furnish the gas, and Major Ray Cooper, of the National Aeronautical Association, who will represent the N. A. A. in the matter of official altitude records.

### S-W Set in Gondola

When Piccard made his record ascent in Switzerland he carried no radio transmitter,

confining himself to speaking over networks in international broadcasts just before taking off and just after landing. This time however, special short-wave equipment will be carried in the gondola, so that its occupants can speak to millions of listeners over NBC networks as they ride high in the stratosphere.




Short-wave enthusiasts are awaiting the event with interest, because of the data on the effectiveness of transmission from enormous altitudes.

### A THOUGHT FOR THE WEEK

"**R**ADIO WORLD is not a luxury—it's of service to its readers." Thus write many newsstand and subscription purchasers of our paper and we believe this explains why thousands of readers continue to renew their subscriptions year after year without a break. RADIO WORLD will continue its policy of service!

# 25Z5 VOLTAGE GAIN

## Separate Load Circuits Improve Output

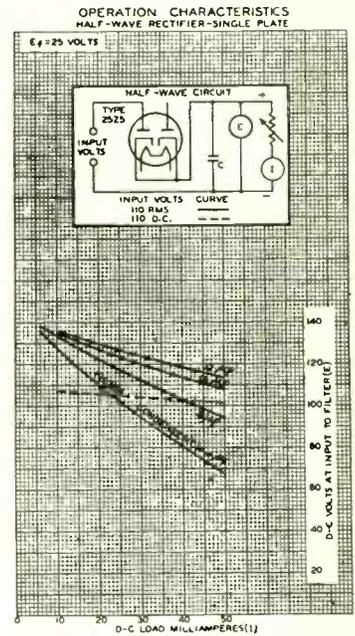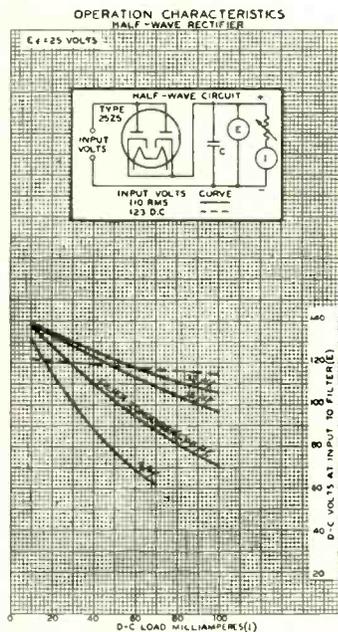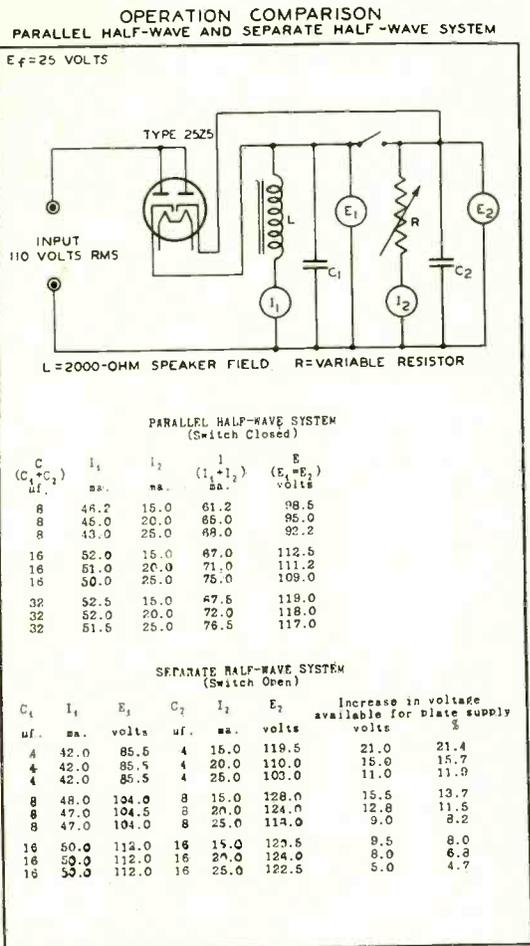

**Circuit for testing 25Z5 for parallel and separate half-wave rectification. At right are the identified performance curves.**

output from small receivers is desirable in that more pleasing tone quality usually accompanies the higher output capability.

The circuit arrangement used in making these tests is shown in diagram at left. In this case, a 2,000-ohm speaker field was used as the load on one unit of the 25Z5; a variable resistance provided an adjustable load for the other unit.

This circuit arrangement of the 25Z5 necessitates the use of an additional filter condenser, or a two-section unit-condenser. However, the advantages which can be derived from the increased voltage available for plate supply should more than offset the cost of the additional filter condenser, or of the two-section unit-condenser.

### Reduced Hum

Another consideration of interest is the hum introduced in the speaker by the ripple present in the field-supply voltage. Tests have been shown that this hum can be reduced to a very low level by the use of a loud speaker employing a suitable hum-eliminating device. The extra cost of such a speaker is about 5 cents or less. If a condenser is used to remove the hum, a capacity of at least 24 mfd. is necessary to reduce the hum level to a satisfactory value. The cost of such a condenser may be prohibitive. It has been found that a suitable device on the speaker will reduce the hum to a level comparable with that obtained using a 32 mfd. condenser in the filter.

—From E. T. Cunningham, Inc., and RCA Radiotron Co.

### APPLICATION NOTE ON RECOMMENDED OPERATING CONDITIONS FOR THE 38, 41, 42, 43, AND 89

**B**ECAUSE of the relatively low signal-voltage input required for high power-outputs, the power-amplifier pentode is particularly suited for use in the output stage of small receivers. In making a selection of the type of power-amplifier pentode to be used in any given application, the signal voltage delivered to the output tube, the plate-supply voltage, and power-output requirements must be considered.

(Continued on next page)

**S**MALL receivers, particularly those of the transformerless universal type, are limited to a great extent in their performance capabilities by the low plate-supply voltages available. For example, an increase of only a few volts in the applied plate voltage will appreciably raise the power output of a 43 with a corresponding improvement in tone quality. Consequently, a satisfactory means of increasing the available plate-supply voltage can be translated by the engineer designing such equipment into improved performance.

When the plate-current drain of all the tubes in a set is less than the speaker field current, a means of increasing the available d-c voltage in small receivers employing an electro-dynamic speaker is utilization of each rectifying unit of the 25Z5 to supply a separate load circuit.

### Increased D-C Voltage

Each unit of the 25Z5 can be operated independently of the other, provided the regulation of the supply voltage is good. Since the rating of the 25Z5 is 100 ma., each half of the tube can handle 50 ma. Thus, it is possible to energize the dynamic speaker from one plate and its cathode of the 25Z5, and to supply plate voltage to the tubes in the receiver from the other unit. The current drain on each unit, with such an arrangement in most small receiver designs will not exceed the allowable 50 ma. Furthermore, with this arrangement, a reduction in ripple voltage is obtainable with the same total filter-condenser capacity.

Tests have been conducted to determine the increase in d-c voltage available for plate supply with this arrangement over the volt-

age available when the plates of the 25Z5 are operated in parallel. The results, as tabulated, together with the attached curves showing the operating characteristics of the 25Z5 with the plates and cathodes paralleled, and with each plate and its cathode operated individually, reveal that a material increase in available voltage may be obtained with the two units of the rectifier operated individually.

Taking the case of a five-tube superheterodyne (employing two 36's, one 39, one 43 and one 25Z5), as an example, the plate and screen current drain for these tubes will be approximately 32 ma. The speaker field will draw approximately 45 ma. With two units of the 25Z5 operated in parallel, the total current to be supplied is 77 ma. With the units operated separately, one plate must supply 32 ma. for the plates of the tubes, and the other 45 ma. for the speaker field.

### Gain of 8 Volts

Assume that with the plates operated in parallel a 16 mfd. condenser is used in the filter and with the separate operation two 8 mfd. condensers, one for each plate, are used. Then, referring to the operation characteristic curves for each condition, it will be seen that the voltage input to the filter will be 102 volts with the plates operated in parallel, and 110 volts with the plates operated individually. This is a gain of 8 volts in available plate-supply voltage.

While this increase in available plate voltage gives noticeable improvement in the operation of the 36's and the 39, the 43 derives the greatest benefit. An 8-volt increase on the plate of the 43 will raise the power output approximately 20 per cent. Increased

# A 6-TUBE BATTERY SET

## T-R-F Receiver Using the 2-Volt Tubes

By Einar Andrews

THOSE living in the country or other places where there is no electric service have been neglected when it comes to radio receivers. The reason is that there are relatively few of them. Yet numerically there are many who cannot use a-c sets or even line d-c sets. Indeed, there are more who have no electric power available than those who have only d-c, but they have not been so insistent about getting circuits to build.

Here is a six-tube t-r-f receiver with which these fellows can try their skill. It is sensitive, selective enough for places where it is likely to be used, and is quite economical in operation. Besides, it has output enough to operate a good magnetic loudspeaker or a permanent field dynamic.

### The Filament Circuit

Five of the tubes in the circuit require 0.06 ampere each at two volts and the sixth tube requires 0.26 ampere at the same voltage. Therefore the total current will be 0.56 ampere. A No. 6 dry cell will deliver about 0.25 ampere. Therefore at least three of them should be connected in parallel. Since each cell has a voltage of 1.5 volts, and the tubes require two volts, there should be two cells in series. Hence the filament battery should be made up of six No. 6 dry cells, three in parallel and two such groups in series. For occasional service four cells would be all right.

A 15-ohm resistance is connected in the negative leg of each of the tubes drawing

0.06 ampere. For the power tube, which draws 0.26 ampere, the filament ballast is 4 ohms. As a means of adjusting the filament voltage more closely and to save current when the full current is not needed, a 6-ohm rheostat is put in the common positive lead. This filament switch should be attached to this rheostat as a means of simplifying the assembly and to result in a symmetrical panel layout.

### Grid Bias

The three r-f amplifiers are biased by the drop in the 15-ohm ballast resistors. This bias is approximately one volt. If it is desired to increase this bias, and thus to reduce the drain from the B battery and make the circuit more stable, the grids should be returned to a suitable point on the grid voltage battery. In order to make this possible and at the same time leave the rotors of the tuning condensers grounded, each of the r-f grid returns should be treated in the same manner as the grid return of the detector. That is, a condenser of 0.1 mfd. is connected between ground and the coil, and the coil is then connected to the grid bias. Three more condensers of 0.1 mfd. would be required if. While only one such condenser is required absolutely, it is well to use one for each circuit in order to minimize feedback. Using three condensers permits placing them so that the leads are short.

The suggested bias for the 230 detector is 9 volts. This, however, is subject to

variation. If the grid bias battery has a tap at every cell different bias values should be tried and that retained which gives the greatest detecting efficiency. The bias on the 230 audio amplifier is 4.5 volts, which is the recommended value for a plate voltage of 90 volts. The bias on the 233 power tube is 13.5 volts, which is the recommended value when the plate and screen voltage is 135 volts.

### Plate Voltages

The voltage on the plates of all the tubes with the exception of the 230s is 135 volts. The plate voltage on the detector is 67½ volts, which is the same as the screen voltage on all the radio frequency amplifier tubes. The voltage on the plate of the 230 audio amplifier is only 90 volts, which is sufficient when the tube precedes a high gain tube like the 233.

The total plate and screen current drawn by the set is 31.5 milliamperes. That is the current when the filament, grid, and plate voltages are normal. Normal grid bias for the 34 tubes is 3 volts. This current is not very large for a six-tube set, and it can be supplied by a dry cell B battery of medium size. Of course, if the set is to be used much, it is better to use large size B batteries because they are more economical.

When the set is used as a portable, and it is quite suitable for that, small B batteries should be used as a matter of convenience, for even when light batteries are

(Continued on next page)

## How to Voltage the 38, 41, 42, 43 and 89

(Continued from preceding page)

The maximum allowable peak signal-voltage input to a power-amplifier pentode is equal to the applied bias voltage. Consequently, the bias voltage is an indication of the signal required to give full output.

Typical recommended operating conditions for the 38, 41, 42, and 89 at 100, 135, 180, and 250 plate volts are shown in the tabulation. Recommended operating conditions for the 43 at 100 and 135 plate volts are also included.

The 41 has only recently been approved for operation at 250 plate volts. This increased voltage rating, with the resulting increase in power output, makes this tube particularly attractive for automobile receiver applications.

The 41 and 42, in comparison with the 38, 43, and 89, require the smallest input-signal voltage to give full output. The power output is approximately the same as that of the 89 operated as a pentode, according to RCA Radiotron Co., Inc., and E. T. Cunningham, Inc.

The 38 requires a relatively low value of input signal, but gives a low value of power output compared to the other types. However, the plate-current requirements of the 38 are very moderate.

The 43 gives much greater power output than any of the other types shown, but it requires a relatively large input signal. Naturally, the plate current requirements of the 43 are large compared to those of the other types.

The importance of utilizing the maximum plate supply voltages available is indicated by the tabulation. It will be noted that the power output for all types shown at 135 plate volts is approximately double the power output at 100 plate volts. Thus, an

| Tube Type                          | Grid Volts | Screen Milliamp. | Plate Milliamp. | Load Resistance Ohms | Max. Allowable Grid Resistor Megohms | Harmonic Distortion Percent | Power Output Watts |
|------------------------------------|------------|------------------|-----------------|----------------------|--------------------------------------|-----------------------------|--------------------|
| <b>PLATE AND SCREEN VOLTS=100</b>  |            |                  |                 |                      |                                      |                             |                    |
| 38                                 | -9.0       | 1.2              | 6.8             | 15,000               | 1.00                                 | 8.0                         | 0.27               |
| 41                                 | -7.0       | 1.6              | 9.0             | 12,000               | .25                                  | 10.0                        | 0.33               |
| 42                                 | -6.5       | 1.8              | 10.0            | 11,000               | .25                                  | 7.0                         | 0.34               |
| 43                                 | -15.0      | 4.0              | 20.0            | 4,500                | .25                                  | 11.0                        | 0.90               |
| 89*                                | -10.0      | 1.6              | 9.5             | 10,700               | .25                                  | 10.0                        | 0.38               |
| <b>PLATE AND SCREEN VOLTS=135</b>  |            |                  |                 |                      |                                      |                             |                    |
| 38                                 | -13.5      | 1.5              | 9.0             | 13,500               | 1.00                                 | 10.0                        | 0.55               |
| 41                                 | -9.0       | 2.2              | 12.5            | 10,400               | .25                                  | 10.0                        | 0.75               |
| 42                                 | -9.0       | 2.6              | 14.5            | 9,600                | .25                                  | 7.0                         | 0.75               |
| 43                                 | -20.0      | 7.0              | 34.0            | 4,000                | .25                                  | 9.0                         | 2.00               |
| 89*                                | -13.5      | 2.2              | 14.0            | 9,200                | .25                                  | 10.0                        | 0.75               |
| <b>PLATE AND SCREEN VOLTS=180</b>  |            |                  |                 |                      |                                      |                             |                    |
| 38                                 | -18.0      | 2.4              | 14.0            | 11,600               | .25                                  | 8.0                         | 1.00               |
| 41                                 | -13.5      | 3.0              | 18.5            | 9,000                | .25                                  | 10.0                        | 1.50               |
| 42                                 | -12.0      | 4.0              | 21.0            | 8,250                | .25                                  | 7.0                         | 1.50               |
| 89*                                | -18.0      | 3.0              | 20.0            | 8,000                | .25                                  | 10.0                        | 1.50               |
| <b>PLATE AND SCREEN VOLTS= 250</b> |            |                  |                 |                      |                                      |                             |                    |
| 38                                 | -25.0      | 3.8              | 22.0            | 10,000               | .25                                  | 8.0                         | 2.50               |
| 41                                 | -18.0      | 5.5              | 32.0            | 7,600                | .25                                  | 10.0                        | 3.40               |
| 42                                 | -16.5      | 6.5              | 34.0            | 7,000                | .25                                  | 7.0                         | 3.00               |
| 89*                                | -25.0      | 5.5              | 32.0            | 6,750                | .25                                  | 10.0                        | 3.40               |

\*As a pentode.

increase of only 35 plate volts allows twice the power output from a set. Even small increases in plate voltages, particularly in small universal receivers, produce noticeable improvements in power output.

In the same way, the increase in plate voltage from 135 to 180 volts approximately doubles the power output, and the increase from 180 to 250 plate volts again doubles

the power output. Consequently, approximately eight times the power output is available with 250 plate volts as with 100 volts. Of course, the plate-current requirements rise with the plate voltages. The distortion, for a given type, remains approximately constant. The input signal required for full output rises in proportion with the higher plate and higher bias voltage.




# AN AUTHENTICATED ANALYZER

By William F. Peck  
Peck Television Corporation

MANY who have a meter, multiplier and shunt resistors, and some other parts, figure that they could build a nice set analyzer if given some preliminary directions, and therefore the present device represents the fulfillment of the purpose. The object is to make the essential tests of set circuits, as to voltage and current readings. Those who like to make resistance tests, too, may include the limiting resistor and battery in each of the two positions between the open switch points at lower right of the diagram and the common line to the left below. The author did not include any resistance measuring method because he has a separate resistance meter.



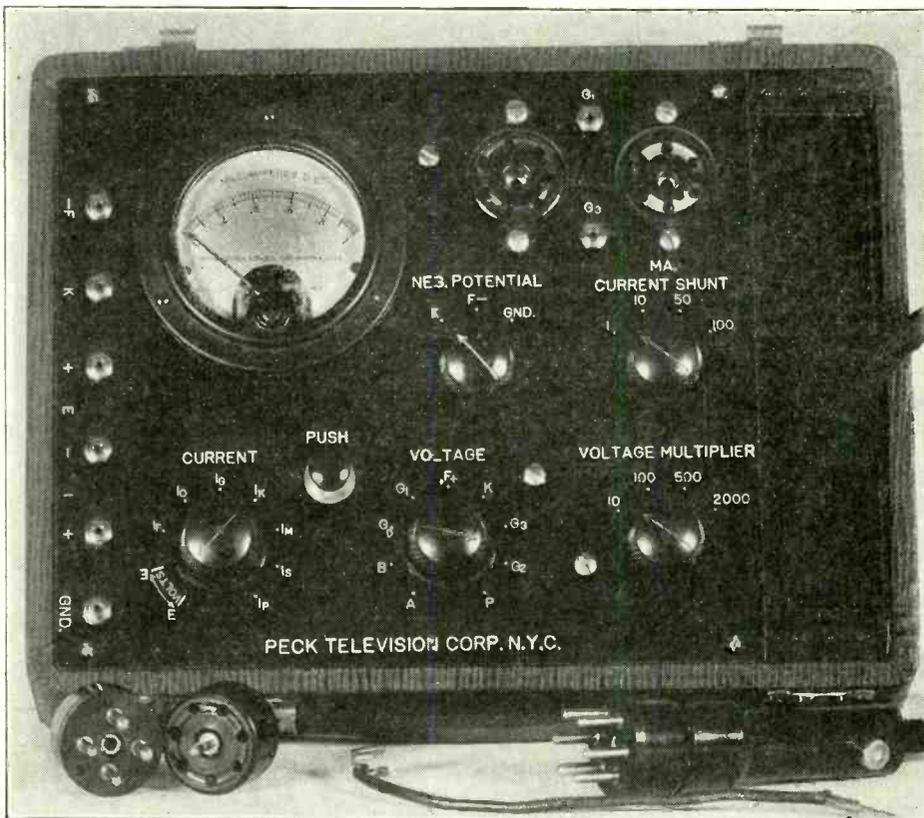Above the author is shown holding the analyzer. At right is the view of the panel top. The analyzer plug is shown in right foreground, while two adapters are also in view.



The principal switch used is one that may be put to any one of nine different positions, and due to the almost complete encompassing of the circle, it is hard to show the switch in physical diagram. However, it should not be hard to visualize the switch. It consists of two sections, simultaneously operated. One section, for each position, is a double-pole switch that picks up the meter, by virtue of the contacts by the two-bladed slider SL. To this extent it is a nine-pole double-throw switch. The simultaneous action of the other section is to open a circuit. Thus as the first section discussed closes a circuit, and the second opens a circuit, the switch enables opening a circuit to insert something in it, i.e., the meter. This is just the condition wanted for current readings, when, for instance, the plate

lead has to be interrupted, the meter put between, and yet the plate lead rendered continuous again the moment some other switch position is utilized. If the opening and closing sections are put in parallel, this is accomplished.

### Overhead Grid Lead

Looking at the diagram, we find that a circle in the form of a socket, with colored leads marked thereon. Actually this represents the bottom view of the plug. From this analyzer plug emerge eight leads. Seven have corresponding pin connections, as shown, but the eighth connects to the eighth lead (green) and is continuous with the two grid caps on the plug. Hence it is the lead for picking up the overhead grids.

Therefore one end of the cable has plug

attached, for insertion in the receiver socket. The colored leads are soldered by the constructor to the analyzer end, or tester, not at either of the two sockets in the tester, but to the lines between switches.

Now, the main switch's functions are diagramed above and below the "plug bottom view," the lower oblong enclosing eighteen dots representing switch lugs, the upper oblong enclosing nine crosses, representing also 18 switch points or nine closed circuits which are pried open by the circuit opener CO. On the switch the two front lugs are for the closing switch (SL).

The two rear lugs are for the opening switch (CO). Hence, front to rear, the second and third lugs in line may be joined together and the front and rear

(Continued on next page)

## Six-Tube Battery-Operated Receiver

(Continued from preceding page)

be necessary in a circuit of this type when it is powered with batteries.

### Terminals

If the batteries are not built into the cabinet, a cable containing the necessary terminal leads should be used. Eight leads are shown in the diagram, three for bias, three for plate voltage, and two for the A battery. The A minus lead should also be used for B minus and C plus. If the bias on the r-f tubes is to be increased as has been suggested, there should be another

lead for the r-f grid bias. The three grid returns are joined together before the lead is brought out. It may be convenient to place the grid battery in the cabinet, in which case all the grid return leads need not be included in the cable. This simplifies the set a great deal.

One binding post should be provided for the antenna and another for the ground connection. There should also be two terminals for the loudspeaker. There are twin terminals available for these purposes, suitably marked, and they are preferable to simple binding posts.

### Layout

The circuit should be built around the three-gang condenser. Its dial should be placed in the center of the front panel and the two other variables, the potentiometer and the rheostat, should be placed symmetrically with respect to the condenser dial and near the bottom of the chassis. Suitable six-tube chassis with panels to match are available. But there is no reason why the circuit should not be built on some other chassis for an extra tube socket makes no difference.

(Continued from preceding page)  
 lugs in line joined together, except that two of the circuit-opening positions are not used (and so marked), while the cathode connection on the closing device is reversed, to give positive reading. The last two closing positions are for meter reversal.

**Range-Increasing Purposes**

Now let us see the sequence of operation so far.

We have a receiver operating. We have a plug and cable. The plug is inserted in the socket of the receiver that is to have that circuit tested. The voltages and currents are thus brought up to the tester, into which the tube removed from the set is put, hence switching must take place between the voltage and current feed and the tube, that is, for current indications the meter is put in series with the measured circuits, while voltage readings may be taken also. See the lower left oblong, under E, which puts the circuit in voltage-reading position, an extra switch at right picking up the desired circuits for such voltage reading, with an independent switch for selecting the proper series multiplier.

We need not only series multipliers, for correct range, but for current readings we need shunt multipliers, and these will be on the basis of the meter used. Assuming a 0-1 milliammeter, which will afford in all instance a voltmeter of 1,000 ohms per volt rating, the multipliers would be 1,000 ohms for every volt; hence, for 0-10 volts, 10,000 ohms, for 0-100 volts, 100,000 ohms, and for 0-1,000 volts, 1,000,000 ohms. Such resistors should be accurate, and the usual wire-wound series multiplier resistors should be used.


**Making a Shunt**


The voltage ranges may be such as you desire, depending on the usual ranges you expect to encounter. So also of the shunts. While the meter itself reads 0-1 milliamperes, infrequently the current is that low, and if three shunts are used they may be for 0-10 milliamperes, 0-50 milliamperes, and 0-100 milliamperes. These selections are left to the constructor, and if he hasn't the necessary shunts, but can get an accurate meter within range, he can make his own shunts by using No. 26 wire or so, winding it around a pencil, and using so much wire as will make his meter read what it should on the basis of the current through the primary meter. Any one point selected will suffice, say, if 50 ma are registered on the primary meter, then the shunt may be adjusted to cause the needle on analyzer meter to read 50 ma, or half position, whereupon full-scale deflection for the analyzer meter would be 100 ma. Or current shunts may be purchased, on the basis of the known resistance of the meter movement. This resistance, indeed the very shunts, may be obtained from the meter manufacturer.

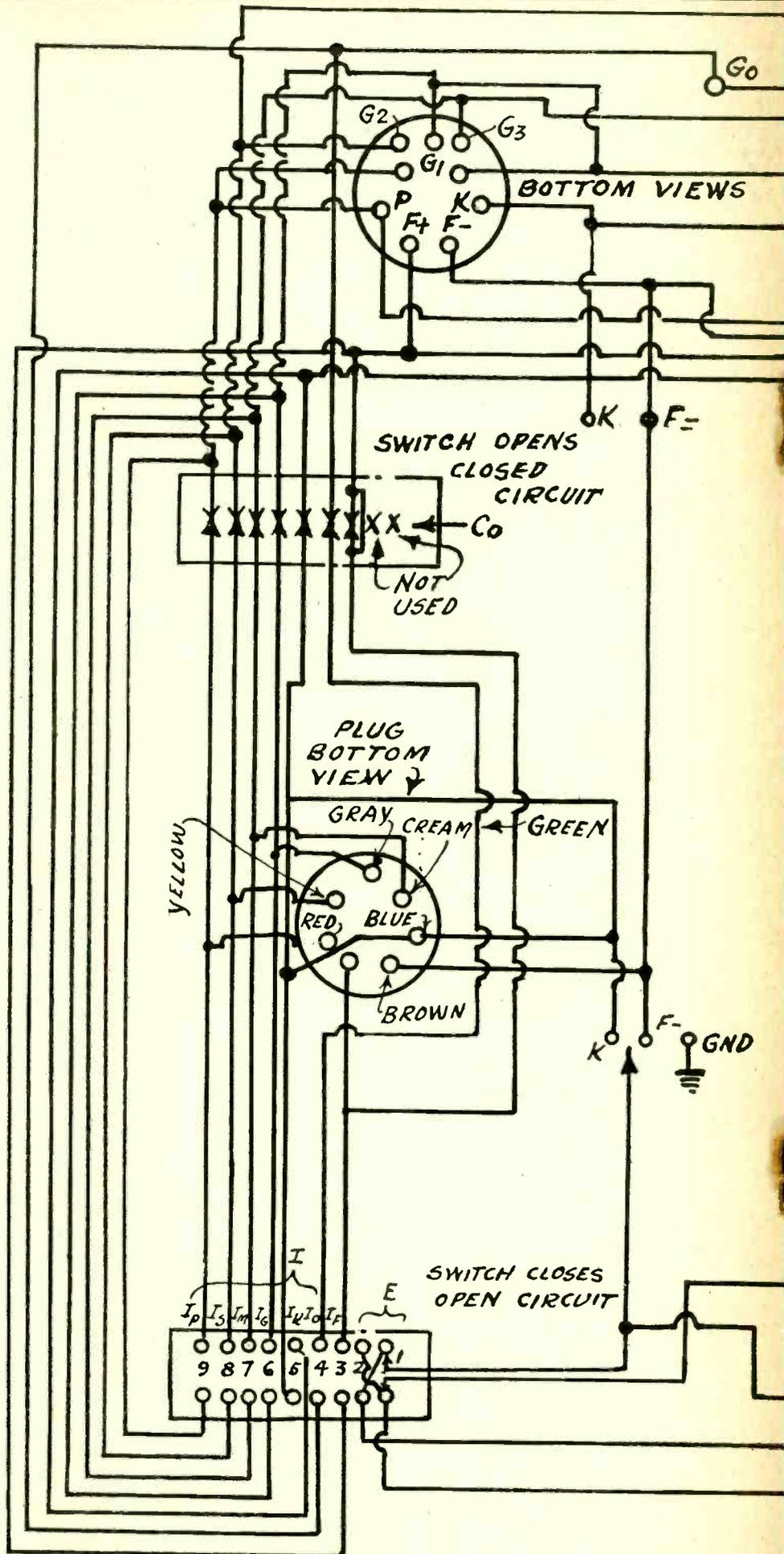**Currents Grouped**

The currents read are grouped under I in the lower oblong, the voltage position for the meter is either obverse or reverse, for the last two (right-hand) positions, and, as stated, a separate switch is manipulated to pick up the correct multipliers, still another for current shunts, and another for to pick up the points between which and, say, B minus, readings are to be taken.

It is usual to read to B minus, as this is always accessible, but this is not necessarily the most desirable datum. Suppose that you desire to read from cathode, which in heater type tubes is the datum.



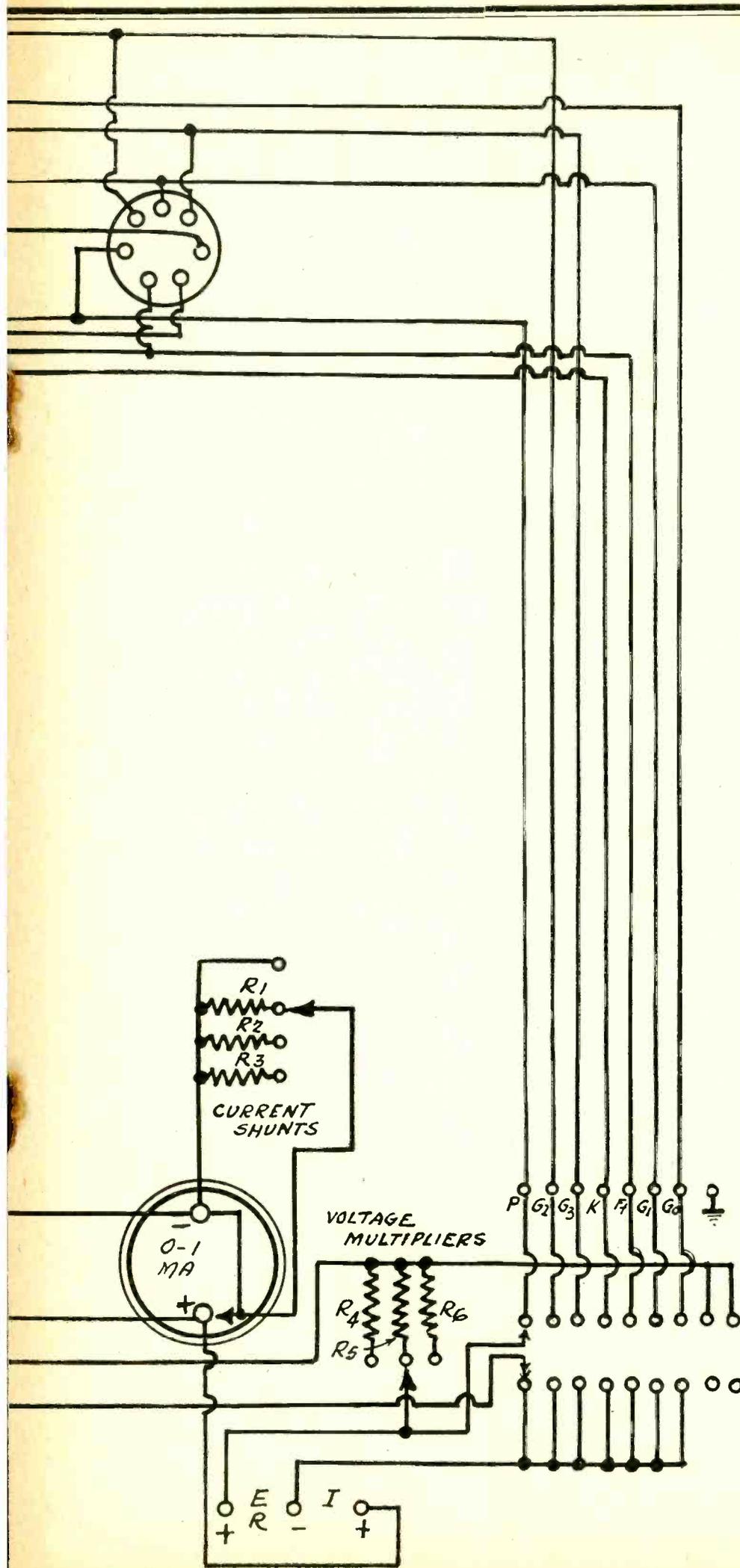

It is then necessary to pick up cathode as one side, and, say, plate as the other. The plate voltage is not that between ground or B minus and plate but between cathode and plate. Suppose that you are testing a battery set where ground may not be the same as B minus, as, for instance, C minus may be grounded. To take care of these three conditions a separate switch is used for picking up K, F minus and ground. K will seldom be B minus, an exception being the case of a 2A5 or other type of power tube with biasing resistor in the negative leg of the rectifier, e. g., tap on a B choke. F minus normally will be B minus in battery sets and in a-c sets where the tube is of the filamentary type. Ground is a point in reference to which numerous readings may be desired, nevertheless normally this would be chassis, and a tester will pick up only the socket connections, none of which may be grounded. Hence a binding post is advisable, and a lead is run from that to chassis, and ground continuity is established.

**The 2B7 and 2A7**

The tester has two sockets, one of the so-called universal type, which, without possibility of error, receives the UX, UY and six-pin base tubes. For the seven-pin-base tube (medium size) the extra socket is used, and connections made from one socket to the other as shown. This medium-sized base for seven pins takes care of the 59, but not of the 2B7 and the 2A7, which require a smaller size, but there are two adapters to take care of this, one to reduce the larger 7-pin socket on the tester the smaller one required, and the other to increase the 7-pin socket in the set to the larger requirement, that of the plug.

**Adapters**

Since the analyzer plug has only one terminal condition, equal to medium-sized seven pin, naturally this plug will not fit into any kind of socket except the very one for which it was intended. Hence adapters are used, and it is fortunate that the adaptation is downward, that is, from a more numerous pin base to a fewer-sprung socket. Hence to use the plug with a six-pin socket, an adapter of the medium seven-hole top is used, to receive the plug, while the bottom of the adapter has six pins. A special locking device prevents the adapter from sticking in the set when the plug is pulled out. A latch must be sprung to release the plug from the adapter.


The designations on the main switch diagram, lower oblong, are: Ip for plate current; Is for screen current; Iu for suppressor current; Ig for grid current; Ik for cathode current; Io for overhead grid current; If for heater or filament current. Since filament or heater current is large, and the meter normally wouldn't read it, the circuit-opening element above is shorted to protect the meter. This may be a permanent short if filament or heater current readings are to be neglected, as they usually are, or may be a short that is opened only by depressing a key.

**The Confusing Grid Numerology**

Ig, for grid current, relates to whatever element occupies the normal control grid position for four-pin tubes, or 227 tube, but of course in the case of the 235 the socket position that would be the control grid in the case of the 227 is the screen grid. For this reason, and other reasons, the numerical grid designations are not consistent, the main reason being that they are not so in the formal numerology  
(Continued on next page)

# Detailed Construction Data on the 8-TUBE DIAMOND

By Herman Bernard

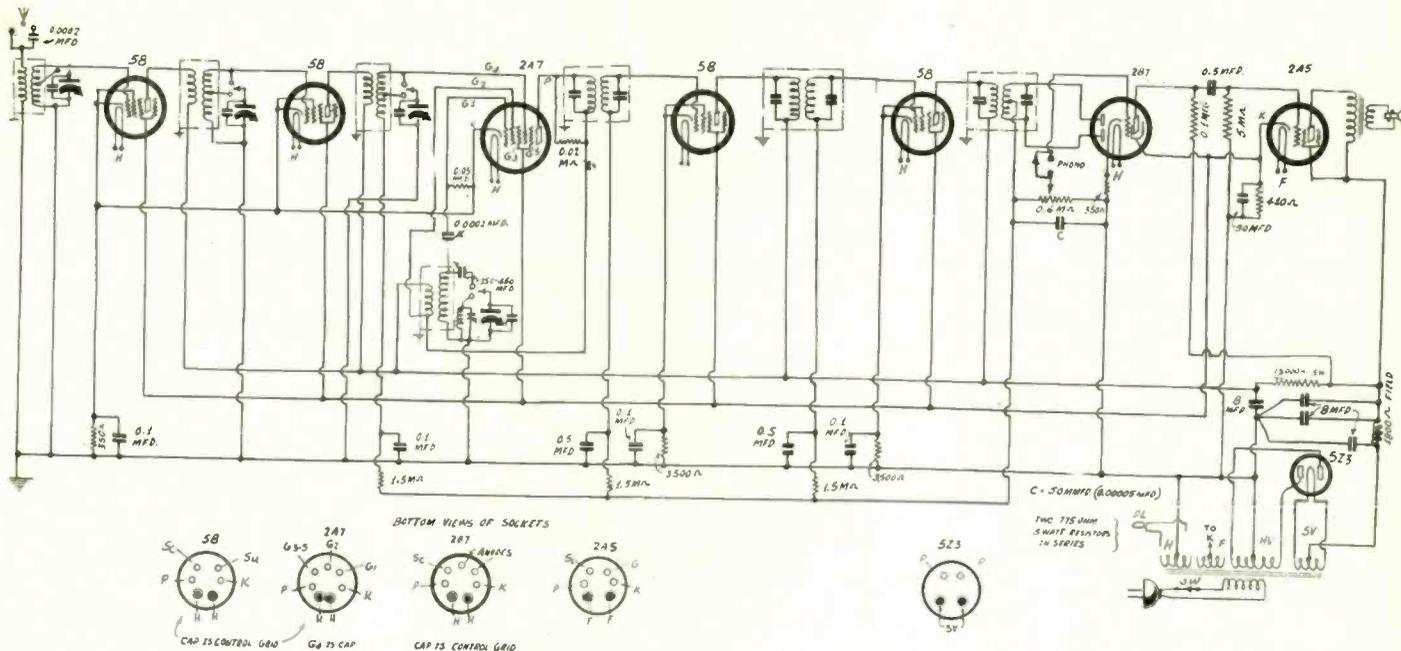

## LIST OF PARTS

**Coils**

Three shielded radio frequency transformers, secondary tapped for 1,400-4,500 kc. One shielded oscillator coil, three windings, separate one for 1,565-4,965 kc.

Two shielded Hammarlund intermediate transformers, air - dielectric - condenser tuned, both as to primary and secondary; 465 kc.

One shielded Hammarlund intermediate transformer, air - dielectric - condenser tuned, both as to primary and secondary; secondary center-tapped; 465 kc.

One 90-watt power transformer; primary, 115 volts, 50-60 cycles; secondaries: (H), 2.5 volts, 8 amperes, center-tapped, for heaters; (F), 2.5 volts, 3 amperes, center-tapped, for power tubes; (c), 5 volts, 3 amperes, center-tapped, for rectifier; (d), 750-volt center-tapped for high voltage of full-wave rectifier; stands 150 ma (@) 400 volts d.c.

One dynamic speaker, 12 inch diameter; 1,800-ohm or higher resistance field, output transformer for 2A3 tube. Cable and plug attached.

**Condensers**

One four gang 0.00041 mfd. tuning condenser with trimmers built in; shaft  $\frac{3}{8}$ -inch diameter,  $1\frac{1}{2}$ -inches long.

One padding condenser, 350-450 mmfd.

One midget variable condenser, not more than 50 mmfd.

One 50 mmfd. mica fixed condenser.

Two 0.0002 mfd. mica grid condensers.

One 0.5 mfd. stopping condenser.

Six 0.1 mfd. bypass condensers.

Four 8 mfd. electrolytic condensers (two in each of two cases).

Two 20 mfd. electrolytic condensers.

**Resistors**

One 350-ohm pigtail resistor.

Two 775-ohm 5-watt pigtail resistors, wire-wound.

Two 3,500-ohm pigtail resistors.

One 15,000-ohm 5-watt pigtail resistor, wire-wound.

One 20,000-ohm pigtail resistor.

Two 50,000-ohm pigtail resistors.

One 100,000-ohm pigtail resistor.

Three 1.5-meg. pigtail resistors.

One 0.6 meg. potentiometer with switch attached.

One 5-meg. pigtail resistor.

**Other Requirements**

One five-pole, double-throw switch insulated shaft type.

Six grid clips.

Nine sockets: four six-hole, one five-hole (UY), two four-hole (UX), two 7-hole medium. The extra UY socket is for speaker plug.

Six tube shields and bases.

One a-c cable and plug.

One antenna-ground binding post assembly.

One phonograph twin jack.

One vernier dial, traveling light type, with pilot lamp and escutcheon.

Length of flexible wire for pilot lamp connections.

One roll of hookup wire.

Four 12/24 nuts for power transformer.

Three dozen 6/32 nuts and bolts.

One a-c cable bracket with lug affixed.

Three knobs.

One chassis 15 x 3 x 10 inches.

One metal bottom piece to fit chassis.

Six insulated bushings tapped at both ends for 6/32 screws.

Six lugs.

One 6/32 bolt,  $1\frac{1}{2}$  inches long, for wave switch.


One a-c cable bracket with lugs affixed.

Three knobs.

Tubes: four 58's, one 2A7, one 2B7, one 2A3 and one 5Z3.

condenser is put across this winding.

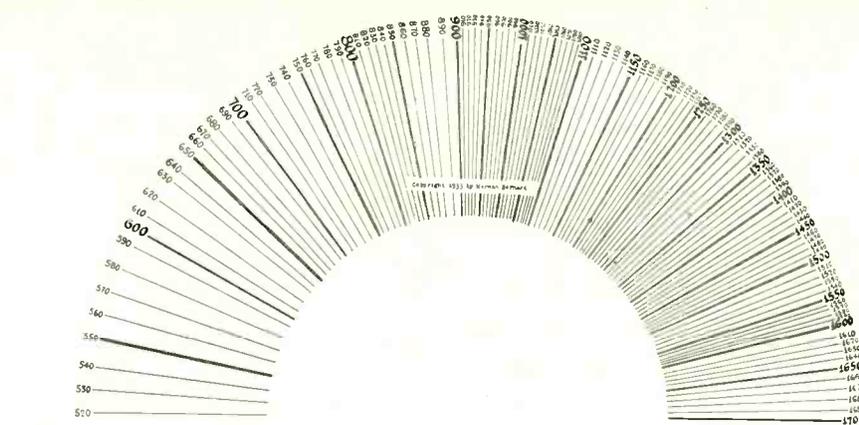The receiver is primarily intended for broadcast reception, and the police band is purely incidental. Nevertheless, since an improvement is achieved by the change, it



Calibration of frequencies tuned in on the broadcast band, with 20 kc overlap at the low-frequency end and 200 kc overlap at the high frequency end. Each of 119 channels is located.

is well to adopt it. Moreover, while it is better to have a smaller and more selective input for the broadcast frequencies, a larger input is advisable for the short waves, where the selectivity doesn't matter so much.

Due to difficulty in padding for short waves by the usual method, most receivers omit padding, although in this instance at least inductive padding is introduced. Much greater sensitivity results when the little manual tuning condenser acts as trimmer for the main tuning condenser of the oscillator, which on the police band isn't padded. The capacity may be up to 50 mmfd., although less would be sufficient, say, 30 mmfd. The usual 50 mmfd. condenser has seven plates.

The circuit then is keenly alive all over the dial when the switch is turned for short waves, although the points at which particular police transmitters come in best must be borne in mind, and calibration will hold, to the extent that when you desire to tune in the station again, turn to the same dial position, and then very slowly adjust the manual trimmer.

**Careful Tuning Needed**

It should be remembered the usual closeness of tuning is, if anything, magnified by the considerable selection ahead of the oscillator, and at least the same patient, careful tuning is required as for any other short-wave reception in this wide band (1,400-4,500 kc).

There are no dead spots on the dial anywhere—on broadcast or short waves.

The diagram for connecting up the coils, including the oscillator in the improved fashion, will be found on the circuit of the 12-tube model.

The intermediate frequency transformers, made by Hammarlund, are peaked at the factory at 465 kc, but when put into a set there would be naturally a slightly different frequency. However, those who desire to build the 8-tube set and have no test oscillator, may leave the first transformer as it is, and peak the remaining transformers on that basis, to give loudest output after the set is built. This is not the best plan in the world, but it will do in a pinch.

The transformers without center-tapped secondary, of which there are two, have grid cap lead emerging from side of the shield, while underneath these are two flexible leads and a brass projector. The B plus connection is made to the projector, the green flexible lead goes to plate of preceding tube while the black is the grid return and, in this circuit, connects to the potentiometer through a bypassed high resistance.

**Speaker Considerations**

The center-tapped transformer feeds the 2B7 and has the same primary connections (green and projector), while the two black leads go to the diode anodes and black is the return or center-tap, connected to the high side of the potentiometer.

The power transformer has all secondary

windings center-tapped.

Although a field coil of 1,800 ohms is specified for the dynamic speaker, constructors who possess speakers with somewhat larger resistance field coils, up to 2,500 ohms, may use what they have, but the output transformer should be for the general type of low- $\mu$  tubes. The usual rating is 2,500 ohms output impedance for a single 2A3, but up to 5,000 ohms output impedance may be used, because of the extraordinarily high negative bias in this particular circuit. Thus, a speaker for single 2A5 tube could be used. For the 2A5 the output load may be 7,000 ohms.

**Condensers**

The four-gang condenser has a maximum capacity of 0.00041 mfd. and will tune from above 1,700 kc to 520 kc at the r-f level, or from 2,165 kc to 985 kc on the local oscillator. The total inductance of the r-f secondaries is 230 microhenries and that of the oscillator secondary is 126 microhenries, for this condenser.

For the oscillator a padding condenser of 350-450 mmfd. is used, and the correct setting is near maximum. As a first approximation, set this condenser at maximum, then turn the setscrew out  $1\frac{1}{4}$  turns. The final and correct adjustment should be made on the basis of a frequency around 600 kc at the signal level, while the other end is trimmed at or near 1,450 kc.

There are two 20 mfd. in the 2A3 circuit, one to bypass the total biasing resistance of 1,550 ohms, the other to bypass half of that resistance, or 775 ohms. The total consists of two series-connected 775-ohm units. Only one 20 mfd. is in the 2A5 circuit.

**Electrolytic Condensers**


For the screens of the 58 tubes the 64 volts as obtained from the 2A3 tube biasing resistor are sufficient, and indeed there may be oscillation at the r-f level and also at i-f, so two extra resistors, to be discussed later, are shown on the diagram. Also the 20-odd 2A5 bias volts are enough for screens.

The 20 mfd. condensers are of a lower voltage rating than the 8 mfd. used in the B filter, hence are much smaller physically. There is room for four cans. However, there are combinations of two 8 mfd. in one can, hence two cans take care of four 8 mfd. condensers, and the two extra chassis holes are used for the separate 20 mfd. units.


**Resistors**

Of the resistors, the 350-ohm unit provides a negative bias of around 4 volts on the two r-f tubes and the 2A7 combination oscillator-modulator. It is true that if the resistance value is somewhat lower, hence the bias voltage reduced, the sensitivity will be increased, but there is likelihood in the first instance that there will be r-f oscillation, and it has always occurred in the sec-

(Continued on next page)

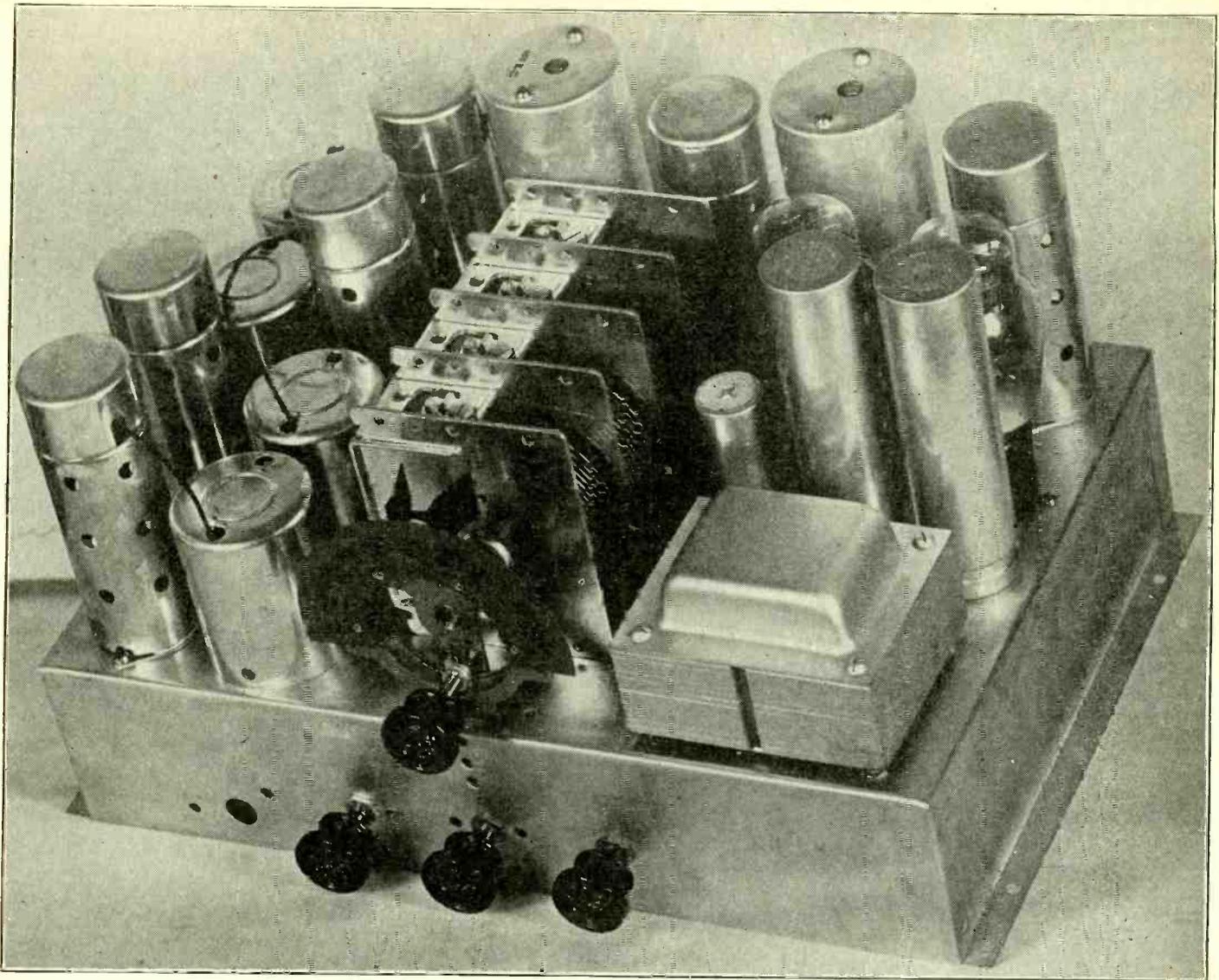

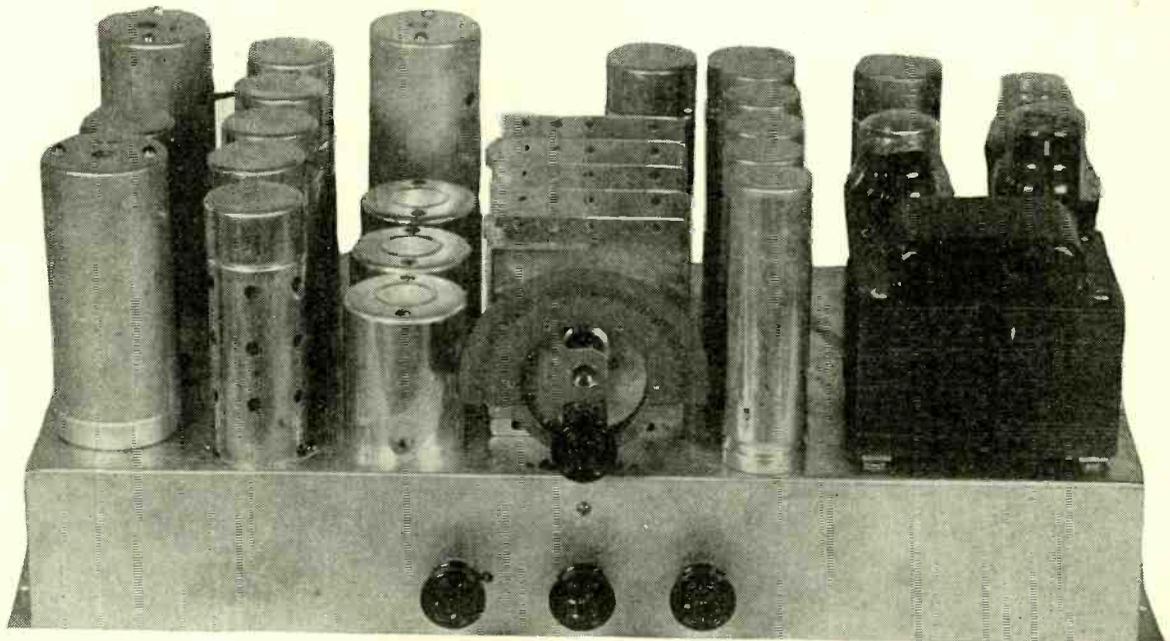The 8-tube chassis is illustrated above and the 12-tube chassis at right. These circuits have the same "front end."



(Continued from preceding page)

ond r-f stage. Hence a resistor of 50,000 ohms is optional across the grid winding or full secondary in the second r-f stage. This always has cured the trouble, but there are other methods, discussed last week in connection with the 12-tube model.

The i-f oscillation is associated almost always with the second i-f tube, but the cure may be applied across the primary of the first i-f transformer, hence a resistor of 20,000 ohms is shown in that position. In exception instances the 20,000 ohms were necessary instead across the next load. However, the better plan is to omit these

two squeal-eliminating resistors in the construction and put them in only if necessary. Moreover, the values are average. Do not use higher values than necessary to correct the trouble, and use lower values if those cited do not produce the result, except that first shift the resistors to different equivalent circuits to make sure that you are not trying to apply the remedy where it will not be most effective. For instance, oscillation at these levels produces a galaxy of squeals, so if you put your hand between grid cap and shield can, using two fingers, or palm and one finger, if the squeals stop that is the stage that is oscillating.

#### Increasing Sensitivity

The 775-ohm resistors will get hot, but that does not matter. The 15,000-ohm resistor should be of 5 watts rating, and will not get so hot. The value of 15,000 ohms was selected as a safe one, in view of the great sensitivity of the set, but there will be somewhat greater sensitivity if this is a smaller resistor, and it is suggested that a 1-watt resistor of 25,000 to 50,000 ohms be placed in parallel with it. Also 800 ohms, more or less, may be put in parallel with the 350-ohm biasing resistor already discussed. If the increased sensitivity is un-

(Continued on page 21)



# Radio University

**A QUESTION and Answer Department.** Only questions from Radio University members are answered. Such membership is obtained by sending subscription order direct to RADIO WORLD for one year (52 issues) at \$6, without any other premium.

RADIO WORLD, 145 WEST 45th STREET, NEW YORK, N. Y.

## Complete Cure for Hum

WILL you kindly explain what to do to eliminate all hum from a broadcast receiver? I have tried everything that has been suggested and there is still some hum left.—W. P. E.

Use batteries for all voltages—plates, screens, grid bias, and filaments. Also use batteries for the speaker field, and after that move away from all electrical power lines and select on those broadcast stations which are completely operated on batteries. Perhaps the hum can be reduced to below audibility with less radical changes, but the question was to reduce the hum completely. To reduce the hum practically you may have to use a heater type tube in the output stage, use filtered current in the field, improve the filtering all around.

\* \* \*

## Measuring Grid Bias

WHEN I connect my voltmeter between the cathodes of the r-f amplifiers and ground I get a reading of 20 volts. This does not change when I vary the volume control which should control the bias on the tubes. The set does not work and I wonder if the trouble is excessive grid bias.—W. R. T.

Apparently you have no connection between the cathodes of the tubes and the chassis until you connect the voltmeter, and then the only connection is the voltmeter. That accounts for the high voltage reading and also for the fact that the circuit does not work. What you are doing is using the voltmeter as a milliammeter and then read the current in volts. The reading is the voltage drop in the meter due to the plate current that flows through the meter. If you put a milliammeter, or a voltmeter, in series with one

of the plate circuits you should not get any reading if the cathode connection is open.

\* \* \*

## 2-Volt or 6.3-Volt Tubes?

IN LOOKING OVER the tubes available for the construction of a battery set, I am at a loss to decide whether to use the 2-volt series or the 6.3-volt series, as the higher voltage heater series seems to afford possibilities for better performance, although at much greater drain. Do you consider the 2-volt series satisfactory?—I. D.

Yes. In fact, the 2-volt series tubes are exclusively intended for battery operation of the filaments. If you use the 2-volt tubes you will make no mistake. The circuit and constants choice will determine the result more than the selection of one tube type or the other, whereas the 2-volt series will prove much more economical.

\* \* \*

## Grids of 2A7

PLEASE define the five grids of the 2A7 mixer tube.—E. J.

Grid No. 1 is oscillator control grid; No. 2 is oscillator plate; No. 3 is screen; No. 4 is modulator control grid (cap). No. 5 is tied to No. 3 in the tube.

\* \* \*

## Transformer Range

WHAT range is possible with audio frequency transformers? That is, is it possible to make the gain uniform up to 10,000 kc, or 20,000 kc? I have heard that it is possible to make audio transformers that will cover all the frequencies required for a television receiver.—A. B.

Transformer manufacturers claim that they can make transformers that have a uniform characteristic from about 30 cycles to 100,000 cycles. But such transformers are very expensive. The wider the uniform transmission characteristic the more the transformers cost.

## Conversion Conductance

WHAT IS MEANT by the conversion conductance of a tube such as the 2A7? Why is the grid current type oscillator invariably recommended for Grids Nos. 1 and 2 of this tube? Would not a negative bias method work better?—P. O.

The conversion conductance is a measure of the efficiency of the tube as a mixer. It is the ratio of the input radio frequency voltage to the output intermediate frequency voltage. The rating for the 2A7 is indeed high, more than 400. The grid current type oscillator is the only one with which highly satisfactory results have been obtained to date with this tube, although perhaps the steady negative bias method may be worked out later. As the tube is made at present, so soon as the bias is more than a little bit negative the tube does not oscillate well. Both methods, however, are really of the negative bias type, though one depends on grid current through a leak to develop this bias, and the other has a steady bias due to the cathode current. It should be observed that if the oscillation amplitude exceeds the steady bias value, grid current starts to flow even in the second instance, therefore grid leak and condenser might be well included as a precaution, or check.

\* \* \*

## Zero Voltage Twice a Cycle

IS IT TRUE that in all radio sets the signal actually stops once in every cycle? And if it is true, why does not this appear as a form of interference?—Y. W.

The stoppage occurs once during each alternation or half-cycle, hence twice each cycle. This is true of alternating current in all its manifestations. Starting from zero, the current (or voltage) builds up to maximum of the positive cycle, then declines to the zero axis, and further builds up to the maximum negative value and declines again to the zero axis. There is actual interference if the frequency is low enough, which it never is in general radio experience, for the radio frequencies are out of consideration in this regard, and if the lowest audio frequency is assumed to be 50 cycles, then the stoppage takes place 100 times a second, and the ear does not detect this, because of the minute duration, compared with the signal frequency. It is about the same situation as in the movies, where flicker is utterly avoided by using 24 pictures a second, in conjunction with a triple shutter. In the movie instance persistence of vision takes care of the absence of the picture, while in the radio example persistence of hearing comes into play.

\* \* \*

## Kerr Cell

FOR TELEVISION PURPOSES, while a Kerr cell may be used as the light source, it is normally necessary to put a high positive bias on it (around 500 volts usually). Can not some way be provided to avoid this high biasing voltage?—U. E.

It should be practical to operate the cell at zero bias, and to have the signal swing it, that is, maintain polarization by signal bias. This method would constitute the cell a detector, and it seems likely that the output of television receivers will be detectors in the near future. Right now there is a sort of television hiatus, but with improved economic conditions no doubt the expensive television research will be carried on even at a greater pace than in the past.

\* \* \*

## Why Two I-F Stages?

IN THE CONSTRUCTION of super-heterodynes, using two intermediate-frequency stages, requiring three coils. I find that there is always considerable oscillation, and I wonder whether one stage (two coils) isn't enough? The introduction of automatic volume control does not seem to diminish the tendency to oscillation.—C. L. F.

Enough gain is obtainable from a single intermediate tube, somewhere between 100 and 200 for the stage, and so the real reason for the extra stage is more selectivity. In the sense that the gain can not be pressed very much beyond that obtainable from a

# Two for the price of One

Get, EXTRA, one-year subscription for any One of these magazines:

- POPULAR SCIENCE MONTHLY.
- RADIO-CRAFT (monthly, 12 issues).
- RADIO INDEX (monthly, 12 issues), stations, programs, etc.
- RADIO (monthly, 12 issues; exclusively trade magazine).
- EVERYDAY SCIENCE AND MECHANICS (monthly).
- RADIO LOG AND LORE. Bi-monthly; 5 issues. Full station lists, cross indexed, etc.
- AMERICAN BOY—YOUTH'S COMPANION (monthly, 12 issues; popular magazine).
- BOYS' LIFE (monthly, 12 issues; popular magazine).
- OPEN ROAD FOR BOYS (monthly, 12 issues).

Select any one of these magazines and get it free for an entire year by sending in a year's subscription for RADIO WORLD at the regular price, \$6.00. Cash in now on this opportunity to get RADIO WORLD WEEKLY, 52 weeks at the standard price for such subscription, plus a full year's subscription for any ONE of the other enumerated magazines FREE. Put a cross in the square next to the magazine of your choice, in the above list, fill out the coupon below, and mail \$6 check, money order or stamps to RADIO WORLD, 145 West 45th Street, New York, N. Y. (Add \$1.50, making \$7.50 in all, for extra foreign or Canadian postage for both publications.)

Your Name.....  
 Your Street Address.....  
 City ..... State .....

**DOUBLE  
VALUE!**

- If renewing an existing or expiring subscription for RADIO WORLD, please put a cross in square at beginning of this sentence.
- If renewing an existing or expiring subscription for other magazines, please put a cross in square at the beginning of this sentence.

RADIO WORLD, 145 West 45th Street, New York. (Just East of Broadway)

single stage without intense filtration, there is hardly an advantage in the extra stage. But from the viewpoint of selectivity there is certainly a real advantage. In fact, some manufacturers have intermediate coils with coupling between primary and secondary adjustable, so that it may be made as loose as necessary consistent with absence of oscillation. Another way of accomplishing the same result is to increase the negative bias on the intermediate tubes. It must be expected that oscillation will be present in the two-stage system, unless the coils are inordinately far apart and the voltages rather low, but the trouble is easily curable. One may put a 20,000-ohm resistor across the primary of the first intermediate-coil, and increase the negative bias by using resistors of around 2,000 to 3,000 ohms or so in the individual i-f cathode legs. The advantage of the two-stage system can be proved rather easily by the separation afforded between a strong local and a weak distant station 10 kc removed from that local. The single i-f stage system will not permit the uninterfered reception of the DX station, but the double-stage system will, despite long aerial.

**Squeals in a Super**

IN THE COURSE of trying out several superheterodynes that I have built I find that there is less squeal interference at 175 kc intermediate frequency, rather more at 465 kc and thereabouts, and also that in all systems there is no sure-fire way of getting rid of squeals. At least two squeals must be expected—unless you have some evidence to the contrary. Which intermediate frequency is preferable?—L. L.

The principal cause of squeals is insufficient selectivity ahead of the modulator, and as a precaution in this direction three tuned stages are commonly employed in the better receivers, not counting the oscillator, i.e., a four-gang condenser is used, although there are not always tubes between coils. The cause is obvious from the consideration of the images, or alternate frequency responses, for if the desired signal frequency (carrier) does not come in exclusively, there is danger that enough voltage is present at the image or alternate frequency to cause a squeal, because the same oscillator frequency is consistent with the reception of both frequencies. The higher the intermediate frequency, the less the danger of image reception, hence at 465 kc there are images possible only from 1,470 kc up. For an i.f. of 175 kc the images may appear from 890 kc up. If the i-f channel is generating harmonics, or if these are present in the second detector for any reason, then squeals will result, due to beating, and the higher i.f. cause more trouble then, because the interfering harmonics are of a lower order (second and third). Finally, if the circuit is not padded correctly, and if the i-f level is not accurately set at one frequency, squeals will be heard. Thus it is very important to have the i-f channel lined up perfectly, for if it cuts off at the equivalent of 10 kc (expressing the situation on the basis of the broadcast channel), two channels will not go through the i-f amplifier. There is not much to choose between 175 kc and the higher intermediate frequencies, except that if shorter waves than broadcasts are to be received, of course the higher i.f. helps reduce image interference, because maintaining a greater frequency difference between oscillator and modulator. See that the r-f and i-f amplifiers are not oscillating or regenerating, pad accurately, line up the i.f. accurately, and use three tuned circuits ahead of the modulator for the broadcast band. Then you should not experience any squeals. Many superheterodynes are being built these days that are utterly squealless.

**Amplification Cutoff**

MY EXPERIENCE with the 55 and 2B7 tubes has been that only so much signal voltage can be put into them, and if this voltage is exceeded the amplification becomes less, and finally when the voltage rises high enough, the amplification cuts off dis-

tortedly. Is this not detrimental? I have not tried the 75 and the 2A6, but I presume they show the same effects.—E. F.

The condition you describe actually exists, but whether to call it a detriment is a matter of opinion. In one sense it may be regarded as a virtue, as it precludes the possibility of overloading the power tube, and besides there is abundant amplification present, that is all-sufficient quantity of sound, before the cutoff or semi-cutoff condition arises. While the volume control may be retarded at any time to introduce correction, if there is automatic volume control this remedy may not be complete, and it would be preferable to reduce the aerial to such size that the pickup prevents the excess signal voltage on the second detector. The antenna reduction may be by series condenser. It is presumed the circuits you built have the diode-biased triode or diode-biased pentode. Otherwise, instead of the cutoff you refer to, the signal keeps on rising, but grid current begins to flow, another form of distortion, and really no better or worse than the form previously discussed. The diode-biased method introduces direct and non-reactive coupling, and thus gets away from the distortion due to the stopping condenser. The formal tube data do not include the diode-pentode tubes (e.g., 2B7) for diode bias, probably because of the low signal voltage handled, around 2 volts, say. However, the amplification in the pentode is so large that at 2 volts input there could be 100 volts output, provided the applied plate voltage were in excess of 200 volts. That is why the plate resistor is often returned to 250 or 300 volts. We do not regard the condition you describe as detrimental at all, especially as a shorter aerial improves the selectivity without requiring the addition of any tuned circuits.

**He Waited Six Years**

BELIEVE IT OR NOT, I have not built a circuit in six years. In fact, the set I have was the Diamond of the 1926 vintage, which I built the next year. So you see I am not a hurried person. However, I would like to build an a-c set now, and would you please recommend a circuit using seven or eight tubes, preferably a superheterodyne from which the bugs have been extracted? I have seen so many differ-

ent circuits, and the claims for them are so extensive (without exception) that I do not know which one to choose.—W. D. S.

We recommend you build the 8-tube Super Diamond, discussed in the present issue. If you want a 7-tube set you may follow the same diagram, but omit one intermediate stage. It is valuable, however, to include the extra intermediate stage if you desire selectivity up to just below the point of sideband-cutting. We believe the bugs have been taken out of this as much as from any other super, and we know that scarcely any trouble has been experienced by others who have built this set.

\* \* \*

**Interference Remedy**

IN MY LOCALITY I am troubled with interference due to a cause unknown, but it is periodic, about 200 throbs per minute, and it causes me no end of displeasure, often ruining programs, so I have to shut off the set and (alas) go to bed, two things I hate to do prematurely. If I could abate the nuisance somewhat, I would be temporarily satisfied. Can you suggest some means of tracking down the trouble?—F. McC.

An easy help is to put a small condenser in series with the aerial, say, 0.0001 mfd., or even half that value. While signal strength will be reduced, the interference will be cut down at a greater rate. We do not know just why this should be so, unless that the natural period of the antenna system becomes so much higher in frequency that the lower frequency interference is substantially bypassed. Anyway, under similar conditions we tried the remedy and it worked well. While the frequency of the interference exists as a modulation, as you report it, the actual source of interference is a higher frequency, obviously, if the interference comes in through the aerial. You may determine the fundamental of the interference by noting the frequencies at which the interference is heard loudest on your set, say, 900, 1,000, 1,100 kc etc. Then as the harmonics are 100 kc apart, the interfering frequency is fundamentally 100 kc. The trouble no doubt is due to an oscillator, that is, a generator of radio frequencies. You can locate it with a loop receiver, encircling the suspected location, and tracking it down by the direction the loop points.

Join Radio World's

# UNIVERSITY CLUB

**And Get Free Question and Answer Service for the Coming 52 Weeks.**

**THIS SERVICE FOR UNIVERSITY SUBSCRIBERS ONLY**

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below or write on a separate sheet of paper, if preferred. Your name will be entered on our subscription and University Club lists by special number and you will be apprised of the number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your query. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

**NO OTHER PREMIUM GIVEN WITH THIS OFFER**

[In sending in your queries to the University Department, please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for Radio World for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name .....

Street .....

City and State.....

# Station Sparks

By Alice Remsen

## Music

### For Channon Collinge, WABC

The Cathedral Hour, Sundays, 4:00 p.m.  
EDST

Through the stained glass the dappled  
sunlight seeps,

Weaving varied patterns on the chancel  
floor;

Into the silence a subdued murmur creeps;  
Wanton breezes enter through the open  
door.

Up from the choir comes harmony pro-  
found,

Angelic music, seemingly supernal,  
Reverberating there, a lovely sound,  
Leaving an echo, magical, eternal!

A. R.

\* \* \*

And during the Cathedral Hour, con-  
ducted by Channon Collinge, you will be  
wafted to a quiet cathedral close; to an  
atmosphere of old-world charm and spirit-  
uality. The blended voices of the choir  
will inspire you with devotion and rever-  
ence. A soothing and beautiful period of  
relaxation.

\* \* \*

## The Radio Rialto

Up at WABC

It did seem like old times the other eve-  
ning up at WABC; in Studio One working  
on the Standard Oil Five Star Theatre  
program with Solly Ward and "Snoony";  
Johnny Hart was the straight man for  
Solly Ward, which made it seem all the  
more homelike. I had a good time singing  
"Tom Thumb's Drum." Something about  
that lively little song that I like. Noticed  
Jackie Osterman floating around the stu-  
dio for no good reason. He's putting on  
weight these days. . . . This was the last  
program of the season. All the Standard  
Oil productions are going off for the sum-  
mer. So it was really in the nature of a  
farewell. . . . Met up with Peter and Ar-  
lene Dixon after the program. They are  
still doing their clever little skit, "Raising  
Junior," on WOR. Getting plenty of mail  
on it. Here's a tried and true program  
which some sponsor should buy. Great  
for a kid's product, interesting to grown-  
ups, too. . . . Potash and Perlmutter are  
due on the air some time in June, spon-  
sored by Health Products, Inc.; network  
not yet decided upon. Joseph Greenwald  
will play Potash, and Lew Welch, Perl-  
mutter. The McCann, Erickson agency is  
handling the account. . . . Carolyn Gray,  
formerly staff pianist for NBC, is now act-  
ing in that capacity for Columbia. This  
clever girl has started a new series of  
programs, each Monday at 2:15 p.m., in  
which she makes a radical departure from  
her usual classical style; she's doing jazz,  
musical comedy, popular and classical se-  
lections, running from one to the other  
without any announcement. . . .

### DAVID ROSS ON DECK

Received an enthusiastic greeting from  
David Ross; we had not seen each other  
for six months—he's still the same happy  
little fellow. Hope he doesn't forget to  
send that autographed picture to his very  
ardent admirer, Peter Grant, the ace an-  
nouncer of WLW, Cincinnati. Peter is a  
great fan of David's; listens in to him  
whenever he gets a chance and thinks  
that David is the greatest reader of poetry

on the air. I think he's pretty good my-  
self. . . . A social organization for radio ar-  
tists has been formed, it has been named  
the Remote Control Club, rumor has it  
that they will rent an entire building  
somewhere in the "Frantic Fifties." . . .  
The National Vaudeville Artists are con-  
ducting a drive to gain radio artists as  
members. Here is a cause which is worthy  
of support. The dues are only ten dollars  
a year, and the benefits to be derived are  
numerous and gratifying. . . . Don Carney,  
(Uncle Don to the kiddies) rejoined the  
N. V. A. after performing at one of their  
Saturday Night get-togethers. It is a  
gracious gesture, when well-to-do artists  
think of their less fortunate brethren and  
help to support an organization like the  
N. V. A., which does so much good for the  
needy and sick of the theatrical profes-  
sion, regardless of creed or race. . . .  
Merle Johnston has a brewery account  
twice weekly on WOR, Mondays and Fri-  
days, 9:00 to 9:30 p.m. It is sponsored by  
King's Brewery. Al and Lee Reiser,  
Elmer Feldkamp, and Irene Taylor are on  
the program. Merle has a fifteen-piece  
band which has the title of "The King's  
Men." . . . Received a nice long letter from  
Gene Brown, the publicity gal of WBAL,  
Baltimore. She tells me that Melva For-  
sythe, the radio contralto, played five  
straight months with Grace Moore in "The  
Dubarry," with a nice speaking part  
n'everything. Understand she is due in  
New York soon and hope she looks me  
up. . . .

### NO SCANDAL; NO, SIR!

Received a letter from one of my read-  
ers asking how come I never print any  
scandal about radio artists. Well, I'll tell  
you. In the first place I don't believe in  
printing scandal, I leave that to the yel-  
low press. If I can't say anything good  
about people I just don't mention them at  
all; and in the second place, I don't be-  
lieve anybody could find much scandal  
among radio artists; they are a pretty  
clean bunch of people; at least, I've found  
them so. . . . Went to see the picture  
"Adorable," with Janet Gaynor, and the  
new Continental star, Henry Garat, at  
Radio City Music Hall. It is a very en-  
joyable film with nice music, and good  
photography but a silly little plot. Garat  
is quite good looking, with a fine screen  
personality. The Music Hall is an im-  
mense place, extraordinarily well wired  
for sound, the singing and talking from  
the stage registered well—but—guess I'm  
a bit of a sentimentalist, for I found my-  
self thinking rather sadly of the cosy,  
homelike little theatres of yesteryear. . . .  
There has been a time change for the  
juvenile program, "The Stamp Adventur-  
ers Club"—for New York, Boston, Hart-  
ford, Buffalo, Philadelphia, Providence,  
Worcester and Albany there will be a  
broadcast each Friday from 6:00 to 6:15  
p.m., EDST. For Baltimore, Cincinnati,  
Columbus, Fort Wayne, Syracuse, Cleve-  
land, Akron, Rochester, Washington,  
Pittsburgh and Toledo, the program will  
be heard one hour later, from 7:00 to 7:15  
p.m., EDST. From Chicago, where the  
program originates from the Columbia  
studios, there will be a special broadcast  
from 6:45 to 7:00 p.m., EDST. . . .

### BY ARRANGEMENT WITH C. B. S.

Acceding to a petition submitted by the  
Columbia Broadcasting System, King  
George has agreed to postpone his open-  
ing address at the World Monetary and  
Economic Conference until 3:00, p.m.

EDST, on June 12th, at which time it will  
be heard over the WABC-Columbia net-  
work from London. . . .

Harriet Britton, who was heard with  
"Sweet Adeline" and "Hit the Deck" in  
New York, with the St. Louis Municipal  
Opera Company, and more recently over  
NBC networks, gave a song recital at the  
Barbizon-Plaza Theatre a short time ago.  
She proved to be a dramatic soprano of  
extreme versatility, including in her pro-  
gram the works of such composers as  
Handel, Sarri, Scarlatti, Strauss, Wagner,  
Brahms, Schubert, Debussy, Saint-Saens,  
Kramer and Campbell-Tipton. Miss Brit-  
ton gave a very excellent performance  
which was thoroughly enjoyed by a large  
audience. . . .

### NO YOU KNOW

Did you know that John Seagle, NBC  
baritone, is married to the former Helen  
Peters, a Smith College graduate and  
his boyhood sweetheart? that Welcome  
Lewis, the blues singer, is the daughter of  
Katherine and John Lewis, professional  
dancers, and that the mother of Bess  
Johnson, dramatic actress, played with Lil-  
lian Russell and other stage celebrities of  
another generation? . . . President Roose-  
velt will get an honorary degree of Doctor  
of Laws from the Catholic University of  
America on June 14th; the event will be  
broadcast over an NBC network and  
WAF at twelve noon, EDST. . . . And I'm  
going to get myself a cup that cheers but  
doesn't inebriate—tea, toasted muffins and  
blackberry jam. . . . and then for the bio-  
graphy of a man who also likes tea and  
muffins, the conductor of the famous  
WABC Cathedral Hour—Channon Col-  
linge.

\* \* \*

## Biographical Brevities

### About Channon Collinge

The story of the life of Channon Col-  
linge reads like an adventure tale. He  
was born in the tiny town of Salterhebble,  
in the West Riding part of Yorkshire,  
England. As an infant he was taken to  
Poona, India, where he lived for three  
years. The following three years of his  
life were spent at sea, sailing the briny  
between England, Asia and Africa. At  
six, young Channon Collinge was attend-  
ing kindergarten in his home county of  
Yorkshire and at twelve he was back in  
India. Two years later he returned to  
England to finish his education. At his  
father's death he was forced to leave  
school and take the family business of  
cotton manufacturing, and despite a com-  
plete distaste for the business, Collinge  
applied himself so diligently that he won  
the gold medal for excellence in work on  
cotton manufacture.

Young Collinge had always shown defi-  
nite talent for music, and as a child had  
improvised tunes on the piano. At the  
age of eight he began the serious study of  
the violin, and at the age of ten had or-  
ganized a children's orchestra. At twelve  
he was composing school operettas, and at  
twenty was a professional musician. He  
later directed the Dublin Choral Society,  
the University Choral Society of Dublin  
and the Drogheda Society of the same  
city. Unable to continue devoting him-  
self to business he left Yorkshire and at-  
tended Dublin University, where he later  
became Professor of Music. During his  
vacations he traveled all over Western  
Europe, Egypt, Algiers, Australia and the  
East Indies.

In 1907, exhausted from overwork, he  
decided to visit America. For more than  
a year he traveled through the United  
States from California to the Atlantic sea-  
board, going down to South America,  
West Indies, Cuba and Bermuda. Coming  
back to New York he wrote the music to  
the opera, "Seminary Girl," and went on  
the road with the company. Then he met  
(Continued on next page)

# PERSONALITIES

Carveth Wells sits up and takes notice when Mrs. Wells says she has been shopping.

"See anything interesting?" asked Wells, absorbed in the writing of his next lecture-broadcast.

"Yes. I bought something."

"What?"

"A place in the country."

Wells bounded from his chair and instead of remonstrating—as most husbands would have done—he danced a sailor's hornpipe! "A place in the country" has been his life-long dream.

Mrs. Wells' purchase turned out to be a delightful old farm house located on a three-acre plot on the Saugatuck River near Norwalk, Conn.

\* \* \*

Three members of the cast of "Penrod," the play in which Ben Grauer, NBC announcer, made his Broadway debut in 1918, are today famous in the theatre. They all made their stage debuts in the Booth Tarkington play at the Globe Theatre. They are Helen Hayes, Helen Chandler and Lillian Roth.

Grauer played the role of Georgie Bassett.

\* \* \*

Whenever Sherlock Holmes' (Richard Gordon) pronunciation of an English word fails to meet with Watson's approval, the Sherlock of the air promptly hears about it from his studio partner, Leigh Lovel. Gordon recently turned the tables and informed Lovel after a program there was one word he always pronounced wrongly.

"What may that be?" Lovel asked, jamming his monocle into an eye.

"Wrongly" quipped Gordon.

\* \* \*

Fannie Brice, the comedienne, has four dogs.

\* \* \*

John Brewster, whose poetry hour, "Golden Treasury," is a weekly chain feature, was called upon to judge a poetry contest recently at Julia Richman High School, New York City.

\* \* \*

Welcome Lewis, radio songbird, is going to Washington for a week's engagement in vaudeville. She will be featured with Kelvin Keech, announcer in her Musical Scrapbook of the Air, the program in which she was heard over networks from New York.

\* \* \*

Lee Sims, pianist who also runs a music school, has a busy business brain. He hopes to launch a chain of music schools, with himself as the long haired maestro at the head . . . the big link of the chain, as it were.

\* \* \*

An organization in Toronto, Canada, requires members to cultivate a dialect like Jack Pearl's. Members must also remain absolutely quiet during a Magic Carpet program featuring the Baron. The penalty is a \$5 fine that is turned over to charity.

\* \* \*

NBC's 19-year-old Loretta Poynton, who has taken up housekeeping near the studios because her home is too far away, has found a place for the jigsaw puzzles in her new abode. She uses them as decorations for the end table because she likes the pictures.

\* \* \*

Lanny Ross' doorbell rang. It was a messenger with one big lily in a flower box. And it was the night that Lanny was opening a week of personal appearances at the Roxy. Lanny thought that it was just someone's grisly sense of humor until he looked at the card in the box. The name of the sender was Johnny Weismuller. How about this, Tarzan?

Reading on, Lanny found that it was all a mistake. The flower had been delivered to the wrong address—but Lanny refuses to divulge the name of the lady.

\* \* \*

"Teach Me to Smile," written a number

of years ago by Don Bestor, is still the orchestra director's theme song for his NBC broadcasts from the Hotel Lexington in New York.

Tom Howard, of the "Musical Grocery Store," says there was a run on his young son's bank during the moratorium, but the kid got there first when daddy tripped.

\* \* \*

While studying voice in Italy, Robert Royce, tenor, had a narrow escape from death. As he was watching a Garibaldi Day parade in Milan disperse, a violent anti-Fascist battle broke out, and the singer found himself caught between the rival lines, bullets whizzing past him from both directions. The battle ended as suddenly as it had begun, and Royce escaped unhurt.

\* \* \*

If Sigmund Spaeth spent much of his time at his clubs, he wouldn't have time to broadcast as the Tune Detective.

A few of the organizations of which he is a member are the Triangle Society, Founders Club, Bachelors Club, Nassau Club, (Princeton), Princeton Club, Dutch Treat, Green Room, Friars, Lambs, University Glee Club, the Bohemians, Kiwanis and National Arts Club. Spaeth is one of the few men in radio with a Ph.D. degree. He obtained it at Princeton. His A.B. and A.M. degrees were received at Haverford College. He is a member of Phi Beta Kappa and Phi Mu Alpha.

\* \* \*

Eddie Duchin has made over 100 records for Columbia, Victor and Brunswick in a year. . . . Aviator "Swanee" Taylor is teaching both Fred Waring and Ted Husing to fly. . . . The Lombardos are getting themselves sunburned, preparatory to donning their traditional white linen suits—an annual rite. . . . When a writer's misprint erroneously reported that only four letters were drawn by the recent New York Philharmonic Symphony broadcasts, several hundred indignant fans wrote CBS, apologizing for not writing sooner. . . . Most said it was the first fan letter they had ever written, but not the last.

## TRADIOGRAMS

By J. Murray Barron

A new 5-tube all-shielded, self-contained electric automobile set is now commanding considerable attention. It employs a late and proved circuit, incorporating the newest tubes and in the majority of cases does not require suppressers. From various known tests this unit came out with an excellent record and stands high. It may be had either in electric or battery type and in each case works efficiently. It comes equipped with remote control and is very simply mounted with two large bolts. The outfit comes completely wired and ready to operate unit, or may be had as a kit, with simplified diagram with complete instructions for assembly of the electric or battery model. A full description is scheduled for publication in RADIO WORLD soon, possibly the June 17th issue, by the Engineers of the Postal Radio Corp., 135 Liberty Street, N. Y. City.

\* \* \*

A new item recently offered to the fan and experimenter and which comes in a variety of combinations is the Shielded Short-Wave Battery Receiver made by Leotone Radio Co., 63 Dey Street, New York City. This uses the low drain tubes, 30, 32, 33 and 34. The outfit comes completely assembled in shielded cabinet and with coils. It is also offered as a complete kit with coils, or the metal case, chassis or shielded compartments may be bought separately.

One of the very finest radio catalogs to be published this season is now making its appearance through the mails and very shortly will be available across the counter. There are 108 pages, listing thousands of items in parts, complete kits, receivers and everything else in radio. It is a beautiful job, complete with fine illustrations and shows the handiwork of a skilled artist. Mr. Sydney Bass, the advertising and merchandising consultant now associated with the Try-Mo Radio Co., Inc., engineered its production. Copies may be obtained by addressing the organization at 85 Cortlandt Street, N. Y. City.

\* \* \*

The small ac-dc universal radio receivers made considerable stir along radio row and chain stores elsewhere on account of an advertised low price. It is not always possible to get sets that are advertised in windows at very low figures, for often the whole story is not always told. When questions of understanding arise it is safer and in the long run better to insist on all the information first. There will be no dissatisfaction if one buys from reliable firms and from advertisements clearly stated.

## 8-Tube Diamond

(Continued from page 16)

accompanied by reappearance of oscillation, of course use the extra sensitivity.

### Other Requirements

The switch used for shifting from one band to the other requires four positions or poles, two throws. Thus the stator of a condenser is moved from the grid terminal of the secondary to the tap. Hence the tuned circuit is between tap and ground, and the secondary itself acts as an auto-transformer, of which the tuned circuit (tap to ground) is the primary and the entire secondary (grid to ground) is the secondary. Since there is a primary already, in the plate circuit of the preceding tube, or in the aerial circuit, the secondary may be considered technically as the tuned circuit when short waves are received, and the full large winding as the tertiary. Hence there is double step-up.

Besides the connections for the band shifting there is another double-pole section that works simultaneously, and this is used for cutting in the full aerial capacity for short waves, but introducing a series capacity for broadcasts. This series capacity may be less than 0.0002 mfd. if a long outdoor aerial is used. The reason is that the input has to be gaited to the capabilities of the 2B7, so as not to introduce the amplification stoppage too soon. Since broadcasting stations deliver greater power input to the antenna winding, and as greater selectivity is needed, the series condenser is introduced. For the opposite reasons the full aerial input is used for short waves, and then the excellent results on the broadcast band are duplicated in the short-wave realm.

## Station Sparks

(Continued from preceding page)

an old friend from a London music house who persuaded him to remain here as the head of the house's American orchestra department. Then he went with Erlanger, and among the stage successes he helped produce were "The Silver Star," "The Girls of Gottenburg" and "Chin-Chin." In 1920 he decided to return to Europe, instead of which he joined the staff of the old New York Tribune as artist for the Children's page of the paper, producing the well-known "Dinny Doodle," "Jingle Jangle" and other comic strips. Tiring of this he returned to music, and in 1927 signed with Columbia and radio.

## Ten Years Ago!

(RADIO WORLD of June 9, 1923, paid type and pictorial attention to the following matters, among other things.)

"How to Build a Battery Charger for Use with 110 Volts A.C." was the title of an article by Stuart A. Hendrick.

Amateur station 5ZA, in Roswell, New Mexico, was described in text and pictures. It was one of the outstanding amateur stations of that period.

C. White told our readers how to make a super amplifier, and a schematic design indicated that things were different in 1923.

The General Electric Company announced that it was starting on the construction of "the first plant to be used exclusively for popular broadcasting."

Secretary of Commerce Herbert Hoover announced the first Interdepartment Radio Advisory Committee to be organized for the Federal Government.

Our own J. E. Anderson was responsible for an article entitled "Simple and Easily-Made Neutrodyne Condensers."

Carl H. Butman, RADIO WORLD'S Washington correspondent, wired that the American broadcasters totaled 592 for the end of that current week. "Swat the Birdies" said

one of that week's contributors in referring to rules for minimizing re-radiation.

Arthur S. Gordon declared that there was no need for roars, clicks, shrieks and the awful scam of interference—and then endeavored to prove that they could be done away with in most cases.

George Freisinger, a noted amateur station owner told our readers all about his new station 2ABT, which cost \$5,000.

Elizabeth, N. J., started a campaign to stop the use of large phonograph horns in front of radio stores. If memory serves us right, Elizabeth didn't get very far with her protest.

## Quick-Action Classified Advertisements

7c a Word—\$1.00 Minimum Cash With Order

**URUGUAY STAMPS**—100 different stamps, \$1.00. 200 different stamps, \$3.50. Stamps will be shipped direct from Uruguay. Heriberto Meyer, care Radio World, 145 West 45th St., New York City.

**SELL ELECTRIC NEONLIKE WINDOW DISPLAY SIGNS.** Complete, 98c. Particulars. Slogans 8 in. x 14 in. Box 63, Rugby Sta., Brooklyn, N. Y.

**ENVELOPES,** \$1.39 per thousand; we pay postage; samples for stamp. Young Printing Company, Fairfield, Penna.

**BARGAINS IN FINEST PARTS!** — Highest grade, new parts, few of each on hand. National dial, flat type, modernistic escutcheon, type G, clockwise, \$2.19; Pilot drum dial No. 1285 @ \$1.89; s-c toggle switch, 19c; triple pole, four-throw Best switch, insulated shaft, \$1.62; double pole, four throw, \$1.08. Direct Radio Co., 145 West 45th St., N. Y. City

**RADIO WORLD AND POPULAR MECHANICS MAGAZINE**—Radio World is \$6.00 a year, and Popular Mechanics Magazine is \$2.50 a year. Popular Mechanics Magazine does not cut rates, but Radio World will send both publications to you for one year for \$7.00. Radio World, 145 West 45th St., New York City.

**"THE MODERN GASOLINE AUTOMOBILE,"** by Victor W. Page, M.S.A.E. New Revised and Up-to-date Edition. A whole library of information now complete in one large octavo volume of 1,146 (6 x 9) pages—1,000 engravings. Bound in flexible scarlet fabrikoid. Price \$5.00. Radio World, 145 W. 45th St., New York, N. Y.

## DIAMOND PARTS

Tuned Radio Frequency Sets

### FIVE-TUBE MODEL

A-C operated circuit, 50-60 cycles, 105-120 volts, using two 58 t-r-f stages, 57 power detector and 47 output, with '80 rectifier. Three gang shielded condenser and shielded coils in a sensitive, selective and pure-tone circuit. Dynamic speaker field coil used as B supply choke. Complete kit of parts, including 8" Rola speaker and all else (except tubes and cabinet). Cat. D5CK @.....\$15.99  
Wired model, Cat. D5CW (less cabinet) @..... 17.19

Kit of five Eveready-Raytheon tubes for this circuit. Cat. D5T ..... 4.97

**FOUNDATION UNIT,** consisting of drilled metal subpanel, 13 1/4 x 8 3/4 x 2 3/4"; three-gang Scovill 0.00035 mfd., brass plates, trimmers, full shield; shields for the 58 and 57 tubes; six sockets (one for speaker plug); two 8 mfd. electrolytic condensers; set of three coils. Cat. D5FU..... 6.19  
Super Diamond parts in stock.


### FOUR-TUBE MODEL

The four-tube model is similar, except that there is one stage of t-r-f, and a two-gang condenser is used. Tubes required, one 58, one 57, one 47 and one '80. Complete kit, including 8" Rola dynamic speaker (less tubes, less cabinet). Cat. D4CK .....\$13.58

Kit of four Eveready-Raytheon tubes for this circuit. Cat. 4D.TK .....\$3.88

**FOUNDATION UNIT,** consisting of drilled metal plated subpanel 13 1/4 x 2 1/2 x 7"; two-gang 0.00035 mfd. SFL condenser; full shield; two shields for 58-57; center-tapped 200-turn honeycomb coil; five sockets (one for speaker plug); two 8 mfd. electrolytics; set of two shielded coils; 20-100 mmfd. Hammarlund equalizer for antenna series condenser. Cat. D4FU .....\$5.48

### INDIVIDUAL PARTS

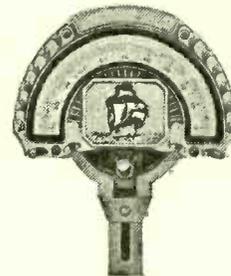

Travelling light vernier dial, full vision, 6-to-1 vernier, projected indication prevents parallax; takes 1/4" or 3/8" shaft; dial, bracket, lamp, escutcheon.

0-100 for 5-tube Diamond, Cat. CRD-0, @ \$0.91.

100-0 for 4-tube Diamond, Cat. CRD-100, @ \$0.91.

[If dial is desired for other circuits state whether condenser

closes to the left or to the right.]

8 mfd. Polymet electrolytic, insulating washers, extra lug. Cat. POLY-8 @.....\$ .49

Rola 8" dynamic for 47 with 1800 ohm field coil tapped @ 300 ohms. Cat. FP @..... 3.83

2 coils for 4-tube. Cat. DP @..... .99

3 coils for 5t-ube. Cat. DT @.....1.39

## DIRECT RADIO CO.

143 WEST 45th STREET  
NEW YORK, N. Y.

**"THE CHEVROLET SIX CAR AND TRUCK"** (Construction—Operation—Repair) by Victor W. Page, author of "Modern Gasoline Automobile," "Ford Model A Car and AA Truck," etc., etc. 450 pages, price \$2.00. Radio World, 145 W. 45th St., N. Y. City.

**PUSH-PULL SUPER DIAMOND:** Construction and trouble-shooting article and double-page picture diagram. In Radio World of March 18, 1933. 15c a copy. Radio World, 145 W. 45th St., New York City.

## SHORT-WAVE COILS and FORMS

Precision short-wave plug-in coils, wound on 1 1/4" diameter. Form has gripping flange. Four coils to a set for each tuned circuit. Appropriate frequencies with 0.00014 mfd. are 1400-3080 kc, 3000-6500 kc, 6000-13200, 13000-30000 kc.

Two-winding coils, UX base. Cat. SWA (four coils) .....\$1.20  
Three-winding coils, 6-pin base (tickler interwound with part of secondary) Cat. SWB @ .....\$1.40

UX sockets for use as coil receptacles. Cat. SX, @ 10c each. Forms, four for 80s, either UX or 6-pin. Six-spring sockets. Cat. SZ @ ..... 11c each.

SCREEN GRID COIL CO., 143 W. 45th Street, New York City

## ANDERSON'S AUTO SET

Designed by J. E. ANDERSON

### FOREIGN RECEPTION ON 6-INCH AERIAL

This new auto set is the most sensitive ear receiver we have ever come across. Mexican and Canadian stations were tuned in from New York City on a 6-inch aerial. The circuit, an 8-tube superheterodyne with automatic volume control. The complete parts, including set chassis and set shield, battery box, remote control, battery cable, all condensers, resistors and coils, speaker with shielded cable; and a kit of RCA tubes (two 239, two 236, two 237, one 59, and one 85) are supplied less aerial. Cat. 898-K @..... \$34.80  
Wired model, licensed by RCA with complete equipment, less aerial, but including RCA tubes. Cat. 898-W .....\$37.40

### DIRECT RADIO CO.

143 West 45th St. N. Y. City

## Special Summer Trial Subscription Offer

FOR

## NEW SUBSCRIBERS

Send \$1.00 in cash, check, P. O. money order or stamps, and receive Radio World postpaid from now until Sept. 2.

Sub. Dept., Radio World, 145 West 45th St., N. Y. City

## STRAIGHT-LINE CHART

Relating Inductance, Capacity and Frequency. Gives The Unknown When Two of the Others Are Known

Edward M. Shiepe, M.A., M.E.E., Massachusetts Institute of Technology, devised the first method of relating inductance, capacity and frequency so that the "curves" are straight lines. He drew the result on graph paper 18 x 20 inches, encompassing the hitherto unachieved ranges of 0.000001 mfd. (1 mmfd.) to 0.1 mfd., 1 microhenry to 100 millihenries, and 5 to 50,000 kc, hence covering from audio frequencies to ultra frequencies. This important document is now published for the first time, and we are the first to offer it. It is full-scale (no reduction from original), and will obviate any computation, as the chart may be read quickly to an accuracy of 1 per cent.

Send \$1.50 for a 13-weeks subscription for RADIO WORLD (13 issues) and order this chart (Cat. PRE-SLCH) sent free.

RADIO WORLD, 145 West 45th Street, New York, N. Y.

# NEW MODEL SHIELDED TEST OSCILLATOR!

**A**n improved modulated test oscillator, fundamental frequencies, 50 to 150 kc, enabling linking up of intermediate frequency amplifiers, t-r-f and oscillator circuits, is now ready. It is shielded in a metal box  $9\frac{1}{2}$ " wide x  $8\frac{1}{2}$ " deep x  $4\frac{1}{2}$ " high, with beautiful Japanese finish. The test oscillator is obtainable in two models, one for a-c operation, the other for battery operation. The same cabinet is used for both.

The a-c model not only is shielded but has the line blocked, that is, radio frequencies generated by the oscillator cannot be communicated to the tested set by way of the a-c line. This is a necessary counterpart to shielding, and a special circuit had to be devised to solve the problem.


The modulation in the a-c model is the a-c line frequency, 60 cycles, effected by using the line voltage on the plate of the tube. In the cabinet there is a very high resistance between the shield cabinet and the a-c, a double preventive of line-shorting and application of a-c line voltage to the user.

The oscillator is equipped with an output post. No ground connection need be used, as the circuit is sufficiently grounded through the power transformer capacity to prevent body capacity effects in tuning.

The frequencies are more accurately read than normal use requires, being never more than 1% off, and usually not more than 1% off, many readings being right on the dot (no discernible difference). The frequency stability is of a high order from 100 to 50 kc, and somewhat less from 100 to 150 kc. Zero beats are guaranteed at all frequencies.

The oscillator was designed by Herman Bernard and is manufactured under the supervision of graduates of the Massachusetts Institute of Technology.

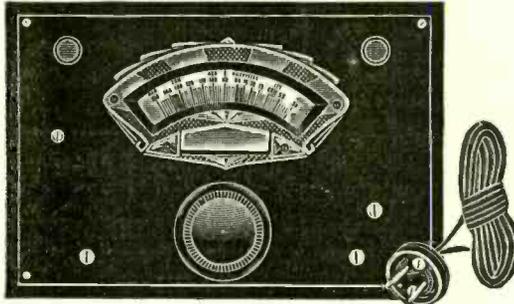Either model FREE with two-year subscription for Radio World (104 issues) \$12.00



The test oscillator has a frequency-calibrated dial, 150 to 50 kc, with 1 kc separation between 50 and 80 kc and 2 kc separation between 80 and 150 kc. Intermediate frequencies are imprinted on the upper tier. Broadcast frequencies are obtainable on tenth harmonics (500 to 1,500 kc).

**T**HE a-c model is completely self-operated and requires a 56 tube. The battery model requires external 22.5-volt small B battery and 1.5-volt dry cell, besides a 230 tube. The use of 1.5 volts instead of 2 volts on the filament increases the plate impedance and the operating stability. The battery model is modulated by a high-pitched note. Zero beats are not obtainable with the battery model.

**Directions for Use**

Remove the four screws and the slip cover, insert the 56 tube in its socket, restore the cover and screws, connect the a-c attachment plug to the wall socket, and the a-c test oscillator is ready for service.

For testing some particular set, follow the directions given by the designer or manufacturer. In the absence of such directions, use the following method.

Mentally affix a cipher to the registered frequencies on the lower tier (so 50 is read as 500, and 150 as 1,500), and set the dial for any desired broadcast frequency. Connect a wire from output post of test oscillator to antenna post of set. Leave aerial on for zero beats, or otherwise. At resonance the hum will be heard. Off resonance it will not be heard. For testing intermediate frequencies, connect the wire to plate of the first detector socket. The first detector tube may be left in place and hared wire pushed into the plate spring. The intermediates then are tuned for strongest hum response. If an output meter is used, tune for greatest needle deflection.

The battery model is connected to voltage sources as marked on oscillator outleads and is used the same way.

## RADIO WORLD

145 West 45th St., New York, N. Y.

## SOLDERING IRON FREE!

Works on 110-120 volts AC or DC, power, 50 watts. A serviceable iron, with copper tip, 5 ft. cable and male plug. Send \$1.50 for 13 weeks' subscription for Radio World and get these free! Please state if you are renewing existing subscription.

RADIO WORLD  
145 West 45th St. N. Y. City

## 115 DIAGRAMS FREE

115 Circuit Diagrams of Commercial Receivers and Power Supplies supplementing the diagrams in John F. Rider's "Trouble Shooter's Manual." These schematic diagrams of factory-made receivers, giving the manufacturer's name and model number on each diagram, include the MOST IMPORTANT SCREEN GRID RECEIVERS.

The 115 diagrams, each in black and white, on sheets  $8\frac{1}{2}$  x 11 inches, punched with three standard holes for loose-leaf binding, constitute a supplement that must be obtained by all possessors of "Trouble Shooter's Manual." to make the manual complete.

Circuits include Bosch 54 D. C. screen grid; Balkite Model F. Crosley 20, 21, 22 screen grid; Eveready series 50 screen grid; Eria 224 A.C. screen grid; Peerless Electrostatic series; Philco 76 screen grid.

Subscribe for Radio World for 8 months at the regular subscription rate of \$1.50, and have these diagrams delivered to you FREE!

Present subscribers may take advantage of this offer. Please put a cross here  to expedite extending your expiration date.  
Radio World, 145 West 45th St., New York, N. Y.

## TROUBLE SHOOTER'S MANUAL, Nos. I and II


Having assembled 2,000 diagrams of commercial receivers, power amplifiers, converters, etc., in 1,200 pages of Volume No. 1 of his Perpetual Trouble Shooter's Manual, John F. Rider, noted radio engineer, has prepared Volume No. 2 on an even more detailed scale, covering all the latest receivers. Volume No. 2 does not duplicate diagrams in Volume No. 1, but contains only new, additional diagrams, and a new all-inclusive information on the circuits covered.

Volume No. 2—Perpetual Trouble Shooter's Manual, by John F. Rider, Shipping weight 6 lbs. Order Cat. RM-VT @ \$5.00  
Volume No. 1 (8 lbs.). Order Cat. RM-VO @ \$5.00  
We pay postage in United States on receipt of purchase price with order. Canadian, Mexican and other foreign remittances must be in funds payable in New York.

RADIO WORLD  
145 West 45th Street New York City
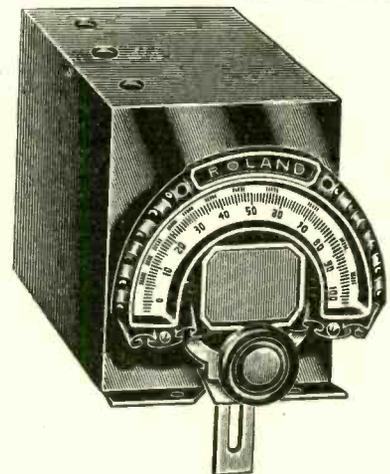
### BOOKS AT A PRICE


"The Superheterodyne," by J. E. Anderson and Herman Bernard. A treatise on the theory and practice of the outstanding circuit of the day. Special Problems of superheterodynes treated authoritatively. Per copy. (Cat. AB-SH), postpaid .50c  
"Fasthold on Radio," by Anderson and Bernard. A simple and elementary exposition of how broadcasting is conducted, with some receiver circuits and an explanation of their functioning. (Cat. AB-FH), postpaid .25c  
Guaranty Radio Goods Co., 145 W. 45th St., N. Y. City



0.0005 mfd. Scovill tuning condenser, brass plates, shaft at both ends so condenser takes 0-100 or 100-0 dials and two can be used with drum dial; sectional shields built in, trimmers affixed; total enclosed in additional shield as illustrated. Access to trimmers with screwdriver. Side holes for bringing out leads to caps of screen grid tubes. Cat. SCSHC @ \$1.95  
Same as above, with ghost type dial (travelling light). Cat. SCSHC-DL @ \$2.50

DIRECT RADIO CO., 145 W. 45 St., New York City
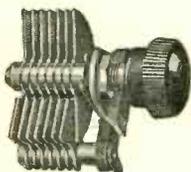
## FREE with a \$1.00 8-weeks Subscription



### NEW STAR MIDGET CONDENSERS

Choice of 15, 25, 50 and 100 mmfd. capacities. Single hole panel mount.

Here is your opportunity to get the latest product of Hammarlund, a Star Midget condenser. Send \$1 for 8 weeks subscription and get any one condenser free. Select the desired capacity.

Any two condensers free with \$2 for 17-week subscription.

Any three condensers free with \$3 for 26-weeks subscription.

Any six condensers free with \$6 for one-year subscription (52 weeks).

RADIO WORLD  
145 West 45th St., New York City

## BLUEPRINTS OF STAR CIRCUITS

### 8-TUBE AUTO SET

Sensitivity of 10 microvolts per meter characterizes the 8-tube auto receiver designed by J. E. Anderson, technical editor of Radio World, and therefore stations come in with only six feet of wire for aerial, and without ground. Most cars will afford greater aerial pickup, and besides the car chassis will be used as ground, so with this receiver you will get results. The blueprint for construction of this set covers all details, including directions for cars with negative A or positive A grounded. The circuit features are: (1) high sensitivity; (2), tunes through powerful locals and gets DX stations, 10 kc either side; (3), latest tubes, two 239 pentode r-f, two 236 screen grid, two 237 and two 238; push-pull pentodes, all of 6-volt automotive series; (4), remote tuning and volume control on steering post, plus automatic volume control due to low screen voltage on first detector; (5), running board aerial. The best car set we've published. This circuit was selected as the most highly prized after tests made on several and is an outstanding design by a recognized authority. Send for Blueprint 631, @ \$2.50


### SHORT-WAVE CONVERTER

If you want to build a short-wave converter that costs only a very few dollars, yet gives good results, furnishing all its own power from 110 volts a-c, and uses no plug-in coils, you can do so from Blueprint 630. Price.....\$2.50

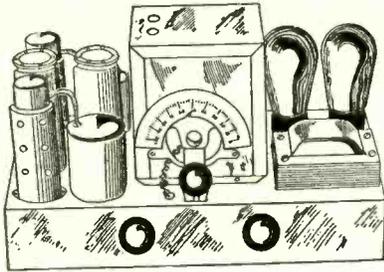
### 5-TUBE AC, T-R-F

Five-tube a-c receivers, using variable mu r-f, power detector, pentode output and 280 rectifier, are not all alike by any means. Forty circuits were carefully tested and one selected as far superior to the others. This prized circuit was the 627, and if you built it, you will always be glad you followed our authentic Blueprint, No. 627. This is the best 5-tube a-c t-r-f broadcast circuit we have ever published. Price .....\$2.50

RADIO WORLD, 145 West 45th Street, New York, N. Y.


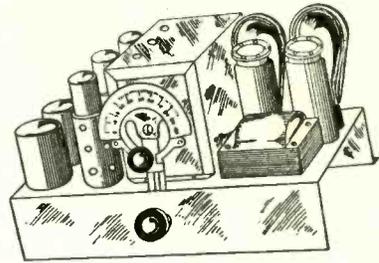
# BLUEPRINTS, COILS and CHASSIS FOR THE TUNED R-F DIAMOND OF THE AIR



## FOUR-TUBE DIAMOND


Extremely fine performance, including fetching tone quality, marks the Four-Tube A-C 1933 Diamond of the Air, blueprint of which is now available (half-scale). Many have been surprised that so much can be accomplished on a t-r-f set costs so little to build. The circuit uses a two-gang 0.00035 mfd condenser. Special coils are required. The chassis is metal, 13.75 x 6.75 x 2.5 inches.

Send \$3.00 for six months subscription (26 issues) and get the blueprint, two official shielded coils and the drilled metal chassis free. Order PRE-D-4-COMB.

## FIVE-TUBE DIAMOND

The Five-Tube A-C 1933 Diamond of the Air provides greater sensitivity than the four-tube model, also somewhat more selectivity, as a three-gang condenser is used. An infallible method of permanently suppressing oscillation is introduced, so that besides having a sensitive and selective set one will have a stable receiver. The tone is most excellent. Send \$4.00 for 34 weeks subscription (34 issues) and get the blueprint, three shielded coils and drilled metal chassis free. Chassis is 13.75 x 9 x 3 inches. Order Cat. PRE-D-5-COMB.

## Analyzer Plug and Adapters

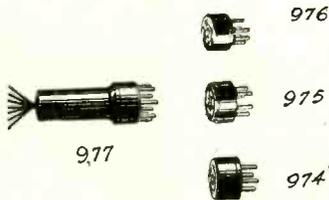

For constructing a set analyzer, an analyzer plug, to go into a receiver socket, is necessary. We offer the exclusive seven-pin analyzer plug, plain long handle as illustrated, and three adapters that enable putting the plug

connections into UX, UY and six-pin receiver sockets. The plug has 5-foot 7-lead cable. All four parts sent free on receipt of \$6.00 for one-year's subscription (52 issues). Order Cat. PRE-ANPLAD.

## 0-10,000-Ohm Resistance Meter

A 0-10,000-ohm ohmmeter and continuity tester. A rheostat is built in for correct zero resistance adjustment. The unit contains a three-cell flashlight battery. Supplied with two 5-foot-long wire leads with tip plugs. Case is 4-inch diameter baked enamel. Sent you for an order for one year's subscription for RADIO WORLD (52 weeks) at the regular rate of \$6. Order Cat. PRE-500.

We do not pay postage on resistance meter. Average postage 17c.

## RADIO WORLD and } \$7.00 RADIO NEWS

Get both of these magazines for one year for \$7.00, although the regular subscription price of RADIO WORLD alone is \$6.00 a year and that of "Radio News" alone is \$2.50 a year. Instead of paying \$8.50 you pay \$7 and you get 52 issues of RADIO WORLD (one a week) and 12 issues of "Radio News" (one a month). "Radio News" recently bought "Citizens Radio Call Book," and "Technical Review" and consolidated them with "Radio News." This offer at this combination price applies only to United States and possessions. Send \$7.00 and order Cat. PRE-RWRN. To Canadian and other Foreign subscribers the combination price offer is at \$8.50 for these two magazines. Order Cat. PRE-FOR-RWRN.

## RIDER'S MANUAL

The standby of the service man is John F. Rider's "Perpetual Trouble Shooter's Manual," of which Vols. 1 and 2 have been published. Vol. 1 consists of 2,000 diagrams of commercial receivers, power amplifiers, converters, etc. Total pages, 1200. Vol. 2 contains additional diagrams on the same basis as above, but in Vol. 2 there is no duplication of any of the diagrams printed in Vol. 1. To get Vol. 1 free, send \$9.00 for 1½-year subscription (78 weeks) and order Cat. PRE-RM-1. To get Vol. 2 free, send \$9.00 for 1½-year subscription (78 weeks) and order Cat. PRE-RM-2.

## PHONOGRAPH MOTOR

Allen-Hough synchronous phonograph motor, 78 revolutions per minute; takes up to 12-inch records. Works from a-c line. 50-60 cycles, 105-120 volts. Equipped with felt-covered turntable. To start the motor give it a slight impetus. Fits into 3-inch depth, hence handy for compact installations. Given free with 34-weeks subscription at \$4.00. Order Cat. PRE-PHOMO.

## A-C, D-C SOLDERING IRON



A serviceable iron that works on a-c (any frequency) and d-c, 105-120 volts. Sent free on receipt of \$1.50 for three-months subscription (13 issues). Order Cat. PRE-SOLIN.

## R-F CHOKE COILS

These coils have 50, 100, 200, 400 and 800 turns, diameter 1 inch, and are suitable for detector plate filtering, screen filtering, grid and plate loads, etc. The 50 is for short waves, 100 for television band, 200 for broadcast band, 400 for high intermediate frequencies (450 to 300) and 800 for lower intermediate frequencies. Any four, or four of a kind, or combinations not exceeding total of four, sent free on receipt of \$1.00 for 8 weeks trial subscription. Order Cat. PRE-4-CH and state chokes desired, by quantity and number of turns.

## TWO BOOKS BY ANDERSON AND BERNARD

"The Superheterodyne," by J. E. Anderson and Herman Bernard. A treatise on the theory and practice of the outstanding circuit of the day. Special problems of superheterodynes treated authoritatively. "Foothold on Radio." A simple and elementary exposition of how broadcasting is conducted, with some receiver circuits and an explanation of their functioning. Both books sent free on receipt of \$1.00 for 8 weeks trial subscription. Order Cats. PRE-SH-FH.

## CHOICE OF PANEL TYPE METERS

One meter sent free with each \$1.00 trial subscription (8 weeks). Order Cat. PRE-MTR and add the number of the meter to the catalogue number. Any number of meters may be ordered on the equivalent extended subscription basis.

|                           |         |
|---------------------------|---------|
| 0-6 Voltmeter D.C.        | No. 326 |
| 0-50 Voltmeter D.C.       | No. 337 |
| 6-Volt Charge Tester D.C. | No. 23  |
| 0-10 Amperes D.C.         | No. 338 |
| 0-25 Milliampere D.C.     | No. 325 |
| 0-50 Milliampere D.C.     | No. 350 |
| 0-100 Milliampere D.C.    | No. 390 |
| 0-300 Milliampere D.C.    | No. 399 |
| 0-400 Milliampere D.C.    | No. 394 |

## HANDY PACKAGE OF PARTS

One grid condenser of 0.00025 mfd., with clips; one 5-to-7 meg. fixed grid leak; one knob with ¼-inch shaft; one a-c cable and plug. All sent on receipt of \$1.00 for 8-weeks trial subscription. Order Cat. PRE-HANPKG.

## SHIELDS FOR 57, 58 TUBES

Aluminium shields of the type specified by the tube manufacturers for sensitive circuits, so that the shield top fits snugly about the tube dome, are obtainable, six free on receipt of \$1.00 for 8 weeks trial subscription. Order Cat. PRE-TUBSH.

**RADIO WORLD, 145 West 45th Street, New York, N. Y.**  
(WE PAY POSTAGE ON ALL PRODUCTS LISTED ON THIS PAGE, EXCEPT OHMMETER).