

SEPT. 9

1933

15c

53 AS A MIXER

RADIO

REG. U.S. PAT. OFF.

WORLD

*Improved Office
Communicator*

**Constant Output Tube
Possibility Discussed**

The First and Only National Radio Weekly
Twelfth Year

598th Consecutive Issue

Television Illumination Gain

★ ★

**CHARTS OF
CHARACTERISTICS
OF ALL TUBES**

With Diagrams of Socket Connections

★ ★

The THOR COMMUNICATOR

AC-DC OPERATION

as described in this issue

For use as a PORTABLE AMPLIFIER, as an INTER-OFFICE COMMUNICATOR, or for RETAIL STORE DEMONSTRATING.

KIT, with drilled Chassis, Cabinet, all necessary parts and S. J. American Microphone, \$12.50 List

(Less Tubes)

\$9.95

Uses 1'77, 2-'43, 1-25Z5 Tube


ON DEMONSTRATION

MAIL ORDERS FILLED

THOR'S BARGAIN BASEMENT

167 Greenwich St., N. Y. City

LAPEL MICROPHONE

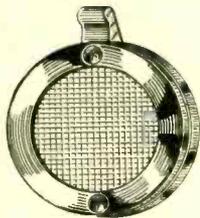

A single-button carbon-granule lapel microphone, impedance 200 ohms, requiring 4.5-volt excitation, of good frequency characteristics, and both handy and inconspicuous. Outside diameter, 1 1/4 inches. The case is chromium-plated brass. The excitation may be provided by introducing the microphone in a cathode circuit carrying around 20 to 25 milliamperes, or a 4.5-volt C biasing battery may be used. Net price, \$2.95.

RELIABLE RADIO COMPANY
145 West 45th Street, New York, N. Y.

SOLDERING IRON FREE!

Works on 110-120 volts AC or DC, power, 50 watts. A serviceable iron, with copper tip, 5 ft. cable and male plug. Send \$1.50 for 13 weeks' subscription for Radio World and get these free! Please state if you are renewing existing subscription.

RADIO WORLD

145 West 45th St. N. Y. City

COMPLETE YOUR SUMMER FILE OF RADIO WORLD

If you are short of any summer issues of Radio World, send us 15c for each copy or any 8 for \$1.00. Or start your subscription with any date you wish. Radio World, 145 W. 45th St., N. Y. C.

AUTO SPECIAL FOR September Only



The complete ALL-ELECTRIC AUTO RECEIVER, as described in the June 17th issue of Radio World, will now be sold for \$19.95. This includes 5 Matched Sylvania Tubes, Remote Control, Dynamic Speaker and all accessories, including spark plug suppressors, aerial wire and ready for complete installation. It employs 1-77, 1-42, 1-84 and 2-39 tubes. It uses a special high-gain Auto circuit that receives distance stations. One Unit, size 8x8x7. Easily installed. Automatic Volume control Tube. Three-Gang Condenser. Totally shielded. Lock Switch. Illuminated Remote Control. Hum free and Noiseless. Packed carefully.
List Price, \$39.50 Net Price, \$19.95
POSTAL RADIO CORP.
133 LIBERTY STREET, NEW YORK CITY

BLUEPRINT

627. Five-tube tuned radio frequency, A-C operated; covers 200 to 550 meters (broadcast band), with optional additional coverage from 80 to 204 meters, for police calls, television, airplane, amateurs, etc. Variable mu and pentode tubes. Order BP-627 @.....25c

RADIO WORLD, 145 W. 45th St., New York, N. Y.

CIRCUITS AND SERVICE DETAILS OF COMMERCIAL RECEIVERS in issues of Radio World as follows: The Philco Model 15 Superheterodyne, Oct. 29, 1932; Philco's 4-tube Superheterodyne, Dec. 10, 1932; The Philco 37, Dec. 31, 1932; Philco Service Bulletin—No. 146, Models 89 and 19, Jan. 21, 1933; The Model 28, Newest Spartan Set, Nov. 5, 1932; Spartan 14, 14A, and 18, Jan. 7, 1933; The Majestic 324, Nov. 12, 1932; Stromberg-Carlson's Latest Circuits, Nos. 37, 38, 39, 40, and 41 Receivers, Nov. 19, 1932; The Pilot Dragon, Nov. 19, 1932; National Co. Short-Wave Receivers, Dec. 3, 1932; The New Fada Chassis, Dec. 24, 1932; Howard Model M, Jan. 7, 1933; The Comet "Pro," Jan. 14, 1933; Gulbransen Series 322, Jan. 14, 1933; United American Bosch Service Corp. Instructions, Jan. 21, 1933; Crosley Models 132-P and 141, Jan. 28, 1933; The Colonial C-995, Feb. 11, 1933; Kennedy Model 563, Feb. 11, 1933; U. S. Radio No. 700, Feb. 18, 1933; Bosch 250 and 251, also Clarion Model 300, and Zenith 430 and 440, Feb. 25, 1933. 15c a copy, any 8 issues, \$1.00. Radio World, 145 W. 45th St., New York City.

Quick-Action Classified Advertisements

7c a Word—\$1.00 Minimum

CHEMISTS, ELECTRICIANS, AMATEUR SCIENTISTS—join Experimenters Club. Apparatus given free! Big monthly magazine. Send 25c for 3 months' subscription and particulars. Science-craft, 5049-N. Bernard, Chicago.

MANUSCRIPTS, typed, paraphrased and corrected, 75c 1000 words. Sylvia Camos, 1107 Chouteau, St. Louis, Mo.

"THE FORD V-EIGHT—'B'-FOUR—'BB'-TRUCK," by C. B. Manly. A New and Practical Book for Everyone Interested in the Construction, Adjustment, Upkeep and Repair of The New Fords. Over 250 pages, 125 illustrations. Complete cross index. Pocket size, flexible leatherette cover. Price \$2.00. Radio World, 145 W. 45th St., New York, N. Y.

"SOUND PICTURES," by Cameron & Rider. Over 1,100 pages, 500 illustrations. The whole question of Sound Motion Pictures treated from a new angle. A Complete Guide for Trouble Shooting. Explains in detail the construction, operation and care of sound recording and reproducing equipment. Price \$7.50. Radio World, 145 W. 45th St., New York City.

RADIO WORLD AND POPULAR MECHANICS MAGAZINE—Radio World is \$6.00 a year, and Popular Mechanics Magazine is \$2.50 a year. Popular Mechanics Magazine does not cut rates, but Radio World will send both publications to you for one year for \$7.00. Radio World, 145 West 45th St., New York City.

HENLEY'S "TWENTIETH CENTURY BOOK OF RECIPES, FORMULAS & PROCESSES," New 1933 Edition. Ten thousand processes, recipes, trade secrets and money-making formulas. For the laboratory, workshop, factory and home. Some subjects fully covered: Dyes, Inks, Waterproofing, Perfumes, Cement, Plating, Glass, Dentifrices, Varnishes, Soaps, Glues, Paints, Adhesives, Emulsifying, Hairdressings, Cosmetics, Oils. Price, \$4.00. Book Dept., Radio World, 145 W. 45th St., New York City.

NEW HANDY SERVICEMEN'S MANUAL

Full of important money-making ideas—data—trouble-shooting, etc.
25c QUANTITY LIMITED
RESERVE YOUR COPY NOW!
TRY-MO RADIO CO., INC.
85 Cortlandt Street, New York City
Dist. RW

NO MORE CALCULATING OF INDUCTANCE!

Get your answers accurately from curves in the only book of its kind in the world, "The Inductance Authority," by Edward M. Shiepe, B.S., M.E.E. Two charts, one in the book, the other (18x20 inches) as a supplement, relate inductance, capacity and frequency, the large one from ultra to audio frequencies. Thirty-five charts, with 13 curves on each, cover the numbers of turns and inductive results for solenoids, for 35 wire sizes and insulation types. Wire sizes are Nos. 14, 16, 18, 20, 22, 24, 26, 28, 30, 31 and 32. Insulations: single silk, double silk—single cotton, double cotton and enamel. Form diameters: 3/4, 7/8, 1, 1 1/8, 1 1/2, 1 3/4, 2, 2 1/4, 2 1/2, 2 3/4 and 3 inches. Pages 9x12, printed on one side only. Price, \$2.00 postpaid, including supplement.

RADIO WORLD
145 WEST 45TH ST., NEW YORK CITY

PRICES GO UP SEPT. 15 TROUBLE SHOOTER'S MANUAL, Nos. I, II and III

Having assembled 2,000 diagrams of commercial receivers, power amplifiers, converters, etc., in 1,200 pages of Volume No. 1 of his Perpetual Trouble Shooter's Manual, John F. Rider, noted radio engineer, has prepared Volume No. 2 on an even more detailed scale, covering all the latest receivers. Volume No. 2 does not duplicate diagrams in Volume No. 1, but contains only new, additional diagrams, and a new all-inclusive information on the circuits covered.
Volume No. 3 (Recently issued). Order Cat. RM\$7.50
Volume No. 2—Perpetual Trouble Shooter's Manual, by John F. Rider, Shipping weight 6 lbs. Order Cat. RM-VT @.....\$5.00
Volume No. 1 (8 lbs.). Order Cat. RM-VO @.....\$5.00
We pay postage in United States on receipt of purchase price with order. Canadian, Mexican and other foreign remittances must be in funds payable in New York.

RADIO WORLD
145 West 45th Street New York City

RADIO WORLD and "RADIO NEWS"

BOTH FOR ONE YEAR \$7.00 Canadian and Foreign \$1.50 extra

You can obtain the two leading radio technical magazines that cater to experimenters, service men and students, the first and only national radio weekly and the leading monthly for one year each, at a saving of \$1.50. The regular mail subscription rate for Radio World for one year, a new and fascinating copy each week for 52 weeks, is \$6.00. Send in \$1.00 extra, get "Radio News" also for a year—a new issue each month for twelve months. Total 64 issues for \$7.00.
RADIO WORLD, 145 West 45th Street, New York, N. Y.

SPECIAL SMALL POWER TRANSFORMER


Filament-plate transformer, for oscillators, 1 or 2-tube sets, etc.
Primary, 110 volts a-c.
Secondary A, 2.5 volts, center-tapped; stands up to 3 amperes.
Secondary B, 110 volts, not center-tapped.
Excellent for test oscillators with a-c in plate.

Price, \$1.10
RADIO WORLD
145 West 45th Street New York, N. Y.

PHONES OR SPEAKER

Served by These Short-Wave Sets

By Herman Bernard

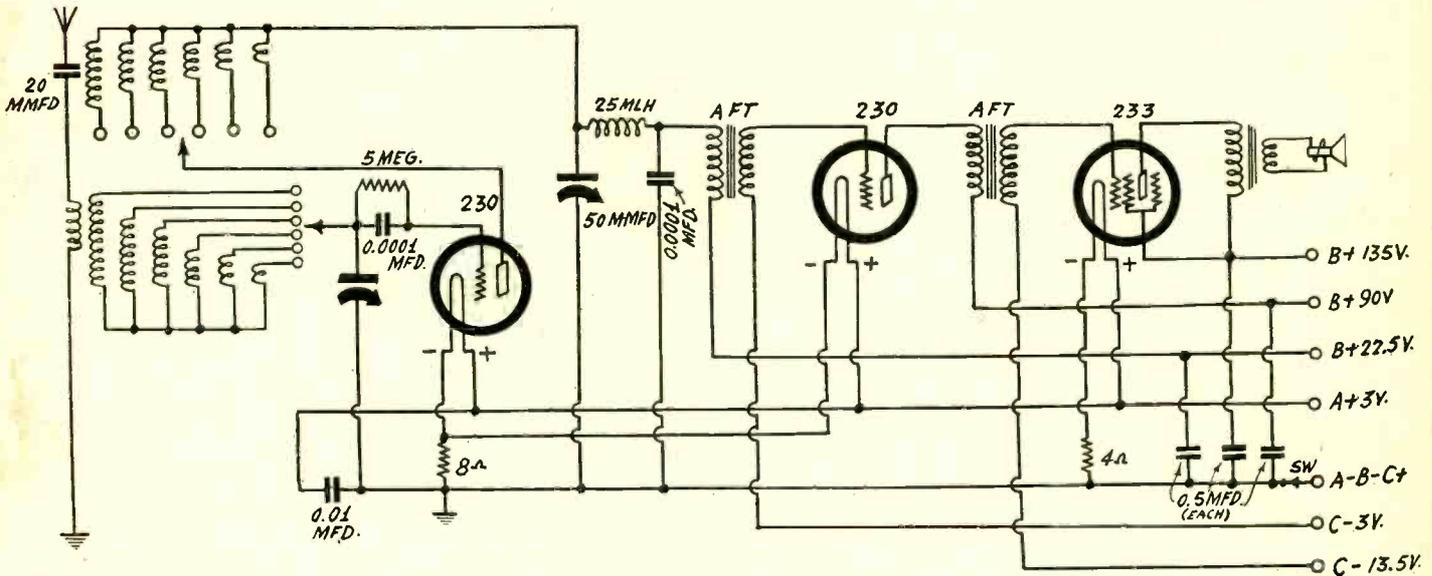

A three-tube short-wave battery-operated set, using 2-volt tubes, and drawing little B current, around 22 milliamperes. A switch is used for band changing.

THE popular two-tube and three-tube short-wave battery sets, one for earphone, the other for speaker reception, are shown herewith as switch-operated. If the tuning condenser is small enough, say, 80 mmfd., then six coils will cover the short-wave band, and the spreadout will be pretty good, in fact, much better than that which results from the four-coil-larger-capacity system.

The antenna series capacity is made small purposely, so that regeneration will be present throughout the tuning scale, a purpose aided by a high value of leak, and so that the antenna may be switched through this condenser to the various coils. This would require simply connecting the ground side of the series condenser to the stator side of the grid leak, and omitting the primary, which is shown as a symbol in case anybody wants to use a primary. If such a primary is used it really should be repeated for each tuned coil, which is a job.

Good Switch Needed

It is all right to have to provide a tickler common to two coils, thus three ticklers, but many would prefer a separate tickler for each tuned secondary, because of the greater flexibility of adjustment to correspond to the 50 mmfd. feedback condenser.

The only rub is the switch, and the only good switch to come to the author's attention was one used in expensive set analyzers and made by a manufacturer of precision instruments. This has low capacity, also positive contacts at all points, infallibly and most agreeably, and, being of the wiping contact type, improves with use. Unless one goes in for a good switch he had much better adhere to plug-in coils.

A 2-to-1 tuning ratio would prevail, as outlined last week (issue of September 2d), and that is not at all bad.

The winding data for the coils, 80

mmfd. maximum capacity for tuning, form diameter 0.75 inch, are as follow:

Coil No.	Frequency Range Mgc.	Inductance	No. Turns	Winding Space
1	1.5 to 3	140.8	111; 32 en.	1"
2	3 to 6	35.2	58.2; 28 en.	1"
3	6 to 12	8.8	33.75; 18 en.	3/4"
4	12 to 24	2.2	11.5; 18 en.	3/4"
5	24 to 48	0.56	4.8; 18 en.	3/4"
6	48 to 96	0.14	2.2; 18 en.	3/8"

70-Mu Power Tube

The ratio of the audio transformers is not critical, as at least 3-to-1 would be used, though it is not especially good for the speaker set to go much beyond 5-to-1, as the quality then begins to decline. The speaker set uses a pentode output tube, the 233, which has a power output of 0.7 watt, which is enough for such a set. And besides the power output should not be confused with the sensitivity. The tube has a voltage amplification factor of 70.

The speaker may be a dynamic, but if so would naturally be used with a storage battery, for field excitation, whereupon the resistors in the filament legs would


be 32 ohms and 16 ohms, respectively, and the one in the earphone set 32 ohms.

However, for dry-cell operation a magnetic speaker may be used, and may be connected directly in the plate circuit, without filtered output or coupling transformer, provided its impedance is high enough (7,000 ohms), otherwise an output transformer would be used.

Transformer Selection

In selecting the transformer, the impedance ratio is that of 7,000 ohms to the actual impedance of your speaker. Most magnetic speakers have an impedance around 4,000 ohms, so the ratio would be 7,000 to 4,000 ohms, primary to secondary.

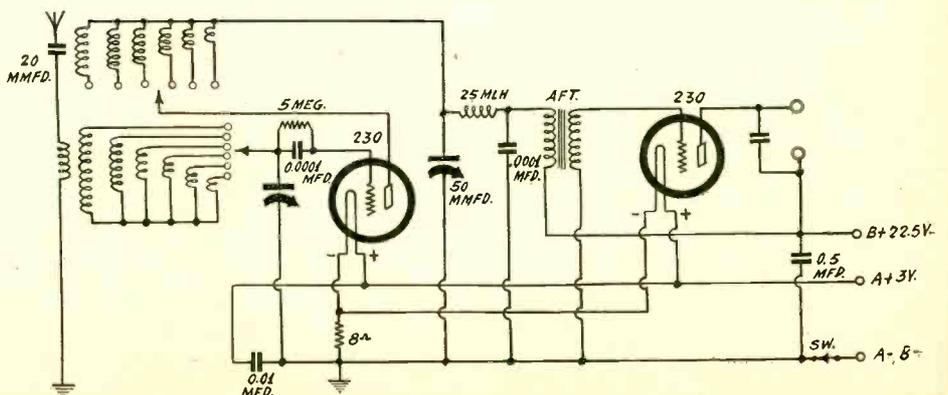The earphone set has phones directly in the audio amplifier tube plate circuit, with any small condenser across the phones, 0.0001 mfd. to 0.001 mfd. If there is body capacity effect in handling the phones, put a 25-millihenry r-f choke coil in series with the plate lead to one phone connection.



The two-tube equivalent for earphone use.

CONSTANT OUTPUT

Tube Would Be Its Own A-V-C Supply

By W. J. Mellish

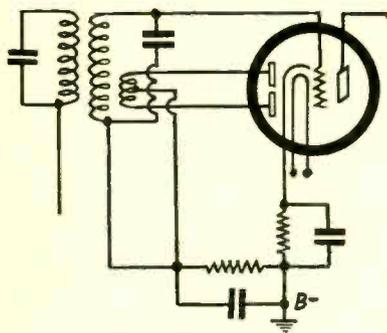


FIG. 1

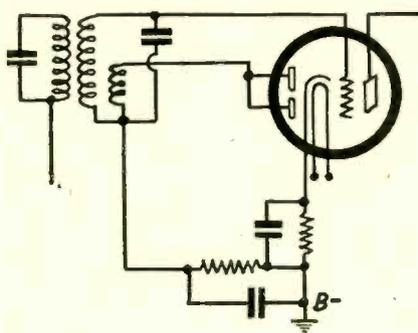


FIG. 2

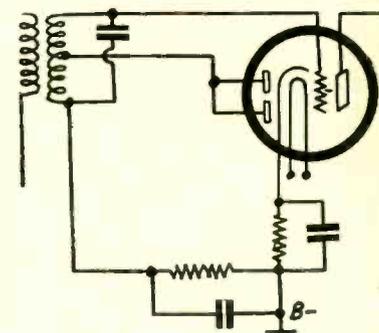


FIG. 3

SOME day there will be a constant-output tube. That is, the tube will be an amplifier and have in the envelope a rectifier that controls the amplifier, so that the output level remains the same despite carrier amplitude rise or fall. This is built-in automatic volume control. An approximation of this result may be obtained with the present 55, which is one diode-and-amplifier tube that has a sufficiently extended cutoff to permit the method to work over large swings. There is no remote cutoff amplifier with diode.

Fig. 1 shows an intermediate transformer, coupled with which is an extra winding, which is center-tapped, to permit full-wave rectification in the diode. The extra winding feeds the load resistor, and the grid return of the amplifier is connected to the ungrounded end of this resistor. A small bias is supplied to the amplifier by the cathode-leg resistor, to prevent zero bias at no signal, or at zero radio-

frequency voltage during any alternation. Fig. 2 shows the same condition, except that the rectifier is half-wave, hence the voltage across the load resistor (the augmentative bias voltage) is twice as great as in the previous example, other factors being equal.

Fig. 3 shows the use of a transformer with a center tap, or tap located off-center, but nearer to the return than to the grid, for half-wave rectification. If the tap is at center the voltage taken off may be too great, provided the tube is one of a chain at the same frequency.

The action in all instances is as follows: The carrier voltage is developed across the primary of a transformer and due to the inductive coupling is present, perhaps in amplified form, in the secondary.

Instead of grounding the secondary directly, which under these circumstances can not be done, a resistor is interposed. It is the same resistor that is the load

on the rectifier. The extra coupling coil is in series with this resistor.

When the anode is positive in respect to the cathode, being made so by the signal, current flows through the rectifier. Thus in the half-wave rectifier, during the negative cycle there is no contribution of auxiliary bias by the device.

In the full-wave system there is always rectification, because one anode at a time is always positive, though at that same instant another anode is negative.

Hence the bias varies with the carrier. It also varies somewhat with the audio frequency, since the audio frequency is an amplitude modulation of the carrier.

The rectifier itself may be linear. Such a tube as the 55 may provide linearity, say, between 5 and 15 volts. If the cathode biasing resistor is such as to make the starting bias 5 volts, then the rectifier has to overcome 5 volts before rectification takes place.

Cities Will Have Vision Transmitters in Relay System, Says Hollis Baird

By Hollis Baird

Chief Engineer, Shortwave and Television Laboratory

Chain television is going to be one of the first requirements of commercial television, but the links in that chain need a wholly new method of interconnection, a method which challenges the skill of the engineer and fires the imagination of the man in the street who wants to know the "how" of things.

Tall buildings, high hills and great towers will be at a premium for television. Ultra-short waves will be used to get the space (or width) in the ether necessary for sending the fine details that will make up the home pictures of the future. As ultra-short waves have more the characteristics of light, they can easily penetrate darkness and fog, but solid objects rapidly weaken them. Thus, the visual horizon, from a given point, promises to be the range limit of an ultra-short wave station.

The television broadcaster will have a range for his main station, depending on how high he can get the transmitting antenna into the air; the higher its location, the broader the horizon and thus the greater

distance the signal will travel satisfactorily. When radio became good entertainment it had to expand its field to meet the public demand. So will television. Present chain radio broadcasting is sent over telephone wires, but the voice requirements are only one four-hundredth of television requirements and no present telephone circuits, nor any that appear in the offing, will be able to carry the television signals.

A relay system is the solution. At the farthest visible point on the horizon from the main transmitter a receiving station will pick up the television signals and relay them to another similar station. This point-to-point transmitting is called "directional" and the action is repeated until the required distance is covered. When the signal reaches the city desired, it will be put out on a non-directional antenna and the program will then cover a circle some 30 miles in radius.

As an instance, a 200-mile airline between two cities would require five 1,000-watt relay stations 30 miles apart. Sending ultra-short waves out on a narrow focused beam

requires but little power. This same signal to be clearly heard over a radius of 30 miles necessitates a transmitter as powerful as that now used for city radio broadcasting stations. This means that every sizable city in the country will eventually have its own powerful television station interconnected by relay stations to various key television stations from which the programs will emanate.

At first thought, the erecting of a sufficient number of powerful stations and small relay stations to provide nation-wide reception appears to be a herculean task but, as in radio, public needs are invariably met when the demands become great enough. Research and invention have a kindly way of meeting such requirements when they arise.

These stations, dotting the countryside, transmitting television from point to point, create an exciting picture of the not-too-distant future when skilled artists will appear in our homes over chain television systems.

Complete Tube Characteristics

TYPE	NAME	BASE	SOCKET CONNECTIONS	DIMENSIONS MAXIMUM OVERALL LENGTH X DIAMETER	CATHODE TYPE #	RATING			USE	PLATE SUPPLY VOLTS	GRID VOLTS	SCREEN VOLTS	SCREEN MILLI-AMP.	PLATE MILLI-AMP.	A-C PLATE RESISTANCE OHMS	MUTUAL CONDUCTANCE MICROHMOS	VOLT-AGE AMPLIFICATION FACTOR	LOAD FOR STATED POWER OUTPUT OHMS	POWER OUTPUT WATTS	TYPE
						FILAMENT OR HEATER	PLATE	SCREEN												
						VOLTS	AMPERES	MAX. VOLTS	MAX. VOLTS	Values to right give operating conditions and characteristics for indicated typical use										
RCA-1A6	PENTAGRID CONVERTER 0	SMALL 6-PIN	FIG. 28	4 1/2" x 1 3/8"	D-C FILAMENT	2.0	0.06	180	67.5	—	—	—	—	—	—	—	—	—	—	C-1A6
RCA-2A3	POWER AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	5 1/2" x 2 1/4"	FILAMENT	2.5	2.5	250	—	—	—	—	—	—	—	—	—	—	—	C-2A3
RCA-2A5	POWER AMPLIFIER PENTODE	MEDIUM 6-PIN	FIG. 15A	4 1/2" x 1 1/2"	HEATER	2.5	1.75	250	250	—	—	—	—	—	—	—	—	—	—	C-2A5
RCA-2A6	DUPLEX-DIODE HIGH-MU TRIODE	SMALL 6-PIN	FIG. 13	4 1/2" x 1 3/8"	HEATER	2.5	0.8	250	—	—	—	—	—	—	—	—	—	—	—	C-2A6
RCA-2A7	PENTAGRID CONVERTER B	SMALL 7-PIN	FIG. 20	4 1/2" x 1 3/8"	HEATER	2.5	0.8	250	100	—	—	—	—	—	—	—	—	—	—	C-2A7
RCA-2B7	DUPLEX-DIODE PENTODE	SMALL 7-PIN	FIG. 21	4 1/2" x 1 3/8"	HEATER	2.5	0.8	250	125	—	—	—	—	—	—	—	—	—	—	C-2B7
RCA-6A4	POWER AMPLIFIER PENTODE	MEDIUM 5-PIN	FIG. 6	4 1/2" x 1 1/2"	FILAMENT	6.3	3.0	180	180	—	—	—	—	—	—	—	—	—	—	C-6A4 also LA
RCA-6A7	PENTAGRID CONVERTER 0	SMALL 7-PIN	FIG. 20	4 1/2" x 1 3/8"	HEATER	6.3	3.0	250	100	—	—	—	—	—	—	—	—	—	—	C-6A7
RCA-6B7	DUPLEX-DIODE PENTODE	SMALL 7-PIN	FIG. 21	4 1/2" x 1 3/8"	HEATER	6.3	3.0	250	125	—	—	—	—	—	—	—	—	—	—	C-6B7

0 Grids #3 and #5 are screen. Grid #4 is signal-input control-grid.

Applied through plate coupling resistor of 200000 ohms. Applied through plate coupling resistor of 250000 ohms.

RCA-6F7	TRIODE-PENTODE	SMALL 7-PIN	FIG. 27	4 1/2" x 1 3/8"	HEATER	6.3	0.3	250	100	—	—	—	—	—	—	—	—	—	—	C-6F7
UX-300-A	DETECTOR TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	5.0	0.25	45	—	—	—	—	—	—	—	—	—	—	—	CX-300-A
RCA-01-A	DETECTOR-AMPLIFIER	MEDIUM 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	5.0	0.25	135	—	—	—	—	—	—	—	—	—	—	—	C-01-A
RCA-10	POWER AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	5 1/2" x 2 1/4"	FILAMENT	7.5	1.25	425	—	—	—	—	—	—	—	—	—	—	—	C-10
WD-11	DETECTOR-AMPLIFIER TRIODE	WD 4-PIN	FIG. 12	4 1/2" x 1 1/2"	D-C FILAMENT	1.1	0.25	135	—	—	—	—	—	—	—	—	—	—	—	C-11
WX-12	DETECTOR-AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	1.1	0.25	135	—	—	—	—	—	—	—	—	—	—	—	CX-12
UX-112-A	DETECTOR-AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	5.0	0.25	150	—	—	—	—	—	—	—	—	—	—	—	CX-112-A
RCA-19	TWIN AMPLIFIER	SMALL 6-PIN	FIG. 25	4 1/2" x 1 3/8"	D-C FILAMENT	2.0	0.26	135	—	—	—	—	—	—	—	—	—	—	—	C-19
UX-120	POWER AMPLIFIER TRIODE	SMALL 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	3.3	0.132	135	—	—	—	—	—	—	—	—	—	—	—	CX-120
RCA-22	R-F AMPLIFIER TETRODE	MEDIUM 4-PIN	FIG. 4	5 1/2" x 1 1/2"	D-C FILAMENT	3.3	0.132	135	67.5	—	—	—	—	—	—	—	—	—	—	C-22
RCA-24-A	R-F AMPLIFIER TETRODE	MEDIUM 5-PIN	FIG. 9	5 1/2" x 1 1/2"	HEATER	2.5	1.75	275	90	—	—	—	—	—	—	—	—	—	—	C-24-A
RCA-26	AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/2" x 1 1/2"	FILAMENT	1.5	1.05	180	—	—	—	—	—	—	—	—	—	—	—	C-26
RCA-27	DETECTOR-AMPLIFIER TRIODE	MEDIUM 5-PIN	FIG. 8	4 1/2" x 1 1/2"	HEATER	2.5	1.75	275	—	—	—	—	—	—	—	—	—	—	—	C-27
RCA-30	DETECTOR-AMPLIFIER TRIODE	SMALL 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	2.0	0.06	180	—	—	—	—	—	—	—	—	—	—	—	C-30

For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode.


Applied through plate coupling resistor of 250000 ohms or 500-henry choke shunted by 0.25 megohm resistor. *Maximum.

RCA-31	POWER AMPLIFIER TRIODE	SMALL 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	2.0	0.13	180	—	—	—	—	—	—	—	—	—	—	—	C-31
RCA-32	R-F AMPLIFIER TETRODE	MEDIUM 4-PIN	FIG. 4	5 1/2" x 1 1/2"	D-C FILAMENT	2.0	0.06	180	67.5	—	—	—	—	—	—	—	—	—	—	C-32
RCA-33	POWER AMPLIFIER PENTODE	MEDIUM 5-PIN	FIG. 9	4 1/2" x 1 1/2"	D-C FILAMENT	2.0	0.26	135	135	—	—	—	—	—	—	—	—	—	—	C-33
RCA-34	SUPER-CONTROL R-F AMPLIFIER PENTODE	MEDIUM 4-PIN	FIG. 4A	5 1/2" x 1 1/2"	D-C FILAMENT	2.0	0.06	180	67.5	—	—	—	—	—	—	—	—	—	—	C-34
RCA-35	SUPER-CONTROL R-F AMPLIFIER TETRODE	MEDIUM 5-PIN	FIG. 9	5 1/2" x 1 1/2"	HEATER	2.5	1.75	275	90	—	—	—	—	—	—	—	—	—	—	C-35
RCA-36	R-F AMPLIFIER TETRODE	SMALL 5-PIN	FIG. 5	4 1/2" x 1 3/8"	HEATER	6.3	0.3	250	90	—	—	—	—	—	—	—	—	—	—	C-36
RCA-37	DETECTOR-AMPLIFIER TRIODE	SMALL 5-PIN	FIG. 8	4 1/2" x 1 3/8"	HEATER	6.3	0.3	250	—	—	—	—	—	—	—	—	—	—	—	C-37
RCA-38	POWER AMPLIFIER PENTODE	SMALL 5-PIN	FIG. 9A	4 1/2" x 1 3/8"	HEATER	6.3	0.3	250	250	—	—	—	—	—	—	—	—	—	—	C-38
RCA-39-44	SUPER-CONTROL R-F AMPLIFIER PENTODE	SMALL 5-PIN	FIG. 9A	4 1/2" x 1 3/8"	HEATER	6.3	0.3	250	90	—	—	—	—	—	—	—	—	—	—	C-39-44
UX-940	VOLTAGE AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/2" x 1 1/2"	D-C FILAMENT	5.0	0.25	180	—	—	—	—	—	—	—	—	—	—	—	CX-140
RCA-41	POWER AMPLIFIER PENTODE	SMALL 6-PIN	FIG. 15A	4 1/2" x 1 3/8"	HEATER	6.3	0.4	250	250	—	—	—	—	—	—	—	—	—	—	C-41
RCA-42	POWER AMPLIFIER PENTODE	MEDIUM 6-PIN	FIG. 15A	4 1/2" x 1 1/2"	HEATER	6.3	0.7	250	250	—	—	—	—	—	—	—	—	—	—	C-42

For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode. Either A, C, or D, C. may be used on filament or heater, except as specifically noted. For use of D, C. on A-C filament types, decrease stated grid volts by 1/2 (approx.) of filament voltage.

Applied through plate coupling resistor of 250000 ohms or 500-henry choke shunted by 0.25 megohm resistor. Applied through plate coupling resistor of 100000 ohms. Applied through plate coupling resistor of 250000 ohms. *Maximum.

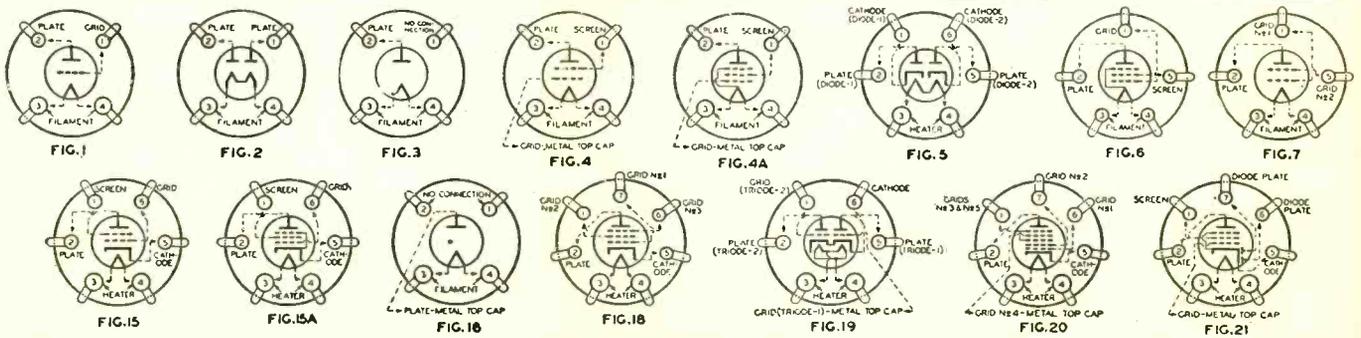TUBE SYMBOLS AND BOTTOM VIEWS OF SOCKET CONNECTIONS



INDEX OF TYPES BY USE AND BY CATHODE VOLTAGE

CATHODE VOLTS	POWER AMPLIFIERS	VOLTAGE AMPLIFIERS Including Duplex-Diode Types	CONVERTERS IN SUPERHETERODYNES	DETECTORS	MIXER TUBES IN SUPERHETERODYNES	RECTIFIERS	CATHODE VOLTS
1.1	—	11, 12, 864	—	11, 12, 864	—	—	1.1
1.5	—	26	—	—	—	—	1.5
2.0	19, 31, 33, 49	30, 32, 34	1A6	30, 32	1A6, 34	—	2.0
2.5	2A3, 2A5, 45, 46, 47, 53, 59	2A6, 2B7, 24-A, 27, 35, 55, 56, 57, 58	2A7	2A6, 2B7, 24-A, 27, 55, 56, 57	2A7, 35, 58	82, 866 (C-366)	2.5
3.3	70	22, 99	—	99	—	—	3.3

Chart, with Socket Connections

TYPE	NAME	BASE	SOCKET CONNECTIONS	DIMENSIONS MAXIMUM OVERALL LENGTH X DIAMETER	CATHODE TYPE #	RATING			USE Values to right give operating conditions and characteristics for indicated typical use	PLATE SUPPLY VOLTS	GRID VOLTS	SCREEN VOLTS	SCREEN MILLI-AMP.	PLATE MILLI-AMP.	A-C PLATE RESISTANCE OHMS	MUTUAL CONDUCTANCE MICRO-MHMS	VOLTAGE AMPLIFICATION FACTOR	LOAD FOR STATED POWER OUTPUT OHMS	POWER OUTPUT WATTS	TYPE	
						FILAMENT OR HEATER VOLTS	PLATE AMPERES	SCREEN MAX. VOLTS													
RCA-43	POWER AMPLIFIER PENTODE	MEDIUM 8-PIN	FIG. 15A	4 1/4" x 1 1/2"	HEATER	25.0	0.3	135	135	CLASS A AMPLIFIER	100	-15.0	100	4.0	20.0	45000	2000	90	4500	0.90	C-43
RCA-45	POWER AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/4" x 1 1/2"	FILAMENT	2.5	1.5	275	---	CLASS A AMPLIFIER	180	-31.5	180	---	31.0	1650	2125	3.5	2700	0.82	C-45
RCA-46	DUAL-GRID POWER AMPLIFIER	MEDIUM 5-PIN	FIG. 7	5 3/8" x 2 1/4"	FILAMENT	2.5	1.75	250	---	CLASS A AMPLIFIER	250	-33.0	---	---	22.0	2380	2350	5.6	6400	1.20	C-46
RCA-47	POWER AMPLIFIER PENTODE	MEDIUM 5-PIN	FIG. 8	5 3/8" x 2 1/4"	FILAMENT	2.5	1.75	250	250	CLASS A AMPLIFIER	90	-16.5	250	6.0	31.0	60000	2500	150	7000	2.7	C-47
RCA-48	POWER AMPLIFIER TRIODE	MEDIUM 6-PIN	FIG. 15	5 3/8" x 2 1/4"	D-C HEATER	30.0	0.4	125	100	CLASS A AMPLIFIER	250	-20.0	95	9.0	47.0	10000	2800	28	2000	1.6	C-48
RCA-49	DUAL-GRID POWER AMPLIFIER	MEDIUM 5-PIN	FIG. 7	4 1/4" x 1 1/2"	D-C FILAMENT	2.0	0.120	180	---	CLASS A AMPLIFIER	135	-20.0	---	---	5.7	4000	1125	4.5	11000	0.15	C-49
UX-250	POWER AMPLIFIER TRIODE	MEDIUM 6-PIN	FIG. 1	6 1/4" x 2 1/4"	FILAMENT	7.5	1.25	450	---	CLASS A AMPLIFIER	300	-54.0	---	---	35.0	2000	1900	3.8	4600	1.6	CX-350
RCA-53	TWIN-TRIODE AMPLIFIER	MEDIUM 7-PIN	FIG. 24	4 1/4" x 1 1/2"	HEATER	2.5	2.0	300	---	CLASS B AMPLIFIER	250	0	---	---	55.0	1800	2100	3.8	3670	3.4	C-53
RCA-55	DUPLEX-DIODE TRIODE	SMALL 8-PIN	FIG. 13	4 1/4" x 1 1/8"	HEATER	2.5	1.0	250	---	TRIODE UNIT AS CLASS A AMPLIFIER	135	-10.5	---	---	3.7	11000	750	8.3	25000	0.075	C-55
RCA-56	SUPER-TRIODE AMPLIFIER DETECTOR	BIAS 5-PIN	FIG. 8	4 1/4" x 1 1/8"	HEATER	2.5	1.0	250	---	CLASS A AMPLIFIER	250	-13.5	---	---	8.0	8500	975	8.3	20000	0.100	C-56
RCA-57	TRIPLE-GRID AMPLIFIER DETECTOR	SMALL 6-PIN	FIG. 11	4 1/4" x 1 1/8"	HEATER	2.5	1.0	250	100	CLASS A AMPLIFIER	250	-3.0	100	0.5	5.0	9500	1450	13.8	---	---	C-57

*For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode. Requires different socket from small 7-pin. □ Grid next to plate tied to plate. †Two grids tied together. **For grid of following tube.

RCA-58	TRIPLE-GRID SUPER-CONTROL AMPLIFIER	SMALL 6-PIN	FIG. 11	4 1/4" x 1 1/8"	HEATER	2.5	1.0	250	100	SCREEN GRID R.F. AMPLIFIER	250	-3.0 min.	100	2.0	8.2	800000	1600	1280	---	---	C-58	
RCA-59	TRIPLE-GRID POWER AMPLIFIER	MEDIUM 7-PIN	FIG. 19	5 3/8" x 2 1/4"	HEATER	2.5	2.0	250	250	AS MIXER IN SUPERHETERODYNE	250	-10.0	100	---	---	---	---	---	---	---	---	C-59
RCA-71-A	POWER AMPLIFIER TRIODE	MEDIUM 4-PIN	FIG. 1	4 1/4" x 1 1/2"	FILAMENT	5.0	0.25	180	---	CLASS A AMPLIFIER	50	-19.0	---	---	10.0	2170	1400	3.0	3000	0.125	C-71-A	
RCA-75	DUPLEX-DIODE HIGH-MU TRIODE	SMALL 8-PIN	FIG. 13	4 1/4" x 1 1/8"	HEATER	6.3	0.3	250	---	TRIODE UNIT AS CLASS A AMPLIFIER	250	-1.35	---	---	30.0	1750	1700	3.0	4800	0.790	C-75	
RCA-77	TRIPLE-GRID AMPLIFIER DETECTOR	SMALL 6-PIN	FIG. 11	4 1/4" x 1 1/8"	HEATER	6.3	0.3	250	100	SCREEN GRID R.F. AMPLIFIER	100	-1.5	60	0.4	1.7	650000	1100	715	---	---	C-77	
RCA-78	TRIPLE-GRID SUPER-CONTROL AMPLIFIER	SMALL 6-PIN	FIG. 11	4 1/4" x 1 1/8"	HEATER	6.3	0.3	250	125	SCREEN GRID R.F. AMPLIFIER	250	-3.0 min.	100	0.5	2.3	1500000	1250	1500	---	---	C-78	
RCA-79	TWIN-TRIODE AMPLIFIER	SMALL 6-PIN	FIG. 19	4 1/4" x 1 1/8"	HEATER	6.3	0.6	250	---	CLASS B AMPLIFIER	180	0	---	---	---	---	---	---	---	---	C-79	
RCA-85	DUPLEX-DIODE TRIODE	SMALL 8-PIN	FIG. 13	4 1/4" x 1 1/8"	HEATER	6.3	0.3	250	---	TRIODE UNIT AS CLASS A AMPLIFIER	135	-10.5	---	---	3.7	11000	750	8.3	25000	0.075	C-85	
RCA-89	TRIPLE-GRID POWER AMPLIFIER	SMALL 6-PIN	FIG. 14	4 1/4" x 1 1/8"	HEATER	6.3	0.4	250	250	AS TRIODE #1 CLASS A AMPLIFIER	160	-20.0	---	---	17.0	3300	1425	4.7	7000	0.300	C-89	
UV-199	DETECTOR AMPLIFIER TRIODE	SMALL 4-PIN	FIG. 10	3 1/4" x 1 1/8"	D-C FILAMENT	3.3	0.063	90	---	CLASS A AMPLIFIER	90	-4.5	---	---	2.5	15500	425	6.6	---	---	C-299	
RCA-864	AMPLIFIER TRIODE	SMALL 4-PIN	FIG. 1	4" x 1 1/8"	D-C FILAMENT	3.1	0.25	135	---	CLASS A AMPLIFIER	90	-4.5	---	---	3.5	12700	610	8.2	---	---	CX-299	

*For Grid-leak Detection—plate volts 45, grid return to + filament or to cathode. †Either A, C, or D, C. may be used on filament or heater, except as specifically noted. For use of D, C. on A-C filament types, decrease stated grid volts by 1/2 (approx.) of filament voltage. **Requires different socket from small 7-pin. ††Grid #1 is control grid. Grid #2 is screen. Grid #3 tied to cathode. †††Grid #1 is control grid. Grids #2 and #3 tied to plate. ††††Applied through plate coupling resistor of 250000 ohms. †††††Grids #1 and #2 connected together. Grid #3 tied to plate. **For grid of following tube.

RECTIFIERS


RCA-523	FULL-WAVE RECTIFIER	MEDIUM 4-PIN	FIG. 2	5 3/8" x 2 1/8"	FILAMENT	5.0	3.0	---	---	Maximum A-C Voltage per Plate.....	500 Volts, RMS	Maximum D-C Output Current.....	250 Milliamperes	---	---	---	---	---	---	---	C-523
RCA-1223	HALF-WAVE RECTIFIER	SMALL 4-PIN	FIG. 22	4 1/4" x 1 1/8"	HEATER	12.6	0.3	---	---	Maximum A-C Voltage per Plate.....	250 Volts, RMS	Maximum D-C Output Current.....	60 Milliamperes	---	---	---	---	---	---	---	C-1223
RCA-2525	RECTIFIER-DOUBLER	SMALL 8-PIN	FIG. 5	4 1/4" x 1 1/8"	HEATER	25.0	0.3	---	---	Maximum A-C Voltage per Plate.....	125 Volts, RMS	Maximum D-C Output Current.....	100 Milliamperes	---	---	---	---	---	---	---	C-2525
RCA-1-v*	HALF-WAVE RECTIFIER	SMALL 4-PIN	FIG. 22	4 1/4" x 1 1/8"	HEATER	6.3	0.3	---	---	Maximum A-C Voltage per Plate.....	350 Volts, RMS	Maximum D-C Output Current.....	50 Milliamperes	---	---	---	---	---	---	---	C-1v*
RCA-80	FULL-WAVE RECTIFIER	MEDIUM 4-PIN	FIG. 2	4 1/4" x 1 1/2"	FILAMENT	5.0	2.0	---	---	A-C Voltage per Plate (Volts RMS).....	350-400-550	D-C Output Current (Maximum MA).....	125-110-135	---	---	---	---	---	---	---	C-80
UX-281	HALF-WAVE RECTIFIER	MEDIUM 4-PIN	FIG. 2	6 1/4" x 2 1/8"	FILAMENT	7.5	1.25	---	---	Maximum A-C Plate Voltage.....	700 Volts, RMS	Maximum D-C Output Current.....	85 Milliamperes	---	---	---	---	---	---	---	CX-381
RCA-82	FULL-WAVE RECTIFIER	MEDIUM 4-PIN	FIG. 2	4 1/4" x 1 1/2"	FILAMENT	2.5	3.0	---	---	Maximum A-C Voltage per Plate.....	500 Volts, RMS	Maximum D-C Output Current.....	125 Milliamperes	---	---	---	---	---	---	---	C-82
RCA-83	FULL-WAVE RECTIFIER	MEDIUM 4-PIN	FIG. 2	5 3/8" x 2 1/8"	FILAMENT	5.0	3.0	---	---	Maximum A-C Voltage per Plate.....	500 Volts, RMS	Maximum D-C Output Current.....	250 Milliamperes	---	---	---	---	---	---	---	C-83
RCA-84	FULL-WAVE RECTIFIER	SMALL 5-PIN	FIG. 23	4 1/4" x 1 1/8"	HEATER	6.3	D.S.	---	---	Maximum A-C Voltage per Plate.....	125 Volts, RMS	Maximum D-C Output Current.....	50 Milliamperes	---	---	---	---	---	---	---	C-84
RCA-866	HALF-WAVE RECTIFIER	MEDIUM 4-PIN	FIG. 16	6 3/8" x 2 1/8"	FILAMENT	2.5	5.0	---	---	Maximum Peak Inverse Voltage.....	7500 Volts	Maximum Peak Plate Current.....	0.6 Ampere	---	---	---	---	---	---	---	C-866

*Mercury Vapor Type. * Interchangeable with type 1.

PHOTOTUBES

RCA-868	PHOTOTUBE	SMALL 4-PIN	FIG. 28	4 1/4" x 1 1/8"	---	---	---	---	---	Max. Anode Supply Voltage, 90 Volts. Max. Anode Current, 20 Microamperes. Static Sensitivity, 55 Microamperes per Lumen. Dynamic Sensitivity, 50 and 48 Microamperes per Lumen at 1000 and 5000 Cycles per second, respectively.	---	---	---	---	---	---	---	---	---	---	---	C-868
---------	-----------	-------------	---------	-----------------	-----	-----	-----	-----	-----	--	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-----	-------

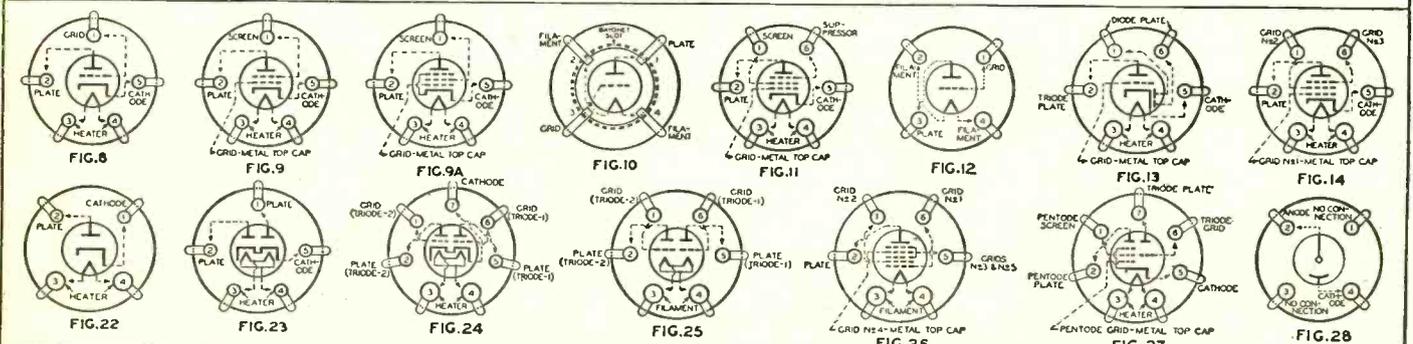TUBE SYMBOLS AND BOTTOM VIEWS OF SOCKET CONNECTIONS



INDEX OF TYPES BY USE AND BY CATHODE VOLTAGE

CATHODE VOLTS	POWER AMPLIFIERS	VOLTAGE AMPLIFIERS Including Duplex-Diode Types	CONVERTERS IN SUPERHETERODYNES	DETECTORS	MIXER TUBES IN SUPERHETERODYNES	RECTIFIERS	CATHODE VOLTS
5.0	112-A, 71-A	01-A, 40, 112-A	---	00-A, 01-A, 40, 112-A	---	523, 80, 83	5.0
6.3	6A4, 38, 41, 42, 79, 89	6B7, 6P7, 36, 37, 39, 44, 75, 77, 78, 85	6A7, 6F7	0B7, 6F7, 36, 37, 75, 77, 85	6A7, 6F7, 39-44, 78	1-v, 84	6.3
7.5	10, 50	---	---	---	---	81	7.5
12.6	---	---	---	---	---	1223	12.6
25.0	43	---	---	---	---	2525	25.0
30.0	48	---	---	---	---	---	30.0

Radio University

A QUESTION and Answer Department. Only questions from Radio University members are answered. Such membership is obtained by sending subscription order direct to RADIO WORLD for one year (52 issues) at \$6, without any other premium.

RADIO WORLD, 145 WEST 45th STREET, NEW YORK, N. Y.

Inductance

WILL YOU PLEASE give me a general idea of how inductance changes? I refer to radio-frequency solenoids.—P. O'L.

The inductance varies as the square of the number of turns, except for small changes in number of turns, when it varies directly according to the number of turns. The relationship of frequency and inductance is that the frequency is approximately proportionate to the inductance. The relationship of inductance for various bands, same variable tuning capacity, is that the inductance should be decreased for higher frequency bands by the reciprocal of the capacity ratio. If the capacity ratio is 3-to-1 the inductance for the next band is one-third of that for the present band.

Inductance is Length

WHAT IS inductance as a quantity? How does it differ from frequency as a quantity? Can one unit be capacity, inductance and resistance?—K. R.

Inductance is a unit of length. Frequency is a unit of time. In fact, frequency is the reciprocal of time. One unit is bound to be a combination of inductance, capacity and resistance. Whatever term predominates gives it its full classification. So, the same element may be an inductance at one frequency, a capacity at another and a resistance at another. At zero frequency a coil of 200 microhenries would be a resistance. At broadcast frequencies it would be an inductance. At ultra frequencies it might be a condenser. Whether the current or the voltage leads determines the classification as between capacity and inductance, whereas if the unit is overwhelmingly d-c resistance it is a resistor.

Matching Pickup

AS I HAVE a transformer that, I think, was intended originally for bell-ringing, I wonder if I might use it as a matching transformer? Its primary is 2 ohms, its secondary 25 ohms. I would want to work into a vacuum tube.—J. H.

No, this transformer can not be used. A 25-ohm impedance in the grid circuit of a vacuum tube at audio frequencies is practically a short circuit. Is it possible what you have given are the d-c resistances? One should really know the impedances instead. Matching transformers can be bought for less than a dollar these days and we suggest you get one of the proper value.

Regenerative Effect

IS IT POSSIBLE to estimate the effect of regeneration? I have been told that it increases the signal 1,000 times or so, but this seems to me an incredible figure for such a simple procedure.—K. Y. L.

The effect of regeneration varies greatly, especially as the variation is steep indeed just a bit to either side of critical value. However, measurements have been made, and has been found that in extreme instances the gain ascribable to the regenerating tube is 15,000, or around 4,000 times the gain without regeneration. The extreme instances may be accomplished by fine tuning of the receiver and just-right setting of the regeneration control. The gain, but not so much the selectivity, depends on the goodness of the coil and condenser. The coil

should have low r-f resistance and the circuit losses throughout should be low. The ratio of inductance to capacity should be as high as practical.

The 57 as a Detector

WILL YOU PLEASE give me data on the operation of the 57 as a detector? I have read that the plate current should be adjusted to 0.1 milliamperes.—K. L.

There are several methods of procedure, and adjustment of the plate current is one way. However, the tube is most sensitive at a lower bias than the 6 volts normally suggested, values between 3 and 4.5 volts being preferable. If not much is to be put into the tube the negative bias may be 3 volts, screen voltage 100 volts and plate voltage (with 0.25 meg. load) 250 volts. It is the most sensitive tube commonly used, since the gaseous 200-A has been virtually discarded as too noisy, and besides is a battery type, which should impair its popularity today, anyhow. It is interesting to note that wherever a 57 is used (except as oscillator) the 58 may be substituted with no circuit changes, although the sensitivity will not be as good.

Pickup Connections

DOES IT MAKE much difference how a phonograph pickup is connected in circuit? I have seen some circuits with pickup in the cathode leg, others with pickup in the grid circuit (across a resistor load already there), again in series with a radio-frequency coil feeding a detector, and have even seen it in the plate circuit. Which is best and what's the difference?—J. E. C.

Phonograph pickups of different types are made for different circuit connections. For instance, as a broad classification, there are low-impedance pickups and high-impedance pickups. The low-impedance ones usually require a matching transformer, so that they may be fed to the high impedance grid or plate circuit for best transfer of energy. With mismatched impedances there is too much loss. The matching transformer would have a primary equaling the impedance of the pickup, and a secondary of high impedance, matching but not necessarily equaling that of the grid or plate circuit. The plate circuit type really looks into a succeeding grid circuit, so may be regarded from the grid circuit viewpoint. The high impedance pickup may be put directly in the grid circuit, as across a leak or an audio transformer secondary, usually a switch serving to cut the pickup in or out. The pickup with high impedance may not be expected to have a sufficiently high impedance, but where cost or space is an item it dispenses with the transformer without serious loss. The grid circuit impedance is very large, and practical values exceed 200,000 ohms, so even a high impedance pickup could stand a matching transformer, as with transformers (no current) it is easy to achieve impedance values around 2,000,000 ohms, if necessary. Some grid circuits have as large an impedance as that and a transformer with such a secondary would work into such grid to advantage. Connection of the pickup in the cathode circuit is a makeshift simplification, as no gain is derived from the tube in whose cathode it is connected, since it is the same as a plate circuit connection, the cathode-to-ground circuit being principally in the plate circuit.

Different R-F Coils

DIFFERENT TYPES of antenna coils are shown from time to time, interstage coils likewise. I would like to know if the type that has an r-f choke as the primary load, with a few turns over the secondary used as a coupling capacity, is all right? What is the difference in performance?—R. B. M.

The various types of coils all serve their good purposes. Designers concoct or select such coils as meet the requirements of their
(Continued on next page)

Two for the price of One

Get, EXTRA, one-year subscription for any One of these magazines:

- POPULAR SCIENCE MONTHLY.
- RADIO-CRAFT (monthly, 12 issues).
- RADIO INDEX (monthly, 12 issues), stations, programs, etc.
- RADIO (monthly, 12 issues; exclusively trade magazine).
- EVERYDAY SCIENCE AND MECHANICS (monthly).
- RADIO LOG AND LORE. Bi-monthly; 5 issues. Full station lists, cross indexed, etc.
- AMERICAN BOY—YOUTH'S COMPANION (monthly, 12 issues; popular magazine).
- BOYS' LIFE (monthly, 12 issues; popular magazine).
- OPEN ROAD FOR BOYS (monthly, 12 issues).

Select any one of these magazines and get it free for an entire year by sending in a year's subscription for RADIO WORLD at the regular price, \$6.00. Cash in now on this opportunity to get RADIO WORLD WEEKLY, 52 weeks at the standard price for such subscription, plus a full year's subscription for any ONE of the other enumerated magazines FREE. Put a cross in the square next to the magazine of your choice, in the above list, fill out the coupon below, and mail \$6 check, money order or stamps to RADIO WORLD, 145 West 45th Street, New York, N. Y. (Add \$1.50, making \$7.50 in all, for extra foreign or Canadian postage for both publications.)

Your Name.....

Your Street Address.....

City..... State.....

- If renewing an existing or expiring subscription for RADIO WORLD, please put a cross in square at beginning of this sentence.
- If renewing an existing or expiring subscription for other magazines, please put a cross in square at the beginning of this sentence.

RADIO WORLD, 145 West 45th Street, New York. (Just East of Broadway)

DOUBLE VALUE!

(Continued from preceding page)

receivers. In general, the standard transformer will be found preferable, that is, primary wound over or adjacent to secondary. The special type with choke primary, and the turn or so over the secondary for capacity coupling effect, one end of this small winding open, is intended to bolster up the gain at the low radio frequencies. This it does well, but at the expense of gain at the higher frequencies, and also of selectivity. Where the circuit gains and selectivities permit, the special coils may be introduced to effect a leveling of the r-f amplification, otherwise the gain would be greater at the higher frequencies. In most receivers this rising characteristic is not atoned for, as the conservation of selectivity at the higher frequencies meets the sentiments of most designers.

Code on T-R-F Set

I HAVE a tuned radio frequency set, and yet I get some code where there should be none, in the middle or so of the broadcast band. If it were a super I could expect it, as I have been told about that, without understanding it, but in a t-r-f set I feel there is a mystery.—J. R. W.

Some few transmissions of code in the broadcast band are licensed and you may be receiving one of them. Another possibility is that some one sending code on a higher or lower frequency than the extremes of the broadcast band may have an extra receiver going that has a broadcast-band oscillator in it, and, unknown to him, the oscillator is being modulated by his dots and dashes. Another possibility is harmonics of low frequency code stations, due to impure wave form of transmitting carrier. The last-named is quite likely. The pickup of code in supers would be due to second or other harmonics of the oscillator beating with fundamentals (code carriers) that get by the radio-frequency tuner. Sometimes the code is at or near the intermediate frequency itself, and the little that gets by at the original frequency is amplified greatly in the i-f channel. The remedy for this would be to put a circuit across the primary of the antenna coil, resonating this circuit at the intermediate frequency, to trap out this direct interference.

Improvements Made in 38, 41, 42, 89 and 2A5 Allow Higher Grid Leak

Recently completed life tests have indicated that tube types 38, 41, 42, 89 and 2A5 will give satisfactory operation with a resistance of 1 meg. in series with the grid, and with 250 plate volts, provided the heater voltage does not rise more than 10 per cent. above the rated value under any conditions of operation.

This increase in the maximum permissible value of resistance in series with the grid of the 38, 41, 42, 89 and 2A5 is of particular interest to the set designer, since it makes possible the obtaining of higher amplification from the preceding tube, together with lower distortion and higher voltage output. This is especially true when the preceding tube is a pentode, a high-mu triode, or a diode, since each of these requires a load of 100,000 ohms or greater.

Heretofore it has not been possible to use high values of grid circuit resistance with the smaller output tubes having close spacing of their elements and comparatively large power output capabilities. Recent improvements in the design of the 38, 41, 42, 89 and 2A5 tubes have made it possible to use the grid resistance of 1 meg.

Stopping I-F Oscillation

AS A CUSTOM-SET builder my principal trouble is stopping intermediate amplifiers from oscillating, particularly two-stage amplifiers (three coils).—C. W. F.

Since the cathode circuit is common to grid, plate and screen circuits, as well as to suppressors, a high degree of filtration of the cathode helps a great deal. It is far more effective than merely using choke-condenser filters in individual plate leads. Use shielded wire on overhead grids and ground the sheath. In the absence of such wire, turn any fine wire

back on itself for the length of the grid lead, and then wind over the grid lead from the grid end toward the coil, grounding the two fine wire terminals at the coil shield. A lug under the head of a machine screw will make a good soldering place. Then try large capacity across each individual biasing resistor, or, if there is a common resistor, a still larger capacity across that. A minimum value for each stage would be 0.5 mfd., and usually 1 mfd. is much more effective. If the foregoing reduces the oscillation greatly (as it will) but does not cure it completely (as it may not), determine which tube is oscillating, and filter each element (screen and plate, for instance) with a high inductance r-f choke and 0.1 mfd. condenser, as and if necessary, ground the suppressor of the tube. The general scheme of grounding all i-f suppressors may be resorted to if all other methods, including the foregoing, do not produce complete stabilization, but the selectivity is reduced a bit that way.

Form-Fitting Shields

RECENTLY I OBTAINED some of those form-fitting tube shields. I use shielded wires on control grid connections of screen grid tubes, and I find that there is oscillation with shielded wire grounded to chassis—L. W.

If oscillation is present when chassis-grounded shielded wire is used, ground the shielded wire to the tube shield instead, as with that type of shield the shield is connected to cathode through a flexible phosphor bronze strip. The difference in r-f potential between cathode and chassis is sometimes enough to produce oscillation.

Push-Pull Resistance Audio

HAS PUSH-PULL resistance-coupled audio been reduced to practice yet, to the extent that it may be safely used and is easily duplicated in production? What methods are suggested?—J. W. C.

There has been considerable trouble with push-pull resistance-coupled audio in the past, but some advance has been made recently, using ideas that have been generally known for several years. A method that works well has been reduced to repeatable practice in our laboratories and will be disclosed next week, in a double-push-pull circuit, a pair of 58's (or a 53 used as two tubes) driving 2A3's. Other methods are under investigation and in following weeks it is expected some especially novel data will be presented, all within the classification of excellent performance.

53 Phase-Inverter

HOW DOES THE 53 work as a phase-inverter tube for push-pull resistance audio?—M. C.

Attempts we have made to get good results with this tube used in the manner you state have not been encouraging, and until a practical circuit is worked out we would not suggest that you use this type of phase inversion, unless your object is purely experimentation.

Transformer Out of 57

CAN A TRANSFORMER be used effectively with primary in the plate circuit of the 57 or 58, and if not, what do you suggest, as I have the transformer and the tube?—I. F.

No, the primary of the transformer is a part short circuit to the very high plate impedance. To use the part and tube you have, connect the plate and the screen together, put a resistive load on the plate circuit, around 50,000 ohms, and use a stopping condenser between plate of tube and plate terminal of primary. Connect return of primary to cathode. Primary inductance has to be very high.

Join Radio World's

UNIVERSITY CLUB

And Get Free Question and Answer Service for the Coming 52 Weeks. THIS SERVICE FOR UNIVERSITY SUBSCRIBERS ONLY

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below or write on a separate sheet of paper, if preferred. Your name will be entered on our subscription and University Club lists by special number and you will be apprised of the number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your query. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

NO OTHER PREMIUM GIVEN WITH THIS OFFER

[In sending in your queries to the University Department, please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for Radio World for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name
Street
City and State.....

Peck's New Television Light Source Increases Illumination 3,000 Times

6-Volt Auto Headlight Bulb Modulated by Secret Inexpensive Element

William Hoyt Peck, one of the nation's leading optical experts, who has been experimenting in the television field for the past several years, has perfected a method of using a 6-volt automobile headlight bulb as the source of illumination in casting a television image covering a screen 20 by 24 inches.

Mr. Peck, president of the Peck Television Corporation, New York City, has evolved a radically new type of reflector system which not only utilizes 83.33% of the light emitted by the bulb, but enables that light to be concentrated to a point no larger than the crater of a neon tube. This is the first time in the history of optics that such a feat has been accomplished.

3,000 Times as Much Light

In practical application, as tested with Weston photometric apparatus, the Peck reflector system gives slightly more than 3,000 times as much light as the best neon crater tube available. This means that bigger, brighter images can be had from a bulb costing only 10c and of nearly indefinite life.

Modulation is accomplished by means of a separate element, which Mr. Peck is unwilling to disclose at present. He did state, however, that his light modulator is not a tube, is unaffected by temperature or humidity, will never need replacement, contains no liquid, will operate on ap-

proximately 1/40 the power produced by an ordinary amplifier, and can be produced for less than \$3 each in lots of 5,000.

This new apparatus has been designed by Mr. Peck for use in conjunction with his particular type of scanning disc, though it can be adapted to any mechanical system.

Transmitter Nearly Ready

The Peck disc, described in RADIO WORLD nearly a year ago, has been proven to transmit four times as much light as any other form of lens wheel, and sixty times as much as a pinhole disc. It consists of a six-inch wheel with a row of sixty reflecting lenses arranged in a circle on the face of the wheel near the periphery, instead of the usual spiral. Scanning is accomplished by tilting the lenses, each lens being angularly displaced from its next preceding lens by 25 minutes for sixty line scanning.

The system can be used equally well for 60, 120, 180 or 240 line scanning.

The same lens system as is used in the receiver can be employed for transmission, the only change necessary being the replacement of the light source with a photo-electric cell. This will enable stations to use direct pick-up, requiring no more light than is used for motion picture photography. Mr. Peck is now completing a transmitter of this type, and expects to give public demonstrations soon.

NEW BOARD OF WMCA HEADED BY AL SMITH

WMCA, New York City, 570 kc, full time, has been bought by the Federal Broadcasting Corporation, a new organization with wealthy young men behind it. Alfred E. Smith, former Governor of the State of New York, has been elected chairman of the board of directors.

While the admitted aim of the undertaking is to establish a chain, as its very name might imply, that accomplishment is regarded as being not imminent, because of the vast amount of preparatory work necessary. However, feelers are being sent out and, with Mr. Smith's name behind the enterprise, as well as the fortunes of the Ryans, Morris and Whitneys, it is expected that the goal will be realized.

Offices and studios are at 1,697 Broadway, New York City, where the first meeting of the board, with Smith presiding, was held the other day.

Associates Listed

Among those actively associated with the enterprise are Clendenin J. Ryan, Jr., John Hay Whitney, Allan A. Ryan, Jr., A. Newbold Morris, John T. Adams, Howard G. Cushing, Maj. T. O. Freeman, Walter S. Mack, Jr., and Bethuel M. Webster, formerly counsel to the Federal Radio Commission.

A statement by Mr. Smith on the acceptance of the chairmanship follows:

"I believe that I can be of service to the public of New York through the medium of this station, which reflects the life, pulse and tempo of New York. The enthusiasm of the industrious young Americans who are members of the board

leads me to believe that the station will serve its listening audience with programs of entertainment and education of the highest degree.

"The potentialities of radio and its intimate association with the home have raised it to institutional proportions with an opportunity for unlimited service to the public."

Would Be Fifth Network

Donald Flamm, the colorful Broadway figure who led the station's activities for the past several years, has returned to the theatrical field as a producer. He was the chief executive, to which position Mr. Adams succeeds.

In the new network it is intended to include only "first-class transmitters." If the venture materializes there will be five networks. The fundamental three are two of the National Broadcasting Company and one of the Columbia Broadcasting System. The fourth is the Amalgamated Broadcasting System, of which Ed Wynn is the head, and in which it is reported he has invested \$250,000. This system is all set to go, and has important financial backing, as well as an existing station grouping. Edsel Ford and a large New York City bank are said to be interested. The opening date is to be announced soon.

Wynn is in Hollywood to make a moving picture. One script he discarded as inadequate and then he set out to find a new one, finally writing much of it himself.

Fernald Directs Sales of Kenyon Transformers

Paul R. Fernald, formerly one of the outstanding custom set builders, and later a successful sales executive, has been appointed director of sales by Kenyon Transformer Co., Inc., 122 Cypress Avenue, New York City.

Kenyon offers a complete line of power, audio and matching transformers, both of the commercial and precision types.

TERMS SOUGHT IN CLASSIFYING SHORT WAVES

There is as yet no general agreement on the classification of frequencies higher than the highest broadcast carrier, so committees of the Institute of Radio Engineers and Radio Manufacturers' Association, Inc., are attempting to reach a satisfactory basis of nomenclature. The American Standards Association also is interested.

One of the proposals under consideration is as follows:

200 to 10 meters—short waves.
10 meters to 1 meter—meter waves.
99.99 to 10 centimeters—decimeter waves.

9.99 centimeters to 1 centimeter—centimeter waves.

9.99 millimeters to 1 millimeter—millimeter waves.

At present the general reference to short waves is taken to include all waves below 200 meters, with the exception that below 10 meters the phrases ultra waves, quasi-optical waves and micro-waves are used. Some start the short-wave classification at 80 meters, calling the waves between 80 and 200 meters intermediate short waves.

The growth in the use of the lower waves, particularly below 10 meters, necessitates greater clarity of definition, and any agreement reached by the committees is expected to be acceptable to the science at large. Previous experience with standardization of terms indicates this. However, formal adoption usually does not take place until the memberships have had an opportunity to express opinions on the tentative proposals.

Station Sparks

By Alice Remsen

TALENT RIGHT AT OUR ELBOWS

The powers that be in radio are worrying over the lack of new talent. The chains have sent out frantic appeals to its affiliated stations for likely prospects. There's plenty of talent right in their own backyards if they'd only use common-sense. For instance—from vaudeville they could gather Harland Dixon, Billy Glason, and Hal Neiman, all clever *ad lib* comedians. Then there is Sidney Teneyck, who drifted over to WCAU, Philadelphia, because he was not appreciated in New York, and Sidney was a lad with a brand-new style of humor. Then there is Maria Cardinale, who has been appearing on NBC morning programs, a soprano with a distinctive style of her own, which is rare in that type of voice, and plenty of ability. The Giersdorf Sisters are another good bet; they have looks, class and talent, and are real troupers. Ivy Scott, on the NBC regular staff, is a soprano who is also a good comedienne; plenty of experience and always does a good job; deserves a build-up. Then there also is little Jean Sothern, former picture star; this lass is chock-full of talent which could be used to good advantage if handed properly. Plenty more, too, with tricks and styles which sound a little different.

THE LISTENERS ARE THE JURY

After all, radio is for the listener only, and the listener judges only by what he hears; he doesn't care whether the singer is blonde, brunette or red-headed, fat or thin, old or young, just so long as the voice pleases; but the powers that be in radio don't figure that way; their first thought is: how much revenue can we derive from this person? Will he or she make a good appearance for vaudeville, pictures or what have you? And therein lies most of the trouble; of course, there are plenty of other angles, too; personal pull and politics play a great part in the radio game; radio executives have their favorites, which after all is just being human, but I do think that a little more real attention paid to talent already available would go a long way toward alleviating the so-called talent depression.

THE GROWTH OF ROMANCE

August 24th was the date on which Florence Golden and Don Becker, of WLW, were married, at St. Anthony's Church, in Forest Hills, Kentucky; I watched this romance grow; it was a very beautiful thing; these two young folks were head over heels in love with each other; there's nothing finer in the world; here's jolly good luck, Don and Florence! May you spend many happy years together. . . . The big noise of the week in radio around New York is the new broadcasting company which has been formed by a group of business men; they call themselves the Federal Radio Corporation, and have taken over WMCA, which they will operate on a big-time basis, linking up a chain in the near future; the young members of old New York families—such as the Thomas Fortune Ryans and the John Hay Whitneys—are at the head of the scheme; they are wise enough to place the managership of the new company into the hands of a real showman, Jack Adams, who knows his business and will no doubt make a success of it. . . . Rumor has it that Alex Gray will return to the air; he'll be welcome. . . . From the same source comes the news that Vera Van, petite blonde songstress, will replace Gertrude

Niesen on that Thursday night Mark Warnow program over WABC. . . . Ex-Lax had an audition at Columbia last week; no less than nineteen female warblers and several bands were heard; Isham Jones and a well-known contralto made the grade for the final audition, but have not been signed up to the present writing.

. . . They say that Alice Fay was pretty well cut up in that auto accident with Rudy Vallee; Miss Fay is still in the hospital as this is being written; Rudy was heard as usual on the Fleischmann program, but did not sound quite so blithe; give him credit for doing anything at all after a car turned turtle with him. . . .

SOME PRORAM CHANGES

Swift and Company's show will be on CBS instead of NBC, starting September 29th; Olson and Johnson will be starred; reason for the change given out as not enough outlets in territory required by Swift. . . . Another new program starts over NBC-WJZ network on September 7th, sponsored by the Borden Milk Company in the interests of Eagle Brand canned milk; Marcella Shields, Walter Scanlon and a piano duo will be featured, with a cooking talk by Jane Ellison. . . . Brad Brown and Al Lewellyn were in, but are out again, for the Household Finance Corporation on WOR; Macey and Smalley have taken over the program. . . . October 8th will find Angelo Patri back on the air again, via WABC for the Cream of Wheat Corporation; this time Mr. Patri will have a band and a comedy skit as added attractions and the bill will be for a half-hour, Sundays at 10:00 p.m., EST; it's a thirteen week contract. . . . Frank Novak, who rejoices in the distinction of being a one-man band, playing almost every instrument used in a dance orchestra, is doing a great deal of field work in the social end of radiodom; he has organized a bridge club at NBC and expects to arrange elimination games this winter in order to find a foursome to compete with other clubs; Frank opens on a three-a-week series for the Jello Company very shortly; the program will be called "The Wizard of Oz," and will contain original music written by Frank; a rather tall order, but he can do it; he is also putting out an illustrated child's book, as a give-away advertising tieup; a very clever lad, Frank. . . . Darrell Woodyard, formerly basso with the Cities Service Cavaliers, has been signed up with The Rondoliers; Darrell, by the way, is a fine-looking chap, happily married and the proud father of a two-year-old boy. . . . John Fogarty, that sweet-voiced Irish tenor, is playing some dates booked for him by Fanchon & Marco. . . . Mabel Jackson, well-known radio soprano, is combining business with pleasure, and is whiling away these hot days singing at the Hollywood Inn at Far Rockaway. . . . Harry Duke and his Georgians are doing some good work over WTNJ, Trenton, N. J., and WPEN, Philadelphia. . . .

DELPHINE MARCH DOING WELL

Delphine March did a grand job in the light opera "Olivette," recently, singing the title role over WABC; her lovely contralto voice is also heard to great advantage during that station's "Cathedral Hour." . . . The new series of "Evening in Paris" programs will open on September 11th with Agnes Moorehead in humorous episodes and Nat Shilkret's Orchestra; a fifteen minute program, Mon-

WLW's 500 KW IN USE SOON

The gigantic undertaking of WLW, Cincinnati, in establishing a transmitter with an output of 500,000 watts, is slowly progressing, as careful tests are made of each new item of advance. It is expected the enormous power output will be ready for use in February or March, and the experiment then made as to whether such great power will constitute the station one of national coverage, that is, "a one-station network."

The field of such high-power transmission is virtually unexplored in this country, although there has been abundant experience in regard to 50,000 watts, compared for instance with 5,000 watts. The 50,000-watt stations are clear-channel occupants, while the 5,000-watt stations are regional.

Not all the higher-power experiments have been consistent with expectations although in general the service area has been increased and the quality as well. Listeners therefore await with especial interest the introduction of enormous power at WLW, an undertaking laden with expense, but one that promises rich returns if it works out satisfactorily. The station is owned by the Crosley Radio Corp.

MORE ECONOMICAL TUBES

Sometimes tubes usually used for automotive sets or for d-c are found in a-c sets, supplied by a power transformer. The main reason for this is economy of power consumption. The tubes, if run at 6.3 volts, 0.3 ampere, dissipate 1.89 watts in the heater, whereas the regular a-c type tubes, 2.5 volts at 1 ampere, dissipate 2.5 watts. Thus there is an economy of about 25 per cent.

days, 9:15 p.m., EDST, on WABC and seventeen other stations. . . . Frederic William Wile starts his eleventh year on the air when he resumes his series of weekly talks over WABC on Saturday, September 16th, at 7:00 p.m. EDST. . . . Gertrude Niesen will be the featured soloist on the Johnny Green programs over WABC, Sunday nights at 8:30 p.m., EDST; Miss Niesen has a low contralto voice which comes over the air excellently. . . . Vera Van is another contralto on WABC who deserves mention, and, though it is not generally known, it was Tom Neeley, erstwhile of NBC's program department, who discovered Miss Van, when she first arrived from California. . . . Alexis Sanderson, WHOM program director, and also possessor of a fine voice, came back from his week-end vacation feeling a trifle out of sorts; too much home cooking, says Alex. . . . If you feel like warbling into a microphone just to prove that you can sing as well as this, that or the other crooner, take a trip up to the WHOM studios, Hotel President, on West 48th St., New York, some bright Saturday afternoon at 2:15 p.m. and you'll be given a chance, for WHOM is holding public auditions at that hour. . . . Harry Richman and Milton Berle have joined Fred Waring's Pennsylvanians, and may now be heard with that great musical aggregation each Wednesday, at 10:00 p.m. EDST, over WABC and network on the Old Gold program; of course, Richman sings and exchanges comedy banter back and forth with Berle. . . . The surprise of the week is the news that Barbara Maurel, CBS contralto, and Phil Whitten, of Station WINS, were secretly married to each other last March. . . . And now I think it's time to call it a day and trudge the highway to West 45th Street and the editorial sanctum.

A SUMMARY OF PROVISIONS IN INDUSTRY CODE

By HERMAN BERNARD

Inclusion of the radio industry under the Code of Fair Competition for the Electrical Manufacturing Industry, instead of under the separate Code offered by Radio Manufacturers Association, Inc., was an entirely salutary step, viewed from the public interest, because the RMA proposed Code was too stiff and discriminatory. It sought to legislate all the evils out of the radio industry, as such evils are considered to exist by the large set manufacturers, and was entirely too detailed and peremptory for a basic code. The general tenor of both Codes is about the same, being consistent with the National Recovery Act and the President's Re-Employment Agreement or so-called blanket Code.

Functionally radio must be classified under the electrical grouping anyway, and the Electrical Industry Code provides for subdivision for branches of that industry, where special problems may be solved as circumstances require, and even some provisions included later that are in contradiction of the present Code. Another point in favor of the action taken is that the Electrical Industry Code already had the approval of President Roosevelt, and thus long hearings and much delay were avoided.

Hours and Pay

Hours and pay provisions are practically the same in both Codes, safeguard of labor rights is the same, and the National Electrical Manufacturers Association becomes the official body to administer the Code. It is well equipped to do this work. It is older and on a more solid foundation than is the RMA.

The minimum age limit of employees under the Code is 16 years, the minimum pay for processing employees (factory help) is 40c an hour, except that if the pay on July 15th, 1929, was less, it may be that, but in no instance less than 32c per hour. The same rates apply no matter what the geographical location of the factory, except that other provisions may be made for special groups or branches of the industry later.

For salaried employees the minimum is \$15 per week.

The exceptions to this pay scale are that office boys and girls and beginners and learners may be paid 80 per cent. of the basic rate, or not less than 25.6c per hour, and not less than \$12 per week, and that commission salespeople are not subject to any pay minimum.

As to hours, these are 36 hours per week maximum for processing employees (factory help), all others 40 hours a week, exceptions being rush seasons and emergencies, but employers are required to report to the administrative agency when they exceed the maximum hours, and limitations are placed on such excesses.

Employers Must Report

Employers are required to report their costs, dollar volume of sales, quantity of sales, stock on hand, etc., so that the administrative agency will have complete and authentic information on which to base any revision of industry practices that experience may prove necessary.

As to prices, the general limitation is that the seller must not dispose of a product at less than its cost to him, exceptions being that close-outs or sur-

TRADIOGRAMS

By J. Murray Barron

An unusual offering to the public of New York City and also the mail order buyers is the Pilot radio receiver sold by Thor's Bargain Basement, a 7-tube superheterodyne with tubes, cabinet and dynamic speaker, complete, ready for operation. These are the last of this model. There is also the K 136 short and long-wave receiver kit with cabinet, very popular with the home constructors.

* * *

West Side Y. M. C. A. Schools announced that the courses conducted at the Twenty-third Street Branch have been consolidated at 5 West 63rd Street, N. Y. City. L. A. Emerson, the director, will send full information.

* * *

An interesting and serviceable advertising novelty that should prove useful to the "ham" or short-wave enthusiast is being distributed free by Postal Radio Corp., 135 Liberty Street, N. Y. City. It is called Slide Commercial Calculator and acts as a slide rule.

* * *

It is well known that buyers in large department stores like to get window space for their merchandise and those who get the choice display room or frequent displays are considered fortunate. It should not be difficult for anyone to understand this for, after all, window space is naturally limited, and offerings displayed therein reflect the standards of the organization, so merchandise should be of the latest, something that is popular or in demand, appreciated, in other words, a good buy. With this thought in mind short-wave kits, converters and complete receivers must be gaining rapidly in popularity, for no less

than five prominent retail radio stores in lower New York City have extensive window displays with a wide choice of short-wave outfits, ranging from a few dollars to \$175. Even those in the lower-price range have testimonials as to their efficiency, and such a performance a few years ago would be considered impossible. Short-wave receivers and broadcasting have indeed made wonderful progress during the past two years, and with a like record in the near future it should be a comparatively easy task, with a good receiver, to bring in short-wave stations from all points of the globe.

* * *

Notwithstanding the great progress made in the radio industry and the highly developed receivers put out by the dozens of manufacturers, we find great numbers still using battery radio receivers. That this fact can be testified to by one organization in New York City that sells considerable B battery eliminators by mail. While some are for use in connection with auto receivers, many are for farms that have 32-volt systems.

* * *

Looking over numerous radio organizations, both retail and mail order, we see a great desire to co-operate with the NRA. We should ever be on guard against what during the World War we termed the slacker. He is always with us. Today, while perhaps it is a little too early to judge entirely, as adjustments in radio Codes will be made, there are many who display the Blue Eagle but to whom it means nothing, for they have done nothing more than to paste the insignia on the window.

Literature Wanted

Readers desiring radio literature from manufacturers and jobbers should send a request for publication of their name and address. Address Literature Editor, RADIO WORLD, 145 West 45th Street, New York, N. Y.

Max Stein, 314 Madison Street, New York City.
John A. Smoot, 1454 Spring Road, N.W., Washington, D. C.
Ralph Williams, Box No. 27-G, Van, Texas.
N. H. Crouse, 1140 W. 37th Place, Los Angeles, Calif.
Craig Goodwin, New Hartford, Conn.
J. J. Black, 1773 Marks Ave., Akron, Ohio.
P. L. Antonich, 620 East Park Ave., Anaconda, Mont.
R. J. Stier, Fountain Square Hotel, Vine Street, bet. 4th & 5th, Cincinnati, Ohio.
C. H. Weant, 4306 Springwood Ave., Baltimore, Md.
Geo. A. Hadsell, Manager, The Radio Laboratory, Galion, Ohio.
Ralph B. Brehm, 92 Nutt Ave., Uniontown, Pa.
George I. Viall, Jr., 5 North Water St., Rochester, N. Y.
Hugo Menzel, Rte. 3, Box 804, San Jose, Calif.
Walter N. Brown, Jr., 15 Pembroke St., Garrett Park, Md.
Rafael Banderas, Uruguay No. 35, Mexico, D.F., Mex.
L. V. Rains, 216 Interurban Bldg., Dallas, Texas.
J. Edson Heath, 2348 No. 65th Ave., Omaha, Nebr.
Paul Clarke, 39 Starbird St., Lowell, Mass.
Emil Streuli, ing., P. O. Box 7942, Mexico, D.F., Mex.
Boris Tolmachoff, Plum Cottage, Vance Ave. Lavalette, N. J.
Alfred Tarot, 571 Bird Ave., San Jose, Calif.
P. J. Walsh, 560 Powell St., San Francisco, Calif.

CORPORATION REPORTS

Sparks-Withington Company, report net loss for the year ended June 30, 1933, after depreciation, taxes and other charges, \$285,137. Last year the net loss was \$1,930,514. For six months ended June 30, 1933, net loss after above charges, \$84,141; for the same period in 1932, \$1,437,857. Weston Electrical Instrument Corporation, for quarter ended June 30, 1933, net loss after taxes and charges, \$31,888, compared with net loss of \$47,298 in preceding quarter. Net loss for six months ended June 30, \$79,186, after depreciation, taxes and other charges, compared with net loss of \$99,454 for the first six months of 1932.

BERMAN 6 FT., 6 IN., 365 LBS.

Herbie Berman, bass fiddler of the Merry Madcaps, Norm Cloutier's dance orchestra which is heard over an NBC-WEAF network on Tuesday and Saturday afternoons from W TIC in Hartford, Conn. He stands six feet, six and a half inches and weighs 365 pounds. He has a tuba made especially large to conform to his dimensions.



POWERTONE

WALLACE

Short Wave Receiver



HOOVER CUP
PRIZE WINNER

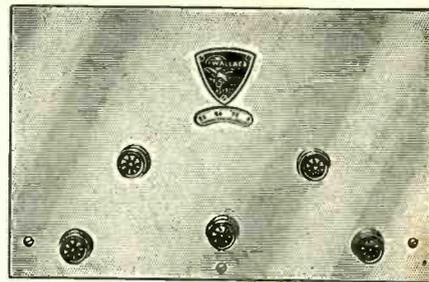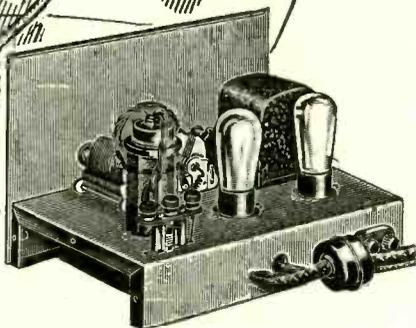

- Control No. 1—"On" and "Off" Switch.
- Control No. 2—Band Spread Switch.
- Control No. 3—Tuning Dial.
- Control No. 4—Antenna Tuning Condenser.
- Control No. 5—Regeneration Control.

Made By Powertone Electric Co. Exclusively

DESIGNED by Don C. Wallace, W6AM-W6ZZA, internationally known short wave expert and amateur. Under competitive tests he was able, when using this receiver, to hear more D.X. stations, and many which were entirely inaudible on any other. As a result he was awarded the "Hoover Cup" for premier short wave design and performance. The receiver is finely built of precision parts throughout. Proper circuit design and layout is the result of much painstaking labor. Each part has a definitely set purpose—and functions at peak efficiency at all times. Band spread tuning of the important amateur bands, 160, 80, 40, 20 meters, is controlled by means of a single panel switch.

The receiver, while fundamentally simple has been refined to the last degree. It produces an extremely high ratio of signal to noise. A control is provided for each important circuit, resulting in peak efficiency under all conditions. Heavily cadmium plated sub-base with black crackle metal front panel.

CIRCUIT:—

Ultra low-loss design to produce peak efficiency from aerial to headphones. A special system is used, which tunes the aerial circuit to the exact frequency of the sending station. Thus none of the energy is wasted, and at the same time considerable additional selectivity is obtained.

Special flat-wound silvered ribbon inductances are employed throughout, producing the highest possible circuit efficiency. A unique panel controlled inductance switching system suits the receiver to amateur "band spread" tuning or short wave listener requirements at will. Thus this receiver answers all short wave requirements.

Employs two 230 tubes. Requires two volts D. C. for filament operation, 45—90 volts of "B" battery.

FEATURES:—

- *Band Spread and Continuous Tuning.
- *Ultra Low-Loss Silver Ribbon Coils.
- *A Control for Each Circuit.
- *Tuned High Efficiency Antenna System.
- *HAMMARLUND Dual Section Isolantite Tuning Condenser.
- *Precision HAMMARLUND Tuning Dial.

- *HAMMARLUND Regeneration Control.
- *Highest Quality Audio Transformer.
- *Precision HAMMARLUND R. F. Choke.
- *Ultra Low-Loss HAMMARLUND Isolantite Sockets.
- *Beautiful Black Crackle - Finished Panel.

- *Rigid Steel Chassis.
- *Equally Suited to Amateur or Short Wave Listener Uses.
- *Precise Layout—The Result of Many Experiments.
- *Zero Body Capacity.
- *15 to 200 Meter Tuning Range.

- No. 1 Coil:— 20- 32 Meters
- No. 2 Coil:— 40- 60 Meters
- No. 3 Coil:— 75-150 Meters
- No. 4 Coil:—150-200 Meters

Price of complete kit of parts, including drilled panel and base, a choice of any one of the four plug-in coils and clear constructional blue print **\$14.70**

Completely wired and tested **\$3.23** extra

Each extra coil..... **\$1.18**

RELIABLE RADIO CO.

145 West 45th Street,

NEW YORK CITY

SEPTEMBER 16th

1933

15c Per Copy

RADIO

REG. U.S. PAT. OFF.

WORLD

*The First
and Only
National
Radio
Weekly*



*599th
Consecutive
Issue.
Twelfth
Year*

Practical Push-Pull Resistance-Coupled Audio Amplifiers

★ ★ ★ ★ ★

1-V or 12Z3 Rectifier Choice

★ ★ ★ ★ ★

10-Tube Broadcast Super

★ ★ ★ ★ ★

Stabilizing Any I-F Amplifier

★ ★ ★ ★ ★

How to Use the 1A6 Tube

New Genuine Makalot S-W and B-C Coils



704SWS



704BCS



706SWS



704

705

706

Here are the new genuine Makalot wound coils and coil forms for your new S-W receiver.

704SWS—4-pin S-W Set.....	List \$2.00
704BCS—4-pin B-C Set.....	List 1.50
706SWS—6-pin S-W Set.....	List 3.00
704—4-pin Form.....	List 25c
705—5-pin Form.....	List 25c
706—6-pin Form.....	List 30c



Order your requirements today. Send for new Catalog Sheets showing how to modernize obsolete test equipment and how to use the new tubes in old sets.

Mention Dept. W3 Alden Products Co., 715 Center St., Brockton, Mass.

NEW PRICES

TROUBLE SHOOTER'S MANUAL, Nos. I, II and III

Having assembled 2,000 diagrams of commercial receivers, power amplifiers, converters, etc., in 1,200 pages of Volume No. 1 of his Perpetual Trouble Shooter's Manual, John F. Rider, noted radio engineer, has prepared Volume No. 2 on an even more detailed scale, covering all the latest receivers. Volume No. 2 does not duplicate diagrams in Volume No. 1, but contains only new, additional diagrams, and a new all-inclusive information on the circuits covered.

Volume No. 3 (Recently issued). Order Cat. RM.....\$7.50
 Volume No. 2—Perpetual Trouble Shooter's Manual, by John F. Rider, Shipping weight 6 lbs. Order Cat. RM-VT @.....\$6.50
 Volume No. 1 (8 lbs.). Order Cat. RM-VO @.....\$7.50
 We pay postage in United States on receipt of purchase price with order. Canadian, Mexican and other foreign remittances must be in funds payable in New York.

RADIO WORLD

145 West 45th Street New York City

BLUEPRINT


627. Five-tube tuned radio frequency, A-C operated; covers 200 to 550 meters (broadcast band), with optional additional coverage from 80 to 204 meters, for police calls, television, airplane, amateurs, etc. Variable mu and pentode tubes. Order BP-627 @.....25c

RADIO WORLD, 145 W. 45th St., New York, N. Y.

COMPLETE TUBE CHARACTERISTICS WITH SOCKET CONNECTIONS

In Radio World dated Sept. 9, 1933. 15c a copy; or start your subscription with that issue. Radio World, 145 West 45th St., New York City.

FREE with a \$1.00 8-weeks Subscription

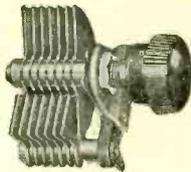

NEW STAR MIDGET CONDENSERS

Choice of 15, 25, 50 and 100 mmfd. capacities. Single hole panel mount.

Here is your opportunity to get the latest product of Hammarlund, a Star Midget condenser. Send \$1 for 8 weeks subscription and get any one condenser free. Select the desired capacity.

Any two condensers free with \$2 for 17-week subscription.

Any three condensers free with \$3 for 26-weeks subscription.

Any six condensers free with \$6 for one-year subscription (52 weeks).

RADIO WORLD

145 West 45th St., New York City

SPECIAL

SMALL POWER TRANSFORMER

Filament-plate transformer, for oscillators, 1 or 2-tube sets, etc.

Primary, 110 volts a-c.

Secondary A, 2.5 volts, center-tapped; stands up to 3 amperes.

Secondary B, 110 volts, not center-tapped.

Excellent for test oscillators with a-c in plate.

Price, \$1.10

RADIO WORLD

145 West 45th Street New York, N. Y.

SHORT-WAVE COILS and FORMS



Precision short-wave plug-in coils, wound on 1 1/2" diameter. Form has gripping flange. Four coils to a set for each tuned circuit. Approximate frequencies with 0.00014 mfd. are 1400-3080 kc, 3000-6800 kc, 6000-13200, 13000-30000 kc.

Two-winding coils, UX base. Cat. SWA (four coils).....\$1.20
 Three-winding coils, 6-pin base (stickler interwound with part of secondary) Cat. SWB @.....\$1.40

UX sockets for use as coil receptacle, Cat. SX, @ 10c each. Forms, four for 60c, either UX or 6-pin. Six-spring sockets, Cat. SZ, @..... 11c each.

SCREEN GRID COIL CO., 145 W. 45th Street, New York City

RADIO WORLD and "RADIO NEWS"

BOTH FOR ONE YEAR

\$7.00

Canadian and Foreign \$1.50 extra

You can obtain the two leading radio technical magazines that cater to experimenters, service men and students, the first and only national radio weekly and the leading monthly for one year each, at a saving of \$1.50. The regular mail subscription rate for Radio World for one year, a new and fascinating copy each week for 52 weeks, is \$6.00. Send in \$1.00 extra, get "Radio News" also for a year—a new issue each month for twelve months. Total 64 issues for \$7.00.

RADIO WORLD, 145 West 45th Street, New York, N. Y.

Quick-Action Classified Advertisements

7c a Word—\$1.00 Minimum

AIR CORPS TRAINS 600 MEN yearly free; flying, radio, mechanics. Information for appointment, 25c. Lieut. Carroll, Box 533R, Taunton, Mass.

MANUSCRIPTS, typed, paragraphed and corrected, 75c 1000 words. Sylvia Camos, 1107 Chouteau, St. Louis, Mo.

"THE CHEVROLET SIX CAR AND TRUCK" (Construction—Operation—Repair) by Victor W. Pagé, author of "Modern Gasoline Automobile," "Ford Model A Car and AA Truck," etc., etc. 450 pages, price \$2.00. Radio World, 145 W. 45th St., N. Y. City.

NEW RADIO AMATEUR'S HANDBOOK, 180,000 words, 207 illustrations, 218 pages (10th edition, issued 1933). Issued by the American Radio Relay League. Price, \$1.00 per copy. Radio World, 145 West 45th Street, New York, N. Y.

S. GERNSBACK'S "RADIO ENCYCLOPEDIA," SECOND EDITION. A Guide-Book of Radio Information typically arranged in Alphabetical Order. Radio in all its branches, described, explained and illustrated. Size 9 x 12, 352 pages, Red Morocco-Keratol Flexible Binding. Loose-Leaf Arrangement. Price \$3.98 postpaid (Foreign and Canada add 35c extra). Radio World, 145 W. 45th St., New York City.

HENLEY'S "TWENTIETH CENTURY BOOK OF RECIPES, FORMULAS & PROCESSES." New 1933 Edition. Ten thousand processes, recipes, trade secrets and money-making formulas. For the laboratory, workshop, factory and home. Some subjects fully covered: Dyes, Inks, Waterproofing, Perfumes, Cement, Plating, Glass, Dentifrices, Varnishes, Soaps, Glues, Paints, Adhesives, Enamelling, Hairdressings, Cosmetics, Oils. Price, \$4.00. Book Dept., Radio World, 145 W. 45th St., New York City.

"THE FORD V-EIGHT-'B'-FOUR-'BB'-TRUCK," by C. B. Manly. A New and Practical Book for Everyone Interested in the Construction, Adjustment, Upkeep and Repair of the New Fords. Over 250 pages, 125 illustrations. Complete cross index. Pocket size, flexible leatherette cover. Price \$2.00. Radio World, 145 W. 45th St., New York, N. Y.

THE FORD MODEL—"A" Car and Model "AA" Truck—Construction, Operation and Repair—Revised New Edition. Ford Car authority. Victor W. Page. 708 pages, 318 illustrations. Price \$2.50. Radio World, 145 W. 45th St., New York.

A Special Issue of Real Interest and Importance!

RADIO WORLD'S

NATIONAL RECOVERY NUMBER

Dated October 14. Issued October 10. Last form closes October 3.

The publishers of RADIO WORLD believe that they can give special service to the radio trade, by issuing this National Recovery Number.

Advertisers in the radio field will have an opportunity of telling their sales stories to RADIO WORLD's thousands of subscription and newsstand readers throughout the radio field, at no extra cost for space. In fact, our special summer rates of \$100 a page, half, quarter and eighth

pro rata, and \$3.50 an inch (instead of the regular rates of \$150 a page and \$5.00 an inch), will be held open for this issue.

Every reader of RADIO WORLD is a potential buyer of your goods.

May we serve you?

Advertising Department, RADIO WORLD, 145 West 45th St., N. Y. City

ROLAND BURKE HENNESSY
Editor

HERMAN BERNARD
Managing Editor

RADIO WORLD

J. MURRAY BARRON
Advertising Manager

The First and Only National Radio Weekly
TWELFTH YEAR

Vol. XXIV

SEPTEMBER, 16th, 1933

No. 1. Whole No. 599.

Published Weekly by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y.

Editorial and Executive Offices: 145 West 45th Street, New York

Telephone: BR-yans 9-0558

OFFICERS: Roland Burke
Hennessy, President and
Treasurer; M. B. Hennessy,
Vice-President; Herman
Bernard, Secretary.

Entered as second-class matter March, 1922, at the Post Office at New York, N. Y., under Act of March 3, 1879. Title registered in U. S. Patent Office. Printed in the United States of America. We do not assume any responsibility for unsolicited manuscripts, photographs, drawings, etc., although we are careful with them.

Price, 15c per Copy; \$6.00
per Year by mail. \$1.00 extra
per year in Foreign countries.
Subscribers' change of ad-
dress becomes effective two
weeks after receipt of notice.

Practical Push-Pull Resistance Couplers

DIODE DETECTION, WITH BOTH THE REACTIVE AND NON-REACTIVE LINKS—THEORY OF DIRECT-COUPLED SYMMETRICAL CIRCUITS

By Herman Bernard

PUSH-PULL resistance-coupled audio is one of the several topics in radio concerning which theoretical aspects have been treated over a period of years, with some reduction to practice, but without the production of any circuit regarded as standard, or, indeed, any circuit which is used much at all. There are practically no receivers with such a circuit. Yet, like television, ultra-wave DX and other topics in the same hopeful class, the push-pull resistance coupler is bound to arrive at a commercially practical stage. Besides, it gives experimenters meanwhile an opportunity to pursue a hobby that offers interesting possibilities.

Push-pull resistance-coupled audio, as considered in this text, relates to the development of the push-pull circuit without the introduction of an input transformer. It is familiar practice to have a push-pull input transformer working out of a normal detector and have the succeeding stages push-pull resistance-coupled, but such a circuit is not considered within the true category because the use of resistance coupling should be exclusive.

Omission of Stopping Condensers

Besides the foregoing considerations, one might bear in mind that true push-pull resistance coupling may be developed in leak-condenser coupling hookups, which are reactive, or in circuits that omit the stopping condensers, and are called non-reactive. The term non-reactive means, in effect, equality of amplification for all

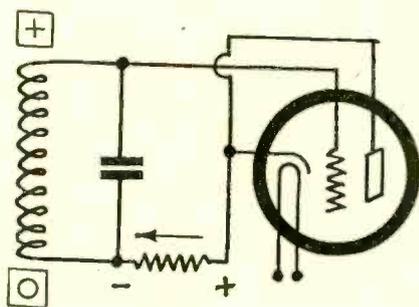


FIG. 1

The 56 used as a diode will stand 40 volts rms input. Diagram shows anode positive to a-c (sign in square), while direction of d-c current flow and d-c polarities of load resistor are designated.

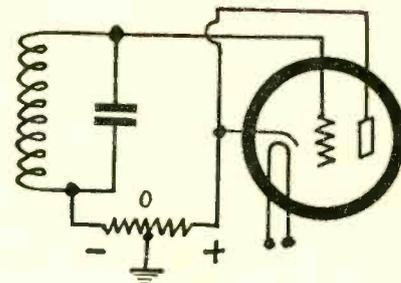


FIG. 2

The direct current through the load resistor is pulsating, so if the center of the resistor is taken as the reference point, at any instant the extremes have equal but opposite signs.

audio frequencies, which is true when a load is a pure resistance.

In actual practice true non-reaction is hardly possible, as effects are to be expected from unavoidable capacities, including even the elemental capacities of tubes used, capacity between wire connectors and capacity to metal chassis. These capacities, though small in quantity, are large in effect because of shunting of high tube or load impedances by small condensers. Nevertheless a circuit will be

considered non-reactive if it omits the stopping condensers.

To realize the problem of push-pull resistance coupling we must understand the rectification fundamental. A typical rectifier is shown in Fig. 1, consisting of a 56 tube used as diode, plate tied to cathode, this combination constituting the operating cathode, while the element that otherwise would be grid is the operating anode. The object of the rectifier is to
(Continued on next page)

These Four Circuits Work All Right

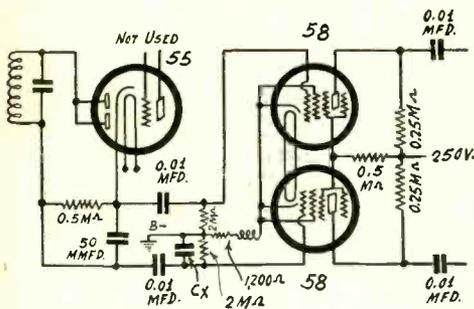


FIG. 3

This is a practical push-pull resistance-coupled circuit, using stopping condensers and grid leaks. The center of the load resistor may be grounded, if desired, but it is not strictly necessary, due to the subsequent leaks as parallel resistors with grounded center, the effect on the signal division being reflected back. Stopping condensers and grid leaks are used. This is a reactive circuit, that is, frequency affects the amount of gain somewhat. The 58's will drive 2A3 output tubes.

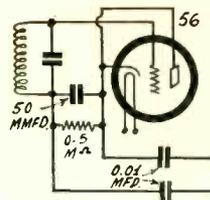


FIG. 4

The 56 used as a diode, with plate tied to cathode to constitute the operating cathode, and otherwise grid is anode.

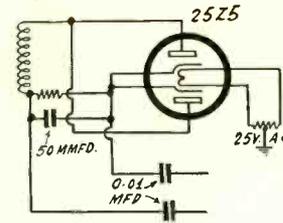


FIG. 5

The 25Z5 used as a half-wave rectifier. This tube requires a 25-volt feed to the heater. The 50 mmfd. condenser across the load resistor may not be necessary here or in Figs. 3 and 4.

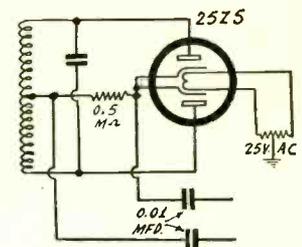


FIG. 6

Here full-wave detection, using the 25Z5, is illustrated, the circuit after the stopping condensers again being as in Fig. 3. By the full-wave method only half the voltage is achieved as by the half-wave rectifier.

(Continued from preceding page)

produce a direct-current output from an alternating-current input. The alternating current in this instance is radio frequency and in this sense all frequencies of the highest used in carrier radiation, to 20 kc, may be considered as radio frequencies.

Rectification Requisites

The alternating voltage in the primary of the transformer develops a voltage across the secondary. We are interested only in voltage except in power output tubes. Since it is alternating, no point along the secondary ever remains at any given voltage, but there is a fluctuation, measured in multiple cycles per second. During each cycle the voltage rises twice to maximum and falls twice to zero. The two maxima, however, are oppositely polarized during any cycle. Zero naturally is the same for both, being an identical quantity. Therefore the upper end of the coil will be negative maximum and positive maximum once each cycle.

The following are requisites for rectification: (1), an alternating-voltage input; (2), a positive anode; (3), a device capable of rectification; (4), a continuous direct-current path. Besides there must be a load to render practical the utilization of the rectification.

We have the a.c. The positive anode occurs once in each cycle, so we have that. The tube will rectify. A continuous current path is provided because the tube impedance is low, sufficient direct current can flow through it, and there is no discontinuity in any part of the external circuit. A load resistor is provided.

Half-wave Type

The rectifier in Fig. 1 is of the half-wave type, because rectification takes place only when the anode is positive, and it is positive only during half the wave period. On the diagram the alternating current signs are in squares, and the anode is shown as positive, bottom end of coil as zero, both a-c values.

The positive a-c sign does not represent a constant value of voltage, but during the alternation when the anode is positive it is so by the effective quantity of a-c voltage. This is obtained by taking the square root of the sum of the squares of

the positive voltages during the alternation and is the familiar root-mean-square voltage (rms.).

Now that we have accomplished rectification we have to consider the flow of the new current, which is direct current. There may be residual fluctuation in the d-c, but a condenser will remove it. Although a-c flows in two directions, d-c flows in only one direction. That is, d-c does not reverse itself.

Direction of Flow

The direction of current flow in an external circuit of a rectifier is from cathode to anode and takes place only when the a-c is at a positive value on the anode. The signs ascribed to this direction are inherited from the earlier and erroneous theory of electricity, but because embedded in the recorded science, are still retained. We say therefore that in the external circuit the current flows from plus to minus. Inside the rectifier it flows from minus to plus, for that is in reality the same direction.

Take a clock as example, turn the hour hand through 360 degrees, starting at 9. The rotation is from left to right, until 3 is reached, when the direction is from right to left, and yet there has been only one actual direction, that of clockwise. The wheels of an automobile are always turning in the same direction at the same time, though by applying some other test, as left-and-right based on an arbitrary zero line, the same anomaly exists as in the case of direction of current flow in a rectifier and its external circuit.

Action During Positive Cycle

Taking the two extreme instances in the rectifier, when anode is positive and when it is negative, we know that rectification takes place only when the a-c voltage on the anode is positive, whereupon d-c flows in a known direction, but what happens when the anode is negative? Since no rectification takes place, nothing happens. The circuit is dead on the negative a-c alternation, just as if the rectifier tube were removed from its socket during each negative excursion of the carrier.

Broadly, there are two frequencies to

consider, the radio-frequency carrier and the modulation of that carrier by the signal, hence the object of the form of rectification used on the carrier, called detection, is to eliminate the carrier and leave only the modulation or signal. When signal is referred to, audio frequencies are meant. When carrier is referred to, radio frequencies are meant. The fact that the modulation is impressed on the carrier need not prove confusing, since the effect is to change the frequency or amplitude of the carrier, which is a radio frequency, even though the rate of change may be at an audio frequency. At least the carrier, modulated or not, is inaudible. The detected component of a modulated carrier is audible to a suitable load.

Signs of the Circuits

The two signs for alternating current and the two for direct current in Fig. 1 have no intrinsic relationship whatever. For instance, the zero point for a-c at a given instant when there is rectification is the same point as negative of the rectifier. The secondary is a short circuit to d-c, therefore the point marked positive for radio frequencies (denoted by sign in square) is negative for audio frequencies, being the same for d-c at one end of the coil as at the other. The d-c signs are not circumscribed. They denote the polarities during rectification. The arrow shows the direction of d-c flow.

How far have we progressed toward push-pull resistance coupling? We have reduced a carrier to direct current and have a permanent d-c positive sign at one end of the load resistor and a permanent negative sign at the other end of the load resistor, for all purposes during full-wave or half-wave rectification, and permanent zero signs during non-rectification.

An Author's Contention

We have considered direct current, but not in its true light as existing in the circuit for detection of broadcasts. It is true that the current is unidirectional, but it is also true that direct current may be continuous or discontinuous. We found discontinuity during the alternation when

Two of These Are Duds and Two Ace-High

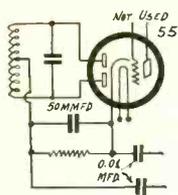


FIG. 7
Full-wave detection, using the 55. The triode elements can not be used, as there is no suitable method of making the B voltage effective without unbalancing the circuit.

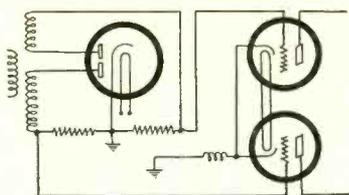


FIG. 8
Considering the omission of stopping condensers as constituting non-reactive coupling, a circuit like this might represent a first attempt. Either the driven tubes have simultaneously negative grids or alternately negative grids, neither instance representing symmetry.

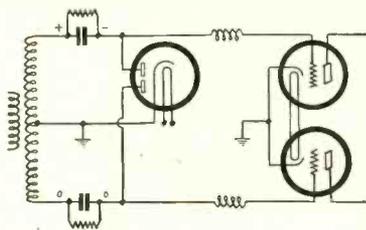


FIG. 9
The danger in non-reactive coupling is that one grid may be driven positive. When the upper diode is conducting the upper driven grid is negative, but the lower driven grid has zero bias, because grid is returned to grounded cathode through a non-current-carrying circuit.

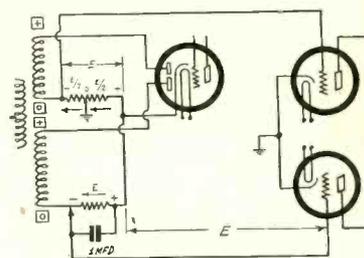


FIG. 10
A true push-pull resistance-coupled circuit. The d-c voltage across the load resistor (upper diode) is divided, center of the resistor grounded, and when negative signal cycles are applied to the upper driven grid positive ones, with bias suitably bucked, are applied to the lower driven grid.

the anode was negative. Likewise, though continuous, it may be steady, or unsteady. If it is unsteady it is called pulsating, and this is the type of direct current existing in detector outputs. The pulses are equivalent to amplitude changes in the steady state of d-c, and these changes are patterned by the original audio frequencies as put into the microphone at the station.

It is the author's contention that in a vacuum tube with only a resistive load in the plate circuit, or output circuit, there is never any alternating current but that there is pulsating direct current, and any presence of alternating current would be due only to a coil in the plate circuit, where reincarnation of a-c is effected by the electro-magnetism.

Whenever we have an a-c voltage or a pulsating d-c voltage across a load we may select the center of the load as the datum or reference point and then the push-pull effect is introduced if we take off the output from the extremes, for the voltages at any instant at these extremes will be equal in quantity but directly opposite in sign. Thus, in Fig. 2 the center point may be taken as zero. The left-hand branch would change from zero to negative maximum and then the right-hand branch from zero to maximum positive. It may be argued that the midpoint is not zero, but half of the maximum, but zero is an arbitrary point, and the termination of the impedance into which the whole works decides the zero point.

A Practical Circuit

So far we have the possibility of a push-pull input, using no transformer but simply a resistor. Now we shall introduce the method in a practical circuit, Fig. 3, and observe precautions that experience has taught.

The load resistor is 0.5 meg. and across it is a small condenser, 50 mmfd. This condenser is not always necessary, as there is usually sufficient inherent capacity to bypass the residual ripple. Two stopping condensers are used, 0.01 mfd. each, or larger, one connected from the coil side of the 0.5 meg. resistor to grid of the succeeding stage, the other connected from cathode of the diode to grid

of the succeeding stage. Two grid leaks are used, 2 meg. or higher resistance, from respective grids to grounded B minus. It is therefore not necessary directly to ground the center of the diode load resistor, for since the grid leaks are in parallel with that load, grounding the center or common point in the leak circuit will suffice. A biasing resistor of 1,200 ohms will do for the two 58's, an r-f choke of 10 mlh. or higher inductance being used to help kill off r-f oscillation that otherwise might be present. If there is still oscillation, additional similar chokes would have to be used between each grid and its grid leak. The output is to be connected to the resistance-loaded grid circuits of push-pull power tubes.

Why the Stopping Condensers

The reason for including the stopping condensers is that the direct connection of one of the grids (upper in Fig. 3) would result in a positive grid. That is, the change would be by from zero bias to positive bias. A way of overcoming this would be to introduce an additional rectifier to buck out the positive bias, as was suggested by J. E. Anderson in the January 21st issue, 1933.

Instead of the 55 the 56 may be used as diode for the Fig. 3 circuit, as shown in Fig. 4, or the 25Z5 as in Fig. 5. These are half-wave rectifiers. For full-wave rectification the circuits are shown in Fig. 6 for the 25Z5 and Fig. 7 for the 55, of which the triode is rendered useless because of unbalance if B voltage is applied. Following the rectifiers there would be the same sort of circuit as in Fig. 3, and of course in addition the power stage would be included, biased as usual.

In connection with all of the foregoing circuits it will be found that the capacity to ground is unequal in the two legs, as represented by the leaks, or, if the load resistor of the diode is grounded at center, by one leg of that load. In general the capacity to ground on the cathode side is larger, and on the other side is compensated for by the additional capacity Cx, in Fig. 3.

Cx for All Circuits

Cx should be included in all circuits.

It should be put on the side that results in appreciable increase in signal intensity. While the capacity value is not extremely critical, for fine adjustment it would be necessary to measure the capacity across each leg, and make up for the deficiency in the one leg. This measurement may be made with any oscillator having a known inductance and generating a known frequency. The tuning condenser capacity can be obtained by computation for this frequency, and the capacity for the new frequency likewise obtained when one and the other legs of the push-pull circuit are used in parallel with the tuning condenser. When the two differences are obtained the smaller is subtracted from the larger, and the final difference is introduced across the smaller to equalize the capacity. All computation may be avoided by consulting "The Inductance Authority," a recent book by Edward M. Shiepe.

So far we have used stopping condensers and considered only half-wave rectifiers. Now let us see what can be accomplished if the condensers are omitted.

A Faulty Circuit

Fig. 8 shows the omission of the stopping condensers, but this is the same situation previously discussed as impossible, because of the positive bias on one of the grids. In direct non-reactive coupling the bias on the succeeding tube may be only that arising from the d-c flow in the carrier-rectified circuit, this being known as diode biasing. Obviously positive biasing of the grid is out of the question.

In Fig. 7 when the lower anode is positive to r.f. the left-hand resistor carries d-c, positive at cathode, negative at the other end of the resistor, so negative may be connected to grid of a following tube. If the upper anode is positive to r.f. at the same time, then the grid of the other tube may be connected to negative side of the second load resistor, to right. However, both grids are negative at the same instant, so the circuit is not push-pull. Let us reverse one of the coils. When one anode is positive the other is negative, so when one diode is conducting the other is not conducting, and the upper grid is positive. The circuit won't work.

(Continued on next page)

(Continued from preceding page)

What is required is that one grid be swung negative at one instant and the other grid be swung equally positive at the same time, but that the bias should not run positive.

Another Try

The more or less arbitrary designation of polarities makes it difficult sometimes to comprehend the aim, but if it is remembered that the requirements consist of making one tube at a time handle the load, without grid of either going positive, the fulfillment can be better gauged.

Using a conventional center-tapped secondary, the non-reactive method may be considered with the load resistors in the negative leg, Fig. 9. Center is connected to cathode and grounded. Also cathodes of the succeeding pair of tubes are grounded. Some question may arise as to where the positive voltage is. The answer is that the cathode is the positive and that the anode ends of the resistors are alternately zero and negative, so the grids of the pair of tubes after the rectifier, if tied to respective anodes, share the work alternately and equally during each cycle. To prevent the detection being communicated to the pair of tubes at right in Fig. 9 large radio-frequency chokes are used, 25 mlh, or greater inductance, and to enable the anodes to be polarized by r.f. large enough bypass condensers have to be used across the individual load resistors.

Not So Hot

A somewhat greater departure from non-reaction results because the condensers across the load resistors have to be large enough not to attenuate the input to the anodes, and the larger they are the more the circuit departs from non-reaction. Also the chokes have to be large enough to prevent any considerable amount of r.f. getting into the first audio tubes. The associated circuit and tubes have to be shielded and even the grid leads to overhead caps of the 58's shielded and shield sheath grounded. Otherwise there will be r.f. oscillation. To avoid excessive attenuation due to the resistance loads the resistors have to be considerably smaller than usual.

In this circuit full-wave rectification is used. One diode-to-cathode circuit rectifies at a time. The object is to avoid a positive grid. Let us see if this is accomplished. When the upper diode is conducting the resistor is negative at anode and positive toward cathode. Grid is connected to negative. All right so far. During the time the upper diode is rectifying the lower one is idling. The grid of the companion succeeding tube is connected to the plate of the lower diode.

If the lower section of the diode is not conducting, then any voltage arising will be in accordance with the upper diode, for this is when the positive-grid danger arises for the lower tube. Tracing the lower tube's d-c circuit, grid is connected to one diode anode through a choke and returns to ground through the lower half of the secondary. Since the grid voltage is that between cathode and grid, and since cathode is grounded and grid goes through a no-current circuit to ground, grid is grounded, and there is zero bias, but no positive grid. But there is no symmetry, no push-pull.

More Likely Circuit

To achieve push-pull it is necessary that when one grid is negative in respect to the signal the other is positive. We have avoided a positively-biased grid but we have not provided opposite signs at the grids at any instant, as no positive signal region is provided.

In Fig. 10 is shown a circuit that subscribes to the requirements. It is a half-wave diode detector, across which is developed the d-c voltage E when the upper

anode is positive to radio frequencies. The center of this resistor is grounded, and as the cathodes of the succeeding pair of tubes are grounded, half the voltage across E is put into the upper driven tube. However, since half-wave detection develops twice the voltage of full-wave, by taking off half from the half-wave type we still have the same amount of signal voltage for the driven stage as if all the voltage from a full-wave circuit were used.

The midpoint may be taken as zero, so when the upper anode is conducting there is a condition across the resistor which develops opposite signs at the extremes. The left-hand end is put into the grid of the upper tube following, and being always negative, the tube is diode-biased exclusively, in the familiar manner, and the bias is equal to the signal voltage.

The Stumbling Block

The lower driven tube is the stumbling block. If its grid were returned to positive of the load resistor in the upper rectifying circuit, when the upper grid is negative the lower one is positive to an equal amount, considering the signal only. But considering also the d-c bias effect of the voltage, when the upper grid is $-E/2$ the lower grid is $+E/2$, whereas there should be a bucking bias introduced in the lower driven tube to keep its grid away from possibility of positive bias.

If we use the lower diode of the 55 as additional rectifier, operating in phase with the other, we can introduce a varying bucking bias that is proportional to the diode-bias above, and we have only to find out what that bucking bias should be and how to insure it. The total voltage in the upper rectifier is E , the input to the upper driven tube is $-E/2$, the unchecked condition of the lower driven grid is $+E/2$, which is a difference of E between grids, and therefore the bucking bias should be equal to E also, so that the biases on the two driven tubes will be the same at any instant.

Bias Adjusted

There is the signal to consider. There may be a little radio frequency in the load resistor of the upper rectifier, which a condenser will remove, as stated, and shown in Fig. 1, etc. In the bucking-bias circuit we do not desire any signal whatsoever, therefore put a large condenser across the load resistor in that circuit, 1 mfd. Thus a bucking bias is present that is always twice the value of the positive bias that otherwise would result from the signal alone. So the static operating condition of the lower driven tube is $-E + E/2$, or $-E/2$, and that is exactly the static operating condition of the upper driven tube. Thus as the positive cycle of the signal is applied to the grid of the lower driven tube the 1 mfd. condenser bypasses the signal to the grid, and the condition of equal but opposite voltages is achieved and "equal and equal" bias safeguarded.

An adjustment is necessary, and the bucking resistor is therefore made variable.

The transformer is predominantly used in push-pull audio circuits because no adjustment is necessary, the gain is generally

greater and the servicing is easier. Such inclusion is more expensive as to parts but less expensive as to testing and adjustment, so that from a broad cost viewpoint the two may be considered about equal.

Servicing is very important, and the inclusion of the transformer simplifies this greatly. Few service men would have the equipment necessary to balance a resistance-coupled push-pull circuit, and possibly not many of them would be equipped with the technical knowledge, not that deep knowledge is required, but that there have been little data available to them. Hence the current articles, as well as previous papers in these columns, will prove of considerable assistance to those desiring to familiarize themselves both theoretically and empirically with this interesting circuit.

Other Circuits

The realm of push-pull resistance coupling is very large, and other circuits than those discussed this week may be used to advantage. Nothing has been written up this week about the phase-shifting tube, but the possibilities in that direction are inviting, rather, however, from the viewpoint of the reactive coupler.

One idea is to use the triode of the 55 or other such tube as the phase shifter, then have push-pull drivers and push-pull output. The 53, being two equal tubes in one envelope, may be used so that one of the tubes is a phase-shifter. Some experiments made with this tube in this manner have not proved successful enough. However, all the circuits shown this week, including those that are fallacious, have been tried out. Those stated as working do work and those stated as not working, while producing a signal, create considerable distortion, and are not even theoretically acceptable.

The increase in the amount of amplification ahead of the audio channel, which has been going on steadily for several years, makes for the reduction in the amount of audio amplification, so that there are many circuits that have the detector feeding directly into the power tube.

Can Drive Triode Output

Generally this consists of a screen grid detector driving a pentode output tube, in smaller sets, but there is no reason why, with higher r-f and i-f gain in larger sets, the detector can not be made to swing the output tube or tubes, provided that the detector will stand the 50 or 60 volts necessary to load up the output.

While the diodes of the duplex-diode-triode tubes will not fulfill this requirement, the rectifiers used for B supplies of course will. There are two considerations: the capacity of the tube elements should not be high, and also, for hum reasons, the rectifier should be of the indirectly-heated cathode type. Therefore diagrams show the 25Z5 used in this way.

Heater Rectifiers

There is also a 6.3-volt half-wave rectifier heater type tube, the 1-v, and a 12.5-volt half-wave heater type rectifier, 12Z3, concerning which some data will be found on page 11. Any one of these may be used. At present they are the only heater type rectifiers. The 1-v and the 12Z3 may be used only for half-wave rectification, the 25Z5 for either half-wave or full-wave.

SOME EXCELLENT RADIO BOOKS


"1932 Official Radio Service Manual," by Gernsback\$4.00
 "This Thing Called Broadcasting," by Alfred N. Goldsmith and Austin C. Lescarboura.. 3.50
 "Audio Power Amplifiers," Anderson, Bernard 1.50
 "Radio Frequency Measurements," by E. B. Moullin12.50
 "Short Waves," by Charles R. Leutz and Robert B. Gable..... 3.00

"Perpetual Trouble Shooter's Manual," Nos. 1 and 2, by Rider. Each.....\$5.00
 "115 Latest Commercial Set Diagrams," by Rider 1.00
 "Drake's Radio Cyclopedia," by Manly..... 6.00
 "Elements of Radio Communication," by Morecroft 6.00

RADIO WORLD, 14b West 45th Street, New York, N. Y.

A 10-TUBE SUPER

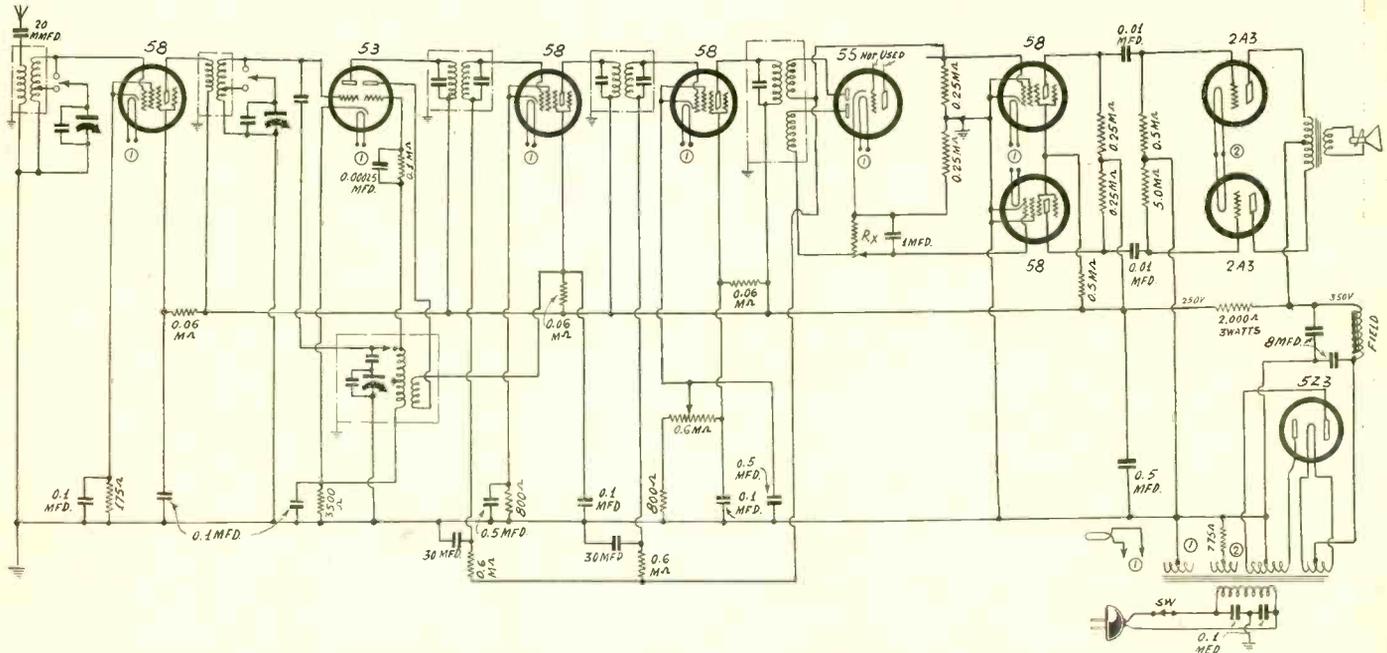With True Push-Pull Resistance-Coupled Audio



One of the anodes of the 55 is used as the separate rectifier to supply a bucking bias to the lower driven 58, the grid of which otherwise would run positive. The grid and plate of the 55 triode are not used because the cathode has to be "left in the air" to support the push-pull circuit.

THE true push-pull resistance-coupled audio amplifier described in the foregoing pages is included in the complete receiver design shown above. Except for the 53 mixer tube, the circuit ahead of the detector is conventional.

The reason for the small series condenser in the aerial circuit is to improve selectivity ahead of the modulator. Only a three-gang condenser is used, therefore, as one section tunes the oscillator and another the modulator, the remaining one is for the t-r-f stage. One such stage without loose coupling between antenna and tuned winding would result in some squeals. These are absent when the selectivity ahead of the modulator is raised high enough, and loose coupling is one of the easiest and most effective ways of doing this, even though the input is reduced somewhat. If larger input, consistent with some squeals, is more satisfactory, the condenser may be made larger.

The 53 as a mixer has not been used much, but works well, when the operating conditions are right. It is critical, in that it will not work at all unless the voltages are right. Thus it resembles the 2B7 tube to this extent. It is advisable to have a low plate voltage, and this may be obtained from the screen of the first intermediate tube.

Tests of Biasing Resistor

The oscillator grid leak, shown as 0.1 meg., and the biasing resistor, marked 3,500 ohms, are critical. Since oscillator grid is returned to cathode, the oscillator bias depends on grid current through the leak. Hence both the leak value and the bias affect the operation, and in actual practice 3,100 ohms proved excellent, but various resistors around that value, say, 3,000 to 3,500 ohms coding, had to be

tested before one was found of exactly the desired value.

The two intermediate tubes are subject to automatic volume control, and the filter circuits are shown with very large electrolytic condensers across the resistors (30 mid. across 0.6 meg.). The reason for specifying the large capacity is that sometimes its inclusion boosts volume considerably. In other instances it does not, and if it doesn't, use 0.1 mfd. or somewhat higher capacity, but it is well first to try the very high electrolytic capacities, which come in small containers, about as long as your finger and twice its diameter. There is greater volume if the electrolytics in this circuit are connected in the a.v.c. filter with positive to a chassis and negative to the resistor.

There should be no trouble in the tuner, as it is familiar and besides follows authenticated lines. Neither should there be any trouble in the succeeding part of the receiver if directions are followed.

Fixing Up One Coil

Perhaps it is just as well to build the audio circuit as shown and try it out. To accomplish the construction with parts normally obtainable it is necessary to get a center-tapped intermediate coil, remove the interconnection of the two wires that create the center, so that you have two separate coils, both fed from the same primary, and also to remove the tuning condenser that was across the center-tapped secondary. This condenser removal consists merely of unsoldering the connections, or one of the connections, if the condenser is used as a supporting bracket for the coil, as is true in some assemblies. Now you have a coil with the required three windings and the secondaries are connected with beginning of one coil to anode, beginning of other to anode, and

ends to loads. Select your own "beginning."

Unfortunately, the ratio is not favorable, as the input to each diode is only half of what it could be if each separate secondary had twice the number of turns it now has, that is, each had the same number as the primary. This is not a serious drawback, however, for trial of the circuit, but merely results in somewhat less quantity of sound than one might expect without knowing a cause of this reduction.


It would be advisable to have the winding serving the lower diode somewhat more closely coupled to the primary than is the other secondary, if this is practical in the coil assembly, because the voltage will tend to lag in the lower branch, where it is preferable to have it higher so that it may be adjusted to equal the other.

The audio resistors used should be measured and equal values included. This applies particularly to the 0.25 meg. and 5.0 meg. values. Then the resistor R_x , which may be 0.5 meg., is adjusted until the same plate current flows through each 0.25 meg. in the 58 circuit, when a steady-modulated oscillation is put into the antenna. This means that broadcasting stations may not be used for the test but a single-tone-modulated test oscillator should be.

Hot Resistor Test

In the absence of instruments or knowledge about devising testing methods additional to what has been suggested, one may simply feel the 0.25 meg. resistors in the 58 plate circuits. The one in the upper branch can't be troublesome, so judge by it. Feel the other one. If it is perceptibly hotter there is grid current in the plate circuit of the lower 58, so use more of R_x , or, if fixed values are being used, include a higher resistance for R_x .

HOW TO Pentagrid Converter

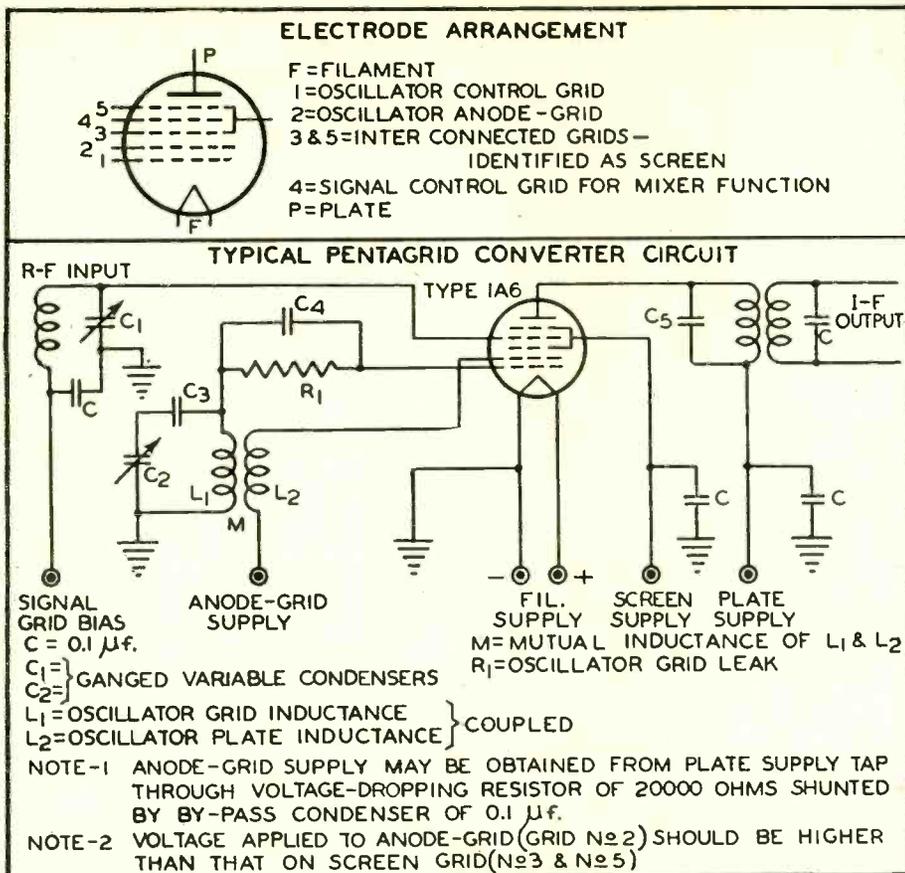

THE type 1A6 tube is a pentagrid converter designed primarily for use as a combined oscillator and mixer in battery-operated superheterodyne receivers. The 1A6 possesses many operating advantages over the oscillator-mixer combinations hitherto employed for battery-operated superheterodynes. Among these advantages are: Economy in A current drain, greater operating stability, higher and more uniform translation gain, volume-control effectiveness comparable with that of a super-control amplifier in an i-f stage, reduction or elimination of the intercoupling effect between the signal and the oscillator circuit, almost entire elimination of radiation from the local oscillator, simplicity of oscillator circuit adjustment, and economy in chassis space requirements.

Resembling the 2A7 and 6A7 in both function and operation, the 1A6 is subject to the same general operating requirements as those applying to other pentagrid converters. The circuit shows a desirable arrangement for the 1A6. An explanation of the various circuit elements is included.

Coupling Between Units


The design of a superheterodyne receiver employing the 1A6 is conventional. There are no unusual features which must be taken into consideration. The r-f input circuit, the i-f transformers, and the gang-tuning condensers are designed in the usual manner. No data are given in this note on the design of these parts, since they will vary greatly with the intermediate frequency used and the frequency band to be covered by the receiver.

In designing oscillator coils for the 1A6, the coupling between oscillator grid-coil and oscillator anode-coil should be slightly greater than that commonly used with triode oscillators. Tests have shown that for the 1A6 the ratio of M/L (the mutual inductance M between the oscillator anode-coil and the oscillator grid-tuning-coil to the inductance L of the oscillator grid-tuning-coil) should be approximately 0.35.

Higher values of coupling than that obtained with the above ratio may cause difficulty in tracking the oscillator frequency with the signal frequency, while lower values of coupling will result in reduced translation gain.


The diagrams show details for the construction of three oscillator coils designed to give good results with the 1A6. There are no unusual features involved in the design or construction of these coils. Two methods of construction are shown to enable the designer to choose the coil form better suited to his space requirements. Each of the three coils shown has an M/L ratio which will give satisfactory operation of the 1A6. The coils shown are suitable for use with an intermediate frequency of 175 kc in a broadcast-band receiver. The use of other intermediate frequencies will necessitate changes in the inductance of the coils. Usually coils which are suitable for the 2A7 or 6A7 will be found to be satisfactory for the 1A6.

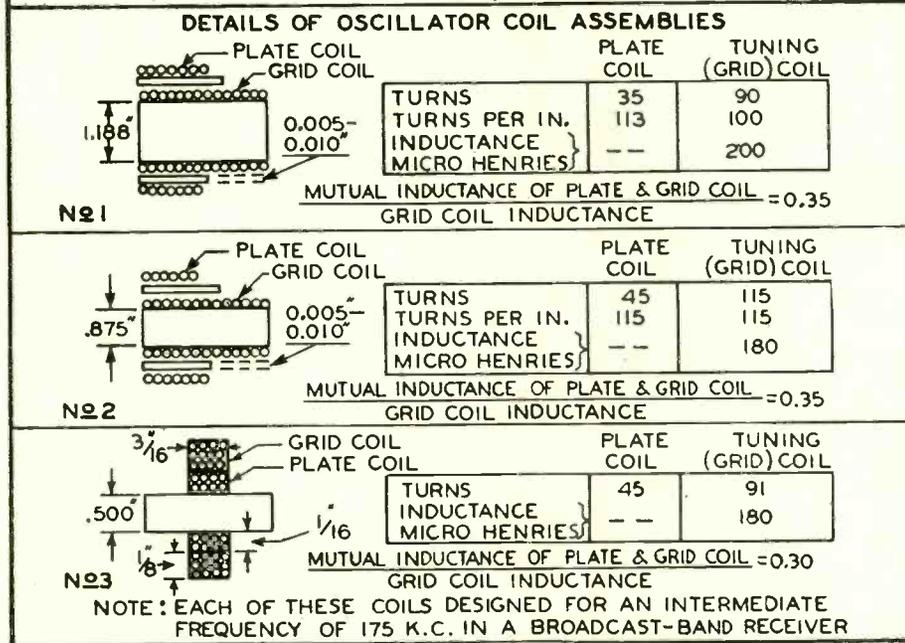The curve sheet shows the conversion transconductance of the 1A6 versus signal-control-grid volts. This curve was taken with 180 volts on the plate of the



A typical circuit for the 1A6, with notation of socket connections. Details are given for oscillator coil assemblies.

Cathode Feedback in Oscillator

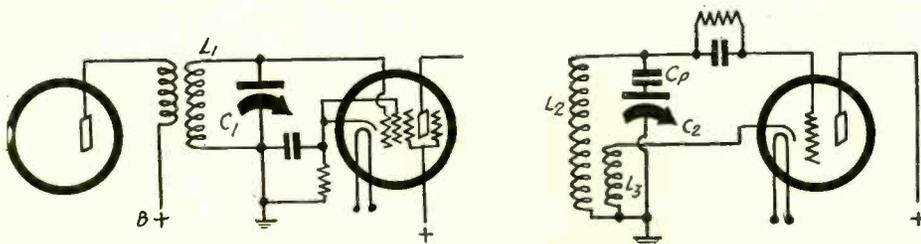

A modulator circuit, as at left, may be coupled with a local oscillator in a superheterodyne where the feedback winding in the oscillator is through the cathode circuit (right).

USE THE 1A6 Converter Tube for Battery Sets

1A6. With 135 volts on the plate, the conversion transconductance usually will be about 90% of the value shown. The volume-control capabilities of the tube are clearly indicated by the curve.

Translation Gain Formula

The translation gain obtainable with the 1A6 is:

$$\frac{a S_c Z_{rP}}{Z + r_p}$$

Where

- a = Voltage ratio of the i-f transformer
- S_c = Conversion transconductance
- Z = Effective impedance of the i-f transformer across the input terminals
- r_p = Plate resistance of the 1A6.

With transformers ordinarily used, the translation gain of the 1A6 approaches 40. With special high-impedance transformers, a gain of approximately 60 can be readily obtained.

TYPICAL OPERATING CONDITIONS

Plate supply voltage	135	180	Volts
Oscillator grid leak (R ₁)	50,000	50,000	Ohms
Oscillator grid condenser	200	200	mmfd.
Oscillator anode-grid supply voltage	135	180*	Volts
Screen supply voltage	67.5	67.5	Volts
Signal control-grid bias voltage	-3	-3	Volts
Oscillator control-grid current	0.2	0.2	Milliamperes
Oscillator anode-grid current	2.3	2.3	Milliamperes
Screen current	2.5	2.4	Milliamperes
Plate current	1.2	1.3	Milliamperes
Total cathode current	6.2	6.2	Milliamperes
Oscillator coil M/L ratio	0.35	0.35	
Conversion transconductance at -3 volts on grid #4	275	300	Micromhos
Conversion transconductance at +22.5 volts on grid #4	4	4	Micromhos
Plate resistance	0.4	0.5	Megohm

*The oscillator anode-grid voltage must not exceed 135 volts. If the oscillator anode grid is supplied from a plate-voltage source of more than 135 volts, a voltage-dropping resistor must be used. With 180 volts plate supply, a 20,000-ohm voltage-dropping resistor in series with the oscillator anode-grid will reduce the voltage to a permissible value.

†Conversion Transconductance is defined as the ratio of the intermediate-frequency component of the mixer output current to the radio-frequency signal voltage applied to grid #4. In determining the performance of a frequency-converter stage, S_c is used in the same way as g_m (mutual conductance) is used in a single-frequency amplifier computations.

Latitude Permitted


The tabulation gives typical operating conditions for the 1A6, but these conditions do not necessarily provide the best results obtainable. The voltages, resistors and coils may be varied within fairly wide limits to fit the conditions of a particular application, provided that maximum ratings are not exceeded.

In general, decreasing the voltage E_{c3} and E_{c5} from 67.5 volts will decrease the gain. The screen voltage must, however, never exceed 67.5 volts under any conditions of operation. The optimum value of screen voltage is dependent on other electrode voltages and on circuit constants. All currents will increase with increasing screen voltage. A reduction in the oscillator grid-leak resistance R_1 increases the gain and, at the same time, the currents.

An increase in the M/L ratio of the oscillator coil operates in the same way.

The total cathode current in the 1A6 should never exceed 9 milliamperes. Varying operating conditions to raise the cathode current above the 6.2 milliamperes shown for typical operating conditions usually will not increase the gain appreciably. Consequently, more satisfactory operation of the 1A6 is obtained with approximately 6 milliamperes cathode current, since higher values tend to shorten the life of the tube.

The typical operating conditions for the 1A6 set forth in this note have given satisfactory results in our laboratory. In designing circuits for the 1A6, it must be remembered that a large number of variable factors is to be taken into consideration, say RCA Radiotron Co. and E. T. Cunningham, Inc. The tubes are quite flexible in their voltage requirements, so that reasonable care in the selection of the supply voltages and circuit constants will insure better operation than provided by combined oscillator-mixer circuits using tube types not especially designed for this dual function.

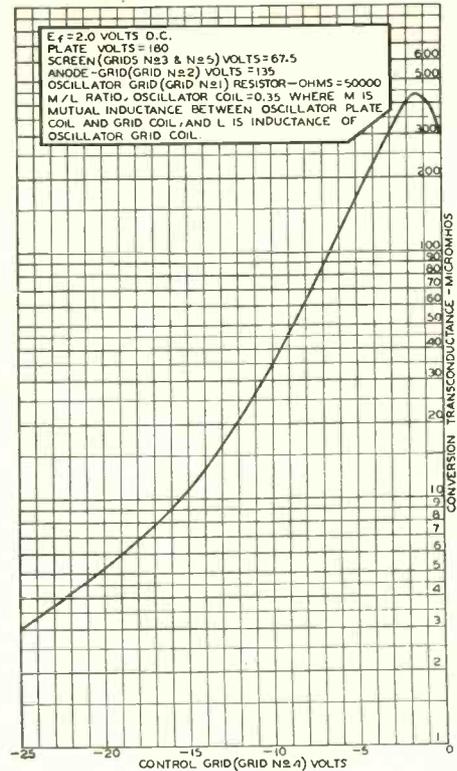

Operation characteristics of the 1A6. The control grid voltages are plotted against conversion transconductance in micromhos.

Right or Wrong?

QUESTIONS

1. Which gives the greater sensitivity, the 56 tube or the 53 as driver of output, transformer coupling between?
2. If a transformer has a skinny primary will the frequency coverage be greater or less than if the primary were large?
3. In a resistance-coupled audio amplifier, is it desirable that there should be a-f regeneration, or should the feedback filtration be made so complete as to eliminate all such regeneration?
4. What are the power output of the 33 and its amplification factor at standard operating voltages? What sort of a tube is it? Is it necessary to filter the output on account of the large plate current?
5. Is there a tube now available that affords a constant output? What is the requirement of a constant-output tube and what would be its advantages?
6. Is there a 1.1-volt amplifier triode, and if so, state its characteristics?
7. Can a B supply be utilized for sound trucks without B batteries?
8. Does a neon tube in television utilize a large percentage of the available light?
9. Is there a standard classification of short waves?
10. What improvements have been made in the 38, 41, 42, 89 and 2A5 and to what purpose?

ANSWERS

1. The 53 gives greater sensitivity. Its two plates may be tied together and its two grids tied together, to constitute a single operating tube, and the amplification factor will be around 16 instead of around 8 for the 56.
2. The frequency coverage, or ratio, will be greater in the case of skinny primaries than with large primaries, because the capacity between primary and secondary is less. This capacity appears as a lumped capacity across the coil terminals

of the tuned secondary and therefore tends to reduce the frequency ratio.

3. It is imperative that there be regeneration to insure sensitivity. However, the amount of regeneration must not exceed a certain level, otherwise motorboating results. The feedback filtration therefore should not be so complete as to remove all possibility of audio regeneration. It would be impractical, anyway, to achieve such approach to perfection of filtration at audio frequencies.

4. The power output of the 33 is 0.7 watt and the amplification factor is 70. The tube is a battery-operated output pentode (power tube), of the 2-volt series. The plate current being small, there is no need of an output filter for the purpose of protecting a speaker winding.

5. There is no constant-output tube. The requirement of such a tube is that its amplifier should have automatic volume control applied in the same envelope, perhaps through special geometry of the single tube. The advantage would be the isolation of a. v. c. to each stage thus self-controlled.

6. Yes, the 864, a 1.1-volt filament type tube, 0.25 ampere filament current, 135 plate volts, 9 volts negative bias. It is a Class A amplifier triode.

7. Yes, an auxiliary generator can be hooked up to the fan belt and made to supply the plate voltage.

8. No, only a small amount of the available light can be utilized in usual practice, with the television neon tube.

9. There is no standard classification for short waves, but engineering committees are holding meetings with the idea of formulating a proposed standard.



10. These five tubes have been improved so that the grid emission is reduced considerably, thus permitting the use of higher values of grid leaks.

STABILIZATION OF I. F.

Method That Is Fool-Proof and Even Enables Three-Stage Amplifier

By Roger Beale Conant

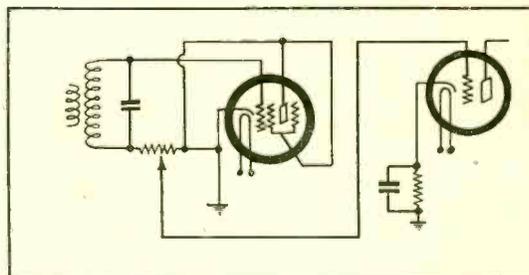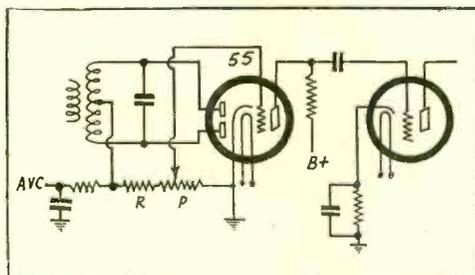At left R is a limiting resistor to prevent putting into the diode-biased triode all the rectified voltage. P is the manual volume control. A grid leak is needed in the next tube. In the drawing at right a 56 works into an audio amplifier.



OSCILLATION in the intermediate amplifier is a common trouble these days, with two-stage high-gain amplifiers, and therefore some pains were taken to achieve a reliable cure that applies generally.

In brief, the cure consists of choke-condenser filtration of each plate circuit in the intermediate amplifier, and including the modulator plate, besides cathode choke-condenser filtration in the first intermediate amplifier, with a choke between the detector and the feed to the first audio, a small bypass condenser on the detector side but none on the audio side, and 1 mfd. for cathode bypass. This method was applied to three viciously oscillatory circuits and quieted them all.

Shielding Necessary, Too

Besides the foregoing, the usual shielding of coils and tubes, using standard tube shields, is necessary. Control grid leads to overhead caps should be shielded and shields grounded. Shielded wire suffices.

It was found that a common screen supply could be used for all tubes served, including r-f and mixer tubes, as well as i-f tubes, without introducing any trouble.

The bypass capacity in the cathode and screen legs had to be 1 mfd., and therefore some expense is incurred, but it is worth while, since the sensitivity is lifted to a high level, with a gain of more than 200 per stage using doubly-tuned coils, and no gain sacrificed to attain stability.

Although it was found preferable to filter the plate circuits as explained, tests showed that most of the trouble was in the cathode branches, which can be understood readily, since the cathode is common not only to the plate, screen and suppressor circuits, but is common to part of the grid circuit as well. That is why the cathode capacities are 1 mfd. for bypassing, and as an extra precaution the stage that has the greatest tendency to oscillate, the first i-f, has a choke in the cathode leg as well.

Three Stages Practical

Using the same fundamental parts, without the precautions outlined being taken to the fullest, the gain in the intermediate amplifier had to be held down considerably to insure stability, and yet when the remedies were introduced the gain could be as high as the circuit, constants and standard voltages permit, and the bias had to be no more negative than standard. It was even possible to use three stages of i.f. (four coils) without oscillation trouble. Anyone who has

experimented with three-stage intermediate amplifiers must know that the stabilization problem is not very simple unless the reasons for the trouble are known and the remedies specifically applied to overcome the known sources of instability.

The full voltages were used on plates and screens, in fact, instead of the usual 250 volts and 100 volts, the values were 270 and 120 volts, respectively, just to make the solution a bit more difficult, and to safeguard freedom from oscillation when the method is reproduced in actual 250-volt and 100-volt practice.

The intermediate amplifier, therefore, can be completely stabilized, and it is not necessary to use large condensers, or even very large chokes, in the separate plate legs. The choke coils used were small honeycombs of 800 turns, inductance 10 millihenries, and the capacities recommended are 0.002 mfd. Larger may be used without any disadvantage, smaller ones may be used, but not so small that the frequency of the choking circuit is higher than that of the intermediate amplifier.

100 kc Maximum

The choking frequency should be considerably lower, as the necessity is to create a low-pass filter. If the capacity is as low as 0.00025 mfd., and the choke is 10 mlh., then the natural period is 100 kc, which is low enough for any of the popular intermediate frequencies, that is, for 175 kc or higher. The highest intermediate frequency used in this class is 520 kc, but even that is not so generally encountered, and is rather special to home-constructors of particular types of kit-sets.

It is obvious that the coupling in the screen circuits is not large, as a condenser gets rid of any tendency to back-couple, provided it is large enough, and 1 mfd. is sufficient. Just why any large capacity should be necessary for relatively high frequencies (and the intermediate frequencies are high compared to such a capacity) is not clear, but it is certain enough that the large capacity did the trick, when aided by the other devices.

Special Cases

The use of standard bias of course is consistent with full amplification. The difference between 800 ohms and 300 ohms as biasing resistors means a difference of almost 60 per cent. in the amplification, which is certainly important. Then, too, the second detector may be used in half-wave fashion, if desired, as this affords

twice the voltage that is obtainable from full-wave detectors.

Some incidental aids are necessary, and if a diode detector is used with direct coupling to the triode, as in a 55, a 10 mlh. or higher inductance choke should be connected between the grid of the tube and the terminal of the coil from which pick-off is taken, and a small condenser put from pickoff point to ground, but none across the other end. Sometimes, in extreme instances, the value of this capacity has to be made consistent with stability, and while 50 mmfd. usually will prove sufficient, in some instances the value had to be doubled. This assumes a load resistor of around 0.5 meg. In the actual instance 0.6 meg. were used, because a meter was handy that had 2,000 ohms per volt resistance, and 300-volt scale, so the voltmeter setup could be used as a current meter directly, because of 600,000 ohms series resistance, and indeed as voltmeter, too, directly disclosing the amount of the rectified voltage.

It was found that with a long aerial the loudest local station developed 70 volts at the diode output, which is palpably too much, especially since any diode-biased audio amplifier, as the triode of the 55, stops doing business soon after 30 volts, and all one hears then is a lot of hash. It wouldn't improve the situation one bit if stopping condenser and leak were used, as the distortion would be just as bad, due to action of the tube on the positive portion of its characteristic.

58 as Diode-Biased Tube

The 55, 2B7, 2A6 and other tubes having diode elements are not the most satisfactory as diode-biased when one has a very sensitive set, uses a long aerial and lives near strong stations, because of the high voltage occasionally put into the first audio amplifier. Of course a volume control ahead of the first a-f tube would provide a check, but a tube with an extremely remote cutoff would be preferable, and therefore a 58 could be used separately as the diode-biased tube, and the 55 triode not used at all, or, if used, devoted to i-f amplification, as the third intermediate amplifier, if three stages are to be used. Even at 50 volts negative bias the mutual conductance of the 58 is something, whereas with the other tubes in the same general amplifier class, it is nothing.

It is advisable with all the diode-biased tubes to have a small starting bias, that is, some bias even if there is no signal. Otherwise, there will be grid current at

(Continued on next page)

1-V OR 12Z3 AS RECTIFIER?

Which One Would You Choose and On What Basis?

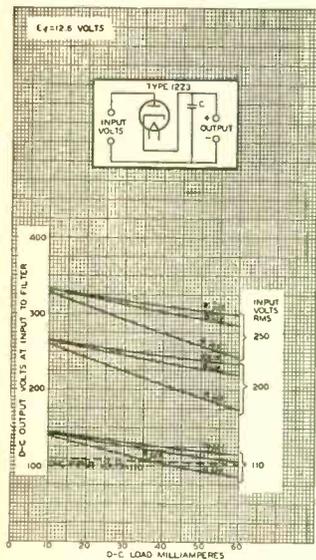


FIG. 1

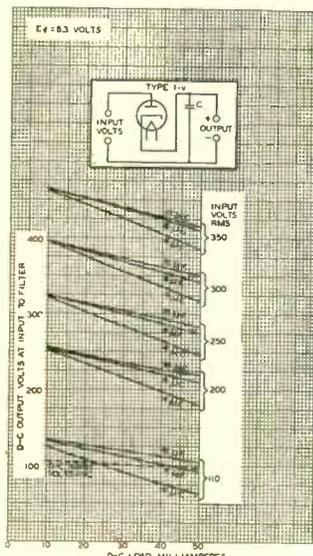


FIG. 2

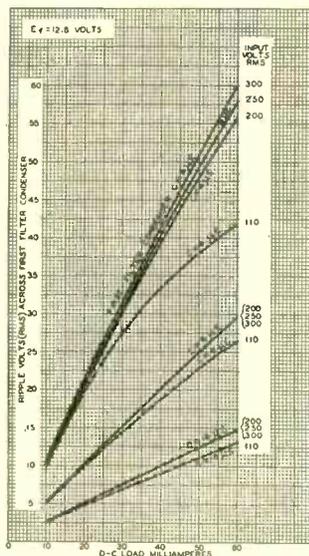


FIG. 3

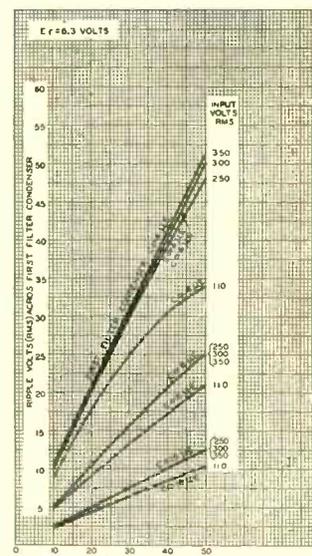


FIG. 4

THE type 1-v and type 12Z3 tubes are half-wave vacuum-type rectifiers having heater voltages of 6.3 and 12.6 volts respectively and heater currents of 0.3 ampere each.

A tabulation of their rated characteristics follows:

	1-v	12Z3
Heater Voltage	6.3	12.6
Heater Current	0.3	0.3
Maximum A-C Plate Voltage (RMS)	350	250
Maximum D-C Output Current	50	60

These two rectifiers may be used in transformerless universal receivers having

series heaters, for which application, the 12Z3 is perhaps the more useful since it has the greater voltage drop across the heater. The 1-v because of its 6.3-volt heater may be used in automobile receivers or in a-c operated receivers employing the 6.3-volt tubes. In general, in making a selection between these two rectifiers, the choice will be determined by the most suitable heater voltage, say RCA Radiotron Company, Inc., and E. T. Cunningham, Inc.

Figs. 1 and 2 showing regulation characteristics of the 12Z3 and 1-v indicate that the 12Z3 has slightly better regulation than the 1-v. The 1-v will supply at 350

volts rms input approximately 400 volts d.c. at 50 milliamperes, and the 12Z3 will supply at 250 volts rms input approximately 300 volts d.c. at 60 milliamperes.

Figs. 3 and 4 show the ripple, or rms voltage developed across the first filter condenser. This is observed to be practically the same for both tubes. From these curves it is apparent that doubling the first filter capacity will halve the ripple voltage developed across the condenser, and that to secure the ripple voltage for any load only one point need be known since these curves are approximately straight lines passing through the origin.

High Gain from I-F Channel

(Continued from preceding page) small signal input or at no signal. The reason for grid current despite a small bias due to signal is that the heater type tubes of the medium amplifier class draw grid current at bias values less than 0.8 volt, so it is well to have 1-volt bias. If the no-signal plate current in the triode of the 55 is 2 ma, for instance, then 500 ohms will afford this single volt, and a bypass condenser across the resistor frees it from a degenerative effect on the circuit.

Time Delay

When the small self-bias is introduced the diode load resistor is returned to grounded B minus, as this is necessary to make the bias effective, for if return were to cathode the drop in the 500 ohms would not be utilized in the grid circuit. With a potential difference of 1 volt between cathode and ground and load resistor returned to ground, the tube naturally will not rectify until the signal is more than 1 volt, that is, until the anode has a positive radio-frequency value of input, measured from B minus.

This situation creates time delay, which means that the detector does not detect until the bias voltage is overcome by the

signal, but the moment it is thus overcome, the bias resistor becomes less and less effective, since the plate current is being cut down.

Some Sacrifice of DX


Nevertheless, though strong signals are hardly affected by the 500 ohms at all, weak ones, below 1 volt, are wiped out, so some distant stations may be sacrificed, but they would not be of the type worth hearing, as less than 1 volt input, with no time delay, results in grid current, hence severe low-note attenuation, or raspiness.

Amplification of different frequencies being relative, the cure for the reduction of low-note intensity on weak signals is to have a volume control that is also a tone control, to cut down the high audio frequency response. This may be accomplished very readily by using a variable condenser across the load resistor. While the volume is not reduced as greatly as with other methods, the low notes continue to be heard well at very small total volume of sound. Some of the more expensive sets have volume controls that also are tone controls working in this direction. The suggested location of the condenser control is such as to reduce

the input to the first audio tube, in line with protecting that tube from danger of overload and hence saturation.

With a minimum of 1 volt required at the detector, if there are two stages of i.f. at 200 gain per stage there is a gain of 40,000 between the modulator output and the detector input. With an r-f stage and good conversion conductance in the mixer (say, 200) there would be a gain of at least 2,000, or now a total of 80,000,000. Remember that audio amplification has not been included, and that has as well to do with sensitivity as has r-f or i-f amplification.

It can be seen, therefore, that large values of voltage can be fed to an output tube, or a pair of output tubes. Since we have found that a three-stage channel can be stabilized, with overall gain of sufficient value to load up a power tube, it is practical to use a diode rectifier and have the power tube direct-coupled by the diode-bias method. This comes within the suggestion of using the triode of the diode tube as last i-f amplifier, but the power tube, due to large plate current, would have to be independently biased, although not necessarily to the full amount usually recommended. The signal would take care of the extra bias.

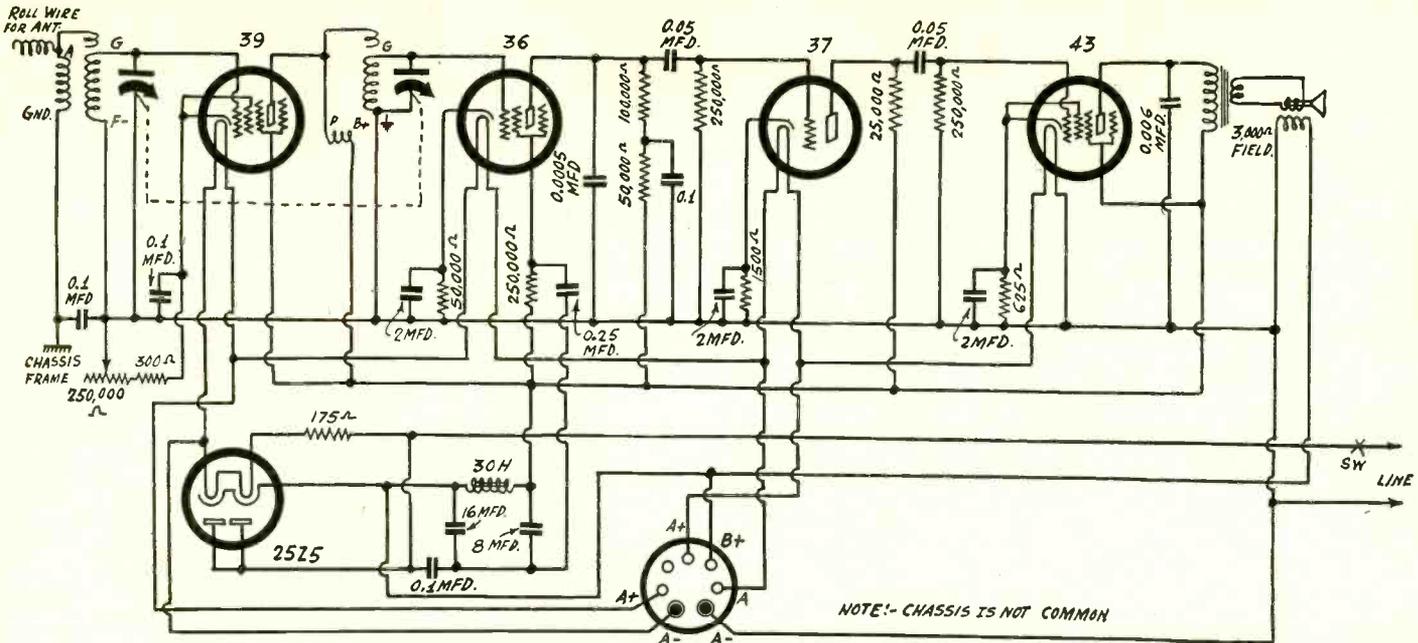

A five-tube universal receiver, using the 25Z5 as rectifier when a-c service is desired, and floating that tube on the line when d.c. is used. A precaution that should be taken is to observe polarity of connection to the outlet, so mark outlet and set plug, and warn the family to plug in the right way.

waves, around 45 centimeters, were received over distances of 160 and 170 miles in his experiments last year and this year, but how he has accomplished it is not definitely known to the science, for he has kept the details secret. It is agreed that ultra waves behave somewhat like light waves, and that is why they are called quasi-optical waves. The general impression has been that their radiation is limited to the horizon distance. This distance is not a fixed quantity but depends on the altitude of the point of radiation. Thus from a high tower the distance to the horizon would be greater than from the ground to the horizon, just as the hypotenuse of a right-angled triangle is always longer than the base. The curvature of the earth is regarded as the deterrent to any considerable distance penetration of ultra waves, but the similarity with light-wave propagation brings up the phenomenon of light "turning a corner," as it were. Einstein in his relativity theory pointed out the effect of magnetism and gravitation on light transmission, and the same condition may cause the ultra waves to go considerably beyond the technical horizon.

Transformerless A-C Set

IS IT PRACTICAL to have a good a-c set, using no transformer, but car type tubes, and heater rectifier? What output tubes would you suggest?—K. C. B.
 Yes, it is entirely practical, for it simply amounts to building a universal type set and not using the d-c option. The rectifier may be the 25Z5, the amplifiers the 78's, with a triode detector push-pull-transformer coupled to a pair of 48 tubes. All heaters, including rectifier, would be in series.

Five-Tube Universal

PLEASE SHOW a design for a five-tube universal receiver, using the 25Z5 rectifier, with limiting resistor value noted (heater circuit).—O. H.
 The circuit diagram is printed herewith and shows choke primaries not inductively related to tuned secondaries, but capacity coupled to the secondaries by the self-capacity of a very small winding (usually one, two or three turns over secondary). Thus one terminal of the small winding goes to plate or antenna, other terminal being left open, so to speak, although due to the condenser effect there exists a closed circuit in reality. The value of the limiting resistor is noted, as requested, and

other values are values constants of other parts are given.

I-F Selectivity

IT HAS BEEN STATED that the doubly-tuned intermediate transformers are more selective than the singly-tuned-circuit intermediate transformers, but I can't understand why this should be, since it has been my experience (consistent with the theory I have studied) that an inevitable band-pass effect or double-hump exists, with the doubly-tuned circuit, and therefore the selectivity should be less. Which is right?—K. R. W.

Either one may be more selective than the other, depending on factors not disclosed. For instance, assume a singly-tuned transformer, untuned winding in the plate grid circuit, tuned winding in the grid circuit. If the coupling is loose the

selectivity will be a certain amount, and may be greater than the selectivity of the doubly-tuned transformer of equal or even looser coupling. However, gain is another consideration, and to keep this high the singly-tuned type uses tight coupling, while the other invariably uses rather loose coupling, and besides affords excellent gain due to both circuits being tuned. When the peaking is accomplished both circuits of the double type transformer are tuned as near as may be to the same frequency, and while the result is not a single frequency, but a narrow band, the attenuation 10 kc off resonance for stated input may be better than in the instance of the singly-tuned transformer. The theory you suggest is of course correct, but the effect of the two types in respect to selectivity depends very much on the degree of coupling.

Join Radio World's

UNIVERSITY CLUB

And Get Free Question and Answer Service for the Coming 52 Weeks.

THIS SERVICE FOR UNIVERSITY SUBSCRIBERS ONLY

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below or write on a separate sheet of paper, if preferred. Your name will be entered on our subscription and University Club lists by special number and you will be apprised of the number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your query. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

NO OTHER PREMIUM GIVEN WITH THIS OFFER:

[In sending in your queries to the University Department, please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for Radio World for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State.....

Station Sparks

By Alice Remsen

AUDITIONS AND CONTRACTS

Auditions and still more auditions for Fall programs! No less than nineteen contralto warblers competed for the Ex-Lax contract. Three made the grade for final auditions—two Columbia artists and one freelance. As might be expected, one of the Columbia staff won out and so you will hear the voice of Gertrude Neissen, combined with the music of Isham Jones' Orchestra and the comedy of Lulu McConnell, when the chocolate laxative reaches the air. . . . At the pre-showing of the Metro-Goldwyn-Mayer film, "Broadway to Hollywood," a great many radio stars were seen. Paul Whiteman was among them; first time I had seen him since the shrinkage; and has he shrunk? Well, rather! He looks great! Ted Husing was popping around all over the place, and so was Nick Kenny, the poetically inclined radio editor of the New York *Daily Mirror*; and music publishers? yes; they were there in droves. The film tells the story of a vaudeville family, from the 1880's to the present day; very true to life. Alice Brady and Frank Morgan give marvelous performances. The National Variety Artists, Inc. attended in a body; marched from the N. V. A. Club to the Capitol Theatre, with flags, torches and a drum corps. Lot of fun; eyes were wet before the end of film. . . . Understand that Rocco Vocco, for many years with the Feist Music, Inc., has left that firm to go with Bobby Crawford and the De Sylva, Brown & Henderson firm; wish him lots of luck! . . . Jack Pearl will retain the role of Baron Munchausen this season; same sponsor, but the show will be for one half hour only, Saturdays 9:00 p. m., WEA; opening program, October 7th. . . .

WHAT THEY'RE DOING—AND WHERE!

American Oil Company (Amco) is the next new show to be auditioned. Style of program not yet decided upon; probably name band and singer, with comedy skit here and there; it will be heard over the Columbia air-waves. . . . J. C. Nugent, the playwright-actor-manager, has a thirty-nine week contract with Dill's Mixture, over NBC, starting some time in October. . . . It is quite likely that you will hear the voice of Patricia, erstwhile vaudeville headliner, on an NBC sustaining series very shortly; her audition was favorable. . . . Peter Dixon has caused considerable talk, and made many literary gents look to their laurels in the field of radio, since his "Children of Israel" skit on Al Jolson's broadcast the other evening, came over the air so well. You did one sweet job Peter! Congrats! . . . Did you hear Roy Atwell on WEA last Friday evening at 9:00. He's as funny as ever. . . . Myrt and Marge are unlucky again. Myrt is in a hospital in Los Angeles after being seriously hurt in an accident; Marge is stranded in the Andes, where she went in search of local color for their skits during the coming season; snowbound, of all things. . . . To those of my readers who have been inquiring as to the whereabouts of Frank Knight, erstwhile Columbia announcer; he has been signed up by WMCA; which reminds me that Al Smith, our own beloved ex-governor of New York, is interested in the management of that station; and the new chain is materializing; within a week or so, WMCA expects to have eleven stations hooked up, reaching as far West as Michigan. . . . Virginia Rae, who was the Olive Palmer on the old Palm-Olive Hour, is scheduled to sing at one of the concerts to be held during September in the

Madison Square Garden, New York. . . . Welcome Lewis is still playing in vaudeville. . . . Jack Arthur made such a hit during his engagement at the old Roxy Theatre, New York recently that a route is being laid out for him immediately at a big figure and Jack will make more money this season than ever before. . . .

ANOTHER NEW CHAIN

Another new local station tie-up has been announced; the Biow Advertising Agency and a noted watch manufacturer have united to establish a local chain, with WODA and WAAM as the nucleus of the hook-up. . . . And now it comes out that Conrad Thibault, the baritone, has so much radio work he is forced to turn down a few programs; he's a lucky man; there are plenty of excellent artists starving to death these days. . . . Muriel Pollock is back from her European trip. . . . Great Moments of History goes into the discard on October 8th and a new show steps into its place, with Ozzie Nelson's Orchestra, singer Harriet Hilliard and comic, Joe Penner. . . . One of my favorite songwriters, Allie Wrubel, has a new song with the Berlin firm which will be heard plenty over the air-waves in the next few weeks; it is titled "And So Good-bye"; think it's a hit. . . . Arthur Pryor, Jr. will be a busy man early in October, when the famous program, "March of Time," goes back on the air; Pryor directs this series, and what a job it is; ten hours a day from Tuesday afternoon, to Friday evening he devotes to its preparation, but the result justifies the time spent and the hard work necessary for its production, for without a doubt it is one of the finest programs ever sent out over the air. . . . A new three-a-week series for housewives made its debut on September 11th, with Mrs. Mary Ellis Ames, widely known economics authority, in charge; each Monday, Wednesday and Friday, 11:30 a. m. EDST; WABC and network; under the title of "Kitchen Close-ups," with Mrs. Ames giving appetizing recipes, authentic tips on kitchen savings and short cuts in the day's routine about the home. . . .

SOME BIG BOYS AND GIRLS

Harriet Lee is back again on WABC, singing with the Happy Bakers program each Monday, Wednesday and Friday; associated with Harriet on the bill are the trio known as Men About Town, although their title in this particular production is Happy Wonder Bakers; they are Phil Duey, Frank Luther and Jack Parker; Joe Green's orchestra supplies the music. . . . The Church of the Air has entered its third year of broadcasting; each Sunday through the Fall and Winter a nation-wide network will carry two half-hour periods devoted to services conducted by outstanding leaders of the Protestant, Catholic and Jewish faiths, morning services at 10:00 o'clock and afternoon services at 1:00, EDST. . . . Singin' Sam (Harry Frankel) is back from his Indiana home; with the other Hoosier member of the Barbasol program, Edwin C. Hill, Sam is warbling over WABC twice weekly, Mr. Hill talking three times weekly and Sam singing the Barbasol theme at each broadcast. . . . Kenneth Roberts, the CBS announcer, motored to Cincinnati for his vacation and spent some time there with his old friend, Paul Stewart, who is working at WLW, announcing, writing, acting and master-of-ceremony-ing. . . . Swift & Company will open their new Fall series some time in October; the program will emanate from Chicago, and Ol-

A THOUGHT FOR THE WEEK

THAT N. R. A. CODE is a great thing for radio, as it is for all other fields of American activities. We're just wondering what effect it will have on the efficiency of some of those sets that don't seem to be willing to do their share in entertaining the family or giving complete satisfaction to the technician. Can a set listen as well as make a noise?

sen and Johnson, those two clever comics, will be starred; band and supporting cast not decided upon at this writing. . . . Those popular and dramatic episodes in the life of "Marie, the Little French Princess," will continue over a Coast-to-Coast network this Fall; Tuesdays, Wednesdays, Thursdays and Fridays, 1:00 p. m. EDST; this program is sponsored by Louis Philippe, Inc., and features Ruth Yorke as the Princess, and James Meighan, nephew of Tom Meighan, as the young American hero. . . .

AND STILL THEY COME

The "Bill and Ginger" program has a contract renewal. Very glad to hear it; these young folk are clever, and the script is fine, written by my old friend from WOR days, Arthur Q. Bryan. . . . Goldy and Dusty are still holding their own on WABC each morning at 9:15. . . . That unique person, known as The Voice of Experience, is back on the air-waves, giving advice to poor human sadly in need of that very useful commodity; he has an evening program now, coast to coast, which started on Tuesday, September 12th, from 8:30 to 8:45 p. m., EDST. . . . Walter Preston is singing just as well as ever; you can hear him in the new NBC Sunday night show, "Light Opera Nights"; this show will bring back memories to you of that fine old show of Philco, when Jessica Dragonette first started to sing over the air; the same theme song, "Memories," will be used; Harold Sanford will conduct, and Henry Neeley, the old stager, will be the musical master of ceremonies. . . . Betty Washington is doing some good work with her combination vocal and instrumental trio over WOR; each Wednesday, 10:15 a. m.; the three girls are Betty Washington, Myrna Westcott and Willa Renard, known as the Rainbow Trio; under the management of Vincent Sorey. . . . Jerry Macey and Ed Smalle, with Roger Bower, have lots of fun during their Household Finance program over WOR each Wednesday at 9:15 p. m.; they dig up the funniest old numbers and put them on with all the trimmings. . . . Sidney Ten Eyck has been retained permanently by WOR and so his engagement with WCAU, Philadelphia has been indefinitely postponed; Sid is looking marvelous, and has developed into a regular Broadway Beau Brummel. . . . Must run along now. See you here next week.

SUBSCRIBE NOW!

RADIO WORLD, 145 West 45th St., New York City. Enclosed please find my remittance for subscription for RADIO WORLD, one copy each week for specified period.

- \$10.00 for two years, 104 issues.
 \$6 for one year, 52 issues.
 \$3 for six months, 26 issues.
 \$1.50 for three months, 13 issues.

\$1.00 extra per year for foreign postage.

- This is a renewal of an existing mail subscription (Check off if true)

Your name

Address

City

TRADIOGRAMS

By J. Murray Barron

The Fansteel Products Co., Inc., of North Chicago, Ill., announces the appointment of Carl G. Howard as sales manager of the battery charger division. Mr. Howard was an early operator of an amateur radio station, from which he branched into the broadcasting and sales activities.

* * *

That the popularity of set construction is widespread was conclusively proved from a survey recently made in connection with the mail order business. A completely wired receiver was offered at a very low price, with little off for the parts to wire the kit yourself, yet the requests for diagrams and parts was so large in proportion that it left no doubt as to whether kits could be sold. In fact, to one who would specialize in kits the competition would be far less than in attempting to sell a wired receiver. With a few good numbers in the kit line, with a

reasonable price and proper publicity, a substantial business could be created. The field is so large that the surface isn't even scratched.

* * *

After the lean years of both storekeeper and the public, now to see the decided change surely makes a fellow feel like living. It's like recovering from a bad illness, or the passing of a terrible storm, with the sun bright after it has been hidden for days. With the aid of the NRA, progress has actually been made and so many of us know dozens who have returned to work, besides other who have had incomes increased and hours shortened, that we just must believe times are on the uptrend.

* * *

RCA Radiotron Co., Inc., manufacturer of radio tubes, has signed the blanket NRA code.

Literature Wanted

Readers desiring radio literature from manufacturers and jobbers should send a request for publication of their name and address. Address Literature Editor, RADIO WORLD, 145 West 45th Street, New York, N. Y.

- Harry E. Coy, County Assessor's Office, Omaha, Nebr.
- Bertram F. Start (Radio Service Engineer), 110 Northumberland Park, Tottenham N. 17, London, England.
- Pope Radio Service, James L. Pope, 1963 East 82nd St., Cleveland, Ohio.
- H. S. Miller, Box 235, Spindale, N. C.
- W. H. Crafts, 3050 West Euclid, Detroit, Mich.
- C. B. Dickey, 1718 Monroe, Toledo, Ohio.
- G. Pasquale, Wellsville S. W. League, 100 Main St., Wellsville, N. Y.
- Aubrey E. Fales, 12 Marvin Ave., Shelby, Ohio.
- Oval L. Robinson, 306 Tippett Ave., Morehead, Ky.
- Harry Boerstler, 2619 Park Ave., Cincinnati, Ohio.
- Joseph Ingentoff, 336 Locust Ave., Port Chester, N. Y.
- M. H. Ryder, 257 So. Palm Drive, Beverly Hills, Calif.
- Fred J. Haskell, 532 Ash St., Waukegan, Ill.
- Gustav Harms, 1318 Addison Street, Chicago, Ill.
- A. E. Philbrick, Roxbury, Conn.
- C. M. Findley, 133 E. State St., Kennett Square, Penna.
- C. A. Kemnitz, Eldorado, Wisc.
- Frs. Coupal, Brebeuf Co., Terrebonne, P. Q., Canada.
- G. B. Martin, 3328 Palmer St., Chicago, Ill.
- John Meehan, 219 Genesee St., Utica, N. Y.
- N. M. Dahlberg, General Merchant, Valemount, B. C., Canada.
- Boris Tolmachoff, "Plum Cottage," Vance Ave., Lavallette, N. J.
- Jack Litwin, 576 James St., N., Hamilton, Ont., Canada.
- D. W. Rosenzweig, 124 Sterling Ave., Lafayette, Louisiana.
- A. N. Horne, care Empire Pipe Line Co., Bartlesville, Okla.
- E. L. Horne, General Radio Repairs, Batesburg, S. C.
- W. M. Horton, Lock Box 462, Douglas, Wyoming.

CORPORATE ACTIVITIES

CORPORATION REPORTS

B. F. Keith Corporation and subsidiary companies —Net loss for quarter ended June 30, 1933, \$187,127, against a net profit of \$43,101 for the quarter ended March 31, 1933. The net loss for the six months ended June 30 was \$144,025, compared with a net income of \$233,424 for the corresponding period of 1932.

BANKRUPTCY PROCEEDINGS

Assignments

Lyman Radio Mfg. Co., Inc., address, 142 Liberty St., New York City, assigned to Fred S. Hare, of 15 Vanderbilt Ave., New York City.

Musique Radio Mfg. Co., Inc., 142 Liberty Street, New York City, also assigned to Fred S. Hare, 15 Vanderbilt Ave., New York City.

Petitions Filed—Against

Plaza Music Co., Inc., radio and music store, of 10 West 20th St., New York City, petition filed by Electric Motive Mfg. Co., for \$624; by William Brand & Co., for \$32; and by Concourse Condenser Co., for \$389.

GOOD RADIO BOOKS

"EXPERIMENTAL RADIO ENGINEERING," by Prof. John H. Morecroft, of the Department of Electrical Engineering, Columbia University. A companion book to the author's "Principles of Radio Communication," but in itself a text on practical radio measurements. Cloth bound, 345 pages 6 x 9, 250 figures.....\$3.54

"FOUNDATIONS OF RADIO," by Rudolph I. Duncan. A treatise for the beginner, setting forth clearly and carefully the electrical phenomena associated with radio. Just the book to give you a firm grip on the subject.....\$2.50

"THE RADIO HANDBOOK," by James A. Moyer and John F. Westrel, both of the Massachusetts Department of Education. Meets the need for a complete digest of authoritative radio data, both theoretical and practical. Flexible binding, 88 pages, 650 illustrations.....\$5.00

Remit with order. We pay transportation.

RADIO WORLD

145 WEST 45th ST., NEW YORK, N. Y.

PIGTAIL RESISTORS

Finest Grade Fixed Resistors Made. RMA Color Coded

1 Watt, 11c Each		COLOR CODE		
RESISTANCE	Meq.	Body	End	Dot
Ohms				
175	0.000175	Brown	Violet	Brown
350	0.00035	Orange	Green	Brown
800	0.0008	Gray	Black	Brown
1,200	0.0012	Brown	Red	Red
2,000	0.002	Red	Black	Red
2,700	0.0027	Red	Violet	Red
3,500	0.0035	Orange	Green	Red
4,200	0.0042	Yellow	Red	Red
5,000	0.005	Red	Black	Red
10,000	0.01	Brown	Black	Orange
20,000	0.02	Red	Black	Orange
25,000	0.025	Red	Green	Orange
50,000	0.05	Green	Black	Orange
60,000	0.06	Blue	Black	Orange
100,000	0.1	Brown	Black	Yellow
250,000	0.25	Red	Green	Yellow
500,000	0.5	Green	Black	Yellow
600,000	0.6	Blue	Black	Yellow
1,500,000	1.5	Brown	Green	Green
2,000,000	2.0	Red	Black	Green
5,000,000	5.0	Green	Black	Green

2 Watts, 16c Each
3,500 0.0035 { Not Color Coded, but
10,000 0.01 { Marked. Size 1 1/2" long
x 3/8" diameter.

3 Watts, 24c Each
2,000 0.002 { Not Color Coded, but
Marked. Size 2 1/2" long
x 1/2" diameter

5 Watts, 42c Each
775 0.00775 { Not Color Coded, but
15,000 0.015 { Marked. Size 2 1/2" long
x 3/8" diameter.

DIRECT RADIO COMPANY

143 WEST 45TH STREET
NEW YORK, N. Y.

WAFER SOCKETS

6/32 mounting holes, 1-11/16 inches apart; central socket hole recommended, 1 3/8 inches, although 1 1/4 inches may be used.

UX, with insulator.....10c
UY, with insulator.....10c
Six-pin, with insulator.....11c
Seven-pin, with insulator.....12c

HENNESSY RADIO PUBS. CORP.

145 WEST 45th STREET, N. Y. CITY

MAGNET WIRE TABLE

Turns Per Inch

B. & S. Gauge	Ω Ohms per 1,000 Feet	Single Silk	Double Silk	Single Cotton	Double Cotton	Enameled	Enameled SS	Enameled DS	Enameled SC	Enameled DC
14	2.525			15.6	13.6	15.2			14.1	13.3
15	3.184	16.9	16.3	16.1	15.1	17.0			15.6	14.8
16	4.016	18.9	18.2	17.9	16.7	19.1	18.4	17.7	17.4	16.3
17	5.064	21.2	20.3	19.9	18.2	21.5	20.5	19.7	19.3	17.9
18	6.385	23.6	22.6	22.1	20.2	23.9	22.8	21.8	21.4	19.7
19	8.051	26.3	25.1	24.4	22.2	26.8	25.4	24.2	23.6	21.5
20	10.15	29.4	27.8	27.0	24.3	30.1	28.4	26.9	26.1	23.6
21	12.80	32.7	30.8	29.8	26.7	33.7	31.6	29.8	28.9	25.9
22	16.14	36.6	34.2	33.0	29.2	37.7	35.0	32.8	31.7	28.1
23	20.36	40.6	37.7	36.2	31.6	42.3	39.0	36.4	34.9	30.6
24	25.67	45.2	41.6	39.8	34.4	47.1	43.1	39.8	38.1	33.1
25	32.37	50.2	45.8	43.6	37.2	52.9	47.8	43.8	42.8	35.8
26	40.81	55.8	50.5	47.8	40.1	59.1	52.9	48.0	45.7	38.6
27	51.47	61.7	55.5	52.0	43.1	66.2	58.4	52.9	49.7	41.4
28	64.90	68.4	60.9	56.8	46.2	74.1	64.5	57.8	54.0	44.4
29	81.83	75.1	67.1	61.3	49.2	83.3	71.4	64.1	58.8	47.6
30	103.20	83.1	73.2	66.5	52.5	92.2	77.8	69.2	63.0	50.3
31	130.10	91.5	79.3	71.9	55.8	103.4	85.6	75.3	68.1	53.5
32	164.10	100.5	86.5	77.2	58.9	115.6	93.8	81.6	73.2	56.6
33	206.90	110.1	93.6	82.8	62.1	129.3	102.7	88.2	78.5	59.7
34	260.90	120.4	101.0	88.4	65.3	144.9	112.3	95.2	84.0	62.8
35	329.00	131.4	108.5	94.3	68.4	162.3	122.5	102.4	89.6	65.9
36	418.80	142.8	116.2	100.0	71.4	181.8	133.3	109.8	95.2	68.9
37	523.10	155.0	124.2	105.8	74.3	202.4	144.1	117.1	100.6	71.7
38	659.60	167.7	132.2	111.6	77.1	227.7	156.4	125.1	106.4	74.6
39	831.80	180.5	140.2	117.2	79.8	252.5	167.7	132.2	111.6	77.1
40	1,049.00	194.5	148.3	122.8	82.3	280.1	179.5	139.4	116.6	79.5

The magnet wire table herewith is useful for determining axial length of coil windings, or, if the length and wire size are known, the number of turns, and indirectly the inductance. Another useful purpose is determination of the approximate amount of wire for current shunts across meters. Moving the decimal point three places to the left, under continuous current ohms per 1,000 feet, gives the resistance per foot. For instance, No. 40 wire has a c-c resistance of a little more than 1 ohm per foot. From the known meter resistance and sensitivity, the required shunt may be calculated, the approximate length of wire obtained from the table. For low resistance shunts do not use the finer wires.

NEW MODEL SHIELDED TEST OSCILLATOR!

Either 50-150 kc Fundamental Model, a-c or battery; or 500 to 1,500 kc Fundamental Model, (broadcast band) a-c or battery, available.

AN improved modulated test oscillator, fundamental frequencies, 50 to 150 kc, enabling lining up of intermediate frequency amplifiers, t-r-f and oscillator circuits, is now ready. It is shielded in a metal box 9 1/2" wide x 6 1/2" deep x 4 1/2" high, with beautiful Japanese finish. The test oscillator is obtainable in two models, one for a-c operation, the other for battery operation. The same cabinet is used for both.

The a-c model not only is shielded but has the line blocked, that is, radio frequencies generated by the oscillator cannot be communicated to the tested set by way of the a-c line. This is a necessary counterpart to shielding, and a special circuit had to be devised to solve the problem.


The modulation in the a-c model is the a-c line frequency, 60 cycles, effected by using the line voltage on the plate of the tube. In the cabinet there is a very high resistance between the shield cabinet and the a-c, a double preventive of line-shorting and application of a-c line voltage to the user.

The oscillator is equipped with an output post. No ground connection need be used, as the circuit is sufficiently grounded through the power transformer capacity to prevent body capacity effects in tuning.

The frequencies are more accurately read than normal use requires, being never more than 2% off, and usually not more than 1% off, many readings being right on the dot (no discernible difference). The frequency stability is of a high order from 100 to 50 kc, and somewhat less from 100 to 150 kc. Zero beats are guaranteed at all frequencies.

The oscillator was designed by Herman Bernard and is manufactured under the supervision of graduates of the Massachusetts Institute of Technology.

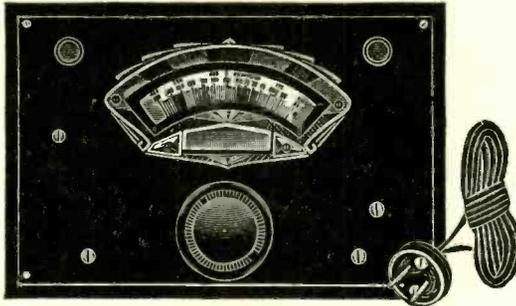Either model FREE with two-year subscription for Radio World (104 issues) \$12.00



The test oscillator has a frequency-calibrated dial, 150 to 50 kc, with 1 kc separation between 50 and 80 kc and 2 kc separation between 80 and 150 kc. Intermediate frequencies are imprinted on the upper tier. Broadcast frequencies are obtainable on tenth harmonics (500 to 1,500 kc).

THE a-c model is completely self-operated and requires a 56 tube. The battery model requires external 22.5-volt small B battery and 1.5-volt dry cell, besides a 230 tube. The use of 1.5 volts instead of 2 volts on the filament increases the plate impedance and the operating stability. The battery model is modulated by a high-pitched note. Zero beats are not obtainable with the battery model.

Directions for Use

Remove the four screws and the slip cover, insert the 56 tube in its socket, restore the cover and screws, connect the a-c attachment plug to the wall socket, and the a-c test oscillator is ready for service.

For testing some particular set, follow the directions given by the designer or manufacturer. In the absence of such directions, use the following method.

Mentally affix a cipher to the registered frequency on the lower tier (so 50 is read as 500, and 150 as 1,500), and set the dial for any desired broadcast frequency. Connect a wire from output post of test oscillator to antenna post of set. Leave aerial on for zero beats, or otherwise. At resonance the hum will be heard. Off resonance it will not be heard. For testing intermediate frequencies, connect the wire to plate of the first detector socket. The first detector tube may be left in place and bared wire pushed into the plate spring. The intermediates then are tuned for strongest hum response. If an output meter is used, tune for greatest needle deflection.

The battery model is connected to voltage sources as marked on oscillator outlets and is used the same way.

RADIO WORLD

145 West 45th St., New York, N. Y.

NO MORE CALCULATING OF INDUCTANCE!


Get your answers accurately from curves in the only book of its kind in the world, "The Inductance Authority," by Edward M. Shepe, B.S., M.E.E. Two charts, one in the book, the other (18x20 inches) as a supplement, relate inductance, capacity and frequency, the large one from ultra to audio frequencies. Thirty-five charts, with 13 curves on each, cover the

numbers of turns and inductive results for solenoids, for 35 wire sizes and insulation types. Wire sizes are Nos. 14, 16, 18, 20, 22, 24, 26, 28, 30, 31 and 32. Insulations: single silk, double silk—single cotton, double cotton and enamel. Form diameters: 3/4, 7/8, 1, 1 1/8, 1 1/4, 1 1/2, 2, 2 1/4, 2 1/2, 2 3/4 and 3 inches. Pages 9x12, printed on one side only. Price, \$2.00 postpaid, including supplement.

RADIO WORLD

145 WEST 45TH ST., NEW YORK CITY

LAPEL MICROPHONE

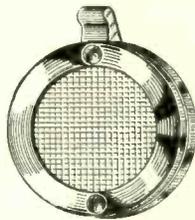

A single-button carbon-granule lapel microphone, impedance 200 ohms, requiring 4.5-volt excitation, of good frequency characteristics, and both handy and inconspicuous. Outside diameter, 1 1/2 inches. The case is chromium-plated brass. The excitation may be provided by introducing the microphone in a cathode circuit carrying around 20 to 25 milliamperes, or a 4.5-volt C biasing battery may be used. Net price, \$2.95.

RELIABLE RADIO COMPANY
145 West 45th Street, New York, N. Y.

COMPLETE YOUR SUMMER FILE OF RADIO WORLD

If you are short of any summer issues of Radio World, send us 15c for each copy or any 8 for \$1.00. Or start your subscription with any date you wish. Radio World, 145 W. 45th St., N. Y. C.

CIRCUITS AND SERVICE DETAILS OF COMMERCIAL RECEIVERS IN ISSUES OF RADIO WORLD AS FOLLOWS:

The Philco Model 15 Superheterodyne, Oct. 29, 1932; Philco's 4-tube Superheterodyne, Dec. 10, 1932; The Philco 37, Dec. 31, 1932; Philco Service Bulletin—No. 146, Models 89 and 19, Jan. 21, 1933; The Model 28, Newest Spartan Set, Nov. 5, 1932; Spartan 14, 14A, and 18, Jan. 7, 1933; The Majestic 324, Nov. 12, 1932; Stromberg-Carlson's Latest Circuits, Nos. 37, 38, 39, 40, and 41 Receivers, Nov. 19, 1932; The Pilot Dragon, Nov. 19, 1932; National Co. Short-Wave Receivers, Dec. 3, 1932; The New Fada Chassis, Dec. 24, 1932; Howard Model M, Jan. 7, 1933; The Comet "Pro," Jan. 14, 1933; Gulbransen Series 322, Jan. 14, 1933; United American Bosch Service Corp. Instructions, Jan. 21, 1933; Crosley Models 132-1 and 141, Jan. 28, 1933; The Colonial C-995, Feb. 11, 1933; Kennedy Model 563, Feb. 11, 1933; U. S. Radio No. 700, Feb. 18, 1933; Bosch 250 and 251, also Clarion Model 300, and Zenith 430 and 440, Feb. 25, 1933. 15c a copy, any 8 issues, \$1.00. Radio World, 145 W. 45th St., New York City.

BOOKS AT A PRICE

"The Superheterodyne," by J. E. Anderson and Herman Bernard. A treatise on the theory and practice of the outstanding circuit of the day. Special problems of superheterodynes treated authoritatively. Per copy. (Cat. AB-3E), postpaid, 50c.
"Foothold on Radio," by Anderson and Bernard. A simple and elementary exposition of how broadcasting is conducted, with some receiver circuits and an explanation of their functioning. (Cat. AB-FE), postpaid, 25c.
HENNESSY RADIO PUBS. CORP.
143 West 45th St. New York City

SOLDERING IRON FREE!

Works on 110-120 volts AC or DC, power, 50 watts. A serviceable iron, with copper tip, 5 ft. cable and male plug. Send \$1.50 for 13 weeks' subscription for Radio World and get these free! Please state if you are renewing existing subscription.

RADIO WORLD

145 West 45th St. N. Y. City

115 DIAGRAMS FREE

115 Circuit Diagrams of Commercial Receivers and Power Supplies supplementing the diagrams in John F. Rider's "Trouble Shooter's Manual." These schematic diagrams of factory-made receivers, giving the manufacturer's name and model number on each diagram, include the MOST IMPORTANT SCREEN GRID RECEIVERS.

The 115 diagrams, each in black and white, on sheets 3 1/2 x 11 inches, punched with three standard holes for loose-leaf binding, constitute a supplement that must be obtained by all possessors of "Trouble Shooter's Manual," to make the manual complete.

Circuits include Bosch 54 D. C. screen grid; Balkite Model F. Crosley 20, 21, 22 screen grid; Eveready series 50 screen grid; Erix 224 A.C. screen grid; Peerless Electrostatic series; Philco 76 screen grid.

Subscribe for Radio World for 8 months at the regular subscription rate of \$1.50, and have these diagrams delivered to you FREE!

Present subscribers may take advantage of this offer. Please put a cross here to expedite extending your expiration date.

Radio World, 145 West 45th St., New York, N. Y.

Vol. III of RIDER'S MANUAL (A New Book)

Just out, John F. Rider's Vol. III Manual weighs nearly 11 lbs. and has 1,100 pages, all diagrams of commercial receivers, etc. (no text). Sets announced up to May 1st, 1933, are included—and complete information on every one, including resistance values. The volume is original and necessary and does not repeat data that are in Vols. I and II.

A Chronological Catalog and Index of all nationally-advertised radio receivers manufactured and sold in the United States between January, 1921 and January, 1933 are contained in Volume III. This list will be of tremendous aid in the identification of receivers for which the model number is not known.

Complete data include schematic wiring diagrams; chassis wiring diagrams; parts layouts; photographic views of chassis; socket layouts; resistor values; condenser values; location of alignment and trimmer condensers; alignment and trimmer adjustment frequencies; intermediate-frequency amplifier peaks; alignment and intermediate-frequency adjustment instructions; color coding; transformer connections; point-to-point data; continuity test data; parts list with prices; special notes.

Complete tabulation of tube data showing electrical characteristics and constants for all of the tubes employed in radio receivers and amplifiers since 1921. Also a table of interchangeable types.

A complete table of I-F. peak frequencies as used in radio receivers. This list augments the information of this type shown upon the diagram pages. Intermediate-frequency amplifier peak information is very important because quite a few of the manufacturers employ more than one figure in their Year's Production. A wrong guess on your part means trouble.

Order Cat. RM-3 @ \$7.50. Remit with order and we pay postage. Order C.O.D. and you pay postage.

Volume I—Order Cat. RM-1 @ \$7.50

Volume II—Order Cat. RM-2 @ \$6.50



Volume III of Rider's Manual has a page sequence in accordance with Vols. I and II, and is not cumulative, or repetitive of the earlier volumes. However, it contains an index for all three volumes.

HENNESSY RADIO PUBLICATIONS CORP.

145 WEST 45th STREET, NEW YORK CITY