

100
JAN. 13
1934



15¢
Per Copy

RADIO

REG. U.S. PAT. OFF.

WORLD

The First and Only National Radio Weekly
616th Consecutive Issue—Twelfth Year


BEST WAY TO USE 2A3 OUTPUT

Permeability Tuning

A Direction Finder

Permeability Tuning
Oscillators

SHORT WAVES ON ONE TUBE

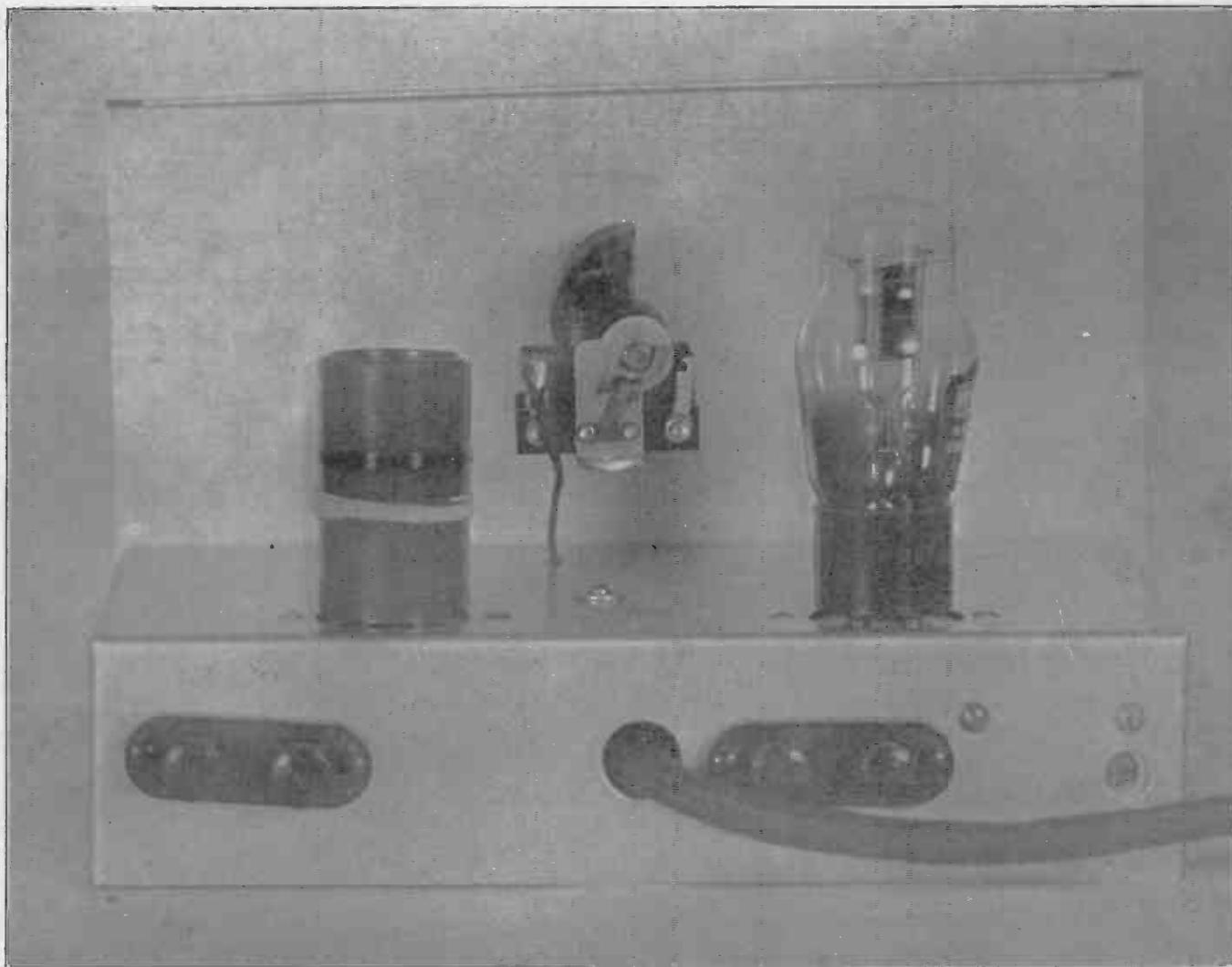

For an earphone listening post or for feeding an audio amplifier this one-tube short-wave set may be used. See page 20.

ROCKET


ONE TUBE BATTERY-OPERATED SHORT-WAVE RECEIVER

Described by Herman Cosman in this issue of RADIO WORLD.
15 to 200 Meters.

ESPECIALLY designed for inexperienced youngsters wishing to explore the short wave spectrum without overstraining their pocketbooks.

The tuning range of this simple set is unbelievably surprising. Many distant stations and domestic short wave stations are audible with a good head-phone and aerial. Requires one 230 screen grid two-volt tube, two 1½-volt dry cells, and one 45-volt "B" battery.

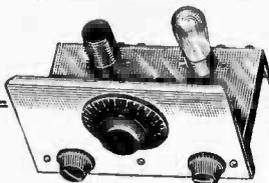The panel of the receiver contains three controls, one for regeneration control, one for tuning and one for filament control. Only a few hours are needed to completely assemble the "Rocket" one and have it receiving with unerring accuracy.



POWERTONE PRODUCTS USE
Hammarlund
PARTS EXCLUSIVELY

Complete kit, including blue-print and four coils ... **\$3.95**
Wired and tested, \$1.00 extra.
Set of batteries for "Rocket" One ... \$1.39
Sylvania 230 tube70

POWERTONE



Universal A.C.-D.C. Short-Wave Receiver

On the first trial, it received Melbourne, Australia — over 11,000 miles from New York City.

Uses 1-43, 1-78 and the new 1-25Z5 tube. Hammarlund parts add to its fine performance. Tunes from 15 to 200 meters.

Kit of parts, 4 coils, cabinet and instructions. **\$8.95**
Wired and Tested.....\$2.00 extra

Handy Servicemen's Manual

Regularly, \$1.00

Full of important information.

25c

Copy FREE with each kit sold.

BAIRD

Universal A.C.-D.C. Short-Wave Converter


Described in RADIO WORLD, Nov. 4, 1933.

Works on all receivers.

Covers the short-wave band from 15 to 200 meters.

Housed in an attractive walnut cabinet. Complete kit of parts, instructions, 4 coils, less tubes.... **\$4.95**

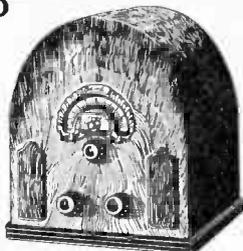Kit of tubes....\$1.25 Cabinet.....\$1.00
Wired and tested.....\$1.50 extra



TRY-MO RADIO CO., INC., Dept. RW, 85 Cortlandt St., New York
Branch: 179 Greenwich Street

METAL-WORKING

LATHE

Precision equipment for the small shop. New designs and manufacturing processes make this amazing bargain possible. Complete metal-working lathe with compound slide-rest, combination face-plate and independent chuck and tail center; 6" swing; 24" length; 30 lbs. Send \$1.00. Balance plus postage C.O.D. Lathe for wood-turning alone, \$4. Attachments for milling, grinding, sanding, saw-table, etc., available at low prices. Order from ad at once and have a complete machine shop. American Machine & Tool Co., 200 Broadway, New York, Dept. R.8.



NEW PRICES

TROUBLE SHOOTER'S MANUAL, Nos. I, II and III

Having assembled 2,000 diagrams of commercial receivers, power amplifiers, converters, etc., in 1,200 pages of Volume No. 1 of his Perpetual Trouble Shooter's Manual, John F. Rider, noted radio engineer, has prepared Volume No. 2 on an even more detailed scale, covering all the latest receivers. Volume No. 2 does not duplicate diagrams in Volume No. 1, but contains only new, additional diagrams, and a new all-inclusive information on the circuits covered.

Volume No. 3 (Recently issued). Order Cat. RM **\$7.50**

Volume No. 2—Perpetual Trouble Shooter's Manual, by John F. Rider, Shipping weight 6 lbs. Order Cat. RM-VT @..... **\$6.50**

Volume No. 1 (8 lbs.). Order Cat. RM-VO @..... **\$7.50**

We pay postage in United States on receipt of purchase price with order. Canadian, Mexican and other foreign remittances must be in funds payable in New York.

RADIO WORLD

145 West 45th Street New York City

BOTH FOR ONE FULL YEAR

RADIO WORLD and "RADIO NEWS"


\$7.00

Canadian and Foreign, \$1.50 extra.

You can obtain the two leading radio technical magazines that cater to experimenters, service men and students, the first national radio weekly and the leading monthly for one year each, at a saving of \$1.50. The regular mail subscription rate for Radio World for one year, a new and fascinating copy each week for 52 weeks, is \$6.00. Send in \$1.00 extra, get "Radio News" also for a year—a new issue each month for twelve months. Total 64 issues for \$7.00.

RADIO WORLD, 145 West 45th Street, New York, N. Y.

WANTED

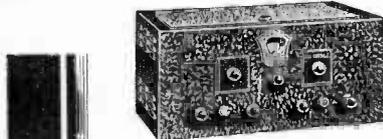


Short Wave Fans, Amateurs and Commercial Operators, who can appreciate the necessity of a genuine T.R.F. Pre-selector Stage, an efficient drawer coil system, a well balanced superhet circuit and many other important developments found only in the new 1934 Custom Built POSTAL INTERNATIONAL. Nine tube superheterodyne 14 to 540 meters—Bandspread—Custom built. Sold direct from our laboratory with a 10-day trial. Foreign loud speaker reception guaranteed or money immediately refunded. Send 3c stamp immediately for circuit diagram, complete illustrated folder and proof of foreign loud speaker reception.

POSTAL RADIO

135-W Liberty St., New York.

ACME TRANSFORMERS

Power Audio Step Down

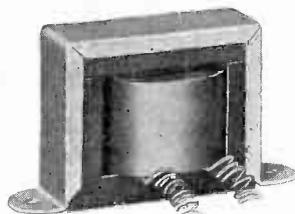

Write for Bulletin 126 describing Power and Audio Transformers. Bulletin 121-A describes Step-Down Transformers.

THE ACME ELECTRIC & MFG. CO.
1445 Hamilton Avenue Cleveland, Ohio

NEW RADIO AMATEURS HANDBOOK, 180,000 words, 207 illustrations, 218 pages (10th edition, issued 1933). Issued by the American Radio Relay League. Price, \$1.00 per copy. Radio World, 145 West 45th Street, New York, N. Y.

Selected Quality Tubes FREE With Subscriptions for Radio World

Here is your opportunity to subscribe for RADIO WORLD and get just the tube or tubes you want, made by a very large, reliable, licensed tube manufacturer; picked tubes you'll appreciate. On this offer you have five days after receipt to put the tube to any logical test, and if not entirely satisfied with its performance, return it for replacement.

For an 8-week subscription (8 issues, one each week), at the regular price, \$1.00, you may select any one of the following tubes as free premium, or more at the same rate (\$2, 16-weeks subscription for two tubes, etc.), from this particular list: 01A, 01AA, IV, 12Z3, 112A, 24A, 26, 27, 30, 31, 35, 36, 37, 38, 39, 45, 47, 51, 56, 71A, 80, 82, 199X.

With a 13-week subscription (13 is-


ues), at the regular price, \$1.50, any one of the following tubes, or more at the same rate, from this particular list (two for a 26-week \$3.00 subscription, three for 39-week \$4.50 subscription, four for 52-weekly, yearly \$6.00 subscription, etc.), 1A6, 5Z3, 2A5, 2A6, 2A7, 2B7, 6A4, 6A7, 6B7, 6F7, 25Z5, 22, 32, 33, 34, 41, 42, 44, 46, 49, 50, 53, 55, 57, 58, 59, 67, 75, 77, 78, 83, 83V, 84, (6Z4), 85, 89, 199V, 483, 485.

For a \$4.00 subscription, 34 weeks (34 issues), one No. 10 tube may be obtained.

You may select any assortment of tubes desired and send in a subscription amount for the total required under the above classifications.

RADIO WORLD, 145 West 45th Street, New York, N. Y.

Power Transformer for a BIG SET

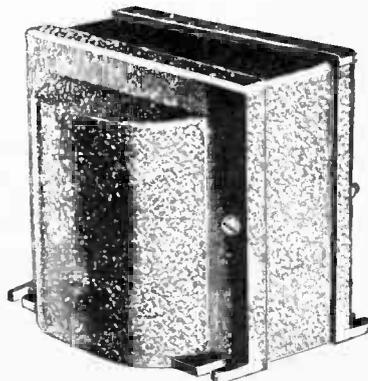

INSTEAD of using undersized, overheating, inefficient power transformers for a big set, why not use a cool-running, efficient transformer and pay the little extra? The Reliable transformer, Model 104-SP, will work an 18-tube set. Provides for C bias supply through 25Z5 rectifier, for quality Class C or Class A.

Primary = 115 v., 60 cycles
Secondary X = 14 amp., 2½ v., ct.
Secondary Y = 6 amp., 2½ v., ct.
Secondary R = 5 v., ct.
Secondary HV = 400-0-400 v., 200 ma.
Secondary Z = 25 v., 0.6 ma.
Lug terminals at bottom
Price, \$3.95
Shipping weight, 13 lbs.
Immediate Delivery

RELIABLE RADIO CO.
145 W. 45th St., New York, N. Y.

**SPECIAL
GIFT
LIST**

Reliable Radio Tips

**Watch for
This Special
Page Weekly**

RELIABLE RADIO RUNS GIANT HOLIDAY SALE!!

FOR A PRACTICAL GIFT SUGGESTS GIVING A
RADIO—LET THE ENTIRE FAMILY ENJOY IT

Reliable Treasure Chest Receiver



A Handsome Four-Tube "Treasure Chest" model receiver which is a splendid piece of furniture and a high quality midget receiver. The beautifully designed cabinet built by craftsmen will satisfy the most critical person. Tubes used: 1-57, 1-58, 1-80 and 1-47 power pentode. Uses a full sized dynamic speaker. Price **\$9.50**
4 tubes\$1.45

4 and 5 Tube A.C. Midgets

A practical gift for the entire family. The most advanced features are embodied in these receivers. Quiet, smooth, distortionless reception.


Four-tube receiver uses 1-57, 1-58, 1-80, and 1-47 pentode; five-tube set uses 1-57, 1-58, 1-80, and 2-47's. Both models use a dynamic speaker especially designed for the output of the pentodes. The receivers are encased in a beautiful hand-rubbed walnut cabinet. Price, 4-tube A. C. receiver **\$9.95**

4 tubes\$1.45
Price, 5-tube A. C. receiver.....\$12.95
5 tubes\$1.95



Four Tube A.C. Short Wave Receiver

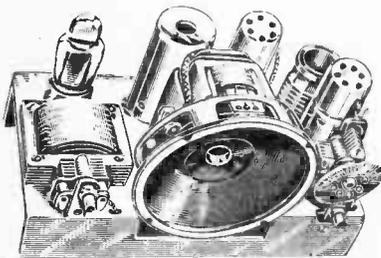COMES MOUNTED INTO A BEAUTIFUL MODERNISTIC CABINET WITH BUILT-IN SPEAKER



Looks like a midget broadcast receiver. Will tune in short wave stations from all parts of the world with ease. Uses four coils to cover the short wave bands from 15 to 200 meters. The built-in power supply is entirely free from hum or disturbing line noises. Uses an ultra-sensitive dynamic speaker to aid in tuning in the weaker signals. Kit of parts.....**\$17.50**

Wired and tested.....\$2.00 extra
Kit of tubes.....\$1.95



Stromberg-Carlson Phonograph Pickup


Makes any radio a modern up-to-date phonograph radio combination. Instruction sheet furnished with the outfit makes it simple to install. Volume control mounted on the pickup enables one to control the volume, without adjusting any part of your receiver. Special Holiday price **\$5.50**

Powertone Sending Key

The most practical gift to one who has just become interested in amateur radio. Widely used as a code practice key. Well balanced and fully adjustable. Price.. **75c**

For The Beginners Rocket Two-Tube Short-Wave Battery Receiver

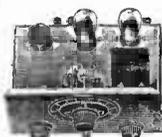Economical! Uses two 2-230 tubes, which assures long battery life. Tunes from 15-200 meters. Pulls in amateurs, police calls, etc. Kit of parts.



\$5.50

Wired..\$2.00 extra Tubes.....\$1.50
Batteries\$2.25

Powertone Two-Tube Battery Receiver

Enclosed in a handsome crystal finished metal cabinet. Can be built by any one. Beautiful full vision modernistic vernier dial aids in logging weaker stations. Will receive all types of short-wave signals, police, amateur, ship-to-shore, airplane, etc.



Kit of parts.....**\$7.95**
Wired..\$2.00 extra Tubes.....\$1.95
Batteries\$2.75

A Power Pack That Converts Any Battery Operated Receiver Into an A.C. Receiver

Will convert any battery receiver to operate on a 110 volt A.C. line. All voltages terminate at binding posts on the chassis. Output; 2½ volts at 10 amperes, 180 volts tapped at 135, 90, and 45. Supplies clear hum-free power regardless of circuit sensitivity. Price including 280 rectifier tube. **\$5.95**

EXTRA! SHORT-WAVE SETS

ACCLAIMED THE IDEAL GIFT FOR RADIO-MINDED FOLKS

If you really want to please your radio-minded son, father, mother, brother, sister or friend this Christmas, give a short wave receiver. On this page are several very fine receivers for both the beginner and the more advanced short wave enthusiast, yet all at extremely low prices.

For A.C. and D.C. Operation


Will work anywhere that 110 volt A.C. or D.C. is available. U. S. amateur reception is assured on loud-speaker by the use of a 43 power tube in the output.

With headphones the entire world is at your finger-tips. Chassis is completely encased in a beautiful crystal finished cabinet. Covers the short wave, band form 15-200 meters. Uses 1-78, 1-25Z5, and 1-43 tube. Price kit **\$8.95**

Wired..\$2.00 extra Tubes.....\$3.25

Beginners Twin Two-Tube Short-Wave Battery Receiver

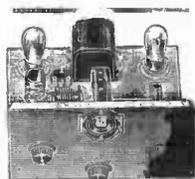A more advanced short-wave receiver for the beginner. Letters from builders verify foreign reception. Uses highest quality parts throughout. Complete with four plug-in coils to cover the entire short-wave band from 15 to 200 meters. Easy to build. Kit of parts.....**\$8.95**



Wired..\$2.00 extra Tubes.....\$1.50
Batteries\$2.50

GIFTS FOR THE SERVICEMAN RESISTORS

Majestic 70 and 90 Condenser Blocks



Replacement condenser blocks for the Majestic 70 and 90 series receivers. Built to the exact specifications of the original. Absolutely guaranteed. Price\$1.35

4 and 8 mfd. Electrolytic Condensers

High quality electrolytic condensers. Can be used as a replacement in many receivers without fear of breakdown. Wet type—thus cannot be injured by slight overload or polarity. Inverted mounting.

4 mfd 35c
8 mfd. 40c

Assortment of 50



An assortment of 50 R.M.A. color coded resistors. Composed of 1/3, 1/2 and 1 watt resistors. All popular sizes are included in the kit ranging from 100 ohms to 10 megohms. **FREE** A beautiful bakelite case—a souvenir of the Chicago Century of Progress Exposition. Price\$2.50

Farrand Inductor Dynamic Speaker Chassis

Not to be confused with the various models now on the market and labeled Farrand Inductors. These models are genuine factory-built Inductors.

Two models are available, a 12" model and a 9" model. Mounting brackets are placed on both models. Price, 9" model.....\$3.95 Price, 12" model.....\$5.95



A Handy Manual Published for SERVICEMEN AND SET DEALERS

Full of information, hookups, charts, trouble shooting hints, etc. Reg. \$1.00 **25c**

RELIABLE RADIO COMPANY, 143 West 45th Street, New York City

ROLAND BURKE HENNESSY
Editor

HERMAN BERNARD
Managing Editor

RADIO WORLD

The First and Only National Radio Weekly
TWELFTH YEAR

J. E. ANDERSON
Technical Editor

J. MURRAY BARRON
Advertising Manager

Vol. XXIV

JANUARY 13th, 1934

No. 18. Whole No. 616

Published Weekly by Hennessy Radio Publications Corporation, 145 West 45th Street, New York, N. Y.

Editorial and Executive Offices: 145 West 45th Street, New York

Telephone: BR-yant 9-0558

OFFICERS: Roland Burke
Hennessy, *President* and
Treasurer.
M. B. Hennessy, *Vice-Presi-*
dent.
Herman Bernard, *Secre-*
tary.

Entered as second-class matter March, 1922, at the Post Office at New York, N. Y., under Act of March 3, 1879. Title registered in U. S. Patent Office. Printed in the United States of America. We do not assume any responsibility for unsolicited manuscripts, photographs, drawings, etc., although we are careful with them.

Price, 15c per Copy; \$6.00
per Year by mail. \$1.00 extra
per year in foreign countries.
Subscribers' change of ad-
dress becomes effective two
weeks after receipt of notice.

A DIRECTION FINDER

BATTERY-OPERATED LOOP RECEIVER THAT ALSO REVEALS THE SENSE—USEFUL ON SMALL BOATS PARTICULARLY

By J. E. Anderson

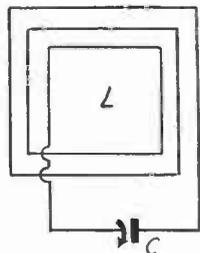


FIG. 1

A loop inductance and a condenser form the essential feature of a radio direction finder.

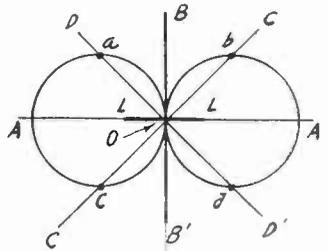


FIG. 2

This diagram shows how a loop receives signals coming from different directions.

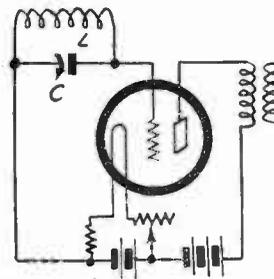


FIG. 3

The loop and condenser are connected to a detector or amplifier to make signals audible.

DIRECTION finding by means of loop antennas is now a well developed art and is used as an aid in navigation both on the sea and in the air. Beacons have been established for ships of both kinds, and both beacons can be used for both air and sea ships. Besides the regular beacons, every broadcast and commercial radio station is a beacon that can be used if its location is known.

All direction finders operate on the principle that a loop antenna will receive signals traveling in the direction of the plane of the loop and that it will not receive signals traveling in the direction at right angles to the plane of the loop. It might be thought at first that the loop is set so that the signals are received loudest, but exactly the opposite is true. When the direction of a beacon is to be determined the loop is turned so that no signal is received because in that manner the most accurate determination is possible.

Principle of Operation

In Fig. 1 we have the essential circuit of a loop antenna. It simply consists of a coil and a tuning condenser, the coil having the

form of a large loop. The loop may be square, circular, octagonal, or any other form. It should be comparatively compact as to the turns, yet the turns should not be too close together for that will increase the distributed capacity. Neither should the axial length of the loop be too large for that increases the capacity of the loop to ground.

In Fig. 2 is shown the reception pattern of the loop antenna, where LL represents the loop seen from above. If the signals travel in the direction AA' or in the opposite direction, the current in the loop is maximum and is proportional to the diameter of either circle. If the signal travels in the direction DD', or in the opposite direction, the current in the loop is proportional to the distance Oa or Od. Likewise, if the signal travels in the direction CC', the current in the loop is proportional to the distance Ob or Oc. If the signal travels along the line BB', which is at right angles to the loop, the current in the loop is zero. It will be noticed that the current changes rapidly from zero to rather large values as the angle changes from the right-angle incidence. It is because of this rapid change

that the loop is turned so that LL is at right angles to the direction of the signal. The source of the signal, of course, is first established when the loop is turned so that the signal is strong, and it is identified by the signal characteristic. If the signal comes from a beacon, that signal has a particular sequence of dots and dashes and time intervals. If the station is a broadcaster it is necessary to wait for the station announcement, unless it is identified by the approximate direction and the frequency on which it is operating.

Errors in the Loop

The pattern shown in Fig. 2 is that for a perfect loop. Ordinarily there is an antenna effect in the loop, due to unsymmetrical distribution of capacity. This will have the effect of distorting the double circle, or figure-eight, pattern. For example signals coming from A' might be weaker than those coming from A. When this is the case signals are not zero along the line BB', nor along any other line. They are not even minimum along the line BB', but the line of minimum strength is bent toward C and D'. If the distortion is great enough,

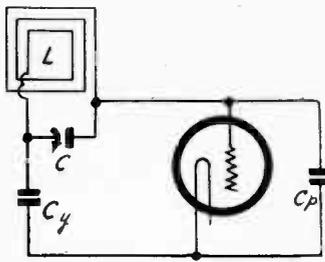


FIG. 4
In this circuit the tuned circuit has been balanced with respect to ground to eliminate direction errors.

there will be only one minimum, or zero, and that will be in the direction A'. To avoid this distortion of the pattern, and hence the error in making direction observations, all distributed capacities must be balanced so that the distributed capacity measured from the center point of the loop, on the upper side, is exactly the same in both directions.

The question of unsymmetry enters when the loop is connected to a detector circuit. In Fig. 3 we have a typical circuit such as is used. L is the loop and C the tuning condenser. Now one side of the loop and the condenser is connected to the grid while the other side is connected to the filament circuit. Naturally, the unbalance is very great, for one side of the circuit is virtually grounded while the other is at high potential. There would be no direction from which the signal received is zero with this circuit. One method used to balance the loop with respect to ground is shown in Fig. 4. A small condenser C_g is connected between the side of the condenser that was grounded and the filament and a similar condenser C_p is connected from the grid to the filament. The filament may now be grounded and by adjusting the two balancing condensers it is possible to effect symmetry. When the two balancing condensers have the proper values the midpoint of the loop is at ground potential and so is the midpoint of condenser C. In other words, there is just as much capacity to ground on one side of the tuned circuit as on the other. Now the reception pattern is that shown in Fig. 2.

Detection of Signals

It will be noticed that C_g is in effect the grid stopping condenser, and therefore a high resistance leak can be connected across it to convert the tube into a detector. In order not to upset the symmetry by this resistance, a similar resistance could be connected across C_p, although the internal grid resistance of the tube would serve this purpose. Hence it would be necessary only to adjust the resistance across C_g to be equal to the internal resistance of the grid circuit when signals are practically zero. The arrangement has the disadvantage that the rotor side of the variable condenser is at a high potential. This, of course, does not matter when the circuit is permanently tuned to the beacon stations, but it would be troublesome when the circuit must be tuned to different frequencies.

Using Balanced Detector

In Fig. 5 is shown one way of balancing the loop and tuning condenser by the use of a symmetrical tube. A suitable tube for this purpose is the Wunderlich, which has two grids, one plate and one cathode. Another is the 53, which consists of two equal triodes in one envelope. When Wunderlich tube is used the balance cannot be extended to the plate circuit, but this is of little importance if the tube is used as a full wave detector. If the 53 is used, on the other hand, the balance can be extended to the plate circuit and the two tubes would be used as a push-pull amplifier. Detection could be effected in another tube.

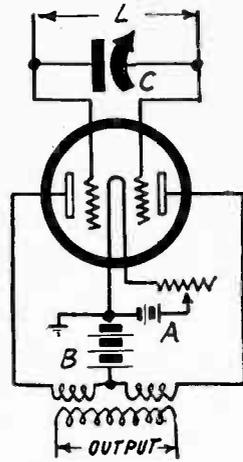


FIG. 5
Here balance is obtained by using a 53 in push-pull.

Grounding of the filament is possible when the symmetrical tube is used, but grounding of the tuning condenser is still to be desired. By making C in two equal units and connecting these in series it is possible to ground the common rotor and still leave the circuit balanced.

The Sense Finder

By referring to Fig. 2 we note that it is impossible to tell whether the signals come from the direction B or that of B'. Obviously a direction finder that cannot tell the difference between north and south, or east and west, is of little use. There must be some way of telling the difference between the two possible directions of a station. A device which does that is called a sense finder. It consists of a means for introducing unbalance. Suppose, for example, that the station lies in the direction A. The circuit will give maximum response when the loop is turned as in the figure. Now if unbalance is introduced, the signal will either increase or decrease, because an additional voltage is either added to the signal or subtracted from it. If there is an increase, it is known that the station lies in the direction A; if there is a decrease, it is known that it lies in the direction A'. Hence by turning the loop at right angles to its position in the figure, zero reception will result provided the circuit has been restored to balance. But now it is definitely known that the station is not in the direction A'.

Fig. 6 shows a balanced circuit with a provision for introducing unbalance when required. The balancing is done by condensers C₁ and C₂ as in the other cases. L₃ is a coil in an antenna of the ordinary

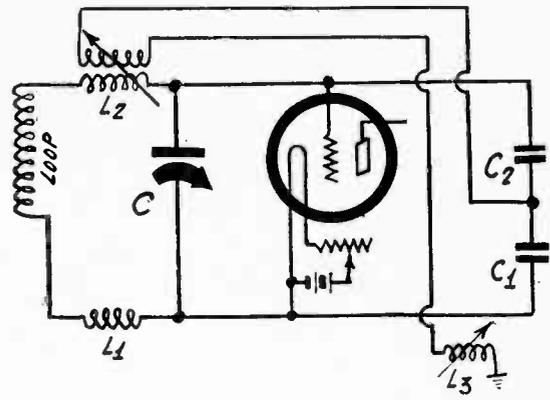


FIG. 6
A sense finder has been inserted in this directional receiver without upsetting the balance.

type. This picks up a signal and part of it is introduced into the tuned circuit by the variable coupler the secondary of which is L₂. Since the coil L₂ would upset the balance, a coil L₁ of equal inductance is put on the opposite side of the circuit.

This arrangement, perhaps, is superior to any of the others for it not only provides a sense finder but it also provides a means of locating the direction of a station without turning the loop to maximum. If L₃ and the coupling between L₂ and its primary are adjusted so that the voltage introduced into the tuned circuit by way of L₂ is exactly equal to that picked up by the loop, the signal will be zero in one direction, A' in Fig. 2, and it will be very large in the opposite direction, A in Fig. 2. In directions B and B' it will be equal to the voltage introduced by either the loop or the antenna. In direction A it will be equal to the sum of these two. Hence if the loop is turned so that no signal is received, it is known definitely that the station lies in that direction. The loop, of course, would be marked so that no ambiguity would result.

Circuit of High Sensitivity

Fig. 7 shows a complete circuit for direction finding. L is the loop, which is tuned by two equal 350 mmfd. condensers, the junction of which is grounded. The two equal 30 tubes are biased by a small battery the voltage of which is chosen for amplification rather than detection. The output of each tube is delivered to another tuned circuit having a 350 mmfd. tuning condenser. The primary of the tuned transformer is tapped at the midpoint so that the first stage is push-pull. Symmetry of
(Continued on next page)

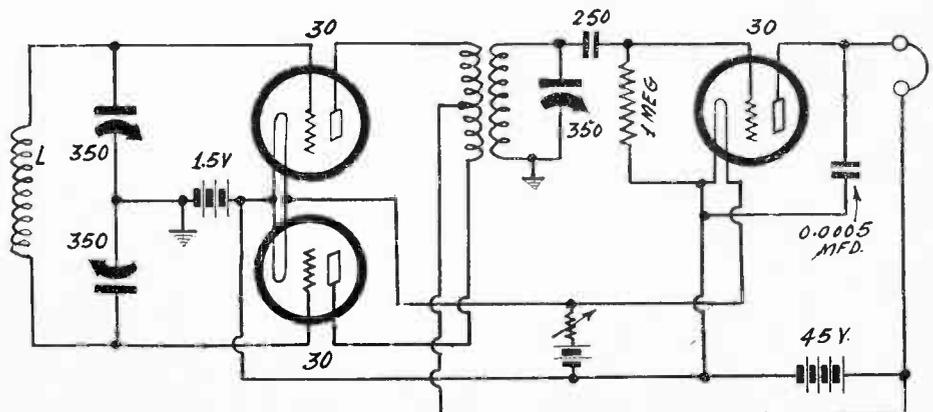


FIG. 7
A complete receiver for direction finding. The tuned circuit is balanced, the amplifier push-pull, and the detector is conventional. A three gang condenser will serve for tuning.

be 5 millihenries. Naturally, this would be a honeycomb coil, and the number of turns ordinarily would be around 700. The tickler would have about half that number of turns, or fewer, and placed far enough away from the secondary so that the oscillation does not cause the neon lamp to glow with great brightness or get unduly hot.

Inductance Selection

When the oscillator is calibrated for the fundamental, which may be done by striking heats with broadcasting stations, harmonics may be used for multiples of the fundamental, and the multiplication done mentally from the scale data.

The secondary inductance has to be selected on the basis of the maximum capacity and the lowest frequency, and then the minor adjustment for the high-frequency and is made by means of the usual trimmer across the variable condenser. In the diagram, Fig. 1, C is the tuning condenser, Cf is the fixed capacity, and Ct is the trimmer. Depending on the value of Ct, which is usually around 35 mmfd. at maximum, Cf may be less than 100 mmfd. by about that amount.

The Universal Model

In the universal model, meaning that the oscillator works on 90-120 volts a.c., d.c. or batteries, the 1A6 tube is used, and external ground is connected only to the metal box and to the slider of the attenuator or volume control.

It is important to observe this precaution against grounding the oscillator circuit directly, otherwise a short of the line may result. To complete the metal surrounding, since the panel will be bakelite or other insulator, a backing of copper foil is cemented to the panel, and oversized holes drilled to pass condenser frame and output post, but a conductive contact with the foil established at one of the corners of the metal box where a screw is to be inserted. The box should have inside corner brackets, and if these are painted or otherwise treated, scrape off the surface and apply some solder. Then the friction contact will be sufficient.

Leak and Condenser

The 1A6 diagram shows the proper way to drop the line voltage for filament supply, so that the difference voltage will be between plate and negative filament, including also the drop in the filament. The filament potential designations apply only to the polarity of the voltage, as this is alternating when a.c. is used, although on d.c., from line or batteries, the polarities are significant of application voltages.

The same values of grid leak and condenser are used, also the same value of stopping condenser in the output. The real reason for the high leak is to insure modulation by grid blocking when d.c. is used in line or battery form, hence 5 to 7 meg. should be used for the universal model, al-

UNIVERSAL MODEL, FOR 90-120 V, A-C OR D-C LINE OR B BATTERIES

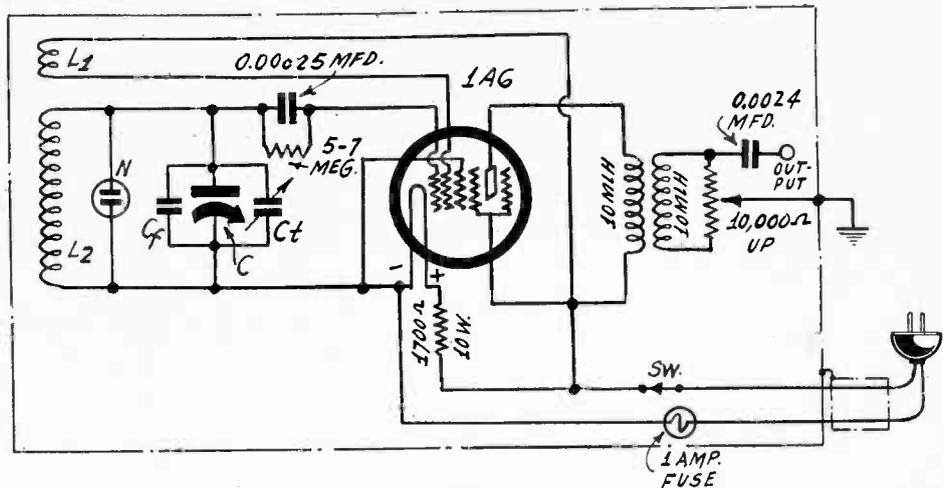


FIG. 2

A universal model test oscillator, using a 1A6 tube. Whether a.c. or d.c. is used from the line, 90 to 120 volts, the same service prevails. While on a.c. the hum is stronger as modulation, nevertheless there is grid-blocking modulation as well, as this must be included so there will be modulation on d-c uses (line or B batteries). Care must be exercised not to connect the oscillator circuit proper to the grounded metal box in this model.

LIST OF PARTS

Coils

- One oscillation transformer, secondary (L2) 5 millihenries inductance, primary (L1) 1 millihenry inductance. Coupling between windings loose enough to avoid overheating of the neon lamp (N).
- One output transformer, consisting of two 10-millihenry r-f chokes closely coupled.

Condensers

- One 0.00035 mfd. tuning condenser (C) with trimmer (Ct) built in.
- One fixed condenser (Cf), so that it plus Ct equal about 100 mmfd.
- One 0.00025 mfd. mica grid condenser (paper condensers unsatisfactory)
- One 0.0024 mfd. mica fixed condenser (smaller capacity may be used)

Resistors

- One potentiometer, 10,000 ohms up, with a-c switch attached

- One 5 to 7-meg. grid leak
- One 1,700-ohm, 10-watt resistor

Other Requirements

- One metal box, 5x5x3 inches
- One insulated front panel to fit
- One copper foil sheet, size of panel
- Four selftapping corner screws for box
- One shielded a-c cable and plug
- One 1-ampere fuse and holder
- One neon lamp, 110-volt type, with candleabra base (may be used as pilot lamp for transparent dial scale).
- One dial and escutcheon
- Two knobs
- One 6-hole socket
- One 1A6 tube
- Two binding posts, one conductive for ground, other insulated for output
- Shielded output lead and shielded ground lead

though smaller grid condenser and smaller resistor may be used on the a-c model, Fig. 1. The stopping condenser, 0.0024 mmfd., is rather large, to insure sufficient coupling at intermediate frequencies, but if the coupling proves ample, it is well to use a smaller capacity here, in either model,

in fact as small as gives satisfactory intermediate-frequency coupling.

The same coil is used in both models, the same attenuator, 10,000 ohms up, without limit, and the same test of steadiness of amplitude is applied by use of the neon lamp (N), as previously outlined.

Four Cathode Ray Tubes, Rectifier and Sweep Oscillator Announced

RCA Radiotron Co., Inc., announced four cathode-ray oscillograph tubes, the 903, 904, 905 and 906, also a high-voltage half-wave rectifier, the 878, and a gas triode, the 885. The rectifier supplies the necessary high voltage for the oscillograph tubes and the gas triode is a saw-tooth-wave sweep oscillator.

The following are data on the cathode-ray tubes:

The 903 has a 9-inch diameter fluorescent viewing screen, designed for use with magnetic deflection control, and has an indirectly-heated cathode. Maximum voltage, 7,000 volts. Six-hole socket required.

The 904 has a 5-inch fluorescent viewing screen and permits both electrostatic and electromagnetic deflection control. Maximum voltage, 4,600 volts. Six-hole socket required.


The 905 has a 5-inch diameter screen with two sets of plates for deflection control. Maximum voltage, 2,000 volts. Five-hole socket required.

The 906 has a 3-inch screen, with two sets of plates for deflection. Maximum voltage, 1,000 volts. Medium seven-hole socket required.

The indirect heater takes 2.5 volts on all the cathode-ray tubes.

As for the rectifier 878, the maximum a-c plate voltage is 7,100 volts at maximum 5 ma continuous. Filament 2.5 volts a-c., at 5 amps. Four-hole socket required.

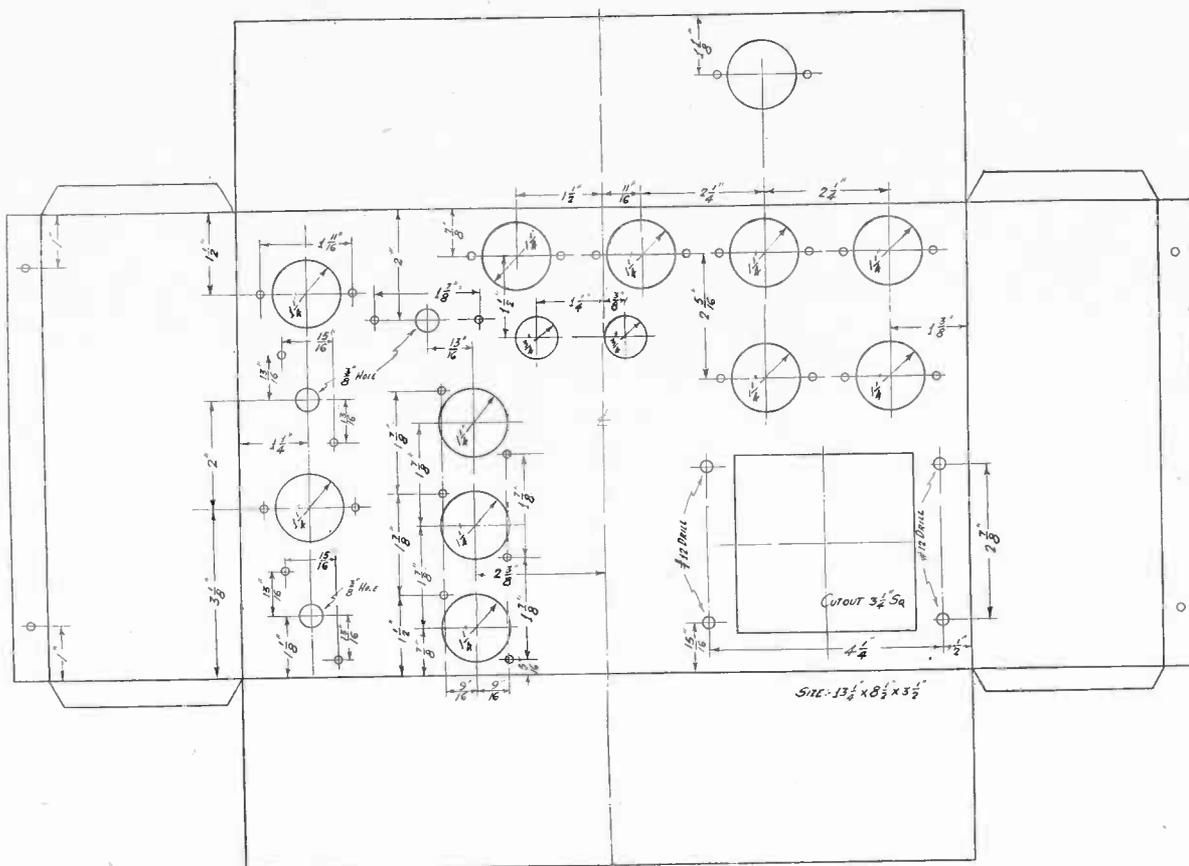The 885 triode, 2.5-volt heater, 200 to 300 volts maximum, is intended for developing a-c voltages at oscillation frequencies for causing a beam to move horizontally. Another would be required if perpendicular sweeping is to be additional, as in television scanning, where the horizontal frequency may be 120 (lines) and the perpendicular frequency (frames) 24. A five-hole socket is required.



Chassis layout for a 25-watt receiver in a small space. The central blank space, forward, is for the tuning condenser. To the left are three holes in a row for the two r-f and mixer sockets, back to front, in that order. At lower left corner, chassis top, goes the first intermediate transformer, behind that the first i-f tube, second i-f transformer next, and second i-f tube at left rear. To right of that tube, third i-f transformer, and next, at rear, hole for the 55 second detector. Just in front the two smaller holes are for the 8 mfd. electrolytic condensers. The rest of the tubes at rear are, left to right, 59, 2A3 and 2A3. The 5Z3 rectifier goes at right behind the power transformer cutout, and the 25Z5 rectifier to left of the other rectifier.

the r-f trimmer adjustment for the broadcast band has to be retained for the police band.

In other words, the oscillator is adjusted backwards, first the trimmer for 5,000 kc. For the broadcast band, since this trimmer remains in service as already established, the extra capacity, estimated at 8 mmfd., is added, and left across the larger secondary.

Padding condensers are required for both bands. For broadcast frequencies the computed capacity, Cp1, is 508.4 mmfd., while for the police band the computed capacity, Cp2, is 756 mmfd. Due to variations in trimmer settings the computed values are not always satisfactory in practice, but the actual values will be close to those stated, for the inductances wound as directed.

Would Tune Too High

The virtual equality of the capacities (omitting padding henceforth), and the room provided to the right of the tuning condenser's center under the chassis, allow for coils for covering higher frequencies.

With a ratio of 3.16, starting at 5,000 kc, the next band would bring you to 15,800 kc and the next band to from 15,000 to 46,400 kc, a region in which there would be little response, because the higher frequencies are too high for this type of construction (around 6 meters).

Less Than Full Condenser

The method of getting around the crowding at the high frequencies, for the fourth or last coil, or even for the third coil, would be to select the inductance for use of less than the full condenser capacity, say, 250 mmfd. for the third coil, and 100 mmfd. for the last coil. The dial would not be turned to higher capacities in these instances. Thus the frequency ratios would be, for the third coil, 2.74 and for the last coil 1.843. The frequency ranges under this system then would be 5,000 to 13,700 kc, and 13,000 to 24,959 kc, or to around 12 meters, a more likely stopping place, as some results can be expected around highest frequency. It is a fact, however, that for the smallest coil

the sensitivity drop will be large, compared to all other coils.

25 Watts Output

It is not the present intention to go beyond the broadcast band, but to ascertain the inductance for any band, take the capacity ratio and divide it into the previous greater inductance (for the lower frequency band). Thus since 20 microhenries are used for the police band, the capacity ratio being 7.5 for the next band, the third coil under the special system just detailed would require an inductance of 2.66 microhenries, and the last coil, capacity ratio here 3.4, an inductance of 0.8 microhenry.

The circuit has the same C supply as outlined last week, and the bias may be somewhat more than 100 volts for class B operation (25 watts) or between 50 and 60 volts for Class A (15 watts). This is possible simply by bias adjustment and without any other changes in the circuit, although for Class A operation, the speaker field may carry the power tubes' plate current, and the 30-henry choke be omitted.

SET'S LEAK-CONDENSER-DETECTOR SERVES AS A FREQUENCY DOUBLER

When one wants to build an oscillator and calibrate it against broadcasting stations he may do so readily if he finds one position on each coil that represents a known oscillator frequency. Since harmonics would be used, the problem is to ascertain which harmonic is which. If the plug-in type coils are used with specified capacities the coil manufac-

turer's frequency-range statement may be accepted for a low-frequency determination on one coil. If it is possible to build two oscillators, one as frequency-doubler, with a station as frequency standard, the work really may be expedited. However, all sets with grid-leak-condenser detection, including t-r-f sets, and supers with such detection in

modulator or demodulator or both, are frequency doublers and their harmonics beat with fundamentals, as well as with harmonics, of the test oscillator to be calibrated. Police signals are a good reference for frequency-determination and besides are frequently heard at night, though not so active during the day.

HOW TO USE 2A3'S T PUSH-PULL CIRCUIT FAV 150-MA FUSE IN COM

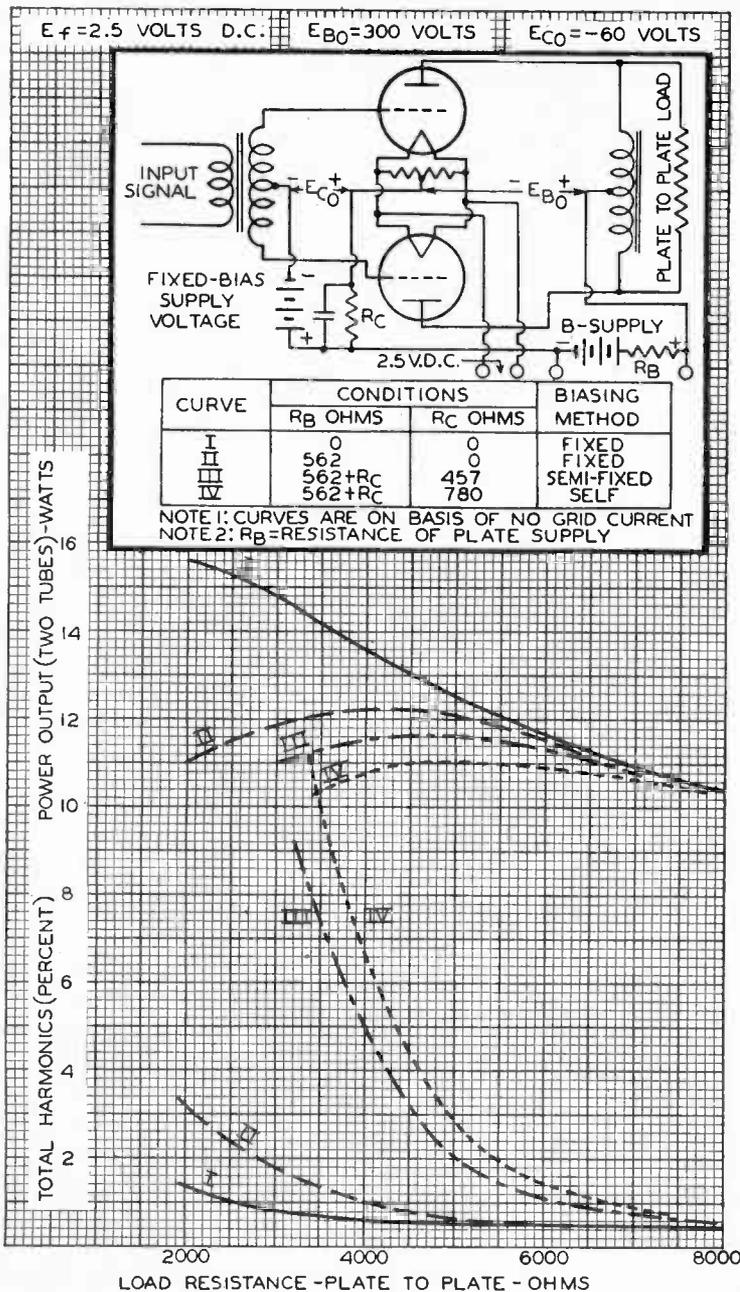


Fig. 1, top left, shows a 56 driving a 2A3 push-pull output, at 60.2 volts negative bias for d.c. on F1 and F2. If a.c. is used the bias should be 62 volts, i. e., L2 slightly higher than 430 ohms d-c resistance. Fig. 2, lower left, shows a 26 used as C bias supply rectifier, when a fuse of 150 ma rating is included.

THE introduction of the 2A3 made possible the design of audio-frequency output systems of unusual power-handling ability and exceptional tone quality. The unique design features incorporated in the 2A3 make possible very high power output at relatively low plate voltages.

In determining the performance obtainable from two 2A3's in Class A push-pull and in selecting output transformer constants, a graphical method of solution can be used. For a general consideration of the method for determining the performance of push-pull audio amplifiers by graphical means, see the paper entitled

"Graphical Determination of Performance of Push-Pull Audio Amplifiers" by B. J. Thompson of our Research and Development Laboratory, say RCA Radiotron Co., Inc., and E. T. Cunningham, Inc. This paper appeared in "Proceedings" of the Institute of Radio Engineers for April, 1933.

Strictly speaking, no type of output tube has absolutely linear characteristics. Consequently, a small amount of rectification of the signal voltage usually occurs. The non-linearity of characteristics is therefore responsible for the distortion produced by the tube.

When two tubes are operated in a Class A push-pull circuit, the non-linear sections of their characteristics are made to complement each other to give a substantially linear overall characteristic. This method produces an output free from second harmonic distortion. For this reason it is possible to use a higher bias voltage for push-pull operation than is usually employed for single-tube operation. An increased bias voltage lowers the internal dissipation of the tube and permits the use of higher plate voltages. Higher plate voltages, in turn, make possible higher power output.

40 Ma Current Limit

In order to obtain the higher power output of which the 2A3 is capable, two of these tubes are operated in push-pull under bias-voltage conditions which cause considerable rectification in each tube. Additional plate current, then, is drawn because of rectification, but this increased plate current is useful in obtaining higher power outputs. Under normal recommended operating conditions in a push-pull amplifier, where a plate-supply voltage of very good regulation and a fixed-bias supply voltage are used, the plate current is not cut off during any fraction of the cycle. Consequently, even though the recommended operating conditions specify over-bias grid voltage, this system may be operated as a strictly Class A amplifier.

2A3's should not be operated with more than 300 volts on the plate. The grid-bias voltage should be minus 62 volts when operated from an a-c filament supply and minus 60 volts when operated from a d-c supply. The corresponding static plate current for an average 2A3 is 40 milliamperes. This voltage and current rating for no signal input should not be exceeded for best results.

Fixed Bias and Over-Bias

Fig. 2 shows a circuit arrangement for the 2A3 in which the bias voltage is obtained from a small triode used as a rectifier. This triode must be a type whose cathode comes to an operating temperature quickly in order that bias will be available to prevent abnormal plate current in the 2A3's. Either a type 26 or 01-A is suitable for use as the bias rectifier.

With the circuit of Fig. 1, changes in the d-c plate current of the 2A3 produce some change in bias. With the circuit of

TO BEST ADVANTAGE LOADED WITH FIXED BIAS; COMMON B RETURN LEAD

Fig. 2, the bias voltage is substantially independent of the plate current of the 2A3's.

The ideal case of fixed-bias operation with a fixed plate-voltage supply gives results as shown by the curves marked (I) in Fig. 3. The curves (II) show the performance with fixed bias but with a plate-supply source having an equivalent internal resistance of 562 ohms. This represents the condition for the circuit of Fig. 2 when a 5Z3 with suitable transformer is used. The performance with an 83 type is intermediate between the values of curves I and II of Fig. 3.

The plate circuits of the 2A3's should be fused in the center-tap lead of the output transformer. This is especially important when fixed bias is used. Should the bias-voltage rectifier tube be removed or damaged, the bias on the 2A3's becomes zero. In that event, unless a fuse is provided for protection, excessive plate current can flow and damage the receiver. A suitable fuse is one similar to the small glass-enclosed type often used to fuse the power-supply line in radio sets and rated at 150 milliamperes.

Self-Bias and Over-Bias Voltage


When 2A3's are operated in a push-pull circuit and are self-biased, a rise in d-c plate current with increasing signal voltages increases the voltage drop across the self-biasing resistor and raises the bias on the tubes. Thus, the operating point on the plate family of the characteristic curves is shifted downward. This shift tends to increase distortion and to lower the power output. Under these conditions, operation intermediate to Class A and Class B is usually obtained at full output since the plate current is cut off for an appreciable fraction of the operating cycle.

When self-biasing circuits are used for the 2A3, it is necessary, therefore, to employ a higher value of plate-load resistance than is used with a fixed or semi-fixed bias arrangement. The purpose of this high resistance is to lessen plate-current swings, limit distortion, and prevent plate-current cut-off at negative signal swings.

Performance of a 2A3 amplifier for self-bias operation (self-bias resistance of 780 ohms) and an assumed internal resistance of the plate-voltage supply of 562 ohms is shown as Curve IV in Fig. 3. A comparison with Curve I, which represents the ideal case of fixed supply voltages, shows the necessity of using a high plate load, as previously stated, in order to obtain high power output and low distortion. Increasing the internal resistance of the plate-voltage supply to the somewhat higher values often used commercially will not materially change results from the values of Curve IV.

Steady Bias Approved

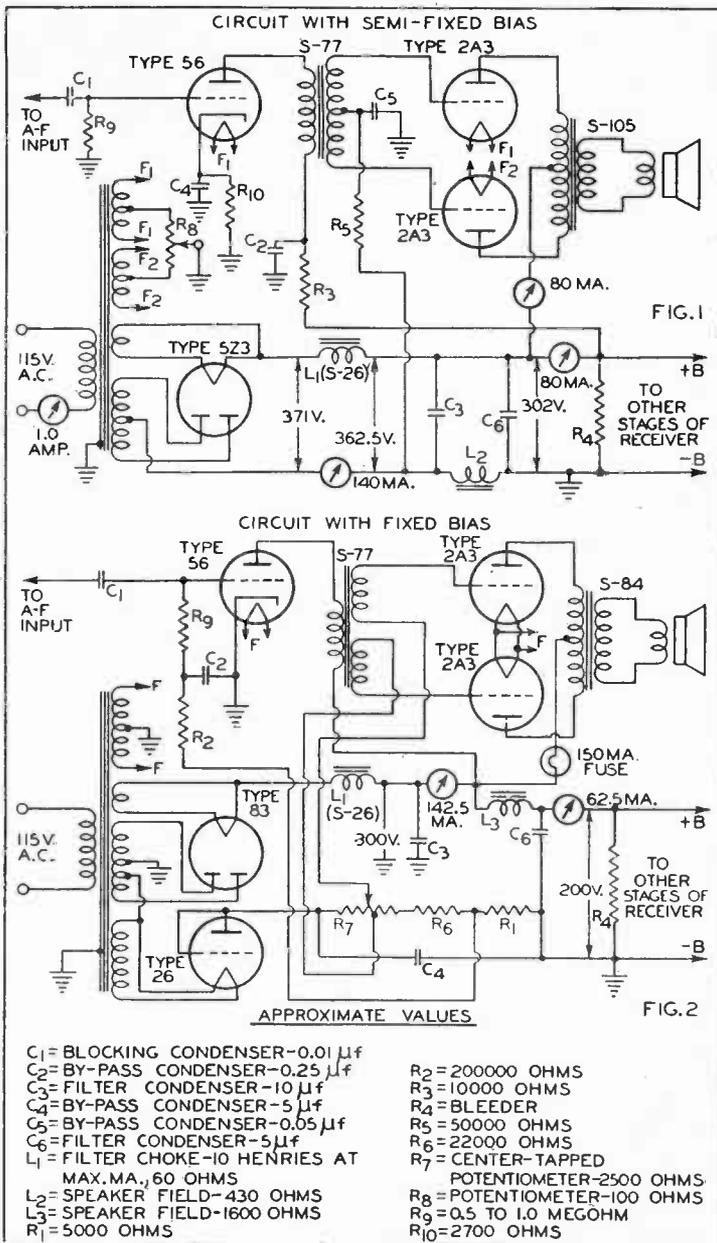The circuit diagram in Fig. 3 shows the equivalent voltage-supply circuit for the plate and grid-voltage supply. The plate and bias voltages on the power tube at zero-input signal are 300 and minus 60 volts, respectively. (For a-c filament



The operating characteristics are shown in Fig. 3, with conditions stated and curves given below.

supply, grid-bias voltage is minus 62 volts.)

Curves I to IV show the performance of the amplifier for four combinations of the internal resistance values of the plate-voltage and grid-voltage supply. The plate- and grid-supply voltages are adjusted to values given above. These curves show that it is desirable to use a bias arrangement which will not give bias-voltage fluctuations when the d-c plate current changes. Semi-fixed and fixed-bias arrangements allow higher power output levels to be maintained with a high degree of fidelity.

Balancing of 2A3 Circuits

It may be advisable to provide some means for balancing the plate currents of the 2A3 tubes, as this has the effect of balancing out hum voltages present in the plate-supply voltage.

Two methods of accomplishing this are shown in the circuit diagrams. In Fig. 1, a small potentiometer (R₈) is connected between the center taps of the filament windings to permit an adjustment of bias voltage.

Both the circuits of Fig. 1 and Fig. 2
(Continued on page 22)

PERMEABILITY TUNING

COMPRESSED IRON DUST CORE OF PLUNGER TYPE AFFORDS WIDE FREQUENCY RANGE

By Einar Andrews

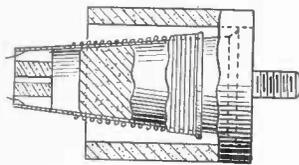


FIG. 1

This shows the construction of an iron dust core radio frequency coil, the inductance of which is varied by permeability.

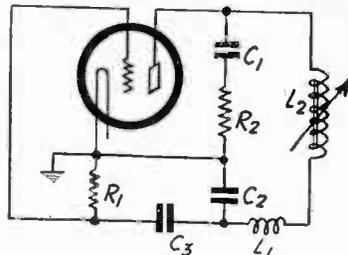


FIG. 2

A Colpitts oscillator in which the tuning inductance is varied by permeability changes. The circuit is shown padded to track with an r-f system.

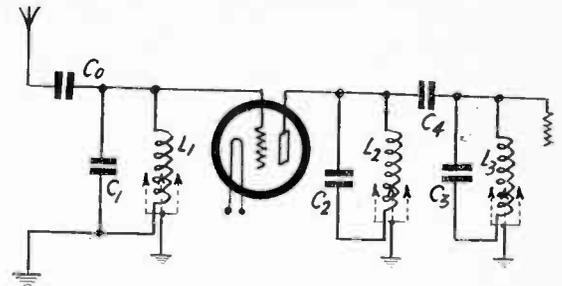


FIG. 3

An example of three permeability-tuned circuits in a radio-frequency amplifier. C_0 is small and C_1 is adjusted on the basis of the reflected antenna capacity included, though C_1 , C_2 and C_3 need not be exactly equal.

TUNING by varying the inductance in a circuit is not new, for it was used long before broadcasting began, and one of the early forms of tuning in broadcast reception employed a means for varying the inductance. We all recall the variometer. Now, this device is usually thought of in connection with squeals and broad tuning, for it was used in regenerative receivers. It cannot be said that it was a good device judging by present standards of reception. Yet it appears that radio is turning back to inductance tuning. No, the old variometer is not coming back. If inductance tuning is to return it must be in a form that is an improvement over anything that we have at present. It appears as if circuits in the future will be tuned by iron, and tuning will be done by varying the permeability of the core of the radio frequency coil.

Let us tell what permeability is. If we have a long solenoid and send a direct current through the winding, there is a certain magnetic flux around the coil, particularly inside it. If a magnetic needle is placed near it, the needle will be deflected. There is a certain magnetic flux "flowing" through the solenoid and the compass needle will line itself up with this flow. Now suppose we put an iron rod through the solenoid. The flux will increase, possibly a thousand fold. Iron conducts magnetic flux better than other ordinary metals or non-metals, just as silver conducts electric current better than, say, a rod of bakelite. The permeability is the ratio of the magnetic flux that "flowed" through the solenoid when the iron is in the coil to that which "flowed" before the iron was inserted, the current remaining constant. Only that space which is occupied by the iron should be considered.

Tuning by Means of Iron

Suppose we have a coil which forms a part of an oscillator. A certain frequency is generated by the circuit, which, let us say, is near the upper limit of audibility so that the oscillation can be detected easily. Now let us bring up a piece of iron to the coil. The frequency generated will become lower. If the iron is a rod and it is inserted into the coil the frequency may become very low. Obviously, the iron affects the property of the coil,

that is, its inductance, for it is not the capacity that changes by any amount that could account for the large change in the frequency. One definition for inductance is that it is the total magnetic flux associated with a circuit when unit current is flowing. It is clear, therefore, that if the iron increases the flux, the current remaining constant, the inductance of the coil increases.

The increase in the inductance due to the iron may range from a factor slightly greater than unity to a factor as high as 2,000, for good magnetic iron, and even many times higher than that for certain iron-nickel alloys. The amount by which the inductance increases depends on the material and on its disposition with respect to the coil. It is clear that if the frequency of an oscillator can be changed by means of iron or other magnetic substances, that the same thing can be done for a tuner. That is, the frequency of resonance can be changed by varying the amount of iron in the coil or by varying its disposition in respect to the turns.

Iron Losses

But there are losses in iron when used as magnetic cores. Some of these losses are due to hysteresis and some to eddy currents. Hysteresis is due to the fact that it takes work to magnetize the iron. In some steels used for permanent magnets this is very great. In soft iron and alloys used for transformers, the work required to magnetize is very small. The smaller it is, the better is the material for transformer cores. Eddy current losses are due to the fact that iron is a conductor and that current will flow in the core. A good core material should have the highest possible electrical resistance and the lowest possible magnetic resistance, or reluctance.

These losses increase rapidly as the frequency goes up. The hysteresis losses increase because the higher the frequency the more frequently will the work of magnetization and demagnetization then have to be done, and there is the same loss each time. Eddy current losses increase with frequency because the higher the frequency the higher the induced voltages causing the currents. The increase in the eddy current losses is about proportional to the square of the fre-

quency. Hysteresis losses do not increase indefinitely, for at radio frequencies they are negligible.

Another factor that affects the losses due to eddy currents is the length of the paths in which the induced currents can flow. The shorter the paths the lower the loss. It is for this reason that transformer cores are laminated. The laminae are placed in the field so that there is no obstruction to the magnetic flux, but so that there is peak obstruction to the flow of induced currents in the core. To make the paths short the laminae are made as thin as practical, and at the same time insulation is placed between them. Sometimes this insulation may simply be the oxide that forms on the surface of the metal, but sometimes actual insulating layers are placed between.

Stranded Cores

Another way of reducing the eddy current losses is to use stranded cores, that is, cores made of magnetic wire bundled together and insulated from each other. If these wires could be made to meet end to end, this would not greatly increase the reluctance of the magnetic circuit, yet eddy currents would be prevented, but it is obviously impracticable to make a core of thousands of fine wire and have each come around and meet itself. In practice the wires are bundled up through the coil and then brought back on the outside so that the ends overlap and lie side by side. Audio frequency transformers have been made this way. But these do not provide any means for varying the permeability of the core. In shell type transformers an airgap is inserted for the purpose of preventing saturation. By shortening and lengthening the gap it would be possible to vary the inductance of the coil. A practical scheme for doing this could be worked out if there were any occasion for it.

Dust Cores

In an endeavor to reduce eddy current losses at the high frequencies and at the same time maintain a reasonably high effective permeability, engineers have experimented with iron dust cores. Pure iron, as a rule, is made into an extremely fine dust, then mixed with an insulating varnish and a binder, and finally com-

pressed under terrific pressure. The resulting compact looks like iron, for it is about 95 per cent. iron, and it is reasonably strong. It can be machined into any desired shape. But since the mass is moulded, the usual thing is to put the mixture in forms having the desired shapes so that no machining is needed. In other words, the dust cores are moulded, under high pressure, just as bakelite is moulded. Indeed, the binder often is bakelite.

The smaller the iron particles the lower will the losses due to eddy currents be, but the lower will also be the permeability. High compression is necessary to maintain a high permeability, and also very thin films of binder and insulating materials. When the size of the grain has been reduced to where the losses at broadcast frequencies are low enough to make selective coils, the permeability is not high enough, being of the order of 5 when the grain has a diameter of 0.000001 meter. This is not enough if the permeability method of tuning is to be used because the permeability must then be greater than the square of the frequency band to be covered. By increasing the size of the particles a little, and also the compression, it is possible to increase the permeability to as high as 20, and that is high enough for broadcast frequency tuning purposes. Indeed, a range of permeability change in the coil of only 7.5 is required.

Tuning by Permeability

When tuning is to be done by varying the permeability of the space around the coil, this is first designed as an air core inductance to be correct at the higher frequency end without the aid of the dust core. A fixed condenser is used for tuning this coil to the high frequency, that is, it is fixed after the first adjustment has been made. When lower frequencies are to be tuned in, the iron dust core is brought nearer the coil and that increases the inductance so that the circuit will resonate to lower frequencies.

In practice, the coil is made slightly conical. An iron dust plug, also conical, is moved into the coil along the axis. At the same time, and part of the same chunk of dust compact, an external sleeve is brought up. Then the inductance of the coil is to be greatest, the turns are practically surrounded by the dust core. Of course, there are different methods of construction. In Fig. 1 is shown the cross section of a coil of this kind. It appears that the inner and outer parts of the core were designed so that core moves in on the coil from the right. If it were arranged so that the outer part moved in from one direction and the inner part from the opposite, a closer fit would be possible. A greater variation in the permeability of the space about the coil could be effected that way when necessary.

Mechanical Arrangement

When tuning a gang of circuits by this method, the cores are mounted rigidly on a frame and the coils are moved in respect to them. To cover the entire broadcast band, a stroke less than half an inch is necessary. Therefore a coil and its mechanism for varying the inductance do not take much room. But a stroke of less than half an inch means that the dial readings will be crowded. This can be avoided, however, by using a lever to multiply the movement. For example, a movement of 3/8-inch at the short end could be made into 3 inches at the long end if the long arm, which would be the pointer, is eight times longer than the short arm.

The mechanism used is of the same type as that used for varying the capacity in the "plunger" condensers. That is, the core is a stator and the coil itself is the

rotor, and the rotor plunges in and out of the core.

Advantages of Permeability Tuning

Does permeability tuning have any advantages not possessed by capacity tuning? Yes, the main advantage is that the selectivity remains constant throughout the tuning band, and also that the gain is nearly constant for all the frequencies covered by the tuner. Just why is the selectivity constant throughout the band? The reason given is that the inductance increases at the same rate as the resistance of the circuit. That is, if L is the inductance and R the resistance of the coil, L/R remains a constant. This is the damping coefficient of the coil, not the usual selectivity.

The gain of an amplifier using a tuning coil of this type is constant for the same reason. If the circuit is of the tuned impedance type, for example, the resonant load on the tube ahead of the coil is L/CR, in which L is the inductance of the coil, C the capacity with which it is tuned, and R the resistance. When tuning is actually done with the inductance by the method discussed, L/R remains constant, and C is a constant. Therefore the load on the tube remains constant. There is nothing then to vary the output for the internal resistance of the tube is also constant, and so is the amplification factor, if we remember that no changes of operating voltages are involved but only a change of frequency.

Therefore, if we tune a circuit by varying the permeability of the space around the coil, we gain constancy of effective selectivity and constancy of amplification throughout the tuning range. Besides, the assembly of a multi-tuner circuit is compact. There is also an increase in the amplification as compared with an air core inductance and capacity tuner. The tuned circuit is designed for the high frequency end where the gain ordinarily is highest. The inductance is then increased to bring in the lower frequencies. Instead of decreasing, the amplification really should increase as the inductance is increased, for it is the exact reverse of capacity tuning. In fact, there is an increase in the gain as the frequency decreases, but the increase is not so large as the increase on the high frequencies when capacity tuning is used. An interesting fact is that the amplification on the low frequencies decreases when the core is grounded, making the gain practically constant throughout the range.

Circuit Shown

Using a 58 tube under normal operating conditions, a dust core coil of 65 microhenries at 1,500 kc, and a fixed capacity of 160 mmfd., the gain per stage was 95 at 700 kilocycles per second, where it was

maximum, a gain of 84 at 1,000 kc, and a gain of 81 between 1,100 and 1,500 kc.

In Fig. 4 is shown a circuit diagram of four-tube amplifier-tuner-detector, in which the tuning is done by varying the inductance of the coils. There are six of these coils, one in the input of the first tube, two between the first and the second, two more between the second and the third, and one in the plate circuit of the third tube. The cores are shown at the bottom of the regular coil symbols and they are grounded. The plate voltage connection to the coils is omitted as is also the grid connection when the grid is not returned to the automatic volume control.

The radio frequency gain of a circuit like this is of the order of 500,000, which should be enough under all practical conditions. The selectivity is also very high and remains practically constant for all the frequencies covered by the inductance tuner.

Dimensions of Practical Coils

It was stated that the dimensions of the coil and tuner were small. A coil has been designed having a mean diameter of 3/4-inch, wound with Litz and has an L/R ratio of 14.5 millionths, which makes the Q of the coil at the highest frequency nearly 150. This is very good for a radio frequency coil at this frequency.

While these coils are recommended primarily for tuned radio frequency receivers, they can also be used in superheterodynes. The tracking problem is solved by padding, somewhat in the same way as it is done in capacity tuning. The circuit employed is the Colpitts, which requires only one coil, therefore suitable. A few turns are removed from the coil that is to be used in the oscillator, and then a padding coil is put in series externally to the variable coil field. It is claimed that such an arrangement, properly adjusted, will track with the radio frequency circuits to within 0.1 per cent. The condenser padding method is capable of tracking to about one per cent. of the intermediate frequency. Therefore if the intermediate frequency is 0.1 of the signal frequency, the two are capable of about the same degree of tracking.

There are other ways of tracking. For example, the inner plug can be molded to a different shape than the plug used in a radio frequency tuner. By giving the plug the proper shape, the oscillator could be made to track at any intermediate frequency. Still another way of making the oscillator track is to make the oscillator coil identical with the r-f coils in all respects except that the outer iron dust sleeve is omitted. This decreases the frequency range of the circuit to about 4 to 1, which is about right for an intermediate frequency of 450 kc.

FILL OUT AND MAIL NOW

SUBSCRIPTION BLANK

RADIO WORLD

RADIO WORLD

145 West 45th Street, New York City

Please send me RADIO WORLD for months, for which

SUBSCRIPTION RATES:

Single Copy.....	\$.15
Three Months.....	1.50
Six Months.....	3.00
One Year, 52 Issues.....	6.00
Two Years, 104 Issues.....	10.00

Add \$1.00 a Year for Foreign and Canadian Postage.


If this is a renewal, put cross in square at left.

please find enclosed

Radio University

A QUESTION and Answer Department. Only questions from Radio University members are answered. Such membership is obtained by sending subscription order direct to RADIO WORLD for one year (52 issues) at \$6 without any other premium.

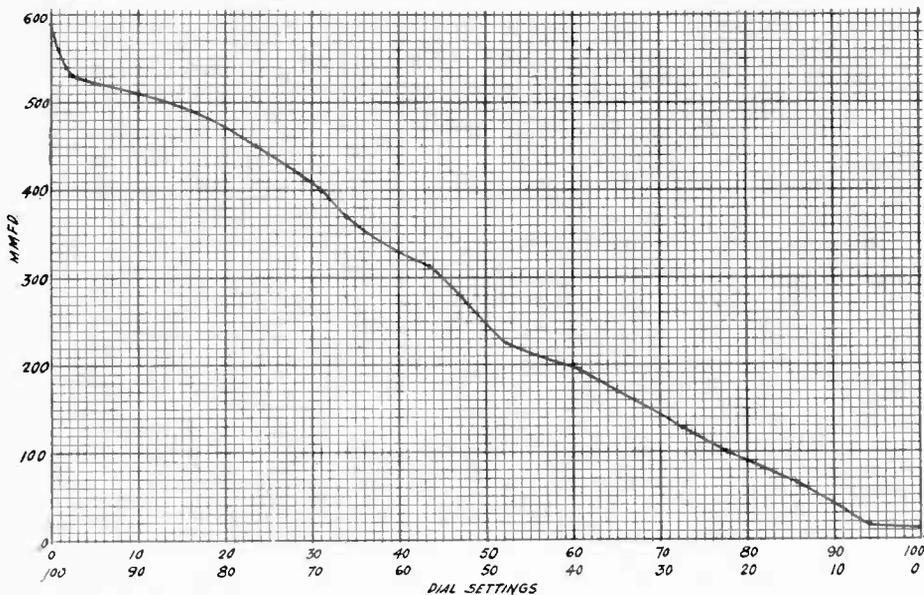RADIO WORLD, 145 WEST 45th STREET, NEW YORK, N. Y.



Capacity curve of the G.R. type 247 condenser. Circuit capacities have been excluded, so that the capacities are those of the condenser alone. The values in micro-microfarads are shown at left upright (ordinate), and the dial settings are on the horizontal (abscissa). The condenser is turned to the left for capacity increase. The dial divisions may be 100-0 or 0-100, so both scales are given. To avoid confusion, select the one applicable and ignore the other. It is generally preferable to have higher numerical settings represent higher capacity.

Pair Broadcasting Stations

WHAT is meant by paired broadcasting stations? I have seen this term but there was no explanation of the meaning.—W. T.

Two stations operating on the same wave and using the same antenna are said to be paired when they take turns delivering the signals. The two stations are working all the time but by means of a mechanical distributor they deliver energy to the antenna alternately. This system is in the early experimental stage and there is no definite information on how well it works out. The scheme works very well on land lines and cables for duplex telegraphy and it should work equally well on radio duplex telegraphy. But the problem being investigated is the possibility of using the same system for voice and music. If the change from one to the other could be accomplished fast enough there is no reason why it should not work. But receiving one or the other of the signals would offer difficulties. But that problem, too, is being solved apparently.

Capacity Curve

CAN YOU GIVE the curve of the General Radio Type 247 condenser, relating capacity with dial settings?—I. D.

The curve is printed herewith. It represents the capacity of the condenser alone at various settings, as other circuit capacities were determined and excluded. Therefore if you are to use the condenser in a tube circuit, the capacity would not be as shown on the curve, but would be greater by the amount added, e.g., tube element capacity, wiring capacity, etc. However, what this amount actually is could be ascertained, by striking a frequency with some random low

capacity of the condenser, using a known inductance, and computing the capacity. Subtract the condenser capacity as obtained from the curve to ascertain this distributed capacity. It is preferable to use around 50 mmfd. or so of the G. R. condenser in making this test. The capacity of this condenser runs uniform enough in production to enable use of the curve given, for any but precision measurements. The capacities are actual for sixteen well-distributed points, the rest being extrapolated to yield the curve. The kink near the middle seems to be due to a metal strap in the condenser construction, for although this strap is at theoretically ground potential, in an oscillator any grounded conductor will be grounded actually perhaps at one point, and then a voltage rise in the conductor will take place even over a short span of a few inches. The upsweep of the curve at high capacity (maximum) is due to the shape of the plates and is the opposite to the minimum capacity effect, where there is practically no capacity change for a few divisions.

How Capacity Meter Works

ON WHAT principle does a capacity meter work, I mean one that is direct reading? I understand how a resistance meter works. Is the capacity meter based on the same principle?—L. M. J.

Yes, you might say that the two work on the same principle, both are based on the reduction of a meter reading, with constant applied voltage, due to the impedance connected in series. When a capacity is to be measured the current must be alternating and the frequency must be taken into account. Suppose you connect an alternating current voltmeter in series with a known

voltage and in series with a known capacity. There will be a certain reading on the voltmeter. That corresponds with that capacity. Another capacity can be inserted to get another reading, and so on until a sufficient number of points have been determined to construct a curve, or a scale.

Electron Coupling

WHAT is the difference between electron coupling and other forms of coupling? How can you tell whether you have electron, inductive, capacitive, or resistive coupling?—W. L. P.

Coupling signifies that there is an impedance common to two circuits. One circuit produces an effect on the other and the effect is mutual. In other words, there is reaction between the two. A mechanical example of coupling is the junction between two railway cars. You can move both cars by putting a motor in either, for there is a reaction between the two. Likewise if two circuits are coupled you can produce currents in both by introducing an electromotive force in either. Electron coupling is unidirectional. If there is an electromotive force in one it will produce a current in the other, but if the electromotive force is placed in the second there will be no current in the first. The reason for this is that electrons will travel in only one way, the potentials being constant as to direction. When they don't know what type of coupling there is, it is customary to call it electron coupling. If you have an oscillator using a 2A7 tube for example, using the inner elements for the oscillator, the current in the plate circuit is varied by electrons shot out from the cathode to the plate. That is electron coupling, for the plate current has little or no effect on oscillation. It was in this connection that the term electron coupling was first used, and the term should be limited to that.

Air Cell Receivers

WHAT has become of the air cell which we heard so much about a few years ago? Much was promised for it but it seems to have been dropped.—R. T. L.

Air cell receivers are being made for country places. Experimenters are not using the cell because of the difficulty of getting it.

Simple Padding

WILL you kindly explain how the inductance of the oscillator coil and the series capacity can be computed without going into elaborate mathematics? I understand there is a simple way of going about it.—B.G.F.

Yes, there is a relatively simple way, and it leads to quite accurate results. First assume that at the high frequency end of the dial the series condenser has no effect and that the difference in frequency is due only to the difference between the inductances in the oscillator and r-f circuits. Select a high frequency about 100 kc less than the highest to be tuned in, for example, 1,400 kc for the broadcast band. Add to this the intermediate frequency. For example, if the intermediate frequency in the above case is 456 kc, we would have an oscillator frequency of 1,856 kc. Now take the square of the ratio of these, that is, $(1,400/1,856)^2$. This is the ratio of the oscillator inductance to the r-f inductance, assuming the tuning condensers have the same values. The ratio squared in this case is 0.569 and the oscillator inductance is $0.569L$, where L is the r-f inductance. Now we are ready to compute the series capacity. Select a low frequency about 50 kc higher than the lowest frequency to be tuned in, say 600 kc. Add the intermediate frequency. We get 1,056 kc. With this frequency and the inductance just obtained, find the total capacity in the oscillator. In the sample case it is $C_0 = 0.04/L$ mmfd. Find what the capacity in the tuning condenser of the r-f circuit is, using 600 kc and L . It is $C_1 = 0.0704/L$ mmfd. Now the question is: what condenser must be connected in series with C_1 to make the capacity C_0 ? We have by the formula

for series condensers $C_s = C_0 C_1 / (C_1 - C_0)$, where C_0 is the capacity we are looking for. Putting in the values we have just obtained, we have $C_s = 0.0926/L$. L we get from the tuning condenser in the r-f circuit or from the known inductance of the coil employed in the r-f tuner. Suppose the inductance is 240 microhenries. The series capacity should be 386 mmfd. Then the oscillator inductance should be 136.5 microhenries. This design is close enough for practical purposes for adjustments can be made at the high frequency end by the trimmer and at the low frequency end by the series condenser.

Tuning by Permeability

I HAVE problem of constructing an audio frequency oscillator covering the range from 5,000 cycles per second to about 15,000. Tuning is to be continuous. Can you suggest a way of varying the frequency? Incidentally, I plan to vary the frequency in steps by means of condensers but it is between the steps I need a continuous variation.—F. W. K.

If the frequency is to cover this range you will undoubtedly use an iron core transformer, possibly of the open core type. The frequency of an oscillator using such a transformer can be varied continuously by varying the permeability of the core, which can be done by moving part or the whole core with respect to the windings. How this works out you can test by hooking up an oscillator with an air-core transformer and adjusting the frequency so that it is audible. By moving a piece of iron in the field of the coil the frequency will change. It may be that the frequency is too high to be audible when the iron is not near the coil, but when it is inserted the frequency becomes low. But a small variable condenser across the large fixed condensers could also be used. Perhaps that is the simpler way now that we have condensers of many different capacities.

Two Resistance Push-Pull Circuits

CAN YOU GIVE me some assistance in my experiments with resistance-coupled push-pull? I would like to have a diode feeding the push-pull output pair.—P. V. O'D.

Here are two diagrams. One shows the simpler form, the 56 used as diode, feeding the output tubes, which must be pentodes, in such an instance, if the sensitivity is to be anywhere near sufficient. An intermediate-frequency transformer, i.e., superheterodyne circuit, is assumed, for that does not have the secondary tuning condenser grounded. The cathode is tied to the erstwhile plate, to constitute the functioning detector cathode, while the erstwhile grid functions as the anode. Hence one end of the secondary is tied to the anode (grid) and the other end goes to one side of the load resistor, R , which may be 0.5 meg. or higher, other side of that resistor to cathode. So we have a direct-current path from anode through secondary through load resistor, to cathode, and through the tube by the electron movement. The center of R may be directly grounded, if R consists of two equal resistors, and then sensitivity is slightly higher. Grounding is effectuated anyway in the grid circuit loads of the 59's, and is reflected back to R , but is not so effective as additional grounding of R at center. The rectified current moves in one direction only, by the extremes of R are equally but oppositely polarized, reckoned from the center of R . Hence only half the rectified voltage across R is utilized at any instant. Stopping condensers connected to succeeding power tube grids, with 1 meg. or more for R_2 , enable independent biasing of the power tubes, R_3 being 400 ohms, and C_2 omitted, unless found necessary for stability, when it should be 8 mfd. or more. The other circuit uses the 55 as full-wave diode detector, the triode element as a second diode to buck the upper grid's positive voltage. L and C constitute the tuned circuit, return which is in the plate of the previous amplifier tube. L_2 is a tuned or untuned secondary, preferably untuned, as shown. L_1 is the auxiliary feed to the C bias supply constituted of the diode-connected triode elements. R_1 and R_2 are equal, say, 0.1 meg., and P is a potentiometer of higher resistance than either. C_4 , C_5 , C_6 are 0.0001 mfd., Ch is 10 millihenries, R_3 and C_2 have values given in the previous example, and C_3 is the filter condenser at output of the B rectifier.

Coupling of Coils

IN A Hartley oscillator I have a coil of 100 turns wound 57 to the inch, 3 inch diameter. The cathode is connected to a point at the exact center of the coil. I want to know what the coefficient of coupling is between the two parts of the coil. I need this not only to study the behavior of the oscillator but also for measurement purpose when the coil is not in the oscillator. How can you figure out the coefficient of coupling in a case like this?—F. G. J.


In this case the coefficient of coupling is 0.413. If you have a table giving the shape factor of solenoids, that is, Nagaoka's constant, then you can compute the coefficient of coupling from the formula $1 + k =$

$K(3/b)/K(6/b)$, where k is the coefficient of coupling, b is the length of the winding, and K is the constant obtained from the table. The length of the coil is the number of turns divided by the turns per inch. The formula applies only when the tap is in the center and when the diameter is 3 inches. One K is obtained for D/b and the other for $2D/b$. Then the formula applies for any diameter provided that the tap is in the middle. If you have a book containing curves giving inductance values for different turns and diameters, you can look up the inductance of the total coil and then that of half of it. If L is the total inductance and L_1 the inductance of half the coil, the coefficient of coupling is obtained from $1 + k = L_2/L_1$. This is not quite as accurate because of the difficulty of finding the right inductances from curves.


Class B Amplifiers

IS IT worth while to install a Class B audio amplifier in a radio receiver that is to be used exclusively in a home, or will the output be too great? What is the best way of installing Class B?—W. G. J.

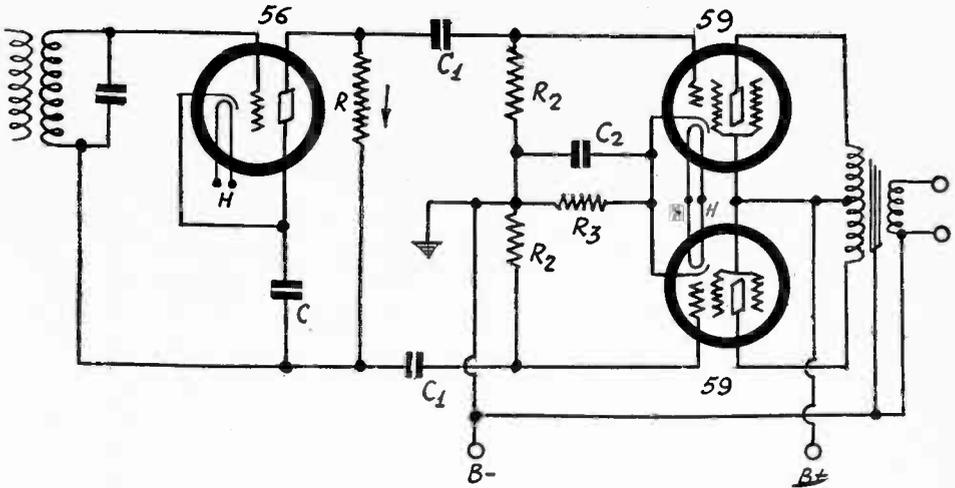The only time Class B amplification would be justified in a home receiver is when
(Continued on next page)




A simple example of push-pull resistance coupling, so called because the voltage across the load resistor R is divided, extremes of R equal in voltage but opposite in polarity, with center grounded either initially, or reflectedly, due to grounding of the juncture of the two R_2 resistors. If R is two equal resistors, center actually grounded, the ground on the other side of the stopping condensers C_1 is retained.

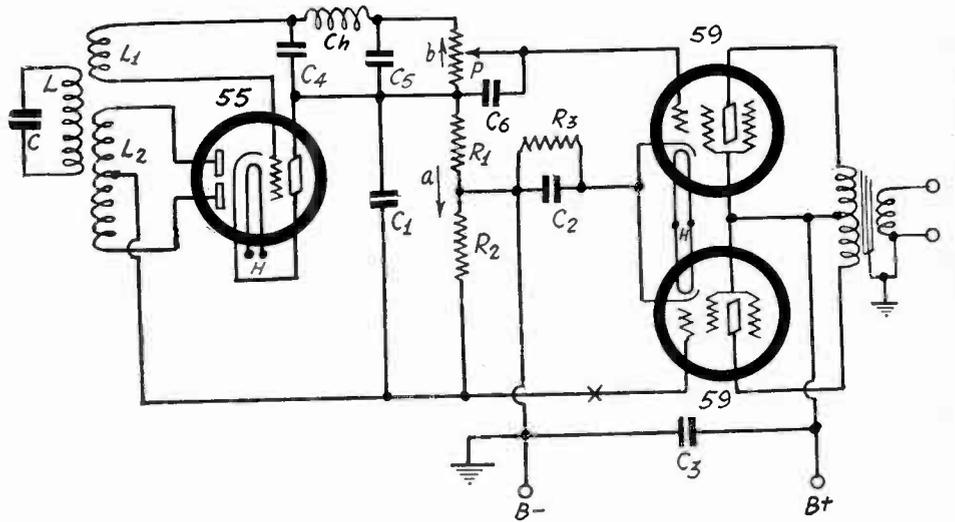

Stopping condensers are omitted in this diagram, hence this represents substantially non-reactive resistance-coupled push-pull audio. The 55 is used as a full-wave diode detector, while the triode elements are connected as a diode for C bias supply to overcome the positive polarity of the upper 59's grid. In both these circuits constants must yield identical voltage values in both legs.

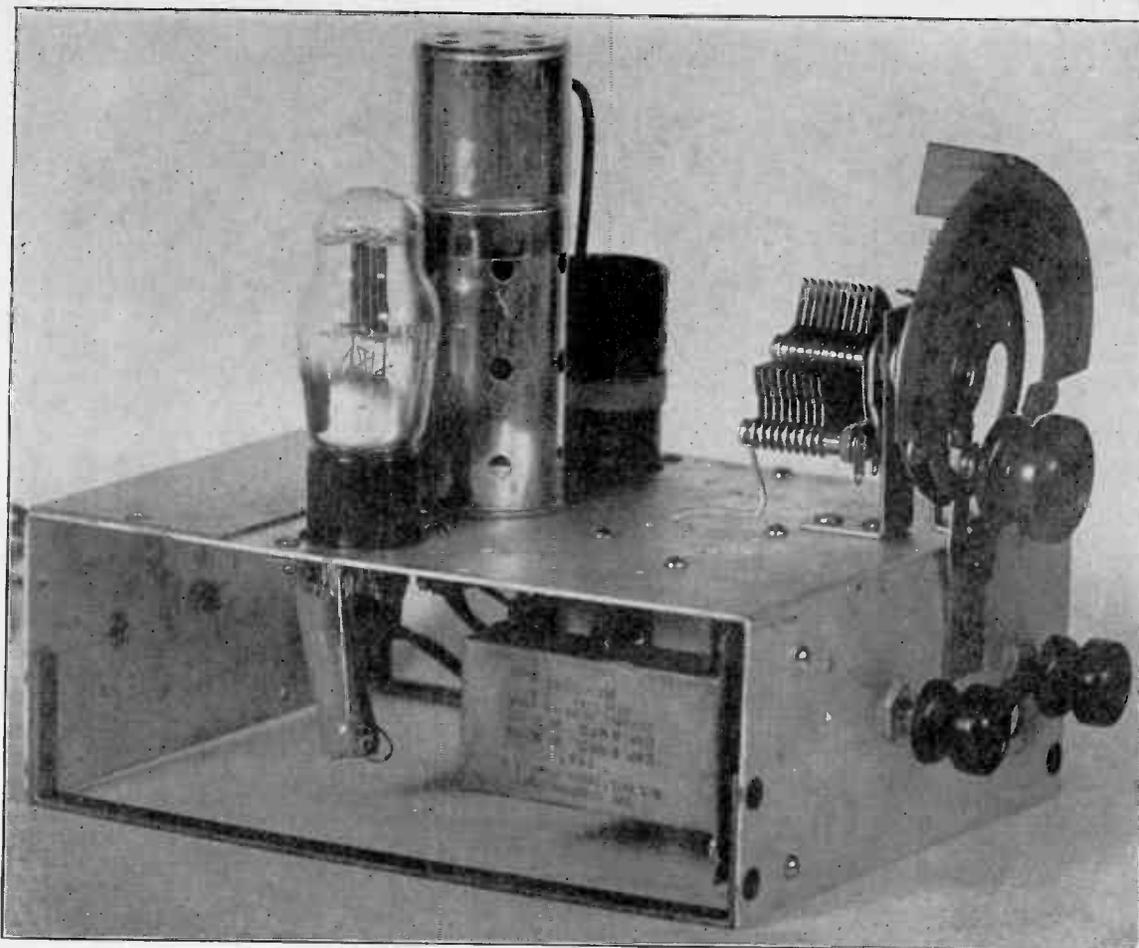Layout for a universal short-wave set, in which there is one tube for regenerative detector. The other tube is the 25Z5 rectifier. The tuning condenser is in view. The feedback condenser is hidden under the chassis. A B choke and some filter capacity for the rectifier are required.



(Continued from preceding page)
the output tubes are miniature. When regular power tubes are used the output of a pair in push-pull, or even of a single one, is much greater than can be utilized in a home. The Class B amplifier would have to be operated with a very low signal voltage, and under these conditions the distortion would be relatively very high.

His Temptation

I AM TEMPTED to try a simple short-wave set, consisting of a 39 or 78 screen grid tube as regenerative detector, and a 25Z5 as rectifier, so I shall have universality, but am wondering whether this is all right, and how about the layout?—J. E. D.

The circuit works consistently with the performance of single-tube short-wave battery sets for earphone use, and if your location is at least fairly good your results

will be satisfactory. The layout, for use of plugin coils, is illustrated herewith.

Magnetostriction Oscillator

YOU have never described the construction of magnetostriction oscillators. I am interested in them and should like to know how they work. Can you suggest a way of making one without going into a detailed description?—W. R. L.

Take a piece of monel rod about four inches long. Mount it so that the support is as near the center point as possible. Put a coil over each end, but not so that the coils touch the rod. It is advisable to place a magnetic screen between the two, and this shield can be an iron plate, which may also serve as support. Connect on coil in the grid circuit of a tube and the other in the plate circuit. Suitable coils are those used for 175 kc intermediate transformers, the

cores having been removed. The coils should be connected in the opposite direction to that used in other oscillators much depends on the monel metal. While this is generally one of the best for the purpose, not every rod will oscillate. Much also depends on the mounting.

Tracking or Padding

WHEN the intermediate frequency is 456 kc in a superheterodyne for broadcast reception, which is the better way of keeping the oscillator in line with the r-f circuit, the use of a tracking condenser or padding?—F. R. N.

Padding can be done to an accuracy of about one per cent of the intermediate frequency. That means that when the intermediate frequency is 456 kc, the deviation from perfect tracking need not exceed more than 5 kc. But with improper padding it may be ten times that. When a tracking condenser is used the oscillator should always generate the correct frequency, assuming that the tracking condenser has been designed properly and that adjustments have been done well. But the actual deviation may be just as great when this method is used. Since selectivity is a matter of ratio, it does not matter what the intermediate frequency is. At 100 kc the maximum deviation may be only 1 kc while at 500 kc it would be 5 kc. But the detuning would amount to the same in both instances.

Oscillation in Detector

PERHAPS you can suggest the cause of an oscillation that occurs in my receiver. It appears to be in the final detector. The circuit is of the grid biased type and the grid return is made to ground. In the plate circuit I have a filtering consisting of a choke of about 10 millihenries and two shunt condensers, each of 0.00025 mfd. These are connected in series across the choke and the junction is connected to the cathode. I have a bias resistance of about 25,000 ohms and this is not shunted by any condenser. When I do put a large condenser across it the oscillation ceases. I know the remedy

Two for the price of One

Get, EXTRA, one-year subscription for any One of these magazines:

- POPULAR SCIENCE MONTHLY.
- RADIO-CRAFT (monthly, 12 issues).
- RADIO INDEX (monthly, 12 issues), stations, programs, etc.
- RADIO (monthly, 12 issues; for Amateurs and short-wave experimenters).
- EVERYDAY SCIENCE AND MECHANICS (monthly).
- RADIO LOG AND LORE. Bi-monthly; 5 issues. Full station lists, cross indexed, etc.
- AMERICAN BOY—YOUTH'S COMPANION (monthly, 12 issues; popular magazine).
- BOYS' LIFE (monthly, 12 issues; popular magazine).
- OPEN ROAD FOR BOYS (monthly, 12 issues).

Select any one of these magazines and get it free for an entire year by sending in a year's subscription for RADIO WORLD at the regular price, \$6.00. Cash in now on this opportunity to get RADIO WORLD WEEKLY, 52 weeks at the standard price for such subscription, plus a full year's subscription for any ONE of the other enumerated magazines FREE. Put a cross in the square next to the magazine of your choice, in the above list, fill out the coupon below, and mail \$6 check, money order or stamps to RADIO WORLD, 145 West 45th Street, New York, N. Y. (Add \$1.50, making \$7.50 in all, for extra foreign or Canadian postage for both publications.)

Your Name.....
 Your Street Address.....
 City..... State.....

DOUBLE VALUE!

- If renewing an existing or expiring subscription for RADIO WORLD, please put a cross in square at beginning of this sentence.
- If renewing an existing or expiring subscription for other magazines, please put a cross in square at the beginning of this sentence.

RADIO WORLD, 145 West 45th Street, New York. (Just East of Broadway)

but I don't know the cause of the oscillation.—W. H. C.

If you connect a coil between the grid and the plate and two condensers in shunt, that is, one from the plate to the cathode and the other from the grid to the cathode, you have a Colpitts oscillator. You have those conditions, and it is quite possible that the circuit oscillates for that reason. The feedback would be through the bias resistance, the ground end of which is equivalent to the grid. When you put a large condenser across the bias resistance you short circuit the grid input in so far as the oscillator is concerned. If the oscillation also stops when the second of the two shunt condensers is removed, that would be additional evidence pointing to the filter as the cause of the oscillation. But then there might be enough stray capacity to keep the circuit oscillating.

* * *

Utilizing Beats Between Stations

WILL YOU kindly show a circuit suitable for the calibration of an intermediate frequency oscillator by utilizing the beats between broadcast stations? I imagine that this is possible and that high accuracy of the beat will result, since nearly all broadcast stations are closely controlled as to frequency.—R. L. B.


You will find a suitable circuit on this page. It is about the simplest arrangement that can be used, but in some locations it may be necessary to amplify the signals before they are impressed on the mixer tube. This tube is a duplex amplifier such as the 53. There are two input circuits, each tuned to one of the beating frequencies. The two plates of the tube are tied together and an intermediate-frequency transformer is connected in the circuit to pick out the beat frequency before it is impressed on a detector tube. The oscillator to be calibrated is very loosely coupled to the grid of the detector tube by a small capacity C_m . The intermediate coupler must be tunable and it should cover the same range as the oscillator to be calibrated. Tune the two radio frequency circuits to any two broadcast stations differing in frequency by the amount desired. Find the corresponding setting of the oscillator by the zero beat (between the first beat and the oscillator frequency). When one point has been found select stations that give another frequency, or one other station and one that is already tuned in. By this means any oscillator can be calibrated in steps of 10 kc from about 10 kc to 1,000 kc., provided, of course, that the radio-frequency receivers are sensitive enough to pick up enough stations.

* * *

Distortion in Resistance Coupled Amplifiers

ARE all audio frequencies really amplified to the same degree in a resistance capacity coupled amplifier, or do the condensers cause discrimination? If so, to what extent and which frequencies are suppressed?—R. L. B.

There are two effects which cause differences in amplification. First, there are the tube capacities which are in shunt with the coupling resistors and for that reason reduces the amplification of the high frequencies. Second, there is the grid stopping condenser, which reduces the amplification on the low frequencies. Therefore the coupler is in effect equivalent to a very broadly tuned circuit in which there is one frequency at which the amplification is maximum. Just what effect the shunt capacities have in suppressing the high frequencies depends on the values of the capacities and also on the values of the coupling resistance and grid leak. The higher the resistances the more the high notes will be suppressed. What effect the series condenser has in suppressing the low frequencies depends on its capacity and also on the value of the grid leak resistance. The greater the product of the grid leak resistance and the capacity, the less will the

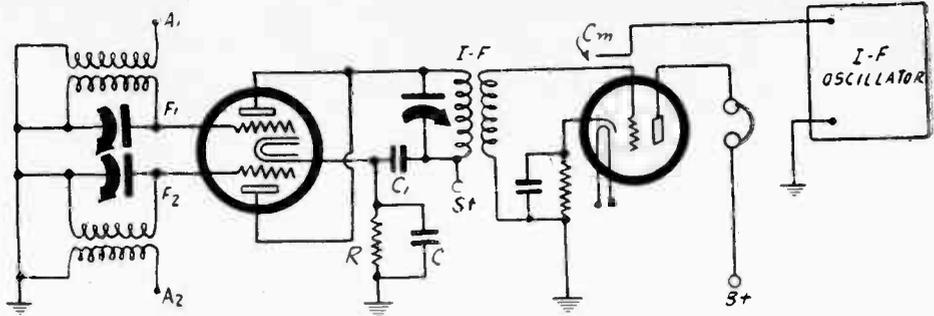

This circuit shows how it is possible to utilize broadcast stations for calibrating an oscillator against the beat frequency of two transmitters. High accuracy is possible because the stations are accurate.

low notes be suppressed. In order to make the circuit amplify all audio frequencies to about the same degree, the stopping condenser capacity should be large and the shunt condensers should be small. High mu tubes and screen grid tubes have higher input and output capacities than low mu triodes. Therefore when high quality is essential low mu tubes should be used, that is, general purpose tubes. It is permissible to use higher plate resistance and grid leak with low mu tubes than with high mu tubes, and since high resistance also improves the wave form, we have another reason for using low mu tubes.

* * *

Type of Oscillator for Super

For a time the 57 and 58 tubes were used as oscillators and mixers in superheterodynes in such a manner that the tuned oscillator circuit was put in the place circuit of the tube and the grid coil in the cathode lead. Is not this a better way of mixing than the method employing the 2A7? What do you consider the best way of producing the oscillation and of mixing?—W. H. L.

Whether you use the 2A7 or similar tube or a 58 in the manner mentioned makes comparatively little difference. However, of the two the 2A7 is the better because it is more reliable. Any mixer should have an

oscillator that is free from harmonics and the coupling between it and the detector should be such that only the fundamental is impressed on the mixer. Moreover, the voltage from the oscillator should not overload the detector, for if it does there will be all kinds of harmonics in the output of the mixer. It is always well to have a means for controlling the signal voltage from the oscillator that is impressed on the mixer.

* * *

Decrease of Permeability

WHY DOES the apparent permeability of an iron core decrease as the frequency of the magnetizing current increases? Is not the same iron in the magnetic circuit all the time?—W. B. J.

The reason the apparent permeability decreases is that as the frequency increases the magnetization is confined to the surface of the core material. In other words, the higher the frequency the less of the iron takes part in the magnetic circuit. It is for the same reason that the resistance of a conductor increases with the frequency. A magnetic field is set up inside the wire and the current is limited to the surface of the wire. This is the so-called skin effect. But the skin effect in the core also limits the hysteresis losses because not so much of the iron is magnetized

Join Radio World's

UNIVERSITY CLUB

And Get Free Question and Answer Service for the Coming 52 Weeks.
THIS SERVICE FOR UNIVERSITY SUBSCRIBERS ONLY

Subscribe for RADIO WORLD for one year (52 numbers). Use the coupon below or write on a separate sheet of paper, if preferred. Your name will be entered on our subscription and University Club lists by special number and you will be apprised of the number. When sending questions, put this number on the outside of the forwarding envelope (not the enclosed return envelope) and also put it at the head of your query. If already a subscriber, send \$6 for renewal from close of present subscription and your name will be entered in Radio University.

NO OTHER PREMIUM GIVEN WITH THIS OFFER

[In sending in your queries to the University Department, please paragraph and number them. Write on one side of sheet only. Always give your University Club Number.]

RADIO WORLD, 145 West 45th Street, New York City.

Enclosed find \$6.00 for Radio World for one year (52 nos.) and also enter my name on the list of members of RADIO WORLD'S UNIVERSITY CLUB, which gives me free answers to radio queries for 52 ensuing weeks, and send me my number indicating membership.

Name

Street

City and State.....

Station Sparks

By Alice Remsen

SOME CHANGES HERE AND THERE

Phil Cook, the "one-man show," will be on the opening program of the Silver Dust Serenaders—this is a new tri-weekly program—Tuesdays, Thursdays and Saturdays, WABC, 7:30 p.m. . . . Connie Gates is now being featured with Mark Warnow's Orchestra, Thursdays at 10:45 p.m. . . . Georgie Jessel's half-hour program has been switched to Tuesday nights; now the inimitable Georgie, with Freddie Rich's Orchestra, the Eton Boys and Edith Murray, may be heard over WABC each Tuesday at 9:30 p.m. . . . Very glad to hear that Jimmy Kemper will be featured on the "Music in the Air" program, with Bob Armbruster's Orchestra, each Monday, Wednesday and Friday at 7:30 p.m. Jimmy has a new style of song-dramatizations to give the radio fans, in which he will be assisted by Neil McFee, well known Broadway actor; a male octet and the Humming Birds trio will also be heard. This series is sponsored by the Tidewater Oil Company and is heard over WABC and a network of eighteen stations.

JULIA AND FRANK ON THE ROAD

And so it's "the road" again for Julia Sanderson and Frank Crumit! With the New Year these two veterans of stage and radio opened in vaudeville and their home, "Dunrovin," will be theirs in name only for a while. They will still be heard over WABC, however, each Sunday at 5:30 p.m. on their Bond program. . . . Nino Martini made his debut on the Metropolitan Opera stage singing the role of the Duke in Verdi's "Rigoletto." The handsome young tenor received numerous ovations in response to his rendition of the principal arias, taking as many as twenty curtain calls in the last act. Lily Pons played opposite him in the role of Gilda, and it was a general comment among the audience that never before had a couple so fitted to the romantic roles of "Rigoletto" appeared on the stage of the "Met." . . . Patricia Dorn decided to take advantage of New York's recent snowstorm and get out her ice-skates; consequently, Patricia appeared at the studios limping with her strained ankle beautifully bandaged; evidently Pat is better at the "mike" than on the ice. . . . Gypsy Nina and Gertrude Neissen staged a sleigh-driving contest in Central Park last week; Gertie won by a nose. . . .

MARY EASTMAN BACK AGAIN

Mary Eastman, beautiful and gifted young soprano, returned to the Columbia network last week; she will be heard on weekly broadcasts with Howard Barlow and his orchestra each Friday at 10:45 p.m. Miss Eastman will devote herself to operatic arias, concert numbers and occasional musical comedy numbers. . . . Colonel Stoopnagle and Budd, who were recently appointed Colonels on the staff of Governor Ruby Laffoon of Kentucky, received their commissions last week bearing the full names of the Colonels, Hon. F. Chase Taylor and Hon. Wilbur Budd Hulick. With the commissions Colonel Stoopnagle and Budd received a letter from "General" C. C. Pettijohn, commander of all the Kentucky Colonels, containing a very fine offer; the "General" said if they would attend the next Kentucky Derby, he would give them the name of a horse that is guaranteed to finish not worse than ninth. . . . Julia and Frank (Crumit and Sanderson) have started their fourth year of broadcasting over the same network for the same sponsor. Not so bad, what! . . . Babe Ruth has started a series of electrical transcription programs over WOR. The program will be in the nature of a boys' club, and may be heard each Monday, Wednesday and Friday evening at 6:30 p.m. Prizes will be awarded each week. . . .

THOSE TYPEWRITER BOYS

A new program called "The Magazine of the Air" will be heard on WOR each

Wednesday at 9:00 p.m. Five leading journalists will be featured—Heywood Broun, Gilbert Seldes, Sigmund Spaeth, Alice Hughes and Jack Kofoed. News of the hour will be dramatized in the opening of every program, with four or five episodes being used. Seldes will provide the editorial comments as well as reporting news of the theatres and the motion picture world; humorous observations will be broadcast by Broun; Miss Hughes will voice things of interest to women; Kofoed will confine himself to current events of the sports world; and Doctor Spaeth is to give a digest of the latest in music and will use the WOR house orchestra for demonstrations. . . . Sally and Sue are still broadcasting each Monday, Wednesday and Friday at 2:15 over WOR, and are receiving quite a lot of audience mail with requests for little known songs. . . . There is a new weekly series on WEAJ, Sundays at 3:30 p.m. featuring Richard Himer's Orchestra, Francis Langford, and the Three Scamps. . . . And Jack Pearl replaced Bert Lahr on those Wednesday night programs over WEAJ at 8:00 p.m. . . .

DROP ME A LINE

Your faithful scribe has opened on a new series over WEAJ each Wednesday morning at 11:15 E.S.T., over the following stations: WEAJ, New York; WTAG, Worcester, Mass.; WEEL, Boston, Mass.; WGY, Schenectady, N. Y.; WBEN, Buffalo, N. Y.; WCAE, Pittsburgh, Pa.; WTAM, Cleveland, Ohio; WWJ, Detroit, Mich.; WSAI, Cincinnati, Ohio; KYW, Chicago, Ill.; KSD, St. Louis, Mo.; WDAF, Kansas City, Mo.; WCSH, Portland, Me.; WSM, Nashville, Tenn.; WTMJ, Milwaukee, Wis.; WEBC, Superior, Wis.; WMC, Memphis, Tenn.; WSB, Atlanta, Ga.; WAPI, Birmingham, Ala.; WSOC, Charlotte, N. C.; WSMB, New Orleans, La.; KTHS, Hot Springs, Ark.; KVOO, Tulsa, Okla.; KPRC, Houston, Texas; WOAI, San Antonio, Texas; WKY, Oklahoma City, Okla.; KOA, Denver, Colo.; WJAR, Providence, R. I.; WFBR, Baltimore, Md.; WLIT, Phila.; WRC, Washington, D. C.; WHOM, Rochester, N. Y.; WOW, Omaha, Neb.; WBAP, Fort Worth, Texas, and KDYL, Salt Lake City, Utah. Hope you'll turn the dial my way and take a listen—if you like it—well, listen again on the following Wednesday; if you have a favorite song you'd like to hear me sing, drop me a line and I'll try to do it for you; address me Station WEAJ, Rockefeller Plaza, New York. Thanks! . . .

OVER THE RADIO FIELD

Jean Sargent has left radio for pictures. . . . Rube Goldberg, the cartoonist, James Melton and Al Goodman's orchestra have signed a contract for a new commercial series over NBC. . . . Very sorry to hear

A THOUGHT FOR THE WEEK

WHEN FRANK CRUMIT and JULIA SANDERSON came on the air you may be quite sure that you are not going to hear anything off-color or a word, line or thought which you might hesitate to explain to the youngsters; and yet they talk and sing for the adult mind also—but their record on the stage and in radio is as clean as it is interesting. Their General Baking Co. and Blackstone programs have always been notable for cheerfulness and warmth and human interest.

Mr. Crumit and Miss Sanderson, we salute you and express the wish that you will be on the air for many years to come and continue to prove that wit and humor and music may be joined together without ever transgressing the good taste and wholesomeness which are yours in a superlative degree.

that the wife of Will Donaldson, the accompanist and arranger for Men About Town, passed away last week. . . . Lulu McConnell will be back on the air again soon, and perhaps for her old sponsor. . . . WLS, Chicago, refused to link up with NBC on the two-hour opera broadcast. Perhaps they used good judgment: there are many listeners who would not care for such a strong dose of highbrow entertainment but would rather listen to a comedian, popular singer, or even a political speaker; it would be a dreary world if we all had the same tastes. . . . The reason Lennie Hayton was off the Crosby show for a time was "union trouble;" that sort of trouble is not always confined to "Cloaks and Suits;" the musicians' union is one of the strongest in the country. . . . The radio slogan nowadays seems patterned after Kingsley's Westward Ho! Among those to make a long trek westward are Ruth Etting, Morton Downey, Guy Lombardo, Phil Regan, Rudy Vallee, Alice Faye, Bing Crosby, Lennie Hayton, Burns and Allen, Lanny Ross, Ted Husing and Kate Smith. . . .

OUTSTANDERS IN 1933

Among the outstanding events of the year 1933 in radio broadcasting were: President Roosevelt's Inauguration, a world-wide broadcast on March 4th; George Bernard Shaw's talk in the United States from the Metropolitan Opera House on April 11th; the description of Wiley Post's arrival after his around-the-world flight on July 22nd; the two-way conversation of Maxim Litvinoff from the White House to his wife in Moscow, November 17th; the Settle-Fordney broadcast from the stratosphere, November 20th, and the Christmas greetings from King George, which were short-waved around the earth on December 25th. There are others which have slipped my memory, but the foregoing were wonderful enough. . . .

LET'S ALL HOPE

I am writing this on New Year's Eve. I can't go out to a party because I'm on the air twice on New Year's Day—at ten a.m. over WEAJ and 2:15 p.m. over WOR. So my New Year's Eve consists of just listening to the dancing parties being broadcast for somebody else to dance—and sitting at a typewriter pounding this out for you to read. But I don't mind; the main thing is to work on New Year's Day, which is quite a superstition among theatrical folk; they say if you work and make money on New Year's Day you'll do the same thing all the year round, and here's hoping we all do just that!

Using 2A3 to Best Advantage in Push-Pull

(Continued from preceding page)

are designed for use with typical commercial power transformers. There are no special features involved in the design of the power transformer. Any make of transformer having the appropriate voltage windings, correct rating, and good regulation may be used.

Pre-Amplifier Stage

A type 56 tube is used in the pre-amplifier stage, since this tube gives excellent power sensitivity. The 56 also is an economical type.

A plate-supply voltage of 200 volts for the 56 is adequate to give the output signal required to swing the 2A3's. This is the voltage available for plate supply to the other tubes in the set under conditions given in Figs. 1 and 2. The 56, with 20-volt plate supply, is operated with a bias of minus 11 volts. The plate current is 3.6 milliamperes.

The same input transformer, specifications for which are given later, is used for both the semi-fixed and fixed-bias arrangements. Commercial-size audio-transformer laminations are used.

The ratio of the input transformer is 1.4 to 1 from the full primary winding to one-half of the secondary winding. The peak voltage which will be induced in the secondary winding is 2x90 or 180 volts at the point at which the 56 begins to draw grid current.

In determining the constants for the input transformer, cost, size, response characteristics, and signal requirements must be considered. In order to obtain a low-cost small-size transformer with primary inductance high enough to give good frequency characteristics, a step-down ratio is used. A step-up ratio would require a larger transformer design in order to provide space for the additional secondary turns. However, under the circuit conditions shown, the step-down ratio can give a signal input to the 2A3's sufficiently large to obtain their full output.

Transformer Specifications

POWER TRANSFORMER S-79A*

Core:
Material—Transformer Steel, Allegheny Steel Co. or equivalent
Punching—EI-13A
Stack—1¾" Weight—4.9 lbs.

Primary
Resistance—2.4 ohms

Secondary
Resistance at 25°C.—2x106 ohms
Induced voltage—2x375 volts RMS
Induced voltage from center tap to tap for bias rectifier—approx. 57 v. RMS.
Total weights of copper—1.0 lb.

INPUT TRANSFORMER S-77*

Core:
Material—Audio B, Allegheny Steel Co. or equivalent
Punching—EI-75
Joint—Butt
Stack—¾" Weight—0.6 lb.

Primary:
Turns—5000
Location—Between two halves of secondary winding

Turns per layer—240 Layers—21
Insulation between layers—0.001" paper
Wire—No. 40 enamelled
Resistance at 25°C.—2000 ohms

Secondary:
Turns—Two windings of 3,600 turns each
Location—One-half over, one-half under primary
Turns per layer—240
Layers—2x15
Insulation between layers—0.001" paper
Wire—No. 40 enamelled
Total weights of copper—0.14 lb.

CHOKE S-26*

Core:
Material—Dynamo Steel—Allegheny Steel Co. or equivalent
Punchings—EI-12
Air gap—0.004" x 2
Stack—1¼" Weight—1.88 lbs.

Winding:
Turns—1780 Turns per inch—81
Layers—22
Insulation between layers—0.003" paper
Resistance at 25°C.—approx. 60 ohms
Weight of copper—0.47 lb.
Inductance—approx. 10 henries (conditions as in Fig. 2)

Westinghouse's Chief Confident of Ultimate Prosperity for Industry

By A. W. Robertson
Chairman, Westinghouse Electric & Manufacturing Company

The United States Government is spending three billion, three hundred million dollars on public works. In 1932 the American people, at the bottom of the depression, spent approximately four hundred billion dollars. These figures are startling.

We see how much more important individual and corporate spending is than Governmental spending. A 10% increase in what the consumer, corporate and individual, spends would amount to forty billions of dollars, or more than ten times the amount the Government is spending on public works. A comparison of this nature shows definitely that the normal exchange of goods and services by persons and corporations is the base upon which business and business recovery must rest. Government cannot by spending or by law create good business. It can feed us and clothe us, perhaps, for a time but it cannot legislate prosperity.

As far as the electrical industry is concerned, it faces the new order confidently. Its resources have been conserved, its technical progress has been uninterrupted, research has discovered many new uses for electricity and new devices have been developed for its utilization.

When capital goods business finally yields to the many forces now being exerted for its improvement, the electrical industry cannot fail to benefit and again resume its rightful place as one of our most essential and most prosperous industries.

Copper Oxide Disc Is Sensitive to Light

A layer of copper oxide on a copper disc has some unusual and interesting properties. Many of us are familiar with the Rectox or copper oxide rectifier which has been widely used for several years. The Photox might be called the cousin of the Rectox. It too is a copper disc with a coating of oxide but instead of rectifying it acts as a tiny primary battery when light strikes its surface. The current generated is measured in micro-amperes but is sufficient to be extremely useful.

The current output is directly proportional to the intensity of the light which strikes it and retains this property indefinitely. Its response to colored light is another interesting characteristic. The response is almost exactly the same as that of the human eye. A colored light which seems bright to the eye seems bright to the Photox. It has become the basis of the light intensity meter and the transparency meter (transometer).

OUTPUT TRANSFORMER S-84*

Core:
Material—Audio C, Allegheny Steel Co. or equivalent
Punching—EI-11
Stack—¾" Joint—Lap
Weight—1.0 lb.

Primary:
Wire—No. 32 enamelled
Turns—1400 tapped at 700
Location—Next to core
Turns per layer—105
Layers—14
Insulation between layers—0.0015" paper
Resistance at 25°C.—98 ohms

Secondary:
Turns—No. 32
Location—Wound over insulated primary
Wire—No. 15 enamelled
Turns per layer—16 Layers—2
Insulation between layers—0.005" paper
Secondary load—Voice coil of electro-dynamic speaker having an impedance at 60 cycles of 1.06 ohms

New Surge Limiters and Indicators of Modulation Impending

Plant managers of KYW, Chicago, and other Westinghouse stations met at Chicopee Falls, Mass., to discuss changes in operating procedures and problems arising from operation under the code of fair competition for the Broadcasting Industry.

The group visited the WBZA transmitter in East Springfield, which has just recently been remodeled, and the transmitter and studios of WBZ, which has been granted permission to operate on 50 kw. In Hartford the group visited WTIC and met its engineers and also representatives of the Travelers Insurance Company to discuss safety measures. A trip was made through the Radio Division plant at Chicopee Falls.

Business discussed included the design of new apparatus to be manufactured for stations. Surge limiters and modulation indicators of a novel design are soon to be installed at the stations to allow higher percentage modulation without distortion.

Hanson Inspects NBC

O. B. Hanson, manager of technical operations and engineering for the National Broadcasting Company, New York, is inspecting the various NBC division headquarters in San Francisco.

As he had been in charge of the designing and construction of the studios in Radio City, Hanson had not been able to make his usual annual tour of inspection for the past three years.

Hanson will inspect the new 50,000-watt transmitter at KPO, San Francisco, and the 50,000-watt which is under construction at KOA, Denver. He also will inspect NBC division headquarters in Chicago and Cleveland.

Hanson has between 500 and 600 radio engineers under his direction.

New Portable Oscillograph

A new portable oscillograph by Westinghouse compares in size and sturdiness with portable instruments. It measures 11½" x 11" x 8", weighs 22 lbs., requires no external auxiliaries and operates from a 110 volt lighting circuit. While it fills a need for a simple low-cost unit it does not replace the more expensive and complete equipment.

A ray of light passes through a new optical system which permits viewing and photographing at the same time and which magnifies the galvanometer deflection. The 2½" x 3½" viewing screen shows a brilliant trace which is clearly seen even in broad daylight and photographing a wave form is much the same as taking a picture with an ordinary camera. A standard Graflex film, 2¼" x 3¼" is used for photographic purposes.

OUTPUT TRANSFORMER S-105*

Core:
Material—Audio C—Allegheny Steel Co. or equivalent
Stack—0.875" Joint—Lap
Weight—1.0 lb.

Primary:
Turns—2000 tapped at 1000
Location—Next to core Wire—No. 33 enamelled
Turns per layer—118 Layers—17
Insulation between layers—0.0015" paper
Resistance at 25°C.—172 ohms total
Inductance—195 henries (at full signal)

Secondary:
Location—Wound over primary
Turns = 2000 divided by the square root of [5400/(R₁ + r₂)]
where,
R₁ = external load resistance on secondary terminals
r₂ = resistance of secondary winding or approx. 6% of R₁
Resistance at 25°C.—0.053 ohms
Output—13.3 watts into a 1.06-ohm load at 60 cycles
Total weight of copper = 0.24 lb.
(Copyright 1933)

*Our design, identification number.

175 KC TUNING UNIT FREE WITH SUBSCRIPTION

For use with 175 kc intermediate frequency. Unit includes four-gang condenser, three r-f coils, the proper oscillator inductance and 800-1,350 mmfd. padding condenser. Send \$12.00 for two-year subscription and order Cat. SUTU-175, which will be sent postpaid.

Radio World
145 West 45th Street
New York City

Vest Pocket Size Flashlight for Radio Repair Work— FREE

Great for getting right down into your set!

Obtain one free with 3 months' subscription for Radio World at the regular rate of \$1.50. Send postpaid.

Sub. Dept.
RADIO WORLD
145 West 45th Street New York, N. Y.

Quick-Action Classified Advertisements

7¢ a Word—\$1.00 Minimum

DEALERS, SERVICE MEN AND AGENTS. Latest Crusader Midget Radios, \$5.85. Write for full particulars. Chicago Radio Distributors, 1325 S. Michigan, Dept. 22, Chicago.

RED HOT RADIO SERVICE IDEA. Will bring business. Only one to territory! \$1.00 postpaid. F. Deming, 1233 No. 42nd St., Lincoln, Nebr.

"AUTOMOBILE REFINISHING," by C. E. Packer, Member of S.A.E. For the car owner and professional refinisher. A practical handbook on the materials, methods and equipment used. 148 pages, 41 illustrations. Price \$1.50. **RADIO WORLD**, 145 W. 45th St., New York City.

"THE FORD V-EIGHT-B-FOUR-BB-TRUCK," by C. B. Manly. A New and Practical Book for Everyone Interested in the Construction, Adjustment, Upkeep and Repair of The New Fords. Over 250 pages, 125 illustrations. Complete cross index. Pocket size, flexible leatherette cover. Price \$2.00. **Radio World**, 145 W. 45th St., New York, N. Y.

MODERN TUBE INDEX, all tubes, all the dope, all manufacturers, socket connections, everything. Most complete of all. Sheet 21 x 27 inches. Price 25c. **RADIO WORLD**, 145 West 45th Street, New York, N. Y.

"THE CHEVROLET SIX CAR AND TRUCK" (Construction—Operation—Repair) by Victor W. Page, author of "Modern Gasoline Automobile," "Ford Model A Car and AA Truck," etc., etc. 450 pages, price \$2.00. **Radio World**, 145 W. 45th St., N. Y. City.

"MODERN ELECTRIC AND GAS REFRIGERATION," by A. D. Althouse and C. H. Turnquist. A timely book of practical and usable information on installation, service, repair of all types of automatic refrigerators. 275 pages, 175 illustrations, diagrams in six and eight colors. Price \$4.00. **RADIO WORLD**, 145 W. 45th St., New York City

"RADIO TROUBLE SHOOTING," Second Edition, by E. R. Haan. Contains the latest on A.C. receivers, dynamic speakers and television. A practical book for practical men. Contains a special chart showing all possible radio troubles and the way to detect them. Size 6 x 9 inches. 361 pages, 300 illustrations. Flexible binding. Price \$3.00. **RADIO WORLD**, 145 W. 45th St., New York City.

Valuable Gifts with Subscriptions for RADIO WORLD

A NEW TEST OSCILLATOR That Works A.C., D.C., or Batteries!

SHOWN ONE-THIRD
ACTUAL SIZE



A NEW TEST oscillator, Model 30, has been produced by Herman Bernard, so that all the requirements for lining up broadcast receivers, both tuned radio frequency and superheterodyne types, will be fully and accurately met. This device may be connected to 90-120-v a.c., any commercial frequency, without regard to polarity of the plug, and will function perfectly. It may be used also on 90-120-volt d.c. line, but plug polarity must be observed. One of the plug prongs has a red spot, denoting the side to be connected to positive of the line. If you don't know the d.c. line polarity, you may connect either way, without danger. The oscillator will work on d.c. only when the connection is made the right way. Moreover, 90 volts of B battery may be used instead of either of the foregoing, simply by connecting two wires between the plug at the batteries, observing polarity. No separate filament excitation is required. The oscillator is modulated with a strong, low note under all circumstances. It uses a 30 tube.

THE dial of the Bernard Model 30 Test Oscillator is directly calibrated in kilocycles, so there is no awkward necessity of consulting a chart. The fundamental frequencies are 135 to 380 kc, so that nearly all commercial intermediate frequencies as used in present-day superheterodynes are read on the fundamental. The points for other intermediate frequencies, e.g., 400, 450, 450 and 465 kc, are registered on the dial also, two harmonics, with which the user need not concern himself, being the basis of these registrations. Besides, the broadcast band is taken care of by the fourth harmonic and the dial is calibrated for that band, also. The divisions on the dial for the fundamental band, 135 to 380 kc, are 1 kc apart from 135 to 140 kc, 2 kc apart for 140 to 180 kc and 5 kc apart for 180 to 380 kc. For the broadcast band, 10 kc apart from 550 to 800 kc, 20 kc apart from 800 to 1,500 kc. The test oscillator may be used also for short waves, by resorting to higher harmonics.

Over-All
Size
Is Only
5x5x3"!
Dial
Reads
Frequencies
Directly!

Send \$12 for 2-year subscription for RADIO WORLD and order Cat. BO-30 sent free, with tube (prepaid in United States and Canada). Another model, BO-30-S, same as above, except frequencies are ten times as high, hence instrument is for short-wave work only, is available on same basis.

THE ONLY BOOK OF ITS KIND IN THE WORLD. "The Inductance Authority" Entirely dispenses with any and all computation for the construction of solenoid coils for tuning with variable or fixed condensers of any capacity, covering from ultra frequencies to the borderline of audio frequencies. All one has to do is to read the charts. Accuracy to 1 per cent. may be attained. It is the first time that any system dispensing with computation has achieved such very high accuracy and at the same time covered such a wide band of frequencies.

"The Inductance Authority" E

ACH turns chart for a given wire has a separate curve for each of the thirteen form diameters. The two other charts are the tri-relationship one and a frequency-ratio chart, which gives the frequency ratio of tuning with any inductance, when using any condenser the maximum and minimum capacities of which are known.

By EDWARD M. SHIEPE, B.S., M.E.E.

There are ten pages of textual discussion by Mr. Shiepe, graduate of the Massachusetts Institute of Technology and of the Polytechnic Institute of Brooklyn, in which the considerations for accuracy in attaining inductive values are set forth. These include original methods.

A condensed chart in the book itself gives the relationship between frequency, capacity and inductance, while a much larger chart, issued as a supplement with the book, at no extra charge, gives the same information, although covering a wider range, and the "curves" are straight lines. The condensed chart is in the book so that when one has the book with him away from home or laboratory he still has sufficient information for everyday work, while the supplement, 18 x 20 inches, is preferable for the most exacting demands of accuracy and wide frequency coverage.

The book contains all the necessary information to give the final word on coil construction to service men engaged in replacement work, home experimenters, short-wave enthusiasts, amateurs, engineers, teachers, students, etc.

From the tri-relationship chart (either one), the required inductance value is read, since frequency and capacity are known by the constant. The size and insulation of wire, as well as the diameter of the tubing on which the coil is to be wound, are selected by the user, and by referring to turns charts for such wires the number of turns on a particular diameter for the desired inductance is ascertained.

The curves are for close-wound inductances, but the text includes information on correction factors for use of spaced winding, as well as for inclusion of the coils in shields. The book therefore covers the field fully and surpasses in its accuracy any and all mechanical aids to obtaining inductance values.

There are thirty-eight charts, of which thirty-six cover the numbers of turns and inductive results for the various wire sizes used in commercial practice (Nos. 14 to 32), as well as the different types of covering (single silk, double silk, single cotton, double cotton and enamel) and diameters of $\frac{1}{8}$, $\frac{1}{16}$, $1\frac{1}{16}$, $1\frac{1}{8}$, $1\frac{1}{4}$, $1\frac{1}{2}$, $1\frac{3}{4}$, 2 , $2\frac{1}{4}$, $2\frac{1}{2}$, $2\frac{3}{4}$ and 3 inches.

The publisher considers this the most useful and practical book so far published in the radio field, in that it dispenses with the great amount of computation otherwise necessary for obtaining inductance values, and disposes of the problem with speed that sacrifices no accuracy.

The book has a flexible colored cover, the page size is 9 x 12 inches and the legibility of all curves (black lines on white field) is excellent.

Send \$4.00 for 84-week subscription for RADIO WORLD and order Cat. PIA sent free, with supplement, postpaid in United States and Canada.


RADIO WORLD

145 West 45th Street New York, N. Y.

An Extraordinary Bargain!

Three-Gang Condenser FREE with 13-week Subscription @ only \$1.50

THE highest grade commercial gang condenser made, die-cast frame, brass plates, $\frac{1}{4}$ " diameter shaft extending at both ends. Condenser can be used therefore with either direction of dial rotation. Rigidity is of highest degree. Rotors can be shifted on shaft and locked tight for peaking at high-frequency end of band, thus dispensing with trimmers. Capacity, 0.0004 mfd. Full band coverage 1,500 to 540 kc (and more) with coils intended for 0.00035 to 0.00041 mfd. Premium sent express collect (shipping weight 5 lbs.) on receipt of \$1.50 for 13 weeks subscription for Radio WORLD (13 issues).

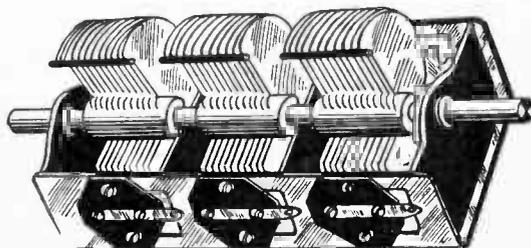

The condenser measures 4 x $8\frac{1}{2}$ inches, overall frame size; shafts extend 1 inch beyond frame.


RADIO WORLD, 145 West 45th Street, New York, N. Y.

Introducing - - -

NEW 1934 DIAMOND of the AIR

A-C OPERATED SHORT-WAVE RECEIVERS

12,500-Mile Reception

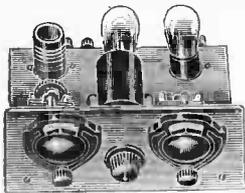


2-TUBE

Introducing the latest in short-wave receivers. The "Diamond of the Air" 2- and 3-tube battery receivers for many months have been acclaimed by owners to be the most remarkable short-wave receivers in their class. Now, for the first time, Reliable Radio Company introduces the 1934 A-C SHORT-WAVE "DIAMOND"—incorporating all the features of the battery-operated sets plus the convenience of a-c operation. The receivers have to be powered additionally and the power pack quotations will be found on this page.

IMPROVED RECEPTIVE QUALITIES

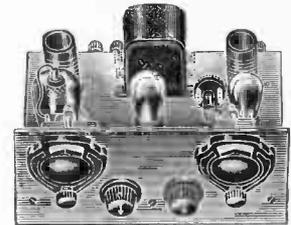All 1934 features have been incorporated in the new "Diamond of the Air" a-c short-wave receiver and, besides, the popular battery-operated models have been improved in a new 1934 design. The lowest in price, yet these sets will log stations from all parts of the world regularly.



3-TUBE

The 3-tube a-c receiver uses a 58 as an r-f amplifier, followed by a 57 detector and a 56 as an output tube. This receiver can be used on batteries by using 77, 78 and 37 tubes as detailed above. Capable of logging stations from all parts of the world.

Employs the Highest-Grade Materials

A receiver is only as good as the parts used in its construction. Only the finest parts are included. Hammarlund condensers, representing the finest, are used. The metal panel eliminates body capacity.

The A-C "Diamond of the Air" Receivers

The a-c receivers have been developed for those who have the benefit of electric service. They use the latest type triode-grid tubes, resulting in more selective and sensitive reception.

The 2-tube model employs a 57 tube, resistance coupled to a 56 type output tube. For those desiring to use this receiver on batteries, simply replace the 57 type tube with a 77 and the 56 tube with a 37, for heater excitation from a 6-volt storage battery and use B batteries for plates. Loudspeaker reception on all local and many distant stations.

DIAMOND OF THE AIR

Battery-Operated Short-Wave Receivers

The battery-operated receivers employ the 2-volt low-current tubes, saving considerable expense to those living in districts where no a-c is available. The two-tube model uses two 30 tubes. Especially designed for headphone reception, although loudspeaker reception may be obtained at ordinary room volume.

The 3-tube two-volt model employs one 34 and two 30 tubes. It will receive short-wave stations from all parts of the globe on a loudspeaker.

Electric Models

- Cat. No. 5025-D. Two-tube A-C kit, with blueprint. Shipping weight, 5 lbs. \$8.45
- Cat. No. 5026-D. Above, wired and tested. Shipping weight, 5 lbs. 9.45
- Cat. No. 5027-D. Complete set of tubes for above, either one 57 and one 56 for a-c operation or one 77 and one 37 for battery operation. Specify which. Shipping weight, 2 lbs. 1.45
- Cat. No. 5028-D. Three-tube a-c kit, with blueprint. Shipping weight, 7 lbs. 11.45


- Cat. No. 5029-D. Above, wired and tested. Shipping weight, 7 lbs. 13.45
- Cat. No. 5030-D. Complete set of tubes, either one 58, one 57 and one 56 for a-c operation or one 78, one 77 and one 37 for battery operation. Specify which 2.45

Two-Volt Battery Models

- Cat. 5019-D. Two-tube kit, with blueprint, less accessories listed below. Shipping weight, 5 lbs. \$7.75
- Cat. No. 5020-D. Above, wired and tested, less accessories listed below. Shipping weight, 5 lbs. 8.75
- Cat. No. 5021-D. Complete accessories including two 230 tubes, one set of standard headphones, two No. 6 dry cells, two standard 45-volt B batteries. Shipping weight, 22 lbs. 4.50
- Cat. No. 5022-D. Three-tube kit, with blueprint, less accessories listed below. Shipping weight, 7 lbs. 9.95
- Cat. No. 5023-D. Above, wired and tested, less accessories listed below. Shipping weight, 7 lbs. 10.95
- Cat. No. 5024-D. Complete accessories, including two 30 tubes and one 34 tube, one set of standard headphones, two No. 6 dry cells, three standard 45-volt B batteries, one 6-inch magnetic speaker. Shipping weight, 32 lbs. 8.95

DIAMOND of the AIR SHORT-WAVE

POWER PACK

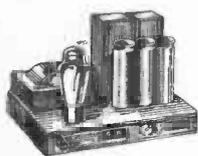

Supplies clear hum-free power regardless of circuit sensitivity. Especially designed for use with the "Diamond of the Air" Short-Wave receivers, but can be

used on any short-wave battery-operated receiver for B supply.


Contains a brute-force filter, employing two heavy-duty 30-henry chokes, specially-designed power transformer, and three electrolytic condensers. These factors assure pure d.c.

Will deliver 180 volts. Supply your own taps. 135, 90 and 45 volts. Supplies 2½ volts at 10 amperes for filament drain. All taps terminate at binding posts on the side of the pack. Employs an 80 rectifier. Will stand up to 75 ma. drain for B current.

All parts are mounted on a sturdy metal base finished in silver.

- Cat. DAPP. Price, including 80 tube \$5.95

Shipping Weight, 20 Lbs.

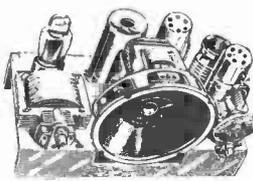

Four-Tube A-C Short-Wave Receiver with Built-In Speaker

Will tune in short-wave stations from all parts of the world with ease. Uses four plug-in coils to cover the entire short-wave band from 15 to 200 meters. The built-in power supply is entirely free from hum or disturbing line noises. Uses an ultra-sensitive dynamic speaker which aids in tuning in the weaker signals.

- Cat. 4TK. Kit of Parts, less cabinet, less tubes \$11.50
- Cat. 4TW. Above, completely wired and tested \$13.75
- Cat. 4TCB. Cabinet only... \$1.50 extra
- Cat. 4TTU. Complete set of licensed tubes \$2.50 extra

Reliable Radio Company

145 West 45th Street
NEW YORK CITY



For A-C and D-C Operation

Will work anywhere that 110 volt A-C or D-C is available. U. S. amateur reception is assured on loudspeaker by the use of a 43 power tube in the output.

With headphones the entire world is at your finger-tips. Chassis is completely encased in a beautiful crystal finished cabinet. Covers the short wave, band from 15-200 meters. Uses one 78, one 25Z5 and one 43 tube.

- Price Kit \$8.95
- Wired \$2.00 extra. Tubes \$3.25

FREE
HANDY SERVICEMEN'S
MANUAL
WITH EACH PURCHASE OF
A SHORT-WAVE RECEIVER



ALL SHIPMENTS MADE EXPRESS COLLECT UNLESS OTHERWISE DIRECTED BY PURCHASER