

It's Not Only Quiet



It's SILENT!

Patent applied for



You Can't Hear It!

and of course . . . It's a

YAXLEY

**Replacement
Volume Control**

Perfect Smooth Taper.



*Pure Silver Shortcuts
for Switch Action.*



*New Spring Wedge
Prevents Loose Terminals.*



Silent—soundless—you can't hear it—here's the answer to the Serviceman's prayer. Mallory-Yaxley has perfected the universal SILENT Replacement Control—and that's news you have been waiting to hear about volume controls for a long time.

The roller that doesn't roll holds the secret of silent, velvety smooth operation. With it goes a track with an exclusive Mallory-Yaxley compound (with twice the wear) that permits no hard, thin surface as on ordinary track. It means perfect, soundless contact; complete prevention of noise-making dust and dirt; with absolute electrical and mechanical smoothness.

Silver to silver contacts eliminate corrosion. Silver shortcuts for switch action. Perfect smooth tapers. Low humidity and low temperature coefficients; no need to fear "damp spots" or "hot spots." Uniform characteristics. Long life. New spring wedge avoids possibility of loose terminals. Equipped with the famous Yaxley attachable switch and other exclusive universal features.

You'll want Yaxley Silent Replacement Volume Controls for every service requirement. If you haven't tried them yet, get after your distributor today. Just say—"I want a Yaxley Silent."

YAXLEY MANUFACTURING DIVISION


of P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA

Cable Address—PELMALLO

MALLORY

YAXLEY

What to do and how to do it . . .

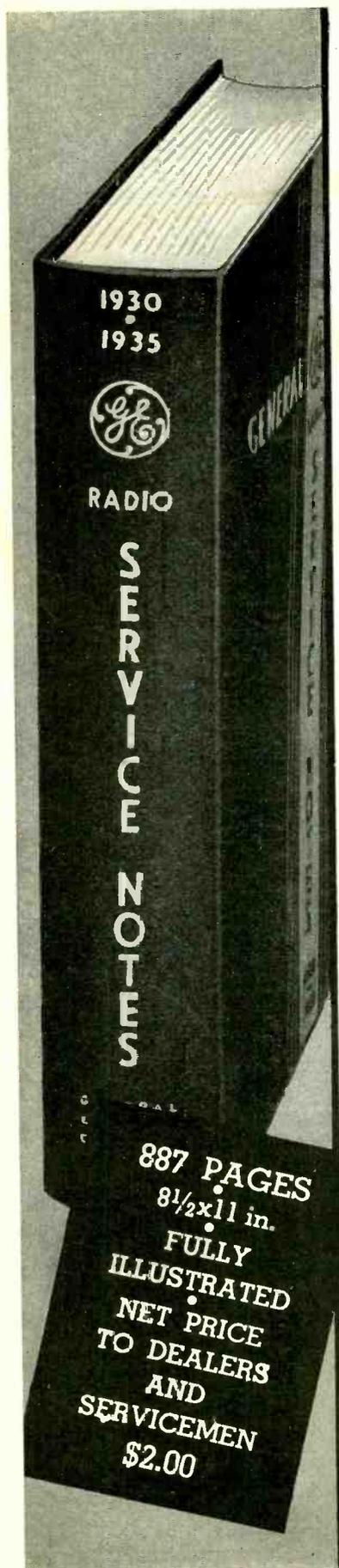

The radio service man who wishes to thrive in his highly competitive business must have adequate service data right at his finger tips, so that he can do his work quickly, accurately . . . economically for the radio set owner . . . and profitably for himself. To this end, General Electric has released a new Bound Volume —

GENERAL ELECTRIC RADIO SERVICE NOTES 1930-1935

From every page of this practical new volume, the alert service man will secure sound instruction and valuable service information on all radio receivers sold by General Electric during the past six years . . . 1930-31-32-33-34-35. This new book also contains a cross-index to certain comparable models of other manufacturers made during the same years.

PARTIAL LIST OF SUBJECTS COVERED


- | | |
|--------------------------------------|--|
| Electrical & Physical Specifications | Recording and Microphone Data |
| Descriptions of Electrical Circuits | Microphone Service Data |
| Schematic Circuit Diagrams | Automatic Record Changer Service Data |
| Chassis Wiring Diagrams | Phonograph Motor Service Data |
| Radiotron Socket Voltages | Remote Control Service Data |
| Locations of Line-up Capacitors | Test Oscillator Data |
| Line-up Procedure | Short-wave Adapters and Converters |
| Continuity Tests | Interference Suppression |
| Condenser Drive Cord Arrangements | Frequency vs. Impedance Chart |
| Line Voltage Adjustments | Inductance vs. Capacity Chart |
| Loudspeaker Wiring | Decibel Chart and Instructions |
| Speaker Cone Alignment | Radiotron Data, Symbols and Socket Connections |
| Auto Radio Installation | Antenna Data |
| Vibrator Service Data | Wave Trap Data |
| Checking with Tuning Wand | Short-wave Reception Notes |
| Replacement Parts and Prices | Station Logs |
| Phonograph Pickup Service Data | |

General Electric's Bound Volume of 1930-35 RADIO SERVICE NOTES gives you a practical and helpful "brass-tack" manual on how to correctly service and replace parts in over 350 radio receivers . . . PLUS considerable extra data applicable to all makes of receivers.

You can purchase the bound volume of GENERAL ELECTRIC RADIO SERVICE NOTES for 1930-1935 direct from your local G-E Radio Distributor.

GENERAL ELECTRIC

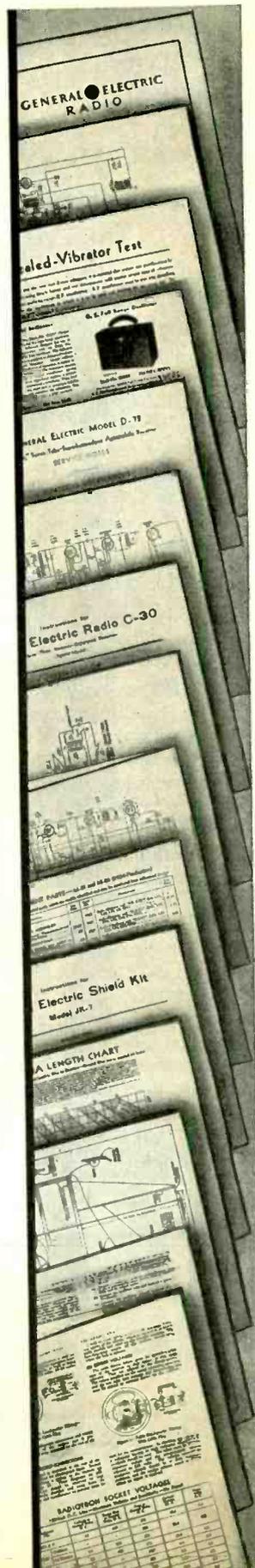Appliance and Merchandise Department
Bridgeport, Connecticut



SERVICE

A Monthly Digest of Radio and Allied Maintenance

Reg. U. S. Patent Office. Member, Audit Bureau of Circulations

NOVEMBER, 1936

EDITOR
Robert G. Herzog

VOL. 5, NO. 11

EDITORIAL CONTENTS

FEATURES

Automatic Frequency Control <i>By Hubert R. Shaw</i>	548
Complete Volume Expansion <i>By C. M. Sinnett</i>	572
Improving Old Power Supplies.....	547
Looking for Trouble <i>By R. M. Purinton</i>	541
Triplett 1240 Condenser Checker.....	578

ANTENNA	534
---------------	-----

ASSOCIATION NEWS	586
------------------------	-----

AUTO RADIO	
Studebaker Philco S-1431.....	567
Wells Gardner 6K.....	568

CIRCUITS	
A Simple Second Detector Stage.....	543
A Typical T-R-F Stage.....	541
An I-F Amplifier Stage.....	543
Breakdown Test Circuit.....	578
Capacity Test Circuit.....	578
Complete AFC Circuit.....	548
Complete Volume Expansion Circuit..Front Cover	
Crosley Model 1016.....	561
Fairbanks-Morse 100.....	555
General Electric E-81 and E-86.....	552
Power Supply Circuits.....	547
RCA Victor R-99 High-Fidelity Phonograph.....	572
Sentinel-Erla 53A.....	551
Stewart-Warner R-149.....	559
Stromberg Carlson Service Change.....	584
Studebaker Philco S-1431 Auto Radio.....	567
Superheterodyne Mixer Stage.....	543
The Campbell Hum Balance Circuit.....	574
Transformer Circuit Triplett 1240.....	578
Triplett 1240 Condenser Checker.....	580
Typical Output Stage.....	544
Wells Gardner 6K.....	568

GENERAL DATA

Automatic Frequency Control <i>By Hubert R. Shaw</i>	548
Color-Coded Resistors and Condensers <i>By J. N. Golten</i>	576
Complete Volume Expansion <i>By C. M. Sinnett</i>	572
Crosley Model 1016.....	561
Fairbanks-Morse 100.....	554
General Electric E-81 and E-86.....	550
Improving Old Power Supplies.....	547
Looking for Trouble <i>By R. M. Purinton</i>	541
Sentinel-Erla 53A.....	550
Stewart-Warner R-149.....	558
Stromberg Carlson Service Notes.....	544
Technical Features of Bosch 1937 Radio Receivers	557
The Campbell Hum Balance.....	574

HIGHLIGHTS	588
------------------	-----

MANUFACTURERS	590-592-594
---------------------	-------------

ON THE JOB

Color-Coded Resistors and Condensers <i>By J. N. Golten</i>	576
Keeping Lapel Microphone in Place.....	576
Using 226 Power Transformers.....	576
Radio Rotors <i>By Eugene Triman</i>	576

PUBLIC ADDRESS

Complete Volume Expansion <i>By C. M. Sinnett</i>	572
--	-----

RECEIVER CASE HISTORIES.....	582-584
------------------------------	---------

TEST EQUIPMENT

Triplett 1240 Condenser Checker.....	578
--------------------------------------	-----

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.
Telephone: Wabash 1903

Wellington, New Zealand—Tearo Book Depot.

Published Monthly by the

Bryan Davis Publishing Co., Inc.

19 East 47th Street

New York City

Telephone: Plaza 3-0483

SANFORD R. COWAN
Advertising Manager

PAUL S. WEIL
*Eastern Advertising
Manager*


A. B. CARLSEN
Circulation Manager

Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.
Telephone: Republic 0905-J

Melbourne, Australia—McGill's Agency.



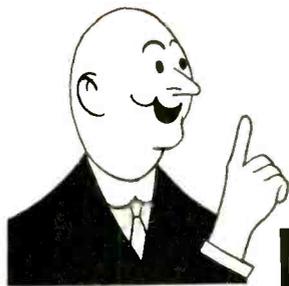Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.



... and let me tell you a few things about this "PRECISION" ELECTRONOMETER

No. 600

FIRST: The new No. 600 Electronometer is a complete modern tube analyzer combined with adequate volts, current and resistance measurements for point to point set testing. . . . Compact in size (12 x 12 x 6), weighs only 12 pounds, and is ruggedly built to withstand rough usage.

SECOND: Accuracy, simplicity, ease and speed for obtaining tube or set analyses, is the keynote of this instrument. No side gadgets to be considered or remembered when obtaining the various tests.

THIRD: It is entirely automatic in operation. For tube analyzing, simply set controls as indicated on the data chart for the tube to be tested. For set testing, a rotary switch selects the desired measurement and pin jacks are employed to select the various ranges. Instructions, although furnished, are almost unnecessary.

FOURTH: Tube analyzing is accomplished with the most advanced engineering principles. . . . Properly rated loads applied; each section of multi-element tubes such as full wave rectifiers, twin triodes, triode diodes, pentode diodes, duo diodes, pentode triodes and frequency converters can be *individually* checked; neon method hot cathode leakage detection; hot neon point to point inter-electrode leakage and short tests between any elements within the tube for detecting noisy and fading conditions; micro line adjustment can be obtained and is shown directly on the meter.

FIFTH: The most important set analyses features have been included in the No. 600 Electronometer: Four D.C. voltage ranges 0-10; 0-100; 0-500; 0-1000 at 1000 ohms per volt. Three D.C. current ranges 0-1; 0-10; 0-100. Three resistance ranges 0-2500; 0-250,000; 0-2½ megs; one scale with large easy reading numerals; center low ohms scale, 35 ohms; readings as low as ½ of an ohm can be obtained; self-contained power supply. Qualitative paper condenser tests available. Provision for measuring leakages of electrolytic condensers in terms of current leakage per microfarad.

SIXTH: Extreme flexibility for future tube releases is provided by means of a group of individual switches giving a complete FREE POINT TUBE ANALYSIS SYSTEM. Each of these switches is connected to the various prong positions of the sockets permitting an arrangement whereby any combination of electrodes desired may be connected to obtain complete tests of various tube elements regardless of electrode pin positions. This method amply affords a means of accommodating future releases without the necessity of wiring. Instructions furnished explain in detail how test limits for future tube releases can very easily be adapted to the tube chart.



Here's an instrument that makes radio men everywhere say, "I'm extremely satisfied in every way with your No. 600 Electronometer" . . . and you'll say so, too! Or, it doesn't cost you a single penny. Go to your nearest distributor—purchase it—and if within two weeks you don't think it's the finest instrument in its class that can be bought for the price, then return it for an unconditional refund.

DISTRIBUTORS: The Precision Apparatus Corporation will stand behind the statement made in the above paragraph.

. . . and it's only \$45.75

SEE IT AT YOUR LOCAL DISTRIBUTOR OR WRITE TO FACTORY FOR DETAILS

PRECISION


Apparatus Corporation

821 EAST NEW YORK AVENUE, BROOKLYN, N. Y.

Give It A Full Test



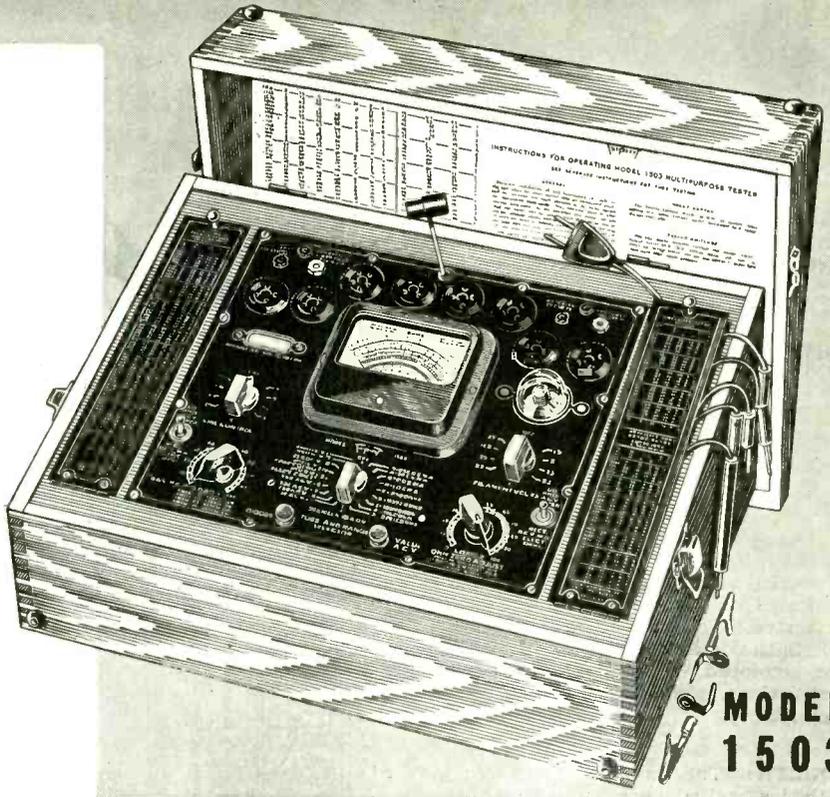Normally the function of most tubes is to amplify a signal. But when tubes are required to deliver power, such as the 6F6, the amplification may test up and yet the tube may distort badly. Reason . . . weak emission . . . particularly at low frequencies. Such tubes demand both amplification and emission test, now available . . .



**MODEL
1503**

on The P.O.E. Tester

(Patented Sept. 15, 1936)



**MODEL
1502**

P.O.E. Tube Tester—tests all types tubes. Tube values are indicated on GOOD-BAD Scale. Has shadow-graph line voltage indicator. Neon inter-element short test made while tube is hot. When new tubes are released, up-to-date tube charts are provided. Complete in quartered oak case with all necessary accessories . . . Dealer Price . . . \$36.67

● Tubes in radios have three different functions: to amplify, to deliver power, to rectify.

For amplifiers (75% or more of all tubes) the power output test is absolutely the final word in determining the worth of the tube. The Power Output Test in Triplet P.O.E. Tester simulates actual operating conditions in the radio set.

For Power Tubes, the Power Output Test determines the amplification factor. The emission test determines the power handling ability. Both tests are necessary to properly analyze these tubes, available only in the P.O.E. Tester.

The function of the diode tube is to rectify. Here the emission test only is made to determine the condition of the tube. P.O.E. tests these under both voltage and current load. The proper high voltages used in the P.O.E. Tester will detect any flash overs. Model 1503 combines all the required servicing instruments in one

- | | |
|--|------------------------------------|
| 1. P.O.E. Test for All Tubes | 6. D.C. Voltmeter and Milliammeter |
| 2. Neon Short Test | 7. Ohmmeter |
| 3. Separate Diode Test | 8. A.C. Voltmeter |
| 4. Condenser Test for Shorts | 9. Decibel Meter |
| 5. Electrolytic Condenser Leakage Test | |

Complete in quartered oak case with all necessary accessories . . . Dealer Price . . . \$46.67

See Your Jobber . . . Write for Catalogue

THE
TRIPLETT ELECTRICAL INSTRUMENT CO.
1711 Harmon Drive, Bluffton, Ohio


Without obligation, please send me:
 . . . More information on Model 1503; . . . 1502.
 . . . I am also interested in . . .

Name
 Address
 City State




The BIG CONDENSER FIGHT

begins!

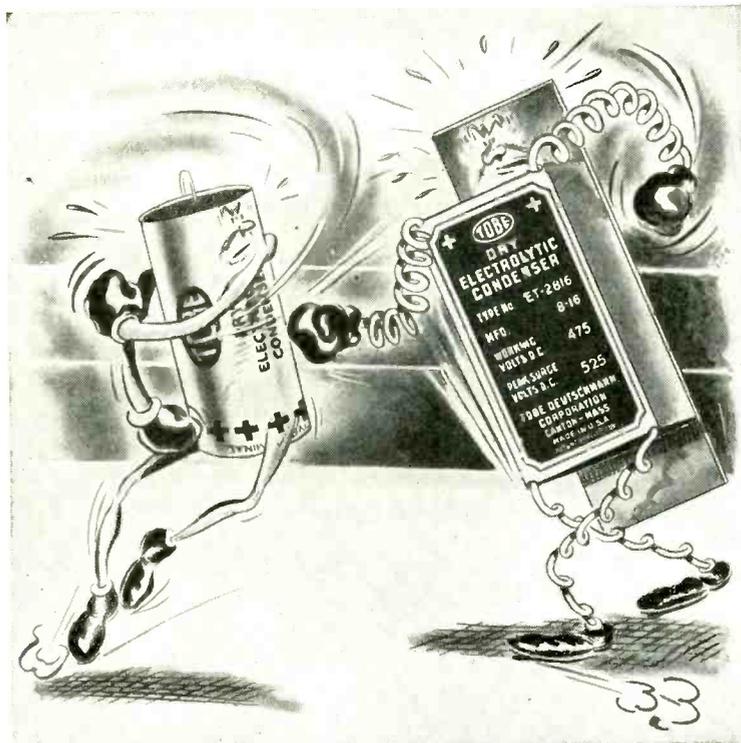

WATCH THAT TOBE FLEXIDON! HE'S LIKE TWO CONDENSERS IN ONE!

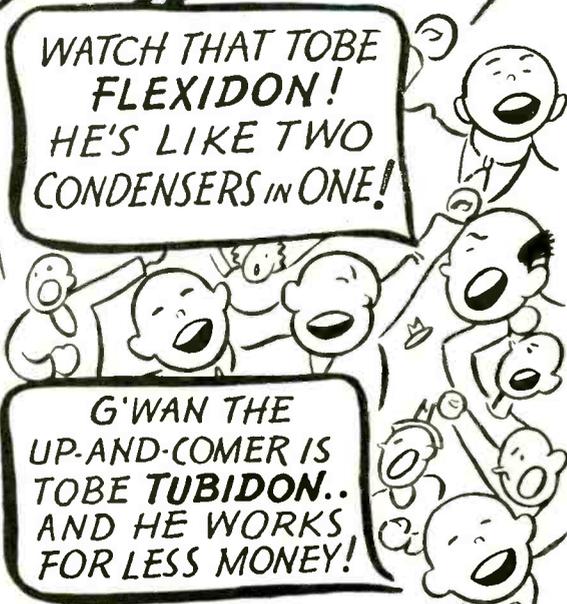G'WAN THE UP-AND-COMER IS TOBE TUBIDON.. AND HE WORKS FOR LESS MONEY!



"TOBE" TUBIDON vs "TOBE" FLEXIDON

We consider TOBE TUBIDON and TOBE FLEXIDON such ultra-fine condensers that we just can't imagine how either can lose in this big fight for condenser supremacy. But the answer is up to you ... compare their advantages: TOBE TUBIDON is tubular-shaped, up to 525 volts, self-supporting, easier to install, and *lower in cost*. TOBE FLEXIDON is rectangular-shaped, up to 525 volts, space-saving design ... with the big feature of *flexibility* (the fact that if one section breaks down, it is necessary to replace *only* the broken section.)


Which do you favor in this big battle? Note how they shape up ... read the exact specifications. Remember that *both are topnotchers* ... thoroughly moisture-proof, double-jacketed, asphalt impregnation and heavy wax seal, added protection against developing open circuit or high resistance contact ... all the features born of skillful manufacture and long experience.

SEE THE CONTESTANTS IN PERSON AT ALL GOOD RADIO JOBBERS

Ask for them by their nicknames, TOBE TUBIDON and TOBE FLEXIDON. And, if you wish to receive our complete illustrated TOBE CATALOG fill in the coupon below, and mail today.

HOW THEY SHAPE UP ...

	TUBIDON	FLEXIDON
VOLTS	35-50-200-525	200-525
MFD.	35v.—5 to 50 50v.—5 to 25 200-525v.—1 to 16	1 to 16 (single) (multiplies up to triple eight)
MAXIMUM SIZE	2-1/4" x 1"	3-1/4" x 1 3/8" x 1 1/8"
MINIMUM SIZE	2-1/4" x 1/2"	2-1/8" x 7/8" x 7/8"
TYPE LEADS	solid bare tinned copper wire	insulated tinned copper wire
LEAD LENGTHS	2-1/2"	6"
MOUNTING	self supporting by leads	metal eyeletted tabs
PRICE (typical 8 mfd.—475v.)	\$.75	\$.95

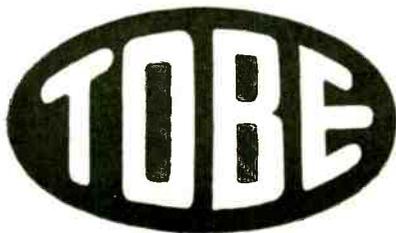

ELECTROLYTIC CONDENSERS

Skillfully Manufactured at Canton, Mass.

TOBE DEUTSCHMANN CORP.
Dept. L-10; Canton, Massachusetts

Please send FREE OF CHARGE full technical description of TOBE TUBIDON and TOBE FLEXIDON, including your complete TOBE catalog.

Name

Street

Town..... State.....

THE ANTENNA . . .

SERVICE MEN'S ASSOCIATIONS

MANY OF THE INDEPENDENT Service Men's associations spend considerable time at their meetings quibbling over constitutions, by-laws, president's powers and similar petty political details. It would seem that in such organizations, where most of the active membership is present at any given meeting, any question can be hashed out on the floor *at the time that question arises*. Written constitutions or by-laws will serve only to *limit* the group and greatly detract from the interest at the meetings.

An independent group need not be hampered with either constitution or by-laws—each bridge can be crossed as they come to it—future actions of the governing officers can be based upon previous actions unless voted otherwise by the membership. In this manner much meaningless discussion can be eliminated and more time devoted at the meetings to interesting programs—programs designed to increase the attendance at the meetings.

Such programs are not difficult to arrange. An outside speaker need not always be the order of the day. Nor is the lure of beer and hot dogs required (except as a last resort). A group of active Service Men in the middle west have what they call a technical papers committee. This committee reads all the technical publications of interest to the Service Man. Regularly, at the meetings, timely articles are brought up for discussion. In this manner the busy Service Man has the opportunity to acquaint himself with advancement in this ever growing industry.

In the same organization another committee puts into practice the numerous hints described in *SERVICE* and other magazines. This committee reports, and in many cases demonstrates, its successes to the assembled members.

Among the members of each organization there are many who could consistently offer suggestions which would draw the membership to the meetings. Ideas along these lines are definitely *not* at a premium. The most capable members of the group (those with the most practical ideas) can be appointed as the program committee and design a specific program for each meeting far enough in advance to give it sufficient publicity. Should any one idea prove more successful than the others it can be used again at intervals.

CHRISTMAS EVE MUSIC

ON THE AFTERNOON BEFORE Christmas many offices and factories stage a Christmas party for their employees. Most school teachers also have a party for their pupils. The local Service Man can earn a suitable fee by supplying the music for these parties.

A small radio receiver with a phonograph connection, the pickup and turntable and a few records would be adequate for any merry group. No more than five or six of the more recent dance selections need be necessary with one of "Stille Nacht" as an encore. Radio programs could be used in between to lend variety.

• • •

NOISELESS RECEPTION

LAST MONTH'S EDITORIAL ON noiseless reception brought an enthusiastic response from many of our readers. We refer these and other interested persons to the several manufacturers of noise-reducing equipment. Among those manufacturers who have done work in advancing the banners of noiseless reception we should like to mention: Aerovox Corporation; Cornell-Dubilier Corporation; P. R. Mallory and Company, Inc.; Solar Manufacturing Corporation; Sprague Products Company, and others who are prepared to render assistance to Service Men in this problem of noise interference elimination.

The difficulty of solving any perplexing noise-reducing problem is now no longer left entirely to the Service Man himself—information and materials for successful installations are available from all sides. It remains only for the Service Man to take advantage of the opportunities offered him.

• • •

ON OUR LECTURE TOUR

WE ARE QUITE PROUD of the warm reception given to *SERVICE* throughout the country. During our lecture tour, upon which we are still engaged, we visited Service Men in their shops and in their homes, and wherever we went they spoke of *SERVICE* in exceedingly complimentary terms. As proof of their high regard for the publication they were able to show complete files dating back to the very first issue of the magazine.

Equally complimentary is the extent to which hints, published in *SERVICE*, were found in use exactly as described in the magazine.

We thank our many readers (and listeners) and assure them that we will continue to make *SERVICE* interesting and instructive.

"EVEREADY LAYERBILT"

Presents two

RECORD - SMASHING VALUES



The Famous 486
"LAYERBILT"

at a new low price **\$1⁹⁸**



The New
"SUPER LAYERBILT"

The Longest Lasting **\$2²⁵**
"B" Battery ever offered at only

Genuine "Eveready Layerbilt" "B" batteries, famous for years for *extra long service*, now cost but a few cents more than ordinary, wasteful, short-lived, old-fashioned round-cell "B" batteries. You can now buy genuine, exclusive "Layerbilt" "B" Batteries for *less* than many makes of round-cell battery. And "Layerbilt" now gives you the new, crack-proof cushion top in addition to the advantages of patented "Layerbilt" construction.

"Layerbilt" gives you longer service because there's no waste space, and because "Layerbilt" construction permits the power-making materials to be more completely used up. For example, the active material in a round-cell battery is contained in 30 zinc cans. The zinc is eaten away to make electricity, and usually tiny holes appear in the zinc long before the battery should be used up. Air gets in, the chemicals dry out, the battery goes dead quickly, before it is used.

In "Layerbilt" batteries, the zinc plates perforate also, but no gas is admitted and no harm done. That's why long after a round-cell battery has quit, the Layerbilt goes on pouring.

Take advantage of this extra long service price.

*Here's the way we're telling your customers about these two new Evereadys—
Are you stocked?*


Standard "Eveready" Round Cell "B" Batteries

NATIONAL CARBON

General Offices: New York, N. Y.
Unit of Union Carbide

The words "Eveready" and "Layerbilt" are trade-marks of the National Carbon Co., Inc.

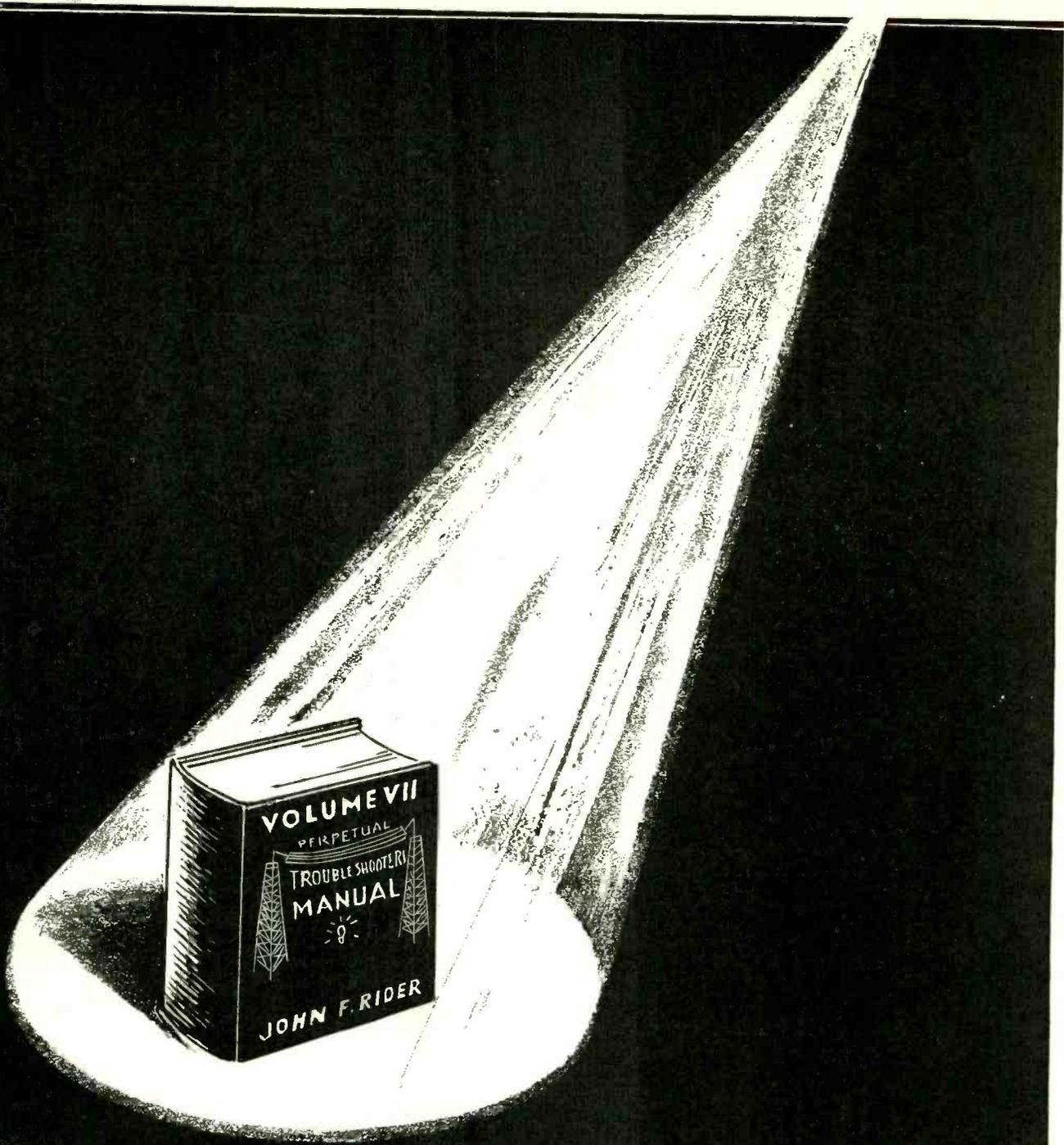Prices slightly higher in Far Western States




***NOW
AVAILABLE
AT ALL
JOBBER'S***

"The Standard by Which Others Are Judged and Valued"

AUDAX *Magneto-Inductive Pick-ups*

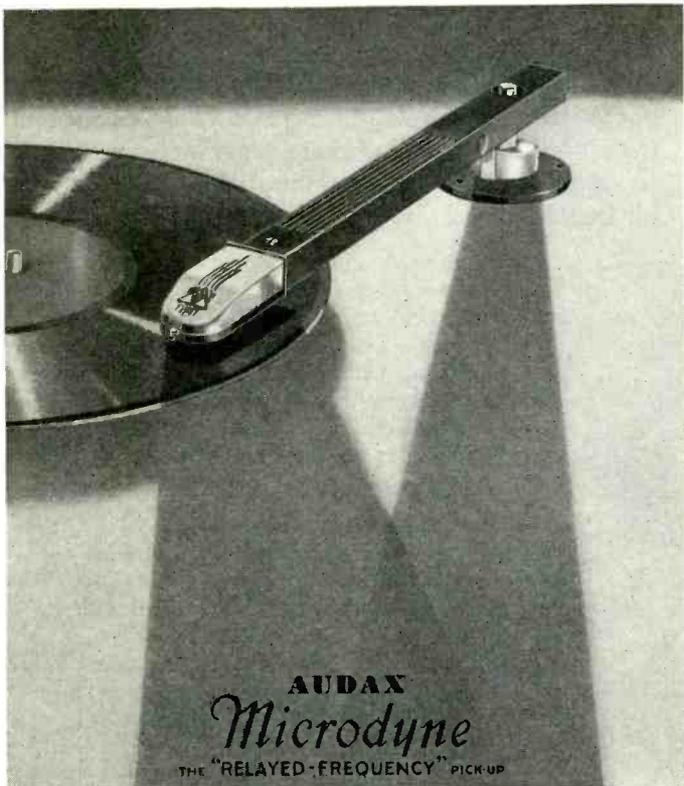Built on the time-tested, unfailing, unvarying Magneto-Induction principle . . . the identical method used in the actual making of the remarkable new high-fidelity records. Preferred by leading Universities, Radio Stations, Theatres and Sound Engineers . . . wherever SOUND must be of the very best!



AUDAX
Microdyne
THE "RELAYED-FREQUENCY" PICK-UP

A sound engineer's pick-up! The more technical and exacting the listener, the better this superfine instrument squares with his ideals. For the first time since the advent of pick-ups in 1926—here is absolute recording-microphone fidelity—uncompromising in *facsimile* performance and scientific uniformity. Yes—it's MAGNETO INDUCTIVE.

AUDAX Recording Heads

All AUDAX cutters are built on the Magneto-Induction principle as used in the actual making of Hi-Fidelity records by the foremost manufacturers. AUDAX cutters are used in leading radio stations, recording studios; wherever quality transcriptions are demanded.

Listed from \$35.00 up

An interesting new brochure—"Pick-up Facts"—is now available to the trade. Write for your copy.

AUDAX COMPANY, 500 Fifth Avenue, New York

"Creators of High Grade Electrical and Acoustical Apparatus Since 1915"

NEW MAGNETO-CHROMATIC



AUDAX PR-66

For use with records up to 18". High frequency range. Ball-bearing compound movement. Low gravity center. Remarkably fine tracking. Featherweight. Low or high impedance.

Listed at \$35.00

AUDAX HR-64

MAGNETO-CHROMATIC—Technically identical with PR-66, for use with records up to 12". Featherweight on record. Low or high impedance.

Listed at \$24.50



AUDAX HR-62

MAGNETO-CHROMATIC—Low priced model for records up to 12". Excellent frequency response. Featherweight on record. Low or high impedance.

Listed at \$15.00

UPRIGHT TYPE



AUDAX PRO Listed at \$65.00

High fidelity. Used in leading radio stations on large transcriptions (up to 18"). Frequency range covers full requirements of the finest commercial records. Special heavy gauge arm has ball-bearing compound movement. Very lightweight on the record. Low or high impedance.

AUDAX PRO-2 Listed at \$35.00

Technically identical with above model, but equipped with lighter gauge arm. For records up to 18".

AUDAX HR-38

Is identical with PRO-2 but for use with 12" records.


Listed at \$17.50

AUDAX HR-34

A lower priced model similar to HR-38.

Listed at \$12.50

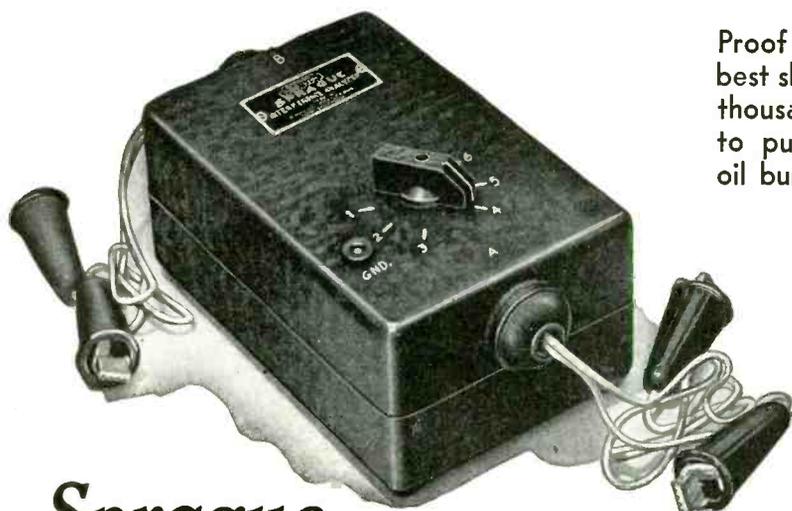SPRAGUE BRINGS YOU THE FIRST PRACTICAL, INEXPENSIVE METHOD FOR INTERFERENCE ELIMINATION



Sprague INTERFERENCE ANALYZER

... Makes it easy to eliminate all types of radio interference caused by electrical appliances, motors, etc. Also enables you to demonstrate to radio set owners just where and how radio noises originate. There are dozens of new business opportunities in every city for the man who is equipped with an Analyzer. Investigate!

SPRAGUE NOISE FILTER MATERIALS →

Sprague Interference Elimination Condensers and Chokes combined with the Sprague Interference Analyzer give you the quickest, most practical and inexpensive means of eliminating radio noises. You save time — you make new profits — and you save money by building your own noise filter combinations as you need them. Sprague supplies you with ALL of the materials—shows you step by step how to proceed with the work.



Proof of the efficiency of the Sprague Method is best shown in the sale, during two years, of several thousand Sprague Interference Analyzers, etc., to public utility trouble-shooting departments, oil burner concerns, and alert radio servicemen.

One prominent utility company writes: "The Sprague Analyzer is most satisfactory. Please send us a lot of your instruction folders for distribution to local servicemen, most of whom are unfamiliar with modern radio interference elimination methods. We believe your plan is the most sensible one offered to date. Hence our willingness to cooperate with you and, at the same time, help our customers enjoy their radios."

In short, here is a wide open field for new profits for alert servicemen. Why not start cashing in on it—today? Send coupon at once for Sprague Catalog giving complete details.

NOW! 48 HOUR SERVICE ON EXACT DUPLICATE CONDENSER REPLACEMENTS

... A new Sprague service of immense value to every serviceman who is faced with the problem of getting duplicate replacements—and getting them in a hurry. Simply send us the defective unit or give us the model number of the radio set and the

capacity, voltage, physical dimensions and type of condenser needed. We'll do the rest — and we GUARANTEE 48-HOUR SERVICE on exact duplicate condenser replacements for ANY type of radio.



These Trademarks Are Your Guarantee of Quality

MAIL COUPON TODAY FOR FREE DETAILS
SPRAGUE PRODUCTS CO. NORTH ADAMS, MASS.
 Without cost or obligation on my part, please rush your new catalog detailing the Sprague Interference Elimination Plan and describing all types of the famous Sprague Condensers.
 NAME.....
 ADDRESS.....

NOW... RADIO SERVICING IS MORE PROFITABLE ... EASIER



MODEL
740
DEALER PRICE
Only \$18.60

VOLT-OHM-MILLIAMMETER

WITH



AVAILABLE NOW IN SINGLE TESTERS, COMBINATIONS
ALSO TO SUIT YOUR NEEDS

EYE APPEAL... PRECISION ACCURACY...

You and Your Customers Will Appreciate the Utmost in Professional Appearance

Yes, Ranger-Examiner Equipment definitely means that Radio Service work can be done more profitably and easier. More profitably because considerably less money is required for precision equipment, and easier because Ranger-Examiner is a completely new line designed from scratch with all the latest improvements for quick and accurate service. Less weight too to carry around in sturdy all-metal cases.

Ranger-Examiner testers are manufactured by the oldest company in the service equipment field whose contacts make them fully acquainted with the needs of

the radio serviceman.

Model 740 Volt-Ohm-Milliammeter has a Triplett 3" square Precision Instrument. Scale readings: 10-50-250-500-1000 A.C. and D.C. Volts at 1000 Ohms per Volt (D.C. Accuracy 2%; A.C. 5%) 1-10-50-250 D.C.M.A.; 0-300 low ohms; high ohms to 250,000 at 1.5 volts. Rheostat adjustment for 13½ volts for ohm readings to 2.5 megohms. Batteries may be added permitting higher resistance readings in 250,000 Ohms steps. Low Ohms to ½ Ohm—with 25 Ohms in center of scale. Backup circuit. Current draw is only 1 M.A.

COMPARE FIRST . . . THEN BUY RANGER-EXAMINER

Be sure to send Coupon for your FREE copy "101 Radio Troubles and Their Cures"

Get this

FREE

BOOKLET

LISTING 101 MOST
FREQUENT RADIO
TROUBLES



**HOW TO DETECT
HOW TO CURE**



**NOTHING LIKE IT BEFORE
GREATLY SIMPLIFIES
EVERYDAY SERVICE**

**SEND
COUPON
NOW . . .**



RANGER EXAMINER

READRITE METER WORKS
1117 College St., Bluffton, Ohio

Without obligation please send me your Free Booklet, "101 Radio Troubles and Their Cures," and complete Ranger-Examiner Catalog.

Name

St. Address

City..... State.....

"These Electrad controls make any volume control replacement a cinch!"



Radio Shop of Mr. Ulmer
371 E. 204th St., Bronx, N. Y. C.

It costs Electrad many thousands of dollars every year for engineering research to build a line of controls *mechanically and electrically right* for any receiver model.

But the result is that any service man who uses Electrads can truthfully say, "Electrad controls make any volume control replacement a cinch."

The new 1937 Electrad Volume Control Guide makes selection of the right control for any job a quick, simple matter. It places almost 150 pages of essential volume control data at your fingertips. Get your copy while present edition lasts—*free* if you will send one flap showing specification number from an Electrad Volume Control carton. Address Dept. S11.

Not Friction-Less But Friction-Right

The resistance element of the Electrad Carbon Volume Control is permanently baked to the outer rim of a warp and wobble proof bakelite ring. On this element the contact shoe moves in direct friction contact.

This contact provides a smooth, stepless graduation of volume, with no gaps to cause stuttering or noise. It is mechanically smooth and electrically quiet, self-cleaning and self-polishing. The more an Electrad Volume Control is used the quieter it gets! Try an Electrad on your next replacement job. Every Electrad Volume Control is noise tested at the factory and fully guaranteed.

**RESISTOR SPECIALISTS
IN RADIO & ELECTRICAL
INDUSTRY SINCE 1923**

ELECTRAD
INC.

**175 VARICK STREET
NEW YORK, N. Y.**

SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR NOVEMBER, 1936

LOOKING FOR TROUBLE

BY R. M. PURINTON

It might be safely said that service work provides trouble without a search. But, when there is trouble a careful hunt for more can provide opportunities for extra work and extra income. The set that goes dead is just plain dead and the Service Man is no longer a miracle worker because he brings it back to life. If he not only produces lifelike action again, but improves on the old performance, he has some claim to the miraculous and an extra charge as well.

Too much service work today is still done on the trial and error or cut-and-try basis. Too much dependence is placed on the circuit diagram of the receiver being serviced. This applies especially to larger receivers and not so much to the small sets of simple design. Yet no group supplying service of any kind does *more* studying than men engaged in radio service, for the work possesses a fascination that makes study and the extension of one's knowledge natural. However, much of the study is applied to circuit diagrams and to the "case" method of service without enough effort on the part of the Service Man to understand the basic reasons for the difficulty. No well equipped Service Man is without a complete file of "case reports" clipped from the exchange pages of SERVICE and other magazines and they are as helpful in diagnosing trouble as a physician's trouble shooter's manual. But the physician usually obtains a complete understanding of the case at hand and the Service Man who handles each opportunity in this way will do much to extend his knowledge and pleasure in serving the radio owner.

To continue our analogy between physician and Service Man very briefly, we can say that the physician must know and understand many complex functions of the human body. The Service Man *must* understand numerous basic principles back of receiver performance and he has the advantage of being able to take his patient apart and put it together again, replacing vital parts many times. Only the dentist has a similar advantage.

RECEIVER FUNDAMENTALS

An examination of fundamentals of the superheterodyne circuit will cover the points of value in all receiver design. The operating functions of the tuned-radio-frequency amplifier, the heterodyne oscillator and first detector either in combination or as separate functions in separate tubes, the interme-

diat-frequency amplifier, the second detector, the audio system and the power supply all constitute divisions which must be understood if full service is to be given. Likewise the interrelated functions such as tracking and automatic volume control merit complete study. It is the purpose here to provide no more than an outline, and it is hoped that the outline will be useful in the start or continuance of a study program. Fortunately, the texts available for the service library are well written in the simple terms so helpful in self-education. Highly technical books are "out" so far as practical knowledge is concerned.

To follow receiver functions in order, we should start with the radio-frequency amplifier. Most good superheterodynes have one stage of tuned-radio-frequency ahead of the first detector or mixer to provide selectivity which will deliver only one signal at a time to the grid of the first-detector tube. Fig. 1 shows the r-f amplifier circuit in its basic form.

THE R-F AMPLIFIER

The antenna tuning system is made up of coils A and L, the capacity coupling link B and the condensers marked C_t and C_{pad} . Coil A is wound with a sufficient number of turns to provide an appreciable resistance to the flow of signal current at low frequencies, for example, the long-wave end of the broadcast band. Thus the voltage built up across the antenna coil A is substantial at the low-frequency end of the tuning range. The capacity coupling link B provides sufficient capacity coupling between the antenna and the grid end of the secondary to

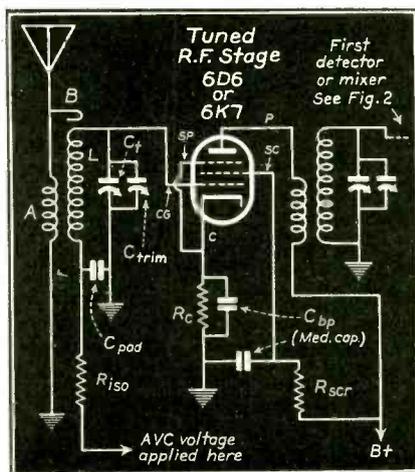


Fig. 1. A typical t-r-f stage.

provide good transfer of signals at high frequencies. Thus the deficiencies in coil A at high frequencies are made up by capacity coupling furnished through the capacity link B. The secondary of the antenna coil L is tuned by the variable condenser C_t which is a part of the gang assembly. The condenser C_{pad} is sufficiently large to have practically no effect on the tuning characteristics of the combination of coil L and condenser C_t . It will be noted that R_{iso} is shown connected between the lower end of coil L and the line supplying automatic voltage control potentials. The purpose of R_{iso} is to isolate the tuned-radio-frequency amplifier circuit from other tuned circuits in the receiver and its use is essential if the receiver is to operate without oscillation. R_c represents the resistance in the cathode circuit which will provide the proper bias voltage for the radio-frequency amplifier tube during those periods of operation when no signal is being received. During such periods or during tuning when no carrier is present in the set, the only bias available for the tuned r-f stage originates in the cathode dropping resistor, R_c in Fig. 1. The by-pass condenser across R_c is of medium capacity and generally is not larger than 0.1 mfd and can be much smaller. There is no necessity for the by-pass condenser at this point to be larger than 0.1 microfarad since the only frequencies present are radio frequencies.

The antenna side of the first tuning coil made up of the winding A and the capacity coupling link B does not present any particular degree of selection to incoming signals. However, the secondary tuning system made up of coil L and condenser C_t does provide a considerable degree of selection. When the condenser is adjusted so that the combination of C_t and L resonates at a given frequency, there will be a voltage developed between the ends of the coil. Since the lower end of the coil is by-passed to ground by C_{pad} and the upper end of the coil is connected to the control grid of the radio-frequency amplifier tube, the full voltage developed is impressed on the radio-frequency amplifier tube. Since resonance is necessary for the development of this voltage, a voltage will appear only at the frequency for which the condenser is set. There is not sufficient space to discuss resonance at length, but it is one subject clearly illustrated by a tuned-radio-frequency amplifier and it should be studied carefully. In Fig. 1, the plate of the amplifier tube is shown connected to the primary of a coupling unit which corresponds to coil A and coil L. This radio frequency transformer performs in much the same manner as

coils A and L and provides further selection of the signal before it is impressed on the grid of the first detector or mixer tube.

THE FIRST DETECTOR OR MIXER

In Fig. 2 on the left side of the diagram we show the radio frequency transformer which feeds the signal energy from the tuned radio frequency amplifier tube to the grid of the mixer tube. The elements which provide the selection are the coil L and the variable condenser C_t which is a part of the gang assembly. As in the case of the radio-frequency amplifier the combination of L and C_t will be resonant to some particular frequency at any given setting of condenser C_t and at that frequency r-f voltage will appear between the ends of coil L. This energy is led into the fourth grid of the mixer which is known as the signal control grid.

In the superheterodyne receiver the greatest step up in radio-frequency amplification is obtained in the intermediate-frequency amplifier. Great amplification can be secured because of the fact that a relatively low frequency can be used such as 175 kc or 456 kc where the radio-frequency losses in coils and tuning condensers are much less than at high frequencies. To transfer the incoming radio signal to the frequency of the intermediate-frequency amplifier it is necessary to use a local oscillator, within the receiver, which is tuned to a frequency above or below (usually above) the incoming radio signal by an amount equal to the frequency at which the i-f amplifier performs. In most receivers today the first detector or mixer tube is of a type which combines the functions of mixer and oscillator in one bulb. The 6A7 glass tube or 6A8 metal tube provides characteristics which give good performance of both functions at the same time. It will be noted on the right side of the diagram that the oscillation circuit has two coils designated L_{osc} and L_{tick} . L_{tick} is the tickler coil in the plate of the oscillator section and is fixed in position with respect to the secondary coil, L_{osc} . Coil L_{osc} is tuned to the proper frequency by condenser C_t . It will be noted that in series with coil L_{osc} and condenser C_t is a variable condenser designated C_{pad} . The purpose of condenser C_{pad} is to make the combination of L_{osc} and C_t tune to a higher frequency than the signal circuit on the left side of the diagram, designated by L and C_t . In the usual superheterodyne the tuning condensers in the condenser gang are alike; similarly the coil L in the signal circuit of the mixer stage, the coil L_{osc} and the L in Fig. 1 are alike. Without the use of the series padding condenser shown between coil L_{osc} and C_t , all of

these tube circuits would be operating at the same resonant frequency. If the oscillator section is made to operate at a fixed higher frequency, 175 kc or 456 kc higher than the signal frequency through the adjustment of C_{pad} , the signal produced by the local oscillator will beat against the signal being received from the antenna and a new signal which is a combination of the two will be fed into the primary of the first intermediate-frequency transformer from the plate of the mixer tube. In this way the intermediate frequency is generated or produced. In magazines and texts oscillograms are used to illustrate the kind of signal which is produced by the mixer. It consists of a carrier having a frequency which will be passed and amplified by the i-f amplifier and it will be found that the audio modulation present on the original signal delivered from the antenna is present on the i-f signal.

One of the best opportunities for service on any superheterodyne receiver is in adjusting the alignment of the tuning system so that the markings on the dial will be accurate. To secure an accurate calibration in any superheterodyne is only a matter of a few minutes' work and it is a service which will be appreciated and readily paid for even though the trouble which required the Service Man's help may have been something in any other part of the set. Receiver manufacturers make a practice of preparing their dial calibration scale with greatest care and at least nine out of ten sets can be adjusted so that the tuning indicator will be accurate over the entire broadcast band at least. Later in this article a particular method of alignment is discussed.

The remaining elements which go to make up the mixer stage are the voltage-dropping resistors for screen grids, 3 and 5 which are tied together within the tube, and the oscillator-plate section, and also the by-pass condensers and the elements which go to make up the oscillator grid circuit. The control grid of the oscillator section of the mixing tube is marked 1. It will be noted that this grid is connected with the cathode through a grid leak and to the tuning coil and condensers through a condenser C_{b1} . This blocking condenser has a low value of capacity and is generally never above 0.0001 mfd. The grid leak usually has a resistance of 25,000 or 50,000 ohms. When the circuits are operating satisfactorily there will be a current of 500 microamperes ($\frac{1}{2}$ ma) or less flowing in the grid leak. To determine the activity of the oscillator section on the broadcast band or on a short-wave band a 0-1 milliammeter can be inserted between the cathode end of the grid leak and the

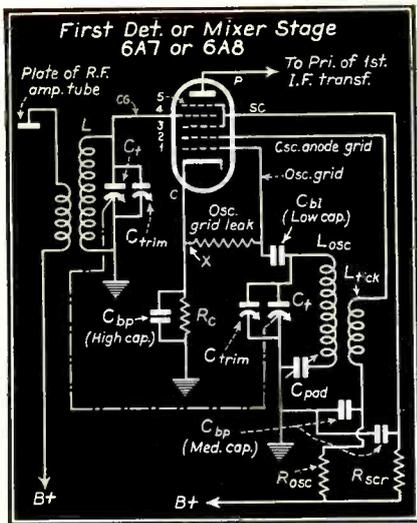


Fig. 2. Superheterodyne mixer stage.

cathode at that point. In general it will be noted that the grid leak current is highest when the rotor plates of the condensers are all the way out and lowest when they are fully meshed. Poor receiver performance can often be traced to poor oscillator performance at this frequency and the insertion of 0-1 milliammeter at the cathode end of the grid leak will provide the complete story of oscillator activity. The grid leak current should never fall below 50 or 70 microamperes if good sensitivity is to be had at the low-frequency end of each band (where the tuning-condenser plates are meshed).

THE I-F AMPLIFIER

In Fig. 3 there are shown the elements of a single stage i-f amplifier. The input transformer and output transformer are quite similar and consist of two coils spaced well apart with individual tuning of each coil. The spacing of the primary and secondary is such that the selectivity or selection qualities of these transformers are better than can be obtained with the transformers coupling the radio-frequency amplifier end of the receiver. The fact that the i-f amplifier operates at a low frequency is helpful and makes it easier to secure good selectivity. In fact some of the smaller receivers have dispensed entirely with a tuned-radio-frequency stage ahead of the first detector and depend altogether upon the selectivity of the i-f amplifier to provide the selectivity needed for reception. In other respects the intermediate-frequency amplifier operates exactly like a tuned-radio amplifier. The condensers marked C_p are simply adjusted so that the coils marked L tune or resonate at the i-f frequency. The condensers C_t should then be left alone until it is evident that realignment or retuning is necessary.

While on the subject of i-f amplifier adjustment and operation it is suggested that the i-f amplifier tuning should be checked on any set which is up for service and especially if new tubes have been put into the receiver. The proper adjustment of i-f amplifier tuning will provide maximum sensitivity and best tone quality in the receiver. It is exceedingly important that the i-f transformers be tuned to the frequency specified by the manufacturer. In some automobile receivers and home sets the oscillator padding condenser (refer to Fig. 2) has been eliminated from the circuit and the difference in tuned frequency between the oscillator section and the signal sections is attained by making the oscillator section of the gang condenser with plates which are specially shaped and smaller than the rotor plates in the other sections of the gang condenser. With this type of tuning system, it is essential that the i-f frequency be main-

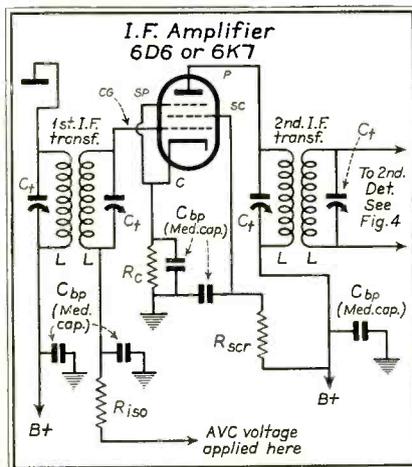


Fig. 3. An i-f amplifier stage.

tained accurately. Otherwise a set will not have equal sensitivity over the entire band covered and strong local signals will appear at more than one point on the dial.

THE SECOND DETECTOR

The second detector of a modern superheterodyne combines diode detection with another section of the detector tube which performs as an audio amplifier. Diode detection has been surrounded with an air of mystery whereas actually it amounts to nothing more than half-wave rectification of signals passed by the intermediate-frequency amplifier. It will be noted in Figure 4 that the two diodes are shown tied together. There are many variations of circuits employing diode rectifiers, but the one shown is perhaps the most simple and the best for use in studying the fundamental performance of this type of detector. As in the case of our tuned-

radio-frequency amplifier circuits we have voltage developed between the ends of the coils designated L and this radio-frequency voltage which appears across the secondary coil L is rectified, or negative half cycles are cut off by the action of the diode rectifier which passes current only in one direction. It may clarify the problem if in considering diode action, the Service Man thinks of the intermediate-frequency current and voltage in the same terms he uses in considering 60-cycle alternating current and voltage. The rectified current must return to the lower end of the intermediate-frequency output transformer secondary coil L. In doing so it flows through the diode load resistor. When this occurs, a voltage drop develops from one end of the diode resistor to the other with the result that the end of the load resistor which is connected to the cathode becomes positive and the end which connects with the i-f transformer secondary becomes negative. Since the positive end is closer to ground than the negative end, the negative voltage can be used to provide bias for the control grids of the r-f and i-f amplifier tubes. When a signal is present and diode load current flows, this automatic volume control voltage is supplied to the r-f and i-f grids and the result is one in which the receiver will always be sensitive to weak signals because the weak signal develops very little diode-load current, and insensitive to strong signals because a strong signal develops considerable diode current and considerable negative voltage when fed back to the grids of the r-f and i-f amplifier tubes reduces their amplifying power. The resistor marked R_{iso} prevents any radio frequency energy which may be present at the point B in Fig. 4 from being fed back to the early stages of the receiver where it might cause oscillation. It will be noted that

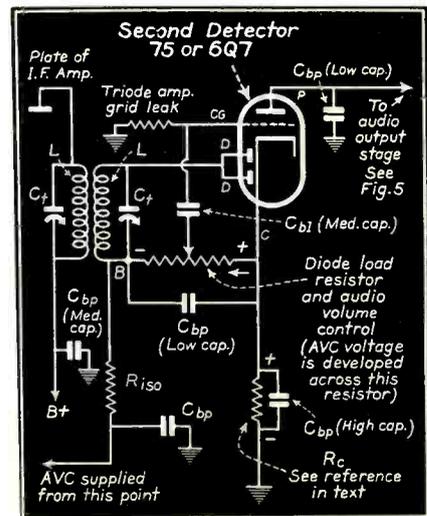


Fig. 4. A simple second detector stage.

the diode load resistor is by-passed with a condenser of low capacity. This is essential to act as a by-pass for any radio-frequency voltage developed at point B—of course the condenser must be small or it will not permit rapid change in voltage across the diode load resistor. The rectified carrier signal produces a pulsating current in the diode load resistor and the envelope of these pulsations (line drawn through the peak of each) has variations up and down corresponding exactly with the voice or music contained in the original signal. These audio variations are fed to the grid of the amplifier section of the second detector through blocking condenser designated C_{b1} of medium capacity. The bias voltage for the audio-amplifier grid of the second detector is obtained by use of the cathode resistor R_c . In Fig. 4 it will be noted that the cathode current flowing to ground makes the upper end of this resistor positive and the lower end negative. It will be noted that the automatic volume control line connects the grid circuits of the r-f and the i-f amplifier tubes through R_{100} to the point B and then through the diode load resistor to the upper end of the bias resistor R_c and thence to ground. When no signal is present, there will be no AVC voltage developed and the positive voltage developed across R_c by the cathode current flowing through it will be impressed on the grids of the r-f and i-f tubes. This positive voltage is usually about 1.5 volts and it must be overcome by a greater cathode bias voltage developed in the cathode of each individual r-f and i-f tube. Otherwise these tubes would operate with a positive bias.

The fundamentals back of automatic volume control are simple and they can be mastered easily if they are regarded just as power supply rectification is considered.

THE OUTPUT STAGE

The audio-output stage is shown as a single tube in Fig. 5. Audio amplifiers are generally well understood although the reasons for the choice of certain values of resistance and capacity in coupling audio stages are not always clear. In Fig. 5 the plate resistance for the triode amplifier which is a part of the second-detector tube is designated R_p . To secure maximum voltage amplification with equal response to all audio frequencies the value of R_p should be several times the plate resistance of the tube. The coupling condenser C and the grid resistor R_g are drawn in a rather unusual arrangement, primarily to show that the coupling condenser and grid resistor in a series form a

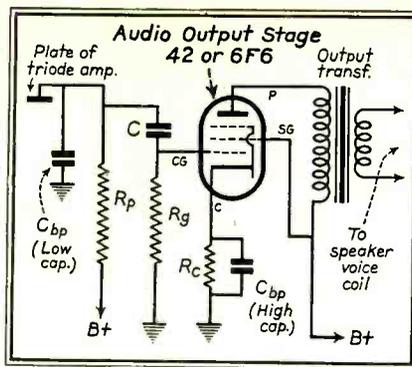


Fig. 5. Typical output stage.

parallel circuit across R_p . The a-c resistance of C and R_g together should be greater than R_p . The control grid of the output tube is connected between condenser C and R_g . These two circuit elements can be compared to a potentiometer with the control grid of the output tube connected to the potentiometer arm. It will be recognized with this type of illustration that if condenser C is of small capacity, having a high impedance to low frequencies, the low-frequency signal fed to the grid of the output tube will be much smaller than the proportion of high-frequency signal which is passed along from the detector. Consequently for good quality R_g should have high resistance ($\frac{1}{2}$ megohm) and condenser C should be reasonably large, 0.1 mfd.

CALIBRATION PROCEDURE

Many broadcast receivers do not follow the dial calibration accurately over the entire dial scale. Most of the inaccuracy will be found at the high-frequency end of the tuning range either due to shift in the trimmer-condenser setting on the oscillator section of the gang condenser or to inaccurate adjustment at the time the set was manufactured. While a receiver can be trimmed so that the dial is accurate on all bands covered, it can be treated with respect to the broadcast band in a relatively short time and with good accuracy. The test oscillator is required, of course.

The first step calls for accurate tuning of the i-f transformers to the frequency specified by the manufacturer.

Next the receiver should be tuned to a 600 kc signal from the test oscillator. If the receiver dial pointer does not rest on the 600 kc marker, move the tuning knob until the dial indicates 600 kc and then adjust the oscillator padding condenser for maximum set output of the 600 kc oscillator signal. The usual method of rocking the tuning condenser back and forth between 590 kc and 610 kc while adjusting the padder condenser is helpful.

Now shut off the oscillator and tune

in a broadcast station somewhere between 550 kc and 650 kc. If the dial marking does not coincide perfectly with the published frequency of the broadcast station, readjust the padder so that the dial reading is correct.

Next, select a station of known frequency between 600 kc and 700 kc and tune it in on the receiver. Turn on the test oscillator and adjust it so that its signal beats (interferes perfectly) with the broadcast station signal. Next, without touching the oscillator, tune the set to twice the frequency of the broadcast station and test oscillator. Suppose that to be twice 660 kc or 1,320 kc. The first harmonic of the oscillator should be heard with the dial set at this point. If it is not heard, leave the dial adjustment untouched and adjust the trimmer condenser, C_{trim} , across the oscillator section of the gang condenser until the harmonic is loudest.

It is well to go back and recheck the 600 kc setting after this and if some slight readjustment is necessary at 600 kc, the harmonic adjustment can be checked again also.

Using this method, accurate calibration is possible at 1,320 kc using WEAJ to set the oscillator accurately at the fundamental frequency, 1,400 kc using WLW and so on.

The customer usually is delighted to find that he can set the dial to a frequency shown by the newspapers or a radio log as the frequency of the station he wants to hear—and find the station there.

It is hoped that this outline will in itself provide some ideas and the inspiration to secure wider understanding through study.

Stromberg Carlson 130 and 140

Sensitivity control: This is a knob on the rear of the chassis, to limit the sensitivity on broadcast reception so that the most powerful nearby broadcast station will not cause rectification in the r-f tube and thus blanket the dial. It is also effective on tweets. Remember to turn this knob clockwise if a newly-installed receiver appears to lack sensitivity.

Stromberg Carlson 145, 150, 160 and 180

Fidelity-tone control: Normal setting is *at the middle*—half red, half white. All red (high fidelity) broadens the tuning and should not be used for distant reception. All white (low fidelity or tone control fully operated) causes muffled tone and reduced volume. A definite bump when passing through "normal" shows that the selectivity is maximum and tone control is set for standard fidelity.



**No Worry
over
Installation Problems**



P. R. MALLORY & CO. Inc.
MALLORY

Replacement Condensers are Universal in Application

Mallory *HAS* solved the question of universal application—and now 69 Mallory Replacement Condensers service 100% of all sets using electrolytic condensers.

Mallory provides practical universal mounting features for both round can and carton type condensers. Mallory has eliminated completely the need for splicing leads. Mallory has produced universal application for a line of humidity-proof, surge-proof, temperature-proof condensers of greater efficiency and smaller size—a quality combination that simply cannot be duplicated. Only Mallory has all these points of superiority! And with it all, Mallory offers a free service to service men that is the finest help ever devised for practical field servicing—the Mallory Condenser Service and Replacement Manual.

20 Minutes of Reading will Yield Big Dividends in Time Saving

Give 20 minutes to the reading of 12 pages in the Mallory Condenser Replacement Manual and save yourself hours of servicing time. That means more profit and satisfied customers. That means quick solution of the knotty problems.

Thousands of service men have written us... "Sure do give satisfaction"... "Your parts are 'tops' with us"... "Best by far—no jobs bounce back"... "The Manual is a real guide"... These are only fragments of enthusiasm, but they tell a mighty story of Mallory quality.


Ask your distributor about Mallory-Yaxley—today. And if you haven't received your Mallory Condenser Manual, write us—today! We'll send your copy free.

*Two examples of new Mallory
Universal Replacements*



U. R. 189

NOTE: UR 189 = UR 188
EXCEPT FOR CARTON

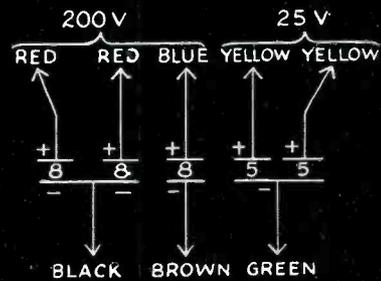

U. R. 188

P. R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address—PELMALLO

YAXLEY

RECTIFIED RF SIGNAL CURRENT

HIGH-MU TRIODE PLATE VOLTAGE

AFC (AUTOMATIC FREQUENCY CONTROL)
DIODE BALANCING CIRCUITS

OSCILLATOR AND POWER
TUBE GRID CURRENTS

POWER DETECTOR BIAS

AVC DIODE CURRENTS

PHOTO-CELL CURRENTS
AND PLATE VOLTAGES

*measure
them* **ALL**

WITH THE

**Super-Sensitive
WESTON**

Model 772


(20,000 OHMS PER VOLT)

\$ 46⁵⁰_{NET}

**TO DEALERS
IN U. S. A.**

and remember . . .

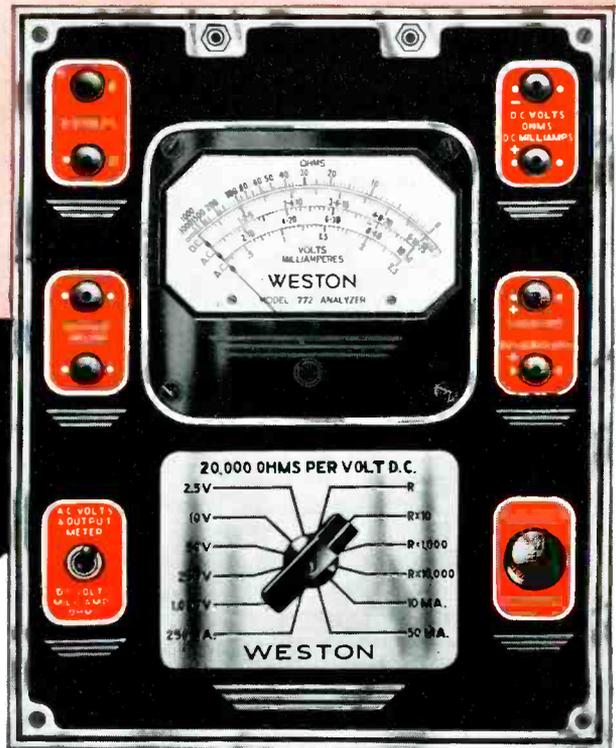you can buy this famous 20,000 ohms per volt analyzer, and other WESTON radio instruments, through the convenient WESTON INVESTMENT PLAN.



No instrument yet offered the serviceman has met with such overwhelming response as Model 772. The reasons are obvious. With its sensitivity of 20,000 ohms per volt, Model 772 is not only ideal for all usual testing routine . . . but it also enables you to get into and thoroughly check circuits which cannot be tested with former servicing instruments. And being built to high WESTON

standards, servicemen know that Model 772 will serve dependably for years. Before you consider the purchase of test equipment be sure to get all the facts on Model 772 and other WESTON instruments for radio servicing. Ask your jobber for full particulars or return the coupon today . . . Weston Electrical Instrument Corporation, 604 Frelinghuysen Avenue, Newark, New Jersey.

WESTON
Radio Instruments

Weston Electrical Instrument Corporation
604 Frelinghuysen Avenue, Newark, N. J.
Send full data on Model 772 and other WESTON Instruments.

NAME _____
ADDRESS _____
CITY _____ STATE _____

IMPROVING OLD POWER SUPPLIES*

THE increased sensitivity of present-day receivers necessitates a more efficient hum filter than that contained in old receivers. Moreover, the advent of high-fidelity receivers made the public more critical of audible hum. It follows that the receivers of the 1937 line must have filters which are far superior to the ones employed five or six years ago. Yet, when looking at the diagram of these receivers it is seen that the number of filter sections is not any greater, and often less. Neither is the use of any kind of trick circuit responsible for their efficiency. The only difference is in the electrical constants of the parts themselves.

EXACT REPLACEMENTS

Service Men who found that parts in an old power pack were defective, have been replacing these parts with others of the same electrical and mechanical dimensions as much as possible. It will occur to many that it would be more expedient for the Service Man to know whether a change in capacity of a condenser would be important. In many cases the Service Man may have parts in stock which have a different rating, while the exact replacement part may have to be procured from a distant dealer. Can the other part be used instead? Very often it can be used and will result in better performance if a few simple rules are observed. In fact, the Service Man has the opportunity to reduce the hum level of many old sets by changing the value of the condensers.

The hum level of a filter is inversely proportional to the size of the chokes and of the condensers. Consequently, when replacing condensers by others of a different size, choice of a larger size will reduce the hum. Doubling the capacity will result in half the hum; tripling the capacity results in one-third of the hum. Such results multiply when the condensers have been replaced in more than one section which makes it possible to realize a substantial improvement. The newer type of electrolytic condenser is smaller, better and more

*From material prepared by the Aerovox Corporation.

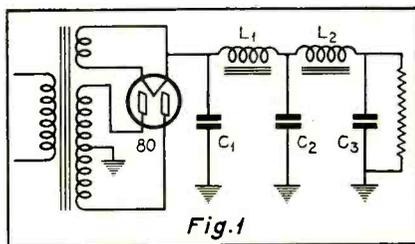


Fig. 1

economical than its predecessor of several years ago. Therefore it is often possible to obtain larger condensers which will fit the same space as the old ones at a reasonable cost. Of course, the increasing of condenser sizes should not be done indiscriminately. For this reason it is best to trace through a typical power pack and see what will happen when condenser sizes are varied.

THE FIRST FILTER

Fig. 1 shows a typical two-section filter, such as one often finds in sets of a few years ago. The function of the first filter condenser is more to keep up the voltage than to reduce the hum. Why is this so? For easier understanding one might represent the circuit of Fig. 1 as the one in Fig. 2. The two circuits are of course not exactly equivalent, but for purposes of explaining the action of the first condenser, no large error is involved.

The source of pulsating d-c charges the condenser through a resistance (the rectifier) at each half cycle. At the same time the condenser is being discharged at nearly the peak voltage when the drain is very small. In that case the

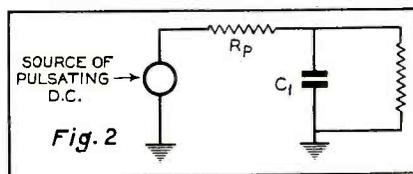


Fig. 2

total current flowing from the given condenser between two charges is only a small fraction of the charge which the condenser is holding. If this total current represented only one twentieth of the charge, for instance, the voltage would have dropped only one twentieth or 5 percent. On the other hand, when the drain is very large or the condenser small, or both, the current between two charges will be so much as to discharge the condenser to a much greater degree with a result in voltage drop. The average voltage will then be much lower and the hum will be greater.

This shows that the condenser need not be as large for a small drain as it is for a large drain. The variation of the condenser capacity results in a change in voltage and that is not always desirable. A large increase in the size of this condenser is not recommended unless one wishes to raise the voltage. Even then, there are limits when mercury-vapor rectifiers are used so as not to exceed the allowable peak current. Since these rectifiers are not common in old

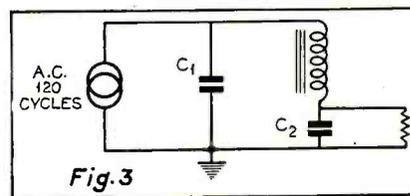


Fig. 3

sets, it is not necessary to go into greater details here.

The voltage rating of the first condensers, that is, "constant working voltage," should be equal to the peak of the applied alternating voltage. Or, in other words, when the constant working voltage is 450 volts, the applied a-c of the transformer should not be more than 315 volts rms. If the a-c supply is higher, the first condenser should be of the paper type. The peak voltage rating of electrolytics refers to surges which may occur when turning the set on or off, but does not refer to continuous peaks.

THE SECOND FILTER

Returning now to Fig. 1, the second condenser C_2 has a material effect on the residual hum. In order to understand this, look at Fig. 3. It may be considered that the hum voltage is applied across the choke and condenser in series and the a-c ripple divides in proportion to the impedance of each circuit element. Now, the impedance of a 15-henry choke at 120 cycles is 113,040 ohms and that of an 8-mfd condenser at the same frequency is 166 ohms. The hum across C_2 is then 166/113,040 times the hum across C_1 , or it has been cut to about seven-tenths of one percent of its original value. When C_2 is increased to 16 mfd, its impedance is only 83 ohms with the result that the hum across C_2 would then be cut to thirty-five hundredths of one percent of its hum across C_1 . Therefore, doubling the condenser size results in half the hum.

Strangely enough, power factors up to 20 percent hardly change these figures. The impedance of an 8-mfd condenser at 120 cycles, having 20 percent power factor is 169 ohms. Replacing 166 in the above paragraph by 169 would not change the total attenuation appreciably. Therefore, replacing a condenser C_2 by another one of better power factor (a paper condenser) and the same capacity will not result in an appreciable improvement of performance. When the electrolytic condenser is replaced by a paper condenser of lower capacity the hum will increase. Replacing the condenser C_2 by one of higher capacity either electrolytic or paper will reduce the hum.

(Continued on page 574)

former which has two separate windings delivering equal voltages. If connected together in one direction, twice the voltage of a single winding will be obtained. If connected the other way, zero voltage will result.

In the third case, things are a little different. One voltage starts $\frac{1}{4}$ cycle or 90° after the other. One voltage has reached its maximum when the other is just starting. If we add up the two waves in this figure, we will obtain a third wave which is the resultant wave of voltage. We find now that the maximum is less than twice the value of one. As a matter of fact, for a phase difference of 90° as shown here, the maximum voltage of the resultant wave is 1.414 times either one of the original waves. For any phase difference between 0° and 180° ; that is, from an in-phase to a completely out-of-phase condition, the amplitude of the resultant wave will vary from maximum to zero.

Now to return to our afc circuit and referring to Fig. 3, let us replace the voltage developed across the choke with an a-c generator. You will recall that this voltage is really the primary coil voltage. Let us also replace the voltage induced in each secondary with an a-c generator.

CIRCUIT CONDITIONS

A simple explanation of the circuit conditions existing at resonance as well as either side of resonance will now be given.

The voltage induced in the top half-secondary is 180° out-of-phase with the primary voltage which is also the choke voltage. However, the phase of the voltage appearing across the top half secondary is something else again because of the inductance of the coils comprising the secondary windings and the phase of the current through them.

At resonance, the top secondary voltage is lagging the choke voltage by 90° as shown in the graph for the top diode. The resultant voltage is shown as the heavy solid line. We know that the volt-

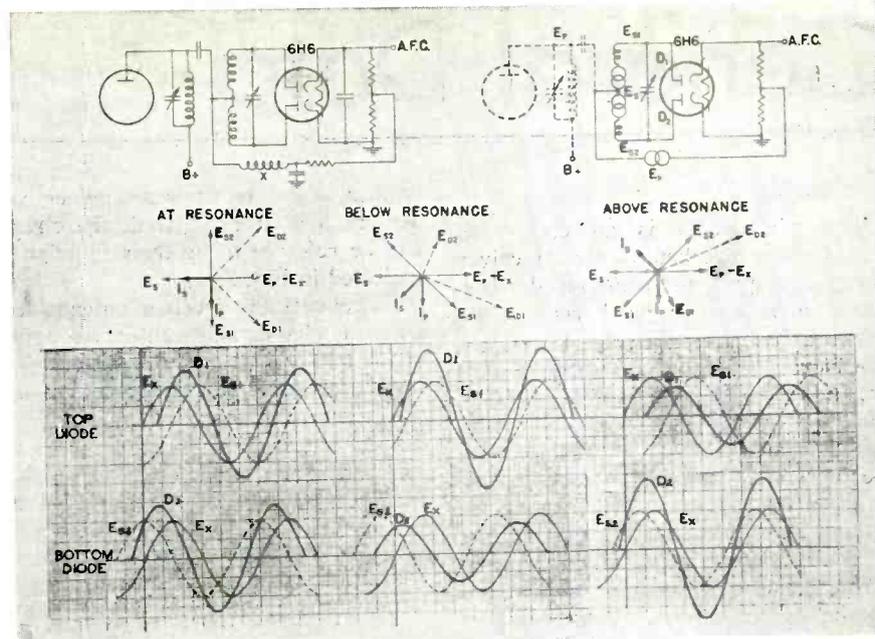


Fig. 4. Circuit conditions.

age across the bottom half-secondary must be 180° out-of-phase with the top; making it lead the choke voltage by 90° . These voltages as well as the resultant are shown in the graph for the bottom diode. Note that the heavy curves in both graphs are of equal amplitude, which means equal voltages applied to the top and bottom diode.

We already know that if equal a-c voltages are applied to the two diodes, then the d-c voltages developed across the load resistors are equal and the resultant d-c voltage, which is the afc control voltage, is zero. This is as it should be, since no control voltage is required if the correct i-f frequency is being generated.

When the i-f carrier is higher than 465 kc, the voltage across the top half-secondary now lags by more than 90° and the voltage across the bottom half secondary consequently leads by less than 90° . Note that the resultant heavy line curves are no longer equal and indicate that the bottom diode has a greater

applied voltage than the top diode.

A greater voltage applied to the bottom diode will result in a greater d-c voltage being developed across the bottom diode load resistor and a negative afc voltage. A negative afc voltage will result in higher grid bias on the control tube and less current will be drawn by the control tube. This is equivalent to making it appear like a larger inductance and the frequency of the oscillator will become lower. If the i-f was above resonance to begin with, that means that the oscillator frequency was too high. Thus it can be seen that the desired action has taken place when the oscillator frequency has been reduced in the manner just described.

When the i-f carrier is less than 465 kc, the conditions are reversed. The voltage across the top half secondary now lags by less than 90° and the voltage across the bottom half secondary now leads by more than 90° . Note that once more the resultant heavy solid resultant curves are unequal. However, this time the top diode has a greater applied voltage than the bottom diode.

A greater voltage applied to the top diode will result in a greater d-c drop across the top diode load resistor and a positive afc voltage. A positive afc voltage will result in a lower grid bias on the control tube and more current will be drawn by the control tube. This is equivalent to making it appear like a smaller inductance and the frequency of the oscillator will be higher. Since the i-f was below resonance to begin with, this means that the oscillator frequency was too low. Thus, the desired action has taken place and the oscillator frequency has been increased.

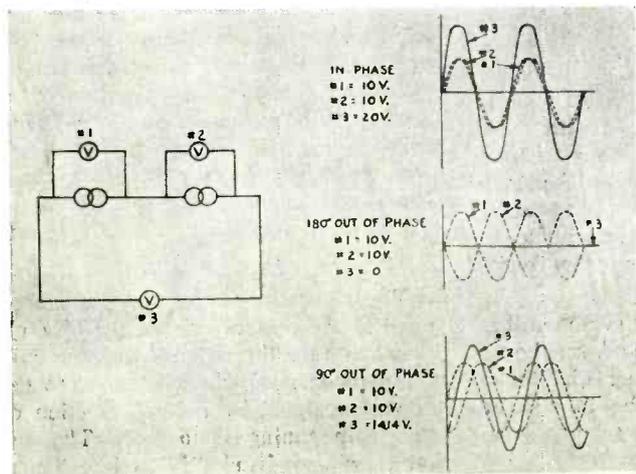


Fig. 3. Phase relationships.

General Data . . .

Sentinel-Erla 53A

The model 53A is an eight-tube, three-band superheterodyne receiver using some glass and some metal tubes. The first or weather band has a range from 140 to 390 kc; the second or broadcast band has a range from 540 to 1720 kc; and the short-wave band has a range from 5.8 to 18.1 mc. A complete circuit diagram is shown in Fig. 1, with the tubes used and their functions lettered on the diagram. The trimmer locations are given in Fig. 2 and an additional figure (No. 3) is shown giving the various voltages encountered on the socket prongs. These voltages were measured with a 1000-ohm-per-volt voltmeter, with the volume control on full, the wave-band switch in the broadcast position and the antenna shorted to the chassis. The line voltage measured 115-volts at the time the measurements were taken. Actual values may vary as much as 15 percent from those given.

ALIGNMENT PROCEDURE

Before attempting to align the various circuits allow the chassis to heat up to normal operating temperature. Connect the output meter from plate to plate of the output tubes in series with an 0.25-mfd paper condenser. Turn the volume control full on.

I-F ALIGNMENT

Short the antenna lead to the chassis. Attenuate the test-oscillator output so that the indication on the output meter is readable. The signal in the speaker should be audible but not loud. Throughout the alignment procedure the signal from the oscillator should be reduced as the stages are brought into alignment so as to prevent AVC action.

With the test oscillator set at exactly 465 kc connect its output to the control grid of the 6A7 oscillator-modulator tube through a 0.02-mfd condenser, with the tubes grid clip in place, and to the receiver chassis. Adjust the i-f trimmers for maximum output starting with the secondary trimmer of the second i-f transformer and working towards the primary trimmer on the first i-f transformer. Repeat the procedure to assure accurate alignment.

R-F ALIGNMENT

It is important when aligning the gang condenser, padder and trimmer condensers to follow the instructions carefully, otherwise the receiver will be insensitive and the dial calibration will

be incorrect. The various trimmer condensers located underneath the chassis will be referred to by their function as indicated in Fig. 2.

Disconnect the receiver antenna lead from the chassis and connect the output of the test oscillator to the antenna lead through a 400-ohm carbon resistor and to the receiver chassis.

Turn the band-selector switch to the 5.8- to 18.1-mc band. Tune the receiver dial to exactly 18 megacycles. Set the test oscillator at exactly 18 megacycles and adjust the 18-mc trimmer for maximum indication on the output meter. When adjusting this trimmer two peaks, the fundamental and the image peak, will be noticed. Care must be taken that the fundamental peak and not the image peak is used for aligning the receiver at 18 mc. Always back off the trimmer to minimum capacity; then screw down the trimmer until the first peak is obtained. This peak is the fundamental and is the proper one to use. If the trimmer is screwed down beyond the point where this first peak is received the incorrect or image peak will be received.

After completing the adjustment of the oscillator trimmer at 18 mc always check to see if the proper peak has been used. To do this leave the test-oscillator frequency set at 18 mc increasing its output. Vary the receiver dial slightly to the right and left of 17 mc and if the fundamental peak was used in aligning at 18 mc the test-oscillator signal will be heard at approximately 17 mc on the receiver dial. If it is not possible to hear the signal then the fundamental was not used and the 18-mc oscillator trimmer must be readjusted.

With the band-selector switch still set on the 5.8- to 18.1-megacycle band tune the receiver and test oscillator to exactly 16 mc. Adjust the 16-mc trimmer for maximum indication on the output meter.

Replace the 400-ohm resistor in series with the test oscillator lead with a 200-mmf condenser. Turn the band-selector switch to the 540- to 1720-mc band and set the dial and test oscillator to exactly 1720 kc. Adjust the 1720-kc trimmer for maximum indication on the output meter.

With the band-selector switch still set on the 540- to 1720-kc band, set the test oscillator and the receiver dial to exactly 1400 kc. Adjust the 1400-kc antenna and preselector trimmers for maximum output.

Tune the receiver dial and the test oscillator to approximately 600 kc. Adjust the 600-kc padder while rocking the tuning condenser rotor through the signal until the maximum output is obtained as a result of the combined operations.

(Note: The 600-kc padder may be adjusted easily in the manner described in the September issue of SERVICE in an article entitled "Impact Excitation Generator.")

Turn the band-selector switch to the 140- to 390-kc band. Tune the receiver dial and the test oscillator to exactly 390 kc. Adjust the 390-kc padder for maximum output.

With the band-selector switch still set on the 140- to 390-kc band, tune the receiver dial and the test-oscillator signal to exactly 340 kc. Adjust the 340-kc trimmer for maximum indication on the output meter.

Tune the receiver dial and the test-oscillator signal to approximately 160 kc. Adjust the 160-kc padder while rocking the tuning condenser rotor through the signal until maximum output is obtained as a result of the combined operations.

(Note: The adjustment of this padder may also be accomplished by the method described in the September issue of SERVICE in an article entitled "Impact Excitation Generator.")

Repeat the r-f alignment to assure more accurate adjustment.

General Electric E-81 and E-86

Models E-81 and E-86 employ eight metal envelope tubes in a superheterodyne circuit, giving the sensitivity and selectivity inherent in this type circuit. The r-f section of this 8-tube chassis utilizes a type of construction known as the "Junior Sentry Box." This construction permits using short connecting leads and isolates each r-f circuit in its own particular shielded section. Separate groups of coils are used for each band in the oscillator section. The antenna and r-f sections are composed of two coils, a separate coil for the "D" band and a composite coil for the "B" band and "C" band. Operation on the "C" band is obtained by shorting out a section of the antenna and r-f "B" band coils. The entire frequency range from 540 to 18,000 kc is covered in three bands. An undistorted power output of 6.5 watts is available.

THE CIRCUIT

The signal from the antenna is applied to the control grid of the 6K7 r-f amplifier tube through the antenna coil, the secondary of which is tuned to the incoming signal by the rear section of the main tuning condenser. The antenna coil, for bands "B" and "C," con-

Sentinel-Erla Model 53A

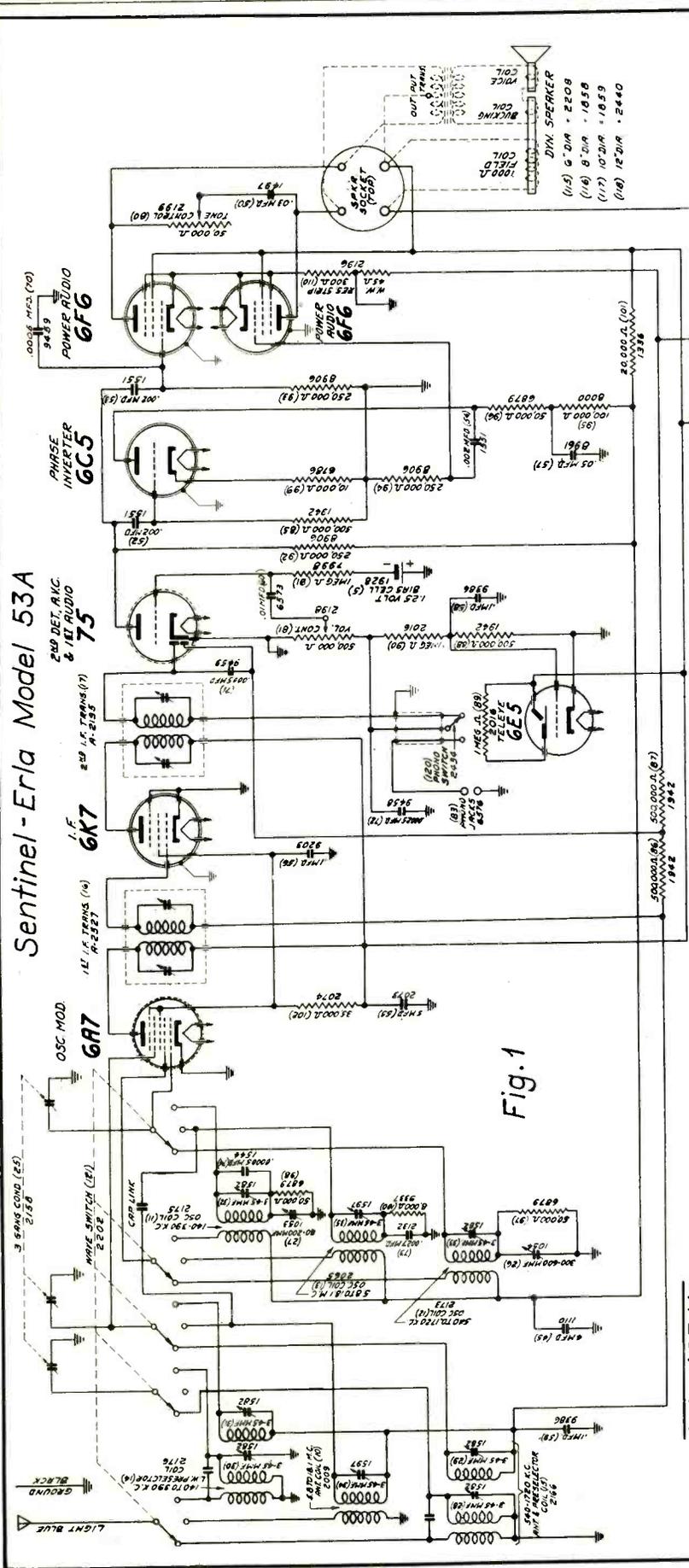


Fig. 1

I.F. = 465 Kc.


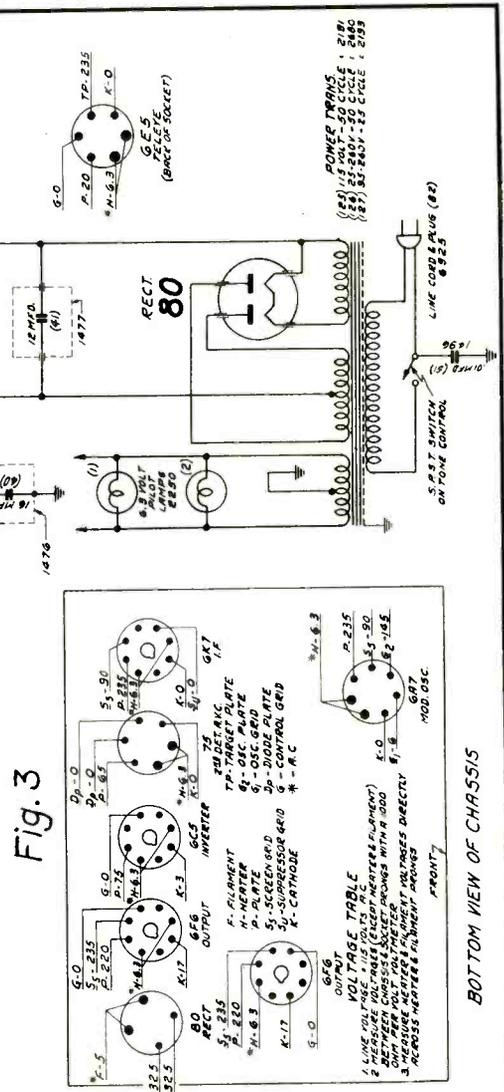


Fig. 2

Fig. 3

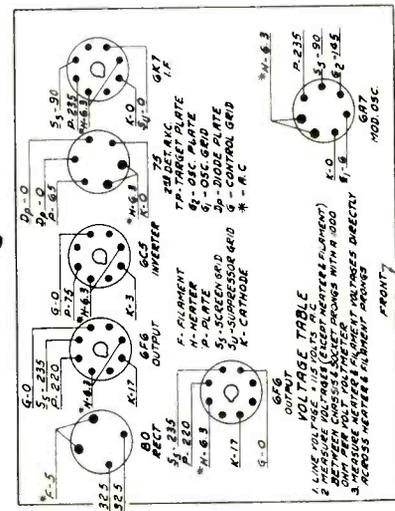

VOLTAGE TABLE

- LINE VOLTAGE
- METER VOLTAGES (EXCEPT METER PLACEMENT)
- COMP. W. OUT. VOLTAGE
- METER VOLTAGE
- VOL. W. DIRECTLY ACROSS METER & VOLTAGE RANGE

BOTTOM VIEW OF CHASSIS

BOTTOM VIEW OF CHASSIS SHOWING LOCATION OF TRIMMERS & PADDERS

GENERAL DATA—continued

tains two primary coils connected for operation on the "B" band; however, when the band switch is turned to the "C" band position, the lower primary coil, L-5, is shorted out. The high-frequency trimming adjustment, for the "B" band antenna and r-f stages, is accomplished by two adjustable trimmers connected from the "C" band tap on each coil to ground. The capacity coupling coil, L-3, acts only on the "C" band and its function is similar to that of a fixed antenna stage trimmer for that band.

The amplified radio-frequency signal is impressed upon the signal control grid of the 6A8 converter tube through the r-f coil, the secondary of which is tuned to the signal frequency by the center section of the main tuning condenser. In the 6A8 tube, the incoming signal is combined with the local oscillator signal which is 465 kc different in frequency. The local signal is generated by the oscillator elements of this tube and the proper frequency difference is maintained throughout the tuning range by the front section of the main tuning condenser in conjunction with the oscillator coils and padding capacitors.

The combination of the signal frequency with the local oscillator frequency in the 6A8 converter tube produces the i-f of 465 kc. This particular intermediate frequency is chosen to reduce image response and improve short-wave performance.

The intermediate-frequency amplifier consists of a two-stage cascade section composed of three i-f transformers and two 6K7 amplifier tubes. Each i-f transformer has two tuned circuits. The first i-f amplifier 6K7 is operated on both self-bias and on avc for the broadcast band, since its grid return connects to the avc bus. On the two short-wave bands the self-bias resistor is shorted out by one of the band switch sections and this tube receives only avc bias. The second i-f amplifier 6K7 tube operates on self-bias for all bands. This enables the second i-f tube to provide maximum power to the 6H6 diode rectifier.

The output of the i-f amplifier is applied to one plate of the 6H6 diode rectifier, which is a combined second detector, initial bias and automatic volume control tube. The direct-current component of the rectified signal, through one diode of this tube, produces a voltage drop across resistor R-10. This voltage

drop provides automatic bias for the r-f amplifier, converter and the first i-f amplifier, and thus gives automatic volume control action. The other diode of the 6H6 provides an initial bias for the tubes on the avc circuit under conditions of little or no signal. This initial bias diode, under conditions of small signal, draws current which flows through resistors R-9 and R-10. The resulting voltage is the required minimum operating bias for the tubes on the avc circuit. Upon receiving signals above the level of the initial bias, the initial bias diode stops drawing current and the automatic volume control diode takes over the controlling bias.

The audio frequency present across R-10 is impressed upon the volume control R-15 through capacitor C-34. The movable arm on the volume control selects the amount of audio signal applied to the control grid of the 6F5 audio amplifier tube and thus regulates the output of the receiver. Across the volume control, R-15 is placed a compensating network of capacitors and a resistor. The music-speech switch is found in this circuit, and when closed places capacitor C-38 in shunt with C-39, which results in the accentuation of the low audio fre-

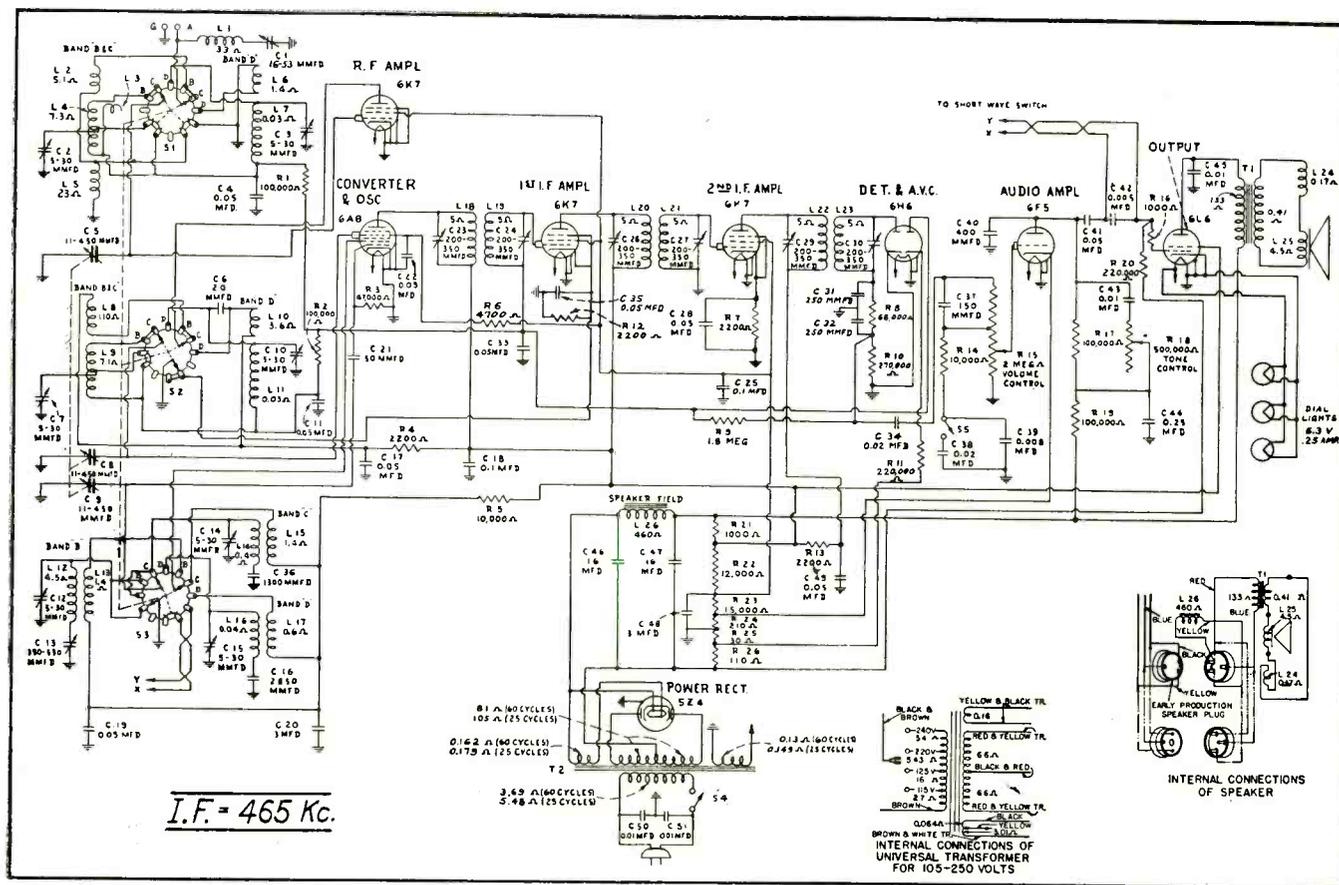


Fig. 1. General Electric E-81 and E-86 circuit.

est level which will give an easily readable output indication.

Now set the test oscillator at 580 kc, and tune the receiver to resonance with this signal. Adjust the 580-kc padding capacitor, C-13, rocking the tuning condenser back and forth through resonance as the padding capacitor is adjusted and note the deflection of the tuning meter each time the receiver is tuned through resonance. Leave the padding capacitor at the setting which gives greatest deflection.

Retune the receiver to 1500 kc, and set the test oscillator for this frequency. Check the alignment by again adjusting the band "B" oscillator, r-f and antenna trimmers for maximum deflection on the tuning meter.

Band "C" (1680-6000 kc): No trimmers are provided for alignment of the r-f and antenna transformers in band "C" of these receivers. Correct tracking between r-f and antenna transformers is obtained by the action of the capacity coil, L-3, and between oscillator and the other tuned circuits by means of the adjustable oscillator trimmer C-14 and the fixed padding capacitor, C-54.

Turn the band switch to band "C." Set the test oscillator at 5220 kc and tune the receiver to resonance at this frequency. Adjust the band "C" oscillator trimmer, C-14, for maximum output indication on the tuning meter, rocking the tuning condenser back and forth through resonance while making this adjustment.

Band "D" (6.0-18.0 mc): Turn the band switch to band "D." Set the test oscillator at 18,000 kc (18.0 mc) and tune the receiver until the pointer coincides with the 18.0-mc mark. Adjust the band "D" oscillator trimmer, C-15, to give maximum output indication. It will probably be found that there will be two settings of the oscillator trimmer that will give an output response. The lower capacity setting of the trimmer is the one that should be used. To be sure that correct adjustment has been obtained, tune for the image signal at 17.07 mc with the test oscillator set at 18.0 mc. It may be necessary to increase the test oscillator output to obtain response at this point.

Retune the receiver to 18.0 mc and adjust band "D" antenna and r-f trimmers, respectively (C-3 and C-10), for maximum output indication. When adjusting the r-f trimmer, C-10, rock the tuning condenser back and forth through resonance as in the 580-kc padding capacitor adjustment.

Alignment of the receiver is now complete.

Fairbanks-Morse 100†

A complete description of the electrical circuit of the Fairbanks-Morse model 100 receiver is given below together with the alignment data, selectivity curves, power-transformer ohmages and circuit diagram.

TUBES AND CIRCUIT

The model 100 chassis employs a type 6D6 tube in the radio-frequency amplifier stage. The incoming signal is fed to this tube through the antenna coil on each of the four bands. Through the use of this stage, high image and signal-to-noise ratios are maintained on all bands. Amplification and some selectivity are also realized in this stage.

A type 6A7 pentagrid converter is employed. This tube serves the dual function of first detector and oscillator. The oscillator section of the tube, on all but the long-wave band, is connected to a McNabb constant voltage oscillator circuit. Through the use of both inductive and capacitive coupling, the output of the oscillator remains at a uniform level over the entire frequency range of the band in use. On the long-wave band, the oscillator tube works easily and with fairly constant intensity on all frequencies and, for this reason, only capacitive coupling is employed.

Two type 6D6 tubes serve as i-f amplifiers. These tubes, together with the 3 i-f transformers, comprise the i-f amplifier. Here most of the gain and selectivity of the receiver is realized.

A type 76 tube, connected as a diode, performs the dual function of second-detector and avc tube. Since no gain is obtained in this stage, the output is resistance coupled to another type 76 tube that serves as audio amplifier. The output of this tube is, in turn, resistance coupled to a type 42 tube, connected as a triode, driving two type 2A3 tubes in a Class A output stage.

The input transformer is of special design, being wound for low-leakage inductance, which makes for high-efficiency, high-fidelity reproduction. Condenser C-22 and resistor R-25 comprise an audio frequency equalizer circuit connected across the secondary of the input transformer. A type 5Z3 full-wave rectifier tube is employed in a conventional power-supply circuit.

TUNING INDICATORS

The tuning indicator on the model 100 is of the magnetic type operating a vane in such a manner as to cast a shadow of variable width on the upper portion of the dial. When the shadow

is contracted to its narrowest possible dimension, the receiver is properly tuned. This indicator is connected into the circuit as shown in the circuit diagram, Fig. 1. It will be noted that the tuning indicator is only in the circuit when the third dimension switch is on the sharp position. This is intended to encourage tuning only on the sharp position.

AUTOMATIC VOLUME CONTROL

A type 76 tube is employed as the second detector in a half-wave rectifier circuit, with the grid and plate tied together. Current flows through the tube to the cathode to ground. Here it is picked up at the point where resistor R-16 is grounded and flows through resistors R-16 and R-17, through the secondary of the i-f transformer back to the grid and plate of the 76 tube, thus forming a complete circuit.

The d-c component produces a voltage drop across resistor R-16 in proportion to the signal strength of the incoming signal. The grid returns of the r-f amplifier, the pentagrid converter and the first i-f amplifier are connected, through the isolating resistors R-6, R-7 and R-15, to the point of juncture between resistors R-16 and R-17, thus adding the voltage drop obtained across R-16 to the fixed bias on the three controlled tubes. The fixed bias is obtained from the individual bias resistors R-2, R-4 and R-11 located in the cathode circuits of the tubes. Resistor R-16 is also the manual volume control. The audio component of the voltage drop across this resistor is taken off on the sliding arm of the control through condenser C-18 and is applied to the grid of the 76 audio-amplifier tube.

ALIGNMENT PROCEDURE

To insure obtaining the performance this receiver is capable of delivering, it is essential that it be aligned perfectly. For this reason, it is urged that the following instructions be carefully studied before any alignment adjustments are attempted.

Proper adjustment of the various tuned circuits will only be possible through the use of an accurate and reliable signal generator employed in conjunction with an output meter connected across the voice-coil leads of the speaker. In the adjustment of the third i-f transformer, it is recommended that a cathode-ray oscilloscope be used for more accurate results. Note: All adjustments, unless otherwise noted, should be made with the volume control on full. Any desired variation in

†From Rider's Volume VII.

the signal strength should be obtained by adjusting the output of the signal generator.

I-F ALIGNMENT

With the range switch in the broadcast position, the fidelity switch in the sharp (clockwise) position and the gang condenser closed (maximum capacity), supply a 456-kc signal, stage-by-stage, to the i-f amplifier, beginning with the grid of the second i-f tube. To accomplish this, a 0.1-mfd condenser should be connected between the generator supply lead and the second i-f tube.

The trimmers of the third i-f transformer should be adjusted for maximum output with minimum input from the signal generator. Then the signal generator lead should be moved to the first i-f tube and the trimmers of the second i-f transformer should be adjusted. The next step is to supply the signal to the grid of the first detector tube and adjust the trimmers of the first i-f transformer. This method of procedure is essential because of the extreme selectivity of the receiver. After each stage has been aligned, it is well to go back overall adjustments to make sure they are accurate.

The next step in the i-f alignment is to supply a very strong (about 1,000 microvolts) signal to the grid of the first detector tube through a 0.1-mfd condenser. *Caution:* Before the signal is applied to the receiver the volume control should be retarded to zero. After the signal is applied, the volume control should be advanced slowly and carefully until a suitable indication appears on the output meter.

The fidelity switch should be turned to the high-fidelity or "third dimension" position. Symmetrical double humps should appear, one on each side of where the sharp resonance point appeared on the "sharp" position (see Fig. 2), when the signal generator is tuned approximately 8 kc on each side of the resonance point. The two humps must be of equal amplitude. If this is not the case, the trimmers of the third i-f transformer must be adjusted until a condition of equal amplitude is obtained. This may be found to be a very difficult adjustment unless an oscilloscope is used.

USE OF THE OSCILLOSCOPE

A signal generator with a sweep circuit must be employed in making this check. The output of the signal generator should be fed to the grid of the first detector tube in the receiver. The grid clip must be removed from the

tube, but, since the first detector is one of the AVC controlled tubes, it is necessary to complete the grid circuit. To accomplish this, connect a large resistor (about 50,000 or 100,000 ohms) between the grid clip and the grid cap of the tube. The low side of the signal generator should be connected to the chassis ground.

The "vertical" binding posts of the oscilloscope should be connected to the audio output of the second detector. The high side connection from the "vertical" plates should be made to the point of juncture between resistors R-15, R-16 and R-17. The low side connection may be made to ground. Thus, the audio voltage is applied to the "vertical" plates of the oscillograph.

With the receiver operating on the "sharp" position, the i-f amplifier resonance curve will appear on the screen. When the receiver is switched to the "third dimension" position, symmetrical double humps, approaching a wide flat top resonance curve, should appear in place of the "sharp" resonance curve (see Fig. 2). Each side of the curve should be of equal amplitude. If this is not the case, the trimmers of the third i-f transformer should be adjusted until the proper curve is obtained. The adjustment of one trimmer, in addition to affecting its own side of the curve, will reflect in the other side and, for this reason, great care must be exercised in making these adjustments.

R-F ALIGNMENT

The parallel or high-frequency trimmer condensers for each coil are housed in the same can with the coil. These trimmers are used for aligning the high-frequency end of each band. It is essential that the bands be aligned in the order they appear in the following instructions. In other words, the police band alignment must be completed before the broadcast band align-

ment is started because of the interlocking effect of the padding condensers on these bands.

Adjustable series padding condensers are used for tracking the oscillator at the low-frequency end of each band. The padding condensers may be adjusted from the top of the chassis, through the holes indicated. Since a fixed mica padding condenser is employed on the short-wave band, no adjustment is necessary. While making padding condenser adjustments, the gang condenser should be rotated back and forth across the signal to insure adjustment to the peak of greatest intensity.

POLICE BAND

With the band selector switch on the police station and the fidelity switch on the "sharp" position, supply a 5-mc signal from the signal generator to the antenna of the receiver, using a 400-ohm carbon resistor in series with the signal-generator lead. Tune the receiver to 5-mc and then adjust the oscillator, r-f and antenna stage police band trimmers for maximum output with minimum input from the signal generator. *Warning:* Care must be exercised to avoid aligning the receiver to the image frequency as outlined under "short-wave band."

Supply a 1.8 mc signal to the receiver and tune the receiver to 1.8 mc. Adjust the police-band oscillator padding condenser for the signal of greatest intensity, rocking the gang condenser back and forth across the signal while making adjustment. Check at 5 mc and then at 1.8 mc to correct for any frequency change.

BROADCAST BAND

With the band selector switch on the broadcast position, supply a 1,500-kc signal from the signal generator to the receiver, using a standard dummy antenna or a 200-mmfid condenser in series between the signal generator and the antenna post of the receiver to serve as the dummy antenna. Make certain that the fidelity switch is on the "sharp" position.

Tune the receiver to 1,500 kc and adjust the r-f, antenna and oscillator stage broadcast-band trimmers for maximum output with minimum input from the signal generator.

Supply a 600-kc signal to the receiver through the same connections. Tune the receiver to 600 kc. Adjust the broadcast band oscillator padding condenser for the peak of greatest intensity while rocking the tuning condenser back and forth across the signal. Recheck at

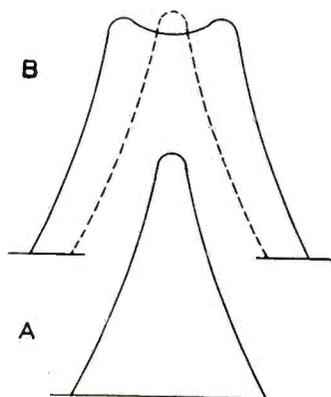


Fig. 2. Resonance curves.

Technical Features of 1937 Bosch Radio Receivers

Model No.	515	600	601	602C	602T	604	605	605C	610	620	625	640	650	660T	660C	670S	670C	680	
Cabinet *	P	T	T	Ce	T	P	P	Ce	P	P	Ce	P	Ce	P	Ce	Ce	Ce	Ce	
Power Supply	A.C.	6 V.	Battery	Battery	Battery	A.C.- D.C.	A.C.	A.C.- D.C.	A.C.- D.C.	A.C.-D.C.	A.C.-D.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	A.C.	
Range (Kc.)	540-3600	540-1725 2000-7000	540-1725 2000-7000	540-1725 2200-16,000	530-3000	540-1700 2000-7200	540-1700 2000-7200	540-1700 2000-7200	540-1700 2000-7200	540-4500 5500-16,500	540-4500 5500-16,500	540-4500 5500-16,500	540-4500 5500-16,500	525-18,500	525-18,500	150-390 525-18,500	150-390 525-18,500	150-390 525-18,500	
Power Consumption Watts	-	/	/	/	44	-	-	-	-	52	47	62	62	60	80	-	-	-	
Audio Power watts	-	-	-	-	1.1	-	-	-	-	1.0	3	3.5	3.5	3.3	6.5	-	-	-	
I.F. Peak (Kc.)	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	465	
CentrOmatic	/	/	/	/	/	/	/	/	/	/	/	/	/	/	Yes	Yes	Yes	Yes	
Tone Control	-	-	-	-	-	-	-	-	-	Continuous	Cont.	Cont.	Cont.	Continuous	Continuous	Continuous	Continuous	Cont.	
Variable Condensers	2	2	2	3	2	2	2	2	2	2	2	2	2	3	3	3	3	3	
Number of Tuned Circuits	6	6	6	7	4	6	6	6	6	6	6	6	6	7	7	7	7	9	
R.F.	/	/	/	/	/	/	/	/	/	/	/	/	/	1A4	6K7	6K7	6K7	6K7	
1st. Det.	6F7	6A7	1C6	1C6	6A7	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	
Oscillator																			
Intermediate Frequency	6D6	6D6	1A4	1A4	/	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	
2nd. Det.					6C6														
A.V.C.	75	75	1B5	1B5	/	75	75	75	75	6H6	6H6	6H6	6H6	6H6	6H6	6H6	6H6	6H6	
1st. Audio										6F5	6F5	6F5	6F5	6F5	6F5	6F5	6F5	6F5	
2nd. Audio	/	/	30	30	/	/	/	/	/	/	/	/	/	/	/	/	/	/	
Output	42	41	19	1J6G	43	6F6	25A6	25A6	25A6	25A6	25A6	6F6	6F6	6F6	6F6	(2) 6F6	6F6	(2) 6L6	
Rectifier	80	/	/	/	25Z5	80	25Z6	25Z6	25Z6	25Z6	25Z6	5Y3	5Y3	5Y3	5Y3	5Y3	5Y3	5Y3	5Z3

Ce = Console

P = Personal

* T = Table

POWER TRANSFORMERS

Part No.	Voltage	Cycle
Part No. 5410	110 Volt	50-60 cycle
Lead Color	Voltage	Resistance
Black	2.5	
Black & Yellow	Center Tap (2.5 volt)	.03 ohm
Blue	5.0	.05 ohm
Green	6.3	.10 ohm
White	110 (Primary)	1.79 ohms
Yellow	High Voltage	115.3 ohms
Green & Yellow	Center Tap (Hi-Volt.)	
Part No. 5566	Universal	40-50-60 cycle
Lead Color	Voltage	Resistance
Black	2.5	
Black & Yellow	Center Tap (2.5 volt)	.03 ohm
Blue	5.0	.10 ohm
Green	6.3	.08 ohm
Yellow	High Voltage	115.3 ohms
Green & Yellow	Center Tap (Hi-Volt.)	
Black	Common Primary	
Red	100-125 Primary	2. ohms
Brown	130-155 Primary	2.2 ohms
White	200-250 Primary	6.2 ohms
Part No. 5589		25 cycle
Lead Color	Voltage	Resistance
Blue	5.0	.06 ohm
Green	6.3	.10 ohm
Yellow	High Voltage	154.5 ohms
Black & Yellow	Center Tap (Hi-Volt.)	
White	110 Primary	2.45 ohms

1,500 kc and then at 600 kc, and make any frequency corrections that appear necessary.

LONG-WAVE BAND

With the band-selector switch on the long-wave position, supply a 350-kc signal from the signal generator to the antenna of the receiver, using a standard dummy antenna or a 200-mmfd condenser in series with the lead. Make sure the fidelity switch is on the "sharp" position. Tune the receiver to 350 kc and adjust the oscillator, r-f and antenna stage trimmer condensers for maximum output with minimum input from the signal generator.

Supply a 175-kc signal to the receiver through the same connections used in the previous adjustment. Tune the receiver to 175 kc. Adjust the long-wave oscillator padding condenser for the peak of greatest intensity while rocking the tuning condenser back and forth across the signal. Readjust at 350 kc and then at 175 kc as many times as may be necessary to obtain satisfactory tracking.

SHORT-WAVE BAND

Turn the band-selector switch to the short-wave position. Supply an 18-mc signal from the signal generator through a 400-ohm carbon resistor (dummy antenna) to the antenna post of the receiver. Tune the receiver to 18 mc on the dial. Adjust the short-wave band oscillator trimmer condenser for maximum output with minimum input from the signal generator, then adjust the short-wave band antenna and r-f stage trimmer condensers for maximum output, at the same time rocking the tuning condenser back and forth across the signal to insure the peak of greatest intensity. Check the calibration and, if necessary, readjust all three stages.

Warning: The image signal should be

received at approximately 17 mc after the above adjustments have been made. If it cannot be located the oscillator has probably been aligned to the image frequency and the oscillator trimmer must be backed out until the proper signal comes in at 18 mc and the somewhat weaker image is received at approximately 17 mc. If this readjustment is necessary, it will also be necessary to again align all three trimmers for maximum output.

GANG-CONDENSER PLATES

The adjustment of the various plates of the gang condenser is very critical, since it must be accurate on all bands. These adjustments are made in the factory with precision equipment and under no condition should it be necessary to change them by bending plates.

10-KC AUDIO TRAP

Because of the band width necessary to obtain high-fidelity reproduction, if a station is operating on a channel adjacent to the station channel being listened to, a 10-kc beat (high-pitched whistle) may be heard in the background. To reduce the possibility of this interference, Fairbanks-Morse engineers have developed a 10-kc wave trap. This trap circuit consists of a large, air-core choke coil and a variable condenser, connected in series. This trap is connected from the plate of the first audio amplifier tube to ground.

It should not be necessary to adjust the trap circuit unless either the coil or the condenser has been replaced. To adjust the trap tune in on two adjacent channels on which two distant stations are operating. Turn the selectivity switch to the third dimension position. Tune the interfering whistle to its loudest point by tuning between the two stations. Adjust the 10-kc

trap trimmer until the whistle is reduced to a minimum.

The secondary of the first and second i-f transformers is composed of three sections, the upper, center and lower (see schematic diagram). The primary is composed of two sections, the upper and lower. The upper sections of the primary and secondary are loosely coupled to each other and constitute the major portion of the primary and secondary inductance respectively. The lower section of the primary and the center section of the secondary are tightly coupled. The coupling between the lower section of the secondary and the primary is loose. When the switch is on the third-dimension position, the lower section of the secondary is out of the circuit and the secondary winding is made up of the other two windings, connected in series. Because the coupling between the lower section of the primary and the center section of the secondary is tight, a broad response will result.

When the switch is on the "sharp" position, the center section of the secondary is cut out of the circuit and the loosely coupled lower section is substituted, thus the selectivity is increased the desired amount. Since the inductance of the center section and the lower section of the secondary are identical, the tuning is not altered when switching from the "sharp" to the third-dimension position. Because of this very practical and unique design, it is possible to arrange the tuning eye circuit in such a manner that it is only engaged on the "sharp" position of the switch. This serves to remind the operator that all tuning should be done on the "sharp" setting to insure perfect resonance and most faithful reproduction.

Stewart Warner R-149

The Stewart-Warner model R-149 chassis is a 12-tube, all-wave superheterodyne with an intermediate frequency of 456 kc. It has four tuning ranges which are 140 to 400 kc, 527 to 1750 kc, 1720 to 5600 kc, and 5.5 to 18.0 mc. Individual coils and trimmer condensers are provided for each band so that each circuit can be adjusted to give maximum efficiency on every frequency range.

THE CIRCUIT

The antenna coils are designed to give efficient reception with either a standard or doublet type antenna without the use of any additional coupling transformer. A small connector is provided on the

GENERAL DATA—continued

antenna terminal strip to short the D and G terminals when a standard antenna is used. If a doublet antenna is used, the connector should be turned or removed to open the connection between the D and G terminals.

Two degrees of selectivity are obtainable by means of the selectivity-sensitivity control operating on the first i-f transformer. When the control is in the sharp position (counterclockwise) the first i-f transformer functions as a typical transformer with sharply tuned primary and secondary circuits. When it is in the broad position (clockwise) the resonant frequency of the primary is decreased and that of the secondary circuit increased. At the same time the selectivity curve of the secondary is broadened and the amplification reduced. The combined effect gives a broad flat top to the intermediate frequency amplifier selectivity curve.

This chassis uses an amplified and dual avc action to keep the second detector signal more constant and still have sharp tuning. The diode of the 6H6 second detector tube which is capacity coupled to the second i-f transformer, produces the avc voltage for the i-f tube and the tuning eye only. The

avc voltage for the r-f and first detector tubes is secured by means of the 6J7 avc amplifier tube and the second 6H6 tube. The control grid of the 6J7 tube is capacity coupled to the control grid of the 6K7 first i-f tube.

A five-point tone control permits variation of the frequencies present in the speaker from a minimum of treble and emphasized bass to a maximum of treble and normal bass.

ALIGNMENT PROCEDURE

During calibration and alignment, keep the receiver volume control in the maximum volume position if noise is not too great, and adjust the oscillator output so that the output meter reads near the center of its scale.

Use the lowest output-meter scale that will provide a steady reading. For making trimmer adjustments, use a bakelite aligning tool which has only a small metal screwdriver tip.

Connect the output meter across the two plates of the two 6L6 power output tubes. *Important:* Do not connect from one 6L6 plate to chassis since this would unbalance the circuit and cause hum.

I-F ALIGNMENT

(a) Turn the volume control to the

maximum volume position and turn the sensitivity-selectivity control to the sharp position (counterclockwise).

(b) Turn the range switch to the broadcast position (second from the right) and set the tuning dial to any point where there is no tuning effect on the oscillator signal.

(c) Connect the test oscillator output leads to the 6A8 control grid and the chassis with a 0.1-mfd or 0.25-mfd condenser in series with the lead to the 6A8 grid. Do not omit this condenser or alignment will be incorrect.

(d) Set the test oscillator to exactly 456 kc. Adjust the output of the test oscillator to give about half-scale deflection on the output meter.

(e) Adjust the four i-f transformer trimmers (trimmers Nos. 1, 2, 3 and 4) for maximum output-meter deflection.

AVC AMPLIFIER ALIGNMENT

(a) Leave the test oscillator set at 456 kc and connected to the 6A8 control grid through a condenser.

(b) Turn the volume control down to protect the output meter and turn the output control of the oscillator up to give enough signal so that the tuning eye closes more than half way. If your

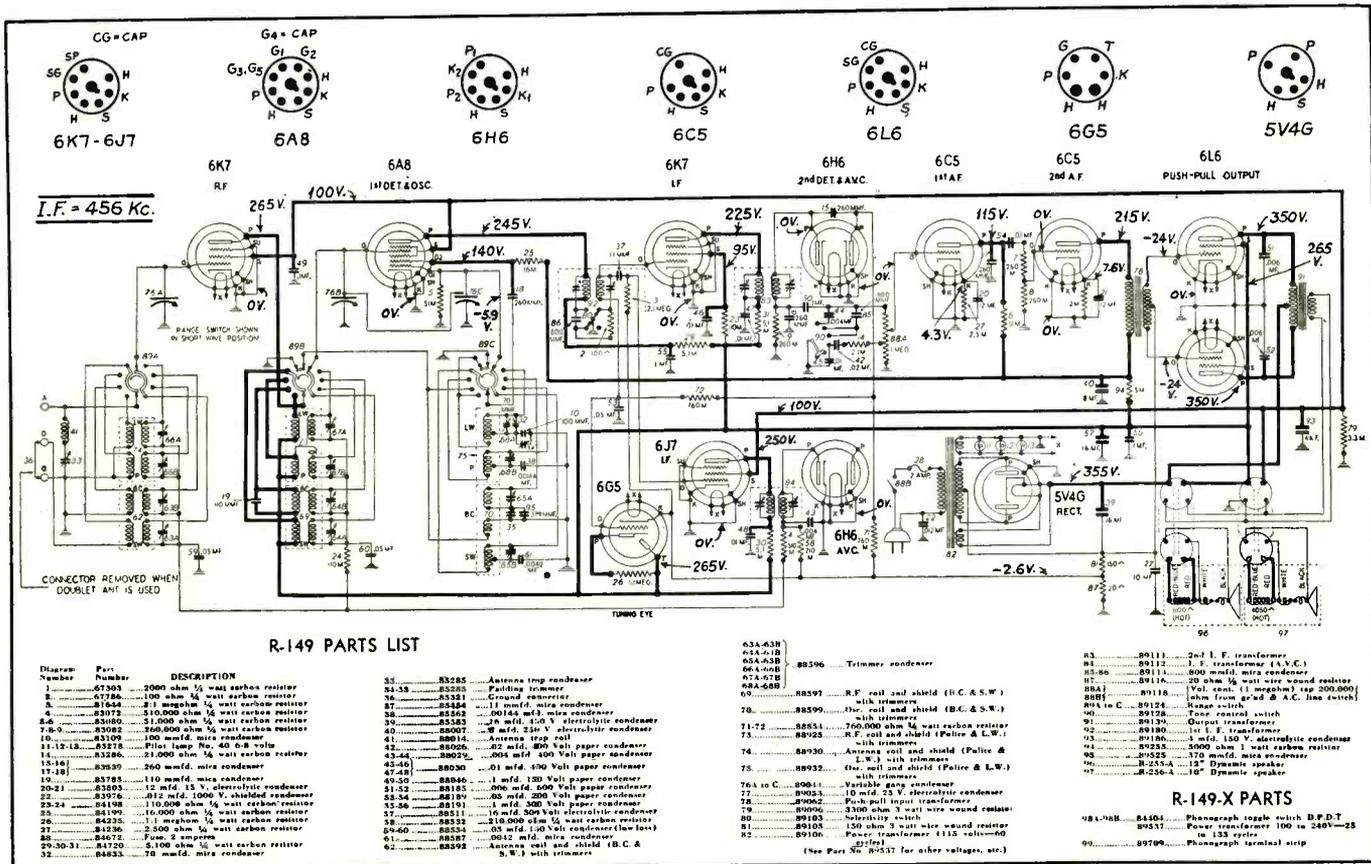


Fig. 1. Stewart Warner R-149 circuit diagram.

GENERAL DATA—continued

oscillator cannot give this much 456-kc output, the avc amplifier can be aligned immediately after completing the broadcast alignment by means of a 1500-kc signal fed into the antenna terminal, with the receiver tuned to the signal.

(c) Readjust the volume control so that the output meter shows about half-scale deflection.

(d) Adjust the two avc amplifier trimmers Nos. 5 and 6 for *minimum output-meter deflection*. Readjust the volume control or oscillator output to the point necessary to obtain a clearly defined point of minimum output when adjusting the trimmers.

(e) Reduce the oscillator output to normal and turn the volume control full on and repeat the adjustment of the i-f trimmers.

ADJUSTMENT OF WAVE TRAP

(a) Leave the test oscillator at 456 kc, but connect the oscillator output to the A and G terminals of the receiver with a 400- or 500-ohm carbon resistor in series with the oscillator output and the A terminal.

(b) Adjust the wave-trap trimmer No. 7 for *minimum output*. Increase the oscillator output as necessary to obtain a clearly defined point of minimum output. If some particular station with a frequency slightly different from 456 kc causes code interference, it may be advisable to adjust trimmer No. 7 on the actual frequency of the interfering station.

DIAL CALIBRATION

(a) Check the position of the dial pointer on its shaft by turning the tuning knob until the rotor plates of the gang condenser are in full mesh. The slow-moving dial pointer should then coincide with the low-frequency end of the dial scale. If it does not, hold the dial gear and turn the pointer to the correct position.


(b) Turn the range-switch control to the broadcast position (second from the right).

(c) Connect a 400- or 500-ohm carbon resistor in series with the test oscillator output and the receiver antenna terminal. *Note:* This resistor should remain connected for all subsequent adjustments.

(d) Ground the receiver.

(e) Adjust the test oscillator to exactly 1500 kc.

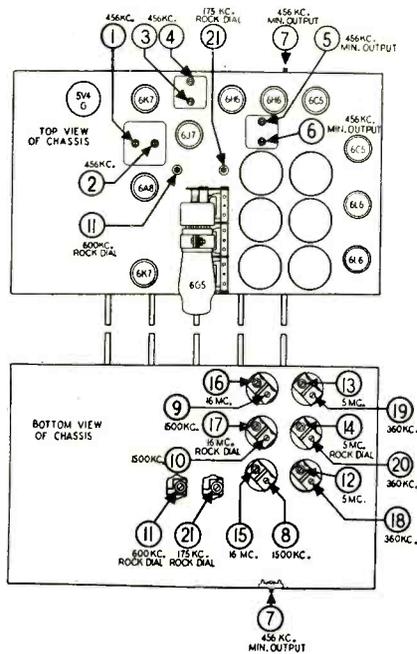(f) Tune in the 1500-kc oscillator signal or a station above 1300 kc on the dial and determine whether the dial calibration is correct at the high-frequency end of the dial. If the calibration is correct, do not adjust the broadcast oscil-



Figs. 2 and 3. Tube and trimmer locations.

lator shunt trimmer No. 8. If the calibration is incorrect, adjust trimmer No. 8 to give proper calibration.

BROADCAST-BAND ALIGNMENT

(a) With the test oscillator set at 1500 kc tune the receiver to the signal for maximum output and adjust the broadcast antenna and detector shunt trimmers Nos. 9 and 10 for maximum output. Do not touch the oscillator shunt trimmer No. 8 as this will change the calibration.

(b) Adjust the test oscillator to exactly 600 kc and tune the receiver to the signal. Adjust the broadcast oscillator series padder No. 11 for maximum output. Then try to increase the output by detuning the padder and retuning the receiver dial. If this reduces the output, detune the padder on the opposite direction. Continue detuning the padder and retuning the dial until a maximum output meter deflection is secured. This operation is commonly known as "rocking." The object of this adjustment is to find the combination of padder adjustment and tuning-condenser position which gives the maximum output. This adjustment should not be changed regardless of whether the dial reads exactly 600 kc or slightly off 600 kc for maximum output.

(c) Check the adjustment of trimmers No. 8, 9 and 10 at 1500 kc.

POLICE-BAND CALIBRATION

(a) Turn the range switch to the band No. 3 (green) position (second from the left).

(b) Adjust the test oscillator to exactly 5.0 megacycles.

(c) Tune in the 5-mc oscillator signal at or near 5 mc on the receiver dial to determine whether the receiver dial calibration is correct at 5 mc. If it is, do not adjust police band oscillator shunt trimmer No. 12. If the calibration is incorrect, set the dial pointer to 5 mc on the dial, and adjust the oscillator shunt trimmer No. 12 until the oscillator signal comes in at this point. If there are two peaks, the proper one is that with the trimmer screw farthest out.

POLICE-BAND ALIGNMENT

(a) With the test oscillator set at 5.0 mc tune the receiver for maximum output.

(b) Adjust the police-band antenna and detector trimmers Nos. 13 and 14 for maximum output. After this is done try to increase the output meter reading by detuning the detector trimmer No. 14 slightly and retuning the receiver dial. If the output goes down, detune the trimmer in the opposite direction. Continue detuning No. 14 and retuning the set until maximum output-meter deflection is secured. Then readjust No. 13.

SHORT-WAVE BAND CALIBRATION

(a) Turn the range switch to the extreme left (counterclockwise).

(b) Be sure that the D and G terminals on the antenna terminal strip are connected together.

(c) Adjust the test oscillator to exactly 16 megacycles.

(d) Tune in the 16-mc oscillator signal at or near 16 mc on the receiver dial to determine whether the receiver dial calibration is correct at 16 mc. If it is, do not adjust the short-wave band oscillator shunt trimmer No. 15. If the calibration is incorrect, set the receiver dial pointer exactly at 16 mc and adjust the oscillator shunt trimmer No. 15 until the oscillator signal comes in at this point.

(e) Check to see that trimmer No. 15 is adjusted to the proper peak by tuning the receiver to approximately 15.1 mc. If a repeat signal is not heard at this point, even with greatly increased oscillator output, retune the receiver to 16.0 mc and adjust trimmer No. 15 to the proper peak with the trimmer screw farther out.

SHORT-WAVE BAND ALIGNMENT

(a) With the test oscillator set at 16 mc tune the receiver for maximum output.

(b) Adjust the short-wave antenna and detector trimmers No. 16 and 17 for maximum output. After this is done, try

GENERAL DATA—continued

to increase the output-meter deflection by detuning the detector trimmer No. 17 slightly and retuning the receiver dial. If this causes the output to drop, detune the trimmer in the opposite direction. Continue detuning No. 17 and retuning the set until the output is at a maximum. Then readjust No. 16.

(c) Check the adjustment of No. 17 by tuning the receiver to the image at 15.1 mc and noting if the image is much weaker than the 16-mc signal. If the signal at 15.1-mc dial setting is equal to or stronger than the 16-mc signal, trimmer No. 17 is not set to the proper peak. Turn the trimmer in a turn or so, then readjust.

LONG-WAVE BAND CALIBRATION

(a) Turn the range switch to the extreme right position (clockwise).

(b) Adjust the test oscillator to exactly 350 kc.

(c) Turn the receiver dial pointer to 350 kc on the tuning dial and adjust the long-wave band oscillator shunt trimmer No. 18 for maximum output.

LONG-WAVE BAND ALIGNMENT

(a) With the test oscillator set at 350

kc, tune the receiver to the signal for maximum output.

(b) Adjust the antenna and detector trimmers Nos. 19 and 20 for maximum output. Do not touch the oscillator trimmer No. 18 as this will change the calibration.

(c) Adjust the test oscillator to exactly 175 kc and tune the receiver to the signal. Adjust the long-wave oscillator series padder No. 21 for maximum output, then try to increase the output by detuning the padder No. 21 and retuning the receiver dial.

(d) Repeat adjustments of trimmers Nos. 18, 19 and 20 at 350 kc.

Crosley Model 1016

The Crosley model 1016 is a ten-tube superheterodyne receiver and is available either with a standard 110 volt—60 cycle power transformer or with a universal power transformer.

The tubes used are 6K7 r-f amplifier, 6A8 modulator, 6C5 oscillator, 6K7 i-f amplifier, 6R7 detector and first audio amplifier, 6C5 second audio amplifier, two 6N6 output tubes, 5Z4 rectifier and the newly developed phantom conductor or volume expander tube.

The tuning range of the receiver is from 540 to 19,000 kc and is divided into three bands as follows: the blue band from 540 to 1,900 kc; the red band from 1.9 to 6.5 mc and the green band from 6.0 to 19.0 mc.


THE AUTO EXPRESSIONATOR

The auto-expressionator tube (phantom conductor) is connected across the voice coil of the speaker. When it is operating its resistance varies so as to increase the volume of loud tones, thus giving a wider volume range to reproduced music which tends to compensate for the electrical limitations of broadcasting equipment.

SOCKET VOLTAGES

The tube socket voltages are measured from the tube socket contacts to the chassis with a 1000-ohm-per-volt, 500-volt voltmeter (except filaments) with the receiver in operating condition and no signal input. The a-c filament voltages should be measured with an accurate low-range voltmeter. Readings may vary plus or minus 10 percent of values given.

The model 1016 chassis for use on

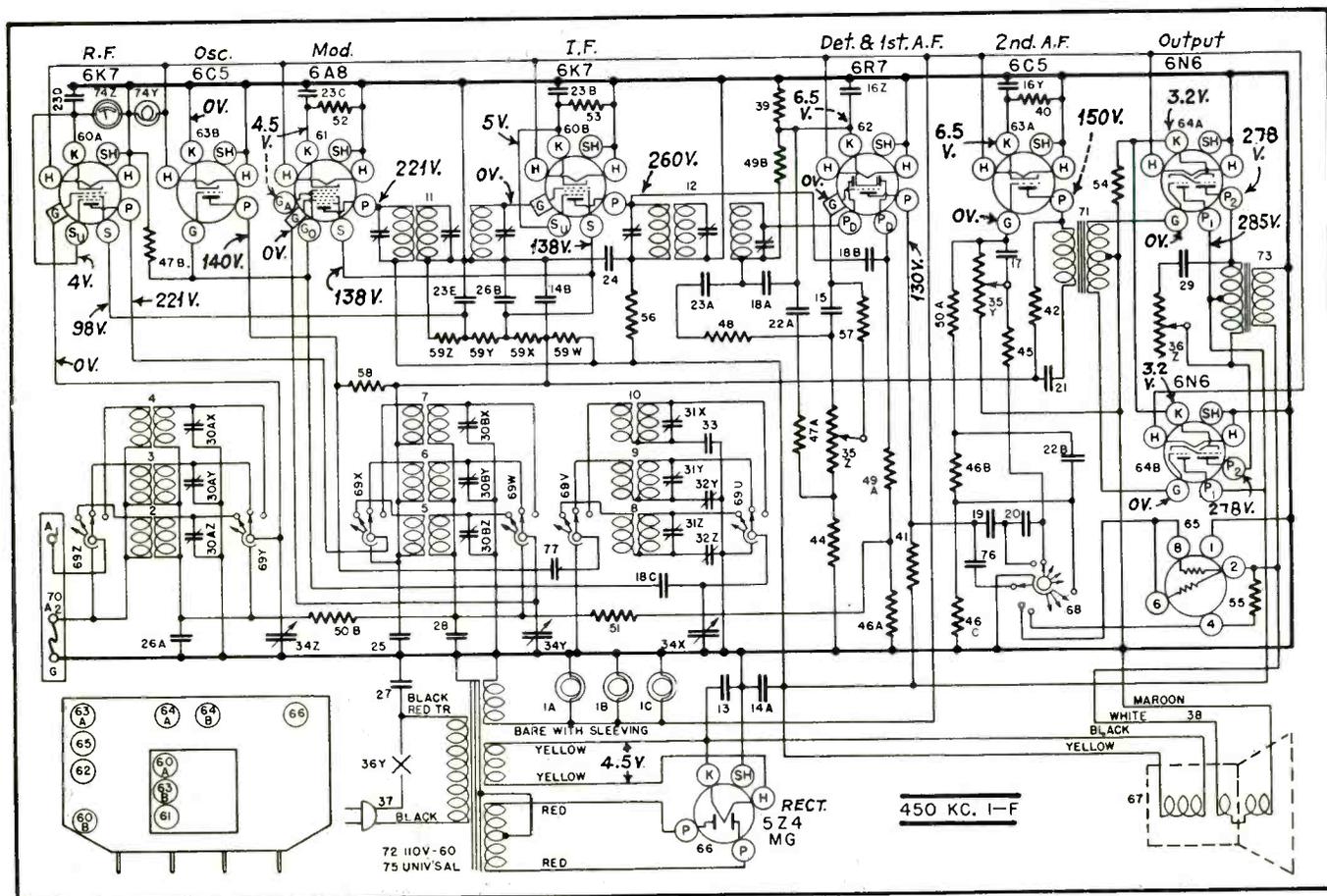

Crosley Model 1016 circuit diagram.

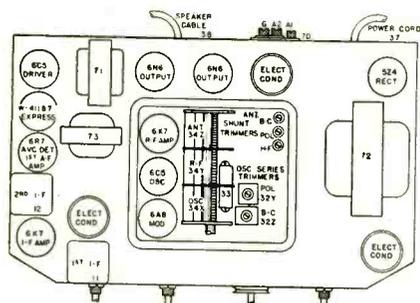


Fig. 2. Tube and trimmer locations.

other than 110 volts—60 cycles, is supplied with a universal power transformer designed to operate on a power supply of from 95 to 267 volts and any commercial frequency of 25 cycles or above. To adapt the set to a different line voltage it is necessary to remove the chassis from the cabinet, remove the bottom from the chassis, locate the terminal strip on the bottom of the power transformer and locate the wire leading from the power switch to the terminal strip. After careful measurement of the maximum values of line voltage, unsolder the wire described above from the lug on the terminal strip and solder it to the correct lug. The correct lug will be the one marked so as to cover or nearly cover the maximum line voltage. The maximum line voltage should not exceed the highest voltage stamped on the terminal strip beside the lug to be used by more than 3 percent.

PHONOGRAPH PICKUP

Chasses equipped with a universal power transformer also have three terminals on the back for connecting a phonograph pickup. These terminals are marked "P C S" and the pickup is connected through a double pole—single throw switch to these terminals as shown in Fig. 4.

ALIGNMENT PROCEDURE

This is a high-fidelity receiver and in order to secure maximum performance the alignment of its circuits should be done with precision instruments.

The i-f amplifier employs two triple-tuned i-f transformers and under no condition should their trimmer condensers be readjusted to determine if they are properly tuned.

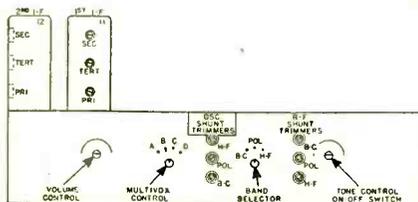


Fig. 3. Trimmer locations.

PARTS LIST (SEE FIG. 1)

Condensers		Resistors	
No.	Capacity	No.	Ohmage
13	35 mfd 400 v	35Z	Volume control 1st a-f 3 meg
14A	40 mfd 300 v	35Y	Volume control 2nd a-f 1 meg
14B	40 mfd 300 v	39	2,700 ohms ¼ w
15	.00001 mfd	40	1,100 ohms ½ w
16Z	12. mfd 25 v	41	65,000 ohms ½ w
16Y	12. mfd 25 v	42	20,000 ohms 1 w
17	.000025 mfd	44	1 megohm ¼ w
18A	.0001 mfd	45	300,000 ohms ¼ w
18B	.0001 mfd	46A	500,000 ohms ¼ w
18C	.0001 mfd	46B	500,000 ohms ¼ w
19	.05 mfd 400 v	46C	500,000 ohms ¼ w
20	.0005 mfd	47A	40,000 ohms ¼ w
21	.3 mfd 160 v	47B	40,000 ohms ¼ w
22A	.023 mfd 200 v	48	150,000 ohms ¼ w
22B	.023 mfd 200 v	49A	400,000 ohms ¼ w
23A } to } 23E }	.02 mfd 160 v	49B	400,000 ohms ¼ w
24	.02 mfd 400 v	50A	100,000 ohms ¼ w
25	.01 mfd 400 v	50B	100,000 ohms ¼ w
26A	.05 mfd 200 v	51	1.5 megohms ¼ w
26B	.05 mfd 200 v	52	350 ohms ½ w
27	.01 mfd 400 v	53	500 ohms ½ w
28	.05 mfd 200 v	54	40 ohms ¾ w
29	.05 mfd 400 v	55	1. ohm 2½ w
33	h-f fixed series cond.	56	2,000 ohms 1¼ w
76	.036 mfd 400 v	57	60,000 ohms ¼ w
77	.006 mfd 400 v	58	15,000 ohms w
		59	Candohm

I-F ALIGNMENT

(a) Connect one terminal of the output meter to P2 of one of the 6N6 output tubes and the other terminal through a 0.1-mfd or larger, condenser (not electrolytic) to P2 of the other 6N6 output tube.

(b) Connect the output of the signal generator through a 0.02-mfd condenser to the top cap of the 6K7 i-f amplifier tube, leaving the tube's grid clip in place. Connect the ground lead from the signal generator to the "Gnd" terminal of the receiver chassis. Keep the generator output lead as far as possible from the grid leads of the other screen-grid tubes.

(c) Set the band selector switch to the broadcast-band and rotate the station selector to approximately 60 on the dial. Turn the volume control knob to the right (On), turn the tone control knob to the left (Treble) and turn the Multivox control knob to the auditorium position (third position in the clockwise direction).

(d) Set the signal generator to 450 kc.

(e) Close the middle trimmer condenser on the second i-f transformer (Tert. Fig. 3) so that it is moderately tight. (Do not force the adjustment screw).

(f) Adjust the top trimmer and then the bottom trimmer (Sec. & Pri) of the second i-f transformer for maximum

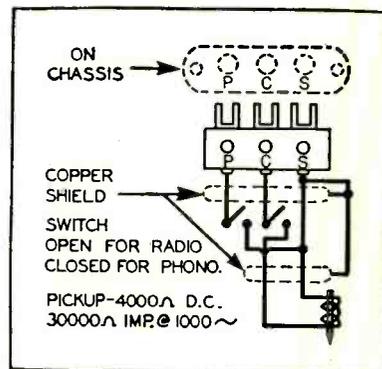


Fig. 4. Phonograph pickup connections.

output. Always use the lowest signal generator output that will give a reasonable reading on the output meter.

(g) Transfer the output lead-of the signal generator from the 6K7 tube to the top cap of the 6A8 modulator tube, leaving the tube's grid clip in place.


(h) Open the middle trimmer of the first i-f transformer three or four turns from the closed position. (Care should be taken that the adjustment screw does not become dislodged from the nut).

(i) Adjust the top trimmer and then the bottom trimmer of the first i-f transformer for maximum output.

(j) Transfer the output lead of the signal generator from the 6A8 tube to the "Ant" terminal of the receiver and increase the output of the signal generator, if necessary.

(Continued on page 580)

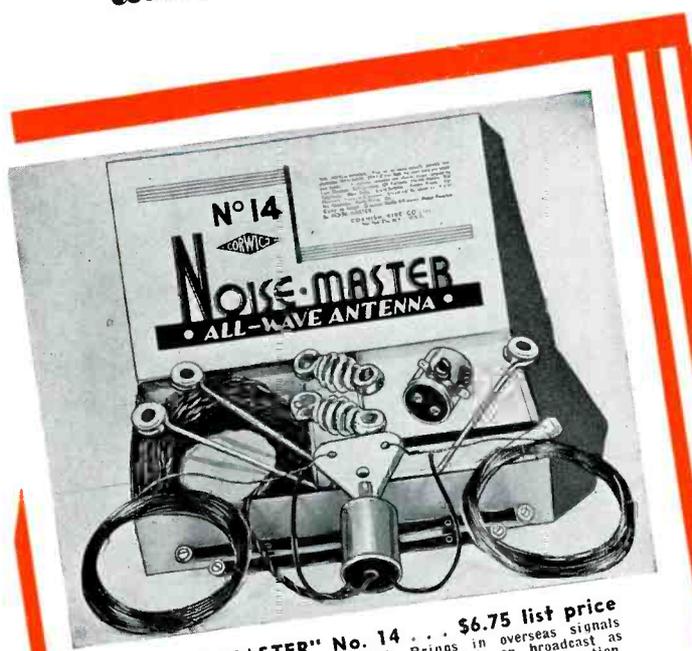
**"man-made" static
and radio don't harmonize**



"NOISE-MASTER" No. 14 . . . \$6.75 list price
Amy, Aceves & King patented. Brings in overseas signals stronger, and eliminates "man-made" static on broadcast as well as shortwave band. For better reception in EVERY location.



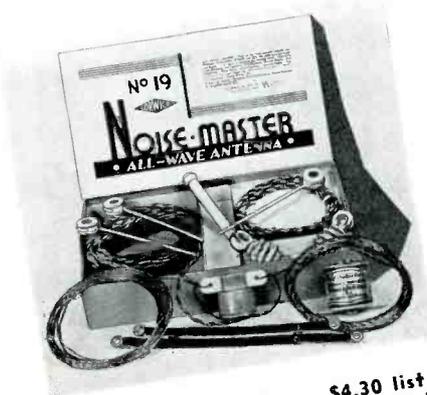"NOISE-MASTER" No. 18 . . . \$3.40 list price
First time at this popular price: licensed Amy, Aceves & King antenna of simple doublet type. SELF-SELECTING. recommended for clarifying shortwave reception.



"NOISE-MASTER" No. 19 . . . \$4.30 list price
SELF-SELECTING doublet type, Amy, Aceves and King licensed, with junction-box in the antenna line. Assures excellent all-wave reception.



EVERY service man knows that refrigerators and burners and numerous other modern electrical appliances play "hob" with radio receiving, unless there is provided some method of combating the nuisance noises which they generate.

"NOISE-MASTER," most modern of antennas, effectually strains this "man-made" static out of any radio set. Properly installed in any location, this masterpiece of radio engineering insures better reception.

**On Broadcast As Well As
On Shortwave Frequencies**

Licensed by Amy, Aceves & King . . . engineered with typical CORWICO thoroughness. Figure this helpful unit into your merchandising plans . . . for profits and GOOD WILL.

Be sure your name is on our mailing list for helpful literature issued from time to time.


CORNISH WIRE CO., INC.
30 CHURCH STREET
NEW YORK CITY



This trademark is your guarantee of the very finest in antennas and radio wire products . . . an acknowledged standard in the field.

SUPREME

585 DELUXE DIAGNOMETER

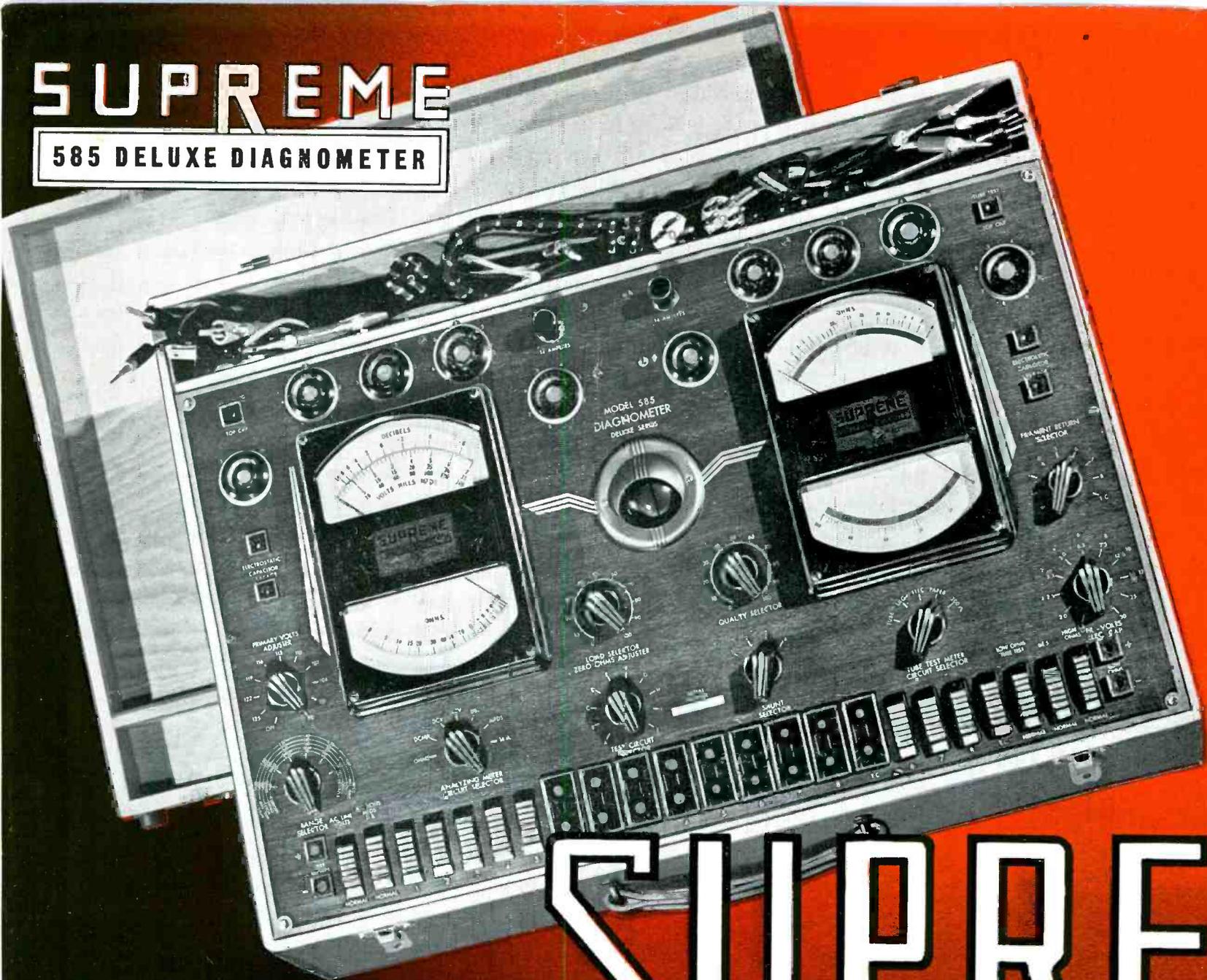


SUPREME

17 NEW TEST INSTRUMENTS

555 DIAGNOMOSCOPE

Every up-to-date serviceman realizes that he must purchase complete cathode ray equipment if he is to remain at the top of his profession and be able to service the new modern receivers in a satisfactory manner. You have probably been considering the purchase of this type of instrument, but have hesitated because you were confused as to which instruments were best suited for your purpose, and were in doubt as to how many of the instruments were actually necessary for a complete servicing installation. Supreme has solved your problem by combining in one instrument all of the equipment necessary for modern up-to-date cathode ray service work and in addition offers you convenient time payment terms so that you may purchase this instrument now without waiting until you are ready to pay all cash.

The Diagonoscope is actually four instruments in one. It includes a complete oscilloscope, an A.C. operated Signal Generator covering all wave bands, a "wobbler" and an adjustable audio oscillator. Without these four instruments, no cathode ray installation is complete. It is certainly much more convenient to have all instruments in one unit, thus requiring less space and with less possibility of confusion. The entire instrument is housed in a beautifully designed, streamlined metal case with all controls arranged in convenient positions. The screen of the cathode ray tube is at a convenient height and at the proper angle, and the entire instrument has been designed to be easy to understand and operate. Ten tubes. Completely A.C. operated.

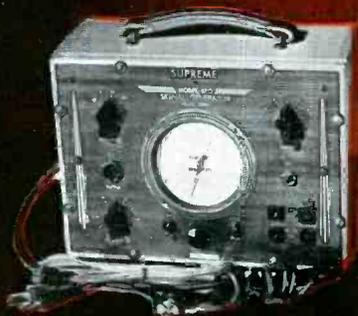

570 SIGNAL GENERATOR

Straight Signal Generator, without "wobbler," but can be used with external "wobbler" for cathode ray work. Seven bands from 125 k.c. to 60 m.c. — first five bands fundamentals — last two harmonic relations of fifths. External or internal modulation. 400 cycle note available externally. Carefully shielded.

\$4.00 Down—\$3.90 per month for 8 months. Cash Price—\$31.95

"I WILL SELL YOU ANY SUPREME INSTRUMENTS ON S. I. C. EASY TERMS"

Your Parts Jobber

SUPREME INSTRUMENTS

EXPORT DEPT., ASSOCIATED EXPORTERS CO., 145 WEST 45th

585 DELUXE DIAGNOMETER

This magnificent instrument (illustrated at the left) is the most complete portable radio test equipment built today. Combines the functions of 19 essential servicing instruments in one compact unit — 47 functions and ranges!

It is a: Point to point analyzer, also Supreme Free Reference Point Analyzer through one master cable. Tube Quality Checker. Tube leakage and short tester. Electrolytic capacitor leakage and capacitor checker. Electrostatic leakage and capacity checker. Multi-range DC voltmeter. Multi-range ohmmeter. Multi-range AC voltmeter. Multi-range Milliammeter. Multi-range decibel meter. Multi-range capacity meter. Multi-range output meter. DC ammeter. Multi-range megohmmeter. Low-range ohmmeter. Built-in power supply.

Model 585 has two big, double-window, illuminated, Quadrimeters — the latest development in test meters, and built under patented Supreme specifications. Housed in a handsome quartered oak carrying case. Write for big Technical Manual "A" on this and other Supreme equipment — OVER 75 PAGES — FREE!

Sold by YOUR Parts Jobber on S. I. C. Easy Terms
— \$10.00 Down — \$8.00 per month for
12 months. Cash Price \$96.95

500 AUTOMATIC

A very popular new model. Incorporates 27 Functions and ranges as follows: English reading scale tube quality A.C. checker. Tube leakage and short indicator. Electrolytic and electrostatic capacitor leakage checker. Multi-range D.C. voltmeter. Multi-range E.C. milliammeter. Multi-range A.C. voltmeter. Multi-range ohmmeter. Multi-range decibel meter. Multi-range output meter.

\$7.50 Down — \$6.61 per month for 10 months.
Cash Price — \$66.95

550 RADIO TESTER

Performs the operations of 13 essential servicing instruments with 43 functions and ranges: Radio and P.A. analyzer. Electrolytic and electrostatic capacitor leakage and capacitor tester. Multi-range ohmmeter. Multi-range D.C. voltmeter. Multi-range A.C. voltmeter. Multi-range milliammeter. Multi-range decibel meter. Multi-range output meter. D.C. ammeter.

\$6.00 Down — \$5.55 monthly for 10 months.
Cash Price — \$55.95



SUPREME

585 DIAGNOSCOPE

ME MENTS

Every serviceman can now own this very latest and most modern test instrument!

Sold by YOUR PARTS JOBBER for only \$15.30 Down — \$12.05 monthly for 12 months
Cash Price — \$147.95

NTS CORP., GREENWOOD, MISSISSIPPI, U. S. A.
STREET, NEW YORK CITY, N. Y. • CABLE ADDRESS, LOPREH, N. Y.

RAYTHEON TUBES
ARE NOT "CHINESE COPIES!"

RAYTHEON
TRADE MARK


MAKERS OF THE FAMOUS 4-PILLAR TUBES

RAYTHEON HAS ONE OF THE LARGEST, MOST PROGRESSIVE TUBE LABORATORIES IN THE WORLD—OPERATED BY INTERNATIONALLY FAMOUS SCIENTISTS.

WITH THE DEVELOPMENT OF NEW TUBES AND CIRCUITS, ENGINEERS OF LEADING SET MANUFACTURERS LOOK TO RAYTHEON'S ENGINEERS TO SUPPLY THEM WITH TUBES OF UNIFORM EXCELLENCE TO MEET THEIR EXACTING REQUIREMENTS THAT IS WHY USING RAYTHEONS AS REPLACEMENTS IS SO WISE—AND PROFITABLE. THEY ARE NOT "CHINESE COPIES"—THEY REPRESENT REAL CONTRIBUTION TO THE RADIO ART. RAYTHEON'S ENGINEERING STAFF AND PRODUCTION FACILITIES GUARANTEE LESS REJECTS, LESS ADJUSTMENT TROUBLE, AND REAL UNIFORMITY. RAYTHEON'S CLOSE INSPECTION TOLERANCE LIMITS ARE YOUR INSURANCE OF GREATER TUBE PROFIT.

LICENSED SET MANUFACTURERS EQUIP THEIR SETS WITH RAYTHEON TUBES BECAUSE THE NAME RAYTHEON INSURES TRADE AND CONSUMER QUALITY APPEAL, AND HIGHER COMPARATIVE SET UNIT PRICES WITH LESS SALES RESISTANCE.

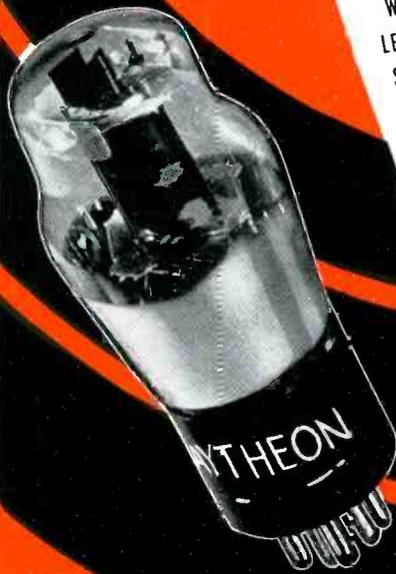USED AND DEMANDED BY ALL LEADING RADIO PARTS DEALERS AND SERVICEMEN.



THE MOST COMPLETE LINE—ALL TYPES OF GLASS, OCTAL BASE, METAL AND AMATEUR TRANSMITTER TUBES

RAYTHEON PRODUCTION CORPORATION
420 Lexington Ave., New York, N. Y.

445 Lake Shore Drive, Chicago, Illinois

415 Peachtree Street, N. E., Atlanta, Ga.

55 Chapel Street, Newton, Mass.

555 Howard Street, San Francisco, Calif.

Auto-Radio . . .

Studebaker Philco S-1431

The model S-1431 is a 6-tube super-heterodyne auto-radio receiver in two units. Power for the operation of the various tube circuits is obtained from the 6-volt storage battery supply. The circuit diagram is shown in Fig. 1.

An r-f stage using a type 78 tube is employed ahead of the 6A7 combination first-detector-oscillator. The front section (nearest the control shaft) together with a padding condenser (No. 18, Fig. 2) tune the oscillator coil maintaining the frequency difference between the local set oscillator and the incoming signal. A single i-f stage is employed using a type 78 tube and a doubly tuned i-f transformer. Another doubly tuned i-f transformer is used to feed the diode plates of the 75 tube used as second detector, avc and first audio stage. A type

41 tube is used as an output amplifier to drive the loudspeaker.

ALIGNMENT PROCEDURE

The output meter should be connected through an 0.25-mfd capacitor, by means of an adaptor, to the plate of the type 41 output tube and to the receiver chassis.

With the receiver and signal generator set up for operation at the prescribed frequency, turn the receiver volume control on full and set the signal generator attenuator so that the output meter gives a readable indication. The signal in the speaker should be audible but not loud.

The shielding on the signal generator output lead should be grounded to the receiver chassis.

I-F ALIGNMENT

Set the signal generator at exactly 260 kc. Connect the generator output

lead to the grid cap of the 78-i-f tube in series with an 0.1-mfd capacitor (without removing the grid cap).

Adjust the secondary screw padder (No. 27, see Fig. 2) on the second i-f transformer for maximum reading on the output meter. Then adjust the primary screw padder (No. 25, Fig. 2) for maximum reading.

Remove the generator lead from the 78 tube to the grid cap of the 6A7 tube in series with a 0.1-mfd capacitor (without removing the grid cap). Adjust the secondary screw padder No. 23 on the first i-f transformer for maximum reading on the output meter. Then adjust the primary screw padder No. 21 for maximum reading. See Fig. 2 for location of the padding condensers.

Always maintain the signal generator attenuator at the lowest possible setting consistent with obtaining a readable indication on the output meter.

Repeat the i-f adjustments to assure correct alignment.

R-F ALIGNMENT

After padding the first i-f stage re-

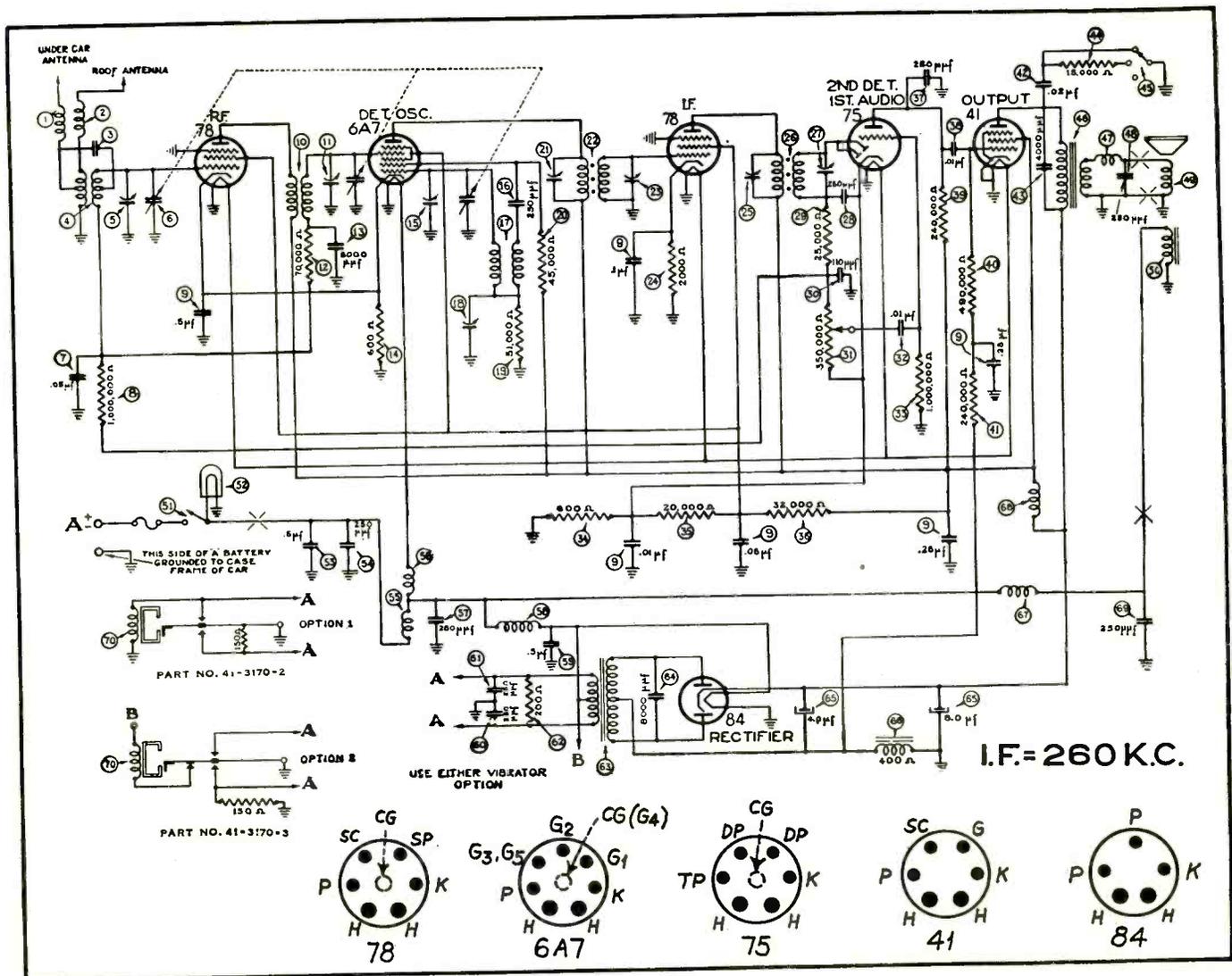


Fig. 1. Studebaker Philco S-1431 auto radio.



Elim-O-Stat

RADIO NOISE-SUPPRESSOR (TYPE RA)

SMALL AND INEXPENSIVE! EFFECTIVE! A reliable product, offering continuous profit possibilities. Built to meet the wide demand for a *really efficient* low-priced noise-eliminator. The attractive carton will do a selling job for you. Ask for details.

Solar supplies a complete line of Elim-O-Stats for suppressing all radio disturbances. A special Solar Interference Laboratory is constantly at work solving appliance-manufacturers' problems in this field, and engineering the most modern types of standard noise eliminators. These Elim-O-Stats are built to increase both Radio Enjoyment and Your Profits. Ask for Solar catalog EL-2.

SOLAR MFG. CORP



599-601 BROADWAY
NEW YORK CITY

MANUFACTURING AFFILIATES IN

LONDON, PARIS, BERLIN, MILAN

NOVEMBER, 1936 •

SAY YOU SAW IT IN SERVICE

569

i-f transformer are tuned by small trimmer condensers.

A local-distance switch is employed to reduce the sensitivity for city driving. When the switch is in the local position, resistor R15 is in series with r-f and i-f bias resistor R8, causing a reduction in sensitivity. When the switch is in the distant position resistor R15 is short circuited and full sensitivity is obtained.

A 6B7 duo-diode pentode tube functions as a diode second detector, avc tube and a one-stage audio amplifier. Avc voltage is applied to the control grid circuits of the 6K7 r-f and i-f tubes. The manual volume control varies the audio voltage applied to the grid of the 6B7 tube.

Resistance coupling is used between the first audio stage and the second audio stage which employs a 41 tube. The latter is transformer coupled to the output stage which uses a 6A6 tube. This tube is a Class B power amplifier and combines 2 triodes in one envelope. A dynamic reproducer is used.

Provision is made for single roof speaker and dual speaker (chassis and roof) connections. The electrical connections for the different speaker installations are shown in the schematic. When single chassis or roof speakers are used the entire output-transformer secondary is connected to the speaker voice coil. When dual 5¼-inch roof and 6-inch chassis speakers are used, the 5¼-inch speaker voice coil is across the entire output transformer secondary and the 6-inch speaker voice coil is connected to the tap on this secondary. When dual 8-inch roof and 6-inch chassis speakers are used, the voice coils of both speakers are connected to the output-transformer secondary tap.

A synchronous type vibrator is used in the power unit. This vibrator interrupts the current through the primary of the power transformer and also rectifies the current in the secondary circuit.

Polarity in inserting the vibrator must be observed. It can be inserted in

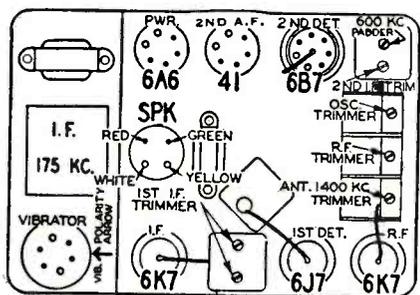


Fig. 2. Tube and trimmer locations.

two ways, and the correct method depends on which terminal of the car storage battery is grounded. Full instructions are on the vibrator.

ALIGNMENT PROCEDURE

Misalignment of condensers generally manifests itself as broad tuning and lack of volume at portions or all of the standard-wave band. The radios are all properly aligned at the factory with precision instruments and realignment should not be attempted unless all other possible causes of the faulty operation have first been investigated and unless the service technician has the proper equipment.

A signal generator that will provide accurately calibrated signals over the standard-wave band and at the intermediate frequency, and an output meter are required for indicating the effect of adjustments.

Use a non-metallic screwdriver for the adjustments. The complete procedure is as follows:

I-F ALIGNMENT

Set the signal generator for a signal of 175 kc.

Connect the output of the signal generator through a 0.05-mfd condenser to the stator of the r-f interstage section of the tuning condenser. (See Fig. 2 for location of this section.)

Connect the ground lead of the signal generator to the chassis ground.

Turn the local-distance switch to the distance position and keep it in this position for all adjustments.

Set the volume control at the maximum position.

Attenuate the signal from the signal generator to prevent the leveling-off action of the avc.

Then adjust the three i-f trimmers until maximum output is obtained. The location of these trimmers is shown in Fig. 2.

R-F ALIGNMENT

1575 kc adjustment: Set the signal generator for 1575 kc. Turn the rotor of the tuning condenser to the full open position.

If a low capacity antenna is used, connect the shielded antenna lead from the chassis through a 150-mmfd condenser to the antenna post of the signal generator. (If high capacity, use 1500 mmfd.) The antenna plug must be correctly inserted, dependent on the capacity of the antenna used.

For this and all subsequent adjustments keep the volume control at the maximum position and attenuate the

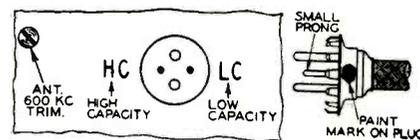


Fig. 3.

signal from the signal generator to prevent avc action.

Adjust the trimmer of the oscillator section of the three-gang condenser until maximum output is obtained—see Fig. 2 for location of this trimmer.

1400 kc adjustment: Set the signal generator for 1400 kc. Turn the rotor of the tuning condenser carefully until maximum output is obtained.

Adjust the r-f interstage and antenna 1400 kc trimmers for maximum output.

Do not change the setting of the oscillator trimmer.

600 kc adjustment: Set the signal generator for 600 kc. Connect the output of the signal generator through a 0.05-mfd condenser to the control grid of the 6K7 r-f tube.

Turn the tuning condenser rotor until maximum output is obtained. Then turn the tuning condenser rotor back and forth, at the same time adjusting the 600-kc padder (see Fig. 2) until the peak of greatest intensity is obtained.

Re-connect the output of the signal generator to the shielded antenna lead through a 150-mmfd condenser (1500 mmfd if antenna is high capacity).

Adjust the 600-kc antenna trimmer to maximum. This trimmer is reached from the outside of the case—see Fig. 3.

Adjusting the 600-kc antenna trimmer: After the receiver is installed and the car antenna is connected, it will be necessary to adjust the antenna trimmer. Tune in a weak signal at approximately 600 kc with the volume control about three-fourths on. Turn the adjusting screw of the antenna 600-kc trimmer up or down until maximum output is obtained. See Fig. 3 for location of this trimmer.

As shown in this illustration, the antenna plug is inserted in one of two ways, depending on whether the car has a high or low capacity antenna.

CALIBRATING THE RADIO


To calibrate the radio, tune in a station of known frequency. At the back of the control head is the calibration screw. Remove the pilot lamp assembly. Insert a fine blade screwdriver and turn this screw until the pointer on the dial scale is at the frequency of the station being received. The knob must be held during this adjustment.



Most Complete Transformer
Line in the World

QUALITY • RELIABILITY

UTC Universal Beam Power Amplifier Kits

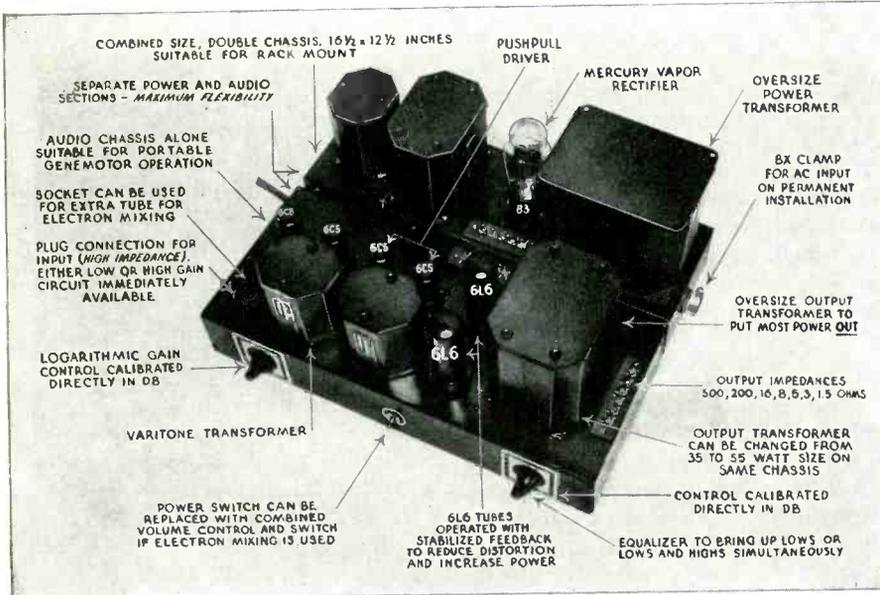

PAK amplifier kits feature:
Power output, 35 watts self bias, 55 watts fixed bias; gain 118 DB, immediate change-over to 95 DB; separate power supply and audio decks; stabilized feedback; mobile operation with genemotor —20 watts output; provision for electron mixer or low impedance input if desired.

PAK-1 Self bias amplifier kit. 35 watt operation. Output transformer impedances 500, 200, 16, 8, 5, 3, 1.5 ohms. Includes all accessories such as resistors, condensers, sockets, calibration plates, chassis, dust covers, hardware . . . except tubes. All fully mounted. **\$45.00**
Net Price

PAK-2 Fixed bias amplifier kit, 55 watts operating condition. Output transformer with impedances of 500, 200, 16, 8, 5, 3, 1.5 ohms. Includes all accessories such as resistors, condensers, sockets, calibration plates, chassis, dust covers, hardware . . . except tubes. All fully mounted. **\$48.00**
Net Price

PAK-1X and **PAK-2X** are available with high impedance output transformers for Ham Service. (No extra cost)

UTC Public Address Units

are a medium priced group of transformer components having the many exclusive and universal features associated with UTC products. Approximately 140 types of units are available in this group to take care of every PA and transmitting requirement.

PA-131 Transformer from 1 plate to 1 grid. 3:1 ratio. **2.70**
PA-1. Net Price

PA-132 From 1 plate to 2 grids. 2:1 ratio each side. Split sec. PA-1. Net Price. **3.00**

PA-133 From 2 plates to 2 grids. 1:75 ratio each side. Primary and secondary each in two sections. PA-1. Net Price. **3.60**

PA-233 From two 56, 6C6 triode, 6C5, or similar tubes to push pull 45's, 2A3's or 6L6's self or fixed bias. PA-1. Net Price. **3.60**

PA-333 This input transformer is designed to operate from 6C5's, or similar driver tubes to two 6L6's fixed bias. PA-1. Net Price. **3.60**

PA-433 From 45 or 2A3 plates to two or four fixed bias 6L6 grids. PA-2. Net Price. **3.90**


PA-134 500, 200, or 50 ohm line to single grid. PA-1. **3.90**
Net Price

PA-135 500, 200, or 50 ohm line to push pull grids. PA-1. **4.50**
Net Price

PA-136 Single plate or pickup and carbon mike or low impedance pickup to one or two grids. PA-1. Net Price. **4.50**

PA-428 Power transformers for push-pull 6L6 tubes, self or fixed bias. Primary, 115 v. a.c., 50-60 cycles. Secondaries 450-0-450 at 250 ma.; 6.3 VCT-4A, 6.3 VCT-2A, tapped at 2 1/2 volts-3A, 2 1/2 VCT-3A, 5 VCT-3A taps provided for bias supply. Net Price. **8.40**

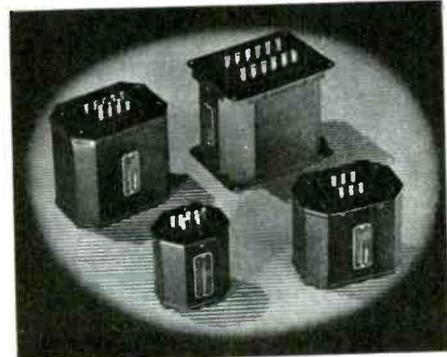PA-2L6 6600 ohms, plate to plate. Will match 35-40 watts output. Secondary impedance, 500, 200, 16, 8, 5, 3, 1.5 ohms. Net Price. **6.00**



PA-4L6 3800 and 3300 ohms, plate to plate. Will match two 6L6's fixed bias, 60 watts output; four 6L6's self bias, 60-80 watts output. Secondary impedance, 500, 200, 16, 8, 5, 3, 1.5 ohms. Net Price. **9.00**

PA-137 Mixing 500, 200, or 50 ohm line to 500, 200 or 50 ohm line. PA-1. Net Price. **3.30**

PA-138 Audio line matching. Will handle 20 watts audio power. Input 500 or 200 ohm line, Output 16, 8, 5, 3 and 1.5 ohms. PA-2. Net Price. **4.50**

PA-139 Audio line matching. Will handle 30 watts audio power. Input 500 or 200 ohm line. Output 16, 8, 5, 3, 1.5 ohms. PA-3. Net Price. **7.50**

UTC COMPONENTS AND CATALOGS ARE AVAILABLE AT YOUR FAVORITE DISTRIBUTOR

UNITED TRANSFORMER CORP.

72 SPRING STREET

NEW YORK, N. Y.

EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: "ARLAB"

Public Address . . .

COMPLETE VOLUME EXPANSION†

(See Front Cover)

By C. M. SINNETT*

DURING the last two years, steady progress has been made in the recording and processing of phonograph records. Better tonal balance and lower surface noise are two outstanding characteristics noted in a direct comparison between older and present-day recordings.

In an effort to parallel this improvement in records the RCA Engineering Department has been engaged in developing a phonograph amplifier that would do justice to these record improvements. The RCA Victor R-99 High-Fidelity Phonograph is the result of this development work.

A complete schematic diagram of the amplifier is shown in Fig. 1. To facilitate a better description of the functions of the various parts the volume-expansion circuit is segregated (on the front cover). Nine db of expansion are provided with a maximum of ten watts output. The frequency characteristic of

the amplifier (alone), feeding a speaker load, is flat within 5 db from 40 to 10,000 cycles. A peak approximately 5 db in height at 8,000 cycles, and a depression 3 db deep at 4,000 cycles, have been deliberately incorporated in the amplifier. Fig. 2 shows the overall frequency characteristic of the amplifier alone.

VOLUME EXPANSION EMPLOYED

The characteristics of the type 6L7 tube permit its use in a comparatively simple volume-expander circuit. This tube has a heater, a cathode, five grids, and a plate. Two of the five grids are control grids; the first (G_1) has a remote cut-off characteristic and the second (G_2) has a sharp cut-off characteristic. Of the three remaining grids, two are screens and one is a suppressor.

The schematic diagram of a volume expander is shown on the front cover. The signal to be expanded is fed to the remote cut-off grid (G_1) of the 6L7 and also to the input of a 6C5, as shown. The

output of the 6C5 is rectified by a 6H6; the positive terminal of the rectified output connects to the sharp cut-off grid (G_2) of the 6L7. The no-signal bias of this grid is such that G_1 -plate transconductance of the 6L7 is low (under 50 micromhos). When a signal is applied, the rectified voltage fed to G_2 increases the transconductance, and hence the gain, of the 6L7. This increase in gain is approximately proportional to the rectified diode voltage and, hence, to the signal amplitude.

THE AMPLIFIER CIRCUIT

The first audio stage employs a 6L7 as the volume-expander tube. Several circuit changes will be noted if comparison is made with the circuit of the RCA Victor D-22, the major ones being a lower value plate resistor R9, self-bias for the No. 1 grid by means of resistor R6, static bias adjusting resistor R20 for the No. 3 grid connected in the 6L7 cathode return, and series feed to the screen through resistor R8. The result is a considerable reduction in the amount of distortion in the tube as an audio amplifier, together with a somewhat less critical adjustment of the expansion starting point or normal gain setting. The 6L7 is resistance coupled to the next tube, a 6C5, which is transformer coupled to the push-pull 2A3 output stage. The 6C5 employs parallel feed in its plate circuit for the purpose of maintaining low frequency response and at the same time insuring that maximum voltage step-up to the next stage is obtained. The leakage reactance of transformer T3 causes a high-frequency peak at about 9,000 cycles. Since a peak at 8,000 is desirable, the two shunt condensers C12 and C13 serve the double purpose of reducing the frequency of the peak and at the same time prevent parasitic troubles in the grid circuits of the 2A3's. The primary shunt condenser C26 serves to depress the curve ahead of the peak as previously mentioned.

As on the D-22 the control amplifier tube is a 6C5 but is operated at higher gain than formerly, since less output is available from the magnetic pickup and input transformer system. Also, it will be noted that the rectifier is now a 6H6, employing a higher value diode resistor to make up for this loss in voltage. Resistor R19 and condenser C21 serve as a filter to prevent hash from the rectifier getting back to the No. 1 grid through the adjusting resistor R20 and grid leak R5. The time delay constants R7 and C7 are the same as were employed on the D-22. The rest of the amplifier is essentially conventional, but it should be noted that throughout the design of this unit special care has been taken to insure a low hum level. The arrangement

†From RCA Service News.
*RCA Engineering Dept.

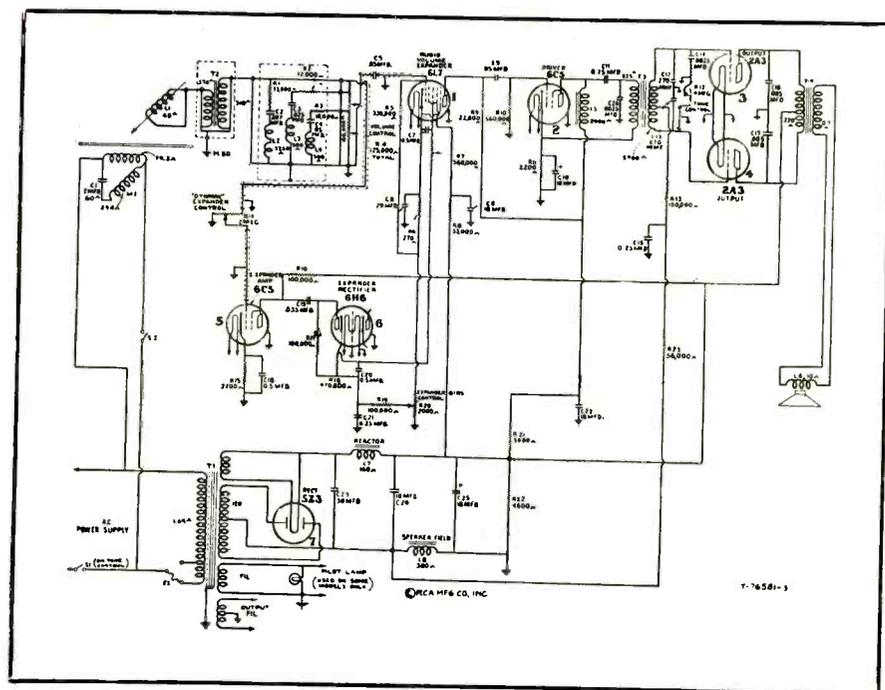


Fig. 1. RCA Victor R-99 high-fidelity phonograph amplifier.

the WHOLESALE WAY




SANDY THE SERVICEMAN
Says

If a few more servicemen could count pennies correctly, there'd be less worryin' 'bout how the rent was goin' t' be paid on the first o' the month. Tak the case o' my competitor. We're good frriends, and I try t' help him when I can. I've figured that his time costs him \$1.60 every hour his shop is open, and that he must get at least \$2.25 an hour if he wants to stay off the bread line like me. He goes doon to the shops and wastes hours and hours shoppin' aroon—and he NEVER GETS PAID FOR THAT TIME. He had a job the other day, and here's how the bill should hae looked:

One Condenser	\$1.20
Labor—1 Hour	2.25
(Time Spent in Shopping Around for the Proper Replacement Part Among Inadequate Stocks) 2 Hours.....	4.50
Gasoline—Wear and Tear on Car25
Total	\$8.20

But the only charge he made was for \$3.45—and he **LOST MONEY**. But I've convertrrt him now. He sent for a "WHOLESALE" catalog and he Shops in his Slippers—he worrks in the daytime and has his ease at night. Best of all, he has learned the value o' a dollar!

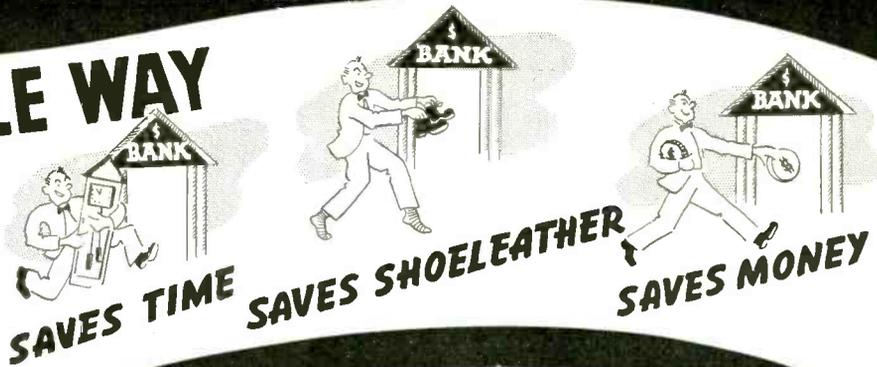He can see that Sandy is makin' a success of the serrvicin' game, and Sandy's best friend is the "Wholesale" catalog. Aye, Mon, 'tis smartt to be thriffty.



THOUSANDS of Smart Servicers have found out that buying the "Wholesale" way actually pays out in dollars and cents. They know that the "Wholesale" way is the Effortless way—the Economical way—the Swift way! Get the habit—Shop in your Slippers!

AT YOUR SERVICE!

From the Big Free Wholesale Radio Catalog you make your selection—the largest stock of radio equipment assures you of getting **WHAT** you want—the incredibly efficient Wholesale "Speed-Up" delivery service brings it **WHEN** you need it!

EVERYTHING YOU NEED IN RADIO

Whatever you require in radio — Wholesale has it! Parts—tubes—P. A. Systems—Amplifiers—test equipment—tools—hardware—a complete line of sets—S. W. and All-wave—farm radio—auto radio—all at "eye opening" low prices.

THERE'S GOLD IN THEM THAR HILLS AND DALES

The sale of phonograph records has increased 308% in the past 12 months . . . due to the vast numbers of radio owners who are having their receivers converted into phono-radio combinations. There's a swell profit margin in the sale and installation of turntables, pickups and automatic record changers. Dealers will find that a phono combination owner will be a steady customer for records.

The "WHOLESALE" radio catalog lists a complete line of pickups, record changers, turntables and two speed motors. The entire line is priced according to the value giving policy of "WHOLESALE," and includes a complete selection in EVERY price class—up to the famous Capehart Automatic Record Changers.

SEND FOR THIS CATALOG TODAY!

SEND NOW FOR FREE CATALOG

WHOLESALE RADIO SERVICE CO., Inc.
901 W. Jackson Blvd. Chicago, Ill.

RUSH FREE BLUE RIBBON RADIO CATALOG 65L5 CHECK
RUSH FREE XMAS ELECTRICAL CATALOG 67L5

NAME _____ STATE _____

STREET _____

CITY _____

WHOLESALE RADIO SERVICE CO., Inc.

CHICAGO, ILL. • NEW YORK, N. Y. • ATLANTA, GA.
901 W. JACKSON BLVD. 100 SIXTH AVENUE 430 W. PEACHTREE ST., N. W.

BRONX, N. Y.
542 E. FORDHAM RD.

NEWARK, N. J.
219 CENTRAL AVE.

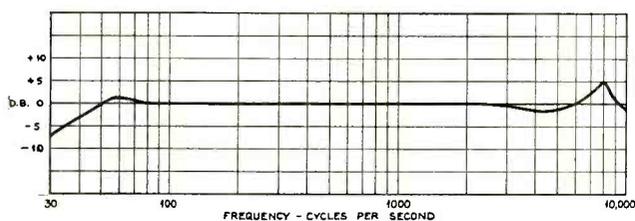


Fig. 2. Overall amplifier response.

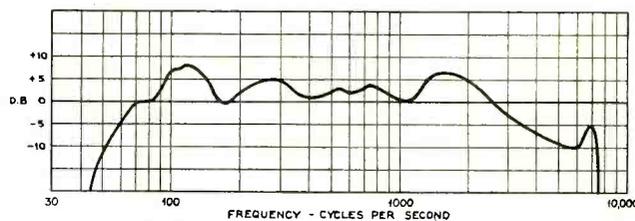


Fig. 3. Overall phonograph response.

of parts on the base, the use of many shielded leads and shielded capacitors have all contributed to an amplifier with a low hum level for the amount of amplification present.

COMPENSATION NETWORK SHIELDED

The input system employed is quite conventional. Transformer T2 is a 40:1 step-up ratio transformer in its own shielding can. The compensation network is also completely shielded in a special steel container to prevent hum pickup from stray fields generated by the power transformer and motor. The fixed compensation circuit, composed of R1, C2 and L2, takes care of the attenuation of low frequencies on the record during recording. Circuits composed of R2, C3, L3 and R3, C4 and L4 are the aural compensation circuits used in connection with the control R4.

The loudspeaker employed has an aluminum voice coil. Its response at the low-frequency end is good down to about 45 cycles. In respects other than the use of an aluminum voice coil, the loudspeaker is of conventional design.

AUDIO-FREQUENCY DISCRIMINATOR USED


In order that the best overall tonal balance could be obtained, at a commercial scratch level, use was made of a device called the audio-frequency discriminator. This device has a control system which permits quick alteration of its frequency characteristic through a division of the audio range (20-10,000 cycles) into eleven bands, each essentially one octave in width. The gain in each of the bands is individually controllable. In addition to this, it is possible to switch the discriminator in and out to obtain a direct comparison between the original and altered fidelities. All the variable controls are suitably calibrated to assist in making preliminary adjustments. An input gain control is provided as a means of adjusting the overall gain through the discriminator for comparison with another system as desired. Output from the pick-up and input system was fed to the discriminator and its output in turn fed to the R99 amplifier and speaker system. The re-

sults indicated that the overall fidelity curve should be essentially flat from 50 to 1,000 cycles, with a gradual decrease in response to 4,000 cycles, at which point it should be down approximately 8 db and then again rise to within 2 db of the 1,000 cycle level at 7,000 cycles. In this way the fundamental frequencies of the various instruments were not suppressed, the depression at 4,000 cycles reduced the bulk of the needle scratch and the rise above that frequency provided reproduction of the higher frequencies recorded on the record without appreciable increase in scratch level. A further reduction in surface noise was obtained, amounting to 6 db, by decreasing the pickup pressure on the record to 2 ounces instead of 4½ ounces as previously used. This reduction in pressure placed a further limitation on the stiffness of the pickup armature suspension system since faulty tracking would occur unless this flexibility were obtained. A spring balance device is employed in the tone arm to overcome the undesirable effect of a large counterweight.

Fig. 2 shows the overall curve of the amplifier alone and Fig. 3 shows the overall sound pressure curves of the instrument. It will be noted that the sound curve is quite flat for an instrument of this type employing a single speaker for covering the frequency range required in this instrument.

The Campbell Hum Balance

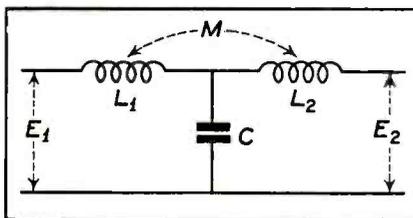The Campbell balance circuit, shown in the accompanying illustration, has been long known. The circuit has found application in comparatively recent times in power supply circuits, measuring equipment, etc.



The Campbell hum balance circuit.

It can be shown by rather simple mathematics that by proper choice of the condenser C and adjustment of the mutual conductance of the coils L₁ and L₂, the ripple voltage (E₂) can be reduced to zero. Mathematically:

$$\text{If } 2\pi fMC = 1 \text{ then } E_2 = 0$$

Thus the hum (ripple voltage) in a power supply may be greatly reduced by a rather simple circuit while d-c can flow readily.

IMPROVING OLD POWER SUPPLIES

(Continued from page 547)

The effect of variation in the capacity of C₂ is the same as that of C₁ and the two results multiply. For instance, suppose C₂ was 8 mfd and C₁ was 8 mfd. If both condensers were replaced by larger ones of 32 mfd, the hum would be cut down to one-sixteenth of its original value with the smaller condensers. Or, multiplying the capacity of C₂ by four and the capacity of C₁ by four, results in a reduction of hum of four times four or sixteen times.


It should not be assumed that 32 mfd is an unreasonably large capacity. The trend of designers is towards very much larger condensers and sizes up to 70 and 80 mfd are being employed.

SUMMARY

Increasing the input condensers to a power-pack filter will result in increased voltage as well as reduction in hum. The effects follow the law of diminishing returns; after one exceeds a certain value, further increase of capacity results in less and less improvement.

Increasing the second and third condenser reduces the residual hum in inverse proportion to the increase in capacity. Multiplying the capacity by any factor will divide the residual hum voltage by the same factor. This law holds, no matter how large the capacity becomes.

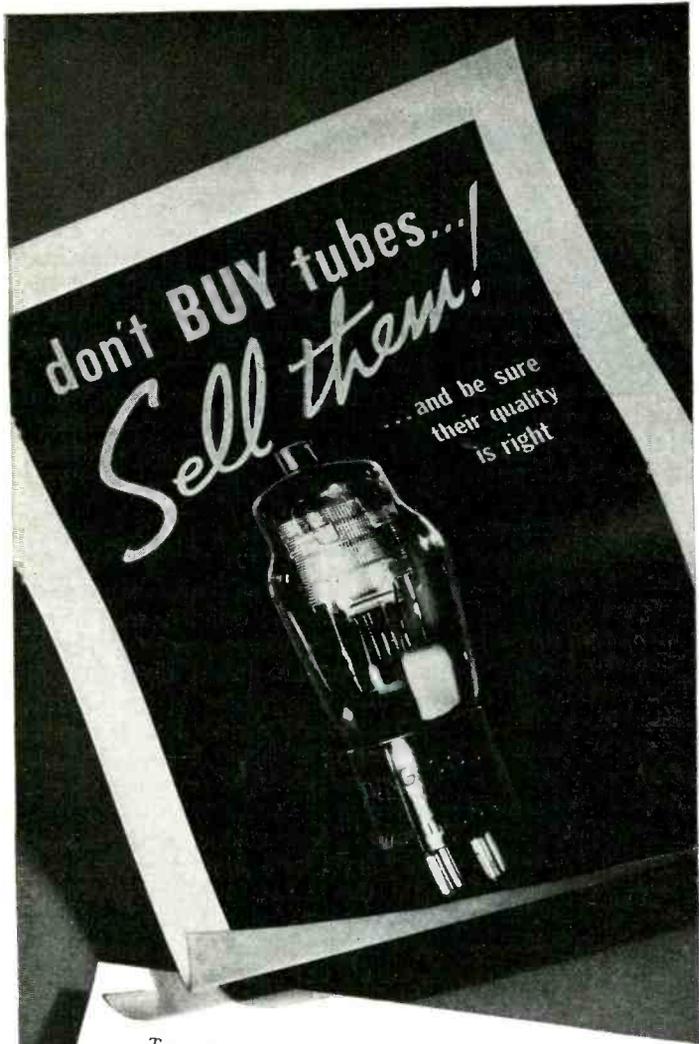When more than one condenser is replaced, the total reduction in hum is equal to the product of the individual reductions.



Tung-Sol radio tubes are the only high-quality tubes now being sold nationally under a consignment plan which permits you to carry an adequate stock *without tying up a cent of capital.*

There are still desirable locations where independent service organizations who can meet requirements may be appointed as Tung-Sol agents. Ask for the name of your nearest Tung-Sol tube wholesaler.

TUNG-SOL
Tone-flow radio Tubes

TUNG-SOL LAMP WORKS, INC.
Radio Tube Division

SALES OFFICES Atlanta, Boston, Charlotte, Chicago, Dallas, Detroit, Kansas City, Los Angeles, New York.
General Offices Newark, N. J.



The RIGHT COMBINATION at your fingertips



New CENTRALAB Selector Switches for

- Analyzers
- Output Meters
- R F Oscillators
- A F Oscillators
- Tube Checkers
- Decade Boxes
- Capacitance
- Resistance
- Ham Equipment
- P A Work
- Volt-Ohm-Am Meter
- Radio Receiver Replacements

Here's some light on that SELECTOR SWITCH PROBLEM, you Knight of the soldering iron.

If the circuit calls for more lugs than a centipede has feet, scam over to your jobber and make up your own SELECTOR SWITCH ... thousands of different combinations possible with a CENTRALAB Kit at his place.

Centralab

Division of Globe-Union Mfg. Co.
Milwaukee, Wisc.

British Centralab, Ltd.

Canterbury Rd., Kilburn, London, N. W. 6, England

French Centralab Co., 118 Ave. Ledru-Rollin
Paris XI, France

VOLUME CONTROLS

FIXED RESISTORS

WAVE CHANGE SWITCHES

ON THE JOB . . .

Keeping Lapel Microphone in Place

A five-inch square of stiff cardboard or some similar material (through which the microphone cable is threaded) placed in the side pocket of the speaker's jacket will prevent tangling of the lapel



microphone cable and also reduce the pull on the cable.

This device not only divides the pull between the lapel and the pocket, but, since the angle is changed to one more nearly along the direction of the pull, the actual amount of this pull is reduced. This allows the speaker a greater freedom of movement.

Color-Coded Resistors and Condensers

Some molded resistors look like small, narrow, mica condensers. These are ordinarily black and are marked with three colored dots. The dot colors are read in proper order the same as the body, end and dot colors on the regular carbon resistors.

Flexible fabric-covered wire-wound resistors are coded the same as carbon resistors. Some have the colors woven into the fabric. The smallest thread color is read as the dot; the larger thread grouping as the end, and the body color as usual.

Molded mica condenser values are expressed in micro-microfarads and also are color coded. A micro-microfarad (mmfd) is one millionth (0.000001) of a microfarad (mfd). To convert mfd to mmfd, move the decimal point six places to the right. To convert mmfd to mfd, move the decimal point six places to the left. For example: 0.00025 mfd is 250 mmfd, or conversely 250 mmfd is 0.00025 mfd. Similarly 0.000051 mfd is 51 mmfd or 51 mmfd is 0.000051 mfd.

On coded mica condensers the capacity in mmfd is marked on the case by three colored dots. The first color indicates the first figure, the second color indicates the second figure and the third color indicates the number of zeros. In order to distinguish the sequence of reading the colors some dots are pointed in the direction to be read, others have an adjacent arrow while some have no clue to the direction but the printing on the case.

Let us consider, by way of example, a condenser having a green, brown and black dot in that order. The green indicates that the first figure is a 5; the brown dot indicates the second figure is 1 and the black dot shows that no zeros should be added. The capacity of the condenser is therefore 51 mmfd or 0.000051 mfd. Similarly a condenser having yellow (first figure 4); red (second figure 2) and brown (1 zero) dots would be 420 mmfd or 0.00042 mfd.

Some condensers have a fourth dot or stripe, as, for example: orange, below the regular three dots. This indicates capacity tolerance—as in this case 3 percent.

All resistors and condensers necessarily are apt to vary somewhat from rated values. Parts are nominally held to plus or minus 10 percent. Some uses permit a wider tolerance of 20 percent. It is for this reason that a resistor or condenser may not measure exactly as it is coded.

Inasmuch as the color coding is universally adopted to cover all resistors and has been extended greatly to cover molded condensers at the risk of repeating, the code is printed below. Every Service Man should memorize the coding so that he can identify the values of the parts marked in code practically at a glance.

The color black represents the figure 0; brown, 1; red, 2; orange, 3; yellow, 4; green, 5; blue, 6; violet, 7; gray, 8, and white, 9.

J. N. Golten, Stewart Warner Corp.

Radio Rotors

All installations of custom-built Chrysler, DeSoto, Dodge, Plymouth and Packard radios are supposed to be completed without the use of spark-plug suppressors. After following the regular procedure a high noise level may still exist. The final trick in clearing up the noise lies in the building up or lengthening of the rotor in the car's dis-


tributor. It is possible to purchase rotors, for these cars, which are already lengthened for this purpose. This eliminates the time and patience needed for a homemade job. These rotors can be obtained at practically any auto-supply dealer with the same serial number as the original shorter ones, but with the addition of an "A" after the number.

Eugene Triman

Using 226 Power Transformers

The older type power transformers designed for use with 226 and 71A type tubes usually hang around the shop their only purpose to collect dust. A profitable use is suggested in the following schematic. All the windings are used to advantage to supply filament and plate power for a four-tube amplifier or radio receiver.

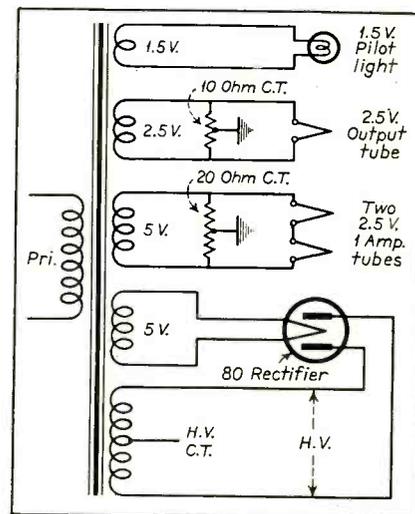The 1.5-volt winding is used to supply the voltage for a pilot light. Pilot lights with this rating are available at the same cost as the regular bulbs. The 2.5-volt winding on these transformers is usually designed for 1.75 amp for use with a 27 type tube. The more modern type output tubes such as the 2A5 draw only the 1.75 amp. Two 1-ampere 2.5-volt tubes, wired in series across the



5-volt winding originally designed for the 71A's, will not overload that winding. If this 5-volt winding is center-tapped, one tube can be connected across each half of the winding. The other 5-volt winding together with the high-voltage winding is used to operate a type 80 tube to supply plate power for the amplifier.

GET YOUR COPY



Act Now!

- 16 Page Sound Manual covering such topics in Public Address as: How to estimate installations... How to install... Hints on obtaining better performance... Points on Selling... Etc... Nothing else like it available... Be Sure to Get Your Copy... Published by

WEBSTER-CHICAGO

One of the oldest manufacturers of sound equipment in the field. Licensed under all important patents.

Products manufactured include:

- Portable Sound Systems, 8 to 20 Watts.
- Fixed Sound Systems, 8 to 120 Watts.
- Electric Phonograph Motors for all Cycles and Voltages.
- High Fidelity Pickups.
- Microphones: Carbon, Crystal or Ribbon.
- Speakers: Electro Dynamic or Permanent Magnet.
- Baffles and Trumpets.
- Sectionalized Sound Systems for Schools, Hotels, Department Stores, Hospitals and other institutions.
- Factory Call Systems.
- Two-Way Communication Systems.
- Custom Built Equipment of All Kinds.

NOTICE TO DEALERS

FREE COPY Every dealer or active radio serviceman can obtain a copy of this Sound Engineering Manual free by signing name and address below and giving this coupon to one of our jobbers.

Name

Address

City..... State.....

Jobber..... O.K. and Send to Webster-Chicago, 3825 W. Lake St., Chicago, Ill., Section N-5.



Radio set and motor car electrical troubleshooting is enormously simplified and speeded by this Bendix-DayRad Series "200" Tester. It swiftly checks any radio or automotive circuit—spots bad tubes, connections, resistance and capacity units, switches



—any portion of the electrical continuity which may be at fault. It has an exclusive Safety Tube-Index Dial which eliminates the danger of blowing out tubes.

What's it worth? It's worth everything to the radio service man! Yet its price is extremely moderate, and Bendix sells it to responsible Radio Service Shops on very easy terms. Send the coupon for details.

EXCLUSIVE SAFETY TUBE-INDEX DIAL

Eliminates Blown-out Tubes! Simply turn dial to the tube you're testing, set the test circuits to proper current-potential readings, and don't worry! Spaces have been provided for entering new tube-values as they come on the market.

* A turn of the switch transforms the "200" into a sensitive volt-ohmmeter.
 Reads AC voltages from 0 to 1250
 Reads DC voltages from 0 to 1250
 Reads Milliampères from 0 to 1250
 Reads Ohms from 0 to 30,000
 Reads Ohms from 0 to 300,000
 Reads Ohms from 0 to 3,000,000
 Reads Amperes from 0 to 25
 (All ranges to an accuracy of 2% plus or minus)

BENDIX DAYRAD

COMBINATION TESTING UNIT

BENDIX PRODUCTS CORPORATION

401 Bendix Drive, Dept. 32, South Bend, Ind.

Send me your new catalog of Bendix DayRad Radio Service Instruments.

Name

Street

City

State

My Jobber's Name

TEST EQUIPMENT...

Triplet 1240 Condenser Checker

A condenser tester must do more than check capacity. In fact measuring capacity in service work is relatively unimportant since the capacity is generally marked on the condenser covering and very seldom changes. Also a shorted or open condenser will throw the circuit out of order making the trouble easy to find with even the simplest test equipment. By far the greatest amount of troubles which occur in condensers are not simple and require specially designed equipment to locate their defects. Intermittent shorts and opens are troubles that are only to familiar; however, a brief review will not be amiss.

SHORTS

An intermittent short causes erratic operation, motor-boating, parasitic oscillation, fading and other troubles—the bane of the Service Man's job. An oft used method to remedy this type of trouble has been the cut-and-try substitution of each condenser found in the ailing receiver. Not only is this method tedious but the trouble is never positively cured—it may lie dormant to recur at some future date. To test a condenser for intermittent shorts the checker must have sufficient voltage available to present at least working conditions for the unit under test. For some condensers this will call for 1,000 volts. At these high voltages the condenser may be tested for both breakdown and leakage. Any intermittent short will burn through and the unit will show up as bad.

The short and breakdown test is accomplished in the model 1240 by applying a voltage to the terminals of the condenser under test as shown in Fig. 1. With a leaky condenser across the binding posts the current flows from the selected voltage tap of the transformer through the selector switch to one binding post. From here it passes through the condenser to the rectifier. The current is rectified and passed to the positive meter terminal, through the meter and shunt to the 1,000-ohm resistor,

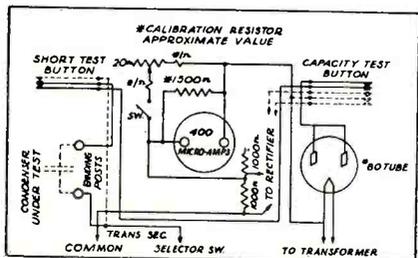


Fig. 1. Breakdown test circuit.

through this resistor and back to the common terminal of the transformer. Thus if the condenser is leaky the current flowing through it will register on the meter. The short-test button is used to complete this circuit and to discharge the condenser when the button is released. With the capacity-test button in the normal position the type 80 tube is placed in the circuit. Pressing this button connects the a-c circuit for the other tests.

OPENS

Intermittently open condensers will also cause erratic operation, motor-boating, parasitic oscillation, fading, etc., and in addition will cause blocking. A test for breakdown followed by a test for an open, using a-c, usually brings

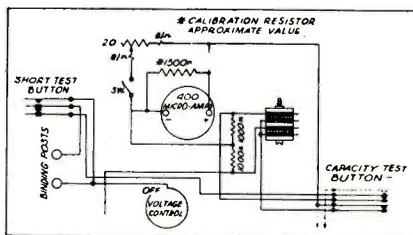


Fig. 2. Capacity test circuit.

this condition to light. Always test paper condensers for shorts or opens with voltages as high or slightly higher than the rated voltage of the condenser. Due to the leakage factor of the electrolytic condenser and the resistance used to protect the meter the voltage never exceeds the safe value of the electrolytic condenser no matter what voltage is applied within the range of the instrument. The circuit used for this test is the same as that used for capacity measurement. To make certain that the voltage and current conditions used during the testing of a unit for opens have not healed the unit temporarily the condenser leads should alternately be subjected to a slight pull and then slight pressure or even a twisting motion. During this procedure the indicating meter should be watched continuously.

LEAKAGES

Condensers with a resistance of about 10 megohms used in critical circuits of the receiver often cause intermittent oscillation rather difficult to locate. The tests described above will locate such defects.

The condenser used in blocking circuits which shows a resistance of less than 100 megohms will cause the grid of the amplifier tube to be several volts more positive than that for which the receiver or amplifier was designed. This

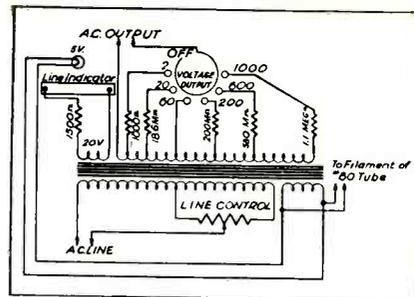


Fig. 3. Transformer circuit Triplet 1240.

naturally upsets the circuit. In high-gain amplifiers these condensers are even more critical. The same is true with a-c circuits. The condensers in this type of circuit must have extremely low leakage (high resistance) since the small currents and voltages available in the d-c circuit are very easily upset by the bucking voltage which would be introduced by a leaking condenser.

The d-c leakage of a condenser causes a lower or higher voltage at the tube element and upsets the circuit. It is not possible, however, to set up a fixed resistance for the various functions of the condenser, but the Service Man's knowledge of radio and circuit constants must tell him when to discard. Due to the low resistance and high voltages involved in some by-pass circuits the leakage factor of such condensers can go as low as one megohm without seriously upsetting the circuit.

CAPACITY

After the above tests have been made on the condenser it may be tested for capacity on the model 1240. The circuit involved is illustrated in Fig. 2. For these tests a-c is applied to the condenser from the transformer. The type 80 rectifier tube is disconnected from the circuit by pressing the capacity-test button. This same button connects a copper-oxide rectifier to the meter for measuring the a-c drop.

Since all the current passes through the meter and the voltage is carefully calibrated it is possible to calibrate the meter directly in microfarads. The introduction of the condenser capacity into the circuit will change the total impedance and hence the current flow. Since the meter is used as a milliammeter it can readily be calibrated directly in capacity by dividing the voltage applied by the impedance of the circuit.

ELECTROLYTIC CONDENSERS

It has been shown elsewhere in this issue that the filtering efficiency of a filter condenser depends upon the power factor or phase angle. As the Service Man is primarily interested in the filtering efficiency when testing electrolytics it is necessary that some means be provided to determine the filtering work these units will accomplish.

This is obtained in the model 1240 by

FLASH! EXTRA!
TIME PAYMENTS
ON DEPOSITS!!

Service experts! Get many latest type service instruments for only a few dollars down and time payments on the initial low N. U. deposit. Remember—deposits are refunded when tube purchases are completed! Get the equipment you need, get it now, the sensational new N. U. way. See your jobber for details.

Free!
**CLOUGH-
 BRENGLE**

INSTRUMENTS

New 1937 MODELS with

NATIONAL UNION TUBES



MODEL OMA
14¢ PER DAY
\$11.40 DOWN
 Deposit Refunded

MODEL OC-A
7¢ PER DAY
\$5.40 DOWN
 Deposit Refunded



1937 Clough-Brengle Signal Generators. Model OMA operates from 110 volts, 50-60 cycle, continuously variable 100 K.C. to 30 M.C. Single and double trace selectivity. Curves for use with output meter or oscillograph; Complete with tubes and accessories. Model OC-A, 100 K.C. to 30 M.C., operates from 110 volts, 50-60 cycles. Complete with tubes and hand drawn calibration curves. Available on N. U. tube deals with time payment plan covering deposit. Investigate.

YES—FREE—THE N. U. WAY

The National Union Way makes the purchase of National Union radio tubes doubly profitable. Besides full protection on the highest quality radio tubes, each National Union tube purchased helps to earn free equipment. But, possession of the equipment is obtained at once with just a nominal cash deposit. (Deposit is rebated when required number of tubes have been purchased.) Over 50,000 completed deals with progressive radio dealers. Don't be misled. See your National Union jobber and get all the facts.

OTHER NATIONAL UNION OFFERS

In **SOUND EQUIPMENT** items available include 17-watt portable system, 10-watt portable system, 6-watt portable system, phonograph pickup and turntable, etc., all manufactured by Webster-Chicago.
 In **SHOP EQUIPMENT** items available include stock cabinets, coats, display signs, etc. All items absolutely free the National Union Way. Get full details.
 In **SERVICE EQUIPMENT** items available include tube testers, analyzers, oscillographs, signal generators, modulators, meters, etc., products of such manufacturers as Supreme, Clough-Brengle, Hickok, Triplett, Readrite, Precision, Radio City, Dumont, J.F.D. and others.

ABOUT NATIONAL UNION RADIO TUBES

National Union manufactures a complete line of radio tubes in glass, metal and G-type. National Union's high quality has made them the outstanding favorite in the radio service profession. All sales policies have been formulated with the idea of making National Union radio tubes the ideal replacement tube for the radio dealer. This has been backed up with a selling program that means real support and help to the wide-awake dealer. Dealers and jobbers handling National Union radio tubes are the leaders in repair parts and service.

**LET NATIONAL UNION HELP YOU
 WRITE FOR INFORMATION**

NATIONAL UNION RADIO CORPORATION
 570 Lexington Ave., New York City

S-11-36

Without obligation please send me more information on


Free offer on Clough-Brengle Model OMA.....; Model OC-A.....
 Free offer on

Dealer's Name

Address

City..... State.....

AS COOL

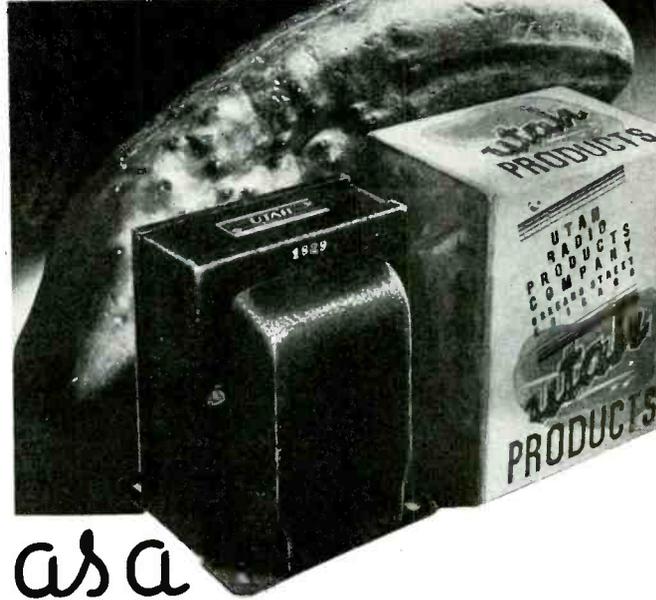

as a
CUCUMBER

Utah **TRANSFORMERS**

DO NOT OVERHEAT

There's real design in Utah Transformers, the result of fifteen years of experience in the design of radio parts.

They are built with thin laminations to provide lower eddy current loss and less consequent heating. Transformer Cores, of Highest Grade Electrical Sheet Steel, are properly sized and shaped to provide the most efficient magnetic field. All Utah Transformers are completely impregnated against moisture and atmospheric conditions. Utah Transformers, like all other Utah parts, are built to the highest standards of quality—the reason for their selection for over 3,000,000 Radio Receivers.

SPECIFY *Utah* PARTS

- Vibrators
- Transformers
- Chokes
- Volume Controls
- Tone Controls
- Speakers
- Resistors
- Plugs
- Jacks
- Jack Switches
- Push Button Switches

UTAH RADIO PRODUCTS CO.

Orleans Street - - - Chicago, U. S. A.

Toronto, Ontario, Canada

Buenos Aires, Argentina, South America—UCOA Radio Products Co.

15 YEARS OF LEADERSHIP

A NEW POLICY *Factory Prices*

30 FEATURE A. C. SIGNAL GENERATOR

- Hairline Accuracy with Spotted Test Frequencies.
- Individually Calibrated—Direct Reading 100 K. C. to 75 M. C.
- Micro-Vernier zero to maximum attenuator.
- 30% 400 Cycle Sine Wave Modulation.
- Selective Modulation Internal or External.
- Look at the price, compare the value. send at once for further details.
- F. O. B. factory.

Model 120 Signal Generator . . . **\$23.95**



A Pocket Volt-Ohmmeter

- Weighs only 20 ozs.
- High sensitivity.
- Selective Range Switch.
- Measures D. C. Volts.
- Ohms to 500,000.
- Meter at easy reading angle.

Your service kit isn't complete without this new marvel of modern test equipment.

Model 310
Volt-Ohmmeter
\$7.85

F. O. B. factory.

Direct from factory saves you up to 35%.

Avoid big Interest Rates.

Eliminate Obsolete Tube Stock.

Complete Dealer Cooperation.

Money Back Guarantee

We stand back of every piece of testing equipment we sell direct. Your money cheerfully refunded on merchandise returned within 10 days in original condition.

TRIUMPH MANUFACTURING CO.

4017 W. Lake St.

Chicago, Ill.

Triumph Manufacturing Company
Dept. S 611, 4017 Lake St., Chicago, Ill.
Check coupon and mail today
Dear Sirs: At no obligation to me please send FREE brochure on the Triumph line of testing equipment.
Dear Sirs: On the basis of your money-back guarantee please find enclosed 25% deposit (\$.....)
Balance to be C.O.D. for model.....
Name.....
Street.....
City..... State.....

FREE!
TRANSFORMER
REPLACEMENT
GUIDE

IT'S GOOD BUSINESS
TO USE

STANCOR TRANSFORMERS

STANCOR

REPLACEMENT TRANSFORMERS
GUIDE AND
CATALOGUE

*Your Jobber
Recommends*

**STANCOR
TRANSFORMERS**

Don't hunt through page after page of catalogs for the right transformer for that replacement job—all the information is here, in the STANCOR complete, exact duplicate replacement guide—listing the right transformer for any receiver. It's FREE. As many copies as you need are available on request. Just pin this ad to your letterhead and the number of copies you request will be mailed to you at once.

If we could take you through the STANCOR Factory, the most modern and scientifically equipped transformer plant in the radio industry—if you could see with what painstaking care every operation is carried out—you would readily be convinced that the STANCOR claim for superiority is more than an idle boast.

The performance of Stancor Transformers and the customer satisfaction they build, is causing more and more service men and dealers to use Stancor products exclusively. Your jobber carries them in stock.

STANDARD TRANSFORMER CORP.
858 BLACKHAWK STREET, CHICAGO, ILL.

RECEIVER CASE HISTORIES

Atwater Kent 275 A-C D-C

Inoperative: Check the triple electrolytic condenser (C-14) for open sections if the voltages are low or missing. Often all the sections have been found normal upon test, but the negative connections (which are brought out separately) sometimes short internally causing the speaker field to be shorted.

Howard J. Surbey

Detrola Warwick Model

Low volume: The 50,000-ohm resistor connecting the plate return of the 58 tube to the screen grids of the 58 and 57 tubes often increases in value, reducing the voltage available for screen supply. A 2-watt resistor of good quality will prevent a recurrence of this increase.

Howard J. Surbey

General Electric Focused Tone Models

To Mount Escutcheon: Care should be taken to use a well-ground screwdriver of proper size for fastening the screws used to hold the escutcheon plate. Holes have been jigged in the panel to insure proper location of the escutcheon plate with respect to the scale housing.

To Replace Drive Cable: Remove the drive cable to be replaced. Referring to Fig. 1, rotate drive wheel (14) counter-clockwise until condenser plates are open. Place the end of the cable having an eyelet in slot (A). Thread cable as shown, making sure cable passes over pin (B), and runs along the correct grooves, the looped end hooking over spring (16). Check the position of the drive wheel on the condenser shaft, making sure that the cable coming off the right-hand idler pulley lines up with the grooves in the drive pulley. Also, as

the condenser plates become fully closed, the drive wheel (14) should just touch the bushing (D) of the tuning shaft (39). With the drive wheel in this position place the pointer on rail (E) and, with the tip of the pointer on the extreme left-hand scale division, crimp pointer tab on to the drive cable.

To Adjust Pointer for Scale Calibration: Three positions of the dial pointer cable are provided to adjust the pointer up or down scale. The position shown on Fig. 1, with the cable over pin (B), is the medium position. By changing the cable to the position between pins (B) and (C) the pointer may be moved down scale. The cable position below pin (C) moves the pointer up scale from the medium position.

To Replace Dial Scale: Remove the band change cable (12). Then remove the end support (8) held by a single self-tapping screw and withdraw the scale assembly from the housing. Replace the end caps on the new scale and re-assemble. Before attaching band change cable (12) to the gear (41), the spring (7) should be given two full turns to give the proper tension to the cable.

To Adjust Rotation of Scale: Bend tab (F) up or down to give the correct position of the scale divisions with respect to the pointer tip. The pointer should slightly overlap the divisions.

To Change Pilot Lamps: Be sure the shipping screw (G) is removed. Lift up the lamp bracket from the tabs under which it is clipped. Care should be taken that the lamp socket leads do not put an undue strain on the drive cable. With the lamp bracket laid back horizontally, the lamps may be replaced. The lamps used in this receiver are the Mazda No.

46. When the lamp bracket is re-inserted, care should be taken to avoid the lamp bracket leads fouling the gang-drive mechanism.

Philco 20

Inoperative: No voltage on the plate of the 24 detector tube or on the plate of the 27 tube caused by an open speaker field coil. The coil may often be repaired by resoldering the lead at the point where it attaches to the fine wire of the coil.

Howard J. Surbey

Stewart Warner 1495

Insufficient deflection of the tuning eye: Since the narrowing of the shadow in a tuning eye depends on the strength of the receiving signal, it will narrow the most for powerful nearby stations, while on distant stations it will close much less. If a set is used with no aerial or too short an aerial the eye will not close the normal amount.

In all models, if the tuning eye does not close enough and if this is not caused by the above reasons, be sure to check the tubes and the alignment.

In the later production of the model 1495 the circuit was changed slightly to give more deflection of the eye on weaker signals. You can determine whether this change has been made without removing the chassis from the cabinet.

Tune in a local station and then remove the 6H6 tube located next to the 6C5 tube. If the proper tube is removed, the radio signal will get louder or distort. In the latest production sets removing this tube should cause the tuning eye shadow to narrow or disappear. If removing the above 6H6 tube causes the shadow to widen to its full width then the eye is not connected properly.

To correct the wiring remove the chassis from the cabinet and trace the wiring of the tuning eye grid wire. This is the green and white wire in the tuning eye cable and will be found connected to the blank pin terminal on the 6H6 socket located adjacent to the 6C5 tube. Disconnect the green and white tuning eye lead from this terminal. This lead should then be connected to the blank pin terminal on the 6H6 tube located nearest to the 6J7 avc-amplifier tube.

The avc, i-f and broadcast trimmers should be realigned after these changes have been completed.

J. N. Goltzen, Stewart Warner Corp.

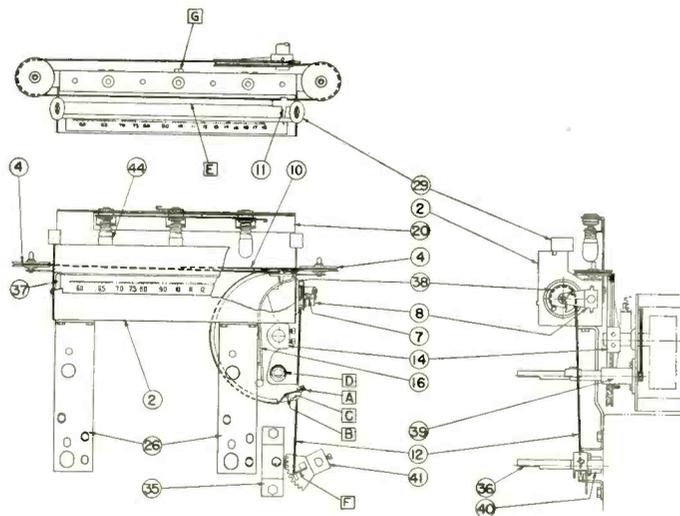


Fig. 1. General Electric focused tone dial.


Big Values in New SERVICE EQUIPMENT IN YOUR ALLIED CATALOG

Newest AND MOST COMPLETE LINES

"What's new in Service Equipment?" You'll find the answer in your new 1937 ALLIED Radio Catalog. This great 152-page book includes a complete section packed with a tremendous assortment of the newest in oscillographs, tube checkers, set-testers, meters—the choicest products of Supreme, Triplet, Readrite, RCA, Jackson, Weston, Clough-Henkle and other leading manufacturers. No matter what type of service instrument you need, you'll find it shown in your new ALLIED Catalog—at the lowest prices.


EARN AS YOU PAY!

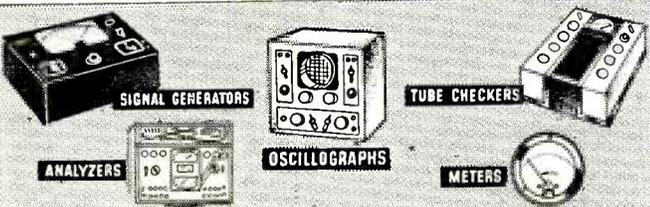ALLIED offers you a new Time-Payment plan on all Supreme service equipment. For a small down payment you get the instrument you want—use your increased profits to pay the monthly installments! Send coupon for details.



10,000 DUPLICATE AND REPLACEMENT PARTS AT LOWEST PRICES...

Your new ALLIED Catalog is crammed with more than 10,000 exact duplicate and replacement parts—any part, any brand you want—when you want it—at radio's lowest prices. Our complete stocks are located under one great roof—our central location means faster service for you—our expert staff of skilled engineers is ready to help you select the equipment you need—conveniently and economically. Thousands of servicemen order exclusively from the ALLIED Catalog—and save time, trouble and money. Send for your Free copy today!

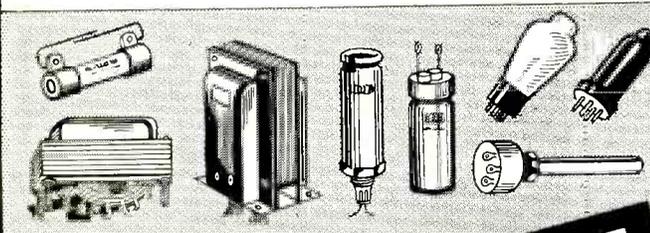

EVERYTHING IN RADIO AT LOWEST PRICES

Besides complete lines of parts and service equipment, the 152-page ALLIED Catalog shows 38 new Knight radios—5 to 19 tubes; latest Amateur transmitting and receiving gear; newest Public Address Equipment, dozens of new set-builders' kits; Ruripower units and Windchargers; books; tools, etc. Whether you are a Serviceman, Amateur, Radio Builder or Sound Man you need this great book. Write for it today!

FREE 1937 CATALOG



ALLIED RADIO CORPORATION
833 W. JACKSON BLVD.
CHICAGO, ILL.

ALLIED RADIO CORP., Dept. 19-L
833 W. Jackson Blvd., Chicago, Ill.

Rush me a Free Copy of your 152-page 1937 Catalog.


Send me details on Supreme Time-Payment Plan.

Name

Address

City State

You Need it... And it's FREE!

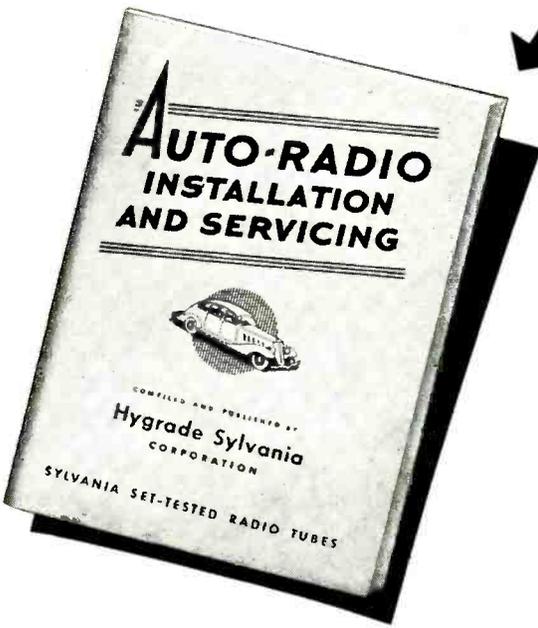

The New 1936-37 Edition of Auto-Radio Installation and Servicing

One of the most expert radio engineering staffs in the world has written this book for you. And you're going to have plenty of opportunity to use it this winter.

Here are just a few of the important subjects covered in this valuable book: Elimination of motor interference for every make of 1936 car. . . . Tube compliment chart for practically all models of automobile radio sets, with I.F. peak frequencies. . . . Set and antenna installation hints, etc. These and hundreds of other problems you will meet in auto-radio installation and servicing are covered in this amazing book.

If this book were for sale you'd be willing to pay out a lot of money for it. But it isn't for sale! *It's absolutely free!* Just fill out the coupon below and send it to us.

Hygrade Sylvania Corporation, makers of Sylvania Radio Tubes and Hygrade Lamps. Factories at Emporium, Pa., Salem, Mass., and St. Mary's, Pa.

SYLVANIA THE SET-TESTED RADIO TUBE

HYGRADE SYLVANIA CORPORATION S-116
Emporium, Pa.

Please send without obligation your new service book, "Auto-Radio Installation and Servicing."

Experimenter Amateur Call.....
Serviceman Employed by dealer Independent

Member Service Organization.....

Name

Address

City..... State.....

Name of Jobber.....

Address

RECEIVER CASE HISTORIES—continued

Stromberg Carlson Models 126, 127, 130 and 140

Replacing dial glass: Dial glasses in early production had cardboard rings cemented to glass for cushioning against the dial pan. Later production used metal shims on bed-plates for point support under clamps. Shims are provided with replacement dial glasses and should be used as instructed.

Remove chassis from cabinet and place on back, with dial up. Loosen four screws allowing clamps to fall away from glass. (Model 140, only) Remove two screws holding center bar. Replace with new glass and center.

Centering dial glass: In some cases, dial glass may slip in transit, throwing receiver off calibration. If calibration is inaccurate at one end, only, of broadcast scale, check for electrical alignment of oscillator rather than dial-glass slippage.

High-frequency discrepancy is caused by shift of oscillator padding condenser and low-frequency discrepancy is caused by shift of oscillator series condenser. If the entire dial scale is off calibration, loosen clamps (and center bar, model 140). Then line up vertical and horizontal centers of glass scale with center marks on the metal dial pan. Dial scale is marked at edge of the glass, but a better alignment can be had by placing a straight-edge along the vertical scale, lining up the arrows on this scale with the center marks on the dial pan.

Replace all clamps (and center bar). Tighten all screws. Check calibration by tuning in several stations at different parts of the dial.

Dial drive (tuning knob) slips: Where a tuning knob rotates without positive drive to the dial check gang condenser against obstructions hindering movement or loosen drive assembly screws and shift drive assembly toward dial discs as far as screw holes will permit. Check dial discs for rubbing or binding against dial pan or replace dial drive if none of above are effective.

Improvements have been made in dial drive assemblies to increase their grip on the dial.

Vernier tuning knob binds or sticks: This usually indicates that vernier knob has been pushed too far on to shaft or that large tuning knob is not far enough on shaft, causing knobs to rub together. **Vernier tuning shaft ineffective or missing:** This indicates breakage at welded joint where ball-bearing is welded to end of shaft. New highly tempered ball bearings have permitted stronger weld in recent drive assemblies.

When unpacking receivers shipped in cartons, be sure to lay the radio on its back when drawing it out of the carton, so that all control shafts will clear the packing material.

Tri-focal eye closes or overlaps: Almost without exception, this is due to variations in characteristics of the 6E5 tube, and is corrected by selection of a suitable tube.

First make sure that the 6E5 tube is not "soft" or "gassy," causing a blue glow in the lens of the tube, which can be seen by looking across the tube in a dim light.

Some "hard" tubes are also unsuitable. Any tube drawing in excess of 5-ma plate current in the receiver circuit (as measured by a set analyzer, not a tube analyzer) should not be used. The percentage of such tubes is rapidly being reduced by the tube manufacturers.

Occasionally the 6E5 tube may be suitable and the difficulty caused by excessive plate current in the 6K7 tube used in the i-f stage.

Tri-focal eye does not close enough: If the shadow on the target of the 6E5 tube does not reduce on nearby signals, check the aerial and ground connections for open lead-in, insufficient pickup, high-resistance joints, etc.

Check sensitivity control knob on rear of chassis (models 130 and 140). Clockwise rotation increases sensitivity. Check for a faulty tube in the r-f system, causing low avc voltage.

Check for a grounded cathode bias resistor at 6K7 r-f or 6K7 i-f socket.

Stromberg Carlson Labyrinth Models

Loudspeaker rattles: Distortion and rattles in these receivers may be traced to the usual sources, such as foreign particles in speaker; damaged or defective speaker cone; loose voice coil; coil off-center; loose grille cloth.

In addition, check the following: Foreign particles on top of labyrinth, or between labyrinth and cabinet; loose screen over labyrinth exhaust in bottom of cabinet; warped sound-spreading vanes striking against cone or leather.

Speaker rattles may not be the fault of the loudspeaker.

If the screen is loose in the bottom of the cabinet, tack it down so it won't rattle. Its purpose is to keep mice, etc., from nesting in the radio cabinet.

Stromberg Carlson 140-P

Lack of undistorted phonograph output or acoustic coupling: If distortion, coupling or hum is complained of, or



phonograph music distorts at low volume, make certain that the phonograph motor-board floats entirely clear of the cabinet.

Be sure all four mounting screws are loosened and, in excessive cases, remove the motor-board and cushion on live rubber (sponge rubber is best) at center of all four sides. This further damps the motor-board against vibration.

If distortion persists, check for dull or defective phonograph needle; old-style records, not electrical recordings; iron particles on pickup, near needle; damaged pickup head; proper mounting of counter-weight; tone control fully operated, limiting volume.

Stromberg Carlson 150 and 160

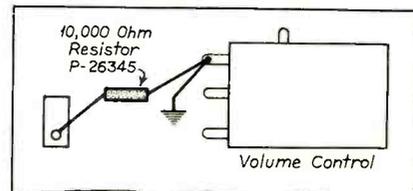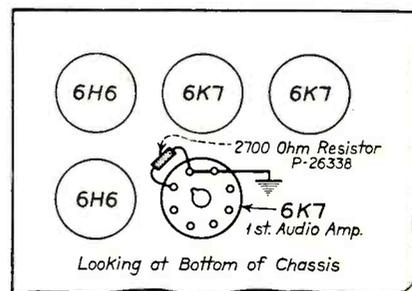Improvement in volume control circuit: Variations in characteristics of the 6K7 tube cause some tubes to draw excessive grid current, which may lead to noisy volume control action as the volume knob is rotated; low power output or



overloading, or excessive bass compensation at low volumes.

To prevent this, circuit changes are being incorporated in all of the more recent receivers and the same changes should be made in receivers in the field, where noisy volume control action is observed.

Two changes are made:

(a) Replace the 1,000-ohm bias resistor with one of 2,700 ohms for increased bias.

(b) Connect a 10,000-ohm resistor across the bass compensating capacitor for smoother bass at low volumes. This connection is made from the volume control to a terminal nearby.

These changes are shown in the accompanying diagrams. Stromberg Carlson Telephone Mfg. Co.



Most extensive listing of sets and their controls.



An exact duplicate for every standard set.



Wire-wound and composition types.



Any resistance, taper, taps and shaft.



External resistor for required bias.



Ad-A-Switch snaps on rear of case.



Smooth, noiseless, dependable, long-lived.

Exact-Duplicate VOLUME CONTROLS

For repairs that must be *right* mechanically, electrically, visually, use CLAROSTAT Exact-Duplicate Controls. They save time, trouble, money. And they build good will.

FREE MANUAL: Big 80-page Replacement Guide—most extensive listing available—is yours for the asking. Meanwhile, your leading jobber stocks CLAROSTAT replacements.


CLAROSTAT

MANUFACTURING CO.
Incorporated
285 North Sixth St.
Brooklyn, N. Y.

BUSINESS at your finger tips!



GLASS

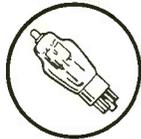

"G"



CORONET THE PERFECTED METAL TUBE



CORONET TO REPLACE OLD GLASS TUBES

if you sell the

ARCTURUS 4-WAY Line

Business is never turned away by the dealer who handles ARCTURUS. For here is the *one* line that enables you to meet the demands of *every* customer—the *only* line that gives you the 4 types of tubes set owners are asking for today!

ARCTURUS has pioneered 7 of the 8 fundamental developments in a.c. tubes. This company has won wide public recognition as a dominant factor in the quality field. And ARCTURUS alone provides a 4-way sales and profit set-up.

See your Arcturus Jobber or write today for full details.

ARCTURUS RADIO TUBE CO., NEWARK, N. J.

ARCTURUS

GLASS—"G"

CORONET—The Perfected Metal

RADIO TUBES



NEW

THE latest power amplifier from the McMurdo Silver Sound Laboratories is the brand new 3A unit which delivers 32 watts undistorted (not over 2% total harmonic content), with an overall gain of 46 db. and any input impedance you ever need. Two of these units with two Super-Giant speakers, to which each 3A supplies 32 watts field power, "blew the roof off" the 18,000-seat Chicago Stockyards Auditorium when driven by a small preamplifier (ready now 100 db. gain, no hum, three-channel mixing, and *all* in $\frac{1}{8}$ of a cubic foot!).

Whenever you need power equal to over 200 watts into ordinary speakers, one 3A amplifier and one Super-Giant speaker will give it to you at less than 35c. per watt—with broadcast station quality. You can drive one to eight 3A with *one* 76 driver—they need no driving volume—each having a driver stage self-contained. One 6J7 feeding a 3A will give nearly 90 db. gain, draw its operating power from the 3A, and turn out 32 watts of better P.A. quality than you've *ever* heard before.

Quite a lot?—Why not write for the details of this and other up-to-the-minute sound units? Just use a postcard.

McMURDO SILVER CORPORATION
2900-L So. Michigan Blvd. Chicago, Ill.

McMURDO SILVER
MASTERPIECE
RADIOS—AMPLIFIERS

ASSOCIATION NEWS . . .

CLEVELAND CHAPTER IRSM

Our Fourth Annual Show is now history and will probably go down in the records as our most successful one (to date). In spite of the fact that we opened the day after Hallowe'en and closed the night before election, the attendance was within two hundred of our previous high in registration.

Then, too, it rained and when it rains it pours here. John Rider, who was due to speak on Sunday night, was grounded (his plane) at Kylertown, Pa. That didn't stop hizzoner, though—he was able to get to a phone. The Cleveland gang rewired a telephone switchboard in the hotel to make proper hookup to the p-a system in the auditorium and everything was okay. In spite of considerable mismatching in line and input equipment (John was using an old-fashioned side-wind wall phone) the lecture came through remarkably clear and distinct. The unusual hookup set the assembled gang on their ears and proved to be one of the highlights of the show.

Earlier in the afternoon and evening on Sunday several other speakers added to the interest of the meeting. Bob Herzog, Editor of SERVICE, opened the technical sessions with a discussion of "Noise Reducing Antenna Systems." Floyd Wenger of Triplet Electrical Instrument Company, demonstrated the uses of the vacuum tube voltmeter in the servicing of radio receivers. Mr. Jenkins of the Weston Electrical Instrument Company lectured on "Super-sensitive Instruments for Present Day Service Work." The welcome address by Al Theriault, Chairman of the Cleveland group, and the Wirephoto Demonstration led up to the dramatic address by John Rider as mentioned above.

Monday's session included a discussion of "Automatic Frequency Control" by Ernie Kochler, Engineer of Ken-Rad Radio Tube and Lamp Company; a continuation of the Wirephoto Demonstration; A talk on "Trouble Shooting with Cathode Ray Equipment" by Walter Weiss, Engineer of Hickok Electrical Instrument Company, and the RCA Victor Service School conducted by Paul Smith of the RCA factory.

Numerous prizes were distributed at the sessions and in the auditorium. The technical talks were well attended and it was long after midnight before the place was clear of Service Men.

L. Vangunten, Sec'y.

WASHINGTON CHAPTER IRSM

The Washington Chapter of the Institute of Radio Service Men held a regular meeting Thursday, October 22, at 1413 Park Road, N. W. Washington, D. C.

Don Craig of the Weston Electrical Instrument Corporation demonstrated the latest Weston equipment, describing its use in modern complex service work.

Bob Herzog, Editor of SERVICE, spoke on "Receiver Circuits"—explaining the function and relative value of each constant in the radio receiver.

A year's subscription to SERVICE was awarded as a door prize.

G. G. Larkin, Secy.

MARYLAND RADIO SERVICE ASSN., INC.

A regular business meeting starting at 8:00 P. M., Friday, October 30, was held by the Maryland Radio Service Association, Inc., at the New Howard Hotel. After the business meeting interesting sound movies were shown and Mr. Henry Hickman, WFBR's Inquiring Reporter, gave a short talk on "Building Good Will."

Wm. A. Thompson, Secy.

RADIO TECHNICIANS GUILD

Al Saunders is trying to prove that Providence Jake O'Leary can't put him under the table. (But we'll bet that Pro-vost can).

We understand that the Hotel Lenox had to remodel the place to take care of the next R. T. G. Exposition—that's what we call looking ahead.

That electrical wizard from New Bedford, "Tarzan" Ted Kurgan, is another one of them there guys what has done a fadeout. Maybe he has holed in for the winter.

The way Frank Kennes and Farn Harling are boasting about their new families, we would think that it's dangerous territory out where they live.

We've got to take our hats off to Arthur Mayer, of the A. W. Mayer Co., for his interest in the Service Men. You boys really ought to look him up.

The above goes for Mr. Childs of the Electrical Supply Co., also.

Wonder if Sig Malo got out his overshoes yet in preparation for the coming winter. It seems he went for a slide last winter, and is death against the N. E. climate. (Seattle papers please copy.)

Joe "Chuckie" Cabral has taken the R. T. G. so seriously that he even dreams about it. The rest of "youse guys" ought to take a few lessons from "Chuckie."

For the benefit of those who are not affiliated with any service organization, we would advise that you hook up with one of your local Service Men's clubs, be it the R. T. G. or any other outfit. You will need their assistance now with so much new stuff coming into being.

George Feldman, Secy.

RADIO SERVICE ASSN. OF CALIFORNIA

Perhaps other organizations would be interested in the way our meetings are conducted. We have found over a period of about five years that it is almost impossible to thresh out business matters at our regular meetings and still be able to hear the speakers, so this important task is delegated to, and carried out by, our executive board who meet for this purpose twice each month.

Because of the diversified interests rep-

resented, we confine our activities almost entirely to education and entertainment. At each session we have, in addition to a guest speaker, two fifteen-minute speakers appointed by the chair, from the membership, who talk on some subject of their own choosing. This is understood to be mandatory and has proven very satisfactory in that it gives everyone an opportunity to be heard and has uncovered some surprisingly good speakers.

We point with pardonable pride to an accomplishment sponsored and carried out by our organization under Carl Penther (then president) of having afforded all interested parties the opportunity of attending a class in radio communication conducted by Dr. Ruekema, professor of Electrical Engineering at the University of California. This attracted an opening attendance of some 300 and continued weekly for 18 months at which time 150 were still regular students. Dr. Ruekema, by the way, is a member of our association and a frequent guest speaker with a never ending choice of interesting and enlightening subjects on which to speak.

Herman A. Schmidt, Pres.

RADIO SERVICE ENGINEERS ASSOCIATION, INC.

On the evening of October 27, at the Essex House, Newark, N. J., the Radio Service Engineers Association, Inc., held a regular meeting. Those present (including a group from distant Staten Island, N. Y.) were amply repaid for the time spent. Matty Hughes presided and introduced the guests of the evening—service engineers from the Emerson Radio and Television Corp. The gentlemen from Emerson not only presented a complete description of the new Emerson line but also distributed circuit diagrams and other service information.

A unique Service Forum was introduced and, from the enthusiastic response, promises to become one of the outstanding features of our new independent organization.

At the present writing we are looking forward to our next meeting to be held at the Essex House on November 10. A representative of the Philco Radio and Television Corp. will describe automatic frequency control.

Ralph Roe, Secretary

NEW YORK CHAPTER NRIAA

The members of the New York Chapter are urged to attend the future meetings of the Chapter. The program committee has arranged a series of surprises. Every Service Man can be assured that his time will be well spent.

The regular meeting dates are the first and third Thursday of each month. The meetings are held at 12 St. Marks Place, New York City.

Allen Arndt, Chairman

• SERVICE FOR

AC CURRENT ANYWHERE!

In CARS . . . On FARMS . . . In DC DISTRICTS

With **ATR** ^{DC}/_{AC} **INVERTERS**

For Operating . . .
Standard 110-Volt or 220-Volt A.C. Radios, Public Address Systems, Electrical Testing Equipment, etc.



LIST PRICE **\$1850***

*Without Radio Filter \$22.50 with Built-in Filter (Standard Discounts Apply)

PROVEN—DEPENDABLE—GUARANTEED

OUTSTANDING FEATURES: • Interference-Free All Wave Radio Operation
• Improved Long Life ATR Vibrators • Four-Point Voltage Regulators
• 16 Different Types for DC Input Voltages ranging from 6 to 220 volts, and having AC output voltages of both 110 and 220 volts.

OTHER ATR PROFIT MAKERS

ATR AUTO "A" BATTERY ELIMINATOR



Specially Designed for Demonstrating and Testing Auto Radio Sets on Regular AC Lines, 105-125 Volts, 50-60 Cycles. Has many other uses. Comes completely equipped with On-Off Switch, Pilot Light Indicator, 10 ampere Fuse, Rubber Mounting Feet, 6 ft. Rubber Cord, Heavy Gauge Metal Cabinet.

DEALERS' NET PRICE **\$12.95**

ATR Automatic Tapering BATTERY CHARGER

Keeps Auto Battery fully charged right in the car! Operates from any 110 volt AC 50-60 cycle line. Equipped with a full wave dry disc type rectifier unit. Current tapers off as battery becomes charged. Comes completely equipped with Polarized Dash Receptacle and Plug, Fuses, 9 feet DC Cord, 12 feet AC Cord, On-Off Toggle Switch, and Complete Instructions.



LIST PRICES (Standard Discounts Apply)
Model 450. Max. charging rate 4 1/2 amp. \$9.67.
Model 600. Max. charging rate, 6 amp. \$11.45.
Model 1000. Max. charging rate, 10 amp. \$14.25.

Write or Wire for Additional Information Sold by Leading Jobbers Everywhere

AMERICAN TELEVISION & RADIO CO.

St. Paul, Minnesota, U. S. A. Cable Address: "Likex" New York

ANTENNA SYSTEMS

fitted to any pocketbook



★ TACO No. 500

All-wave. Self-selecting. Noise-reducing. Increased signal strength.

Complete kit. No extras to buy. Factory assembled, wired, soldered. Corrosion-proof. Just string up.

Attractively packaged. Complete instructions. Sells over counter or on service calls. Only \$4.50 list.

★ TACO No. 200

A D-Luxe System. All-wave. Self-selecting. And NOISE-LESS. Highest signal strength.

Complete kit. Ready to string up. Will last for many years.

Neatly packaged. Complete instructions. Positively the outstanding performance kit calling for minimum installation trouble. Only \$6.75 list.



Write for money-making facts

TECHNICAL APPLIANCE CORP.

17 East 16th Street

New York City



Stop that Noise!



At the connection cord—with Type IN-26 used as the plug.

At the receptacle (left) — with Type IN-25 fitted on face plate.

At the motor or source—Types IN-24 and IN-44 for use with heavy-duty equipment.

As its contribution to better all-wave reception, AEROVOX has developed and now offers a line of interference filters. • Simple. Effective. Inexpensive. • It will pay you to install these units wherever set owners complain about background noises.

Above: IN-25 model.
Below: IN-44 model.



Below: IN-26 model.




Write for latest catalog featuring interference filters as well as general line of condensers and resistors.



CORPORATION

70 Washington St. : : Brooklyn, N. Y.

Appearance matches quality

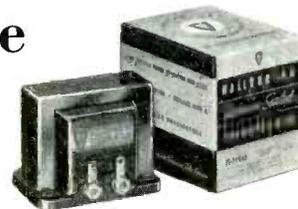

● Look for the yellow and black Halldorson box. It's distinctive . . . Rich Looking . . . In perfect keeping with Halldorson quality. All Halldorson transformers are vacuum-sealed and therefore impervious to moisture. Play safe . . . Follow the lead of old-time service experts who have cured their transformer troubles . . . Insist on

Halldorson

Vacuum Sealed Transformers

The Halldorson Co., 4500 Ravenswood Ave., Chicago, Ill. S-1136
Please send me your new catalogue of Vacuum Sealed Transformers.

Name
Address
City..... State.....

HIGHLIGHTS . . .

NATIONAL UNION APPOINTMENT

National Union Radio Corp. announced this week the appointment of J. H. Robinson as Director of New Products Research. Mr. Robinson assumes the new title and duties, in addition to his regular work as Export Manager.

It is said that Mr. Robinson has been assigned the task of seeking out and analyzing the marketability of new products, patents and ideas having to do with radio, electronics, television and electrical industries.

Inventors are invited to correspond in strict confidence with Mr. Robinson, care National Union Radio Corp., 570 Lexington Ave., New York, N. Y. It is the belief of the National Union organization that an era of great development and advancement is at hand and they are prepared to encourage the promotion of new practicable ideas.

SHURE CATALOG

A 6-page 1937 catalog of microphones and accessories has been issued by Shure Brothers, 225 W. Huron St., Chicago. Copies are available upon request.


Among the latest additions to the Shure line shown in this catalog are the "Ultra"-wide-range crystal microphones, in spherical, swivel and "Grille-type" models, the model 85A high-fidelity sound-cell type crystal microphone, and a series of crystal and carbon microphones with 4-way utility features.

ARCTURUS CARRYING CASE

To help dealers and Service Men increase their tube sales, the Arcturus Radio Tube Company, Newark, N. J., has made available to the trade a cardboard carrying case for consumer's use in bringing complete sets of tubes to the store for testing.

This case comes flat and requires no assembling. Opening like a shopping bag, it contains compartments to hold ten tubes.

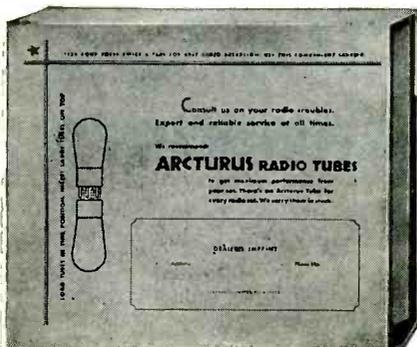Space is provided for the dealer's imprint, making this case suitable as a business card or mailing piece for dealers. With the dealer's imprint, these Arcturus cases are available at a low price through Arcturus Distributors.



588

MANUFACTURERS REPRESENTATIVES

WHEN MANUFACTURERS of radio parts and accessories require representation in various parts of the country, they usually ask SERVICE for recommendations. Such requests have been especially numerous of late. As a result SERVICE is endeavoring to bring its lists up-to-the-minute. Representatives are urged to send a complete record of their territory and lines to SERVICE Magazine, 19 East 47th Street, New York City. With complete data on hand SERVICE may be instrumental in increasing the number of lines of many representatives.

AUDAK BROCHURE

A brochure entitled "Pickup Facts" has been released by the Audak Company, 500 Fifth Avenue, New York City. This booklet contains a treatise on Relayed-Frequency Pickups which is said to be of interest to every broadcast and sound engineer. Illustrations and details of the entire Audax line of pickups, which are built on the magneto-induction principle, are also included. Audak will mail a copy of "Pickup Facts" upon request.

AMPLIFIER CO. BOOKLET

A booklet illustrating and describing the ACA Citation Series Gold Medal amplifiers has been prepared by the Amplifier Co. of America, 39 West 20th St., New York City. It's full of data for public address and sound engineers. Copies may be had by writing to the manufacturer.

CONTINENTAL MOTORS REPRESENTATIVE

Continental Motors Corp., Detroit, Mich., announces the appointment of John J. Kopp, 60 E. 42 St., New York City, as Eastern District Sales Representative. Mr. Kopp will handle "Tiny Tim" portable battery charger and lighting plant, "Perm-O-Flux" permanent magnet dynamic speakers and "Kleen-Aire" portable air conditioner.

"KENYON ENGINEERING NEWS"

Vol. 1, No. 1 of *Kenyon Engineering News* will make its appearance at an early date. This monthly publication, which will be edited by J. B. Carter, is to be devoted entirely to the amateur, sound technician and experimenter. The first issue will feature, among other things, the following: a new combination mixer and preamplifier; tone equalization; audio amplifiers; modulation improvements in transmitters, and four handy engineering data charts, known as Ken-O-Grafs.

Kenyon Engineering News is published by the Kenyon Transformer Company, 840 Barry Street, New York, N. Y.

CURTIS CATALOG

The Curtis Condenser Corp., 3088 W. 106th St., Cleveland, Ohio, have published a catalog of their filter, by-pass and replacement condensers. Copies may be had by writing directly to the manufacturer.

WEBSTER-CHICAGO APPOINTMENT

R. M. Gray (Rocky) has been appointed sales manager of Webster-Chicago.

Rocky is one of the best informed individuals in the sound-sales field, having been in sound work since 1929, and from 1931 to 1932 was manager of the parts and sound division of Silver Marshall, Inc. From the spring of 1933 until December, 1934, he supervised installation and operation of all p-a equipment at the Century of Progress, Chicago.

U. S. TRANSMITTER CORP.

Rocke International Electric Corp., 100 Varick St., New York City, announces the formation of the U. S. Transmitter Corp., an organization manufacturing all types of communication apparatus. Transmitters, receivers and amplifiers for the government and export market are now being manufactured at their plant, 75 Crosby St., New York City.

A. Pleasanton is plant manager. Frank Edmonds is chief engineer.

TERRA FIRMA LEON

One of the best customers the commercial airlines boast of is busy Leon L. Adelman, sales manager of the Cornell-Dubilier Corp., So. Plainfield, N. J. During the last two months, however, the flying personnel have missed Leon's smiling features. Result—personal cards from pilot pals (a couple from pretty hostesses, too), which called for an explanation.

Leon has been practically tied to his desk for more than 90 days. Both New York and Plainfield plants of the Cornell-Dubilier Corp. are said to be operating at full capacity and production of C-D condensers has reached 60 per cent above the peak of 1935.



• SERVICE FOR

There is no other
Permanent Magnet Speaker
like the **NOKOIL**



No.
1984

Cadmium plating makes all parts thoroughly rust-proof which is essential to perfect permanent performance. A super-sensitive high power Public Address NOKOIL Reproducer at a price that is within the reach of any sound engineer.

LIST PRICE **\$19.84** Dust proof
Rust proof
Weather proof

Write for catalog showing the World's most complete line of NOKOIL Reproducers, and the name of our nearest distributor. Wright-DeCoster distributors are always anxious to cooperate.

WRIGHT-DECOSTER, Inc.

2253 UNIVERSITY AVENUE, ST. PAUL, MINN.

Export Dept.: M. Simons & Son Co., N. Y.

Cable Address: "Simontrice"

Canadian Office: Associated Sales Co., Guelph, Ont.

BRUSH General Purpose MICROPHONE

The Brush G2S2P sound cell microphone—an all around general purpose microphone for program—remote pickup and announcing work. Widely used in high grade public address installations. A typical sound cell microphone built to Brush's traditionally high mechanical and electrical standards. Non-directional. No diaphragms. No distortion from close speaking. Trouble-free operation. No button current or input transformer to cause hum.

Beautifully finished in dull chromium. Output level minus 70 D.B. Size 3 inches by 1 1/4 x 1 1/8 inches. Furnished complete, at no extra cost, with a Brush S-1 socket that facilitates easy installation. Full details will be found in Data Sheet No. 4 Free. Send for one.



BRUSH Headphones



Meet every headphone requirement. Response 60 to 10,000 cycles. No magnets to cause diaphragm chatter. Specially designed cases minimize breakage. Light in weight. Only 6 oz., complete with headband and cords. A quality product at a low price. Details, Data Sheet No. 10. Copies on request. Send for one.


The **BRUSH** DEVELOPMENT COMPANY
PIEZO ELECTRIC CLEVELAND, O.
1882 E. 40th St.
MICROPHONES • MIKE STANDS • TWEETERS • HEAD PHONES • LOUD SPEAKERS

NOVEMBER, 1936 •


SAY YOU SAW IT IN SERVICE



PULL-PUSH
MOISTURE PROOFED
TRANSFORMERS

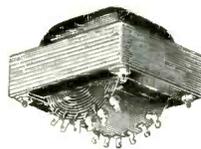

Type "P"
See note below

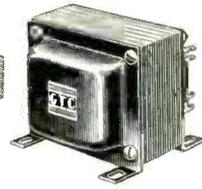

All half-shell "P" type are supplied with four brackets in each carton so that the units may be mounted either flush, horizontal or vertical as shown above.

**2.5 Volt Double Fil. Winding
Combination 2.5 V. and 6.3 V. Single-Heater Winding**

These require one-half the investment in stock to enable giving immediate renewal of performance in most cases of transformer trouble.

Any Capacity Set—4 Tube Midget to 12 or More Tubes

"PULL-PUSH" Impregnation of coils PULLS out all moisture (by means of preheating ovens and high vacuum tanks) and PUSHES in Special 9X Moisture-proofing Wax (under high compression). Sealing is perfect. No dripping of the 9X High Melting-point Wax, and subsequent shorting under normal operation in the hottest, most humid climates. This is very essential in humid sea coast climate or where hot days followed by cool nights causes condensation on the coils.

GTC Transformers are built with a low loss high permeability silicon steel core of sufficient stack to leave a factor of safety over the highest rating specified for the unit. In many instances several tubes might be added to each rating with safety were there no fluctuation of supply current.

Greater customer satisfaction means increased business for you. ALWAYS INSIST ON GENERAL Highest Efficiency "PULL-PUSH" Impregnated Transformers!—with the GTC label on the carton!

Free for the Asking!

**GENERAL TRANSFORMER
CORPORATION**

502 S. Throop Street
Chicago, Ill.

Form 31—bulletin listing transformers and chokes to meet service engineers' every need.

Mr. Service Man THE RADIO'S DOWNSTAIRS!

So down you go and fix it. Of course you will use Ward Leonard replacement parts. You will do a good job and be called in again when your services are needed. That is how a permanent and profitable business is built. Send for the new Ward Leonard Servicemen's bulletin 507A. It shows the Ward Leonard Line and gives prices. Write for it today.



WARD LEONARD ELECTRIC CO.

South Street, Mount Vernon, N. Y.

Please send me free copy of Bulletin 507A.

Name
Address
City State
Jobber

589

THE MANUFACTURERS . . .

ARCTURUS 25B5 AND 25N6G

The Arcturus Radio Tube Co., Newark, N. J., has added to its line the 25B5 and its octal base counterpart, the 25N6-G. This is a duplex-triode power output tube particularly designed for a-c, d-c sets.

As a single ended Class A amplifier with 110 volts d-c supply, this tube will develop 2 watts of audio at 9 percent total harmonic distortion, about twice the output available from other pentode tubes in a-c, d-c circuits.

The tube operates without C bias, obviating the need for bias resistor with its necessary filter network. Because the grid does not draw current since an automatic bias is applied within the tube, the input impedance is high and the tube needs no special driving equipment such as is necessary for Class B operation.

The resultant reduction in cost of parts and the simplicity of its circuit recommends this tube as well in large receivers where greater power is desired by conventional push-pull operation.


SHIELDED TEST ROOM

The need for accurate information on the construction of an effective shielded test room, in which the Service Man may fully utilize modern test equipment without interference from strong local fields of either man-made static or broadcasting stations, is met by a set of specifications just issued by the Tobe Deutschman Corp., Filterette Division, Canton, Mass.

These specifications show the construction of a shielded test room approximately 6-ft. square, and enable the Service Man or any local builder to construct the shielded room without difficulty.

SOLAR REPLACEMENT LINE

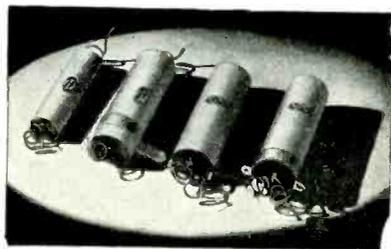An expanded exact replacement line is announced by Solar Mfg. Corp., 599 Broadway, New York City. Many of the types used in the current receiver models, such as the universal cardboard-tube units with



various mounting arrangements, are included in the line.

The quality of these replacements is equal to that found in other Solar products.


Literature will be furnished by Solar Mfg. Corp. upon request.

RCA-956

RCA-956 is a heater-cathode tube of the remote cut-off type for use by radio amateurs and experimenters as a radio- and intermediate-frequency amplifier, or mixer, in receivers operating at wave lengths as low as 0.7 meter.

The super-control feature of the 956 makes the tube effective in reducing cross-modulation and modulation-distortion over the entire range of received signals. This feature also makes the tube well adapted to circuits incorporating automatic volume control, without the necessity for using local-distance switches or antenna potentiometers.

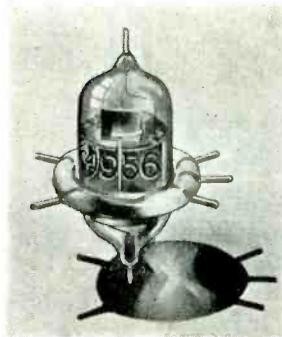At a wavelength of one meter, the 956 is capable of giving a gain of four or more when it is used as an r-f amplifier in circuits of conventional design. Higher gains are, of course, attainable at longer wavelengths. Operation at short wavelengths is made possible by means of an unconventional tube structure having small size, close electrode spacing and short terminal connections.



Tentative Characteristics		
Heater voltage (ac or dc)	6.3	volts
Heater current	0.15	ampere
Plate voltage	250 max.	volts
Screen voltage	100 max.	volts
Grid voltage (min.)	-3	volts
Suppressor	Connected to cathode	at socket
Plate current	5.5	ma
Screen current	1.8	ma
Plate Resistance	0.8	megohm
Amplification factor	1,440	
Mutual conductance	1,800	micromhos
Mutual conductance (at -45 volts bias)	2	micromhos
Grid-plate capacitance (with shield-baffle)	0.007 max.	mmfd
Input capacitance	2.7	mmfd
Output capacitance	3.5	mmfd

The 956 may be held by means of a special socket or by means of a mounting using the clips supplied with each tube. The two small clips are for the control grid and the plate terminal at the bottom and top of the bulb, respectively.

TEST EQUIPMENT TRAILER

Chas. F. Zehner, manufacturers' representative, 5718 Keniston Ave., Los Angeles, Cal., uses the trailer shown in the



accompanying illustration to demonstrate radio test equipment to Service Men.

OPERADIO PRE-AMPLIFIER

The Operadio model 660 a-c operated microphone pre-amplifier is designed to mix two microphones of the velocity or grille type of crystal. It has an overall gain of 65 db with a low hum level. Electronic mixing of the microphones is provided with a tone control for shading.

The 660 is a two-stage amplifier with first stage tubes cushion mounted to decrease microphonics. The entire unit is housed in a steel carrying case with provision for plug-in connections at the input and output. Two units may be used together to form a four-position electronic mixer and pre-amplifier.

Additional information can be obtained from the Operadio Manufacturing Co., St. Charles, Ill.

TURNER MICROPHONE

The model VT-73 is a crystal microphone being announced by The Turner Co.

This microphone has been designed to have suitable response for voice transmission. The output level is higher than on previous models.


Several new constructional features insure the microphone against adverse climatic conditions.

MEISSNER COIL ASSEMBLY

The Meissner Manufacturing Co., Mt. Carmel, Ill., has announced an all-wave coil assembly with air-dielectric trimmer condensers. Separate coils are used for each band in each stage. The coils are mounted directly on the band switch, with the coil terminal lugs serving as the connection and support. The assembly is designed to operate with a three-gang 410-mmfd condenser and 456-kc i-f transformers.

Additional information may be obtained from the manufacturer.

HERE IS *Your* CHANCE

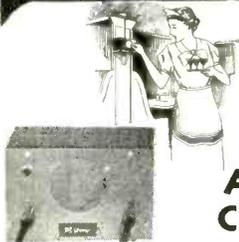

TO CASH IN ON A BUSINESS ESSENTIAL
BELfone
A COMPLETE TWO-WAY COMMUNICATING SYSTEM

for \$39.50
Slightly higher west of the Rockies.

The market is unlimited. Every business needs the economy—the convenience—of the new BELfone method of communicating between departments. You merely flip a key on a little unit (the size of midget radio) and have clear and distinct conversation with other departments. Arranged for two stations or multiple stations for desk-to-desk use, — or FOR CONVERSING WITH A PERSON FROM ANY POINT HE MAY BE IN A LARGE ROOM — BELfone saves time, steps and effort. BELfone actually sells itself on demonstration. It's as easy to install as a buzzer system and works on your regular current . . . economical in every respect! Convince yourself on this new money-maker by installing a BELfone for your own use.

Write TODAY for the facts on BELfone. Only BELfone gives you quality construction necessary for permanent customer satisfaction.

Mr. Jobber: Here's a product worthy of your investigation.



Export Office: 308 West Washington Street., Chicago, Ill.

BELL Sound Systems, Inc. **BELL SOUND SYSTEMS**
61-62 East Goodale St. Columbus, Ohio



Metal-Can Electrolytics



The most capacity in least bulk . . . lowest cost . . . longest trouble-proof service. That's the story of AEROVOX metal-can electrolytics. Also, the greatest variety of electrolytics to meet every requirement.

New CATALOG More pages. More items. More choice. Lower prices. Ask your local AEROVOX Jobber for copy, or write us direct.

Series E: Vertical mounting. Grounded can. Single, dual, triple sections.



Series I: Inverted, insulated mounting.



Series GL: Inverted, insulated mounting. Single, dual, triple. Individual leads.



Series GLS: Midget units. Inverted, insulated mounting. 1" dia. Half height of usual units.

AEROVOX
CORPORATION
70 Washington St. Brooklyn, N. Y.

Hot off the Press

THORDARSON'S BIG 1937 Radio Servicing Guide. Here are a few features which make this new — profusely illustrated guide, the **Biggest Bargain** you have seen. 32 pages of tested ideas and suggestions. How to build a direct reading voltmeter. 4 pages of truly worthwhile auto installation hints. Hundreds of ideas—suggestions and helpful articles. Buy your copy from your parts distributor or write direct to the factory **today**. Only 15c post paid.



FREE — NEW FALL CATALOGS — FREE
Catalog No. 400—Complete line of Thordarson Transformers.
Catalog No. 500—Tru-Fidelity by THORDARSON.

THORDARSON ELECTRIC MFG. CO.
500 W. HURON ST., CHICAGO, ILL.
Demand "Power by Thordarson"

from now on
it's
UNIT-MATCHED P.A. EQUIPMENT *for me!*



I've been doing P. A. installation work for a long time. I started buying parts . . . a microphone here, an amplifier there, a speaker from still another manufacturer.

Well, after the job was all set, it worked all right, but somehow or other I always had to keep running back to fix this and that . . . in short the equipment never seemed to work 100% right . . . and the calls were costing me money.

It wasn't until I started buying OPERADIO Unit-Matched P. A. Equipment, that I really could depend on installations working right and staying right.

I want to tell you that for real satisfaction, no complaints and a good sizeable profit, you can't beat the OPERADIO line.

Address Dept. S for Catalog.

Ask About Our Convenient Time Payment Plan.



OPERADIO
MANUFACTURING COMPANY
Unit-Matched P. A. Equipment at its Finest
ST. CHARLES, ILLINOIS

MANUFACTURERS—continued

CONTINENTAL CARBON FILTERNOYS

The three different types of Continental Carbon noise elimination devices known respectively as Filternoys Rejectors for use between a radio receiver and the power supply line; Filternoys Diverters consisting of pure capacity units for connection across the power supply line and Filternoys Suppressors for use on equipment causing interference will be marketed by Continental Carbon, Inc., 13912 Lorain Ave., Cleveland, Ohio.

A booklet containing full information can be obtained by writing directly to the manufacturer.

POWERTONE VOLT-OHMMETER

The Powertone Electric Co., 179 Greenwich St., New York City, announce their model 801 volt-ohmmeter. The 801 is built in a 5- by 3- by 2-in. metal case and contains a 3-in. 1,000-ohm-per-volt meter.

Additional descriptive material can be obtained by writing to the manufacturer.

RAYTHEON TYPE 6H5

The 6H5 high-vacuum, tuning-indicator tube is designed to visually indicate the effect of changing the control grid bias. The 6H5 is similar to the 6G5 except that the current to the target is controlled by a grid tied to the cathode within the tube instead of by emission saturation as in the 6G5. The addition of this grid causes a fixed 90° shadow to appear on the screen opposite the controlled shadow.

Additional information as well as characteristics of the new tube can be obtained from the Raytheon Production Corp., 420 Lexington Ave., New York City.

TRIUMPH INSTRUMENTS

The Triumph Manufacturing Co., 4017 W. Lake St., Chicago, has developed three new instruments. A 20-ounce pocket size volt-ohmmeter with a selective range switch and direct-reading scales designed around a bakelite-cased 50-mv meter; a 30 feature a-c signal generator calibrated from 100 kc to 75 mc and a multirange meter comprise the new additions.

More complete descriptions as well as electrical specifications can be obtained from the manufacturer.

TRIAD FREE TUBE


A radio-tube merchandising plan, announced by Triad, makes it possible for Service Men and dealers to obtain one free Triad tube. By distributing a great number of free tubes the Triad Manufacturing Co. expects to awaken the interest of dealers and Service Men to the profit possibilities of Triad tubes.

Additional details can be obtained directly from the manufacturer.

FOX BAFFLE HORN

Announcement of the Fox B-5 universal baffle type horn is made by The Fox Sound Equipment Corp., Toledo, Ohio.

Any standard 12-inch speaker can be

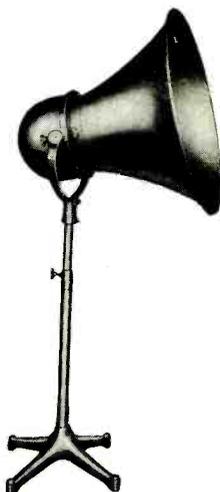


used. The horn is supported by a sturdy adjustable cradle complete with lock-screw adjustment.

The bell is made of Fox special alloy horn material and is designed for utmost output. The cast-aluminum throat collar reinforces the entire assembly, forming a foundation for speaker mounting and cradle.

The back cover is of heavy horn material and has an air by-pass so that the speaker can breathe. The B-5 is finished in standard aluminum gloss or special Fox wrinkle and is complete with adjustable stand.

WESTERN ELECTRIC 316A

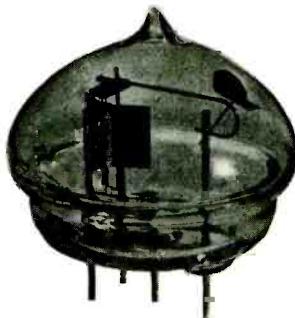The 316A vacuum tube, recently announced by the Western Electric Company, is shown in an accompanying illustration.



This tube, a filamentary air-cooled triode, is for use by experimenters and amateurs, and is suitable for ultra-high-frequency oscillator and amplifier applications, the frequency limit being 750 megacycles (approx. 0.4 meter).

As will be noticed no base is provided for the 316A. The grid, plate and filament leads are tungsten rods projecting from a flat face of the bulb, and the tube may be supported by these leads, providing flexibility is maintained so that no glass strains are produced. The nominal filament voltage is 2.0 volts, a-c or d-c, the nominal filament current is 3.65 amperes, and the average thermionic emission is 0.4 ampere.

The following performance data are based upon a typical tube and variations can be expected with different tubes of this type and with different circuits.

Average Characteristics at maximum direct plate voltage and dissipation ($E_b = 450$ volts, $I_b = 67$ milliamperes).

Amplification factor..... 6.5
Plate resistance..... 2,700 ohms
Grid-to-plate transconductance..... 2,400 micromhos

Average Direct Interelectrode Capacitances

Plate-to-grid 1.6 mmfd
Grid-to-filament 1.2 mmfd
Plate-to-filament 0.8 mmfd

OPERATION

Maximum Ratings

Max. direct plate voltage 450 volts
Max. direct plate current. 80 ma
Max. direct grid current. 12 ma
Max. plate dissipation... 30 watts

R-F Oscillator or Amplifier—Unmodulated

Max. direct plate voltage 450 volts
Max. direct plate current. 80 ma
Max. direct grid current. 12 ma
Nominal power output at 500 mc..... 7.5 watts

R-F Oscillator or Amplifier—Plate Modulated

Max. direct plate voltage 400 volts
Max. direct plate current. 80 ma
Max. direct grid current. 12 ma
Nominal carrier power at 500 mc..... 6.5 watts

The following table indicates the nominal output obtainable from the 316A as an unmodulated oscillator with an input of 400 volts and 80 ma d-c.

Frequency—mc	Power Output—watts
300	8.5
400	8.0
500	6.5
600	4.0
750	limit of oscillation

When the 316A tube is used at frequencies above 300 mc, several precautions must be observed in circuit design in order to obtain good efficiency. It is necessary to provide tuning in the filament to ground circuit. The use of adjustable concentric lines of approximately $\frac{1}{4}$ wavelength for each filament lead is probably the most satisfactory method. It is also desirable to avoid the use of dielectric material as much as possible and to confine that which is necessary for mounting circuit elements to points of low r-f voltage. The grid and plate supply leads should be connected at nodal points if possible.

Clarion
PUBLIC ADDRESS EQUIPMENT

**"AS UP TO DATE
as Tomorrow"**

Visit the authorized CLARION Distributor in your vicinity . . . ask him to demonstrate this "Year Ahead" line . . . ask him to explain the CLARION sales policy which protects the Sound Engineer who makes the sale. THEN . . . ask him to tell you the prices — you'll be AMAZED that so fine a line, engineered to the most exacting standards and built to stand a world of abuse can be manufactured at such low prices. The answer is, of course, CLARION mass production!

**TRANSFORMER
CORP. OF AMERICA**
Dept. L15
69 Wooster St., New York City

**HOW DO YOU
DO IT?**

How do you solve the many servicing problems with which you have to contend . . . what special kinks have you worked out which help you in servicing receivers . . . have you developed shortcut schemes for testing, or built test devices that do the work better and faster?

No matter what the scheme or the device, there are many Service Men who would like to know the how's and why's—just as you would like to know about the schemes and devices employed by others.

All you have to do is give us the outstanding points, and a rough pencil sketch of the device if it happens to be such—and we will do the rest.

Write up those ideas now and send them in to the . . .

ON THE JOB DEPARTMENT
SERVICE
19 East 47th Street New York City

Filternoys

Rejectors, Suppressors, Diverters



F505DH



F01D



F1005DH



R01H

Filternoys—the new name for CONTINENTAL Carbon line noise interference filters!

Sell a Filternoys rejector for every radio receiver. Sell Filternoys suppressors for domestic electrical appliances. Sell Filternoys diverters for industrial electric devices that cause interference.

CONTINENTAL Carbon offers a complete assortment of supply line noise filters, priced right for quick sales over the counter or on the job.

Stock up for Christmas business. F505DH is recommended to suppress interference from flashing tree lights, toy trains, sweepers, and heater pads; F01D to divert the interference from electric cash registers, scales, soft drink mixers, etc., to ground; F1005DH to block interference from entering on a main house line; R01H to reject line noise at the radio.

Write for full details
or ask your jobber.

CONTINENTAL CARBON Inc.

13912 Lorain Ave., Cleveland, Ohio

Toronto, Canada

TO DEALERS AND SERVICEMEN

TRIAD RADIO TUBE FREE!

UP TO \$1.25 LIST

A DARING NEW PLAN
To convince you of the superior quality of Triad Radio Tubes—we are offering absolutely free any Triad Tube up to \$1.25 list with your purchase of Triad Radio Tubes; also free Engineering Data Chart. Mail coupon below—back will come your Free Tube Certificate. Present it to your jobber when you purchase Triad Tubes and get your Free Tube—save \$1.25.

MAIL TODAY!

TRIAD MANUFACTURING CO., Inc. THIS COUPON
Dept. L-12 Pawtucket, R. I. WORTH \$1.25

Sure I'll try Triads. Send me Free Tube Certificate . . . good for \$1.25. Also FREE Engineering Data Chart.

Name _____
Address _____
Town _____ State _____
Jobber's Name _____

"THE QUALITY NAME IN RADIO TUBES"

WESTON LINE DESCRIBED

The complete line of Weston radio servicing instruments, including the new Model 772 analyzer which operates at a sensitivity of 20,000 ohms-per-volt, are described and illustrated in a new folder published by the Weston Electrical Instrument Corporation, Newark, N. J. Specifications for sixteen fundamental test instruments each designed to meet the requirements of some particular phase of service work, are included in the folder. The instruments described not only permit analysis of modern receivers and their component parts, but extend dependable direct-reading measurement to many other types of electronic circuits and equipment—television, public-address system, talking picture recording, and the like.

Fields of application, ranges, operating characteristics, size and price are shown for each instrument, thus providing the basis for selecting a coordinated group to meet specific needs. In addition, the new models are described point-by-point, with emphasis on features of design essential for servicing present and future receivers of increasing complexity.

AUTO RADIO TESTING

The accompanying illustration shows an auto-radio Service Man making a complete diagnosis of a sick car radio as the owner watches. A Bendix Day-Rad (Model 200) radio testing device is being used. This unit—as well as a complete Day-Rad line of similar instruments—is the latest member of the large family of Bendix manufactured devices. This Day-Rad also tests a car's ignition



system and gives data upon modern radio tubes.

ALADDIN TRANSFORMERS

A new series of Polyiron-core i-f transformers has been made available by

Aladdin Radio Industries, Inc., 466 W. Superior Street, Chicago, Ill. These transformers are tuned by means of movable Polyiron cores, the resonant circuits being completed by high-quality fixed condensers. The gain and selectivity of the units are said to be entirely adequate for present-day requirements.

MUTER ZIPOHM

Zipohm, a wire-wound replacement resistor, designed for Service Men, is available in 5- and 10-watt sizes. This unit is noiseless, compact, accurate and impregnated with waterproof cement. Each resistor value is marked with an aluminum tag. The Zipohm Servicemen's Kit contains 57 units in 27 different values which have been selected from frequency charts to cover 80 per cent of average requirements. The Muter Co., 1255 S. Michigan Ave., Chicago, has prepared a bulletin giv-



ing complete details, which is available upon request.

HIGHLIGHTS—Continued

RIDER'S VOLUME VII INDEX

Time and again you may find it necessary to identify a receiver when you do not know the model number but have established the chassis number. In previous editions of the Rider Manual Index, the chassis number was always associated with the model number and oftentimes its presence in the index was completely missed. Each and every chassis number shown in the seven Rider Manuals is separately listed in numerical or alphabetical sequence, in addition to the regular listing of the receiver model number.


Another problem has been solved at considerable expense. Specific reference is made to manufacturers who have identified some of their chassis by certain model numbers, but never released any data concerning these models. Investigation during the past year disclosed that in many cases these specific models were identical in circuit arrangements to other models, but did not bear such identifying data. Rider has been successful in securing the required information from the manufacturers and this material is also identified in the Volume VII index.

CENTRALAB CATALOG

A new catalog of controls, resistors and selector switches has been received from Centralab, 900 E. Keefe Ave., Milwaukee, Wis. Among the many items listed will be found the new Isolantite-insulated switches recently developed by Centralab, and a complete list of replacement volume controls.

FERRANTI R-F VOLTMETER

A new Ferranti instrument with a full-

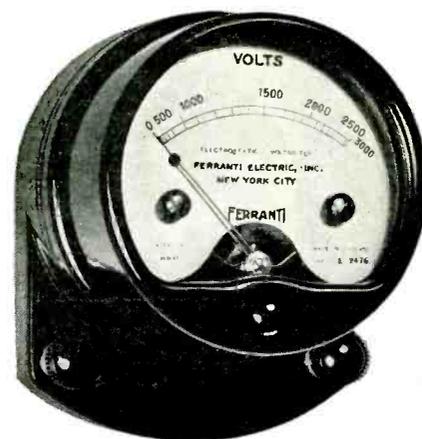

scale reading of 3,000 volts and a (full-scale) capacitance of only 8 mmfd can be connected across r-f circuits up to 1,500 kc. Ten different full-scale readings of from 150 to 3,500 volts are available. Three models can be obtained: portable, projecting or flush, in 2½ in., 3¼ in. or 4 in. dials.

Complete description can be obtained by writing to Ferranti Electric, Inc., 30 Rockefeller Plaza, New York City.

GHIRARDI SERVICE DATA

A new service for Service Men is announced by Radio & Technical Publishing Co. in connection with the second revised edition of Ghirardi's "Radio Field Service Data." Supplement sheets will be issued periodically to keep the data up to date. The new edition of the book is in loose-leaf form to accommodate the supplements as they are issued.

The edition contains 436 pages, 81 diagrams, including 62 electrical wiring diagrams of automobiles, 27 data charts and tables, the i-f peak listings for 5,226 superhet receivers (representing the sets of 154 different manufacturers), etc. All sections of the book have been enlarged and revised—the new book is twice as large as the old one. A circular describing the contents of this latest "Ghirardi" book in more detail may be obtained by writing Radio & Technical Publishing Co., 45-S Astor Pl., New York, N. Y.

AEROVOX CATALOG

An enlarged and revised catalog has just been issued by Aerovox Corporation, 70 Washington St., Brooklyn, N. Y., and is now ready for distribution. Known as the Second Edition 1936 Catalog, this literature covers an extensive line of condensers and resistors for radio and allied applications. Many new condensers are announced. A copy of the catalog may be obtained from the local Aerovox jobber or by writing the company direct.

• SERVICE FOR



ANNOUNCING The New Fox B-5 Universal Baffle Type Horn

Outstanding features:

Quality construction.
Completely universal in directional characteristics.

Supported by a sturdy adjustable cradle complete with lock screw adjustment.

The Bell is made of FOX special alloy horn material and is correctly designed for utmost output.

The cast aluminum throat collar reinforces the entire assembly, forming a perfect foundation for speaker mounting and cradle.

All standard 12-inch speakers can be used.
The Back Cover is of heavy horn material and has the proper air by-pass so that the speaker can breathe, thus eliminating distortion.

Available complete with adjustable stand.
A perfect combination for indoor or outdoor work.
Finished in standard aluminum gloss or Fox special wrinkle.

Write for catalog sheets and prices.

FOX SOUND EQUIPMENT CORP.

3121 Monroe Street

Toledo, Ohio

POWERTONE

Model 801 Volt-Ohmmeter

A sensitive, compact, and accurate volt-ohmmeter that in all probability will be the busiest piece of test equipment in your shop or out on jobs. Slips easily into the side pocket of your coat. D.C. Voltage readings 0-5-50-500-1000. Resistance readings from 1/2 to 500 and 200 to 500,000 ohms. Will also read from 0-1 Ma. Meter has 1000 ohms per volt sensitivity. Battery is self contained. Panel clearly engraved. Compensator provided for zero adjustment.

NET DEALERS PRICE \$5.75
With Battery

Send for Illustrated circular of POWERTONE test equipment.

Distributor: TRY-MO RADIO, 85 Cortlandt Street, New York City
POWERTONE ELECTRIC COMPANY
179 GREENWICH STREET NEW YORK CITY



RADIO AMATEUR CALL BOOK



is the only publication listing all radio amateurs throughout the entire world.

It also includes a complete list of High Frequency Commercial Stations, International Abbreviations and "Q" Signals, High Frequency Press and Weather Schedules, "Q", "R" and "T" Signals, U.S. Radio Inspection Districts, International Prefixes.

Every radio amateur should have a copy of this valuable book. Always up-to-date, published quarterly, single copies \$1.25, annual subscription \$4.

RADIO AMATEUR CALL BOOK, Inc.

612 So. Dearborn Street

Chicago, Illinois

NEW ZIPOHMS
A SUPERIOR WIRE WOUND REPLACEMENT RESISTOR

PIN THIS AD TO YOUR LETTERHEAD AND MAIL FOR COMPLETE DETAILS

MORE WATTS PER INCH
MORE WATTS PER DOLLAR

Servicemen—learn the advantages of this new, different and superior resistor. It's flat, taking less room—noiseless—cement impregnated—equipped with adjustable leads. Zipohms are made in all standard values, clearly marked. Write for Special Introductory Kit offer today.

THE MUTER COMPANY
1255 SOUTH MICHIGAN AVE. CHICAGO, ILLINOIS

ELECTRO-VOICE



Public Address men, everywhere, are standardizing on ELECTRO-VOICE microphones. Constant improvement resulting from unceasing research keeps this line ahead of the field. When you buy an ELECTRO-VOICE product, you buy the latest in engineering design.


Six Velocity models priced from \$19.50 to \$75.00 list. Carried in stock by leading distributors.

ELECTRO-VOICE MFG. CO., INC.

332 E. Colfax Ave., South Bend, Ind.

Export Office: 100 Varick St., New York, N. Y.

NEW SERIES METAL TUBE AMPLIFIERS

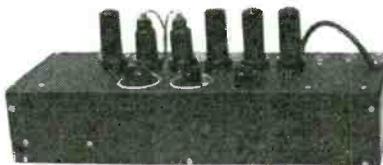

PA-7-C

FLEXIBILITY PLUS

Each "SSI" amplifier from 7 to 50 Watts is offered in

from three to five models to meet every need of the dealer or ultimate user for permanent or portable installation.

SOUND SYSTEMS, INC.

6545 CARNEGIE AVE.,

CLEVELAND, OHIO



NEW ALL WAVE ANTENNA KIT
with unusual features

Here is an all-wave antenna kit that really will improve your reception because it has been factory connected and soldered to eliminate incorrect and poor connections.

FEATURES include: Easy to Install. Antenna Transformer matches impedance to transmission. No signal loss in transmission to receiver coupler. No switching for s.w. or broadcast. 2 Models: No. 375—All Wave Antenna.....\$4.25 ea. list No. 376—All Wave Antenna for sets with built-in aerial selector.....\$3.50 ea. list

See your Jobber. If he cannot supply you, write direct to Dept. S-11.

BIRNBACH RADIO CO.
145 HUDSON ST. BIRCO NEW YORK, N. Y.

AERIALS FOR 1937

What Will **WARD PRODUCTS** Show for 1937?

TOP AERIALS • WHIPS • POLES
RUNNING BOARD AERIALS

WARD PRODUCTS CORP.
Cleveland, O.

CANADA: ATLAS RADIO CORP., TORONTO, ONT
FOREIGN: LINCOLN EXPORT CO., N. Y.

USE THIS COUPON

WARD PRODUCTS CORP.
Ward Bldg. - Cleveland, O.

Send information of Ward's 1937 Auto Aerials.

Name

Address


Check Dealer Jobber Service Man

Be
Wise

Meissnerize

Use **MEISSNER QUALITY COILS** throughout your service work. Your trade will pay more for a service job that's Meissnerized.

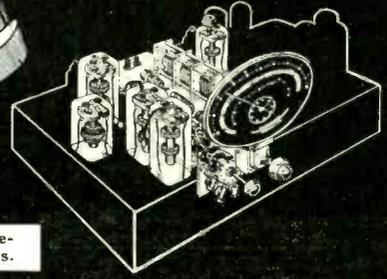Our new bulletin No. 510 contains the most complete coil listing ever presented. Copies are obtainable at all leading supply houses or directly from us.



MEISSNER MANUFACTURING Co.

Mt. Carmel, Ill.

JACKSON

TEST EQUIPMENT

for
1937

NEW 1937 MODELS NOW ON DISPLAY—See Your Jobber

Complete Service Lab. - Tube Testers - OSCILLATORS, D.C. & A.C. - ANALYZERS - Frequency Modulated Oscillators - Oscillographs - Multi-meters.

JACKSON

ELECTRICAL INSTRUMENT CO.

DAYTON, OHIO

**YOUR
JOBBER
SELLS**

AMPERITE
VELOCITY MICROPHONES

*Watch for
Sensational
Announcement!*

INDEX TO ADVERTISERS

A	I	S
Aerovox Corp. 587-591	Insuline Corp. of America 597	Solar Mfg. Corp. ... 569 & Third Cover
Allied Radio Corp. 583		Sound Systems, Inc. 595
American Television & Radio Co. 587	J	Sprague Products Co. 538
Amperite Co. 596	Jackson Elec. Inst. Co. 596	Standard Transformer Corp. 581
Amplifier Co. of America 597	K	Supreme Instruments Corp. 564-565
Arcturus Radio Tube Co. 585	Ken-Rad Tube & Lamp Corp., Inc. 597	T
Audak Co. 537	Mc	Technical Appliance Corp. 587
B	McMurdo Silver Corp. 585	Thordarson Elec. Mfg. Co. 591
Bell Sound Systems, Inc. 591	M	Tobe Deutschmann Corp. 533
Bendix Products Corp. 577	Mallory & Co., Inc., P. R. 545	Transformer Corp. of America ... 593
Birnback Radio Co. 595	Meissner Mfg. Co. 596	Triad Mfg. Co., Inc. 593
Brush Development Co., The. 589	Muter Co., The. 595	Triplett Elec. Inst. Co. 532
Burstein-Applebee Co. 597	N	Triumph Mfg. Co. 581
C	National Carbon Co., Inc. 535	Tung-Sol Lamp Works, Inc. 575
Centralab 575	National Union Radio Corp. 579	U
Clavostat Mfg. Co., Inc. 585	O	United Transformer Corp. 571
Continental Carbon, Inc. 593	Ohmite Mfg. Co. 598	Universal Microphone Co., Ltd. 597
Cornell-Dubilier Corp. 598	Operadio Mfg. Co. 591	Utah Radio Products Co. 579
Cornish Wire Co., Inc. 563	P	W
Curtis Condenser Corp. 597	Powertone Electric Co. 595	Ward Leonard Elec. Co. 589
E	Precision Apparatus Corp. 531	Ward Products Corp. 595
Electrad, Inc. 540	R	Webster-Chicago 577
Electro-Voice Mfg. Co., Inc., The. 595	RCA Mfg. Co., Inc. Fourth Cover	Weston Elec. Inst. Corp. 546
F	Racon Elec. Co. 597	Wholesale Radio Service Co., Inc. 573
Fox Sound Equip. Corp. 595	Radiart Corp., The. 598	Wright-DeCoster, Inc. 589
G	Radio & Tech. Publ. Co. 598	Y
General Electric Co. 529		Yaxley Manufacturing Division
General Transformer Corp. 589		Second Cover, 545
H		
Halldorson Co., The. 587		
Hickok Elec. Inst. Co. 597		
Hygrade Sylvania Corp. 583		

★ ALWAYS CARRY
Ken-Rad
Radio Tubes

Ken-Rad genuine all-metal radio tubes are dependable. They give outstanding performance. Write for information.

KEN-RAD TUBE & LAMP CORP., INC.
 Owensboro, Ky.

Also manufacturers of Ken-Rad Incandescent Electric Lamps

ICA "DE LUXE" NEUTRALIZING and ALIGNING TOOL KIT



Price **\$4.50**

INSULINE CORP. OF AMERICA
 25 PARK PLACE NEW YORK, N. Y.

COMPLETE FOR EVERY SERVICE NEED
 The ICA "Deluxe" Neutralizing and Aligning Kit is the answer to a Serviceman's prayer. It is compact, can be carried in the pocket or attached to the belt. It contains all of the "called for" Radio tools, including the ICA Magic Tuning Alignment Tool and the recently developed ICA flexible screwdriver. Cat. No. 994. Complete with rugged carrying case and fourteen tools.

AT YOUR JOBBERS
 Write for free 1937 Catalog describing complete ICA line of interest to every Serviceman.

LOW WHOLESALE PRICES GET THIS FREE CATALOG!



• Over 10,000 items in this big catalog including radio receivers, nationally known radio parts and broadcasting equipment. A catalog of great value to dealers and service men offering the best in radio at low wholesale prices. Write today for your FREE copy of this big catalog. Get on the list to receive monthly "Hot Shot" Bulletins.

BURSTEIN-APPLEBEE CO.

1012-14 McGee St. Kansas City, Mo.

RACON
 6 FOOT
UNBREAKABLE TRUMPETS



"The World's Finest"

Demountable into three sections. Made of RACON Acoustic Storm Proof material, reinforced throughout, and guaranteed unbreakable. The ultimate in trumpet design, highly efficient and able to stand the roughest treatment.

Send for RACON catalog S-11 describing the complete line of RACON Horns, Electro-dynamic Units, and Acoustical Sound Projectors.

RACON ELECTRIC COMPANY, INC.
 52 EAST 19TH STREET NEW YORK CITY



FREE!

The World's Finest Catalog of **AMPLIFIERS** and **P. A. Sound Systems** . . .

Write for Catalog No. 3709 and complete details of the latest anti-howl, automatic audio volume control, volume expander, and floating audio beam power amplifiers. No P.A. Technician can afford to be without it.

Dealers, Jobbers, and Distributors write for *Attractive Proposition*.

Public Address Division

AMPLIFIER CO. of AMERICA
 39 West 20th Street New York, N. Y.
 Territory still open for active manufacturer's representatives.

Curtis
 Electrolytic
CONDENSERS
 BUILT TO A STANDARD NOT TO A PRICE



Patent No. 1950352

HAVE YOU SEEN OUR NEW CATALOG?

CURTIS CONDENSER CORPORATION

3088 WEST 106TH ST CLEVELAND, OHIO

Hickok Model 4955 Volt-Ohm-Milliammeter with NEW LOW OHM READING



For general circuit testing—AC and DC. Scale ranges are as follows:

- A.C. Volts 0-10, 0-50, 0-250, 0-500, 0-1000.
- D.C. Volts 0-10, 0-50, 0-250, 0-500, 0-1000.
- Ohms, .05-30, .5-10,000, 50 ohms to 1 megohm, 500 ohms to 10 megohms.
- D.C. Milliampers, 01, 0-10, 0-50, 0-250.
- Resistor built in to read 10 megohms with external battery.
- A.C. Voltmeter usable as Output Meter.

Send for complete catalog of Hickok Radio Testing Instruments

THE HICKOK ELECTRICAL INSTRUMENT CO.
 10514 Dupont Ave., Cleveland, Ohio



Record Piano Music
 at 33 1/2 R.P.M. with
UNIVERSAL Professional Recording Machine

New, improved design—Scientifically correct—Superlative performance—Solid, heavy, dependable—Precision machined for long and continued use—16-in. distortion proof turntable disc—Constant speed rim drive—110 volt A.C. 100% synchronous reversible motor—Individually calibrated timing bar provides for both 33 1/2 and 78 R.P.M. at 90, 110, and 130 lines per in.—Solid steel bar slide—The climax of four years of research and experiment—Positively the last word in instantaneous recording equipment.

Write for latest folder giving detailed description.


UNIVERSAL MICROPHONE CO., Ltd.
 424 Warren Lane, Inglewood, Calif., U. S. A.

GUTSELLING them all...

THE
NATION-WIDE
ACCEPTANCE



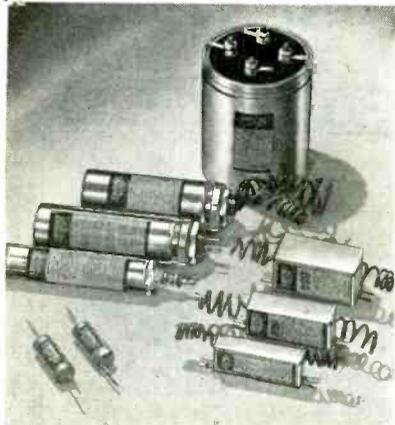by SERVICEMEN of Types DT, "DWARF-TIGER" Paper Tubulars, Types JR, etched foil dwarf-midget electrolytics, Types PE-B Paper Replacements, and Types I-W micas, is outstanding proof of the superiority of the complete C-D condenser line.



The successful serviceman standardizes on C-D for all service requirements.

Available at all leading C-D distributors. Complete descriptive catalog No. 128 on the entire line available free on request.

Wet and Dry Electrolytics . . . Paper . . . Mica . . . Dykanol

World's Largest Exclusive Manufacturer of Condensers

Cornell-Dubilier Corp.
1026 Hamilton Boulevard
South Plainfield, N. J.

CORNELL  DUBILIER



You need this...

HERE



GHIRARDI'S

New 2nd Revised Edition RADIO FIELD SERVICE DATA

Now in greatly-enlarged loose-leaf form, this handy time-saver is easily kept right up-to-the-minute with Supplements issued every Jan. and June. 436 pages jammed full of valuable dope for everyday use in the shop or on the job—l. F. peaks, Case Histories, Trouble-Shooting, Auto Radio data, Tube data, etc., etc., 81 Diagrams. 26 Charts and Tables. Free Circular on request. Money-back Guarantee.

\$2.50

with Jan. & June '37 Supplements

Combination Offer — THIS BOOK together with Ghirardi's 1300-page MODERN RADIO SERVICING \$6



Radio & Tech. Pub. Co., 45 Astor Pl., N.Y.C., Dept. S-116
Encl. find \$2.50 for Field Data book with Jan. and June '37 Supplements, pp. (Foreign \$3.)
 Encl. find \$6 for both books, incl. Supplements, pp. (Foreign \$6.50.)
Name..... Address.....



BROWN DEVILS ARE "ONE CALL" RESISTORS

says BILL FIXIT

"There's little profit and less glory in reseriving a job because the resistor you replaced has gone out again. That's why I stick to BROWN DEVILS. They protect my profit—and my reputation."

Brown Devils, wire wound on porcelain cores, are protected against electrical and mechanical damage by famous OHMITE Vitreous Enamel coating. Tinned lead wires make for easy installation. 10 and 20 watt sizes; resistance values through 100,000 ohms. Ask your jobber or get Catalog 14—Free!




OHMITE
MANUFACTURING CO.
4827 FLOURNOY ST.
CHICAGO, ILL.

MAKERS OF RESISTORS OF ALL TYPES



Mr. C. A. Nutting of Detroit
says:

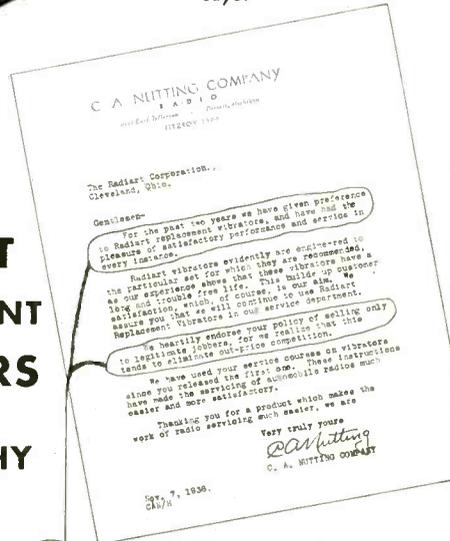
INSIST
UPON
**RADIART
REPLACEMENT
VIBRATORS**
HERE'S WHY



For the past two years we have given preference to Radiart replacement vibrators, and have had the pleasure of satisfactory performance and service in every instance.

We heartily endorse your policy of selling only to legitimate jobbers, for we realize that this tends to eliminate cut-price competition.

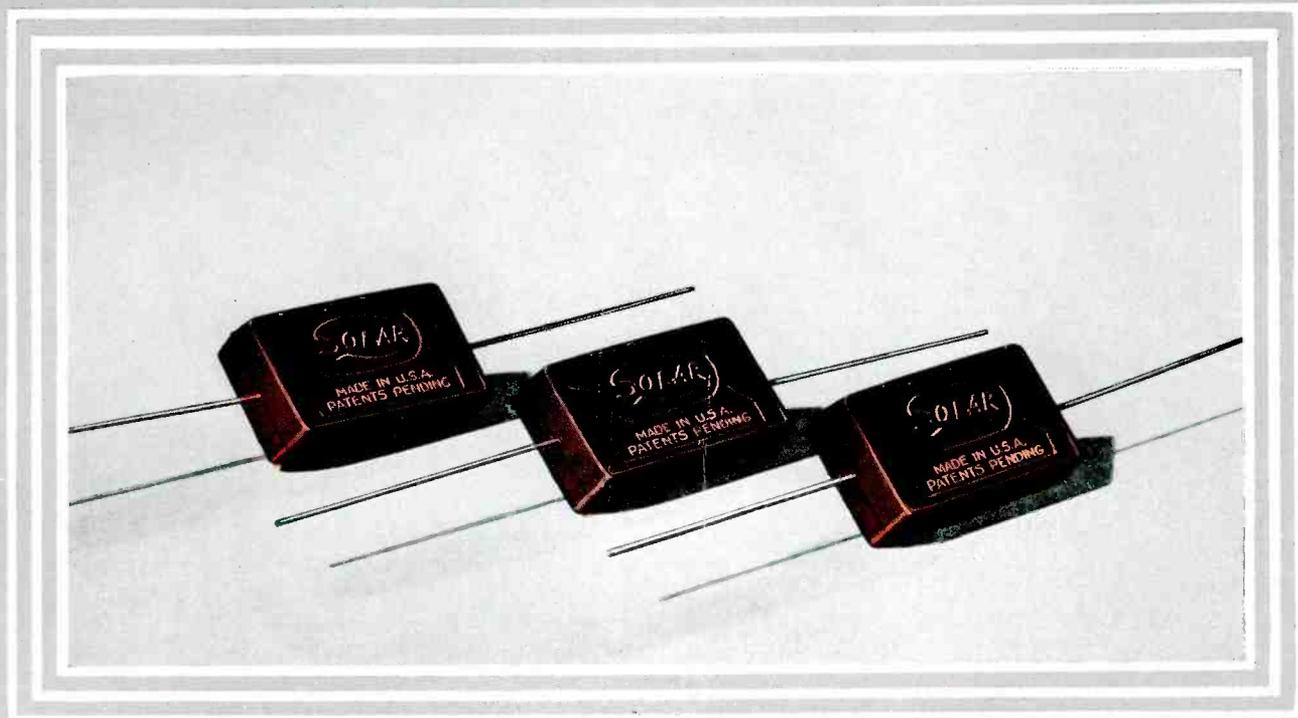THE RADIART CORPORATION
Shaw Ave. at East 133rd St. Cleveland, Ohio




QUALITY ABOVE ALL

Solar
DOMINO
molded BAKELITE paper capacitors

SOLAR MANUFACTURING CORP., 599-601 BROADWAY, NEW YORK

5 IN 1

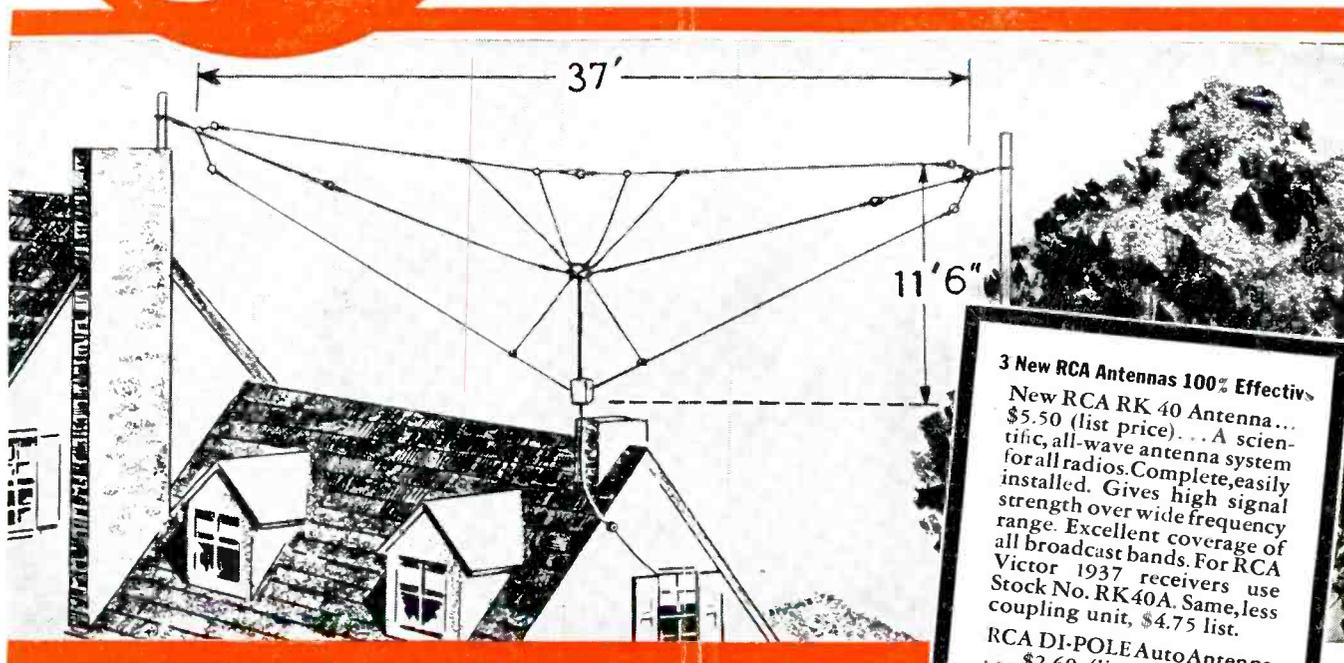**RCA'S OWN QUINTUPLET
SENSATION THE
SPIDERWEB
ANTENNA**



THE RCA Spiderweb Antenna is really five antennas in one. Operates as a T from 140 to 4000 kc., multiple doublet system above to 23,000 kc. With individual antennas for all important short-wave bands, it gives more signals, less noise and better reception on all wave bands. Stock No. 9689 high frequency kit extends coverage to 70 megacycles. This clears up 5-meter complaints that ordinary antennas will not reach.

The RCA Spiderweb Antenna is sensationally effective and remark-

ably easy to install. Requires span of only 38 feet and clearance of only 12 feet. The kit is completely assembled and soldered at the factory.

Without sacrificing efficiency, greater freedom from noise may be obtained by selecting the most ideal location for the antenna. The special transmission line, a unique feature of the RCA Spiderweb Antenna, permits the antenna proper to be erected at a considerable distance from the receiver. Stock No. 9685 system, \$8.95; Stock No. 9689 high frequency kit, \$1.50 (list prices).

3 New RCA Antennas 100% Effective

New RCA RK 40 Antenna... \$5.50 (list price)... A scientific, all-wave antenna system for all radios. Complete, easily installed. Gives high signal strength over wide frequency range. Excellent coverage of all broadcast bands. For RCA Victor 1937 receivers use Stock No. RK40A. Same, less coupling unit, \$4.75 list.

RCA DI-POLE Auto Antenna ... \$2.60 (list price). Latest development especially effective on new steel top cars. Efficient station pickup. No ignition-noise pickup. Quick — simple installation.

RCA INLANTENNA—Uni-versal type... All cars except Oldsmobile. Stock No. 12322. \$5.50 (list price).

Oldsmobile Type... Oldsmobile cars only. Stock No. 12328. \$6.00 (list price).

Ideal double running board type auto antenna, especially desirable for metal top cars at locations where broadcast signals are generally weak. Complete with all fittings in both types. Easily installed.



Parts for **PROFIT**

RCA Manufacturing Co., Inc., Camden, N. J. • A service of the Radio Corporation of America