


NATIONAL TRADE SHOW ISSUE

SERVICE

A Monthly Digest of

RADIO

and Allied Maintenance

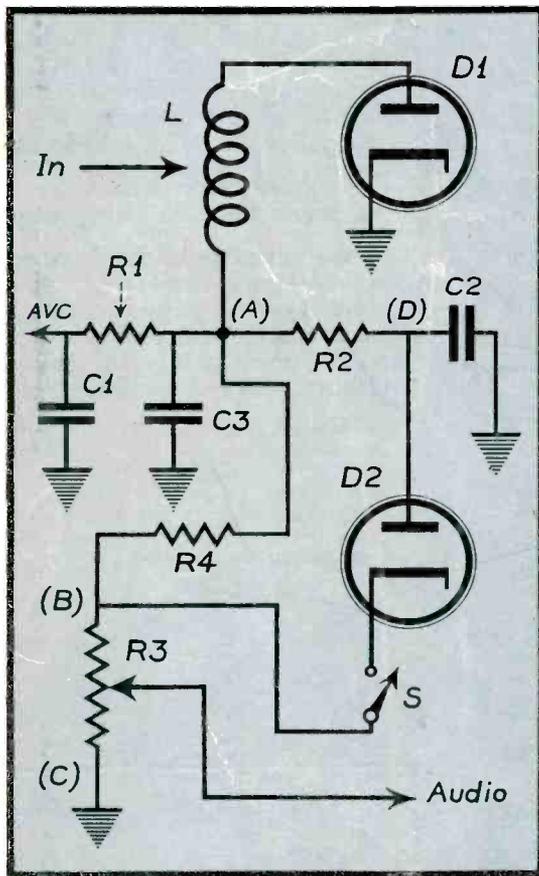

Noise Control


(See page 338)

PER COPY
25 CENTS

JUNE
1937

YES...

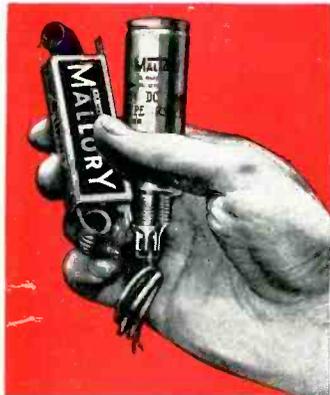MALLORY-YAXLEY has done more... but MALLORY-YAXLEY does not charge more!



MALLORY
CONDENSERS
cost
no more!



YAXLEY
VOLUME
CONTROLS
cost
no more!



MALLORY
VIBRATORS
cost
no more!

MALLORY-YAXLEY Precision Radio REPLACEMENT PARTS COST NO MORE THAN ORDINARY PRODUCTS

Every once in a while there's an idea that because Mallory-Yaxley products have a reputation for higher quality that they must be higher in price. A service man feels that he ought to use them but he thinks that maybe he can't afford to use them.

Mallory-Yaxley are *big*, he reasons, they'd have to be big to put out a help like the Mallory-Yaxley Radio Service Encyclopedia. They'd have to be big to have given the industry its first real honest-to-goodness Vibrator, Volume Control, and Condenser Service and Replacement Manuals. And the very size of Mallory-Yaxley—the wide scope and the great help of Mallory-Yaxley activities gives him a bad case of "price fright".

He thinks the products of the little fellow may be cheaper . . . and of course he finds plenty of people who'll encourage this belief.

Then some day he checks prices and makes comparisons. He finds that Mallory-Yaxley products *do not* "cost too much"—he finds that Mallory-Yaxley Precision Radio Replacement Parts *do not cost any more than ordinary replacement parts*. He finds they create the kind of customer satisfaction that helps his reputation and his bank account. He puts his radio servicing on easier and a more profitable basis.

It may be that *you* believe that because Mallory-Yaxley have done more for the service man that they expect to *charge more from* the service man. We say that isn't true and don't want you to take our word for it—or any man's word for it. You can compare prices and see for yourself! And—the more Mallory-Yaxley installations you make, the more you'll realize that the complete satisfaction assured by these precision replacement parts makes them *actually cost less in the long run*.



THE RIGHT "DOPE" On
Over 12,000 Different Radios

. . . Completely analyzed under *one cover* . . . in the MALLORY-YAXLEY RADIO SERVICE ENCYCLOPEDIA. The book that gives the correct answers to all questions—always! Ask the Mallory-Yaxley distributor about *your copy* now!

Use
P. R. MALLORY & CO., Inc.
MALLORY
REPLACEMENT
CONDENSERS, . . . VIBRATORS

P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
CABLE ADDRESS—PEI.MALLO

Use
YAXLEY
REPLACEMENT
VOLUME CONTROLS

If it's a
STANCOR
it's Good


It's not only a good product . . . carefully designed, conservatively rated and honestly built . . . but its sale is governed by a firm policy that gives everyone a break.

Stancor's insistence that no Stancor product be over-rated — either in performance or price — is your best guarantee of value . . . whether you buy Stancor Products for personal use, re-manufacture or re-sale. Stancor Products are good . . . and it's "good business" to buy them.


**S T A N D A R D
 T R A N S F O R M E R
 C O R P O R A T I O N**

850 Blackhawk Street


Chicago

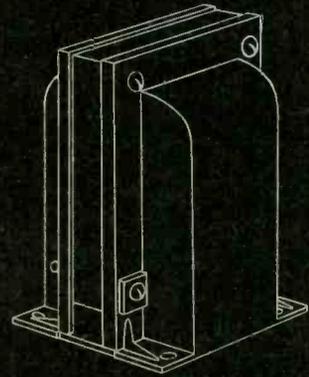


EXACT DUPLICATE TRANSFORMERS

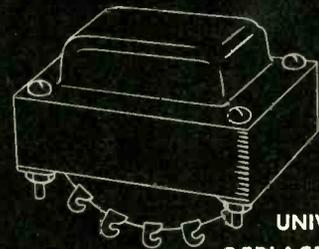


UNIVERSAL
 REPLACEMENT
 TRANSFORMERS

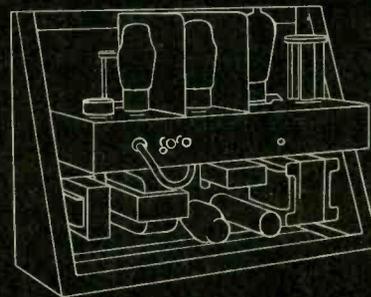

AMATEUR
 RADIO KITS

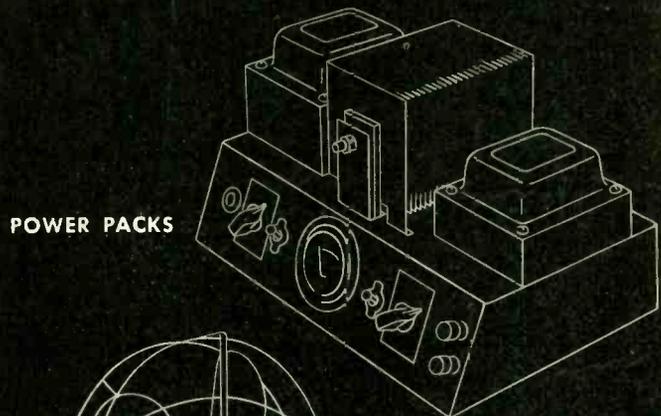

POWER PACKS

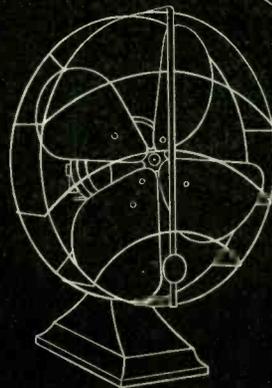

FANS

SERVICE

A Monthly Digest of Radio and Allied Maintenance
Reg. U. S. Patent Office. Member, Audit Bureau of Circulations

JUNE, 1937

EDITOR
Robert G. Herzog

VOL. 6, NO. 6

EDITORIAL CONTENTS

FEATURES

DuMont 164 Service Oscillograph.....	374
Graphs By Joseph Schoenbaum.....	333
Noise Control By J. E. Dickert.....	338
P-A Service Problems By Aaron Nadell.....	384
Practical Notes on Matching Transformers By Emil Buchwald.....	336
Technical Features of 1937 Auto-Radio Receivers.....	379
Zero-Current Voltmeter By Bradley Thompson.....	370

ANTENNA.....	330
--------------	-----

ASSOCIATION NEWS.....	388
-----------------------	-----

AUTO RADIO

Ford-Philco F-1440.....	378
Motorola Auto Radios (Service Note)..	376
Technical Features of 1937 Auto-Radio Receivers.....	379
Zenith 5803 (8-M-195).....	380

BOOK REVIEW.....	391
------------------	-----

CIRCUITS

Belmont 878.....	342
DuMont 164 Service Oscillograph.....	376
Emerson G-127.....	346
Ford-Philco F-1440.....	378
Fundamental Circuit of Zero-Current Voltmeter.....	370
Hickok 4900 Set Tester.....	374
"Magic Brain" Wiring Diagram.....	352

Noise Control.....	Front Cover
Noise Suppression Circuit.....	339
RCA 9T, 9K2, 9U, 9U2.....	348
RCA 9T, 9K2, 9U, 9U2 Assembly Wiring	364
RCA 9T, 9K2, 9U, 9U2 Loudspeaker Wiring.....	362
Switching Arrangement for Zero-Current Voltmeter.....	372
Typical AVC Circuit with 6H6 Rectifier..	370
Zenith 5803 (8-M-195).....	380
Zero-Current Voltmeter.....	372

GENERAL DATA

Belmont 420, 430 (Service Note).....	382
Belmont 878.....	342
Emerson G-127.....	344
Noise Control By J. E. Dickert.....	338
RCA 9T, 9K2, 9U, 9U2.....	348

HIGHLIGHTS.....	390-391
-----------------	---------

MANUFACTURERS.....	392-393-394-395
--------------------	-----------------

ON THE JOB.....	356
-----------------	-----

PUBLIC ADDRESS

P-A Service Problems By Aaron Nadell.....	384
Practical Notes on Matching Transformers By Emil Buchwald.....	336

TEST EQUIPMENT

DuMont 164 Service Oscillograph.....	374
Zero-Current Voltmeter By Bradley Thompson.....	370

Copyright 1937—Bryan Davis Publishing Co., Inc.

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Chicago Office—608 S. Dearborn St.—C. O. Stimpson, Mgr.
Telephone: Wabash 1903

Wellington, New Zealand—Tearo Book Depot.

Published Monthly by the

Bryan Davis Publishing Co., Inc.

19 East 47th Street

New York City

Telephone: Plaza 3-0483

SANFORD R. COWAN
Advertising Manager

PAUL S. WEIL
Eastern Advertising
Manager

A. B. CARLSEN
Circulation Manager


Cleveland Office—10515 Wilbur Ave.—J. C. Munn, Mgr.
Telephone: Republic 0605-J

Melbourne, Australia—McGill's Agency.




Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

The **LONGEST** path is the **SHORTEST**

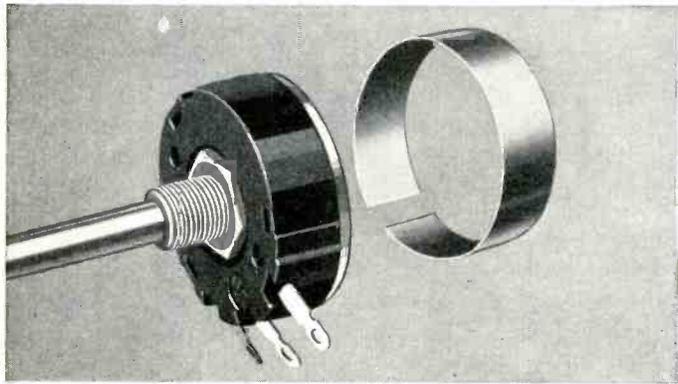

STANDARD RADIOHM

Servicemen
prefer
**Centralab
Controls**

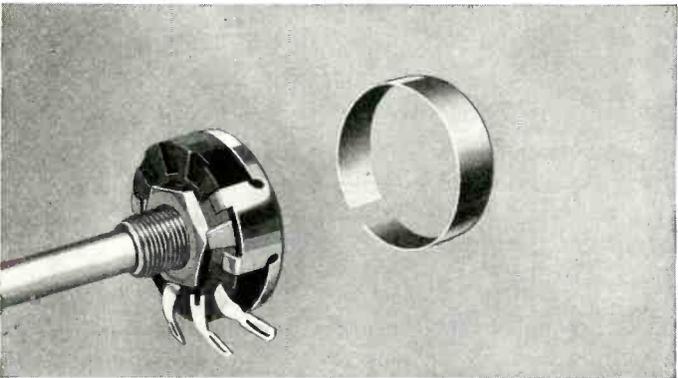

MIDGET RADIOHM

in
Centralab
Variable
Resistors

● Yes . . . the shortest path to good control is a Centralab Variable Resistor . . . for the "wall type" resistor illustrated with each control hugs the inner circumference of the case.

1. Maximum resistor length for case diameter.
2. Close uniformity between resistors.
3. Accurate tapers.
4. Uniform current distribution.
5. Lower specific resistance and attendant low noise level.
6. Better power dissipation.
7. Longer life.

**Get Your 1937
Volume Control
Guide**

By all means get your copy—more listings—more pages—including '36 and early '37 receivers.

Centralab

Division of Globe Union, Inc.
Milwaukee, Wis.

BRITISH CENTRALAB, LTD.
Canterbury Rd., Kilburn, London N.W.6, England

FRENCH CENTRALAB CO.
118 Avenue Ledru-Rollin, Paris XI, France

THE ANTENNA . . .

NATIONAL PARTS SHOW

AS THIS ISSUE COMES OFF the press the National Parts Show opens at the Stevens Hotel in Chicago. The Show and attending conventions are scheduled for four days, June 10 to 13 inclusive. Sales managers, distributors and engineers representing every parts manufacturer will be there personally to meet the Service Man, discuss his many problems and make possible suggestions for better cooperation in the future.

These shows present quite a problem to those who stage them; the cost to the manufacturers is enormous . . . yet it is all for your benefit, to help you do a better job and make more money from it.

Your part in this affair is your attendance at the show and technical sessions . . . bring your ears and your problems . . . see what's new . . . much can be learned to help increase your profits.

. . .

HANDY-MEN AND TINKERERS

NO MATTER HOW REMOTE OUR connection with radio, we all continually find ourselves taunted with:

"My wife's cousin has a Blank radio, I think it has six tubes . . . well, it makes funny little noises. Do you think if I changed the power transformer . . ."
or maybe

"I've got a radio, it's eight years old and it plays swell, better than any of these new pieces of junk . . . but the other day . . ."

You should have a series of tactful answers, when these are directed at you, some humorous, or technical or serious as the case might warrant. In any event the reply should be such as to completely discourage the owner from tinkering with the receiver.

There isn't one of you who has not encountered receivers in which parts were interchanged or "mended" by owners without regard to circuit constants. Certainly you have all met with the chassis in which the trimmer condensers were "adjusted" until their screwheads were worn ragged.

This tinkering with expensive receivers when trouble develops may be partly a hangover from the earlier days in radio when many otherwise respectable citizens were

radio bugs, built their own sets and discussed wavelengths, vacuum tubes, regeneration, etc., with the same enthusiasm now reserved for the pitching abilities of Carl Hubbell or Dizzy Dean.

The reluctance of many people to call in their Service Man may also be partly a result of the "fix anything" handy-man type of owner whose ability to take anything apart, whether it be a dollar alarm clock, a hundred dollar radio or a thousand dollar automobile, is considered ample to cope with any receiver trouble without the need of such gadgets as tube testers, vacuum tube voltmeters or cathode-ray oscillographs.

In a good many cases, however, this reluctance is due to a sad lack of confidence in the local Service Man, or more correctly, in Service Men in general, and a fear that he will overcharge. . . . The practice of unscrupulous dabblers styling themselves "Service Men" has undoubtedly done much to strengthen this attitude.

But a new day is due! The competent and thoroughly conscientious honest service rendered by the vast majority of Service Men should be brought to the attention of the public. Many Service Men's associations are considering this as one of their prime functions. Advertisements in daily newspapers, phone books, shop windows, etc., are carrying the banners of a competent and honest service industry. The National Trade Show in Chicago and the attendant publicity should also go far toward convincing the public of the competence of the service industry.


. . .

INTERCOMMUNICATING SYSTEMS

FOR SEVERAL MONTHS WE have been stressing the fact that the sale of intercommunicating systems is a natural for the Service Man. Reports from wide awake Service Men who have already taken our advice show ever increasing sales.

In every locality there are undoubtedly innumerable factories, offices and homes that can be sold some type of system. If making a living from the sale of radio devices and service is your job, you owe it to yourself to go out after this business. With a good line you will find, as others have, that the sale of these systems will make your business show *real* profits.

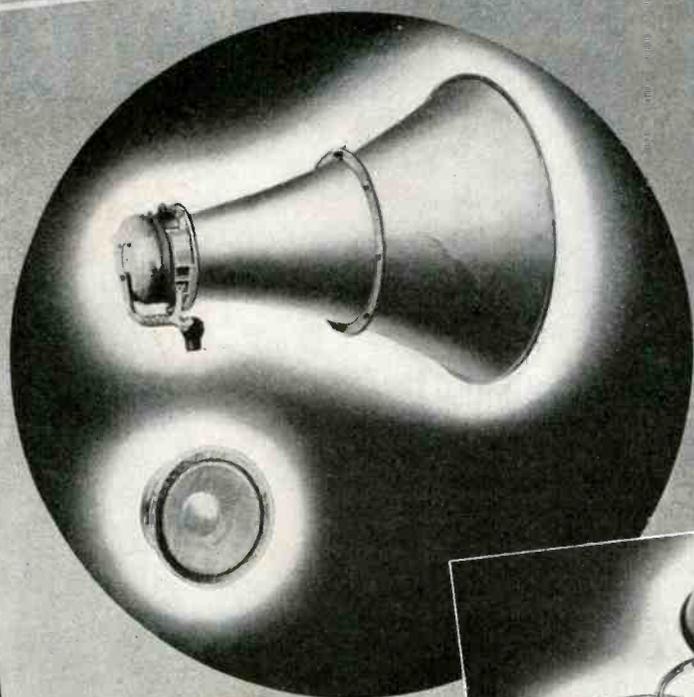RECOGNITION—the REWARD FOR ACCOMPLISHMENT



MODEL SUA—A powerful exponential unit with 3½" voice coil—the ultimate in air column sound projectors.

CINAUDAGRAPH CORPORATION, with its extensive background of engineering experience and modern manufacturing facilities, has justifiably earned leadership recognition from the entire radio industry. This is because its line of speakers is outstanding in performance, quality of materials and workmanship. CINAUDAGRAPH Speakers are styled and built to meet today's requirements — they are sold on a competitive price basis.



COUPLING RING UNIT ASSEMBLY Assures Permanent Voice Coil Alignment and Simplifies Cone Replacement.



Send for Literature

CINAUDAGRAPH will continue to set the pace in Speaker design, improvement and efficiency. Send NOW for latest descriptive literature.

CINAUDAGRAPH CORPORATION

Speaker Division • Stamford, Conn.

A complete line of Magic Magnet Speakers ranging in size from 5 to 18 in.

FINEST IN QUALITY ... yet COMPETITIVE in price ...

The
AMPERITE

VELOCITY



PREFERRED by leading P.A. Men the world over!

FEATURES
Compact, streamline, modern, the Amperite Velocity now features ...

1. Output increased 6 DB.
2. Triple Shielded—against all RF or magnetic fields, entirely eliminating hum pickup.
3. Eliminates feedback troubles.
4. Excellent for close talking and distant pickup.
5. Acoustically designed to eliminate any possibility of cavity resonance.

The remarkable success of the Amperite Velocity is the result of Amperite's P.A. Policy—to give P.A. Men the finest possible microphones at prices no higher than what they would pay for other mikes. A letter from Ridley's P.A. Systems is typical of the general response of the P.A. industry. It says: "Your Velocity is the finest type of microphone I have ever used. . . . Please duplicate my order."

You, too, will duplicate orders . . . improve installations . . . and enjoy better quality at a competitive price by using Amperite Velocity Microphones. There's a model for every type of installation.

CONSULT YOUR JOBBER NOW!

LEADING MODELS

MODELS RBHn (High Impedance); RBMn (200 ohms); with Cable Connector and Switch. \$42.00 LIST

MODELS RBSn, RSHn, streamline design, slightly lower output than above, with switch only. \$32.00 LIST

With Cable Connector . . . \$34.00 LIST

FINISHES: All microphones have the new standard gunmetal finish. Chrome or Egg Shell. . . . Extra \$1.00 LIST

Other pastel shades . . . Extra \$2.00 LIST

NEW! Desk Stand



New and novel. Ideal for desk, pulpit, footlights, banquets. Microphone can be rotated in the horizontal plane, and used in various positions, as desired. LEAF SPRING SUSPENSION ACTS AS AN EXTRA SHOCK ABSORBER. Unusually stable. STAND ONLY. \$4.00 LIST. Name plate with maximum of 10 letters, \$2.00 LIST.

NEW! "Ham Mike"



No peaks! No splashing! Real broadcast quality. Output, -68 db. RF Choke Circuit included in microphone. Operates directly into grid of tube. Rugged. Not affected by temperature or pressure changes. MODEL HAM (high impedance); MODEL HAL (200 ohms) . . . \$22.00 LIST

Price includes new special Ham Desk Stand, call letters, and 6 feet of cable.

AMPERITE JUNIOR



A "lapel" Velocity of surpassing quality. Size of a match box. Ideal for lectures and specialty acts. Can be hidden under coat. Output constant with any position of the head. Transformer included in microphone case. MODEL 7J (200 ohms), or MODEL 7J-H (2000 ohms) \$30.00 LIST

FREE

WINDOW DECAL advertising your Sound Service. Size 5 1/4 x 9 1/4, finished in 4 striking colors. WINDOW DISPLAY, 11 x 17, and . . . New illustrated bulletins. Write for these valuable sales helps today.

A POPULAR AMPERITE VELOCITY \$22.00 LIST

A Velocity Microphone of very high excellence. Built to Amperite standards. Used for both speech and music with great success. No peaks. Flat response over audible range. Output, -68 db; Triple shielded. Fitted with shock absorber and swivel bracket. Model RAL (200 ohms) with 8 ft. of cable; Model RAH (2000 ohms) high impedance, with 12 ft. of cable.



AMPERITE © 561 BROADWAY, N. Y. U.S.A.

Cable Address: Alkem, New York

VELOCITY AMPERITE MICROPHONES

SERVICE

A Monthly Digest of Radio and Allied Maintenance

FOR JUNE, 1937

GRAPHS

By JOSEPH SCHOENBAUM

GRAPHIC: Syn. vivid.—suggests telling, vivid, salient, forcible. (*Webster's Collegiate Dictionary*.)

GRAPHS are to numbers what the tabloids are to the everyday news of the world. They present in condensed comprehensive form complete pictures that in other modes of expression require thousands of words or complex formulae. One might spend fifteen minutes reading a report of the types of uniforms worn in a parade, while one graphic photo will show all at once, and in detail that a written report would not attempt to cover. Similarly a graph is a picture, not only of a mathematical equation or series of equations, but a picture of these equations in action.

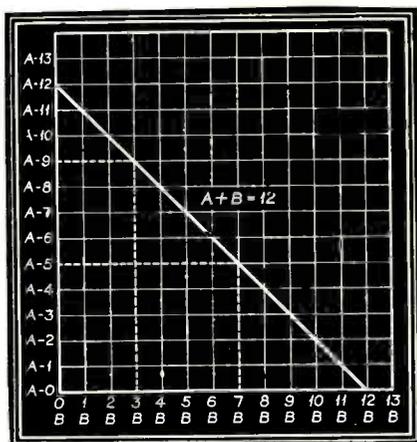


Fig. 1. Graph of the sum of any two numbers equal to 12.

THE ARTICLE presented below is quite elementary and is written largely as an introduction to this subject for the Service Man who is wholly unfamiliar with graphs. It should, however, prove of interest to practically every Service Man.

Graphs are used profusely throughout all radio literature. If any iota of value can be gleaned from reading an article on this all-important subject, the time may be considered well spent.

In another sense a graph is like a map of a city. It might be quite difficult to explain to a stranger just how to get to a distant point, but give him a map and show him just where he stands on the map, and he will have little difficulty in finding his way. In like fashion, one can easily read a graph while the complex formulas which go to make up the graph are often beyond the abilities of even advanced students.

GRAPH PRESENTS ALL SOLUTIONS

A graph is the only mathematical instrument that presents all the solutions to a problem at once, in addition to solving the problem. Graphs, too, can give the answers to several related problems all at the same time. They are actually a method of solving arithmetic and algebraic problems, and require only an understanding of their simple basic principles to accomplish mathematical wonders.

HOW TO READ THEM

The reading of a graph is one of the quickest solutions to any problem. If we did not know how to perform addition we could still get a correct answer to a problem if a graph of the problem were at hand. Let us suppose that we had a graph as shown in Fig. 1 with horizontal lines representing A from $A = 0$ and $A = 1$ to $A = 12$, and vertical lines representing B from $B = 0$ to $B = 12$. The slanted dark line represents the equation

$$A + B = 12$$

which means the sum of any two numbers that equals 12. We want to know what B equals when A is equal to 5. But we do not know how to add so we

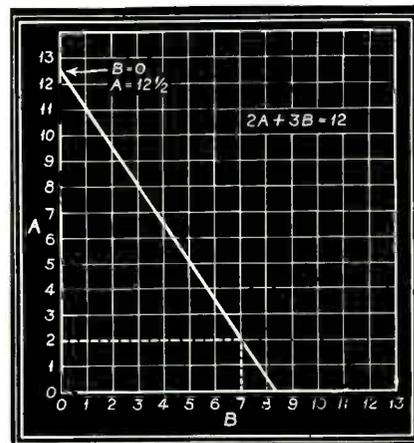


Fig. 2. The sum of two products.

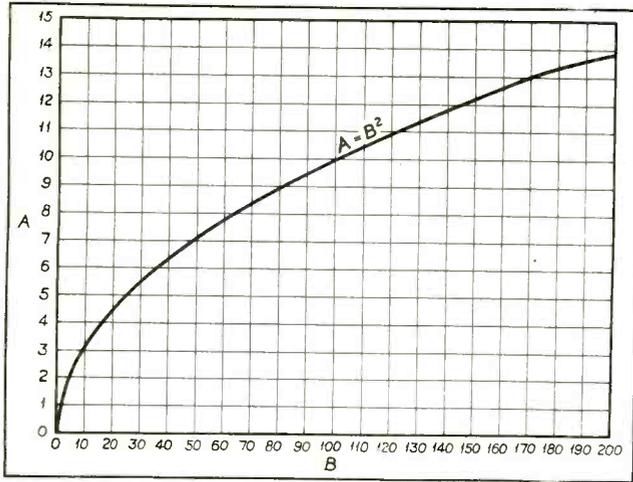


Fig. 3. Square and square-root graph.

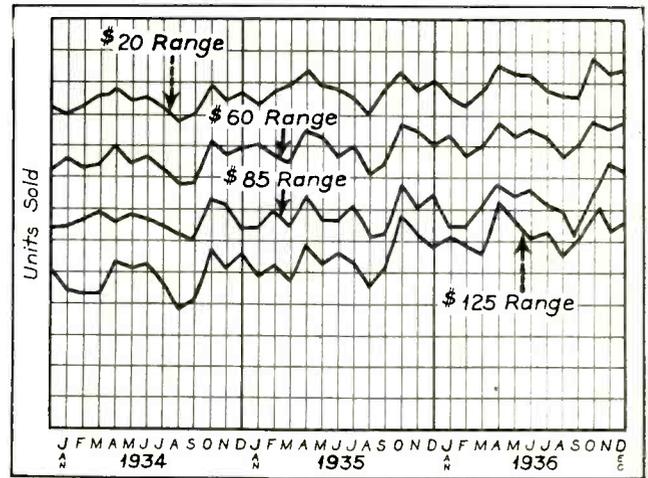


Fig. 4. Sales trend graph.

start at the point $A = 5$ and go to the right along the dotted line. When we reach the slant line we stop and change our direction downward. When we reach the end of this new line we find that we are on the line $B=7$, or B is equal to 7. Similarly if B is 3, to find A , we start at the line $B=3$, go up until stopped by the formula line, and find ourselves on the line $A=9$.

If we could add and subtract but had not yet learned to multiply, we would find ourselves stopped by the equation

$$2A + 3B = 25$$

Having at hand in Fig. 2 the graph for this equation we can find the value of B for any value of A or vice versa. The question is to find B when A is 2. Starting with 2 in the A group we go to the right until we reach the formula line, and then go down along the line at that point. Our answer, it is apparent, is that B is 7.

In the case where B is zero, we follow upward along the $B=0$ line, which is the A axis, until we reach the formula line. Since we are already on the A line, and need not go to the left, our answer is right there, or $A = 12\frac{1}{2}$.

To illustrate a problem easily solved in a finished graph, but quite difficult without the graph, we see in Fig. 3 the solution of the equation $A = B^2$, which in graph form gives to a fraction the squares and square roots of numbers, limited only by the size and form of the sheet of graph paper. The square of 13, for instance, if we follow the horizontal line numbered 13 from the left to the equation line and then down, is 169. In reverse, the square root of 158, if we go vertically along the 158 line until we reach the equation curve and then go left, is 12.6.

WHY THEY ARE USED

Frequently in the everyday world it becomes necessary to compile long lists

of statistical figures, as in the study of automobile accidents, stock market figures, birth rates, sales trends, etc. These figures by themselves give certain definite information which may have various uses. However, their value is quite limited unless they are

of such a graph which is produced by competent authorities will lead a manufacturer to balance his purchases, production and sales, and will show him where and in what manner he must put forth special effort to balance his annual schedule.

Almost any list of figures leads to a graph. If one were to try to examine the tabulations of one day's operations on the stock exchange, he would find it necessary to spend considerably more time making enough comparisons from which to draw conclusions of any value than results arrived at in such manner would be worth. A rapid transfer of these figures to a graph sheet would show a comprehensive picture of the day's operations as well as provide a quick means of comparison with previous days. Further, the trend of the market at every moment is indicated so that a relationship between cause—the economic occurrences of the time—and result—price fluctuations—may be observed for future use.

HOW TO MAKE THEM

There are several variations in the ruled forms used in making graphs, some more convenient than others depending upon the exact form of the graph desired. Some of these forms have widely spaced lines, ruled in squares, from four to eight to the inch. Frequently finer spacing is used, about ten lines to the inch both vertically and horizontally. This gives us 100 squares to the square inch. Usually in this ruling every fifth line is slightly heavier than the other lines, and every tenth line still darker, thus providing a more convenient form for the rapid construction and easy reading of the graph.

In Fig. 5 is shown a sheet of graph paper on which we are going to plot, as an illustration, the graph used earlier, of the formula

$$A + B = 12$$

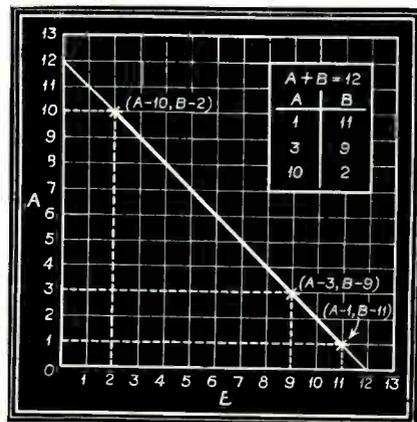


Fig. 5. Plotting the graph.

indicated graphically. The plain figures have no way of indicating change or rate of change, which are the most important factors in life. When pictured in the form of a graph these figures convey new meaning. They may be compared—the slopes of the graph indicate how rapidly and to what extent changes are occurring; they indicate any possible periodic variation and when new highs and lows may be expected in the future. Truly when once cold figures are assembled in graphic form, a complete picture unfolds. For instance, in Fig. 4 is a sales graph showing the result of a three-year survey of sales in four price ranges. At practically a single glance one can see a definite seasonal trend with its different variations for the different price groups, and just how the sales of the several models are related. Observation

MATCHING TRANSFORMERS

By EMIL BUCHWALD

MANY Service Men consider that a transformer's specifications adapt it only to a given type of service—that it is suitable for coupling a definite source to a fixed load. This, however, is not the case since, if the theoretical considerations governing the use of coupling transformers are known, wider application for each unit is readily apparent.

THEORETICAL CONSIDERATION

(1) The primary impedance of a transformer depends on the secondary load; (2) A transformer may be used for impedances other than those for which it is rated without appreciable loss provided the variation is not too far from the manufacturer's rating—the original impedance ratio will still apply; and (3) A transformer operating with a lower source impedance than normal will generally give a better frequency response¹. . . these are the considerations which govern coupling transformer application.

The primary impedance, secondary impedance and the turn ratio of the transformer are factors which are related to each other. To determine any one of these three factors in terms of the other two the following formulas may be used.

$$T = \sqrt{\frac{R_p}{R_s}}$$

$$R_p = R_s \times T^2$$

$$R_s = \frac{R_p}{T^2}$$

where T is the turn ratio, R_p is the primary impedance and R_s is the secondary impedance.

PRACTICAL EXAMPLES

A few examples will be given to show how this information can be put to practical use.

A speaker having a voice coil of 15 ohms impedance is to be connected to

a pair of 45 output tubes in push-pull, requiring a load resistance of 9,200 ohms. What ratio is necessary in the output transformer? The turn ratio of the transformer is the square root of the quotient of the primary impedance divided by the secondary impedance; hence,

Dividing

$$9,200 \div 15 = 613$$

Extracting the square root

$$\sqrt{613} = 24.8$$

The turn ratio necessary is 24.8; however, a ratio of 25 may be used.

DETERMINING TURN RATIO

It is necessary to find the impedance of a burned-out voice coil in the speaker used on a battery operated job which uses a single 33 pentode as the output tube. For economical reasons the output transformer will be retained and to make a low cost repair only the speaker will be replaced. Since the impedance of the voice coil can no longer be measured it is necessary to seek another method of obtaining the same result.

The turn ratio of the output transformer can be determined by applying 2 or 3 volts. a-c across the secondary terminals. The voltage appearing across the primary can be read with a high resistance a-c voltmeter. This may be a

vacuum-tube voltmeter or a copper-oxide rectifier type meter. Since the current in the transformer is low, the turn ratio is proportional to the voltages, viz:

$$T = \frac{E_p}{E_s}$$

where T is the turn ratio, E_s is the secondary voltage and E_p is the primary voltage. Suppose the secondary input voltage is 2 volts and the voltage across the primary measures 70 volts, it is found that the turn ratio is 35.

The recommended load resistance of a 33 pentode is 6,000 ohms, according to the handbook on tubes. With these two figures the secondary load may now be determined. Since this is equal to the primary load divided by the square of the turn ratio it is found that; multiplying,

$$35 \times 35 = 1225$$

dividing,

$$6,000 \div 1225 = 4.9 \text{ ohms approximately.}$$

Hence the impedance of the voice coil may be 5 ohms which is close enough for this type of work.

Data pertaining to the output transformer on a particular make of speaker is often found only on the speaker carton. It may happen that cartons become mixed and the Service Man or dealer is not sure as to just which speaker belongs to which carton.

Practically all of the speaker manufacturers have standardized on the voice coils of their various types of speakers, that is, all the speakers of one type have the same voice-coil impedance. The value of this impedance may be found in the manufacturers' catalogs.

Consider the case of a speaker whose carton was misplaced. The manufacturer's catalog gives the voice-coil impedance, at the reference frequency, as 10 ohms. The voice coil is temporarily disconnected from the output transformer and its turn ratio determined as described above. It is found that the turn ratio of the particular speaker is 26.5.

The third step is the primary impedance and since this is equal to the secondary load times the square of the

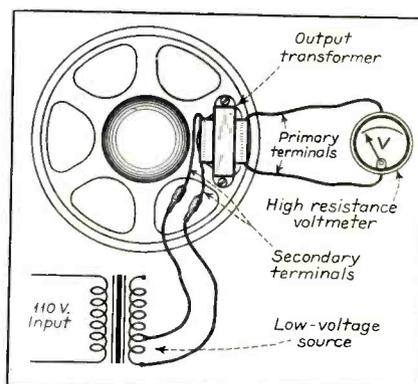


Fig. 1. Determining turns ratio of an output transformer.

¹Matching Transformers to Special Purposes, by I. A. Mitchell, SERVICE, May 1936, p. 222.

turn ratio, it is found that; multiplying

$$26.5 \times 26.5 = 702.25$$

$$10 \times 702.25 = 7022.5 \text{ ohms}$$

primary impedance. Hence this speaker and output transformer may be used with a 2A5, or a 47 or any tube having a recommended load impedance of 7,000 ohms.

VOLTAGE ANALOGY

The fact that a matching transformer may be used for other impedances than those for which it is rated may be explained by an analogy. When the deviation is in the direction of a higher source impedance connected to a transformer with a lower impedance rating, losses occur. The extent of the losses is dependent upon the amount of deviation. If the transformer is considered in terms of voltage rather than impedances, the picture then becomes somewhat clearer and the reason for losses becomes apparent. Suppose the power transformer as used in the typical radio set is taken as the basis for an analogy. These transformers are usually rated at 110 volts, 60 cycles alternating current. So long as this transformer is connected to a 110-volt source, all is well, but if it is connected to a 220-volt source, disaster is inevitable and manifests itself immediately in the form of a burned-out primary and possibly a blown fuse in the lighting circuit. The reason is that the impedance of the primary is not high enough to limit the current to a safe operating value at the higher source of voltage. This is equivalent to a coupling transformer rated for a 500-ohm line and connected to a 600-ohm source, the only difference, however, is a loss of low frequencies rather than a burned-out transformer, since the audio powers involved are generally of a small magnitude.

The power transformer, however, may be used at 220 volts with some measure of success if the frequency is doubled, that is, 120 cycles instead of 60. In this case the inductive reactance of the primary is doubled but the impedance falls somewhat short of twice


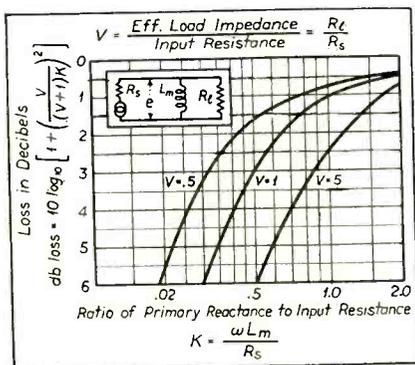


Fig. 2. Loss in low-frequency response caused by the primary inductance with the source and load impedances considered.

Fig. 4. Operation characteristics of a typical line-to-grid transformer with various source impedances.

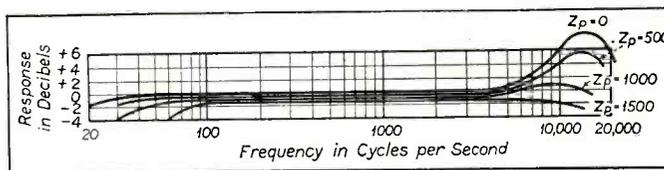

the value at 60 cycles due to the copper and core losses. Some additional loss occurs then at 120 cycles and 220 volts, but for analogous reasons it may be assumed that the transformer operates as well, when both the frequency and voltage is doubled, as it does at the original ratings. If the voltage is held constant at 220 volts and the frequency is reduced from 120 cycles more and more power is used in heating the primary than is transmitted to the secondary. This is equivalent to a partial short circuit. For the same reason attenuation of low frequencies occurs when a coupling transformer is used in

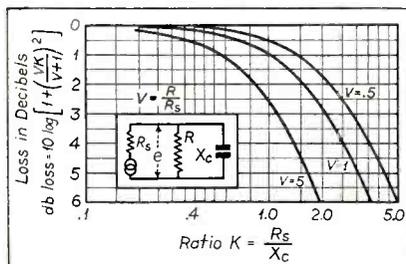


Fig. 3. Loss in low-frequency response caused by the distributed capacitance with the source and load impedances considered.

a circuit which has a higher source impedance than that for which it is rated.

OTHER LOSSES

In addition to the low frequency loss, losses also occur at the higher frequencies. These, however, are caused by different conditions. The capacity between adjacent turns of wire on both the primary and secondary account for the distributed capacity, which has the same loss effects as a condenser would have connected across the secondary.

Leakage inductance is also a factor and is caused by some of the magnetic flux traveling through the air instead of the core. This acts the same as if an inductance were connected in series with the load. At low frequencies, the impedance of the leakage inductance is low and the impedance of the distributed capacity is high, so the losses from these two causes are not appreciable. At high frequencies, the converse holds true and for a definite voltage and frequency a certain loss takes place; say 1 watt.

If the voltage is doubled, as in the case of the power transformer, it will be seen that the losses are augmented, so that a loss of 2 watts takes place at high frequencies. Figuratively, this explains to a certain extent the loss that

occurs at high frequencies when the source impedance is higher than the rating of the transformer. In a transformer especially designed for a higher voltage, or impedance, these losses are taken into consideration during the design and compensations made accordingly.

In low-power audio-frequency work, deviation from the rating is possible, since no damage will result as far as the transformer is concerned. The amount of deviation from the transformer rating may be considered as dependent upon the ear, that is, as far as the quality of the signal is concerned. For instance; an output transformer labeled 10,000 ohms primary and 10 ohms secondary of 12,000 ohms to a 12-ohm voice coil. This variation is within 20 per cent which is considered the maximum deviation consistent with fair quality.

Considering the power transformer again, it will be remembered that if the voltage source is increased beyond that of the transformer rating, a power loss takes place. On the other hand, if the applied voltage is reduced below the rating, little power loss takes place and the transformer works as well on, say 75 volts, as it does on 110 volts. Here the impedance of the primary is ample to take care of the lowered applied voltage and very little power is wasted in heating the primary. In fact, since the applied voltage has been reduced from that of the transformer rating, it is possible to work the transformer at a lower frequency, say 40 cycles, and still realize good efficiency.

For the same reasons it is possible to work the transformer at higher frequencies since the secondary voltage is proportionately less, the high frequency losses are proportionately less. From this it will be seen that the frequency range of the transformer may be increased both on the low end and the high end of the spectrum consistent with good results. A similar effect occurs when a coupling transformer of a definite rating is coupled to a lower source impedance, as for instance, a transformer labeled 500 ohms and connected to a 400-ohm source.

LOWER SOURCE IMPEDANCES

Coupling transformers may be used with lower source impedances as follows: a dynamic microphone of 250 ohms is to be connected to a transformer feeding

(Continued on page 340)

NOISE CONTROL†

(See Front Cover)

By J. E. DICKERT

THE defeat of noise, whether a natural physical phenomena or man-made, is the hidden bogey man constantly prodding the engineering brains to further accomplishments.

DISCRIMINATING CHARACTERISTIC

Any attempt at noise reduction in radio reception must start necessarily with a search for some discriminating characteristic of noise not found in the signal. Diversity reception is as old as radio and as new as this year's automobile receiver. It depends for its efficacy on the assumption that radio signals are unlike noise or static in directional qualities. Generally two antenna systems are used, each picking up the same amount of noise but different amounts of signal. If the energy from one antenna is combined out of phase with the other with such accuracy that the noise is balanced out there still exists an unbalance in signal which passes on to the receiver by an amount which will depend upon the unbalance. Certain other advantages accrue to make this method advantageous for fixed-station use, and the variety of its applications is enormous.

Another method, and quite similar to the diversity system, assumed that noise picked up ten or twenty kilocycles from the received carrier could be combined with noise present with the carrier in such a way as to balance out. The fallacy was that noise is not identical at different frequencies, but strangely enough a slightly different application of the theory has been used successfully on the ultra-high frequencies quite recently.

NOISELESS ANTENNAS

While common static is still with us as much as ever, the effects of it in many cases are submerged by the barrage of high-powered transmitters. Coincident, however, with the general increase in power is an even greater increase in man-made noises caused by home and commercial electrical appliances. The answer to this from the commercial radio and communications

angle is to locate the receiving system away from the noise area, but the answer from the man-on-the-street angle is to purchase "noiseless" antennas offered by many manufacturers. The latter depend upon the assumption that radio-frequency transmission lines can be so well balanced that when properly terminated they are immune to alternating fields or radiation and that they will conduct, without serious attenuation, radio-frequency energy from an antenna located far enough away from the noise source. This method is successful, particularly if the input to the receiver is properly balanced and shielded against capacity coupling.

Significantly, as reception means for ultra-high frequencies improves, interference energy picked up by the flat-top antenna increases. In the case of motor-car and airplane ignition system, radiation is destructive to fairly high signal intensities over comparatively great distances. In the vicinity of fifty to sixty megacycles ignition interference has been experienced from planes flying at distances up to five miles and from automobiles within a radius of more than a half-mile.

The distinguishing characteristic of this type of interference is the high ratio of peak to root-mean-square value, together with a comparatively long time interval between individual pulses. Because of this feature such noise is not psychologically objectionable until the peak voltage exceeds the received carrier level. Noise which is of greater value than the signal, then, possesses the discriminating characteristic used for suppression by the limiting method.

In the category of noise limiters comes first non-linear electro-acoustic transducers giving rise to a high degree of amplitude distortion, which definitely determines the maximum output of the device. The assumption is that auditory response for ordinary sounds is masked by extremely loud noise which, if suppressed in level, would render the underlying signal intelligible though distorted. Practical distortion means, such as, easily over-

loaded audio stages, saturable core reactors, gaseous discharge tubes, and in fact most all non-linear devices, constitute limiters of this type. The obvious disadvantage is severe distortion and more or less lack of control. Limiting is applied not only to noise but to the modulation component of the signal as well, without planned regard to the possible deleterious effect on the intelligibility and consequent fatigue to the listener.

In consideration of the needs of noise control and with a view toward simplicity and reliability, a method for such control is herein submitted.

NOISE LIMITER

Referring to the circuit on the front cover, L and D-1 represent a normal diode detector circuit where L is the inductance which may be the secondary of an intermediate-frequency transformer. Elements R-4 and R-3 constitute the resistive diode load. The constants of R-1 and C-1 may be any suitable value for normal automatic-volume-control voltage. C-3 is indicated as an intermediate-frequency filter and audio load capacity. Also R-2 and C-2 make up a separate automatic volume reservoir determined by the rectified carrier voltage in the same manner as the regular automatic-volume-control circuit. However, both values are made rather large in order that the time constants of the combination will be somewhere between a tenth and one second. Element D-2 represents, what we shall term, the noise diode and may ordinarily be combined in the same envelope with D-1, such as, the type 6H6 tube.

The switch and the cathode lead of D-2 indicates the proper position for breaking the noise-silencer circuit. To obtain an idea as to the action of the circuit let us assume a signal of such magnitude that after rectification, a negative potential of 10 volts appears at point A in Fig. 1. Then at point B the potential would be a function of the ratio of R-3 and R-4, since point C is already at ground potential. If R-4 be made equal to R-3, it is obvious that point B would have an average poten-

†The material for this article was obtained from the April 1937 issue of COMMUNICATION AND BROADCAST ENGINEERING.

tial of minus 5 volts. Point D, which is the reservoir for noise diode bias voltage, also will be at a potential of minus 10 volts. This leaves the plate of D-2 five volts more negative than the cathode so that the diode is essentially non-conductive. If, however, a high instantaneous noise-voltage peak reaches a value of, let us say, minus 40 volts after rectification, the instantaneous value at point B will be half of that, or minus 20 volts, which at the same time is the instantaneous potential at the cathode of the noise diode. The plate of the noise diode, however, remains at the original value of minus 10 volts due to the delay occasioned by the ratio of R-2 and C-2. In other words, the plate of D-2 is instantaneously 10 volts more positive than the cathode, which allows a current to flow through the lowered impedance of the diode. What happens essentially is that the alternating-current impedance for point B through D-2 and C-2 to ground is instantaneously much lower than the impedance of R-3 which is normally the audio load circuit to ground. At the termination of the noise pulse, which may last for only a thousandth of a second or even less, the circuit returns to normal almost instantly. Condenser C-2 because of its high capacity contains a sufficient amount of energy so that its normal charge is not altered materially by noise voltages appearing via R-2.

Assuming our original 10-volt rectified carrier is one hundred percent modulated, the pulsating voltage appears at point A as varying at modulation frequencies between the values of minus 20 volts and zero. At point B these values are divided by two, making a total variation from minus 10 volts to zero, so that even during one hundred percent modulation peaks the cathode of D-2 never is more negative than the plate, but merely approaches that value. In other words, this system is capable of squelching noise peaks of higher than carrier value but still does not distort the demodulated signal.

Since the action is a function of signal strength, the threshold value of noise suppression changes with signal strength. Hence, if the received signal strength goes down, the potential at point D goes down with it, and the differential audio potential at point B maintains automatically its proper ratio. Carrying the illustration to the extreme, or to no-signal value, point D is essentially at zero potential, so that any instantaneous noise present between carriers will automatically take the path to ground through D-2. Thus the system operates as a practical squelch for inter-carrier noises.

In the preceding illustration we have made R-4 equal to R-3, the reason being

that the noise circuit was not to distort a rectified signal. We can assume, however, in most cases that modulation on sustained tones will seldom exceed the fifty percent value. Therefore, R-4 can be only half the value of R-3, thus immediately improving the noise-silencing action to something below the one hundred percent modulation level. Heavy modulation peaks of instantaneous character will be by-passed through D-2 the same as noise. However, these peaks much like noise go quite unnoticed by their absence. This does not mean that one hundred percent modulation is not the ideal value for commercial and broadcast stations, but that in practice the full capabilities of modulation are seldom obtained.

For many types of communication work, where some audio distortion is acceptable, R-4 can be left out or maintained at a very low value, thus suppressing all noise down to the average unmodulated carrier level, with the positive modulation peaks as well. In practice—particularly on voice modulation—the deletion of the positive modulation peaks does not detract from the intelligibility of the rectified signal, nor is the resulting quality displeasing even after long periods of listening.

Fig. 2 shows a more desirable method of obtaining a high degree of noise suppression along with some audio distortion. Elements R-4 and R-3 can still be maintained at equal values, but R-4 is shunted by a small capacity C-4 which is of such a value as to equalize for the difference in modulation for the various voice frequencies. It has been shown that the percentage of modulation of an average voice varies with frequency to the extent that above 500 cycles the percentage curve drops very rapidly to a point in the neighborhood of a fraction of one percent at 5000 cycles. While this procedure in itself distorts the received frequency characteristic, it adds

rather than detracts from the intelligibility since the higher modulation frequencies are given a rising characteristic, as far as the load circuit R-3 is concerned. It is significant that the noise-suppression ability is increased at the same time so that the effect is just the opposite from what might be expected by those accustomed to tone controls and drooping characteristics for practical noise suppression.

Since all peak-type noises are characterized by exceedingly steep wave fronts and high damping, a pulse is similar to a single lobe of a very high-frequency wave. The appearance of this noise, as regards point B, is the same as if R-4 were not present, since C-4 offers such low impedance. Thus in most cases the full noise voltage appears at B and the cathode of D-2, allowing more complete suppression. Condenser C-3 is the intermediate-frequency filter capacity in a new position. This change is necessary in order that C-4 may exhibit its full effect without shunting action through the filter capacity. Note that in Fig. 2 the type of audio coupling indicated is prescribed where the grid bias is obtained from the drop across R-3, and known generally as diode-biasing. Elements C-5 and R-5 merely determine the limiting bias for the audio tube. By the use of C-4 under certain conditions of instantaneous voltages, the potential at B can even go slightly positive—at which time the audio tube becomes non-linear due to a positive grid, and the resulting bucking bias obtained through R-5 from change in plate current.

PRECAUTIONS

A few precautions in the installation and use of the circuit in either Fig. 1 or Fig. 2 may not be amiss. C-3 should be kept as small as possible. The reason for this is that in order to obtain good silencing action the original characteristics of the noise pulse must be retained. The discriminating characteristic used in this type of suppression is due to the fact that the noise pulses have a very high ratio of peak voltage to total power. The steepness of the wave front in making the pulse appear as a very high frequency means that any shunting capacity tending to attenuate high frequencies will distort the characteristic of the pulse and reduce the difference between it and the signal. This applies also to small inductances used in conjunction with capacities for intermediate-frequency filtering.

The aim should be to maintain high fidelity in the associated circuits of both signal and noise diodes whether or not such fidelity is warranted by intermediate-frequency sideband cutting and audio

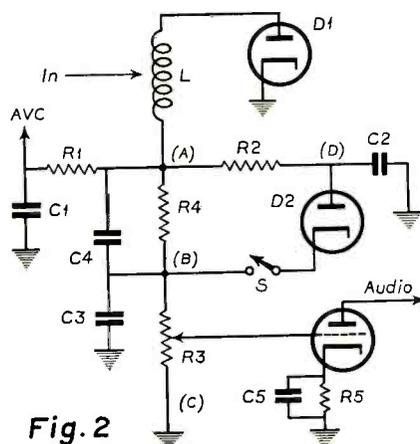


Fig. 2

A more desirable method of obtaining a high degree of noise suppression along with some audio distortion.

restrictions. To aid this condition the sum of R-3 and R-4 should be made fairly low in resistance—in the neighborhood of 100,000 to 150,000 ohms. While this necessitates a fairly high value of signal to be rectified with good fidelity, the attenuation of high frequencies is less pronounced due to stray capacity in the circuit. Leads to the resistors or noise diodes and to the audio amplifier should be kept short in order to eliminate the necessity for shielding.

In obtaining the proper time constant for the noise diode bias reservoir at D, R-2 should be a rather high value of resistance up to perhaps one megohm in order not to shunt the signal diode load. C-2 should also be a large value in order that the a-c impedance from the noise diode to ground be minimized. It is important that C-2 be non-inductive in order to be a low impedance also at very high frequencies, and good practice is to shunt this capacity with a mica condenser of smaller capacity. In any case, diode biasing of the first audio is recommended where at all possible, since coupling capacity and grid leaks complicate the detector load.

As applies to communications receivers the circuit of Fig. 2 allows practically quiet operation on all frequencies regardless of the signal strength received. Since the action is entirely automatic no controls are indicated with the exception of the switch S to cut the silencer in or out.

Noise of a sine wave character, as differentiated from the peak spark-discharge type, is suppressed to a lesser degree since the character constitutes what is more like a signal in its action on the second detector. In other words, the type of noise which changes the normal avc voltage of the receiver to any great degree is difficult to suppress by this method, but happily is the type noise not ordinarily picked up by an antenna in the clear, coupled to the receiver through an efficient transmission line.

SLIGHT LOSS

Obviously, when using the type of circuit herein described, a fraction of the audio voltage available at the plate of the signal diode is used for control bias on the noise diode so that a slight loss—never more than three decibels—is apparent in audio gain. Ordinarily such loss is negligible and can be made up easily if thought necessary. Standard practice indicates total receiver sensitivity to include audio gain, whereas radio-frequency and intermediate-frequency gain—admittedly most important—can be measured at the input to the second detector just as easily, and it may

be a more accurate yardstick for receiver excellence.

Using this standard, inclusion of the suppressor circuit causes no loss whatever to sensitivity, and in fact may apparently increase it. High noise pulses at fast interruption rates, which ordinarily reduce sensitivity through avc action, due to the relatively fast time constant of the avc resistance-capacity network, are rendered ineffectual to this end by virtue of suppression. Also, because of the lack of noise, audio gain may be maintained at a higher level with more comfort.

None of the remaining high-frequency functions are disturbed. Selectivity is not changed by addition of shunt intermediate circuits, and the suppressor has no feature which conceivably can cause unstable operation in any part of the receiver.

APPLICATIONS

Size and space are important considerations when installation is contemplated for portable and mobile use. A few ounces at most are added to the weight of airplane equipment and, if the noise diode is combined in the same envelope with the signal diode, the extra space necessary is only that used for a few resistors and capacities.

As regards aviation, it has been noted that when a suppressor-equipped receiver is left idling on one of the three or five megacycle channels, the stand-by between transmissions is remarkably free from normal inter-channel noise. Even key-clicks from adjacent or image channels are attenuated satisfactorily. No trouble was experienced with delay on quick break-ins on these channels, but since these transmissions are audio equalized for efficiency it may be advisable to decrease the time constant of R-2, C-2 by making C-2 a lower value.

While ultra-high-frequency installations in police cars can well use suppression of this type it is anticipated that some additional suppression will take care of the source of ignition interference. It is found that, while such exceedingly heavy noise is limited to the pre-determined value, the length of the silent period during pulses may become objectionable unless the ignition system is maintained at perfect adjustment. Happily, interference from passing cars is practically eliminated—which is not the case with the diversity method of noise control as installed in some mobile receivers.

It is suggested that all-wave and multi-band amateur-commercial receivers incorporate, as part of the band change switch, means for allowing suppression with high-fidelity response for

the broadcast frequencies and varying degrees of suppression for the other bands. The automatic feature otherwise will take care of different signal levels encountered within certain bands including the rapid fading encountered above ten megacycles.

COMPLETE SATISFACTION NOT ANTICIPATED

It is believed that no single method for noise reduction can be expected to accomplish complete satisfaction. Because of the various types of interference encountered—each with a favored method for elimination—the ultimate must necessarily be a combination of tactics. Hundreds of thousands of dollars are spent annually in noise research by aviation, communications and television companies. New methods are known to be in the laboratories and it is hoped that, when television becomes a reality, extraneous noise must cease to exist.


MATCHING TRANSFORMERS

(Continued from page 337)


into a grid. If a 250-ohm transformer is not on hand, one of the popular brands labeled: 125-500 ohms-to-grid, may be used. Since the difference between the 125- and 500-ohm taps is 375 ohms, the mike may be connected to these two taps. Here the source impedance is lower than the transformer rating and since this improves the frequency characteristic, good results may be expected. In the same way a low impedance pickup, say 20 ohms, may be connected to a transformer having a rating of 50 ohms to grid.

Similar arrangements may be made with output transformers, and speaking of output transformers, they may be used for other purposes than to couple a tube or tubes to a voice coil. Suppose it is desired to couple a low impedance pickup of 8 ohms to a grid. An output transformer having a high impedance ratio may be used as for instance, one to couple a pair of 2A5s to an 8-ohm voice coil. The transformer is used in the reverse way, that is, the voice coil side is used as the primary and the original primary is considered the secondary. The pickup is connected to the primary and the secondary is connected to the grid and ground, or cathode as the case may be. The center tap is disregarded. A 15,000-ohm volume control may be connected across the secondary for attenuation purposes. The voltage ratio is not as high as the conventional pickup-to-grid transformer, but it will serve with fair results.

The Best "BUYS" Are Made For Cash!

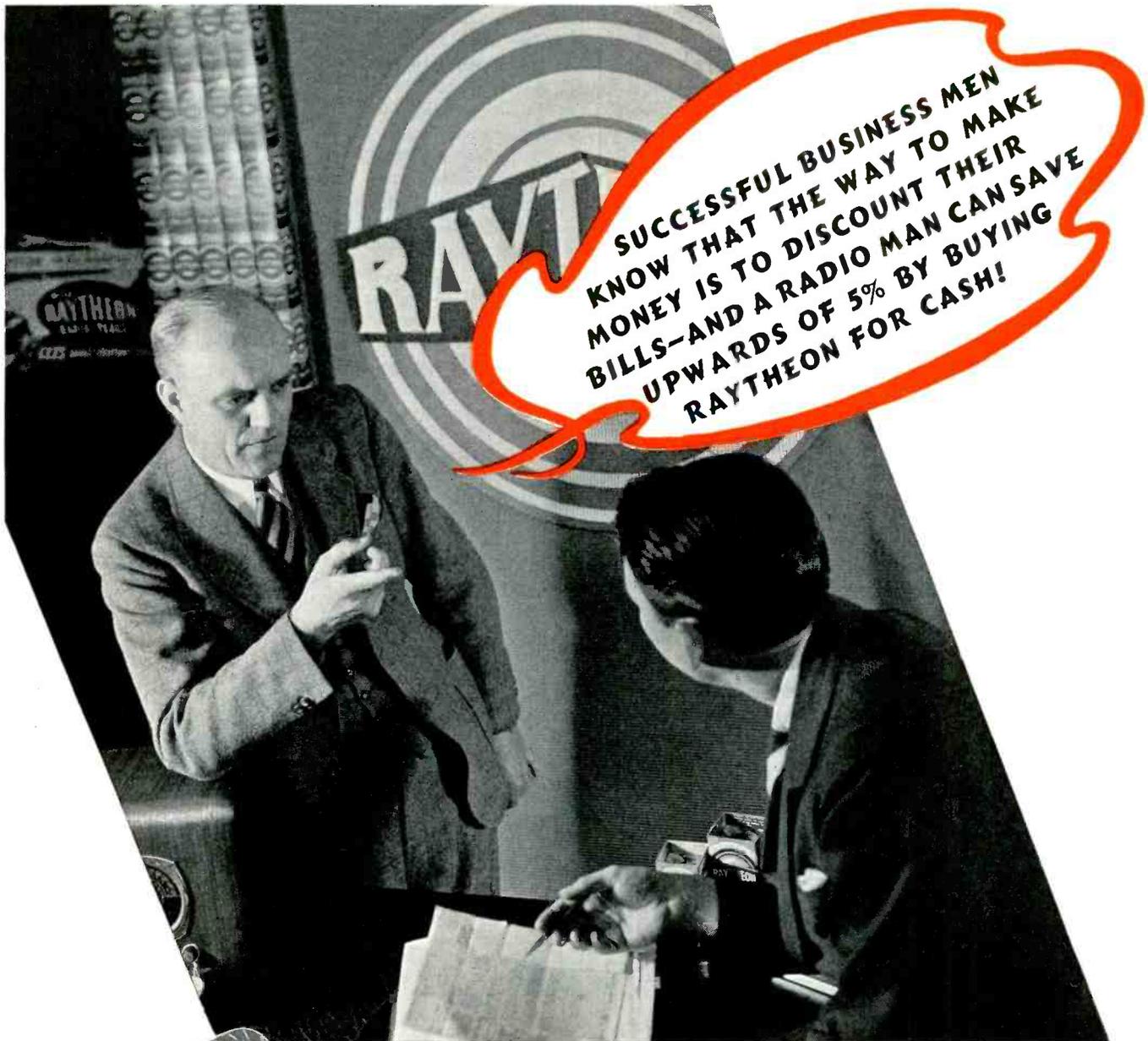

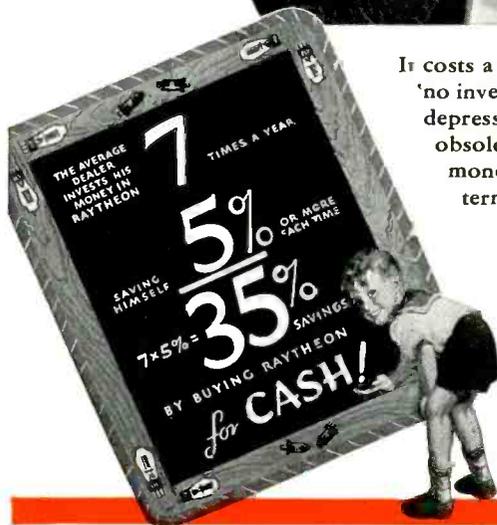SUCCESSFUL BUSINESS MEN
KNOW THAT THE WAY TO MAKE
MONEY IS TO DISCOUNT THEIR
BILLS—AND A RADIO MAN CAN SAVE
UPWARDS OF 5% BY BUYING
RAYTHEON FOR CASH!



It costs a distributor or a dealer at least 5% to sell and handle tubes on any of the 'no investment' finance plans. You, the dealer, have to pay this 5% or more . . . The depression is over and depression methods of doing business are rapidly becoming obsolete. That is why increasing thousands of dealers and service men are saving money and getting the highest quality tube by buying RAYTHEONS on regular terms. ASK YOUR RAYTHEON JOBBER.

RAYTHEON

445 Lake Shore Drive, Chicago, Illinois
555 Howard Street, San Francisco, Cal.

420 Lexington Ave., New York, N. Y.
55 Chapel Street, Newton, Mass.

415 Peachtree Street, N. E., Atlanta, Ga.

General Data . . .

Belmont 878

The Belmont Model 878 is a 3-band, high-fidelity, a-c superheterodyne receiver using 7 metal tubes and a glass tuning indicator tube. A circuit diagram of the Series B receiver is shown in Fig. 1. The Series A is almost identical. In the oscillator padding circuit of the Series A receiver an additional 300- μ mfd (working capacity) adjustable padder (C25) is connected across the fixed padder C23. The capacity of the latter is 0.0021 mfd, instead of 0.0034 mfd as indicated for the Series B receiver. Other changes are negligible.

Transformers are available and chassis are sometimes equipped with universal transformers for operation on 25, 40 and 60 cycles and with primary taps for 108, 127, 150, 225, and 260 volts and also sometimes equipped with 25 cycle transformers with 105-115 volt or 220 volt primaries, not universals.

Voltages taken from different points

of circuit to chassis are measured with volume control full on, all tubes in their sockets and speaker connected, with a volt meter having a resistance of 1000-ohms-per-volt. These voltages are indicated on the circuit diagram.

In order to prevent the signal from acting upon the avc and affecting the accuracy of the voltage measurements the aerial and ground leads should be shorted together while making the measurements.

The voltages were measured with 119 volts on the primary of the power transformer. The d-c resistances of the various coils and transformer windings are also lettered on the circuit diagram of Fig. 1.

The frequency range is from 535 kc to 18.1 mc and is identical for both the Series A and B receivers. The i-f peak is 465 kc for both types.

ALIGNMENT PROCEDURE

Dummy antennas: The following dummy antennas are used in aligning

the Model 878 and are referred to in the aligning instructions as dummy 1, 2 and 3 respectively. Dummy 1, used in the i-f alignment, consists of a 0.1-mfd condenser connected in series with the external test oscillator. Dummy 2, used on the broadcast band, consists of a 200- μ mfd condenser and a 20-ohm resistor connected in series with each other and the external test oscillator. Dummy 3, used on the shorter wavebands, consists of a 0.1-mfd condenser and a 400-ohm resistor connected in series with each other and the external test oscillator.

Resonance indicator: Use as a resonance indicator an output meter connected across the primary of the speaker input transformer or by means of an adapter between the plate and screen terminals of the type 6F6 output tube. Maximum deflection of the meter indicates resonance. Use only enough signal to get a readily readable output. A low range output meter or the low scale of a multi-range meter should be used.

Caution: No aligning adjustments should be attempted without first thoroughly checking over all other possible causes of trouble, such as poor installations, open or grounded antenna

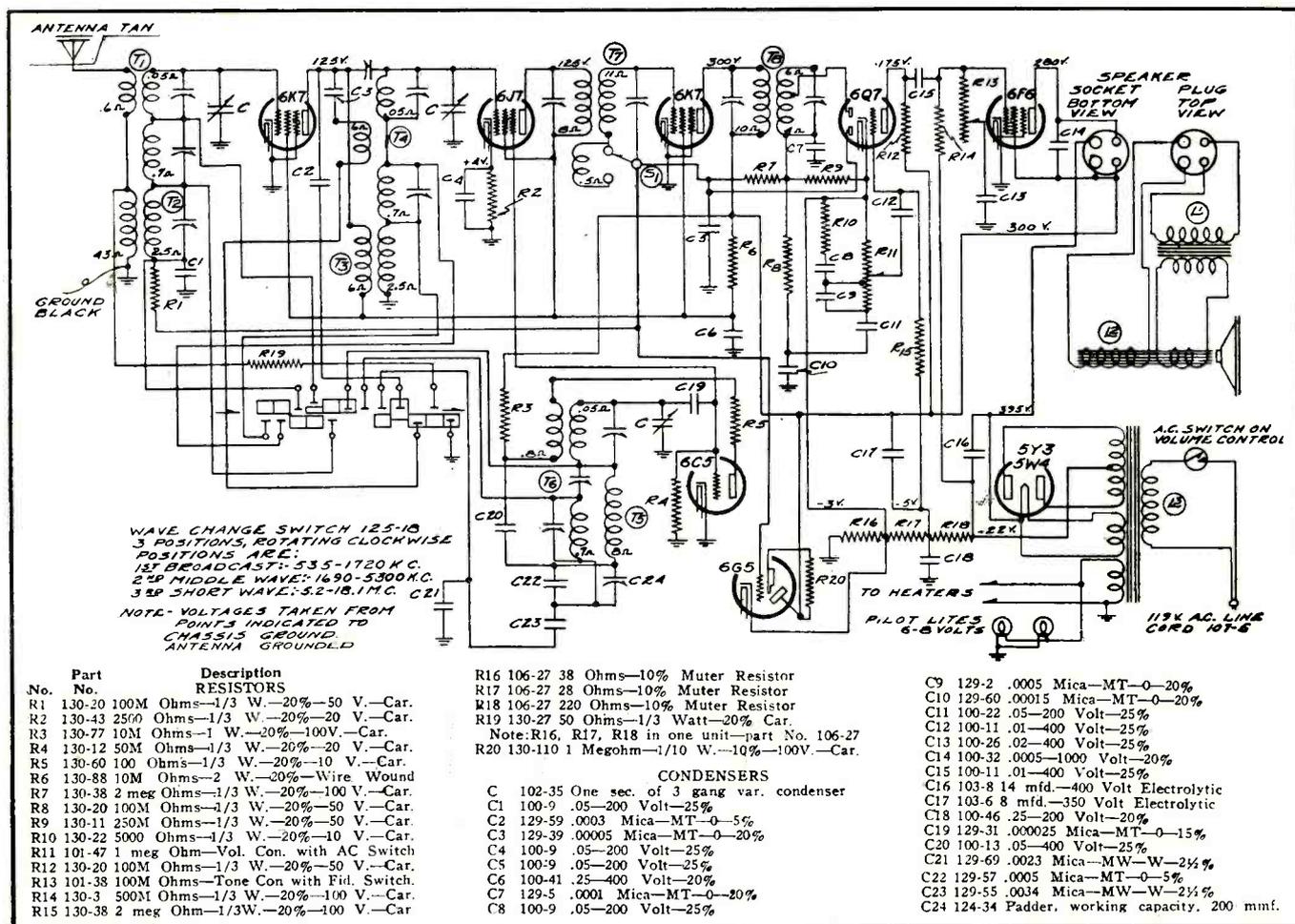


Fig. 1. Belmont 878 circuit diagram.

NOW TRANSFORMER REPLACEMENT DATA IN A FLASH WITH THE NEW

**THORDARSON
REPLACEMENT
TRANSFORMER
ENCYCLOPEDIA**

**COVERS 98.9% OF
RIDER'S 7 VOLUMES**

Like a flash your eye spots the exact Replacement Transformer needed. Never before has a radio parts manufacturer given the service man such a value. A servicing helper that will make history. Practically every set mentioned in Rider's 7 volumes is cataloged. Eliminate time wasting check-up of wiring or letters to manufacturers. Now it's in this one book under one cover. No more guessing.

**GET YOUR COPY NOW!
LIST PRICE—25c**

15c Postpaid direct from factory on request or

FREE From Your Distributor Through Registration.
Ask about it TODAY!

BE SURE TO SEE US AT THE RADIO PARTS SHOW, BOOTH No. 128 STEVENS HOTEL, CHICAGO

THORDARSON ELECTRIC MFG. CO.

500 W. HURON ST., CHICAGO, ILL.

Demand "Power by Thordarson"

RADIO'S FOUNDATION—A GOOD ANTENNA

- A complete line of couplers available for existing doublet antennae. Also inexpensive straight wire kits.



- TACO No. 400 System. Economical All-Wave job. Includes aerial wire, insulators, transfer unit, download and set coupler. \$3.75 list.



- TACO No. 510 System. All-Wave. Full Noise-Reducing in all bands. Factory assembled and soldered. Complete with all accessories.



- TACO No. 210 DeLuxe System. Lic. A.A.K. Patent 1965539. Re-issued as Re. 19854. Improved circuit. All-Wave. Full Noise-Reducing. Greater efficiency in entire short-wave spectrum and also in broadcast band. For superlative performance. \$6.75 list
- TACO Wave-Traps. Three models covering the broadcast band. Adjustable. Tunes out annoying local station. Only \$0.95 list.

Your Chance to Cash In!

YOU can sell a TACO Antenna System for every set, new or old, in your territory. That means extra money from your calls. Also better satisfied customers, because TACO Antenna Systems positively improve the performance of ANY set.

MASTER ANTENNA SYSTEM for Apartment or Private Dwelling


Just the thing for private dwellings. An Antenna-Ground Outlet for every room. Ideal results. Simple, practical, inexpensive. The TACO Master Antenna System is equally applicable to private dwelling or giant apartment house, hotel, hospital, etc.

System available in handy foundation unit kit for aerial and download, and as many outlet units as required. Exposed or concealed wiring. Foolproof installation.

Hundreds of installations now in use. Enthusiastic reports from property owners and radio listeners. Remember, there's a handsome profit in every job. So why not get your share?



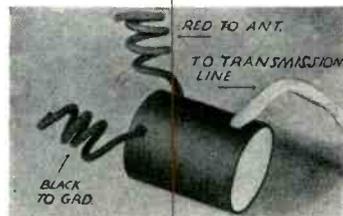Exposed wiring type outlet coupler (above) and concealed wiring type outlet shown below.



Ask for DATA: Literature covering Master and other TACO systems available through your local jobber or direct from us.

TACO

TECHNICAL APPLIANCE CORP.
17 East 16th St. New York City

IN CANADA: 414 BAY STREET, TORONTO

A Fully-wired Building is Wired for Radio

GENERAL DATA—continued

board is the on-off switch for the phonograph motor.

A circuit diagram of the G-127 is shown in Fig. 1 with the tubes used and the various voltages encountered on the socket prongs lettered on the diagram. These voltage readings were taken with a 1000-ohm-per-volt voltmeter from the point indicated to the receiver chassis with the volume control on full. The antenna was shorted to the chassis while making the measurements. The line voltage was 117.5 volts.

On the circuit diagram (Fig. 1) the various resistors and condensers are numbered. These numbers correspond to values given in the accompanying parts list.

Several production changes have been incorporated in the model G-127 and are shown on the diagram. Early receivers differed from the schematic diagram as follows:

(a) A 50,000-ohm resistor, bypassed with a 0.1-mfd, 200-volt condenser was used in the plate circuit of

the 75 tube as an R-C filter.

(b) The rotor of C28 was returned to ground instead of the coil, as shown on the schematic.

(c) R11 and R12 were 250,000-ohm carbon resistors.

(d) The 6A7 and 6D6 cathodes were connected together. R2 was a 150-ohm, ½-watt wire-wound resistor, and C7 was 0.15-mfd, 200-volt condenser. R9 and C26 were not in the circuit.

(e) C1 was an 0.01-mfd, 200-volt condenser.

ALIGNMENT PROCEDURE

The set's oscillator is higher in frequency than the signal; images should be observed on the low frequency side of the signals.

Always choose the minimum capacity peak on oscillator trimmers and maximum capacity peaks on antenna trimmers. The last motion in adjusting trimmers should always be a tightening one, not a loosening one.

Always use as weak a test signal as possible during alignment.

Never leave a trimmer with the out-

side plate so loose that there is no tension on the screw. Either bend the plate up or remove the screw entirely.

An output meter should be used across the voice coil or the output for observing maximum response.

TRIMMER LOCATIONS

The broadcast antenna coil, the short-wave antenna coil and the 456-kc wave trap are one assembly mounted underneath the chassis deck to the right of the variable condenser. The trimmers for these coils are accessible through three holes in the top of the chassis. The trimmer closest to the front of the chassis is for the short-wave antenna coil. The central trimmer is for the broadcast antenna coil and the trimmer farthest from the chassis front is for the 456-kc wave trap.

The broadcast oscillator and short-wave oscillator coils are wound on one tubing and mounted on the inside of the rear chassis wall. The trimmers for these coils are accessible through two holes in the rear chassis wall. The left-hand trimmer (looking at the rear wall)


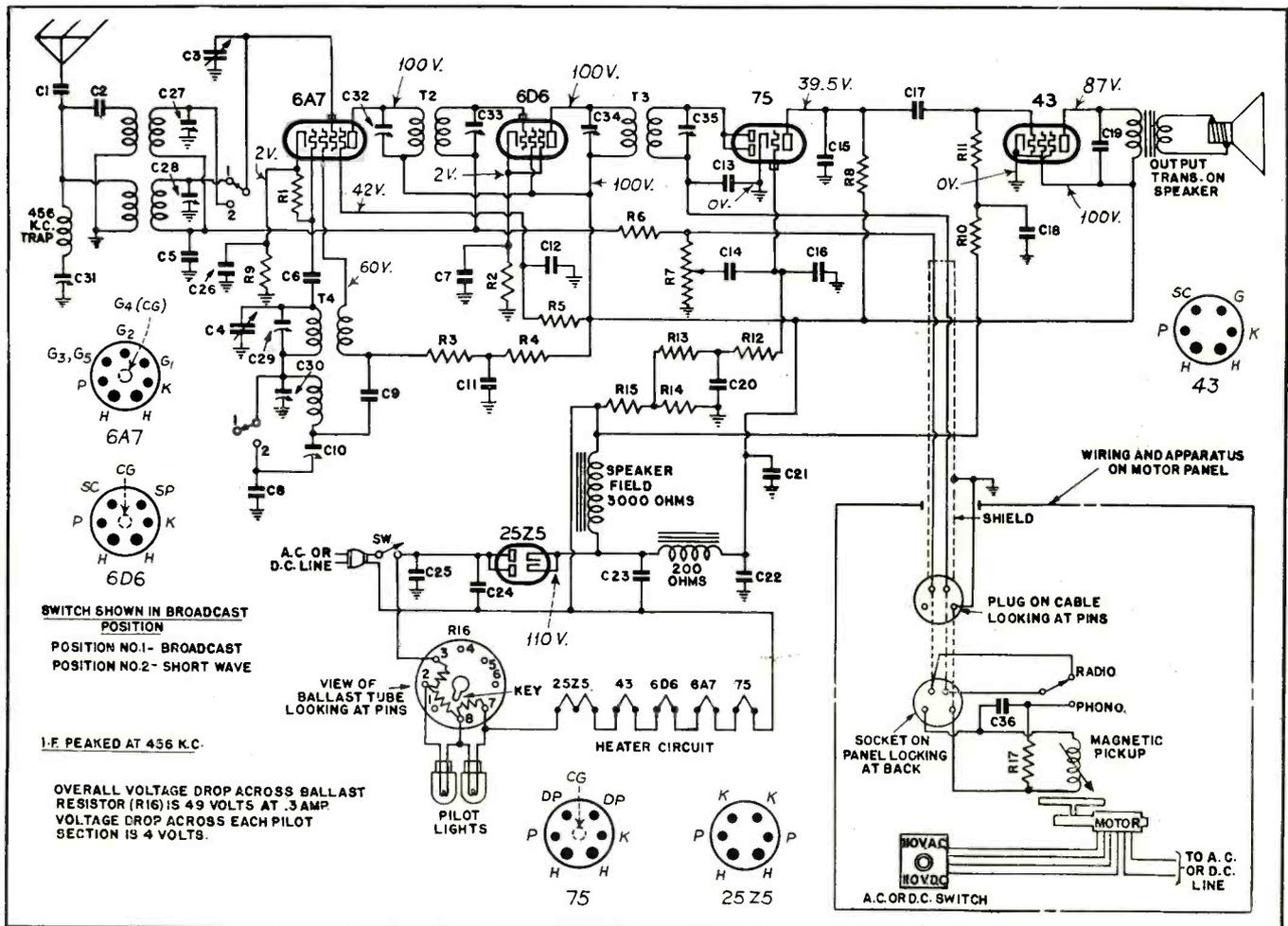


Fig. 1. Emerson G-127 circuit diagram.

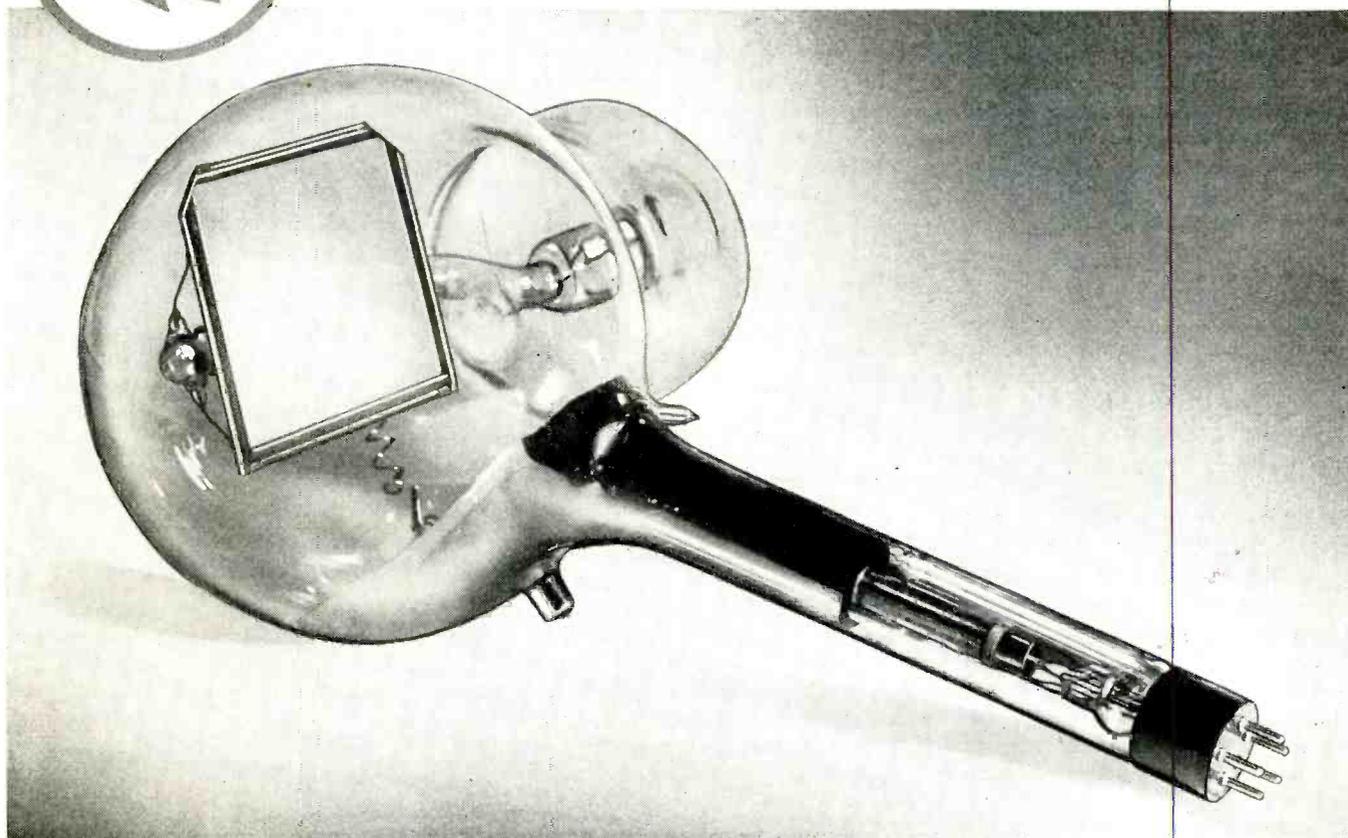

Symbol of the Radio Age



MMUSIC, drama, news, laughter... messages across oceans and mountain ranges... directions to mariners at sea... whenever electric images of sound travel through space, their passage has been facilitated by the research and technology of RCA.

Each individual phase of radio is represented by an RCA service that is a specialist in that particular field. Each of these services does better work in its own line for the fact that it freely taps the knowledge and experience of all the other RCA services.

In this fast-moving radio age, merchants, broadcasters, and advertisers who associate

their interests with RCA products or facilities automatically participate in every modern development of the radio art.

RCA REVIEW

A quarterly of Radio Progress, and a source of news and reference material of value to engineers and laymen alike who wish to keep abreast of progress in radio and allied arts.

RCA Review now offers most attractive subscription terms of \$1.50 for one year, or \$2.50 for two years, or \$3.50 for three years, to U.S. and Canada; to other countries, add 35 cents per year.

RCA INSTITUTES TECHNICAL PRESS

75 Varick Street, New York

RADIO CORPORATION OF AMERICA

RCA Building, New York

Radiomarine Corporation of America • RCA Manufacturing Company, Inc. (RCA Victor products)
RCA Institutes, Inc. • National Broadcasting Company • RCA Communications, Inc.

RCA PRESENTS THE "MAGIC KEY" EVERY SUNDAY, 2 TO 3 P. M., E. D. T., ON COMPLETE NBC BLUE NETWORK

JUNE, 1937 •

SAY YOU SAW IT IN SERVICE

347

GENERAL DATA—continued

is for the short-wave oscillator coil and the right-hand trimmer is for the broadcast oscillator coil.

The two i-f transformers are in oblong coil cans located on the top of the chassis. The first i-f transformer is the one behind the variable condenser. The trimmers for these transformers are accessible through holes in the tops of the cans.

The broadcast series padding condenser is located on the rear wall of the chassis below the 6A7 tube.

I-F ALIGNMENT

Turn the switch clockwise to the broadcast position and rotate the variable condenser to the minimum capacity position. Feed 456 kc to the grip cap of the 6A7 tube and adjust the four i-f trimmers for maximum response. Feed 456 kc to the antenna and adjust the wave-trap trimmer (rear screw beside variable condenser) for minimum response.

SHORT-WAVE ALIGNMENT

Use a dummy antenna (400-ohm resistor) when aligning the short-wave coils.

Rotate the wave-band switch counterclockwise to the short-wave position and set the dial pointer to 15 megacycles. Feed 15 megacycles through the dummy

EMERSON G-127 PARTS LIST

Item	Resistor	Item	Condenser
R1	50,000 ohms	C1	0.001 mfd
R2	300 ohms	C2	0.00005 mfd
R3	10,000 ohms	C5	0.05 mfd
R4	10,000 ohms	C6	0.00005 mfd
R5	30,000 ohms	C7	0.1 mfd
R6	1 megohm	C8	0.0042 mfd
R7	250,000 ohms	C9	0.01 mfd
R8	250,000 ohms	C11	4 mfd
R9	300 ohms	C12	0.1 mfd
R10	25,000 ohms	C13	0.00025 mfd
R11	500,000 ohms	C14	0.02 mfd
R12	500,000 ohms	C15	0.00025 mfd
R13	250,000 ohms	C17	0.02 mfd
R14	20 ohms	C18	0.1 mfd
R15	230 ohms	C19	0.01 mfd
R16	Ballast	C20	0.1 mfd
R17	100,000 ohms	C21	0.1 mfd
		C22	20 mfd
		C23	20 mfd
		C24	0.1 mfd
		C25	0.01 mfd
		C26	0.1 mfd

antenna and adjust the short-wave oscillator trimmer (left-hand screw on rear chassis wall) for maximum response and then adjust the short-wave antenna trimmer (front screw beside variable condenser) for maximum response. The variable condenser should be rocked while adjusting the antenna trimmer. (Rotate variable condenser rotor shaft back and forth through a small arc).

BROADCAST ALIGNMENT

Rotate the wave-band switch to the broadcast position, clockwise, and set the dial pointer at 60. Feed 600 kc through a standard dummy antenna (a 0.0002-mfd condenser may be used as a substitute).

Adjust the broadcast series padding condenser (on rear chassis wall below 6A7 tube) for maximum response. Move pointer to 142.5, feed 1425 kc and adjust the broadcast oscillator trimmer (right-hand screw on rear chassis wall) for maximum response and then adjust the broadcast antenna trimmer (central screw beside variable condenser) for maximum response. Return pointer to 60, feed 600 kc and readjust the series padding condenser rocking the variable condenser for maximum response.

The alignment procedure should be repeated.

RCA 9T, 9K2, 9U, 9U2

These models are 9-tube "Magic Brain" receivers using 7 metal tubes, a glass rectifier and a glass tuning eye. The long-wave range from 150 to 410 kc is covered in Band X. Four additional bands cover the ranges from 530 kc to 60.0 mc. The radio receiver

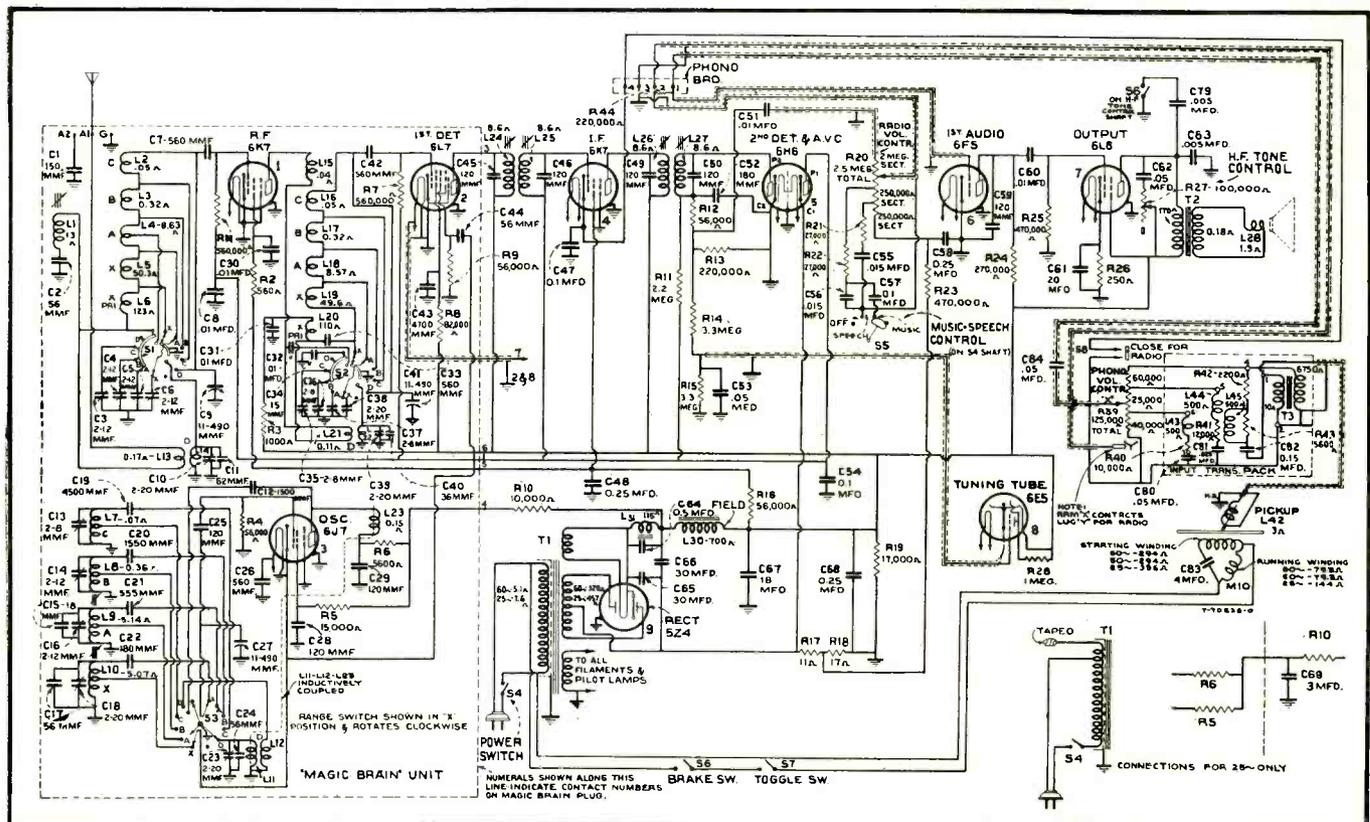


Fig. 1. RCA 9T, 9K2, 9U, 9U2 circuit diagram.



QUIET... HIGH FIDELITY...



ARCTURUS

6F6G

PERFECTION OF DETAIL AGAIN BRINGS YOU A BETTER TUBE



**MAKING
TUBES
IS A SCIENCE**

*demanding precise
detail engineering*

ARCTURUS PIONEERED "G" TUBES

QUESTION: Why do technicians who know their tubes insist on Arcturus 6F6G's for output pentode applications?

ANSWER: Because they know Arcturus engineers have definitely conquered the weaknesses of ordinary tubes of this type. They know the Arcturus 6F6G gives uniformly good tone over a longer period of time and further that it eliminates the noise, distortion and "gargling" commonly noticeable in this type.

Advanced processing and improved cathode coating tends to lower grid emission and other forms of grid

current—and keeps them low. Also, like other Arcturus types, each 6F6G is individually tested many times during manufacture. Then to make doubly sure, all tube elements are given an excessive voltage that immediately discloses any grid emission defect. The final test in a highly sensitive receiver is triple assurance that you receive trouble-free tubes.

Thus, not only are Arcturus Tubes made better in the first place. They are likewise more carefully tested so that each and every tube coming to you will measure fully up to our slogan "*None but the very best!*"

ARCTURUS RADIO TUBE CO., NEWARK, N. J., U. S. A.

ARCTURUS

INDEPENDENT TUBES FOR DEALERS WHO DO THEIR OWN INDEPENDENT THINKING

GENERAL DATA—continued

and amplifier will draw 150 watts from the 60-cycle, 115-volt, a-c line. The phonograph motor will draw an additional 25 watts.

The Model 9T is a table type with an 8-in speaker. The Model 9K2 is of the console type with a 12-in speaker.

The Models 9U and 9U2 are combination receivers and automatically operated phonographs. These instruments are electrically identical but differ in mechanical construction and cabinet design. Model 9U has the radio chassis mounted directly below the phonograph motor board with its controls operated from the front of the cabinet. Model 9U2 has its radio chassis mounted vertically to the right of the phonograph motor board. The respective controls in the phonograph and the radio compartments are made accessible by means of separate hinged covers at the top of the cabinet. Both instruments employ 12-in speakers.

The Models 9K2, 9U and 9U2 incorporate the "Magic-Voice."

Five watts of undistorted output is available from all models with a maximum of 9 watts. Electrodynamic speakers are used with a voice-coil impedance of 2.2-ohms at 400 cycles.

Design features include a built-in doublet antenna coupler; "Magic Brain"; improved plunger-type air-dielectric adjustable trimming capacitors in the antenna, detector, and oscillator coil circuits; tuned r-f amplifier; high-efficiency first detector (converter) with separate oscillator; beam-type power amplifier; magnetite core adjusted i-f transformers, low-frequency oscillator tracking, and wave-trap; two-point aural compensated radio and phonograph volume controls; music-speech switch; automatic volume control; continuously-variable high-frequency tone control; improved selector dial; dust-proof electrodynamic loud-speaker; and an automatic record player employing a synchronous motor.

Service convenience has been a controlling factor in the layout of the chassis parts and wiring. The assembly of these various elements is such that the number of conductors is minimized, with all important connections being readily accessible.

R-F CIRCUIT

The conventional type of superheterodyne circuit is used. It consists of an r-f amplifier stage, first-detector (converter) stage, separate oscillator stage, an i-f amplifier stage, a diode-detector — automatic - volume - control

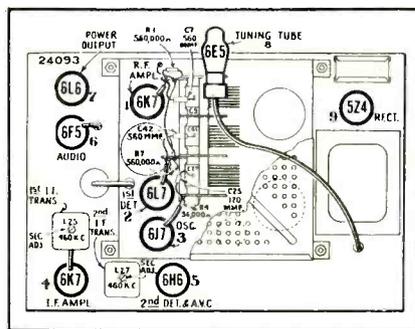


Fig. 2. Tube and i-f trimmer locations.

stage, an audio voltage-amplifier stage, a beam-type power-amplifier stage, a tuning indicator "Magic Eye," and a full-wave rectifier.

The "Magic Brain" is constructed as a separate, self-contained, completely shielded, five-band, oscillator-detector-antenna-tuning unit which plugs into the main chassis.

A single-wire antenna, or a doublet antenna, when connected to the proper input terminals of the receiver, is coupled to the control grid of the 6K7 r-f amplifier tube through the tuned r-f transformer consisting of L6, L5, L4, L3, and L2 (except when range selector is in ultra-short wave position). The primary coil L13 of the ultra-short wave (D) band tuned r-f transformer remains in the antenna circuit at all times. A unique method of switching is used. In the long-wave (X) band, L6 becomes the primary with L5, L4, L3, and L2 as secondary. In the standard-broadcast (A) band, L5 becomes the primary with L4, L3, and L2 as secondary (L6 shorted out). In the medium-wave (B) band, L4 becomes the primary with L3 and L2 as secondary (L6 and L5 shorted out). In the short-wave (C) band, L3 becomes the primary with L2 as secondary (L6,

L5, L4, and tap on L4 shorted out). The tap on L4 is provided to prevent interaction with L3 and L2 when operating receiver in short-wave band. In the ultra-short-wave (D) band, L6, L5, L4, and L3 are shorted out and grounded, and secondary L14 is placed in shunt with L2. The latter connection prevents undesirable interaction of L2 with L14. This method of switching reduces the total number of coils and leads, and results in having a low-loss primary and secondary winding for each band with high efficiency of operation.

The band switching of the detector circuits is similar to that of the antenna circuits. Coils L15, L21, and L20 are always connected in series with the plate circuit of the 6K7 r-f amplifier tube. In the long-wave (X) band, L19, L18, L17, and L16 are connected in series as the secondary circuit. The ground of the coil system is at the low end of L19. L20 acts as the primary which transfers energy to the secondary L19. Capacitor C33 resonates primary L20 at the proper frequency. In the standard-broadcast (A) band, L18, L17, and L16 are connected in series as the secondary circuit. The ground of the coil system is now between L18 and L19. L19 is used as the primary and is resonated at the proper frequency by capacitors C34 and C35 which are in shunt with this coil. Capacitor C33 is connected to transfer energy to the primary coil L19. In the medium-wave (B) band, L17 and L16 are connected in series as the secondary. The ground of the coil system is now between L17 and L18. L18 is used as the primary and is resonated at the proper frequency by capacitor C34 which is in shunt with this coil. L19 is shorted by the range selector. Capacitor C33 transfers the r-f energy from the plate circuit to the primary L18. In the short-wave (C) band, L16 is the secondary. The ground of the coil system is now between L16 and L17. L17 is used as the primary and is resonated to the proper frequency by capacitor C34. In addition, L15 acts as a high-frequency primary which resonates above 20 mc and improves the gain at the high-frequency end of the short-wave band. Coils L19 and L18 are shorted by the range selector. L21 is effectively r-f by-passed in this position by capacitor C32. In the ultra-short-wave (D) band, L22 is the secondary, or grid coil, and consists of approximately a single turn of silver plated strap around a 7/8-in coil form. The primary coils, L21 and L15 are in series on this band, with L21 acting as a low-frequency primary and L15 as a high-frequency primary. L16 is

CATHODE CURRENT READINGS


Measured with Milliammeter Connected at Tube Socket Cathode Terminal under Conditions Similar to Those of Voltage Measurements

(1) 6K7—R-F	8.0 ma
(2) 6L7—First Det.	4.4 ma
(3) 6J7—Osc.	6.7 ma
(4) 6K7—I.F.	8.0 ma
(5) 6H6—Second Det.-A.V.C.	—
(6) 6F5—A.F.	0.3 ma
(7) 6L6—Power	63 ma
(8) 6E5—Eye	3.0 ma
(9) 5Z4—Rect.	110 ma*

(*Cannot be measured at socket)

NEW UTC BEAM POWER AMPLIFIERS

The UTC PAK kits are now acknowledged by the PA field as ideal Universal amplifiers. PAK power amplifier kits are available with outputs of 8, 15, 35, 55, 70, 110 and 250 watts. Stabilized feedback can be used in the PAK-1, PAK-2, PAK-3 and the PA output transformers have special feedback windings for this purpose. There is provision for mixing of two high impedance inputs. An etched panel providing a dual gain, two position mixer with gain links for high or low gain on each position and a VARITONE equalizer control are now standard equipment on these kits.

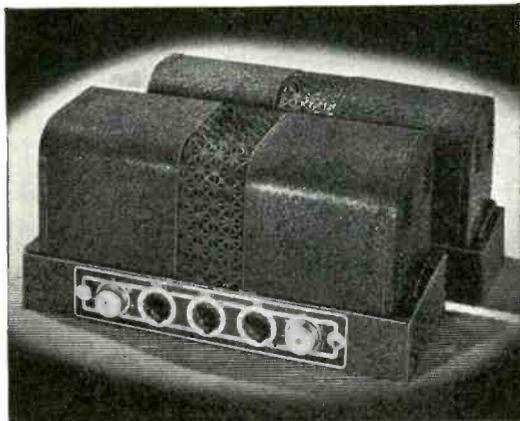


PAK-1M

Self bias 35 watt output. Audio and power on separate chassis for rack or cabinet mounting. High impedance input 110 to 120 DB gain. Provision for immediate switchover to 95 DB gain with connections either for triode plate or 500-200 ohm input line. Output transformer impedances 500, 200, 16, 8, 5, 3, 1.5 ohms. Includes all components and accessories such as resistors, condensers, sockets, calibration plates, etched mixer panel, controls and accessories for a dual gain, two position high impedance mixer, chassis, dust covers with handles, hardware—**\$48.00** except tubes—all fully mounted. Net price.....

PAK-2M


Same chassis layout as PAK-1M but has output of 55 watts in fixed bias. Net price..... **\$51.00**

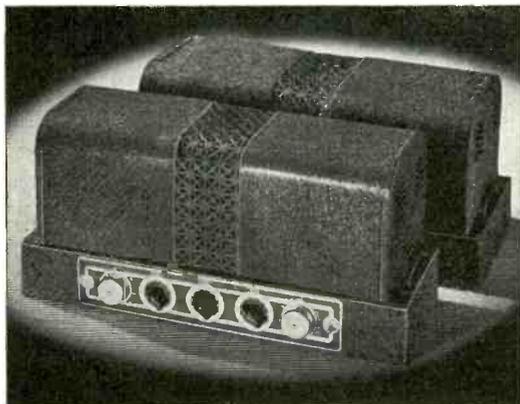Tubes required for PAK-1M and PAK-2M kits are 1-6J7, 3-6C5's, 2-6L6's, 1-83.



PAK-3M

Uses 4-6L6's—70 watts self bias—110 watts fixed bias, total gain 110 DB. High impedance input. Separate chassis for power and audio for rack or cabinet mounting. Tubes are 1-6J5, 1-6C5, 2-6A5G's, 4-6L6's, 3-83's, 1-80. Output transformer impedances 500, 200, 16, 8, 5, 3, 1.5 ohms. Includes all accessories such as resistors, condensers, sockets, calibration plates, etched mixer panel, controls and accessories for a dual gain, two position high impedance mixer, chassis, dust covers, handles, hardware—except tubes—all fully mounted. Net **\$78.00** Price

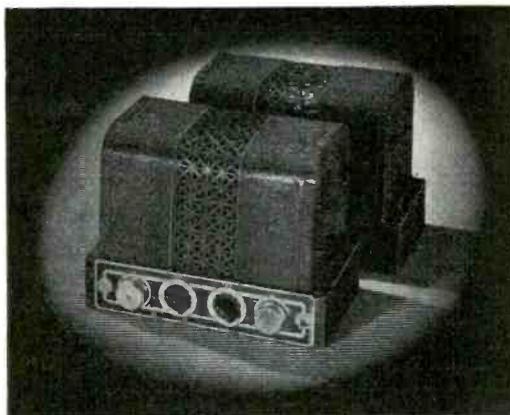

PAK-4M

DC-AC amplifier. Four 25L6 Beam Power tubes are used to deliver 8 watts output on 115 volts. Tubes used are 1-6J7, 1-6C5, 3-25L6's, High impedance input—100 DB gain. The audio section is self contained (6 x 8 x 10 1/2 inches) and can be operated directly on DC. For AC operation a separate power supply (6 x 8 x 10 1/2) is used. Audio amplifier kit only, output impedance 500, 200, 15, 8, 5, 3, 1 1/2 ohms, including all accessories, with dual gain, two position mixer and VARITONE equalizer control, less tubes, fully mounted. Net price..... **\$21.00**


PAK-4P

AC power supply components and accessories for PAK-4M. Net **\$15.00** price



PAK-5M

15 watt compact power amplifier. Uses two 6V6 Beam Power tubes. Power supply and audio amplifier on one chassis 6 x 9 x 12 inches. Tubes are 6J7, 6C5, 2-6V6's—120 DB gain. High impedance input, 500, 200, 15, 8, 5, 3, 1 1/2 ohms output. Kit includes all accessories and pre-wired resistor—condenser strip, mixer panel, controls and accessories for a dual gain, two position mixer and VARITONE equalizer control, less tubes. Net price..... **\$33.00**

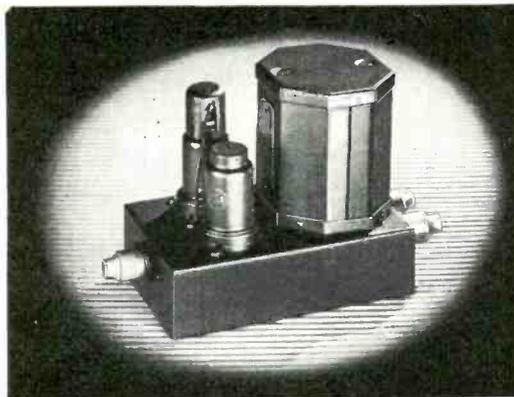

PAK-7A

Pre-amplifier. High gain well filtered pre-amplifier designed to operate from power supply in main amplifier. High impedance input, 6F5 resistance coupled to 6C5—50, 200, 500 ohm output. Gain 60 DB. Amplifier kit only including all accessories, less tubes. Net price..... **\$9.00**

PAK-7P

Power supply—components and accessories for 7A preamplifier. Net **\$9.00** price

UNITED TRANSFORMER CORP.

72 SPRING STREET

NEW YORK, N. Y.

EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: "ARLAB"

GENERAL DATA—continued

shunted by L22 instead of being shorted directly by the range selector. Any inductive effect of L16 is thus eliminated. L19, L18, and L17 are shorted directly by the range selector.

Separate windings, with the exception of L23, are employed in the oscillator stage for each position of the range selector. L23 (inductively coupled to L11 and L12) is placed in the oscillator plate circuit to provide additional feedback when operating receiver on the ultra-short-wave (D) band. This coil is effectively r-f by-passed by capacitor C12, when range selector is in the short-wave (C) position, to prevent undesirable reactions. Its effect on the remaining bands is negligible. The inherent stability of the oscillator circuit provides minimum frequency drift which is especially advantageous for high-frequency reception. The locally generated signal is capacitance coupled to grid No. 3 of the 6L7 first detector.

The output of the "Magic Brain" is fed to the i-f amplifier through a plug-in cable. This cable also supplies all power required to the "Magic Brain" unit.

The i-f amplifier consists of a 6K7 in a transformer-coupled circuit. The windings of these transformers are res-

onated with fixed capacitors, and are adjusted by molded magnetite cores (both primary and secondary) to tune to 460 kc.

The modulated signal as obtained from the output of the i-f stage is detected by a 6H6 twin-diode tube (No. 2 diode). The audio frequency secured by this process is transferred to the a-f system for amplification and final reproduction. The d-c voltage which results from detection of the signal is used for automatic volume control. This voltage, which develops across resistors R12 and R13, is applied as automatic control-grid bias to the r-f, first-detector, and i-f tubes. The No. 1 diode of the 6H6 is used to supply residual bias to the controlled tubes under conditions of little or no signal. This diode, under such conditions, draws current which flows through resistors R11, R12, and R13, thereby maintaining the desired operating bias on such tubes. On application of signal energy above a certain level, however, the No. 1 diode ceases to draw current and the a-v-c diode takes over the biasing function.

A-F CIRCUIT

The manual radio volume control consists of an acoustically tapered po-

tentimeter in the audio circuit between the output of the detector-diode and the input grid of the 6F5 audio voltage-amplifier tube. This control has a two-point tone-compensating filter connected to it so that the correct aural balance will be obtained at different volume settings.

The output of the voltage amplifier is resistance-capacitance coupled to the control grid of the 6L6 power output tube. The output of this stage is transformer coupled to the voice coil of the speaker.

The music-speech control consists of a switch S5 which, in the speech position, places an additional capacitor C57 in shunt with the capacitor C56 in one of the tone-compensating filters. This reduces the low-frequency response of the amplifier and provides maximum intelligibility of the voice frequencies.

The high-frequency tone control consists essentially of the combinations of capacitor C62 and variable resistor R27, capacitor C79 and switch S6 shunting the plate circuit of the output tube. When the tone control is in its extreme counter-clockwise position the resistance of R27 is a minimum, making capacitor C62 most effective, and switch S6 remains closed, connecting capacitor

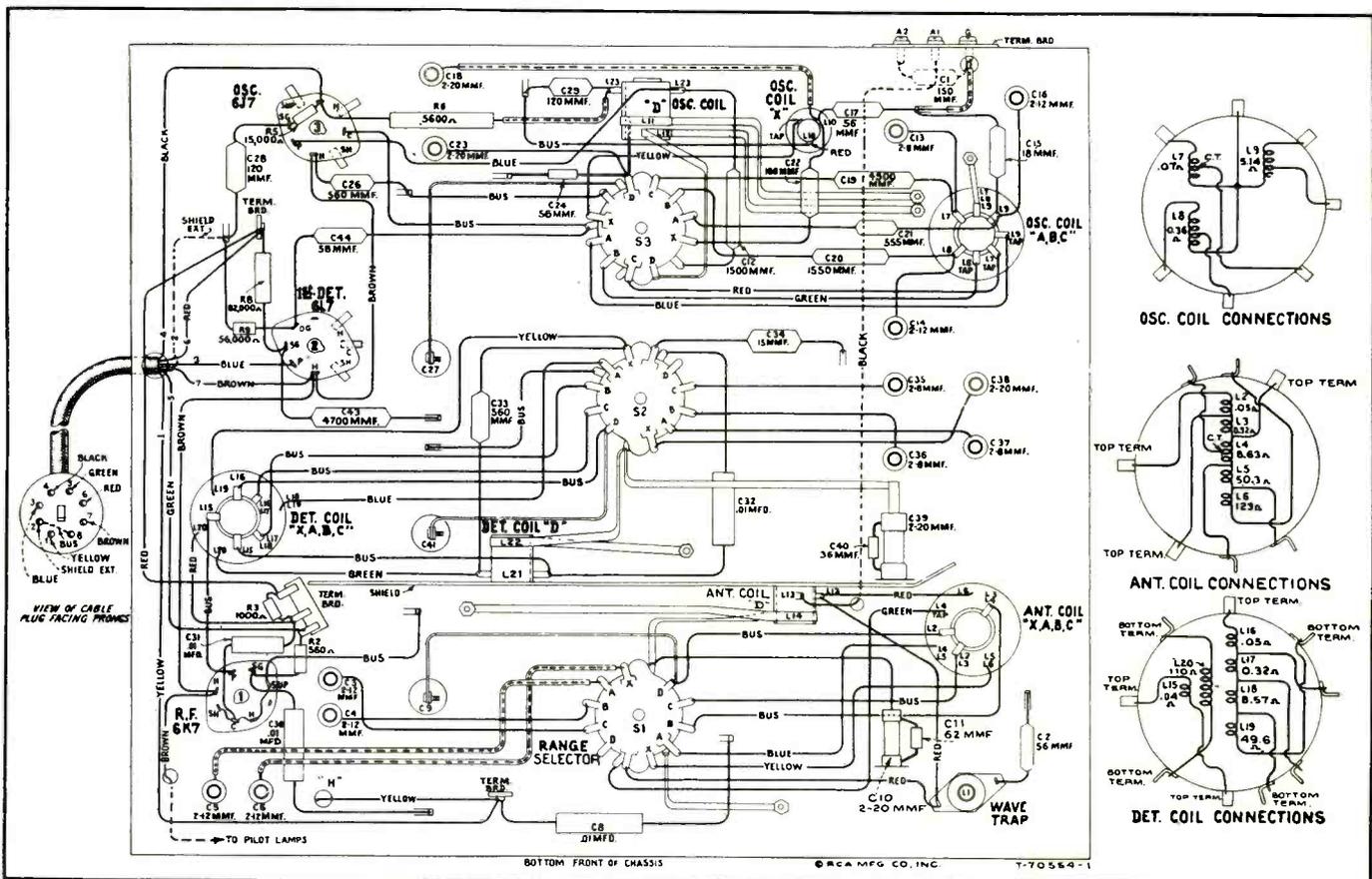


Fig. 3. "Magic Brain" wiring diagram.

A Natural FOR "772" OWNERS!

Your Model

"772"

fits here — in this light-weight, solid-wood combination carrying case with real luggage handle... along with —

**A Companion TUBE CHECKER
EQUALLY OUTSTANDING!**

This New Model

"773"

Tube Checker which matches your "772" ... giving you a complete, modern, servicing combination.

Simply mount your Model "772" Analyzer in this handsome, combination carrying case along with the matched Model "773" Tube Checker, and you have the most modern, up-to-the-minute servicing unit available. Model "773" represents the last word in tube checkers ... in design ... in operating characteristics ... in simplicity and dependability! But if you don't own Model "772"... purchase the *complete* unit (Model "775" SERVISSET). Be set for better business in the active season ahead ... be able to service sound movies, P.A. systems, electronic circuits and television, as well as all receivers. Have a servicing unit that will enable you to get the profits from *all* these sources ... and one that will remain serviceable and dependable for years to come. Be sure to get complete information. Return the coupon.

Remember ...
WESTON Instruments can be purchased under the WESTON INVESTMENT PLAN.



Model "773" also is available for counter use in this striking, polished, solid-wood case. Note the new WESTON Rotator-Type Tube Chart. You "spot" your tube instantly. Charts easily replaceable.



Here is Model "773" Tube Checker in the polished, solid-wood, individual carrying case. Send coupon for full details.

WESTON
ELECTRICAL
INSTRUMENT
CORPORATION
604 Frelinghuysen Avenue,
Newark, New Jersey
Send data on Models 773,
and 775 combination.

NAME

ADDRESS

CITY..... STATE.....

GENERAL DATA—continued

C79 across the plate circuit, providing maximum attenuation of the higher audio frequencies. As the control is turned clockwise, placing more resistance in series with capacitor C62, this capacitor becomes less and less effective and the upper frequency range of the audio amplifier is extended. When the tone control nears its extreme clockwise position, resistor R27 and switch S6 open, removing capacitors C62 and C79 respectively from the audio circuit, thereby increasing the higher audio frequency range of the system.

PHONOGRAPH CIRCUIT

The electrical impulses generated in the pickup coil L42 are boosted in the input transformer T3 before they are fed to the input grid of the 6F5 audio voltage-amplifier tube through the acoustically tapered phonograph volume control R39. The phonograph volume control also functions as a radio-phono transfer switch (see schematic diagram, Fig. 1). In the extreme counter-clockwise (radio) position, switch S8 is closed, completing the cathode circuit of the 6K7 i-f amplifier tube, and the movable arm "X" (which is connected to the input grid of the 6F5 through coupling capacitor C84) contacts lug "Y" (which is connected to the movable arm of the radio volume control R20), permitting normal radio reception. As the phonograph control is rotated clockwise, switch S8 is immediately opened (opening the i-f cathode circuit and making the i-f amplifier inoperative), and the movable arm "X" slides over the tapped resistance strip, thereby functioning as a phonograph volume control. A compensation filter is placed in shunt with the output of transformer T3 to correct the frequency response of the reproducing system so as to compensate for the recording characteristic.

AUTOMATIC RECORD CHANGER

An improved automatic mechanism, employing a synchronous motor, is used in these models. It is of the record ejector type, having a record capacity of seven for the 10-in type, and a capacity of six for the 12-in type. The turntable speed is fixed at 78 rpm by the design of the drive motor and the intermediate gear mechanism. This speed does not vary as long as the supply line frequency remains constant. The instrument may be purchased with any one of several ratings. It is very important that a machine of any particular rating be operated only at the voltage and frequency for which it is designed and rated. Attempts to oper-

ate on other voltages or frequencies will result in improper reproduction from the phonograph system and possible damage to the equipment. The ejecting mechanism is arranged so that it will trip on various types of records. This is obtained by having a trip mechanism which is actuated by the rate of needle acceleration toward the center of the record.

"MAGIC EYE"

A 6E5 cathode-ray tuning tube is used as a means of visually indicating when the receiver is accurately tuned to the incoming signal. This tube consists of an amplifier section and a cathode-ray section built in the same glass envelope. A portion of the signal voltage developed across resistor R13 is used to actuate the grid of the amplifier section. Maximum voltage is applied to this grid when the receiver is tuned to resonance with an incoming carrier. This condition is evidenced by the minimum width of the dark sector on the fluorescent screen.

"MAGIC VOICE"

These instruments are designed with cabinets incorporating the "Magic Voice." This is accomplished by having the rear of the speaker compartment completely enclosed by a tight-fitting back.

Five metal open-end pipes of equal diameter but of three different lengths are inserted in holes in the cabinet base and extend upward in the speaker compartment. The effect is to cause the lower-frequency waves, reaching the front of the cabinet through the pipes, to arrive approximately in-phase with the sound waves emitted from the front of the speaker, giving extended low-frequency response without boominess, or cabinet resonance.

ALIGNMENT PROCEDURE

The various diagrams contain such

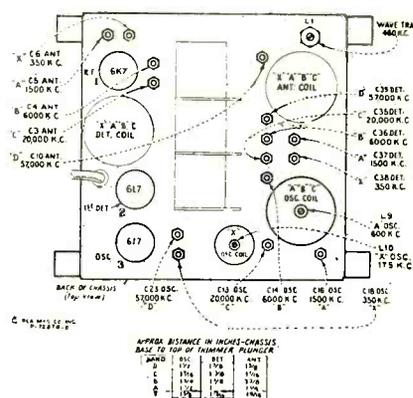


Fig. 4. "Magic Brain" trimmer locations.

information as will be needed to locate causes for defective operation if such develops. The values of the various resistors, capacitors, coils, etc., are indicated adjacent to the symbols signifying these parts on the diagram. Identification titles, such as C1, L2, R1, etc., are provided for reference between the illustrations. The coils, reactors, and transformer windings are rated in terms of their d-c resistance only. Resistance values of less than one ohm are generally omitted.

There are seventeen adjustments required for the alignment of the oscillator, first-detector, and antenna-tuned circuits; one adjustment for the wave-trap; and four adjustments for the i-f system. Fifteen of these adjustments are made with plunger-type air trimming capacitors and require the use of an (RCA stock No. 12636) adjusting tool. Each of these capacitors has a lock nut for securing the plunger in place after adjustment. The remaining seven adjustments are made by means of screws attached to molded magnetite cores. These cores change the inductance of the particular coils in which they are inserted to provide exact alignment. Loss of sensitivity, improper tone quality, and poor selectivity are the usual indications of improper alignment. Such conditions will usually exist simultaneously.

The extensive frequency range of this receiver necessitates a more or less involved method of alignment. However, if the following directions are carefully applied in the sequence given, normal performance of the instrument will be obtained.

The plunger-type air trimming capacitors have their approximate plunger settings tabulated on Fig. 4. If the plungers have been disturbed from their original adjustments, they may be roughly set to the specified dimensions prior to alignment.

In performing services on the "Magic Brain," the leads should be restored to their original positions, since the lead-dress is important for proper operation and dial calibration.

PRECAUTIONARY DRESSING OF LEADS FOR "MAGIC BRAIN" ALIGNMENT

Band X:

(1) Keep blue lead A of S1 to antenna coil L4-5 dressed away from chassis, and from yellow lead X of S1 to antenna coil L5-6.

(2) Bus lead from C10 to S1 should be as short as possible.

(3) Keep blue lead A of S2 to detector coil L18-19 clear of chassis, coil shield, coil, and other leads.

THE PIONEER MANUFACTURERS OF QUALITY CRYSTAL DEVICES

CRYSTAL MICROPHONES WITH TWO NEW FEATURES



A microphone for every purpose of amateur, public address or studio—with the special Astatic Plug and Socket Connector which permits instant interchange of microphones on the same cable or the use of several lengths of cable on the same microphone. PLUS the new Astatic Spring Cable Protector which prevents cable breakage at mounting.

**SEE YOUR
ASTATIC
JOBBER**

THE NEW TRU-TAN QUALITY CRYSTAL PICKUP

Featuring the exclusive Astatic Offset Head Design which, by holding needle practically true to tangent throughout playing surface of recording, insures finer life-like reproduction and longer record service. In two models: B-10 for recordings up to 12 inches and B-16 for lateral recordings of all sizes.




Licensed under
Patents of Brush
Development Co.

ASTATIC MICROPHONE LABORATORY, INC., DEPT. S, YOUNGSTOWN, OHIO, U. S. A.

SEE US AT BOOTH 118—NATIONAL RADIO TRADE SHOW


YOU'LL DO BETTER with MUTER PARTS

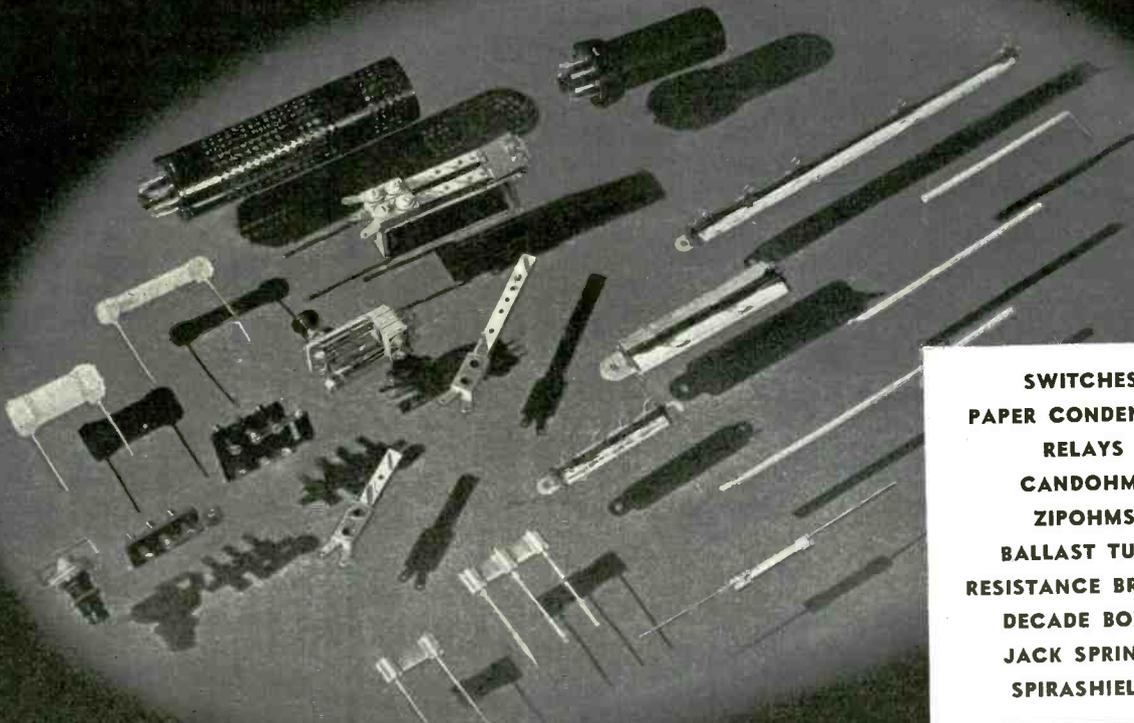

SWITCHES
PAPER CONDENSERS
RELAYS
CANDOHMS
ZIPOHMS
BALLAST TUBES
RESISTANCE BRIDGES
DECADE BOXES
JACK SPRINGS
SPIRASHIELDS

THE MUTER COMPANY

1255 S. MICHIGAN AVE.
CHICAGO • ILLINOIS

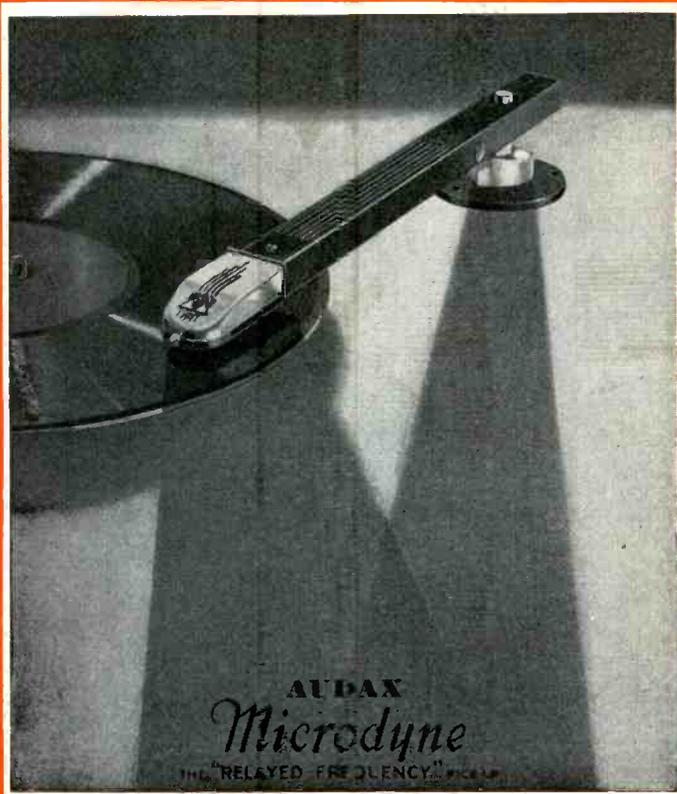

***"The Standard by Which Others
Are Judged and Valued"***

When MICRODYNE'S astonishing *facsimile* performance was first demonstrated, skeptical sound experts exclaimed, "That's THE answer to the wide-range problem!" Throughout the industry spreads the fame of this inspired reproducing system that makes recording-microphone fidelity at the pick-up an accomplished fact. Not since pick-ups became commercial in 1926 has there been so startling an evolution. *Look to a leader for leadership!*

\$9.50 to \$350.00 LIST

A pick-up for every need from the humblest midget to the most exacting transcription requirement . . . and each AUDA model delivers wider range, truer fidelity and greater stability than you can secure elsewhere at the price.

Write for your copy of "PICK-UP FACTS".

AUDA COMPANY

500 Fifth Avenue


New York

"Creators of High Grade Electrical and Acoustical Apparatus since 1915"

ON THE JOB

Excessive Hum

In many receivers the filter choke or speaker field, as the case may be, is connected in the negative return of the high-voltage supply. In such circuits leakage between the two plates of the electrolytic condenser may occur where the filters are in a common container with a common positive lead as shown in the accompanying illustration. The possibility for this leakage increases directly with the magnitude of the voltage drop across the choke and, of course, depends upon the insulation

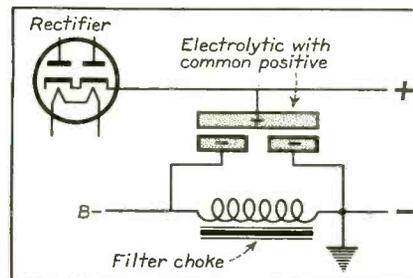

used between the two sections. Because of this latter reason small a-c, d-c sets are usually the worst offenders. In these because of attempts to save space and costs the insulation is cut to a minimum.

The condition will be eliminated if two individual condensers are substituted for the dual unit. Where price is a consideration, a single unit may be used for the second condenser and the two negative connections on the original filter connected together for use as the first condenser (across the rectifier).

Harold C. Dow

Auto-Antenna Capacities


Many of the 1937 auto-radio receivers have provision for adjusting the antenna input circuit for proper matching with most of the numerous types of antennas available. For this reason it is desirable for the Service Man to know the approximate capacities of the various antennas.

The metal insert roof antenna used in the 1936 Chrysler, Dodge and DeSoto cars has an approximate capacity of 1,500 mmfd. The capacity of a typical running board antenna is about 200 mmfd. Wire-mesh roof antennas (In cars having a non-metallic top) vary in capacity from about 175 to 225 mmfd. Fishpole antennas have an approximate capacity of 70 mmfd and over the roof types average about 90 mmfd.

EVEN IF NEXT YEAR'S TUBES LOOK LIKE THIS
THE NEW

SUPREME

502
WILL TEST THEM!

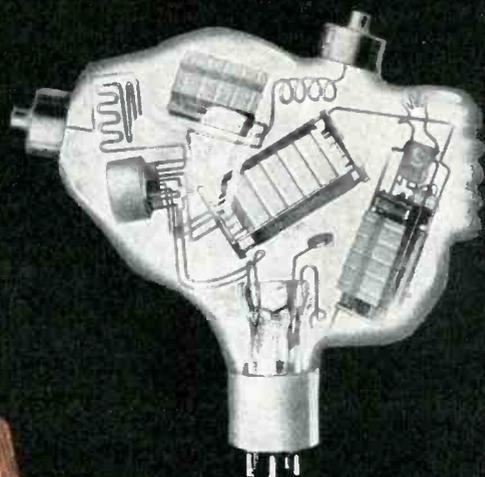

ONLY \$49.95
\$5.50 DOWN
\$4.95 FOR 10 MONTHS

FEATURING:

- 1 Tube testing circuit uses exclusive "Floating Filament" return selector circuit which deals old man "obsolescence" a knockout blow. It will test any 4, 5, 6, 7 or 8 prong tube regardless of whether the filament terminates on the regular two pin terminations or not. It could even test any future tube with one of the filament connections terminating on a "top cap"!
- 2 Supreme Square meter with large easily read scales and 1 m. a. movement (1000 ohms per volt).
- 3 New tube testing circuit which is easier to operate and more accurate than ever before. Sells more tubes. Results shown on English reading "Good Tube—Bad Tube" scale.
- 4 Tests all elements for opens; tests shorts and leakages between any two elements, all while the tube is HOT and on neon bulb.
- 5 Simple tube testing system requires minimum controls, maximum saving of time and more profit to you.
- 6 Primary Volts adjuster using tapped transformer, the most accurate line voltage adjustment method.
- 7 Extra multimeter ranges too! A combination tube checker and multimeter—just the instrument to carry on service calls.
- 8 Four A. C. Voltage ranges of 0/7/140/350/1400 volts.
- 9 Four D. C. Voltage ranges of 0/7/140/350/1400 volts.
- 10 Three Ohmmeter ranges—0 200/2000/20,000 ohms.
- 11 Two Megohms ranges—2/2 megs, 0/20 megs.
- 12 Electrolytic Filter Capacitor leakage test on "Good-Bad" English reading scale.
- 13 Electrostatic Capacitor leakage test on neon bulb.
- 14 Four Output measuring ranges, 0/7/140/350/1400 A. C. volts.
- 15 Nineteen multimeter ranges and functions besides the best tube tester design ever offered the serviceman.
- 16 Only six sockets test all tubes. No question as to which is the proper socket to use.
- 17 Panel only 13½ inches by 9 inches of Beautiful Antique Bronze.
- 18 Golden Oak Carrying Case.
- 19 Low ohms 0/200 ohm range has center scale reading of only 3.5 ohms! Just the unit to accurately measure voice coil and R. F. coil resistances, first division on this range is 0.1 ohms!

SOLD ON SUPREME S. I. C. TERMS—THE WORLD'S EASIEST INSTALLMENT TERMS!

SUPREME INSTRUMENTS CORP.
GREENWOOD MISSISSIPPI

GENERAL DATA—continued

follow using the frequency modulator. Shift the oscillograph "Timing" switch to "Ext." Insert plug of frequency-modulator cable in test-oscillator jack. Turn the test-oscillator modulation switch to "Off." Turn on the frequency modulator and place its sweep-range switch to "Hi."

(e) Increase the frequency of the test oscillator by slowly turning its tuning control until two separate, distinct, and similar waves appear on the screen. If only one wave appears, increase the "Freq." control on the oscillograph to obtain two waves. These waves will be identical in shape, totally disconnected, and appear in reversed positions. They will have a common base line, which is discontinuous. Adjust the "Freq." and "Sync." controls of the oscillograph to make them remain motionless on the screen. Continue increasing the test-oscillator frequency until these forward and reverse curves move together and overlap, with their highest points exactly coincident.

(f) With the images established as in (e), re-adjust the two magnetite core screws L27 and L26 on the second i-f transformer so that they cause the curves on the oscillograph screen to become exactly coincident throughout their lengths and have maximum amplitude.

(g) Without altering the adjustments of the apparatus, shift the "Ant." output of the test oscillator to the input of the i-f system, i.e., to the 6L7 first-detector grid cap, through a 0.001-mfd capacitor (with grid lead in place). Regulate the test-oscillator output so that the amplitude of the oscillographic image is approximately the same as used for adjustment (f) above.

(h) The two first i-f transformer magnetite core screws L25 and L24 (one on top and one on bottom) should then be adjusted so that they cause the forward and reverse curves to become coincident throughout their lengths and have maximum amplitude. The composite wave obtained in this manner represents the resonance characteristic of the total i-f system. Lack of symmetry or irregularity of the resultant image will indicate the presence of a defect in the i-f system.

R-F ADJUSTMENTS

Alignment must be made in sequence of wave-trap, ultra-short-wave band, short-wave band, medium-wave band, standard-broadcast band, and long-wave band.

Wave-Trap Adjustment:

(a) Connect output of test oscillator

to antenna terminal "A1" through a 200-mmfd (important) capacitor. Remove the plug of the frequency-modulator cable from the test-oscillator jack. Turn test-oscillator modulation switch to "On." Shift the oscillograph "Timing" switch to "Int." Place receiver range selector in standard-broadcast position. Set the receiver dial to a position of no extraneous signals near 600 kc. Tune the test oscillator to 460 kc. Adjust the wave-trap magnetite core screw to the point which causes minimum amplitude of output (maximum suppression of signal) as shown by the waves on the oscillograph. An increase of the test-oscillator output may be necessary before this point of minimum amplitude, obtained by correct adjustment of wave-trap screw, becomes apparent on oscillograph screen.

Ultra-Short-Wave Band:

(b) Connect "Ant." output of test oscillator to antenna terminal "A1" of the receiver through a 300-ohm resistor. Set the receiver range selector to its ultra-short-wave position and its dial pointer to 57,000 kc. Adjust the test oscillator to 19,000 kc. The 3d harmonic of 19,000 kc is used for this adjustment. If the indication on the oscillograph screen is not sufficient for the following adjustments at 57,000 kc, the vertical-input terminals of the cathode-ray oscillograph may be connected thus: "Hi" to the plate contact of the 6L6 power-output tube socket with the "0" terminal to chassis-ground. The receiver should be turned off while making this connection since the plate potential is impressed across the oscillograph input and a severe shock will result if contact is made between these two points. If this connection is made, advance the receiver volume control to its maximum

position. Adjust oscillator air-trimmer C23 for maximum (peak) output. Two positions, each producing maximum output, may be found. The position of minimum capacitance (plunger near out) should be used. This places the receiver heterodyne oscillator 460 kc higher in frequency than the incoming signal. Tighten lock nut. Adjust the detector air-trimmer C39, while slightly rocking the gang tuning condenser back and forth through the signal, for maximum (peak) output. Two peaks may be found on this trimmer. The peak of maximum capacitance (plunger near in) should be used. Tighten lock nut. Adjust the antenna air-trimmer C10 for maximum (peak) output while slightly rocking the gang tuning condenser back and forth through the signal. Two peaks may be found on this trimmer which produce maximum output. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Check the image frequency by changing the receiver dial setting to 56,080 kc. If the image signal is received at this position, the adjustment of the oscillator air-trimmer C23 has been correctly made. No adjustments should be made while checking for the image signal.

(c) Retune receiver for maximum response to 57,000 kc (not image response) without disturbing test oscillator adjustments. Change test oscillator to 6,800-14,000 kc range. Tune test oscillator until signal is heard in speaker. Two test-oscillator settings (230 kc apart) will produce a signal at this point. The lower frequency test-oscillator setting should be used, as this places the test oscillator harmonic 460 kc below the frequency of the receiver heterodyne oscillator.

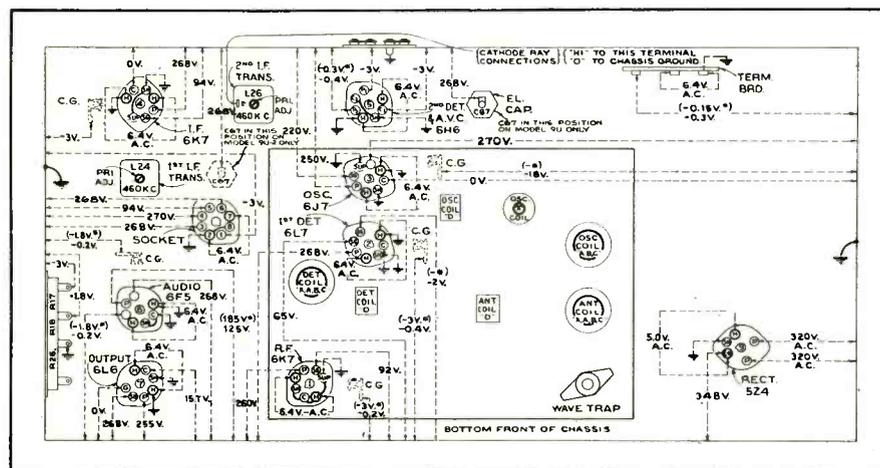


Fig. 6. Underchassis view with voltage measurements for various terminals indicated.

GENERAL DATA—continued

Tune receiver for maximum response at a dial setting of approximately 28,500 kc (image should tune in at a dial setting approximately 27,580 kc) without altering test-oscillator adjustment. Test-oscillator second harmonic of 14,250 kc is used for the following check. Check calibration of receiver dial. A receiver-dial reading of less than 28,500 kc indicates that the inductance of the oscillator secondary coil L11 is too low and should be increased. If the receiver dial reading is greater than 28,500 kc, the inductance of L11 is too high and should be decreased. If it is necessary to change the inductance of L11, first remove bottom cover of "Magic Brain" and then set receiver dial pointer to 28,500 kc. To decrease inductance, move the grounded ends (straps) of L11 and L12 (see Fig. 3) nearer chassis. Do not allow straps to touch chassis except where connected. To increase inductance, move the straps farther away from chassis. Adjust position of straps until maximum (peak) output results. The alignment of the detector tuned circuit should next be checked at 28,500 kc without changing either the receiver or test-oscillator adjustments. An increase of output when the brass end of a tuning wand is brought near L22 indicates that L22 is too high in inductance, while an increase when the iron end is brought near the coil indicates that the inductance is too low. The inductance of L22 may be varied by changing the spacing between the grounded end (strap) of L22 and the strap connected from C41 to contact on S2 (Fig. 3). Adjust the spacing until maximum (peak) output results. Replace "Magic Brain" bottom cover and repeat adjustments in (b) prior to those of short-wave band.

Short-Wave Band:

(d) Set the receiver range selector to its short-wave position and its dial pointer to 20,000 kc. Adjust the test oscillator to 20,000 kc. Adjust oscillator air trimmer C13 until maximum (peak) output is reached. Two peaks may be found with this circuit. The peak with minimum capacitance (plunger near out) should be used. Tighten lock nut. Adjust detector air-trimmer C35 until maximum (peak) output is reached, while slightly rocking the gang tuning condensers back and forth through the signal. Two peaks may be found with this circuit. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Adjust antenna air-trimmer C3 until maximum (peak) output is reached while slightly

rocking the gang tuning condenser back and forth through the signal. Two peaks may be found with this circuit. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Check the image frequency by changing the receiver dial setting to 19,080 kc. The image signal should be received at this position indicating that the adjustment of C13 has been correctly made. No adjustments should be made while checking for the image signal.

Medium-Wave Band:

(e) Place receiver range selector to its medium-wave position with its dial pointer set to 6,000 kc. Tune the test oscillator to 6,000 kc. Adjust oscillator air-trimmer C14 to produce maximum (peak) output as shown by the waves on the oscillograph. Two peaks may be found with this circuit. The peak with minimum capacitance (plunger near out) should be used. Tighten lock nut. Adjust the detector air-trimmer C36 for maximum (peak) output while slightly rocking the gang tuning condenser back and forth through the signal. Two peaks may be found with this circuit. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Adjust antenna air-trimmer C4 to produce maximum (peak) output. Tighten lock nut.

Standard-Broadcast Band:

(f) Remove the 300-ohm resistor from between the test-oscillator "Ant." post and receiver antenna terminal "A1" and insert a 200-mmfd capacitor in its place. Place receiver range selector to standard-broadcast position with receiver dial pointer set to 600 kc. Tune the test oscillator to 600 kc. Adjust oscillator magnetite core screw L9 (top of large oscillator coil can) for maximum (peak) output as shown by the waves on the oscillograph screen.

(g) Set receiver dial pointer to 1,500 kc. Tune test oscillator to 1,500 kc (1,500-3,100-kc range) and increase its output to produce a registration on the oscillograph screen. Carefully adjust the oscillator, detector, and antenna air-trimmers C16, C37 and C5, respectively, to produce maximum (peak) output as shown by the waves on the oscillograph screen. Shift the oscillograph "Timing" switch to "Ext." Place the frequency modulator sweep-range switch to its "Lo" position and insert plug of the frequency-modulator cable in test-oscillator jack. Turn test-oscillator modulation switch to "Off." Retune the test oscillator (increase frequency) un-

til the forward and reverse waves show on the oscillograph screen and become coincident at their highest points. This will occur at a test-oscillator setting of approximately 1,680 kc. Adjust trimmers C16, C37, and C5 again, setting each to the point which produces the best coincidence and maximum amplitude of the images.


(h) Remove the plug of the frequency-modulator cable from the test-oscillator jack. Turn test-oscillator modulation switch to "On." Set oscillograph "Timing" switch to "Int." Tune test oscillator to 200 kc (200-400 kc range). Tune receiver for maximum response to this signal at a dial reading of approximately 600 kc. The third harmonic of the 200-kc signal is used for this adjustment. Shift oscillograph "Timing" switch to "Ext." Insert the plug of the frequency modulator cable in test-oscillator jack. Turn test-oscillator modulation switch to "Off." Retune the test oscillator (increase frequency) until the forward and reverse waves show on the oscillograph screen. This will occur at a test-oscillator setting of approximately 230 kc. Disregarding the fact that the two traces may or may not come together, adjust the oscillator magnetite-core screw L9 (top of large oscillator coil can) to produce maximum (peak) amplitude of the traces. Shift the oscillograph "Timing" switch to "Int." Remove the plug of the frequency-modulator cable from the test-oscillator jack. Turn the test-oscillator modulation switch to "On." Repeat adjustments in (g) above to compensate for any changes caused by the adjustment of L9 core, tightening lock nuts on C16, C37, and C5, respectively, after each is adjusted.

Long-Wave Band:

(i) Shift the oscillograph "Timing" switch to "Int." Remove the plug of the frequency-modulator cable from the test-oscillator jack. Turn the test-oscillator modulation switch to "on." Place receiver range selector to its long-wave position. Set the receiver dial pointer to 175 kc. Tune the test oscillator to 175 kc and increase its output until a deflection is noticeable on the oscillograph screen. Adjust oscillator magnetite-core screw L10 (located on top of small oscillator coil can) so that maximum (peak) amplitude of output is shown on the oscillograph screen.

(j) Set receiver dial pointer to 350 kc. Tune test oscillator to 350 kc. Adjust the oscillator, detector, and antenna air-trimmers C18, C38, and C6 to pro-

Wherever You Go..

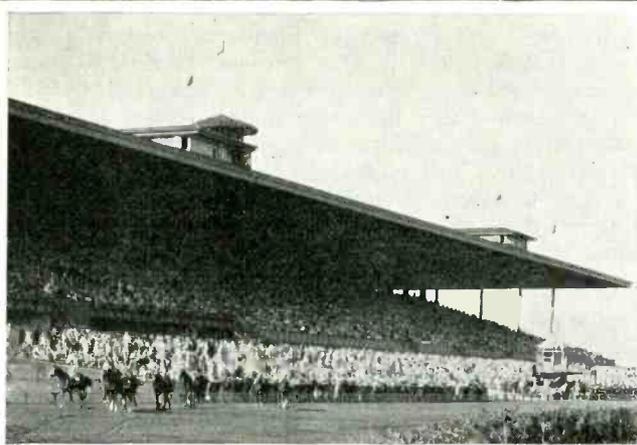

WASHINGTON PARK

WHILE AT THE CHICAGO TRADE SHOW

- SOUTH SHORE COUNTRY CLUB
- OLD HEIDELBERG
- COLLEGE INN of the Sherman
- WALNUT ROOM of the Bismarck
- WRIGLEY FIELD
- WBBM AIR THEATER—Key Station of the Columbia Broadcasting System
- CHICAGO PARKS—Outdoor Programs

Your Pleasure will be greater because an

ELECTRO · ACOUSTIC

HIGH FIDELITY SYSTEM WITH MAGNAVOX SPEAKERS is a permanent feature at these outstanding spots.

DON'T FORGET—get a "close-up" of the latest in sound equipment . . .

BOOTHS 15 - 16 - 17 AT THE STEVENS

ELECTRO ACOUSTIC PRODUCTS COMPANY
 SUBSIDIARY OF THE MAGNAVOX COMPANY
FORT WAYNE, IND.
 EXPORT SALES DIVISION • 330 SOUTH WELLS ST. CHICAGO, ILL.
 CABLE ADDRESS • EAPCOMPY, U.S.A.



Worth Looking Into

The Tung-Sol Radio Tube dealer is assured every aid and protection which modern sales engineering can devise. All these advantages are gathered together in the TUNG-SOL CONSIGNMENT PLAN which is endorsed by 8000 retail agents.

Naturally, a proposition so attractive must be limited. Yet there are still desirable locations to be allotted to dealers who have the necessary qualifications. Write for name of your nearest Tung-Sol wholesaler.

TUNG-SOL

Tone-flow radio Tubes

TUNG-SOL LAMP WORKS, INC.
 Radio Tube Division

Sales Offices: Atlanta, Boston, Charlotte, Chicago, Dallas, Detroit, Kansas City, Los Angeles, New York. General Office: Newark, N. J.

duce maximum (peak) output as shown by the waves on the oscillograph screen. Without disturbing the connections, shift the oscillograph "Timing" switch to "Ext." Place the frequency-modulator sweep-range switch to its "Hi" position and insert plug of frequency-modulator cable in test-oscillator jack. Turn test-oscillator modulation switch to "Off." Return the test oscillator (decrease frequency) until the forward and reverse waves show on the oscillograph screen and become coincident at their highest points. This setting places the test-oscillator frequency to 175 kc. The second harmonic is now used for the 350 kc adjustment. Adjust air-trimmers C18, C38, and C6, again, to produce maximum amplitude of the images and best coincidence throughout their lengths.

(k) Retune the receiver to approximately 175 kc so that the forward and reverse waves appear on the oscillograph screen. Adjust the oscillator magnetite core screw L10 to produce maximum (peak) amplitude of the waves, disregarding the fact that the two traces may or may not come together.

(l) Shift the receiver dial setting to 350 kc without altering any other adjustments (frequency modulator still in operation). Adjust air-trimmers C18, C38, and C6, respectively, to produce maximum amplitude and best coincidence of the waves. These adjustments compensate for any changes caused by the adjustment of the magnetite core screw L10. Tighten lock nuts on C18, C38, and C6, respectively, after each is adjusted.

OUTPUT INDICATOR ALIGNMENT

Attach the output indicator across the loudspeaker voice-coil circuit. Advance the receiver volume control to its maximum position, letting it remain in such position for all adjustments. For each adjusting operation, regulate the test-oscillator output so that the signal level is as low as possible and still be observable at the receiver output. Use of such small signal will obviate broadness of tuning which would otherwise result from AVC action on a stronger one.

I-F ADJUSTMENTS

(a) Connect the "Ant." output of the test oscillator to the grid cap of the 6L7 first detector tube (with grid lead in place) through a 0.001-mfd capacitor, with "Gnd." to receiver chassis. Tune the test oscillator to 460 kc. Place its modulation switch to "On" and its output switch to "Hi."

(b) Adjust the two magnetite core

screws of the second i-f transformer (one on top and one on bottom) to produce maximum (peak) output.

(c) The two first i-f transformer magnetite core screws (one on top and one on bottom) should be adjusted to produce maximum (peak) output. It is advisable to repeat the adjustment of all i-f magnetite core screws to assure that the interaction between them has not disturbed the original adjustments.

R-F ADJUSTMENTS

Alignment must be made in sequence of wave-trap, ultra-short wave band, short-wave band, medium-wave band, standard-broadcast band, and long-wave band.

Wave-Trap Adjustment:

(a) Connect the "Ant." output of the test oscillator to the antenna terminal "A1" on the receiver through a 200-

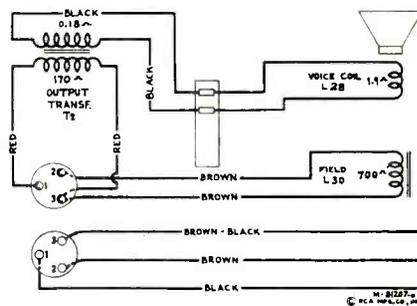


Fig. 7. RCA 9T, 9K2, 9U, 9U2 loudspeaker wiring.

mmfd (important) capacitor. Place the range selector to its standard-broadcast position and set the receiver dial pointer to a position of no extraneous signals near 600 kc. Tune the test oscillator to 460 kc. Adjust the wave-trap magnetite core screw to the point which causes minimum output (maximum suppression of signal). An increase of the test-oscillator output may be necessary before the point of minimum output, obtained by adjustment of wave-trap screw, becomes apparent on the output indicator.

Ultra-Short-Wave Band:

(b) Connect the "Ant." output of the test oscillator to the antenna terminal "A1" through a 300-ohm resistor. Set receiver range selector to its ultra-short-wave position and its dial pointer to 57,000 kc. Adjust the test oscillator to 19,000 kc. The third harmonic of 19,000 kc is used for this adjustment. Adjust the oscillator air-trimmer C23 for maximum (peak) output. Two positions for maximum output may be found. The position of minimum capacitance (plunger near out) should be

used. This places the receiver heterodyne oscillator 460 kc higher in frequency than the incoming signal. Tighten lock nut. Adjust the detector air-trimmer C39 while slightly rocking the gang tuning condenser back and forth through the signal for maximum (peak) output. Two peaks may be found on this trimmer. The peak of maximum capacitance (plunger near in) should be used. Tighten lock nut. Adjust the antenna air-trimmer C10 for maximum (peak) output while slightly rocking the gang tuning condenser back and forth through the signal. Two peaks may be found on this trimmer which produce maximum output. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Check the image frequency by changing the receiver dial setting to 56,080 kc. If the image signal is received at this position, the adjustment of the oscillator air-trimmer C23 has been correctly made. No adjustments should be made while checking for the image signal.

(c) Retune receiver for maximum response to 57,000 kc (not image response) without disturbing test-oscillator adjustments. Change test oscillator to 6,800-14,000-kc range. Tune test oscillator until signal is heard in speaker. Two test-oscillator settings (230 kc apart) will produce a signal at this point. The lower frequency test-oscillator setting should be used, as this places the test oscillator harmonic 460 kc below the frequency of the receiver heterodyne oscillator. Tune receiver for maximum response at a dial setting of approximately 28,500 kc (image should tune in at a dial setting of approximately 27,580 kc) without altering test-oscillator adjustment. Test-oscillator second harmonic of 14,250 kc is used for the following check. Check calibration of receiver dial. A receiver-dial reading of less than 28,500 kc indicates that the inductance of the oscillator secondary coil L11 is too low and should be increased. If the receiver-dial reading is greater than 28,500 kc, the inductance of L11 is too high and should be decreased. If it is necessary to change the inductance of L11, first remove bottom cover of "Magic Brain" and then set receiver dial pointer to 28,500 kc. To decrease inductance, move the grounded ends (straps) of L11 and L12 (see Fig. 3) nearer chassis. Do not allow straps to touch chassis except where connected. To increase inductance move the straps farther away from chassis. Adjust position of straps till maximum (peak) output results.

I AM AMPLIFIER 855

THE
ARISTOCRAT
OF ALL
AMPLIFIERS



THEY call me the pride of the Operadio crowd. I'm not the result of any brainstorm. Months and months of patient toil went into my designing, testing. I was tried and tried again under conditions that would test any Amp's metal.

Dealers take a look at me and say: "Boy, she's a beauty." But the thing that's most important is what's inside me, and the job I'll do out in the field. And believe me, I've never let a jobber, dealer or service man down.

I'm packed with exclusive, up-to-the-minute Operadio features such as Volume Expansion and Volume Compression (the cure for microphone feedback).

Twelve beam power tubes in the latest, most efficient type

circuit make my wheels go 'round for maximum performance. I've a four channel input. In other words, I electronically mix three microphones simultaneously with phonograph or auxiliary input.

With my electronic visual overload indicator and my electronic visual output level indicator, you can tell at a glance whether or not I'm being overloaded. And you can check the average watts output going into your speaker system. Tone balancing for both high and low frequencies is no trick for me—balancing with my new non-resonant equalizer. *With these and many more features, all I cost you, complete with tubes, is \$180.00.*

I can't give you more than the highlights, but clip and mail the coupon and you get my complete story.

MODEL 835 35-52 Watt Amplifier

This amplifier is a package of dynamite. It has more clean, undistorted watts output per cubic content than any amplifier on the market today. Can be bolted down on table or desk, mounted on a wall, or on a standard 19-inch rack.

Price, complete with Tubes . . \$120



MODEL 870 70-104 Watt Booster Amplifier

Designed specifically to be used as a booster amplifier with the Model 835 Power Amplifier. It makes available an additional 70 watts per unit, under normal rating, to the already 35 watts normal rating of the Model 835. Furnishes field for as many as four electrodynamic speakers, or may be used with A. C. type dynamic or permanent magnet dynamic speakers.

Price, complete with Tubes . . \$125



OPERADIO
MANUFACTURING COMPANY
ST. CHARLES • • • ILLINOIS

OPERADIO MANUFACTURING COMPANY Dept. 70 St. Charles, Illinois

Please send me complete information on the following:

- AMPLIFIER 855 Amplifier Booster 870
 Amplifier 835 Intercommunicating Systems
(Check mark what interests you.)

Name

Street Address

City State

Send me your NEW CATALOG NO. 12

P. A. EQUIPMENT AND SPEAKER HEADQUARTERS FOR THE NATION

GENERAL DATA—continued

The alignment of the detector-tuned circuit should next be checked at 28,500 kc without changing either the receiver or test oscillator adjustments. An increase of output when the brass end of a tuning wand is brought near L22 indicates that L22 is too high in inductance, while an increase when the iron end is brought near the coil indicates that the inductance is too low. The inductance of L22 may be varied by changing the spacing between the grounded end strap of L22 and the strap connected from C41 to the contact on S2. An increase of spacing will increase the inductance, while a decrease of spacing will decrease the inductance. Adjust the spacing until maximum (peak) output results. Replace "Magic Brain" bottom cover and repeat adjustments in (b) prior to those of short-wave band.

Short-Wave Band:

(d) Set the receiver range selector to its short-wave position and its dial pointer to 20,000 kc. Adjust the test oscillator to 20,000 kc. Adjust oscillator air-trimmer C13 until maximum (peak) output is reached. Two peaks may be found for this circuit. The peak with minimum capacity (plunger near out) should be used. Tighten lock nut. Adjust detector air-trimmer C35 until maximum (peak) output is reached, while rocking the gang tuning condenser back and forth through the signal. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Adjust antenna air-trimmer C3 until maximum output is reached, while slightly rocking the tuning condenser back and forth through the signal. Two peaks may be found

for this circuit. The peak with maximum capacity (plunger near in) should be used. Tighten lock nut. Check the image frequency by changing the receiver dial setting to 19,080 kc. The signal should be received at this position indicating that the adjustment of C13 has been correctly made. No adjustments should be made while checking for the image signal.

Medium-Wave Band:

(e) Place the receiver range selector to its medium-wave position with the receiver dial pointer set to 6000 kc. Tune the test oscillator to 6000 kc. Adjust the oscillator air-trimmer C14 to produce maximum output. Two peaks may be found with this circuit. The peak with minimum capacitance (plunger near out) should be used. Tighten lock nut. Adjust the detector air-trimmer C36 for maximum (peak) output while slightly rocking the receiver gang tuning condenser back and forth through the signal. Two peaks may be found with this circuit. The peak with maximum capacitance (plunger near in) should be used. Tighten lock nut. Adjust antenna air-trimmer C4 to produce maximum (peak) output. Tighten lock nut.

Standard Broadcast Band:

(f) Remove the 300-ohm resistor from between the test-oscillator "Ant" post and receiver antenna terminal "A1" and insert a 200-mmfd capacitor in its place. Place receiver range selector to its standard-broadcast position with the receiver dial pointer set to 600 kc. Tune the test oscillator to 600 kc. Adjust the oscillator magnetite-core screw L9 (top of large oscillator coil can) for maximum (peak) output.

(g) Set receiver dial pointer to 1,500 kc. Tune test oscillator to 1,500 kc and regulate its output until a slight indication of output is visible. Carefully adjust the oscillator, detector, and antenna air-trimmers C16, C37, and C5, respectively, to produce maximum (peak) output.

(h) Tune test oscillator to 600 kc. Tune the receiver to pick up this signal near 600 kc, disregarding the dial reading at which it is best received. Adjust oscillator magnetite core screw L9 (top of large oscillator coil can) for maximum (peak) output while slightly rocking the gang tuning condenser back and forth through the signal. Repeat adjustments in (g) above to compensate for any change caused by adjustment of L9 magnetite core screw, tightening lock nuts on C16, C37, and C5, respectively, after each is adjusted.


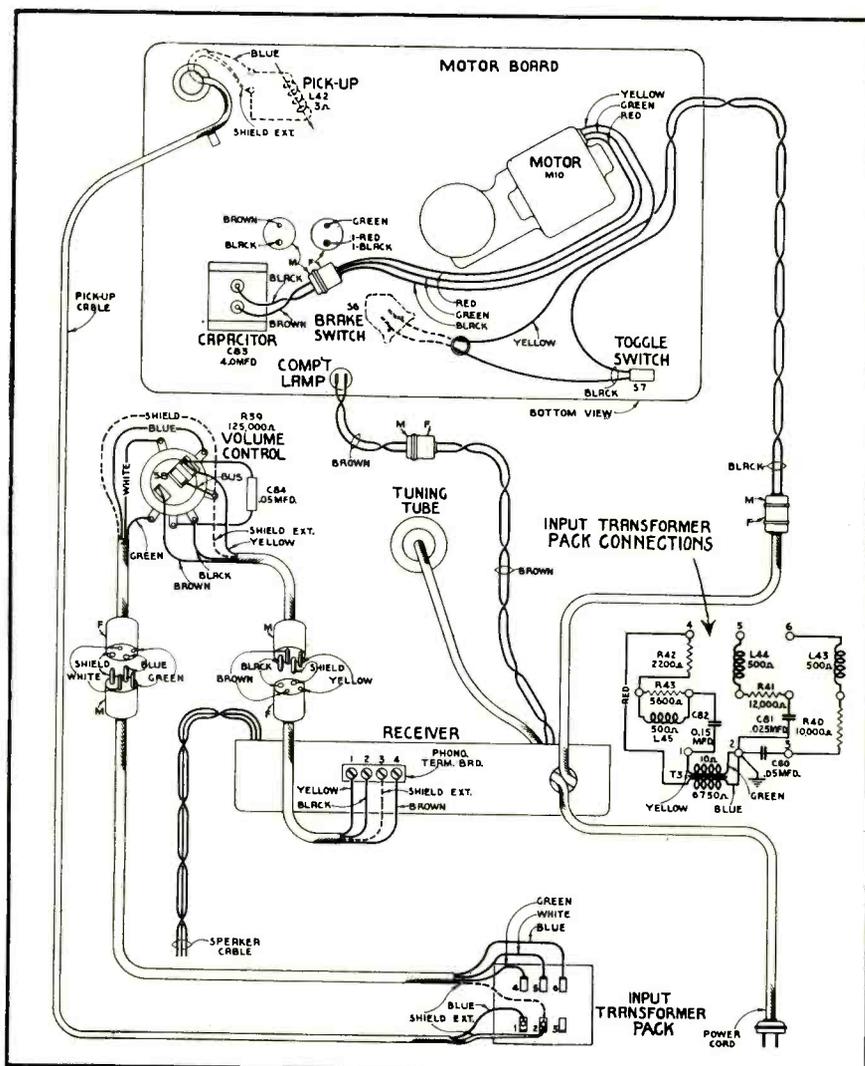


Fig. 8. Assembly wiring.

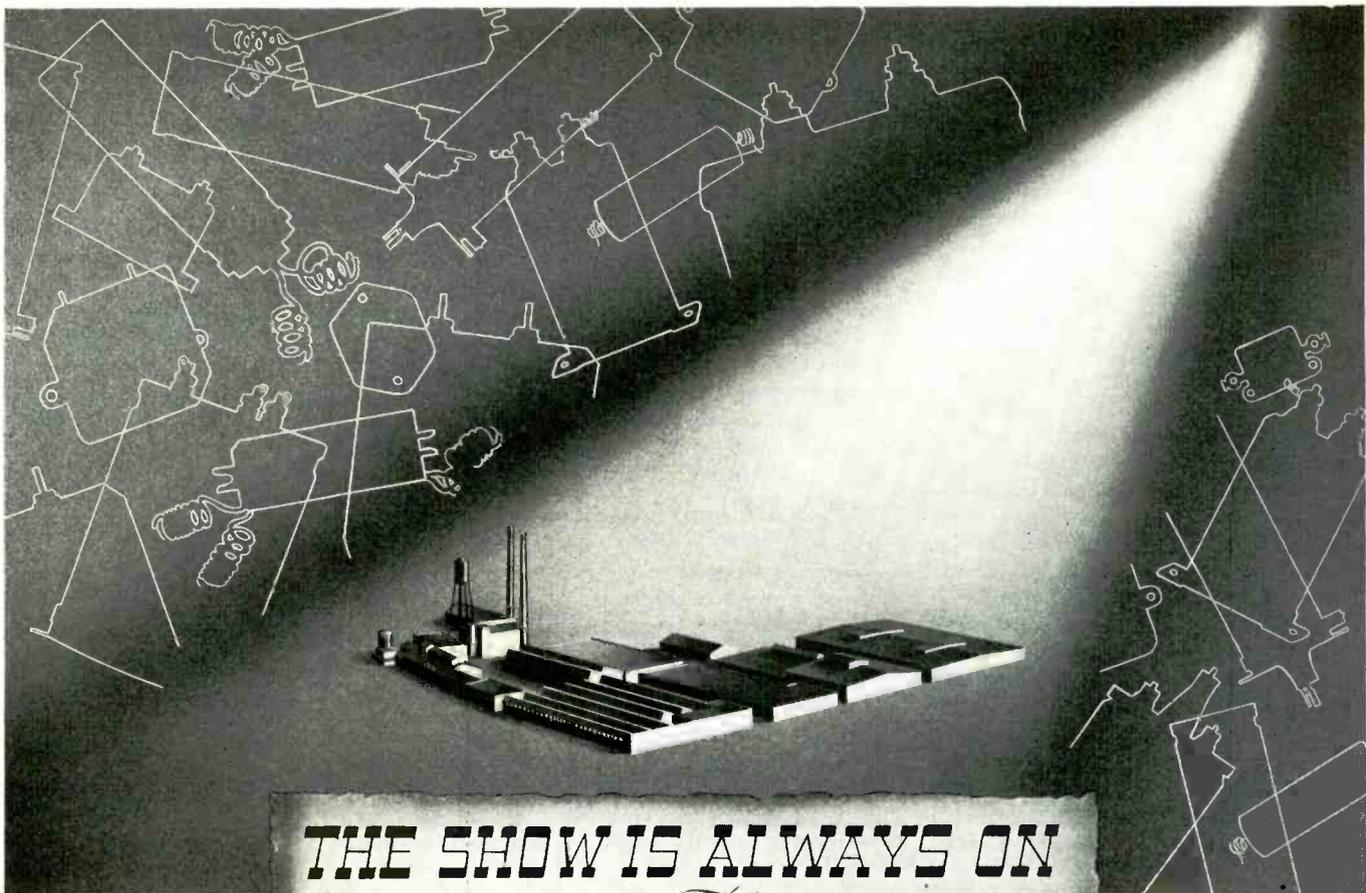

THE SHOW IS ALWAYS ON
at
CORNELL-DUBILIER

HAVING watched the opening and closing of so many Trade Shows in our 27 years, we cannot help but reminisce about the show that never ends at Cornell-Dubilier. Here at our great South Plainfield plant, the stage is always set . . . a stage covering 33 acres . . . the cast of more than 3,000 skilled workers is hard at it year in and out . . . busily engaged in the manufacture of more than 500,000 condenser units a day. It is only natural that our chest should swell with pride as we review our part in the in-

dustry. Veterans in the condenser manufacturing business that we are, we combine the wisdom of an old stage-hand with the enthusiasm of youth.

Upon this occasion, Cornell-Dubilier renews its pledge for the continuance of its policy of quality first—prompt and efficient service—and square-shooting business tactics to all.

For complete customer satisfaction and utmost profits get in on the C-D “show.” We cordially invite you to visit with us at the Chicago Convention (Booth 86).

MICA • DYKANOL • PAPER • WET AND DRY ELECTROLYTIC CAPACITORS

CORNELL-DUBILIER CORPORATION



SOUTH PLAINFIELD • NEW JERSEY

demand C-D and you demand Dependability

GENERAL DATA—continued

Long-Wave Band:

(i) Place receiver range selector to its long-wave position, with dial pointer set to 175 kc. Tune the test oscillator to 175 kc and increase its output until a slight indication of output is visible. Adjust oscillator magnetite core screw L10 (top of small oscillator coil can) for maximum (peak) output.

(j) Set receiver dial position to 350 kc. Tune test oscillator to 350 kc. Adjust the oscillator, detector, and antenna air-trimmers C18, C38, and C6, respectively, to produce maximum (peak) output.

(k) Tune test oscillator to 175 kc. Tune receiver to pick up this signal near 175 kc, disregarding the dial reading at which it is best received. Adjust oscillator magnetite core screw L10 (top of small oscillator coil can) for maximum (peak) output while slightly rocking the gang tuning condenser back and forth through the signal. Repeat adjustments in (j) above to compensate for any changes caused by the adjustment of the magnetite core screw L10. Tighten

lock nuts on C18, C38, and C6 respectively, after each is adjusted.

LOUDSPEAKER

Centering of the loudspeaker voice coil is made in the usual manner with three narrow paper feelers after first removing the front paper dust cover. This may be removed by softening its cement with a very light application of acetone using care not to allow the acetone to flow down into the air gap. The dust cover may be cemented back in place with ambroid upon completion of adjustment.

ANTENNA AND GROUND TERMINALS

These receivers are equipped with an antenna-ground terminal board having three terminals. These terminals are marked "A2," "A1" and "G," the latter being the ground terminal and should always be connected to a good external ground. The transmission-line leads of an RCA RK-40A antenna system should be connected to terminals "A2" and "A1." The receiver coupling units of the RK-40 and the Spider-Webb an-

tenna systems should be connected to terminals "A1" and "G." Connect a single-wire antenna to terminal "A1."

RESISTANCE VALUES

The resistance values shown between socket contacts, grid caps, resistors and terminals to receiver chassis or to other pertinent point on Fig. 5, were taken with the a-c supply disconnected, tubes in their respective sockets, the tuning condenser in full-mesh, range selector in the standard-broadcast position and the volume control at maximum. The use of this diagram in conjunction with the circuit diagram, Fig. 1, and wiring diagram, Fig. 3, will permit the location of certain troubles which might otherwise be difficult to ascertain. Each value as specified should hold within $\pm 20\%$. Variations in excess of this limit will usually be indicative of trouble in circuit under test.

SOCKET VOLTAGES

Note: Two voltage values are shown for some readings. The values shown in parenthesis with asterisk (*) indicates

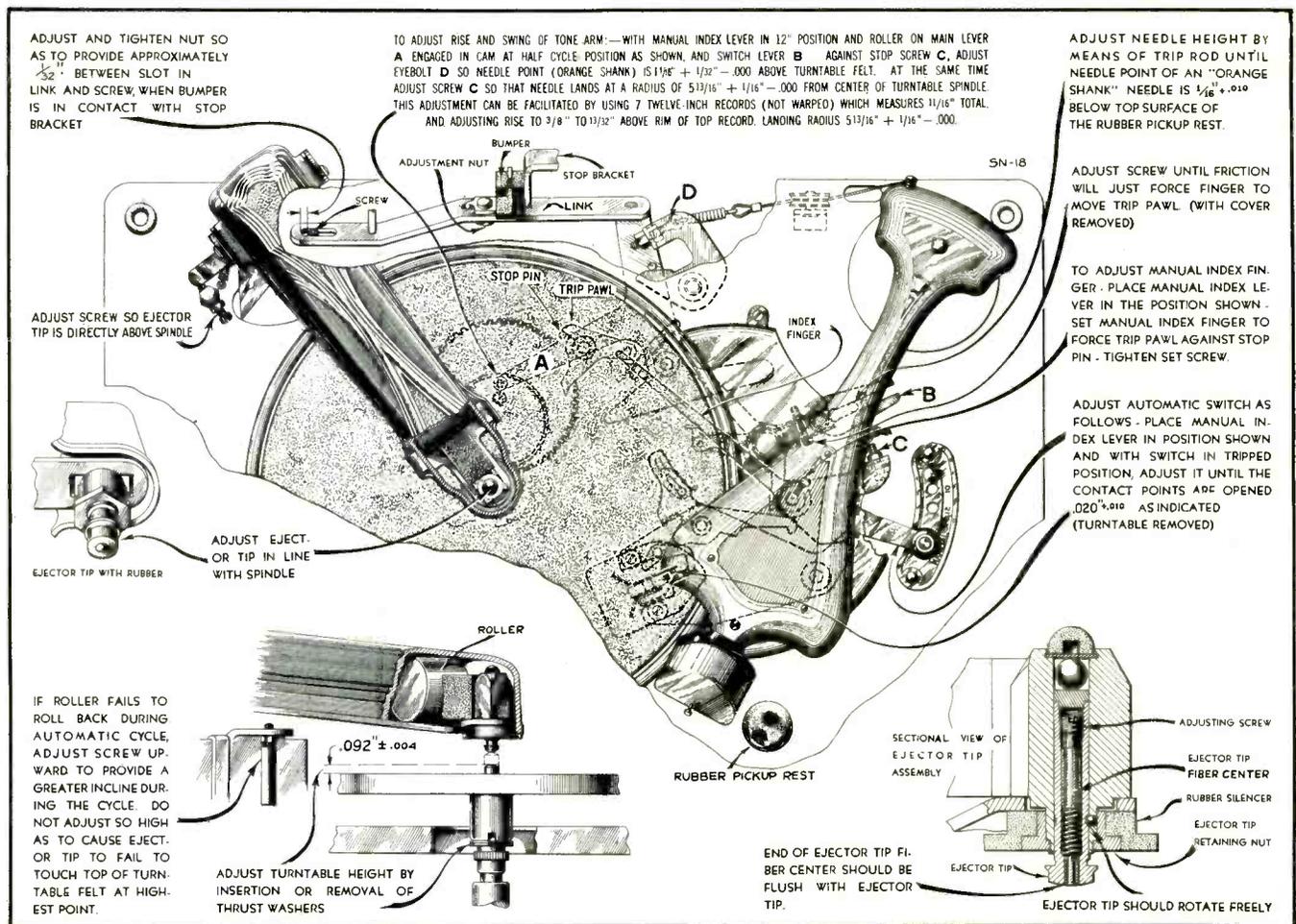


Fig. 9.—Automatic record changer adjustments.

operating conditions without voltmeter loading. The other value (generally lower) is the actual measured voltage and differs from the value shown in parenthesis because of the additional loading of the voltmeter through the high series circuit resistance.

The voltage values indicated from the socket contacts, grid caps, resistors, and terminals to receiver chassis on Fig. 6 were taken with a 115-volt line supply and the receiver tuned to approximately 1,000 kc. The antenna was shorted to the chassis and the radio volume control turned off. The phonograph volume control was also turned off during the measurements.

Each value as specified should hold within $\pm 20\%$ when the receiver is normally operative at its rated line voltage. Variations in excess of this limit will usually be indicative of trouble in the basic circuits. To duplicate the conditions under which the voltages were measured requires a 1,000-ohm-per-volt d-c meter, having ranges of 10, 50, 250,

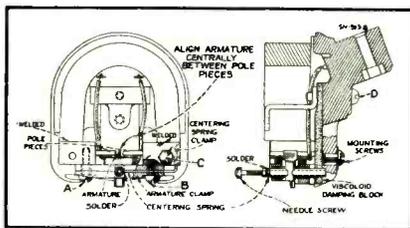


Fig. 10. Phonograph pickup details.

500, and 1,000 volts. Use the nearest range above the specified measured voltage. A-c voltages were measured with a corresponding a-c meter.

MAGNETIC PICKUP

The pickup used in the phonograph unit employs a horseshoe magnet which is rigidly welded to the pole pieces and cannot be taken apart. There is a centering spring attached to the armature to maintain proper adjustment and to provide a limiting effect on the movement of the armature. The frequency response is substantially uniform over a wide range. Service operations which may be necessary on the pickup are as follows:

CENTERING ARMATURE

Refer to Fig. 10 showing the pickup inner structure. The armature is shown in its proper relation to the magnet pole pieces, i.e., exactly centered. Whenever this centering adjustment has been disturbed, the screws A, B, and C should be loosened and the armature clamp adjusted to the point where the vertical axis of the armature is at right angles

to the horizontal axis of the pole pieces, and centered between them. This centering operation may be facilitated by inserting a small rod or nail into the armature needle hole, using it as a lever to test the angular movement of the armature. The limitations of the movement in each direction will be caused by the armature striking the pole pieces. The proper adjustment is obtained when there is equal angular displacement of the armature and adjustment rod or nail to each side of the vertical axis of the magnet and coil assembly. The screws A and B should then be secured, observing care not to disturb the adjustment of the armature clamp. Then place the pickup in a vise and secure the centering spring-clamp by means of the screw C, allowing the centering spring to remain in the position at which the armature is exactly centered between the pole pieces. With a little practice, the correct adjustment of the armature may be readily obtained. The air gap between the pole pieces and the armature should be kept free from dust, filings, and other such foreign materials which would obstruct the movement of the pickup armature.

DAMPING BLOCK

The viscoloid block which is attached to the back end of the armature shank serves as a mechanical filter to eliminate undesirable resonances and to cause the frequency response to be uniform. Should it be necessary to replace this damping block, it may be done by removing screw D and the cover support bracket from the mechanism and taking off the old viscoloid block. The surface of the armature which is in contact with the viscoloid should be thoroughly cleaned with fine emery cloth. Then insert the new block so that it occupies the same position as it did originally. Make certain that the block is in correct vertical alignment with the armature. The hole in the new viscoloid block is somewhat smaller than the diameter of the armature in order to permit a snug fit. With the viscoloid aligned on the armature, screw D and the cover support bracket should then be replaced. Heat should be applied to the armature (viscoloid side) so that the viscoloid block will fuse at the point of contact and become rigidly attached to the armature. A special-tip soldering iron constructed as shown in Fig. 11 will be found very useful in performing this operation. The iron should be applied only long enough to slightly melt the block and cause a small bulge on both sides.

REPLACING COIL

Whenever there is defective operation due to an open or shorted pickup coil, this coil should be replaced. The method of replacement will be obvious upon inspection of the pickup assembly and by study of the cut-a-way illustrations. Make sure that the new coil is properly centered with the hole in the support strip and glued securely in that position. It is important to readjust the armature as previously explained after reassembly of the mechanism. Only rosin core solder should be used for soldering the coil leads in the pickup. This same type of solder should be used when necessary for soldering the centering spring to the armature.

MAGNETIZING

Loss of magnetization will not usually occur when the pickup has received normal care because the magnet and pole pieces are one unit and the magnetic circuit remains practically closed at all times. When the pickup has been mis-

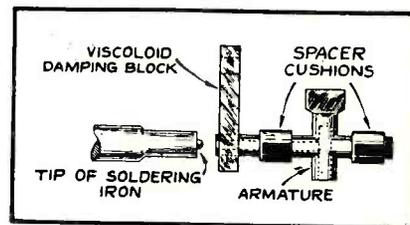


Fig. 11. Special soldering iron tip.

handled, subjected to a strong a-c field, jolted, or dropped, there may be an appreciable loss of magnetic strength, in which case it will be necessary to remagnetize the entire structure. To do this, it will be necessary to first remove the pickup mechanism from the tone arm, and then remove the magnet assembly. Place the magnet assembly on the poles of a standard pickup magnetizer such as the (RCA stock No. 9549) pickup magnetizer and charge the magnet.

AUTOMATIC RECORD EJECTOR


The record changing mechanism is designed to be simple and fool-proof. Occasionally, however, certain adjustments may be required. These adjustments are illustrated and explained in Fig. 9.

It is important when servicing the automatic mechanism, to have it placed on a level support. It is also important to refrain from forcing the mechanism if there is a tendency to bind or jam, since bent levers and possibly broken parts may result.

DU MONT TYPE 164

THE BEST THREE INCH OSCILLOGRAPH

AT ANY PRICE

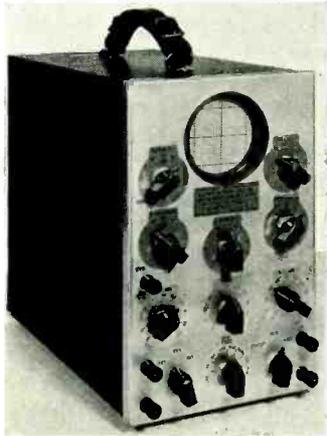

Dealers Net, \$54.50

Vertical and horizontal amplifiers, amplified sweep, internal or external positive synchronization, designed to operate with any standard type frequency modulated oscillator and every other important feature is incorporated in this modern oscillograph.

and another exclusive OUTSTANDING DEVELOPMENT

A Two Inch Cathode Ray Tube, Type 24-XH

Designed and engineered with the same care that has made Du Mont's 3, 5, and 9-inch Cathode Ray Tubes the standard quality for over six years. The 24-XH is of the high vacuum type with four electrostatic deflection plates, two common, mounted in a glass envelope having a full two-inch fluorescent screen. It is 7 $\frac{5}{8}$ inches overall in length and a large octal base is used.



Dealers Net,
\$7.50

The heater voltage A.C. or D.C. is 6.3 volts making this tube interchangeable with the 913. From 300 to 600 volts may be used on the second anode.

Ask Your Jobber Or Write
Allen B. Du Mont Laboratories, Inc.
Upper Montclair, New Jersey

ONLY
\$54.50

Complete

Designed and manufactured by Du-Mont the pioneers in Cathode Ray Instruments especially for the progressive Service Engineer who wants the best.



MODEL
1504
DEALER'S PRICE
\$56.67

*Simulates
Set Operating
Conditions*

*Give All Radio
Tubes a Com-
plete Test*

P.O.E. Tester

POWER • OUTPUT • EMISSION

Model 1504 Combines in One Tester the Following Instruments:

1. Power Output Test for All Amplifying Tubes
2. Emission Test for All Tubes
3. Free Point Tester
4. Neon Short Test
5. Separate Diode Test
6. D.C. Voltmeter
7. D.C. Milliammeter
8. A.C. Voltmeter
9. Ohmmeter
10. Condenser Test for Shorts
11. Electrolytic Condenser Leakage Test
12. Decibel Meter

OTHER MODEL P. O. E. TESTERS
Models 1502, \$36.67; 1503, \$46.67.

Remember Booth 79, Radio Parts Show, Hotel Stevens. Many New Items in the Ever-Enlarging Triplett Line Will Be Displayed.

See Your Jobber — Write for Catalog



THE TRIPLETT ELECTRICAL INSTRUMENT CO.
176 Harmon Avenue, Bluffton, Ohio

Without obligation please send me more information on Model 1504;
..... Model 1503; Model 1502. I am also interested

In

Name

Address

City State

TEST EQUIPMENT...

ZERO-CURRENT VOLTMETER

By BRADLEY THOMPSON*

THE advent of automatic volume control and automatic tuning in modern receivers has presented a special requirement in test equipment. The Service Man must have instruments capable of measuring voltages accurately in high resistance networks in these circuits without disturbing the operation of the receiver.

AVC CIRCUITS

Fig. 1 shows a typical avc circuit with a 6H6 as the rectifier. In operation when no signal is applied to the plates of the 6H6 no plate current flows in the tube and there is no voltage across the resistor R1 and the grids of the r-f and i-f tubes are at ground potential. Minimum bias for these tubes is maintained by the cathode bias resistor R2. When a signal is applied to the plates of the 6H6 it acts as a rectifier in exactly the same way as the familiar full-wave rectifier in a receiver power supply. Current flows between the plates and cathode and through the resistor R1 causing a voltage drop in R1 which makes point X negative with respect to ground. Since the amount of current flowing in the circuit is very small it is necessary that R1 be high. From 100,000 ohms to 2 megohms are

*Hickok Electrical Instrument Co.

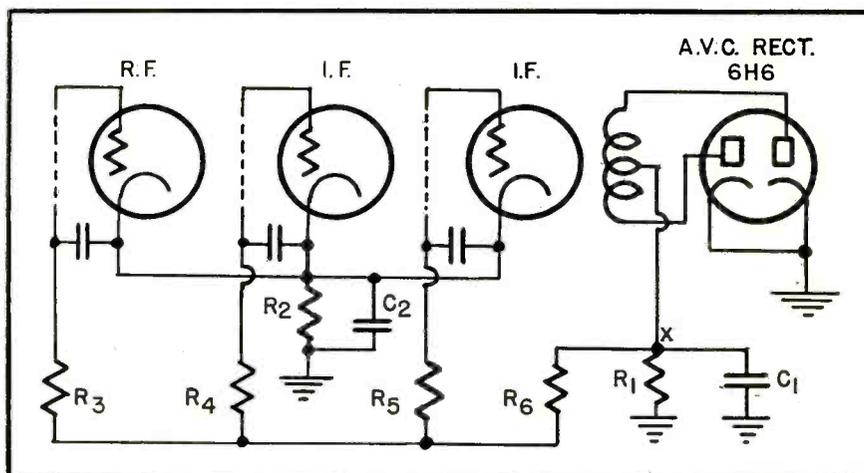


Fig. 1. Typical avc circuit with 6H6 rectifier.

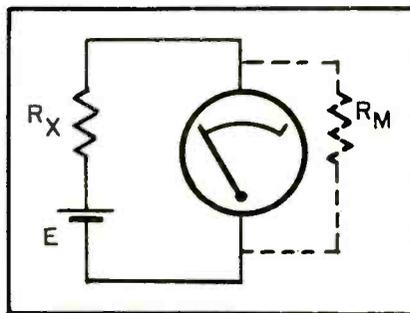


Fig. 2. Equivalent circuit which will result if a d-c voltmeter is connected from grid to ground of one of the tubes of Fig. 1.

used depending on the number and type of tubes used in the r-f and i-f amplifiers. Since no current can flow from point X through the grids of the r-f and i-f tubes these grids assume a negative potential or bias equal to the voltage drop across R1. When the signal to the 6H6 is increased more current flows through the tube and a higher voltage is developed across R1 increasing the bias on the grids and lowering the volume of the set. When the signal to the 6H6 is decreased less current flows through R1 and a lower voltage is developed across it lowering the bias on the grids and raising the volume of the set. The resistors R3, R4, R5 and R6 are decoupling or isolating resistors

which prevent the signal getting into the automatic volume control line. The size of these resistors and the capacity of condenser C1 determine the time constant or lag of the circuit. It is necessary to have a slight delay in the avc action to prevent static chopping up the signal. This lag may be increased by increasing resistors, R3, R4, R5 and R6 or by raising the capacity of C1.

ATTEMPTING MEASUREMENTS

If an attempt is made to measure the bias voltage on the grid of one of these tubes with an ordinary d-c voltmeter practically no indication will be obtained because the meter will draw enough current through the resistors in the avc line to drop the bias to a very low value. This may be seen by referring to Fig. 2 which shows the equivalent circuit which will result if a d-c voltmeter is connected from grid to ground or cathode of one of the tubes in Fig. 1. The bias voltage developed by the avc tube is represented by the battery E. The total series resistance in the avc line is Rx. Rm, shown in

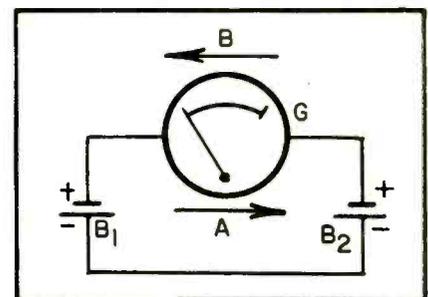


Fig. 3. Fundamental circuit of the zero-current voltmeter.

dotted lines, is the resistance of the voltmeter. From this circuit it can be seen that the voltage of E will be divided between Rx and Rm in direct proportion to the ratio of their resistance. If the 10-volt range of a standard 1000-ohms-per-volt meter is used Rm will be 10,000 ohms. Then if E is 6 volts and Rx is 500,000 ohms the actual voltage which the meter will indicate can be determined by the formula:

$$\begin{aligned}
 E_m &= \frac{6}{R_x + R_m} \times R_m \\
 &= \frac{6}{500,000 + 10,000} \times 10,000 \\
 &= 0.11 \text{ volts}
 \end{aligned}$$

If the sensitivity of the voltmeter is in-

Don't miss the
WARD
EXHIBIT




Booth 5
NATIONAL RADIO
PARTS TRADE SHOW
Stevens Hotel, Chicago
June 10, 11, 12 and 13

also at


ALL OTHER
IMPORTANT
RADIO SHOWS

NEW WARD AERIALS

Town and Country Series

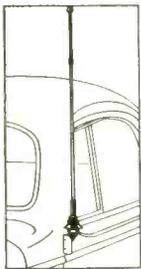


MAINLINER
MODEL M.L. \$2.45

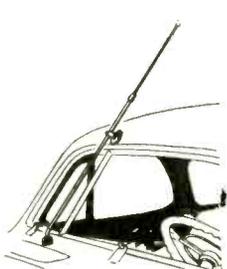

CHIEFTAIN
MODEL F.M. \$2.45



CORONATION
MODEL C.O. \$2.45

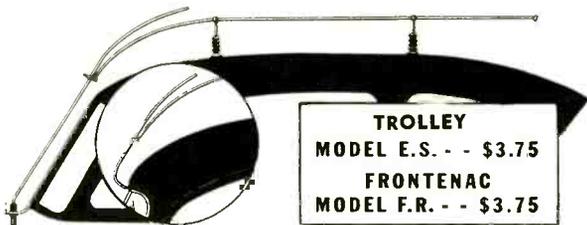

TROLLEY
MODEL E.S. - - \$3.75
FRONTENAC
MODEL F.R. - - \$3.75

PROMPT DELIVERIES GUARANTEED

Ward Products Corporation manufactures the world's finest line of Top, Pole and Undercar Aerials. Insist on GENUINE Ward Aerials.

WRITE FOR CATALOG TODAY

The WARD PRODUCTS Corp.
WARD BUILDING CLEVELAND, OHIO

HERE'S PROOF of



ACCEPTANCE!

MAY JUNE JULY

SEPT OCT. NOV. DEC.

MAR. APR.

**12 CONSECUTIVE MONTHS
OF UNINTERRUPTED SALES
INCREASE!**

In rapidly increasing numbers, Servicemen are turning to Utah as a source of supply for replacement parts, that is dependable in quality and service. This acceptance is reflected in Utah's Jobber Sales, which show a phenomenal and unbroken record of increase for a solid year—incontrovertible proof of the "swing to Utah."

What does it mean? It means that Utah's high standards of quality are meeting recognition among servicemen everywhere—and who should be a better judge than these men with first hand knowledge of Utah's inherent economy and quality? Join the "swing to Utah"—you'll be repaid with greater customer satisfaction.



SPEAKERS



A complete line of speakers of every type, precision-engineered and precision-built to Utah's standards, that have won universal recognition among service men, set-builders and the general public for quality of tone and superlative performance. Send for complete Utah Speaker Catalog.



VIBRATORS



Here's a vibrator that can really take abuse. built by the organization that has pioneered practically all of the developments in vibrator design. Use Utah Vibrators on all your replacement jobs—you'll find they work better, last longer and cost no more!

SEE THE UTAH DISPLAY AT BOOTH 69-70 AT THE NATIONAL RADIO PARTS SHOW!

UTAH RADIO PRODUCTS CO.
CHICAGO, U. S. A.

TORONTO BUENOS AIRES
ONTARIO, CANADA (UCOA RADIO PRODUCTS CO.)

"16 YEARS OF LEADERSHIP"

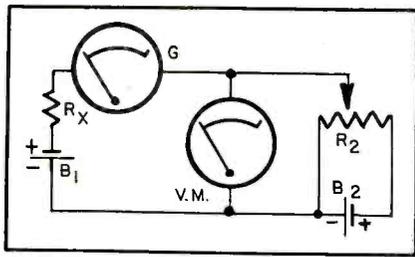


Fig. 4. Reading the voltage taken from the potentiometer with a d-c voltmeter.

creased to 20,000-ohms-per-volt the voltage indicated would be

$$E_m = \frac{6}{500,000 + 200,000} \times 200,000 = 1.7 \text{ volts}$$

The results obtained in these two examples indicate that if a very sensitive meter of several megohms per volt were used the indicated voltage would be very nearly the same as the voltage being measured.

A well-constructed vacuum-tube voltmeter will give slightly better results, but it is subject to some error since it is very difficult to obtain stable operation of a vacuum tube with more than two or three megohms in the grid circuit. This grid circuit resistance will draw current from the voltage being measured and cause a corresponding drop in voltage.

ZERO-CURRENT VOLTMETER

It may be seen from these examples that in order to accurately measure voltage in a high resistance network such as the automatic volume control circuit in Fig. 1 it is necessary to use an instrument that will draw no current from the circuit and may be connected to the grid of the tube without disturbing the voltage to be measured.

The zero current voltmeter to be

described is just what its name implies. A null reading d-c voltmeter which presents an infinite resistance to the unknown voltage to be measured. The fundamental circuit is shown in Fig. 3. Two batteries B1 and B2 are connected in series with a galvanometer G. The polarity of the batteries is such that the negative terminals of both are connected together and the positive of B1 connects to one side of the galvanometer while the positive of B2 connects to the other side of the galvanometer. Now if the voltage of B2 is greater than B1 current will flow in



Hickok 4900 set tester, illustrated above, uses the zero-current voltmeter.

the circuit in the direction shown by arrow B causing an indication in the galvanometer. However, if the voltage of B2 is less than B1 current will flow in the direction of arrow A and cause an indication in the galvanometer, but in the opposite direction. If the voltages of B1 and B2 are exactly equal no current will flow in the circuit and there will be no indication in the galvanometer. If a potentiometer is connected across B2 so that the voltage taken from it can be varied it will be possible to balance the galvanometer

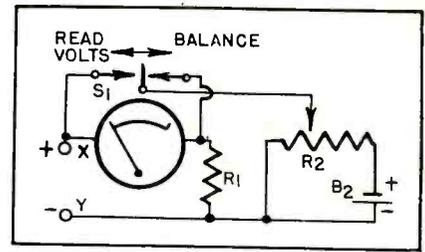


Fig. 5. Switching arrangement permitting the use of one meter as both galvanometer and voltmeter.

against any voltage of B1 which is less than B2. Then if a d-c voltmeter of suitable range is connected as shown in Fig. 4 to read the voltage taken from the potentiometer it will indicate a voltage equal to B1 when the galvanometer is balanced.

Since the voltmeter is read when the galvanometer indicates that there is no current flowing through B1 any resistance that might be in series with it would not change the readings. However, as the resistance in series with B1 is increased it becomes more difficult to balance the galvanometer due to the current limiting effect on the off balance indications of the galvanometer. The accuracy depends on the sensitivity of the galvanometer. If a d-c milliammeter of the type commonly used in radio set testers having a full-scale sensitivity of 1/4 milliampere or better is used the battery of 6 volts in series with 500,000 ohms shown in Fig. 2 may be measured with an accuracy of about 5 percent.

SINGLE METER USED

One meter may be used as both the galvanometer and the voltmeter by means of a suitable switching arrangement as shown in the circuit of Fig. 5. A single-pole double-throw switch is used to connect the slider of R2 to one side of the meter movement to indicate balance or to the other side to indicate voltage. R1 is the voltmeter series resistance. The meter must have low internal resistance. Otherwise there will be a voltage change when the potentiometer slider is switched from one side to the other. If the meter resistance is less than one percent of R1 it will be satisfactory. When the arm of switch S1 is thrown to the right the meter acts as a galvanometer and may be balanced for zero indication by adjusting the slider of potentiometer R2. After the meter is balanced switch S1 is thrown to the left and the voltage read on the voltmeter scale. If the two terminals X and Y are connected to the


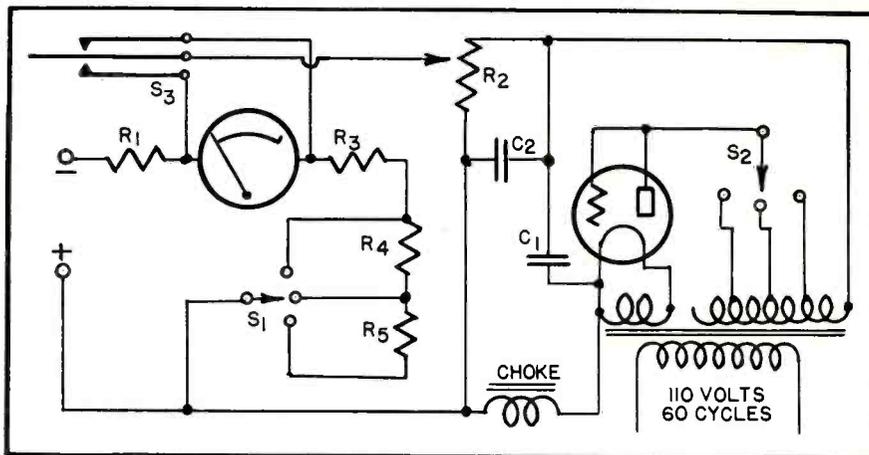


Fig. 6. The zero-current voltmeter circuit as adapted for the Hickok 4900 set tester.

**HANDIEST
TOOL I OWN!**

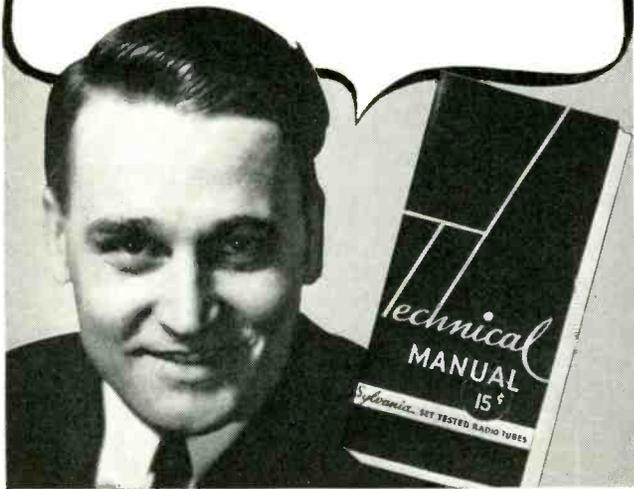

"I use it on almost every job—and it cost me just 15c!"

Every day, more and more service men write in for their copy of the new Sylvania Technical Manual. Every day, more and more service men are finding out how *really helpful* the Technical Manual is—solving their problems, saving them the expense of wasted time and needless mistakes. You need this book in your tool kit. It's a *whale* of a value—yet it costs you only 15c.

Quick! Get Your Copy Now!

This convenient, pocket-size manual contains 184 pages . . . lists 193 tube types with important circuit application information on each—tells all about glass, metal and "G" type tubes, as well as those for Majestic receivers. Gives full information on Sylvania "Ballast Tubes." Send the coupon and 15c *now* . . . and leave the rest to us!

Hygrade Sylvania Corporation, makers of Sylvania Radio Tubes and Hygrade Lamp Bulbs. Factories at Emporium, Pa.; Salem, Mass.; and St. Mary's, Pa.

SYLVANIA
SET-TESTED RADIO TUBES

HYGRADE SYLVANIA CORPORATION, S-67
Emporium, Pa.

I enclose 15c for which please send me a copy of the new Sylvania Technical Manual. I am (check below):

Experimenter.....; Amateur.....; Call.....; Service-
man.....; Employed by dealer.....; Independent.....
Member Service Organization.....

Name

Address

City State

Name of Jobber

Address

**1st VOCAGRAPH Challenged
all to Quality Leadership**



**NOW a CHALLENGE
to meet
PRICE plus QUALITY**

Here are the finest, most dependable amplifiers, at prices that set new standards in the sound industry—and open great new markets because of the low cost installations they make possible.

30 Watts \$39.90 18 Watts \$29.70

A super-power amplifier conservatively rated with less than 6% harmonic distortion. Two 6L6G beam power tubes in class A output stage, two 6F5G input amplifier stages for two crystal, dynamic, or velocity microphones, a 79 mixer, and a 76 driver. Universal output impedances. 35-Watt field supply. Priced, less tubes and shield, dealer net F. O. B. Chicago.

Power enough for practically any auditorium or dining place. Conservatively rated at less than 6% harmonic distortion. High and low gain channels. Uses one 6FG input, a 79 mixer, two 4Z's in power output, and an 83 rectifier. Priced, less tubes and shield, net to the dealer, F. O. B. Chicago.

Portable Systems

VOCAGRAPH complete sound systems and fully portable units cover every need of the sound specialist—all at startling new low prices. Write for the complete catalog listing over twenty combinations.

10 Watts \$19.44

Ideal for tavern and restaurant use. High gain input for crystal, dynamic, etc. microphones. Low gain for carbon microphone (sup. button current) radio or phono. Can be wired with stand-by switch for paging application. Priced, less tubes and shield, net to dealer, F. O. B. Chicago.

Buy from Your Own Parts Jobber

VOCAGRAPH helps complete the service he renders you. Now, for the first time, he is able to supply your entire needs at low cost from a single amplifier line, thus enabling him to carry a full stock and insure speedy deliveries. Visit him today and ask for a VOCAGRAPH amplifier demonstration. FREE—New Sound Catalog.

Division of ELECTRONIC DESIGN CORP.

VOCAGRAPH SOUND SYSTEMS

162-B N. May Street, Chicago, U. S. A.
Send at once the complete VOCAGRAPH Sound Catalog

Name.....
Address.....
City..... State.....
My Jobber is.....

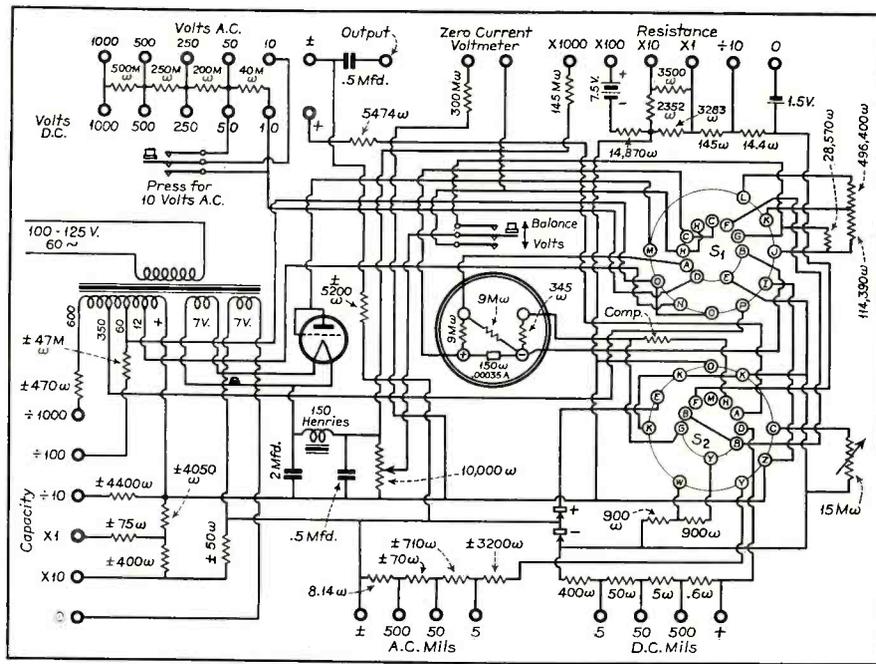


Fig. 7. Hickok 4900 set tester. The complete circuit of the instrument is given which includes the 3-range zero-current voltmeter.

grid and cathode of a tube instead of the battery and the galvanometer is balanced as before the voltmeter will indicate the bias on the grid. Since the meter will indicate only d-c the readings will not be upset by any signal voltage which may be present.

Fig. 6 shows the circuit as it has been adapted for use in a commercial instrument which has been recently announced. The battery for supplying balancing voltage has been replaced by a power supply consisting of a transformer, a half-wave rectifier and a suitable filter network. The switches S1 and S2 are operated simultaneously from the same shaft and change the voltage of the power supply and the range of the voltmeter. The ranges available are: 0-10, 0-50 and 0-250 volts. The power supply must have a well-designed filter network to prevent any a-c ripple voltage being applied to the grids in the receiver. The presence of any ripple voltage here would tend to operate the automatic volume control and change the bias. In the filter shown C1 is 2 mfd, C2 is 0.5 mfd and the choke is 150 henrys. The switch S3 is a three leaf push-button type which connects the meter as a galvanometer to indicate balance in the normal position.

OPERATION

The operation is very simple. The terminals of the instrument are connected to grid and cathode of the tube

on which it is desired to measure the bias. The negative terminal connects to grid and the positive terminal to cathode. Switch S1 is set on the 0-10 volt range and the slider of potentiometer R2 is adjusted until the meter is balanced or shows no indication. The meter must be balanced very carefully for accurate results. Then the push-button S3 is pressed and the voltage read on the 0-10 volt scale of the voltmeter. If it is impossible to balance the meter change to the 0-50 range and try again. If it is still impossible to obtain balance change to the 0-250 range. When using the 0-50 or 0-250 ranges the voltage is read on the corresponding scale of the voltmeter. If the meter indicates off scale backwards and cannot be balanced the polarity of the voltage being measured is wrong and the leads should be reversed. When making adjustments in a circuit to cause a zero indication on a meter it is convenient to have some means by which any current flowing in the circuit may be switched into or out of the meter causing it to assume actual zero indication when the current is switched out. This is accomplished by adjusting the springs of S3 so that they short the meter when the push-button is partly depressed. When adjusting R2 for balance the push-button is pressed half way down then released. This is repeated while adjusting R2 until no indication is observed. Very slight deflections of the needle may be observed

in this way. When measuring voltages which give only a small indication the exact zero may be determined by adjusting R2 until the smallest noticeable deflection is observed in the meter then turn R2 until an equal deflection is observed in the opposite direction. The exact zero will be half way between these two settings of R2.

The complete circuit of the tester which includes the 3-range zero-current voltmeter and the usual ranges of a-c and d-c volts at the 1000 ohms-per-volt, a-c and d-c milliamperes, resistance, capacity and output measurements is shown in Fig. 7. The ohmmeter is a combination battery and a-c operated type using two small batteries for the 4 ranges covering from 0.05 ohms to 1 megohm and rectified a-c for the high range; 0-10 megohms.

DuMont 164 Service Oscillograph

The DuMont Model 164 service oscillograph is designed to meet the requirements of the Service Man. The type 34-XH 3-inch cathode-ray tube is supplied with the unit. This tube is of the high vacuum type with four electrostatic deflection plates mounted in a glass envelope having a full 3-inch screen. The sensitivity of the type 34-XH is 0.38 millimeter per volt. It is interchangeable with the type 906.

THE CIRCUIT

The amplified sweep circuit, contained in the unit, consists of an 885 gaseous discharge tube used as a sawtooth wave generator so biased that it uses only the linear portion of the condenser charging curve. The small signal thus obtained is amplified to a usable amplitude by means of the 6C6 horizontal amplifier. The frequency range of the sweep circuit is from 15 to 30,000 cycles. Both fine and coarse control of the sweep frequency is provided.

The instrument contains separately controlled horizontal and vertical amplifiers. These amplifiers have a linear range between 30 and 30,000 cycles. The horizontal amplifier has a gain of 40 and an input resistance of 800,000 ohms. The vertical amplifier has a gain of 70 and an input resistance of 1 megohm. The maximum allowable rms a-c input to either amplifier is 300 volts.

In order to prevent interaction of the controls and to produce a brilliant trace two power supply circuits are used. These supplies deliver 1,125 and 415 volts d-c, respectively. The unit is completely a-c operated from the 60-cycle,



The **20-C AMPLIFIER** Type



- 20 Watts output
- Dual mike input
- Electric Eye monitor

Modern in Appearance and Performance

A complete line of sound systems for every application illustrated in U. S. E.'s new 16 page catalog.

Write for new Catalog No. 107 and proposition.

United Sound Engineering Co.

2245 UNIVERSITY AVENUE ST. PAUL, MINNESOTA
Licensed by arrangement with E.R.P.I. under patents owned and controlled by A. T. & T. and Western Electric Co., Inc.

THE WORLD'S SMALLEST PERMAG SPEAKER



3" OXFORD PERMAG . . . a high quality permanent magnet dynamic speaker with remarkable sensitivity for its size. Has excellent speech range—can be used as both microphone and speaker. Ideal for Inter-office Communication Systems, and applications where low-current drain is desired.

This is just one of the many advanced models in the new COMPLETE line of OXFORD PERMAG (permanent magnet) SPEAKERS now available from 3" to 14" . . . including a trumpet-type permanent magnet speaker with a 6" cone for use with an exponential horn.

Write now for complete data -- or see them at Booth 48, Radio Parts Manufacturers National Trade Show, Hotel Stevens, Chicago, June 10 - 13.

New York Office: 27 Park Place, New York City

OXFORD-TARTAK
RADIO CORPORATION
915 W. VAN BUREN ST. • CHICAGO, U. S. A.
SPEAKERS BY OXFORD

A COMPLETE NEW LINE FOR SALES AND PROFITS



GENERAL ELECTRIC **PRE-TESTED METAL TUBES**

GENERAL ELECTRIC **PRE-TESTED GLASS TUBES**

FOR CUSTOMER SATISFACTION Use G-E RADIO TUBES

Memo to: **Dealers and Servicemen**
Ask your G-E Radio Distributor for details of the G-E Radio Tube Merchandising Plan, or write to Radio Tube Sales Section, General Electric Company, Bridgeport, Conn.



GENERAL ELECTRIC

APPLIANCE AND MERCHANDISE DEPARTMENT
GENERAL ELECTRIC COMPANY, BRIDGEPORT, CONN.

FIRST IN EARNINGS!

Besides this complete, compact **RADIO SERVICE LABORATORY**, Webber manufactures a complete line of portable radio testing instruments—for every servicing purpose.



Handles with un-failing accuracy every radio testing job. Hundreds from coast to coast—everyone speeding work towards new profits.

The demand for Webber engineered, precision testing and servicing equipment proves without question that service men and dealers everywhere want profitable, prestige-building instruments. The unit illustrated and other Webber portable testing instruments are priced to be within the reach of every service shop, radio technician and service man. Write for complete catalog.

EARL WEBBER COMPANY
1307 WEST RANDOLPH STREET • CHICAGO, ILLINOIS

TEST EQUIPMENT—continued


110-120 volt lines. The total power consumption is 50 watts.

The vertical input is to the binding posts on the left side of the panel, the lower post of the pair being the ground. The horizontal input is on the right side and as in the previous pair the bottom post is the ground.

On the back of the machine is a plate with five screw type binding posts. These permit the disconnecting of either or both circuits allowing direct connection to the deflection plates. This feature will be found a convenience to amateurs or others working with d-c or high frequency applications.

THE CONTROLS

All controls of the type 164 oscillograph are on the front panel and are plainly marked. Because all the controls are on the front panel it was deemed advisable to distinguish in some manner, the controls frequently adjusted from those more permanently set. Hence the synchronizing, rough and fine frequency and the horizontal and vertical amplifier controls have red bar knobs. In the upper left corner is the intensity control, it controls the intensity of the trace and also carries with it the off and on power switch. At the upper right is the focus control. Just below the intensity control is the vertical positioning knob which controls the up and down movement of the spot or

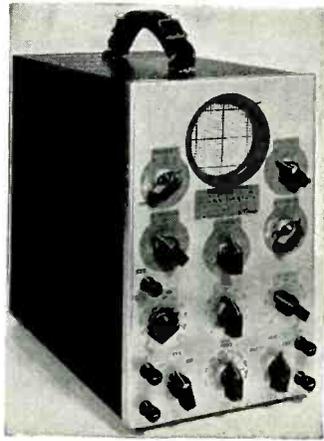

DuMont 164 service oscillograph.

trace while directly below the focus control is the horizontal positioning which controls the left to right movement of the pattern. The synchronizing control is in the center of the panel just below the cathode-ray tube. Directly below the position controls are the amplifier gain controls; the vertical on the left, and the horizontal on the right. In the center of the panel under synchronizing is the vernier or fine frequency control of the linear sweep while directly below it is the rotary switch which controls the frequency in rough steps. The approximate range of these steps are as follows: (1) off; (2) 15 to

60 cycles; (3) 60 to 220 cycles; (4) 220 to 900; (5) 900 to 3,000; (6) 3,000 to 10,000; and (7) 10,000 to 30,000 cycles.

At the bottom of the panel on the left side is the switch which permits either internal or external synchronization while on the right, a switch places the horizontal amplifier in operation with the sweep or connects it to the post for external use.

The controls are arranged so that the minimum setting is obtained when the knobs are turned counter-clockwise and maximum when turned clockwise.

A removable calibrated scale is supplied with the unit so that quantitative measurements may be made.

Motorola Auto Radios

Chassis pickup: Because the field strength of ignition interference is high in the 1937 model Chrysler cars and 1937 Ford cars, some cases of chassis pickup may be encountered.

In most cases this can be overcome by removing the front cover from the set and cleaning the surfaces of the joints with fine sandpaper to provide greater area of metallic contact between the set cover and the set housing.

Also check the Acoustinator plug carefully to see that it is securing a good ground to its grounding contacts.

Dress the A lead directly away from the set. Do not allow it to run too close and parallel to the right side of the receiver.

In all Chrysler cars the field intensity can be materially reduced by grounding the "over drive" cable, gasoline gauge, tube, etc., at the point where they pass through the bulkhead of the car.

In the most severe cases it may be necessary to remove the chassis from the set housing and clean all the joints where the chassis intersects its housing. This cleaning should be done with fine sandpaper as in the case of cleaning the cover joint.

In those localities along the sea coast where salt air causes excessive corrosion of metal, be careful when cleaning the various joints that the plating is not removed from the steel, otherwise rust will occur at the points where the sand paper has cut through the plating.

When checking for chassis pickup in the Model 65 make sure that the right-hand breather screen secures a good ground to the set housing. Spotting it with solder to the housing at several places is sufficient to prevent interference from feeding in at this point.

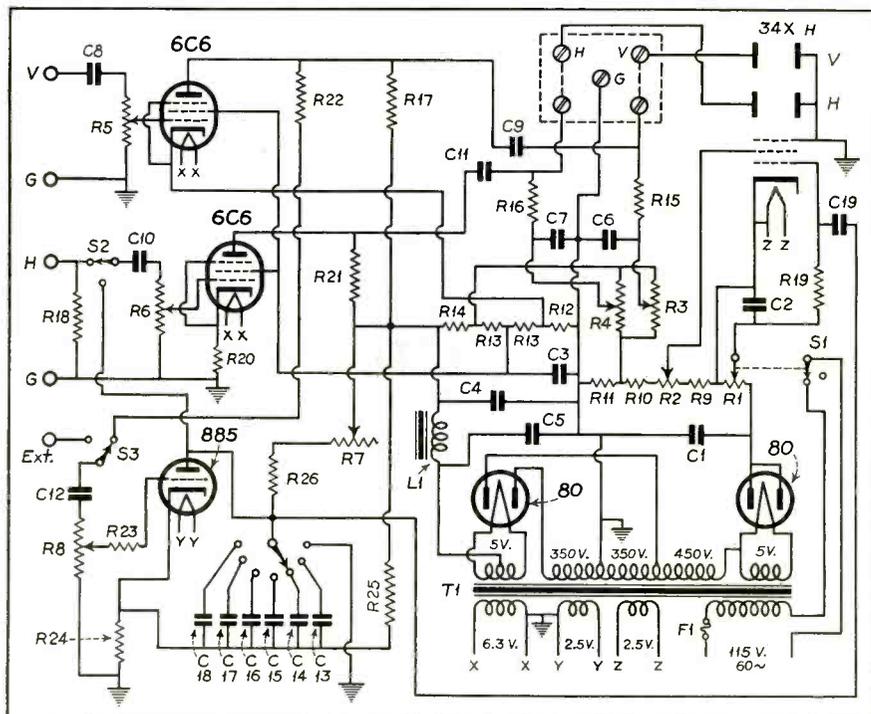


Fig. 1. DuMont 164 service oscillograph circuit.

**FOR PERFECT DEMONSTRATION
OF AUTO AND OTHER
D.C. RADIOS**



**Epco
STORAGE BATTERY
ELIMINATOR**

**HELPS YOU TO MAKE
SALES MORE EASILY—
MORE ECONOMICALLY!**

Perfect demonstration of auto and battery radios. Delivers 10 amps at 6 volts pure filtered D.C. from 110 volts A.C. Adjustable voltage provides proper current for all types of radios. Completely dependable! Ends messy battery charging nuisance! Efficient as battery charger (high rate).

\$19.75 as illustrated, variable voltage



ELECTROPAK

Supplies D.C. (rectified A.C.) for operating solenoids and remote controls. Available in voltage ranges from 60 to 24 volts at 2 to 15 amps. Operates on 110 volts A.C.

ADAPTOPAK

Operates A.C. radios in D.C. districts and 110 volt A.C. radios in autos and trailers.

ELECTRICAL PRODUCTS CO.
6529 Russell St. DETROIT, MICH.


Bell Performance

Insures Customer Satisfaction

When you sell Bell Sound Systems for either portable or permanent use your customer is better satisfied . . . and you make a profit and have no servicing worries! They are dependably constructed to the highest standards by an established, reputable concern and have tone qualities that identifies them as truly fine equipment. They are low in price and available in models for any purpose.

**NEW! BELL Public
Address System**

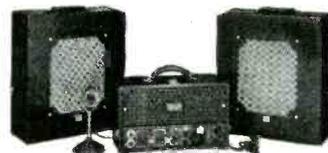20 Watt undistorted output . . . infinite baffle speakers . . . crystal microphone . . . dual input channel . . . complete in two compact carrying cases. A flexible, high quality Public Address System at a price that can't be duplicated. Write for details.



BELfone Communicating Systems

A business essential in America! Permits conversation between departments by merely flipping a key and talking. Saves time, steps and effort. Also used for call system. Can be arranged for any number of stations and operates off of regular line current. Market for BELfone is practically unlimited. Write for Bell Catalog.

BELL SOUND SYSTEMS, INC.

61-62 E. Goodale St., Columbus, Ohio

Export } 308 West Washington St.
Office } Chicago, Illinois, U. S. A.



**All Purpose
SOUND EQUIPMENT**

**FREE TO OWNERS
OF ALL SEVEN
RIDER MANUALS**



That you may let customers know you know—merchandise your Rider Manuals—and benefit from a selling stunt proved by other servicemen—we will send FREE to every owner of all seven Rider Manuals the materials listed at left.

This Rider 100% Group Certificate will prove to your customer that you are equipped with the circuit information necessary for servicing any American made radio.

Send us the seven title pages from your seven Rider Manuals and we will send you your material.

Vol. VII—1600 Pages—Covering 1936-37—\$10.00

Six other volumes covering sets issued between 1920 and 1936—\$7.50 each.


**AUTOMATIC FREQUENCY
CONTROL SYSTEMS
HARD COVERS — 144 PAGES — \$1.00**

With Automatic Frequency Control Circuits in many new higher-priced models, knowledge of "AFC" means money in your pocket!

Learn the practical facts, from the easy to understand explanations by John Rider. Get your copy today and have the timely information enabling you to cash in on profitable "AFC" repair work.

**A NEW
RIDER
BOOK
JUST
OUT!**

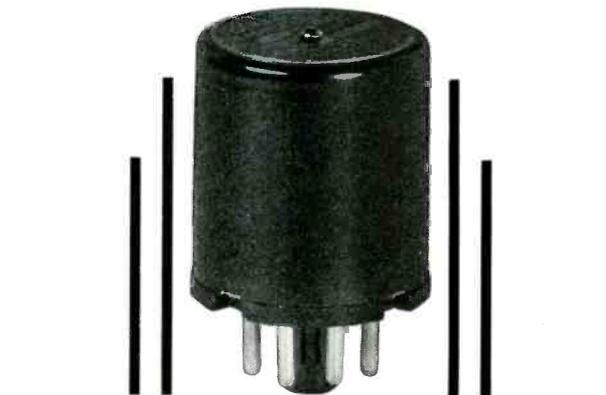JOHN F. RIDER, Publisher, 1440 Broadway, N.Y.C.



**THE BRUSH TRANSFILTER
FILLS THE GAP**

● The transfilter fills the selectivity gap between the electrically tuned circuit and the quartz filter. A transfilter can be employed in any superheterodyne whose intermediate frequency amplifier can be tuned to 465 kilocycles.

Technical data on request

See us at Booth 95, Chicago Trade Show

**The BRUSH
Development Company**
3317 Perkins Avenue, Cleveland, Ohio

Auto-Radio . . .

Ford-Philco F-1440

The Ford-Philco auto-radio receiver is a 6-tube, superheterodyne using glass tubes. The frequency range is from 540 to 1550 kc. A complete circuit diagram is given in Fig. 1.

The model is designed for use with the Ford rotary "reserve power" roof aerial and a concealed header bar speaker. A special antenna transformer is supplied as standard equipment which matches the receiver input to the unique antenna.

ALIGNMENT PROCEDURE

The i-f transformers are assembled complete with padding condensers. Both the primary and secondary padders are placed side by side in the top of the transformer shield. The adjusting screws are accessible through the holes in the top of the shield. (See Fig. 2.)

An output meter should be connected to the plate of the type 41 output tube through an 0.25 mfd condenser and to the receiver chassis, or across the speaker voice coil.

With the receiver and signal generator set for operation at the prescribed

frequency, turn the receiver volume control on full and set the signal generator attenuator so that a half scale reading is obtained on the output meter. The signal in the speaker should be audible but not loud. The shielding on the signal generator output lead should be connected to the receiver chassis.

Allow both the receiver and signal generator about 15 minutes to warm up before attempting adjustment.

I-F ALIGNMENT

Set the signal generator at exactly 260 kc. Connect the generator output lead to the grid cap of the 78 i-f tube in series with a 0.1 mfd condenser (without removing the grid cap connection).

Adjust the secondary screw padder No. 28 on the second i-f transformer for maximum reading on the output meter. Then adjust the primary screw padder No. 26 for maximum reading, keeping the reading near the middle of the output meter scale by means of the attenuator on the signal generator. See Fig. 2 for the location of the padders.

Remove the generator lead from the grid cap of the 78 i-f tube and connect

it to the grid cap of the type 6A7 tube in series with the 0.1-mfd condenser (without removing the grid cap). Adjust the secondary (No. 24) and primary (No. 22) screw padders in that order for maximum output meter reading. Then readjust padders Nos. 28 and 26 with the generator lead still connected to the 6A7 tube's grid. See Fig. 2 for the location of padder condensers.

R-F ALIGNMENT

After padding the first i-f stage remove the generator lead from the 6A7 tube. Set the signal generator at 1550 kc and then connect the generator lead to the grid cap of the 78 r-f tube in series with a 0.1-mfd condenser (without removing the grid cap).

Using a piece of paper approximately 0.006-in. thick as a gauge between the heel of the rotor plates and the stator plates, turn the rotor plates in mesh until they strike against the paper.

With the tuning condenser in this position adjust the high-frequency padder 16 and the r-f padder 12 until the maximum reading is obtained on the output meter. This is the true setting for 1550 kc, 155 on the dial scale.

Turn the tuning condenser plates in mesh to approximately 600 kc, 60 on the dial scale and set the signal generator at 600 kc. Roll the tuning condenser and adjust the low frequency

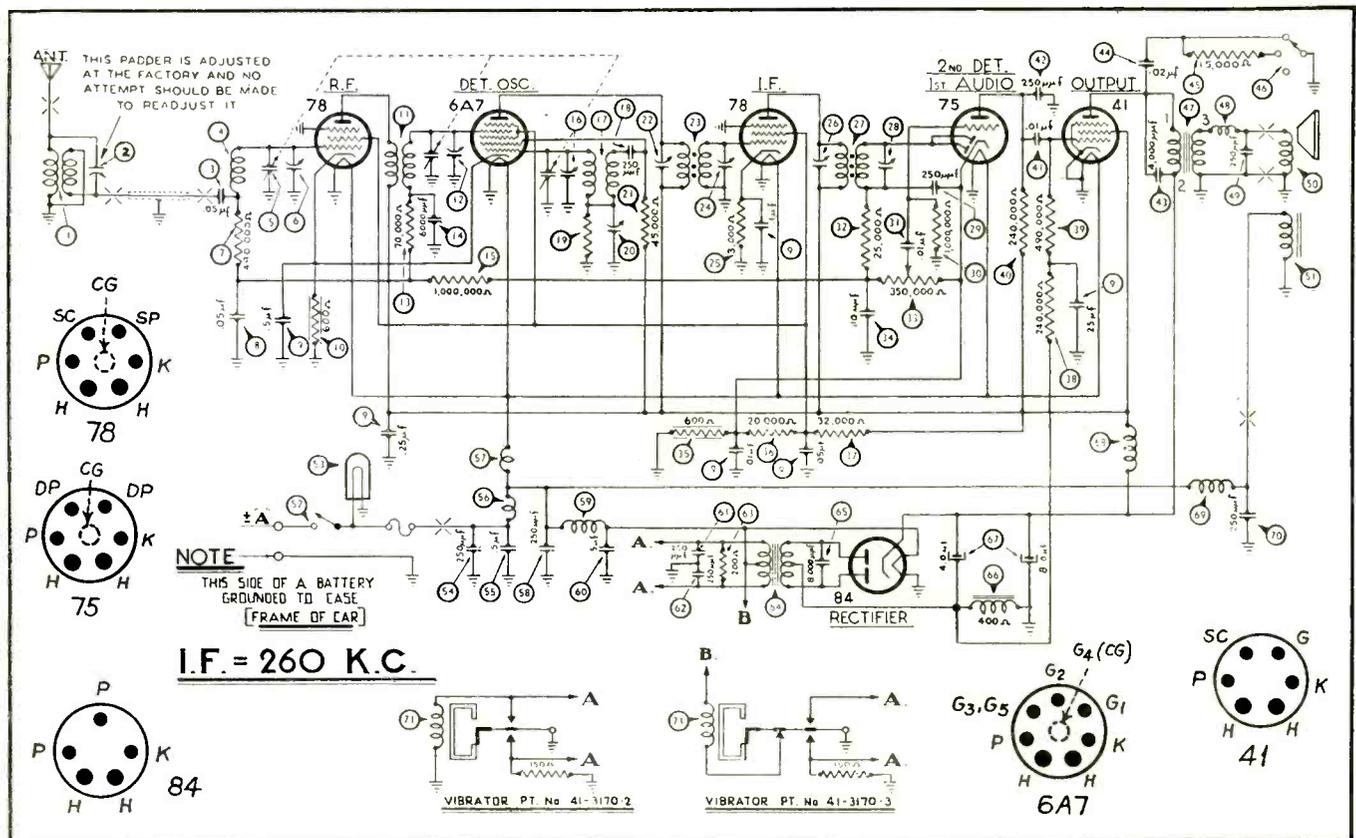


Fig. 1. Ford-Philco F-1440 circuit diagram.

Technical Features of 1937 Auto - Radio Receivers

Model No.	ADMIRAL -		AMERICAN - BOSCH -				ARVIN -		AUTOMATIC			CADILLAC LASALLE	CHAMPION	CHRISLER PHILCO	CROSLLEY	DETROIT																		
	66 and 660	77 and 770	78 and 780	88 and 880	5368	636	736	737	738	838	19	29	39	M10	M20	M60	M80	661	667	5X	6KB	50VD	60/84	C-1450	C-1452	A-268A	366	111						
Range (Kc.)	550 to 1500		540 to 1500				540 to 1575					528 to 1581		530 to 1610	550 to 1550		540 to 1570																	
Output Watts	3	4	4	6	3	3	3	5.5	3.5	4.5	7.5	2	3	7	2.5	4	2.4	5.5		2.5	2.5													
Dynamic Sp'k'r	6"	6 1/2"	8"	8"	6"	5"	6"	8"	10"	6"	8"	5"	5"	5"	5"	6"	6"	8"																
I.F. Peak (Kc.)	175		175				170		456			175			262.5			175	262	260	262	262												
Current Drain	7	8	7	9	6.5	6.5	6.5	7.5	6.1	6.7	7.2	4.6	5	6	6.5	6.5	6.3	8.1																
Control Drive Ratio	16 to 1		16 to 1																															
Tone Control	250M w		250M w				100M w		500M w			500M w			50M w			1 Meg.	1 Meg.															
Volume Control	500M w		500M w				500M w		250M w			250M w			500M w			500M w																
Sensitivity at 1 Watt Output	Taps		Taps				Taps		Taps			Taps			Taps			20 MV.	20 MV.															
Sensitivity Control	Taps		Taps				Taps		Taps			Taps			Taps			3M w	115 w															
R.F.	6D6	6D6	6D6	6D6	77	77	6K7	6K7	6K7	78	6K7G	6K7G	6A7	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A7	6A7										
1st. Det.	6A7	6A7	6A7	6A7	77	77	6A8	6A8	6A8	6A7	6A8G	6A7	6A7	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A7	6A7	6A7										
Oscillator	6D6	6K7	6K7	6K7	78	78	6K7	6K7	6K7	78	6K7G	6K7G	6D6	6D6	6D6	6D6	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7		
Intermediate Frequency	75		75				75		75			75			75			6F7	6F7															
2nd. Det.	6C5		6C5				6C5		6C5			6C5			6C5			6F7	6F7															
AVC	6C5		6C5				6C5		6C5			6C5			6C5			6F7	6F7															
1st. Audio	41	6V6	6V6	6V6	42	42	6F6	6F6	6F6	41	6V6G	6N7G	41	41	41	6F6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	
2nd. Audio	84	84	84	84	84	84	OZ4	OZ4	OZ4	84	6X5	OZ4	84	6X5	84	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5		
Output	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	
Rectifier	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	
Pilot Light No.	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51	#51

S after Tone or Volume control means with switch attached ; T = Tapped (Continued on Next Page)

denser for the oscillator section of the tube.

A 6K7G tube is used with two double-tuned i-f transformers in an i-f stage. One diode of the 6H6 tube is used as the second detector and the other diode is used as an avc rectifier. The cathodes of the controlled tubes are returned directly to the chassis. Minimum bias is obtained by connecting the avc return to a suitable tap in the negative leg of the voltage divider circuit.

A 6C5G is used as an audio amplifier, the desired amount of signal is fed to the control grid from the volume control (R9) located in the tuning head. Another 6C5G is used to drive the 6N7G power output stage. A tone control is also located in the control head.

A vibrator and step-up transformer are used to obtain the high voltage necessary for the power supply circuits. A 6X5G rectifier and a suitable filter network are used to convert the high voltage a-c thus obtained to smooth d-c used in the plate, screen and grid circuits.

ALIGNMENT PROCEDURE

Connect the service oscillator output leads to the control grid of the 6A8G oscillator-modulator tube and to the receiver chassis. Connect an output meter across the primary of the speaker transformer or across the voice coil.

Turn on the service oscillator and the receiver and allow both at least 15 minutes to warm up before attempting adjustments.

The sensitivity control should be in the extreme clockwise position when making adjustments.

Because of the high gain of the i-f transformers used in this model it is essential that a non-metallic screw-

driver be used in making the adjustments.

I-F ALIGNMENTS

Set the service oscillator to 262½ kc and adjust the i-f trimmers to the point giving the greatest output reading on the output meter, starting with the secondary trimmer on the second i-f transformer and working toward the primary trimmer on the first i-f transformer. These as well as the following adjustments should be made using as small an output from the service oscillator that will give a readable indication on the output meter so that the avc action will be least effective.

Repeat the i-f adjustments to assure greater accuracy.

R-F ALIGNMENT

Change the service oscillator lead from the grid of the 6A8G to the antenna connection. A male Delco-Remy connector may be used in making the connection to the antenna lead.

Set the service oscillator to 1600 kc and rotate the gang condenser until the plates are entirely out of mesh. Adjust the oscillator section trimmer until the 1600-kc signal is tuned to maximum.

Change the service oscillator setting to 1400 kc. Rotate the gang condenser until this signal is tuned to a maximum and adjust the r-f trimmer on the gang condenser to the point giving the greatest output reading.

Set the service oscillator at 600 kc and rock the gang condenser slowly to and fro through the point where this signal is received, meanwhile adjusting the padder condenser for a setting which gives the greatest output reading.

Repeat the 1600 and 1800 kc adjustments.

ANTENNA STAGE ALIGNMENT

There is such an extremely wide variation in antenna capacities that it is difficult to match the set to the antenna without some means of variable antenna alignment. To accomplish this, an antenna compensating adjustment is provided through the small hole directly above the antenna cable connector on the receiver case. In addition to this, a tapped antenna transformer is also incorporated. The proper method of alignment is as follows: After completely connecting receiver, tune in a signal between 1400 and 1450 kc and adjust the antenna compensator shown in Fig. 2, for either the roof antenna, or single or double under-car antenna. The receiver is shipped from the factory with the antenna tap set to the No. 2 position, and, therefore, need not be changed for either of the two types of antennas mentioned.


For Zenith "Fleet Wing," and "Over the Top Antennas," unsolder the antenna lead from the No. 2 lug, and resolder it to the No. 3 lug. After this is done, tune in a station between 1450 and 1400 kc and adjust the antenna compensator shown in Fig. 2 to resonance.

For high-capacity antennas such as the 1936 Dodge solid steel roof, or the Lincoln Zephyr luggage compartment, drawer antenna, etc., remove the antenna lead from the No. 2 lug, as it comes from the factory, and resolder it to the No. 1 connector. After this is done, the same procedure of tuning in a signal from 1450 to 1400 kc and balancing to resonance with the antenna compensator, as described above, should be followed.

This system of tapped transformer, and variable compensating adjustment gives a flexible means of resonating the receiver to any type of antenna, and it should be noted that the tap need only be changed in two cases.

Belmont 420, 430

Won't tune down to 1712 kc: If trouble is experienced in making the receiver tune down to 1712 kc, during alignment, inspect the green grid and black ground wires connected to the antenna coil. These should be well separated from each other. Both the green leads to the grid cap and the antenna should be clear of the tube shield. This reduces to a minimum the external capacity of the antenna coil circuit and will help in making the receiver tune to the higher frequency.

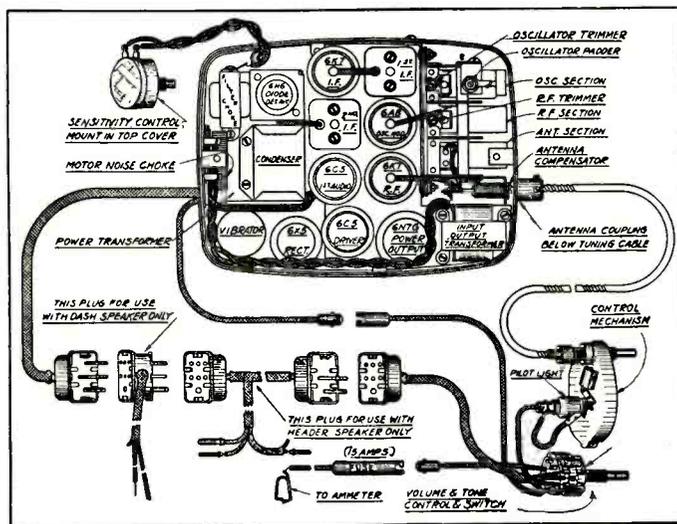

Zenith 5803 (8-M-195) tube and trimmer locations.

Technical Features of 1937 Auto-Radio Receivers

Model No.	PACKARD PHILCO		PHILCO			RCA		SILENTONE		SPARTON		STEWART WANNER		TRUESTONE		WELLS-GARDNER		WESTINGHOUSE					ZENITH					
	P-471	P-K30	826	827	827K	828	828K	829	67M	67M1	67M2	67M3	4601	4601†	R-160	D-734	D-743	D-744	6K	6L	WR-502	WR-503	5M-191	6M-192	6M-193	6M-194	6M-195	
Range (Kc.)	550 to 1550	580 to 1550	540 to 1540			540 to 1600		540 to 1540		530 to 1550		530 to 1575		530 to 1550		530 to 1575		540 to 1600					540 to 1600					
Output Watts	2.5	2.5	2.5	4	6	3.5	9	-	-	-	-	3	3	3	3	3	3	3	3	3	3	3	3.2	4.5	4.5	9	9	
Dynamic Sp'kr	-	5"	6 1/4"	7 1/2"	6 1/4"	7 1/2"	8"	8"	8"	8"	8"	8"	8"	8"	8"	8"	8"	8"	6"	5 1/4"	6"	5 1/4"	5 1/4"	5 1/4"	5 1/4"	6"	6"	8"
I.F. Peak (Kc.)	260	260	260			260		262		172.5		177.5		262.5		175		175					252.5					
Current Drain	-	-	-	-	-	7.3	7.5	7.5	9	7.6	8.25	-	-	-	-	-	-	-	7.8	7.0	6.5	6.5	5.5	7.5	6.0	6.0	9.2	
Control Drive Ratio	16 to 1	16 to 1	16 to 1			16 to 1		16 to 1		16 to 1					16 to 1													
Tone Control	Taps	Taps	Taps	Taps	Taps	Taps	Taps	Taps	100M ω	500M ω	500M ω	500M ω	500M ω	500M ω	500M ω	500M ω	500M ω	500M ω	1 Meg.	150M ω	1 Meg.	250M ω	1 Meg.	2 Meg.	2 Meg.	2 Meg.	2 Meg.	
Volume Control	350M ω	350M ω	350M ω	350M ω	350M ω	350M ω	350M ω	350M ω	250M ω	250M ω	250M ω	250M ω	250M ω	250M ω	250M ω	250M ω	250M ω	250M ω	500M ω									
Sensitivity at 1 Watt Output	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	-	1.0 MV.	1.0 MV.	-	-	5 MV.	0.9 MV.	0.9 MV.	0.9 MV.	0.9 MV.	
Sensitivity Control	1000 ω	1000 ω	1000 ω			1000 ω		1000 ω		1000 ω		1000 ω		1000 ω		1000 ω					1000 ω							
R.F.	78	78	78	78	78	78	78	78	6D6	6D6	6D6	6D6	6D6	6D6	6D6	6D6	6D6	6D6	6K7	6D6	6K7							
1st. Det.	6A7	6A7	6A7	6A7	6A7	6A7	6A7	6A7	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6A8	6J7	6C6	77	77	6A8	6A8G	6A8G	6A8G	6A8G	
Oscillator	78	78	78	78	78	78	78	78	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6D6								
Intermediate Frequency	78	78	78	78	78	78	78	78	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6K7	6D6								
2nd. Det.	75	75	75	75	75	75	75	75	85	85	85	85	85	85	85	85	85	85	6H6									
AVC	75	75	75	75	75	75	75	75	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	6B7	
1st. Audio	41	41	41	41	41	41	41	41	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	
2nd. Audio	41	41	41	41	41	41	41	41	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	6C5	
Output	41	41	41	41	41	41	41	41	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	6A6	
Rectifier	84	84	84	84	84	84	84	84	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	6X5	
Pilot Light No.	-	-	-	-	-	-	-	-	#44	#44	#44	#44	#44	#44	#44	#44	#44	#44	7-50	T-50								

† High-Fidelity Models

Public Address . . .

P-A SERVICE PROBLEMS

By AARON NADELL

WHILE servicing public address equipment is and can always be made more profitable than receiver service work it is more intricate and extensive in nature and in fact rests upon somewhat different requirements. The two appear similar only at first glance. It is, of course, true that standard radio methods, both technical and commercial, have their own proper place in p-a service work, but seldom as more than one part of an inherently larger procedure.

The basic differences between these two kinds of servicing are responsible not only for the fact that p-a work, job for job, is much better paid, but also for further opportunities it offers of a kind that are not found in radio work at all.

In general, there are four essential distinctions—two technical and two commercial.

The set owner is less exacting; he can afford to tolerate some minor trouble, such as a hum or a small degree of distortion, much longer than the p-a user can. The latter will call on the Service Man far more readily—and wants correspondingly perfect results.

PROMPTNESS REQUIRED

Therefore, one of the two commercial differences between radio and p-a servicing may be summarized as an imperative demand for quick and perfect results in time of trouble.

A second difference arises out of this one, namely, that p-a offers opportunities for maintenance work to an extent unknown to the radio field.

Economically speaking, p-a requires promptness of repair to a degree that is practiced very little in radio servicing. There is seldom any such thing as taking a p-a system back to the shop and keeping it there a week to find out what's wrong with it. P-a equipment is not used in the home, but in business, and the dance hall, sound truck or other business enterprise using it may be exposed to serious losses if repairs are not made promptly. Consider, for example, the case of a cabaret owner whose system breaks down at the beginning of a holiday or even a Saturday evening. The equipment may be only a matter of entertainment to those who listen to it, but it means dollars and cents to the

man who owns it. He will be willing to pay a reasonable repair charge without waiting to shop around. But he will not welcome delay.

Such delay as, for instance, wiring to a supply source for a new transformer will be as intolerable as any other, and here lies still another opportunity for the Service Man.

In some cases, it is to the owner's best interest to install an emergency channel for instant protection in case of failure of the equipment; in nearly all cases he should stock spare parts—not only spare tubes but any uncommon part, such as a power transformer or disc rectifier, that may delay repairs materially if it should go bad.

The danger of a breakdown on a busy day is so serious to many (though, of course, not to all) p-a owners that it is distinctly to their advantage to pay a reasonable weekly or monthly sum for regular inspection of their equipment. Such inspection is designed to keep the apparatus in condition to deliver the best possible results at all times, and also to catch and cure such troubles as overheating, leaky condensers, bad tubes and others that may lead to breakdown if left unchecked.

Another striking difference between p-a and receiver servicing often makes the former easier. Unlike the receiver, the larger p-a system is composed of more than one unit. Trouble is often easily isolated by testing along the con-


necting lines and at the connection terminals. Finding the exact nature of the difficulty is greatly simplified in consequence. Very frequently the need for haste stops the trouble-shooting as soon as the defective unit has been located; instead of proceeding to repair that unit the Service Man simply replaces it on a temporary basis. Further and complete repairs can then be carried out at his leisure. Thus in one sense it is possible to take a p-a system back to the shop for deferred attention—a single part of the system can be treated that way, provided a satisfactory substitute is available.

Where a regular inspection contract has been arranged with the user, it is naturally the business of the Service Man to know the exact specifications for any component that may ever have to be replaced and where it can be obtained quickly if the owner does not stock a duplicate. Also to know in advance how connections can be modified to dispense with some unit temporarily—one speaker for example—still maintaining satisfactory impedance match and other qualifications for reasonable emergency performance.

ACOUSTIC PROBLEMS

The difference between the commercial requirements here outlined and those encountered in receiver servicing is sufficiently obvious; the divergence in technical requirements is in some ways equally striking.

One point of prime importance is that p-a work involves acoustic troubles and acoustic servicing, where radio work, of course, does not. Every Service Man knows that the tone of radio reproduction can be modified by placing the receiver in different parts of the same room but the differences so obtained are not very great and considerations of domestic convenience and appearance outweigh them. When sound at the loudspeaker is satisfactory as to quality and volume no more is asked. The

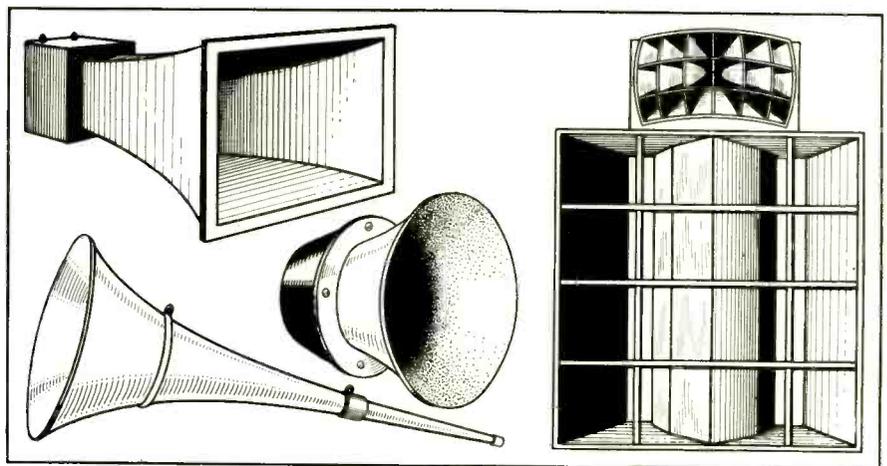

Typical directional baffles used for acoustical control in p-a installation and service.

A SPECIAL CHECK ✓ ON
Open Elements
 and
BAD WELDS
 ONLY ONE OF 15 **ERTL** FEATURES



A SPECIAL check during the output test shows intermittent opens and loose welds—the most difficult of all faults to locate with ordinary tube testers. This test for opens, the triple test for shorts, and the "twin test" for output, provide a tube analysis so complete as to double and triple tube sales.

ASK FOR FOLDER

See Radiotechnic Display at National Radio Trade Show, Stevens Hotel, Chicago, June 10-11-12—BOOTH 1271

THE RADIOTECHNIC LABORATORY
 1328 Sherman Ave., Dept. S., EVANSTON, ILL.

SEE YOUR JOBBER

A Complete Line of
 Tube Test **ERTL** Equipment

RADIOTECHNIC

TALK-BAK*

The first word used to abbreviate inter-communication systems.

NOKOIL

The first small permanent magnet dynamic speaker to be used in Talk-Bak* Systems.



Model 482 T.B. 5"
 Model 582 T.B. 6"
 Model 682 T.B. 8"

Write for information regarding these brand new speakers manufactured especially for Talk-Bak* Systems and requiring no equalization.

Ask for the name of our nearest distributor. Wright-DeCoster distributors are always anxious to cooperate.

WRIGHT-DeCOSTER, Inc.
 2253 UNIVERSITY AVE., ST. PAUL, MINNESOTA
 Export Dept.: M. Simons & Son Co., New York
 Cable Address: "Simontrice"
 Canadian Office: Associated Sales Co., Guelph, Ont.

*Copyrighted.

BETTER SERVICE **MORE PROFIT**

A Complete Line of Radio Parts For Service Men Under One Trade Name




Condensers
 Resistors
 Tubes
 Transformers
 Vibrators
 Volume Control
 Antenna Kits

SERVICE TO THE RADIO INDUSTRY
 If You Are Handicapped in Rendering SERVICE to Your Customers and or—if You Are Handicapped in Realizing SUFFICIENT PROFIT for Yourself and—if Your Reputation Warrants Our Assistance—
 Send for Details and Application Blank to
AMERICAN APPLIANCE ASSOCIATES, INC.
 Central Terminal Bldg., Albany, N. Y.

"ASK ANY MECHANIC" he'll tell you

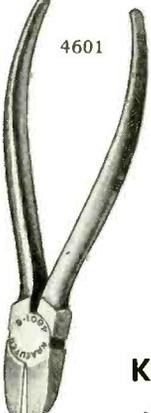IF IT'S QUALITY YOU'RE LOOKING FOR, REMEMBER THE NAME **KRAEUTER**



4601

That's because Kraeuter Pliers do the job quicker and better. As, for example, the diagonal cutting pliers 4601 shown here, made especially for close cutting and precisely fitted for exact work.



KRAEUTER & CO., Newark, N. J.
 (Pronounced KROY-TER)
 Manufacturers of Highest Quality Pliers and Tools Since 1860

"then send an old man to fix my radio!"




Even the sultan knows that the old, experienced radio man will use Ward Leonard Replacement Units. They enable the service man to do satisfactory work that lasts and thus build up customer "good will."
 Visit our booth 107, Radio Parts Show


WARD LEONARD ELECTRIC COMPANY
 36 SOUTH STREET, MOUNT VERNON, N. Y.

Please send me Bulletin 507-A.

Name
 Street
 City State
 Jobber

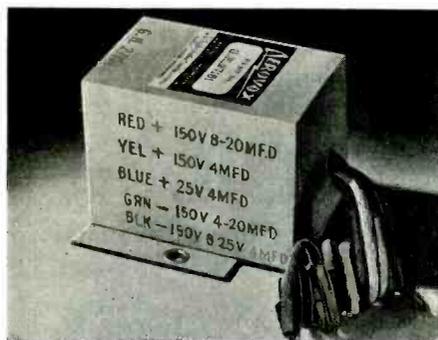

**WHICH
WILL YOU USE?**

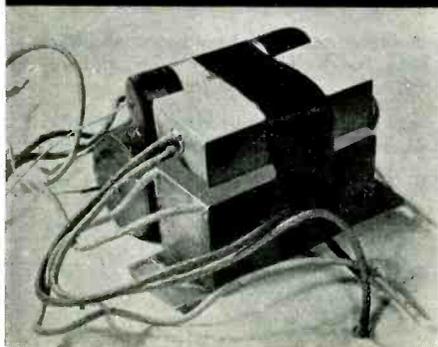

The AEROVOX Exact-Duplicate Replacement Condenser, of course, rather than the improvised collection of standard units taped together and jammed in place. And that's a wise choice, because

- ★ AEROVOX Exact-Duplicate Replacements fit right, work right, look right.
- ★ They restore the radio set to original condition. Set owner bound to be pleased.
- ★ Meanwhile, you save time, trouble and actual money, for an exact duplicate usually costs less than makeshift arrangement.
- ★ You build up reputation for good work. Customer pays promptly. No return calls to make good.
- ★ And now, most condenser manufacturers are following in the AEROVOX footsteps!

SEE US at Booth 62 Radio Parts Show, Chicago! We've much to show you and tell you. But if you can't make it, write for brand new catalog.



PUBLIC ADDRESS—continued

rooms of any normal home are comparatively small and well filled with furniture.

Places of public assembly present a different picture. Since sound moves slowly (about 1,000 feet per second) there is an appreciable lapse of time between reflections of sound waves from opposing walls. There are large blank surfaces that will reflect waves of even the lowest frequency without breaking them up. These factors permit and encourage various types of acoustic distortion. The quality of sound at the loudspeaker may be no criterion at all of the quality heard by the audience.

Acoustic problems include the acoustic distortion of quality and acoustic feedback that all Service Men know is likely to accompany use of a microphone.

Acoustic problems also include the question of volume distribution, seeing to it that sound is loud enough in the furthest seats without being too loud in the nearest seats, and overcoming dead spots and loud spots which may appear almost anywhere by virtue of acoustic conditions.

VOLUME DISTRIBUTION

Taking the last point first, bad distribution can be caused by using the wrong speakers for the job, by improper placement or pointing of the speakers and by acoustic reflections that emphasize sound at some points and destroy it at others.

Volume distribution is selective with reference to sound frequency. The ideal distribution presents an equal volume of every frequency to the ear of every listener. The ideal is never reached in actual practice, but it can be very closely approached.

However, even moderately satisfactory distribution is difficult or impossible to obtain unless a sufficient number of speakers equipped with the necessary type of baffle are used. Where sound is to be distributed over reasonably large distances, indoors or outdoors, the trumpet-type of baffle is usually most effective. Unless sound can be projected there is little chance of getting enough volume far back without blasting the ears of the nearest listeners. With trumpets, however, the main beam is sent out over their heads; they get the spillage, and if the trumpet is pointed with sufficient care the spillage in front will substantially equal the beam volume at the rear. Where the positioning is done properly the middle seats, at which the spillage begins to fall off, are those in which the beam just begins to cut in.

Where sound is to be spread over a

wide lateral range, a sufficient number of trumpets should be used.

Since 3 db represents that difference in loudspeaker volume which the ear is capable of detecting, the volume control may be calibrated in 3 db points. A frequency test record may be played, and the volume control turned down until sound is lost. The control is then raised 3 db, and sound is heard. In any portion of the area to be supplied, sound should still be heard, and, in any portion of that area sound should be so low that turning the volume control down 3 db will cause it to be lost. If this can be done at some central frequency, such as 1,000 cycles, and if playing a standard phono record of music recorded at fairly even level shows no glaring discrepancy in the overall volume at all frequencies, distribution may be considered commercially satisfactory in the present stage of the art. The musical record must follow the single-frequency test, for sound at one frequency is deceptive by reason of the possibility of standing waves. These are repeated reflections of sound between two opposing surfaces, in which the reflections happen to be so phased that the sound is strongly reinforced. Of course, at other frequencies (except harmonics) the phase relations will not be the same, and the same reinforcement will not take place. A standing wave may, with the single-frequency test just described, show excellent results in a spot that really is dead to overall sound.


In indoor work sound reflection may seriously interfere with the desired distribution. Very often the best pointing for the speakers is not all that which the eye would guess it to be and can be obtained only after prolonged and repeated tests and adjustments checked by ear.

REVERBERATION

Reflection is also responsible for many forms of acoustic distortion of quality.

Of these, the commonest is too much reverberation—that is, excessive reflections repeated from wall to wall and prolonging the sound after it should normally die away. This condition not only makes for an unnatural quality, but also causes sound to overlap with the result that the audience has difficulty in hearing and understanding it. Reverberation is essentially an indoor trouble. Acoustic treatment for it involves the introduction of extensive areas of sound absorbing material, which is a costly process. In the absence of such treatment the best remedy is to keep the volume just as low as is

60 watt amplifier
for 6L6 tubes

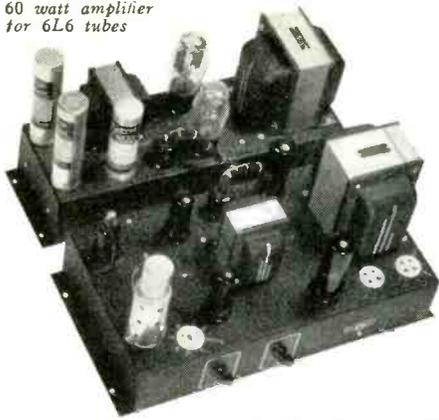

Sound Engineers! Build your own Amplifiers from STENTORIAN Nuclei

YOU may hunt high and search low, but you won't find elsewhere such uniformly good response at ALL frequencies . . . such low hum level and low distortion at full output. New circuits for 15, 30 and 60 watt units feature high gain—for crystal or velocity mikes. Attenuated input for line or phono. Terminals for single or D.B. mikes with built-in mike current supply. Outputs for all standard voice coils or lines. Best of all, you build it with **LARGE PROFIT** using only screw-driver, pliers and soldering iron. Get Bulletin 46!

Booth 100-101, TRADE SHOW, June 10-13



GENERAL TRANSFORMER CORP.

502 S. Throop St., Chicago

PUSH P.A. FOR REAL PROFIT

LOOK AT
THIS BUY—
20

WATT PORTABLE
SYSTEM WITH
SLIP-IN CASE
NOTHING ELSE
TO BUY—READY
FOR OPERATION

\$82.95
MODEL
860-P



The above is a typical value in the most complete line of P.A. Systems in the world. Three or four rentals will pay for the complete LAFAYETTE system—and after that the alert servicer is "pushing" up his bank balance. Remember—just around the corner from almost anywhere is a P.A. prospect. There is gold in them thar P.A. jobs—start "pushing."

WHOLESALE RADIO SERVICE CO. INC.

NEW YORK, N. Y. • CHICAGO, ILL. • ATLANTA, GA.
100 SIXTH AVENUE • 901 W. JACKSON BLVD. • 430 W. PEACHTREE ST. N. W.
BRONX, N. Y. • NEWARK, N. J. • JAMAICA, L. I.
542 E. FORDHAM RD. • 219 CENTRAL AVE. • 90-08 • 166th STREET
(MAY 1937)

WHOLESALE RADIO SERVICE CO., INC.

100 Sixth Avenue • New York, N. Y.

Rush FREE catalog No. 68-5F7

NAME.....
ADDRESS.....
CITY..... STATE.....



FREE

PUBLIC ADDRESS—continued

consistent with good hearing. Another remedy is to point the sound directly at the audience. Human beings and their clothing have very high absorption factors. An average individual will absorb as much sound as would be lost through a window opening of four and a half square feet.

Concentrated reverberation is echo; the remedy lies in finding the reflecting surface and pointing sound away from it. If this cannot be done the surface in question must be covered with absorbing material.

Insufficient reverberation destroys the illusion of natural sound—takes out the sparkle and life. "Dead" rooms are encountered occasionally, and are somewhat common where sound treatment to reduce reverberation has been overdone. Primarily, however, insufficient reverberation is an outdoor trouble, and is the reason why outdoor band stands and the like are built with concrete sound reflectors.

Reflection of sound is never the same at all frequencies; neither is the efficiency of sound-absorbing materials. Frequency discrimination in the reflection of sound proves troublesome occasionally, but becomes particularly serious when standing waves are created since these cause an intense reinforcement of some frequencies in some areas. Repointing the speakers (being careful to maintain sufficiently satisfactory distribution in the process) usually helps eliminate the more drastic manifestations of this trouble. Stubborn cases may require extensive treatment with acoustic materials.

ACOUSTIC FEEDBACK

Acoustic feedback between loudspeakers and microphone is familiar to everyone who has done p-a work. There are a number of remedies which may be used alone or in combination: (1) directional baffles to point sound away from the microphone or from surfaces that may reflect it to the microphone; (2) directional microphone to limit the angle of response, and (3) microphone, amplifier and speakers—speakers especially—of flat characteristic which will avoid feedback caused by peaks at some one frequency while the overall volume still remains low, using the mike close-up (which requires one that doesn't sound boomy when so used) to limit the sensitivity of the system. A precaution that scarcely deserves the name of remedy, but still is sometimes overlooked, is, of course, the obvious one of placing microphones and loudspeakers in such relative locations that the former will receive a minimum of the sound emitted by the latter.




DOUBLE-UNIT DESIGN—
a distinctive CROWE feature—permits providing each car manufacturer's official style dial (airplane or porthole) with panel mounting kit!

QUICK, EASY ASSEMBLY

Assembly of all parts on sub-panel bracket previous to installation in car panel assures perfect alignment and correct operation. Flexible connection from tuning control to dial is adjustable for smooth performance.

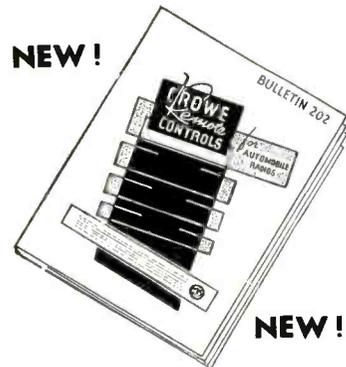SAME CONTROLS FOR ALL CARS! Same controls and shafts can be put on any car and used again when moving radio to another car. A panel kit is the only new part required on re-installation jobs.



Send for NEW Bulletin 202

—containing complete line of CROWE Auto-Radio Remote Controls. Also, valuable ready reference data sheet showing exactly what controls to use with each of 100 different models of auto-radios.

CROWE NAME PLATE & MFG. CO.
1775 Grace Street
CHICAGO, ILLINOIS

ASSOCIATION NEWS . . .

IRSM REPORTS

Convention and Trade Show

The convention committee reports a complete program for the fifth annual convention of the Institute of Radio Service Men, to be held at the Stevens Hotel, Chicago, June 10 to 13. A lecture hall in which the technical sessions are to be conducted is located in one corner of the exhibition hall where the trade show will progress. During the duration of the show the following program will be presented:

Thursday, June 10

2:00 P.M.-7:30 P.M.

Registration and viewing of exhibits.

7:30 P.M.

"Radio Tomorrow," by O. H. Caldwell, *Radio Today*, New York City.

8:00 P.M.

"Proven Merchandising Ideas That Will Boost Profits," by Sandy Cowan, *SERVICE Magazine*, New York City.

8:30 P.M.

"Universal Coils," by Charles S. Linell, Carron Manufacturing Co.

9:00 P.M.

"Psychology of Selling Service," by J. P. Kennedy, Triumph Manufacturing Co., Chicago.

Friday, June 11

2:00 P.M.

"Crystal Devices in the Service Field," by J. A. Altmeyer, Brush Development Co., Cleveland, Ohio.

2:30 P.M.

"Recent Developments in Crystal Microphones and Phonograph Pickups," by Ralph P. Glover, Shure Brothers, Chicago.

3:00 P.M.

"New Developments in Crystal Microphone Cable," by N. Hogenbirk, Belden Manufacturing Co., Chicago.

3:30 P.M.

"The Development of Heavy Duty Vibrators and Converters," by W. W. Garstang, Electronic Laboratories, Inc., Indianapolis, Ind.

4:00 P.M.

"Mutual Conductance Tube Testers," by J. R. Barnhard, Hickok Electrical Instrument Co., Cleveland, Ohio.

The evening program will be under the auspices of the IRE.

6:00 P.M.

Institute of Radio Engineers' Banquet.

"Tubes," by Roger Wise, Chief Engineer, Hygrade-Sylvania Corp., Emporium, Pa.

"Instruments," by Kendall Clough, Clough-Brengle Co., Chicago.

"Receivers," speaker to be announced.

The Saturday afternoon program will be under the auspices of the ARRL.

2:00 P.M.

"Amateur Transmitting Tubes," by A. Anderson, Taylor Tube Co., Chicago.

2:30 P.M.

"Antennas and Antenna Systems," by Robert Wood, Galvin Manufacturing Corp., Chicago.

3:00 P.M.

"Recent Research Developments on Ultra-High-Frequency Problems," by Dave Elam, Montgomery Ward & Co., Chicago.

3:30 P.M.

"Modern Transmitter Design," by Henry Argento, Raytheon Production Corp., Waltham, Mass.

4:00 P.M.

"Amateur Receiver Design," by K. W. Miles, The Hallicrafters, Inc., Chicago.

4:30 P.M.

"Oscillographic Measurements on Amateur Transmitter and Receiver Equipment," by Floyd Faucett, Supreme Instrument Corp., Greenwood, Miss.

5:00 P.M.

"Scientific Method of Improving Code Speed," by T. R. McElroy, National Code Champ.

8:00 P.M.

Installation of IRSM Officers; John T. Rose, presiding.

8:30 P.M.

"How to Choose Test Instruments," by John S. Meck, Electronic Design Corp., Chicago.

9:00 P.M.

"A Technical Discussion of Inter-Office Communication Systems," by Robert G. Herzog, Editor, *SERVICE Magazine*, New York City.

9:30 P.M.

"Oscillographic Demonstration of New Developments in Receiver Circuits," by Charles Herbst, RCA Manufacturing Co., Inc., Camden, N. J.

Sunday, June 13

1:30 P.M.

"A-C, D-C Ballast Tube Resistors," by Edward Trefz, Clarostat Manufacturing Co., Inc., Brooklyn, New York.

2:00 P.M.

"Twenty-Thousand-Ohms-per-Volt Radio Testing Instruments," by O. J. Morelock, Weston Electrical Instrument Corp., Newark, N. J.

2:30 P.M.

"Auto Antennas," by Neal Bear, Ward Products Corp., Cleveland, Ohio.

3:00 P.M.

"New Tube Developments," by Walter Jones, Hygrade-Sylvania Corp., Emporium, Pa.

4:00 P.M.

"Practical Testing of Vibrators," by I. M. Slater, P. R. Mallory & Co., Inc., Indianapolis, Ind.

4:30 P.M.

"Hum and Distortion Problems in P-A Work," by J. H. Kleker, Thordarson Electric Manufacturing Co., Chicago.

7:30 P.M.

"Noise in Volume Control Circuits," by W. H. Fritz, Centralab, Milwaukee, Wis.

8:00 P.M.

"Speakers and Speaker Systems; Their Proper Selection and Application," by Austin Ellmore, Utah Radio Products Co., Chicago.

8:30 P.M.

"Vacuum Tube Voltmeters and Their Applications to receiver Test Problems," by R. L. Barr, Clough-Brengle Co., Chicago.

9:00 P.M.

"Identification of Interference Sources, Including a Demonstration of Their Sound and Wave Form," by C. W. Metcalf, Tobe Deutschman Corp., Canton, Mass.

11:00 P.M.

Exhibits close.

Newark Chapter

The Newark Chapter of the Institute of Radio Service Men held a regular meeting May 27, 1937, at the Hotel Douglas, Newark, New Jersey.

The guest speaker was Bruce Burlingame, well known as an authority on test equipment. The subject of the talk was "Application of Test Equipment to Various Stages of Receiver."

RADIO SERVICE ASSN. OF CALIFORNIA

At the May 17 meeting, held at 921 Harrison Street, Oakland, Cal., B. C. Bridges of the Alameda Police Dept., spoke on "Fingerprinting and Criminal Investigation." This was a welcome and interesting diversion from the usual radio technicalities.

"Ocktail" Al Grabau has a couple of newly painted, higher priced tubes for our consideration. And we still have some more election to get off our chests. We plumb overlooked the fact that Wil Styles and Wally Wahlgren have been serving on the Board on borrowed time. So two new members must be elected at the next meeting. . . . Frank Jallu, Carl Penther, Claire Lanam, and Al Schoss have been nominated, so take your pick and come and vote for two.

At last meeting the nominating committee reported that of our members, the one most suitable, and who was able and willing to take the job of Treasurer, was Don Caples. This choice seemed to be mutually satisfactory and a white ballot was cast. Take a bow, Treasurer Caples! (Looks to us like he might be full of Wim and Winegar and it might be a good idea to bring along some Dough for Dues.) Carl Penther reviewed an RCA article on External Cross-Modulation which answered a lot of puzzling questions. . . . Al Grabau gave the dope on the 5T4. . . . Our speaker, Jules Cohn of the Jensen Company gave a fine talk and an eye-opening demonstration with a gadget known as a "Bass-Reflex" baffle. . . . Of which more anon.

Members and their families and friends have been invited to hear Prof. Lester E. Reukema give a talk on Earthquakes. This was scheduled for Monday, May 24, at 8:00 P. M., in Room 2503 of the Life-Science building, on the Berkeley Campus. Those of us who have heard Prof. Reukema when he gets turned loose on an engrossing subject such as this needed no further invitation.

We have an interesting talk scheduled for our meeting of June 7. Robert S. Prussia, Lighting Engineer, will speak on Light and Lighting Effects and demonstrate various phenomena with his equipment.

Hundreds of units to choose from.



Composition and wire-wound types.



Exact resistance and taper required.




Correct shafts—no sawing or forcing.



Grid bias resistors supplied where needed.



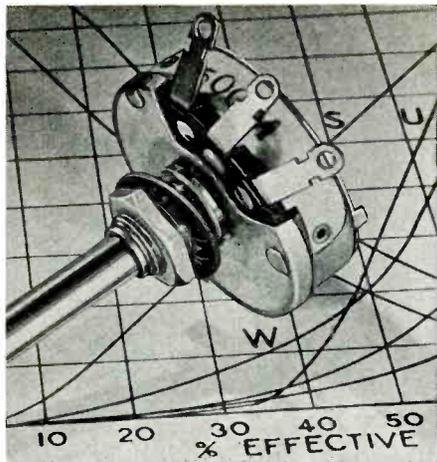Backed by most accurate and complete listing.



Matched!

You save time, trouble and money when you insist on CLAROSTAT Exact Duplicate Controls. • These units are right electrically, mechanically, visually. • And that fussy customer is satisfied. • So ask for your copy of our Volume Control Replacement Guide.

CLAROSTAT Manufacturing Co. Inc.



285-287 NORTH SIXTH STREET
BROOKLYN, NEW YORK, U.S.A.

• OFFICES IN PRINCIPAL CITIES •

DUMONT

ELECTROLYTIC CONDENSERS

GUARANTEED QUALITY

NOW AT REDUCED PRICES



MR. SERVICE MAN

Regardless of the prices you pay for condensers, you will find DUMONT QUALITY far superior. Self-healing prevents any possibility of breakdown even if overloaded. This exclusive feature (patent pending) is found only in DUMONT Electrolytics. Try an assortment today and be convinced. Used by the U. S. Government in large quantities—ample testimony of their true quality.

Exact duplicates for every radio.

Licensed under U. S. A.
Patent reissue No. 19604.

For free catalog and your nearest Dumont jobber, write to us.
SALES AND JOBBER TERRITORY OPEN

Manufactured by
Dumont Electric Co., Inc.

514-516 BROADWAY
NEW YORK, N. Y.



Paper — Mica — Electrolytic Capacitors

NOISE-MASTER

ALL-WAVE ANTENNA

Kills

"Man-made" Static

"NOISE-MASTER"
No. 14
List Price \$6.75

Brings in overseas signals stronger, and eliminates "man made" static on broadcast as well as short-wave band. For better reception in EVERY location.

"NOISE-MASTER"
No. 18
List Price \$3.40

First time at this popular price a SELF-SELECTING antenna of the simple doublet type, designed to clear up short-wave reception.

"NOISE-MASTER"
No. 19
List Price \$4.30

This is another SELF-SELECTING model of the doublet type, with junction-box in the antenna line. Assures finer all-wave reception.



This trademark guarantees the best in antenna and radio wire products.



On Broadcast as Well as
on Shortwave Frequencies

Licensed by Amy, Acevas & King, engineered by Corwico . . . every Service Man knows that's plenty to say about any antennal! Try one of these modern units on your next installation . . . a real good will builder for YOU!

Write for descriptive literature

CORNISH WIRE CO., Inc.

30 CHURCH STREET

NEW YORK CITY

TRIAD

INVITES THE TRADE
TO VISIT

Booth No. 102

National Trade Show
Radio Parts Manufacturers

AT

STEVENS HOTEL—CHICAGO

JUNE 10-13, INCL.

TRIAD MANUFACTURING CO., INC.
PAWTUCKET RHODE ISLAND

THE QUALITY NAME IN RADIO TUBES


HIGHLIGHTS ...

INTERFERENCE ELIMINATION LESSON

Recognizing a steadily growing importance of interference elimination as a profit-builder for Service Men, the Sprague Products Co., North Adams, Mass., makers of Sprague Condensers, have made arrangements with the National Radio Institute of Washington, D. C., to distribute a number of free copies of the N. R. I. Lesson, "How to Eliminate Man-Made Interference." Requests for the lesson booklet should be made directly to the Sprague Products Co.

RIDER DISPLAYS

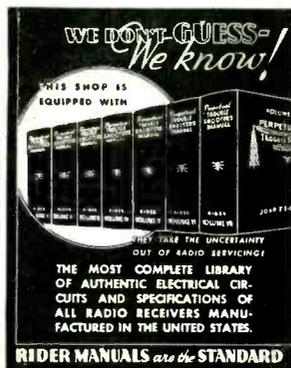Service Men who own the complete set of 7 Rider Manuals can obtain two certificates, one for framing and the other for the bill folder, as well as the display illustrated. These devices are intended as a means whereby the Service Man can assure his customers that he has all the in-



formation needed to repair any receiver.

The certificates and display may be obtained by sending the title pages from the seven Rider Manuals together with a return address to John F. Rider, Publisher, 1440 Broadway, New York City.

STEWART DISPLAY

The F. W. Stewart Mfg. Corp., 340 W. Huron St., Chicago, have added an all-metal display to their line. The 23- by 50-in. stand is designed for displaying the Stewart custom built radio panel plates as they would appear on the car instrument panel.

The display board consists of 29, 1937 panel kits, 1 tuning unit, 1 volume control (with on-off switch), 1 pair of flexible control shafts, necessary wiring with fuse and the display board with the panels mounted.

An illustrated folder explaining the features of the display may be obtained from the manufacturer.

George and Victor Mueher looking over a resistance brain child. George heads the engineering activities for Clarostat Mfg. Co., Inc., Brooklyn, N. Y., while Vic is in charge of sales.



Executives of the Cinaudagraph Corp., Stamford, Conn. Sitting: S. R. Hoyt; H. W. Harwell and H. C. Seaman. Standing: L. B. Cornwell and H. H. Friend.

SOLAR CATALOG

Listing their line of dry electrolytic, wet electrolytic and paper exact replacement condensers, the Solar 1-R catalog also carries a-c motor starting replacements.

This catalog is companion to and supplements Solar catalog 8-S, general condenser catalog recently announced; both are available on request from the Solar Manufacturing Corp., 599 Broadway, New York City.

AMPERITE CONTEST FORM

The Amperite Company, 561 Broadway, New York City, has prepared a special form stipulating the details of their recently announced contest. A microphone and stand is offered as first prize in the contest in an effort to find the best name for the stand. Duplicate prizes will be awarded in case of ties. The ten next best

Sam Ruttenberg, of Amperite, New York City, inspecting a RBH microphone retrieved from the Portsmouth, Ohio, flood. The microphone still worked after having been under water for 10 days.



names will receive a stand free. The contest closes July 1. The stand is illustrated and described on the form.

Copies of this form may be obtained by requesting Bulletin NSH directly from Amperite.

This contest will be one of the features of the Amperite display—booth 36—at the Chicago Trade Show.

OPEN HOUSE AT QUAM-NICHOLS

The Quam-Nichols Co., manufacturers of radio speakers and equipment, is holding open house at their factory during the Convention and Show in Chicago. All manufacturers, jobbers, dealers and Service Men are cordially invited to visit this plant. Here is an opportunity to see a speaker factory in action. Capacity is 10,000 speakers per day. Interesting innovations in manufacturing procedure and equipment, as well as useful speaker information make this trip worth while. The factory is located at 33 Place and Cottage Grove Ave.

AEROVOX CATALOG

Aerovox Corp., 70 Washington St., Brooklyn, N. Y., is issuing its largest catalog in years—twice the number of pages of recent editions.

Copies of the catalog may be obtained directly from Aerovox.

Aerovox will display their complete line at the National Trade Show, booth 62.

Tore Lundahl, sales manager of Technical Appliance Corp., New York City, at his desk working on correspondence.



HIGHLIGHTS—continued

NATIONAL UNION CLOCKS

National Union Corp., 570 Lexington Ave., New York City, have released to the service trade a specially designed electric clock. The face glass size is 16 by 24 in. with a 1-in. two-tone black and silver frame. The face design is in five colors with a silver mirror.

The copy has been developed by a pat-



ented process to produce a neon effect when illuminated. The clock is equipped with a switch for light control so that the lights can be extinguished without affecting the operation of the clock movement. The movement is driven by a Hammond motor.

National Union is giving this clock to Service Men throughout the country with the purchase of National Union tubes.

BOOK REVIEW


ALTERNATING CURRENTS IN RADIO RECEIVERS, written and published by John F. Rider, 1440 Broadway, New York. 96 pages, hard covers, price 60 cents.

In this latest volume in the Hour a Day with Rider series, John F. Rider covers the subject of alternating currents in a manner which should appeal to the Service Man. In the opening sections of the book, the Service Man is introduced to the fundamental ideas associated with alternating currents, such as the physical concept of an alternating current, clear explanations of the meaning of cycle, frequency, amplitude, sine wave, and average, peak and effective values of alternating currents.

The explanations of phase are of special interest in view of the widespread use of phase inversion, push-pull, a. f. c., and other circuits which depend for their action upon the presence of certain phase relations. From the standpoint of the service field the author's treatment of the subject of sine waves and complex waves is to be recommended. In this connection, the origin of harmonic frequencies and their effect upon the waveform of alternating currents and voltages is well illustrated with numerous drawings and actual unretouched oscillograms made in the author's laboratory. Service Men will find much of value in this practical, well illustrated volume.

**For Quiet Radio and Amplifier Performance,
For Radio Service Work Which Satisfies . . .
CHOOSE CONTINENTAL Carbon Products!**

Insulated Carbon Resistors

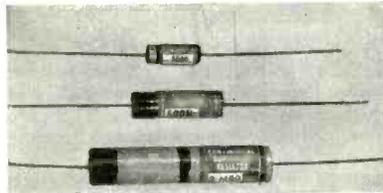

Quiet, moisture-proof insulated resistors are now the standard of the radio industry. This style of resistor was pioneered by CONTINENTAL Carbon, who now offers the choice of bakelite or ceramic insulation.

- | | |
|--------------------------------------|--------|
| | List |
| 1/2 Watt, M1/2, 5/8"x7/32", bakelite | \$.017 |
| 1 Watt, M1, 1"x9/32", bakelite | .20 |
| 3 Watt, M3, 2"x13/32", bakelite | .30 |
| 1/2 Watt, G4, 1"x1/4", ceramic | .17 |
| 1 Watt, D2, 1 3/4"x1/4", ceramic | .20 |
| 3 Watt, E2, 2"x3/8", ceramic | .30 |
| 5 Watt, H5, 3"x9/16", ceramic | .50 |

FREE, Service Engineering Bulletin 104-B

High Efficiency Capacitors



Charge any CONTINENTAL condenser at full rated voltage. Let it stand an hour and discharge it. The crackling blue-white spark which results is proof of negligible leakage and high efficiency! CONTINENTAL condensers range in size from small tubular T models, to Model P illustrated above, to Models E & L, which are available in standard sizes to more than 20 mfd.s! Special high voltage Model W condensers are designed for transmitters of commercial, police, or amateur design. Ask your jobber to stock CONTINENTAL condensers.

FREE, Service Engineering Bulletin 103-A

Auto-Radio Accessories



Suppressors which do not affect the performance of your car and always improve auto-radio reception are the features of CONTINENTAL's new 5,000 ohm insulated spark suppressors! A complete line of ignition noise suppressors at a list of only 30 cents each! CONTINENTAL makes Filternoys devices for every circuit of an auto electrical system—offering the certain method of keeping an auto radio sold—from list prices of 40 cents to \$1.00 in standard sizes.

FREE, Service Engineering Bulletin 101-A

Filternoys Suppression Devices



Noise elimination offers the most fertile field for experienced radio servicemen, and CONTINENTAL Filternoys provide the means of capitalizing upon this market. Filternoys are made in three types: Suppressors to block interference at its source; Rejectors to block interference out of a receiver; and Diverters to tune out power line interference elimination. Send 10 cents for Handy Pocket Data on Interference, postpaid.

FREE, Service Engineering Bulletin 105

CONTINENTAL CARBON Inc.

13900 Lorain Ave. Cleveland, Ohio
Canadian Plant, Toronto, Ontario

TWO WAY COMMUNICATION



Inter-'phones, office to office, studio to studio, factory, shipping depts., house to garage, and hundreds of other uses. Positive in operation.

Simple to install. Modern in appearance. Any number of 'phones on same line.

\$15. per station (dealers and jobbers write for discounts).

UNIVERSAL MICROPHONE CO., LTD.

Box 299

INGLEWOOD, CALIF., U. S. A.

THE MANUFACTURERS . . .



ARVIN AUTO RADIO

The makers of Arvin auto radios, Noblitt-Sparks Industries, Inc., Columbus, Ind., have announced a low-priced 6-tube tailor-fit auto radio complete with in-the-set speaker and any one of the 47 Arvin matching panel or universal controls.

The new Arvin radio is known as the Model 9A. The chassis and speaker are packed as one unit. All Arvin controls—matching panel and universal types—are packed individually. Dealers may order any one of the 47 Arvin types for installation with the 9A.

This receiver has a 3-gang condenser and a 5-in dynamic speaker. Many of the improvements of the higher priced Arvins are built into the model. The metal case is finished in taupe morocco.

PANEL INSTRUMENTS

A line of low-priced panel instruments with bridge type construction and soft iron pole-pieces has been announced by the Simpson Electric Company, 5216 Kinsie Street, Chicago. This type of construction, states the Simpson organization, has only been available in instruments selling at considerably higher prices. Increased initial accuracy and lasting accuracy over a period of years are the advantages claimed for this construction.

CENTRALAB TONE SWITCHES

Centralab, 900 E. Keefe Ave., Milwaukee, Wis., have announced a tone switch. The switch is available in 3 types: 1 pole, 2 positions; 1 pole, 3 positions and 2 pole, 2 positions. The common terminal is insulated from the shaft and bushing in all




types. The controls are designed chiefly for use as step-type tone controls in mid-get receivers. The switch may be adapted to other uses, however.

Additional information may be obtained from the manufacturer.

CORNELL-DUBILIER CAPACITORS

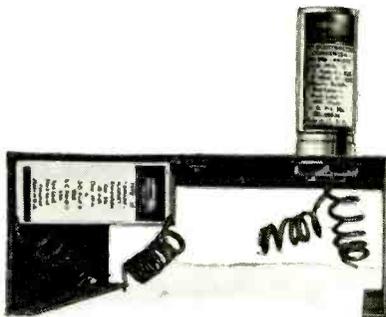Flexibility in mounting and compactness in design makes the Cornell-Dubilier JR and KR series of etched foil dry electrolytic capacitors valuable to the Service Man, it is said. The type JR is enclosed in a square silver container. The type KR, shown mounted on top of the chassis, is less than one-half the size of a similar



can-type electrolytic.


Additional information may be obtained from the Cornell-Dubilier Corp., South Plainfield, N. J.

ICA AUTO ANTENNAS

The Insuline Corporation of America, 25 Park Place, New York City, are marketing a series of 6 streamlined auto antennas. Five are finished in chromium. The top of the car need not be drilled to install any of the models.

The Moto-Whip, a streamlined antenna, can be adjusted for city and country driving. The Hinge Whip is a telescopic antenna attached to the hinge pin of any car while the Auto-Whip is similar to the Hinge Whip except that it is a solid one-piece flexible rod.

The Windo-Pole is a black Duco parker-

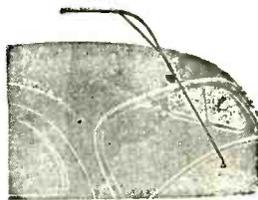

ized finish antenna for home use. It is a telescopic antenna, extends to a height of 8 feet and may be attached to any window sill.

Additional information may be obtained directly from ICA.

CROSLEY AUTO RADIO

Crosley Radio Corp., Cincinnati, Ohio, have announced a new low priced auto-radio receiver.

The set is complete in itself, uses five tubes and is mounted in one piece under the instrument panel of any make car. One bolt mounts the receiver to the dash and two fasten it to the instrument panel. No remote control cables are used.



ELECTRO-ACOUSTIC AMPLIFIER

A Class A heavy-duty booster power amplifier, designed for general p-a applications requiring more than 30 watts of power, has been announced by Electro-Acoustic Products Co., Fort Wayne, Ind. The new amplifier, Model A-3041, may be used and added to the base Electro-Acoustic Model A-1831, 15-watt amplifier or the Model A-3023, 30-watt amplifier, either of which will supply sufficient input voltage for operation of any number of A-3041 amplifiers.

The combination is recommended for race courses, convention halls, cemeteries, organ and chime tower installations, large rentals, fair grounds, industrial call systems and other applications having high power output requirements.

The Model A-3041 incorporates beam power output tubes and is built with all parts enclosed. Connections between the base system and the A-3041 power stages are made through flexible cables and plugs.

Additional information may be obtained from the manufacturer.


RCA RECORD PLAYERS

As a successor to the R-93 model RCA Victor introduces the record-player model 93-A. In appearance the new instrument resembles a chest or a cigar humidor.

To replace the model R-93-2, the model R-94 has been announced. This instrument is housed in a hinged cabinet of walnut veneers. Both 10- and 12-inch records can be played on the R-94 with the lid closed. Automatic starting of the turntable and bass compensation are two of its features.

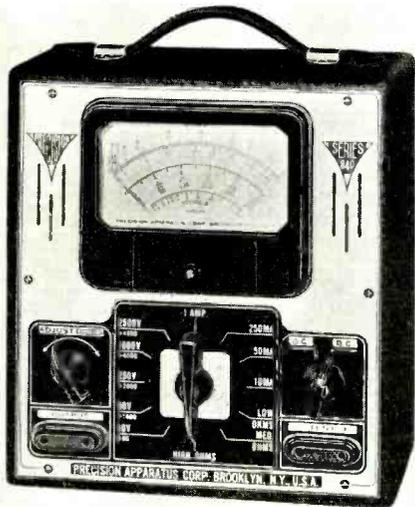The new instruments are of the type which reproduces phonograph records when connected to electrically operated receivers.





New PRECISION

MULTIMETER No. 840

Large D'Arsonval type meter (4 x 4 1/2). Molded metalized resistors. Shunts individually wire wound. Ball bearing type switches. "Telephone" cabled wiring. Leatherette covered, lock-cornered cases (7 1/2 x 8 1/2 x 4). Weight 5 1/2 lbs.

26 RANGES: A.C. volts at 1000 ohms per volt: 0-10 v., 0-50 v., 0-250 v., 0-1000 v., 0-2500 v. D. C. volts at 1000 ohms per volt: 0-10 v., 0-50 v., 0-250 v., 0-1000 v., 0-2500 v. D. C. current: 0-10 MA, 0-50 MA, 0-250 MA, 0-1000 MA. Resistance: Low ohms (shunt method) 0-400 ohms, 20 ohms center. Resistance as low as 1/4 of an ohm. Medium ohms, 0-1 megohm. High ohms, 0-10 megohms. Decibel ranges: -10 to +15; +4 to +29; +18 to +43; +30 to +65; +38 to +63. Output ranges: 0-10 v., 0-50 v., 0-250 v., 0-1000 v.

Net, less test leads and batteries
Model 840-P, Closed type with
removable cover, \$21.95.....

\$19.95

Precision Apparatus Corp.

821 EAST NEW YORK AVE., BROOKLYN, N. Y.

JULY SERVICE

A complete résumé and full technical description of new 1937-'38 radio receivers.


PLUS

Up-to-the-minute news on new developments in public address, auto-radios, test equipment and many other valuable features.

MANUFACTURERS—continued

SINE-WAVE GENERATOR

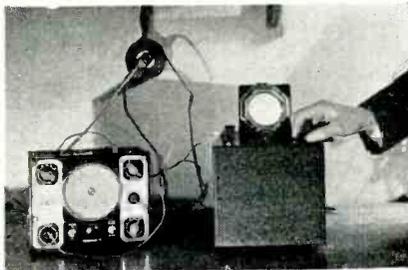The new Triumph Model 120A signal generator delivers both r-f and a-f or r-f modulated with the a-f in a sine-wave pattern. The generator covers a frequency band of 100 kc to 75 mc and the audio



modulation is a tone of 380 cycles.

A calibrated attenuator on the signal generator provides for accurate attenuation of the r-f output from 0 to 50,000 microvolts. The oscillograph in the illustration is a standard Triumph Model 800 3-inch combination oscillograph and linear sweep.

Further information may be obtained from the Triumph Manufacturing Co., 4017-19 West Lake St., Chicago.

ERIE INSULATED RESISTORS


The Erie Resistor Corp., Erie, Pa., announces a line of insulated resistors in 1/4 and 1/2 watt sizes.

The units are called "ceramic-sealed" insulated resistors and are completely covered with a preformed ceramic case and sealed at the ends with a high-dielectric ceramic cement which bonds itself to the insulating case, the tinned-copper terminal wires and to the brass cap covering the end of the solid molded carbon resistance pin.

Both the 1/4 and 1/2 watt insulated "ceramic-sealed" resistors are obtainable in all resistance values from a few ohms to several megohms. 1/4 watt unit measures approximately 1/4 by 1/2 in. The 1/2 watt size measures 1/4 by 3/4 in. Both sizes have 2-in. tinned-copper terminal wires.

UTC PREAMPLIFIER

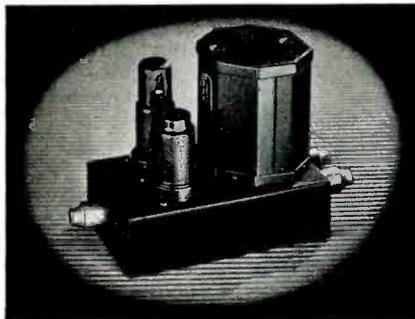
The United Transformer Corp., 72 Spring St., New York, N. Y., have just brought out a preamplifier which obtains its power supply directly from the main amplifier. It incorporates a 6F5 resistance coupled to a 6C5 providing 60 db of gain.



The input is high impedance and the output provides universal line impedance. Filtering is provided in the preamplifier to assure low hum level. If desired, a separate power supply can also be obtained for this unit.



POWER TYPE WIREWOUND RESISTORS

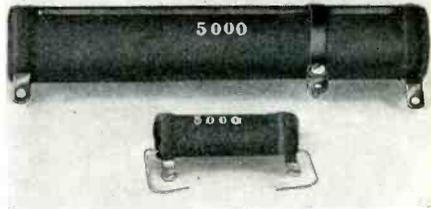

Coated with a cement that is treated with live steam in the process, these resistors are absolutely not affected by moisture. An alloy resistance wire is used for the element, which has a negligible change of resistance with temperature. This wire is hard soldered to the lugs so that there is no possibility of the connection opening.

Made in various ratings from 10 watts up, in both fixed and variable types . . . sizes from 25 watts up are provided with mounting feet . . . variable resistors are each provided with two sliders. . . .

FOLLOW THE ARROW
AND YOU FOLLOW THE LEADER

MICAMOLD PRODUCTS CORP.

Flushing and Porter Aves., Brooklyn, N. Y.

AUTO-RADIO Re-Installations

TRANSFER JOBS MADE EASY WITH Pre-Assembled UNIVERSALS

Universal Dashboard Controls have opened up a rich new market for extra profits. Now you can transfer ANY set to ANY car in only a few minutes' time. Mail the coupon today for illustrated Catalog.



No fussing around with loose parts. Single-unit control head—ready to slip into the dashboard opening. Hooks up with any set.

Beautifully-finished dashboard plates custom-styled for perfect match. Stocked for all car models (1937-36-35).

AT THE RADIO PARTS SHOW

JUNE 10-13

See the "MAGIC PRE-ASSEMBLER"

72 different parts miraculously transformed into one single unit! Come to Booth E—Stevens Hotel.

Universal

DASHBOARD CONTROLS

UNIVERSAL CONTROLS, INC.

21-07 40th Ave., Long Is. City, N. Y.



Please send your new Catalog D-4

Name


Address

Dealer Service Man Jobber

MANUFACTURERS—continued

OPERADIO 55-80 WATT AMPLIFIER

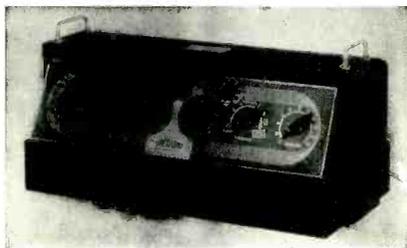The Operadio Model 855 incorporates four channel input, volume expansion, volume compression, visual overload indicator and visual output indicator. An



equalizer is also used for tone balancing.

Twelve tubes are used in the six stage high-gain unit.

Specifications and other details may be obtained directly from Operadio Manufacturing Co., St. Charles, Ill. Write for catalog S-12.

WESTON "MATCHED TWIN"

A servicing set, comprising both the Weston 20,000-ohm-per-volt analyzer and its "matched twin" tube tester in a single portable case, is now available to Service Men. Though the two instruments are electrically independent, it is said, that they form a balanced operating unit in function and design.

The flexibility of this dual-unit arrangement makes it possible for those who already own the supersensitive analyzer to utilize it as part of the new combination instrument by transferring it from its present case.

The "matched twin" servicing instruments may also be used conveniently for workshop panel mounting. This permits a symmetrical arrangement for built-in shop equipment.

Additional information and prices may be obtained from the Weston Electrical Instrument Corp., Newark, N. J.

WEBSTER INCREASES INTERCOMMUNICATING LINE

Webster-Chicago has added two systems and have revised and improved their two previous systems, for interoffice communication. All systems are now contained in plastic cases and can be secured in various color combinations.

Webster-Chicago has planned a complete display of their intercommunicating system line at the National Trade Show.

Additional information can be obtained directly from Webster Co., 5622 Bloomingdale Ave., Chicago.

FOX SPEAKER UNIT


The Fox Sound Equipment Corp., Toledo, Ohio, announces a 10-watt Alnico permanent magnet type dynamic unit. The unit contains the regular Fox type diaphragm, is enclosed in a water-tight aluminum case and is equipped with a standard connecting flange.

A one-piece metal diaphragm, electric dynamic units, aluminum trumpet horns, the B-5 Universal baffle type horn, and low level speaker, are among the items manufactured by the Fox Sound Equipment Corp.

MALLORY VIBRAPACKS

To provide portable power for radio transmitters, p-a equipment and similar apparatus, P. R. Mallory & Co., Inc., Indianapolis, Ind., have introduced a line of six-volt power supplies, called Vibrapacks.

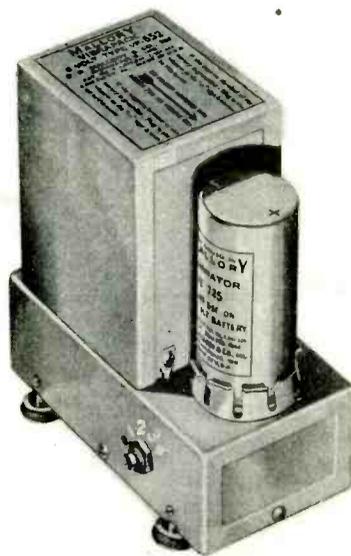The two high voltage models of Vibrapacks have a maximum rated output of 300 volts, 100 ma of rectified d-c with three lower voltages of 275, 250 and 225



volts available at the turn of a tap switch.

The lower voltage models of the Vibrapacks deliver 200-, 175-, 150- and 125-volts output and may be used for converting 110-volt a-c receivers for 6-volt battery operation.

Mallory Vibrapacks are manufactured in both synchronous or self-rectifying types, and in interrupter or tube rectifying types, the latter are required only when B— can not be at ground potential.

Additional information may be obtained directly from P. R. Mallory & Co., Inc.

UNITED SOUND AMPLIFIER

The United Sound Engineering Com-



pany's amplifier Model 20-E, shown in the accompanying illustration, is an example of recent design in 6-volt d-c, 110-volt a-c amplifiers and includes the electric eye monitor. Complete details of the 20-E are given in catalog 107S which may be obtained directly from the United Sound Engineering Company, St. Paul, Minn.

DEPENDABLE TEST INSTRUMENTS

The Radio City Products Co., New York City, announce their Dependable Models 306 tube tester and 701 signal generator.

The tube tester is designed with a view toward future advances in tube types, it is said.

The signal generator features attenuation from 1 microvolt to 1/2 volt through a constant impedance ladder network of 5 steps. The frequency range from 125 kc to 60 mc is covered.

Radio City Products Co. will display their products at booth 67 at the National Trade Show.

Additional information on Radio City Products may be obtained directly from the manufacturer.

UTAH P.M. SPEAKERS

Utah Radio Products Co. have expanded their line of permanent magnet dynamic speakers. Thirty-four models are available, with cone diameters ranging from five inches to fourteen inches, employing magnets weighing from five to forty-six ounces and with output capacities as high as thirty watts.

Inquiries on specifications and prices are invited. Visit booths 69 and 70 at the National Radio Parts Trade Show, or write Utah Radio Products Co., Orleans St., Chicago.

PRECISION MULTIMETER

Precision Apparatus Corp., Brooklyn, N. Y., announce their Model 840 Multimeter with five a-c voltage ranges; five d-c voltage ranges; four d-c ranges; three resistance ranges and five db ranges. The instrument uses a square type meter (approx. 4-in.) and has an accuracy of 2 percent.

Additional information can be obtained from the manufacturer.

VOCAGRAPH AMPLIFIERS

Vocagraph amplifiers and portable sound systems, announced by the Electronic Design Corp., 164 N. May St., Chicago, feature a reproducing principle termed "Hushed-Power." It is claimed that this development makes possible an amplifier with greater usable power output than can be achieved through former designs.


These amplifiers are offered in output ratings of twenty, forty and sixty watts. All have streamlined cases with built-in monitor speaker and indirect lighting of



the entire control panel.

An engineering bulletin, entitled "None Have Dared," may be secured without cost directly from the manufacturer.

6 New Auto Antennas by I C A

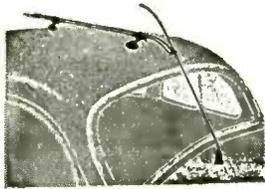

EAGLET
Twin Flow
A handsome Broadcast and Short Wave Antenna Utilizing the Doublet system of noise cancellation. Chromium finished, no drilling on top of car, easily installed any type of auto.

No. 4507 (Open windshield installation) List\$4.25
No. 4506 (Permanently closed windshield) List\$4.50


HINGE-WHIP TELESCOPIC ANTENNA

As illustrated; triple chrome finish; extends from 27" to 50". Attached to hinge pin of any car. Complete with lead in and hardware.....\$2.50

AUTO-WHIP NON TELESCOPIC ANTENNA

Similar to Hinge-Whip in mounting, but in one 40" length. Completely assembled. List\$1.95

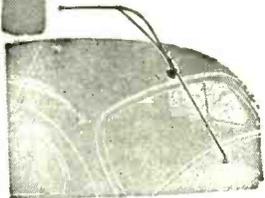WINDO-POLE HOME ANTENNA
Fastens to the window sill; telescopic, extending to 8 feet. Black Duco finish. Ideal for Broadcast and Short Wave reception. Complete\$2.25



MOTO WHIP
Streamlined Triple chrome finish, 62" length; adjustable for city and country driving. Easily installed. Used on any type car. Complete\$2.25

Write for FREE illustrated descriptive folder on Auto Radio items and complete ICA Catalog.

INSULINE CORPORATION OF AMERICA

25 Park Place, New York City
Mfg. Radio Parts since 1921



FREE

New 1938

Standard Brand Radio Catalog Listing more than 500 sets

SERVICEMEN and RADIO SALESMEN—represent **MODELL'S** in your territory and establish an independent business for yourself without a penny of investment.

We carry RCA - Philco - GE - Zenith — and many other makes of home electric sets, auto and boat sets, farm and camp sets of Nationally known manufacturers. Every set is brand new, guaranteed perfect and shipped in the original factory sealed cartons. Send for this new catalog TODAY. Write to Dept. It and mail to address nearest you.

Modell's - Wholesale Radio Division

NEW YORK, N. Y., 58 Cortlandt St.
CHICAGO, ILL., 56 W. Washington St.
ATLANTA, GA., 57 Forsyth St.

MODELL'S — WHOLESALE RADIO DIVISION

Send me free the new 1938 catalog listing over 500 Nationally known Standard Brand Radios—also your agency proposition on how to make money without any investment.

NAME
ADDRESS
TOWN STATE

MANUFACTURERS—continued

SYLVANIA TYPE 6T5

Hygrade-Sylvania Corporation, Emporium, Pa., have announced the type 6T5 tuning indicator tube. The 6T5 is designed for operation on 6.3 volts at 0.3 amperes.

Sylvania type 6T5 is a new tuning indicator tube which has operating conditions similar to those for the 250 volt rating of type 6G5. It differs from the 6G5 in that the visible indication is annular in shape. The lighted portion covers only a very narrow region at the periphery of the target when no voltage is applied to the central grid of the tube. When negative voltage is applied to the control grid the width of the fluorescent ring increases until it covers practically all of the target. Changes in annular width, or diameter of the shaded section, are more readily detected than are changes in the shaded angular sector when type 6G5 is employed.

Technical data and characteristics can be obtained directly from Hygrade-Sylvania.

SHURE STETHOPHONE

A new improved non-acoustic piezoelectric stethophone, Model 66A, is announced by Shure Brothers, 225 W. Huron St., Chicago. The new device is designed for pickup of heartbeats and chest sounds for reproduction and recording.

Extremely faint noises can be heard clearly and fully with the stethophone which would be difficult or impossible to



detect with the ordinary stethoscope. The stethophone is specially designed for high sensitivity to vibrations produced by the body and insensitive to "air-borne" or acoustic sounds. An outstanding feature of this new model is the anti-feedback design which permits the stethophone to be used near loudspeakers without acoustic feedback.

WRIGHT DECOSTER CABINET

Wright DeCoster, Inc., St. Paul, Minn., have announced a suede vehicle cabinet of modernistic design. A black grille is used which contrasts with the taupe cabinet. Chrome plated metal ornaments are at the top and bottom.

Across the back of the cabinet is a 4-



inch metal strip with a single stud for mounting. This arrangement makes the cabinet carry the weight of the speaker. The cabinet also has holes on the bottom for base mounting. The cabinet is square with rounded corners. Sizes are available for both 8- and 10-inch speakers.

An illustrative and descriptive sheet may be obtained directly from the manufacturer.



ELECTRIC RAZOR FILTERETTE



Ends Interference Caused By All Electric Razors!

Electric razors are fast becoming established as the perfect shaving device. Well over three million are now in use and the number of new users is growing rapidly. Electric razors invariably cause severe radio interference.

You can share in the profits of the rapidly mounting electric razor sale by selling the new TOBE ELECTRIC RAZOR FILTERETTE. Simply plug it in to the socket. This unit reduces interference remarkably. Early morning programs will again be popular in electric razor homes. List price, ONLY \$1.00.

There's a Tobe Filterette For Every Noise Problem

Of course, there's a complete line of larger TOBE FILTERETTES carried by many jobbers. TOBE is widely acknowledged as the leader in noise reduction. Don't think that just any filter will do. BE SURE YOU INSIST ON THE ORIGINAL and the BEST . . . TOBE FILTERETTES!



FILTERETTES

Skilfully Manufactured by

Tobe Deutschmann Corp., Canton, Mass.

..... and don't forget
At the CHICAGO SHOW
June 10th to 13th

See the new
TOBE LINE
FILTERETTES—CONDENSERS
INSTRUMENTS

Designed to Withstand ROUGH FIELD SERVICING

See Our Display, Booth 123, Radio Parts Show, Hotel Stevens. Headquarters for Practical Servicing Testers.

BUY RANGER EXAMINER



Model 640-740

COMBINATION VOLT-OHM-MILLIAMMETER and FREE POINT TESTER
No Extra Cases to Buy

PRECISION BUILT ONLY \$2700

• For That Duplicate Set of Servicing Instruments Advocated by Leading Radio Servicemen

• The Ranger-Examiner Model 640 Free Point Tester has eight automatic switch type and ten single action jacks. Five sockets for any type radio tube.

Model 740 Volt-Ohm-Milliammeter has 3" Square Triplett Precision Instrument. Scale readings: 10-50-250-500-1000 AC and DC Volts at 1000 Ohms per Volt (DC Accuracy 2%; AC 5%); 1-10-50-250 DC M.A.; 0-300 Low Ohms; High Ohms to 250,000 at 1 1/2 Volts. (Rheostat adjustment for 13 1/2 Volts for Ohm readings to 2 1/2 Megohms.) Batteries may be added permitting such readings in 250,000 Ohm steps. Low Ohms to 1/2 Ohm with 25 Ohms in center of scale. Backup circuit used. Current draw is only 1 M.A.

ALSO AVAILABLE AS SINGLE TESTERS,

READRITE METER WORKS
617 College Dr., Bluffton, Ohio

Please send me more information on Model 640-740; Model 640; Model 740. I am also interested in

Name

Address

City State

INDEX TO ADVERTISERS

A	H	S
Aerovox Corp. 386	Hygrade Sylvania Corp. 373	Solar Mfg. Corp. Third Cover
American Appliance Associates, Inc. 385	I	Standard Transformer Corp. 327
American Microphone Co., Inc., Ltd. 397	Insuline Corp. of America 395	Supreme Instruments Corp. 357
Amperite Co. 332-398	K	T
Amplifier Co. of America 398	Ken-Rad Tube & Lamp Corp., Inc. 397	Technical Appliance Corp. 345
Areturus Radio Tube Co. 349	Kraeuter & Co. 385	Thordarson Elec. Mfg. Co. 343
Astatic Microphone Lab., Inc. 355	M	Tohe Deutschmann Corp. 395
Audak Company 356	Mallory & Co., Inc., P. R. Second Cover	Triad Mfg. Co., Inc. 389
B	Micamold Prod. Corp. 393	Triplett Elec. Inst. Co. 369
Bell Sound Systems, Inc. 377	Modell's 395	Tung-Sol Lamp Works, Inc. 361
Birnback Radio Co. 398	Mueller Electric Co. 397	U
Brush Development Co., The. 377	Muter Co., The. 355	United Sound Engineering Co. 375
C	N	United Transformer Corp. 351
Centralab 329	National Union Radio Corp. 367	Universal Controls, Inc. 393
Cinaudagraph Corp. 331	O	Universal Microphone Co., Ltd. 391
Clarostat Mfg. Co., Inc. 380	Ohmite Mfg. Co. 398	Utah Radio Products Co. 371
Continental Carbon, Inc. 391	Operadio Mfg. Co. 363	W
Cornell-Dubilier Corp. 365	Oxford-Tartak Radio Corp. 375	Ward Leonard Elec. Co. 385
Cornish Wire Co., Inc. 389	P	Ward Products Corp. 371
Crowe Name Plate & Mfg. Co. 387	Precision Apparatus Co. 393	Webber Co., Earl. 375
Curtis Condenser Corp. 397	R	Webster-Chicago 367
D	RCA Mfg. Co., Inc. Fourth Cover	Weston Elec. Inst. Corp. 353
Dumont Electric Co., Inc. 380	Racon Elec. Co., Inc. 397	Wholesale Radio Service Co., Inc. 387
DuMont Labs., Inc., Allen B. 369	Radio Corporation of America. 347	Wright-DeCoster, Inc. 385
E	Radiotechnic Lab., The. 385	Y
Eastern Mike-Stand Co. 398	Radolek Co. 397	Yaxley Manufacturing Division
Electrical Products Co. 377	Raytheon Production Corp. 341	Second Cover
Electronic Design Corp. 373	Readrite Meter Works. 396	
Electro-Acoustic Products Co. 361	Rider, John F., Publisher. 377	
Electro-Voice Mfg. Co. 397		
G		
General Electric Co. 375		
General Transformer Corp. 387		

ELECTRO-VOICE

Velocity MICROPHONES Carbon "V" SERIES

An efficient all-feature velocity microphone, preferred by broadcast, sound and public address engineers throughout the world. Three models —\$35.00 to \$75.00, list

Write for complete descriptive literature immediately.

"K" SERIES.
Three models with genuine quality, listing from \$19.50 to \$29.50. Also a Static-Velocity model at \$20 list.
Five popular carbon "mikes" from \$5 to \$25 list. Repair service on all makes.

Ask Your Jobber
ELECTRO-VOICE MFG. CO.
332 E. COLFAX AVE., SO. BEND, IND.



Curtis Electrolytic CONDENSERS



For competently engineered condensers—specify CURTIS—High voltage 550, 575, 630 volts. Exact Duplicates and all the low voltages from 6 to 350.

Patent
No. 1,950,352

Write today for complete catalog.

CURTIS CONDENSER CORPORATION

3088 WEST 106TH ST. CLEVELAND, OHIO

★ ALWAYS CARRY Ken-Rad Radio Tubes

Ken-Rad genuine all-metal radio tubes are dependable. They give outstanding performance. Write for information.
KEN-RAD TUBE & LAMP CORP., INC.
Owensboro, Ky.

Also manufacturers of Ken-Rad Incandescent Electric Lamp

Here's an ALLIGATOR

You Can Keep for 

a Pet Around Your Own Shop

Send for him—he's FREE. You can dress him in a rubber insulator and he's absolutely harmless! Mueller Alligator Clips are trained to crawl into any kind of a hole and bite hard.

WRITE FOR CATALOG 690 AND FREE SAMPLES
Mueller Clips Are Stocked by Jobbers Everywhere

Mueller Electric Co.

1583 East 31st Street, Cleveland, Ohio

RACON PIONEERS AGAIN!

Permanent Magnet Horn Units



These efficient P.M. units require no outside excitation. Available in two types; both the 36% Cobalt steel and the newest high flux Alnico type magnets are used to supply maximum flux density in the air gap.

Cast bronze case, completely enclosed, makes unit water tight. Continuous operating capacity 10 watts. Peak load capacity 30 watts. 15 ohm impedance at 1000 cycles.

Electro-dynamic type units also available in all sizes.
RACON'S catalog S-6 describes the complete line of Horns, Electro-dynamic Units and Acoustical Sound Projectors.

RACON ELECTRIC CO., INC.
52 EAST 19th STREET NEW YORK CITY

American's New DYNAMIC

(High or Low Impedance)

D-5 50 Ohms List 27.50 **D-5-T** 10,000 Ohms List 32.50
(Both include 25' Cable and Plug)



- Rugged
- Excellent Frequency Response
- High Output
- Low Price
- MULTI-PURPOSE

Write for Catalogue on DYNAMIC, CRYSTAL, CARBON, and CONDENSER MICROPHONES, STANDS, and ACCESSORIES.

AMERICAN MICROPHONE COMPANY, Inc., Ltd.
1915 S. Western, Los Angeles, Cal.

"The Greatest Radio Show On Earth!"

THE NEWEST BOOK IN RADIO

THE SUMMER AND EARLY FALL EDITION of the 1937 Radolek Profit Guide is the most complete and up-to-date radio parts book ever published. The only absolutely NEW parts book in Radio! New repair parts. New test instruments. New auto radios. New home receivers . . . and New P.A. equipment. Contains the most extensive listings of replacement condensers, resistors, volume controls, transformers, and auto radio parts and accessories ever assembled under one cover. Over 12,000 repair parts always in stock ready for immediate shipment.

RADOLEK SERVICE IS FAST AND DEPENDABLE. There's no Sit-Down, Lay-Down, or Slow-Down at Radolek our organization is geared-up to serve you best, to give you what you want when you want it and at the Right Prices. Send for your FREE copy of this Big New Book NOW!

YOUR NEW 1937 RADOLEK

Profit Guide!



RADOLEK


601 W. RANDOLPH, CHICAGO, DEPT. R-1
Send me the Radolek Radio Profit Guide FREE.

Name
Address
Serviceman? Dealer? Experimenter?

New! AC-DC AMPERITE WITH STARTING RESISTOR! Prevents Untimely Burnouts



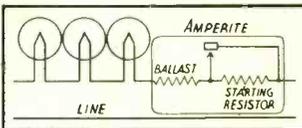When your set is turned on, the Patented Automatic Starting Resistor allows only 75 volts to pass through. . . Then it increases the voltage to normal as the tubes warm up, thus preventing sudden overloading and burnouts.



WRITE FOR
CHART CVS

Only 3 types of AC-DC AMPERITE are required to replace any of the 60 types of AC-DC ballast tubes. NEW LOW PRICE: List \$1.00. (Also new low price on replacements for 2-Volt Battery Sets, List \$1.25.)

AMPERITE Company 561 BROADWAY NEW YORK

NO!

We're not at the show. We're so busy that we just couldn't make it. But congratulations on a grand attendance . . . and bear in mind that when you want antenna systems, insulators, jacks, plugs, auto radio essentials, cable, wire or any of a score of other good radio products . . .

there's one name that has stood out from the crowd for more than 16 years.

BIRNBACH RADIO CO.
145 HUDSON ST. BIRCO NEW YORK, N. Y.

MANUFACTURERS, JOBBERS, SOUND MEN

Do Your Public Address Systems Suffer
from "STAND-TOSIS"



EASTERN MIKE STANDS not only add appearance to your systems, but also give it that desirable professional touch. Write for NEW CATALOG covering the EASTERN "SELECT-UR-OWN" line of over 77 distinct microphone floor stands. A model for every purpose.

EASTERN MIKE-STAND CO.

56 CHRISTOPHER AVENUE BROOKLYN, N. Y.
PHONE: DICKENS 2-3538



BROWN DEVIL WIRE WOUND RESISTORS

They Stay on the Job
says Bill Finit

Here is the ideal replacement resistor. OHMITE construction and specially developed vitreous enamel coating insure long, trouble-free service. 10 and 20 watt sizes; resistance values through 100,000 ohms. Ask your jobber or send for Catalog 16—FREE!



OHMITE

MANUFACTURING CO.
Manufacturers of Rheostats,
Resistors and Tapswitches
4827 Flournoy St.
Chicago, Ill.

THE Group Subscription Plan for Service enables a group of service men, dealers or jobbers to subscribe at one-half the usual yearly rate.

The regular individual rate is \$2.00 a year. In groups of 4 or more, the subscription rate is \$1.00 a year. (In foreign countries, \$2.00.)

The service departments of thousands of dealers, independent service men, etc., have used this Group Plan for years, in renewing their subscriptions to Service.

Each subscriber should print his name and address clearly and state his occupation—whether a dealer, jobber, independent service man, service organization, etc.

Remember this Group Plan when Your Subscription Expires

(Service)

Bryan Davis Publishing Co., Inc.

19 East 47th Street

New York, N. Y.

"We Don't Keep Them—We Sell Them" is what any Solar jobber can say about "little giant" Dry Electrolytics. The reason is in the condenser itself: it is there you find **QUALITY ABOVE ALL!** . . .



SOLAR MFG. CORP., 599-601 BROADWAY, NEW YORK

COMPARE THESE FEATURES

40,000 ohms impedance
Matches direct to grid of input tube
Triple chromium-plated finish
Modern streamlined appearance
Added eye appeal for every installation
Admirably suited for universal applications, including amateur field
Dynamic type—pressure operated
Insensitive to mechanical vibrations
Requires no excitation or power supply
May be located from one to over 1,000 feet distant from amplifier
Not affected by temperature, humidity or barometric pressure
Completely shielded—not affected by r-f or a-c fields
Engineered and guaranteed by RCA
30 feet of shielded cable

SPECIFICATIONS

Type: Pressure operated
Impedance: 40,000 ohms
Average Operating Level: -68 db (10 bar signal across open circuit)
Frequency range: 100 to 6,000 cycles
Dimensions: 2 5-8" wide, 3" high, 3 3-8" deep
Net Weight: 1 1-4 lbs.
Shipping Weight: 3 lbs.
Finish: Polished Chromium
Stand Fitting Size: 1-8" Pipe Thread
Cable: 30 feet shielded



LIST PRICE

\$29.95

LESS STAND

Here's the new RCA High Impedance Aerodynamic Mike!



Two New Mike Stands

At left is shown stand MI-4074 which is continuously adjustable from 20 to 55 inches. Price \$16.50. Above, microphone stand MI-6227, excellent for table or hand use. 6" high, list price \$3.75.

*Small, Streamlined Microphone offers
40,000 Ohms Impedance!
Matches Direct to Grid of Input Tube*

Once again RCA makes available a quality microphone at a very low price.

Note the many splendid features listed above that only this fine micro-

phone offers. Remember, it's a product of RCA and incorporates all the manufacturing and technical skill of this organization. Write for details.

RCA presents the "Magic Key" every Sunday, 2 to 3 P. M., E. D. T., on NBC Blue Network



Parts FOR PROFIT

RCA MANUFACTURING CO., INC., CAMDEN, N. J.
A Service of the Radio Corporation of America