

***FP** (*Fabricated Plate*)

TRADE MARK REG. U. S. PAT. OFF.

CONDENSERS

made by

P. R. MALLORY & CO., Inc.
MALLORY..

**Put the Come-back Odds
2000 to 1
in Your
Favor**

With over 5,000,000 FP Condensers in use as original equipment . . . the field returns on 1,000,000 . . . purchased by representative manufacturers were accurately checked. The answer has made radio history. Out of 1,000,000 FP Condensers made by Mallory only 512 were returned as defective. That's just 5/100th of 1%!


As a radio service engineer, this is news that you can't afford to overlook. FP Replacement Condensers, made by Mallory, are identical in every specification and quality to those used in original equipment—and made by Mallory. They offer you a replacement opportunity that to all practical purposes eliminates the possibility of troublesome call-backs.

But there's this to remember. The outstanding success of FP Condensers has caused them to be imitated. But the imitation is only skin deep. So don't make the mistake of expecting Fabricated Plate performance from a condenser that merely *looks* like a genuine FP Condenser.

In the sets you service . . . you'll recognize genuine FP Condensers by the name MALLORY or by the figure (1) enclosed in a circle.

For all your other condenser replacement needs Mallory's full line offers similar opportunities for full profit and complete customer satisfaction. Get details on the entire line from your Mallory Distributor today.

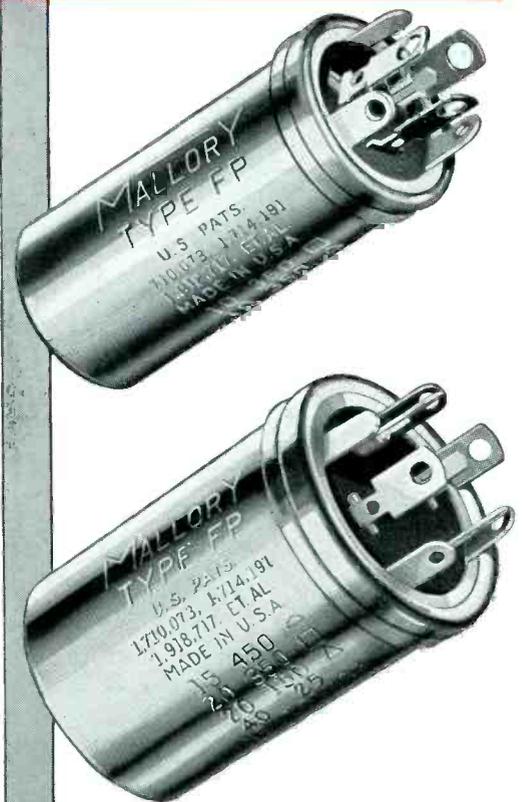P. R. MALLORY & CO., Inc.
INDIANAPOLIS INDIANA
Cable Address—PELMALLO



**Not etched construction*

Use

P. R. MALLORY & CO., Inc.
MALLORY
APPROVED
PRECISION PRODUCTS

Include

VIBRATORS • VIBRAPACKS • CONDENSERS • VOLUME CONTROLS • ROTARY SWITCHES • SINGLE AND MULTIPLE PUSH BUTTON SWITCHES • RESISTORS
RADIO HARDWARE

Frequency Modulation

EXTENDED RANGE—HIGH FIDELITY

THERE is now available a complete family of special Jensen products for Frequency Modulation and Television receivers—as well as for monitoring and studio work. ¶ Illustrated below is the beautiful new Walnut "CA" type *Bass Reflex* cabinet—available in two sizes. One houses the new 12-inch PM extended range speaker. The other utilizes the new dual-unit 15-inch PM speaker complete with filter network. ¶ Below is also illustrated the "M" type *Bass Reflex* reproducer finished in brown lacquer—available with either the 8", 12" or 15" dual-unit extended range speaker. They are all extremely modestly priced. The three speakers are, of course, obtainable without the enclosures. The 15-inch dual-unit in Permanent Magnet design complete with filter network is only \$46.50 LIST. The 8" and 12" speakers show an extended high frequency response up to 10,000 cycles. The 15-inch dual-unit model is extended to 14,000 cps. ¶ Jensen Radio Mfg. Co., 6601 S. Laramie, Chicago.

Jensen
Bass Reflex
REPRODUCERS





A Monthly Digest of Radio and Allied Maintenance

Reg. U. S. Patent Office

NEXT year, the National Radio Trade Parts Show will again be held at the Stevens Hotel in Chicago. The dates: June 10th through 13th. If you missed this year's successful show, start making plans to be present next year. It's an experience which is better than worthwhile.



BELL pushing seems to be a forgotten method of getting business. We know of several people who have receivers in their homes that need a bit of attention. Oh, yes, the sets work after a fashion, but they could stand a bit of inspection and repairs. Yet, as is a common failing, these people just don't get around to looking up a Service Man. If, however, a business-like, well appearing Service Man should push the doorbell some evening, we are sure that he would be more than welcome. Similar cases must exist by the thousands throughout the country. On your toes, boys.



EACH month we present to the readers of SERVICE at least one profitable business building idea. This month's offering, on page 20, discusses a successful tieup with the local movie house for the purpose of attracting better class customers. We have dozens of these proved ideas from successful Service Men throughout the country, and as time goes on we will unfold them to you. It is up to you then to give action to the words and reap a golden harvest.



ON PAGES 6, 7, 8 and 9 of this issue we present a series of charts of battery replacements, of practically every manufacture, for the various battery portables which have been placed upon the market within the last three years. The remainder of these charts will be published in an early issue.

We have attempted to make the listings as complete and accurate as possible in the face of pages of conflicting data. We feel safe in saying that ours is the most complete and the most accurate of any such compilations. To help the industry maintain these listings accurately, we are prepared to offer our full cooperation to such battery manufacturers who desire it.

CONTENTS

	Page
Batteries for Portables. <i>By Robert G. Herzog</i>	5
Circuits. <i>By Henry Howard</i>	10
Comparative Batteries for Portables	6
Comparative Packs for Portables	8
Confidence. <i>By Ruel McDaniel</i>	25
Intermittent Condensers	28
Philco Photoelectric Phonograph	22
RCA BP10 (Camera) Battery Portable	26
RCA Rider VoltOhmyst	19
Replacement Batteries for Portables	7
Sound Ideas. <i>By S. Gordon Taylor</i>	14
Theatre Display <i>By M. Hover</i>	20
Associations	23
Circuits	
Airline 93BR392A Driver and Output Stages	11
Airline 93BR719A Audio and Power Supply Stages	11
Crosley 548, 5548 Driver and Output Stages	10
DeWald 545LW, 545SW First Detector-Converter	11
DeWald 545LW, 545SW Rectifier and Battery Switching	11
DeWald 663, 666 Ballast Circuits	23
G. E. J805, RJS805	10
G. E. HJ905, HJ908 Output and Power Supply Stages	11
Motorola B150 Bike Radio	Front Cover
RCA BP10 (Camera) Battery Portable	26
RCA 46X1 Ballast Circuits	23
RCA 46X11, 46X12, 46X13 First Detector-Converter	12
RCA Rider VoltOhmyst	19
RSE Condenser Tester	28
Silvertone 6324, 6493	12
Silvertone 6368, 6382 6-volt, 110-volt Power Supply and Switching Circuits	12
Cover Diagram	
Bike Radio (Motorola B150)	10
Highlights and Manufacturers	26, 27, 29, 30, 31
Index to Advertisers	32
On the Job	
Confidence. <i>By Ruel McDaniel</i>	25
Intermittent Condensers	28
Philco Photoelectric Phonograph	22
RCA BP10 (Camera) Portable	26
Test Equipment	
Intermittent Condensers	28
RCA Rider VoltOhmyst	19

Copyright, 1940, Bryan Davis Publishing Co., Inc.

BRYAN S. DAVIS
President

JAS. A. WALKER
Secretary

Chicago Office:
608 S. Dearborn Street
C. O. Stimpson, Mgr.
Telephone: Wabash 1903

Published Monthly by the
**Bryan Davis
Publishing Co.**
Inc.
19 East 47th Street
New York City
Telephone: PLaza 3-0483



PAUL S. WEIL
Advertising Manager

A. GOEBEL
Circulation Manager

Wellington, New Zealand:
Tearo Book Depot

Melbourne, Australia:
McGill's Agency

Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

for Every Application

Series II

Centralab SOUND PROJECTION CONTROLS

CENTRALAB SERIES II



Controls are the finest for input circuits in broadcast stations, public address systems, and recording apparatus of new or old design. Will prove faultless in the most critical service.

The curve chart above shows the change in impedance and attenuation plotted against clockwise rotation for a "T" pad attenuator. The impedance characteristic (dotted line) is substantially the same at any setting. The attenuation curve (solid line) varies from infinity at zero rotation to zero Db. at full rotation. No insertion loss.

Electrostatic and electromagnetic shielding provided by a black finished steel case. Bakelite screw type terminal strip on back of case. All resistance elements insulated from shaft and bushing. Single hole mounting. Mounting bushing $\frac{3}{4}$ " long with 2 locknuts and lockwashers. Case diameter $2\frac{3}{4}$ ". Depth back of panel "T" Pad — $2\frac{3}{8}$ "; Gain Control — $1\frac{3}{8}$ ". Maximum load dissipation 1 watt.

For detailed information, write for technical booklet.

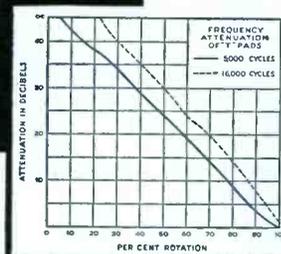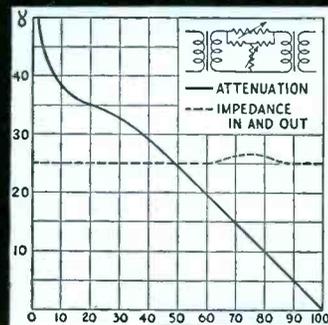CENTRALAB: Division of Globe-Union Inc.
MILWAUKEE, WISCONSIN



ECONOMY P/A CONTROLS

These controls are intermediate to the series II line and the older series I types. As their name implies, they are economy controls designed primarily for inexpensive sound equipment, where original cost is a limiting factor. They are designed for all types of fading and mixing systems. All units have soft aluminum shaft $2\frac{1}{4}$ " from end of $\frac{3}{8}$ " brass bushing. Small diameter bakelite case same dimension as Standard Radiohm. Non-rubbing contact for smooth, quiet operation. Limited to input applications. Maximum power rating for all units one watt.



WHAT HAS HE GOT THAT I HAVEN'T GOT?

DID you ever stop to wonder how some servicemen get more business and make more money than you? Here, perhaps, is the answer. The most successful men in *any* business are those who have learned never to pass up *anything* that will help them to accomplish an important job *in less time*.

This practice of taking advantage of every aid to *better work in less time* is often the only thing that stands between success and failure. In the radio service business, the man who uses all the information he can get to make troubleshooting quicker and surer is the one who forges ahead. *He's* the man who has always had a complete set of RIDER MANUALS. He knows how foolish it is to depend on his own memory or intuition when complete, authoritative data can be at his fingertips for only 3c a day.

RIDER MANUALS give you, in the most convenient form, complete data on every set you may be called upon to service . . . data on alignment, I-F peaks, operating voltages, parts lists and values, voltage ratings of condensers, wattage ratings of resistors, coil resistance data, etc.

If *you* don't have a complete set of eleven RIDER MANUALS, you are overlooking one

of the surest ways of speeding up your trouble shooting and increasing your profits.

JOHN F. RIDER Publisher, Inc.
404 Fourth Avenue New York City

Export Division: Rocke-International Elec. Corp.,
100 Varick St., New York City. Cable: ARLAB.

You Need All Eleven Rider Manuals

Volume	Price	Covering	Volume	Price	Covering
XI	\$10.00	Up to May 15, 1940	V	7.50	1934-35
X	10.00	1939-40	VI	\$7.50	1935-36
IX	10.00	1938-39	IV	7.50	1933-34
VIII	10.00	1937-38	III	7.50	1932-33
VII	10.00	1936-37	II	7.50	1931-32
			I	7.50	1920-31

VOLUME XI HAS MANY *New* FEATURES

Includes data on FM receivers released up to press time.

New Index . . . cross-indexed for easy reference.

New "How It Works" section, with up-to-date information on the latest developments.

New Vest Pocket Supplement contains much useful information for on-the-spot reference.

You NEED RIDER MANUALS

BATTERIES FOR PORTABLES

By ROBERT G. HERZOG

EDITOR

BATTERIES, batteries, batteries and more batteries. Since the advent of the battery portable there has been a veritable flood of battery types of every size and shape. Yet to the Service Man it would seem that just that size and shape which his customer requires is missing in the particular brand that he carries.

No Two Alike

Although there are numerous comparative types listed in Table I on the following page, no two similar types, made by different manufacturers, are identical in size. There is often as much as a quarter of an inch or more difference in one or more of the dimensions. In listings published by some of the battery manufacturers themselves there is often as much as a half-inch difference in one or more dimensions of types listed as comparative.

In the listings of comparative packs, in Table II, there is as much as a half-inch difference between comparative types in one or more dimensions.

Battery listings bid fair to become more and more complicated, especially as a result of the special types of tiny batteries and packs required to accommodate the latest "camera" portables.

Battery Drain

In the interest of low-battery drain


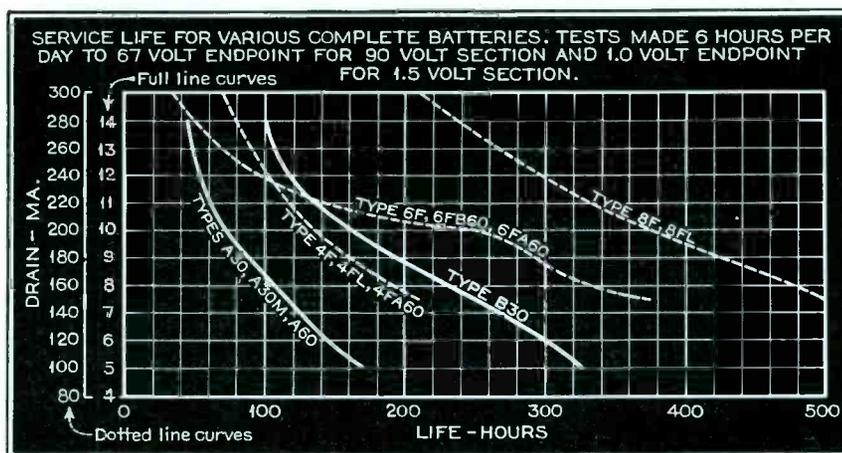


Fig. 2. The life of a battery is a function of the conditions under which the battery is used. The curves above give the life of various units specified conditions.

all the portables use over-biased power tubes. This practice, while increasing the percentage of harmonics, seems justified as the quality is quite acceptable. Power outputs vary from 100 milliwatts for sets with 1A5G pentode to 275 milliwatts developed by the 1Q5G (or GT)

Fig. 1. Battery manufacture has advanced to the stage where the makers can predict the approximate life if the conditions of operation are known. Life charts of single cells are shown for specified conditions.

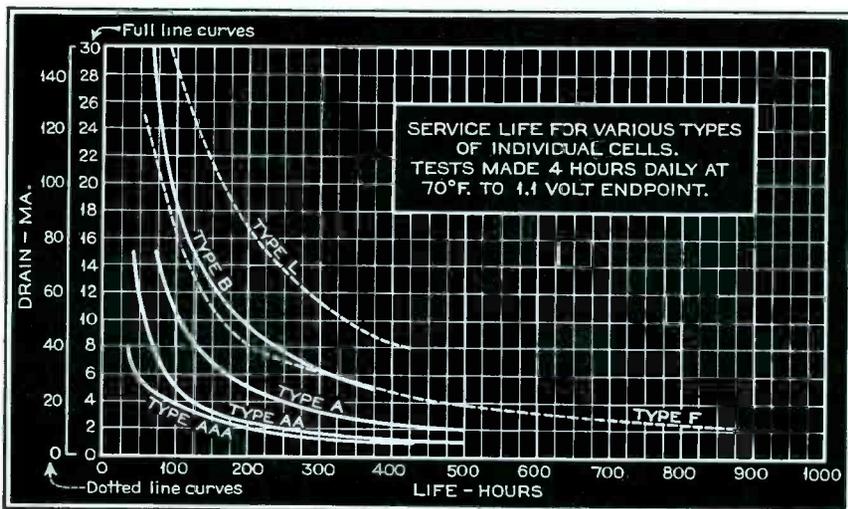

or the 3Q5G beam power tubes. A few recent models still use the 1C5G with an output of 200 milliwatts. Many employ the 1T5G, which has a filament drain of only 0.05 amp, with an output of 170 milliwatts.

Practically all the portables draw between 9 and 12 milliamperes B current with no signal, the current increasing by a few milliamperes with strong signals.

The typical 4-tube set draws 250 ma for the filaments, on one-and-a-half volts, or (using the 3Q5G) 50 ma on seven-and-a-half volts. Those models which employ the 1T5G draw only 200 ma on one-and-a-half volts or 50 ma on 6 volts. A five-tube set draws 300 ma on one-and-a-half volts, 50 ma on nine volts.

The A-battery life is the same for circuits which have the filaments connected in series as it is for those which are connected in parallel, in spite of the lower current drain and higher voltages required for the former. This is so because the batteries are made up of a multiple number of cells which are connected in series in one case and in parallel in the other. The total power available is the same for the one-and-a-half volt and the six-volt batteries.

Battery Life

Battery life is a direct function of the conditions under which the battery

COMPARATIVE NUMBERS OF BATTERIES FOR PORTABLES

Acme	Advance	Bond	Bright Star	Burgess	Eveready	General	National Union	Philco	Rayovac	Usalite	Willard	Winchester
1½ VOLT A UNITS												
111	2	102	10M	D	950	D	D	D	2	1094	D	—
—	—	—	—	—	—	—	—	—	P24A	—	—	—
—	—	—	461	—	—	—	—	—	—	—	—	—
—	—	—	—	2F	—	—	—	—	—	—	—	—
114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
—	—	—	—	—	—	4H1	—	—	—	—	4H1	—
—	—	—	—	—	—	4L1	—	—	—	—	4L1	—
115	—	—	—	—	—	—	—	—	—	—	—	—
116	—	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1	4814
118	147	4829	860	8F	741	8F1	A833	—	—	635	8F1	4819
—	447	—	—	—	—	3L1	—	—	—	—	3L1	—
—	—	—	—	—	—	—	—	—	—	644	—	—
118FM	547	—	865	8FL	745	8CF1	—	—	P98L	645	—	—
123M	—	—	465	4FL	—	—	—	—	P94L	642	—	—
—	—	—	—	FX	—	—	—	—	—	—	—	—
4½ VOLT A UNITS												
123	647	4928	361	G3	746	3H3	—	—	P83A	683	3H3	4919
6 VOLT A UNITS												
114S	—	—	—	—	—	—	—	—	—	—	—	—
—	2476	—	646	F4P1	—	4F4	—	—	P694A	639	4F4	—
—	—	—	—	F4PIX	—	—	—	—	—	636	—	—
—	—	—	661	—	—	—	—	—	—	—	—	—
118S	817	4827	866	2F4	718	8F4	A834	—	P698A	638	8F4	4817
—	—	—	—	—	—	—	—	—	—	643	—	—
118S6	747	—	868	2F4L	747	8CF4	—	—	P698L	646	—	—
7½ VOLT A UNITS												
115S	—	—	—	—	—	—	—	—	—	—	—	—
—	—	—	561	G5	—	5H5	—	—	P85A	687	—	—
45 VOLT B UNITS												
—	—	—	—	—	727*	F30A	—	—	BB30P	—	—	—
330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
—	—	—	—	—	—	—	—	620	—	620	—	—
430	—	—	30-55	A30	—	V30A	—	—	430P	621	V30A	—
—	—	—	—	—	—	—	—	—	—	622	—	—
530	—	—	—	—	—	—	—	—	—	—	—	—
—	—	—	30-50	A30M	—	—	—	—	—	—	—	—
—	—	—	—	A30X	—	—	—	—	—	—	—	—
830	284	—	30-33	M30	482	—	B861	—	P5S30	640	—	—
—	—	—	—	Z30	738	V30AA	—	—	P7R30	—	V30AA	—
—	—	—	—	—	733	V30AAA	—	—	P3A30	—	—	—
—	—	—	—	W30P1	—	—	—	—	—	—	—	—

* Type 482 should be used.

Table 1. Although the chart indicates that the various types of the different manufacturers may be interchanged, this is not always the case. There may be as much as a quarter of an inch difference in one or more dimensions between types. It may be said almost without exception that no two types of different manufacture are identical in size.

REPLACEMENT BATTERIES FOR PORTABLES

Model	Acme	Advance	Bond	Bright Star	Burgess	Eveready	Gen-eral	National Union	Philco	Rayo-vac	Usalite	Wil-lard	Win-chester
ADMIRAL (Continental Radio & Television Corp.)													
33F5, 34F5, 35G6, 37G6, B34G6	AB	6FA60	...	60A4L	...	P60A4L	AB84	AB667
164-4D, 335-4Z	1A	116	...	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
311-4D	1A	116	...	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1
	2B	430	30-55	A30	738	V30A	430P	621	V30A
319-4Z	1A	123M	465	4FL	...	3L1	P94L	642	...
	2B	430	30-55	A30	738	V30A	430P	621	V30A
331-4F	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1
	2B	430	30-55	A30	738	V30A	430P	621	V30A
336-5N	1A	561	G5	...	5H5	P85A	687	...
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
AEOLIAN (Aeolian Manufacturing Co.)													
BP4, BP5, BP8	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
BP6, BP10	1A	F4PIX	636	...
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
BP36	2A	123	647	4928	361	G3	746	3H3	P83A	683	3H3
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640	...
AIR CASTLE (Speigel, Inc.)													
560-1, 561-1, 561-1M	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
611-1	1A	...	2476	...	646	F4PI	...	4F4	P694A	639	4F4
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
AIR CHIEF (See Firestone Tire & Rubber Co.)													
AIR KING (Air King Products Co.)													
3905, 3912	AB	460-15	411	5DA60	...	60A2L	AB665	...
3906, 3910	1A	118	147	4829	860	8F	741	8F1	A833	A96	P96A	635	8F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
3916	1A	116	...	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
3950, 4112	1A	118S6	747	...	868	2F4L	747	8CF4	P698L	646	...
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
4012	AB	460-14S	659	D4A60	AB664	...
4016	1A	118S6	747	...	868	2F4L	747	8CF4	P698L	646	...
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640	...
AIRLINE (See Montgomery Ward)													
ANDREA (Andrea Radio Corp.)													
6G61, 6G61A, (G61)	2A	123	647	4928	361	G3	746	3H3	P83A	683	3H3
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
21AF5, 21F5, (UF51)	A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1
	B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
ANSLEY (See Port-O-Radio)													
ARCADIA (See Wells Gardner)													
ARIA (See Wells Gardner)													
ARLINGTON (See Wells Gardner)													
ARVIN (Noblitt Sparks Industries)													
802, 803	1A	118FM	547	...	865	8FL	745	8CF1	P98L	645	...
	2B	830	284	...	30-33	M30	482	V30A	B861	...	P5S30	640	V30A
AUTOCRAT (Autocrat Radio Co.)													
90, 98	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
120	A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4
	B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
131, 132	A	...	2476	...	646	F4P1	...	4F4	P694A	639	4F4
	B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
161	AB	AB94
AUTOMATIC (Automatic Radio Mfg. Co. Inc.)													
P40, P41, P50, P51	1A	643	...
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640	...
P43, P45	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
P57, P58, P61, P72	1A	F4PIX	636	...
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
P80, P81	1A	118-S6	747	...	868	2F4L	747	P698L	646	...
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640	...
BELMONT (Belmont Radio Co.)													
403, 460	1A	118	147	4829	860	8F	741	8F1	A833	P96	P96A	635	8F1
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B
407	1A	123M	465	4FL	...	3L1	P94L	642	3L1
	2B	430	30-55	A30	...	V30A	430P	621	V30A
507, 513	1A	...	2476	...	646	F4P1	...	4F4	P694A	639	4F4
	2B	430	30-55	A30	...	V30A	430P	621	V30A
BLACK HAWK (See Wells Gardner)													
CARRYETTE (See Westinghouse)													
CARRYOLA (See Garod)													

COMPARATIVE BATTERY PACKS FOR PORTABLES

Voltage	Acme	Advance	Burgess	General	Philco	Rayovac	Usalite	Zenith
30	—	—	W20PI	20AAAG	—	—	—	—
51	—	—	W34	34AAAG	—	—	—	—
60	—	—	W40	—	—	—	—	—
88½	—	—	Z59	—	—	—	—	—
90	—	—	A60	—	—	BB60P	—	—
90	—	—	—	—	—	7S60P	—	—
1½-61	—	—	—	—	P41A4G	—	AB672	—
1½-63	442-4	41AD7	4GA42	41A4FL	P41A4FL	AB419	AB669	—
1½-63	—	—	8TA42	—	—	—	—	—
6-61½	—	—	F4A41	—	—	—	—	—
6-75	—	—	GB4B60	—	—	—	AB670	Z675
1½-90	460-15MS	—	2AG60	—	—	—	—	—
1½-90	860-41	—	4FA60	—	—	—	—	Z9B
1½-90	—	—	4TA60	—	—	—	—	—
1½-90	460-15	411	5DA60	60A2L	—	—	AB665	—
1½-90	—	837	—	60A4H	—	—	—	—
1½-90	—	—	6FA60	60A4L	P60A4L	AB84	AB667	—
1½-90	—	—	—	—	P60A110	—	—	—
1½-90	—	—	6FB60	—	—	—	—	—
1½-90	—	—	6TA60	—	—	—	—	—
1½-90	—	—	—	—	—	AB94	—	—
6-90	—	—	2F4B60	—	—	—	—	—
6-90	—	—	F4B60	—	—	—	—	Z659
6-90	—	—	G4B60	60B4H	—	—	—	—
6-90	460-14S	659	D4A60	—	—	—	AB664	—
6-90	—	—	—	—	—	AB684	AB671	—
6-90	—	—	—	—	—	AB694	AB668	—
6-90	—	—	—	—	P60A8F4	AB673	—	—
6-90	—	—	—	—	—	—	AB674	—
7½-90	460-15S	—	—	—	—	—	—	—

Table II. The various types listed as such, are generally interchangeable. Occasionally some slight difficulty may be experienced, however, since there are differences up to a half inch in one or more dimensions among similar batteries of different manufacture.

is used. The numbers of hours of life can vary as much as ten to one with the batteries connected to the same receiver, depending upon these conditions.

Practically every dry battery is designed for intermittent service. If the receiver is placed in a warm closet and left on, it will be only a matter of a few hours before the batteries will be completely exhausted. Similarly if the receiver is used for long stretches its life will be considerably less than if it is used for say an hour or less a day.

Battery manufacture has advanced to such a stage that if the makers know the exact conditions of use they can design a unit which will deliver the most power per dollar. They therefore recommend that replacements be made from their listings for a particular service. That is to say, a battery designed for a lantern would not necessarily be a good

replacement for a radio set, although some set manufacturers seem to think so. To crowd more service into units for some purposes, compromises are made with such things as shelf life, etc. If the total life of one unit is to be say, two to five hours, it need not have a shelf life of over two years!

The retail cost to the battery-portable user under consecutive conditions of operation is somewhere between one and one-and-a-half cents per hour for most sets. This increases, naturally, as the set gets smaller, till it reaches about eight cents per hour for the new "camera" portables.

The approximate life under specified conditions for single cells and for complete batteries is shown in Figs. 1 and 2. These figures are somewhat conservative, however, since the average portable would not be used as often as

indicated by these tests.

Excessive heat also shortens battery life materially. It is for this reason that manufacturers advise owners of a-c, d-c, battery portables to remove the batteries if line operation is contemplated for a considerable period.

Plug Connections

When battery portables were first introduced they all required a one-and-a-half volt A battery. Manufacturers provided these units with a two prong socket and plug arrangement to accommodate easy replacement. It was not long, however, before the portables went a-c, d-c and many required six and seven-and-a-half volt A batteries. To prevent the inadvertent connection of a volt-and-a-half set to a six-volt battery, the manufacturers of the earliest of these units utilized a three-prong socket which would in no way accept the two-prong volt-and-a-half plug. Later it was realized that a two-prong plug would suffice for any voltage, the different voltages employing prongs suitably separated.

Several sets are on the market, however, which employ six-volt A batteries using the three-prong plug. In the absence of a suitable replacement in the brand which you carry, it is only necessary for you to change the plug connection on the end of the receiver cable or to use an adaptor and sell the corresponding six-volt battery with a two-prong socket. In rare cases it may be necessary to employ an adaptor to connect some packs to special receivers.

Recently plug connections have been standardized by the Radio Manufacturers Association.

Install Proper Battery

Some manufacturers recommend that Service Men install a larger battery than that specified, wherever such a battery will fit in the receiver case. This is not necessarily the best practice. It is usually better to use that combination of A and B batteries which will run down approximately at the same time. Should either the A or B battery run down sooner, and be replaced alone, it will not be long before the other battery will require replacement. The set will thus require just twice as much attention and will be out of action twice as often as it would be if both batteries had been replaced at the same time. Upon each occasion there is no doubt that the deficiency will be discovered only after the set has been carted along somewhere with the expectation that it would give service.

It is advisable, however, to use larger As and Bs, should it be possible to increase the size of both units.

(Continued on pages 9 and 24)

Model	Acme	Advance	Bond	Bright Star	Burgess	Eveready	General	National Union	Philco	Rayo-vac	Usalite	Willard	Winchester	
CHEVROLET (Chevrolet Division, General Motors Corp.)														
985514	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
CLARION (Clarion Radio Co.)														
0-464	1A	118FM	547	...	865	8FL	745	8CF1	P98L	645
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640
0-534, 535, 539	1A	...	2476	...	646	F4P1	...	4F4	P694A	639	4F4	...
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
CLARK (See Warwick)														
CLIMAX (See General)														
COLONIAL (Colonial Radio Corp.)														
575	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
CORONADO (See Gamble Stores, Inc.)														
CROSLEY (Crosley Radio Corp.)														
27, 27BD, 27BE	1A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4	4817
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
429, 429A, B429A	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	637	8F1	4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
439, 439A	1AB	442-4	41AD7	4GA42	...	41A4FL	...	P41A4FL	...	AB669
549, 549A	1AB	F4A41
5549, 5549A	1A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4	4817
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640
DELCO (Delco Radio Division, General Motors Corp.)														
R1400	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1	4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
R1401, R1402	1A	123M	465	4FL	P94L	642
	2B	430	30-55	A30	738	V30A	430P	621	V30A	...
DETROLA (Detrola Radio Corp.)														
282 (Pee-Wee)	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
	1B	A60	BB60P
286, 288	1A	118	147	4829	860	8F	741	8F1	A833	P96	P96A	635	8F1	4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
295	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
299, 289	1A	116	...	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1	4814
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
303, 303A, Treasure Chest	1AB	442-4	41AD7	4GA42	...	41A4FL	...	P41A4FL	...	AB669
339, 339-1, 340-1, 341-1,	2A	123	647	4928	361	G3	746	3H3	P83A	683	3H3	4919
341-2, 360-1	2B	830	284	...	30-33	M30	482	F30A	B861	...	P5S30	640
DEWALD (DeWald Radio Mfg. Co.)														
408	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
408R, 409	1A	118	147	4829	860	8F	741	8F1	A833	P96	P96A	635	8F1	4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
415	1AB	460-15	411	5DA60	...	60A2L	AB665
415R	1A	116	...	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1	4814
	2B	830	284	...	30-33	A30X	727	F30A	BB30P	640
544, 544L	1A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4	4817
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
545, 545LW, 545SW	1A	118S6	747	...	868	2F4L	747	8CF4	P698L	646
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640
EMERSON (Emerson Radio & Television Co.)														
EA338, 339, 340, 357, 363	2A	123	647	4928	361	G3	746	3H3	P83A	683	3H3	4919
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640
CE259	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1	4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
CE263, CE265, CX263, CE275, CT275, CX283, CX292, CX284, CX308, DC308, CX305	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1	4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
DF302, DF306	2A	123	647	4928	361	G3	746	3H3	P83A	683	3H3	4919
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
DJ310, DJ311, DJ312	2A	123	647	4928	361	G3	746	3H3	P83A	683	3H3	4919
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640
ENDURANCE (Western Tire & Auto Stores, Inc.) (See Detrola)														
ESPEY (Espey Mfg. Co.)														
942 Series	1AB	6TA60
943, 958	1AB	460-15	411	5DA60	...	60A2L	AB665
040	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1	4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
050	1A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4	4817
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218
052, 053	1A	F4PIX	636
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B	6218

(Continued on page 24)

CIRCUITS

See Front Cover

By HENRY HOWARD



(Above) The Motorola Model B150 battery radio is designed for use on the handlebars of a bicycle. (Also see front cover.)

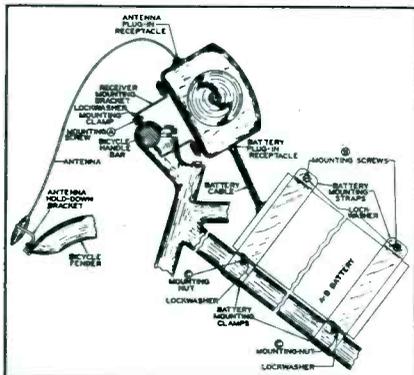


Fig. 2. (Above) Suitable brackets are provided for proper mounting of the set, and its associated battery pack, to the bicycle frame. A rod type antenna fastens to the front fender and plugs into a special receptacle on the set.

Fig. 1. (Below) The G. E. Models J805 and RJS805 utilize a p-m speaker and provide dual resistance filtering for the B supply. The set employs dual Beam-O-Scopes and incorporates a novel tone control circuit.

DESIGN engineers continue to have brainstorm, ideas or reveries and versatile imaginations as is evidenced by the concoction of circuits that follows. Nevertheless, there are many circuits of receivers made by different manufacturers that are so much alike that the blueprints might be interchanged with only a few minor changes such as resistor or condenser values.

G. E. J805, RJS805

These models are 8-tube, 3-band superheterodynes incorporating an r-f stage on all bands and having two Beam-A-Scope loops, a p-m speaker, double section resistance filter, novel tone control and wide-band untuned im-

pedance-capacity coupling between the r-f stage and the converter. (See Fig. 1.)

Up to the present we have seen p-m speakers used mostly on a-c, d-c and auto-radio sets. It is a good sign to see them employed on high-quality sets where there should be complete freedom from 60-cycle (and harmonics) modulation which imparts that hoarse, rough characteristic to spoil an otherwise high-quality output. Plate power for the push-pull output stage is taken from the rectifier directly, or filter input. Although the hum voltage at this point is considerable, it is canceled out in the output transformer due to the balancing effect of the two push-pull tubes. This is strictly true only when the tubes are matched. In any case, it is a good policy to replace both tubes even if only a single one is found to be weak.

The first filter section consists of a 30-mfd, 350-volt condenser, an 1800-ohm resistor and a 15-mfd condenser. The push-pull screens and r-f and i-f plates are fed from this section. The second section contains an 8200-ohm resistor and 10-mfd condenser providing additional filtering for the r-f and i-f screens. (See Fig. 1.)

The antenna-loop circuit is interesting. For broadcast, the B band loop is used. For automatic, or push-button tuning, individual condensers are shunted across the loop. When an external antenna is added to the set, energy is transferred magnetically to


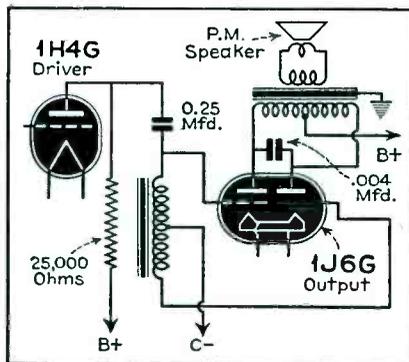


Fig. 6. (Above) The Crosley Models 548 and 5548, 5-tube farm sets, which use the 1J6G output tube, provide 2 watts of output on 135 volts of B supply.

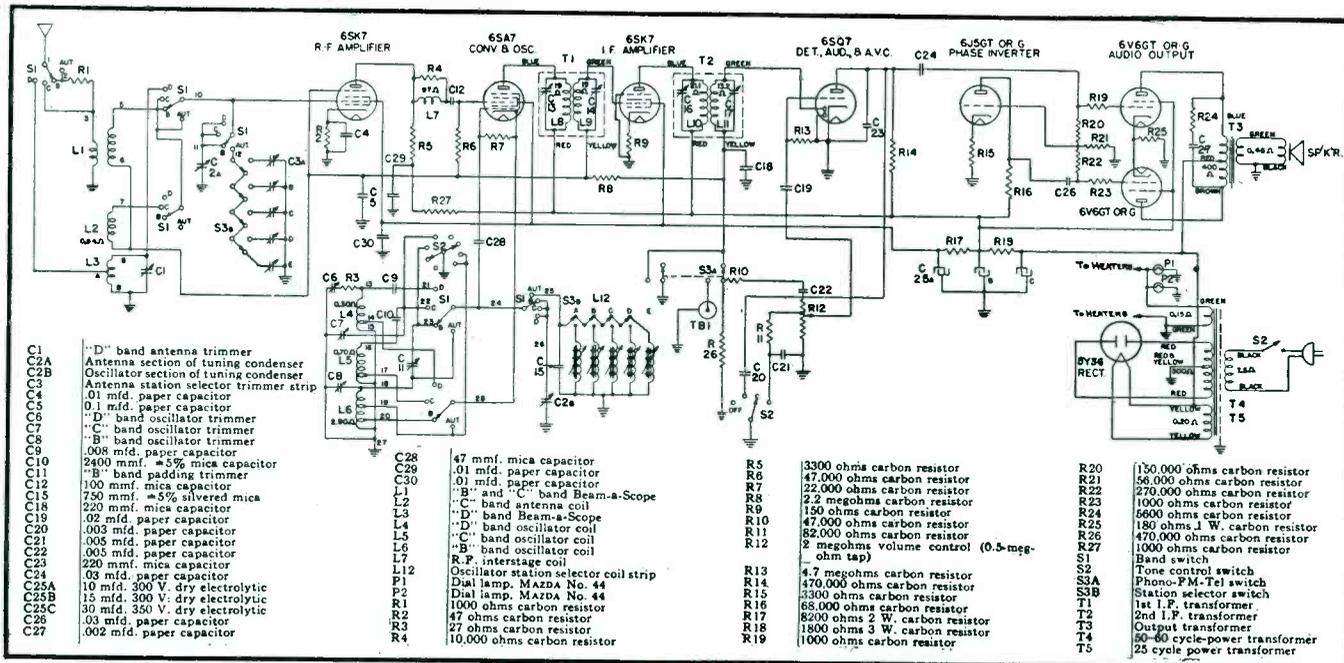

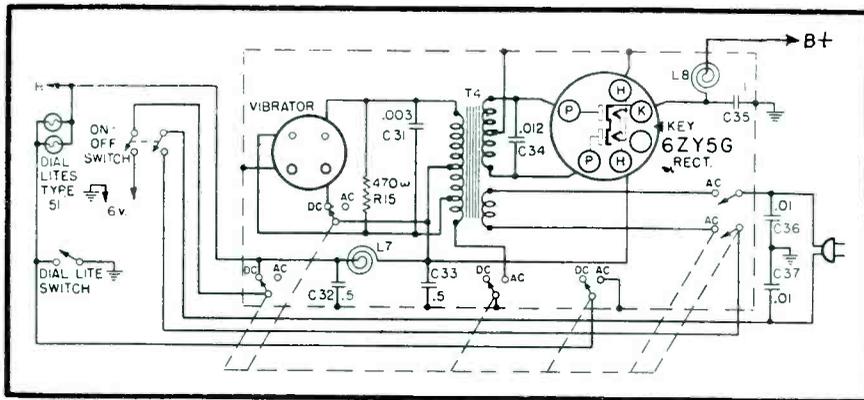


Fig. 10. The Silvertone Models 6368 and 6382 are designed for operation from either the 110-volt, 60-cycle power lines or from a 6-volt d-c source.

loop technique.

DeWald 545SW, 545LW

The DeWald portable Model 545 is available in two models also, the long wave and broadcast (545LW) or short wave and broadcast (545SW). Both include a 35Z4GT rectifier for a-c, d-c line operation. (See Fig. 4.) Note the long-wave loading coil in series with the loop. Note also the very simple battery-to-line switching arrangement using a dpdt slide switch.

Crosley 548, 5548

Crosley Models 548 and 5548 are 5-tube farm sets made for air cell battery operation and 135-volt B. A similar model, 558, uses the new 1J6G Class B output tube giving an output of 2 watts! All new tubes are used in this series of sets. (See Fig. 6.)

Airline 93BR392A


We next have a series of receivers with unusual AF ends. Take the Airline Model 93BR392A in Fig. 7. This is a seven-tube a-c, d-c set with three bands and dual p-m speakers. Note the 25N6G internally coupled Class A dual triode power-output stage.

G.E. HJ905, HJ908

General Electric also has some surprises in Fig. 8 showing part of models HJ905 and HJ908, large 9-tube phono combination models having no power transformer! Nine tubes are used including two 25Z6Gs in a voltage doubler circuit. Two strings of heaters

are needed to accommodate all the tubes. A special tertiary winding is put on the output transformer for degenerative feedback to the second audio cathode. A 14-inch p-m speaker is used.

Fig. 11. The RCA 46X11, 46X12 and 46X13 employ a small multturn coupling coil for loop-antenna coupling. This provides greater energy transfer at the low frequencies than the single turn used by many manufacturers.

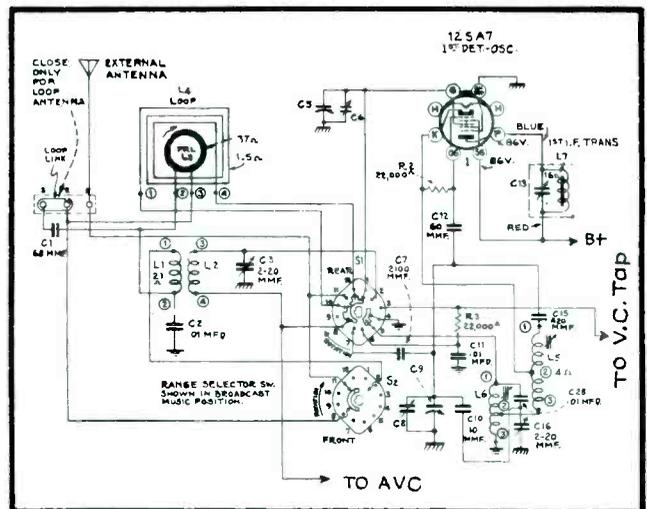

Airline 93BR719A

Wards have another unusual Model

Fig. 14. Silvertone Models 6324, 6424 and 6493 have a 2-position tone control with an unusual arrangement, in the power tube plate circuit.

93BR719A in Fig. 9. This set has a 35 volt, 1/2-wave rectifier and push-pull 35L6GTs operating from a power transformer as well as a 12-volt series of tubes for the r-i end. A 12Q7GT is used as inverter and the feedback loop runs from the high side of the output secondary to the grid circuit of the first audio instead of to cathode, as in most sets.

Silvertone 6368, 6382


The Sears Roebuck Silvertone Models 6368 and 6382 are seven-tube, three-band supers operating from either 6 volts d-c or 115 volts a-c. The power transformer has a full-wave primary winding for the 6-volt vibrator, an auxiliary primary winding for 115 volts a-c, the usual full-wave secondary winding for high voltage and a 6.3-volt heater winding. For economical operation on battery, the dial lights are arranged to light only while tuning—called Dial Flash-O-Lite. On a-c they

burn continuously. The battery drain is only 2.3 amp. The 60-cycle drain is 18 watts, giving an output of 1.42 watts undistorted, 2.8 watts maximum. A p-m speaker explains the low battery current. Plate voltages are reduced about 25% on d-c cutting the power output to 0.78 watts undistorted, 1.43 maximum. The 6T7G detector-a-f amplifier is operated with cathode grounded, bias being obtained via a 15-meg grid leak, an increasingly popular system. A separate triode, acting as a diode, is used for avc. Note the switching circuit in Fig. 10.

RCA 46X11, 46X12, 46X13


RCA Victor models 46X11, 46X12, 46X13, 5-tube, 2-band, a-c, d-c, superhets have a novel loop-antenna coupling system using a small, multi-turn coupling coil. This provides greater energy transfer at the low frequencies than the single turn used by many manufacturers. See

(Continued on page 23)

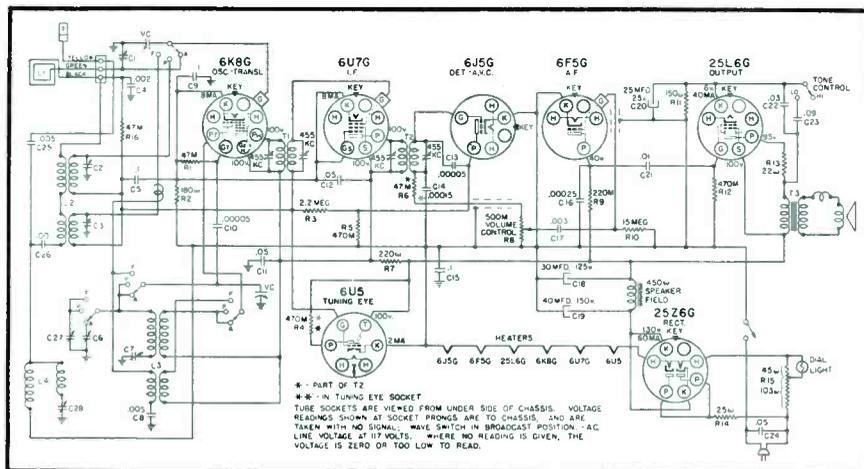



LEADS THE FIELD

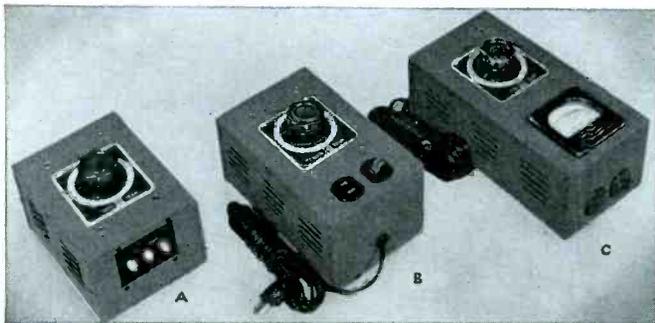

Varitran Controls

- ★ New roller contact . . . practically eliminates contact wear.
- ★ New glass-insulated wire . . . for positive dependability.
- ★ New large, copper, heat radiating disc . . . for cooler operation.
- ★ New copper alloy collector ring . . . eliminates pigtails and loose connections.
- ★ Core type lamination . . . for maximum ruggedness and minimum space.
- ★ New top and bottom mounting . . . for panel, chassis, or bench service.

FOR CONTROLLING: Line Voltage, Rectifier Output, Motors, Lights, Heaters, etc.

Variable voltage transformers for smooth voltage control. VARITRAN units employ a special non-fusing roller contact to contact the exposed turns of an auto-transformer winding. Rugged construction is employed, with glass insulation to assure dependability. Output of 115 Volt unit variable from 0-130 volts (230 Volt unit, 0-260 v.) smoothly without interrupting circuit. Output voltage independent of load.

Maximum Amp. rating applies from 0 to 20 and 95 to 130 volts. Between 20 and 95 volts current rating tapers off to 50% of rated current at 65 v. point.

Top and bottom mounting for laboratory bench or panel mounting. All units supplied mounted with terminal strips as in Fig. A, except V-1 (Fig. B) and V-1M (Fig. C.)

Type	Input Voltage	Output Voltage	Watts	Maximum Amps.	Approx. Wt. Lbs.	Net Price
V-0	115 volts	0-130	230	2	8	\$7.50
V-0-B	230 volts	0-260	230	1	10	9.50
V-1	115 volts	0-130	570	5	11	10.00
V-1-M	115 volts	0-130	570	5	12	15.00
V-2	115 volts	0-130	570	5	11	9.00
V-2-B	230 volts	0-260	570	5.5	14	11.50
V-3	115 volts	0-130	850	7.5	14	14.00
V-3-B	230 volts	0-260	850	3.75	18	18.00
V-4	115 volts	0-130	1250	11	32	20.00
V-4-B	230 volts	0-260	1250	5.5	38	25.00
V-5	115 volts	0-130	1950	17	45	32.00
V-5-B	230 volts	0-260	1950	8.5	56	37.00
V-6	115 volts	0-130	3500	30	90	60.00
V-6-B	230 volts	0-260	3500	15	90	70.00
V-7	115 volts	0-130	5000	44	120	87.00
V-7-B	230 volts	0-260	5000	22	120	95.00

Model 3A EQUALIZER



The universal characteristics of the UTC 3-A equalizer have made it the most popular item for broadcast and recording equalization. This unique unit, with which most communications engineers are already familiar is an accurately calibrated, quickly adjustable combined low and high frequency equalizer. Four controls are provided on the panel. The low frequency controls include a switch for adjusting the maximum equalization frequency to 25, 50, or 100 cycles and a calibrated T-pad for exact adjustment of the amount of equalization. The high frequency portion of this unit includes a switch to obtain resonance at 4000, 6000, 8000 or 10,000 cycles, and a similar calibrated control reading directly in DB. It is ideal for equalizing lines, pickup and recording equipment, due to its flexible nature. Dimensions of panel 3 1/2" x 19". Depth 7 1/2". The new model 3-A is NOW THOROUGHLY SHIELDED AGAINST INDUCTIVE PICKUP WITH UTC TRI-ALLOY SHIELDING. Net price to broadcast stations or recording studios **\$85**

Linear Standard Transformers

UTC Linear Standard Transformers are available in sizes from minus 130 DB operating level to 50 kw. All standard units are guaranteed to be ± 1 DB from 30 to 20,000 cycles. The UTC LS-10 input transformer illustrated, incorporates tri-alloy magnetic filtering, which, combined with the UTC hum balanced coil structure, assures lowest hum pickup ever attained in an input transformer.



UTC has been supplying hum-balanced power supply equipment to Western Electric, Electrical Research Products, and other organizations for over four years. The use of hum-balanced construction plus the UTC high permeability cast shield reduces external flux to extremely small values. All UTC Linear Standard power supply components can be obtained in this form of construction at a 30% increase above normal list prices.

UNITED TRANSFORMER CORP.

150 VARICK STREET ★ NEW YORK, N. Y.
EXPORT DIVISION: 100 VARICK STREET NEW YORK, N. Y. CABLES: "ARLAB"

SOUND IDEAS

By S. GORDON TAYLOR

A SOUND installation recently made in the Temple B'nai Jeshurun, a beautifully modern Synagogue at Newark, New Jersey, represents an interesting example of effectiveness combined with simplicity. It also displays how the sound man can often take advantage of existing conditions to aid him in his planning. An example, too, demonstrating that tricky installations, high power and special speaker equipment so common in larger churches are not by any means always essential to successful results.

In this installation the sound system is used exclusively for speech reinforcement. The seating area takes the form of a rectangle with its four corners cut out with balconies extending across the rear and entirely down both sides. The general arrangement is that shown in Fig. 1. Above this the cathedral-like structure towers perhaps eighty feet, the walls converging into a great dome.


The common practice in such installations of grouping directional speakers overhead was considered impractical. First it would mar the architectural beauty, but, more important, the relatively deep but low balconies would result in large shadow areas beneath. Unless placed directly overhead, sound distribution even through the unshadowed portion of the main floor would be non-uniform. If placed directly over the center of the floor those seated in the front half would experience the undesirable effect of hearing the speaker's voice coming from behind them. Added to all this, uniform-

ity of distribution would require considerable elevation and the propagation of sound over such a distance would involve the use of relatively high power.

The solution of the problem was found in the use of a total of ten standard speakers, eight of them distributed around the walls below the balcony and two over the rear balcony. Off-hand this might suggest trouble from phase relationships, confusing multi-point sources, etc., but no trouble is experienced from these because the speakers are operated at low level. Theoretically, with some overlapping of the fields of the different speakers, such troubles cannot be completely overcome. Practically,



however, it goes unnoticed. Except for a small area in the center of the main floor, each member of the congregation is serviced primarily by some one speaker. Those in the center may be simultaneously in the fields of two speakers but because these are symmetrically disposed, one on either side of him, the effect is neither displeasing nor confusing.

An important consideration in this

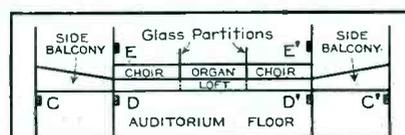

E, E' = Speakers in balcony.
All others located on main floor.

Fig. 1. (Right) Floor plan and elevation of the seating areas of the Temple with single-deck balconies at each side and rear. The speaker arrangement is shown with the eight speakers on the main floor and two in rear balcony, all directed away from the microphone by their sloping-face wall baffles. Shown below is a panorama view of interior of Temple B'nai Jeshurun as viewed from the rear. Three loudspeakers may be seen in each side view, just below the balcony. A total of 10 speakers operated at low level provide highly uniform coverage of a congregation of 2,000 persons distributed over approximately 13,000 square feet of floor space on main floor and balconies. A Lafayette amplifier, Model 480-T, rated at normal output of 45 watts, provides more than ample power to drive these speakers. Walls are of brick imported from Jerusalem which, surprisingly, provide excellent natural sound-absorbing characteristics.

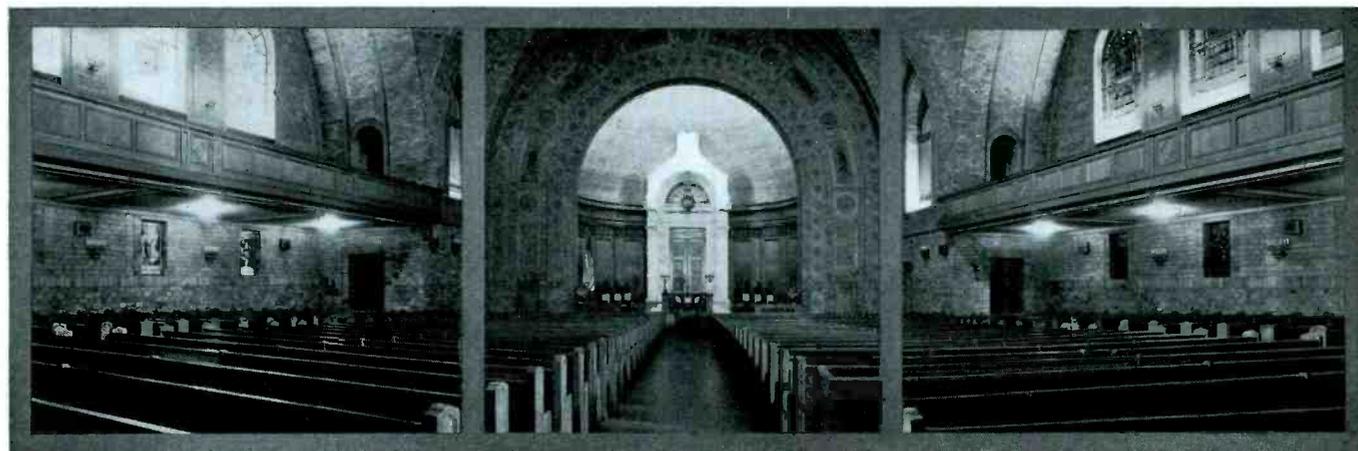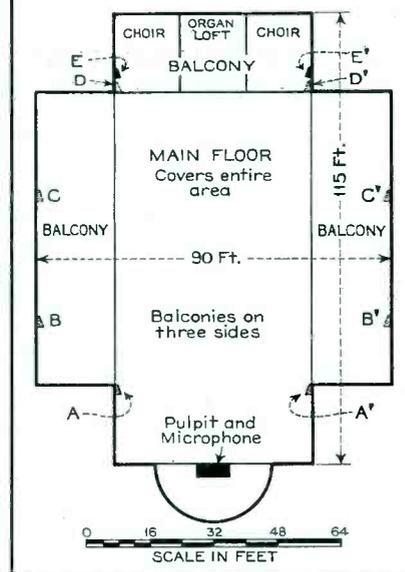



connection is that all speakers are in angular wall baffles and are so placed that the speaker output is directed about 20 degrees toward the rear. This arrangement not only tends to reduce undesirable overlapping of adjacent speaker fields but helps to maintain the impression of sound coming from the front and helps avoid acoustic feed-back.

The use of several speakers operating at relatively low levels tends to provide uniform distribution of sound. In

speakers above these balconies.

This was not, however, true of the rear balcony where the choir and organ are located. This is partly due to the fact that this balcony faces the long dimension of the auditorium, and further, that glass partitions inclosing the organ loft probably tend to break up this area. In any event it was found desirable to install one speaker in each of the choir areas.

The speakers are all Jensen Type

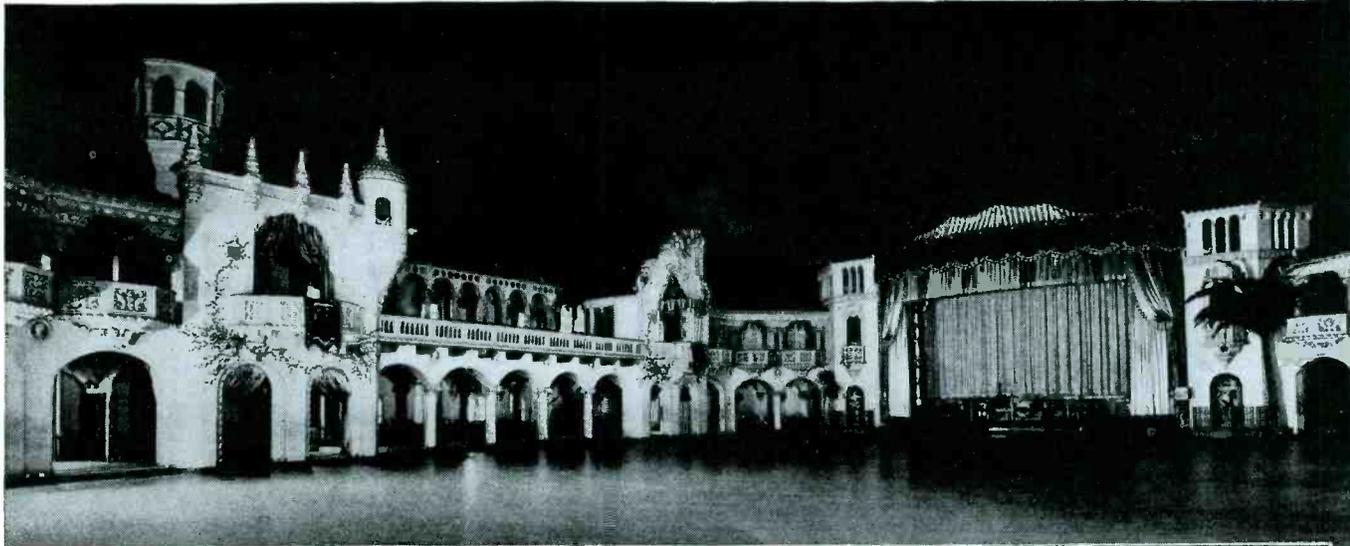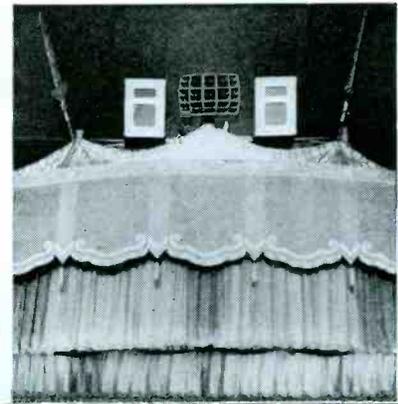

addition to this (and this is one of the things referred to above in the mention of existing conditions which may be utilized advantageously) by placing the speakers well up, close to the underside of the balconies, this horizontal surface and the wall serve to project the sound outward and somewhat downward, concentrating it on those seated at a distance. The elevation of the speakers above their heads, on the other hand prevents unnatural loudness in the case of those near the speakers. Add to this the further fact that those seated in the center of the floor hear sound from both sides and it becomes quite understandable why a difference in level of only a very few db is experienced as one moves from a speaker out toward the center of the floor.

An interesting phase of this installation is that no special provision had to be made for those seated in the side balconies. Tests showed that the spill-over from the downstairs speakers provided adequate level for complete comfort, although the sound reaching these listeners is necessarily practically all by reflection. The level is, of course, somewhat below that encountered on the main floor, but not so much lower as to justify the installation of additional

Fig. 2. Chicago's beautiful Aragon Ballroom where more than 6,000 couples dance on one giant floor. The resulting background noise, together with a unique acoustic situation created by the domed ceiling, posed a difficult problem in sound distribution for the sound engineers. They solved it by installing special sound equipment which made maximum use of both directional microphones and directional loudspeakers.

A12PM in Lafayette walnut wall baffles. Each is equipped with variable T pad which, adjusted during preliminary tests, remains fixed. These adjustments in the case of speakers B, B1, C and C1 (Fig. 1), are for normal level. The others are all set for considerably below maximum output. The balanced effect obtained in this way contributes importantly to the uniformity of level throughout the area.

The amplifier is a Lafayette Model 480T with a normal rating of 45 watts, peak 65 watts. The fact that it is never necessary to open up this amplifier more than about half-way is an indication of the efficacy of the speaker system. The amplifier, conveniently located in a passageway just off the rostrum, includes an output level indicator meter, overall



Illustration courtesy Western Electric

gain control and both bass and treble compensator controls on the front panel.

In this location it is reasonably close to the Shure Unidyne microphone and is freely accessible at all times during services. The volume indicator simplifies adjustment for the lay operator.

An amplifier of lower output could have been used here but it was the feeling that reserve power to more than meet all possible requirements was more desirable than the economy that could have been gained through the purchase of a smaller amplifier. This is quite in keeping with the stress laid throughout on effectiveness as the primary requirement and economy as a highly important

(Continued on page 18)

... HOW TO MAKE MORE



Everything you want **NOW**

All the latest models of leading manufacturers available

GET THE EQUIPMENT **FREE** YOU WANT THE N.U. WAY...

Ask your N.U. jobber how much down deposit is required on the equipment you want. Sign the N.U. agreement for purchase points. (Deposit refunded when purchase points reached.) No delay . . . equipment comes directly to you. *Thousands of Dealers have Completed N. U. Deals.*

Over 50,000 N.U. Equipment deals have been completed and dealers' deposits rebated. Here's how it works—Your N.U. jobber keeps a record of your purchases of N.U. tubes, condensers and batteries. As soon as required number of purchase points are reached, N.U. immediately rebates a merchandise credit to you for full amount of original deposit and sends you a clear Bill of Sale on the equipment. The simplest and easiest way to get efficient equipment in the radio service industry.



Own Better Equipment

use the **N.U. FREE Equipment Plan**
Widest Assortment Leading Makes
Paid for by Your Purchases of



NATIONAL UNION RADIO TUBES

Quality is the National Union BY-WORD. Radio Service Dealers everywhere recognize the research, skill and time-proven experience that backs every National Union Tube. Just ask any National Union Dealer about his freedom from trouble or call-backs. For absolute customer satisfaction feature National Union QUALITY.




NATIONAL UNION SOUND X/TRA TUBES

N.U. presents a new line of tubes for heavy duty audio work branded SOUND X/TRA. These tubes are interchangeable with ordinary tubes of like characteristics, but in performance they are demonstrably superior. SOUND X/TRA Tubes are exceptionally uniform, low in hum, non-microphonic, and have high power handling capacity with minimum distortion and long life. Now available at your National Union distributors. SOUND X/TRA tubes count as purchase points on National Union deals.



NATIONAL UNION CONDENSERS

Feature high breakdown voltage . . . uniformity . . . close tolerances . . . low leakage . . . low power factor . . . a complete line of replacement condensers tailor-made to the radio service dealer's needs. Uniformity and excellent electrical characteristics eliminate call-backs and field difficulties. Smaller sizes and mechanical ruggedness assure quick and easy replacement installations. You owe it to yourself to standardize on National Union Condensers. They count as purchase points on N.U. Equipment deals.

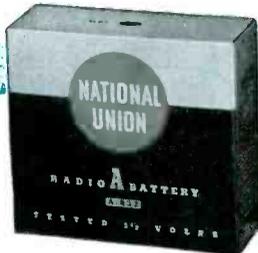

NATIONAL UNION BATTERIES

Who is going to get the profitable battery business? You as a Radio Dealer or the drug store and filling station? Push National Union Batteries—N.U. will back you up with sales-helpers that *get* the business. National Union Batteries are absolutely tops for quality and are fully guaranteed. You profit further by using National

Union Batteries as purchase points on N.U. Equipment Deals.

NATIONAL UNION . . . *Supreme in Quality*

RCA RIDER VOLTOHMYST

THE RCA Rider VoltOhmyst is designed to measure d-c voltages and d-c resistances over a wide range. As a d-c voltage measuring device its range of operation is from 0.05 volt to 5000 volts. Its input resistance is constant at 16 meg on all ranges up to 500 volts and constant at 160 meg on all ranges between 500 and 5000 volts.

The instrument will measure d-c voltages which are positive or negative with respect to ground, without switching leads and can be used for the measurement of d-c operating and control voltages up to 500 volts in signal-carrying circuits with the signals present. The instrument will not interfere with the operation of the circuit or element across which it may be connected. It is not necessary to reset the zero when changing voltage ranges. The accuracy of the voltmeter is within 2% of full scale.

The ohmmeter operates over a range from 0.1 ohm to 1000 meg without requiring resetting of the zero when changing ranges. The ohmmeter test voltage varies from 0.03 volts across 0.1 ohm to a maximum of 3 volts across 1000 meg. The accuracy of the ohmmeter is within 3% at center scale.

Circuit

The VoltOhmyst uses a push-pull electronic vacuum-tube voltmeter circuit of which is shown in Fig. 1. The two tubes V1 and V2 are linked by means of a common high resistance R40. Because of this coupling, any change in the input voltage to the grid of V1 changes the cathode bias of V2 and as a result the change in the plate current of V1 is accompanied by a simultaneous change in the

plate current of V2 in the opposite direction. The differential voltage thus developed across the load resistors R45 and R43 is applied to the meter, which is calibrated in terms of the voltage applied to the input and in terms of the resistance being measured when the instrument is used as an ohmmeter.

In addition to the push-pull action, a high degree of self-regulation is obtained as a direct result of the high value of coupling resistance R40. This is analogous to the regulating effect secured through the use of self-bias but because R40 is approximately 100 times as large as the value of cathode resistance which it is possible to use in conventional circuits, the self-regulating action is correspondingly increased. At the same time the excessive loss of sensitivity normally experienced when using such a high cathode resistance is eliminated in the VoltOhmyst because of the balanced nature of the circuit. A controlled amount of inverse feedback to obtain independence of tube characteristics is secured by means of the two resistors R41 and R42.

The voltmeter probe has a 1-meg isolating resistor built into the bakelite sleeve, thereby preventing the capacitance of the shielded cable and input circuit from reacting upon the circuit under test. Because of this construction, dynamic d-c voltage measurements can be made in circuits where a-f, i-f or r-f signals are present.

When checking the d-c voltage in circuits where a-c is present, the a-c component is attenuated by means of a filter network (constituting a series resistor hav-

ing a minimum value of 8.5 meg and condenser of 0.005 mfd). Since the VoltOhmyst is essentially linear there will be no error as a result of rectification unless the peak a-c voltage after attenuation exceeds the full scale reading of the range to which the instrument is set. For all ordinary measurements the attenuation of the

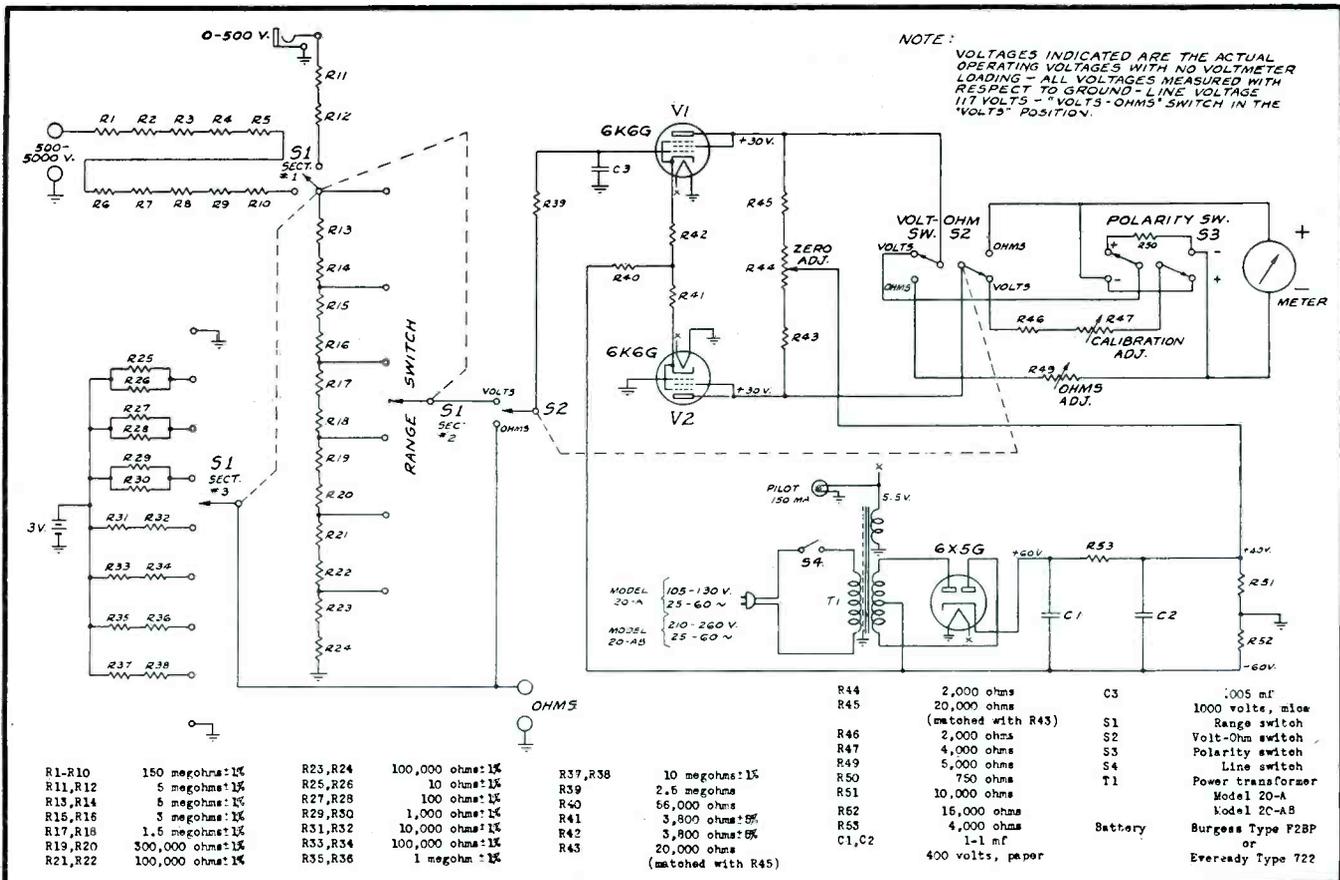


Fig. 2. A single adjustment of the ohmmeter zero point is all that is required for every range of the instrument.

filter is sufficiently great so that an a-c component present will have no effect on the reading.

Oscillator operation can be checked with the VoltOhmyst by measuring the rectified voltage present at the control grid of the oscillator tube. To make this measurement the voltmeter probe is placed in contact
(Continued on page 25)

Fig. 1. The VoltOhmyst uses a push-pull electronic vacuum-tube voltmeter circuit. The vtvm is also used as an indicator in the ohmmeter circuits.



T H E A T R E D I S P L A Y

By M. HOVER

The success of this service shop can be attributed, by and large, to the employment of novel business getting ideas. Herewith is one, which, aside from attracting a favorable clientele, will do much toward increasing the shop's prestige and also promote friendly relations with the local theatre.



The Allied Engineering Services, 410 Marion Avenue, Lima, Ohio, of which the author is sales manager, placed this display in the lobby of their local theatre a few weeks before H. G. Wells' picture, "Things to Come", was featured. Another attractive display in the window of their own shop tied in with that in the theatre. This is only one of many business getting ideas which help make Allied one of the most prosperous service shops in the East.

OVER a period of years we have built up a business catering to almost every branch of the electronic art. We handle talking picture service, custom built amplifiers, recording equipment, p-a systems, and photoelectric controls. We also service x-ray equipment.

The tendency of our line is to be rather unsteady and business goes by spurts. In order to take up the slack and keep our shop busy at all times, we were confronted with the problem of building up a radio service business, preferably among clients with ample financial means who would demand precision work and be willing to pay for it.

Previous experience had shown us that ordinary forms of advertising attracted too many customers who were interested in free service, free tube testing, and maximum repair per dollar. We solved this problem by cooperating with the management of our largest theatre.

More than once each year some picture is presented which offers a tie-in with our business, such as "The Big Broadcast," "Things To Come," "Young Tom Edison," etc. With pictures of this type we assemble an elaborate lobby display, closely related to the subject of the picture. This display is placed in operation at least two weeks in advance of the picture, and in some cases has been retained through the run of the play, due to public interest.

The accompanying photograph shows a display assembled for the H. G. Wells picture, "Things to Come." An amplifier, microphone, and oscillograph were hooked up and a printed card invited the patrons to see their voices. Both ancient and modern vacuum tubes, particularly those developed for the talkies, were given considerable space. A slowly rotating mirror picked up the beam from a spotlight, passed it to a photocell control which operated a slide projector, intermittently flashing on the small screen the announcement of the coming attraction. Only a small card was used to identify the owner of the equipment, but one of our employees was in attendance most of the time to answer questions and assist in the display. *Considerable newspaper space was devoted to the unique demonstration.* About one patron out of twenty inquired as to who built the equipment and all about it. The attendant could then bring up the matter of radio service, and in many cases was able to get the telephone number and address. After that, the going was easy. The customers seemed more willing to talk business, and what was just as important, to pay for it.

At present, we are working on a tie-in with Metro's "Thomas Edison, the Man." We will display some of the original Edison motors, motion picture projectors, dictographs, telautographs, an historic lamp display, and the modern counterparts of this equipment. All this will be through the courtesy of our company, Allied Engineering Services, Precision Radio Service Our Specialty.

As a business builder this plan has been very successful.

MONEY IN RADIO SERVICE

Sell yourself

TO YOUR COMMUNITY

WITH

N. U.'s Outstanding Assortment of Dealer Helps

You may be the best radio technician in the world, but unless the public knows it—how are you going to sell yourself and get new business? National Union has helped thousands of dealers to sell themselves and to make more money. N.U. can help you, too.

Remember, National Union specializes in selling through the radio service dealer and the radio parts distributor. Because of this specialization National Union understands the radio service dealers' problems. In helping Service Dealers to better business, N.U. has developed the most varied assortment of *Sales-Helps* of any company in the industry. Every piece (see illustration to right) is of time-tested, practical value. Select the sales-help that will best help you sell yourself to your community. Your N.U. Distributor will gladly cooperate with you.

- | | | |
|----------------------------------------------------|--------------------------------------------------------------------|----------------------------------------------------------------|
| 1. Official Radio Service Analysis and Test Report | 7. Guarantee Form | for N.U. Stock Tabs |
| 2. DeLuxe Radio Log | 8. Radio Tube Handbook | 18. Complete Stationery Kit with Letterheads, Bill Forms, etc. |
| 3. Price Card and Interchangeability Guide | 9 10, 11, 13, 14, 15. Various Mailing pieces and business letters. | 19. Job Ticket & Invoicing System |
| 4. Cartoon Post Card Series | 12. Outdoor Sign | 20. Quick Reference Condenser Listing |
| 5. N.U. Electric Clock | 16. Large Window Display | |
| 6. N.U. Radio Date Labels | 17. Inventory Control Carton | |



Get into SOUND SERVICE



The Ideal Sound System for Demonstration or Rental. Erwood Model 1420 is a 20-watt Mobile Sound System for 6 Volt D.C. or 120 Volt A.C. Phonograph turntable is integral part of system. Complete in one case with microphone and two 12" P.M. speakers. Equipped with National Union SOUND X/TRA Tubes. See your N.U. Distributor for complete details.

If you can service radio sets, you can learn to service Sound Systems. National Union is continually collecting and issuing valuable information on Sound Service. The volume of Sound Sales and Service is growing all the time. It is a business that all better Radio Service Dealers will eventually want to get into. If you are interested in Sound Service, be sure to fill out coupon below.

S-7

NATIONAL UNION RADIO CORPORATION, 57 State Street, Newark, N. J.

I am interested in obtaining the following equipment—FREE . . . THE N.U. WAY . . .

I am interested in learning more about SOUND SERVICE. Name . . .

I would like to know more about SOUND X/TRA Tubes. Address . . .

Please add my name for free copies of your House Organ "What's New in Radio." City . . . State . . .

NATIONAL UNION . . . Choice of Leading Technicians

SOUND IDEAS

(Continued from page 15)

tant but definitely secondary consideration.

Proving that a good job is the sound man's best advertisement, a second



Illustration Courtesy Western Electric

Fig. 3. All instrument enhancement, at the Aragon installation, takes place at a single control panel. An individual monitor speaker provides the operator's ears with a continuous check on the musical balance while his eye follows the volume level on a standard VI meter.

sound system was later installed in the large assembly hall used for entertainments and various other social activities. Here the requirements were met with a Lafayette 30-watt amplifier, two Jensen A12PM speakers, Shure crystal mike and a record player.

Ballroom

In marked contrast to the hushed stillness of the Temple B'nai Jeshurun, Chicago's Aragon Ballroom presented the ear-disturbing shuffle of twelve thousand dancing feet on a hard maple floor. Because of the size and peculiar acoustics of the Aragon, the strains of Dick Jurgens' orchestra failed, particularly in the remote sections of the ballroom, to dominate the welter of laughter, conversation and other incidental crowd noise. After months of pondering over the problem, bandmaster Jurgens finally hit upon the solution: employing a Western Electric sound system which uses directional microphones and speakers in which separate elements project the upper and lower register sounds. This directional apparatus solved the problem of achieving uniform distribution. Proper balance of the amplified music is restored by means of controllable amplifiers in which both the bass and treble tones may be varied

at will. Following the initial tryout of the system, Mr. Jurgens said, "That is one of the most natural reproductions of tone I have ever heard over a sound system."

According to Walter Boom of the Boom Electric Company, which made the installation, the new system is extremely simple to operate despite its seeming complexity. All instrumental enhancement takes place at a control panel which resembles the console of a pipe organ. An individual monitor speaker provides the operator's ears with a continuous check on musical balance while his eye follows the volume level on a VI meter.

Fire Departments

FIRE departments have been slow to give up the old gong systems, but there is much to be said for the substitution of city-wide sound sys-

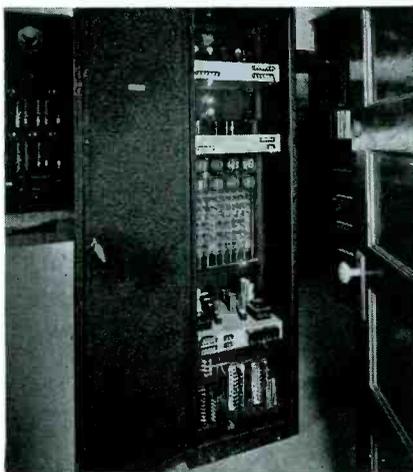


Fig. 4. In Beaumont, Texas, the local fire department features a centralized sound system with 70 speakers for its 11 stations. All of the station fire chiefs' cars are equipped with two-way radio, as are some of the larger fire apparatus. The entire system is interconnected with the police system so that reports are broadcast over the latter system as well.

tems which permit alarms to be spoken, accompanied by detailed directions for apparatus, etc. It is understood that many cities have evidenced interest in such installations, indicating possibilities of an important market.

In Beaumont, Texas, each of the 11 fire houses has been equipped with one or more sound units which not only replace the old gong for fire alarms, but permit two-way voice communication between stations and police headquarters. Work and design was under the supervision of John D. Southwell, Su-

perintendent of the signal division.

The central system is housed in a signal building which also has a dispatcher and his console or switchboard. There are 11 fire stations in the city, all of which are equipped with an amplifier and speaker (see Fig. 5) for talk-back. In several of the larger stations extra units are in operation as well as in the homes of the fire chief, his first and second assistant, police station, officials, etc. A total of 70 Oxford 12-in p-m speakers are used. Two separate conversations can be carried on simultaneously, but should an alarm come in, the dispatcher operates a switch that breaks in and clears all lines of conversation so he may report the fire over the system without delay. At the same time the report is broadcast over the police radio. All of the station fire chief's cars are equipped with 2-way radio, as are some of the larger fire equipment.

A further use that the system is put to is in the direction of apparatus during a fire. Each piece of equipment is carefully directed and stations emptied are reinforced with apparatus from near-by stations. Reinforcements are sent up and shifts made at the scene of the fire which are directed by the chief through his radio transmitter. Later each piece of fire equipment is checked in and reports received as to the amount of water used, chemical, hose, etc. . . . A perfect system of coordination and cooperation has been worked out and is participated in by the police department.

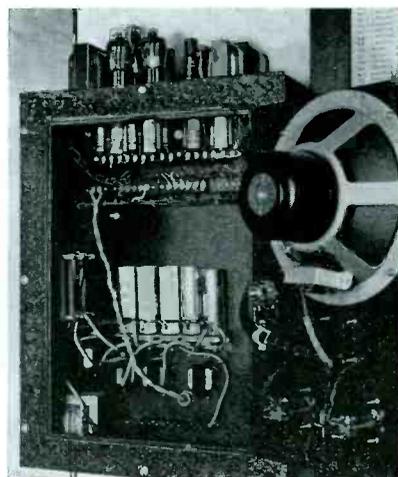


Fig. 5. Extra units, such as that shown above, are in operation in several of the larger stations as well as in the homes of the fire chief and his first and second assistants. Two two-way conversations can be carried on simultaneously but, should an alarm come in, the dispatcher can clear the lines so that he may report the fire over the entire system without delay.

YOU SAVE \$1⁰⁰

by using the
**Group
Subscription Plan**

OUR GROUP SUBSCRIPTION PLAN enables you and three or more of your co-workers to subscribe to SERVICE at one-half the regular yearly rate. In other words it will cost you and your friends only \$1.00 each for twelve issues of SERVICE. The G-S-Plan low rate only applies when 4 or more subscriptions are ordered at one time. (Foreign \$2.00.)

Speak to three or more of your friends . . . let them sign up with you and then you can remit for the whole group. (Renewals or extended subscriptions are acceptable as part of a group.)

TEAR OUT AND MAIL

SERVICE—19 E. 47th St., N. Y. C.

Please enter annual subscriptions (12 issues) for each of the undersigned for which payment is enclosed at the rate of \$1.00 each; foreign \$2.00. (This rate applies only on 4 or more subscriptions when occupations are given.)

Name
Address
City-State
Occupation
Employed by
State whether Employer is a Service Organization, Dealer, Jobber
or Manufacturer

Name
Address
City-State
Occupation
Employed by
State whether Employer is a Service Organization, Dealer, Jobber
or Manufacturer

Name
Address
City-State
Occupation
Employed by
State whether Employer is a Service Organization, Dealer, Jobber
or Manufacturer

Name
Address
City-State
Occupation
Employed by
State whether Employer is a Service Organization, Dealer, Jobber
or Manufacturer

PREPARE NOW!

**It's Easier to Keep Abreast
Of These New Develop-
ments Than It Will Be
To Catch Up With Them!**



Your future in the servicing business will depend largely upon your knowledge of these new developments in radio. NOW is the time to prepare . . . if you expect to be able to compete successfully for the service that will soon be required. Don't put it off! Start now, by devoting a few minutes each day to study of these easy-to-understand books by John Rider. You can look them over at your jobber's. Do it today!

FREQUENCY MODULATION

by John F. Rider

The most talked of subject of the moment, Rider offers this introduction to frequency modulation with special attention to F-M receivers and the problems they will present to the serviceman. Get this now—be ready. 136 pages—only \$1.00.

erator you now are using. Get your copy TODAY! 256 pages—illustrated—\$1.50.

AUTOMATIC FREQUENCY CONTROL SYSTEMS

by John F. Rider

With Automatic Frequency Control Circuits in most new higher priced models, knowledge of "AFC" means money in your pocket! Learn the practical facts from these easy-to-understand explanations. Get your copy today. Cash-in on profitable "AFC" work. Hard covers—144 pages—\$1.00.

SERVICING BY SIGNAL TRACING

by John F. Rider

Use the system of servicing which is proved and endorsed, fastest—most modern, the system you can apply to all receivers regardless of age, type or make. Servicing by Signal Tracing operates independently of every limiting factor heretofore encountered. In this new book you learn how all receivers are brought to a common servicing level. Learn how components receive a functional check! This is the most definite and positive form of trouble localization! Over 360 pages—hard covers—only \$2.00.

THE CATHODE RAY TUBE AT WORK

by John F. Rider

This is the most complete and practical book ever written on the subject—the only one prepared especially for the radio serviceman. New applications of the cathode ray tube during the past five years require that servicemen know its operation. 336 pages—over 450 illustrations—\$2.50.

OSCILLATOR AT WORK

by John F. Rider

Don't guess—KNOW! This new book tells all about ALL oscillators. Explains theory by means of simple illustrations, diagrams and curves. Gives you practical facts. Make certain to get your full money's worth from the test oscillator or signal gen-

AN HOUR A DAY WITH RIDER BOOKS

On Resonance and Alignment . . . On Automatic Volume Control . . . On D-C Voltage Distribution in Radio Receivers . . . On Alternating Currents in Radio Receivers. 60c each.

JOHN F. RIDER Publisher, Inc.

404 Fourth Avenue, New York City
Export Div.: Rocke-Int. Elec. Corp., 100 Varick St., N. Y. C.
Cable: ARLAB

Read RIDER BOOKS



Oil

CAPACITORS

- ★ **AEROVOX** climaxes its conservative ratings policy in the **HYVOL** line of oil-filled high-voltage paper condensers. From the more-than-generous paper sections and the special **HYVOL** oil filling, to the hermetically-sealed metal container, the **AEROVOX** aim is to provide that extra safety factor so essential to builders of quality radio and electronic equipment. And note this choice of types . . .



Series -09 Rectangular **HYVOL**s are intended for heavy-duty continuous service at rated voltages, with ample margin for unexpected abuse. Heavy welded steel container; high-tension pillar terminals; adjustable mounting bracket permitting upright or inverted mounting at any height above or below chassis platform. 600 to 5000 v. D.C.W. 1 to 4 mfd. A quality product—at a popular price.

Series -05 Round-Can **HYVOL**s have long been the popular choice of amateurs. Conservative ratings for continuous, cool, troubleproof operation. Round aluminum can. Adjustable mounting ring. High-tension pillar terminals. 600 to 3000 v. D.C.W. 1 to 4 mfd.

Series -10 Inverted Screw Mounting. Same appearance and dimensions as usual metal-can electrolytic. Ideal for compact assemblies. 600, 1000 and 1500 v. D.C.W. .5 to 4 mfd.



Ask Your Jobber . . .


- ★ He'll gladly show you these **HYVOL** capacitors for transmitting and power amplifier uses. Ask for latest 1940 catalog, and also about free subscription to the monthly **AEROVOX RESEARCH WORKER**. Or write us direct.




PHILCO PHOTOELECTRIC PHONOGRAPH

IN AN attempt to increase record life and eliminate the necessity of frequently changing the needle as well as improve reproduction, Philco engineers have developed a photoelectric phonograph pickup.

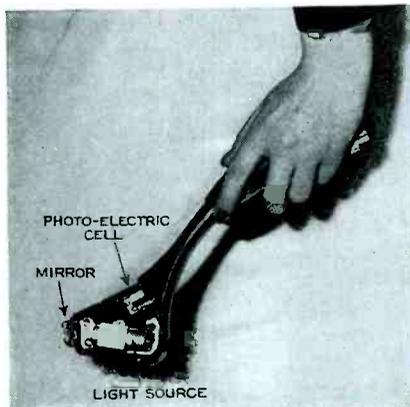The pickup consists essentially of a floating jewel (which replaces the



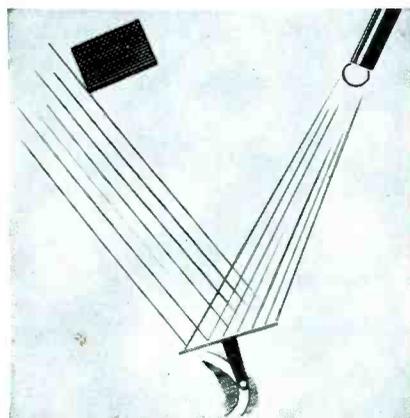A photoelectric cell, a light source and a tiny mirror, properly arranged on the end of the pickup arm, comprise Philco's latest development in record reproducing equipment. A 1.8-mc oscillator lights the filament of a special bulb. The record vibrations, transferred by the tiny mirror modulate this beam to operate the photocell.



needle) connected to a tiny mirror, a light source and a photoelectric cell.

As the floating jewel moves along the curve of the record groove, the mirror swings from side to side on its axis, flashing the beam of light on and off the photoelectric cell. Since the photoelectric cell translates light into electrical energy the flow of current generated in the photoelectric cell varies in proportion to the amount of light flashed in the cell as the mirror is swung by the jewel.

To minimize the amount of energy

required for the jewel to swing the mirror, it was necessary to utilize a paper-thin mirror specially designed for use in galvanometers. This is silvered with a vaporized aluminum and mounted on a tiny block which swings on an axis that floats on two flexible bearings.

To meet technical requirements as to size and weight a tiny bulb filled with gas to lighten the life of the filament was designed. It is also necessary that the beam of light at its source have no waver or flicker as this would register on the sensitive photoelectric cell in addition to the music and result in a hum in the speaker. Consequently, the household alternating current which operates the radio-phonograph had to be transformed into a steady flow of light by an oscillator which generates high frequency currents, stepping up ordinary domestic a-c from 60 to 1,800,000 cycles.

In this same connection—to insure a steady and unvarying flow of light—it was necessary to build the filament supports in the little bulb in the photoelectric reproducer of extra heavy wire to minimize any shaking on the part of the filament. Otherwise the musical reproduction would be marred by microphonic howl or noise generated by the flickering beam of light.

The tiny arm which supports the floating jewel is made of phosphor bronze of the exact thickness and length required to make that arm vibrate when a high note is reproduced. In other words, both the jewel and the jewel arm are vibrating with extra intensity in the high-frequency range, consequently an additional motivating force acts on the mirror, causing it to flash more light-signal to the photoelectric cell than if only the needle were vibrating in this range.

A special transformer is used to relay the currents generated in the photoelectric cell to the amplifier input.

The floating jewel has a rounded tip instead of the usual needle-like point.


WHEN YOU CHANGE YOUR ADDRESS

Be sure to notify the Subscription Department of **SERVICE** at 19 E. Forty-seventh St., New York City, giving the old as well as the new address, and do this at least four weeks in advance. The Post Office Department does not forward magazines unless you pay additional postage, and we cannot duplicate copies mailed to the old address. We ask your cooperation.


CIRCUITS

(Continued from page 12)

Fig. 11. In many new RCA Victor sets the dial lamp (Mazda No. 47) is operated directly from the line through a 790-ohm plug-in resistor. The resistor has a jumper which acts as a switch in

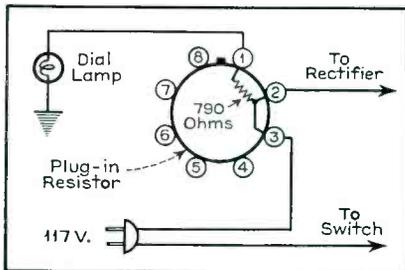

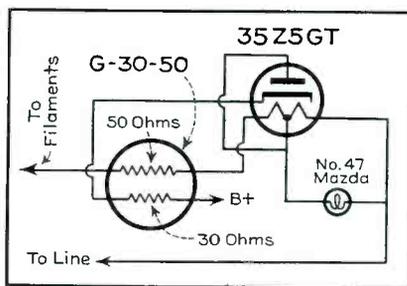The RCA 46X1 (Fig. 12, above) and the DeWald 663, 666 (Fig. 13, below) employ unique ballast circuits.



the line circuit so with the resistor removed there is no juice. See Fig. 12.

DeWald 663, 666

Some DeWald models also have a plug-in resistor but with dual functions. See Fig. 13. In model 666 there are two surge preventing resistors, a 50-ohm unit in series with the heaters and a 30-ohm unit in the rectifier cathode.

Silvertone 6324, 6424, 6493

The Silvertone seven tube, three band, a-c, d-c superhet models 6324, 6424 and 6493 have a 2-position tone control with an unusual arrangement in the power tube plate circuit. See Fig. 14. These sets use a 6J5G for detector and amplified avc and a 6F5G audio amplifier.

ASSOCIATIONS

Rochester, RTG

The RTG of Rochester held its annual dinner meeting at Canandaigua, N. Y., May 27. Twenty-four members attended and, after a fine steak dinner, listened to a stirring talk on Salesmanship by Frank M. Houston of the Rochester Gas and Electric Corp. On June 17 we were regaled with an instructive talk on radio gadgets for the service shop by John M. Thompson of Canandaigua.

A. T. MARSH, Sec.-Treasurer

NRPDA

The annual convention of the NRPDA took place at the Stevens Hotel, Chicago, during the week of June 10.

The annual meeting of the directors was called to order Monday, June 10. The first annual dinner

meeting of the NRPDA membership was opened on Thursday, June 13, at the Stevens Hotel, Chicago.

The report of the nominating committee recommending the reelection of the seven directors whose terms expired was approved and those directors were reelected. The membership was advised that commencing with 1941 the Board recommended that seven new directors be elected who had not previously served.

The new board of directors retired to elect the officers for the coming year and the following were unanimously chosen: George Barbey, president; Elliott Wilkinson, Abe Davis, Alex Hirsch, Aaron Lippman, vice presidents; William Schoning, treasurer; John Stern, secretary. Arthur Moss had again been retained as the executive secretary.

Sectional group meetings have

proven to be very effective and it is the immediate aim of NRPDA to establish sectional chapters in every important trading area in the United States.

The Representatives


The Representatives of Radio Parts Manufacturers held their fifth annual convention at the Stevens Hotel in Chicago on Thursday, June 13. Almost 100 members from all over the country attended the morning meeting, which was followed by a luncheon to which most of the members attended. The meeting was opened by our president, Sam MacDonald, who reviewed the progress of the organizations during his term of office and during the last five years. Starting with a group of 38 men in October, 1931. The Representatives have grown considerably year by year until today its roster numbers 150.

Progress during the last year in membership has been excellent, taking into account a small number of members who were taken off, the increase in membership during the last year was almost 30 members.

Trade Show

The Radio Parts National Trade Show will be held, next year, in the Stevens Hotel, Chicago, June 10 to 13, inclusive.

This was the unanimous decision reached at the annual meeting of the exhibiting members of the Trade Show Corporation Friday (June 14.) At the same time the following four directors were elected: A. A. Berard, representing the Sales Managers Club, eastern division; H. W. Clough, representing the Sales Managers Club, western division; and H. E. Osmun and J. J. Kahn, representing the Radio Manufacturers Association.

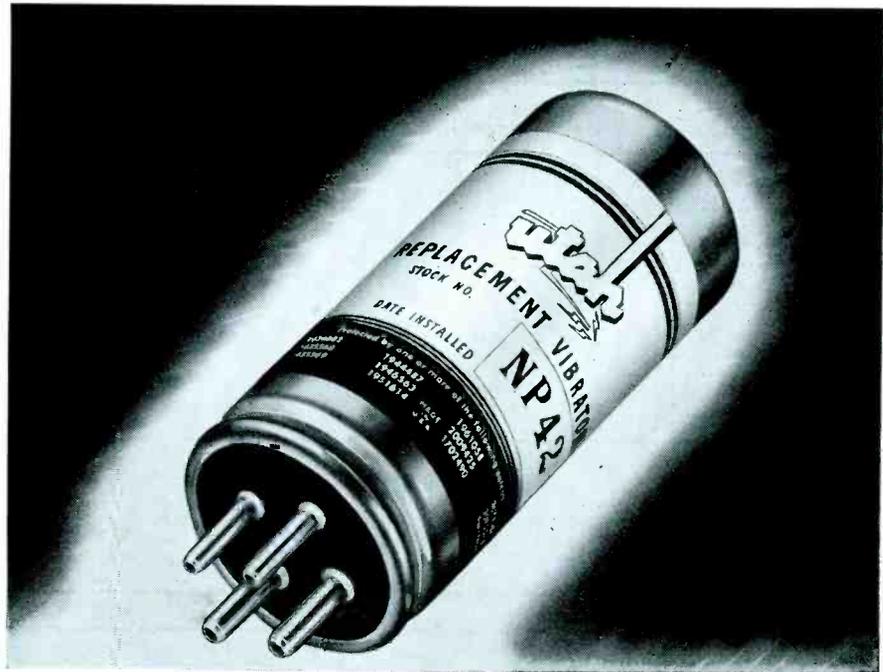

5

REASONS WHY THE DEMAND FOR UTAH VIBRATORS INCREASED 63%

The preference for Utah Vibrators has grown with the industry, because most of the important vibrator developments have originated in the Utah laboratory. Outstanding design and advanced engineering have maintained their leadership. In 1939 the demand for Utah Vibrators increased 63% because:

- 1 Complete exact replacements can be made with the Utah line.
- 2 Absolute dependability is assured by Utah's rugged, time-proved construction.
- 3 Finest materials obtainable are used in the manufacture of Utah Vibrators.
- 4 "Life Tested" in Utah's laboratory—the industry's most versatile and best equipped.
- 5 12 months guarantee—against defective workmanship and materials.

The assurance of complete satisfaction has led thousands of users to standardize on Utah Vibrators. You, too, can be sure of all these advantages by insisting on vibrators that carry the Utah label. For vibrator information, write Utah Radio Products Co., 816 Orleans Street, Chicago, Illinois. Canadian Sales Office: 560 King Street, W., Toronto, Ont., Canada. Cable Address: Utaradio, Chicago. In the Argentine: UCOA RADIO PRODUCTS COMPANY, S. R. L., Buenos Aires.



V I B R A T O R S
SPEAKERS • TRANSFORMERS • UTAH-CARTER PARTS

BATTERIES FOR PORTABLES

(Continued from page 9)

Model	Acme	Advance	Bond	Bright Star	Burgess	Eveready	Gen- eral	National Union	Philco	Rayo- vac	Usalite	Wil- lard	Win- chester
FADA (Fada Radio & Electric Co.)													
P22, PD22, PL22, P28, PD28	1A	118S6	747	...	868	2F4L	747	8CF4	...	P698L	646
	2B	830	284	...	30-33	M30	482	...	B861	P5S30	640
P24	1A	116	...	4824	660	6F	743	6F1	A831	P96	P96A	637	6F1 4814
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218
PL24	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1 4819
	2B	830	284	...	30-33	M30	482	...	B861	...	P5S30	640	...
P40, PD40, PL40, P47, PD47, PL58, PD49SW, P49SW	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1 4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218
P49, PD49, P58	1A	114	247	4826	462	4F	742	4F1	A830	P94	P94A	634	4F1 4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218
FARNSWORTH (Farnsworth Television & Radio Corp.)													
AT30 (C6-1)	1A	114	247	4826	462	4F	745	4F1	A830	P94	P94A	634	4F1 4816
	2B	Z30	482	V30AA	P7R30	...	V30AA ...
AT31 (C7-1)	1A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4 4817
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218
BT58, BT68 (C67, C68)	1AB	6FA60	...	60A4L	...	P60A4L	AB84	AB667	...
FEARNOLA (See Wells Gardner)													
FIDELITONE (See Wells Gardner)													
FIRESTONE (Firestone Tire & Rubber Co.)													
S7426-6, S7426-7, S7426-9, S7427-5	1AB	460-15	411	5DA60	...	60A2L	AB665	...
S7402-6	1AB	G4B60	...	60B4H
GAMBLE (Gamble Stores, Inc.)													
4B5, 5B3	1A	118	147	4829	860	8F	741	8F1	A833	...	P96A	635	8F1 4819
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218
1F465KC	1A	114	247	4826	462	4F	745	4F1	A830	P94	P94A	634	4F1 4816
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218
Coronado	1A	118S	817	4827	866	2F4	718	8F4	A834	...	P698A	638	8F4 4817
	2B	330	267	3017	30-03	B30	762	V30B	B860	P305	P5303	624	V30B 6218

(To be continued)

Mr. Radio Serviceman:

A NEW SEASON BEGINS— MOVE FORWARD WITH RSA!

Plans announced at the Radio Parts Trade Show make it more imperative than ever that you belong to RSA. All the new developments planned by manufacturers place increased responsibility on trained top-flight servicemen. Join other good servicemen in RSA! Send the Coupon today!

MAIL THIS COUPON NOW!

RADIO SERVICEMEN OF AMERICA, INC.
304 S. Dearborn St., Chicago, Ill.

Name

Address

City State.....

I am interested in R.S.A. Membership. Tell me about it.....

I am enclosing \$4.00 for National dues and initiation. Covers dues up to Jan. 1, 1941.....

(Does not include Local Chapter dues where Local Chapters are organized.) S-740

*Let's Grow Together
in 1940!*



RADIO SERVICEMEN OF AMERICA, Inc.


JOE MARTY, JR., EXECUTIVE SECRETARY
304 S. DEARBORN STREET, CHICAGO, U.S.A.

RCA VOLTOHMYST

(Continued from page 19)

with the control grid of the rectified voltage. The high input resistance of the Volt-Ohmyst and the design of the voltmeter probe reduce the reaction on the circuit being measured to a negligible value.

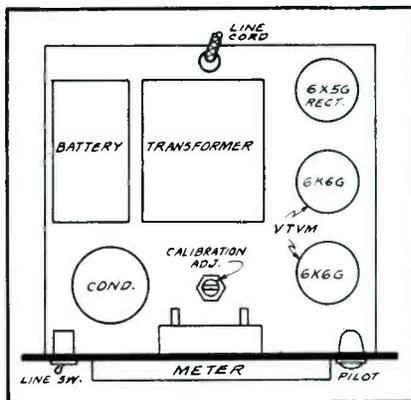The value of the rectified voltage across the oscillator grid leak is a direct measure



of the oscillator output. This voltage is negative and will, in general, vary as the oscillator is tuned. Dead spots at certain frequencies will be indicated by zero voltage or by a voltage dependent upon the grid return in the oscillator system.

The ohmmeter circuit utilizes the vacuum-tube voltmeter described above to measure the ratio between the voltage across the unknown resistance and one of seven standard resistors. The latter range in value from 10 ohms to 10 meg so that multiplying factors from $R \times 1$ to $R \times 1,000,000$ are provided. No readjustment of zero is required when changing ranges. The circuit is essentially independent of changes in the voltage and tube characteristics.

CONFIDENCE

J. A. BERRY, Berry Radio Service, Abilene, Texas, finds that confidence on the part of the public in his ability and equipment for rendering satisfactory service is most vital and helps him in obtaining a flat service charge for all service calls.

He makes his service car help to build that confidence. He not only keeps a comparatively new service car on the streets all the time but he periodically paints it, including the lettering, to keep it in such



an attractive condition that people not only see it but admire it.

"It creates an unconscious feeling of confidence that the man back of the truck knows his business," Mr. Berry declares.

He makes a minimum charge of one dollar for checking a radio set; and he believes the attractive appearance of his service car has a lot to do with selling people on the idea that the minimum check charge is just and fair. *Ruel McDaniel*

IT'S RCA FOR UNMATCHED QUALITY..UNBEATABLE LOW PRICES!

RCA AERODYNAMIC "MIKE"

Priced right for even the lowest cost job!



RCA Aerodynamic Microphone...MI-6226D (low impedance) MI-6228B (high impedance).



RCA Junior Velocity Microphone MI-4036G.



RCA Uni-Directional Microphone MI-4043, RCA 3-Way Microphone MI-4044.



RCA Pressure Microphone MI-4048A.



RCA Velocity Microphone MI-4027B.

THE RCA Aerodynamic Microphone is typical of the world's most complete line of "mikes"! It's tops in quality, low in cost. Has proved its value through splendid performance under the most difficult conditions. In the air, on the ground—even in a diver's helmet under water, the quality is outstanding.

No matter what kind of installation you make you have satisfied customers when you use RCA microphones. Pressure, velocity, lapel, uni-directional, bi-directional, non-directional—all types are available, for use outdoors or in. And remember—the prices are right.



Commercial Sound

RCA Mfg. Co., Inc., Camden, N. J. • A Service of Radio Corporation of America

Any sound system sounds better, equipped with RCA Radio Tubes

AGAIN IT'S...
WILCOX-GAY

**NOW SELL LOW-COST
SIMPLIFIED
HOME RECORDING**

**New!
GI-R70**



To cut records—place cutting arm over uncut record blank. To play back—place pickup on record. It's just as easy as that.

GET these new, profitable extra sales to service customers—sell them new GI-R70 low cost, simplified home recording.

Prospects in countless homes—also business executives, lawyers, actors—music, drama and public-speaking teachers and pupils—many others.

GI-R70 Home Recording Assembly includes: Feed-screw cutting mechanism—concealed for attractive appearance—with separate arms for pickup, and cutter; powerful rim-drive motor of special design; weighted turntable with retractable record driving pin. Complete unit, mounted on sturdy base plate, ready for case or cabinet.

Go after your share of the rapidly-growing business in home recorders and repeat sales of recording accessories—blanks, needles, etc.—with this popular new assembly, made by the world's largest phonograph motor manufacturer.

Send today for new catalog and price list

The GENERAL INDUSTRIES CO.

4043 Taylor Street, Elyria, Ohio



At a Triplett general sales meeting held June 7, 8 and 9, Triplett representatives from the United States and Canada posed for their picture. It was taken in front of the Triplett farm just outside of Bluffton, Ohio, where all sales meetings are conducted.

RCA BP10 BATTERY PORTABLE

THE RCA BP10 is a personal receiver housed in a small case with a hinged lid and may be carried about conveniently. The receiver is designed for operation on a single large flashlight cell and a special 67.5 volt B battery which fit into the back of the receiver as shown in Fig. 2.

The loop antenna is housed in the plastic lid and is connected to the receiver circuits through two thin metal strips. The tuning and volume controls are two knurled finger wheels extending through slots at the end of the set just under the

lid. A small rectangular opening in the panel under the dial numbers. The off-on switch is arranged so that the set turns itself off when the lid is closed.

A superheterodyne circuit employing the miniature 7-prong tubes is utilized. Avc is also provided.

Specifications

- Chassis No.: RC544.
- Type: Camera portable.
- Cabinet dimensions: 3 by 8 $\frac{1}{8}$ by 3 $\frac{3}{8}$ in.
- Weight: 3 $\frac{3}{4}$ lbs net.
- Tuning ratio: 1 to 1.
- Range: 540 to 1600 kc.
- I-f peak: 455 kc.
- Power supply: A, 1.5 v.; B, 67.5 v.
- Power consumption: A, 0.25 amp; B, 8.5 ma.
- Power output: 0.05 watts, undistorted.
- Speaker: 3-in, p-m; voice coil, 3 ohms at 400 c.


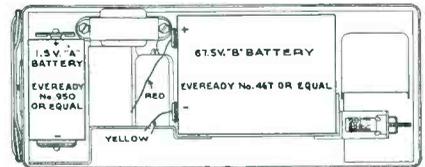


Fig. 2. (Above)

The RCA BP10 camera type battery portable employs a special 67 $\frac{1}{2}$ -volt B battery and a regular 1 $\frac{1}{2}$ -volt flashlight cell as A battery.

Fig. 1. (Below)

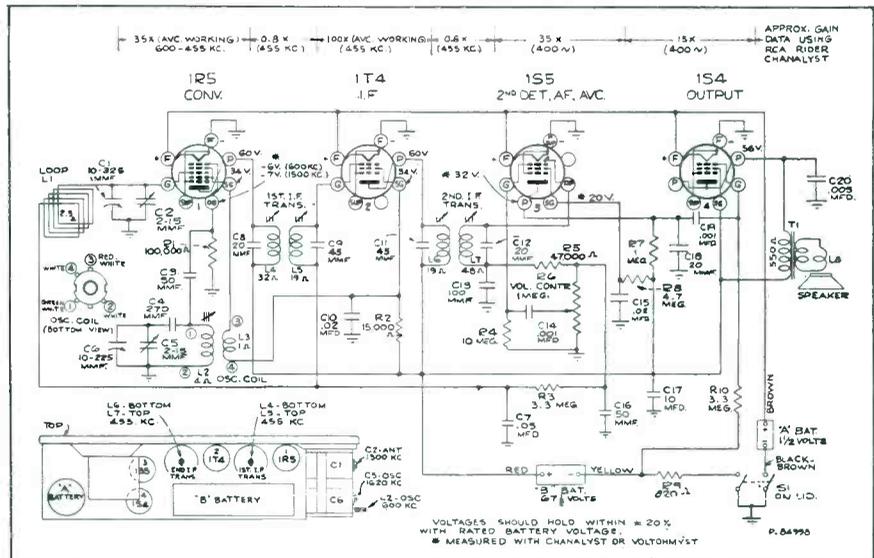

SOLAR

Sealdtite

WAX-MOLDED

Tubular Paper Capacitors . . . molded in hard wax . . . no moisture can enter . . . much longer life . . . buy from your jobber in factory-sealed cartons.

Write for Catalog

SOLAR MFG. CORP. Bayonne, New Jersey

A GOOD NAME GOES A LONG WAY


Ken-Rad Radio Tubes can be depended upon to bring you profits because they are dependable in service and easy to sell.

KEN-RAD TUBE & LAMP CORPORATION
Owensboro, Kentucky

KEN-RAD

DEPENDABLE RADIO TUBES

BIG BOY

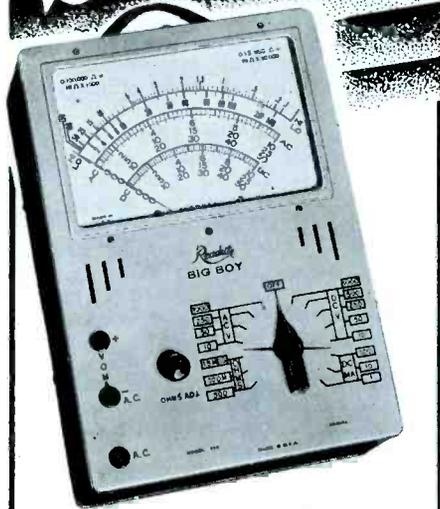

MODEL 860

Readrite
RANGER

Performance . . Eye Appeal . . Value . .
Sensationally Priced at **\$17.85**,
Dealer Net Price.

Here is an AC-DC Volt-Ohm-Milliammeter with all the ranges you want . . . easily readable on the large 7" instrument with extra-long 6" scale, in a new up-to-the-minute three-tone case. DC Volts 0-10-50-250-500-1000 at 5000 Ohms per volt DC; 1000 ohms per volt AC. AC Volts 0-10-50-250-1000 at 400 ohms per volt; DC Ma. 0-1-10-100; Resistance ranges: 0-1500 Low Ohms; 0-750,000 Ohms and 0-7.5 and 0-15 Megohms. Maroon case with cream panel, attached handle.
Dealer Net Price, \$17.85

For Catalog Write—Section 717, College Ave.

READRITE METER WORKS, Bluffton, Ohio

MIDGET SPEAKER

Oxford Tartak Radio Corp., 915 W. Van Buren St., Chicago, is now ready to market their small Permag cabinet speaker, Model 3ZM-CA. Measuring 4½"x4"x1⅞",



this little unit is expected to find innumerable applications. A second unit, Model 3ZM-CM, designed for use as a microphone, is equipped with a special shielded transformer. Descriptive literature will be sent upon request.

GENERAL INDUSTRIES BULLETIN

A new catalog illustrating and describing phonograph mechanisms has been made available by the General Industries Co., Elyria, Ohio. Electric and spring motors as well as record changers and recording assemblies are discussed.

PORTABLE RECORDER

A new development by Webster-Chicago is a portable recording system which will cut records up to 10" in size. The cutting head and pickup are of the crystal type. Both 78 and 33⅓ r-p-m models are available. An amplifier is included as a part of the system. Write to The Webster Co., 5622-5660 Bloomingdale Ave., Chicago, for catalogs.

POWER RESISTOR DECADE BOX


A power resistor decade box that can be inserted in actual circuits to simulate working condition, is announced by Clarostat Mfg. Co., Inc., 285-7 N. 6 St., Brooklyn, N. Y. It is intended primarily for laboratory use, for calibration of meters and



for development work generally. It covers a resistance range of from 1 ohm to 999,999 ohms at a maximum of 1,000 volts, by means of six decade switches on the sloping front panel. Each decade will dissipate up to 225 watts. The maximum current per decade is as follows: No. 1, 5 amp; No. 2, 1.5 amp; No. 3, .5 amp; No. 4, .15 amp; No. 5, .05 amp; No. 6, .005 amp.

SIMPSON TUBE TESTER

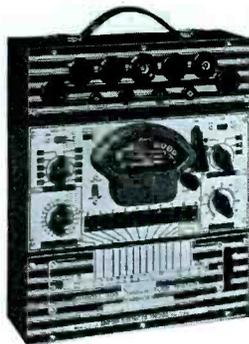The front panel of the new Simpson tube tester is divided into three sections: the socket panel, the meter with its knobs and switches, and a handy speed roll chart which shows the proper settings for each




tube. The roll chart and the socket panel are designed as separate units and can be removed in just a few minutes without disturbing the meter. This unit design means that the Model 400 can be kept up-to-date at the price of a new unit rather than a complete new tester. In addition these replacement units can be secured without returning the tester to the factory. When the new units have been received and installed the old ones can be returned for credit.

Additional information may be obtained directly from Simpson Electric Co., 5216 Kinzie St., Chicago.

*Only WARD can
give you these features*

Flex-Angle Patent Applied For

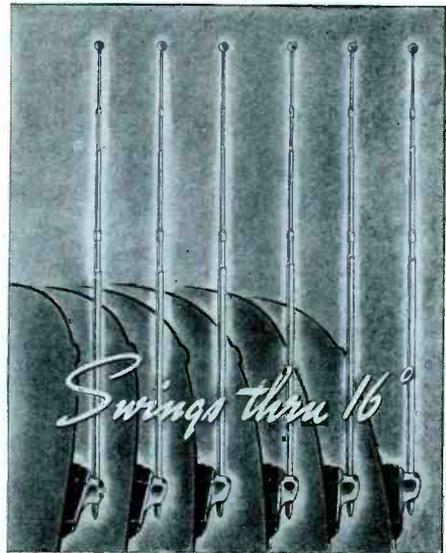


**THE AERIAL THAT FITS
ALL COWL CONTOURS
Without Conversion Parts**

● One mounting, with 16° adjustment, adapts it to Torpedo or Chrysler bodies. 3-section aerial, 68", lists at \$3.35.

CERAMIC STANCHIONS

Three section aeriels (5XXL, 66", and 8XL, 93") and four section aeriels (151L, 100") are available with Ceramic low-loss Stanchions.

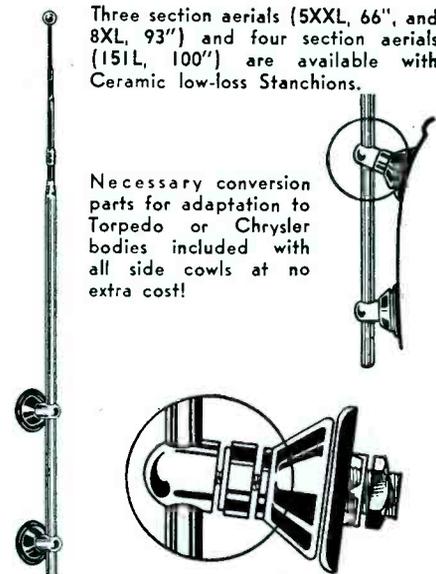Necessary conversion parts for adaptation to Torpedo or Chrysler bodies included with all side cowls at no extra cost!



SEND FOR COMPLETE CATALOG

The WARD PRODUCTS CORP.
WARD BUILDING CLEVELAND, OHIO

VELOCITY **AMPERITE** **P.G. DYNAMIC**
2 GREAT MIKES!



AMPERITE VELOCITY
 with exclusive
ACOUSTIC COMPENSATOR

Actually a combination Velocity-Dynamic, having best features of both types.

Model RBHk, hi-imp: (RBMk, 200 ohms); LIST \$42.00
 Model RBSHk, hi-imp: (RBSk, 200 ohms); LIST \$32.00



ELIPSOID PICKUP PATTERN
 Features new superior **UNI-DIRECTIONAL elipsoid pickup pattern.**
ELIMINATES FEEDBACK TROUBLE. HAS FLAT RESPONSE.



Model PGH, hi-imp: (PGL, 200 ohms); 40-10,000 CPS,..... Chrome LIST \$32.00
 Model PGAH, hi-imp: (PGAL, 200 ohms); 70-8000 CPS,..... Chrome LIST \$25.00

AMPERITE KONTAK MIKE
 Puts musical instruments across. Beautiful results with any amplifier, record player, and most radio sets.

MODEL SKH (hi-imp).....LIST \$12.00
 MODEL KKH, with hand volume control, LIST \$18.00
 Plug extraLIST \$1.50

AMPERITE WRITE FOR FREE SALES AIDS
 561 BROADWAY NEW YORK

INTERMITTENT CONDENSERS

ONE of the most perplexing and difficult problems in radio servicing is that arising from intermittent bypass and coupling condensers. Usually this condition is indicated by complete interruption of the signal, a sudden drop in volume, or intermittent oscillation.


As a rule, cutting out or oscillation due to faulty condensers occurs at infrequent intervals. Normal operation may temporarily be restored in many cases by a burst of static, an unusually loud signal, the snapping on and off of a light switch, or any sudden surge of energy through the circuit. Normal reception may follow for a considerable period, and it is in this condition the Service Man frequently finds the receiver.

The erratic and hair trigger nature of this type of condenser failure makes it particularly difficult to trace. It may occur once or twice a day, once in two or three days, or once a week. In some cases it appears when the set is first turned on, while in others several hours of operation are necessary before failure takes place. Frequently the application of test prods at various parts of the circuit is sufficient to restore normal operation. Shunting a suspected condenser with one known to be perfect fails to give a definite indication because, in many cases, the slight r-f disturbance or charging surge is sufficient to reestablish continuity in the defective unit, even though the latter may be in an entirely different portion of the circuit. In fact, the shunting operation often may be performed on several condensers with identical results.

A great deal of time may be spent locat-



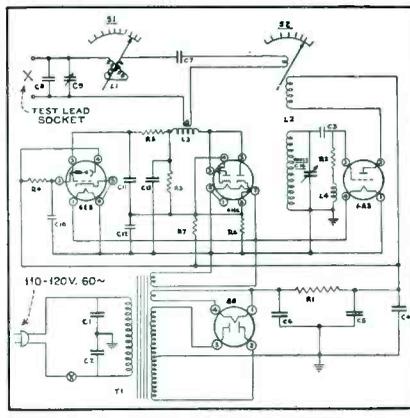This tester employs a low impedance resonant circuit which passes a r-f current up to 1 1/2 amperes, at low voltage, through the suspected condenser while it is still connected in the circuit.



ing faulty condensers by ordinary methods with results that are far from certain. If more than one condenser is intermittent, as is often the case, the problem is correspondingly difficult. The fault will not be revealed unless the intermittent occurs while the test is in progress and continues long enough to be localized. Under normal test conditions intermittents occur no more frequently than under ordinary operating conditions.

The reason for the failure of such methods to locate the faulty unit is apparent when it is considered that little has been done to accelerate or amplify the fault.

The test method to be described was designed to overcome this difficulty. By means of a low-impedance circuit, a r-f current up to 1 1/2 amperes, at low voltage, is passed through the condenser under test, while a sensitive indicator detects variations in this current. Shunt resistance has little effect unless low enough to approach the reactance of the condenser, a condition not met in the ordinary radio circuit. Therefore, condensers may be tested by this method without removal from the circuit.

Operating on this principle, the tester employs a r-f oscillator, operating at a fixed frequency, and variably coupled to a low-impedance condenser test circuit so designed that it may be tuned to resonance with the oscillator circuit. At this setting the tuning control indicates the capacity of the unit under test.

Included in the condenser test circuit is the indicating device, a 6E5 magic eye tube with its associated network, which is arranged to show resonance as well as to indicate variations of current.

For operation of the tester two controls are necessary; one of these regulates the amount of current passing through the condenser and the other tunes the condenser test circuit to resonance, indicating the capacity of the condenser under test.

Circuit

The power supply and oscillator arrangement are conventional and require no explanation. The condenser test circuit, including C7, 8, 9, L1 and the primary of L3, is variably coupled to the oscillator by a rotating coil, the position of which is controlled by S2. C14 is set and locked during calibration of the capacity indicator, S1. The variable trimming condenser, C9, is also adjusted during this operation.

The low-inductance variometer, L1, controlled by S1, tunes the test circuit to resonance according to the capacity of the condenser under test. A portion of the total current in the test circuit is carried by C8 and C9; this portion is small when Cx is large, and increases as the latter decreases.

When the test circuit is tuned to resonance and the coupling set at the normal test position, the secondary output of the current transformer, L3, rectified by the 6H6 tube, produces a voltage at the load resistor, R3, approximately three times greater than necessary to actuate the shadow angle of the 6E5 tube from 90° to 0°. However, a positive voltage is applied to the 6E5 grid from the voltage divider R6-R7 to delay actuation of the magic eye until the test circuit current reaches a value of approximately one ampere. Between this value and 1 1/2 amperes the full range of shadow deflection from 90° to 0° occurs.

Take a
Serviceman's Word
AND YOU'LL BUY
RCP Test Equipment

Model 801M

"About two months ago,"
writes G.M., Newark,
N. J., "I purchased a
combination Tube and
Set Tester Model 801M
. . . I find this instru-
ment is the answer to a
serviceman's prayer."



TWO TEST INSTRUMENTS IN ONE!

RCP Combination Model 801M is a complete, ultra-modern tube tester and comprehensive set tester. Providing the essential background for service business, it outperforms many higher priced instruments. Equipped to test new miniature tubes, all old tubes, all ballast tubes. Tests at standard R.M.A. plate voltages and loads. Noise test for tubes which otherwise test good. Complete with batteries. **\$27.95** tube and test leads ready to use.

LOW PRICE NEVER bought a better value. See your jobber at once. Or write direct for new, complete RCP Test Equipment Catalog No. 122
*Photostatic copy of letter will be forwarded on request.

RADIO CITY

PRODUCTS CO. INC.
88 PARK PLACE, N. Y. C.

THE NEW R. S. E. CONDENSER TESTER



- Quickly and Definitely Locates Intermittently Open By-Pass and Coupling Condensers.
- No waiting for Condensers to Open—Reveals Condition Immediately.
- Direct Reading of Capacity Values.
- Tests Without Removal from Circuit.
- ALL Types—Tubular, Twin, "Bathub", Block, Moulded, Metal Cartridge—All Makes of Radio—In Those Hard-To-Get-At Places.
- Turns the "Cut-Out" Job into Source of Real Profit Instead of Loss.
- Time-Tried and Proved in Regular Service Work.

Completely equipped, with four **MODEL 12-B**
tubes—1 6A3, 1 6E5, 1 6H6, and 1 80. **\$39.50**

Instructions accompany each instrument.
For use on 110-120-volt, 60-cycle only.

RADIO SERVICE ENGINEERS
110 W. Packard Ave., Fort Wayne, Ind.

MICROPHONE TRANSFORMER


Three new microphone cable transformers, just released by United Transformer Corp., are designed to be inserted in the cable circuit. The units are constructed to withstand mechanical abuse, it is said. Cable connections are made through



the spring strain relief to terminal boards inside and end caps. Standard fidelity and high fidelity line to grid models are available, as well as a crystal to line matching unit. United Transformer Corp., 150 Varick St., New York City.

DIRECTION-INDICATOR RHEOSTAT

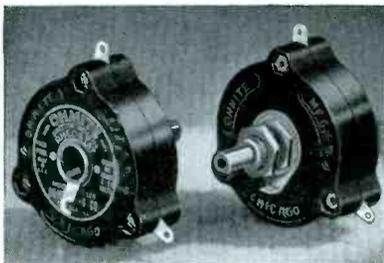
A new, Model DR-125 direction-indicator rheostat is now offered by Ohmite Manufacturing Co., 4835 Flournoy St., Chicago. This device is connected to the



moving part of radio rotary beam antennas, direction finding loop antennas, wind-vanes, etc. The Model DR-125 rheostat has a 360° continuous winding. It is designed for use on d-c up to 24 volts. It consists of a glazed ceramic housing which is 1 7/8" diameter and 13/16" deep behind panel. Mounted by a 3/8"-32 bushing and nut on any panel up to 1/4" maximum. Equipped with non-turn washer. Shaft 1/4".

SILVER MICA CAPACITORS

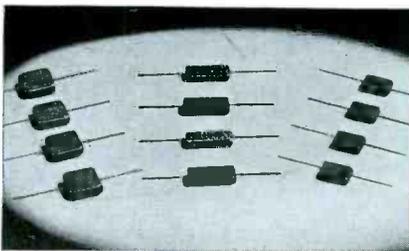Cornell-Dubilier announces an improved line of silvered mica capacitors. They find use in i-f tuned circuits, in fixed-capacitor tuned push-button circuits, in fixed-capaci-



tor tuned push-button selector, in high-frequency oscillator circuits, etc. These capacitors are available in values from .000001 to .0025 mfd with d-c voltage rating of 500; and in capacities from .003 to .005 mfd at 300-volt rating. Catalog No. 160T describing these capacitors free upon application. Cornell-Dubilier Electric Corp., South Plainfield, N. J.

Can You Answer
THESE TUBE
QUESTIONS?

1. In television what does the term "blooming" mean when applied to a picture?
2. In using 1.4 volt battery tubes why should mounting the speaker directly on the chassis be avoided?
3. What method of controlling volume replaced that of varying the screen voltage applied to the tubes?
4. What type tube would you use to change alternating current into pulsating direct current?
5. What is Ripple Voltage?
6. In a three-element tube which is generally the most important—the interelectrode capacitance between the cathode and grid, the grid and plate, or the plate and cathode?

If you aren't positive of the answers to these and thousands of other questions about radio tubes and their application, the latest edition of the Sylvania Technical Manual has all the answers in useful, handy form. 272 pages of information including operating conditions, characteristics and circuit applications on 374 types of tubes. Write to Hygrade Sylvania Corp., Dept. S70, Emporium, Pa., enclosing 35c for your copy of this great book today.

SYLVANIA


SET-TESTED RADIO TUBES

Another in the new series of
Micamold
DEVELOPMENTS

DRY

"WET" ELECTROLYTICS

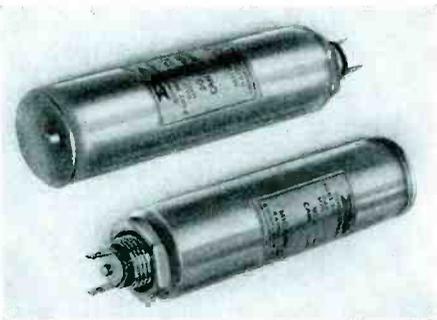are the first of this season's developments to be added to the regular MICAMOLD line of replacements. Leading radio receiver manufacturers who, incidentally, have not used wets for the past two years, agree that dry electrolytics are much more satisfactory.



- * They LOOK like "Wets"
- * They WORK like "Wets"
- * and are PRICED the same

PLUS these ADVANTAGES

- * Will NOT lose their electrical qualities when not in use
- * CANNOT FREEZE in cold weather
- * CANNOT LEAK electrolyte
- * Eliminate scintillation (sizzle when set is turned on)

SEE THEM AT YOUR JOBBER

MICAMOLD RADIO CORP.
 1087 FLUSHING AVENUE
 BROOKLYN, NEW YORK

TRIPLETT AUTOMATIC MULTIMETER
 Triplett Model 1200F volt-ohm-milliammeter provides push-button switching for



25 ranges in a-c and d-c volts, d-c milliamperes and microamperes, ohms and output voltages. The d-c voltage ranges are at 25,000-ohms-per-volt, the a-c at 1000-ohms-per-volt.


STANCOR SERVICE GUIDE

The 125B Service Guide is offered to readers of SERVICE, by the Standard Transformer Corp., 1500 N. Halsted St., Chicago, in addition to their other catalogs and bulletins. The Service Guide has 4300 listings of receivers manufactured by over 70 manufacturers and provides information on their transformer and filter choke requirements. Tube data are given in addition.

DACO RADIOMETER

The Daco Radiometer has been announced as "the master instrument" by the Dayton Acme Co., 2339 Gilbert Ave., Cincinnati, Ohio. It has been designed to provide a complete laboratory for the Service Man in one compact instrument.

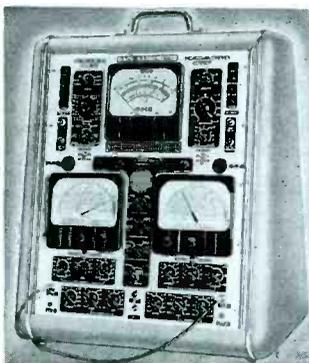The instrument includes a vacuum tube volt-ohm-milliammeter, an a-f and super-



sonic oscillator, an r-f, i-f oscillator, with frequency and video modulation, a 2-in oscilloscope and a p-m speaker.

Additional details and prices may be obtained directly from Dayton Acme.

JAMES VIBRAPOWR PATENT

The United States Patent Office has recently issued a patent, No. 2,200,064, on a vibrator and vibrator circuit, to Stephen F. James of the James Vibrapowr Co., 341 N. Crawford Ave., Chicago.


SUPREME ELECTRONIC VOLTMETER

The Supreme Model 549 electronic voltmeter has 28 ranges in five functions. Six d-c voltage ranges from 0.1 to 6,000 volts, with a minimum input impedance of 15 meg; 5 ohmmeter ranges to 1,000 meg; 5 a-c voltage ranges to 500 volts; 7 current ranges from 10 microamperes to 15 amperes d-c and 5 output ranges are provided in this single instrument.

A booklet, illustrating and describing this and other Supreme test instruments for the Service Man may be obtained directly from Supreme Instruments Corp., Greenwood, Miss.

PRONG-BASE ELECTROLYTICS

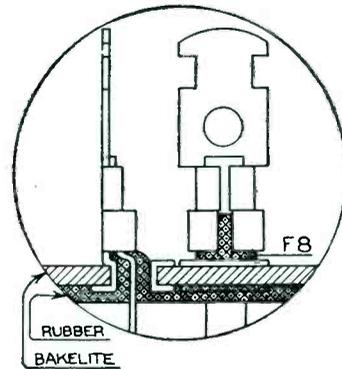Several refinements have been announced by Aerovox Corp., New Bedford, Mass., in prong base electrolytics and are made



available in their series AF units. Gains are claimed in sealing of base and prongs, reduction of corrosion and mechanical construction.

MECK BULLETIN

John Meck Industries, 1313 Randolph St., Chicago, have issued a bulletin dealing with speaker matching problems in designing public address systems. The material offered is said to present much practical data that should be in the hands of every sound technician. Copies of the bulletin may be obtained directly from Meck.

HICKOK MULTIMETER

Hickok Electrical Instrument Co., 10514 DuPont Ave., Cleveland, Ohio, have introduced their Model 133 radio set tester. The instrument features a 5-in square



meter and has a four-color scale. Some twenty odd ranges are provided for 6 functions. The d-c voltage ranges are at 25,000-ohms-per-volt. Additional data may be obtained directly from Hickok.

JUST OUT

1940-41 EDITION

RADIART VIBRATOR MANUAL

and Professional Servicemen's
AUTO RADIO GUIDE


YOUR
RADIART JOBBER
HAS THEM

THE RADIART CORP.
CLEVELAND, OHIO

RADIO CITY MULTITESTER

The RCP Model 414 (universal deluxe multitester) is now available in four additional series: V7, V9, RP7 and RP9, each with its own characteristics in addition to the multipurpose features of Model 414, it has been announced by Radio City Products Co., 88 Park Pl., New York City.

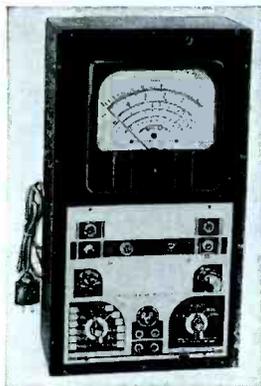Model 414 Series V7 has a large 7 $\frac{1}{4}$ "



bakelite square meter with jewel indicating light. In black crackle finish steel case. RCP Model V9 is the same, except that meter is the 9-inch jumbo round type.


Similar to V7 is Model RP7, except that here the panel is arranged horizontally for rack mounting and there is no overall case. The 414 unit (less meter) is housed in an open-faced case and may be removed from the panel for convenience while working some distance away. Model RP9 is identical to RP7 with the exception of the meter which is a 9-inch round type. Send for new catalog No. 122.

SIGNAL CATALOG

The Signal Indicator Corp., 16 Hudson St., New York, has released a new illustrated catalog, covering their complete line of signal lights, indicator units, pilot assemblies, dial lights and bull's eyes. Copies are available to the trade. Write directly to the manufacturer.

MICROPHONE CABLE TRANSFORMER

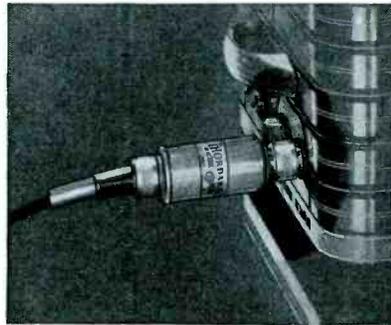The Thordarson Electric Mfg. Co., Chicago, announces a new microphone cable transformer which adds to the serviceability of amplifiers—having only high impe-



dance microphone circuits. Low impedance microphones are an advantage when the microphone is to be used long distances away from the amplifier.

The cable transformer is available in two types which are designed for voice coil connection of dynamic or velocity microphones which have self-contained line transformers.

Fully described in catalog No. 600E, available from Thordarson Electric Mfg. Co., 500 W. Huron St., Chicago.

PERMO BOOKLET

Permo Products Corp., 6415 Ravenswood Ave., Chicago, have prepared a comprehensive booklet for the layman on home recording which gives information on cutting needles, records and how to improve all kinds of recordings. This booklet also gives information on how to record different musical instruments, where to place microphones for better pick-up, pertinent information or details on how to make better recordings and general useful information for anyone using the new home recording instruments as manufactured by the various companies who have placed equipment of this type on the market recently.

PHILCO BUYS INTEREST IN NATIONAL UNION

A substantial interest in National Union Radio Corp., manufacturers of radio tubes for equipment of new sets and replacements, has been purchased by Philco Corp. as the first step in a program to expand the scope and activities of National Union Radio Corp., it was announced by S. W. Muldowny, president.

"National Union will continue as a separate company to manufacture its products and distribute them nationally under its own trade-mark, as in the past," Mr. Muldowny said in discussing the transaction.

RECORDISC CATALOG

The RecorDisc Corp., 395 Broadway, New York City, has released a catalog and price list on their new line of recording blanks. The booklet gives many hints on satisfactory home recording methods and is available to distributors, dealers and service shops upon application to the manufacturer.

Tube Tester

TRIPLET

Model 1621



Combining simplicity of operation with absolute flexibility, Triplet's new lever switching permits individual control for each tube element—yet test procedure is simple and quick. The switch setting will permit tests of 45 commonly used different type tubes without change of position of the levers. Many tubes require only two lever switch settings—more than half, only three settings. This revolutionary lever switching development with individual control for each tube element, takes care of roaming filaments, tapped filaments, plural cathode structures and dual function tubes—conclusively checks all present receiving tubes, including Miniatures, Bantam Jr., and the new Midgets. Neon shorts test and noise test jack included.

Model 1621 also features four additional "quick change" non-obsolescent features, including the above switching section. Red • DOT Lifetime Guaranteed Instrument panel may be returned for replacement or repairs, in case of accidental damage. . . . Speed Roll Chart complete with mechanism can be replaced in the case of new factory releases, by removing only four screws from front of panel. . . . New socket panel to meet future radical tube changes which present spare socket cannot accommodate will be available at nominal charge upon return of old panel. . . . Switching section with power supply also can be replaced should unanticipated changes make it necessary.

MODEL 1621 Portable Tube Tester. Dealer Net Price. . . . **\$34.84**

MODEL 1200-F

This new Automatic Volt - Ohm - Milliammeter is Push-Button Operated—with 19 AC-DC Ranges; 25,000 Ohms per Volt DC, 1000 Ohms per Volt AC. Only one button need be pressed for any range and test setting. RED • DOT Lifetime Guaranteed Instrument. Furnished in attractive metal case with rich brown suede enamel finish. Dealer Net Price. . . . **\$27.84**



Write for Catalog—Section 177, Harmon Dr.

THE TRIPLET ELECTRICAL INSTRUMENT CO.
Bluffton, Ohio

The HIT of
the Chicago Show!



XCELITE SCORES AGAIN

A practical combination of a genuine Phillips Screwdriver with an XceLite . . . all in one unit.

Yes, now you can buy this latest XceLite product with a No. 2 Phillips blade on one end and a 1/4" XceLite blade on the other at little more than you have to pay for a No. 2 Phillips Screwdriver.

But—that's not all. You can buy additional blades of other sizes which will fit this same handle. The blade not in use slips inside the handle.

BLADE COMBINATIONS

No. 1—1/2" XceLite and No. 1 Phillips
No. 2—No. 2 Phillips and 1/4" XceLite
No. 3—3/16" XceLite and 1/4" XceLite
Also supplied with stubby handle


Price With Any Blade	
Combination . . . \$1.45	Stubby . . . \$1.10
Extra handles75	Stubby65
Extra handles75	Stubby50

Packed on Individual Display Cards

Your parts jobber should carry XceLite products—otherwise write direct for complete literature and prices.

Write for catalog sheet
giving complete detail.

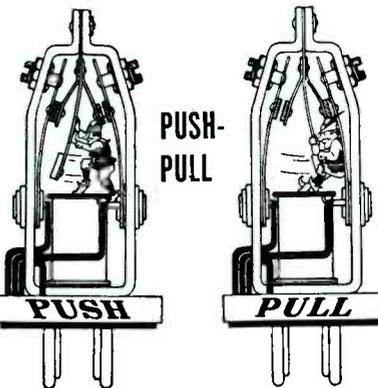PARK METALWARE CO., Inc.
Orchard Park New York



PUSH-PULL AUTO RADIO VIBRATORS

A new, revolutionary principle in vibrator design—providing higher frequency of the reed with increased amplitude—positive contact of points with wiping action—50% less R.F. interference—more stable operation and increased life span. Internal assembly accessible for servicing.

James Vibrapowr units are available in both synchronous and non-synchronous types—in a wide range of models to meet every replacement need. Packed in factory sealed cartons with terminals exposed for testing.

James Vibrapowr units list at \$2.95 for the non-synchronous types—and \$4.95 for the DeLuxe Push-Pull synchronous types. All types are guaranteed for one year.

Literature and Discounts on Request

James Vibrapowr Co., Inc.
Chicago, Illinois, U. S. A.

Index to Advertisers

	Page
A	
Aerovox Corp.	22
Amperite Co.	28
C	
Centralab	3
G	
General Industries Co., The	26
H	
Hygrade Sylvania Corp.	29
J	
James Vibrapowr Co., Inc.	32
Jensen Radio Mfg. Co.	1
K	
Ken-Rad Tube & Lamp Corp.	26
M	
Mallory & Co., P. R.	Inside Front Cover
Micamold Radio Corp.	30
N	
National Union Radio Corp.	16, 17
Neely, Norman B.	32
P	
Park Metalware Co., Inc.	32
Precision Apparatus Corp.	Inside Back Cover
R	
RCA Mfg. Co., Inc.	25, Back Cover
Radiart Corp., The	31
Radio Amateur Call Book, Inc.	32
Radio City Products Co., Inc.	29
Radio Service Engineers	29
Radio Servicemen of America, Inc.	24
Readrite Meter Works	27
Rider, John F., Publisher	4, 21
S	
Solar Mfg. Co.	26
T	
Triplett Elec. Inst. Co., The	31
U	
United Transformer Corp.	13
Utah Radio Products Co.	23
W	
Ward Products Corp., The	27
Wilcox-Gay Corp.	25
Y	
Yaxley Mfg. Division	Second Cover

DETERMINE RESISTOR VALUES FOR PADS

without resorting to extended calculations.

USE THE McPROUD PADGET

to SAVE TIME and
INSURE ACCURACY
in Attenuator Design

Supplies data for all commonly used 500-ohm pads and most unsymmetrical pads.

PADGET is an indispensable aid to every radio and electronic engineer and technician. Easier to use than a slide rule.


PRICE **\$1.25** Net

Complete with carrier envelope and instructions. Money refunded without question if not entirely satisfied.

DISTRIBUTORS,

write for quantity discounts.

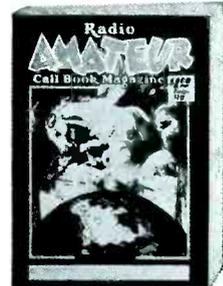NORMAN B. NEELY
1656 N. Serrano St., Los Angeles, Calif.



SERVICEMEN who are RADIO AMATEURS buy a fresh copy today of the RADIO AMATEUR CALL BOOK

The CALLBOOK is the only publication that lists all licensed radio amateurs in the United States and foreign countries.

Complete . . . Accurate . . . Up-to-Date


Issued Quarterly
MARCH . . . JUNE . . . SEPTEMBER
and DECEMBER

Annual subscription \$4.00
Single copies \$1.25

Buy your copy now from your radio jobber
or direct from:

Radio Amateur Call Book, Inc.
608 S. Dearborn St., Chicago, Ill., U. S. A.

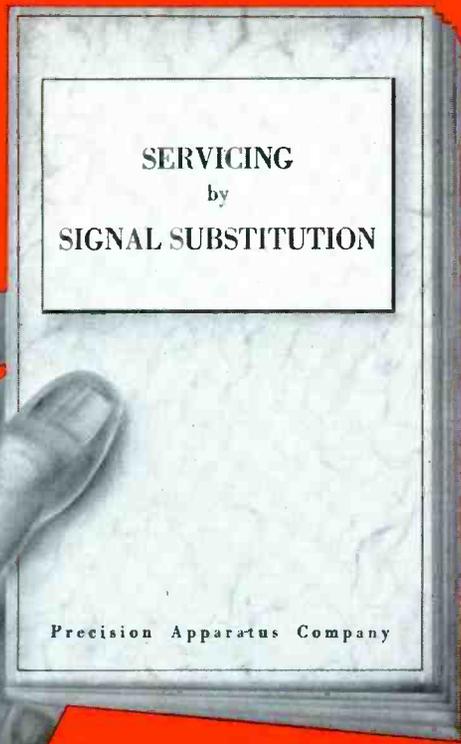HAVE YOU RECEIVED YOUR COPY of SERVICING by SIGNAL SUBSTITUTION




The NEW 120 page illustrated text describing this amazingly economical and simplified speed approach to all receiver adjustment problems

FREE This new 120 page illustrated text is now furnished absolutely FREE to all present owners and future purchasers of the Series E-200 LABORATORY SIGNAL GENERATOR. Also available at your favorite distributor or directly from the factory at only 35c.

"S-S-S" ----- Requires NO EXTRANEIOUS APPARATUS

and gives unsurpassed dollar value and service because "S-S-S" employs only basic test equipment as is normally required in the service laboratory . . . JUST 3 BASIC UNITS: — a reliable dynamic mutual conductance type tube tester such as PRECISION Series 910 . . . an accurate wide-range sensitive multi-tester such as PRECISION Series 854 . . . and the PRECISION Series E-200 Signal Generator, SPECIFICALLY DESIGNED for the purposes of "Servicing by Signal Substitution".

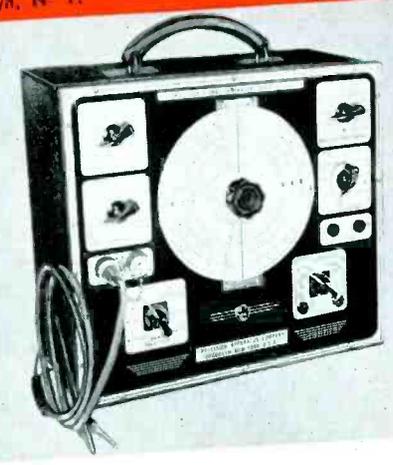★ "Servicing by Signal Substitution". Copyright, 1940, by Precision Apparatus Co., Brooklyn, N. Y.



★ Series 910

DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

The first step in "S-S-S" is the rapid, unailing selection and elimination of defective tubes. The PRECISION series of Dynamic Mutual Conductance Type Tube Testers. (Series 910, 912, 915, 920 or 922) permanently and efficiently removes the "Question Mark" from your tube test problems.

PRECISION Series 910P, (illustrated), in attractive, hardwood, walnut finished carrying case, also available in counter or standard panel mount. Dealer net price . . . \$33.95

Series 910MCP, in dull black wrinkle finished, open face metal cabinet, as illustrated for Series E-200; dealer net price . . .

\$29.95

★ Series 854

SUPER-SENSITIVE TESTER

37 Range A.C.-D.C. volt-ohm-decibel-milliammeter-ammeter . . . Including ranges to 6000 volts A.C.-D.C. 60 microamperes, 12 AMPERES AND 60 MEGOHMS.

A single Master Rotary Range Selector and the high sensitivity of 20,000 ohms per volt D.C., permits rapid check of voltage, current, resistance, etc., in troublesome stages, quickly localized through "Servicing by Signal Substitution."

PRECISION Series 854P, (illustrated) in attractive hardwood walnut finished carrying case or in standard panel mount as 854PM; dealer net price (complete with batteries and high-voltage test leads) . . . \$39.95

Series 854L, in hardwood open face, walnut finished carrying case; dealer net price (complete) . . .

\$37.95

★ Series E-200

LABORATORY SIGNAL GENERATOR

The key to "S-S-S" . . . the simplified method of dynamic receiver analysis, employing ONLY BASIC TEST EQUIPMENT.

Not only an unsurpassed, efficient, laboratory Signal Generator for purposes of alignment but also SPECIFICALLY DESIGNED as the heart of "Servicing by Signal Substitution" and priced easily within the reach of every progressive radio service engineer.

PRECISION Series E-200, (illustrated), housed in attractive dull black wrinkle finished, open face metal cabinet. Dealer net price (complete with tubes and coaxial output cable) . . .

\$35.95

Also available in standard panel mount—complete \$39.95

More than 40 models in the PRECISION 1941 LINE . . . 15 Mutual Conductance Tube Tester and Set Tester models ranging in price from as low as \$29.95 . . . 16 Multi-Range Tester models from as low as \$10.95 . . . Signal Generators from \$24.95 . . . See them at your local distributor. . . . Ask for the PRECISION TEST EQUIPMENT 1941 CATALOG.



PRECISION TEST EQUIPMENT

Standard of Accuracy



SEE THEM AT YOUR JOBBER

PRECISION APPARATUS COMPANY • 647 KENT AVENUE • BROOKLYN, NEW YORK
EXPORT DIVISION: 458 BROADWAY, NEW YORK CITY, U. S. A. Cable Address: MORHANEX

MORE ACCURATE SIGNALS BY



BIG Helps to Better Servicing!

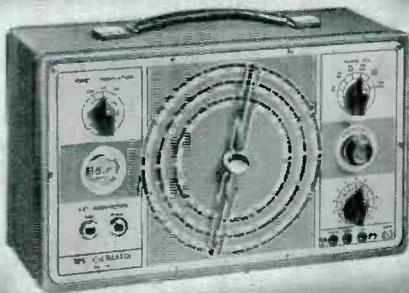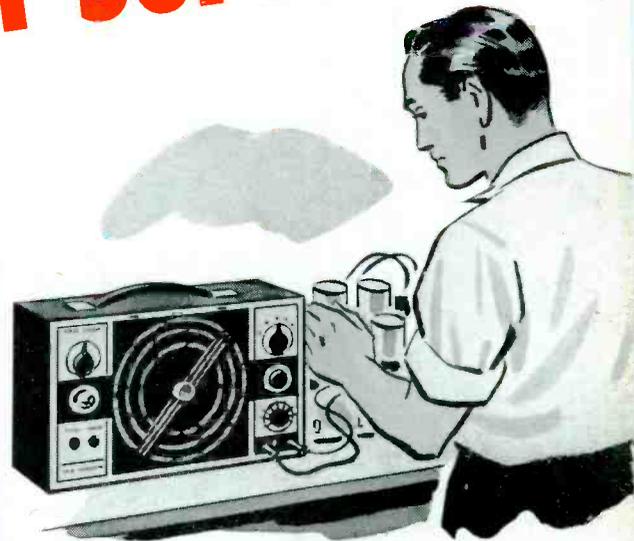


NEW RCA TEST OSCILLATOR No. 167 . . . Accurate, Easy-Reading Dial makes "right-on-the-nose" settings a cinch! Full 1.0 Volt R.F. maximum output for single-stage alignment, or for sets misaligned completely. 100-30,000 kc. in fundamentals on six bands—with sixth-band harmonics usable for U.H.F. testing. 400-cycle, 30% modulation. Only \$34.50 complete with cable.



ELECTRONIC SWEEP TEST OSCILLATOR No. 150 . . . Internal Electronic Frequency Modulator for visual oscillographic alignment . . . plus every important feature for fast servicing of all receivers. 90-32,000 kc. fundamentals, 400-cycle, 30% amplitude modulation; 120-cycle frequency modulation, with sweep adjustable from 1 to 40 kc. at any frequency. 1% accuracy. Direct-reading, illuminated dial. . . . \$64.50



NEW RCA SIGNALYST—TOMORROW'S SIGNAL GENERATOR . . . For receiver-alignment . . . for television . . . for every complex job today and tomorrow! 100 kc. to 120 mc. in fundamentals. Unique Buffer-Modulator Stage isolates the oscillator from the output—prevents frequency-changes regardless of circuit characteristics "loading" the output—one of the most important aids to precision servicing ever offered! A laboratory-type signal generator with metered output—for only \$107.50

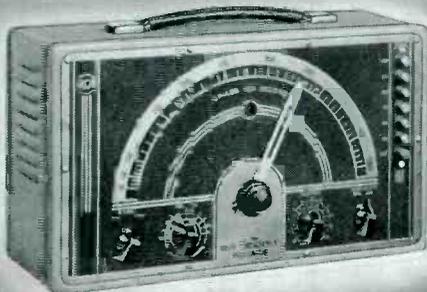

BEAT-FREQUENCY AUDIO OSCILLATOR No. 154 . . . A necessity in every shop that works with audio amplifiers, P.A. systems, loudspeakers and quality radio receivers. Variable from 30 to 15,000 cycles over the entire audible range. 3 output impedances. Ideal for audio-response curves, and for locating speaker and cabinet rattles. With 5 RCA tubes, only \$49.95

ACCURATE signals in radio servicing go a long way towards making servicing simple . . . and swift . . . and *profitable!* Here are four top-quality test instruments . . . RCA All the Way . . . at rock-bottom prices for real *quality equipment!*

It's no accident that so many of the country's top servicemen—the men who know servicing best—use only RCA Test Equipment. They know that instruments less accurate, less flexible, less reliable, are expensive at any price! And they know that RCA Equipment helps them to do their *best work* quickly . . . without guesswork!

Towards the single aim of helping you to do your job more quickly, more efficiently, more profitably, *all* of RCA's experience in set designing, building and servicing is focused on RCA Test Equipment. In any price range, you can buy nothing better . . . for any job, refuse to be satisfied with *less!* See these and other RCA instruments at your distributor's soon!

. . . .

Over 380 million RCA radio tubes have been purchased by radio users. In tubes, as in parts and test equipment, it pays to go RCA All the Way. See exhibit of all RCA Services . . . including Television . . . at RCA Building, New York World's Fair—and Golden Gate Exposition, San Francisco.



Test Equipment

RCA MANUFACTURING CO., INC.,
CAMDEN, N. J. • A SERVICE OF THE
RADIO CORPORATION OF AMERICA