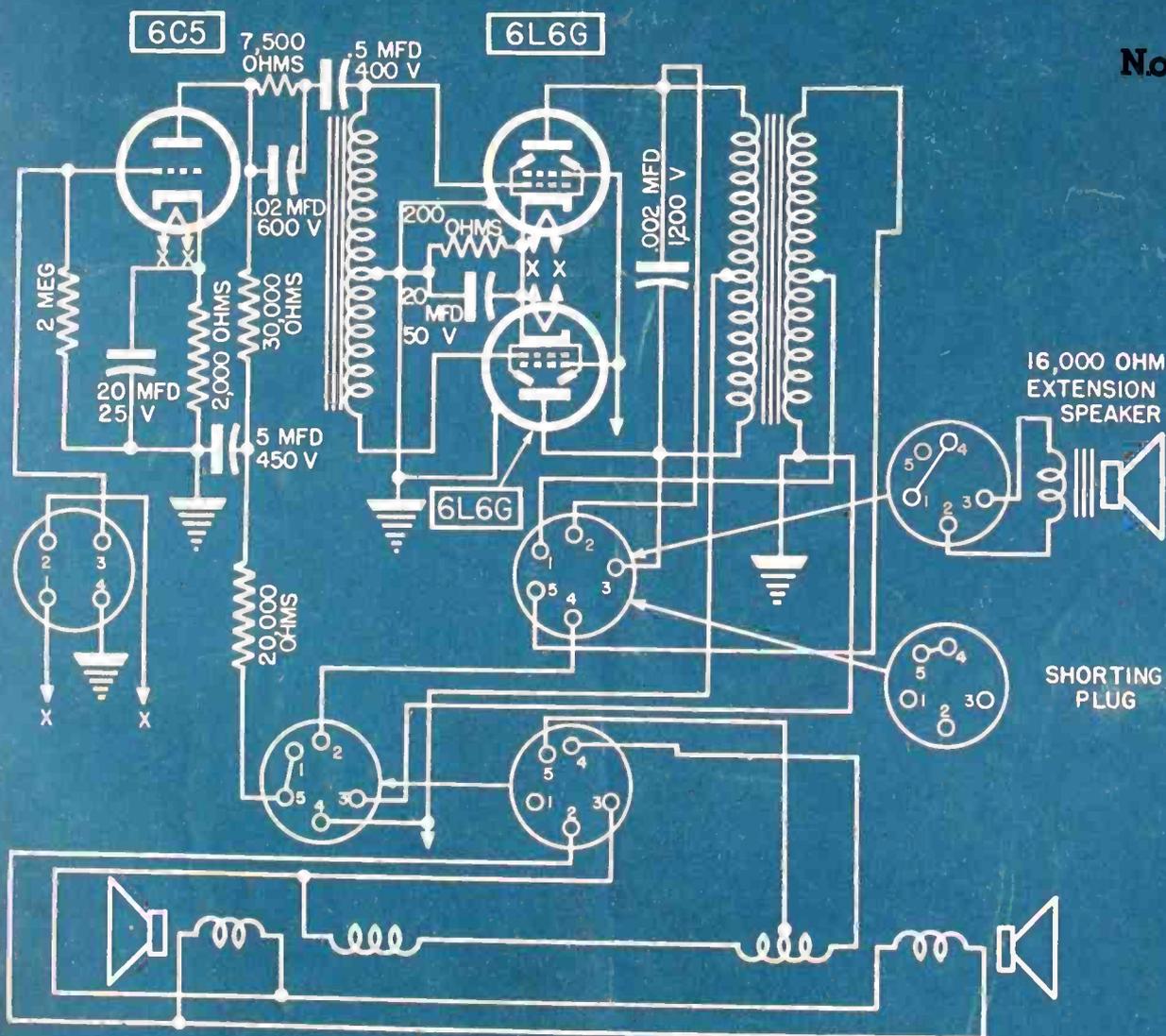


SERVICE

November
1945



High-fidelity 25-watt amplifier featuring bass-reducing control and provision for dual speaker operation. (See pages 46 and 47.)

He reads the "C-D Capacitor" and gets a chance to look around



He's not a stunt man. Just a regular radio guy like you and all the others. The reason he rides so easy is that he gets a good head start . . . keeps his nose to the ground, but has his eyes wide open. Every month he pinches a couple of minutes off his working time to read the C-D Capacitor and get the tip-off on short cuts in servicing.

Imagine! A whole month's worth of service helps that you can swallow at one sitting! Nothing for you to do . . . not a penny to send; just write us and "The Capacitor" will come to you by mail regularly. Twelve times a year we'll send you this helpful, pocket-sized magazine. Write to: "The Capacitor", Cornell-Dubilier Electric Corporation, South Plainfield, N.J.



A TIMELY POSTER FOR YOU!



An attractive blue and yellow display card for your window or wall that reads "we use no war-weary surplus". It conveys to your customers that you use only genuine and original C-D Capacitors in all service jobs. Ask your local jobber for this poster today!


HAVE YOU SEEN THIS CATALOG?



Quick, easy, condensed reference that gives you a comprehensive listing of the most complete line of capacitors made. Remember Cornell-Dubilier for all your servicing needs. Send for Catalog #195.



PRACTICAL E Z's!

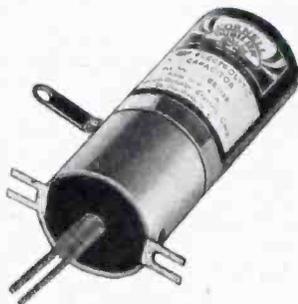

Here's one of several types of capacitors that wins the serviceman's award for "all-around replacement." Adaptable for upright or under-chassis mounting, E Z's incorporate C-D's famous etched foil features in design and construction.

CORNELL-DUBILIER
the greatest name in
CAPACITORS

KEN-RAD

Little Giant **MINIATURE TUBES**



Better than ever

● Power-packed Ken-Rad Miniature Tubes have helped to popularize the friendly companionship of portable radios . . . Now still finer tube performance is assured by Ken-Rad's association with new, large research and engineering facilities . . . The ever-growing consumer demand for Ken-Rad *quality* means increased *profits* for Ken-Rad Tube Dealers!

Write for your copy of
"Essential Characteristics"
the most complete digest of
tube information available.

174-313-8850

KEN-RAD

DIVISION OF GENERAL ELECTRIC COMPANY

OWENSBORO, KENTUCKY

THE intensive postwar expansion plans of the aircraft industry, indicating a production of around 50,000 planes for civilian travel, projects many unusual opportunities for the Service Man. For this large program will require wide-scale installation, servicing, and maintenance facilities for the planes' receivers and transmitters . . . a program that will tax the present facilities.

Servicing of this equipment will, of course, demand not only a specialized knowledge of aircraft units, but the acquiring of either of two licenses; a first-class commercial license for transmitter tests and a CAA license to permit testing of equipment, as well as installation, or any necessary plane alteration to accommodate equipment changes. While these license examinations will require schooling and hours of study, the results should prove quite profitable.

The hundreds of airports scheduled for construction will demand one or more shops on the field for radio equipment servicing. Such servicing will call for quite a profitable rate structure, commensurate with the specialized training needed for the aircraft activities. In most instances, it will be possible to arrange for a weekly maintenance and service fee, since some equipment will require checkups quite often.

Components, accessories and battery sales will also be a profitable feature of aircraft service shops. Battery sales alone will be substantial, since all planes will use battery-operated units, dry and wet. The wet-cell batteries will require charging, another medium of income.

The CAA has published a list of current airports and will soon publish a list of those airports to be constructed. You can secure such listings from the CAA department of information.

Aircraft radio servicing offers many advantages. Study its possibilities in your community now.

THE postwar f-m receivers covering the new bands are scheduled to feature an unusual tuning-dial numbering system. The first frequency (88.1 mc) will be designated as 201. The second assignment (88.3 mc) will be known as 202. This will continue up to 300. It had been planned to begin with 1 for the first channel, but the FCC said that the bands may be extended up or below the new assignments and thus provision should be made for such extensions.

This is a standard that will undoubtedly be adopted by all manufacturers to simplify f-m tuning. A wise move!

LEWIS WINNER

Editor

ALFRED A. GHIRARDI

Advisory Editor

F. WALEN

Managing Editor

Crystal-Controlled Oscillators. By J. George Stewart	13
Crystal Filters Used in Communications Receivers. By Thomas T. Donald	22
C-R Oscillographs (Applications . . . Servicing . . . Part V). By S. J. Murcek	34
Electronic Alarm Systems. By Willard Moody	24
I-F Amplifiers. By L. E. Edwards	18
Old Timer's Corner	54
Ser-Cuits. By Henry Howard	41
Servicing Helps. (Recentering Loudspeaker Cones). By Frank C. Keene	16
Superheterodyne Mixers (Part II). By Martin W. Elliott	32
Volume and Tone Control Resistors (Part IX of a Series on Receiver Components). By Alfred A. Ghirardi	26

Circuits

Air King 4034 (I-F Amplifier)	20
Allied D-366 (I-F Amplifier)	18
Detrola 571 (Postwar Model)	41
Detrola 568 (Postwar Model)	44
Garod High Fidelity Receiver	44
G.E. L-243 (I-F Amplifier)	20
G.E. 60 (I-F Amplifier)	48
Hallicrafters SX 18 (Crystal Filter)	23
Hallicrafters SX 28 (Crystal Filter)	23
Hammarlund Super-Pro (Crystal Filter)	50
Lafayette C-37 (Mixer)	32
Magnavox A-3001C (Cover)	46
Meck Industries RC-5C5 (Postwar Model)	41
National NC 100 XAB (Crystal Filter)	22
RME 41-43 (Crystal Filter)	50
Spiegel 1-40 (I-F Amplifier)	18
Ward O4WG-2672 (I-F Amplifier)	20
Ward 62-262 (Mixer)	32
Ward 62-319 (I-F Amplifier)	48
Wells-Gardner A-7 (I-F Amplifier)	48
Westinghouse WR 678 (I-F Amplifier)	18
Westinghouse M 104 (I-F Amplifier)	48

Cover

High Fidelity Amplifier (Magnavox A-3001 C)	46
---	----

Servicing Helps

Recentering Loudspeaker Cones	16
-------------------------------	----

Index to Advertisers

	64
--	----

Manufacturers

News	56
New Products	61
Jots and Flashes	64

Copyright, 1945, Bryan Davis Publishing Co., Inc.

Published monthly by Bryan Davis Publishing Co., Inc.

52 Vanderbilt Avenue, New York 17, N. Y. Telephone MUrray Hill 4-0170



Bryan S. Davis, President
Paul S. Weil, Vice Pres.-Gen. Mgr.




A. Goebel, Circulation Manager
F. Walen, Secretary

James C. Munn, 10515 Wilbur Avenue, Cleveland 6, Ohio; Telephone SWeetbriar 0052

Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif.; Telephone Michigan 1732

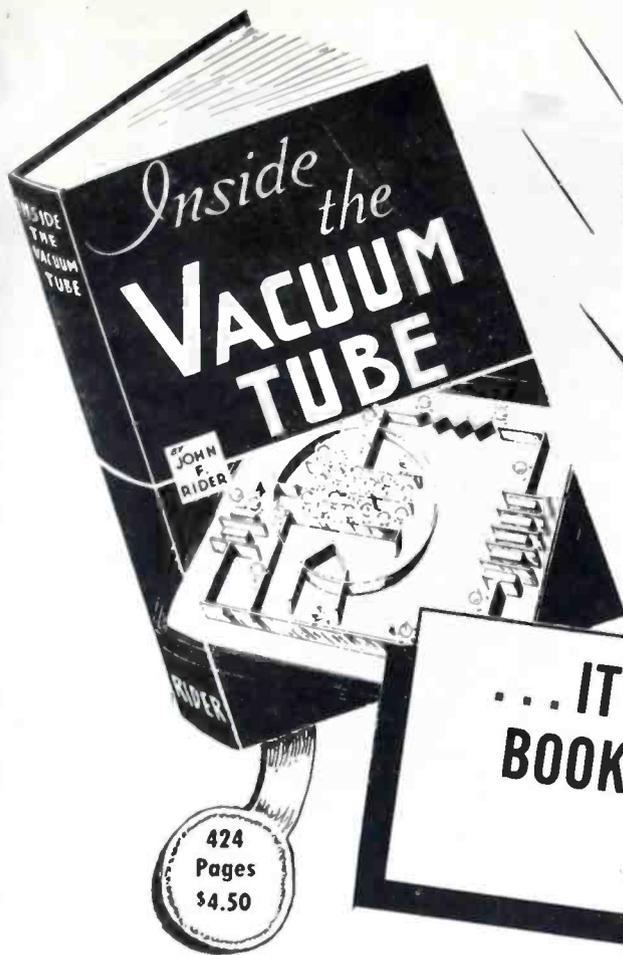Entered as second-class matter June 14, 1932, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.



IT'S EASY TO UNDERSTAND

IT'S EASY TO READ

IT'S TIMELY

IT'S NOVEL

IT'S NEW

... IT'S JUST THE KIND OF
BOOK YOU'D EXPECT FROM
RIDER

OUT IN DECEMBER

This is not just another book on the vacuum tube, but a typical Rider Book, offering a new approach to the subject—presented with a technique that makes its message clear and easy to understand. Here is a solid, elementary concept of the theory and operation of the basic types of vacuum tubes upon which can be built more advanced knowledge.

After explaining the electron theory, the text presents a discussion on electrostatic fields, on the theory that the reader's understanding of the distribution and behavior of the fields within a tube will give him a better picture of why amplification is accomplished within a tube and how the grids and plates are interrelated.

To give a clear physical picture of its subject, the book

employs novel physical devices. For example, certain diagrams and graphs are repeated, to reduce to a minimum the bother of turning pages back and forth to read text and drawings. Another innovation is the use of anaglyphs, "three-dimensional" pictures of phenomena heretofore seen only in two dimensions. Viewed through glasses supplied with the book, they are invaluable aids toward the rapid understanding of the text.

Although this is an elementary book on a fundamental subject, therefore a goldmine for the student; developments in radio and the new fields of television and microwaves make it a must for the libraries of servicemen, amateurs and engineers. Place your order today.

OTHER RIDER BOOKS

- RIDER MANUALS (14 VOLUMES)**
 Volumes XIV to VII . . . \$12.50 each volume
 Volumes VI to III . . . 9.50 each volume
 Abridged Manuals I to V
 (1 volume) \$15.00
 Automatic Record Changers and
 Recorders 7.50
 The Cathode Ray Tube at Work
 Accepted authority on subject 4.00

- Frequency Modulation
 Gives principles of FM radio \$2.00
 Servicing by Signal Tracing
 Basic Method of radio servicing 4.00
 The Meter at Work
 An elementary text on meters 2.00
 The Oscillator at Work
 How to use, test and repair 2.50
 Vacuum Tube Voltmeters
 Both theory and practice 2.50

- Automatic Frequency Control Systems
 —also automatic tuning systems . . . \$1.75
 A-C Calculation Charts.
 Two to five times as fast as slide rule . 7.50
 Hour-A-Day-with-Rider Series—
 On "Alternating Currents in Radio Receivers"
 On "Resonance & Alignment"
 On "Automatic Volume Control"
 On "D-C Voltage Distribution" . . . 1.25 each

JOHN F. RIDER PUBLISHER, INC. 404 FOURTH AVE., N. Y. 16, N. Y.


Export Division: Rocke-International Electric Corp. 13 E. 40th Street, New York Cable: ARLAB

—and Don't
Forget

RIDER MANUALS

are Now Complete
in 14 Volumes

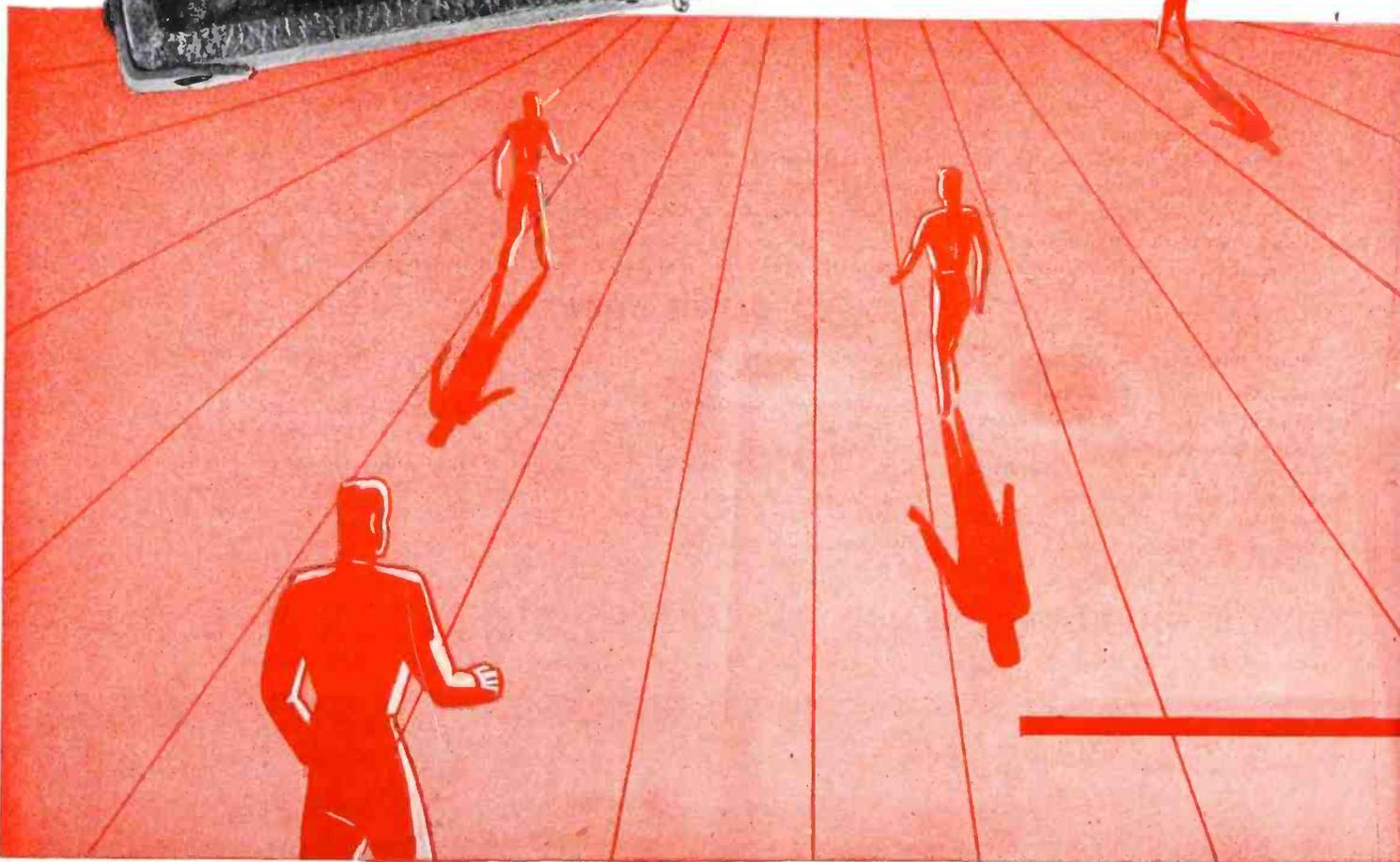They Provide Schematics and Essential Servicing Data on American Made Radio Receivers.



With this instrument a new era in tube testing begins

... Remember ...

As you read below the many other features of this pioneering instrument, remember this: It is a Simpson instrument, with all that implies in creative engineering research, in controlled testing and manufacture. Simpson products are not "assembled", they are engineered and built in the Simpson plant. Practically every component part, from the dial and movement to the beautifully designed panels and the bakelite cases and panels, is made by Simpson. It is this that makes Simpson's the "instruments that stay accurate" with ideas that stay ahead.

SIMPSON MODEL 330 MUTUAL CONDUCTANCE TUBE TESTER

1. Size—15½" x 9½" x 6½".
2. Case—Sturdy plywood construction, with heavy fabricoid covering, corners trimmed in leather, rustproof hardware—removable cover with slip type hinges.
3. Panel—Heavy molded bakelite, beautiful satin grained finish. All characters, numerals, and dial divisions are engraved and filled in white, insuring long wearing qualities.
4. Meter—4½" rectangular of modern design with artistic four-colored dial indicating good, fair, doubtful, and bad—also "Percentage of Mutual Conductance" scale.
5. Sockets provided for all types of tubes with two spare socket positions.
6. Neon glow tube incorporated to indicate shorted tubes.
7. New simplified revolutionary switching arrangement (see description above).
8. The tube chart provided is arranged for quickly identifying the tube and setting the controls.
9. Tests tubes with voltage applied automatically over the entire operating range and under conditions approximating actual operation in a radio set.

Ask Your Jobber

The New Simpson Mutual Conductance Tube Tester Brings To Radio Servicemen and Dealers An Entirely New Method of Testing Tubes And A Revolutionary New Switching Arrangement!

Tube manufacturers consider that a radio tube has reached the end of its usable life when it falls to 70% of its rated value. Until now there has never been an instrument to test tubes in percentage terms.

But now here is such an instrument. The new Simpson Model 330 tests tubes in terms of percentage of rated dynamic mutual conductance—a comparison of the tube under test against the standard rated micromho value of that tube. The colored zones on the dial coincide with the micromho rating or the percent of mutual conductance, indicating that the tube is good, fair, doubtful or definitely bad. Thus, at a glance, you can check the tube against manufacturers' ratings. If, for any reason, it becomes desirable to know the actual value in micromhos, the percentage reading may be easily converted.

This is the way tubes should be tested—the way testers always should have worked—but Simpson is first again in bringing this needed development. It tests tubes with voltage applied automatically over the entire operating range, reproducing more completely than ever before the actual conditions under which a tube functions in a radio set. No instrument, not even delicately adjusted laboratory devices, can do this 100%. But this new Simpson Mutual Conductance Tester approaches perfection as never before.

Besides this revolutionary new method, Simpson offers you an equally revolutionary switching arrangement. The circuit is so arranged that, even though there are numerous combinations possible, very few switches require moving to test any one tube. Many of the popular tubes are tested in the "normal" position without moving any of the nine tube circuit switches.

Ten push button switches and nine rotating switches of six positions each provide infinite combinations in tube element and circuit selection. Only a few settings are necessary for the most complicated tube. The tube chart provided is arranged for quickly identifying the tube and setting the controls.

When you have finished a tube test, the Automatic Reset takes over to speed and simplify the next test. Just press the reset button and instantly all switches, both push button and rotary, return to normal automatically!

Here is the test instrument you have had a right to expect from Simpson. With greater flexibility in its circuit and switching arrangement than any other tester can provide, it gives maximum provision against obsolescence. It's the tester of a new era.

SIMPSON ELECTRIC COMPANY
5216 W. KINZIE ST., CHICAGO 44, ILLINOIS

Simpson

INSTRUMENTS THAT STAY ACCURATE

SPRAGUE TRADING POST

A FREE Buy-Exchange-Sell Service for Radio Men



THE IDEAL REPLACEMENTS FOR ALL DRY ELECTROLYTIC CAPACITOR TYPES

FOR SALE—Phileo 32 v. receiver and 800 Delco 32 v. plant, with or without fairlv good batteries. Ted Hamilton, What Cheer, Iowa.

SELL OR TRADE—500 tubes. Want 0-500v d-c panel meter and other individual range types. Walter F. Kapinos, 304 Front St., Chicopee, Mass.

WANTED—Complete recording set. M. Taonouchi, 6713 A. Siskya Ave., Newell, Calif.

SELL OR TRADE—Hammarlund variable condensers and several sets of plug-in coils for Comet Pro. What have you? D. Pommiss, 401 Schenectady Ave., Brooklyn, N. Y.

WANTED—Recorder for amplifier. Describe fully. Oliver Berliner, 1007 N. Roxbury Drive, Beverly Hills, Calif.

FOR SALE—Four 4' morning glory horns; 4' flat horn for car; 4 Fox driver units with 1000 ohm fields; 1 Fox driver unit with 6 volt field; 4 Rola G-12 6 volt heavy duty field speakers; \$150 for lot. Also 6 volt 20-watt amplifier and 30-watt electric, \$50 ea.; G:E portable recorder and record player; Federal symphonic 16 complete and large supply recording disc. Loren Beatty, 2408 Queen Ave., Middletown, Ohio.

WILL TRADE—Triplet portable lab model 1181; multimeter and signal generator. Want 12" P.M. speakers or a condenser analyzer. A. T. Zintner, 3153 Agate St., Phila., 34, Pa.

SELL OR TRADE—SW-3 with coils and power pack. Want camera or record player. Walt Westman, 2310 Midlothian Drive, Altadena, Calif.

WANTED—RCA #816K chassis, less tubes and speaker. State condition and price. Kuehne Radio, Bryan, Ohio.

WILL TRADE—Ihagee revolving back camera with Carl Zeiss Tessar f4.5 lens focal plane shutter 1/15 to 1/1000 sec. filters and accessories. Want medium power transmitter or good communications receiver. John T. Craig, 611 S. Silver, Deming, New Mex.

WILL TRADE—Wells-Gardner Model 6F, 16 tube. Want ultra stratosphere "10" or other long-wave radio. H. F. Teisinger, 1256 Walker St., Waterloo, Iowa.

FOR SALE—Tubes and parts at bargain prices. Send for list. Want to rent code tape machine and tapes. Fred Humphrey, 117 N. 20th St., Philadelphia 3, Pa.

WANTED—Riders #6, 7, 8 and 10. Elliott Reames, 1149 Washington Ave., Muskegon, Mich.

FOR SALE—Triplet #1212 tube tester, complete with instructions and wiring diagram; A-1 condition \$18 postpaid. F. S. Tourillatte, 11 Lauren Park, Norwich, Conn.

SELL OR TRADE—Dumot 5" scope model #148. Want communications receiver, test equipment or camera. Ben L. Sandberg, 36 Washington Village, Asbury Park, N. J.

WANTED—Echophone model EC-1 or Hallcrafters model S-36. Joseph C. Baker, Weedsport, New York, R.F.D. #2.

FOR SALE—New tubes at list; Meissner ac-dc kits, 2-tube, \$7; 3-tube, \$8 plus 20c. postage per kit. Need test instruments. Edward Howell, Route 2, Dillon, S. Carolina.

WANTED—Multitester, signal generator, tube tester and set tester in good condition. Write, stating full description and price. Wm. H. Womack, Box 589, Mayfield, Ky.

FOR SALE—Teco tube tester T-10, almost new; Pldico auto radio and one home radio; also meters, parts, etc. Write for list. Harold Mueller, Box 323, Rugby, N. Dak.

URGENTLY NEEDED—Communications receiver with or without tubes; any condition. Will pay cash or trade broadcast receivers, radio parts and test equipment. Wm. Britton, 4 O'Brien St., Norwalk, Conn.

FOR SALE—12" beam power radio tube SC1632, \$1 ea. Lewis, Room 702, Boyce Bldg., Chicago 10, Ill.

FOR SALE—Western Electric 5" oscilloscopes with 5 BP4 white television tube. Extra heavy duty transformers, chokes, condensers, etc., complete with 12 tubes and carrying case. Tested and demonstrated, \$50. Island Instrument Co., 368 Willis Ave., Mineola, N. Y.

WANTED—Rider's Manuals, late model tube checker, signal tracer or vacuum tube voltmeter. Bill's Radio Service, 11 Halsey St., Providence 6, R. I.

FOR SALE—Green Flyer dual speed phono motor, type 3DG4, complete with turntable and speed dials, \$12. A. P. Bondgill, 509 Hancock St., Wollaston 70, Mass.

WANTED—Majestic model 60 or 160 tuning motor; Majestic 60 chassis and speaker G5. Reasonable. Will sell 4 years back Radio World Weekly. C. E. Peters, 2925 Apple St., Lincoln, Nebr.

FOR SALE—Over 2,000 tubes at O.P.A. list prices or less, many pre-war. M. E. Dominick, Chicago, Ill.

WANTED—National SW58 or Sargeant regenerative radio. Must be in good condition. J. W. King, 525 Meridian, Anderson, Ind.

FOR SALE—Two used Phileo auto radios and used Arvin 8-tube radio, \$25 ea.; also two ¼ h.p. motors, \$14 ea., and one 25 Cabbes automatic, \$15. Paul Capito, 637 W. 21st St., Erie, Pa.

SELL OR TRADE—Martin handcraft cornet and case, cost \$150. Want signal generator, multimeter and Rider's Manuals. Francis E. Manigold, Box 3003 Sta. A, El Paso, Texas.

FOR SALE—Crosley car radio, single unit, with lead-in, \$12; other radios; small assortment volume controls, resistors, P.M. and dynamic speakers; earphones; condensers; coils; power and audio transformers, and some tubes. Also 28 back issues Radio Craft; 20 of Radio News, and 13 of Radio. Hal Bundy, 119 Chlp-deva Ave., Manistique, Mich.

FOR SALE—Sensitive d-c relays, coil resistance, 8,000 ohms, contacts; single pole, double throw, rated 2 amps, at 115v a-c, \$1 ea. Mack, P. O. Box 123, New Hyde Park, N. Y.

WANTED—Rider's Manuals 1 to 14. Write, giving number, condition and price. Melvin Kelch, 1625 Natura Road, Towson 4, Md.

SELL OR TRADE—Pilot Super Wasp, also SW5, both with coils, tubes and speakers; also two short-wave radios, 3 and 4 tubes; plug-in coils in panel, built-in power supply. G. H. Gerhold, 9307 114th St., Richmond Hill, Long Island, N. Y.

WANTED—Receiver, 550 kc to 40 or 42 mc. Will pay cash. J. Kalenak, 30 Joralemon St., Brooklyn 2, N. Y.

FOR SALE—Used radios and tubes. Will buy good used radios and tube tester. Glenn E. Cruzan, Osgood, Ind.

WILL TRADE—Hockey type shoe skates, size 8, almost new. Want Ghirardi Radio Physics course. George E. Aldrich, 150 W. 98th St., Apt. 31-W, New York 25, N. Y.

FOR SALE—Superior signal generator, 100-105 mc; 955 type tubes, \$1.95 ea.; 1,000 nu 2½ meter chokes, 5c. ea.;

Isolanlite 1½" x ¼" diameter forms, threaded 2½ meter work, 5c. ea., and point stand off insulators, 2½ meter, ea. H. Arras, 277 E. 1st St., Mansfield, Ohio.

SELL OR TRADE—Radio Physics Course Radio Troubleshooters Handbook 3rd revised 1943, by A. A. Ghirardi, C. Mathematics for Electrician and Radiomen, by Cooke. Want 8" rim-drive tube table top, 1-11726, 1-3523, 1-2525, 2 tubes. William C. Stadler, 49 Mt. Ave., Brooklyn 7, N. Y.

FOR SALE—New R.C.P. #804 tube set tester, \$87. Triplet new #1213 0 tester, \$30. J. J. Lubin, 2049 McGee Ave., New York 62, N. Y.

WANTED—Transmitter plate transformer (1500, 1750 or 2000 volt); also, 200 300 m.a. swinging and smoothing chokes. Louis C. Selez, 357 S. 1st St., Ishpeming, Mich.

FOR SALE—Vacuum tube voltmeter re grid bias; AVC voltage, oscillator volt without affecting receiver operation. Re to 600v d-c in four ranges; also a-c; complete with tubes. Used, but perfect \$19.50. John S. Jackson, 166 North St. Bonita, Pasadena 4, Calif.

SELL OR TRADE—G.E. unimeter UM Readrite tube tester #432-A; and Superior signal generator #1230. John Gruniken, Jr., 1113 Hudson St., Hartsburg, Pa.

FOR SALE—Weston tube, condenser and resistance checker. Tests all tubes & Acorn. Price \$45. John H. Oxley, 1905 - 17th Ave., Vero Beach, Fla.

5 TIMES HONORED
by distinguished
service citations



YOUR OWN AD RUN FREE!

For three wartime years, the Sprague Trading Post helped radio men sell, trade or buy needed materials. Now, with the advent of Peace, this free advertising service will continue as long as the need exists.

We'll gladly run your ad free in the first available issue of one of the 5 magazines in which the Trading Post appears. All we ask is that it be written clearly and concisely, that it be confined to radio materials, and that it fit in with the spirit of this service.

As always we know we can count on you to use Sprague Condensers and Koolohm Resistors—and to ask for them by name! HARRY KALKER, Sales Manager

Dept. S-115, SPRAGUE PRODUCTS CO., North Adams, Mass.



SPRAGUE CONDENSERS KOOLOHM RESISTORS

TM. REGISTERED, U. S. PATENT OFFICE

Obviously, Sprague cannot assume any responsibility, or guarantee goods, services, etc., which might be exchanged through the above advertisement.



A background of *Performance*—over 50 years—is the *inside story* of the popularity that has brought leadership to *Thordarson* transformers. *Performance* over the years, after all, is the only true test of product quality.

Consumer acceptance will continue because *Thordarson* research and design engineers are never satisfied just keeping abreast of the times. These men are continually developing many transformer components which are instrumental in the production of new and better performing devices and equipment for the electronics industry.

This same pioneering spirit has been responsible for many new *Thordarson* transformer applications and developments during the war . . . all of which will be available shortly for civilian requirements.

Thordarson's well-tested methods of sales promotion and distribution will continue their joint task of making *Thordarson* Transformers, together with complete information on their applications and use, available to everyone in the field.


Always think of *Thordarson* for top-notch transformers!

500 WEST HURON ST., CHICAGO, ILL.



ORIGINATORS OF TRU-FIDELITY AMPLIFIERS

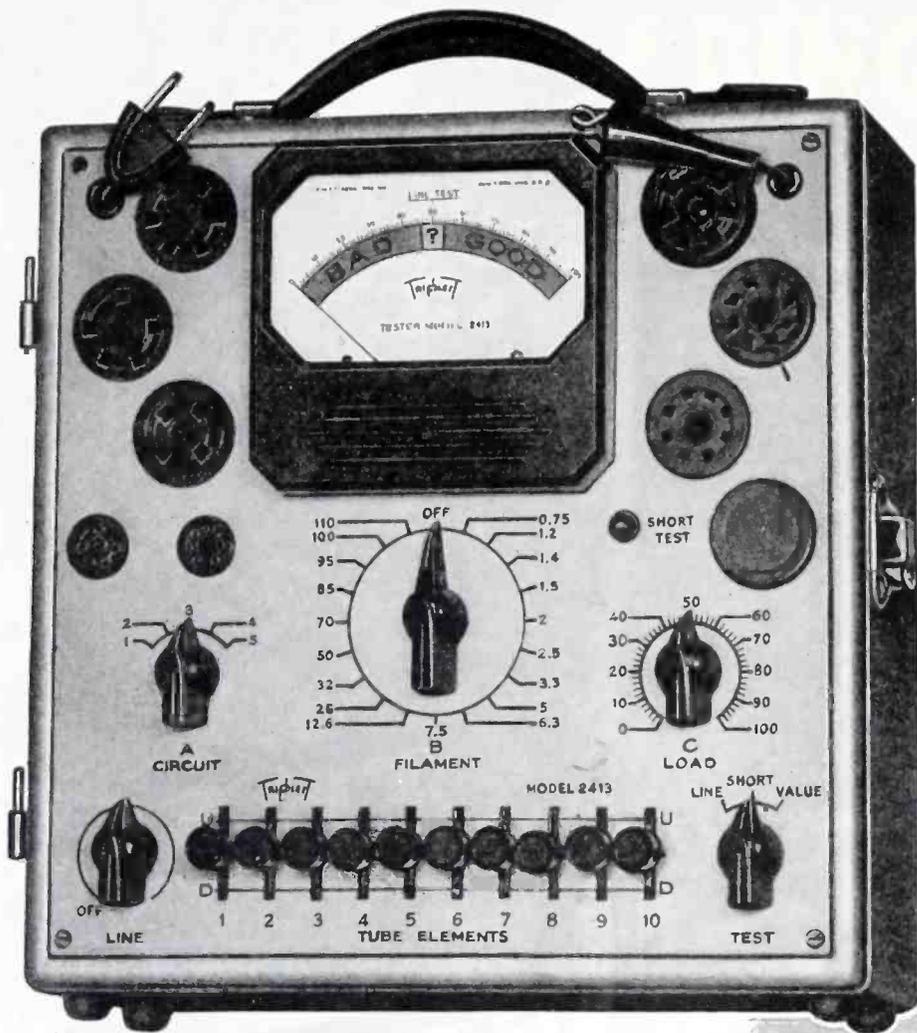THORDARSON
 ELECTRIC MANUFACTURING DIVISION
 MAGUIRE INDUSTRIES, INCORPORATED



**MODEL
2413**
 is another
 member of the
**NEW TRIPLETT
 Square Line**

The New Speed-Chek Tube Tester

MORE FLEXIBLE • FAR FASTER • MORE ACCURATE

Three-position lever switching makes this sensational new model one of the most flexible and speediest of all tube testers. Its multi-purpose test circuit provides for standardized VALUE test; SHORT AND OPEN element test and TRANSCONDUCTANCE comparison test. Large 4" square RED • DOT life-time guaranteed meter.

Simplicity of operation provides for the fastest settings ever developed for practical tube testing. Gives individual control of each tube element.

New SQUARE LINE series metal case 10" x 10" x 5 1/2", striking two-tone hammered baked-on enamel finish. Detachable cover. Tube chart 8" x 9" with the simple settings marked in large easy to read type. Attractively priced. Write for details.

Additional Features

- Authoritative tests for tube value; shorts, open elements, and transconductance (mutual conductance) comparison for matching tubes.
- Flexible lever-switching gives individual control for each tube element; provides for roaming elements, dual cathode structures, multi-purpose tubes, etc.
- Line voltage adjustment control.
- Filament Voltages, 0.75 to 110 volts, through 19 steps.
- Sockets: One only each kind required socket plus one spare.
- Distinctive appearance with 4" meter makes impressive counter tester—also suitable for portable use.



Triplet

ELECTRICAL INSTRUMENT CO. BLUFFTON, OHIO





designs of
DISTINCTION

In medieval times discriminating knights journeyed to Toledo, Spain, to obtain hand-wrought blades of steel. Only the famed guildsmen of Toledo could produce the flawless metal from which they fashioned graceful foils and swords of sleek beauty.

For hundreds of years these proud guildsmen stamped their guild marks or signatures on their creations.

A few firms today still preserve that spirit of craftsmanship. You find it in the plants of Detrola Radio. That is why the "guild mark" of Detrola Radio on a radio receiver, record changer or other electronic instrument is a guarantee of production quality. The world's finest merchants, and their customers recognize the value of this mark.

DIVISION OF INTERNATIONAL DETROLA CORPORATION  DETROIT 9, MICHIGAN



PRECISION MACHINERY plus PRECISION-EL means QUALITY in Mt. Carmel, Ill.

Precision machinery is part of Meissner's famed "precision-el" corps, too, and the men and women who build Meissner quality electronic equipment are the first to share the credit with their bench and tool-room friends. The photographs on this page show typical precision-el "teams" at work.




Here's a man who smiles proudly as his "helper"—a precision lathe—does a good job of holding extremely close tolerances.




His "partner" receives a delicate adjustment with all the skill he can command. This care of equipment by Meissner *precision-el* has meant higher quality and fewer shut-downs for repairs on a big war job.



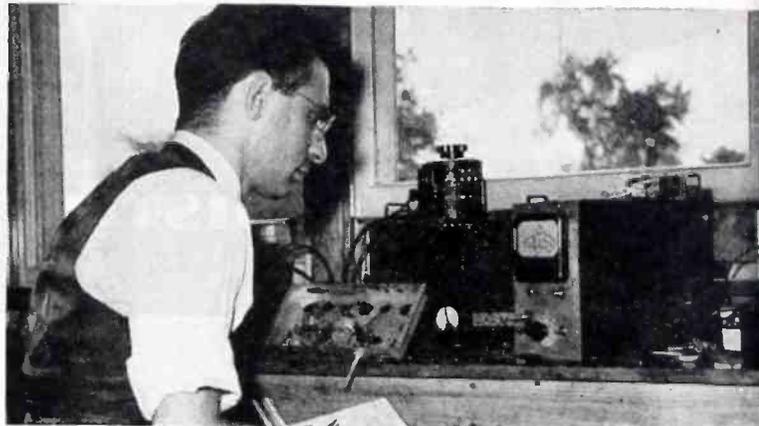Here's another winning combination. Even the smallest parts warrant careful machining at Meissner. It's another reason for precision performance by Meissner products.



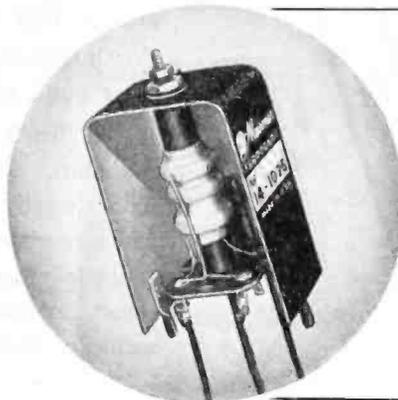This is the proof of the pudding. "Rejects" are surprisingly few, even under the sharp eye of the sensitive testing instruments used by this member of Meissner's *precision-el*.



Replace Broadcast Band Coils Easily

These Adjustable-Inductance Ferrocart (iron core) coils will replace Antenna, RF or Oscillator coils without the trouble of locating "exact duplicates" because they are continuously variable in inductance over a wide range. The inductance of the old coil is easily matched by simple screwdriver adjustment. Ferrocart iron cores add gain and selectivity to the receiver. Available shielded or unshielded, shipped with complete instructions. Order by number. 14-1026 Univ. Ant. Coil; 14-1027 Univ. R.F. Coil; 14-1028 Univ. Osc. Coil. Price \$1.50 each.




MEISSNER

MANUFACTURING COMPANY • MT. CARMEL, ILL.

ADVANCED ELECTRONIC RESEARCH AND MANUFACTURE
Export Division: 25 Warren St., New York; Cable: Simontrico

The New Model CA-11

SIGNAL TRACER

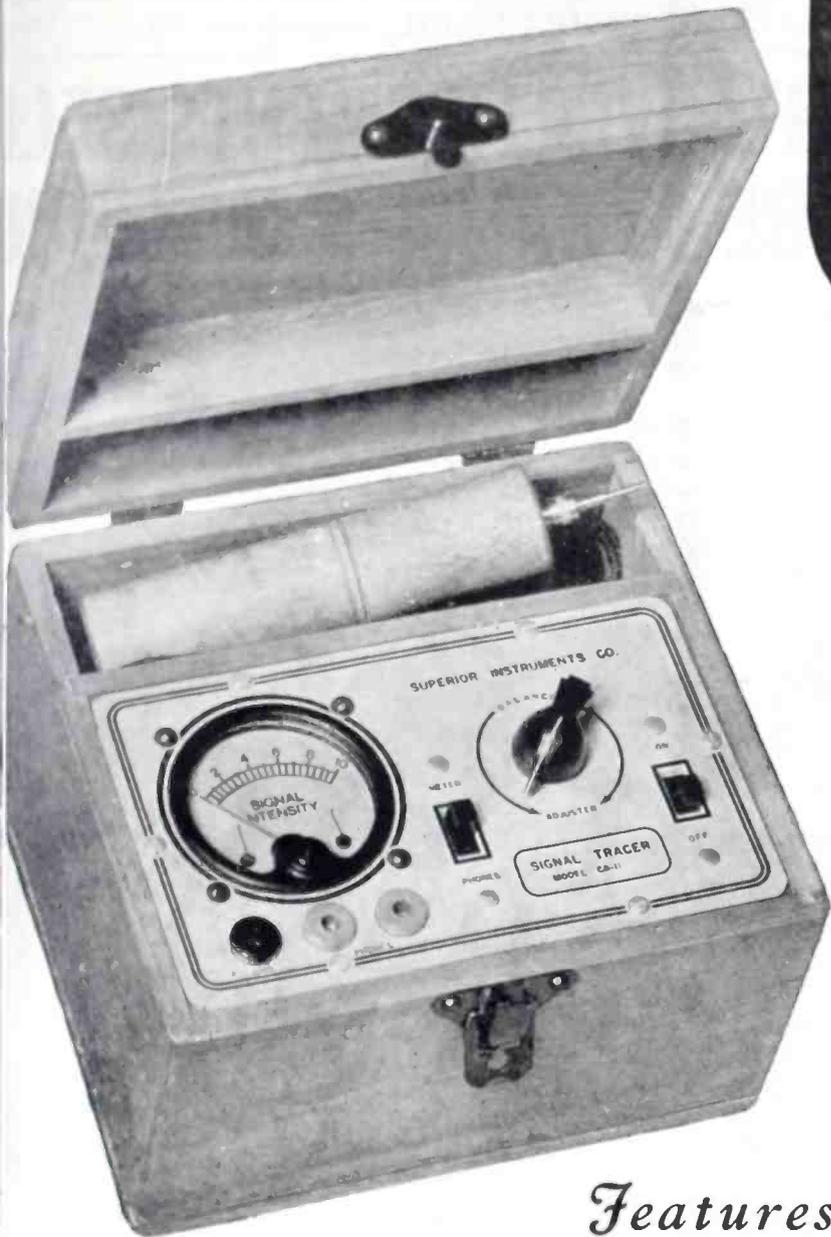

Simple to operate
... because it has only
ONE connecting cable-
NO tuning controls!

INTRODUCED in 1939-1940 Signal Tracing, the "short-cut" method of Radio Servicing quickly became established as the accepted method of localizing the cause of trouble in defective radio receivers. Most of the pre-war testers (including ours) were bulky requiring a number of connections before the unit was "set for operation" and included a tuned amplifier which had to be "retuned" to compensate for signal shift.

The new model CA-11 affords all the advantages offered by the pre-war models and only weighs 5 lbs. and measures 5"x6"x7".

Always ready for immediate use without the necessity of connecting cables, this amazingly versatile unit has **NO TUNING CONTROLS**.

Essentially "Signal Tracing" means following the signal in a radio receiver and using the signal itself as a basis of measurement and as a means of locating the cause of trouble. In the CA-11 the Detector Probe is used to follow the signal from the antenna to the speaker—with relative signal intensity readings available on the scale of the meter which is calibrated to permit constant comparison of signal intensity as the probe is moved to follow the signal through the various stages.

Features

- ★ **SIMPLE TO OPERATE**—only 1 connecting cable—**NO TUNING CONTROLS**.
- ★ **HIGHLY SENSITIVE**—uses an improved Vacuum Tube Voltmeter circuit. Tube and resistor-capacity network are built into the Detector Probe.

- ★ **COMPLETELY PORTABLE**—weighs 5 lbs. and measures 5"x6"x7".
- ★ **Comparative Signal Intensity** readings are indicated directly on the meter as the Detector Probe is moved to follow the Signal from Antenna to Speaker.
- ★ Provision is made for insertion of phones.

Please place your order with your regular radio parts jobber. If your local jobber cannot supply you kindly write for a list of jobbers in your state who do distribute our instruments or send your order directly to us.

The Model CA-11 comes housed in a beautiful hand-rubbed wooden cabinet. Complete with Probe, test leads and instructions.

\$18.75
NET PRICE



SUPERIOR INSTRUMENTS CO.
DEPT. B-227 FULTON STREET
NEW YORK 7, N. Y.

SYLVANIA NEWS

RADIO SERVICE EDITION

NOV.

Published by SYLVANIA ELECTRIC PRODUCTS INC., Emporium, Pa.

194

SYLVANIA "LOCK-IN" ADVERTISEMENTS SEL THIS SUPERIOR TUBE TO NATION'S MILLIONS

**SYLVANIA
SERVICEMAN
SERVICE**

by
FRANK FAX

A large, attractive, three-color display banner featuring the phrase "Complete Radio Service" is now ready for distribution to servicemen by Sylvania.

The banner measures 46 by 28 inches, is printed in black, green and white on special weather-proofed "duckine" material, making it suitable for use either inside or outside of the store. It has six metal grommets to provide extra reinforcement.

This useful, durable and attractive display banner may be obtained for only \$.40—or three for a dollar—from your local Sylvania distributor, or by writing to me at Sylvania Electric Products Inc., Emporium, Pa.

This banner is only one of the items on an extensive list of Sylvania promotional material designed to help servicemen merchandise both their own service and Sylvania radio tubes.

YOUR NEXT RADIO NEEDS "LOCK-IN!"

"PROVED IN RADAR!
BEST FOR YOUR SET!"

LOOK FOR LOCK-IN TUBES BEFORE YOU BUY A RADIO!
Why? Because more than any other tubes, Lock-Ins are in step with the trend in modern radio—a trend toward higher and higher frequencies.
Proved in Radar and secret radio equipment—Lock-Ins are perfect for FM and Television.
Be sure your next radio is truly up-to-date! Look for Lock-Ins!

"PERFECT FOR EVERY TYPE OF RADIO!"

"TOPS FOR FM AND TELEVISION!"

"DEFIES JARRING—STAYS PUT!"

**SYLVANIA
ELECTRIC**

Executive Office: 300 Fifth Ave., New York 10, N.Y.
Makers of Radio Tubes, Fluorescent Lamps, Fixtures, Wiring Devices, Electric Light Bulbs, Electronic Devices

Servicemen will find even more people asking about the war-famed Sylvania Lock-In Tube—because of big, full-page Lock-In advertisements appearing in eight national magazines. These ads are telling over ten million people that Lock-Ins have advantages possessed by no other radio tube.

Lock-Ins are noted for their electrical efficiency and rugged durability. Element leads are brought directly through a low-loss glass header to become sturdy

socket pins—effecting a much desired reduction in lead inductance and interelement capacitance. Support rods are stronger and thicker. There are few welded joints and no soldered joints. These remarkable tubes are designed and built to handle the high and ultrahigh frequencies of FM and Television—as well as the lower frequencies. Today, set-manufacturers are looking for the Lock-In Tube as the perfect electronic unit for all new radios.

SYLVANIA ELECTRIC

Emporium, Pa.

MAKERS OF RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES; ELECTRIC LIGHT BULBS

Fig. 1 (right) A crystal unit in its holder, with the cover removed. The two springs serve to hold the electrodes against the crystal surface. (Courtesy Crystal Research Laboratories)

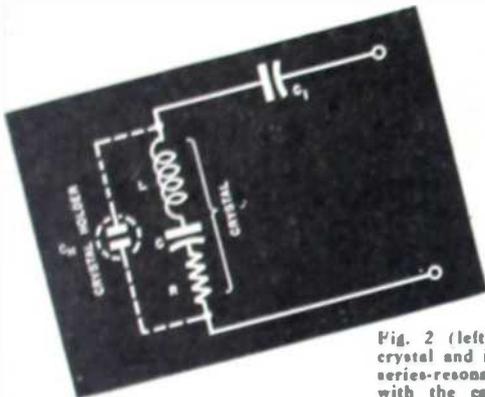


Fig. 2 (left). The electrical equivalent of the crystal and its holder. In effect, the crystal is a series-resonant circuit, consisting of L , C , and R , with the capacitance of the holder across the entire system. C_1 represents the series capacitance between the crystal proper, and the electrodes.

CRYSTAL-CONTROLLED OSCILLATORS

IN many types of postwar receivers crystal-controlled oscillators will be quite an important feature. The extensive use of these oscillators in Army-Navy equipment has developed crystal manufacture to the point where they are economically feasible for mass production. At the winter IRE meeting last January, we were shown a receiver which tuned the entire b-c band through the use of push-button crystal oscillators.

Most of the new f-m receivers will use crystal-controlled oscillators. Stability requirements in the newly assigned v-h-f band will create a need for double superheterodyning, in which one of the fixed oscillators will probably be crystal controlled.

In the past most Service Men have had little opportunity to work with crystal controlled oscillators, since their use has been restricted to transmitters and fixed frequency receivers.

Physical Properties of Crystals

Physically, the quartz crystal is less than an inch square and only several thousandths of an inch thick. This crystal is sandwiched between two small, flat squares of metal, called electrodes, which serve as surface con-

by J. GEORGE STEWART

tacts. Spring pressure is usually applied to these metal squares to hold them firmly in place, and leads are brought out from these electrodes to external pins or contacts. The entire assembly is housed in a unit called the crystal holder. This has been the practice in the past. However, cost economy factors in receiver design may change the form of crystal holder, so that a simpler device embodying the same principles may be used.

Electrical Crystal Properties

The crystal may be likened to a two-plate condenser, with the crystal acting as the dielectric, Fig. 1.

Electrically, the crystal is equivalent to a high Q , parallel resonant-tuned circuit, whose frequency is largely determined by the physical dimensions of the quartz crystal. Its electrical equivalent is shown in Fig. 2, where L , C and R are the series electrical constants of the crystal unit, and C_H represents the capacitance between the metal electrodes, with the crystal acting as the dielectric. C_1 represents the

series capacitance between the crystal proper, and the electrodes.

Crystal Operation

When an electrical current of approximately resonant frequency is applied across the crystal, sympathetic vibrations are set up in the crystal structure. This vibration, in turn, causes large voltages to appear between the electrodes. For this reason, the crystal may be used in place of an LC element in the grid circuit of an oscillator to supply the necessary grid driving voltage. Since the physical dimensions of the crystal are constant, and do not expand appreciably with heat, and since these same dimensions determine the frequency of operation, in the same way that the dimensions of a tuning fork determine its audible frequency, it can be seen that a high degree of frequency stability is thus obtained.

Grid Circuit Activity

When installed in the grid circuit of an oscillator, the value of C_H is further increased by the input capacitance of the tube, and the capacitance of the associated wiring. The resul-

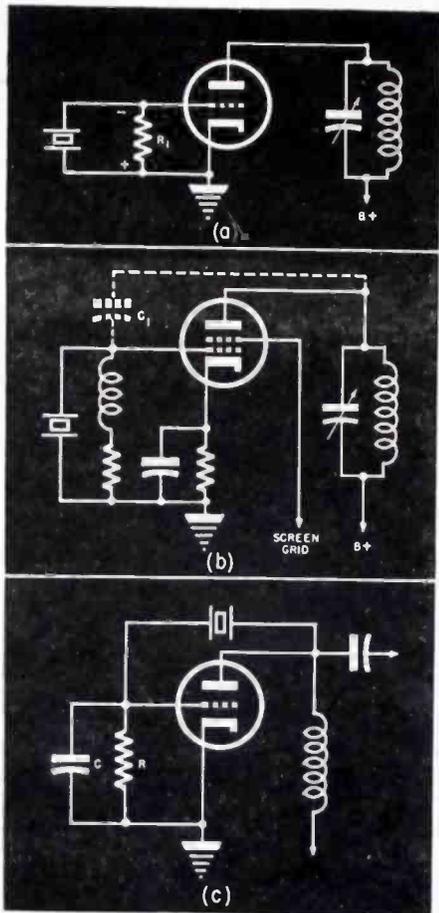


Fig. 3. Three circuits employing crystals for frequency control. In *a*, a triode circuit in its simplest form is shown. In *b*, we have a pentode circuit, while *c* shows the Pierce oscillator, which does not require a resonant circuit in the plate.

ages used, and they must be watched carefully to make sure that they are not excessive. Since power is not important in a receiver, high value grid resistors, and low grid and plate voltages may be used.

Pierce Oscillators

Fig. 3c shows a third method of crystal control for frequency stability the Pierce oscillator circuit. A triode is used, although a pentode may be used too. Here, the crystal is used as the coupling element between the plate and grid circuits. Note that the plate circuit is untuned. Its use in a crystal filter, in which only resonant voltages are passed by the crystal, the crystal performing as a series resonant circuit. For all other frequencies, the crystal acts as a pure capacitor. C_1 and the crystal may be considered as a load across the output of the tube. Therefore increasing the value of C_1 increases the load across the output circuit and the resultant grid current. Because of its position in the circuit the crystal is subject to high voltage strains. Therefore the plate voltage of Pierce oscillators is usually lower than for other crystal circuits.

must be kept below the crystal rating, else the crystal may be punctured and rendered inoperative. Expressed another way, the activity of the crystal is a function of the r-f voltage across it. If this voltage exceeds the limits of the crystal, the overactivity will shatter the crystal. Therefore, decreasing the value of the grid resistor reduces the current through the crystal. In Fig. 3a the cathode has been returned to ground, so that the grid bias is a function of the grid current which creates the bias across the grid resistor.

Pentode Circuit

In Fig. 3b a pentode has been substituted for the triode. Since the gain of a pentode is higher than that of a triode, less grid excitation is needed. The feedback from the plate to the grid has been reduced by the lower g-p capacitance inherent in the pentode structure. If this capacitance is too low, an external coupling capacitor represented by C_1 is added, so that sufficient feedback is available. The size of the grid resistor for pentode crystal oscillators is usually 20,000 ohms or less. Since the lower value of resistor may shunt the crystal too effectively, and prevent oscillation, a r-f choke is usually added in series with the resistor. The choke supplies the necessary a-c impedance to reduce the shunting effect of the resistor, at the same time introducing a negligible amount of d-c resistance. Where cathode bias is used, the size of the grid resistor is reduced.

Harmonic Oscillators

Fundamental frequency operation of crystal oscillators is limited by crystal size to about 15 mc. Crystals for frequencies above 6 or 7 mc are very expensive. To overcome this condition, the crystal may be cut to operate on a mechanical harmonic of its fundamental frequency, or may be employed in a circuit where some harmonic of the fundamental frequency of the crystal is amplified. When the crystal is operated on a mechanical harmonic of its fundamental frequency, the resonant circuit in the plate of the oscillator is tuned to the desired harmonic. The crystal then behaves as though it were oscillating fundamentally at the harmonic frequency. When the crystal is used to drive the frequency multiplier,

tant influence on the crystal frequency is quite small, and insofar as related to receivers, may be considered negligible.

Crystal Outputs

Crystal units are capable of delivering large values of r-f voltage, depending on the tube used, and the circuit voltages. However, in receiver applications, the amount of power required is small, and the circuit components reflect this in their size.

Any of several standard circuits may be employed using a crystal as the frequency-controlling element. Three typical circuits are shown in Fig. 3a, b, and c.

Triode-Crystal Oscillators

In Fig. 3a is shown a triode-crystal oscillator in its simplest form. This circuit is essentially a tuned-plate tuned-grid oscillator, with the feedback supplied by the grid-plate capacitance of the tube. Since the crystal itself is a discontinuous d-c circuit, the grid of the tube is returned to ground through the resistor R_1 . This resistor serves a second purpose, since it also limits the r-f current in the grid circuit. This grid current limitation is important, since the permissible current through the crystal

Crystal Excitation

The crystal excitation is a direct function of the plate and screen volt-

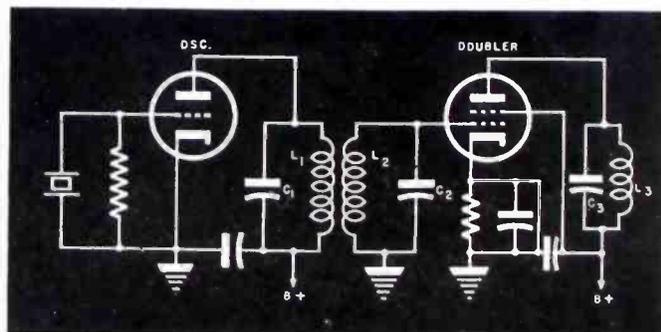


Fig. 4. A method for doubling the frequency of the crystal circuit. The first r-f transformer is tuned to the crystal frequency, while L_3C_3 is tuned to twice the crystal frequency.

he crystal first oscillates at its fundamental frequency. This fundamental frequency is then used to drive the multiplier stage. Sometimes, where the desired frequency is quite high, both methods are used concurrently.

Frequency Multiplier

Fig. 4 shows a typical crystal oscillator and frequency multiplier. In this circuit, L_1C_1 and L_2C_2 are tuned to the crystal frequency. L_2C_2 is tuned to twice the crystal frequency. Thus, the output of the doubler stage is twice the fundamental or crystal frequency.

Tri-tet Circuits

This same principle may be so used that only one tube is necessary for both operations. For example, the crystal oscillator may be one-half of a twin triode, and the doubler may be the other half. Or, a pentode may be used, as shown in Fig. 5. This circuit is known as the *tri-tet*. Here, the control grid, cathode, and screen grid perform as a triode-crystal oscillator. The screen grid serves as the plate of the triode. The plate of the tube is then used as the multiplier, with L_2C_2 tuned to the desired harmonic. This circuit is usually used where even multiples of the fundamental frequency are desired. The circuit of Fig. 6 is used where odd multiples of the fundamental frequency are desired. This circuit is known as the *grid-plate oscillator*. The essential difference between the two circuits is that in Fig. 5 the crystal is returned to ground through the resonant circuit L_1C_1 , whereas in Fig. 6 the crystal is returned to ground directly.

Resonant Circuit and Cathode Return

Actually, the circuit of Fig. 6 is a Pierce oscillator, since the screen grid, which is being used as the plate of a triode oscillator, and the crystal return, are connected together through their common ground terminals. Since the cathode of a tube may be considered as a continuation of the plate circuit, the placing of the resonant circuit in the cathode return does not change the relationship, other than placing the actual plate of the tube at -f ground.

Oscillator Tuning

All crystal oscillators are tuned in essentially the same way. Fig. 7 shows a typical plate-current characteristic

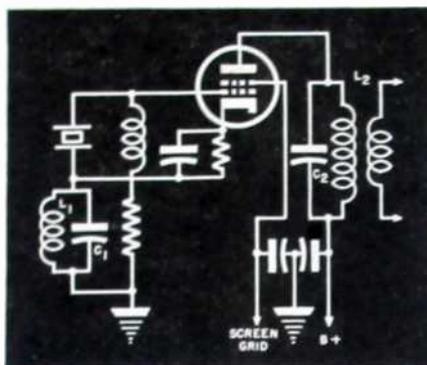


Fig. 5. A crystal frequency multiplier using one tube. L_1C_1 is tuned to the crystal frequency, while L_2C_2 is tuned to a multiple of this frequency. This circuit is used where even multiples of the crystal frequency are desired.

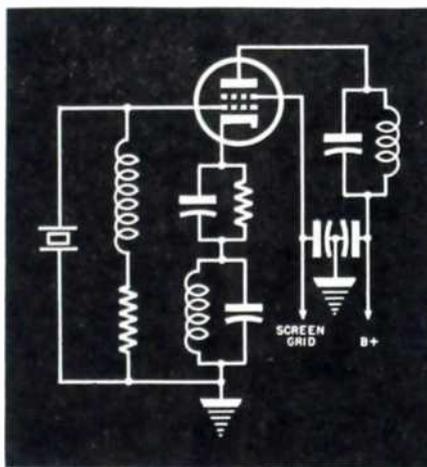


Fig. 6. This multiplier circuit is used where odd multiples of the crystal frequency are desired. The crystal portion of the circuit is essentially a Pierce oscillator, with the screen grid acting as the plate of a triode oscillator.

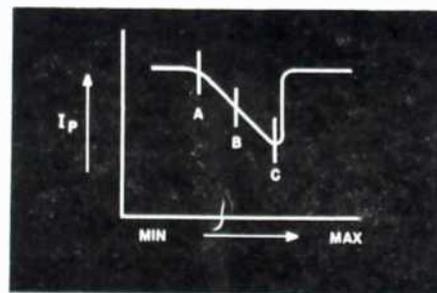


Fig. 7. Plate current characteristic of a crystal oscillator. For stability requirements, the circuit is tuned so that the current is in the vicinity of point B. This also prolongs the life of the crystal.

for a crystal oscillator. When the oscillator is in the non-oscillating stage, the plate current will be found to be at some high level. As the plate-tank tuning capacitor is tuned from minimum capacitance, the plate current will dip as shown in Fig. 7; the

current decreases slowly until it reaches some minimum value, and then rises sharply. The maximum oscillation will take place at the point of minimum plate current. However, for stability purposes, it is best to operate the crystal oscillator at some point about halfway between maximum and minimum plate current. This point of operation also limits the amount of r-f current in the crystal, and will help prolong its useful life.

Causes of Non-Oscillation

If the crystal oscillator stops oscillating, the cause may be traced to physical and electrical problems.


For instance, dirt on the crystal faces will interfere with oscillation. To clean crystals, carbon tetrachloride should be used. The faces of the crystal should be immersed in the liquid and then carefully dried on some lint-free cloth. The faces of the crystal should never be touched with the fingers, since a light film of grease is thus deposited on the crystal impairing its performance. The crystal should always be picked up by its edges, and care should be exercised not to chip the edges. The electrodes should receive similar care, since dirt or grease on their faces will produce the same effects as they would on the crystal.

Tight Coupling

If the crystal oscillator is coupled too tightly to the load, oscillations will cease. This condition will be rare in receivers, but is mentioned here in case some variable coupling method is used.

Other Sources of Trouble

Detuning of the plate tank circuit is another source of trouble. The cure is obvious. All bypasses and coupling capacitors should be checked if some unusual condition appears. For example, an open g-p coupling capacitor, or if a variable coupling capacitor is used, a low value of coupling capacitance will prevent oscillations from starting. An open screen-grid bypass, or a reduction in its value, may cause excessive excitation of the crystal. Another cause of excessive excitation is high bias. This should be checked with a v-t voltmeter in the grid circuit. For other troubles, the crystal-controlled oscillator may be treated in the same manner as any oscillator.

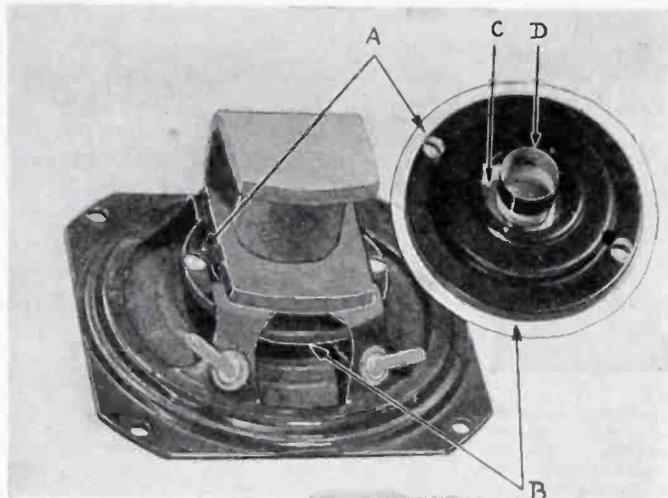

Construction of the Adjust-A-Cone assembly; the spider is kept in position with a pressure or clamping ring, which in turn is held down by two machine screws. In insert view, we have a closeup of pressure ring, which is underneath at B. At C is the spider; D shows the voice coil.

SERVICING HELPS

RECENTERING LOUDSPEAKER CONES WITH QUAM-NICHOLS ADJUST-A-CONE

THE loudspeaker is a device for the conversion of electrical energy into sound. It is composed of electrical and mechanical parts which acting in conjunction with each other make the conversion possible. Thus the electrical components control the mechanical ones, and the electrical impulses to which the loudspeaker is subjected are converted into mechanical action which creates the sound waves.

Analysis of Two Types

In this discussion we will consider only two types of loudspeakers (though there are at least three others). The most commonly used, namely, the electrodynamic and the permanent magnet type will be discussed. Both of these function exactly alike, the sole difference lying in the method employed to obtain the magnetic flux in the field in which the voice coil moves. In the former, it is created by an electromagnet and in the latter by a permanent magnet.

The electrical parts of the loudspeaker are the magnet, pot assembly, and the voice coil; while the mechanical parts are the housing and the cone or diaphragm. The voice coil assembly, known as the driver mechanism, is rigidly attached to the cone so that whatever movement is electrically caused in the driver is transmitted directly to the cone. The movement of the cone against the air in contact with it causes the radiation of air waves, or sound.¹

In order for the voice coil to func-

by FRANK C. KEENE

tion, it must be concentrically located around the end of the magnetic pole-piece of the loudspeaker with a clearance between it and the pole-piece. The clearance between the pole-piece and the pot is very close so that the air gap energy is held at a maximum. It is the action of the audio currents through the voice coil while it is in the direct-current magnetic field that causes the voice coil to move in and out.² This movement, when transmitted to the cone to which the voice coil has been rigidly attached, causes the propagation of sound waves and hence sound.³

Clearances

Clearances must be close for optimum results, but it is imperative that the voice coil ride free within the space between the pole-piece and the pot which is termed the gap. If, for instance, grit or dust gets into the gap, the efficiency and work of the voice coil is thereby impeded. Similarly, the voice coil cannot rub either against the pole-piece or against the pot and give good reproduction.

To center the voice coil within the gap, a membrane, called a spider is built

¹Terman, *Radio Engineering*, page 767.

²Terman, *Radio Engineering*, page 765.

³Olson-Massa, *Allied Acoustics*; Massa, *Electronics*, Feb. 1936; Seabert, *Electrodynamical Speaker Design Considerations*, Proc. IRE, June 1934.

into the loudspeaker assembly. This supports the voice coil at the pole-piece, while the housing (or basket, as it is termed) supports the outer edge of the cone. The spider normally permits movement of the voice coil parallel with the side of the pole-piece, but restricts all side-way movements. If the spider itself gets off center, then the voice coil is no longer concentrically located over the end of the pole-piece and a rubbing voice coil results. The same would occur if the voice coil itself were bent at its junction with the spider.

Rubbing Voice Coils

A rubbing voice coil not only causes losses in power because of the friction developed between the voice coil and the pole-piece or the pot, as the case may be, but it also introduces distortion.⁴ Such off-center operation is apparent in the reproduction in the sound by rasps and rattles and by highly distorted frequency responses. This widely divergent output response from that of a normal speaker cannot be reconciled by the human ear which, while not intolerant of small aberrations and distortions,⁵ does and can register those of this magnitude.

The result is that the user of a loudspeaker with an off-center or rubbing voice coil usually calls in the Service-Man to restore the quality which has

(Continued on page 51)

⁴Knowles, *Electronics*, Sept. 1933; Terman, *Radio Engineering*, page 774.

⁵Terman, *Radio Engineering*, page 763.

Many headlines like this
have raised the question

**RADIO RACKETEERS
ASSAILED BY COURT**

Declaring that radio repairmen were fleecing customers by charging all the traffic

Should Radio Service Dealers be *Licensed?*

RAYTHEON

HAS THE ANSWER!

and will announce it shortly . . .

Screaming headlines in the New York Times, the World Telegram, the Herald-Tribune, articles in *The Reader's Digest*—you know the unfavorable talk they have helped spread, the hardship they have worked on every *honest* radio service dealer.

DEALER LICENSES DISCUSSED

You are well aware that federal regulation, *dealer-licensing* and even finger printing, are being suggested and discussed by a lot of influential people.

What's the answer? *Raytheon will announce it shortly* for Raytheon has been working for years on a new, foolproof way to protect the public—and to help the *ethical radio service man*. A revolutionary new merchandising plan that will raise the public's opinion of the radio servicing profession and protect the reliable service dealer from outside interests.

GREAT COMPETITIVE ADVANTAGE

You can see the tremendous competitive advantage this Raytheon plan will give every dealer who can qualify! Watch for all the facts on the Raytheon program to protect the public — and help the honest service-dealer!

Raytheon Manufacturing Company

RADIO RECEIVING TUBE DIVISION

NEWTON MASSACHUSETTS · LOS ANGELES · NEW YORK
CHICAGO · ATLANTA

COPYRIGHT 1945 RAYTHEON MANUFACTURING COMPANY



RAYTHEON

Radio Tubes

DEVOTED TO RESEARCH AND THE MANUFACTURE OF TUBES FOR THE NEW ERA OF ELECTRONICS

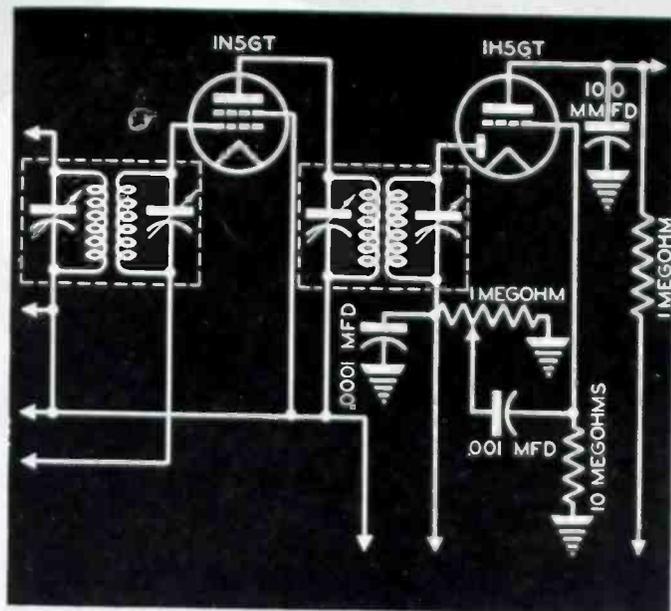


Fig. 1. The i-f system of the Westinghouse WR-678. The sensitivity of portable-receivers is about 30 μ P for an output of 50 mw. Most of this gain is supplied by the high gain i-f stage.

by L. E. EDWARDS

I - F A M P L I F I E R S

DURING the past few months we have been discussing some of the important circuit systems that constitute the modern receiver. Thus far we have covered inputs. (Martin W. Elliott's analysis of mixers appeared last month and continues in this issue on page 32.) In the i-f amplifier we have another vital element of receivers. For this section provides both sensitivity and selectivity.

High-gain remote cut-off pentodes are the most suitable amplifier tubes, allowing a wide range of avc control without detuning, and have thus been used in most i-f amplifiers.

I-F Transformers



I-f transformers may be divided into

two classes based upon their inductance; high-inductance coils of 2.0 to 2.5 mh and low-inductance coils of 1.0 mh or less. The former are tuned to 455 kc by low-capacity trimmers of 50 to 100 mmfd, giving a high L/C ratio and a high anti-resonant impedance which presents a good match to the pentode plate resistance. However, this arrangement is extremely critical to adjust to resonance and still harder to keep there because the trimmer is subject to change with temperature and age. Mechanical fatigue and warping are also annoying. Therefore, the attainable gain is not usually obtained for very long. On the other hand, low L transformers can use larger tuning capacitors, 150 mmfd and up, which are less subject to mistuning or detun-

ing because they are not so critical. Small changes in capacity cause less change in resonant frequency.

Personal receivers using only 45 or 67 volts B must use very high quality, high Q transformers of the order of 80 to 100, to obtain sufficient overall gain. Some of these types are potted, forming a closed magnetic circuit like two E laminations, or shell type which greatly reduces absorption in the shield, or even eliminates the shield in some instances.

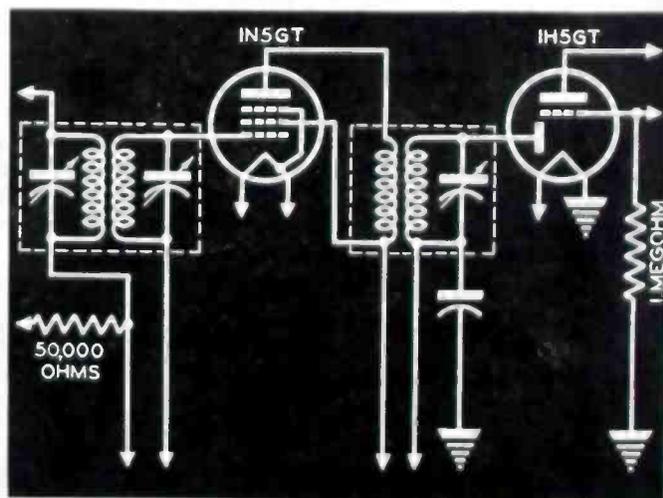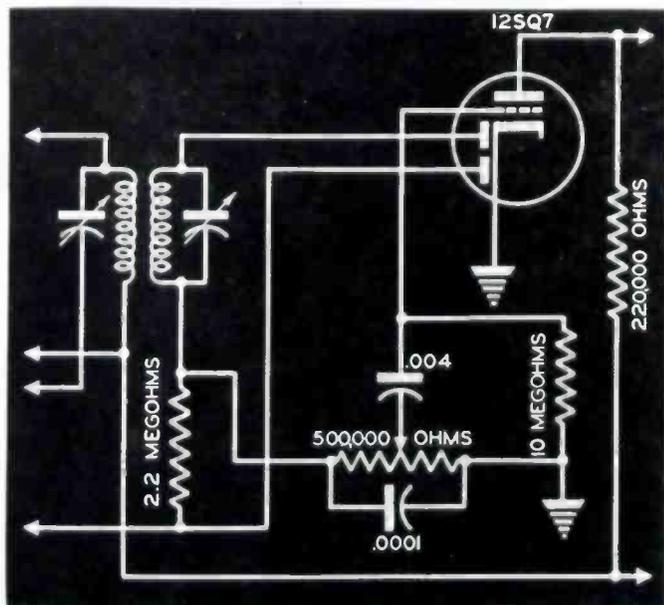I-f coils of the low-priced a-c/d-c receivers are wound with No. 37 or 38 solid copper, while the higher-priced receiver i-f's use 3 to 5 strand Litz for the input and either solid or Litz for the output, or second detector transformer. The i-f's of the very high



Figs. 2 (left) and 3 (above). Fig. 2 shows the i-f section of the Spiegel 1-40. No i-f tube is used, the gain of the single i-f transformer being enhanced by a small amount of regeneration. Fig. 3. I-f section of the Allied D-366. Primary of the second i-f transformer is untuned. The elimination of this tuned stage reduces both the gain and the selectivity of the receiver.

HOW'D YOU LIKE TO GET THESE 2 GHIRARDI BOOKS for CHRISTMAS?

What could be finer for Christmas, more appreciated or long remembered, than a gift that will help for years to come in building for a successful future in Radio-Electronic servicing? And so here's a Christmas gift tip: If you're buying a gift for a radio-inclined friend give him one or both of these helpful money-making books—or, take advantage of the combination offer and buy one for him and keep the other for yourself. Or, if a friend or relative is wondering what to get you this year, why not drop a hint that nothing would please you more than a Ghirardi book? Hand him the the coupon below!

▲ CUTS TESTING TIME **IN HALF** STOPS GUESSWORK ON SERVICE JOBS

A. A. Ghirardi's **RADIO TROUBLE-SHOOTER'S HANDBOOK** is a service "short cut" that really works. Actually, it is a definite, dependable guide for diagnosing, locating and repairing troubles in almost every receiver ever made. Tells you **WHAT** to do—**exactly HOW** to do it on over 4,800 different receiver models. Eliminates useless testing! Saves time! Helps you make more money!

When a receiver comes in for repairs, simply look up the notes on that particular make and model in the 404-page Case History section. **Nine times out of ten** you'll find **EXACTLY** the information you require. The Handbook tells you what the trouble is, how to

repair it. Ideal for training new helpers, handling tough jobs in half the usual time, repairing cheap sets rapidly—or substituting tubes and parts properly. Hundreds of additional pages are devoted to I-F alignment peaks; transformer troubles; tube substitution data; and literally dozens of charts, graphs, diagrams, data and helpful hints designed to help you do every job easier, better and a whole of a lot faster. Pays for itself in time saved the very first time you use it! Weighs 4½ lbs., contains 744 big manual-size, fully-indexed pages. Only \$5 complete—on our 5-Day Money-Back Guarantee offer.

▲ THE ONLY COMPLETE GUIDE TO MODERN Professional SERVICE WORK

A. A. Ghirardi's **MODERN RADIO SERVICING** gives you a **COMPLETE, MODERN EDUCATION** in truly professional service methods of the kind that will be your "Open Sesame!" to the big-money opportunities that only **well-trained servicemen** will be in a position to grasp. Now as never before the call is for **HIGHLY TRAINED MEN** having a broad knowledge of modern test equipment and testing techniques—**NOT** for "screw-driver" mechanics of only limited ability and technical understanding.

MODERN RADIO SERVICING is a complete servicing course from A to Z. Nothing is omitted. Nothing is condensed. You'll be amazed how easily understandable it makes subjects that other books and courses make seem highly complicated. And, even though you've been in service work for years, you'll be pleasantly surprised how this big book will serve as a "refresher" to help you handle almost every job, quicker, faster and more profitably. From beginning to end, it brings you the kind of modern, professional "Know How" that will pay you big dividends for years to come. 1300 pages; 706 clear illustrations; 720 self-test review questions. \$5 (\$5.50 foreign). Absolute 5-Day Money-Back Guarantee.



5-DAY MONEY-BACK GUARANTEE

MURRAY HILL BOOKS, Inc., Dept. S115, 232 Madison Ave., New York 16, N. Y.

Enclosed find \$..... for books checked, sent postpaid; or send C.O.D. (in U.S.A. only) for this amount plus postage. If not fully satisfied, I may return the books within 5 days and have my money refunded.

Ghirardi's **RADIO TROUBLE-SHOOTER'S HANDBOOK** \$5 Ghirardi's **MODERN RADIO SERVICING**, \$5 (\$5.50 foreign)

MONEY-SAVING COMBINATION OFFER—Both big books (Over 2040 pages of invaluable data for only \$9.50 for the two (\$10.50 foreign).)



Name
Address
City & Dist. No. State

COVERS EVERY CONCEIVABLE SERVICE SUBJECT!

Following are only a few of the subjects covered in **MODERN RADIO SERVICING**: Milliammeters, ammeters and voltmeters; Methods and instruments for measuring resistance; How, Why, When, Where to use instruments of all types; How to build your own; Tube checkers; Set analyzers; Point-to-Point testing; Test oscillators; Preliminary trouble checks; AVC and QAVC circuits; Troubleshooting; Testing components; Secure Radio Troubles; Aligning and neutralizing; Auto radios; All-ive radio servicing; Marine radio; Interference reduction; How to start a successful Radio-Electronic service business... and dozens of others.

MONEY-SAVING OFFER! We'll send you **BOTH** of the big books listed above—a total of over 2040 pages of the finest, most helpful service data on the market—for only \$9.50 (\$10.50 foreign). Use coupon.

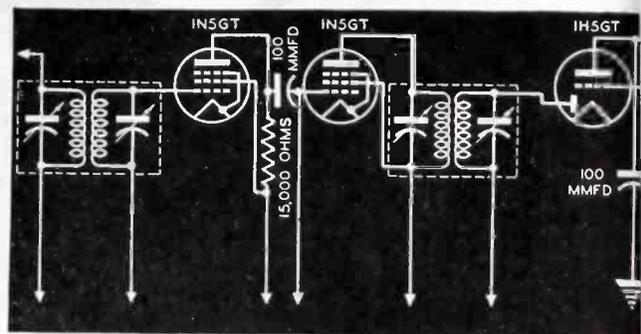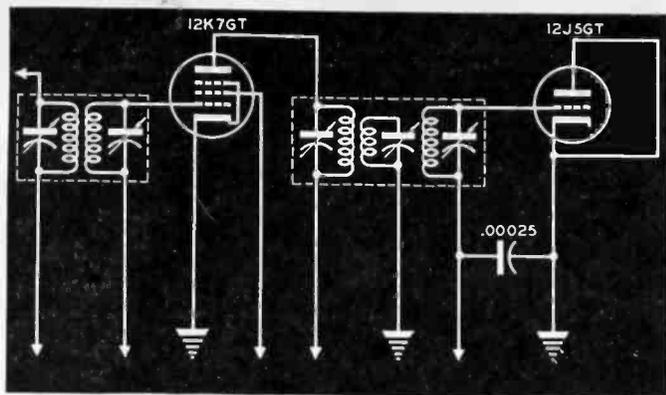The books that help you repair ANY kind of Radio equipment **EASIER—BETTER—FASTER—MORE PROFITABLY**



quality receivers have been wound with 7 to 10 strand Litz on larger coils, and often are triple-tuned or iron-cored, and encased in cans. For improved stability, the tuning capacity is often divided between a fixed silver mica capacitor and a small trimmer, any variation in the latter representing only a small part of the total.

Westinghouse WR-679

In Fig. 1 we have a conventional i-f amplifier of a portable, Westinghouse WR-679, using a 1N5GT with standard dual air-core transformers. Portables of this type have a sensitivity of about 30 microvolts from converter grid to speaker for an output of 50 milliwatts, the principal part of the gain coming from the i-f. For comparison, a typical a-c/d-c job has a sensitivity of about 180 microvolts.

The detector transformer is loaded by a 1H5 diode and its load resistance, a 1-megohm volume control. It is important that the second detector be well grounded to the chassis to prevent coupling to the loop antenna. Sometimes eddy currents are formed in the chassis which act as coupling loops. This condition is worse where the loops are poorly designed, since this prompts broad tuning because the i-f frequency

Figs. 4, (above left) and 5 (above right). In Fig. 4 appears the i-f system of the Air-King 4034. Triple tuning in the second i-f transformer provides good gain. At the same time the band-pass characteristic is improved, resulting in high fidelity reception. Fig. 5. Resistance coupling in an i-f stage in the Ward O4WG-2672. This is an inexpensive way of increasing the gain of a receiver with very few parts. The increase in gain is of the order of 12-20.

of 455 kc is quite close to the 540-kc setting at the low end of the band.

Spiegel 1-40

The i-f section of a midget 3-tube and rectifier superhet without an i-f amplifier tube is shown in Fig. 2. In this receiver, Spiegel 1-40, a 12SA7 modulator feeds a 12SQ7 second detector through the single i-f transformer. Sensitivity and selectivity are both enhanced by regeneration by returning the primary tuning capacitor to an RC-feedback element in the cathode circuit. One diode is used as detector, the other as a gate on the avc system.

Allied D-367

In Fig. 3, we have another portable receiver, Allied D-367, which contains a conventional i-f input transformer but uses a single-tuned detector transformer. This transformer is a cartwheel type, wound on a single ceramic

base, with the windings very closely coupled. This type of unit hasn't much selectivity.

Air-King 4034

In Fig. 4 appears the i-f system of the Air-King model 4034. In this system we have a triple-tuned second detector transformer which provides good gain and, at the same time, band-pass characteristics for passing a wide band for high fidelity. This may be accomplished by staggering the tuning of the three circuits so they resonate at three equally separated frequencies. The added tank circuit is grounded to prevent electrostatic coupling. The detector is a 12J5 used as a diode with 1/2-megohm load resistance. The input i-f transformer is standard.

Ward O4WG-2672

A Ward portable, model O4WG-2672, with a resistance-coupled second i-f stage, is shown in Fig. 5. This method is ideal for portables, since it provides an additional gain of 12-20 with but one extra tube, two resistors and a coupling capacitor. Its use is generally limited to applications in which selectivity is not a problem. There is a further disadvantage in the reduction of the signal/noise ratio. With the additional i-f gain in this type of receiver, the circuits are pretty hot compared to the standard single i-f circuits; hence, such items of stability as bypass capacitors must be watched carefully. Replacement units must be of good quality and adequate capacity.

The first i-f plate load consists of 15,000 ohms. Some designers have used up to 75,000 ohms. The coupling capacitor is 100 mmfd.

G. E. L-643, 653, 663, 673

In Fig. 6 (G. E. L-643, 653, 663, 673), we have an iron-core i-f input system, with a large air-core unit for the second detector, the pair providing exceptionally good i-f gain without the use of high-inductance coils. In some receivers the cores are sometimes made

(Continued on page 48)


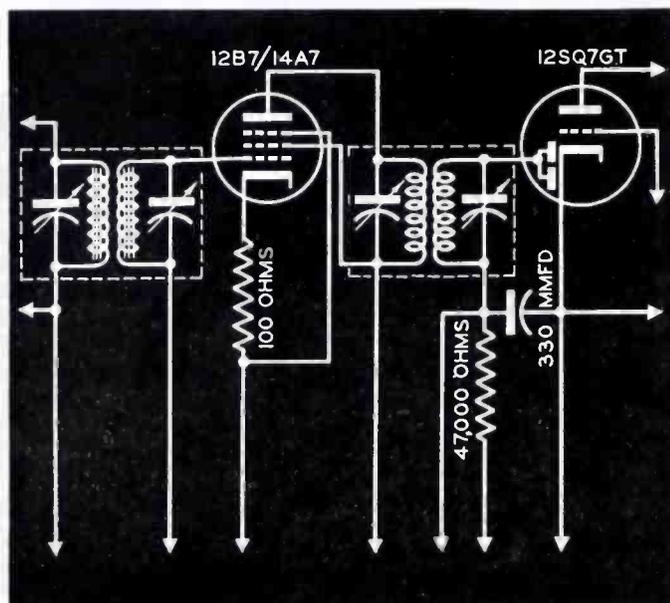


Fig. 6. The G.E. L-243 i-f system. Iron core coils are used to improve the Q of the i-f system. In some receivers, the cores are made adjustable, permitting the use of stable, fixed capacitors.

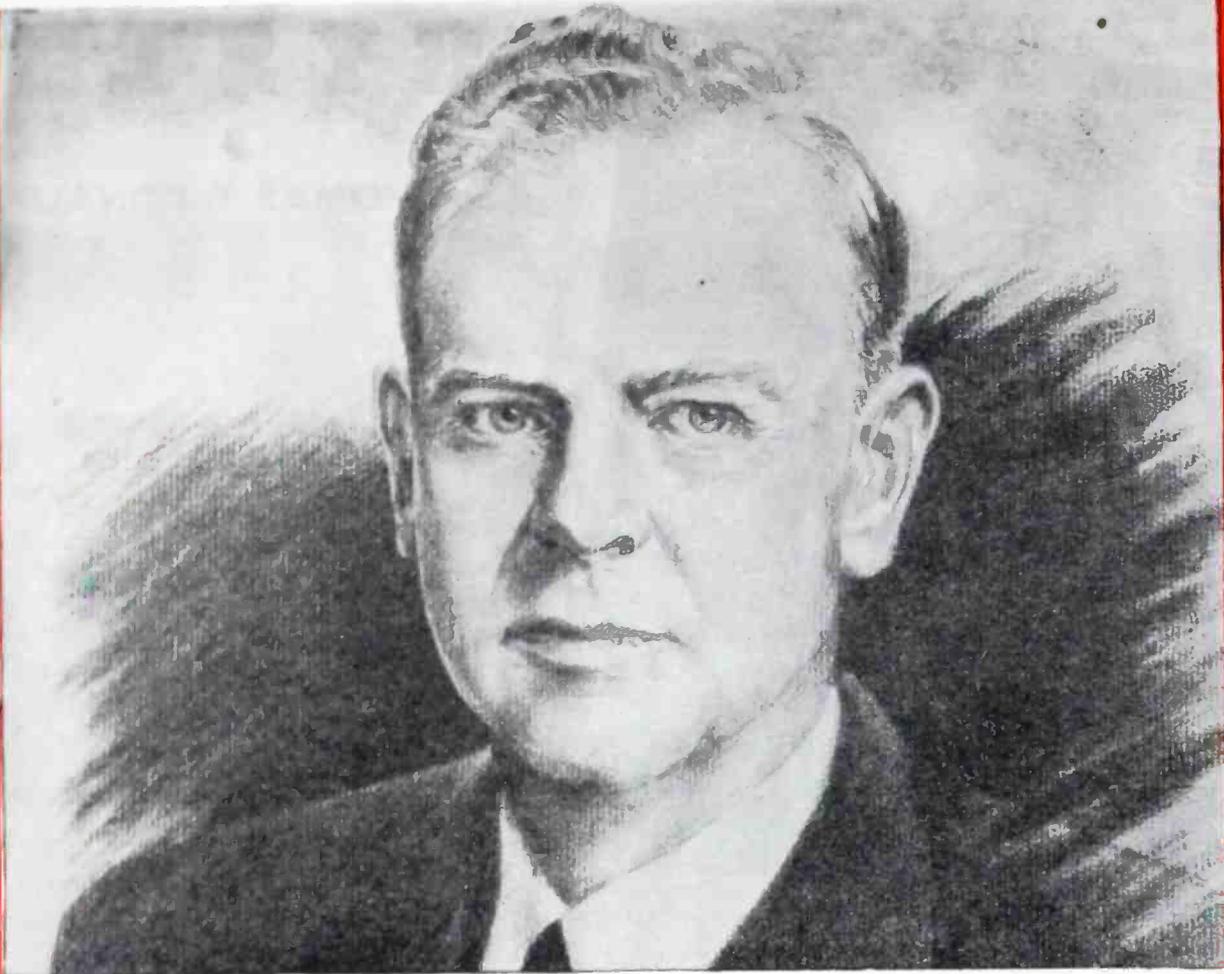

Portrait of Randolph C. Walker by John Carlton

Engineers of Victory

NOW SERVE MEN AT PEACE

The creative engineering which armed our fighting men for Victory has no less a responsibility in the years of peace ahead. Now that the war is won, we have the job of making this a better world.

AIREON produced huge quantities of communications and radar equipment and other machinery for waging war. Its achievements were equal to its heavy responsibilities, and its workers established an outstanding record of performance.

AIREON enters peacetime production with a notable engineering organization, highly skilled personnel and great confidence in the future. We have developed many products which will contribute to better living, for the manufacture of which all 15 AIREON plants will continue in production.

In order to extend our usefulness we recently established an experimental laboratory in Greenwich. AIREON's creative engineering in radio communications, electronics, musonics and hydraulics will team with production proficiency in contributing devices for future service.

In peace, as in war, AIREON will stand for quality and performance.

Randolph C. Walker
PRESIDENT



Cinaudagraph Speakers

A DIVISION OF Aireon

3911 SOUTH MICHIGAN AVENUE, CHICAGO

CRYSTAL

by THOMAS T. DONALD

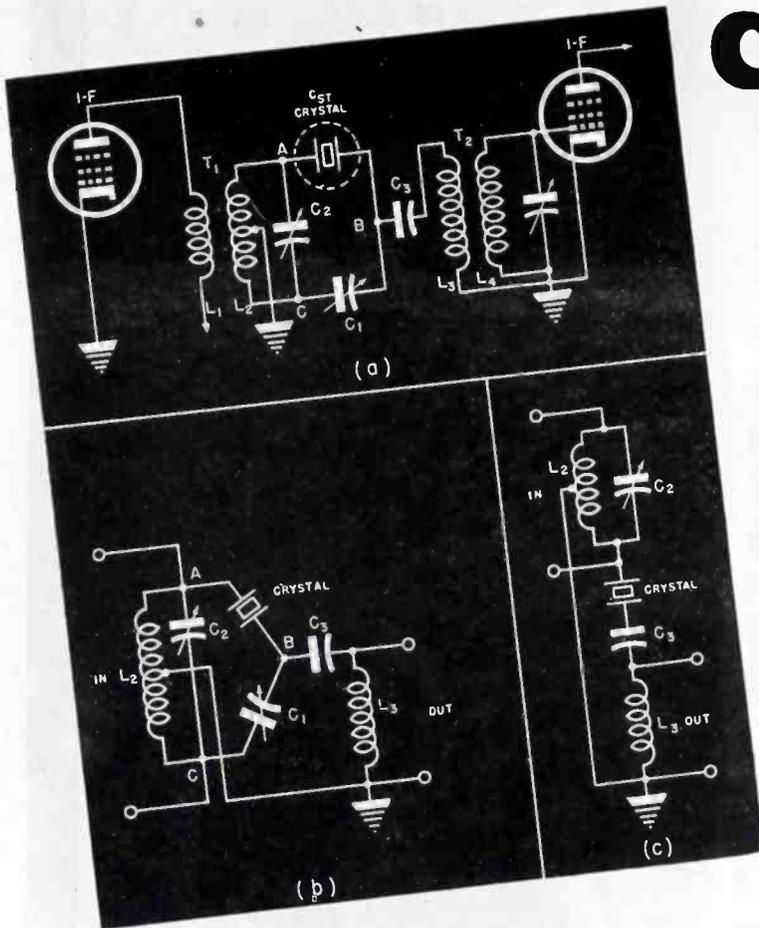


Fig. 1. A typical crystal filter i-f network. In *a*, the crystal filter circuit is shown; *b* shows its close relationship to a balanced-bridge type network; *c* shows how the series resonant characteristic of the crystal is used to provide extreme selectivity.

MANY types of communications receivers feature single-signal circuit design for c-w or code reception.

In c-w (continuous waves) we have the transmission of an r-f carrier only, with no audio modulation. The carrier is then broken up into short and long dashes, or coded. Since there is no audio modulation, the only means of detecting the signal, is through the use of a beat-frequency oscillator or b-f-o which was analyzed in last month's article. However, in the bands used for this type of communication, two adjacent signals may be no more than a few cycles apart, since the volume of air traffic is quite heavy. Therefore, the selectivity of a broadcast type receiver, and its band acceptance of ten kc required to accommodate the side band transmissions necessary for true fidelity of music and voice, would be unaccept-

able for c-w work. It therefore becomes necessary to improve the selectivity of the receiver to a point where the band acceptance is 100 cycles or less. The best method for accomplishing this is through the use of a crystal filter. In addition, a narrow band acceptance helps to reduce static as well as other types of interference. Many Service Men may have noted that when European pickups are retransmitted in this country c-w signals are heard in the background. With a sharp crystal filter, it is possible to receive the code signal, and almost completely obliterate the broadcast signal.

Crystal Filter Positions

Crystal filters are usually installed between the first detector of a superheterodyne receiver, and the following i-f stage, or between i-f stages. A typical crystal filter i-f network is shown in Fig. 1a. It is redrawn in

Fig. 1b to show its close relationship to a bridge type, or balanced network. In this figure C_1 is the phasing control. If the crystal could be installed in the circuit without the accompanying capacitance introduced by the crystal holder and associated wiring, C_1 as well as the balanced type circuit, would be unnecessary. However, due to the introduction of this stray capacitance, represented by C_{ST} in Fig. 1a, it is necessary to balance out its effect. This is accomplished with C_1 , the phasing control. If this were not done, the circuit enclosed by the dotted line in Fig. 1a, would act as a coupling capacitor, with the crystal assuming the role of a dielectric, serving to link T_1 and T_2 , and permitting the passage of all r-f signals present in T_1 . However, when C_1 is adjusted so that it is equal in value to C_{ST} , any non-crystal-resonant voltage developed between points *A* and *B*, is cancelled out by a like voltage between points *C* and *B*. A study of Fig. 2b shows how the balanced-type circuit accomplishes this. For crystal resonant voltages, the crystal acts as a series resonant circuit, thereby providing a coupling path between T_1 and T_2 .

Phasing Controls

The phasing control, C_1 , also performs another function. Since it is a

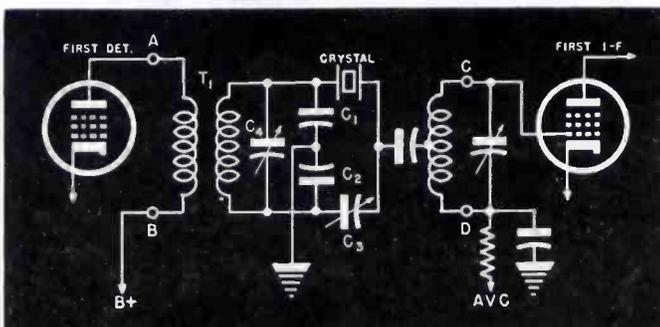


Fig. 2. The crystal filter network of the National NC 100 XAB. C_1 and C_2 split the secondary of the first i-f transformer capacitively. C_3 is the phasing control. This is a plug-in type stage, *A*, *B*, *C*, and *D* representing the four prongs of the plug.

FILTERS USED IN COMMUNICATIONS RECEIVERS

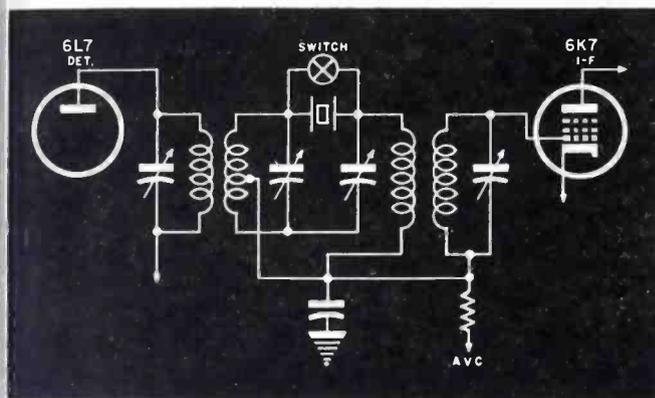


Fig. 3 (above). Crystal filter of the Hallicrafters SX 18. Here, the transformer is split inductively. A panel switch is provided to cut out the crystal for voice reception.

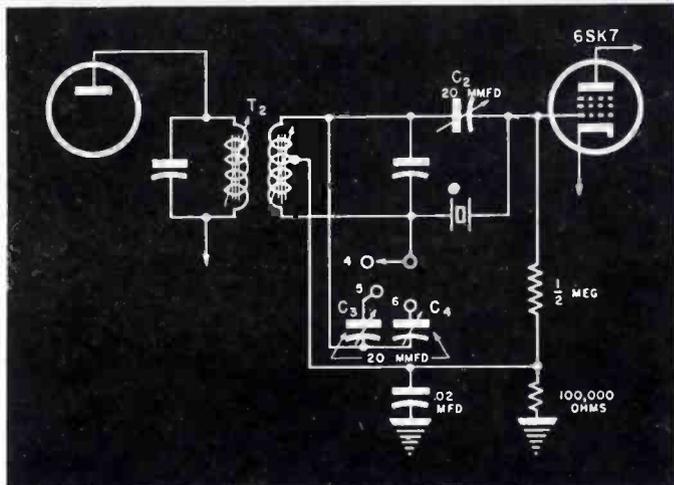


Fig. 4. The variable-selectivity system used in the Hallicrafters SX 28. Capacitors C_3 and C_4 detune the secondary of T_2 , thereby increasing the effectiveness of the crystal and improving the selectivity of the system.

ancelling agent, any partial cancellation of the distributed capacity in the crystal circuit would tend to decrease its selectivity. Therefore, the phasing control may also be used to control the selectivity of the crystal filter.

Selectivity Control

The adjustment of C_2 , which tunes T_1 , may also be used as a selectivity control. When C_2L_2 is tuned to the resonant frequency of the crystal, it places a high resistance in series with the crystal, since, at resonance, a parallel tuned circuit offers the greatest impedance, or resistance. (The circuit is shown in Fig. 1c.) Therefore the effectiveness of the crystal Q is reduced, since it only represents a small portion of the entire resistive network represented by L_2C_2 , the crystal, C_3 , and L_3 . However, if L_2C_2 is detuned, the resistance of this portion of the network is reduced to the reactance of either L_2 or C_2 , whichever is smaller, and the effectiveness of the crystal is increased. Thus, the selectivity of the circuit is increased.

Basic Designs

The three points previously discussed are important since they are not only the basis of most of the crystal-filter network communications

receiver designs, but a major factor in servicing and alignment.

National NC 100 XAB

Figs. 2 to 6 show the crystal-filter networks used in typical communications receivers.

Fig. 2 is the crystal-filter circuit of the National NC 100 XAB. C_1 and C_2 are used to split the secondary of T_1 to obtain a balanced circuit. C_3 and C_4 are the phasing and selectivity controls, respectively. This particular model is so arranged that a standard i-f transformer of the plug-in type may be used instead of the crystal-filter unit, which is also a plug-in type. The plug-in points are represented by A , B , C , and D . The selectivity of the crystal unit is preset, before insertion.

Hallicrafters SX 18

Fig. 3 shows the crystal system used in the Hallicrafters SX 18. Here, the primary of the first i-f transformer is tuned, and its secondary split inductively. A panel switch is provided to cut out the crystal when the set is used for b-c reception. Note the similarity of this circuit to Fig. 1a.

Variable Selectivity Filters

The circuits shown previously have been simple versions of crystal filters. More expensive types of communications receivers feature a variable selec-

tivity i-f system, with and without crystal filters.

All variable selectivity crystal-filter systems revolve around some method of decreasing the Q , or band acceptance, of the crystal. This is necessary, since it permits easier tuning of c-w signals when noise conditions are not restrictive. It can be appreciated that when dialing for a signal with an i-f channel that is only 100-cycles wide, the slightest movement of the dial would pass over the signal. Figures 4 to 6 show three such systems.

Hallicrafters SX 28

Fig. 4 shows the variable selectivity system used in the Hallicrafters SX 28. Three positions, 4, 5 and 6, are provided for crystal *broad*, *medium*, and *sharp*. In position 4, T_2 is tuned accurately to the crystal frequency. This causes broad-band acceptance, as explained in Figure 1c. Position 5 adds trimmer C_3 , which detunes T_2 slightly, thereby increasing the effectiveness of the crystal filter. Position 6 further

(Continued on page 50)

ELECTRONIC ALARM SYSTEMS

SYSTEMS

by WILLARD MOODY

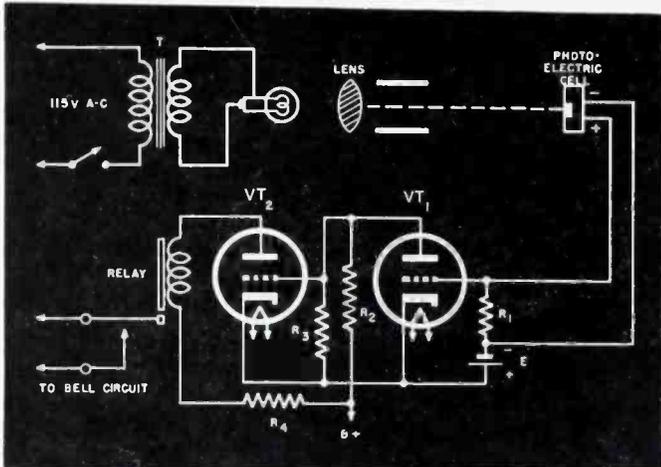


Fig. 1. An elementary photoelectric alarm system. Interruption of the light source reduces the voltage across R_1 , which is bucking the bias voltage. This reduces the plate current, and thereby actuates the bell system.

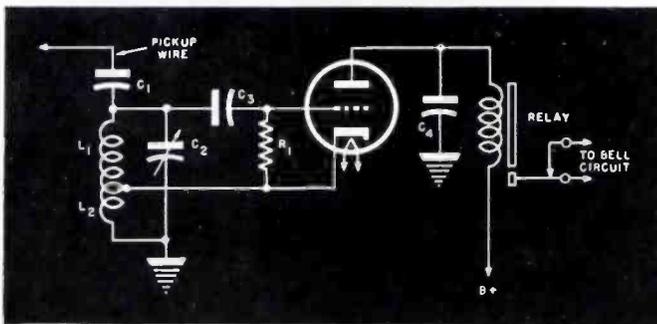


Fig. 2. A circuit typical of r-f types of alarm systems. Variation in the capacity across the grid circuit of the oscillator causes a decrease in plate current, which in turn closes or opens a relay.

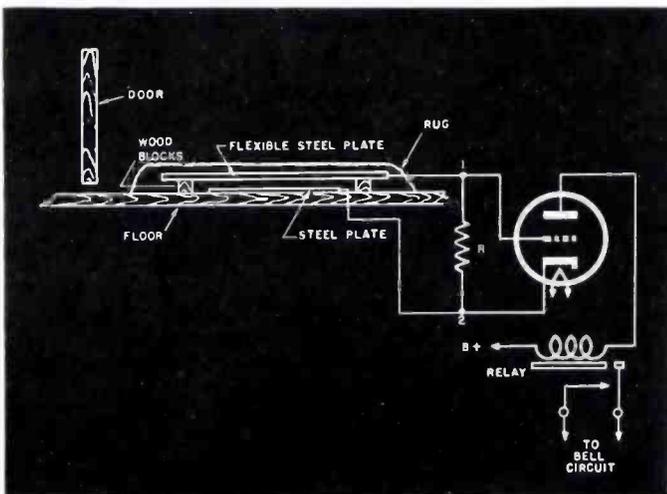


Fig. 3. A step-operated type of alarm system. Resistor R is usually of the order of 10 to 15 megohms. Shorting of the flexible steel plates by stepping on them shorts out the grid resistor, causes the plate current to rise, and actuates the relay.

ELECTRONIC circuit developments have introduced many unusual tube applications, such as the electronic alarm. During the war electronic alarms were used in a variety of installations. The postwar era will see an extensive use of these alarms in industry and the home.

Types of Alarm Systems

There are several types of electronic alarm systems. In Fig. 1 we have one where light from an auto type bulb is directed through a lens and barrel-like tube to a photoelectric cell which may be four or five feet away. In some cases a filter is used in front of the barrel for passing invisible infrared rays only. In other cases, ordinary white light is used. In operation, the light strikes the photocell which develops a potential across the cell terminals. This voltage is applied to the grid of the first tube and is bucked out by a bias voltage. When light no longer strikes the cell, the voltage is zero and the grid bias potential causes a decrease in the plate current, since the bias is more negative.


Relay Activity

The interruption of the light beam thus actuates the alarm system. That is, the drop in plate current, with an increased negative grid potential, causes less current flow in R_2 and a decreased voltage drop across R_2 . Then, the increased positive potential on the grid of the second tube causes a rise in plate current and the relay closes. A latching or lock-in arrangement may be used on the relay, so that

(Continued on page 38)

IT'S A HUNDRED TO ONE YOU'LL FIND THE RIGHT CONTROL



In IRC'S New CENTURY LINE

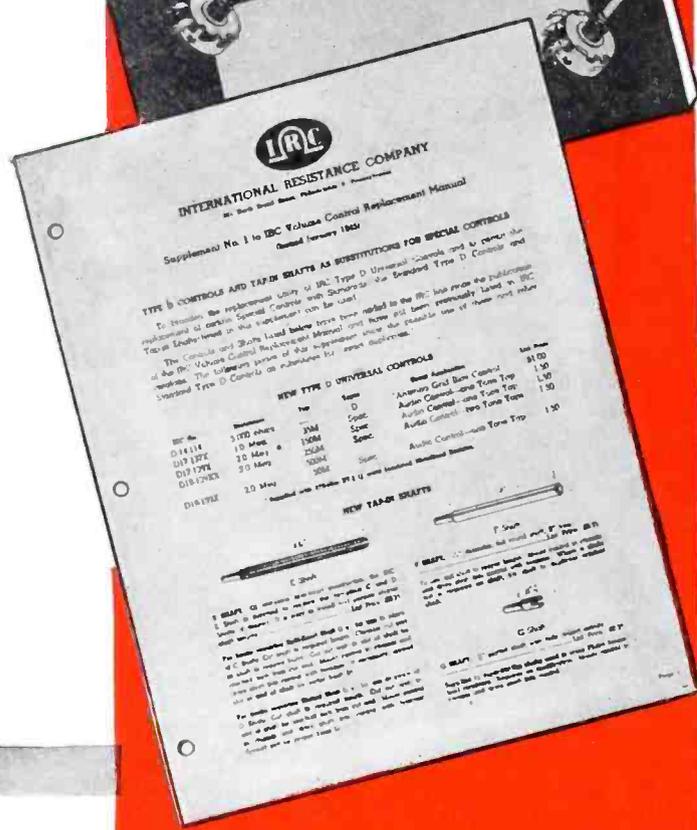

HERE'S WHY... In order to keep Servicemen supplied with the volume controls they require for a vast majority of their replacement needs, IRC recently introduced the "Century Line." Through concentration of manufacturing efforts on these carefully selected, one hundred controls you are assured sufficient quantities in a selection that will solve over 90% of your day-to-day service problems. All controls included in the "Century Line" are of the same high IRC quality for which the industry has always shown preference.


HERE'S HOW... To select the right control for the job at hand, look up the make and model of the set in the alphabetical listing in IRC's Volume Control Replacement Manual. Chances are you'll find the IRC control number listed right there. If however, an exact duplicate is called for, one further step is necessary. Look up the "J" number (exact duplicate) in Supplement No. 1. Directly opposite the duplicate part number you'll find the IRC "Century Line" number you can use for satisfactory replacement. It's as easy as that!

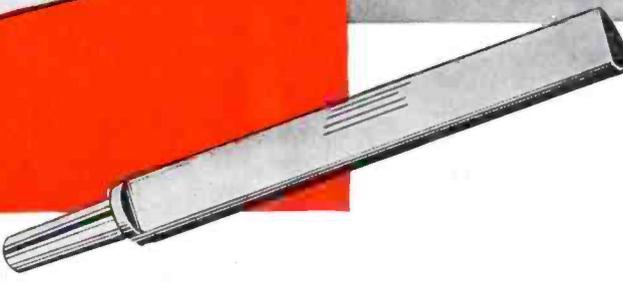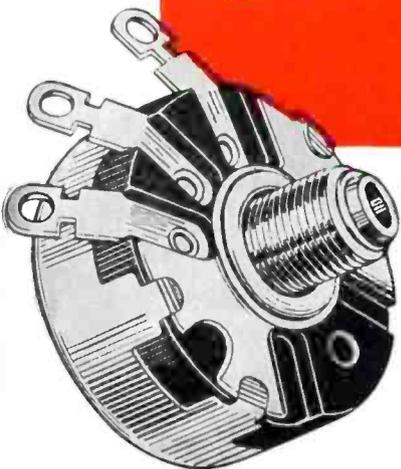If you do not have an IRC Volume Control Replacement Manual or a copy of Supplement No. 1 you can readily obtain one from your IRC Distributor—or by writing direct to Dept.




INTERNATIONAL RESISTANCE CO.
401 N. BROAD STREET • PHILADELPHIA 8, PA.

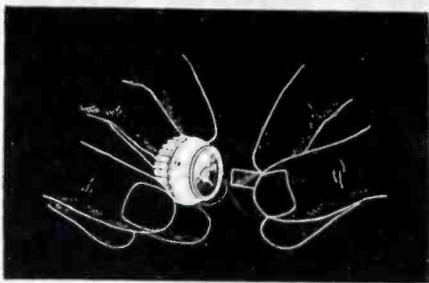IRC makes more types of resistor units, in more shapes, for more applications than any other manufacturer in the world.



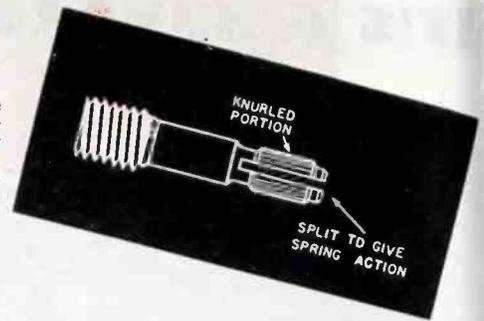Figs. 1 (left) and 2 (right). Fig. 1. How the metal spacer is inserted in the knob against the flat spring in push-on type knobs requiring only a $1/32$ " flat. (Courtesy P. R. Mallory & Co., Inc.) Fig. 2. Split-knurled type shaft that makes a set screw or spring in the control knob unnecessary.



VOLUME AND TONE CONTROL RESISTORS

VOLUME and tone controls have, in part, reached standardization of certain mechanical dimensions. In general, the tendency has been toward a reduction in overall size, particularly for automobile and midget receiver applications. Perhaps the greatest variance in the controls used as original equipment concerns the length of shaft and the method of fastening the control knob to the shaft.

Control Shafts and Knobs

The knobs used on most of the home and portable receivers have been of two general designs, the *set-screw* type and the *push-on* type knob. The shaft diameter has (practically from the start) been $1/4$ " in diameter and the bushing $3/8$ " in diameter, so from the replacement-control angle, the main problem involves the providing of a universal means which will allow the use of either the screw type or the push-on type of knob.

Provision of a *flat* on the shaft accommodates the screw type; it provides a secure mounting. The *push-on* type also utilizes a flat on the shaft, but in the design of such knobs two sizes have been developed, one which uses a shaft milled down $3/32$ " and one which uses a $1/32$ " milling. The former was extensively used in earlier receivers. The problem of making a universal line of home receiver controls has been met by one manufacturer by milling all shafts to $3/32$ ". This covers the majority of *push-on* type knobs and also accommodates the *screw* type. Then, for those cases which require a $1/32$ " milling, a small $1/16$ " metal insert or spacer is used on the deeper milling to bring it up to $1/32$ ". This spacer is inserted in the

Part Nine of a Series on Receiver Components

by **ALFREDA. GHIRARDI**

Advisory Editor

knob, resting it on the flat spring member (as illustrated in Fig. 1) before assembling the knob to the shaft. When this assembly is pushed on the shaft, it provides a secure and simple method of application. The milled side of the shaft is turned to the downward position allowing the insert to remain in the proper location in the knob during assembly.

Split-knurled shafts and correspondingly knurled knobs also have become popular, especially in auto-radio receivers, because the split gives a spring action and no additional set-screw or spring insert is needed in the knob. Furthermore, the knob can be pushed on the shaft in any relation to the sliding contact arm of the control. A split-knurled shaft is illustrated in Fig. 2. The knobs for split-knurled shafts will not fit the conventional flattened shaft.


Plug-in Shafts


The *plug-in* type shaft is a recent

innovation in universal shaft design. Such shafts are made in plug-in form to fit a special line of controls made by the particular manufacturer. The shaft is easily attached or detached to a special fitting in the bushing, and is held rigid. A recent shaft design employing a tapered plug-in portion is illustrated in Fig. 3; a complete line of plug-in shafts is illustrated in Fig. 4. With this entire set, the Service Man is sure of always having the right replacement control shaft at hand for nearly every job. For household receivers a kit comprising eight shafts (SS1, 2, 5, 16, 18, 22, 25 and 26) answers most needs. For automobile radios, a kit comprising twenty-two shafts (SS1, 2, 3, 4, 6, 10, 11, 12, 14, 15, 17, 19, 20, 21, 23, 24, 27, 28, 29, 30, 31 and 32) will meet all requirements.

Plug-in type shafts are becoming increasingly popular for the following reasons: (1)—They result in a tremendous increase in the flexibility of control applications, for only a few types of controls are required to service the large majority of receivers. Hence they reduce the stocking and inventory problem. (2)—They either replace the original shaft exactly, or they can be made into exact replicas by simply cutting to the required length.

Fig. 3. A recent design of tap-in (plug-in) shaft. (Courtesy IRC)

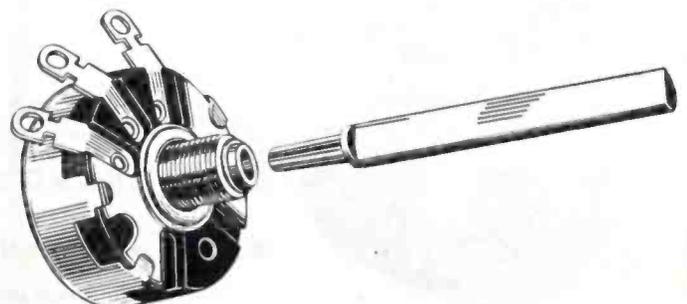

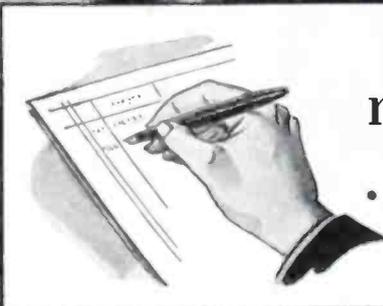

more efficient
... in miniature

The old quill was picturesque but it lacked the compactness, convenience and dependability of our modern fountain pen. Its development was the usual evolution. Changes and reduction in size made for greater efficiency. The same took place in the development of the modern miniature electronic tube.

While the reduced size of TUNG-SOL Miniatures alone warrants a preference for them, their greater efficiency has resulted in their general adoption, especially for high frequency circuits. Smaller elements make them more rigid. Shorter leads result in lower lead inductance. TUNG-SOL Miniatures have low ca-

capacity and high mutual conductance.

The many advantages of TUNG-SOL Miniatures will cause them to be used in much of the new equipment. It is important that TUNG-SOL Jobbers and Dealers are in position to supply miniatures as well as G-G's-metal and large glass tubes.



ACTUAL SIZE

TUNG-SOL

vibration-tested

ELECTRONIC TUBES

TUNG-SOL LAMP WORKS INC., NEWARK 4, NEW JERSEY
Also Manufacturers of Miniature Incandescent Lamps, All-Glass Sealed Beam Headlight Lamps and Current Intermittors

SERVICE, NOVEMBER, 1945 • 27


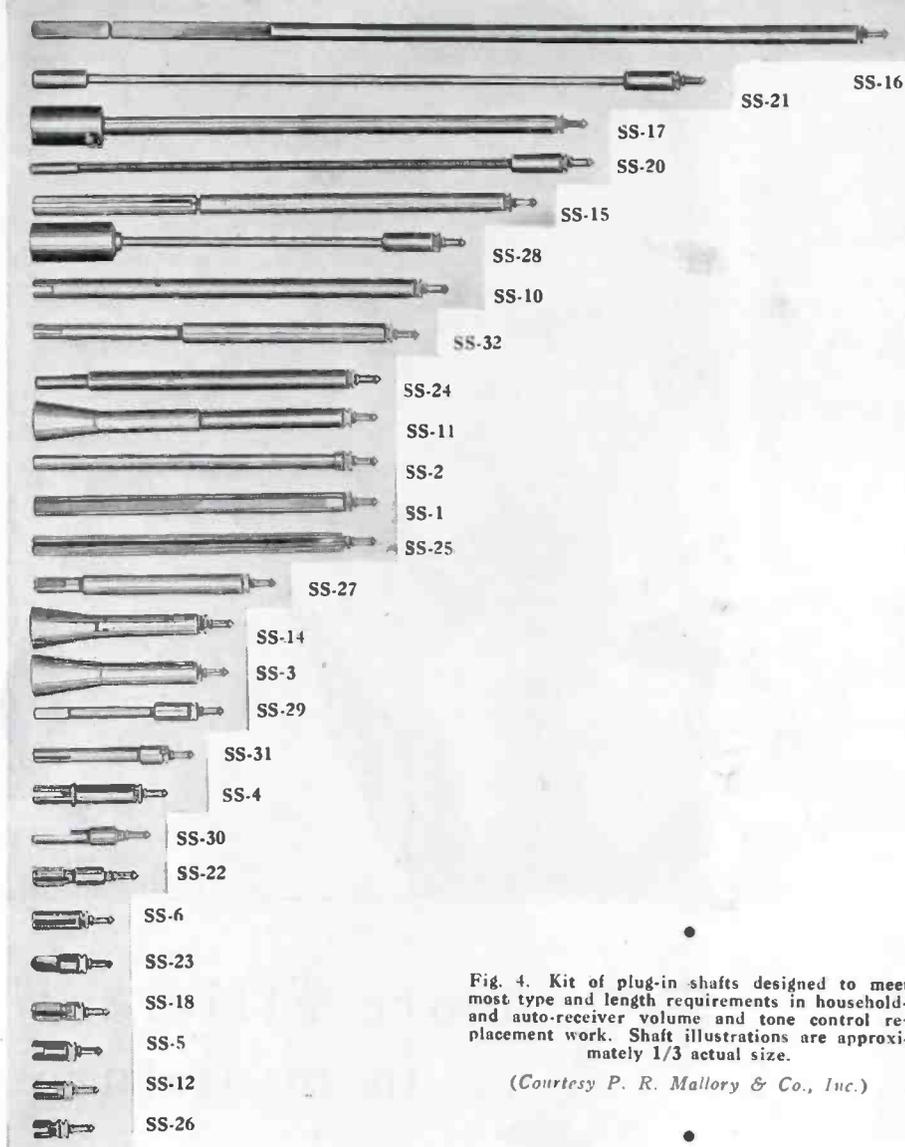


Fig. 4. Kit of plug-in shafts designed to meet most type and length requirements in household and auto-receiver volume and tone control replacement work. Shaft illustrations are approximately 1/3 actual size.

(Courtesy P. R. Mallory & Co., Inc.)

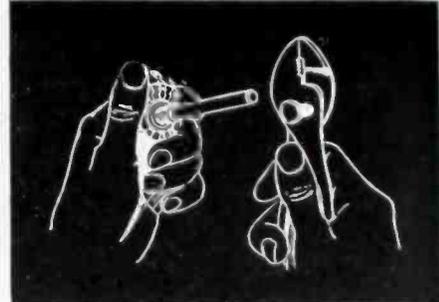

A sharp tap is all that is necessary to drive the shaft into the control.

depends on the chassis mounting, thickness of the receiver panel, etc. This dimension varies from 1/2" to 6" or more, with the majority of controls having shaft lengths of 1" to 1 1/2". To adapt a line of fixed-shaft replacement controls to all receivers, the shaft usually is made 3" or 4" in length. For the few receivers having longer shaft controls, extension shafts are obtainable. For shorter shaft controls the ordinary shaft (which usually is made from a special grade of aluminum or other fairly soft alloy) can be notched at the required length by means of a file or knife, as shown in Fig. 5, after which it can be easily broken, as shown.

A set of knurled, plug-in shafts of three different lengths up to 4", illustrated in Fig. 6, provide a flexible kit for plug-in shaft type replacement controls where a simple type of shaft is required. These may be cut to the required dimensions to make plug-in shafts of any desired shorter lengths.

Clutch Type Controls

A large number of auto-radio receivers have been constructed with the on-off switch that is in or upon the control head located on the car instrument panel, instead of being attached to the volume control in the receiver, Fig. 7.


This arrangement requires a special type of control known as the friction clutch type because it contains a friction clutch which permits the shaft to

(Continued on page 30)

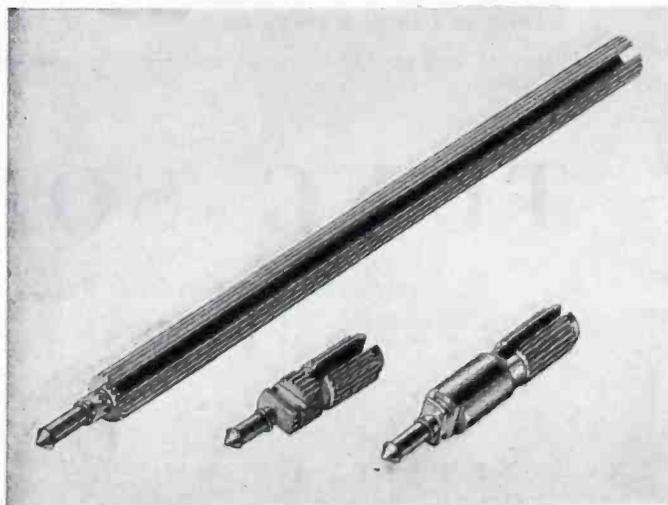
(3)—They speed up volume and tone control replacement in the many receivers in which other components are crowded against the back of the control. In such cases, the replacement control may be inserted in place before attaching the shaft, thus eliminating the necessity of first having to disconnect and remove nearby components from behind the control to

provide sufficient space in which to work. (In such cases, if the defective control that is to be replaced is constructed so its shaft is not removable, it may be slipped out from a crowded place by first cutting off its shaft as close to the panel as possible by means of a hacksaw).

The length of shaft used on controls in receivers is a variable. It de-



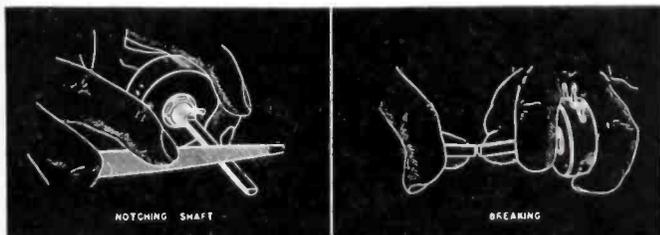Figs. 5 (below) and 6 (left). Fig. 5 Shortening a long shaft to the correct length. Fig. 6. Knurled plug-in shafts in three sizes up to 4". (Courtesy P. R. Mallory & Co., Inc.)



Want a share of Leadership?

Carry **RCA**
Preferred Type Tubes
The Tubes with the
Best Known Name




Now RCA Offers
a Complete Line
of Dry Batteries, Too

Metal, Miniature, or Glass—
THE FOUNTAINHEAD OF MODERN
TUBE DEVELOPMENT IS RCA

Listen to
"The RCA Victor Show,"
Sundays, 4:30 P. M.,
EST, NBC Network




62-6636-98

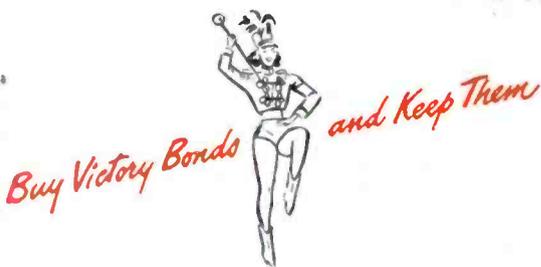


RADIO CORPORATION OF AMERICA

TUBE DIVISION • HARRISON, N. J.

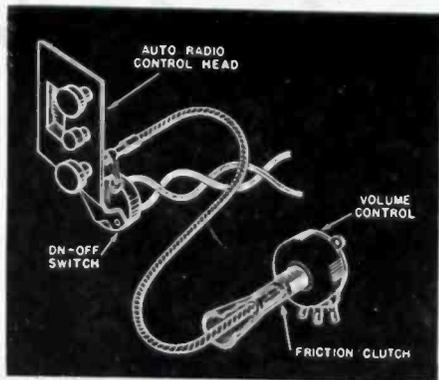LEADS THE WAY . . . In Radio . . . Television . . . Tubes . . .
Phonographs . . . Records . . . Electronics



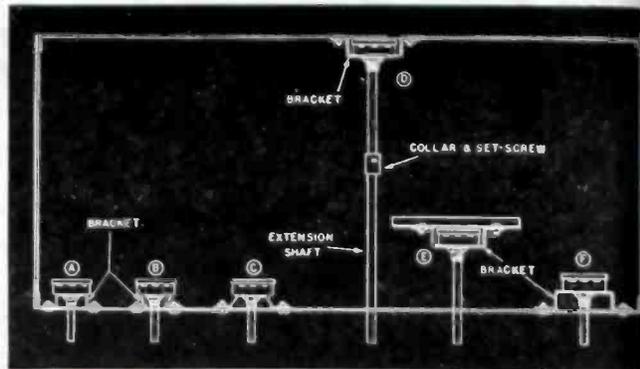Figs. 7 (left) and 8 (right).
 Fig. 7. Application of special type controls having a friction clutch-drive arm which permits the shaft to slip. Used in auto sets. Fig. 8 illustrates the use of brackets for mounting volume and tone controls to front panel and sub panels; also the use of an extension shaft where an extra long shaft is required.
 (P. R. Mallory & Co., Inc.)



slip in order to allow alignment of the contact arm of the control with the knob indicator on the tuning head so that the on-off switch operates at the correct position. When installing a repaired or replacement control of this type, we must first install the control and insert the driving shaft; then the control knob is turned through its full rotation in both directions. The result is the proper alignment of the contact arm of the control with the driving knob so that the switch operates at the correct position.

Controls having this clutch feature are usually provided with a plain cover, but with a proper portion of the resistance shorted out, so the volume control does not begin to function until the switch has been operated.

Several clutch-type control shaft assemblies of the plug-in type and in different lengths for various models of auto-radio receivers are illustrated at SS-3, SS-14 and SS-11 in Fig. 4.

Mounting Brackets, Extension Shafts and Bushings

Metal mounting brackets with slotted mounting holes are available to enable the Service Man to accommodate available replacement controls to most of the special methods of control mounting which are found in some radio chassis, or for attaching the controls to special mounting brackets provided on the receiver chassis. Fig. 8 illustrates several ways of using such brackets.

A narrow bracket may be used, as

shown at *A*, *B*, and *C*, where the control is to be fastened to the panel by means of two screws instead of by its bushing. In arrangements *B* and *C* the bracket is simply bent so that the spacing between the centers of its mounting-screw holes will be the same as that of the holes already in the receiver panel.

Illustration *D* shows the use of a longer mounting bracket, and an extension shaft with its collar and set-screw, when the control is to be mounted to a panel behind the front panel of the receiver. Notice the inverted position of this longer bracket.

In *E* we see the same type of mounting where however the shaft of the control is long enough to make the use of an extension shaft unnecessary. The mounting bracket can be used in the same way as in illustration *F*, if more convenient.

In some types of receivers, particularly auto-radio and communications-type receivers, many parts are mounted by means of such brackets, so some should be included in the Service Man's kit as a matter of convenience and to promote rapid replacement work.

Most controls employed as original equipment on receivers use a standard bushing $\frac{3}{8}$ " long. This has been adopted as standard by the RMA standards committee. Accordingly, a standard $\frac{3}{8}$ -32 bushing, $\frac{3}{8}$ " long is supplied on most commercial replacement controls.

In a few cases it is necessary to

mount replacement controls on extra thick panels. To accomplish this at minimum cost, hex-type shoulder nuts are available as accessories to the control and are sold separately. In using these hex-type shoulder nuts, it is necessary to enlarge the hole in the panel slightly by reaming it. These nuts are screwed on over the standard bushing; the regular flat nut supplied with all controls is not used.

Wire-Wound/Composition-Element Control Applications

Two broad types of volume controls are in general use . . . the composition-element or so-called carbon type and the wire-wound type¹. The former is popular applications of volume controls in cathode and voltage-supply circuits required controls having fair low resistance but a definite current-carrying capacity. Thus wire-wound controls were mostly employed in such circuits. However, the increasing popular practice of using a volume control that controls the audio circuit in AVC receivers, calls for a high-resistance type control which is not required to dissipate much power.


Because it is possible to manufacture the carbon-type control in a greater resistance range and flexibility in the matter of resistance taper², it is the type most used for such control circuits today, especially when intricate resistance tapers are required.

It is obvious that both types have a definite receiver application. It cannot be said that either one type or another is best for all purposes, for each has distinct advantages and disadvantages. Consequently, each type of control is limited in its application to the circuits or conditions requiring the particular advantages of its type.

Substituting Controls

Although volume- and tone-control manufacturers offer both types of controls

(Continued on page 61)

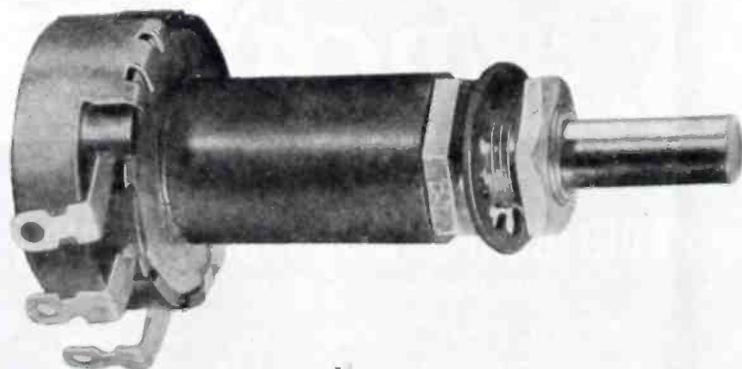


High-voltage insulating coupler applied to control that must be used in high-voltage circuits such as in television, c-r oscillographs, etc.

(Courtesy Clorostat Mfg. Co., Inc.) [Additional data on these couplers will appear in next month's installment.]

¹See Part 6 of this series, August 1944 SERVICE.

²See Part 7 of this series, September 1944 SERVICE.

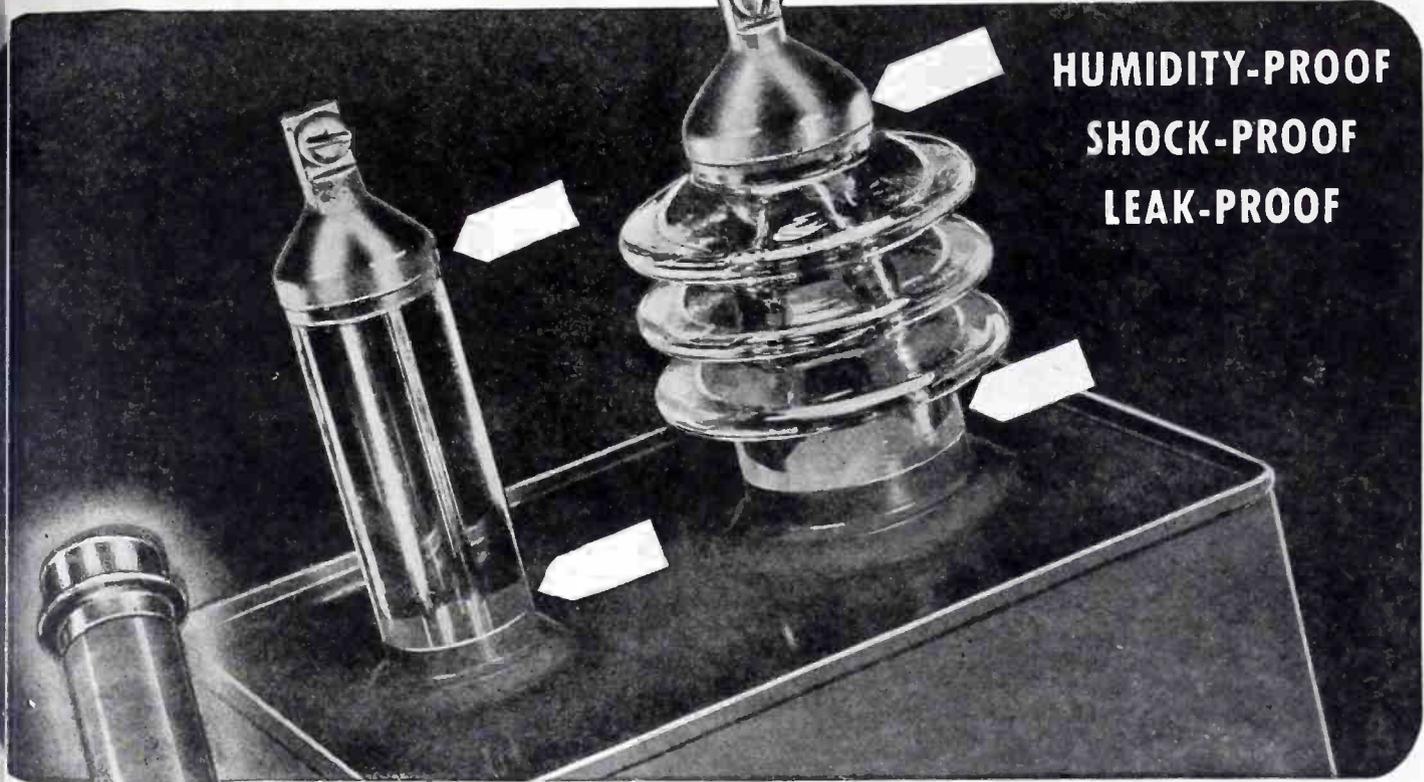WELDING GLASS TO METAL "COULDN'T BE DONE"...



**HUMIDITY-PROOF
SHOCK-PROOF
LEAK-PROOF**

... but here it is!

If you want to have a look at the Capacitors and Resistors of tomorrow, step in and see what has been going on in the Sprague Engineering Laboratories (if wartime restrictions would permit!). Then it will be easy to understand why Sprague has been a FIVE TIME WINNER of the coveted Army-Navy "E" Award!

against shock—and doing it without the use of glass bushings or adjacent metal rings with "matched" temperature coefficients of expansion. Actually, there were many "scientific" reasons why glass could not be fused to metal—but Sprague not only proved that it could be done, but done economically and in tremendous quantities.

A typical example is the Sprague Electric Co. glass-to-metal seal. This amazing development answers the old problem of sealing Capacitors and Resistors against leaks and moisture, guarding them

This sort of accelerated wartime engineering is reflected throughout the entire Sprague line—and that means unsurpassed quality for every unit used on every day radio work!

THE TRADING POST CONTINUES!

SPRAGUE PRODUCTS COMPANY, North Adams, Mass.

(Jobber Sales Organization for Products of the Sprague Electric Co.)

Sprague's famous free buy, sell, or exchange advertising service "THE SPRAGUE TRADING POST" appears on page 6 — of this issue — and will continue to appear as long as wartime shortages create a need for it. Meanwhile, we'll appreciate it if you continue to use Sprague Capacitors and Koolohm Resistors—and to ask for them by name!

SPRAGUE



CAPACITORS FOR EVERY SERVICE, AMATEUR AND EXPERIMENTAL NEED

SUPERHETERODYNE MIXERS

by MARTIN W. ELLIOTT

[Part Two]


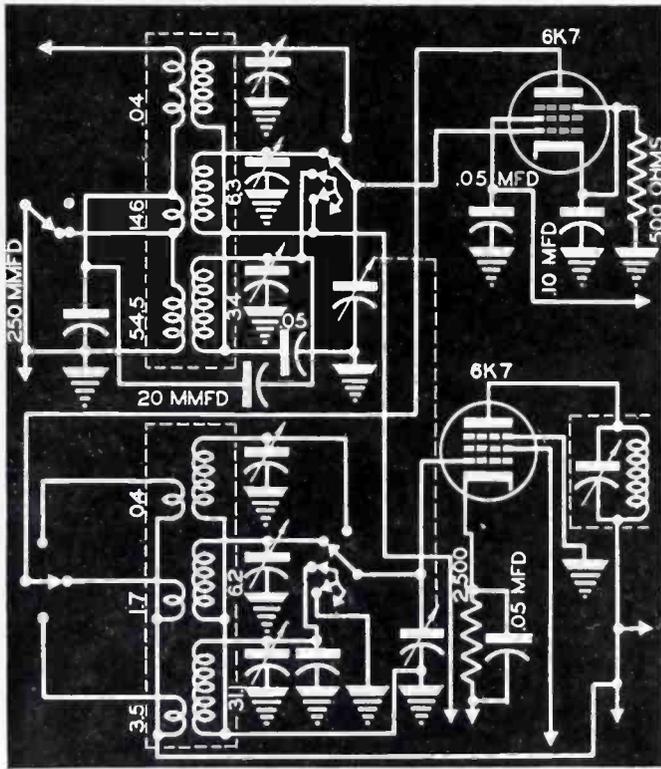


Fig. 11. Mixer circuit of the Ward 62-262. Here, a separate oscillator, not shown, is used. Coupling to the mixer tube is accomplished by tying the oscillator plate to the mixer screen grid.

Fig. 10 (below). Mixer circuit of the Lafayette C-37. A Colpitts-type oscillator is used to simplify the wiring, since only two terminals are required. Note the d-p-d-t switch used to change from manual to automatic tuning.

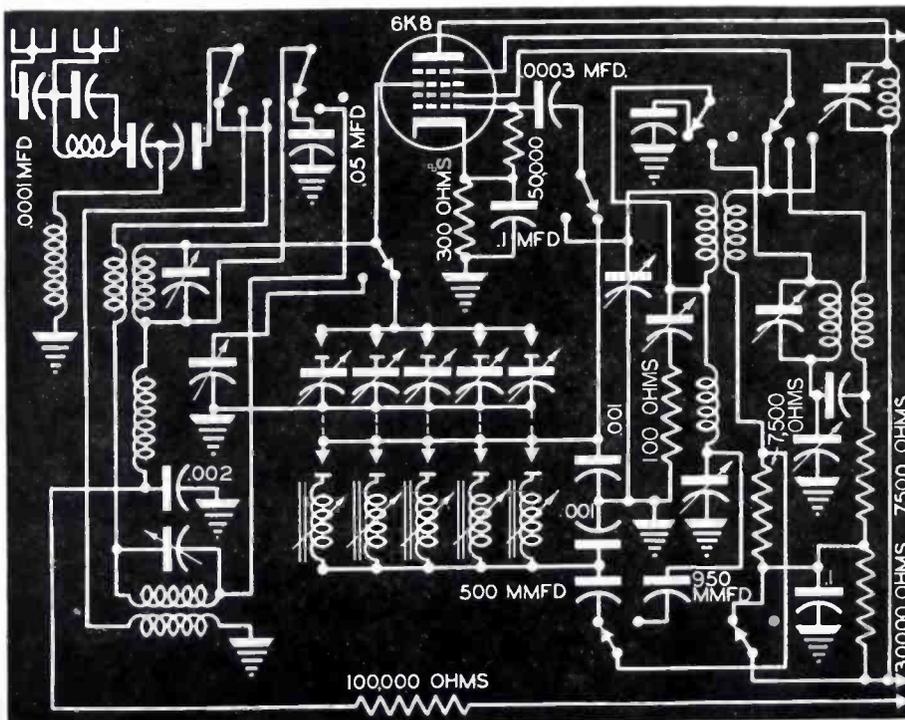

THE mixer of a 3-band receive Lafayette C-37, using a 6K8, shown in Fig. 10. Provision made for long and short antennas, 456-kc i-f wavetrap, a shunt r-f choke isolated by two capacitors and push button automatic tuning with capacitor tuning for the signal frequency, a permeability tuning for the oscillator frequency. A 300-ohm cathode resistor and 50,000-ohm grid leak provide tube biasing. A Colpitts oscillator circuit with the grid at one end of the coil and the plate at the other end, and the cathode at the potential of the center of the coil by virtue of two .001-mfd capacitors affords a convenient tuning circuit because only two coil terminals are required. The grid is connected through a large .0003-mfd grid capacitor, while the plate is connected through a .0005-mfd capacitor. This is called a shunt-feed system. A 50,000-ohm leak is connected between the grid and cathode. Manual to automatic tuning is controlled by a d-p-d-t switch.


Capacitor-Tuned Oscillator Control

The capacitor-tuned oscillator used in the manual position is also unconventional. On the s-w position shown the grid is connected to the top of the oscillator-tuned circuit. The plate is connected through a tickler coil and .00075-mfd capacitor to the opposite end of the tuned circuit. The junction of the two coils in the tuned circuit is connected to ground through a trimmer and 100 ohms, also through a switch to ground through a .0065-mfd capacitor, virtually shorting the lower coil. On the police band the lower coil is shunted by a grid coil of second-oscillation transformer. The

(Continued on page 39)

RADIART VIBRATOR GUIDE (Most Complete Published)

Makes
Vibrator Servicing
Easy!

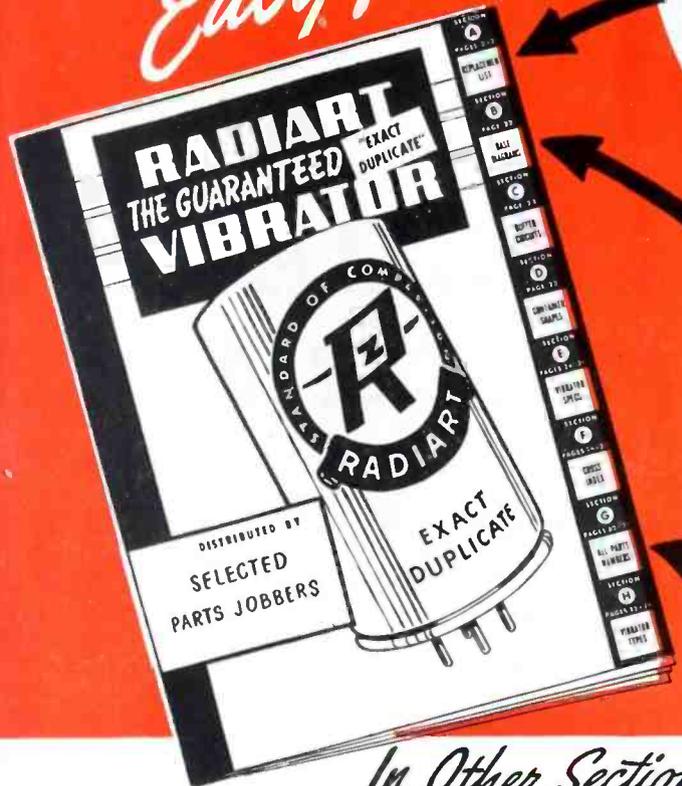

Section A...Vibrator

MFRS. PART NO.
SERIES NO. SET MFR. YEAR MADE
RADIART NO.
BASE DIA.
LIST PRICE
BUFFER COND.
CAR MAKER

Name, Model No.	Mfrs. Part Number	Radiart Number	List Price	Base Dia.	Buffer Condenser
CHRYSLER					
C1808 (Elec. P. B.) (Philco—1941)...	83-0027	5326P	3.00	A	.005
25C6 (Wells-Gardner—1938)...	19A32	5437	5.95	AB	.018
600 (Mech. P. B.) (Colonial—1941)...	43697	5301	3.55	A	.004
601 (Colonial—1942)...	911545	5301	3.55	A	.004
800 (Philco—1941)...	83-0027	5326P	3.00	A	.005

Every model listed includes all available data. The correct Radiart Replacement number and other essential information is determined instantly.

SECTION "B"—Cross

Diagram Number	Shape	Voltage	Diam.	Ht.	Freq.	Identifying Characteristics	Max. Load Amps
B	3417	2	6	1 1/4	4 1/2	105	6
	3815	9	6	1 1/8	4 1/2	105 Spec. Cup	6
C	5309	1	6	1 1/2	2 3/4	105	6
	5331	1	6	1 1/2	3 1/4	105	6
D	4256	1	6	1 1/2	3 3/4	105	10
	4256-12	1	12	1 1/2	3 3/4	105	6

In addition to conventional base diagram drawings this section is unique in that it groups all similar base types together indicating readily the differences between vibrators with the same base wiring. All characteristics are shown, including frequency and maximum load limit of each type.

In Other Sections..

- Section "C"**—Buffer Condenser Values and Circuits.
- Section "D"**—Container Shapes permitting an easy method of "visual" identification.
- Section "E"**—Complete Vibrator Specifications arranged numerically by number. Contains necessary data not published in any other replacement guide.
- Section "F"**—Long a favorite with users of this guide. The only cross-index of all other manufacturers or merchandisers of vibrators, converting their type numbers to the Correct Radiart Replacement.
- Section "H"**—Numerical Listing of Radiart Vibrators. Furnishes complete information as to all models serviced by each unit. Also advises year each type was originated.

Auto Radio Service Dealers:

Obtain this Guide free of charge from your Radiart Distributor. Ask him to furnish you with a stock of the popular 12 types of Radiart Vibrators each of which is guaranteed to CORRECTLY service the applications listed for it in this guide. With these 12 types you can satisfy nearly all of the "Demand" types. But — RADIART is a complete line and your Radiart Distributor renders a complete service and can quickly furnish all of the necessary slower moving correct Radiart Replacement Vibrators as well.

Manufactured by the makers of RADIART Rust Proof Aerials.

SECTION "G"—Radiart and Original Equipment

Original Equipment Part No.	Radiart Part No.	Original Equipment Part No.	Radiart Part No.	Original Equipment Part No.
75	3283	1974	5301	8539
80-161	5421	2080	3417	8540
82B	5341M	2110	3417	8541
83-0017	5326P	2269	5413	8542
83-0025	5326P	2404	5340M	8601
83-0026	5326P	2501	5411	8602

Another Radiart Vibrator Guide EXCLUSIVE feature. When called upon to duplicate a vibrator and no information is available except the number on the old one, use this cross-index which shows the original manufacturer's number (as stamped on vibrator) and the CORRECT Radiart Replacement.



Radiart Corporation

3571 W. 62nd STREET • CLEVELAND 2, OHIO
 Export Division 25 Warren St., New York 7, N.Y.
 Canadian Office 455 Craig St., W., Montreal, Canada

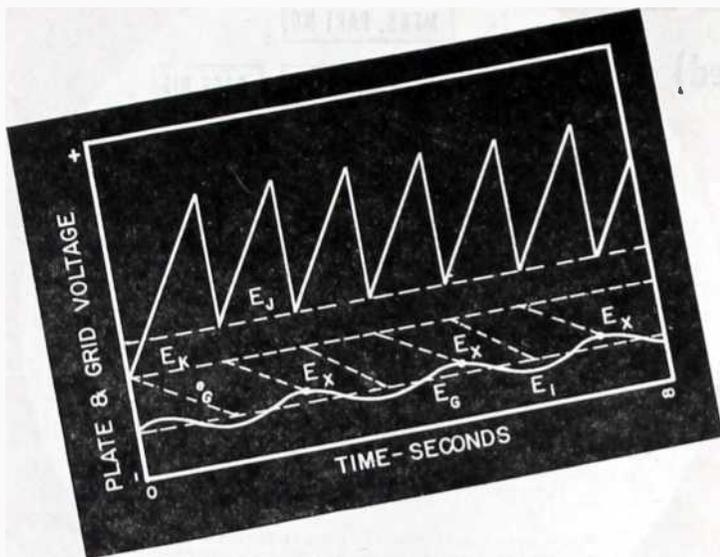


Fig. 1. Graphical synchronization of the linear time-base oscillator system. The critical grid voltage E_g , at which the thyatron conducts, is proportional to the plate-to-cathode voltage E_p . Thus when the timing capacitor voltage, which is the thyatron plate voltage, is near a maximum value, the signal voltage component E_i exceeds the critical grid-to-cathode voltage level. This condition occurs at the critical grid voltage level E_x , and the thyatron relaxes the capacitor charge synchronously with the arrival of the maximum positive potential level of the signal voltage.

C-R OSCILLOGRAPHS SERVICING... APPLICATIONS...

WHERE the oscillograph is utilized to provide a visual analysis of voltage variations, under the condition that the linear time-base oscillation system is not synchronized to oscillate in phase with the frequency of the variation under observation, the image appearing on the screen appears to be in continuous motion. This condition results from the existence of the heterodyne or beat frequency which is developed between the frequency of the voltage under analysis and that of the linear time-base system output.

In order that the waveform appearing on the screen be stationary, it is imperative that the frequencies of the incoming signal voltage and of the linear time-base oscillator synchronize perfectly. Thus, if the image or waveform which is written on the screen varies in exactly the same pattern with each positive motion or sweep of the electron beam, the image of the waveform is written on the screen in exactly the same manner with each succeeding sweep. If, however, the subject waveform occurs earlier in each of the succeeding sweeps of the electron beam, the waveform written on the screen is altered in position with each sweep. Moreover, since the waveform is recurrent earlier in each charging of the linear time-base timing capacitor, the resulting image of the waveform on the electron screen appears to *move to the left*. Again, if the waveform should occur later in each positive motion of the electron beam, a similar alteration of the wave

[Part Five of a Series]

by S. J. MURCEK

image position obtains, and the image appears to move to the *right*.

As a direct consequence of the definite motion which is imparted to the wave image written on the screen by the beat which is present between the two frequencies, it becomes possible to determine accurately the frequency of the voltage variation which is under visual analysis. This, if the motion of the written image is in a left hand direction, the frequency of the signal voltage is greater than that of the linear time-base oscillator. Conversely, if the image motion is in a right hand direction the signal voltage frequency is less than that of the linear time-base oscillator. Zero beat, or synchronization of the two frequencies, occurs when the image is stationary.

For wave- or voltage-variation analysis, it is essential that the image remain stationary. This, in turn, requires that the oscillation of the linear time-base oscillator occur in exact synchronism with the voltage variation which is under analysis. Commercial oscillographs are, therefore, provided with suitable means for the necessary synchronization of the linear time-base system and the signal voltage frequencies. In all of these oscillographs, the

synchronization is usually effected through the modulation of the linear time-base relaxation tube grid bias potential by a portion of the voltage variation.

The synchronizing system utilized in the du Mont 164E oscillograph is shown in the circuit diagram, Fig. 2. Here, the voltage which is under observation is impressed across the synchronization system input terminals H and G . Since the capacitance of the dynamic coupling capacitor C_{12} is large, and the resistance of the synchronization potentiometer R_s is high, the voltage variation impressed across the input terminals EXT and G appears, in the greatest part, across the resistance element of the synchronization control potentiometer. Further, since a portion of this potential appears between the slider arm and the grounded terminal of the synchronization control potentiometer, and is thus directly in series with the control grid of the $2B4$ thyatron, together with the grid current limiting resistor R_{g1} , a part of the signal voltage variation is effectively in series with the thyatron control grid-to-cathode bias potential, the latter maintaining the thyatron control-grid negative. Hence, each positive alternation of the signal voltage effects a reduction of the negative grid-bias voltage present between these electrodes.

The effects of the signal-voltage modulation of the $2B4$ grid-to-cathode potential are evident from the graphical illustration of Fig. 1. Here the

Here's your big, profitable tube market!

—the millions of radio owners who

HEAR

G-E programs on the air



READ

G-E magazine advertising



USE

G-E lamps and appliances



● These people all are G.E. conscious. In 7,000,000 homes they listen to programs featuring General Electric tubes and radio sets. National magazines with a total circulation of 30,000,000 give them a similar message. And everywhere they see the famous G-E monogram on lamps, refrigerators, ranges, electric irons, and other home appliances.

● YOU can profit from this big, hungry market by selling G-E radio tubes. Arrange now for a sharp increase in your tube business in the months ahead. Write for information about G-E tube selling rights to *Electronics Department, General Electric Company, Schenectady 5, N. Y.*



Hear the G-E radio programs: "The World Today" news, Monday through Friday, CBS. "The G-E All-Girl Orchestra," Sunday, NBC. "The G-E House Party," Monday through Friday, CBS.

GENERAL ELECTRIC

176-05-8880

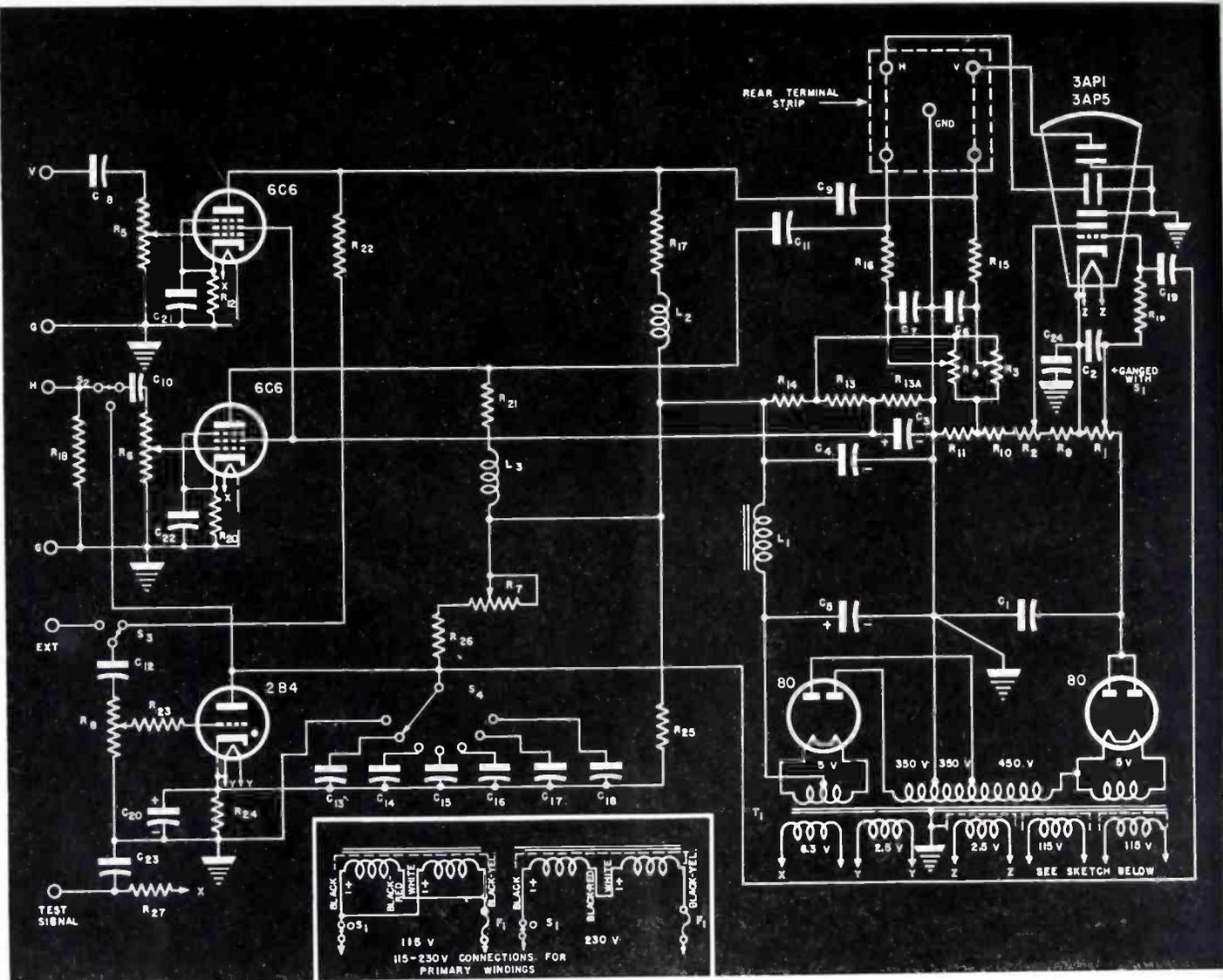


Fig. 2. Circuit of Du Mont 164 E oscillograph.

relations of the various voltage variations occurring in the synchronized linear time-base oscillator operation are plotted with respect to the 2B4 cathode potential level E_k . The d-c component of E_c , which is negative, is shown to be modulated by a portion of the signal voltage variation E_s . Since the critical grid potential E_r is increasingly negative with each increase of the plate-to-cathode potential, E_p , and the latter increases directly in proportion with the charge on the timing capacitor, the positive variations of the grid-to-cathode control voltage eventually exceed the critical voltage E_r . Thus the control grid of the thyratron is effectively positive and becomes conductive, at which instant the tube relaxes the charge on the timing capacitor. Therefore, when the linear time-base oscillation circuit is so adjusted that the frequency of the relaxations is near that of the signal voltage, as we see in Fig. 1, each relaxation must occur in synchronism with each positive alternation or peak of the signal voltage.

Further study of Fig. 1 indicates that thyratron breakdown and the relaxation of the charge on the timing

capacitor occur when the signal voltage attains its maximum positive crest, under the condition that the signal voltage wave is of sine wave form. Since the maximum positive voltage level in any sine wave alternation occurs 90° after the inception of the cycle, the relaxations of the linear time-base capacitor charge occur 90° out of phase with the signal voltage variation. The wave image written on the screen is consequently initiated at the maximum positive potential level in its pattern.

Studying the circuit of Fig. 2, we note that the signal voltage variation required for the synchronization of the linear time-base oscillations is obtained either from the plate circuit of the vertical amplifier, or from the external signal synchronizing voltage source, available through the input terminals *EXT* and *G*. A convenient switch, S_3 , is provided to connect the ungrounded terminal of the synchronization control potentiometer, R_8 , to either voltage source. The series resistor, R_{22} , connected between the *INT* contact of the

switch S_3 and the plate of the vertical amplifier pentode prevents excessive loading of the vertical amplifier plate circuit by the linear time-base synchronizing input circuit. Only a very small portion of the vertical amplifier output voltage is necessary to effect satisfactory synchronization of the two frequencies.

In general, modern electronic apparatus is designed for synchronous operation from low-frequency commercial power sources. Hence, synchronization of the horizontal sweep frequency in the oscillograph with that of the voltage variations usually encountered in industrial electronic apparatus, is most effectively accomplished through a linear time-base synchronization circuit connected directly to a voltage source of the same frequency. This type of operation is especially important where the phase relation of the voltage variation under observation to that of the source voltage wave must be ascertained, inasmuch as such phase relationships are not evident when the synchronizing system is activated by the plate circuit of the vertical amplifier.

Where the synchronization of the

linear time-base frequency to that of the voltage under study is accomplished by exciting the plate circuit of the vertical-amplifier pentode, relaxation of the timing capacitor charge must always occur at the maximum positive voltage level attained by the amplified signal voltage.

Thus, if the maximum positive voltage crest occurs when the vertical-amplifier output voltage is completely out of phase with that of the voltage source wave, the linear time-base capacitor relaxations occur at the maximum positive peak of the amplifier output voltage and are, therefore, completely out of phase with relation to the source voltage wave. Further, if the phase position of the amplifier positive peak voltage swing varies with relation to its initial position, the linear-time base capacitor relaxations must also vary in phase position, and the wave image written on the screen shows no resultant motion. This factor is of great importance where the signal voltage is, for example, the a-c component of a phase-controlled rectifier grid-to-cathode control potential, where the phase position of the a-c component must be shown to vary directly with the operation of the phase-control potentiometer.

When it is necessary to synchronize the oscillograph horizontal sweep voltage with that of the line frequency, or that of the source, it is only necessary to connect the terminal, *test signal*, to that marked *EXT*, and to operate the switch, S_8 , to the *EXT* position. Then the horizontal sweep voltage will be synchronized with the a-c or source voltage frequency, at a 90° phase lead angle. When the oscillograph is operated with this form of horizontal frequency synchronization, application of the input voltage results in the development of a wave image which is initiated at the *positive* zero voltage inflection of the sine voltage wave. The maximum positive crest of the signal potential is shown clearly as a positive peak or cusp in the screen image. Moreover, if the phase position of the signal voltage wave with relation to that of the source voltage wave is varied, the extent of the variation is clearly visible in the motion of the screen image.

Where the oscillograph is operated from a stable voltage source, the voltage present across the phase-shifting capacitor, C_{20} , may be readily utilized to calibrate the vertical deflection system. The calibration is accomplished through connection of the capacitor terminal, *test signal*, to the vertical amplifier input terminal, V , and the subsequent adjustment of the vertical gain control to such a position that the height of the vertical motion of

the luminous spot on screen is twice the division number.

The horizontal voltage sweep-frequency range is arranged for operation over a frequency range extending from a low frequency limit of approximately 12 cps to a high-frequency limit approaching 50 kc. Since this extended range cannot be practicably arranged in a circuit comprising a single capacitor and a single variable resistor or potentiometer, a multiplicity of capacitors, $C_{13-14-15-16-17-18}$, of various capacities are used, together with a *vernier frequency* control potentiometer, R_{20} , and range selector switch, S_4 . Each of these capacitors is so selected that the frequency ranges covered appreciably overlaps the ranges covered by the capacitors adjacent to the former. It should be observed here that the shield terminal of each capacitor is common with the cathode of the relaxation thyatron, and that the maximum potential which is developed across these capacitors is relatively low in level. Further, because of the low-capacitor operational potential, the charge stored is correspondingly low, necessitating the application of high capacitances in the lower-frequency ranges.

It is the horizontal deflection system, together with the linear time-base oscillator, which must be generally depended upon to effect the writing of recognizable waveforms on the screen. Where the signal input or dynamic voltage variation applied to the input terminals of the vertical deflection amplifier is subject to sporadic disturbances or interruptions, the continuous horizontal motion of the beam, effected by the linear time-base oscillator and the horizontal deflection amplifier, prevents accidental damage to the screen which would result with a stationary luminous spot. Hence, before any cathode-ray oscillograph is placed into actual operation, it is prudent to be sure that the beam will be in motion when the cathode of the tube reaches operating temperature.

In the du Mont unit of Fig. 2 the *intensity* or beam control is ganged with the primary or power input control switch, S_1 . Thus, when the unit is placed into operation, it is only necessary to partially turn the intensity control to the a-c line control switch, S_1 to the *on* position. The slider arm is then placed so that the grid is maintained quite negative. This prevents further development of an electron beam during the period in which the tube heaters rise to operating temperature. Then, it is necessary to see that the horizontal amplifier input control switch, S_2 , which is usually ganged with the linear time-base *coarse-frequency* control switch, S_4 , is in the

linear sweep position, if no other form of horizontal deflection potential input is to be used. In this way we can be sure that the beam will be in motion when the beam is permitted to strike the screen.

Since the first plate, or accelerating electrode, is effective in the development of the beam, it is necessary to turn the *focus* control potentiometer knob a complete half-turn in a clockwise direction. The *vertical* and *horizontal* positioning controls determine the normal or *idle* position of the electron screen pattern.

The length of the horizontal sweep pattern is governed by the amplification level at which the horizontal amplifier operates. Inasmuch as no actual deflection of the electron beam occurs if this control is left in the minimum or zero position, it is advisable to advance the horizontal or X axis amplifier gain control, in a clockwise direction, at least to the 50% dial position. At this time, the intensity control may be advanced in a clockwise direction until a visible green trace is written on the screen. The intensity of the luminous trace is then carefully adjusted to the desired level or brightness, and focussed to the desired clarity, by manipulation of both the intensity and the focus control potentiometers. Here, it may be found that the horizontal sweep voltage causes the written trace to extend beyond the edges of the electron screen area, causing a visible parasitic glow at either of its extremities. This condition is corrected by appropriate reduction of the horizontal amplifier gain. The final position of the trace may be brought to the geometric center of the screen by the proper manipulation of the vertical and horizontal positioning controls. In the instance of the vertical control, the screen pattern moves *upward* when the vertical control is turned in a clockwise direction, and, in the instance of the horizontal control potentiometer, the pattern moves to the *right* when the control is turned in a clockwise direction.

Under the condition that the controls are in the position just described, the pattern written on the screen will be a short, straight line. If, at this time, an a-c potential is applied to the input terminals V and G of the vertical amplifier, and the vertical gain control is advanced slightly, the beam will be subjected to deflection voltages which operate at a right angle with respect to each other. Briefly, the vertical deflection is perpendicular to the horizontal deflection. The pattern written on the screen is reformed into rectangular coordinates, the actual

(Continued on page 52)

ONLY 5 SWITCHES

**FOR COMPLETE
TUBE
AND SET
TESTING**



MODEL 802 N COMBINATION TUBE AND SET TESTER

Five simple switches are all that is needed for both tube and set testing with this one economical unit. The complete instrument is protected against burn-out by a line fuse, immediately replaceable.

RANGES—DC voltmeter 0/10/50/500/1000 at 1000 ohms per volt. AC voltmeter 0/10/50/500/1000. DC milliammeter 0/1/10/100/1000. DC Ammeter 0/10. Ohmmeter 0/500/5000/1,000,000/10,000,000. Low ohm center. Db Meter—8+15/15 to 29/29 to 49/32 to 55 decibels. Output Meter—same as AC volts.

MODEL 802N. Size: 12 $\frac{3}{4}$ " x 12" x 5 $\frac{1}{4}$ ". Weight: 11 $\frac{1}{2}$ lbs. In handsome hardwood case, with special compartment for small tools, etc., complete ready to operate with self-contained batteries\$57.50

CHECK THESE FEATURES

TUBE TESTER—Tests new and old type tubes. Separate noise tester for tubes that otherwise test "good." Gives speedy leakage short tests between all elements.

SET TESTER—R.C.P. unique rectifier circuit gives AC measurements free from temperature and frequency errors. AC voltage scales coincide with DC. A leakage test is provided for electrostatic condensers.

METER—Large scale 4 $\frac{1}{2}$ " rectangular meter protected against burn-out by special fuse for both multitester and tube tester.

RADIO CITY PRODUCTS COMPANY, INC.

127 West 26th Street



New York 1, N. Y.

ELECTRONIC ALARMS

(Continued from page 24)

once it is tripped it remains closed until opened manually. R_1 limits the plate voltage on tube 2, so that the plate current will not be too high for the positive grid condition of operation.

Although circuits of this kind can be developed experimentally, it usually is better to purchase commercially manufactured products which have had the kinks removed.

Another type of alarm control is

shown in Fig. 2.* The operation is very simple. The oscillator may be tuned to a fairly high frequency, perhaps 7000 kc. If a small change in capacity occurs in the grid circuit, the oscillator plate current will change. Adding capacity to the grid circuit causes a decrease in the operating frequency, which, in turn, causes the oscillator plate current to rise. This increase in current may be sufficient to

cause the closing of a sensitive relay in the plate circuit of the oscillator tube. When the relay contacts close, an external bell system circuit is set in operation, giving the alarm.

In this circuit, C_1 is a small capacitance to limit the detuning effect. L_1 and L_2 represent the oscillator coil, the lower section L_2 serving to provide inductive coupling between grid and plate circuits and develop oscillations. C_2 the tuning capacitor to set the frequency of operation. C_3 and R_1 are the usual gridleak and capacitor, and C_4 is a plate circuit r-f bypass capacitor which keeps the plate-circuit impedance low in value, and aids oscillation.

In a typical installation the pickup wire would be connected to the object to be protected. If the object were a safe, it would be insulated from the ground by rubber pads and serve as the pickup wire. Anyone coming near the safe would upset the capacity of the circuit and detune the oscillator, setting off the alarm. Anyone approaching a door or window where the pickup would be located would also cause the alarm to be set off.

Another type of alarm is shown in Fig. 3. Two metal plate electrodes are used. Normally, they are separated, but when anyone exerts pressure on them the plates touch and the alarm is set off. Once the alarm is set, the relay stays closed, due to a locking arrangement, until turned off manually. Normally, with the plates not touching, the grid circuit of the tube is open, since R may have a value of 10 or 15 megohms. Closing the grid circuit causes the plate current of the tube to rise and the relay swings into operation, causing the alarm to go off.

Thin steel plates are probably the best to use, for they are quite tough and flexible.

Electrically, the steel is not very conductive, but since the resistance can be fairly high and still permit efficient operation of the tube this is no particular disadvantage.

Alarm circuits may also be devised to actuate cameras. The cameras may be concealed in the walls. The relay contacts are simply connected in series with a flashbulb circuit using a couple of dry cells to set off the bulb. The shutter on the camera can be left open. The speed of the flash explosion is sufficient to catch the action without using intricate timing arrangements.

*Some of these circuits are covered by patents and cannot be duplicated for sale to others.

MIXERS

(Continued from page 32)

plate is switched to the tickler of the second transformer. On b-c both the coils of the first transformer are used in series. The plate voltage is increased for automatic tuning by shorting a 30,000-ohm series resistor in the B supply.

Ward 62-262

A complex mixer system with a tuned r-f stage, 3-gang capacitor and a separate 6C5 triode oscillator, Ward 62-262, is shown in Fig. 11. This model uses 6K7s for both r-f amplifier and mixer. Three bands are covered; 148 to 380 kc, b-c and s-w. The antenna transformer has three primary coils in series with a shorting switch for the l-f and b-c primaries, as well as a .00025-mfd capacitor across them. A 20-mmfd coupling capacitor links the b-c primary and the l-f secondary for additional l-f coupling. A separate secondary is used for each band with a combination selector and shorting switch for wavechanging. The interstage transformer is similar except that the r-f amplifier plate is switched to individual primaries.

The oscillator transformer uses separate cathode ticklers for l-f and b-c and a combination of cathode-tapped Hartley and plate tickler for s-w. The mixer tube is excited by cathode-to-cathode coupling through a bias resistor of 2500 ohms and its .05-mfd bypass. The oscillator plate is also directly connected to the mixer screen. The plate is at ground potential at l-f and b-c but is hot on the short-wave band because of the plate tickler. Therefore, this tie to the screen constitutes an additional source of excitation. In some receivers with a separate oscillator, supplementary short-wave coupling is supplied to the signal grid. Still other sets use magnetic coupling between oscillator and converter by winding the coils on the same coil form.

VIDEO WINDOW DISPLAY



One of a series of five window displays used by Gimbel's-Philadelphia to promote the RCA in-store television demonstration being staged by Gimbel's.

Communications WELL IN HAND



• Transmitting equipment designed and manufactured by Wilcox Electric Company of Kansas City, Missouri.

THE inclusion of Astatic's GDN Series Dynamic Microphone in this modern airline dispatching office installation speaks for itself. Present-day communications systems demand the finest possible equipment. Astatic products measure up to these high standards of operating efficiency.



SHOWN in the installation pictured above is a Dynamic, semi-directional, all-purpose Microphone of the Astatic DN Series, mounted on Grip-to-Talk Desk Stand. This stand embodies a relay-operating ON-OFF Switch for remote control of transmitters and amplifiers, the switch itself being operated by a slight pressure of the fingers upon a convenient grip bar.

Astatic Microphones, Phonograph Pickups and Cartridges are going forward daily in an ever-increasing volume to manufacturers of radio, phonograph, communications and public address equipment, and to authorized Astatic jobber outlets.

You'll HEAR MORE
from Astatic

THE
Astatic
ASTATIC CORPORATION
CONNEAUT, OHIO

IN CANADA CANADIAN ASTATIC LTD. TORONTO, ONTARIO

*You've Made Money on Radio Sets,
Parts, Service, RCA Tubes—*

**NOW YOU HAVE A NEW OPPORTUNITY
WITH RCA RADIO BATTERIES—**

The Batteries That Are Radio-Engineered For Extra Listening Hours!



RCA Radio-Engineered Batteries for All Types of Sets...and a Complete Line of RCA Dry Batteries.

"RCA All The Way" means even more today—for the new RCA battery line is a volume builder that can't be beat! The battery line ties in perfectly with other RCA products you sell...whether it be tubes, parts, radio sets, or your own service.

Small Inventory— In RCA radio batteries you get a high-volume line of merchandise that can be handled on a small inventory. The RCA battery line has been streamlined—only 35 types enable you to replace batteries in 99% of all battery-operated sets, both portable and farm types.

Customer Acceptance— Radio-set owners respect the name RCA. They know it represents a quarter of a century of radio experience

National Advertising Keeps RCA Products Moving— Your RCA products—including batteries—benefit from all of RCA's continuing national advertising. Top-flight sales-promotion ideas are developed to keep your RCA products moving in a steady stream from factory to your customers. Counter displays, booklets, catalogs, and many other items, will be made available to you to help sell RCA batteries.

Get in touch with your RCA tube distributor *today*. Let him help you get on the RCA battery handwagon of profit.

Listen to
"THE RCA SHOW,"
Sunday, 4:30 P. M.,
EST, NBC Network



MAIL THIS COUPON TODAY!

Dear Mr. RCA Tube Distributor:

I'm interested in increasing my battery profits by handling the new line of RCA Radio-Engineered batteries. Please mail me all details of the RCA battery plan as soon as possible.

Name.....

Company.....

Address.....

City.....State.....

62-6736-107

RADIO CORPORATION OF AMERICA


TUBE DIVISION • HARRISON, N. J.

LEADS THE WAY... In Radio... Television... Tubes...
Phonographs... Records... Electronics

Everything FOR THE SERVICE DEALER

We have, ready for immediate delivery, a complete stock of tools, replacement parts, inter-communication systems, public address systems, test equipment . . . everything in radio equipment for the progressive service dealer. For big profit items . . . for quick delivery . . . place your order now with Leo.

6 TUBE AC-DC KIT

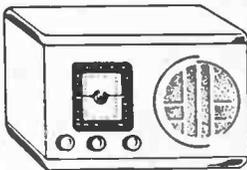

Complete, ready for assembly.

\$23.75

Cat. No. 7-691

A two-band, superheterodyne kit with all tubes, speaker, chassis, and all parts for easy assembly. Broadcast band from 540 to 1620 KC. Short wave from 5.7 to 18.3 MC. Cabinet, \$5.25.


WRL MULTITESTER

All purpose tester. Money back guarantee.

\$18.75


less leads

Cat. No. 16-439

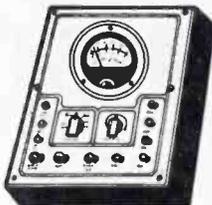

Handles AC DC Voltmeter, DC Milliammeter, high and low range Ohmmeter. 3" meter with sturdy D'Aronsva movement. Size 5½x8x3¼.

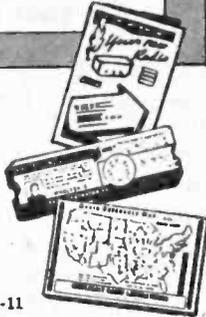Exclusive at WRL
Our latest flyer . . .
12 page V-J edition
of merchandise and
radio values. FREE.
Handy Tube-Base
Calculator25c
Giant Radio Reference
Map, 3½x4½ ft. . .15c



MAIL TODAY 8-11

Wholesale Radio Laboratory
744 West Broadway Council Bluffs, Iowa

Rush _____ WRL Multitesters. Cost, \$_____

Send _____ 6-tube AC DC Kits and cabinets. Cost, \$_____

I want a tube-calculator. 25c enclosed.

Ship me your radio map. 15c enclosed.

Send me your new V-J Flyer free.

Enclosed is \$_____; Balance C.O.D.

Name _____
Address _____
Town _____ State _____

I am an amateur; experimenter;
 service man.

We invite industrial inquiries for electronic equipment and devices of all kinds.

QUICK SERVICE FROM LEO
"same day" delivery service
from the heart of the nation
on anything in radio.
Order today.



**Wholesale
RADIO LABORATORIES**

SER-CUITS

(Continued from page 41)

electrolytic being a triple 20-mfd capacitor.

Detrola 568

A postwar a-c/dc 2-band receiver, Detrola, model 568, is shown in Fig. 3 (page 44). This model has an unusual bandswitch system. The signal grid of a 12SA7 is switched to either the short-wave or broadcast transformer. A supplementary 2.2-mmfd capacitor acts as a capacity coupling from antenna to grid, boosting the high-frequency end. In the circuit diagram the switch is shown in short-wave position. Here the antenna is connected to the short-wave primary through a .002-mfd capacitor, the primary circuit being completed through the bandswitch to B-. The same switch member also shorts the unused broadcast oscillator coil, completing the short-wave oscillator circuit to B-. A third section of the switch connects the 12SA7 cathode to a tap on the short-wave oscillator coil, or to the cathode tickler of the broadcast coil.

A 150-ohm resistor is connected in series with a 100-mmfd grid capacitor. A 5100-mmfd padder is in series with the oscillator coils. Bias for the 50L6 is supplied by an unbypassed 150-ohm resistor. The chassis is connected to B- through a 0.1-mfd capacitor and 220,000 ohms, in parallel.

Garod High-Fidelity Receiver

A prewar high-fidelity a-m receiver with several interesting design features is shown in Fig. 4 (page 44). This model has a variable bandwidth and separate low and high-frequency p-m speakers. The tuner and power amplifier are built on separate chassis, each with its own power supply. A 2-section 10-kc low-pass filter has been included. This may be switched into the audio amplifier between the tuner and power amplifier to minimize interference in the high-frequency audio range, including the 10-kc beat between adjacent channel carriers.

In the input is an iron-core antenna transformer, designed for a short antenna or a long antenna, in series with a .0001-mfd capacitor. A .006-mfd blocking capacitor prevents grounding the antenna. In the tuned secondary circuit is a 150-ohm series resistor. There is a similar 50-ohm unit in the tuned first detector circuit to broaden the response of these circuits for acceptance of an extended treble range.

A 6SA7 converter employs a 300-



STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACTS OF CONGRESS OF AUGUST 24, 1912, AND MARCH 3, 1933

OF SERVICE, published monthly at New York, N. Y., for October 1, 1945.
State of New York } ss.:
County of New York }

Before me, a Notary Public, in and for the State and county aforesaid, personally appeared B. S. Davis, who, having been duly sworn according to law, deposes and says that he is the Business Manager of SERVICE, and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management, etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, as amended by the Act of March 3, 1933, embodied in section 537, Postal Laws and Regulations, to wit: 1. That the names and addresses of the publisher, editor, managing editor, and business manager are: Publisher, Bryan Davis Publishing Co., Inc., 52 Vanderbilt Avenue, New York 17, N. Y.; Editor, Lewis Winner, New York, N. Y.; Managing Editor, F. Walen, Union City, N. J.; Business Manager, B. S. Davis, Ghent, N. Y.; 2. That the owners are: Bryan Davis Publishing Co., Inc., 52 Vanderbilt Avenue, New York 17, N. Y.; B. S. Davis, Ghent, N. Y.; J. C. Munn, Union City, Pa.; A. B. Goodenough, Port Chester, N. Y.; P. S. Weil, Great Neck, N. Y.; F. Walen, Union City, N. J.; G. Weil, Great Neck, N. Y.; L. Winner, New York, N. Y. 3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities, are: None. 4. That the two paragraphs next above, giving the names of the owners, stockholders and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company, but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock, and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.

(Signed) B. S. DAVIS, Business Manager.
Sworn to and subscribed before me, this 27th day of September, 1945.
(Seal) FRANKLIN B. GOOLD, Notary Public.
Commission expires March, 1948.

PROTECT YOUR HOME FROM
TUBERCULOSIS



BUY CHRISTMAS SEALS

ohm bias resistor without bypass and a decoupling filter of 5,000 ohms and 0.1 md.

Two 6SK7 i-f stages are coupled by special variable-selectivity transformers having a third winding, tapped to provide regeneration or degeneration. This is accomplished by connecting the tertiary to the secondary in a series-aiding or series-opposing manner. Series resistors of 25 or 39 ohms are also involved in obtaining the correct amount of selectivity in both transformers. The third i-f transformer is more conventional, although a tap is provided for the diodes. This would be expected to sharpen the tuning and thus be inconsistent with the rest of the amplifier. However, considerable damping is provided by parallel diodes which allows the passage of a wide band.

The r-f, converter and two i-f screens are tied to a common supply. The first three stages are supplied with avc bias. The r-f detection components are filtered out by a low-pass filter consisting of 50 mmfd, 100,000 ohms and another 50 mmfd. A ¼-megohm resistor is connected in series with the volume control to prevent overloading of the detector with the consequent distortion. The treble tone control is connected in parallel with the volume control. When the grounded arm is at the lower end of the control, a .001-mfd capacitor is connected in shunt with the volume control, cutting the highs. When the arm is at the top, the .001-mfd unit is in series with a ½-megohm resistor making the shunting ineffective. However a .05-mfd capacitor is connected across a 2,000-ohm cathode bias resistor which causes an increase in highs. This action may be called selective degeneration because the bypassing action of the .05-mfd unit is confined to the treble only, increasing the gain in proportion to the frequency. Low frequencies are not bypassed, so the full amount of degeneration is present.

The 6J5 first audio has a grid leak of only 150,000 ohms. A 6C8G is used for the second and third a-f stages, the gain being limited by interposed feedback from the second audio plate to the first audio cathode and by a 1,000-ohm second a-f bias resistor without bypass. There is also some attenuation in the bass tone control and the associated 15,000-ohm grid leak in the third a-f stage. This control consists of a 2-megohm potentiometer which acts as a variable shunt to a .001-mfd audio-coupling capacitor. The capacitor is so small

(Continued on page 44)



Which for You—
SCREWDRIVER
or SLIDE RULE?



Face the Facts:

You Must Train Now to Step Ahead of Competition Into A Good-Paying Job in Radio-Electronics

— or be left behind because you lack the understanding of new electronic techniques

CREI home-study courses are for professional radio-men only and this CREI message is for those who are not afraid to face the facts! The bars are down on radio-electronics progress! You are facing a completely new era in the radio-electronics world. The war-restricted curtains of secrecy have been pulled aside, revealing each day momentous, revolutionary applications of new radio-electronic principles and theories, and their complicated circuits, equipment, individual parts, etc.

No matter what your past radio-electronics experience has been, no matter what your training, you must start anew to add to your store of radio-electronics knowledge. You must keep pace with the new developments and ahead of competition if you expect to get ahead in this new world of radio-electronics—or even maintain your present position in the field.

How much do you know about U.H.F. Circuits, Cavity Resonators, Wave Guides, Klystrons, Magnetrons, and other tubes? All these revolve largely around U.H.F. applications. And here is where CREI training can help you. In our proved home study course, you learn not only how . . . but why! Easy-to-read-and-understand lessons are provided well in advance, and each student has his personal instructor who corrects, criticizes and offers suggestions on each lesson examination.

Let CREI train you now to trade that "screw-driver" for a slide rule. Do something about increasing your technical ability and advance to the better-paying radio jobs that offer security and opportunity. The facts are in the free booklet. Send for it today.



WRITE FOR FREE 36-PAGE BOOKLET

"Your Opportunity In the New World of Electronics"

If you have had professional or amateur radio experience and want to make more money, let us prove to you we have something you need to qualify for a better radio job. To help us intelligently answer your inquiry—**PLEASE STATE BRIEFLY YOUR BACKGROUND OF EXPERIENCE, EDUCATION AND PRESENT POSITION.**

CAPITOL RADIO ENGINEERING INSTITUTE

HOME STUDY COURSES IN PRACTICAL RADIO-ELECTRONICS
ENGINEERING FOR PROFESSIONAL SELF-IMPROVEMENT


Dept. S-11, 3224—16th Street, N. W., Washington 10, D. C.

Contractors to U. S. Navy — U. S. Coast Guard — Canadian Broadcasting Corp.
Producers of Well-trained Technical Radlomen for Industry.

MEMBER: NATIONAL COUNCIL OF TECHNICAL SCHOOLS

NOW AVAILABLE

FOR ALL CIVILIAN USE...

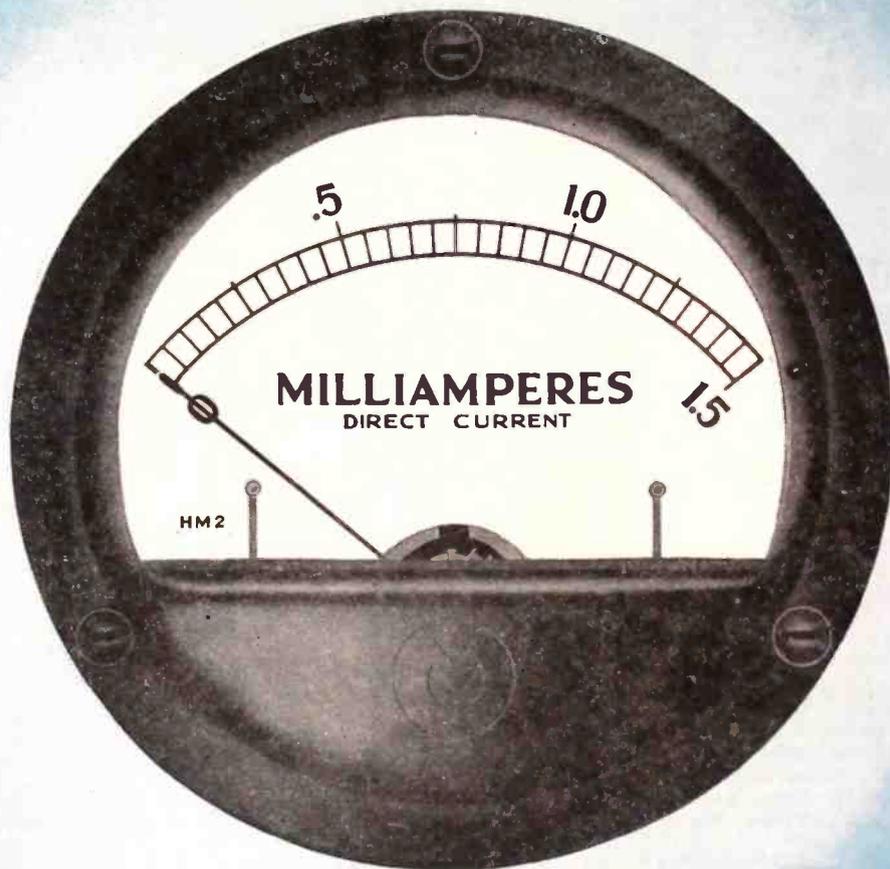

..... AT NO MORE COST THAN
STANDARD UNSEALED INSTRUMENTS

**Marion Glass-to-Metal Truly Hermetically Sealed
2 1/2" and 3 1/2" Electrical Indicating Instruments**

IMPROVED PRODUCT • APPEARANCE • PERFORMANCE • SALABILITY

Write for details of a Marion Franchise to our Jobber Sales Division




MARION ELECTRICAL INSTRUMENT CO.

MANCHESTER, NEW HAMPSHIRE

Jobber Sales Division: Electrical Instrument Distributing Co.
458 BROADWAY NEW YORK, N. Y.

EXPORT DIVISION • 458 BROADWAY - NEW YORK 13, N. Y., U. S. A. • CABLES: MORHANEX

Long and Satisfying Service

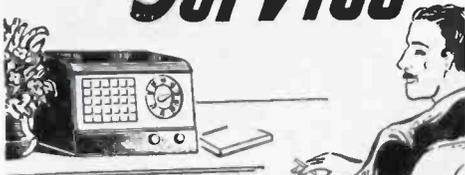


IT'S ENGINEERED WITH **HI-Q** COMPONENTS

Ask any service man with years of radio set repair experience and he'll tell you most sets "go bad" because of the failure of some insignificant component. That's why it's important to give more than ordinary consideration to the selection of capacitors. Engineer a unit with Hi-Q components and you have strengthened every link in the chain of satisfying performance. Hi-Q ceramic capacitors are individually tested at every step of their manufacture. They'll stand up under the severest conditions of temperature, humidity, vibration and shock. Send for samples and complete data.



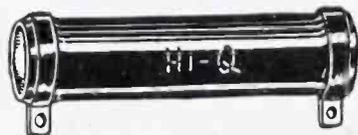CERAMIC CAPACITORS
CN type with parallel leads
CI type with axial leads



WIRE WOUND RESISTORS
Sizes and quantities available promptly to required specifications.



CHOKE COILS
Uniform in quality — rugged construction tested for performance.

ELECTRICAL REACTANCE CORPORATION
FRANKLINVILLE, N. Y.

HIGH FIDELITY AMPLIFIER

(See Front Cover)

A 25-WATT high-fidelity phono amplifier system, Magnavox A-3001C, has been diagrammed on this month's cover.

Pickup-to-Input Circuit

To effect a complete trace of the circuit, the pickup to the first-audio

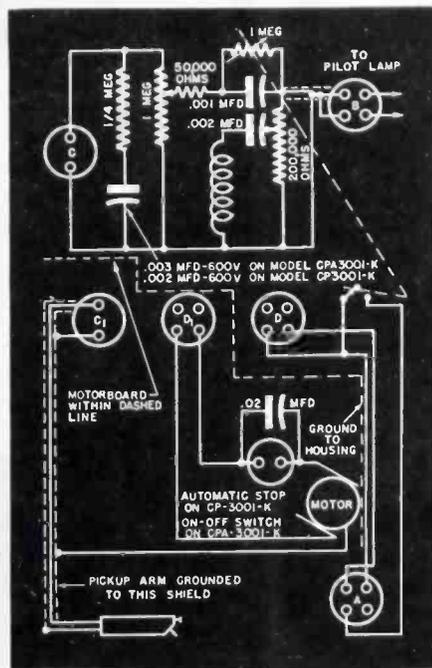


Fig. 1. Input plug system of amplifier, showing pickup and equalizer circuit.

input plug part of the system appears in a separate diagram, Fig. 1. A high-impedance pickup terminates in a 2-pin plug for easy servicing. An equalizer consisting of a .003-mfd capacitor in series with a 1/4-megohm resistor is connected directly across the pickup and a 1-megohm volume control. A 50,000-ohm resistor and bass tone control are located between the control arm and the plug feeding the input grid.

Tone Control Use

This tone control, which is attached to the on-off switch operates a .001-mfd audio coupling capacitor which favors the high frequencies. This is shunted by a 1-megohm control which brings up the bass notes as the resistance is decreased.

Reactance Ratios

Analyzing the actual capacitor-reactance ratios and their effect on bass control we find that a 1-mfd capacitor has a reactance of about 2,600 ohms at 60 cycles and 1,300 ohms at about 120 cycles, which is usually in the vicinity of the lowest bass note reproduced. So a .001-mfd capacitor has a reactance of about 1.3 megohms at 120 cycles and about 32,000 ohms at 4,800

SPEED UP REPAIRS WITH THESE G-C AIDS!



FREE STEEL CABINET



G-C Dial Drive Cables

G-C has a complete line of Dial Drive replacement cables. Available by the spool for prompt servicing of all sets. Every Serviceman should have a complete assortment. Best quality—extra strength. Preferred by Radio Men everywhere.

G-C Dial Belt Kits

Every Serviceman needs a G-C Dial Belt Kit. Save money—be ready for that repair job. Finest woven fabric replacements. Easy to install—no stretch—no adjustments. Supplied in kits of 25, 50, 100, 200 or 300 Belts in sturdy metal box with slide-in drawer. Free Belt Guide and measuring device.

G-C Radio Service Cement



The best Cement for Speaker and Radio Work. Especially suitable for cementing replacement cones and repairing rattling and torn cones. Also used on glass, to seal adjustments, hold wires in place, etc. Dependable, vibration proof, waterproof and fast drying.

Write for New G-C Catalog No. 146 and G-C Dial Belt and Service Book

Immediate Delivery on all G-C Products

Order From Your Radio Parts Jobber
ALWAYS ASK FOR G-C PRODUCTS



GENERAL CEMENT MFG. CO.
ROCKFORD, ILLINOIS

cles which is around the highest
 te normally reproduced, a difference
 40 to 1. The 1-megohm shunt helps
 e bass along but it has little effect on
 e treble. As the resistance is de-
 ceased, we note that the bass is in-
 creased considerably while the treble
 increased only slightly.

Treble Booster

A treble-boosting tone control is
 so included. More correctly, per-
 aps, this control should be termed a
 ss-reducing control as it shunts a
 oke coil across the line which by-
 sses the low frequencies but allows
 ost of the highs to go by unmolested.
 .002-mfd capacitor in series with
 e choke makes the control non-
 ear, particularly near the resonant
 equency of the choke and capacitor.

Hum and Decoupling Filter

A 2-megohm grid leak establishes
 e input impedance of the amplifier
 2 megohms for bass frequencies and
 bit less than 2 megohms for the
 reble. The 6C5 first audio is biased by
 000 ohms and a 20-mfd capacitor.
 ere we also have a separate R-C
 um and decoupling filter. Coupling
 p the power stage is completed by a
 0,000-ohm plate resistor and a center-
 apped grid choke. An equalizer, .02-
 pfd and 7,500 ohms, is in series with
 he blocking capacitor.

External Speakers

Two output impedance taps, 1.12
 nd 2.25 ohms, and an extra plug is
 rovided for an external speaker. The
 oice coils are arranged in parallel
 with the fields in series, excitation be-
 ng provided by the current in the
 5L6 screens and 6C5 plate. A .002-
 nfd 1,200-volt bypass capacitor is
 onnected from plate to plate in the
 output stage. The entire record player
 draws an average of 134 watts from
 he power line.

FIRST G.E. SETS ON BIG MO



Captain S. S. Murray, U.S.S. Missouri skipper,
 and Commander A. F. Spring, executive officer,
 with the first home G.E. sets produced. Presen-
 tation was made by Dr. W. R. G. Baker (left),
 G.E. vice president, and J. L. Busey, G.E. Sup-
 ply Corp. president.

The Line That Reaches 'Round the World

Depend upon

AMPHENOL

Quality

With a proven background of honorable service on far-
 flung battlefronts around the world, Amphenol com-
 ponents—greatly improved by wartime experience and
 augmented in number, style and type—are now avail-
 able to normal markets. Simplifying both buying and
 selling, this wider selection of high quality, tested items
 can be procured from one manufacturer. To know these
 popular Amphenol products better—write today for
 the new Condensed Catalog No. 72.

AMERICAN PHENOLIC CORPORATION
 CHICAGO 50, ILLINOIS
 In Canada • Amphenol Limited • Toronto

U.H.F. Cables and Connectors • Conduit • Cable Assemblies
 Connectors (A-N, U.H.F., British) • Radio Parts • Plastics for Industry

New!

Series 200


A RELAY BY GUARDIAN

with *Interchangeable Coils*

BUILT IN TWO PARTS

★ Two basic parts—a coil assembly and a contact assembly—comprise this simple, yet versatile relay. The coil assembly consists of the coil and field piece. The contact assembly consists of switch blades, armature, return spring, and mounting bracket. The coil and contact assembly are easily aligned by two locator pins on the back end of the contact assembly which fit into two holes on the coil assembly. They are then rigidly held together with the two screws and lock washers. Assembly takes only a few seconds and requires no adjustment on factory built units.

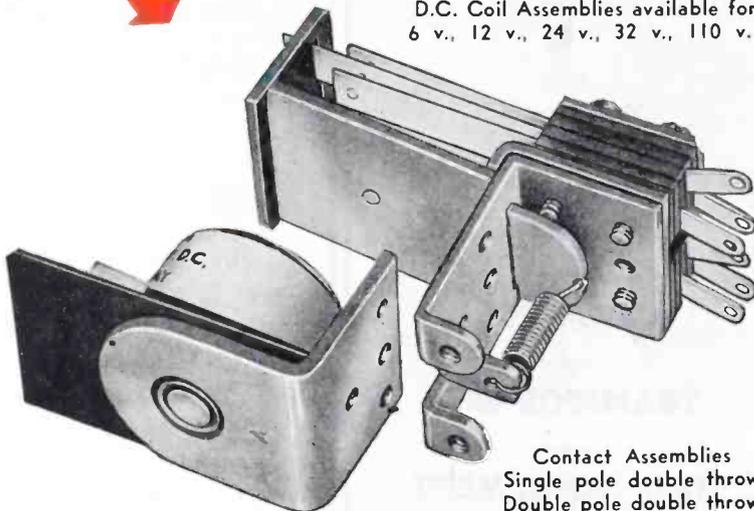A.C. Coil Assemblies available for 6 v., 12 v., 24 v., 115 v.
D.C. Coil Assemblies available for 6 v., 12 v., 24 v., 32 v., 110 v.



Contact Assemblies
Single pole double throw
Double pole double throw

SERIES 200 RELAY

On Sale at Your Nearest Jobber NOW!

See it today! . . . this amazing new relay with interchangeable coils. See how you can operate it on any of nine different a-c or d-c voltages—simply by changing the coil. Ideal for experimenters, inventors, engineers.



TWO CONTACT ASSEMBLIES

The Series 200 is available with a single pole double throw, or a double pole double throw contact assembly. In addition, a set of Series 200 Contact Switch Parts, which you can buy separately, enables you to build dozens of other combinations. Instructions in each box.

NINE COIL ASSEMBLIES

Four a-c coils and five d-c coils are available. Interchangeability of coils enables you to operate the Series 200 relay on one voltage or current and change it over to operate on another type simply by changing coils.



Your jobber has this sensational new relay on sale now. Ask him about it. Or write for descriptive bulletin.

GUARDIAN ELECTRIC

1617-P W. WALNUT STREET

CHICAGO 12, ILLINOIS

A COMPLETE LINE OF RELAYS SERVING AMERICAN INDUSTRY

WHOLESALE

suppliers of radio
and electronic parts

**HIGHEST QUALITY—
LOWEST PRICES—
FASTEST SERVICE**

Complete supplies
available for
SERVICEMEN

We stock in
large quantities

TUBES

SPEAKERS

TRANSFORMERS

TEST EQUIPMENT

**ELECTROLYTIC
CONDENSERS**

**REPLACEMENT
WOOD CABINETS**

And 1001 other
essential parts

Write for **FREE**
descriptive catalog.

**RADIO DEALERS
SUPPLY COMPANY**

135 LIBERTY ST.
NEW YORK 6, N. Y.

CRYSTAL FILTERS

(Continued from page 23)


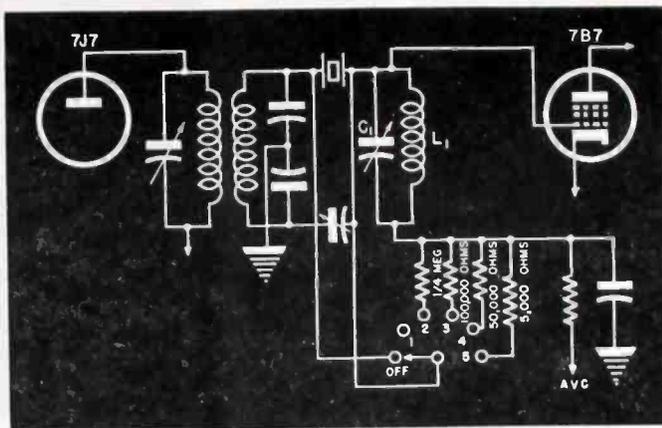


Fig. 5. The variable selectivity system of the RME 41-43. Variable selectivity is accomplished by varying the size of the resistor across L_1C_1 , the larger the value of resistor the greater the selectivity.

Fig. 6. Hammarlund Super-Pro variable selectivity system. Here, the selectivity is varied by inserting resistance in series with L_1C_1 . Increasing the value of resistance improves the selectivity by increasing the effectiveness of the crystal.

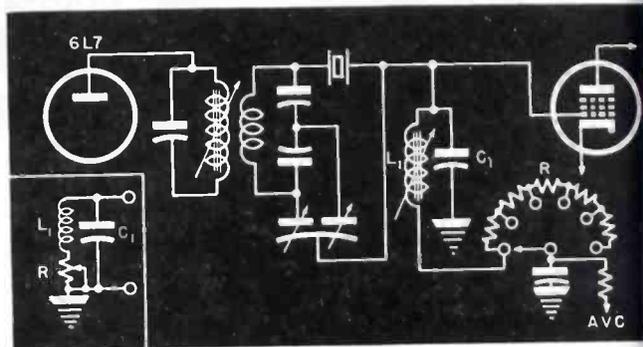

detunes the circuit, and permits the crystal to exert its greatest influence on circuit Q , or sharpness of resonance.

RME 41-43

Fig. 5 shows the variable-selective circuit used in the RME model 41-43. The tuned circuit here is on the crystal output side instead of the input. The effective resistance of the tuned circuit represented by C_1 and L_1 in series with the crystal is varied by shunting it with various size resistors, in very much the same manner as is used to broaden the response of i-f transformers used in f-m receivers. The lower the value of the shunting resistor, the greater will be the effectiveness of the

crystal and the resultant selectivity.

Hammarlund Super-Pro

In Fig. 6 we have the method applied in the Hammarlund Super-Pro. Here again, resistance is used to increase the effectiveness of a tuned circuit in series with a crystal filter. However, the resistance is used differently than for the circuit shown in Fig. 5. The Q of a coil is a function of its reactance over its resistance, $Q = X/R$. Since the resistance is introduced into the tuned circuit so that it is in series with L_1 , and C_1 is across both the resistance and the inductance, the effective resistance of the circuit as represented by L_1C_1R is reduced and C_1 then acts as a bypass capacitor. Thus the effectiveness of the crystal is increased.

Get **EVERYTHING!**

Standardize on

STANCOR

Transformers

Call your nearest Stancor Jobber...
or write us for his address

STANDARD TRANSFORMER CORPORATION
1500 N. HALSTED STREET • CHICAGO



CENTERING CONES

(Continued from page 16)

lost. Every effort is made by the manufacturer to build his loudspeaker so it will stand up not only for normal operation, but that it has a safety factor which will permit some limited amount of abuse or abnormal operation without affecting the performance.

When confronted with a rubbing voice coil the Service-Man can do one of two things.

First, he can replace the whole speaker with a new one and second, he can try to repair the one that is damaged.

In these days when production is so high the demand so much, there is little chance in trying to replace the unit when the chances of getting a new speaker are slim indeed. Therefore, the Service-Man usually tries to repair it.

A new development, the *Adjust-A-Coil* unit, developed by Quam-Nichols, is an effective solution to the rubbing voice-coil problem. In this unit, the voice coil, instead of being permanently attached or fastened to the housing, is kept in position with a pressure or clamping ring which is in turn held down by two clamping screws. This construction is illustrated at A in Figure 1, the inset showing a closeup of the pressure ring, which is underneath, at B, and the spider which is in turn held down by two clamping screws. The voice coil is designated at D.

Loosening the screws holding the pressure ring (A in the illustration) will permit a small amount of movement of the spider in a lateral manner which will allow the voice-coil to be centered around the pole-piece and within the gap.

It is to be noted that the screws holding the clamping ring are so positioned that it will be often unnecessary for the Service-Man to remove the loudspeaker cabinet to re-center the voice coil.

In conditions of severe rubbing voice coils, a better job can be done by moving the speaker from the cabinet; when in either instance, no audio signal generator is necessary, and only the radio (or public address system) or voice signals are required for testing and maintenance.

The repair of a speaker with this new unit is quite simple. Before attempting to re-center the voice coil, one first determines on which side the voice coil is rubbing by pushing it up and down in the gap. Then it is necessary to loosen the clamping ring screw nearest the point of the rubbing is found. Using the screwdriver, the voice coil is gently pulled toward the loosened clamping screw. The screw is then tightened and a check made to see if the voice coil now rides freely.

Caution should be used at this time not to be too violent with the adjustment because of the possibility of breaking the juncture of the voice coil and the cone neck.

If this operation does not correct the rubbing voice coil, another method will have to be employed. One must first remove the felt dust cap over the voice coil by saturating it with lacquer or thinner, allowing it to soak a few minutes before picking it off. Then strips of ordinary wrapping paper approximately 5/16" wide by 1 1/2" long should be cut.

The clamping ring screws should be loosened until the clamping ring is free, then the wrapping paper shims are inserted.

(Continued on page 52)



CONDENSER TESTER

Model 650-A

RANGE—.00001 to 1,000 mfd.

Automatic Push Button Controlled—Amazing in speed and simplicity of use. Capacity readings almost instantaneous! Leakage test by just pressing a button.

The Model 650 is a modern, accurate and complete instrument for detecting faulty condensers—ELECTROLYTIC, PAPER or MICA.

Scale is glass enclosed and is equipped with **SCALE EXPANDER** indicating pointer—doubles effective scale length.

Measures all values direct reading in Microfarads.

Ranges

.1 to 100 mfd. .001 to .1 mfd.
.00001 to .001 mfd. 50 to 1000 mfd.

Measures power factor on direct reading dial. Power Factor range calibrated from 0 to 60%.

Complete selection of test voltage. 20 volts to 500 volts.

Electron ray tube indicates exact balance or shows if leakage is present.

Instantaneous leakage indication—No guess-work with this modern tester. Has

built-in amplifier stage which responds to slightest leakage, if present.

Dimensions—8 1/2" x 8 1/2" x 6"—Unit welded steel, finished in grey morocco. Equipped with removable hinged metal lid and completely equipped with tubes, test leads and ready to operate.



The Jackson "Service Lab"

When steel again becomes plentiful, standard size Jackson instruments will be available conveniently assembled in a complete testing unit.

BUY WAR BONDS



AND STAMPS TODAY

JACKSON

Fine Electrical Testing Instruments

JACKSON ELECTRICAL INSTRUMENT COMPANY, DAYTON, OHIO

SERVICE, NOVEMBER, 1945 • 51

BOOKS THAT TELL YOU HOW

3 new books that give you the basic knowledge for successful work in post-war radio.

1. PRINCIPLES OF RADIO FOR OPERATORS



By Atherton. Clear instruction on the operating principles of all parts of radio, including antennas, with full details about equipment and procedures for construction and operation. Many visual aids to help the beginner. \$3.75.

2. INTRODUCTION TO ELECTRONICS



By Hudson. A simply written but scientifically reliable explanation of the theory, construction, and uses of the various electron tubes and other electronic devices, showing their enormous potentialities for future developments. \$3.

3. INTRODUCTION TO PRACTICAL RADIO



By Tucker. An outstandingly clear, thorough training in the basic principles of radio circuits and their components, with full explanations of the necessary mathematics at the points where it is used. \$3.

FREE EXAMINATION

By using the coupon below you can procure copies of these books to look over for 7 days without cost or obligation on your part. Send for your copies today.

Special note to Dealers

YOU CAN MAKE A DOUBLE PROFIT THROUGH HANDLING BOOKS

1. Books bring you better buyers. They stimulate the interest and knowledge that makes steady customers. The more your customers learn about radio the more they will buy from you.

2. Books are a profitable stock item. Our trade discounts allow you a good profit on each sale. Our wide promotion insures their sale without effort on your part.

Let these books be salesmen for you. Let them make you an easy profit. By returning the coupon below you can get copies for your book counter at the full dealer's discount. Cuts and copy for your catalog listings are also available. Write to our Technical Book Dept. for information.

The Macmillan Co., 60 5th Ave., New York 11

Please fill my order for the books checked by number below, with the understanding that if I return them within 7 days my bill will be cancelled.

Please fill my order, at dealer's discount, for _____ copies of the books checked.

SIGNED _____

ADDRESS _____

1 2 3


C-R OSCILLOGRAPHS

(Continued from page 37)

form depending on the settings of the linear time-base oscillator controls. In any event, the characteristic sine wave form of the a-c supply frequency waveform is evident in the pattern.

Manipulation of the linear time base coarse and vernier sweep frequency controls permits the reduction of the pattern written on the screen to either a single a-c wave pattern, or to a pattern containing a number of similar a-c cycle forms, whichever may be desired. In either case, the pattern will appear to be in motion, and complete synchronization of the sweep frequency with that of the a-c supply source will be found difficult. If, however, the test signal terminal is connected to the linear time-base synchronizing voltage input terminal *EXT*, synchronization control selector switch, *S_s*, turned to the *EXT* position, and the synchronization control potentiometer advanced slightly, the written wave pattern will stabilize completely. The wave pattern being written from the positive zero voltage inflection due to the phase-shift will be effected by the positioning capacitor *C₂₃*.

MINIATURE POCKET SETS

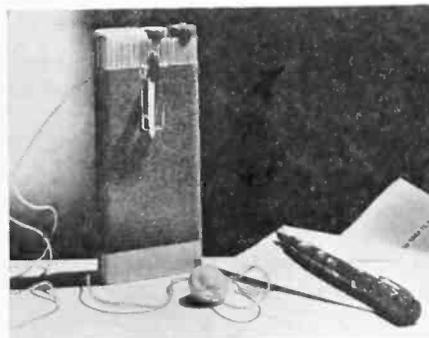

Five-tube pocket receivers produced by Belmont, using Raytheon sub-miniature tubes. Case is 3" wide, 1/4" thick and 6 1/4" high. Weighs 10 ounces, including batteries. Circuit is super-heterodyne. Cases will be supplied in solid gold, sterling silver, morocco, suede, etc.



RECENTERING CONES

(Continued from page 51)

serted between the voice coil and pole-piece (the inside of the voice coil). The three strips are not used one on top of the other, but merely to assure that at least one thickness of the strip circumscribes the pole-piece entirely. The final step the clamping ring screw should be tightened a little at a time, tightening first one, then the other, gradually and alternately so as to bring clamping action to bear on the ring evenly all around.

This should result in a perfectly centered voice coil. The wrapping papers can then be removed, and the dust cap glued back on with lacquer cement.

I-F AMPLIFIERS

(Continued from page 48)

third transformer which feeds the limiter stage is a conventional detuned job.

Ward 62-319, 329, 409, 419

Another receiver using sharp-tuning (i-f of 465 kc) is shown in Fig. 10, Ward 62-319, 329, 409, 419. The input transformer has a switchable tertiary winding similar to that shown in Fig. 7. The output transformer feeding the 6H6 detector is standard.

RADOLEK

Radio-Electronic Service Parts



Large stocks assure the finest and complete selections of all available at lowest prevailing prices. Those active buyers depend on us for the Radio repair and replacement requirements. Because we understand service parts every order is expedited for delivery double quick time. Everything is planned for convenience and satisfaction our customers. You will find it profitable to make Radolek your buying headquarters.

FREE BUYING GUIDE

Because of existing conditions we will send our customers right up to the minute and valuable merchandise by releasing supplements frequently instead of sending our Big Profit Guide once a year. Send the coupon now to get these Free Buying Guide Supplements as they are issued.


FAST SERVICE!

RADOLEK CO., Dept. S-108
601 W. Randolph St., Chicago 6, Ill.

Please send FREE Buying Guide Supplements

NAME _____
ADDRESS _____

ORDER FROM RADOLEK

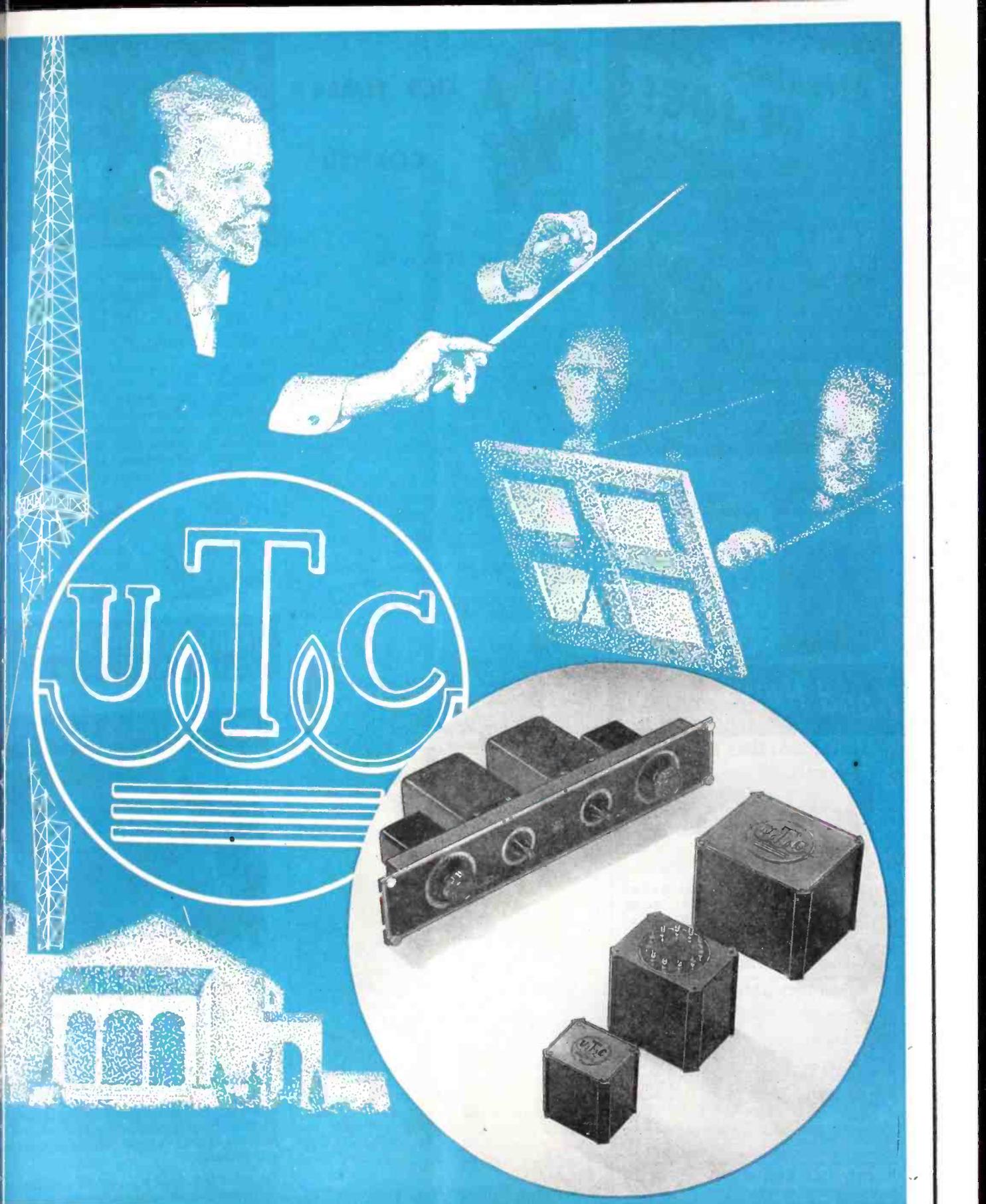

BROADCAST STATION COMPONENTS

United Transformer Corp.

150 VARICK STREET

NEW YORK 13, N. Y.

EXPORT DIVISION: 13 EAST 40th STREET, NEW YORK 16, N. Y.

CABLES: "ARLAB"



ALL PLANTS

Attention GI JOE!

Here's Your Opportunity to be First to Start Your Own RADIO SERVICE SHOP

Complete Starting-in-Business
Package Stocks of

TEST EQUIPMENT
TUBES, PARTS, TOOLS **\$350 up**

Act quickly! Meet the pent up demand for radio service. Turn your special service training into a profitable business of your own. No fuss. No worry. Here's everything you need—\$350 up. Details upon request! Write, wire or phone



TRIPLETT Volt-Ohm-Milliammeter

A. C.-D. C. Volts
0-10-50-250-1000-5000
at 1000 ohms per volt.
D. C. Milliamperes
0-10-100-500
Ohms 0-300-250,000
Case Black molded
3 1/4" x 5 1/8" x 2 1/8"

\$16.00 net

Good News! ALL
PRIORITIES LIFTED

HALLICRAFTERS SX-28A



\$223

SUPER DEFIANT	SX25	\$94.50
SKY CHAMPION	S20R	60.00
SKYRIDER MARINE	S22R	74.50
SKY RANGER	S39	110.00
ECHOPHONE	EC1A	29.50

ORDERS FILLED AS RECEIVED!!!

MASCO AMPLIFIERS



17 Watt with Phono-top	42.30
25 Watt with Phono-top	52.20
35 Watt with Record-changer	89.10

Complete with tubes.

17 Watt	30.30
25 Watt	42.60
35 Watt	54.60
50 Watt	70.50

PHILCO BEAM OF LIGHT

Selenium Cell only, no holder **1.80**

20% deposit required on all C.O.D. orders. 2% transportation allowance on orders of \$25.00 or more accompanied by payment in full.

Write for
FREE CATALOG

**RADIO SUPPLY &
ENGINEERING CO., Inc.**
126 SELDEN AVE. DETROIT 1, MICH.



OLD TIMER'S CORNER

by **SERVICER**

WE had quite an unusual session at an end-of-the-day get-together some weeks ago, a session that provided many unusually interesting and useful facts.

It all began when Roy walked in quite pleased with himself.

"What's with you, Roy?" I asked. "You sure look spirited."

"Well, fellows," said Roy with a grin, "I have just made a swell contact."

"What kind?" we asked.

"With a manufacturer of capacitors," answered Roy. "With my plans I will be able to cut out everybody except the manufacturer. No more distributor, and no more company representative for me. I'll deal right with the capacitor maker, direct."

"What will that mean in dollars and cents?" we asked him.

"Well, I should be able to buy at better prices. Then deliveries will be faster, and also I'll have a wider choice than any of you have been able to get from John's Radio Company, the distributor up here. That in itself is worth the deal to me. But best of all I will be buying at rock-bottom, manufacturer's prices!"

"I think you're dead wrong, Roy," said Bill.

Bill's Opinion

We picked up our ears. Bill was one of the older crowd who usually did not have anything much to say. He and his type just went ahead year in and year out, not making a very big splash in the waters of radio servicing business, but at the same time syphoning off a fair share of profits and keeping themselves high in the opinions of the community. Bill was not only conservative, but he was also highly respected for his ethics, business acumen and community pride. He was no world-winner, but his hard-headedness and carefully thought out plans often wrung a lot of silent (and sometimes not so silent) acclaim from our gang.

So when Bill fired his opinion at Roy, we were quite surprised.

"You see, boys, Roy thinks that he has made a world-winning deal by cutting out the distributor! Well, instead he has just done himself a great disservice! Sure, this particular manufacturer probably now has almost everything in stock that Roy could want. And he's anxious to get it out. So he'll do almost anything to see that Roy gets what he wants. But wait until this man-

For Soldering in
Tight Places . . .

DRAKE

No. 400 Soldering Iron

Smallest Industrial Iron
Ever Designed

60 Watts — 1/4 in. Tip
Only 9 in. long. Wt. only 8 oz.

This mighty mite is backed by DRAKE's 25 years of soldering iron manufacturing experience. The high quality and long-service of DRAKE Soldering Irons have made them outstanding favorites with all types of radio men everywhere. The DRAKE No. 400 is an outstanding value at




Only **\$4.50**
List

Drake Has an Iron
for Every Purpose.
Ask Your Radio
Parts Jobber

DRAKE ELECTRIC WORKS, INC.

3656 LINCOLN AVE. CHICAGO 13, ILL.

AN ENTIRELY NEW LINE

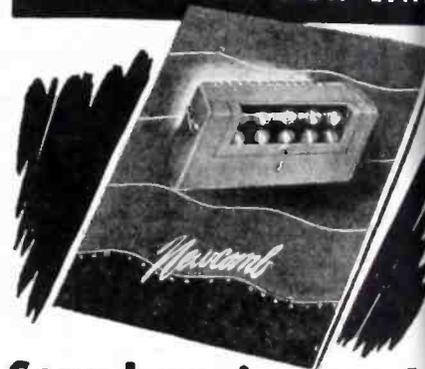

Sound equipment by
NEWCOMB

Our newest amplifiers offer greater excellence in sound reproduction than ever before available to the public address field. Designed by an organization devoted exclusively for seven years to the perfection of sound equipment, they embody all the benefits of today's most advanced electronic achievements.

Send for the catalog . . . you'll find no other amplifier has so many advantages.

THE SOUND OF QUALITY

Newcomb

AUDIO PRODUCTS CO.
MANUFACTURERS

DEPT. E. 2815 S. HILL STREET
LOS ANGELES 7, CALIFORNIA

er—and I'm sure that he is not the old line men—gets going. He gave a big business some day. And he will recognize that it doesn't have Roy's orders lying for, say, ten 25-mfd 25-volt electro's, and two dozen .05 mfd's and a couple ten half mikes at 450 volts. He is to tell his production men to set aside until he gets into those runs for a set manufacturer. Thus of the capacitors Roy wants, will be only run through with the manufacturer. Now the .05 mfd's that are made for the set manufacturer are very different in size than the type ordered before, and so Roy gets the size which may or may not fit. Also price may be different each time, due to change in specifications.

Replacement Problems

and that isn't all. Suppose that Roy ordered some faulty capacitors. Can he get immediate replacements? No, not, for at that very time the type he ordered is out of stock, and another size is being run through, a size of no use to him.

So poor Roy will have to wait until the manufacturer runs through the kind Roy wants before he can get his replacements. Now since Roy has been dealing with the manufacturer directly, he not only has lost contact with the local distributor, but he has also encouraged that worthy to discontinue him. As a result, Roy can't get his capacitors from the distributor.

So he must go out and buy them himself, or hope that one of you—or me—will help him out for the time being. Normally, we would be more than willing to help out a fellow Service Man—especially Roy, because we all like to help. But business is business, and we don't like to have the returned capacitors be similar to those we gave Roy. We are not interested in the few cents that the capacitors cost. What we are interested in is some of Roy's units when his next shipment gets in. But Roy isn't going to receive the same standard parts we have been using, even when his shipment arrives. And we are not sure of exactly he is going to get. So don't let him have any of ours, and he will find himself in quite a spot!

Virtues of Distributors

Now, if Roy trades with the local distributor he'll get what he needs right from the distributor's stock. The distributor pools all of his orders and sends them in to his standard manufacturers as they make, taking in all the Service Men accounts of the distributor, and order and quite a run. If something goes bad with the units, the manufacturer cannot afford to ignore the distributor, and so he makes it good. The distributor knows that and will replace defective units for Roy on sight. Then, the distributor is a local man. Every time Roy buys from him and pays his bill promptly, he establishes a better relationship. That may come in handy when time rolls around and Roy needs a reference. Some of the boys just think much of references from an out-of-the-state place where people don't know each other except via the postage stamp route.

33 well overlapped ranges

plus long-life dependability!



WESTON

(Model 665 Type 1)

VOLT-OHM-MILLIAMMETER

Its compactness, versatility and rugged dependability make Model 665 the ideal instrument for use in the field, or in the shop . . . whether servicing communications equipment, testing electrical components in production, or research or maintenance work. Provides 33 AC and DC voltage, DC current, and resistance ranges . . . with simplified switching arrangement for rapid operation. Built to WESTON standards to assure dependable measurement accuracy throughout the years. Full details on request. Weston Electrical Instrument Corporation, 605 Frelinghuysen Avenue, Newark 5, N. J.

WESTON Instruments

"So if you want some sound advice, play ball with your local distributor. The prices may seem a bit higher than those a manufacturer selling direct may offer. But when the smoke clears away, you are getting so very much more for your dollar in the form of reputation, good will and fine service, that in reality the costs are cheaper."

No Sale

"I think you have something there, Bill," said Roy. And from the way he spoke, I guess that a certain manufacturer, who sells capacitors directly to the radio Service Man, had just lost a fairly nice account.

POSTWAR RECEIVER



Receiver of the future shown at a recent postwar display by the Hallicrafters, Chicago.



Plug in METAL TUBE RESISTORS

★ To facilitate the servicing of AC-DC sets equipped with plug-in metal-tube resistors, Clarostat offers 10 Universal Types which replace 90% or better of the original numbers.

The Clarostat Universal Type operates within voltage ranges specified on tube, regardless of what pilot current is drawn or of any pilot light combination. Operates regardless of burnt-out pilot lights, and well within the .3 ampere range required for tube filaments. Operates efficiently regardless of line-voltage variation.

★ Ask Your Jobber . . .

Ask for these Clarostat plug-in metal tube resistors. Type MT. Ask for other servicing aids—controls, resistors, attenuators, etc. Ask for latest catalog—or write us direct.



CLAROSTAT MFG. CO., Inc. • 285-7 N. 6th St., Brooklyn, N. Y.



RAYTHEON BONDED SERVICE MAN PROGRAM

A Bonded Electronic Technician Program to improve standards of practice among Service Men and provide work guarantees, has been announced by the Raytheon Manufacturing Company. The program provides for the bonding of Service Men through the facilities of Raytheon distributors, Raytheon and a bonding group.

According to Arthur E. Akeroyd, distributor sales manager, the program will assist the Service Man in building a solid foundation for postwar activities.


It will offer deserving newcomers such as returning veterans, the opportunity to establish themselves in business, without being handicapped by the questionable practices of some widely publicized repairmen.

Mr. Akeroyd said that it was felt that the plan should be based on guarantees to the much maligned Service Man as well as the customer. Every radio shop is entitled to a legitimate profit, he said. Thus with widely divergent costs under different conditions and in different locations, any bonding program must not interfere with the established business policies of the ethical shop. By the same token, the program must also recognize the fact that the majority of Service Men are honest. The bond provided by this program will assure the public of the Service Man's honesty and integrity, said Mr. Akeroyd.

To qualify as a Raytheon Bonded Electronic Technician, a Service Man will have to meet certain qualifications of experience, reputation and ability, and also state that he has and will use adequate equipment to do skilled service work efficiently.

The Service Man's application will have to be approved by his Raytheon distributor, Raytheon and the bonding company. When accepted by all parties, he will become bonded for the period of one year by the Western National Indemnity Company of the Firemen's Fund Group. The bond states that the Service Man agrees to guarantee complete satisfaction

POSTWAR ANTENNAS

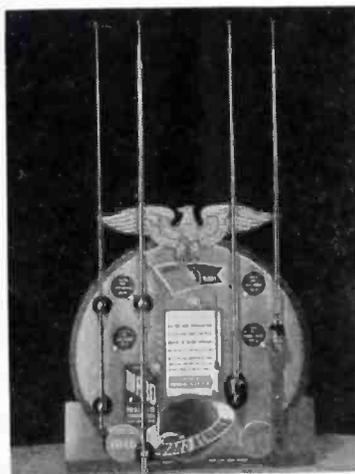

Ward store display featuring four postwar antennas. Highlights of the antennas are said to be H-Q low-loss detachable polyethylene lead with silver-to-silver contact; one man installation and fluid type anti-rattle construction.

MUELLER



CLIPS

For Quick Temporary Connections

- Made in 10 sizes—from the tiny wee-pee-wee to the 300 ampere Big Brute.
- Offered in both steel and solid copper.
- Red and black rubber insulators to fit each size.
- A complete line with

A CLIP FOR EVERY PURPOSE

Send for free samples and catalog 810

Mueller Electric Co.

1565 E. 31st St. - Cleveland, Ohio

MONEY-SAVING SPECIALS

Immediate Delivery. Orders filled same day received.



AIRPLANE CODE KEY \$2.25

Knee type. Strong spring holds securely. Black enamel and brass finish. Complete with plug and cord. Limited supply. Order now. Only—\$2.25

DESK TYPE KEY—\$1.69

Cadmium plated. A good practice key for amateurs.



PL-55 PLUG—34¢

A high grade, dependable plug.

G. E. AMMETER

General Electric Thermocouple R.F. type—only \$4.95.

NEW ITEMS DAILY
Tubes . . . test equipment
. . . meters . . . cords and
cables . . . condensers . . .
resistors . . . switches . . .
speakers.



Write for bulletin listing hundreds of items

Lifetime

SOUND EQUIP. CO., Dept. 65

911-913 JEFFERSON AVE., TOLEDO 2, OHIO

every radio repair job for 90 days, outlines a code of ethics that he expects to observe in the conduct of his business.

Mr. Akeroyd said that the requirements for certification have been drawn up so that they parallel the now generally accepted practices and standards of the competent qualified Service Man. The requirements do not represent the ideas of any single group, but rather the suggestions and opinions of hundreds of Service Men. Adequate provision is said to be provided to prevent the exclusion of any Service Men from this program, without prejudice, in the event that they feel rejection is not justified.



A. E. Akeroyd

GRENBY BUYS CARDWELL

Grenby Mfg. Co., Plainville, Conn., has acquired full control of The Allen Cardwell Mfg. Corp., Brooklyn, N. Y.

W. L. Gray, president of Grenby, has been elected chairman of the Cardwell board. He will handle the sales and development engineering departments of Cardwell while the manufacturing departments of Cardwell will continue to operate from their present location at 81 Prospect St. The manufacturing division has been moved to Plainville, Conn.

John H. Soby, vice president and director of Grenby, has been elected president of Cardwell, following the retirement of Mr. Cardwell. Joseph K. Fabel will continue to serve as vice president and sales manager of the Cardwell development and engineering division. Ray Brehouse will also continue as Cardwell sales manager.



C. A. Gray

CAPACITOR COLOR CODE CARDS

Color code charts and cards for small capacitors with RMA six-dot color code and three-dot color code as well as Army-Navy standards, have been prepared. (Continued on page 58)

N. U. DISTRIBUTOR ON RANCH



Olsen, National Union distributor in San Antonio, with Jack Clune, N.U. sales manager, on the Olsen ranch.

Wait for these new


HICKOK

Radio Service Instruments



Model 532
Tube Tester

If It Isn't A Hickok Indicating
Micromhos It's Not
Dynamic Mutual Conductance

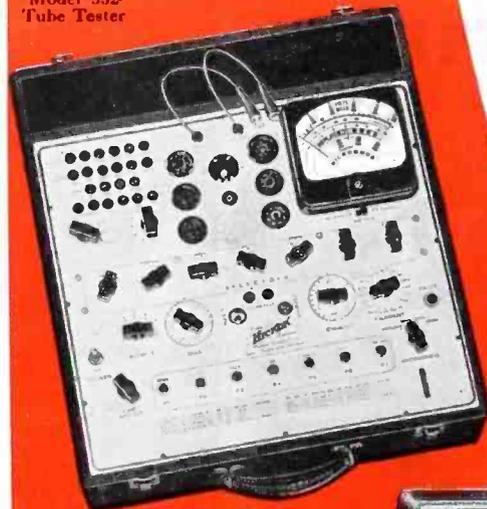

Model 534
All Purpose Tube and Set Tester

Your patience in waiting for these new 1946 HICKOK models will be richly rewarded for these new HICKOK tube and set testers make still closer tests, with finer accuracy, rejecting tubes that might get by with an ordinary tester.

Now you have 7 selector switches instead of 2. That aims to prevent obsolescence. Isn't that worth waiting for?

What's more, Dynamic Mutual Conductance, indicated in Micromhos, is a duplicate of the manufacturer's method of checking when he makes the tubes. Remember, if it isn't a HICKOK Indicating Micromhos, it isn't Dynamic Mutual Conductance.

The new Electronic Volt-Ohm-Capacity Milliammeter Model 203 reads as low as 1.0 mmf and up. It will measure at frequencies to over 10 mc with no frequency error and the ohm meter will measure up to 10,000 megohms.

Keep patiently in touch with your jobber and you will soon get the instruments that are held in highest esteem.



Model 203
Electronic Volt-Ohm-Capacity Milliammeter

THE HICKOK ELECTRICAL INSTRUMENT CO.

10521 Dupont Avenue
Cleveland 8, Ohio

NEW SOLDERING GUN

THE SPEED IRON*



Patent Applied For

100 Watts 115 Volts 60 Cycles

Soldering Heat in 5 Seconds

Wherever you have a soldered joint in radio, electrical or electronic repair and service work, the Speed Iron will do the job faster and better.

The transformer principle gives high heat—in 5 seconds—after you press the trigger switch. Convenient to hold with a pistol grip handle, the compact dimensions of this new soldering tool permit you to get close to the

*T.M. Reg. U. S. Pat. Off.

joint. The copper loop soldering tip permits working in tight spots. The heat is produced by the high current flowing through the soldering tip—permitting direct and fast transfer to the soldered connection.

If you want to save time on soldering jobs with a tool that is ready to use in 5 seconds, get a Speed Iron today. See your radio parts distributor or write direct.

WELLER MFG. CO.
DEPT. S-1 • EASTON, PA.



UNIMETER


This unit fulfills an extremely important need for general utility portable service equipment. It has wide range coverage for both a-c and d-c measurements of voltage, current measurements on d-c and the popular ranges on resistance.

The UM-3 is designed to clearly indicate all the functions which aid in the prevention of application of high voltages when preparing for current or resistance measurements.

Other G-E units for better servicing include: Tube Checker TC-3, Unimeter UM-4, and Oscilloscope CRO-3A.

For details write: *Electronics Department, Specialty Division, General Electric, Syracuse, New York.*

Electronic Measuring Instruments

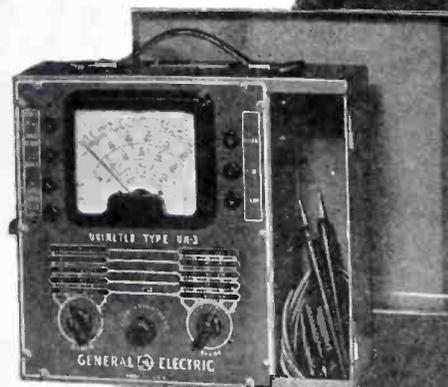

GENERAL ELECTRIC **UM-3**

NEWS

(Continued from page 57)

pared by Cornell-Dubilier Electric Corporation, New Bedford, Mass.

The basis of the code is the use of distinct color for every number from zero to nine inclusive.

TECHNICAL APPLIANCE CONSOLIDATES PLANTS

Technical Appliance Corporation consolidated its wartime New York City and Flushing plants and will hereafter be located at 41-06 DeLong Street, Flushing, N. Y.

The postwar Taco line will include antenna systems and kits for broadcast reception and also for f-m and television purposes.

RADIONIC EQUIPMENT CATALOG

A 32-page catalog listing components, test instruments, sound equipment and accessories, and technical books, has been released by the Radionic Equipment Company, 170 Nassau Street, New York, N. Y.

NEWS OF THE REPRESENTATIVE

John B. Tubergen, 1406 S. Grand Ave., Los Angeles 15, and Joe W. Marsh, 1100 West Pica Blvd., Los Angeles 15, have become members of the Los Angeles chapter. Jerry W. Miller, 5917 S. Normandie St., Los Angeles 3, Cal., has become an associate member of the Los Angeles chapter.

T. M. Graner, 600 Camelia St., Berkeley, is now a California chapter member.

O. N. Jones, 1085 The Arcade, Cleveland 14, O., is now a member of the Buckeye chapter.

At a recent meeting of the Wolverine chapter, H. E. Walton was elected president; J. C. P. Davenport, vice president; and Robert Milsk, secretary-treasurer.

The Hoosier chapter elected Leslie DeVoe president; Chuck Southern, president; Bruce McPherson, treasurer; and Bud M. W. Fisch, secretary.

Martin Friedman, a member of the Mid-Lantic chapter has moved to the Real Estate Trust Bldg., Philadelphia, Pa.

H. E. HARRIS PROMOTED BY BELL SOUND

Harry E. Harris, formerly sales manager of the Bell Sound Systems, Columbus, Ohio, has been appointed general sales manager of the manufacturing and jobbers sales division.

CANNON CONNECTOR BULLETIN

A revised 64-page edition of the Cannon Electric K bulletin on electric connectors has been released by Cannon.

AT EASTERN AMPLIFIER "E" CEREMONIES



Left to right, Lt. Col. Harold L. Lister, Comdr. William J. Warburton, Harry Friedman and Leonard Meyerson of Eastern Amp Corp., and Major Meredith J. Roberts

Development Company, 3209
 1st St., Los Angeles 31, California.
 This publication contains data on receptacles,
 taps, junction shells, stowage re-
 ceptacles for instruments, radio, motors,
 and general electrical applications.

TRANSFORMER BROCHURE

A 18-page brochure, *Engineering a Transformer*, covering lamination size, degage and magnetic performance; size, type and gage; winding details; transformer-reactor physical and electrical aspects; electrical-mechanical considerations of core laminations; im-
 position, assembling and casing; and
 and sealing, has been released by
 Transformer Corporation, Chi-
 cago, Ill.



LABORATORY REPLACEMENT VIBRATOR GUIDE

A 16-page replacement vibrator guide
 replacement listings for auto radio
 battery-operated household receiv-
 er circuit diagrams, installation
 cross references of vibrators and
 connections, buffer capacitor reference
 list, and notes on an assortment of

FREE TO YOU

COLOR CODE OHMS LAW CALCULATOR

Great Time Saver
 Burstein-Applebee of Kansas
 City offers you this great con-
 venience FREE. Easy to work.
 Solves many problems in a jiffy.
 FREE to Radio men, electronic
 engineers and others in the
 business. Attach coupon to
 your letterhead.

MAIL COUPON NOW

B-A

BURSTEIN-APPLEBEE CO.
 222 McGEE ST.
 KANSAS CITY 6, MO.

Send me FREE Color Code and Ohms Law Cal-
 culator along with latest catalog.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____

vibrators, has been published by P. R.
 Mallory & Co., Inc., Indianapolis 6, Indi-
 ana.

CAMBURN TO PRODUCE AUTO/FM/ TELEVISION ANTENNAS

A variety of antennas for auto sets,
 and f-m, television and marine receivers
 will be included in the postwar line of
 the Camburn Products Company, 490
 Broome Street, New York 13, N. Y.

A new plant will be built on Long
 Island to produce the new postwar items.
 M. B. Bernstein is president of Camburn
 Products Co.

BROWNING JOINS NORMAN B. NEELY

Robert Browning has been appointed
 special field engineer for Norman B.
 Neely Enterprises, Hollywood, California.
 Mr. Browning was formerly with
 Western Electric as a radar field engi-
 neer.

PLYTUBE F-M MAST KIT

A plytube antenna kit for f-m and
 television has been announced by the
 Plymold Corporation, Lawrence, Massa-
 chusetts.

The mast is supplied with fittings for
 attachment atop a roof or side of a build-
 ing. Mast, antenna system, and all fit-
 tings are offered as a unit.

JACK BEEBE JOINS SWAIN NELSON

Jack Beebe has joined the transformer
 division of the Swain Nelson Company,
 Glenview, Illinois, and will be in charge
 of manufacturing and distributing of
 S-N-C transformers. Mr. Beebe was
 formerly general sales manager of the
 Thordarson Electric Manufacturing Com-
 pany.



MUELLER INCREASES PLANT FACILITIES

A postwar plant expansion program
 has been announced by the Mueller Elec-
 tric Co., Cleveland.

The first step in this program pro-
 vides for the installation of new plating
 and finishing facilities.

BURGESS BATTERY REPLACEMENT GUIDE

A guide listing replacement batteries
 for approximately 1,000 models of port-
 ables and farm type receivers has been
 prepared by the Burgess Battery Com-
 pany, Freeport, Ill. Included also are
 a list of private brand portables. Also

(Continued on page 60)

HEAVY-DUTY Electrolytics

Now that V-J Day has come and
 gone, those heavy-duty metal-can
 electrolytics are once again be-
 coming available for civilian use.
 Once again the Aerovox electro-
 lytic line is providing that outstand-
 ing choice of types for the better
 jobs you are out to do, in this post-
 war radio and electronic world.

For your very best maintenance
 work where equipment must be
 kept going day in and day out;
 for those power packs that have
 to keep delivering properly filtered
 voltages hour after hour; for those
 radio sets that "must stay put" —
 you can depend on these Aerovox
 metal-can heavy-duty electrolytics.

Ask Our Jobber...

Ask him about the Aerovox heavy-duty elec-
 trolytics that are now starting to come through
 for civilian use. Ask about the other types in
 the outstanding choice of Aerovox capacitors.
 Ask for a catalog—or write us direct.

AEROVOX Capacitors
 INDIVIDUALLY TESTED

AEROVOX CORP., NEW BEDFORD, MASS., U. S. A.
 In Canada: AEROVOX CANADA LTD., HAMILTON, ONT.
 Export: 13 E, 40 St., New York 16, N. Y. Cable: 'ARLAB'



PHONO - RADIO MATCHING UNIT

BOON FOR SERVICERS! A time-saver and moneymaker that just had to come . . . fruit of ADAPTOL initiative and research, supported by technical help from your own profession.

HOW SIMPLE! Without removing anything from either housing . . . without even breaking a circuit . . . you can install this long-wanted convenience wherever there is a radio to be utilized for reproducing record entertainment!

THINK OF THE technical data you DO NOT have to wade through! And the time you can save! And the satisfaction for your customers, while you are making a nice profit and adding to your professional prestige!

ANY
RECORD
PLAYER

ADAPTOL
supplies the
MISSING LINK

write
QUICK
for the
WHOLE STORY

ANY
RADIO

ADAPTOL COMPANY
260 Utica Avenue, Brooklyn 13, New York

NEWS

(Continued from page 59)

presented is a numerical and alphabetic listing of all Burgess Battery products. Free copies of the guide are available from department RG.

* * *

JENKINS JOINS FORSHAY

Victor E. Jenkins, formerly test equipment sales manager for the Weston Electrical Instrument Corp., has joined Joe M. Forshay, 27 Park Place, N. Y., N. Y., factory representative in New York City and New Jersey for Simple Electric Company and Industrial Condenser Corporation.

* * *

COLEMAN NOW ASST. DIRECTOR RCA VICTOR ENGINEERING DIV.

J. B. Coleman has been named assistant director of engineering for the RCA Victor division. M. C. Batsel has been named chief engineer of engineering products. Mr. Coleman will make his headquarters at the company's home office, Camden, N. J.

Previous to his new assignment, Batsel was chief engineer at the RCA Victor plant in Indianapolis, Ind.

* * *

COMMUNICATIONS PARTS MOVES NEW PLANT

Communication Parts has moved to 1101 North Paulina Street, Chicago.

•

POSTWAR RECEIVERS



Portable and phono-table postwar models Westinghouse. Unit, above, can be mounted on wall or set up on flat surface. Combination unit, below, can be operated as a phono-receiver or with separate units, it being possible to remove receiver and using as a straight table model.



FIRST CHOICE . . . OF AMERICA'S RADIO DEALERS

Radio dealers, too, recognize the factors that long ago made Ward Antennas most popular with auto manufacturers and dealers. They see the top quality, precision workmanship, and now the new war-created designs that make Ward better than ever! The world's finest antennas for car and home were made, are made, and will continue to be made by Ward. Place your order for Ward Antennas now!



BUY VICTORY BONDS

THE WARD PRODUCTS CORPORATION
1523 EAST 45th STREET - CLEVELAND 3, OHIO

VOLUME AND TONE CONTROLS

(Continued from page 30)

in practically all the necessary resistance values and tapers in the wide range of resistance wherein the type may be used, the Service Man should make it a policy, when confronted with the replacing of controls of either type, to replace an original wire-wound control with a similar wire-wound control, and an original carbon type control with a similar carbon type control whenever possible to do so. By adhering to this policy, customer dissatisfaction will be avoided in most cases.

The circuit design of many receivers recently includes special considerations which make it necessary for proper operation to replace the volume control with one of the same type. There are many receivers (especially older models) in which the use of a wire-wound control is definitely indicated, and where the carbon type will not give satisfactory service. Wire-wound units are frequently used in control circuits which require a comparatively high circuit-carrying capacity. Compact, low-resistance controls of this type can be made to handle greater currents than a carbon control. They are also used in critical circuits where it is necessary to have a higher degree of resistance permanence, or much closer resistance tolerance, than is possible with the carbon type.

There are certain conditions where

it might be desirable or even necessary to change the type of control; i. e., use a carbon control having the proper resistance value, taper and wattage rating to replace an original wire-wound control or vice versa. This is a matter of discretion for the Service Man. Unless it cannot be avoided, the exchange should not be made unless the advantages to be gained are not offset by the disadvantages of the particular type control. Quite often this can be correctly ascertained only by trial and error.

Midget Versus Large Size Controls

In some receivers, particularly in off brand or a few trade name receivers in which small midget-type volume controls are used in current-carrying circuits of the antenna-bias type, repeated volume-control trouble due to the overheating may be experienced. If the original midget control is damaged or burned out and a check reveals that the failure is due to excessive current in the control, the defective unit should be replaced with one of the larger type controls if there is space available.

On the other hand, a midget type may be used to replace a large type control in an audio type of control circuit whenever this procedure tends to simplify a crowded installation.

(To Be Continued)

NEW PRODUCTS

NE-O-LITE TESTER

Best unit, Ne-O-Lite Test-Lite, for testing a-c lines, checking polarity of a-c or d-c, and tracing ground lines, has been announced by the Ne-O-Lite Mfg. Co., Rockford, Illinois. Tests voltage from 60 volts a-c to 550 volts a-c or d-c by variable light intensity. Has a neon lamp. Has a clear plastic shell and insulated test points.




HICKOK CHARGICATOR

Chargicator to indicate electrically equivalent gravity of any lead-acid storage battery, regardless of size or voltage has been developed by the Hickok Electrical Instrument Company, 10521 East Avenue, Cleveland 8, Ohio.

Probe type, illustrated, gives instantaneous measurement of battery condition. It shows what charging rate to use, either for trickle charging or for an efficient, safe, high-rate charge. It indicates the percentage of charge and charging danger and warns of destructive overcharging.

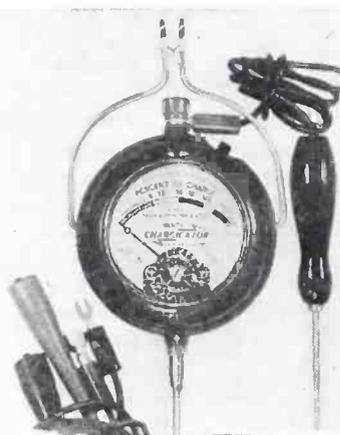Has a four-color scale dial. All models are sealed in molded acid-proof bakelite cases.



RADIART MIDGET VIBRATORS


Midget vibrators, type VR-2, 2 1/8" high x 1 1/8" in diameter, have been announced (Continued on page 62)

LAKE

has a better selection of
RADIO
Parts, Cabinets
and Equipment!



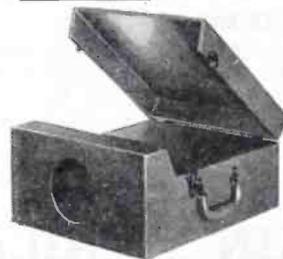Portable Phonograph Case of sturdy durable plywood, in handsome brown leatherette finish. Inside dimensions 16 1/2" long, 14" wide, 9 1/2" high. Has blank motor board. As illustrated above, specially priced at **\$6.95**



Portable Phonograph Case in brown leatherette covering. Inside dimensions 17 1/2" long, 13" wide, 7 1/2" high. Has blank motor board and opening for speaker. As illustrated at left, specially priced at

\$7.95

SOUND EQUIPMENT

Complete line of amplifiers, microphones, speakers and sound accessories. WRITE TODAY!

Also blank table cabinets of walnut veneer in the following sizes, with speaker opening on left front side:

(Note: *7 has center speaker grill.)				
#1	8 1/4"	L x 5 1/2"	H x 4"	D \$1.95
#2	10 1/4"	L x 6 3/8"	H x 5"	D \$2.75
#3	13 1/2"	L x 7 7/8"	H x 6 1/4"	D \$3.25
#7	10 3/4"	L x 7"	H x 5 1/2"	D \$2.50
#8	17"	L x 9"	H x 9 1/2"	D \$4.50
#9	21"	L x 9 1/4"	H x 10 1/2"	D \$5.50

*Speaker Opening in center of front side. Cabinets available in ivory color and Swedish Modern. Write for prices.

POWER TRANSFORMERS

4, 5, or 6 Tube—6.3 V at 2 amp	\$1.49
50 Mill Power Transformer.....	
7, 8 or 9 Tube—6.3 V at 3 an	\$1.89
70 Mill Power Transformer.....	



All types of radio cabinets, equipment and parts are available at Lake's lower prices. A large stock is listed in our catalog.

SERVICEMEN! Join our customer list today. Write for Our Free New 12-page, elaborate, Illustrated Catalog!

Order from Lake!
You'll make no mistake! Dept. D

Lake Radio Sales Co.
615 W. Randolph Street
Chicago 6, Ill.

by the Radiart Corporation, 3571 W. 62nd St., Cleveland 2, Ohio. Designed for operation from a small 6-volt storage battery.

Vibrator frequency, 185 cps $\pm 10\%$; input voltage (nominal), 6.0; input voltage range, 4.5 to 7.5; input current, 1.5 amperes maximum at 6.0 v; output voltage, 200 d-c maximum; and potential difference between primary reed and secondary reed, 25 v maximum.



INSULINE MIDGET JACKS

A series of midget-sized jacks has been developed by the Insuline Corporation of America, Long Island City, N. Y. Models include single closed-circuit,

NEW PRODUCTS

(Continued from page 61)

single open-circuit, and three-way microphone types. Jacks have a tooled-brass body with phosphor-bronze spring members, nickel plated.

SHALLCROSS AXIAL LEAD RESISTORS

Fixed wirewound axial lead 1-megohm, 1-watt resistors have been announced by the Shallcross Manufacturing Co., Jackson & Pusey Avenues, Collingdale, Pa. Known as Akra-Ohm type 188, the resistors are 1 3/16" long x 3/8" diameter. Axial leads, 3" long, of No. 20 tinned copper wire. Standard tolerance is said to be $\pm 1\%$.



WESTON DIRECT-READING INSULATION TESTER

A direct-reading insulation measuring device, model 799, providing a single range for .1 to 10,000 megohms with the 10,000 mark at 8% of the scale length, has been announced by Weston Electrical Instrument Corporation, 617 Frelinghuysen

sen Avenue, Newark 5, New Jersey. The circuit is said to have a test potential of less than 50 volts d-c. Its use includes checking leakage between windings in transformers, leakage of low-voltage paper and mica condensers, etc. Size 5 3/8" x 3 1/4" x 4 7/8".



REINER VACUUM-TUBE VOLTMETER

A vacuum-tube voltmeter, 451, amplifier, 101, featuring 25 millivolts on the lowest range, 1,000 volts on the highest range, 10 cps to 700 mc frequency range, and 7 mmfd input capacity has been announced by Reiner Electronic Co., Inc., 152 West 25th Street, New York 1, N. Y. Model 451 ranges are: a-c volts, 0-.02-1-25, (with amplifier)-2.5-10-25-100-250-1,000; d-c volts, 0-2.5-10-25-100-250-1,000; d-c current, 0-2.5-10-25-100-250-1,000; ohms; 1 ohm to 1,000 megohms.

AGAIN AVAILABLE!

RADIO · TELEVISION · ELECTRONIC

SERVICE

GROUP SUBSCRIPTION PLAN

12 ISSUES ONLY \$1

Saves Fifty Per Cent of the Subscription Price if Four or More Orders, Including Your Own, Are Properly Entered on This Form

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Name
 Address
 City-State
 Occupation
 Title (Service Mgr., etc.)
 Employed by
 State whether Employer is a Service Organization, Dealer, Jobber or Manufacturer

Please enter annual subscriptions (12 issues) for each of the above for which payment is enclosed at the rate of \$1.00 each. (This rate applies only on 4 or more subscriptions when occupations are given.)

SERVICE, 52 Vanderbilt Ave., New York 17, N.Y.

frequency range, 10 to 5,000 cps, amplifier) 50 cps to 700 mc. D-c ohm and current accuracy is said to be 2% on full scale. A-c volt accuracy to be 2%, 50 cps to 50 mc; entire frequency range 5% accuracy. Weight, 20 lbs. Size, 10 3/4" x 9" x 8".



OHMITE PIE-WOUND RESISTORS

A series of pie-wound resistors, Rite-types 844A/844B/842A, that can be mounted by means of a through-bolt, has been announced by the Ohmite Manufacturing Company, 4835 Flournoy St., Chicago 44, Ill.

Available in 3 sizes: 9/16" diameter x 1/2" long, 9/16" diameter by 7/8" long,

and 3/4" diameter x 1 3/16" long. The smallest is a 2 pie while the other two are 4-pie units. The minimum resistance is 1 ohm for the 2-pie unit and small 4-pie unit, and .10 ohm for the large 4-pie unit. The maximum resistance is 200,000 ohms for the 2-pie, 400,000 ohms for the small 4-pie, and 1.5 megohms for the large 4-pie unit.

Uses enameled alloy resistance wire non-inductively pie-wound on a non-hydroscopic ceramic bobbin.



CARTER MOTOR FREQUENCY-CONTROLLED D-C TO A-C CONVERTER

A frequency-controlled d-c to a-c rotary converter has been announced by Carter Motor Company, 1608 Milwaukee Avenue, Chicago, Illinois.

Designed with the frequency control in the base, including a vibration reed-type meter to visually indicate the frequency of the output.

In the 110-120 volt d-c to 117-volt a-c models, the output control is said to be within ± 10 volts at 60 cycles, over a ± 10-volt d-c fluctuation.

Models can be supplied with input voltages ranging from 6 through 64 volts for battery conversion and also 110-120 volts d-c for line conversion. Wattage ranges are from 40 through 250, continuous duty.



FREE CATALOG

Radio parts, test equipment, P.A. accessories, amateur supplies, technical books. Send today for your free copy to Dept. A-2.

RADIONIC EQUIPMENT CO.

"Chancellor Radio"

170 NASSAU STREET, NEW YORK 7, N. Y.

RADIO SERVICE—FLAT RATE SCHEDULES

Simplify pricing, eliminate losses, reduce arguments and make estimating easier.

If your jobber does not have them, write for information.

RADIO EQUIPMENT CO. 1415 W. FRANKLIN AVE. MINNEAPOLIS 5, MINN.

ATTENTION—SERVICEMEN

Send for our Latest FREE Catalogue of hard-to-get tubes and parts.

Immediate Delivery

PARAGON RADIO DISTRIBUTORS 35 LIBERTY STREET, DEPT. S., NEW YORK 6, N. Y.

Ted McElroy

World's Largest Manufacturer of Wireless Telegraphic Apparatus

COMPLETE CENTRAL OFFICE EQUIPMENT

McElroy Manufacturing Corp.

32 Brookline Avenue • Boston, Massachusetts

EFFECTIVE JANUARY ISSUE

TRIM SIZE OF SERVICE WILL BE INCREASED TO 8 7/8" x 11 3/4" BLEED PLATES SHOULD MEASURE 9" x 12"

PAID CIRCULATION OVER 10,000 ABC

Need Any Radio Tubes?

SEND US YOUR LIST

Insulated Resistor Kit—100 most pop. sized Deluxe Asst. 1/4, 1/2, 1 Watt R.M.A. color coded per kit \$2.75

Radio Knob Kit—50 Bakelite Set Screw for 1/4" shaft Deluxe Asst. per kit \$3.69

Hookup Wire—No. 20 Vinylite Covered. Solid Copper Core. 100 ft. indiv. boxed. 69c

By-Pass Condensers—600 v. fully guaranteed, all sizes up to .05 mfd. ea. 7c—per hundred \$5.50

Aerial Kits (Indiv. Boxed) 75c

Write for Complete Catalog of Hard-to-Get Items

NATIONAL RADIO DISTRIBUTORS

Dept. S, 140 West 42nd Street, New York 18, N. Y.

TUBES—PARTS

RADIO DEALERS—SERVICEMEN

Send for our list of available tubes and repair parts. Sylvania, Tung-Sol, Ken-Rad.

M. V. MANSFIELD CO.

937 LIBERTY AVE. PITTSBURGH 22, PA.

IMMEDIATE DELIVERY

ON TEST INSTRUMENTS!

SIMPSON 260 v.o.m. \$33.25	RADIO CITY 704 sig. gen. \$46.50
TRIPLETT 625-N v.o.m. 37.50	RCP 805 tube & set tester 89.50
TRIPLETT 666-H v.o.m. 16.00	DUMONT 3" oscillograph 105.00
TRIPLETT 2413 tube tester 45.00	Also, many other types available.
SOLAR CE-1-60 cond. checker 44.90	Write to us on your needs.
SUPERIOR CA-11 sig. tracer 18.75	25% deposit should accompany
SUPERIOR 400 multimeter 52.50	C.O.D. orders.

SCENIC RADIO & ELECTRONICS CO., 53a Park Pl., N. Y. 7

WARTIME RADIO SERVICE

1500 tested radio tube substitutions and other valuable information.

Keeps 'em Playing in spite of the tube shortage — only \$3 postpaid. Order now.

CITY RADIO COMPANY

East Washington at 5th St.

Phoenix, Ariz.

**YOU NAME IT,
WE'LL SUPPLY IT**



**EVERYTHING IN RADIO
AND ELECTRONICS**

R. W. T., world's oldest and largest Radio Supply House is ready again with tremendous stocks of sets, parts and equipment. You can depend on our quarter-century reputation for quality, sound values and super-speed service. Orders shipped out same day received. All standard lines already here or on the way, including: National, Hammarlund, R. C. A., Hallicrafters, Bud, Cardwell, Bliley and all the others you know so well.

Originators and
Marketers of
the Famous

Lafayette Radio

**Radio Wire
Television Inc.**

100 Avenue of the Americas, New York 13
(Formerly Sixth Avenue)
Boston, Mass. • Newark, N. J.

"No supplier anywhere has a bigger stock of Radio and Electronic equipment, Test equipment, Public Address equipment, Communications equipment. If your engineering problem requires special equipment, we'll make it. Write today. Dept. F-K-5."

JOYS AND FLASHES

OVER 10,000,000 f-m sets will be sold during the next two or three years, according to Frank Mansfield, director of sales research of Sylvania, who based his data on a survey recently completed. . . . Irving P. Wolfe has become a distributor and opened a store at 224 Main Street, Poughkeepsie, New York. His company will be known as Chief Electronics. . . . Olson Radio Warehouse, 73 E. Mill Street, Akron, Ohio, have been appointed distributors for Philco. . . . John Meck Industries now have a Cessna T 50 plane for transportation of company personnel and special equipment. . . . Jack Kaufman, former president of Heintz and Kaufman, Ltd., has been named vice president of Aireon Manufacturing Corporation and manager of the San Francisco office of Aireon. . . . A one-story plant on a 7½-acre tract on Skokie Highway near Waukegan, Illinois, has been purchased by Belmont Radio. This will supplement the Belmont plant on Dickens Avenue, Chicago for receiver production. . . . Ray T. Schottenberg, jobber sales manager of Astatic Corporation, visited jobbers in the New England states recently. H. A. Chamberlin, Astatic New England rep., accompanied Mr. Schottenberg. . . . George Balsam has been named ad manager and director of sales promotion of Aerovox Corporation, New Bedford, Mass. . . . Westchester Electronic Supply Company, 333 Mamaroneck Avenue, White Plains, N. Y., was recently appointed distributor for RCA, IRC and Cornell-Dubilier. . . . T. R. McElroy, president of the McElroy Manufacturing Corporation, 62 Brookline Avenue, Boston, Mass., has rejoined the Merchant Marine as a radio operator, Lt. Senior Grade, and is now making the regular run between Europe and U. S. . . . Amphinol Phenolic Corporation, 1830 South 54th Avenue, Chicago, Ill., are expanding their plastics manufacturing facilities and building a three-story building next to their present plant. . . . V. Hutto has been named Georgia factory representative for Universal Microphone Company, Inglewood, Calif. . . . Radiart Industries, Cleveland, Ohio, has been bought by Maguire Industries, Inc., Leslie K. Wildberg and William H. Lamar of Radiart have sold all their common and preferred stock to Maguire. . . . James H. Hickey has been appointed general manager of the Zenith Radio Distributing Corporation.

ADVERTISERS IN THIS ISSUE

SERVICE INDEX—NOVEMBER, 1945

ADAPTOL CO.	Agency: Hart Lehman, Advertising
AEROVOX CORPORATION	Agency: Austin C. Lescarboura & Staff
AMERICAN PHENOLIC CORPORATION	Agency: Evans Associates, Inc.
THE ASTATIC CORPORATION	Agency: Wearstler Advertising, Inc.
BURSTEIN-APPLEBEE CO.	Agency: Frank E. Whalen Adv. Co.
CAPITOL RADIO ENGINEERING INSTITUTE	Agency: Henry J. Kaufman & Associates
CINAUDAGRAPH SPEAKERS DIV. AIREON	Agency: Michael F. Mayer
CITY RADIO CO.	
CLAROSTAT MFG. CO., INC.	Agency: Austin C. Lescarboura & Staff
CORNELL-DUBILIER ELECTRIC CORP.	Agency: Reiss Advertising, Inc.
DETROLA RADIO DIV. INTERNATIONAL DETROLA CORP.	Agency: Zimmer-Keller, Inc.
DRAKE ELECTRIC WORKS, INC.	Agency: William Hoffman & Associates
ELECTRICAL REACTANCE CORP.	Agency: Scheel Adv. Agency
GENERAL CEMENT MFG. CO.	Agency: Turner Adv. Agency
GENERAL ELECTRIC CO.	Agency: Maxon, Inc.
GUARDIAN ELECTRIC	Agency: Kennedy & Co.
HICKOK ELECTRICAL INSTRUMENT CO.	Agency: White Adv. Co.
INTERNATIONAL RESISTANCE CO.	Agency: The Lavenson Bureau
JACKSON ELECTRICAL INSTRUMENT CO.	Agency: Kircher, Helton & Collett, Inc.
KEN-RAD DIV. GENERAL ELECTRIC CO.	Agency: Maxon, Inc.
LAKE RADIO SALES CO.	Agency: Sander Hodkin Adv. Agency
LIFETIME SOUND EQUIPMENT CO.	Agency: The Miller Agency Co.
McELROY MFG. CORP.	Agency: Shappe-Wilkes, Inc.
THE MacMILLAN CO.	Agency: Atherton & Currier, Inc.
M. V. MANSFIELD CO.	Agency: Shappe-Wilkes, Inc.
MARION ELECTRICAL INSTRUMENT CO.	Agency: Shappe-Wilkes, Inc.
MEISSNER MFG. CO.	Agency: Gardner Adv. Co.
MUELLER ELECTRIC CO.	Agency: Gardner Adv. Co.
MURRAY HILL BOOKS, INC.	Agency: The Harry P. Bridge Co.
NATIONAL RADIO DISTRIBUTORS	Agency: Burke & Wayburn Adv. Co.
NATIONAL UNION RADIO CORP.	Agency: Hutchins Adv. Co., Inc.
NEWCOMB AUDIO PRODUCTS CO.	Agency: Gail Hall Advertising
OHMITE MFG. CO.	Agency: Henry H. Teplitz, Advertising
PARAGON RADIO DISTRIBUTORS	
RADIART CORPORATION	Agency: Kenneth H. Kolpien
RADIO CITY PRODUCTS CO.	Agency: Reiss Advertising, Inc.
RADIO CORPORATION OF AMERICA	Agency: Kenyon & Eckhardt, Inc.
RADIO DEALERS SUPPLY CO.	
RADIO EQUIPMENT CO.	
RADIONIC EQUIPMENT CO.	Agency: Hirsch-Garfield Co.
RADIO SUPPLY & ENGINEERING CO.	Agency: Karl G. Bohr Adv. Agency
RADIO WIRE TELEVISION, INC.	Agency: S. T. Seidman & Co.
THE RADOLEK CO.	Agency: Turner Adv. Co.
RAYTHEON MFG. CO.	Agency: Burton Browne, Advertising
JOHN F. RIDER PUBLISHER, INC.	Agency: Lansford F. King
SCENIC RADIO & ELECTRONICS CO.	
SIMPSON ELECTRIC CO.	Agency: Kretzker & Meloan, Inc.
SOLAR CAPACITOR SALES CORP.	Agency: O. S. Tyson & Co., Inc.
SPRAGUE PRODUCTS CO.	Agency: The Harry P. Bridge Co.
STANDARD TRANSFORMER CORP.	Agency: Burnet-Kuhn Adv. Co.
SUPERIOR INSTRUMENTS CO.	Agency: Mitchell Adv. Agency
SYLVANIA ELECTRIC PRODUCTS, INC.	Agency: Newell-Emmett Co.
THORBARSON ELECTRIC MFG. DIV. MAGUIRE INDUSTRIES, INC.	Agency: Park City Adv. Agency, Inc.
TRIPLETT ELECTRICAL INSTRUMENT CO.	Agency: Western Adv. Agency, Inc.
TUNG-SOL LAMP WORKS, INC.	Agency: E. M. Freystadt Associates
UNITED TRANSFORMER CORP.	Agency: Shappe-Wilkes, Inc.
THE WARD PRODUCTS CO.	Agency: Burton Browne, Advertising
WELLER MFG. CO.	Agency: Beaumont, Heller & Sperling, Inc.
WESTON ELECTRICAL INSTRUMENT CO.	Agency: G. M. Basford Co.
WHOLESALE RADIO LABORATORIES	Agency: Pfeiffer Adv. Agency

THE EYES
HAVE IT




BACK AGAIN!

Solar Elim-O-Stats for noise suppression in all Household Electrical Appliances. Order now from your Solar Distributor.



Quick as a wink the Fairchild Night Owl Camera records enemy movements intended to be hidden by darkness. Quick as a flash the radio of the photo-reconnaissance plane keeps touch with its base — and clearly — for Solar Elim-O-Stats are part of the electronic equipment of these highly perfected cameras. This is but one of many instances where Solar Elim-O-Stats are being used to absorb local interference and keep speech channels free. Let Solar advise you on radio-noise suppression.

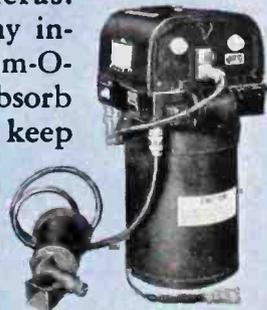


WEST N. Y. BAYONNE PLANT PLANT

A TOTAL OF TEN ARMY-NAVY EXCELLENCE AWARDS

SOLAR MANUFACTURING CORP.
285 Madison Avenue • New York 17, N. Y.



**20,000
VOLTS
IN A
2³/₈" BULB!**

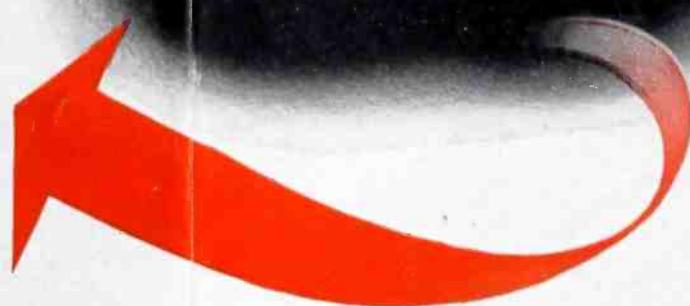

ANOTHER "FIRST" BY NATIONAL UNION RESEARCH LABORATORIES

AN example of how war-time research by National Union engineers is helping to lay the foundation for vastly improved post-war Television, FM and radio reception, is this new half wave high vacuum rectifier—the NU 1Z2.

Here is a miniature with the voltage handling capabilities heretofore possible only in full size tubes. For a high voltage rectified supply in the operation of radar and television equipment, the NU 1Z2 saves space—operates with increased efficiency—is exceptionally rugged. Its low filament power consumption suggests many new fields in circuit design and application, especially to the "ham" and experimenter.

For the distributor and service dealer, such original N. U. electron tube developments are creating new opportunities for profitable N. U. Tube replacement sales—today and in the future.

*National Union 1Z2
High Voltage Rectifier*

Inverse peak anode voltage- max.....	20,000 volts
Peak anode Current.....	10 ma.
DC Output Current.....	2 ma.
Filament Voltage.....	1.5 volts
Filament Current.....	300 ma.

The NU 1Z2 is designed to withstand shocks in excess of 500 G's.

Maximum overall length.....	2.70"
Maximum seated height.....	2.37"
Maximum diameter.....	.75"
Bulb.....	T5½
Base Miniature Button.....	7 pin
Mounting position.....	Any

**NATIONAL UNION
RADIO AND ELECTRON TUBES**

NATIONAL UNION RADIO CORPORATION • NEWARK 2, N. J.