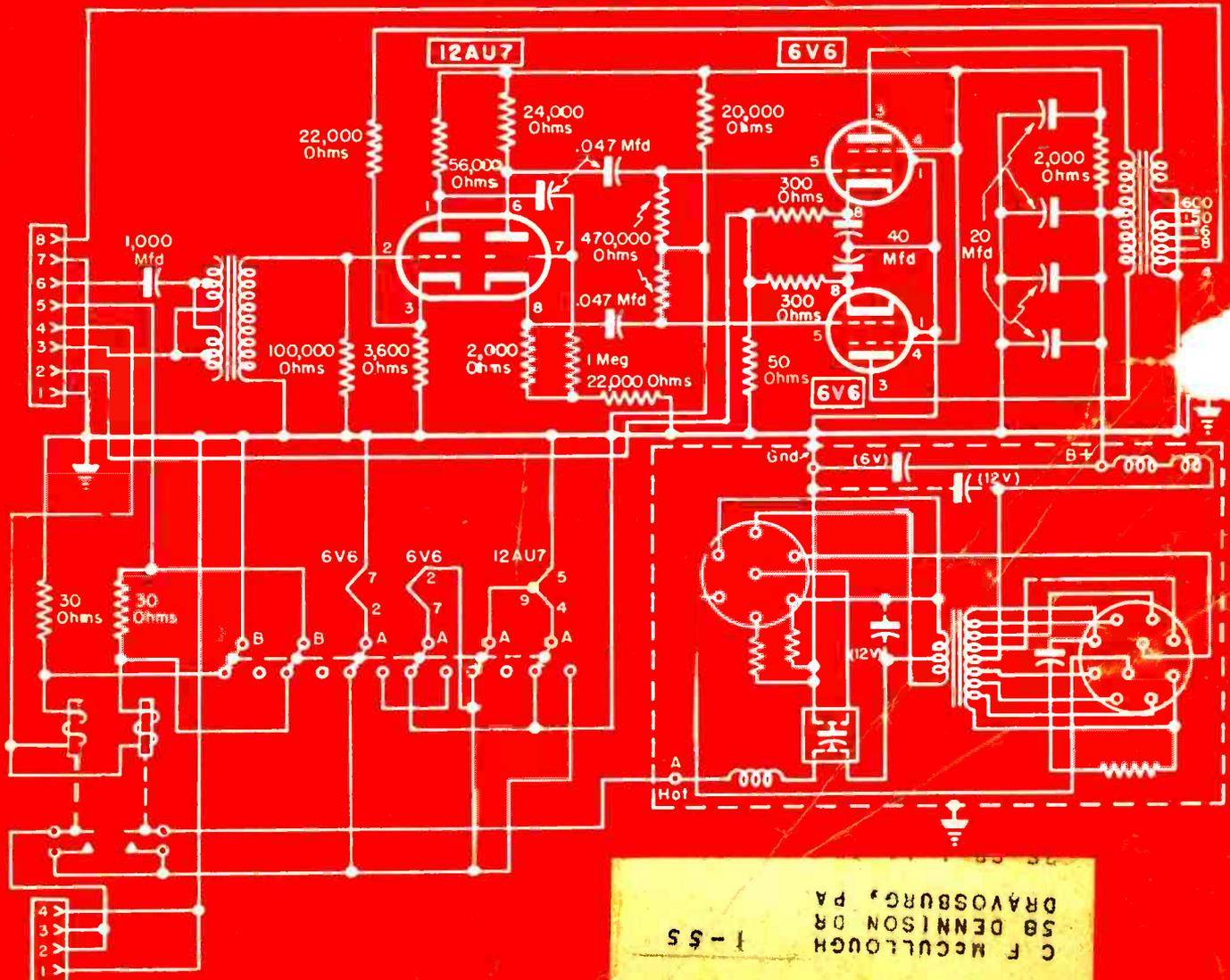


SERVICE

VOL. 22

THE TECHNICAL JOURNAL OF THE TELEVISION-RADIO TRADE

OCTOBER
1953




Mobile audio amplifier (6/12 v) with 8 to 10 watts output.

[See circuit analysis, this issue]

C F MCCULLOUGH
 58 DENNISON DR
 DRAYSSBURG, PA
 1-55
 29 S 1-24-52

another original!


Entirely New!

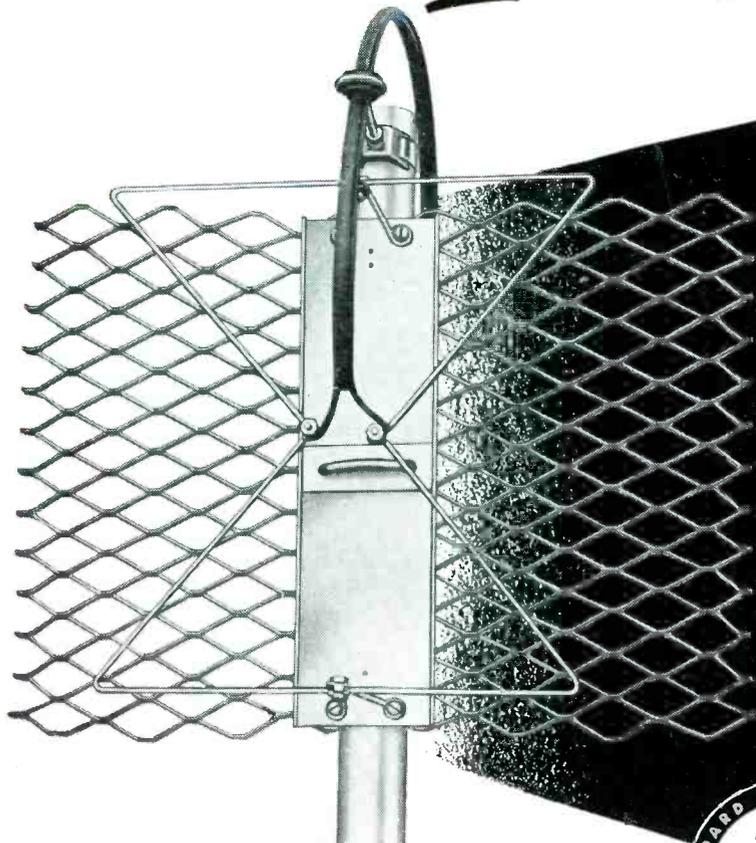

The last word in

UHF
TV Antennas
the
UW-2

Here's The One They've All Copied!

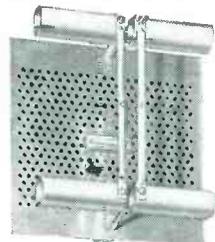

...NOW
AT NEW
LOW PRICES

UHF
TV Antennas
MODEL U-4

A superb quality UHF antenna featuring uniform gain with low vertical radiation (no ghosts). 300 ohm terminal impedance... measures 12x12x15 inches.



Here is another ORIGINAL... entirely NEW UHF TV antenna that far excels anything yet seen! It is a completely balanced broad band antenna covering ALL channels from 14 to 82 and terminating in 300 ohms with a very low voltage standing wave ratio! Some of the features include:

- Minimum wind resistance, (a double stacked UW-2 offers less wind resistance than many single bay antennas).
- The UW-2 assumes NO potential difference between itself and the mast, allowing MAXIMUM lightning protection when the mast is grounded.
- COMPLETELY FREE of insulators and their offending results.
- Excellent directivity, single lobe horizontal field pattern, 470 to 850 M.C.



SUBSIDIARY OF



THE RADIART CORPORATION CLEVELAND 13, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTORS • POWER SUPPLIES

ASTRON SM* CAPACITORS

These SAFETY MARGIN capacitors offer the assurance of greater all-around built-in dependability because of the most exacting engineering specifications. To you, as it does to thousands of other service men, SM* means absolute customer satisfaction.

ASTRON SM* TWIST PRONG

dry electrolytics are individually tested and guaranteed. They have earned wide acceptance by original equipment manufacturers. For quality replacement, you can rely on Astron's high standards of quality manufacture. Your jobber stocks all popular replacement ratings. Catalog AC-3A lists all available SM twist prong ratings.




ASTRON SM* BLUE-POINT*

fabulous new member of the Astron line, offers the "tightest seal and toughest shell" in molded plastic paper capacitors. They give outstanding performance under the most adverse temperature and moisture conditions. Look for the eye-catching yellow jacket with the easy-to-spot Blue-Point end seal. Write for Bulletin AB-20A for the complete story.

*Trade Mark

PATENT
PENDING

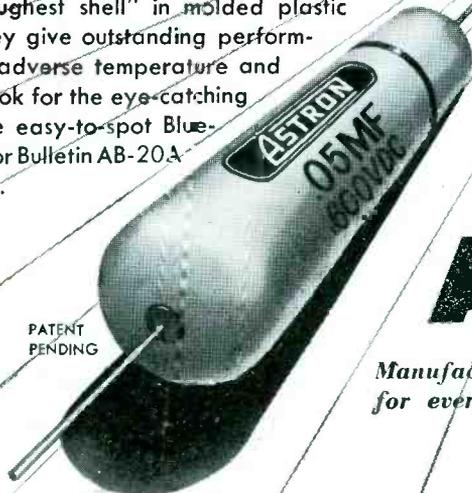

DEPEND ON—INSIST ON

ASTRON

*Manufacturers of a complete line of capacitors and filters
for every television, radio and electronic application.*



ASTRON CORPORATION

255 GRANT AVE., EAST NEWARK,

NEW JERSEY

In Canada: Charles W. Pointon, 1926 Gerrard St. East, Toronto

SERVICE, OCTOBER, 1953 • 1

NEW JFD "3-in-one" LIGHTNING ARRESTER

No. AT110 with hardware for wall or window sill mounting, \$1.50, list.

No. AT110S with stainless steel strap for pipe mounting, \$1.75 list.


Both feature the patented JFD strain-relief lips which prevent contact washers from ripping the lead-in wires apart!



lip →

one for all... all for one

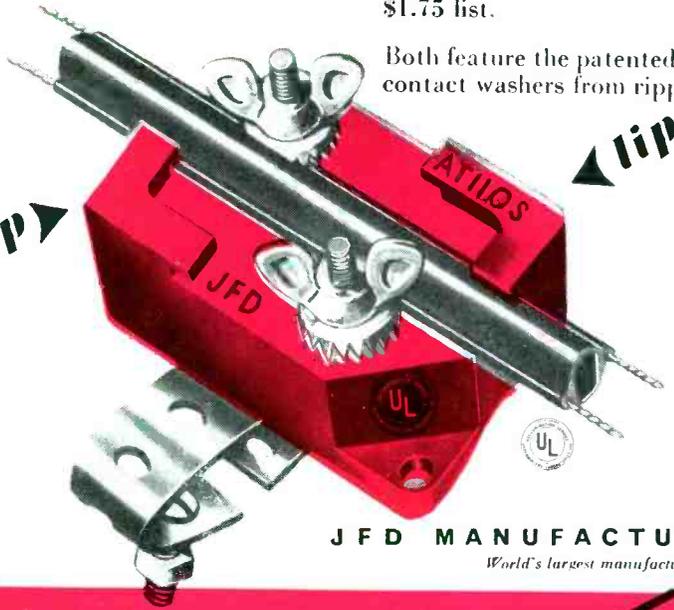1. for UHF or VHF tubular twin lead
2. for VHF flat twin lead
3. for VHF or UHF open wire



Burton Brothers Advertising

JFD MANUFACTURING COMPANY, INC.

World's largest manufacturer of tv antennas and accessories, Brooklyn 4, New York

Use the JFD Cascode Yagi...


Put an end to "GOLDFISH BOWL" reception!

For sets whose TV world is as limited as the goldfish world, JFD teams up the gain and directivity of the Yagi with the broad band coverage of the all-channel antenna. The JFD Cascode Yagi crashes through the fringe barrier to bring brilliant VHF reception to formerly barren TV areas. Noteworthy too: the famous JFD "Baline" Balanced Line design, the aircraft aluminum construction and the "Quik-Rig" pre-assembly. Write for bulletin 207A.

Order today in 5 or 10 element designs (5B or 10B series)

JFD MFG. CO., BROOKLYN 4, N. Y.

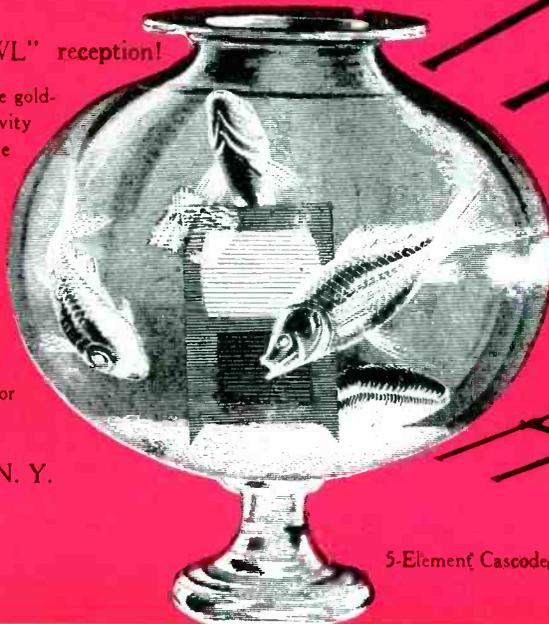World's largest manufacturer of television antennas and accessories




5-Element Cascode Baline Yagi

Models
5B26 5B2345
5B345 5B3456
5B456 5B713

10-Element
Cascode Baline Yagi
Models
10B26
10B2345
10B3456
10B456
10B713



metamorphosis of an antenna

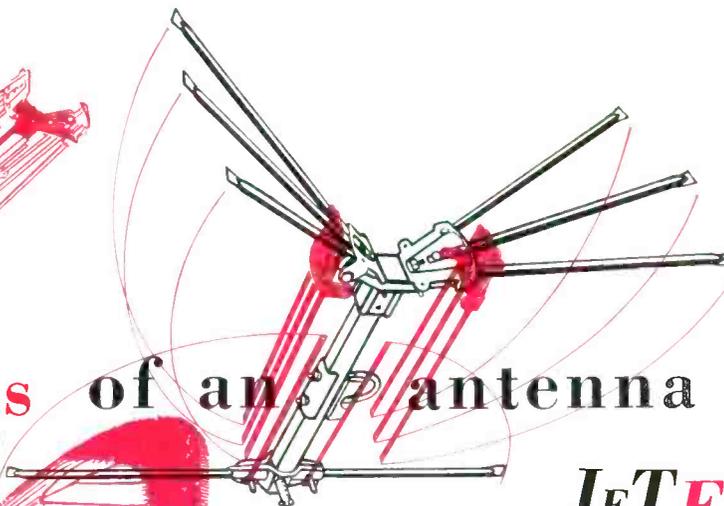

Like a butterfly emerging from a cocoon, the JFD **JETENNA** is practically ready for work when it emerges from the carton! No other fan conical assemblies so fast — performs so well! Available in single, two or four bays; including models JET 660, JET 661, JET 664. Write for bulletin 165.

JETENNA

JFD MFG. CO., BROOKLYN 4, N. Y.

World's largest manufacturer of TV antennas and accessories.

RADIO • TELEVISION • ELECTRONIC
SERVICE

LEWIS WINNER
Editor

B. BLOCK
F. WALEN
Assistant Editors

Including SERVICE—A Monthly Digest of Radio and Allied Maintenance; RADIO MERCHANDISING, and TELEVISION MERCHANDISING. Registered U. S. Patent Office.

A Report on Dual-Track 2-Speed Tape Recorder-Playback Equipment. By D. S. Cevans . . .	36
Association News	69
Audio Installation and Service (Troubleshooting Hum At the Audio Fairs). By Kenneth Stewart and Paul Edwards	74
Intermittent Fault Location in Electronic Equipment. By Sidney Wald	47
In the Field (Ratio-Detector S Curve Horizontal Sawtooth 60-Cycle Harmonic Waveform Analyses)	66
Miniaturized Mobile PA System Using PC Units. By Jack Darr	43
Ser-Cuits (Push-Pull Hi-Fi TV Chassis). By M. W. Percy	56
Service Engineering (Electronic Timer Operation Maintenance) By Thomas K. Beamer Service Men Can Convert TV Sets for Station Monitoring and Cueing. By John B. Ledbetter	61
Service The National Scene	34
Service The National Scene	49
Servicing Helps. By T. L. Gilford	53
Summary of Video Response Factors (Circuit Review)	45
10-Watt 6/12-Volt Mobile Audio Amplifier (Cover). By G. H. Floyd	30
Ten Years Ago	77
The Maintenance of Hi-Fi Audio Systems. By Mark Vino	38
Tube News (27" Picture Tube HD/HV Circuitry). By E. A. Teverson	78
TV Antenna Digest (Results of Easton, Pa., UHF Survey New Product Review). By Ralph G. Peters	70
TV Station Listing (Now on the Air and Authorized to Operate)	64
Video Amplifier Performance Factors (Chart Analysis). By Clark R. Alisen	44
Views and News. By Lewis Winner	29
What Happened to the DC Restorer: Will It Return With Color? By J. C. Geist	32

CIRCUITS

Electronic Timer Schematic	61
G. E. Control Unit for 2-Way Amplifier	30
G. E. 835 Video-Audio Section Modified for Monitoring	34
G. E. 10-Watt 6/12-Volt Mobile Amplifier (Cover)	31
Hoffman 403 Push-Pull Hi-Fi 24" Chassis	57
Horizontal Deflection and HV Circuit for Big Picture Tubes	79
Intermittent Test Arrangements For RF, AF, IF Signal Generators	47
Medium-Mu 6BQ7A Twin-Triode Circuit	79
Motorola Transformerless TV Power Supply	46
Phase Shifter Networks	53
Printed-Circuit Audio Amplifier	42
Push-Pull Output DC Balance Check Setup	38
Push-Pull Output Signal Balance Check With Phones	38
Push-Pull Output Signal Balance Probe Setup	38
Sentinel 401 Video-Sound Circuit Altered for Cueing	34
Simplified Schematic of Common DC Restorer	90
Single-Stage Response Crystal-Probe Test Setup	54
Triode-Connected 6W6GT Vertical-Deflection Schematic	79
TV Power-Supply System	46
Vertical/Horizontal Retrace-Blanking Circuit	91
Video Amplifier Schematic	46
Video Amplifier Schematic to Be Added for Picture Polarity	35
Video Detector/Video Amp/DC Restorer Circuitry	45
Video Detector Working Into Class A Amplifier	32
Wilcox-Gay 3A01 2/4-Watt Tape Amplifier	37

COVER

10-Watt 6/12-Volt Mobile Audio Amplifier (G.E.)	30
---	----

Index to Advertisers

Index to Advertisers	111
--------------------------------	-----

Manufacturers

Catalogs and Bulletins	105
Jots and Flashes	111
News	73
New Parts Tools Instruments	97, 100
On Book Row	110
Personnel	108
Rep Talk	106
TV Parts Antennas Accessories	102, 104



Entire Contents Copyright 1953, Bryan Davis Publishing Co., Inc.
Published monthly by Bryan Davis Publishing Co., Inc.

52 Vanderbilt Avenue, New York 17, N. Y. Telephone Murray Hill 4-0170

Bryan S. Davis, Pres. Paul S. Weil, Vice-President F. Walen, Sec. A. Goebel, Cir. Prom. Mgr.
Mid-West Representative: Stuart J. Osten, 333 N. Michigan Ave., Chicago 1, Ill. Telephone DEarborn 2-3507
East-Central Representative: James C. Munn, 2253 Delaware Dr., Cleveland 6, Ohio. Telephone: ERievview 1-1726
Pacific Coast Representative: Brand & Brand, 1052 W. Sixth St., Los Angeles 14, Calif. Telephone: Michigan 1732
Metropolitan District Manager: Donald C. Weil, 52 Vanderbilt Ave., New York 17, N. Y.

Entered as second-class matter June 14, 1931, at the Post Office at New York, N. Y., under the Act of March 3, 1879. Subscription price: \$2.00 per year in the United States of America and Canada; 25 cents per copy. \$3.00 per year in foreign countries; 35 cents per copy.

THE NEW

Carry-all
tube caddy
TRADE MARK



Only \$13.95*
8 x 15 x 21 in.
Mailable.

**MOST COMPLETE,
VERSATILE**

A proud new "tube caddy"—
to save even more time and
money for the TV serviceman.
PAYS FOR ITSELF.
Carries up to 262 tubes. A
complete tool and tube kit—
helps technician to give efficient
service that builds confidence.
Ruggedly built with


*Craftsmanship
in Cabinets*




*Net to Service dealer.
Other tube caddies
from \$7.75 to \$14.95.
Write for FREE FOLD-
ER. Sold only thru
Parts Jobbers. Slightly
higher West of Rockies.




FALCON Introduces -

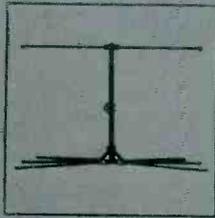


Channels 2-13, peaked for low channels (2 thru 6)

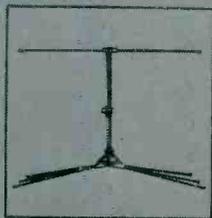


Channels 2-13, normal position, peaked for all VHF channels (2 thru 13)

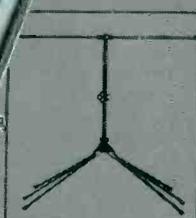


Channels 2-13, peaked for high channels (7 thru 13)

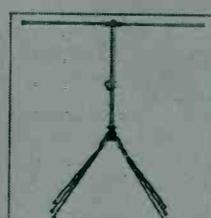

Channels 2-83, peaked for UHF channels

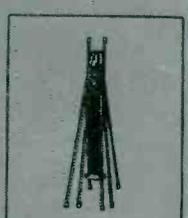

Falcon "VARI-CON" folded for packing

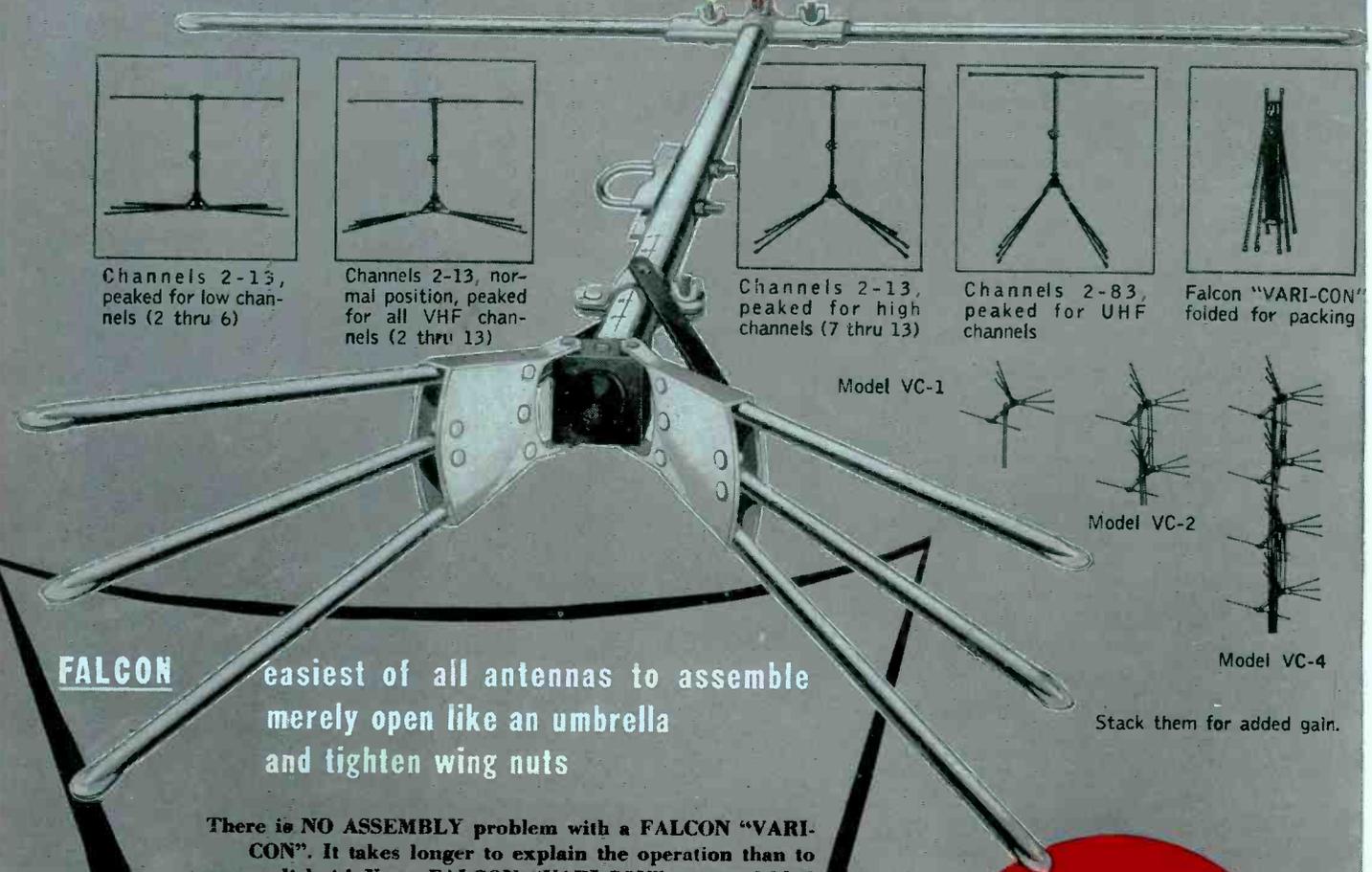

Model VC-1



Model VC-2



Model VC-4

Stack them for added gain.

FALCON

easiest of all antennas to assemble merely open like an umbrella and tighten wing nuts

There is **NO ASSEMBLY** problem with a FALCON "VARI-CON". It takes longer to explain the operation than to accomplish it! Your FALCON "VARI-CON" comes folded into one compact unit. You need only swing the reflector into position and tighten the wing nuts. Move the sliding sleeve to the calibrated channel setting you desire and tighten. The butterfly springs snap the elements into position and lock them securely. The FALCON "VARI-CON" is ready to install, ready to provide peak performance. *Changing the channel peaking of the "VARI-CON" is just as simple and easy as making the original setting. No tools are needed for either operation.*



Calibrated sleeve for quick peaking of antenna.

THE HEART OF THE "VARI-CON"

Above is a view of the new mechanism which enables anyone to adjust the peaking of the FALCON "VARI-CON" to any range of channels desired. The sliding sleeve, on the calibrated boom, automatically fans out the elements to their correct position.

A simple, trouble-proof, snap-action spring in the

butterfly keeps the elements solidly in place. The insulated hinge assembly is extremely strong, durable and weather-resistant and has an extra long leakage path. Weight has been kept to a minimum, strength at a maximum in order to assure long life and freedom from wind and weather damage. A heavily plated mast clamp is supplied.

the "VARI-CON"

(The conical that's variable)

Provides all Channel Performance...

Yet can be Peaked for Increased Gain on any Channel Range

The FALCON "VARI-CON" was designed for today, tomorrow and years to come. Its unusual construction permits setting the "VARI-CON" for all-channel performance peaked to provide the additional gain needed on special channels. In addition, the variable patterns obtainable are of great value in ghost elimination.

There is no guess work; no tedious assembly; no field strength equipment needed to peak the "VARI-CON" for high-gain, sharp pattern performance in your area. It's as simple and easy as opening an umbrella. Here's all you do: Unpack the "VARI-CON"—Slide the adjusting sleeve to the calibrated marking on the boom for the best reception of channels in your area—Fan out the reflector elements—Tighten the locking wing nuts. The "VARI-CON" is

automatically peaked WHERE YOU WANT IT and ready to install. It is the only conical that enables you to provide a custom-made installation resulting in higher gain and increased customer satisfaction.

The NEW FALCON "VARI-CON" is ruggedly constructed. Heavy-duty heads will not crack or break. The steel spring snap-action butterfly assemblies are unbreakable. Full length, 48 inch, elements are used. One of the most capable engineering staffs in the industry has worked out every last detail of this truly remarkable TV antenna. To the high gain all-channel performance and excellent line match of the conical, FALCON engineers have added the "plus" feature—adjustable, calibrated channel range peaking!

FALCON

The new "VARI-CON" is one of the most significant additions to antenna design. Watch for the other new FALCON antennas which will be announced in the near future! Each will represent the most advanced, most efficient antenna design of its type.

WRITE FOR ILLUSTRATED FOLDER AND PRICES



FALCON ELECTRONICS COMPANY • 2003 CEDAR ST. • QUINCY, ILLINOIS



NATIONAL ADVERTISING TO BACK NEW FALCON "VARI-CON"

To stimulate sales on all levels, FALCON is conducting one of the most aggressive advertising campaigns in the industry. Full two-page color spreads are appearing regularly in many of the nation's top trade and consumer publications.

Your **BEST** antenna buy
for channels 2 to 83!

telrex
"DUO-BAND"
"CONICAL-V-BEAM"*

- ★ UNIFORMLY HIGH GAIN
- ★ EXCELLENT DIRECTIVITY
- ★ AUTOMATIC TRANSITION FROM UHF TO VHF
- ★ HIGH SIGNAL-TO-NOISE RATIO
- ★ ALL ALUMINUM RUGGED CONSTRUCTION



Ask the
DEALER!



INSTALL ONE ANTENNA, ONE TRANSMISSION LINE—Full UHF and VHF reception. The Telrex Duo-Band extends the famous "CONICAL-V-BEAM" principle. The addition of two supplementary V splines compacts and adds in-phase the higher frequency signals.

AUTOMATIC, PERFECT TRANSITION FROM VHF TO UHF—No "lossy" filters or isolation networks are employed in the Telrex design. Both UHF and VHF signals are picked up at the same cone apex.

Ask the
JOBBER!



ONLY A SINGLE TRANSMISSION LINE IS REQUIRED — Duo-Band provides uniformly high gain with one major lobe, channels 2 to 83 and actually improves reception on channels 7 to 13.

ASSURES HIGH SIGNAL-TO-NOISE RATIO . . . FREE FROM GHOSTS — Excellent directivity on VHF and UHF. A clear, unidirectional pattern makes Duo-Band the perfect array for reception near or far.



Ask the
**SERVICE
MAN!**



Ask the
CUSTOMER!

DUO-BAND features include all aluminum rugged design, light weight. Practical design can be used single bay or stacked for increased sensitivity.

60 Models Available to meet every Antenna Requirement. Write for Illustrated Catalog on the Complete TELREX Line.

"CONICAL-V-BEAMS" are produced under Re-issue Patent No. 23,346. Canadian and Foreign Patents Pending.



SERVICE MEN! Modify existing "CONICAL-V-BEAMS" with DUO-BAND! Existing antennas can be modified to operate efficiently on channels 2 to 83 by means of the new Telrex Modification Kit.

ASBURY PARK 11, N. J.

Originators and Manufacturers of "CONICAL-V-BEAMS" — insist on the Original! Look for the Telrex Trademark.

YOU'VE HEARD ABOUT THE *Telechief*[®]



It's HERE—Sangamo's new premium molded paper tubular capacitor that will outlast and outperform any other tubular... built for better TV performance.

NOW...

see your jobber
for this

**SPECIAL
INTRODUCTORY
OFFER!**



Only
\$24.00

Slightly higher in Canada

Here's a deal you can't afford to miss. You get a basic balanced inventory of fast-moving "Telechiefs"—assortment based on national popularity—PLUS a heavy gauge steel chest with two extra drawers for small parts—PLUS 100 attractive folders of your choice to promote your business. You get all this for only \$24.00—the dealer net price of the capacitors alone. (They list at \$40.00.)

Get acquainted with the Telechief today—your Jobber has these kits in stock.



You can have 100 of any of these business-building folders without extra cost—a sample of each is enclosed in the kit.



Those who know...choose Sangamo

BC53-12

SANGAMO ELECTRIC COMPANY MARION ILLINOIS

SERVICE, OCTOBER, 1953 • 7

Versatile!

NEW!

Exclusive!

PHILCO[®] Cross Dot TV Linearity Pattern Generator



Model G-8004

Specifications: — Self stabilized oscillator • Variable output frequencies • Power consumption approximately 10 watts • Power supply—105-125 Volts, 60 cycles • large easy-to-tune dial • high level output controllable with variable attenuator.

PHILCO
Test Equipment
Specifically Designed for the Serviceman

More Stable Operation at
1/3 the Cost
of Comparable Generators

Again . . . Philco leads the field! For the finest possible linearity adjustments without station pattern, here is the all new *cross dot* linearity pattern generator. This unit not only lets you make TV linearity adjustments more quickly and accurately but also permits precise routine adjustments and trouble shooting with amazing economy of operation . . . Light, rugged, portable, heavy gauge steel case . . . finished in durable gray hammertone . . . See your Philco distributor now or write Philco, Accessory Division, "A" & Allegheny, Philadelphia, Pa.

Now Yours on New
Special Payment Plan



Model M-8104—TV Field Strength Meter • Offers more features than any unit at this popular price . . . Super Colorado Tuner for low noise and high gain . . . May be used to check TV boosters, antenna combinations, interfering signals and picture signal strength.



Model 7008—Visual alignment Generator • Combines in one economical unit functions ordinarily found only in a cumbersome collection of costly devices . . . Includes extra sensitive built-in oscilloscope . . . AM, FM, and audio generators. Sweep output flat to within .2 DB/MC.

2 NEW SERVICE AIDS . . .

DESIGNED

BY AND FOR

YOU!

New CBS-HYTRON Tube-and-Tool Caddy ▶

Another Tube Caddy? Yes, but *you* service-dealers helped us design this one. Helped us throw out a dozen almost-right designs. Stayed with us until the CBS-Hytron Tube-and-Tool Caddy became *your* Caddy. Built the way *you* want it.


Your new Caddy has literally dozens of features . . . many unique. Here are only a few: *Roomy* . . . holds 218 tubes! Also all your necessary tools, small parts, volt-ohmmeter, flashlight, and reference data. *Compact* . . . functional design wastes not one inch of space. *Accessible* . . . everything in sight and reach. *Rugged* . . . strong, tip-proof — used safely as seat. *Test Mirror* . . . reversible for protection — mounted in cover supported by adjustable friction hinge.

Sorry, there's just not enough space to tell all. But see your new Caddy yourself at your CBS-Hytron distributor's. He has a red-hot deal for you. He'll show you how *amazingly easy* it is for you to own this unique CBS-Hytron Tube-and-Tool Caddy. See him today.



Open back view.

Open front and top views.

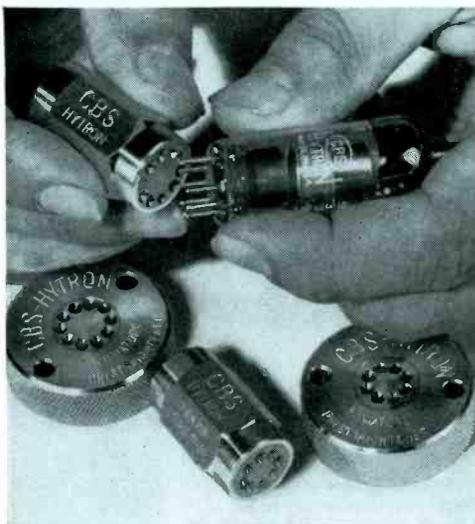

◀ New CBS-HYTRON Twin Pin Straightener



Ever wished you had a combination 7-Pin and 9-Pin Straightener? One that was handy, compact, light? But also a precision job, just like CBS-Hytron's original 7-Pin and 9-Pin Straighteners?

Here it is: The new CBS-Hytron Twin Pin Straightener, SH79. Same life-time, wear-and-corrosion-resistant steel dies. Same individually drilled, precision pin-circle holes. Same absence of guide-posts, permitting that final touch of sidewise straightening. The "Twin" is also roll-proof.

And the Twin is only 98¢ net. Get at least two . . . for pocket, tool kit, bench. Call your CBS-Hytron distributor today. Yes, he still has the famous individual CBS-Hytron 7-Pin and 9-Pin Straighteners at only 65¢ each net. Get them, too.

CUTTING YOUR CALL-BACKS WITH CBS-HYTRON CTS-RATED* 5AW4 and 6CU6?

They're the most talked-about tubes in TV today. CBS-Hytron CTS-Rated 5AW4 and 6CU6 are both rated for dependable Continuous Television Service. Heavy-duty work horses, they replace the 5U4G and 6BQ6GT respectively.


Brand new designs, not just improved tubes, the 5AW4 and 6CU6 have big safety factors. Give you long . . . long trouble-free life. Loaf in those hard-working, heavily

loaded rectifier and horizontal amplifier sockets . . . even in 21-inch jobs.

Start slashing your call-backs with these tubes right now. 5AW4 and 6CU6 are available only from your CBS-Hytron distributor. See him today. Ask for complete 5AW4 and 6CU6 data. Or write direct. Above all, don't let another day slip by without trying these wonderful, new CBS-Hytron CTS-Rated tubes.



*Rated for Continuous Television Service

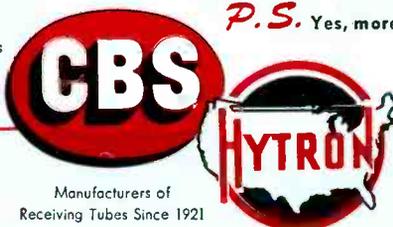

P.S. Yes, more CBS-Hytron CTS-Rated tubes are coming. Watch for them.

CBS-HYTRON Main Office: Danvers, Massachusetts

A Division of Columbia Broadcasting System, Inc.

A MEMBER OF THE CBS FAMILY: CBS Radio • CBS Television • Columbia Records, Inc. CBS Laboratories • CBS-Columbia, Inc. • and CBS-Hytron

RECEIVING . . . TRANSMITTING . . . SPECIAL-PURPOSE AND TV PICTURE TUBES • GERMANIUM DIODES AND TRANSISTORS

there are **4** points to a triangle...

THE POINT OF APPLICATION

determines the type of loudspeaker best capable of providing optimum performance at lowest possible cost. There are over 50 different University models to choose from... each designed to serve most efficiently and economically in its intended application.

- Radial type projectors and paging speakers with 360° dispersion for maximum coverage at lowest cost and ease of installation.
- Reflex trumpets in various sizes for incomparable efficiency, distance, and noise penetration.
- Wide-angle and bi-directional types, marine and submergence models for heavy industry.
- Paging and "talk-back" speakers in numerous sizes, power and frequency characteristics and mounting arrangements.
- "Explosion-proof", blastproof, and even super-power types from 100 to 720 watts capacity.
- High fidelity, full-frequency response types for indoor and outdoor use.

University Loudspeakers are application-engineered to assure customer satisfaction, avoid waste of amplifier power and speaker capacity and reduce initial equipment and installation costs. University helps you to sell more sound jobs... make more profit you can pocket. Why spend more for more than you need—CHECK UNIVERSITY FIRST!



FREE—new 1953 copy of the University Technilog • Complete up-to-date manual of sound theory, application and installation requirements • SEND for your copy today.




UNIVERSITY LOUDSPEAKERS • INC.
80 SOUTH KENSICO AVENUE, WHITE PLAINS, N. Y.




VEE-D-X PROUDLY PRESENTS . . .

THE ONE AND ONLY **ALL-CHANNEL YAGI**

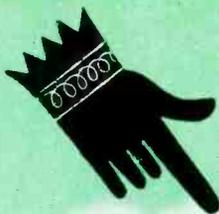


VEE-D-X tra Special

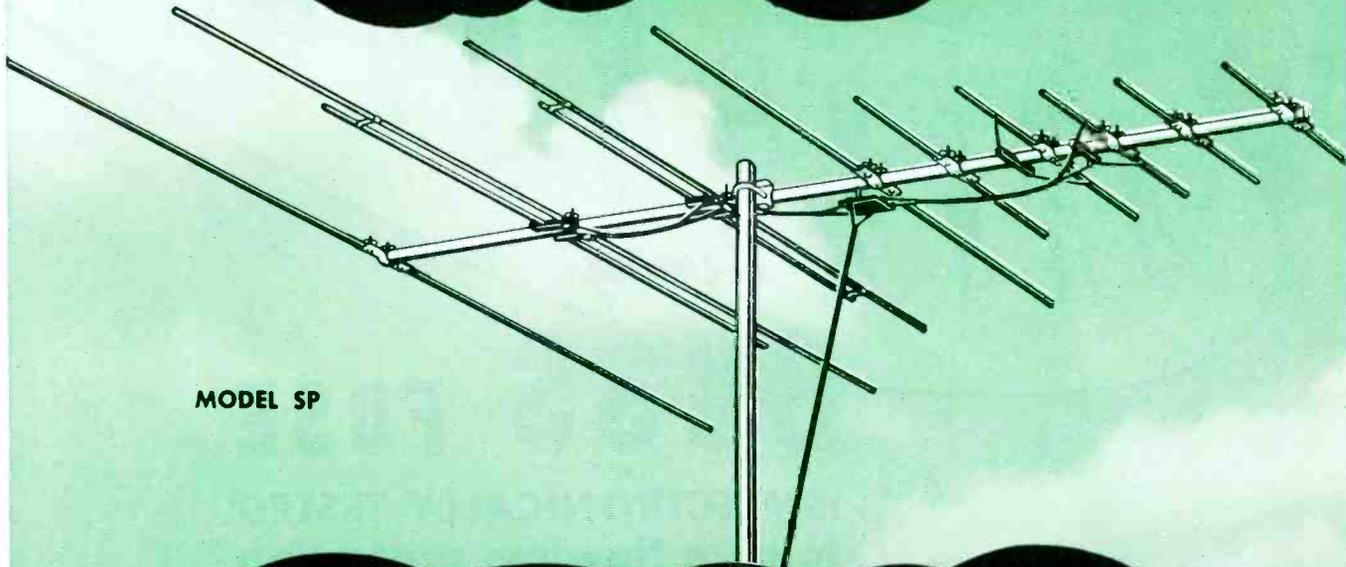


MODEL SP

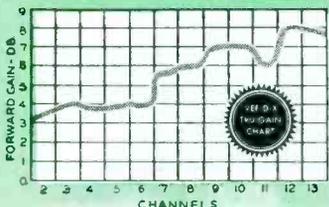AT LAST YAGI POWER AND DIRECTIVITY WITH ALL-CHANNEL PERFORMANCE



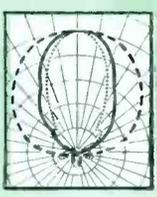CAUTION: It is the policy of VEE-D-X not to falsify gain charts for advertising purposes. This Tru-Gain Chart is exact and is based on standard specifications using a single dipole as reference.



FEATURES


- Powerful all-channel VHF performance
- High forward gain and sharp directivity
- Extremely high front-to-back ratio (important toward eliminating interference from unwanted stations)
- Rugged, pre-assembled construction
- One piece drawn aluminum boom
- Better rooftop appearance with clean yagi lines
- Ideal for use with VEE-D-X Antenna Rotator

VEE-D-X engineering has produced another truly great antenna — the VEE-D-Xtra Special. Think of it — all the desirable features of a yagi — yet with all-channel performance in a single easy-to-install antenna. Technically, it is a nine-element hi-low yagi (5 elements on high channel — 4 on low) "T" matched. The hi-low sections are phased together with the new isolation filter (MM-25). Here is the ideal all-channel antenna — and especially wherever interference from unwanted stations must be eliminated. A honey for use with the VEE-D-X Rotator.

La Pointe ELECTRONICS INC.
ROCKVILLE, CONNECTICUT

VEE-D-X

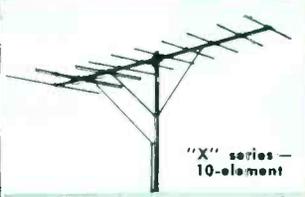VEE-D-X also announces two great new series of Broad Band Yagis. The extra powerful "X" series 10-element and the "V" series 5 and 6-element. Both in three cuttings, 2-6, 4-6, 7-13.



over **99%***
hit the bull's-eye
for quality!

that's why we call

Federal
PICTURE TUBES

"BEST-IN-SIGHT"



Thousands of famous-name picture tubes were quality-tested by a famous-name TV set manufacturer.* When the scoring was over, Federal led all the brands tested . . . with an "OK" on over 99% of its tubes!

Here's proof, Mr. Serviceman, that it pays to replace with *Federal* . . . here's assurance of top performance . . . of less time wasted on call-backs . . . of more profit per tube replaced!

Federal quality brings to servicemen a tremendous opportunity to create customer-goodwill . . . to build steady replacement business.

Federal quality *stands by* servicemen, because it *stands up* in service . . . backs up their years of experience and know-how . . . their *trained* judgment. That's one of many big reasons why more and more servicemen are specifying Federal "Best-in-Sight" picture tubes.

Join the trend today . . . ask your Federal Distributor about the popular-size line that takes care of over 90% of all TV replacements . . . ! For information, write to Dept. N-356.

"Federal always has made better tubes"


Federal
Telephone and Radio Company



100 KINGSLAND ROAD, CLIFTON, N. J.

In Canada: Federal Electric Manufacturing Company, Ltd., Montreal, P. Q.
Export Distributors: International Standard Electric Corp., 67 Broad St., N. Y.

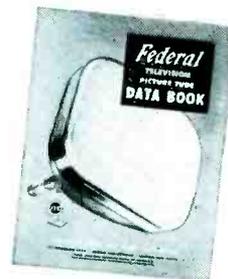Get Your Copy of
Federal's
TV Picture Tube
DATA BOOK



12-page booklet with information on interchangeability, basing diagrams, bulb outlines, dimensions, characteristics. Address your inquiry to Dept. listed above.



"OUR CUSTOMERS TELL US THAT THE PICTURES ARE BETTER THAN WHEN THEIR SETS WERE BRAND-NEW."

*Says W. T. Gerlach
Roselle Radio and TV Service
1027 Chestnut St., Roselle, N. J.*

"Since the first TV sets were delivered in this area, we've installed almost every type and brand of picture tube, but we've yet to find any that gives a picture like the G-E Aluminized Tube.

"Our tube customers are not only satisfied—they are downright pleased! As a result, **more than two out of every three tubes we are installing are G-E Aluminized Picture Tubes.**"

"2 OUT OF EVERY 3 TUBES ARE G-E ALUMINIZED"

Give your customers TV's finest picture—and make more money!

"65% OF OUR PICTURE TUBES SOLD ARE G-E ALUMINIZED. ONE OWNER TELLS ANOTHER."

*Says Kenneth L. Middleton . . . HILLENS
740 N. Garey Ave., Pomona, Cal.*




"GENERAL ELECTRIC ALUMINIZED PICTURE TUBES ARE ONE OF MY REAL BIG MONEY-MAKERS!"

*Says Norman Foster . . . Foster Television
2922 Milwaukee Ave., Chicago, Ill.*



**BRAND-NEW
MIRROR DISPLAY**

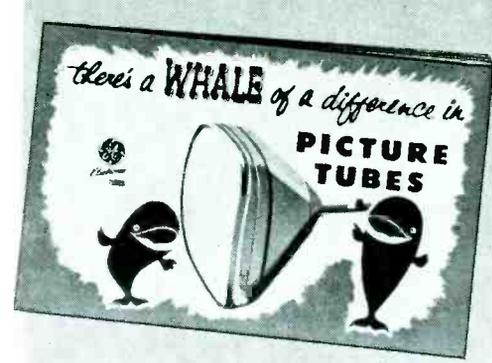Eye-evidence why a G-E Aluminized Tube is up to 100% brighter. The mirror does it! . . . This 3-color display with polished, gleaming mirror sticks front or back to any flat surface—your store-window, door, or wall. A real attention-getter!



FACT-CRAMMED BOOKLET FOR TV OWNERS




COLORFUL STREAMERS

WE INSTALL PICTURE TUBES!"

Ask for new 6-piece promotion kit!

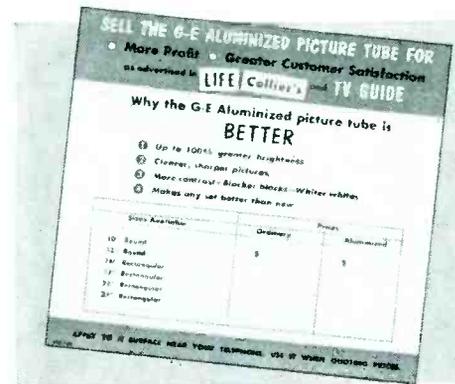All these helps are waiting for you at your G-E tube distributor!



PHONE-SELLING PRICE GUIDE

GET the full kit of G-E Aluminized Tube sales aids! Use them to sell better-than-new TV! It's a sure-fire way to lick competition from inferior picture tubes offered to your customers.

This mirror, booklet, and other helps will work hard for you, developing profitable tube sales. General Electric further supports your efforts by a strong coast-to-coast advertising campaign to TV owners. Ads in LIFE, COLLIER'S, and TV GUIDE, reaching some 40,000,000 readers, tell why the G-E Aluminized Tube is brighter, better, the finest tube any set can have!

Today many leading TV builders are featuring new-model receivers with General Electric Aluminized Tubes. Demand for replacement tubes will skyrocket as the finer performance of the aluminized tube is made known by enthusiastic set owners.

Take a tip from successful service dealers everywhere! Sell TV's finest picture profitably! Tube Department, General Electric Co., Schenectady 5, New York.



MAIL CARD THAT BUILDS INQUIRIES




NEWSPAPER AD MAT



GENERAL ELECTRIC

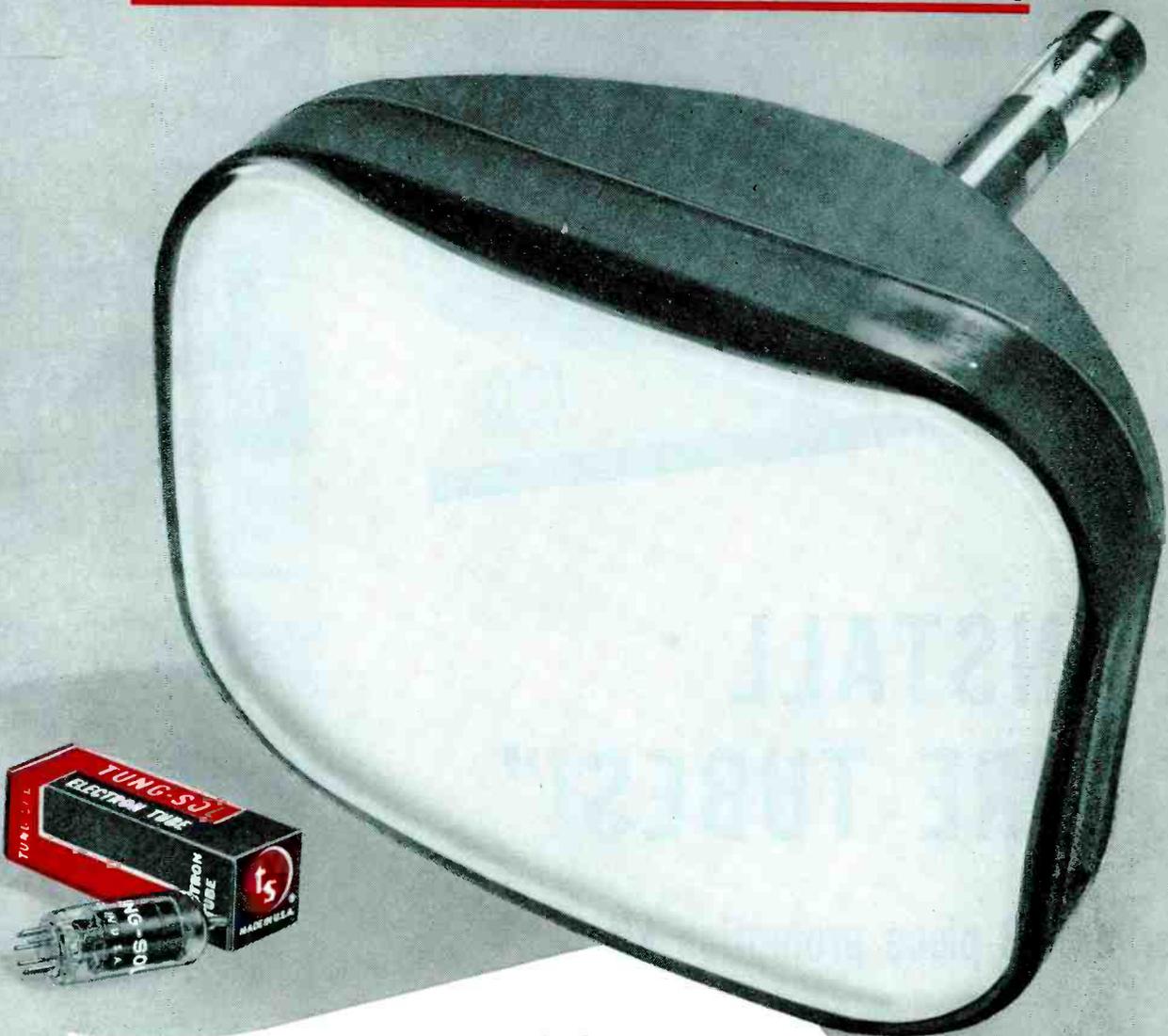You can build a reputation on Tung-Sol Quality



Tung-Sol Picture Tubes have these outstanding quality features

Gun made of best grade non-magnetic steel.

Glass bead type assembly is stronger both mechanically and electrically — gives greater protection against electrical leakage.

Rolled edges in gun minimize corona.

Custom built stem with greater spacing between leads assures minimum leakage.

Low resistance of outside conductive coating minimizes radiation of horizontal oscillator sweep frequency.

Double cathode tab provides double protection against cathode circuit failure.

Selected screen composition resists burning (X pattern).

Rigid control of internal conductive coating provides utmost service reliability.

Designed for use with single or double field ion trap designs.


One-piece construction of parts assures better alignment.

Maximum dispersion of screen coating assures uniform screen distribution.

TUNG-SOL ELECTRIC INC., Newark 4, N. J. Sales Offices: Atlanta, Chicago, Columbus, Culver City (Los Angeles), Dallas, Denver, Detroit, Newark, Seattle
TUNG-SOL makes All-Glass Sealed Beam Lamps, Miniature Lamps, Signal Flashers, Picture Tubes, Radio, TV and Special Purpose Electron Tubes and Semiconductor Products.


are you ready... **ALLEZ OOPS!**

You'd better be ready for a big turnover this fall, because REGENCY is flipping thousands of interested customers right into your hands! **LIFE! HOUSE BEAUTIFUL! HOUSE AND GARDEN! ATLANTIC MONTHLY! SATURDAY REVIEW! AND NATION-WIDE TELEVISION!** Aimed at FIFTY MILLION customers! This biggest-ever promotional program is comprised of the kind of sales-stimulating REGENCY advertising that has always proved so effective for you! And you'll hear about and see more of this functional merchandising program in the sales packed months ahead.

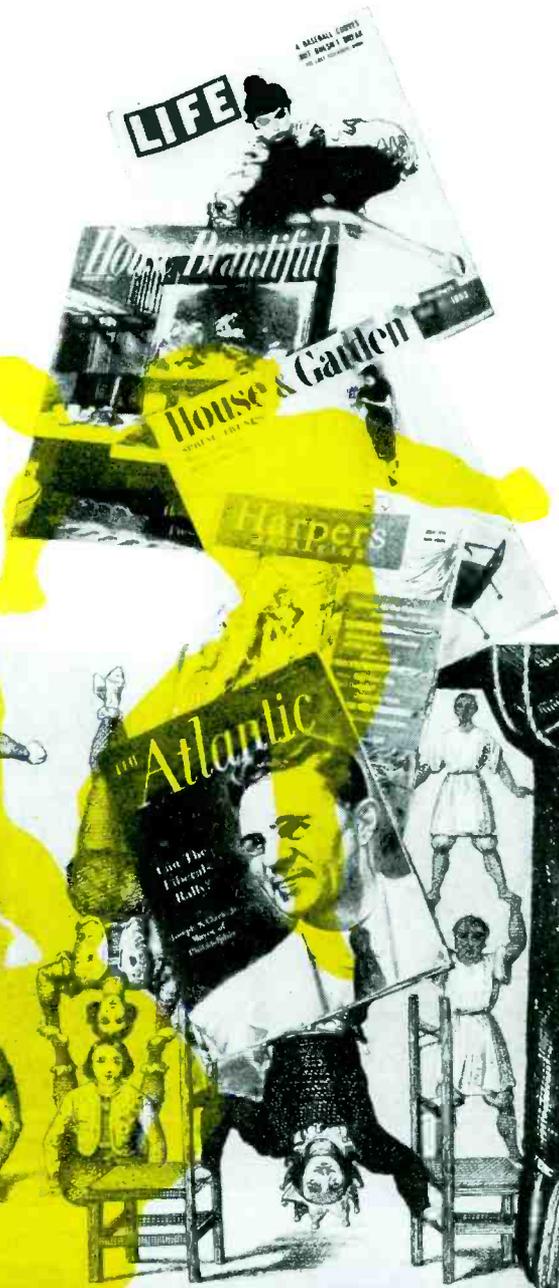

Regency
DIVISION OF I.D.E.A., INC.


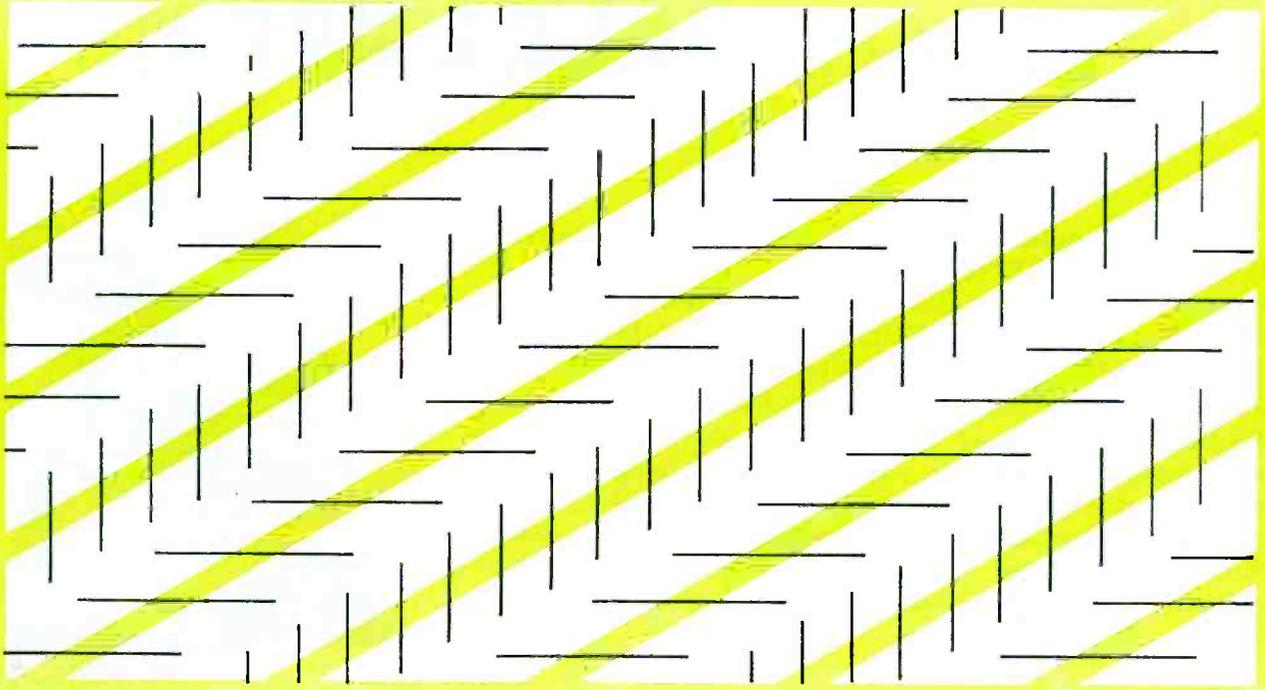
Makers of VHF Boosters, FM Boosters, UHF Converters, Professional High Fidelity Equipment and Remote Control for Television



THINGS ARE NOT AS THEY SEEM...

The long lines are strictly parallel—that they appear otherwise is an optical illusion.

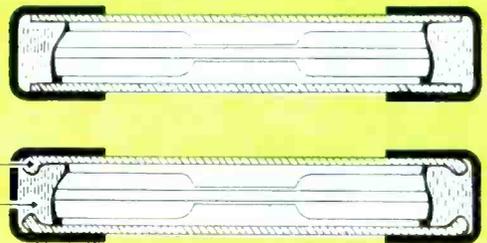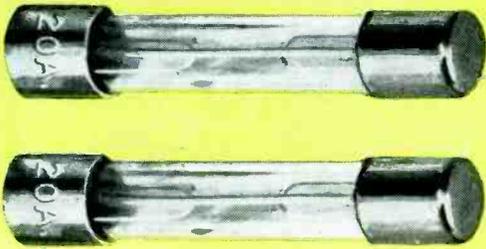This fuse merely has the metal caps cemented to the glass.



The difference between these two fuses is no illusion . . .


This Littelfuse has the caps locked to glass like this.

The ends of the glass are formed^A. The solder which is bonded in a separate operation to the cap reflows through the small aperture and spreads out to form a permanent collar-button lock^B between cap and glass—impervious to moisture and vibration. The exclusive Littelfuse feature eliminates fuse failure due to loose caps.

LITTELFUSE

DES PLAINES, ILLINOIS

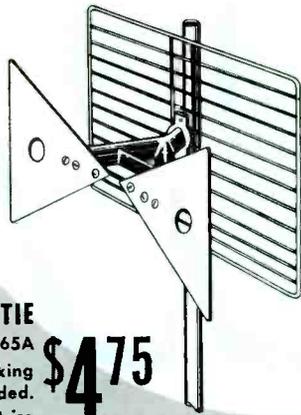
Littelfuse leads all other fuse manufacturers in design patents on fuses. Lock-cap assembly patent no. 1922642



Admiral BOW TIE
UHF Antenna, No. AN65A

Each antenna furnished with stacking bar. Mast mounting bracket included. Mast not included. Suggested List Price

\$4.75

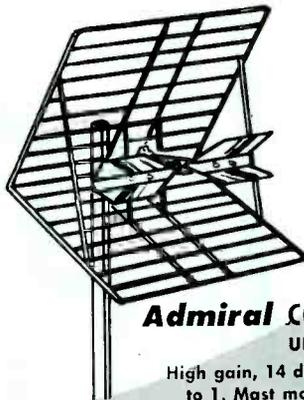

Admiral CORNER REFLECTOR
UHF Antenna No. AN56A

High gain, 14 db. Front to back ratio 15 to 1. Mast mounting bracket included. Mast not included. Suggested List Price

\$9.95

Admiral all-channel UHF antennas


HIGH GAIN

LOW COST

Now you can make an extra profit on installations using these high gain UHF antennas. In good signal areas, the Admiral Bow-Tie No. AN65A gets excellent reception on any of the 70 UHF channels...and lists for only \$4.75! For troublesome locations, where ghosts, reflections and interference are encountered, install the Admiral Corner Reflector Antenna No. AN56A. It lists for only \$9.95.

Both these antennas are made with aircraft aluminum antenna elements and vibration-proof reflectors. Both come completely assembled, ready to mount. "A-frame" insulators provide plenty of free air space around elements. The units have high mechanical strength, low wind resistance, and are treated to resist weathering. They can be easily fastened to existing masts and towers.

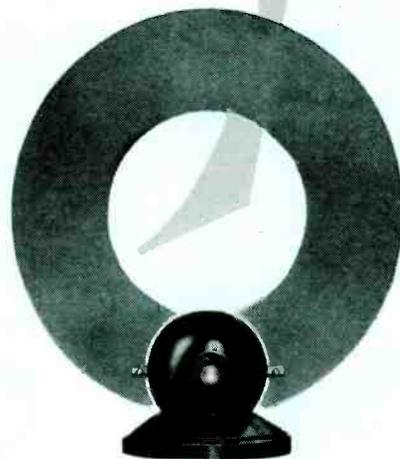Where an indoor UHF antenna is needed, give your customer the Admiral Target No. 94A10-7. Smartly styled in rose-gold colored anodized aluminum with mahogany phenolic base, it stands only 10 inches high. The base is weighted and felt padded...can be placed on top of receiver...picks up all UHF channels. Order by part number from your Admiral distributor.




Admiral TARGET
Indoor Antenna No. 94A10-7
Complete with lead-in
Suggested List Price

\$4.95

Admiral Corporation
Accessories and Equipment Division • Chicago 47, Illinois

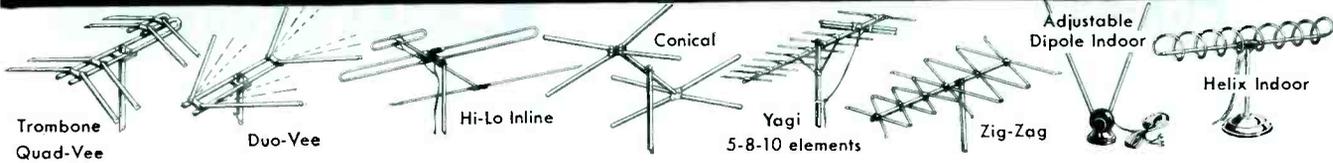
A COMPLETE LINE OF ADMIRAL TV ANTENNAS . . . NOW AVAILABLE FROM YOUR ADMIRAL DISTRIBUTOR



NEW!

4 P.E.C.* KITS

(NO EXTRA CHARGE FOR CABINETS)

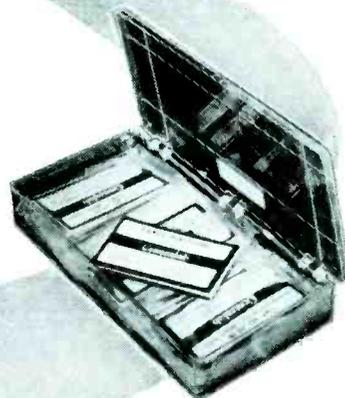


PCK-18 18 P.E.C. units. Replace 42 old-style resistors and 52 old-style capacitors. Net - - - - - **\$9.00**



PCK-110 110 P.E.C. units. Replace 255 old-style resistors and 52 old-style capacitors. Net - **\$55.80**

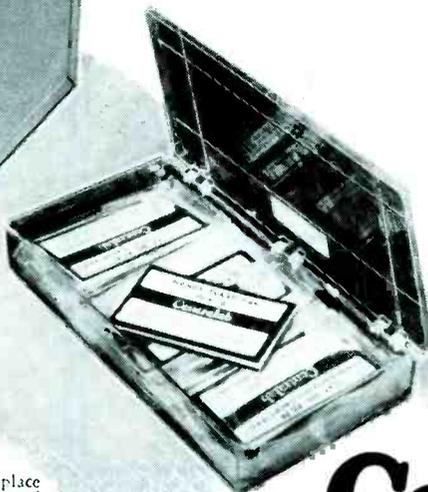PCK-220 220 P.E.C. units. Replace 525 old-style resistors and 620 old-style capacitors. Net **\$115.80**



Handy P.E.C. Guide No. 2 is included with each kit. Shows part listings, schematics, and test data.



Write for a list of the Centralab distributors in your area who have P.E.C. Kits.

PCK-45 45 P.E.C. units. Replace 106 old-style resistors and 133 old-style capacitors. Net - **\$24.00**

Centralab

A Division of Globe-Union Inc.

908J E. Keefe Avenue • Milwaukee 1, Wisconsin
In Canada, Box 208, Ajax, Ontario

*Trade Mark — Printed Electronic Circuit



TO SELL MORE MASTS

be a **BAKER** Dealer


Sales pick up quick when you stock Baker Television Masts—Most in demand by dealers.

Dealers prefer Baker 10', 20', and 30' television masts because they are better engineered and better built for quicker sales, quicker installation and more complete buyer satisfaction.


And not only are Baker masts built better, sold quicker and installed faster but they are priced better too.

BAKER 20' AND 30' TELESCOPING MASTS

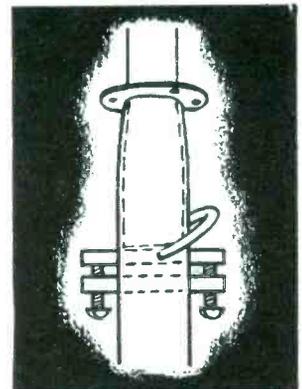
The Baker telescoping masts feature an exclusive patented Baker joint for quicker, easier vertical erection eliminating cumbersome tip-ups. The sections stop and lock automatically in place when fully extended and will not pull completely out. The special snap action safety catch prevents sections from sliding back during erection. Installer has hands free.



Exclusive Baker joint

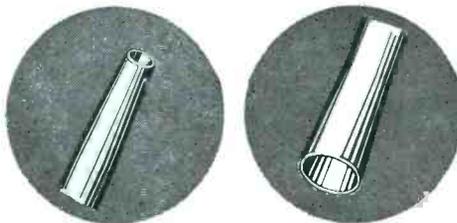

◀ **10' FITTED END MAST**

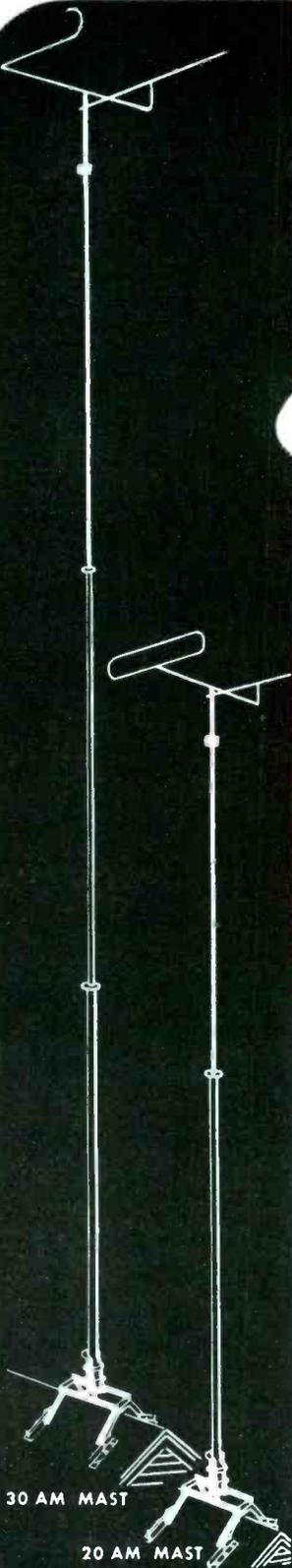

**FOR MORE MAST SALES AND PROFITS—
BE A BAKER DEALER**

SEND FOR COMPLETE DEALER INFORMATION TODAY. →

BAKER MFG. COMPANY
EVANSVILLE, WISCONSIN

BAKER MFG. COMPANY
DEPT. B
EVANSVILLE, WISCONSIN


Please send me complete information concerning
Baker Television Masts

Name _____

Company _____

Address _____

City _____ Zone _____ State _____

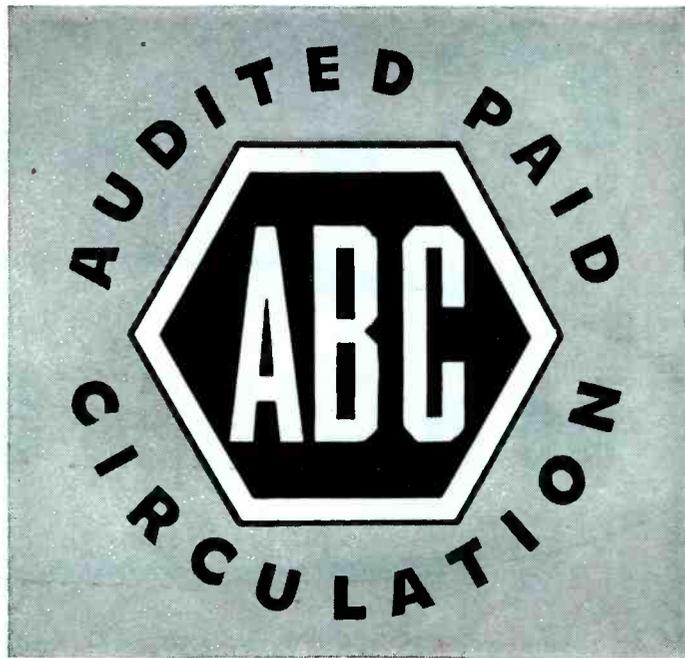

The Hallmark of Circulation Value

Three thousand four hundred and fifty advertiser, agency and publisher members of the Audit Bureau of Circulations have a voice in establishing and maintaining the standards responsible for the recognition of this emblem as the Hallmark of Circulation Value. It represents the standard of value that these buyers and sellers of advertising space have jointly established as measurement for the circulation of printed media.

The basis for arriving at the advertising value of a publication is the Bureau's single definition of net paid circulation. With this as the standard, the circulation records of A.B.C. publisher members are audited by experienced circulation auditors. As specified in the Bureau's Bylaws, A.B.C. auditors have "access to all books and records."

Subscription and renewal orders, payments from subscribers, paper purchases, postal receipts, arrears are among the

publisher's circulation records that are painstakingly checked by auditors and the resulting data are condensed and published in A.B.C. Reports.

Experienced space buyers use the audited information in A.B.C. Reports as a factual basis for their decisions in evaluating, comparing and selecting media. The FACTS in A.B.C. Reports for business publications include: • How much paid circulation • How much unpaid distribution • Occupational or business breakdown of subscribers • Where they are located • How much subscribers pay • Whether or not premiums are used • How many subscribers in arrears • What percentage of subscribers renew.

This publication is a member of the Audit Bureau of Circulations and is proud to display the Hallmark of Circulation Value as the emblem of our cooperation with advertisers. Ask for a copy of our A.B.C. Report and then study it.

SEND THE RIGHT MESSAGE TO THE RIGHT PEOPLE

Paid subscriptions and renewals, as defined by A.B.C. standards, indicate an audience that has responded to a publication's editorial appeal. With the interests of readers thus identified, it becomes possible to reach specialized groups effectively with specialized advertising appeals.



SERVICE

A. B. C. REPORTS — FACTS AS A BASIC MEASURE OF ADVERTISING VALUE

sees all...

tells all...



TEL-OHMIKE®

capacitor-resistor analyzer

"Better than a crystal ball" . . . that's what TV and radio service technicians everywhere are saying about the sensational Sprague TO-4 Tel-Ohmike Capacitor-Resistor Analyzer. It *sees all, tells all* with its resistance and capacitance bridges using magic eye balancing . . . direct meter readings of leakage current and insulation resistance . . . power factor measurement . . . continuously adjustable test voltage for checking electrolytics at exact rated voltage . . . push-button range selection.

Tel-Ohmike's many other *plus* features in-

clude capacitor measurements up to 2000 mf., with an exclusive special low range of 1 mmf. to 100 mmf.; resistance readings from 2.5 ohms to 25 megohms; and automatic capacitor discharge upon release of all push-buttons for greater safety.

This handsome laboratory-type instrument is sturdy, reliable and a cinch to use—and it's priced right!

See it in operation at your Sprague distributor's TODAY . . . or write for descriptive circular M-499 to:

ONLY
\$73⁵⁰

SPRAGUE PRODUCTS COMPANY

61 Marshall Street • North Adams, Massachusetts

don't be vague . . . ask for

SPRAGUE

ACCEPT NO SUBSTITUTES! There is a Sprague distributor in every sales area in the U.S. Write for name of nearest source of supply today.

WORLD'S LARGEST CAPACITOR MANUFACTURER




Servicemen! Here's Your Sylvania

T-N-T CHEST

(TUBE AND TOOL)

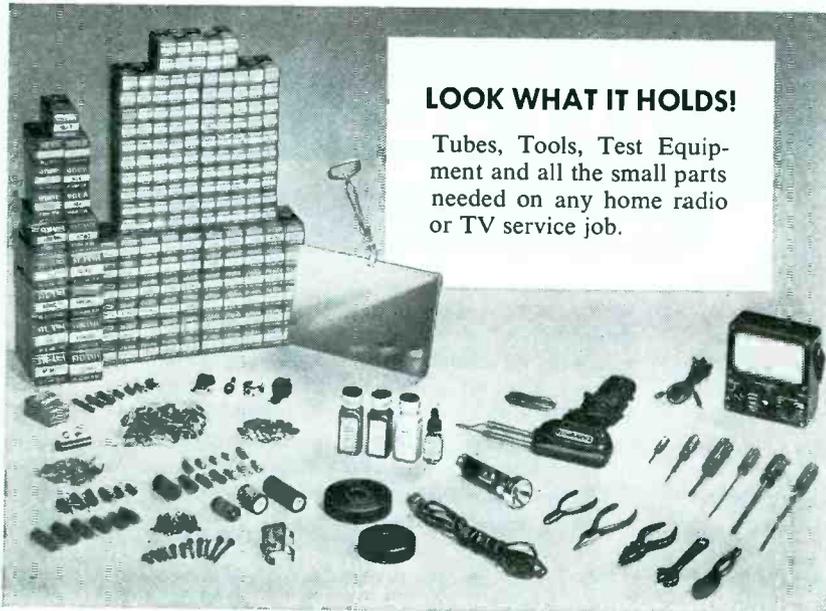The Most Valuable Service Aid You've Ever Seen!



Talk about a useful servicing aid . . . this Sylvania T-N-T (Tube and Tool) Chest is really it! Carries more tubes, tools and parts than any chest on the market!

LOOK AT THESE FEATURES:

- Bass and fir plywood case
- Waterproof Du Pont Fabrikoid cover
- Holds 187 receiving tubes
- Lightweight folding aluminum tool and parts tray
- Unbreakable plastic handle
- Brass-plated hardware
- Room for mirror and ohmmeter
- It's a complete, portable service shop!

ACT NOW . . . Offer Limited!

This chest is now yours for only \$5.00 and 30 Sylvania Premium Tokens. Offer good only between August 1st and November 15th. See your Sylvania Distributor who has these kits now.

SYLVANIA

Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

LIGHTING • RADIO • ELECTRONICS • TELEVISION

In Canada: Sylvania Electric (Canada) Ltd.
University Tower Building, St. Catherine St., Montreal, P. Q.

Remember, you get 1 Sylvania Premium Token with every 25 receiving tubes or with every picture tube you buy.

HIGHEST POWERED...

MOST RUGGED

of all rotors

the GREAT, NEW

jeb

ROTOR

model JEB-10

BIGGER MOTOR — (with 3/4" lamination) develops 40 ft. lbs. torque at antenna mast... drives heaviest arrays!

MOISTURE-TIGHT — completely closed aluminum housing with gasket seal against entrance of atmosphere.


RUST-PROOF thrust bearings... all parts anti-rust finished — lifetime factory lubricated.

POSITIVE ALIGNMENT — gears are locked at both ends of shaft; they're bigger, broader — for smoother rotation.

NO DRIFT — 2000% greater braking surface! Also electric cut-offs for strain-free stop at end of rotor travel!

Package becomes attractive display!

\$44⁹⁵
List

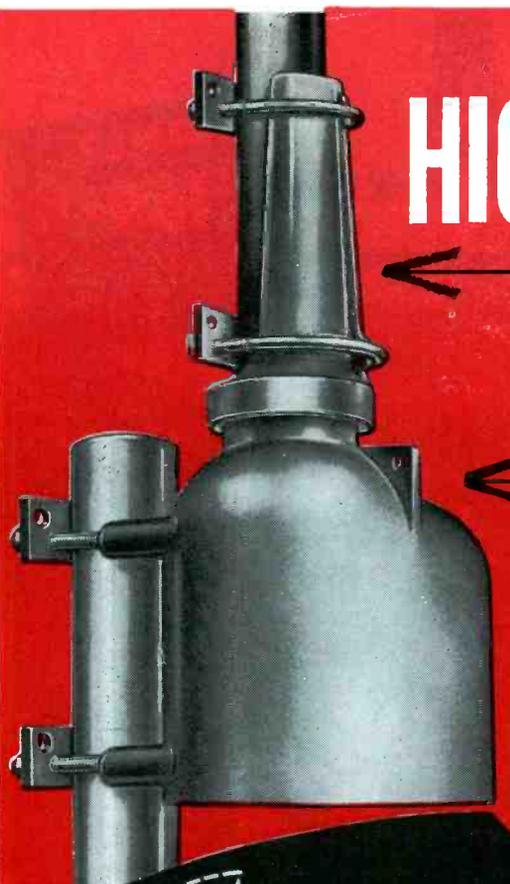

CONTROL CASE—just 2 1/2" high; mahogany color; one switch instantly reverses or stops rotor.


jeb

SALES CORPORATION
BROOKLYN 37, NEW YORK

RCA WO-88 A...

ONLY \$169.50
Suggested User Price
Complete with Matched
Probes and Cables

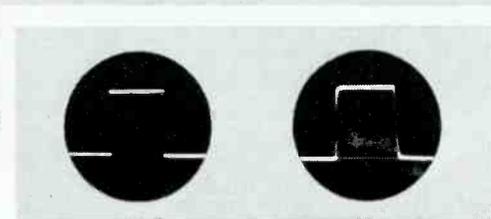**Read P-P Voltage
as you observe
TV wave-shapes!**



Unretouched photographs of 60-cycle and 50 Kc square waves reproduced on screen of WO-88A. Note fast retrace.



**INSIST UPON THESE
IMPORTANT FEATURES . . .**

- Direct-coupled, push-pull, two-stage vertical amplifier; push-pull horizontal amplifier.
- Frequency-compensated and voltage-calibrated attenuators.
- Front-panel source of 1-volt peak-to-peak calibrating voltage.
- Graph screen scaled directly in peak-to-peak voltage.
- Metal shield enclosing CRT gun to minimize hum-pickup from stray fields.
- Plus and minus internal sync.
- Built-in 60-cycle sweep with phasing control.

SPECIFICATIONS -

- Deflection Sensitivity: (vertical amplifier) 25 rms millivolts or better per inch.
- Vertical Amplifier Frequency Response: Flat from dc to 100 Kc; within -3 db at 500 Kc; within -10 db at 1 Mc.
- Input Resistance and Capacitance: 10 megohms and 9.5 uuf with WG-216B Low-Capacitance Probe.
- Sweep-Circuit Frequency (four ranges): 15 cps to 30 Kc.
- Square-Wave Response: Negligible tilt and overshoot.
- Power Supply: 105/125 volts, 50/60 cycles.
- Size 13 1/2" high, 9" wide, 16 1/2" deep. Weight only 25 lbs (approx.).

**ESSENTIAL
for Critical
TV Deflection
Circuit**

Measurements, the

New WG-216B Low-Capacitance Probe gives the WO-88A an overall input resistance of 10 megohms shunted by less than 10 uuf.

The WO-88A combines the features required for TV receiver servicing, and the high stability and ruggedness essential for continuous production-line duty.

The outstanding feature of the WO-88A is its remarkably true square-wave response, obtained by adequate band-width, negligible phase shift, and a complete absence of peaking circuits. Vertical and horizontal sync pulses, as well as other complex wave forms, are reproduced with fidelity characteristic of expensive laboratory instruments. Furthermore, uniform frequency response is maintained over the entire range of the attenuators.

The two-stage dc vertical amplifier has more than enough gain for all usual applications. Moreover, all of the gain is useable because the input circuits are shielded against extraneous noise and hum right out to the probe tips. Push-pull circuitry in both stages of the vertical amplifier minimizes "line bounce"; and direct cou-

pling provides instantaneous "recovery" time.

For operating convenience, the controls for push-pull balance, astigmatism adjustment, and interstage dc coupling are accessible from outside the cabinet.

Voltage measurements and wave-shape observations can be made simultaneously with the WO-88A. A front-panel terminal provides a 1-volt peak-to-peak reference voltage; the green graph screen is scaled in peak-to-peak voltage divisions, which are multiplied by the settings of the step attenuator to determine the voltage.

The WO-88A incorporates other quality 'scope features such as fast retrace, 60-cycle sweep and phasing, and a shield around the CRT gun.

For complete details on the WO-88A, see your RCA Test Equipment Distributor, or write RCA, Commercial Engineering, Section 56JX, Harrison, New Jersey.



RADIO CORPORATION of AMERICA
TEST EQUIPMENT
HARRISON, N. J.

FOR ALL OF TODAY'S REPLACEMENT CONTROL NEEDS



IRC Volume Control Plant, Asheville, North Carolina.

Name your requirement; it's in full production now at IRC's new volume control manufacturing plant. From no other single source can you get such wide replacement coverage. And no other replacement control gives you the IRC combination of easy installation and trouble-free performance.

Compare IRC's Replacement Control Line with any other:



For Widest Replacement Coverage Type Q Volume Control

82 values—7 tapers—give greatest TV, AM, FM coverage with least stock. Flatted, knurled and slotted Knobmaster Fixed Shaft fits most knobs without alteration. 13 Interchangeable Fixed Shafts give fast conversion to "specials" with fixed shaft security. Small $\frac{1}{4}$ " long bushing and compact $\frac{3}{16}$ " design ideal for small sets—yet handle large set needs as well. Cushioned-turn rotation. Quiet element. Handsome appearance.



For Fast Assembly of Ganged Controls IRC MULTISECTIONS

In just a few minutes you can assemble standard duals, triples, even quadruples—with IRC Multisections and Q Controls. Simply remove control cover and attach Multisection. Over 15,000,000 combinations. 20 resistance values. Switches can be added. Use to provide low-cost L Pads and T Pads.




Factory-Assembled IRC EXACT DUPLICATES

IRC's complete line includes 492 Factory-Assembled Exact Duplicate Concentric Duals. Mechanical fit and electrical operation double-money-back guaranteed—specifications are based on set manufacturers' procurement prints. Resistance values are matched; tapers are closely followed; shaft lengths are never less than manufacturers' nominal—never more than $\frac{1}{16}$ " longer. Cover more than 5,000 TV sets. Carbon and wire wound.

For Concentric Duals in Less Than A Minute IRC CONCENTRIKITS



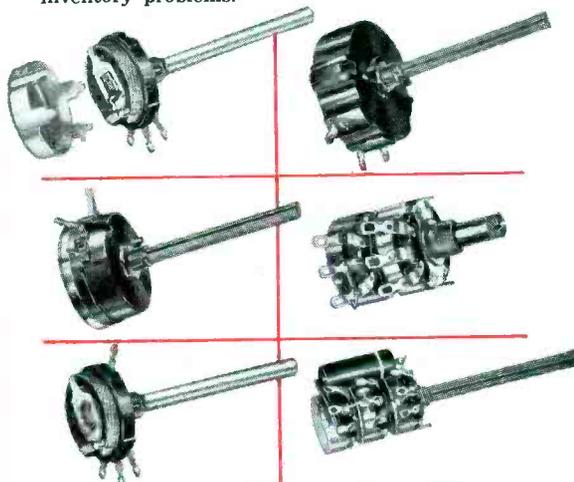Here's coverage of more than 5,000 TV models. Revolutionary 4-piece Universal Concentrikits assemble with shafts and elements in less than a minute to give you the exact duplicate replacement control you want. Mechanical fit and electrical operation double-money-back guaranteed. Assemble both carbons and wire wounds. Fewer inventory problems.



For Special Purpose Controls IRC's Complete Line

2-Watt Wire Wounds—2 styles, full rounded shaft and Knobmaster shaft. **High Voltage Controls**—2-watt carbon-element control with Knobmaster shaft. **4-Watt Wire Wounds**—2 styles, short, knurled and slotted shaft or Knobmaster shaft. **TV Attenuators**—Carbon-element control for adjustment of signal input. **TV Centering Controls**—2-Watt Wire Wound Control with centering tap. **Loudness Controls**—Continuously variable, bring higher fidelity to ordinary audio.

No other brand of replacement controls offers you wider variety—greater efficiency. Send for New IRC Control Catalog DC1D.

For one-source-service on all your control requirements, order from your IRC Distributor.

INTERNATIONAL RESISTANCE COMPANY

413A N. Broad Street, Philadelphia 8, Pa.
In Canada: International Resistance Co., Ltd., Toronto, licensee

Whenever the Circuit Says



RAYTHEON

the new

SERVICE SAVER

SPEEDS SERVICE — MAKES MONEY — PLEASES CUSTOMERS

How'd you like to know what's wrong with a customer's TV receiver *before you make your service call?* You do with the new RAYTHEON TV SERVICE SAVER plan.

Here's how this wonderful new Raytheon servicing method works:

Both you and your customer have booklets in which are photographs showing 40 different picture conditions that may occur on the screen of a defective TV receiver. From 90 to 95% of all the troubles that may develop in a TV receiver are covered by these pictures. Illustrations are numbered and when a set falters, the

customer simply finds the picture in the booklet that matches the condition on the screen and then calls you and tells you what number it is, and which of 5 sound conditions exist.

Your booklet and a wall chart which you can place near your phone show the same set of numbered picture patterns, and in addition the booklet explains exactly what tubes, components or circuits may be causing the trouble and suggests what and where to test.

This pre-call knowledge of what ails a receiver helps you to greater profit in three ways: (1) You can go on a job with complete technical information about the required repair; (2) You can go on the job with all necessary parts and tubes; (3) You can clean up nuisance calls and avoid many needless call-backs by telephone. Then, too, it means satisfied customers — customers who see you go right to the root of the trouble and make repairs quickly and expertly.

Be sure to ask your Raytheon Tube Distributor how you can get in on this exclusive servicing asset — the RAYTHEON TV SERVICE SAVER plan. Act now, and be the first in your locality.



RAYTHEON

RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division
Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

Excellence in Electronics

RAYTHEON MAKES ALL THESE:

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • NUCLEONIC TUBES • MICROWAVE TUBES

RADIO · TELEVISION · ELECTRONIC
SERVICE

TO EARN the *ABC* insigne displayed here, *SERVICE* has joined with more than 2,500 other publications, with many of the companies who talk to you through advertising in our pages and with professional advertising agencies who prepare their messages, to set firm, well-understood rules through mutual agreement for the important intangible commodity called *circulation*. As a reader of *SERVICE*, you benefit directly by our *ABC* membership. How?

Before 1914, the word *circulation* had dozens of meanings. *Circulation* was so loosely defined that one would have found clear facts almost unobtainable.

Then, in comparing rival publishers' circulation claims, or trying to determine if a publisher's advertising rates were fair and reasonable, one found it necessary to match page rates asked with such claims as . . . "First in buyer coverage" . . . "Vast circulation of proven reader interest" . . . "Preferred by more verified readers" . . . "Complete nation-wide coverage," and then doubt the validity of one's own conclusions.

The advertising and publishing industry thirty-nine years ago successfully met this critical need for dependable, standardized circulation figures instead of optimistic coverage claims. To bring order out of chaos that existed before 1914, either of two solutions was possible.

Every business man knows the first possibility—regulation by government. Laws could have been enacted and circulation practice restricted by government edict.

But, wisely, our business chose a better way—voluntary self-regulation *through mutual understanding and by self-imposed rules of good practice*.

The instrumentality set up was the Audit Bureau of Circulations; the first step in the Bureau's work, an accurate definition of just what *net paid circulation* meant. With this as a starting point, answers to important questions such as: How much circulation as measured by this definition? How much do people pay to get this publication? Where does the publication go? What do the readers do to earn their livings? became possible on an industry-wide basis. Sixty-five skilled circulation *ABC* auditors today answer such questions accurately for business men.



Methods for obtaining circulation, once limited only by the ingenuity and consciences of publishers, are disclosed today. The fact that *ABC* membership makes circulation-getting actively public, has discouraged marginal practices of dubious value. And any buyer of space can today form a considered judgment as to the advertising value of any *ABC* publication by going beyond summary paragraph 8 in its *ABC* report, and analyzing the precise audited figures in the other paragraphs.

Modern advertising practice is based on the *ABC*-audited facts that have made space-buying an investment in known values, and have made publication advertising the effective marketing instrument that lowers unit sales costs by increasing sales, and therefore production and employment in our dynamically-expanding economy.

But, you may ask: "What's in this for me? What do I get out of *your ABC* membership? I can see that you profit—show me where I come in."

Turn to the articles in this issue—and look at them for your answer. Ask yourself: "Is it information I want?" "Can they speed up my work?" "Do they contain ideas that can increase my net profit?" "Do they tell me clearly how to improve my efficiency?"

Your answer will almost always be "*Yes!*"

Why? Because you *paid good money* to read them! You invest your dollars with *SERVICE* to have regularly sent to you such current information on servicing problems and procedures.


The known and published subscription price you pay for *SERVICE* requires us constantly to seek and achieve editorial leadership to stay in business. Your needs keep us on our editorial toes. We must help and serve you to merit your continued patronage.

By subscribing, by renewing your subscription, and by reading *SERVICE*, you keep us on top, as an editorial leader—to make sure that you will always agree that to you, we're worth the *price of admission*.

For almost two decades *SERVICE* has been a member of the Audit Bureau of Circulations and proudly displayed the *ABC* emblem . . . a symbol of publication integrity.—L. W.

by G. H. FLOYD
 Electronics Division, General Electric


10-Watt 6/12-Volt

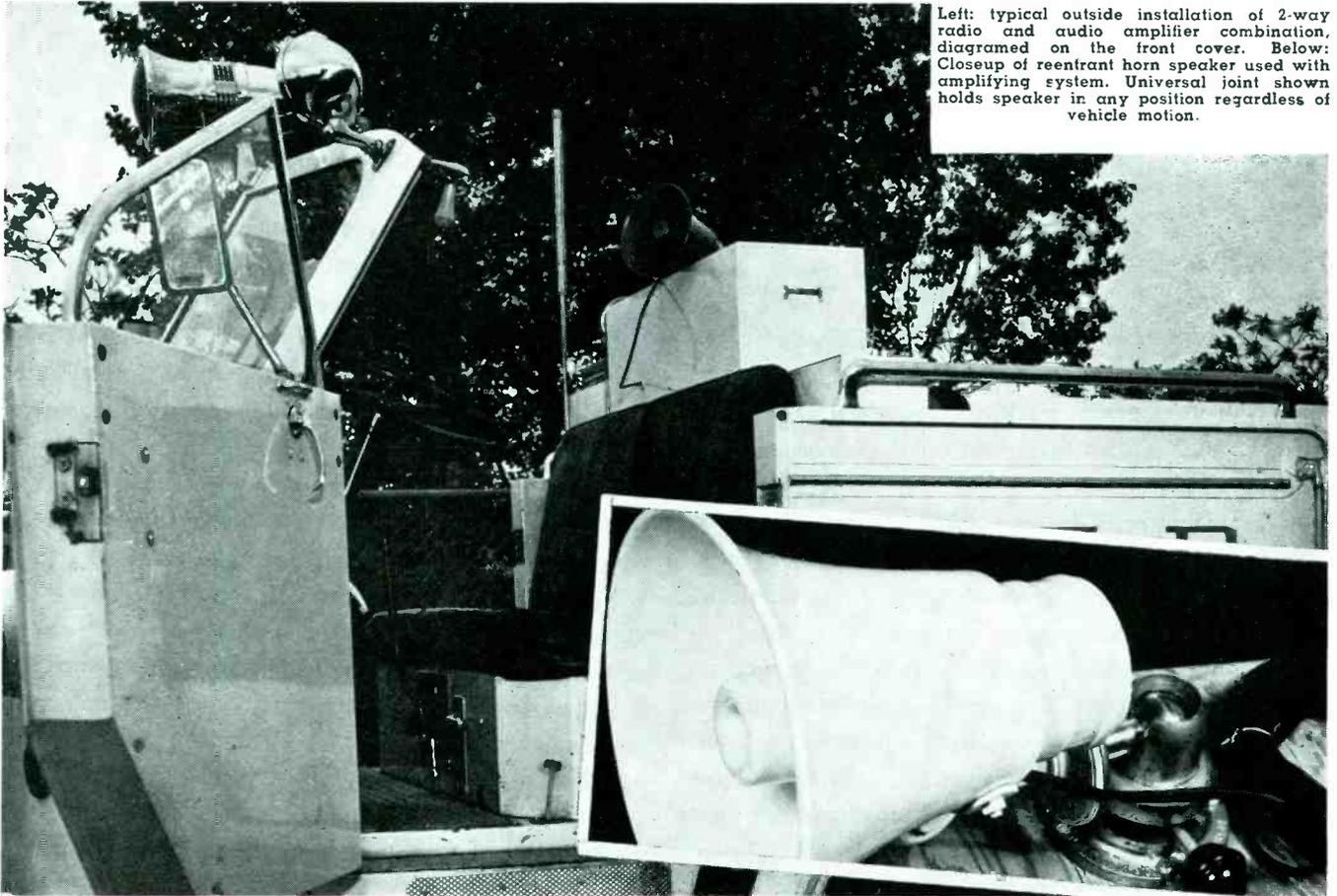

Left: typical outside installation of 2-way radio and audio amplifier combination, diagrammed on the front cover. Below: Closeup of reentrant horn speaker used with amplifying system. Universal joint shown holds speaker in any position regardless of vehicle motion.

(Below)

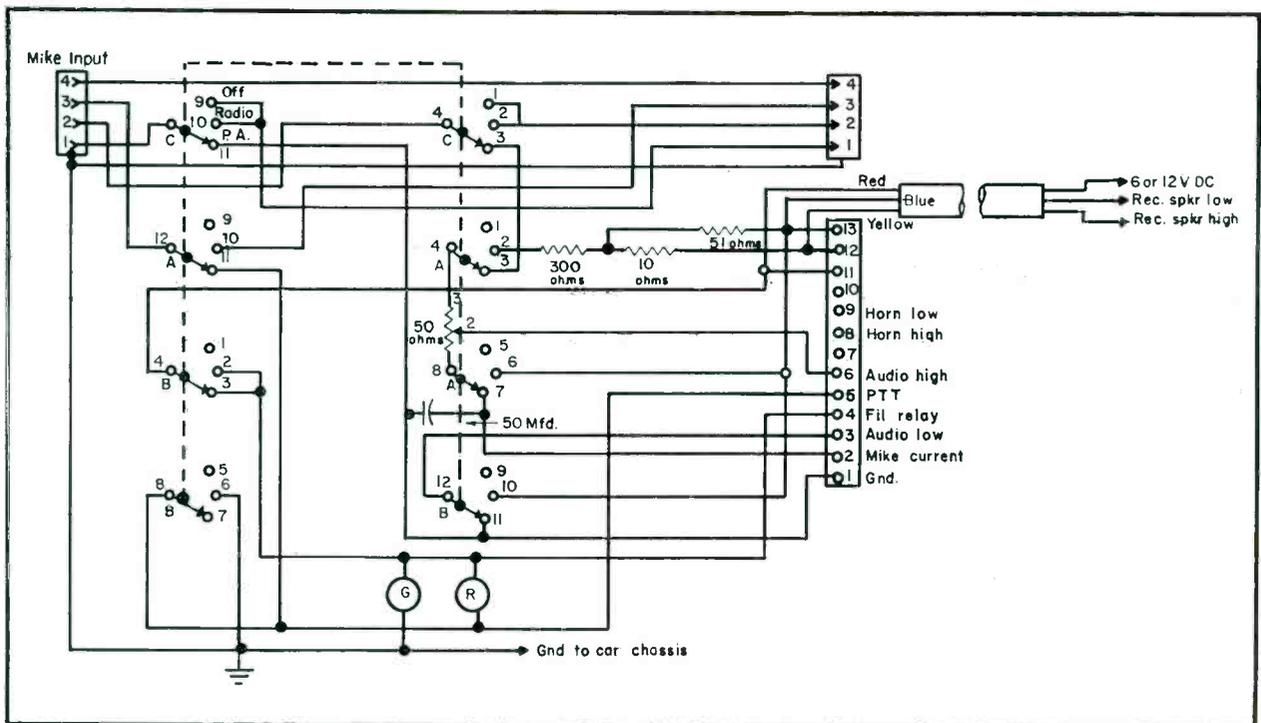Control unit schematic for 2-way mobile-system amplifier.



by J. C. GEIST



What Happened to the Will It Return

(Below)

Fig. 1. Video detector operating into a class A amplifier; peaking coils have been omitted for simplification.

(Right)

Fig. 2. Detection of sound modulation in AM: Carriers with sine-wave modulation, illustrating voltage relationships for two conditions of carrier modulation.

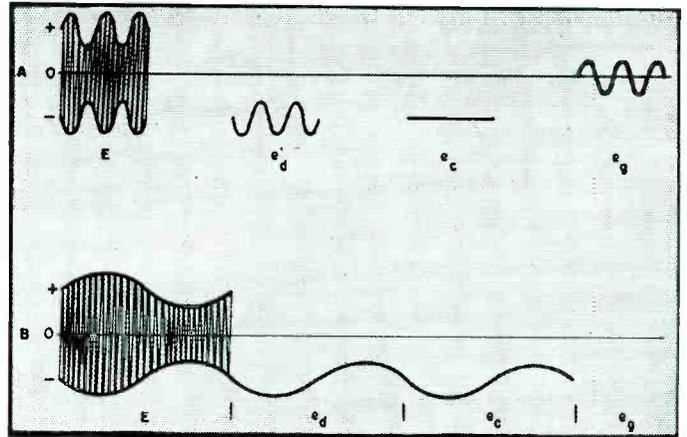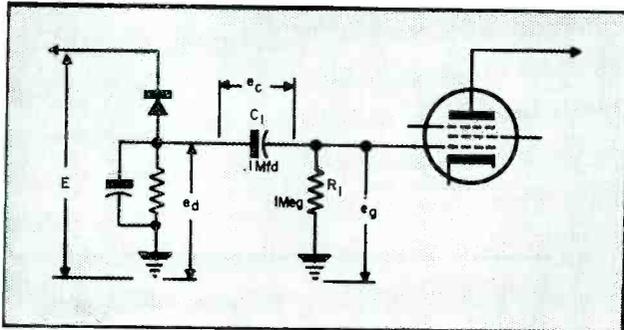

THE DESIGN CONCEPTS involved in TV receiver video *dc* restoration have changed considerably since television was introduced as a practical working system just after World War II. This new trend has been prompted by a demand for circuit simplicity and control ease, felt to be more important than faithful reproduction of average brightness levels.

To trace the relationship between reproduction requirements and circuitry let us review the process of demodulation and video amplification.

Stage-Coupling Time Constants

As a first, let us consider the video detector operating into a class-A amplifier shown in Fig. 1. Peaking coils have been omitted for simplification, since they are not pertinent to the discussion. Voltage relationships in the circuit for various conditions of carrier modulation are shown in Figs. 2 to 4. A carrier with sine-wave modulation is shown in Fig. 2. Let us assume that the modulation frequency in *a* of this illustration is 1,000 cps.

well within the operating range of the circuit. The voltage developed across the detector load, e_a , follows the peak value of the negative half of the carrier and is therefore a signal corresponding to the modulation signal superimposed on a *dc* voltage representing the average value of the carrier. The carrier frequency is eliminated by the detector load bypass capacitor. Voltage e_a is impressed across C_1 and R_1 in series. Under steady-state conditions, C_1 takes on a charge equal to the average value of e_a , as shown by e_c . That is, the total *dc* voltage drop is across the capacitor: no *dc* voltage is across R_1 , and no *dc* signal is applied to the grid of the video amplifier. C_1 offers very low impedance to the *ac* component of e_a , so the total *ac* voltage drop is across R_1 . This *ac* signal is impressed on the grid, as shown by e_g , and is amplified by the video amplifier. The charge on C_1 is not able to respond to the 1,000-cps modulation, because the rate at which it can change its charge is limited by the time constant of the cir-

cuit, which in this case is R_1C_1 or .1 second. Since the time required for the 1,000-cps signal to change from its maximum to its minimum value is only a small fraction of .1 second, the charge on C_1 cannot change rapidly enough to be affected by the signal.

Now let us assume that the modulation frequency in (b) of Fig. 2 is 1 cps. As before, e_a follows the value of the negative half of the carrier and constitutes a 1-cps signal superimposed on a negative *dc* voltage. In this case the time required for the modulating signal to vary from its negative peak to its positive peak is .5 second and C_1 is capable of changing its charge at this rate. Hence, all of the 1-cps voltage drop is across the capacitor, as shown by e_c , and none is across R_1 , as shown by e_g . In other words, the low-frequency response is determined by the grid-coupling time constant R_1C_1 and for this circuit performance would start to fall off at about 50-cps.

Fig. 3 shows the performance in the presence of a step increase in carrier level. As before, the detector follows

Searching Analysis of Restorer Systems and Design Philosophy, Recently Revised, Because Faithful Reproduction of Average Brightness Levels Has Been Found Secondary—in Monochrome Chassis—to Ease of Adjustment, Maintenance of Good Contrast and Circuit Simplicity: With Advent of COLOR, Where Faithful Reproduction of Brightness Levels Will be Necessary to Avoid Unnatural Coloring on Picture Tube Screens, the Restorer May Return

DC Restorer: with COLOR?

the peak values of the negative half of the carrier. Since C_1 cannot charge instantaneously, a step voltage is developed across R_1 , as shown by e_g . This signal gradually decreases to zero in about .2 second as C_1 takes on a charge equal to the new peak carrier level. The length of step function which can be faithfully passed to the grid then depends on the low-frequency response or time constant of the circuit. In this case any step function or square-wave duration longer than about .02 second (25-cps) will be noticeably distorted.

Let us now consider the performance of the circuit in the presence of a TV-signal, such as in Fig. 4. In this figure the spikes represent horizontal sync pulses. The video signal is representative of a dark object against a background gradually changing from light to dark. In (A) the change in background level is relatively fast, taking place in less than one field, as might be encountered in a scene with a light sky above a landscape, and hence represents a fundamental signal frequency of 60 cps. In a manner similar to that previously discussed, C_1 is holding a charge representing the average value of the carrier level as shown in e_c , and e_g represents a faithful reproduction of the ac component of the modulating signal. The circuit is therefore able to reproduce the relatively fast changes represented by the sync pulses; the black object and the changing background brightness. (It will be noted also that the bottom of the sync pulses are all at the same negative voltage level.)

The signal shown in Fig. 4b is similar to that in (a) except that in this case the change in background level is relatively slow, taking place over a large number of fields, as might be encountered as the background lighting of a scene shifts to a new darker level in a few seconds. Vertical sync pulses are not shown, to simplify the presentation. In this case, the charge on C_1 is able to follow the background level change as shown by e_c . This change therefore is of a lower frequency than can be passed by the circuit, and the voltage impressed on the grid includes only the signal representing the sync pulses and the dark

(Continued on page 86)

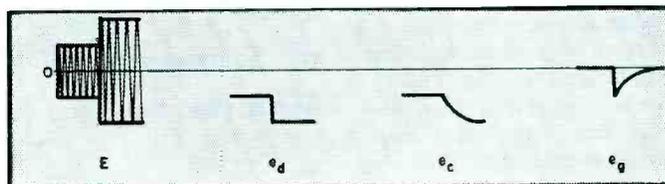


Fig. 3. Circuit performance in the presence of a step increase in carrier level.


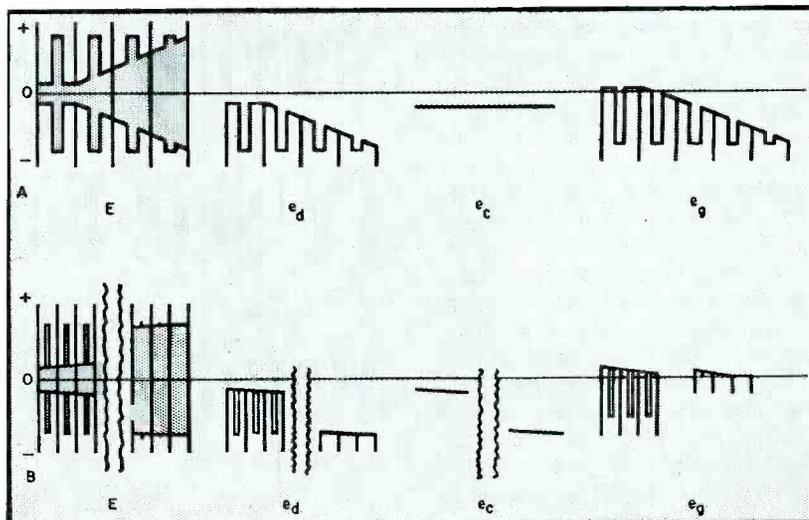



Fig. 4. Performance of the circuit in the presence of a TV signal. Spikes represent horizontal sync pulses.

Fig. 5. Significance of the elimination of the dc component of e_g in B of Fig. 4, when it is amplified and applied to the picture tube, is illustrated here. Curve represents the grid voltage versus beam current or brightness characteristic of a picture tube.

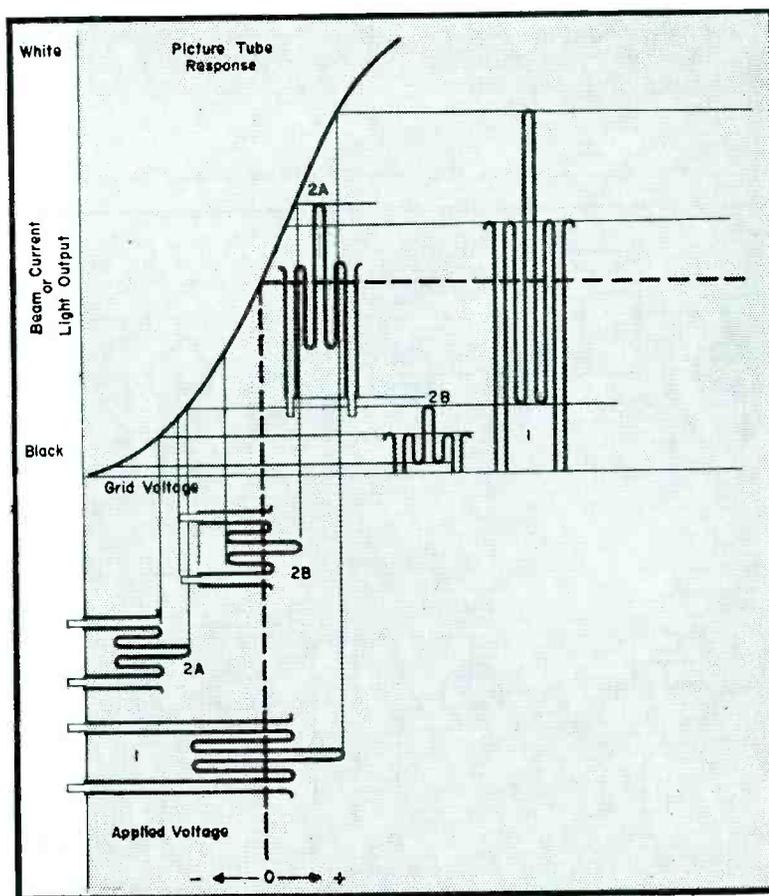

(Right)

Fig. 3. Typical video amplifier circuit that can be added to chassis to obtain proper picture polarity.

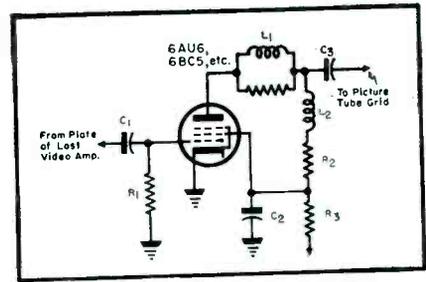

than that delivered by the receiver's video detector and consequently would overload the video amplifier, with resultant tearing or picture instability.

Coax Connectors for Inputs

Two coax input connectors (one used as a multiple) allow any number of monitor receivers to be bridged across the line. (If only one receiver is to be operated, increased stability and better contrast will result if a 75-ohm terminating resistor (see Fig. 4) is plugged into the multiple coax connector. This assumes, of course, that the line is a normal 75-ohm monitor bus, without previous termination at another unit.) If the monitor line has been previously terminated, the 75-ohm resistor must be left off at the receiver end to prevent double-termination and degradation of signal. If the receiver is to be a permanent installation, it is suggested that the terminating resistor be mounted at the receiver input.

Monitor for Switch Leads

The two leads used to connect the monitor selector switch (S_1) to the points indicated by (x) can be scrap pieces of 75-ohm coax line. (This coax section is not necessary insofar as matching the circuit impedance is concerned, but it does help to shield the video detector plate circuit and the amplifier grid leads. The leads to the audio jacks are somewhat longer, and

should be completely shielded to keep hum pickup at a minimum.)

Modification for Rebroadcast Use

The coupling capacitor C_1 (1 mfd, 600-volts, or larger) and its associated female coax connector permit use of the chassis for rebroadcasting. With this arrangement, signals picked up by air (from another vhf or uhf station) can be fed into a stabilizing amplifier and into the master control console, or directly into the console if it has sufficient gain. With normal input at the receiver's antenna, an output voltage of 1 volt, peak-to-peak should be obtained.¹

Coupling Capacitor Values

It is suggested that C_1 be at least 4 mfd to keep the vertical pulse wavefront as steep as possible. However, no serious depreciation in low-


frequency response will be detected with a 1-mfd capacitor. This capacitor, whatever the value used, must be paper, with a voltage rating of at least 600 volts, *dcw*.

Other Uses for Chassis

It can be seen that rather flexible operation can be obtained through the foregoing changes. In addition to the use described, the receiver's audio system can be fed from any desired source, independently of the video monitor input. The receiver can also be used as a master air monitor to feed a number of similarly modified receivers. As a studio monitor, the video input can be taken from either a local, network or remote distribution amplifier in the control room, while the audio can be fed from the regular audio console, remote or telephone cue line, or the program director's cue amplifier.

Circuitry Precautions

The main requirement in receiver conversion is that the input (or output) connections be such that the picture will maintain its proper polarity. Connecting to the *cathode* of the second half of the 12AU7 video amplifier in Fig. 1, for example, would result in 180° inversion, or a negative picture. If the particular receiver does not lend itself to conversion for the foregoing reason, a simple video amplifier (similar to Fig. 3) can be added to obtain proper picture polarity.

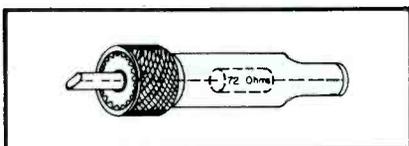


(Above)

Fig. 4. Construction of coax plug with line-terminating resistor. In circuit, shown in Fig. 1 (left), S_1 is a spdt toggle switch; J_1 , J_2 and J_3 are the female coax connectors; J_4 is a closed-circuit phone jack, and J_5 is an open-circuit phone jack.

(Right)

Fig. 5. Layout of parts on converted chassis.

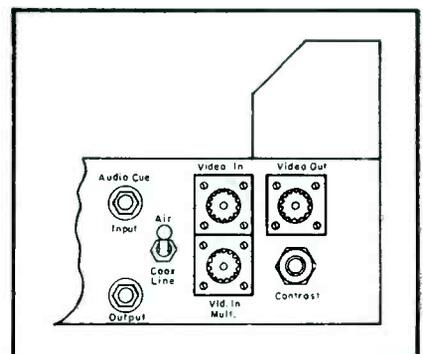

A Report on Dual-Track 2-Speed

First of a Series Detailing the Design, Operation and Servicing of Current Models

by D. S. CEVANS

MAGNETIC TAPE, not too long ago, completely restricted to involved and expensive equipment, is today being used in a host of simplified and popularly priced units that are highly efficient.

The trend has been sparked by the improvement in tape and the development of ingenious mechanical and electronic advancements including electrical switching, positive-action indicators, compact motors, wide-range amplifiers and allied accessories.

Most tape instruments now being made are dual-track type and can be used for single or dual speeds. Some have been so designed that tapes from high-grade tape libraries or from other tape instruments can be used without sacrifice of frequency response or dynamic range. One series¹ provides this interchangeability feature via an absolute alignment of the instrument azimuth to exactly $90^\circ \pm \frac{1}{8}$ of 1° , in addition to an exact tape speed control.

Five push-buttons, in a row, control all of the tape transport mechanisms in these models, and in this instance no relays are used.

An Alnico pm^2 erase has been included to provide a positive erase of undesired material from the tape, if desired, even though the material has been inadvertently recorded at excessively high levels.

Also included are a pair of neon indicators set by an exclusive system² to provide correct *normal* as well as correct *overload* indications.

In addition to a microphone input there is a *radio*, *pa* and *phono* input jack.

The frequency response and impedance termination of the radio, *pa* and *phono* inputs are such that two tape units³ can be connected together to make tape duplicates. The amplifiers of the tape recorders can also be used as *pa* systems when an external speaker is used.

In operation, to insure the full brilliance of recorded material, the *tone* control on these models is disconnected

while recordings are made, and thus the tape has the full frequency response of the source recorded upon it. The units feature bass and treble boosts, intentionally designed into the system so as to help compensate for most radio, microphone, etc., deficiencies. Yet, if one should ever be so fortunate as to record from a substantially flat source, the tone control can be adjusted to flatten out practically the region above 2 kc, and yet retain *bass* boost.

The response also varies with the volume-control setting, perhaps not as much to attain exact correlation to the Fletcher-Munson curves, but rather to overcome the deficiencies of microphones. For example, when recording for best signal to noise and best frequency response, one should hold the microphone about 8" away from the mouth while speaking. It will be found that the volume should be set at about 50% rotation; since the signal is quite high the full bass and treble boost can be used to assist the microphone to make an excellent life-like crisp recording. On the other hand, when recording at say 15' or 20' from the microphone it will be found that less treble and bass compensation is desirable to reduce hiss and noise and rumble.

Even line-voltage variations, particularly those encountered during field applications, have been considered in the design of these new models. To provide complete operation at all practical line voltages rewind time has been set at 2 minutes and 45 seconds for a full 1,200' reel (at 115 volts). The load so provided upon the motor and its oilite bearings is kept low enough to provide continuous service without overheating or overloading the motor or associated components.

The *stop* position on these models not only operates the self-actuating

brakes, but disengages *neoprene* idlers as well, to prevent flat spots on the idlers.

Recording is possible at either $3\frac{3}{4}$ or $7\frac{1}{2}$ ips. This together with dual track recording enables one to record as long as two hours on one 7" reel.

Tube Types Used

In one model³ four tubes are used in *play* position; a 5879 first preamp; 12AX7 as second and third stage amplifiers, a 6AQ5 as the fourth stage power amplifier, and a 6X4 full-wave rectifier. In *record* position the 5879 operates as a 40-kc bias oscillator.

Two other models in this series⁴ are considerably different. The bias is 80 kc, and different tube types are used.

In *play* position, a 12AY7 serves as the first and second stage preamp; a 12AX7 as the third and fourth stage amplifier (and phase inverter); two 6AQ5s are used in push-pull output, and 5Y3 is used as a full-wave rectifier.

In *record* position $\frac{1}{2}$ of the 12AY7 functions as a bias oscillator.

During development work, it was found that the very low hum of the 12AY7 was greater than desired in the high gain units; thus a special adjustable hum-balancing arrangement was inserted to reduce the hum another 6 to 12 db.

Since the signal picked up from the tape by the head is on the order of 150 to 400 microvolts, or about that obtained from a near-fringe television antenna, certain criteria exist for best design; namely, tube thermal noise, hum and in addition, microphonics.

These have been met through adequate shielding, circuit design, component, part placement and tube suspension to provide a gain of approximately 12 db greater than that required to produce 60 db output from a *normal* tape.

Normal Tape Signals

It has been found that signals from 4 to over 200 millivolts are adequate for making *normal* tapes when using the mike input. This is said to be adequate for controlled reluctance microphones, reluctance pickups, cera-

¹Wilcox-Gay Recordios 3A10, 3F10, 3F40.

²Pat. Pending.

³Wilcox-Gay 3A10, 3F10 and 3F40.

*Based on an exclusive analysis prepared by Edward Jahns, chief engineer of the Wilcox-Gay Corporation.

TAPE Recorder-Playback Equipment*

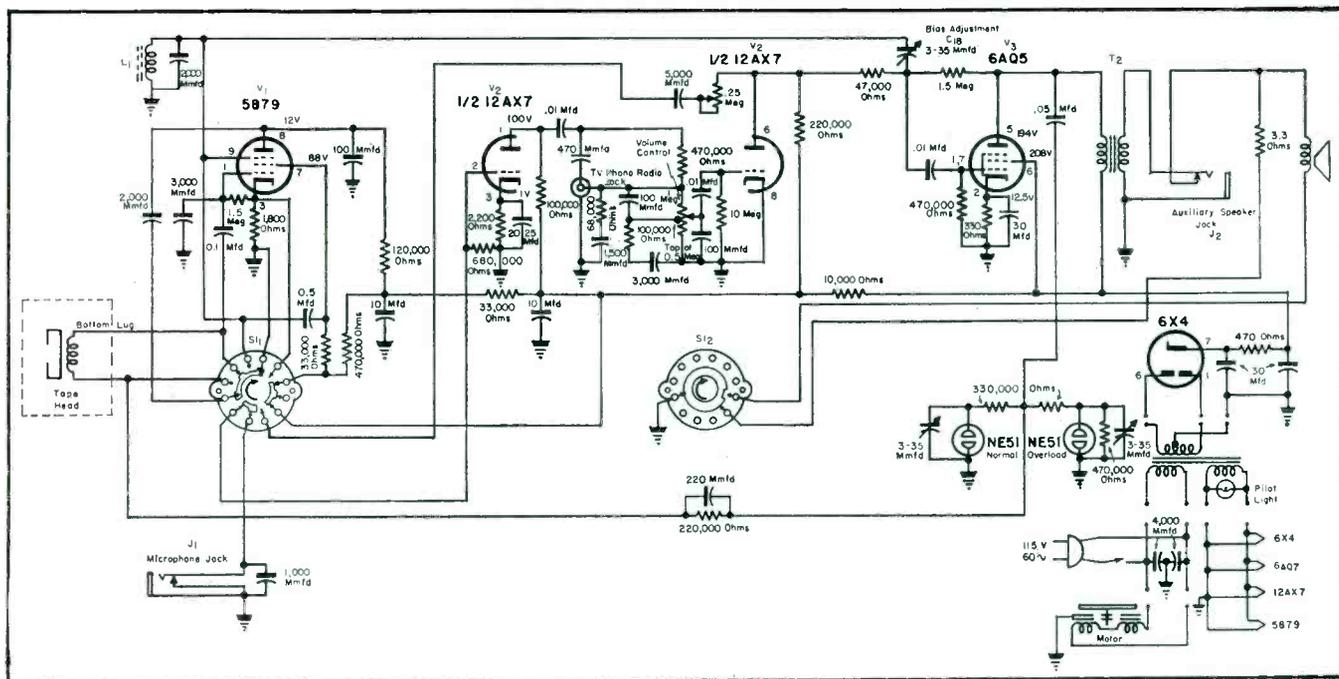


Fig. 1. Schematic of amplifying system used in Wilcox-Gay 3A01, which provides 2-watts undistorted output and 4-watts maximum.

mic and rochelle-salt crystals, as well as most dynamic microphones.

The second input handles signals of from 100 millivolts up to at least 30 volts *rms*.

Overloading Problem

Probably more tapes have been made poorly because of overloading them than all other reasons combined. This problem can be overcome by making a few trials to determine the correct level; adjusting the level so that the *normal* neon lights once for every three or four words which are spoken, and for music about once every five seconds, except when recording some passages in which case it should light even less often; and preventing the *overload* neon from lighting more than once every 20 or 30 seconds.

In repeated tests, it has been found that a properly made tape will have a greater dynamic range and lower noise level than any other medium and further does not deteriorate with replaying.

Fletcher-Munson Curves

Considerable data has been prepared reviewing the advantages or disadvantages of the Fletcher-Munson curves. It has been found that unless the sound pressure output from the speaker is taken into consideration, a

qualitative estimate of their action cannot be obtained. For one thing, the speakers and microphones furnished with these models display a decided increase in output at from 2 to 4 *kc*, as do practically all other microphones and speakers, regardless of size.

Speaker Capabilities

Enclosed speakers (5 x 7 and 6 x 9, respectively) are used in these units and are excellent for their size; but for maximum fidelity, it will be found

that large, well-baffled, external speakers are best.

Hi-Fi Possibilities

The foregoing is not meant to belittle the enclosed speakers, but rather to point out that fidelity, low inter-modulation distortion, low wow and flutter, high signal-to-noise ratio and wide range have been built-in to these recorders and a larger speaker system can capitalize on these features more effectively.

Fig. 2. Overall response at 7½ ips. In processing this waveform, the record volume was on full, and input was 2 millivolts. This response represents the result obtained from the entire system; recording on tape to playing back.


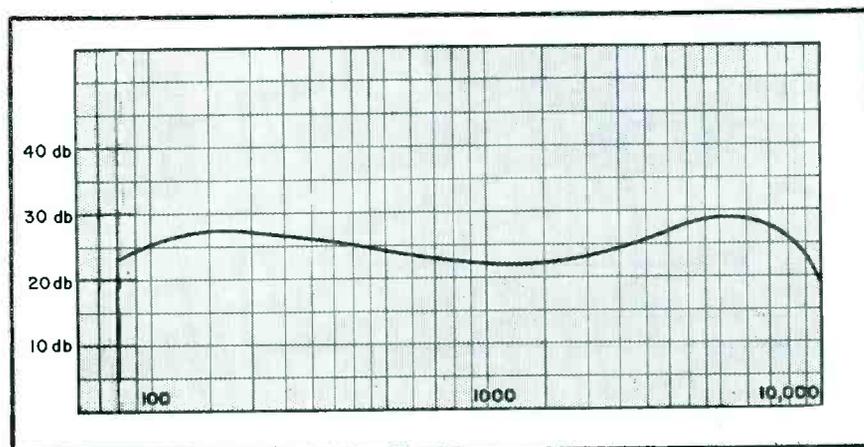
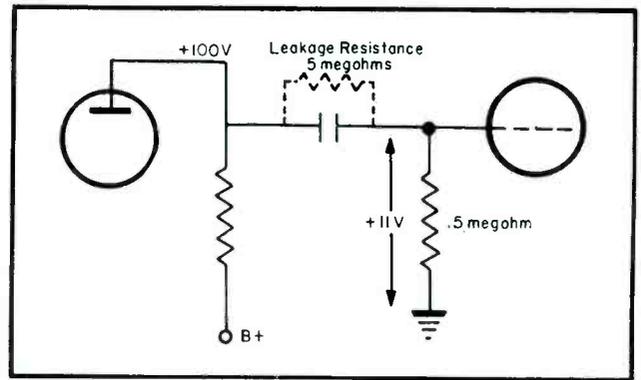


Fig. 2. Method of checking dc balance of push-pull output stage. The dc voltage across the whole of the transformer primary should be zero, or as close to zero as possible; preferably less than 1 volt.

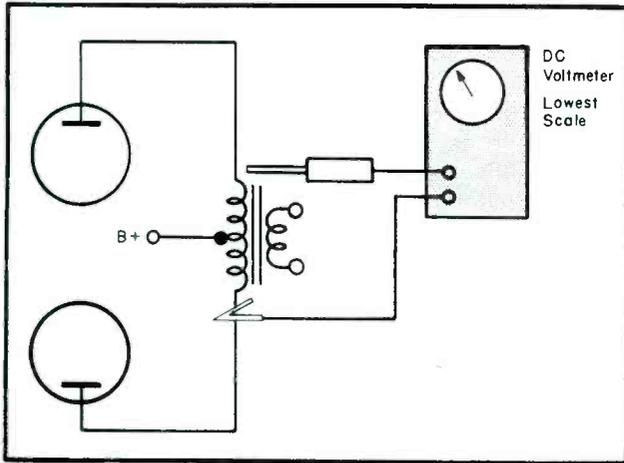

(Above)

Fig. 1. Application of positive voltage to grid through dc leakage resistance of coupling capacitor, upsetting proper bias. A good paper capacitor will have a leakage resistance of hundreds of megohms.

The Maintenance of

THE PROPER MAINTENANCE of *hi-fi* audio systems is as important as the proper design of the original installation.

The basic *approach* to the diagnosis of trouble in audio or radio and TV installations is the same, *but* there is *one change of emphasis*. Servicing of conventional radios is normally concentrated on the chassis, while in the audio field attention is directed to the whole system. For example, many small mechanical defects associated with cartridges, record player motors, or other components, which would have been obscured by poor frequency response and higher distortion levels of ordinary systems, create a dramatic contrast to normal performance in *hi-fi* systems.


In audio servicing, it is first necessary to localize the trouble, not to a

single circuit, but to a complete unit or interconnecting cable network. Cable connections are especially liable to cause trouble when the separate units are not anchored in their places, and where the owner can move components around for the purpose of dusting the shelf underneath.

The best procedure for trouble localization is the substitution of a unit known to be in good working order, for each of the components of the ailing system in turn. While this may not be practical in many cases, the principle may be applied to units feeding the amplifier. If FM reception is bad, but AM and phono are normal, the amplifier and speaker are clearly not at fault: the trouble can be narrowed down to the FM circuits prior to the *AM/FM/Phono* switch, or to the switch contacts themselves. The tuner chassis

alone, *with its associated cables*, can then be removed for servicing.

When the amplifier is not working, no opportunity is available to check between the various signal sources feeding the amplifier's input jack. The overall operation of the amplifier and speaker in a dead system can be checked very simply, however, by touching the *hot* input signal terminal with a finger or screwdriver. (The screwdriver should be in electrical contact with one's hand, and the test signal should not be grounded out by contact between the other hand and the chassis.) A healthy, raucous hum should result in the speaker. If the speaker is silent, or only emits faint sound, the amplifier-speaker system is at fault. Substitution of a test speaker, headphones, 'scope, or even a low scale *ac* voltmeter for the speaker will usu-

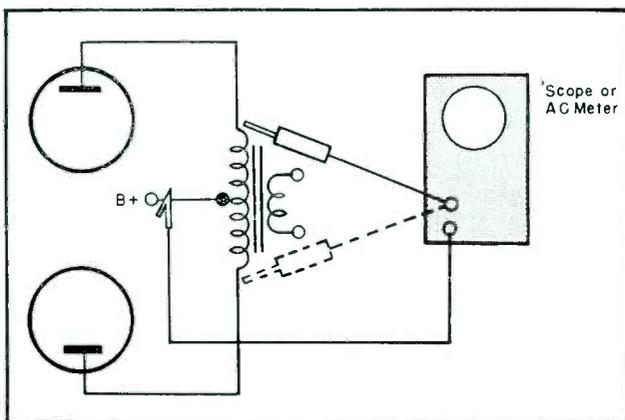

(Left)

Fig. 3. Checking signal balance of a push-pull output stage by comparing signal voltages across each half of the transformer primary.


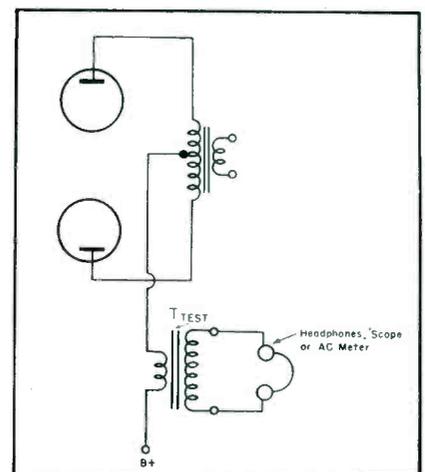


Fig. 4 (right). Circuit for checking push-pull signal balance with pair of headphones. *T_{TEST}* represents output transformer; the position of the secondary and primary windings reversed. With the amplifier putting out a signal, there should be zero or very little signal in the phones.

Servicing Audio Amplifiers—Through Tube and Push-Pull Balance Checks... Tracing and Curing Amplifier Oscillation... Diagnosing Troubles in Record Players

by MARK VINO

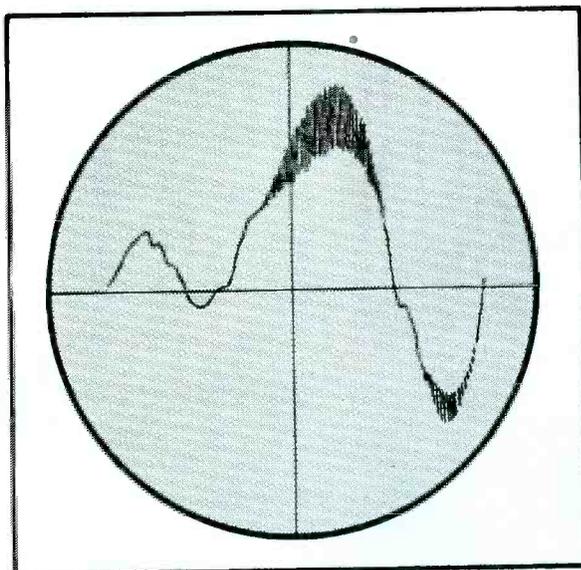

HI-FI AUDIO Systems

ally, but not always, convict the amplifier. Quality speakers are not infallible, but they are very reliable.

Servicing Audio Amplifiers

Modern vacuum-tubes have been designed to plug into tube sockets, and for a very good reason. The experienced Service Man knows that, of all the parts used in electronic devices, the tube is the most subject to failure, and is the greatest single source of trouble. Before removing a defective amplifier from the system and turning it upside down, therefore, the tubes should be checked, preferably by temporary substitution of new ones.

Certain conclusions can be drawn from a visual inspection of the tubes in operation. A bluish glow in an output tube may indicate only slight gasiness, and is not necessarily a trouble symptom, although if the glow extends to the electrodes the tube must be suspected of being defective. A violet-pink glow, however, is an indication of air leaking into the glass-envelope, and means a bad tube. If the plates of the rectifier tube begin to turn cherry red, overload of the *B+* supply is clearly indicated. The amplifier should be turned off immediately and

(Above, right)

Fig. 5. 'Scope trace of supersonic oscillation that breaks out on signal peaks only. This type of oscillation may sound very much like speaker rattle.

Fig. 6. Connection of stopping resistors in a push-pull parallel output stage, to prevent parasitic oscillations.

not operated again until the short (whether in a filter, tube, or other component) is cleared up.


Similarly, if a rectifier tube checks bad, the resistance from *B+* to ground should be measured prior to putting in a new rectifier. In many radios this resistance consists exclusively of filter capacitor leakage, and can be of the order of several megohms after the first initial acceptance of current from the ohmmeter. Most audio amplifiers, on the other hand, employ a *bleeder* resistor between *B+* and ground, whose resistance may be 15,000 ohms or lower.

Even if the ohmmeter shows no short from *B+* to ground, the new rectifier tube should be watched carefully during its first minutes of operation. The old rectifier may have been

blown by a *hot* short; that is, a short within a tube that only exists when the electrodes bend with the heat. If there is any suggestion of cherry glow from the rectifier plates, or of fireworks from other tubes, the amplifier must be turned off again immediately. Operating an amplifier with a *B+* short for any length of time will result in destruction of the power transformer if the rectifier does not go first.

Other techniques for localizing trouble within the amplifier are the same as those for conventional radios. Since the entire signal channel is audio, the use of an abbreviated signal injection technique, using a screwdriver as referred to, rather than a signal generator, is especially applicable. The grids of the tubes are stimulated in turn,

(Continued on page 81)

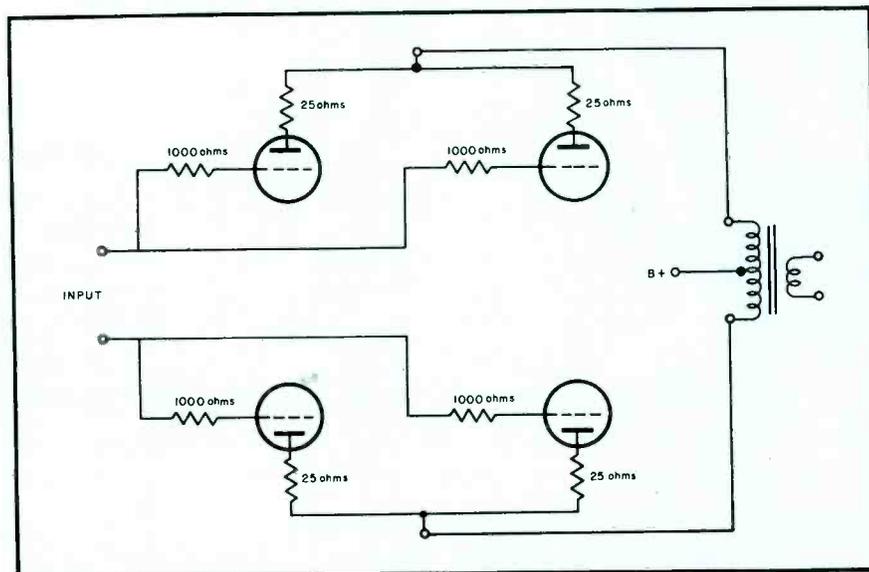



CHANNEL MASTER

introduces a

**basically new type
of VHF antenna**

the **CHAMPION***

**the highest gain
all-channel VHF antenna
ever developed!**

Featuring the unique new "Tri-Pole"

TRIPLE-POWERED DIPOLE

The "Tri-Pole" is a new antenna system in which the Low Band folded dipole also functions as three folded dipoles tied together in phase on the High Band. This is the heart of the Champion, the secret of its phenomenal performance on all 12 VHF channels.

The **CHAMPION** is another great development of the world famous Channel Master laboratories.

*Pat. Pending

the **CHAMPION** is the most sensitive all-channel VHF antenna ever designed!

Stacked **CHAMPION** provides:
11-13 D B High Band gain
6½-7½ D B Low Band gain

Here is a totally NEW kind of antenna, completely different — in principal and performance — from any VHF antenna you've ever seen! Since the lifting of the TV freeze means a gradual disappearance of the single-channel VHF area, the VHF antenna of the future will be a *multi-channel* antenna. Prepare now for outstanding reception on *all* VHF channels — present and future — with Channel Master's super-sensitive **CHAMPION**! Outperforms every all-channel VHF antenna made today — and many Yagis, too!

COMPARE these features with the antenna you are now using:

- Folded dipoles throughout — give close to 300 ohms impedance across the entire band.
- Screen-type reflector provides high uniform gain on every channel, 2 through 13. Not frequency sensitive — this reflector provides more than twice as much extra gain as straight bar reflectors.
- Phase-correcting harness is built-in and fully assembled; the only wiring you do is to attach the lead-in.
- All-aluminum construction . . . lightweight, durable, non-corrosive.

MARVEL OF PRE-ASSEMBLY


assembles faster than a
5-element yagi!

Collapsed "Pop-Up" screen opens instantly — no loose rods, elements or hardware. "Tri-Pole" assembly features automatic Spring Lock Action — all dipoles snap permanently into place without wing nuts or any other hardware.


It's a **CHAMPION** in any area!

- 1-bay—local areas
- 2-bay—secondary and fringe areas
- 4-bay—super-fringe areas

THIS ANTENNA...

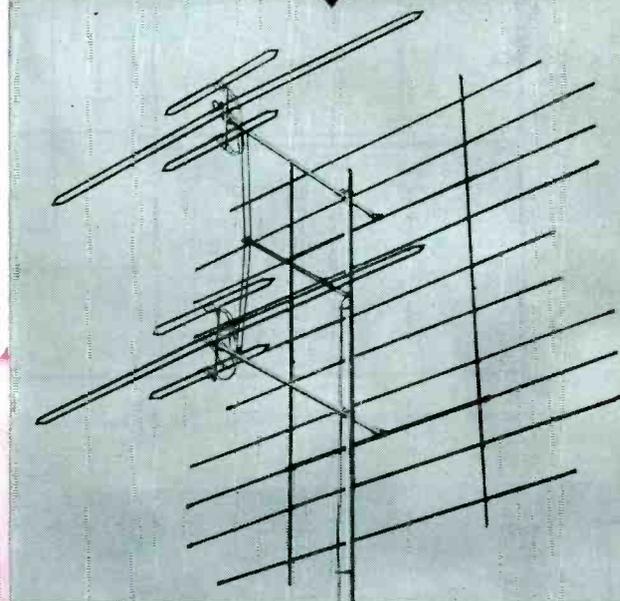


OUT-PERFORMS:

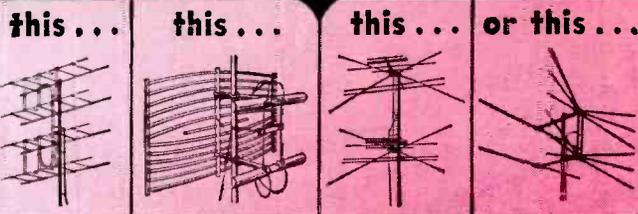

The 2-Bay **CHAMPION** actually gives you the performance of:

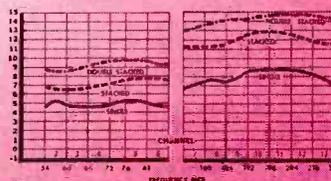- Separate 5-element Yagis for every Low Band channel!
- Separate 10-element Yagis for every High Band channel!



channel
10

Model No.		List Price
325	Single Bay	\$20.00
325-2	2-Bay	\$42.38
325-4	4-Bay	\$88.09
Separate Stacking Harness		
325-3	2-Bay Harness	\$ 2.08
325-5	4-Bay Harness	\$ 4.15


Send for complete technical literature.

CHANNEL MASTER CORP.

ELLENVILLE, N. Y.



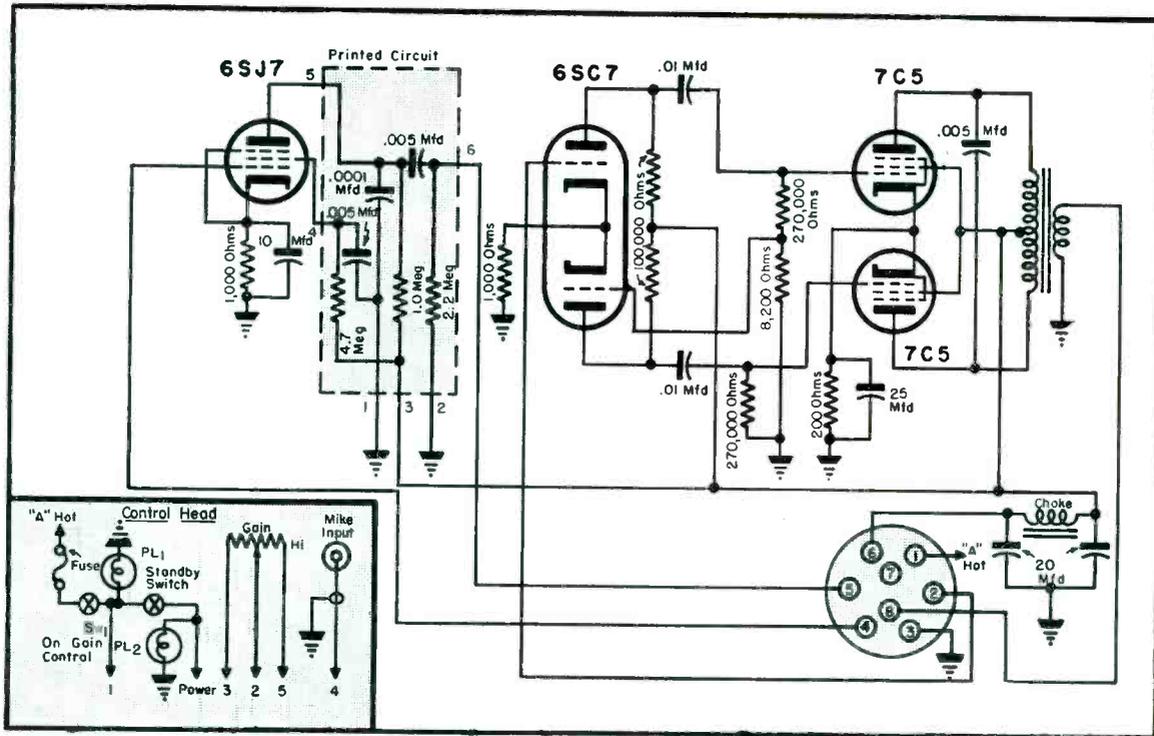
Compact Amplifier, Draws Less Than 9 Amperes or




Schematic of printed circuit amplifier. The B supply can be switched on and off into standby by a toggle switch in the control head.



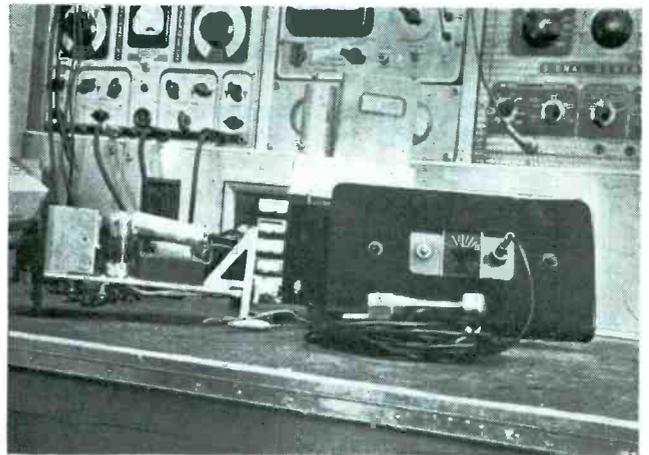View of amplifier unit and power supply installed in car. Power pack is just to right of knob, while amplifier chassis is just above steering column. This view was taken through hole where control panel was eventually installed.



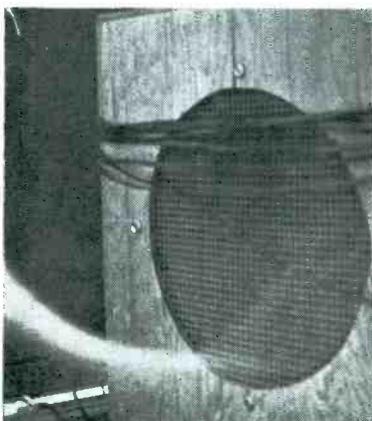Side view of amplifier chassis at left. Control panel is at right and power pack at center atop cabinet. Microphone is on bench before control panel.



(Right)

Bottom view of amplifier chassis. Printed circuit is at upper end of chassis (light-color patch). Input plug is on bench below chassis. Back view of control panel also appears in this photo.

(Left)

Baffle with one of the 12-inch pm speakers mounted in car.



About As Much As Average Auto Radio

Miniaturized Mobile PA System Using Printed-Circuit Units

by JACK DARR

AT OUTDOOR REAL-ESTATE auctions and other events where *ac* is not always available or convenient, compact, low-drain mobile *pa* systems are mighty handy. Drawing less than 9 amperes, or about the same as a modern auto radio, such units can be used for periods ranging up to three or four hours, without undue drain.

Fig. 1 illustrates an amplifier of this type, *miniaturized* as much as possible. A printed circuit is used in the pre-amp stage and all other parts and wiring arranged to save as much space as possible.

High voltage is furnished by a separate-unit power pack,¹ with a reversible synchronous vibrator, enabling it to be used with any battery polarity. The *A* input and *B* output voltages are brought out to a two-terminal strip on one end of the chassis, while the chassis of the car itself furnishes the common return path.

The gain control, a .5-megohm unit, with audio taper and master on-off switch, high-voltage *standby* switch, microphone connector and the two pilot lights are mounted on the left-hand panel of the car's dash, in the area designed for the custom radio receiver. The dummy cover-plate and the two snap-buttons can be removed and saved. Another plate can be used to mount the controls; the two pilot lights will fit exactly into the two holes left by the snap-buttons.

The amplifier provides an overall power output of around ten watts. It uses two 7C5s, operating in class *AB-1*. These power amplifiers are

driven by a twin-triode phase-inverter driver, using a 6SC7. A 6SJ7 serves as the microphone preamp; this is coupled into the input of the driver by a printed circuit.² As couplers, 01-mfd ceramics are used; all resistors except those used for 7C5 bias resistor are $\frac{1}{2}$ watt size.

Originally, the circuit had the gain control in the very first stage, across the microphone itself. This was found to produce a bad hum, together with a tendency toward oscillation; thus the control was moved back to a better location, between the output of the first 6SJ7 stage and the input of the 6SC7 driver. This called for more shielded wiring, but gave considerably better results. All power, speaker output and audio input wiring goes to an 8-prong plug and socket assembly mounted on the back of the chassis.

Only one wire is used to feed the speakers, the other side being grounded. This type of arrangement provides plenty of good grounds; an extra grounding wire should be run from the control head to the chassis. If the grounded shield of the wiring carrying the gain control circuits is allowed to pick up any of the return currents flowing to the vibrator pack, a bad hum and possibly oscillation will result. If any hash is present after installation, the addition of extra heavy binding will probably eliminate it.

In a typical installation, the three units were installed in a car in the space provided for the car-radio. The dash panel was removed and amplifier

chassis mounted on top of the wide brace running from firewall to dashboard. Two short *J* bolts were used, hooked into holes in the side of the chassis, and run through holes drilled in brackets mounted on the sides of the brace. The power supply chassis was mounted on the firewall itself; four spade bolts were placed on its underside. These were fastened to two heavy metal straps, with holes drilled in appropriate places, and the straps then bolted to the firewall.

A standard auto-radio fuse holder was used, and the hot end connected to the accessory bolt of the ignition switch. This was done to prevent operation of the amplifier by unauthorized persons and prevent accidental discharge of the battery; the amplifier cannot be turned on without the ignition key.

The volume control and microphone input cable are shown running in individual shielded leads, with the shields soldered together at intervals. Due to peculiarities of this circuit, it was found that better results will obtain if a three-conductor, overall-shielded cable is used for the gain control, and an individual shielded lead for the microphone input. These leads must not be allowed to ground anywhere outside of the amplifier: if they do, they will become a part of the return path for the supply current, and induce a loud buzz into the sensitive input. It may be necessary to insulate the *control-panel* from the chassis of the car to stop the hum and tendency toward oscillation in the front end.

The speaker wiring was carried up and over the doors on the left side of the car, being tucked inside the trim, out of sight. At the back, a hole was cut in a masonite lining, and a 6-prong socket mounted. The hot wire was connected to terminal 2 of this socket, and 5 grounded, by a wire under a nearby screw.

The system uses two light-duty 12" *pm* dynamic speakers, enclosed in homemade plywood baffles. Extension cables and plugs were provided for them, so that they could be used either atop the car, as was originally planned, or carried some distance away. An extension cable was also provided for the microphone³. All microphone cables were provided with plugs⁴ which have *floating* locking-rings: these may be screwed off the plug, permitting use as either a male or female type plug. Thus, all extensions can be readily joined into one long cord, for long runs. A total of 100' of microphone cable was used.

¹Mallory VP-552 Vibrapack.

²Centralab PS-91.

³Turner candlestick type used. ⁴Amphenol.

Video Amplifier Performance Factors

Chart Analysis of Buzz . . . Saturation . . . Hum Bars



by **CLARK R. ALISEN**

Grain . . Smear . . Trailing Reversal

Condition	Reason	Control Method
Buzz in the sound at high contrast levels; when not due to <i>if</i> amplifier trouble. (11)	Intermodulation of picture and sound signals due to non-linear tube operation.	The signal-handling capability of the video amplifier should be increased by using selected tube. Electrode voltages and value of plate-load resistors should be checked: See circuit at right; circle (1).
Horizontal wedges darker than vertical wedges; not due to <i>rf</i> or <i>if</i> misalignment. (12)	Rising response at low video frequencies.	Values of plate-load resistor and peaking coils should be checked; the latter for opens or shorts: See circuit and characteristic waveforms at right; circle (2).
Vertical wedges darker than horizontal wedges; not due to <i>rf</i> or <i>if</i> misalignment. (13)	Rising response at high video frequencies.	Values of plate-load resistors and damping resistors across peaking coils should be checked: See circuit and characteristic waveforms at right; circle (3).
Artificial ghosts, or ringing in picture; not due to <i>if</i> misalignment. (14)	Excessive peaking of video amplifier.	Values of damping resistors across peaking coils should be checked: See circuit and characteristic waveforms at right; circle (4).
Fine detail of picture weak; peaking coils and load resistors okeh. (15)	Excessive capacitance at output of video amplifier.	Drum of lead to grid of picture tube should be checked; must be dressed clean and as far along chassis for any appreciable distance: See circuit and characteristic waveforms at right; circle (5).
Trailing reversal in picture; not due to <i>if</i> misalignment. (16)	Excessive high-video peaking.	Damping resistor across peaking coil and bypass capacitor across video amplifier center tap should be checked: See circuit and characteristic waveforms at right; circle (6).
Black and white saturation of picture; not due to overdrive, or to <i>if</i> amplifier trouble. (17)	Incorrect bias on video amplifier; subnormal plate and screen voltages.	The <i>dc</i> operating voltages should be checked and corrected as indicated: See circuit at right; circle (7).
Hum bars in picture; not due to <i>if</i> trouble. (18)	60-cycle modulation of video signal, or 120-cycle modulation.	Heater to cathode leakage in picture amplifier should be checked; check also for <i>ac</i> or <i>dc</i> supply voltages: See circuit at right; circle (8).
Dark screen; not due to <i>rf</i> or <i>if</i> trouble, or to picture-tube difficulty. (19)	Break in video signal path.	Progress of signal should be checked with scope, and the faulty component repaired: See circuit at right; circle (9).
Picture weak and washed out; signal out of picture detector okeh. (10)	Leaky grid-coupling capacitor (grid of amplifier, or grid of picture tube).	Grid bias should be checked with <i>vtrm</i> ; faulty capacitor should be replaced: See circuit at right; circle (10).
Grain (4.5-mc beat) visible in picture. (11)	Grain trap(s) tuned to incorrect frequency.	Trap(s) should be tuned for minimum grain in picture; may be in <i>if</i> (4½-mc trap may be wired in series with picture-tube grid): See circuit at right; circle (11).
Smear in picture. (12)	Time delay not constant for all video frequencies.	Values of coupling, bypass, decoupling, and low-frequency compensating capacitors should be checked: See circuit at right; circle (12).

(Right): Schematic of video detector, video amp and *dc* restorer of a typical TV chassis. Waveforms at (a)=video-response curve, plate-load resistance increased; (b)=video-response curve, plate-load resistance decreased; (c)=video-response curve, detector series-peaking coil shorted; (e)=video-response curve; output series-peaking coil shorted; (i)=video-response curve, damping resistor of detector series *pc* open; (g)=video-response curve, excessive capacitance of output lead to chassis. (Numbers in circle serve to identify portion of circuit similarly numbered and discussed in table.) Note: Curve A does not exhibit truly a loss of low frequencies, because practical commercial situations are involved in this report. In these instances, the normal condition utilizes a rise at high frequencies to compensate for loss of the highs in the *if* amplifier. Such a normal video curve appears in A¹.

Figs. 1 (left) and 2 (right). Intermittent test setups. In arrangement shown in Fig. 1 at (a), f_c from the rf or if signal generator is adjusted to be acceptable to amplifier under test, and the output amplitude is set for best sensitivity. The low-pass filter (shown at b) is adjusted to reject f_c . In the Fig. 2 setup, f_1 out of the audio signal generator is adjusted to 10-kc (approximately) and amplitude set for best sensitivity. Here the low-pass filter (b) is adjusted so that it will not pass f_1 .

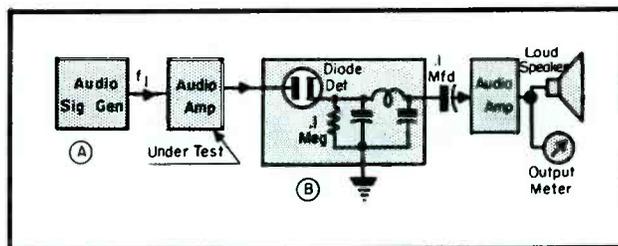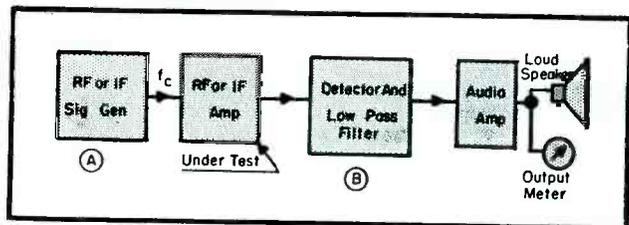

INTERMITTENT FAULT LOCATION In Electronic Equipment

by SIDNEY WALD

THE DETECTION OF intermittent faults in electronic equipment is an art in which the chief tools have been experience, ingenuity, intuition and patience. Technical skill and scientific ability have played comparatively minor roles because of the very nature of the problem; which by definition, exists only at random moments.

The general methods of attack have been to attempt to extend the duration of the fault; to attempt to apply orthodox maintenance routines such as signal tracing, voltage measurements and continuity tests. Not knowing the cause of the intermittent fault, however, it is difficult to prescribe a universal treatment designed to make it more amenable to leisurely analysis.

One of the *treatments* which has been attempted from time to time consists of applying excessive potentials to filaments and plate circuits in the hope that whatever has been breaking down or *opening* intermittently will be adversely influenced by such cruel treatment and revert to a permanent cessation of operation.

Too often this practice has no effect on the elusive original fault and succeeds only in creating a new one which obviously multiplies the difficulty.

Another popular treatment consists of standing by patiently until the fault should decide to show itself and then to creep up on it stealthily with either ohmmeter, spare capacitor or mallet, whichever way intuition seems to lead.

Finally, the method used most fre-

Carrier Amplification Technique Adopted to Simplify Troubleshooting and Predict Problem-Areas Before They Seriously Affect Equipment Usefulness

quently also happens to be the most violent. The individual to whose sad lot the task has fallen grasps the equipment firmly, elevates it from the work bench and then sets it down with a mighty crash; the drop height varying approximately with the exasperation.

In direct contrast to the foregoing *brute-force* methods of locating *intermittents*, there is a rational approach to the problem.

The method is particularly adapted to receiving and amplifying systems normally handling modulated carriers or continuous signals.

Briefly, the technique consists of the following steps:

(1)—A strong, unmodulated signal of a frequency acceptable to the input of the system is applied.

(2)—The output of the equipment being tested is brought to an audio frequency detector or demodulator.

(3)—The detector output is increased further by means of an audio amplifier and the resulting output monitored by either a loudspeaker or an output meter.

Block diagrams of the setup are shown in Figs. 1 and 2. The system, now in a condition highly sensitive to

random gain changes, is explored, component by component, for microphonism. That is, each component and junction is lightly tapped with an insulated rod. The defective component or joint will reveal itself as a high amplitude noise in the monitoring device.

The foregoing method, which has proved highly successful in practice, is based on the premise that most types of intermittent conditions, when they exist at all, are present almost continuously.

Due to their minute magnitude, however, during much of the time, they are difficult to detect and localize.

If we consider this condition as a continuously occurring random gain fluctuation, it is reasonable to assume that such variations may amplitude modulate on impressed carrier frequency, be amplified and reclaimed after detection as a noise output.

Typical intermittent faults which can be detected and located effectively by this method are:

(1)—Microphonic tubes:

A tendency toward microphonism, which may become progressively worse

(Continued on page 59)


now . . . new beauty

for the

housetops

DAVE CHAPMAN, S. I. D.

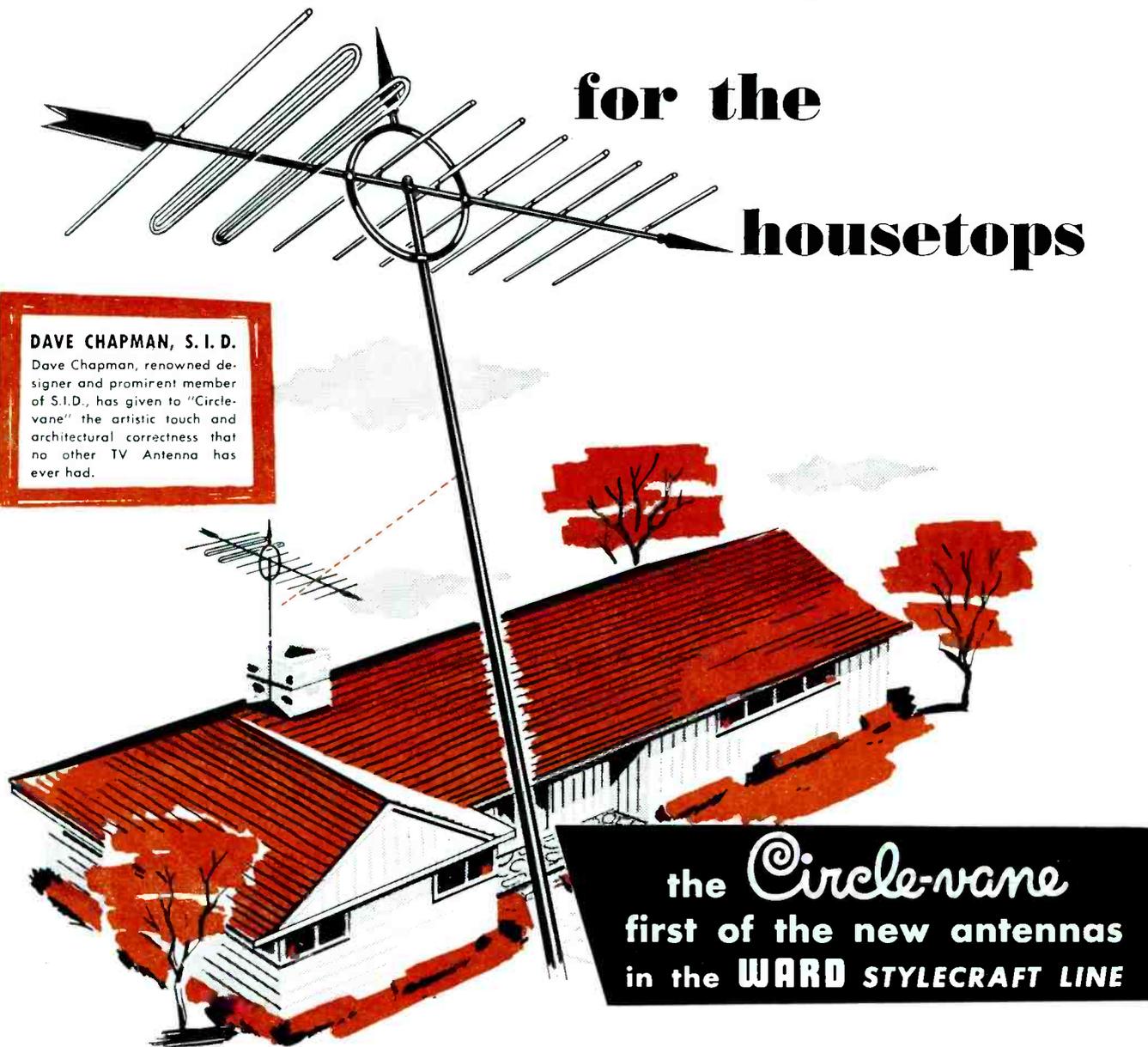Dave Chapman, renowned designer and prominent member of S.I.D., has given to "Circle-vane" the artistic touch and architectural correctness that no other TV Antenna has ever had.



the *Circle-vane*
first of the new antennas
in the **WARD STYLECRAFT LINE**

Antennas, styled to the modern tempo . . . cleverly patterned to enrich the appearance of any house . . . expertly engineered to give finer pictures . . . skillfully designed by the famous Dave Chapman, (S.I.D.) . . . these new Ward Circle-vane Antennas complement the home and add dignified charm and beauty. Everybody, dealers and owners alike, have been waiting for "something new" in antennas—
The new, finer Ward Circle-vane supplies the answer.
The Ward Circle-vane is constructed of aluminum elements with a cross-arm of durable Permatube . . . Comes completely pre-assembled.

Be first with this Ward FIRST in your territory. Order today.

THE WARD PRODUCTS CORP.
DIVISION OF THE GABRIEL COMPANY



1148 Euclid Avenue, Cleveland 15, Ohio • In Canada: Atlas Radio-Co., Ltd., Toronto, Ont.

SERVICE... The National Scene

INGENIOUS WIRELESS MIKE SYSTEM UNVEILED AT ELECTRONIC CONFERENCE--An FM cableless-microphone system, designed for pa use to cover areas up to 5000 square feet, and utilizing induction coupling between transmitter and receiver, eliminating the need for a license, was described during the recent National Electronic Conference in Chicago.¹ Featuring a subminiature transmitter, completely contained in a stick-type microphone housing, the setup consists of a 5-tube, printed-circuit FM transmitter, self-contained ferrite antenna inductor, a microphone (with omnidirectional ceramic cartridge), and batteries, all weighing less than one pound. . . . To limit radiation, accommodate bandwidth required in an FM system, and avoid the use of broadcast, amateur, police and Loran bands which lie between .5 and 2 mc, a compromise carrier frequency of approximately 2.1 mc was chosen.

THE TRANSMITTER CIRCUIT, it was said, is divided into two sections; a two-tube audio stage, and a three-tube rf unit. A pair of tetrode voltage amplifiers are cascaded in the audio unit to provide a gain of 55 db at 1000 cps. A miniature volume control between these two stages permits adjustment of gain for the desired degree of modulation. . . . To obtain the best possible signal-to-noise ratio, 80 microsecond preemphasis has been included in the transmitter, and corresponding deemphasis in the receiver. . . . The rf section of the transmitter consists of a self-controlled oscillator, reactance modulator and rf amplifier. . . . The complete circuitry for the transmitter, excluding antenna and tubes, occupies a volume of only about 1 cubic inch. The chassis casting, which contains 8 capacitors, 11 resistors, 1 volume control, 5 subminiature tube sockets and a powered iron-core oscillator coil, is nothing more than a cylinder 1" in diameter and 1.3" long.

FOR POWER, the transmitter uses a 30-volt hearing-aid battery, and a 1.3-volt mercury cell. . . . The antenna, a ferrite core, is 3" long and weighs but 2 ounces.

THE RECEIVER employs a pentode mixer, separate triode oscillator, afc (via pentode reactance modulator), wide-bend if with two pentode amp stages, two cascaded triode limiters and discriminator. Output is fed through gated cathode-follower triode to af output of set. Triode dc amp is provided in a carrier-operated squelch circuit. The rf has a bandwidth of 150 kc.

IN ANOTHER REVEALING NEC PAPER, the significant value of ferrites was analyzed.² It was noted that the high permeability, low losses and high resistivity of ferrites, have made it possible to design many improved components for TV, highly efficient antenna cores of the types used in the wireless system described above, and miniature transformers. . . . In a comparison of metals and ferrites, it was disclosed that metals even when laminated have excessive eddy losses when used as a magnetic core for TV components handling the horizontal scanning frequency of 15.75 kc and related harmonics. Ferrites, on the other hand, are ideal for such an application, for at these frequencies all the losses, except hysteresis, are extremely small. . . . In a forecast of the future of ferrites, it was noted that this unusual material will find wide use in color-TV chassis because of its remarkably low-loss factors.

250 TV STATIONS NOW OPERATING IN 166 MARKETS--Of the 525 stations that have been authorized since the freeze lift, 250 are now actually on the air in 166 market areas. So declared the headman of the FCC at a meeting in Chicago. About 112 of these areas have but one station. And, in 48 of these one-station markets, additional stations have been approved for operation. . . . The FCC spokesman declared that by December at least 50 more stations will begin telecasting, and by the end of next year at least another 100 or more will be approved for TV broadcasting.

¹Paper delivered by Thomas W. Phinney, Shure Bros., Inc. ²Report offered by Robert L. Harvey, RCA.

SERVICE... The National Scene

ANTENNA REPAIR CODES RECEIVE NOD IN SOUTH AND WEST--Ordinances to control antenna installation and general TV repair, have been favorably received by legislatures and Service Men in Idaho and North Carolina. . . . In Idaho Falls members of the City Council cast a unanimous vote for a tentative code which would not only license all TV Service Men, but require those who install only to post a \$10,000 bond. Special permits will be required for the installation of towers that are 15' or higher. . . . In Durham, N. C., a stringent measure, approved by dealers and Service Men, is now before the City Council. This ordinance would require the posting of a \$500 bond by those who install, alter or repair antennas, and a general \$2 fee for permission to operate as an installer. . . . Detailed specifications of the materials to be used in installation, and mounting positions, are emphasized in this new proposal. All antenna structures, it is noted, will have to be of corrosive-resistant materials, and capable of withstanding wind and ice loadings. It will be out of order to mount antennas more than 40' above the roof, and no part of any antenna system including the guy wires will be allowed to extend above or below any electric line carrying more than 250 volts. All external leadin conductors will have to either be of copper, copper-clad steel or bronze, and in sizes approved in the rules of the National Electrical Code. The ruling also prescribes the supports that shall be used for leadins. Specifically, it was noted, leadins will have to be rigidly supported on approved insulators which provide a clearance of 4" from the roof, wall, gutter, and electric and telephone wires; between any point and a lightning arrester and TV set it will not be necessary to provide any clearance. All outside antennas, the ruling continues, will have to have a ground conductor installed, and lightning arresters will be imperative in every installation. . . . The city electrician and his assistants will receive full authority to inspect these installations, and he will be empowered to issue complaints which will have to be satisfied within 48 hours before penalties are imposed.


FORT WAYNE GROUP PLEDGE TO STRINGENT AD-SELLING RULES--A tough code, specifying statements that should and should not be made by Service Men in their advertisements and during service calls, is now in force in Fort Wayne, Ind. Prepared by the Fort Wayne TV-Radio Appliance Association, the rules cover service offers, speed of service, and uhf converter and conversion service. No unqualified statement as to the speed of service to be expected shall be made, the code states. And, performance claims for various types of converters must be limited to provable facts, with supporting evidence readily available on request. No claims or statements about converters of conversion service must be used, the code continues, if such claims are conjectural or demonstrably at variance with the currently prevailing circumstances and stages of development of ultrahigh-telecasting facilities in Fort Wayne.

UHF ADVERTISING SCORED BY ST. LOUIS BBB--Charging that many manufacturers are still firing away with loose claims in their consumer ads on uhf performance, the Better Business Bureau of St. Louis warned, in a sizzling bulletin, that such misrepresentation can only lead to disaster. Conversion ads that make it look as if all that is needed by the setowner to assure himself of proper reception is a screwdriver and five minutes of his time, are dangerous, the BBB said. It is well known that in some locations even expert Service Men have to struggle for hours to locate the spot for an outside antenna that will insure best results. . . . The BBB pointed out that it would be wise for every manufacturer, dealer and distributor to avoid the use of the following statements in their consumer copy: "With ---'s powerful all-channel tuner, you can receive every uhf or vhf station within range of your home." (Can you, in every location without an outside antenna?) . . . "A ---- uhf converter can be attached easily and quickly to a vhf set. Every channel in your area, as well as those coming through in the future, will be available. No expensive installation service necessary. Just plug it in." (What happens if you plug it in and get nothing; will the consumer get a free outside antenna installation?) . . . "Top-of-set cabinet can be installed in 5 minutes with a screwdriver." (This is probably true, but what if the converter will not work without an outside antenna?) . . . Accolades to this vigorous group for their driving plan to help Mr. and Mrs. Consumer, and particularly, the Service Man.--L. W.

NEW

WALSCO *Imperial*

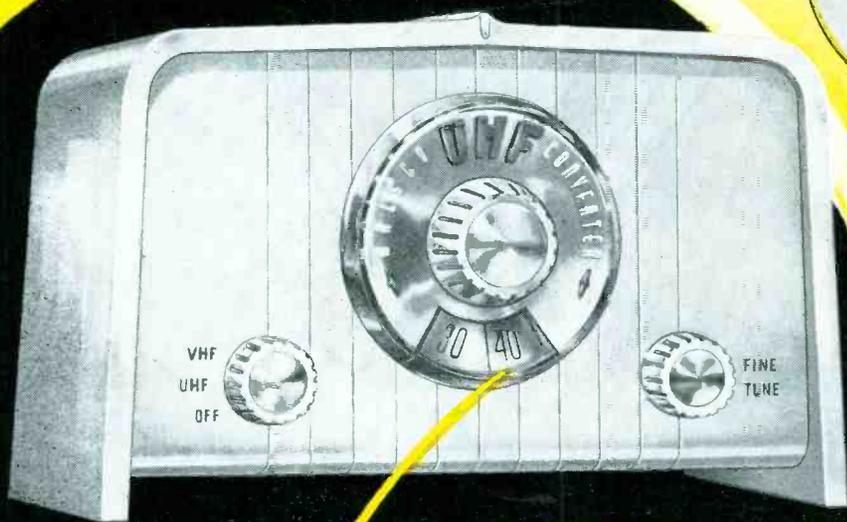*** PROVEN THE MOST ADVANCED
UHF CONVERTER IN AMERICA**



NEW distinctive cabinet design available in beautiful assortment of COLORS

WITH EXCLUSIVE
Surreture

UP TO

98%
GREATER POWER
GAIN

UP TO

88%
LESS NOISE
FACTOR

*** FACTS** from one of America's leading, independent research laboratories proved the WALSCO Imperial will out-perform all other UHF converters . . . anywhere!

	Average Power Gain DB			Average Noise Factor DB		
	500 mc	650 mc	800 mc	500 mc	650 mc	800 mc
WALSCO Imperial	10.0	9.5	9.5	15.0	15.5	16.0
Converter A	6.0	5.4	3.5	18.5	20.0	21.0
Converter B	7.0	6.5	5.0	18.0	18.5	20.0

WRITE FOR COMPLETE INFORMATION

WALSCO ELECTRONICS CORPORATION

3602 Crenshaw Blvd. • Los Angeles 16, California

easy...split second installation!



corner reflector *Golden Grid* uhf antenna

Identified by its golden screen

FACTORY-ASSEMBLED

- vibration-proof
- ready to install
- reduces installation cost
 - sturdily constructed
- only 1 mast bracket to attach
- anti-corrosion plating meets government specifications


Exclusive

UHF "WISHBONE" INSULATOR


Only Telco gives you this remarkable "plus" feature

1-2-3 Ready To Go!

- 1 OPEN CARTON . . . REMOVE FACTORY-ASSEMBLED UNIT
- 2 OPEN LIKE A BOOK . . . FASTEN STRUT WIRES
- 3 MOUNT ON MAST . . . JOB COMPLETE

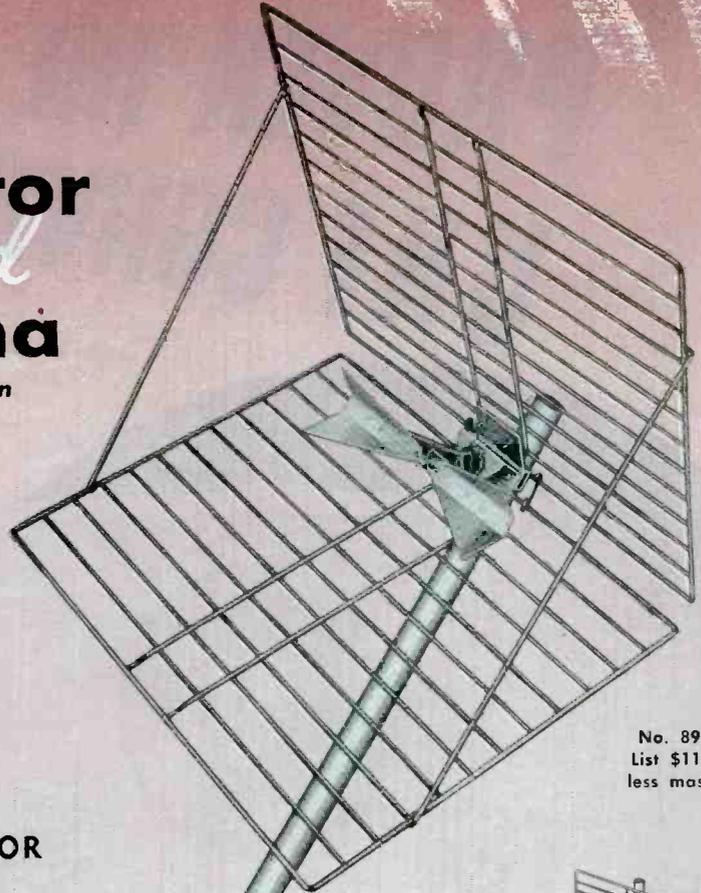

No. 8984
List \$11.75
less mast

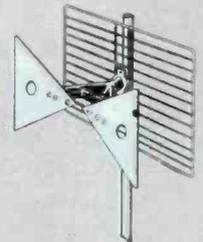

NO. 8965 Butterfly
Wishbone Antenna
List \$5.50
With Stacking Bar



No. 8642 Universal
Lightning Arrestor
U. L. Approved
List \$1.25

No. 9000 "Golden Halo"
Indoor UHF Antenna
Pure Gold Plated
List \$4.95



WRITE FOR FREE TELCO CATALOG



television hardware mfg. co.

DIVISION OF GENERAL CEMENT MFG. CO.
904 TAYLOR STREET., ROCKFORD, ILL.

by T. L. GILFORD

Servicing Helps

IN VISUAL ALIGNMENT, one often encounters kinks and hangovers, caused, in some cases, by harmonics in a sine-wave 'scope sweep.

It is not always easy to interpret what is seen on the 'scope screen in terms of what is wrong, and what should be done about it. For example, Fig. 1 shows an *if* response curve displayed on a sawtooth sweep (a), and on a 60-cycle sine-wave sweep (b). The trouble present in the sine-wave sweep is due to harmonics in the supply voltage.‡

The supply voltage always contains harmonics, but the harmonic content is usually so small that no trouble is encountered. Trouble arises when the ground connection between the sweep and 'scope is defective, for example, so that the ground circuit has to be completed through the line-filter capacitors of sweep and 'scope; since the reactance of these capacitors is smaller at higher frequencies, the harmonic content of the sweep voltage is thereby increased, because the harmonics have higher frequencies than the 60-cycle fundamental.

Phase-shifter networks (Fig. 2) can be utilized to phase the trace and retrace together when 60-cycle sine-

wave sweep is used; when the value of the phase-shifting capacitor is chosen too small, the harmonic content of the sweep voltage becomes increased.

Crystal Demodulator Probe Application*


THE CRYSTAL DEMODULATOR probe has a number of very practical applications in general circuit testing. It can be used in signal tracing in *rf*, *if* and video amplifiers; buzz analysis in 4.5-mc amplifiers, or in the sound *if* amplifier strips (split-sound TV); ratio-detector marking; marker-generator calibration; stage-by-stage alignment, and any test which requires demodulation of the signal as long as the peak test voltage does not exceed approximately 65 v.

Signal tracing is a straightforward procedure, and can be done in the same general manner as conventional signal tracing of a broadcast receiver. The demodulator probe picks up the signal at any point in the tuned circuits or in the video amplifier, and will display


‡See *In the Field* notes, this issue p. 66.

*From notes prepared by the engineering department of Precision Apparatus Co., Inc.

Fig. 3. Development of undershoot distortion in an *if* curve, caused by grid-current flow in the first video amplifier. (Courtesy Precision Apparatus)

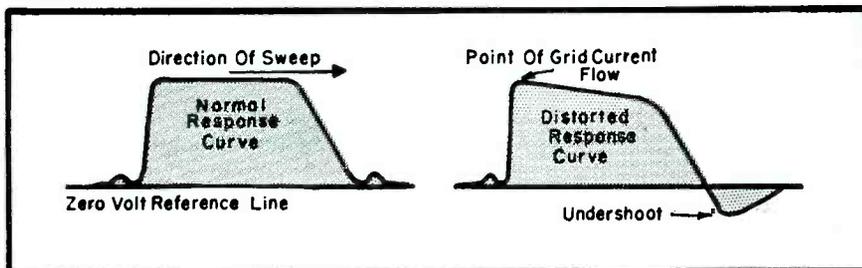

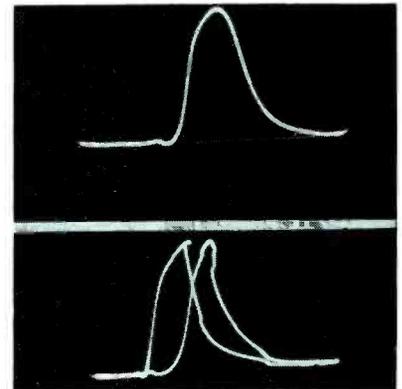Supply Voltage Harmonic Problems in 'Scope Work . . . Crystal Demodulator Probe Applications . . . Buzz Analysis . . . Marker-Generator Calibration



(Above)

Fig. 1. How harmonics in the sweep voltage distort the response-curve display: (a) = response curve as seen on 60-cycle sawtooth sweep; (b) = same response curve as seen on 60-cycle line sweep when excessive harmonic content is present.

(Below)

Fig. 2. Typical phase-shifter networks which can be used in visual-alignment procedures. A defect in the circuit, which effectively places a small capacitance in series with the source, accentuates the harmonics in the line. The harmonic content of power lines in various areas also is subject to considerable variation.

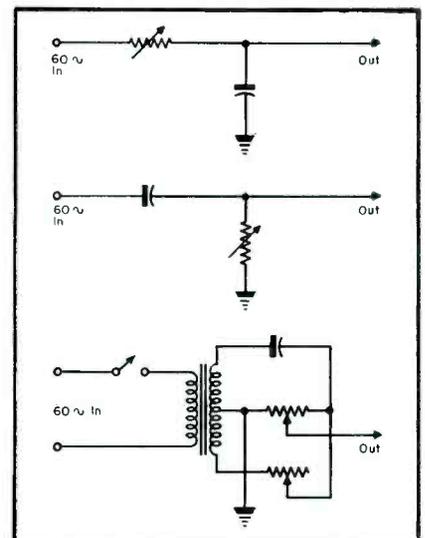


Fig. 4 (right). The operation of a demodulator probe in an amplifier. (Courtesy Precision Apparatus)

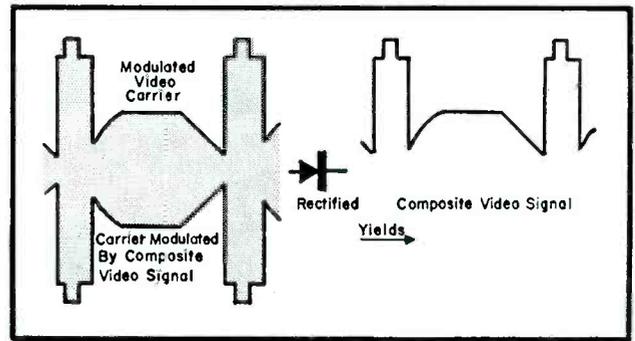
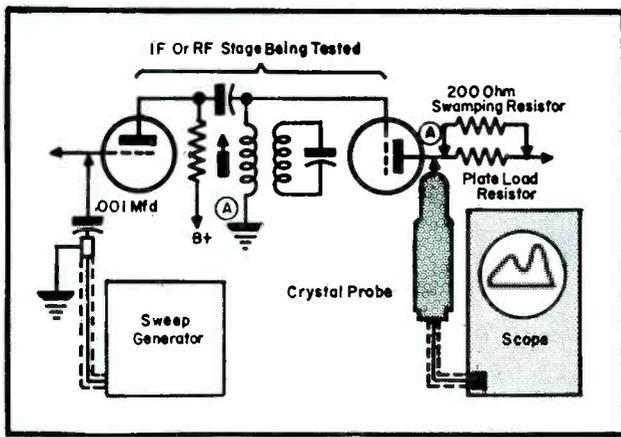


Fig. 5 (left). Test setup for checking single-stage response using a crystal probe.² (Courtesy Precision Apparatus)

²Precision Apparatus model SP-5B.

the waveform upon the 'scope screen. It should be noted that if signal tracing is necessary in TV *rf* circuits, it will usually be necessary to use a swept signal, rather than a TV station signal, because the signal voltage may otherwise be too low for satisfactory deflection on the 'scope screen.

By the use of the signal-tracing technique, it is possible to pinpoint a dead or weak *hf* stage, a regenerative or an oscillating stage. A dead stage develops no deflection on the 'scope screen. A weak stage will exhibit less deflection than the previous stage, i.e., a loss instead of a gain. A regenerative stage will show up in either of two ways, depending upon whether the Service Man is using a sweep signal or a TV station signal in the circuits; a sweep signal which passes through a regenerative stage will show an extremely large response at one end or in the middle, but very low response over the rest of the curve. If the regeneration is excessive, spurious markers may also appear. An oscillating stage shows up as a curve which has *gone to pieces* and also often exhibits undershoot due to the grid overdrive and flow of grid current. Strong oscillation may paralyze the stage, which may then be confused with a dead stage; however, the supplementary use of a *vtrm* and a *hf* probe will distinguish between the two cases, since the oscillating stage will cause a strong deflection on the *vtrm*, whereas a *dead stage* causes no deflection of the pointer.

If a station signal is used for the tracing procedure, regeneration may show up as severe distortion of the composite video signal, either with the equalizing pulses much lower than the level of the vertical sync pulse, or with severe overshoot and ringing along the top of the vertical sync pulse.

Buzz Analysis

BUZZ ANALYSIS is also a straightforward testing procedure. When the

4.5-mc sound signal is displayed on the 'scope screen, excessive buzz voltage in this circuit will become apparent as a 60-cycle pulse which usually has a vague resemblance to the vertical sync pulse from which it is derived; in the case of tunable buzz. In the case of untunable buzz, the pulse more often appears as a sharply-pointed 60-cycle spike voltage.

Ratio-Detector Marking

RATIO-DETECTOR MARKING is sometimes a problem, in view of the fact that the inherent AM rejection of a ratio detector circuit is often sufficient to suppress completely a beat marker. In such cases, one should temporarily substitute a crystal probe for the circuit under test, i.e., the output of the sweep generator should be connected directly to the input of the crystal probe. The probe has no AM rejection, and the 4.5-mc marker will now be clearly visible along the horizontal baseline. The exact position along the horizontal baseline at which the marker appears should be noted. The circuit under test can then be reconnected in place of the crystal probe, and although the marker is now invisible, its position is now known, and will remain known as long as the tuning dial of the sweep generator, and the 'scope sweep controls remain untouched.

Marker-Generator Calibration

MARKER GENERATOR calibration can be facilitated by the use of a crystal probe. To calibrate a marker generator, one should parallel the output from the marker generator and a 2-mc crystal oscillator. The mixed outputs should then be applied to the crystal probe. Although the frequencies from the generator and oscillator are too high to affect the 'scope directly, the crystal probe develops a beat envelope which will be visible on the 'scope

screen. As the marker-generator dial is tuned from 20-25 mc, for example, it will be noted that sine-wave beat patterns appear in the vicinity of 20.22 and 24 mc. That is, the beat pattern appears at integral multiples of 2 mc. The 'scope is swept at any convenient *lf* rate, such as 60 cycles.

Stage-By-Stage Alignment

STAGE-BY-STAGE alignment is recommended when manufacturers provide stage-by-stage response curves, or if severe difficulty is being experienced in obtaining the proper curve. The sweep signal and marker should be applied at the grid of the tube in the stage under test. The crystal probe should then be applied at the plate of the tube following the stage under test, and a 200-ohm carbon resistor shunted across the plate-load resistor of the tube following the stage under test.

The Swamping Resistor

The swamping resistor shown in Fig. 5 flattens out the resonant response of the following stage, thereby permitting a view of the true single-stage response. The low impedance of the generator cable likewise flattens out the resonant response of the preceding stage, so that the true single-stage response is unaffected by the preceding stage.

Although the probe could be applied at the grid of the tube following the stage under test, this procedure is less desirable because the small input capacitance of the probe tends to detune slightly the stage under test under such circumstances, and does not provide an entirely true replica of the stage response.

General demodulation tests can also be made with the crystal probe, such as testing for parasitic voltages in audio amplifiers, checking for standing waves on transmission lines, etc.

FREE! A FAMOUS CBS-HYTRON Soldering Aid to every contestant in this, your **BIG Certified QUALITY SERVICE CONTEST!**

CBS-HYTRON SOLDERING AID



FIRST PRIZE
... FORD
PANEL TRUCK
 (painted with your name and address and delivered to your door)

9 Other BIG Prizes!

- Second Prize: \$1000 in Savings Bonds
- Third prize: 600 in Savings Bonds
- Fourth prize: 500 in Savings Bonds
- Fifth prize: 400 in Savings Bonds
- Sixth prize: 300 in Savings Bonds
- Seventh prize: 200 in Savings Bonds
- Eighth prize: 100 in Savings Bonds
- Ninth prize: 50 in Savings Bonds
- Tenth prize: 25 in Savings Bonds

Get an ENTRY BLANK with the EASY CONTEST RULES from your CBS-HYTRON DISTRIBUTOR

On this entry blank, complete in 25 additional words or less: "I like the CBS-Hytron Certified Quality Service plan because . . ." Sign your name, then *print* your name and address below your signature. Ask your Distributor's Salesman or Counterpart to help you. *Be sure to print his name and company on line indicated.* (If you win, he wins.) Mail to CBS-Hytron, Dept. (A), A Division of Columbia Broadcasting System, Inc., Danvers, Massachusetts.

GET YOUR KIT AND CONTEST ENTRY BLANK TODAY! ASK YOUR DISTRIBUTOR . . . OR MAIL COUPON,

BUT DO IT NOW!



CBS-HYTRON, Danvers, Massachusetts

Manufacturers of Receiving Tubes Since 1921

A Division of Columbia Broadcasting System, Inc.

A member of the CBS family . . . CBS Radio • CBS Television • Columbia Records, Inc. • CBS Laboratories • CBS-Columbia, Inc. • and CBS-Hytron

FACTS ABOUT YOUR Certified QUALITY SERVICE Plan

If you could advertise nationally, chances are you'd do just what CBS-Hytron is doing for you. You'd tell the world in LIFE and the POST that you promise quality TV and Radio service, parts, and tubes . . . and at fair charges. And that's just what CBS-Hytron is doing for you with advertisements that sell you as a Certified Quality Service dealer . . . a dealer in whom the public can have confidence.

You'd identify your service repair shop as the one people are reading about in the magazines.

You'd use a Certified Quality Service decalcomania on your door. You'd use a Certified Quality Service window streamer and the big LIFE and POST easel display blow-up. Above all you'd use Certified Quality Service tags that tell your customer he is getting more for his money when he

calls your service repair shop . . . because you *Certify* the quality of service, parts, and tubes . . . and at fair charges.

Yes, by using all this material, and more to come, you cash in on your big Certified Quality Service advertising campaign. Get your kit. It contains all the material you need to identify you as a Certified Quality Service dealer. Ask your CBS-Hytron distributor for special deal.

To be eligible for Contest prizes, you must be actively participating as a Certified Quality Service dealer by using the CBS-Hytron Certified Quality Service Promotion Kit; including tags, decalcomania, window streamer, and easel display blow-up. Awards will not be made to any dealer or serviceman not participating by December 15, 1953.



CBS-HYTRON, Danvers, Mass.

Please rush me the Certified Quality Service promotion kit, containing:

1. 18- by 28-inch LIFE and POST easel display . . .
2. New Certified Quality Service decal . . .
3. 8- by 23-inch window streamer . . .
4. AND 250 Certified Quality Service tags imprinted with MY name and address.

HERE IS MY 3-LINE IMPRINT:

Name _____ (please print)

Street _____

City _____ State _____

I enclose \$2.00 to cover the cost of imprinting.

Signed: _____

P.S. Please send me also entry blank with easy Contest rules.

Circuitry Report on 24-Inch TV Chassis Featuring Push-Pull Hi-Fi

AUDIO, once sadly neglected on most TV chassis, at long last has won the attention of the designers, who have become convinced that it merits careful attention.

An interesting example of this new trend appears in the circuit shown in Fig. 1; *Hoffman chassis 403*. A dual triode is used here, with the second half of the triode acting as an audio driver. This drives a push-pull network. A *hi-fi* push-pull type audio circuit, which incorporates two tetrodes, is used. A unique phase inversion scheme is employed; one of the push-pull tubes receives its driving voltage from the audio amplifier in the conventional manner, whereas the second tube receives its equal and opposite phase voltage from a tertiary winding on the audio output transformer, thus eliminating the need for a tube phase inverter. The triode in the audio stage is preceded by a ratio or second sound detector.


The receiver also features use of $\frac{1}{2}$ of a miniature dual diode as a video detector, with the second half providing the clamping voltage for delayed *agc*. The output from this video detector is coupled directly to the video amplifier, through high-frequency compensating shunt and series-peaking coils. A single stage of video amplification is directly coupled to the cathode of the picture tube through high-frequency compensating shunt and series peaking coils. Direct coupling is employed; thus no *dc* restoration¹ circuit is needed. A keyer tube provides the necessary *agc* bias for the first and third *if* stages.

An intercarrier type sound system is employed, the 4.5-mc sound take-off occurring at the output of the video detector. The sound is fed into the first of two 4.5-mc *if* stages. A 39.75-mc adjacent channel picture trap, two 41.25-mc co-sound traps, and a 47.25-mc adjacent channel sound trap are employed in the video *if* stages. The picture carrier frequency is 45.75 mc.

Two Stages of Sync Separation

Two stages of sync separation have been designed into the receiver. They receive the composite video signal from a tap on a video-amplifier load resistor.

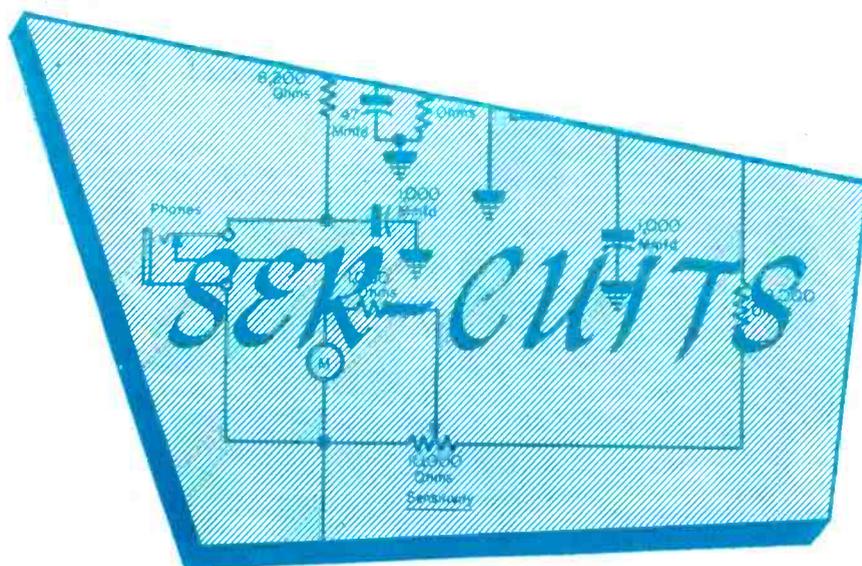A second sync separator serves the additional function of a phase splitter for feeding approximately equal and opposite sync pulses to the balanced horizontal phase detector. A negative sync pulse is taken from a tap on cathode resistor, and this pulse is fed to a vertical integrating network to



by M. W. PERCY

sync the vertical oscillator; a cathode-coupled multivibrator type. This drives a single-power output stage which is coupled to the vertical deflection coils through an output transformer. The positive pulse of the retrace portion of the vertical sweep output voltage is reversed in phase by the transformer action of the output transformer, and the resulting negative voltage pulse is coupled to the picture tube control grid through a .022-mfd capacitor which also serves to sharpen the pulse, so that it is only effective during the retrace portion of the sweep. The negative voltage pulse biases the picture tube beyond cutoff during the retrace portion of the vertical sweep, and the bright retrace lines are blanked out.

Cathode-Coupled Multivibrator

A cathode-coupled type of multivibrator serves as the horizontal oscillator. The stabilizing influence of a parallel tuned *l-c* circuit has been used as part of the plate load of one of the triodes in the multivibrator circuit. The natural frequency of the tuned circuit is very close to the horizontal sweep frequency. The frequency of the horizontal multivibrator has been further stabilized by a balanced horizontal phase detector circuit which consists of a dual diode. The horizontal oscillator drives a stage of power amplification coupled to the horizontal

deflection coils through an output transformer. The horizontal output transformer is also an active member of the high voltage supply.

Horizontal Phase Detector


The horizontal oscillator is preceded by a balanced horizontal phase detector, with many unique operational features.

Without a control voltage on the grid of the horizontal multivibrator, the horizontal sweep section operates at a free-running frequency which is determined by the inductance of the horizontal frequency coil and the horizontal hold control, all other factors remaining constant. These other factors are *r* and *c* component values, *B+* supply voltage, and control voltage at grid 1, which at the moment is assumed to be zero. The nature of the frequency versus *dc* control voltage, characteristic of the common cathode type of multivibrator used in these chassis, is such that a positive change in *dc* voltage on grid No. 1 produces a decrease in frequency and a negative change produces an increase in frequency, all other factors remaining constant. Since *B+* supply voltage changes with line voltage variations and signal strength changes, and the *r*, *l*, and *c* component values change slightly with temperature and humidity, these frequency determining factors do not remain constant. It remains necessary to hold the multivi-

¹See *Geist* article, this issue (p. 32) for revealing study of *dc* restoration.

(Continued on page 58)

Fig. 1. Schematic of 24-inch Hoffman chassis 403, with a push-pull hi-fi output, indicated in dashed outline.

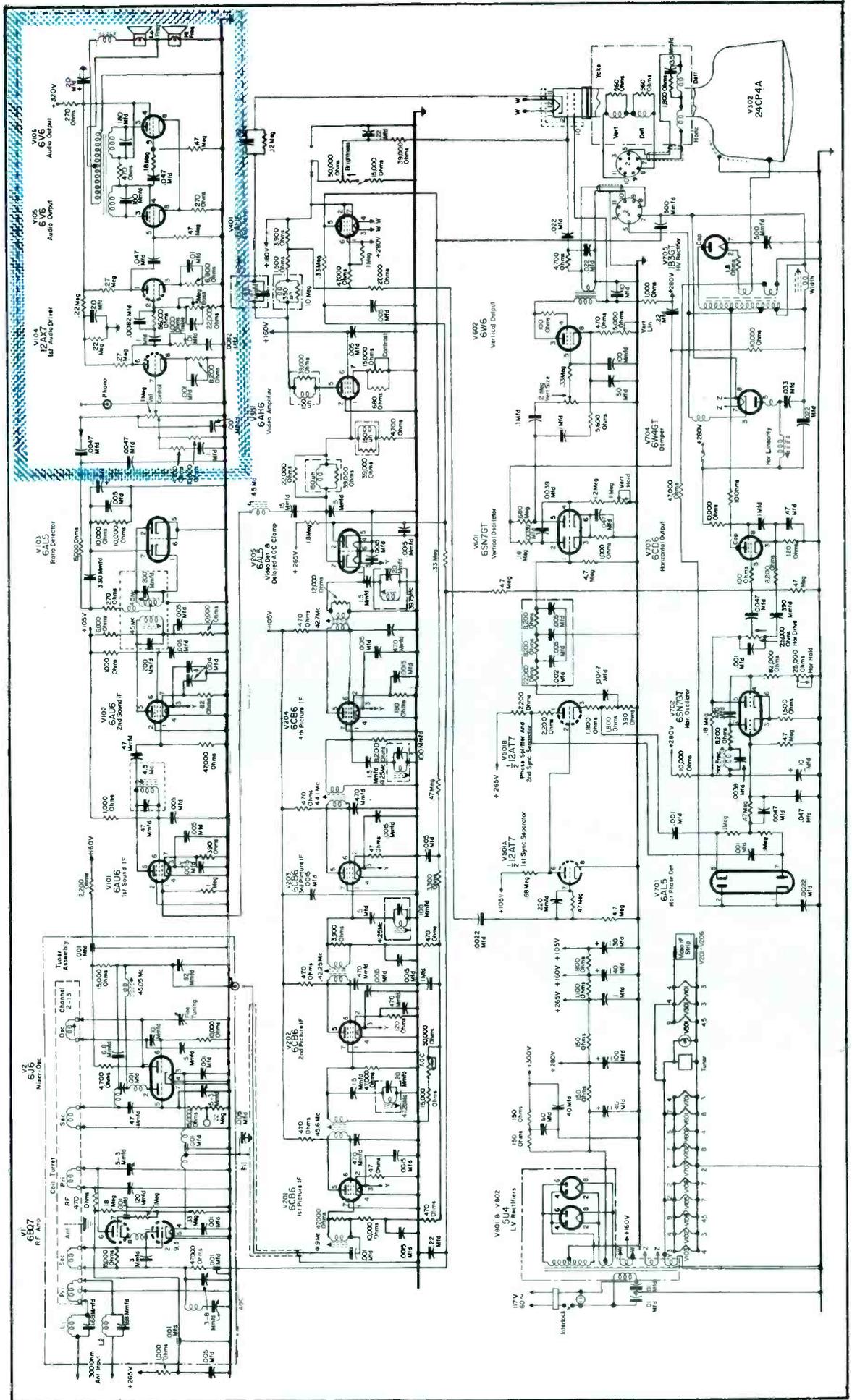

SERVICEMEN NOW... you can have your own needle inspection Kit... FREE!

Here's a chance to have the new 50 Power large field hand microscope for nothing... a scope with a wide angle lens which makes it easy to examine needles—no difficulty in bringing the needle into view quickly to tell if it is worn! But that's not all! You also receive a plastic carrying case; a new

amazing ELECTRO-WIPE cloth; a professional tool for quickly replacing needles. All of this is free if you accept a real bargain, DUOTONE's offer of \$25.00 worth of needles for only \$12.50. Place your order today direct with your jobber!

replacement needles —	\$25.00
one microscope —	5.00
one electro-wipe cloth —	1.50
one plastic kit —	.50
one professional tool —	.50
	\$32.50

ONLY \$12.50



DUOTONE
KEYPORT, NEW JERSEY
Canadian Representative: CHARLES W. POINTON, TORONTO, CANADA
Export Division: AD. AURJEMA, INC., NEW YORK CITY, N. Y.

Terrific wide angle 50. power scope makes it easy to examine needles without even removing them from the cartridge!

Ser-Cuits

(Continued from page 56)

brator to a constant frequency by employing some factor which does remain constant for all practical purposes. This factor is the horizontal sync pulse frequency which originates at the transmitting source. This source is not used directly because of its poor immunity from random noise pulses, but it is used as a reference standard from which the correct value of *dc* control voltage is derived.

It remains to be shown how the *dc*

control voltage is made to vary in such a manner as to counteract changes in the other factors so that the frequency will remain constant. Fundamentally, this is accomplished by comparing a sampling of the instantaneous frequency of the multivibrator output with the standard frequency source.

The difference between the two frequencies is made to generate a *dc* control voltage of such magnitude and polarity that the difference tends to remain zero for all practical purposes. The saw-tooth potential at the input to cathode and plate of the 6AL5 phase-detector tube has an *ac* axis, since *dc*

is blocked by a 1-mmf capacitor in the grid circuit of the 6CD6 horizontal-output tube. The saw-tooth current frequency is the same as the horizontal multivibrator frequency so that the derived saw tooth is used as a sampling voltage. A pair of .001-mfd capacitors serve to couple the sync pulses to the phase detector and to block *dc* as well as to serve as an active part of the phase detector circuit. A 4.7-megohm resistor in the 6SN7GT grid input is used only as a grid leak for the horizontal multivibrator grid 1. Without this grid leak, a failure in the horizontal control tube would leave grid 1 with insufficient bias. Therefore plate and screen dissipation of the 6CD6 would exceed the rated values.

Each diode in conjunction with its respective coupling capacitor forms a rectifier circuit. The capacitor charges during the conduction period of the diode by an amount which is a function of the voltage applied between the diode electrodes.

The most stable state of equilibrium and the one that produces the correct picture frame phase relative to the blanking bar is the zero voltage state. The multivibrator will operate in a state of equilibrium for which the *dc* output of the phase detector is either slightly positive or negative, but this state is less stable. The picture frame phase will be found wrong, and the multivibrator likely to lose sync (equilibrium) when switching channels or interrupting the horizontal sync pulse in some other manner.

Chassis Controls

Phono reproduction may be provided by the use of a double pull, double throw switch; this is accomplished by 1/2 of the brightness control switch. This selector switch performs the function of switching the audio amplifier from the ratio detector output to the phono input and switching the picture tube control grid from the brightness control circuit to ground, cutting off the picture tube raster when the phono is being played.

The *volume* control is part of a dual-type potentiometer, associated with a *contrast* control. The chassis power switch is mechanically linked to the volume potentiometer.

The *contrast* control varies the gain of the video amplifier. With the *agc* system used for maintaining constant signal level, the *contrast* control becomes primarily useful in setting background level for best viewing under various room lighting levels or different average program contrast levels.

The *agc* and its associated circuits regulate *rf* and *if agc* voltages (within

the limits of the *agc* system). When the *agc* control is turned full clockwise the greatest bias appears on the *if agc* bus, and the lowest bias appears on the *rf agc* bus for a given signal. When the control is reversed the *if agc* bias voltage is minimum and the *rf agc* bias is maximum for a given signal. This source of high *rf* bias is useful when strong signals cause the video stages to overload, clipping the sync pulses. In very strong signal areas the *agc* control must be turned counter-clockwise until loss of sync is eliminated. It must not be turned more than necessary because increased bias on the *rf* amplifier, with simultaneous decrease in *if* bias will lead to excessive noise in the picture after a certain point. Conversely, in weaker signal areas the control should be turned clockwise so that the *rf* bias is reduced and the *if* bias increased. This condition will improve the signal-to-noise ratio.

Fault Location

(Continued from page 47)

under conditions of vibration and shock can be predicted before the equipment becomes unserviceable.

(2)—Mechanical tube defects such as faulty or loose welds, partial shorts between tube elements will generate violent output noise signals under the influence of the lightest mechanical taps.

(3)—Cold or rosin joints in wiring to terminals or the points.

(4)—Intermittent wiring or component *shorts* to ground.

(5)—Fixed capacitors with intermittently *open* internal connections. This is one of the most elusive of random failures since it is not detectable through continuity checks and it is obviously impractical to remove each part from the circuit for a capacitance test. Much of the difficulty which has been experienced along these lines has been due to faulty soldering between the aluminum foil and the connecting lead in non-inclusive tubular capacitors.

(6)—Poor contact in circuit controlling devices, such as relays, rotary switches, toggle switches and the like.

(7)—Defective internal joints in molded composition fixed resistors.

(8)—Poor contact between shield cans and chassis in the presence of fairly strong fields or in weak fields associated with low level circuits. Faults of this type may cause random malfunction under changing environmental conditions.

Summarizing, the advantage in using *carrier-amplification* for intermittent fault location lies in the ease

GENERAL INSTRUMENT

all channel UHF converter

sharpest picture ...

For the clearest, sharpest picture, with least interference — make your choice General Instrument. Select General Instrument, the converter that receives all stations in your community. General Instrument is the all channel UHF converter with the SILVER LINES ... cuts forms all others ... is easiest to tune (all channels are spaced evenly around the dial) ... features simple plug-in installation. For the finest UHF converter—General Instrument! *Some choice territories still remain open. Write for details.*



General Instrument & Appliance
CORPORATION

Subsidiary of GENERAL INSTRUMENT CORPORATION • 825 Newark Avenue • Elizabeth 3, N. J.

with which faults may be uncovered and in the ability to predict such troubles before they seriously impair equipment reliability.

The amplification of noise by modulation of a carrier can be deduced from an analysis of a modulated wave.

$$e = E_o (1 + m \sin W_c t) \sin W_c t \quad (1)$$

where:

e = instantaneous amplitude of the wave.

E_o = average amplitude of the wave.
 m = degree of modulation caused by the intermittent fault.


W_c = angular noise frequency component.

W_c = angular carrier frequency.


This may be rewritten as the sum of three voltages as follows:

$$e = E_o \sin W_c t + \frac{mE_o}{2} \cos (W_c - W_o) t - \frac{mE_o}{2} \cos (W_c + W_o) t \quad (2)$$

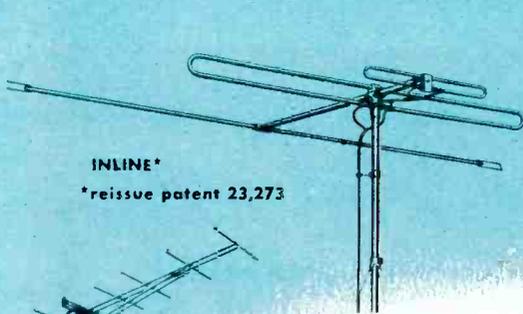The second and third terms of equation (2) show output components whose amplitude is proportional to mE_o . Thus, the more intense the applied carrier frequency, the more susceptible the equipment becomes to the random gain changes induced by intermittent faults.



INLINE*
*reissue patent 23,273

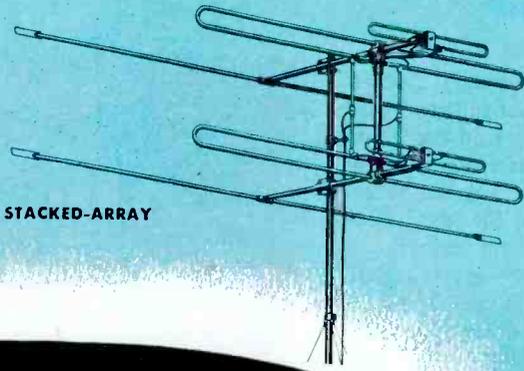

STACKED-ARRAY




YAGI



CORNER REFLECTOR



BO-TY

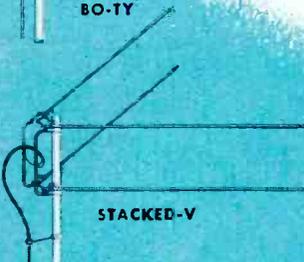

STACKED-V



RHOMBIC



Better Installations

with **AMPHENOL**

TELEVISION ANTENNAS

AMPHENOL antennas have many features of value to servicemen and installers. Because each AMPHENOL antenna is designed with the installer in mind, the entire line of UHF and VHF antennas incorporate *easy-to-install* construction and are factory pre-assembled into an absolute minimum of parts. Because each AMPHENOL antenna is designed with the serviceman also in mind, they feature *stay-up* construction. Craftmanship care in manufacture and the use of fine materials insure longer lasting antenna performance—in all kinds of weather. Finally, the superb electrical characteristics of all AMPHENOL antennas mean better TV picture quality and therefore *customer satisfaction*.

AMPHENOL antennas: *easy-to-install, stay-up* construction and *customer satisfaction*—points to remember in every new or replacement antenna installation.

have you seen it?



Now being shown to enthusiastic audiences of dealers and servicemen-installers all over the country. AMPHENOL'S "The UHF-VHF Television Antenna Story" is a film that you won't want to miss. It fully explains the technical details of UHF—makes it easier to understand by comparing the characteristics of UHF and VHF—and gives, as well, full antenna data. Contact your AMPHENOL distributor for details and be sure and see "The UHF-VHF Television Antenna Story."



the Amphenol "TVAntenna Folio"

A NEW KIND OF PRACTICAL AID FOR TELEVISION SERVICEMEN

Designed to furnish every installer-serviceman with helpful information on UHF/VHF television and thus further aid him in making better antenna installations, the brand new AMPHENOL "TVAntenna Folio" has just been published. It contains a concise resume of television facts and is illustrated with actual Kodachromes from the AMPHENOL film "The UHF-VHF Television Antenna Story." It also contains the latest AMPHENOL antenna and accessories catalog sheets.

AMERICAN PHENOLIC CORPORATION
1830 South 54th Ave., Chicago 50, Illinois
Please send me my free copy of the "TVAntenna Folio"
NAME _____
COMPANY _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____



Fill in the coupon and send to AMPHENOL for your free copy of the "TVAntenna Folio."


AMPHENOL antennas for Better TV Pictures

Electronic Timer Operation, Maintenance and Servicing* . . . 2-Way Installation Hints . . .

Service Engineering

field and shop notes

by **THOMAS K. BEAMER**

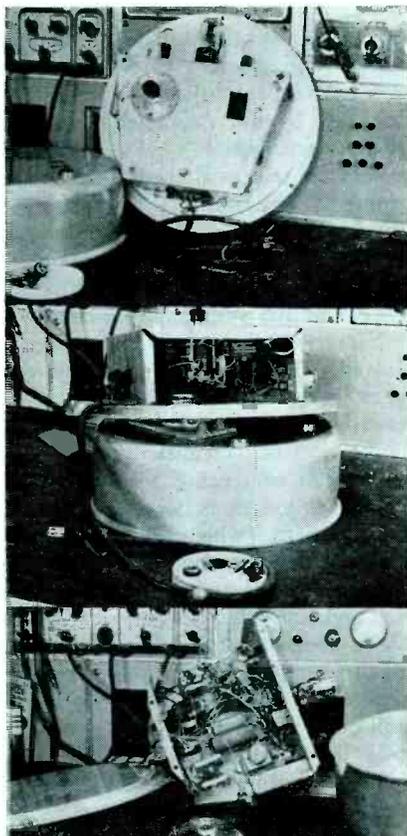

(Top)
Front view of timer chassis, cover removed, with timer dial-scale replaced.

(Center)
Right side view of timer. Relay visible in RL₁, the ac relay. Points of both are accessible from sides.

(Bottom)
Bottom view of timer chassis, removed from backplate. Filters are in center of chassis, two fuses are at bottom, calibrating potentiometer is at lower right side of photo.

THE USE OF TUBES in timing devices has not only increased the effectiveness of timers, but multiplied their application possibilities. Today, for instance, the electronic timer is a key device in the dairy industry; on countless farms such timers (electronic-interval type) are used to control milk flow to the opaque waxed-paper cartons.

These timers control a solenoid-type flow valve. The milk-filling machines¹ employ a microswitch on a *filling-table*, which operates when an empty carton is pushed into position; it opens the valve, holds it open for a predetermined number of seconds, then


closes it. When the machine has been properly set up, each carton receives identical amounts of milk.

The basic principle of the electronic interval-timer is not new, of course, having been employed in numerous circuits, chief among them photographic timers. This application, however, is decidedly novel. All electronic timers operate on the same principle, basically; the charging and discharging of a capacitor. The interval of time involved is determined by the electrical size of the capacitor, the charging voltage, and the value of

(Continued on page 62)

*From notes prepared by Jack Darr.

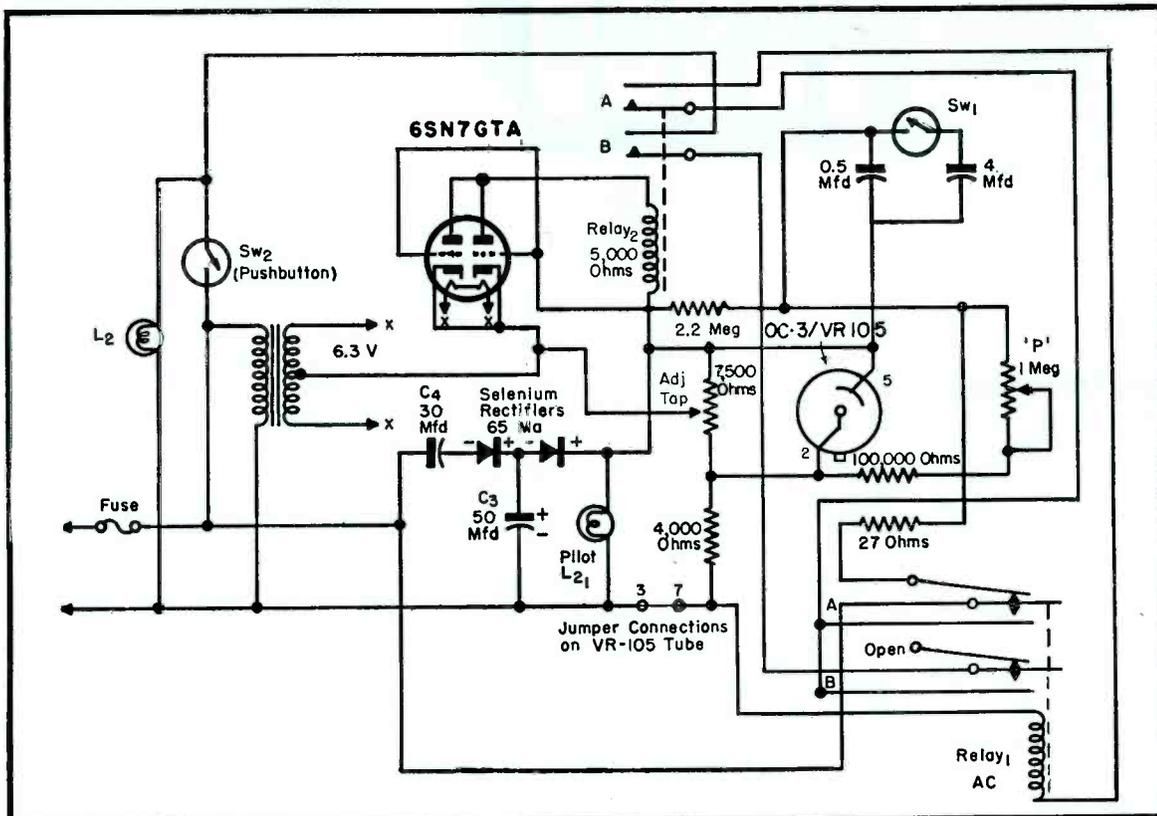¹One typical machine is manufactured by the Mojonner-Dawson Co., Franklin Park, Ill.



Schematic of electronic timer used to control filling of milk containers. P is a calibrating resistance.

face lifting... for a view of TESCO's new
triple-tie cross-over filter...

Printed circuit combines UHF and VHF in a single antenna system requiring only one down-lead

Eliminates signal losses due to interaction between UHF and VHF antennas


Fully impregnated — moisture proof and fungus proof

Wide spaced terminals prevent possibility of shorting out due to ice, rain, snow

Easiest device for connecting a single down-lead to converter or TV set wired for both UHF and VHF

No switches • Favorably priced • Less than 1 db loss

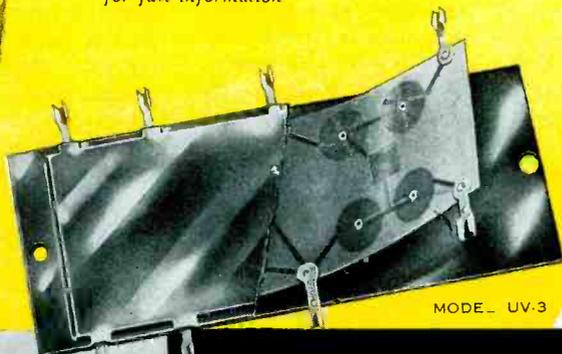Ask your local distributor or write for full information



MODEL UV-3

TV
PRODUCTS
COMPANY
SPRINGFIELD GARDENS
13, N. Y.

TESCO



it's
the
cats
whiskers ... and just as sensitive



the circuit, including the 6SN7 plate relay. The solenoid valve closes, and will not reopen until the cycle is again initiated by the microswitch or *test-switch* pushbutton, SW_2 , which is across the microswitch contacts. Time elapsed is determined by the setting of the 1-megohm potentiometer; the more resistance in the circuit, the longer it takes for the capacitors to reach a charge of 105 volts and discharge.

Service of these units is not too involved. Tubes and all operating voltages must be checked, as on all electronic devices. The power supply, under normal conditions, will read about 300 *vdc*, using a *vtvm*. If the voltage is low, it is necessary to check the rectifiers, (which are 65-ma units) and the doubler and filter capacitors, (which are 30 and 50-mfd units), at 450 and 150 volts, respectively; C_2 and C_1 on the schematic. The 30-mfd unit is the input doubler capacitor; if it weakens or opens up, the high-voltage will drop considerably. Other troubles will be found mainly in the relay points, as might be expected. These units operate under conditions of extremely high humidity; in the milk-room of a dairy, due to the constant sterilizing, washing, etc., the room is always pretty steamy. Some trouble will be found due to corrosion of the points. Although the units are fairly well sealed, some trouble, due to internal dampness will be encountered. A rubber ring gasket, provided under the outer cover, must be carefully replaced each time the unit is serviced.

Two pilot lights are used; a red and a green. The red light indicates when the unit is turned *on*, and the green lights when the unit is actually cycling.

To insure best continuing results, monthly maintenance checks are a must. During such inspections, contact points can be probed. If they are *papered* each time, they will give fairly long life. In this operation a small strip of clean, fairly-course paper should be drawn between each pair of points, while holding them closed; the surface of the paper will polish them to a high degree, and will not cause pitting. If the points are found to be badly pitted, they should be removed from the relay, and smoothed on a very fine oilstone, keeping them perfectly flat; finishing can be completed by polishing with jeweler's rouge or *plug-polish* as used in telephone exchanges, until a mirror-smoothness is obtained.

Wiring in the cable, connecting the timer unit and the solenoid, etc., on the filling table is subject to trouble. In one instance, the *strain-relief* clamp on the plug was not fastened properly;

Service Engineering

(Continued from page 61)

the calibrating resistance in the circuit.

This particular unit uses two capacitors; 4 and .05-mfd 600 working-volt types. For normal use, they are connected in parallel; for shorter time intervals, the larger capacitor may be switched out by means of SW_1 shown in the schematic (p. 61). This results in a much faster time-constant. The capacitors are charged through a 1-megohm calibrating resistance; P on the drawing. An OC-3/VR-105 voltage-regulator serves as the discharging element; action is initiated by a 6SN7GT,

used with both triode elements connected in parallel.

When a carton is placed in the machine, the microswitch is closed, and the 6SN7 closes a 3,000-ohm plate relay. This closes the main relay RL_1 , an *ac*-operated type, and the contacts of this unit open the solenoid valve, through a 6-contact plug. High voltage from the power supply, a half-wave voltage doubler using two selenium rectifiers, is applied to the capacitors. The voltage gradually builds up until it reaches the level set by the VR-105, which then fires, discharging the capacitors and opening

this must be checked when servicing, as this cable is subject to much strain and wear. (Color code of the wiring into the plug is: Pin 7, heavy red lead; pin 8, heavy black lead; pin 9 small rubber-covered wire (white); pin 10, small RC wire, (brown); pin 11, small RC wire (green . . . this is a ground wire); and pin 12, no connection.)

If the machine is electrically hot to the ordinarily very damp floor, the polarity of the ac supply plug should be checked to determine which side is grounded. It should be connected this way, and the plug and socket marked with bright nail-polish, scotch tape, or something similar, so that it may be replaced correctly, if removed for any reason.

2-Way Installation‡

SOME FORM of noise suppression is required whenever a 2-way system is installed in a motor vehicle. Since the receivers in these setups are sensitive to very small electrical disturbances, it is important that unwanted disturbances be eliminated. Such disturbances are produced by the ignition system, electrically-operated accessories, and static discharge (between the front wheels and their bearings, between tie rods, or between other parts of the vehicle which are in intermittent contact). Noise-elimination procedures may vary from installation to installation, and the effectiveness of any procedure can be determined only by trial. A suppressor should always be installed in the high-tension lead to the distributor; by pulling the center lead out of the distributor cap, cutting the lead about 1/2" from the distributor end, screwing the ends of the suppressor into the cable ends just formed, and then reconnecting the cable to the distributor cap. In operating areas where the signal strength is high, additional noise suppression may not be required.

A high-pitched sound (heard only when the motor is running) can, in most cases, be eliminated by connecting a 1-mfd paper capacitor between the output terminal on the generator and the motor block. If generator noise persists, it is recommended that a filter (made by close winding 22 turns of No. 12 enamel wire on a 1 1/8" diameter form) be connected in series with the generator output. Each end of this filter should be bypassed to the motor block through a 1500-mmfd mica capacitor.

Maintenance and Troubleshooting

UNDER FCC regulations, all transmitter tuning adjustments must be
(Continued on page 77)

‡Based on RCA engineering department notes.



There's REAL Money in TV Signal Distribution

with the

Add-A-Unit

MASTER TV SYSTEM for UHF and VHF



**The B-T Add-A-Unit System is a new tool.
It is your 'open sesame' to the biggest boom
that has ever hit the TV servicing industry.**

Hotels, motels, schools, apartment houses, community developments, hospitals, and hundreds of others with multi-receiver problems are clamoring for low cost, easy-maintenance, efficient TV distribution systems.

This is YOUR BIG MARKET...your real money market

The B-T Add-A-Unit System offers you these advantages:


1. It is the lowest cost amplified distribution system ever designed.
2. It is the easiest system to install under all conditions . . . requires no special tools and no outside engineering assistance.
3. Its flexibility is practically unlimited and it can serve 2000 TV receivers as effectively as it can serve 2.
4. It has no 'bugs' and requires little or no maintenance.
5. It permits complete control of signal strength: amplification or attenuation, as may be required, assuring high quality reception at all TV outlets from all available channels.
6. Every B-T Master System installed by you is a sure fire 'clinch' for additional business.

**Let the B-T System
Work for You.**


The B-T Add-A-Unit Master TV System consists of the following B-T units:

- MIXER AMPLIFIER
- DISTRIBUTION AMPLIFIERS
- COMMERCIAL ANTENSIFIER
- RESISTOR OUTLET BOX
- TV SYSTEM ACCESSORIES

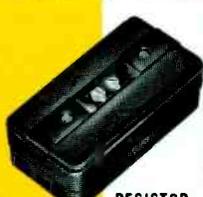Attenuator Matching Transformer
Remote Control Line Splitters
Line Loss Equalizer
Weather-Proof Housing



RESISTOR
OUTLET BOX

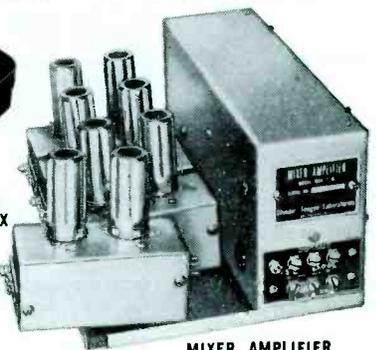

MIXER AMPLIFIER

Write to Dept. NK-8 for Free Installation Manual
and Complete Specification Data.

BLONDER-TONGUE LABORATORIES, INC.

Westfield, New Jersey



TV Station Listing: Part 3

Now on the Air and
Authorized to
Operate**

City	Call Letters	Channel	City	Call Letters	Channel	City	Call Letters	Channel
OHIO			OREGON			PENNSYLVANIA		
Akron	WAKR-TV	Summit Radio Corp., 106 S. Main St. 49*	Eugene	KTVF	W. Gordon Allen, 260 Henderson Ave., Salem 20	PENNSYLVANIA		
Ashtabula	WICA-TV	WICA, Inc., 221 Center St. 15	Medford	KBES-TV	Eugene Tele. Inc., Box 112 13	PENNSYLVANIA		
Cincinnati	WCPO-TV	Scripps-Howard Radio, Inc., 2345 Symmes St. 9†	Portland	KPTV	Southern Oregon Bcstg Co., Box 148, Grants Pass 5	Wilkes Barre	WBRE-TV	Louis G. Baltimore, 62 S. Franklin St. 28*
	WKRC-TV	Radio Cincinnati, Inc. 12‡			Empire Coil Co., Inc., 85 Beechwood Ave., New Rochelle, N. Y. 27*	Williamsport York	WRAK-TV	WRAK, Inc., 244 W. 4th St. 36
	WLWT	Crosley Bcstg Corp., 140 W. 9th St. 5‡	Salem	KPIC	Lawrence A. Harvey, 19200 S. Western Ave., Torrance, Calif. 24		WNOW-TV	The Helm Coal Co., Box 226 49
	WCIN-TV	Rounsaville-Clark Tele. Co., 3165 Mathieson Dr., N.E., Atlanta, Ga. 54	PENNSYLVANIA				WSBA-TV	Susquehanna Bcstg Co., 53 N. Duke St. 43*
Cleveland	WEWS	Scripps-Howard Radio, Inc., 1816 E. 13th St. 5‡	Altoona	WFBG-TV	The Gable Co., 1320 11th Ave. 10*	RHODE ISLAND		
	WNBK	Nat'l Bcstg Co., Inc., 815 Superior Ave. 4 (3)†	Bethlehem	WLEV-TV	Associated Bcstrs Inc., 516 Northampton St., Easton, Pa. 51*	Providence	WJAR-TV	The Outlet Co., 176 Weybosset St. Channel 16 of Rhode Island, Inc., Industrial Trust Bldg. 16
	WXEL	Empire Coil Co., Inc., 1630 Euclid Ave. 9 (8)†	Chambersburg	WCHA-TV	Chambersburg Bcstg Co., Craft Press Bldg. 46	SOUTH CAROLINA		
	WERE-TV	Cleveland Bcstg Inc., 1501 Euclid Ave. 65	Easton	WGLV	Easton Publ. Co., 30 N. 4th St. 57	Camden	WACA-TV	Camden Bcstg Corp., Sta. WACA 14
Columbus	WBNS-TV	Dispatch Printing Co., 34 S. 3d St. 10‡	Erie	WICU	Dispatch, Inc., 3514 State St. 12‡	Charleston	WCSC-TV	WCSC, Inc., Francis Marion Hotel 5*
	WLWC	Crosley Bcstg Corp., 3165 Olen-tangy River Rd. 3 (4)†	Harrisburg	WTPA	Harrisburg Bcstrs Inc. 11 N. 2nd St. 71*	Columbia	WCOS-TV	Radio Columbia, Cornel Arms Bldg. 25*
	WTVN	WTVN, Inc., LeVogue Lincoln Tower 6‡		WHP-TV	WHP, Inc., 216 Locust St. 55*		WNOK-TV	Palmetto Radio Corp., Box 5307 67
Dayton	WHIO-TV	Miami Valley Bcstg Corp., 45 S. Ludlow St. 7‡	Hazleton	WAZL-TV	Hazleton Tele. Corp., Hazleton Nat'l Bank Bldg 63		WIS-TV	WIS-TV Corp., 1111 Bull St. 10
	WLWD	Crosley Bcstg Corp., 4595 S. Dixie Highway 7‡	Johnstown	WJAC-TV	WJAC, Inc., 329 Main St. 6‡	Greenville	WGVL	Greenville Tele. Co., Calhoun Towers 23
	WIFE	Skyland Bcstg Corp., 5 S. Jefferson St. 22	Lancaster	WARD-TV	Rivoli Realty Co., 502 1st Nat'l Bank Bldg. 56	Greenwood	WCRS-TV	Greenco, Inc., Box 868 21
Lima	WLOK-TV	WLOK, Inc., 1101 Nat'l Bank Bldg. 73*	Lebanon	WGAL-TV	WGAL, Inc., 8 W. King St. 8‡	SOUTH DAKOTA		
	WIMA-TV	Northwestern Ohio Bcstg Corp., 223 N. Main St. 35	Lewiston	WMRF-TV	Lewiston Bcstg Co., 5 W. Market St. 38	Sioux Falls	KELO-TV	Midcontinent Bcstg Co., 8th & Phillips Ave. 11*
Massillon	WMAC-TV	Midwest TV Co., 500 Security Bldg., Toledo 23	New Castle	WKST-TV	WKST, Inc., Cathedral Bldg., E. Lincoln Ave. 45*	TENNESSEE		
Sandusky	WLEC-TV	Lake Erie Bcstg Co., Cleveland Rd & Huntington Ave. 42	Philadelphia	WCAU-TV	WCAU, Inc., City Line & Monument Ave. 10‡	Chattanooga	WOUC	Chattanooga TV-Inc., 1024 James Bldg. 49
Toledo	WSPD-TV	Storer Bcstg Co., 136 Huron St. 13‡		WFIL-TV	Triangle Publications Inc., 400 N. Broad St. 6‡		WTVT	Tom Potter, 1032 Life of America Bldg., Dallas, Tex. 43
Warren	WHHH-TV	The Warren Tribune Radio Sta. Inc., 108 Main St. 67		WPTZ	Westinghouse Radio Stations Inc. 3‡	Johnson City	WJHL-TV	WJHL, Inc., 145 W. Main St. 11
Younastown	WFMJ-TV	The Vindicator Printing Co., Vindicator Sq. 73*		WIP-TV	Penna. Bcstg Co., 35 S. 9th St. 29	Knoxville	WCEE-TV	Tele. Services of Knoxville 26
	WKBN-TV	WKBN Bcstg Corp., 17 N. Champion St. 27*	Pittsburgh	WDTV	Allen B. DuMont Labs., Inc., Chamber of Commerce Bldg. 2‡	Memphis	WHBQ-TV	Harding College, Gayosa Hotel 13
	WUTV	Polan Industries, 321 8th St., Huntington, W. Va. 21		WTVQ	Golden Triangle Tele. Corp., 5 S. Jefferson Dr., Dayton, Ohio 47	Nashville	WMCT	Memphis Publ. Co., 495 Union Ave. 5‡
Zanesville	WHIZ-TV	Southeastern Ohio Tele. System, 48-52 N. 5th St. 50*		WENS	Telecasting Co. of Pittsburgh, Pa., 535 Smithfield St. 16		WSM-TV	WSM, Inc., National Bldg. 4‡
OKLAHOMA				WKJF-TV	Agnes J. Reeves Greer, 238 Spruce St., Morgantown, W. Va. 53*	TEXAS		
Lawton	KSWO-TV	Okla. Quality Bcstg Co., Box 699 7*	Reading	WHUM-TV	Eastern Radio Corp., Berkshire Hotel 61*	Abilene	KRBC-TV	The Reporter Bcstg Co., 984 N. 4th St. 8
Miami	KMIV	Miami Tele. Co., Box 420, Wichita Falls, Tex. 58		WEEU-TV	Hawley Bcstg Co., 433 Penn St. 33*	Amarillo	KGNC-TV	Plains Radio Bcstg Co., 8th & Harrison 4*
Oklahoma City	WKY-TV	WKY Radiophone Co., 500 E. Britton Ave. 4‡	Scranton	WTVU	Appalachian Co., 519 Mulberry St. 73		KFDA-TV	Amarillo Bcstg Co., Inc., 800 Hawkins St. Brownsville, Texas 10*
	KTVO	Okla. County Tele. & Bcstg Co., c/o KWCO, Chickasha, Okla. 25	Footnotes:			Austin	KTBC-TV	Texas Bcstg Corp., Box 717 7*
	KMPT	KLPR Tele. Inc., 128½ W. Commerce 19	‡Licensed pre-freeze station.			Beaumont	KBMT	Television Bcstrs, Box 1592 3‡
Tulsa	KOTV	Wrather-Alvarez, Inc., 302 S. Frankfort St. 6‡	*Operating under special authority since freeze lift.			Dallas	KRLD-TV	KRLD Radio Corp., Herald Square 4‡
	KCEB	Elfred Beck 3302 S. Florence St. 23	†Sharing time.				KDTX	UHF Tele. Co., Magnolia Bldg. 23
			‡Old and new channel assignment.			Footnotes:		
			**Stations without superscripts have been authorized to operate, but have not begun to telecast.			(Continued on page 98)		



Why didn't someone do this before?



Only Superotor®


has the Quick Detachable Drive Unit



A **Leader** FIRST!




"TERRIFIC!" say TV servicemen — and you'll echo their words when you see the amazing new Superotor. Imagine — a drive unit as easy to replace as a light bulb! Strictly a one-man job! No fussin', no cussin', — no need to dismount the antenna — no need to interrupt TV viewing while the drive unit is being serviced. Great? Yes! — and this is just one of FIVE major advances that put Superotor years ahead of anything on the market. No wonder the big switch is to Superotor!

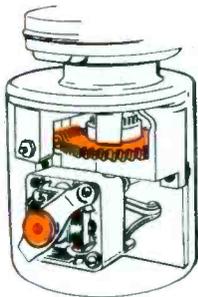

- Double Lock Stop Prevents Drift & Coast

A **Leader** FIRST!

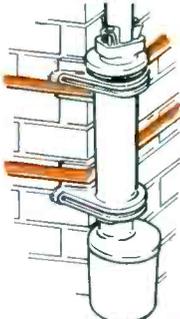

- Built-in Chimney Mount Design

A **Leader** FIRST!



- Steel Reinforced Construction

A **Leader** FIRST!

VP* Tuning

*Vernier Precision

A **Leader** FIRST!



Patent Applied for Copyright



2925 EAST 55th ST., CLEVELAND 27, OHIO

... LEADING THE WAY TO BETTER PRODUCTS

In The Field[†]

Problem



Analysis

WHY DO ratio-detector S curves appear entirely below or above zero-reference lines; and 4.5-mc marker indications not go through nulls?



HALF OF the bleeder resistor across the stabilizing capacitor may be shorted. In addition, AM rejection of the circuit may also be poor. Strong sync buzz may also be passing into the audio circuits.

Fig. 1. Waveforms illustrating conditions obtained when strong sync buzz is passed into audio circuits, or half of the bleeder resistor across the stabilizing capacitor is shorted.

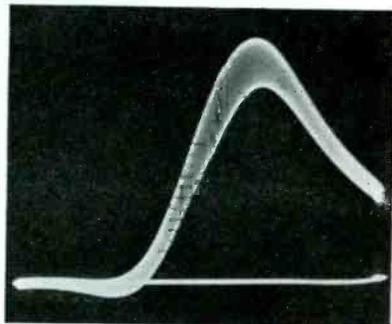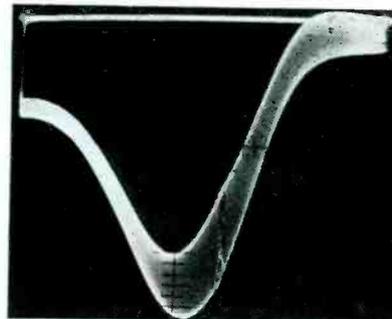


WHAT HAPPENS when the horizontal sawtooth reveals very sharp corners and indicates stronger, higher harmonics?



THIS CONDITION can cause interference in radio receivers.

Fig. 2. Horizontal sawtooth with sharp corners which can result in interference to radio sets.

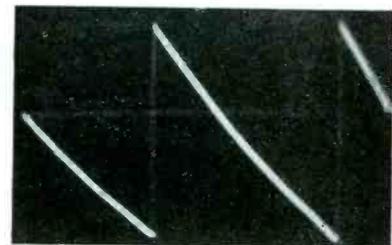


WHAT HAPPENS if the horizontal sawtooth has rounded corners, and also shows weaker higher harmonics?



THIS CONDITION is less likely to produce interference in radio sets.

Fig. 3. Rounded-corner horizontal sawtooth waveform which is less likely to produce interference to AM sets.

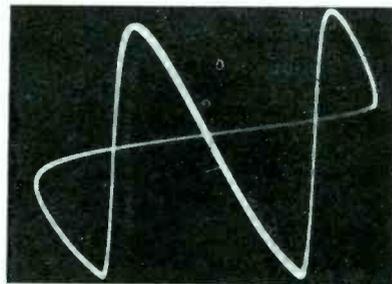


WHAT DOES spurious ac voltage in the B+ line cause?



IT PERMITS voltage from one section to back up into other receiver sections, and produces extremely hard-to-find troubles.

Fig. 4. Spurious ac voltage in B+ line.

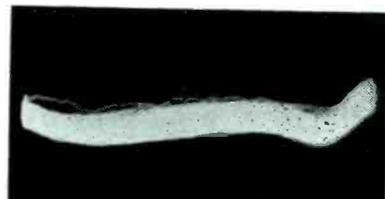

Analysis of Ratio-Detector S Curves Appearing Below and Above Zero-Reference Lines . . . Characteristics of Horizontal Sawtooths . . . 60-Cycle Line-Voltage Harmonics . . . Damper Output-Waveforms

Problem

Analysis

WHAT OCCURS when there are harmonics in the 60-cycle line voltage?



SUCH HARMONICS can be disturbing when used to sweep the 'scope in visual-alignment procedures. The harmonics are usually enhanced by small series capacitors.


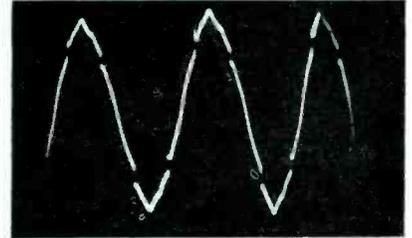


Fig. 5. Waveform which appears when there are harmonics in the 60-cycle line.

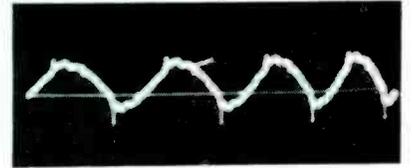

Fig. 5a. Another example of harmonic trouble, enhanced by passage through capacitor probe. This can cause operator to draw false conclusions if the passage through probe is not recognized.



WHAT WILL HAPPEN if the damper-output waveform has sharp peaks which contain high harmonics?



PICTURE (*spook*) interference will result. This can be trapped out.

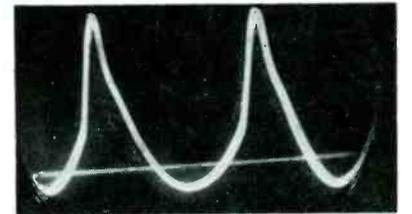


Fig. 6. Sharp peak damper output waveform with high harmonics which usually indicates picture or spook interference.

WHAT DOES OVERSHOOT in a square-wave test of the video amplifier indicate?



THIS INDICATES an underdamped circuit, and can produce a trailing reversal in the picture.

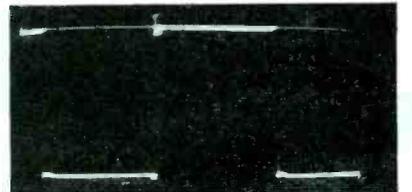


Fig. 7. Overshoot in square-wave test of video amplifier.

WHAT CAUSES ringing and excessively slow rise in a square-wave test of the video amplifier?



A FAULTY high-frequency response of the video amplifier. It produces a smear in the picture.

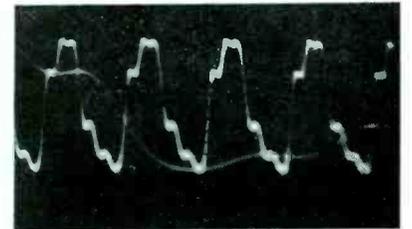


Fig. 8. Waveform produced by a faulty hi response of the video amplifier.

WHAT KIND of a pattern will appear when there is a mismatch of the antenna to the lead-in on a swept channel?



SUCH a pattern is shown in Fig. 9. Some video frequencies are attenuated in voltage with respect to other video frequencies, and thus the waveform shown. Extreme mismatch also produces smear.

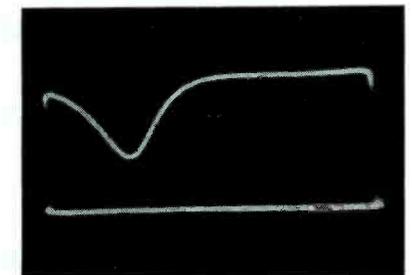


Fig. 9. Waveform obtained on swept channel when antenna is mismatched to a lead-in: Video frequencies are attenuated in voltage with respect to other video frequencies.

‡Based on question posed during meetings conducted by R. G. Middleton, senior engineer at Precision Apparatus Co., Inc., and author of *TV Trouble-Shooting and Repair Guide Book*, published by John F. Rider.

IMPACT IN UHF

FINCO

series 500

Great UHF ANTENNAS

Engineered To Give
HIGHEST GAIN and
NARROWEST PATTERNS
 to solve difficult "GHOST"
 problems in the **FRINGE**
AREA AND IN CLOSE
TO THE STATION

IMPACT

Through Advertising

LOCAL NEWSPAPERS

LIFE

FARM MAGAZINES

RADIO

TELEVISION

**FINCO IS A NAME
 YOUR CUSTOMERS
 KNOW BECAUSE OF
 THIS POWERFUL
 NATIONAL ADVERTISING
 PROGRAM!**


**THE
 FINNEY COMPANY**

Dept. S-310 - 4612 St. Clair Ave., Cleveland 3, O.


This great series once again reaffirms Finco leadership! Model 502 is a 2-bay unit of the colateral* type with a "snap-out" screen for instantaneous installation. Model 504 is the 4-bay version, highly effective in super fringe areas where ultra high gain is consistently required. Both models feature high front to back ratio and excellent impedance match to 300 OHM line for low signal fringe areas. Completely preassembled — corrosion proof aluminum throughout (including screen) — one antenna, one transmission line!

Both Units available in 3 models which peak on channel ranges shown below and maintain high gain on balance of frequencies:

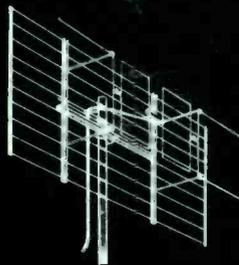- # 502A — channels 14-32
- # 502B — channels 29-55
- # 502C — channels 53-83



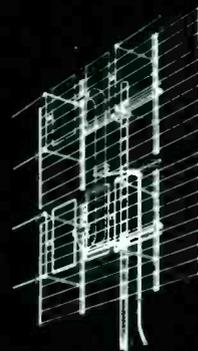- # 504A — channels 14-32
- # 504B — channels 29-55
- # 504C — channels 53-83



Patent No. 2,566,287
 *Reg. U.S. Pat. Off.



Leonard R. Smith, TEA president.

Highlights of the Radio and TV Service Clinic and Electronics Fair Held in Fort Worth, Texas



THE SWIFT GROWTH of TV since the freeze lift received a booming tribute in Texas a short while ago, when the Texas Electronic Association held its first Radio and Television Service Clinic and Electronics Fair, a 3-day conclave, in the Texas Hotel, Fort Worth.

Over 500 Service Men, dealers and manufacturer's reps came to see a host of outstanding exhibits, and listen to the nation's best review all phases of TV.

Among those who addressed the boys were *James Secrest*, executive veep of RETMA, who described the tremendous potential in TV; *Forrest L. Baker*, immediate past prexy of TEA, analyzing service costs; *Al Robertson*, an Oklahoma City Service Shop operator, reviewing methods that can be used to merchandise servicing; *William D. Renner* of Howard Sams, covering uhf; *Hal Chase*, president of the Television Service Association of Michigan, reporting on business management of service shops; *John F. Rider*, surveying new developments in color TV and transistors; *Mort Farr*, past prexy of NARDA, offering advice to the new TV Service Man; *Clint Walters*, RCA Service Co., explaining transistor operation and application; and *Leonard R. Smith*, prexy of the association, who delivered the keynote address. Also featured was a panel discussion of problems in industry. Among those who participated were *Russel C. Hansen*, manager of the contract service department of Motorola; *R. J. Yeranko*, general service manager of Magnavox; *Bill Satterfield*, national electronics service manager of Philco; and *Dan Creato*, vice prexy of RCA Service Co. *James Palmer*, electronics service manager of the West Texas Appliance Company, acted as panel moderator.

In a bristling talk, Len Smith struck out at those who charged that all Service Men were guilty of malpractice and chicanery.

He said that he refused to believe that there is any large element of service which is not dedicated to the highest standards of operation. "I refuse to condone any contentions from any source," he emphasized, "that our field is peppered with racketeers and dishonest practitioners. Yet it would be blindness not to recognize that there are practices which, if they were destroyed, would better the industry and better the calibre of service we can render the public."

In a review of these problems, it was noted that when manufacturers require that Service Men maintain a special type

of in-warranty parts replacement tag for his brand, work is only complicated unnecessarily. Overlong delays and excessive red tape can only handicap Service Men, and when obscure, unknown replacement parts are used to save a few pennies and perhaps force unnecessary added service, a wrong is done, Smith added.

Continuing, the new prexy said that false claims in advertising, books that state the owner can repair his set, distorted statements about the cost of service which compel artificial charges for parts, incompetent men entrusted with advanced technical assignments, installations made with mounting brackets and hardware that are not corrosion-proof and rust-proof, inadequate safety precautions and insurance, hurt every Service Man whether we indulge in them or abhor them.

Hammering away at retail salesmen who give the customer the distinctly false impression that the set does not require service or that the warranty includes service, Smith declared that the customer should be taught at the time he buys the set to expect to pay for service, just as the car purchaser today expects to pay for service when he buys his car. In conclusion, the TEA headman said: "We meet in harmony here. We hope that harmony grows to where our parts jobbers wouldn't think of selling to the consumer—often our customer—at the same prices we pay for our quantity purchases. In turn, we must show them the same kind of loyalty we expect from them, buy from our own suppliers in our

own markets rather than from some surplus jobber who may well betray us on any order they ship. . . . Our industry is too big, too constructive, too rich with potential, too needed by the public for us to permit ugly little practices to arise in it. Let's band together, then, for a cause we know is right, and we can have the satisfying knowledge that we will have all right-thinking people with us, working to make a tomorrow we can look forward to with satisfaction, dignity and pride."

RETMA's spokesman, Jim Secrest, also stressed the import of the Service Man. In his opinion, the Service Man, given a satisfactory product, is probably more often responsible than the manufacturer for the consumer's satisfaction or complaints. In all instances, it was noted, he is closer to the set owner than the manufacturer and therefore in a better position to create good or ill will for the product and the industry.


"The role of the Service Man has become much more important since the advent of television," added Secrest. "In the radio-only days many set owners did their own servicing and some found, like my young son of that day, that a few hard knocks on the plastic cabinet of a table radio produced remarkable results. . . . As for manufacturing, it was a stock joke in the industry—and very nearly true—that anyone with a screwdriver, a pair of pliers, and a soldering iron could get in the business and often did. It was the heyday of the loft operator."

Television, it was emphasized, changed this situation from a bonanza for ama-

(Continued on page 76)

At recent Service Men meeting in Chicago sponsored by Raytheon and Allied Radio which featured talks by C. W. Hoshour, Raytheon service manager, William Ashby of Raytheon, Jack Lizars of Allied Radio, John F. Rider, and Frank Mock, president of TISA. Left to right: J. Lizars; E. Ralph Haines, Raytheon tube rep in Chicago area; William Ashby; Carroll Hoshour; and F. E. Anderson, distributor sales manager, Raytheon receiving tube division.



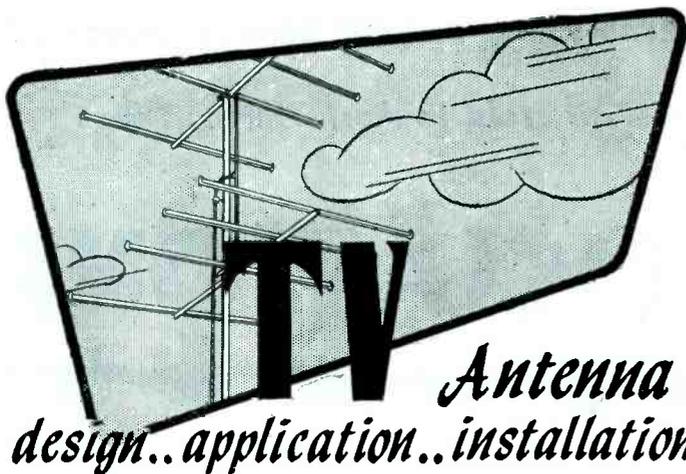

Antenna Digest

design.. application.. installation.. service

Results of UHF Area Survey in Easton-Allentown-Bethlehem, Penna.*

by RALPH G. PETERS

AREA SURVEYS are extremely helpful in predetermining receiving possibilities, providing an accurate gage of locations and the antennas that will work best. With the advent of *uhf*, such surveys have become increasingly important because of the extreme beam-like direction of ultrahigh signals.

On several occasions,¹ the results of surveys conducted in the east and mid-west have been published in these columns. A short time ago, the Easton-Allentown-Bethlehem area in Pennsylvania was the scene of a comprehensive area study, prompted by the installation of a new *uhf* station, WGLV.²

In planning this survey, six to seven sites were chosen for their relative local importance, in each of the three major cities.

Busy intersections in the downtown areas, as well as central spots in vari-

ous residential districts, were selected without regard to conditions which might promote favorable reception. Several sites were chosen in nearby communities of importance, and a single representative location was used in a number of outlying towns.

Procedure

Upon arrival at a previously selected site measuring equipment was set up and an antenna moved about and oriented for optimum reception on each channel. During all measurements the antenna was at a height of 12' above the ground. Since signal strength is commonly discussed in terms of micro-

volts per meter at an elevation of 30', the data tabulated was corrected to the 30' level.

All *uhf* signals were monitored on a standard TV receiver with a built-in *uhf* tuner. In no instance was man-made noise seen to produce interference. In practically all cases, without any antenna connected to the receiver terminal, the picture was found to be completely noise free. It was possible to eliminate completely ghosting or multi-path transmission in all but one or two locations.

In the tests, it was also decided to evaluate *uhf* versus *vhf* picture quality and reception.

Since the physical dimensions of an antenna vary inversely with frequency, the *uhf* antenna intercepts fewer lines of the electromagnetic field than does the larger *vhf* antenna. This means that a greater field intensity is required to produce a picture from *uhf* than from *vhf*.

The *uhf* antenna because of its relatively small dimensions, however, is easily adapted for high gain and may be expected to provide twice the gain which is practical in a comparable situation on *vhf*.

Man-made and atmospheric noise is almost non-existent at *uhf* frequencies. Thus, surplus *uhf* signal is unneces-

(Continued on page 93)

Table 1: Measured TV fields in outlying towns.

Site	VHF Station		UHF Station	
	A	B	A	WGLV
Nazareth				
Town Square..	43	205	900	4,400 (8.2 mi.)
Pen Argyle				
Fire House ...	168	298	330	2,800 (16.5 mi.)
Frenchtown				
Rte 29 down- town	13	140	...	1,350 (12.4 mi.)
Catasqua				
6th and Chapel.	23	173	1,750	10,000 (11.5 mi.)
Northampton				
8th and Dewey	45	130	1,400	12,000 (13 mi.)
Bangor				
Main and Market	23	35	...	950 (16.5 mi.)
Bangor				
On Hill S.E. of Center.....	130	7,800 (16.4 mi.)

Table 2: Typical results of measured TV fields in Allentown and Bethlehem. Measurements were made at 12' and corrected to 30' in accordance with FCC standards. Fields shown are in microvolts-per-meter.

Site	VHF Station		UHF Station	
	A	B	A	WGLV
Allentown				
Hamilton and 7th	30	65	700	4,400
Route 22 and Schoenersville Rd.	35	123	5,500	10,500
Route 309 and Susquehanna St. ...	28	100	1,350	1,350
Hamilton and 15th	10	180	700	2,100
Route 22 and 19th	25	198	5,000	5,500
Route 22 at Span- ish War Monu- ment	18	138	1,100	3,500
19th and Rath...	50	122	1,600	12,500
Bethlehem				
Alt. Rte 22 and Minsi Trail ...	13	123	3,000	15,500
Alt. Rte 22 and New	10	38	630	3,300
Rte 22 and Nazareth Pike.	20	73	2,100	5,000
Center and Illick's Mill Rd.	23	85	2,350	17,500
Rte 22 and 8th...	23	58	560	10,000
4th and Cherokee (South Side) ..	28	38	140	1,100
4th and Lynn (South Side) ..	20	125	560	25,000

*From a report prepared by Paul Godley Company, consulting engineers.

¹SERVICE; January, June, July, August, 1953.


²Channel 57, operating at 100,000 watts, effective radiated power from Gaffney Hill with antenna 1,460' above sea level.

Table 3: Noise-free and usable picture requirements in microvolts-per meter. These data are based on the assumption that a properly installed outdoor antenna is used. Indoor and built-in antennas require considerably more field intensity for equivalent pictures.


Picture Quality	Area	Channels		
		2-6	7-13	14-83
Noise-free	Urban	500	500	1,000*
Good-Usable..	Urban	300	300	500*
Noise-free	Rural	150	300	1,000*
Good-Usable..	Rural	75	150	500*

*UHF conversion strips used in *vhf* receivers require approximately twice this signal. Figures are for *uhf* receivers and converters.

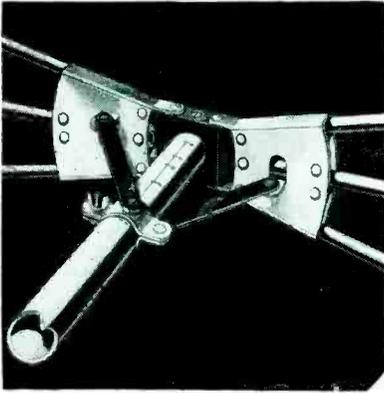
Pictorial Review of Latest in UHF/VHF Antennas . . . Rotators . . . Boosters



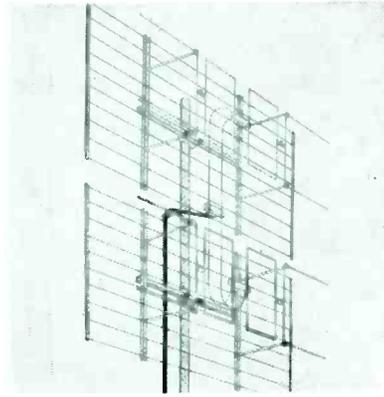
A conical, that's variable, with element heads coupled to a sliding sleeve on the boom. Sliding sleeve is moved to calibration mark on the boom which is said to correspond to the channel peaking desired. Butterfly springs snap elements into position and lock them. (Vari-Con; Falcon Electronics Co., 2003 Cedar St., Quincy, Ill.)




Antenna designed for uhf and constructed on colateral design. Model illustrated is a 4-bay unit. Has a snap-out type screen reflector. Extremely narrow patterns and a high front-to-back ratio are claimed to be features engineered to solve ghost problems due to multiple signals. Variations of setups designed to peak on channels 14 to 32; 29 to 55; 53 to 83. (Model 504; Finney Co., 4612 St. Clair Ave., Cleveland 3, O.)

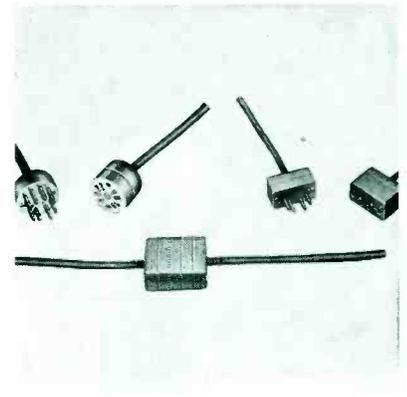

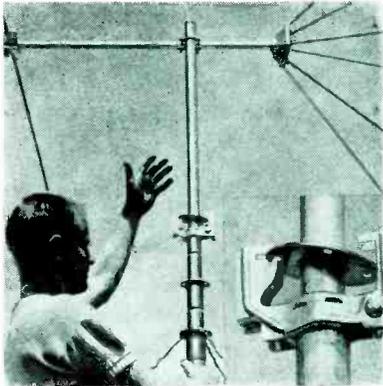
Series of plugs and sockets for connecting 4, 5 and 8-wire rotator cables. Connectors are molded of polystyrene, have phosphor bronze contact strips, and are solderless. Plug pins are plated brass. Base sockets may be mounted on wood or metal. Connectors are designed for either flat or round multi-wire cable. (Mosley Electronics, Inc., 8622 St. Charles, St. Louis 14, Mo.)



Antenna mast, featuring safety device called the third hand, which is said to permit one-hand extension. Major feature of this mast is an automatic, removable locking device that holds mast sections up when one lets go. Another feature is a step-up key, a metal stamping that permits mast indexing; key automatically extends each mast section for elevation. (Strato-Matic lines, series 16 (16-gauge hot dipped galvanized); and series 18 (18-gauge; electroplated with coating of bright zinc); Channel Master Corp., Ellenville, N. Y.)

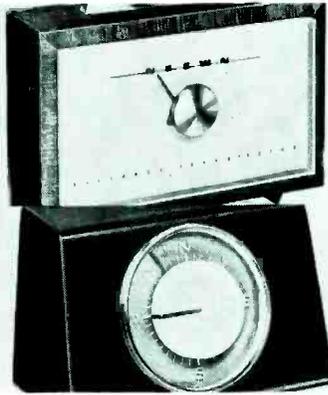


Antenna rotators, designed for manual and automatic operation. Model at bottom is fully automatic, which supplies fully automatic rotation to any pre-selected stop position. The control case for model above is manually operated with control bar across the top of case. Other improvements include faster rotation; new magnetic brake; and guy wire attachment on clamp plate. (Model U-83—fully automatic, and Model T-10—manually operated; Alliance Manufacturing Co., Alliance, O.)

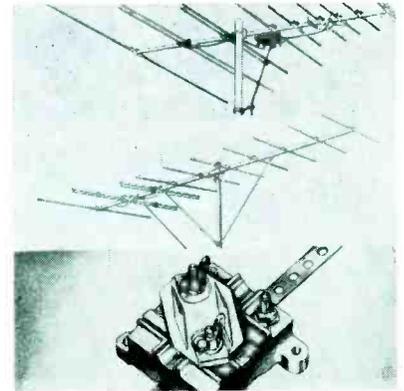


Top: Hi-low yagi phased together with printed circuit isolation filter. There are five elements for high channel reception and four elements for low. Center: broad-band yagi available in both 10- and 5-element models. The 10-element antennas are available for Channels 2, 3, 4, 5 and 6; 4, 5 and 6; and 7 through 13. Bottom: Universal lightning arrester, believed to be the first hermetically sealed model with completely encased electrodes. Unit will accommodate flat, tubular, oval, round and open wire lines. (Vee-D-X models; LaPointe Electronics, Inc., Rockville, Conn.)

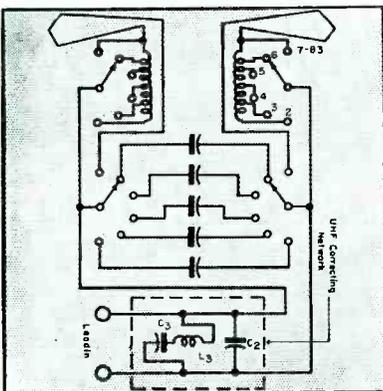Schematic of switched-tuned uhf-vhf indoor antenna. C₃, a 1-mmfd capacitor, serves to correct for mismatch at uhf caused by selector switch. It is placed 1" from switch terminals and a series-resonant circuit (C₂, L₂) resonant at 400 mc, which is shunted across the lead 7" from C₂. (Model 600; Tricraft Products Co., Chicago 22, Ill.)



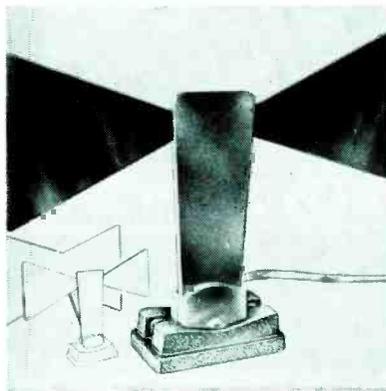Indoor uhf bowtie, with bowtie elements of high-tempered aluminum. Stands about 8 1/2" high in a metal base which it is said cannot be tipped over. In critical areas, gain of the unit, it is claimed, can be doubled by the addition of a reflector, which plugs into fitting at back of the antenna. (Model IBT-500; Radio Merchandise Sales, Inc., 2016 Bronxdale Ave., N. Y. 62.)



TV antenna designed for trailer installation. When traveling, antenna anchors to a position 2" above the roof, mounted on a telescopic pole. When the trailer is parked, antenna can be raised for reception. (Trailer Tenna; Clear Beam, Inc., Burbank, Calif.)



No dust-catchers in Merit's line




but complete coverage where it counts!

Keep inventory at a minimum, profits high with Merit's designed-for-action line. Among the new, quick-turnover items recently added: flybacks for Motorola replacement, a new series of yokes and TV power transformers. Find Merit's complete line listed in John Rider's Tek-File and Howard Sam's Counter Facts and Photo Facts—Tape Marked* to help you.



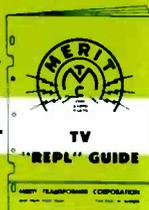And! Be sure to get Merit's new, really complete Replacement Guide. Forty pages of replacement data and schematics, including IF-RF coils, an exclusive Merit feature.



*originated by Merit

Merit Coil and Transformer Corporation
 4425 NORTH CLARK STREET, CHICAGO 40, ILLINOIS

SILVER ANNIVERSARY



Henry T. Paiste, Jr. (left), vice president of Philco in charge of product performance and service, receiving congratulations from Philco's general service manager, Russell M. Oliver, and a sterling silver bowl commemorating Paiste's 25 years with Philco, presented by Philco's TV and appliance distributor service managers. Inscription on the silver bowl read: "To Uncle Henry, 'Mr. Service, himself,' on his 25th Philco anniversary . . . our heartfelt thanks for making Service a profession."

O'LEARY ADVERTISING NOW G-C AGENCY

O'Leary Advertising, Rockford, Ill., has been appointed by *General Cement Mfg. Co.* to handle ad programs for General Cement and its subsidiaries, Television Hardware, Gee-Lar, and Wood Specialty. *Richard Long* is account executive.

* * *

V-M WINDOW DISPLAY CONTEST

A window display contest, featuring V-M phono and record players, has been announced by *V-M Corp.*, Benton Harbor, Mich.

Both distributor salesmen and retailers will be winners in this contest. First four winning retailers will receive \$100, \$75, \$50 and \$25, respectively. A panel of judges will select the four winning displays from photographs or snapshots submitted by contestants. Distributor salesman within each V-M rep's territory, responsible for the greatest number of window displays in the territory, will receive \$100 as an award.

* * *

VHF BOOSTER COUNTER DISPLAY



Counter display rack now in use by jobbers to feature the Regency vhf booster. Rack was created by *Burton Browne Advertising*.

NEWS

BURGESS BATTERY ENGINEERS GRANTED PATENTS

J. J. Coleman and *Milton E. Wilke*, *Burgess Battery Co.*, Freeport, Ill., have been granted two patents on cell construction developments in deferred-action type batteries.

Batteries of the deferred action type, that are energized or activated by contact with liquids, are said to tend to short circuit because of a local action caused by the activation liquid going into the cells and remaining on the cell surfaces which results in the forming of a bridge between adjoining cells. New-type construction invented by the Burgess engineers is claimed to eliminate substantially local action and short circuits.

* * *

K-G ELECTRONICS MOVES

To provide additional space and facilities, *K-G Electronic Corp.* has moved factory and offices to a new building at 2738 N. Sheffield Ave., Chicago, Ill.



New K-G Electronic Corp. Building

* * *

YESTERYEAR AND TODAY



The oldest and newest pieces of equipment in plant of the *Mueller Electric Co.*, Cleveland. In the early days the push cart shown was navigated daily several blocks through down-town Cleveland carrying packages to the post office. The pusher was *Al Flynn*. A truck to carry parcel-post has replaced the push cart for outdoor use, but it is still serviceable and affectionately known as the *Cadillac*; each year it is fitted with a new set of discarded auto license plates. Today, *Al Flynn* is *Mueller's* superintendent and he is concerned with the operation of many huge machines, one of which is shown above; it is an injection machine for the molding of vinylite insulators. Machine stands about 10' high and weighs nine tons. Four electric heating zones plus 20,000 pounds per square inch pressure plasticize the vinylite and cause it to flow into the molds. With a ten-cavity mold and amolding cycle of about 41 seconds, it can produce over 5,000 medium-sized insulators per day.

NEW PARTS SHOW OFFICERS



Harry A. Ehle, *IRC*, newly elected president of the *Radio Parts & Electronic Equipment Shows, Inc.* (second from left), being congratulated by (left) *Francis F. Florsheim*, *Columbia Wire*, new secretary; and (right), *Bernard L. Cahn*, *Insuline Corp. of America, Inc.*, who will serve as treasurer.

EICO DECAL

Three-color decals that can be attached to windows or vehicles are available from *Electronic Instrument Co., Inc.*, 84 Withers St., Brooklyn 11, N. Y.

* * *

NAME CHANGE

The *Grayburne Corp.*, 4-6 Radford Place, Yonkers, N. Y., has officially changed its name to *Rayburne*.

* * *

NEW GUY WIRE TRADE NAME

Guy Wire, manufactured by *Fenton Co.*, is now being marketed under the new tradename, *Tuf-Guy*.


* * *

TRANSVISION TO CUSTOM-BUILD COILS

A special transformer and coil manufacturing division, devoted to the design, engineering, and manufacture of coils, such as *hf* air core, multi-layer solenoids, peaking, synchro winding, and *TV rf, if*, and transformers for audio, power, high voltage and pulse application, has been set up by *Transvision, Inc.*, New Rochelle, N. Y.

* * *

PHALO PRODUCT DISPLAY

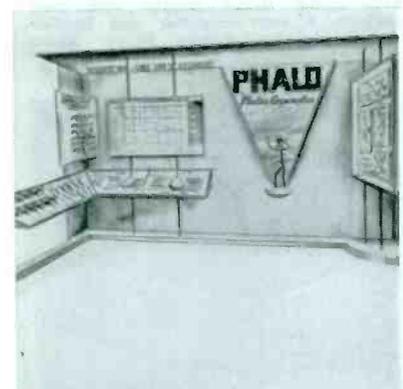

Product exhibit designed to feature special *Phalo* harness assemblies, wires, cables, etc. Display also features a blowup of the product application chart which is a part of the 46-page catalog recently completed.


On View at Audio Fairs in San Francisco, Philadelphia, Chicago, and




Right: A huge four-speaker assembly. Left: small apartment size speaker system which measures 11" x 10" x 2 3/4". Small unit features use of 8" speaker unit, tuned acoustic element enclosed case, and a multielement compression hf driver. (Small model is known as Duette; Jensen Manufacturing Co., 6601 South Laramie Ave., Chicago 38, Illinois.)




Single-speed tape recorder (7.5 ips), featuring a rear illuminated vu meter which provides level indication in both record and playback positions. Has separate preamp gain control and inputs for microphone and radio-phono. Output 600 ohms; cathode follower. Power output 2 watts (4 1/2 peak). Can be used vertically or horizontally. (Model HF-500; TapeMaster, Inc., 13 W. Hubbard St., Chicago 10, Ill.)

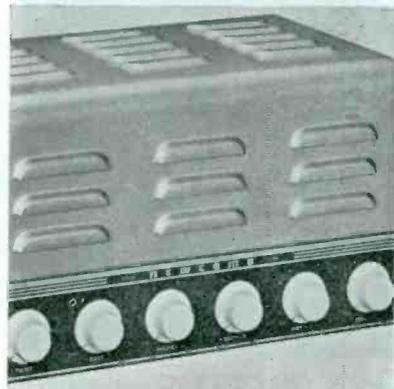

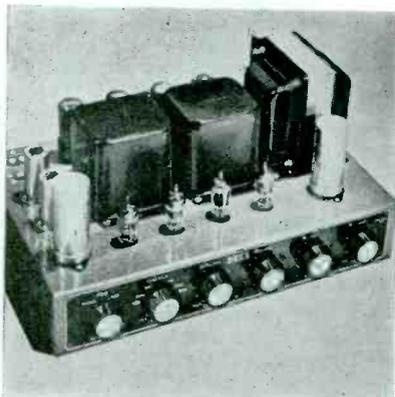
A 25-watt amplifier with four-channel mixer, three mike inputs and a phono input. Socket knockout and input contacts provided to expedite conversion to low impedance mike inputs. Individual tone controls for bass and treble. Multi-stage inverse feedback. Said to employ cellulose-acetate-insulated output transformer. (E-254; Newcomb Audio Products Co., 6824 Lexington Ave., Hollywood 38, Calif.)



Binaural amplifier which includes three dual sets of inputs; dual flat inputs for radio and tape, and a pair of dual inputs for phono records (for use of either high or low magnetic pickups). Unit also has six-position function switch to select binaural, monaural, or reverse binaural either with or without loudness control. Power output: 20 watts (10 watts each channel). Dual output impedance: 4, 8, 16 ohms plus dual hi-Z for tape recorders. Tubes: two 12AY7s; two 12AT7s; two 12AX7s; four 6V6GTs; and one 5U4G. (Bell Sound Systems, Inc., Columbus 7, O.)

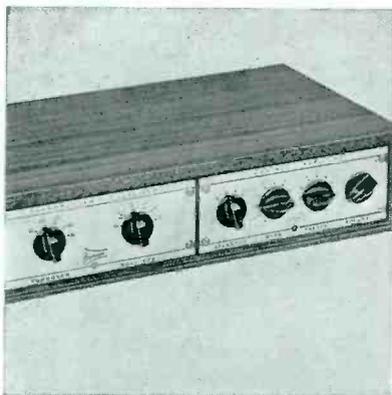


Audio control center, which consists of a phono preamp-equalizer, with separate turnover and roll-off controls, and control amplifier which provides input selector switch, bass boost and cut control, treble cutoff and boost control, and volume control. Features of the units are step switch controls for permanent calibration; universal pickup compensation; adjustable treble cutoff filter; maximum of 28 db bass boost; adjustable loudness control; low impedance output; tape recorder takeoff jack; and negative feedback. (Model A100-CA2; Brociner Electronics Lab., 344 E. 32 St., N. Y. 16.)

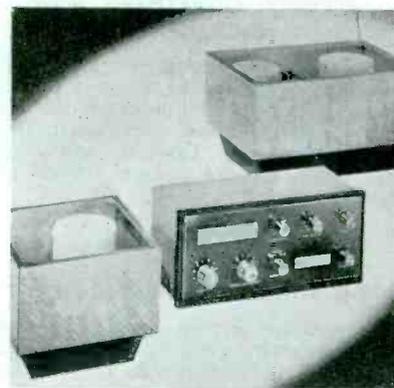


Audio ensemble which consists of three separate units: a preamp-equalizer, power amplifier and power supply. All units are claimed to be non-hygroscopic, providing protection against adverse effects of moisture. Each unit is also said to feature individual calibration and each has an individual response curve. Has a variable crossover compensator. One low and two high-impedance inputs are provided; each with a continuously variable level compensator. Also has a continuous variable loudness control and a six position crossover selector for adjustment to various recording characteristics. (Model 1000; Regency Division (IDEA), 7900 Pendleton Pike, Indianapolis 26, Ind.)


Table model record player with dual speakers, 6 watt amplifier and English 3-speed changer. (Model HF-90; Video Corp. of America.)

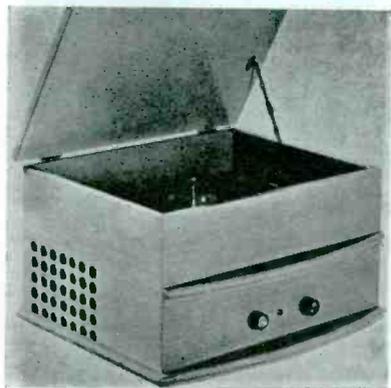

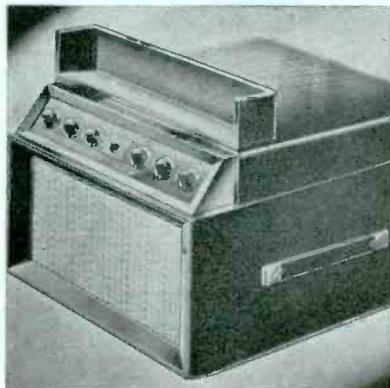Tape recorder which, it is said, can play for 16 consecutive hours. (Lion Manufacturing Corp., 2640 West Belmont Ave., Chicago, Ill.)



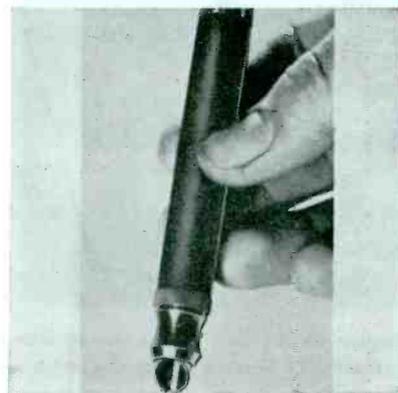A 50 power wide-angle hand microscope for checking phono needles while in cartridge. (Duotone; Keyport, N. J.)



New York † . . . Troubleshooting Hum in Audio Amplifiers* . . .

HUM has always been a particularly provoking problem in the audio system. Frequently it can be tracked down to the input circuit.

If shorting the grid of the input tube, or turning off the gain control, eliminates the hum, it is obviously coming from some element associated with the input stage. But that only represents a partial diagnosis. There are many ways in which hum can break into the input circuits.

Hum can be induced into different parts of the circuit electrically, magnetically, or electromagnetically. Electrically-induced hum is characterized by its appearance in a high-impedance circuit; hence this is sometimes called an open circuit hum. It is audibly different from other types in that it contains a dominance of higher harmonics, causing it to sound ticky or tizzy. The other forms of induction give rise to a deeper note; almost pure 60 or 120 cps.

To trace hum, the input tube circuit should be checked initially: The input circuit should be disconnected from the grid, and a grid return, in the form of a simple resistor, provided with the shortest possible leads; its value should be the same as the input circuit impedance at the grid, and it should be placed inside of whatever screening is provided for the input stage. If the hum still persists, but disappears when the grid return is shorted, the hum must be in the tube.

If the tube is of the straight heater construction type, probably it is radiating sufficient field to be picked up on the grid, as soon as any impedance at all is inserted in its return. The spiral heater type tube intended to be hum-free, should not introduce noticeable hum; occasionally tubes of this type have been found to cause hum, due to magnetization of some part of the electrode assembly. A permanent magnetic field is produced in the electron path, so that the small residual portions of *ac* field from the heater,



by **KENNETH STEWART**
and **PAUL EDWARDS**

which would normally cancel out, form a pattern (interacting with the grid structure) to produce a hum. Demagnetizing will cure this; a demagnetizer similar to that used for demagnetizing clocks and watches should be used.

Having cleared the tube, any hum now picked up must emanate from somewhere in the input circuits. It may be magnetically induced in the transformer core. In this case, shorting either primary or secondary will stop the hum; changing the position of the transformer will alter the hum, but this may not be easy to do. Shorting the windings can also stop hums due to other causes. If, however, the hum is of the deep variety (which means it is of the magnetic or electromagnetic type), stoppage when the primary is shorted offers fairly conclusive evidence that the trouble stems from the transformer core, because shorting the input side increases electromagnetic effects when the actual input is disconnected. One can try reorienting the transformer, taking

care to keep the case grounded while making the change. If altering the position varies the hum, a component with better shielding is required.

Open-Circuit Type Hum

If the hum is of the open-circuit type, and the tube has been cleared, the problem is most likely a pick-up type, coming from either the secondary, because the wiring to the grid is not sufficiently screened, or by capacitance transfer from primary to secondary of the input transformer. Connection of one side of the primary to the cold end of the secondary will eliminate the latter possibility. If any hum remains, the hot lead from the transformer case should be screened to the grid, and the screening returned to the cold end of the transformer secondary.

If the hum is due to capacitance transfer between windings, and connection between primary and secondary is not possible as on *ac/dc* chassis, a special screened transformer, or
(Continued on page 88)

†See detailed reports on new audio developments and equipment displayed at Fairs on pages 30, 36, 38, 42, and 107.

*From notes prepared by Norman Crowhurst, British audio consultant.

Fig. 1. Minimizing hum through use of twin screened lead.


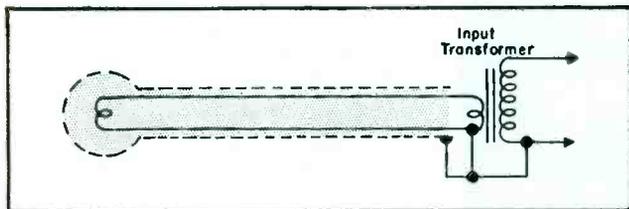


Fig. 2. Balancing or screening input leads at line impedance (500 or 600 ohms) to eliminate hum pickup.

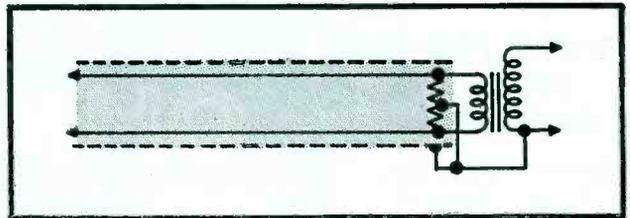

To PROVIDE adequate deflection voltage for the larger picture tubes, such as the 27MP4, which have horizontal-deflection angles of about 85° and diagonal-deflection angles of about 90°, a horizontal-deflection circuit, with a deflecting yoke,² designed to provide the good corner resolution, desirable with large rectangular tubes, is necessary. Such a circuit is illustrated in Fig. 1. It employs a ferrite-core¹ transformer and two ferrite-core coils for linearity and width control. The width control has an inductance range of approximately 3.9 to 22 millihenries. The approximate inductance range of the linearity control² is 1.5 to 8.3 millihenries.

Suppression Capacitor Values


A capacitor, whose value may range from 75 to 200 mmfd, and is connected between terminals 3 and 5 of the horizontal-deflection output/hv transformer affects the natural period of the entire circuit and at the same time aids in suppressing undesirable ripple and interference effects. The specific value of this capacitor must be chosen to provide a retrace pulse having a duration and shape which gives best performance, particularly with respect to scanning amplitude and high-voltage output. When this system is used with picture tubes having slightly different deflection angles, the capacitor must be adjusted to provide the correct ratio of scanning amplitude to high voltage for each tube used. The required value of this capacitor has been found to be affected by the capacitance to ground of the 6W4GT heater winding and the length of the deflecting-yoke leads; thus its exact value is usually determined by trial during development work because the physical arrangement of the parts in the system affects the natural period.

HD Circuit Drivers

The horizontal-deflection circuit may be driven with either a blocking or a multivibrator-type oscillator. Both drive circuits utilize automatic frequency control for better noise immunity and work equally well. Keyed *agc* pulses can be obtained from terminals 3, T, 4, 5, or 7 of the transformer, depending upon the magnitude of the desired positive voltage pulse.

Vertical Deflection

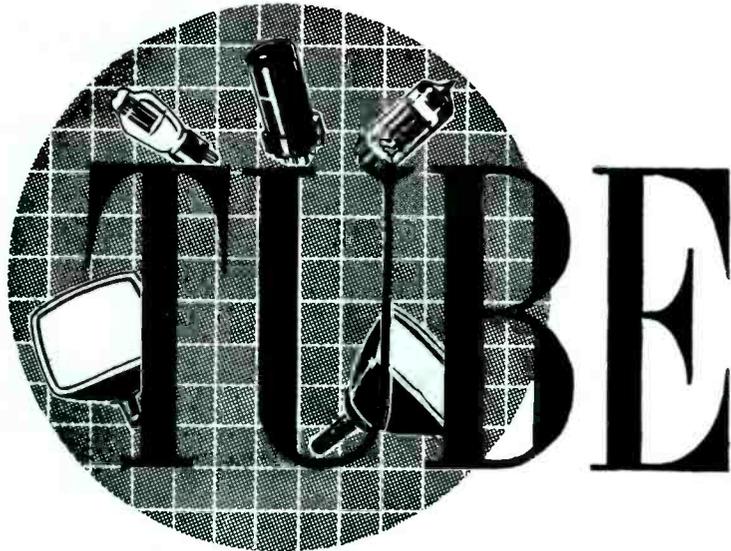The *hd/hv* circuit is used with a vertical-deflection circuit (of the type shown in Fig. 2, which utilizes one triode-connected 6W6GT operating



News — by E. A. TEVERSON

Horizontal Deflection and HV Circuits for 27-Inch Picture Tubes* . . . Miniatures and Subminiatures for 12-V Auto, and Mobile and Aircraft Receivers

directly from the B- supply with a current drain of approximately 28 ma. A 500-ohm resistor is used between plate and grid 2 to prevent parasitic oscillations. Operation directly from the B- supply permits the use of a lower system B- voltage than would be required if vertical deflection were obtained from the boosted B- supply.

Boosted B Supply

The vertical-deflection circuit can also be operated from the boosted B- supply in a circuit in which a single 6S4 and a vertical output transformer having a turns ratio of 18:1 are used. In this case, the design-center B- supply voltage must be increased from 265 to 285 volts, and a second damper diode used to handle the increased current which flows in the damper circuit as a result of the load on the boosted B- supply. The cathode of the damper tube must also be connected to terminal 5 instead of terminal 7 of the horizontal output transformer to preserve good horizontal linearity. With this arrangement, the

boosted B- supply drain will be approximately 14 ma.

Lead Dress

As noted in earlier *hd* analyses, special attention must be given to wiring techniques utilized with horizontal-deflection and high-voltage circuits to minimize stray capacitance and prevent corona or arc-overs. It is particularly important to dress the 1B3GT plate lead away from other leads and the chassis. Other leads having rela-

Sticker placed on G.E. replacement picture tubes and their cartons to discourage the home handyman from tampering with his set, and also to call attention to the experienced technical service available from his Service Man.



*Based on copyrighted application notes prepared by the tube department of RCA.

¹RCA 235T1. ²RCA 219D1. ³RCA 213R1.

tively high pulse voltages are: 6CD6G plate lead, 6W4GT cathode lead, and leads to transformer terminals 3, T, 4, and 5.

Adjustments

Correct adjustment of the *drive* control is important for proper circuit performance. The drive should first be increased until a white vertical bar appears near the center of the raster, and then be decreased until this bar just disappears. The linearity control should then be adjusted for best linearity. Because minimum cathode current in the 6CD6G occurs in this circuit very near the optimum setting of the linearity control, a preliminary adjustment of linearity may be made by setting the linearity control for minimum voltage across the 6CD6G cathode resistor. The adjustment of drive is somewhat dependent upon the linearity adjustment and must be rechecked after other adjustments are completed.

New Tube Developments

A beam power amplifier⁴ of the 7-pin miniature type, intended primarily for use in the output amplifier of auto radio receivers operating from a 12-volt storage battery, has been announced. Within its maximum ratings, the tube, a 12AQ5, is the performance equivalent of the larger glass-octal type 12V 6GT.

High Power Output

The tube features the application of directed electron beam principles, which it is claimed, makes it capable of producing relatively high power output with high power sensitivity. For example, it is said, a single 12AQ5 operated with a plate and screen voltage of 250 volts can deliver a maximum-signal power output of 4.5 watts with a peak driving voltage of only about 12 volts.

Subminiature Tubes

Also announced for mobile and aircraft receivers is a *premium high-mu* triode⁵ of the subminiature type for use primarily as an audio amplifier where dependable performance under shock and vibration is a prime consideration.

Featured in this tube, type 5719, is a pure-tungsten heater designed to give long life under conditions of frequent *on-off* switching.

⁴RCA 12AQ5. ⁵RCA 5719.


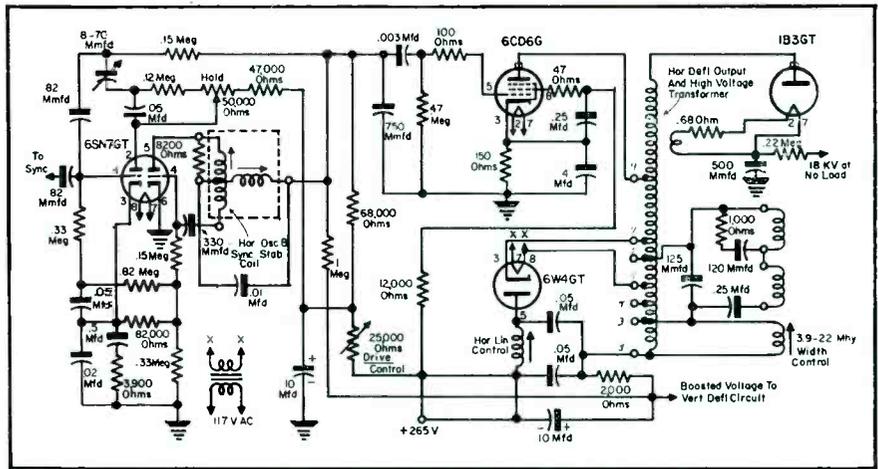


Fig. 1. Horizontal-deflection and hv circuit developed for large-screen picture tubes. System, operating in conjunction with vertical-deflection circuit using a 6W6GT vertical output tube, operates from a 265-v B supply and provides an output of 18 kv.


Fig. 2. Vertical deflection system, which uses a triode-connected 6W6GT, and operates directly from B-supply. Circuit also can be operated from a boosted B-supply, in which instance a 6S4 and a vertical output transformer, having a turns ratio of 18:1, are used.

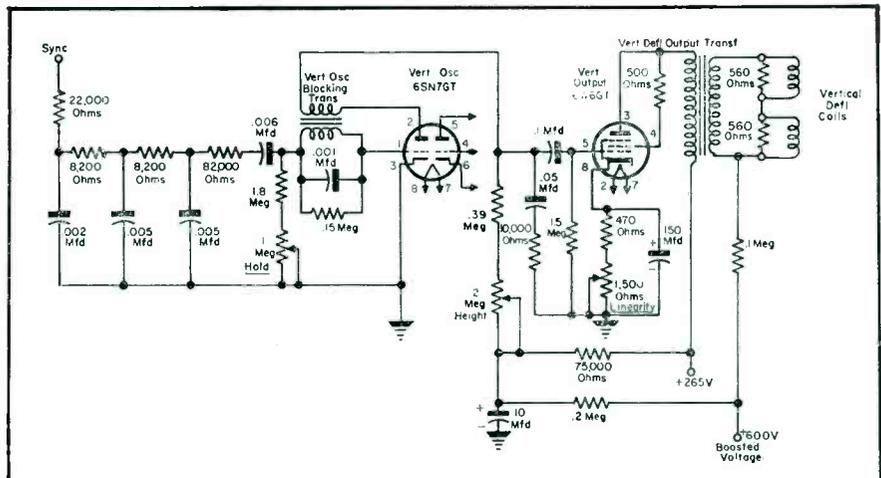

(Below)

Fig. 3. Medium-mu 6BQ7A twin triode in a driven *rf*-grounded grid amplifier circuit with direct-coupled drive. Tube, a 9-pin miniature type, can be used in a first *rf* amplifier in tuners of *vhf* television receivers or as a low noise *if* preamp in *uhf* television receivers employing a crystal mixer. Tube has high transconductance, low input capacitance, low input loading and low plate-to-cathode capacitance. These features make the tube especially useful in direct-coupled *rf* stage of TV receivers utilizing a driven *rf*-grounded-grid amplifier circuit such as the one shown or the cascade type of circuit. The two triode units of the 6BQ7A are shielded from each other. A = tuned circuit element of tuner; value depends on distributed circuit capacitances. B = tuned circuit element of tuner; value also depends on distributed circuit capacitances. C = bifilar chokes, each 10 turns, No. 18 enamel wire on 1/4" coil form.

(Courtesy RCA)

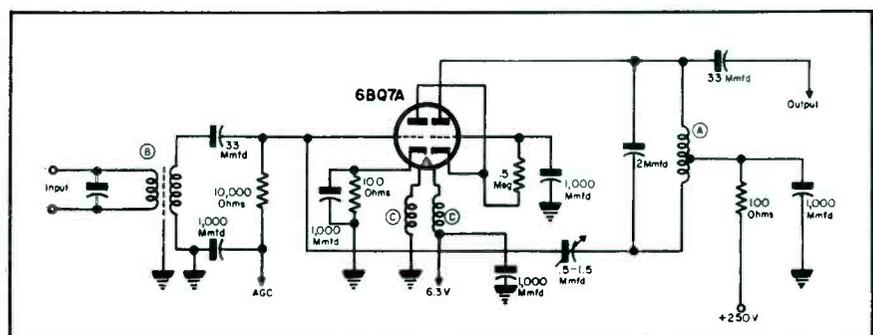

FACTS YOU SHOULD KNOW ABOUT UHF CONVERTERS

Many converters on the market today are unsatisfactory in fringe and shadow areas where signal strength is low. Before you install a UHF converter in these areas you should know these facts:

- 1** Signal power loss in the preselector seriously affects picture quality. Most UHF converters use sliding-contact shorted line tuners in the preselector with a fixed power loss of 6 db. The Turner converter uses High Q coaxial cavity tuners with no sliding contacts. Signal power loss is cut to 3 db. The resulting low noise figure keeps picture quality high.
- 2** Oscillator radiation often causes disturbing interference with neighboring sets. In the Turner converter the oscillator tube socket and all associated circuits are inside the coaxial cavity, self-shielded. Removable covers provide a second shield against radiation.
- 3** High amplifier noise figure can further damage picture quality. The Turner converter uses a special broadband amplifier with Cascode circuit. It retains the preselector signal savings without appreciably increasing the noise figure. The Turner amplifier noise figure is only 4 db.

Whether you're selling converters for installations in shadow or fringe areas or putting one in your own home, remember . . . the Turner converter often means the difference between good reception and bad.

EXCLUSIVE TURNER FEATURES

- Higher sensitivity
- Extremely low noise figure
- Exceptional frequency stability
- Double shielding
- Hi-Q silver plated coaxial cavities
- No sliding contacts

OTHER MAJOR TURNER FEATURES

Continuous single-knob tuning. Illuminated slide-rule dial. Smaller size: 8"x6"x6". Use with UHF or combination antennas. Self powered, uses channels 5 or 6. Complete installation instructions for 110-120 volts 50-60 cycles AC. Schematic included.



List price \$49.50

In VHF fringe and shadow areas, the Turner Booster is a superior performer, too.

THE TURNER COMPANY

930 17th St., N.E., Cedar Rapids, Iowa
 Export: Ad Auriema, Inc.,
 89 Broad St., New York 4, N. Y.
 Canada: Canadian Marconi Co.,
 Toronto, Ont. & Branches

Service Engineering

(Continued from page 77)

test is to replace a suspected tube with one known to be good.

Vibrators should be checked with a 'scope to locate worn contacts. Replacement vibrators should be installed with the same polarity, or orientation, as on the defective item.

Sealed bearings are utilized on the dynamotor, and no periodic lubrication is required. Occasional checks should be made, however, for evidence of excessive brush sparking, pitted commutator surface, or worn brushes, all indicative of need for servicing.

To insure adequate voltage at all times, the battery and generator must be maintained in good operating condition. The battery water level must be kept at the proper height, and the generator output adjusted for the load conditions on the battery.

Faults and Checks

When there is no background noise, the squelch setting should be checked. If there is excessive background noise, antenna connections, ignition and vibrator supply filter should be inspected for faulty operation. In noisy or intermittent conditions, the squelch circuit, loose tubes or wiring, and the vibrator may be the source of the trouble. Weak or fading signals may be caused by tubes, battery or the terrain.

During transmission, low-output may be due to the battery or the *pa* plate tuning and grid drive. When poor modulation exists, the microphone, input transformer or the modulation control may be causing the trouble.

2-Way System Design

THE RECEIVING circuit of some 2-way FM communication systems, such as the RCA CMV-3E1², employs a 6BH6 in a Pierce type crystal-oscillator. The two heterodyning frequencies are derived from the oscillator stage; the sixth harmonic being used in the first 6BH6 mixer, and the crystal fundamental in the second 6BH6 mixer. Frequencies in each stage vary; the crystal fundamental ranges from 4.155 to 7.012 mc.

Incoming signals are fed through the contacts of a transfer relay to the 6BH6 *rf* stage. Automatic gain control is incorporated in this stage through grid bias obtained from the 6BH6 first limiter. In the 6BH6 first mixer, the output of the *rf* stage is heterodyned with the sixth crystal harmonic (24.93 to 43.07 mc). The

HICKOK
Model 665

TELEVISION
5" 'SCOPE
with

- Frequency: 0.5 cycles to 700 KC.
- Push-Pull Amplifier
- Sensitivity: 20 M.V. per inch.
- Excellent Square Wave Response.
- Stable, dependable, built-in trace.
- Write for technical details . . .

THE HICKOK ELECTRICAL INSTRUMENT CO.
10521 DUPONT AVE., CLEVELAND 8, O.

difference frequency is amplified in a 6BH6 first *if* amp, and then heterodyned with the crystal fundamental in the 6BH6 second mixer. Frequencies in the second mixer include the high *if* 5.07 to 7.93 mc, and the crystal frequency, 4.155 to 7.012 mc. Output of the second mixer is the low *if*, whose center frequency is 915 kc.

Two 6BH6 low-*if* stages, and two 6BH6 limiters are utilized before the signal reaches the 6AL5 discriminator tube.

A squelch and noise-amplifier circuit is used to control squelch action in the first *af* stage, elements 6-7-8 of a 12AX7. These elements are used as a noise amplifier, grid 7 being connected to the output of the discriminator. After amplification the noise is rectified in the other half of the duotriode, the grid and plate of this half of the tube being connected together.

In the squelch control section, elements 1-2-3 of the 12AX7 receive the positive output of the noise rectifier. The positive cathode bias on pin 3 permits plate-current flow during no-signal periods, causing a decrease in the potential on grid 7 to a value less

²For schematic, see p. 57, SERVICE; June, 1953.

than the positive bias on cathode 8. Under this condition the first *af* section, elements 6-7-8, are biased to cut-off, and the receiver silenced during absence of a signal.

When a signal is received, the squelch circuit becomes non-conductive by reduction of the noise-produced bias on pin 2 of the 12AX7. Resultant rise in voltage on plate 1 and, consequently, on grid 7 will permit the first *af* stage to function and pass audio signals.

Plate Voltage Supplies

High voltage for this system is derived from two sources: a vibrator supply and a dynamotor. The vibrator circuit uses a self-rectifying vibrator, to supply plate voltage for the receiver and for all but the last two *rf* stages in the transmitter. This circuit operates continuously while the equipment is on. In the *standby* position, the vibrator supplies plate voltage to the entire receiver, and to the oscillator, modulator, and audio amplifier tubes in the transmitter. During transmission, plate voltage is switched by a relay from the receiver to the first and second tripler, and the screen grid of the oscillator tube in the transmitter. Only the squelch and 12AX7 first *af* tube remain energized during transmission, to insure instantaneous squelch action when the push-to-talk button is released.

Hi-Fi Audio

(Continued from page 39)


working back from the output tubes until a point is found where stimulation of the next grid farther back does not create an increase hum, or does not induce any hum at all. The trouble will be between the no-response grid and the last point from which normal response was obtained.

There are certain procedures that are especially important in high-quality amplifier service. If there is even a suspicion of distortion, the bias voltage on the output tubes should be measured and checked against the manufacturer's specifications or against tube manual data. A leaky or shorted cathode bypass, or leaky coupling capacitors, can change the bias so that the output stage no longer operates properly. Fig. 1 (p. 38) illustrates how a seemingly insignificant *dc* leakage resistance of 5 megohms in a coupling capacitor can place a positive potential of 11 volts on the following grid. The plate voltage is applied to a voltage

(Continued on page 82)

GUARANTEED!

to outperform all others

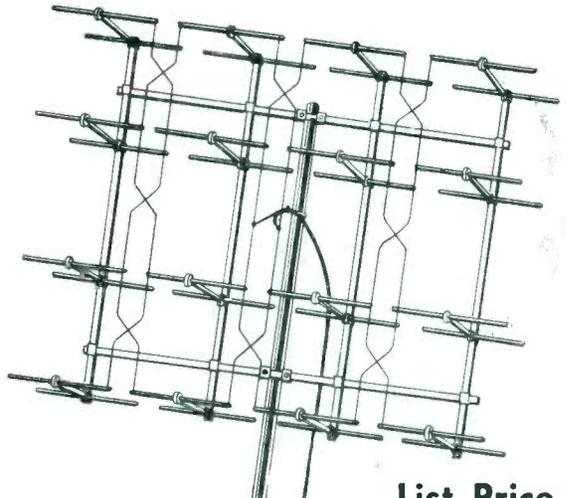

Tel-a-Ray

800 D-A

UHF

List Price
\$ 31.90

Super Fringe Master

ANTENNA

A Broad Band cut to channel, Colinear Antenna - covers 10 and more channels on each side of cut channel

Testimonials have been received to verify perfect reception up to 60 miles and more from station.

PROVIN UNSURPASSED . . . in Little Rock, Ft. Smith, West Palm Beach, Muncie, Dayton, Henderson, Handford, Cal. and all other new UHF areas.

ELIMINATES . . . the most difficult fringe problems — brings in PERFECT reception where picture is snowy with other antennas . . . eliminates ghosts . . . has high front to back ratio, very sharp directivity and very low noise level.

COMPLETELY ASSEMBLED . . . READY TO MOUNT ON MAST.

Take this coupon to your Tel-A-Ray Distributor and get your Sample Super Fringe Master on this money back guarantee today!
If you do not have a Tel-A-Ray Distributor in your area, mail the coupon direct to Tel-A-Ray Enterprises, Box 332, Henderson, Ky.

Please rush me one (1) Stacked Array UHF Super Fringe Master cut to channel Via Railway Express Prepaid today. I understand that if this antenna does not out perform all other UHF antennas I may return it within 15 days Freight Collect and my money will be refunded or bill cancelled.

Name..... Firm.....
Street Address.....City..... State.....
I am a.....Distributor.....Dealer.....Consumer

Bill me Ship C. O. D. I am enclosing check

NEW! ANACONDA UHF FOAM POLYETHYLENE

Transmission Line



- No Moisture Problems!
- No Termination Problems!
- Extremely Lightweight!
- Low Attenuation!

Has all-channel reception for both **UHF and VHF**

High strength 22 Ga. solid conductors firmly enclosed and accurately spaced in foamed polyethylene. No danger of impedance changes due to crushing of cable. Uni-cellular construction provides all the advantages of an air dielectric so necessary for UHF in a strong, solid type cable. Ideal for use in coastal areas where salt air deteriorates ordinary transmission lines. Installs as easily as flat television line.

NOTE: A special wire stripper and a UL lightning arrester for this foam cable will soon be available.

Write for Samples and New Descriptive Literature. Sold through recognized jobbers only!

"National distributors and warehouse for ANACONDA denshath television and radio wires and cables"

Columbia
WIRE & SUPPLY CO.
2850 Irving Park Road - Chicago 18, Ill.

Hi-Fi Audio

(Continued from page 81)


divider consisting of the coupling capacitor leakage resistance as upper arm, and the grid resistor as lower arm. A *vtom* must be used to detect the voltage across the grid resistor.

Push-Pull Balance

Another possible cause of increased distortion is lack of balance between the two halves of the push-pull stage, an unbalance which can be created by aging or defective tubes, or circuit components. Where the amplifier does not provide facilities for adjusting push-pull balance, good results have often been obtained simply by changing tubes until a matching pair have been found. One rough indication of the balance of the output stage is in the degree of hum cancellation. With the phase inverter tube removed, various combinations of output tubes should be tried until the quietest pair have been selected.

Figs. 2 and 3 (p. 38) illustrate methods of checking push-pull balance more accurately. Zero or close to zero *dc* voltage (with no signal present) across the whole of the output transformer primary indicates good *dc* balance. To check dynamic or signal balance, a test signal should be applied to the amplifier input—the 400-cycle audio output of the standard signal generator may be used—and the *ac* voltages across each half of the output transformer primary compared. These two signal voltages, referred to the center tap, are opposite in phase, but should be substantially equal in magnitude.

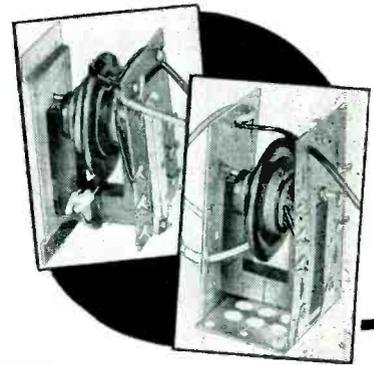Another method for checking push-pull balance is shown in Fig. 4 (p. 38). This method has been suggested by *D. T. Williamson* (designer of the well-known amplifier circuit bearing his name), and does not require any test



FLYBACKS

- **FRANKLIN** is your dependable source for a complete line of replacements in Flyback Transformers—for all makes of TV Sets.
- **SERVICEMEN:** For complete satisfaction, ask your local jobber for FRANKLIN Flybacks. If he does not handle our line, please write us and we will give you the name of a distributor in your locality who stocks our Flybacks.

FRANKLIN

TELEVISION LABORATORIES, INC.

"Coils of Quality"



18 JOHNSON AVENUE
BROOKLYN 6, N. Y.

Now Ready! New Sprayberry Book!
"HOW TO CONVERT TV SETS
for LARGER PICTURE TUBES"



Covers Step-by-Step Method for Converting any TV Receiver

This new book opens exceptional extra money opportunity for the alert serviceman . . . converting older small screen TV sets to modern, large screen 17", 21" or 24" receivers. Fully illustrated with diagrams, charts and pictures. Covers every step: planning, wiring, final adjustment. Special introductory price . . . 50¢ Mail coin (no stamps, please) today.

SEND ONLY
50¢

SPRAYBERRY ACADEMY OF RADIO
111 N. CANAL STREET, Dept. 6-B
CHICAGO 6, ILLINOIS

MOSLEY

ROTATOR CONNECTORS

- Models for EVERY Rotator!
- Line Plugs—Line Sockets—Base Sockets—Flush Mounted Sockets!
- Solderless!
- Precision Molded Polystyrene!



Available at Radio & Television Parts Distributors — everywhere

WRITE FOR FOLDER 1002:



MOSLEY Electronics, Inc.

8622 St. Charles Rock Road

St. Louis 14, Missouri

instruments at all, except for some sort of device for detecting *ac* which can be a simple pair of headphones. It does require, however, that the *B+* lead to the output transformer be unsoldered.

The signals from the two halves of the push-pull output stage combine in-phase across the whole of the output transformer, but they combine out-of-phase when they enter the common *B+* line. Good signal balance can therefore be indicated by zero or at least minimum signal across the secondary of *T_{out}* (an inexpensive output transformer of any standard design), while the amplifier is carrying either a test signal or normal program material. The greater the signal input to the amplifier, the more rigorous the test.

Amplifier Oscillation

One amplifier trouble that has on occasion fooled even experienced Service Men is supersonic oscillation. Amplifiers with output tubes connected in push-pull-parallel are especially liable to this defect. The oscillation can be seen without difficulty on the screen, but the operational symptoms may be misleading, especially when the oscillation breaks out only on signal peaks, as illustrated in Fig. 5 (p. 39). In such a case the defect may be diagnosed incorrectly as speaker rattle, which it imitates expertly. With steadier and heavier supersonic oscillation, the amplifier will overload and distort in a more obvious way.

This oscillation can be caused by improper dress of the output stage leads. The plate leads of one-half of the push-pull stage must not be inadvertently coupled capacitively to the grid leads of the other half. If the oscillation cannot be cured by lead dress, stopping resistors should be inserted in series between the output tube grids and the circuit leads connected to them. The resistors should be about 1,000 ohms each, wired close to the socket pins. Plate-stopping resistors of 25 to 50 ohms can also be used to advantage, connected to the plates in the same way. Fig. 6 (p. 39) illustrates the connection of stopping resistors, which do not affect the quality of performance in any way.

Subsonic oscillation, or motorboating, is another type of trouble that may arise in audio amplifiers. The usual loss of filter capacitance should be suspected immediately, and checked by bridging the filters. When the system has low-level stages, such as preamps for magnetic pickups or microphones, the proper functioning of

(Continued on page 84)



Standardize on

WEBSTER ELECTRIC
Featheride®

REPLACEMENT CARTRIDGES

When you stock these five models of Featheride Replacement Cartridges, you can handle virtually *all* replacement needs—regardless of make of record player or changer—quickly, easily, profitably, and with a minimum inventory investment.

Mail the coupon for free copy of our handy new Replacement Chart YF-2, showing how you can most profitably fill your replacement needs.

these 5 models are all you need!


Model WS • A versatile unit capable of replacing the majority of 78 RPM Cartridges in the field.

Model AX • A complete unit for three-speed application, furnished with a removable twist mechanism.

Model BX • Designed primarily for RCA Automatic record changers and Columbia players. Unusually high fidelity.

Model CX • May be used with a three-mil needle for 78 RPM or two-mil needle for three-speed application.

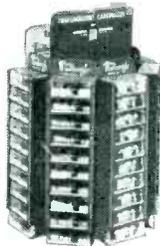Model FX • A two-needle twist cartridge; delivering high or low output.



THIS NEW DISPENSER WILL INCREASE YOUR SALES

• This attractive Featheride Replacement Cartridge Dispenser on your counter or wall will boost your sales and profits. It comes with a basic stock of 10 each of the 5 models shown above—each cartridge packaged with all needed fittings, instructions and data, all in individual transparent plastic box. Replacement chart included in back of dispenser.

Send coupon for details of our Special Dispenser Offer, whereby you save \$10 if you order promptly.

WEBSTER ELECTRIC
RACINE WISCONSIN

"Where Quality is a Responsibility and Fair Dealing an Obligation"
WEBSTER ELECTRIC COMPANY, RACINE, WISCONSIN • EST. 1909

Webster Electric Co., Dept. S-10, Racine, Wisconsin

Send me, without obligation, the items checked below:

Free Featheride Replacement Chart YF-2

Details of Special Dispenser Offer, whereby we can save \$10.00

Ordered by _____

Company _____

Address _____

City _____ State _____ Zone _____

Latest Books for TV "KNOW-HOW"!



TV MANUFACTURERS' RECEIVER TROUBLE CURES VOL. 1, VOL. 2, VOL. 3 and VOL. 4.

Positive cures for TV troubles! Gives you exact directions for correcting TV receiver performance "bugs". Each cure is official, factory-authorized, direct from the receiver's manufacturer. Listings by manufacturer and model or chassis number. Helps correct the most difficult faults—picture jitter, hum, instability, buzz, tearing, etc.

- Vol. 1, 115 pages (5¼ x 8¼")..... **\$1.80**
Covers 12 brands, Admiral through Dumont
- Vol. 2, 117 pages (5¼ x 8¼")..... **\$1.80**
Covers 11 brands, Emerson through Jackson
- Vol. 3, 119 pages (5¼ x 8¼")..... **\$1.80**
Covers 16 brands, Kaye-Halbert through Philco
- Vol. 4, over 115 pages (5¼ x 8¼")..... **\$1.80**
Covers 10 brands, Philharmonic through Shaw TV

VOLUME 5 COMING SOON!

Prominent manufacturers not in first 4 volumes
ONE SERVICE JOB WILL MORE THAN PAY THE COST OF THIS SERIES OF BOOKS!

OBTAINING AND INTERPRETING TEST SCOPE TRACES

by J. F. Rider

Over 500 actual photographs of test scope traces. Shows how to use scopes and what traces mean. Valuable for servicing TV receivers, FM and AM radio receivers, audio systems and test equipment. Specific test equipment set-ups shown with each application. No other book like it! Over 140 pages... **Only \$2.40**

HOW TO USE METERS

by J. F. Rider

Panel type, volt-ohm-milliammeters, vacuum tube voltmeters for servicing radio and TV receivers, audio amplifiers, power supplies; for use and repair of ham transmitters. Written for the service technician, the TV and Radio student and hams. Over 140 pages..... **Only \$2.40**

TV SWEEP ALIGNMENT TECHNIQUES

by Art Liebscher, Test Equipment Specialist

Never before has there been a book such as this on TV sweep alignment! An expert gives you accurate time-saving methods—and tells you how they work. Introduces the new Supermark method. Chock-full of sweep curve pictures. Valuable for servicing in UHF signal areas. 123 (5½ x 8½") pp., illus..... **\$2.10**

HOW TO USE SIGNAL AND SWEEP GENERATORS

By J. R. Johnson

First book on all types of signal and sweep generators. Gives test uses and discusses problems and their solutions in using this equipment. Applications of all signal and sweep generators in AM, FM radio and TV servicing. Over 120 (5½ x 8½") pages..... **\$2.10**

GUIDE TO AUDIO REPRODUCTION

By David Fidelman

A to Z explanation of the reproduction of sound. Design, construction, assembly and testing of sound systems and their components. Valuable for service technicians, engineers, amateurs. Over 250 (5½ x 8½") pp., illus.

RADIO TROUBLESHOOTING GUIDEBOOK

By J. F. Rider and J. R. Johnson

Here is a troubleshooting guidebook that covers the more than 100 million radio receivers now in use! Explicit information about troubles and possible causes. Completely practical for the radio service technician and student. Over 140 (5½ x 8½") pages.

Write for information on all RIDER books.

Buy these books now from your jobber... bookstore... If not available from these sources, write to:

JOHN F. RIDER Publisher, Inc.
Dept. 510 480 Canal Street, New York 13, N. Y.

Hi-Fi Audio

(Continued from page 83)

filter and decoupling networks will be found especially critical.

One should *never* replace a coupling capacitor with one lower in value, even when the original value seems unusually high. If the stage involved is within a feedback loop, increased phase-shift created by the lower value capacitor can produce motorboating; sounding just like that due to bad filters.

Very low-frequency oscillation appears as a slow, visible but inaudible back-and-forth movement of the speaker cone, sometimes referred to as *breathing*. This should be treated as motorboating.

All capacitors used in low-level stages must be of especially high-quality construction to guard against a very annoying type of crackling noise that can be introduced. Plate resistors in preamps have also been known to cause circuit noise.

The Record Player

Next to tubes, phono needles would probably take second prize as a source of trouble in audio systems. Distortion, noise, and groove skipping are often traced to a worn stylus, although the user may have no idea that his player is ready for a needle change. He may have the wrong impression about how many playing hours his needle is designed for, or he may not realize how much he has used it. In any case the life expectancy of a needle in a *hi-fi* system is far less than in a standard commercial phonograph. Although the actual needle point wear in the *hi-fi* player will very likely be less, due to proper adjustment of tracking force, and the use of high-compliance cartridges, the *effect* of needle wear shows up much more quickly. High-frequency distortion as well as *hf* program material is suppressed by an audio system of limited frequency range. In addition, a blunted needle will not skip grooves as readily when it is mounted in a relatively heavy cartridge and arm.

The diagnosis of distortion, buzzing, and rattling from records should, therefore, always start by suspecting the most probable source—the needle. When on an audio call, in which the complaint is phono trouble, Service Men should try to find out beforehand what type of cartridge and needle are used, and bring spares with him if possible.

In checking to see if the phono is *live*, it has been common practice in the past to stroke the needle with one's finger, while listening for output from



"Better make sure first that it's equipped with a Jensen needle."

the speaker. This procedure must now be revamped, because many record changers have muting switches. These keep the signal cable shorted until the arm has gone through its normal cycle and is dropped onto the record in playing position.

An amplifying channel with a preamp for magnetic pickups may have as much as one hundred times more gain than the most sensitive of amplifiers designed for radio or crystal cartridges. A particular tube may thus introduce unacceptable noise or hum, but may operate normally in other positions.

It is possible for phono distortion to originate in the playing mechanism itself, due to a mechanical vibration of the phonomotor called rumble. The phono cartridge is protected, to a certain extent, from picking up this rumble by the spring mounting of the changer plate, and by the rubber suspensions of the motor hanging from the plate. The effect of the spring mounting can be reduced by allowing any part of the changer to touch the cabinet, but the most serious danger lies in possible hardening of the motor suspensions. When this occurs the re-produced rumble may become very great. Over and above the annoy-

(Continued on page 85)

Donald M. McNicol



DONALD MONROE McNICOL, who served as editor of *RADIO ENGINEERING*, published by the *Bryan Davis Publishing Co., Inc.*, in the early 30's, died recently at his home in Roselle Park, N. J. His age was 78.

He was extremely active until his final illness as a writer of communication and electronic technical papers, acting, too, as a technical consultant to *Wire and Radio Communications*. He was the author of *Radio Telegraphy*, an early work and many major texts on radio transmission.

DM, as he was known to everyone, was elected Mayor of Roselle Park in '28 and served for two terms.

Early in his career he was a Western railroad telegrapher. He became a Postal Telegraph engineer early in 1900. In 1922 he became editor of *Telegraph and Telephone Age* in New York. Subsequently he joined RCA as assistant to the president.

For many years, DM taught at many universities. He was an instructor in Teachers College of Columbia University, lecturer in the Sheffield Scientific School of Yale University and Cooper Union in New York.

In 1926 he was elected president of the IRE. For over a score of years he was active on a number of key IRE committees. For six years he was a member of the board of directors. He also had been chairman of the publication committee of the AIEE.

Hi-Fi Audio

(Continued from page 84)

ance created by the low-frequency noise, rumble intermodulation can create large amounts of distortion, of a type similar in nature to that caused by open filters. The motor mounts and changer springs should be checked and necessary corrections or replacements made. If the rumble persists, the rim drive mechanism should be checked. The rubber idler wheel coupling the turntable rim to the motor bushing should be replaced if there seems to be the least bit of uneven wear. When this, too, fails to cure the trouble, the motor itself may be faulty and may require replacement.


[To Be Continued]

the master

of television signal generators

- more sweep
- greater RF output
- better stability
- increased accuracy
- unlimited flexibility
- lower cost

model TVG-2

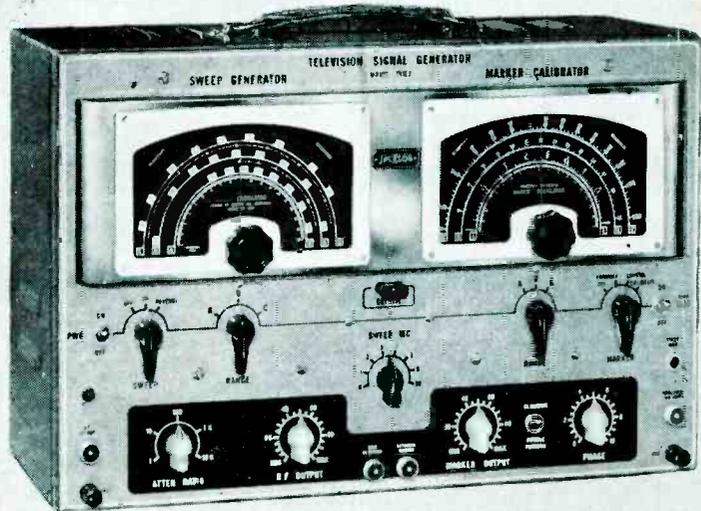

See your electronics distributor or write.

JACKSON


"service engineered" test equipment

JACKSON ELECTRICAL INSTRUMENT CO.
DAYTON 2, OHIO

IN CANADA:
THE CANADIAN MARCONI CO.

TV Voltage Trouble?

WRITE FOR
THIS HELPFUL
TeleVolt BULLETIN

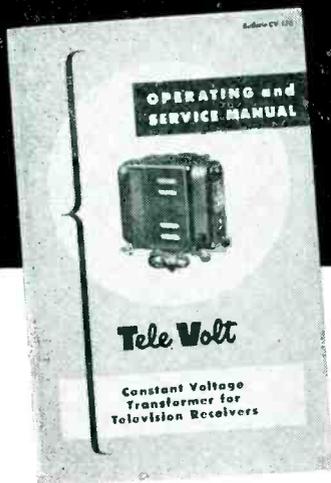

The Sola TeleVolt Bulletin can save you many hours and make you many dollars. It shows how you can automatically correct bad line voltage . . . high, low, and fluctuating voltage. The TeleVolt automatically maintains proper voltage levels for proper performance and protects costly TV components against damaging high voltage surges.

The Sola TeleVolt, Constant Voltage Transformer, is not a voltage booster . . . it is a patented voltage regulator that automatically stabilizes voltage to within $\pm 3\%$ of nominal value, regardless of line voltage variations as great as $\pm 15\%$.

Write today for Bulletin AD-CV-175
or see your electronic distributor



SOLA
Tele Volt

Automatic Constant Voltage
TRANSFORMERS

SOLA ELECTRIC CO.
4633 W. 16th St. Chicago 50, Ill.

DC Restorer

(Continued from page 33)

object as shown by e_g . (It will be noted here that the bottom of the sync pulses does not remain at a constant negative voltage level.)

Enter the DC Restorer

In the detection of sound modulation in AM radio, as represented by Fig. 2 (p. 32) there is no significance to the *dc* component of the signal. The *ac* component represents the audio signal, and the time constant of the circuit is made large enough so that the lowest desired audio frequency is passed by the circuit. In television, however, as shown by Fig. 4 (p. 33), the *dc* component is actually part of the transmitted signal in that it represents the average brightness level of the televised scene. The elimination of the *dc* level, as resulted in e_g of Fig. 4b, eliminates some of the transmitted information, for it is no longer apparent that there has been a large change from a light to a dark background. Of even greater practical significance is the fact that the sync pulse tips do not remain at the same level with changing background level. The significance of the elimination of the *dc* component of e_g in Fig. 4b, when it is amplified and applied to the picture tube, is shown in Fig. 5 (p. 33). The curve represents the grid voltage versus beam-current or brightness characteristic of a picture tube. Signal *I* represents a signal with a bright background level. The picture brightness control has been adjusted so that the blanking level of the applied signal coincides with the cutoff point on the picture-tube characteristic as desired, to allow maximum contrast range while at the same time providing retrace blanking. The picture-tube beam current is cut off for the duration of the blanking pedestal, so that the electron beam will not be visible as it returns to start each new horizontal and vertical scan. Signal *2a* represents a signal which has shifted to a dark background level as it should be with the *dc* component present. The top of the blanking pedestal still coincides with the picture tube cutoff and the output from the video portion of the signal has moved down toward the black end of the tube characteristic. In *2b* we have a signal with a dark background as it appears with the *dc* component removed. The average value of this signal is now at the zero applied signal level, so that the resulting picture has essentially the same background level as signal *I*; and since the blank-

The COMPLETE line



DR Double-Reentrant
Projectors




Paging
& Talk-Back
Speakers

for EVERY




ALNICO-V-PLUS
Driver Units

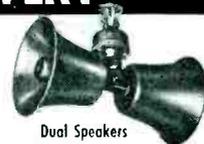

Dual Speakers

Public Address need!

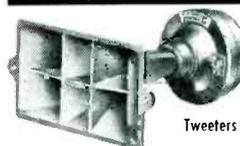

Tweeters




FULL-GRIP, VELVET-ACTION
Mike Stands

WRITE NOW
for FREE Catalog 553



**ATLAS
SOUND CORP.**

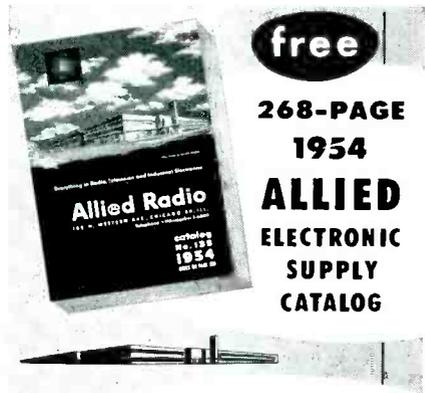1442 39th St., Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.



free

268-PAGE
1954
**ALLIED
ELECTRONIC
SUPPLY
CATALOG**

Everything in Electronics
For Service Technicians and Engineers

You'll want the complete, up-to-date ALLIED Catalog. It's packed with the world's largest selection of TV and radio parts and accessories, test instruments, amplifiers, P.A. systems, tubes, tools—everything for service work and industrial electronic application. Depend on ALLIED for quick shipment from the world's largest stocks—save time and money. Send today for your FREE 268-page Catalog.

ALLIED RADIO

ALLIED RADIO CORP., Dept. 23-K-3
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1954 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

ing pedestal does not reach picture-tube cutoff the scanning retrace lines will be visible on the picture.

One way to overcome the difficulty just described is to use direct-coupled amplifiers from the video detector to the picture tube grid (or cathode). In this way, since the coupling capacitors are eliminated between each stage, the entire video signal including the *dc* component will be amplified and applied to the picture-tube signal element. While this method is probably the most straightforward to understand it becomes difficult in practice; first, because direct-coupled amplifiers are subject to drift, and second, since the *dc* output level of each stage is directly connected to the grid of the following stage, it is difficult to obtain proper plate, grid and cathode-voltage relationships. The trick for overcoming these difficulties which became generally accepted was, of course, the use of *dc* restoration.

Fig. 6 (p. 90) shows a simplified schematic of a commonly used *dc* restorer circuit. The *dc* restorer is a rectifier to obtain a picture-tube compensating bias from the sync-pulse tips. The *ac* output of the video amplifier is applied to the diode detector through C_1 . In the circuit shown the sync pulses are negative, and the signal is applied to the cathode of the diode, so that the negative pulses cause C_1 to charge rapidly. The charge leaks off slowly through R_1 . Since the time constant of R_1C_1 is sufficiently long so that the charge on C_1 is maintained over several sync pulses, the circuit is effectively a peak-reading voltmeter, the output of which is proportional to the peak value of sync pulses. The bias developed prevents current from flowing except on sync pulse tips; no current flows on any video signal peaks because they are never greater than the blanking level, which is a constant value below the sync pulse tips.

As indicated in Fig. 5, the peak value of the sync pulses is a measure of the average brightness of the picture. For instance, signal *I* in Fig. 5 has a large peak value of sync pulses. Its average value falls high upon the picture-tube characteristic curve and it therefore produces a high value of average brightness. Signal *2a* on the other hand has a low peak value of sync pulse; its average value falls far down on the curve and it produces a low value of average brightness. The bias developed across R_1 applied to the picture-tube grid through R_2 , as shown in Fig. 6, therefore accomplishes *dc* restoration. That is, it com-

(Continued on page 90)



JONTZ

TV INSTALLATION ACCESSORIES

**SAFE... LONG LASTING
... EASY TO INSTALL**

Jontz TV Installation Accessories give you extra quality, greater economy.

All Jontz products are heavily zinc-plated with an additional chromate coating... six times more weather protection than ordinary zinc-plating.

JONTZ
Pioneers in the field
of TV Reception

MODEL 200 "SUPER" KWICK CLIMB TOWER*


Finest self-supporting 50-ft. tower available. Withstands wind loads up to 100 m.p.h. . . . assures maximum safety with no guy wires. Approved by one of the world's leading liability insurance companies, when properly installed according to specifications. Constructed of highest quality rust-resistant 1-in., 14 gauge tubular steel . . . easy to erect, easy to climb. Available in 10-ft. sections . . . shipped complete with foundation mounting. Additional height up to 150 feet if required.

*Twelve men in photograph represent 2018 pounds!

Your inquiries will receive prompt attention.
Don't delay . . . write us today!

QUALITY CONSTRUCTION

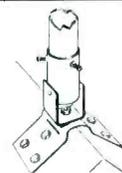Jontz masts are made of highest quality electric weld steel tubing, with heavy zinc galvanized coating . . . your assurance of tubular strength and durability




APEX MOUNT, MODEL A-S

4-way swivel mount for any type of installation. Fully adaptable to flat surface, peak roof, or corner mounting.



ROTARY MOUNT, MODEL S

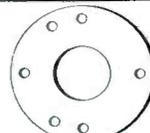4-way rotary base mount. Fits along roof peak for safe, easy installation.



GUY RINGS BY JONTZ

The answer to your guy ring needs. Handy Jontz guy rings may be used with either 3 or 4 guy wires . . . your choice of 5 l. D.'s.

QUALITY  ECONOMY

MANUFACTURED BY

JONTZ MANUFACTURING CO.

1101 East McKinley, Mishawaka, Indiana, Mishawaka 5-5178



FREE!
NEW '54
EDITION

SIMPLIFIES
TV ANTENNA
INSTALLATIONS
AND SALES



INCLUDES
LATEST UHF/VHF
DATA & EXCLUSIVE
"ANTENNA SELECTOR"

Completely revised by TV authorities Matt Mandl and Ed Noll, this essential pocket size manual includes the exclusive "Antenna Selector", Directronic Antennas, Dimension Guide, Channel Frequencies, Proper Feed Methods, Helpful Hints... everything about every type of TV antenna.

FREE To TV Servicemen,
Service Dealers,
Dealers, Distributors, Hams,
Salesmen, Manufacturers

Publication Price \$1.
Yours free if you write at once.
MAIL THIS COUPON TODAY

SNYDER MFG. CO., Dept. A
22nd & Ontario Sts., Phila. 40, Pa.
Please send free copy of TV 'TENNA TIPS

Name _____
Address _____
City _____ Zone _____ State _____

Audio

(Continued from page 75)

an input isolating transformer may be necessary.

Hum can, of course, also be picked up in the input circuit, by the leads from the microphone or pickup, or in the microphone or pickup head itself. Care in placement will take care of the latter.

Inductive hum in a low-impedance circuit is due to a loop in an alternating field. To avoid this possibility, the whole length of the lead, both inside and outside of the amplifier, should be run with as little space as possible between the pair, and they should be twisted together throughout their length.

In checking where pickup occurs, the line may be disconnected at any stage and a resistor equal to the working impedance connected to the open input at that point. If the hum disappears, its origin is further from the amplifier; if the hum doesn't vanish, it is nearer to the source.

Low-impedance circuits often do not need screening, but where the line is long, it may sometimes reduce hum pickup; in this case, twin screened lead should be used. The internal lead should be used for the signal circuit, and the outer screen should be connected to the signal circuit at one point.

In some equipment lines are run at 500 or 600 ohms; in these instances it is always a good precaution to use twin screened cable. If successive lengths of line are coupled together, the screening and two inner conductors should be kept separate, except at the amplifier input. The best plan in this case is to use a balanced circuit. If the screening is quite com-

Hi-Fi Flexo-Rack, of wood construction and secured by thumbscrews and bolts, which it is said can be adapted to accommodate any audio system to its best advantage. Rack, available in kit form, can aid in deciding on final cabinet design. (Model 730; River Edge Industries, River Edge, N. J.)



AMPLIFIER

You can change an outmoded radio, phonograph or TV receiver into a high fidelity instrument with a VC-6 amplifier. Low cost, yet supplies more power than required by the largest size house... so simple to install, anyone can do it. The VC-6 is made for quick, easy mounting. It's compact, light weight. No extensive cabinet alterations. R.T.M.A. guarantee.

Service! The VC-6 cuts your conversion costs — makes more jobs more profitable. Matching speaker systems available.

Push-pull power output—6 watts.
Frequency response 50 to 30,000 c.p.s.
Bass boost of 6DB or treble boost of 6DB from single control.

Impedance—8 ohms
Self-contained power supply,
110 V., 60 cycles, A.C. only
Size 1 3/8" x 3 1/8" x 11" long
Ship. Weight 3 lbs.

ONLY
\$26.95

F. O. B. N. Y. C.



Order your VC-6 Amplifier Today!
Quantity Discounts.

VIDEO CORPORATION OF AMERICA
229 West 28th St., New York 1, N. Y.

plete (there is no point at which the line is exposed), the center tapped resistor can be omitted, as the symmetrical capacitance of the line will insure balance.

The foregoing data applies to low-impedance circuits using a transformer to step up to the grid circuit. High-

Amplifier with loudness contour selector; seven magnetic phono equalization positions for all types of records; separate bass and treble tone controls; built-in preamp with dc heated filaments for minimum hum; five feedback loops; and partial cathode loaded output circuit. Preamp for G.E., Pickering, Audax and similar magnetic pickups. This is not in the circuit when a high level pickup or a tuner is fed into amp. Power output said to be 20 watts at 0.3% peak, 30 watts. (DB-20; David Bogen Co., Inc., 29 Ninth Ave. N. Y. 14).




Sky hook universal clamp designed to fasten to almost every type of surface ledge, round pipe or irregularly shaped stanchion. Microphone can be attached directly to $\frac{3}{8}$ "-27 tube supplied with clamp. Casting is finished in gun metal shrivel; chrome tube is 3" long. (Model SK-1; Atlas Sound Corp., 1451 39th St., Brooklyn 18, N. Y.)



impedance inputs from crystal or condenser microphones require quite different treatment. As stated earlier, the impedance loading must be kept very high, and the grid circuit impedance is highest of all at the low, hum frequencies. This means extreme care must be taken to prevent electric pick-up. Screening must be absolutely complete. Even a hole in the screening can let hum in. The screened return virtually requires plumbing from the head right to the grid of the input tube. If any connecting plugs or sockets are used, they must maintain concentric screening throughout; otherwise trouble can arise.

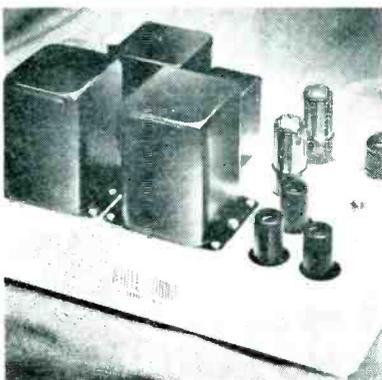A 25-watt amplifier featuring a balanced impedance phase inverter; balanced impedance drive; balanced drive; zero phase shift through dc phase inverter and voltage amplifier; plate degeneration as well as cathode degeneration; voltage amplifier; carbon brush volume pot and feedback of 20 db around four stages of amplification. (Model 1020; White Sound, Inc., 105 W. Madison St., Chicago 2.)



W 42 BH

78

This "Dual Voltage" cartridge is an excellent all-around replacement for old-style 78 r.p.m. cartridges. It guarantees improved performance in many cases. A unique "Slip-On" condenser harness provides choice of output voltage—1.5 with condenser harness installed and 3.75 without condenser. For fine quality at low cost your best bet is the Model W42BH at only \$5.50 list.



W 31 AR

WC 31 AR

33 1/3

45

This high output (2.1 volts!) "Direct Drive" cartridge was specifically designed for use with all fine-groove records. Universal mounting bracket provides quick, easy installation in RCA-type 45 r.p.m. changers. (Fits $\frac{1}{2}$ " and $\frac{3}{8}$ " mounting centers.) Has easy-to-replace needle. For maximum quality, highest output, and low cost, specify Model W31AR at the low list price of only \$6.50

33 1/3

45

Also available as ceramic cartridge (same price)—Model WC31AR. Highly recommended in areas where heat and humidity make use of conventional crystal cartridges impractical. List price.....\$6.50



W 26 B

33 1/3

45

78

This "Vertical Drive" "all-purpose" cartridge provides superlative reproduction for all types of records. Low tracking pressure (only 6 grams) and high needle compliance guarantee faithful tracking and longer record life. Uses exclusive Shure "Unipoint" needle, scientifically designed for maximum performance and long life. List price.....\$7.50



W 22 AB

33 1/3

45

78

This "Vertical Drive" "turnover-type" cartridge provides extended frequency response (50 to 10,000 c.p.s.) at extremely low needle point pressure—only 8 grams. One of the most popular, widely used cartridges in original equipment. Highly recommended as replacement in phonographs equipped with turnover mechanism. Individual needles—one for fine-groove and the other for standard records—guarantee maximum results. List price.....\$9.50



W 22 AB-T

33 1/3

45

78

Offers all the advantages provided by the Model W22AB, plus a long-life turnover mechanism. Furnishes replacement of old, worn-out turnover mechanisms as well as cartridges. Also an excellent replacement for converting all-purpose phonographs into turnover type. List price.....\$10.00

Patented by Shure Brothers, Inc., and Licensed under Patents of the Brush Development Co.



SHURE BROTHERS, Inc. ☆
225 W. HURON ST., CHICAGO 10, ILL.

Manufacturers of Microphones
and Acoustic Devices

Cable Address: SHUREMICRO

Service Technicians!



NOW you can own
the invaluable
PHOTOFACT Library
this **EASY** way!

- ✓ Own the **COMPLETE** Library
- ✓ Fill in your present Library

Yes, now you can get through your PHOTOFACT Distributor, the complete PHOTOFACT Library (200 Sets of Folders) for only \$25.00 down and 18 full months to pay! Or you can fill in your present library and bring it up-to-date on the same amazing terms. Absolutely no interest and no carrying charge! You get immediate *prepaid* delivery of the world's finest service data. You use it *now*. It earns for you while it *pays for itself*! See your PHOTOFACT Distributor today!

Yes ONLY \$25.00 DOWN!
UP TO 18 MONTHS TO PAY
No Interest • No Carrying Charge

PLUS the ultimate in
filing convenience. Your choice of:



BINDERS: Handsome, sturdy permanent binders that make up into handy volumes of 10 sets of Folders each. Order 20 for the 200 set Library or as many as you need to fill in. Shipped prepaid.



FILING CABINET: Sturdy 4-drawer file cabinet to hold your PHOTOFACT Library in ship-shape, easy-reference order. Shipped FOB factory.

Yes, you get either Binders or File Cabinet with your PHOTOFACT Library under the same Easy Terms—the entire deal for just \$25.00 down, up to 18 months to pay!

ORDER TODAY!

PAY AS YOU PROFIT with
The World's Finest Service Data

See your PHOTOFACT Distributor for full details. If you don't know his name, write us for it. Address: HOWARD W. SAMS & CO., INC., 2201 E. 46th St., Indianapolis 5, Ind.

DC Restorer

(Continued from page 87)


lines on the picture-tube grid a signal proportional to the *dc* level of the video-detector output with the *ac* signal from the video amplifier. More explicitly, if the brightness control is adjusted to provide retrace blanking on very dark (low peak-to-peak values) pictures, any brighter picture will have a larger peak-to-peak value, which will cause an increased positive diode bias to be applied to the picture tube grid, thus causing the average of the signal to move up on the tube characteristic to provide a bright picture as it should. A signal of any value develops the proper amount of bias to place it automatically on the portion of the tube characteristic which corresponds to its proper *dc* value, so as to provide the correct level of average brightness.

Another DC Restorer Method

Another way to obtain *dc* restoration, which found some acceptance, was to develop the picture-tube compensating bias by grid rectification in one of the video amplifiers. Since it is necessary to develop the grid-leak bias on sync pulses, it must be developed in a stage preceding the picture tube where the polarity of the pulses can be positive. The last video amplifier must therefore be direct coupled to the picture tube grid. Grid-leak restoration is therefore probably only an advantage over complete direct coupling, where more than one video amplifier stage is used. Some receiver designs attempted to obtain a measure of *dc* restoration by the use of a grid rectification in the picture tube itself, by allowing the positive peaks of video signal to draw current and develop a negative bias on the picture tube grid. This method was not too satisfactory since, to develop grid current, the video peaks

NOW GIVE BETTER . FASTER SERVICE

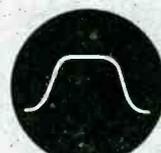
INVEST in KAY INSTRUMENTS THAT SAVE YOU TIME AND INCREASE YOUR PROFITS




Calibrated MEGA-SWEEP
50 kc to 950 mc range
Sweep width at least 30 mc



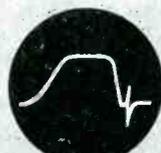MEGALIGNER—a calibrated
variable frequency
IF marker pip generator



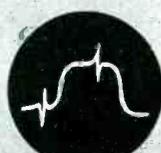MEGA-MARKER SR
crystal controlled, 12-channel
TV RF sound carrier generator



DUAL MEGA-MARKER SR—same
as Mega-Marker Sr. with RF
picture carrier generator added

Consult
this latest
64-page
catalog
FREE



Write . . .

KAY ELECTRIC CO.

12 MAPLE AVE.


PINE BROOK, N. J.

had to be at a high level where saturation and blooming was encountered.

Exit the DC Restorer

Even with *dc* restoration, it proved difficult to hold blanking levels constant enough to prevent vertical retrace lines from becoming visible in the presence of large variations in average picture brightness levels. In practice, the point at which retrace lines became visible was in some cases a limitation on the maximum brightness setting. Also, as the larger tube sizes put more demands on the horizontal deflection system it became increasingly difficult to keep the horizontal retrace time sufficiently short

Fig. 6
Simplified schematic
of commonly-used *dc*
restorer circuit.

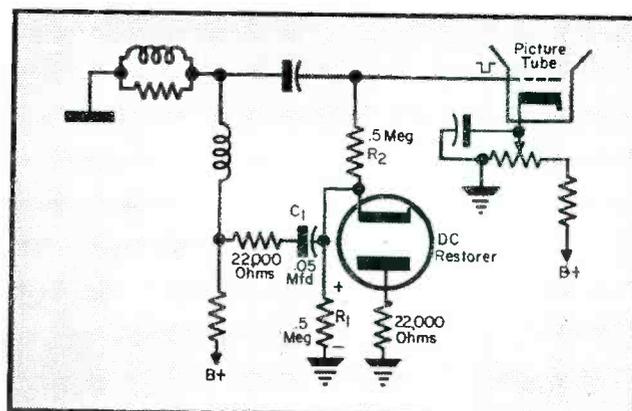

to prevent horizontal foldover. Vertical and horizontal retrace blanking has come into general use to overcome these two difficulties. Service Men have become generally familiar with the operation of these circuits, one form of which is shown in a simplified schematic in Fig. 7. In these retrace-blanking circuits a pulse is derived from the retrace kick of both the horizontal and vertical-deflection systems and applied to the picture grid or cathode (depending on pulse polarity), so as to cut off the beam current during the entire retrace time. In this way horizontal foldover is prevented and the vertical retrace lines are not visible regardless of the setting of the brightness control.

With the general use of vertical retrace blanking one of the uses of the *dc* restorer disappeared; it was no longer necessary to clamp the sync pulses at a constant level to prevent vertical retrace lines from becoming visible in the picture. It now became possible to review the need for *dc* restoration on the basis of *picture tone quality* alone.

Some information on the results of omitting *dc* restoration may be obtained from further inspection of Fig. 5 (p. 33). Since all signals will operate with their average value at the point set by the brightness control, operation will be in the linear range of the tube characteristic regardless of transmitted average brightness level. There will be less tendency for dark pictures to lose contrast. The reason for this improvement is shown by the two methods of operation with signal 2. Signal 2a is held at its transmitted *dc* level and the video portion of the signal is operating in the non-linear region of the tube characteristic near cutoff. The contrast range of the resulting picture is therefore compressed by the curvature of the characteristic in this region.

There are, on the other hand, two apparent disadvantages to utilizing only the *ac* components of the television signal. First, of course, the average brightness levels are not faithfully reproduced. Second, the brightness range available for dark pictures is decreased. For instance, in signal 2b very bright highlights will reach into the saturated white portion of the picture-tube characteristic much before highlights in signal 2a. In practice, operation without *dc* restoration seems to have provided good results. The eye is more sensitive to relative brightness (contrast) than to absolute brightness (average brightness). Therefore, the viewer does not recognize the lack of faithful reproduction

MONEY BACK GUARANTEED

TO RECEIVE *All* UHF and *All* VHF STATIONS IN *All* DIRECTIONS FOR 60 MILES WITHOUT A ROTORMOTOR OF ANY KIND!!



WORLD'S MOST POWERFUL UHF-VHF TELEVISION ANTENNA

While antenna reception is guaranteed for 60 miles, perfect pictures have been consistently received as far as 160 miles from stations.

All NEW DESIGN FOR '54

- LOW-LOSS SWITCH
- LOW-LOSS PHENOLIC INSULATORS
- USES NEW 4-CONDUCTOR MATCHED IMPEDANCE LINE
- ONLY 10 INCH SPACING BETWEEN ANTENNA BAYS

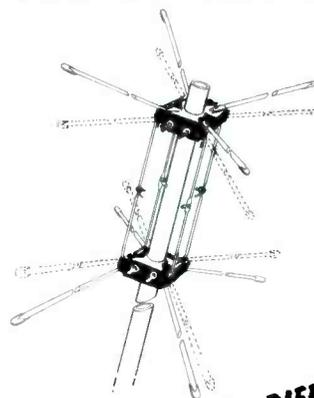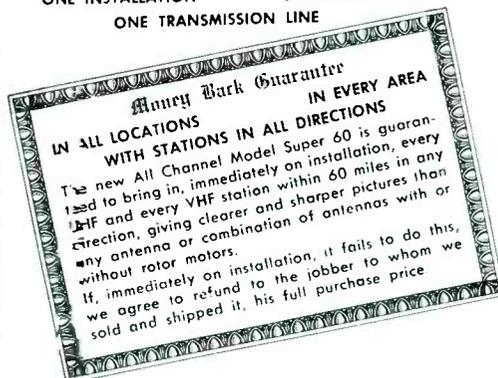ONE INSTALLATION ONE ANTENNA
ONE TRANSMISSION LINE



MODEL
**SUPER
60**

**SO NEW! SO DIFFERENT!
IT'S PATENTED!**

2,585,670
2,609,503
2,625,655
2,644,091



The 9 position selector switch electronically rotates the antenna in a stationary position.

LIST PRICE
\$36⁷⁵
SEE YOUR LOCAL JOBBER

PRICE INCLUDES
Complete stacked array • 4 stacking bars • 9 position switch • Switch-to-set coupler • 3 - 7 1/2" stand offs • Individually boxed in mailable carton

ALL CHANNEL ANTENNA CORP.


70-07 Queens Blvd., Woodside 77, N. Y.

Hickory 6-2304

of average brightness levels, and in fact finds pictures generally improved because good contrast is maintained. The decrease in brightness range for dark pictures has proved to be no serious disadvantage. Furthermore, since the *dc* voltage applied to the picture tube remains constant there is no interaction between the brightness and contrast controls, as is the case with receivers employing *dc* restoration. In one experience with an older receiver using *dc* restoration and no retrace blanking, there was a tendency to re-adjust continually the brightness control for program or sometimes even

scene changes. On a newer receiver incorporating retrace blanking, but without *dc* restoration, there is no such tendency. In fact, the brightness control is a covered shaft adjustment (Continued on page 92)

Fig. 7. A vertical and horizontal retrace blanking circuit.

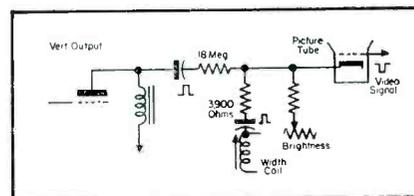

This book will save you
30 Minutes
a day



ONLY 35¢

- COMPLETELY NEW
 - FIRST EDITION
- JUST OFF THE PRESS

FIND TUBE RATINGS, CONNECTIONS IN SECONDS

This big new Westinghouse *Ready-Guide* is a completely new kind of handbook of receiving tube data. Designed to save time for busy servicemen and engineers. Eliminates "squinting" at tiny data listings.

BIG — BOLD — CLEAR

Just 9 tube types are listed on each 8½" x 11" page. Not 30 or 40 tiny type listings as in most condensed data books. Best of all, large clear base diagrams are located on the same page as ratings. Bothersome cross referencing, footnotes cut to the bone.

COMPLETE, ACCURATE, UP-TO-DATE

This new Westinghouse *Ready-Guide* lists complete data on receiving tubes which account for more than 98% of tube usage. 48 pages. 385 pictures and diagrams. 342 types listed.

SPECIAL: 3 for \$1.00

This *Ready-Guide* is being sold at less than cost as an introductory offer only. Price is only 35¢—3 for \$1.00. Order from your nearest RELIATRON Tube Distributor or mail coupon below.

ET-9503B

Westinghouse **RELIATRON TUBES** TM

Westinghouse Electric Corporation
Electronic Tube Division, Dept. N-210
Box 284, Elmira, N. Y.

.....Enclosed is \$1.00 for 3 copies of
Ready-Guide
.....Enclosed is 35¢ for 1 copy

NAME.....
ADDRESS.....
CITY.....STATE.....
Please Print

DC Restorer

(Continued from page 91)

and there is no need to know of its existence.

If two TV receivers, one with, and one without *dc* restoration are observed simultaneously the difference in average brightness levels can be observed, particularly if the two sets are switched back and forth between channels carrying programs of quite different brightness. However, when observing one without restoration alone no particular deficiency will be recognized. An interesting way to observe the results of the lack of the *dc* component in the video signal is to adjust the vertical hold control until the vertical blanking bar appears on the picture. The lighter portion of this bar, which represents the vertical blanking pedestal, will be seen to vary in brightness as the televised scenes change. On a receiver incorporating *dc* restoration, the blanking bar will maintain a constant brightness on all but the most drastic scene brightness changes. A measurement of the picture-tube *dc* grid-cathode voltage will, of course, show a constant value without restoration, and a voltage which varies with scene changes if restoration is present.


Thus, in answer to the original question: The *dc* restorer has been eliminated in most receivers because faithful reproduction of average brightness levels has been found secondary to ease of adjustment, maintenance of good contrast and a small step toward circuit simplicity. Some designs continue to use a single video amplifier with direct coupling to provide true *dc* brightness levels. However, it is common in late models to find both horizontal and vertical retrace, blanking, *ac* video coupling and no *dc* restoration.

Another interesting by-product of eliminating the *dc* restorer is a decrease in airplane flutter. Airplane reflections result in fluttering ghosts and alternating variations in signal level. The lack of a *dc* restorer has no effect on the presence of ghosts. However, the visible signal-level flutter is in the frequency range below about 10 cps; so, if *ac* coupling is used (no *dc* restorer), these low frequencies will not be passed to the picture tube and one annoying aspect of flutter will not be present.

Color TV

Our old friend, the *dc* restorer, may, however, return to work in *color TV* receivers. Since the eye does not have an equal sensitivity range for all colors, reproducing the picture at a

RADELCO
INDOOR ANTENNA

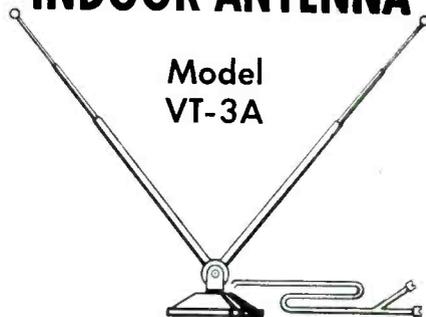


Model VT-3A

... A high quality antenna, attractively designed and finished in mahogany lacquer to harmonize with all room furnishings. Three section, brass tubing masts with lustrous plate finish extend to 45" for fine reception. Heavily weighted base. Lead and terminals included. A real value!

ORDER FROM YOUR
NEAREST PARTS JOBBER

LIST PRICE
\$3.45

South River
★★ NEWS ★★

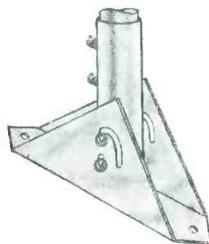

ROOF MOUNT
Model RM-15

This improved model carries the new drop-lock feature, enabling mount to be "walked up" to the vertical position, where it drops and locks securely. Made of heavy-gauge steel and embossed at all critical points, this fixture accommodates masts measuring to 1½" O.D. Assembled.

Write for your copy of our new 1953 catalog.

In Canada — A. T. R. Armstrong Co., Toronto

SOUTH RIVER METAL PRODUCTS CO., INC.
SOUTH RIVER, N. J.

PIONEER AND OUTSTANDING PRODUCER
OF FINEST LINE OF ANTENNA MOUNTS

brightness level different from that at which it is televised may appear to the eye as actual color distortion. In other words, color may appear unnatural if faithful reproduction of brightness levels is not maintained.

TV Antennas

(Continued from page 70)

sary for overcoming the ignition, neon light, electric motor noises, etc., often seen on *vhf*.

Measuring Equipment

For all *vhf* measurements, an instrument covering 50 to 220 mc and utilizing a half-wave dipole was used.

This instrument contains a built-in calibrating oscillator and is supplied with correction factors for antenna, attenuator, transmission line, etc., which render the instrument direct reading.


For *vhf* a 2-stacked bowtie antenna with reflector was used. Signals were fed into the set and replaced by direct substitution with a calibrated *vhf* signal generator. The signal generator output was then adjusted to give the same reading on the receiver output meter as noted with the antenna connected. Voltage at the receiver terminals could then be read directly from the signal generator.



Dick Morris (right), sales manager of Snyder Manufacturing Co., presenting Frank Corbin of M. V. Mansfield Co., Pittsburgh, with the first of the Snyder bowtie reflector antennas. Antenna features diamond embossed aircraft aluminum elements, an all welded reflector screen and single U-bolt installation. (Model UHF-5.)



PREFERRED

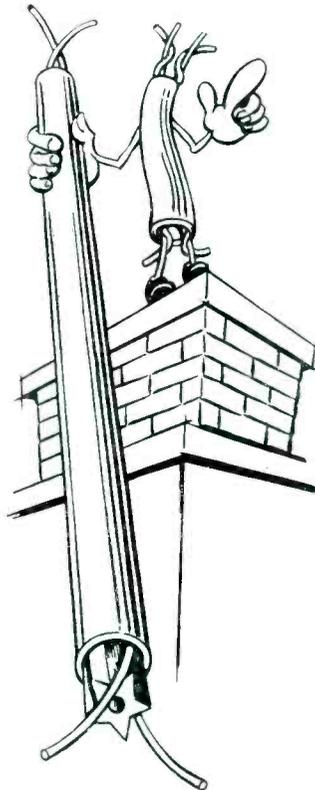

by

SERVICEMEN EVERYWHERE

FENTUBE - AIRSPACED

TWISTUBE

TUF-GUY

Sold through qualified jobbers only

Frequency—mc:	50	100	500	700	900
Attenuation-db/100:					
FENTUBE-AIRSPACED*	.72	1.06	2.6	3.2	3.8
TWISTUBE*	.74	1.16	2.68	3.29	3.93

*Pat. Pend.

Tuf-Guy*



Toughest, Most Durable
Guy Wire on the Market

FENTON COMPANY

15 MOORE ST., NEW YORK 4, N. Y.

Tel.: Bowling Green 9-3445-6





(Left)

Crossover network designed to permit the use of *vhf* and *vhf* antennas from a single lead-in and elimination of antenna controls or switches for all-channel TV reception. (United Technical Labs., Morristown, N. J.)


(Right)

VHF conical featuring use of extended conical type driven element. Full gain is claimed to be realized from this type of construction. High channel section consists of 2 driven elements and 2 directors. The receiving element for the low end of the high channels is located in the center of the flat plane conical assembly. Transformer type receiving element is used to sustain the gain level at the higher end. (Model Jet 213; JFD Mfg. Co., Inc., Brooklyn 4, N. Y.)

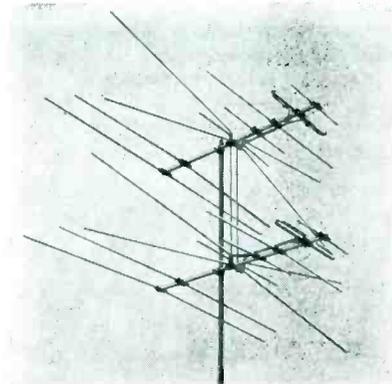

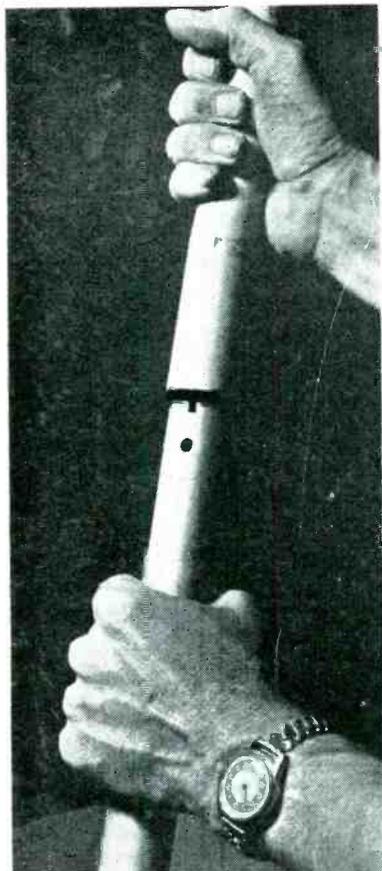

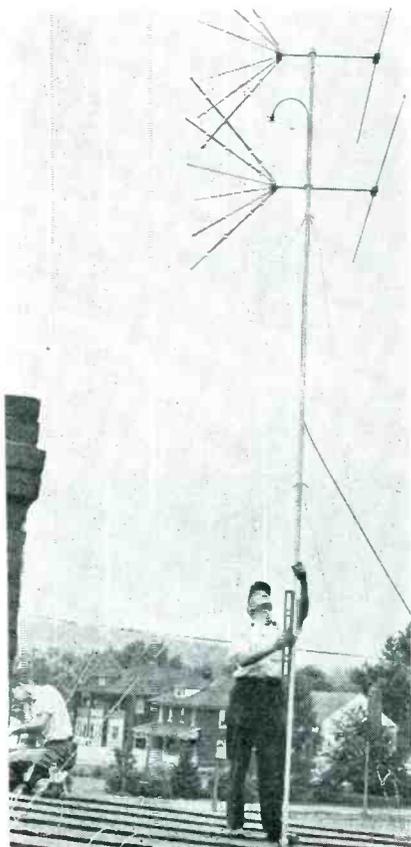Assembling two sections of Perma-Tube. Here expanded end of the upper mast section is about to be slipped over the reduced end of the lower section to form a machine-tight fit. The positioning device is said to prevent the mast from turning at the joint once it is oriented.



V-M High Fidelity RECORD CHANGER

EXCLUSIVE RESONANCE-FREE DIE CAST TONE ARM.

TWO DIE CAST PLUG-IN TONE ARM HEADS FIT MOST CARTRIDGES.

EXCLUSIVE SILENT 4-COIL MOTOR.

LAMINATED TURNTABLE ON 3-BALL THRUST BEARING.

**more exclusive
high fidelity features
than any other changer**

* V-M TRI-O-MATIC® 936HF CHANGER ATTACHMENT: V-M 45 spindle included. Also available, less metal pan, as Model 935HF.

V-M leads the industry in providing well-designed, properly built hi fi record changer features! V-M's superior record protecting, record handling features also contribute directly to the faithful reproduction and lasting enjoyment of fine records of all three speeds and sizes.

SEND FOR COMPLETE DATA on these and many more features offered by V-M Corporation, world's largest manufacturer of phonographs and record changers exclusively.

Visit V-M Display • New York Audio Fair • Room 740 • Hotel New Yorker, Oct. 14-17

**MAIL
THIS
COUPON
TODAY**

V-M Corporation,
Benton Harbor 6, Michigan

Please send complete data on V-M Models 935HF and 936HF.

Name _____

Address _____

City _____ State _____

(Right)

Fringe area antenna engineered for coverage of all vhf channels. Said to have one major forward lobe, narrow beam to reduce ghosts and noise pickup and high signal-to-noise ratio. (Model CP-1; Wells and Winegard, Television Accessory Mfg., Burlington, Ia.)


(Left)

Installing 20' antenna mast mounted on a roof bracket, supported by 18-gauge wires in York, Pa. Mast is electricwelded steel tubing, coated inside and out with plastic to prevent corrosion. (Photos courtesy Jones and McLaughlin Steel Corp. and George Cooper, TV Specialist in York, Pa.)

SERVICE, OCTOBER, 1953 • 95

www.americanradiohistory.com

KESTER

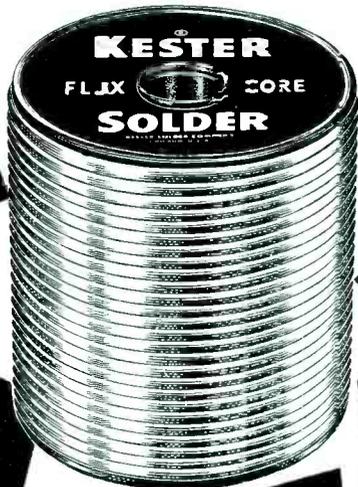

Since the most important single step in Radio-Television Servicing is soldering... it's just plain good sense to use the best — KESTER SOLDER... Key Name in Solder for More Than 50 Years.




KESTER SOLDER COMPANY
1248 Wrightwood Avenue • Chicago 39, Illinois
Newark 5, New Jersey • Brantford, Canada

SOLDER

NEW EASIER WAY TO DISPENSE RESISTORS

with
**RESIST-O-FILE
CABINETS**

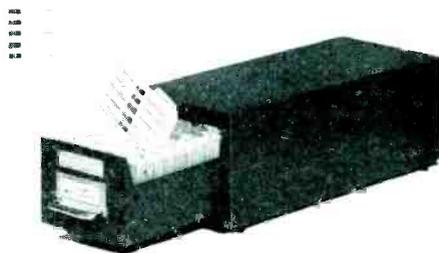

Saves inventory checking time. Finds desired resistor and quantity quickly. Five "CARBOMITE" resistors firmly mounted on a 5 x 3 indexed file card for instant selection. A handy color code chart is printed on the back of each card. The cabinet assortments consist of a variety most commonly used in the replacement field. The cabinet is furnished free, you pay for the resistors only.

CABINETS-Quantity and size

		LIST PRICE
MC $\frac{1}{2}$	200 Resistors (40 cards, MR $\frac{1}{2}$) $\frac{1}{2}$ Watt	\$34.00
MC1	200 Resistors (40 cards, MR1) 1 Watt	50.00
MC2	150 Resistors (30 cards, MR2) 2 Watt	49.50

SEE YOUR LOCAL DISTRIBUTOR
FOR NET PRICES AND DELIVERY TODAY


CONTINENTAL CARBON, INC.



13900 LORAIN AVE. CLEVELAND 11, OHIO CLEARWATER 1-6500

TV Antennas

(Continued from page 95)


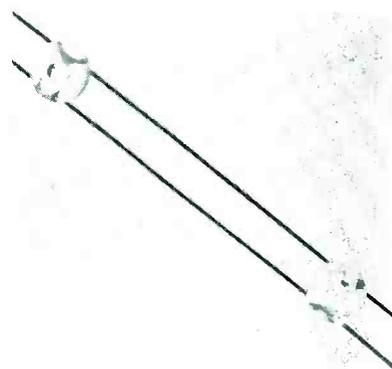


Open wire transmission line for uhf and vhf. Insulator (polythymalyne) is said to be designed for minimum signal loss. The impedance of the wire is 300 ohms. No standoffs are necessary, it is claimed, or if preferred regular standoffs can be used. (Saucerline; Pretco, Inc., 406 N. Craig St., Pittsburgh, Pa.)

†Pat. Pending.

(Below)

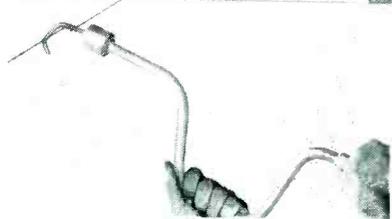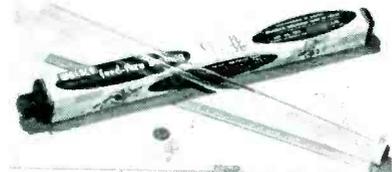Feed-thru bushing that, it is said, can accommodate all popular TV lead-in wires; coax or twin-lead wires including shielded and tubular, as well as rotator control cable. Also has provision for terminating to open line. Bushing is 1 $\frac{1}{2}$ " over-all and fits walls up to 14" thick. It requires a $\frac{3}{4}$ " hole. (Walsco.)




(Above)

Guy-wire tightener, which looks much like a typical drill bit, except that the end is curved to hook around the guy-wire. By revolving the handle included in the kit, guy-wire can be coiled and tightened evenly. (Guy-Tite; Walsco.)

(Below)

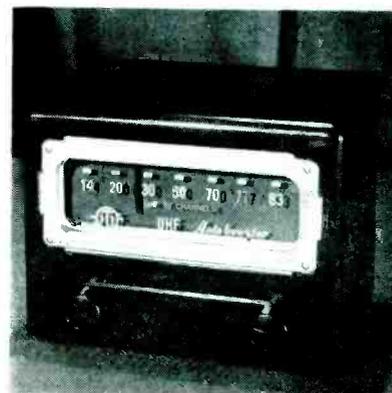Continuously tunable uhf booster. Uses a 6AJ4 low noise uhf triode. (Model IT-133; Industrial Television, Inc., 369 Lexington Ave., Clifton, N. J.)



Tools . . . Parts Instruments . . .

[See page 100 for additional new product news.]

MALLORY DUAL-OUTPUT POWER SUPPLY

A dual-output service bench power supply, *Rectopower 12RS6D*, designed to test 12-volt auto radios, as well as the standard 6-volt sets, has been introduced by *P. R. Mallory and Co., Inc.*, 3029 E. Washington St., Indianapolis 6, Ind.

Unit is equipped with both a *dc* voltmeter and ammeter for the measurement of current drawn by the equipment as well as the voltage applied to it. An infinitely variable output-voltage control is featured, and is said to be valuable in duplicating voltage fluctuations encountered under actual operating conditions. Has fuse in *ac* line and a self-reclosing overload circuit-breaker in the *dc* circuit.


Specifications: 0-8 volts at 10 amperes or 0-16 volts at 6 amperes, variable, continuous duty; 20 amperes on low range or 14 amperes on high range, intermittent duty; filtered *dc* output to less than .8 volt *rms*; and 12,000 mfd filter capacitor.

* * *

ASSCO NUT AND SCREW STARTER

A nut and screw starter, to aid in starting small nuts as well as screws in difficult, hard-to-reach places, has been developed by Aviation Service Supply Co., Stapleton Field, Denver, Colorado. Tool has a lever-mechanism in the handle which controls movable blades and adjusts them for gripping all standard sizes of small nuts and screws.

Starter has a pair of movable blades projecting from a sleeve attached to the handle. As these blades are pushed into the sleeve, mechanism inside the handle causes them to rotate inward, thus forming a *V*-shaped end, which grips the screw head and maintains the necessary tension to hold it until the screw is started. Available with lightweight aluminum handle and body, and blades of specially tempered drill-rod steel in six different sizes designed to accommodate all standard sizes of small nuts and screws from a 6 to a 1/4" nut, and from a 4 to a 10 screw.

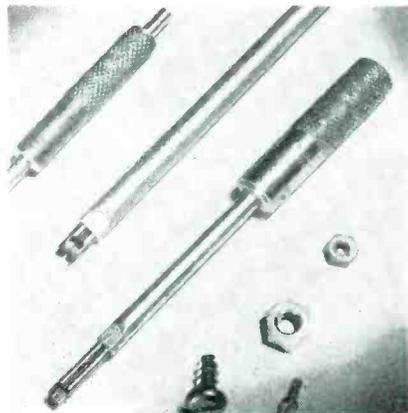

THERE ARE

QUAM
Adjust-a-Cone[®]
SPEAKERS

FOR ALL* YOUR
REPLACEMENT NEEDS



Be sure to get the latest Quam catalog, listing 94 replacement speakers—at the best distributors in every city—or write us for your FREE copy.

Quam replacement speakers are listed in Photofact Folders and in Counterfacts.

QUAM-NICHOLS CO.
232 East Marquette Road
Chicago 37, Illinois

*Quam cataloged speakers are available in any voice coil impedance and field resistance.

Manufacturers of

High Fidelity
Speakers

Outdoor Theatre
Speakers

Quam Focalizer
Units

Tru-Match Output
Transformers

Quam Ion Traps

XCELITE SCREWHOLDER

A screwholding device, that is claimed to have sufficient holding power to start and loosen screws even when they are too small for the screwdriver, and fits any round-bladed screwdriver in its range, has been developed by Xcelite, Inc., Dept. V, Orchard Park, N. Y. Tool slips up and out of the way when not in use.

Screwholder features wedge-grip tempered spring steel holders that prevent dropping of screws. Available in 3/16".



INTERNATIONAL INSTRUMENTS MINIATURE MULTITESTER

A miniature multitester combination volt-ohmmeter, for testing resistances and *ac* or *dc* voltages, has been announced by *International Instruments, Inc.*, P.O. Box 2954, New Haven 15, Conn.

Tester, which is 4 1/4" x 3" x 1 1/2", has four *dc* voltage ranges reading to 300 *v*, four *ac* voltage ranges reading to 600 *v*, and four resistance ranges reading to 2,000,000 ohms. A sensitivity of 10,000 ohms-per-volt with accuracy of $\pm 2\%$ of full-scale deflection for *dc* voltages is claimed and for *ac* voltages, a sensitivity of 8,000 ohms-per-volt with accuracy of $\pm 5\%$ of full-scale deflection. Power for resistance measurements comes from self-contained batteries.



"Nothing bothers Tom since he's switched to using G-E radio dial lamps"

You'll feel like passing out cigars, too, when you change over to General Electric dial lamps. Hundreds of laboratory tests assure dependable lamp performance, longer lamp life, fewer early burnouts. General Electric radio dial lamps won't cause annoying static. Always give your customers the best . . . always give them G-E.



GENERAL  ELECTRIC

Coming Event

**Radio Engineering Show . . .
Kingsbridge Armory, Bronx, N.Y.C.
March 22, 23, 24 and 25, 1954**

**DON'T LET 'EM GET
OVERLOADED!**

**GET 'EM Vidaire
TEL★ATTEN**



- Eliminates overloading due to strong signals
- Reduces buzz in intercarrier sets
- 1000 to 1 change in signal reaching antenna posts
- Vernier adjustment for all signal areas
- Simple installation, connects with only 3 leads

*Sold only through
authorized
VIDAIRE distributors
send for catalog A*

Vidaire ELECTRONICS MFG., CO. 


Manufacturers of:
TV COLOR EQUIPMENT • TV AMPLIFIERS • ELECTRONIC DEVICES
Factory: LYNBROOK, N. Y. Nat'l. Sales Office: 6 EAST 39th ST., NEW YORK 16, N. Y. Phone No.: LE 2-7372

TV Stations

(Continued from page 64)

City	Call Letters	Channel
TEXAS		
	KLIF	Trinity Bcstg Corp., 2104 Jackson St. 29
	WFAA-TV	A. H. Belo Corp., Young & Houston Streets 8½
El Paso	KROD-TV	Roderick Bcstg Corp., Wyo. & Walnut Sts. 4*
	KTSM-TV	Tri-State Bcstg Co., Inc., 801 N. Oregon St. 9*
	KEPO-TV	KEPO, Inc., 706 Capital Nat'l Bank Bldg., Austin 13
Fort Worth	WBAP-TV	Carter Publications Inc., 400 W. 7th St. 5½
	KTCO	Tarrant County Tele. Co., 1101 W. 7th 20
Galveston	Rudman Tele. Co., c/o M. E. Rudman 41
	KGUL-TV	Gulf Tele. Co., 801 Union Station Bldg. 11*
Harlingen	KGBS-TV	The Magic Triangle Televisors, Inc., Box 711 4
Houston	KPRC-TV	Houston Post Co., 2318 Polk Ave. 2½
	KTVP	UHF Tele. Co., Magnolia Bldg., Dallas 23
	KNUZ-TV	KNUZ Tele. Co., Box 2135 39
	KXYZ-TV	Shamrock Bcstg Co., Gulf Bldg. 29
Longview	KTVE	E. Texas Tele. c/o James Henry, Rt. 3 32
Lubbock	KFYO-TV	Plains Radio Bcstg Co., 914 Ave. J 5
	KLBD-TV	Bryant Radio & Tele. Inc., 1805 Broadway 11*
	KBUD-TV	Texas Telecstg Inc., 3601 Ave. H 13*
Lufkin	KTRE-TV	Forest Capital Bcstg Co., Box 701 9
Marshall	Marshall Tele. Corp., 270 Park Ave., New York 17, N. Y. 16
San Angelo	KTXL-TV	Westex Tele. Co., 1901 W. Bureau-gard St. 8
San Antonio	KEYL	San Antonio Tele. Co., Transit Tower Bldg. 5½
	WOAI-TV	Southland Industries, Inc., 1031 Navarro St. 4½
	Alamo Tele. Co., Kirby Bldg. 35
Sherman	KSHM	Sherman Tele. Co., Life of America Bldg., Dallas, Tex. 46
Temple	KCEN-TV	Bell Publishing Co., Box 419 6
Tyler	KETX	Jacob A. Newborn, Jr., Box 1572, Beaumont, Tex. 19
Texarkana	KCMC-TV	KCMC, Inc., 317 Pine St. 6
Victoria	KNAL-TV	KNAL-Tele. Co., Victoria Band & Trust Bldg. 19
Waco	KANG-TV	Central Texas c/o Clyde Weatherby 34
Wichita Falls	KTVW	White Tele. Co., 1507 Lamar 22
	KFDX-TV	Wichita Radio & Tele. Co., 801 Scott St., City Nat'l Bank Bldg. 3*
	KWFT-TV	Wichita Falls, Tele. Inc., c/o Kenyon Brown, Box 420 6*
UTAH		
Salt Lake City	KDYL-TV	TLF Bcstg Corp., 143 S. Main St. 4½
	KSL-TV	Radio Service Corp. of Utah, 10 S. Main St. 5½
	KUTV	Utah Bcstg & Tele. Corp., 29 S. State St. 2
VIRGINIA		
Charlottesville	WCHV-TV	Barham & Barham, Box 631 64
Danville	WBIM-TV	Piedmont Bcstg Corp., Hotel Danville 24

City	Letters Call	Channel
VIRGINIA		
Harrisonburg	WSAV-TV	Shenandoah Valley Bcstg Corp., Rawley Pike 3
Lynchburg	WWOD-TV	Old Dominion Bcstg Corp., Box 918 16
	WLVA-TV	Lynchburg Bcstg Corp., 925 Church St. 13*
Marion	WMEV-TV	Mountain Empire Bcstg Corp., Park Blvd. 50
Newport News	WACH	Eastern Bcstg Corp., 114 24th St. 33
Norfolk	WTAR-TV	WTAR Radio Corp., 720 Boush St. 4 (3)†
Hampton (area) Norfolk	WVEC-TV	Peninsula Bcstg Corp., Box 481 15
Richmond	WTVR	Havens & Martin, Inc., 3301 W. Broad St. 6†
Roanoke	WROV-TV	Radio Roanoke, Inc., Mountain Trust Bldg. 27*
	WSLS-TV	Shenandoah Life Stations, Inc., Shenandoah Bldg., 301 1st St. S.W. 10*
WASHINGTON		
Bellingham	KVOS-TV	KVOS, Inc., 1321 Commercial St. 12*
Seattle	KING-TV	King Bcstg Co., 301 Galer St. 5†
	KOMO-TV	Fisher's Blend Stations, Inc., 100 4th Ave. N. 4
Spokane	KXLY-TV	KXLY TV, 315 W. Sprague 4*
	KHQ-TV	KHQ, Inc., 700 Radio Central Bldg. 6*
Tacoma	KTNT-TV	Tribune Publ. Co., 711 S. Helena Ave. 11*
	KMO-TV	KMO, Inc., 914½ Broadway 13
Yakima	KIMA-TV	Cascade Bcstg Co., Inc., Box 702 29
	KIT-TV	KIT, Inc., Box 1651 Tacoma 23
WEST VIRGINIA		
Beckley	Appalachian Tele. Corp., 270 Park Ave., New York, N. Y. 21
Charleston	WKNA-TV	Joe L. Smith, Jr., Inc., Main and Kanawha Sts., Beckley, W. Va. 49
Huntington	WSAZ-TV	WSAZ, Inc., 912½ 3rd Ave. 3†
Parkersburg	WTAP	W. Va. Enterprises, 309 Charleston Nat'l Bank Bldg. 15
Wheeling	WLTV	Polan Industries, 321 8th St., Huntington, W. Va. 51
.....	Tri-City Bcstg Co., Box 767, Bellaire, Ohio 7
WISCONSIN		
Beloit	WRBJ	Beloit Bcstg Co., Hotel Hilton 57
Eau Claire	WEAU-TV	Central Bcstg Co., 203 Barstow St. 13
Green Bay	WBAY-TV	Norbertine Fathers, P. O. Box 633 2*
Madison	WKOW-TV	Monona Bcstg Co., 215 W. Washington Ave. 27*
	WMTV	Bartell Tele. Corp., 710 N. Plankington Ave., Milwaukee 33
Milwaukee	WTMJ-TV	The Journal Co., 333 W. State St. 3 (4)†
	WCAN-TV	Midwest Bcstg Co., 723 N. 3rd St. 25
	WOKY-TV	Bartell Bcstrs, Inc., 710 N. Plankington Ave. 19
Neenah	WNAM-TV	Neenah-Menasha Bcstg Co., 101 E. Wis. Ave. 42
Oshkosh	WOSH-TV	Oshkosh Bcstg Co., 1235 Bowen St. 48*
WYOMING		
Casper	KSPR-TV	Donald Lewis Hathaway, Box 930 2
Cheyenne	KFBC-TV	Frontier Bcstg Co., Plains Hotel 5

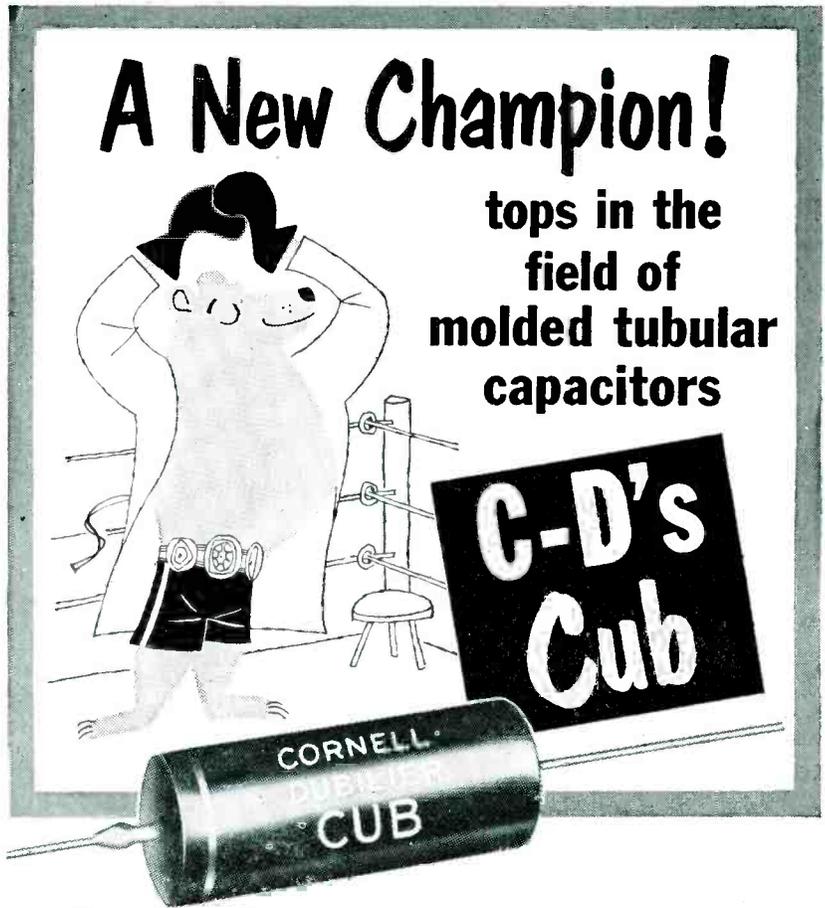

A New Champion!

tops in the field of molded tubular capacitors

C-D's Cub

- * Outperforms all other molded tubulars in humidity tests!
- * Stands up under temperatures up to 100°C.
- * Ask your C-D jobber about the special "Cub-Kit"!
- * You get more for your dollar with this premium tubular designed and built especially for replacement needs, with "better-than-the-original" performance!

For the name of your C-D distributor, see the yellow pages of your classified phone book. Write for Catalog to: Dept. S-103, Cornell-Dubilier Electric Corp., South Plainfield, N. J.

CONSISTENTLY DEPENDABLE CORNELL-DUBILIER

There are more C-D capacitors in use today than any other make.



PLANTS IN SOUTH PLAINFIELD, NEW JERSEY; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASSACHUSETTS; PROVIDENCE AND HOPE VALLEY, RHODE ISLAND; INDIANAPOLIS, INDIANA; SANFORD AND FUGUAY SPRINGS, NORTH CAROLINA. SUBSIDIARY RADIART CORPORATION, CLEVELAND, OHIO

DIAMOND NEEDLE MANUFACTURE

HAWAII		
Honolulu	KGMB-TV	Hawaiian Bcstg System, Ltd., 1534 Kapiolau Blvd. 9*
	KONA	Radio Honolulu, Ltd., P. O. Box 2727 11*
	American Bcstg Stations, Inc., Barr Bldg., Washington, D. C. 4
PUERTO RICO		
San Juan	WKAQ-TV	El Mundo Bcstg Corp., Box 1072 2

[Revisions and Additions, Next Month]

(Right)

Careful examination of needle diamonds with a binocular stereoscopic microscope. This is one of many inspections conducted in grading diamonds. (Photo courtesy Tetrad)



Tools . . . Instruments Parts . . .

ERIE CERAMIC DISC CAPACITORS

A line of ceramic disc capacitors, *K-Lok*, available in four styles, with a capacitance range from 220 to 4500 mfd. are now available from the *Erie Resistor Corp.*, Erie, Pa.

Units are said to undergo a maximum decrease in capacitance value of only 1% per decade; greatest capacitance change from 25° C value is ±5% from -55° C, to +105° C and +5%, -10% from -55° C to +125° C.

In linear circuit operation, both voltage coefficient of capacitance and piezoelectric effect are low. Life rating is up to 1000 *vdew* at 85° C and 500 *vdew* at 125° C. Other features are: power factor, 1% maximum; insulation resistance, 10,000 megohms.

* * *

NATIONAL BANANA PLUGS

A banana-type plug, *FWT*, molded of mica-filled bakelite in accordance with JAN specifications, and styled for easy gripping, is now available from the *Components Division, National Company, Inc.*, 61 Sherman St., Malden, Mass.

Leads can be brought directly from the base of the prongs or through a hole at the bottom of the plug. Top has been designed to accept additional plugs. All contacts and screws are nickel-plated brass.

* * *

RCP PEAK-TO-PEAK VTVM

A peak-to-peak *vtrm*, 655, that provides for *ac* measurements of from .2 to 4200 volts, *ac rms* measurements of .1 to 1500 *v*, *dc* measurements of from .02 to 1500 *v*, and resistance measurements of from .2 ohm to 1000 megohms, all on 7 ranges, has been announced by *Radio City Products Co., Inc.*, 152 W. 25th St., New York 1, N. Y.

Measuring circuit uses a balanced bridge-type *dc* amplifier and meter together with a high-impedance voltage divider. A 1-megohm isolation resistor provides an input impedance of 11 megohms on *dc*. An additional peak-to-peak rectifier together with compensated attenuator are used for the *ac* measurements.



WILLIAMS CLOSE-QUARTER DRILLING BIT

A drilling bit, *Close-Quarter*, for boring a hole through the upper plate of a building wall, under a hip roof, has been introduced by the *Williams Electric Co.*, 1010 S.E. 39th Ave., Portland 15, Oregon.

Bit is provided with a special head and a ratchet drive, with the entire assembly short enough, it is said, to get under the ordinary hip roof. Available in two sizes: 1" and 12/16".


* * *

INSULINE ALLIGATOR CLIP AND SCREWDRIVER COMBINATION



A fully-insulated alligator clip, designed to facilitate the testing of live circuits in TV and radio receivers, has been announced by the *Insuline Corporation of America*, 3602-35th Ave., Long Island City 1, N. Y.

Spring-loaded jaws, which are acuated by a thumb button in the body of the clip, hold on conductors up to 1/4" in diameter. Connection to the clip is made with standard banana plugs. Available in two body colors: 524B black and 524R red.

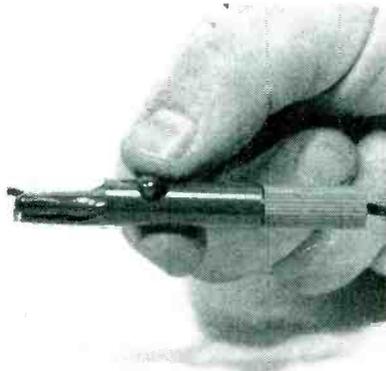A screwdriver combination, *Mini-Kit 989*, for precision work on miniaturized electronic equipment using tiny screws, has also been introduced. Consists of a swivel-top handle into which can be fitted any of four hardened steel blades measuring .100", .080", .070" and .055".



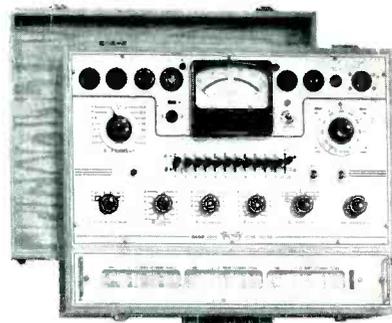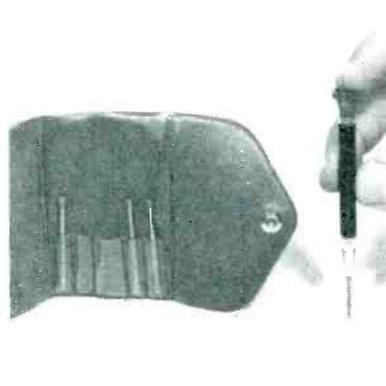Above: Insuline Alligator Clip
Below: Insuline Screwdriver Combination



TRIPLETT MUTUAL CONDUCTANCE TUBE TESTER

A mutual conductance tube tester, 3423, that tests tubes by applying a *hf* signal to the grid and measuring the signal component in the output, has been developed by the *Triplett Electrical Instrument Co.*, Bluffton, Ohio.

In the plate circuit, a high *Q* tuned circuit which responds only to 4 kc is used to extract the amplified signal. Thus, it is said, hum and ripple, and tubes with open grids, present no problem to the tester, and cannot give false readings. Tubes with widely varying characteristics can be checked, it is claimed, without overloading or other damage to the tube because of a wide selection of tube parameters.

* * *

C-D STEATITE-CASED TUBULAR CAPACITORS

Steatite-cased paper tubular capacitors, *Budroc*, available in a capacity range from .0005 to 1 mfd at voltage ratings of 200, 400, 600, 1000 and 1600 *vdew*, have been introduced by *Cornell-Dubilier Electric Corp.*, Industrial Division, 333 Hamilton Blvd., South Plainfield, N. J.

Tubular capacitor is of non-inductive construction and housed in a ceramic (steatite) tube with Polykane end seals.

* * *

MALLORY LINE VOLTAGE ADJUSTER AND ISOLATION TRANSFORMER

A line voltage adjuster and isolation transformer, *LI-12*, that provides infinitely variable *ac*-line adjustment from 90 to 130 *v* at 1200 watts; infinitely variable low voltage from 0 to 40 *v ac* at 4 amperes in the isolation position, or 0 to 40 *v ac* at 8 amperes in the common line position, and an isolated, infinitely variable 90 to 130 *v ac* output at 350 watts, is now available from *P. R. Mallory and Co. Inc.*, *Distributor Division*, P.O. Box 1558, Indianapolis, Ind.

Metal case dimensions are 7 7/8" high x 5 3/4" deep x 6 1/4" wide. Supplied with a 6' rubber-covered line cord.



Engineered for the Purpose . . .

Copperweld GUY STRAND

provides REAL GUYING CONFIDENCE

Copperweld DOESN'T STRETCH

Soft wire guys frequently stretch badly in service and go slack. This means a wobbly antenna and poor reception. Copperweld Guy Strand is hard drawn—has the strength to stay taut—holds the antenna firmly in place—improves reception.

Copperweld COMBATS RUST

A guy weakened by rust may go unnoticed until a storm brings down the antenna, causing damage many times the cost of the guy. Copperweld Guy Strand is protected against rust by a molten-welded layer of pure copper on each wire. Its strength is lasting.


SOLD BY
RECOGNIZED
PARTS DISTRIBUTORS

Copperweld is EASY TO INSTALL


No clamps or clips are needed. An ingenious serving tool—one furnished free with each standard length of strand—turns out neat, tightly wrapped dead-ends as strong and permanent as the strand itself.

Write today for further details.

COPPERWELD STEEL COMPANY
Glassport, Pa.

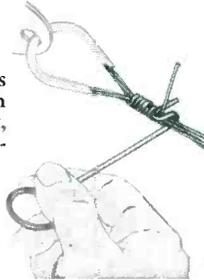

Servicemen

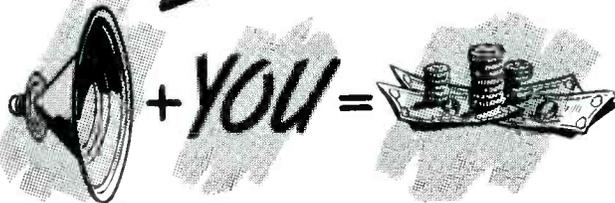

This should interest you

Reconing is Preferred . . .

WHEN exact replacement speakers are not available, reconing immediately solves mounting problems.

WHEN greater profits for you and greater savings for customers are desired.

WHEN you want quality and fidelity of performance.


Prove this to yourself!

Write to us for location of Reconing Station in your area.

**WALDOM
ELECTRONICS INC.**

909 N. Larrabee Street
Chicago 10, Illinois

NEW RMS "PRE-FAB"

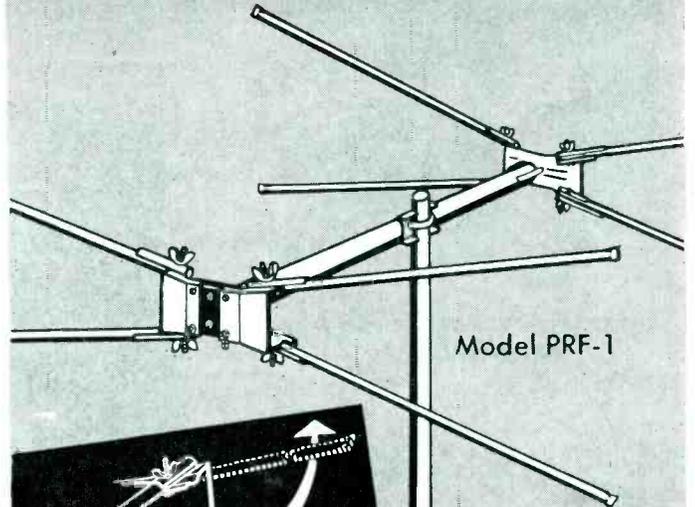

Model PRF-1



the lowest priced — most rugged
completely

PREASSEMBLED CONICAL


on the market!

This is not an economy model . . . it is virtually a deluxe 4-front-4-back conical being mass produced by RMS in such vast quantities that costs are lowered . . . not quality!

- Rugged brackets hold elements securely—are triple-thick plated.
- 3/8" aluminum elements with pinched ends.
- Standard 36" aluminum crossarm dowel-reinforced at both ends and at the U-bolt.
- Tenna-Tek for signal terminal protection with each antenna.
- Six to the carton. Available in stacked and 4-bay.

AVAILABLE ALSO WITH
STEEL CROSSARM

See your local RMS Jobber

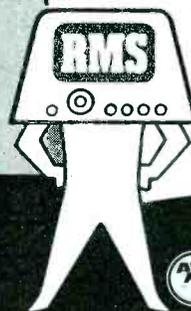

In Canada, MJS TV Accessories Co.
Mexico: Industrias Comerciales

RMS. NEW YORK 62, N. Y.

TV Parts . . . Accessories



GONSET REMOTE TUNER-BOOSTER-UHF CONVERTER

A universal TV remote control unit, which it is said may be attached to any conventional TV receiver, is now available from the *Gonset Company*, 801 South Main St., Burbank, Calif.

Featuring a Standard Coil cascade tuner ahead of a booster amplifier, unit permits channel selection from the viewing position (including volume, contrast, and fine tuning adjustments). Remote Control takes the place of both a booster and a *uhf* converter, as the turret tuner has provision for snap-in coil strips. A sound output connection is provided for headphones, to permit silent viewing. Unit is available for either 21 or 40 mc if.

LION MOBILE TV CART

A mobile cart, for use with a remote control TV set, has been designed by the *Lion Manufacturing Corp.*, 2640 West Belmont Ave., Chicago, Ill.



TV cart facilitates the movement of the set from room to room.

HICKOK 5-INCH 'SCOPE

A 5" 'scope, 665, with a frequency range from .5 cycle to 700 kc, down 3 db has been announced by *The Hickok Electrical Instrument Co.*, 10521 Dupont Ave., Cleveland 8, Ohio.

Instrument is said to have no drift, less than 1% tilt, and less than 2% overshoot; accelerating potential is 1775 v. power consumption 35 watts. Square wave response is claimed to be flat from 60 cps to 100 kc.

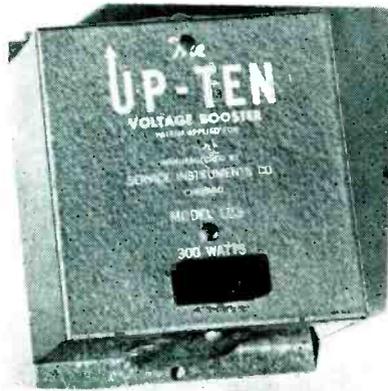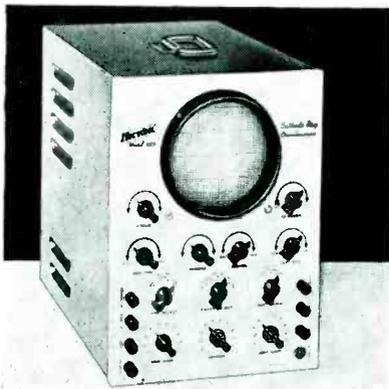A feature of the 'scope is a fusing arrangement for the *B+* line; a dual fuse is provided so that the *B+* line is entirely fused. 'Scope has been designed with push-pull amplifiers with a vertical sensitivity of .020 millivolt per inch; horizontal sensitivity is .030 millivolt per inch. Vertical input impedance is 15 mmfd, 2.2 megohms; horizontal impedance, 52 mmfd, .1 megohm.



SERVICE INSTRUMENTS 10-VOLT LINE BOOSTER

A voltage booster, *Up-Ten*, designed to add ten volts to the existing line voltage when used with TV set or electrical appliance, up to 300 watts, is available from *Service Instruments Co.*, 422 S. Dearborn St., Chicago, Ill.

RAM VERTICAL SWEEP COMPONENTS


Twelve types of vertical scanning output transformers and five vertical blocking oscillator transformers, have been added to the line of Ram flyback transformers.

Available in five basic mountings. Further details available from *Ram Electronics Sales Co.*, Irvington-on-Hudson, N.Y.

MAGNE-PULSE INTERMITTENT RECORDER

An intermittent recorder, 202, that is said to be capable of automatically detecting and locating intermittent troubles, has been developed by *Magne-Pulse Corp.*, 140 Nassau St., New York 38, N. Y.

Instrument consists, in effect, of three *vtoms* which monitor as many as three separate voltages in a chassis. With the set operating normally, each of the three voltages being monitored are *zero set* in the recorder so that meter pointer is at 0 for all three circuits. If any of the three voltages deviates beyond preset limits from the normal value, the voltage change is detected by the associated *vtom*, a relay is actuated causing the appropriate lamp to light and a buzzer is sounded.

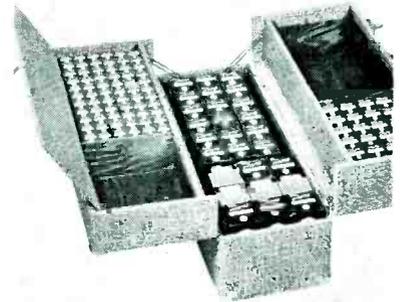

ARGOS CARRY-ALL TUBE CADDY

A carrying case, *Carry-all Tube Caddy*, that opens from the top in spread eagle fashion, has been announced by *Argos Products Co.*, Genoa, Ill.


Tube caddy can carry up to 262 receiving-type tubes in the various sizes normally needed. Compartments are said to be large enough to accommodate a soldering gun, meter, or other equipment. Size: 21" x 15" x 8".


[See page 104 for additional new product news]

E-M RF-AF-CRYSTAL MARKER-TV BAR GENERATOR

A *rf-af* crystal marker-TV bar generator, 700, that is said to provide complete coverage from 18 cycles to 108 mc on fundamentals, has been introduced by the *Electronic Measurements Corp.*, 280 Lafayette St., New York, N. Y.

Unit provides a bar generator for TV adjustment with a variable number of bars available for horizontal or vertical alignment. Included is a Wien-bridge *af* oscillator with sinewave output from 18 cycles to 300-kc, and crystal marker and amplitude control. Other features include individually tuned coils, constant *rf* output impedance, stepped *rf* attenuator, electrostatically shielded transformer, Colpitts *rf* oscillator from 300 kc to 108 mc on fundamentals; up to 216 mc on second harmonic and variable percentage of modulation.

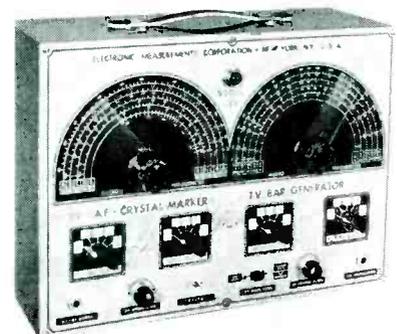

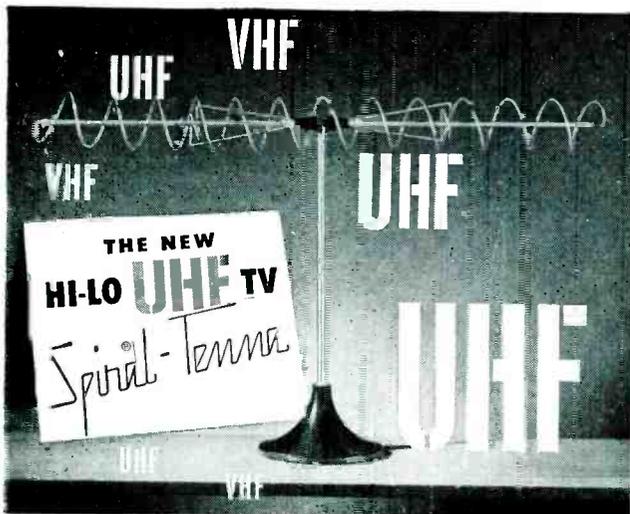

Peak Performance for Indoor UHF and VHF Television Reception

Now — the nationally advertised, consumer accepted HI-LO TV Indoor Spiral-Tenna is applicable for both VHF and UHF with our exclusive UHF antenna adapter from channels 2-83. But, you still get the volume by selling at the same low, low price.

The Hi-Lo UHF antenna adapter is available separately for all previous HI-LO antennas. List Price \$2.00.

at the same low list price!

U. S. Patent No. 2,495,579 Canadian patents 1951 — other patents pending

ORDER HI-LO UHF-VHF TV Spiral-Tenna TODAY!

Hi-Lo TV ANTENNA CORP.
3540 N. Ravenswood • Chicago, 13, Illinois

\$9.95
LIST PRICE

Replace with



SELETRON RECTIFIERS




and be safe!

No arc-over, short circuits or excessive heating when you replace with SELETRON. Proof? Millions are giving top performance as original equipment in many famous make radio and TV sets right now! See H. W. Sam's Red Book Supplement listing SELETRON selenium rectifier replacements. Write us for the name of our nearest jobber.



Seletron and Germanium Division
RADIO RECEPTOR COMPANY, INC.
Since 1922 in Radio & Electronics
Sales Dept.: 251 West 19th Street, New York 11
Factories in Brooklyn, N. Y.

Compare...
prove EMC superiority

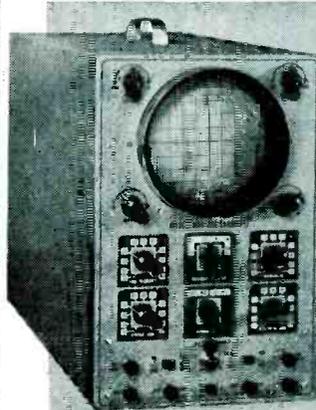

model 600

EMC MODEL 600 SCOPE features the use of a 5U1 new 5 inch scope tube. The 2-stage, push pull, vertical amplifier has a sensitivity of .02 volts per inch and can be used up to 5 megacycles. A two step attenuator input is available. Synchronization is available on either positive or negative phase of input voltage through the vertical amplifier or from an external source. A multi-vibrator type of sweep from 15 cycles to 75 kilocycles is incorporated. Direct connections to scope plate available.

MODEL 600 (completely wired and tested)..... **\$99.50**

model 106
VACUUM TUBE VOLTMETER

Check these features
SPECIFICATIONS



All functions completely electronic — meter cannot burn out.
DC VOLTAGE: Input resistance 16.5 megohms or 1 1/2 megohms per volt. Ranges 0 to 1.5, 10, 100, 300, 1000 up to 30,000 volts (with accessory probe).
AC VOLTAGE: Input resistance 2 megohms. Ranges 0 to 1.5, 10, 100, 300, 1000. Frequency response flat from: 25-100,000 cycles.
OHMS: 1000 — 10,000 — 100,000 — 10 megohms, 1000 megohms.
COMPACT, portable bakelite case measures 4 1/4 x 5 1/4 x 2 3/8"

- MODEL 106 (complete with 1 meg isolating probe) **\$35.90**
- IN KIT FORM **23.90**
- MODEL HVP, 30,000 Volt Probe for Model 106 **8.75**
- MODEL RFP, High Frequency Probe (useful to 200 megacycles) **6.95**

— See them at your Jobbers —



Write Dept. S-10
for free complete catalogue
of these and
other instruments.

ELECTRONIC MEASUREMENTS CORPORATION
280 LAFAYETTE STREET • NEW YORK 12, N. Y.

EXPORT DEPARTMENT 136 LIBERTY STREET, N. Y. C. 6, N. Y.

SERVICE, OCTOBER, 1953 • 103

Years in business. No. of mechanics employed.

84 Withers Street, Brooklyn 11, N. Y.

SERVICE, OCTOBER, 1953 • 105

using a single 6SC7.

and TV Service Men, displayed by G.E.'s
Addie Chandler.

4055 Redwood Ave., Venice, Calif.

SERVICE, OCTOBER, 1953 • 107

Ren Talk

Sales Co., 530 Gough St., San Francisco, Calif. (northern California and Nevada).



! NOW VIKING SELLS DIRECT!

"THERE'S NO SALE LIKE WHOLESALE"

70% TO 90% OFF LIST

VEE

BOXED—BRANDED—
FULLY GUARANTEED

TUBES

1B3	\$.63	6BA6	\$.45	12AT6	\$.48
1R5	.56	6BC5	.53	12AT7	.68
1S4	.61	6BE6	.46	12AU6	.43
1S5	.47	6BG6	1.34	12AU7	.53
1T4	.56	6BJ6	.48	12AV6	.37
1U4	.55	6BK7	.88	12AV7	.79
1U5	.46	6BQ6	.89	12BA6	.45
1X2	.67	6BQ7	.98	12BE6	.47
3Q4	.60	6C4	.37	12BH7	.63
3Q5	.65	6CB6	.53	12SA7	.52
3S4	.55	6CD6	1.85	12SK7	.50
3V4	.56	6J5	.40	12SN7	.54
5U4	.40	6J6	.62	12SQ7	.42
5V4	.73	6K6	.41	19BG6	1.39
5Y3	.29	6S4	.46	25BQ6	.89
6AB4	.46	6SA7	.52	25L6	.48
6AC7	.75	6SK7	.50	25W4	.48
6AG5	.54	6SN7	.54	25Z6	.42
6AK5	.95	6SQ7	.42	35L6	.47
6AL5	.40	6T8	.77	35W4	.30
6AQ5	.46	6V6	.46	35Z3	.18
6AT6	.38	6W4	.45	35Z5	.30
6AU5	.78	6W6	.57	50B5	.47
6AV6	.43	6X4	.34	50C5	.47
6AV6	.78	6X5	.33	50L6	.47
6AV6	.37			117Z3	.39

All Orders sent C.O.D. plus Postage.
Quantities limited. Minimum order \$5.
Prices subject to change.


ORDERS SHIPPED PREPAID
IF CHECK IS ENCLOSED.



VIKING ELECTRONICS CORP

112-07 FRANCIS LEWIS BOULEVARD, Dept. S-10
QUEENS VILLAGE 29, N. Y.

NEW!

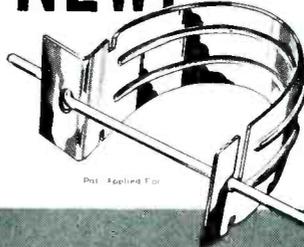

**LOK-ON MAST
STANDOFF**

BY **IE**
MANUFACTURING

**SNAPS-ON!
LOKS-ON!**

Won't walk!
Won't twist!
Won't rotate!

New improved LOK-ON STAND-OFF snaps on without effort, remains secure under severest conditions. By forming the final enclosure about the diameter of the mast, the standoff wire acts as a positive locking device and together with IE's "snapback" ribbed clamp and raised edge construction eliminates "walking", "twisting" and "rotating."

Available in three sizes:

- No. 1214 1" masts
- No. 1215 1 1/4" masts
- No. 1216 1 1/2" masts



Full details described in new IE catalog No. 16. Send for your free copy!

SPECIFY IE STANDOFF INSERTS FOR ALL YOUR LEAD-IN REQUIREMENTS

FLAT-LINE

Designed for All VHF installations and the new open line.

LARGE CO-AX
Made specifically to carry the large round lead-in.

NEW! UNIVERSAL UHF-VHF INSERT

The most versatile insert made. Designed to carry the tubular cable, small oval, large oval, anaronda and 300 ohm line.

325 NORTH HOYNE AVE., CHICAGO 12, ILL.
ANTENNAS • MOUNTS • ACCESSORIES

ROBERT S. WINDT, formerly vice president of David O. Alber Associates, has been appointed publicity and promotion manager for CBS-Columbia Inc. He will make his headquarters at 3400-47th Ave., Long Island City, N. Y.

ALFRED E. BOURASSA, formerly assistant advertising manager of Carter's Ink Co., has been appointed assistant to the advertising manager of CBS-Hytron, Danvers, Mass.

PAUL G. MATHES is now advertising manager of Trio Manufacturing Co., Griggsville, Ill.



Paul G. Mathes



Robert A. Elliot

ROBERT A. ELLIOT is now manager of the distributor sales division for Erie Resistor Corp., Erie, Pa.

PERSONNEL



W. O. SPINK is now assistant equipment sales manager of the electronic product sales department of Sylvania Electric Products Inc.

M. L. FINNEBURGH has become vice president of The Finney Co., 4612 St. Clair Ave., Cleveland, O., joining his brother, L. H. Finneburgh, Jr., president of the firm. Finneburgh recently retired as general sales manager of the Liquid Carbonic Corp.



M. L. Finneburgh



Larry H. Kline

LARRY H. KLINE has been named general sales and merchandise manager of the Ward Products Co., Division of The Gabriel Co., 1148 Euclid Ave., Cleveland, Ohio.

K. L. BISHOP has been named general sales manager of V-M Corp.

ELWOOD W. SCHAFER, former vice president of the National Union Radio Corp., has been named assistant to Charles F. Stromeyer, CBS-Hytron vice president in charge of manufacturing and engineering.

STANLEY NICIEJEWSKI has been appointed sales manager of the rectifier division of Sarkes Tarzian, Inc.

ALFRED D'URSO is now assistant sales manager of distributor sales at Sarkes Tarzian, Inc.

JOE STARR has been appointed assistant sales manager, manufacturers division, of the Pyramid Electric Co., North Bergen, N. J.




Sheldon Rutter



Joe Starr

SHELDON RUTTER, Evanston, Ill., has been retained by the Channel Master Corp., Ellenville, N. Y., to create all product design, and to serve as packaging and art consultant.

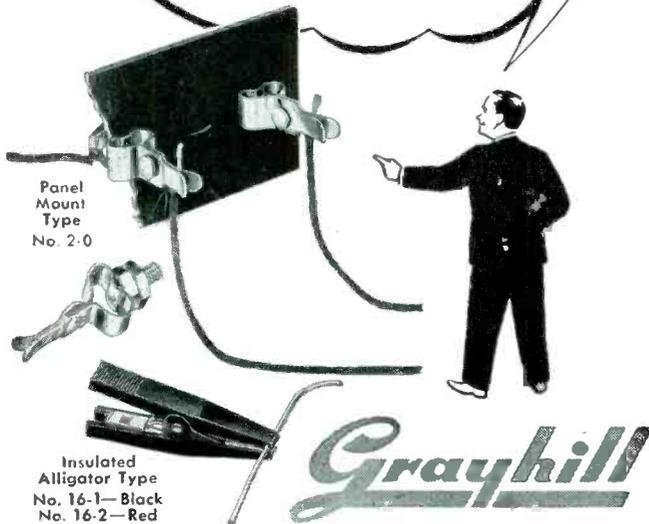
THERE IS NO FASTER OR BETTER WAY TO MAKE TEST CONNECTIONS THAN OFFERED BY THE SIMPLIFIED GRAYHILL PANEL MOUNT, SPRING PRONG CLIP AND THE GRAYHILL FULLY INSULATED, TIGHT-GRIP TEST CLIP.



533 Hillgrove Ave., La Grange, Ill.
Phone: La Grange 8000

Antenna of the Year? **SCREWBALL!**

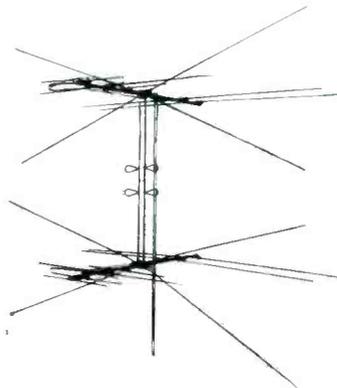Something **NEW** has been added by **FRETCO**



DID YOU EVER SEE ONE?

The prize taking performance of the Screwball has made it the antenna of the year. There is only one Screwball, and it answers all the problems of UHF and VHF long distance reception. This antenna is medium priced and gives more gain per dollar than any other antenna except the Fretaray. The Screwball is a perfect match to any type of lead-in but let us recommend that Soucerline be used for outstanding results.



INCORPORATED
406 N. Craig St., Pgh. 13, Pa.
PATENT PENDING

CHRISTIAN J. REIMULLER, formerly vice president in charge of engineering and sales at the Studebaker plant in Maywood, Ill., has been named publicity-public relations head of Javex, Redlands, Calif.

* * *

G. MILTON EHLERS is now chief research engineer of the Aerovox Corp., New Bedford, Mass.

* * *

HAROLD BLUMENTHAL has been appointed sales manager, manufacturers division, for Shure Brothers, Inc., Chicago, Ill.

* * *

COMMANDER R. H. G. MATHEWS, formerly general sales manager of the Honan-Crane Corp., has been named executive vice president of Burton Browne Advertising, Chicago, Ill.



Jerry B. Minter



R. H. G. Mathews

JERRY B. MINTER, vice president, Measurement Corp., Boonton, N. J., and president, Components Corp., Denville, N. J. has been elected president of the Audio Engineering Society.

A. L. CHAMPIGNY has been appointed manager of advertising and sales promotion for the General Electric tube department. . . . G. A. BRADFORD, former manager, has been named manager of advertising and sales promotion for the G.E. radio and TV department.

* * *

C. J. STEVENS has been appointed sales coordinator for the jobber sales division of the V-M Corp.



Richard L. Grose (right), sales and ad manager of V-M, and C. J. Stevens, recently appointed sales coordinator for jobber sales at V-M.

J. C. VAN ARSDELL, formerly manager of sales engineering, electronics division, has been appointed assistant general manager of the division, at Erie Resistor Corp. . . . WILLIAMS KLEVANS, field sales engineer, has been promoted to manager of sales engineering, succeeding Van Arsdell. . . . WILLIAM J. WERVEY succeeds Klevans as electronics sales rep in Indiana and southern Ohio. . . . MALCOLM YOUNG, formerly manager of quality control, has been made assistant general manager of the plastics division. . . . RALPH L. HATHAWAY has been promoted from superintendent to works manager of the electronics division. . . . PHILIP B. EHRMAN has been named assistant superintendent. . . . HORACE S. HERRICK is now manager of quality control, electronics division.

* * *




Joseph H. Morin

JOSEPH H. MORIN, who was distributor sales manager of Shure Brothers, Inc., has been named sales promotion manager of Howard W. Sams, Inc., Indianapolis, Inc.

It's Here! It's New!

ELECTROX BATTERY ELIMINATOR

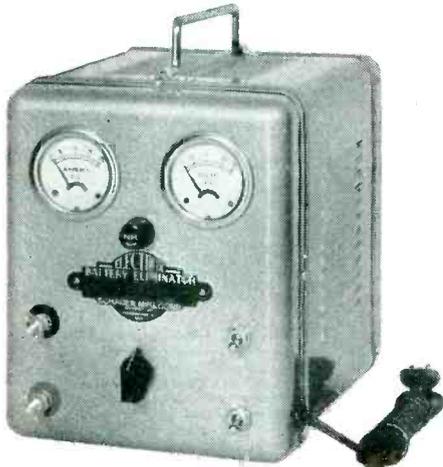For Servicing Both
6 and 12 VOLT AUTO RADIOS



MODEL AR 56-12

**Quality Built Throughout
Outstanding Value at \$52.50**

Service both 6 and 12 Volt auto radios with this one, dependable power source. Electrox Model AR-56-12 provides amply filtered, adjustable D.C. that will operate any type and size auto radio, either push-button or manually tuned.

OUTPUT: Low range: 7½ volts at 12 amps., continuous; 20 amps., intermittent. High range: 15 volts at 6 amps., continuous; 11 amps., intermittent. High and low range controlled by selector switch.

Built of quality components throughout. Selenium rectifiers. Equipped with accurate 0-20 V. and 0-20 A. meters.

ALSO AVAILABLE: Model AR 46-12, only \$41.50. Built to same quality standards as AR 56-12. Output not adjustable. Equipped with high-low switch to change from nominal 6-volt to nominal 12-volt power.

SEE YOUR ELECTROX JOBBER OR
WRITE FOR FULL DETAILS

Rectifier Division
SCHAUER MANUFACTURING CORP.
4512 Alpine Ave. Cincinnati 36, Ohio

CARBON-TET

Finest Cleaner for Electrical Parts

1. Quickly removes oil, grease, tar and other soils from electrical parts!
2. Safe, Won't burn! Won't explode!
3. Won't harm finest surface or finish!
4. Dries instantly—no odor or residue!
5. Economical for cleaning sliding contacts, condenser plates and chassis. Also as a wash for carbon deposits.

In gal. cans, qt. cans, 8-oz. bottles.
Order from your jobber.



THE KERDEN CHEMICAL CO.
5717 WALWORTH AVENUE • CLEVELAND 2, OHIO

On Book Row

TELEVISION FUNDAMENTALS: THEORY, CIRCUITS AND SERVICING. . . . BY KENNETH FOWLER AND HAROLD B. LIPPERT: An excellent discourse on the basic principles that should be known by Service Men who install and service TV chassis. Book describes each of the elements of the receiver system—from the antenna to the picture tube—leading to the more complex circuitry and theory of television. Treatment omits the use of mathematical and engineering analyses. Includes practical installation procedure for receivers and antennas, detailing how to make up antennas for varying receiving conditions, and how to use typical test equipment, and troubleshoot TV receivers by picture analysis.—524 pages, priced at \$7.00; McGraw-Hill Book Co., Inc., 330 W. 42nd St., New York 36, N. Y.

MOST-OFTEN-NEEDED 1953 RADIO DIAGRAMS AND SERVICING INFORMATION. . . . COMPILED BY M. N. BEITMAN: Volume 13, this service manual includes material on home and auto sets, portables, clock radios, combinations and automatic changers. Accompanying schematics are voltage data, alignment procedures, tube and trimmer locations, service hints and parts lists.—192 pages, 8½" x 10½", paper bound, priced at \$2.50; Submic Publications, 3727 W. 13th St., Chicago 23, Ill.

TELEVISION AND FM RECEIVER SERVICING (THIRD EDITION). . . . BY MILTON S. KIVER: A revised edition, this text includes information on alignment and servicing instructions, cascade tuners, keyed *agc* systems, keyed sync separators, direct-drive horizontal output systems, vertical retrace suppression circuits, *uhf* TV, reducing and eliminating interference, test instruments, integrated system of coordinating troubles with circuits, and locating defects in horizontal *afc* systems.—320 pages, 8½" x 11" paper bound, priced at \$4.20; D. Van Nostrand Co., Inc., 250-4th Ave., New York 3, N. Y.

UHF TELEVISION ANTENNAS AND CONVERTERS. . . . BY ALLEN LYTEL: Book covers *uhf* TV antennas, transmission lines, converters and tuners. Diagrams, performance charts and photographs of all types of *uhf* TV antennas now on the market are included. Described are assorted types of transmission lines, their application and operation; analysis revolves about use of lines as antenna lead-in and circuit element. UHF TV converter circuits are broken down stage by stage with schematics, and the purpose, function and layout of each stage is discussed. UHF all-channel tuners are also described.—128 pages, paper binding; John F. Rider Publisher, Inc., 480 Canal St., New York 13, N. Y.

NARDA TV BLUE BOOK: A 1954 edition, book features suggested trade-in values on over 4000 TV sets produced since '46, the products of over 50 manufacturers. Also featured are reports on the market in '54, selling in '54 and the servicing and selling of trade-ins.—Priced at \$5.00; National Appliance Trade-In Guide Co., 2132 Fordem Ave., Madison 1, Wis.



Introducing The New HUSH Jr. KIT SERVICER

The Amazing, New
TV-Tuner Cleaner
That Sprays On!

The new, "handy" size for TV and Radio Service Men to pack right along in their tube kits. So convenient on home service calls.

HUSH Jr. KIT SERVICER—\$1.25
2-ounce bottle, complete with 24 karat gold plate spray attachment.
8-ounce refill bottle only \$1.95


HUSH is made by the manufacturers of EVER QUIET—for volume controls—contact restorer.

EVER KLEER—for cleaning and keeping TV tubes clean.

Ask your local distributor for HUSH or write:

**CHEMICAL ELECTRONIC
ENGINEERING, INC.**
283 Main St. Matawan, N. J.

THE NEW TV DYNATRACER

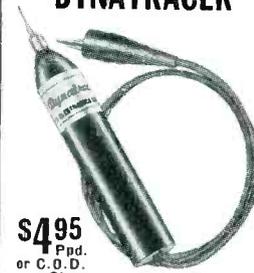

\$4.95
4 Ppd.
or C.O.D.
+ Chgs.

TRACES TV
SIGNALS AND
VOLTAGES

LOCATES
DEFECTIVE
COMPONENTS
INSTANTLY

REQUIRES NO
ADDITIONAL
EQUIPMENT

Makes Television
Servicing Easier,
Faster and
More Accurate
—AT LOW COST

Ideal for trouble-shooting television in the field or on the bench. Used under actual operating conditions, will out-perform more expensive testers.

A MUST FOR EVERY ALERT TV TECHNICIAN!
SPECIFICATIONS: The "DYNATRACER" is a self-powered quality instrument designed to trace TV signals through any Video, Sound, Sync, AFC or Vertical and Horizontal Sweep Circuit—will isolate trouble to a stage or component.

ADDED FEATURE: The "DYNATRACER" will also trace voltages and instantly locate open, shorted or intermittent condensers, resistors, coils, speakers, transformers, etc.

**COMPLETE INSTRUCTION BOOK ENCLOSED
10-DAY MONEY BACK GUARANTEE**
Clip adv., write name and address in margin, attach \$5.00 Bill, Check or M. O. and mail to

Century ELECTRONICS CO.


8509-21st Ave., Dept. 302, Brooklyn 14, N. Y.

Every issue of **SERVICE** features top technical coverage on every phase of radio, TV and electronic servicing . . . vital information for Service Men every month!

JOTS AND FLASHES

THERE ARE MORE electronic tubes in every TV-radio home than electric light bulbs, according to a recent survey. Specifically, it was reported that the average TV home has 21.5 tubes in the TV set, plus 9.5 more in radios or 31 tubes, in contrast to an estimate of 19.5 light bulbs in the average home. Even in total numbers in all homes, it was noted that the tubes come out ahead. It was estimated that the total number of home light bulbs add up to 905 million, and the total of home tubes at 964 million. . . . Top award of \$2,500 in the G. E. tube department's *Write Your Own Ticket* contest for radio and TV Service Men will go to *George Champlin*, 106-B N. Tower, Centralia, Wash. Four \$500 winners are: *Albert N. Giddis*, 145 Bellevue St., Lowell, Mass.; *Russell A. Vogt*, 16930 Plymouth, Detroit, Mich.; *Ben Chew*, 2205 S. Carmona, Los Angeles, Calif., and *Thomas Radio and Electric*, 208 Oley St., Reading, Pa. . . . A West Coast office has been opened by the Radio-Electronics-Television Manufacturers Association. Office is

located in the Ambassador Hotel, Los Angeles; telephone number is Dunkirk 5-2179. *Joseph J. Peterson* will serve as manager of the office. . . . Opening of the first class of the pilot training course for TV Service Men sponsored by RETMA at the New York Trade School, featured talks by *Harold J. Schulman*, chairman of the RETMA Service Committee and service manager of the Allen B. DuMont Laboratories, Inc., *John F. Rider*, chairman of the local industry advisory committee to the New York Trade School, and *G. E. McLaughlin*, superintendent of the New York Trade School. . . . *Dr. William L. Everett*, Dean of the College of Engineering, University of Illinois, has been named the recipient of the IRE Medal of Honor for 1954. . . . *Brociner Electronics Lab* are now located at 344 East 32nd Street, N. Y. 16. . . . A carload of Raytheon picture tubes were delivered to Allied Radio recently, coincident with the opening of Allied's new home in Chicago. . . . *Javex*, Box 646, Redlands, Calif., has released an 8-page catalog, 252, describing 28 new electronic items.

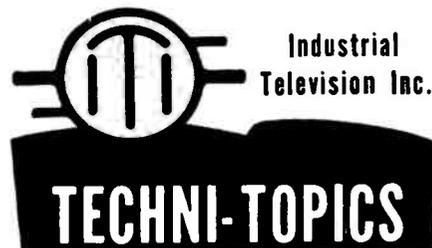

By WALTER V. TYMINSKI

AN EVALUATION OF PASSIVE TELEVISION RECEIVER COUPLERS

The general characteristics of two set couplers were discussed in parts one and two. Included in this evaluation were resistive decouplers, the IT-117A transmission line coupler, the IT-131A VHF transformer coupler, and the IT-135A UHF wide band hybrid ring coupler.

PART III

The techniques developed for two set couplers are also applicable for signal distribution to a greater number of receivers. For example, all I.T.I. two set couplers can be used to feed additional couplers, with the number of couplers limited only by the signal strength and sensitivity of the receivers.

For resistive decouplers, using a resistive terminated transmission line, the lead-in is tapped with an additional center unit for each receiver. If four receivers were operated in this manner the system would have the following characteristics:

Loss Ant. to Set = 14.3db (P/27)
Loss Set to Set = 24.6db (P/288)
Directivity = 10.3db (11)
Freq. Range = VHF and UHF

If the terminating resistor is omitted the performance becomes:

Loss Ant. to Set = 11.1db (P/13)
Loss Set to Set = 21.5db (P/140)
Directivity = 10.2db (11)
Freq. Range = VHF and UHF

Since the use of several units results in a relatively high cost, even four resistive couplers list at approx. \$8.00. I.T.I. has developed four set couplers featuring good performance at low cost.

The IT-118A Four Set AutoCoupler utilizes the same transmission line principles found in the IT-117A Two Set AutoCoupler. However, in the IT-118A two 300 ohm TV receivers are connected in parallel to terminate the 150 ohm lumped transmission lines. The characteristics of this arrangement are:

Loss Ant. to Set = 6.0db (P/4)
Min. Loss Set to Set = 12.0db (P/16)
Min. Directivity = 6.0db (4.0)
Freq. Range = VHF

If, for comparison to the resistive decoupler arrangement, 8.5db pads are used at each of the outputs, the characteristics become:

Loss Ant. to Set = 14.5db (P/28)
Min. Loss Set to Set = 29.0db (P/790)
Min. Directivity = 14.5db (28)
Freq. Range = VHF and UHF

(To be continued)



Industrial Television, Inc.
369 LEXINGTON AVENUE CLIFTON, N. J.
Gregory 3-9000

ADVERTISERS IN SERVICE, OCTOBER, 1953

Admiral Corp.	19	LaPointe Electronics Inc. (VEE-D-X)	11
All Channel Antenna Corp.	91	Leader Electronics, Inc.	65
Allied Radio Corp.	86	Leotone Radio Corp.	9.
American Phenolic Corp.	60	Littlefuse, Inc.	18
American Television & Radio Co.	77	P. R. Mallory & Co., Inc. Inside Back Cover	
Argos Products Co., Inc.	3	Merit Coil & Transformer Corp.	72
Astron Corp.	1	Mosley Electronics	82
Atlas Sound Corp.	86	Ohmite Manufacturing Co.	76
Audit Bureau of Circulations	22	Philco Corp.	8
Baker Mfg. Co.	21	Quam-Nichols Co.	97
Blonder-Tongue Laboratories, Inc.	63	Rad-El-Co Mfg. Co.	92
Busmann Mfg. Co.	12	The Radiart Corp. Inside Front Cover	
CBS-Hytron (Div. Columbia Broadcasting System)	9, 55	Radio City Products Co., Inc.	11.
Centralab (Div. Globe-Union, Inc.)	20	Radio Corporation of America	
Century Electronics Co.	110	Radio Merchandise Sales, Inc. 25, Back Cover	
Channel Master Corp.	40, 41	Radio Receptor Co., Inc.	103
Chemical Electronic Engineering Co.	110	Raytheon Mfg. Co.	23
H. G. Cisin	94	Regency Div., I.D.E.A., Inc.	17
Columbia Wire & Supply Co.	82	John F. Rider Publisher, Inc.	84
Continental Carbon, Inc.	96	Howard W. Sams & Co., Inc.	90
Copperweld Steel Co.	101	Sangamo Electric Co.	7
Cornell-Dubilier Electric Corp.	99	Schauer Mfg. Corp.	110
Duotone Co.	58	Shure Brothers, Inc.	89
Electra-craft Appliance Co.	105	Snyder Mfg. Co.	88
Electronic Chemical Corp.	94	Sola Electric Co.	86
Electronic Instrument Co., Inc.	105	South River Metal Products Co., Inc.	92
Electronic Measurements Corp.	103	Sprague Products Co.	23
Falcon Electronics Co.	4, 5	Sprayberry Academy of Radio	82
Federal Telephone & Radio Corp.	13	Sylvania Electric Products Inc.	24
Fenton Co.	93	T.V. Products Co., Inc.	62
The Finney Co.	68	Tel-A-Ray Enterprises, Inc.	81
Franklin Television Labs., Inc.	82	Television Hardware Mfg. Co.	52
Fretco Inc.	109	Telrex, Inc.	6
General Electric	14, 15	Transamerica Electronics Corp.	104
General Electric Lamp Dept.	98	Triad Transformer Mfg. Co.	107
General Instrument & Appliance Corp.	59	Tung-Sol Electric, Inc.	16
Grayhill	109	Turner Co.	80
The Heath Co.	104	University Loudspeakers, Inc.	10
Hickok Electrical Instrument Co.	80	V-M Corp.	95
Hi-Lo TV Antenna Corp.	103	Vidaire, Inc.	98
I. E. Mfg. Co.	108	Video Corp. of America	88
Industrial Television Inc.	111	Viking Electronics Corp.	108
International Resistance Co.	27	Waldom Electronics, Inc.	101
JFD Mfg. Co., Inc.	2	Walsco Electronics Corp.	51
Jackson Electrical Instrument Co.	85	The Ward Products Corp. (Div. The Gabriel Co.)	48
Jeb Sales Corp.	25	Webster Electric	83
Jensen Industries, Inc.	84	Westinghouse Electric Corp. (Electronic Tube Div.)	92
Jontz Mfg. Co.	87	Workman TV, Inc.	106
Kay Electric Co.	90		
Kerden Chemical Co.	110		
Kester Solder Co.	96		



**PORTABLE, COMPACT, VERSATILE, COMPLETE
IN THE HOME...
AND IN THE SHOP**

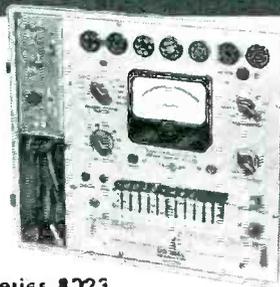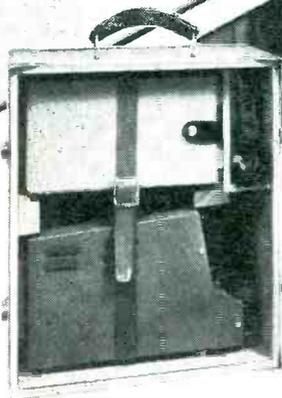

Series 8023

RCP

"DO-ALL" Servishop Sets You Up In Business

Rapidly and efficiently services the 75 out of 100 TV sets which can be serviced at home... all the measurements at your fingertips.

With the RCP Servishop you can check, test and align set from antenna to picture tube. Whether it be AM-FM or TV—UHF or VHF—there is nothing that does the complete job as expertly and professionally as the RCP Servishop.

Series 8023 includes:

1. **Model 750**—for UHF and VHF... serves as signal, marker and pattern generator.
2. **Model 533M**—a portable 3" scope with high sensitivity and wide band response.
3. **Model 808A**—a tube and set tester which also serves as cathode ray tube tester and reactivator plus a vacuum tube voltmeter with ohmmeter.
4. **Model 730**—AF-AM (RF) FM signal generator—easily aligns and checks all circuits in AM and FM receivers.
5. **Model HVMP-1**—Hi-Voltage Multiplier Probe. Complete, including all necessary leads. **\$341.00 Net.**

Series 8020—Same as the 8023

less Model 730 Signaligner.

Complete **\$310.00 Net.**


Model 8873A—Servishop—A compact, convenient service package to meet your AM-FM, and TV test needs... includes 808A "DO-ALL" Tube and Set Tester and Model 730 Signaligner AF-AM (RF) FM Signal Generator. Complete with tubes, batteries and leads. **\$139.95 Net.**

TIME PAYMENT PLAN

Ask your local distributor about the new RCP Finance Plan... Gives you 1 year to pay and allows you to buy the equipment package you need to do the complete job.




Model 750
"DC-ALL" TV Signal
Generator

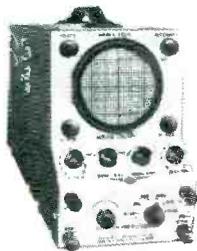

Model 533M
The Midgetscope



Model 730
Universal Signaligner

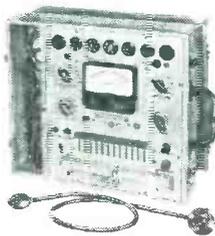


Model 808A
"DO-ALL" Tube and
Set Tester

See Your Local Parts Distributor Or Write For New RCP Catalog Department S-10.

RADIO CITY PRODUCTS CO., Inc.
152 WEST 25th STREET • NEW YORK 1, N. Y.

RCP

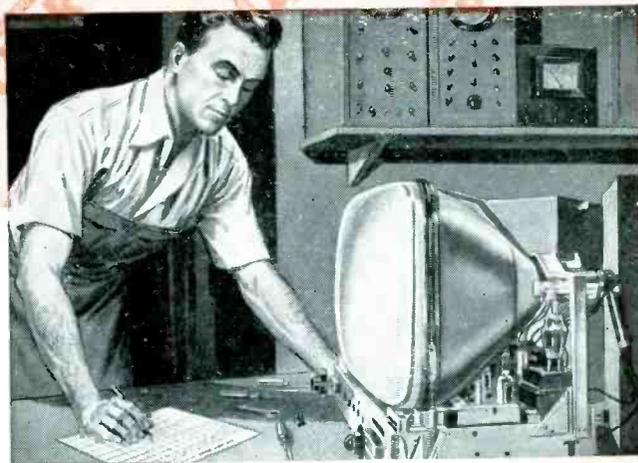Depend on Mallory
for
Approved Precision Quality



Put **More** Service Life Into All Your Jobs



Whenever Mallory FP Capacitors go into a service job, your customers can be sure of more hours of entertainment . . . you can be sure the job is done right . . . once and for all. For all your service work, you'll get better results with Mallory Capacitors. They are engineered to meet the electrical requirements of any TV or radio set. They'll give performance that is equal to . . . and often better than . . . the original equipment.

What's more, Mallory FP Capacitors are the only fabricated plate capacitors available to the replacement market. You can depend on them to give longer life at higher temperatures and greater ripple currents. They will give trouble-free performance at 185° F. (85° C.).

Any way you look at it, dependable service work builds satisfied customers. The next time you order capacitors, ask for Mallory FP's. They will put an end to call-backs due to capacitor failure . . . yet they cost no more.



For plastic tubular replacements, specify Mallory Plascaps®. Their improved moisture proofing will put an end to shorts. No off-center cartridges . . . leads are permanently secured.

P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
RECTIFIERS • POWER SUPPLIES • FILTERS • MERCURY BATTERIES
APPROVED PRECISION PRODUCTS

P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA

A serviceman's

"best friend"

is an RCA Tube

An RCA Tube starts working for you from the instant the customer first sees the familiar red, black, and white carton. You have her confidence from the start, because she knows and respects the RCA trademark.

But the big payoff to you begins when the tube goes to work. For, experience has proven that the superior quality of RCA Receiving Tubes and Kinescopes is your best measure of protection against premature tube failures. With RCA Tubes, you can be sure the job is well done.

Helping you to safeguard your reputation is a vital, everyday service of RCA Tubes. And that protection is yours at no extra cost.



**UNLOCK
THE DOOR TO
BIGGER
PROFITS**

Here's *your* key to better business... RCA's dynamic Dealer Identification Program. Ask your **RCA Tube Distributor** for your copy of the colorful, 16-page booklet "A Magic Pass-Key to Customer Confidence." It tells you how you can become a Registered Dealer... and get *extra* sales benefits.



RADIO CORPORATION of AMERICA
ELECTRON TUBES

HARRISON, N. J.