

# ELECTRONICS WORLD

Denmark DKr. 70.00  
Germany DM 15.00  
Greece Dra.760  
Holland Dfl. 14  
Italy L. 7300  
IR £3.30  
Spain Pts. 780  
Singapore S\$ 12.60  
USA \$6.70

## + WIRELESS WORLD

SOR DISTRIBUTION

A REED BUSINESS PUBLICATION

JANUARY 1994 £1.95

### **THEORY**

The meaning of  
square law in fets

### **PC ENGINEERING**

A case for  
CASE tools?

### **APPLICATIONS**

Using an 850MHz  
op-amp, Lowest  
noise audio

### **RF ENGINEERING**


Tailoring the IF  
passband

### **DESIGN**


Micro-controlled  
programmable  
power supply

### **AUDIO**

End to amplifier  
distortion?

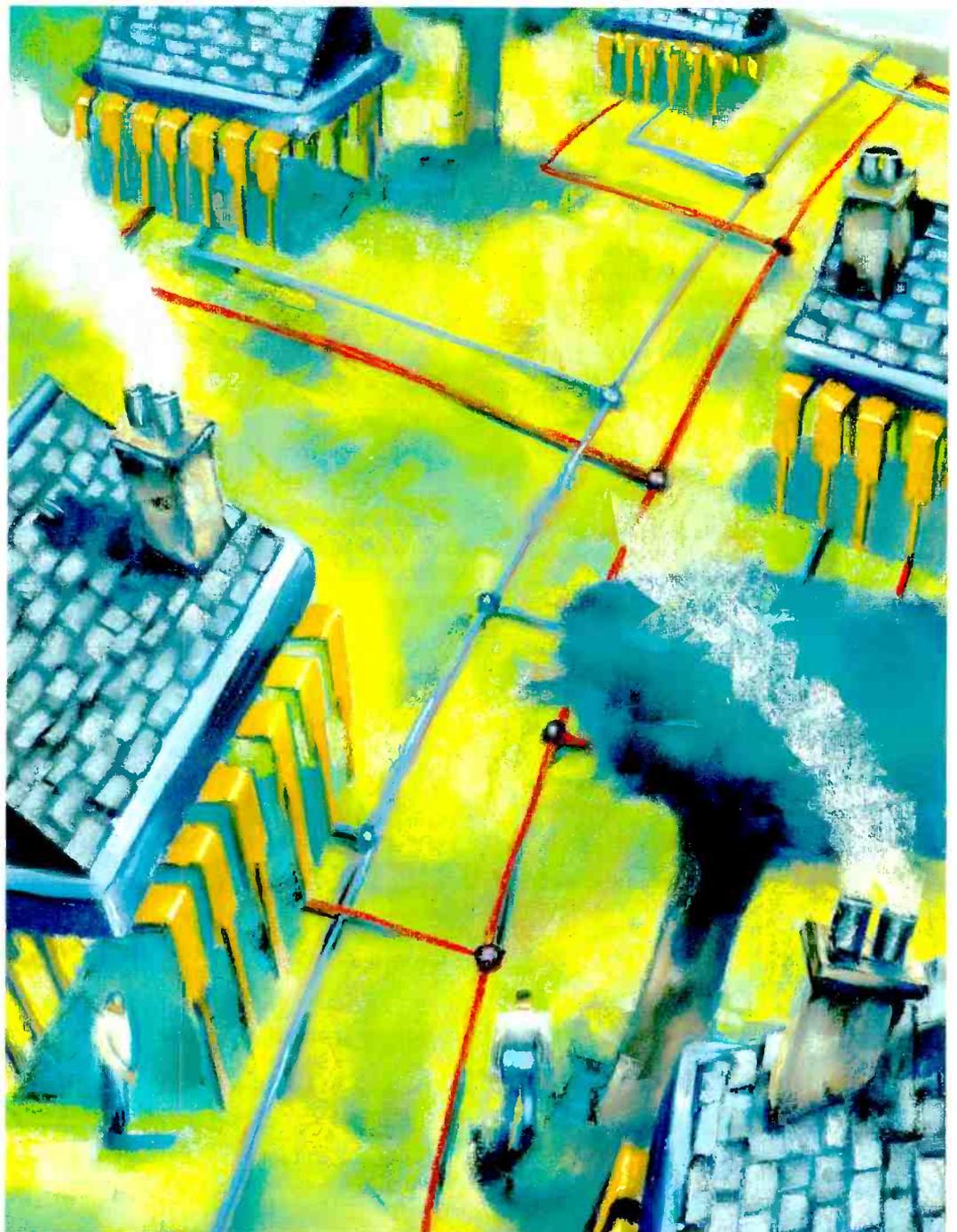

## **BUSMAN'S GUIDE TO I<sup>2</sup>C**

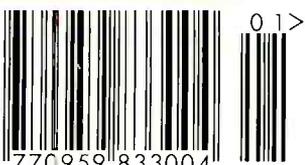

0.1 >

9 770959 833004



# THE WORLDS No.1 BEST SELLING UNIVERSAL PROGRAMMING AND TESTING SYSTEM.

The PC82 Universal Programmer and Tester is a PC-based development tool designed to program and test more than 1500 ICs. The latest version of the PC82 is based on the experience gained after a 7 year production run of over 100,000 units.

The PC82 is the US version of the Sunshine Expro 60, and therefore can be offered at a very competitive price for a product of such high quality. The PC82 has undergone extensive testing and inspection by various major IC manufacturers and has won their professional approval and support. Many do in fact use the PC82 for their own use!

The PC82 can program E/EPROM, Serial PROM, BPROM, MPU, DSP, PLD, EPLD, PEEL, GAL, FPL, MACH, MAX, and many more. It comes with a 40 pin DIP socket capable of programming devices with 8 to 40 pins. Adding special adaptors, the PC82 can program devices up to 84 pins in DIP, PLCC, LCC, QFP, SOP and PGA packages.

The unit can also test digital ICs such as the TTL 74/54 series, CMOS 40/45 series, DRAM (even SIMM/SIP modules) and SRAM. The PC82 can even check and identify unmarked devices.

Customers can write their own test vectors to program non standard devices. Furthermore it can perform functional vector testing of PLDs using the JEDEC standard test vectors created by PLD compilers such as PALASM, OPALjr, ABLE, CUPL etc. or by the user.

The PC82's hardware circuits are composed of 40 set pin-driver circuits each with TTL I/O control, D/A voltage output control, ground control, noise filter circuit control, and OSC crystal frequency control. The PC82 shares all the PC's resources such as CPU, memory, I/O hard disk, keyboard, display and power supply.

A dedicated plug in card with rugged connecting cable ensures fast transfer of data to the programmer without tying up a standard parallel or serial port. Will work in all PC compatibles from PC XT to 486.

The pull-down menus of the software makes the PC82 one of the easiest and most user-friendly programmers available. A full library of file conversion utilities is supplied as standard.

The frequent software updates provided by Sunshine enables the customer to immediately program newly released ICs. It even supports EPROMs to 16Mbit.

Over 20 engineers are employed by Sunshine to develop new software and hardware for the PC82. Not many competitors can boast of similar support!

Citadel, a 32 year old company are the UK agents and service centre for the Sunshine range of programmers, testers and in circuit emulators and have a team of engineers trained to give local support in Europe.

- \* More sold worldwide than any other of its type.
- \* UK users include BT, IBM, MOD, THORN EMI, MOTOROLA, SANYO, RACAL
- \* High quality Textool or Yamaichi zero insertion force sockets.
- \* Rugged screened cabling.
- \* High speed PC interface card designed for use with all PC models from XT to 486.
- \* Over 1500 different devices (including more than 100 MPU's) supported.
- \* Tests and or identifies a wide range of logic devices.
- \* Software supplied to write own test vectors for custom ICs and ASICs etc.
- \* Protection circuitry to protect against wrong insertion of devices.
- \* Ground control circuitry using relay switching.
- \* One model covers the widest range of devices, at the lowest cost.
- \* No need to tie up a slow parallel port.
- \* Two year free software update.
- \* Speed optimised range of programming algorithms.



**NOW SUPPLIED WITH SPECIAL VALUE ADDED SOFTWARE** (worth over £300 if bought seperately):

- \* MICROTEC disassemblers for Z8, 8085, 8048, 8051, 6809 & 68HC11.

- \* NATIONAL SEMICONDUCTOR OPALjr PAL/PLD development software.

- \* BATCH SOFTWARE for production programming.

Our stocked range of own manufactured and imported Sunshine products include:

- \* Super fast EPROM Erasers.
- \* 1, 4 & 8 gang EPROM 8Mbit production programmers.
- \* Battery operated portable EPROM programmers.
- \* "In circuit" Emulators.
- \* Handy pocket IC testers.



## ORDERING INFORMATION

PC82 complete with interface card, cable, software and manual only **£395**

Please add £7 carriage (by overnight courier) for UK orders, £20 for export orders, and VAT where applicable.

ACCESS, MASTERCARD, VISA or CWO. Official orders are welcome from Government bodies & local authorities.

Free demo disk with device list available.



**CITADEL PRODUCTS LTD**  
DEPT. WW, 50 HIGH ST.,  
EDGWARE, MIDDX. HA8 7EP.

Phone now on: 081 951 1848/9



**EDITOR**

Frank Ogden  
081-652 3128

**DEPUTY EDITOR**

Martin Eccles  
081-652 8638

**CONSULTANT**

Derek Rowe

**DESIGN & PRODUCTION**

Alan Kerr

**EDITORIAL ADMINISTRATION**

Lorraine Spindler  
081-652 3614

**ADVERTISEMENT MANAGER**

Carol Nobbs  
081-652 8327

**SALES EXECUTIVE**

Pat Bunce  
081-652 8339

**ADVERTISING PRODUCTION**

Paul Burgess  
081-652 8355

**PUBLISHER**

Susan Downey

**EDITORIAL FACSIMILE**

081-652 8956

**CLASSIFIED FACSIMILE**

081-652 8931

**SUBSCRIPTION HOTLINE**

0622721666  
Quote ref INJ

**SUBSCRIPTION QUERIES**

0444 445566

**NEWSTRADE DISTRIBUTION****ENQUIRIES**

Martin Parr  
081 652 8171

**BACK ISSUES**

Available at £2.50  
081-652 3614

## A nasty case of slipped disks

Please allow me to share with you a personal dream. All desktop computer operating systems rely on hard disks, which in a world of solid-state electronics, are anachronistic. The majority of computer failures derive from mechanical components. Replacing mechanics with electronics results in faster, more reliable products. I contend that what the desktop computing world needs is not *Chicago*, *Windows NT*, Apples and Acorns but machines which integrate all aspects of their operation into electronics.

Of course, this is not an original thought. Every high street techie shop is alive with things called PDAs – personal digital assistants. These are miniature computer devices which combine all sorts of features which nobody has asked for with a data entry system which nobody wants to use. But they do have technical merit. They contain their operating systems in silicon and are thus probably reliable while their absence of motors reduces power consumption to the point where they can do more than boot themselves up before the battery goes flat. I would like to see a desktop computer, full sized keyboard and a built-in solid state operating system. And, of course, the applications software to run on it. This remains a dream because solid-state storage devices with sufficient capacity do not exist... yet.

Here is the reality. Microsoft and other vendors of computer operating systems have misplaced objectives. First, a few facts. Microsoft has spent more than £100 million developing *Windows NT*, a true 32-bit operating system designed to subvert the unix world. As such it provides all sorts of security mechanisms for networked computer applications. However, it occupies no less than 70Mbytes of disk space and is noticeably slower in use than the already sluggish and restrictive *Windows 3.1*. On the plus side, it breaks away from the Intel monopoly by eventually being available for *PowerPC* and other microprocessor architectures. This should allow applications software to become independent of machine and microprocessor type. Indeed, since IBM opened its doors to merchant chip sales, I would only buy a PC with *IBM Inside*, preferably the 100MHz *Blue Lightning* which knocks spots off Intel's *Pentium*. But that is another story.

Ignore for a moment the needs of the power user; you don't want to run a network or file-serving system or sort a 200MB of mailing list. Just the ordinary things which 90 per cent of computer users want: spreadsheets, wordprocessors, calculators and graphics. These are the uses which are ripe for a solid-state computer.

With current technology, your probable choice of operating system will be *Chicago*, the forthcoming successor to *Windows 3.1* combining its own Dos 7 operating layer. You won't be alone. Its predecessor has already sold some 40 million copies. Once again it is slow and cumbersome and will eat up 16 Mbytes of disk space. One might have chosen an Apple Macintosh or something else but these alternatives aren't much better. This raises a couple of points. Firstly software writers no longer feel constrained to writing compact code. I suggest that current user applications simply incorporate more unused features than their smaller forbears. Most could usefully be compacted to fit restricted memory space without a return to command line programming; an effective GUI would be part of the silicon operating system.

Secondly, semiconductor companies think too conventionally. The largest flash eeprom chips, currently some 16Mbit/chip, are guaranteed 100 per cent functional which makes large memory arrays built from them expensive. The concept of wafer scale integration is some 25 years old but deserves rediscovery. In the same way that hard disk sectors are mapped and excluded, a similar redundancy EDC system could be made for large, low cost silicon storage. I would like to buy silicon memory arrays with their own built-in operating system rather than as individual chips. My consultant Derek Rowe – a founder of Abacus Computers – insists that if WSI were that easy, it would have been done years ago. Also, a viable computer system requires a low cost data exchange – floppy disk. I insist that, if semiconductor companies directed as much of their effort into memory system function as they put into process technology, WSI could be reality. I also say "smart card". It seems incredible that the computer industry alone shows virtually no technological progress while making so much money out of inappropriately engineered products.

**Frank Ogden.**

*Electronics World + Wireless World* is published monthly. By post, current issue £2.25, back issues (if available) £2.50. Orders, payments and general correspondence to L333, **Electronics World + Wireless World, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.**

Telex: 892984 REED BP G. Cheques should be made payable to Reed Business Publishing Group.

**Newtrade:** IPC Marketforce, 071 261 5108

**Subscriptions:** Quadrant Subscription Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 441212. Please notify a change of address. Subscription rates 1 year (normal rate) £30 UK and £35 outside UK.

**USA:** \$116.00 airmail. Reed Business Publishing (USA), Subscriptions office, 205 E. 42nd Street, NY 10117.

**Overseas advertising agents.** France and Belgium: Pierre Mussard, 18-20 Place de la Madeleine, Paris 75008. United States of America: Ray Barnes, Reed Business Publishing Ltd, 205 E. 42nd Street, NY 10117. Telephone (212) 867-2080. Telex 23827.

**USA mailing agents:** Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. 2nd class postage paid at Rahway NJ Postmaster. Send address changes to above.

**Printed by** BPPC Magazines (Carlisle) Ltd, Newtown Trading Estate, Carlisle, Cumbria, CA2 7NR

**Typeset by** Marlin Graphics 2-4 Powerscroft Road, Sidcup, Kent DA11 5DT

©Reed Business Publishing Ltd 1992 ISSN 0959 8332



# Welcome to the world of DSP.

"A Simple Approach to Digital Signal Processing" is Texas Instruments' new publication for anyone who needs to know about DSP but who doesn't have the first idea what it's all about.

Ideal for students and mature engineers who want to get into the world of DSP, this book gives a very readable introduction to highly technical subjects such as sampling, filters, frequency transforms, data compression and design decisions.

Unlike other DSP publications, the book is light on complicated mathematics and heavy on diagrams, examples and clear explanations. It also includes a typical development cycle for engineers who need to design and build a DSP system.

Order your copy now and open up a new world of DSP designs. Just mail the coupon below with your cheque to:

Texas Instruments, Black Horse Road,  
London SE8 5NH,  
Fax 81 694 0099, Tel. 81 691 9000

**SPECIAL LAUNCH OFFER**  
**£15.00**



This is my order for A Simple Approach to Digital Signal Processing. My cheque for £ \_\_\_\_\_ is enclosed.

Name \_\_\_\_\_ Title \_\_\_\_\_  
Company \_\_\_\_\_  
Address \_\_\_\_\_  
Postal Code \_\_\_\_\_ City \_\_\_\_\_  
Country \_\_\_\_\_ Telephone \_\_\_\_\_

CIRCLE NO. 102 ON REPLY CARD

## RF MODULES UP TO 2GHz

### GASFET LNAs 5MHz-2GHz

Two-stage. High Q filters. Masthead or local use.

**TYPE 9006** Freq: 5-250MHz. B/W up to 40% of CF. Gain 10-40dB variable. 50 ohms. NF 0.6dB. £105

**TYPE 9004** Freq: 250-1000MHz. B/W up to 10% of CF. NF 0.6dB. Gain 25dB. 50 ohms. £135

**TYPE 9304** Freq: 1-2GHz. B/W up to 10% of CF. NF 0.4dB. Gain 20dB. 50 ohms. £185

**TYPE 9035** Transient protected mains power supply for above amplifiers. £58

**TYPE 9010** Masthead weatherproof unit for above amplifiers. £16

### PHASE LOCK FREQUENCY CONVERTERS

**TYPE 9315** Down converter. I/p frequencies 250MHz-2GHz. O/p frequencies 20MHz-1GHz. B/W up to 10MHz. NF 0.7 dB. Gain 30dB variable. £350

**TYPE 9316** Up/down converter. I/p & o/p frequencies 20MHz-2GHz. B/W up to 100MHz. NF 0.7dB. Gain 40dB variable. £550

**TYPE 9115A** Up/down converter. I/p & o/p frequencies 20MHz to 1GHz. B/W up to 100MHz. NF 0.7dB. Gain 60dB variable. O/p up to 10mW + 10dBm. AGC. £650

### VOLTAGE TUNABLE DOWN CONVERTER

**TYPE 9317** I/p will tune 30% of CF specified in the range 300MHz-2GHz. O/p 70MHz. NF 0.6B. Gain 60dB. O/p up to 10mW + 10dBm. AGC. £950

### PHASE LOCK SIGNAL SOURCES 20-2000MHz

**TYPE 8034** Freq. as specified in the range 20-250MHz O/p 10mW. £194

**TYPE 9036** Freq. as specified in the range 250-1000MHz. O/p 10mW. £291

**TYPE 9038** Freq. as specified in the range 1-2GHz. O/p 10mW. £350

**TYPE 9282** FM up to ±75KHz max. Freq. as specified in the range 30-2000MHz. O/p 10mW. £378

### WIDEBAND AMPLIFIERS

**TYPE 9301** 100KHz-500MHz. NF 2dB at 500MHz. Gain 30dB. Output 12.5dBm, 18mW. 50 ohms. £165

**TYPE 9302** 10MHz-1GHz. NF 2dB at 500MHz. Gain 30dB. Output 12.5dBm, 18mW. 50 ohms. £165

**TYPE 9008** Gasfet. 10MHz-2GHz. NF 2.5dB at 1GHz. Gain 10dB. Output 18dBm, 65mW. 50 ohms. £165

**TYPE 9009** Gasfet. 10MHz-2GHz. NF 3.8dB at 1GHz. Gain 20dB. Output 20dBm, 100mW. 50 ohms. £185

### WIDEBAND LINEAR POWER AMPLIFIERS

**TYPE 9246** 1 watt output. 100KHz-175MHz. 13dB gain. £192

**TYPE 9036** 1 watt output. 10MHz-1GHz. 15dB gain. £312

**TYPE 9247** 4 watt output. 1-50MHz. 13dB gain. £215

**TYPE 9051** 4 watt output. 20-200MHz. 13dB gain. £215

**TYPE 9176** 4 watts output. 1-50MHz. 26dB gain. £345

**TYPE 9177** 4 watts output. 20-200MHz. 26dB gain. £345

**TYPE 9178** 10 watts output. 1-50MHz. 13dB gain. £304

**TYPE 9179** 10 watts output. 20-200MHz. 13dB gain. £304

**TYPE 9173** 20 watts output. 1-50MHz. 17dB gain. £395

**TYPE 9174** 20 watts output. 20-160MHz. 10dB gain. £395

**TYPE 9271** 40 watts output. 1-50MHz. 16dB gain. £748

**TYPE 9172** 40 watts output. 20-160MHz. 10dB gain. £748

**TYPE 9660** 60 watts output. 25-75MHz. 10dB gain. £898

### UHF LINEAR POWER AMPLIFIERS

Tuned to your specified frequency in the range 250-470 MHz

**TYPE 9123** 500mW input, 5 watts output. £350

**TYPE 9124** 2-3 watts input, 25 watts output. £510

**TYPE 9126** 8 watts input, 50 watts output. £1495

Prices exclude p&p charges and VAT

## RESEARCH COMMUNICATIONS LTD

Unit 1, Aerodrome Industrial Complex, Aerodrome Road, Hawkinge, Folkestone, Kent CT18 7AG

Tel: 0303 893631 Fax: 0303 893838

CIRCLE NO. 103 ON REPLY CARD

# CONTENTS

## FEATURES




Cover: Illustration  
Jamel Akib

### BUSMAN'S GUIDE TO I<sup>2</sup>C.....24

When system flexibility is more important than access speed, I<sup>2</sup>C bus provides the ideal choice. Originally designed for communication around a PCB, it is now used as a communication channel between equipment. Design consultant Mike Button reveals why this simple two-wire interface has become so popular.
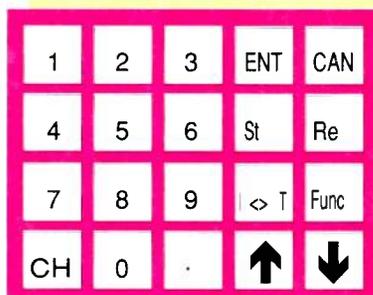
### MICRO CONTROLLED POWER SUPPLY.....12

As well as making output easier to set and read accurately, adding a microprocessor to a power supply increases flexibility. Matthew Rahman and Robin Thick present a fully programmable design based on a Z80, with program code available on disk.



### MARCONI'S 200kW TRANSATLANTIC TRANSMITTER.....29

In 1916, Marconi built a massive wireless station for transatlantic traffic representing the world's most powerful spark transmitter. By recreating some of the essential technology, George Pickworth sheds new light on a spark transmitting system with a power conversion efficiency comparable to thermionic tube transmitters.

### DISTORTION IN POWER AMPLIFIERS.....41

Douglas Self continues his quest for perfect audio reproduction, discussing an often overlooked aspect of power amplifier design – physical layout.

### WORKING WITH PROGRAMMABLE LOGIC.....49

Discrete logic blocks are a hallmark of an old-fashioned design. Don't give people the chance to laugh at yours. Move to generic and gate array logic with Geoff Bostock.

### USING RF TRANSISTORS .....76

Class and bias are important topics in RF amplifier design. Norm Dye and Helge Granberg investigate the relative merits of common base and common emitter configurations for both bipolar and fets.

### MAKING A DIFFERENCE TO SQUARE-LAW FETS...82

According to Michael Williams, the familiar difference between two squares concept could be a route to the perfect fet amplifier, whether for radio or audio applications.

## REGULARS

### COMMENT.....3

A nasty case of slipped disks.

### UPDATE .....4

Will synchronous drums be quick enough? Silicon Valley in space. HDTV debate. Buckyballs for semiconductor film?. Bit reversal speeds up computing 500 times. Plasma promotes clean soldering.

### RESEARCH NOTES .....9

Macho behaviour affects the universe, High efficiency organic leds, Power line cancer? Music and IQ, Looking for life on Earth, New visions of image analysis.

### PC ENGINEERING.....21

Being costly, computer aided software engineering tools have traditionally been the domain of the big user. John Anderson looks at a new package that has a price tag within the reach of small businesses.

### DESIGN BRIEF.....34

Synchronously tuned IF stages. Ian Hickman describes shaping IF response for instruments and pulse/data receivers: the passband characteristic has a significant effect on its settling time. Settle your IF strip fast...

### LETTERS.....46

Sun spots and power lines, Audio cable mythology, Listening versus hearing, EM radiation – killer or cure?

### APPLICATIONS .....58

Combined notch and low-pass filter, Low noise mic preamplifier with phantom power, Bidirectional coaxial driving, Efficient DC converter, Magnetic current sensor.

### CIRCUIT IDEAS .....65

Cascode oscillator, Battery backup, 1GHz prescaler, Remote motor control, DC modulator, ESR tester.

### NEW PRODUCTS .....71

Round up of active, passive and computer components including literature.


### In next month's EW+WW: Special bass issue.

Bass reproduction tends to be the single most significant factor in determining the perceived performance of an audio system. Five separate luminaries look for the ultimate in bass reproduction technology. We consider the theory, the practice, the materials, the size, the electronics, the arrangement and the room. A heavyweight investigation for heavyweight bass reproduction.

JANUARY ISSUE IS ON SALE DECEMBER 30
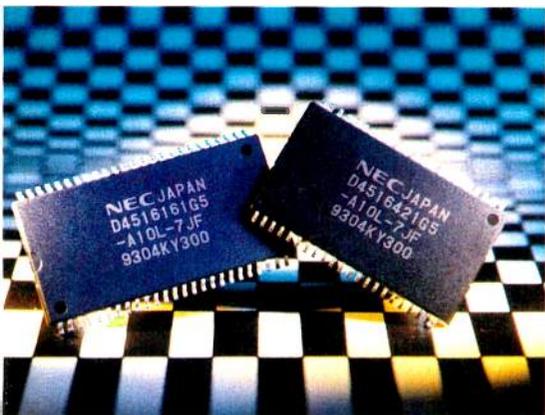
## Synchronous drams: better mass memory technology?

A recent announcement by NEC that it is ready to begin production of 16Mbit synchronous drams places the technology on the starting blocks. But it is clear there is little – almost minimal – demand for the devices currently and that future demand will depend on whether it is a practical and cost effective solution for high speed system design.



Other synchronous dram manufacturers, principally Hitachi, Samsung and Toshiba, are in a similar position to NEC. However, they are being more reticent in forecasting production of 16Mbit devices and some are sceptical of there being a sizeable market much before 1995.

In synchronous dram all inputs and outputs are synchronised to the rising edge of the system clock operating up to 100MHz. This contrasts with traditional dram technology which is controlled asynchronously; the processor dispatches a set of addresses and waits, while the DRAM performs several internal functions such as activating the word and bit lines, until the data is returned.

Conversely under synchronous control of the system clock, the addresses are latched in the dram until the device is ready to deliver the data after a preprogrammed number of clock cycles. During this time the processor can perform other functions.

The synchronous dram has two internally interleaved banks and the row address strobe will need only a single pulse signal while hidden precharge and a programmable burst sequence provide the high bandwidth.

The row address is strobed in on the rising edge of the system clock activating a row or word line. A column address is then latched in after three clock cycles (30ns minimum). A byte of data appears on the outputs after three more cycles are taken to decode the address and deliver data to the output buffers – just six cycles in total.

Synchronous dram can reduce access time further by pipelining addresses. The input latch stores the next address while the dram is processing the previous one.

Burst mode is similar to the old nibble mode in which four bits of sequential data are provided in rapid succession without having to provide new address information. In the synchronous dram however, as much as an entire page, typically 1024-bits, can be provided after the first 60ns access at the rate of one byte every 10ns. This burst mode can also be combined with a wrap feature to give access to strings of data stored both before and after the initial bit location. It will be useful for cache line filling where data tends to have spatial locality properties. The wrap feature has a programmable length of 1, 2, 4 or 8 bytes or a full page.

A further benefit of the interleaving is that active rows in separate banks can emulate a cache; the row is held active and reselected simply by supplying a new column address.

There are many other features such as clock enable/disable which will suspend the device, in its current state and put it into a low power standby mode. Self refresh is also included.

Jedec published the specification for synchronous dram in October. To date the only bus interface contained in the specification is low voltage LVTTTL.

According to Desi Rhoden, one of the subcommittee chairmen on the JC42.3 committee which is overseeing the development of synchronous dram, the LVTTTL interface is good for 100MHz, but no higher. The committee is therefore looking at other interfaces including GTL, CTT and ECL to raise performance to 200 to 250MHz.

"GTL is under investigation and is not yet proven to work in a system at any reasonable frequency," said Rhoden. "I expect some modifications will be needed. ECL and CTT are also high power alternatives and that doesn't really track well with what we are trying to do. GTL is also actually high power because of all the terminations needed in a system."

All of these interface standards have limited voltage swing in common. Our overall goal is to limit the amount of charge flowing between buffers. So a 1V swing would seem a logical objective. We may have to go for a compromise between all the alternatives to get the kind of performance we want."


Rhoden admits though that 200MHz dram performance is unlikely to be demanded by systems designers for at least two years – pretty much when the current generation of synchronous drams is expected to be in volume production.

The ultimate success of synchronous dram will depend on whether it can effectively replace a second level cache, which currently relies on expensive sram, and on there being little or no price premium for the chips.

According to some industry experts, how successful synchronous dram is at replacing caches cannot be judged at present because most major systems houses are keeping their conclusions to themselves.

The price issue is more easily judged. Anne West, NEC UK's assistant product manager for memory, says the current price of an ordinary 16Mbit dram is about £50. A 16Mbit synchronous dram will be at least double that initially," she said. Only market demand will drop that price".

*Simon Parry, Electronics Weekly*

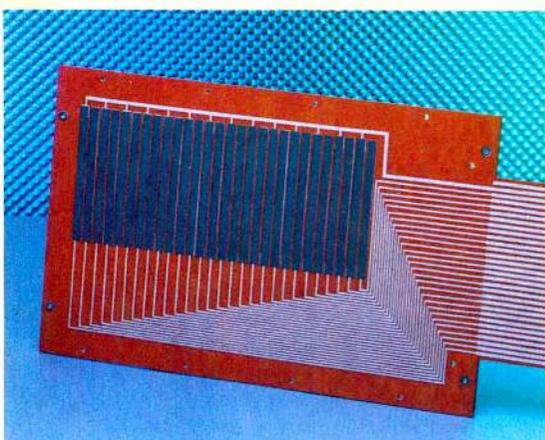

*A team from University College London has been researching new ways to help measure disabled peoples' feet so that correctly fitting shoes can be made. Their 'three dimensional' measurement method involved carbon tracks custom printed onto a PCB. According to the source of the PCB, Omeg, theirs was the only company in Europe able to produce it.*

## Space for Silicon Valley

If NASA has its way, there will be two Silicon Valleys – one in California and the other in space.

In January of next year, the Space Shuttle will launch the Wake Shield Facility – the first commercial production facility designed to produce near-perfect gallium arsenide wafers while circling the Earth in low orbit.

The space-grown wafers will result in integrated circuits which can run eight times faster than circuits made from silicon and three times faster than gallium arsenide chips made on earth, according to University of Houston researchers.

Conceived by the Space Vacuum Epitaxy Center at the University of Houston and by Space Industries in League City, Texas, the Wake Shield Facility will use molecular beam epitaxy to produce near perfect crystal wafers of gallium arsenide. The gallium arsenide wafers are made by laying down ultrathin layers of molecules in a vacuum.

During the flight, the Wake Shield Facility, a 12ft stainless steel disc, will travel at close to 17,000 miles an hour, pushing the thin atmosphere out of its way and leaving in its wake a vacuum more than 10,000 times purer than the best vacuum chambers on earth.

Because the vacuum created in space is so pure, the crystals will not be contaminated by unwanted atoms, which slow down conduction of electronic signals.

If all goes well in January, NASA is planning to use the Wake Shield Facility to make other thin crystalline films for lasers and superfast computer circuits.

## Warning on digital TV

Europe should move as fast as possible to establish digital terrestrial television services, with simulcasting of existing TV channels in digital and analogue forms starting as early as 1997, and it should also move as soon as possible to an all-digital world. So says a report published last week by city firm Coopers and Lybrand. Co-author Dermot Nolan said existing terrestrial broadcasters are likely to go under if they miss the digital boat.

## Picture firms up for digital HDTV

There is still a considerable amount of HDTV research in the pipeline if the recent conference in Ottawa is anything to go by. But a number of the remaining problems stem from the sometimes diverse interests of the broadcast, cable, satellite and computer industries.

For example, to placate the latter, square pixels have been included in the latest North American draft specification even though the corners will become rounded in the display medium.

The digital tv system is now defined as a four layer model: the picture or image layer; the compression layer; the transport layer; and the transmission layer.

The picture layer defines a strategy that is perhaps future proof, providing for 24, 30 and 60 frames a second with progressive scanning. The long term aim of 1050 lines has been upgraded to 1080 lines with 1920 samples per line.

The compression layer is defined around the MPEG-2 standard, at least as far as the video signal is concerned. It has been decided that Dolby AC-3 at 384Kbit/s suits the North American environment better than the European Musicam system. But the final specification may include both as alternative sound systems.

The transport layer relates to the protocol of packetisation, prioritisation and universal headers in the bitstream and is accepted as

pure MPEG-2.

And the transmission layer is to be based on quadrature amplitude modulation or vestigial sideband, rejecting the European coded orthogonal frequency division multiplex system.

It was reported at the conference that the MPEG-4 committee is close to producing a draft report dealing with the future needs for audio-visual processing, addressing the applications and operational environment for very low (a few 10s of kHz) bit rate coding.

The introduction of HDTV will mean simulcasting from existing transmission sites and many masts won't be able to take the extra weight. It poses a particular problem in the US where a substantial number of the 1600 or so US transmitters operate in the vhf band. Because their masts are ageing, it is doubtful if they can meet current construction standards because of the heavier vhf arrays. A similar situation may arise in Europe.

As well as nuts and bolts issues, a significant number of papers dealt with ultra high definition TV – pictures made up from more than 2000 lines and pictures in 3D.

On hardware, German company Digitale Video-systems showed its ISP500 image sequence processor using up to 16Mbyte of ram. It can store several minutes of real time video images in any format, including high definition versions, under software control.

*Geoff Lewis*



## Diamonds and bucky balls feature in new films

Two newly developed carbon-based films, one diamond and one fullerene C<sub>60</sub>, are being explored by researchers at Bell Labs for use in microelectronics.

The films have radically different properties. As is well known, diamond is extremely hard with excellent thermal properties. Fullerene C<sub>60</sub> on the other hand has unique properties that could trigger "thousands of new uses" according to AT&T.

Thin-film diamond, shown in the top photo, makes a highly efficient heat sink for high-power semiconductor lasers such as those used for long distance communications via optical fibres.

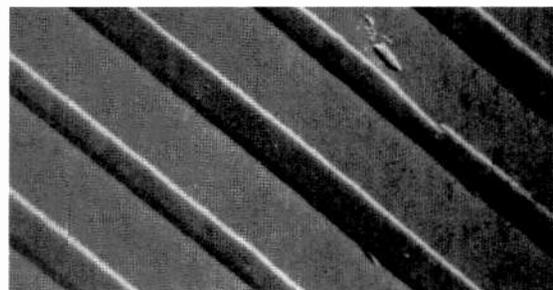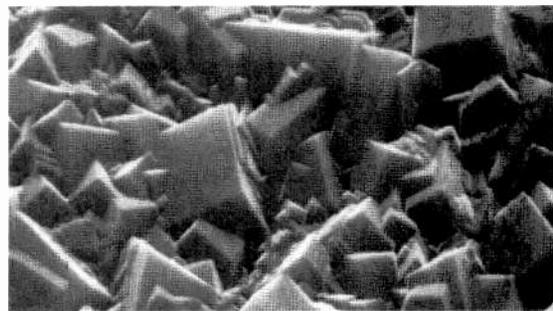Derived from soot, fullerene C<sub>60</sub> has recently been found to be photoresistive and sensitive to ultraviolet light. There may be uses for it in semiconductor manufacture. Earlier research showed that C<sub>60</sub>, shown in the bottom photograph, becomes superconducting when compounded with potassium or rubidium.



## Significant bits first speeds up digital filters

Digital signal processing system designers are doing their arithmetic the wrong way round, jokes Professor John McCanny of Belfast University. To prove his point, engineers there have designed an IIR (infinite impulse response) filter chip which is about 500 times faster than a comparable implementation on a programmable DSP.

Samples of the chip were recently delivered to Professor McCanny's team. Manufactured by GEC-Plessey using its CLA70000 series gate array, the IIR chip has a 30MHz clock speed and has five modes, giving filters up to 16th order, and operates on 16bit two's complement data. GPS is considering making the chip one of its standard signal processing products.

The crux of the IIR filter, however, is that the latency is only two clock cycles despite the extensive pipelining employed in the chip's architecture and is independent of word length. The reason is an arithmetic scheme used in the chip's architecture which calculates the most significant bits (MSBs) first – unlike traditional approaches which start at the least significant bit (LSB).

Professor McCanny says MSB-first arithmetic offers significant performance benefits and these are most apparent in high speed systems that require some form of pipelining. "If MSB-first arithmetic is used in a pipeline then, crucially, you do not have to wait until the end of the pipeline to begin using the result," he said. "This is how you can reduce the latency of feedback loops.

The outcome is that for signal processing operations that are recursive in nature (hence which require a feedback loop) the sampling rate can be lower to attain a chosen performance, or the silicon can operate at much higher sampling rates than would otherwise have been possible.

The breakthrough at Belfast University was to realise that MSB-first arithmetic – made possible by use of a signed binary number representation – could be implemented on conventional 'carry-save' arithmetic circuits widely used in digital signal processing systems. Carry-save arithmetic is inherently redundant making it an ideal fit to an MSB first scheme. Also, these circuits need only conventional binary numbers and, hence, would not require special conversion circuitry.

The IIR chip comprises two biquad filter sections (since any order IIR filter can be built from cascaded biquad sections) with each section integrating four multiply-accumulate (MAC) blocks and a shifter circuit. Carry-save and MSB-first arithmetic is used inside the MACs.

The MAC blocks generate the most significant digits of the result after just two clock cycles which can be fed back immediately and used in another computation. For this reason the chip can process two separate data streams allowing two independent fourth order IIR filters to be implemented. Both of them can operate at a sampling rate of 15MHz (corresponding to a clock speed of 30MHz).

Professor McCanny says that the success of the IIR filter chip has proved the concept but there are other benefits to be gained from MSB-first arithmetic. "Signal processing operations usually have some truncation or rounding process after a calculation in which the LSBs are thrown away," he said. "So why start at the LSBs? It would be quicker and less computationally intensive if the MSBs were done first." The arithmetic can also be successfully extended to other mathematical functions such as division and square root extraction. "In a processor the multiply operation is typically much faster than division or square root operations," said Professor McCanny.

"But, if you think about it, a square root calculation is inherently most significant digit first. Using our technique we can perform division and square root calculations in times comparable to a multiply operation."

However, Professor McCanny thinks the efficiency of the technique is perhaps its biggest advantage. The filter chip contains 30,000 gates and can perform up to 300 million multiplications and additions per second. That is 10,000 per gate which is impressively high." *Simon Parry* ■

## Plasma leaves soldering out in the cold

Cold plasma technology can be used to remove organic contaminations from pcbs, eliminating fluxing and post cleaning in production.

The process leaves pcbs clean, dry and solder ready says German firm Grasmann.

To work, a vacuum chamber with a pressure of 1000Pa is needed, incorporating a high frequency generator that ionises oxygen and passive tetrafluoromethane (CF<sub>4</sub>) gas.

This plasma cloud oxidises organic compounds on the solder surfaces leaving them ready for wave soldering. Even small voids are penetrated so that through holes are correctly conditioned.

Low temperatures from 30 to 100°C may be used since the free wavelength of the elemental parts is very high.

This treatment can be used on any components and has no visible effect on plastics surfaces; ram chips are already prepared in plasma for printing.

And the treated solder surface degrades


very slowly so that fast transfer between plasma treatment and soldering process is not essential.

Grasmann has developed a two-stage production machine available in the UK from Parkheath of Cardiff. It comprises a plasma preparation unit and a soldering module. The plasma unit can be used separately with an existing inert atmosphere soldering line.

Tests on the process include metallographic analysis, REM photographs, x-ray analysis, temperature cycle, shear, and wetting angle.

The firm describes beta test results as "excellent" saying they resulted in "yields of perfect pcbs as high as could be achieved by conventional methods".

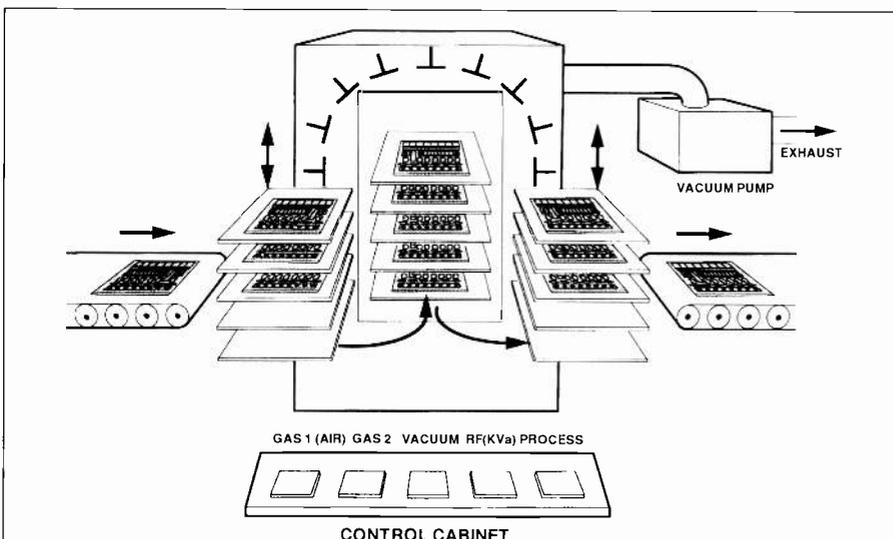The major benefit though is savings in materials and machine cleaning time, which the firm claims gives a projected payback period of two years.



**AMSTRAD DMP4000** Entire printer assemblies including printhead, platen, cables, stepper motors etc. Everything bar the electronics and case. Good stripper! Clearance price just £5 REF: MAG5 or 2 for £8 REF: MAG8

**VIEWDATA SYSTEMS** Brandnew units made by TANDATA complete with 1200/75 built in modem, infra red remote controlled keyboard, BT approved, Prestel compatible, Centronice printer port, RGB colour and composite output (works with any TV) complete with power supply and fully cased. Price is just £20 REF: MAG20 Also some customer returned units available at £10 each REF: MAG10

**PPC MODEM CARDS** These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

**INFRARED REMOTE CONTROLLERS** Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

**TOWERS INTERNATIONAL TRANSISTOR GUIDE.** A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

**SINCLAIR C6 MOTORS** We have a few left without gearboxes. These are 12V DC 3,300 rpm 6"x4", 1/4" OP shaft. £25 REF: MAG25

**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the above motor but suitable for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

**VIDEO SENDER UNIT.** Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range (tune TV to a spare channel) 12V DC Op. Price is £15 REF: MAG15 12vpsu is £5 extra REF: MAG5P2

**\*FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

**LOW COST WALKIE TALKIES** Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG8P1 2 x PP3 req'd.

**\*MINATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x5x2x155mm. Complete with cases and earpieces. 2xPP3 req'd. £30.00 pair REF: MAG30.

**COMPOSITE VIDEO KIT.** Converts composite video into separate H sync, V sync, and video. 12v DC operation £8.00 REF: MAG8P2.

**LQ3600 PRINTER ASSEMBLIES** Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc. In fact everything bar the case and electronics, a good stripper! £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

**PHILIPS LASER 2MW** helium neon tube. Brand new full spec £40 REF: MAG40. Mains power supply kit £20 REF: MAG20P2. Fully built and tested unit £75 REF: MAG75.

**SPEAKER WIRE** Brown two core, 100 foot hank £2 REF: MAG2P1

**LED PACK** of 100 standard red 5mm leds £5 REF: MAG5P4

**JUG KETTLE ELEMENTS** good general purpose heating element (about 2kw) ideal for all sorts of heating projects etc. 2 for £3 REF: MAG3

**UNIVERSAL PC POWER SUPPLY** complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: MAG15P2 (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

**OZONE FRIENDLY LATEX** 250ml bottle of liquid rubber, sets in 2 hours. Ideal for mounting PCB's, fixing wires etc £2 each REF: MAG2P2

**\*FM TRANSMITTER** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever! why pay £700? or price is £26 REF: MAG26 Transmits to any FM radio.

**\*FM BUG KIT** New design with PCB embedded coil for extra stability. Transmits to any FM radio. 9v battery req'd. £5 REF: MAG6P5

**\*FM BUG BUILT AND TESTED** superior design to kit, as supplied to detective agencies etc. 9v battery req'd. £14 REF: MAG14

**TALKING COINBOX STRIPPER** originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units we have generally have the locks missing and sometimes broken hinges. However they can be adapted for their original purpose or used for something else? Price is just £3 REF: MAG3P1

**100 WATT MOSFET PAIR** Same spec as 2SK343 and 2SJ413 (8A, 140v, 100w) 1 N channel and 1 P channel, £3 a pair REF: MAG3P2

**VELCRO** 1 metre length of each side 20mm wide (quick way of fixing for temporary jobs etc) £2 REF: MAG2P3

**MAGNETIC AGITATORS** Consisting of a cased mains motor with lead. The motor has two magnets fixed to a rotor that spin round inside. There are also 2 plastic covered magnets supplied. Made for remotely stirring liquids! you may have a use? £3 each REF: MAG3P3 2 for £5 REF: MAG5P6

**TOP QUALITY SPEAKERS** Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality general purpose speaker. £2 each REF: MAG2P4 or 4 for £6 REF: MAG8P2

**TWEETERS** 2" diameter good quality tweeter 140R (would be good with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

**AT KEYBOARDS** Made by Apricot these quality keyboards need just a small modification to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG8P3

**XT KEYBOARDS** Mixed types, some returns, some good, some foreign etc but all good for spares! Price is £2 each REF: MAG2P6 or 4 for £6 REF: MAG8P4

**PC CASES** Again mixed types so you take a chance next one off the pile! £12 REF: MAG12 or two identical ones for £20 REF: MAG20P4 component pack bargain 1,000 resistors +1,000 capacitors (all same value) £2.50 a pack. REF: MAG2P7

**1994 CATALOGUE  
OUT NOW**

## BULL'S BULLETIN BOARD

**MASSIVE  
WAREHOUSE CLEARANCE  
FANTASTIC £20.00 REDUCTION**

REFURBISHED PC BASE UNITS  
COMPLETE WITH KEYBOARD

FROM ONLY **£29.00**

**AMSTRAD 1512 BASE UNITS  
GUARANTEED  
PERFECT WORKING ORDER.**

A LOW COST INTRODUCTION TO THE HOME COMPUTER MARKET

**AMSTRAD 1512SD**

1512 BASE UNIT, 5.25" FLOPPY DRIVE AND  
KEYBOARD. ALL YOU NEED IS A MONITOR AND  
POWER SUPPLY. WAS £49.00

NOW ONLY **£29.00**  
REF: MAG29

**AMSTRAD 1512DD**

1512 BASE UNIT AND KEYBOARD AND TWO  
5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR  
AND POWER SUPPLY. WAS £59.00

NOW ONLY **£39.00**  
REF: MAG39

## SOLAR POWER PANELS

**3FT X 1FT 10WATT GLASS PANELS  
14.5v/700ma**

**NOW AVAILABLE BY MAIL ORDER  
£33.95**

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A  
TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE  
APPLICATIONS. SOME OF WHICH MAY BE CAR BATTERY  
CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANY-  
WHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

ALSO 1FT X 1FT GLASS SOLAR PANELS 12v 200mA  
ONLY £15.00. REF: MAG15P3

## FREE SOFTWARE!

Brand new, UNUSED top quality Famous brand  
licensed software discs. Available in 5.25" DSD or 5.25"  
HD only. You buy the disk and it comes with free BRAND  
NEW UNUSED SOFTWARE. We are actually selling you the  
floppy disc for your own 'MEGA CHEAP' storage facilities,  
if you happen to get software that you want/need/like as  
well..... you get a 'MEGA BARGAIN' to!  
DSD PKT10 £2.99 REF: MAG3P7 PKT100 £16.00 REF: MAG16  
HD PKT10 £3.99 REF: MAG4P3 PKT100 £26.00 REF: MAG26P1

LARGER QUANTITY PRICES AVAILABLE ON APPLICATION

\*\*\*\*\*WE BUY SURPLUS STOCK\*\*\*\*\*

TURN YOUR SURPLUS STOCK INTO CASH  
IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR  
COMPLETE FACTORY CLEARANCE.  
COMING SOON

## 1994 CATALOGUE

PLEASE SEND 42P, A4 SIZED SAE FOR YOUR FREE COPY.  
MINIMUM GOODS ORDER 45.00 TRADE ORDERS FROM GOVERNMENT, SCHOOLS,  
UNIVERSITIES & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO  
OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30  
DAYS RIGHTS REVERTER TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR  
NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILL ONLY GIVEN FOR QUANTITIES  
HIGHER THAN THOSE STATED.

\*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

**BULL ELECTRICAL**  
250 PORTLAND ROAD HOVE SUSSEX  
BN3 5QT

MAIL ORDER TERMS: CASH PO OR CHEQUE  
WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY  
TELEPHONE ORDERS WELCOME

TEL: 0273 303500

FAX: 0273 323077



**COMMODORE MICRODRIVE SYSTEM** mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just £12 REF: MAG12P1

**SCHOOL STRIPPERS** We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know now many you need at just 50p a unit (minimum 10).

**HEADPHONES 16P** These are ex Virgin Atlantic. You can have 8 pairs for £2 REF: MAG2P8

**PROXIMITY SENSORS** These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with flyleads. Pack of 5 £3 REF: MAG: 3P5 or 20 for £8 REF: MAG8P4

**FIBRE OPTIC CABLE** Made for Hewlett Packard so pretty good stuff! you can have any length you want (min5m) first 5m £7 REF: MAG7 thereafter £1 a metre (ie 20m is £22) REF: MAG1 Max length 250m.

**SNOOPERS EAR?** Original made to clip over the earpiece of telephone to amplify the sound-it also works quite well on the cable running along the wall! Price is £5 REF: MAG5P7

**DOS PACKS** Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual! 5.25" only.

**DOS PACK** Microsoft version 5 Original software but no manuals hence only £3 REF: MAG3P6 5.25" only.

**FOREIGN DOS 3.3** German, French, Italian etc £2 a pack with manual. 5.25" only. REF: MAG2P9

**MONO VGA MONITOR** Made by Amstrad, refurbished £49 REF: MAG49

**CTM644 COLOUR MONITOR.** Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished £59.00 REF: MAG59

**JUST A TALKIE SELECTION** of what we have to see more get our 1994 catalogue (42p stamp) or call in Mon-Sat 9-5.30

**HAND HELD TONE DIALERS** ideal for the control of the Response 200 and 400 machines. £5 REF: MAG5P9

**PIR DETECTOR** Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £3 REF: MAG8P5

**WINDUP SOLAR POWERED RADIO** AM/FM radio complete with hand charger and solar panel! £14 REF: MAG14P1

**COMMODORE 64** Customer returns but ok for spares etc £12 REF: MAG12P2 Tested and working units are £69.00 REF: MAG69

**COMMODORE 64 TAPE DRIVES** Customer returns at £4 REF: MAG4P9 Fully tested and working units are £12 REF: MAG12P5

**COMPUTER TERMINALS** complete with screen, keyboard and RS232 input/output. Ex equipment. Price is £27 REF: MAG27

**MAINS CABLES** These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects, low cost manufacturing etc. Pack of 10 for £3 REF: MAG3P8 Pack of 100 £20 REF: MAG20P5

**SURFACE MOUNT STRIPPER** Originally made as some form of high frequency amplifier (main chip is a TSA5611T 1.3GHz synthesiser) but good stripper value, an excellent way to play with surface mount components £1.00 REF: MAG1P1.

**MICROWAVE TIMER** Electronic timer with relay output suitable to make a larger timer etc £4 REF: MAG4P4

**PLUG 4207** showing your age? pack of 10 with leads for £2 REF: MAG2P11

**MOBILE CAR PHONE £5.99** Well almost complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

**ALARM BEACONS** Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG5P11

**FIRE ALARM CONTROL PANEL** High quality metal cased alarm panel 350x165x80mm. Comes with electronics but no information. £15 REF: MAG15P4

**SUPER SIZE HEATSINK** Superb quality aluminium heatsink 365 x 183 x 61mm, 15 fins enable high heat dissipation. No holes! £9.99 REF: MAG10P1P

**REMOTE CONTROL PCB** These are receiver boards for garage door opening systems. You may have other uses? £4 ea REF: MAG4P5

**LOPTX** Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones! £2 each REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3.

## PORTABLE RADIATION DETECTOR

**£49.99**

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30KeV to over 1.2MeV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.

REF: MAG50


CIRCLE NO. 104 ON REPLY CARD

# Quickroute

"... there is no doubt that running under *Windows* puts it ahead of the field and makes it a visually attractive package." **Electronics World + Wireless World July 1993**

*High Quality PCB and Schematic Design for Windows 3/3.1 and DOS*

- Supports over 150 printers/plotters including 9 or 24 pin dot-matrix, DeskJet, LaserJet, Postscript, and HPGL. Professional Edition imports GERBER files, and exports GERBER and NC-DRILL files.
- Up to 200,000 pads/track nodes depending on memory. Simple auto-router and schematic capture tools with SPICE compatible net-list output.
- Low cost DOS version (reduced features) also available. Ring for full details!

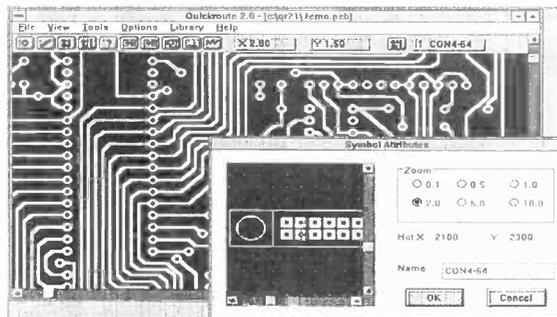

"Quickroute provides a comprehensive and effective introduction to PCB design which is a pleasure to use" **Radio Communication May 1993.**



POWERware, Dept EW, 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, UK.  
Ring us on 061 449 7101 or write, for a full information pack.


Quickroute is available for Windows 3/3.1 in Professional (£99.00) and Standard (£59.00) editions, and for DOS with reduced features (£39.00). All prices inclusive. Add £5 P+P outside UK.

from  
**£39**

CIRCLE NO. 105 ON REPLY CARD


## Electronic Designs Right First Time?

### Schematic Design and Capture

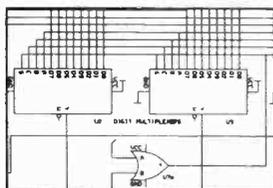


Create your schematics quickly and efficiently using EASY-PC Professional. Areas of the circuit can be highlighted on screen and simulated automatically using PULSAR, ANALYSER III and Z-MATCH our simulation and design programs.


### Digital and Analogue Simulation

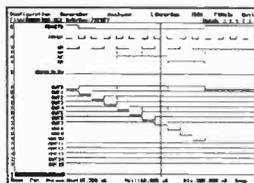

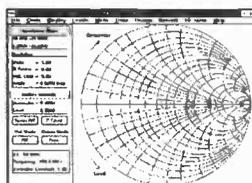Modify the configuration and change component values until the required performance is achieved.



### PCB Design

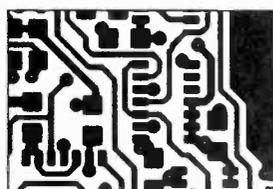

The design, complete with connectivity, can then be translated into the PCB. The connectivity and design rules can be checked automatically to ensure that the PCB matches the schematic.

Visa, MasterCard, Amex welcome

### Affordable Electronics CAD

<b>EASY-PC:</b> Low cost PCB and Schematic CAD	<b>£98.00</b>
<b>EASY-PC Professional:</b> Schematic Capture and PCB CAD. Links to ANALYSER III and PULSAR.	<b>£195.00</b>
<b>PULSAR:</b> Low cost Digital Circuit Simulator ~ 1500 gate capacity.	<b>£98.00</b>
<b>PULSAR Professional:</b> Digital Circuit Simulator ~ 50,000 gate capacity.	<b>£195.00</b>
<b>ANALYSER III:</b> Low cost Linear Analogue Circuit Simulator ~ 130 nodes	<b>£98.00</b>
<b>ANALYSER III Professional:</b> Linear Analogue Circuit Simulator ~ 750 nodes	<b>£195.00</b>
<b>Z-MATCH for Windows:</b> Smith Chart Program for R.F. Engineers	<b>£245.00</b>

No penalty upgrade policy. Prices exclude P&P and VAT.

### Number One Systems Ltd.

Ref WW. Harding Way, St. Ives, Huntingdon, Cambs. PE17 4WR, UK.

For Full Information Please Write, Phone or Fax.

**Tel: 0480 461778**

**Fax: 0480 494042**

CIRCLE NO. 106 ON REPLY CARD

# RESEARCH NOTES

## Macho behaviour that could unlock the universe

Three separate groups of astronomers say they have tracked down the mysterious dark matter that is believed to permeate the universe.

Cosmological theory has long suggested that there is much more to space than meets the eye – at least 90% more. So far this dark matter has remained elusive, with evidence for it coming largely from its effect on the universe we can see.

For the cosmos to behave as it does, scientists believe there must be something exerting a pronounced gravitational effect, a phenomenon that dominates the movements of the stars and something that will ultimately determine the fate of the universe.

Charles Alcock, Head of astrophysics at the Lawrence Livermore Laboratory in California, says that current measurements of the mass of our own Galaxy exceed the mass of what we can directly observe by a factor of between 10 and 20. So where is all this "missing mass"?

The first (and obvious) conclusion is that it can not exist in the form of stars or gas clouds, because if it did, it would not be dark. Nor can it exist as dust clouds, because it would periodically eclipse other, more luminous, objects. Cosmologists have therefore proposed the existence of several forms of exotic matter, such as axions, massive neutrinos and wimps – weakly interacting massive particles.

There is no real evidence that any such particles actually exist. So attention has turned to the search for more conventional forms of dark matter, objects such as planets and defunct stars. Real evidence for the existence of such objects in a halo around our galaxy has led astronomers to coin the memorable acronym for non-radiating things around the galaxy: machos - massive compact halo objects.

Back in 1986, Princeton Astronomer Bohdan Paczynski (with colleagues at the University of Warsaw and the Carnegie Institute in Washington) suggested machos might be detected by an effect called microlensing.

The idea is simple, and depends on a fact recognised earlier this century by Einstein, namely that a gravitational field can act as a sort of converging lens on light from a distant source. Astronomers have already discovered examples of what purport to be two identical stars, but which are actually a single star whose rays are bent along two different paths by the gravity of an intervening galaxy.

Paczynski reasoned that a macho would have a similar but less pronounced effect. Being small, it would not split the image of a distant star completely, but it might



How a macho results in microlensing – and points to the presence of dark matter.

modulate its intensity considerably as it passed between that star and Earth. Teams from Australia, France and the USA have all now simultaneously announced the discovery of what appears to be the first observations of microlensing. The groups found their evidence for dark matter from computer analyses of overlapping sky images.

Paczynski's group published its findings in the quarterly journal *Acta Astronomica*; the US/Australian and French groups gave details at scientific conferences in Italy, followed by publication in *Nature* (Vol 365,

No 6447). The fact that only a few microlensing events have been observed is not surprising, considering the precise alignment necessary. Paczynski calculates that the odds of any star being microlensed is about one in a million – even if 90% of the Universe consists of such stuff.

Ken Freeman of the Australian team at Mt Stromlo observatory says that, for each team to have found a single event strongly suggests that the halo around the galaxy is made up very largely of this kind of object, probably a dim star known as an M-dwarf.

## Organic leds offer bright prospects

Organic materials are set to make further inroads into electronic devices, following the announcement of a massive increase in the efficiency of polymer leds.

Polymer leds were first created by a Cambridge group in 1990 using PPV poly (*p*-phenylene vinylene) sandwiched between electrodes with a forward bias of 14V. This arrangement emitted yellow/green light with an internal efficiency of 0.01%. The system worked, but only just. For every 10,000 electrons injected into the material, only one caused the emission of a photon. Since then, the Cambridge team, from the University Chemical Laboratory and the Cavendish Laboratory, have made a leap forward. Using ingenious techniques they have raised the efficiency of their polymer light-emitting diodes to 4%, higher than for many inorganic leds.

First step in this search for greater efficiency lay in confining the singlet exciton generated in the polymer when opposite charges meet. In a led, these singlet excitons should ideally decay by emission of a photon. But what they often do is migrate to a quenching site where they decay without emitting any radiation.

Last year the Cambridge scientists published details of a co-polymer system designed to confine the singlet state and prevent non-radiative decay. Efficiency rose to 0.3% and it was possible by clever chemical processing to produce two colour emission (*J Am Chem Soc.* 1993, Nov 3). Further improvements came about by tackling the fact that, for most semiconducting polymers, holes are much



Patterned films of copolymer viewed in fluorescence. These are not the first polymer LEDs but they represent a significant step forward in terms of efficiency.

more easily injected than electrons.

Addition of a special electron-transporting layer was one ingenious way by which the team lifted the efficiency figure to 1%. What the Cambridge group have now done is to balance charge injection by chemically increasing the electronegativity of the polymer.

But the most recent development (*Nature*, Vol 365, No 6447) shows how cooperation between chemists and physicists can bring breakthroughs. Chemists Stephen Moratti and Andrew Holmes used what is called a Knoevenagel condensation to prepare co-polymers with cyano groups substituted along a PPV backbone. Physicists Neil Greenham, Donal Bradley and Richard Friend then designed a bi-layer device using this material, in conjunction with PPV and stable aluminium electrodes, to produce working leds.

The team attributes the 4% efficiency of the latest devices to the significant charge confinement at the interface between the PPV and the cyano-substituted material.

## Statistics complicate power line cancer search

Publication of more studies showing a positive, though small, correlation between AC fields from power lines and cancer means the still-inconclusive debate is set to rumble on.

Two studies, one in Finland and the other in Denmark (*The British Medical Journal*, Vol 307, No 6909) looked at children living near overhead power lines where exposure to an AC magnetic field was an order of magnitude greater than the level normally found in a typical home away from overhead power lines. They found the cancer risk was increased.

But Jorgen Olsen of the Danish Cancer Society and principal author of one of the studies admits that research in this area is made extraordinarily difficult by the fact that people frequently move home and that, at any one time, fewer than 0.5% of the childhood population live near power lines.


To make the statisticians' job even worse, cancer in children is extremely rare – regardless of where they live. With those provisos, Olsen explained in an interview for the BBC World Service that: "For those children who live near power lines [in Denmark] there is a significantly increased risk of childhood cancer when they are exposed to a magnetic field of more than  $0.4\mu\text{T}$ ."

To avoid undue alarm, Jorgen Olsen emphasises that there is no hard evidence to implicate the AC magnetic fields

directly. It could, he says, be some socio-economic factor or exposure to other factors that are merely associated with power lines. It is also worth pointing out, he says, that if magnetic fields are responsible, the risk must be extremely small. Otherwise, the widespread introduction of electricity 50 years ago would have led to a massive public health problem.

Olsen and his colleagues have checked the registration of cancer deaths in Denmark since the 1940s and as he says with blunt conviction: "We don't see any increase."

To make the whole scenario even more intriguing, there are reports from Russia of 100Hz magnetic fields being used to treat cancer. Researchers at the AZ Science and Production Association are said to have developed a "magnetoturbotron", a device rather like the stator of a large AC motor. The patient sits inside the device and is exposed to a powerful field that rotates at 6000rev/min. The rotating field produced is claimed to suppress the growth of various kinds of cancerous cells, especially those of the thyroid, breast and skin. The patient apparently sits inside and is given a dose appropriate to the condition, usually about 40min. No detailed results are available and no mechanism is suggested. The only curious observation is that the patient's temperature falls by one degree during the treatment.

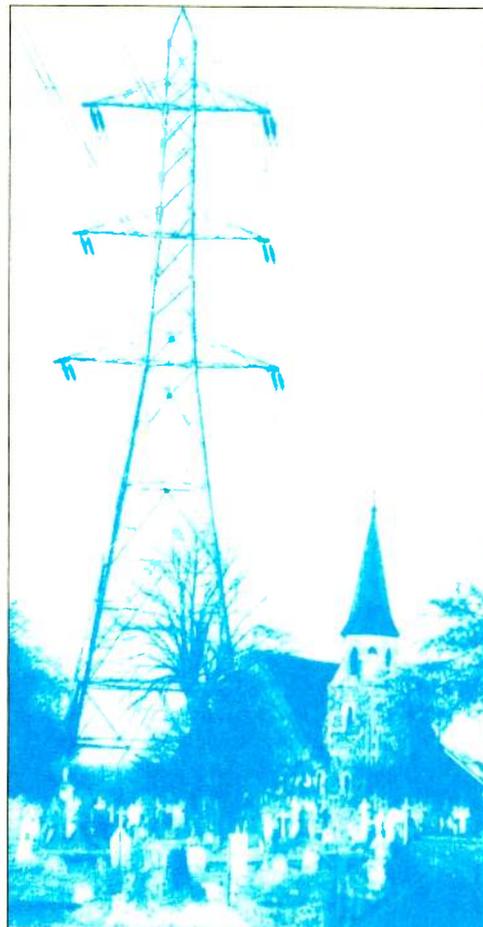

## Could a Magic Flute make you smarter?

Developing a taste for classical music could improve your intelligence... at least for a short while. But don't listen while you work, according to the Center for the Neurobiology of Learning and Memory at the University of California, Irvine, or you could overload your neurones.

The conclusions are the results of studying the IQs of 36 college students before and after they had listened to a variety of audio tapes.

Those who listened to a Mozart piece experienced a temporary IQ boost compared to those who had heard either a relaxation tape or nothing at all. Researcher Frances Rauscher, who led the study (*Nature*, Vol 365, No 6447) says that the results were conclusive beyond any doubt.

Tests were designed to measure one particular aspect of intelligence – spatial ability – and a typical example would be to imagine how a piece of paper with complex folds would look when unfolded.

All 36 students completed the exercise several times, following a period of silence, after listening to a relaxation tape or after listening to a recording of Mozart's Sonata in D major for two pianos (K448).

The IQ improvements were so marked that Rauscher estimates the odds of it happening by chance are only two in a thousand.

Lots of unanswered questions remain. The team still does not know how long the effect lasts. All that can be said is that it is less than 25 minutes.

Why Mozart boosts IQ is also a mystery. The only hypothesis is that the neuronal firing patterns of the brain in both music and in abstract reasoning skills are similar. So if those firing patterns are stimulated by listening to music, then they will be more ready to perform the sort of skills needed for spatial tasks.

Rauscher believes that Mozart is particularly good because the music has a complex structure and is therefore more

effective in exercising the relevant parts of the brain. She is now about to undertake experiments to demonstrate another hypothesis: that dull, thumping, repetitive music dulls the reasoning powers.

Eventually the Californian research team plans to carry out studies to find out if a person's taste in music affects the results, and whether musicians differ from non-musicians.

One thing is already abundantly clear: you can not boost your performance at any task requiring abstract thought if you listen to music at the same time. The reason is quite simply that the nerve pathways become overloaded trying to perform two similar functions in parallel.

So the next time someone claims their irritating tzz-t-t-zzz-t-t-zzz personal stereo is helping them concentrate – you can now offer at least two good reasons why it won't.

## Life found – but is it intelligent?

Of the 60-odd planets, comets, asteroids and moons encountered by our spacecraft, no mission has ever sent back unequivocal evidence of life. But would we recognise ET life, even if it were there?

This was a question tackled by a team of scientists led by Carl Sagan, Director of the Laboratory of Planetary Sciences at Cornell University. The team decided to turn the usual search for life upside down – and look for it on Earth. They did this with the help of an interplanetary probe that swooped in from space and visited the Earth three years ago.

Fiction? Not at all! The probe in question was Galileo, a spacecraft launched primarily to explore Jupiter. To reach the giant planet, Galileo had to head away from earth, then swoop back, using the Earth's gravitational attraction as a sort of slingshot to gain extra momentum before heading off to the giant planet. It was on this return path that Sagan and his colleagues decided to put its equipment to the test by studying our own planet. They agreed, for the purposes of this study, that life on Earth would be a "hypothesis of last resort".

Galileo analysed reflected light from the Earth to determine the nature of the atmosphere and the surface chemistry. Sagan says: "We saw the continents of the

Earth tainted with a strange pigment that absorbs light in a very special way, just beyond the red end of the spectrum." The team had discovered chlorophyll, the green pigment in plants.

They also discovered oxygen in the atmosphere, something that would be hard to explain except for the existence of some sort of life processes.

Where Galileo failed to find any trace of life was when it looked for evidence of artificial structures. In the course of examining 4% of the Earth's surface at a resolution of 1km, nothing was found at all – a cautionary lesson for those who expect to find huge artificial structures on alien planets. But Galileo scored a resounding triumph when it searched the Earth in the radio spectrum.

Scanning the hf region, the probe discovered hundreds of signals with forms of modulation that could not have been generated by any known natural system. These signals, say the scientists, must have been coming from the Earth's surface because their escape was blocked by ionised layers (the ionosphere) in a way that was dependent on the presence or absence of sunlight.

Reluctantly, the team concludes from the Galileo observations that there must be some



*To test how successful we might be at detecting whether there is life on other planets, scientists tried finding it here on Earth via Galileo.*

sort of intelligent life on Earth. A trivial exercise? Not at all. The real lesson is that if we want unequivocal evidence of life elsewhere in the cosmos, we might as well forget photography and chemistry and concentrate on good old short wave radio!

## Making less of a meal of image analysis


In theory a computer can solve any problem – given enough processing power. But looking at all the options and choosing the best is a sledge-hammer approach. In the real world, computing power costs money and researchers are for ever striving to develop more efficient software.

At Rochester University in New York, graduate Ray Rimey has been looking at new ways for computer vision systems to analyse images. In the past, researchers involved with artificial intelligence have often overlooked the fact that robots need to be selective in where they put their attention. Ray's work is devoted to structuring which methods the computer should adopt and in what order.

"A computer only has so much processing power," says Rimey. "If it needs to solve a problem in a given amount of time, it needs to prioritise. A doctor analysing a patient could run endless tests costing thousands of dollars but it could take so long that the patient could die. Instead, a doctor uses prior knowledge to decide on tests needed to maximise useful information and minimise diagnosis time," adds Rimey.

Analysing different kinds of place settings for a dining table proved to be a perfect test.

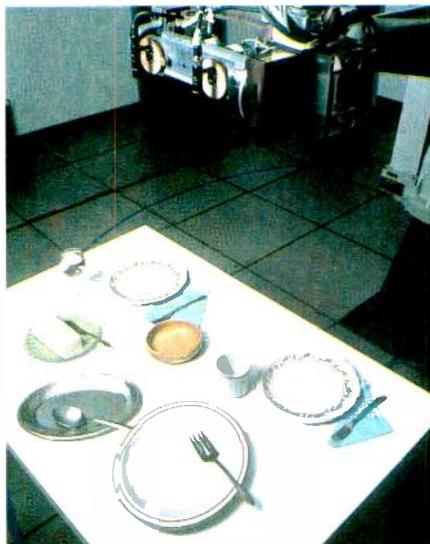Rimey taught his robot to collect visual clues and sequentially gain confidence in its answer. It could tell, for example, whether the setting is formal or informal and whether it was breakfast, lunch, dinner or desert. The



*Dinner service – according to researchers at Rochester in New York, place settings are an excellent test of a robot's analytical capabilities.*

method extends to judging whether the table is messy, how many guests there are, and whether they have begun eating.

The focus of the research is on teaching a processing system how to scan a scene and home in on the most important information. As well as helping set the table, this work is expected to be useful in applications including medical diagnostics and satellite image analysis.

Rimey taught the robot its analysis tricks through extensive programming using decision theory and mathematical constructs known as Bayes Nets. His computer vision system is due to be described in a forthcoming issue of *International Journal of Computer Vision*.

Honeywell is said to be interested in using Ray's ideas to analyse infrared images from roving vehicles. Colleagues of his are also interested in tracking moving objects such as trains and cows. Others are investigating decisions involving both observing and interacting with moving objects, namely herding mechanical sheep. We will be following that one closely.

*Research Notes is written by John Wilson of the BBC World Service.*

# Microprocessor controlled power supply

*Adding a microprocessor brings new meaning to the word power in power supply. This cost-effective design from Matthew Rahman and Robin Thick features a user friendly interface.*

This design is for those of you who are fed up with tweaking a potentiometer every time you want to set the voltage on your power supply. As described, the system provides microprocessor control for two positive and two negative output supply lines. By breaking the design down into modules however, any combination of output rails can be created.

The design is economical yet comparable to commercial supplies costing many hundreds of pounds. It originally formed part of a project that we undertook as part of our training as air traffic engineers with the Civil Aviation Authority and is fully tested.

## Specifications

When implemented in full, the design allows keypad entry of two independent positive and negative voltage outputs, each programmable to a resolution of 100mV from 0V to 25V. All outputs can deliver nominally about 1.2A across the whole voltage range. Below 18V current capability rises to 1.5A.

Each output can be monitored if need be. By feeding the monitoring information back to the microprocessor, software correction can be applied to the outputs to stop the voltage drifting. This feature also forms part of a digital voltmeter function included in the software.

A standard liquid-crystal display module displays all operations and other information. It is possible to use a larger display without

modifying the design, but the software held in rom may need to be modified.

Other features when the full design is used with our software include audible feedback for the keypad, output voltage tracking and program memories to store all your settings. Single stepping of the voltage from the keypad in either 100mV or 1V steps is also possible.

## System overview

At the heart of the design is a Z80 microprocessor with 8Kbyte rom and 2Kbyte ram. Figure 1 is a basic block diagram of the microprocessor control unit showing that each voltage output can be independently controlled via a digital to analogue converter, or dac.

Sampled input voltage is in fact multiplexed and can be any one of the output voltages selected by an analogue switch controlled by the processor. This has the advantage of reducing costs by requiring only one analogue to digital converter, ADC.

There are 20 keys on the entry keypad. All of the decoding is done by software to simplify the keypad scanning electronics relatively simple.

The liquid crystal display is a 2-line-by-20-character module. We recommend a backlit type but a standard reflective type could easily be used.

Figure 2 shows a block diagram of two of the four voltage regulators used in this design. Channels 1 and 3 are positive outputs while channels 2 and 4 are negative, each with current limited outputs. These circuits will be discussed later.

## Microprocessor unit

Figure 3 shows the circuit diagram of the main microprocessor unit and its related control circuits. The circuit is fairly standard and operates as follows.

Clocking of the Z80 CPU, IC<sub>1</sub>, at 2MHz is performed by the crystal oscillator circuit based on IC<sub>2</sub>. This frequency is divided down using a ripple counter, IC<sub>3</sub>, to provide a 125kHz clock for the analogue-to-digital converter. Note that it may be necessary to tweak the variable capacitor C<sub>2</sub> to obtain the correct pulse shape for the Z80.

On power-up, the reset line on pin 26 of IC<sub>1</sub> is pulsed low by means of C<sub>1</sub> and R<sub>6</sub>. All

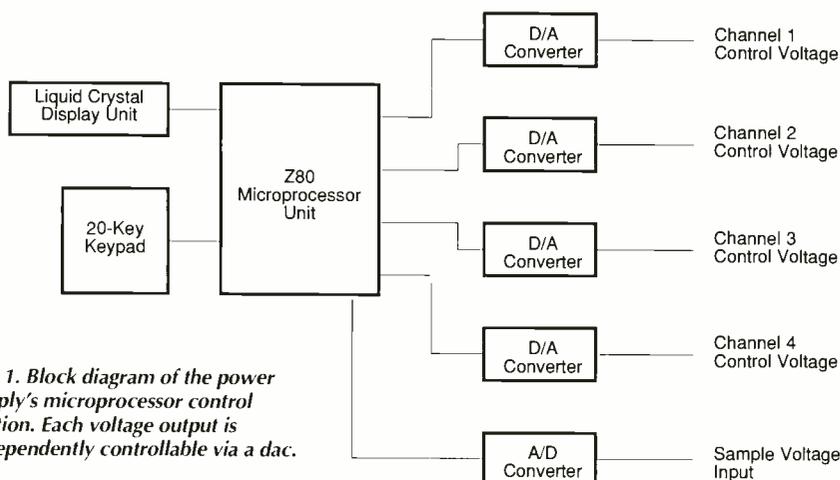


Fig. 1. Block diagram of the power supply's microprocessor control section. Each voltage output is independently controllable via a dac.

unused control pins are taken to the positive supply via 10kΩ resistors. The clock pin is also pulled up via  $R_5$  to ensure that the minimum 4.4V is present for a high pulse.

Address and data lines are connected conventionally to the 8K rom,  $IC_2$ , and 2K static ram,  $IC_3$ . Addresses for these and other devices are decoded by  $IC_7$ . This IC is a 3-to-8-line decoder dividing the 64K address space into 8Kbyte block outputs, used to select external devices when addressed. The ram only occupies 2K of address space and has not been fully decoded for ease of design. As a result, the ram is shadowed throughout the second 8K block. This is not a problem since nothing else occupies any of that block.

A select line for i/o devices, such as digital to analogue converters, and a line for the LCD are also provided by  $IC_7$ . A complete memory map of the system is shown under the software explanation later. The ram is battery backed. It holds data about the system and stores several user settings which need to be retained when the unit is switched off.

To prevent data being corrupted when the ram is in standby mode, the select line to the ram's chip select input, CS, is gated via  $IC_8$  with a line called POWER\_STATE from the battery back-up circuit. This ensures that the ram is de-selected when the main power is not pre-

Fig. 2. Two of the four programmable-voltage regulators. Channels 1 and 3 are positive, channels 2 and 4 negative, each with current limiting.

sent. Circuit  $IC_8$  is powered by the +V<sub>bb</sub> supply.

Finally, a free-running 555 timer,  $IC_6$ , is used to generate a pulse for the processor's interrupt line, INT. It runs at approximately 12Hz with a very small duty cycle to prevent it from still being low when the processor

completes the interrupt service routine.

Details about the software used are presented further into the article.

### Data input/output

Figure 4 shows the input/output address decoder for the processor. Decoder  $IC_9$  is only

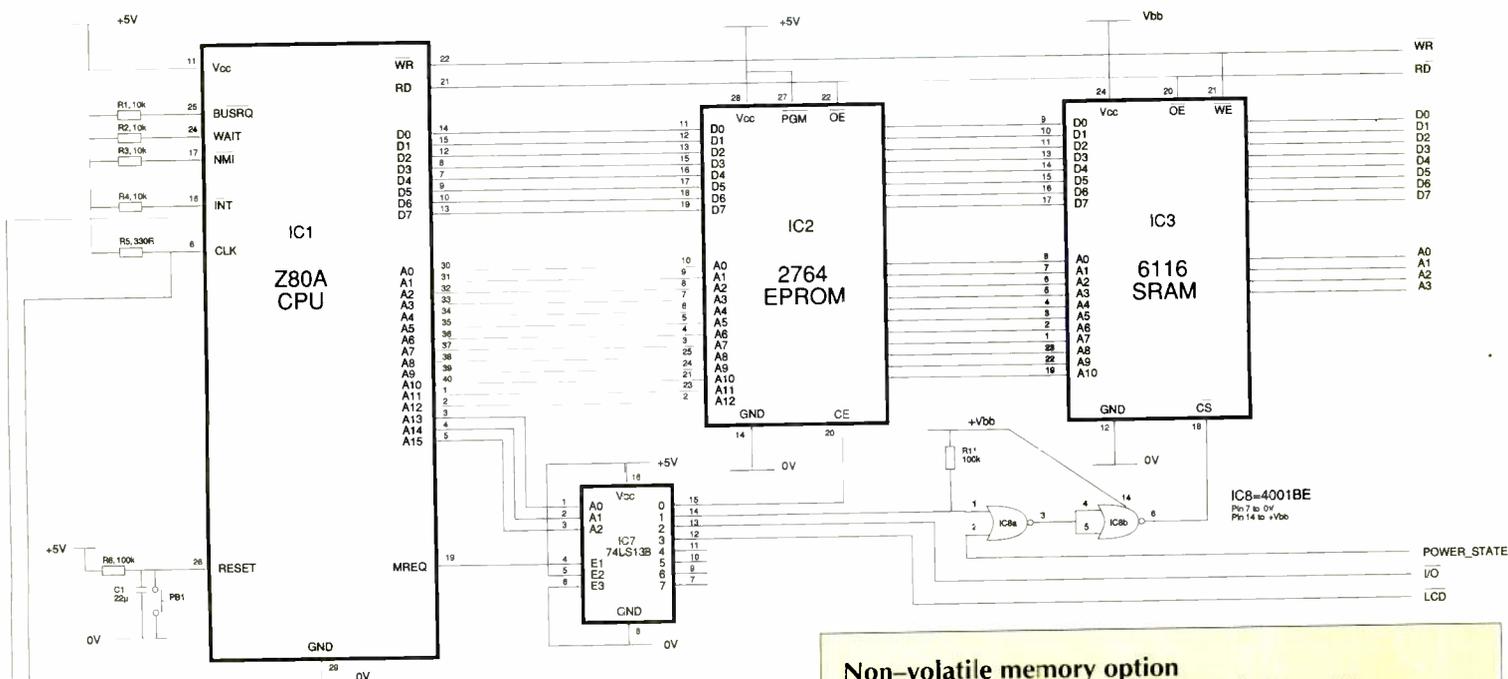
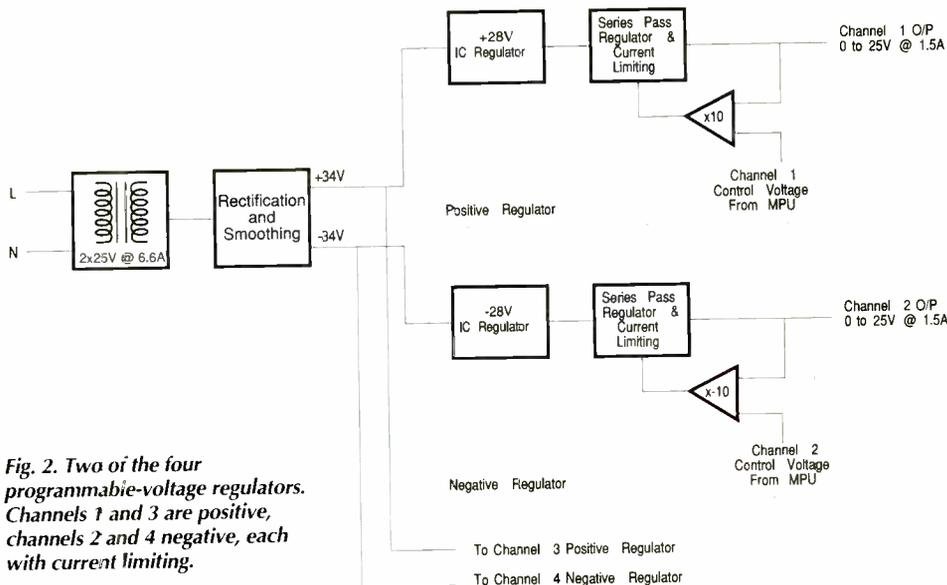



Fig. 3. Main Z80 microprocessor unit with related control circuits. Address decoding and bussing are straightforward. The 555 timer provides interrupts at 12Hz while the divider produces the signal for clocking the data converter.

**Non-volatile memory option**

For designers wanting to simplify ram back-up, Xicor manufactures static rams with *Novstor* – a technology that automatically saves the contents of ram to its own internal eeprom on power-down and recall them back on power-up. Quoted data-retention time for these parts is a minimum of 100 years and  $10^6$  write cycle to the eeprom can be performed.

Because they are quite new on the market we have yet to use them in this application, but we don't envisage any problems with them. With these devices, the control gates of  $IC_8$  and the battery back-up supply can be eliminated. The Xicor 20C17 could be used as a replacement for the 2764 in our design.

**Fig. 4. Input/output address decoder with control dacs.** This second decoder enables one location between 400016 and 400716 when i/o from the first decoder and MREQ are active.

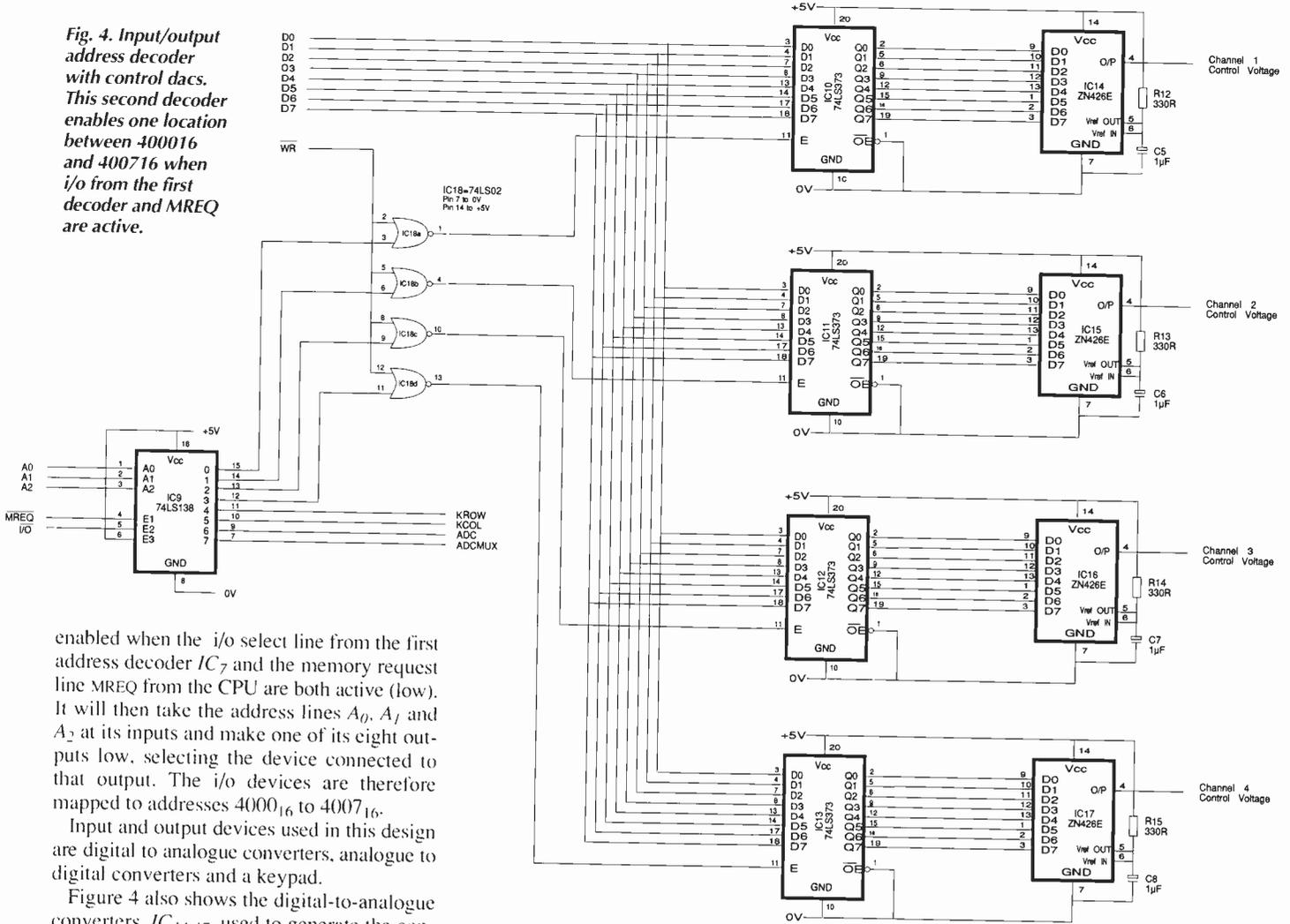

enabled when the i/o select line from the first address decoder IC<sub>7</sub> and the memory request line MREQ from the CPU are both active (low). It will then take the address lines A<sub>0</sub>, A<sub>1</sub> and A<sub>2</sub> at its inputs and make one of its eight outputs low, selecting the device connected to that output. The i/o devices are therefore mapped to addresses 4000<sub>16</sub> to 4007<sub>16</sub>.

Input and output devices used in this design are digital to analogue converters, analogue to digital converters and a keypad.

Figure 4 also shows the digital-to-analogue converters, IC<sub>12-15</sub>, used to generate the control voltage for each of the voltage regulator circuits. The resistor on each dac, R<sub>12-15</sub>, is required to load the internal reference voltage and capacitors C<sub>5-7</sub> decouple the reference. Output from each dac is between 0V and 2.55V depending on the binary value in its data inputs (0 to 255).

The dacs used here do not have internal data latches so the job of latching the data from the processor is performed by 74LS373 octal latches, IC<sub>10-13</sub>, between the data bus and each dac. When the Z80 wants to write data to a dac, its corresponding latch is selected by the address decoder which clocks in the data from

the data bus and holds it until changed again by the Z80. The nor-gate IC<sub>18</sub> on the clock input pin 11 of each latch ensures that data is changed only when write line WR is low, i.e. when the processor is actually writing.

It is quite feasible to replace these converters with other types, maybe ones that include latches or are more accurate, so long as the addressing is the same.

**Lcd module**

This design has the added flexibility of using a dot-matrix liquid crystal display, rather than the standard 7-segment led types found on commercial units. With this, the status of all four outputs can be monitored simultaneously and menus can be used when setting up the system. It is also more user-friendly when entering commands on the power supply's keypad.

Our design uses the Hitachi LM032L LCD module, a 2-line-by-20-character display which can be bought for less than £20. Connection of this to the processor is shown in Fig. 5.

You are not restricted to using this particular module, and you may want to use a larger 4-line display or any other Hitachi or Densitron display that has a HD44780 controller IC. We

recommend that if you use our software, then the LM032L type or its backlit equivalent should be chosen.

Circuit IC<sub>21a</sub> acts as an inverter to provide an active high ENABLE line.


**Keypad scanning**

Rather than use a dedicated keypad scanning chip, we decided that a simple scanning circuit could be used under control from the micro-processor.

Figure 6 shows that the circuit uses just one octal latch IC<sub>20</sub> and one octal buffer, IC<sub>19</sub>. The processor writes data to the keypad latch and reads the result of any key presses by enabling the buffer to transfer data to the data bus. Details of how the software does this will be explained later.

In addition, the latch will control a 'KEYPAD ENTRY' led and a piezo sounder. Buffer IC<sub>19</sub> also accepts the BUSY signal from the analogue to digital converter, discussed later.

Layout for the keypad switch matrix can be seen in Fig. 7, with the keypad's legend for each key also shown. The keypad used in the our original design was a Maplin 20-way membrane type. Pin connections shown in brackets in Fig. 7 correspond to this particular keypad.

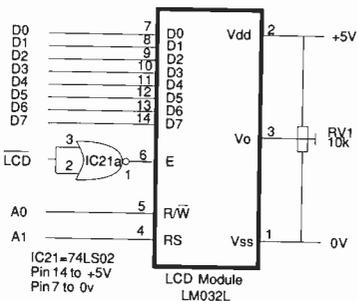

**Fig. 5. Interfacing the Hitachi LM032L liquid-crystal display - a two line by 20-character display costing under £20. Viewing angle is optimised via the potentiometer.**

### Output voltage regulation

Final output from the power supply is a regulated, current limited supply from 0 to 25V, providing up to 1.5A.

Figure 8 shows the circuit for one positive and one negative output. The positive regulator works as follows. The positive 34V rail from the mains transformer is regulated by a standard monolithic regulator, IC<sub>21</sub>, programmed to provide 28V. This is a smooth, noise free output and gives protection against overload from the next stage. Devices Tr<sub>1</sub>, 2 and IC<sub>22</sub> form the final output regulator.

Op-amp IC<sub>22</sub> takes the control voltage from the dac and amplifies it by 10 to produce an output of 0 to 25V. Transistor Tr<sub>1</sub> current amplifies this voltage using the supply from IC<sub>21</sub>, while Tr<sub>2</sub> and R<sub>28</sub> form a fold-back current limiting circuit at approximately 1.5A. Feedback is provided by R<sub>29</sub> and RV<sub>2</sub>.

The negative regulator works in a similar way, except that the control voltage is inverted to a negative value by IC<sub>24a</sub> before being amplified by IC<sub>24b</sub>. Note also that IC<sub>24</sub> uses a positive supply of +5V in addition to its -28V supply. The -28V regulator takes its power from the -34V supply. Heatsinks with suitable compound must be used for all the power transistors and voltage regulators, as a fair amount of heat needs to be dissipated by the devices. Additional cooling can be achieved by adding a small 12V fan. We found using a fan very effective in keeping the ambient temperature low inside the case.

Output voltage is set up using the variable resistors in the feedback circuit of the regulator, RV<sub>2,3</sub>. To do this it requires the control

Fig. 8. Channels 1 and 2 of the main output voltage regulation circuitry. Two variable regulators provide preregulation down to 28V. The op-amps and TIP transistors vary output under control of the dacs while the BC transistors add current limiting.

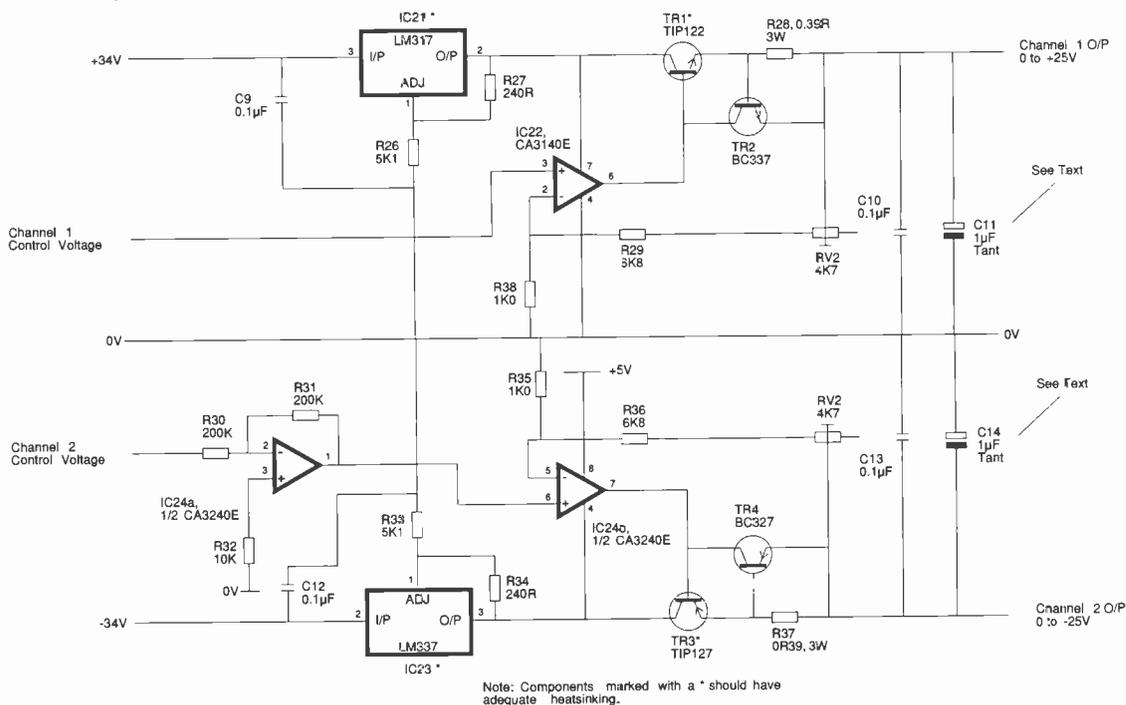


Fig. 6. Scanning the keypad is carried out by the microprocessor with the aid of these two octal latches. Column/row labels correspond to those on Fig. 7. Note that BUSY from the ADC uses the same register.

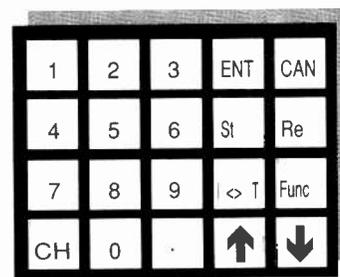
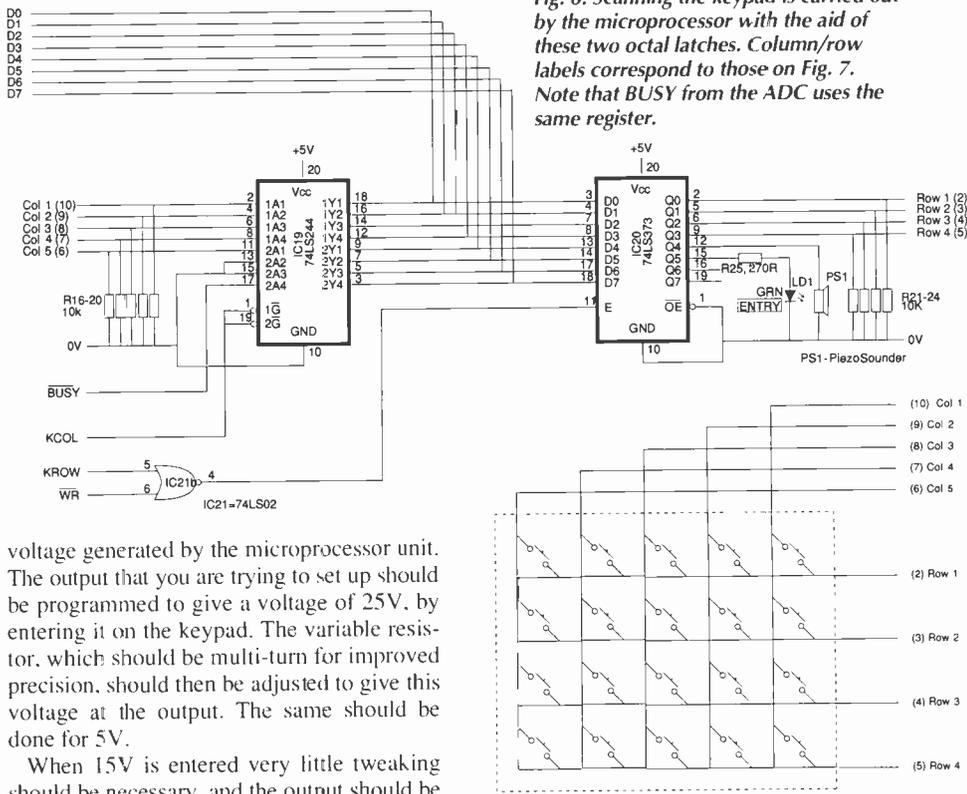


Fig. 7. Layout and legending for the power supply's keypad switch matrix. Using software to read the keypad avoids using a dedicated key decoder IC.

voltage generated by the microprocessor unit. The output that you are trying to set up should be programmed to give a voltage of 25V, by entering it on the keypad. The variable resistor, which should be multi-turn for improved precision, should then be adjusted to give this voltage at the output. The same should be done for 5V.

When 15V is entered very little tweaking should be necessary, and the output should be accurate across the range 0 to 25V with an error of 200mV or so. When setting up the outputs, the correction option should be switched off if using our software.

Capacitors C<sub>11</sub> and C<sub>14</sub> are used for suppressing digital noise from the microprocessor. We found that these were best placed directly at the output connectors, inside the case, to eliminate any noise picked up in the wires along the way.

### Analogue to digital converter

The analogue to digital converter circuit, Fig. 9, is included so that each output can be mon-

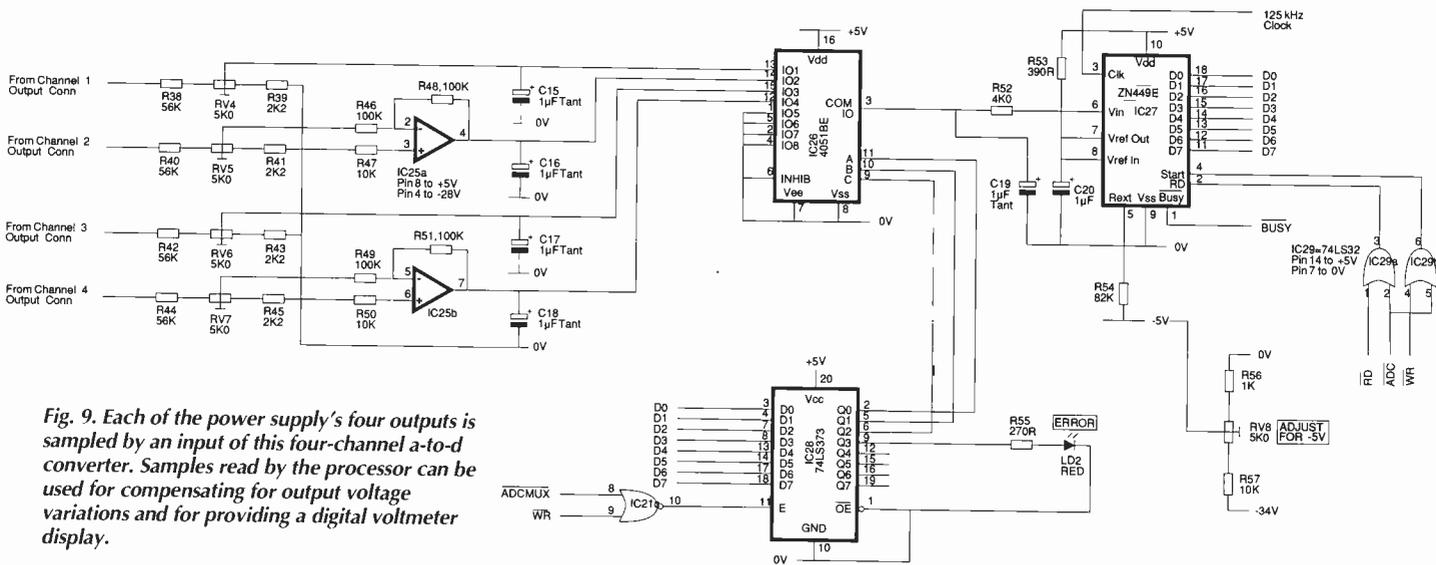


Fig. 9. Each of the power supply's four outputs is sampled by an input of this four-channel a-to-d converter. Samples read by the processor can be used for compensating for output voltage variations and for providing a digital voltmeter display.

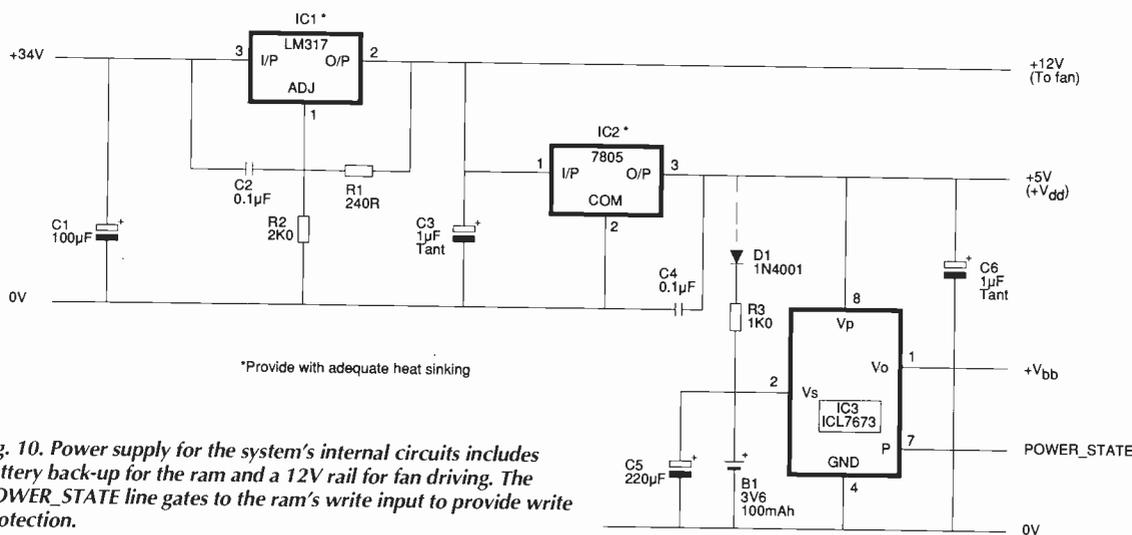


Fig. 10. Power supply for the system's internal circuits includes battery back-up for the ram and a 12V rail for fan driving. The POWER\_STATE line gates to the ram's write input to provide write protection.

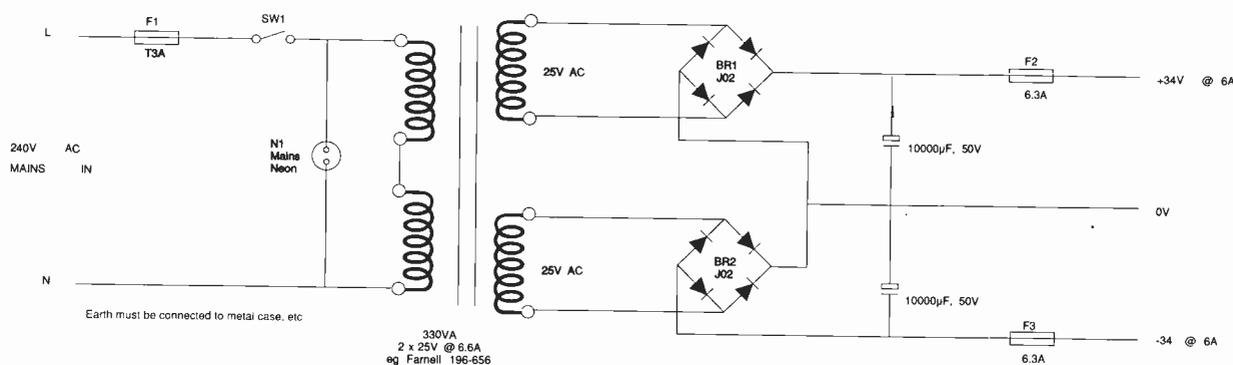


Fig. 11. Mains isolation and rectification. The toroidal transformer we used was conservatively rated. If a smaller one is used, it should be capable of providing at least 4A per winding.

itored and, if required, corrected for small errors. This allows the inclusion of a digital voltmeter function so that the true output voltages can be shown on the display.

First of all, each output voltage is tapped off and attenuated by a resistor network to give a tenth of its value. Current actually drawn from this tap-off is so minimal that it is perfectly

feasible to use a resistor divider.

Variable resistors  $RV_{4,7}$  should be adjusted so that one-tenth of the channel output voltage appears at the input of the analogue switch. This ensures that the conversion will be fairly accurate. Using multi-turn pots improves the precision at which the voltages can be set-up. Negative voltages are inverted by  $IC_{25}$  to

give a positive voltage. Each sample of voltage is decoupled by  $C_{15-18}$  to remove any digital noise. The signals are then fed to analogue switch  $IC_{26}$ . Via latch  $IC_{28}$ , the microprocessor selects the channel to be converted by the ADC,  $IC_{27}$ . The latch also drives the ERROR LED.

The microprocessor tells the ADC when to

### Microprocessor controlled power supply – features

- User-friendly interface
- Keypad programming of each output
- Switchable audio feedback for keypad
- Settings remembered from when the unit was last used
- Nine memories for storing different voltage configurations
- Single key stepping of voltage in 100mV or 1V increments
- Tracking of positive and negative channels – user-selectable
- Automatic error correction for outputs – user-selectable
- Digital voltmeter optional display
- Options all menu-driven

start converting and monitors the BUSY line, via  $IC_{19}$ . In this way it knows when the ADC has finished converting before reading the sampled data. A 125kHz sample clock is used, derived from the system clock, making a conversion period of approximately 75 $\mu$ s.

In the ZN449 data sheet, it states that the chip needs a negative supply for the tail current of the fast comparator. This is a very low current of about 150 $\mu$ A maximum and can be derived by connecting pin 5 to a -5V supply via an 82k $\Omega$  resistor. Rather than generate another power supply regulator just for this, we used a potential divider,  $R_{56,57}$  with  $RV_8$ , to derive -5V from the main -34V supply. Potentiometer  $RV_8$  should be adjusted for -5V without it being connected to the ADC and  $R_{54}$  to prevent any large voltages appearing at pin 5 of the chip.

Improving the accuracy of conversion can be done by using the pin-for-pin compatible ZN447 or ZN448 ADCs instead of a ZN449 but these tend to be more expensive.

### Internal circuit supplies

Nearly all of the internal control circuits run from a single +5V supply, apart from the ADC which has been dealt with above. A battery back-up supply is also required for the ram. Figure 10 is the circuit for the internal supplies.

First of all, the main +34V has to be reduced since it is too high for the 7805 1A voltage regulator,  $IC_2$ , used to power all of the internal circuits. Stepping-down is done by a LM317,  $IC_1$ , which can take a 34V input. It is programmed for a regulated output of 12V (it is actually more likely to be about 11.7V) at 1.5A. A 12V fan can be driven from this supply, if required. It is probably a good idea to use a fan, as the regulators and power transistors get hot.

Monitoring the +5V supply is a battery back-up switch,  $IC_3$ . This will switch in the battery to power the ram and its control gates. It generates a signal telling the ram control gates the state of the power to prevent writes to the ram when the main +5V is down.

The battery we used was a 100mAh 3.6V

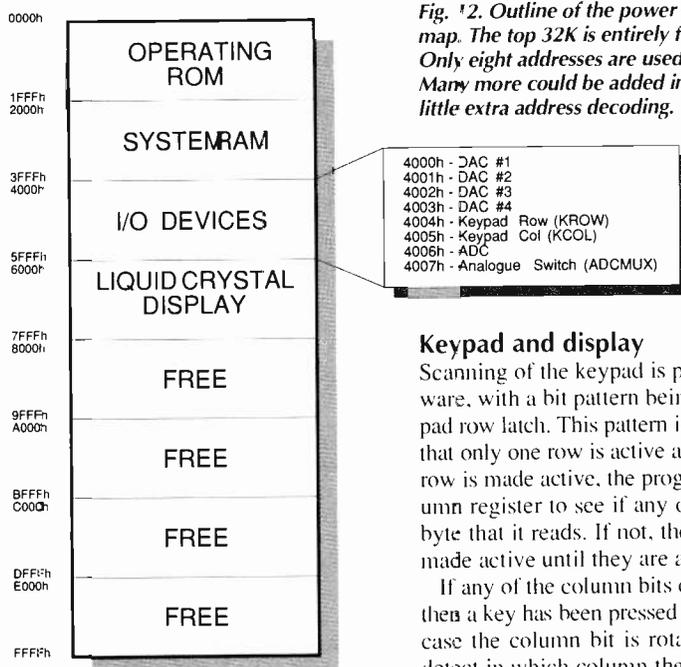


Fig. 12. Outline of the power supply's memory map. The top 32K is entirely free for expansion. Only eight addresses are used for i/o devices. Many more could be added in this area with a little extra address decoding.

### Keypad and display

Scanning of the keypad is performed by software, with a bit pattern being sent to the keypad row latch. This pattern is a walking one so that only one row is active at any time. After a row is made active, the program reads the column register to see if any ones appear in the byte that it reads. If not, then the next row is made active until they are all done.

If any of the column bits does contain a one then a key has been pressed in that row. In this case the column bit is rotated so that it can detect in which column the key was pressed. Rotating the bits this way means that the first bit it comes to, it accepts, avoiding any ambiguity if more than one key is pressed.

Now that the program knows the row and the column in which the key was pressed, it can convert this into a key scan code, say between 1 and 20. This can be done by multiplying the column number (0 to 4) by 4 and then adding the row number, assuming a 20-way keypad is used.

This operation is laid out in the flow chart Fig. 13. Suggested layout for the keypad was shown earlier in Fig. 7. Functions of each key is explained in Table 1, along with its key scan number.

Programming the LCD is pretty straight forward, but we recommend that the data sheet is to hand so that you have access to all of the commands available. The LCD module used here has four addresses, Table 2.

To send a command to the display, you just write a command byte to address 6000<sub>16</sub>. A list of some of the commands, along with their command byte is given in Table 3.

Flow diagrams are shown in Fig. 14 for the processes of writing a character to the display, (a), and sending a command to the display, (b). Our software includes many subroutines for the display functions, taking all of the hard work out of dealing with cursor positions, displaying strings etc.

NiCd type which will probably preserve the data in the ram for many months without the unit being switched on. While the unit is on, the battery is charged via  $D_1$  and  $R_3$ .

Figure 11 is the mains input and  $\pm 34$ V supply circuit. For stepping down the mains, we used a toroidal transformer with two 25V windings delivering up to 6.6A each. A smaller transformer will suffice, but it must be able to deliver at least 4A per winding. The 10000 $\mu$ F capacitors are recommended for a smooth supply when drawing large currents.

### Software

A disk is available from EW&WW containing all of the software required for a complete system that is even better than commercial systems we have seen. The complete rom dump is 4Kbyte and contains the features shown in the panel.

In Fig. 12 you can see a diagram outlining the power supply's memory map. The first 8K of address space is taken up by the rom while the next 8K is occupied by the ram, only 2K of which is used). Input/output devices take up the next 8Kbyte but as you can see from Fig. 12, only eight addresses are used. This leaves plenty of room for expansion. The liquid crystal display occupies four addresses from 6000<sub>16</sub>. Remaining address space is free.

### LED/beeper driving

Both LEDs and beeper are programmed via existing latches. Address and bit numbers of each device are as follows

Piezo beeper	Addr 4004 <sub>16</sub>	Bit 4	Used for audio feedback and warnings
Entry led	Addr 4005 <sub>16</sub>	Bit 5	Visual feedback for keypad
Error led	Addr 4007 <sub>16</sub>	Bit 3	Used when the system encounters an error

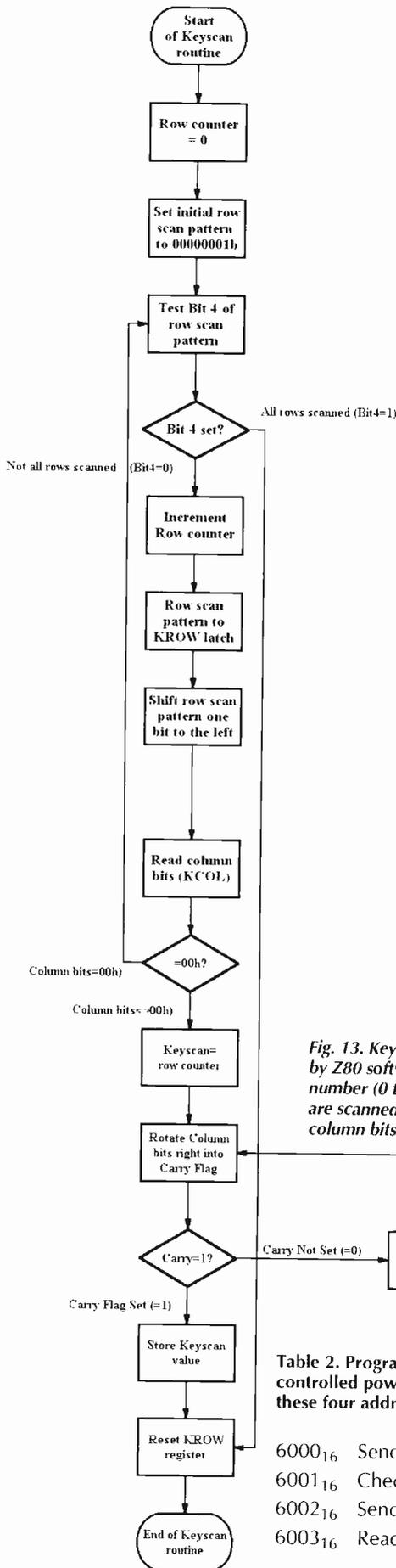


Fig. 13. Key presses are converted to a code between 1 and 20 by Z80 software. This is done by multiplying the column number (0 to 4) by four and then adding the row number. Rows are scanned, columns are read. If a key press is detected, column bits are read by rotating to avoid ambiguities.

Table 2. Programming the LCD used for the microprocessor controlled power supply is straightforward. The display has these four addresses.

6000 <sub>16</sub>	Send command to display controller	Write
6001 <sub>16</sub>	Check if the display is ready or busy	Read
6002 <sub>16</sub>	Send character to display ram	Write
6003 <sub>16</sub>	Read data from display ram	Read

Table 1. Assigning these functions to the power supply's keypad makes for an ergonomical design.

Label	Function	Key scan No
Command entries...		
[CAN]	CANCEL current operation	1
[ENT]	ENTER or accept command or entry	5
[ST]	STORE present voltage and tracking settings to one of the nine memories	6
[RE]	RECALL one of the nine memories	2
[I<>T]	TOGGLE tracked and independent output modes for channels 1&3 or 2&4, which ever was last selected	7
[FUNC]	GO INTO FUNCTION mode. Pressing one of the nine number keys will short cut into a function. Pressing [FUNC] again brings up the function menu.	3
[UP]	INCREMENTS currently selected output by 1V or 100mV, whichever is chosen	8
[DOWN]	DECREMENTS currently selected output	4
[CH]	SELECT another CHANNEL to program. Followed by channel number, 1-4)	20
Numeric entries...		
[.]	Decimal point	12
[0]	Zero	16
[1]	One	17
[2]	Two	13
[3]	Three	9
[4]	Four	18
[5]	Five	14
[6]	Six	10
[7]	Seven	19
[8]	Eight	15
[9]	Nine	11

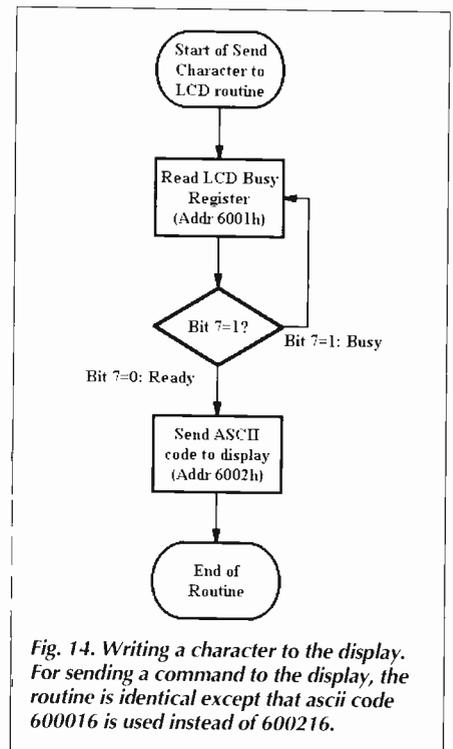


Fig. 14. Writing a character to the display. For sending a command to the display, the routine is identical except that ascii code 600016 is used instead of 600216.

## Comprehensive software on disk

A disk containing software and supplementary information can be obtained by sending a cheque or postal order for £10 plus vat to EW&WW's editorial offices at the address in the front of the magazine. Included on this disk is the hex dump in various formats – ascii, Motorola, etc. – for downloading into an eeprom programmer. There is also a user manual that can be printed out, in various word processor formats and ascii, together with details of how you can obtain a preprogrammed rom. In addition, an assembly listing is included so that you can modify the program. The assembly listing is fully annotated, and is built up from a library of subroutines. This helps the programmer enhance the software easily as all entry and exit conditions are given for most subroutines. The program includes many arithmetic, i/o and display subroutines.

### System initialization


The first things that should be done when the unit is powered up are to initialise any variables and registers and set up the processor's stack and interrupts. A flow chart for general initialization is shown in Fig. 15. Initially, the dacs are reset to prevent spurious voltages from appearing at the outputs on power-up. In our software, the outputs are then restored to their previous state before the unit was switched off.

Figure 16 shows the process involved in entering a voltage for a particular channel. Routines are needed to decode keypad entries and error-check the entries, ensuring no illegal values are entered. This entry would then be converted to BCD for storage and conversion to ascii is required to echo entries to the LCD. Finally, the entered voltage has to be converted to an eight-bit binary number ready for writing to the appropriate dac address location.

### Adc sampling

Figure 17 shows the process of sampling a voltage via the analogue to digital converter. First, the analogue switch should be programmed to select the correct input. It may be a good idea to introduce a short delay of, say, a few milliseconds, to allow the voltage to settle. Conversion can then be started by writing any byte to the ADC. The status of the ADC can be monitored by reading bit seven of address 4005<sub>16</sub>. When it is set, data is available for reading at address 4006<sub>16</sub>.

By using the above functions, a more simple or a complex system can be built up with whatever features you want. There is plenty of expansion space, in regards to memory addressing, for adding features. For example, an RS232 interface could be added so that the unit may be connected to a PC for use as automatic test equipment. We are currently working on such an interface at the moment. ■

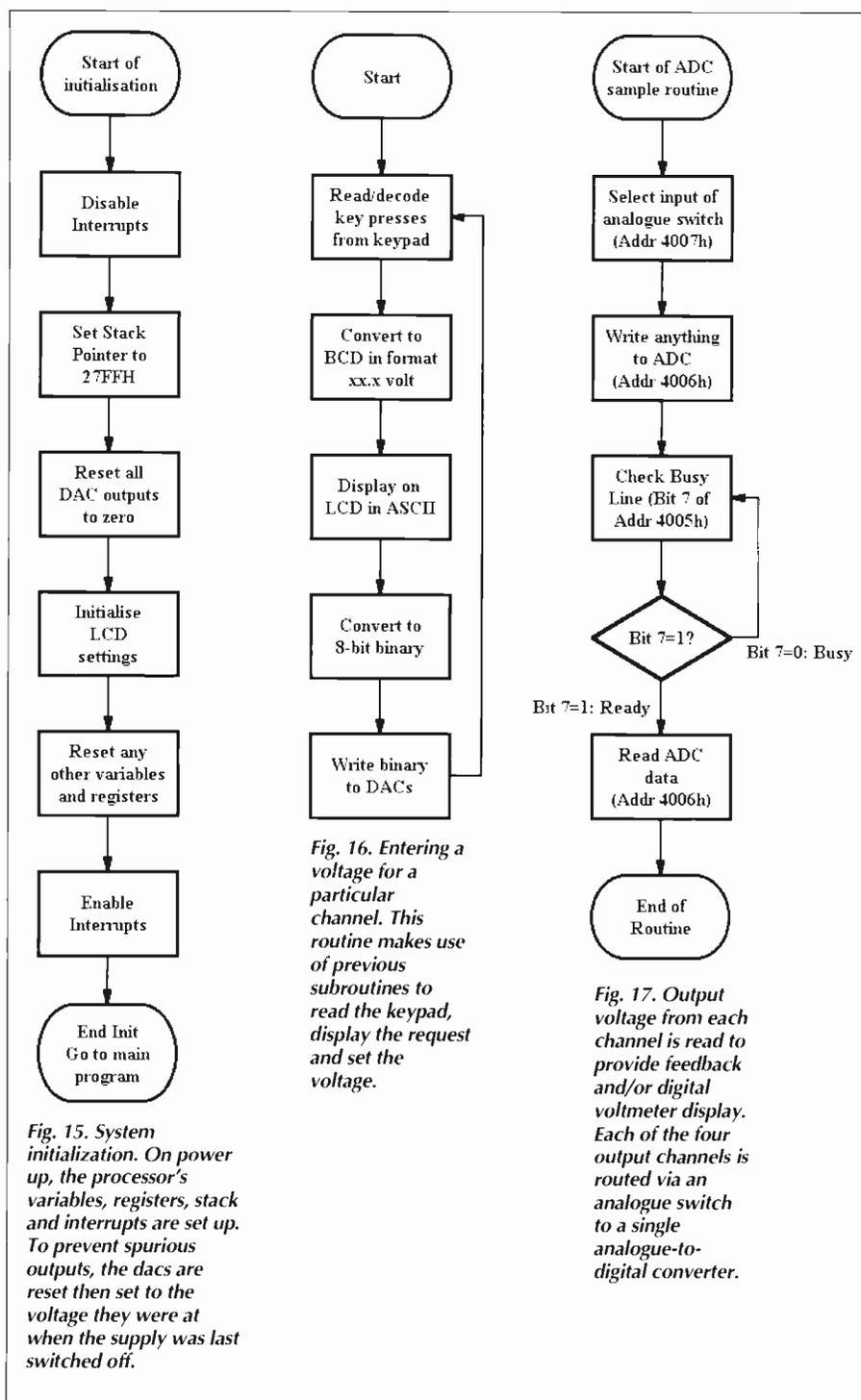


**Table 3. Command codes for display operations. To send a command to the display, you simply write a command byte to address 6000<sub>16</sub>.**

Clear display and home cursor	0116 <sub>16</sub>
Home cursor	0216 <sub>16</sub>
Set next display data ram address (first line)	8016 <sub>16</sub> +column
Set next display data ram address (second line)	C016 <sub>16</sub> +column
Cursor off	0C16 <sub>16</sub>
Display blank (memory retained)	0A16 <sub>16</sub> , 0B16 <sub>16</sub>
Display on	0D16 <sub>16</sub>

These are just a few options. There are many more relating to storing your own characters, changing the cursor type, shifting data etc and these will be found in the manufacturer's data.


# PROTEUS
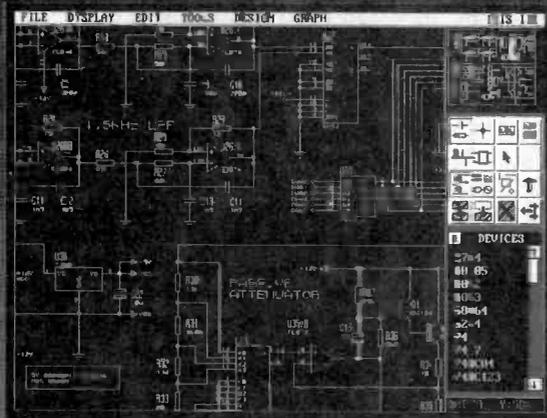
## The Complete Electronics Design System



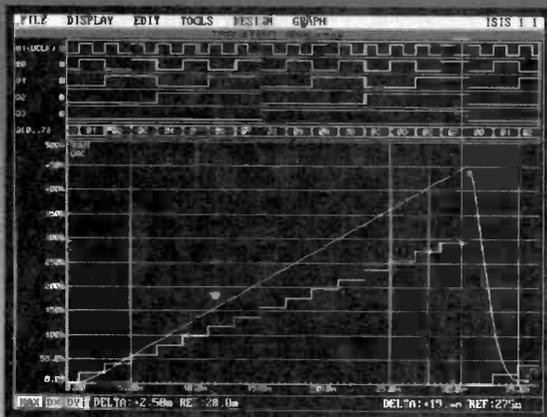
### Schematic Capture

- Easy to Use Graphical Interface.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.


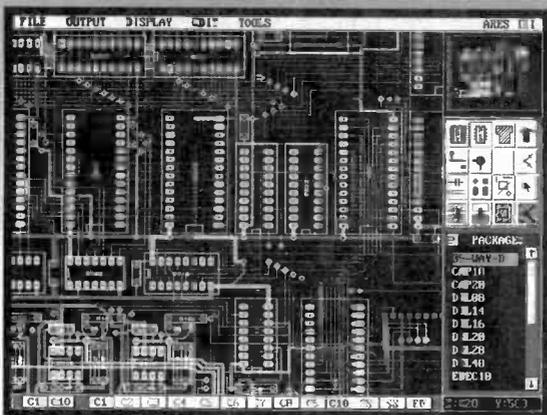
### Simulation

- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



### PCB Design

- Multi-Layer and SMT support.
- Unlimited Design Capacity.
- Full DRC and Connectivity Checking.
- Advanced Multi-Strategy Autorouting.
- Output to printers, plotters, Postscript, Gerber, DXF and DTP bitmaps.
- Gerber View and Import capability.

**labcenter**  
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.  
Tel: 0274 542868. Fax: 0274 481078.  
14 Marriner's Drive, Bradford BD9 4JT.

Proteus software is for PC 386 compatibles and runs under MS-DOS. Prices start from £475 ex VAT; full system costs £1495. Call for information about our budget, educational & Windows products. All manufacturers' trademarks acknowledged.

CIRCLE NO. 108 ON REPLY CARD

# A suitable CASE for development?

*For high-end applications, designing software via effective but expensive computer-aided engineering tools is becoming standard practice. John Anderson looks at Select Yourdon – a new CASE tool within the reach of small businesses.*

Most of the software I review is intended to help design hardware. This month's review discusses a software design tool generically referred to as a computer aided software engineering, or CASE, tool. The term computer aided software engineering describes a range of tools aimed at formally describing and documenting computer software before – and during – its production.

## Installation and manual

Called *Select Yourdon*, the package comes as a single disc together with a 250 page paperback manual. Installation follows the usual windows set-up routine, with the license identification being entered the first time the software is called up.

On running *Yourdon I* sometimes experienced Windows exception errors, but selecting the 'ignore' box started the software. The software was reinstalled to determine whether there had been an error at that stage but to no avail.

## Tutorial

The tutorial represents a large section of the manual amounting to over 150 pages. With a volume of material like this, you would expect that the manual would cover the fundamentals of CASE and the ideas behind formal software control methodology. However this is far from the case.

Much of the tutorial is taken up with describing the obvious – how to click on a windows bar, how to insert an object (click on insert) etc. So if you need some background material on this subject don't expect to learn the technique from the *Select Yourdon* documentation. On the other hand, there are some good examples in the tutorial, and working through these should give a good idea of how the system operates.

As you would expect, full Windows-style help is available on screen.

## Diagrams

Select Yourdon uses two types of diagram – one type for contexts and one for data flow. Context diagrams show how the information flows between the system being

specified and the external entities. Data flow diagrams are the primary tool for depicting the functional requirements of the system being analysed. They partition these requirements into processes interconnected by data flows. In a CASE tool, it is this formal decomposition of complex programs into clear routes of data flow that enables formal control over software development and maintenance.


Diagrams are generated by selecting specific data entities from the menu, and then adding the flows between them. The diagrams can be arranged on the screen, and on page, by selecting an item and dragging it with the mouse. Flow lines move accordingly.


Unfortunately, the drawing outlines and the text fonts are not always scaled together properly. This can result in an unpleasant display with the text completely out of proportion to the boxes which should contain it.
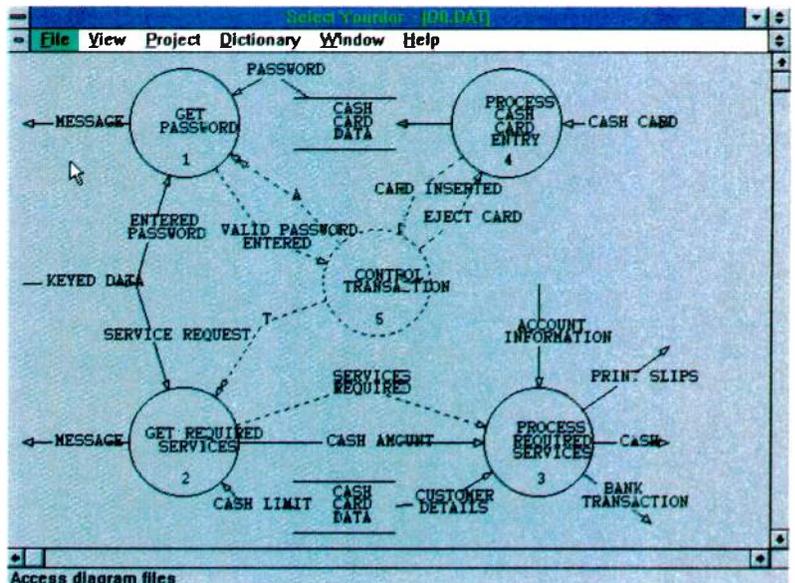
## Case background

CASE is an embodiment of structured programming methods. It has been developed over the past twenty years in response to the need for better control over software

*Writing software by linking action blocks makes structured programming unavoidable. This example of data flow is control software for a bank service till.*



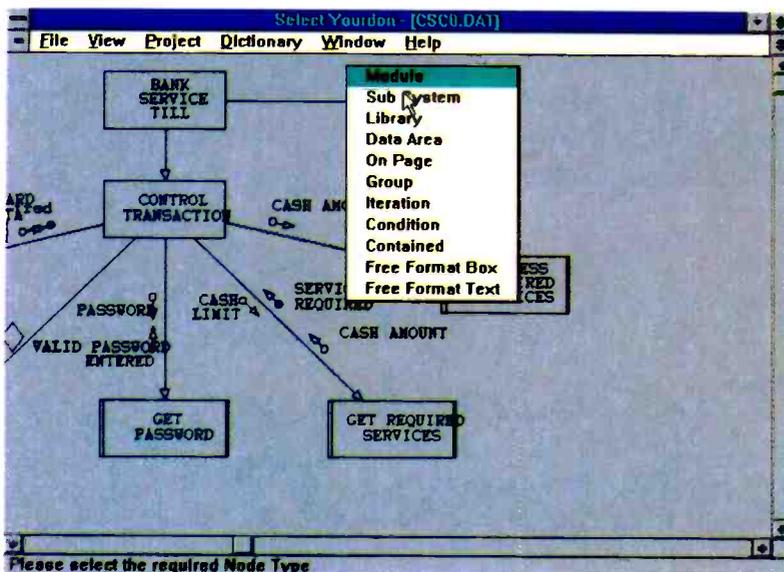

Amending software written with a CASE tool is simple. Add modules or other constructs – then specify the flows between them.

projects where reliability is critical - in military, life support or aerospace applications for example.

Edward Yourdon developed the original ideas in the 1970s. He has been so influential in the subject that his name is now synonymous with structured analysis and design.

In the early 1980s two workers, namely Ward and Mellor, developed additional features within the Yourdon framework. These involved control information for data flow diagrams and the use of state transition diagrams to specify dynamic behaviour. These extensions make the Yourdon method applicable to documentation of real time event and multi-tasking systems.

**Conclusion**

Select Yourdon is a CASE tool for software systems with its roots in the control of large software projects. Its functionality and price however are targeted at more mundane microcontroller systems.


The Windows GUI environment is ideally suited to this type of product. Although the display sometimes looks untidy, the ability to switch quickly between between diagrams and layers is an important part of maintaining the diagrams.

With the Ministry of Defence demanding the use of CASE tools for its real time systems, and pressure from quality systems and life support applications for formal software documentation, Select Yourdon is assured part of a growing market. There are competitive products priced at an order of magnitude more than Select Yourdon. If you need to use formal software control methods with minimal outlay, then this package is well worth considering.

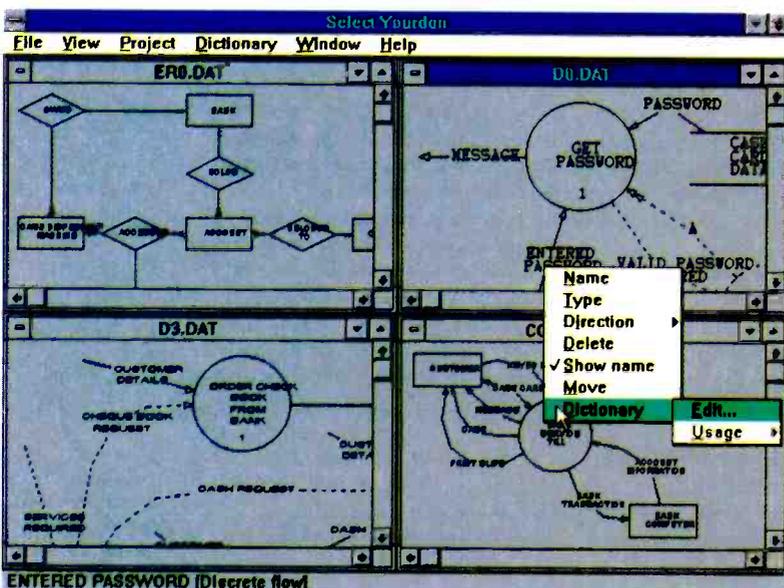
**Further reading**

Modern Structured Analysis by Edward Yourdon, Prentice Hall.

Software Design for Real-Time Systems by Jim Cooling, Chapman and Hall.



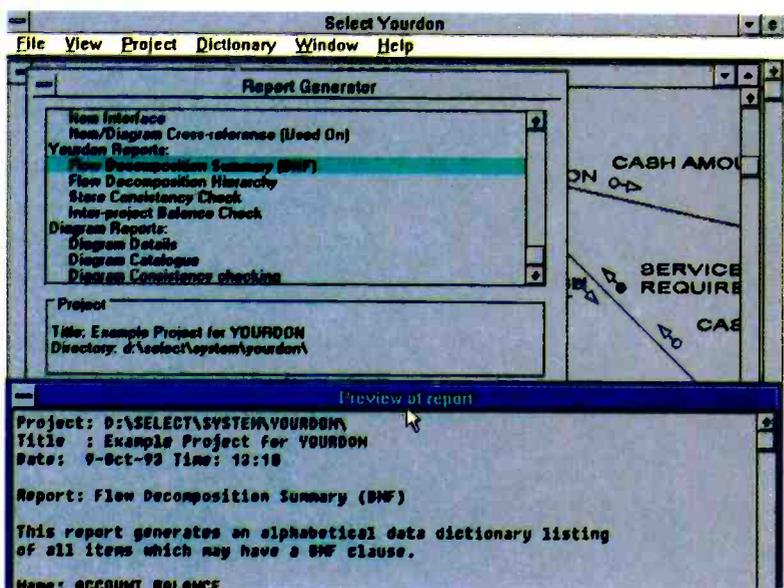Modify a diagram by simply clicking on an entity. This automatically brings up a menu tree.



A wide range of reports are previewable on screen.


**SYSTEM REQUIREMENTS**

- Windows 3.1 under MS Dos 5.0
- Config.sys must have FILES=40
- 80386 or 80486 processor
- VGA 640x480, 16 colours
- 3 Mbyte of ram
- 3 Mbyte hard disc space
- Mouse
- Windows supported printer

**SUPPLIER DETAILS**

Manufactured by Select Software Tools, Select Yourdon is available in the UK via Computer Solutions Ltd, 1A New Haw Road, Addlestone, Surrey KT15 2BZ. Tel. 0932 829460. Its price is £495.
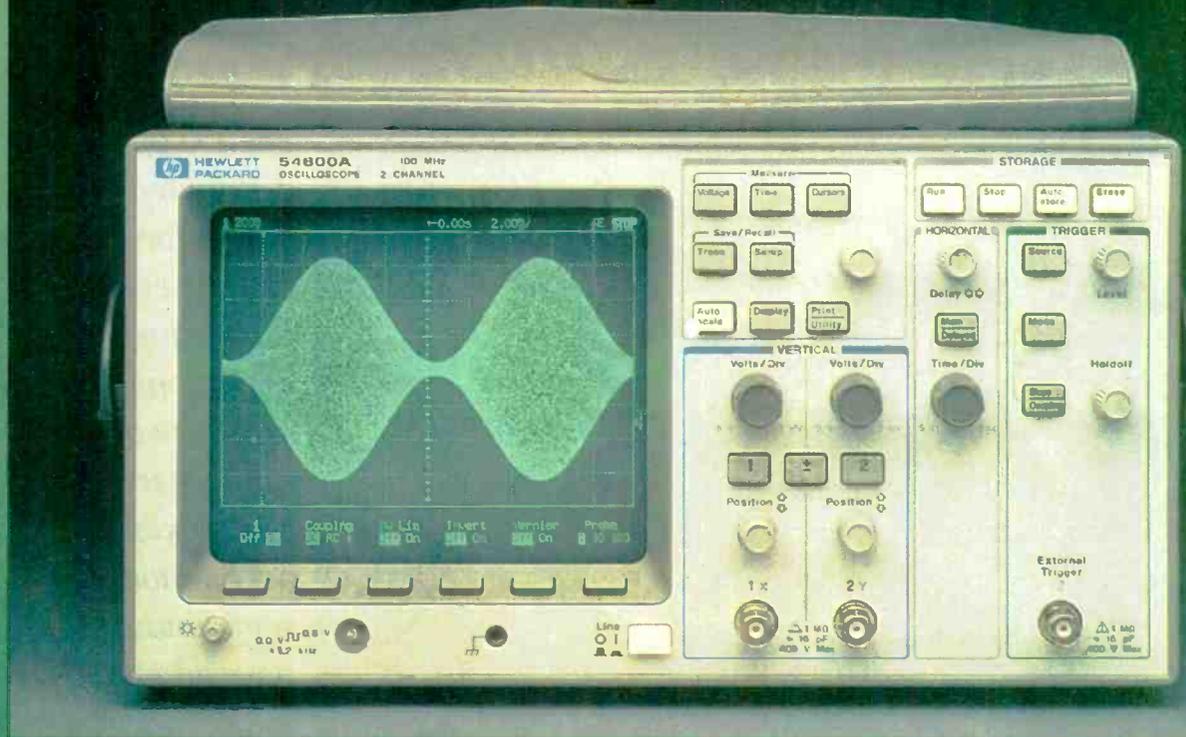
# Your best design could win you this £2500 H-P Oscilloscope



**T**HIS Hewlett-Packard oscilloscope combines the feel and display of a top line analogue instrument with the precision and programmability of digital electronics. This DSO is easy to use because it was designed by electronics engineers for electronics engineers.

Electronics World is looking for freelance authors who can bring applied electronics design alive for other electronics professionals through their writing. We want to commission articles on circuit design using the wealth of modern components now available to electronics engineers. Possible areas of interest could be RF, microwave, audio, video, consumer electronics, data acquisition, signal processing and computer peripherals.

All articles accepted for publication will be paid for – in the region of several hundred pounds for a typical design feature.

The author of the best script received over the period June 1, 1993 to May 30, 1994 will receive an HP54600A oscilloscope in addition to the normal author's fee.

The judging panel will be drawn from Electronics World and Hewlett-Packard.

A Hewlett-Packard  
HP54600A  
100MHz digital  
storage scope could  
be yours when you  
write for **Electronics  
World + Wireless  
World**,  
the journal that  
design engineers pay  
to read.

For further details about our quest for  
the best call or write to:

Frank Ogder, Editor, **ELECTRONICS WORLD**,  
Quadrant House, The Quadrant, Sutton  
SM2 5AS Tel 081-652 3128



*The I<sup>2</sup>C approach to distributed processing allows the designer to include every kind of processing and signal conditioning function on a simple two-wire bus. This proprietary Philips concept is so flexible and accommodating that other semiconductor companies have adopted it and added to the function range. Design consultant Mike Button\* reveals the secrets of its success.*

## BUSMAN'S GUIDE TO I<sup>2</sup>C

**T**he low cost of microprocessor devices makes it common sense to provide future compatibility in all but the most trivial of designs. Consequently the majority of electrical and electronic circuits employ the ubiquitous microprocessor to implement logical functions. With the advent of the microcontroller with on-chip prom or eprom in the 70's, single chip solutions are now a norm.

Control functions, often involving human reaction times, are the norm in the majority of systems. The high speed data transfer rate of an 8-bit parallel data bus is likely to be unnecessary and expensive. A simple, two-wire serial interface often provides enough performance for a surprising range of applications.

The Inter-Integrated Circuit Bus, written I<sup>2</sup>C

for short and pronounced "I squared C", was invented and patented by Signetics and Philips and has become a *de facto* standard in chip to chip and board to board communication. Due to Philips' involvement in audio, television and telecoms, a legion of I<sup>2</sup>C bus devices is now available. Other semiconductor manufacturers are also making devices for the bus.

The range includes 8-bit data converters, adc/dac, audio frequency generators, clock timers, ram, eeprom, led/lcd display drivers and a range of audio, radio and television control circuits. Several microcontrollers have on-chip hardware to ease programming and relieve the processor of software overheads. The PCB8XC552 and PCB8XC652 are of particular note.

The ability to add more master devices at

any time puts great power at the finger tips of a system designer. When the microcontroller software becomes overloaded additional microcontrollers can be added. Alternatively external test equipment can contain a master and slaves to exercise, test and report on system functionality. In control functions where response time in the order of 1ms is acceptable, the I<sup>2</sup>C bus provides a convenient adaptable and low cost solution.

### Definitions

The I<sup>2</sup>C bus is a bi-directional two wire serial bus having a defined protocol which allows data transfer between compatible integrated circuits. The number of devices that can be

\*TDR Ltd.

attached to the bus is limited only by the bus capacitance. The bus is so designed that the addition or removal of a device will not affect the working of any devices still on the bus. Philips defines the bus as multi-master, multi-slave working.

The standard-mode of operation can handle data and clock signals at baud rates up to 100kHz. Fast-mode devices are now being made available that will work at 400kHz. The low speed mode is used when microprocessors need to poll the bus in software. A 10-bit address mode was recently introduced to provide more independent slave addresses. All modes of operation conform to the same protocol and provide enhancements for use in special cases.

The I<sup>2</sup>C bus uses two leads plus a common (earth) return. The SCL lead carries the clock pulses, the SDA lead carries the data information. Commencement of a data transfer is indicated by a START condition [S]. The end of transfer is indicated by a STOP condition [P].

Data is transferred in a 9-bit word, comprising of eight data bits plus an acknowledge bit. The acknowledge signal, ACK, is sent after every data byte to indicate that data transfer may continue. The NACK (not ACK) signal indicates that no further data transfer is possible and a STOP or repeated START condition should be sent. The device that generates the START and STOP conditions and provides clock pulses is called a MASTER. Devices that respond to a MASTER are called SLAVES.

All SLAVES devices are provided with a unique SLAVE ADDRESS. A MASTER, wishing to transfer data to or from a SLAVE must, prior to data transfer, generate the address appropriate to the required SLAVE. A SLAVE on recognising its own address will generate an ACK signal.

The device that sends data is called a TRANSMITTER. Conversely, the device that accepts data is called a RECEIVER. Except for the condition when a SLAVE acknowledges its own address, it is the RECEIVER that generates the ACK signal.


Thus an I<sup>2</sup>C bus device can be any one of four types dependent on its function during data transfer. The majority of devices produced for the bus are slave devices and can be either transmitters or receivers dependent on function or mode of operation. The master

## Hypothetical complex microcontroller system

The I<sup>2</sup>C bus provides a two wire communications channel for both commands and data for all elements of the system. It replaces a multiple line address/data bus with consequent savings in PCB complexity and area. It was designed as a simple communications channel between individual ICs but is increasingly used as a local network between systems, providing they are not speed sensitive.

System inputs may include: converted analogue to digital signals from transducers such as temperature sensors, analogue joysticks, etc. and logical signals from level switches, key contacts, etc.

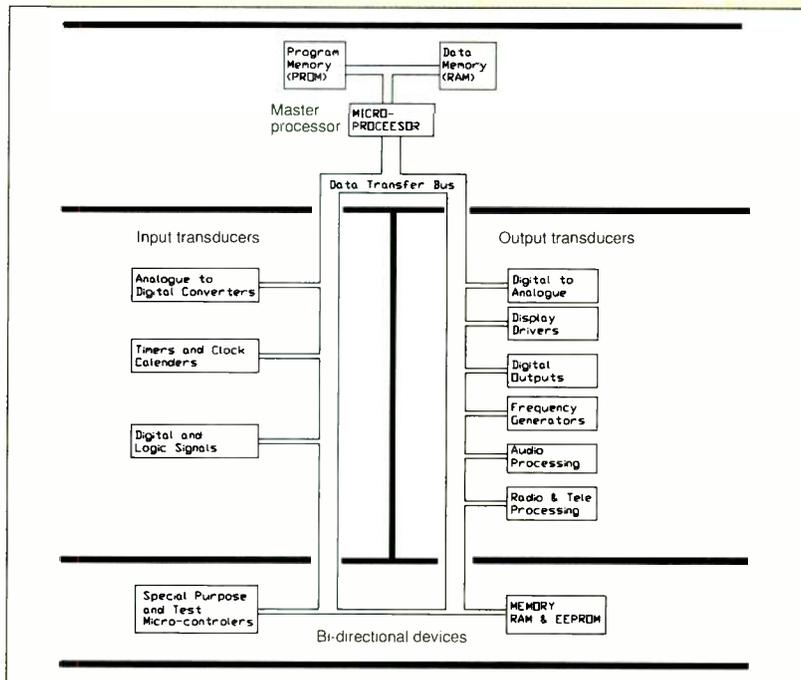Transducer outputs may include: converted digital to analogue signals to drive motors, current loops, etc., digital signals to switch relays or lamps and drivers for led or lcd displays. Special functions such as television receiver channel selection or teletext reception and display may also be included.



function is normally provided from a micro-processor with an I<sup>2</sup>C bus controller chip (PCD8584) or a microcontroller with on-chip I<sup>2</sup>C bus hardware.

Master transmitter → direction of data → slave receiver

Master receiver → direction of data → slave transmitter


Subject to bus capacitance limitations, there

can be any number of masters or slaves but only one transmitter-receiver pair are allowed to use the bus at any one time.

### Electrical properties


The electrical connections to the I<sup>2</sup>C bus rely on open collector wired-and-logic gating. Both the SDA and SCL leads have the same electrical configuration.

Figure 1 shows a typical bus connection for one of the wires (SCL or SDA). If all the device transmitters (devices 1 2... n) are at logic-high the bus wire will be pulled high to V<sub>CC</sub> (normally but not necessarily +5V) via the bus pull-up resistor. All of the device receivers will see this high state on the bus as a logic-high signal. If any of the device transmitters go to logic-low the bus wire will be pulled to ground potential and all of the device receivers, including the receiver of the device

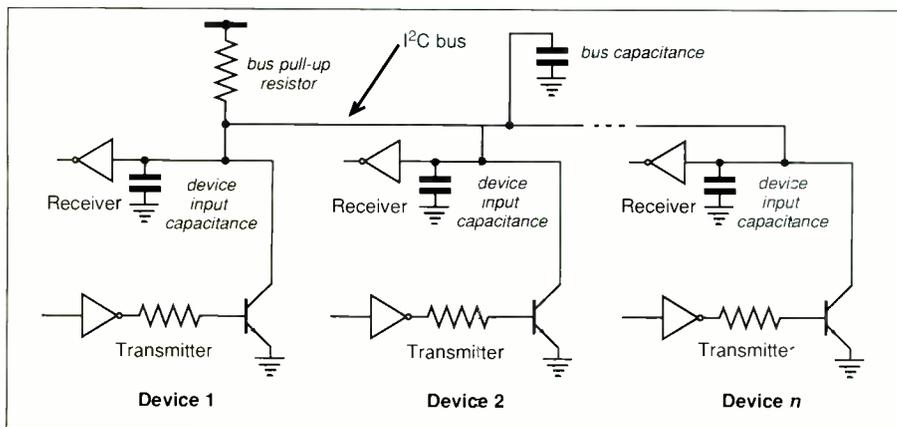


*Electrical and logic circuit of the SDA & SCL leads. The wired-and connection allows each device to simultaneously monitor the bus while transmitting data. When a device transmits a logic-high it expects to see a logic-high on its input, if a logic low is received then another device is using the bus.*


## Data transfer under I<sup>2</sup>C

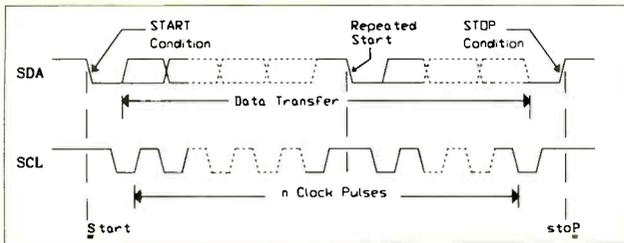

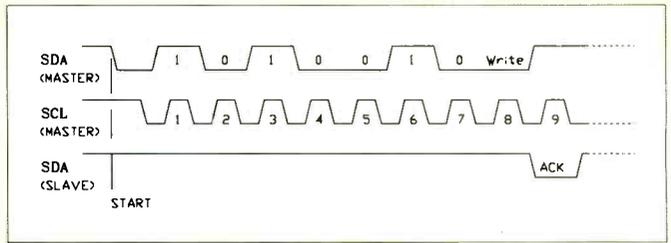
Start and stop conditions shows the relationship of the start, repeated start and stop conditions on the SDA lead with reference to the SCL Lead. The repeated start condition is used when a master needs to retain control of the bus during a combined write/read transfer, for example, when accessing a memory device.



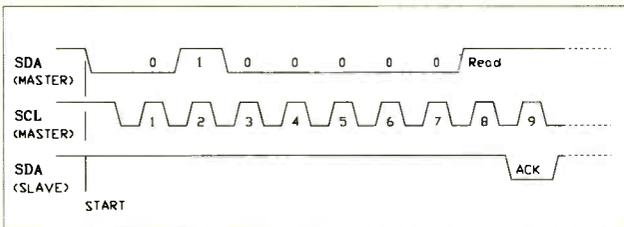Addressing a slave receiver. Shows waveform to write to slave address A0. (Eprom PCF8582). Note that the SDA lead is low (write) during the 8th SCL clock pulse. The ACK signal, during the 9th SCL clock pulse is generated by the slave.



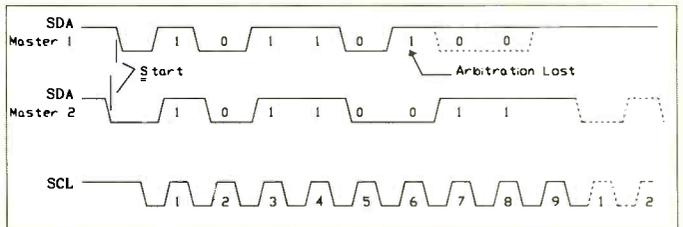Addressing a slave transmitter. Shows waveform to read from slave address 80. (8-bit I/O PCF8574). Note that the SDA lead is high (read) during the 8th SCL clock pulse.



Arbitration. When a master sends a start condition it must check the bus for arbitration. The waveform shows two masters starting at the same time. The first master to send a logic-low on the SDA lead when the other master sends a logic-high wins the arbitration. In the waveform above master 1 is attempting to address slave 1011 010 and master 2 addresses slave 1011 001. Master 1 loses arbitration on clock pulse 6 and releases the bus. (Leaves the SDA lead high).

transmitting the signal, will receive a logic-low signal.

Both the clock lead (SCL) and the data lead (SDA) use this wired-and function to perform checks on data transfer. If the MASTER monitors its own transmitted signals it will expect to see the bus responding to these signals. The presence of another device on the bus can be detected if a logic-low is received when transmitting a logic-high. This feature is used to control the clock rate on the SCL lead and to obtain data arbitration on the SDA lead.

A slave can optionally control the clock pulses received from the master by holding the SCL lead at logic-low. Thus data speed and synchronisation of data exchange may be controlled by the slave device.

The transmitting device can check for the presence of other transmitters on the bus by monitoring the state of the SDA lead. If a logic-low is received when transmitting a logic-high then another device is also transmitting on the bus. This condition is known as lost arbitration. The bus specification requires that any master transmitter shall check the bus for arbitration and, if the presence of another transmitter is detected, the master shall relinquish any control of the bus.

### Data transfer

When the I<sup>2</sup>C bus is idle both the SDA and SCL leads are high. A start condition is

### SDA & SCL lead DC requirements

Parameter	Symbol	Standard Mode		Fast Mode		Unit
		Min	Max	Min	Max	
Low level input voltage	V <sub>IL</sub>	-	0.3V <sub>DD</sub>	-	0.3V <sub>DD</sub>	V
High level input voltage	V <sub>IH</sub>	0.7V <sub>DD</sub>	-	0.7V <sub>DD</sub>	-	V
Low level output voltage	V <sub>OL</sub>	0	0.4	0	0.4	V
at 3mA sink current				0	0.6	V
at 6mA sink current	-	-	-	-	-	-
Input capacitance, each lead	C <sub>i</sub>	-	-	10	10	pF


### I<sup>2</sup>C bus line length limitations

Because of the non active pull-up feature of the wired-and bus, the capacitance on each of the bus wires restrict both the number of devices connected and the working distance. This capacitance comprises of the total input capacitance of the connected devices and the bus wire leakage capacitance. The minimum value of the pull-up resistor is defined by the maximum low level sink current of the devices. It may also be necessary to provide a resistor in series with each device to provide input protection against voltage spikes on the bus.

Data sheets for all of the Philips devices give information on how to calculate the pull-up and series resistor values for a given bus. To obtain maximum distance the pull-up resistor should be a minimum value, without series resistor. With a 5V system and 3mA maximum sink current the minimum value of the pull-up is 1.7kΩ (5.1V/3mA).

## SDA and SCL lead timing requirements.

Parameter	Symbol	Standard Mode		Fast Mode		Unit	Philips Symbol
		Min	Max	Min	Max		
SCL clock frequency	$f_{CL}$	0	100	0	400	kHz	$F_{scl}$
Low period of SCL clock	$t_{LC}$	4.7	-	1.3	-	$\mu s$	$t_{LOW}$
High period of SCL clock	$t_{HC}$	4.0	-	0.6	-	$\mu s$	$t_{HIGH}$
Bus free time between stop & start condition	$t_{BUF}$	4.7	-	1.3	-	$\mu s$	$t_{BUF}$
Time SCL must be high before start or repeated start	$t_{AS}$	4.7	-	0.6	-	$\mu s$	$t_{SU.STA}$
Hold time SCL must be high after start or repeated start	$t_{BS}$	4.0	-	0.6	-	$\mu s$	$t_{HD.STA}$
Time SDA must be stable before rising edge of SCL	$t_{BC}$	300	-	300	-	ns	$t_{HD.DAT}$
Time SDA must be stable after falling edge of SCL	$t_{AC}$	250	-	100	-	ns	$t_{SU.DAT}$
Time SDA must be low after a rising edge on SCL prior to a stop (rising edge on SDA)	$t_{BP}$	4.0	-	0.6	-	$\mu s$	$t_{SU.STO}$
Rise time of both SDA and SCL signals	$t_R$	0	1000	0	300	ns	$t_R$
Fall time of both SDA and SCL signals	$t_F$	0	300	0	300	ns	$t_F$
Capacitance load for each line	$C_b$	0	400	0	400	pF	$C_b$

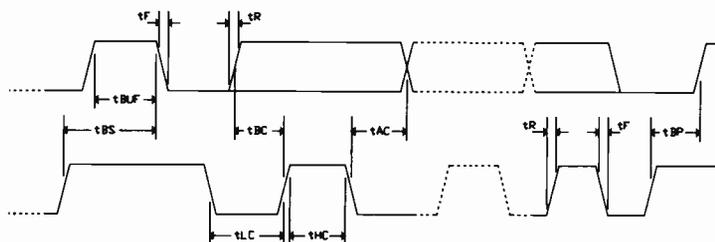

Conventional I<sup>2</sup>C devices handle clock signals and bit rates to 100kHz but fast mode devices are now appearing that are capable of working at 400kHz. These timings cover both fast and slow modes.

defined as a falling edge on the SDA lead when SCL is high. A stop condition is defined as a rising edge on SDA when the SCL is high. It follows that to avoid false start and stop conditions being generated during data transfer, the state of the SDA lead must be stable while the SCL lead is high.

The generation of a start condition indicates to all other devices that the bus is busy until a stop condition is generated. Masters wait for this stop condition before attempting to send a start. All slaves, on detecting a start, will reset their hardware and prepare to receive the slave address. A slave recognising its own address will generate an ACK signal.

The ACK signal is a logic-low signal during the ninth clock pulse. The NACK signal is, therefore, a logic-high. The generation of a non-existent slave device address automatically generates a NACK because the bus is inherently in the high state.

It is possible that two masters could simultaneously generate a start followed by a slave address. For this reason all masters must always check the SDA lead for arbitration. As two or more masters could attempt to address the same slave, the check for arbitration must continue for the whole of the data transfer. (Until the stop condition is generated.)

### Slave addressing

All slave devices are designed with a unique address which, when recognised and accepted, sets the slave in data transfer mode. There are two modes of addressing, both using the same protocol. The "standard" seven bit address is used by most of the devices available at present. The ten bit address mode will be provided on some future devices.

To address a slave device, a master will generate a start followed by a nine bit word. This

word comprises seven data bits (ADDRESS), a read/write (W) bit and an acknowledge (ACK) bit. The read/write bit determines the data direction. A logic-high (read) sets the slave as a transmitter, a logic-low (write) makes the slave a receiver.

If an addressed slave device is capable of responding to the master it will generate an ACK signal (a low level on the SDA lead during the ninth clock pulse) and set its internal hardware or software for the data transfer. Any slave not addressed will ignore any further action on the bus until another start condition is generated.

The seven bit address has several reserved codes used for special purposes.

### Slave address byte

	Bit no.
Allocation	6543 210 W
General call	0000 000 0
Start byte	0000 000 1
CBUS	0000 001 X
Reserved	0000 1XX X
10 bit addressing	1111 0XX X
Reserved	1111 XXX X

X = any state

### Data transfer

All currently available devices perform data transfer in a 9-bit word comprising eight data bits plus a ninth ACK bit. An astute reader will observe that the I<sup>2</sup>C bus protocol does not necessarily require an eight bit format for addressing and data transfer. Provided that a master is capable of generating the clock pulses and the slave is configured to receive them, then the word format can be any number of bits. Early bus formats, particularly systems using the

8048 type microcontroller, were open and allowed the user to choose the word length.

Transmitters send data on the SDA lead, receivers read data from the SDA lead and generate the ACK signal. Masters generate clock pulses on the SCL lead and control the bus by generating start and stop conditions.

A data transfer can be of any number of data words. The transfer is terminated when a (repeated) start or a stop condition is sent by the master. The bus is considered to be busy during the period between an initial start condition and a stop condition. A receiver can indicate that the transfer is over by sending a NACK signal but it is the responsibility of the master to send a stop.

### General calls

The slave address 0000 0000 (a write to slave address 00) is reserved for a general call to devices that require "broadcast" information. The second byte of the transfer will indicate what type of information is being transmitted. General calls are used to globally set slaves to a defined state or to send global configuration data. A full discussion is beyond the scope of this article. Interested readers should obtain the relevant Philips data sheets.

### Other modes

**Low speed mode.** This mode is an extension of the bus protocol to allow relatively slow slave devices to respond to a "normal" master using an optional lower clock rate, preceded by a longer start procedure. The start procedure is as follows:

- A standard start condition.
  - A start-byte 0000 0001. (This is equivalent to "read address 0")
  - A repeated START condition.
- The start-word is seven clock pulses long

### Putting in an extra feature

We had a requirement to add an auxiliary keypad to one of our existing designs. This product used a *PCB80C552* micro controller with I<sup>2</sup>C bus software drivers already installed (clock timer and a led display). Expecting future enhancements and modifications we arranged the original circuit layout such that all spare '552 port leads were made accessible on suitable connecting points.

The *PCF8574*, a remote 8-bit i/o expander, has the necessary functions. It is an 8-bit quasi-bidirectional port similar in function to the *8051* microcontroller ports. It has an interrupt facility which is activated when the input to one or more of the port leads changes state. The interrupt signal is cleared when a bus read or write is sent to the device. There are two versions of the *PCF8574*; one version has an allocated slave address 0100 XXX, the other (*PCF8574A*) 0111 XXX.


The *PCF8574* was mounted on a small daughter board attached to the hex keypad. The eight wires from the keypad were connected to the device ports. The 5V supply, ground, SCL, SDA and interrupt leads were wired to a suitable connector. Hardwire links set the address to 0100 000. In the idle (waiting for a key depression) state the *PCF8574* port bits 4-7 are set to binary 0000, which applies a ground potential to the four row pins on the keyboard. Bits 0-3 are set to binary 1111. When a key is pressed one of the column pins (bits 0-3) is pulled to ground via the key connection. This change of input causes the internal logic in the *PCF8574* to apply a ground potential on the "int" pin 13 which is detected by the microcontroller. The software then performed the following I<sup>2</sup>C bus transfer.

Slave address bit no.				Transferred data bit no.		
S	6543 210	W		7654 3210		
R	0100 000	0	A	1110 1111	A	start & select column "0"
R	0100 000	1	A	1110 KKKK	A	Read state of keys 048C
R	0100 000	0	A	1101 1111	A	Select Column "1"
R	0100 000	1	A	1101 KKKK	A	Read state of keys 159D
R	0100 000	0	A	1011 1111	A	Select Column "2"
R	0100 000	1	A	1011 KKKK	A	Read state if keys 26AE
R	0100 000	0	A	0111 1111	A	Select Column "3"
R	0100 000	1	A	0111 KKKK	A	Read state of keys 37BF
R	0100 000	1	A	0000 1111	A P	Set "idle" state and STOP

S start; P stop sent or R repeated start; A ack; W read/write 1=read, 0= write

All of the bits (K) in the received data bits 0-3 will be logic-high except for the bit(s) corresponding to the pressed key(s). Note that only one stop condition is sent. The repeated start feature was used to prevent other masters from interfering, and thus delaying, the bus transfer. When the key is released the *PCF8574* will detect another change on its inputs and present a further signal on the "int" pin. The software must now perform another read or write to the device to clear this signal.

Initial concern whether the bus would be fast enough to detect and process the key depressions was soon dispelled by a calculation. With a baud rate of 100kHz and nine bits required for each data byte and with a total of 18 bytes, the maximum time to scan the keyboard was 9x18/100=1.6ms. This time was less than the contact bounce period of the keys and appropriate software delay routines were needed to insure that valid readings were obtained.

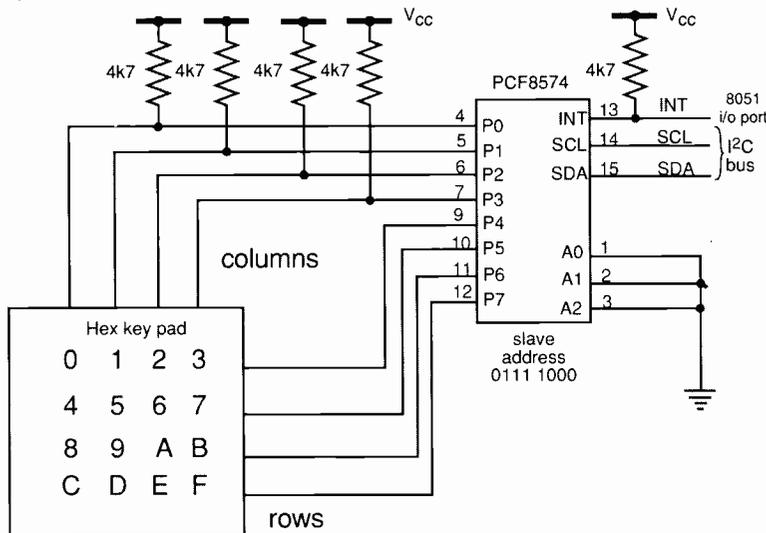

which, combined with a slower clock rate, gives ample time for microprocessor to respond and prepare for data transfer. After the repeated start condition the "real" slave address is sent. No slave device is allowed to acknowledge this start byte.

**Fast mode.** In fast-mode the I<sup>2</sup>C bus protocol remains unchanged. The maximum baud rate has been increased to 400kHz thus tightening the timing specification for the SDA and SCL leads. Devices designed for the fast-mode will still perform satisfactorily at standard-mode baud rates.

**Ten bit slave addresses.** The 10-bit addressing has been introduced because most of the 112 addresses allowed by the 7-bit scheme have been allocated more than once. The bus protocol and byte length remain the same. The reserved slave address 1111 0XX is used to provide an extra two bits for the address. The remaining eight bits are sent in the next byte. Full details of this mode are outside the scope of this article and, as I understand from Philips, there are no devices yet using this mode. Further information can be obtained from Philips Components and the handbook "I<sup>2</sup>C Peripherals for Microcontrollers" gives full details on this – at present fairly academic – mode.

A future article will deal with practical applications such as the use of an I<sup>2</sup>C bus controller to adapt an existing micro system and a list of available devices. ■

### Bibliography

- Philips Components Data Handbooks: I<sup>2</sup>C bus specification
- I<sup>2</sup>C bus compatible ICs, Book 4 Parts 12a & 12b 1989
- I<sup>2</sup>C Peripherals for Microcontrollers, 1992
- Single Chip 8-bit Microcontrollers PCB83C552
- Integrated Circuits Designers Guide.

Help and further information may be obtained from the author at TDR Ltd. Tel 0666 577464.

### Acknowledgements

The author is grateful for the help and information, given over several years, from Philips Components, Gothic Crellon and Quarndon Ltd.

# Marconi's 200kW transatlantic transmitter

*Enigma surrounds Marconi's massive 200kW wireless station, built nearly eighty years ago. George Pickworth pieces together the technology behind the world's most powerful spark transmitter.*

**M**arconi's 200kW timed-spark continuous-wave transmitter was the ultimate spark-type transmitter. It was installed at Marconi's Caernarvon transatlantic 'super' station in Wales and came into service in 1916 to handle North Atlantic traffic. This was after the original synchronous-spark, wave-train transmitter was taken over by the military in 1914 for long range strategic signalling.

The timed-spark transmitter worked US stations at New Brunswick, Tuckerton, Marion and the Central Radio Station at Long Island. In 1919 it transmitted the first signals directly to Australia. Wavelength was given as 14km, which is approximately 21.5kHz.

To take advantage of the Earth/ionosphere waveguide effect, all transoceanic 'super' stations operated frequencies less than about 50kHz. However the lowest useable frequency, typically 20kHz, was set by physical constraints imposed by antenna structures: even the largest practical structures were very inefficient at 20kHz.

Because all transoceanic stations were confined to a 30kHz bandwidth, a high level of selectivity became vital to reduce mutual interference as the numbers of stations progressively increased. The only way of attaining this was with continuous wave systems. With these, oscillations progressively built up in the receiver tuner by virtue of resonance: this was known as syntony – a term invented by Lodge.

Remarkably, Marconi's 1906 Clifden

transatlantic super-station in Ireland, which originally radiated continuous waves, was a quenched-arc type. It had a plain triple disc discharger that was inherently self cooling, and the draught created by the rotating discs dispersed ionized gases, **Fig. 1**.

On the other hand, Poulsen, with his quenched-arc system incorporated 'rod' type electrodes, comparable with an arc lamp. These required elaborate water cooling and a strong magnetic field to drive ionized gases from the arc-gap.

The Clifden transmitter was powered by a DC generator which charged 6000 lead acid accumulators. However, the Clifden discharger was modified by attaching transverse electrodes to the main disc, similar to the 1916 synchronous discharger. These electrodes, described in the November issue, radiated wave trains; the official explanation was so that signals could be received by Marconi's magnetic detector which responded only to wave trains. There is some evidence that the magnetic detector will demodulate AM signals but I have not been able to confirm it.


## Options


Originally, the Caernarvon transmitter was a 200kW synchronous spark type radiating wave trains. It only allowed a very limited degree of syntony since there were too few waves in each train. These declined too quickly for resonance to be effective. In 1916 however, it was replaced with a continuous wave transmitter to increase receiver selectivity.

As early as 1906, Fessenden and Goltschmidt adopted rf alternator-type continuous wave transmitters for their north Atlantic service. Poulsen adopted the quenched-arc continuous wave system for his Hawaii/San Francisco link. Marconi's approach on the other hand was to indirectly produce continuous waves. He used spark systems to generate wave trains in rapid succession so that in effect they overlapped in phase. This led to the development of the Caernarvon timed-spark discharger.


Although the waves were continuous, they undulated in amplitude. Provided they remained in phase, this in itself did not significantly effect syntony. Indeed the undula-

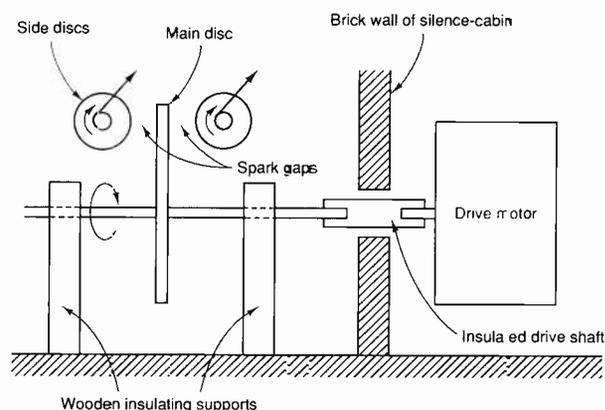**Fig. 1. Marconi's 1906 Clifden transatlantic super-station was powered by a DC generator charging 6000 lead acid accumulators. It radiated wave trains.**




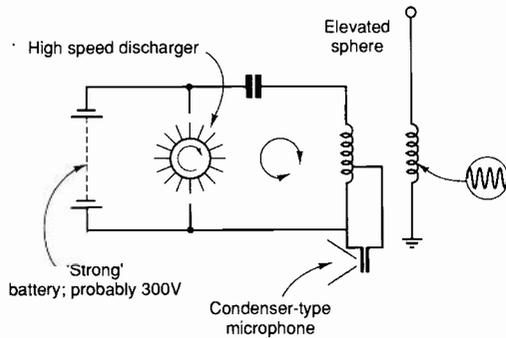


**Fig. 2. Tesla's 1899 radio telephony transmitter. There is little information on how it worked but it probably relied on the battery's internal resistance to limit the capacitor charge rate and a critical hub rotation rate.**

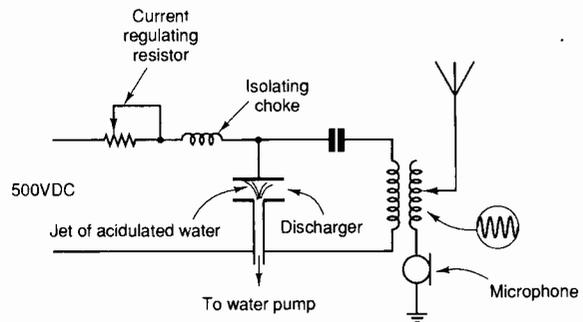

**Fig. 3. Morrietti's 'hydrothermic' discharge transmitter. Unlike most of its contemporaries, it had no moving parts.**

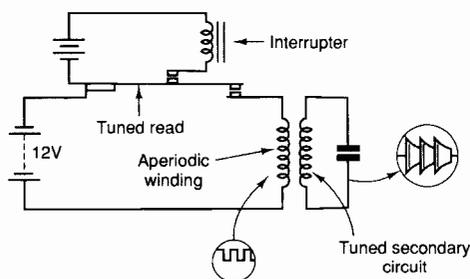

**Fig. 4. Fessenden's continuous-wave oscillator was the first to use a vibrating reed interrupter tuned to set transmitter frequency.**

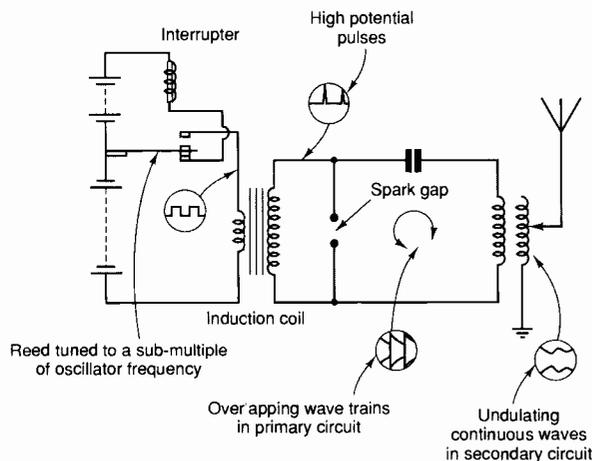

**Fig. 5. Early CW spark transmitter with a tuned-reed interrupter had limited power and contact bounce problems when operating above a few kilohertz.**

tions modulated the transmission with a tone. This article is about generating continuous waves by causing wave trains to overlap.

### Overlapping wave trains

My experiments have shown the number of significant waves in a train to be around 25. When creating continuous waves by progressively reducing the period between trains they eventually overlap. Repetition rate must therefore be at least 1/25th of the transmission frequency, but undulation is unacceptable at this rate. The Caernarvon transmitter generated wave trains that overlapped every 13.5 waves which produced slightly undulating continuous waves.

A repetition rate equal to the 25th sub-multiple presented no particular problem at the 20 to 50kHz transoceanic frequencies. But timing the wave trains – hence the term 'timed' – so that they overlapped in phase required extraordinary technical expertise. However, at the 500kHz and 1MHz maritime frequencies used with mechanical dischargers this repetition rate was out of the question.

### Tesla systems

Radio telephony, as pioneered by Tesla was the original motivation for continuous waves. In 1899 he employed a discharger, or 'break' as Tesla called it. This consisted of a hub with

16 – or sometimes more – radial electrodes rotating at very high speed between a pair of fixed electrodes. The device was energised with DC and a discharge occurred each time a pair of rotating electrodes aligned with a fixed pair. The discharge was quenched as the gaps widened, **Fig. 2.**

I am unsure how the device actually worked; indeed Tesla himself does not make this clear. A possible explanation is that the internal resistance of the battery limited the capacitor charge rate. During discharge, current is drawn from the capacitor faster than it is replaced, so potential falls. Then, as the hub continues to rotate, the discharge is quenched. In this way, the capacitor is charged and discharged synchronously with alignment of pairs of electrodes. At a critical rotation speed, this corresponds to the resonant frequency of the circuit.

The 'flywheel' effect of the tuned circuit converted charging and discharging into continuous sine waves. Operation can therefore be compared to the quenched-arc system. The effect of the capacitor-type microphone was to de-tune the circuit so that power output corresponded to sound pressure waves.

In later versions, Tesla used a pair of toothed wheels rotating at very high, but at slightly differing speeds, in opposite directions. This was reported to give up to 10,000

discharges a second. For an even greater discharge rate, Tesla added a jet of mercury intercepted by projections on a disc rotating at extremely high speed, but this was a low power device intended as an oscillator for use with his regenerative receivers.

### Fessenden's experiments

In 1900, during early radio telephone experiments prior to adopting radio frequency alternators, Fessenden built a system whose main elements were a battery, a vibrating-reed type interrupter and a transformer. The interrupter was tuned to 10kHz, in series with the aperiodic primary winding of the hf transformer. In turn, the transformer's secondary winding was tuned to the interrupter frequency. This was the first transmitter to use a vibrating reed to set transmitter frequency, **Fig. 4.**

My replication of Fessenden's experiments showed that the method worked well when the vibrator was tuned to a low sub-multiple of the resonant frequency. Here, the oscillation trains overlapped. Operation seems to have been by each DC pulse shocking the tuned circuit into oscillation.

Before thermionic valve type oscillators, there were many ingenious spark systems. Despite these, rf alternators were the only devices capable of producing continuous waves pure enough for practical radio tele-

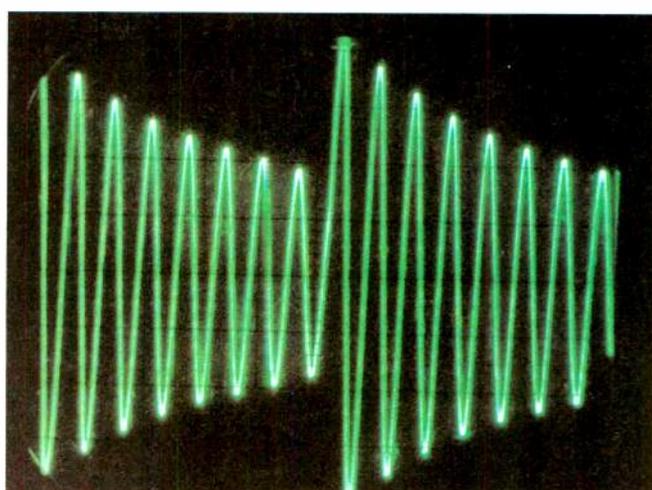
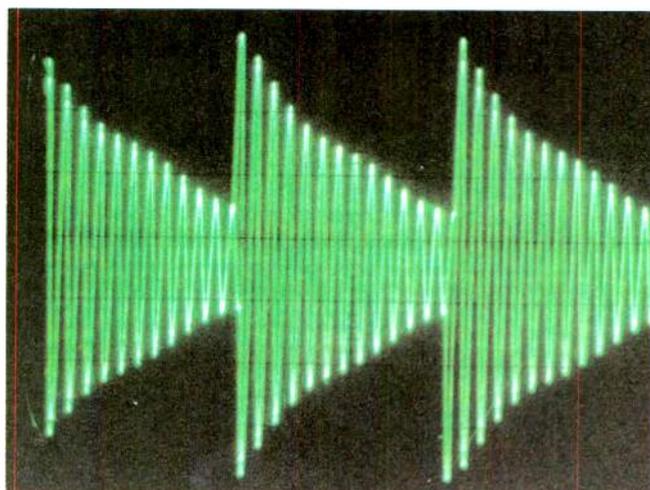


Fig. 6. Reproduction of Fessenden's experiments produced the overlapping wave trains of (a). Wave trains overlapping in phase are detailed in (b).

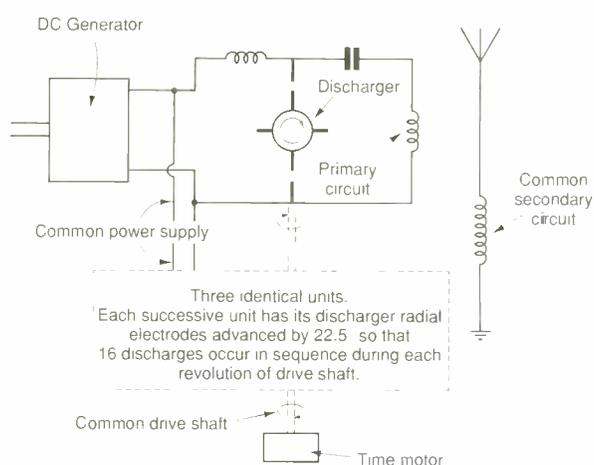


Fig. 7. Marconi's experimental timed discharger comprised four rotary dischargers each with four radial electrodes rotating between a pair of fixed electrodes. Each revolution of the common shaft caused 16 discharges.

### Marconi's timed discharger

Marconi's 1913 experimental consisted of a bank of four rotary dischargers. Each comprised four radial electrodes rotating between a pair of fixed electrodes and driven by a common shaft extending from the drive motor. Individual primary circuits, one per discharger, were inductively coupled to a common secondary circuit. The device was powered by a DC generator, Fig. 7.

Discharge commenced while the gaps were still narrowing. Further narrowing as the electrodes rotated reduced resistance across the gaps. Amplitude of the oscillations declined and energy was transferred to the secondary circuit. Then the gaps widened and the draught created by the rotating electrodes dispersed ionized gases, thus quenching the discharge and returning the gaps to a high resistance state.

Bearing in mind that the device was energised by DC, I am not sure which mode it ran in. The primary circuit could have operated in quenched-arc mode and transferred energy to the secondary by induction. Alternatively, current pulses through the primary circuit could have shock excited the secondary circuit into oscillation. It was most probably a combination of both these modes. Whichever, discharges occurred consecutively, giving a total of 16 discharges per revolution.

Assuming operation in quenched-arc mode, the quenching effect caused by the rotating electrodes would limit the number of oscillations in each train to 15 or fewer, insufficient to overlap. As a result, wave trains in the primary circuit were discrete. Provided they were in phase with oscillations in the secondary circuit, they would be reinforced to create continuous oscillations with undulations corresponding to their reinforcement points, Fig. 8. Reinforcement of oscillations in the secondary circuit would be exactly the same with shock excitation of the secondary circuit.

Consider for example a frequency of 10kHz reinforced every 13th oscillation. This makes the reinforcement frequency  $10^4/13$  which is 769.2Hz. As each revolution produces 16 reinforcements, it needs to run at  $769.2/16$ , or

phony. Using rf alternators, Fessenden radiated his voice from his Brant Rock station in the USA. As early as 1906, these broadcasts were reported to be heard by operators at his station in Scotland.

However, Marconi still rejected alternators, probably because they were still in their infancy and ran at very high speed. Frequency raisers which allowed alternators to run at lower speed had yet to be developed; so had the inductor type alternator, which eliminated windings on the rotor and thereby the major problem with rotor windings flying out of their slots.

### Early spark cw

The Marconi company had considerable expertise in the manufacture of spark apparatus. Having progressed so far with arc/spark systems, particularly for maritime use, it is understandable that Marconi should have pursued this path.

Early attempts to produce continuous waves with spark systems were based on tuning the interrupter of an induction-coil type spark-transmitter to a sub-multiple of the oscillator frequency, Fig. 5. However, while tuning the vibrator to a sub-multiple presented no special problem. Contact bounce made precise timing extremely difficult and almost impossible to maintain at frequencies above a few kilohertz.


Moreover, the vibrating reed was essentially a low power device. In my 7kHz reproduction, fine tuning to bring the wave trains into phase was by adjusting the oscillator frequency, Figs 6(a,b). I found using shock excitation simpler however.

### Morrietti's system

Morrietti's 'hydrothermic' discharger, used for experimental radio telephony between Rome and Tripoli around 1910, consisted of a pair of copper discs set horizontally, one above the other. The lower disc had a tiny hole drilled through the centre. Through this hole, acidulated water was steadily pumped so as to form a jet that impinged on the upper disc, Fig. 3.

Current immediately vapourised the jet. This interrupted the circuit which was then re-established – to be interrupted again to create current pulses. Operation was therefore automatic and required no moving parts. Each pulse shock excited the secondary circuit at a submultiple of its resonant frequency. In this way, oscillations persisting in the secondary circuit were continually reinforced to produce slightly undulating continuous waves.

Morrietti's device drew power from a 500V DC generator via a variable resistor. This component was presumably intended to synchronize the discharges and bring them in phase with oscillations in the antenna circuit.

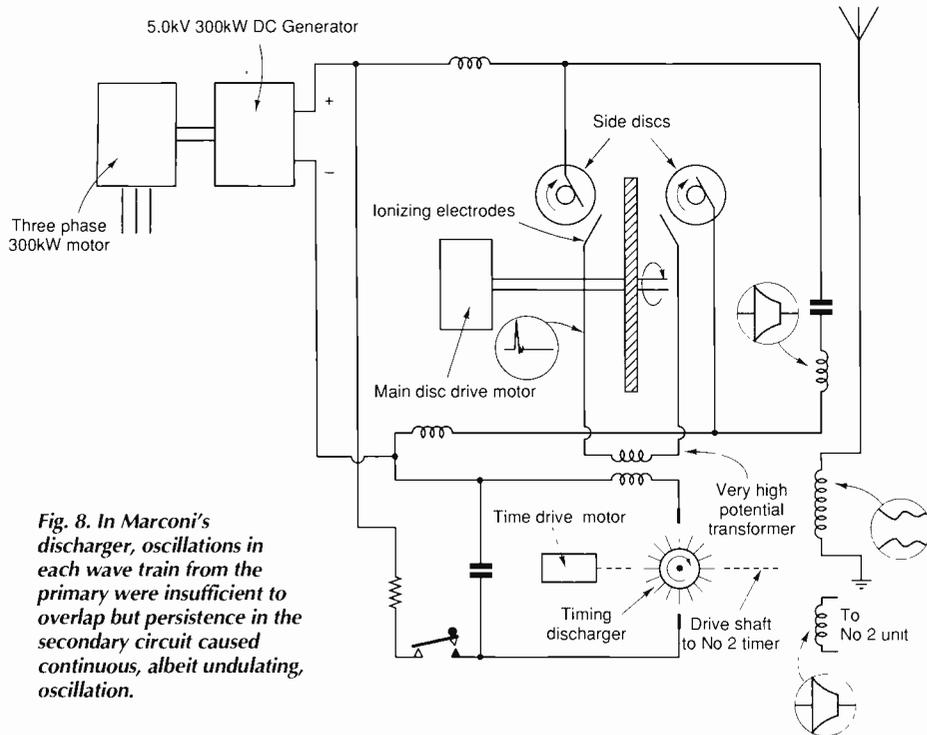

**Fig. 8.** In Marconi's discharger, oscillations in each wave train from the primary were insufficient to overlap but persistence in the secondary circuit caused continuous, albeit undulating, oscillation.

48rev/s (2888rev/min). Precise speed control was vital to keep the trains in phase.

Reinforcement could be made to occur at other points by changing drive speed. By the same token, resonant frequency of the tuned circuits could also be changed, but then drive speed would have to be adjusted to keep wave trains in phase with oscillations persisting in the secondary circuit. However, maximum drive speed was unlikely to have exceeded 50rev/s (3000rev/min) which limited operating frequency to the order of 15kHz. Moreover, the device had an inherent drawback.

In order to handle considerable power, the electrodes had large surface area. Because potentials were high, spark-gaps were fairly

wide. Changes in atmospheric pressure, humidity and presence of ionized gases significantly altered the dielectric strength of air. Therefore, the point at which discharge occurred, varied and this upset timing.

**Caernarvon 200kW timed discharger**

Unfortunately very little information on the operation of the 200kW Caernarvon timed-spark transmitter has been published. Some information regarding the timer even seems to be misleading. This is understandable as there was great commercial rivalry between exponents of alternator and quenched arc systems. Nonetheless, by gleaning information from various sources, and by making a few assump-

tions, I believe that the following notes truly explain the operation of this remarkable transmitter, Fig. 9.

In essence, operation was similar to the experimental timed discharger, but the Caernarvon timed-spark discharger employed two pairs of discharge assemblies. Each of these consisted of a tuned primary circuit, a power discharger and a timing discharger. The timer had a common drive shaft arranged so that discharges occurred in sequence, but in alternate assemblies, as the shaft rotated. Both primary circuits were inductively coupled to the common secondary circuit.

The power dischargers were plain triple-disc types, i.e. with one main disc and two side discs. Discharge was from side disc to main disc to side disc. Independent electric motors rotated the main and side discs. This assisted cooling and created a draught that dispersed ionized gases. Drive speed was not critical and it seems as if they rotated at a relatively low speed, in the order of a few hundred rev/min.


The remarkable feature of these systems was that the distance between the main disc and the side discs was so wide that a discharge could not ordinarily occur at the energising potential of 5kV DC. However, set close to the side discs were a pair of ionizing electrodes.

**Timing discharger**

Both timing dischargers were connected to a common drive shaft and drive motor so that both timing dischargers rotated synchronously. Each discharger had a number of radial electrodes, probably 16, but because timing current was low, the timing electrodes had small face areas. Also, because the potential was relatively low, gap-width was narrow. This allowed close mechanical tolerances which minimised timing errors caused by changes in the dielectric strength of air. When the electrodes of the timing discharger were aligned, gap-width was less than a millimetre.

At each alignment the timer capacitor, charged to 5kV, discharged across the gap and through the primary of an induction-type coil. This induced a very high potential in its secondary winding which in turn caused a spark across the ionizing electrodes which created a conductive path for the main discharge. As a result, the timer can be likened to an automotive capacitor discharge ignition system. Because the power discharger electrodes were in the form of discs, discharge could occur at any time so timing could be precisely controlled.

The 5kV DC 300kW generator delivered 50A charging current to the primary circuit capacitors. This could be generated with dynamos without undue arcing across the commutator segments. Because of the ionizing spark, the power discharge occurred at this relatively low potential of 5kV; moreover, the wide spark gap caused the discharge to be quenched immediately the ionizing spark ceased. Keying was by interrupting the charging current to the timer capacitor as this circuit took only 300mA. Incidentally, although

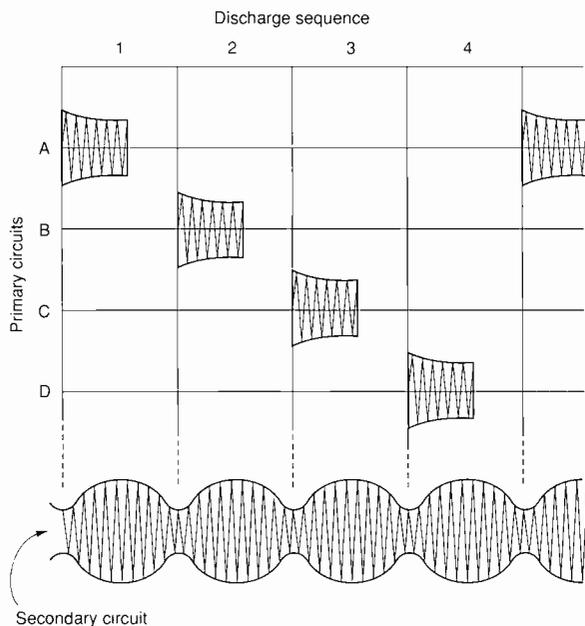

**Fig. 9.** Principles of Marconi's 200kW Caernarvon discharger. Distance between the main disc and side disc would have been too great for discharge were it not for ionizing electrodes.

installed in a brick-silence cabin, the noise caused considerable stress among operators.

### Operation

My original experiments suggest that the time duration of the timing-spark, and consequently the main discharge was probably in the order of 250µs. On this assumption, at 21.42kHz, or 47µs, each train in the primary circuit probably consisted of about five oscillations. Subsequent research suggested that the primary circuit was effectively untuned and discharge was virtually a DC pulse which shock excited the secondary circuit into oscillation. But as I have already explained, the operating mode does not affect timing.

The reason for the half cycle was probably because the two primary inductors were arranged 180° out of phase so that trains started with alternate negative and positive half cycles. Rotational speed of the timer discharger can be determined in exactly the same way as for the experimental timed discharger.

Because the antenna system was in effect a large LC tuned circuit and the linear elements were only a fraction of a wavelength long, it was a poor radiator. This allowed oscillations to persist in the antenna system and progressively build up in amplitude as a result of periodic reinforcement. These aspects made the system workable. But, because of the signifi-

cant time taken for oscillations to build up, signalling speed was limited to about 100 words a minute. Antenna current was 280A and efficiency from generator to antenna was given as 66%.

Although requiring careful adjustment and maintenance, the timed-spark transmitter was reliable. It proved so successful that the manufacture of a duplicate machine was put in hand immediately it came into service, but this was delayed because of difficulty in obtaining materials during the war. It does however seem to have been prone to radiating harmonics. In the meantime, a Poulsen quenched arc was installed as a reserve, but this was incapable of delivering antenna current of more than 170A and could not be worked for long periods without giving trouble.

### Alternators

In 1921, it was decided that in order to increase keying speed and take advantage of improvements in receiver selectivity, it was necessary to replace the timed-spark transmitter with one that produced continuous waves of constant amplitude. Thermionic valve transmitters could meet this criterion with low power installations, but valves that could handle high power had yet to be developed. The only option was the radio frequency alternator. In September 1921, a pair of

200kW Alexanderson rf alternators were installed at Caernarvon and remained in service until about 1923.

In hindsight, Marconi might just as well have adopted alternators in 1906, rather than build the Clifden quenched-arc transmitter. Unfortunately, history never gives the alternative, so we will never know what the outcome would have been if he had. However one thing is certain – neither the synchronous-spark nor the timed-spark transmitters would have been made, and technical historians like myself would not be trying to figure out how these remarkable machines actually worked. ■

### Further reading

Fahie, J. J., *A history of wireless telegraphy*, Dodd-Mead & Co, New York 1901.

Stanley, Rupert, *Text book on wireless telegraphy*, Longmans-Green & Co., Vols I & II, 1914/19.

Baker W. J., *A history of the Marconi Company*, Methuen, 1970.

Laughter, V. H., *The operator's wireless, telegraphy and telephone handbook*, Frederick I. Drake, Chicago, 1909.

Tesla, Nikola, *Colorado Springs notes*, Beograd, Hungary, 1899.

Vyvyan, R. N., *Wireless over thirty years*, 1933. Constable, A., *Early wireless*, 1980.

## LOW COST RANGER1 PCB DESIGN FROM SEETRAX

- **Circuit Schematic**
  - **Circuit Capture**
  - **PCB Design**
  - **Host Of Outputs**
- All-In-One Design System**

**£100**

**Fully Integrated Auto Router**

**£50**

**Ask Us About Trade-In Deals**

**Call Now For Demo Disk on 0705 591037**

Seetrax CAE • Hinton Daubnay House

Broadway Lane • Lovedean • Hants • PO8 0SG

Tel: 0705 591037 • Fax: 0705 599036

**REDUCED PRICE!**

### What The Press Said About RANGER1

For most small users, Seetrax Ranger1 provides a sophisticated system at an affordable price. It is better than EasyPC or Tsien's Boardmaker since it provides a lot more automation and takes the design all the way from schematic to PCB - other packages separate designs for both, that is, no schematic capture. It is more expensive but the ability to draw in the circuit diagram and quickly turn it into a board design easily makes up for this.

**Source JUNE 1991 Practical Electronics**

Pay by Visa or Access



CIRCLE NO. 109 ON REPLY CARD

# Tuning in IF stages

*Ian Hickman sheds light on synchronously tuned IF stages – the design route to the best-shaped IF response for rf instrumentation and pulse/data receivers.*

Most of the selectivity in a single superheterodyne receiver is obtained in one of two sections. These are the intermediate frequency stages, IFs, following the mixer, or in those following the second or third mixer in a multiple superheterodyne design.

In a professional HF communications receiver covering typically 1.6 to 30MHz, the front-end tuning may consist of just a few half-octave filters. Designs with a wide-open front end, apart from a 30MHz low-pass filter, have even appeared. However with ever heavier use of the HF bands, proper front-end tuning is now reappearing.

Whatever the receiver, HF, MW AM, VHF FM or TV, the requirement is the same – to pass with equal amplitude the whole of the band of frequencies occupied by the wanted signal while rejecting all else. This leads to a brick-wall filter design with a flat top and very steep skirts.

For a few specialised receivers, a flat IF filter pass-band with steep skirts is *not* desirable. Two examples are radar receivers and spectrum analysers. In both cases, the IF strip is required to pass pulses. In radar the pulses are reflections of transmitted pulses from a target while in analysers they are the energy of a signal as it is swept through the IF passband by the analyser's tuning sweep.

Of course, selectivity is still required. In the case of the radar receiver selectivity is needed to minimize the noise bandwidth so that only the return-pulse energy is passed. In the case of the spectrum analyser selectivity provides resolving power. A small signal, little removed in frequency from a large one, needs to be seen without it being lost in the skirt of the IF filter's response to the large signal.


According to Zverev<sup>1</sup> a Gaussian filter shape is optimum for pulse response, but he goes on to say that a true Gaussian response is not practicable. The group delay of such a filter would be infinite, so you would wait for ever for a signal applied at the input to come out the other end. So he goes on to give designs that approximate a Gaussian response down to 6 or 12dB.

Modern spectrum analysers often claim a Gaussian response, though how accurate it is is another matter: certainly earlier analysers made do with synchronously tuned IF strips. These are easy to design, build and adjust and are satisfactory for many applications. Further, as far as dynamic response goes, they have the advantage of being free from overshoot, however many stages are cascaded. It is these filters that form the subject of this design brief.

*In a synchronously tuned IF strip, all the tuned circuits are usually identical not only in centre frequency but also in Q. This simplifying assumption is made here.*

Figure 1 outlines a stage which is typical of the strip, together with its equivalent circuit. At an IF between 30 and 40MHz say, the high output impedance provided by a grounded base driver stage and the comparatively high input impedance of a subsequent emitter-follower buffer stage may result in

Fig. 1. Simplified single-tuned IF stage, (a). The transistor driving the tuned circuit has a mutual conductance. To avoid internal feedback to its input, it might be a grounded base stage or the output transistor of a cascode stage. To minimize the reduction of the tuned circuit's unloaded Q, the following stage might be an emitter follower. An equivalent circuit is shown in (b).

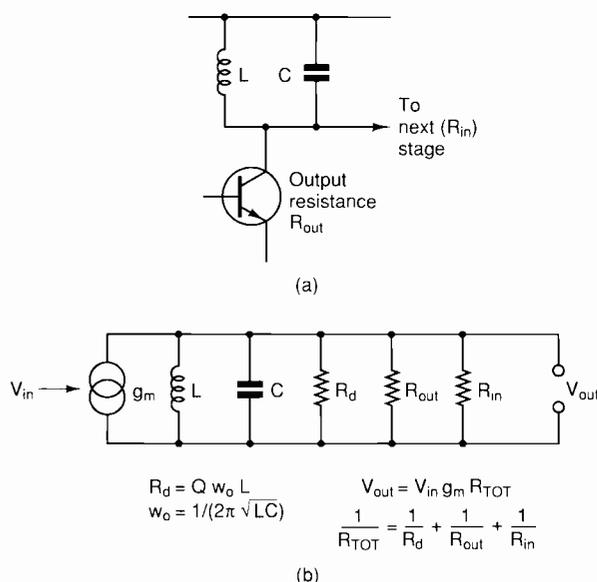

over-heavy damping of the tuned circuit in Figure 1. As a result, the connection to the tuned circuit might be tapped down the coil<sup>2</sup>.

Whatever the working  $Q$ , the stage gain exactly on tune is given approximately by  $g_m R_d$ . Parameter  $g_m$  is the transconductance of the driving stage while  $R_d$  is the operating dynamic resistance of the tuned circuit. Resistance  $R_d$  is equal to  $Q\omega L$  in parallel with the shunt resistive components of the driving and load impedances, ignoring any regeneration.

Selectivity can be increased by tapping the connection further down the coil. This brings the tuned circuit nearer to its unloaded  $Q$  and reduces gain. Conversely increased gain can only be bought at the expense of reduced selectivity.

A good compromise is a working  $Q$  of half the unloaded  $Q$ . There is little more selectivity to be had but gain is much reduced. Demanding any more gain results in a disproportionate sacrifice in selectivity. If input impedance of the following stage is virtually infinite, the driving stage can be matched to the tuned circuit. This corresponds to the half-unloaded  $Q$  condition. Conversely, if the driving impedance is so high as to be an ideal current source, the following stage can be so matched. But in no way is it possible to match both simultaneously.

How the gain varies at frequencies other than the resonant frequency  $f_r$  is discussed in the panel. Armed with the results in the panel, the performance of a synchronously tuned IF strip can be calculated. Figure 2(a) shows the response of a single tuned circuit. It can also represent the response of several synchronously tuned identical circuits, since as Hot Carrier noted, you can "just add the dBs".

From the formula in the panel, you can calculate the 6dB and 60dB bandwidths and hence the 60dB to 6dB shape factor. For a brick-wall filter in a communications receiver this might be well under 3:1. For a spectrum analyser however, using either a Gaussian or a synchronously-tuned filter, it may be typically between 10:1 and 20:1.

To calculate the 60dB to 6dB shape factor for an IF strip with four synchronously tuned stages, Fig. 2(b), simply evaluate the 1.5dB to 15dB shape factor for a single tuned circuit. I have done this for several shape factors and numbers of stages, Fig. 3. If the working  $Q$  of the tuned circuits was very high, the 60dB to 6dB shape factor of the  $N=2$  IF strip of Ref. 2 would be 31.7:1.

Also shown in Fig. 3 is the 6dB to 1dB shape factor, which it turns out actually improves with the number of stages. The passband becomes squarer with an increasing number of stages – something I had not previously realised. The improvement is not dramatic. There is little change beyond three stages. But it is nonetheless useful.

Note the assumption that  $x_L - x_C$  (or *vice versa*) is still small compared to  $2\pi f r_L$  or, equally, to the reactance of the capacitor at resonance. For a single tuned circuit, this means that the calculated detuning to  $A=60\text{dB}$  is only accurate if  $\omega L$  is very much greater than  $1000\Omega$ . This is an impossible specification for a discrete LC circuit but not so for a crystal. Even a very mediocre crystal has a  $Q$  of 10,000 and some 100,000 or more.

Crystals are used in the more selective filters in a spectrum analyser to permit better resolution of closely spaced signals. This is especially important in an instrument having an on-screen logarithmic display of 60dB or more. In a simple instrument with a linear

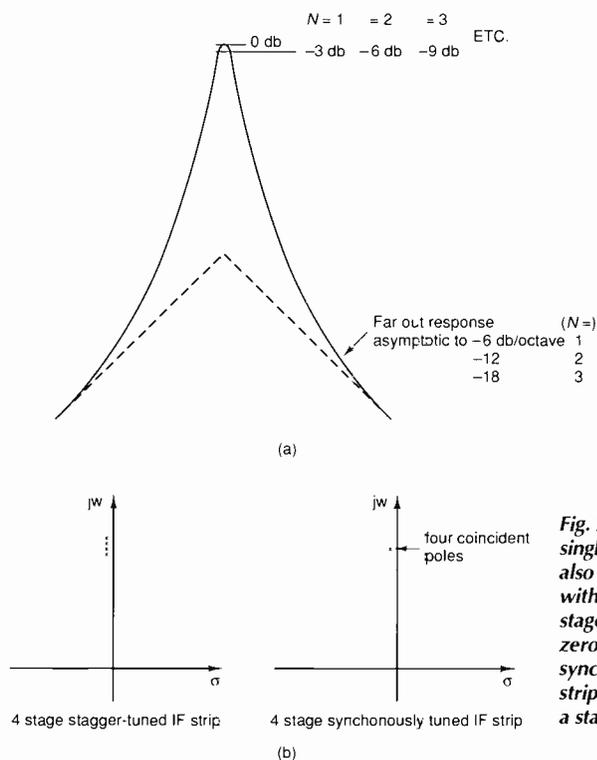


Fig. 2. Response curve for a single tuned circuit can also represent an IF strip with several identical stages (a). At (b) is a pole zero diagram of a synchronously tuned IF strip compared with that of a stagger tuned strip.

Shape factor	Poles (stages)	1	2	3	4	5
1 : 60 db		1 : 1965	90.5	35.2	22.7	17.8
3 : 60 db		1 : 1002	49.2	19.6	12.7	10.0
6 : 60 db		1 : 579	31.7	13.0	8.6	6.8
1 : 60 db		1 : 3.4	2.85	2.71	2.64	2.62

Fig. 3. Pole versus shape-factor ratios for synchronously tuned IF strips with different numbers of stages.



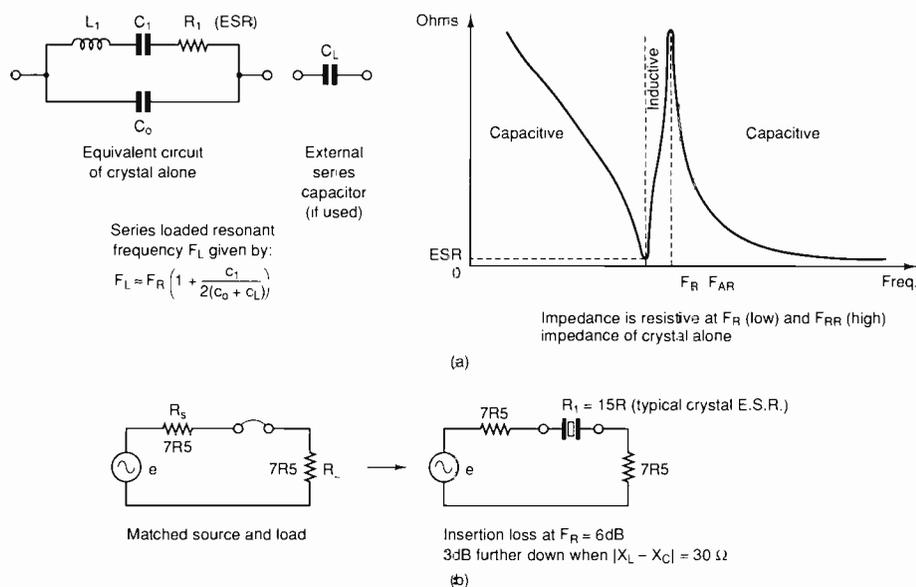


Fig. 4. Equivalent circuit of a quartz crystal, and the variation of its impedance in the vicinity of series resonance, including parallel resonance. Diagram (b) shows how, ignoring  $C_0$ , series resonance can provide a very narrow passband when working between source and load impedances comparable with its equivalent series resistance.

# DESIGN BRIEF

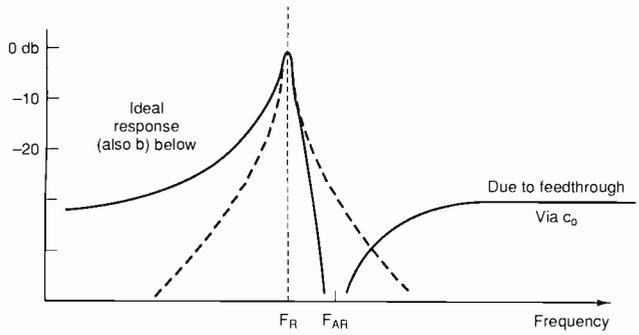

(a)

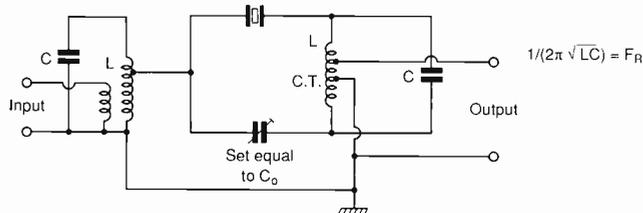

(b)


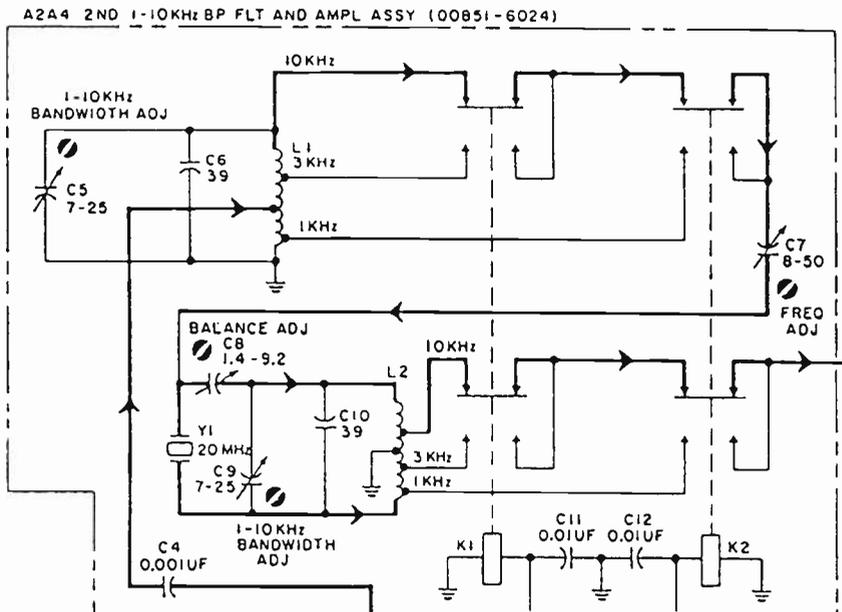


Fig. 5. Response of filter of Fig. 4 (b) taking into account  $C_o$  is shown in the graph. Middle circuit illustrates obtaining a symmetrical response and high out-of-band attenuation by out-phasing the signal via  $C_o$ . Capacitance  $C_o$ , the trimmer and the centre tapped tank circuit form a balanced bridge, suppressing the effect of  $C_o$ . Main circuit (c) is as used in an early HP852A spectrum analyser to obtain resolution bandwidths of 1, 3 and 10kHz using a single crystal. Two such synchronously tuned stages were employed in cascade to obtain a satisfactory shape factor.

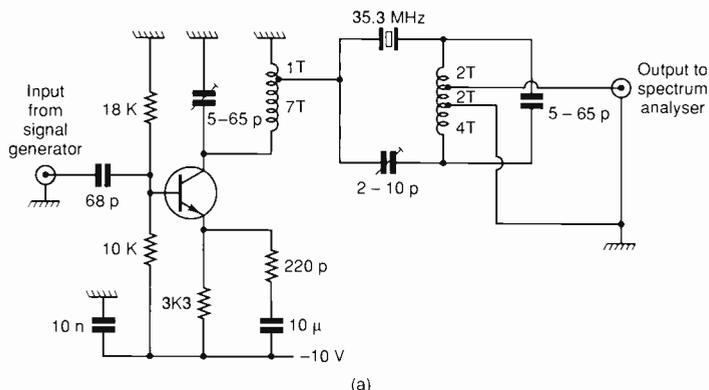

(a)

display however, as in Ref. 2, lower selectivity is acceptable.

Figure 4(a) shows the equivalent circuit of a crystal,  $C_o$  being the capacitance between the two electrodes plus the strays due mounting and encapsulation. Components  $L_1$ ,  $C_1$  and  $R_1$  are the electrical equivalents of the crystal's motional inductance and capacitance, and damping. Although the vibrational resonance of the crystal has a very high  $Q$ , there is some inevitable loss partly due to the quartz itself and partly due to the mounting arrangements.

In addition to a very high  $Q$ , the crystal has a very high  $L/C$  ratio, the significance of which will become apparent. A typical 35MHz crystal has an inductance of 8.8mH and a motional capacitance  $C_1$  of 0.0023pF. The equivalent series resistance,  $R_1$ , might be typically 15Ω. The crystal's shunt capacitance  $C_o$  is around 5pF. Figure 4(b) shows how, ignoring  $C_o$  for the moment, the series resonance of a crystal can be used to provide a very narrow bandwidth filter. When it is introduced into the particular circuit shown, insertion loss at resonance will be 6dB. Total circuit resistance will be 30Ω.

As an input signal is tuned away from resonance, the response will be a further 3dB down when the reactance of the crystal has risen to 30Ω. This corresponds to a fractional detuning  $\delta$  which is easily arrived at. The reactance at resonance of  $L_1$  or  $C_1$  for

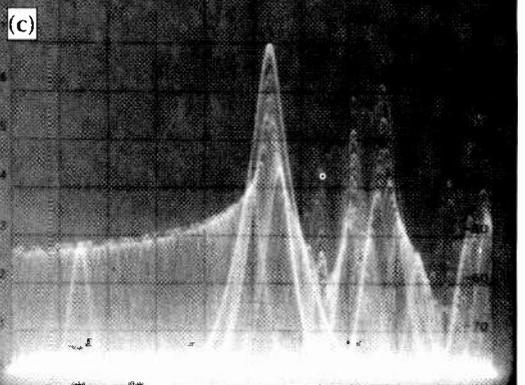
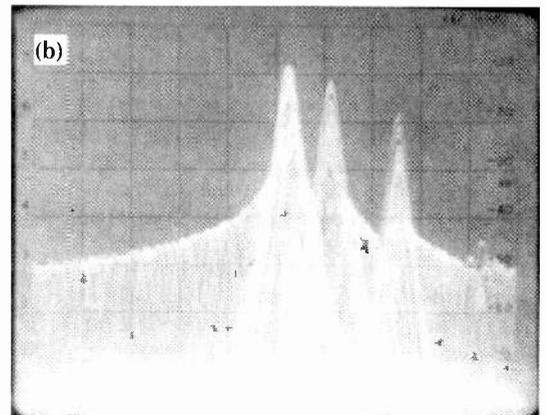


Fig. 6. Circuit diagram of an experimental crystal filter stage (a) using a 35.3MHz crystal with 5mm electrodes.

In (b), main (centre) and spurious responses of (a) are shown at 50kHz/div horizontal, 10dB/div. vertical, and analyser bandwidth of 10kHz. Actual filter responses are only a few hundred hertz wide. Much wider analyser bandwidth was selected for clarity.

Curve (c) is as (b) but for a crystal with 3mm electrodes. Note that spurious responses come in different places.

the typical crystal quoted is given by

$$2\pi \times 35\,000\,000 \times 8.8 \times 10^{-3}, \text{ or } 1.935\text{M}\Omega.$$

Reactance of the crystal will have risen to  $30\Omega$  when the reactance of the inductance has increased by  $15\Omega$ . This is because reactance of the capacitance will have fallen by the same amount. Since reactance of an inductor is directly proportional to frequency, it will have increased by  $15\Omega$  for a frequency increase of 15 parts in 1 935 000. At 35MHz, this amounts to 271Hz, giving a 3dB bandwidth of only 542Hz. The significance of the very high  $L/C$  ratio is now apparent. Assume however that the source and load impedances had each been  $75\Omega$ , giving an insertion loss in Fig. 4(b) of not 6dB but less than 1dB. Now the reactance of the crystal would need to rise to  $165\Omega$  to increase the loss by 3dB, giving about ten times as great a 3dB bandwidth.

Unfortunately, the presence of  $C_0$  means the simple filter of Fig. 4(b) is not practical. At frequencies above the series resonance of  $L_1$  and  $C_1$ , the series

arm of the crystal looks inductive. At some frequency this inductance will form a parallel resonant circuit with  $C_0$ . This is often called the crystal's antiresonant frequency.

Reactance of 5pF at 35MHz is  $910\Omega$  so parallel resonance occurs when the reactance of  $L_1$  has risen by  $455\Omega$ , i.e. at 35.008 230MHz. This is about 8kHz above the series resonance. In Fig. 4(b), this would result in a very large attenuation at that frequency. At other frequencies, the out-of-band attenuation would be limited to a modest figure due to signal feed-through via  $C_0$ .

Limiting can be avoided by the arrangement in Fig. 5(b). Another capacitor, equal to  $C_0$ , is used to outphase the effect of  $C_0$  itself, by incorporating it into a balanced bridge. Figure 5(c) shows one of two such stages employed in the 20MHz IF stages of an early design of spectrum analyser. Working the crystal between a low source resistance (tapped well down the driving tank-circuit) and a low load resistance (second tank circuit very heavily loaded)

## The tuned circuit

In the tuned circuit shown, drive is inductively coupled via a single closely coupled turn. This effectively generates a small voltage from a near zero source impedance generator in series with the inductor. The arrangement is actually a series resonant circuit. However for values of  $Q$  high enough to be useful, say twenty or greater, the performance is virtually the same as the current-fed parallel circuit of Fig. 1.

This is illustrated in the diagram below, which shows the situation at a frequency slightly above  $f_r$ . Here the reactance of the inductor is somewhat greater than that of the capacitor. The usual assumption that the capacitor is loss free, and the  $Q$  determined solely by the inductor, has been made. It is also assumed that  $Q$  is large so that  $\omega L \gg r$ , the coil's series rf loss resistance.

At  $f_r$ , i.e. on tune,  $\theta$  is zero and circulating current  $i$  is  $e/r$ . Output voltage across the capacitor  $V_0$  is  $i \cdot x_c$  where  $x_c$  is the capacitor's reactance at  $f_r$ , namely  $1/(2\pi f_r C)$ . If, for example, frequency rises by 1%, then so does the reactance of the inductor. Reactance of the capacitor on the other hand falls by 1% – almost exactly. This result is due to the Binomial Theorem. The difference between  $x_L - x_C$ , shown in the second diagram below, has risen from zero to 2% of the

reactance of either at resonance.


The third side of the triangle  $z$  is the impedance in which  $i$  now flows. If the value of  $i$  at resonance is taken to be unity, the off-tune value is  $r/z = \cos\theta$ . So if in the example  $Q$  were 50,  $x_L - x_C$  would be 2% of  $Qr$ , namely equal to  $r$ . Thus  $\theta$  would be  $45^\circ$  and  $1/z = \cos\theta = 0.707$ , or -3dB. This is the fall in the value of  $i$ , but since  $x_c$  has only fallen by 1% it is also approximately the fall in  $V_0$ . Cosine  $\theta$  is thus the approximate per unit response of the circuit, i.e. the output relative to an assumed on-tune output of unity. Tan  $\theta$  is  $(x_L - x_C)/r$  which works out to be  $Q(\omega/\omega_c - \omega_c/\omega)$  or approximately, courtesy of the Binomial Theorem again,  $2Q\delta$ , where  $\delta$  is the 'per-unit' detuning; for 5% off tune  $\delta$  is 0.05.

Armed with these approximate results, finding the detuning corresponding to any given relative attenuation is easy. For example, for 6dB down, first convert the attenuation to a 'per unit' value, i.e. -6dB is equivalent to 0.5. Now take the inverse cosine, in this case  $60^\circ$ , take the tangent of  $60^\circ$  1.73 and this value equals  $2Q\delta$ . So any tuned circuit for which our approximations are valid is 6dB down at  $\delta = 1.73/(2Q)$ , e.g. at  $\delta$  is 0.0173 (1.73% off tune) if  $Q$  is 50.



The following works out the 'per unit' or fractional detuning  $\delta$

for any attenuation  $A$  dB down, for any number of stages  $N$  the selectivity of each being given by  $Q$ , on a calculator.

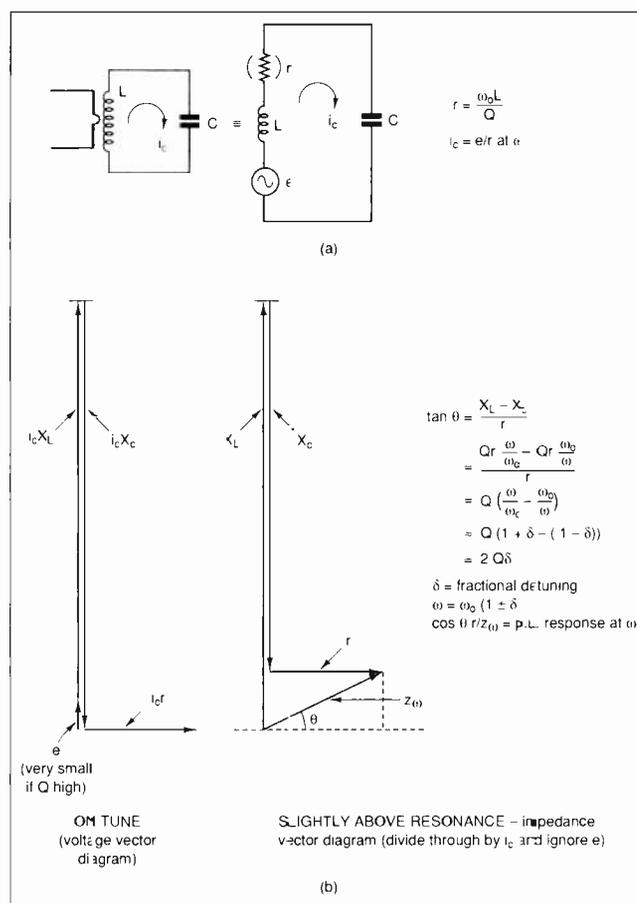ENTER  $N$  Kin1 ENTER  $A$   
divide  $Kout1 =$  divide  $20 =$   
 $10^{x/20}$   $1/x$  inv  $\cos$  tan  
divide 2 = divide  $Q =$   
(answer)



Inductively coupled tuned circuit and its equivalent in series-excited form. Associated vector diagrams are also shown.

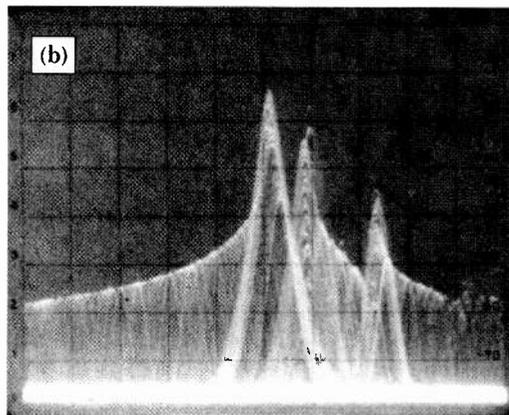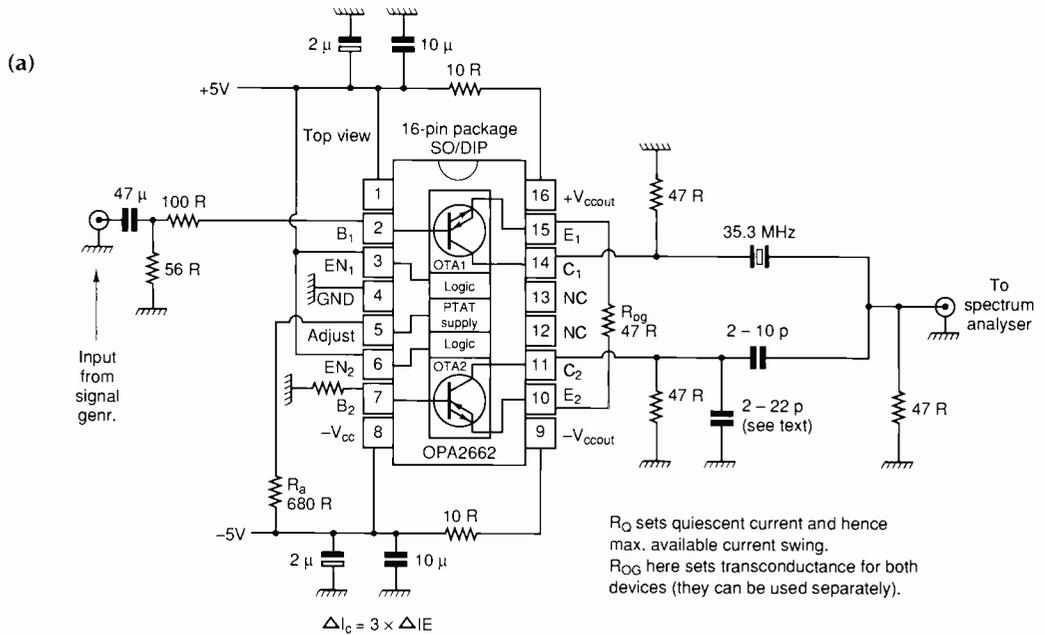

**Fig. 7.** Using a OPA2662 dual transconductance amplifier to provide a balanced drive to the filter section without a centre-tapped coil (a). In addition to providing complementary outputs, this IC also handles single-ended to balanced conversion. Performance of (a) using the 35.3MHz crystal with 5mm electrodes is shown in (b). It is identical to that of the circuit of Fig. 6(a) – compare with Fig. 6(b).

provides the narrowest bandwidth. Between high source and load resistances it provides the widest bandwidth.

When using crystals to implement narrow-band synchronously-tuned filters, there are other problems to cope with, in addition to  $C_o$ . For instance, at frequencies somewhat above  $f_r$  a crystal usually has one or more subsidiary resonances or “spurious responses”. This is illustrated in Figs 6(a) and (b). The spectrum analyser used had no built in tracking generator; a signal generator was swept slowly back and forth across the band. Actual filter responses are very narrow, a much wider analyser resolution bandwidth being selected for clarity.

Since at least two such stages would usually be necessary to obtain the required shape factor, the second stage would use a crystal with the same  $f_r$ , but where the spurious resonances fell at different frequencies. While that in Fig. 6(b) has 5mm electrodes, the crystal in Fig. 6(c) has 3mm electrodes (from McKnight Fordahl, Hythe). Note that the two halves of the centre-tapped second tank-circuit, Fig. 6(a), should ideally be very tightly coupled, especially if output is being taken from another tap on the coil.

Alternatively, the coil could be replaced by a centre-tapped resistor, the two ends connecting to an op-amp whose common-mode rejection is maintained up to radio frequencies. Example of such ICs are the LT1193 from Linear Technology and the MAX436

from Maxim. Both these devices have gain-defining arrangements independent of the inverting and non-inverting inputs. This makes both inputs high impedance nodes. The filter section itself, being entirely passive, could be used in reverse, i.e. the balanced end could be the input.


Using the filter in reverse provides yet another opportunity to replace the centre-tapped tank circuit with an IC, as shown in Fig. 7. This circuit uses a Burr-Brown OPA2662 dual transconductance amplifier. A small trimmer from pin 14 to ground was necessary to maximise the stop-band rejection by adjusting the balanced outputs for exact anti-phase.

When using crystals in synchronously tuned IF strips, the final hurdle to overcome is the selection tolerance on  $f_r$ . The tighter the tolerance the higher the cost. As a result, the final adjustment is made with the aid of a series trimmer, shown in Figure 5(c) as  $C_7$ . A fixed capacitor is used in this position as in the other crystal filter stage. The crystals are thus operated slightly above series resonance, where their inductive reactance resonates with the series capacitor or trimmer. ■

**References**

1. Zverev, A. I., *Handbook of Filter Synthesis*, John Wiley and Sons, 1967.
2. Wheeler, N., *Spectrum analysis on the cheap*, EW+WW, March 1992, pp 205 & 205.

# PROMulators

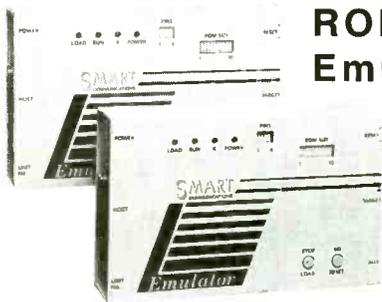

ROM/RAM Emulators

Fast Flexible

from only **£99**

- ✓ Emulate up to 4 by 8 Mbit EPROMs via one standard printer port
- ✓ Download 4 Mbit in 10 seconds
- ✓ Accepts Intel Hex, Motorola S-Records and Binary files
- ✓ Emulates 24, 28, 32, 40 and 42 pin devices
- ✓ Full screen editor
- ✓ Bi-directional communications between your target board and the PC

CALL FOR FULL DATA SHEETS

Tel: 081-441 3890  
Fax: 081-441 1843

**SMART**  
COMMUNICATIONS

CIRCLE NO. 110 ON REPLY CARD

**NEW**

## THE DEFINITIVE 'OFF-AIR' FREQUENCY STANDARD



Only **£195** + VAT carriage extra

- ★ Provides 10MHz, 5MHz & 1MHz, VXCOs, oven crystals
- ★ Phase locks to DRO/TWICH (rubidium controlled and traceable to NPL)
- ★ For ADDED VALUE also phase locks to ALLOUIS (cesium controlled and traceable to OP — French eq to NPL)
- ★ British designed and British manufactured
- ★ Now with Sine Wave Option, output 1 volt into 50Ω

Output frequencies — 10MHz, 5MHz, 1MHz  
Short term stability — better than  $1 \times 10^{-8}$  (1 sec)  
Typical —  $\pm 4 \times 10^{-9}$  (1 sec)  
Long term — tends to  $2 \times 10^{-12}$  (1000 sec)

DAWE 140SD SOUND LEVEL METER 0-120dB(A)	£75	UPS MICROPAC SX250 250W	£135
IWATSU SS5116 DUAL TRACE, 10MHZ	£175	CITOH CX6000 6PEN A4 PLOTTER, CENT/RS232	£135
TELEQUIPMENT D1011 10MHZ DUAL TRACE	£165	GENERAL RADIO 1531A XENON STROBOTAC	£79
IWATSU SS-5802 DIGITAL STORAGE	POA	THANDART G501 FUNC GEN 0.005HZ-5MHZ	£165
SCOPEX 456 6MHZ SINGLE TRACE	£95	BACHARACH MV2 MERCURY SNIFFERS	£79
TEKTRONIX 2215 60MHZ 2 TRACE DEL T/B	£450	FISONS FI-MONITORS LIQ LEVEL SENSORS	£85
TEKTRONIX 453A 50MHZ 2 TRACE DEL T/B	£249	JANKE & KUNKEL HI SPEED MIXERS 20KRPM	£29
TELEQUIPMENT S62 SINGLE TRACE 5MHZ SCOPE	£95	JAQUET TIMER 1110SECS RES'N 01SEC	£59
H.P. 8405A VECTOR V/METER 1GHZ	£595	COMMODORE PETS, DDRIVES, PRINTERS	£29EA
PLESSEY TCT10 SIG GEN/ANAL 50-300 BDS	£95	COMARC 2303 MV SOURCES, DUAL RANGE	£49
TELEQUIPMENT D61A 10MHZ DUAL TRACE	FROM £99	INTRON IFG422 FUNC GEN 0.1HZ-2MHZ	£125
TEK 465B 100MHZ DUAL TRACE DEL T/B	£475	ECG MONITOR SEM430 WITH SEM420/2	£75
TELEQUIPMENT D67A 25MHZ, 2T, DEL T/B	£215	GOULD 2400 4-PEN CHART RECORDER	£195
H.P. 1700A 35MHZ DUAL TRACE	£249	X-Y PLOTTERS A3 & A4	FROM £35 to £139
HITACHI VC 6015 10MHZ DIGITAL STORAGE	£345	PHILIPS PM6456 FM STEREO GENERATOR	£115 & £190
HP1340A X-Y DISPLAYS	£149	7SEG 12" & 9" DISPLAYS DIGITEX/SIGNALEX	£15 to £110
OERTLING V20 SINGLE PAN BAL 0.1MG/200GM	£69	VALVE TESTERS AVO MK 1.2.3	from £49 to £89
ANALYTICAL BALANCES WITH WEIGHTS 250GM	£69	MARCONI TF2300 FM/AM MODULATION METER	£95
VACUUM PUMPS 1.5 & 2.8 CU./MHR	£125 & £149	McKENZIE 7 DAY TEMP/HUMIDITY RECORDER	£95
KINGSHILL NS1540 15V 40A PSU'S CASED, AS NEW	£195	FEEDBACK SS0603 1MHz SINE/SQ OSC	£125
ACRON 402P SYNCHRONISING PULSE GEN & 60SP ENCODER	£375 Sea £695/pr	FARNELL E350 0-350v 100mA, 2 x 6.3V	£59 to £69
RADIOMETER BKF6 DIST. METER 20HZ-20KHZ	POA	FARNELL FG1 FUNC GEN 2-2.2MHZ	£129
RADIOMETER AFM2 MOD. METER 7MHZ-1GHZ	POA	COMMUNICATIONS RECEIVERS, HF, LF, VHF	POA
MARCONI TF2304 AM/FM MOD METER PR/BL	£249	LCR MARCONI TF1313 0.25%	£95
MARCONI TF2330 WAVE ANALYSER 20HZ-50MHZ	£149	LCR COMPONENT COMPARATOR AVO CZ457/5	£95
H.P. 5315A 1GHz F/CTR. OPTS 1, 2 & 3	£750	LEVELL TM68 MICRO V-METER 450MHZ	£95
		LEVELL TM38 MICRO V-METER 3MHZ	£85

LIST AVAILABLE BUT 1000's OF UNLISTED BARGAINS FOR CALLERS. ALL PRICES EXC. OF P&P AND VAT QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED

**HALCYON ELECTRONICS**  
423, KINGSTON ROAD, WIMBLEDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383. FAX 081-542 0340

CIRCLE NO. 111 ON REPLY CARD


## SpiceAge for Windows

### Are you up to date with the latest in circuit simulation?

Development on SpiceAge for Windows since its introduction in 1991 has been moving at a pace. SpiceAge 2 for Windows arrived in the autumn of last year. SpiceAge 3 for Windows is available for Christmas 1993.

V3 provides digital simulation an order of magnitude faster than before. It has a 32 channel logic analyser display, input signal bus grouping plus more digital models, but unlike logic simulators, you can of course see the analogue effects of capacitive loads, pull-ups, diodes etc. Analogue developments include bundling of the Zetex SPICE library and a brand new opamp model.

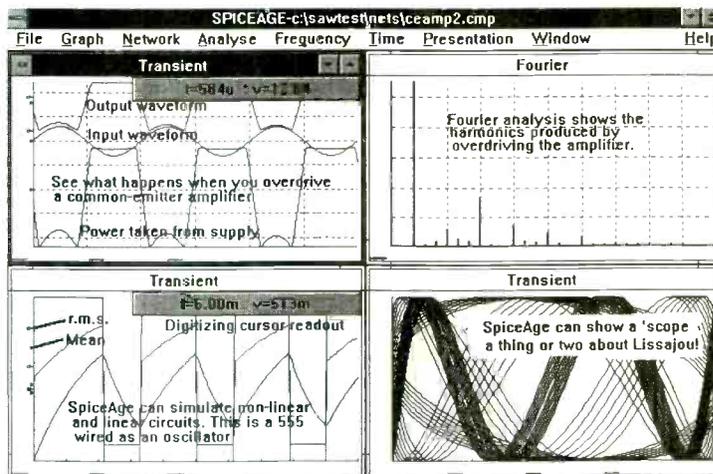
Existing SpiceAge for Windows owners will be notified of these developments by post. Owners of the Original SPICE-AGE, BITSPICE, LOGANOU and NODALOU should contact us for upgrade details. If you are new to SpiceAge for Windows, please phone us for a demonstration kit. Those Engineers Ltd, 31 Birkbeck Road, LONDON NW7 4BP. Tel: 081-906 0155, Fax: 081-906 0969.



CIRCLE NO. 112 ON REPLY CARD

# LIVELINES
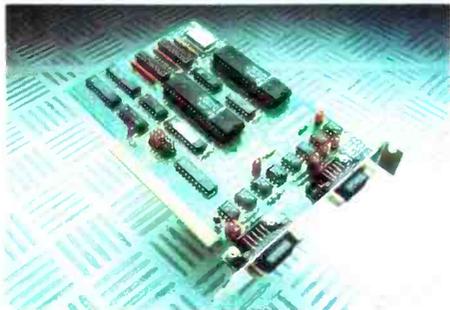
## Dual port serial communications for your PC



The PC 47, 48 and 49AT boards each provide two independent serial ports for any PC/XT/AT(ISA) computer. RS232, RS422 and RS485 standards are supported and all combinations are possible with this range of low power boards.

9 pin D connectors are provided for the RS422 and 485 ports. RS232 can be connected via 9 or 25 way D connectors and charge pump circuitry ensures signal levels in excess of 7V are transmitted.

Interrupt and base addresses are independently selectable for each port, full, half duplex and multidrop communications are fully supported and all boards use the industry standard 82C450, UART.

Designed and manufactured by Amplicon Liveline each board is supplied with a comprehensive technical manual and interrupt driven device driver software is available.

**Write in number 1**


## 750kHz professional data acquisition with Windows support

PC226 from Amplicon Liveline provides 16 true differential 12 bit analog inputs each with dynamically programmable gain. PC226 has sample rates up to 400kHz multichannel and 750kHz single channel, programmable scanning hardware, flexible triggers and a 2048 sample FIFO to ease programming in high speed applications.

PC 226 is supplied with menu driven software for DOS and Windows, LabTech Notebook drivers and comprehensive well documented libraries for most popular high level languages.

Optional software support for Microsoft Windows includes a complete Dynamic Link Library (DLL) and two icon driven packages, Signal Centre for signal capture and analysis and TRACS for process monitoring, visualisation and control.

**Write in number 2**

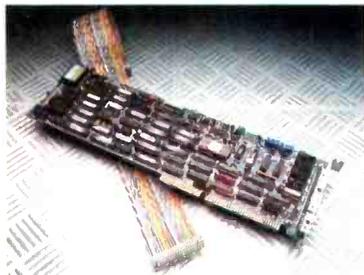


## 48 lines TTL I/O with 16bit counter timers

PC 14AT available from Amplicon Liveline is a high quality general purpose interface board for PC/XT/AT(ISA) computers.

The board has 48 lines of TTL compatible digital I/O provided as six 8 bit ports four of which can be programmed to be all inputs or all outputs and two which can be split to be 4 inputs and 4 outputs if required. There are also three 16bit counter timers which can be used to generate and measure pulses at up to 5MHz.

An on board 4MHz crystal oscillator is also included on PC 14AT along with LEDs showing the status of a selection of the I/O ports, these can be used as programming and debugging aids.

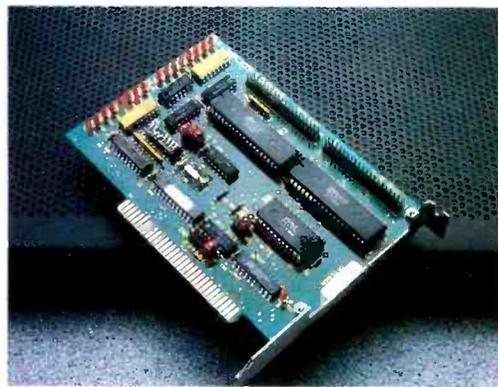PC 14AT is suitable for a wide variety of interface, monitoring and control applications



and an LP (low power) version PC 14LP is available for installation in laptop computers, both boards have flexible base address and interrupt support. **Write in number 3**

# THE WINNING LINE.

-  *Large colour catalogue - free*
-  *24 hour phone and fax lines*
-  *Knowledgeable engineers for help*
-  *Same day despatch*
-  *Excellent support material*
-  *Certified quality FM 15094*
-  *After sales support*

For up to the minute information on over 1,000 high quality, high specification electronic products, make sure you've got the latest AMPLICON catalogue.

It's not just first class equipment that makes AMPLICON your first choice- we provide outstanding service too: like telesales engineers for pre and post sales support. Easy to manage corporate accounts. Excellent documentation... and same day despatch for orders received before 5 pm.

To order your free catalogue, simply phone the winning line today.

# AMPLICON

## LIVELINE

### 0800 52 53 35

**GET ON... WITH AMPLICON.**

DATA ACQUISITION POWER SUPPLIES  
INSTRUMENTATION INDUSTRIAL DATACOMMS  
TEST AND MEASUREMENT

*Some of the most common sources of distortion in audio power amplifiers relate to the electrical and physical layout of the circuit, an area overlooked by many designers. In his continuing search for the perfect audio amplifier Douglas Self explains the mechanisms.*

# Distortion in power amplifiers

## 6: the remaining distortions

The previous two parts of this series considered closely the distortion produced by amplifier output stages: a basically conventional but well designed Class-B amplifier with proper precautions taken against the various sources of nonlinearity can produce insignificant levels of distortion. That which is generated is mainly due to the difficulty of reducing high order crossover nonlinearities with negative feedback that has declining effectiveness with frequency. For  $8\Omega$  loads this is the major source of distortion. For convenience, I have chosen to call such a device a *blameless* amplifier.

### Distortion 3: quiescent current control

An optimised amplifier requires minimisation of output stage gain irregularities around the crossover point by holding the quiescent current  $I_q$  at its optimal value. Increasing  $I_q$  to move into Class-AB makes the distortion worse, not better, as  $g_m$ -doubling artifacts are generated.

The initial setting of quiescent current is simple, given a distortion analyser to get a good view of the residual: keeping that setting under varying operating conditions is a much greater problem because  $I_q$  depends on small voltages established across low value resistors by power devices with thermally dependant  $V_{be}$  drops.

How accurately does quiescent current need to be maintained? I wish I could be more specific on this. Some informal experiments with Blameless CFP type outputs at 1kHz indicate that crossover artefacts on THD residual seem to stay at roughly the same level, partly submerged in the noise, over an  $I_q$  range of about 2:1, the centre of this region being around

20mA. Results may well be different for emitter follower type outputs.


This may seem a wide enough target, but given that junction temperature of power devices may vary over a  $100^\circ\text{C}$  range, this is not so. Some kinds of amplifier (eg current dumping types) manage to evade the problem altogether, but in general the solution is thermal compensation: the output stage bias voltage is set by a temperature sensor (usually a  $V_{be}$  multiplier transistor) coupled as closely as possible to the power devices.

There are inherent inaccuracies and thermal lags in this sort of arrangement leading to programme dependency of  $I_q$ . A sudden period of high power dissipation will begin with the bias current increasing above optimum, as the junctions will heat up very quickly. Eventually the thermal mass of the heatsink will respond, and the bias voltage will be reduced. When the power dissipation falls again, the bias voltage will now be too low to match the cooling junctions and the amplifier will be under biased, producing crossover spikes that may persist for some minutes. This is well illustrated in an important paper by Sato<sup>1</sup>.
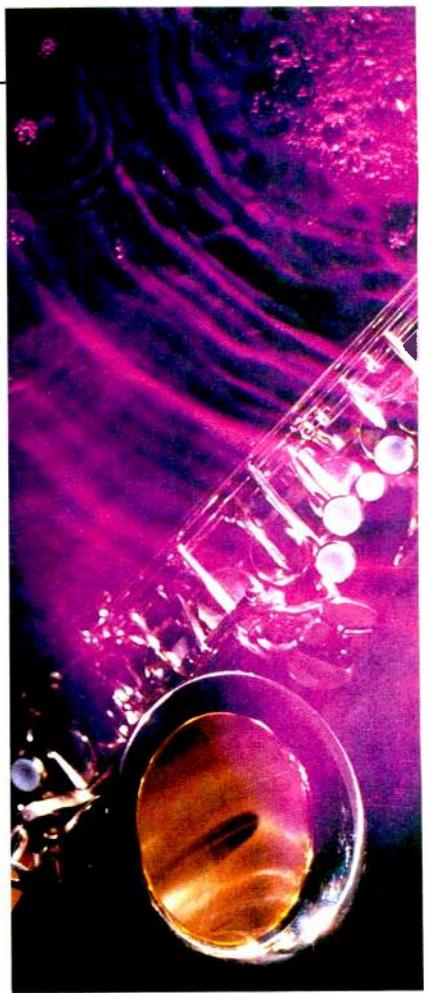
### Blameless amplifiers

I have adopted the term *blameless* to describe a Class-B amplifier designed in accordance with the philosophy of this series, with the use of simple circuit enhancements to minimise distortions 1,2 and 4, and correct layout to prevent distortions 5,6 and 7. Such a device will still suffer from output stage distortion 3, and so exhibit measurable distortion at high frequencies due to the difficulty that NFB has in dealing with the high order crossover distortion products generated by a conventional (but well designed) output stage. Distortion will usually be greater when driving loads below  $8\Omega$ .

The word is specifically chosen to imply the avoidance of error but not perfection.



### Emitter follower outputs

The major drawback of emitter follower output stages is thermal stabilisation. This can cause production problems in initial setting up since any drift of quiescent current will be very slow as a lot of metal must warm up.

For EF outputs, the bias generator must attempt to establish an output bias voltage that is a summation of four driver and output  $V_{be}$ 's. These do not vary in the same way. It seems at first a bit of a mystery how the EF stage, which still seems to be the most popular output topology, works as well as it does. The probable answer is Fig. 1, which shows how driver dissipation (averaged over a complete cycle) varies with peak output level for the three kinds of EF output, and for the CFP configuration. The Spice simulations used to generate this graph used a triangle waveform to give a slightly closer approximation to the peak-average ratio of real waveforms. The rails were  $\pm 50\text{V}$ , and the load  $8\Omega$ .

It is clear that the driver dissipation for the EF types is relatively constant with power output, while the CFP driver dissipation, although generally lower, varies strongly. This is a con-

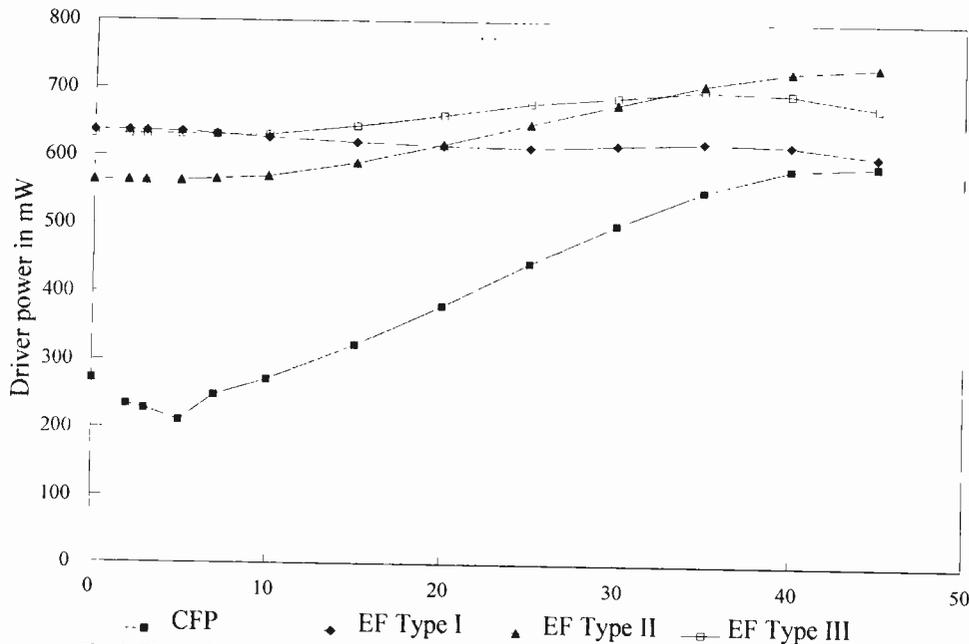


Fig. 1. The variation in driver dissipation with output for the three EF output topologies and the CFP output. All three EF types keep driver power fairly constant, simplifying the thermal compensation problem.

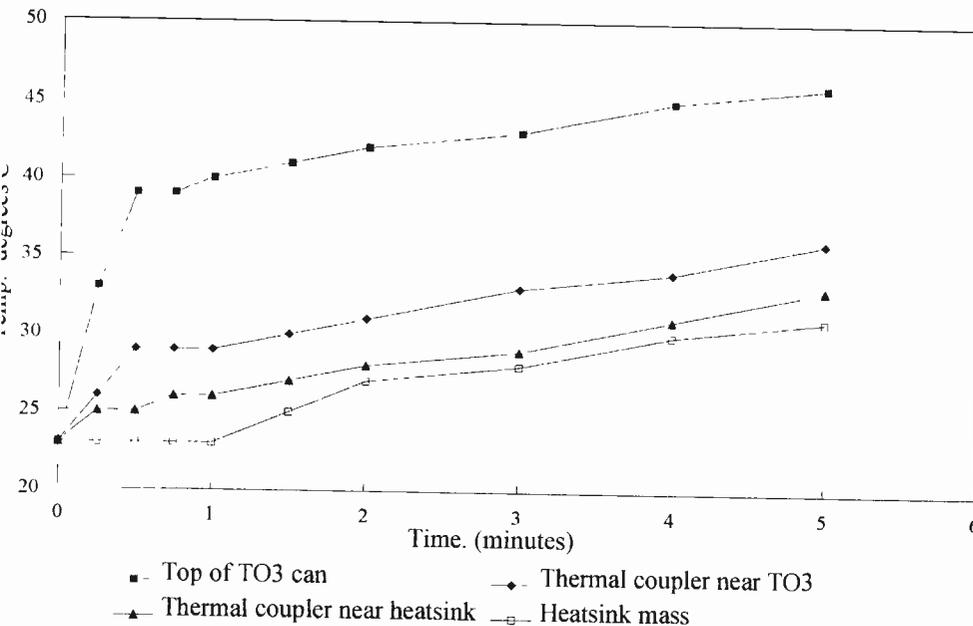


Fig. 2. Thermal response of a TO3 coupled to a large heatsink when power is abruptly applied. The top of the TO3 can responds most rapidly.

sequence of the different operation of these two kinds of output. In general, the drivers of an EF output remain conducting to some degree for most or all of a cycle, although the output devices are certainly off half the time.

In the CFP, however, the drivers turn off almost in synchrony with the outputs, dissipating an amount of power that varies much more with output. This implies that EF drivers will work at roughly the same temperature, and can be neglected in arranging thermal compensation; the temperature dependent element is usually attached to the heatsink to compensate for the junction temperature of the output devices alone. The Type I EF output keeps its drivers at the most constant temperature.

The above does not apply to integrated Darlington outputs, with drivers and assorted emitter resistors combined in one ill-conceived package where the driver sections are directly heated by the output junctions. This works directly against quiescent stability.

The drawback with most thermal compensation schemes is the slow response of the heatsink mass to thermal transients. The obvious solution is to find some way of getting the sensor closer to one of the output junctions. If TO3 devices are used, then the flange on which the actual transistor is mounted is as close as one can get without a hacksaw. This is however clamped to the heatsink, and almost inaccessible, though it might be possible to hold a sensor under one of the mounting

bolts. A simpler solution is to mount the sensor on the top of the TO3 can. This is probably not as accurate an estimate of junction temperature as the flange would give, but measurement shows the top gets much hotter much faster than the heatsink mass, so while it may appear unconventional, it is probably the best sensor position for an EF output stage.

Fig. 2 shows the results of an experiment designed to test this. A TO3 device was mounted on a thick aluminium L-section thermal coupler in turn clamped to a heatsink; this construction represents many typical designs. Dissipation equivalent to 100W/8Ω was suddenly initiated, and the temperature of the various parts monitored with thermocouples. The graph clearly shows that the top of the TO3 responds much faster, and with a larger temperature change, though after the first two minutes the temperatures are all increasing at the same rate. The whole assembly took more than an hour to asymptote to thermal equilibrium.

### The CFP output

In the CFP configuration, the output devices are inside a local feedback loop, and play no significant part in setting  $I_q$ , which is affected only by thermal changes in the drivers'  $V_{be}$ . Such stages are virtually immune to thermal runaway; I have found that assailing the output devices with a powerful heat gun induces only insignificant  $I_q$  changes. Thermal compensation is mechanically simpler as the  $V_{be}$  multiplier transistor is simply mounted on one of the driver heatsinks, where it aspires to mimic the driver junction temperature. It is now practical to make the bias transistor of the same type as the drivers, which should give the best matching of  $V_{be}$ , though how important this is in practice I wouldn't like to say<sup>2</sup>.

Because driver heatsinks are much smaller than the main heatsink, the thermal compensation time constant is now measured in tens of seconds rather than tens of minutes, and should give much shorter periods of non optimal quiescent current than the EF output topology.

**Distortion 4:** nonlinear loading of the voltage amplifier stage by the nonlinear impedance of the output stage.

This distortion mechanism was examined in Part 3 from the point of view of the voltage amplifier stage. Essentially, since the VAS provides all the voltage gain, its collector impedance tends to be made high. This renders it vulnerable to nonlinear loading unless it is buffered.

Making a linear VAS is most easily done by applying a healthy amount of local negative feedback via the dominant pole Miller capacitor, and if VAS distortion needs further reduction, then the open loop gain of the VAS stage must be raised to increase this local feedback. The direct connection of a Class-B output can make this difficult for, if the gain increase is attempted by cascoding with intent to raise the impedance at the VAS collector, the output stage loading will render this almost

completely ineffective. The use of a VAS buffer eliminates this effect.

As explained previously, the collector impedance, while high at LF compared with other circuit nodes, falls with frequency as soon as  $C_{dom}$  starts to take effect, and so the fourth distortion mechanism is usually only visible at LF. It is also masked by the increase in output stage distortion above dominant pole frequency  $P1$  as the amount of global NFB reduces.

The fall in VAS impedance with frequency is demonstrated in Fig. 3, obtained from the Spice conceptual model outlined previously, with real life values. The LF impedance is basically that of the VAS collector resistance, but halves with each octave once  $P1$  is reached. By 3kHz it is down to  $1k\Omega$  and still falling. Nevertheless, it can remain high enough for the input impedance of a Class-B output stage to significantly degrade linearity, the actual effect being shown in Fig. 4.

An alternative to cascoding for VAS linearisation is to add an emitter follower within the VAS local feedback loop, increasing the local NFB factor by raising effective beta rather than the collector impedance. Preliminary tests show that as well as providing good VAS linearity, it establishes a lower VAS collector impedance across the audio band. It should be more resistant to this type of distortion than the cascode version.

Figure 5 confirms that the input impedance of a conventional EF Type I output stage is anything but linear; the data is derived from a Spice output stage simulation with optimal  $I_q$ . Even with an undemanding  $8\Omega$  load, the impedance varies by 10:1 over the output voltage swing. Interestingly, the Type II EF output (using a shared drive emitter resistance) has a 50% higher impedance around crossover, but the variation ratio is rather greater. CFP output stages have a more complex variation that includes a precipitous drop to less than  $20k\Omega$  around the crossover point. With all types under biasing produces additional sharp impedance changes at crossover.

### Distortion 5: supply ground loops

Virtually all amplifiers include some form of rail decoupling apart from the main reservoir capacitors; this is usually required to improve HF stability. The standard decoupling arrangements include small to medium sized electrolytics (say 10 -  $1000\mu F$ ) connected between each rail and ground, and an inevitable consequence is that voltage variations on the rails cause current to flow into the ground connection chosen. This is just one mechanism that defines the power supply rejection ratio (PSRR) of an amplifier, but it is one that can do serious damage to linearity. If we assume a simple unregulated power supply, (and there are excellent reasons for using such a supply<sup>3</sup>) then these rails have a significant AC impedance and superimposed voltage will be due to amplifier load currents as well as 100Hz ripple. In Class-B, these supply rail currents are halfwave rectified sine pulses with strong harmonic content, and if they contam-

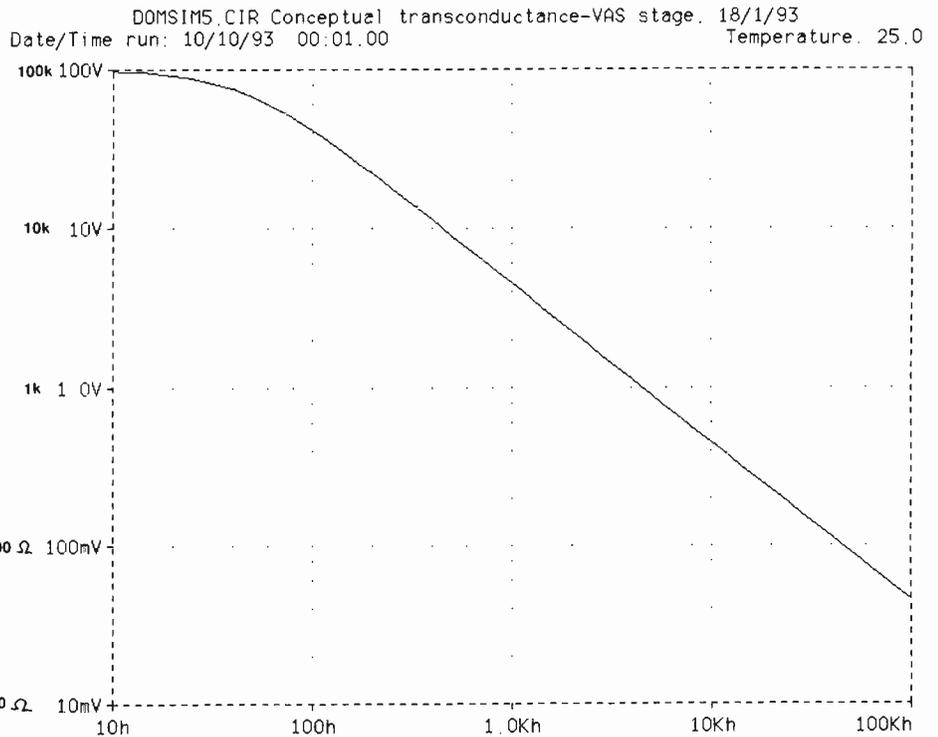


Fig. 3. Distortion 4. The impedance at the VAS collector falls at 6dB/octave with frequency.

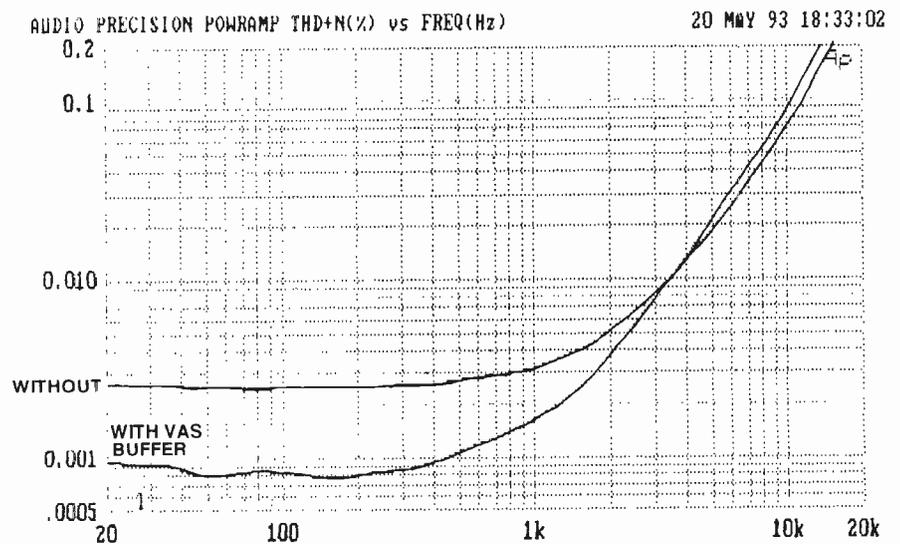


Fig. 4. Distortion 4 in action. The lower trace shows the result of its elimination by the use of a VAS buffer.

inate the signal, then distortion will degrade badly. A common route for interaction is via decoupling grounds shared with input or feedback networks, and a completely separate decoupler ground usually effects a total cure. This point is easy to overlook, and attempts to improve amplifier linearity by labouring on the input pair, VAS, etc., are doomed to failure unless this distortion mechanism is eliminated first.

As a rule it is simply necessary to take the decoupling ground separately back to the ground star point, as shown in Fig. 6. Note that the star point A is defined on a short spur from the heavy connection joining the reservoirs; trying to use B as the star point will

introduce ripple due to the large reservoir charging current pulses passing through it.

Figure 7 shows the effect on an otherwise optimised amplifier delivering 60W/8Ω, with 220μF rail decoupling capacitors. At 1kHz distortion has increased by more than ten times, which is quite bad enough. However, at 20Hz the THD has increased at least 100 fold, turning a very good amplifier into a profoundly mediocre one with a single misconceived connection.

If the residual on the supply rails is examined, the ripple amplitude will usually be found to exceed the pulses due to Class-B signal current, and so some of the "distortion" on the upper curve of the plot is actually due to

OUTEF2C CIR: EF O/P, MPSA42/92, MJ802/4502, 18/6/93  
 Date/Time run: 10/19/93 20:47:31 Temperature: 25.0

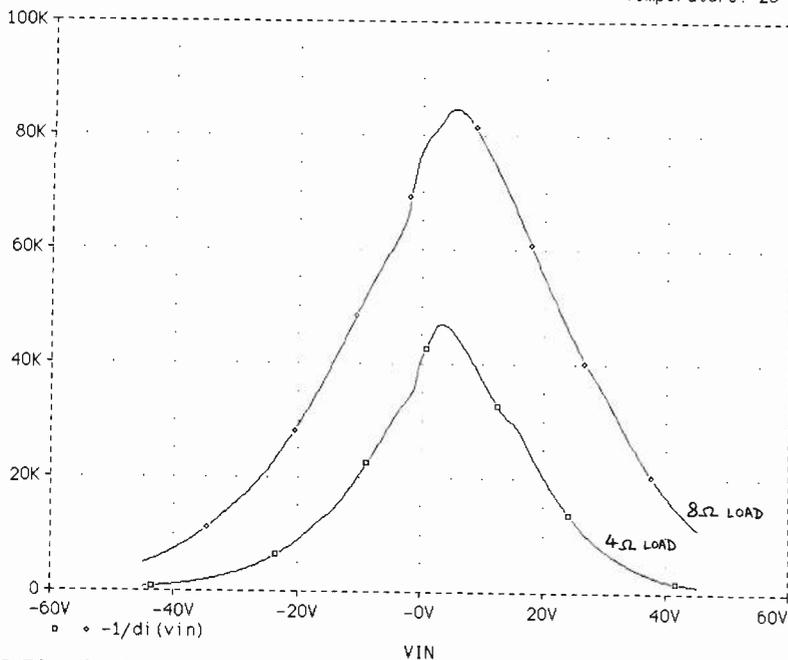


Fig. 5: Distortion 4 and its root cause. The nonlinear input impedance of an EF Class B output stage.

AUDIO PRECISION POWRAMP THD+N(%) vs FREQ(Hz) 20 MAY 93 19:09:10

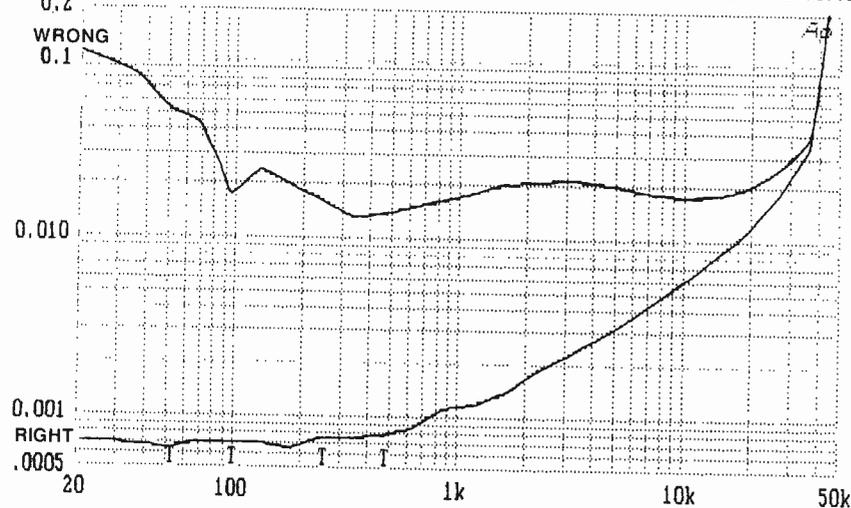


Fig. 7: Distortion 5 in action. The upper trace was produced simply by taking the decoupler ground from the star point and connecting it via the input ground line instead.

AUDIO PRECISION POWRAMP THD+N(%) vs FREQ(Hz) 15 APR 93 19:29:51

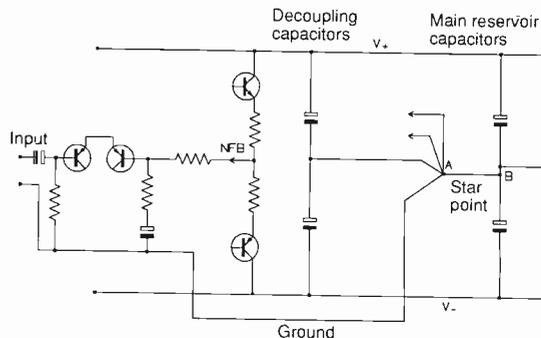
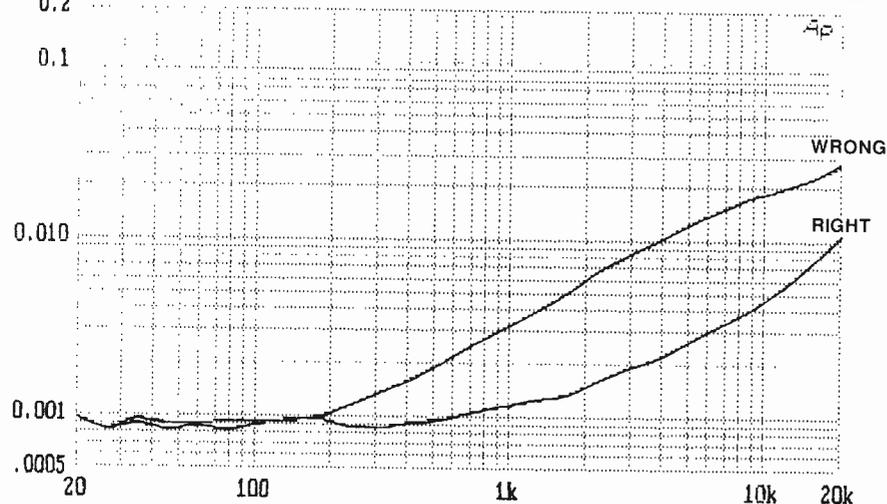


Fig. 6. Distortion 5. The correct way to route decouple grounding to the star point.

ripple injection. This is hinted at by the phase crevasse at 100Hz, where ripple partly cancelled the signal at the instant of measurement. Below 100Hz the curve rises as greater demands are made on the reservoirs, the signal voltage on the rails increases, and so more distorted current is forced into the ground system.

Generally, if an amplifier is made free from ripple injection under drive conditions, shown by a THD residual without ripple components, there will be no distortion from the supply rails and the complications and inefficiency of high current rail regulators are unnecessary.

There has been much discussion of PSRR induced distortion in *EW+WW* recently, led by Ben Duncan<sup>4</sup> and Greg Ball<sup>5</sup>. I part company with Ben Duncan on this issue where he assumes that a power amplifier is likely to have 25dB PSRR, making expensive high power DC regulators the only answer. He agrees that this sort of PSRR is highly unlikely with the relatively conventional amplifier topologies I have been considering<sup>6</sup>.

Greg Ball also initially assumes that a power amp has the same PSRR characteristics as an op-amp, ie falling steadily at 6dB/octave. There is absolutely no need for this to be so, given a little RC decoupling, and Ball states at the end of his article that "a more elegant solution... is to depend on a high PSRR in the amplifier proper."

### Power supply rejection

For low noise and distortion, all the obvious methods of rail injection must be attended to as a matter of routine. I therefore give here some guidelines that I have found effective with unregulated supplies:

- The input pair must have a tail current source. A tail made of two resistors decoupled mid way is simply not adequate.
- This tail source will probably be biased by a pair of diodes or a led fed from a resistor to ground. This resistor should be split and the midpoint decoupled with an electrolytic of about 10μF to the appropriate rail.
- If a cascode transistor is used in the VAS, then its base will need to be biased about 1.2V above whichever rail the VAS emitter sits on; if this is implemented with a pair of diodes then further decoupling seems unnecessary.
- Having taken care of the above, the PSRR will now be limited by injection from the neg-

Fig. 8. Distortion 6 exposed. The upper trace shows the effects of Class B rail induction into signal circuitry.

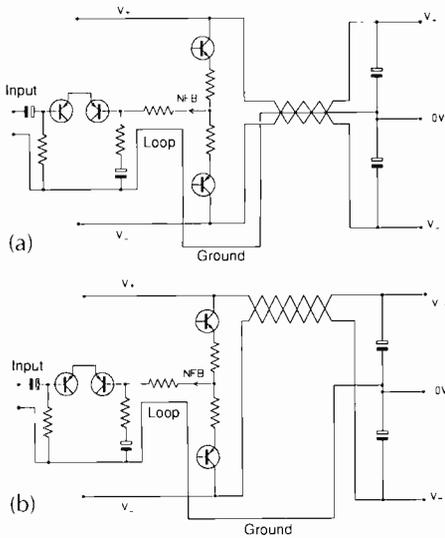


Fig. 9. Distortion 6. Countermeasures against the induction of distortion from the supply rails. 9b is usually more effective.

ative rail by a mechanism that is not yet fully clear. RC decoupling can however reduce this to negligible levels.

This is not the whole story on power rail rejection, but it does provide a starting point.

**Distortion 6: induced output current coupling**

This distortion mechanism, like the previous case, stems directly from the Class-B nature of the output stage. Assuming a sine input, the output hopefully carries a good sine wave, but the supply rail currents are halfwave rectified sine pulses, which are quite capable of inductive crosstalk into sensitive parts of the circuit. This can be very damaging to the distortion performance, as Fig. 8 shows.

The distortion signal may intrude into the input circuitry, the feedback path, or even the cables to the output terminals. The result is a kind of sawtooth on the distortion residual that is very distinctive, an extra distortion component which rises at 6dB/octave with frequency.

This effect appears to have been first publicised by Cherry<sup>7</sup>, in a paper that deserves much more attention than it appears to have got. Having examined many power amplifiers, I feel that this effect is probably the most widespread cause of unnecessary distortion.

Effects of this distortion mechanism can be reduced below the measurement threshold by taking care over supply rail cabling layout relative to signal leads, and avoiding loops that will induce or pick up magnetic fields. There are no precise rules for layout that would guarantee freedom from rail induction since each amplifier has its own physical layout and the cabling topology needs to take this into account. All I can do is give guidelines:

- Firstly, implement rigorous minimisation of loop area in the input and feedback circuitry: keep each signal line as close to its ground return as possible.
- Secondly, minimise the ability of the supply wiring to create magnetic fields.
- Thirdly, put as much distance between these two areas as you can. Fresh air beats shielding

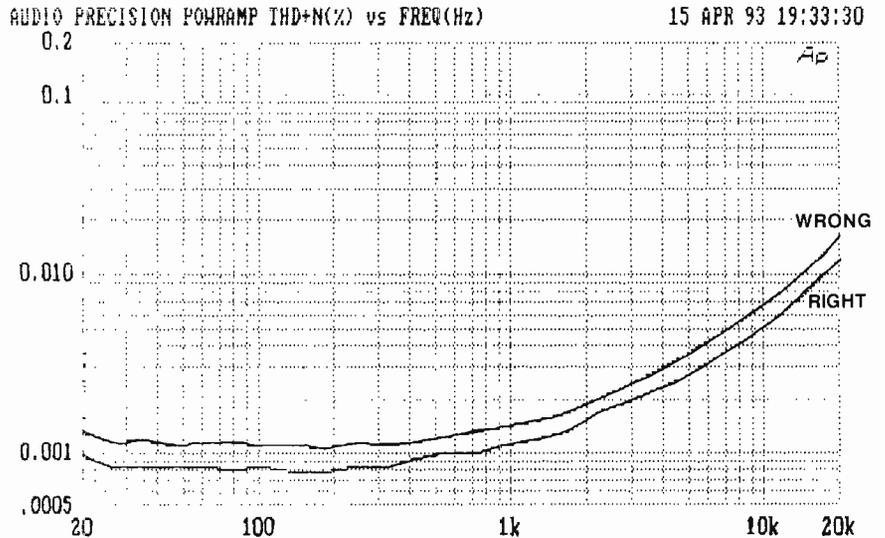


Fig. 11. Distortion 7 at work. The upper trace shows the result of a mere 6mm of heavy gauge wire between the output and the feedback point.

on price every time. Fig. 9a shows one straightforward approach to tackling the problem; the supply and ground wires are tightly twisted together to reduce radiation. In practice this doesn't seem too effective for reasons that are not wholly clear, but appear to involve the difficulty of ensuring exactly equal coupling between three twisted conductors.

In Fig 9b, the supply rails are twisted together but kept well away from the ground return. This allows field generation, but if currents in the two rails butt together to make a sine wave at the output, they should do the same when the magnetic fields from each rail sum. There is an obvious risk of interchannel crosstalk with this approach in a stereo amplifier, but it does seem to deal most effectively with the induced distortion problem.

**Distortion 7: nonlinearity from incorrect NFB connection point**

Negative feedback is a powerful technique and must be used with care. Designers are repeatedly told that too much feedback can affect slew rate. Possibly true, though the greater danger is that an excess amplifier may produce tweeter frying HF instability.

However, there is another and more subtle danger. Class-B output stages are a hotbed of high amplitude halfwave rectified currents, and if the feedback takeoff point is even slightly asymmetric, these will contaminate the feedback signal making it an inaccurate representation of the output voltage. This will manifest itself as distortion, Fig. 10.

At the current levels in question, all wires and PCB tracks must be treated as resistances, and it follows that point C is not at the same potential as point D whenever  $TR_1$  conducts. If feedback is taken from D, then a clean signal will be established here, but the signal at output point C will have a half wave rectified sine wave added to it, due to the resistance C-D. The output will be distorted but the feedback loop will do nothing about it as it does not know about the error.

Figure 11 shows the practical result for an

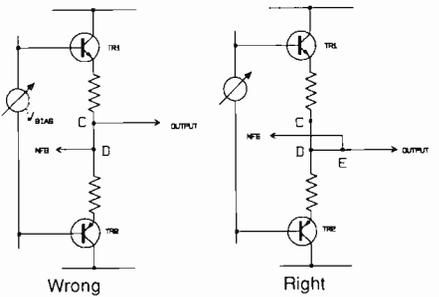


Fig. 10. Distortion 7. Wrong and right ways of arranging the critical negative feedback takeoff point.

amplifier driving 100W into 8Ω, with the extra distortion shadowing the original curve as it rises with frequency. Resistive path C-D that did the damage was a mere 6mm length of heavy gauge wirewound resistor lead.

Elimination of this distortion is easy, once you know the danger. Connecting the feedback arm to D is not advisable as it will not be a mathematical point, but will have a physical extent inside which the current distribution is unknown. Point E on the output line is much better, as the half wave currents do not flow through this arm of the circuit.

Next month: an example of a complete amplifier designed according to the principles in this series.

**References**

1. Sato Amplifier Transient Crossover Distortion. AES Preprint for 72nd Convention, Oct 1982.
2. Evans, J Audio Amplifier Bias Current Letters, *Electronics + Wireless World*, Jan 1991, p53.
3. Self, D Sound mosfet design *Electronics + Wireless World*, Sept 1990, p760.
4. Duncan, B PSU regulation boosts audio performance, *Electronics + Wireless World*, Oct 92, p818.
5. Ball, G Distorting power supplies *Electronics + Wireless World*, Dec 1990, p1084.
6. Duncan, B, Private communication, Oct 93.
7. Cherry A New Distortion Mechanism in Class-B Amplifiers, *JAES* May 1981, p327.

# LETTERS

## Making ripples

I was very interested to see AM Wilkes' article "Simulating capacitor ripple" (*EW + WW*, September 1993), since I have analysed the behaviour of this circuit.

Wilkes' program makes the same assumption as most textbooks, that the transformer acts as a perfect voltage source, whose output voltage is not affected by the current drawn from it. One consequence of this assumption is that the peak voltage on the capacitor will always equal the  $V_{pk}$  of the supply.

In reality, the output voltage is subject to Ohm's Law due to the finite resistance of the secondary and primary windings. When the rectifier diodes are conducting, the transformer sees the capacitor effectively as a short circuit, and its own resistance is the predominant factor in limiting the charging current.

The effective voltage in the circuit equals the difference between the instantaneous induced voltage in the secondary and the voltage on the capacitor.

An immediate effect of this is to reduce the ripple voltage, since the peak voltage on the capacitor is reduced.

For example, suppose the load is such that the average voltage on the

capacitor equals the rms of the transformer output. If the transformer was a perfect voltage source, the ripple voltage would necessarily be at least  $V_{pk} - V_{rms}$ . In reality, reasonable capacitor values can give a much smaller ripple voltage than this.

To give an example, I have just measured the dc resistance of the secondary of a nominal 10V, 1.2A transformer. It is about  $0.4\Omega$ .

Supposing the smoothing capacitor has 10V across it when the peak voltage of 14.1V occurs, then a charging current of 10.3A will be flowing (ignoring diode drops), and the voltage seen by the capacitor will be 10V, with  $dV/dt$  depending on the capacitor value.

This analysis is simplified since it ignores other current-limiting factors, such as the dc resistance of the transformer primary and the current drawn by the load.

**John Harper**  
*Valbonne, France*

## Lightning response

I found the report of a link between lightning and cosmic radiation (Research Notes, *EW + WW*, November 1993) established by Moscow and Los Alamos researchers rather exciting because it suggests the conditions close to

terrestrial power lines may also enhance sky radiation and help explain the observations I reported in a previous article (*EW + WW*, November 1992).

Since the article appeared, a single joint test with the NRPB in mid 1993 on a 400kV line carrying 800A per phase showed a raw count increase of about 4% close to the line, which was not regarded as significant because it could have been due to local geology.

More recently, tests by the Swedish Radiation Research Institute using more sophisticated equipment produced rate curves rather resembling the plots in Fig. 2 of the November 1992 article.

The problem is that relevant solar particle emission has fallen by about 70% since my original field work in 1990 and 1991, close to the peak of solar cycle 22, so exact replication of my original observations will have to wait for the peak of cycle 23 in about five years. In the meantime, research into the theoretical and practical implication of my observations may help to explain the growing body of epidemiological evidence that people living close to power lines may suffer some ill effects.

Research should also concentrate on detecting an 11 year cycle for human disease. Such a cycle would suggest that solar ionising radiation at levels well below those considered hazardous leads to power line focusing of natural radiation that may pose real dangers for those with a genetic susceptibility.

**Anthony Hopwood**  
*Upton-on-Severn, Worcester*

## Valve mystery

Older readers of your magazine will remember with nostalgia valves manufactured with trade names such as Cossor, Ferranti, Mullard, Marconi, Mazda, Osram and Tungram.

There were also many lesser known companies who made or distributed valves during the 1920s and 1930s. Among these were Hivac, Lissen, Octron and 363.

I would be pleased to hear from readers who have any knowledge of these companies' valve manufacturing or distributing activities, particularly Lissen whose valve making is clouded in mystery.

**Keith Thrower**  
*Old Cedar, 12 Wychcotes  
Caversham, Reading RG4 7DA*

## Sad subjectivism

I was interested to read Jerry Mead's defence of subjectivist listening tests (*EW + WW*, November 1993) but

sad to see that his procedures apparently have no chance of deciding whether one amplifier is better than another.

The trouble is that his manifesto nowhere mentions double-blind A/B testing, or indeed any kind of A/B comparison at all. As far as I can discover, he simply listens to one amplifier, relying on his claimed ability to retain mental performance maps for several days between amplifier versions.

Such a procedure would be absolutely unacceptable even in a first-year psychology project, as decades of experience in psychoacoustics and related fields have shown beyond any possible quibble that experimenter expectancy renders the results valueless.

The fact that no audible differences are likely to exist unless the circuitry is seriously misconceived sets the final seal of sterility on the whole proceedings.

It is a well-worn debating technique to call for an open-mind when discussing these matters, though I can see no hint that Mead has considered the possibility that he might himself be wrong or misled.

Surely, to sail into an allegedly scientific investigation with an open-mind as to whether or not to measure things properly is not a triumph for tolerance, but a complete misunderstanding of what constitutes the scientific method.

Taking this philosophy to its logical conclusions debars us from any progress, as it becomes impossible to determine between truth and falsity.

Mead is absolutely correct when he says the mere fact that something cannot be measured or quantified does not mean it doesn't exist. However, if after 20 years of talking about it you still can't measure, or even demonstrate what you claim to be studying, most of us would regard this as a rather suspicious circumstance.

He also appears to overlook the two classic proofs that mysterious subjective nuances have no existence – the Hafler<sup>1</sup> and Baxandall<sup>2</sup> demonstrations. I have yet to meet a subjectivist who was able to argue his way past either of them.

Since no equally positive demonstration of the non-existence of ufos has been made one could argue that subjectivism is actually in rather worse shape than ufology.

I was glad to see the Mead-Duncan team take level matching seriously – until on a closer look I saw that it was just channel balance that was being so effectively policed.

Level matching between the A and

## Complex cables defy physics

The behaviour of an audio signal in a cable is far more complex than a simple first year text book explanation of Ohm's Law, which Drs Blake-Coleman and Yorke assume (*EW + WW*, May 1993).

The flow of ac electricity in a conductor is not uniform over the cross sectional area. Also the metal on the surface of a conductor is likely to be different from that at the centre due to oxidation. An oxidised metal is more likely to have semiconducting properties than the same conduction properties of the metal at the centre of the conductor.

There is no perfect insulator and insulating materials exhibit power loss and dielectric absorption, which can be easily measured.

The most significant influence on sound quality is the conductor used. Although copper is the most common metal used, other metals offer better sound, in particular silver. Silver plated copper offers a high quality performance where pure silver is too expensive.

Insulation will affect sound quality due to dielectric absorption. PTFE not only has the best sound quality as an insulator, but also the lowest measured dielectric absorption of common insulating materials. A PTFE insulated cable will give a more focused sound, like a pair of binoculars adjusted to give a sharper visual focus.

Conductor size affects sound quality. Even on high impedance connections between preamp and power amp, increasing the cross sectional area of conductor increases bass frequencies. Also some large diameter solid core cables attenuate treble frequencies.

Other factors claimed to influence sound quality include heat treatment, larger crystal size and purity of metal. Cables also sound better when the screen is removed, or when a shorter length of the same cable is used.

The engineering of a cable to reproduce music in the form of rapidly changing dynamically variable electrical voltage is a complex art that needs the scientific application of knowledge and skill to achieve success.

**Graham Nalty Derby**

*Mr Nalty should have declared an interest – he sells exotic audio cables. Editor*

the B of an A/B comparison has long been known to be critical – the oldest trick in the book is to make amplifier A sound repeatedly better by making it 1dB or so louder – the listener usually perceiving this as an improvement in clarity rather than amplitude. Of course, if you don't do A/B comparisons then this trick is harder to pull.

I refuse to believe in the existence of a sea-sickness capacitor until further proof is forthcoming. I simply can't believe that a capacitor in any position in an audio amplifier could induce anything resembling motion sickness.

How about showing us the circuit so we can judge for ourselves? The only audio-related uneasiness I usually experience is that which wells up when for the umpteenth time I am told: "I have evidence that backs up my views, but I am going to keep it secret."

I note Mead is curious about the mechanisms of hearing. Fortunately, there exists a huge body of knowledge on the subject of psychoacoustics and psychophysiology, though no-one would claim the subject is either an easy read or fully understood; after all, at the higher levels of processing it is the human brain doing the work,

and understanding that may well be the ultimate challenge that faces us.

What is known in considerable detail is the low-level functioning of the ear, with particular reference to what is perceptible and what is not. It really is not on to claim that perceived amplifier performance is shrouded in mystery.

**Douglas Self**  
Forest Gate, London

1. D Hafler, "A listening test for amplifier distortion", *HiFi News & RR*, Nov 1986.
2. P Baxandall, "Audible amplifier distortion is not a mystery", *Wireless World*, Nov 1977.

## Doctor WHO

Douglas Self (Letters, *EW + WW*, October) should search a little wider before he condemns earlier writers on adverse and beneficial effects of exposure to elf, rf and microwave fields.

The World Health Organisation has just published in its environmental health series, "Electromagnetic fields 300Hz - 300GHz". It details hundreds of references from scientific, medical and physics authors on the effects on humans, animals and cel. lines in

*vivo* and *in vitro*.

He should also pause to muse that the WHO published in 1989 a text called "Non-ionising radiation protection". This is divided into sections on rf, ir, uv, sonic, elf and so on.

Is it likely that it would publish these books unless there are perceived hazards soundly based in research? Fracture and ulcer healing studies are reported from many sources worldwide. Indeed, St. Thomas' and Bart's hospitals are working on these lines.

It is especially interesting that many studies indicate that there are windows of frequency and amplitude which can, and do, affect immunocompetence (via free radical mechanisms at cellular level), bone healing, wound healing and subclinical electrosyndromes.

As a very wise military signals officer told me "all radiation is radiation". Too much uv from the sun can trigger malignant melanoma, too much ir from furnaces can lead to glass blowers cataract (unless protective measures are taken), and too much exposure to microwaves (WHO 1993) can trigger thermal and athermal effects, including brain damage of varying degree.

Dr Allen in *Journal of Radiological Protection* 1991 describes reactive near fields, which he says "can affect people and objects", as against radiating near and far fields.

In June the International Bioelectromagnetics Society met in the USA. There were 700 attendees with 486 papers and posters; 250 were from the US, 50 from China, 20 from most European countries, nine from Yugoslavia and seven from the UK. In November Eure held a conference in Bad Neuheim called "Biological effects of magnetic fields", (Verband Deutscher Elektrotechniker). *Radio Electronics* in the US in September 1960 carried a six page article on the effects of rf energy on the body and detailed many experiments carried out on healing, production of aggression, hallucinations and so on.


Lastly, Elizabeth Davies' paper "The healing face of electromagnetic fields" (*EW + WW*, April 1993) calls for "research into the signal/tissue response. A timely invitation as the WHO calls for urgent multidisciplinary epidemiological research into the effects of fields on the human body."  
**Anne C Arnold Silk**  
Great Missenden, Bucks

Finally an upgradeable PCB CAD system to suit any budget...

# Board Capture
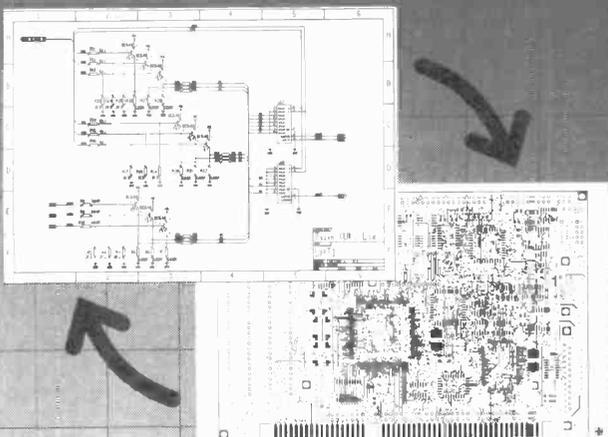
## BoardCapture - Schematic Capture

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2



# Board Maker

## BoardMaker1 - Entry level

- PCB and schematic drawing
- Easy and intuitive to use
- Surface mount support
- 90, 45 and curved inner corners
- Ground plane fill
- Copper highlight and clearance checking

## BoardMaker2 - Advanced level

- All the features of BoardMaker1 plus
- Full netlist support - OrCAD, Schema, Tango, CadStar
- Full Design Rule Checking - mechanical & electrical
- Top down modification from the schematic
- Component resymbol with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRC

# Board Router

## BoardRouter - Gridless autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

## Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Plotters - HP, Graphtec, Roland & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill / Annotated drill drawings (BM2)

Call for info or full evaluation kit  
Tsien (UK) Limited  
Tel (0354) 695959  
Fax (0354) 695957



**tsien**

Tsien (UK) Ltd, Aylesbury House, Wenny Road, Chatteris, Cambridge CB16 8UT

CIRCLE NO. 114 ON REPLY CARD


Surplus always wanted for cash!

# THE ORIGINAL SURPLUS WONDERLAND!

Surplus always wanted for cash!

## LOW COST PC SPECIALISTS - ALL EXPANDABLE - ALL PC COMPATIBLE

### 8088 XT - PC99

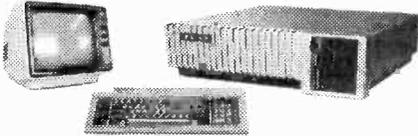

- 256k RAM - expandable to 640k
- 4.7 Mhz speed
- 360k 5-1/4" floppy
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Factory burnt-in
- Standard 84 key keyboard
- 12" green screen included
- In good used condition

Optional FITTED extras: 640K RAM £39. 12" CGA colour monitor with card £39. 2nd 5-1/4" 360K floppy £29.95. 20 mbyte MFM hard drive £99.

Only **£99.00** (F)

### FLOPPY DISK DRIVES

5 1/4" from £22.95 - 3 1/2" from £21.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported).

- 3.5" Panasonic JU363/4 720K or equivalent £29.95(B)
- 3.5" Mitsubishi MF355C-L. 1.4 Meg. Laptops only £29.95(B)
- 3.5" Mitsubishi MF355C-D. 1.4 Meg. Non laptop £29.95(B)
- 5.25" EXTRA SPECIAL BRAND NEW Mitsubishi MF501B 360K. Absolutely standard fits most computers £22.95(B)

\* Data cable included in price.

- Shugart 800/801 SS refurbished & tested £175.00(E)
- Shugart 851 double sided refurbished & tested £275.00(E)
- Mitsubishi M2894-63 double sided switchable hard or soft sectors - BRAND NEW £250.00(E)

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! £499.00(F)

End of line purchase scoop! Brand new NEC D2246 8" 85 megabyte of hard disk storage! Full CPU control and industry standard SMD interface. Ultra high speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only £299(E)

### THE AMAZING TELEBOX!

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television or video channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Composite and RGB video outputs are located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

- Telebox ST for composite video input monitors £32.95
  - Telebox STL as ST but with integral speaker £36.50
  - Telebox MB as ST with Multiband tuner VHF-UHF-Cable. & hyperband For overseas PAL versions state 5.5 or 6mhz sound specification. £69.95
  - Telebox RGB for analogue RGB monitors (15khz) £69.95
- Shipping code on all Teleboxes is (B)
- RGB Telebox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM/NTSC not available.

### No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from Densel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AHBD is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals.....MUK.....£249 (F) MUD.....£525 (G)

### 286 AT - PC286



- 640k RAM expandable with standard SIMMS
- 12 Mhz Landmark speed
- 20 meg hard disk
- 12 meg 5-1/4" floppy
- 1.4 meg 3-1/2" floppy
- EGA driver on board
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Co-processor socket
- Enhanced 102 key keyboard
- Clock & calendar with battery back up

BRAND NEW AND BOXED!

Only **£249.00** (F)

The Philips 9CM073 is suggested for the PC286 and the CM8873 for the PC386. Either may use the SVGA MTS-960C if a suitable card is installed. We can fit this at a cost of £49.00 for the PC286 and £39.00 for the PC386.

### POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, -5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. £85.00 (B)

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24 v (2A). 5v @ 20A. ± 12v @ 1.5A. Switch mode. New. £59.95(B)

Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a. +12v @ 2a. -12v @ 0.1a. 6-1/4" x 4" x 1-3/4". New £22.95(B)

Greendale 19AB0E 60 watts switch mode. +5v @ 6a. ± 12v @ 1a. +15v @ 1a. RFE and fully tested. 11 x 20 x 5.5cms. £24.95(C)

Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a. -5v @ 1a. ± 12v @ 6a. 27 x 12.5 x 6.5cms. New. £49.95(C)

Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a. +12v @ 2.5a. -12v @ 0.5a. -5v @ 0.5a. £29.95(B)

Farnell G6/40A. Switch mode. 5v @ 40a. Encased £95.00(C)

Farnell G24/5S. As above but 24v @ 5a. £65.00(C)

### BBC Model B APM Board

WIN £100 CASH!

£100 CASH FOR THE MOST NOVEL DEMONSTRATABLE APPLICATION!

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board! It is supplied complete with a connector panel which brings all the I/O to 'D' and BNC type connectors - all you have to do is provide +5 and ± 12 v DC. The APM consists of a single PCB with most major ic's socketed. The ic's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27129 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10". I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only **£29.95** or **2 for £53** (B)

### SPECIAL INTEREST

- Trio 0-18 vdc bench PSU. 30 amps. New £ 470
- Fujitsu M3041 600 LPM band printer £2950
- DEC LS/02 CPU board £ 150
- Rhode & Schwarz SBUF TV test transmitter 25-1000mhz. Complete with SBTF2 Modulator £6500
- Calcomp 1036 large drum 3 pen plotter £ 650
- Thurlby LA 160B logic analyser £ 375
- 1.5kw 115v 60hz power source £ 950
- Anton Pillar 400 Hz 3 phase frequency converter 75Kw POA
- Newton Derby 400 Hz 70 Kw converter POA
- Nikon PL-2 Projection lens meter/scope £750
- Sekonic SD 150H 18 channel Hybrid recorder £2003
- HP 7580A A1 8 pen high speed drum plotter £1853
- Kenwood DA-3501 CD tester, laser pickup simulator £ 353

### BRAND NEW PRINTERS

- Microline 183. NLQ 17x17 dot matrix. Full width. £139 (C)
- Hyundai HDP-920. NLQ 24x18 dot matrix full width. £149 (C)
- Qume LetterPro 20 daisy. Qume QS-3 interface. £39.95 (D)
- Centronics 152-2 9 x 7 dot matrix. Full width. £149 (C)
- Centronics 159-4 9 x 7 dot matrix. Serial. 9-1/2" width £ 99 (C)

### 386 AT - PC386



- 2 meg RAM expanded by slots
- 20 Mhz with 32k cache. Expandable to 64k
- 40 meg hard disk
- 1.2 meg 5-1/4" floppy
- VGA card installed
- 2 serial & 1 parallel ports
- MS-DOS 4.01
- Co-processor socket
- Enhanced 102 keyboard
- Kwik Disk Accelerator Software - FREE

BRAND NEW AND BOXED!

Only **£425.00** (F)

### MONITORS

14" Forefront Model MTS-9600 SVGA multisync with resolution of 1024 x 768. 0.28 pitch. "Text" switch for word processing etc. Overscan switch included. Ideal for the PC-386 or PC-286 with SVGA card added. Also compatible with BBC, Amiga, Atari (including the monochrome high resolution mode), Archimedes etc. In good used condition (possible minor screen bums). 90 day guarantee. 15" x 14" x 12". Only £159(E)

14" Philips Model CM8873 VGA multisync with 640 x 480 resolution. CGA, EGA or VGA, digital/analog, switch selectable. Sound with volume control. There is also a special "Text" switch for word processing, spreadsheets and the like. Compatible with IBM PC's, Amiga, Atari (excluding the monochrome high resolution mode), BBC, Archimedes etc. Good used condition (possible minor screen bums) 90 day guarantee. 15" x 14" x 12". Only £139(E)

Philips 9CM073 similar (not identical) to above for EGA/CGA PC and compats. 640 x 350 resolution. With Text switch with amber or green screen selection. 14" x 12" x 13-1/2". £99(E)

KME 10" high definition colour monitors. Nice tight 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13.5" x 12" x 11". Also works as quality TV with our HiB Telebox. Good used condition. 90 days guarantee. Only £125 (E)

KME as above for PC EGA standard.....£145 (E)

Brand new Centronic 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 MHz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only £129 (E)

NEC CGA 12" IBM-PC compatible. High quality ex-equipment fully tested with a 90 day guarantee. In an attractive two tone ribbed grey plastic case measuring 15" L x 13" W x 12" H. The front cosmetic bezel has been removed for contractual reasons. Only £69 (E)

20", 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs. In EXCELLENT little used condition with full 90 day guarantee. 20"....£135 22"....£155 26"....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

Superb Quality 6 foot 40u

### 19" Rack Cabinets

Massive Reductions

Virtually New, Ultra Smart!

Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready

punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions are 77-1/2" H x 32-1/2" D x 22" W. Order as:

Rack 1 Complete with removable side panels.....£275.00 (G)

Rack 2 Less side panels.....£145.00 (G)

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

5000

DISPLAY

MAIL ORDER & OFFICES  
Open Mon-Fri 9.00-5.30  
Dept WW, 32 Biggin Way,  
Upper Norwood,  
London SE19 3XF.

LONDON SHOP  
Open Mon-Sat 9-5.30  
Thursday till 9.00pm  
215 Whitehorse Lane,  
South Norwood,  
London. SE25.

DISTEL © The Original  
Free dial-up database!  
1000's of items+info on line  
V21, V22 & V22 bis  
081-679-1888

ALL ENQUIRIES  
081-679-4414  
Fax- 081-679-1927



-ELECTRONICS-

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government Universities, Schools & Local Authorities welcome-minimum account order £30. Carriage charges (A)=£2.00. (A1)=£3.75. (B)=£5.50. (C)=£8.50. (D)=£11.50. (E)=£14.00 (F)=£18.00 (G)=Call. Scotland surcharge applies. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. Rights reserved to change prices & specifications without prior notice. Orders subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always wanted for cash.

CIRCLE NO. 115 ON REPLY CARD

# Working with programmable logic

## 3: generic and gate array logic

*The first two articles of this series considered methods of designing logic to fit into combinatorial and registered PLDs. In this final part, Geoff Bostock looks at generic logic and field programmable gate arrays*

A common element among standard logic PLDs is their fixed architecture. For example, a *PAL16R6* has eight fixed inputs, two bidirectional i/o pins and six registered outputs; a *PLS173* has twelve fixed inputs and ten i/o pins.

In the mid-1980s, Lattice Semiconductor unveiled a device whose architecture itself could be programmed. It was designed to be capable of emulating any of the standard combinatorial or registered pals and, as a further innovation, it was fabricated with cmos technology.

This device, the *GAL16V8* and its 24-pin counterpart the *GAL20V8*, featured a programmable macrocell whose design is shown in Fig. 1.

The basis of gals (generic array logic) is the introduction of programmable multiplexers into the output structure. The basic device features four multiplexers: for output enable, register by-pass, feedback and the eighth product term.

The output enable can be driven in four ways. It may be always enabled as in an output pin of a simple *10L8* family pal, or it may be always disabled as in an input pin from the same range. In *PAL16L8s* it is derived from a dedicated product term, while in registered pals there is a common enable from pin 11 (or pin 13 in the 24-pin family).

The 'eighth product term' is used as the output enable in the *PAL16L8*, but as a pure logic term in all other pals.

Register by-pass allows both combinatorial and registered outputs to be derived from the same output macrocell. The feedback multiplexer has four possible signal sources. It must come from the output flip-flop in registered pals, from the output pin in bidirectional i/os and be disabled in fixed outputs.

The fourth source is an adjacent output pin.

In the *PAL16L8*, pins 12 and 19 are fixed outputs while pins 13 to 18 are i/o; in the *PAL12L6* family (apart from *10L8* and *10H8*) pins 12 and 19 are fixed inputs, and the middle pins may be either fixed input or output according to the device type. Also, pin 1 is the clock input in registered pals but a logic input in combinatorial pals.

The feedback from the top macrocell to the and-array must come from pin 1 in a combinatorial pal but from pin 19 in a *PAL16R6* or *PAL16R4* (where it is an i/o pin).

Likewise, the feedback from the second macrocell

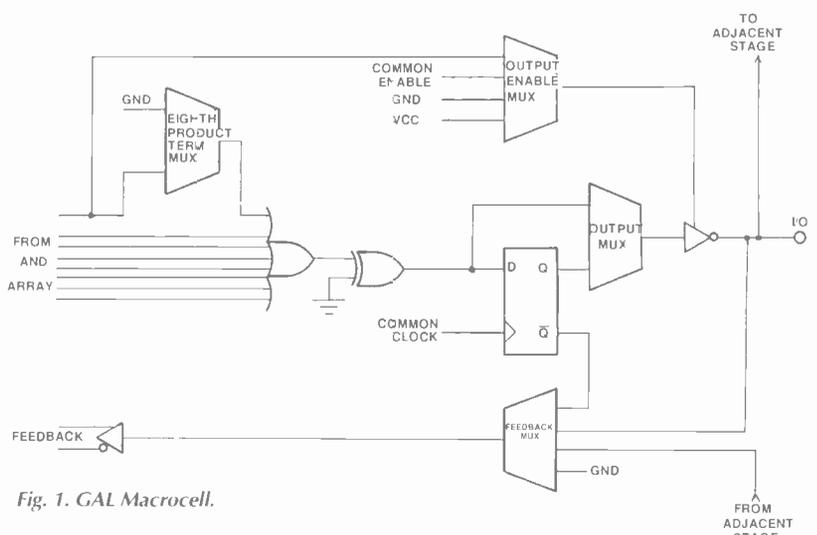
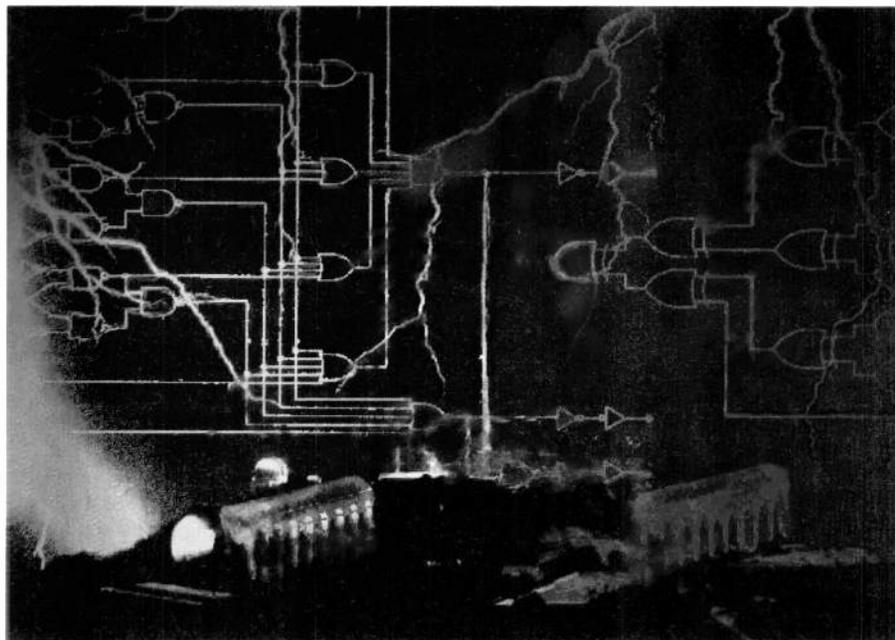


Fig. 1. GAL Macrocell.

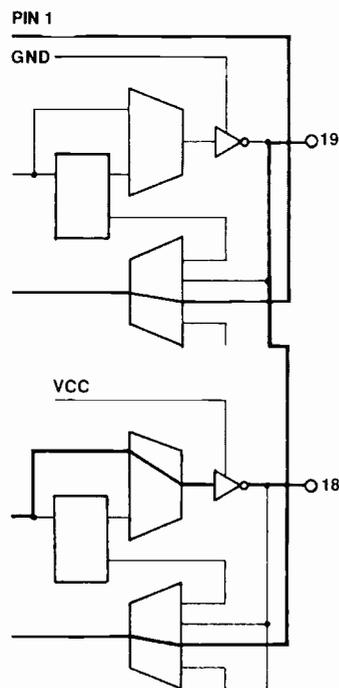


Fig. 2a. GAL16V8 top two macrocells in PAL12L6 configuration.

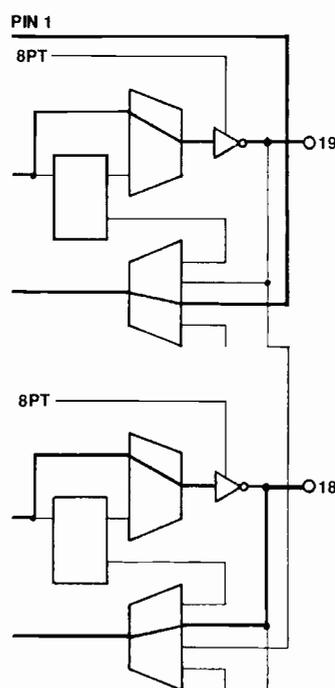


Fig. 2b. GAL16V8 top two macrocells in PAL16L8 configuration.

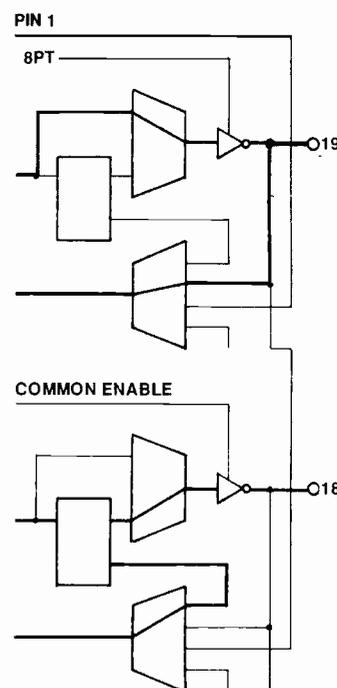


Fig. 2c. GAL16V8 top two macrocells in PAL16R6 configuration.

Complex PLDs, of which gals are an early example, rely on multiplexers to provide output function programmability. Gals, in particular, are able to emulate nearly all of the standard pals by routing the output, feedback and enable signals through the output macrocell.

In the PAL12L6 emulation, the 'adjacent stage' lines route the pin 1 input to the pin 19 feedback multiplexer, and pin 19 to pin 18 feedback; pin 18 becomes a direct output.

The PAL16L8 also routes pin 1 to pin 19 feedback but pin 19 is also a direct output with no feedback. Pin 18 is an output with feedback. Both pins use the output multiplexer register by-

pass path and the 'eighth product term' in the enable multiplexer.

PAL16R6s have a mixture of combinatorial and registered outputs. Pin 19 is combinatorial so the register by-pass output, direct pin feedback and 'eighth product term' enable are selected. The registered pins, such as pin 18, use registered output, feedback from the flip-flop and common enable.

Fortunately, in practice these selections are performed automatically by the software built into most programmers, which set the correct bits for the macrocell multiplexers. Gal design software will also set the select bits if architectures which do not correspond to standard Pals are chosen.

comes from pin 18 in a PAL16L8 or PAL16R4, but pin 19 in any other combinatorial pal in which pin 19 is an input.

The feedback and output multiplexing for the top two macrocells is shown in Fig. 2 for emulations of pals 12L6, 16L8 and 16R6.

The other feature of the gal macrocell is the programmable polarity output. This makes it possible to emulate active-high as well as active-low pals.

Although gals can emulate nearly all standard pals, their architectural possibilities are not limited to these alone. For example, it is possible to use a gal as a pal with three registered and five combinatorial outputs, and to mix these as active-high and active-low, as desired.

There are a few restrictions though; for example, pins 12 and 19 cannot be used as inputs in some modes because of the way in which the multiplexer program cells set the feedback multiplexer.

We have not described the operation of the multiplexer program cells because this is all taken care of by the device programmer or the design software. Device programmers which can program gals have the emulations built into them so that the correct architecture fuses are set when the pal being emulated is selected. Assemblers for gals also set the appropriate bits for the chosen architecture even if this is not a pal emulation.

While Lattice were bringing out the GAL16V8 and GAL20V8, AMD introduced the PAL22V10. This device

also features output macrocells which can be set as combinatorial i/o or registered outputs, although their design differs slightly from the Lattice circuit. This is because the 22V10 is not aimed at replacing standard pals, although it can emulate the PAL20L10 family, but it is a more complex device altogether.

The most powerful feature of the 22V10 is the variable number of and-terms in the and-array. As Fig. 3 shows, the lowest number of and-terms in any output is eight (pins 14 and 23) and increases to sixteen for pins 18 and 19. This goes some way to overcoming the transition term restrictions which can be found when trying to use pals for state machines.

There is also a separate and-term for the output enable in each output pin. Separate and-terms are also provided for synchronous preset and asynchronous reset across the whole device. These features are also helpful in state machines for setting the device to a known state for test or start-up.

### Low power logic

The gals were designed as cmos PLDs, and the PAL22V10 is also available in cmos from several manufacturers. Their data sheets indicate that they still consume tens of milliamps of supply current, about half as much as the equivalent bipolar PLDs which they may replace. While this is still a useful saving, it is not much help to designers

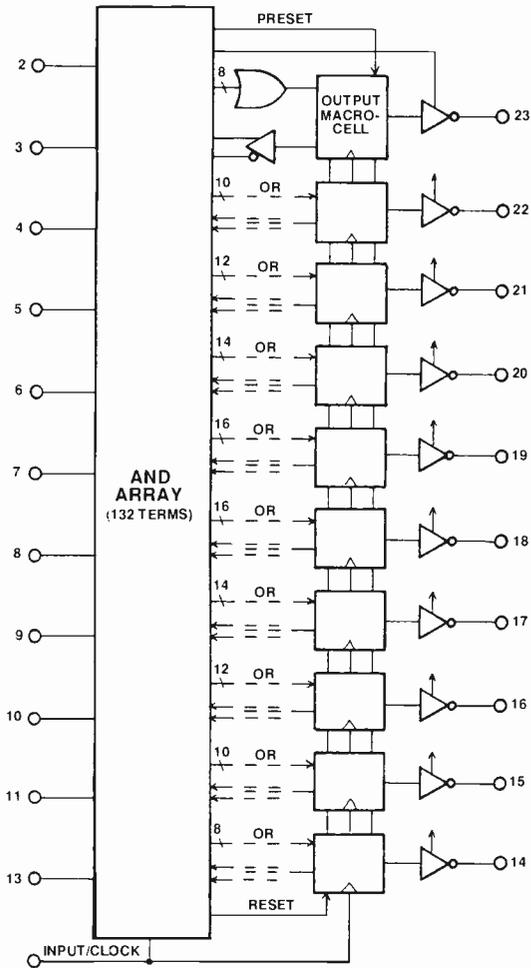


Fig. 3. Block diagram of PAL22V10.

of portable or battery-powered equipment.

The reason is to be found in the structure of the internal logic. A standard CMOS gate, as in Fig. 4, consists of a parallel transistor structure topped by a serial transistor structure, one half being p-channel the other n-channel. In this NOR gate, if all inputs are low the top conducts but none of the bottom n-channel transistors are turned on.

If an input goes high it switches off its p-channel transistor in the top half, thereby preventing conduction, but turns on its n-channel transistor, pulling the output low. The net result is that no direct current flows in the gate, only charging current when the output changes sense. A typical and-term in a PLD has 32 or more inputs, but it is not feasible to construct a CMOS gate with 32 transistors in series because of the threshold voltage of the individual transistors in the chain, and the voltage drop across the channel resistance when current is taken from the chain. Instead, each and-term has to be powered by a current source which is always supplying some current to the multiple input gate. The main power saving comes from building the peripheral components, such as input and output buffers and flip-flops from true CMOS.

Some PLDs are available with stand-by current of a few microamps. The way in which this is achieved is shown in Fig. 5. The logic arrays are powered via a switchable current source; while there is no activity at the inputs the current is switched off, so there is virtually no current taken by the device. The activity detector at the inputs switches the current source on for a sufficient time to allow the logic array to react to the new inputs.

The resulting output is latched at the device outputs so that it remains in place when the array current source

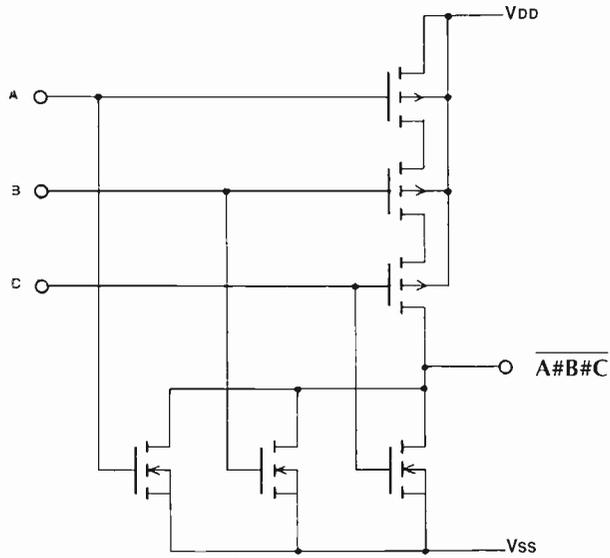


Fig. 4. Circuit diagram of CMOS NOR-gate.

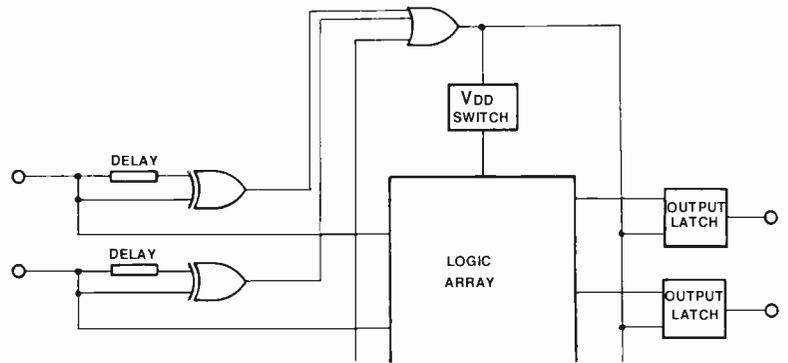


Fig. 5. CMOS PAL block diagram

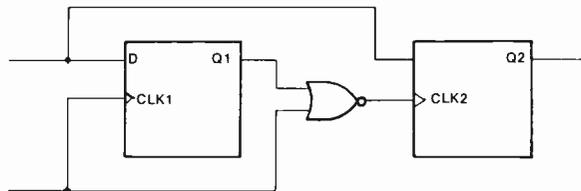


Fig. 6. Simple asynchronous circuit (detects relative position of data rising edge).

switches off again. Zero-power versions of many PLDs are now available such as the GAL16V8Z, GAL20V8Z, PAL22V10Z and PLC18V8Z, a more universal version of the GAL16V8Z.

**Asynchronous registered PLDs**

All the registered PLDs described so far have a single clock signal input. This ensures that all the flip-flops in the output register are clocked simultaneously, a necessary condition in a state machine.

There are many instances of simultaneous clocking being unnecessary or not possible. Examples are multiple state machines and random logic.

It is quite conceivable that two or more state machines can be fitted into a single PLD; the only restriction is that the total number of inputs and outputs does not exceed the resources available. It is not necessarily the case that each machine will use the same clock, although they often will. If they do not, the PLDs described so far will not be suitable.

There is no reason why random logic cannot involve flip-flops as well as combinatorial devices. One example

of a standard logic function which does not use simultaneous clocking is a ripple counter. In this case, the output from one flip-flop is the clock input for the next.

Figure 6 illustrates a simple random logic circuit involving flip-flops; it detects whether the rising edge of the data input occurs before or after the falling clock edge. The output could be used to synchronise the data with the clock, by feeding it back to a voltage controlled oscillator.

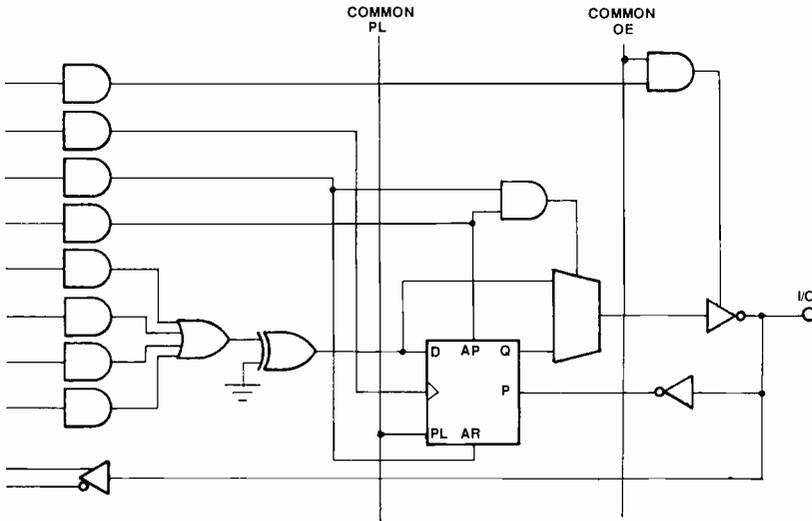


Fig. 7. Macrocell for asynchronous PAL20RA10.

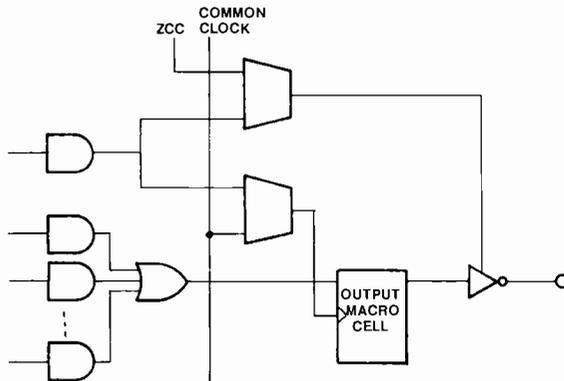


Fig. 8. General asynchronous macrocell.

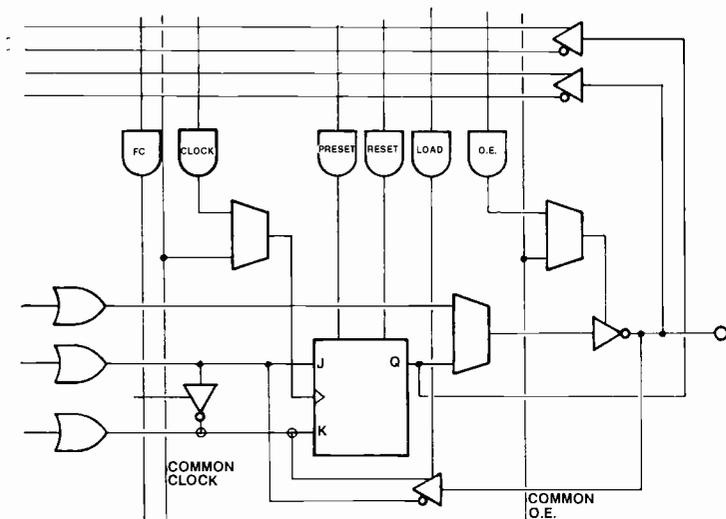


Fig. 9. PLC42VA12 macrocell

The equations for this circuit use the following format:

$$\begin{aligned} Q1 &:= D \\ Q1.CLK &= CLK1 \\ Q2 &:= D \\ Q2.CLK &= !Q1 \& !CLK1 \end{aligned}$$

the CLK extension denoting that this is the clock input to the flip-flop whose output is Q1 or Q2 respectively.

The PAL20RA10 is a common asynchronous pal; a macrocell from this pal is shown in Fig. 7. Each macrocell has eight and-terms, four of these are logic terms, the other four drive the output enable, clock, set and reset. The clock input can be any logical combination of the input and output signals, provided that it can be described in a single and-term. In the above example, the clock input is drawn as  $!(Q1 + CLK1)$  but can be transformed to  $!Q1 * !CLK1$  to fit into one and-term.

The set and reset behave as usual for a flip-flop, except for the usually forbidden combination of set and reset both high. This condition in the PAL20RA10 bypasses the flip-flop and converts the output into a combinatorial i/o.

Many other PLDs are now made with an asynchronous option. A common way of implementing this is to use a double multiplexer, as in Fig. 8. One multiplexer feeds the clock, the other drives the output enable.

The clock multiplexer has inputs from an and-term and the common clock, the output enable multiplexer is driven by the same and-term and either a common output enable or an 'always enabled' input. The multiplexer select bit is arranged so that the and-term is available to either clock or output enable.

### Buried register PLDs

Although some FPLDs have buried registers, these are designed into the part and the designer has no choice in the proportion of flip-flops which are internal, and those which are outputs.

Another failing of some PLDs is the waste of resources when an output flip-flop is by-passed to provide a combinatorial i/o. Some of the more advanced PLDs overcome both of these shortcomings by allowing by-passed flip-flops to be used as internal components, but with no direct access to the outside world.

One of the most versatile programmable logic devices in the 20 to 28 pin range, is the PLC42VA12. This is an FPLD which can emulate the PLS179, PAL22V10 or PAL20RA10. Figure 9 shows the output stage of the device. There are separate and-terms for the ten clock inputs and ten output enable signals, as well as the set and reset lines and direct load facility, which is found on the PLS179.

Each output has three or-terms and two feedback lines to the and-array. If the flip-flop is bypassed, so that the output becomes a combinatorial i/o pin, the feedback from the flip-flop is still available.

A by-passed flip-flop becomes a buried flip-flop, so this resource need not be wasted.

When designing for the PLC42VA12 with Snap, which is the Philips PLD software, all nodes in the design can be defined irrespective of whether they are internal or external. All flip-flop outputs are treated equally, whether they are by-passed or fed to output pins.

It is only at the time when nodes are assigned to pins that the software will allocate logical nodes to physical elements within the PLD.

Many PLD compilers require the designer to define buried nodes at the start of the design.

The circuit of Fig. 10a can be used as an indication of the complexity of design which may be incorporated into the PLC42VA12. Eight internal flip-flops are used to form a two digit decade counter whose outputs feed a quadruple

two-bit multiplexer. The multiplexer output drives a seven segment decoder which is output from the device. Selection of the multiplexer is by a two bit state machine which also provides digit select outputs. Different clocks are used for the counter and the digit select. This circuit uses only three inputs and nine outputs leaving three i/os and seven inputs unused. As we shall see, the counters need nine terms each, the decoder/multiplexer uses 32 terms while the digit select takes just two terms. There are, therefore, twelve and-terms spare for using with the leftover inputs and i/o.

The design may be split into four sections.

Let us first examine the decade counters; their state diagram is shown in Fig. 10b. The most efficient way of building counters is, usually, with toggle flip-flops, so we will follow this approach. To find the minimum solution we can draw out the Karnaugh maps for each counter bit; this is done in Fig. 10c.

A toggle must be entered on every occasion when a bit changes from 1 to 0 or from 0 to 1, remembering that above 9 (1001b) the counter must jump direct to 0 (0000b). The numbers 10 to 15 have been included in case the counter should find itself in one of these states, perhaps because of some malfunction. If they were not included, the counter could get stuck.

From the Karnaugh maps we can write the following equations:

$$\begin{aligned}
 B3.T &= CE \& (B3 \& B2 \\
 &\quad \# B3 \& !B1 \& B0 \\
 &\quad \# B2 \& B1 \& B0 \\
 &\quad \# B3 \& B1); \\
 B2.T &= CE \& (B3 \& B2 \\
 &\quad \# !B3 \& B1 \& B0); \\
 B1.T &= CE \& (!B3 \& B0 \\
 &\quad \# B3 \& B1); \\
 B0.T &= CE \& (!B3 \\
 &\quad \# B2 \& B0 \\
 &\quad \# B1 \& B0);
 \end{aligned}$$

although there are eleven terms, two of them are duplicated, B3 & B2 and B3 & B1, so a single and-term is used for each making nine terms needed in all. The MSB counter, A3 to A0, will use the same equations except that it only toggles when the LSB is nine; the term B3 & !B2 & !B1 & B0 must, therefore, be and-ed with every term giving:

$$A3.T = CE \& B3 \& !B2 \& !B1 \& B0 \& (A3 \& B2 \& \dots \text{ etc.}$$

We must also define the clock to be used; this is done as follows:

$$\begin{aligned}
 B3.CLK &= CLK \\
 B2.CLK &= CLK \\
 \text{etc.}
 \end{aligned}$$

These definitions do not use up any and-terms.

The third section we can define is the multiplexer/decoder.

The seven segment decoder is a straightforward combinatorial design.

Segment 'a', for example, is used in every number except '1' and '4'; the basic equation for segment 'a' is therefore:

$$\begin{aligned}
 !SEG_a &= !B3 \& !B2 \& !B1 \& B0 \\
 &\quad \# !B3 \& B2 \& !B1 \& !B0 \text{ for the LSB}
 \end{aligned}$$

In order to select the MSB or LSB this basic function must be gated with the appropriate select function. We can define these as D1 & !D0 for the MSB and !D1 & D0 for the LSB. The full equation becomes:

$$\begin{aligned}
 !SEG_a &= !D1 \& D0 \& !B3 \& !B2 \& !B1 \& B0 \\
 &\quad \# !D1 \& D0 \& !B3 \& B2 \& !B1 \& !B0 \\
 &\quad \# D1 \& !D0 \& !A3 \& !A2 \& !A1 \& A0 \\
 &\quad \# D1 \& !D0 \& !A3 \& A2 \& !A1 \& !A0
 \end{aligned}$$

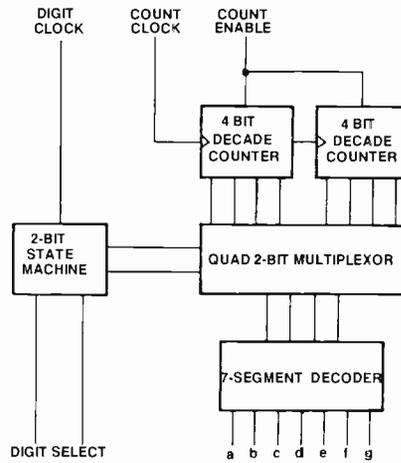


Fig. 10a. block diagram of multi state machine example.

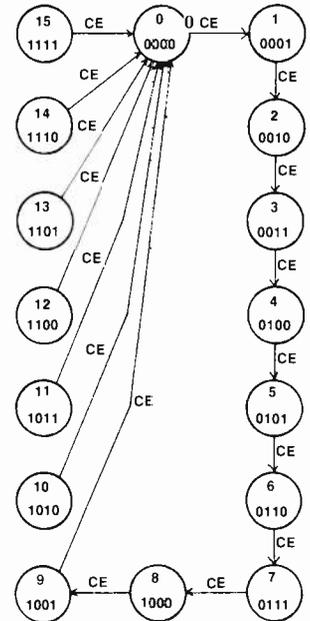


Fig. 10b. State diagram for decade counter

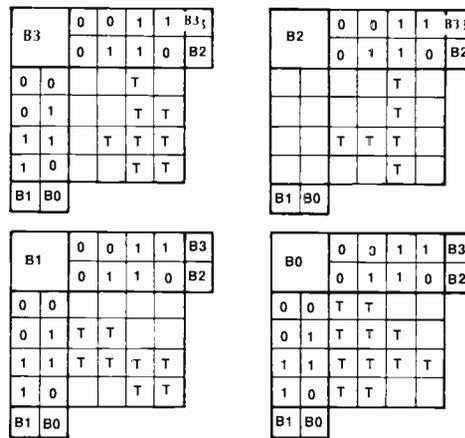


Fig. 10c. State diagram for digit select.

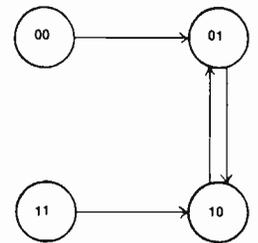


Fig. 10d. Karnaugh maps for decade counter

While asynchronous pals may be used for random logic which also includes flip-flops, it is also useful to be able to use them for systems where more than one clock is used. Fig. 10 illustrates a design which contains two state machines driven by different clocks.

One half of the circuit is a two stage decade counter whose design proceeds via a state diagram and Karnaugh Maps. A single seven segment decoder allows the count of each digit to be displayed in the standard format. The second state machine merely toggles between two states to drive the multiplexer and select each digit in turn for the decoder. Outputs from this machine provide digit select signals for driving a multiplexed display. This design fits PLC42VA12 or GAL6001. Both have selectable clock inputs for all flip-flops.

Similar equations may be derived for the other segments; in all, 32 terms are needed for the whole decade.

The state diagram for the final section is shown in Fig. 10d. The basic function is a toggle between D1 & !D0 and !D1 & D0, but we must also include the illegal states D1 & D0 and !D1 & !D0. The transitions are unconditional so we can easily derive the equations as:

$$\begin{aligned}
 D1.J &= D0D1.K = !D0 \\
 D0.J &= !D0 \\
 D0.K &= D0 \\
 D1.CLK &= DCLK \\
 D0.CLK &= DCLK
 \end{aligned}$$

These use just two and-terms as the two D0 and the two

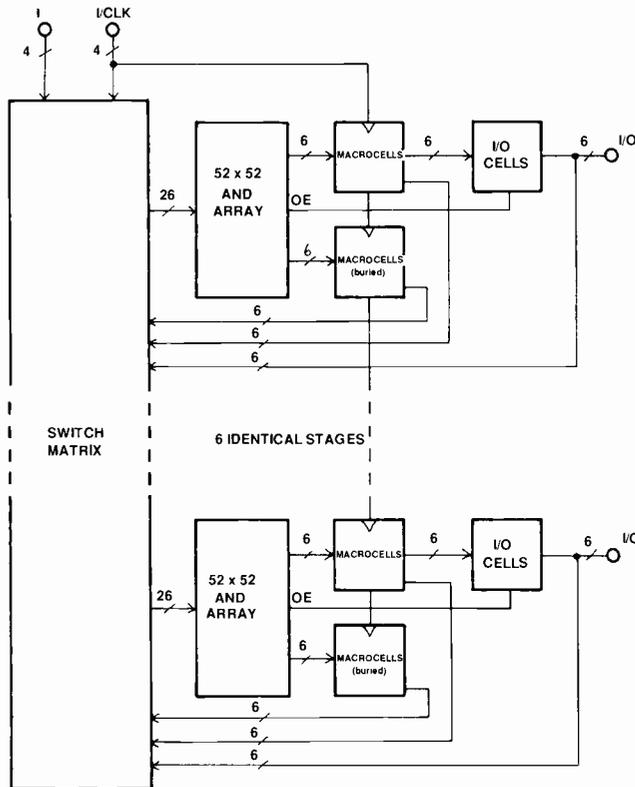


Fig. 11. Block diagram of MACH220.

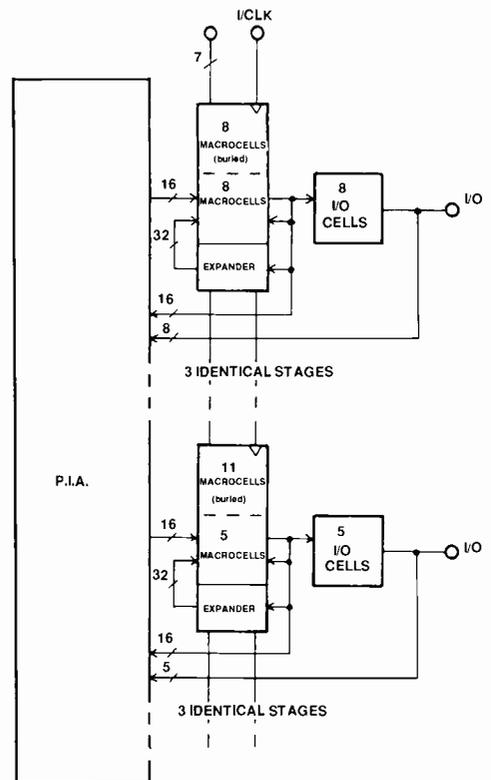


Fig. 12. Block diagram of EPM5128 (MAX).

!D0 terms each use just one and-term which is used twice in the OR-array.

While this design has been aimed at the *PLC42VA12*, there are other PLDs with similar capabilities. Among these is the *GAL6001*; this device has input flip-flops but no direct load facility. It uses D-type flip-flops with a clock enable input allowing J-K flip-flop emulation.

It also has an eight bit wide dedicated buried register making it more powerful in some applications than the *PLC42VA12*.

Other complex PLDs exhibiting buried registers include the *PALCE29M16* and *PALCE29MA16* from AMD, *CY7C330* and *CY7C331* from Cypress, *5AC312* from Intel, *ATV750* from Atmel and *XL78C800* from Exel. All these use pal architecture (i.e. fixed or-array) except the *XL78C800*, which has a nor-nor structure in a single array.

This is equivalent to an and-or structure because:

$$!(!(A\#B) \# !(C\#D)) = (A\#B) \& (C\#D)$$

by de Morgan's Laws.

### LSI PLDs

So far we have described PLDs with up to 28 pins but, in the last few years, technology has moved on to the point where PLDs are being made with over one hundred pins and the capability to replace a dozen or more *16V8*s.

LSI has followed three basic paths, the simplest of which is a multi-pal approach. The main families are the AMD *Mach* and Altera *Max*; the chief difference between them is the way in which the pal blocks are interconnected.

Large pal type devices engender problems with propagation delay introduced by the and-array. Each programmable cell adds capacitance to the array and, for example, in an 84 pin device, there could be about 160 inputs to the and-array if all the inputs and i/o were directly connected to the array. This compares with just 32 array inputs in a *GAL16V8* making the structure

significantly slower than a basic gal.

In the *Mach* family, the device inputs are fed to a switch array which allocates them to the pal blocks, with a maximum of 22 or 26 into each block. The actual size of each pal block varies according to the actual device, but they are of the form *22V12*, *26V16* etc.

Each fixed-or term is fed by only four and-terms but a logic allocator combines up to four or-terms into each output. Thus, the and-terms associated with i/o used as inputs need not be wasted. Half the devices in the basic *Mach* family have macrocells which are all routed to i/o pins, while the rest have half the macrocells buried.

Figure 11 is the block diagram of the *Mach220*, a middle size device with 68 pins and buried registers.

*Max* devices are based on a logic array block (lab) which has sixteen i/o macrocells, some buried, and a logic expander. The logic expander consists of 32 nand-terms which are fed back into the and-array and may be used as additional logic for any of the macrocells in the lab.

Each macrocell has three and-terms, plus an exclusive-or for J-K emulation, but, unlike the *machs*, none of the i/o macrocells can be buried if the pin is used as an input. The signal routing is handled by the programmable interconnect array (pia), which has all the i/o and macrocell feedbacks available.

As with *Machs*, each lab is fed those signals which it requires; unlike *Machs*, all direct inputs and local lab feedbacks are always available to each lab. The block diagram of a 68 pin *Max*, the *EPM5128*, is shown in Fig. 12. Both families have similar logic capability with the slight edge going to the *Max* family. This advantage is bought by having a higher connectivity into each lab.

The result is a slightly slower device, and one with variable delays.

Because all *Mach* signals pass through the switch array they all have virtually the same delay time; in the *Max*

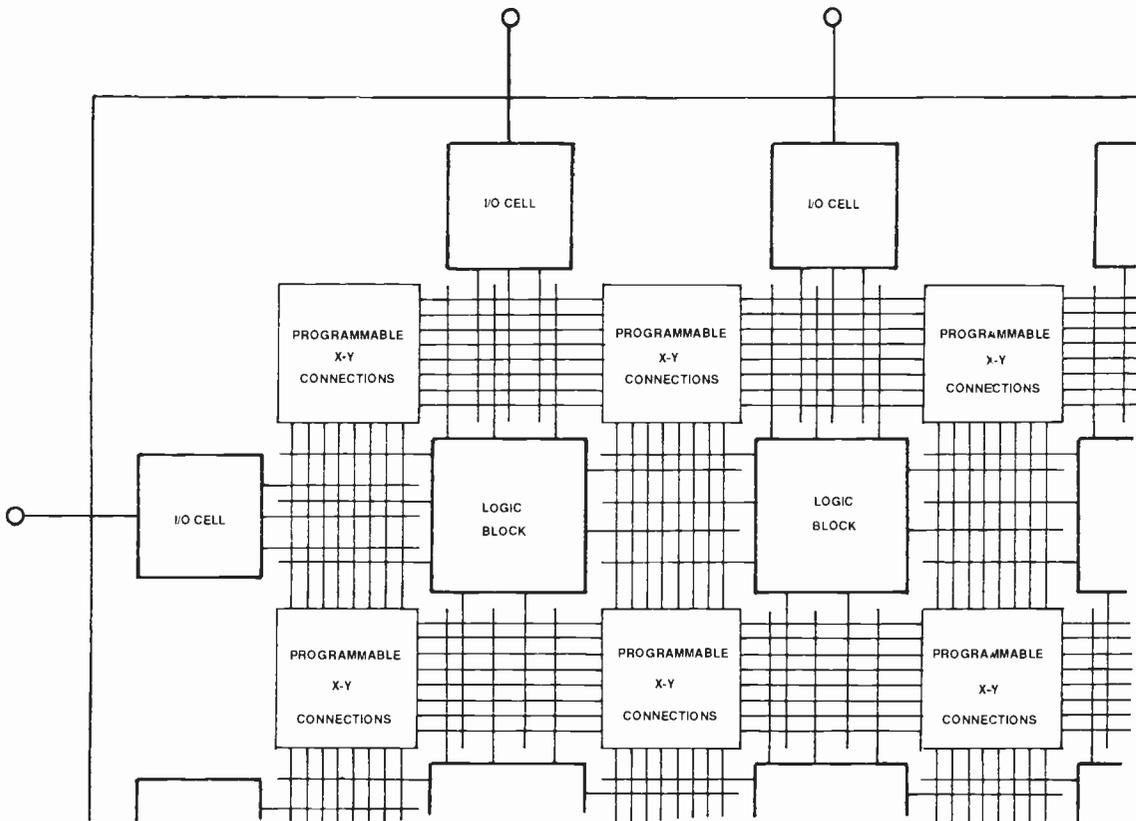


Fig. 13a. Floor plan of a typical FPGA.

The traditional way to mop up large quantities of logic elements has been with masked asics, particularly gate arrays. PLD design files can even be used as data input for many asic design packages. FPGAs are the PLD answer to masked asics. The floor plan of a typical FPGA is shown in Fig. 13a; the similarity to a gate array is self evident. The same four principal components exist in both structures.

Logic signals enter and leave the FPGA via i/o cells, which offer the usual features, such as tri-state, cmos/TTL interfacing, edge speed selection, and so on.

The logic functions are defined in internal logic blocks. These are often more complex than masked gate array logic cells. Two examples are shown in Figures 13b and 13c. The Xilinx cell is the more complex, and includes configuration bits to define the logic paths through the macrocell. The Actel macrocell is smaller and, apart from the flip-flop bypass, has a fixed architecture. Connections between macrocells are made by horizontal and vertical routing lines in channels between the macrocells. Fuses or, in the case of Xilinx, ram cells at crossing points define the interconnections, and the logic paths in and out of the macrocells and i/o cells.

Design path is very similar to a masked asic, with logic capture, simulation, place and route, and timing simulation as the main steps. The advantage of FPGAs is that turn-round is very much quicker, and the minimum quantity is very much lower.

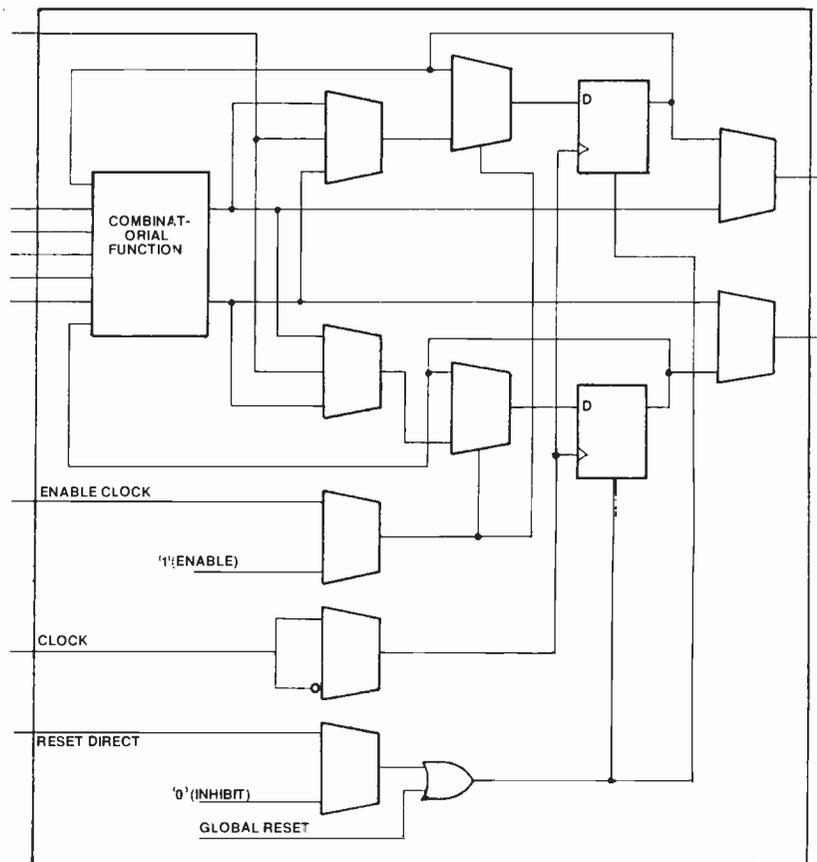


Fig. 13b. Xilinx macrocell.

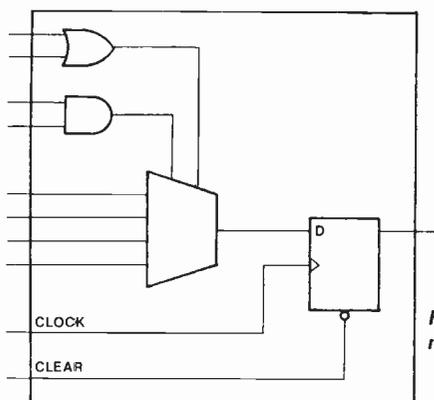


Fig. 13c. Actel macrocell.

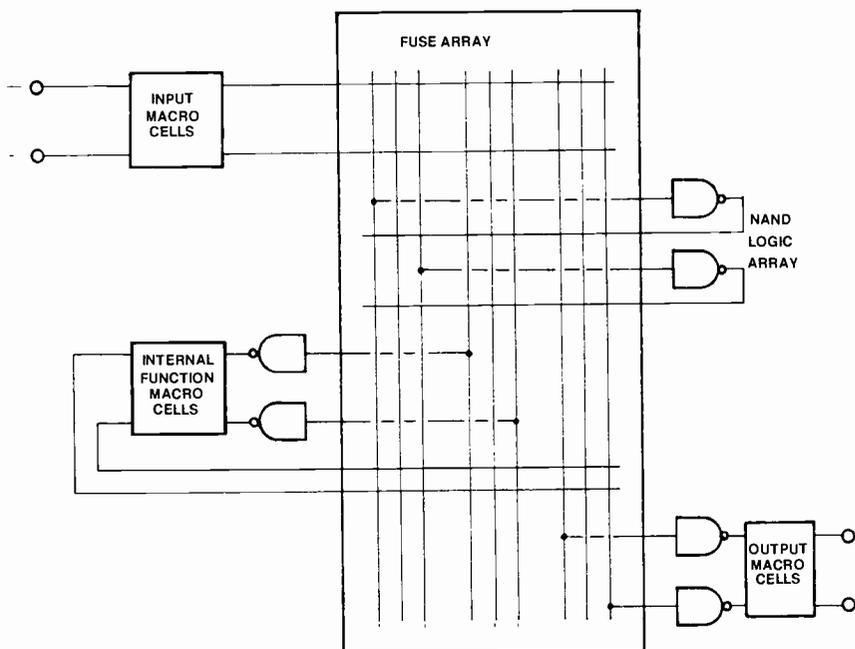


Fig. 14. PML structure.

family, signals can pass direct to the *Lab*, via the PIA or be further delayed in the logic expander. While these delays are predictable, they can lead to skews or races both internally and externally.

Similar architectures are also exhibited by the *ATV2500* and *ATV5000* from Atmel, and by the *Plus* family from Plus Logic.

AMD and Altera have also introduced advanced versions of their basic families.

The second type of LSI structure uses a more distributed architecture, more like masked gate arrays. In fact they are commonly known as field programmable gate arrays (FPGAs). This term is sometimes applied to all LSI PLDs but it is quite easy to distinguish between them.

Very large pal-type structures are just that; their primary logic capability is achieved by wide and-gates which are or-ed together in small groups, each or-gate being committed to one particular output pin. Much of the potential logic resource is wasted because only a few inputs are connected to each and-gate, and many of the and-gates in each or-grouping are often not used.

Figure 13a shows the structure of a typical FPGA. Each logic block has only ten or a dozen i/o lines; these are fed via programmable connections to the routing channels which surround the logic blocks, allowing them to be joined to other logic blocks and the device i/o.

The logic blocks themselves contain relatively simple components which can be configured to a number of standard logic functions.

The internal structure of two types of FPGA are shown in figures 13b and 13c. These two devices, introduced by Xilinx and Actel respectively, exhibit some differences. The Xilinx logic block is more powerful than Actel's so the smallest arrays, both available in 68PLCC packages, contain 64 and 295 blocks respectively, although both claim to be equivalent to 1200 gates.

The most profound difference between the two is the

way in which they are programmed. Xilinx arrays use ram cells to define both interconnections and logic block configuration. The program data is usually stored in an adjacent eeprom which is automatically downloaded into the array on power up, because the ram cells lose their data when switched off. This additional board space can be a disadvantage, but product development can be much simplified, and it might be possible to use the same circuit board for more than one function.

The Actel FPGAs do not need their cells configuring, because they are a much simpler design. Array connections are made with an 'anti-fuse': this consists of a thin dielectric layer sandwiched between polysilicon and the silicon surface. The programming pulse ruptures the dielectric and alloys the two silicon layers together. The connections in this case are therefore hard wired and the device cannot be reprogrammed.

Designing FPGAs involves more steps than pal structure devices.

The basic logic design is the same but, once the desired function is defined, it must be broken into modules which fit the architecture of the FPGA logic blocks. The modules must be allocated to blocks and then connections routed between them. These are the same place and route steps which are needed to define masked gate arrays.

Once the design is placed in the array, timing simulation is necessary for the delay of internal signals will be affected by the lengths of tracks they use. From this point of view it may be more difficult to achieve instant success than with a pal structure, but the final result should give more efficient use of silicon, and therefore a cheaper solution.

The third class of LSI is based on an FPLS structure; two examples are the MAPL (multiple array programmable logic) from National Semiconductor and PML (programmable macro logic) from Philips.

MAPL is a large FPLS with additional gal outputs on larger devices.

The chief innovation is the use of page mode power-up, so that only a small portion of the array is consuming power at any one time.

As well as a 'next state' output from each transition equation, there is a 'next page' which powers up the page containing possible jumps from the next state. This allows the array to achieve high speed without an excessive power consumption.

PML, in Fig. 14, uses a single foldback array of nand-gates for logic implementation. This uses the equivalence:

$$\begin{aligned} &!(A * B) * !(C * D) \\ &= (A * B) + (C * D) \end{aligned}$$


which can be deduced from de Morgan's Laws.

In PML, the logic core is surrounded by macro logic elements with inputs and outputs to the NAND array. Device inputs and outputs are also connected to the logic core so that the macro elements can be used either internally or as output functions.

The *PML2552*, for example, has 29 dedicated inputs, 16 of which have by-passable flip-flops; there are 24 bi-directional i/o lines including 16 by-passable registered outputs.

Internally there are 20 J-K flip-flops with a separate clock array, and a logic core of 96 nand-gates.

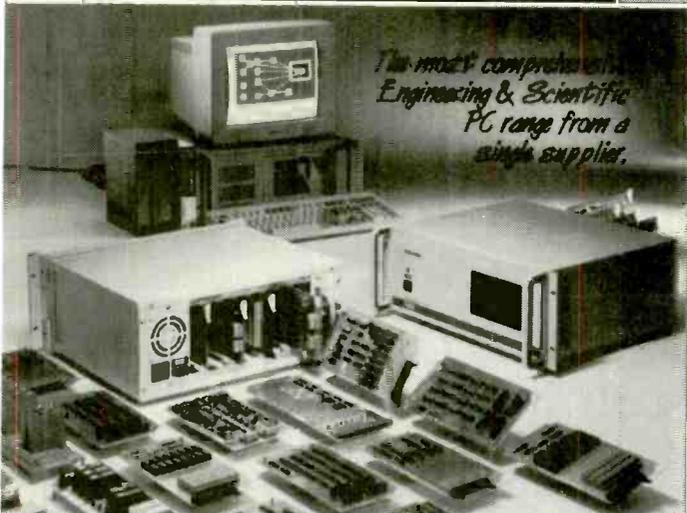This structure is freer than pal-type LSI, although this particular device has not quite the power of 68PLCC *Mach* or *Max* parts in terms of gate and flip-flop count. Neither does it match FPGAs for potential logic complexity. There is no reason why, with denser internal logic, this structure



<p>Multibit A/D, I/A, D, I/O, Timer Card</p>	<p>4.5 Digit DVM (A, R) Card</p>	<p>8 Chan A/D, D/A, Dig. O, Timer Card</p>
<p>Lab. Notebook &amp; Control Software</p>	<p>2 Axis Stepper (Digital) to Lab. Cart</p>	<p>5 Slot PC Bus Chassis with PSU</p>
<p>IEEE-83 (GPIB) Instrument Interface</p>	<p>8 Port Intel like 4 Buffered RS232 I/O</p>	<p>PC Lab Data Acquisition &amp; Control Cards</p>
<p>Remote Data Acquisition Modules</p>	<p>Windows Acquisition Control Charting</p>	<p>Solid State RAM/EPROM Disk Cards</p>
<p>286/386/486 CPUs &amp; Backplanes</p>	<p>16 Chan Relay Switch</p>	<p>8 Slot Card Cage &amp; PC Bus Backplane</p>
<p>Solid State Memory Disk &amp; Card</p>	<p>RS232/422/485 Communications Cards</p>	<p>Signal Conditioning &amp; Amplifier Modules</p>
<p>PC Bus Slot Extenders (0.16 Bit)</p>	<p>3 Slot Micro-Bus CBUs Chassis</p>	<p>Relay Switch &amp; Isolated Dig. I/P</p>

**Plus MUCH more...**  
Please CALL for your FREE copy of our latest Catalogue  
OEM, Dealer & Educational Enquiries Welcome

**INTEGRATED MEASUREMENT SYSTEMS**  
Integrated Measurement Systems Ltd.  
305-308 Solent Business Centre,  
Millbrook Rd West  
Southampton SO1 0HW, HAMPSHIRE

Tel: (0703) 771143 Fax: (0703) 704301  
ADVANTECH. UK Distributor  
Designers & Suppliers of Measurement, Test & Control Systems & Software

CIRCLE NO. 116 ON REPLY CARD

## Multi-Device Programmer



only **£325**

- ✓ Fast Programming - Intelligent Algorithms
  - ✓ Connects direct to printer port
  - ✓ On line "HELP" System
  - ✓ Easy to use menu driven software
  - ✓ Supports a wide range of devices
- All without adapters

Including:-  
EPROMs E<sup>2</sup>PROMs Flash (28F..and 29F..)  
PLDs GALs PALCEs  
8748 and 8051 families Including 87C751  
Additional modules include:-  
Serial E<sup>2</sup>PROMs (93C.. and 24C..)  
PIC, Motorola and Zilog microcontrollers  
New parts added all the time

Contact SMART Communications for our full range of programmers including stand-alone programmers, gang programmers and our comprehensive universal device programmer

Tel: 081-441 3890  
Fax: 081-441 1843



CIRCLE NO. 117 ON REPLY CARD

OSCILLOSCOPES	
HEWLETT PACKARD 54600A - 100 MHz DIGITISING CHANNEL	£1400
HEWLETT PACKARD 1740A, 1741A, 1744A - 100MHz DUAL CHANNEL	£350
HEWLETT PACKARD 1707A, 1707B - 75MHz DUAL CHANNEL	£275
HEWLETT PACKARD 182c - 100MHz FOUR CHANNEL	£350
TEKTRONIX 453, 454, 465, 465B, 475, 475A, 466, 468 - 100 to 800MHz DUAL CHANNEL	from £250
TEKTRONIX 7603, 7613, 7623, 7633, 7313, 7704A, 7844, 7904 - 100 to 600 MHz TWO or FOUR CHANNEL	from £350
(Various plug in options available)	
TELEQUIPMENT DM63, D75, D83-50MHz DUAL CHANNEL	from £175
GOULD MODELS OS 245, OS 4000, OS 4020, OS 4200	from £125
GOULD 400 20MHz BAND WIDTH - 100Ma/s SAMPLING RATE - AS NEW	£1350
PHILIPS 3211, 3212, 3217, 3228, 3240, 3243, 3244, 3261, 3262 - 15 to 120MHz TWO AND FOUR CHANNEL	from £125 to £350
SOLARTRON/SCHLUMBERGER CD 1740 - 20MHz - FOUR CHANNEL	from £250
DUMART 1062 - 50MHz - DUAL CHANNEL	£250
SPECTRUM ANALYSERS	
HEWLETT PACKARD 3580A - 5Hz to 80KHz	£1250
HEWLETT PACKARD 3582A - 25KHz DUAL CHANNEL	£3000
HEWLETT PACKARD 3585A - 20Hz to 40KHz (GPIB)	£4750
HEWLETT PACKARD 1827 - MAINFRAME WITH 8559A (10MHz to 21GHz)	£3750
HEWLETT PACKARD 8590A - 10MHz to 1.90GHz PORTABLE	£4500
ADITEC 727 - 20GHz	£2200
MARCOINI 2370 - 110MHz	£1250
MARCOINI 2371 - 200 MHz	£1750
MISCELLANEOUS	
HEWLETT PACKARD 3701A/3702A/3703A - MICROWAVE LINK ANALYSER	£1000
HEWLETT PACKARD 3702B/3705A/3710A/3710A - MICROWAVE LINK ANALYSER	£1500
HEWLETT PACKARD 3779A PRIMARY MULTIPLEX ANALYSER	£1000
HEWLETT PACKARD 418E - S.W.R. METER	£275
HEWLETT PACKARD 8750A - STORAGE NORMALISER	£400
HEWLETT PACKARD 5342A FREQUENCY COUNTER (18GHz)	£1400
HEWLETT PACKARD 8443A TRACKING GENERATOR/COUNTER	£450
HEWLETT PACKARD 8445B AUTOMATIC PRE-SELECTOR	£700
HEWLETT PACKARD 4953A - PROTOCOL ANALYSER	£2500
HEWLETT PACKARD 3456A DIGITAL VOLTMETER	£675
HEWLETT PACKARD 8011A PULSE GENERATOR	£500
HEWLETT PACKARD 8013B PULSE GENERATOR	£750
KEITELY 197A AUTO D.M.M. WITH IEEE	£400
MARCOINI 2830 PCM MULTIPLEX TESTER	£1250
MARCOINI 2831 CHANNEL ACCESS SWITCH	£500
RACAL-DANA 9081 SYNTHESISED SIGNAL GENERATOR (520 MHz)	£550
RACAL-DANA 9084 SYNTHESISED SIGNAL GENERATOR	£500
RACAL-DANA 9303 TRUE RMS - R.F. LEVEL METER	£650
ANRITSU - ME588C - MICRO WAVE SYSTEM ANALYSER (AS NEW)	£3500
AVO - RM215 L2 - BREAKDOWN/LEAKAGE + IONISATION TESTER	£500
DATRON 1061A - AUTOCAL MULTI-FUNCTIONAL VOLTMETER (6.5 DIGITS)	£950
DATRON 1071A - AUTOCAL MULTI-FUNCTIONAL VOLTMETER (7.5 DIGITS)	£1150
FARNELL RB 1090-35 ELECTRONIC LOAD	£450
GALLENKEMP 300+ SERIES THERMOSTAT/CYCLE TIMER/TEMPERATURE CYCLING OVEN	£750
MULTICORE SOLDERABILITY TESTER	£250
ROBDE + SCHWARTZ QDM BN 38711 DIGITAL 'O' METER	£400
PHILIPS 5167 1-10 MHz FUNCTION GENERATOR	£400
PHILIPS PM6672 TIMER COUNTER 1GHz WITH IEEE	£650
SOLARTRON/SCHLUMBERGER 1170 - FREQUENCY RESPONSE ANALYSER	£500
SOLARTRON/SCHLUMBERGER 3530 - ORION DATA LOGGING SYSTEM	£750
WAYNE KERR B905 - AUTOMATIC PRECISION BRIDGE	£800
WAYNE KERR 3245 - PRECISION INDUCTANCE ANALYSER	£2500
WAYNE KERR 6425 - PRECISION COMPONENTS ANALYSER	£2500
WILTRON 352 - LOW FREQUENCY DIFFERENTIAL INPUT PHASE METER	£350
WILTRON 560 - SCALAR NETWORK ANALYSER	£650
YOKOGAWA YEW 3685 ANALYSING RECORDER	£650
B & K - 2511 VIBRATION METER	£1100
B & K - 2512 VIBRATION METER (2511 + 1821)	£1750
B & K - 2515 VIBRATION METER (FFT)	£4500

MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT  
ALL EQUIPMENT LISTED HERE IS USED, WITH 30 DAYS GUARANTEE  
Please check availability before ordering. Carriage + VAT to be added to all goods

## TELNET

8 Cavans Way, Binley Ind. Estate, Coventry CV3 2SF  
(Premises situated close to Eastern Bypass in Coventry with easy access to M1, M6, M40, M42, M69, M45)  
**TELEPHONE 0203 650702 FAX 0203 650773**

CIRCLE NO. 118 ON REPLY CARD

# APPLICATIONS


## Switched capacitor filter combines notch and low-pass functions

It is increasingly common to reserve a very narrow band of the audio spectrum for data, control or coding information. Provided that very sharp band stop and pass filtering is used for insertion and recovery, adding the information sacrifices very little in audio quality.

GEC Plessey has produced a switched-capacitor device in cmos asic technology called the MA6882. As *Application Note 137* describes, the device combines both sharp notch and low-pass filter functions.

For the low-pass filter section, the  $-3\text{dB}$  point is fixed at the clock frequency divided by 1470. Clocking at 5MHz for example will cause cut-off at 3.4kHz. The notch filter however can be placed at four jumper-selectable points, at divisions of the clock frequency of 1870, 2493, 3740 or 7480.


Further suggested applications for the

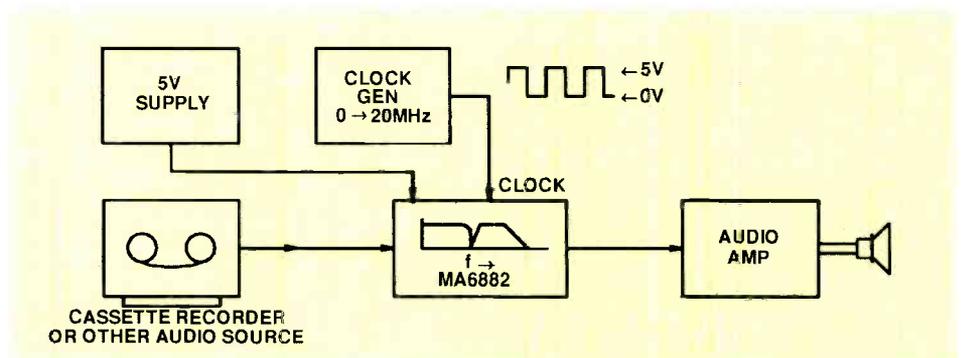


notch information are wow and flutter correction, AGC, noise reduction and sound effects.

**GEC Plessey Semiconductors**, Cheney Manor, Swindon, Wiltshire SN2 2QW. Tel. 0793 518000.

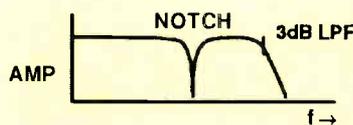*Combined switched-capacitor notch and low-pass filtering for audio frequencies. For the low-pass filter, the  $-3\text{dB}$  is entirely governed by the clock but the notch filter can be placed in any one of four frequency slots, depending on the NA switches.*



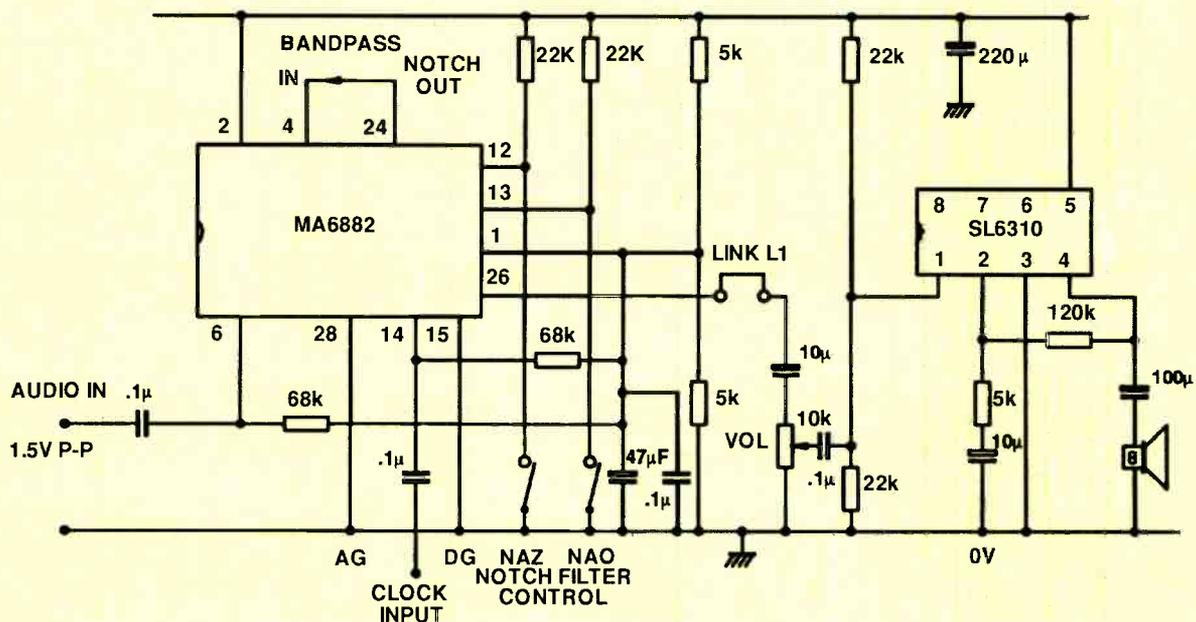*By reserving a fine notch of the audio spectrum for data, it is possible to insert a wide range of useful control functions without subjectively degrading sound quality. With a cassette recorder source for example, it is possible to insert signals to help reduce wow and flutter.*



# Low-noise microphone preamplifier exhibits less than $1\text{nV}/\sqrt{\text{Hz}}$ noise

Instrumentation amplifier configurations are useful as microphone preamplifiers. Besides allowing gain to be set via one resistor, they remove the need for a transformer while keeping common-mode rejection high.



This low-noise circuit from Analog Devices note AN242 features a phantom power option with input protection and is gain adjustable via one resistor,  $R_G$ .

Input-referred noise is less than  $1\text{nV}/\sqrt{\text{Hz}}$  over a gain range of 2 to 2000 while common-mode rejection capability is 90dB or more. For gains to 200, the THD plus noise figure is well below 0.01% at all frequencies to 20kHz.

Phantom power involves inserting a DC voltage, typically between 10 and 48V, on the preamplifier input. This voltage is needed to power capacitive microphones.

In its steady state the phantom voltage presents no problems. At power up or down, or when the microphone is plugged or unplugged however, protection is needed to avoid damaging the preamplifier inputs. Given a phantom voltage of 48V, the input capacitors can discharge several amps into the amplifier inputs.

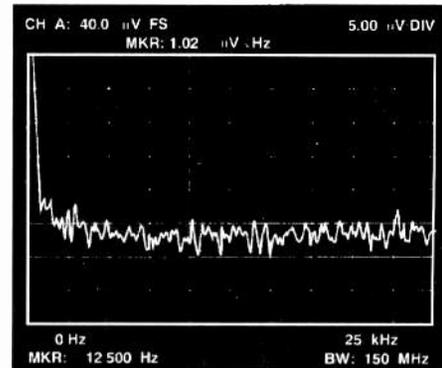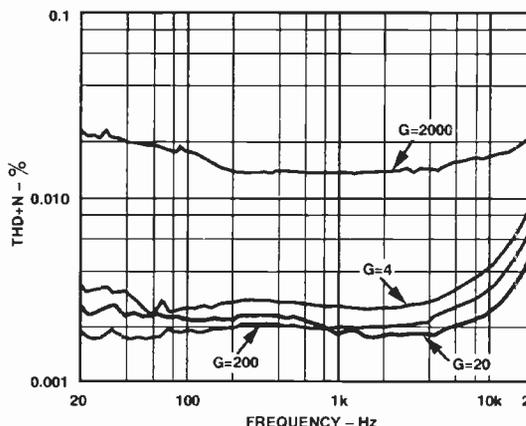In this circuit, protection is provided by two zener diode pairs and resistors for limiting peak current. The 1N752 diodes are 400mW types, equivalent to a European 5.6V BZX79, and limit peak transients to 10V or below.



CONDITIONS:  
SSM-2017 GAIN = -500; OP-275 GAIN = -2  
TOTAL GAIN = 1000  
 $V_S = \pm 20\text{V}$ ;  $R_L / C_L = 1\text{M}\Omega / <60\text{pF}$


Noise display and distortion curves for the high-performance balanced microphone preamplifier. Although vertical graduations on the noise display are  $1\mu\text{V}/\sqrt{\text{Hz}}$ , gain is 1000 so input referred noise is within  $1\text{nV}/\sqrt{\text{Hz}}$ .

Adding protection circuitry increases noise slightly due to the input series resistances. This is countered to an extent however since phantom-powered microphones tend to have a higher than usual output.

Power supply circuitry should not allow the phantom power to be switched independently of the bipolar supply to the op-amp. Capacitor  $C_N$  is added to filter RFI above 130kHz while  $R_2$  and  $C_5$  provide roll-off above 240kHz in the second stage.

Further details in the note cover the op-amp, circuit design, performance and the importance of selecting the right components. There is also a discussion of how to further reduce the circuit's RF sensitivity.

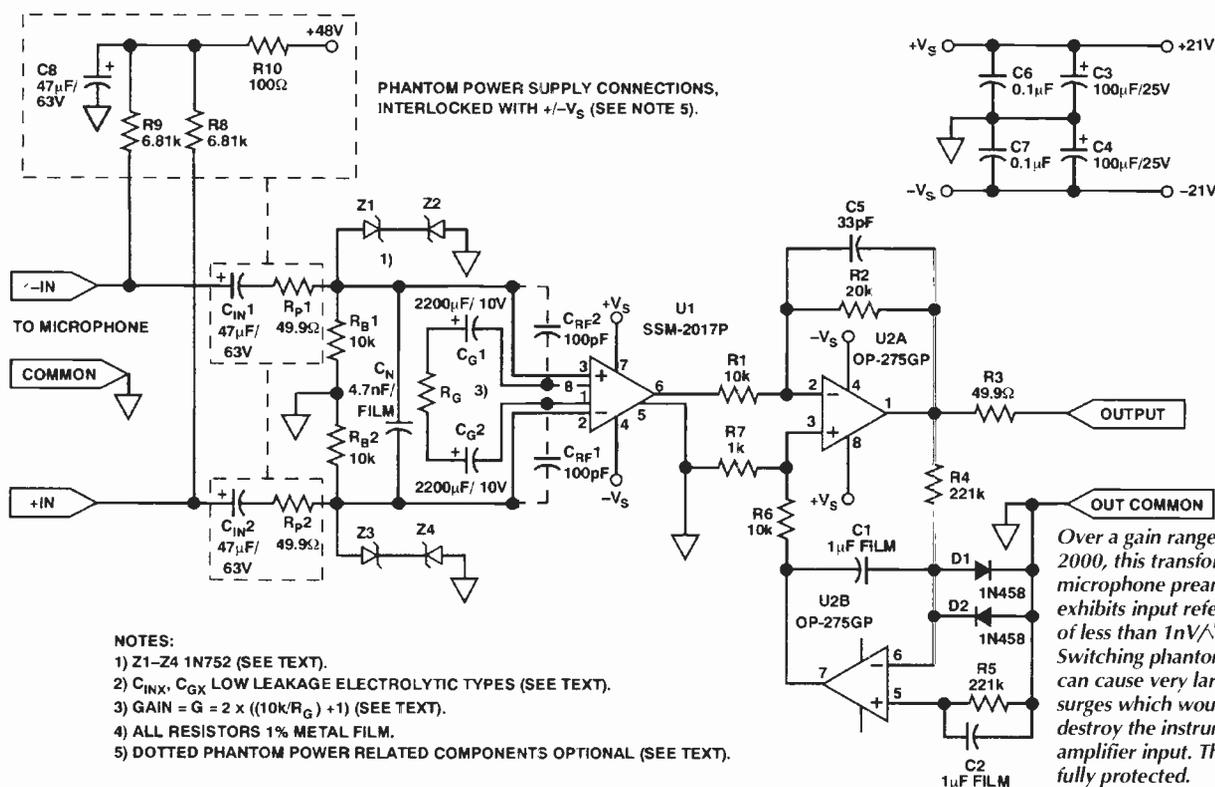Analog Devices, Station Avenue, Walton-on-Thames, Surrey KT12 1PF. Telephone 0932 232222.



# Bidirectional drive for coaxial cable

For voice-band signals, designing a single-cable bidirectional link is quite simple. Similar links for megahertz bandwidth however involve high-speed amplifiers and well-controlled impedance matching.

Programmable wideband transconductance amplifiers can provide such a wideband bidirectional coaxial interface, as illustrated in this diagram from Maxim's twelfth *Engineering Journal*.

Functionally, the circuit is similar to ones used in telephone interfaces and offers the same benefit – it saves the cost of a return cable. Components shown are for a 50Ω system but with appropriate modifications, the circuit is equally suited to 75Ω video and other impedance levels.

Identical circuits terminate each end of the cable. As well as performing signal reception, each return amplifier (the top two) also cancels all signals originating at its end of the link.

On either side, input signals drive both the inverting input of their receiver and the non-inverting input of their transmitter. In this way, the signal passes through the transmitter unchanged but is inverted in the receiver, which results in its cancellation.

To achieve the cancellation, the amplifier transconductances must be set for unity gain throughout. Several factors can degrade the cancellation. First, phase shift in the line

driver prevents the return amplifier from subtracting identical signals.

Secondly, any transconductance mismatch in the amplifiers causes the signals to have different amplitudes, which again disturbs the output nulling. Finally, any impedance mismatch along the cable causes reflections. The non-adaptive circuits shown cannot distinguish between such echoes and the desired incoming signal.

Signal cancellation depends on the tolerances of termination resistors  $R_{1,5,6,10}$ . Their degree of mismatch with the cable impedance is also important. Similarly, the transconductance for each amplifier is affected by resistors  $R_{2,3,8,9}$ . Transconductance,  $g_m$ , is  $8/R$ . The '8' is a property of the IC and guaranteed to be within  $\pm 2.5\%$ .


Outputs test traces are shown. Those at the top show both outputs when one end of the link is driven with a 1MHz signal, the other with 2MHz. Both generators are 50Ω impedance.

On the lower pair of traces, one input is driven while the other is terminated with 50Ω. On the receive side, the receiver outputs the full signal as required, top trace. The receiver on the transmit side however should show none of the transmitted signal.


The small residual signal shown in the lowermost trace results from 30dB

cancellation in the low megahertz range, which will be acceptable for most applications. To achieve it, resistors need to be matched to 1%.

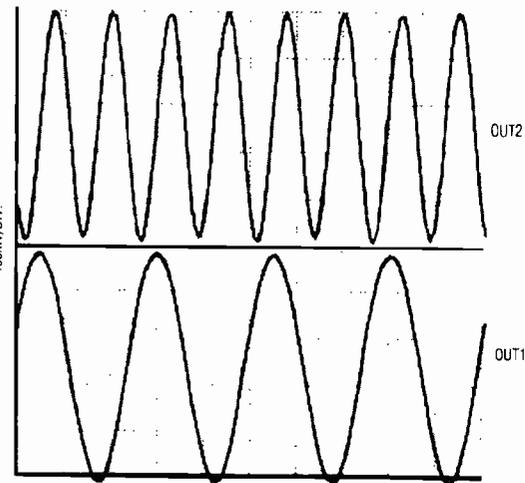
Maxim, 21C Horseshoe Park, Pangbourne, Reading RG8 7JW. Tel. 0734 845255.



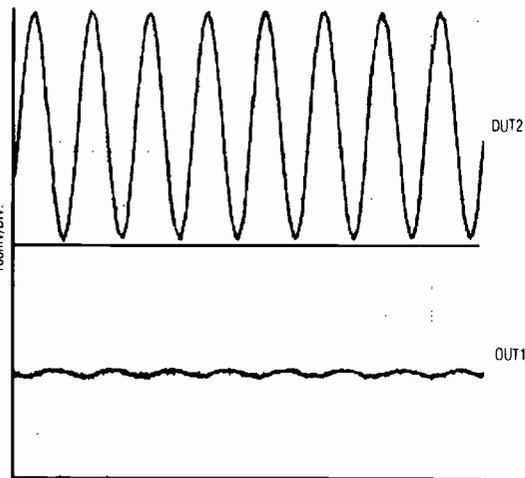These two signals, recovered from either end of a single-cable bidirectional link, are 2 and 1MHz respectively.



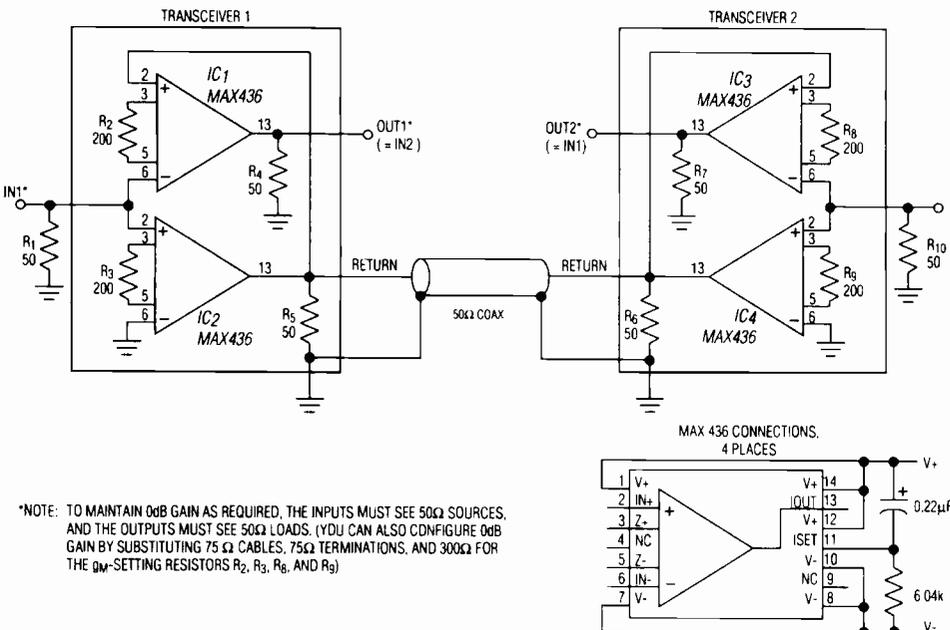In a high-speed bidirectional link, one of the main problems is getting the receiver at the transmitting end to ignore the transmitted signal. If 1% resistors are used, the circuit shown can cancel to about 30dB (lowest trace).




Two transconductance amplifiers form a high-frequency coaxial cable interface similar to the hybrid-circuit interface found in telephones.

# Step-down converter remains efficient at low currents

At currents of around an amp and an input of 12V, this step-down converter is 93% efficient. Many switching converters are highly efficient at a specific output current near their maximum but this design remains efficient as current falls. Although efficiency is highest at low input voltages, the circuit operates from supplies up to 48V.

Designed for use in battery and low power applications, the *LTC1149-5* is a synchronous switching step-down controller capable of operating in 'burst mode'. As Linear Technology's *Power Solutions 1993* brochure explains, it is this mode that allows the device to maintain efficiency with low output currents.

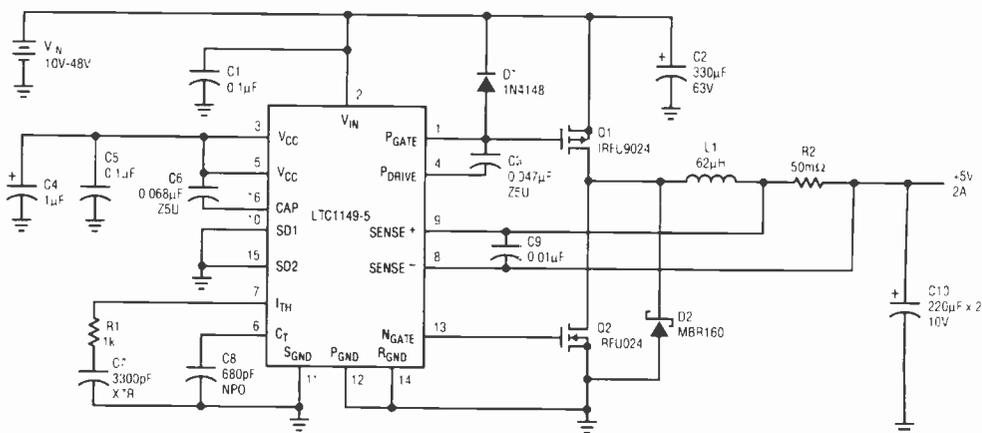At very low battery voltages the IC produces a 100% duty cycle, i.e. the circuit stops switching and passes current directly to the output. The only losses are those in



- C2 UNITEO CHEMI-CON (AL) LXF63VB331M12 5 x 30 ESR = 0.170Ω I<sub>RMS</sub> = 1.280A
- C4 1TAI
- C10 SANYO (OS CON) 10SA220M ESR = 0.035Ω I<sub>RMS</sub> = 2.360A
- D1 IR PMOS B<sub>V</sub>DSS = 60V R<sub>DS(ON)</sub> = 0.280Ω C<sub>ISS</sub> = 65pF Q<sub>g</sub> = 19nC
- D2 IR NMOS B<sub>V</sub>DSS = 60V R<sub>DS(ON)</sub> = 0.100Ω C<sub>ISS</sub> = 79pF Q<sub>g</sub> = 28nC
- D\* SILICON VBR = 75V
- D2 MOTOROLA SCHOTTKY VBR = 60V
- R2 KRL NP-1A-C1-0R050J Pd = 1W
- L1 COILTRONICS CTX62-2-MP OCR = 0.040Ω MMP CORE

QUIESCENCE CURRENT = 1.5mA  
TRANSITION CURRENT (BURST MODE™ OPERATION/CONTINUOUS OPERATION) = 570mA

ALL OTHER CAPACITORS ARE CERAMIC

**When battery input voltage falls to a predefined level, this switching converter stops switching so the only losses are those in the mosfet, inductor and sense resistor.**

the mosfet, inductor and sense resistor.


In normal mode, the two mosfets switch synchronously. Constant off-time control maintains constant ripple current in the inductor, easing the design in applications needing a wide input voltage range.

Current mode control ensures good line and load regulation. This circuit provides 5V at 2A load current with ±5% regulation over load and line variations. Although efficiency is maximum at low input voltages, it stays

above 80% for load currents down to 20mA under most conditions. In shut-down mode, current consumption falls to less than 420µA.

A 3.3V version of the IC is available, namely the *LTC1149-3.3*. There are over forty more circuits in *Power Solutions 1993*.

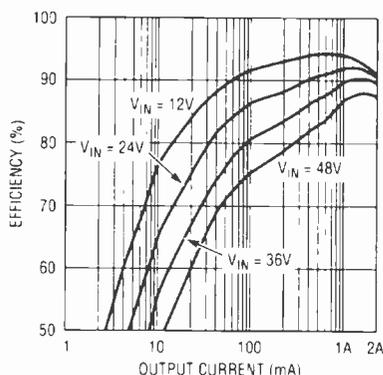**Linear Technology Corporation,**  
Coliseum Business Centre, Riverside Way, Camberley, Surrey GU15 3YL. Tel. 0276 677676.



Most switching regulators are efficient near the limit of their operating current but this one remains efficient at low currents.

# New solution to current sensing

By sensing current via the magnetic field it produces, a new type of transducer from Zetex combines the features of low measurement voltage drop and galvanic isolation.

As this circuit from the *KMC10* data sheet


implies, the shunt is isolated from the sensor to 2kV. In systems where only one power supply is available, this reduces grounding problems and removes the need for a separate supply. Additionally, the magnetic circuit is sensitive. As a result the shunt

resistance is small and causes little effect when inserted in the circuit being measured.

Maximum current handled by the *KMC10* is 10A while resistance of its shunt is 0.7mΩ. Offset trimming is provided in the application circuit to compensate for the sensing bridge's maximum offset of ±2mV.

The bridge makes use of the magnetostrictive effect of thin-film permalloy and operates up to 100kHz. Temperature limits of the device are -65° and 120°C.

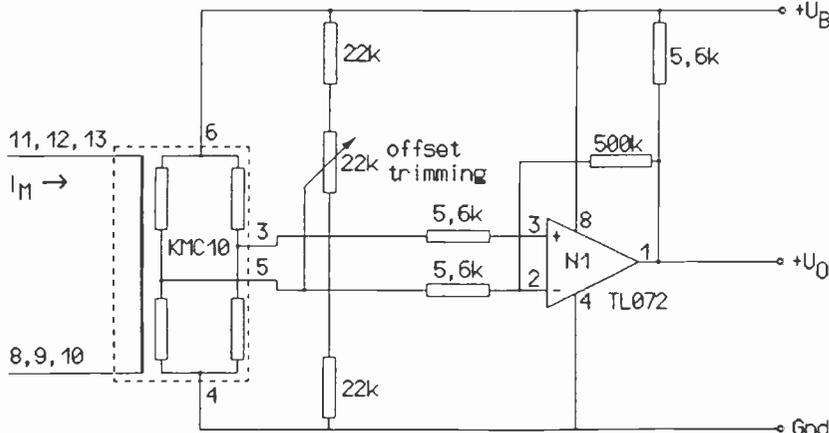**Zetex,** Fields New Road, Chadderton, Oldham OL9 8NP. Tel. 061 627 4963.




**Measuring current by sensing magnetic field strength in a series shunt can offer low voltage drop combined with galvanic isolation. This circuit incorporates a specially designed current sensing IC from Zetex.**

## Low cost data acquisition for IBM PCs & compatibles

All our products are easy to install - they connect directly to either the printer or serial port and require no programming. They are supplied with easy to use software which can be used for either display or print-out.


### ADC-10

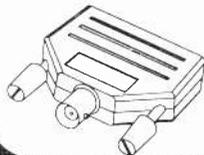

- 8-bit resolution
- one channel
- 10-25K samples per second
- Oscilloscope/Voltmeter software
- 0-5V input range
- Connects to printer port

**£49**


### ADC-11

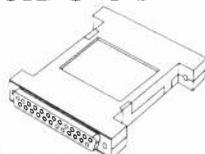

- 10-bit resolution
- 11 channel
- 5-10K samples per second
- Data logger software
- 0-2.5V input range
- Connects to printer port

**£75**

### ADC-16

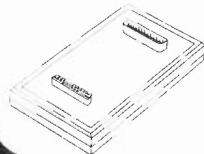

- 8, 12, 16-bit resolution + sign
- 8 s/e or 4 differential inputs
- 216 or 300 8-bit samples per second
- ± 2.5V input range
- Data logger software
- Connects to serial port

**£99**

All prices exclusive of V.A.T.

## PICO TECHNOLOGY LTD

Broadway House, 149 - 151 St Neots Road, Hardwick, Cambridge CB3 7QJ

ACCESS **TEL: 0954 - 211716 FAX: 0954 - 211880**

CIRCLE NO. 119 ON REPLY CARD

# 8031

## System Developers Kit

If you've a project in mind which includes a 8 bit microcontroller, there's a fair chance you'll end up using an 8031.

If so, our new 8031 System Developers Kit will certainly be of interest to you. It includes:

- ◆ C-51 ANSI compatible C Compiler
- ◆ MA-51 Macro Assembler + Linker + Librarian
- ◆ SLD-51 Software Simulator/Debugger
- ◆ Tiny-ICE plug in card In-Circuit-Emulator

Comprehensive manuals are also included together with application examples on disk to get you started. The SDK-31 is priced at just:

**£549**

For further details contact:

**Logicom Communications Ltd.**  
☎ 081 756 1284 Fax 081 813 7589

CIRCLE NO. 120 ON REPLY CARD

# KESTREL ELECTRONIC COMPONENTS LTD

- ☆ All items guaranteed to manufacturers' spec.
- ☆ Many other items available.

'Exclusive of V.A.T. and post and package'

	1+	100+		1+	100+
<b>EPROMS</b>			<b>STATIC RAMS</b>		
2764A-250	2.50	2.20	62256ALP-10	3.30	2.60
27C64-150	2.50	2.20	6264ALP-10	1.95	1.48
27128A-200	2.40	2.20	6116ALP-10	1.10	0.80
27256-250	2.30	2.10	628128LP-10	12.00	10.00
27C256-150	2.90	2.30	HD63B21P	1.95	1.50
27C512-150	3.30	2.55	6522P	2.40	1.80
27C010-150	5.80	4.20	65C02P2	2.90	2.50
27C020-150	9.00	7.60	65C21P2	2.90	2.50
68B50P	1.40	0.85	65C22P2	2.75	2.40
D8749H	4.40	3.75	Z80A CPU	1.30	0.99
MM58274CN	7.00	3.95	Z80A P10	0.95	0.75
80C31-12meg	2.60	2.10	Z80A CTC	0.90	0.70
75176BP	1.90	0.95	Z80A DART	2.20	1.38

74LS, 74HC, 74HCT Series available

Phone for full price list

All memory prices are fluctuating daily, please phone to confirm prices

**178 Brighton Road,  
Purley, Surrey CR8 4HA**  
**Tel: 081-668 7522. Fax: 081-668 4190.**

CIRCLE NO. 121 ON REPLY CARD

# JPG Electronics

Inventor toroidal transformers 225VA 10.5-0-10.5 primary 0-260-285 secondary ... £29.95	SL952 UHF Tuning amplifier LC 16 surface mounting package with data sheet ... £1.95
LFDC 3mm or 5mm, red or green ... 6p each	AM 27802 ... £1.25 each 90p 100+
Yellow ... 11p each	CD1007CB ... 10p
High intensity red, green or yellow 3mm ... 30p each	100+(6p, 1000+)
Cable ties, 1p each, £5.95 per 1000, £19.50 per 10,000	Suction light gun terminated with a jack plug and PPT3 chip gives a signal when pointed at 50Hz flickering light with output wave form chart ... £3.95
Small stepping motor 1 phase 12v 7.5° step 50 ohms ... £8.95	DC-DC converter Reliability model V12P5 12s in 5v 200ma out 300v input to output isolation with data ... £1.95 each or pack of 10 ... £39.50
SAA1027 stepping motor driver chip ... £1.95	1hour counter used 7 digit 230k at 50Hz ... £1.15
High quality photo resist copper clad epoxy glass boards	QWERY1 keyboard 58 key good quality switches new ... £5.00
single sided	Anipax A82903-C large stepping motor 11v 7.5° step 27ohm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 50
double sided	
384 inches ... £0.95	Polyester capacitor box type 22.5mm lead pitch 0.9uF 250Vdc 18p each 14p 100+ 9p 1000+
188 inches ... £2.10	1uF 250Vdc 20p each 15p 100+ 10p 1000+
6x12 inches ... £5.37	2.2uF 250Vdc 30p each 20p 100+ 15p 1000+
12x12 inches ... £10.66	8.2uF 100Vdc 30p each 20p 100+ 15p 1000+
Rechargeable batteries	1uF 50v bipolar electrolytic axial leads each 7.5p, 1000+
A A (H P 7)	0.22uF 250v polyester axial leads ... 15p each, 7.5p 100+
AA 500mAh with solder tags ... £1.55	Philips 123 series solid aluminium axial leads - 33uF 10v & 22uF 10v ... 10p each, 25p 100+
AA 700mAh ... £1.95	Philips 108 series 22uF 63v axial ... 30p each 15p 1000+
C (HP1) 1.8AH £2.20	Multi-layer V-X ceramic capacitors all 5mm pitch 100p 100p 150p 220p 10,000p (10n) 10p each 5p 100+ 3.5p 1000+
C 2AH with solder tags ... £3.60	500pF compression trimmer ... 60p
D 1AH with solder tags ... £4.95	10 uF 370vac motor start capacitor (electrolyte type containing no PCBs) ... £3.95 or £19.50 for 10
1/2 AA with solder tags ... £1.55	Weibau W239W 120ohm 35p each 20p 100+
A A A (H P 1 C)	680ohm 2W metal film resistor 4p 100+ 2p 1000+
180mAh £1.75	Solid carbon resistors very low inductance ideal for RF circuits 27ohm 2W, 68ohm 2W ... 25p each 15p each 100+
Standard charge charges 1 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1.2, 3 or 1.5) may be charged at a time) ... £5.95	We have a range of 0.25w 0.5w 1w and 2w solid carbon resistors, please send SAE for list
High power charges as above but charges the Cs and Ds in 5 hours AAs, Cs and Ds must be charged in 2 or 1s ... £10.95	Intelligent 4 digit alphanumeric (5x7 dot 0.115") LED display 12 pin 0.6 inch wide package Sams type DLR411 ... £2.50 each £2.00 30+ Data sheets £1.00
Special offers, please check for availability	AMD 27256-3 EProms ... £2.00 each £1.25 100+
P cells 3/2 dia x F cell with solder tags 87mm ... £3.95 12s ... £1.30	DIP switch SP30 12 pin (ERG-SDC-3-023) 60p each 10p 100+
1.2 x 1.6 mm dia £1.15	Disk drive boxes for 5.25 disk drive with room for a power supply, light grey plastic ... £3.95
1.2 x 1.6 mm dia with red & black leads 18v ... £5.95	CV2180 gas relay, 30x10mm dia with 3 wire terminals, will also work as a neon light ... 20p each £7.50 per 100
4 cell battery 94x25mm dia (1/2 C cells) ... £5.50	A23 12s battery for car alarms or lighters ... 75p each £50.00 per 100
Computer grade capacitors with screw terminals 38000uf 20v ... £2.50	
87000uF 1.0A ... £1.95 6.8000uF 415v ... £2.95 1000uF 16v ... £1.50 58000uF 60v ... £1.95	
7 segment common anode led display 12mm ... £0.15	
LM2931A 1.5 0 low drop out 5v regulator 10220 package ... £0.85	
7812 and 7912 12v IA regulators ... £20.00 per 100	
LM337K 103 case variable regulator ... £1.60 (£1.10 100+)	
6AAs FF 1 low leakage current S8873 ... £12.95 each (£5.95 10+, £7.95 100+)	
BS250 P channel mosfet 40 15 BC559 transistor ... £3.95 per 100	
74LS05 hex inverter £10.00 per 100 Used 8718 Microcontroller ... £3.50	

All products advertised are new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors etc. Rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards p&p. VAT included in all prices.

**JPG Electronics, 276-278 Chatsworth Road, Chesterfield S40 2BH**  
Access/Visa **(0246) 211202** Callers welcome

CIRCLE NO. 122 ON REPLY CARD

# Custom metalwork — good & quick!


Plus a wide range of rack-mounting cases etc. from stock.  
Send for our new Product Catalogue.



**IPK Broadcast Systems**  
3 Darwin Close Reading Berks RG2 0TB  
Tel: (0734) 311030 Fax: (0734) 313836

CIRCLE NO. 123 ON REPLY CARD

## SYSTEM 200 DEVICE PROGRAMMER

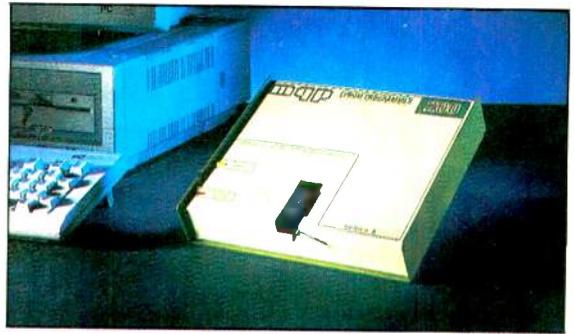

**SYSTEM:** Programs 24,28,32 pin EPROMS, EEPROMS, FLASH and Emulators as standard, quickly, reliably and at low cost.

Expandable to cover virtually any programmable part including serial E<sup>2</sup>, PALS, GALS, EPLD's and microcontrollers from all manufacturers.

**DESIGN:** Not a plug in card but connecting to the PC serial or parallel port; it comes complete with powerful yet easy to control software, cable and manual.

**SUPPORT:** UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.



**MOP ELECTRONICS Ltd.**

Park Road Centre  
Malmesbury, Wiltshire. SN16 0BX. UK  
TEL. 0666 825146 FAX. 0666 825141



**ASK FOR FREE INFORMATION PACK**

GERMANY 089/4602071  
NORWAY 0702-17890  
ITALY 02 92 10 35 54  
FRANCE (1)69.30.13.79  
Also from VEROSPEED UK

CIRCLE NO. 124 ON REPLY CARD

# M & B RADIO (LEEDS)

THE NORTH'S LEADING USED TEST/EQUIPMENT DEALER

### OSCILLOSCOPES

TEKTRONIX 2445A 150MHz GPIB	£1500
TEKTRONIX 475 200MHz DUAL TRACE WITH PROBES	£400
TEKTRONIX 466 100MHz STORAGE	£395
TEKTRONIX SC504/TM503/DM501 PORTABLE 80MHz SCOPE + DVM	£650
KIKUSUI CO6100 100MHz 5 CHANNEL	£500
IWATSUI S54121 100MHz 4 TRACE CURSOR READOUT	£900
HITACHI V233 20MHz DUAL TRACE WITH MANUAL	£225
GOULD OS4000 10MHz DIGITAL STORAGE	£195
GOULD OS250B 15MHz DUAL TRACE	£135
FARNELL DT C12 12MHz DUAL TRACE/COMPONENT TESTER	£175
FARNELL DT 1215 12MHz DUAL TRACE	£195
HP 1722B 275MHz MICROPROCESSOR CAL MEASUREMENTS	£750
HP 1725A 275MHz OSCILLOSCOPES (AS NEW)	£600
TEKTRONIX 465A/B 100MHz DUAL TRACE PRICES FROM	£300
TEKTRONIX 2205 20MHz	£295
BECKMAN 9020 20MHz DUAL TRACE	£225
GOULD OS300 20MHz DUAL TRACE	£195
TELEQUIPMENT D34 15MHz PORTABLE	£150
NICOLET 4094A DIGITAL OSCILLOSCOPE	£500

### SIGNAL GENERATORS

MARCONI 2019 80KHZ TO 1040MHZ	£1900
MARCONI 2018A 80KHZ TO 520MHZ	£1250
MARCONI 2018 80KHZ TO 520MHZ SYNTHESIZED	£750
MARCONI 2008 10KHZ TO 520MHZ INC RF PROBE KIT MANUAL	£300
MARCONI 2015/12171 SYNCHRONIZER 10MHZ TO 520MHZ (AS NEW)	£325
HP 8640B 500KHZ TO 550MHZ OPT 001	£650
HP 8616A 1.8GHZ TO 4.5GHZ	£295
HP 3310B 005GHZ TO 5MHZ	£250
HP 4204A 10KHZ TO 10MHz OSCILLATOR	£250
HP 8165A 001HZ TO 50MHz PROG SIGNAL GENERATOR	£950
ADRET 740A 10KHZ TO 1.1GHZ SYNTHESIZED	£1500
FARNELL SSG2000 10KHZ TO 2GHZ SYNTHESIZED (AS NEW)	£2250
FARNELL SSG1000 10KHZ TO 1GHZ SYNTHESIZED (AS NEW)	£1500
FARNELL SSG520 10MHZ TO 520MHZ & TTS 520 TRANSMISSION TEST SET	£800
ADRET 20230A 1MHz SYNTHESIZED SOURCE	£195
POLRAD 1104ET 1.8 TO 4.6GHZ WITH MODULATOR	£400
RHODE & SCHWARZ TYPE SMC 1.48GHZ TO 12.6GHZ	£500
RHODE & SCHWARZ NOISE GENERATOR 1 TO 1000MHz SKTU (NEW)	£195
WAVETEK 193 20MHz SWEEP FUNCTION GENERATOR	£150
MARCONI 2020 50KHZ TO 520MHz SYNTHESIZED	£500
MARCONI 2000 20KHZ TO 20KHZ WITH METERED ATTENUATOR	£125
TEXSCAN VS60B SWEEP GENERATOR	£250
SAYROSA FREQUENCY OSCILLATOR MA30 10KHZ TO 10KHZ	£250
EXACT 628 20MHz PULSE/SWEEP FUNCTION GENERATOR	£650
GIGA GR1101A 12 TO 18GHZ PULSE GENERATOR (NEW)	£750

### TEST EQUIPMENT

EPFRATOM FRT AOMIC FREQUENCY STANDARD	£2500
HP 5065A RUBIDIUM VAPOR FREQUENCY STANDARD	£2000

MARCONI 2955 COMMUNICATIONS TEST SET	£3000
MARCONI 2305 MODULATION METER	£2000
MARCONI TF2300B MODULATION METER	£395
MARCONI 2331 DISTORTION FACTOR METER	£250
FARNELL LA520 RF AMPLIFIER 1.5MHZ TO 520MHZ	£150
FARNELL LF44 AUDIO OSCILLATOR	£200
FARNELL TM8 TRUE RMS SAMPLING RF METER (AS NEW) 1GHZ	£350
TEKTRONIX 521A PAL VECTORSCOPE	£1000
DYMAR 2005 AF POWER METER	£225
BIRD TENULINE B343 100W 6DB ATTENUATOR (NEW)	£100
NARDA 3022 B1 DIRECTIONAL COUPLER 1GHZ TO 4GHZ	£250
NARDA 3001 30 DIRECTIONAL COUPLER 400MHZ TO 960MHZ	£300
AVO RM215 L/2 AC/DC BREAKDOWN TESTER	£300
ROTEK AC/DC PRECISION CALIBRATOR	£650
EXACT 334 CURRENT PRECISION CALIBRATOR	£195
HP 11667A POWER SPLITTER (NEW) 18GHZ	£400
HP 11683A POWER METER CALIBRATOR	£300
NARDA 769/6 150W 6DB HIGH POWER ATT (NEW)	£100
RACAL DANA 5002 WIDEBAND LEVEL METER	£700
RACAL DANA 9303 TRUE RMS RF LEVEL METER	£700
RACAL DANA 4000 MICROPROCESSING DVM	£100
RACAL DANA 9000 MICROPROCESSING TIMER CC UNITS	£275
RACAL DANA 488 IEEE STD 488 BUS ANALYSER	£250
RACAL DANA 1002 THERMAL PRINTER	£150
RACAL DANA 9302 RF MILLIVOLTMETER 10KHZ TO 1500MHZ	£400
RACAL 9301A RF MILLIVOLTMETER 10KHZ TO 1500MHz	£250
RACAL 9008 MODULATION METER	£300
RACAL DANA 1998 1.3GHZ FREQ COUNTER/TIMER	£750
RACAL 9841 3GHZ FREQUENCY COUNTER	£225
RACAL 9921 3GHZ FREQUENCY COUNTER	£400
RACAL 9903 TIMER COUNTER	£100
RACAL 9904 TIMER COUNTER	£150
RACAL 9915 10HZ TO 520MHz FREQUENCY COUNTER	£150
RACAL 9919 1.1GHZ FREQUENCY COUNTER/TIMER	£325
HP 435A POWER METER 9402H HEAD	£650
BICC/TEST T43 1M CABLE TEST SET	£250
BICC/TEST 437 CABLE LOGGER	£250
FARNELL B3075 POWER SUPPLY 0.30VOLT 5AMP	£45
FARNELL B3020 POWER SUPPLY 0.30VOLT 20AMF	£100
RACAL 9063 TWO TONE GENERATOR	£250
FARNELL ELECTRONIC LOAD RB1030/35	£495
FARNELL TRIPLE OUTPUT POWER SUPPLY TOPS 33	£225
FARNELL 15005 SAMP POWER SUPPLY	£95
MARCONI TF2910/4 TV LINEAR DISTORTION ANALYSER	£750
MARCONI TF2913 TEST LINE GENERATOR + INSERTER	£750
MARCONI TF2914A INSERTION SIGNAL ANALYSER	£750
FLUKE 103A FREQUENCY COMPARATOR	£200
FEEDBACK SSO603 SINE/SQUARE AUDIO OSCILLATOR	£85
FEEDBACK 602 VARIABLE SWEEP OSCILLATOR	£145
FEEDBACK SF611 12MHz SWEEP FUNCTION GENERATOR	£245
FEEDBACK TFA TRANSFER FUNCTION ANALYSER	£295
FEEDBACK EW604 ELECTRONIC WATTMETER	£195
HP 3455A HIGH STABILITY VOLTMETER GPIB	£1200
HP 8405A VECTOR VOLTMETER & ACCESSORIES	£850
HP 8406A COMB FREQUENCY GENERATOR	£250
HP 3448D DIGITAL MULTIMETER	£400
HP 3466A DIGITAL MULTIMETER	£200
HP 8750A STORAGE NORMALIZER	£395
HP 3400A TRUE RMS VOLTMETER	£145

HP 3463C TRUE RMS VOLTMETER DIGITAL	£150
HP 394A VARIABLE ATTENUATOR 1GHZ TO 2GHZ	£85
HP 3406A SAMPLING VOLTMETER	£225
WALCON 500B/521A UNIVERSAL TEST SYSTEM	£650
TEKTRONIX 574 CURVE TRACER & 172 PROGRAMMEABLE TEST FIXTURE	£200
PSI A1001 WAVEFORM GENERATOR	£225
HP 10529A LOGIC COMPARATOR	£85
IWATSUI G100 FREQUENCY COUNTER	£225
HP 5006A SIGNATURE ANALYSER	£395
KEMO DPM1 PHASE METER 1HZ TO 100KHZ	£150
WIDE KEIRN CT496 LCR BRIDGE PORTABLE	£95
MARCONI TF2700 LCR BRIDGE PRICES FROM	£95
PHILIPS PM825A DUAL PEN RECORDER	£300
HP 334A DISTORTION METER	£250
FLUKE 3330B PROG CONSTANT CURRENT/VOLTAGE CALIBRATOR	£750
UNAOHM FIELD STRENGTH METER	£65
HP 5004A SIGNATURE ANALYSER	£200
WIRD 43 THROUGHLINE WATTMETERS	£145
PACIFIC MEASUREMENTS 103A RF POWER METER 1MHZ TO 18GHZ	£450
PHILIPS PM565 VIDEO WAVEFORM MONITOR	£225
BALLANTINE 6125C PROG TIME/AMPLITUDE TESTSET	£500
FERROGRAN 8RTS/A/TU1 AUDIO TESTSET	£300
TEKTRONIX 1421 VECTOR SCOPE	£400
TEKTRONIX 528A VIDEO WAVEFORM MONITOR	£300
ALTECH 533K-11 CALIBRATOR	£400
SIEMENS 2233 PSOPHOMETER (NEW)	£500

### SPECTRUM ANALYSERS

HP 8558B 10MHz TO 1.5GHZ WITH 182T MAINFRAME	£1800
HP 141T 8552B IF 8554B/8553B RF UNITS	£2000
HP 3580A 5KHZ TO 50KHZ ANALYSER (NEW)	£175
B&K 2133 AUDIO ANALYSER 1HZ TO 20KHZ	£2750
TEKTRONIX 2370 110MHz ANALYSER	£950
HP 141T 8553B/8552B 110MHz WITH 8443A TRACKING GENERATOR (AS NEW)	£2000
HP 8444A TRACKING GENERATOR 0.5 TO 1300MHz	£1000
TEKTRONIX 492 50KHZ TO 18GHZ PORTABLE	£5500
TEKTRONIX 492AP 10KHZ TO 22GHZ (325GHZ)	£7000
HP 3581A WAVE ANALYSER 15KHZ TO 50KHZ (AS NEW)	£850
HP 8585A NETWORK ANALYSER 500KHZ TO 1300MHz	£5000

### RADIO EQUIPMENT

RACAL RA1797 HF RECEIVERS	£1600
RACAL RA2309B/RA2395 90MHz TO 400MHz	£900
PHILIPS 88MHz TO 108MHz BROADCAST TX 10KW	£3000
EDDYSTONE 9905 UHF 250 TO 850MHz	£159
EDDYSTONE 19903 RECEIVER 25 TO 500MHz	£450
ROCKWELL COLLINS HF801AA EXCITER (NEW)	£200
RACAL SYNICAL 30 TRANSCEIVERS	£300
RACAL RA1799/MA1107 HF RECEIVER	£1700
REDIFON R500 SYNTHESIZED HF RECEIVER	£500
MARCONI HF DRIVE UNITS SYNTHESIZED	£300



### BULK PURCHASE SPECIALS

MARCONI I101 RC OSCILLATOR 20HZ TO 20KHZ	£45
ADCOLLA 777 DESOLDERING STATION	£100

ALL PRICES PLUS VAT AND CARRIAGE


**86 Bishopgate Street, Leeds LS1 4BB**  
Tel: (0532) 435649 Fax: (0532) 426881

# Design and Verify Circuits. Fast.

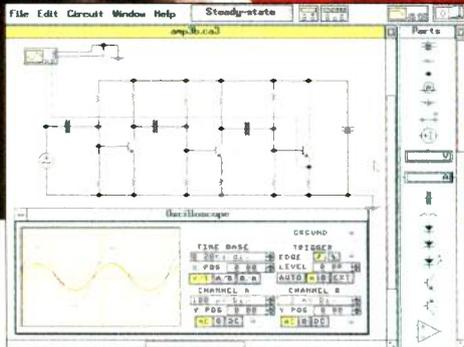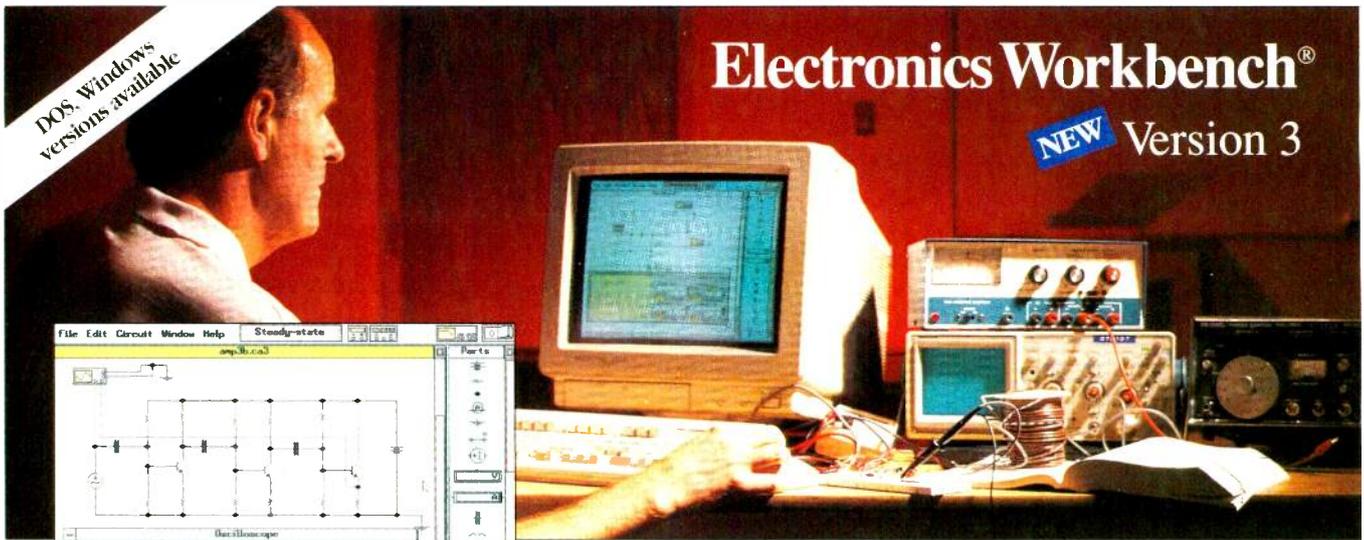
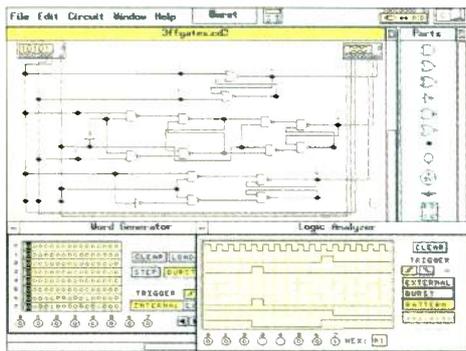
## Analog Module includes:

- complete control over all component values
- ideal and real-world models for active components
- resistors, capacitors, inductors, transformers, relays, diodes, Zener diodes, LEDs, BJTs, opamps, bulbs, fuses, JFETs, and MOSFETs
- manual, time-delay, voltage-controlled and current-controlled switches
- independent, voltage-controlled and current-controlled sources
- multimeter
- function generator (1 Hz to 1 GHz)
- dual-trace oscilloscope (1 Hz to 1 GHz)
- Bode plotter (1 MHz to 10 GHz)
- SPICE simulation of transient and steady-state response



## Digital Module includes:

- fast simulation of ideal components
- AND, OR, XOR, NOT, NAND and NOR gates
- RS, JK and D flip-flops
- LED probes, half-adders, switches and seven-segment displays
- word generator (16 eight-bit words)
- logic analyzer (eight-channel)
- logic converter (converts among gates, truth table and Boolean representations)

Electronics Workbench®

NEW Version 3


## Complement Your Test Bench

Here's why Electronics Workbench belongs on *your* test bench: Wires route themselves. Connections are always perfect. And the simulated components and test instruments work just like the real thing. The instruments are indestructible and the parts bin holds an unlimited supply of each component. The result: thousands of electronics professionals and hobbyists save precious time and money. **Over 90% would recommend it to their friends and colleagues.** Electronics Workbench: the ideal, affordable tool to design and verify your analog and digital circuits before you breadboard.

And now the best is even better - Electronics Workbench Version 3.0 is here. It simulates more and bigger circuits, and sets the standard for ease of use. Guaranteed!
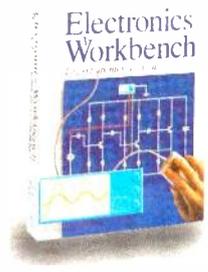
## NEW Features in Version 3

- new components include JFETs, MOSFETs, voltage-controlled and current-controlled sources and manual, time-delay, voltage-controlled and current-controlled switches
- real-world models for opamps, BJTs, JFETs, MOSFETs and diodes - over 100 models available
- MS-DOS version now supports up to 16 MB of RAM for simulation of bigger circuits
- new Microsoft® Windows™ version available
- technical support now also available on CompuServe®



Just £199!

# Electronics Workbench®

The electronics lab in a computer™

## Call: (0827) 66212



ROBINSON MARSHALL (EUROPE) LTD.  
17 Middle Entry, Tamworth, Staffordshire, England B79 7NJ  
Fax: (0827) 58533

\*30-day money-back guarantee.

Shipping charges - UK £4.99. All prices are plus V.A.T.  
All trademarks are the property of their respective owners.




CIRCLE NO. 126 ON REPLY CARD

**DO YOU HAVE A £100 CIRCUIT? EACH MONTH'S TOP CIRCUIT IDEA AUTHOR WILL RECEIVE £100. ALL OTHER PUBLISHED IDEAS WILL BE WORTH £25. WE ARE LOOKING FOR INGENUITY AND ORIGINALITY IN THE USE OF MODERN COMPONENTS**

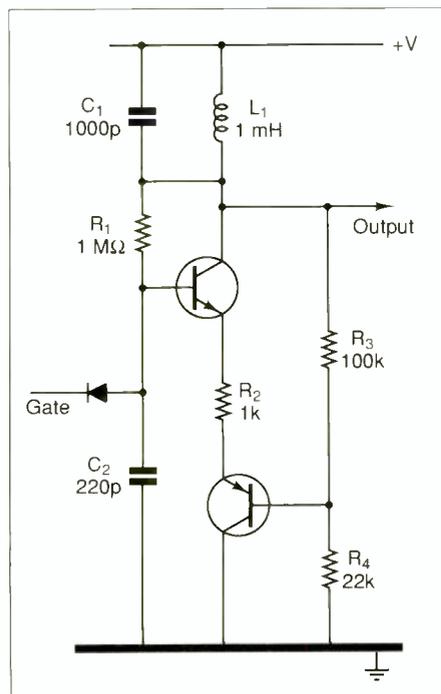
## Cascode oscillator

This is a simple oscillator, but is very reliable and exhibits many of the features of a near-perfect circuit. It uses a two-terminal coil with no taps, self starts and draws only 1mA at 12V, the drive being inherently Class D. Output impedance is small and output swing large. Over the supply-voltage range of 2-24V, frequency stability and waveform purity are exceptional. Taking the gate input to 0V starts the oscillator at the same point in the cycle and the earthy end of  $R_4$  has a similar, but reversed effect. Tuned circuit  $L_1C_2$  determines frequency – 160kHz in the case shown – and the time constant  $R_1C_2$  must be longer than the period.

**J J Hyland**  
Glazertron Ltd  
Rochester  
Kent



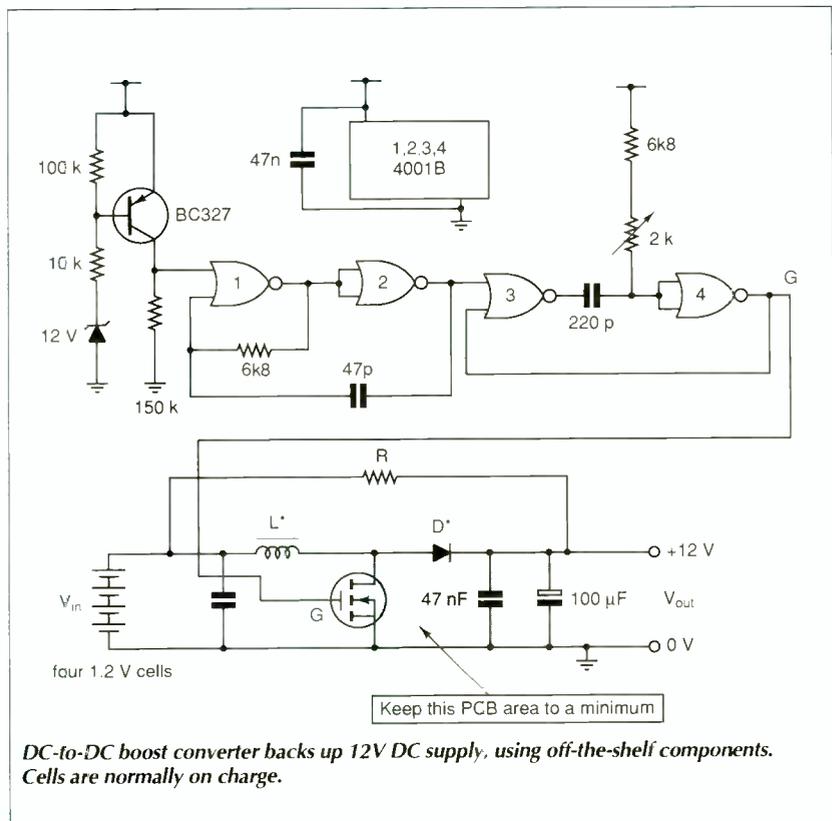Reliable and frugal oscillator has low output impedance and is easily gated to start consistently at the same point.



DC-to-DC boost converter backs up 12V DC supply, using off-the-shelf components. Cells are normally on charge.

## Battery backup

This provides 12V DC to an alarm clock when the mains-derived supply fails, the 12V coming from four 1.2V cells in a boost converter. The circuit is simply connected in parallel with the existing DC supply, which maintains charge on the cells through R.

If the mains supply falls, the BC327 circuitry detects the drop and turns on the 1MHz multivibrator of gates 1 and 2, which triggers the monostable of gates 3 and 4, the output pulse of which is variable in width.

The pulse, G, drives the converter mosfet, a low-voltage, low- $R_{DS(on)}$  type

such as the BUZ10. Diode D is an ultra-fast device (an MUR110 was used) and inductor L is five turns of doubled 0.2mm diameter enamelled-copper wire on a ferrite bead, inductance being 20µH. It must not enter saturation.

With a 100kΩ load, 3V from the cells gives 12V output, this increasing to 5V for loads of 1kΩ or less down to a practical limit of a 220Ω load (around 50mA).

**Dominique Bergogne**  
Saint Etienne  
France

# 1GHz frequency divider


To extend the frequency range of a 10MHz counter frequency meter to 1GHz, the input frequency must be divided by 100, to give a convenient reading. The frequency divider used in PLL tuners, shown as IC<sub>1</sub> in the circuit diagram, divides by 64, so that a further division of 25/16 remains to be carried out.

IC<sub>2a,b</sub> are a dual binary counter, which would normally count to 256, but which is

reset at a count of 25 by the fed-back A, D and E outputs via And gates IC<sub>3a,b</sub>, as shown in the timing diagram. Outputs B, C and A are further used by IC<sub>4</sub> and IC<sub>3c</sub> to allow 16 input pulses to proceed to the output during this time, so that the division ratio is 25/16.

**W Dijkstra**  
Waalre  
The Netherlands

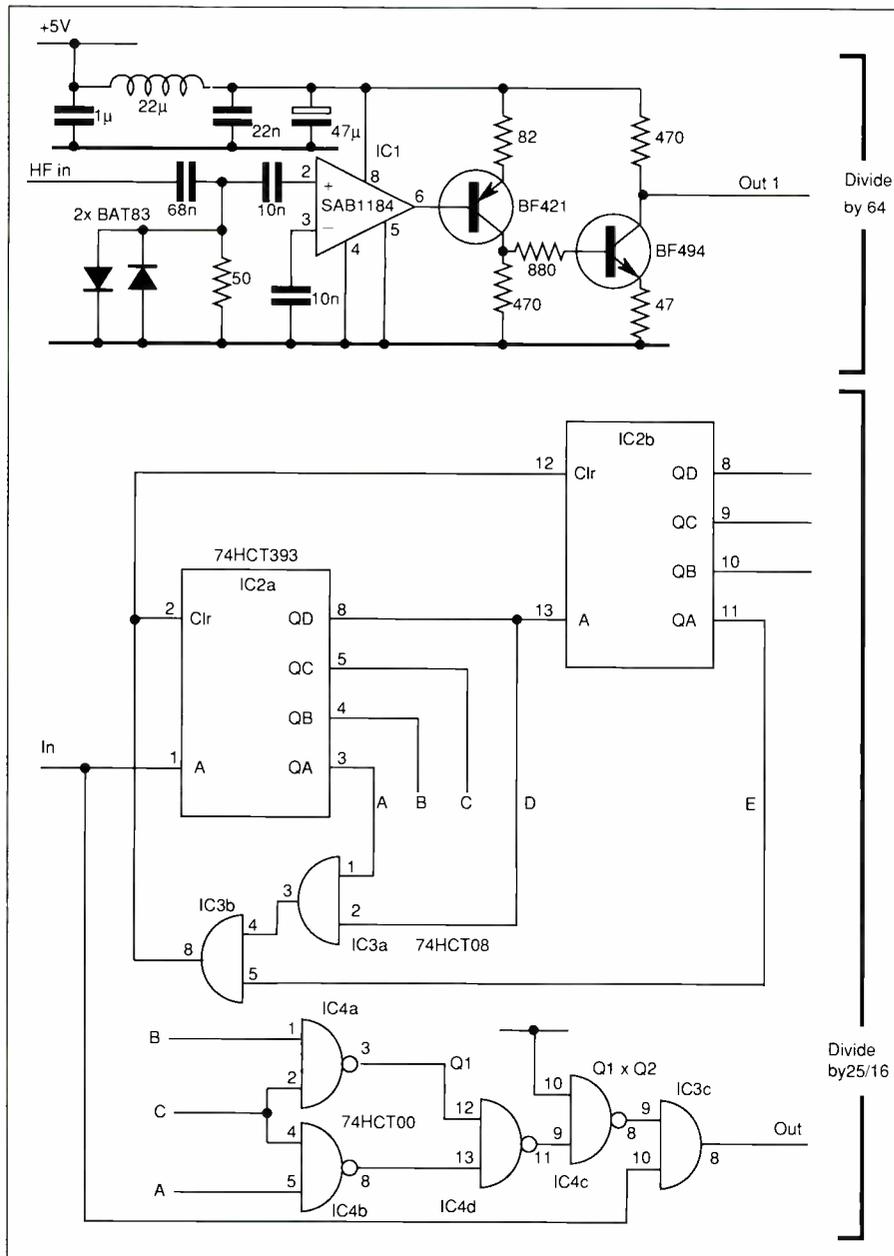*Wide-band 64 divider, followed by 25/16 divider, gives division by 100 to extend measuring range of lower-frequency counter frequency meter.*



# Remote motor control

Using only the two DC power-supply leads, this circuit switches the motors in a remote unit such as a television camera over a distance up to 100m or more with a different control signal. An LM3914 bar-graph IC in dot mode forms the core of the system, its input being the "raw" power supply itself, varied in steps at the remote control point.

Since the power line varies, a voltage regulator restores the correct level to the control circuitry, the type depending on the motors. Eight op-amps in two LM324 quads, boosted by transistor pairs if necessary, select motors and direction. Op-amp IC<sub>4a</sub> amplifies the IC<sub>3</sub> reference voltage and reapplies it to the internal resistor chain after adjustment to about 7V by RV<sub>1</sub>. This output is also used as adjustable offset to IC<sub>4b</sub>.

Resistors R<sub>28,29</sub> apply line changes to the input op-amp. Figure 2 shows the selector circuit, in which a switched resistor chain varies the output of a regulator from 13V to 15V.


To set up, adjust RV<sub>1</sub> so that pin 12 of the bar graph is selected with 15V applied to the input (a led array on the bar graph output assists here). Then, with 13V applied, adjust RV<sub>2</sub> to select pin 1, repeating the process if necessary.

For greater distances than around 100m, a 4-20mA current loop could be used, R<sub>28</sub> being removed.

**Ken Bedwell**  
Rees Instruments Ltd  
Godalming  
Surrey

*Shown top-right, Fig. 1. Bar-graph IC controls motors in response to remote signals carried on power lines.*

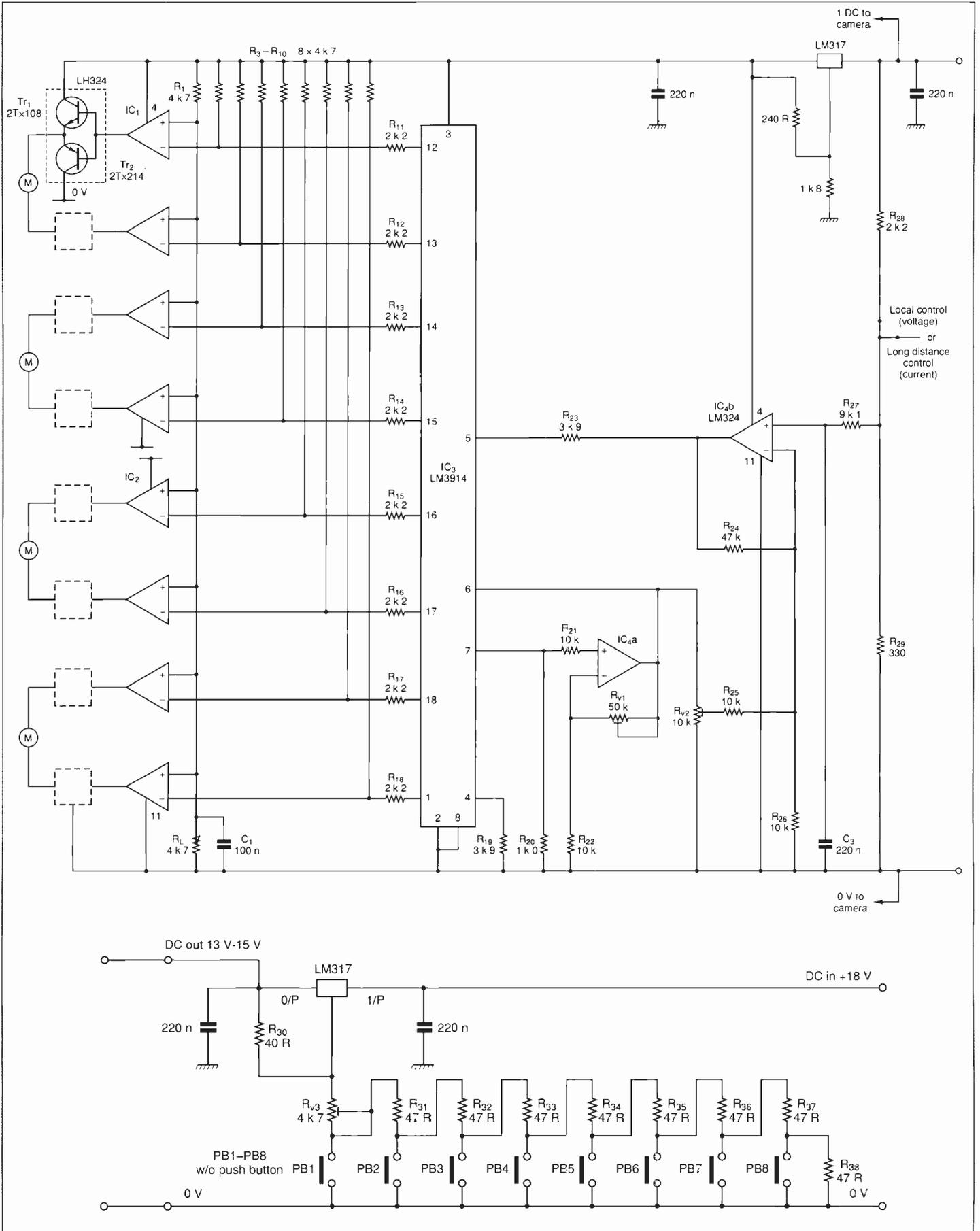*Shown right, Fig. 2. Remote selector circuit for distances up to around 100m; for greater distances, a current loop would be better.*



## Simple DC modulator

In addition to its requirement for only a single switch, this modulator does not isolate the input. As the feedback loop of the op-amp in Fig.1 is varied by  $v_{mod}$ , its gain changes

and is given by  $(R_2 + R_4 + R_2R_4/R_3)/R_1$ . The output is not, however, symmetrical about zero. In Fig.2, the op-amp forms either an inverting amplifier or a voltage follower, depending on  $v_{mod}$ , to give an output

about zero.  
**N I Lavrantiev**  
*Schiulkovo*  
*Moscow Region*

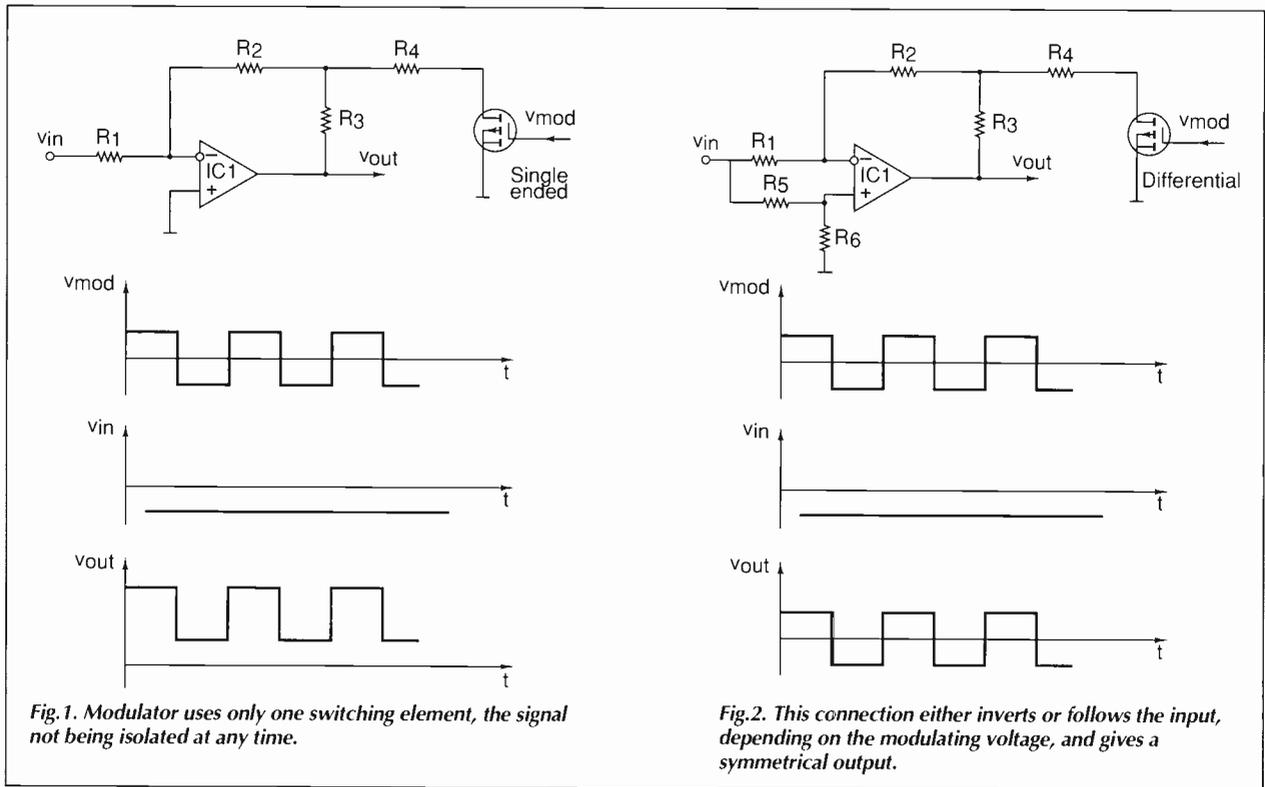


Fig.1. Modulator uses only one switching element, the signal not being isolated at any time.

Fig.2. This connection either inverts or follows the input, depending on the modulating voltage, and gives a symmetrical output.

## Electrolytic ESR tester

In sensitive circuitry, for example in a feedback loop, it is often necessary to know the equivalent series resistance of an electrolytic capacitor. This circuit measures ESR quickly and simply, assuming access to a digital storage oscilloscope.

Operation is simple: press the push-button switch and view the DSO trace. Calculate ESR from  $ESR=(v_1/v_2)-1$  in ohms, the two voltages being those indicated in Fig. 2.

Replacement of the pushbutton switch with a logic switched mosfet would eliminate switch bounce effects. It would also allow operation at higher voltages for greater signal output. The channel resistance and self capacitance of the device need to be taken into account however.

**A M Wilkes**  
*Glasgow*

### Faulty circuit

There was an unfortunate printing error in my circuit idea (*EW+WW*, November 1993). Propagation delay decreases and not increases as  $V_{cc}$  is increased.

This is fundamental to understanding the whole design.

**Laurence Richardson**  
*Horsham, Surrey*

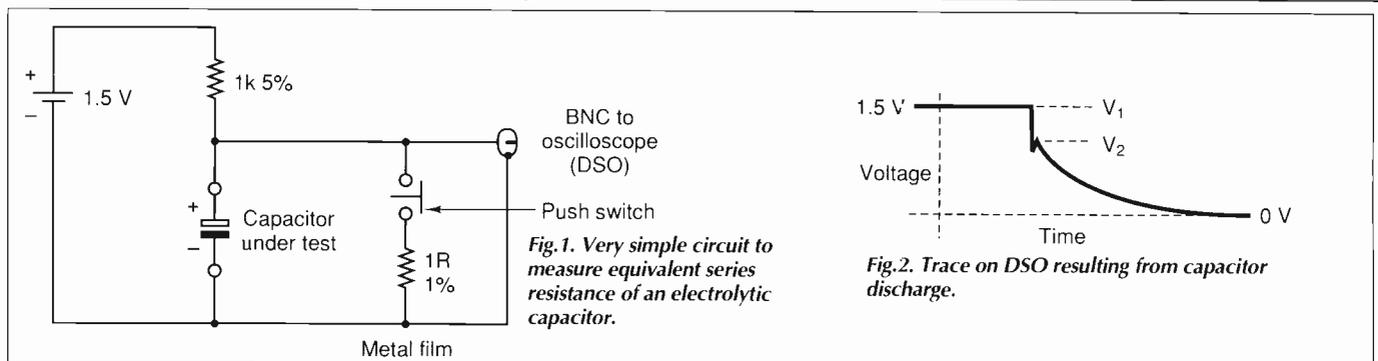


Fig.1. Very simple circuit to measure equivalent series resistance of an electrolytic capacitor.

Fig.2. Trace on DSO resulting from capacitor discharge.

**SMALL SELECTION ONLY LISTED - EXPORT TRADE AND QUANTITY DISCOUNTS - RING US FOR YOUR REQUIREMENTS WHICH MAY BE IN STOCK**

Marconi TF2008 - AM-FM signal generator - Also sweeper - 10Kc/s - 510Mc/s - from £350 tested to £500 as new with manual - probe kit in wooden carrying box.  
 HP Frequency comb generator type 8406A - £400  
 HP Sampling Voltmeter (Broadband) type 3406A - £200  
 HP Vector Voltmeter type 8405A - £400 to £600 - old or new colour.  
 HP Synthesiser/signal generator type 8672A - 2 to 18GHz £4000  
 HP Oscillographic recorder type 7404A - 4 track - £350  
 HP Plotter type 9872B - 4 pen - £300  
 HP Sweeper Oscillators type 8690 A & B + plug-ins from 10Mc/s to 18GHz also 18 40GHz P O R  
 HP Network Analyser type 8407A - 8412A + 8601A - 100Kc/s - 110Mc/s - £500-£1000.  
 HP Down Converter type 11710B - 01-11Mc/s - £450  
 HP Pulse Modulator type 11720A - 2-18GHz - £1000.  
 HP Modulator type 8403A - £100-£200  
 HP Pin Modulators for above-many different frequencies - £150  
 HP Counter type 5342A - 18GHz - LED readout - £1500  
 HP Signal Generator type 8640B - Opt1001 + 003 - 5-512Mc/s AM/FM - £1000  
 HP Amplifier type 8447A - 1-400Mc/s £200 - HP8447F 1-1300Mc/s £400  
 HP Frequency Counter type 5340A - 18GHz £1000 - rear output £800.  
 HP 8410 - A - B - C Network Analyser 110Mc/s to 12GHz or 18GHz - plus most other units and displays used in this set-up - 8411A - 8412 - 8413 - 8414 - 8418 - 8740 - 8741 - 8742 - 8743 - 8746 - 8650. From £1000  
 HP Signal Generator type 8660C - 1-2600Mc/s. AM/FM - £3000. 1300Mc/s £2000  
 HP Signal Generator type 8656A - 0.1-990Mc/s. AM/FM - £2000.  
 HP 8699B Sweep Pl - 0.1-4GHz £750 - HP8690B Mainframe £250  
 Racal/Dana 9301A-9302 RF Millivoltmeter - 1.5-2GHz - £250-£400  
 Racal/Dana Counters 9915M - 9916 - 9917 - 9921 - £150 to £450 Fitted FX standards  
 Racal/Dana Modulation Meter type 9009 - 8Mc/s - 1.5GHz - £250.  
 Racal - SG Brown Comprehensive Headset Tester (with artificial head) Z1A200/1 - £350.  
 Marconi AF Power Meter type 893B - £200.  
 Marconi RCL Bridge type TF2700 - £150.  
 Marconi/Saunders Signal Sources type - 6058B - 6070A - 6055B - 6059A - 6057B - 6056 - £250-£350. 400Mc/s to 18GHz  
 Marconi TF1245 Circuit magnification meter + 1246 & 1247 Oscillators - £100-£300  
 Marconi microwave 6600A sweep osc. mainframe with 6650 Pl - 18-26.5GHz or 6651 Pl - 26.5-40GHz - £1000 or Pl only £600  
 Marconi distortion meter type TF2331 - £150. TF2331A - £200.  
 Microwave Systems MOS/3600 Microwave frequency stabilizer - 1GHz to 40GHz £1k  
 Tektronix Plug-ins 7A13 - 7A14 - 7A18 - 7A24 - 7A26 - 7A11 - 7M11 - 7S11 - 7D10 - 7S12 - S1 - S2 - S6 - S52 - PG506 - SC504 - SG502 - SG503 - SG504 - DC503 - DC508 - DD501 - WR501 - DM501A - FG501A - TG501 - PG502 - DC505A - FG504 - P.O.R  
 Ailtech Stoddart receiver type 17-27A - 01-32Mc/s - £2500  
 Ailtech Stoddart receiver type 37/57 - 30-1000Mc/s - £2500.  
 Ailtech Stoddart receiver type NM65T - 1 to 10GHz - £1500.  
 Gould J3B Test oscillator + manual - £200  
 Infra-red Binoculars in fibre-glass carrying case - tested - £100. Infra-red AFV sights £100.  
 ACL Field Intensity meter receiver type SR - 209 - 6. Plugs-ins from 5Mc/s to 4GHz - P.O.R  
 Tektronix 491 spectrum analyser - 1.5GHz-40GHz - as new - £1000 or 10Mc/s 40GHz  
 Tektronix Mainframes - 7603 - 7623A - 7633 - 7704A - 7844 - 7904 - TM501 - TM503 - TM506 - 7904 - 7834 - 7104.  
 Knott Polyskanner WM1001 + WM5001 + WM3002 + WM4001 - £500.  
 Ailtech 136 Precision test RX + 13505 head 2 - 4GHz - £350.  
 SE Lab Eight Four - FM 4 Channel recorder - £200.  
 Ailtech 757 Spectrum Analyser - 001 22GHz - Digital Storage + Readout - £3000  
 Dranetz 606 Power line disturbance analyser - £250  
 Precision Aneroid barometers - 900-1050Mb - mechanical digit readout with electronic indicator - battery powered. Housed in polished wood carrying box - tested - £100-£200-£250. 1, 2 or 3  
 HP141T SPECTRUM ANALYSERS - ALL NEW COLOURS  
 TESTED WITH OPERATING MANUAL  
 HP141T + 8552A or B IF-8553B RF - 1kHz-110Mc/s-A IF - £1300 or B IF - £1400  
 HP141T + 8552A or B IF-8554B RF - 100kHz-1250Mc/s-A IF - £1400 or B IF - £1500  
 HP141T + 8552A or B IF-8555A RF - 10Mc/s-18GHz-A IF - £2400 or B IF - £2500  
 HP141T + 8552A or B IF-8556A RF - 20Hz, 300kHz-A IF-A IF - £1200 or B IF - £1300  
 HP8443A tracking generator/counter - 100kHz-110Mc/s - £500  
 HP8445B tracking pre-selector DC-18GHz - £750  
 HP ANZ UNITS AVAILABLE SEPARATELY - NEW COLOURS - TESTED.  
 HP141T mainframe - £550 - 8552A IF - £450 - 8552B IF - £550 - 8553B RF - 1kHz-110Mc/s - £550 - 8554B RF - 100kHz-1250Mc/s - £650 - 8555A RF - 10Mc/s-18GHz - £1550  
 HP 3580A LF-spectrum analyser - 5kHz to 50kHz - LED readout - digital storage - £1600 with instruction manual - internal rechargeable battery.  
 Tektronix 7D20 plug-in 2-channel programmable digitizer - 70 Mc/s - for 7000 mainframes - £500 - manual - £50.  
 Datron 1065 Auto Cal digital multimeter with instruction manual - £500  
 Racal MA 259 FX standard. Output 100kc/s-1Mc/s-5Mc/s - internal NiCad battery - £150  
 Aerial array on metal plate 9 x 9 containing 4 aerials plus Narda detector - 100-11GHz. Using N type and SMA plugs & sockets - ex eqpt - £100.  
 EIP 451 microwave pulse counter 18GHz - £1000.  
 Marconi RF Power Amplifier TF2175 - 1.5Mc/s to 520Mc/s with book - £100  
 Marconi 6155A Signal Source - 1 to 2 GHz - LED readout - £600  
 Schlumberger 2741 Programmable Microwave Counter - 10Hz to 7 GHz - £750  
 Schlumberger 2720 Programmable Universal Counter 0 to 1250Mc/s - £600  
 HP 2225CR Thinkjet Printer - £100.  
 TEK 576 Calibration Fixture - 067-0597-99 - £250.  
 HP 8006A Word Generator - £150  
 HP 1645A Data Error Analyser - £150  
 Texscan Rotary Attenuators - BNC/SMA 0.10-60-100DBS - £50-£150  
 HP 809C Slotted Line Carriages - various frequencies to 18GHz - £150 to £300  
 HP 532-536-537 Frequency Meters - various frequencies - £150-£250  
 Barr & Stroud variable filter EF3 0.1Hz - 100kc/s + high pass + low pass - £150  
 S.E. Lab SM215 Mk11 transfer standard voltmeter - 1000 volts.  
 Ailtech Stoddart P7 programmer - £200  
 H.P. 6941B multiprogrammer extender. £100  
 Fluke Y2000 RTD selector + Fluke 1120A IEEE-488-translator + Fluke 2180 RTD digital thermometer + 9 probes. £350 all three items  
 H.P. 6181 DC current source. £150  
 H.P. 59501A - HP-IB isolated D/A power supply programmer  
 H.P. 3438A digital multimeter.  
 H.P. 6177C DC current source. £150.  
 H.P. 6207B DC power supply  
 H.P. 741B AC DC differential voltmeter standard (old colour) £100  
 H.P. 6209B DC power unit.  
 Fluke 80 high voltage divider  
 Fluke 431C high voltage DC supply.  
 Tektronix M2 gated delay calibration fixture. 067-0712-00  
 Tektronix precision DC divider calibration fixture. 067-0503-00  
 Tektronix overdrive recovery calibration fixture. 067-0608-00.  
 Avo VCM163 valve tester + book £300.  
 H.P. 5011T logic trouble shooting kit. £150  
 Marconi TF2163S attenuator - 1GHz. £200  
 PPM 8000 programmable scanner.  
 Fluke 730A DC transfer standard.  
 B&K 481S calibrator head.

B&K 4812 calibrator head.  
 Farnell power unit H60/50 - £400 tested  
 H.P. FX doubler 938A or 940A - £300  
 Racal/Dana 9300 RMS voltmeter - £250  
 H.P. sweeper plug-ins - 86240A - 2-8 GHz - 86260A - 12.4-18GHz - 86260AH03 - 10-15GHz - 86290B - 2-18.6GHz. 86245A 5.9-12.4GHz  
 Tequipment CT71 curve tracer - £200  
 H.P. 461A amplifier - 1kc-150Mc/s - old colour - £100  
 H.P. 8750A storage normalizer.  
 Tektronix oscilloscopes type 2215A - 60Mc/s - c/w book & probe - £400.  
 Tektronix monitor type 604 - £100  
 Marconi TF2330 or TF2330A wave analysers - £100-£150  
 HP5006A Signature Analyser £250 + book  
 HP10783A numeric display. £150  
 HP 3763A error detector. £250.  
 Racal/Dana signal generator 9082 - 1.5-520Mc/s - £800.  
 Racal/Dana signal generator 9082H - 1.5-520Mc/s - £900  
 Claude Lyons Compuline - line condition monitor - in case - LMP1 + LCM1 £500.  
 Efratom Atomic FX standard FRT - FRK - 1-1-5-10Mc/s. £3K tested.  
 Racal 4D recorder - £350 - £450 in carrying bag as new.  
 HP8350A sweep oscillator mainframe + HP11869A RF Pl adaptor - £1500.  
 Ailtech - precision automatic noise figure indicator type 75 - £250.  
 Adret FX synthesizer 2230A - 1Mc/s. £250  
 Tektronix - 7S12-7S14-7T11-7S11-S1-S52-S53  
 Rotek 610 AC/DC calibrator. £2K + book.  
 Marconi TF2512 RF power meter - 10 or 30 watts - 50 ohms - £80.  
 Marconi multiplex tester type 2830  
 Marconi digital simulator type 2828A  
 Marconi channel access switch type 2831  
 Marconi automatic distortion meter type TF2337A - £150  
 Marconi mod meters type TF2304 - £250  
 HP 5240A counter - 10Hz to 12.4GHz - £400.  
 HP 3763A error detector.  
 HP 8016A word generator.  
 HP 489A micro-wave amp - 1-2GHz  
 HP 8565A spectrum analyser - 01-22GHz - £4k  
 HP 5065A rubidium vapour FX standard - £5k.  
 Fluke 893A differential meters - £100 ea  
 Systron Donner counter type 6054B - 20Mc/s-24GHz - LED readout - £1k  
 Takeda Riken TR4120 tracking scope + TR1604P digital memory  
 EG&G Parc model 4001 indicator + 420C signal averager Pl.  
 Systron Donner 6120 counter/timer A + 3 + C inputs - 18GHz - £1k.  
 Racal/Dana 9083 signal source - two tone - £250  
 Systron Donner signal generator 1702 - synthesized to 1GHz - AM/FM.  
 Systron Donner microwave counter 6057 - 18GHz - Nixey tube - £600  
 Racal/Dana synthesized signal generator 9081 - 520Mc/s - AM-FM. £600.  
 Farnell SSG520 synthesized signal generator - 520Mc/s - £500.  
 Farnell TTS520 test set - £500 - both £900  
 Tektronix plug-ins - AM503 - PG501 - PG508 - PS503A  
 Tektronix TM515 mainframe + TM5006 mainframe.  
 Cole power line monitor T1085 - £250  
 Claude Lyons LCM1P line condition monitor - £250  
 Rhodes & Schwarz power signal generator SLRD-280 - 2750Mc/s. £250-£800.  
 Rhodes & Schwarz vector analyser - ZPV + E1 + E3 tuners - 3-2000Mc/s  
 Bell & Howell TMA3000 tape motion analyser - £250.  
 Ball Efratom PTB-100 rubidium standard mounted in Tek Pl.  
 Ball Efratom rubidium standard PT2568-FRKL.  
 Trend Data tester type 100 - £150.  
 Farnell electronic load type RB1030-35.  
 Fairchild interference analyser model EMC-25 - 14kc/s-1GHz.  
 Fluke 1720A instrument controller + keyboard  
 Marconi 2442 - microwave counter - 26.5GHz - £1500  
 Racal/Dana counters - 9904 - 9905 - 9906 - 9915 - 9916 - 9917 - 9921 - 50Mc/s - 3GHz - £100-£450 - all fitted with FX standards  
 B&K 7003 tape recorder - £300.  
 B&K 2425 voltmeter - £150  
 B&K 4921 - 4149 outdoor microphone  
 Wiltron sweeper mainframe 610D - £500  
 HP3200B VHF oscillator - 10-500Mc/s - £200  
 HP3747A selective level measuring set  
 HP3586A selective level meter  
 HP5345A electronic counter.  
 HP4815A RF vector impedance meter c/w probe. £500-£600  
 Marconi TF2092 noise receiver. A, B or C plus filters.  
 Marconi TF2091 noise generator. A, B or C plus filters.  
 Tektronix oscilloscope 485 - 350Mc/s - £500  
 HP180TR, HP182T mainframes £300-£500.  
 Bell & Howell CSM2000B recorders  
 HP5345A automatic frequency converter - 0.15-4GHz.  
 Fluke 8506A thermal RMS digital multimeter.  
 HP3581A wave analyser  
 Phillips panoramic receiver type PM7800 - 1 to 20GHz.  
 Marconi 6700A sweep oscillator + 6730A - 1 to 2GHz.  
 Wiltron scaler network analyser 560 + 3 heads. £1k  
 R&S signal generator SMS - 0.4-104Mc/s - £1500.  
 HP8558B spectrum ANZ Pl - 1-1500Mc/s - o/c - £1000. N/C - £1500 - To fit HP180 series mainframe available - £100 to £500.  
 HP8505A network ANZ + 8503A S parameter test set + 8501A normalizer - £4k.  
 HP8505A network ANZ + 8502A test set - £3k  
 Racal/Dana 9087 signal generator - 1800Mc/s - £2k  
 Racal Dana VLF frequency standard equipment. Tracor receiver type 900A + difference meter type 527E - rubidium standard type 9475 - £2750.  
 Marconi 6960-6960A power meters with 6910 heads - 10Mc/s - 20GHz or 6912 - 30kHz - 4.2GHz - £800-£1000  
 HP8444A-HP8444A opt 59 tracking generator £1k-£2k  
 B&K dual recorder type 2308  
 HP8755A scaler ANZ with heads £1k.  
 Tektronix 475 - 200Mc/s oscilloscopes - £350 less attachments to £500 c/w manual, probes etc.  
 HP signal generators type 626 - 628 - frequency 10GHz - 21GHz  
 HP 432A-435A or B-436A - power meters + powerheads - 10Mc/s-40GHz - £200-£280.  
 HP3730B down converter - £200  
 Bradley oscilloscope calibrator type 192 - £600  
 Spectrascope SD330A LF realtime ANZ - 20Hz - 50kHz - LED readout - tested - £500.  
 HP8620A or 8620C sweep generators - £250 to £1k with IEEE.  
 Barr & Stroud variable filter EF3 0.1Hz-100kc/s + high pass + low pass - £150  
 Tektronix 7L12 analyser - 1Mc/s-1.8GHz - £1500 - 7L14 ANZ - £2k  
 Marconi TF2370 spectrum ANZ - 110Mc/s - £1200-£2k  
 Marconi TF2370 spectrum ANZ + TK2473 FX extender 1250Mc/s + trk gen - £2.5k-£3k  
 Racal receivers - RA17L-RA1217-RA1218-RA1772-RA1792 - P.O.R  
 Systron Donner microwave counter 6057 - 18GHz - nixey tube - £600.  
 HP8614A signal gen 800Mc/s-2.4GHz old colour £200, new colour £400.  
 HP8616A signal gen 1.8GHz-4.5GHz old colour £200, new colour £400

ITEMS BOUGHT FROM HM GOVERNMENT BEING SURPLUS. PRICE IS EX WORKS. S.A.E. FOR ENQUIRIES. PHONE FOR APPOINTMENT OR FOR DEMONSTRATION OF ANY ITEMS. AVAILABILITY OR PRICE CHANGE. VAT AND CARR.. EXTRA  
 ITEMS MARKED TESTED HAVE 30-DAY WARRANTY. WANTED: TEST EQPT - VALVES & SOCKETS - SYNCROS - TRANSMITTING & RECEIVING EQPT. ETC.

**Johns Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. No. (0274) 684007. Fax 651150.**

CIRCLE NO. 127 ON REPLY CARD

## MOTORS - BATTERY 1-12V

3 Different model motors, £1, Order Ref. 35  
Spin to start 3v dc motors for model aircraft etc. 5 for £1, Order Ref. 134  
Cassette motor 1.5-12v powerful speed increases with voltage, £1, Order Ref. 224  
Mini cassette motor 6-9v working, £1, Order Ref. 944.  
High efficiency motor for solar cell working, £1, Order Ref. 643.  
12v motor ex BSR record player, £1, Order Ref. 687.  
9v cassette motor, brushless, £1.50, Order Ref. 1.5P14  
1/4hp 12v dc motor Smiths, £4, Order Ref. 4P22  
1/4hp 12v motor, Smiths, £6, Order Ref. 6P1  
1/4hp 12v motor, Smiths, £8, Order Ref. 8P14  
1/4hp motor (Sinclair C5), £15, Order Ref. 15P8

## MAINS MOTORS WITH GEARBOXES

5rpm 60W £5, Order Ref. 5P54  
40rpm 100W, £6, Order Ref. 6P21  
50rpm 60W, £5, Order Ref. 5P168  
60rpm 60W, £5, Order Ref. 5P171  
110rpm 60W, £5, Order Ref. 5P172  
150rpm 60W, £5, Order Ref. 5P169  
200rpm 60W, £5, Order Ref. 5P216  
500W motor with gearbox & variable speed selector 100rpm upwards, £5, Order Ref. 5P220  
1 rev per 24 hours 2W motor, £1, Order Ref. 89  
1 rev per 12 hours 2W motor, £1, Order Ref. 90  
1 rev per 4 hours 2W motor, £2, Order Ref. 2P239  
1 rev per hour 2W extra small motor, 2 for £1, Order Ref. 500  
1/2 rpm mini motor, £3, Order Ref. 3P64  
1 rpm mini motor, £2, Order Ref. 3P328  
4rpm 2W motor, £1, Order Ref. 446  
15rpm 2W motor, £2, Order Ref. 2P321  
25rpm 2W motor, £2, Order Ref. 2P322  
200rpm 2W motor, £1, Order Ref. 175  
250rpm 2W motor, £1, Order Ref. 750

## MAINS MOTORS

3/4 stack motor with 1/4" spindle, £1, Order Ref. 85  
Motor 1 1/2" stack with good length spindle from each side, £2, Order Ref. 2P55  
Motor 1 1/4" stack with 4" long spindle, £2, Order Ref. 2P203  
Motor by Crompton .06hp but little soiled, £3, Order Ref. 3P4  
Jap made precision motor balanced rotor & reversible, 1500rpm, £2, Order Ref. 2P12  
Tape motor by EMI 2 speed & reversible, £2, Order Ref. 2P70  
1/4hp 1000rpm, £8, Order Ref. 8P7  
Very Powerful Mains Motor, with extra long (2 1/2") shafts extending out each side. Makes it ideal for a reversing arrangement for, as you know, shaded pole motors are not reversible, £3, Order Ref. 3P157

## MOTORS - STEPPER

Mini motor by Philips 12v-7.5 degree step, quite standard data supplied, only £1, Order Ref. 910  
Medium powered Jap made 1.5 degree step, £3, Order Ref. 3P162  
Very powerful motor by American Philips 10-14v 7.5 degree step, £5, Order Ref. 5P81

## LOUDSPEAKERS

2" round 50 ohm coil 1/2W, 2 for £1, Order Ref. 908  
2 1/4" 8 ohm, 2 for £1, Order Ref. 454  
2 1/2" 35 ohm, 2 for £1, Order Ref. 514  
3 1/2" 8 ohm, 2 for £1, Order Ref. 682  
6 1/2" 4 ohm with tweeter, £1, Order Ref. 895  
6 1/2" 6 ohm, £1, Order Ref. 896  
6 1/2" 8 ohm, with tweeter, £1, Order Ref. 897  
6" x 4" 4 ohm, £1, Order Ref. 242  
5" x 3" 15 ohm, £1, Order Ref. 906  
5" x 3" 16 ohm, £1, Order Ref. 725  
6" x 4" 16 ohm, 2 for £1, Order Ref. 684  
8", 15 ohm auxd, £1, Order Ref. 504  
9" x 3" 8 ohm 5", £1, Order Ref. 138  
3" 4 ohm tweeter, £1, Order Ref. 433  
Goodmans 6 1/2" 10W 4 ohm, £2, Order Ref. 2P27  
Horn speaker 4 1/2" 8 ohm, £3, Order Ref. 3P82  
20W 5" by Goodman, £3, Order Ref. 3P145  
20W 4 ohm tweeter, £1.50, Order Ref. 1.8P9  
Amstrad 8" 15W 8 ohm with matching tweeter, £4, Order Ref. 4P57  
Cased pair of stereo speakers by Bush 4 ohm £5 per pair, Order Ref. 5P141  
Double wound voice coil 25W, ITT, £7, Order Ref. 7P12  
Bulkhead speaker, metal cased, £10, Order Ref. 1043  
25W 2 way crossover, 2 for £1, Order Ref. 22  
40W 3 way crossover, £1, Order Ref. 23

## MONITORS AND BITS

Philips 9" high resolution monitor, £15, Order Ref. 15P1  
Metal case for the above Philips monitor, £12, Order Ref. 12P3  
Philips 9" high resolution tube Ref. M24 306W, £12, Order Ref. 12P7  
6" electrostatic monitor tube Ref. SE5J31, £10, Order Ref. 10P104  
Mini scope tube face size 2"x2 1/2", electrostatic 3v heater 1Kv in new metal shield, £10, Order Ref. 10P73

## SOME POPULAR BARGAINS

LCD 3 1/2 DIGIT PANEL METER, this is a multi range voltmeter/ammeter using the A-D converter chip 7106 to provide 5 ranges each of volts and amps. Supplied with full data sheet. Special snip price of £12, Order Ref. 12P19  
12V-0-12V PCB MOUNTING MAINS TRANSFORMER, normal 230v primary and conventional open winding construction, £1, Order Ref. 938

AMSTRAD 3" DISK DRIVE, brand new. Standard replacement or why not have an extra one? £20, Order Ref. 20P28

THIS COULD SAVE YOU EXPENSIVE BATTERIES, an in-car unit for operating 6v radio, cassette layer, etc from car lighter socket, £2, Order Ref. 2P318

MEDICINE CUPBOARD ALARM, or it could be used to warn when any cupboard door is opened, built and neatly cased requires only a battery, £3, Order Ref. 3P155

FULLY ENCLOSED MAINS TRANSFORMER, on a 2m 3 core lead terminating with a 13A plug. Secondary rated at 6v 4A. Brought out on a well insulated push on tags, £3, Order Ref. 3P152, Ditto but 8A, Order Ref. 4P69

DON'T LET IT OVERFLOW, be it bath, sink, cellar, sump or any other thing that could flood. This device will tell you when the water has risen to the pre-set level. Adjustable over quite a useful range, neatly cased for wall mounting, ready to work when battery fitted, £3, Order Ref. 3P156

DIGITAL MULTI TESTER MG3800, single switching covers 30 ranges including 20A ac and dc 10meg input impedance, 3 1/2 LCD display. Complete with lead. Currently advertised by many dealers at nearly £40, our price only £25, Order Ref. 25P14

ANALOGUE TESTER, input impedance 2K ohms per volt. It has 14 ranges, ac volts 0-500 dc volts 0-500, dc current 500 micro amps at 250 milliamper, resistance 0-1meg-ohm, decibels 20 56dB. Fitted diode protection, overall size 90x60x30mm. Complete with test prods, price £7.50, Order Ref. 7.5P8

LCD CLOCK MODULE, 1.5v battery operated, fits nicely into our 50p project box, Order Ref. 876. Only £2, Order Ref. 2P307

SENTINEL COMPONENT BOARD, amongst hundreds of other parts, this has 15 ICs all plug in so don't need desoldering. Cost well over £100, yours for £4, Order Ref. 4P67

AMSTRAD KEYBOARD MODEL KB5, this is a most comprehensive keyboard, having over 100 keys including, of course, full numerical and qwerty. Brand new, still in maker's packing, £5, Order Ref. 5P202

SOLAR PANEL BARGAIN, gives 3v @ 200mA, £2, Order Ref. 2P324

ULTRA SONIC TRANSDUCERS, 2 metal cased units, one transmits, one receives. Built to operate around 40kHz, £1.50 the pair, Order Ref. 1.5P4

INSULATION TESTER WITH MULTIMETER, internally generates voltages which enables you to read insulation directly in megohms. The multimeter has 4 ranges ac/dc volts, 3 ranges dc milliamps, 3 ranges resistance and 5 amps. These instruments are ex BT but in very good condition, tested and guaranteed OK, yours for only £7.50, with leads, carrying case £2 extra, Order Ref. 7.5P4

MAINS ISOLATION TRANSFORMER, stops you getting to earth shocks, 230v in and 230v out. 150W upright mounting, £7.50, Order Ref. 7.5P5 and a 250W toroidal isolation, £10, Order Ref. 10P97

MINI MONO AMP on pcb. Size 4"x2" with front panel holding volume control and with spare hole for switch or tone control. Output is 4W into 4 ohm speaker using 12v or 1W into 8 ohm using 9v. Brand new and perfect, only £1 each, Order Ref. 495

EXPERIMENTING WITH VALVES, don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250v at 75mA and 6.3v at 3A, £5, Order Ref. 5P167

0-1MA FULL VISION PANEL METER, 2 3/4" square, scaled 0-100 but scale easily removed for re-writing, £1, Order Ref. 756

PCB DRILLS, 12 assorted sizes between .75 and 1.5mm, £1 the lot, Order Ref. 128.

12V AXIAL FAN, for only £1, ideal for equipment cooling, brand new, made by West German company. Brushless so virtually everlasting. Supplied complete with diagram of simple transistor driver, £1, Order Ref. 918.

PC OPERATING SYSTEMS, fully user documented and including software, MS-DOS 3.20, with 5" disk, £5, Order Ref. 5P2076: MS-DOS 3.3 with 3 1/2" disk, £5, Order Ref. 5P208, or with 5" disk, £5, Order Ref. 5P208/5: MS-DOS 4.01 with 3 1/2" disk, £10, Order Ref. 10P99.

45A DOUBLE POLE MAINS SWITCH. Mounted on a 6x3 1/2 aluminium plate, beautifully finished in gold, with pilot light. Top quality, made by MEM. £2, Order Ref. 2P316.

SOLAR ENERGY EDUCATIONAL KIT. It shows how to make solar circuits and electrical circuits, how to increase voltage or current, to work a radio, calculator, cassette player and to charge nicad batteries. The kit comprises 8 solar cells, one solar motor, fan blades to fit motor and metal frame to hold it to complete a free-standing electric fan. A really well written instruction manual, £8, Order Ref. 842B.

## POWER SUPPLIES - SWITCH MODE

(all 230v mains operated)  
Astec ref. B51052 with outputs +12v .5A, -12v .1A, +5v 3A, +10v .05A, +5v .02A unboxed on pcb size 180x130mm, £5, Order Ref. 5P188.  
Astec ref. BM4 1004 with outputs +5v 3 1/2A, +12vc 1.3A, -12v 1.2A, £5, Order Ref. 5P199  
Astec No. 12530 +12v 1A, -12v .1A, +5v 3A, uncased on pcb size 160x100mm, £3, Order Ref. 3P141  
Astec No. BM41001 110W 38v 2.5A, 25.1v 3A part metal cased with instrument type main input socket & on/off dp rocker switch size 35x4118x84mm, £8.50, Order Ref. 8.5P2  
Astec model No. BM135-3302 +12v 4A, +5v 16A, -12v 0.5A totally encased in plated steel with mains input plug, mains output socket & double pole on/off switch size 400x130x65mm, £9.50, Order Ref. 9.5P4

## POWER SUPPLIES - LINEAR

(all cased unless stated)  
4.5v dc 150mA, £1, Order Ref. 104  
5v dc 2 1/2A psu with filtering & volt regulation, uncased, £4, Order Ref. 4P63  
6v dc 700mA, £1, Order Ref. 103  
6v dc 200mA output in 13A case, £2, Order Ref. 2P112  
6-12v dc for models with switch to vary voltage and reverse polarity, £2, order Ref. 2P3  
9v dc 150mA, £1, Order Ref. 762  
9v dc 2.1A by Sinclair, £3, Order Ref. 3P151  
9v dc 100mA, £1, Order Ref. 733  
12v dc 200mA output in 13A case, £2, Order Ref. 2P114  
12v 500mA on 13A base, £2.50, Order Ref. 2.5P4  
12v 1A filtered & regulated on pcb with relays & Piezo sander, uncased, £3, Order Ref. 3P80  
Amstrad 13.5v dc at 1.8A or 12v dc at 2A, £6, Order Ref. 6P23  
24v dc at 200mA twice for stereo amplifiers, £2, Order Ref. 2P4  
9.5v ac 600mA made for BT, £1.50m, Order Ref. 1.5P7  
15v 500mA ac on 13A base, £2, Order Ref. 2P281  
AC out 9.8v @ 60mA & 15.3v @ 150mA, £1, Order Ref. 751  
BT power supply unit 206AS, charges 12v battery and cuts off output should voltage fall below pre-set, £16, Order Ref. 16P6  
Sinclair microvision psu, £5, Order Ref. 5P148

## LASERS & LASER BITS

2mW laser, helium neon by Philips, full spec. £30, Order Ref. 30P1  
Power supply for this in kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well, £18, Order Ref. 18P2.  
The larger unit, made up, tested and ready to use, complete with laser tube, £69, Order Ref. 69P1

## HEATING UNITS

Linear quartz glass tubes 360W, 2 in series for mains, £1, Order Ref. 907  
1000W spiral elements for repairing fires etc. 3 for £1, Order Ref. 223  
1000W pencil elements, 2 for £1, Order Ref. 376  
1.2kW mini tangential heater, ideal for under desk etc, £5, Order Ref. 5P23  
2kW tangential heater, £6, Order Ref. 6P30  
3kW tangential heater, £8, Order Ref. 8P24  
12' tubular heater, slightly storage soiled, £6, Order Ref. 6P31  
Water-proof heating wire, 60ohms per metre, 15m is right length for connecting to mains, £5, Order Ref. 5P109

The above prices include VAT but please add £3 towards our packing and carriage if your order is under £50. Send cheque or postal orders or phone & quote credit card number.

## M & B ELECTRICAL SUPPLIES LTD

Pilgrim Works  
(Dept. WW),  
Stairbridge Lane, Bolney,  
Sussex RH17 5PA  
Telephone 0444 881965  
(Also fax but phone first)  
Callers to 12 Boundary Road,  
Hove, Sussex

# NEW PRODUCTS CLASSIFIED

## ACTIVE

### A-to-D & D-to-A converters

**30Msample/s A-to-D.** Two-step analogue-to-digital converter from Signal Processing Technologies, the *SPT1175*, produces 8-bit words at conversion rates up to 30msample/s. Signal-to-noise ratio is 45dB for 3.58MHz input at 20Msample/s and differential gain and phase are 1% and 0.7° respectively; large-signal bandwidth 12MHz; and input capacitance less than 15pF. Differential non-linearity is ±0.6LSB and there are no missing codes over the entire operating range. Ambar Cascom Ltd, 0296 434141.

**Small, 12-bit A-to-D.** *LTC1257* from Linear is a complete 12-bit, voltage-output, single-supply digital-to-analogue converter in a surface-mounting SO-8 package, with output buffer amplifier, 2.048V reference and three-wire serial interface. Differential non-linearity error is 0.5 LSB. Power supply needed is 4.7-15.75V, current being 350µA at 5V. Linear Technology (UK) Ltd, 0276 677676.

**3.3V, 10-bit A-to-Ds.** TI's new family of A-to-D converters have 10-bit resolution, 21µs conversion time, on-chip, microprocessor-controlled sample-and-hold and a serial interface supporting the Serial Peripheral Interface and Microwire. The single-input *TLV1549* is contained in an 8-pin dip or SO and the 11-input *TLV1543* in a 20-pin dip or wide-body SO. Texas Instruments, 0234 223252.

### Discrete active devices

**Disk-drive Schottky.** Dual Schottky barrier diode from Allegro is meant chiefly for use in hard-disk drives. The *A8920SL* exhibits a 440mV forward drop at 150mA, a 500mA maximum forward current and 20V reverse voltage and reverse recovery time at 100mA of 32ns. A multi-chip version, the *TND8000*, has three pairs of diodes in a 16-lead SOIC package. Allegro Microsystems Ltd, 0932 253355.

**Fast diodes.** Silicon epitaxial planar

diodes in ITT's new range provide extremely fast switching. *BAS16* handles 100Vpk reverse, 150mA average rectified current and 500mA surge forward at 25°C. Dual, common-cathode diodes, *BAZ70* and *BAV99*, and the *BAW56* common-anode type offer 70Vpk reverse and 250mA continuous forward. Power dissipation is 350mW. ITT Semiconductors, 0932 336116.

**Smart fets.** *IRSF3010* SmartFET transistors by International Rectifier feature over-current shutdown, gate/drain clamp and gate/source clamp for ESD protection. There is also over-temperature protection which is latched, as is the over-current circuit. Polar Electronics Ltd, 0525 377093.

**Fast rectifiers.** Super fast rectifier diodes from Semtech have reverse voltages from 2.5kV to 10kV, recovery time of 60ns and forward currents of 100mA-1A. Reverse current is 0.2µA-1µA. Type numbers are *1FFXX*, *2FFXX*, *5FFXX* and *10FFXX*. Semtech Ltd, 0592 773520.

**Power mosfet.** Siliconix's *S19936DY Little Foot* power mosfet is meant for use in disk drives and portable computers, delivering 5A with a rated on-resistance of 50mΩ. It is a dual n-channel device and replaces two typical SM or TO-220 devices. Voltage rating is 30V. Siliconix/TEMIC Marketing, 0344 485757

### Digital signal processor

**32-bit DSPs.** TI announces its first low-power 32-bit digital signal processor. The 33Mflop/s performance achieved by the 5V *TMS320C31* is now available in the 3.3V version, the *TMS320LC31*, with no increase in price. Two power-down modes are provided to either reduce the instruction rate or shut down an inactive device while retaining memory contents. A new version of the 5V device runs at 50Mflop/s. Texas Instruments Ltd, 0234 223252.

### Linear integrated circuits

**Photodiode amplifier.** A low-cost photodiode amplifier from Centronic, the *CA-100*, measures currents from 200pA to 2mA, giving an output of 2V at an accuracy of 1% FSD on all eight ranges. It can be operated in optical-power mode, in which the calibration adjust control sets the amplifier to a known optical power to give direct reading of optical power on the LC

display. Detectors are available as extras. Centronic Ltd, 0689 842121.

**Phase control.** GEC Plessey's *TDA2088* bipolar IC is for current feedback phase control in motor-speed controllers; it is also usable in open-loop mode. Power comes from an AC or DC supply, the IC incorporating a -5V regulator for internal functions and to power external circuitry. Output triac drive is 100mA maximum. Gothic Crellon Ltd, 0734 788878.

**Cheap 900MHz chipset.** Five chips from Motorola, *MR1C2001/2/3/4/5/6*, form a 900MHz chipset for personal communication. Costing \$13.57 in low volumes, the set is designed for use as front end for CT-2 cordless telephones, but is also suitable for GSM, ISM and 915MHz cordless. The chipset consists of a down-converter LNA/mixer, transmit mixer, GaAs antenna switch, driver and ramp and a two-stage power amplifier. Motorola Inc., (USA) 602 994 6561.

**TV signal encoders.** *TDA8501* and *TDA8505* television signal encoders by Philips convert RGB or YUV video input to standard composite video, *8501* for Pal or NTSC and *8505* for Secam. Both types produce separate luminance and chrominance for equipment such as VHS-C recorders. A minimum of external components is needed: a luminance delay line, a few CRs and a crystal for the *8501*. *TDA8501* needs no alignment and *TDA8505* only one operation. Philips Semiconductors, (Europe)+31 40722091

**ICE stereo decoder.** *TDA1592* is a development of Philips's existing *TDA1591* stereo decoder/noise blanker for high-performance car radio. It features 50mV muting offset to give RDS switching without clicks, an S:N ratio of 82dB, input overdrive of 6dB and automatic FM/AM high-cut control for weak signal conditions. An analogue voltage from the level detector allows smooth stereo/mono changeover with signal level. Philips Semiconductors, (Europe)+31 40722091

### Logic building blocks

**Small clock.** A clock module measuring 10.31 by 5 by 3.35mm, the *RTC-8583* by Epson, has a built-in 32kHz crystal oscillator, an I<sup>2</sup>C-bus interface and alarm and timer functions. It operates at supply voltages down to 2.5V and offers a data-hold range of 1-6V. Epson, 0442 227331.



**Microcontroller.** Hitachi has a new member of its *H8* series of microcontrollers operating with supply voltages of 2.7-5.5V. It is based on a 16-bit register architecture addressing up to 16Mbyte and has a 1.9Ml/s performance in a Dhrystone benchmark at 16MHz. Hitachi Europe Ltd, 0628 585000.

### Microprocessors and controllers

**Microcontrollers.** New versions of Hitachi's *H8/500* microcontrollers in 0.8µm CMOS offer a choice of higher speed or low-voltage operation and different packages. *H8/535* and */536* have 32K or 62K of rom or eeprom and 2K of on-chip ram, the "S" versions operating at up to 16MHz at 5V to give a minimum instruction time of 125µs. 16 by 16-bit multiplications take up 1.4µs and 32/16-bit division 1.63µs. Several timers are provided, as is a 10-bit A-to-D converter. New packaging is the Thin QFP, which is only 1.2mm thick. Hitachi Europe Ltd, 0628 585000.

**Low-power microprocessor.** Motorola's *PowerPC 603* is a low-power design intended for use in notebook and laptop computers, running all the popular operating systems including OS, OS/2, MS-Dos via emulation, standard variations of *Unix* and pen-based systems. Its superscalar architecture allows three instructions per clock cycle at frequencies up to 80MHz. Motorola Ltd, 0296 395252.

**64-bit risc processor.** A low-power, low-cost, 64-bit risc processor, the *VR4200* by NEC, achieves an 80MHz

## NEW PRODUCTS CLASSIFIED

Please quote "Electronics World + Wireless World" when seeking further information

clock speed, derived from a 40MHz external clock, and operates on 3.3V at 1.5W (0.4W standby). Functions include calibration adjustment, floating calculation unit and a cache memory for 16Kb of instructions and 8Kb of data. Packages are a 179-pin PGA or a 208-pin QFP. NEC Electronics (UK) Ltd, 0908 691133.

**Fuzzy co-processor.** The *VY86C570* is a 12-bit, high-performance fuzzy co-processor capable of carrying out full fuzzy rule evaluations 20-30 times faster than software-only methods, being capable of more than 850 000 rule evaluations per second at 20MHz. Its integral rule base eliminates the need for external rule-base memory in most cases. VLSI Technology Ltd, 0908 667595.

### Mixed-signal ICs.

**Data retiming.** Analog's *AD805* is a 155Mb/s PLL for data retiming in which the clock-recovery technique eliminates incompatibility between types A and B regenerators, overcoming the jitter-tolerance limitations of type B circuits. The IC exploits the 1° RMS jitter of an external crystal oscillator and has an independent phase-control feedback path to track data with jitter. Analog Devices Ltd, 0932 253320.

**Telecomm switch.** C P Clare's *TS* series is a combined hookswitch and ring detector in an 8-pin dip, using an optically-isolated mosfet relay for hookswitch, dial pulse or loop start switching, with a bidirectional optocoupler for ringing current or loop current detection. Switches handle voltages up to 400V pk, AC or DC, and currents to 170mA. Switching speed is 3ms. C P Clare Corporation, 0460 41771.

**Audio decoder.** Complete audio decompression system in one IC, the *CS4920* by Crystal, contains everything needed to receive and process compressed audio and convert it stereo analogue output; the built-in digital signal processor supporting a range of decompression standards. Signal-to-noise ratio is up to 90dB and THD less than 0.01%. A digital output derived from the decompressed audio conforms to the Sony/Philips Digital Interface Format or the AES/EBU format. Crystal Semiconductor, (US) (512)445-7222.

**Real-time MPEG encoders.** Details of C-Cube's VideoRISC Compression Architecture (VCA), the first architecture specifically designed to compress and decompress digital video in real time, have been announced. VCA supports encoding and decoding for a variety of international standards, including MPEG, JPEC and H.261. First in the range are the *CLM4600* broadcast MPEG 2 video encoder and the

*CLM4500* consumer MPEG 1 version. Kudos Thame Ltd, 0734 351010.

### Oscillators

**Voltage-controlled oscillators.** M/A-COM's *MLO 30000*, *40000* and *50000* series of VCOs use a resonator-stabilised bipolar transistor as a negative-resistance generator and have a Varactor diode for tuning. Doubling extends the fundamental to 18GHz. Low phase noise is obtained in the *30000* series by means of a hyperabrupt Varactor. M/A-COM, 0344 869595.

### Programmable logic arrays

**2500-gate device.** With 282 registers and 2500 usable gates, Altera's *EPF8282* is the newest member of the *FLEX8000* family of programmable logic devices, which Altera claims gives better performance at lower cost than field-programmable arrays. The device is in a 0.8µm CMOS static ram process in 3.3V and 5V versions. Average benchmark speed is 40MHz. Altera Ltd, 0628 488811.

### Power semiconductors

**8A IGBT.** Harris claims its *HGTD8P5G1* to be the world's first p-channel, enhancement-mode, insulated-gate bipolar transistor. Main features are 8A collector current and 500V breakdown. The use of a p-

**Air-cored coils.** Cambion air-wound coils come in any internal diameter from 1.5mm to 10mm as standard, using wire diameters from 0.315mm to 2mm in lengths up to 25mm. They are supplied with tinned or untinned leads and for through-hole or surface mounting. Interconnection Products Ltd, 0433 621555.

channel device in conjunction with n-channel types greatly simplifies the design of circuitry such as half bridges. Harris Semiconductor (UK), 0276 686886.

**Voltage regulators.** Voltage regulators in SOT223 and E-line packages from Zetex come in five voltages from 3.3V to 10V and give a 200mA output. Power dissipation is 2W for the SM package or 0.6W for the E-line type. Voltage constancy is around 10mV under both line and load variation and quiescent current is held down to 400µA. Zetex plc, 061-627 5105.

### Passive components

**"Smallest" capacitors** Panasonic claims its Series *EL Gold* double-layer capacitors to be the world's smallest, having values in the 0.1F-2F range and measuring 6.8mm in diameter by 1.4mm. Rated working voltage is 2.5V from -25 to 70°C and life is 100 000 charge/discharge cycles. The company also claims the world's largest capacitor — the *Power* range, with a value of 1500F. Panasonic Industrial Europe, 0344 353827.

### Displays

**Touch screen controller.** The *SMT-1* miniaturised, surface-mounted touch screen controller by MicroTouch can be mounted on the back or at the bottom of a CRT and is designed for external retrofitting. It needs only one supply voltage between 5 and 16V at 70mA, obtainable from the monitor. MicroTouch Systems Ltd, 0844 260123.

**Fluorescent panel.** NEC's chip-in-glass fluorescent display panels have only 22 lead terminals instead of the 198 used in conventional types. The module has an in-built microcomputer, character generator, power supplies and rese-. Serial receive data rate is 9600baud. NEC Electronics (UK) Ltd, 0908 691133.

## PASSIVE

**Bargraph display.** Babcock's *SP-410-003* DC planar gas display is hermetically sealed in a thin glass package for front-panel mounting. Only seven drivers are needed for the 201 elements in each bar, the display emitting neon-orange light at 40fL against a dark background, with a 130° viewing angle. Selectronic Ltd, 0993 778000.

**Dot-matrix module.** *GD-032D128-01* from Babcock is a dot-matrix display with a fully populated field of 32 by 128 pixels in an area of 3.15in by 12.75in, displaying four lines of 21 characters, each 0.8in high, or any combination of pixels to represent symbolic images or animation. Drive and signal conditioning is on-board. Typical brightness of the neon-orange light is 55fL. Selectronic Ltd, 0993 778000.

### Hardware

**Wavesoldering fluids.** Soldering fluids from Fry's use nitrogen to produce an oxygen-free soldering path, so that extremely low-activity fluxes can be used to leave a minimum of residue. *1174*, *1175* and *1220* fluids leave even less than conventional low-solids fluxes and no cleaning is needed, giving good results in oxygen concentrations up to 500ppm. Fry's Metals Ltd, 081-665 6666.

### Instrumentation

**Miniature controller.** CAL's model *3200* controller is contained in a 1/32 DIN unit and "auto-tunes" itself to configure it for a range of process variables. Inputs can come from most thermocouples, *PT100* or from five linear process ranges, the 4-digit led display presenting one-digit units, degrees of temperature or engineering units. CAL Controls Ltd, 0462 436161.

**Cable data analyser.** *Halcyon* is billed as the world's first parallel cable data analyser, which analyses a data stream at very high speed, byte-by-byte and bit-by-bit, correcting it before driving the printer. Its effectiveness is such that its maker, End Design, says it will handle 50kbyte/s over half a kilometre of cable. The unit is plugged into a cable run just before the printer, where it obtains its 2mA of supply current from the PC and printer. End Design Ltd, 0372 458080.

**Low-cost H-P T&M.** Hewlett-Packard has four new instruments in its low-



cost range. Benchlink software allows the import of test data to a PC. *HP33120A* is a direct digital synthesised function generator producing standard or arbitrary waveforms to 12-bit resolution and with linear/log. sweep. *HP54610A* is a 500MHz oscilloscope with very accurate measurement and 1ns/division sweep rate. And the 35W *HPE3630A* triple-output power supply provides 0-6V at 1-2.5A and 0 to  $\pm 20V$  at 0.5A. Hewlett-Packard Ltd, 0344 362867.

**EMC kit.** Martron's EMC laboratory kit allows all electromagnetic compatibility and radio-frequency interference tests required by current and future EC legislation. The kit costs around £12 000 and covers both conducted and radiated emissions to CISPR over the 9kHz-1GHz frequency range. A PC-based software program produces a representation on screen of results and a hard-copy report. Martron Instruments Ltd, 0494 459200.

**20MHz function generators.** Three programmable function generators by Thurlby Thandar cover the 2mHz-20MHz frequency range to an accuracy within 0.1%. Model *8020* generates sine, triangle and symmetrical square waves, symmetrical pulses and DC, also including eight log/lin sweep modes, VCO, gating and triggering pulses. *8021* offers the same, but with six controllable pulse and two ramp modes. *8022* provides all that plus AM and carrier control. Thurlby Thandar Instruments, 0480 412451.

**Multimeter with PC interface.** Thurlby Thandar's *1906* benchtop digital multimeter is a 5.5-digit auto/manual ranging instrument that connects directly to the serial port of a PC, which controls function, range and configuration, reading results individually or in blocks. Up to 32 instruments can be controlled in this way, using the RS232 interface in addressable mode. The meter will perform linear scaling with offset, percentage deviation, limits comparison, min/max storage and data logging. Thurlby Thandar Instruments, 0480 412451.

## Interfaces

**Card readers.** New versions of MR Sensors's magnetic card readers incorporate serial outputs and come in RS232, RS422 or RS485 versions. Since all is contained within the reader housing, no external interface is needed. Magnetoresistive techniques make for increased reliability and other features include selectable baud rate, handshake and parity and high/low level coercivity compatibility. MR Sensors Ltd, 0222 520022.

**Talking modem.** Mutek designs and makes the *DiSPatch* digital signal processor-based modem, a technique that, being software-based, allows simple addition of features by means of a rom exchange. It also enables the use of voice synthesis. The unit meets V42, V42bis, V32bis and G3 fax specifications and the relevant lower-speed function with sync. and async. input. Mutek Data Communications Ltd, 0225 866502.

**PCMCIA interface kit.** To connect laptop PCs to GPIB instruments, National Instruments has introduced an IEEE488 interface for the PCMCIA bus, including the PCMCIA-GPIB plug-in board, NI's *NI-488.2* for dos and Windows software and a GPIB-terminated 2m cable. National Instruments UK, 0635 523545.

## Literature

**Test & measurement catalogue.** Fluke's 1994 catalogue is now available, covering a range of test and measurement equipment from basic multimeters to data acquisition systems. This is the first Fluke catalogue since the firm's acquisition of the Philips T&M operation. It is obtainable free. Fluke (UK) Ltd, 0923 240511.

**Cambion guide.** Interconnection Products has produced a guide to its wide range of Cambion electromechanical and magnetic product, which includes lists of product literature and quality approvals. Interconnection Products Ltd, 0433 621555.

## Materials

**Conductive paints.** Enco has introduced a method of spray masking for the spraying of conductive paint, spraying being necessary for the paint to keep its properties. Instead of labour-intensive masking tape or precision hard masks, Enco's masks are CNC machined plastic inserts, economic up to 600 units per day, and the method is said to be one-third as expensive as hard tooling. Enco Industries Ltd, 05057 5151.

## Power supplies

**DC-to-DC converters.** Ericsson announces the *PKF-MacroDens* series of 3-7W DC-to-DC converters usable as SM or through-hole components for automatic insertion. Isolation is 1.5kV and the devices may be paralleled. They are provided with output voltage adjustment and low-input turn-off for battery protection; outputs are from 2V/3W to 12V/7W. Ericsson Components AB, 0793 488300.

**40W DC-DC converter.** Ericsson's *PKE* series of low-profile DC-to-DC



power modules now includes the *PKE 4431 PI*, which measures 76mm square and 10.7mm high, while providing 40W in three outputs: 5V and  $\pm 12V$ . Input voltage range is 38-72V DC and efficiency is around 83%. There is under-voltage lockout and remote on/off switching. Ericsson Components AB, 0793 488300.

## Radio communication products

**Feedforward amplifiers.** RF amplifiers from Pacific Amplifier are now available here in a range of broad-band, high-power amplifiers covering 0.1-2000MHz. Examples are a 400W design working at VHF for medical use and a 150-1200MHz, 50W type working in Class A with a flatness of  $\pm 1dB$  over the band, a 47dB gain and harmonics of less than -20dB. A recent model is microprocessor-controlled at 850MHz and -60dBc intermodulation at 80W. Anglia Microwaves Ltd, 0277 630000.

**18GHz dividers/combiners.** Two-way, stripline, in-phase power dividers in octave and multi-octave bandwidths to 18GHz are announced by KDI Electronics. The *YL* and *D300* series use a ceramic pad as the internal resistive element, handling 1W CW and 1kW peak powers. Isolation is 20dB and connectors

**IR thermometers.** Six instruments in Digitron's D200 range of infrared thermometers exhibit accuracies of  $\pm 1\%$  of reading  $\pm 1^\circ C$  over the -20 to 250 $^\circ C$  temperature range. The seventh is a high-accuracy type, offering 0.1 $^\circ$  resolution to an accuracy of  $\pm 1^\circ C$  from -20 to 70 $^\circ C$ . A new feature on these low-cost units is adjustable emissivity for direct setting or to obtain the emissivity of a material of known temperature. Digitron Instrumentation Ltd, 0992 587441.

include SMA, N or TNC types. Three, four, eight and sixteen-way models are available. Anglia Microwaves Ltd, 0277 630000.

**UHF bandsplitter.** Diplexer *Type 2800-660* splits or combines the lower and upper halves of the UHF band (4700-890MHz) to connect two UHF antennas to a single transmission line or to allow two low-power transmitters to use the same antenna. Crossover frequency is 630MHz and passbands, on separate connectors, are 470-600MHz and 660-890MHz, passband loss being 1dB maximum. Power rating is 5W. Communications & Energy Corp., (US)(315) 452-0709.

Please quote "Electronics World + Wireless World" when seeking further information

**GPS IC set.** GEC Plessey's three-piece chipset for GPS consists of the *GP1010* front end, the *GP1020* correlator and a *DW9230* saw filter, which works with both the GPS Coarse/Acquisition code or Glonass signal. *GP1010* is a silicon device in the company's 15GHz bipolar process, converting the L1-band spread-spectrum signal to two-bit digital data for correlation in *GP1020*. This is a six-channel, 1µm cmos gate array, using code from six satellites to calculate three-dimensional position to within 100m. GEC Plessey Semiconductors, 0793 518510.

**GPS receiver.** Rockwell's *NavCard* is a Global Position System receiver on a PCMCIA Type II card, with an average power consumption of 750mW. An integrated, removable antenna is provided, with external antenna kits available. The card provides a time-to-first-fix of 20-30 seconds and dynamic tracking, even in foliage and an urban environment and in the presence of vibration and shock. Rockwell International, 010 33 93 00 33 01.

**Scanning telemetry.** Designed solely for telemetry and thereby avoiding problems associated with voice radios adapted to telemetry, Wood & Douglas's *MPT1411 ScanLink* consists of a duplex base station, semi-duplex outstation and a monitor, providing scanning telemetry to public utilities. Outstations operate in semi-duplex, with receive and transmit separated by 5.5MHz, one version operating at 10W and the second at 500mW. Switching time is better than 10ms. Wood & Douglas Ltd, 0734 811444.

**Switches and relays**

**HV relays.** FR has a new series of high-voltage relays that handle stand-off voltages up to 10kV DC (7kV AC), with over 15kV DC isolation between coil and contacts. First model is in Form A and will shortly be followed by a Form B and a flying-lead version. FR Electronics, 0202 897969.

**Optical relays.** Having four relays in one sil package, Matsushita's *AQX photoMOS* device can be used as either four independent relays, each with its own input and normally open output or as a single input with four independent outputs. Each output carries up to 80mA at 400V AC or DC, with negligible output offset. Isolation is 1500V. Matsushita Automation Controls, 0908 231555.

**Immersible microswitch.** Matsushita's new microswitch conforms to IP67 for waterproofing and to IP50 against dust. An ultrasonic swaging process seals the rubber seal round the mechanism and the terminals are sealed by potting the base in epoxy resin. Capability is 3A at 250V AC or 1mA at 24V DC. Pin plunger, hinge lever or roller lever types are available and the smallest

switch measures 12.8mm by 6mm by 6.5mm. Matsushita Automation Controls 0908 231555.

**Transducers and sensors**

**Pressure transducer.** The *Sensit P-192* pressure transducer is compatible with wet and corrosive substances by virtue of its construction, in which the bridge is fused into the rear face of an alumina diaphragm, which in turn is assembled into a brass housing carrying a male thread pressure port. Spans are in the 10-40bar range, with a twice-span overload without calibration. Burst pressure tolerance is four times span. Errors from all causes lie within 1% and are typically below 0.15%. Eurosensor, 071-405 6060.

**Audio signaller.** Producing a sound level of 75dBa at two feet, the Mallory *Sonalert II* measures only 23mm in diameter and 9mm in height. It operates at 3-20V DC, drawing 1-12mA, and produces a 3.4kHz signal. It is surface-mounted and an octagonal version is made for use with insertion equipment. Highland Electronics Ltd, 0444 236000.



**Computer board level products**

**PC A-to-D.** Made by Amplicon Liveline, the *PC26AT* is a 16-channel, 12-bit analogue-to-digital converter add-on board for PCs that has a crystal oscillator to drive the three 16-bit counter timers, offering a DMA capability of 90kHz throughout. Conversion time of the successive-approximation device is 10µs and it can operate in unipolar mode with full scale of 3V-10V, or in bipolar mode from ±1.5V to ±10V. Demo software is written in *QuickBasic*, *Microsoft C*, *Turbo C* and *Turbo Pascal*. Amplicon Liveline Ltd, (Free)0800 525335.

**12MHz DDS.** The model *DDS3 PC* 12MHz direct digital synthesiser on a PC card provides 5ppm accuracy, 10ppm/year stability and good spectral purity while generating sine and TTL/CMOS clock signals simultaneously from 2Hz to 12MHz in 2Hz steps. Phase noise is less than -90dBc at 1kHz offset from carrier, spurious signals are below -45dBc and harmonics below -40dBc. The card comes with a C program running under dos. Novatech Instruments Inc., (US) 206 328 6902.

**MPEG decoder card.** Polar offer a PC card performing real-time MPEG

decoding for video-by-wire and conferencing systems, claimed by the company to be the first in the field. It gives full audio and video decoding at resolutions of 720 by 376 at 25Hz or 720 by 480 at 30Hz. Decompressed video can be seen in a screen window, depending on system configuration. Polar Electronics Ltd, 0525 377093.

**Image acquisition.** *VideoWizard* is a low-cost image acquisition system for Windows that includes the VVL miniature *Peach* camera, tripod, mono framegrabber card and *PhotoFinish* software. The camera takes power from the PC. The six image formats include .TIF, .PCX and .BMP. Total cost is £285. VLSI Vision Ltd, 031-539 7111.

**Development and evaluation**

**Windows FPGA design.** Data I/O's *Synario* is a Windows-based FPGA design system to ease the transition from PLDs to FPGAs and to allow FPGA designers to work with multiple architectures. It allows the creation, simulation and verification of designs, independently of architecture, so that the best architecture for a given application may be selected. Since it runs under Windows, users can move between applications through a standard interface. Data I/O Ltd, 0734 440011.

**Return of the Stag.** Stag ended production of the *SE100T* eeprom eraser recently and stopped advertising it two years ago, but continuing demand has forced the company to restart manufacture. The UV instrument erases up to 104 24-pin devices at a time, a 60-minute timer and full safety interlocks being provided. Stag Programmers Ltd, 0707 332148.

**Software**

**LabWindows/CVI.** National has the new *LabWindows/CVI*, which is

software running under Windows for developing virtual instruments using the C programming language. It expands on *LabWindows* for dos, which uses C and Basic. *LabWindows/CVI* is a 32-bit, multiplatform environment including all tools for C-compatible test, measurement and control applications on a PC or as X Window systems for *Unix SPARCstations*. Dos-based *LabWindows* applications run in */CVI*. National Instruments UK, 0635 523545.


**Windows neural network.** A new version of the *NeuDesk* Windows-based neural-network PC package is a low-cost means of evaluating the networks by means of an intuitive GUI, with the option of embedding programs so created in other Windows applications. Version 2.11 handles larger problems to greater accuracy and two optional algorithms optimise networks for classes of problem such as forecasting and classifying data. Neural Computer Sciences, 0703 667775.

**PC STEbus board.** Arcom has the *SCIM-X STEbus* board for embedded dos/Windows applications, using a *486SLC* CPU with over 10Mbyte of ram and flash eeprom. It integrates the hardware of three *STEbus* modules. There is ample expansion facility, including enough ram to run systems such as *Unix*, and the display can take several forms, the drive being a plug-in module. Software can be developed on-board, since it is PC-compatible, and software is provided to blow the result into rom-disk or ram-disk for use in hostile conditions. Arcom Control Systems Ltd, 0223 411200.



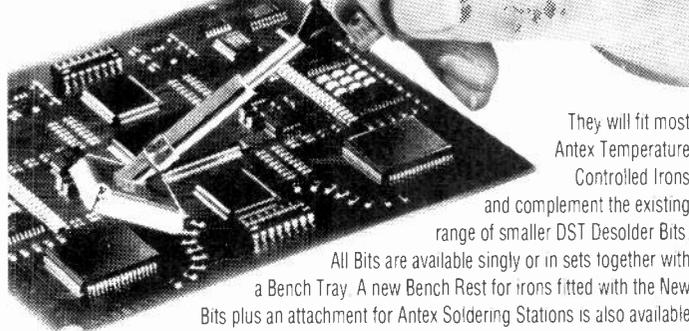
# New low-priced Desolder Bits from Antex

Removing larger components from PCB boards can be a problem in rework and repair shops. The new Antex range of 10 SMT Desolder Bits have been produced to fit components from S018 through to PLCC 68.



They will fit most Antex Temperature Controlled Irons and complement the existing range of smaller DST Desolder Bits.

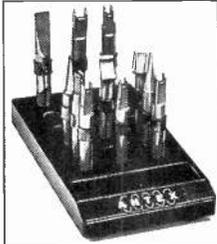All Bits are available singly or in sets together with a Bench Tray. A new Bench Rest for irons fitted with the New Bits plus an attachment for Antex Soldering Stations is also available from leading Electronic Distributors.




# ANTEX

Antex (Electronics) Ltd.

2 Westbridge Industrial Estate, Tavistock, Devon PL21 8DE  
Tel: (0822) 613565 Fax: (0822) 617598

CIRCLE NO. 129 ON REPLY CARD

## 10 OUTLET DISTRIBUTION AMPLIFIER 4

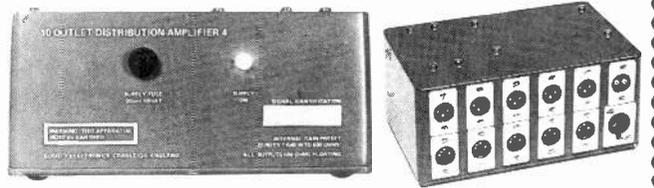

A compact mains powered unit with one balanced input and ten AC and DC isolated floating line outputs.

- Exemplary RF breakthrough specifications giving trouble-free operation in close proximity to radio telephones and links.
- Excellent figures for noise THD, static and dynamic IMD.
- Any desired number of outlets may be provided at microphone level to suit certain video and audio recorders used at press conferences.
- Meets IEC65-2, BS415 safety.

\*Advanced Active Aerial 4kHz-30MHz \*PPM10 in-vision PPM and chart recorder \*Twin PPM Rack and Box Units \*Stabilizers and Fixed Shift Circuit Boards for howl reduction \*Broadcast Monitor Receiver 150kHz-30MHz \*Stereo Variable Emphasis Limiter 3 \*Stereo Disc Amplifier \*Peak Deviation Meter \*PPM5 hybrid. PPM9 microprocessor and PPM8 IEC/DIN -50/+5dB drives and movements \*Broadcast Stereo Coders

**SURREY ELECTRONICS LTD**  
The Forge, Lucks Green, Cranleigh,  
Surrey GU6 7BG.  
Telephone: 0483 275997. Fax: 276477.

### WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

**TEXTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200. PLUG-INS SOLD SEPARATELY**

TEXTRONIX 2235 Dual Trace 100MHz Delay Sweep	£800
PHILIPS 2065 2+1 Channels 100MHz Dual TB Delay Sweep	£700
TEXTRONIX 475 Dual Trace 200 MHz Delay Sweep	£550
TEXTRONIX 465 Dual Trace 200 MHz Delay Sweep	£450
N.P. 1725A Dual Trace 275MHz Delay Sweep	£550
N.P. 1715A Dual Trace 200MHz Delay Sweep	£500
HAMEG 605 Dual Trace 60MHz Delay	£400
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£400
PHILIPS PM3244 4 Trace 50MHz Delay Sweep	£350
TELEQUIPMENT D63 Dual Trace 50MHz Delay Sweep	£200
IWATSU SS5705 3 Channel 40MHz Delay Sweep	£400
WITACHI Y422 Dual Trace 40MHz	£325
KINUSUI 5530 Dual Trace 35MHz	£180
GOLD 051100 Dual Trace 30MHz	£180
HITACHI V23 Dual Trace 20MHz Dual Sweep	£300
HAMEG 203 6 Dual Trace 20MHz Component Tester	£260
GOLD 05300 Dual Trace 20MHz	£200
GOLD 052500 Dual Trace 15MHz	£125
TEXTRONIX 2430 Dual Trace 150MHz Digital Storage	£P.O.A.
TEXTRONIX 466 Dual Trace 100MHz Delay Sweep Analogue Storage	£450
N.P. 1741A Dual Trace 100MHz Delay Sweep Analogue Storage	£450

THIS IS JUST A SAMPLE. MANY OTHERS AVAILABLE

PHILIPS PM5193 Programmable Synthesizer-Function Generator 0.1MHz-50MHz IEEE-488 As new	£1500
MARCONI 2018 Synthesised AM/FM Sig Gen 80kHz-1040MHz	£2000
MARCONI 2018 Synthesised AM/FM Sig Gen 80kHz-520MHz	£950
EIP-DANA 3511 Microwave Frequency Counter 20Hz-18GHz	£950
RACAL 9521 Frequency Counter 3GHz	£300
RACAL/DANA 1991 Nanosecond Universal Counter	£450
RACAL 9302 Millivoltmeter True RMS 10MHz-1.5GHz	£450
RACAL 9301A RF Millivoltmeter True RMS 10MHz-1.5GHz	£450
RACAL 9009 Automatic Mod Meter 10MHz-1.5GHz Wide Deviation	£250
LYONS PG37N Pulse Gen PRF 1Hz-20MHz	£150
GOLD Bricomation K5000D Logic Analyser	£500
FARNELL P50520W Synthesised Sig Gen AM/FM 100kHz-520MHz	£600
LEADER L50216 AM/FM Sig Gen 0.1-30MHz & 75-115MHz	£400
BRUEL & KJER Vibration Exciter System Consisting of exciter control 1047, Power Amp 2708 & Exciter Body 4802 (Up to 1780N - 400Hz)	

### OTHER B&K EQUIPMENT AVAILABLE

<b>SPECTRUM ANALYSERS</b>	
HP 1411 with 8555A & IF Plug-in 10MHz-18GHz	£2000
HP 1411 with 8554B & 8552B 500kHz-1250MHz	£1300
HP 1401 with 8554A & 8552A 500kHz-1250MHz	£1000
HP 1411 with 8556A & 8552B 20Hz-300kHz	£1000
HP 1401 with 8553A & 8552A 1kHz-110MHz	£800
MARCONI T2370 30Hz-110MHz	£1500
HP 182C with 8558B 100kHz-1500MHz	£1500
HP 3182A 0.2Hz-25.5MHz	£2000

**Used Equipment - GUARANTEED. Manuals supplied if possible.**  
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

### STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: (0734) 268041. Fax: (0734) 351696  
Callers Welcome 9am-5.30pm Monday to Friday (until 8pm Thursday)



CIRCLE NO. 130 ON REPLY CARD

### CHASE MFR 2000 INTERFERENCE MEASURING RECEIVER WITH MAINS NETWORK


CHASE MFR 2000 Interference Measuring Receiver with Mains Network	£1750
DATRON 1061A - 6 1/2 digit True RMS AC/Current	£1250
DATRON 1065 Multimeter 5 1/2 digit AC/DC Ohms IEEE	£600
HEWLETT PACKARD 3490A Bench Multimeter 5 1/2 digit AC/DC/Ohms	£200
PHILIPS PM2534 Multifunction DMM 6 1/2 digit GND/IEEE	£450
MARCONI Digital Frequency Meter 2430A 10Hz-80MHz	£125
MARCONI Digital Frequency Meter 2431A 10Hz-200MHz	£150
MARCONI Universal Counter Timer 2430C-100MHz	£175
HP 3311A Function Generator 0.1Hz-1MHz Sine Sq/Tri	£225
FEEDBACK FG600 Sine Sq/Tri 0.01Hz-100kHz	£60
MULTIMETERS Hand Held M235-32 ranges AC DC 10 Amps/Diode Transistor Tester Freq Counter	£32.50
FARNELL ELECTRONIC LOAD RB1030 35 1kw 30Amp 25 Volt	£600
HP 8690 Sweep Disc with 86574 Plug-in 25.5 400Hz	£300
RACAL/DANA RF Power Meter 9104	£400
RACAL/DANA 9341 Databridge Automatic LCR D	£350
WAYNE KERR B905 Automatic Precision Bridge 0.05%	£900
WAYNE KERR B665 Automatic Component Bridge 0.1%	£250
FARNELL PSU TVS700M2 70V 5A 30V/10A	£300
FARNELL PSU H60/25 0-50V 0-5Amps Metered	£400
FARNELL PSU L30E 0-30V 0-5Amps Metered	£80
FARNELL B30/20 0-30V 20Amps	£250
FARNELL B30/10 0-30V 10Amps	£200
N.P. 2709B 0-320V 0-0.1Amps Metered	£125
MARCONI TF2700 Universal LCR Bridge Battery from AVO Characteristic Meter VCM153	£300
FARNELL LA20 RF Power Amp 1.5-520MHz 300mW	£175
RACAL 9100 Absorption Wattmeter 1MHz-1GHz 3W	£100
FARNELL Isolating Transformers GUS500 240v 500VA unused	£50

### NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase	£847
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep	£653
HAMEG OSCILLOSCOPE HM203 7 Dual Trace 20MHz Component Tester	£362
HAMEG OSCILLOSCOPE HM205 3 Dual Trace 20MHz Digital Storage	£653
All other models available - all oscilloscopes supplied with 2 probes	
<b>BLACK STAR EQUIPMENT (P&amp;P all units £5)</b>	
APOLLO 10-100MHz Counter/Timer Rat/Period	£222
APOLLO 100-100MHz (As above with more functions)	£325
METOR 100 FREQUENCY COUNTER 100MHz	£119
METOR 600 FREQUENCY COUNTER 600MHz	£145
METOR 1000 FREQUENCY COUNTER 1GHz	£189
JUPITER 500 FUNCTION GEN 0.1Hz-500kHz Sine Sq/Tri	£119
ORION COLOUR BAR GENERATOR Pal-TV/Video	£229
All other Black Star Equipment available	
OSCILLOSCOPE PROBES Switchable x1 x10 (P&P £3)	£12
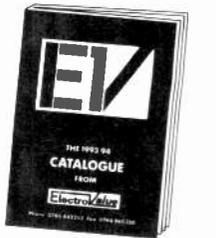
# THIS IS THE COUPON that brings the 1993-94 CATALOGUE

140 pages, A4, copiously illustrated, bang up to date and with bonus vouchers. Send cheque/PO for £1.50



# that brings the SERVICE

with choice of very wide ranges of famous-name quality electronic components and associated gear sent promptly on receipt of your order. A service

# that ElectroValue

have been providing constructors with continuously since 1965. With this Catalogue, you will find our service the best ever. Send for your copy NOW!

**ELECTROVALUE LTD., 3 CENTRAL TRADING ESTATE, STAINES TW18 4UX**  
Telephone 0784 442253 Fax 0784 460320

I enclose Cheque/PO Order/Credit Card No .....  
value £1.50 for your 1993-94 CATALOGUE  
Name.....  
Address.....  
Post Code.....

CIRCLE NO. 131 ON REPLY CARD

# USING RF TRANSISTORS

## 4: factors affecting amplifier design

*How do you choose the right device configuration? In an extract from their book Radio frequency transistors: principles and practical applications, Norm Dye and Helge Granberg supply the answers, show the importance of class and explain about bias for linear applications.*

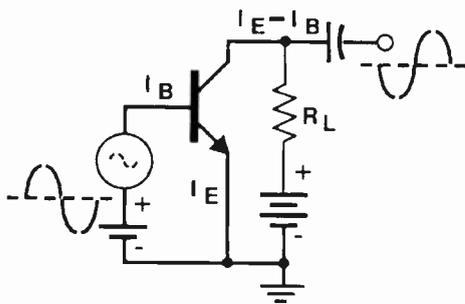


Fig. 1. Common emitter circuit configuration, the only one with phase reversal between input and output.

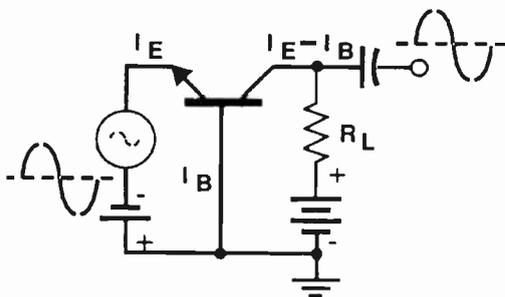


Fig. 2. Common base circuit configuration has the lowest input impedance and no phase reversal between the input and the output.

Common emitter and common source circuit configurations are some of the most widely used because of their stability, good linearity and high power gain up to uhf. They are also the only configurations where input and output are out of phase, enhancing their stability – except for the half  $f_0$  mode and at frequencies where the feedback capacitance delays are close to  $180^\circ$ .

But if the common emitter or source inductance is increased, the power gain will drop due to the negative feedback generated by the reactance. So for proper operation the common element inductance must be kept as low as physically possible.

Gain is inversely proportional to the frequency and increases approximately 5dB per octave until the  $\beta$  cutoff is reached. At this point it may be as high as 30-40dB.

A common emitter circuit (Fig. 1) can be directly adapted to mosfets, but in that case since  $I_B = 0$ ,  $I_D = I_E$ . Lumped-constant matching elements are practical in narrow band circuits up to vhf. But at over 300-400MHz, microstrip techniques – or a combination of microstrip and transformer impedance matching techniques – are normally used.

For broadband performance, the initially-higher device impedance levels make impedance matching easier to implement to a  $50\Omega$  interface with a push-pull configuration. In multi-stage systems the interstage impedance matching is usually carried out at lower than  $50\Omega$  levels, and in some instances very little impedance transformation is required. The result may be better broadband performance than with  $50\Omega$  interfaces between each stage, but it does not have the advantage that each stage can be individually tested in a standard  $50\Omega$  set-up.

Up to vhf and low uhf, input impedance of a mosfet is high compared to that of a bjt but at higher frequencies they reach similar values, and the matching procedures become almost identical.

In practice, virtually all multi-octave amplifier designs independent of frequency spectrum and device type are push-pull. Another advantage is that the power levels of two devices are automatically combined for higher power output levels. So electrically-smaller individual devices can be used for a given power output.

RF power transistors housed in push-pull headers have been available since the mid-

1970s. But it was the development of high frequency fets that really made the push-pull package so popular. Now fets and bjts are both available in push-pull headers, most as the "Gemini" type where two individual and independent transistors are mounted on a common flange next to each other. Gemini packages are manufactured in several physical sizes, the largest being able to dissipate up to 500-600W. A big attraction of the push-pull transistor – whether in a single push-pull header or in a Gemini package – is the close electrical proximity of the two dice. Device performance of a push-pull circuit is greatly enhanced as a result, where the important factor is a low emitter-to-emitter (source-to-source) inductance and not the emitter-to-ground inductance.

In all Gemini housed devices, the emitter (or source) is connected to the mounting flange – the electrical dc ground.

No significant difference in efficiency is apparent between amplifiers using either fets or bipolars. The higher saturation voltage of fets probably make them less efficient but this may be true only at low operating voltages (12V and lower).

At higher frequencies, device output capacitance has a much larger effect on efficiency, though part of it can be tuned out in narrow band circuits.

### Common base and common gate

At uhf and microwave frequencies, common base circuits with bjts are widely used because their  $\alpha$  cut-off is higher than the  $\beta$  cut-off. Higher power gains are possible than with the common emitter configuration.

If base-to-ground inductance is added, power gain of a common base amplifier increases where positive feedback is generated. Add more inductance and the gain will increase to a point of instability, finally leading to steady oscillation – usually at a frequency where the matching networks resonate.

All common base transistors have some positive feedback, generated by the inductances of the base bonding wires and the internal part of the base lead. But this inductance is generally low enough not to generate sufficient positive feedback to create instability.

As in the common emitter circuit, a common base transistor's gain is inversely proportional to its frequency of operation. The

slope is also the same, approximately 5dB/octave, but only up to the  $\alpha$  cut-off. Below  $\alpha$  cut-off, the gain flattens out to 12-15dB and remains at that level down to dc.

Input power need not be fed through in a common base amplifier circuit, so the power output is actual and not  $P_{in} + P_{out}$  as in a common emitter amplifier. The effect is that device ruggedness (ability to withstand load mismatches) is probably improved through reduced dissipation.

In a common base circuit (Fig. 2), the total current flows through the emitter, so the input matching network, or an emitter dc return choke, must be able to carry  $I_B + I_C$ . The normal output capacitance ( $C_{ob}$ ) and feedback capacitance ( $C_{rb}$ ) are reversed. Fortunately, except at low bias voltages where  $C_{rb}$  can be several times higher than  $C_{ob}$ , their values are about equal.

Under normal drive conditions there should be little difference in output capacitance or impedance between common emitter and common base circuits. But the highly non-linear  $C_{rb}$  reportedly creates increased tendencies for the well known half  $f_0$  phenomenon.

### Common gate and base

Mosfets, operated as a common gate amplifier, create a totally different situation. Their feedback capacitance ( $C_{rss}$ ) has a value many times lower than the output capacitance ( $C_{oss}$ ). When these are reversed, the actual feedback capacitance goes high with respect to the input and output capacitances, creating an unstable condition.

Even if the common gate inductance can be minimised, stability may not be achievable. The input impedance is lower than in a common source circuit because of the high value of feedback capacitance enhanced by the Miller effect.

Stable single-frequency or narrow-band circuits with fractional octave bandwidths are possible using the common base configuration. But wide-band circuits are difficult to design if internal matching is required.

Neutralisation can improve stability in some cases, though it is not easy to implement except in push-pull designs. In high power circuits, biasing to a linear mode is difficult as an opposite polarity supply is required at the emitter. There is also a rectification effect which tends to reduce the bias voltage with rf drive.

In small signal circuits, where the class of operation is mostly class A, some bypassed base-to-ground resistance can be used to generate a self bias.

Push-pull common base circuits are not normally seen at higher power levels, at high uhf or higher frequencies. One reason may be that the 180° phase shift is difficult to achieve and hold except for very narrow band widths.

But push-pull common base circuits are widely employed at power levels up to 0.5-1W in applications such as cable tv amplifiers, where an un-bypassed common base resistance can be used for self biasing to a linear mode of operation.

For each configuration – common emitter and common base – push-pull offers the same advantages, the most important of which is the non-critical base or emitter common mode inductance.

Power gain and stability of the push-pull circuit depends to a large extent on base-to-base inductance. Mosfets must always be biased to a level close to or greater than the gate threshold voltage to overcome  $V_g(th)$  with rf input drive (excluding class D and other switch-mode systems). The bias source must be able to carry the full drain current: at a gate threshold voltage of 4-5V this would amount to considerable dissipation. But with bjts the voltage is only 0.6-0.7V and so much more tolerable.

Common gate mosfet circuits are most useful in relatively low power applications, in circuits where neutralisation can be easily realised and their high age range (power gain/gate voltage) is an advantage.

Disadvantages of the common base amplifier circuit include the need for two dc power supplies for classes A, AB and B; poor linearity due to regeneration; low input impedance; no possibility to implement negative feedback (except in push-pull), and high susceptibility to half  $f_0$  instability.

### Common collector

Common collector, emitter follower circuits (Fig. 3) are widely used for high input and low output impedance levels.

As in a common base configuration, there is no phase reversal between input and output. The emitter follower has a voltage gain of less than unity, and amplification is obtained from the current gain through impedance transformation. Output impedance is directly related to the input impedance divided by current gain ( $h_{FE}$ ). Conversely, input impedance equals the output load multiplied by  $h_{FE}$ .

The circuit is less suitable for rf power amplifiers than the two other configurations since variations in load impedance are directly reflected back to the input. So its widest use is as a wideband buffer amplifier, driving low impedance or capacitive loads.

In fact, the circuit offers one of the best drivers for capacitive loads – especially in a complementary configuration providing active “pull-up” and “pull-down” in the output. Applications include crt video drivers and mosfet gate drivers in class D/E amplifier systems.

### Common drain

In bipolar circuits, the emitter follower is represented by a common drain or source follower circuit configuration. As before, input impedance is high and output impedance low.

Compared to common source and common gate circuits, input capacitance, drain-to-gate, is low – considerably lower for the fet (because of absence of the forward biased collector-base diode junction) than for a bipolar of comparable electrical size. A source follower also has a voltage gain of less than unity, and since it is not a current amplifier, discussion of current gain is not appropriate.

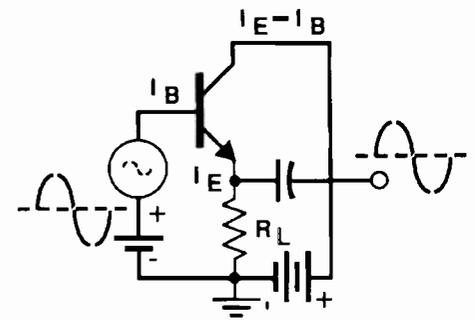


Fig. 3. The common collector circuit configuration has the highest input impedance and lowest output impedance. No phase reversal exists between input and output.

But amplification takes place through impedance transformation as is the case in a bipolar circuit.

Extremely high input impedance, more variable with frequency than in common source and common gate circuits, means heavy resistive loading at the gate must be used for any broadband application. Negative feedback is not needed, nor is it easy to implement due to equal phase of the input and output.

For these reasons, common source circuits exhibit exceptional stability. But excessive stray inductances in the circuit lay-out can lead to low frequency oscillations.

Unlike the emitter follower, variations in load impedance are not reflected to the input, making the source follower suitable for rf power amplifier applications – at least up to vhf.

Push-pull broadband circuits for 2-50MHz have been designed for 200-300W power levels, having inherent good linearity, stability and gain flatness without levelling networks.

High power linear amplifiers are probably the most suitable application for this mode of operation. The age range is comparable to that in common source, but a higher voltage swing is required.

One problem to watch for is that during high voltage operation, gate rupture voltage can easily be exceeded, since during the negative half cycle of the input signal the gate voltage can approach the level of  $V_{DS}$ .

### Biasing to linear operation

All solid-state devices and vacuum tubes intended for linear operation must have a certain amount of “forward bias” dc idle current to place their operating points in the linear region of the transfer curve (Fig. 4).

Perfect linearity means that power output follows the power input in a linear fashion: a  $P_{in}$  of 1W produces a  $P_{out}$  of 10W, 2W results in a  $P_{out}$  of 20W etc.

It can also mean that the power gain must be constant from almost zero to the maximum  $P_{out}$  level. This can also be expressed as gain compression in dB, or as the third order intercept point as widely used in low power and catv applications.

In large signal voice communication, linearity is usually measured as intermodulation

**Performance of an amplifier depends on how it is biased.**

Low power transistors are characterised as class A and many high power amplifiers are characterised as class C. Any user of rf transistors must understand these classes and their significance in determining amplifier characteristics and choice of transistors for a specific application.

Each of the basic classes of operation is limited to a specified portion of the input signal when current flows in the amplifying device. The class definitions apply regardless whether the amplifier is a vacuum tube or a transistor; or whether it is a bipolar transistor or a fet.

For example, Class A requires that current flows for all 360° (all the time) of the input signal which is assumed to be in the form of a sine wave. Likewise, class C requires current to flow for less than half the time, or less than 180° (Table 1).

Class D amplifiers split into two basic types: the current switching amplifier, driven by a square wave signal; and the voltage switching amplifier, driven by either a square wave or the more common sine wave input. With sine wave drive, the gate voltage swing must be large enough to ensure complete saturation and cut-off of the fet.

Input and output waveforms are approximately identical except that the current and voltage waveforms are reversed.

Demanding applications are better suited by the current switching class D amplifier, since its duty cycle is easily defined and is not affected by amplitude

**Table 1. Maximum theoretical efficiencies for basic classes of amplifier operation.**

Class	Configuration	Efficiency %	Comments
A	all	50	
B	all	78.5	
AB	all	50-78.5	depending on angle of conduction
C	non-saturating	85-90	depending on angle of conduction
D	all	100	assumes infinite switching speed
E	-	100	assumes no overlap for the output rf currents and voltages

of input drive.

Class E is a variation of class D with an LC network added to the output. It compensates for part of the fet's output capacitance and helps to reduce overlap between the switching currents and voltages – boosting efficiency.

The improvement can be around 5-10%. But the system is relatively narrow band due to the LC network, whereas plain class D can operate at bandwidths of several octaves.

Output power of Class D/E amplifiers is limited by mosfet switching speeds and by the capacitive loads presented to driver stages.

**Class questions**

A logical question would be: "Can class A characterised transistors be used as class C amplifiers?". The obvious answer is yes. Similarly class C characterised transistors can be used in class A amplifiers – provided certain conditions are met. The condition involves a "derating" of the class C transistor to a lower power level, with the amount of derating depending on

the class of operation.

If a class C transistor is used in a truly linear class A amplifier, it should be derated by a factor of four. So if it can deliver, say, 60W class C, it should not be used class A at level greater than 15W.


Class AB use requires a safe derating factor of three.

Two factors make these deratings necessary for use in a more linear mode.

First, linear classes of operation require bias. Not uncommonly, a Class AB high power transistor will be biased at several amperes of current, resulting in a large amount of power dissipated in the device.

Second, efficiency of the more-linear forms of amplification decreases as linearity increases. So for the same amount of output power, the power dissipated in the transistor will increase.

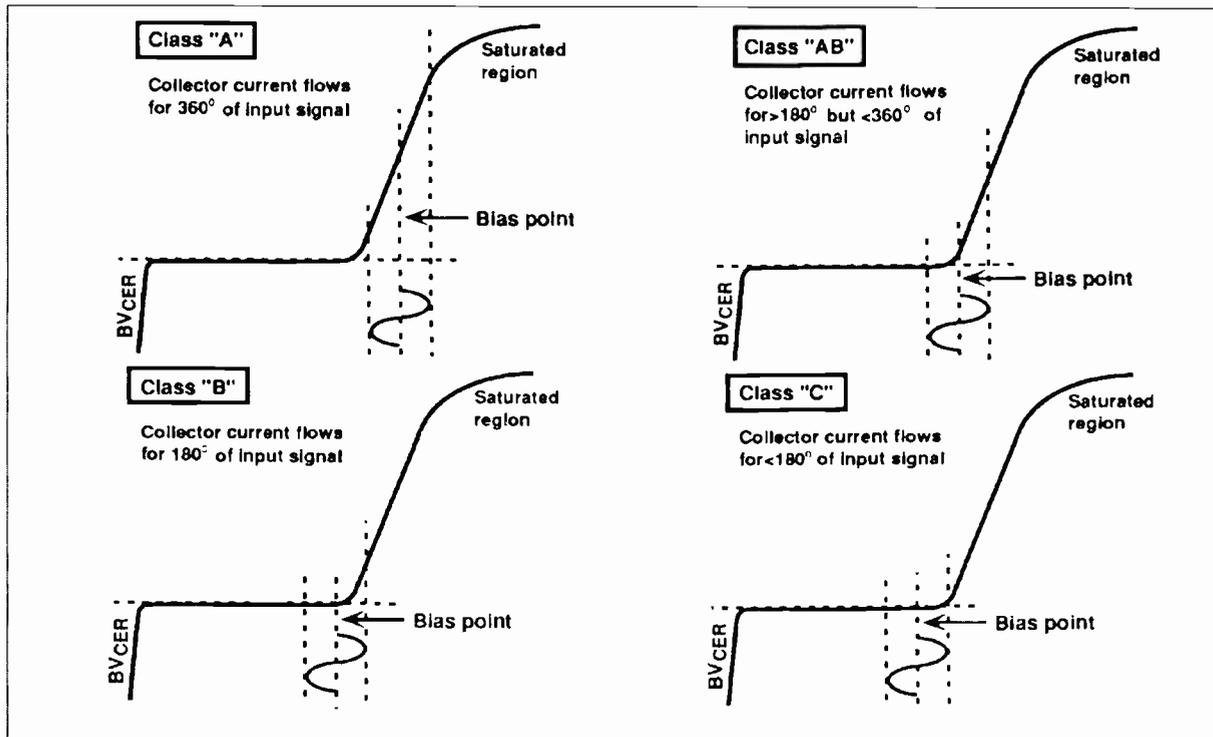Dissipated power raises the die temperature of a device, for a given heat sink temperature, and for silicon devices this should not exceed 200°C.



distortion (imd) using two test frequencies (tones) spaced kHz apart as a standard.

Testing amplifying devices for linear use in television, requires two or three test frequencies to be employed (depending on the specifications) with their spacings in the MHz range.

Three test frequencies (triple beat) are common with low power device specifications and are standard in catv device testing, where distortion levels are very low. A wider spectrum can be analysed as a result, which better simulates multichannel systems.

Distortion expressed as imd – because it is easier to relate to actual numbers – is the method by which linearity is initially measured, and can be converted to third order intercept. The test frequencies are viewed on a spectrum analyser screen and the distortion products (third, fifth, seventh order, etc.) appear on each side of the test tones. Their amplitudes can be read directly and are expressed either in dB below one of the tones (Mil Std) or below the peak power (EIA standard). Numerous ways can be used to generate the test tones.

Conversion to third order intercept can be done by

$$IP^3 = P_{out} + imd/2$$

where  $IP^3$  = third order intercept point,  $P_{out}$  = power output (one tone, dBm), imd = third order intermodulation distortion below one tone (dB).

Reversing the equation gives  $imd = 2(IP^3 - P_{out})$ . For example, if an amplifier has an  $IP^3$  of +20dBm and the  $P_{out} = +5dBm$ /tone, the third order imd is  $2[20 - (+5)]$  which is 30dB below one of the +5dBm tones.

Either the power input or the power output can be used for the power reference. In circuits having an insertion loss, such as mixers, the  $P_{in}$  is generally used as a reference.  $P_{out}$  is preferred in circuits with power gain due to a smaller factor of possible error.

Bipolar devices require a constant voltage source, whereas mosfets can be biased with simple resistor divider networks. But both become more complex where temperature stability is required.

In addition, enhancement-mode mosfets always need some gate bias voltage to overcome the gate threshold. Exceptions are mosfets operated in class D or in other switch-mode classes.

Apart from those applications already discussed that call for amplifier linearity, examples include all amplitude-modulated systems for communications and broadcast, nuclear magnetic resonance, magnetic resonance imaging, digital cellular telephone, and signal sources for instrumentation.

One of the requirements for transistor linearity is the flatness of  $f_T$  (gain-bandwidth product) vs  $I_C$  (collector current). Variation in collector current results in a change of  $f_T$ , and so a variation in power gain.

The low  $I_C$  area (Fig. 5) is not very critical and produces only cross-over distortion, which in most cases can be reduced by increasing the bias idle current. If the "knee" from zero cur-


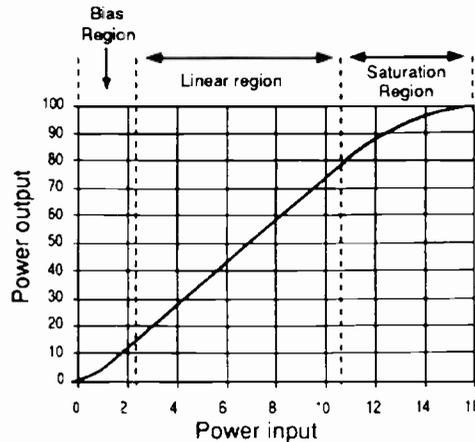


Fig. 4. Typical input-output transfer curve of a solid-state amplifier. Non-linearity can be seen in the bias region. The purpose of the forward bias is to move the operating point to the linear portion of the curve.

Fig. 5. Gain-bandwidth product vs collector current.

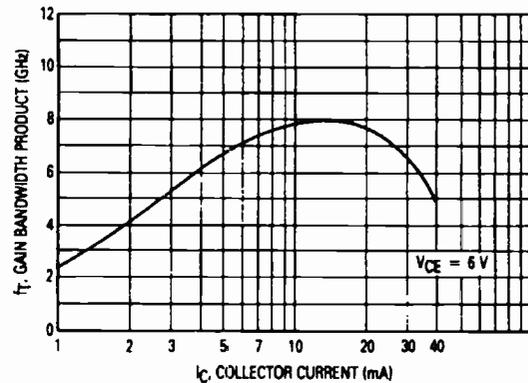

rent to maximum  $f_T$  is sharp, a smaller amount of bias or idle current is required.

Mosfets will produce a similar  $f_T$  vs  $I_D$  curve, except that their low current knee is not as sharp as that of a bjt, explaining their need for higher bias idle currents.

The input signal can drive the transistor to peak current levels significantly above the bias current. So the slope of the  $f_T$  curve, from the bias current level to the maximum current caused by the input signal, determines the

transistor's linearity performance at high current.

Some reduction with increasing current is tolerable without noticeable non-linearities, Fig. 5. Excessive downward sloping however would cause early saturation of the amplifier and flat topping of the output modulation peaks.

Finally, measurements of  $f_T$  vs  $I_C$  are usually carried out under pulse conditions, which excludes thermal effects. Thus the  $f_T$  vs  $I_C$  curve shows less sloping down than will be experienced in actual use of the transistor. ■

Norm Dye is Motorola's product planning manager in the Semiconductor Products Sector, and Helge Granberg is Member of Technical Staff, Radio Frequency Power Group (Semiconductor Products) at Motorola. Their rf transistors book includes practical examples from the frequency spectrum from 2MHz to microwaves, with special emphasis on the UHF frequencies.


*RF Transistors: Principles and practical applications* is available by postal application to room L333 EW+WW, **Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.** Cheques made payable to Reed Books Services. Credit card orders accepted by phone (081 652 3614). **288pp HARDBACK 07506 9059 3 Cost £19.95 + Postage £2.50**

**Radio Frequency Transistors**  
Principles and Practical Applications

Norm Dye and Helge Granberg

EDM MOTOROLA

# BOOKS TO BUY

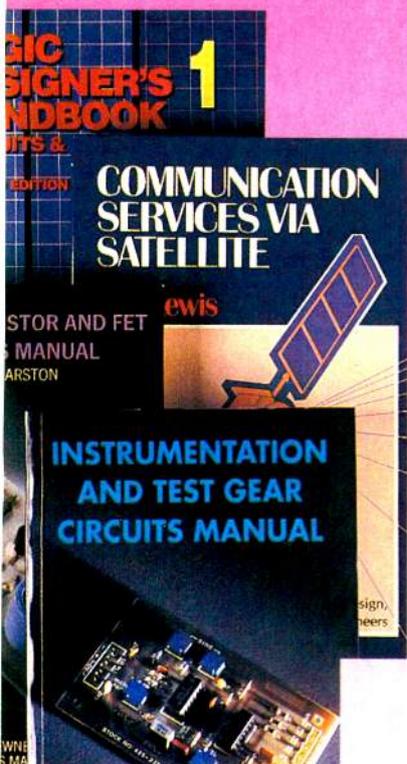

in grasping electrical and electronics theory. This book has been written to help such students to understand the mathematical principles underlying their subject so that they can go on with confidence to tackle problems in practical circuits. Paperback 256 pages.  
**Price £14.95 0 7506 0924 9**

## CIRCUIT MANUALS

**Ray Marston**

A series of books dealing with their subjects in an easy-to-read and non-mathematical manner, presenting the reader with many practical applications and circuits. They are specifically written, for the design engineer, technician and the experimenter, as well as the electronics student and amateur. All the titles are written by Ray Marston, a freelance electronics design engineer and international writer.

### Op-amp Circuits Manual

**Paperback 224 pages**  
**Price £13.95 0 434 912077**

### Audio IC Circuits Manual

**Paperback 168 pages**  
**Price £13.95 0 434 912107**

### CMOS Circuits Manual

**Paperback 192 pages**  
**Price £13.95 0 434 912123**

### Electronic Alarm Circuits Manual

**Paperback 144 pages**  
**Price £13.95 0 7506 00640**

### Timer/Generator Circuits Manual

**Paperback 224 pages**  
**Price £13.95 0 434 912913**

### Diode, Transistor and FET Circuits Manual

**Paperback 240 pages**  
**Price £13.95 0 7506 0228 7**

### Instrumentation and Test Gear Circuits Manual

**Ray Marston**  
Modern instrumentation and test gear circuits of value to the industrial, commercial, or amateur electronic engineer or designer make up this book. Almost 500 outstandingly useful and carefully selected practical circuits are in here. This is one book you must have if you need access to practical working circuits ranging from simple attenuators and bridges to complex digital panel meters, waveform generators, and scope trace doublers. Paperback 400 pages.  
**Price £16.95 0 7506 0758 0**

### Logic Designers Handbook

**Andrew Parr**  
Easy to read, but none the less thorough, this book on digital circuits is for use by students and engineers and provides an accessible source of data on devices in the TTL and CMOS families. It's a 'Designers Handbook' that will live on the designer's bench rather than on the bookshelf. The basic theory is explained and then supported with specific practical examples. Paperback 488 pages.  
**Price £25.00 0 7506 0535 9**

### Digital Audio and Compact Disc Technology

**Luc Baert, Luc Theunissen & Guido Vergult**  
Essential reading for audio engineers, students and hi-fi enthusiasts. A clear and easy-to-follow introduction and includes a technical description of DAT (digital audio tape). Contents includes principles of digital signal processing, sampling, quantization, A/D conversion systems, codes for digital magnetic recording, principles of error correction, the compact disc, CD encoding, opto-electronics and the optical block, servo circuits in CD players, signal processing, digital audio recording systems, PCM, Video 8, R-DAT and S-DAT. Paperback 240 pages.  
**Price £16.95 0 7506 0614 2**

### NEWNES POCKET BOOKS

A series of handy, inexpensive, pocket sized books to be kept by your side and used every day. Their size makes them an ideal 'travelling' companion as well.

### Newnes Electronics Engineer's Pocket Book

**Keith Brindley**  
**Hardback 319 pages**  
**Price £12.95 0 7506 0937 0**

### Newnes Electronics Assembly Pocket Book

**Keith Brindley**  
**Hardback 304 pages**  
**Price £10.95 0 7506 0222 8**

### Newnes Television and Video Engineer's Pocket Book

**Eugene Trundle**  
**Hardback 384 pages**  
**Price £12.95 0 7506 0677 0**

### Newnes Circuit Calculations Pocket Book

**T Davies**  
**Hardback 300 pages**  
**Price £10.95 0 7506 0195 7**

### Newnes Data Communications Pocket Book

**Michael Tooley**  
**Hardback 192 pages**  
**Price £12.95 0 7506 0427 1**

### Newnes Telecommunications Pocket Book

**JE Varrall & EA Edis**  
**Hardback 400 pages**  
**Price £12.95 0 7506 0307 0**

### Newnes Z80 Pocket Book

**Chris Roberts**  
**Hardback 185 pages**  
**Price £12.95 0 7506 0308 9**

### Newnes 68000 Pocket Book

**Mike Tooley**  
**Hardback 257 pages**  
**Price £12.95 0 7506 0309 7**

### Newnes Electrical Pocket Book

**21st edition**  
**E A Parr**  
**Paperback 526 pages**  
**£12.95 0 7506 05138**

### Newnes Electric Circuits Pocket Book Linear IC

**Ray Marston**  
**Hardback 336 pages**  
**Price £12.95 0 7506 0132 9**

### Newnes Guide to Satellite TV

**D J Stephenson**  
A practical guide, without excessive theory of mathematics, to the installation and servicing of satellite TV receiving equipment for those professionally employed in the aerial rigging/TV trades. Hardback 256 pages.  
**Price £17.95 0 7506 0215 5**

### Newnes Practical RF Handbook

**Ian Hickman**  
Pressure on the RF spectrum has never been greater and it's people with knowledge and skills of RF design who are now in demand in the electronics industry to design, produce, maintain and use equipment capable of working in this crowded environment. This practical introduction to modern RF circuit design will equip you with the necessary RF knowledge and skills to enable you to compete effectively in the industry. Paperback 320 pages.  
**Price £16.95 0 7506 0871 4**

### Troubleshooting Analog Circuits

**R A Pease**  
Bob Pease is one of the legends of analog design. Over the years, he's developed techniques and methods to expedite the often-difficult tasks of debugging and

### Programmable Logic Handbook

**Geoff Bostock**  
Logic circuit designers are increasingly turning to programmable logic devices as a means of solving problems. This book, for the established electronics engineer, student and technician, is a thorough introduction to programmable logic. Geoff Bostock will take you to a level where you, as a designer, can take full advantage of the growing product range of ASICs and other self-programmable arrays used in computer and control systems. Paperback 256 pages.  
**Price £19.95 0 7506 0808 0**

### Understand Electrical and Electronic Maths

**Owen Bishop**  
People who find maths difficult often have, as a result, difficulty

troubleshooting analog circuits. Now, Bob has compiled his 'battle-tested' methods in the pages of this book. Based on his immensely popular series in EDN Magazine, the book contains a wealth of new material and advice for Digital/Analog electronics engineers on using simple equipment to troubleshoot. Paperback 217 pages.

**Price £14.95 0 7506 16326**

**PC-Based Instrumentation and Control**

**M Tooley**

Do you need information to enable you to select the necessary hardware and software to implement a wide range of practical PC-based instrumentation and control systems? Then this book is for you. Paperback 320 pages.

**Price £14.95 0 7506 1631 8**

**Electronic Circuits Handbook**

**M Tooley**

Provides you with a unique collection of practical working circuits together with supporting information so that circuits can be produced in the shortest possible time and without recourse to theoretical texts. Paperback 345 pages.

**Price £24.95 0 7506 0750 5**

**Communication Services via Satellite**

**G E Lewis**

DBS is already with us, and will create a series of new technical problems for engineers/technicians in television and communication services. This book gives you the solutions to these problems by:

explaining how the system functions; describing several actual systems and giving several analyses and design rules. You can't afford to be without this invaluable technology update if you're a systems design engineer, service engineer or technician. Paperback 400 pages.

**Price £25.00 0 7506 0437 9**

**Digital Logic Design**

**Brian Holdsworth**

As one of the most successful and well established electronics textbooks on digital logic design, this book reflects recent developments in the digital fields. The book also covers new functional logic symbols and logic design using MSI and programmable logic arrays. Paperback 448 pages.

**Price £19. 50 0 7506 0501 4**

**The Circuit Designers Companion**

**T Williams**

This compendium of practical wisdom concerning the real-world aspects of electronic circuit design is invaluable for linear and digital designers alike. Hardback 320 pages.

**Price £25 00 0 7506 1142 1**

**Credit card orders accepted by phone 081 652 3614**

**Return to: Lorraine Spindler, Room L333, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS**

**Please supply the following titles:**

Qty	Title	ISBN	Price
	Programmable Logic Handbook	07506 0808 0	19.95
	Understanding Electrical & Elec Maths	07506 0924 9	14.95
	Op-amp Circuits Manual	0434 912077	13.95
	Audio IC Circuits Manual	0434 912107	13.95
	CMOS Circuit Manual	0434 912123	13.95
	Electronic Alarm Circuits Manual	07506 0064 0	13.95
	Power Control Circuits Manual	07506 06908	13.95
	Timer/Generator Circuits Manual	0434 91291 3	13.95
	Diode, Transistor & FET Circuits Man	07506 0228 7	13.95
	Instrumentation & Test Gear Circuits Man	07506 0758 0	16.95
	Logic Designers Handbook	07506 0535 9	25.00
	Digital Audio and Compact Disc	07506 0614 2	16.95
	Newnes Elec Engineers Pkt Bk	0 7506 0937 0	12.95
	Newnes Elec Assembly Pkt Bk	07506 0222 8	10.95
	Newnes TV and Video Eng Pkt Bk	07506 0677 0	12.95
	Newnes Circuit Calculations Pkt Bk	07506 0427 1	10.95
	Newnes Data Communications Pkt Bk	07506 0308 9	12.95
	Newnes Telecommunications Pkt Bk	07506 0307 0	12.95
	Newnes Z80 Pkt Bk	07506 0308 9	12.95
	Newnes 68000 Pkt Bk	07506 0309 7	12.95
	Newnes Electrical Pkt Bk	07506 05138	12.95
	Newnes Electric Circuits Pocket Bk	07506 0132 9	12.95
	Newnes Guide to Satellite TV	07506 0215 5	12.95
	Newnes Practical RF Handbook	07506 0871 4	16.95
	Troubleshooting Analog Circuits	07506 16326	14.95
	PC-Based Instrumentation and Control	07506 1631 8	14.95
	Electronic Circuits Handbook	07506 0750 5	24.95
	Communication Services via Satellite	07506 0437 9	25.00
	Digital Logic Design	07506 0501 4	19.50

PLEASE ADD £2.50 FOR POSTAGE  
Add VAT at local rate  
NB ZERO RATE FOR UK & EIRE TOTAL

**Business purchase:** Please send me the books listed with an invoice. I will arrange for my company to pay the accompanying invoice within 30 days. I will attach my business card/letterhead and have signed the form below.

**Guarantee:** If you are not completely satisfied, books may be returned within 30 days in a resaleable condition for a full refund.

Remittance enclosed £

Cheques should be made payable to **Reed Book Services Ltd.**

Please debit my credit card as follows:

Access/Master      Barclay/Visa      Amex      Diners

Credit Card No.      Exp date

NAME (Please print)

ORGANISATION

STREET

TOWN

COUNTY      POST CODE      COUNTRY

DATE      TELEPHONE NUMBER

SIGNATURE

T3000


**VAT RATES**

6% Belgium, 25% Denmark, 5.5% France, 7% Germany, 4% Greece, 4% Italy, 3% Luxembourg, 6% Netherlands, 5% Portugal, 3% Spain. FOR COMPANIES REGISTERED FOR VAT, PLEASE SUPPLY YOUR REGISTRATION NUMBER BELOW (customers outside the EEC should leave this part blank)

VAT NO.

If in the UK please allow 28 days for delivery. All prices are correct at time of going to press but may be subject to change. Please delete as appropriate. I do/do not wish to receive further details about books, journals and information services.

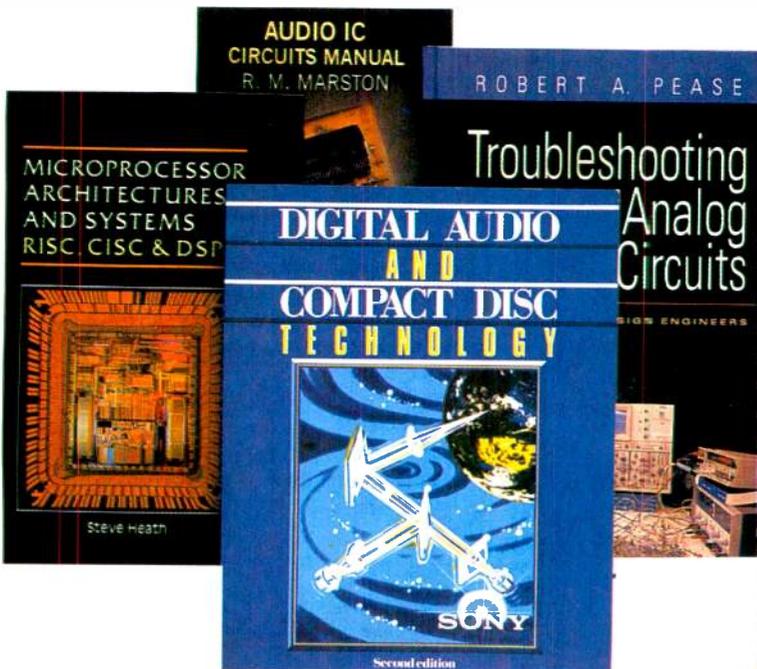Reed Business Publishing - Registered Office - Quadrant Hse The Quadrant Sutton Surrey SM2 5AS Registered in England 151537



# Making a linear difference to square law fets

*Michael Williams shows how the familiar "difference of two squares" could produce a linear output from a pair of fets, forming the basis for a perfect linear amplifier*

Plot a graph of output volts versus input volts for an amplifier and the result will be a simple straight line through the origin – up to certain limits anyway. The implication is that the various devices in the amplifier must also have linear characteristics. Certainly some – resistors and capacitors for example – can be very linear and were once thought inherently perfect. Thermionic valve characteristics can also be pretty linear. But fets have a square law characteristic. My contention is that by using the familiar "difference of two squares" (D2S), a linear output could be produced. The law seems to offer the prospect of a perfect linear amplifier from devices with a perfect square law.

I have always been surprised to find that though books quote the square law formula – even give mathematical proofs of it – nobody actually offers any hard evidence for it. Graphs might be drawn, but only to illustrate the formula, which seems to be untested.

## Finding matched pairs

While lecturing at the (then) Middlesex Polytechnic, I decided to test some devices, so set up a laboratory experiment for first year BEng electronics students. Their task was stated roughly as follows:

"The FET is said to follow the law  $I_d(1 - V/V_p)^2$  where  $I$  is the drain current through

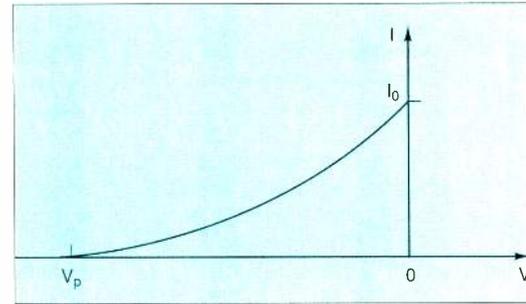


Fig. 1. Ideal fet square-law transfer characteristic: but does it exist in practice?

the fet.  $V$  is the input gate voltage and  $V_p$  (the "pinch-off voltage") is a value of  $V$  which just cuts off the current.

Investigate how valid this is for your fet."

A graph of this form, **Fig. 1**, has an output current of  $I_0$  when input  $V$  is zero, falling smoothly to zero as  $V$  approaches  $V_p$  – negative for our students' fets – but the principles apply to all types.

Year after year, the exercise revealed that some fets had a characteristic very close to the square law over the whole range between pinch-off and zero bias; but many did not. Of these, most had a square law for higher currents, but the pinch-off region extended to the left more than expected from extrapolation from the upper part of the graph. Some graphs were well behaved at low currents, but then mysteriously reached a limit as they got near the vertical axis.

In addition to these deviations from the square law, fets are very variable devices – even two square law characteristics may be perfect but different. To find matched pairs of fets with perfect square law characteristics, implies mass testing and recording. So for many years I set the design of a square law tester as a project for all second-year BEng students. They found it extremely difficult. It took at least six weeks of team effort before anyone could even say roughly what the problem was. Working solutions were rare. Design is a lot harder than people think, especially of a new kind of device.

## Effort repaid?

Is all the trouble worth the effort? To answer that, let us look at the way the two characteristics combine, and then at applications.

## Square history

About three decades ago, I was working in a team researching superconductors. We were using a magnetoresistor to measure magnetic fields at low temperatures, and were grumbling about its non-linear characteristic; its square law behaviour, in fact.

But a colleague surprised us all by suggesting: "Why not use two?" He was referring to the standard mathematical method where a difference of two squares gives a linear characteristic. We were all baffled, not to say humiliated by the simple algebra:  $(x + y)^2 - (x - y)^2 = 4xy$ . Just fix  $x$ , and the difference is

linear in  $y$ .

Examination of the formula for the difference of two squares – call it D2S for short – clarifies the technical problem; if we could apply opposite fixed bias fields to two magnetoresistors in the field to be measured, we should get a straight line graph of reading versus field. Well, we couldn't, so we didn't.

Nevertheless, the principle was intriguing though no application of D2S ever came up in my research days. But the strangest thing is that I have never found anybody (original proposer apart) who had heard of the "standard" D2S principle.

### D2S at a glance

Write out a row of consecutive digits, and square the row. Then repeat this row of squares but displace it to one side by any amount. The differences between the latter rows form a linear sequence. For example:

```

-6 -5 -4 -3 -2 -1  0 +1 +2 +3 +4 +5 +6
36 25 16  9  4  1  0  1  4  9 16 25 36
25 16  9  4  1  0  1  4  9 16 25 36 49
11  9  7  5  3  1 -1 -3 -5 -7 -9 -11 -13
    
```

Results can be displayed graphically – just plot squares against the original numbers – and it does not have to be limited to integers. It works for all displacements. Just take the difference of offset identical-square-law graphs – and a linear graph results.

Take a simple circuit (Fig. 2) of a matched pair of fets with a positive bias  $V_b$  on their (joined) sources, and equal and opposite signals fed to their two gates. Push-pull triodes are hardly a novelty, but there is something new in this approach.

Bias  $V_b$  pushes the transfer characteristic  $I_1(V_1)$  sideways (Fig. 3). Note that  $V_1$  is the gate potential (ie pd from ground), whereas the resultant input to the fet is the potential difference between the gate and the positively biased source. (We could have used negative gate bias instead of positive source bias.)

This displaced characteristic can be written algebraically as:

$$I_1 = (I_0/V_p^2)\{V_1 - (V_p + V_b)\}^2$$

Amplification is proportional to the slope at the working point ( $V_1$ ), ie to the mutual conductance,  $g_m$  and

$$g_m = dI_1/dV_1 = (2I_0/V_p^2)\{V_1 - (V_p + V_b)\}$$

This varies with bias and also with signal  $V_1$ , so  $V_1$  has to be kept very small if  $g_m$  is not to change with signal change.

The characteristic  $I_2(V_2)$  of the second fet is the same as the first,  $I_1(V_1)$ . But, to display the two currents and their differences together, they must all be plotted against  $V_1$ .  $V_2 = -V_1$ , so plotting  $I_2$  against  $V_1$ , instead of against  $V_2$ , just reverses the characteristic left to right (Fig. 4). Since the difference curve is straight, the two non-linear devices have combined to make a linear one – at least, in the range where both fets are on. This range is for values of input  $V_1$  in the range  $\pm V_b$  or  $\pm(V_p + V_b)$ , whichever is the smaller. The largest range is found with the bias set half way to pinch-off, when the full characteristics can be used.

Algebraically, the second characteristic is

$$I_2 = (I_0/V_p^2)\{-V_1 - (V_p + V_b)\}^2$$

By subtraction, the difference graph has the equation

$$I_1 - I_2 = -(4I_0/V_p^2)(V_p + V_b)V_1$$

a straight line through the origin. Redefining mutual conductance as  $g_m = d(I_1 - I_2)/dV_1$ , then

$$g_m = -(4I_0/V_p^2)(V_p + V_b)$$

The first bracketed term is simply a constant. The second is constant for any fixed value of bias,  $V_b$ , but the bias can be varied. Remember that  $V_p$  is negative, whereas the (variable) source bias  $V_b$  is positive.

As the bias  $V_b$  goes from zero to  $|V_p|$ ,  $g_m$  varies from  $-4I_0/V_p$  to zero. But it never varies with the strength of the signal. So, even for large inputs, as long as the signal is kept in the range, amplification is distortionless.

The behaviour is in complete contrast to that of the old "variable mu" circuit, where only tiny segments of the curved characteristic can be considered even quasi-linear.

If the bias is set at  $|V_p|/2$  for the largest symmetrical swing, then  $g_m = 2I_0/|V_p|$ , the value for a single fet at zero bias.

Figure 5 shows a set of linear characteristics calculated for a D2S pair with a pinch-off voltage of  $-4V$  as the bias varies between pinch-off and zero. The slopes of the characteristics vary by a factor of seven, as the bias

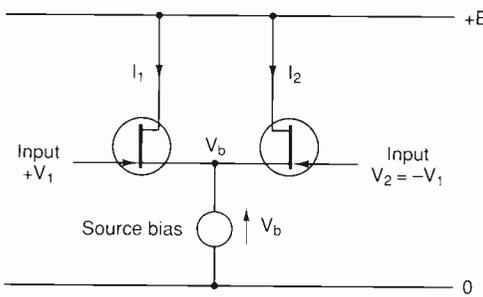


Fig. 2. Measured quantities in a push-pull matched pair of fets whose current difference should be linear in  $V_1$ .

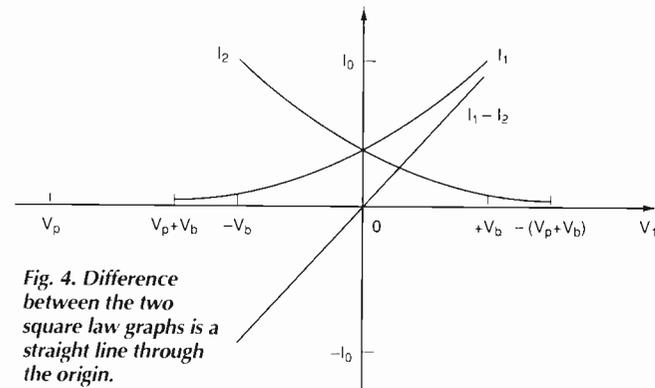


Fig. 4. Difference between the two square law graphs is a straight line through the origin.

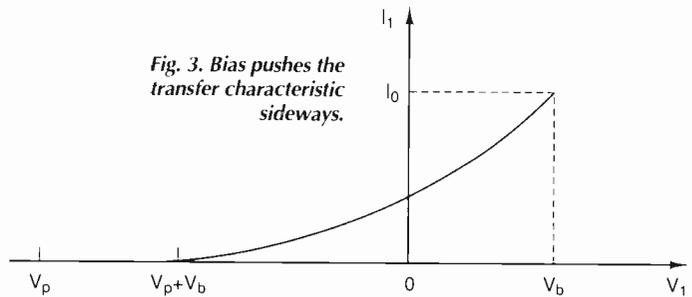


Fig. 3. Bias pushes the transfer characteristic sideways.

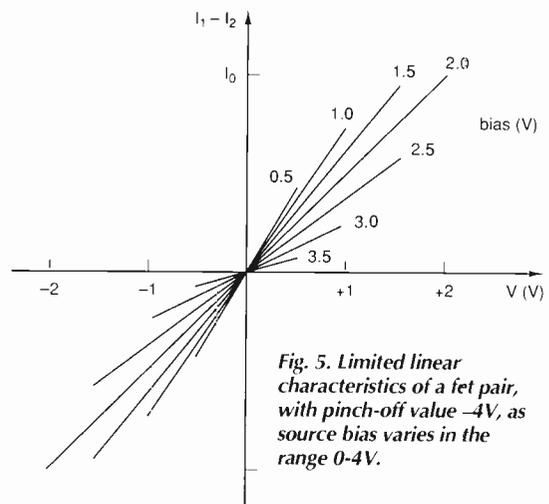


Fig. 5. Limited linear characteristics of a fet pair, with pinch-off value  $-4V$ , as source bias varies in the range 0-4V.

goes from -3.5V to -0.5V, and the minimum input range shown is  $\pm 0.5V$ .

Generally, with characteristics described by polynomials, sinusoidal input gives a distorted output, which can be described as linear plus added harmonics. Normally, push-pull reduces some of the harmonics; in the special case of a square-law, it cancels them completely.

Another useful feature is that with Class A mid bias, the standing current is not the usual half of the maximum - as it is in linear devices such as thermionic valves. Instead, it is only a quarter of the maximum current, giving less power loss in the quiescent state (perhaps it should have a special title, such as *Curvilinear Class A*).

The usual push-pull arrangement in small-signal stages, the "long-tailed pair", involves an unbiased resistor between the common source and ground. The effect is simultaneous equal but opposite current (rather than voltage) swings in the two fets, and so does not produce the distortionless result for all swings.

In principle, two fets can be paired to obey square laws which are not identical. Output current differences can be matched by use of different transformer windings or different loads. The input voltage swing to one fet can be attenuated to balance differences in pinch-off voltage. It may not seem like a strategy for mass production, but will probably appeal to the amateur "tweaker".

**Applications of D2S.**

The most obvious application of the D2S pair is in audio power output stages. People must be doing this without realising what is happening, though few makers of amplifiers have probably consciously selected their output fet pair for square law characteristics. More likely is that devices are selected for best linearity - if at all. A recent article<sup>1</sup> shows curves for power fets following a square law at low current but a linear law at high current. With fets like these, biasing in the middle of the square law region should give a totally linear difference curve over the whole range, because just as one fet goes off the other goes linear.

In small signal amplifications, a D2S pair might provide a current feed to a bipolar transistor which is linear in current amplification.

For audio work, the variable gain might be useful in volume expansion or compression, while a mid-biased D2S pair would be useful in radio frequency amplifiers which amplify signals from many stations at once, as it would give no intermodulation of signals for peak inputs up to  $V_p/2$ .

Similarly, there are obvious uses in oscillators. All oscillators need some gain control or their outputs would go on rising for ever. In the simplest transistor oscillators, gain control is provided by saturation of the transistor - which then has a very distorted current waveform. The hope is always that the resonant cir-

cuit will clean up the output waveform.

An oscillator could use D2S to provide distortionless variable gain to keep the loop gain verging on unity. The effect would be to remove distortion in the oscillator.

Occasionally it should be possible to use just one fet twice over! In chopper amplifiers for dc amplification, an input direct voltage passes through a reversing switch, giving a symmetrical voltage square wave to the input electrode. With a square law fet amplifier stage, the output should be an asymmetrical square wave, whose pk-pk value is proportional to the input voltage.

To summarise, there seems little doubt that matched fets can offer truly linear amplification in push-pull circuits. This linearity can be expected for all bias settings, though the allowable input swing depends on bias. Varying the bias varies mutual conductance, allowing distortionless automatic gain control. The only drawback to the approach is that fets tend to vary widely, and practical testing and selection of matched pairs with suitable characteristics remains a problem. ■

**Reference.**

1. Finnegan, T. "Going linear with power mosfets, part 2, *Electronics World + Wireless World*, Vol 97, No 1678, September 1992.

R.S.T.

**LANGREX SUPPLIES LTD**

R.S.T.

**One of the largest stockists and distributors of electronic valves, tubes and semiconductors in this country**

Over 5 million items in stock covering more than 6,000 different types, including CRT's camera tubes, diodes, ignitrons, image intensifiers, IC's, klystrons, magnetrons, microwave devices, opto electronics, photomultipliers, receiving tubes, rectifiers, tetrodes, thyratons, transistors, transmitting tubes, triodes, vidicons.

All from major UK & USA manufacturers.

Where still available.

Obsolete items a speciality. Quotations by return. Telephone/telex or fax despatch within 24 hours on stock items. Accounts to approved customers. Mail order service available.

**LANGREX SUPPLIES LTD**  
**1 Mayo Road, Croydon, Surrey CR0 2QP**  
**Tel: 081-684 1166**  
**Telex: 946708**  
**Fax: 081-684 3056**

CIRCLE NO. 132 ON REPLY CARD

**Field Electric Ltd. Tel: 0438-353781.**

**Unit 2, Marymead Workshops,  
 Willows Link, Stevenage. Herts. SG2 8AB.**

We have moved to Unit 2, Marymead Workshops, Willows Link, Stevenage, Herts. SG2 8AB. 0438 353781. 0836 640328. 0438 353959. 0438 716931.

Please ring or send S.A.E. for the following equipment: Test & Measurement Equipment Power Supplies: Transformers: Audio/Telephone Equipment: Tape Streamers: Hard Disk Drives: Simms Sips: Monitors: Comms Equipment: Computers: Motherboards: Expansion Cards etc:  
 Callers by appointment please.

**TEST AND MEASUREMENT EQUIPMENT**

- H.P. 18180A Protocol Analyzer c/w manual etc: RS232C V24/RS449 **£1250.**
- H.P.86A Computer New & Boxed **£70.**
- Tektronix 454 150MHz 2.4ns rise time scope **£250.**
- Tektronix 455 50MHz scope **£250.**
- Tektronix TM504 M/Frame c/w with DD501/WR501 LA 501 **£90.**
- Tektronix 434 25MHz scope **£95.**
- Tektronix 7B92/7A18N Plug ins **£95.**
- Tequipment D75 50MHz c/w with V4 & S2A Plug ins **£130.**
- Gould OS1100A 30MHz scope (faulty HT) **£75.**
- Lambda LES-F-03-OV-V. 0-36v 24A Digital PSU **£375.**
- Lambda LK 342A FMV 0-36v 5.2A **£120.**
- AVO RM 215F3 AC Breakdown Tester **£95.**
- Schlumberger 4000 Precision Sig: Gen: **£150.**
- Schlumberger 4900 RF-AF Measuring Unit **£150.**
- RFL 912 Gaussmeter **£120.**
- Wyse 60A Terminals new & boxed with keyboards **£195.**
- Sony Videotex Terminal KTX 1000.
- Datatruck 7 short haul multiplexer.
- Gandalf GLM 518 Line miser.

All above equipment + 17.5% vat. Please ring for c/p prices



We would like the opportunity to tender for surplus equipment Official orders credit card telephone orders accepted with Access, Amex, Diners, Visa cards. Overseas enquiries welcome c/p rates U.K. mainland only. Please ring for c/p rates not shown. All prices inc. V.A.T. unless stated. Stock list available.

CIRCLE NO. 133 ON REPLY CARD

# CLASSIFIED

TEL 081 652 8339

FAX 081 652 8931

## ARTICLES FOR SALE



### Cooke International SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS,  
VOLTMETERS, GENERATORS, OSCILLOSCOPES,  
POWER METERS, ETC. **ALWAYS AVAILABLE**  
SPECIALIST REPAIR WORK & CALIBRATION  
UNDERTAKEN

ORIGINAL SERVICE MANUALS FOR SALE  
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.,K. ENQUIRIES WELCOME,  
SEND LARGE "A3" S.A.E. FOR LISTS OF EQUIPMENT  
AND MANUALS.

ALL PRICES EXCLUDE VAT AND CARRIAGE  
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED  
OPEN MONDAY-FRIDAY 9AM-5PM

### Cooke International

ELECTRONIC TEST & MEASURING INSTRUMENTS  
Unit Four, Fordingbridge Site, Main Road, Barnham,  
Bognor Regis, West Sussex, PO22 0EB

Tel: (+44) 0243 545111/2 Fax: (+44) 0243 542457

HIGH END TEST & COMMUNICATIONS  
EQUIPMENT PURCHASED

### TURN YOUR SURPLUS TRANSISTORS, ICS ETC. INTO CASH

Immediate settlement  
We also welcome the opportunity to quote for  
complete factory clearance.

Contact:

COLES-HARDING & CO. 103 South Brink  
Wisbech, Cambs PE14 0RJ.  
ESTABLISHED OVER 15 YEARS  
Buyers of Surplus Inventory  
Tel: 0945 584188 Fax: 0945 475216

### AMAZING 486-66 OFFER

LOCAL BUS, GRAPHICS ACCELERATOR,  
8MB RAM, 250MB CACHING HARD DRIVE,  
3.52 I.44 FDD, 102 KEY UK KEYBOARD,  
12 MONTHS WARRANTY.  
£1099+VAT

486-50, 486-33, 386-33 SYSTEMS  
FOR VERBAL WRITTEN QUOTATIONS.

**GD** Graeme Duncan  
COMPUTERS LTD  
0444 244498

FOR SALE 2 Claude Lyons AC voltage stabiliser series TS o/p ut 240-0.5% V 16A 3.9 KVA complete with handbook any offers. Tel 081 940 7866.

## FREE CLASSIFIED

FOR SALE Original thinking disciplined design development & prototype engineer. Sensing & process control any location M.J. Nicholas 0202 432506

G.R. 1607-A Transfer-function and impedance bridge £200 rare valves KT88 EL34 klystrons CRTS 0635 868112. Mr Mansell, 48 Bowling Green, Thatcham RG13 3DA.

SALE 1993 issue communications engineer for use in working environment any offer considered will deliver if tried K.P. Nash/0795 660695.

WANTED W.W.2 R.1155 original as possible. Please search attics. Working? Cost reasonable as retired but could collect. Michael Lawdham 071-352-4174.

### ADVERTISERS PLEASE NOTE

For all your future enquiries  
on advertising rates,  
please contact Pat Bunce on:

Tel: 081-652 8339 Fax: 081-652 8931

## ARTICLES WANTED

### WANTED

Test equipment, receivers, valves,  
transmitters, components, cable  
and electronic scrap and quantity.  
Prompt service and cash.

M & B RADIO  
86 Bishopgate Street,  
Leeds LS1 4BB  
Tel: 0532 435649  
Fax: 0532 426881

9956

### STEWART OF READING

110 WYKEHAM ROAD,  
READING, RG6 1PL.  
TEL. 0734 268041  
FAX: 0734 351696

TOP PRICES PAID FOR ALL  
TYPES OF SURPLUS TEST  
EQUIPMENT, COMPUTER  
EQUIPMENT,  
COMPONENTS, etc.  
ANY QUANTITY

103

### WANTED

Receivers, Transmitters, Test  
Equipment, Components, Cable  
and Electronic, Scrap, Boxes,  
PCB's, Plugs and Sockets,  
Computers, Edge Connectors.  
TOP PRICES PAID FOR ALL TYPES OF  
ELECTRONICS EQUIPMENT

A.R. Sinclair, Electronics, Stockholders,  
2 Normans Lane, Rabley Heath, Welwyn,  
Herts AL6 9TQ. Telephone: 0438 812 193.  
Mobile: 0860 214302. Fax: 0438 812 347  
Telephone: 0763 246939

780

### WANTED

High-end Test Equipment, only brand  
names as Hewlett-Packard,  
Tektronix, Rhode & Schwarz, Marconi  
etc. Top prices paid.

Please send or fax your offer to:  
**HTB ELEKTRONIK**  
Alter Apeler Weg 5, 2858 Schiffdorf,  
West Germany  
TEL: 01049 4706 7044  
FAX: 01049 4706 7049

A very  
**Merry Christmas**  
to all our  
 advertisers

WANTED VALVES especially KT66,  
KY88, PX4, PX25 (also transistors IC's  
capacitors, valve radios/hi-fi). If possible  
send written list for offer by return to  
Billington Export, 1E Gilmans Ind  
Estate, Billingham, Sussex, RH14 9EZ.  
Tel 0403 784961. Fax 0403 783519.

## WE WANT TO BUY !!

**IN VIEW OF THE EXREMELY  
RAPID CHANGE TAKING PLACE  
IN THE ELECTRONICS  
INDUSTRY, LARGE QUANTITIES  
OF COMPONENTS BECOME  
REDUNDANT. WE ARE CASH  
PURCHASERS OF SUCH  
MATERIALS AND WOULD  
APPRECIATE A TELEPHONE  
CALL OR A LIST IF AVAILABLE.  
WE PAY TOP PRICES AND  
COLLECT.**

**R.HENSON LTD.**

**21 Lodge Lane, N.Finchley,  
London N12 8JG.**

**5 Mins, from Tally Ho Corner.  
TELEPHONE**

**081-445-2713/0749**


**FAX 081-445-5702.**


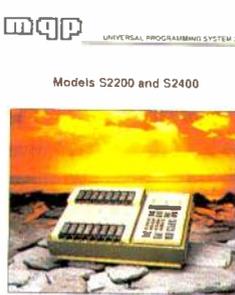
# ELECTRONIC UPDATE

Contact Pat Bunce on  
081-652 8339

A regular advertising feature enabling  
readers to obtain more information  
on companies' products or services.




**mqp** UNIVERSAL PROGRAMMING SYSTEM 2000  
Models S2200 and S2400

Gang and Set Programmers for  
24, 28 & 32 pin EPROMs, EEPROMs,  
FLASH, Emulators and OTPs up to 8M bit.

The system 2000 is an ideal programmer for the production environment. Fast programming results in high throughput and rigorous verification leads to improved quality control. Single key functions and checks against misoperation facilitates its use by unskilled staff.

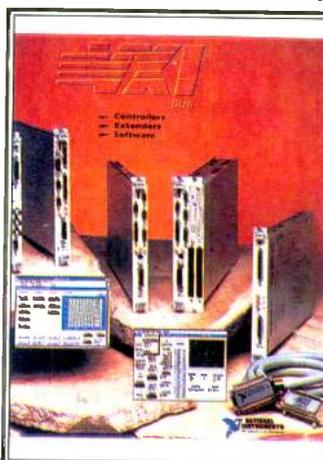**MQP ELECTRONICS LTD.**  
Tel: 0666 825146  
Fax: 0666 825141  
CIRCLE NO. 142 ON REPLY CARD



## FREE VXI BROCHURE

The National Instruments VXI brochure describes the company's embedded PC and GPIB controllers, MXibus interface kits for multiple platforms, and NI-VXI, LabWindows, and LabVIEW software for developing and controlling VXI instrumentation systems.

**NATIONAL INSTRUMENTS**  
Tel: 0800 289877  
CIRCLE NO. 146 ON REPLY CARD

**OLSON** FUSED SUPER SLIM MAINS DISTRIBUTION PANELS WITH DOUBLE POLE SWITCHED SOCKETS

OLSON ELECTRONICS LIMITED is a leading manufacturer in the field of mains distribution panels of every shape and size to suit a variety of needs. For use in Broadcasting, Computing, Data Communications, Defence, Education, Finance, Health etc. All panels are manufactured to BS5733. BRITISH AMERICAN, FRENCH, GERMAN CEE22/IEC and many other sockets. Most countries catered for. All panels are available ex-stock and can be bought direct from OLSON.

**Olson Electronics Limited**  
Tel: 081 885 2884  
Fax: 081 885 2496  
CIRCLE NO. 143 ON REPLY CARD



DATAUPDATE is Electronics Weekly's section for advertisers to market their product information. From catalogues to newsletters Data Update is designed to present your product information in a clear and attractive manner, whilst our colour coded enquiry numbers help readers to obtain the information they need fast.

CIRCLE NO. 147 ON REPLY CARD

**IR GROUP** FIRST FOR QUALITY AND SERVICE

TRIED AND TESTED USED EQUIPMENT

LONDON 0753 670000 MANCHESTER 061 971 4231  
0753 677000 061 903 276  
APRIL 1993

IR Group, Europe's leading supplier of used instrumentation, has published the latest update of models available. With a range from power supplies to network analysers, most items are available on short delivery and come with a 12 month parts and labour warranty. For a detailed quotation call

**0753 670000.**  
CIRCLE NO. 144 ON REPLY CARD

**Cirkit**

Inductors  
Variable Coils  
Filters  
Surface Mount  
Comms ICs  
Switches

**TOKO** 2nd Edition  
RF CATALOGUE

## 2nd EDITION TOKO RF CATALOGUE

Cirkit have just published the 2nd Edition of the Toko RF Catalogue, featuring details of Tokos' extensive range of RF coils, inductors, filters and comms ICs.

The 128 page catalogue includes many new products such as; Surface mount high current inductors, surface mount multilayer inductors, helical filters at 2.5GHz and a new section of push button and tact switches.

**Cirkit Distribution Ltd, Park Lane, Broxbourne, Herts, EN10 7NQ**  
Tel: (0992) 441306  
Fax: (0992) 441306  
CIRCLE NO. 148 ON REPLY CARD

**ELECTRONIC WORLD**  
+ WIRELESS WORLD

Cheap DSP to transform audio crop design?

Working with switched capacitor filters

Germany's Imperial wireless system

Tests discredit CFA theory

Squashing parasitic oscillations

SPECIAL FEATURE: BUILDING BLOCKS FOR POWER LOCKING LOGS

ELECTRONIC UPDATE is Electronic World and Wireless World's section for advertisers to market their product information. From catalogues to newsletters, Data Update is designed to present your product information in a clear and attractive manner while our "CIRCLE NUMBERS" help readers to obtain the information they need fast.

CIRCLE NO. 145 ON REPLY CARD

**£295.00 vat**


## High Speed EPROM & FLASH Programming from your PC

- Programs EPROMs to 4 Mbits/32-pins
- Superfast 8, 16 & 32-bit programming
- Approved algorithms
- Menu driven software included
- Sophisticated editor functions
- Easy file management
- FREE demo disk available

**Stag Programmers Limited**  
Marlfield Welwyn Garden City,  
Hertfordshire, AL7 1JT UK  
Tel: (0707) 332148  
Fax: (0707) 371503

CIRCLE NO. 149 ON REPLY CARD


**SPECTRUM ANALYSERS**

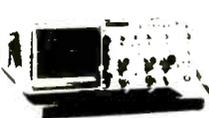

ADVANTEST TR4131 3.5GHz portable analyser £4500  
 HP3580A 5Hz-50kHz audio spectrum analyser £1500  
 HP3582A dual-channel 25kHz analyser £3500  
 HP3585A 20Hz-40MHz GPIB analyser £4500  
 HP8558B 182C 1500MHz analyser £2000  
 HP182C 8559A 0.01-21GHz spectrum analyser £4500  
 HP8565A 0.01-22GHz (or 40GHz with ext mixers) £4500  
 HP8569A 10MHz-22GHz (external mixing to 115GHz) HPIB £6000  
 MARCONI TF2370 110MHz £1250  
 MARCONI TF2370/2373 as above but extended to 1250MHz £2500  
 TEKTRONIX 2711 1.8GHz portable analyser £4950

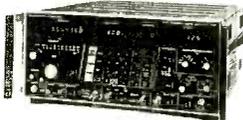**MARCONI INSTRUMENTS**

2017 signal generator 10kHz-1024MHz  
 microprocessor-controlled cavity-tuned low-noise AM/FM, +194dbm output. Few only FREE CALIBRATION INCLUDING FREE CALIBRATION - £2000 each.



2828A/2829 digital simulator/analyser £1000  
 2830 multiplex tester £1500  
 6059A signal source 12-18GHz £750  
 6140 GPIB adapter £100  
 6460/6420 power meter 10MHz-12.4GHz 0.3uW-10mW £350  
 6460/6423 power meter 10MHz-12.4GHz 0.3mW-3W £400  
 6600A sweep generator 26.5-40GHz £1000  
 6700B sweep oscillator 8-12.4GHz & 12.4-18GHz £1000  
 6960/6910 digital RF power meter 10MHz-20GHz GPIB £1000  
 6912 power sensor 30kHz-4.2GHz for above series £150  
 893B audio power meter £350  
 OA2805A PCM regenerator test set £750  
 TF2370 110MHz spectrum analyser £1750  
 TF2910/4 non-linear distortion (video) analyser £1000  
 TF2914A TV insertion signal analyser £1250  
 TF2910 TV interval timer £500

**RALFE ELECTRONICS**

36 EASTCOTE LANE S HARROW MIDDLESEX HA2 8DB  
 TEL: 081-422 3593. FAX: 081-423 4009

**NOW IN 40th YEAR**



DISTRIBUZIONE E ASSISTENZA ITALY: TCL RADIO, ROMA (06)890763

**TEST EQUIPMENT**

BRUEL & KJAER 2511 vibration meter set/1621 filter £2250  
 BRUEL & KJAER 2610 measuring amplifier £1000  
 BRUEL & KJAER 2307 level recorder £1000  
 BRUEL & KJAER 2317 portable level recorder £1850  
 BRUEL & KJAER 1618 band pass filter £750  
 BRUEL & KJAER 3204 tapping machine £1000  
 BRUEL & KJAER 3513 portable vibration analyser £3500  
 BRUEL & KJAER 2515 vibration analyser £5000  
 AVO RM215L-2 insulation & breakdown tester £650  
 DATRON 1065 digital multimeter £750  
 DRANETZ 626 mains disturbance analyser/2x PA-6001 £1250  
 DRANETZ 606-3 line disturbance analyser £275  
 FLANN MICROWAVE 27072 frequency meter 73-113GHz £275  
 FLUKE 5100A calibrator £8000  
 KEITHLEY 192 programmable dmm £400

**MUCH MORE, FULLY RE-FURBISHED, FULLY GUARANTEED TEST EQUIPMENT AVAILABLE FROM STOCK. PLEASE REQUEST OUR CURRENT LISTINGS. WE CAN FAX LIST & SHIP GOODS WORLD-WIDE. HIGH-END EQUIPMENT ALWAYS WANTED FOR STOCK.**

■ CALL US NOW ■

MAURY MICROWAVE 8650E TNC-calibration kit £1500  
 NAGRA IV - S1 tape recorder £2000  
 PHILIPS PM5193 synthesised function generator £1500  
 PHILIPS PM2534 digital multimeter £450  
 PHILIPS PM8272 XY & Xtdual-gen analogue plotter £550  
 RACAL 2101 frequency counter 21GHz £1600  
 RACAL 9008 automatic modulation meter £325 9009 £300  
 RACAL 9081 synthesised AM/FM sig' gen' 5-520mHz £650  
 RACAL 9300 RMS voltmeter -80dB to +50dB £350  
 RACAL 9341 LCR databridge component tester £450  
 RACAL-DANA 9302 RF milli-voltmeter 1.5GHz £1000  
 RACAL-DANA 9303 level meter, digital £500  
 ROBERTS & ARMSTRONG 10-cable end-cur measure' unit £150  
 TEKTRONIX TM503/SG503/TG501/PG506 scope calibrator £2250  
 TEKTRONIX J16 digital photometer £250  
 TEKTRONIX J16 digital photometer £2750  
 TEKTRONIX AA501A distortion analyser (plug-in) unit £750  
 TEKTRONIX 7000-series MANY CONFIGURATIONS, PLEASE CALL £2750  
 TELONIC 1205A 1-1500MHz sweep generator £1000  
 WAVETEK 2000 0-1400MHz sweep generator £750  
 WAYNE KERR B905 automatic precision bridge £950

**HEWLETT PACKARD**



331A distortion meter £200  
 339A distortion meter £1500  
 3406A sampling voltmeter £250  
 355C attenuator DC-1GHz 0-11db & 355D 0-120db £125  
 3325A synthesizer/function generator £1500  
 3335A synthesizer/level generator with option 01 £1500  
 3552A transmission test set £1250  
 3562A dynamic signal analyser £7000  
 3711A/3712A microwave link analyser (MLA) with 3793B & 3730B/3736B RF down-converter (1.7-4.2GHz) £4000  
 3781A pattern generator £1250  
 3782A error detector £1250  
 400FL mV-Meter 100uV-300V Is. 20Hz-4MHz £350  
 415E swr meter £350  
 4274A multi-frequency (100Hz-100kHz) LCR component meter £4000  
 4276A/001 LCZ meter £1750  
 432A/478A microwave power meter 10MHz-10GHz £400  
 432A/486A uwave power meter 26.5-40GHz (waveguide) £600  
 5005B signature multi-melet, programmable £500  
 532A (R) frequency meter 26.5-40GHz waveguide WG28 £150  
 5342A 18GHz frequency counter HPIB option £1500  
 6253A dual power supply 0-20V 0-3A twice £225  
 6825A bipolar power supply/amp - 20 to + 20vdc 0-1A £350  
 70300A tracking generator plug-in unit £2000  
 70907A external mixer for 70000-ser spectrum analyser £1750  
 7035B X-Y single pen analogue chart recorder £350  
 779D dual-directional coupler 1.7-12.4GHz (also others) £350  
 8011A pulse generator 0.1Hz-20MHz £500  
 816A slotted line 1.8-18GHz with carriage 809C & 447B £500  
 8405A vector voltmeter, voltage & phase to 1000MHz £950  
 8406A comb generator £1000  
 8447A RF amplifier 0.1-1300MHz, 22db gain, 0.1W o/p £500  
 8505A network analyser system including 8503A S-parameter test set and 8501A storage normaliser £5000  
 8601A 110MHz sweep generator £500  
 8620C sweep generator, many plug-in units available £500  
 8671A synthesised signal generator 2-6.2GHz £2500

**PLEASE NOTE: ALL OUR EQUIPMENT IS NOW OPERATION-VERIFICATION TESTED BEFORE DESPATCH BY INDEPENDENT LABORATORY**

We would be pleased to handle all grades of calibration or NAMAS certification by same laboratory at cost price. All items covered by our 90-day parts and labour guarantee and 7-day 'Right to Refuse' (money back) warranty.


**ALL PRICES SUBJECT TO ADDITIONAL VAT AND CARRIAGE**

CIRCLE NO. 134 ON REPLY CARD

**INDEX TO ADVERTISERS**

	PAGE		PAGE
Amplicon Liveline	40	M & B Electrical Supplies Ltd	70
Antex	75	M & B Radio (Leeds)	63
Bull Electrical	7	MQP Electronics	63
Citadel Products Ltd	IFC	Number One Systems	8
Dataman Programmers Ltd	OBC	Pico Technology Ltd	62
Display Electronics Ltd	48	Powerware	8
Electrovalue Ltd	75	Ralfe Electronics	88
Field Electric	84	Research Communications	2
Halcyon Electronics Ltd	39	Robinson Marshall	64
Integrated Measurement	57	Seetrax Ltd	33
Johns Radio	69	Smart Communications	39, 57
JPG Electronics	62	Stewart of Reading	75
Kinloch	63	Surrey Electronics Ltd	75
Kestral Electronics	62	Telnet	57
Labcentre	20	Texas Instruments	2
Langrex	84	Those Engineers	39
Logicom	62	Tsien Ltd	47
		Ultimate Technology	IBC


# FROM CONCEPT TO ARTWORK IN 1 DAY

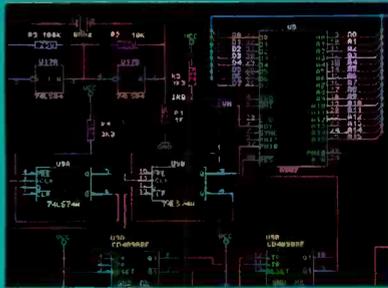


Your design ideas are quickly captured using the ULTIcap schematic design Tool. ULTIcap uses REAL-TIME checks to prevent logic errors. Schematic editing is painless; simply click your start and end points and ULTIcap automatically wires them for you. ULTIcap's auto snap to pin and auto junction features ensure your netlist is complete, thereby relieving you of tedious netlist checking.




ULTIshell, the integrated user interface, makes sure all your design information is transferred correctly from ULTIcap to ULTIboard. Good manual placement tools are vital to the progress of your design, therefore ULTIboard gives you a powerful suite of REAL-TIME functions such as, FORCE VECTORS, RATS NEST RECONNECT and DENSITY HISTOGRAMS. Pin and gate swapping allows you to further optimise your layout.

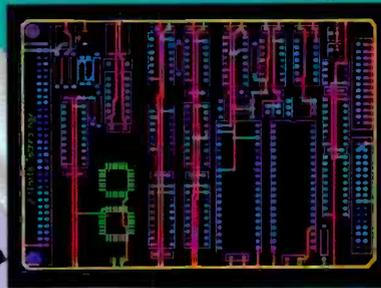

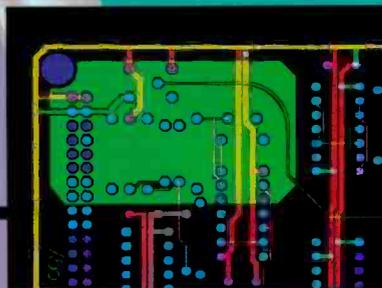
Now you can quickly route your critical tracks. ULTIboard's REAL-TIME DESIGN RULE CHECK will not allow you to make illegal connections or violate your design rules. ULTIboard's powerful TRACE SHOVE, and REROUTE-WHILE-MOVE algorithms guarantee that any manual track editing is flawless. Blind and buried vias and surface mount designs are fully supported.



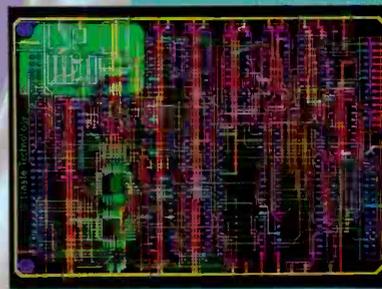If you need partial ground planes, then with the Dos extended board systems you can automatically create copper polygons simply by drawing the outline. The polygon is then filled with copper of the desired net, all correct pins are connected to the polygon with thermal relief-connections and user defined gaps are respected around all other pads and tracks.



ULTIboard's autorouter allows you to control which parts of your board are autorouted, either selected nets, or a component, or a window of the board, or the whole board. ULTIboard's intelligent router uses copper sharing techniques to minimise route lengths. Automatic via minimisation reduces the number of vias to decrease production costs. The autorouter will handle up to 32 layers, as well as single sided routing.

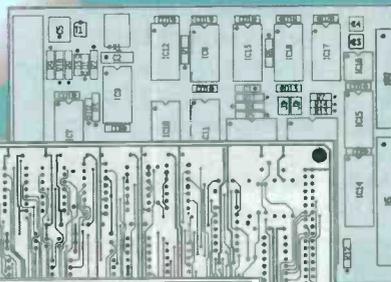

ULTIboard's backannotation automatically updates your ULTIcap schematic with any pin and gate swaps or component renumbering. Finally, your design is post processed to generate pen / photo plots, dot matrix/laser or postscript prints and custom drill files.

**CIRCLE NO. 100 ON REPLY CARD**


## NEW

ULTIboard/ULTIcap evaluation system:

- all features of the bigger versions
- full set of manuals
- design capacity 350 pins.

Price incl. S & H, excl. VAT: **£ 75**

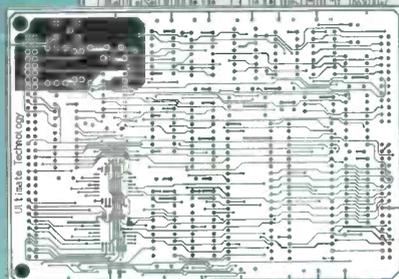Purchase price is 100% credited when upgrading to a bigger version. \* Also suitable for study & hobby



ULTIboard PCB Design/ULTIcap Schematic Design Systems are available in low-cost DOS versions, fully compatible with and upgradable to the 16 and 32 bit DOS-extended and UNIX versions, featuring unlimited design capacity.

*The European quality alternative*

## ULTICAP + ULTIBOARD = MAXIMUM PRODUCTIVITY

ULTimate Technology UK Ltd. • 2 Bacchus House, Calleva Park, Aldermaston Berkshire RG7 4QW • Fax: 0734 - 815323 • Phone: 0734 - 812030

# The smallest, most powerful personal programmer you can buy!

Owning the worlds best selling portable programmer/emulator is just a phone call away. From engine management to Antarctic survey teams, the powerful and versatile S4 goes where others get left behind.

A 32 pin ZIF socket programs a huge library of EPROMs, EEPROMs and FLASH devices up to 8Mbit. And our unique user loadable Library means that new parts can be added quickly, and at no cost. All software upgrades are free and available for 24hr download from our high speed bulletin boards.

## Emulation

See your code running before committing yourself to an EPROM. With S4's powerful and easy-to-use internal emulation system, download your code to S4, press 'EMULATE', and your target system runs in real time as if an EPROM was plugged in to the socket. Use S4's 'EDIT' command to make minor alterations to your code and see the changes happen *immediately* - just one reason why S4 is used by the world's car manufacturers to develop advanced engine management systems in real time! With S4 emulation there's no need for trailing cables or external power sources; earth loop problems are a thing of the past. S4 even emulates RAM.

## Remote Control

As well as being totally stand alone and self contained, S4 can be operated remotely via it's serial port at speeds up to 115,200 Baud. We supply you with a FREE disk containing custom terminal software and a pop-up TSR communications utility.

## The Company

If you are looking for a supplier with longevity and stability, then you'll be pleased to learn that

Dataman has been designing and selling innovative programmers world-wide for over 15 years. As well as having sales and support offices in both the UK and the USA, we supply the world demand for our products via a network of approved dealers stretching from Norway to Australia.

## The Package

S4 comes fully charged and configured for immediate use. You get a mains charger, emulation lead, write lead, personal organiser instruction manual, MS-DOS communications software, spare Library ROM and a 3 year guarantee. Optional modules available for serial EPROMs, 40 pin EPROMs and microcontrollers.

## Availability

S4 is always in stock. Phone through your credit card details to ensure *next working day* delivery. Full 30 day no-risk refund.

Only **£495** plus VAT  
4 Mbit upgrade £95 plus VAT  
Full 30 day money back guarantee!



Size: 186 x 111 x 46mm  
Weight: 515g

**DATAMAN**  
Dataman Programmers Ltd

**Credit card hotline:**  
**0300 320719**  
for same-day dispatch

