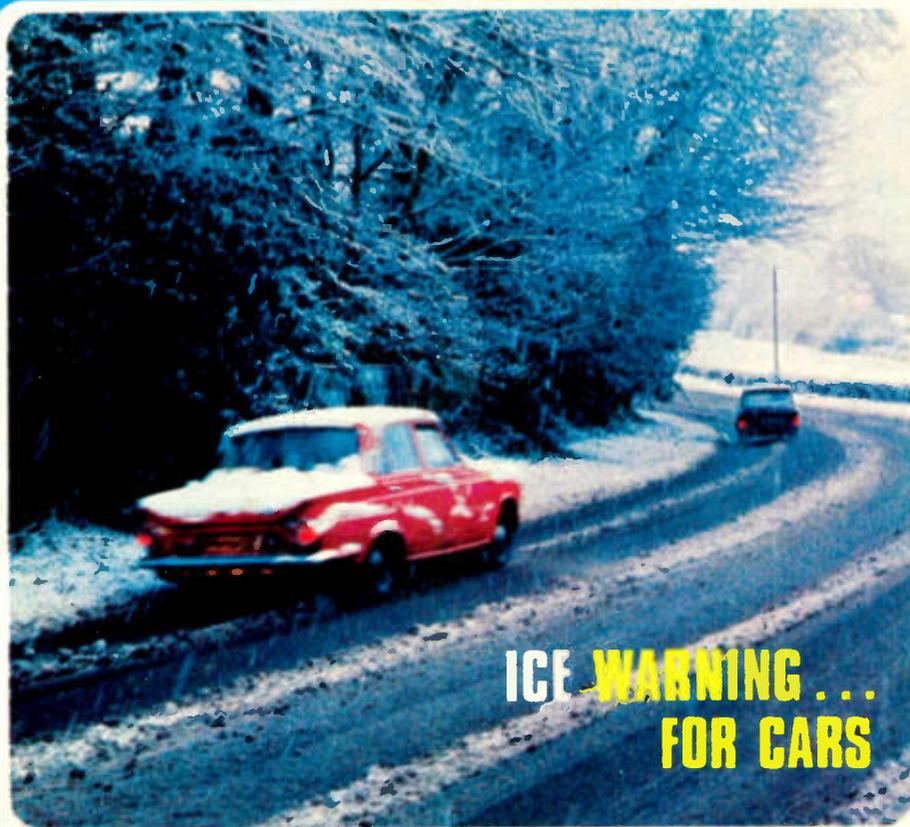


Practical projects to build at home

everyday electronics

JAN. 75
20p



ICE WARNING ...
FOR CARS

PLUS!

THEORY

PRACTICE

**POPULAR
FEATURES**

*Electronics
made easy!*

2 Band Superhet



TUNER



**RAIN
ALARM**



NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT.

BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER.


★ 4 Transistor Earpiece Radio ★ Signal Tracer ★ Signal Injector ★ Transistor Tester NPN-PNP ★ 4 Transistor Push Pull Amplifier ★ 5 Transistor Push Pull Amplifier ★ 7 Transistor Loudspeaker Radio MW/LW ★ 5 Transistor Short Wave Radio ★ Electronic Metronome ★ Electronic Noise Generator ★ Batteryless Crystal Radio ★ One Transistor Radio ★ 2 Transistor Regenerative Radio ★ 3 Transistor Regenerative Radio ★ Audible Continuity Tester ★ Sensitive Pre-Amplifier.

★ 24 Resistors ★ 21 Capacitors ★ 10 Transistors ★ 31 loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12-way connectors ★ 2 Volume controls ★ 2 Slider Switches ★ 1 Tuning Condenser ★ 3 Knobs ★ Ready Wound Coils ★ Ferrite Rod ★ 64 yards of wire ★ 1 yard of sleeving, etc. ★ Parts price list and plans 50p (FREE with parts).

Total Building Costs
£7-23 P.P. & Ins. 44p.
(Overseas P & P £1-85p.)
(+ 8% VAT 57p)

ROAMER TEN

with VHF including aircraft. 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeakers. 9 Tunable Wavebands. MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600 mw transistors. Car Aerial and Tape Recording Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band, Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts). **Total building costs** £8-50 P.P. & Ins. 52p (Overseas P & P £1-85) (+ 8% VAT 66p)

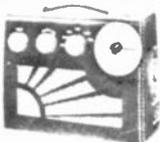

NEW EVERYDAY SERIES

Build this exciting New series of designs
E.V. 5 6 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5½" x 2½" approx. Parts price list and Plans 20p. Free with parts.

Total Building Costs £2-95 P.P. & Ins. 30p (Overseas P & P £1-25p) (+ 8% VAT 23p)

E.V. 6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts price list and Plans 30p. Free with parts.

Total Building Costs £3-60 P.P. & Ins. 30p (Overseas P & P £1-25p) (+ 8% VAT 29p)

E.V. 7 Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" loudspeaker. Parts price list and easy build plans 35p. Free with parts.

Total Building Costs £4-08 P.P. & Ins. 31p (Overseas P & P £1-85) (+ 8% VAT 32p)

ROAMER EIGHT Mk 1

NOW WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mw transistors. Car aerial and Tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet Loudspeakers. Air spaced ganged tuning condenser Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

Total Building Costs £6-98 P.P. & Ins. 47p (Overseas P & P £1-85) (+ 8% VAT 56p)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT



Nine Transistors, 9 Tunable wavebands as Roamer Ten, built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mw transistors. 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange control. Attractive all white case with red grille and carrying strap. Size 9½" x 7" x 2½" approx. Parts Price list and Plans 40p (FREE with parts)


Total Building Costs £6-95 P.P. & Ins. 44p (Overseas P & P £1-85p) (+ 8% VAT 55p)

POCKET FIVE

Now with 3" loudspeaker

3 Tunable wavebands. MW, LW, and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5½" x 1½" x 3½" approx. Plans and parts price list 20p. (Free with parts).

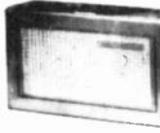Total Building Costs £2-50 P.P. & Ins. 26p (Overseas P & P £1-25p) (+ 8% VAT 20p)



TRANSONA FIVE

now with 3" loudspeaker Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 20p (Free with parts).

Total Building Costs £2-75 P.P. & Ins. 28p (Overseas P & P £1-25p) (+ 8% VAT 21p)


TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5½ x 2½in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 35p (FREE with parts).

Total Building Costs £4-48 P.P. & Ins. 38p (Overseas P & P £1-25) (+ 8% V.A.T., 36p)

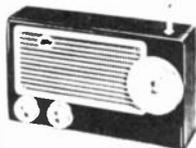• Callers side entrance "Lavelis" Shop
• Open 10-1, 2.30-4.30 Mon.-Fri.—9-12 Sat.



RADIO EXCHANGE CO

61a HIGH STREET, BEDFORD, MK40 1SA Tel. 0234 52367

Reg. no. 788372

I enclose £..... for.....

Name.....

Address.....

(Dept. E.E.1.)



Well here's a fine how d'y do! Santa himself caught in the act of 'borrowing' a few of our catalogues . . . and Rudolph laughing his silly head off! We can't see the old chap getting away with it, but we did warn him to lay in a large stock of catalogues. Well, let's hope he gets bailed out in time to deliver one to you. The demand for this famous components catalogue grows by leaps and bounds each year. We at Home Radio Components work hard on it to make sure it more than comes up to everybody's expectations. If you haven't seen one you really should treat yourself for Christmas. It costs 65 pence plus 33p packing and postage, but with it we give you 14 vouchers, each worth 5p when used as directed. That means you can get 70 pence back. In which case this magnificent publication will have cost you only 28 pence! It can be bought over our counter at Mitcham for only 65p . . . or send the coupon below with a cheque or postal order today for 98 pence. If by any chance Santa Claus is still 'detained for questioning' we'll send your catalogue round by postman!

The price of 98p applies only to customers in the U.K. and to B.F.P.O. addresses.



**A Happy
Christmas
to all our
readers.**

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADID (Components) LTD., Dept. EE,
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No.
London 912966)



HOME RADIO (Components) LTD, Dept EE, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

Everyday Electronics, January 1975

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50. 3 for ONLY 55p + p & p 30p
SPECIAL One as above PLUS Power Transistors ONLY 55p each + p & p 15p
FAXOLINE BOARDS 71" x 9" approx. 4 for 80p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16 1/2" x 4" approx. 2 for 55p

DECON-DALO 33PC Marker

Fine resistant printed circuit marker pen 99p each

VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 1 matric 55p

REPANCO CHOKES & COILS

HF Chokes
 CH1. 2.5mH 25p CH2. 5.0mH 30p
 CH3. 7.5mH 31p CH4. 10mH 33p
 CH5. 1.5mH 28p

COILS
 DRX1 Crystal set 21p DR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1/2" Cores & Formers 8p
 1/4" Cores & Formers 10p

SWITCHES

1P/DT Toggle 36p 8P/ST Toggle 80p

FUSES

1/4" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
 QUICK-BLOW 5p ea.

EARPHONES

Crystal 2.5mm plug 42p
 Crystal 3.5mm plug 42p
 8 ohms 2.5mm plug 22p
 8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

R1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.85

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007. 60 ohms Imp. Insertion loss 3dB £1.21

CAR STEREO SPEAKERS

(Angled) £8.85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)
 No. Length Width Height Price
 BV1 8" x 5 1/2" x 2" £1.10
 BV2 11" x 6" x 3" £1.45

ALUMINIUM BOXES

BA1 5 1/2" x 2 1/2" x 1 1/2" 45p
 BA2 4" x 4" x 1 1/2" 42p
 BA3 4" x 2 1/2" x 1 1/2" 42p
 BA4 5 1/2" x 4" x 1 1/2" 50p
 BA5 4" x 2 1/2" x 2" 42p
 BA6 3" x 2" x 1" 34p
 BA7 7" x 6" x 2 1/2" 70p
 BA8 8" x 6" x 3" 80p
 BA9 8" x 4" x 2" 85p
 P & P 10p on each box

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9.5.30 p.m. Tel. 61593


BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50

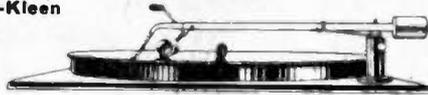

Ref. B Stylus & Turntable Cleaning Kit 34p
 Ref. 36A. Record/Stylus Cleaning Kit 33p
 Ref. 43. Record Care Kit £2.42
 Ref. 31. Cassette Head Cleaner 58p
 Ref. 32. Tape Editing Kit £1.68
 Model 9. Wire Stripper/Cutter 83p

Ref. 46. Spirit level 62p
 Ref. P. Hi-Fi Cleaner 31p
 Ref. 32A. Stylus Balance £1.87
 Ref. J. Tape Head Cleaning Kit 62p
 Ref. 56. Hi-Fi Stereo Hints & Tips 42p
 Ref. 45. Auto changer groove cleaner £1.08

ANTEX SOLDERING IRONS

X25. 25 watt £2.05
 CCN 240. 15 watt £2.48
 Model G. 18 watt £2.26
 SK2. Soldering Kit £3.25
 STANDS: ST3. Suitable for all models £1
 SOLDER: 188WG Multicore 7oz £1.61
 228WG 7oz £1.61. 188WG 22ft 51p
 228WG Tube 33p

PLUGS AND SOCKETS

PLUGS
 P8 1 D.I.N. 2 Pin (Speaker) 0-11
 P8 2 D.I.N. 3 Pin 0-12
 P8 3 D.I.N. 4 Pin 0-18
 P8 4 D.I.N. 5 Pin 180° 0-16
 P8 5 D.I.N. 5 Pin 240° 0-17
 P8 6 D.I.N. 6 Pin 0-18
 P8 7 S.I.N. 7 Pin 0-18
 P8 8 Jack 2.5mm Screened 0-18
 P8 9 Jack 3.5mm Plastic 0-12
 P8 10 Jack 3.5mm Screened 0-18
 P8 11 Jack 1/2" Plastic 0-15
 P8 12 Jack 1/2" Screened 0-22
 P8 13 Jack Stereo Screened 0-26
 P8 14 Phono 0-10
 P8 15 Car Aerial 0-22
 P8 16 Co-Axial 0-18

ANTEX BITS and ELEMENTS

Bits No.
 102 For model CN240 3/32" 42p
 104 For model CCN240 3/16" 42p
 1100 For model CCN240 3/32" 42p
 1101 For model CCN240 3/8" 42p
 1102 For model CCN240 1/2" 42p
 1020 For model G240 3/32" 42p
 1021 For model G240 1/8" 42p
 1022 For model G240 3/16" 42p
 50 For model X25 3/32" 48p
 51 For model X25 1/8" 48p
 52 For model X25 3/16" 48p

ELEMENTS

ECN 240 £1.30 EOCN 240 £1.32
 EG 240 £1.07 EX 25 £1.18

ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No. Qty. Description Price
 C1 200 Resistors mixed values approx. count by weight 0.55
 C2 150 Capacitors mixed values approx. count by weight 0.55
 C3 50 Precision Resistors 1%, 2%, mixed values 0.55
 C4 75 1/4W Resistors mixed preferred values 0.55
 C5 5 Pieces assorted Ferrite Rods 0.55
 C6 2 Tuning Gangs, MW/LW VHF 0.55
 C7 1 Pack Wire 50 metres assorted colours 0.55
 C 8 10 Reed Switches 0.55
 C 9 3 Micro Switches 0.55
 C10 15 Assorted Pots & Pre-Set 0.55
 C11 5 Jack Sockets 3 x 3.5m 2 Standard Switch Type 0.55
 C12 30 Paper Condensers preferred types mixed values 0.55
 C13 20 Electrolytics Trans. types 0.55
 C14 1 Pack assorted Hardware—Nuts/Bolts, Grommets etc. 0.55
 C15 5 Mains Slide Switches 0.55
 C16 20 Assorted Tag strips & Panels 0.55
 C17 10 Assorted Control Knobs 0.55
 C18 4 Rotary Wave Change Switches 0.55
 C19 2 Relays 6—24V Operating 0.55
 C20 1 Pack sheets of Copper Laminate 20 sq. ins 0.55

INLINE SOCKETS

P8 21 D.I.N. 2 Pin (Speaker) 0-14
 P8 22 D.I.N. 3 Pin 0-20
 P8 23 D.I.N. 5 Pin 180° 0-20
 P8 24 D.I.N. 5 Pin 240° 0-20
 P8 25 Jack 2.5mm Plastic 0-16
 P8 26 Jack 3.5mm Plastic 0-16
 P8 27 Jack 1/2" Plastic 0-30
 P8 28 Jack 1/2" Screened 0-35
 P8 29 Jack Stereo Plastic 0-30
 P8 30 Jack Stereo Screened 0-38
 P8 31 Phono Screened 0-18
 P8 32 Car Aerial 0-22
 P8 33 Co-Axial 0-22

SOCKETS

P8 35 D.I.N. 2 Pin (Speaker) 0-08
 P8 36 D.I.N. 3 Pin 0-11
 P8 37 D.I.N. 5 Pin 180° 0-11
 P8 38 D.I.N. 5 Pin 240° 0-11
 P8 39 Jack 2.5mm Switched 0-12
 P8 40 Jack 3.5mm Switched 0-12
 P8 41 Jack 1/2" Switched 0-20
 P8 42 Jack Stereo Switched 0-30
 P8 43 Phono Single 0-08
 P8 44 Phono Double 0-10
 P8 46 Co-Axial Surface 0-10
 P8 47 Co-Axial Flush 0-20

LEADS

LS1 Speaker lead 2 pin D.I.N. plug to open ends approx. 3 metres long (coded) 0.20

CABLES

CP 1 Single Lapped Screen 0.07
 CP 2 Twin Common Screen 0-11
 CP 3 Stereo Screened 0-12
 CP 4 Four Core Common Screen 0-22
 CP 5 Four Core Individually Screened 0-20
 CP 6 Microphone Fully Braided Cable 0-10
 CP 7 Three Core Mains Cable 0-09
 CP 8 Twin Oval Mains Cable 0-07
 CP 9 Speaker Cable 0-05
 CP 10 Low Loss Co-Axial 0-18

CARBON POTENTIOMETERS

Log and Lin
 47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
 VC 1 Single Leas Switch 0-15
 VC 2 Single D.P. Switch 0-28
 VC 3 Tandem Leas Switch 0-48
 VC 4 1K Lin Leas Switch 0-15
 VC 5 100K Log anti-Log 0-48

HORIZONTAL CARBON PRESETS

0-1 watt 0.06 each
 100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

IT'S NEW IT'S POWERFUL AND— IT LOOKS GOOD!



THE LEGIONAIRE STEREO AMPLIFIER
ORDER NOW— ONLY £39.95 p & p 50p.
 Or write for full details

WORLD SCOOP JUMBO SEMICONDUCTOR PACK

Transistors - Germ. and Silicon Rectifiers Diodes - Triacs - Thyristors - I.C.'s and Zeners ALL NEW AND CODED.
APPROX 100 PIECES
 Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.
Only £2 p. & p. 20p

RECORD STORAGE/ CARRY CASES

7" EP. 18 1/2" x 7" x 8". (50 records) £2.10
 12" LP. 13 1/2" x 7 1/2" x 12 1/2". (50 records) £2.95

CASSETTE CASES

Hold 12. 10" x 3 1/2" x 5". Lock & Handle. £1.30

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able 115v. T03. Metal Case.
OUR SPECIAL PRICE 8 for 61

LOW COST CAPACITORS

0.1µF 400v. 8p. each
 500µF 50v. Elect. 10p each

REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tapplings 4v, 7v, 8v, 10v, 14v, 15v, 17v, 19v, 21v, 25v, 31v, 33v, 40, 50 and 25v-0-25v.

CARTRIDGES

ACOS
 GP91-18C 200mV at 1.2cm/sec £1.55
 GP93-1 280mV at 1cm/sec £1.95
 GP96-1 100mV at 1cm/sec £2.80
 TTC
 J-2005 Crystal/Hi Output £1.05
 J-2010C " " " " Compatible £1.20
 J-20088 Stereo/Hi Output £1.75
 J-2105 Ceramic/Med Output £1.95
 J-2203 Magnetic 5mV/cm/sec. including stylus £1.05
 J-22038 Replacement stylus for above £2.85
 AT-55 Audio-technica magnetic cartridge 4mV/cm/sec £3.30

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1/8th watt available in PAKS of 50 pieces, assorted into the following groups:—
 R1 50 Mixed 100 ohms-820 ohms 50p
 R2 50 Mixed 1K ohms-8.2K ohms 50p
 R3 50 Mixed 10K ohms-82K ohms 50p
 R4 50 Mixed 100K ohms-1 Meg. ohms 50p
 THESE ARE UNBEATABLE PRICES JUST 1p EACH INCL. V.A.T.

BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C60, 36p C90, 48p C120, 60p

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 2 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f=1KHz	0.25%
LOAD IMPEDANCE	—	8 - 16 Ω
INPUT IMPEDANCE	f=1KHz	100 k Ω
FREQUENCY RESPONSE ± 3dB	Po=2 WATTS	50 Hz - 25KHz
SENSITIVITY FOR RATED O/P	Vs=25V. Ri=8 Ω f=1KHz	75mV. RMS
DIMENSIONS	—	3" x 2 1/4" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 Ω f = 1 KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts RMS	£2.50
AL 20. 5 watts RMS	£2.85
AL 30. 10 watts RMS	£3.20

POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30) 95p
SPM 80. (Use with AL60) £3.25
FRONT PANELS F.P. 12 with Knobs £1.10

PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 & AL30)	£4.35
PA 100. (Use with AL60)	£13.15

TRANSFORMERS

T461 (Use with AL10)	£1.60 P & P 15p
T538 (Use with AL20, AL30)	£1.30 P & P 15p
BMT80 (Use with AL60)	£2.75 P & P 25p

PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with Ceramic cartridges while the auxiliary input will suit most Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—	20Hz - 50KHz (-3dB)
Bass control—	± 12dB at 60Hz
Treble control—	± 14dB at 14KHz
*Input 1. Impedance	1 Meg. ohm
Sensitivity 300mV	
†Input 2. Impedance	30 K ohms
Sensitivity 4mV	

Look for our

SEMICONDUCTOR ADVERTISEMENTS in
Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 20Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ±12dB at 60Hz typically 0.25% at 1 watt. Treble con. ±14dB at 14KHz.


£14.45

TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) size 10 1/2" x 8 1/2" x 3", £3.95, plus 30p postage

SHP80 STEREO HEADPHONES

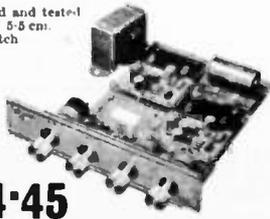4-16 ohms impedance. Frequency response 20 to 20,000Hz Stereo/mono switch and volume controls £4.95



NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3.95

- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 0-1KHz
- Supply voltage 15-50 volts

- Thermal Feedback
- Latest Design Improvements
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.



STABILISED POWER MODULE SPM80

SPM80 is especially designed to power 2 the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address Intercom Units, etc. Handbook available 10p

PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market. The PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz - 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs: 1. Tape Head	3-25 mV into 50K Ω
2. Radio, Tuner	75 mV into 50K Ω
3. Magnetic P.U.	3 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20 KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than -65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £13.15

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £28.75 plus 30p postage

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets etc. Kit price: £9.95 plus 30p postage

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

BI-PRE-PAK Audio Bargains



**STEREO
DECODER
£4.50**


Incl. P. & P.

Ready-built unit, ready for connection to the IF stages of existing FM Radio or Tuner. The very latest 2nd Generation coil less integrated circuit design, operating on this phase locked loop system, offering even better stereo separation. Only owing to our bulk buying capacity are we able to offer this at the old price. LED stereo indicator lights available. **RED at 25p. GREEN at 40p.**


**3 W_{R.M.S.} I.C. AMP
£1.50**

Incl. P. & P.
Order Code I.C.A.1

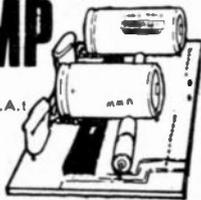on P.C. Board with all components or 2 on one board for £2.66
Order Code I.C.A.1/S
These amps. are supplied with a free booklet on connecting up, specifications and easy to build projects using the I.C.A.1



5W & 10W AMPS

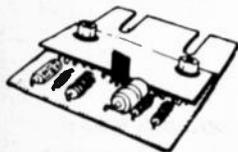

**5W ONLY £1.80
10W ONLY £2.26**

inc. P. & P.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2½" x 1½". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. **Cheapest in the UK. Built and tested.**

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit .15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain crystal or ceramic pick-up cartridges. **£1.10**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. **£1.55**

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.10**

Instruction leaflet supplied with all units. Post and packing included in prices. Add VAT at current rate.

I enclose £..... for..... Decoders/.....

3W Amps/..... 5W Amps/..... 10W Amps/.....

Stereo Pre-Amps 1..... Stereo Pre-Amps 2.....

Stereo Tone Controls.....

(Please insert quantities and delete those not applicable)

Name.....

Address.....

BI-PRE-PAK Dept. D, 222/224 West Road,
Westcliffe-on-Sea, Essex SS0 9DF
Co. Regn. No. 820919 Telephone: Southend (0702) 46344



MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/
volt High Sensitivity Meter
£14.40.

**TAPE
RECORDER
LEVEL
METER**
500µA, 70p



**CARDIOD
DYNAMIC
MICROPHONE**

Model UD-130. Fre-
quency response 50-
15,000c/s. Impedance
Dual 50K and 600 ohms,
£4.55.



4½in x 3½in **METER.** 30µA,
50µA or 100µA, £3.65.

**MULTI-
METER**

Model D62
20,000 ohm/
volt, £7.00.



**3 WATT STEREO
AMPLIFIER**
£4.30

All above prices include 8% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 10. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA



become a RADIO-AMATEUR!

learn how to become a radio-amateur
in contact with the whole world. We give
skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS
SCHOOL** Dept EEB 15 P.O. Box 156, JERSEY

NAME:

ADDRESS:

BLOCK CAPS please

ELECTROVALUE

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

Present

top quality electronic components for price-minded buyers

112 p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

A 100 OF THE BEST

From our transistor stock

2N1307	47p	BC149C	14p
2N2644	51p	BC158B	15p
2N3053	26p	BC159	15p
2N3054	40p	BC167B	13p
2N3055	70p	BC168B	12p
2N3702	11p	BC169B	12p
2N3703	10p	BC198C	13p
2N3704	11p	BC179B	26p
2N3705	10p	BC182L	26p
2N3794	18p	BC184L	26p
2N3819	25p	BC212L	12p
2N4082	11p	BC214L	14p
2N4443	93p	BC257A	14p
2N5082	42p	BC259B	14p
2N5163	20p	BC158	30p
2N5459	32p	BD130	90p
40361	44p	BD131	48p
40362	44p	BD132	52p
40602	46p	BD135	37p
40636	£1-36	BD136	39p
40669	£1-10	BD170	83p
AC128	17p	BF194	15p
AC151R	23p	BF193	23p
AC153	27p	BF179	23p
AC153K	37p	BF129	33p
AC176	24p	BF184	27p
AC176K	36p	BF151	23p
AC187K	31p	BRV39	45p
AC188K	29p	BY164	51p
AD133	£1-92	C106B1	42p
AD136	£1-11	C106D1	62p
AD149	65p	C1406	78p
AD161	42p	MJ481	81p
AD162	40p	MJ491	81p
AF200U	70p	MJ2955	80p
AF239	60p	MJE371	88p
B1906	36p	MJE521	81p
BA138	31p	MJE2955	£1-12
BB103	24p	MJE3055	68p
BB105	34p	OA91	8p
BB109	18p	SD4	8p
BC107A	15p	TIP31A	70p
BC107B	15p	TIP32A	80p
BC108B	14p	TIP41A	80p
BC108C	14p	TIP42A	£1-10
BC109B	18p	W02	30p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	24p
BC147B	13p	ZTX500	14p
BC148B	12p	ZTX504	45p

100s MORE IN CATALOGUE 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90.

The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2-30. Loudspeaker Unit 59RM109, £2-45. Cabinet Kit (to Baxandall design), £10-45. Cross-over choke for additional woofer to above, £1-50.

DISCOUNTS

Available on all items except those shown with NETT PRICES 10% on orders from £5 to £14-99. 15% on orders £15 and over.

FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders - carriage charged at cost. Giro A/C No. 38/871/4002

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
(see note below)					
C	1/3	4-7-470K	1-3	1-1	0-9 nett
C	1/2	4-7-10M	1-3	1-1	0-9 nett
C	3/4	4-7-10M	1-5	1-2	0-97 nett
C	1	4-7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
*WW	1	0-22-3-9Ω	11	10	8
*WW	3	1-10K	9	8	8
*WW	7	1-10K	11	10	8

* Values under 12Ω, add 40%.

Codes: C - carbon film, high stability, low noise. MO - metal oxide. Electroil TR5 ultra low noise. WW - wire wound, Plessey.

Values: All E12 except C, W, C, W and MO, W. E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances: W 5% except WW 10% ± 0-05Ω below 10Ω and W MO 2%. Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order). Prices for 100 up in units of 100 only

POTENTIOMETERS ROTARY, CARBON TRACK.

Double wipers for good contact and long working life
P.20 SINGLE linear 100 ohms to 4-7 megohms, each 14p
P.20 SINGLE log. 4-7 Kohms to 2-2 megohms, each 14p
JP.20 DUAL GANG 1in. 4-7 Kohms to 2-2 megohms, each 48p
JP.20 DUAL GANG log. 4-7 Kohms to 2-2 megohms, each 48p
JP.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only, each 48p
JP.20 DUAL GANG antilog 10K only 48p

2A DP mains switch for any of above 14p extra.

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets, Type PR, horizontal or vertical 8p each.

SLIDER

Linear or log mono 4-7K to 1 meg. in all popular values each 30p

STEREO, matched tracks, lin. or log in all popular values from 4-7K to 1 meg. 60p

Escutcheon plates, mono, black, white or light grey, each 10p

Control knobs, blk/wht/red/yel/gm/ blue/dk. grey/lt. grey, each 7p

ELECTROLYTIC CAPACITORS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
qF								
0-47	—	—	—	—	—	—	—	11p
1-0	—	—	—	—	—	—	—	8p
2-2	—	—	—	—	—	—	—	8p
4-7	—	—	—	—	—	—	—	8p
10	—	—	—	—	—	—	—	8p
22	—	—	—	—	—	—	—	8p
47	—	—	—	—	—	—	—	8p
100	—	—	—	—	—	—	—	8p
220	—	—	—	—	—	—	—	8p
470	—	—	—	—	—	—	—	8p
1,000	—	—	—	—	—	—	—	8p
2,200	—	—	—	—	—	—	—	8p
4,700	—	—	—	—	—	—	—	8p
10,000	—	—	—	—	—	—	—	8p

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point: 9mm characters in 16 lead DIL. Suitable BCD decoder driver 7447 3015G showing + or - & 1 dec. pt. LEDs (Light Emitting Diodes) Photo Cells, each

ANTEX Soldering Irons

CN240 £2-15 Spare bits 32p
CCN240 £2-76 Spare bits 40p

DESOLDER BRAID

6 ft strip 79p

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way
3 pole 4 way; 4 pole 3 way each 29p
TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

in lots of 100 each
4BA Nuts 28p
4BA Screws 28p
1/4" 4B Screws 28p
1/4" 6BA Screws 24p
Threaded pillars 6BA, 1/4" hexagonal
£1-68

Plain spacers 1/4" round £1-12
Other sizes available

ENAMEL COPPER

WIRE in 2 ounce reels

16, 18, 20, 22 SWG 34p
24, 26, 28, 30 SWG 40p
32, 34 46p 36, 38, 40 50p

DIN CONNECTORS

1 way loudspeaker	10p	Socket Plug	12p
3 way audio	10p	12p	12p
5 way audio 180	12p	15p	15p
5 way audio 240	12p	15p	15p
6 way audio	13p	15p	15p

EV CATALOGUE 7

2nd printing - Green and yellow

112 pages, thousands of items; illustrations; diagrams; much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 25p post free including refund voucher for 25p for spending when ordering goods list value £5 or more.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such - standard merchandise is offered for sale. Prices quoted do not include V.A.T. for which 8% must be added to total net value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.

ELECTROVALUE LTD

All postal communications, mail orders etc. to Head Office at Egham address, Dept. EE.1. S.A.E. with enquiries requiring answers.
28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.
NORTHERN BRANCH: 680, Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-1 p.m. 2-5.30 daily: Sat. 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

DISCOUNTS UP TO 60%

FANTASTIC OFFER



GARRARD SP25 MkIV P/Inth & Cover

Garrard SP25 MkIV deck, Goldring G800 Cartridge, Teak finished P/Inth/Cover (Non Hinged) All Leads.
GLOBAL'S PRICE £19.95
 Carr. & Ins. £1.93

TURNABLES

Please add £1.05 for p. & p. & ins.
 Garrard SP25 Mk IV Chassis £12.95
 Garrard 86SB P/C Cart (Mod) £47.50
 Garrard 86SB Chassis £22.40
 Garrard 401 Chassis £33.25
 Garrard Zero 100SB (CH1) £33.75
 Goldring 101 Mk II P/C G800 £23.70
 Goldring GL75 P/C G800 £39.95
 Goldring GL78 P/C G800 £44.40
 Goldring GL85 P/C £66.95
 Pioneer PL 12D .. P.O.A.
 Sansul SR212 .. P.O.A.
 Thorens TD125 MkII .. £73.75
 Thorens TD125AB Mk II .. £111.95
 Thorens TD180 ABC .. £84.85
 Thorens TD185 ABC .. £53.95

Transcriptor Saturn With Vestigial Arm .. £63.95

AMPLIFIERS

Please add £1.05 for p & p & ins.
 Amstrad Integra 4000 Mk II .. £25.75
 Amstrad IC2000 MkII .. £31.95
 Amstrad 8000 MkIII .. £18.50
 Eagle A44 .. £43.10
 Eagle A46 .. £51.25
 Metro-Sound ST20E MkII .. £26.95
 Metro-Sound ST40 .. £34.25
 Metro-Sound ST60 .. £46.75
 Sansul AU101 .. P.O.A.
 Sinclair 2000 .. £29.95
 Sinclair 4000 .. £44.95
 Teleton GA202 .. £30.50
 Teleton SAQ206B .. £23.95
 Teleton SAQ307D .. £27.20

COMBINATION UNITS

Please add £1.10 for p & p & ins.
 Goodmans Compact 80 (Teak) £131.15
 Goodmans Compact 90 .. £169.99
 Goodmans Compact 1-10 (Teak) .. £191.00

TUNERS

Please add £1.05 for p & p & ins.
 Amstrad MLX 3000 .. £28.25
 Eagle A48 .. £47.50
 Eagle TST 152 .. £32.95
 Metro-Sound FMS 20 Mk II .. £33.35
 Teleton T300 .. £53.35

Teleton ST202 .. £36.60
 Sinclair 2000 MkIII .. £29.95
 Sinclair 4000 .. £37.45

TUNER/AMPLIFIERS

Please add £1.21 for p & p & ins.
 Amstrad 5000 .. £56.95
 Goodmans Module 90 .. £92.90
 Goodmans 1-10 Module .. £110.50
 Goodmans 120 .. £113.95

SPEAKERS

Add £1.82 for p & p & ins per Pair
 Amstrad 1500 .. £25.65
 Amstrad 2500 .. £29.95
 Celestion County .. £46.25
 Celestion Dilton 15 .. £67.50
 Celestion Dilton 25 .. £132.50
 Celestion Dilton 44 .. £109.95
 Celestion Dilton 66 .. £39.25
 Celestion Hadleigh .. £265.75
 Goodmans Dimension 8 .. £127.85
 Goodmans Havant SL .. £44.95
 Goodmans Magisters .. £107.75
 Goodmans Magnum K2 SL .. £84.95
 Goodmans Minister .. £36.00
 Goodmans Mezo 3SL .. £87.35
 Marsden Hall XL10F/C N/P .. £31.95
 Marsden Hall XL15F/C N/P .. £36.25
 Marsden Hall XL20F/C N/P .. £44.95
 Marsden Hall XL30F/C N/P .. £87.50
 Wharfedale Denton 2 .. £32.25
 Wharfedale Dove Dale .. £85.75
 Wharfedale Glendale .. £59.75

CARTRIDGES

Please add 12p for p & p & ins.
 Goldring G800H .. £3.87
 Goldring G800E .. £8.20
 Goldring G800 .. £3.40
 Shure V15 Type 3 .. £28.40
 Shure M75EJ Type 2 .. £7.90

Shure M75EJ Type 2 .. £9.10
 Shure 91ED .. £8.20
 Shure MSD .. £3.10
 Sonotone 9 TACHD .. £1.30

FABULOUS OFFER



AMSTRAD IC2000 MkII STEREO SYSTEM

Amstrad IC2000 MkII with increased power 25+25 watts amplifier. Complete with a pair of Amstrad Acoustra 2500 speakers, Garrard SP25 MkIV deck, G800 Cart, P/Inth/Cover (Non Hinged) all leads.

GLOBAL'S PRICE £80.75

Carr. & Ins. £3.30

STEREO HEADPHONES

Please add 42p for p & p ins.
 Koss ESP 6 .. £48.85
 Koss ESP 7 .. £65.75
 Koss K7/11 Red Devil .. £10.99
 Koss K6 .. £11.70
 Koss K6/LC .. £13.25
 Koss KD72E .. £14.90
 Koss 747 .. £19.75
 Koss HV1 1A N/P .. £20.95
 Koss HV1/LC 1A N/P .. £24.80
 Koss PRO 3/LC .. £28.15
 Koss K7/11 Black .. £9.90
 Sennheiser HD414 .. £10.75
 Sennheiser HD424 .. £15.55

GLOBAL AUDIO

Please Note Every effort is made to ensure prices listed are correct at time of going to press, but are subject to alteration without prior notice. (E&OE)

FULL 12 MONTH AFTER SALES SERVICE

We give a **FULL 12 MONTH GUARANTEE** on all products purchased at any branch parts and labour absolutely **FREE**

BIRMINGHAM

Tivoli Shopping Centre,
 1536 Coventry Road, Yardley
 Tel: 021-706 9949

ESSEX

4 High View Parade,
 Redbridge Lane East,
 Woodford Avenue, Ilford,
 Tel: 01-550 1086

LONDON

328 Edgware Road, W2.
 Tel: 01-262 3847
 246, Pentonville Rd, N.1
 Tel: 01-832-5535
 120 Notting Hill Gate, W11
 Tel: 01-229 1437
 50 Stamford Hill, N16.
 Tel: 01-406 4699

PORTSMOUTH

12 London Road, North End
 Tel: 0705 68321

READING

46 Market Place,
 Tel: 0734 595331

WALFORD

105 St Albans Rd, Tel: 39832


H.P. FACILITIES

AVAILABLE FOR
 PERSONAL CALLERS ONLY
MAIL ORDERS
 TO 174 PENTONVILLE
 ROAD, LONDON, N1.
 Order with confidence.
 Send Postal Order,
 Cheque, Money Order,
 Bank Draft, Giro or
 Cash by Reg. Mail

NO HIDDEN PRICES AT GLOBAL AUDIO - ALL OUR PRICES ARE SHOWN WITH VAT INCLUDED

PERSONAL CALLERS VERY WELCOME!
 COMPARE OUR PRICES WITH ANY IN THE BOOK!
 OPEN MONDAY TO SATURDAY 9.30 am - 6 pm
 LATE NIGHT FRIDAY OPEN UNTIL 7pm

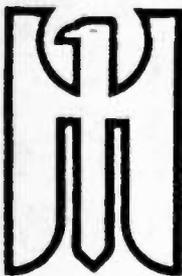PLEASE NOTE All Cheques, Money Orders, Postal Orders, Bank Draft, or Giro to be made payable to MAUTHEAD LTD



Phoenix Electronics
 (Portsmouth) Ltd.
 139-141 Havant Road
 Drayton, Portsmouth, Hants
 PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

COMPONENTS FOR I.C. APPLICATIONS BY

MR. J. B. DANCE

SAJ110	£1.96	SAJ180	£1.96	SAK110/115	£1.23
TAA775G	£1.23	TAA930A	£1.23	TBA790KSD	£1.96
TBA800	£1.96	TBA950	£1.76	TCA250	£1.96

Please send your catalogue—free!

Name

Address

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Electrical Engineering	<input type="checkbox"/>	General Radio and TV Engineering	<input type="checkbox"/>	CITY AND GUILDS Electrical Technicians	<input type="checkbox"/>
Electrical Installations and Wiring	<input type="checkbox"/>	Radio Servicing, Maintenance and Repairs	<input type="checkbox"/>	CITY AND GUILDS Telecommunications	<input type="checkbox"/>
Electrical Draughtsmanship	<input type="checkbox"/>	Transistor Technology	<input type="checkbox"/>	Radio Amateurs' Exam.	<input type="checkbox"/>
Electrical Mathematics	<input type="checkbox"/>	CITY AND GUILDS Installations and Wiring	<input type="checkbox"/>	etc. etc.	
Electronic Engineering	<input type="checkbox"/>				
Computer Programming	<input type="checkbox"/>				

ALDERMASTON COLLEGE
 Dept EEV01 Reading RG7 4PF

NAME (Block Capitals Please)
 ADDRESS

Other subjects Age

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



and make no mistake

TMK 200 MULTIMETER KIT

Build yourself a quality 20000 opv. multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test leads and instructions. Ranges: 0/0.6/30/120/600/1200V D.C. 0/0.6/30/120/600/1200V A.C. Current: 0/0.6/6/60/600mA. Resistance: 0/10/100k/1/10 Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm



OUR PRICE £7.95 P & P 30p

AUDIOTRONIC Model ATM1

Top value 1,000 opv pocket multi-meter. Ranges: -0/10/50/250/1,000 volt AC and DC. DC current 0-1mA/100mA. Resistance: 0/150k ohms. Decibels: -10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £3.25 P & P 15p

AUDIOTRONIC Model ATM5

Jewel movement, attractively moulded case with edgewise ohms adjustment. Ranges: 0-3/15/150/300/1200V AC. (2500 opv). 0.6/30/300/600V DC. (5000 opv). 0-300 uA/0.300mA DC. Resistance: x 10 & x 100. -10 to +16dB. Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm.



OUR PRICE £3.95 P & P 20p

MODEL TH12

20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50uA/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.



OUR PRICE £5.95 P & P 30p

HIKOKI 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/25/100/500/1000V DC. 0/10/50/250/1000V AC. 0-50uA/250mA. 0-20k/2 Megohms.



OUR PRICE £5.97 P & P 30p

MOEEL PL436


20,000 opv DC. 8000 opv AC. Mirror scale. Ranges: 0/3/12/30/120/600V DC. 3/30/120/600V AC. 0/50uA/250mA. 0-20k/2 Megohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £6.97 P & P 30p.

U4323 MULTIMETER

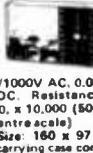20,000 opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: x 10, x 100, x 1,000, x 10,000 (50k, 500k), 5k(1, 50k); centre scale. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.



OUR PRICE £7.70 P & P 30p

HIKOKI 730X

30,000 opv. Overload protection. Ranges: 0/6/30/60/300/600/1200V DC. 12/60/120/600/1200V AC. 30uA/30mA/300mA. 2k/200k Ohm. 20 to +13 dB.



OUR PRICE £7.50 P & P 30p

U4324 MULTIMETER

High sensitivity, overload protected. 20,000 opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/1200V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.



OUR PRICE £9.25 P & P 30p

U435 MULTIMETER

20,000 opv. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2/5/10V DC. 5/25/100mA/0.5/2/5/10V AC. Resistance: 0.2/2/20/200k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.



OUR PRICE £8.75 P & P 30p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 6870 opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/6/15/50/150/60/600mA/1.5/5A DC. 0/1.5/5/15/60/150/600mA/1.5/5A AC. 0/200k/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.



OUR PRICE £10.25 P & P 50p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuse.



OUR PRICE £13.50 P & P 30p

MOEEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA. 12A DC. 0/60k/6 meg/60 megohms.



OUR PRICE £13.95 Carr. paid

HIKOKI 750X VOLT-OHM-MILLIAMMETER

43 ranges, mirror scale. 0-0.3/0.6/1.5/3/12/30/60/150/300/600/1200V DC. 0-3/6/15/30/60/120/200/600/1200V AC. Current: 0-30/60uA/1.5/3/15/30/150/300mA/6/12A. Resistance: 0.3/300-3300ohms. Decibels: -10 to +17dB. Output: -0.3-6/15/30/60/120/300V. Accuracy: 3% DC & 4% AC. Sensitivity: 500/500 opv DC, 5000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm.



OUR PRICE £11.95 P & P 40p

TMK MODEL TW50K


46 ranges, mirror scale. 50k/V DC. 50k/V AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000 AC Volts: 0.15/0.3/1.5/3/7.5/15/30/60/120/250/500/1000 DC current 25/50uA/2.5/5/25/50/250/500mA/5/10A. Resistance: 10k/100k/1 Meg/10 Meg ohms. -20 to +81.5dB.



OUR PRICE £12.50 P & P 20p

HIKOKI MODEL 700X

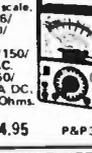100,000 opv. Overload protection. Mirror scale. 0.3/0.6/1.2/1.5/3/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/300mA/6/12A DC. 2k/20k/20k/20M Ohms. -20 to +63dB.



OUR PRICE £14.95 P & P 30p

MODEL HT1008A MULTIMETER

Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 0.3/0.6/1.2/1.5/3/12/30/60/120/300/600/1200V AC. DC resistance 0-20/200k/2/20 Meg ohms. DC current: 0/20/50uA/2.5/25/250/500V AC. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm.



OUR PRICE £17.50 P & P 40p

MOEEL AS.1000 VOM

100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0/6/30/120/300V AC. 0/10uA/60/300mA/12 A m.p. 0/2/20 Meg Ohm. -20 to +17dB.



OUR PRICE £17.50 P & P 30p.

MOEEL C720ZEN

20,000 o.p.v. DC. 10,000 o.p.v. AC. Mirror Scale. 5/25/150/500/1000/2500V DC. 10/50/100/500/1000V AC. DC Resistance x 10, x 1000 (30k centre scale) DC Current 50uA/2.5mA/250mA. -20 to +68 dB.



OUR PRICE £6.50 P & P 30p

KAMOEN HM720B FET VOM

Input impedance 10 Megohms. Ranges: 0/25/125/250/500/1000V DC. 0/2.5/10/50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms.



OUR PRICE £21.00 P & P 40p

KAMOEN 360 MULTIMETER

High sensitivity. DC 100k ohms. AC 10k ohm/V. 5" mirror scale, overload protection. Ranges: 0/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. 0.01mA/0.5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100M ohms. Decibels: -20 to +82dB. Accuracy up to 20000 Ohms. Size: 180 x 140 x 80mm. Supplied complete with test leads etc.



OUR PRICE £17.50 P & P 40p

TMK MODEL 117 FET ELECTRONIC VOLTMETER

Battery operated. 11 Meg input, 35 ranges. Large 4 1/2" mirror scale. Size: 149 x 117 x 60mm. 0.3-1200V AC. 3-3000 RMS AC. 8-800V P.P. DC current 0.12-12mA. Resistance up to 20000 Ohms. Decibels: -20 to +51dB. Supplied complete with leads and instructions.



OUR PRICE £18.50 P & P 20p

TMK 100K LAB TESTER


100,000 opv. 6 1/2" scale. Buzzer short circuit check. Sensitivity 100,000 opv DC/1000V AC. DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC current 10/100uA/10/100/25/10A. Resistance: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: -10 to +68dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.



OUR PRICE £19.95 P & P 30p

370WTR MULTIMETER

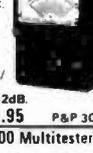Features AC current ranges. 20,000 opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB.



OUR PRICE £19.95 P & P 30p

KAMOEN 72.200 Multitester


High sensitivity tester. 200,000 opv. Overload protection. Mirror scale. Ranges: -0/0.6/3/30/120/600/1200V DC. 0/3/12/60/120/300/600/1200V AC. 0/12A AC. -20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.



OUR PRICE £22.50 P & P 30p

U4317 MULTIMETER

High sensitivity instrument for field and laboratory work. Knife edge pointer, mirror scale. Ranges: 0/0.5/2.5/10/25/50/100/250/500/1000V DC. 0/5/25/100/250/500/1000V AC. Current: 50uA/0.5/1.5/10/50/250mA/1.5/5A DC. 0.25/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +100dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

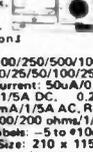

OUR PRICE £16.50 P & P 40p

MODEL C720BFM

30,000 opv DC. 15,000 opv AC. 6.3/15/60/300/600/1200V DC. 6/30/120/600/1200V AC. DC Resistance x 1, x 10, x 100, x 1000 (50k centre scale) DC Current 30uA/30/600mA. -20 to +63dB.



OUR PRICE £8.95 P & P 30p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity: 1000 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750uA/1.5/3/7.5/30/30/75/150/300/750mA/1.5/3/7.5A DC. 0/3/7.5/15/30/150/300/750mA/1.5/3/7.5A AC. 0/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test cards.



OUR PRICE £52.00 P & P 50p

MODEL AF.105 VOM

50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V AC. 0/30uA/6/60/300 mA/12 Amp. 0/10k/1m/100/100 Meg Ohms. -20 to +17dB.



OUR PRICE £12.50 P & P 30p

LB3 TRANSISTOR TESTER

Tests ICB and B. PNP/NPN. Operates from 9V battery. Instructions supplied.



OUR PRICE £3.95 P & P 20p

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indicator. Operates from two 1.5V batteries. Complete with instructions etc.



OUR PRICE £4.50 P & P 20p

KAMOEN TT35 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of PNP, PNP, diodes, transistors. SCR's etc. 4 square scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.



OUR PRICE £17.50 P & P 40p

U4341 Multimeter & Transistor Tester

27 ranges. 16,700 opv. Overload protected. Ranges: 0/3/1.5/3/30/60/150/300/600/1200V DC. 1.5/7.5/30/150/300/750V AC. 0.06/0.6/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.08/0.8/25/200/600k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.



OUR PRICE £10.50 P & P 30p

ST00TR MULTIMETER TRANSISTOR TESTER

100,000 opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/60uA/12/300mA/12 DC. 0/10k/1 Meg/100 Meg. -20 to +50dB. 0.01-0.2 MF. Transistor tester measures Alpha, Beta and ICB. Complete with instructions, batteries and leads.



OUR PRICE £19.95 P & P 25p

ALL PRICES EXCLUDE VAT

Also see following pages

SWR METER Model SWR3
Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedance 52" Inductor 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.
OUR PRICE £4.25 P&P 30p

CIS PULSE OSCILLOSCOPE
For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1-25; 100K-1MHz: 0.1-25; 500kHz. Sensitivity at 100kHz VRMS/mm: 0.3-25. Preset triggered sweep 1-3000usec. Free running 20-200 kHz in nine ranges. Calibrator pips 220 x 360 x 430mm. 115-230V AC.
OUR PRICE £43.00 Carr. paid

RUSSIAN C116 Double Beam OSCILLOSCOPE
5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 8" x 4" CRT. Calibrated triggered sweep from 0.2usec. to 100 milli-sec/cm. Free running time base 50Hz-1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.
OUR PRICE £87.00 Carr. paid

MODEL TE15 GRID DIP METER
Transistorised. Operates as Grid Dip, Oscillator, Absorbent Wave Meter and Oscillating Detector. Frequency range 40kHz-280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.
OUR PRICE £17.50 P&P 30p

TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE
A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm x 1% Inductance: 6 ranges: 1 microhenry-111 henries x 2% Capacity: 6 ranges: 10pf-1110 mfd x 2% Turns Ratio: 6 ranges: 1:1/1000:1-11100 x 1% Bridge Voltage at 1.000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 7 1/2" x 5" x 2"
OUR PRICE £25.00 P&P 30p

TE-200 RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 MHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220/240V a.s. Brand new with instructions. Size 140mm x 215mm x 170mm.
OUR PRICE £17.50 P&P 50p

TE22 SINE SQUARE WAVE AUDIO GENERATOR
Sine 20cps to 200kHz. Square wave 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.
OUR PRICE £24.95 P&P 50p

ARF 300 AF/RF SIGNAL GENERATOR
All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P.P. RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.
OUR PRICE £37.50 P&P 50p

WALKIE TALKIES SKYFON NV7
Super low cost transmitter/receiver. 100Watt with call buzzer and on/off volume control. 7 transistor. Telescopic rod antenna.
OUR PRICE £28.95 per PAIR P.&P 50p
NOT LICENSABLE IN THE U.K.

MODEL MG100 SINE SQUARE WAVE AUDIO GENERATOR
Range 19-220,000Hz Sine Wave
Wav 19-100,000 Hz Square Wave
Output Sine or Square wave 10V. P. to P
Size 180 x 90 x 90mm. Operation 220/240V. A.C.
OUR PRICE £19.95 P&P 50p

POWER RHEOSTATS
High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating.
Single hole fitting. 1/2" diameter shafts. Bulk quantities available.
25 WATT 10/25/50/100/200/500/1000/2500 ohms. **£1.15** P&P 10p
50 WATT 10/50/100/250/500/1500/5000 ohms. **£1.62** P&P 10p
100 WATT 1/5/10/25/50/250/500/2500 ohms. **£2.34** P&P 15p

EMI LOUSPEAKERS
Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 16 ohms.
OUR PRICE £7.50 each P&P 37p
Model 450 13 x 8" with twin tweeter/crossover. 55-13,000Hz. 8 watts RMS. Available 8 or 15 ohms.
OUR PRICE £3.62 each P&P 35p

SPECIAL PURCHASE LIMITED QUANTITY!
Tannoy IZ'DR/8 Bass Speakers
8 ohms. 30 watt Heavy duty, ideal for Hi-Fi. P.A. Group.
OUR PRICE £12.50 P&P 50p.

PS200 Regulated POWER SUPPLY UNIT
Solid state. Variable output. 220/240V AC. Size: 190 x 136 x 98mm.
OUR PRICE £19.95 P&P 50p

AUDIOTRONIC LE-102A INTERCOM
Beautifully made and finished in two-tone ivory/buff, the LE-102A is useful in 20 home, office or shop and is suitable for use as baby alarm. Wall or desk mounting. 67mm speaker/mic gives clear 2-way communication with on/off and volume control on master unit. Operates on 9V batt. Approx. 60ft lead.
OUR PRICE £3.95 P & P 30p

TRITON 4318 PORTABLE 8 TRACK CARTRIDGE PLAYER WITH MW/LW RADIO
Will play 8 track stereo cartridge monaurally. Channel selector switch. Covers medium and long wave bands. Volume and tone controls. Earphone socket. Battery/Maina operation.
OUR PRICE £11.95 P & P 50p

E441 REVERBERATION AMPLIFIER
Self contained, transistorised, battery operated. Simply insert microphone into microphone, guitar etc. and output to your amplifier. Volume control and depth of reverberation control. Beautiful cabinet. 184 x 77 x 108mm.
OUR PRICE £7.50 P&P 30p

SPECIAL PURCHASE! RECORD DECK PACKAGE
By Famous Manufacturer
GARRARD SP25 Mark 111 with G800 cartridge in luxurious plinth with cover.
OUR PRICE £13.95 P & P 75p
GARRARD SP25 Mark 111 Record deck fitted KS 40A cartridge.
OUR PRICE £9.95 P & P 50p

LHO2S STEREO HEADPHONES
Light weight head Phones with padded ear pieces, 4/16 ohms 20-20,000Hz. Complete with cable and stereo jack plug.
OUR PRICE £1.97 P&P 30p

OH2S STEREO HEADPHONES
Wonderful value and excellent performance. Combined adjustable head band. Impedance 8 ohms. 20-20,000Hz. Complete with cable and lead plug.
OUR PRICE £2.25 P&P 30p

TE103S Stereo HEADPHONES
Low cost with excellent response. Foam rubber earcups. Adjustable headband. 8 ohms impedance. Frequency response 25Hz-18kHz. Complete with cable and stereo jack plug.
OUR PRICE £2.50 P&P 30p

SDH8V MONO/STEREO HEADPHONES
Volume control for each channel. 4/16 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.
OUR PRICE £4.97 P&P 30p

BH01 HEADSET and Boom Microphone
Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.
OUR PRICE £5.95 P&P 30p

HANIMEX HRC 3075 CASSETTE RADIO
Covers Medium and FM wave. Hands free lidar volume and tone controls. Battery/Maina operation. Will record direct from radio or through built in condenser microphone. Complete with batteries, earphone, and cassette.
OUR PRICE £24.30 P & P 80p

SPECIAL BARGAIN !! STEREO SOUND SPEAKERS
Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size 368 x 229 x 190mm. 8 ohms. 8 watts RMS. 16 watts peak. Complete with Din lead.
OUR PRICE £12.95 PAIR P&P 50p

FM TUNER CHASSIS
6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 I/F stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.
OUR PRICE £8.95 P&P 20p
Stereo Multiplex Adapter £8.95 extra

SPECIAL OFFER! SAVE OVER 50%
AMSTRAD 8000/2 Stereo amplifier
7 watts per channel rms. Inputs for tuner tape, phone. Headphone socket. List price £29.95.
OUR PRICE £12.95 P & P 60p

SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 40 SOUND FOR UNDER £16
Exclusive offer of GOODWIN 4. CHANNEL CONVERTER and a pair of AD15 10 watt 8 ohm bookshelf speakers enables you to add 4D sound to your existing system. Complete with simple connection details. Normal retail value £25.50.
OUR PRICE £15.80 P & P £1.
GOODWIN CONVERTER available separately £3.95 P & P 50p.

Model A1018 FM TUNER
6 transistor high quality unit - 11 F stages and double tuned discriminator. For use with most amplifiers. Covers 88-108MHz. Powered by 9V battery.
OUR PRICE £13.50 P&P 30p
Stereo multiplex adapter £8.95 extra.

ELECTRONIC CALCULATORS
We carry a tremendous range of both pocket and desk calculators from as little as £8.90. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call us on any branch.

MINIATURE ORGAN MUSIC MASTER AM100
Spanning nearly two octaves, including semi-tones.
This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket.
OUR PRICE £7.95 P&P 50p.

BINATONE DIGITAL CLOCK
Attractive ivory case. For use with 2 AF310... £23.98
GP312 Circuit board... £10.02
GP304 Circuit board... £5.33
HF380 lw/hf aerial amplifier... £2.02
HF395 broadband aerial amp... £2.10
NT10 Stabilised power supply... £6.27
NT300 Stabilised p. supply... £13.16
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2 amps... £5.64
NT305 Voltage converter... £5.64
NT315 Power supply 240V AC to 4x15V DC, 500mA... £12.06

SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER
Complete with printed circuit mounting board.
OUR PRICE £1.50 P & P 15p

SINCLAIR Project 80 Modules
240 Power Amp. £5.95 P & P 15p
250 Power Amp. £7.45 P & P 15p
Stereo 80 Pre-Amp. £13.95 P & P 15p
Active Filter Unit. £7.45 P & P 15p
FM Tuner. £8.95 P & P 15p
Stereo Decoder. £8.95 P & P 15p
PZ5 Power Supply. £5.95 P & P 30p
PZ8 Power Supply. £8.95 P & P 30p
PZ8 Power Supply. £8.45 P & P 30p
Transformer for PZ8. £4.05 P & P 15p
IC 20 Stereo Amp. kit. £7.95 P & P 15p
PZ20 Power Supply kit. £5.45 P & P 30p
SINCLAIR Project 80 Packages
2x240/Stereo 80/PZ5 £28.60
2x240/Stereo 80/PZ8 £31.30
2x240/Stereo 80/PZ8 £33.55 each

TE1021 Stereo Listening Station
For balancing and gain selection of independent channels with additional facility for stereo headcircuit switching. Two gain controls, speakers on-off slide switch, stereo headphone socket.
OUR PRICE £2.25 P&P 15p

AUDIOTRONIC LOW NOISE CASSETTES
TYPE 5 10 25
C80 £1.57 £3.00 £7.08
C90 £2.24 £4.25 £10.24
C120 £2.27 £5.17 £12.24
P&P 3p each. 10 and over Post Free

MP7 MIXER-PREAMPLIFIER
5 Microphone inputs each with independent gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 75mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms; Phono. Mag. 4mV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.
OUR PRICE £8.97 P&P 20p

AUDIOTRONIC AHA101 Stereo Headphone Amplifier
All silicon, transistorised gain amplifier operates from magnetic, ceramic or tubular inputs. Inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.
OUR PRICE £8.50 P&P 30p

HIGH QUALITY CONSTRUCTION KITS
WE ARE APPOINTED STOCKISTS AT Oxford Street, 42 & 267 Tottenham Court Road, 34 Little Street, 152, Fleet Street, 311 Edgeware Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantees.
Post and Packing 15p per kit.

AF20 Mono amplifier... £5.61
AF25 Mixer amplifier... £3.28
AF30 Mono pre-amplifier... £3.20
AF35 Emitter amplifier... £2.42
AF80 0.5W mic. amplifier... £4.86
AF305 Intercom... £7.57
AF310 2 Mono Amplifier... £7.57
M160 Multi-vibrator... £2.18
M1302 Transistor tester... £8.33
M191 VU Meter... £5.37
M192 Stereo balance meter... £5.93
LF380 Quad stereo device... £8.42
AT5 Automatic light control... £3.75
AT30 Photo call switch unit... £6.68
AT50 400V triac light... £5.18
AT52 2 200V triac light... £6.75
dimmer/speed control... £10.82
AT60 3 channel light control... £16.52
AT630 Transistor unit... £8.10
HF61 Diode detector... £3.87
HF65 FM transmitter... £3.21
HF75 FM receiver... £3.66
HF310 FM tuner... £16.32
HF325 Deluxe FM tuner... £26.33
HF330 Decoder (HF310/325) 10.55
GP310 Stereo pre-amplifier... £23.98
for use with 2 AF310... £10.02
GP312 Circuit board... £5.33
GP304 Circuit board... £5.33
HF380 lw/hf aerial amplifier... £2.02
HF395 broadband aerial amp... £2.10
NT10 Stabilised power supply... £6.27
NT300 Stabilised p. supply... £13.16
NT310 Power Supply 240 V AC or 2 x 18 V D.C. at 2 amps... £5.64
NT305 Voltage converter... £5.64
NT315 Power supply 240V AC to 4x15V DC, 500mA... £12.06

Amateur Electronics by Josty-Kit, the professional book for the amateur - covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for AE1 to AE10 listed below.
OUR PRICE £3.30 (No VAT) P&P 25p plus VAT.

AE1 100mW output stage... £1.86
AE2 Pre-amplifier... £1.32
AE3 Diode receiver... £2.08
AE4 Flasher... £1.28
AE5 Astable multi-vibrator... £1.14
AE6 Monostable multi-vibrator... £1.11
AE7 RC generator... £1.08
AE8 Bass filter... £1.08
AE9 Treble filter... £1.08
AE10 CCR filter... £1.05

Also see previous page
ALL PRICES EXCLUDE VAT



PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR 3 LISLE ST., 311 EDGWARE RD., & 152 FLEET ST., BRANCHES or order by post.



USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3.80
100uA	£3.78
200uA	£3.70
500uA	£3.85
50-0-500uA	£3.76
100-0-100uA	£3.70
1mA	£3.68
5mA	£3.88
10mA	£3.98
50mA	£3.68
100mA	£3.68
500mA	£3.68
1A DC	£3.85
5A DC	£3.68
10A DC	£3.85
5V DC	£3.65



*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD330

Size: 110 x 83mm

50uA	£4.30
100uA	£4.28
200uA	£4.20
500uA	£4.18
50-0-500uA	£4.28
100-0-100uA	£4.20
1mA	£4.10
5mA	£4.10
10mA	£4.10
50mA	£4.10
100mA	£4.10
500mA	£4.10
1A DC	£4.10
5A DC	£4.10
10A DC	£4.10
5V DC	£4.10



CLEAR PLASTIC MODEL MR 85P

Size: 85 x 78mm

50uA	£3.98
100uA	£3.85
200uA	£3.80
500uA	£3.78
50-0-500uA	£3.88
100-0-100uA	£3.80
500-0-500uA	£3.70
1mA	£3.70
1-0-1mA	£3.70
5mA	£3.70
10mA	£3.70
50mA	£3.70
100mA	£3.70
500mA	£3.70
1A DC	£3.70
5A DC	£3.70
10A DC	£3.70
15A DC	£3.70
20A DC	£3.70
30A DC	£3.85
50A DC	£4.08
5V DC	£3.70
10V DC	£3.70
15V DC	£3.70
20V DC	£3.70
50V DC	£3.70
150V DC	£3.70



CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4.60
100uA	£4.50
500uA	£4.30
50-0-500uA	£4.50
100-0-100uA	£4.45
1mA	£4.30
1A DC	£4.40
5A DC	£4.30
20V DC	£4.30
50V DC	£4.30
300V DC	£4.30



CLEAR PLASTIC MODEL MR 45P

Size: 90 x 50mm

50uA	£3.20
100uA	£3.15
200uA	£3.10
500uA	£3.00
50-0-500uA	£3.10
100-0-100uA	£3.10
1mA	£2.95
5mA	£2.95
10mA	£2.95
50mA	£2.95
100mA	£2.95
500mA	£2.95
1A DC	£2.95
5A DC	£2.95
10V DC	£2.95
20V DC	£2.95
50V DC	£2.95
300V DC	£2.95
15V DC	£2.95



BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4.50
100uA	£4.45
500uA	£4.20
50-0-500uA	£4.45
100-0-100uA	£4.40
1mA	£4.20
5mA	£4.20
10mA	£4.20
50V DC	£4.20
300V DC	£4.20
50V DC	£4.20
VU Meter	£4.70



EDGWISE MODEL PE70

Size: 90 x 34mm

50uA	£4.15
100uA	£4.10
200uA	£4.05
500uA	£3.90
50-0-500uA	£4.10
100-0-100uA	£4.05
1mA	£3.85
300V AC	£3.95
VU Meter	£4.30



CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3.10
100uA	£3.05
200uA	£3.00
500uA	£2.95
50-0-500uA	£3.05
100-0-100uA	£3.00
500-0-500uA	£2.90
1mA	£2.80
1-0-1mA	£2.80
2mA	£2.80
5mA	£2.80
10mA	£2.80
20mA	£2.80
50mA	£2.80
100mA	£2.80
150mA	£2.80
200mA	£2.80
300mA	£2.80
500mA	£2.80
750mA	£2.80
1A DC	£2.80
2A DC	£2.80
5A DC	£2.80
10A DC	£2.80
3V DC	£2.80
10V DC	£2.80
15V DC	£2.80



CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3.70
100uA	£3.50
500uA	£3.35
50-0-500uA	£3.50
100-0-100uA	£3.45
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
10V DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30
15V AC	£3.40
30V AC	£3.40



MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.



50uA	£8.50
100uA	£7.90
50-0-500uA	£7.90
1mA	£7.60
1-0-1mA	£7.60
1A DC	£7.60
5A DC	£7.60
5V DC	£7.60
10V DC	£7.60
15V DC	£7.60

20V DC	£7.80
50V DC	£7.60
300V DC	£7.60
500mA/5A DC	£8.60
5V/150V DC	£8.60
5V/15V DC	£8.60
1/5A DC	£8.60
1A/15A DC	£8.60

CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5.45
100uA	£5.40
200uA	£5.35
500uA	£5.25
50-0-500uA	£5.40
100-0-100uA	£5.35
500-0-500uA	£5.20
1mA	£5.20
1-0-1mA	£5.20
5mA	£5.20
10mA	£5.20
50mA	£5.20
100mA	£5.20
500mA	£5.20
1A DC	£5.20
5A DC	£5.20
15A DC	£5.20
30A DC	£5.20
10V DC	£5.20
20V DC	£5.20
50V DC	£5.20
150V DC	£5.20



CLEAR PLASTIC MODEL SD460

Size: 58 x 46mm

50uA	£3.80
100uA	£3.45
200uA	£3.40
500uA	£3.35
50-0-500uA	£3.45
100-0-100uA	£3.40
1mA	£3.30
5mA	£3.30
10mA	£3.30
50mA	£3.30
100mA	£3.30
500mA	£3.30
1A DC	£3.30
5A DC	£3.30
10A DC	£3.30
5V DC	£3.30



BAKELITE MODEL MR 85 Size: 80 x 80mm

25uA	£5.25
50uA	£4.00
100uA	£3.95
500uA	£3.85
50-0-500uA	£3.95
100-0-100uA	£3.90
500-0-500uA	£3.80
1mA	£3.60
1-2-1mA	£3.60
5mA	£3.60
10mA	£3.60
50mA	£3.60
100mA	£3.60
500mA	£3.60
1A DC	£3.60
2A DC	£3.60
5A DC	£3.60
10A DC	£3.60
15A DC	£3.60
30A DC	£3.60
50A DC	£3.60
5V DC	£3.60
10V DC	£3.60
15V DC	£3.60
20V DC	£3.60
50V DC	£3.60
150V DC	£3.60



POSTAGE & PACKING 15p

240° Wide Angle

1mA METERS

MW1-5 60 x 80 mm

£8.50 P & P 15p

MW1-8 80 x 80 mm

£8.95 P & P 15p



YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-250V.

MODEL S2808 BENCH MOUNTING

P&P

1A £10.50 50p

2.5A £12.00 50p

5A £17.50 80p

8A £20.35 £1.00

10A £23.75 £1.00

12A £28.40 £1.00

20A £38.00 £1.00

25A £45.00 £1.00

40A £120.00 £1.50

MODEL S2808 PANEL MOUNTING

2.5A £12.00 50p



FOR MAIL ORDER

We offer a speedy and efficient service by mail order. Remember to add 8% VAT to total value of goods including post and packing.

TO LASKYS CUSTOMER SERVICES DIVISION
Audiotronic House, The Hyde, London NW9 6JJ Tel. 01-200 1321

Please send me the following items

TOTAL PURCHASE PRICE (inc P&P and VAT)

I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is

NAME

ADDRESS

Signature

Reg. in England No. 347947 at 12 Lower Grosvenor Place London SW1W 0EX

32 Page HI-FI PRICE LIST

BARCLAYCARD & ACCESS

Phone your order to 01-200 0037 or call into any branch

NO DEPOSIT TERMS available on most goods for personal callers

CHEQUES TO THE VALUE OF £30. ACCEPTED FROM PERSONAL SHOPPERS WITH BANKERS CASH. IN OTHER CASES AND FOR AMOUNTS IN EXCESS OF £30. PLEASE ALLOW TIME FOR CLEARANCE. BANKERS DRAFTS ACCEPTED.

All prices correct at 6/11/74 but subject to change without notice E.&O.E.

A member of the Audiotronic Group of Companies

everyday electronics

PROJECTS...
THEORY.....

BRIGHT INTERVALS—WE HOPE

As many readers will have noticed, yet another prototype "self-supporting house" has been unveiled for our amazement. The idea is good and sensible of course, the only problem is the siting. A roof-ful of solar cells is likely to be very rewarding in Bulawayo, Bomba, or Brasilia. But in Ballachulish, Burnley, or Basingstoke the prospect seems rather less encouraging.

From our own recent dampening experience of deluge following deluge, what we in the UK do urgently need is a system for converting rain into electric power. A rainmill for example. The thought of all those gallons of that most abundant natural resource falling to waste is simply horrific. No doubt technology will catch up with this, one damp day—hopefully before we local inhabitants assume submariner status.

Those continuous downpourings have scarcely required any electronic aid to announce their oncoming. Actually we blush a little when mentioning one of this month's projects—the Rain Alarm. Yet in the course of time, this extremely simple device will come into its own—mark our words. It is really intended for those crafty intermittent showers that have a habit of appearing out of the blue (remember?) when least expected.

So, to you lads in particular among our readers, here's a bit of advice. Don't overlook

this chance to get the right side of mum. For when this rain alarm has had a chance to demonstrate its value as a "laundry protector" your squatter's rights on the kitchen table for constructional purposes should be amicably conceded.

ANOTHER SOLID STATE?

Rain, rain. But what price mere rain when the 21st Ice Age is upon !! EVERYDAY ELECTRONICS could surely claim a world scoop with this month's Ice Warning Device. But it's still a trifle premature to prepare for *that* catastrophe. As a matter of fact it is the motorist we have in mind on this occasion. And what could be more timely as winter begins to get its cold and treacherous grip on things—roads in particular.

Sorry that two of the main attractions in this issue bring attention to some of the least agreeable aspects of the weather. Perhaps, to be more reasonable we should have included a snow detector. But at any rate we have covered the two extremes, the liquid and the solid state of H₂O.

Best wishes to all our readers this Christmas-tide, and may the outlook be set fair.



Our February issue will be published on Friday, January 17

EDITOR F. E. Bennett • ASSISTANT EDITOR M. Kenward • B. W. Terrell B.Sc.

ART EDITOR J. D. Pountney • P. A. Loates • K. A. Woodruff

ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1975. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Everyday Electronics Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.

EASY TO CONSTRUCT SIMPLY EXPLAINED



VOL. 4 NO. 1

JANUARY 1975

CONSTRUCTIONAL PROJECTS

ICE WARNING FOR CARS Warns of the danger of ice on the road by Malcolm Plant	12
ULTRASONIC REMOTE CONTROL Part 2 Transmitter by J. B. Dance	26
RAIN ALARM A simple device to protect the washing by L. Hardman	30
TWO - BAND SUPERHET TUNER A l.w. and m.w. tuner by F. G. Rayer	34

GENERAL FEATURES

EDITORIAL	10
PLEASE TAKE NOTE	15
SHOP TALK Component buying for constructional projects by Mike Kenward	16
JACK PLUG AND FAMILY Cartoon	16
HOW RADAR WORKS by G. A. G. Brooke	17
COUNTER INTELLIGENCE A retailer comments by Paul Young	21
PHYSICS IS FUN Batteries by Derrick Daines	22
BEGIN HERE—2 Semiconductors by Donald Maynard	23
RUMINATIONS by Sensor	25
BOOK REVIEWS	32
READERS' LETTERS Your news and views	39
PROFESSOR ERNEST EVERSURE The Extraordinary Experiments of. by Anthony J. Bassett	41
BRIGHT IDEAS Readers' constructional hints	43
HELP! Common queries answered	44
FOR YOUR ENTERTAINMENT Calculators by Adrian Hope	47
DOWN TO EARTH Biasing by George Hylton	48

Publisher's Annual Subscription Rate, including postage Inland £2.95, Overseas £3.00. International Giro facilities Account No. 5122007. State reason for payment "message to payee". Address to Everyday Electronics, Subscription Department, Carlton House, Great Queen Street, London, WC2E 9PR. Binders for volumes 1 to 3 (state which) and indexes for volume 1 and 2 available for £1.25 and 30p respectively, including postage, from Binding Department, at the above address.

We are unable to supply back copies of Everyday Electronics or reprints of articles and cannot undertake to answer readers' letters requesting designs, modifications or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, both at the address shown opposite.



CIRCUITS which respond to changes in air or liquid temperature are easy to build because of the ready availability of thermistors.

This project describes how to use a thermistor as a transducer in a circuit which repeatedly flashes a lamp when the temperature of the thermistor has fallen to a preset temperature—in this case 0 degrees C. Thus the circuit can be used to provide a warning that the temperature in a greenhouse, for example, has reached frost point. Or, as described for this project, the circuit could be used to warn the driver of a car that icy roads are likely.

Apart from two bipolar transistors, an *n*pn and a *p*np type, the circuit also uses three other types of semiconductor devices. Firstly, the *thermistor*, consisting of a bead of semiconducting material, is a glass-encapsulated negative-temperature-coefficient (n.t.c.) type. Its small size enables it to respond rapidly to temperature changes and the glass encapsulation protects the bead from the electrical effects of conducting liquids which might come into contact with it. Note that an n.t.c. thermistor has an electrical resistance which increases with temperature fall.

Secondly, an integrated circuit operational amplifier (op amp)—the general purpose 741 type—is used as a sensitive detector of voltage change across a Wheatstone bridge, one arm of which contains the thermistor.

Thirdly, a light-emitting diode (l.e.d.) is the solid state lamp which flashes the warning signal. This lamp is small, robust and requires very little current to light compared with a tungsten filament lamp.

THE CIRCUIT

The complete circuit of the "frost" alarm is shown in Fig. 1. The design shown is powered by

a 12V car battery, although should the circuit be used for other applications a 9V battery would suffice to operate the circuit.

The circuit may be considered to consist of two parts divided by the dotted line. To the left of this line is the temperature-sensitive Wheatstone bridge, the output from which is sensed by the op amp acting as a differential amplifier. To the right of the dotted line is the two-transistor oscillator which flashes the l.e.d. when the thermistor reaches a predetermined temperature.


The Wheatstone bridge consists of resistors R1 and R2 which set the voltage at the inverting terminal of the op amp at about 8V with respect to the negative line (for a 12V supply). The preset resistor VR1 and the thermistor RTH1 form the other arms of the bridge.

Since the thermistor is an n.t.c. type, as its temperature falls its resistance increases, and the voltage at pin 3 rises. As this voltage just exceeds that at pin 2, the voltage at the output of the op amp goes from near zero to a few volts positive. The temperature at which the output goes sharply positive can be selected by adjustment of the preset resistor VR1.

The sudden rise of voltage at the output of the

FOR
GUIDANCE
ONLY

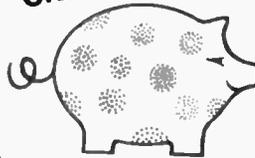ESTIMATED COST*
OF COMPONENTS
including V.A.T.



£2.20

excluding case

*Based on prices prevailing at
time of going to press

ICE WARNING



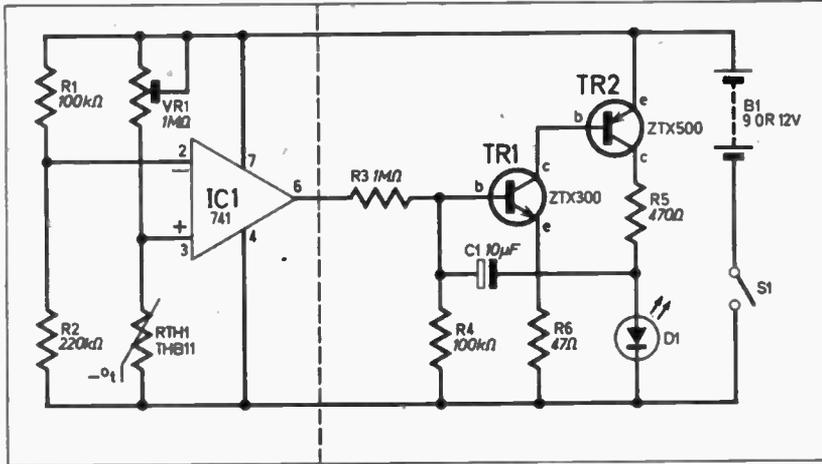


Fig. 1. The circuit diagram of the Ice Warning device.

op amp switches on the oscillator to the right of the dotted line, resistor R3 coupling this voltage change to the base of transistor TR1. The capacitor C1 provides the positive feedback which is necessary to maintain the low-frequency oscillations.

The *pnp* transistor TR2 has the l.e.d. in its collector circuit as well as a suitable series resistor R5 which restricts the current passing through the l.e.d. to below its maximum rated value. The frequency of the flashes of the l.e.d. are determined partly by its own resistance but can be adjusted to the required rate by selecting a suitable value for C1.

Transistors TR1 and TR2 should be a complementary pair if the circuit is to work satisfactorily. The pairs 2N2926/2N3702 and BC182L/

BC212L are suggested alternatives to the types in the circuit.

CIRCUIT ASSEMBLY

All of the components, excepting battery, switch and l.e.d., can be mounted on 0.1 inch matrix Veroboard as shown in Fig. 2 although the actual layout may depend upon the physical size of the components which are obtained by the constructor.

The thermistor must be sited in a position where it cannot receive heat from the engine. It must be close to the ground since the conditions for ground frost, giving icy patches on roads, cannot be predicted a few feet above the ground.


The thermistor must be protected from con-

.....FOR CARS


Be alerted when the roads start to ice by installing this simple unit in your car.

By Malcolm PLANT M.Sc.

ICE WARNING FOR CARS

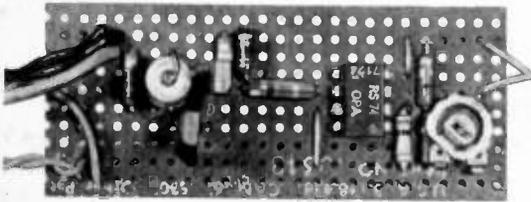

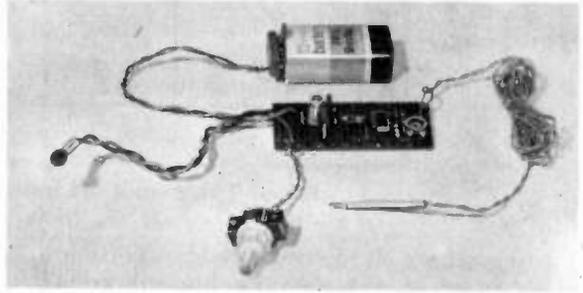Photograph of the completed prototype component board.



The prototype unit wired up and ready for installation.

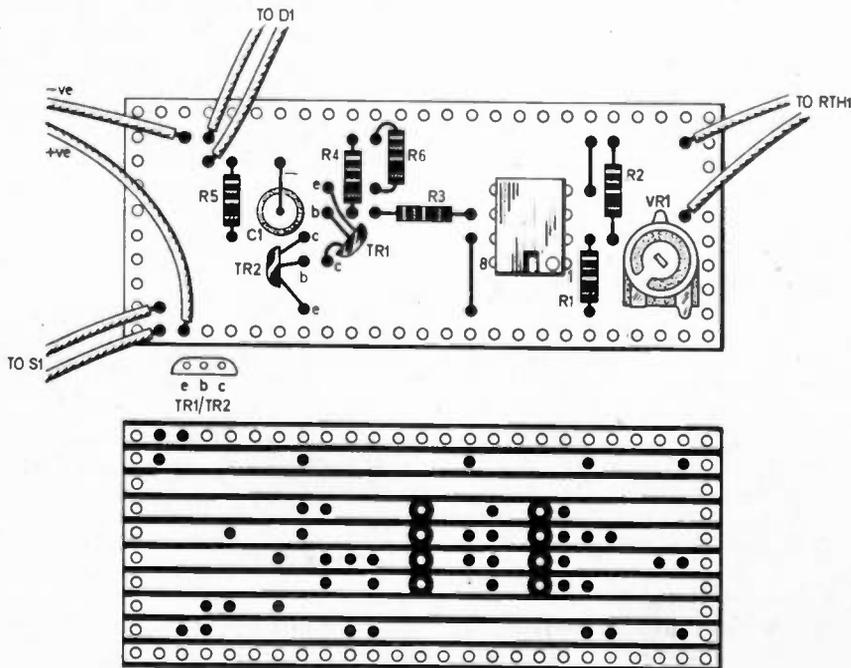


Fig. 2. The layout of the components on the Veroboard and the breaks to be made along the copper strips on the underside.

Components

Resistors

R1	100k Ω
R2	220k Ω
R3	1M Ω
R4	100k Ω
R5	470 Ω
R6	47 Ω
All $\frac{1}{4}$ W \pm 10% carbon	

SEE
**SHOP
TALK**

Capacitor

C1	10 μ F elect. 15V
----	-----------------------

Semiconductors

IC1	μ A 741C or similar 741 type with holder
TR1	ZTX 300, 2N2926 or BC182L silicon <i>n</i> p <i>n</i>
TR2	ZTX500, 2N3702 or BC212L silicon <i>p</i> n <i>p</i>
D1	red light emitting diode, any type
RTH1	THB11 thermistor

Miscellaneous

B1	9V battery or 12V car supply
S1	s.p.s.t. switch or car ignition switch
Veroboard 25 holes x 10 strips, 0.1 inch matrix, connecting wire, suitable small plastic case approx 75 x 30 x 30mm.	

tact with water splashes and rain, for the cooling produced by water evaporating from the thermistor will cause it to fall to a temperature below the true air temperature. A good position for the thermistor is behind the front bumper although the best position will be determined by the type of car.

Having decided the position for the thermistor, you will need to estimate the length of flex required between the thermistor and the circuit. Care should be exercised in soldering the flex to the thermistor since the soldered joints should be insulated with sleeving to prevent them coming into contact with water; heat-shrinkable sleeving is ideal for this purpose. The thermistor should be glued into the end of a short length of plastic tubing so that although air can circulate round it, it is protected from water splashes.

Any small plastic box can be used to house the circuit and to locate it unobtrusively behind the dashboard of the car. Three pairs of leads should leave the box through a grommet: two leads to the battery, two to the thermistor, and two to the light-emitting diode. Choose a position on the dash where it is easy to see the flashing of the l.e.d. Drill a hole to take the l.e.d. so that it can be fixed by pushing it through a plastic grommet.

The l.e.d. must be connected correctly to the circuit so that it is forward-biased by TR2 switching on. It is easy to find the anode of an l.e.d. by means of a multimeter switched to its ohms range. Indeed, when the diode is forward biased (giving a low resistance reading), the l.e.d. will often light, being energised by the internal battery of the multimeter. Before finally fixing the

circuit to the car, it must be set to respond to an air temperature of 0 degrees C in the following way.

CALIBRATION

Crush some ice in a container until it is a "slush". Ensure that the ice is melting, for then it is at 0 degrees C (the ice point) but check the temperature with a thermometer if you have one available. Immerse the thermistor in the melting ice and adjust the preset resistor until the l.e.d. just begins flashing. Take the thermistor out of the iced water and as it warms up the l.e.d. will cease to flash.

Of course, you may decide to choose an alternative temperature for the l.e.d. to start flashing. The circuit is relatively immune to changing supply voltages which might cause the l.e.d. to flash at temperatures other than that set. Incidentally, resistor R5 has been included in the circuit to prevent the l.e.d. from occasionally flashing when the thermistor is above the set level. This resistor provides a slow discharge path for the capacitor.

MODIFICATION

Should it be required to convert the circuit to one which provides an audible warning rather than a visible alarm, the following alteration may be made. Change C1 to about 0.1 μ F (select its value for the desired frequency), and replace R5 and the l.e.d. by an 80 ohm miniature speaker, C1 now being connected directly to the collector of TR2. For an audio-visual indication, make this modification but also replace R4 by the l.e.d.

In use it is interesting to note, as one drives along during a frosty evening, the indication given by the device. The likely conditions for ice to form on the road is clearly indicated—under trees or other sheltered places, in hollows where cold air collects and even a change from cloudy to clear sky. □

PLEASE TAKE NOTE

Windscreen Wiper Controller (Nov. 74). In Fig.3, diode D1 is drawn the wrong way round. The circuit diagram and Fig.2 show the correct polarity.

M. W. Reflex Receiver (Dec. 74). Under the heading **Adjustments**, in the last sentence of the second paragraph "increase" should be changed to "decrease".

We would like to apologise for an error on the **Data Check Card** given free with the December issue of E.E. The formula for the net value of two capacitors wired in series should read

$$C_{\text{total}} = \frac{C1 \times C2}{C1 + C2}$$

New products and component buying for constructional projects

SHOP TALK

By Mike Kenward

By the time this issue hits the bookstalls it will be nearly Christmas—it seems very far away at the time of writing (early November) and one wonders how it will be upon us so quickly. No doubt many readers will be getting soldering irons or small multi-meters for Christmas and excellent presents they make too.

One of the smaller meters costing about £10 should last a lifetime if carefully looked after and will soon prove itself invaluable to any constructor. The available range is vast and it would be necessary to choose the one you want instead of leaving the choice to some well meaning, but electronically unaware, relative. The things to go for are high sensitivity (ohms/volt), about 20,000Ω/V is required, and a good number of ranges with reasonable accuracy.

Ice Warning Device

Few if any components for the *Ice Warning For Cars* should cause problems. The author has provided alternative transistor types should the Ferranti ZTX ones not be available in your area. The thermistor could prove difficult but the larger suppliers should have it and if not they may be able to offer a device with similar characteristics.

To enhance the finished unit an l.e.d. with chrome mounting case can be purchased although this will add to the cost. The prototype unit was housed in a plastic photographic slide box providing excellent protection within the car. The case can be packed with foam rubber inside to protect the board from shocks, and the lid held on with Sellotape.

2 Band Superhet Tuner

A fairly complex project and not one recommended for the new constructor, the *2 Band Superhet Tuner* is the first superhet design that we have published. Readers will notice that it is fairly expensive when compared with a complete Japanese superhet receiver and these days it is simply not possible to make a superhet receiver more cheaply than a similar one can be purchased for.

However this does not detract from the knowledge gained and the satisfaction of producing ones own unit and this design will make an excellent "add on" for the hi fi enthusiast who wants to listen to an a.m. station occasionally and only has an f.m. receiver.

One or two of the components

are rather special, in particular all the Denco parts. These are available from some retailers or direct from Denco at 357/9, Old Road, Clacton-on-Sea, Essex. The combined cost of all their parts plus post, packing and V.A.T. is £3.40. The parts must be specified individually as shown in the components list. Add 20p if the trimming tool is required.

Another component which may cause some difficulty is the Jackson 00 capacitor (208/176pF with trimmers) that forms C1, C2, C6 and C7. This should be available from the larger retailers—again giving the full specifications when ordering.

Rain Alarm


Certainly the most simple *Rain Alarm* we have ever published and probably one of the most simple designs possible. The few parts for this device should not cause any problems. Doram are the suppliers of the audible warning device (12V version), they do advertise in our pages. The cost of this item including post, packing and V.A.T. is £1.70.

Ultrasonic Remote Control

The parts for the ultrasonic transmitter are all readily available except possibly the transducer which comes from Hall Electronics. The cost of this item including post, packing and V.A.T. is £3.75. Hall are at 38 Avondale Rd., Leyton E17.

If you have any difficulty in getting the diecast case shown, write to Doram who can supply it for £1.23 inclusive (type 994).

JACK PLUG & FAMILY...

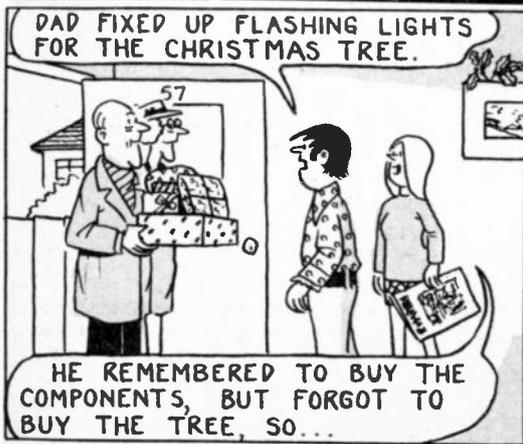

HOW RADAR WORKS

By G. A. G. BROOKE

RADAR in some form—for ships, airports, speed traps, weapons—is now so commonplace that manufacturers and others in the business are inclined to take for granted that everyone else knows exactly how it works. The reverse is often the case and this article sets out to explain the salient points, mainly with reference to marine equipment.

DEVELOPMENT

Although it took the pressures of impending hostilities to produce a practical design some years before World War II, Hertz had proved that radio waves can be reflected by metallic bodies as much as 50 years before. Marconi alluded to the possibilities of obtaining reflections from targets in 1922 and, although much money and effort had to be expended, it is hard to see why radar took so long in gestation at a period when advances were being made in many other technical directions.

Modern radar really has its roots in the works of scientists in the mid-twenties and early thirties, mainly in England and the U.S.A. who were concerned with the heights above the earth of the electrically conductive layers of the atmosphere which reflect radio waves. Sir Edward Appleton, M. A. F. Barrett and R. A. (later Sir Robert) Watson Watt were prominent in this country.

Sir Robert, who died only recently, became of course the great pioneer and it was under him that the development of radar was concentrated prior to and during the last war. Randall and Boot are two names almost as significant, as it was they who produced the cavity magnetron at Birmingham University in 1940. It elevated radar from v.h.f. to microwave frequencies, and made possible a much smaller and highly directional aerial that provided greater power by concentrating it in a narrow beam.

The magnetron is still with us, though it and the cathode ray tube are the only valves to be found in modern solid-state equipment.

BASIC PRINCIPLE

The basic principle of radar is simplicity itself: if radio energy at high frequency (usually between 1GHz and 40GHz) is emitted with high power, it will be reflected off hard objects in much the same way as audible sound. Since the speed of both the emitted and reflected energy is known, it is only necessary to construct an electronic timing device for the range of the object returning an echo to be measurable.

This sounds easy, but accounts for one of the intricate parts of a standard marine radar (the whole costing from £600 for the simplest yacht model to £10,000 for the largest standard big ship set). The position of the echo in azimuth (its bearing) is much more easily determined, of which more later.

In practice a radar consists of a transmitter to generate pulses of radio-frequency energy; a rotating aerial for sending these out into space as a narrow beam of radio waves; a receiver for accepting the echoes returned (via the aerial) from any suitable target; and a display for presenting them visually so that range and bearing are evident. (There also has to be a power supply for converting the electricity available into the special form required by the radar.)

TRANSMITTER

Ranging by radar is very analogous to making use of echoes of the human voice. If one shouts in order to time the echo, the best results are obtained if "transmission" consists of short, sharp sounds. The shortness ensures that the transmission will have ceased before the echoes return and the sudden rise to full power will make the instant of return immediately perceptible.

Similarly, the radar transmission which must operate for ranges varying from 25 yards to, say, 48 miles, has to produce a short pulse of oscillation rising rapidly to full amplitude, which it maintains until cut off. The duration of the pulse is called the pulse length and its frequency, the pulse repetition frequency (p.r.f.).

If, for instance, the target is only 50 yards from the transmitter, the pulse will have to be cut off before the beginning of the wave has had time to travel to the target and back; a total distance of 100 yards. A radio wave travels 328 yards in one microsecond so that the pulse, in this case, must not be longer than 0.3 microseconds.

If it is also desired to receive echoes from targets up to, say, a 30 mile range, the interval between pulses must be long enough to enable the wave to travel twice this distance, i.e. 370.4 microseconds. This gives a maximum p.r.f. of 2700 pulses per second. (The pulse has to be further shortened in order to separate echoes of the same bearing and of very small difference in range. With too long a pulse, the echoes would be merged.) In practice a choice of two or three p.r.f.s may be provided for use at different ranges.

OPERATION

It will be noticed that in the case mentioned the transmitter is required to oscillate for 0.3 microseconds and then to rest for 370.1 microseconds. Because of this, a small valve (the magnetron) may be used to generate very high power since it has relatively long intervals in which to cool. In practice the p.r.f. is usually between 500 and 4,000 pulses per second. In these circumstances a magnetron no bigger than 250 watt lamp can give a peak power of 60kW.

The "firing" of the magnetron (an apt description) is the last action from a chain of four basic circuits in the transmitter. Traditionally—in the latest solid-state equipment there is some varia-

tion—these and their functions are:

1. The sync. trigger, which synchronises the display with the transmitter;
2. The sub-modulator, which is a timing device determining pulse width;
3. The modulator, which stores energy and then releases it to the magnetron on command from the sub-modulator;
4. The magnetron itself which converts electrical energy into electromagnetic waves.

These circuits are so designed that, after the sudden initial rise, the discharge is as near as possible at a constant rate and is completed in the time of the desired pulse length; that is to say, it takes the form of a short square pulse. The magnetron bursts into oscillation when the energy is released and ceases to oscillate when the supply is cut off.

Though it has but two electrodes, the action of the magnetron is complex. Suffice it to say that it is known as a cavity resonator and operates between the poles of a very strong magnet.


As described earlier, the key to range measurement by radar is the time interval between transmitted pulse and returning echo. To measure this, the sync. trigger sets off the timing arrangements in the display at the same time that the magnetron is fired and the radio frequency (r.f.) pulse begins. We will return later to the display.

The r.f. pulse, so produced, passes from the transmitter to the aerial via a waveguide, simply a tube (usually of copper) of rectangular section and engineered to high limits. Its internal dimensions are critically dependent on the frequency used and must be uniform.

THE AERIAL

There have been several types of aerial over the years but in marine practice the most usual

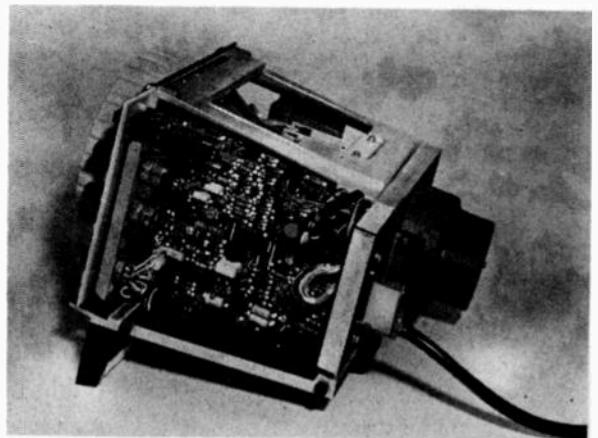One side of a Decca small boat radar display showing virtually all the display electronics mounted on one board.





A sophisticated anti-collision display that indicates risk of collision with any echoes investigated. The separate anti-collision component is being lifted out.

these days is the slotted waveguide design. This virtually consists of a length of waveguide mounted horizontally on a turntable so that it can be revolved. The front face has a series of slots cut in it, again engineered to very high limits in both pitch, angle and depth.

The aerial has an electric motor which drives it at about 30 r.p.m., the whole assembly being known as the scanner. The beam radiated is narrow in the horizontal plane—usually less than three degrees—an important factor in bearing discrimination, the ability to separate adjacent echoes. In marine radar the vertical beamwidth is about 27 degrees, to allow for the roll of the ship.

It is in fact difficult to concentrate all the energy into a single narrow beam; some of it is radiated at various angles on either side. These fractions are known as side-lobes and, though weak, can produce unwanted echoes on the display in certain close range conditions.

The advantages of the slotted waveguide design (others being the tilted parabolic cylinder and the cheese) are in the realms of weight, wind resistance and side-lobe performance. Construction is, however, expensive and the other types are sometimes found in the cheaper small boat equipment. Double aeriels exist where one is used for transmission and the other for recep-

tion. Usually, however, the reflected energy is made to return through the same aerial and is passed down the waveguide to the receiver.

THE RECEIVER

The transmitted pulse is extremely powerful—anything up to 60kW in marine radar—and the returning pulse naturally very small (much of it having been scattered in unsuitable directions); so the sensitive receiver must be protected from the transmitted pulse. The usual protective method is to use a transmit receive cell which blocks the transmitter pulse from the receiver input.

The receiver's function is to amplify the minute returning echo pulses while retaining their distinctive shape so that they will be capable of employment in the display. Since it is expensive to amplify the returning pulses at their own radio frequency (e.g. 9MHz), the first duty of the receiver is to change the frequency to a more suitable one. This change is effected in the mixer, the main components of which are the local oscillator and the mixer crystals.

The principle is the same as in superhetrodyne radio receiver, i.e. mixing of the received signal with one of different frequency produces another of intermediate (difference) frequency; this, after suitable amplification, is detected to produce video pulses suitable for acceptance by the video amplifier of the display. (A major problem is in keeping down the level of noise generated by the receiver mixer and input circuits. Noise appears as a speckled background on the radar display and must be kept to a minimum if weak legitimate echoes are to be seen.)

THE DISPLAY

The display is the name given to the entire unit, including screen, electronics, controls and in some modern sets an integral power supply. The proper description for the screen itself is the plan position indicator (p.p.i.). This is a cathode ray tube (c.r.t.) which, as the name implies, presents the same picture of the area around the transmitting aerial as would be seen by a helicopter flying so as to remain always immediately over "own ship". The object of the display designer is thus to provide echoes on the p.p.i. which are as near as possible in the correct positions relative to the centre spot, which represents own ship.

Taking range first, consider the situation with the scanner stopped. It is sending out pulses and receiving echoes from another ship. Now the magnetron's trigger also starts a spot on the p.p.i. moving out from own ship to the circumference, at a predetermined speed. (This spot is actually moving at such a rate that it appears as a solid line, known as the timebase or "trace", in practice dimmed to a barely visible level.)

When the receiver picks up the returning echo,

it causes the spot to increase in brightness. Because the spot is travelling at a predetermined speed, its distance from the centre when brightened can be measured in time. This time is the same as that taken for the radar pulse to go out and its echo to be received. We know the speed of the pulse and so we can assess the distance away of the ship returning the echoes.

In fact, to paint the echo on the p.p.i., the momentary increase of spot brightness calls for variation of one of the voltages applied to the c.r.t. For the echo pulse to provide this variation, it must (after being processed in the receiver as described) receive a final amplification by the video amplifier. The video amplifier is also responsible for the painting of measuring marks on the p.p.i.


Still considering range only, a choice of scales is provided so that at the turn of a control, the radius of the p.p.i. can be altered to represent, say, 24, 12, 6, 3, 1½, or ½ mile. (As implied earlier, it is often necessary to vary pulse repetition frequency with range and this is affected automatically by the same control.) If the display is on the six mile scale and a ship three miles off, the echo will of course appear exactly half way to the circumference.

To facilitate judgment, range rings are provided at set intervals. If an echo exactly cuts a ring, its range is clear but, if not, interpolation is necessary by eye or with a ruler (except with the more sophisticated sets; these have a variable range marker which provides the answer in digits on completion of a simple measuring action).

BEARING

What of bearing? The receiver will only register an echo when the aerial is pointing at a target. Therefore, if we rotate the trace in the display exactly in synchronisation with the aerial, the spot going out along the trace will be

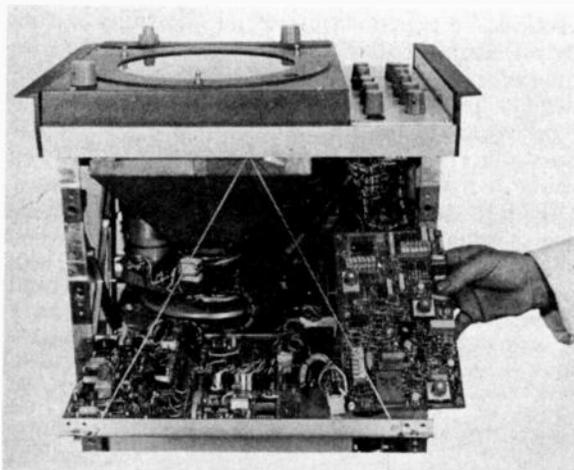Main components of a Decca medium sized radar display (the power supply is out of picture below).



momentarily brightened at the exact moment the aerial is pointed at a target; and therefore the echo will show up on exactly the right bearing.

In practice the face of the c.r.t. is coated with phosphor which ensures that the echo continues to glow after the trace has passed and it can be arranged that all targets within range glow all the time, renewed in brightness at each revolution of the trace. A bearing cursor is provided (a sheet of glass or Perspex over the face of the p.p.i.) which is revolved until a line thereon—the bearing marker—cuts the echo in question. The bearing can then be read off either side.

The bearing will of course be purely relative to the ship's head. (As with the variable range marker, in some cases the bearing may appear digitised in a "window" as the bearing marker is aligned.)

ACTUAL UNITS

In practice, the transmitter and receiver are combined in one unit, often called the transceiver. Thus with the scanner, the display and the power unit, there are four components to the standard radar system. In some small craft sets, the transceiver is located integrally with the scanner, not only simplifying installation by reducing the number of separate units to three, but improving performance by obviating the loss-making waveguides that would otherwise join the two.

Very small boat radars usually have the aerial enclosed in a radome to save cost and electrical power by permitting the use of a smaller turning motor (due to reduced wind resistance and a lighter aerial). A radome simplifies weather-proofing and usually has room for the power unit so that in these instances the number of separate components is further reduced to two.

TRUE MOTION

Since we have been considering marine radar in particular, it is worth mentioning an alternative form of presentation—true motion. This was introduced by Decca in 1956. Simple displays, as described above, are relative motion where the p.p.i. shows you what a helicopter would see flying so as to remain permanently over own ship. In true motion our helicopter is hovering perpetually *in space*, and everything below that is on the move—including own ship this time—passes beneath it.

The effect is produced by actually moving the centre spot about the p.p.i.—via inputs from compass and log—with the same course and speed as own ship's. The advantages are considerable: instead of all courses, etc. being only relative and needing a further (plotting) operation to be changed to true courses, etc., these can now be read direct off the p.p.i.

Put another way, everything happens as in real life; when going up a river in relative motion everything (be it a hovercraft doing 60 knots) appears stationary and the river banks slide past,

but in true motion the river banks stay put and own ship moves up between them. Of course own ship eventually comes to the edge of the p.p.i. whence it is quickly reset. True motion does involve greater complexity and is seldom found in small craft.

ALTERNATIVES

Another alternative frequently encountered is that of wavelength. The standard marine wavelength is 3cm but, in large vessels carrying two radars, the second is often of 10cm because of superior performance in rain, other forms of precipitation and "sea clutter".

"Rain clutter" and "sea clutter" are perpetual bugbears needing special circuits to nullify them as far as possible. Sea clutter produces a cotton-wool effect on the p.p.i. in the vicinity of own ship, caused by the echoes from wave-tops in choppy weather; rain clutter is similar, though at any position, and caused by the myriad reflections from rain drops.

The pulses of 10cm wavelength have a considerable though by no means total ability to ignore such unwanted targets. A disadvantage of the 10cm wavelength is the larger size of the equipment necessary, particularly the aerial which is 3.5m long. This makes it difficult to fit on smaller craft, some of which (such as fishing

vessels that frequent northern waters) could benefit greatly thereby.

Where radars for special purposes are concerned, there are several variations in the general description above. For instance, in the case of the airfield surface movement indication, radar which needs very high definition and discrimination over a short range, the wavelength is only 8mm and the aerial rotation rate 750 r.p.m. But the basic principles still apply.

As far as future developments are concerned, it is likely that the magnetron valve will be replaced by solid-state devices as improved low-noise receiver innovations continue to reduce the transmitter power required (e.g. one new 48 mile radar requires only 3kW, where its predecessor needed 10kW. Another set with a range of 12 miles requires only 1½kW and has an input of only 75 watts).

Aerials of the phased array type, which do not rotate, are already in use for military purposes but are still many years away from commercial application. The solid-state display is in a very similar category.

Miniaturisation will continue with attendant advantages but it is presumed that separate aerials and displays will always be required. Marine radar at any rate is about static in value, inevitable increases in manufacturing costs being offset by very real advances in performance. □



...Counter Intelligence

BY PAUL YOUNG

A retailer discusses component supply matters.

JUST after the Second World War, my brother and I had a small radio business. Life was hard for many reasons. New radio receivers were non-existent and all we had to offer for sale were re-conditioned second-hand ones. Consequently we would tackle anything! We would rewire your house, or convert your favourite vase into a table lamp. One day, just before Christmas, a tall highly perfumed Indian gentleman in a rainbow coloured turban walked into our shop and asked us to make him a talking kettle!!!

Well we had the rent to pay and children to feed and presents to buy, so we agreed. We did however, admit our ignorance as to the form this particular kitchen utensil took. He then produced an American catalogue of conjuror's equipment, and sure enough on one of the pages was listed a talking kettle. It appeared that this gentleman, "Ashraf" I think he was called, had a small

stand at a nearby department store, from which he sold scent. To pep up sales, he decided that every customer who purchased a bottle, would get a free glimpse into the future. Having smelt the concoction we reckoned a free gas mask would have been more appropriate!!

To intrigue his customers still further, Ashraf would ask them what they wanted to know, and then tell them to pick up the kettle and put the spout in their ear. To their utter astonishment they would hear the answer! We had to produce the kettle and necessary electronics! The electronics were fairly straightforward. We had a small speaker in the lid of the kettle, fed from a coil of heavy gauge wire in the base. Another coil of wire was concealed under a table top and this was fed from the output of a 20 watt amplifier.


One snag was, that the screening effect of the bottom of the kettle prevented any pick-up. We

needed a non metallic kettle. Rather than risk personal injury by asking the local ironmonger for a wooden kettle, we cut the bottom out of our existing one, and it appeared quite normal. The finished product was very satisfactory, and with the kettle lifted off the table, up to a distance of three feet speech was audible.

In operation, small hidden microphones in the edge of the table would pick up the customers voice and relay it to the "fortune teller" in a back room. He would give his prognostication, which would arrive via the kettle spout.

In those days our workshop was just a bench near the wall. Imagine the dismay of a potential customer entering the shop and seeing my brother apparently talking to himself and then picking up a kettle and sticking the spout in his ear! !

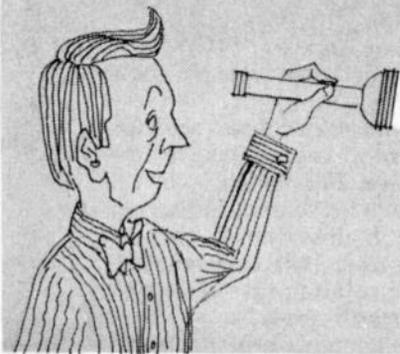By way of compensation, it gave us many laughs. Our friend Ashraf seemed delighted with the result and said, "You must come over to my house and have a real Indian dinner." I still have the scars on my tongue, of second degree burns, caused by the Curry!! Well a merry Christmas to you all and a successful 1975.



Physics IS FUN!

By Derrick DAINES



THE TORCH BATTERY

If a run-down torch battery is taken to pieces it will be found to consist of a carbon rod held in the centre of a zinc tub. Between the rod and the walls of the tub is white "goo" or paste made of ammonia solution thickened by starch or gelatine.

Sometimes the zinc tub is surrounded by a cardboard tube with the maker's name on it, but sometimes the outer sheath is of steel for strength and to prevent the "goo" leaking out, Fig. 1.

Now we cannot make the battery as good as new, but we can get some more life out of it quite simply. Discard the steel sheath and thoroughly wash the carbon rod and zinc tube free of ammonia paste.

You will need two or perhaps three old batteries to light a torch bulb. You also need some paper-clips and wire.

Solder a piece of wire to each of the brass caps at the end of the carbon rods and at the other end of the wire fasten a paper-clip. Now make a simple frame of wood or Meccano and hang the carbon rods in their zinc tubs, making sure that they do not touch the tub walls.

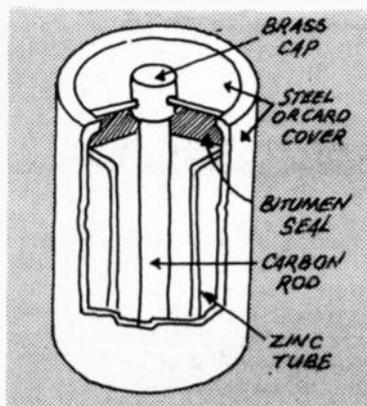


Fig. 1. Details of the inside of a dry cell.

The circuit of Fig. 2 can now be completed by clipping the wires to the zinc tub next to it, etc., making a circuit or circle of wires.

Now mix some ordinary common salt with warm water, stirring in more salt until no more will dissolve. Pour this salt water into the tubs. The bulb will light.

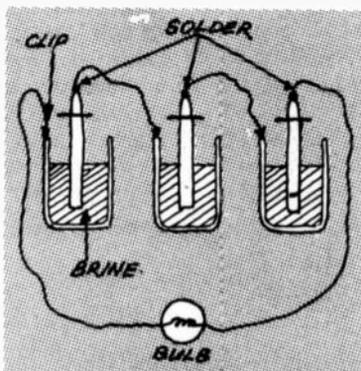


Fig. 2. The remains from three old batteries to make a new one.

What is happening? The carbon terminal is called positive, the zinc negative and the liquid (salt solution) is called an electrolyte. Electrons—remember these are parts of atoms—float across the electrolyte from the positive to the negative terminal. They then bustle along the wire, through the lamp back to the positive terminal again, doing work on the way—heating the wire of the bulb to white-hot brightness. This is one type of simple electric cell, caused by chemical action.

An Italian called Galvani hung up some frogs' legs expecting them to jerk with the approach of a thunderstorm. It so happened that he used a copper hook and hung the legs near an iron balcony.

He was amazed to see that the frogs' legs jerked every time the wind blew them against the iron grill. (You might try this your-

self!) Galvani thought that the electricity was produced by the frogs' legs, but it was left to another chap Volta to show that the real cause lay in the *dissimilarity* of the metals used—copper and iron—with a weak acid between them.

Any two dissimilar metals with a weak acid between them will make a source of electricity.

Volta used copper and zinc with sulphuric acid between. The car battery uses lead and zinc—there are many combinations.

If the reader has a voltmeter he can conduct a series of experiments using different metals and find out which gives the best results. For the electrolyte—a citrus fruit can be used! Fig. 3.

Put an iron nail in one side of a cut lemon and a copper nail in the other side. The voltage will be low, but the method has been used to light a torch bulb!

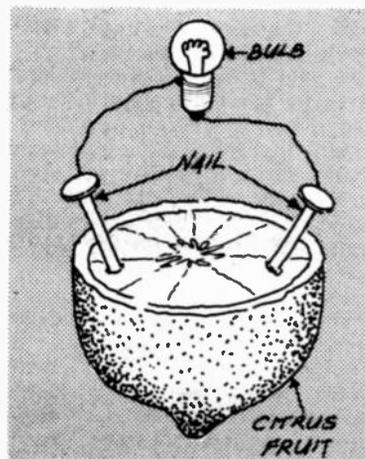


Fig. 3. A "fruit battery". The nails must be of dissimilar metals.

BEGIN HERE

PART TWO SEMICONDUCTOR DEVICES

By DONALD MAYNARD



In Part One we looked at the basic components found in electronic circuits. This month we are concerned with semiconductor devices. The most common of these are diodes, thyristors, transistors and integrated circuits and as before the information will mainly be aimed at those wishing to construct circuits but feel themselves lacking in knowledge.

JUNCTION DIODES

The junction diode is a device with two leads having the property that it will ideally pass a current through it in one direction but not in the other. In practice there is a very small reverse current, but in most applications this can be ignored. The symbol for a diode is shown in Fig 2.1a.

Logically one would expect that a positive voltage applied to B would cause the diode to conduct i.e. a current would flow through the diode. Unfortunately, because the early discoverers of electricity were not aware of the existence of electrons, this is not the case. Consider the convention that current flows from positive to negative.

The arrowhead in the symbol shows the direction of the "conventional" current. We sometimes

talk about the anode (A) and cathode (B) of the diode, comparing it with its thermionic valve counterpart. In this instance the cathode is the positive *marked* end of the device.

If we should measure the diode's resistance with a multimeter we are in for another surprise. Despite what has been said above, connecting the positive lead to B and the negative lead to A produces the lowest reading of resistance showing that the current is much larger with that polarity. This is because the voltage on the positive lead is in fact negative and vice versa. Two wrongs do make a right sometimes!

There is a small voltage drop across the diode when it conducts i.e. it is forward biased—Fig. 2.2a. This is of the order of 0.2 volt for a germanium diode or around 0.8 volt for silicon types. When the diode is off i.e. it is reverse biased (Fig. 2.2b), a large voltage may be present across the device. If the voltage is increased beyond a certain point however, the diode will be destroyed. This is called the breakdown voltage. The peak inverse voltage (p.i.v.) quoted is slightly less than the breakdown voltage to avoid damage if used "on the limit".

When considering a replacement for a specified diode it is important to consider the peak

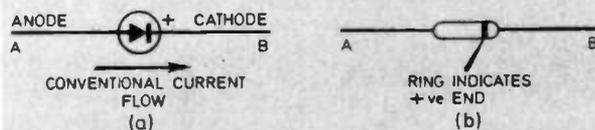


Fig. 2.1. The junction diode (a) diode symbol (b) a small junction diode.

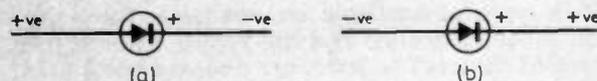


Fig. 2.2. Biasing of a diode (a) forward biased (b) reverse biased.

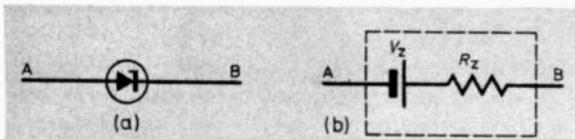


Fig. 2.3. The Zener diode (a) symbol (b) equivalent circuit.

inverse voltage and the maximum forward current. In addition it is usually important to keep to the same type as that stated e.g. silicon junction, or germanium point-contact.

ZENER DIODES

Strictly speaking the heading should read "Zener and avalanche diodes". The difference between them is in the internal action of electrons which produce different reference voltages and also different temperature coefficients. For our purposes we can consider them both to be voltage reference diodes.

The diodes operate in their reverse biased state at the breakdown voltage. While in junction diodes this would prove disastrous, by limiting the current through the Zener diode we can use it as voltage reference. The symbol for such a diode is shown in Fig. 2.3a, while Fig. 2.3b shows its equivalent circuit, which helps us to see how the device operates.

The battery voltage V_z gives us a voltage reference while the internal Zener resistance R_z tells us that as we draw more current through the diode the overall voltage across A to B will vary. This variation will only be slight as R_z is quite small.

The figures quoted for voltage reference diodes in advertisements usually show the nominal Zener voltage (V_z) and the maximum power dissipation (P_z). From this it is easy to determine the maximum Zener current (I_z) because:

$$P_z = I_z \times V_z$$

Therefore a 7.5 volt, 400mW Zener diode has a maximum Zener current of 0.053 amps or 53mA. A series resistor is always used with a voltage reference diode to bias it and also to limit the Zener current.

THYRISTORS

The thyristor, or controlled semiconductor rectifier, is a device with three leads. It has both anode and cathode like a diode but it then has a third connection called the gate or grid. The purpose of the gate is to cause the thyristor to "fire", i.e. to produce a short-circuit between its anode and cathode.

Symbols for the thyristor are shown in Fig. 2.4. Two types of thyristor are available, the *n*-gate or anode controlled and the *p*-gate, cathode controlled device. The latter are almost always used, the thyristor being operated with the anode more positive than the cathode.

These devices are mainly used as semiconductor switches so as to control the voltages reach-

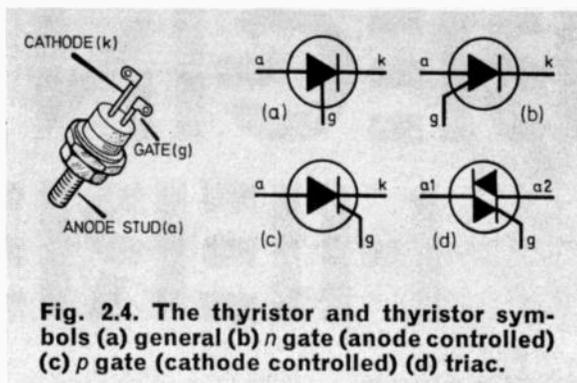


Fig. 2.4. The thyristor and thyristor symbols (a) general (b) *n* gate (anode controlled) (c) *p* gate (cathode controlled) (d) triac.

ing a load. Bi-directional thyristors can be obtained and they are then usually called triacs (Fig. 2.4d). These devices "fire" in the same way as a thyristor but can pass current in both directions.

BIPOLAR TRANSISTORS

Bipolar transistors come in two main configurations—*pnp* and *npn*. The first type is usually operated with a positive earth and the second with negative earth. Older transistors tend to be made from germanium although silicon is now generally preferred for reasons to do with stability, gain and low leakage currents. The three leads are called the emitter (e), base (b), and collector (c). There may be a fourth lead connected to the transistor's case acting as a screen (s).

The *pnp* transistor is shown schematically in Fig. 2.5a together with the voltage polarities. The double negative on the collector shows that normally its voltage is much more negative than the base which in turn is slightly more negative than the emitter.

The action of the base is to "turn on" the current flowing from emitter to collector. If the current in the base lead is I_b then the current flowing in the emitter and collector leads will be approximately βI_b , where β is the common emitter amplification factor (sometimes known as h_{fe}). The value of β may vary from ten up to a few hundreds. The operation of the transistor is complex and it uses numerous, the devices will not be covered in more detail in this series.

The *npn* transistor operates in exactly the same way, except that the voltage polarities are reversed (Fig. 2.6b). In addition, all currents will flow in the opposite direction. Note that it is only the arrow in the emitter lead which shows whether the transistor is *npn* or *pnp*. The base-emitter voltage under normal conditions is about

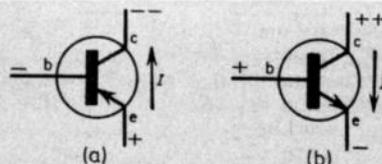


Fig. 2.5. Bipolar transistors (a) *pnp* transistor (b) *npn* transistor.

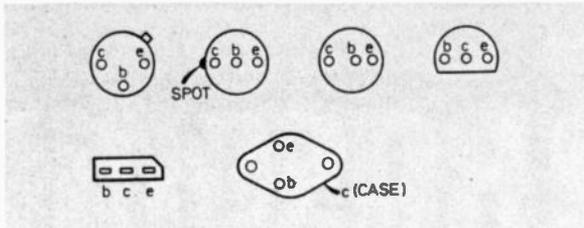


Fig. 2.6. Some transistor lead-outs.

0.2 for germanium, and 0.7 for silicon. This applies to both *pnp* and *nnp* types.

Transistors come in a variety of shapes and sizes, and some of the lead arrangements are shown in Fig. 2.6. For accurate substitution of different types of transistor a good substitu-

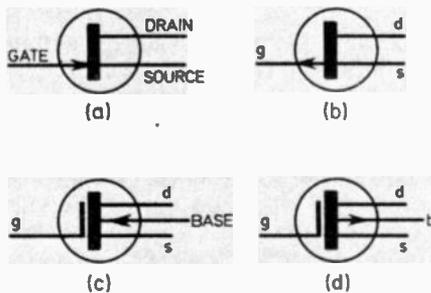


Fig. 2.7. Field effect transistors (a) *n* channel (b) *p* channel (c) *n* channel junction gate f.e.t. (d) *p* channel junction gate f.e.t.

tion book is desirable, but for general purposes one should allow for maximum collector current, maximum collector/emitter voltage, maximum power dissipation and common emitter amplification factor.

UNIPOLAR TRANSISTORS

There are various types of unipolar transistor but they can all be lumped under the title, field effect transistors (f.e.t.). They can have the characteristic of an extremely high input impedance and they exhibit characteristics associated more with valves than with bipolar transistors. Because of low inter-electrode capacitances these devices are ideal for use at high frequencies.

A few different types of f.e.t. are shown in Fig. 2.7. The insulated gate f.e.t. is also known as the metal-oxide-silicon transistor (M.O.S.T.). Constructors are most likely to come across these devices used in applications requiring a high input impedance and low noise amplification. Lead-out arrangements vary but two common types are shown in Fig. 2.8.

Next month: Integrated circuits.



Fig. 2.8. Two f.e.t. lead-outs.

Ruminations

By Sensor

Adding it up

"Who has got a calculator?" Perhaps the question ought to be "Who has not got a calculator?", for I seem to be one of the few who still relies upon mental arithmetic, slide rule, or pencil and paper. I find, increasingly, that my traditional methods of calculation are too slow when compared with even quite a modest electronic calculator. This fact was brought home to me when I was watching the last general election broadcast on TV.

A few years ago one had time to calculate percentage swings and to forecast the number of seats likely to be lost and won by the various parties, working from the results as they were displayed. I used to try to beat the cephalogists (I think that's the right word)

at arriving at these analysis figures, but no longer. The programme has become much too slick and polished. There is no room now for the amateur.

"Swingometer" and "slideometer" fed by experts aided I suspect, by dozens of electronics calculators, display the forecasted results before I can get my slide rule moving. One becomes just a passive observer; the "audience participation" of election programmes years ago has disappeared, it's hardly worth staying up any more!

Working it out

I welcome the calculator, it takes the sheer drudgery out of calculation, we ought to have had them years ago. Mercifully, decimalisation has simplified many previously tedious arithmetical tasks; do you remember the long division of money sums that we were taught at school? What a grind that was! And anyone who studied electrical or mechanical engineering before S.I. units came

into use had to cope with a host of different units and umpteen conversion factors. Those brought up under the old system tend to cling to it because it is familiar, but even the most diehard must admit that it is quite illogical.

I wonder if we shall see a time when those who know how to do traditional arithmetic or work in Imperial units will be as rare as thatchers and drystone walls. I can imagine them working in industrial museums translating old drawings and specifications, being called upon by the archeologists and historians of the future to demonstrate how to extract a cube root in the manner of the 19th Century.

But I must admit that one unit in particular has always intrigued me, perhaps because it has three names, this is the good old "rod, pole or perch". What a fine strong, upright and honest unit that is! It is sad to see these old units go, for they are part of our history and heritage. But we must accept the new, with its many advantages, in the interest of progress.

It's invisible... it's inaudible... Make it ULTRASONIC

LAST month details were given to build the ultrasonic receiver. This month the article is concluded with the transmitter.

THE TRANSMITTER

The transmitter circuit is shown in Fig. 4, and uses the NE555V integrated circuit wired as an astable multivibrator. This is an eight pin dual-in-line device, but a similar device can also be obtained in a metal-can encapsulation.

The output at pin 3 switches between a potential just above that of the negative supply line to a value just below that of the positive supply. The capacitor C1 alternately charges and discharges through VR1 and R1, the frequency being set by VR1.

Each time the potential at pin 6 rises to two-thirds of the positive supply potential, the output at pin 3 is switched to the low voltage state. Similarly, whenever the potential at pin 2 falls

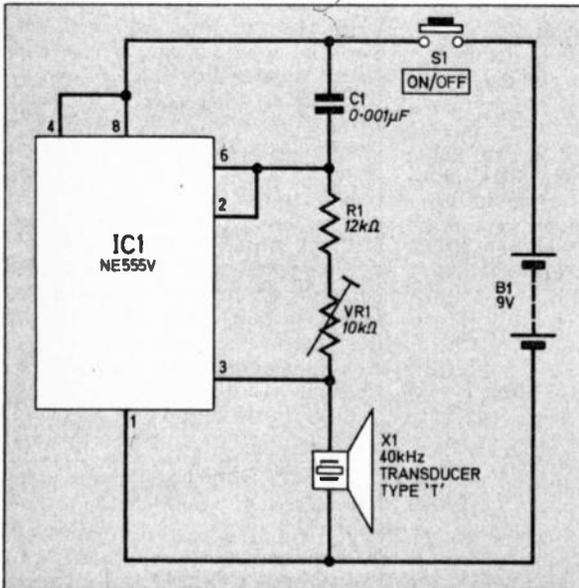


Fig. 4. The circuit diagram of the Ultrasonic Transmitter.

to one-third of the positive line potential, the output at pin 3 is switched to its high voltage state.

The maximum permissible power supply voltage to the NE555V is 16 volts, but it is wise to regard 15 volts as the maximum so as to allow some margin of safety.

The circuit will operate from a 6 volt supply, but the power output and the range are then very limited. A 9 volt PP3 battery is very convenient for operating the transmitter unit, but the maximum distance for satisfactory operation will be increased by a few yards if the supply voltage is increased to 15 volts.

The power supply current is quite small, being typically 4 milliamps at 6 volts and 10 milliamps at 15 volts.

The capacitor C1 should be a mica or polystyrene type, the smaller polystyrene type having been used in the prototype.

The type of ceramic capacitors intended for decoupling purposes are unsuitable for this application, since they have a very wide tolerance in their value and this may prevent the correct frequency from being obtained.

TRANSMITTER CONSTRUCTION

In the prototype the transmitter circuit was constructed in an Eddystone die-cast box size approximately 120 x 95 x 55mm. Plenty of space is available for either a large battery or mains power supply.

The transmitter circuit was built on a piece of 0.1inch plain matrix board size 85 x 48mm approximately.

FOR
GUIDANCE
ONLY

ESTIMATED COST*
OF COMPONENTS
including V.A.T.



£5.50
excluding case

*Based on prices prevailing at
time of going to press

work for you — (No licence required!)

REMOTE CONTROL

PART 2 TRANSMITTER

By J.B. DANCE

Begin construction by cutting the board to size and drilling the fixing holes. Now insert the transducer (T type), the 8-pin socket and the components in the board as shown in Fig. 5 and wire up as detailed. Insert the i.c. in the socket paying attention to polarity. Note that components are mounted on both sides of the board.

The trimmer potentiometer VR1 must be fixed in such a position that it can easily be adjusted when the circuit board is fitted inside the box.

Drill a 12mm diameter hole in the box along one of the short sides in such a position that the ultrasonic transducer grille is directly behind this hole when the board is fitted in the box. Now secure the board to the case with three 6BA nuts, bolts, spacers and washers, such that the transducer does not touch the case.

Components

R1	12k Ω $\frac{1}{2}$ W carbon \pm 10% resistor	SEE SHOP TALK
VR1	10k Ω lin. skeleton preset potentiometer	
C1	0.001 μ F mica or polystyrene capacitor	
IC1	NE555V timer integrated circuit	
S1	s.p.s.t. push button type to suit	
X1	96D-40(T) ultrasonic transducer (Hall Electronics)	
B1	9V battery type PP3	
0.1in. plain matrix board size 85 x 48mm (approx.); 8-pin d.i.l. socket for IC1; diecast aluminum case size 120 x 100 x 55mm; battery clips to suit B1; 6BA fixings; connecting wire.		

TESTING AND ADJUSTMENT

Thoroughly check out the circuit construction and when completely satisfied, the power supply (battery or other) may be connected to the receiver and current consumption monitored. The relay may close each time the power is first applied.

Place the two boxes such that the two transducers are facing each other about 10cm apart and apply power to the transmitter circuit. The receiver relay will probably close, but if it does not do so, VR1 should be adjusted fairly coarsely until the relay closes.

If the relay still does not close, a high resistance meter should be connected across points XX in Fig. 1. If the part of the circuit containing the TAA 930B and the diode pump is functioning correctly, a reading of over 5 volts will be obtained. This reading should decrease as the transmitter and receiver are separated and as the transducers are moved so that they no longer face one another.

The positions of the units should be adjusted so that only a small reading is obtained on the meter; VR1 of the transmitter should now be adjusted for the maximum meter reading.

It is possible to adjust VR1 without a meter by adjusting it for the greatest sensitivity of relay closing.


PERFORMANCE

The maximum range of the prototype equipment was about 12 metres (40 feet) in the open air. It is possible that a unit could have been designed with a somewhat greater range, but it would then have been more sensitive to stray vibration.


In the prototype the relay may close if the grille of the receiver transducer is tapped, but the time constants have been chosen so that the equipment is fairly insensitive to transient vibrations.

If the equipment is operated in a corridor, an increased range may be expected, since the walls will reflect some of the ultrasonic energy towards the transducer in the receiver. The waves are also readily reflected from the walls of a room or from a ceiling.

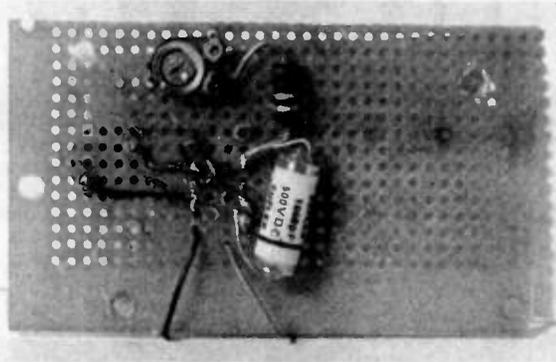The 40 kilohertz ultrasonic waves are fairly directional. If the transmitter and receiver are taken into the open air, the transducers can be placed fairly near to one another without the relay being operated if they are facing in opposite directions or have an angle of over 90



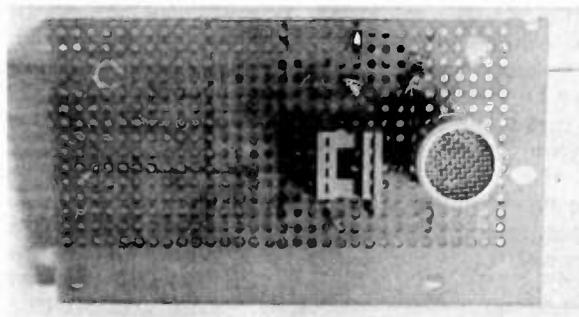Photographs, above and below of the prototype component board.



ULTRASONIC REMOTE CONTROLLER

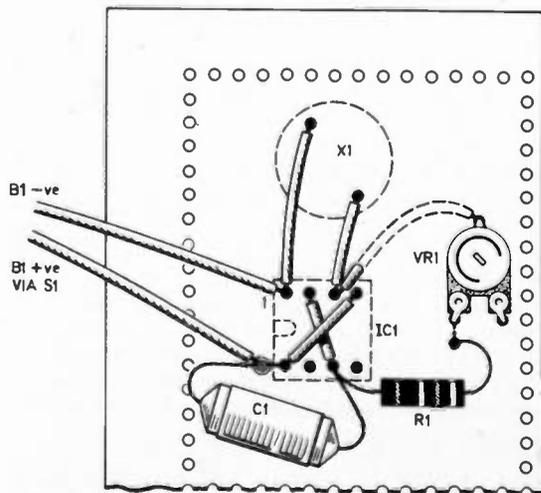


Fig. 5. Layout of the components and wiring up details on the plain matrix board. Wiring on the top of the board is shown dotted.

degrees of arc between them.

In a small room one may find that the relay will close whenever the transmitter is switched on irrespective of position; this is due to reflection.

The mechanical resonance of the transducers causes them to "ring" for a millisecond or so after the transmitter waveform has ceased and it would seem that this effect and the limited bandwidth would prevent speech being conveyed as a modulated ultrasonic wave using these techniques.

APPLICATIONS

Ultrasonic waves can be used for a variety of applications, but unfortunately they are attenuated fairly strongly in air and therefore their range is fairly limited in all applications. The following applications are typical ones for a transmitter-receiver system, but readers will doubtless find many other applications.

Remote Control

A small transmitter unit carried by a person can be employed to switch any other piece of equipment to which the receiver is connected. For example, channel changing in a television or radio receiver may be accomplished using an ultrasonic link. A pulse from the transmitter can be employed to cause the relay to rotate a switch or coil turret in the receiver.

One can thus rotate the channel selector switch from one's chair with repeated pulses until one returns to the same channel as was first being received if one wishes. In this type of equipment the transmitter could be battery driven, whilst the ultrasonic receiver (which is always switched on when the equipment is in use) could be driven from the equipment supply.

Ultrasonic beams are also useful for garage door opening or closing. When a driver reaches his home, he can press a button in his car to switch on an ultrasonic transmitter mounted under the car's front bumper. This signal operates a receiver mounted by the side of the garage door so that a relay closes and provides power to the door operating mechanism. When the motorist takes his car out again, a similar ultrasonic signal can be used to close the door.

An elderly or infirm person could carry a small ultrasonic transmitter which could be used to switch on an illuminated sign in the window calling for help. The sign could be switched on from anywhere within the room or even from the next room if the door between the rooms was open.

The range of ultrasonic waves is too limited for them to be used to control model aircraft. However, they can be used to control many types of children's toys. They are suitable for the remote control of small model boats provided that the range is reasonable. It will be

necessary to fit more than one transducer on the boat so that the waves can be received no matter in which direction the boat is travelling at the time.

Ultrasonic waves are also used by the police to switch motorway fog warning lights without stopping their cars.

Communication

The Post Office Act of 1969, Section 24(1) confers the exclusive privilege of running systems for the conveyance, through the agency of electric, magnetic, electro-magnetic, electro-chemical or electro-mechanical energy of speech, music, other sounds, visual images, etc. In view of the fact that the repulsive forces between the air molecules in an ultrasonic wave are electrical in nature, the writer did check with the Post Office that an ultrasonic communication system would not infringe their monopoly and received their confirmation that no licence is required.

One can therefore communicate with one's neighbour by means of an ultrasonic beam, but it is not permissible to adopt the much simpler method of throwing a wire over the fence between the houses!

The transmitter could be modulated by switching it on and off to produce a morse signal, but the receiver time constant may have to be reduced.

Intruder Alarm

If the transmitter is placed at one side of a corridor and the receiver at the opposite side, any intruder interrupting the beam will cause the relay to open. This could be used to sound an alarm. If the alarm does not sound in the corridor or room, the intruder will not know he has been detected.

If the intruder rotates either the transmitter or receiver or switches either of them off, it can be arranged that the alarm will sound. In this application it is best to reduce the transmitter supply voltage so that it is only slightly above the level at which the relay keeps closed.

Leak Testing

If the transmitter is placed inside a car, the interior of the vehicle is filled with ultrasonic waves. One can then pass the transducer in the receiver around the edges of the doors and windows and find any small leaks.

Leaks in the sealing rubber of refrigerator doors can be found in a similar way. It is better to use a receiver employing a voltmeter, as indicated in Fig. 1, rather than a relay for leak testing.

Leaks in pressure pipes can also be found using a receiver with a meter, since such leaks generate ultrasonic waves. □

RAIN ALARM

By L. HARDMAN

An audible warning is sounded when it rains or snows.

THIS is a particularly useful device for the housewife. With this unit she does not have to keep a watchful eye on the state of the weather if clothes are drying on the garden clothes line. As soon as rain (or snow) falls on the sensor an audible alarm sounds drawing ones attention to the fact that it is raining.

CIRCUIT

The circuit diagram of the Rain Alarm is shown in Fig. 1 and is seen to be extremely simple. With S1 in the "on" position, 12 volts is placed across the series combination of the thyristor CSR1 and audible warning device WD1.

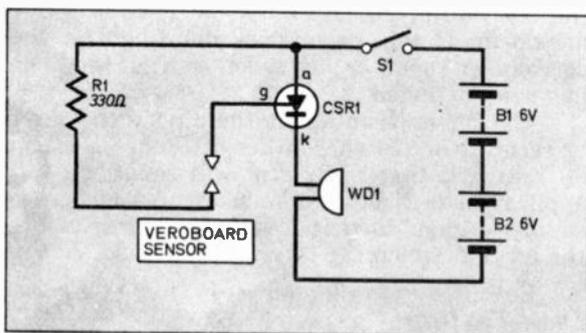


Fig. 1. The circuit diagram of the Rain Alarm.

When the sensor is dry, the gate of the thyristor is not connected, hence CSR1 is "off", i.e. no current flows. Now when the strips of the sensor are shorted, or rain bridges any two adjacent strips, a positive voltage is applied to the gate of CSR1, thus turning it "on". Current then flows through the thyristor and alarm device producing an audible tone.

The alarm can only be muted by switching off at S1. Resistor R1 is included to limit the gate current to a safe level.

Components....

R1 330Ω ½ watt carbon resistor
 CSR1 CRS1/05 or any similar thyristor
 S1 on/off toggle switch
 WD1 12V audible warning device (Doram)
 B1, B2 PP1 6V battery (2 off)
 Veroboard: 0.1in. matrix, 100 x 100mm (see text); aluminium for case; rubber grommet; length of twin-cable; battery clips for PP1 (2 pairs); tag strip.

CONSTRUCTION

The prototype unit was housed in an aluminium case, dimensions and front panel layout shown in Fig. 2. The rear panel of the case is to be made removable.

Begin construction by making the case and the cut-outs to suit S1, WD1 and the lead-out to the sensor.

The circuit is built on a short length of tag strip. Begin by soldering R1 and CSR1 to the tag strip and fix to the case as detailed in Fig. 3. Secure S1 and WD1 to the case and wire up according to Fig. 3.

Pass the two external wires through the grommet and place the two batteries in position, and

FOR
GUIDANCE
ONLY

ESTIMATED COST*
OF COMPONENTS
including V.A.T.



£3.00
less cable

*Based on prices prevailing at time of going to press

RAIN ALARM

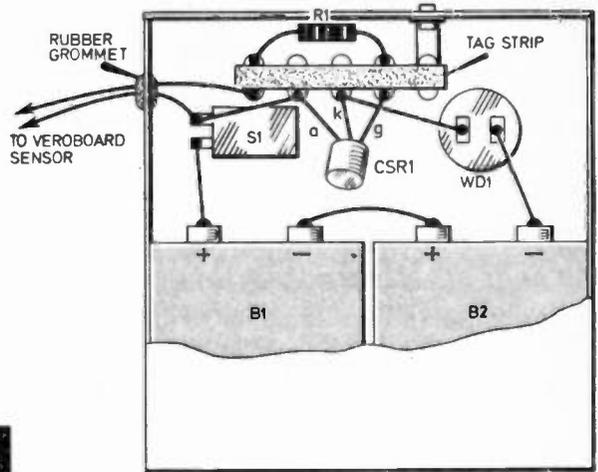


Fig. 3. Wiring up details.

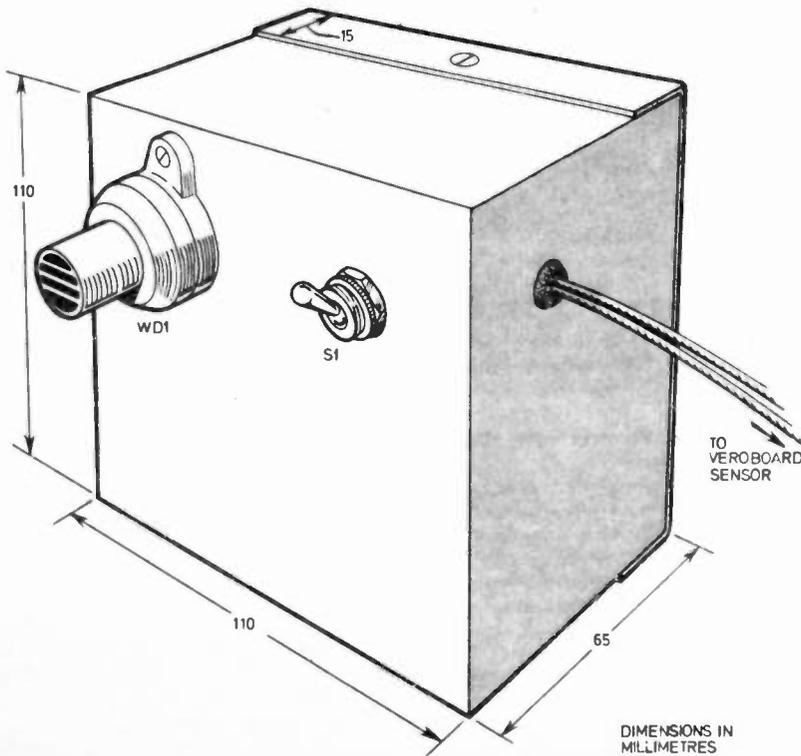


Fig. 2. Details of the aluminium case used to house the prototype showing positioning of components on the front panel.

screw on the back panel. The case has been designed so that the batteries fit snugly into the base of the case, eliminating the need for a fixing bracket.

SENSOR

The sensor should be made from a piece of 0.1in. matrix Veroboard. The size of this board is not critical, but the larger it is the more sensitive. A suitable size is about 100×100mm.

Make the board by simply soldering a length of wire across all the strips at each end of the board and then make breaks at each end to alternate tracks as shown in Fig. 4.

INSTALLATION AND USE

The Veroboard sensor should be located in the garden in an unsheltered position out of reach of the wet washing, on top of the line pole for example. It is advisable to mount the sensor at an angle so that rain falling on the sensor can run off more easily.

The case itself should be mounted inside the house (e.g. kitchen) so that the alarm can be easily heard from all parts of the house. The two units should be joined with a suitable length of twin cable.

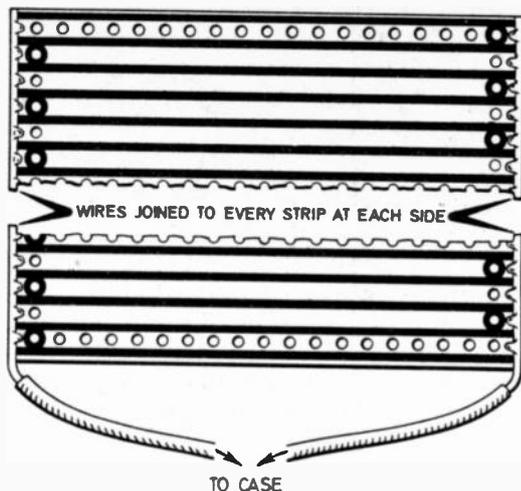


Fig. 4. Details of the sensor board.

Normally, the unit should be switched off and only turned on when washing is on the line. If the alarm sounds, due to falling rain, switch off at S1. When the unit is next switched on it may be necessary to wipe the sensor board with a dry cloth. □

BOOK REVIEWS

ELECTRONICS: AN ELEMENTARY INTRODUCTION FOR BEGINNERS

By L. W. Owers, C.Eng. M.I.E.R.E.

Published by Publication Mailing Services,

P.O. Box 6, Crawley, Sussex RH10 6LH

Size: 119 pages perfect bound, 21 x 15 cm.

PRICE: £1.45 including post and packing from above address.

This book has been written for students and is not intended to teach the constructor the basics of electronic circuit theory. The first third of the book is concerned exclusively with static electricity, fundamental particles and electron theory.

We are then led quickly through current, and passive components before meeting the valve and its derivations which are again dealt with very briefly. Semiconductor devices take up 12 pages, most of which is used to describe semiconductor theory and the action of electrons and holes in diodes and transistors. There is no introduction to actual circuits or circuitry.

The explanations are good and the maths is kept to the minimum. The drawings are clear and uncluttered but tend to take up larger areas than necessary. For the convenience of teachers the illustrations are available as 35mm colour slides.

A good grounding for the "O" level student but not much else, most readers would very quickly require more information.

M.K.

BEGINNERS' GUIDE TO ELECTRONICS (Third Edition)

By T. L. Squires and C. M. Deason

Published by Newnes-Butterworths

Size: 240 pages, 20 x 12cm.

PRICE: £1.90

This is a somewhat old-fashioned style of book that crams in as many different topics (areas of application) of electronics as possible. There is not one photograph in the whole 240 pages, although photographs would have been much better in some cases than some of the line drawings.

However, illustrations are clear and many circuit diagrams are supplemented by pictorial schematic diagrams of the physical circuit set-up. This is a great help for the beginner.

First published in 1964, this third edition has been updated (!) to include a chapter on the digital computer and a chapter on microminiature electronic components—18 pages each chapter.

A quick scan through the book can be off-putting through the number of valve drawings and symbols one will see. Clearly this third edition has not been updated sufficiently.

In this age of integrated circuits, a book published in 1974, containing as many valve references as this one, is coming it a bit.

The authors say this book is intended for those thinking of a career in electronics. It has been written without the use of mathematics, which makes for easy reading for those with no technical knowledge in the electronics field. It would prove most useful on the shelf of a school library.

B.W.T.

NEXT MONTH...

A high power stereo amplifier designed using modules for ease of construction. Providing 20 watts r.m.s. per channel (40 watts total), this amplifier has the added facility of a guitar input.



modula 3 STEREO AMPLIFIER



Lighting up Warning FOR THE MOTORIST


Don't get caught with no lights on. This device provides a warning as night falls or when driving away at night.

MORSE PRACTICE UNIT

A unique design practice unit for use with a normal or cassette recorder and providing audible and/or visual output.

everyday electronics

FEBRUARY ISSUE
ON SALE FRIDAY
JANUARY 17

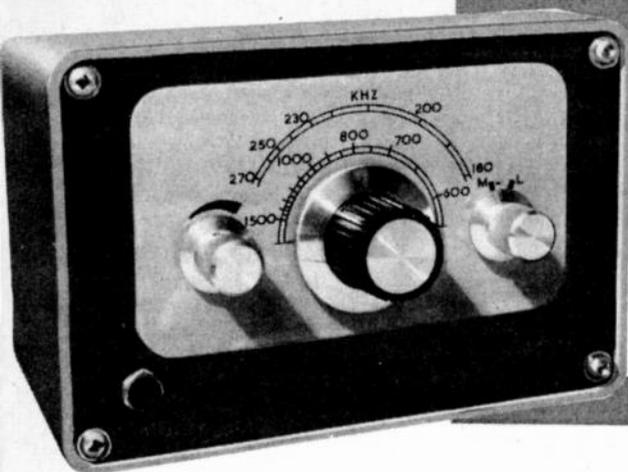

2 BAND SUPERHET TUNER

BY F. G. RAYER

You can plug this tuner into almost any audio amplifier, to obtain radio reception with all the power the amplifier is capable of giving. The tuner is completely portable and self-contained, operating from its own internal battery.

A superhet circuit has a greater number of components than the simpler type of "local station" tuner, but is much more selective and sensitive. This circuit has only two transistors and a diode, but will be found to give excellent results. Some simplification is possible by constructing the tuner for medium wave reception only, and long wave reception can be provided later if required.

OPERATION

The circuit diagram is shown in Fig. 1. Signals are picked up by the ferrite rod aerial, producing a signal voltage in the coil L1, which is tuned by the variable capacitor C2. Signals reach the base of TR1 from the coupling winding L2. This transistor also has emitter and collector coupling windings to the oscillator coil L3, which is tuned by C7. Capacitor C7 is the second section of the ganged tuning capacitor.

Throughout the tuning range a constant frequency difference of 465kHz is maintained between circuit L1 and L3. As a result, of the mixing of received signals with the oscillator frequency to which L3 is tuned, all signals provide a 465 kHz output from TR1. Both windings of the intermediate frequency transformer IFT1 are permanently tuned to 465kHz. Signals pass to the intermediate frequency amplifier TR2, and to the second intermediate frequency transformer IFT2, also tuned to 465kHz.

Diode D1 operates as a detector and by its demodulator action makes available the audio signal, or programme, at VR1. Potentiometer VR1 is a volume control, the wanted level of signal being taken from the slider, via C12, to the output socket and hence the audio amplifier being used.

Diode D1 also produces bias for TR2, through resistor R6. This provides automatic volume control. Strong signals produce more bias to reduce

the gain of TR2, but when signals are weak, gain is allowed to rise. This results in a more equable volume from signals of widely different strength, and helps counteract fading, or variations in signal strength.

No values are shown for trimmers C1 and C6 because these are integral with the tuning capacitor. Should a capacitor without trimmers be used, extra trimmers, each of 30pF or 60pF, must be added. The capacitors associated with the IFT windings are also present inside these components already. The IFTs listed are pre-tuned to 465kHz by the maker, so the cores should be left untouched, except for possibly small adjustments made as described later.

It is convenient to have the individual volume control VR1 on the tuner. Any volume and tone controls on the amplifier can be left in those positions found most suitable.

CIRCUIT BOARD

Most components are mounted on a plain perforated board measuring about 20 by 17 holes (0.15 inch matrix), Fig. 2. Begin by drilling holes for the pins of L3, IFT1 and IFT2. If these items do not fit easily, the holes can be enlarged with a small round file. Also drill holes for the brackets and paxolin strips X-X which will support the ferrite rod.

The metal sub-panel is 90 x 50 mm with a flange to which the board is fixed with two 6BA bolts. It can be bent in a vice, or a ready-angled "universal chassis" flanged member can be used. This panel allows the tuner to be mounted to the case panel by the screws which will secure C2/C7.

FOR
GUIDANCE
ONLY

ESTIMATED COST*
OF COMPONENTS
including V.A.T.



£6.60
excluding case

*Based on prices prevailing at
time of going to press

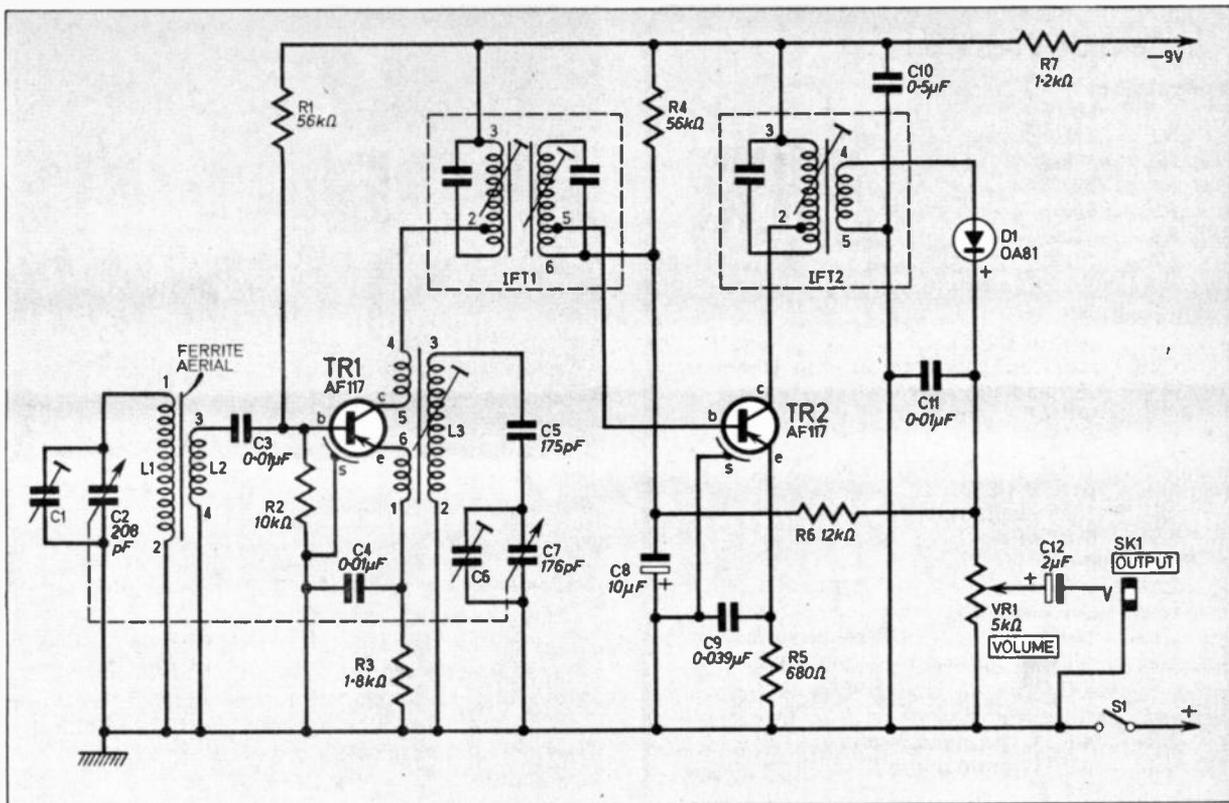


Fig. 1. The circuit diagram of the 2 Band Superhet Tuner.

Components are placed as in Fig. 2, temporarily omitting the aerial, transistors, and tuning capacitor. Underneath wiring is also shown in Fig. 2.

Two tags form an earth return to the sub-panel and frame of C2/C7 when this is fixed. Secure L3 and the IFTs by bending out the can tags, and note that these are wired to the earth line.

The wire ends of resistors and capacitors come through the holes as in Fig. 2, they are bent over, soldered to the correct points, and cut off. In a few places some 22 s.w.g. or other connecting wire will be required. Put insulating sleeving on any leads which come near other leads or joints.

Note that C8 has positive and negative ends, and that positive goes to earth. In the same way, when C12 is wired, its positive lead is taken to the slider or centre tag of VR1.

GANGED CAPACITOR

The tuning capacitor is fixed to the sub-panel with three short 4BA bolts, which run into holes provided in the front plate of the capacitor. These bolts must be short, so that they will pass through the case panel, sub-panel and capacitor without projecting and thereby shorting or damaging this item. Alternatively, sufficient washers can be put between the capacitor and sub-panel, provided the spindle projects enough for the control knob.

Solder C5 to the back tag (C7), as in Fig. 2.

TRANSISTORS

Arrange the transistor leads so that they emerge as in Fig. 2, allowing about 10 mm of lead above the board. The wires must be positioned so that they cannot touch each other, or short lengths of insulated sleeving can be put on before inserting the transistors.

Emitter e, base b, collector c and screen s leads can then be cut to length and soldered as in Fig. 2. If the iron has reached its proper temperature and is removed immediately the joint is made, these joints can be soldered in the usual manner without danger.

Diode D1 can also be fitted now, noting its polarity as shown.

FERRITE AERIAL

The two strips X-X, Fig. 2, are about 50 mm high and 12 mm wide, and can be Veroboard (plain type), Paxolin, wood, or similar material. Cut a "V" shaped notch in the top of each, and drill a small hole below this.

The rod rests across the strips, and is held by thread or thin string passing round it and through the small holes. Place the centre of the rod about level with the spindle of the tuning capacitor so that the tuner can fit into its case.

Place the medium wave section on as in Fig. 2. Solder (1) the beginning of L1 to C2, and the end (2) to the metal frame tag of C2/C7 as in Fig. 2. Take (3) of L2 to C3, and (4) of L2 to earth on the tuning capacitor.

Components

Resistors

- R1 56k Ω
 - R2 10k Ω
 - R3 1.8k Ω
 - R4 56k Ω
 - R5 680 Ω
 - R6 12k Ω
 - R7 1.2k Ω
- All $\frac{1}{4}$ W \pm 10% carbon

SEE
**SHOP
TALK**

Capacitors

- C1 part of C2/C7
 - C2/C7 208/176pF Jackson 00 with trimmers (C1 and C6)
 - C3 0.01 μ F
 - C4 0.01 μ F
 - C5 175pF \pm 1% silver mica
 - C6 part of C2/C7
 - C8 10 μ F elect. 6V
 - C9 0.039 μ F
 - C10 0.5 μ F
 - C11 0.01 μ F
 - C12 2 μ F elect. 6V
 - C13 150pF
 - C14 60pF compression trimmer
- } required for long wave only

Semiconductors

- TR1 AF 117 germanium pnp
- TR2 AF 117 germanium pnp
- DI OA 81

Inductors

- L1/L2/L4 Denco MW/LW/5FR ferrite rod aerial
- L3 Denco TOC.1 oscillator transformer
- IFT1 Denco IFT 18/465
- IFT2 Denco IFT 14/465



Miscellaneous

- VR1 5k Ω log. potentiometer with s.p.s.t. switch (S1)
 - S2 s.p.d.t. rotary switch—required for long wave
 - SK1 3.5mm output jack socket with plug to suit
- Plain perforated Veroboard 20 x 16 holes, 0.15 inch matrix, sub panel 100 x 50mm Universal Chassis flanged member (CU133, Home Radio), case approx 150 x 100 x 100mm, three knobs, battery connecting clips, connecting wire, 4BA fixings.

OTHER CONSTRUCTION

Potentiometer VR1 fits to the panel as in Fig. 2, with the jack outlet (SK1) near. The associated connections can now be made. As the tuner only requires about 2mA, a PP4 battery is adequate and there is no point in using a larger battery. Solder a lead with positive clip to S1. The negative lead runs to R7, or to a Veropin inserted here as an anchor point.

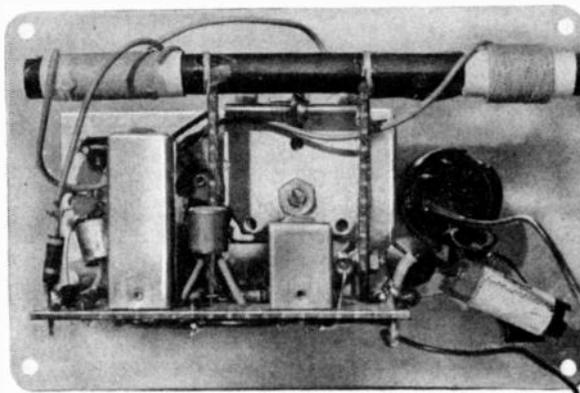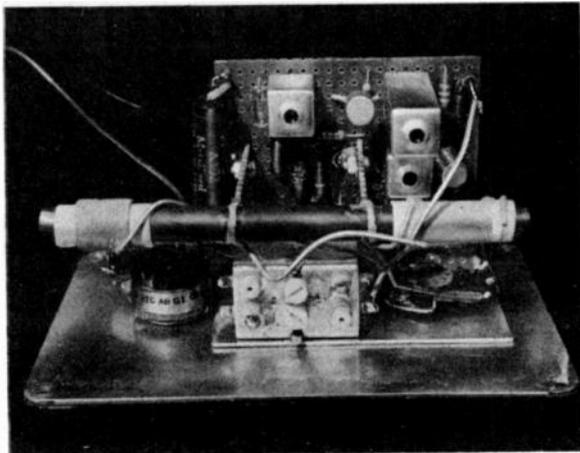The tuner can be tested if wished by plugging in headphones. High-impedance phones (about 2 to 4 kilohms) are most suitable, but many headsets other than low-impedance units will operate satisfactorily.



Photographs of the completed prototype front panel assembly.

To connect the tuner to an amplifier, fit a 3.5 mm jack plug to one end of a screened lead. The jack tip goes to the inner conductor, and the jack sleeve to the outer, braid conductor. At the other end of the lead, fit a plug of the type required by the amplifier, using the outer braid as the "earthed" side of this circuit, in the usual manner.

ADJUSTMENTS

A properly shaped tool is necessary to adjust the cores of L3, IFT1 and IFT2. A steel blade is not suitable, and a screwdriver or other wedge-shaped tool may break the cores. A suitable adjusting tool (TT5) is available from the IFT manufacturer.

Assuming that no signal generator is available, first screw C1 and C6 nearly fully down, and place L1/L2 about 3mm from the end of the rod. Rotating the tuning control should bring in a local station. Tune this in correctly.

The two cores of IFT1 and single core of IFT2 can now be adjusted for best results. Only a small rotation of any core is likely to be needed. A meter, on a range to read around 2mA, may be connected in one battery lead, and these and other adjustments can then be for *minimum* battery current. This corresponds to maximum a.g.c.

2 BAND SUPERHET TUNER

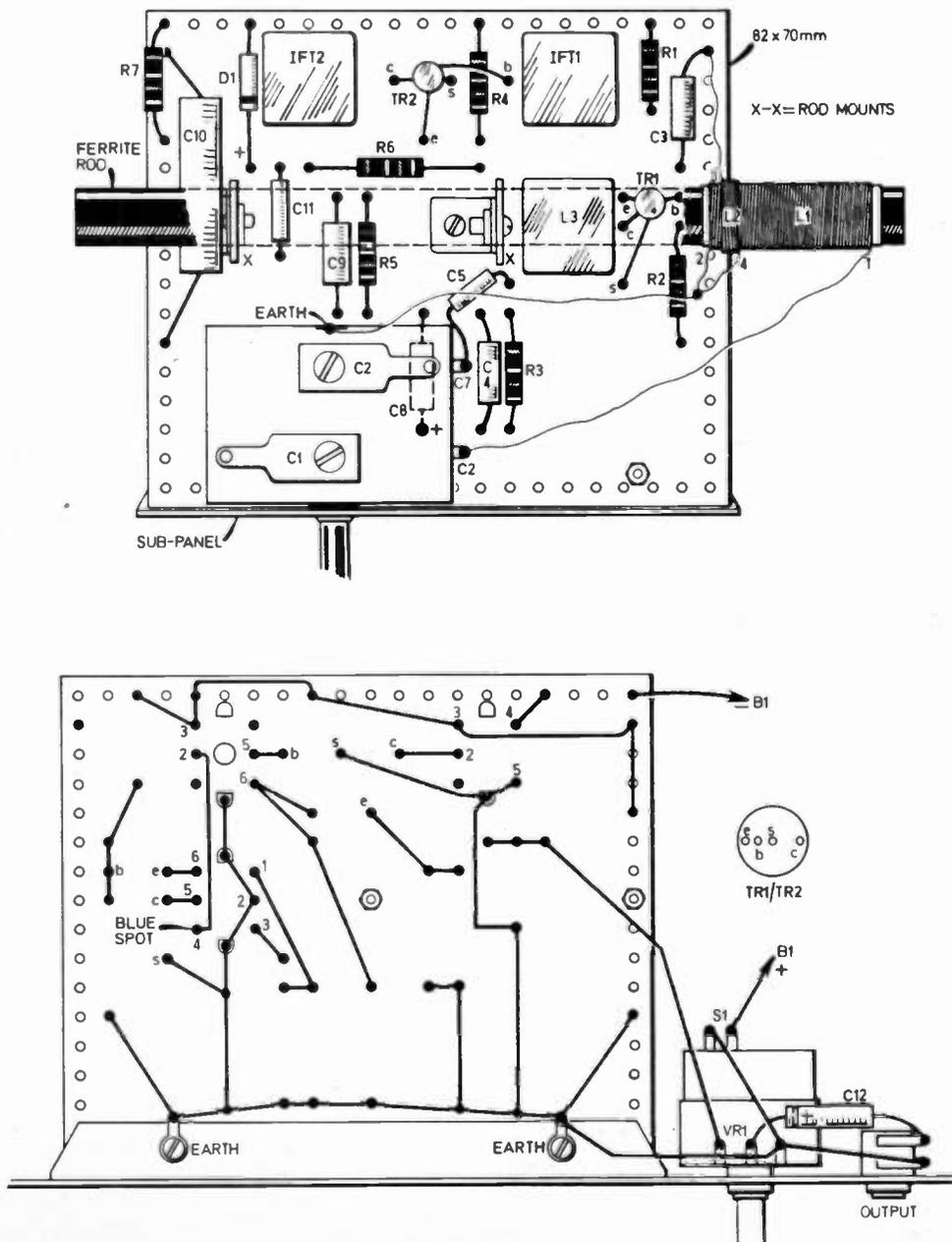


Fig. 2. Complete wiring up and layout details on both sides of the component panel and case front panel.

voltage and optimum adjustment of circuits, and small changes are more easily seen than heard with phones or an amplifier. However, if adjustments are made by ear, check them with a very weak signal tuned in.

Once the IFT cores are peaked for best results, they should be left as they are and they need no further adjustment.

It is now necessary to align L1 and L3 so that they track suitably throughout the tuning range. This is done by adjusting C1 for best results near the high frequency end of the band (C2/C7 nearly fully open) and by adjusting the position of L1 on the rod near the low frequency end of the band (C2/C7 nearly closed).

Tune in a signal near the high frequency end, and rotate C1 with a screwdriver, for best volume (or minimum reading on the meter). Then find a signal near the low frequency end of the band, and slide L1 along the rod, to peak up the signal. As adjustments influence each other, return to the h.f. end of the band, to check C1, then to the l.f. end of the band, to check the position of L1. Continue until no further improvement can be obtained.

BAND COVERAGE

If it is necessary to adjust the coverage of the band, this is done by adjusting C6 and the core of L3. With C2/C7 fully closed, the dial reading should be that of the maximum clockwise mark. A BBC or other known frequency can then be tuned in, and the core of L3 can be adjusted until the actual dial reading agrees with that of the station received. For adjustment of L3 core, the station should be near the l.f. end of the band.

A signal can then be tuned in near the h.f. end of the band, and C6 can be adjusted to secure good agreement with the frequency shown on the dial. Repeat h.f. and l.f. band end adjustments (e.g., C6 and L3) a few times. After this, tuning should agree closely with the dial. It is necessary to touch up the positions of C1 and L1, as mentioned earlier, after adjusting C6 and L3.

If a superhet circuit has not been made before, this may seem rather complicated. However, the procedure, which was given in detail, is easily summarised and carried through:

- (1) Adjust all IFT cores for best results.
- (2) If necessary, adjust C6 at the h.f. end of the band, and L3 at the l.f. end of the band, to secure suitable tuning coverage.
- (3) Adjust C1 near the h.f. end of the band, and L1 near the l.f. end of the band, for best reception.

LONG WAVES

In some areas in particular, l.w. reception is very useful. The circuit is adapted for m.w./l.w. reception by adding a l.w. coil to the rod, with wavechange switch, and an additional trimmer and parallel fixed capacitor.

The details for this modification are shown in Fig. 3; L4 is the long wave section on the ferrite

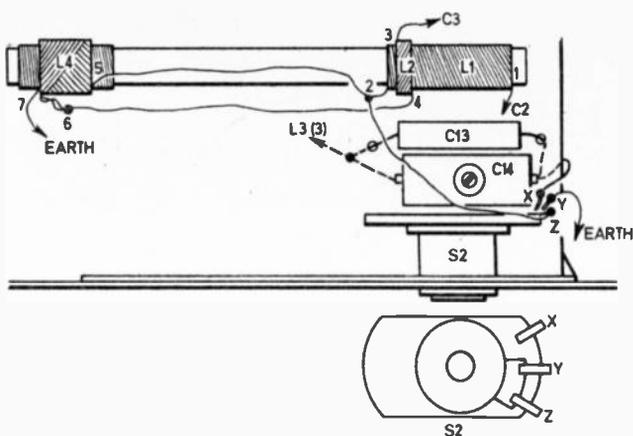


Fig. 3. Modification to the construction to enable long wave reception.

rod. When the bandswitch S2 is in the medium wave position, L4 is shorted out, and m.w. tuning is obtained as originally. When the switch is moved for long wave reception, L4 is in series with L1, so that the ferrite aerial covers long waves. In addition, C13 and C14 are introduced across L3, so that the oscillator coil coverage is suitably changed.

Fit S2 to the right of the tuning capacitor. Disconnect 2 of L1 from earth, and join it to the beginning of L4, wiring both to the new switch as in Fig. 3. Also disconnect 4 of L2 from earth, and take this to the tapping 6 on L4. Wire the end 7 of L4 to earth.

Drill the board to clear the tags and centre screw of C14, and place this and C13 as in Fig. 3. Wire to X on the switch, and pin 3 of L3, as shown. Wire Y of the switch to earth at one of the tags underneath the board. All other connections remain as before.

After this change, a little re-adjustment of m.w. alignment and trimming will be required, due to stray capacitance in the switch and new wiring, etc. Do this with the switch at m.w. Only when this is done switch to l.w. and with the dial set at 200kHz adjust C14 and the position of L4 on the rod for best reception. If L4 has no definite position, take it off and turn it over (to bring its windings into the same "sense" as those of L1). Subsequently, L4 may be moved on the rod for best reception at the l.f. end of this band.

CASE

The case used is fully insulated, and it should be noted that a metal case cannot be used. The battery rests to the left of the circuit board, and four screws secure the panel.

Provided component values in the tuned circuits are as given, with the components listed, the tuning dial in Fig. 4 may be fixed to the front of the panel. The whole panel can be covered with transparent material as used for book covers, to protect the paper scale.

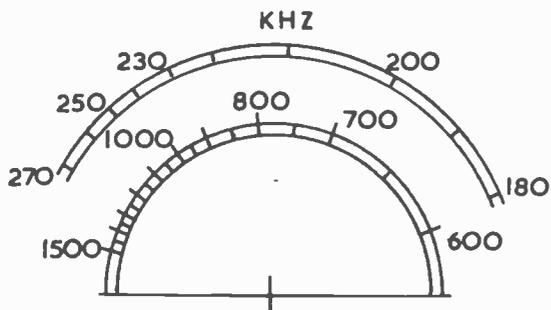


Fig. 4. The tuning dial, drawn actual size, as used on the prototype.

MW OSCILLATION

Due to the high gain of TR1, it may be found that oscillation and continuous whistles arise at the *extreme* high frequency end of the medium wave band (that is, with C2/C7 nearly fully open). This depends on the actual transistor fitted for TR1, and on the exact adjustments of C1 and C6, which limit the highest frequency which can be tuned. This defect is easily corrected either by removing a turn or two from L2, or by placing a resistor between C3 and 3 of L2. A suitable value is 470 ohms, but the value only need be high enough to prevent oscillation, and may well not be required in any case. □



Danger!

Neither Mr. Hartley nor yourselves appear to be aware of the danger presented by the *Bright Ideas* article in the October edition of EVERYDAY ELECTRONICS.

I strongly urge readers not to use benzene for the cleaning of printed circuit boards, or for any other purpose during which it is allowed to come into contact with skin.

This chemical is believed carcinogenic; i.e., it could cause cancer. It is absorbed through the skin and its effects may take years to become apparent. However, it usually only induces cancer after many occasions of contact with it; its effects are cumulative and only

build up during regular contact. However, the precise amount that could be dangerous is unknown as it varies from person to person.

There must be many safe organic solvents available that would do the job equally well (has anyone tried surgical spirit—available at chemists' shops?) So it does not seem worth the risk in using benzene.

G. L. Manning,
Edgware.

Nuts!

Could you please tell me how the distances between frets on a guitar, such as the *Delta Guitar* described in the October issue of E.E., are worked out. Could you also please tell me why the O fret on the *Delta Guitar* is so near the nut. Normally with a guitar the nut would be in the same position as the O fret on the *Delta*, and the first fret would be approximately in the same position as the first fret on the *Delta*. Does this mean that for some reason the strings rest on the fret in the *Delta* guitar and if so why not put the nut at the O fret position?

P. J. Arden,
Sheffield.

You readers are hard to please! When, with the Beta guitar (November '72), we used the nut as the O fret as suggested, we got letters asking why no separate fret was used—now you want it as before! In fact both methods are used on commercial guitars. With no O fret, the nut would have to perform two functions (1) a guide for the strings and (2) to keep all the strings at a set distance above the fingerboard. This means it would have to be precision made. The O fret on the

Delta Guitar keeps all the strings at the same distance above the fingerboard and other frets. Therefore the guide cuts on the nut can be made to any depth below the O fret height.

To work out the distances between the frets, a very good approximation (to within carpenters accuracy) is to divide by 18 the distance between nut and bridge to give first fret dimension from nut. For next fret, divide by 18 distance from first fret to bridge. This process is repeated for number of frets required.

Wiper Control

I've just completed and installed the *Windscreen Wiper Controller* by Eric Moore in November EVERYDAY ELECTRONICS. I tested the device prior to installation actually using a .12 volt car battery. As a result I have had to modify the circuit by using a 500 kilohm in place of 1 megohm for VR1. Also I increased C1 to 220 microfarad. This gave a delay of from normal to about 45 seconds.

A most peculiar and inexplicable phenomenon has occurred since installation. At very short delay setting the relay actually latches onto the frequency of the normal wiper speed. There is then no delay obtainable between normal and about 10 seconds, i.e. you can't get a five second delay for example.

One would have thought that there could be no connection at all between the timing of the NE 555 and the normal frequency of the wipers as there is no electrical connection—only mechanical via the relay. I have very carefully checked the wiring of the relay

and the rest of the circuit. Nevertheless, it is impossible to obtain a brief (i.e. under 10 secs delay) as any setting below 10 secs "latches on" to the normal frequency of the wipers.

Do you have any thoughts on the matter?

B. R. Sanders,
Cheadle Hulme.

We suspect that a small voltage pulse caused by the wiper motor turning off is triggering the sensitive i.c. Try putting a 220 ohm resistor in the supply line to the i.c. and potentiometers and a 100 microfarad 25V electrolytic capacitor across the i.c. supply.

Voltage Flow!

Reference school boy howler, "How many volts will pass through a relay coil?" (*Electronics At School* Oct. '74). I thought you might be interested in the following quotes from recent newspapers.

"The new class 87 engines (railway) operate on 25,000 volts of current."

"Somehow he slipped (off a pylon). His hand clawed through empty air and instinctively clutched the nearest object—a live cable with 33,000 volts of electricity flowing through it."

Perhaps the pupil left school to become a journalist?

Terence Davey,
Stoke on Trent.

Repeats?

First of all, having recently started getting EVERYDAY ELECTRONICS, I must say how I enjoy it—very suitable for a beginner in electronics like myself. However I would like to make a suggestion.

Over the last few years E.E. must have printed many very good projects and there must be many people like myself who have only recently started subscribing to E.E. How about reprinting some of the more popular projects you have printed in the past, I'm sure this would be appreciated by a lot of your readers.

J. P. Cross,
Frailingham,
Suffolk.

It is not our policy to reprint articles, however we have repeated various projects employing different or updated circuitry and

over the years will continue to do this.

Simple Sums?

You really have some nit-pickers! In fact Adrian Hope does himself an injustice since the expression $11-2+4\times 2$ is not a well formed formula of arithmetic any more than $+ - 3$ is. This being so he is entitled to mean by it just what he likes and what this in the context makes clear.

Your readers may be amused to learn that the Polish notion was originated by one Lesniewski (less-nee-eff-ski) in Warsaw before the last war. It is an alternative way of writing logical formulae, the other one being Bertrand Russell's (Russellian or Russellese).

Formulae like CCCKpqrst appear where the big letters are logical operations and the little ones sentences. Thus, save us, we get: If if if both p and q then r then s then t. Reverse Polish (I guess) puts numbers before the arithmetical operations. Then the true "reverse polish" for $(11-2+4)\times 2$ should be 2, 4, 2, 11, -, +, \times .

Lesniewski had some followers: Lukasiewicz, Sobocinski, and my old teacher Lejewski. But for those with shorter names it is all toomuchski.

P. Moll,
Department of Philosophy,
University of Lancaster.

On the subject of calculators, *For Your Entertainment* (September 1974), and taking the example given $11-2+4\times 2$, the answer (26) is correct for full flow arithmetic which discounts bracketing rules. Taking each operation in turn the operation $\times 2$ might not have yet occurred. Thus the calculation as your critics would have it would appear as $11-2+(4\times ?)$, not very solvable if one does the brackets first.

Further a calculation involving sum of the products e.g. $(2\times 3)+(4\times 5)+(6\times 7)$ would need partial results to be written down then added.

To solve this on a calculator using full flow one would use the expression:

$$2\times 3-4+5\times 4-6+7\times 6.$$

If the usual brackets were included it would make nonsense.

I hope this clears up some doubts on full flow compared with conventional arithmetic, both of

which can be done on a calculator. It depends what you want.

A. M. Coppin,
Feltham, Middlesex.

It must now be much more clear to someone! See For Your Entertainment for more on this subject.

Stereo Noise!

With reference to the *Tape Noise Limiter* in your November issue. Would you advise me whether it is possible to use this with a stereo cassette deck, e.g. by using two tape noise limiters one for each channel, and where in my system would I fit it—between the cassette deck and amplifier?

K. Kirk,
Welwyn Garden City.

Two noise limiters can be used for stereo and fitted as you surmise, between the deck pre-amplifiers and the power amplifier.

Soldering

Your article *Soldering For Beginners* recommends a conventional electric soldering iron, but I understand that whether or not such irons are earthed is important when soldering transistors or i.c.s which can be destroyed by voltage at the bit.

I, and probably many other beginners, would appreciate any available information on the effects of earthed or unearthed electric irons whether we need one of each and if so, when and how to use them on transistors or i.c.s.

S. Coward,
Durham.


It is normal not to earth a soldering iron so that "live" circuitry can be soldered without shorting (only do this on low voltage circuits). However when soldering to m.o.s. (metal oxide semiconductor) devices—some i.c.s. and mosfets etc.—it is best to unplug the iron and earth the contact of the device. Most i.c.s and semiconductors can be soldered with an unearthed iron in the normal way.

Please note: We cannot undertake to answer readers' letters that do not concern published articles and not enclosing an s.a.e.

Everyday Electronics, January 1975

The Extra-ordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett

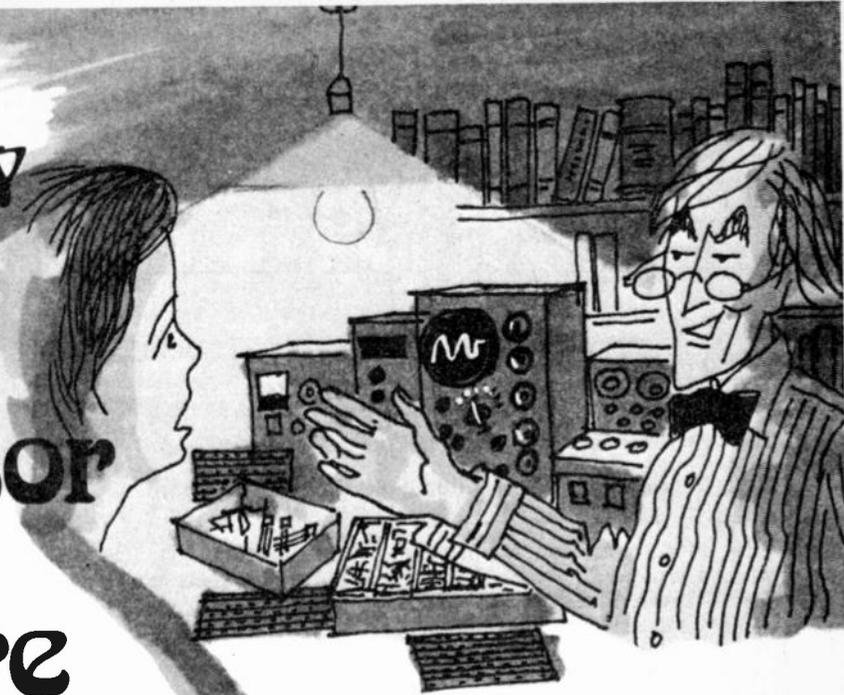

Professor Ernest Eversure, or the Prof. as his friends call him, has been experimenting in electronics for more years than anyone can remember and we thought that you might like to hear of, and perhaps repeat, some of his extraordinary experiments. Anthony J. Bassett recounts some of the experiments every month so why not follow the Prof's work and learn along with young Bob, his friend.

PROFESSOR Ernest Eversure appeared quite calm and collected. He pursed his lips and emitted a series of clicks and whistles. The robot immediately appeared, approaching one of the control-panels at the other side of the laboratory. It made some adjustments to the controls, and the alarm signal immediately ceased.

"What a relief!" sighed Bob.

"We can leave the robot to take care of that experiment," remarked the Prof., "While we get on with the musical note-selector for your oscillator."

The Prof. began to draw a number of diagrams. The first was a sketch of one of the experimental resistors described in last month's issue.

"Now," said the Prof., "If we wish to connect a number of these resistors together in series, it could be done like this—"

He drew a diagram of a longer piece of Paxolin with several nuts, bolts and solder tags joined by graphite lines (Fig. 1).

"Another method would be to use a piece of printed circuit-board, copper clad plastic or fibre-


glass sheet. If you remove some of the copper, either with a craft knife and tweezers, or by etching, to produce a pattern like this (Fig. 2), it is quite easy to put either short or long carbon tracks on the board, between the remaining pieces of copper, to produce either low-value or high-value resistors. Connections can easily be made to each resistor by solder-

ing wires to the copper."

"These wires could be connected to microswitches or contacts placed under keys from an old piano or wind-organ!" remarked Bob, "Or even built into an accordion!"

"If it were built into an accordion," the Prof. observed shrewdly, "When the accordionist played a chord, the top note of the chord would be generated electronically. It would automatically accompany the chord! I have been told about an instrument like this, which was built by an electronics experimenter, and had a separate oscillator for bass notes!"

Fig. 1. The Prof's basic resistors joined up in series.

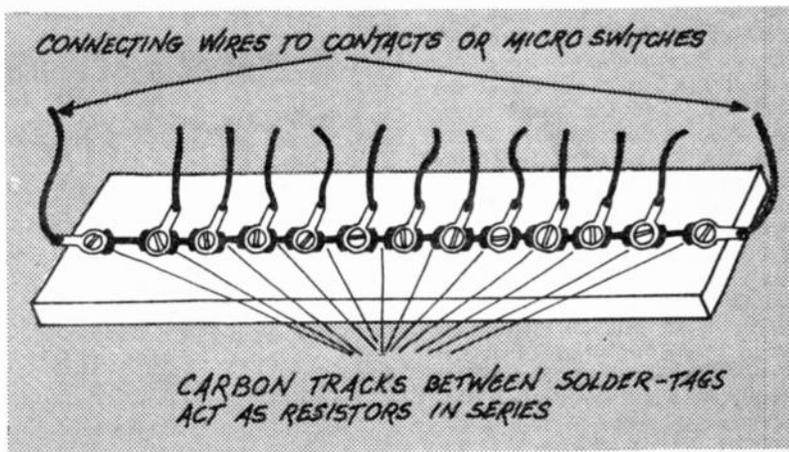

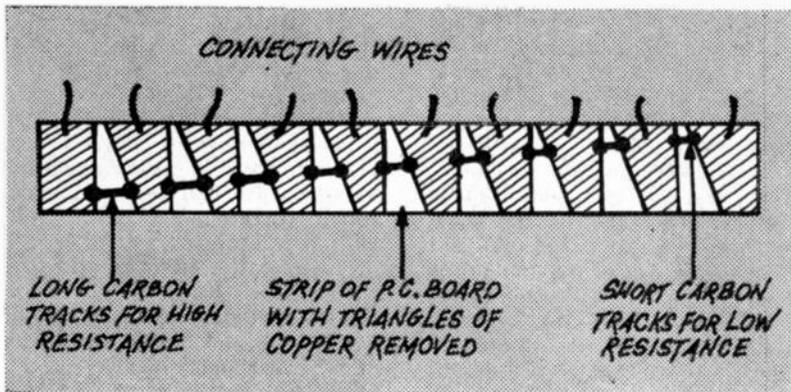


Fig. 2. The resistors formed on a printed circuit board.

The Prof. continued to draw, and soon produced another sketch which is shown in Fig. 3.

"Here is a design we could use to fit the tuning resistors and also copper 'keys', all on one printed circuit board," he said, "and notes can be played by touching the 'keys' with a metal rod connected by a piece of wire to the note generator."

"This board can be made by standard printed-circuit techniques, or by removing the unwanted copper with a craft knife and tweezers."

Assisted by the Prof., young Bob set to work busily, and soon he had made a printed circuit board to the Prof's design. He soldered a wire from it to the connection previously used to join VR1 to the emitter of TR2 in the oscillator.

Then he used a fine artist's paintbrush to apply a mixture of fine graphite powder and thin, quick-drying varnish between the copper sections at the places shown in the diagram. Near the right hand end of the board, used for high notes, he applied the mixture where the copper sections approached closest, to give low-value resistors.

Near the left hand end of the keyboard, used for lower notes, Bob applied the mixture where the copper sections did not approach so closely, to give higher value resistors. Then he put an extra quantity of the mixture on the board, to provide a graphite "pad" near the right-hand end of the note selector.

The note selector was now nearly ready for use; Bob left it for the varnish to dry, and looked around for a suitable keyboard instrument to assist in tuning the selector. He could have tuned it

to a piano, an organ, accordion, or a guitar. But there appeared to be nothing suitable.

"Prof.," he queried, "Is your sound-synthesizer keyboard ready for use yet? The note-selector is nearly ready for tuning, and I will need a reference instrument to tune it to."

"No," replied the Prof., "It is not finished yet. But robots can do almost anything."

He summoned the robot, which came and stood near to the workbench on which were Bob's note selector and oscillator.

"You will need to tune the selector from the top note downwards," observed the Prof., "And I see that the first note you will require is an 'F'!"

Pursing his lips, he gave the robot some more instructions in a code of clicks and whistles. The

robot whistled back, a continuous musical note 'F'.

"Wow!" exclaimed Bob in amazement, "Now I'll have a robot-tuned note selector!"

Young Bob quickly connected up his oscillator and switched it on. He used a crocodile-clip to attach the other tuning wire from the oscillator to the top 'F' note on the selector. The printed resistor at the top end of the keyboard now replaced VR1 in the oscillator circuit, but the note produced was higher than that produced by the robot. Young Bob used a typist's eraser to remove a small quantity of the graphite mixture.


As he rubbed the resistor carefully, with the eraser, the note from the oscillator gradually became lower, until it was very nearly in tune with the 'F' note produced by the robot.

"Just a little bit more, and it'll be in tune," thought Bob.

But he rubbed just a little too much of the mixture away, and the note from his oscillator went below the note he was aiming for. Bob exchanged his eraser for a medium graphite pencil, and, by carefully rubbing the surface of the resistor with the tip of the pencil, gradually brought the pitch of the note exactly to 'F'!

Moving the crocodile clip on to the next note, which was 'E', Bob was amazed to find that the Robot automatically began to whistle an 'E' note! He quickly adjusted the next resistor so that an 'E' note

Fig. 3. The "keyboard" and "glissando strip" produced by Bob.

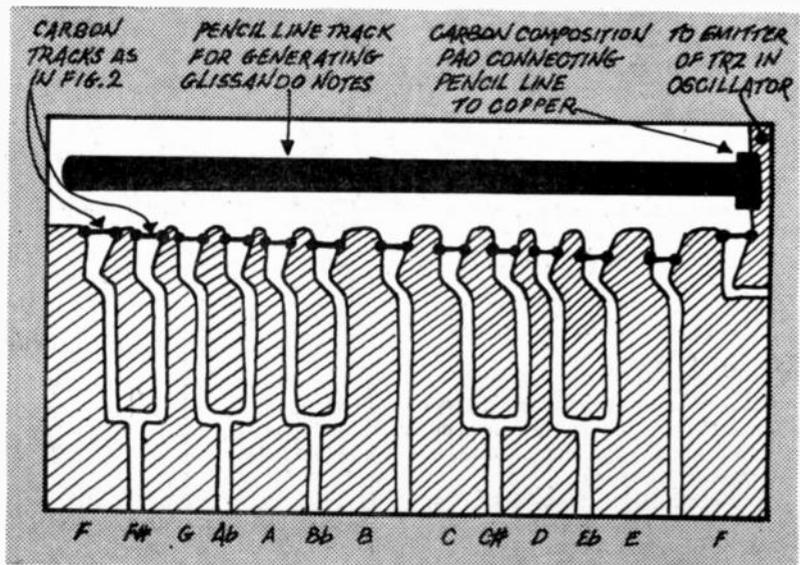

was produced by the oscillator, and went on to tune the remaining notes on the selector the same way, each with its own resistor.

Then he drew a thick black pencil line on the printed circuit board, joining up with the pad of graphite mixture at the right hand end of the keyboard. He went over the line several times with a soft graphite pencil until the line was about 10mm.

By sliding the crocodile clip connected to the oscillator along the line, Bob found that he could obtain interesting glissando sound-effects, whilst melodies could be obtained by touching the copper "keys" with the clip!

"Look Prof!" he exclaimed, "I've made a two-in-one instrument now! It doesn't just play notes like a keyboard instrument; it can be used to give sliding glissando effects as well!"

Whilst Bob demonstrated, Professor Eversure examined the instrument carefully.

"Now," he said, "I can think of quite a few improvements which we could make. First, if you continue to use that crocodile-clip on your pencil-line track, it will quickly scratch the track away. I suggest you replace it with a spare multimeter probe. Either round-off the end of the probe with a file and polish it perfectly

smooth, or solder a small shiny ball-bearing onto the end."

"Another improvement would be to carefully trim the pencil-line track so that points along the track each correspond with the nearest note on the keyboard. That way, you will know that if you put the probe on the track near the 'A' note, an 'A' will sound, and if you put the probe near 'C', a 'C' will sound, yet you will be able to slide the probe gradually from one note to another, and the pitch will gradually alter!"

"Just as you tuned the 'keyboard' part of the selector by starting with the top notes, so it will be necessary to trim the pencil-line track by starting at the high end."

The Prof. found a meter-probe with a worn, rounded end, and connected it in place of the crocodile clip. Then he compared the note obtained by touching the upper 'F' note on the note selector, with that obtained by touching the centre of the pencil-line track nearest the same note. The note obtained from the pencil-line track was too low, so the Prof. used a soft graphite pencil to rub more graphite onto the paxolin near the 'F' note, and to the right of it, until the correct note was obtained.


He then continued down the scale, comparing the note produced on the track with the nearest note on the keyboard, and correcting them by using either a pencil to raise the pitch, or an eraser to lower it, until a smoothly varying track had been produced which corresponded quite well with the "keyboard" section.

"Now, Bob," said the Prof., "I think that's about as far as we can go for today, as it's becoming quite late, and there are some other experiments which I want to do. But I'm sure your friends from school will be very interested in your note selector, and would like to practise tunes and sound-effects on it. Why not take it and show them?"

"Thanks, Prof.," said Bob gratefully, "and if I come round again soon, will you have time to show me how I can make my own experimental microphones?"


"Yes," said the Prof., "and we have planned to try experimental gramophone pickups as well, so it should be quite an interesting session! "Bye Bob," he said as Bob carefully carried his oscillator and note selector towards the Laboratory exit.

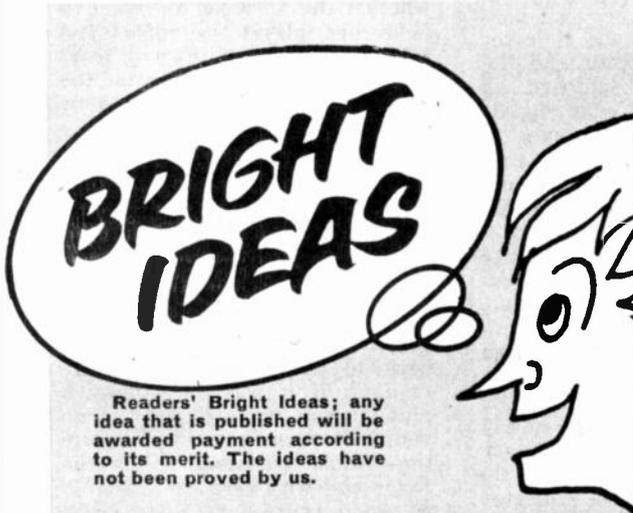"Bye, Prof; see you soon!" called Bob, setting off happily to show his note selector to some of his friends.



With reference to the *Delta Electric Guitar* featured in the October issue, I have found a very cheap and effective way of making a bridge. All one needs is an old chrome plated brass drawer handle, one only has to drill two holes in the body of the guitar.

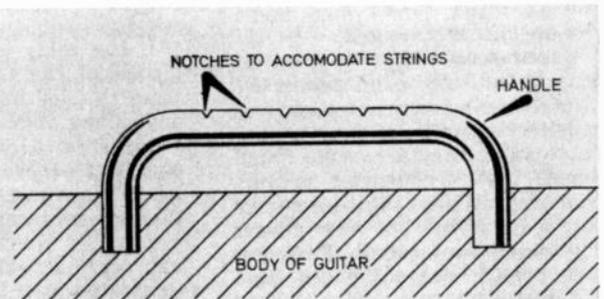The notches can be cut with a small hacksaw or a triangular file. The height of the bridge is semi-adjustable



in that one can drill the holes fairly deep and get them to the right depth by inserting small washers. This bridge will be held in by the tension of the strings.

A. T. Scaramanga,
Reading, Berks.

PRACTICAL ELECTRONICS

- ★ MARINE SPEEDOMETER
- ★ AC/DC MILLIVOLTMETER
- ★ PROBABILITY ANOMALY DETECTOR

Details in February issue, on sale
January 10



Capacitors

I am thoroughly confused by the different types of capacitors available — plastic foil, polystyrene etc. What are the differences and are they interchangeable?

The different names describe their construction and the type of insulator used for the dielectric. Some insulators are of good quality, others are not so good and can be "leaky" under high voltage stress and when radio frequencies are applied.

Polystyrene and silver mica devices show very good properties at high radio frequencies—and as they are usually of low capacitance value they are to be found where high frequencies prevail. You can usually substitute mica for polystyrene but not always the other way round. Polyester and polycarbonate devices have higher capacitance values as have paper capacitors and plastic foil.

Unless specifically stated with a good reason one can usually substitute one for another amongst this group but remember that paper capacitors (these are very good quality) are much more bulky than the others. In the capacitance range of 0.47 μ F to about 2.2 μ F you can always substitute polyester capacitors for electrolytics but not vice versa. NEVER use an electrolytic capacitor as a substitute for a non polarity sensitive device. This is particularly important if you ever think of using a polarity sensitive tantalum capacitor instead of a polyester device.

Transformer Identification

Is there any simple way of finding the values of transformers that are unmarked?

We appreciate that it is most frustrating to be in possession of an expensive looking unmarked transformer and one feels duty bound to use it rather than buy one having a more certain pedigree. Unfortunately there are many different types of transformer—mains, auto, coupling, output, etc., and they may have inductances to suit certain specific frequencies; e.g. transformers from aircraft—even though they may have voltage transformation markings on them they should not be used on the mains because they are designed to operate at 400Hz. Applying the correct voltages at 50Hz would cause them to overheat.

We feel we should dissuade readers from using transformers of dubious origin simply because of the safety angle and in any case the techniques for carrying out the requested tests can be extremely complex.

Back e.m.f.

In some of your circuits that use relays you show a diode connected across the relay's coil and say this is for "protection purposes". What is it protecting from what?

If the relay is in the collector circuit of the transistor and the transistor is being switched on and off by very fast edge signals—e.g. from a Schmitt trigger or such like—there is a danger that when the transistor goes non-conducting very rapidly (the relay's current is quickly broken) you can get a very high voltage generated as a back e.m.f. across the relay coil—caused by inductive action.

The polarity of this voltage tends to make the potential at the collector of the transistor go very much higher than the supply rail voltage and there is a danger of exceeding the reverse breakdown voltage between collector and base. The diode catches this "over swing" and shorts any voltage straight back to the power rail.

Microwaves

Is there any way I can check if there is any escape of microwaves from a microwave oven. Also are microwaves harmful?

We do not know of any sure way of checking your oven for leakage but would think that holding a small neon tester close to the unit should give some indication. If the neon lights up when held close to (but NOT in contact with) the oven there is certainly an escape of microwave energy. If, however it does not light up we cannot say for sure that there is no escape, but if there is it is unlikely to be harmful.

Under certain circumstances high energy microwaves are extremely harmful—otherwise the meat would not cook in the oven—but it is unlikely that there is any hazard external to a commercial oven as they are heavily screened. Fine steel wool is an excellent absorber of stray microwaves but we do not recommend you stuff this into any potential gaps in the casing of your oven!

If you are particularly concerned over this point we suggest you contact the manufacturers who, we are sure, would be only too pleased to advise you and set your mind at rest.

Hum

I have purchased a commercial v.h.f. tuner unit but when connected up and switched on it emits a hum irrespective of whether the amplifier is switched to record player or radio. The hum does not seem to come from my loudspeaker but from the tuner itself.

Is there any possible reason for this? I have had the electricity board along to check the house wiring for interference but they found nothing wrong.



More than likely the hum is caused by the laminations of the mains transformer inside the tuner unit. This is most aggravating and should really be referred back to the manufacturer—particularly if it was an expensive unit. If you want to have a go yourself we suggest you locate the mains transformer in the tuner and with care use a length of wood pressed to your ear—the other end touching the metalwork of the transformer. If you hear a pronounced hum then you have confirmed our guess.

The only thing you can do is tighten up any mechanical fixing screws and squeeze the laminations clamp together with a Mole Wrench if the transformer is of the open lamination type.

look! electronics really mastered

... practical
... visual
... exciting!

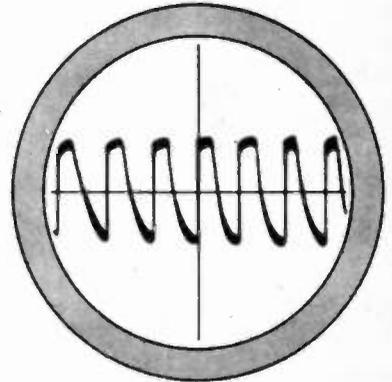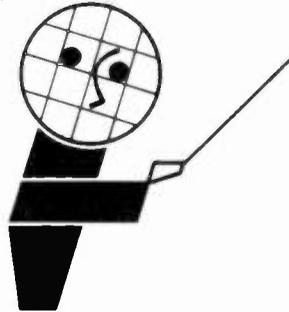no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

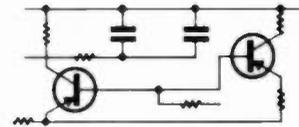2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To: BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. EEL 15,
P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives


NAME

BLOCK CAPS

ADDRESS

PLEASE

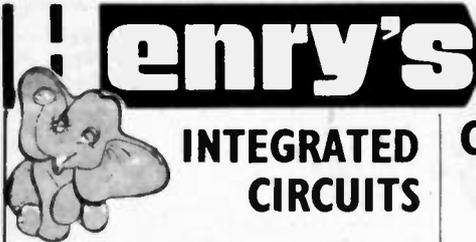special free gift also to all our students



**UK'S LARGEST RANGE OF TRANSISTORS, IC'S
RECTIFIERS, ALL SEMICONDUCTOR DEVICES**
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL

**INTEGRATED
CIRCUITS**

EXTRA DISCOUNTS

Semi-conductors
Any one type or mixed
SN 74 Series 'IC'
12 EXTRA 10%
25 EXTRA 15%
100 EXTRA 20%



74 Series	£ p	SN7485N	£ p	SN74191N	£ p
SN7400N	0-16	SN7486N	0-67	SN74192N	2-00
SN7401N	0-16	SN7489N	3-87	SN74193N	2-00
SN7403N	0-16	SN7490N	0-55	SN74194N	1-30
SN7404N	0-16	SN7491AN	0-00	SN74195N	1-10
SN7405N	0-16	SN7492N	0-70	SN74196N	1-20
SN7406N	0-42	SN7493N	0-70	SN74197N	1-20
SN7407N	0-42	SN7494N	0-80	SN74198N	2-77
SN7408N	0-28	SN7495N	0-80	SN74199N	2-52
SN7409N	0-28	SN7496N	0-95	Linear	
SN7410N	0-16	SN7497N	1-87	RCA	
SN7411N	0-25	SN74100N	1-89	CA3012	1-32
SN7412N	0-30	SN74104N	0-58	CA3014	1-80
SN7413N	0-36	SN74105N	0-53	CA3018	1-02
SN7414N	0-36	SN74110N	0-45	CA3019	1-13
SN7416N	0-36	SN74111N	0-88	CA3020	1-80
SN7417N	0-16	SN74116N	1-89	CA3022	1-93
SN7420N	0-16	SN74118N	0-90	CA3028A	1-03
SN7421N	0-33	SN74118N	0-99	CA3036	1-08
SN7422N	0-25	SN74119N	0-68	CA3046	1-03
SN7423N	0-37	SN74120N	0-95	CA3048	2-78
SN7425N	0-37	SN74121N	0-70	CA3075	1-73
SN7426N	0-32	SN74122N	0-70	CA3081	1-80
SN7427N	0-37	SN74123N	1-00	CA3089E	2-94
SN7428N	0-40	SN74125N	0-65	CA3090Q	5-40
SN7430N	0-16	SN74132N	0-72	Signetics	
SN7432N	0-37	SN74141N	0-20	NE555	0-85
SN7433N	0-37	SN74145N	1-28	NE560B	5-00
SN7437N	0-37	SN74150N	1-35	NE561B	5-00
SN7438N	0-37	SN74151N	1-00	NE562B	5-00
SN7440N	0-22	SN74153N	0-95	NE567B	3-50
SN7441AN	0-92	SN74154N	2-00	Motorola	
SN7442N	0-79	SN74155N	1-00	MCI1301	1-42
SN7443N	1-20	SN74156N	1-00	MCI1304P	1-79
SN7444N	1-27	SN74157N	0-95	MCI1310P	2-91
SN7445N	1-60	SN74160N	1-38	MCI458CP	0-77
SN7446N	1-35	SN74161N	1-38	MCI1710CCO	8-00
SN7447AN	1-60	SN74162N	1-38	MFC4000P	0-46
SN7448N	1-27	SN74163N	1-38	MFC4010P	0-56
SN7450N	0-16	SN74164N	1-76	MFC6040P	1-00
SN7451N	0-16	SN74165N	1-76	Others	
SN7453N	0-16	SN74166N	1-60	TEA800	1-50
SN7454N	0-16	SN74167N	0-30	SN76003N	1-50
SN7460N	0-16	SN74170N	2-52	SN72741P	0-60
SN7470N	0-38	SN74173N	1-66	SN72748P	0-81
SN7472N	0-38	SN74174N	1-57	702C	0-75
SN7473N	0-41	SN74175N	1-10	709P	0-39
SN7474N	0-42	SN74176N	1-26	723C	0-90
SN7475N	0-59	SN74177N	1-26	728C	0-46
SN7476N	0-45	SN74180N	1-26	741C	0-50
SN7480N	0-60	SN74181N	3-95	747C	1-10
SN7481N	1-10	SN74182N	1-26	748C	0-61
SN7482N	0-87	SN74184N	1-80	LM309K	2-00
SN7483N	1-10	SN74185N	1-80	TAA960	1-75
SN7484N	1-00	SN74190N	2-00		

**COSMOS INTEGRATED
CIRCUITS — FULL
RANGE IN STOCK**

AAZ13	£ p	BLY36	£ p	TIP42A	£ p
AC107	0-31	B5X20	0-13	TIS43	0-26
AC128	0-15	BUI05	2-20	V405A	0-22
AC187	0-21	BY100	0-27	ZTX108	0-08
ACY17	0-40	BY127	0-12	ZTX300	0-13
ACY39	0-78	BY233	0-42	ZTX302	0-18
AD149	0-58	C106D	0-54	ZTX500	0-13
AD161	0-44	GET111	0-72	2N697	0-16
AD162	0-44	GET115	0-90	2N706	0-12
AF117	0-24	GET880	0-60	2N930	0-18
AF118	0-57	LN109K	2-00	2N987	0-42
AF139	0-41	MAT121	0-25	2N1132	0-24
AF186	0-48	MIE340	0-47	2N1304	0-28
AF239	0-44	MIE520	0-63	2N1613	0-21
AS27	0-33	MIE3055	0-77	2N1671	1-20
BA115	0-10	MIE2955	1-27	2N2147	0-78
BAX10	0-05	MPI105	0-26	2N2160	0-78
BC107	0-14	NK17404	0-26	2N2166	0-12
BC108	0-13	OAS1	0-72	2N3053	0-18
BC109	0-14	OAS1	0-18	2N3054	0-48
BC109C	0-16	OA200	0-08	2N3055	0-45
BC113	0-15	OA202	0-06	2N3440	0-58
BC147	0-10	OC28	0-66	2N3442	1-39
BC148	0-08	OC34	0-60	2N3525	0-91
BC149	0-10	OC35	0-60	2N3614	0-65
BC169C	0-15	OC44	0-20	2N3702	0-11
BC182	0-12	OC45	0-20	2N3714	1-41
BCY32	0-85	OC71	0-18	2N3771	1-77
BCY39	1-50	OC72	0-28	2N3773	2-40
BCY55	2-64	OC77	0-34	2N3790	2-10
BCY70	0-18	OC81	0-25	2N3819	0-38
BCY71	0-22	OC83	0-27	2N3886	0-72
BCY72	0-12	OC140	1-14	2N3903	0-14
BD124	0-65	OC170	0-30	2N4002	0-15
BD131	0-42	OC200	0-54	2N4126	0-15
BF115	0-20	OC202	0-90	2N4871	0-34
BF180	0-36	OC271	1-20	2N4557	0-30
BF194	0-10	ORP12	0-60	25303	0-60
BFX13	0-26	ORP60	0-55	40550	0-54
BFX34	0-70	P346A	0-18	40361	0-45
BFX88	0-24	LT209	0-20	40362	0-40
BFX50	0-21	TIP29A	0-49	40408	0-80
BFX51	0-20	TIP30A	0-37	40486	0-55
BFX64	0-36	TIP11A	0-41	40636	1-00
BFX90	0-31	TIP41A	0-74	40430	0-85

**TEST
EQUIPMENT
MULTI-
METERS**



(carr./packing 35p)
U4324, 20kV with case £9-25
U435, 20kV with steel case £8-75
U4313, 20kV with steel case £12-50
U4317, 20kV with case £16-50
U4341, 33kV + transistor tester steel case £10-50
U4323, 20kV plus 1KHZ OSC with case £7-70
ITI-2, 20kV/slim type £5-90
THL33D (L33DX) 2kV Robust £7-50
TP53N, 20kV (Case £2-00) £8-25
TP105 2kV £6-25
TW205 20kV £10-20
TW50K 50kV £11-25
EPI0KN 10kV £9-95
AF105 50kV Deluxe (case £1-90) £12-50
5100TR 100kV Plus trans. tester £22-50

GENERAL TEST EQUIPMENT

(† carr./pack 50p. *c/p 30p unless stated)
New Revolutionary Supertracer 680R
680R Multi-tester £18-50
Accessories
Transistor tester £11-00
Electronic volt. £18-00
Amplamp £11-95
Temp. probe £11-95
Gauss meter £11-95
Signal injector £5-95
Phase Sequence £5-95
EHT Probe £5-95
Shunts 25/50/10A £4-50
†1300 IMA Stripchart recorder £44-00
†TE40 AC Multi voltmeter £19-75
†TE15 Grid dip meter 400KHZ-28MHz £19-95
†TE65 2B Range valve voltmeter £22-50
†TK20D RF Generator 120-KHZ 500MHz £18-95
†TK22D AF Gen 20HZ-200KHZ £19-95
*HM350 In circuit transistor tester £19-50
*C3025 Deluxe meter 1-300 MHz £6-95
*TI145 Compact transistor tester £14-75
†G3-36 R/C osc. 20HZ-200KHZ £19-75
*C3042 SWR Meter £5-75
*SE350A Deluxe signal tracer £12-95
*SE400 Mini-lab all in one tester £15-50
C1-5 Scope 500,000KHZ (carr. £1) £43-00
*C30435 CH F/A meter 1-300MHz £5-75
Resistance sub box + Post. etc. £12-40
Capacitor £2-10
2 amp var. transformers (carr. £1) £6-55
Radio activity counter 0-10 (carr. £1) £9-97

Mains unit for above (carr. 50p) £3-75

PA-DISCO-LIGHTING Equipment



Without doubt UK's best range of modular and complete equipment, Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc. FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF AT HENRY'S DISCO CENTRE 309 EDGWARE ROAD 01-723 6963.

QUALITY CASSETTE TAPES

"Living Sound" made specially for Henry's by EMI Tapes Ltd.
S crew type with library case Post paid (GB)
C60 3 for £10 6 for £20 10 for £25 for £40
C90 £1-47 £2-83 £4-65 £11-37
C120 £1-83 £3-54 £5-60 £14-00

**8% VAT TO BE ADDED
TO ALL ORDERS
(EXPORT VAT FREE)**

ELECTRONIC COMPONENTS

Strobe Tubes
ZFTA (similar to 4A) £4-00
ZFT12A £5-00.
7 segment indicators 3015F with data £1-70 ea
Spring delay units
Ultrasonic transducers with data/circuits £5-90 pr

Ceramic Filters
Miniature 10-7 MHz filters 40p pair.
ZN414 Radio IC with circuit £1-20

SPECIAL OFFER CASSETTE STORAGE


Rotating unit up to 32 cassettes stackable £3-60 pp 15p
Car unit with bracket for 10 cassettes £2-80 pp 10p

ELECTRONIC COMPONENTS & EQUIPMENT

More selection — bigger stocks of electronic components and equipment for supply purpose. Let us quote for your requirements.
(Please enclose large SAE with all enquiries).

**BRIDGE SILICON
RECTIFIERS**

£ Amp	£ p	£ Amp	£ p
B025/025	0-14	B4/20	0-54
B025/05	0-16	B4/40	0-60
B1/05	0-20	B4/60	0-70
B1/20	0-24	B4/80	0-90
B1/60	0-23	B6/10	0-30
B1/100	0-30	B6/15	0-38
2 Amp	0-30	B6/20	0-58
B2/05	0-35	B6/40	0-68
B2/10	0-40	B6/60	0-75
B2/40	0-44	B6/60	0-88
B2/60	0-45	1 Amp Tubular	
B2/100	0-53	W005	0-27
4 Amp		W01	0-29
B4/05	0-45	W02	0-30
B4/10	0-48	W06	0-33

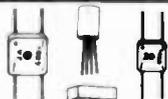

for your Entertainment...

By Adrian Hope

THE correspondence on calculator logic and the sum $11-2+4 \times 2$ is especially welcome because it neatly sums up what I see this column is all about—namely, electronics as the servant of man rather than vice versa. It also neatly reminds us that most computer mistakes (for instance in accounts and statements) are not machine mistakes at all, they are the fault of the machine operator.

Of course, using legitimate mathematics, the correct answer to the sum $11-2+4 \times 2$ is 17 and not 26, because multiplication and division take precedence over addition and subtraction.

Legitimately the answer 26 can only be arrived at by writing the sum as $(11-2+4) \times 2$. A chain flow logic calculator automatically puts the brackets into the sum to produce the answer 26.

If the operator (either through ignorance or by subconsciously regarding the brackets as implied) would move from left to right through the sum to produce the answer 26, then a chain flow calculator will follow his train of thought and produce the same answer. So the calculator becomes a simple human tool, neither introducing errors nor correcting those made by the operator.

This is why I suggest that a chain flow logic calculator is more likely to be of practical domestic use than a reverse logic machine. But of course those who prefer reverse logic machines are in luck, because, as previously pointed out, it is just these machines that are now going cheap.

SPOT CHECK

I did a spot check round a cross section of my friends and

Everyday Electronics, January 1975

acquaintances, see below, to see just how people working and earning their living with figures would work out the sum $11-2+4 \times 2$, in that form.

Every one of them obviously realised that the question must have a catch, because I was, after all, phoning them up one evening out of the blue and asking them to write out and solve a simple sum!

Housewife	26
BBC bandleader (paying musicians, handling VAT and tax)	26
Company secretary	26
Lecturer in Economics	26
Insurance Broker	26
Director of firm manufacturing and selling commercial vehicles (dealing in large quantities of money and crucial chassis and body measurements)	26
Professor of Physics	17
Schoolteacher	17
University Lecturer in Technology	26
Practising doctor	26
Architect	26
Book-keeper (handling the books of a large firm)	26
Pharmacist	26
University Lecturer in Maths	17
University Maths graduate ...	17
Ten-year-old child	21

(Yes, 21: he half knew what to do but ended up using the 4 twice)

I don't say this proves anything but I do say it is interesting. I also say it suggests that the average man and woman in the street would not only work out the sum incorrectly but also would write it incorrectly if they wanted the answer 26, i.e. it is natural for some educated people to move left-to-right through a sum and subconsciously add brackets.

Yes, I know this is wrong and

there are very good arguments for preserving correct form at all times. But there are also equally good arguments in favour of admitting an abuse into the language when it is more confusing to exclude it.

Take, for example, the word "sophisticated." Many of us use it to describe complicated or advanced circuitry and some modern dictionary definitions are beginning to acknowledge this—but try looking the word up in an older dictionary and you may have a surprise.

Also, try looking up the word "nearby". It is used almost daily by the BBC newsreaders as an adjective (eg. "nearby trees") and the modern Penguin dictionary lists it as such. But try looking in an older dictionary and if you can find it at all you are quite likely to see it listed as an adverb.

TALKING MACHINE

By the way—

If you want to feel you are one up on a computer, try fooling your pocket calculator by making it talk.

These machines all have digital read out figures, some of which happen to look like letters of the alphabet when viewed upside down. For instance 0=O, 1=1, 2=Z, 3=E, 4=h, 5=S, 7=L, 8=B and 9=G.

See how this works out in practice try punching in $1 \cdot 1601 \times 4 + 6$. Then turn the calculator round and read out the answer upside down.



"How come I'm always £1 short on my housekeeping since you got that calculator?"

DOWN TO EARTH

By GEORGE HYLTON

"I read that, in the circuit of Fig. 1, maximum output is obtained when R_b is h_{FE} times R_c . Is this true, and if so, why?"

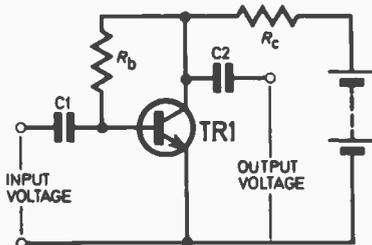


Fig. 1. A simple one-stage amplifier with feedback biasing.

Here we are concerned with voltages. The important ones are shown in Fig. 2. The output voltage is produced by changes in the collector current flowing in R_c , changes which are governed by the input signal, which we can take to be a small a.c. voltage applied to the base-emitter junction. Its effect is to impress small to-and-fro variations on the steady base-emitter voltage V_{be} .

The corresponding small variations in the collector current I_c produce corresponding changes in the voltage drop across R_c . These variations are the a.c. output voltage and they are taken out of the circuit, without upsetting the d.c. conditions, via a capacitor (C2 of Fig. 1).

PEAK SWING

If the input is an audio signal, made up of mixtures of sine waves, then on average it swings just as far positive as it does negative. For this reason V_{be} is made such that the circuit overloads at the same peak voltage, positive or negative. A peak positive swing then just increases the collector current to the point where R_c drops all the supply voltage V_{cc} .

Any further increase of input cannot increase the output because the transistor is turned on as hard as the circuit will allow; it is "bottomed"; i.e. its collector voltage is zero, or very nearly so.

A peak negative swing just cuts off the collector current; there is now no current in R_c and the collector voltage is the full supply voltage V_{cc} . Once again, no further increase is possible since the transistor is already cut off and the output at a maximum.

Common sense says that to allow equally large swings of collector voltage in either direction, the collector voltage V_{cc} should have a steady, d.c. value of half the supply voltage, V_{cc} . If V_{cc} is 12V d.c., and V_{ce} is 6V d.c., the peak a.c. output is 6V positive or 6V negative. The peak-to-peak a.c. output is 12V, the same as V_{cc} , and we can't do better than that. If the collector were sitting at 4V, the peak output would be only 4V in the negative direction before distortion set in.

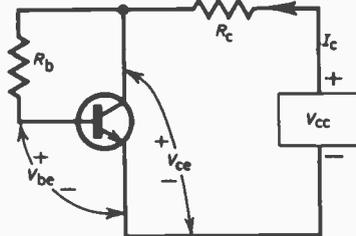


Fig. 2. D.C. conditions only for Fig. 1.

APPLICATION

So the problem is to set up the d.c. conditions so that V_{ce} is half V_{cc} . The rule for doing this is to make $R_b = h_{FE} \times R_c$. Here h_{FE} is what the data sheets call the "large-signal current gain". However, like most practical rules, it is only an approximation. It gives good results for high values of V_{ce} but not when V_{ce} is small.

First, why does the rule work, at all? Well, the form of biasing of the transistor shown here involves some d.c. negative feedback. When R_b passes current into the base, the collector current

which then flows pulls down the collector voltage. This leaves less voltage to drive base current through R_b , with the result that the circuit settles down with V_{ce} somewhere between 0 and V_{cc} .

The exact voltage depends on how much collector current flows for a particular base current, i.e. on the gain of the transistor. But, obviously, it depends also on the resistances in the circuit. It turns out that, approximately anyway, the collector voltage adjusts itself to half V_{cc} when $R_b = h_{FE} \times R_c$.

What prevents the rule from being completely accurate is that not all of the collector/emitter voltage is available for driving current through R_b . The voltage across R_b is not V_{cc} but V_{cc} minus V_{be} . In a silicon transistor V_{be} is around 0.7V, which makes quite a difference when V_{cc} is not very large, as in circuits worked from 3V batteries.

The value of h_{FE} used in calculating R_b should be the true large-signal current amplification factor for the particular transistor you are using at the particular collector current. Since transistors vary, even though nominally of the same type, and since h_{FE} varies with I_c , the only certain way to get the right R_b is by experiment. This can be tedious.

If the limits of h_{FE} for the transistor type are known, at the collector current to be used in your circuit, then an average value of R_b can be calculated which will be all right for an average transistor and, hopefully, not too far out for a non-average one. Thus if h_{FE} is 100-200 you can take it as 150 with good results.

Unfortunately some transistor types have a much greater "spread" than this 2:1 ratio. A type with $h_{FE} = 80-500$ will give less repeatable results. The best average value for h_{FE} is not the simple arithmetic mean which I just used but the "geometric mean", found by multiplying the upper and lower limits of h_{FE} together and then taking the square root. For the 100-200 transistor this gives 140 instead of the 150 I used, which hardly makes any difference. But in the 80-500 transistor the geometric mean h_{FE} of 200 is very different from the simple average of 290.

To allow for low V_{ce} , calculate R_b as before then multiply by

$$\left(\frac{1 - 2V_{be}}{V_{cc}} \right)$$

PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

- * 6 OR 12 VOLT
- * +VE AND - VE GROUND

Here's the new, improved version of the original Scorpio Electronic Ignition System - with a big plus over all the other kits - the Electro Spares Kit is designed for *both* positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car or motor cycle.

When your Scorpio Mk. 2 is installed, you instantly benefit from all these Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.
Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

PE FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

PE GEMINI STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES




The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE(B)
Tel: Sheffield (0742) 668888

With a kit as complete as this, all you need add is a little time.



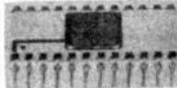You may have found, from past experience, that your definition of 'complete' is not quite the same as other people's. And your so called complete kit comes minus a cabinet, or knobs, or a multitude of other bits and pieces.



That won't happen with a Heathkit.

Take our very popular digital alarm clock kit. Every part you need will be there, right down to the solder. And you'll also receive a very easy to understand instruction manual that makes light work of assembly.

In fact all you need are a few basic tools and a few enjoyable hours of your time.

After which you may like to try your hand at our AR-1214 stereo receiver. Or even a TV.



And how about an ultrasonic burglar alarm disguised as a book?

Or, for a bookful of other ideas, just clip the coupon and we'll send you the Heathkit catalogue.

Otherwise call in and see us at the London Heathkit Centre, 233 Tottenham Court Road. Or at our showroom in Bristol Road, Gloucester.

You'll find it well worth your time.

Heath (Gloucester) Limited, Dept. EE-15.

Bristol Road, Gloucester, GL2 6EE.
Tel: Gloucester (0452) 29451.



To: Heath (Gloucester) Limited,
Dept. EE-15, Gloucester, GL2 6EE.
My free Heathkit catalogue, please.

Name _____
Address _____

Postcode _____

Remember easy terms are available
with the Heathkit Monthly Budget Plan.



CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM). 803 1685

ABS PLASTIC BOXES

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1006 - 109mm x 73mm x 45mm - 81p.
1006 - 180mm x 74mm x 47mm - 99p.
1007 - 158mm x 124mm x 60mm - 99p.
1021 - 106mm x 74mm x 45mm - 69p.
(sloping front)

CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 36mm hole for mounting.

ME6 - 0 to 50 micro amp Full Scale
ME7 - 0 to 100 micro amp " "
ME8 - 0 to 500 micro amp " "
ME9 - 0 to 1mA " "
ME10 - 0 to 5mA " "
ME11 - 0 to 10mA " "
ME12 - 0 to 50mA " "
ME13 - 0 to 100mA " "
ME14 - 0 to 500mA " "
ME15 - 0 to 1 amp " "
ME16 - 0 to 50 volts A.C. Full Scale
ME17 - 0 to 500 volts A.C. Full Scale
ME18 - "µg" Meter
ME19 - "VU" Meter

OUR PRICE
£3.00



LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control. Is suitable for 9V a.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. £2.00



LIGHT EMITTING DIODES

TL 209 (Red) with Clip 25p each
TL 208 (Green) with Clip 25p each
TL 209 (Yellow) with Clip 60p each
Mied 500 T092 Type ... 18p each

LED READOUTS

Litronix
DL707 - 3 Character 14 Pin DIL £3.00
DL701 As above but ±1 .. £3.00
DL747 - 8 Character .. £3.00
Minitron
8015 7 Segment 16 Pin DIL .. £1.18
80160 As above but ±1 .. £1.18

CLOCK CHIP

CT7001 MOS/LSI Digital Clock/Calendar Chip plus full Circuits and Information Leaflet ... £3.95
Circuits and Information Sheet 18p
Lit704 Led Display for above £1.35
Or 4 for £3.25

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Red - Blue - Green. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18.50 plus 35p P. & P.

U.K. CARR.
15p unless otherwise stated

V.A.T.
8% VAT to be added to all orders

Send 50p for a CRESCENT CATALOGUE

VEROBOARD

	.1	.15	Plain .15
2 1/2 x 3 1/2	30p	34p	18p
3 1/2 x 5	34p	34p	18p
3 1/2 x 8	34p	34p	18p
3 1/2 x 12	34p	34p	18p
17 x 8 1/2	1.45p	1.10p	75p
17 x 8	1.45p	1.10p	75p

Pin insertion tool 65p
Spot face Cutter 45p
Pkt 36 pins (size .1 or .15) 85p

LOUDSPEAKERS

2 1/2" 8 ohm 50p
2 1/2" 40 ohm 30p
2 1/2" 80 ohm 50p
5 1/2" 8 ohm ceramic £1.25
6 1/2" 8 ohm Dual cone ceramic £2.50
10" 8 ohm Dual cone ceramic £3.75
7" x 8" 8 ohm ceramic £1.90
8" x 5" 8 ohm Permanent Magnet £1.90
*EMI 13" x 8" 450 Kit 3-5-15 ohm £4.10
*EMI 13" x 8" 350 Kit 8 ohm £7.50
Fane Ultra high power loudspeakers
*Pop 25/3 30 watt 15ohm 12" £8.20
*Pop 55 50 Watt 8/15ohm 12" £14.50
*Pop 50 50 Watt 15ohm 12" £11.90
*Pop 60 60 Watt 8/15ohm 15" £15.70
*Pop 100 100 Watt 8/15ohm 15" £28.70
*Car on L/S over 13" x 8" and 15" 50p per 1.00

S. G. BROWN "DIPLOMAT" HEADSET

Finest quality British made Lightweight Headphones. Incorporates ceramic piezo electric transducers. Specification:— Frequency—20-17,500 CPS. Impedance—Predominantly capacitive, at 601MHz per capsule can be regarded as 150K at 1Kcs. Weight—3.5oz. (98 grams). A Bargain at £1.25 each set

TWO WAY STEREO ADAPTOR

Stereo jack plug to two stereo line sockets complete with 110 mm of cable. For plugging two stereo inputs into one. A Bargain at 65p.

STEREO/MONO HEADPHONE VOLUME CONTROL BOX

Plug Stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/mono switch. Complete with stereo jack plug and 2 m cable. A Bargain at 81p.

12-0-12 VOLT 500mA/240 VOLT PRIMARY TRANSFORMER

approx. size = 60mm x 40mm x 50mm. Fixing centres—75mm. A REAL BARGAIN AT £1.99 each.

DECON-DALO 33 PC ETCH RESIST PEN

The Decon-Dalo 33PC is a unique instrument for the professional and amateur electronics engineer. Enabling him to prepare in minutes a perfect printed circuit board.

OUR PRICE 90p + VAT

POWER PACKS

PP1 Switched 3-6-7.5-volt 400MA Transistor & Zener Stabilised ON/OFF switch & Polarity Reversal switch, in a black metal case. £5.95 each
PP2 Switched 6-7.5-9 volt Battery Eliminator. Approx size 2 1/2" x 3 1/2". Ideal for cassette recorders. £3.75 each (Phillips type £3.00)
PP3 Car converter. From 12v Pos. or Neg to = 6-7.5-9 volt. Easy to fit and transistor regulated. £3.50 each.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering - yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits—assemble components—build things—experiment. You enjoy every minute of it! You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics. You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire high-powered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book - see how easy it is - read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE DEPT. CEE 01 READING RG7 4PF

CEE 01

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME ADDRESS



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

Normal Household Type

EX. G.P.O.

only **99p** P & P 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

only **25p** POST & PACKING 15p

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, 1" long, 1/4" dia. High Speed P.O. type	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types	50p
H39	6	Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945	50p
H41	2	Sil Power transistors comp pair BD131/132	50p
H63	4	2N3055 type NPN Sil. power transistors. Below spec. devices	50p
H64	4	3819 N Channel FETs 2N3819 in plastic case	50p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Transistors, manufacturers rejects, AF, RF, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p
H67	10	3819N Channel FETs plastic case type	50p

Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.00p each

Electronic Transistor Ignition £6.00

Complete kit p. & p. 11p

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Extension Telephones

Ideal for childrens toys **70p** each P. & P. 25p.

New X Hatch

Our new vastly Improved Mark Two Cross Hatch Generator is now available

Essential for alignment of colour guns on all colour T.V. receivers. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3".

Ready built unit only **£9.95** Complete kit **£7.95**

(Includes p. & p. but no batteries)



LM380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL60745.

This fantastic little 3 watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea complete with data and projects book

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can
TYPE "B" PNP Silicon, plastic encapsulation
TYPE "E" PNP Germanium AF or RF
TYPE "F" PNP Silicon plastic encapsulation
TYPE "G" NPN silicon similar ZTX 300 range

8 RELAYS FOR various types p & p 27p **£1.00p**

UHF TV Tuner Units

Brand new by a famous manufacturer
Data supplied **£2.50**

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1. VCE. Min 15.	HFE Min 15.	1-12	13-25	26-50
40 Watt	20p	18p	18p	18p
90 Watt	24p	22p	20p	20p
Range 2. VCE. Min. 40.	HFE Min 40	1-12	13-25	26-50
40 Watt	30p	28p	28p	28p
90 Watt	35p	33p	30p	30p

Please state NPN or PNP on order.

High Speed Magnetic Counters 4 digit (non-react) 24V or 48V 4 x 1 x 1 in 33p p & p 5p.

INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc.

Pocket Size 12p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS
14 pin type at 15p each | Now new low profile 16 pin type at 17p each | type

BOOKS

We have a large selection of Reference and Technical Books in stock. Details are in our latest Catalogue. Send for it TODAY, using the coupon below. N.B. Books are sold of V.A.T.

Send for lists of publications

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE Bi-Pre-Pak Catalogue I enclose large SAE with 5p stamp

NAME

ADDRESS

Please add VAT at current rate
MINIMUM ORDER 50p. CASH WITH ORDER
PLEASE. Add 15p post and packing per order
OVERSEAS ADD EXTRA FOR POSTAGE
BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co. Reg. No B20919

Dept. D. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept E.E.C. 15
P.O. Box 156, Jersey, C.I.
Please send FREE BROCHURE to

NAME Block
ADDRESS Caps.
..... Please
.....

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL

QUALITY STEREO SOUND

SOLENT AUDIO SYSTEM

ALMOST 1/2 PRICE OFFER!

MADE TO SELL AT
DOUBLE THE PRICE
IN CABINET FORM
OUR PRICE £49.95

£5
down



*Stereo Tuner Amplifier chassis with AM FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. Power output 7 watts R.M.S. per channel (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £2.50. Send £7.50 today.

Chassis only available for cash at £35.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every order.

LEWIS radio

E.E. 1/75. 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL Telephone: 01-882-1644

SPARKRITE MK II

Electronic Ignition... Better on all points

Because you keep your points!



The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly — with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of norm, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes.
- Up to 20% better fuel consumption.
- Instant all weather starting.
- Cleaner plugs — they last 5 times longer without attention.
- Faster acceleration.
- Faster top speeds.
- Coil and battery last longer.
- Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components, full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

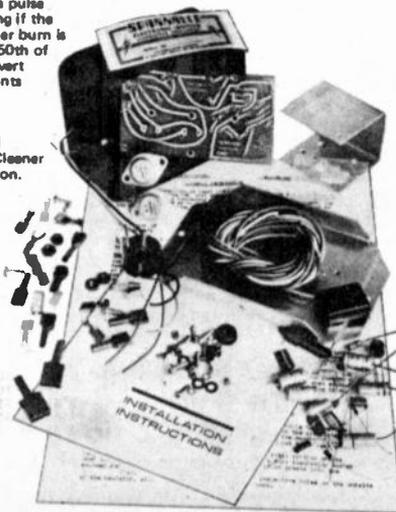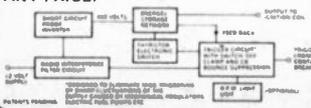WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!



Sparkrite MK II — full capacitive discharge electronic system — not just a transistorised inductive discharge booster.



PRICES

D.I.Y. Kit only £10.93 incl. VAT and P & P
Ready Built Unit £13.86 incl. VAT and P & P
(Both to fit all cars with coil/distributor ignition up to 8 cylinders).

We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration.

ORDER NOW TO:

ELECTRONICS DESIGN ASSOCIATES
(Dept EE. 1.) 82 Bath Street,
Walsall WS1 3DE Phone 33652

- Please supply:
- Sparkrite Mk.2 D.I.Y. Kit(s) at £10.93 each incl. VAT and P & P (Will make pos. or neg. earth).
 - Sparkrite Ready Built Neg. Earth Unit(s) at £13.86 each incl. VAT and P & P
 - Sparkrite Ready Built Positive Earth Unit(s) at £13.86 each incl. VAT and P & P

NAME _____

ADDRESS _____

I enclose cheque/P.O. for £
Send SAE for brochure.

Marshall's

A. Marshall (London) Ltd. Dept. EE
42 Cricklewood Broadway London NW2 3HD Telephone 01-452 0161/2 Telex 21492
& 85 West Regent Street Glasgow G2 2OD Telephone 041-332 4133

Everything you need is in our
New Catalogue
available now price 20p
(100 pages of prices and data)

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat

Trade and export enquiries welcome

Popular Semiconductors

2N456	0.75	2N2647	1.12	2N3905	0.24	ACY28	0.20	BC169B	0.13	BD132	0.50	BFY19	0.62	MJ490	0.98
2N456A	0.75	2N2904	0.22	2N3906	0.27	ACY30	0.58	BC169C	0.13	BD135	0.43	BFY20	0.60	MJ491	1.38
2N457A	1.35	2N2904A		2N4036	0.63	AD142	0.59	BC170	0.11	BD136	0.46	BFY29	0.40	MJE340	0.45
2N490	3.16		0.24	2N4037	0.42	AD143	0.53	BC171	0.11	BD137	0.35	BFY50	0.23	MJE2955	1.12
2N491	3.58	2N3905	0.24	2N4058	0.16	AD149V	0.06	BC172	0.11	BD138	0.63	BFY51	0.23	MJE3055	0.68
2N492	2.99	2N3905A		2N4059	0.09	AD150	0.63	BC182	0.12	BD139	0.71	BFY52	0.21	MP8111	0.32
2N493	4.20		0.26	2N4060	0.11	AD161	0.45	BC182L	0.12	BD140	0.87	BFY53	0.18	MP8112	0.40
2N696	0.22	2N2906	0.19	2N4061	0.11	AD162	0.45	BC183	0.09	BDY20	1.05	BFY90	0.75	MP8113	0.47
2N697	0.16	2N2906A		2N4062	0.11	AD161	pr	BC183L	0.09	BF115	0.25	BRY39	0.48	MPF102	0.30
2N698	0.40		0.21	2N4126	0.20	AD162	1.05	BC184	0.11	BF116	0.23	BU104	2.00	MPSA05	0.25
2N699	0.45	2N2907	0.22	2N4289	0.84	AF109R		BC184L	0.11	BF117	0.43	BU105	2.25	MPSA06	0.26
2N706	0.14	2N2907A		2N4919	0.84	AF115	0.24	BC186	0.25	BF119	0.58	CI06A	0.46	MPSA5	0.26
2N708	0.14		0.24	2N4920	0.99	AF116	0.23	BC187	0.27	BF121	0.25	CI06B	0.35	MPSA56	0.27
2N708A	0.17	2N2924	0.14	2N4921	0.73	AF117	0.20	BC207	0.12	BF123	0.27	CI06D	0.65	NE555W	0.70
2N709	0.42	2N2926	0.11	2N4922	0.84	AF118	0.55	BC208	0.11	BF125	0.25	CI06E	0.43	NE560	4.48
2N711	0.50	2N3053	0.25	2N4923	0.83	AF124	0.30	BC212K	0.10	BF152	0.20	CA3020A		NE561	4.48
2N718	0.23	2N3054	0.60	2N5172	0.12	AF125	0.30	BC212L	0.16	BF153	0.21		1.80	NE565A	4.48
2N718A	0.28	2N3055	0.75	2N5174	0.22	AF126	0.28	BC214L	0.19	BF154	0.16	CA3046	0.70	OC23	1.35
2N720	0.50	2N3390	0.26	2N5175	0.26	AF127	0.28	BC237	0.28	BF158	0.23	CA3048	2.11	OC28	0.76
2N721	0.55	2N3391	0.23	2N5176	0.32	AF139	0.39	BC238	0.09	BF159	0.27	CA3089E1	96	OC35	0.60
2N914	0.22	2N3391A		2N5190	0.92	AF170	0.25	BC239	0.09	BF160	0.23	CA3090Q		OC42	0.50
2N916	0.28		0.29	2N5191	0.95	AF172	0.25	BC251	0.20	BF161	0.42	CD4000	4.23	OC45	0.32
2N918	0.32	2N3392	0.13	2N5192	1.24	AF178	0.55	BC252	0.18	BF163	0.32	CD4001	0.51	OC71	0.20
2N929	0.30	2N3393	0.13	2N5195	1.46	AF179	0.65	BC253	0.23	BF166	0.32	CD4002	0.51	OC72	0.23
2N1302	0.19	2N3394	0.13	2N5245	0.43	AF180	0.50	BC258	0.09	BF167	0.21	CD4002	0.51	OC73	0.25
2N1303	0.19	2N3402	0.18	2N5457	0.49	AF186	0.46	BC258	0.09	BF173	0.43	CD4009	1.07	OC83	0.24
2N1304	0.24	2N3403	0.19	2N5458	0.45	AF200	0.35	BC259	0.13	BF177	0.29	CD4010	1.07	ORP12	0.35
2N1305A	0.24	2N3440	0.59	2N5459	0.49	AF239	0.51	BC261	0.20	BF178	0.35	CD4011	0.51	RS3	1.20
2N1306	0.31	2N3441	0.97	40361	0.48	AF240	0.72	BC262	0.18	BF179	0.39	CD4015	2.66	RL54	0.15
2N13107	0.22	2N3442	1.69	40362	0.50	AF279	0.54	BC263	0.23	BF180	0.43	CD4016	1.02	SC35D	1.68
2N1308	0.25	2N3414	0.10	40363	0.88	AF280	0.54	BC300	1.12	BF181	0.34	CD4017	2.66	SC36D	1.46
2N1309	0.36	2N3415	0.10	40364	0.46	AF281	0.75	BC301	0.34	BF182	0.40	CD4018	1.89	SC40D	1.82
2N1316	1.44	2N3416	0.15	40394	0.56	AL103	0.70	BC302	0.29	BF183	0.33	CD4023	0.31	SC41D	3.22
2N1671A		2N3417	0.21	40395	0.65	BC107	0.16	BC303	0.54	BF184	0.30	CD4024	1.90	SC45D	1.89
2N1671B	1.54	2N3638	0.15	40406	0.44	BC108	0.15	BC307	1.10	BF185	0.30	CD4027	1.56	SC46D	1.96
2N1671B1	72	2N3638A		40407	0.33	BC109	0.19	BC307A	1.10	BF194	0.12	CD4028	2.34	SC50D	2.60
2N1671C			0.15	40408	0.50	BC113	0.15	BC308	0.09	BF195	0.12	CD4029	3.79	SC51D	2.39
2N171	4.32	2N3639	0.27	40409	0.52	BC115	0.17	BC308A	1.2	BF196	0.13	CD4041	2.11	SL41A	1.80
2N1707	0.45	2N3641	0.17	40410	0.52	BC116	0.17	BC308B	0.09	BF197	0.15	CD4044	2.11	SL62J	4.59
2N1901	5.50	2N3702	0.11	40411	2.25	BC116A	0.18	BC309	0.10	BF198	0.18	CD4047	1.65	TAA263	1.00
2N2102	0.50	2N3703	0.12	40414	3.55	BC117	0.21	BC309A	0.10	BF199	0.18	CD4049	0.90	TAA350	2.10
2N2147	0.78	2N3704	0.14	40430	0.85	BC118	0.11	BC309B	0.10	BF200	0.40	CD4050	0.90	TAA621	2.03
2N2148	0.94	2N3705	0.12	40583	0.23	BC119	0.29	BC237	0.19	BF225	0.19	LM301A	0.48	TAA661B	
2N2160	0.60	2N3706	0.09	40601	0.67	BC113	0.23	BC238	0.21	BF227	0.22	LM304A	2.03	TAD100	1.32
2N2192	0.40	2N3707	0.10	40602	0.46	BC125	0.16	BC337	0.19	BF238	0.22	LM309K	1.88	TAD100	1.32
2N2192A		2N3708	0.70	40603	0.53	BC126	0.23	BC338	0.19	BF244	0.40	Filter	0.75	TB217	0.64
2N2913	0.40	2N3709	0.11	40604	0.56	BC132	0.30	BCY30	0.64	BF245	0.58	LM709T099		TBA61B	
2N2913A	0.40	2N3710	0.12	40636	1.10	BC134	0.13	BCY31	0.64	BF246	0.58	8DIL	0.48		1.25
2N2913B		2N3711	0.11	40669	1.00	BC135	0.13	BCY32	1.15	BF247	0.23	14DIL	0.40	TBA800	1.50
2N2914	0.61	2N3712	0.96	40673	0.70	BC136	0.17	BCY33	0.45	BF254	0.16	14DIL	0.40	TBA810	1.50
2N2914A	0.73	2N3713	1.20	AC107	0.51	BC137	0.17	BCY34	0.49	BF255	0.17	LM723C	0.90	TIL209	0.30
2N2218A	0.30	2N3714	1.33	AC113	0.16	BC138	0.24	BCY38	0.55	BF257	0.46	LM741T099		TIP29A	0.49
2N2218B		2N3715	1.50	AC117	0.20	BC140	0.34	BCY39	1.50	BF258	0.59	BDIL	0.40	TIP30A	0.58
2N2219	0.22	2N3716	1.80	AC126	0.20	BC141	0.29	BCY40	0.87	BF259	0.55	14DIL	0.38	TIP31A	0.62
2N2219A	0.24	2N3717	2.20	AC127	0.20	BC142	0.23	BCY42	0.28	BF251A	2.30	LM747	1.00	TIP32A	0.74
2N2219B	0.26	2N3718	2.65	AC151V	0.25	BC145	0.21	BCY58	0.21	BF258	0.92	LM748BDIL		TIP33A	1.01
2N2220	0.25	2N3720	4.00	AC153	0.25	BC148	0.13	BCY59	0.22	BF261	0.27	LM748BDIL		TIP34A	1.51
2N2221	0.18	2N3721	2.35	AC153K	0.25	BC149	0.12	BCY72	0.13	BFX30	0.30	LM7805	2.00	TIP35A	2.90
2N2221A		2N3722	6.69	AC154	0.20	BC153	0.18	BCY87	3.54	BFX44	0.33	LM7805	2.00	TIP36A	3.70
2N2222	0.21	2N3729	1.10	AC176	0.18	BC154	0.18	BCY88	2.42	BFX63	2.48	MC1303p		TIP41A	0.79
2N2222A	0.20	2N3819	0.37	AC176K	0.25	BC157	0.14	BCY89	0.97	BFX68	0.30	MC1310p		TIP295S	0.90
2N2222B	0.25	2N3820	0.38	AC187K	0.23	BC158	0.13	BD115	0.75	BFX84	0.24	MC1310	0.92	TIP305S	0.60
2N2368	0.25	2N3823	1.12	AC188K	0.34	BC159	0.14	BD116	1.00	BFX85	0.28	MC1458CP1		TIP300	1.3
2N2369	0.37	2N3901	0.32	ACY19	0.27	BC160	0.37	BD121	0.75	BFX87	0.24		0.70	ZTX302	2.00
2N2369A	0.41	2N3903	0.24	ACY19	0.27	BC167B	0.13	BD123	0.32	BFX88	0.25		0.70	ZTX500	1.15
2N2646	0.55	2N3904	0.27	ACY21	0.26	BC168B	0.13	BD124	0.67	BFX89	0.45	MJ480	0.90	ZTX502	1.18
						BC168C	0.11	BD131	0.40	BFY18	0.52	MJ481	1.14	ZTX530	0.21

PW Teletennis Kit as featured on BBC Nationwide and in the Daily Mail 2 Oct '74. Ideal game for whole family. No need to modify your TV set, just plug in to aerial socket.

Parts list as follows: A Resistor Pack £1.00 p & p 20p; B Potentiometer Pack £1.25 p & p 20p; C Capacitor Pack £3.10 p & p 20p; D Semi-conductor Pack £14.50 p & p 20p; E IC Sockets £4.00 p & p 20p; F Transformer £1.15 p & p 25p; G PCB's £7.50 p & p 20p; H Switches £4.50 p & p 20p; I UHF Modular Kit £7.20 p & p 20p.

Special Prices—complete kit excluding case £42.00 p & p 50p. Sections A-F incl. £23.50 p & p 30p. Assembly instructions with complete kit or 75p on request.

P.C. Marker Pen Dalo 33pc Price 87p. Zeners 400MW 2.7V-43V 11p, 1W 3-3V-120V 17p, 1C 5k resistors 8DIL-16p, 14DIL-17p, 16DIL-20p.

Liquid Crystals—£13.00. Ex stock S.A.E. for details of CMOS battery operated clock kit using LCD's.

Scorpio Car Ignition Kit—£11.50 + VAT 1HF 440V £1.10 BST80246 £1.05 Transformer £2.75 Minitron £1.55 DL 707 £2.35 or 4 for £8.00

Resistors	W	Tol	Price	Tant Beads	Value
± 5%	1p			1/35	14p
± 5%	1.5p			22/35	14p
± 5%	2p			47/35	14p
1	10%	2.5p		2.2/35	14p
2	10%	6p		4.7/35	18p
2½	5%	7p		10/16	18p
5	5%	9p		47/6	3V 10p
10	5%	10p		100/3V	20p

Trade and Retail Supplied

Potentiometers	Linear or Log	Single Double
Rotary Pots	18p	45p
Rotary Switched	28p	—
Sliders	50p	80p

Full range of Capacitors stocked. See catalogue for details

Presets Horizontal or Vertical
1W 6p 2W 6p 3W 6p

Everyday Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words). Box No. 30p. extra. Semi-display—£7-50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farrington Road, London EC4A 4AD.

RECEIVERS and COMPONENTS

TUNBRIDGE WELLS. Components from Ballard's, 108, Camden Road, Tunbridge Wells. Tel: Tunbridge Wells 31803. S.a.e. for all enquiries.

RADIO, TV and other valves. Large stocks 1930 to 1974. Many obsolete types. SAE for quotation. Price List 15p. Also available a large range of Transistor and Still. Cox Radio, The Parade, East Wittering, Sussex. West Wittering 2023.

LOWEST COST IC SOCKETS. Use Soldercon IC socket pins for 8 to 40 pin DIL's. In strips of 100 pins: 100+ pins 70p, 300+ 50p, 1000+ 40p. Instructions supplied. 10p p&p for orders under £2. Add 8% VAT. SINTEL, 53c Aston Street, Oxford.

3 Ass. M.C. meters £1-15 (35p). Large Computer Panels. 35-50 Transistors, Long Leads 85p (35p). Copper Clad PCB Panels 5" x 5", 6-8p c.p. 7" x 9", 6-21-30 c.p. Silicon Diodes 650V 11A. 10 on Tagboard 50p c.p. T.V. Convergence Panels 2 x AC128 3 Slugged Coils, 3 Slide Switches, 11 W.W. Pots, 3 Carbon Presets, 2 Ferrite Chokes etc. £1-10 c.p. Valupaks, Pp 100 3/Mica Caps 87p c.p. send 10p for Lists of others plus Panels etc. Refund on purchase. 7 lbs Assorted Components £1-75 c.p.

J.W.B. RADIO
2 Barnfield Crescent, Sale, Cheshire M33 1NL
Postage in brackets Mail Order only

COMPONENTS GALORE. Pack of 500 mixed components manufacturers surplus plus once used. Pack includes Resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1-10p p. and p. c.w.o. to CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

FOR SALE

BACK NUMBERS, first 28 issues. Offers: Baker, 144, Chanctonbury Road, Burgess Hill, Sussex.

MICROPHONES: AKG D109, £12-65; AKG D202E1, £43-45; AKG D190C, £18-70; AKG D190E, £20; AKG D224, £55; Sennheiser MD211N, £49-50; Sennheiser MD413N, £29-70. All brand new and boxed. Send CWO to J. J. Francis (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

SERVICE SHEETS

SERVICE SHEETS for over 6,000 models of Television, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only 30p plus S.A.E. with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. S.A.E. enquiries. Catalogue 20p plus S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

BELL'S TELEVISION SERVICES for Service Sheets, Manuals, Books on Radio's TVs etc. Service Sheets 40p plus S.a.e. Free book lists on request. Back issues of PW, PE, EE, TV available 25p + 7p post. S.a.e. with enquiries—B. T. S. (Mail Order Dept.) 190, Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

MISCELLANEOUS

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit board-masters, negatives and boards, one-off or small numbers. Send 6p for list. **RAMAR CONSTRUCTOR SERVICES,** 29 Shelbourne Road, Stratford-on-Avon, Warks.

AUTUMN BONANZA!

S.B. SUPPLIES offer:

LEVER key switch, 4-pole, lock-off-lock, in black plastic stackable case app. 120mm x 120mm x 25mm. Brand new **75p**
PUSH button switching unit, 3 two-pole c/o units, one cancels others, room for one more unit. App. 75mm x 60mm x 35mm. Brand new (wired and numbered) **50p**
RELAY, 24 volt, 3800 ohms, 4 c/o contacts, size: 40mm x 33mm x 15mm (wired and covered), Brand new **50p**
LAMP fitting, 6 volt—contained in hammer finished, grey steel box on wood plinth. Ideal case for small projects. Size app. 75mm x 75mm x 70mm. Brand new **50p**
SPECIAL price until 28.2.75 for all 4 above items + useful accessory. **£2-00**
4T S energising erpieces (salvaged) **20p**

All prices include VAT and p. & p. Man & other Govt. surplus, new and surplus items at bargain prices. S.A.E. for Autumn Catalogue of electronic parts to:

38 HEATHWOOD GARDENS, SWANLEY KENT BR7 7HN

SUPERB instrument cases by Bazelli, manufactured from heavy duty P.V.C. faced steel. Hundreds of Radio, Electronic and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount, prompt dispatch. Free literature, Bazelli, Department No. 24, St. Wilfrids, Foundry Lane, Halton, Lancaster, LA2 6LT.

PSYCHEDELICATESSEN

is the only way to describe the paradise of FREAKY gear now available from Boffin

LOOK!

Kits

NO LICENCE EXAM. Transmitter/Receiver **£6-90**

Variable-rate, BRIGHT-FLASH, Pocket Mini-Strobe **£2-90**

Ready-Made Experimental Modules

Maxi-Volt SPARK GENERATOR (1inch spark), 15,000 Volts. **£1-90**

Mini DREAM-LABORATORY **£2-20**

SENSITIVE non-anatomical electronic STETHOSCOPE **£3-20**

Electronic 'VOICE-TROWER' **£3-20**

GHOST-HUNTING AID **£3-20**

PEOPLE DETECTOR **£3-20**

SPEAK-THRU-WATER-FONE **£6-40**

PSYCHEDELIC MEDITATION AID **£3-20**

Bird-Watchers' REMOTE MONITOR **£3-20**

Psychological CROSS-EYED EARS **£6-40**

Device **£3-20**

'Big Ear' SOUND-CATCHER **£3-20**

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh,

Ewell, Surrey

(Mail order U.K. only)

Or for more details, send 20p for lists, plus free design project sheet



ONE OF EUROPE'S LEADING ELECTRONIC KITS

POST FREE MAIL ORDER
S.A.E. FOR CATALOGUE

TELEVIEW

414, CATCOTE ROAD,
HARTLEPOOL,
CLEVELAND.

TV and Electronic Publications. TV Repair Manuals £5-00 each plus 35p post. Send stamp for brochure to Duon Enterprises, Grange Farm, Wyaston, Ashbourne, Derbys.



MULTIMETER Type U4324

20,000 Ω/V, Overload protected, Ranges: 0-6, 1-2, 3, 12, 30, 60, 120, 600, 1200V DC; 3, 6, 15, 60, 150, 300, 600, 900V AC; 0-0.6, 0-6, 0-60, 600mA, 3A DC; 0-3, 3, 30, 300mA, 3A AC; 5 resistance ranges to 5M Ω, dBs, -10 to +12. Size 167 x 98 x 63mm. Supplied complete with test leads, clips spare diode and instructions.

ONLY £10-00

PC ETCHING KIT

Contains 1lb Ferric chloride, DALO etch-resist pen, 100 sq ins copper clad board, etching dish, abrasive cleaner and instructions. £3-30

FERRIC CHLORIDE

Anhydrous to Mill-spec in double-sealed 1lb packs. 1lb 90p; 3lb £3-65; 10lb £4-40.

VEROBOARD

100 sq ins 0-1, 0-15 & 0-2" good-size offsets (About 8 pieces) £1-16.

TRANSFORMERS

Miniature 15p, mains primary, 100mA sec. 6-0-6V 85p; 9-0-9V 90p; 12-0-12V 95p. 16-0-16V with 9V tap @ 11A 22.

COMPUTER PANELS

31bs aasid £1-60; 71b £2-60; 501b £18; 12 high quality panels with trimtops, power transistors, IC's etc. £2-50. Pack of boards with 500 components inc. at least 50 transistors 90p.

GREENWELD ELECTRONICS [E99]
51 SHIRLEY PARK ROAD,
SOUTHAMPTON SO1 4PX

Tel (0703) 772501. Also at 38 Lower Addiscombe Rd, Croydon & 21 Deptford Bdy SE8.

ALL PRICES INCLUDE 9% VAT AND UK POSTAGE. SAE LIST, ENQUIRIES. CALLERS WELCOME.

TREASURE TRACER MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete Kit P&P 45p.	£9-80	Built, tested and guaranteed P&P, 45p.	£13-75
-----------------------	--------------	--	---------------

MINIKITS ELECTRONICS
35b LANGLEY DRIVE, WANSTEAD
LONDON, E11 2LN (Mail order only)

FLUORESCENT LIGHT KIT

12 v
8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B., instructions, etc.

Price only £3-19
Ready built £3-78
Diffuser only 59p extra

inc VAT
post &
packing

ALUMINIUM BOXES

Prices include lid, screws, and V.A.T.
Post and packing 10p extra on all orders.

7	5 1/2"	by	2 1/2"	by	1 1/2"	high	28p
8	4"	by	4"	by	1 1/2"	high	28p
9	3 1/2"	by	2 1/2"	by	1 1/2"	high	28p
10	3 1/2"	by	4"	by	1 1/2"	high	28p
11	4"	by	2 1/2"	by	2"	high	28p
12	3"	by	2"	by	1 1/2"	high	28p
13	6"	by	4"	by	2"	high	60p
14	7"	by	5"	by	2 1/2"	high	60p
15	8"	by	6"	by	3"	high	60p
16	10"	by	7"	by	3"	high	60p

Order now to —

ELECTRONICS DESIGN ASSOCIATES
DEPT. E.E.
82 Bath St., Walsall, WS1 3DE. Phone 33652

INSTRUMENTAL AUDIO EFFECTS

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPERATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £3-00 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC.. UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUCTIONS. KIT PRICE: £3-00 post paid.

MAIL ORDER ONLY.
S.A.E. ALL ENQUIRIES.
PLEASE ADD V.A.T. TO ALL ORDERS

DABAR ELECTRONIC PRODUCTS

98, LICHFIELD STREET,
WALSALL, STAFFS. WS1 1UZ

ELECTRONI-KIT

Electronic fun for all ages

The most versatile electronics kits. All components are beautifully encapsulated in unbreakable transparent plastic blocks. Perfect connections are made WITHOUT SOLDERING, SCREWING OR WIRING.

INCREDIBLE VALUE. Build, dismantle and rebuild projects any number of times and invent your own experiments too.

COMPLETELY SAFE. Instructive and FUN—all kits operate from 9v. battery only.

VALUABLE MANUALS included with every kit. No previous knowledge is required, even with the largest kits.

KIT 2A—30 projects £10-45. Radios, amplifiers, alarms, microphones, Morse, etc.
KIT 3A—100 projects £20-45. As 2A plus electronic birds, cats, sirens, organs, metronomes, guns, light and sound, burglar alarms, etc.

3ADX—105 projects £25-25. As 3A plus solar cell experiments and complete sophisticated control panel, etc.

4ADX—150 projects £33-95. As 3ADX plus Relay and Meter experiments; ion concentration—, volume—, out-put—, field intensity—, volt—, resistance meters, ammeter, illuminometer, etc. and many, many more.

ADD-ON parts and manuals available as required.

The three larger kits include Electrical experiments too.

All prices include Battery, Manual, VAT & p. & p.

Cheque/P.O. (or 6p for literature) to:
Satisfaction guaranteed
ELECTRONI-KIT LTD, 408 St. John's Street,
London, EC1. (01-278 4579)

AERIAL BOOSTERS—£3-30

We make three types of aerial boosters B45-UHF-TV, B12-VHF-TV, B11-VHF-Radio.


VALVES BARGAINS

ANY 5-50p, 10-75p, 50-£3-30.
ECC82, EF80, EF183, EF184, PCC189, PCF80, PCF802, PCL82, PCL84, PCL85/808, PFL200, PL38, PL504, PY800, PY86.

COLOUR TV VALVES—PL508, PL509, PY500-25p each.

Prices includes VAT. PAP 10p, SAE—leaflet
Electronic Mail Order Ltd, 62 Bridge Street,
Ramsbottom, Bury, Lancs. Tel RAMS 3836.

LOUDSPEAKERS

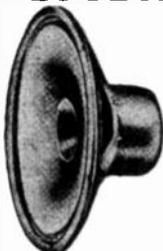

Speakers, kits and cabinets for D.I.Y., Hi Fi, P.A., Disco, etc. by EMI, Fane, Goodmans, Baker, Elac, Richard Allan, Wharfedale, etc. Send for free booklet "Choosing a speaker"

WILMSLOW AUDIO


Dept. H, Swan Works, Bank Square,
Wilmslow, Cheshire SK9 1HF
Tel. Wilmslow 29599

ELECTROSPARES

We regret that due to a printing error, the above company's advertisement in the December 1974 issue contained a reference to the supply of component kits for most projects featured editorially in this publication.

Readers are advised that Messrs. Electrospares have temporarily withdrawn this service.

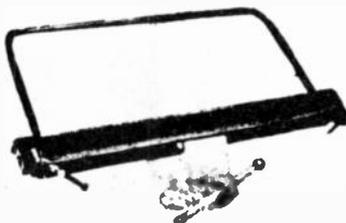PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel x 36in. wide ... £21-00 carr. free
No. 2. Capacity 18 gauge mild steel x 24in. wide ... £15-00 carr. free
No. 3. Capacity 16 gauge mild steel x 18in. wide ... £15-00 carr. free
Also new bench models. Capacities 36in. x 18 gauge £40-00 24 in. x 16 gauge £38-00. Carriage free. Add 8% VAT to total price of machine.
End folding attachments for radio chassis, tray and box making. Steel angle 36" model, 40p per ft. Other models 30p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works,
Upper George St., Heckmondwike, Yorks. Heckmondwike 403997

Trannies

4 Bush House
Harlow, Essex

- ★ Price inclusive of VAT
- ★ Retail shop open 9-5.30 Mon to Sat.
- ★ Post & Packing 15p

£1 BARGAIN PACKS

- £1 10 NPN Power transistors (like 2N3055) tested no opens no shorts.
- £1 30 Plastic FET'S like 2N3819 U/Test random test shows good yield.
- £1 30 Plastic power NPN transistors like 2N3055 untested.
- £1 250 mixed capacitors.
- £1 500 mixed resistors.
- £1 25 potentiometers.

★ Any 5 packs £4.50 + p. & p. 10p per pack.

We stock a large range of electronic semi-conductors at competitive prices. Our new '74 catalogue is now available at 20p.

Electrolytic Capacitors

6.3 VOLT	16 VOLT	40 VOLT
68µF 6½p	220µF 9p	47µF 6½p
150µF 6½p	680µF 9p	100µF 9p
470µF 11p	1000µF 17p	68µF 10p
680µF 13p	1500µF 25p	220µF 11p
1500µF 18p	2000µF 43p	470µF 19p
2200µF 18p		680µF 25p
3300µF 26p		1000µF 25p
	25 VOLT	63 VOLT
	10µF 6½p	220µF 11p
	47µF 6½p	1µF 6½p
	100µF 6½p	2-2µF 6½p
	220µF 8p	4-7µF 6½p
	330µF 10p	6-8µF 6½p
	470µF 16p	10µF 6½p
	1000µF 11p	1500µF 20p
	1500µF 20p	220µF 6½p
	2200µF 24p	2200µF 39p
		68µF 10p
		100µF 11p
	16 VOLT	150µF 13p
	15µF 6½p	150µF 19p
	33µF 6½p	6-8µF 6½p
	150µF 6½p	330µF 22p
	150µF 8p	470µF 26p
		1000µF 44p

Volume Controls Potentiometers
Carbon track 500Ω to 2.2 meg Ω Log or Linear.
Single 13p. Dual gang (stereo) 44p.
Single type with D.P. switch 26p.

Veroboard matrix	0-15 0-1 matrix
2½ x 3½	17p 22p
2½ x 5	22p 24p
3½ x 3½	22p 24p
3½ x 5	28p 28p
2½ x 7	60p 79p
3½ x 7	81p 110p
Pin insertion tool	82p
Spot face cutter	52p 52p
Pack of 36 pins	42p 42p
	20p 20p

Resistors
½ watt 5% carbon 1p
½ watt 5% carbon 1p
1 watt 10% carbon 31p

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-022µF, 0-22µF, 3½p, 0-33µF, 0-047µF, 0-068µF, 4p, 0-1µF, 4½p, 0-15µF, 0-22µF, 5½p, 0-33µF, 7p, 0-47µF, 9½p, 0-68µF, 12p, 1-0µF, 14p, 1-5µF, 22p, 2-2µF, 27p.
MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 2½p, 0-0068µF, 0-01µF, 0-015µF, 0-022µF, 0-033µF, 3½p, 0-047µF, 0-068µF, 0-1µF, 4½p, 0-15µF, 6½p, 0-22µF, 8½p, 0-33µF, 12p, 0-47µF, 14p.

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course". Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to Aldermaston College, Dept. TEE01, Reading RG7 4PF.

ALDERMASTON COLLEGE

Dept. TEE01, Reading RG7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

MECHANICAL	DRAUGHTSMANSHIP	Construction
Society of Engineers—	Institute of Engineering Designers (A.M.I.E.D.)	Surveyors Institute I.C.S.I.
A.M.S.E. (Mech)	General Draughtsman-ship	City & Guilds General Building (all branches)
Institute of Engineer & Technicians (A.M.I.E.)	Elec. Draughtsman-ship	Heating & Vent. Inst. Clerk of Works
CITY & GUILDS	Architectural Draughtsman-ship	Site Surveying
Gen. Mech. Eng. Maintenance Eng. Welding	Technical Drawing	Health Engineering
Sheet Metal Work		Road Construction
Gen. Diesel Eng. Eng. Inspection		Quantities
Eng. Metallurgy		Estimates
		Hydraulics
		Structural Eng.
ELECTRICAL & ELECTRONIC	RADIO & TELECOMMUNICATIONS	GENERAL
CITY & GUILDS	City & Guilds Telecoms.	Agricultural Eng. Council of Eng. Institutions
Gen. Electrical Engineering	Gen. Radio & TV Eng.	Farm Science
Electrical Installations	Radio Amateurs	Plastics
Electrical Maths	Radio Servicing	
Computer Electronics		Supplementary courses for Nat. Certificates.
Electronic Eng.	AUTOMOBILE & AERONAUTICAL	
Practical Radio & Electronics (with kit)	Institute of the Motor Industry (A.M.I.)	
	M.A.M.I.	
MANAGEMENT & PRODUCTION	City & Guilds Auto Eng.	
Institute of Cost & Management Acc'ts.	Gen. Auto Eng. Motor Mechanics	
Computer Programming	Auto Diesel Eng. Garage Mgmt	
Works Mgmt	AEC Aero Engineering Exams	
Work Study	Gen. Aero Eng.	
Gen. Production Eng.		
Estimating & Planning	CONSTRUCTIONAL	
Store-keeping	Institute of Building L.I.A.B.	Coaching for many exams, including C.A.C.
Management Skills	A.B.T. Clerk of Works	
Quality Control		

G.C.E.
—choose from 58 'O' & 'A' level subjects

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College,
Dept. TEE01 Reading

NAME.....
Block capitals please
ADDRESS.....
.....
.....
.....
POST CODE.....
OTHER SUBJECTS.....
.....
.....
.....
Accredited by C.A.C.C. Member of A.B.C.C.

Henry's SO MUCH MORE—AND YOU PAY LESS VAT WITH HENRY'S LOW PRICES

UK's No. 1
for
Electronics
and Hi Fi

You can build the Texan and Stereo FM Tuner TEXAN 20 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardeners low field transformer, 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15½" x 2½" x 6½" (also built and tested sleeve with every kit. **£31.00 (GB post paid) (also built and tested £37.50)**

STEREO FM TUNER Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2½" x 6½". Complete kit with teak sleeve **£21.00 (GB post paid) (also built and tested £24.95)**

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

TRANSISTORISED MODULES

Tuners - Power Suppliers - Amplifiers

AMPLIFIERS (All single channel unless stated)

	£ p
4-300 9 volt 300 MW	1-95
2004 9 volt 250 MW	2-70
104 9 volt 1 watt	3-10
304 9 volt 3 watt	3-95
555 12 volt 3 watt	4-10
555ST 12 volt 1½ + 1½ watt	5-95
E1208 12 volt 5 watt	5-10
608 24 volt 10 watt	4-95
410 28 volt 10 watt	4-95
620 45 volt 30 watt	9-95
Z40 30/35 volt 15 watt	5-45
Z60 45/50 volt 25 watt	6-95
SA6817 24 volt 6 + 6	10-20

AMPLIFIERS WITH CONTROLS

	£ p
E1210 12 volt 2½ + 2½ watts 8 ohms, Stereo	8-25
RE500 Mains 5 watts 4-16 ohms, Mono	6-30
SAC14 Mains 7 + 7 watts 8 ohms, Stereo	11-75
SAC30 Mains 15 + 15 watts 8 ohms, Stereo	14-95
CAO38 9 volt 1½ + 1½ watts 8 ohms, Stereo	6-95
CAO68 12 volt 3 + 3 watts 8 ohms, Stereo	10-50

FM MODULES

Mullard LP 1186 FM tuner (front end) with data 10.7 MHz O/P	4-85
Mullard LP 1185 10.7 MHz IF unit with data	4-50
Gorler Permeability FM tuner (front end) 10.7 MHz O/P	4-20

FM and AM tuners and decoders

FM 5231 (Tu 2) 6 volt FM tuner	7-95
TU3 12 volt version (FM use with Decoder)	7-95
SD4912 Stereo Decoder for Tu 3, 12 volt	7-95
SP62H 6 volt stereo FM tuner	14-95
A1007 9 volt MW-AM tuner	11-95
Sinclair 12/45 volt FM tuner stereo recorder for above	7-45
A1018 9 volt FM tuner in cabinet	13-95
A1005M (S) 9-12 volt Stereo decoder FM for above	7-50
1062 12 volt Stereo decoder general purpose	6-50

PREAMPLIFIERS

Sinclair Stereo 60 Preamplifier	6-75
E1300 Cart/Tape/Mic Inputs 9 volt	2-85
E1310 Stereo 3-30 mV mag cart 9 volt	4-75
FF3 Stereo 3 mV tape head 9 volt	4-95
3042 Stereo 5-20 mV Mag cart mains	5-95
EQ25 Mono 3-250 mV Tape/Cart/Play 9 volt	5-95

HENRY'S HOME ENTERTAINMENT CENTRES

London:
354/6 Edgware Rd., W2 (01-402 5854).
378/8 Edgware Rd., W2 (01-723 0818).
372 Edgware Rd., W2 (01-402 8140).
120 Shaftesbury Ave., W1 (01-437 9692).
230 Tottenham Court Rd., W1 (01-580 1785).
144 Burnt Oak B'way, Burnt Oak, Edgware (01-952 7402).
190/4 Station Rd., Harrow, Middx. (01-863 7788).
Out of Town:
256 Banbury Rd., Summertown, Oxford (0865) 53072).
55 Gloucester Rd., Bristol 7 (0272) 4591).

SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS. 8% VAT TO BE ADDED TO ALL ORDERS. VAT—UK ONLY.

Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Prices correct at time of preparation. Subject to change without notice. E. & O. E.

CALCULATORS

Sinclair Cambridge Kit £13.50	
Sinclair Cambridge (Built)	£17.50
Sinclair Memory	£22.50
Sinclair Scientific	£26.95
Sinclair Scientific Kit	£18.50

SINCLAIR SPECIAL PURCHASE

Project '60' stereo pre-amplifiers £6.75 pp 20p
Project '60S' Kit £19.95 pp 25p
I.C. 12.6W AMP. £2.10 pp 15p

PORTABLE RADIO

ACTIVITY COUNTER
COMPLETE WITH POWER
PACK £9.97 pp £1

DOSIEMETERS

0-5R 62p | 45p
0-50R 62p | EACH PER
0-150R 62p | DOZEN

GRAVNER INFRA RED DETECTOR

DESIGNED FOR HEAT
OR LIGHT DETECTOR.
CONTAINING 931A
PHOTO MULTIPLIER &
GK45 & NETWORK £3.50

L450 RECHARGEABLE BATTERY

2V 400MA/HR 50p p & p 15p

STC & ITT MINIATURE RELAYS

150 Ω	6V	2p.c.o.
180 Ω	6/12V	..
185 Ω	12V	..
125 Ω	12.5V	..
1700 Ω	18/24V	..
1800 Ω	24V	4p.c.o.
2500 Ω	18/24V	2p.c.o.
4000 Ω	24V	..
BRAND NEW 60p p & p 15p		

10.7 MHZ MINIATURE CERAMIC IF FILTER

40p per pair p & p 15p

SL414 PLESSEY 5W POWER AMP IC

£1.65 p & p 15p

40KHZ ULTRA-SONIC TRANSDUCERS

£5.90 p & p 25p

TAA 960 40KHZ AMP

£1.75 p & p 15p

SEND FOR YOUR FREE
BROCHURE LIST NO. 36
FOR COMPLETE RANGE
OF SEMI CONDUCTORS.

EMI SPEAKERS SPECIAL PURCHASE

13In x 8In chassis speakers (Carr.packing 30p each or 50p pr.)
*150 TC 10 watts 8 ohms twin cone £2.20
*450 10 watts 4, 8, 15 ohm with twin tweeters and crossover £3.85 each
EW 15 watt 8 ohm with tweeter £5.25
350 20 watts 8, 15 ohm with tweeter £7.80 ea.
* Polished wood cabinet £4.80 carr., etc. 35p each or 50p pair.

PHILIPS 8 WATT FLUORESCENT UNIT EXCLUSIVE PURCHASE

Brand new Philips 12 volt operated 8 watt fluorescent tube units for standby lighting Complete with tube and instructions Price £3.50 p & p 25p.

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price £1.50 each or 2 for £2.85 Printed Circuit Panels. 50p.

UHF TV TUNERS

625 line receiver UHF transistorised tuners FM UK operation. Brand new. (Post/packing 25p each). TYPE C variable tuning £2.50
TYPE B 4-button push-button (adjustable) £3.50

INVERTOR KITS

15 WATT £5.20 pp 30p
40 WATT £6.80 pp 40p

P.P.9 BATTERY ELIMINATOR COMPLETE KITS OF PARTS INCLUDING P/C BOARDS £1.95 COMPLETE KIT

AMTRON KITS

AVAILABLE EX-STOCK
SEND FOR FREE LISTS

JOSTY KITS

AVAILABLE EX-STOCK
SEND FOR FREE LISTS

