

Practical projects to build at home

everyday electronics

JAN. 77
35p



MULTI-TESTER

ALSO INSIDE...
PHOTOCUBE RECEIVER
CAR BRAKE WARNING DEVICE

Special Offer
SOLDERING KIT

SOLDERING in EASY STEPS

Stirling Sound

QV[★] MODULES FOR COST-CONSCIOUS CONSTRUCTORS


STIRLING SOUND policy is to ensure customer satisfaction by designing and making their products in their own factory in Essex and selling direct. Production control-checked throughout. All QV Modules are compatible within the range and with much other equipment.

PRE-AMP/TONE CONTROL MODULES

SS.100 Active tone control, stereo. $\pm 15\text{dB}$ on bass and on treble £1.60


SS.101 Pre-amp for ceramic cartridges, radio, tape. Stereo. Passive tone control circuit shown in date supplied £1.60

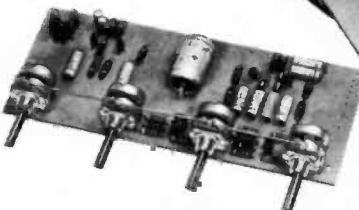SS.102 Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected. Linear feedback facility. £2.65




UNIT ONE PRE-AMP/TONE CONTROL

Combined pre-amp with active tone-control circuits. $\pm 15\text{dB}$ at 10Khz treble and 30 Hz bass. Stereo. Vol./balance/treble/bass. 200mV out for 50mV in. Takes 10-16V. £7.80

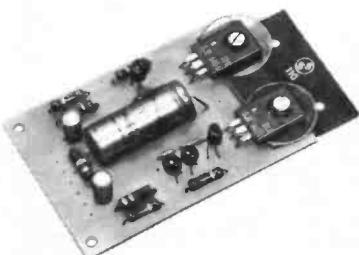

SS.110

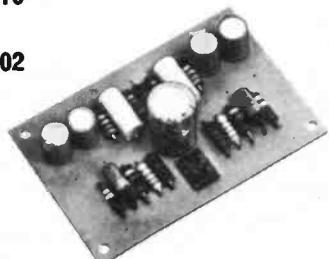

SS.102



SS.140

40 watts r.m.s. into 4 ohms using 45V supply such as SS345. Ideal for small discos and P.A. 101 x 76 x 19mm (4" x 3" x 2")

£3.95

POWER AMPLIFIERS

SS.103 3 watt r.m.s. mono I.C. with built-in current, short, and thermal protection £1.75

SS.103-3 Stereo version of above £3.75

SS.105 5 watts r.m.s. Into 4 ohms. using 12V £2.25

SS.110 10 watts r.m.s. using 24V and 4 ohm load £2.75

SS.120 20 watts r.m.s. Into 4 ohms, using 34V £3.25

The above all measure 89 x 50 x 19mm (3½ x 2 x 2 ins) Suitable power supplies will be found in the accompanying range.

FM TUNING MODULES


SS.201 Front end tuner, slow geared drive, two gang. A.F.C. facility. Tunes 88-108 MHz £5.00

SS.202 I.F. amplifier. Metering and A.F.C. facilities £2.65

SS.203 Stereo Decoder for use with the above or other FM mono tuners. A LED may be fitted £3.85

TODAY'S BEST VALUE IN POWER SUPPLY UNITS

With 13-15v take-off points

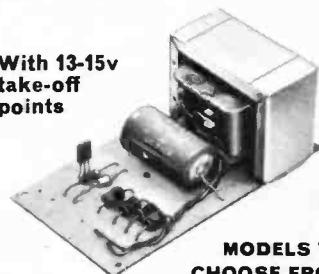

7

MODELS TO CHOOSE FROM

Complete with mains transformer and low volt take-off points. (except SS.300) All at 8% V.A.T. rate. Add 50p for p/p any model.

SS.312 12V/1A £3.75*

SS.318 18V/1A £4.15*

SS.324 24V/1A £4.60*

SS.334 34V/2A £5.20*

SS.345 45V/2A £6.25*

SS.350 50V/2A £6.75*

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built-in protection against short circuit (p/p 35p) £3.25



SS.310/50
Stabilised power supply with variable output from 10 to 50V/2A. Built-in protection against short circuit.

£11.95*

WHEN ORDERING

Add 35p for p/p unless stated otherwise. V.A.T. add 12½% to total value of order unless price is shown when the rate is 8%. Make cheques, etc., payable to Bi-Pre-Pak Ltd. Every effort is made to ensure correctness of information at time of going to press. Prices subject to alteration without notice

★ THE BUILT-IN QV FACTOR

means Stirling Sound's guarantee of QUALITY AND VALUE to give you today's best value all round.

Stirling Sound

A member of the BI-PRE-PAK group of companies

220-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF

Telephone: Southend (0702) 46344

PERSONAL CALLERS WELCOME

Unique full-function 8-digit wrist calculator... available only as a kit.

A wrist calculator is the ultimate in common-sense portable calculating power. Even a pocket calculator goes where your pocket goes - take your jacket off, and you're lost!

But a wrist-calculator is only worth having if it offers a genuinely comprehensive range of functions, with a full-size 8-digit display.

This one does. What's more, because it is a kit, supplied direct from the manufacturer, it costs only a very reasonable £9.95 (plus 8% VAT, P&P). And for that, you get not only a high-calibre calculator, but the fascination of building it yourself.

How to make 10 keys do the work of 27


The Sinclair Instrument wrist calculator offers the full range of arithmetic functions. It uses normal algebraic logic ('enter it as you write it'). But in addition, it offers a % key; plus the convenience functions \sqrt{x} , $1/x$, x^2 ; plus a full 5-function memory.

All this, from just 10 keys! The secret? An ingenious, simple three-position switch. It works like this.



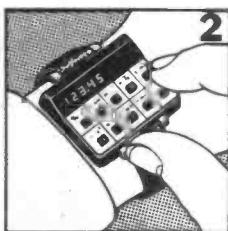1. The switch in its normal, central position. With the switch centred, numbers - which make up the vast majority of key-strokes - are tapped in the normal way
2. Hold the switch to the left to use the functions to the left above the keys...
3. and hold it to the right to use the functions to the right above the keys.

The display uses 8 full-size red LED digits, and the calculator runs on readily-available hearing-aid batteries to give weeks of normal use.



KIT
ONLY
£9.95
PLUS VAT,
P&P

Sinclair Instrument Ltd,
6 Kings Parade, Cambridge,
Cambs., CB2 1SN.
Tel: Cambridge (0223) 311488.

Assembling the Sinclair Instrument wrist calculator

The wrist calculator kit comes to you complete and ready for assembly. All you need is a reasonable degree of skill with a fine-point soldering iron. It takes about three hours to assemble. If anything goes wrong, Sinclair Instrument will replace any damaged components free: we want you to enjoy assembling the kit, and to end up with a valuable and useful calculator.



Contents
Case and display window.
Strap.
Printed circuit board.
Switches.
Special direct-drive chip (no interface chip needed).
Display.
Batteries.

Everything is packaged in a neat plastic box, and is accompanied by full instructions. The only thing you need is a fine-point soldering iron.

All components are fully guaranteed, and any which are damaged during assembly will be replaced free.

The wrist-calculator kit is available only direct from Sinclair Instrument. Take advantage of this 10-day money-back undertaking.

Send the coupon today.

To: Sinclair Instrument Ltd,
6 Kings Parade, Cambridge, Cambs., CB2 1SN.

* Please send me ... (qty) Sinclair Instrument wrist-calculator kits at £9.95 plus 80p VAT plus 25p P&P (Total £11).

* I enclose cheque/PO/money order for £

* Complete as applicable.

Name
Address
.....

(Please print)
I understand that you will refund my money in full if I return the kit undamaged within 10 days of receipt.

EE/1

PAKS-PARTS-AUDIO MODULES

PANEL METERS

4" RANGE

Size 4" x 3½" x 1½"

Value	No.	Price
0-50UA	1302	£4-50
0-100UA	1303	£4-50
0-500UA	1304	£4-50
0-1MA	1305	£6-00
0-50V	1306	£6-00

2" RANGE

Size 2" x 1½" x 1½"

Value	No.	Price
0-50UA	1307	£3-50
0-100UA	1308	£3-50
0-500UA	1309	£3-50
0-1MA	1310	£3-50
0-50V	1311	£3-50

MR2P TYPE

Size 42 x 42 x 30mm

Value	No.	Price
0-50UA	1313	£4-80
0-1MA	1315	£3-20

EDGEWISE

Size 3½" x 1½" x 2½"

Cut out 2½" x 1½"

Value	No.	Price
0-1MA	1316	£4-05
0-500UA	1317	£4-05

MINIATURE BALANCE/TUNING METER

Size 23 x 22 x 26mm

Sensitivity 100/0/100MA

No.	Price
1318	£1-95

BALANCE/TUNING

Size 45 x 22 x 34mm

Sensitivity 100/0/100UA

No.	Price
1319	£2-00

MIN. LEVEL METER

Size 23 x 22 x 26mm

Sensitivity 200UA

No.	Price
1320	£1-95

VU METER

Size 40 x 40 x 29mm

Sensitivity 130UA

No.	Price
1321	£2-00

MINI MULTI-METER

Size 60 x 24 x 90mm

Sensitivity 1000 ohms/V

AC VOLTS 0-10, 50, 250, 1000

DC VOLTS 0-10, 50, 250, 1000

DC CURRENT 0-1-100mA

Resistance 0-150K ohms

No.	Price
1322	£5-95

P&P

Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.

PAKS-PARTS-AUDIO MODULES

TRANSISTORS BRAND NEW — FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	0-16	BC109B	0-08	BC550	0-14	BFX90	0-55	TIP42B	0-78	2N3707	*0-08		
AC127	0-14	BC109C	0-08	BC556	0-14	BFY50	0-14	TIP42C	0-95	2N3708	*0-07		
AC128	0-12	BC147	0-09	BC557	0-13	BFY51	0-14	TIP2955	0-95	2N3708A	*0-07		
AC128K	0-26	BC148	0-09	BC558	0-12	BFY52	0-14	TIP3055	0-75	2N3709	*0-07		
AC132	0-15	BC149	0-12	BD115	0-50	BIP19	0-38	TIS43	0-22	2N3710	*0-07		
AC134	0-15	BC157	0-12	BD116	0-80	BIP20	0-38	TIS90	0-18	2N3711	*0-07		
AC137	0-15	BC158	0-12	BD121	0-65	2N3819	0-20	UT46	0-20	2N3819	0-20		
AC141	0-18	BC159	0-12	BD123	0-65	BRD29	0-45	ZTX107	0-10	2N3820	0-40		
AC142	0-12	BC160	0-12	BD124	0-70	BU105	1-90	ZTX108	0-10	2N3821	0-40		
AC145	0-12	BC169	0-12	BD131	0-35	BU105/02	1-95	ZTX300	0-12	2N3823	0-40		
AC176	0-26	BC170C	0-12	BD132	0-38	BU205	1-70	ZTX500	0-14	2N4059	0-14		
AC178	0-25	BC171	0-10	132 MP	0-80	BU208	2-40	ZT111	0-20	2N4061	0-12		
AC180	0-20	BC172	0-10	BD133	0-60	BU208/02	2-95	ZT118	0-18	2N4062	0-12		
AC180K	0-30	BC173	0-12	BD135	0-34	E122	0-38	ZT119	0-18	2N4090	0-18		
AC181	0-20	BC177	0-16	BD135	0-36	MJE2955	0-88	ZT120	0-30	2N4285	0-18		
AC181K	0-30	BC178	0-16	BD137	0-38	MJE3055	0-60	ZT121	0-75	2N4286	0-18		
AC187	0-16	BC179	0-16	BD138	0-45	MJE3440	0-45	ZT124	0-70	2N4287	0-18		
AC187K	0-26	BC180	0-25	BD139	0-54	MPE813	0-45	ZT125	0-60	2N4288	0-18		
AC188	0-16	BC181	0-25	BD140	0-60	MPE102	0-35	ZT126	0-38	2N4289	0-18		
AD140	0-60	BC183	0-10	140 MP	1-20	MPE105	0-39	ZT127	0-38	2N4291	0-18		
AD142	0-85	BC183L	0-10	BD155	0-80	MPSA05	0-20	ZT128	0-22	2N4292	0-18		
AD143	0-75	BC184	0-10	BD175	0-60	MPSA06	0-20	ZT129	0-22	2N4293	0-18		
AD149	0-60	BC184L	0-10	BD176	0-60	MPSA55	0-20	ZT129A	0-20	2N4923	0-65		
AD161	0-35	BC207	0-11	BD177	0-68	OC22	1-50	ZT129B	0-24	2N5135	*0-10		
AD162	0-36	BC208	0-11	BD178	0-68	OC23	1-50	ZT129C	0-18	2N5136	*0-10		
AF114	0-20	BC212	0-20	BD201	0-40	OC4	1-40	ZT129D	0-20	2N5138	*0-10		
AF115	0-20	BC212L	0-20	BD202	0-40	OC5	1-25	ZT129E	0-20	2N5139	*0-10		
AF116	0-20	BC213	0-11	BD203	0-80	OC6	1-60	ZT129F	0-18	2N5205	0-28		
AF117	0-20	BC213L	0-11	BD204	0-80	OC8	0-90	ZT129G	0-16	2N5294	0-34		
AF118	0-48	BC214	0-12	BD203/	0-20	OC9	1-00	ZT129H	0-19	2N5296	0-35		
AF124	0-30	BC214L	0-12	BD204	0-20	OC35	0-90	ZT129I	0-20	2N5457	0-32		
AF125	0-30	BC237	0-16	BDY20	0-80	OC36	0-90	ZT129J	0-22	2N5458	0-32		
AF126	0-30	BC238	0-16	BDXT7	0-90	OC70	0-15	ZT129K	0-22	2N5459	0-38		
AF127	0-32	BC251	0-15	BDXT7	0-90	OC71	0-15	ZT129L	0-20	2N5551	*0-30		
AF139	0-58	BC251A	0-16	BF457	0-37	TIC44	0-25	ZT129M	0-08	2N6027	0-32		
AF180	0-58	BC301	0-30	BF458	0-37	TIC45	0-25	ZT129N	0-08	2N6121	0-70		
AF181	0-58	BC302	0-32	BF459	0-38	TIP29A	0-44	ZT129O	0-08	2N6122	0-70		
AF186	0-58	BC304	0-38	BF594	0-15	TIP29B	0-52	ZT129P	0-16	2N3053	0-16	0-36	
AF239	0-38	BC327	0-16	BF595	0-17	TIP30A	0-50	ZT129Q	0-16	2N3055	0-16	0-58	
AL102	0-95	BC328	0-15	BF597	0-25	TIP30B	0-60	ZT129R	0-16	2N3414	0-16	0-36	
AL103	0-95	BC337	0-15	BF598	0-25	TIP30C	0-70	ZT129S	0-16	2N3415	0-16	0-36	
AU104	1-00	BC410	0-23	BF79	0-28	TIP31A	0-54	ZT129T	0-16	2N3416	0-20	0-45	
AU110	1-00	BC441	0-27	BF80	0-28	TIP31B	0-35	ZT129U	0-29	2N3417	0-42	0-42	
AU113	1-00	BC460	0-38	BF28X	0-25	TIP32A	0-64	ZT129V	0-08	2N3616	0-90	0-55	
BC107A	0-08	BC477	0-20	BFX84	0-23	TIP32C	0-80	ZT129W	0-09	2N3646	0-90	0-36	
BC107C	0-08	BC478	0-19	BFX85	0-24	TIP41A	0-66	ZT129X	0-08	2N3702	0-08	0-38	
BC108A	0-08	BC479	0-20	BFX86	0-25	TIP41B	0-70	ZT129Y	0-07	2N3704	0-07	0-40	
BC108B	0-08	BC547	0-12	BFX87	0-22	TIP41C	0-80	ZT129Z	0-07	2N3705	0-07	0-48	
BC108C	0-08	BC548	0-12	BFX88	0-22	TIP42A	0-72	ZT129AA	0-08	2N3706	0-08	0-40	

LINEAR IC'S

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
CA3011	* 0-80	LM309K	1-75 MC1469R	2-50	TA711C	* 32 ZT2748	0-35	TA621A	* 2-00				
CA3014	* 1-37	LM320-5V	2-00 MC1496Z	0-90	ZT2711	* 32 ZT48P	0-35	TA661A	* 1-50				
CA3018	* 0-70	LM320-12V	2-00 NE533A	2-00	ZT2723	0-50 SN76023	* 1-40	TA100D	* 1-30				
CA3020	* 1-40	LM320-15V	2-00 NE535A	2-00	ZT2723	0-50 SN76023	* 1-40	TA5400	* 2-50				
CA3028A	* 1-10	LM320-24V	2-00 NE540	2-40	ZT2741	0-20 SN76110	* 1-50 TA641B	* 2-25					
CA3035	* 1-35	LM380N	* 1-00 NE556	2-00	ZT2741	0-20 SN76660	* 1-50 TA641B	* 2-25					
CA3042	* 1-15	LM381AN	* 0-63 NE561	2-35	ZT2747C	* 70 SL4030	* 75 TA9202	* 3-40					
CA3043	* 1-15	LM384P	* 1-45 NE562B	2-95	ZT2747	* 79 SL414A	* 75 TA9202	* 3-40					
CA3046	* 0-50	MC1303	* 1-45 NE565A	2-00	ZT2748	* 35 TAA550B	* 35 TCA2705	* 3-90					
CA3052	* 1-60	MC1304P	* 3-50 NE566	1-50									
CA3054	* 1-84	MC1310P	* 1-80 NE567	2-50									
CA3075	* 1-50	MC1312PQ	* 1-50 UA702C	0-46									
CA3081	* 1-50	MC1330	* 35 ZT2702	0-46									
CA3089	* 1-50	MC1339	* 1-50 UA703A	0-25					</				

SEMICONDUCTORS-COMPONENTS

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA129	0.08	BY100	0.16	BYZ11	0.31	OA91	0.07
AAY30	0.09	BY107	0.12	BYZ12	0.31	OA95	0.07
AAZ13	0.10	BY105	0.18	BYZ13	0.26	OA182	0.07
AZ17	0.10	BY114	0.12	BYZ15	0.41	OA200	0.08
BA100	0.10	BY124	0.12	BYZ17	0.36	OA202	0.08
BA102	0.32	BY125	0.13	BYZ18	0.35	SD10	0.06
BA115	0.15	BY127	0.16	BYZ19	0.35	SD19	0.06
BA154	0.12	BY128	0.16	OA10	0.35	IN34	0.07
BA155	0.14	BY130	0.17	OA47	0.07	IN34A	0.07
BA156	0.14	BY133	0.21	OA70	0.07	IN914	0.06
BA173	0.15	BY154	0.51	QA9	0.07	IN916	0.06
BB104	0.15	BY176	0.75	OA81	0.07	IN4148	0.06
BAX13	0.07	BY206	0.00	OA85	0.09	IS44	0.05
BAX16	0.08	BYZ10	0.36	OA90	0.07	IN920	0.06

SILICON RECTIFIERS

Type	Price	Type	Price	Type	Price	Type	Price
IS920	0.06	IN4003	0.07	ISO20	0.10	ISO31	0.25
IS921	0.07	IN4004	0.08	ISO21	0.11	IN5400	0.13
IS922	0.08	IN4005	0.09	ISO23	0.13	IN5401	0.15
IS923	0.09	IN4006	0.10	ISO25	0.14	IN5402	0.16
IS924	0.10	IN4007	0.11	ISO27	0.16	IN5404	0.17
IN4001	0.05			ISO29	0.20	IN5406	0.21
IN4002	0.06					IN5407	0.25

TRIACS

2 Amp.	T05	Case	10 Amp.	TO48	Case
Volts	No.	Price	Volts	No.	Price
100	TR12A/100	0.31	100	TR110A/100	0.77
200	TR12A/200	0.51	200	TR110A/200	0.92
400	TR12A/400	0.71	400	TR110A/400	1.12
6 Amp.	TO66	Case	10 Amp.	TO220	Case
Volts	No.	Price	Volts	No.	Price
100	TR16A/100	0.51	400	TR110A/400P	1.12
200	TR16A/200	0.61			
400	TR16A/400	0.77	BR100	0.23	D32

THYRISTORS

600mA	TO18	Case	7 Amp	TO48	Case
Volts	No.	Price	Volts	No.	Price
10	THY600/10	0.13	50	THY7A/50	0.48
20	THY600/20	0.13	100	THY7A/100	0.51
30	THY600/30	0.19	200	THY7A/200	0.57
50	THY600/50	0.22	400	THY7A/400	0.62
100	THY600/100	0.25	600	THY7A/600	0.78
200	THY600/200	0.38	800	THY7A/800	0.92
400	THY600/400	0.45			

1 Amp	T05	Case	10 Amp	TO48	Case
Volts	No.	Price	Volts	No.	Price
50	THY1/50	0.25	100	THY1A/100	0.57
100	THY1A/100	0.27	200	THY1A/200	0.62
200	THY1A/200	0.28	400	THY1A/400	0.71
400	THY1A/400	0.36	600	THY1A/600	0.86
600	THY1A/600	0.45	800	THY1A/800	0.98
800	THY1A/800	0.58			

3 Amp	TO66	Case	10 Amp	TO48	Case
Volts	No.	Price	Volts	No.	Price
50	THY3A/50	0.25	100	THY15A/100	0.58
100	THY3A/100	0.27	200	THY15A/200	0.62
200	THY3A/200	0.33	400	THY15A/400	0.77
400	THY3A/400	0.42	600	THY15A/600	0.90
600	THY3A/600	0.50	800	THY15A/800	1.39
800	THY3A/800	0.65			

5 Amp	TO66	Case	10 Amp	TO48	Case
Volts	No.	Price	Volts	No.	Price
50	THY5A/50	0.30	100	THY30A/100	1.43
200	THY5A/200	0.50	200	THY30A/200	1.63
400	THY5A/400	0.57	400	THY30A/400	1.79
600	THY5A/600	0.69	600	THY30A/600	3.50
800	THY5A/800	0.81			

5 Amp	TO220	Case	10 Amp	TO48	Case
Volts	No.	Price	Volts	No.	Price
400	THY5A/400P	0.57	2N3282	0.77	
600	THY5A/600P	0.69	BTX30/50L	0.33	
800	THY5A/800P	0.81	BT106	1.25	
			BT107	0.93	
			BT108	0.98	
			BT102/500R	0.70	
			BT102/500R	0.80	
			BTX30/400L	0.46	
			C106/4	0.80	

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER.

VAT

ADD 12½% TO PRICES MARKED *
ADD 8% TO OTHERS EXCEPTING THOSE
MARKED † THESE ARE ZERO RATED

SUPER UNTESTED PAKS

Pak No.	Description	Order No.	Price
U50	100 Germ. Gold bonded OA47 diode	16130	0.50
U51	100 Germ. OA70/81 diode	16131	0.60
U52	100 Silicon Diodes 200mA OA200	16132	0.60
U53	150 diodes 75mA 1N4148	16133	0.60
U54	50 Sili Top Hat 750mA	16134	0.60
U55	20 Sili Rect Stud Type 3 Amp	16135	0.60
U56	30 NPN Trans BC107/8 Plastic	16136	0.60
U57	30 PNP Trans BC117/8 Plastic	16137	0.60
U58	25 PNPN TO39 2N2905 silicon	16138	0.60
U59	25 PNPN TO39 2N6567/2N171 silicon	16139	0.60
U60	25 PNPN TO59 2N2905 silicon	16140	0.60
U61	30 NPN TO18 2N703 silicon	16141	0.60
U62	25 PNPN 2N50V/51	16142	0.60
U63	30 NPN Plastic 2N3906 silicon	16143	0.60
U64	30 PNP Plastic 2N3905 silicon	16144	0.60
U65	30 Germ. 0071 PNP	16145	0.60
U66	15 Plastic Power 2N3055 NPN	16146	1.20
U67	10 TO3 Metal 2N3055 NPN	16147	1.20
U68	20 Transistor 2N3055 NPN	16148	1.20
U69	10 lamp SCR TO39	16149	1.20
U70	8 3 amo SCR TO66 case	16150	1.20

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

COMPONENT PAKS

Pack No.	Qty.	Order No.	Price	
C1	200	Resistor mixed value approx. (Count by weight)	16164	*0.60
C2	150	Capacitors mixed value approx. (Count by weight)	16165	*0.60
C3	50	Precision resistors. Mixed values	16166	0.60
C4	80	10W resistors mixed preferred values	16167	*0.60
C5	5	Plates associated ferrite rods	16168	*0.60
C6	2	Tuning capacitors MW/1W VHF	16169	*0.60
C7	1	Pack wire 50 meters assorted colours single strand	16170	0.60
C8	10	Reed switches	16171	*0.60
C9	3	Micro switches	16172	*0.60
C10	15	Assorted pots.	16173	*0.60
C11	5	Metal jack sockets 3 x 3.5mm 2 x standard switch types	16174	*0.60
C12	30	Paper condensers mixed types	16175	*0.60
C13	20	Electrolytics trans. types	16176	*0.60
C14	1	Pack assorted hardware— Nuts/bolts, gromets etc.	16177	0.60
C15	5	Mains slide switches ass.	16178	*0.60
C16	20	Assorted tag strips and panels	16179	*0.60
C17	15	Assorted control knobs	16180	*0.60
C18	4	Relay 2 position change switches	16181	*0.60
C19	2	Relay 6-24 operating	16182	*0.60
C20	1	Pack copper laminate approx. 200 sq ins	16183	0.60
C21	15	Assorted fuses 100mA—5 amp.	16184	*0.60
C22	50	Metres PVC sleeving assorted size and colour	16185	0.60
C23	60	1 watt resistors mixed preferred values	16186	*0.60
C24	25	Presets assorted type and value colours	16187	*0.60

CERAMIC PAKS

Pack No.	Qty.	Order No.	Price	
MC1	24	miniature ceramic capacitors, 3 of each value—20pf, 27pf, 33pf, 39pf, 47pf, 63pf, 82pf,	16160	*0.60
MC2	24	miniature ceramic capacitors 3 of each value—100pf, 120pf, 150pf, 180pf, 220pf, 330pf & 390pf, 270pf,	16161	*0.60
MC3	24	miniature ceramic capacitors 3 of each value—470pf, 560pf, 680pf, 820pf, 1000pf, 1200pf, 1500pf & 3300pf	16162	*0.60
MC4	21	miniature ceramic capacitors, 3 of each value—4700pf, 6800pf, .01uf, .015uf, .03uf & .047uf, .022uf	16163	*0.60

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

126 pages packed with valuable
information

ORDER NOW

ONLY 50p plus 15p p & p

LINEAR PAKS

Manufacturers "Fall Outs" which include
Functional and part Functional Units.
These are classed as "out-of-spec" from
the maker's very rigid specifications, but
are ideal for learning about I.C.'s and
experimental work.

U721 36 Assorted Linear Types 709-
741-747-748-710-581 Etc.

ORDER No. 16227 Price £1.50*

U765 FM STEREO DECODER
S.I.C.'s 76110 Equ. to MC1310P-MA767.

Data supplied with pak.

ORDER No. 16228 Price £1.50*

U768 AUDIO POWER OUTPUT
8 Assorted types. SL403 76013, 76003

Etc. Data supplied with Pak.

ORDER No. 16229 Price £1.00*

74 SERIES PAKS

Manufacturers "Fall Outs" which include
Functional and part Functional Units.

These are classed as "out-of-spec" from
the maker's very rigid specifications, but
are ideal for learning about I.C.'s and
experimental work.

74G 100 Gates assorted 7400-01-04-18

50-60 etc.

ORDER No. 16224 Price £1.20*

74F 50 Flip-Flops assorted

740-72-73-74-104-109 Etc.

ORDER No. 16225 Price £1.20*

74M 30 MSI. Assorted Types.

7441-47-90-

Get a great deal from Marshall's

A. Marshall (London) Ltd Dept: EE

40-42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2 Telex: 21492
& 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133
& 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272-654201/2
& 27 Rue Danton Issy Les Moulineaux Paris 92

168 page Catalogue price 55p

(40p to callers)

Please enquire for types not listed

WE ARE NOW AT NEWCASTLE-ON-TYNE!

Marshall Aitken Ltd., 35 High Bridge, Newcastle-on-Tyne
Tel: 0632 2679


		POPULAR SEMICONDUCTORS									
CA3020A	£1.45	CD4050	56p	NES56	£1.30	SN7448	89p	SN74160	£1.20	25p	2N3906
CA3028A	85p	CD4510	£1.54	NE560	£4.48	SN7450	21p	SN74161	£1.20	16p	2N4058
CA3035	£1.35	CD4511	£1.54	NE565	£1.30	SN7451	21p	SN74162	£1.20	55p	2N4062
CA3046	73p	CD4516	£1.54	SL414A	£2.35	SN7453	21p	SN74163	£1.20	21p	2N4921
CA3048	£1.15	CD4518	£1.38	SL610C	£2.35	SN7454	21p	SN74164	98p	21p	2N5245
CA3052	£1.62	CD4520	£1.38	SL611C	£2.35	SN7460	21p	SN74165	69p	21p	2N5294
CA3089E	£2.00	LM301AH	47p	SL612C	£2.35	SN7470	35p	SN74167	£2.20	21p	2N1023
CA3090Q	£4.25	LM308N	£1.17	SL620C	£3.50	SN7472	29p	SN74174	98p	21p	2N1062
CD4000	20p	LM309N	£1.80	SL621C	£3.50	SN7473	33p	SN74175	98p	21p	2N1062
CD4001	20p	LM380	98p	SL623C	£5.73	SN7474	33p	SN74176	98p	21p	2N148
CD4002	20p	LM381AN	£2.07	SL640C	£4.00	SN7475	46p	SN74180	£2.96	21p	2N218A
CD4006	£1.16	LM702C	57p	SN7400	21p	SN7476	55p	SN74181	£2.85	21p	2N219A
CD4007	20p	LM709	57p	SN7401	21p	SN7480	55p	SN74180	£1.48	21p	2N220
CD4008	97p	TO99	40p	SN7402	21p	SN7481	55p	SN74181	£1.27	21p	2N221
CD4009	57p	BDIL	40p	SN7403	21p	SN7482	72p	SN74182	£1.27	21p	2N222
CD4010	57p	BDIL	40p	SN7404	26p	SN7483	£1.00	SN74183	£1.27	21p	2N2369
CD4011	20p	LM710	45p	SN7405	26p	SN7484	£1.00	SN74184	£1.61	21p	2N2464
CD4012	20p	LM723C	60p	SN7406	59p	SN7485	£1.48	SN74187	90p	21p	2N2905
CD4013	59p	LM741C	59p	SN7407	59p	SN7486	32p	SN74188	90p	21p	2N2906
CD4014	£1.01	TO99	38p	SN7408	22p	SN7489	49p	SN74199	£2.28	21p	2N2907
CD4015	£1.01	BDIL	38p	SN7409	22p	SN7491	77p	SN76003N	21p	21p	2N2956G
CD4016	56p	14DL	40p	SN7410	21p	SN7492	49p	SN76003N	£2.28	13p	40594
CD4017	£1.40	LM747C	78p	SN7412	21p	SN7493	49p	SN76013N	21p	21p	40595
CD4018	£1.01	LM748	78p	SN7413	51p	SN7494	85p	SN76013N	£1.90	21p	2N3054
CD4019	£1.51	BDIL	44p	SN7416	46p	SN7495	61p	SN76023N	21p	65p	40636
CD4020	£1.56	14DL	41p	SN7417	46p	SN7496	88p	SN76023N	£1.91	21p	2N3391
CD4021	£1.01	LM3900N	55p	SN7420	21p	SN74100	£1.23	SN76033N	21p	21p	2N3393
CD4022	£1.63	LM7805P	£1.39	SN7423	30p	SN74107	33p	£2.50	21p	21p	2N3440
CD4023	20p	LM7812P	£1.39	SN7425	30p	SN74118	99p	TAA263	£1.25	21p	2N3442
CD4024	79p	LM7815P	£1.39	SN7427	30p	SN74119	£2.02	TAA300	£2.67	21p	2N3638
CD4025	20p	LM7824P	£1.39	SN7430	21p	SN74121	39p	TAA350A	£2.48	21p	2N3702
CD4027	56p	MCI303P	£1.09	SN7431	30p	SN74122	34p	TAA550	40p	15p	AC187K
CD4028	91p	MCI304P	£1.09	SN7432	42p	SN74123	42p	TAA550	£2.15	21p	370703
CD4029	£1.01	MCI320P	92p	SN7438	30p	SN74141	80p	TAA621	£2.15	14p	AC161
CD4030	57p	MCI351P	97p	SN7440	21p	SN74145	83p	TAA661C	£2.15	21p	3716
CD4031	£2.26	MCI453A	£3.00	SN7441	80p	SN74150	£1.66	TAA641B	£2.50	21p	40512
CD4037	97p	MCI466L	£4.59	SN7442	61p	SN74151	85p	TBA651	£1.80	21p	37789
CD4041	83p	MCI469B	£9.00	SN7446	96p	SN74153	95p	TBA800	£1.19	21p	37819
CD4049	56p	NE555Y	48p	SN7447	89p	SN74154	£1.48	TBA810	£1.28	21p	3904
				SN74157	78p	TBA820	£1.00				

SEND FOR OUR NEW 168 PAGE CATALOGUE WITH 500 NEW LINES—ONLY 55p POST, PAID OR 40p TO CALLERS.

PRICES CORRECT AT 19 NOVEMBER 1976, BUT PLEASE ADD VAT. P. & P. 30p.

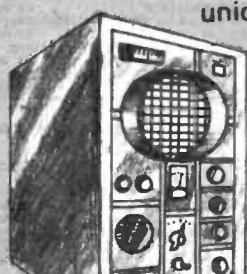I. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

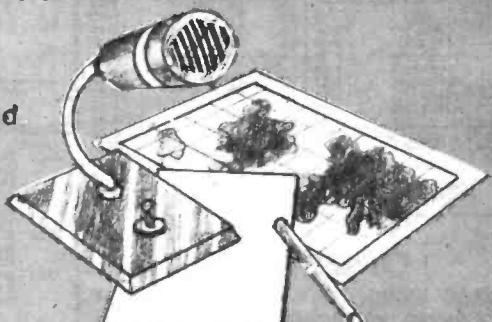2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

EEC 17

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

RETURN OF POST MAIL-ORDER SERVICE

R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE CHASSIS



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details. Suitable carrying cabinet £14. Price £85 Carr. £2.60

ANOTHER R.C.S. BARGAIN !

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.

Price £3.25 Post 40p



8" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 80-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts. Post 40p £4.45

TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in.
For 12 in. dia. or £13.50 Post 95p
10in. speaker. Illustrated

MODEL "B".
For 13 x 8in. £7.50 Post 75p
8 in. speaker

R.C.S. ROSEWOOD
SPEAKERS

Size 12in. x 9in. 5in.
Response 50 to 14,000 cps.
8 watts rms 3 or 8 or 18 ohms.
£12 pair Post 75p

LOUDSPEAKER CABINET
WADDING 18in. wide, 20p It.



GOODMANS CONE TWEETER

3in. diam. 18,000 C.P.S. 25 WATTS 8Ω £3.25
8 inch woofer 15 watts 20.75.



BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights to your sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. £5.75

STEREO VERSION OF ABOVE £7.50.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply £2.85.



THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. Leaflet S.A.E. £4.25 Post 40p

WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10¹/₂ x 8¹/₂ x 1in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely providing safe Black heat. British-made for use in photocopies and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc. to make efficient clothes dryer, towel rails—ideal for airing cupboards. Ideal anti-frost device for the garage—preventing frozen radiators. As is our own heater. Use in greenhouse for seed raising and plant protection. invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

RADIO COMPONENT SPECIALISTS

Minimum post 30p. Components Lists 10p.

BAKER MAJOR 12" £14.95



Post £1

30-14,500 c/s, 12in. double cone, woofers and tweeter cones together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £18.95

Please state 3 or 8 or 15 ohms. Post £1.60

BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

GROUP "25"

12in. 30 watt
3 or 8 or 15 ohms.

£11.95

Post £1

GROUP "35"

12in. 40 watt
3 or 8 or 15 ohms.

£13.95

Post £1

GROUP "50/12"

12in. 60 watt professional model. 8 ohms or 16 ohms. With aluminium presence dome. Post £1.60

£20.95

Post £1.60

GROUP "50/15"

15in. 75 watt
8 or 15 ohms.

£24.95

Post £1.60

BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER

Professional amplifier using advanced circuit design. Ideal for local groups, P.A., musical instruments. 4 inputs 4 way mixing. Master tone, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers. 4 to 18 ohms. Slave output. A/C mains. Guaranteed. Details S.A.E. 150w SLAVE £60

Latest 50 watt Model £49



£68 Carr. £1.00

100 WATT DISCO AMPLIFIER CHASSIS

MADE BY JENNINGS MUSICAL INSTRUMENTS 4 speaker outputs, vol., treble, bass controls. CAN BE USED AS 100WATT SLAVE

£52 Carr. £1

B.S.R. SINGLE PLAYER DECK

3 speed. Plays all size records. Stereo Cartridge. Cueing. Ideal Disco Deck. Post 75p £13.50

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered fin thick wood cabinet. Size 18in. x 18in. x 8in. Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 8in. Woofer. £5.95. Rosewood Version £6.95. Carr. £1.60. Baffle could be cut for larger speaker.



P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 800 to 1,000 watts each. As featured in Practical Wireless. Cabinet extra £3. Price £12.50

8 inch PHILIPS LOUDSPEAKER

4 ohm. 4 watt ceramic magnet General purpose replacement unit.

£1.95

MAINS TRANSFORMERS

6 VOLT 1 AMP. £1.00 3 AMP. £1.40
12 VOLT 300 MA. £1.00 750 MA. £1.30
30 VOLT 5AMP. and 34 VOLT 2AMP. G.T. £3.45
20 VOLT 1 AMP. £1.75 1 AMP. £2.00 2 AMP. £2.20
20-0-20 VOLT 1 AMP. £2.30 30 VOLT 1 AMP. £1.75
40 VOLT 2 AMP. £2.95. 0-20-40-80 VOLT 1 AMP. £3.50

Post 50p

E.M.I. TAPE MOTOR

4 pole, 240 v. Size 3¹/₂ x 2¹/₂in. 1200 rpm. Spindle 7/16 in. dia. 75v version £1.

£1.85

E.M.I. GRAM MOTOR

240V a.c. 2,400 rpm 2-pole. Size 2¹/₂ x 2¹/₂in. Collar gram motor 120v. 75p.

£1.25

Post 35p

BAKER DISCO SPEAKERS HIGH QUALITY-BRITISH MADE

2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black finish. Other cabinets in stock. SAE for leaflet

50

WATT

R.M.S.

£50

Carr. £8

70

WATT

R.M.S.

£55

Carr. £8

100

WATT

R.M.S.

£69

Carr. £8



1x 15" + 1x 12" 100 WATT CABINET

Size 36" x 24" x 15" £75.00. Carr. £5

Ideal for Disco, Organ or PA work.

Full range.

"SUPERB HI-FI"

12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass.

Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps

Flux Density 16,600 gauss

Useful response 20-17,000cps

8 or 15 ohms models.

£21.95 Post £1.60

"AUDITORIUM"

12in. 35 watts

A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for HI-FI and Discos.

Bass Resonance 35cps

Flux Density 15,000 gauss

Useful response 20-18,000cps

8 or 15 ohms models.

£20.95 Post £1.60

"AUDITORIUM"

15in. 45 watts

A high wattage loudspeaker of exceptional quality with a low resonance to give a wide 8,000 cps. Ideal for Public Address, Discos, Electronic instruments and the home HI-FI.

Bass Resonance 35cps

Flux Density 15,000 gauss

Useful response 20-14,000cps

8 or 15 ohms models.

£24.95 Post £1.60

Loudspeaker Cabinet Wadding 18in wide. 20p per It.

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p



Incredible Value in Precision Test Meters

AVAILABLE FROM SELECTED STOCKISTS. WRITE OR PHONE FOR LIST

MICROTEST 80—I.C.E. 20,000 Ohms/Volt 40 RANGES

20,000 Ohms/Volt, (d.c.) 4,000 Ohms/Volt (a.c.) 2% accuracy. V d.c. 100mV to 1kV (6 Ranges). I d.c. 50 μ A to 5A (6 Ranges). V a.c. 1.5V to 1kV (5 Ranges) I a.c. 250 μ A to 2.5A (5 Ranges). Resistance, Low Ohms, Ohms \times 1, Ohms \times 10, Ohms \times 100. Output Level Measurements 1.5V to 1000V (5 Ranges) + 6dB to + 62dB (5 Ranges). Capacitance 25 μ F to 25,000 μ F (4 Ranges). 1000 times overload protection (on Resistance ranges). Meter movement diode protection. Size (without case) 90 \times 70 \times 18mm. Automatic zero, non-parallax mirror scale. Unbreakable carrying case and probes supplied. Full After Sales Service available. Price £15.66 inc. VAT



The I.C.E. Measurement System includes a comprehensive range of accessories: shunts, transformers, specialised probes, transistor-tester etc. I.C.E. High-Voltage d.c. Probe, Model 18. Input Impedance: 500M Ohm, nominal (Other values available to order). The Model 18 d.c. Probe consists of a highly insulated moulded plastic body, fitted with a hand guard-ring, containing a stable, precision 500M Ohm resistor, which may be used to extend the d.c. voltage measuring capability of analogue multi-meters or electronic voltmeters, to a maximum value of 25kV. The probe is fitted with a prod-tip for connection to the voltage source to be measured and a connecting lead terminating in a 2mm plug for insertion into the measuring instrument's d.c. voltage input socket. (4mm plug available to order). £6.42 inc. VAT

Sole Importers
and Distributors


Electronic Brokers Ltd

49-53 Pancras Rd., London NW1 2QB. Tel: 01-837 7781

SUPER TESTER 680R—I.C.E.

20,000 Ohms/Volt 80 RANGES

20,000 Ohms/Volt 1% d.c. 4,000 Ohms/Volt a.c. 2% V d.c. 100mV to 2kV (13 ranges). V a.c. 2V to 2kV (11 ranges). I d.c. 50 μ A to 10A (12 ranges). I a.c. 250 μ A to 5A (10 ranges). Resistance Ohms \times 1, \times 100, \times 1,000, \times 10,000 and Low Ohms. Reactance Detector 0-10M Ohms. Freq. Measurement 0-5000 Hz (2 ranges). Output Level 10-2000V (9 ranges). Decibels -24-+70dB (10 ranges). Capacitance 0-500,000 pF (2 ranges using mains supply) 0-20,000 μ F (4 ranges using internal 3 Volt battery). 1000 times overload protection on Resistance ranges and meter movement diode protection. 10 Measurement Functions and 80 Ranges. Size 128 \times 95 \times 32mm. Non-parallax mirror scale. Unbreakable carrying case supplied which contains probes, mains lead, crocodile clips and shorting link. Price £24.30 inc. VAT

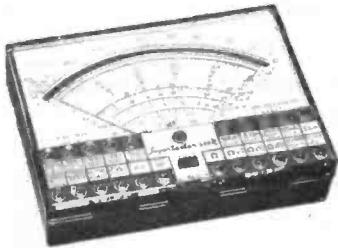

CALLING ALL SANTAS!

Of course, by 'Santas' I mean Dads, Grand-dads and Uncles who, at this time of the year, are often desperate for inspiration! Well, if your son, grandson or nephew is keen on electronics may I make a suggestion? Buy a Home Radio Catalogue. In it you will find dozens of wonderful presents. When you give him the present you have chosen you can double his pleasure by giving him the catalogue as well!

This is the one catalogue every electronic enthusiast must have. Its 200 pages are crammed with over 5,000 items, well over 1,000 of them illustrated. It's a present that will last for years, because it can be updated with new price lists, supplied free on request. With every catalogue comes a free bargain list—another worthwhile bonus. At the price of £1 plus 40p for postage and packing it's certainly wonderful value; so send off the coupon with a cheque or P.O. for £1.40... and become the Santa of the year!



A Happy
Christmas
to all our
readers

Please write your Name and Address in block capitals

NAME

ADDRESS



**POST
THIS
COUPON
with cheque
or P.O. for
£1.40**



(Regn. No.
London 912966)

HOME RADIO (Components) LTD., Dept. EE,
234-240 London Road, Mitcham, Surrey CR4 3HD

HOME RADIO (Components) LTD. Dept. EE., 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

Everyday Electronics, January 1977

Bring 'scope' to your interest.

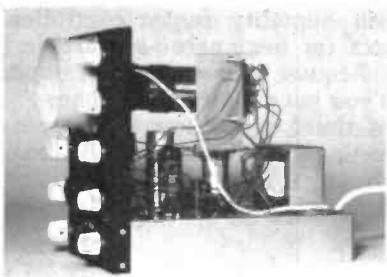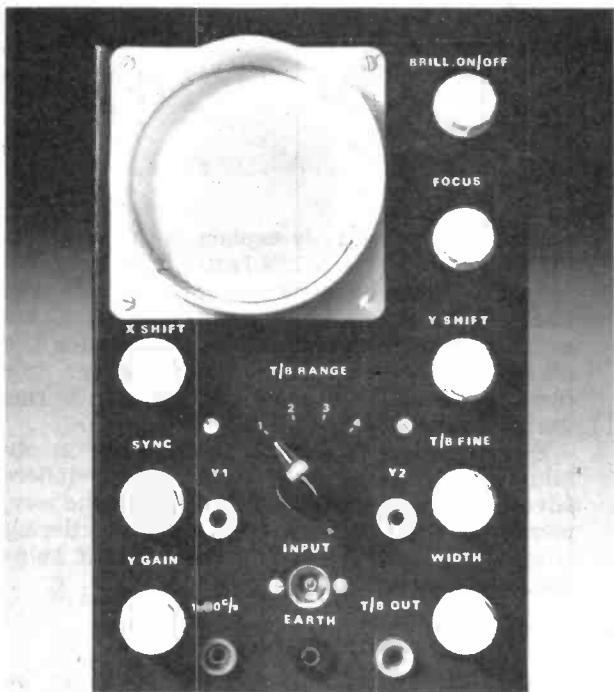

1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



**FREE
GIFT**



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

2 Read, draw and understand circuit diagrams.

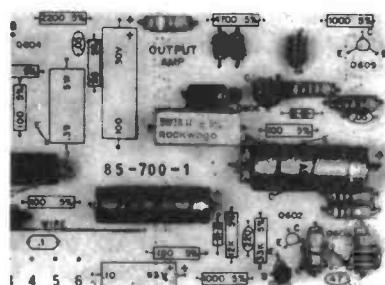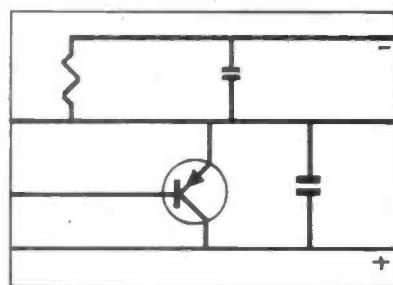In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.
Write to:- British National Radio & Electronics School,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

EEB 17

everyday electronics

PROJECTS.
THEORY....

JOINTS AND JQINTS

There is one immediate way to judge the quality of a constructor. Look at his or her joints—the soldered variety. They will speak volumes. But it is not only the external appearance—though this is important. The lustreless, messy and untidy kind of joint is likely to be unsound and unsatisfactory the whole way through—and that's just where it really counts.

No one should be frightened of soldering. Like most things, it requires knack, yet this can be easily acquired by a little patient practice. Soldering techniques have changed of course with the reduction of size of components. And rather more adroitness is demanded than in days of yore.

So those returning to the subject after some years absence as well as those approaching electronics for the first time will find themselves in need of guidance and advice on the art of soldering. A special illustrated feature awaits them within our pages this month.

If an iron has yet to be acquired our Special Offer for a soldering kit will meet this requirement perfectly.

MADE TO MEASURE

If a soldering iron is number one item, a multimeter is a hot contender for second place amongst those essential items to be purchased when taking up constructing. You can't make your own soldering iron, but you can make a

multi-tester, as we fully explain in this issue.

Incidentally, this *Multi-Tester* has been designed around components specified for the *Teach-In 76* experiments. So followers of that series will have already in their possession the majority of parts needed. These items can now find a permanent and most worthy home in this useful instrument.

Other readers will have no difficulty in obtaining all required components from retailers advertising in *Everyday Electronics*. By the way, please do mention this magazine when ordering from our advertisers. This helps them, it helps you, and it helps us.

HOME AND DRY

Someone's wife, or mum, is going to be pleased with our *Tumble Dryer Controller*. Just what the doctor ordered for those machines without a built-in humidity sensor/controller. (But not a project for beginners—see article.) Another Special Request and another example of how EE helps you keep up with the times.

And talking of times, right now it is opportune to send greetings to all our readers, from all of us at EE. Happy Christmas and may it be a brighter and more cheerful New Year.



Our February issue will be published on Friday, January 21
See page 35 for details.

EDITOR F. E. Bennett

• ASSISTANT EDITOR M. Kenward

• TECHNICAL EDITOR B. W. Terrell B.Sc.

ART EDITOR J. D. Pountney

• P. A. Loates

• K. A. Woodruff

ADVERTISEMENT MANAGER D. W. B. Tillear

• P. Mew

© IPC Magazines Limited 1977. Copyright in all drawings, photographs, and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduction or imitation in whole or part are expressly forbidden.

All reasonable precautions are taken by **EVERYDAY ELECTRONICS** to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

Editorial Department: Everyday Electronics, Fleetway House, Farringdon Street, London EC4 4AD. Phone 01-634 4452.

Advertisement Departments: Everyday Electronics Advertisements, Fleetway House, Farringdon Street, London EC4 4AD. Phone 01-634 4504. Everyday Electronics Classified Advertisements, Kings Reach Tower, Stamford St., London SE1 9LS.



...EASY TO CONSTRUCT ...SIMPLY EXPLAINED

VOL. 6 NO. 1

JANUARY 1977

CONSTRUCTIONAL PROJECTS

TUMBLE DRYER CONTROLLER	Turns off the dryer at preset dryness level	by A. J. Bassett	10
PHOTOCUBE RECEIVER	A m.w./f.m. receiver in an unusual case	by F. G. Rayer	15
MULTI-TESTER	Versatile test instrument	by A. P. Stephenson	28
BRAKE LIGHT WARNING DEVICE	For most modern cars	by T. R. de Vaux-Balbirnie	37

GENERAL FEATURES

EDITORIAL			8
PHYSICS IS FUN	Radio Resonance	by Derrick Daines	19
DOING IT DIGITALLY	Part 4 The J-K Flip Flop	by O. N. Bishop	20
READERS' LETTERS			22
FOR YOUR ENTERTAINMENT	Projector lamp protection and calculator batteries	by Adrian Hope	23
SOLDERING IN EASY STEPS			24
NOISE REDUCTION SYSTEMS	Part 4	by Adrian Hope	26
PLEASE TAKE NOTE			27
COUNTER INTELLIGENCE	A retailer's comments	by Paul Young	33
LET'S FIGURE IT OUT	Take the sting out of maths Part 2	by Phil Alcock	34
SPECIAL OFFER	Soldering kit		36
JACK PLUG AND FAMILY	Cartoon		39
PROFESSOR ERNEST EVERSURE	The Extraordinary Experiments of.	by Anthony J. Bassett	40
SHOP TALK	Component buying	by Mike Kenward	43
DOWN TO EARTH	Inductance Calculations—How To Avoid Them	by George Hylton	44

BACK NUMBERS, LETTERS AND BINDERS

We are unable to supply back copies of *Everyday Electronics* or reprints of articles and cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertising Manager, at the address shown opposite.

Binders for volumes 1 to 6 (state which) are available for £2.10, including postage, from Post Sales Department, Lavington House, 25 Lavington St., London SE1 0PF

New Year's Resolution

I will place a regular order for EE
with my newsagent.

Tumble Dryer CONTROLLER

By A.J. BASSETT

TUMBLE dryers have in recent years been steadily gaining in popularity as a washday aid in the home, but in many homes there is a tendency to allow the machine to continue working after the clothes are dry enough.

A reader has suggested a "humidity-sniffer" to be placed near to the outlet of the dryer, to sound an audible warning when the relative humidity of the effluent air falls to a predetermined level.

The author has taken this interesting suggestion a stage further with a design which will switch the tumble-dryer off when the effluent air becomes dry enough. By this prompt and direct action the device will save even more electricity than the "audible warning" version, which calls for a human response in order to be effective.

The prototype is furnished with a level control to allow adjustment of the humidity level at which switching off takes place, and by pressing a button the controller can be over-ridden for a short period to enable the tumble dryer to re-start.

The design for the controller described here employs mains and the mains neutral appears on the sensor, which must be placed in the air outlet of the machine. Therefore not only is it important that the unit is correctly constructed and earthed but it is also very important that the sensor is

enclosed in a suitable earthed housing and permanently mounted out of reach.


If any constructor is in doubt about any of the above points we would suggest that he leaves this design well alone and chooses instead the Audible Warning Device which is battery powered, more simple, cheaper and which will be published shortly.

SENSOR

The sensor consists of a piece of thin blotting paper or tissue paper soaked in sea water or a 3 per cent (approx.) solution of sea salt in distilled water or rainwater.

The sensor may be constructed

Fig. 1. Sensor construction and mounting.

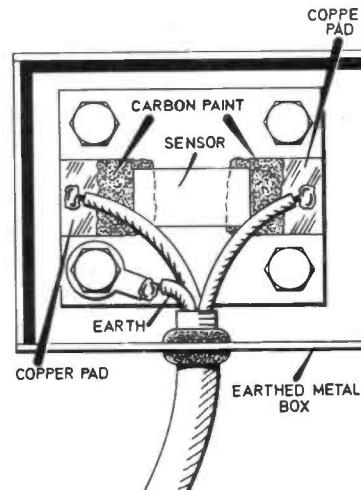


according to Fig. 1. It employs a piece of printed circuit board for mounting the sensor paper, with graphite conducting paint used to make the connections between copper and sensor, to avoid corrosion.

THE VERY IDEA

The idea for a Tumble Dryer Controller was proposed by Mr. C. P. Kidger of Wigan who receives our special award.



**FOR
GUIDANCE
ONLY**

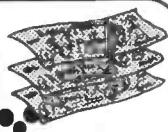

**ESTIMATED COST
OF COMPONENTS ***
excluding V.A.T.

**£12.00
excluding cases**

The special paint is made by mixing 1 part varnish, 2 parts thinners with powdered graphite taken, if necessary, from a very soft pencil. This forms a thin paste which when dried is a conductor.

CIRCUIT

When this type of humidity sensor is used we are measuring the electrical resistance of the electrolyte (salt water), and a d.c. measuring circuit would cause problems due to polarisation effects.

To overcome this problem the sensor is placed in a potential divider (R2, R3) which is placed across an a.c. voltage derived from the mains via C1 (Fig. 2). With variation in the resistance of the sensor the voltage across it will vary—rising as the sensor dries out—and this voltage is rectified, smoothed and its level is then sensed by TR1 to TR4 and

Fig. 2. Circuit diagram of the Tumble Dryer Control.

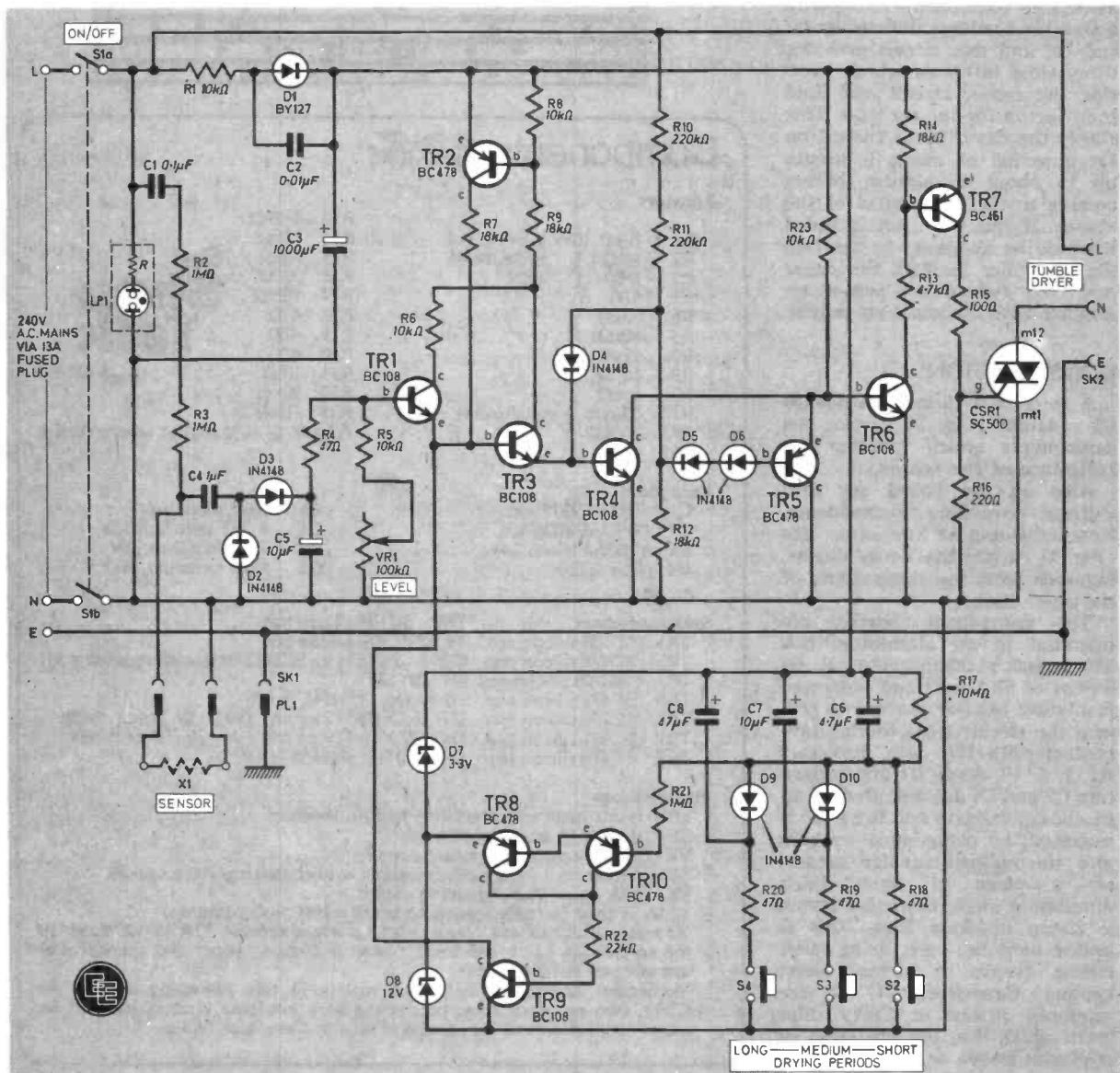


Fig. 3. Layout and wiring of the main circuit board.

used to prevent drive to a triac, when a certain point is reached, via TR6 and TR7. The triac supplies mains voltage to SK2 and hence the dryer. Potentiometer VR1 sets the turn off level.

The circuitry comprising TR5 and associated components is a zero voltage switch, which makes sure triggering of the triac occurs when the mains voltage is at or near zero, thus preventing r.f. radiation and interference problems.


The timing section of the circuit comprising TR8 to TR10 and associated components is fed with a stabilised voltage derived by D7 and D8 and this circuit provides three time intervals which override the sensor circuit and hold the triac on for the set time. This allows the dryer to be turned on for a period of about 1 minute up to about 5 minutes before coming under the control of the sensor. If this were not included it would be necessary to override the controller to start the dryer and thus reduce the sensor resistance with the moist air output.

CONSTRUCTION

A piece of 0.15 inch Veroboard 95 x 41mm (Fig. 3) carries the components which monitor the resistance of the sensor.

Also on the board are zero voltage - switching components. Another board of the same size (Fig. 4) carries the Zener diodes, together with the components of the timer circuit.

The component boards are mounted in an aluminium box 150 x 100 x 50mm (Fig. 5) by means of 6BA nuts and bolts and insulating tubular spacers to prevent the circuit from coming into contact with the case. Resistors R1, 2, 3, 10, diode D1 and capacitors C2 and C4 are mounted on an insulating tagstrip and the triac is mounted, by using mica washers and silicon heat-transfer grease, on a piece of 3mm thick aluminium angle extrusion 50mm x 25mm x 50mm long. This is bolted onto the case, using more silicon grease to further assist cooling. Capacitors C1, C3 are mounted firmly in Terry clips from which they are insulated by a plastic sleeve or p.v.c. tape.

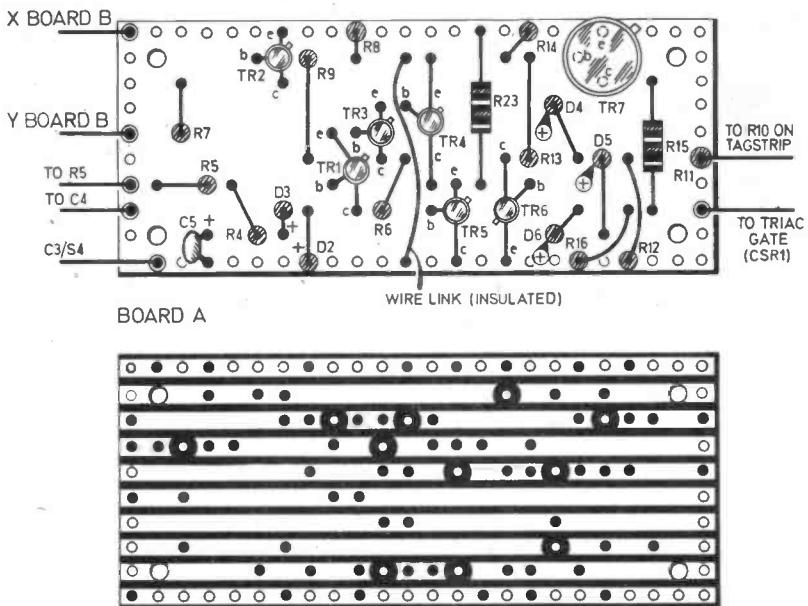

Components

Resistors

R1	10kΩ 10W wirewound	R13	4.7kΩ
R2	1MΩ } metal oxide	R14	18kΩ
R3	1MΩ } 250V	R15	100Ω
R4	47Ω	R16	220Ω
R5	10kΩ	R17	10MΩ
R6	10kΩ	R18	47Ω
R7	18kΩ	R19	47Ω
R8	10kΩ	R20	47Ω
R9	18kΩ	R21	1MΩ
R10	220kΩ } metal oxide	R22	22kΩ
R11	220kΩ } 250V	R23	10kΩ
R12	18kΩ		All 1W ± 10% except where stated

See
Shop Talk

page 43

Capacitors

C1	0.1μF 300V a.c.	C5	10μF elect. 16V
C2	0.01μF 300V a.c.	C6	4.7μF tantalum 35V
C3	1000μF elect. 24V	C7	10μF tantalum 35V
C4	1μF C280	C8	47μF tantalum 16V



Semiconductors

TR1	BC108 silicon npn	TR9	BC108 silicon npn
TR2	BC478 silicon pnp	TR10	BC478 silicon pnp
TR3, 4	BC108 silicon npn	CSR1	2N5574 or SC50D triac with mounting kit
TR5	BC478 silicon pnp	DI	BY127
TR6	BC108 silicon npn	D2 to D6	IN4148 (5 off)
TR7	BC461 silicon pnp	D7	BZX85-3V3 or any 1W 3.3V Zener diode
TR8	BC478 silicon pnp	D8	BZX61-12V or any 1W 12V Zener diode
		D9 to D11	IN4148 (3 off)

Miscellaneous

LPI	mains neon indicator with built-in resistors
SI	d.p.s.t. 15 amp mains switch
VR1	100kΩ carbon lin. potentiometer
SK1	miniature 3 pin mains connector with chassis mounted socket
SK2	13A mains flush mounting socket
S2 to S4	push to make release to break mains push buttons
X1	materials for sensor, copper clad p.c. board approx. 30 x 25mm, materials for conducting paint (see text), tissue or blotting paper and sea water or sea salt and distilled water.
	Veroboard 92 x 38mm, 0.15 inch matrix (2 off). Mounting bracket for CSR1, two capacitor clips, connecting wire insulated knob mains lead for mains connection and connection of sensor. Case, 6BA fixings.

Tumble Dryer CONTROLLER

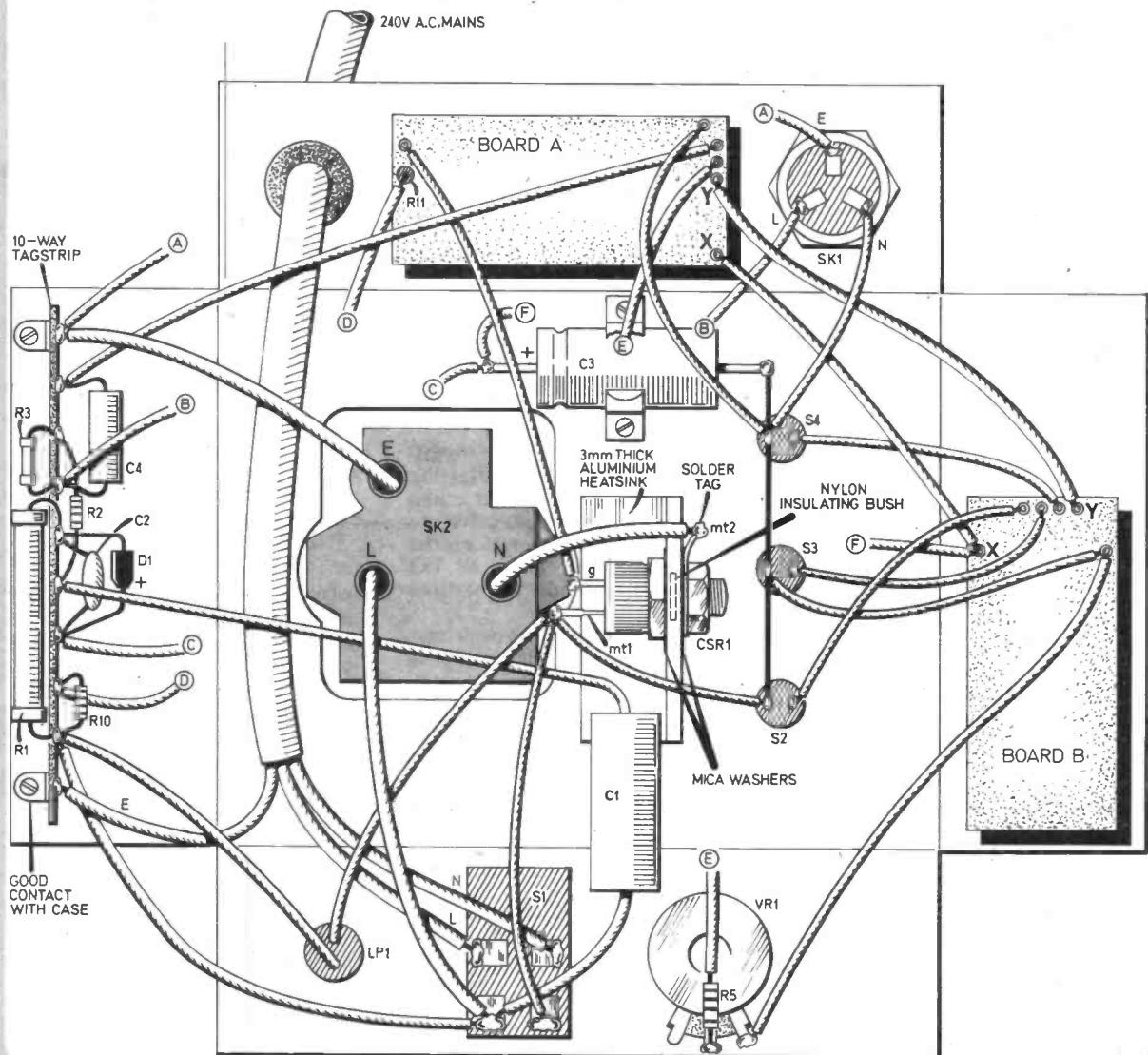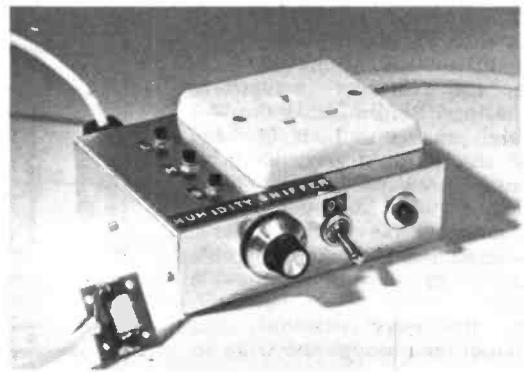

Drill and cut the aluminium box to accommodate the 13A socket SK1, the sensor socket SK2, humidity control VR1, on/off switch S1, the neon indicator, the three push-buttons S2, 3, 4, and the internal component mountings. Before fitting the 13A socket, connect to L, N, E using 13A single cable flex, as it is usually awkward to wire after fitting. Fit the 13A socket, then 3A mains cable using a p.v.c. grommet, and clamping the cable securely by means of a cable clamp.

Fit the other external components, then mount the triac on the aluminium angle, taking care that there are no rough edges to damage the insulating washers, and that the triac stud, case and fixing nut cannot short-circuit to the aluminium. Electrical connection to the triac stud is by a large solder tag fitted on the stud.

Bolt the aluminium angle firmly into place inside the box, and fit the two Veroboard panels, and the tagstrips and other internal components. Wire up according to Fig. 3. The sensor socket is wired up although the sensor is not connected until preliminary tests have been completed.

Check all circuitry and wiring being especially careful to ensure that the earth wire is securely connected to the metal case, and to the 13A socket and sensor socket.

TESTING

When you are sure that it has been wired and built correctly, test the unit, first of all by plugging an electric lamp into the socket using a 3 amp fuse in the plug. Switch on and allow a few seconds for C3 to charge up to working voltage. Set VR1 to maximum resistance and press the short time button S2. The lamp should light and stay on for nearly a minute, then extinguish.

Pressing the other buttons S3, S4 should give a longer period (up to 5 minutes) before the lamp goes out.

Set VR1 to minimum resistance and once again press S2. The lamp should still come on, and go out after about 1 minute. If it does not go out, gradually adjust VR1 until the light goes out, then unplug the unit from the mains. Disconnect one wire from VR1 and measure the combined resist-

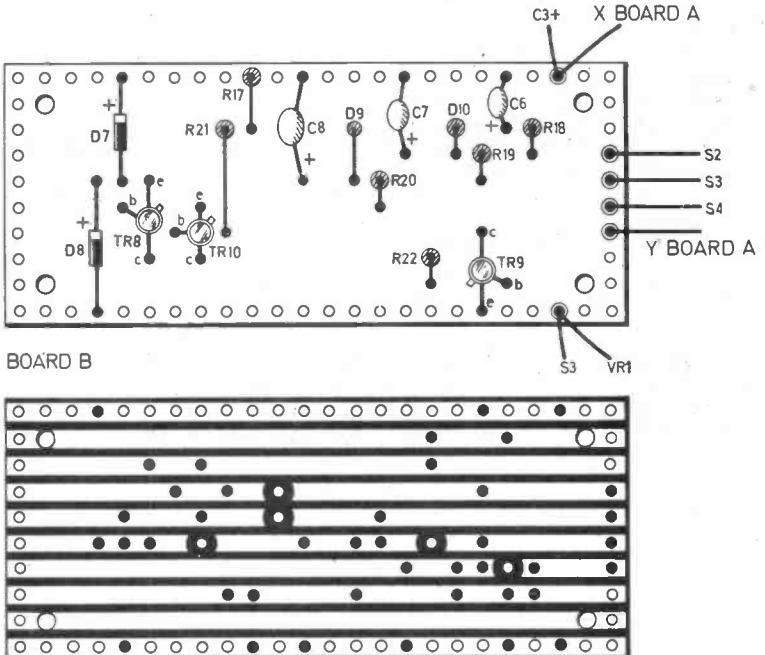


Fig. 4. Layout and wiring of the timer board.

ance of VR1 and R5 necessary to cause reliable extinguishing of the lamp. Replace R5 with a resistor of this value or slightly more, and re-connect.


Make up a connecting lead to fit the sensor input socket, using thin mains, 3-core wire, but before fitting sensor to the other end of the lead, fit instead a one meg-ohm variable resistor VR2.

Set VR2 to minimum resistance. Remember when adjusting this potentiometer that one terminal of it is connected to mains neutral, so it should not be touched, and the body of the potentiometer should be earthed for safety.

Using an insulated screwdriver, momentarily short the collector (case) of TR9 to the nearby neutral pin on the Veroboard. The lamp should light and remain lit. (If it does not remain lit, VR2 is probably not at minimum).

By adjusting VR2 a point should be found at which the lamp goes out. But by altering VR1 this point will be varied. Confirm that at all the settings of VR1, the lamp can be extinguished by adjusting VR2, and this being so, unplug the unit and replace VR2 with the humidity sensor. The sensor should be mounted in an aluminium container, which must be earthed for safety. Small holes drilled over the sensor face will allow it to sense the humidity level.

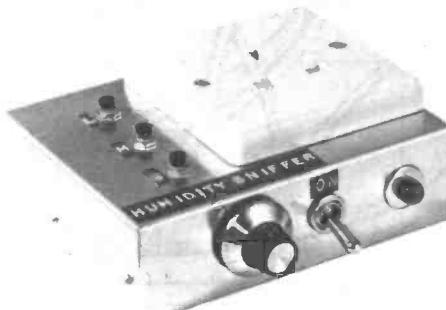The unit should now be ready for action, although it may be necessary to use several applications of salt solution to the paper, drying it out between one application and the next before the best response is obtained. Unplug the sensor when applying salt solution or making any other adjustments, for safety reasons.



THIS receiver utilises one of the transparent "snap box" or photo cubical boxes as a case, and the sides and back can be left clear, or filled in with 90×90mm photographs in the way originally intended. Apart from being a novelty in this way, it will provide very good loudspeaker reception, or allow personal listening by plugging a personal earpiece or headphones into the socket fitted.

The receiver is straightforward and employs one integrated circuit and four transistors. As there are no alignment or other adjustments to be made, and headphones can be operated from the i.c. alone, or i.c. and one transistor, it is ideal for a beginner. The circuit can also be tested initially before adding long wave coverage, and this extra waveband can be included at any stage wished.

INTEGRATED CIRCUIT

The integrated circuit is designated IC1, Fig. 1. It has only three leads, and is particularly intended for receivers of this and similar types. It provides radio frequency amplification, detection, and automatic volume control. Input is from the tuned circuit inductors L1/L2, and audio output (lead 1) is sufficient to operate headphones.

The medium wave winding of the ferrite rod aerial is L1, and L2 is the long wave winding. Both these windings have high Q, or provide high efficiency, L1 being Litz wound. Switch section S1

shorts out L2 for m.w. reception. For l.w. reception, L1 and L2 are in series.

For m.w. tuning only, a little simplification can be obtained, if wished, by omitting L2 and connections to S1. The free end of L1 is then taken directly to the frame of VC1; L2 and connections to S1 can be provided at any later date.

An initial test that this part of the circuit is working can be made by connecting medium or high impedance phones to points X-X. Only the tuned circuit, C1, C2, C3 and C4, R1, R2, R3 and R4 need have been wired, with IC1. If all is in order, this will give moderate headphone volume reception of those m.w. stations which are strongly received in the area, plus the BBC transmission on 1500m, if L2 is provided and the receiver is within the coverage of this long wave station.

Resistors R3 and R4 are a potential divider, providing about 1.3V for IC1. It would be possible to take R2 directly to a 1.5V dry cell, instead of using the 9V battery, but this is scarcely worth while in the present receiver.

AUDIO AMPLIFIER

Transistor TR1 is the first audio amplifier, and VR1 the volume control; C6 and R6 are to decouple the collector supply to this stage. Audio signals are normally from C7 to the output pair driver stage TR2.


The operation of TR1 can be checked by connecting the phones

from Y to Y. Reception should be as before, but at considerably higher volume — probably too loud for comfort with VR1 at maximum. Should a personal headphone receiver be wanted, leads can be taken from Y-Y to the jack socket, and the remaining stages can be omitted.

DRIVER AND OUTPUT

Transistor TR2 is the driver, and TR3/TR4 the complementary output pair. Direct coupling is used and d.c. feedback from the emitter circuits of TR3/TR4 to the base of TR2 stabilise working conditions.

FOR
GUIDANCE
ONLY

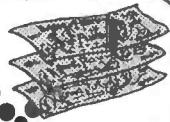

**ESTIMATED COST
OF COMPONENTS
excluding V.A.T.**

£10.00

excluding case

This particular circuit requires few components, has a low current consumption, yet can provide ample volume for this kind of receiver, and also operates well with a wide range of output loads. The speaker may be 35 to 80 ohms, the latter being used here, and most headphones or personal earpieces of 30 ohms or

PHOTOCUBE RECEIVER

By F. G. RAYER

A mw/lw receiver that can be built and tested in easy stages making it ideal for the less experienced constructor.



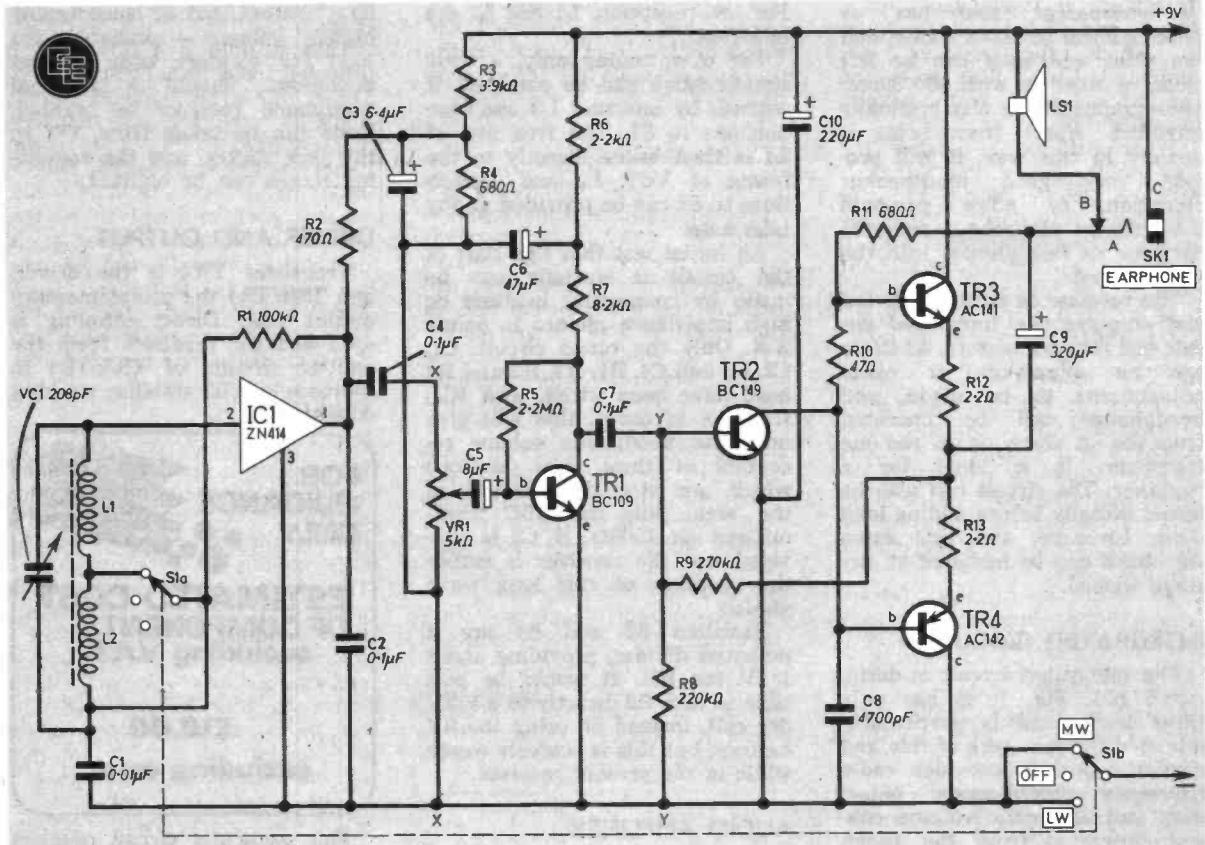


Fig. 1. The circuit diagram of the Photocube Receiver.

more (but not crystal earpieces) will be satisfactory.

If the receiver has been tested with phones as described, it is only necessary to add R8 to R13, C8, C9 and C10, with TR2, TR3 and TR4, and the speaker, to complete the receiver.

The output jack is connected so that when a plug is inserted the circuit to the speaker is broken. The shape and construction of jack sockets varies considerably, but it is usually possible to see which tags to use. If not, test with a meter to see that the circuit is from A to B with no plug in, and from A to C (via the phones) with a plug inserted. If phones will never be wanted, wire the speaker directly from C9 positive, to battery positive.

CASE PREPARATION

The box consists of two U-shaped sections, and the receiver is constructed wholly in one. Drills should be sharp, and used with relatively light pressure,

moderate speed, to avoid cracking the plastic material, or melting it so that it clogs the cutting edge.

Tuning capacitor VC1 is centrally placed, about 30mm down from the inside edge of the "panel". With VC1 located as in Fig. 3, mark and drill for the three 4BA bolts which run into the tapped holes of the capacitor. Countersunk headed bolts are most suitable here. They must be short, or cut down or filed, so that they do not project through the front plate and foul the moving plates. Alternatively, washers can be put between the panel and capacitor, provided the spindle projects enough for the tuning knob to fit properly.

Two 10mm holes are needed for VR1 and the switch. If necessary, smaller holes can be carefully enlarged with a reamer or file. Also drill holes for two 6BA bolts, which will secure small angle brackets, Fig. 3.

It is essential to support the panel by resting the back of the

panel on a piece of wood, or on the work table or bench. Drill matching holes for 6BA bolts in the bottom of the case, also supporting the material as described.

The front (taking the speaker) is then drilled. A grille of 21 holes at 12mm centres, each about 5mm in diameter, was used for the



speaker. The front was backed by a piece of 2mm paxolin, 90 × 90mm, and with matching holes, to which the speaker was cemented. Three 6BA bolts and the jack outlet secure the paxolin in position.

When drilling is finished the case can be dusted, and the parts fitted. A piece of thin tinted card 90 × 90mm is cut to fit under the panel. A scale marked 0-10 is drawn on this for tuning, and the volume control is marked, and also the switch, for m.w., off, and l.w. positions.

CIRCUIT BOARD

The circuit board is 90mm high, so that it will fit correctly, and 85mm wide (to clear the paxolin mentioned). It is secured to the small angle brackets at both the top and bottom, and also serves to brace the top and bottom of the box.

A strip of similar material about 16mm wide is cut and fixed at the other side of the case, again with top and bottom brackets. The ferrite rod is secured to this strip, with glued thread passed through small holes.

The circuit board can be wired and then fitted in position, or components can be inserted and wired to the fitted board, as the board "underside" is fully accessible.

BOARD WIRING

Both sides of the board are shown in Fig. 2, and the layout is arranged so that no connections cross each other. In most places the wire ends of components will be long enough to reach, but for the negative line in particular, 22swg or similar wire is needed.

The electrolytic capacitors have polarity marked, and must be put so that leads come as shown. Bend resistor and capacitor leads over, cut them as required, and solder on the underside of the board. If connections are run approximately as indicated, insulated sleeving is not necessary here.

Leads for IC1 and the other semiconductors can be identified from Fig. 2. The wires are spread so that they cannot touch each other, and are taken down through the holes shown. These joints in particular should not be

subjected to prolonged and unnecessary heating when soldering them.

Thin flexible flying leads are provided for external connections. These may be colour coded. Black is used for the negative battery line, to S2. Red is for battery positive, from R3. Yellow leads from C9 positive and battery positive line run to the speaker or output jack socket. A green lead from C1 and R1 passes through the board and is soldered to one of the tags of the frame of the tuning capacitor. Connections to VR1 are as shown.

FERRITE ROD

The 125mm ferrite rod has to be reduced to a length of about 85mm (some variation from this length is not important, except that if the rod is too long the case cannot be fitted together). The rod can be shortened by filing a notch or groove in it all round, then holding it securely at this point and tapping the unwanted end sharply with a metal tool.

Thread and adhesive holds the rod to the strip. It is shown out of position in Fig. 3 so that switch connections can be seen.

The tuning capacitor is a 2-gang component, having a front section of 208pF, and rear section of 176pF. This type is used because it is easily available, and L1/L2 are intended to be tuned by 208pF. So the rear section is unused. Fitting a capacitor of different value will not change efficiency, but will of course modify the actual tuning ranges.

Coil L1 has a small coupling winding, not required here, which can be unwound. Coil L2 has a tapping, also not needed, and this can be wound round the tube and secured with a little adhesive.

Place L2 so that its turns are in the same direction as those of L1. Each winding is pushed about 6 to 8mm on from the end of the rod (similar to Fig. 3). As movement of the windings will change the tuning position of stations, they are glued in place.

BATTERY ETC.

A PP6 9 volt battery is most suitable. Take care that the snap connectors are soldered to the receiver leads for correct polarity.

The tuning capacitor has threaded holes, one of which can take a 4BA bolt to secure the two parts of the box together. It

Components



Resistors

R1	100kΩ
R2	470Ω
R3	3.9kΩ
R4	680Ω
R5	2.2MΩ
R6	2.2kΩ
R7	8.2kΩ
R8	220kΩ
R9	270kΩ
R10	47Ω
R11	680Ω
R12	2.2Ω
R13	2.2Ω
VR1	5kΩ log. pot
All	±5% 1/2 watt carbon

Semiconductors


IC1	ZN414 integrated circuit
TR1	BC109 silicon npn
TR2	BC149 silicon npn
TR3	AC141 silicon npn
TR4	AC142 silicon pnp

Miscellaneous

L1/L2	Denco MW/LW FR5 ferrite aerial.
SI	2-pole 3-way rotary switch. 90 mm photocube box
LSI	80Ω 60mm or similar speaker
SKI	3.5mm jack socket (switched)
BI	PP6 battery, with connector 40mm knob; two small knobs. Veroboard, 0.15 inch matrix plain, 90 × 85mm 4BA and 6BA fixings etc.

SEE SHOP TALK

page 43

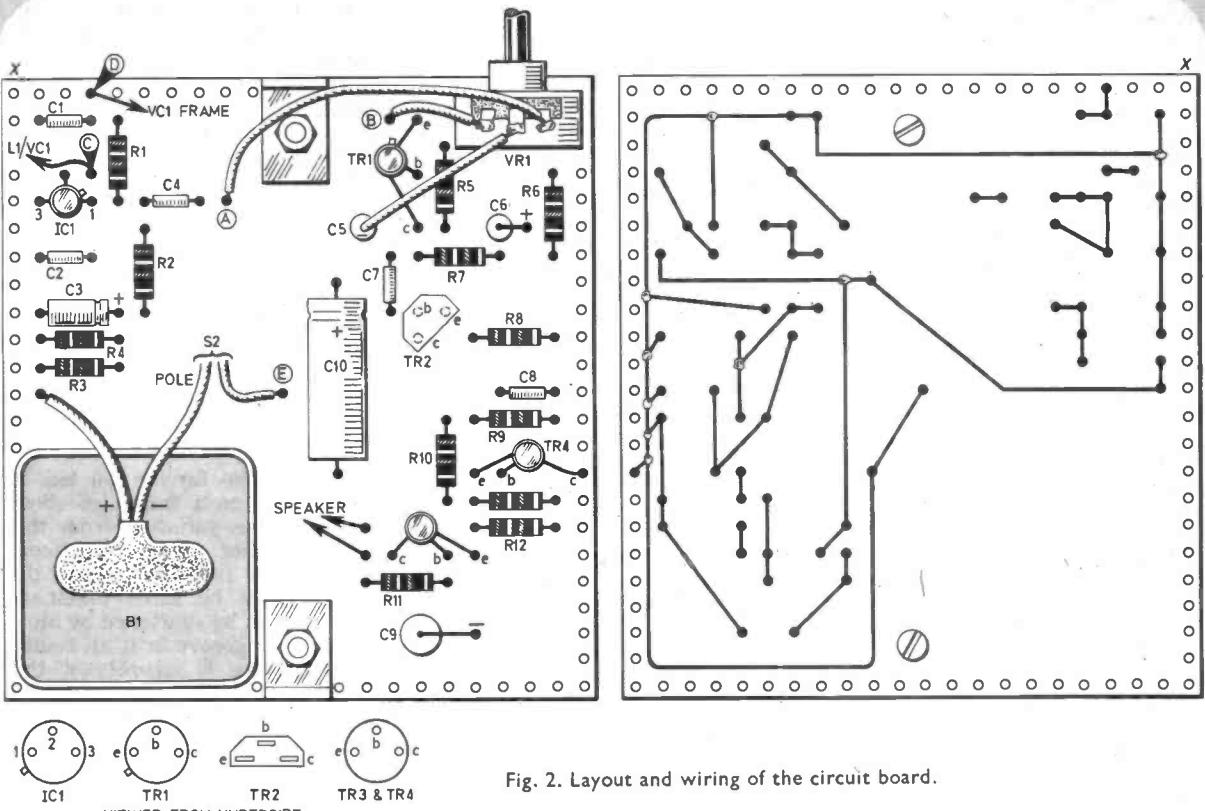

PHOTOCUBE RECEIVER

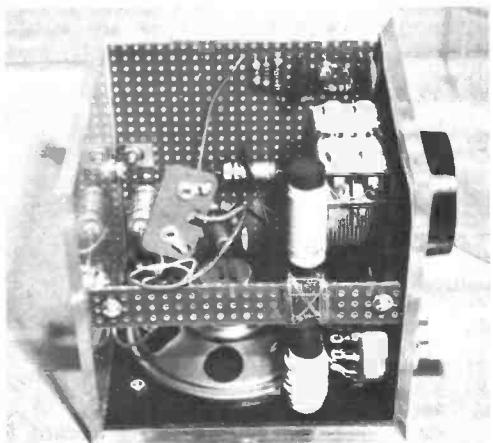
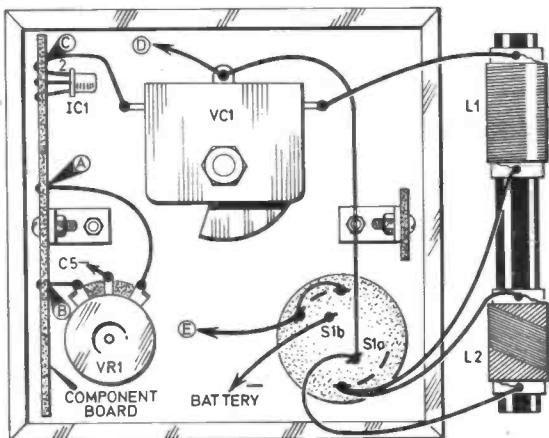


Fig. 3. Connection of the board to the remaining components

should not penetrate beyond the thickness of the capacitor frame.

Occasionally it may be worth while turning the receiver so that the aerial provides best reception or freedom from interference.


NOTE ON COMPONENTS

The 2-pole 3-way switch may be manufactured as a 6-way item with a stop which can be adjusted when the bush nut is removed. Place this for three ways only. If there is any doubt about the tags to use, test with a meter or similar means of show-

ing continuity. Switch S1a is closed in the medium wave position only; S1b is closed except for the central off position.

The switch and VR1 will normally have long spindles. Grip the free end of the spindle in a vice and cut off so that 10mm of spindle remains for the knob.

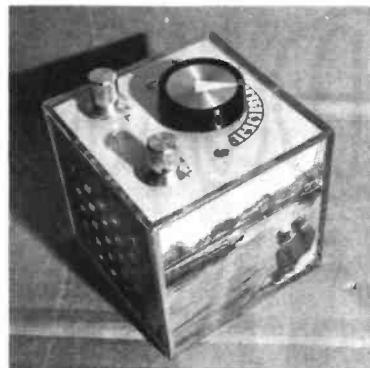As usual, electrolytic capacitors can be of higher voltage rating. There is a fair amount of free space, if some components are larger than the original items; C6 could be $50\mu F$; C3 need not be $6.4\mu F$, as $4\mu F$ to $10\mu F$ is suitable; C5 can be $2\mu F$ to $8\mu F$. □



Physics is FUN!

By DERRICK DAINES

Radio Resonance

Resonance is the acoustic or electrical parallel to reverberation. Let me explain. If we set a swing in motion it will swing to and fro until friction brings it to a halt. Similarly, in certain circumstances electricity may—for the sake of simplicity—be thought of as surging backwards and forwards in a circuit rather like bath water sloshing up and down the length of the bath. Similar effects are observable with radio waves.

Take the spark equipment of last month, see Fig. 1. Wind two coils L1 and L2, each of about 35 turns of any thin insulated wire wound flat round the hand giving a flat coil some 80 to 90mm diameter. Hold the coils with Sellotape. Capacitor C1 should be of paper or polystyrene, about $500\mu F$; C2 is also $500\mu F$, but a variable tuning capacitor. Make up the circuit as shown and we are ready to go.

Switch on the battery and obtain a spark across the gap, then shield it with a tin to prevent radio interference as mentioned last month. Lay coil L1 on top of L2 and adjust the variable capacitor until the neon lamp lights.

Try moving the coils away from each other. Now unwrap a few turns from one of the coils and it will be found that the neon lamp will go out, necessitating an adjustment of C2 to get it to glow again.

There are a lot of important lessons to be learned from this apparently meaningless experiment. First, both electrodes of the neon lamp glow, clearly indicating that alternating current flows through it. If we disconnect C1, this phenomenon ceases, which proves two things. First, that the a.c. of the last circuit is induced by a.c. of the second; and secondly, that the capacitor C1 is vital to this process.

When a spark is used to close a circuit, resonance is set up between the coil and capacitor. The period of oscillation (or frequency) depends upon the inductance of the coil and the capacitance C1. If one could observe on an oscilloscope the waveform through the inductance L1 caused by just one spark, one would see not just a simple waveform but a damped sinewave, that is, a decaying sinewave as shown in Fig. 2.

Removal of L2 from L1 for some short distance without affecting the

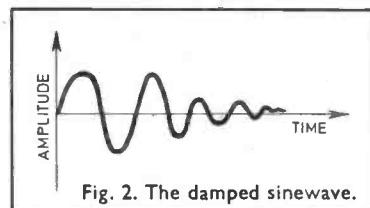


Fig. 2. The damped sinewave.

glow of the neon lamp indicates the presence of some sort of radio magnetic waves between the two and indeed, as the presence of radio interference shows (mainly on long wave), the section of the circuit containing the spark gap is indeed a radio transmitter. By means of the insertion of a Morse key almost anywhere in this part of the circuit, Morse can be transmitted and read off at the neon.

Finally, consider the role of the variable capacitor C2. The function of this capacitor is to adjust the tuning of the resonant circuit of the final stage to match the resonance of L1/C1. In short, of the three stages of the circuit of Fig. 1, the first stage is the power-pack, the middle stage is the transmitter and the last section is the receiver.

Altogether, the circuit is a most valuable piece of equipment for the understanding and study of radio, and for those readers who would like to make up this gadget for regular use but who are worried about interference on local radio receivers, let me add that the addition of a small capacitor across the spark gap will obviate this problem entirely.

It is impossible to give an exact value, but I suggest experiments starting with $0.047\mu F$ and working downwards.

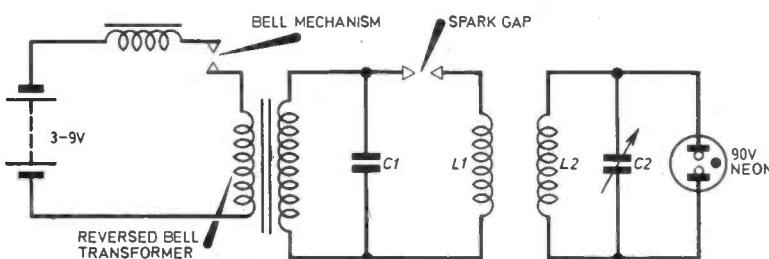


Fig. 1. The circuit of the spark equipment.

Doing it Digitally...

PART 4

By O.N. Bishop

HAVING LOOKED at integrated circuits containing simple two-input gates in previous parts of this series, we now go on to more complex integrated circuits, looking in particular at the dual J-K flip-flop i.c. type 7473.

THE FLIP-FLOP

A flip-flop is a bistable with several control inputs. The changes of state of the J-K bistable are controlled by three types of control signal:

- 1) **CLOCK** The bistable can only change state when its clock input changes from a high to low. By setting each of these inputs to either high or low, four outcomes are possible when the clock pulse occurs. The bistable can be made to:
 - a) Stay in the same state
 - b) Go low
 - c) Go high
 - d) Reverse state
- 2) **J, K**
- 3) **CLEAR** Irrespective of the clock, this input sets the Q output low.

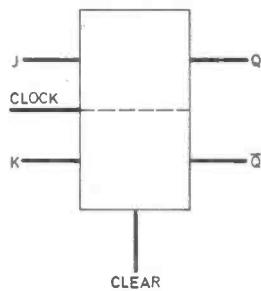


Fig. 4.1. Symbol for the J-K flip flop.

The 7473 integrated circuit contains two J-K flip-flops. The symbol for the J-K flip-flop is shown in Fig. 4.1 and the pin connections of the i.c. in Fig. 4.2. Note that outputs are provided from both halves of the bistable, these being designated Q and \bar{Q} , the bar over the second output indicating that it is the inverse of the former.

The symbol for the flip-flop does not indicate the complexity of the actual circuitry: a total of 22 transistors and 20 resistors are used to make each, and there are two of these for the price of about five cheap transistors.

EXPERIMENTS WITH FLIP-FLOPS

The 7473 i.c. has its power

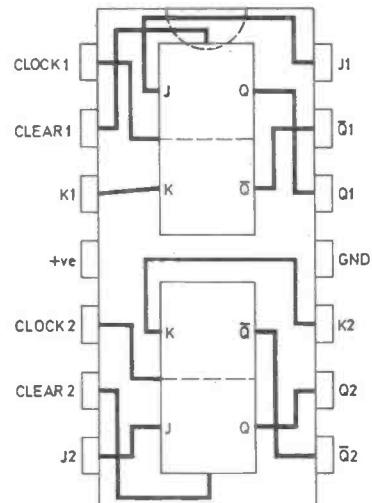


Fig. 4.2. Pin connections of the 7473 integrated circuit.

supply connections made to pins 4 and 11 so make sure that this is remembered when using the i.c.

As a start, the i.c. should be put in the top left position on the experimental board and wired up as shown in Fig. 4.3.

In part 3 we saw how the 7400 i.c. can be made into a "clock" or pulse generator and this circuit is just what is needed to drive the clock input of the 7473. Connect up the 7400 i.c. as a clock using the circuit of Fig. 3.11 with $470\mu F$ capacitors to give a slow frequency. Connect up the output from the clock (pin 3, 7400) to pin 1 of the 7473.

It is not essential to use the electronic clock input, connecting the clock input wire alternately to ground and 6V will do just as well (see section on "contact bounce").

At this point the J and K input wires should be left free. Now try all possible variations of J and K inputs clocking the bistable after each change. Make up a Truth Table showing the state of the Q output before and after the clock pulse with all the different J-K inputs. Table 4.1 is how it should appear.

One important point to note is that if the J or K, or both inputs are allowed to go high while the clock is high, this will count as a high input when the clock next goes low, even if the input is put back to low before then.

Which setting of the J and K inputs always makes the flip-flop change state? Which makes it always stay the same?

If during the experiments it is necessary to make the Q output low, touch the clear wire (from pin 2) to ground.

FLIP-FLOPS IN COMBINATION

So far the second flip-flop in the 7473 i.c. has not been used but

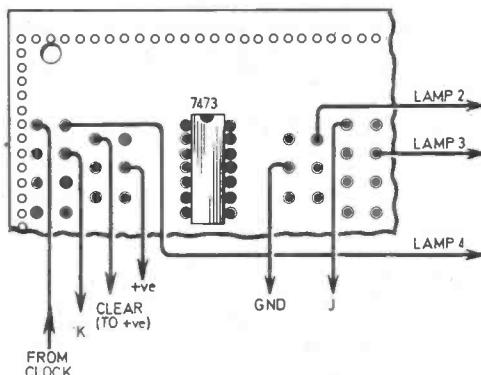


Fig. 4.3. Wiring of one flip-flop on the circuit board.

this state of affairs will now be rectified.

The circuit of Fig. 4.4 shows how to wire the i.c. Again the electronic clock circuit is a useful addition.

In this circuit both J inputs, both K inputs and both clears are too high so the flip-flops will change state whenever the clock input goes low.

Flip-flop 1 is fed from the clock and its Q output is fed to the clock input of flip-flop 2. The three

lamps indicate the state of the clock, the state of flip-flop 1 and the state of flip-flop 2 respectively. Switch on and see what happens.

Wait till all the lamps are out then begin to record the sequence. Table 4.2 shows what will be recorded.

Rewrite the table using a 0 in place of an L and a 1 in place of an H. It will be seen that the outputs indicate the binary numbers from 0 (000) to 7 (111) in ascending order. In other words the cir-

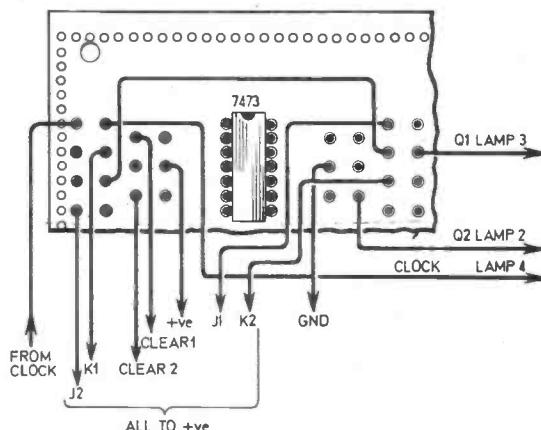


Fig. 4.4. Wiring of both flip-flops in the 7473.

Table 4.1: Truth Table of J-K flip-flop operation

Before clock goes low Inputs		After clock goes low Output	
J	K	Q	Q
L	L	L	L
L	L	H	H
L	H	L	L
L	H	H	L
H	L	L	H
H	L	H	H
H	H	L	H
H	H	H	L

cuit is counting from 0 to 7!

In the experimental circuit the clock pulses were obtained from another i.c. connected as a pulse generator but, in fact, the pulses could be derived in other ways. For instance if a light sensitive switch were connected across a doorway in such a way as to produce a clock pulse each time a light beam was broken, then the counting circuit would keep a record of the number of times the beam was broken.

Table 4.2: Lamp sequence in Fig. 4.5

2	Lamp 3	4
L	L	L
L	L	H
L	H	L
L	H	H
H	L	L
H	L	H
H	H	L
H	H	H

HIGHER FREQUENCIES

Reconnect the circuit of Fig. 4.4 but instead of using large capacitors in the clock generator, use $0.1\mu F$ capacitors to give a clock frequency of several hundred pulses per second (hertz). Can the flip-flops count these fast pulses? It is a bit hard to tell by looking at the lamps as they flash too quickly, but here again we can use an earphone (or the loudspeaker unit of Part 3) to see what is going on.

Connect the earphone or loudspeaker unit to the clock, flip-flop 1 and flip-flop 2 outputs in turn.

The output from flip-flop 1 is a note an octave lower than (i.e. half the frequency of) the note from the clock and the output from flip-flop 2 an octave lower again. Thus the flip-flops are deal-

ing well with the high frequency pulses.

This sort of circuit finds use in electronic pianos or organs where a master clock (or oscillator as we call it) produces a note of the required frequency (say the highest G on a piano) and the G's for all the octaves below it are produced by a series of flip-flops, the frequency being divided by two at each stage.

Thus a series of flip-flops can act as either a counter or a frequency divider.

The second flip-flop changes state after every fourth clock pulse so two flip-flops can divide by four. To count larger numbers or divide by larger numbers more flip-flops can be connected. There are some i.c.s available which have four flip-flops in cascade thus enabling counts up to 16 or

division by 16 to be achieved. Other integrated circuits are available with as many as 14 flip-flops in a single package enabling counts of 16,384 to be carried out.

CONTACT BOUNCE

There is a problem which might have occurred if the clock input to the flip-flop was made by touching the wire alternately to ground and 6V, which can be identified by erratic jumps in the sequence.

The electronic clock produces "clean" pulses with sharp transitions between states but touching the wire to a voltage rail or even using a mechanical switch produces what is called "contact bounce" where, instead of a high-low transition, a high-low-high-low transition may be produced. When fed to the clock input of the flip-flop, these transitions are interpreted as a series of pulses which, because they are very rapid, cause the flip-flops to jump several counts in the sequence.

To operate counting chains of flip-flops, the clock pulses must have a clean change from high to low, so if a mechanical switch must be used a "cleaning up" circuit must be placed between it and the flip-flops. This will be described in a later section.

To be continued



Soldering

I am a regular reader of **EVERYDAY ELECTRONICS** and am re-soldering a project in which I think there may be one or two dry joints. Two problems have arisen.

Firstly, I find that when I try to remove the iron from a joint solder sticks to the bit and leaves solder sticking up in points. Please could you tell why this is and how it can be avoided.

Secondly, is it possible that flux from

solder could cause a bridge on Veroboard or is flux a good insulator.

N. Staunton
Taunton.

Providing your iron is reaching the correct temperature, the first problem is caused by the lack of flux, you should always use new solder even when resoldering as a dry joint is caused if all the flux is burnt off before the iron is removed (see page 24). Flux is a good insulator but is best cleaned off as it may hide a solder bridge.

Symbols


I am a beginner when it comes to i.c.s and was pleased to see a Series started on them in E.E.

Having just received November's issue I feel as though I've taken a step backward, because of the way the OR gate is drawn on page 601.


My company have issued a booklet showing signs and symbols for components, and gates are as follows.

Could you please state who is right, if anyone or does it matter?

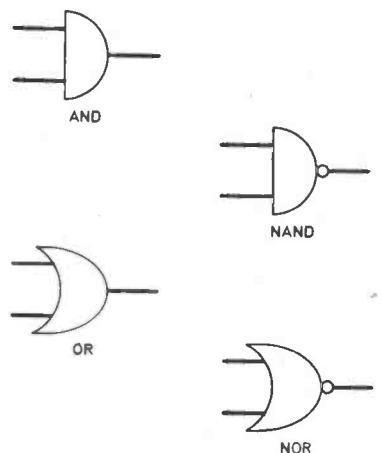Thanks for a very helpful magazine.
L. Miller,
Oldham.



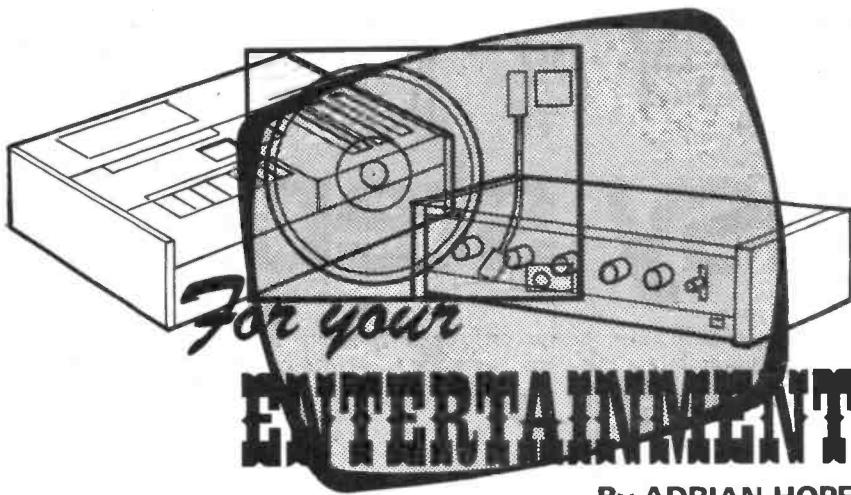The symbols you show are to the MIL STD 806B specification which is an American spec. used by some i.c. manufacturers. Our symbols for the gates you show are in accordance with BS 3939 section 21 which is the relevant British standard specification. Maybe you work for an American company?



SOMETIMES in technology the tail wags the dog. In other words, we are left looking for applications for new developments. This can produce some quite daft examples of oversophistication. Recently one project feature in a magazine detailed the design and circuitry for a car burglar alarm. All manner of transistor switching devices are hooked up to the simple microswitch which is normally used automatically to switch on the car interior light whenever the car door is opened so that an alarm sounds whenever the car door is opened.

A self-hold relay, triggered by the switching transistors, stays "on" even when the microswitch is opened again, so that closure of the car door can't stop the alarm. But wait a minute, wouldn't it be easier just to use the self-hold relay in direct connection with the door microswitch, without all those intermediate transistors?

Thermistor

It's also easy, with all the solid-state sophistication now available, to forget about the existence of a handy little gadget called a thermistor or brimistor. These were developed many years ago to protect sensitive circuitry, for instance in TV sets, from the high current surges which usually result when any system is switched on from cold.

A thermistor is a small rod device, looking like an ordinary resistor, which has a high resistance when cold and a much lower resistance when hot. And it is intended to get hot in use. Thus, if it is placed in series with a component that needs protection from a current surge, it very conveniently lets only a small amount of current through to begin with and then an increasing amount of current as it heats up.

The bright idea dawned a while back of using thermistors in series with

projector lamps, which can have their working life dramatically extended if protected from switch-on current surges. Remember that projector lamps are expensive beasts which, when cold, have a resistance of only about 1/20th their resistance when hot, and can be subjected to instantaneous current flows of well over ten times their normal operating current. This is why most lamps usually blow at the moment of switch-on.

For a while many people used thermistors in series with expensive lamps, but now all that seems to have been forgotten and the thyristor has taken over—with all its attendant problems of radio and audio interference.

Availability

For the benefit of anyone wanting to take the simple way out, I checked up on the current availability of thermistors. ITT Components still make a full range (all referenced CZ), and ITT confirm that these cheap and useful little gadgets can (if your normal component supplier can't help) be obtained through their distributor, Nobel Electronics, Nobel House, Bowater Road, London SE18 5TN.

All you do is select a thermistor of the correct rating (e.g. a CZ-12 for 500 watt lamp with 200-250 volt supply; a CZ-11 for a 300-watt lamp and similar supply voltage, and so on), and wire it in series. Take care to leave plenty of air space round the thermistor because it has an operating body temperature of up to 250 degrees C. A good idea is to put a by-pass switch across the thermistor to short it out of the circuit once the lamp has warmed up, the surge is over and the thermistor's job is done. One word of warning, however. As learned years ago the hard way, thermistors are: essentially current conscious devices and need to be in series with

a fairly high resistance to achieve working equilibrium without burning out. If your projector lamp runs at mains voltage without a transformer, there is no problem, because the current flow is relatively small. But they should not be used in direct series connection with a low-voltage, high-wattage lamp on the secondary side of a transformer, as the current flow will be too great. Thus if the projector incorporates a mains transformer which drops the voltage, for instance to 12 or 24 volts, you should use the thermistor in series with a transformer primary.

This point has been widely overlooked, for instance by at least one photographic manual, obviously written by someone who had never actually used a thermistor.

Calculator Batteries

London readers may have noticed large spreads in their newspapers advertising the new Ever-Ready calculator batteries. The reason these adverts are initially appearing only in London is that the batteries are so far only being test-marketed, and whether they are sold more widely will depend entirely on London's reaction.

The IEC has drawn up provisional suggestions for the ideal battery to use in a calculator, and have based this on an assumption that most calculators are used for around 30 minutes a day and require more current than a radio but less than a shaver. This means that none of the ordinary cheap Leclanche batteries currently on sale fit the bill.

So Ever-Ready is test-marketing a modified Leclanche to fill the gap. The new batteries cost around a third as much again compared with conventional "blue" radio equivalents, but should be up to 100 per cent cheaper (in terms of pennies per useful hour) than the expensive alkaline-manganese types that many people now buy for their calculators.


Warning!

But one word of warning: Ever-Ready readily acknowledge that, being Leclanche's, these new calculator batteries will very probably leak if left unused in a calculator for a matter of months (or for that matter destructively drained by a calculator being left on overnight). As Ever-Ready sum up the situation—"With batteries, it is horses for courses, and when you buy you must always choose between use and storage".

Personally, as someone who has several times ruined equipment by leaving leak-prone Leclanche batteries inside for too long or inadvertently draining them too fast, I would no more use Leclanche's in expensive electronic gear than bathe it in sea water.


Soldering in easy steps

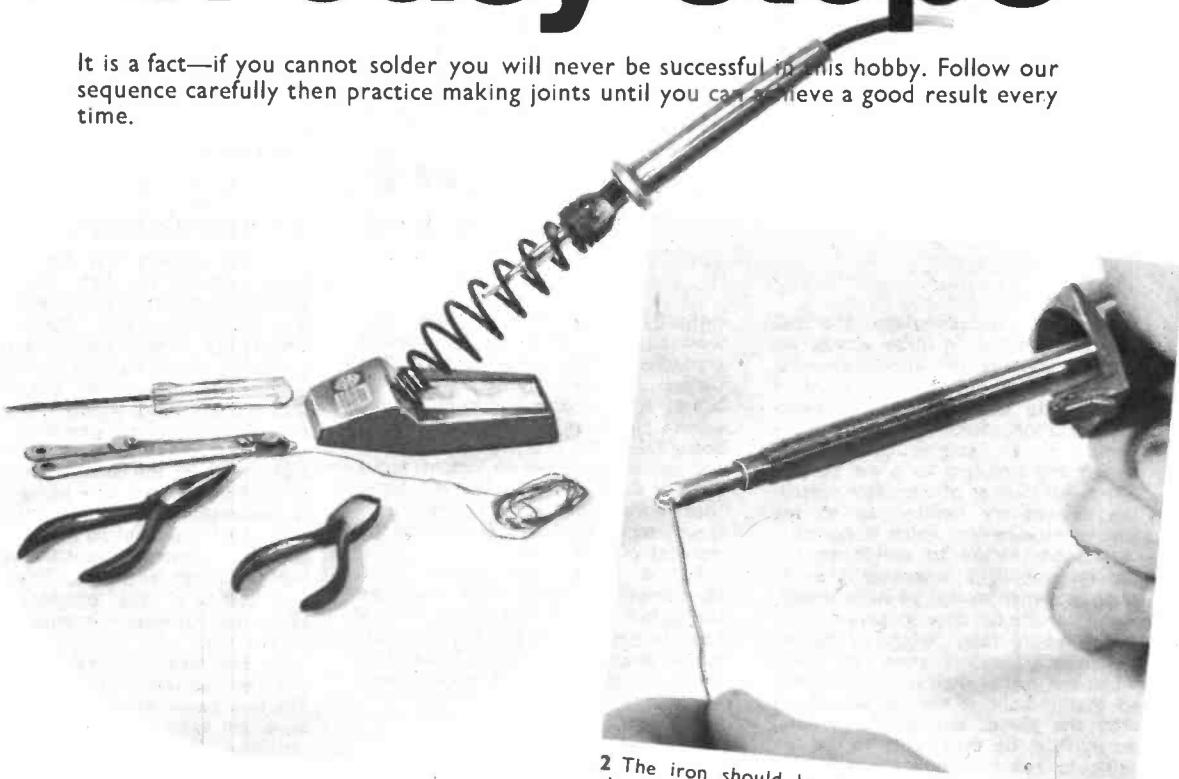It is a fact—if you cannot solder you will never be successful in this hobby. Follow our sequence carefully then practice making joints until you can achieve a good result every time.




1 You will need a lightweight soldering iron with a 3 to 5mm bit, some flux cored solder and a few general tools.

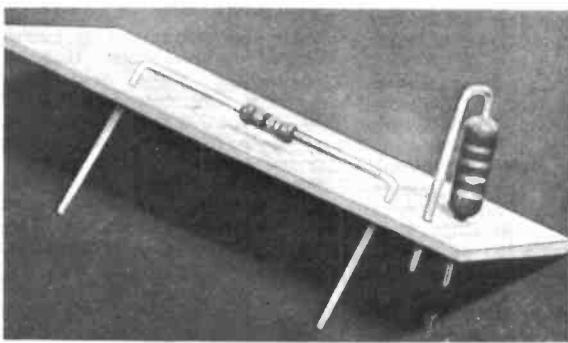
2 The iron should be at the correct temperature, it should melt the solder easily without causing the flux to spit violently, and should always carry a small amount of solder.



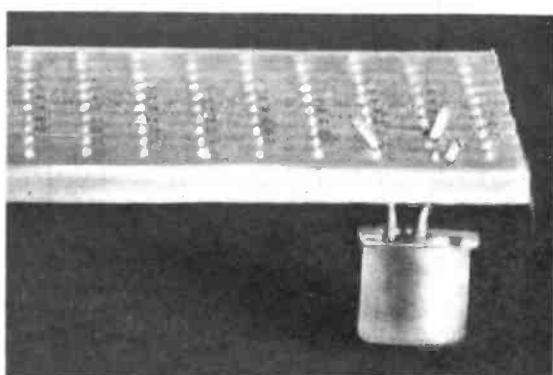
3 Two methods of component mounting on Veroboard. Bend the leads down in line with the strips and cut off leaving about 2 to 3mm.



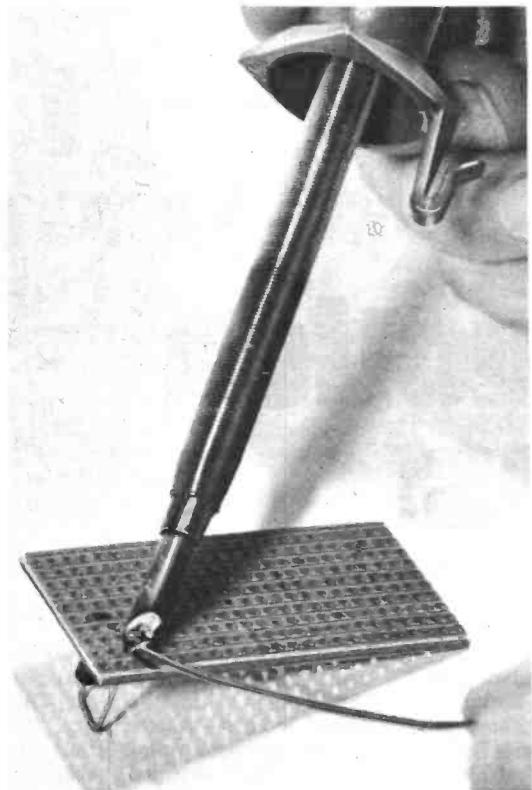
4 Transistors are easier to remove later if their leads are only slightly bent over. Be careful not to overheat them when soldering.



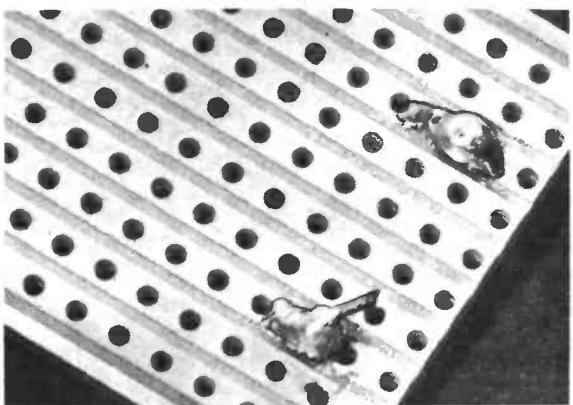
5 Making the joint. Melt a small amount of solder onto the joint, *not onto the iron*, wait just long enough for it to run evenly over the whole area then remove the iron.



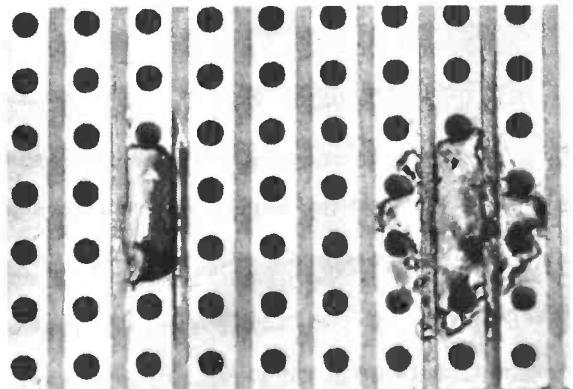
6 Two poor joints. In the upper one the solder has formed a blob on top of the copper and not run evenly over it. In the other the wire was not bent down, or cut short enough.



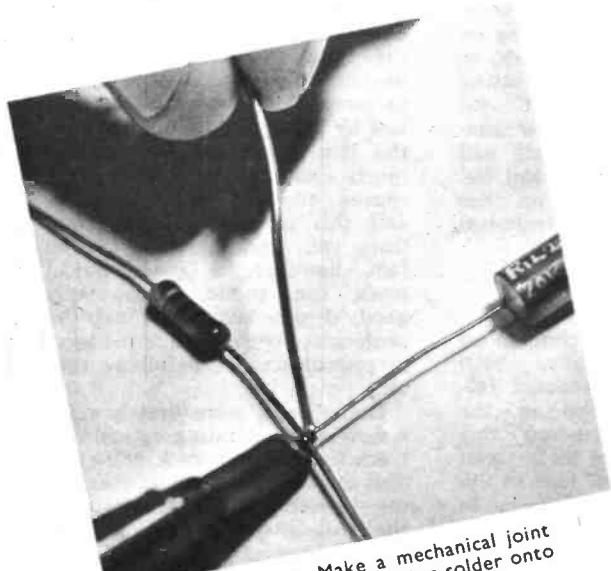
7 On the left how a good joint should look. On the right a mess made by using too much solder and keeping the iron on too long, burning off all the flux.



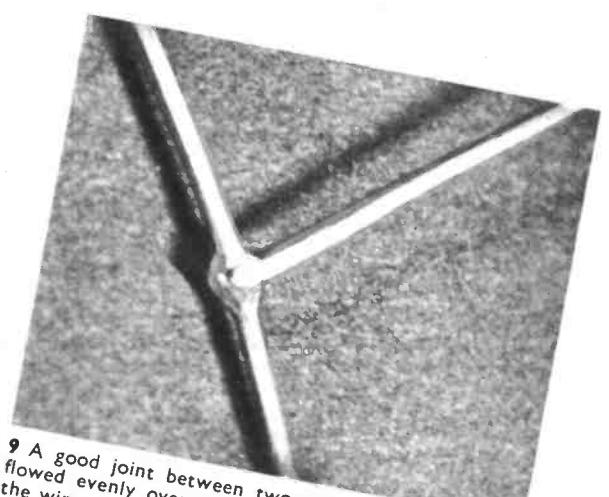8 Joining two wires. Make a mechanical joint first then proceed as in 5, melting solder onto the wires not the iron.



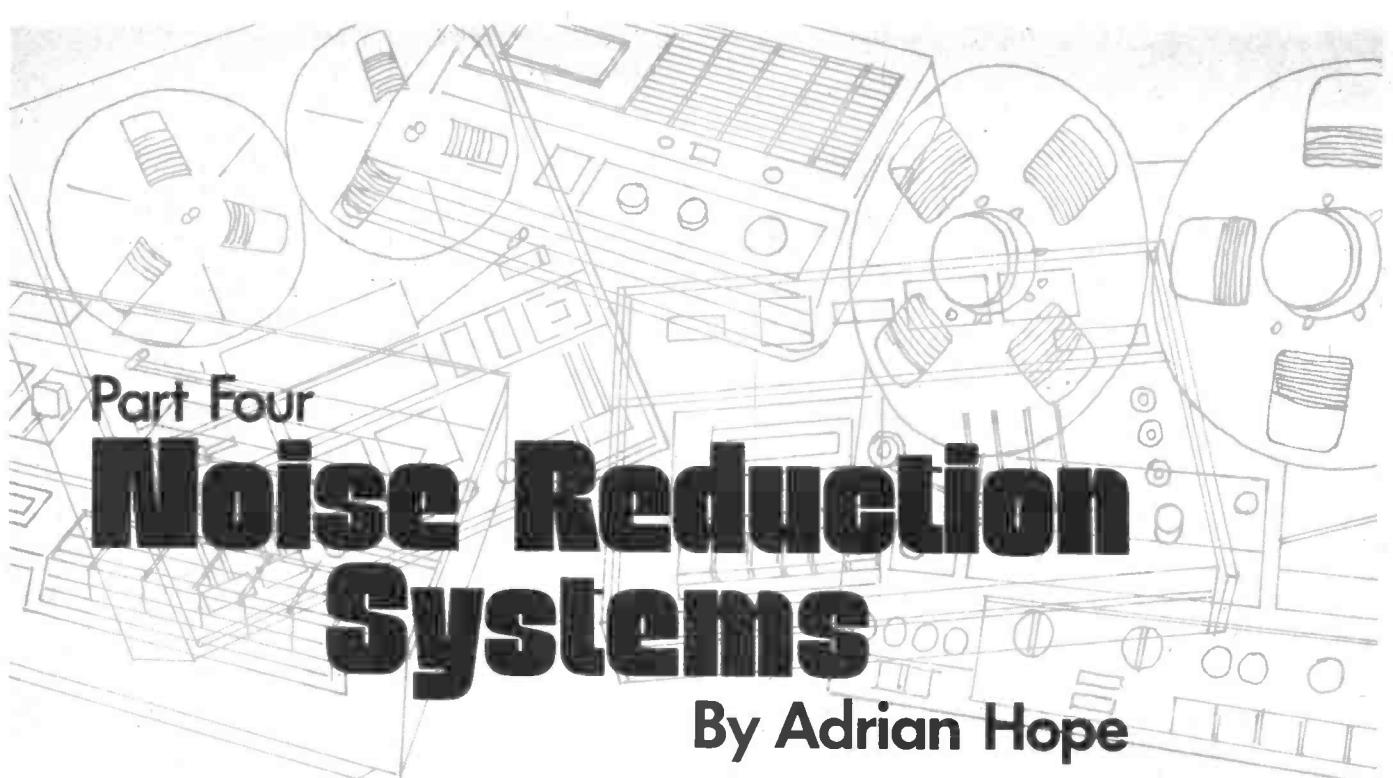9 A good joint between two wires, the solder has flowed evenly over the area, but not too far along the wires, and is clean and bright.



Part Four

Noise Reduction Systems

By Adrian Hope

WE conclude this short series by looking briefly at the availability of the final two systems and at some other areas.

BURWEN

At the time of writing, there is no sign of any Burwen equipment on the domestic market, and dbx is still largely an unknown quantity.

As a guide, however, on the professional level there is no doubt that dbx is regarded by European studios as an addition to Dolby rather than an alternative; it would be commercial suicide for any recording studio to offer dbx but no Dolby. But, on the other hand, some record producers would prefer to use dbx rather than Dolby if the possibility exists.

Mike Oldfield, for instance, recorded the LP *Ommadawn* using the dbx system, and the only time that Dolby master tapes of this recording were produced was when the need arose to send them abroad to studios equipped only with Dolby. Also dbx is often found in studios handling master tapes recorded, or partly recorded, in the USA.

On the domestic level, it is likely that some tape machines from Japan will soon be incorporating dbx 120 circuitry as an integrated feature, in the manner

that many machines now incorporate Dolby B. It is to be hoped, however, that such machines will incorporate both dbx and Dolby, rather than dbx instead of Dolby, because a Dolbyised tape replayed on a dbx machine or vice versa will produce decidedly odd results.

Whether dbx add-on units (either the 120 series, for encoding on "record" and decoding on "playback" or decoding discs; or the 110 series, for compressing and expanding on "record" and "playback" or expanding or compressing existing material) will succeed commercially in the UK must depend largely on the economic climate and technical reviews in the audio press.

CINEMA SOUND

What of future technological developments? Already, both Dolby and dbx professional formats are being used in the cinema. Dolby pioneered this work and it remains to be seen whether their current lead in the field is maintained. (There is in fact already a dbx version of the film *Tommy* showing abroad.)

The train of thought linking Dolby to the cinema is logical once it has been explained. In the early days of the professional cinema, it was soon recognised that optical soundtracks were noisy, due to the presence of

optical grain on the track and to the ravages of dust and dirt. This noise is hiss which since the thirties has been rolled off according to the so-called Academy Curve.

The curve quite simply takes an axe to all the upper frequencies and in an effort to compensate for the dullness which results, engineers started using equalisation techniques to boost the high frequency content heavily. The idea, as always, was to compensate for what would be lost by putting too much there in the first place. But putting too much sound on an optical track causes clipping and distortion, and this is why a bad optical track can sound terrible. (To be fair, however, a good optical track can sound astoundingly good, if one bears in mind the problems involved in equalising to counteract the Academy roll-off.)

Dolby Labs. were first to offer a system for encoding optical film track to cut down track noise and thus enable engineers to abandon the Academy roll-off and with it the excessive equalisation techniques. Several films with Dolbyised optical tracks have now been produced and released (some in stereo) and the results are impressive.

The frequency range is much wider than has been conventional for cinemas but there is as little,

or less, background hiss than with the Academy curve and the wider frequency range makes for crisper, cleaner dialogue, music and effects. At the time of writing there has been no opportunity in this country of hearing a rival system, whereby several tracks are recorded optically, using a hue-modulated system.

BROADCAST

In the area of broadcast, dbx have their broadcast encoder, but there are no signs of any move towards dbx-encoded broadcasting in Europe, and there are certainly no receivers with the necessary decoder built in. It is more likely that, if noise reduction broadcasting is ever adopted in Europe, it will centre round another clever idea put forward by Dolby Laboratories and adopted by more than a hundred USA radio stations to date.

The proposal is that FM broadcasts should be Dolby B-encoded at transmission, but with modified pre-emphasis of the broadcast signal. If this signal is received on a set which is equipped both with Dolby B decoding facility and circuitry adapted to de-emphasise the signal in mirror image fashion to the modified pre-emphasis, then the listener will hear the full benefit of noise reduction.

If, however, the signal is received on a conventional set which has neither Dolby B nor modified de-emphasis facilities, then the "wrongness" of the un-decoded signal will compensate for the "wrongness" of the incor-

rect de-emphasis offered by the set. The result of this compensation is claimed to be an overall return to normality, with improved reception over a wider area as a by-product of the higher modulation levels made possible by the modifications of the transmission with respect to conventional transmissions.

In other words, the system is claimed to be compatible, providing improved results for those with facilities to obtain them and no change for the worse for those with no inclination to go out and buy new equipment. Whether the system works as claimed is still open to argument, because neither the IBA nor the BBC will yet countenance even experimental broadcasts in this country to test the system.

However, experience in the USA and some tests carried out in Europe, unbeknown to the listening public, suggest that if problems do exist they are not noticeable to the majority of listeners.

COMPATIBILITY

This point on compatibility neatly sums up the main reason why Dolby has so far succeeded where others have failed. Although the Dolby B system has been criticised for the relatively limited amount of noise reduction that it offers, it has the overriding advantages of being inaudible in action and generally compatible.

If a Dolby-encoded tape is replayed without decoding, it will not sound unduly objectionable.

Indeed because Dolby-encoding involves artificial boosting of low level high frequencies, when replay is on a cheap non-Dolby machine (which almost by definition has poor high frequency response), the unnatural brightness of the encoded recording will be an advantage rather than a disadvantage. Moreover, any listener who finds the resultant sound slightly too bright can always turn back the treble tone control of his machine, thereby trimming the top frequencies to restore a more natural sound and in so doing reduce hiss noise.

Although the future is an open book, the past is a closed book. It is already written that the advent of Dolby B as a compatible noise reduction system provided massive impetus to the cassette as a domestic recording medium. On the professional level it is already written that the advent of Dolby A made it possible for recording studios to cram 16, 24, and even 32 separate tracks of recorded sound on a single piece of 2-inch tape, and thereby opened up all the possibilities of modern multi-track recording.

On a final note, and with an eye to the more distant future, it is worth noting that the original work that produced the Dolby A system was clearly directed more at the field of video than audio. In the event, Dolby A, and then B, emerged as salvation for various audio fields. And work by Dolby Labs in other areas continues. It is likely for instance that in the not too distant future the system will be adopted in the field of facsimile transmission. □


PLEASE TAKE NOTE

In Fig. 2 (page 657) of the Light Flasher, November '76. The underside view of the transistor shows e and c transposed.

Some breaks on the Veroboard were omitted in the Scratch and Rumble Filter article, page 591 November '76 issue. In Fig. 6 breaks should also be made at M9 to 15 and M26 to 31 to separate channels. Also, in Fig. 8, the two right hand wires to S1 should be transposed. Earthing of SK1 and SK2 is achieved through the metal chassis, if a non-metallic case is used, earth wires should be connected back to the solder tag. The OV connection on T1 should also be connected to earth.

The diagram shown below was omitted from the Min Organ article last month. It should have been included as Fig. 3.

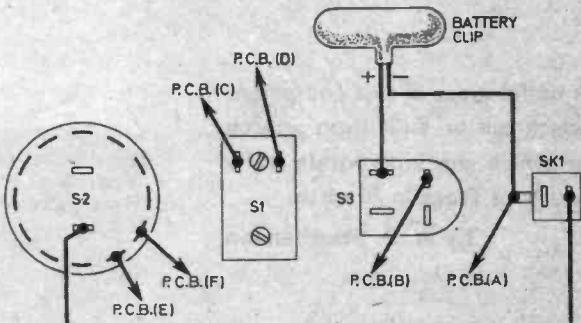We apologise to readers for these errors.



Some readers have had problems with spurious and even continuous triggering of the Clunk-Click Jogger in the September '76 issue. This should be overcome by reducing the value of C1 to 0.01μF.

THE Multi-Tester has been designed primarily for readers who have been following the Teach-In 76 series and will already have most of the components (it will obviously appeal to all constructors to no less a degree). The additional expenditure is modest—a couple of rotary switches, a few resistors and capacitors. The case can be home made to save money but a Veroboard Type 103 will certainly professionalise the appearance and make it at least look nice.

The facilities available are as follows:

- (a) *Measurement of d.c. Voltage and Current* in the ranges 50V, 10V, 5V, 1V, 0.5V, 0.1V and 50mA, 10mA, 1mA, 0.5mA, 0.1mA. In the writer's opinion, these ranges are the best compromise where, for reasons of switch economy, ease of scale marking and simplicity, the choice must be limited to six. However, for those that disagree, it will be a simple matter to vary a few resistor values.
- (b) *Measurement of Resistance* is available, unfortunately on only one range with a mid-scale reading of 90 kilohms. Because the ohms scale on any multimeter must range from "zero" to "infinity" the scale markings are always cramped at one end. The choice of a single 9 volt battery and a meter f.s.d. of $100\mu A$ results


inevitably in the figure of 90 kilohms at centre. The extra switching necessary to bring another battery into circuit was considered an unnecessary complication.

- (c) *Continuity Testing* is an "extra" seldom found in a testmeter. The normal resistance scale can detect continuity between two points because it will read "zero" ohms. However, there are distinct advantages in using a system which gives an audible tone when two points are electrically continuous—the most obvious being the avoidance of neck ache. There is nothing more irritating than trying to balance a meter at some perilous angle in order to see the scale without dislocating the cervical vertebrae. When the two terminals marked continuity are short circuited a low level, but easily audible whistle of around 800Hz escapes from the case. (If a morse key is connected across these terminals a convenient practice unit is formed.)
- (d) *Audio Signal Injector* To utilise the oscillator (required for continuity) two terminals are provided which will deliver waveforms at 800Hz. One terminal provides a "triangular" wave—or more strictly an exponential sawtooth. The other provides a negative-going pulse wave-

form. Both of these signals have an amplitude of about 3 volts. It would have been easy to provide two additional pots to control both frequency and amplitude but unless a firm hand is taken in the design the panel could end up like a scene from Star Trek.

- (e) *Visual warning of ohms and mA* Many multimeters throughout the laboratories, workshops and backrooms of the world end up in dustbins, their pointers twisted in agony due to a few seconds lapse of attention. The most common cause of this catastrophe is to attempt a voltage reading when the meter is selected on ohms or current. On our in-

FOR
GUIDANCE
ONLY

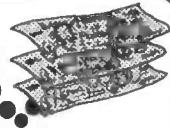

**ESTIMATED COST
OF COMPONENTS ***
excluding V.A.T.

**for all parts
except case
£9.50**

Multi-Tester...

A useful piece of test equipment which can be built from scratch or which can incorporate parts from the Teach-In 76 series

by A. P. Stephenson



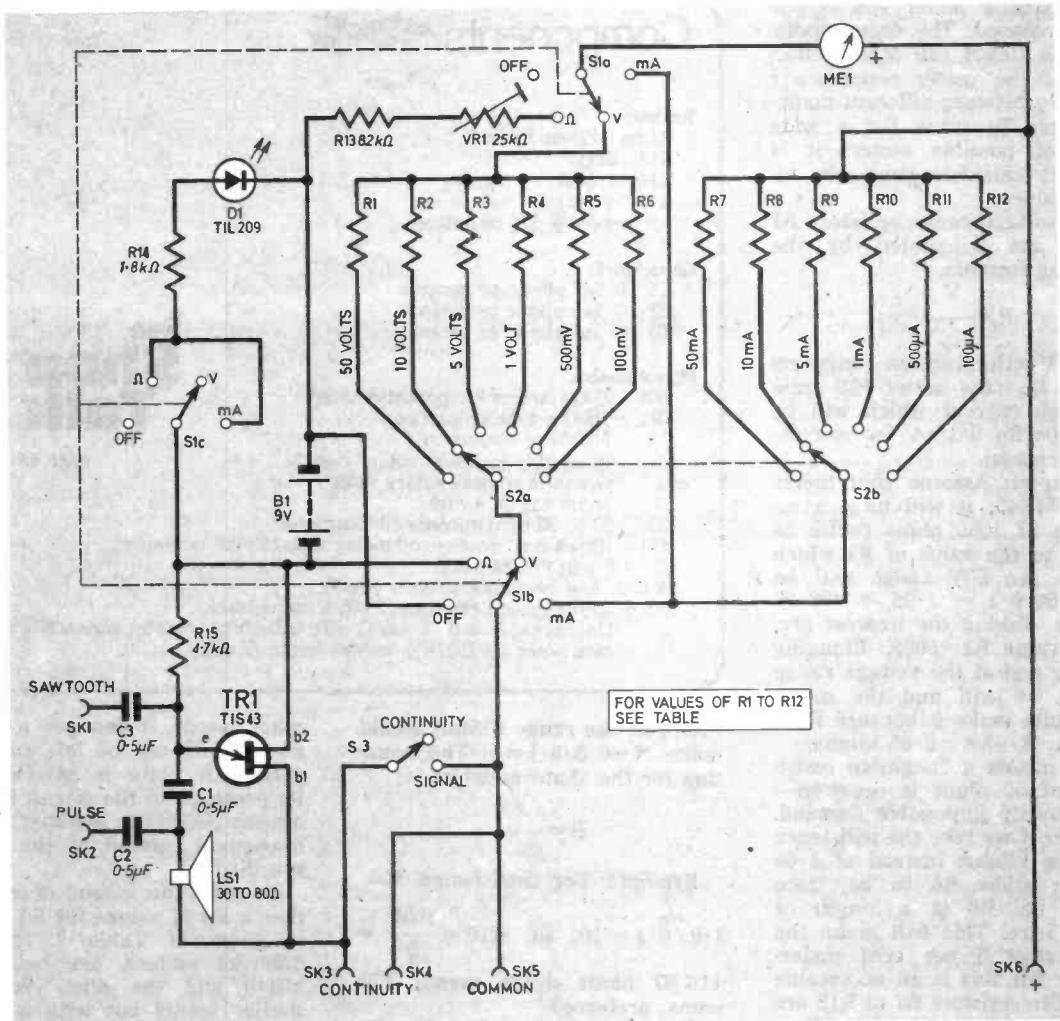


Fig. 1. The circuit diagram of the Multi-Tester.

strument, a red light glows whenever these two ranges are selected—warning the user to take care.

CIRCUIT

Multiway switches are always difficult for the beginner to follow. Switch S1 is used to select which particular function is operative and is defined as three pole—four way. This means that *three separate* switch arms can be moved together by the control knob to any of *four positions*. The separate arms are labelled a, b, and c and the dotted lines indicate mechanical synchronism. Arm S1b is used to switch the common terminal, arm S1a is to switch the negative meter terminal and S1c decides when the l.e.d. warning light comes on. The switch S2 is a two-pole six way

used to select which series resistor is used or which parallel resistor; S2a is the arm which selects the appropriate series resistor when volts is selected and S2b selects the parallel resistor when mA is selected.

The oscillator uses a unijunction transistor (u.j.t.) which generates a sawtooth wave-form at the emitter. Capacitor C1 charges via R15 until the emitter reaches a certain critical voltage which initiates a "short-circuit" action to base 1. This quickly discharges C1 causing a current pulse through the speaker. The action repeats ad infinitum—hence the whistle.

Note from Fig. 1 that oscillations can only start when:

- (a) S1 is selected to off (arm b puts battery negative to the common terminal and the

right hand continuity terminal) and

- (b) either the continuity terminals are shorted or S3 is closed.

The switch S3 is not strictly necessary but does allow the output signals to be on without the need to short the continuity terminals; it can be omitted if desired. Capacitors C2 and C3 are simply blocking capacitors which isolate the d.c. from the pulse and triangular output terminals, rendering them safe to inject into other equipments. The warning light turns on when appropriate and passes about 4mA via R14 and S1c.

RESISTOR VALUES

Notice from Fig. 1 that no values have been given for R1 to R12 because they will depend on

the particular meter you originally purchased. The only stipulation was 100 μ A full scale deflection but the meter resistance r may vary between different manufacturers. To cater for a wide range of possible meters it is better to calculate your own resistor values.

The voltage range resistors R1 to R6 are calculated by the following formula,

$$R = \frac{V}{I_{fsd}}$$

where V =the voltage range required; I_{fsd} =the meter full scale deflection current which will be 100 μ A (write 0.1mA for calculation purposes).

Examples: Assume your meter is the MR45; it will have a resistance of 1050 ohms (write as 1.05K) so the value of R1 which handles the 50V range will be $R1 = 50/0.1 - 1.05 = 498.95$ kilohms. Taking the nearest preferred value $R1=500K$. Plunging to other end of the voltage range (0.1V) we will find the meter can't quite make it because $R6 = 0.1/0.1 - 1.05 = -0.05$ kilohm.

This means a "negative resistance" of 50 ohms is required—an obviously impossible demand. However if we take the resistance r as one kilohm instead of 1.05 we can allow R6 to be "zero ohms", i.e. R6 is a length of copper wire. This will make the 0.1V range 5 per cent underreading but this is an acceptable error. The resistors R7 to R12 are used as current "shunts". They can easily be calculated providing a ratio N is first defined.

Let N be the ratio of required f.s.d. to the meter f.s.d. For

Components

Resistors

R1 to R12 see Table I

R13 82k Ω

R14 1.8k Ω

R15 4.7k Ω

All carbon $\pm 5\%$ or better

Capacitors

C1 0.5 μ F plastic or ceramic

C2 0.5 μ F plastic or ceramic

C3 0.5 μ F plastic or ceramic

Miscellaneous

VRI 25k Ω carbon lin. potentiometer

TRI TIS43 n-type unijunction

DI TIL209 or similar l.e.d.

S1 three-pole four-way rotary switch

S2 two-pole six-way rotary switch

S3 on/off toggle switch

LS1 30 to 80 ohm miniature loudspeaker

ME1 100 μ A d.c. moving coil meter type MR45P or similar

B1 9 volt PP3 battery

SK1, 2, 3, 4 miniature sockets (4 off)

SK5,6 spring-loaded terminal (2 off, 1 red, 1 black)

Double tag-board 14-way (2-off); battery connector; connecting wire; case (Vero 65-2522K); pointer knobs (3 off).

See Shop Talk

page 43

example, the range 0.5mA would make $N=0.5/0.1=5$. The equation for the shunt resistors is:

$$R = \frac{r}{N-1}$$

Example: For 1mA range, $N=$

$$1.0/0.1 = 10 \text{ so } R10 = \frac{1050}{9} =$$

116.67 ohms which means 120 ohms, preferred.

The lowest range 0.1mA will not require a shunt at all because

$$N=1, \text{ so } R12 = \frac{1050}{0} = \text{infinity. In}$$

other words, if you use a 100 μ A meter, R12 can be left out altogether. A place is reserved for its presence in the circuit in case anyone decides to use say, a 50 μ A movement instead of the 100 μ A specified.

To save the labour of calculation, a set of values for R1 to R12 is given in Table I for two different meters, one being the MR45 and the other being a similar model but with a resistance of 720 ohms. (The 720 ohm model appears to be superseding the MR45).

CONSTRUCTION

Commence by drilling the case as indicated in Fig. 2. It is better to provisionally lay out the switches, knobs etc before finally drilling in order to ensure clearance.

Fit all the front panel components. The miniature sockets for continuity and signal outputs can be held in place by a few spots of glue. The small speaker can be fixed by a thin coating of Tensol—not too much and restrict to the outer rim of the speaker. Fit the two tag boards to the side—again use glue to avoid unsightly screws. The tag boards were specified instead of the more usual Veroboard because they are easier for beginners to solder and

Table I: Meter Resistance using 100 μ A Movement

Range and Resistor No.	1050 ohms (MR 45) preferred		720 ohms	
	calculated	calculated	calculated	preferred
50V R1	498.9k Ω	500k Ω	499.2k Ω	500k Ω
10V R2	98.95k Ω	100k Ω	99.28k Ω	100k Ω
5V R3	48.95k Ω	47k Ω	44.28k Ω	47k Ω
1V R4	8.95k Ω	9.1k Ω	9.28k Ω	9.1k Ω
0.5V R5	3.95k Ω	3.9k Ω	4.28k Ω	3.9k Ω
0.1V R6	—50 Ω	zero	280 Ω	270 Ω
50mA R7	2.1 Ω	2.2 Ω	1.44 Ω	1.5 Ω
10mA R8	10.61 Ω	10 Ω	7.27 Ω	6.8 Ω
5mA R9	21.43 Ω	22 Ω	14.69 Ω	15 Ω
1mA R10	116.7 Ω	120 Ω	80 Ω	82 Ω
500 μ A R11	262.5 Ω	270 Ω	180 Ω	180 Ω
100 μ A "R12"	infinity	leave out	infinity	leave out

The available preferred resistors often lead to a few per cent error. For higher accuracy use a preferred value carbon resistor lower than calculated and gently file away the body until the correct reading is obtained.

Multi-Tester...

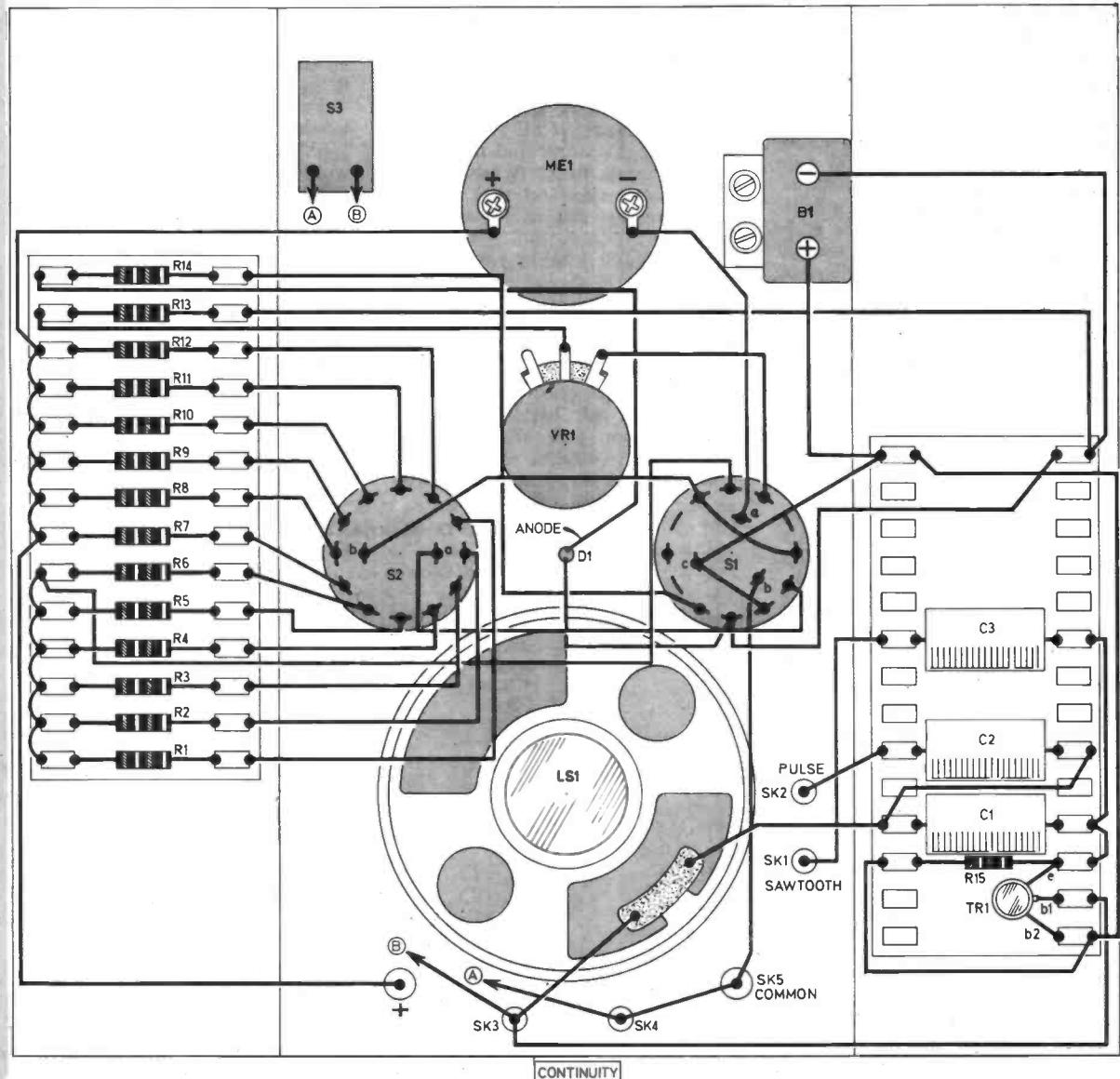
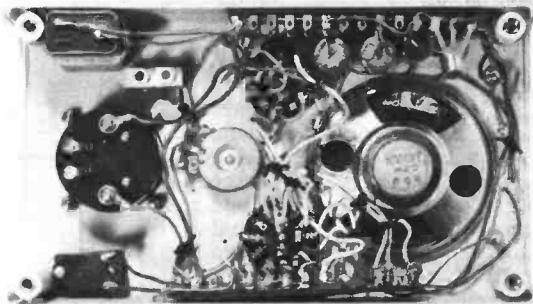


Fig. 2. Construction and wiring of the Multi-Tester.

because they take more kindly to unsoldering if you decide to file some of the resistors; this operation is really a trial and error exercise.

Stick labels on to the tagboard with R1, R2—C1 etc., on them. This is a valuable aid when wiring up and fault finding. Solder the resistors, capacitors and TR1 into position, taking great care that emitter, base 1 and base 2 are correctly positioned.

Wire all connections as shown in Fig. 2 except the wires to the two rotary switches because it is in this area where you are the most likely to make errors. Do not connect the battery yet. Be careful about the l.e.d.—the long wire is the anode and must go to R14.

The two rotary switches must now be attacked. First remove them from the panel, fix a knob to them and check that S2 can only be moved in six positions and S1 can only be moved in four positions. If this is not so, the end-stop locking ring is in the wrong hole. Experiment with different positions until correct. In fact it is wise to test the switch arms with the aid of a battery and lamp to ensure the arms are correctly switching. This will also help you to understand multiple switching, particularly if you draw a diagram to match up with Fig. 1.

Replace S1 and S2 and make sure the underside exactly lines up with Fig. 2 (if you get this wrong, every wire on your switch will be wrong with perhaps disastrous results to your meter). Complete the wiring to the switch. Stick some provisional labels on the front panel prior to testing out. The permanent lettering with Letraset (or equivalent) is best left until after the final test.

TESTING

Install the battery either by using a proper clip or solder direct to terminals. Check that l.e.d. lights when on ohms and mA. Switch S3 to signal and selector switch to off. The speaker should whistle. Switch S3 to continuity and the whistle should stop. Short continuity terminals with a piece of wire. Whistle should sound again.

Do not proceed with further tests until the previous tests are proved. Check wiring if faults exist.

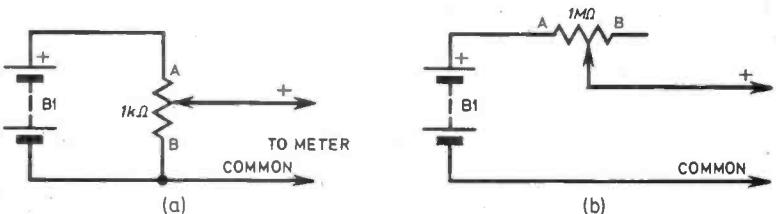


Fig. 3. Connections for testing the Multi-Tester.

Switch to ohms and momentarily touch the meter leads together. The needle should go calmly to about full scale. Keep leads together and adjust zero ohms for exactly full scale.

The word calmly means just that. If the needle rushed like mad across the scale, stop testing and re-check wiring. In fact it is important in all these tests to expect the worst and the habit of the "quick flick" (whilst keeping a fixed stare on that expensive meter) should become a ritual.

Test a 100 kilohm resistor on ohms scale. It should read a little less than half-scale.

The volts range should now be systematically checked by the following method, see Fig. 3(a):

Connect a one kilohm pot across a 9 volt battery and use the "bottom and slider" as a source of voltage, controllable from zero to 9V. Set the control

to the zero-volts end, set the meter to 50 volt range and connect the voltage. Very slowly advance the control until the meter begins to read. At full 9 volts, the meter should read just under 1/5th full scale. Repeat again on 10 volts range, and then through to 1 volt range.

To test the 0.1 volt range it would be better to change to a 1.5V battery because the control would be too fierce at the bottom end. While performing these checks a reasonable estimation of meter accuracy can be obtained by comparing the degrees of rotation of the pot with the scale reading (the pot must be linear—log pots are useless for this purpose).

To check the current ranges is a somewhat hazardous task because, unlike voltage ranges, a badly soldered parallel resistor (R7 to R12) will result in all the test current passing through the

Table 2: Ohms Scale Calibration

R_x	Meter Reading (N)
(approaching full scale deflection)	
10kΩ	0.9
20kΩ	0.82
30kΩ	0.75
40kΩ	0.69
50kΩ	0.64
60kΩ	0.6
70kΩ	0.56
80kΩ	0.53
90kΩ	0.5
100kΩ	0.47
200kΩ	0.31
300kΩ	0.23
400kΩ	0.18
500kΩ	0.15
600kΩ	0.13
700kΩ	0.12
800kΩ	0.1
900kΩ	0.09
1MΩ	0.08

The relevant formula, in a convenient form, is

$$N = \frac{1}{1 + 0.0111 R_x}$$

Where N = the fraction off.s.d. produced and R_x is the resistor being measured in kilohms.

poor meter. (Most of it is supposed to be diverted through the parallel resistor).

A source of test current can be obtained by using a 9V battery and one megohm pot, but using only one outer and the slider—in fact using the pot as a series resistance as in Fig. 3(b). Make sure the resistance is initially set to maximum and connect the meter set to 10mA range. Only $9\mu A$ can pass so the meter cannot be harmed even if there is a fault. The meter actually should barely read at all.

Very slowly advance the control and somewhere near the bottom end the meter should start to rise sharply. Stop this test and start again with the meter set to 5mA then 1mA then 0.5mA and finally 0.1mA.

Then recheck the higher current ranges again using a one kilohm pot which can now deliver a minimum of 9mA.


The initial tests are now complete.

FINAL COSMETIC TREATMENT

Remove the knobs (and the switches if they are in the way) and label the panel carefully with Letraset or similar type lettering. The marking of the meter scale itself is tricky. Carefully remove the meter cover and mark out the ohms scale by using known resistors and putting pencil points at, say, 5k, 20k, 50k, 100k, 1M, 10M. Don't attempt too many because you will find difficulty in fixing the numbers. This can be done with the scale removed, using a very fine pen and Indian ink or very small transfers. (Table 2 can be used if desired.) If you think this task is too difficult paste Table 2 to the back of the instrument and convert the readings.

Finally fix a crock clip to the common flex lead and make some sort of probe to fix to positive lead—brass rod or knitting needle

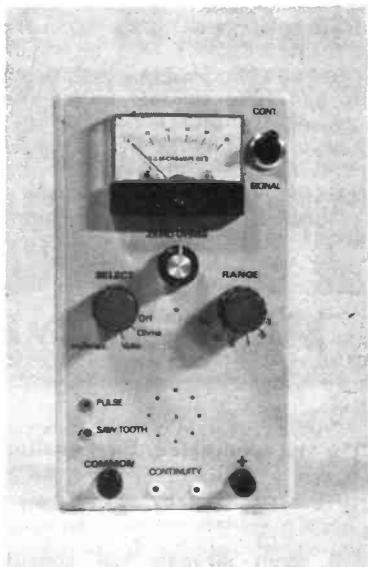inside a ball point pen makes a good probe. Make up two longer leads to plug into the continuity terminals. □



machine on and the dot of light began to move in all directions, first this way and then that, quite at random. Your job was to keep it right in the middle by the use of your two controls. If you allowed it to move outside the square a mark was recorded against you.

As a further distraction, there was a small lever on your left hand side, and if a red light came on you pushed it forward, and if a green light came on you pulled it back. The machine ran for about four minutes and then switched itself off.

I climbed in and all the doctors crowded round to see how I would make out. Then they switched on. At the end of the allotted time I had chalked up four errors. The doctors were amazed: nobody up to then had scored under twenty. Being big headed even at that early age, I said let me have another go. This time my errors were nil.

To me the interesting thing was this, that the second time I kept the dot in the centre of the cross the whole time, and to do this I must have foreseen which way it was going to move and made the corrections just as it was about to happen. In other words I was looking into the future, admittedly only by a fraction of a second, and although I have thought about it many times since I can see no other explanation.

So if you have an old cathode ray tube and a couple of pots, you might like to knock up one of these contraptions yourself one Sunday afternoon. Then you can test out whether you have pilot potential, or, more interesting still, if you have E.S.P.

Here's to looking into the future and hoping it's bright.



I WANT to talk about E.S.P., or Extra Sensory Perception. This covers such things as telepathy, precognition, and psychokinetics.

Professor J. B. Rhine established with a fair amount of certainty, that we are able to see a short distance into the future, a matter of seconds, perhaps minutes, and many years ago I proved it, at least to my own satisfaction.

At the beginning of World War II the King decided to give me his commission, but first he decided to send me to Oxford for a medical examination to see if I was fit enough. Now at this time thousands of would-be pilots were striving to enter the Royal Air Force. Many were highly unsuitable; for example, it is a great advantage, if you want to be a pilot, if you can co-ordinate your arms, legs, and eyes. So the boffins were trying to invent a gadget that would speed up the selection.

When I arrived at Oxford they had just received the first prototype. They had tried it out on themselves, and also

on some of their new entrants, but they had never yet had a real live pilot to try it out on. Now they had one in the shape of Pilot Officer Young. Needless to say, they pounced on me, and said you must try out our new machine.

The machine consisted of a small cockpit which you sat in and between your legs was a joystick which would move backwards and forwards, and on the floor in front of you was a rudder bar on which you placed your feet. When seated you found yourself facing a cathode ray tube about a foot in diameter. On the screen was a small dot of light. The joystick made it traverse up and down, and the rudder pedals made it traverse from side to side. By combining the two you could make it move anywhere on the screen. However that was not the idea.

In the centre of the screen was marked a small square about 100x100mm, and in the centre of the square was a small black cross. When you were ready they switched the

DO MATHS BOTHER YOU?... LET'S FIGURE IT OUT

Part 2 By PHIL ALCOCK

To THE UNINITIATED, the equation

$$V_{AB} = I(R_1 + R_2)$$

will seem strange and convey nothing, yet the equation is a very useful concept and is really just a form of shorthand notation. The letters or symbols V , I , R_1 , R_2 are used to represent the values of certain electrical quantities according to some specific code.

Thus " V_{AB} " could stand for voltage, " R_1 " could stand for the resistance of a component (shown as R_1) in some diagram, and " I " could stand for the value of a particular current in the circuit, also possibly shown on the diagram. We use letters simply as a shorthand notation, especially if the actual value of the component is not yet known. Thus the above equation in words might read as follows:

The voltage between points A and B (V_{AB}) is equal (=) to the sum of the two resistance values ($R_1 + R_2$) multiplied by the value of the current (I).

Obviously the equation is a big space saver. In addition, equations can be manipulated to achieve some particular purpose. If the values of V_{AB} , R_1 and I are known, then the equation can be rearranged to allow us to find the value of R_2 that satisfies the equation, i.e. makes the equation correct by producing the same value on both sides of the equal sign (=).

The equation is rather like a "balance" type of weighing machine in which the contents of

one pan are compared against the contents of the other with the system at balance.

We can change one side of the equation in any way we wish providing we make similar changes to the other side to keep the balance. Notice that in the above equation the sum of the two resistors is shown enclosed inside a bracket ($R_1 + R_2$). This means that we treat the contents of the bracket as one entity.

Since I multiplies the "bracket" it must multiply all the contents of the bracket, not just the first term R_1 . Notice that the normal multiplication sign (\times) is not shown but is implied, i.e.

$I \times (R_1 + R_2)$ is written $I(R_1 + R_2)$

Rather than listing the various algebraic operations in a formal manner the following examples illustrate some of the important features of basic equations and the guidance notes for each should be studied carefully.

Since circuit diagrams may employ several resistors it is usual to show these in EVERYDAY ELECTRONICS as R_1 , R_2 , R_3 , etc. Do not confuse this with say $2.R$, $3.R$ which means $2 \times R$ and $3 \times R$ respectively. In some cases, subscripts are used to avoid possible confusion, e.g. R_1 , V_{AB} , h_{fe} , etc. Where ambiguity may exist the use of brackets can help. Thus $10(R)$, $I(R_1)$, etc.

Continued next month

Table 2.1 Some Mathematical Terms Explained

Shorthand Notation	Guidance Notes
$A - B$	Subtract quantity B from quantity A
$A + B$	Add A and B together
$V \times I$ or V/I	Multiply V and I together
$V = 6$	V equals 6 (units are normally shown)
$R/6$ or $R \div 6$	Quantity R is divided by six
$I(R + 6)$	Add R and 6 together, then multiply result by value of I
$I.Y - 10$	Multiply I and Y together, then subtract 10 from result
$R > 10$	Value of R is greater than 10
$R_1 < 5$	Value of R_1 is less than 5
$V_z \geq 4.7$	Voltage V_z is equal to or greater than 4.7 (subscript "z" may stand for some word, such as Zener)
$R \approx 22 \text{ k}\Omega$ or $R \approx 22 \text{ k}\Omega$	R is approximately equal to $22 \text{ k}\Omega$
ΔI or ΔI	Usually means "A small change in the quantity I"
$\%$	Percentage (one hundredth part of)
$[]$, $()$, $\{ \}$	Different shapes of brackets
10^3	10 multiplied by itself 3 times, i.e. $10 \times 10 \times 10 = 1000$

Next Month...

Wiper Delay

The dirty weather is now with us and this windscreens wiper delay unit will help keep your screen clean when it is not raining hard enough to keep the wipers on continuously.




Electronic **STOP CLOCK**

An unusual design with many applications.



Guitar Practice Amplifier

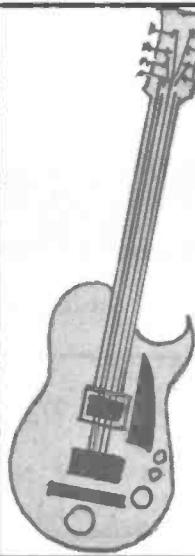

A small amplifier unit which can feed either a speaker or headphone for private practice anywhere.

Transistor Checker

Simple unit for checking basic parameters of transistors and diodes.



**Plus POPULAR FEATURES
for EVERYONE!**

Avoid



disappointment

REGULAR ORDER



by PLACING A

WITH YOUR

NEWSAGENT... NOW!

everyday electronics

FEBRUARY ISSUE ON
SALE FRIDAY
JANUARY 21

SPECIAL Introductory OFFER! for E.E. Readers


ADCOLA SOLDERING KIT

WITH SAFETY APPROVED IRON

£5.95

Inclusive of post and packing

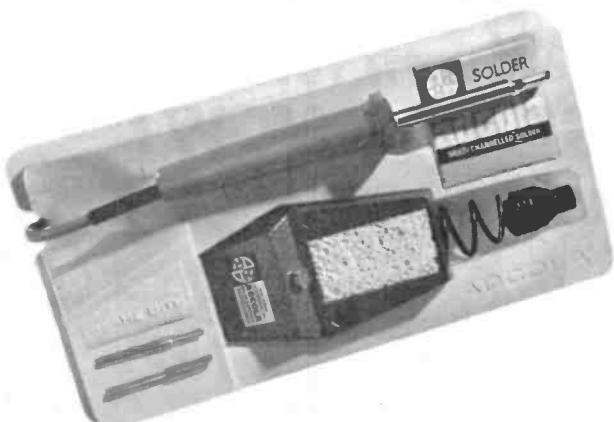Manufacturer's recommended retail price £6.75



A new soldering instrument is the star feature of this Adcola Products soldering kit. It has been developed to conform generally to British Standard BS 3456, 2:14 and to worldwide safety precautions. Known as the Invader "S" 646—the "S" stands for "safety"—it is flash tested at 2,000 V (far in excess of most safety standards) and the accent is on complete user safety without sacrificing efficiency or ease of use. The iron is thermally controlled to provide a constant level of the correct heat for soldering at 400 degrees C. Each model weighs less than 2 oz, and two metres of cable, fitted with a cable protector, are provided. The standard soldering tip provided is $\frac{1}{16}$ in. (4.7 mm) diameter but two alternative bits of $\frac{1}{8}$ in. (3.2 mm) and $\frac{1}{4}$ in. (6.3 mm) diameter are included to provide complete versatility in use. These bits are easily inserted in the hexagonal shim at the end of the tool as required.

An invader stand is also contained in the kit to provide the user with a mobile and safe receptacle for the hot soldering instrument. The stand features an integral sponge for cleaning excess solder from the soldering bits and two holders to contain the spare bits. A wide angle spring holder is mounted on the base of the stand at an angle of about 45 degrees and the soldering tool is simply inserted into the holder when not in use.

To complete the kit a packet dispenser of Adcola solder wire—which contains its own flux—and a guide to soldering are also included.

The kit is presented in an eye-catching pack consisting of a lemon coloured plastic tray which incorporates recessed areas to locate each part. This base is covered by a crystal clear plastic lid to display the components in an effective manner.

Remittances must be by postal order or cheque (name and address on back of cheque please), crossed, and made payable to Adcola Products Ltd.

Please allow
28 days for delivery

Please complete both parts of the coupon below in BLOCK CAPITALS

To: Adcola Products Ltd. (E.E. Offer)
Adcola House, Gauden Road, London SW4
6LH

Please send me the Soldering Kit(s) as indicated at £5.95 each.

I enclose P.O./Cheque No.....Value.....

No. of kits required

Name

Address

Tel. No. (Home or Work)

No. of kits required

Name

Address

From: Adcola Products Ltd. (E.E. Offer) Adcola
House, Gauden Road, London SW4 6LH

Cut Round Dotted Line

BRAKE LIGHT WARNING DEVICE

By T.I.R. de Vaux-Balbirnie
B.Sc.

IT is an offence to drive a motor vehicle with defective brake lights. Along with checking tyres and so on, the careful driver would see that his brake lights were working correctly each time he drove the car. It is a safe assumption that few people do this and even if the will is there it is not an easy job without assistance.


Of course, a bulb may blow at any time in the course of driving and this is unlikely to reach the driver's attention for some time. Meanwhile, it will be causing annoyance and possible danger to other road users because intermittent use of the brakes could easily be mistaken for a turning signal—remember that red is a legal colour for rear traffic indicators. A false right turn signal could be especially dangerous for a following car.

There certainly seems to be a case for a device which will signal the driver in the event of failure in the brake light system. This could be due to a bulb blowing or a faulty earth connection at a lighting unit at the rear of the car. The suggested circuit would give a visible dashboard warning when the brakes were applied. If the circuit as a whole is at fault e.g. due to a blown fuse the circuit will not work. Usually this sort of fault is quickly apparent because other electrical equipment fails at the same time.

CIRCUIT DESCRIPTION

The circuit diagram of the Brake Light Warning is shown in Fig. 1. It has been designed for

FOR
GUIDANCE
ONLY

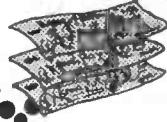

**ESTIMATED COST
OF COMPONENTS**
excluding V.A.T.

£1.00


excluding case

a 12 volt negative earth system as this is used in most modern cars. The unit uses an operational amplifier type 741. This device has two inputs one inverting (-) pin 2 and one non-inverting (+) pin 3. The 741 has very high gain and the output is proportional to this gain and the difference in voltage present at the two inputs with respect to ground; thus the output can be moved towards either supply line.

Imagine two positive voltages one applied to pin 2 and the other to pin 3. These voltages are measured with respect to the negative "earth" line. If the pin 2 voltage is greater than the pin 3 voltage the output will go to "earth" potential. Under these conditions, the l.e.d. indicator D1 turns on. If the conditions were reversed i.e., if the voltage at the inverting input were less than that at the non-inverting input the l.e.d. would remain off. A filament light indicator would be unsatisfactory as its power consumption would be too great.

The input voltages to the

Fig. 1. The circuit diagram of the Car Brake Light Warning Device.

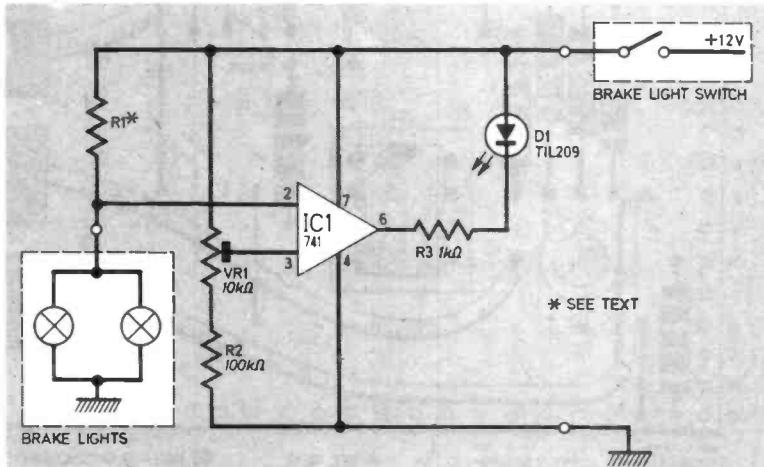

operational amplifier are derived from potential dividers across the supply lines. An adjustable reference voltage is produced by means of the divider action of R2 and VR1 in series. The input to pin 3 being taken from the wiper of VR1. The latter is used for limited fine adjustment. With VR1 set to midway position there is about 11.5 volts on pin 3.

The voltage at pin 2 is derived from the divider action of R1 in series with the two brake lamps (in parallel).

By choosing a suitable value for R1 it is possible to obtain a similar 11.5 volts or so at pin 2 with both lamps working. Due to the potential divider action, however, this voltage will be higher if one bulb fails and will be the full 12 volts with both out of action. By adjusting VR1, a setting can be found when the pin 2 voltage will be slightly less than the pin 3 voltage with both lights on, but slightly greater when only one light (or both) is off. This critical setting for VR1 will be found when setting up.

It should be noted that the half-volt drop mentioned above means that half a volt less will be available to operate the stop lights. This is perfectly in order and no difference in brightness should be noticed. In any case, this small voltage drop is well within the differences which may be expected from other causes.

VALUE FOR R1

A calculation is needed to give the value of R1.

A standard brake light bulb is rated at 21 watts so the total wattage is 42 watts.

The current in the brake light circuit with both lamps working is given by $(W/V) = (42/12) = 3.5$ amps.

As the voltage required across R1 is 0.5 volt, then by Ohm's law $R1 = (V/I) = (0.5/3.5) \approx 0.14$ ohms. The power rating for R1 is given by $W = I \times V = (3.5 \times 0.5) = 1.75$ watts.

Theoretically R1 should be a 0.14 ohms resistor rated at 2 watts or so. This causes a problem because this sort of value is far away from those used in most electronic circuits. The constructor has two possible courses of action. He can either make his own resistor from scratch, or use a combination of easily obtainable types.

A home-made resistor was made using resistance wire for the prototype and this worked very well.

Alternatively, four 0.47 ohm $\frac{1}{2}$ watt resistors can be wired in parallel to give a value of 0.12 ohms which is near enough to the required value. This method is shown in Fig. 2.

Resistor(s) R1 becomes quite warm in prolonged operation and should be stood away from the

circuit board to allow the heat to dissipate unimpeded.

The purpose of resistor R3 is to limit the current through the l.e.d. to a safe level. Its value may be reduced to about 470 ohms if slightly more brightness is required.

COMPONENT BOARD

The circuit was built on a piece of 0.1 inch matrix stripboard size 16 strips by 19 holes. The layout of the components on the board is shown in Fig. 2; it is not critical and may be changed to suit individual requirements.


It is recommended that an i.c. socket be used to mount IC1 thereby eliminating possible damage from soldering iron heat; removal is an easy matter should it be necessary.

Begin by making the breaks on the underside of the board, fix the terminal block and then solder the link wires in position followed by the resistors, preset, i.c. holder. Finally solder the flying leads to the l.e.d. and wire up to the fitted terminal block. Use heavy gauge wire for the positive supply lead as this will be carrying about 3.5 amps.

FITTING IN THE CAR

When the circuit has been built and carefully checked it will be necessary to connect it temporarily in the car to make the

Fig. 2. Complete wiring up details and layout of the components on the circuit board.

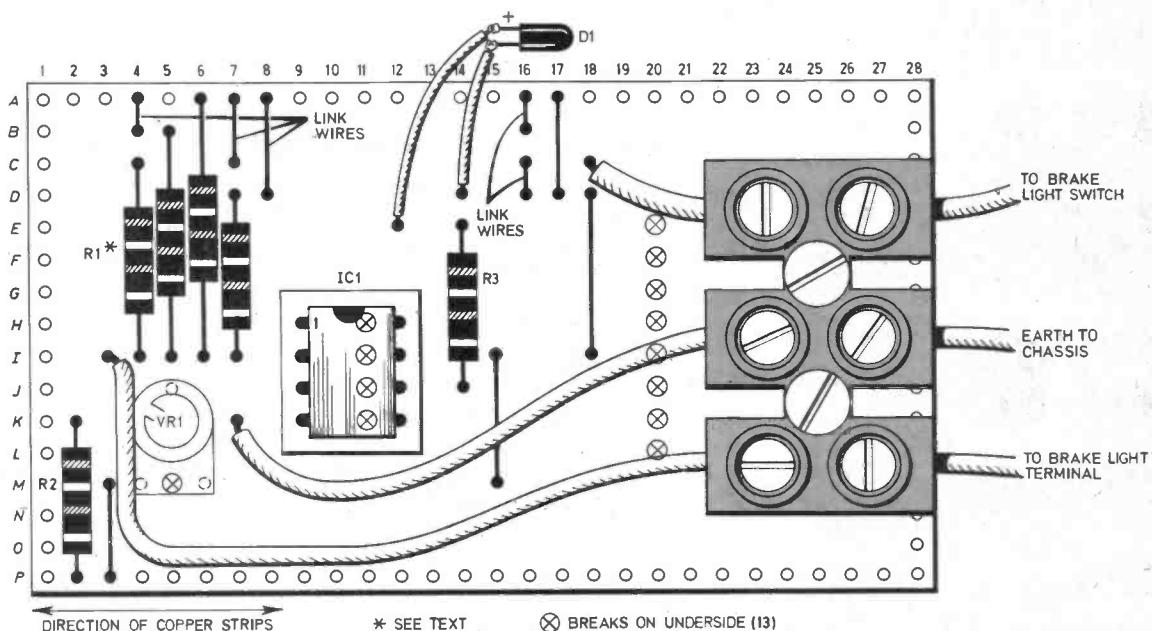

Components



Resistors

R1 See text
R2 100kΩ ±W
R3 1kΩ ±W
All carbon ±10%

Semiconductors

IC1 741 operational amplifier 8 pin d.i.l.
DI TIL209 or similar l.e.d.

Miscellaneous

VR1 10kΩ horizontal preset
Stripboard 0.1 inch matrix 16 strips x 19 holes; 8 pin d.i.l. socket; 5A terminal block; auto-type wire; case; spade connectors.

See **Shop Talk**

(apart from the actual earth connection). When finally fitting it this must also be observed.

To check operation of the circuit, the ignition switch must be operated and the brake pedal gently pressed. VR1 should then be adjusted until the l.e.d. comes on. It should then be backed off until the light just goes out. With one of the brake light bulbs removed to simulate a fault, the l.e.d. should light. The operation may be checked with the other bulb removed and then both bulbs removed. Adjustment of VR1 should be made to give reliable operation.

If all is well, the unit may be fitted in the car permanently. It is suggested that the unit be enclosed in a small plastic container, such as those used for holding soap, and the leads brought out through holes drilled in the side.

The l.e.d. needs to be mounted in an easily visible place on the car dashboard. Red is the obvious colour choice for the l.e.d., but green or yellow could be used especially when other red indicators are in use. The appearance of the project could perhaps be enhanced by using an l.e.d. with a chrome bezel.

Replacement of one or both the brake light lamps should not demand resetting of VR1.

Having built and installed this warning device the only trouble is you will probably drive for thousands of miles without so much as a wink from the l.e.d. One day, however, the faithful little light will glow and keep you out of trouble. □

operational checks and to set VR1, unless the constructor has available outside the car a car battery and two 21 watt bulbs. The circuit will not work properly if the correct wattage bulbs are not used, so a high power battery is necessary for setting up.

When connecting the circuit to the car's electrical system it is wise to disconnect the car battery. This will eliminate the possibility of inadvertent shorts. The necessary precautions should be taken i.e. proper wire should be used, bought from a car accessory shop, rather than the wire used for general electronics work. Single strand wire must not be used as it soon breaks under vibration. When wires have to be led through holes in the car body work grommets should be used.

Using the car wiring diagram locate the wire which leads from the brake pedal switch to the

brake lights. This should either be cut at a convenient point or disconnected from the switch itself and then an extension fitted to the switch. From the two new ends, extension wires of the right type should be made up, and led to a convenient place close to the dashboard for connection to the board. A third connection from the circuit board terminal block should be made to a nearby earth point, i.e., joined to the metal body of the car.

If such a point is not to be found, then a small hole will need to be drilled and a self-tapping screw fitted. The wire may be soldered into the form of a loop to go under this screw or a proper "eye" attached to it.

Before reconnecting the car battery to make the tests, care should be taken to ensure that the circuit is entirely isolated from the metalwork of the car

JACK PLUG & FAMILY...

YOUR DAD SAYS THE BLEEP FROM HIS CLEAR SKY INDICATOR LACKS CLARITY, SO HE'S RECONSTRUCTING THE WHOLE THING AND INCORPORATING A SCRATCH AND RUMBLE FILTER.

DO YOU SUPPOSE HE'S STILL FEVERISH FROM THAT LAST ATTACK OF FLU?



The Extra-ordinary Experiments of Professor Ernest Eversure

by Anthony John Bassett


THE Prof. showed the boys how to set the bias on each of the Darlington power transistors of the impedance-converter.

First he connected the input terminal to the zero voltage tag on the tag board, and connected the output terminal to an 8-ohm wirewound resistor wired to the zero voltage terminal of the power-supply, then re-connected the mains to the power-supply and once again switched on.

BIAS ADJUSTMENT

He switched a multimeter to measure millivolts, and connected it from the emitter of the MJ3001 Darlington power-transistor to the output terminal. At first there was zero reading on the meter, but the Prof. carefully adjusted VR1 until the meter needle moved slightly to give a reading of a few millivolts.

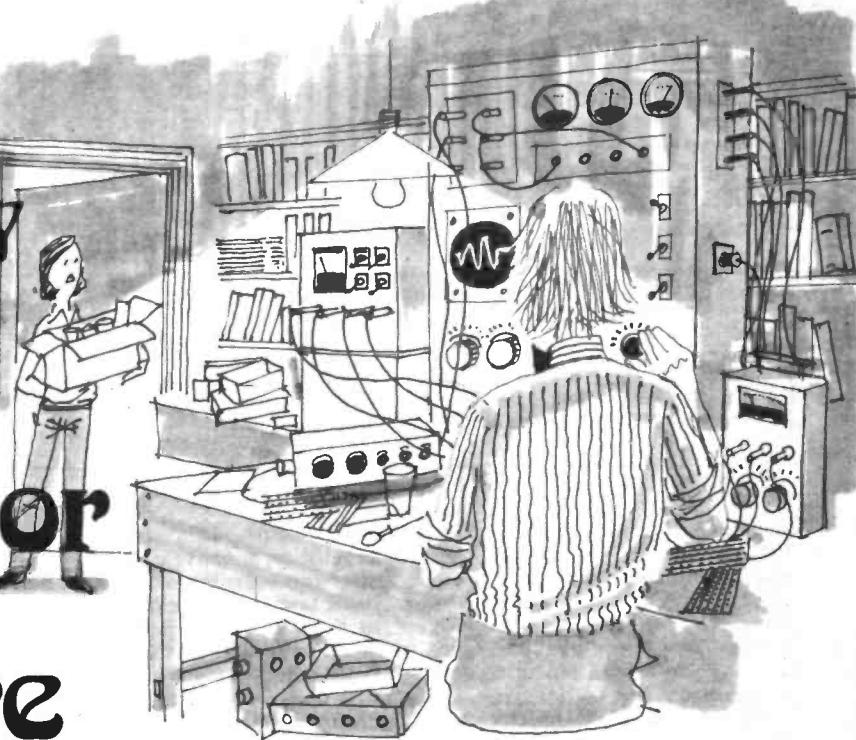"Because we are measuring the d.c. voltage across a 0.47 ohm resistor," the Prof. informed Bob, "every 0.47mV we measure will be an indication of 1mA flowing in the resistor. To obtain a current of 20mA we would need to adjust the preset until the voltage across the resistor is 9.4mV. But to begin with we will set it a little lower."



The Prof. adjusted VR1 until the meter reading was 5mV, then transferred the meter leads to measure the voltage across the other 0.47ohm resistor. This he adjusted by means of VR2 until a reading of 5mV was obtained here also.

Now by alternate small adjustments to VR1 and VR2 he brought the voltage across each resistor up to about 10mV, then by final small adjustments, with the meter connected across the 8ohm resistor he brought the voltage across this resistor to zero, then switched the mains supply off.

Allowing a few minutes for the power-supply capacitors to discharge, he explained to Bob and Maurice: "When the input of the impedance-converter is at 0V, its output should also be at 0V, as it is a d.c. coupled circuit, and I have used VR1 and VR2 not only to adjust the quiescent current to a suitable value, but also to 'balance out' component tolerances and bring the output voltage to zero, so that when the circuit is in use there is no flow of current in the speaker until a sound is produced".

IMPEDANCE

Now Maurice, who had been

contemplating the circuit diagrams thoughtfully, asked, "What is the input impedance of the converter, Prof?"

"A few kilohms, Maurice," the Prof. replied.

"Then how does it match the output impedance of the amplifier, which is only 8 ohms?" Maurice wanted to know, "Because according to one of these circuit diagrams we are connecting it to convert an impedance of 8 ohms to one of 4 ohms (Fig 1), yet if we connect the 8 ohm output of an amplifier to a load of several kilohms surely this might cause damage to the amplifier."

"I wondered who would be the first to spot that," commented the Prof., "and although most modern transistorised amplifiers would not be damaged by too high an impedance, some amplifiers are vulnerable to this condition. So the impedance-converter which we have built is designed to operate in a slightly different manner (Fig 2). Here the high impedance of the input of the converter is placed in parallel with one of the speakers, and does not make much difference to the load seen by the amplifier. Then the output of the converter drives a further 8 ohm speaker."



DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions £3.45 including post & VAT. Made up model £1.00 extra.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor condensers and instructions. Real snap at only £1.50 VAT & Postage 50p.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £7.95 plus 95p VAT & Postage



MOTORIZED DISCO SWITCHES

With six 10 amp changeover switches. Multi-adjustable switches are rated at 10 amp each so a total of 2000W can be controlled and this would provide a magnificent display. For mains operating £4.25 post & VAT Paid. Ditto 9 switch £4.95 Post & VAT Paid. DITTO BUT 12 SWITCH £5.75 POST & VAT PAID.

SWITCH TRIGGER MATS

So underneath is undetectable carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in £2.33. Post & VAT 50p.



MAINS TRANSFORMERS

All standard 230-250 volt primaries £ p
24v 5 amp 1.05
6.3v 2 amp 1.57
6.3v 3 amp 2.19
9v 1 amp 1.19
9v 3.6 amp 3.13
12v 1.4 amp 1.45
12v 1 amp 1.25
6.5v-0.6-6v 1 amp 1.85
18v 1 amp 1.85
24v 2 amp 2.82
24v 3 amp 4.75
12-0-12v 50mA 1.56
6.0-6v 50mA 1.56
8.0-8v 1 amp 1.85
25v 1.4 amps 2.44
50v 2 amp & 6.3v 1 amp 5.63
60v 5 amp & 6v 1 amp 9.95
27v 8 amp 5.63
30v 37 amp 27.50
80v tapped 75v & 70v 4 amp 6.87
250v-60mA & 6.3v 1.6 amps 1.19
270v-0.275s at 90mA & 3 amps 2.62
6.4v EHT Transformer 5000v 23mA (Intermittent) 6.87
Charger Transformers 6v and 12v 2amps 1.87
6v and 12v 3amps 2.82
6v and 12v 5amps 4.25
Add 30p per £1 to cover postage and VAT

MULTI SPEED MOTORS

Six speeds are available 500, 850 and 1,100 r.p.m. and 7,000, 9,000 and 11,000 r.p.m. Shaft is 1 in. diameter and approximately 1 in long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia x 5 in. long. Price £2.00 including Post & VAT.



SPIT MOTOR WITH CARTER GEAR BOX

Probably one of the best spit motors made. Originally intended to be used in very high priced cookers, however this can be put to plenty of other uses, for instance your garden barbecue or to drive a tumbler for stone polishing; in fact, there are no ends to its uses. Normal mains operation. £3.25 including POST & VAT.



TELESCOPIC AERIALS

for portable car radio or transmitter. Chrome plated—six sections, extending from 7s to 47in. 50p + 10p. Post & VAT.

NUCKLED MODEL PORT F.M. 80p + 17p Post and VAT.

RADIO STETHOSCOPE

Easiest way to fault find, traces signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece, £2.95, twin set instead of earpiece. £1.00 VAT and postage incl.



MULLARD UNILEX


A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Celestion speakers normally £8. This should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £17 including VAT and postage.



TANGENTIAL HEATER UNIT

This heater unit is most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £5.83 plus VAT & post £1. 2kW Model as above except 2kW £4.25 plus VAT & post 75p. Don't miss this. Control Switch 44p. P. & P. 40p.

ISA ELECTRICAL PROGRAMMER

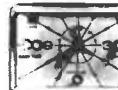

Leave in your sleep! Have radio playing and kettle boiling as you wake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.95, VAT & Postage 60p, or with glass front, chrome bezel, £1.50 extra.

ROOM THERMOSTAT

Famous Batchwell, elegant design, intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0-30°C. Special snap this month £2.50, post and VAT paid.

ITS FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous lists.

Price Postage

Mullard Unilex with £8.8" round speakers	17.00	1.50
Full-Fi stereo amplifier in teak-look case	9.95	1.00
7 watt stereo amplifier with pre-amp and control	7.00	.40
Buzzo amplifier for headphones	3.50	.25
Luxistor amplifier in case with speaker	8.50	.50
AM/FM Tuner with scale and drive shaft	11.50	.40
FM Tuner with scale and drive shaft	9.00	.40
Decoder for stereo to work with above tuner	9.50	.40
Celestion 8" speaker 12½ watts	4.00	.75
10 Watt Speaker System in polished wood cabinet	9.00	3.00
5 Watt Speaker in wood cabinet	4.50	1.50
Heavy duty Light Dimmer, 1250 watts, disco model	12.50	2.00
2000 watt motor driven disco light flasher	4.25	.20
9 Switch motor driven disco light controller	4.00	.20
Black light (UV) lamp for disco	7.00	.50
Sound to Light unit	8.50	.25
Remington 7 transistor pocket radio	2.00	.20
Crystal set kit	2.00	.25
BBG Glenbourn Auto Changer, ceramic cartridge & clutch arm	10.95	1.50
Atlas car battery charger with panel meter, 6v and 12v	3.50	1.00
Battery charger kit-transformer	2.25	.50
—full wave rectifier & flush meter	2.40	.80
Motorised car aerial 12v with controls	3.95	.40
Autoset Timer heart 24 hours on/off	7.00	.30
Smiths Central heating controller	7.50	.90
Randall central heating controller	7.00	.30
Horstmann central heating controller	6.00	.30
Clock with 25 amp switch	3.00	.30
Clock with 25 amp switch, but with glass front & chrome bezel	4.50	.30
12v Mains unit for driving models, cassette, etc.	2.95	.40
Drill speed controller kit	2.50	.40
Drill speed controller, but made up	3.95	.40
Battery operated fluorescent light unit 12"	3.05	1.00
ICE Multi tester, 40 range	15.85	.65
ICE Multi tester, 80 range	24.30	.85
Multi-range test meter C1000.	4.95	.30
Pack of 8 battery motors for model making	2.00	
5 Computer boards (at least 250 components, I.C.s, etc.)	1.00	.50
Batteries (10-7v) pack of 25	1.00	.40
Antex soldering iron kit	4.50	.45
Twin output power packs 6v, 7½v, 9v, 12v, 24v (state volt)	3.50	.40
PC board marker pen	.99	.10
Fluorescent kitchen light 20 watt with tube	2.95	1.50
Jug heater 900 watt immersion heater	3.50	.30
Multi-speed motor	1.50	.45
Automatic night light switch 240v	4.00	.25
Automatic night light switch 12v	1.50	.25
Immersion heater 2kw, standard fitting	2.00	.60
Soil heating kit	3.50	.75
Claymore Intercom/Baby Alarm	5.75	.20
Technical books published by Iliffe—		
50 Photo electric circuits and systems	1.30	
110 Transistor Projects	1.40	.10
20 Solid State Projects for the home	1.00	or two or more post free
20 Solid State Projects for the car and garage	1.20	
110 Integrated circuit projects for home constructors	1.20	
110 Semiconductor projects for home constructors	1.20	
International data books	1.20	
Digital equivalent tables (128 pages)		
Transistor data tables (227 pages)		
Transistor equivalent tables (176 pages)		
Thyristor data tables (169 pages)		
Photoelectric circuits and systems	1.30	
110 Transistor Projects	1.40	.10
20 Solid State Projects for the home	1.00	or two or more post free
20 Solid State Projects for the car and garage	1.20	
110 Integrated circuit projects for home constructors	1.20	
110 Semiconductor projects for home constructors	1.20	
International data books	1.20	
Digital equivalent tables (128 pages)		
Transistor data tables (227 pages)		
Transistor equivalent tables (176 pages)		
Thyristor data tables (169 pages)		

TERMS: Where order is under £5 please add 40p surcharge to offset packing expenses

J. BULL (ELECTRICAL) LTD.
(Dept. E.E.), 103 TAMWORTH ROAD,
CROYDON CR9 1SG.

Sparkrite mk2

Capacitive discharge electronic ignition kit

VOTED BEST OF SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition and up to 8 cylinders.

THE KIT COMPRIDES EVERYTHING NEEDED

Ready drilled, pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device. Includes switch connectors, mounting bracket and instructions. Cables excluded. Also available: RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Croydon tuning and fitting service - phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

Note: vehicles with current impulse tachometers (Smiths code on dia. RV1) will require a tachometer pulse slave unit. Price £3.35 inc. VAT post & packing.

POST TODAY!

**Quick installation
No engine modification required**

Electronics Design Associates, DEPT EE/1
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQ'D.
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's for £ _____
Cheque No. _____
Send SAE if brochure only required.

CRESCENT RADIO LTD.

164-166 HIGH ROAD LONDON N22 6EJ
(also) 13 SOUTH MALL, Edmonton, N.9
MAIL ORDER DEPT. 1 St Michaels Terrace Wood Green
London N22 4SJ Phone 888 3206 & MAIL ORDER 888-4474

POWER PACKS
PPI Switched 3, 4, 6, 7, 9 and 12 volt @ 500 mA, with on/off switch and pilot light.
Size = 130 mm x 55 mm x 75 mm
ONLY = £4.50 + 5%

CASSETTE MICROPHONE
On/Off switch for Remote Control. Split Lead with 2.5mm and 3.5mm plugs. Standard Cassette Mics to suit all types. Complete with Des. Rest. Please state which Impedance required 200ohm/50K.ohm.
PRICE £1.60 + 12½% VAT.

P.C. ETCHING KIT
This kit contains all that the constructor will need to etch the circuits of his own design.
Contents - Plastic etching dish. Sample copper clad board. Laminate Cutter. 1 lb Ferric Chloride. Large Plastic Spoon. Etch Resist Pen. Full Etching Instructions.
Complete and Big Kit Value at £3.75p + 8% VAT.

FERRIC CHLORIDE
Anhydrous ferric chloride in double sealed one pound Poly packs.
OUR PRICE — 65p + PP + 8% per lb.

3 KWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three channel Base Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed).
£18.50 plus 75p P. & P. + 8%



AIRCRAFT BAND CONVERTER
A most popular unit providing instant conversion of any medium wave radio to cover the fascinating V.H.F. aircraft band. Spec.: 9 volts. Used with any AM or FM radio without requiring to be connected. Tunes: 110-135 MHz. Size: 100 x 70 x 40mm. Our price £5.50 + 12½% VAT.

"CL100" 100WATT AMPLIFIER
All built and tested, mounted on a plain aluminium chassis which measures 180 x 91 x 4" and which you can mount in a cabinet of your own. Four Controlled Inputs, Master Volume, Treble, Middle and Bass Controls. S/C protected output. 100 watts Clean into 8ohm L/S. Ideal for Disco, Music Groups, PA and Clubs.
A Bargain at £42 + £1 carr. + 8% VAT.

T1 MULTI-METER

Ideal tester for everybody interested in electronics. Weighing less than 100 grammes and only 60mm x 24mm x 90mm. Ranges: AC volta: 0-10v, 50v, 250v, 1,000v. DC volta: 0-10v, 50v, 250v, 1,000v. DC current: 0-1mA, 0-100mA. Resistance: 0-150K ohm.
PRICE £4.75 + VAT 8%

MINI LOUDSPEAKERS

2½" 80 ohm 90p + 12½%
2½" 40 ohm 90p + 12½%
2½" 8 ohm 90p + 12½% VAT

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).
OUR PRICE 50p + 8%

U.K. CARR.

50p unless otherwise stated

All prices are excluding VAT. Please add to each item the VAT rate indicated to all orders

PHILIPS

YOU & PHILIPS HI-FI KITS

The top sellers for home assembly in Europe - now available in the U.K.

Now - read all about the Philips range of quality kits for home assembly - mixers, amplifiers, speakers, etc, etc. Send today to S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London N17 ORN

Please send me, quickly, the new colour catalogue.

EE21

Name

Address

Postcode



free SEND TODAY!
S.S.T. Distributors is a member of the Philips Group of Companies.


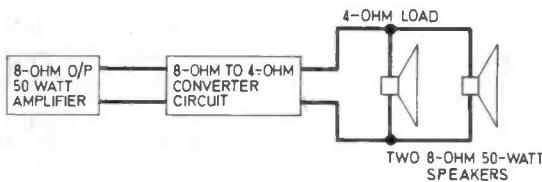


Fig. 1. (left) The circuit to which Maurice referred.

Fig. 2. (below) The diagram showing actual connection of the converter.

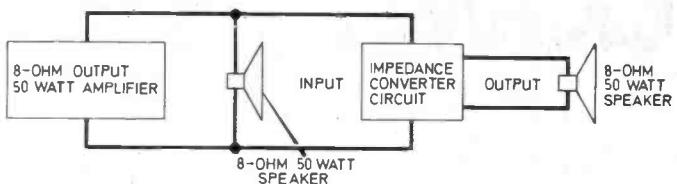

At this moment Tom appeared perspiring from another part of the laboratory, where he had been making a case for the impedance-converters. He had obviously been working very hard, sawing, filing, drilling and bending the metal to make the case which he now brought, and showed proudly to the Prof. and his friends Maurice and Bob.

CASE

"Can we fit the impedance-converters into this case now?" he asked, "Then we could check out the system and maybe give it a trial run."

"Not yet, Tom, hang on, we've only made one of them!" replied Maurice, "We need another for the other channel of the stereo amplifier!"

"Oh, Maurice," said the Prof. with a suppressed grin and a twinkle in his eye, "Would you mind opening that package for me?"

Maurice brought over the package which the robot had earlier delivered, and as he looked inside it, gave a sudden yelp of amazement.

"There are three more impedance-converters in here!" he exclaimed, "Where did they come from?"


The robot made them, Maurice."

"But it only took him a few

minutes from the time you gave him his instructions, to the time he brought this package, and it took all of us ages just to make one converter!"

"That's right," replied the Prof., "But I thought that if we made one converter ourselves, and let the robot handle the routine labour of producing another three, then we could use the time we have saved, to carry out a few other interesting projects!"

Continued next month

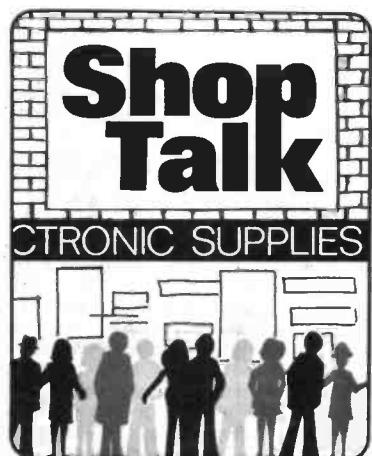

By Mike Kenward

A RECENT visit to the D.I.Y. Exhibition at Olympia did not reveal any great displays of electronics and we feel it is a pity that this popular hobby, which anyone can undertake, has been completely neglected. One item of interest did however present itself.

The item we spotted was a tool rack from Hoga Products. The rack is made in England using 22 gauge mild steel with a stove-enamelled finish. It is 91cms long and holds a double row of tools tidily and on display for easy access. The retail price is £3.99 including VAT and they are available through Interore Ltd., 29 Thurloe Street, London SW7 2LQ.

Brake Warning Indicator

None of the parts for the Brake Warning Indicator should provide any buying problems. It is important that heavy gauge auto wire is used for the connections to and from the unit and that all joints involved in the lamp circuit wiring are of good quality, this is because the supply current for the brake lights flows through this chain. This is also the reason four strips on the board are linked together.

Photocube Receiver

Photocubes are now generally available from photographic shops; they are designed to hold photographs and one is used for the case of the Photocube Receiver. As far as the electronic components go there should be no buying problems, if any parts are not available locally one of the large mail order firms should be able to help.

The Denco aerial can be obtained direct from Denco they supply either MW/LW or MW only type 5FR the price is 94p and 70p respectively plus 12.5 per cent VAT plus 16p postage.

Multi-Tester

For those who have completed the Teach-In 76 course the Multi-Tester project is a good way of putting some of the parts to use—another in the form of a power supply will be published shortly. Buying the parts should not present any problems.

Tumbler Dryer Control

One problem that may arise when constructing the Tumbler Dryer Control is a source of supply for sea salt if sea water is not available. I am informed that many grocers, chemists and aquarium shops (particularly those selling salt water fish) can supply this. It is not possible to use ordinary table salt because of the additives in it.

The angle bracket for the triac mounting is made from a piece of angle aluminium of fairly solid proportions to provide a heat sink. You should be able to obtain suitable material from a good d.i.y. or metal shop—they may even have an off cut!

The triac specified comes in a TO48 case which is easily mounted using a single hole for the stud but it must be insulated from the metal with the correct mounting washers.

Literature

Finally brief news of a change of ownership of Arrow Electronics, its new shop and catalogue. The new owner is Peter Clarke who says "My staff are second to none and our large technical library enables us to trace or substitute most of the items used in electronics today, and in most cases supply from our now vastly increased stocks of over 6000 lines".

A new catalogue is now available price 40p.

GEORGE HYLTON brings it down

Inductance Calculations— How to Avoid Them

HERE comes a time in the life of every electronics enthusiast when he must answer the terrible question: How many turns should I put on? Strong men have been known to run away screaming at the thought of having to work it out for themselves. It isn't surprising.

Opening a well-known textbook at the pages on inductance calculations I find a magnificent collection of formulae, all purporting to tell you the inductance of a coil and all different. Here's a selection:

$$L = \frac{a^2 N^2}{9a + 10l}$$

$$L = \frac{a^2 N^2}{(9 - (a/5l)) a + 10l}$$

$$L = \frac{0.252 \cdot d^2 N^2}{1 + 0.46(d/l)}$$

It becomes clear, on reading the words that accompany this mathematical feast, that these formulae have one thing in common. They are all wrong! Not very wrong, perhaps, but wrong. In order to make life easier for himself

the mathematician makes the assumption that the coil is wound with flat tape, infinitely thin. Since real coils are wound with round wire their inductances are different.

You'll notice too that the formulae all give the inductance L . The number of turns N cannot be obtained directly. Before you can do that the formulae have to be rearranged. A mathematician will have no problem here. He'll probably tell you that all that's needed is a trivial piece of manipulation. That's his way of saying: "I'm all right, Jack. I can do it".

What can the rest of us do? We can resort to a few simple "wrinkles" plus trial and error. One thing you will find in all these formulae is the term N^2 , which is the square of the number of turns. What this means is that, other things being equal, twice the number of turns gives four times the inductance, trebling the turns gives nine times, quadrupling gives 16 times, and so on. By the same token, halving the turns reduces the inductance to a quarter of what it was, using one-tenth the number gives one hundredth the inductance, etc.

Thick Ones!

In practice, however, it doesn't work out quite like that. If you have a coil like the one in Fig. 1, with 16 turns, and you remove 8 of them, you have done something else, too. You have changed the shape. What started off as a coil about twice as long as it was thick, ends up as one whose length is about the same as its thickness (i.e. diameter).

This upsets the situation. The assumption that we now have a quarter of the original inductance isn't quite true. To make it true we'd have to spread out the turns so that they occupied the same length of the former as the original complete coil.

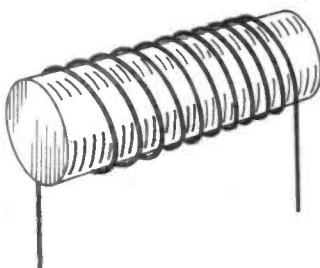


Fig. 1. A solenoid coil.

All the same, you can get a fair idea of the number of turns to add or take off by applying the "squaring" rule. It's even easier to adjust the turns if the coil is part of an LC tuned circuit which has to be set to the right frequency by altering L . In this case, the relation between turns and frequency is quite straightforward.

To double the tuned frequency you just halve the turns and so on. To take a practical example, suppose a coil is designed to tune to 2MHz with 400pF.

To make it tune to 4MHz with 400pF you halve the turns. To make it tune to 1MHz you double the turns. Remember that this is only approximate, and leave enough loose wire to make a final adjustment!

So far we've been considering different numbers of turns on the same coil-former. If the former is different, too, (smaller or larger diameter) then the inductance is different even when the number of turns is the same.

Looking back, we've discovered three things which influence the inductance:

Number of turns.

Shape.

Size.

This is why those formulae are so complicated. They take all three factors into consideration. (For any courageous reader with a calculator, the first formula is approximately right for coils of ordinary shape, like Fig 1. Formula (2) is for short coils. Formula (3) is for ordinary coils but is more accurate than (1). All dimensions are in inches and the inductance is in micro-henries. All coils are "single layer", that is, with just one layer of wire, not several on top of each other.)

Core

The inductance of a coil also depends on the material near it, and in particular on the material inside it. If, for example, a coil is wound on a ferrite rod, the material inside it is a magnetic material. This increases the inductance. In general, magnetic materials increase the inductance, non-magnetic insulators like plastics or paper leave it unchanged, and non-magnetic metals reduce it.

These effects are commonly used to enable inductances to be adjusted. A "core" of material is provided which can be screwed into the bore of the coil former. Depending on how far it is screwed in, the inductance is changed by a little or by quite a lot. Cores are usually made of ferrite or iron "dust" cemented together, but for u.h.f. working are often of brass.

What if the core is of a magnetic metal? Laminated transformer cores are, and their effect is to increase the inductance enormously, at low frequencies. But as the frequency increases the "metal" effect gains on the "magnetic" effect, and the core becomes ineffective. Iron cores (which must be of "soft" non-magnetisable iron, not steel or any permanent-magnet alloy) are seldom used above the audio frequency range nowadays.

Ferrite cores are used from the higher audio frequencies up into the radio frequency range. Dust-iron is used mainly at radio frequencies. The extent to which the inductance of a coil is increased by a magnetic screw core varies from a few per cent to a factor of several times, depending on the size, shape and material.

The effect of enclosing a coil in a metal "screening can" is to reduce the inductance.

to
earth

FREE!

STEREO HEADPHONES
SUPPLIED WITH
EVERY COMPLETE ORDER

SOLENT MARK II STEREO AUDIO SYSTEM £5 down



Solent Mark II Stereo Tuner Amplifier chassis with AM/FM radio covering long, medium, short and stereo FM wavebands.

Separate Bass and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) AFC Switching. Dimensions 18½" x 9" x 3½". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units. Order early limited stocks available cash price £69·95. Credit Sale £5·00 deposit 9 monthly payments of £8·70 (Total Credit price £83·30). P. & P. £4·00. Send £9·00 today.

Chassis only available for cash at £49·00 + p. & p. £3·00
Full 12 months Guarantee.

Access and Barclaycard Orders Accepted by Telephone
CALLERS WELCOME

LEWIS radio

EE/1/77, 100 CHASE SIDE SOUTHGATE
LONDON N14 5PL Telephone: 01-882-1644

YES SIR 1st class post TONIGHT!
We specialise in high spec components
with express service for phone customers



HIGH SPEC components FAST!

Agents for VERO - ANTEX -
BIB MULTICORE SOLDER

- OPEN 9am-5pm, 6 days - Phone orders 9am-4pm.
- S.A.E. for stock list including pots, presets, I.C.'s 7400 & CMOS, capacitors, plugs, sockets, switches, cable, etc.
- Post free envelope included for your next order.
- SUPER EXPRESS phone service - ask for details.
- Shop at keen prices 5 days per week. Late night - Fri. 7-10pm.m.

TRANSISTORS + 200 OTHER TYPES IN STOCK

AC125	20p	BC109	11p	BC262A	19p	BFX29	26p	TIP41A	87p
126	20p	109B	12p	287	20p	84	22p	42A	80p
127	20p	109C	13p	300	30p	88	22p	T1SA	35p
128	20p	117	18p*	301	34p	BFY10	17p	ZTX300	13p*
151	35p	142	24p	303	35p	51	16p	160	30p
153	35p	143	24p	338	16p*	52	18p	500	15p*
176	20p	147A	9p*	557	15p*	BY164	40p	502	18p
187	20p	147B	10p*	BCY71	18p	ME0401	18p*	1N914	5p
188	20p	148	9p*	72	14p	0411	18p	1N4001	5p
AD149	68p	148B	10p*	BD123	90p	ME4001	10p*	4002	8p
161	42p	149B	11p*	124	90p	4101	11p*	4005	9p
162	42p	149C	11p*	131	36p	MPP102	32p*	4006	10p
MCH/PR	154	18p*	132	38p	O A47	9p	4148	5p	
1-04		157B	12p*	139	54p*	90	5p	2N2219	20p
AF116	24p	177	17p	155	75p*	91	4p	2646	40p
117	24p	178B	18p	BF158	20p	200	6p	29260	13p*
124	30p	179B	19p	184	25p	O C28	90p	2926G	15p*
239	37p	184B	12p*	185	21p	035	80p	3053	18p
AU113	1-50*	184A	11p*	194	30p	3055	60p		
BC107	11p	187	26p	196	12p*	44	30p	3702	11p*
107A	12p	212A	13p*	197	12p*	71	25p	3703	10p*
108	10p	212L	15p*	199	11p*	ORP12	65p	3704	13p
CL108	6p	213B	12p*	200	38p	TIP29A	47p*	3705	10p*
BC108B	11p	214	15p*	338	34p	30A	56p*	3707	12p
108C	12p	214L	17p*	BFW11	68p	31A	57p	3819E	25p*

DIODES BRIDGES

50V 3A	13p	100V 1A	28p	RESISTORS 1½W each	LINEAR 1/C's
100V 3A	45p	200V 1A	30p	½ WATT E12 (5%)	33p
200V 3A	18p	400V J/A	32p	1 ohm - 10 ohm	LM380SL607451-29*
400V 3A	21p			LM3900N	6p
THYRISTORS				NES55	6p
60V 1A	20p			SN76013ND	1-60*
600V 1A	60p	TAG 1 600		SN76013ND	1-60*
700V 1A	1-20	BT 106		SN76023N	1-75*
400V 4A	58p	C106D1		SN76023N	1-75*
500V 6½A 1-25	21p			TBA800	1-35*
		BT 109		TBA810S	1-49*
				TBA820	1-20*
				ZN414	1-60*


Post & Packing 25p per order. VAT please add to total * 12½%, rest 8%.

ORCHARD ELECTRONICS

FLINT HOUSE, HIGH STREET, WALLINGFORD, OXON, OX10 0DE
Telephone 0491 35529.



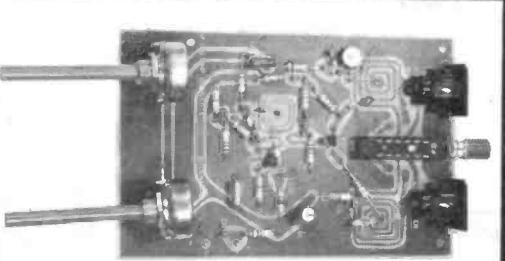Announcement Electronic Construction Kits for 1976/77



HF 305 £6.70

AF 25	Mixer
AF 30	Pre-amplifier
AF 300	3 Watt audio amplifier
AF 310-3	Power amplifier
AF 340	40 watt AF power amplifier
AF 380	2 Watt IC universal amplifier
AT 5	Automatic light control
AT 30	Photo-cell amplifier
AT 50	Triac AC regulator up to 440W
AT 56	Triac AC regulator up to 2200W
AT 320	All-round AC/DC regulator
AT 325	Interval and flasher unit
AT 347	Electronic Roulette
AT 365	Light show
AT 405	Low-cost light/hear control
AT 460	Monoflite
AT 465	Superlite
AT 466	Strobolite
AT 468	Quarolite
GP 304	Motor circuit unit
GP 310	Hi-Fi pre-amplifier
GP 340	Hi-Fi pre-amplifier
GU 330	Guitar tremolo
HF 61	Diode medium wave receiver
HF 65	FM transmitter/Signal Test Generator
HF 305	Amateur band 2 metre VHF 144 MHZ converter
HF 310	FM tuner
HF 325-2	FM tuner module
HF 330	Stereo decoder
HF 375	Mini FM receiver
HF 385	VHF/UHF aerial amplifier
HF 395	Aerial amplifier AM-FM
LF 380	4d-stereo
MI 310	Stereo VU module
MI 330	S-meter module/amplifier
MI 360	Multivibrator/signal generator
MI 390	Dial module (meter not included)
MI 391	VU module (meter not included)
MI 392	Balance module (meter not included)
MI 393	Tuning module (meter not included)
MI 402	Semi-conductor tester for diodes/transistors
NT 300	Power pack (transformer not included)
NT 305	Voltage converter
NT 311	Voltage stabiliser
NT 315	Power pack
NT 330	Power pack
NT 400	Power Supply (transformer not included)
NT 410	Power supply
NT 415	Power supply (transformer not included)

Please enclose 25p for p & p with order.

All prices include VAT

Send for free Catalogue to:
JOSTYKIT (UK) LTD., Mail Order Division
P.O. Box 68, Middlesborough,
Cleveland, TS1 5DG

NAME . . .

ADDRESS . . .



RECEIVERS and COMPONENTS

COPPER CLAD PC BOARDS 5½" x 5½"
6—85p 12½" x 9"—50p 10" x 7"—50p all p.
TV CONVERENCE PANELS 2 x AC128 3
slugged colls, 3 slide switches 11 WW pots.
3 Carbon presets, 2 ferrite chokes etc £1. (50p)
NEONS 20mm—25mm (20p).
C 20 POLYESTER CAPS 100—£1 (15p)
THREE TRANSISTOR AUDIO AMPS
EQUIV OC71, AC128 40p (10p) 3—£1 pp
3LBS ASS Computer Panels £1 (70p)
J.W.B. RADIO
2 Barnfield Crescent, Sale Cheshire M33 1NL
Postage in brackets Mail order only

NO LICENSE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £8.25 plus 20p P&P. 'Brain-Freeze' 'em with a MINI-STROBE Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £3.80 plus 20p P&P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made modules. £4.75 each plus 20p P&P. LOTS MORE! Send 20p for lists. Prices include VAT. (Mail order U.K. only).

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey. (E.E.)

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc., 50p and SAE. Catalogue 20p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

BELL'S TELEVISION SERVICE for service sheets of Radio, TV etc. 75p plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

MISCELLANEOUS

RECHARGEABLE NICAD BATTERIES
'AA'—£1.05. Sub 'C'—£1.29. 'C'
(HP1)—£2.02. 'D' (HP2)—£2.92. PP3—
£4.98. Matching chargers, respectively,
£4.48, £4.48, £5.24, £5.24, £3.98. All
prices include VAT add 10% Post &
Package. SAE for full list, 1 plus, if
wanted, 35p for 'Nickel Cadmium
Power' Booklet. Sandwell Plant Ltd.,
1 Denholm Road, Sutton Coldfield,
West Midlands B73 6PP. Tel. 021-354
9764.

SMALL ADS

The prepaid rate for classified advertisements is 14 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £9.00 per single column inch (2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5918).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printer's errors or their consequences.

LOUDSPEAKERS



Speakers, kits and cabinets for D.I.Y., HIFI, P.A., Disco, etc. by EMI, Fane, Goodmans, Baker, Kef, Elac, Richard Allan, Wharfedale, etc. Send stamp for free booklet "Choosing a speaker".

WILMSLOW AUDIO

Dept. EE, Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF
Tel. Wilmslow 29599

MUSICAL EFFECTS

Build them yourself with EXPRESS-KIT

Available NOW

**AUTOMATIC PHASE £5.90 incl.
FUZZ-TONE £5.50 p. & pkg.**

Available LATER: Treble Boost, Tremolo, Auto-Waa & others

EXPRESS-KITS are modern designs on fibreglass p.c.b. using top quality components and include easy-to-follow instructions. Case and batteries not supplied.

SAE All Enquiries—Mail Order only

EXPRESS COMPONENTS

29 White Road, Stratford,
London E15 4HA

ENAMELLED COPPER WIRE

swg	1 lb	4oz	2oz
14-19	2.44	.69	.50
20-23	2.45	.82	
24-34	2.60	.89	.64
35-40	2.85	1.04	.75

Inclusive of p&p and VAT.

SAE brings Catalogue of copper and resistance wires in all coverings.

THE SCIENTIFIC WIRE COMPANY
PO Box 30, London E4 9BW

NEW! From H.M. ELECTRONICS A BASIC D.I.Y. CASE

- ★ One piece aluminium chassis.
- ★ Whitewood Ply end cheeks, that can be painted, stained, etc.
- ★ Simulated black leathergrain lid.



REAL VALUE
FOR MONEY

TREASURE TRACER
MK III Metal Locator

• Varicap tuning
• Britain's best selling metal locator kit; 1000 sold
• Weights only 22oz. Fitted with
Fridley shield
• Speaker and earphone operation
• Knocks down to only 17in
• Prebuilt search coil assembly
• Thoroughly professional finish
• As seen on BBC1 and BBC2 TV
• You only need soldering iron,
screwdriver, pliers and snips
• Five transistor circuit
• Send stamped addressed
envelope for leaflet

Complete £14.75 Built & tested £19.75

Post £1.00—£1.18 VAT (8%) Post £1.00—£1.58 VAT (8%)

MINIKITS ELECTRONICS
6b CLEVELAND ROAD,
LONDON, E12 2AN
(Mail order only)

GB1	14" x 6" x 2"	£2.65	Post and Packing
GB1a	9" x 6" x 2"	£2.05	
GB2	14" x 7" x 3"	£3.25	90p
GB3	14" x 9" x 4"	£3.95	Plus £1.75 V.A.T.
Mini-Bec	7" x 5" x 3"		Other Types and Styles. Dry Transfer lettering. Send 15p for leaflets to: 275a Fulwood Road, Broomhill, Sheffield, S10 3BD

BOOKS and PUBLICATIONS

Start your own business printing pound notes

Printing pound notes? Well not quite—but "Start your own business rewinding electric motors" could easily be your licence to make money in 1976.

Lavishly illustrated, this unique instruction manual shows step by step how to rewind motors, working part or full time, without experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc., etc.

A goldmine of information and knowledge. Only £3.90 plus 26p P & P from:

MAGNUM PUBLICATIONS, Dept. EE5,
Brinksway Trading Estate, Brinksway,
Stockport SK3 0BZ.

PRINTED CIRCUIT KIT £4.25*

Make your own printed circuits. Contains etching dish, 100 sq ins of pc board, 1 lb ferric chloride, dalo pen, drill bit, laminate cutter.

JC12 AMPLIFIER

8W IC audio amp with free data and printed circuit £2.25*

**DELUXE KIT FOR JC12**

Contains extra parts except JC12 needed to complete the amp including balance, volume, bass and treble controls. Mono £2.33. Stereo £4.95.

JC12 POWER KIT

Supplies 25V 1 Amp £3.75.

JC12 PREAMP KITS

Type 1 for magnetic pickups, mics and tuners. Mono £1.50. Stereo £3.00. Type 2 for ceramic or crystal pickups. Mono 88p. Stereo £1.70.

SINCLAIR IC20

IC20 10W+10W stereo integrated circuit amplifier kit with free printed circuit + data £4.95.

PZ20 Power supply kit for above £3.95.

VP20 Volume, tone-control and preamp kit £7.95.

JC40 AMPLIFIER

New Integrated circuit 20W amplifier kit complete with chip, printed circuit and data £4.45.

FERRANTI ZN44

IC radio chip £1.44. Extra parts and PCB for radio £3.85. Case £1. Send see for free data.

BATTERY ELIMINATOR BARGAINS**STABILIZED POWER UNITS***

Millenia series. Switched 1 to 30V In 0.1V steps. 1Amp Kit £12.45. Kit + case £14.95. Built N/A. 2Amp Kit £14.95. Kit + case £17.90. Built N/A.

6-WAY SPECIAL £5.20*

Switched output

of 3, 4, 6, 7, 8,

9, 12V at 500mA

3-WAY MODELS*

With switched output and 4-way multi-jack connector. Type 1: 3/4/5V at 100mA £3.20.

Type 2: 6/7/9V at 150mA £3.30.

RADIO MODELS

50mA with press-stud battery connectors. 9V £3.45. 6V £3.45. 9V+9V £5.45. 6V+6V £5.45. 4V+4V £5.45.

CASSETTE MAINS UNITS

73V with 5 pin din plug. 150mA £3.95.

CAR CONVERTERS £5.10*

Input 12V DC. Output 6/7/9V DC 1Amp stabilized.

BATTERY ELIMINATOR KITS

Send see for free leaflet on range. 100mA radio types with press-stud battery terminals. 4V £2.10. 6V £2.10. 9V £2.10. 4V+4V £2.20. 6V+6V £2.20. 9V+9V £2.20.

100mA cassette type 7½V with 5 pin plug £2.10.

Transistor stabilized 8-way type for low hum. 3/4/6/7/8/9/12/15/18V. 50mA £3.95. 1Amp £5.50.

Heavy duty 13-way types 4/6/7/8/9/11/12/14/17/21/24/28/34/42V. 1Amp model £4.95. 2Amp model £7.95.

Car converter kit Input 12V DC. Output 6/7/9V DC 1A transistor stabilized £1.95.

MAINS TRANSFORMERS

6-0.6V 100mA £1. 9-0.9V 75mA £1. 18V 1A £1.95. 0/12/15/20/24/30V 1A £4.30. 12-0-12V 50mA £1. 0/12/15/20/24/30V 2A £5.95. 20V 2½A £2.95.

6-0.6V 13A £2.85. 9-0.9V 1A £2.55. 12-0-12V 1A £2.95. 15-0-15V 1A £3.20. 30-0-30V 1A £4.10.

S-DEC'S AND T-DEC'S*

S-Dec £2.24.

T-Dec £4.05.


μ-DecA £4.45.

μ-DecB £7.85.

IC carriers with

sockets:-

16 dili £2.95. 10T 05 £1.95.

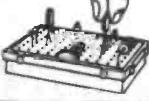**SINCLAIR CALCULATORS AND WATCHES***

Cambridge Universal £6.80. Cambridge Scientific £8.95. Oxford 300 £13.30. Programmable Scientific with free mains unit £24.95. Mains adaptors for other models (state type) £3.20. Assembled Grey Watch with free stainless steel bracelet £16.45.

SINCLAIR PROJECT 80 AUDIO MODULES

PZ5 £4.95. PZ6 £8.70. Z40 £5.75. Project 805Q £18.95.

BI-PAK AUDIO MODULES

S450 tuner £20.95. AL60 £4.33. PA100 £13.45. MK60 audio kit £27.20. Teak 60 £6.95. Stereo 30 £16.95. SPM80 £4.25. BMT 80 £3.70. Send see for free data.


SWANLEY ELECTRONICS

Dept E.E. PO BOX 68,
SWANLEY, KENT BR8 8TQ.

Send see for free leaflets on all kits. Post 30p on orders under £2.23, otherwise free. Prices include VAT. Overseas customers deduct 7% on items marked *, otherwise 11%. Official orders welcome.

DENCO (CLACTON) LIMITED

Dept. E.E.

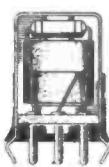357-8-9 OLD RD., CLACTON-ON-SEA, ESSEX CO15 3RH

Our components are chosen by technical authors and constructors throughout the world for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment.

General Catalogue showing full product range 32p. Overseas Customers 70p, Air-Mail Post Paid.

U.K. & OVERSEAS MANUFACTURERS/STOCKISTS ENQUIRIES WELCOME

Australian Readers Please Note— Our Complete Range of Coils are available from Hobipak, Box 224, South Carlton, 3053, Victoria, Australia and Watkin Wynne Pty. Ltd., 32, Falcon Street, CROWS NEST, 2065, AUSTRALIA. P.O. Box 392.

NEW FROM AMERICA**LIQUID CRYSTAL DISPLAY WATCHES FROM FAIRCHILD TIMEBAND**

5 + 4 functions. Continuous readout of Hrs, Mins, and pulsating Secs. Single command button, push once for Month/Date-auto reset; twice for Secs-manual reset.

PLUS
Programmed 4 Yr calendar, Backlight for night viewing, Optional continuously alternating Time/Date display, AM/PM setting indicator.

High contrast L.C.D. display visible in bright sunlight. Supplied in Presentation Boxes these are superb watches selling in Jewellers shops for up to £80.
TC 411 White £29.50
TC 410 Gold £32.50
On Leather Strap
TC 413 White £34.50
TC 412 Gold £37.50
Matching adjustable bracelet.

OUR SPECIAL L.E.D.

GALAXY 6 + 3 functions. At the touch of a button—Hrs, Mins, Secs, Alpha Day, Month & Date. + PLUS+—Programmed 4 Yr calendar, Auto Hold & Fadeout, AM/PM setting indicator. Available In S/S or Gold plated with S/S back & matching adj. bracelet. Sold elsewhere at £22.90.
NEW LOW PRICE £17.50.

No moving parts to wear out, clean or oil. Accuracy to a few secs/month. We believe our prices are the lowest anywhere and include V.A.T. at 8% & P. & P. Free battery/s. No quibble 1 Year Guarantee.

Send Cheque/Money Order to—

TEMPUS, Dept. EE 5-7, Norfolk Street, CAMBRIDGE, CB1 2LD. Tel. 55094

A LOT OF TIME FOR THE MONEY



GIRO NO. 331 7056. Access and Barclaycard accepted. C.W.O. only. Terms of business as in our Catalogue. Export Order enquiries welcome (E.M.L.N.)

1977 ISSUE

66 PAGES—3 000 ITEMS FULLY ILLUSTRATED

*20p CREDIT VOUCHERS

• ALL NEW STOCK

• SATISFACTION GUARANTEED

• DISCOUNTS

Boxes - Cases - Kits - PC Materials - Tools - Resistors - Test Meters - Capacitors - Hardware - Semiconductors - Books - Pots - Colls - Audio Accessories - Screws - Connectors - Audio Modules - Veroboard - Transformers - Knobs - Calculators - Audio Leads - Batteries - S dec Storage Units - Heatsinks, etc., etc.

SPECIAL CAPACITOR KITS

C280 Kit—PC Mounting polyester 250V 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22μF, 2 of 0.47, 1μF, £1.98 net

C296 Kit—Tubular polyester, 400V, 5 of each value 0.01, 0.022, 0.047, 0.1, 0.22μF, 2 of 0.47μF, £2.67 net.

"DIGITAL MULTIMETER KIT" AS IN E.T.I. SAE FOR LIST

SPECIAL RESISTOR KITS (CARBON FILM 5%) (Prices include post & packing) 10E12—V or 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 £5.29 net. 25E12 1W or 1W KIT: 25 of each E12 value, 22ohms—1M, a total of 1425 £12.64 net.

B. H. COMPONENT FACTORS LTD.**MULTIMETER U4323**

22 ranges plus AF/IF Oscillator 20,000Ω/Volt. Vdc—0.5—1000V In 7 ranges Vac—2.5—1000V In 6 ranges Idc—0.05—500mA In 5 ranges Resistance—5Ω—1MΩ In 4 ranges Accuracy—5% of F.S.D. OSCILLATOR—1KHz and 455KHz (A.M.) at approx. 1 Volt. Size—160 x 97 x 40mm. Supplied complete with carrying case, test leads and battery. PRICE £13.96



U4323

"DOING IT DIGITALLY"

DIGITAL TEACHING KIT TKI
Complete Parts as specified in October E.E. (including case). £12.00 Inc. V.A.T. & P.P. (Deduct £2.73 if case not required)

**MULTIMETER U4313**

33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy, mVdc—75mV. Vdc—1.5—600V In 9 ranges. Vac—2.5—600V In 9 ranges. Idc—60—120 microamps In 2. Idc—0.6—1500mA In 6 ranges. Iac—0.6—1500mA In 6 ranges. Resistance—1KΩ—1MΩ In 4 ranges. db scale—10dB + 12dB. Accuracy—dc—1%, ac—2%. Size—115 x 215 x 90mm. Complete with carrying case, test leads and battery. PRICE £19.90 net



U4313

(E.E.), LEIGHTON ELECTRONICS CENTRE

59 North Street, Leighton Buzzard, LU7 7EG. Tel.: Leighton Buzzard 2316 (Std. Code 05253)

An exciting **NEW** series from ...



Newnes Technical Books

Each of the books in this series is written by an expert in his own particular field. The books are authoritative yet easily understood by those with no technical knowledge whatsoever, and the texts are supplemented by many highly informative illustrations.

MASTER ELECTRONICS IN MUSIC

T. D. Towers

Contents: Creating Musical Sounds by Electricity — Making Musical Instruments Louder — Musical Special Effects by Electronics — Electronic Keyboard Instruments — Electric Guitars — Magnetic Tape Music — The Robot Drummer — Music Synthesisers — Music by Computer — Index.

130 pages 0 408 00262 X £2.50

MASTER HI-FI INSTALLATION

Gordon J. King

Contents: How it Works — The Amplifier — Programme Signal Sources — Importance of a Good F.M. Signal — The Loudspeaker — Mono, Stereo and Quadrophonic Sound — Four-channel Techniques — Room Effects — Best Use of Controls — Terminology — Index.

150 pages 0 408 00237 9 £2.50

MASTER STEREO CASSETTE RECORDING

I. R. Sinclair

Contents: Stereo Systems — Signal Sources — Controls and Facilities — Making the Recording — Replaying and Monitoring — Essential Maintenance — Aids to Better Recording — Noise Reduction Systems — Cassette Recorder and Hi-Fi.

140 pages 0 408 00238 7 £2.50



NEWNES TECHNICAL BOOKS, Newnes-Butterworths, Borough Green, Sevenoaks, Kent

OVER 2,000 ELECTRONIC COMPONENTS IN A
BIG NEW FREE
100 PAGE CATALOGUE

YOURS BY
POSTING
TODAY

Please send me
the 100 page
Tandy catalogue

Name _____

Address _____



TANDY

Nationwide supermarket of sound!

EE/5
Tandy Corporation (Branch UK), Bilton Road,
Wednesbury, W. Midlands WS10 7JN.

MAGENTA
electronics ltd.

EE1 61 Newton Leys,
Burton on Trent, Staffs.
DE15 0DW

COMPONENTS & HARDWARE

LATEST CATALOGUE contains NEW PRODUCTS sheet 11.
(see for sheet 11 only). NEW PRODUCTS. SHEET ONLY.
25p VOUCHER INCLUDED.
Send for your copy now—25p.

BUILD THESE PROJECTS!

EXPERIMENTERS' POWER SUPPLY.

TRANSISTOR TESTER.

TEST METER RANGE EXTENDER.

Circuits & details—send 20p per item—refunded when all parts are ordered.

Or send see for further information.

THE OPEN DOOR TO QUALITY



This 144 page catalogue—Electrovalue Catalogue No. 8 (Issue 2, up-dated) offers items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The Company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases; Access and Barclaycard orders are accepted. **FREE POSTAGE** on all C.W.O. mail orders in U.K. over £2.00 list value (excluding V.A.T.) if under add 15p handling charge.

**EVERYDAY ELECTRONICS
TEACH-IN KIT** nett £15.75 inc. V.A.T.

40p

inc. refund
voucher worth
40p

All communications to Dept. EE.17
28 ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY
TW20 0HE. Phone Egham 3603. Telex 284475.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester
M19 1NA. Phone (061) 432 4946.
Shop hours both addresses 9-5.30 p.m.; 1 pm Sat.

ELECTROVALUE LTD

Published approximately the third Friday of each month by IPC Magazines Ltd., Fleetway House, Farringdon St., London EC4 4AD. Printed in England by Index Printers Ltd., Dunstable Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (A/S) Ltd. South Africa—Central News Agency Ltd. Everyday Electronics is sold subject to the following conditions namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold, or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

B. BAMBER ELECTRONICS

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

A Happy New Year to all our Customers

VARIABLE STABILISED POWER SUPPLY. mains input. 24V output, stabilised and current limiting at 500mA - 32V at 50mA. Brand new by British manufacturer. Size approx. 7x 2x 4in. complete with external 5kohm 3-turn pot for voltage control. Connection data supplied. £7.

50W (25-0.25W) EDGEWISE METERS. modern type by Sangamo Western, display area 3x 1in with 2 mounting lugs. (Can be zeroed left or right hand.) £1.50 each, while stocks last.

MAINS ISOLATION TRANSFORMERS. Tapped mains input. 240V at 3A + 12V at 500mA output. New, boxed, made by Gardners. £12.

SOLDER SUCKERS. (Plunger Type). Standard Model £4.50. Skirted Model. £4.95. Spare Nozzles. 50p each.

Good Quality Pressure Gauges. 2½in dia. flange mounting. 2 models avail. 0-60 lbf/in. 0-100 lbf/in. In. state which. £1.25 each.

2N3055 type Transistors. O.K., but unmarked. 5 for £1.50.

110V NEONS, SCREW-IN-TYPE. 4 for 50p.

SLOW MOTION MOTORS (suitable for programmers, displays, etc.) 230-240V a.c. input rotation. I rev. every two to three minutes £1.25 each.

MINIATURE PLIERS High quality "Crescent". made in USA. £4.35 + VAT (35p).

SIDE CUTTERS, high quality. £3.70 + VAT 30p.

MIXED COMPONENT PACKS, containing resistors, capacitors, diodes, etc. All new (random sample bag revealed approx. 700 items). £2 per pack, while stocks last.

4 MHz CRYSTAL PACKS (10 assorted crystals between 4 MHz and 5 MHz). Our selection only £1 per pack.

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE with ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN. CALLERS SATURDAYS ONLY 9.30-12.00, 1.30-5.00.

Dept EE, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

TO3 transistor insulator sets. 10 for 50p.

ALU-SOL ALUMINIUM SOLDER (made by Multicore). Solids: aluminium to itself or copper, brass, steel, nickel or tinplate. 16 s.w.g. with multicore flux, with instructions. Approx. 1 metre coil 30p pack. Large reel £2.75.

VARICAP TUNERS. Mallard Type ELC 1043/45, brand new £4.40.

I.C.'s, some coded, 14 DIL type, untested, mixed, 20 for 25p.

Mobile Converters. 24V DC input 13.8V at approx 3.4A DC output, fully stabilised. £3.50 each (ideal for running 12V car radio from 24V battery supply).

We now stock Spiralux Tools for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, pop rivet guns, etc. S.A.E. for list.

Miniature earphones with min. jack plug. 2 for 50p + 12½% VAT.

I.F. Cans. 1in square, suitable for rewind. 6 for 30p + 12½% VAT.

TWIN I.F. CANS. approx. 1in x 1in x 1in high, around 3-5MHz. 2 separate transformers in 1 can. Internally screened. 5 for 50p + 12½% VAT.

Dubiller Electrolytics. 500µF, 450V, 2 for 50p. Dubiller Electrolytics. 100µF, 275V, 2 for 50p. Plessey Electrolytics. 470µF, 63V, 3 for 50p. TCC Electrolytics. 1000µF, 30V, 3 for 60p. Plessey Electrolytics. 1000µF, 180V, 40p each (3 for £1).

Dubiller Electrolytics. 5000µF, 35V, 50p each. Dubiller Electrolytics. 5000µF, 50V, 50p each. ITT Electrolytics. 6800µF, 25V, high grade, screw terminals, with mounting clips. 50p each. Plessey Electrolytics. 10,000µF at 63V, 75p each. Plessey Cathode Ray Capacitors. 0.0-4µF at 12.5kV DC. Screw terminals. £1.50 each.

PLEASE ADD 12½% VAT TO ALL CAPACITORS

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES. S.A.E. FOR LIST.

TV PLUGS AND SOCKETS

TV Plugs (metal type), 5 for 50p.

TV Sockets (metal type), 4 for 50p.

TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 12½% VAT.

PLUGS AND SOCKETS

N-Type Plugs 50 ohm. 50p each. 3 for £1.50.

N-Type Sockets (4-hole chassis mounting), 50 ohms (a small coax lead type). 50p each.

Plugs and Sockets (PTFE) and new, packed with reducers, 50p or 5 for £3.

SO239 Sockets (PTFE), brand new (4-hole fixing type). 50p each or 5 for £2.25.

5-way (IEP) Plugs and Sockets. 40p set (1 plug + 4 teks).

Plugs and sockets sold separately at 25p each. Bulgin Round Free Skts. 3p, for mains input on test equipment, etc. 25p each.

WELLER SOLDERING IRONS

EXPERT. Built-in spot-light illuminates work pistol grip with finger tip trigger. High efficiency copper soldering tip.

EXPERT SOLDER GUN. £8.80 + VAT (54p)

EXPERT SOLDER GUN KIT (spare bit case, pistol grip, etc.). £12.50 + VAT (12p)

SPARE BITS, PAIR 30p - VAT (2p)

MARKSMAN SOLDERING IRONS

SP15D 15W £3 + VAT (24p)

SP25D 25W £3 + VAT (24p)

SP25DK 25W + bits, etc. kit £3.85 + VAT (31p)

SP40D 40W £3.44 + VAT (28p)

SEARCH STAND with spring for Marksman Irons. £2.25 + VAT (18p)

SPARE BITS

MT8 for 15W. 40p + VAT (4p).

MT4 for 25W. 30p + VAT (3p)

MT10 for 40W. 42p + VAT (3p)

THERMISTOR TEMPERATURE CONTROLLED IRON. Temperature controlled iron & PSU. £2.00 + VAT (£1.80)

SPARE TIPS

Type CC single flat, Type K double flat fine tip.

Type P, very fine tip. £1 each + VAT (8p).

MOST SPARES AVAILABLE

MULTICORE SOLDER

Size 5 Savbit 18 s.w.g. in alloy dispenser. 32p + VAT (3p).

Size C1SAV10 Savbit 18s.w.g.. 56p + VAT (4p).

Size 12 SAVBIT 18s.w.g. on plastic reel £1.80 + VAT (15p)

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates:

Telecommunications Technicians

Radio, TV, Electronics Technicians

Technical Communications

Radio Servicing Theory

Radio Amateurs

Electrical Installation Work

MPT Radio Communications Certificate

Diploma Courses:

Colour TV Servicing

Electronic Engineering and Maintenance

Computer Engineering and Programming

Radio, TV, Audio Engineering and Servicing

Electrical Engineering, Installation

and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

Dept.710B Intertex House, London SW8 4UJ or telephone 622 9911

Subject of Interest _____

Name _____

Address _____

Tel: _____

VALVE BARGAINS

Any 5-54p, 10-£1.00, 50-£4.50.
Your choice from the list below.

ECC82, EF80, EF183, EF184,
EH90, PCF80, PCF802, PCL82,
PCL84, PCL85, PCL86, PCL805,
PL504, PY81/800, PY88, 30PL14,
6F28.

Colour Valves—PL508, PL509,
PL519, PY500/A. All tested.
30p each.

Television Aerial Splitters
2-way, inside type. £1.50

Press Button UHF Tuners—4 Button Transistor—British made—£2.50 each.

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11—For TH stereo and standard VHF/FM radio.

B12—For the older VHF television—Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. £3.80

50p BARGAIN PACKS

All Packs Un-used Parts—PK1-40-C280 (Mullard) Axial Lead Capacitor mixed values from .01µF to .47µF (250V/W). PK2-30-C281 (Mullard) Radial Lead Capacitors mixed values from .015µF to 1.5µF (250V/W). PK3-6 Co-ax plugs. PK4-6 Co-ax connectors, PK5-8-5m/m formers with slugs. PK6-25-AC128 Transistors. PK7-3 BF200 (VHF) Transistors. PK8-2 BF182 (UHF) Transistors, PK9 Any 6 Transistors—BC108, BC113, BC135, BC153, BC171B, C172, BF194, BF195, BF196, BE197. PK10 8-1 amp 400 volts rectifiers. PK11 4.5 pin din plugs (180°), PK12-5 PP3 Battery Connectors.

All prices include VAT. P&P 20p per order. Please send uncrossed P.O. or Cheques for returning if we are out of stock of Bargain Packs or older types of new valves.

ELECTRONIC MAILORDER LTD.

62 BRIDGE STREET, RAMSBOTTOM, BURY, LANCS.
Tel. Rams. (070 682) 3036

The new Maplin Catalogue is no ordinary catalogue...



Catalogue includes a very wide range of components: hundreds of different capacitors; resistors; transistors; I.C.'s; diodes; wires and cables; discotheque equipment; organ components; musical effects units; microphones; turntables; cartridges; styli; test equipment; boxes and instrument cases; knobs, plugs and sockets; audio leads; switches; loudspeakers; books; tools – AND MANY MANY MORE.



* Our bi-monthly newsletter keeps you up to date with latest guaranteed prices – our latest special offers (they save you pounds) – details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

SEND THIS COUPON FOR YOUR COPY OF OUR CATALOGUE
ON APPROVAL! Price 50p – SEND NO MONEY NOW.
Please rush me a copy of your brand new 1977/78 catalogue the instant it is published. Only if I am completely satisfied that it is worth every penny, will I send 50p within 14 days of receipt. If I am not satisfied, I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

ADDRESS _____

EE12
Maplin Electronic Supplies P.O. Box 3, Rayleigh, Essex, SS6 8LR

Owing to delay in completion of larger warehouse, catalogue will be delayed by up to four weeks – so there's still time to order before publication and get your pack of ten super special offer coupons, giving big discounts on ten different popular items. YOU COULD SAVE POUNDS! – SO DON'T DELAY – FILL IN AND POST COUPON NOW!

MAPLIN

ELECTRONIC SUPPLIES
P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR

Shop: 284, London Road, Westcliff-on-Sea, Essex
(Closed on Monday) Telephone: Southend (0702) 44101