





Easy to build projects for everyone

# Everett ELECTRONICS

KIOSKS KIOSKS KIOSKS  
*McLeod*

MAY 80  
50p

## FREE

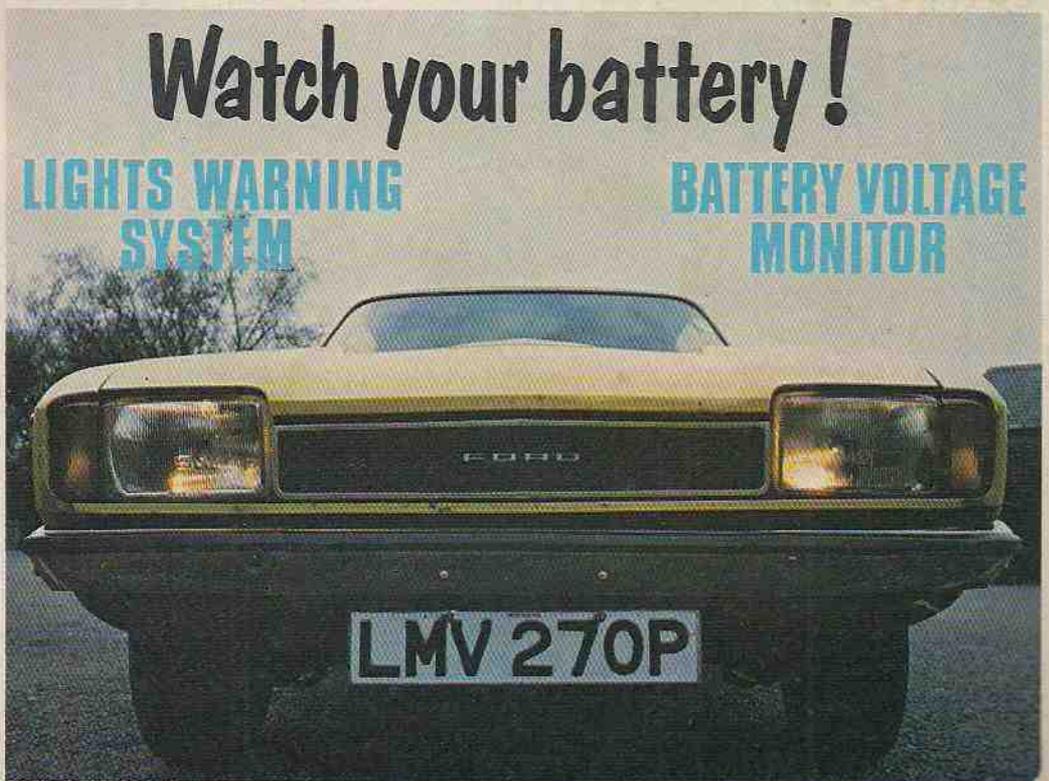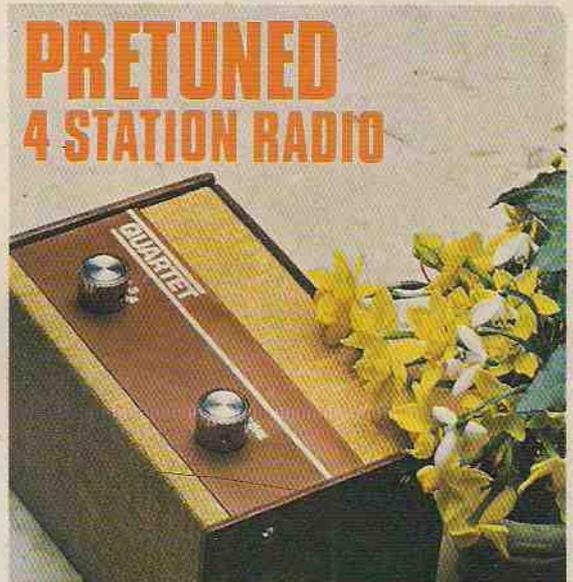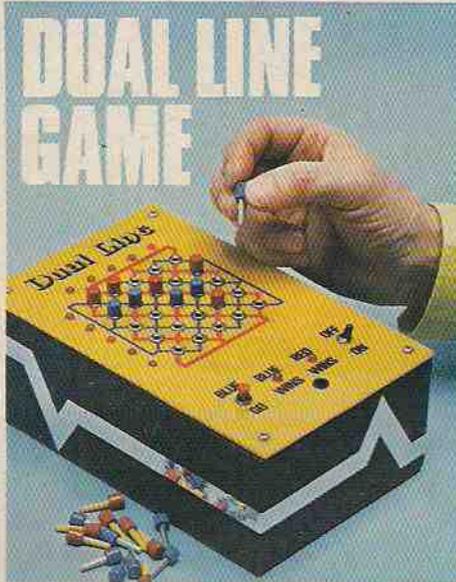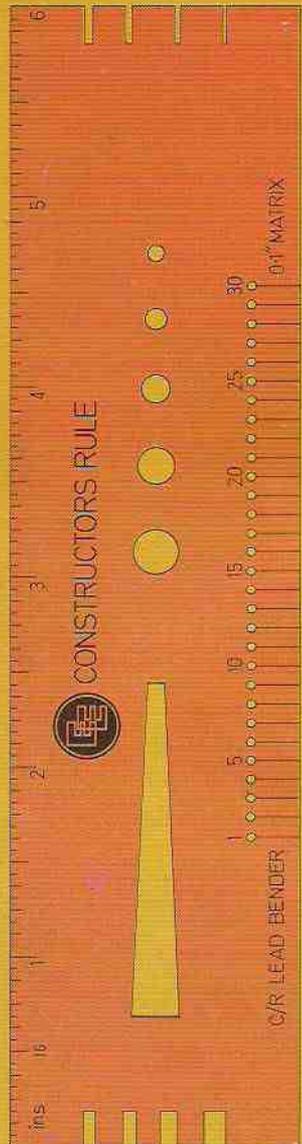

# MORE BIG VALUE FROM YOUR TANDY STORE

## 1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current: 0-150 mA. Resistance: 0-100,000 ohms. Accuracy:  $\pm$  3% full scale on DC ranges,  $\pm$  4% on AC ranges. Complete battery.



REG. PRICE

**£6.95**

## 6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then  $\pm$  30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Reg. 9V battery.




REG. PRICE

**£79.95**
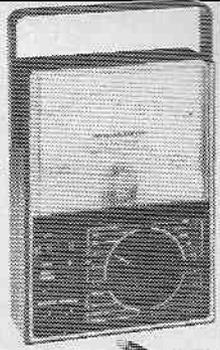
## MULTITESTER\*

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1.3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megaohm. 0-100-1k-101C-100k-3 megaohms. Reg. 9V battery. 22-209.




REG. PRICE

**£29.95**
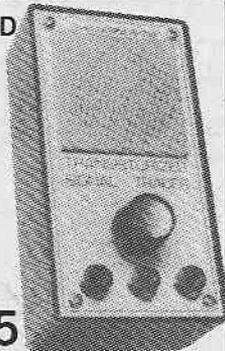
## TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.



REG. PRICE

**£9.95**

## DIGITAL IC LOGIC PROBE




Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE

**£19.95**
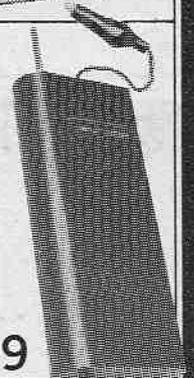
## SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.



REG. PRICE

**£2.79**

## AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE

**£1.99**

## REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.




REG. PRICE

**£229.95**
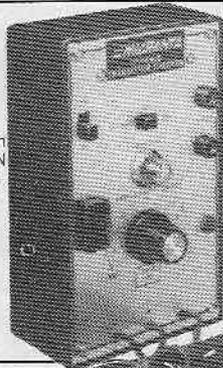
## DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.




REG. PRICE

**£9.95**
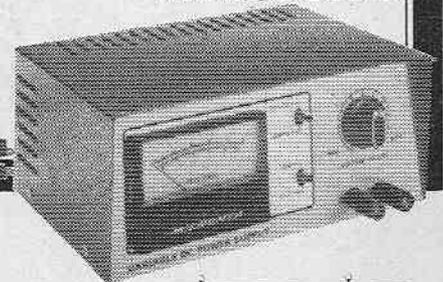
## VARIABLE POWER SUPPLY

Power project boards, IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123



REG. PRICE

**£35.95**

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for, or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

# TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



## TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.

Access: Barclaycard and Trustcard welcome. Prices may vary at individual stores.


# BEWARE! RADIO ACTIVITY



The new MK III FM tuner sitting under the Dorchester multiband AM/FM tuner

Revisions to the Mark III include a centre zero tuning indicator meter and silent preset switching

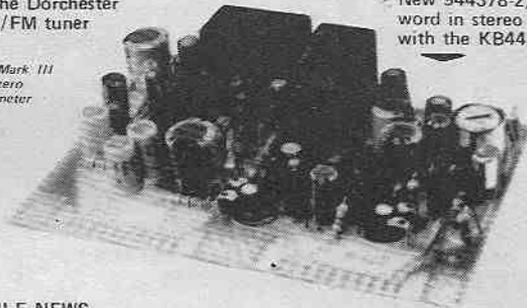New 944378-2, the last word in stereo decoders with the KB4437/4438.



Choosing the products to advertise each month can be quite a task at AMBIT, since we tend to introduce at least one new line per week. So it is nearly impossible to say all we would like in this space - other than to bring you as far up to date as possible with current events. The major medium for finding out about what we have to offer is our unique catalogue system, and we ask that you invest in a copy of parts 1, 2 & 3 since many questions we are asked can be readily answered by reference to these.

Each part costs 60p, or £1.60 for all three current editions. We are also launching a new and greatly elongated version of our PRICE LIST, which now includes a large number of quantity listings, and many items not previously listed. The new style price list is a quick reference short form to our general catalogues - available FOC with a large (A4) SAE please.

As a result of the soaring price of oil - and the subsequent huge increases in the cost of wax for Mr Tom Jackson's famous moustache, the Post Office have increased their charges (Feb. 4th). Accordingly, our standard cover charge has been increased to 35p per order (CWO).

## COMPONENTS

### DIGITAL FREQUENCY READOUTS / SYNTHESIZER SYSTEMS

Ambit has the biggest range of digital frequency readout systems for various applications in Broadcast and Communications. Prices range from £18.50 for a complete AM/FM broadcast frequency display (kit of DFM2). Most are detailed in the latest catalogue.

TUNING SYNTHESIZERS are also heavily featured, and we offer our first complete system covering MW/LW/SW2 and FM based on Hitachi parts. The unit is retrofittable to voltage tuned radio systems - and will shortly be incorporated in a complete tuner project. Cost for the synthesiser will be circa £40. A versatile communications system based on the new Mullard 2 IC system is nearing completion, together with 16 station CMOS memory and optical shaft encoder system with fast tune facility. Synthesiser circa £70, memory £50.

### Latest semiconductor news:

CMOS, TTL and LPSN TTL are in stock (ask for our OSTs price leaflet). Some of the very popular types are still "difficult" but we have things like 4011s, 4017s at the time of writing.

RADIO ICs - interesting developments here, we now have the Hitachi HA11225 and the HA12412 ultra high specification members of the CA3089E family. The PLESSEY SL1600 range now includes the SL6600 high performance PLL NBFM IF and detector.

CA3089E	2.11	HA1197	1.61	SD6000	4.31	SL1610	1.84	SL1626	2.80
CA3189E	2.53	CA3123E	1.61	TDA4420	2.59	SL1611	1.84	SL1630	1.86
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38	SL1612	1.84	SL1640	2.17
HA11225	2.47	TBA651	2.53	MC1350P	1.38	SL1613	2.17	SL1641	2.17
HA12412	2.81	TDA1090	3.51	KB4412	2.24	SL1620	2.90	SL6600	4.31
KB4420	1.95	TDA1220	1.61	KB4413	2.24	SL1623	2.90	SL6640	3.16
TBA1205	1.15	TDA1083	2.24	KB4417	2.53	SL1624	3.77	SL6690	3.58
KB4406	0.80	TDA1082	2.24	MC3357P	3.16	SL1625	2.50	MC1496	1.44

TRANSISTORS - New lower prices, wider range, large stocks. Also the world's lowest noise audio devices (2SC2546E and 2SA1084E) first from AMBIT of course. Power MOSFETs & all sorts of other devices. Our 3SK51 MOSFET replaces the 400XX and 40673 families.

BC237-8-9	0.092	2SC1775	0.207	2SA1084E	0.368	BF256	0.437	BFY90	1.03
BC307-8-9	0.092	2SA872A	0.207	2SC2547E	0.391	2SK55	0.368	BF224	0.253
BC413-5	0.115	2SD666A	0.345	2SA1085E	0.391	2SK168	0.402	BF274	0.207
BD414-6	0.126	2SB646A	0.345	2SK133	6.32	3SK51	0.62	BF195	1.139
BC546-556	0.138	2SD760	0.52	2SJ48	6.32	3SK60	0.667	VN66AF	1.092
BC550-560	0.138	2SB720	0.52	2SK135	7.29	BF960	1.426	2N4427	0.977
BC639-640	0.265	2SC2546E	0.368	2SJ60	7.29	3SK48	1.426	J176	0.747

RADIO CONTROL: A special section for all RC fans. New and exciting stuff: KB4445/KB4446 - complete 4 channel RX/TX dig.prop IC pair RF&control in one 4.75p; MSL9362/MSL9363 - logic section of a four channel dig.prop link, with switch opt. 3.75p; NE5044 - Signetics versatile 7 channel encoder, suitable for mixing etc. £2.14 ea; NE544 Signetics famous servo driver IC £2.07; MC3357P as used in RCME design £3.16 ea; AMBIT RCRX4 - RCME FM system compatible, complete RX kit with box/connector and AMBIT design screened front end with 27MHz ceramic filter £16.10 (kit); XTALS: FM pairs £3.74 (no splits) TX is fund. 1/2 opt frequency, RX 3rd OT - 455kHz AM pairs £3.57 (no splits). Both 3rd OT types, again RX IF at 455kHz

CATALOGUES 60p ea., all three for £1.60. PRICES SHOWN HERE INCLUDE VAT. POST/PACKAGE CHARGE NOW 35p

### MODULE NEWS

We are at last able to quote for quantities of our modules, following a program of standardization and revision to speed manufacture and test. The following types are the results of the standardization program:

UM1181	5 varicap MOSFET input VHF band 2 tunerhead	£12.00 inc
911225 A	High Performance FM IF system, with switched BW	£23.95 inc
911225 B	Single BW filters, single tuned detector	£14.95 inc
91072 A	DC tuned and single pole switched MW LW tuner	£14.43 inc
91072 B	As type 'A' but with either SW1 or SW2 band	£15.90 inc
92242 A	Combined LW/MW tuner, with FM IF/detector section	£29.00 inc
92242 B	As 92242A but with 5-10MHz SW section	£34.00 inc

All are supplied housed in screened metal cases 97x56x24mm, with all connections along a single edge, suitable for verticle or horizontal mounting.

Previously advertised units are still available - although there may have been some price changes in the latest edition of the Price List (Date Feb.80). A separate leaflet covering the new range of modules is available from April 80, with an A4 SAE please.

NEW LINE - ALPS switches and rotary potentiometers. With a general catalogue that's over 3 inches thick, we cannot begin to offer a comprehensive list of what we can offer - but we are already stocking the keyboard switches, keyswitches, pushbutton switches etc. In particular, the pushbutton switches really put all others in the shade (shadow?) when it comes to quality and price. A special new shortform is being prepared (and may be ready when you read this). All the potentiometers and switches you could ever need from a single source. Keypad switches cost as little as 15p ea (1 off), with a range of two part caps for easy ledgending. You must see the shortform catalogue (30p) and our new price list for full details of this huge range of components.




### AMBIT SHOP NOW OPEN

We are gradually getting our caller sales area sorted out, with displays of the products on offer and a browsers corner to sit and study data/catalogues. Call in next time you are in the area - parking outside the door.
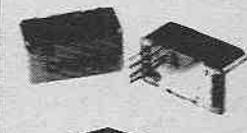
### COMPUTER CAPABILITIES

Ambit has been keeping a low profile on the subject of the MPU and its applications. Interestingly enough, the first project we offer with MPU content does rather more in the way of processing than simply playing a data game, or looking like an enormous calculator. Our MPU facility and expertise is now for hire on a fully commercial basis. Z80, 6800, 6809, 2650 etc.

Keyboard switch SCK41505 typ 6m ops 23p each (1-24)



NEW LINE - DC/DC+AC converters for fluorescent displays. TOKO CPS series 12v 1In, -20 and 3v AC out at 65mA. Thick film design £2.34 ea Qty. prices OA



### GENERAL INFORMATION

Ambit stocks the following ranges of components for ex-stock volume delivery: SIGNAL COILS, CERAMIC, MECHANICAL and CRYSTAL FILTERS, RADIO ICs for AM/FM/SSB, TOROID CORES FOR RADIO and EMI FILTER CIRCUITS, INDICATING AND PANEL METERS, AUDIO ICs, RF TRANSISTORS, FETS, MOSFETS, DIODES (PIN, VARICAP, SCHOTTKY), PASSIVE DBMs (like MD108 etc), IC SOCKETS, LEDs, TRIMMER CAPS, SWITCHES, KEYBOARD SWITCHES, TUNERHEADS, IF AMPS, AM RADIO MODULES, etc etc.

NEW LINE - DVM176 - the definitive ICM7106 LCD DVM module. 3 1/2 digit £22.37 ea.

CM161:	LCD 12/24hr alarm clock/day/date/backlight (eq.RS308-499) 7mm digits	£11.44 each
CM174:	LCD 12hr alarm clock/stopwatch/backlight with 30mm height digits	£14.32 each

**ambit**  
INTERNATIONAL

CWO PLEASE - Commercial MA terms on application. Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

# All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

## ..in kit form

SPARKRITE X5 is a high performance, top quality, inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no moisture due to contact breaker bounce which has eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light systems, function light, and security changeover switch. Will work all rev counters.

**Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.**

THE KIT COMPRISE SE VERYTHING NEE DED.

Die pressed case. Ready drilled aluminium extruded base and heat sink. coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.


Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy"


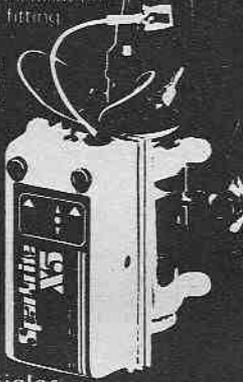
# Sparkrite

HIGH PERFORMANCE  
ELECTRONIC IGNITION

Electronics Design Assoc.  
82 Bath Street, Walsall WS1 3DE



# How do you put over 2,000 different tools and toolkits into one envelope?



The New Toolrange Catalogue is still the only comprehensive single source of electronic tools and production aids.

Products from over 100 top manufacturers are available from stock.

For your free copy of the new catalogue contact Toolrange today.

# toolrange

Upton Road, Reading, Berks. RG3 4JA

Telephone: Reading (0734) 22245 Telex: 847917

Everyday Electronics, May 1980

Electronics Design Associates, Dept. EE 580  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name \_\_\_\_\_

Address \_\_\_\_\_

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X5KIT £16.95

£

ACCESS OR BARCLAY CARD No.

Cheque No.

Send SAE if brochure only required.

# MAGENTA ELECTRONICS LTD.

## E.E. PROJECT KITS

Make us **YOUR No. 1 SUPPLIER OF KITS AND COMPONENTS** for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Project kits include **ALL THE ELECTRONICS AND HARDWARE NEEDED**—we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own **FREE COMPONENT IDENTIFICATION SHEET**. We supply—you construct. **PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED.** IF YOU DO NOT HAVE THE ISSUE OF E.E. WHICH CONTAINS THE PROJECT—YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA—39p. each.

**CABLE & PIPE LOCATOR.** Mar. 80. £3-40 less coil former.  
**KITCHEN TIMER.** Mar. 80. £12-46.  
**DOORBELL REGISTER.** Mar. 80. £3-39.  
**TOUCH SWITCH.** Mar. 80. £8-65.  
**STEREO HEADPHONE AMPLIFIER.** Mar. 80. £14-94.  
**5 RANGE CURRENT LIMITER.** Mar. 80. £2-24.  
**MICRO MUSIC BOX.** Feb. 80. £13-02. Grey Case £3-63 extra.  
**SIMPLE SHORT WAVE RECEIVER.** Feb. 80. £20-47, headphones £3-28.  
**SLIDE/TAPE SYNCHRONISER.** Feb. 80. £19-46.  
**MORSE PRACTICE OSCILLATOR.** Feb. 80. £3-75.  
**UNIBOARD BURGLAR ALARM.** Dec. 79. £4-95.  
**LIGHTCALL.** Dec. 79. £8-30.  
**BABY ALARM.** Nov. 79. £8-20.  
**OPTO ALARM.** Nov. 79. £5-77 inc. optional parts.  
**MW/LW RADIO TUNER.** Nov. 79. £15-90 less dial.  
**3 FUNCTION GENERATOR.** Nov. 79. £18-44 less pointer, case extra £7-18.  
**ONE ARMED BANDIT.** Oct. 79. £18-38. case extra £3-98.  
**HIGH IMPEDANCE VOLTMETER.** Oct. 79. £15-87.  
**LIGHTS ON REMINDER.** Oct. 79. £4-85.  
**CHASER LIGHTS.** Sept. 79. £18-95.  
**VARICAP M.W. RADIO.** Sept. 79. £8-98.  
**SIMPLE TRANSISTOR TESTER.** Sept. 79. £8-28.  
**ELECTRONIC TUNING FORK.** Aug. 79. £9-15. Suitable microphone & plug £1-59 extra.  
**WARBLING TIMER.** Aug. 79. £8-25.  
**9V POWER SUPPLY.** Aug. 79. £9-94 inc. pcb.  
**SWANEE WHISTLER.** Aug. 79. £3-19.  
**TOUCH ON PILOT LIGHT.** Aug. 79. £3-98.  
**QUIZ REFEREE.** Aug. 79. £5-85.  
**DARKROOM TIMER.** July 79. £2-47.  
**WATER LEVEL INDICATOR.** July 79. £4-60.  
**TREMOLO UNIT.** June 79. £11-26.  
**ELECTRONIC CANARY.** June 79. £4-99.  
**LOW COST METAL LOCATOR.** June 79. £5-44.  
 Handle & coil former parts extra £5-55.  
**METER AMPLIFIER.** June 79. £4-32.  
**QUAD SIMULATOR.** June 79. £6-25.  
**INTRUDER ALARM.** May 1979. £16-71. Less Ext. Buzzer & Lamp and Loop Components.  
**SHORT WAVE CONVERTER.** May 79. £15-98 inc. cases.  
**THERMOSTAT. 'PHOTO' SOLUTIONS.** May 79. £18-02. Less socket, tube and grease.  
**TRANSISTOR TESTER.** April 79. £3-87.  
**TOUCH BLEEPER.** April 79. £3-34.  
**LATEST KITS: S.A.E. OR 'PHONE FOR PRICES**

**ONE TRANSISTOR RADIO.** Mar. 79. with Amplifier & Headset. Less case. £6-93.  
**TIME DELAY INDICATOR.** Mar. 79. £4-21.  
**VERSATILE POWER SUPPLY.** Mar. 79. £8-99.  
**AUDIO MODULATOR.** Feb. 79. £1-58 less case and pins.  
**LW CONVERTER.** Feb. 79. £6-46.  
**THYRISTOR TESTER.** Feb. 79. £3-03.  
**ADJUSTABLE PSU.** Feb. 79. £24-60. Case (horizontal layout) £5-21 extra.  
**CONTINUITY TESTER.** Jan. 79. £5-02.  
**FUZZ BOX.** Dec. 78. £5-83.  
**VEHICLE IMMOBILISER.** Inc. PCB. Dec. 78. £5-74.  
**"HOT LINE" GAME.** Nov. 78. £4-65 less case & rod.  
**AUDIO EFFECTS OSCILLATOR.** Nov. 78. £3-81 inc. board.  
**FUSE CHECKER.** Oct. 78. £1-97.  
**C.MOS RADIO.** Oct. 78. £9-39.  
**TREASURE HUNTER.** Oct. 78. £17-85 less handle & coil former.  
**GUITAR TONE BOOSTER.** Sept. 78. £4-99 inc. p.c.b.  
**BOUND TO LIGHT.** Sept. 78. £5-98.  
**FILTER.** £1-66.  
**SLAVE FLASH.** Aug. 78. £3-20 less SK1.  
**LOGIC PROBE.** July 78. £2-53.  
**IN SITU TRANSISTOR TESTER.** June 78. £5-76.  
**VISUAL CONTINUITY CHECKER.** June 78. £3-72 inc. probes.  
**FLASHMETER.** May 78. £12-94 less calc and diffuser.  
**POCKET TIMER.** April 78. £2-99.  
**WEIRD SOUND EFFECTS GENERATOR.** Mar. 78. £4-81.  
**CHASER LIGHT DISPLAY.** Feb. 78. £23-59 inc. p.c.b. case extra £5-21.  
**AUDIO VISUAL METRONOME.** Jan. 78. £4-93.  
**RAPID DIODE CHECK.** Jan. 78. £2-34.  
**AUTOMATIC PHASE BOX.** Dec. 77. £9-55 inc. p.c.b.  
**VHF RADIO.** Nov. 77. £14-36.  
**ULTRASONIC REMOTE CONTROL.** Nov./Dec. 77. £16-09.  
**TREASURE LOCATOR.** Oct. 77. £10-81 case extra. £3-33. Less handle, etc.  
**ELECTRONIC DICE.** March 77. £4-63.  
**SOIL MOISTURE INDICATOR.** June 77. £4-07 inc. probe.  
**PHONE/DOORBELL REPEATER.** July 77. £8-38.  
**CAR BATTERY STATE INDICATOR.** Sept. 78. £1-79 less case inc. PCB.  
**R.F. SIGNAL GENERATOR.** Sept. 78. £18-17 less case.  
**ADD-ON CAPACITANCE UNIT.** Sept. 77. £5-99.  
**A.F. SIGNAL GENERATOR.** Aug. 78. less dial. £12-89.  
**HEADPHONE ENHANCER.** Jan. 79. £2-60.  
**PASSIVE MIXER.** Oct. 78. £3-72.  
**MIC AMP.** Dec. 78. £2-80.  
**AUDIBLE FLASHER.** Dec. 78. £1-21.

Board & Case. Instructions are included with this kit.  
 KIT: £18-97. Headphones extra £3-26.

### MARCH 80 KITS

**CABLE & PIPE LOCATOR.** £3-40 less coil former.  
**STEREO HEADPHONE AMPLIFIER.** £14-94  
**DOORBELL REGISTER.** £3-39  
**5 RANGE CURRENT LIMITER.** £4-24.  
**KITCHEN TIMER.** £12-46.  
**UNIBOARD TOUCH SWITCH.** £8-65.

### LOW COST METAL LOCATOR

COMPLETE KIT WITH HANDLE, COIL FORMER, SCREWS etc., ELECTRONIC COMPONENTS and Case £10-99. OR SEPARATELY ELECTRONICS & CASE £5-44. HARDWARE £5-55.  
**3 BAND S.W. RADIO**  
 Simple T.R.F. Design. Covering most Amateur Bands and Short Wave Broadcast Bands. Five controls—Bandset, Bandspread, Reaction, Wavechange and Attenuator. Coil selection is by Wavechange Switch. Use with Headphones or a Crystal earpiece. Kit contains all the components required, including the P.C.

MAGENTA gives you **FAST DELIVERY BY FIRST CLASS POST OF QUALITY COMPONENTS & KITS.** All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

**MAGENTA ELECTRONICS LTD.**  
 ES16, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.

OFFICIAL ORDERS FROM SCHOOLS, UNIVERSITIES ETC. WELCOME. MAIL ORDER ONLY.  
 ALL PRICES INCLUDE 15% VAT ADD 35p POSTAGE TO ALL ORDERS. ALL ORDERS SENT FIRST CLASS. ENQUIRIES MUST INCLUDE S.A.E.

## 1980 ELECTRONICS CATALOGUE

Magenta's Catalogue has been carefully designed for E.E. Readers. Product Data and Illustrations make the Magenta Catalogue an indispensable guide for the constructor. Catalogue includes: Electronic Components, Hardware, Cases, Tools, Test Equipment, details of advertised items and Circuit Ideas for you to build.  
 No minimum order—all products are stock lines. First class delivery of first class

components. Send for your copy and see how easy it is to use the Magenta Catalogue! Write today enclosing 6 x 10p stamps.

**FEB-APRIL NEWSHEET**—Send large S.A.E. Automatically included with catalogues and orders. Keeps you up to date with Magenta and includes extra circuit ideas.

**EUROBOARD BOARD.** £6-20.  
**LOW COST LONG NOSE PLIERS.** £1-97.  
**LOW COST CUTTERS.** £1-98.  
**SWING STORAGE DRAWERS** £5-98.  
**MULTIMETER TYPE 3** 100,000 o.p.v. with transistor tester ranges £39-95.  
**WIRELESS INTERCOM 2 STATION** £42-95.  
**SIREN.** 12V £5-95.  
**P.C.B. ASSEMBLY JIG.** £11-98.  
**P.C.B. ETCHING KIT.** £4-98.  
**A.M.-F.M. AIRCRAFT BAND PORTABLE RADIO** £10-95.  
**WIRE STRIPPERS & CUTTERS** £2-21.  
**ULTRASONIC TRANSDUCERS.** £5-50 pair.  
**P.A. MICROPHONE** coiled lead & switch £4-68.  
**STEREO MICROPHONE PAIR** £10-95.  
**MULTIMETER TYPE 1.** 1,000 o.p.v. with probes. 2" x 3 1/2" x 1". £8-98.  
**MULTIMETER TYPE 2.** 20,000 o.p.v. with probes. 5" x 3 1/2" x 1 1/2". £14-25.  
**F.M. INDOOR AERIAL.** 57p.  
**TELESCOPIC AERIAL.** 120 c.m. £2-38.  
**TELEPHONE PICK-UP COIL.** 72p.  
**CRYSTAL MICROPHONE INSERT.** 55p.  
**SPEAKERS MINIATURE.** 8 ohm 87p. 84 ohm 98p. 80 ohm £1-28.  
**PILLOW SPEAKER.** 8 ohm 98p.  
**8" ROUND SPEAKER.** 8 ohm, SW. £2-28.  
**CABINET SPEAKER.** 8 ohm, SW. 5" speaker. Cabinet 10" x 7" x 4". £5-75.  
**RE-ENTRANT HORN SPEAKER.** 8 ohm S.W. Horn dia. 5 1/2". £5-27.  
**EARPIECES.** Crystal 48p. Magnetic 18p.  
**STETHOSCOPE ATTACHMENT.** Fits our earpieces 69p.  
**BUZZER.** 6V 82p. 12V 85p.  
**MONO HEADPHONES.** 2K Padded. Superior. Sensitive. £3-28.  
**STEREO HEADPHONES.** 8 ohm. Padded. £4-35.

**INTERCOM.** 2 Station. Desk. £7-68.  
**MICROPHONE DYNAMIC.** 600 ohm. Cassette type. £1-38.  
**DENTISTS MIRROR.** Adjustable. £2-44.  
**JEWELLERS EYEGLASS.** £1-08p  
**TRIPLE MAGNIFIER.** £1-63.  
**HAND MAGNIFIER.** 3" Lens. £3-43.  
**SPECTACLE MAGNIFIER.** Clips on to spectacle frame. £4-65  
**ILLUMINATED MAGNIFIERS.** 1 1/2" lens £1-10. 3" lens £2-06.  
**POCKET TOOL SET.** 20 piece. £4-09.  
**SCREWDRIVER SET.** Six piece. £2-18.  
**Q MAX PUNCH.** 1" £2-98. 1/2" £3-06. 1 1/2" £3-24.  
**DRILL 12V.** Hand or stand use. £10-95. Stand £6-88.  
**CAPACITANCE SUBSTITUTION BOX.** Nine values, 100pF—0.22uF. £2-98.  
**QUICKTEST.** Mains connector. £7-38.  
**PLUG IN POWER SUPPLY.** 6, 7.5-9V d.c. 300mA. £4-65.  
**SPRINGS—SMALL.** 100 Asstd. £1-06.  
**CROC CLIP TEST LEAD SET.** 10 leads with 20 clips. £1-15.  
**DIMMER SWITCH.** 240V. 800W. £4-48.  
**TRADITIONAL STYLE BELL.** 3-8V. 70mm chrome gong. £1-60.  
**UNDERDOME BELL.** 4-10V. Smart. Dia. 70mm. £2-48.  
**F.M. TUNER CHASSIS.** 88-108MHz. 9V d.c. £9-49.  
**MORSE KEY.** High speed. £4-28.  
**PANEL METERS.** 60 x 45mm. Modern style. 50uA, 100uA, 1mA, 1A, 25V d.c. £5-98.  
**NIGHT LIGHT.** Plug type. £1-08.  
**CONNECTING WIRE PACK.** 5 x 5yd. coils. 55p.  
**VERO SPOT FACE CUTTER.** £1-21.  
**VERO PIN INSERTION TOOL.** 0-1" £1-66. 0-15" £1-67.  
**RESISTOR COLOUR CODE CALCULATOR.** 21p.

## ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects—including 3 radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S Dec and the components for the projects.

Adventures With Electronics £1-75.  
 Component Pack £16-72 less battery.

ALSO AVAILABLE  
**ADVENTURES WITH MICROELECTRONICS**  
 BOOK £2-35  
 COMPONENTS £30-59

# TEACH IN 80

**E.E. SERIES—ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY.** All top quality components as specified by Everyday Electronics. Our kit comes complete with **FREE COMPONENT IDENTIFICATION SHEET**. Follow this educational series and learn about electronics—Start today LIST A & B components £22-95 also available LIST C (parts 7-12) £2-45. All orders sent by **FIRST CLASS POST**. Our kit contains all these parts:—**LIST A & B:** METER, BREADBOARD, TRANSFORMER, LEDS, POTENTIOMETERS, SWITCHES, SPEAKER, PLUGS, SOCKETS, BATTERY CLIPS, WIRE, CABLE, FUSES, FUSE-HOLDERS, KNOBS, RESISTORS, PHOTOCCELL, DIODES, CAPACITORS.

**CASE WOODWORK KIT** £5-98 extra. Complete kit for tutor desk woodwork, contains all the softwood, hardboard, ramin, panel pins, adhesive, screws, feet, strap-handle, and fixings. Cut to size and ready to assemble.

### IDEAL SOLDERING EQUIPMENT FOR THE TEACH IN AND ELECTRONICS

**ANTEX X25 SOLDERING IRON** 25W £4-98  
**SOLDERING IRON STAND** £2-03  
**SPARE BITS.** Small. Standard, Large. 65p each.  
**SOLDER.** Handy size 78p.  
**DESOLDER BRAID** 69p  
**HOW TO SOLDER BOOKLET** 12p  
**HEAT SINK TWEEZERS** 15p.  
**SOLDER BOBBIN** 30p  
**DESOLDER PUMP** £6-98

# Metrac

## ELECTRONICS & TIME CENTRES

### QUARTZ LCD 11 Function Slim Chronograph

12:30<sup>pm</sup>  
Hours mins secs

8 14<sup>TH</sup>  
Month date day

0:00<sup>00</sup>  
Min secs 1/10 1/100



6 digit, 11 functions, Hours, mins., secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Price only  
**£9.95**

Also available:  
SOLAR CHRONOGRAPH  
M9 Price £11.95

SAME DAY DESPATCH.

M3 Price includes POST & PACKING

### QUARTZ LCD ALARM with Snooze Alarm

12:30<sup>pm</sup>  
Hours mins secs

8 14<sup>TH</sup>  
Month date day

7:30<sup>A</sup>  
Alarm



6 functions plus Alarm. Conference signal, 5 minute snooze alarm, Conference signal sounds 4 secs. before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins. after main alarm and is always preceded by the conference signal.

Price only  
**£9.95**

SAME DAY DESPATCH.

M4 Price includes POST & PACKING

### QUARTZ LCD ALARM CHRONOGRAPH with 12/24 display

12:30<sup>pm</sup>  
Hours mins secs

8 14<sup>TH</sup>  
Month date day

0:00<sup>0</sup>  
Min sec 1/10th



Alarm  
Hours, mins, secs, day of week. Month, date, day of week, alarm, hour, mins., a.m./p.m. 24 or 12 hour display mode. Alarm test. Chronograph, lap time, stop watch 1/10 secs.

Price only  
**£13.95**

Also available:  
SOLAR ALARM CHRONO  
M7 Price £17.95

M16 Price includes POST & PACKING

### QUARTZ LCD Ladies Day Watch

Hours, mins., secs., day, date, back light, auto calendar.

12:30  
Hours mins

8 14  
Month date

:45  
Secs



Fully adjustable bracelet. Only 25 x 20mm and 6mm thick. Silver or Gold.

Price only  
**£7.95**

M15 SAME DAY DESPATCH. P.&P. included


### QUARTZ LCD Ladies Cocktail Watch

Beautifully designed with a very thin bracelet.

12:30  
Hours mins

8 14  
Month date

:45  
Secs

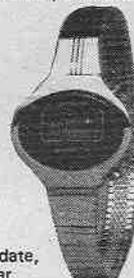

Hours, mins., secs., day, date, backlight and autocalendar. Bracelet fully adjustable to suit slim wrists. State Gold or Silver finish. Only 25 x 20 x 6mm.


Price only  
**£14.95**

M18 SAME DAY DESPATCH. P.&P. included
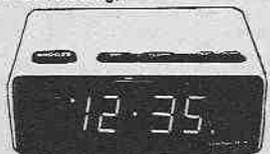
### HANIMEX Electronic LED Alarm Clock

Features and Specification:

Hour, minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).



M13

Price only Mains operated.  
**£10.20** Thousands sold!


### QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back light, quality metal bracelet. 6mm thick.

12:30  
Hours mins

8 14  
Month date

:45  
Secs

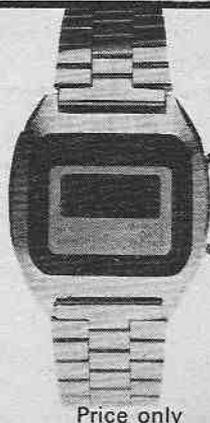

Price only

M1 SAME DAY DESPATCH. **£6.95** P.&P. included

### METAC GUARANTEE

All METAC products carry 12 months guarantee and we also refund your money if not satisfied with our goods or service in the first 10 days.

METAC's well equipped service centre minimises service delays. Please note, we do not delay your order to clear cheques.

Telephone your order using Barclaycard/Access Number on on



**03272 - 76545**  
or  
**01-723 4753**

24 hour answering service  
OR COMPLETE THE  
COUPON

### WHOLESALE MAIL ORDER

Send for our trade price list and order details. Sell our products to your friends and earn yourself

**£££'s**

**NEW 24 HOUR  
DESPATCH SERVICE**

METAC have opened a new even faster Mail Order and Service Centre at DAVENTRY. Orders received before 3.30 p.m. will be despatched same day.

**VISIT OUR ELECTRONIC TIME CENTRES  
AND SEE ONE OF THE MOST IMPRESSIVE QUARTZ WATCH  
RANGES IN BRITAIN**

**LONDON**  
327 EDGWARE ROAD,  
LONDON W.2  
Telephone: 01-723 4753

**DAVENTRY**  
67 HIGH STREET,  
DAVENTRY, NORTHANTS.  
Tel: 03272 76545/77659

**NORTHAMPTON**  
ST. GILES SQUARE,  
NORTHAMPTON  
(Opens 1st February, 1980)

**QUARTZ MELODY  
Alarm Chronograph**

INCREDIBLE WATCH

34 Functions



5 independent working modes, day of week in English, French or German. (Just select the one you like). Hours, mins., secs., day, date, countdown alarm, dual time zone, 1/100th sec., stopwatch. Lap/split time, 1st and 2nd place times. Melody test function.

Price only  
**£17.95**

Price includes  
POST & PACKING

M30 SAME DAY DESPATCH.

**CASIO CHRONO  
95QS - 32B**

Stainless steel case, water resistant to 66 feet. Hours, mins., secs., am/pm, year, month, date, day. Auto calendar. Pre-programmed until the year 2029. 12/24 hour. Stopwatch function. Range 7 hours, 1/100 sec. (Mode) Net time/lap-time/1st - 2nd place times. Dual time function. Accuracy 15 secs. per month. Battery life approx. 4 years.



Price only  
**£23.95**

M22 SAME DAY DESPATCH.

**CASIO F-200  
Sports Chrono**

Attractive Mens watch in black resin with mineral glass. Hours, mins., secs., am/pm. Month, date, alpha-numeric day. Auto-calendar set 28th Feb. Stopwatch working range 1 hour, units 1/100 sec. Mode, Net Time/lap/time/1st - 2nd place times. Accuracy approx. 15 secs. per month. Battery 12 months.



Price only  
**£15.95**

M24 SAME DAY DESPATCH.

**CASIO ALARM  
CHRONO  
81CS - 36B**

Hours, mins, secs., day, and also day, month and year perpetual automatic calendar. 100th sec. chronograph to 7 hours. Net time/lap/time/1st and 2nd place times. User optional 12/24 hr. display. 24 Alarm. User optional, hourly chime. Backlight. mineral glass, stainless steel. Water resistant to 100 ft. Battery life approx. 4 years.



Price only  
**£35.95**

M25 SAME DAY DESPATCH.

**CASIO F-8C  
3 year battery life**

Hours, mins., secs., am/pm, date, day. Auto calendar set 28th February. Accuracy 15 secs. per month. Battery life approx. 3 years.



Price only  
**£10.95**

M36 SAME DAY DESPATCH.

**SEIKO  
CHRONOGRAPH**

Hours, mins., secs., and day of the week. Month date and day of the week. Stopwatch display - Hours., mins., secs., up to 12 hours (mins., secs., 1/100 secs. up to 20 minutes). Lap timing. Continuous time measurement of two competitors. Stainless steel, mineral glass.



Price only  
**£39.95**

SAME DAY DESPATCH.  
M33 including POST & PACKING

**SEIKO ALARM  
CHRONOGRAPH**

With WEEKLY Alarm, Hours, mins., secs., month, date, day, am/pm. Weekly alarm - can be set for every day at designated time, e.g. 6.30 am on Monday, Wednesday and Friday. Alarm set time displayed above time of day. Full stopwatch functions, laptime, split etc.



Price only  
**£57.50**

SAME DAY DESPATCH.  
M10 including POST & PACKING

**SEIKO DIGI-ANA  
CHRONOGRAPH**

TIME AND CALENDAR FUNCTION  
Analog part display Hour, mins., secs. Digital part display: Hour, mins., secs., date, day and colon. Calendar-month, date, day, stopwatch - Hour, mins., secs., 1/100 secs. LAP/STOP and stop marks. Counter-function. Time and calendar setting function.



Price only  
**£69.95**

SAME DAY DESPATCH.  
M62 including POST & PACKING

POST COUPON TO: METAC (24 hour despatch centre), FREEPOST, 47a High Street, Daventry, Northants.

PLEASE COMPLETE BOTH COUPONS

Please send me .....

I enclose P.O./Cheque value .....

Barclaycard/Access No. ....

Name .....

Address .....

FROM:

**METAC ELECTRONICS & TIME CENTRE, EE/5/80,  
67 HIGH STREET, DAVENTRY, NORTHANTS.**

Name .....


Address .....

POST, PACKING AND VAT INCLUDED IN PRICE.

## 24 TUNE DOOR CHIMES
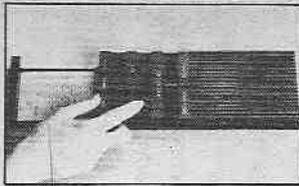
### DOOR TUNES £17.13 + VAT.

Waddington's Videomaster announce a doorbell that doesn't go Brrringg, Ding-Dong or Buzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functional and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES

### PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



#### EXTRA CARTRIDGES:

ROAD RACE - £8.87 + VAT.

Grand Prix motor racing with gear changes, crash noises

SUPER WIPEOUT - £9.17 + VAT.

10 different games of blasting obstacles off the screen

STUNT RIDER - £12.16 + VAT.

Motorcycle speed trials; jumping obstacles, leaping various rows of up to 24 buses etc.

NON-PROGRAMMABLE TV GAMES

6 Game - COLOURSCORE II - £13.50 + VAT.

10 Game COLOUR SPORTSWORLD £22.50 + VAT.

## CHESS COMPUTERS

### STAR CHESS - £55.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces, Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess, it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



### CHESS CHALLENGER 7 - £85.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.


The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black and white and against itself and comes complete with a mains adaptor and 12 months guarantee.

OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:

CHESS CHAMPION - 6 LEVELS £47.39 + VAT.  
CHESS CHALLENGER - 10 LEVELS £138.70 + VAT.

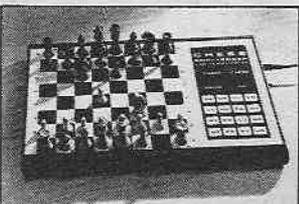BORIS - MULTI-LEVEL TALKING DISPLAY  
£163.04 + VAT.



### ELECTRONIC CHESS BOARD TUTOR £17.17 + VAT.


A special bulk purchase of these amazing chess teaching machines enables us to offer them at only 1/7.17 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game night up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 5 beginners cards, 16 check mate positions, 9 miniature games, 5 openings, 3 end games, 28 chess problems and 2 master games.

## DRAUGHTS COMPUTERS

### CHECKER 2 LEVELS £43.00 + VAT. CHALLENGER 4 LEVELS £77.78 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.
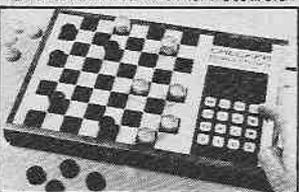
### PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER



## FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon-Sat (Sat 1pm Wed).


To order by telephone please quote your name, address and Access/Barclaycard number.

Postage and Packing FREE.

AJD DIRECT SUPPLIES LIMITED, Dept. EE 5 102 Bellegrave Road,  
Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)
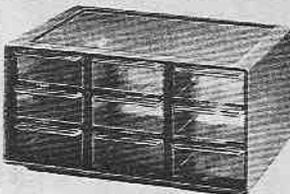
# GREENWELD

443D MILLBROOK ROAD, SOUTHAMPTON SO1 0HX  
All prices include VAT-just add 40p post. Tel (0703) 772501



## COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors diodes and I.C.'s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts!

All parts contained in clearly marked bags in a plastic storage cabinet 228 x 121 x 165mm with 9 drawers into which all parts can be neatly located.

If bought individually parts plus case would cost over £47 but we are offering this for ONLY £31.95 + £1 p & p. Simply send a cheque or P/O for £32.95 for immediate despatch.

#### CONTENTS:

- 200 1/2 watt resistors
- 20 Wire wound resistors
- 70 Ceramic Capacitors
- 70 Mylar Capacitors
- 50 Polyester Capacitors
- 56 Electrolytic Capacitors
- 61 Transistors
- 12 I.C.'s
- 20 L.E.D.'s
- 55 Diodes and rectifiers

Altogether 614 components.


Price includes current catalogue and Greenweld plan for reordering supplies. Plus FREE surprise gift.

### PC ETCHING KIT MK III

Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, D.A.L.O. etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.95
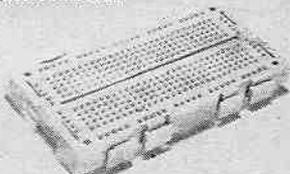
## KITS OF BITS FOR EE PROJECTS

We supply parts for nearly all EE projects - for a detailed components list of this month's, and previous articles, please send SAE.



### VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocks and are joined together. Bus strips on X & Y axes - total 360 connexion points for just £3.70.

### VU METERS

V002 Twin type, 2 meters 40 x 40mm and driver board, supplied with circuit and connexion data, £3.50.

V003 New type, just in. Twin type moulded in one piece, 80 x 40mm (no driver board but suitable circuit supplied). £2.50.

## THE NEW 1980 GREENWELD CATALOGUE

#### FEATURES INCLUDE:

- 60p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 40p + 20p POST

#### WIRE & FLEX

Solid core - ideal for breadboards etc. 50 x 2m lengths many assorted colours, total 100m for £1.30.  
Flex packs - 5 x 5m lengths of multi-strand thin flex, ideal for wiring up circuits. Only 35p

#### EX-COMPUTER PANELS

Z528 Pack of boards containing 100's R's, C's diodes, including at least 50 transistors. Only £1.30.


Z529 TTL pack - Panels with 74 series on, together with code sheet. From simple gates to complex counters, 20 IC's at 1; 100 IC's £4.

#### COMPONENT TRAY

Attractive yellow tray 285 x 165 x 42mm with clear hinged lid and movable compartments. Up to 15 can be made from dividers supplied. As an added bonus, a selection of new surplus components are included, all for the special low price of £3.95.
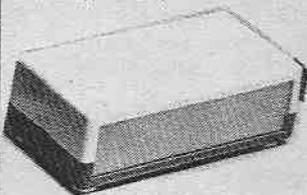
#### INVERTER

Prepare for the Power Cuts! Ready built inverter, 24V DC 200 x 55 x 37mm. In, will power 6 x 8W fluorescent tubes. Circuit supplied. Only £2.90.



#### VEROCASE SALE!!

3 popular sizes of Verocase at drastically reduced prices - these were part of their standard range (15-1411 etc.) but are in GREEN and have been discontinued by Vero. We have purchased their entire stock and offer them as below:

Type No.	Size	Price
21051	180 x 120 x 65mm	£2.30
21052	154 x 85 x 60mm	£1.75
21053	125 x 65 x 40mm	£1.45

#### VERO OFFCUTS

Packs of 100 sq. ins of good size pieces about 4 x 3" in the following types:  
K511 0.1" copper clad ..... £2.00  
Also pieces 2 1/2" x 1" - 10/£1.20, 100/£9  
17 x 32" x 0.1" sheets - 10/£17.50

#### BUZZERS & MOTORS & RELAYS

Z401 Powerful 6V DC Buzzer all metal construction 50mm dia x 20mm 70p.  
Z402 Miniature type Buzzer 5, 9 or 12V, only 22 x 15 x 16mm. Very neat 53p.

Z450 Miniature 6V DC motor, high quality type IC. 2mm dia x 25mm high, with 12mm spindle. Only £1.

Z459 115/230V ac high torque motor with geared reduction down to 50 rpm. Sturdy construction, 70mm dia x 20mm. Spindle 6mm dia x 20mm long. Only £2.00.

W892 Heavy duty 12V relay, ideal for car use - single 15A make contact. Coil 25R. 85p.

W890 DIL reed relay - SPCC 2.4V-10V 200R coil. Only £2.20.

W847 Low profile PC mntg 10 x 33 x 20mm 6V coil. SPCC 3A contacts. 93p.

# TEACH IN 80

We are again supplying all parts required for this major series which started last October. The price for all the Tutor Deck parts is £19.50. Also supplied without breadboard for £13.50. The price for the additional components required for Parts 1-6 is £2.00 and Parts 7-12 is £3.00. All prices include VAT and Postage. Reprints of parts 30p per month

# MAPLIN

## ELECTRONIC SUPPLIES




### SOLDER

A high quality standard solder by Erso Multicore. Ideal for miniature components 22swg. 1kg reel, about 163 metres. Order as **FY70M** Price **£8.50**



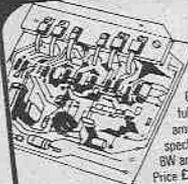
### MINIATURE TRANSFORMERS

Good quality mains transformers to BS415. 6V type: secondaries 0-6V at 500mA - 0-9V at 500mA. Order as **WB06G** Price **£2.63**  
9V type: secondaries 0-9V at 500mA - 0-9V at 500mA. Order as **WB11M** Price **£3.40**  
12V type: secondaries 0-12V at 250mA - 0-12V at 250mA. Order as **WB10L** Price **£2.63**  
15V type: secondaries 0-15V at 200mA - 0-15V at 200mA. Order as **WB15R** Price **£2.63**


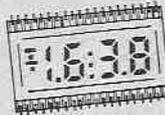
### AMP KITS

Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications. 6W amp kit: Order as **LW36P** Price **£3.83**  
50W amp kit: Order as **LW35Q** Price **£13.73**  
150W amp kit: Order as **LW32K** Price **£14.89**




### LIQUID CRYSTAL DISPLAY

High quality 3 1/2 digit 12.7mm (1/2 inch) high figures. Display has centre colon for use plus and minus signs and overflow indicator for use in panel meters. In 12-hour clocks and decimal points. Order as **FY89W** Price **£8.89**



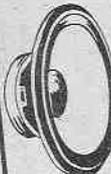
### SIREN

A small, but penetrating siren operating on 12V DC (1.2A) Dia. 75mm. Order as **YB25C** Price **£9.81**


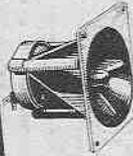
### McKENZIE POWER SPEAKERS

High quality, high power speakers. 12in. 50W 8Ω Order as **XQ79L** Price **£19.60**  
12in. 50W 16Ω Order as **XQ80B** Price **£19.60**  
12in. 80W 8Ω Order as **XQ81C** Price **£26.92**  
12in. 80W 16Ω Order as **XQ82D** Price **£26.92**  
15in. 150W 8Ω Order as **XQ83E** Price **£37.80**  
15in. 150W 16Ω Order as **XQ84F** Price **£37.80**



### PIEZO HORN TWEETER

Very simply added to any speaker system up to 100W rms. No crossover required. Distortion < 1%. Order as **WF09K** Price **£5.27**




### 20,000 OHM/VOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 250kΩ; 50kΩ; Decibels -20 to -72dB. Complete with test leads, battery and instruction leaflet. Order as **YB83E** Price **£13.70**


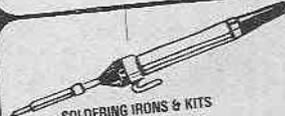
### MIC STAND

Quality microphone stand extends to 1.5m. Boom arm 1m long adjustable. Stand: Order as **XB45Y** Price **£12.71**  
Boom: Order as **XB46A** Price **£11.25**



### SOLDERING IRONS & KITS

Antex CX iron, 17W miniature Order as **FY62S** Price **£5.25**  
Antex X25 iron, 25W Order as **FR12N** Price **£4.98**  
CX iron with stand in presentation pack. Order as **FY68Y** Price **£6.89**  
X25 iron with stand in presentation pack. Order as **FY69A** Price **£6.89**



### CLOCK MODULE

Module requires only transformer and two push switches to operate 4-digit, 0.7m red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue. Order as **XL14Q** Price **£8.41**



### QUICK CHARGE RECHARGEABLE CELL

1.2V. Size AA(HF7). Fully recharged in 5 hours with 150mA. Capacity: 450mAh. Will last for at least 500 full charge/discharge cycles. Charge cells now! Change to quick-charge cells now! Order as **LR74R** Price **£1.49**

### POCKET MULTIMETER

Amazing value 4,000 ohms per volt DC jewelled moving coil meter. Ranges: DC volts 5, 25, 250, 500; AC volts 10, 50, 500, 1,000; DC amps 0 to 0.25mA, 0 to 250mA; Resistance 0 to 800kΩ; Decibels -10 to +22dB. Size only 3 1/2 x 2 1/4 x 1 1/4 inches. Complete with test leads, battery and instructions. Order as **FL60Q** Price **£6.75**



### REVERBERATION SYSTEM

The 'concert hall' sound in your living room. Driver module: Order as **XB85G** Price **£6.14**  
Requires + and - 15V 20mA power supply ready built suitable for Driver Module. Order as **YL17T** Price **£4.73**  
Spring line with 3 sec. reverb time: Order as **XL08J** Price **£5.43**  
Spring line with 7 sec. reverb time: Order as **XB84F** Price **£11.13**



### KEYBOARDS

High quality keyboards with hard-wearing sloping fronted plastic keys. With keys mounted on nylon bushed steel levers 49 note C to C.

Order as **XB15R** Price **£26.42**  
61-note C to C. Order as **XB16S** Price **£32.33**  
With keys pivoted on a hard-wearing moulded fulcrum. Order as **XB17T** Price **£21.87**  
49 note C to C.




### MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A; Resistance 5k, 50k, 500k ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet. Order as **YB87U** Price **£39.30**


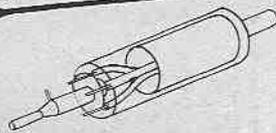
### TURNTABLES

Autochanger complete with stereo ceramic cartridge and circuit to make a complete low cost record player ideal for the young pop fan. Order as **XD06A** Price **£18.48**  
Single-play rim drive turntable with stereo ceramic cartridge. Order as **XB23A** Price **£28.19**  
Single-play belt-drive turntable 'S'-shaped tone arm. Order as **XB25C** Price **£30.83**



### LASER TUBE

A helium-neon 0.5mW laser tube. Full details on page 262 or our catalogue. Order as **XL11M** Price **£124.00**



### ADJUSTABLE LAMP

Adjustable to get a bright light on miniature components. With bracket for clamping or bolting to bench or wall. Shade and position fully adjustable and stable. Finished in white. Order as **XY25C** Price **£12.96**

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until JUNE 15th 1980. Export customers deduct 13% and export postage will be charged extra at cost. Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER.

# MAPLIN

## ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155.  
Shop: 284 London Road, Westcliff-on-Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000.

# BIPAK SEMICONDUCTORS,

## TRANSISTORS

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	£0.23	BC134	£0.17	BF478	£0.78	BF840	£0.98	ZTX108	£0.12	2N3415	£0.18
AC113	£0.23	BC135	£0.17	BD179	£0.85	BF879	£0.82	ZTX109	£0.12	2N3416	£0.18
AC115	£0.23	BC136	£0.17	BD180	£0.85	BF880	£0.82	ZTX109	£0.12	2N3417	£0.18
AC117	£0.35	BC137	£0.21	BD181	£0.90	BF829	£0.25	ZTX301	£0.14	2N3614	£1.15
AC117K	£0.35	BC139	£0.37	BD182	£1.04	BFX30	£0.35	ZTX302	£0.18	2N3615	£1.21
AC121	£0.23	BC140	£0.35	BD183	£1.09	BFX54	£0.25	ZTX303	£0.18	2N3616	£1.21
AC122	£0.16	BC141	£0.32	BD184	£1.27	BFX55	£0.28	ZTX304	£0.23	2N3707	£0.09
AC125	£0.21	BC142	£0.25	BD185	£0.78	BFX56	£0.29	ZTX305	£0.17	2N3702	£0.09
AC126	£0.21	BC143	£0.25	BD186	£0.78	BFX57	£0.25	ZTX500	£0.15	2N3703	£0.09
AC127	£0.21	BC145	£0.53	BD187	£0.86	BFX88	£0.25	ZTX501	£0.14	2N3704	£0.08
AC128	£0.18	BC147	£0.08	BD188	£0.88	BFX90	£0.43	ZTX502	£0.18	2N3705	£0.08
AC128K	£0.30	BC148	£0.08	BD189	£0.90	BFY30	£0.18	ZTX503	£0.14	2N3706	£0.09
AC132	£0.23	BC149	£0.08	BD190	£0.90	BFY51	£0.20	ZTX504	£0.23	2N3707	£0.09
AC134	£0.23	BC150	£0.23	BD195	£1.04	BFY52	£1.04	ZTX505	£0.23	2N3708	£0.08
AC137	£0.23	BC151	£0.25	BD196	£1.04	BFY53	£0.20	ZTX550	£0.18	2N3708A	£0.08
AC141	£0.25	BC152	£0.25	BD197	£1.09	BP19	£0.44	2N388	£0.41	2N3709	£0.08
AC141K	£0.35	BC154	£0.25	BD198	£1.09	BP20	£0.44	2N388A	£0.64	2N3710	£0.08
AC142	£0.42	BC157	£0.12	BD199	£1.14	BSX25	£0.92	2N404	£0.23	2N3711	£0.08
AC142K	£0.23	BC158	£0.12	BD200	£1.14	BSX19/20	£0.92	2N404	£0.23	2N3712	£0.08
AC153	£0.25	BC159	£0.12	BD201	£0.92	BSX25	£0.92	2N404	£0.23	2N3713	£0.08
AC153K	£0.35	BC160	£0.30	BD202	£0.92	BSY25	£0.18	2N999	£0.53	2N3820	£0.40
AC154	£0.23	BC161	£0.44	BD201	£0.92	BSY26	£0.18	2N996	£0.15	2N3821	£0.09
AC155	£0.23	BC167	£0.17	BD206	£1.96	BSY27	£0.18	2N997	£0.14	2N3822	£0.09
AC156	£0.23	BC168	£0.10	BD203	£0.92	BSY28	£0.18	2N998	£0.14	2N3823	£0.09
AC157	£0.23	BC169	£0.10	BD204	£0.92	BSY29	£0.18	2N999	£0.37	2N3824	£0.12
AC158	£0.23	BC169C	£0.12	BD203/204mp	£1.96	BSY30	£0.18	2N705	£0.12	2N3905	£0.12
AC168	£0.23	BC170	£0.10	BD205	£0.92	BSY31	£0.18	2N706A	£0.14	2N3906	£0.12
AC167	£0.23	BC171	£0.10	BD206	£0.92	BSY40	£0.33	2N707	£0.55	2N4058	£0.12
AC168	£0.23	BC172	£0.10	BD206	£0.92	BSY41	£0.33	2N708	£0.16	2N4059	£0.16
AC169	£0.23	BC173	£0.10	BD207	£0.92	BSY42	£0.15	2N711	£0.35	2N4061	£0.14
AC171	£0.23	BC174	£0.10	BD208	£0.92	BSY43	£0.15	2N711	£0.35	2N4061	£0.14
AC176	£0.21	BC175	£0.40	BD222	£0.90	BSY95A	£0.15	2N718	£0.29	2N4062	£0.14
AC176K	£0.30	BC177	£0.18	BD225	£0.54	BRY39	£0.52	2N718A	£0.58	2N4062	£0.63
AC178	£0.29	BC178	£0.18	BD232	£0.63	BU105	£1.84	2N718	£0.33	2N4063	£0.75
AC178K	£0.35	BC179	£0.18	BD233	£0.55	BU105/02	£2.24	2N727	£0.33	2N4135	£0.12
AC180	£0.23	BC180	£0.29	BD230	£0.63	BU105/02	£2.24	2N727	£0.33	2N4135	£0.12
AC180K	£0.32	BC181	£0.10	BD235	£0.63	BU205	£1.81	2N744	£0.23	2N4138	£0.12
AC181	£0.23	BC182	£1.25	BD236	£0.67	BU208	£2.19	2N914	£0.17	2N5172	£0.16
AC181K	£0.32	BC182L	£0.10	BD237	£0.63	BU208/02	£2.59	2N918	£0.35	2N5194	£0.64
AC187	£0.32	BC183	£0.10	BD238	£0.69	MJE2955	£1.04	2N929	£0.23	2N5245	£0.46
AC187K	£0.32	BC183L	£0.10	BD239A	£0.58	MJE3055	£0.69	2N930	£0.21	2N5294	£0.38
AC188	£0.32	BC184	£0.10	BD240A	£0.58	MJE3440	£0.60	2N946	£0.46	2N5296	£0.41
AC188K	£0.32	BC184L	£0.10	BDX32	£2.53	MP8113	£0.60	2N1131	£0.21	2N5457	£0.37
AC197	£0.40	BC185	£0.25	BDY11	£1.50	MPP102	£0.32	2N132	£0.21	2N5458	£0.37
AC198	£0.40	BC187	£0.25	BDY17	£2.07	MPP104	£0.40	2N1302	£0.17	2N5459	£0.40
AC199	£0.40	BC207	£0.13	BDY20	£0.92	MPP105	£0.40	2N1303	£0.21	2N5551	£0.41
AC200	£0.40	BC208	£0.13	BDX77	£2.04	MPS A05	£0.23	2N1304	£0.21	2N6027	£0.38
AC201	£0.40	BC209	£0.14	BDX78	£2.04	MPS A06	£0.23	2N1305	£0.21	2N6121	£0.81
AC202	£0.40	BC212	£0.10	BF117	£0.58	MPS A55	£0.23	2N1306	£0.29	2N6122	£0.81
AC227	£0.40	BC212L	£0.10	BF118	£0.80	MPS A56	£0.23	2N1307	£0.29	2S301	£0.58
AC228	£0.37	BC213	£0.10	BF119	£0.88	ND120	£0.21	2N1308	£0.35	2S302	£0.49
AC229	£0.58	BC213L	£0.10	BF121	£0.58	OC20	£2.13	2N1309	£0.35	2S302A	£0.49
AC230	£0.40	BC214	£0.10	BF123	£0.69	OC22	£1.73	2N1309	£0.40	2S303	£0.64
AD130	£0.40	BC214K	£0.10	BF124	£0.69	OC23	£1.73	2N1310	£0.40	2S403	£0.82
AD130K	£0.81	BC225	£0.30	BF127	£0.68	OC24	£1.55	2N1711	£0.23	2S305	£0.82
AD140	£0.69	BC226	£0.41	BF152	£0.29	OC25	£1.15	2N1889	£0.52	2S306	£0.92
AD142	£0.98	BC227	£0.18	BF153	£0.29	OC26	£1.15	2N1890	£0.52	2S307	£0.92
AD143	£0.86	BC228	£0.18	BF154	£0.25	OC28	£0.92	2N1893	£0.35	2S321	£0.66
AD149	£0.69	BC231	£0.18	BF155	£0.40	OC29	£1.08	2N247	£0.86	2S322	£0.66
AD161	£0.69	BC281A	£0.18	BF156	£0.32	OC33	£1.04	2N247	£0.86	2S322A	£0.66
AD162	£0.40	BC301	£0.32	BF157	£0.32	OC36	£1.04	2N2160	£0.00	2S323	£0.66
AD161/2	£0.81	BC302	£0.33	BF158	£0.32	OC41	£0.23	2N2192	£0.44	2S324	£0.82
AF124	£0.35	BC303	£0.32	BF159	£0.32	OC42	£0.25	2N2193	£0.44	2S325	£0.82
AF125	£0.35	BC304	£0.44	BF160	£0.35	OC44	£0.28	2N2194	£0.44	2S326	£0.82
AF126	£0.35	BC307	£0.44	BF161	£0.35	OC45	£0.23	2N2195	£0.25	2S327	£0.82
AF127	£0.37	BC328	£0.17	BF163	£0.55	OC70	£0.17	2N2218	£0.23	2S327	£0.82
AF128	£0.37	BC337	£0.17	BF164	£0.55	OC71	£0.17	2N2218A	£0.23	2S331	£1.09
AF178	£0.69	BC338	£0.17	BF165	£0.55	OC72	£0.28	2N2219	£0.23	2S331B	£1.09
AF179	£0.69	BC440	£0.35	BF167	£0.28	OC74	£0.30	2N2219A	£0.23	2S337	£0.46
AF180	£0.69	BC441	£0.35	BF173	£0.23	OC75	£0.35	2N2220	£0.23	2S337B	£0.46
AF181	£0.69	BC442	£0.35	BF174	£0.23	OC76	£0.35	2N2221	£0.23	2S337C	£0.46
AF186	£0.58	BC461	£0.44	BF177	£0.30	OC77	£0.58	2N2221A	£0.23	2S346	£0.52
AF239	£0.44	BC477	£0.23	BF178	£0.30	OC81	£0.25	2N2222	£0.23	2S347	£0.75
AL102	£1.38	BC478	£0.23	BF179	£0.30	OC81DD	£0.28	2N2222A	£0.23	2S348	£0.92
AL103	£1.36	BC479	£0.23	BF180	£0.35	OC82	£0.28	2N2268	£0.21	2S390	£0.41
AS226	£0.44	BC547	£0.12	BF181	£0.35	OC82D	£0.35	2N2389	£0.16	2S392	£0.44
AS227	£0.44	BC548	£0.12	BF182	£0.35	OC83	£0.35	2N2389A	£0.16	2S406	£0.52
AS228	£0.44	BC549	£0.12	BF183	£0.35	OC84	£0.44	2N2411	£0.29	2S407	£0.40
AS229	£0.44	BC550	£0.16	BF184	£0.23	OC139	£0.92	2N2412	£0.29	2S408	£0.60
AS230	£0.35	BC556	£0.16	BF185	£0.23	OC140	£0.92	2N2645	£0.54	2S409	£0.86
AS231	£0.35	BC557	£0.15	BF186	£0.30	OC169	£0.40	2N2711	£0.25	2S410	£0.86
AS232	£0.35	BC558	£0.14	BF187	£0.30	OC170	£0.40	2N2712	£0.25	2S411	£0.86
AS233	£0.35	BC559	£0.33	BF188	£0.30	OC171	£0.40	2N2714	£0.21	2S412	£0.86
AS234	£0.35	BC560	£0.33	BF189	£0.30	OC200	£0.44	2N2904	£0.21	2S413	£1.84
AS235	£0.35	BCY31	£0.63	BF194	£0.12	OC201	£1.09	2N2904A	£0.24	2S414	£0.81
AS236	£0.35	BCY32	£0.63	BF195	£0.12	OC202	£1.38	2N2905	£0.24	2S415	£0.81
AS237	£0.35	BCY33	£0.63	BF196	£0.12	OC203	£0.98	2N2905A	£0.23	2S416	£1.55
AS238	£0.35	BCY34	£0.69	BF197	£0.14	OC204	£1.04	2N2906	£0.18	2S417	£1.55
AS239	£0.35	BCY70	£0.17	BF198	£0.16	OC205	£1.32	2N2906A	£0.22	2S418	£1.55
AL104	£1.61	BCY71	£0.17	BF199	£0.16	OC205	£1.32	2N2906A	£0.22	2S419	£1.55
AU110	£1.61	BCY72	£0.17	BF200	£0.35	TIC44	£0.33	2N2907	£0.25	2S420	£1.55
AU113	£1.61	BCZ10	£0.69	BF202	£1.04	TIC45	£0.40	2N2907A	£0.25	2S421	£1.55
BC107	£0.09	BCZ11	£0.69	BF222	£1.04	TIP29A	£0.46	2N2923	£0.17	2S422	£1.55
BC107A	£0.09	BCZ12	£0.69	BF224	£2.20	TIP29B	£0.46	2N2924	£0.17	2S423	£1.55
BC107B	£0.10	BD115	£0.58	BF240	£0.20	TIP29C	£0.51	2N2925	£0.17	2S424	£1.55
BC108	£0.09	BD116	£0.58	BF241	£0.20	TIP30	£0.46	2N2926	£0.17	2S425	£1.55
BC108A	£0.09	BD121	£0.75	BF244	£0.35	TIP30B	£0.48	2N2926B	£0.09	2S426	£1.55
BC108B	£0.09	BD123	£0.75	BF257	£0.29	TIP30C	£0.51	2N2926C	£0.09	2S427	£1.55
BC108C	£0.10	BD124	£0.81	BF258	£0.29	TIP31A	£0.46	2N2926R	£0.09	2S428	£1.55
BC109	£0.12	BD131	£0.40	BF259	£0.40	TIP31B					

DEPT. EE5, PO BOX 6, WARE, HERTS. Tel: 0920-3182

Visit our NEW shop: 3 BALDOCK ST., WARE, HERTS. Telex: 817861

### BOOKS BY BABANI

BP6	Engineers & Machinists Ref. Tables	£0.50
BP14	2nd Book Transistor Equivs. & Subs.	£1.10
BP24	52 Projects Using IC741 (or Equiv.)	£0.95
BP26	Radio Antenna Book Long Distance Reception & Transmission	£0.85
BP27	Giant Chart of Radio Electronic Semiconductor & Logic Symbols	£0.60
BP32	Build Metal & Treasure Locators	£1.00
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	£1.25
BP36	50 Ccts. use Germ/Si/Zener Diodes	£0.75
BP39	50 Field Effect Trans Projects	£1.25
BP40	Digital IC Equivs. & Pin Connection	£2.50
BP41	Linear IC Equivs. & Pin Connection	£2.75
BP42	50 Simple LED Circuits	£0.75
BP43	How to make Walkie-Talkies	£1.25
BP45	Projects on Opto-electronics	£1.25
BP46	Radio Circuits Using IC's	£1.35
BP47	Mobile Discotheque Handbook	£1.35
BP48	Electronics Projects for Beginners	£1.35
BP49	Popular Electronic Projects	£1.45
BP50	IC LM3909 Projects	£1.35
BP55	Radio Stations Guide	£1.45
BP160	Coil Design & Construction Manual	£0.75
BP202	Handbook of Integrated Circuits Equivalents & Substitutes	£1.00
BP205	1st Book Hi-Fi Speaker Enclosures	£0.75
BP213	Circuits for Model Railways	£1.00
BP215	Shortwave Circuits & Gear for Experimenters & Radio Hams	£0.85
BP217	Solid State Power Supply Handbook	£0.85
BP221	28 Tested Transistor Projects	£1.25
BP222	Short-wave Receivers for Beginners	£0.95
BP223	30 Projects using IC CA3130	£0.95
BP224	50 CMOS IC Projects	£0.95
BP225	A Practical Intro to Digital IC's	£0.95
BP226	Build Advanced Short-wave Receivers	£1.20
BP227	Beginners Guide to Building Electronic Projects	£1.25
RCC	Resistor Colour Code Chart	£0.10

### NEWNES BOOKS

216	Transistors 3rd Ed.	£1.00
218	Radio & Television	£1.25
219	Electronics	£1.15
220	Colour TV 2nd Ed.	£1.15
221	Hi-Fi	£1.15
223	20 Solid State Proj. for Home	£1.95
224	110 Int. Circ. Proj. for Home	£2.95

231	Beginners Guide to Transistors	£2.25
232	Beginners Guide to Electric Wiring	£2.25
233	Beginners Guide to Radio	£2.25
234	Guide to Colour TV	£2.75
235	Electronic Diagrams	£1.80
236	Electronic Components	£1.80
237	Printed Circuit Assembly	£1.80
238	Transistor Pocket Book	£3.90

240	Semiconductor Handbook Part 1	£5.25
241	Semiconductor Handbook Part 2	£4.25
242	Electronic Pocket Book	£3.90
244	Beginners Guide to Integrated Circuits	£2.75

BI-PAK CMOS Data Book 50p

### SWITCHES

Description	No.	Price
DPDT miniature slide	1973	£0.16
DPDT standard slide	1974	£0.17
Toggle switch SPST 12 amp 250V ac	1975	£0.38
Toggle switch DPDT 1 amp 250V ac	1976	£0.48
Rotary on-off mains switch	1977	£0.58
Push switch—Push to make	1978	£0.18
Push switch—Push to break	1979	£0.21

ROCKER SWITCH	Colour	No.	Price
A range of rocker switches SPST—moulded in high insulation material available in a choice of colours ideal for small apparatus	RED	1980	£0.35
	BLACK	1981	£0.35
	WHITE	1982	£0.35
	BLUE	1983	£0.35
	YELLOW	1984	£0.35
	LUMINOUS	1985	£0.35

Description	No.	Price
Miniature SPST toggle 2 amp 250V ac	1958	£0.81
Miniature SPST toggle 2 amp 250V ac	1959	£0.86
Miniature DPDT toggle 2 amp 250V ac	1960	£0.91
Miniature DPDT toggle centre off 2 amp 250V ac	1961	£1.07
Push-button SPST 2 amp 250V ac	1962	£1.04
Push-button SPST 2 amp 250V ac	1963	£1.09
Push-button DPDT 2 amp 250V ac	1964	£1.34

**MIDGET WAFER SWITCHES**  
Single bank wafer type—suitable for switching at 250V ac 100mA or 150V dc non-reactive loads make-before-break contacts. These switches have a spindle 0.25 in dia. and 30 indexing.

Description	No.	Price
1 pole 12 way	1965	£0.55
2 pole 6 way	1966	£0.55
3 pole 4 way	1967	£0.55
4 pole 3 way	1968	£0.55

MICRO SWITCHES	No.	Price
Plastic button gives simple 1 pole change over action	1970	£0.29
Rating 10 amp 250V ac		

### OPTOELECTRONICS

**NEW INCREASED RANGE—ALL 1ST QUALITY LEDS (diffused)**

O/No.	Type	Size	Colour	Price
1501	ARL209 (TIL209)	3mm (-125)	RED	£0.10
1502	MIL322 (TIL21)	3mm (-125)	GREEN	£0.16
1503	MIL331 (OPT121A)	3mm (-125)	YELLOW	£0.16
1504	ARL4950 (FLV117)	5mm (-2)	RED	£0.10
1505	MIL5251 (TIL222)	5mm (-2)	GREEN	£0.16
1506	MIL5351 (MV5353)	5mm (-2)	YELLOW	£0.16
1509	FLV111	5mm (-2)	CLEAR (iii, Red)	£0.13

**SUPER 'HI-BRITE' TYPE**

O/No.	Type	Size	Colour	Price
1521	MIL32	3mm (-125)	RED	£0.11
1522	MIL52	5mm (-2)	RED	£0.11
1514	ORP12	Light dependent resistor		£0.70
1520	OCPT7	Photo transistor		£0.40

**LED CLIPS**

O/No.	Type	Price
1508/125	pack of 5 125 clips	£0.17
1508/2	pack of 5 2 clips	£0.21

**DISPLAYS**

O/No.	Type	Price
DL703	7 segment D P left (30" height)	Common Anode £0.85
DL707	7 segment D P left (30" height)	O/N/O. 1523 Common Anode
DL707	7 segment D P left (30" height)	O/N/O. 1510 Common Anode
DL527	7 segment D P left (50" height)	Common Anode £2.00
RED	Two-Digit Reflector	O/N/O. 1524 Common Anode
DL727	7 segment D P right (510" height)	Common Anode £2.07
DL747	7 segment D P left (630" height)	Common Anode £1.73
RED	Single Digit Light Pipe	O/N/O. 1511

**OPTO-ISOLATORS**  
Isolation Breakdown—Voltage 1500—continuous fwd. current 100 mA

O/No.	Type	Price
IL74	Single Channel 6 pin DIP standard type—optically coupled pair with Infra-red LED Emitter and NPN Silicon Photo Transistor	O/N/O. 1497 £0.61
ILD74	Multi-Channel 8 pin DIP Two Isolated Channels	O/N/O. 1498 £1.22
ILQ74	Multi-Channel 16 pin DIP Four Isolated Channels	O/N/O. 1499 £2.69

**MEL II (TIL8) NPN LIGHT DETECTOR**  
Silicon Photo Darlington Amplifier—VCBO 30V VECO 10V Ic 100mA Ptot 300mW I Min. 0-5 Typ 2mA Id 100mA/NA  
O/N/O. 1496 £0.29  
O/N/O. 1495 £0.29

### TEACH-IN 80

We can offer ex stock all the parts required (except battery and euroboard) for this series of projects as listed in the October issue of Everyday Electronics.

- (a) KIT 1 TUTOR DECK (except Battery & Euroboard) £14.00 inc. P & P AND V.A.T.
- (b) KIT 2 ADDITIONAL COMPONENTS for Parts 1-6 £1.75 inc P & P AND V.A.T.
- (c) KIT 3 ADDITIONAL COMPONENTS for Parts 7-12 £2.55 inc P & P AND V.A.T.

OR buy ALL the above 3 kits for the total price of £18.00 including P & P AND V.A.T.

### FUSE HOLDERS AND FUSES

Description	No.	Price
20mm x 5mm chassis mounting	506	£0.14
1 1/2 in. x 1/2 in. chassis mounting	507	£0.14
1 in. car inline type	508	£0.18
Panel mounting 20mm	509	£0.23
Panel mounting 1 1/2 in.	510	£0.37

**QUICK BLOW 20mm**

Type	No.	Type	No.	Price
150mA	611	7p 1A	615	5p
250mA	612	6p 1.5A	616	7p
500mA	613	6p 2A	617	6p
800mA	614	6p 2.5A	618	7p

**ANTI-SURGE 20mm**

Type	No.	Type	No.	Price
100mA	622	1A	625	2.5A
250mA	623	2A	626	3.15A
500mA	624	1/6A	627	5A

**QUICK-BLOW 1 1/2 in.**

Type	No.	Type	No.	Price
250mA	631	500mA	632	800mA

Type	No.	Type	No.	Price
1A	635	2.5A	638	4A
2A	637	3A	639	5A

### NUTS AND BOLTS

**BA BOLTS**—packs of BA threaded cadmium plated crews slotted cheese head. Supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
1 in. OBA	839	£1.38	1/2 in. 4BA	846	£0.37
1/2 in. OBA	840	£0.85	1/4 in. 4BA	847	£0.29
1 in. 2BA	842	£0.75	1 in. 5BA	848	£0.46
1/2 in. 2BA	843	£0.52	1/2 in. 6BA	849	£0.24
1/4 in. 2BA	844	£0.60	1/4 in. 6BA	850	£0.29
1 in. 4BA	845	£0.51			

**BA NUTS**—packs of cadmium plated full nuts in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	855	£0.83	4BA	857	£0.35
2BA	856	£0.55	6BA	858	£0.28

**BA WASHERS**—flat cadmium plated plain stamped washers supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	859	£0.16	4BA	861	£0.14
OBA	860	£0.14	6BA	862	£0.14

**SOLDER TAGS**—Hot tinned supplied in multiples of 50.

Type	No.	Price	Type	No.	Price
OBA	851	£0.46	4BA	853	£0.25
2BA	852	£0.32	6BA	854	£0.25

### AUDIO LEADS

No.	Type	Price
107	FM Indoor Ribbon Aerial	£0.69
113	3.5mm Jack plug to 3.5mm Jack plug length 1.5m	£0.85
114	5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5 length 1.5m	£0.98
115	5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4 length 1.5m	£0.98
116	Car aerial extension screened insulated lead. Fitted plug and socket	£1.44
117	AC mains connecting lead for cassette recorders and radios 2 metres	£0.78
118	5 pin DIN phono plug to stereo headphone. Jack socket	£1.21
119	2 + 2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m	£1.04
120	Car stereo connector. Variable geometry plug to fit most car cassettes. 8-track cartridge and combination units. Supplies with inlined fuse power lead and instructions	£0.69
123	6.6m Coiled Guitar Lead Mono Jack plug to Mono Jack plug Black	£1.72
124	3 pin DIN plug to 3 pin DIN plug. Length 1.5m	£0.85
126	5 pin DIN plug to Tinned open end. Length 1.5m	£0.85
127	5 pin DIN plug to 4 Phono Plugs. All colour coded. Length 1.5m	£1.49
128	5 pin DIN plug to 5 pin DIN socket. Length 1.5m	£0.82
129	5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m	£1.21
130	2 pin DIN plug to 2 pin DIN inline socket. Length 5m	£0.78
131	5 pin DIN plug to 3 pin DIN plug 1 & 4 & 3 & 5 Length 1.5m	£0.95
132	2 pin DIN plug to 2 pin DIN socket. Length 10m	£1.13
133	5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m	£0.86
134	5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm	£0.78
135	5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm	£0.78
136	Coiled stereo headphone extension lead. Black. Length 6m	£2.01
178	AC mains lead for calculators, etc.	£0.52

### TRANSFORMERS

**MINIATURE MAINS** Primary 240V

No.	Secondary	Price
2021	6V-6V 100mA	£1.04
2023	12V-0-12V 100mA	£1.29

**MINIATURE MAINS** Primary 240V with two independent secondary windings

No.	Type	Price
2024	MT1200-6V 0-6V RMS	£1.84
2025	MT150-0-12V 0-12V RMS	£1.84

**1 AMP MAINS** Primary 240V

No.	Secondary	Price
2026	6V-0-6V 1 amp	£2.88 P & P 45p
2027	9V-0-9V 1 amp	£2.30 P & P 45p
2028	12V-0-12V 1 amp	£2.99 P & P 55p
2029	15V-0-15V 1 amp	£3.16 P & P 55p
2030	30V-0-30V 1 amp	£3.97 P & P 85p

**STANDARD MAINS** Primary 240V  
Multi-tapped secondary mains transformers available in 1 amp, 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50V. Voltages available by use of taps.

No.	Rating	Price
2031	1/2 amp	£3.91 P & P 85p
2032	1 amp	£5.08 P & P 85p
2033	2 amp	£6.27 P & P £1
2035	24V Primary 0-55V @ 2A Secondary	£7.30 P & P £1

**SPECIAL OFFER**  
2042 240V Primary 0-20V @ 2A Secondary. By removing 5 turns for each volt from the secondary winding any voltage up to 20V @ 2A is easily obtainable ideal for the experimenter.  
£1.50 P & P 85p

### CASES AND BOXES

**INSTRUMENT CASES** In two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.73
156	11in	6in	3in	£2.02
157	6in	4 1/2in	1 1/2in	£1.79
158	9in	5 1/2in	2 1/2in	£2.43

**ALUMINIUM BOXES** Made from bright all. folded construction each box complete with half-inch-deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.85
160	4in	4in	1 1/2in	£0.85
161	4in	2 1/2in		

**EDITOR**

F. E. BENNETT

**ASSISTANT EDITOR**

B. W. TERRELL B.Sc.

**PRODUCTION EDITOR**

D. G. BARRINGTON

**TECHNICAL SUB-EDITOR**

S. E. DOLLIN B.Sc.

**ART EDITOR**

R. F. PALMER

**ASSISTANT ART EDITOR**

P. A. LOATES

**TECHNICAL ILLUSTRATOR**

D. J. GOODING

**EDITORIAL OFFICES**

Kings Reach Tower,  
Stamford Street,  
London SE1 9LS  
Phone: 01-261 6873

**ADVERTISEMENT MANAGER**

R. SMITH  
Phone: 01-261 6671

**REPRESENTATIVE**

N. BELLWOOD  
Phone: 01-261 6865

**CLASSIFIED MANAGER**

C. R. BROWN  
Phone: 01-261 5762

**MAKE-UP AND COPY DEPARTMENT**

Phone 01-261 6615

**ADVERTISEMENT OFFICES**

Kings Reach Tower  
Stamford Street,  
London SE1 9LS

# Projects... Theory... and Popular Features ...

The integrated circuit ("microchip") is nowadays a commonplace component widely used in all manner of projects, from the simplest to the quite complex designs.

Indeed we have become dependent on this device to a very marked degree, for without it many projects would just not be possible. This month, as it happens, four out of the six projects presented use i.c.s.

The circuit diagram of any project where one or several i.c.s are used gives a much simplified picture of the true or actual state of affairs circuit-wise. Within the outline symbol representing the i.c. exists another world of microcircuitry, made up of elements that are the microscopic counterpart of those discrete resistors, diodes and transistors we are also dependent upon.

But is it important what lies within the i.c.? Maybe not to the average constructor who sticks to published designs. The i.c.s can remain simply "black boxes" performing their allotted functions. The inside "works" need not concern the user.

Most significantly of all, thanks to the widespread use of i.c.s we have become accustomed to low component counts for many projects. So when some moderately ambitious circuit is presented today in an entirely discrete form we are likely to be staggered by the number of individual components involved.

The *Dual Line Game* (an analogue computing system) uses 67 resistors, 49 transistors and 139 diodes. Truly profligate, one might exclaim. But we needs must refocus to the discrete scene, and regain true perspective in terms of actual basic circuit elements.

Of course using a large number of discrete components makes for more physical assembly work. But to the hobbyist that should not be any punishment. As a matter of fact the method of assembly adopted for the *Dual Line Game* is interesting and instructive in itself; it illustrates a compact "book form" of construction where stacked circuit boards are interconnected by ribbon wiring—a method often used in advanced professional equipment.

The hobby of electronics construction undoubtedly owes much of its advancement and popular appeal to microelectronics. Yet there is still plenty of fun and instruction to be derived from the use of discrete semiconductors, which bring one into more intimate contact with the basic circuitry. And suitable devices are generally obtainable at attractive prices.



Our June issue will be published on Friday, May 16. See page 337 for details.

**Readers' Enquiries**


We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

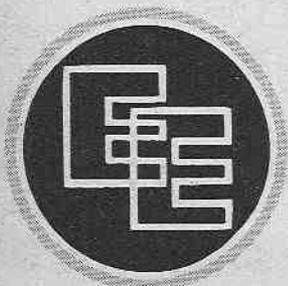**Component Supplies**

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.



# Everyday ELECTRONICS

VOL. 9 NO. 5

MAY 1980

## CONSTRUCTIONAL PROJECTS

- PRETUNED 4-STATION RADIO** Programme change at the turn of a switch by F. G. Rayer 316
- LIGHTS WARNING SYSTEM** Guards against a flat battery by K. Cummins 320
- BATTERY VOLTAGE MONITOR** Keep an eye on battery state by A. P. Donleavy 334
- DUAL LINE GAME** Can you beat it? by A. Russell 338
- AUTOFADE** Voice operated switch for disco or P.A. by S. R. Beeching 350
- UNIBOARDS: 5—AUDIO TONE GENERATOR** Low power replacement for an electrical buzzer  
by A. R. Winstanley 354

## GENERAL FEATURES

### EDITORIAL

- SHOP TALK** Retail news, products and component buying by Dave Barrington 314
- TEACH-IN '80** Part 8: The transistor as a two-state device by S. R. Lewis, B.Sc. 323
- ELECTRONIC WARFARE** Electronics for the military by G. A. G. Brooke 324
- JACK PLUG AND FAMILY** Cartoon by Doug Baker 330
- COUNTER INTELLIGENCE** A retailer comments by Paul Young 336
- FOR YOUR ENTERTAINMENT** Electronic jargon and binaural sound by Adrian Hope 336
- EVERDAY NEWS** What's happening in the world of electronics 346
- RADIO WORLD** A commentary by Pat Hawker 348
- SQUARE ONE** Beginners Page: Stocking up, capacitors 356
- PROFESSOR ERNEST EVERSURE** The Extraordinary Experiments of. by A. J. Bassett 358
- THE ADVENTURES OF TANTY BEAD** Cartoon by Matthew A. Reed 361
- WORKSHOP MATTERS** Choice of signal sources by Harry T. Kitchen 362
- E.E. SPECIAL REPORT** The Casio fx-7100 scientific calculator 365

**FREE WITH THIS ISSUE** E.E. CONSTRUCTORS RULE (Mounted on front cover)

### Back Issues

Certain back issues\* of EVERYDAY ELECTRONICS are available worldwide price 70p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

\* Not available: October 1978 to May 1979.

### Binders

Binders to hold one volume (12 issues) are available from the above address for £4.10 (home and overseas) inclusive of postage and packing. Please state which Volume.

### Subscriptions

Annual subscription for delivery direct to any address in the UK: £9.00, overseas: £10.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613 Kings Reach Tower, Stamford Street, London SE1 9LS.

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproductions or imitations in whole or in part are expressly forbidden.



# PRETUNED



# 4-STATION RADIO

THIS receiver allows switch-selection of Radio 1, 2, 3 or 4, without any need for tuning adjustments when in use. For a good performance without too much circuit complication, two i.c.s and a transistor are employed.

With the aerial and trimmer values shown, approximate possible coverage at each switch position is: 1 and 3, 1800-850kHz; 2 500-950kHz; and 4 150-230kHz (longwave). This includes the alternative programme frequencies where applicable.

Note that in the London area, Radio 4 is best received using the 720kHz frequency (medium wave), switch position 2. Other frequencies include the following: Radio 1, 1053kHz, 1089kHz; Radio 2, 693kHz, 909kHz; Radio 3, 1215kHz; Radio 4, 720kHz, 200kHz; Radio Wales 882kHz; LBC, 1152kHz; Radio London 1458kHz; Luxembourg 1439kHz; Capital 1548kHz.

## DETECTOR SECTION

The circuit diagram is shown in Fig. 1. The 2-pole 4-way switch S1a allows the choice of four pre-set frequencies. With S1 at 1 trimmer C1 is in circuit, while position 2 introduces C2 instead, and 3 connects C3. Positions 1, 2 and 3 of S1b short the longwave aerial winding L2, for medium wave reception by L1. Position 4 gives longwave reception, with trimmer C4.

To avoid the additional tuning and extra components of the superhet, the ZN414 10-transistor t.r.f. integrated circuit IC1 is used. The r.f. resulting from the resonant tuned circuit composed of C1, 2, 3 or 4 with L1 and L2 is fed to the input (pin 2) of IC1 which provides audio frequency output at pin 1, so that it is only necessary to follow this with an audio amplification stage.

The ZN414 i.c. requires a supply of about 1.3 volts and small changes in voltage have a significant effect on its

### Frequency Coverage

1	— Range	850 - 1800kHz
2	— Range	500 - 950kHz
3	— Range	850 - 1800kHz
4	— Range	150 - 230kHz

performance. Insufficient voltage reduces sensitivity, while excessive voltage tends to cause instability.

The positive supply is at pin 1, via R3, and obtained from a potential divider formed by R2 to the battery negative line, and VR1 with R5 to the positive line. VR1 allows adjustment to cover component tolerances, to avoid any difficulty in this direction.

Audio output is via R4 and C9 to the volume control VR2.

## AUDIO SECTION


The amplification section consists of TR1 and IC2, the latter requiring very few external components.

Transistor TR1 is connected as a common emitter amplifier with feedback biasing via R6. This acts as a pre-amplifier for IC2 giving additional boost to the output of IC1.

IC2 has a gain of 50, set internally and an output power rating of over 1 watt into a 4 ohm loudspeaker. In this design an 8 ohm loudspeaker is used to reduce the peak current drawn and conserve battery. This still provides adequate power output for normal listening.

In areas of strong signal TR1 could be omitted. Anyone wishing to reduce the number of components and experiment with this can omit R4, R6, R7, R8, TR1, C10, C11 and C12, taking pin 2 of IC2 to the wiper tag of VR2.


## HOW IT WORKS

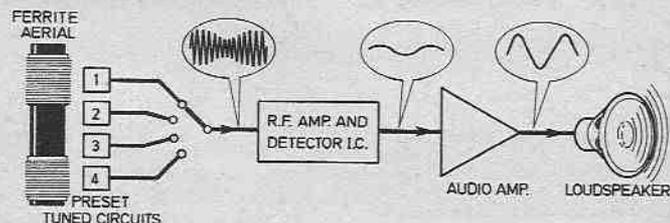

Radio frequency signals from the transmitter induce voltages in the coils on the ferrite rod aerial. Four r.f. tuned circuits are formed with the aerial which can each be inputted to the r.f. amplifier/detector i.c. The output from this is the required audio signal which receives boost from the audio amplifier to be heard in the loudspeaker.



# PRETUNED 4-STATION RADIO

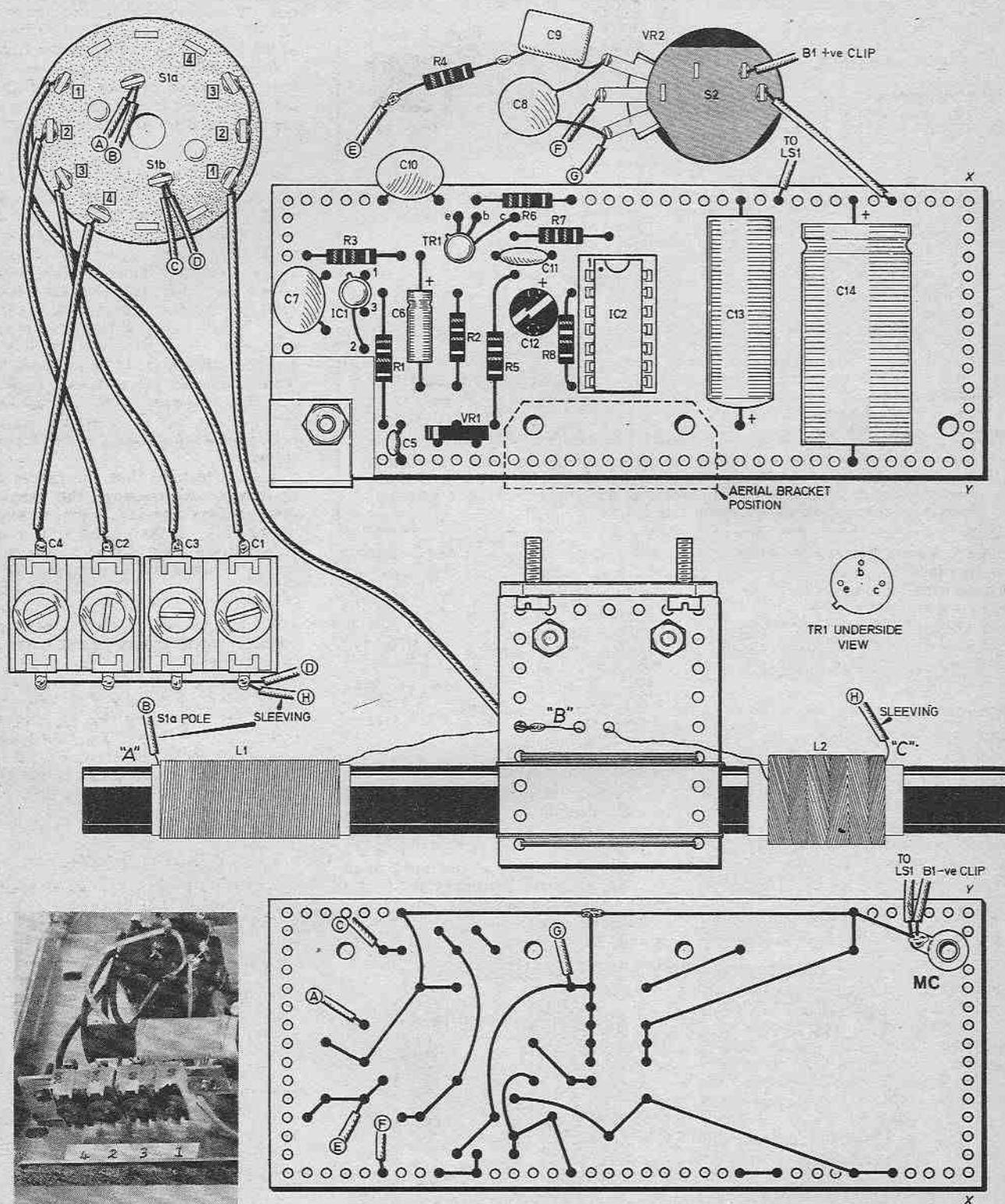

A close-up view of the trimmer capacitor bank showing fixing brackets used in the prototype.

Fig. 2. Full construction details showing the board and components in their relative positions in the case. The L-shaped aerial bracket is bolted to the circuit board. The trimmer capacitor brackets will need to be constructed to suit the trimmers obtained. One bracket is fitted by one of the board fixing bolts with the other on the chassis. However, this may need alteration.

# COMPONENTS

## Resistors

R1 100k $\Omega$	R5 3.3k $\Omega$
R2 680 $\Omega$	R6 820k $\Omega$
R3 470 $\Omega$	R7 10k $\Omega$
R4 4.7k $\Omega$	R8 33k $\Omega$

All  $\frac{1}{2}$ W carbon  $\pm 5\%$

## Potentiometers

VR1 1k $\Omega$  vertical miniature pre-set  
 VR2/S2 10k $\Omega$  log. pot with ganged switch

## Capacitors

C1 60pF	} Compression trimmers (type VC 29LC 60pF or VC29L 180pF suitable —Home Radio)	C8 10nF ceramic
C2 200pF		C9 0.1 $\mu$ F ceramic or polyester
C3 60pF		C10 0.47 $\mu$ F ceramic or polyester
C4 200pF		C11 10nF ceramic
C5 10nF ceramic	C12 4.7 $\mu$ F 10V elect.	
C6 4.7 $\mu$ F 10V elect.	C13 470 $\mu$ F 10V elect.	
C7 0.1 $\mu$ F ceramic	C14 1000 $\mu$ F 10V elect.	

## Semiconductors

TR1 2N706 npn silicon  
 IC1 ZN414 t.r.f. radio i.c.  
 IC2 LM380 audio amplifier i.c.

## Miscellaneous

S1 2-pole 4-way rotary switch  
 LS1 8 ohm moving coil loudspeaker  
 L1/L2 ferrite rod aerial type MW/LW FR5 (Denco)  
 0.1 inch perforated s.r.b.p. size 37  $\times$  15 holes; s.r.b.p. board size 30  $\times$  40mm (for aerial mount); 14 pin d.i.l. socket; control knobs (2 off); PP9 battery clips; materials for case; aluminium for brackets; 6BA nuts, bolts and washers; "universal chassis" flanged member size 7  $\times$  4 inch (2 off).

COMPONENTS  
 approximate  
 cost **£8.50**  
 excluding case

mounted. Fixing the switch holds the stop in place.

Those with an experimental inclination can use the two spare ways of a 6-way switch for l.w. and m.w. manual tuning, with a 200pF variable capacitor.

## FERRITE AERIAL

Bolt a strip of perforated board 30  $\times$  40mm (approx) to the central bracket. Secure the rod to this, as shown in Fig. 2, with adhesive and cotton passed through holes in the board. L1 (medium wave) and L2 (long wave) windings are then slid on. The small coupling winding provided on L1 is not needed, so this should be removed.

The beginning of L1 is denoted by A. Put sleeving on this lead and solder


it to S1a. The end of L1 and beginning of L2 is denoted by B, and these are joined at the strip supporting the rod, and a lead run from this point to S1b.

The end of L2, C, runs to one side of all trimmers and then S1b. The windings of L1 and L2 must be in the same direction. This can be seen. Alternatively, if tuning of 200kHz is impossible, take L2 off the rod, reverse it and replace it.
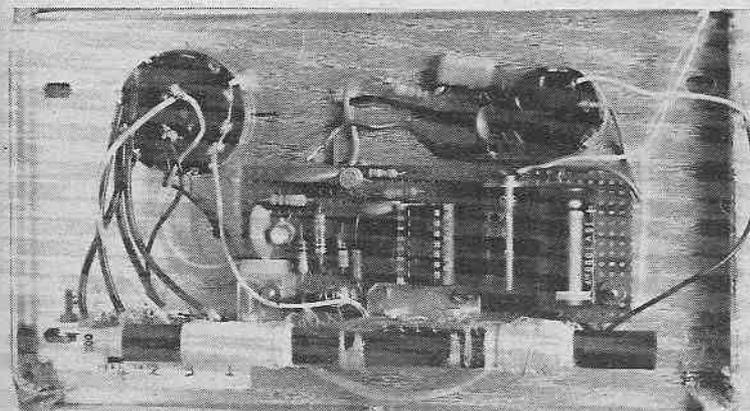
## TRIMMER BANK

The four trimmers are supported by a strip spanning two brackets, see photo. Stick a strip of paper marked 1, 3, 2, 4 close to the trimmers on the chassis to identify adjustment from behind. Wire the trimmers to S1, connect LS1 and a battery.

Initially position L1 and L2 each about 20mm from the ends of the



The fully wired chassis assembly with aerial secured to board.

rod, and check that with S1 in position 1, Radio 1 can be received with adjustment of C1. Similarly, that positions 2, 3 and 4 allow Radio 2, Radio 3 and Radio 4 to be tuned by C2, C3 and C4 respectively. If not, move L1 slightly, or L2 for Radio 4. When in order, cement L1 and L2 to the rod.

Other radio stations may be pre-tuned in place of any of the above mentioned; see frequencies and recommended position discussed earlier.

## CASE

The case can be made with negligible cost and difficulty, but with good appearance. In the prototype, another 7  $\times$  4in "universal chassis" flanged member formed the bottom panel. Each side is wood, cut 115mm high by 130mm. Four 6BA countersunk bolts fit each side to the chassis members. The bottom is flush, but the top panel is set down 5mm or so. The front is another piece of 4mm plywood size 178  $\times$  115mm, with an aperture cut for the speaker, which is held with countersunk bolts, or self-tapping screws.

After checking that the pieces will fit, temporarily remove the sides. A piece of fabric about 215mm wide and 305mm long is then fixed with a suitable quick-drying adhesive along the front of the bottom member. When this is dry, stretch the fabric upwards over the front, across the top panel, and cement it at the back edge of this panel. It is necessary to cut holes for the controls.

When the adhesive is dry, apply more adhesive to the end flanges at one side, and along the edge of the front. Pull the fabric taut, fold it over, and screw on the side. Repeat for the other side. The back panel is the same size as the front panel and held with self-tapping screws.

## FINAL ADJUSTMENTS

Glue on a fascia and label as seen in the photographs. Carefully check the four trimmers. Also set VR1 so that about 1.2V to 1.3V is present across C6 (using a high resistance voltmeter) or so that sensitivity is good without instability.

For best reception in some areas it will be found necessary to rotate the receiver, for best volume of the wanted transmission, and minimum pick-up of other signals.

In many areas VR2 should not need to be advanced very far and the receiver will in general be operated at considerably lower volume than the maximum which could be obtained.

Final adjustment to the trimmers, for the transmissions which are required in any particular region, are preferably made with a completely insulated tool, with all the assembly completed.  $\square$

# LIGHTS WARNING SYSTEM

K. CUMMINS

ALL drivers must at some time have left their lights on when parking. This is particularly likely to happen when driving in daytime with lights on, during rain or foggy conditions, and also when setting off in darkness and arriving at one's destination in daylight.

The circuit to be described will alert one to this condition. It has the advantage that no setting or cancelling switches are required; in some cases, no additional warning light may be needed. Instead, an existing panel lamp may be used.

The indicator lamp (which may be replaced by a buzzer if required)

flashes when the engine is switched off with the lights left on. Turning the lights off cancels the alarm. If required, the lights can then be turned on again without any alarm indication. This allows for parking with lights in awkward or hazardous circumstances. If the alarm is activated and the engine re-started, the alarm is cancelled.

## CIRCUIT DESCRIPTION


The circuit diagram is shown in Fig. 1. The circuit has three basic inputs, +12V, IGNITION and LIGHTS.


The 12 volt supply (car battery) is connected at all times. The current drain of the circuit is negligible and the car could be left for weeks without the battery becoming flattened. A car clock consumes far more.

The +12V supply is filtered by R1 and C3 which removes any noise on the line. The filtered supply is taken to R5, R7 and pin 14 of IC1, a quad dual-input NOR gate.

The ignition line is also filtered, this time by R2 and C1. When the ignition is turned on, TR1 is turned on via the flow of current through its base network R3 and R4. The collector of TR1 is therefore pulled low, taking the input to pin 6 with it.

Fig. 1. The complete circuit diagram of the Lights Warning System. LP1 is a 12V bulb up to 2 watts and is only required if no in-built panel light is available.

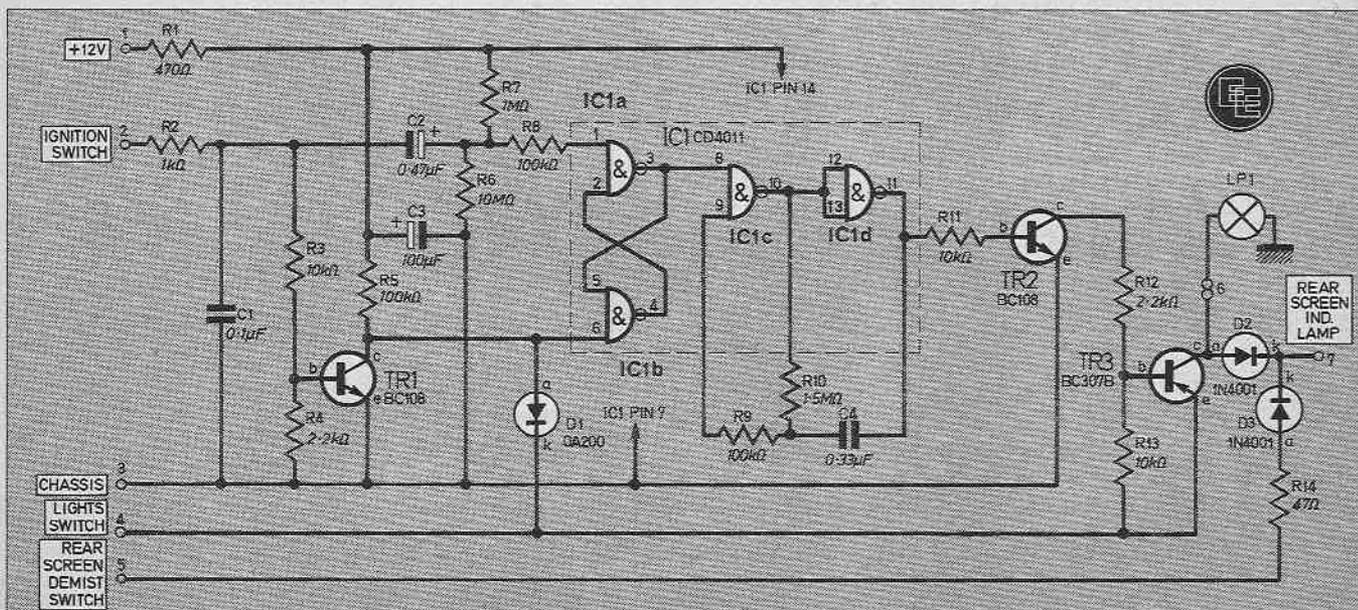

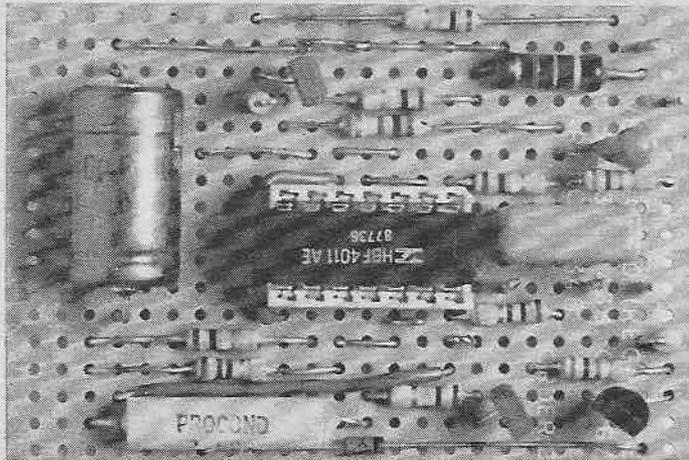

The prototype component board. This differs from that shown below where D2, D3 and R14 have been incorporated on the board.

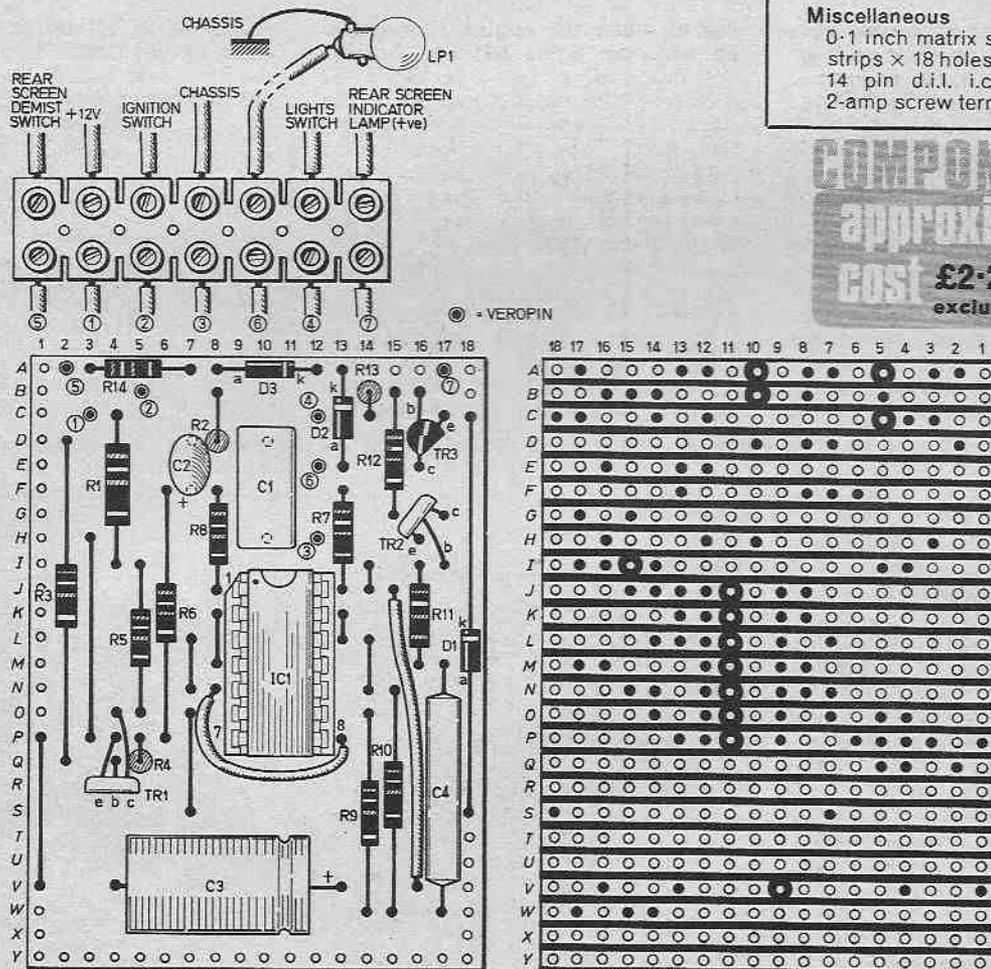


Fig. 2. The layout of the components on the topside of the board and the breaks to be made in the copper strips. Numbered leads from the terminal block refer to Veropins on board. Only one indicator lamp should be used, either LP1 or existing panel lamp for some other function (e.g. rear screen demister indicator).

## COMPONENTS

### Resistors

R1	470Ω ½W	R8	100kΩ
R2	1kΩ	R9	100kΩ
R3	10kΩ	R10	1.5MΩ
R4	2.2kΩ	R11	10kΩ
R5	100kΩ	R12	2.2kΩ
R6	10MΩ	R13	10kΩ
R7	1MΩ	R14	47Ω ½W

All ½W carbon ± 5% unless stated otherwise

### Capacitors

C1	0.1μF polyester
C2	0.47μF 16V tantalum
C3	100μF 16V elect.
C4	0.33μF polyester

### Semiconductors

D1	OA200 or similar silicon diode
D2, 3	1N4001 or similar 1A rectifier (2 off)
TR1, 2	BC108 npn silicon (2 off)
TR3	BC307B pnp silicon
IC1	CD4011 CMOS Quad 2-input NAND gates


### Miscellaneous

0.1 inch matrix stripboard size 25 strips × 18 holes; Veropins (7 off); 14 pin d.i.l. i.c. socket; 7-way 2-amp screw terminal block; case.

See  
**Shop Talk**  
page 323

COMPONENTS  
approximate  
cost **£2.20**  
excluding case

## HOW IT WORKS

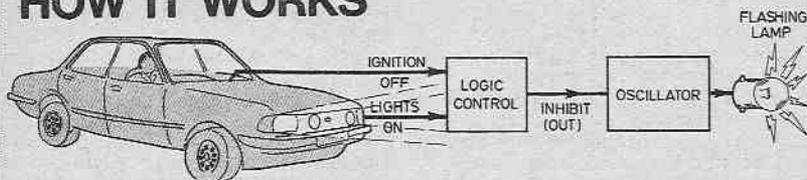

The logic control circuitry normally provides an output to inhibit the operation of the oscillator (it does not oscillate). However, when a condition arises where the lights are on and the ignition is turned off, the logic output changes and allows the oscillator to operate. This activates a warning lamp (or buzzer) inside the car to flash (or sound). The logic circuitry has a built-in parking facility which is enabled by turning the lights off and then on after the alarm has sounded.

A bistable latch is formed with IC1a and IC1b which can be set and reset by placing a low on pins 1 and 6 respectively. Once the latch is set or reset it remains in that condition indefinitely until the corresponding input is taken low to change it.

Pin 1 is normally held slightly below positive rail voltage (logic 1) by the network R6 to R8. We shall now assume that the car is being driven with the lights on. The IGNITION and LIGHTS lines are both high (logic 1) and TR1 collector is low. The output from pin 3 is low.

### OPERATION STAGES

The driver arrives at his destination and turns off the ignition. The ignition line goes low, and TR1 turns off; pin 6 goes high. The low excursion of the ignition line takes pin 1 low, via C3. Capacitor C3 then charges via R7 so that pin 1 is high again. The low on pin 1 has, however, set the latch, so that the output from pin 3 is high. This output is taken to pin 8 where it enables the relaxation oscillator consisting of IC1c and IC1d to operate.

The output from pin 11 pulses alternately high and low, at a rate determined by the time constant ( $C4 \times R10$ ). In this case a rate of approximately 1Hz is obtained.

The output from pin 11 is taken via R11 to TR2, and turns TR2 on and off. Likewise, the output from TR2 turns TR3 on and off, via the network R12 and R13. Transistor TR3 is a *pnp* transistor fed from the LIGHTS rail. Its output is taken to a suitable indicator lamp LP1, for example 12V 100mA.

In the author's prototype, the lamp used was the fitted rear screen demister indicator. This is fed via D2, R14 and D3, so that the light is on dimly when the demister is in use, but when the alarm turns on, the lamp flashes brightly.

### PARKING FACILITY

It will be noticed that D1 is also connected to the LIGHTS line. When

the driver turns the lights off, the cathode of D1 goes low, and the input to pin 6 is pulled low. This resets the latch, and cancels the alarm. The lights can then be turned on again, but since the latch has been reset, the alarm condition is no longer given. The output at pin 3 will now be low, and so will pin 11. Thus TR2 and TR3 are turned off.

If the driver, instead of switching his lights off, starts his engine after an alarm has been given, TR1 turns on again and pulls pin 6 low, so resetting the latch and cancelling the alarm.

It will be observed that pin 6 is permanently low while driving. This ensures that no transient pulses from the car can set the latch and give a spurious alarm. This could be a most disturbing situation in the middle of a motorway, for example.

This system has been in use from the winter of 1977 onwards without malfunction and has proved very useful.

Those readers wishing to use a separate alarm lamp or buzzer may dispense with D2, D3 and R14. The lamp is then connected between chassis and the collector of TR3.



### CIRCUIT BOARD

All the components (except the indicator lamp or buzzer) are mounted on a small piece of 0.1 inch matrix stripboard size 25 strips by 18 holes. The component layout on the topside of the board and the breaks to be made on the underside are shown in Fig. 2. This differs slightly from the author's prototype as shown in the

photograph where D2, D3 and R14 were mounted around the alarm lamp.

The prototype was wrapped in foam sponge and this held the board in position in the case. If a bolt fixing is preferred, the board should be extended to accommodate the fixing holes. The screw-terminal block can be fitted to the outside of the case which should be equipped with lugs.

### ASSEMBLY

Begin by making the breaks on the underside and fitting the Veropins and i.c. socket. Continue with the link wires, resistors, capacitors and semiconductors in this order. Solder sufficient lengths of flying leads and secure these to the terminal block. Finally insert IC1 and the unit is ready for assembly in its case and installation in the vehicle.

Note that if a buzzer is used in place of a lamp, a diode, must be connected across its coil to prevent the back e.m.f. generated when activated, from damaging TR3. The cathode of the diode should connect to TR3 collector with its anode connected to chassis, i.e. the diode is normally reversed biased.

### INSTALLATION

It is recommended that the unit be installed inside the car in an area not prone to excessive temperature changes (e.g. heater flow duct) or moisture build-up. The glove compartment is a likely position.

All the connections from the terminal block should be made with flexible (multistrand) wiring to reduce possibility of vibration fractures. Connection to the required points in the electrical system are best made with push-fit spade connectors or the "piggy-back" type. Self-adhesive foam pads are suitable for fixing the case to a horizontal surface and do provide some form of shock absorption.



"I was going to construct a Time Machine, but there's no future in it."



**By Dave Barrington**

**For The Workbench**

We would think that with the "shrinkage" in size of most electronic components over the years, a light duty vice is now considered a must for most workshops. Two such products worthy of consideration for addition to the workshop are the OK VV-1 vice and the Absonglen Mini-bench.


Both professional and amateur will find OK's new VV-1 light duty vice ideal for handling small components and assemblies.

The 33mm jaws are adjusted by a knob which takes the place of the usual "tommy" bar. Normally the vice would be fixed to worksurfaces by a lever operated suction mechanism but where permanent installation is required it can be screwed down.

The VV-1 vice is available from OK Machine & Tool (UK) Ltd., Dept EE, Dutton Lane, Eastleigh, Hants., SO5 4AA, price £3.58 inclusive of packaging.

Although we have not had the pleasure of trying the Minibench we like the idea of gripping small boards in its jaws and being able to "flip" the workpiece over for component mounting and soldering. Another good feature is the facility for flexible arms terminating in crocodile clips to hold components and possibly to act as heat sinks.

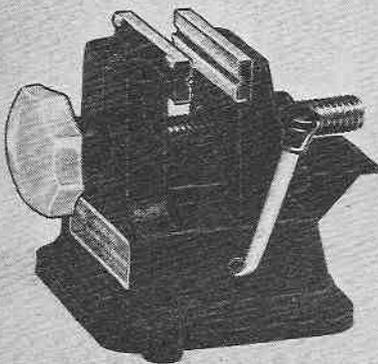Further information can be obtained from Absonglen Ltd., Dept EE, The Forge, Staplow Cottage, Staplow, Ledbury, Herefordshire, HR8 1NP.



VV-1 vice from OK Machine & Tool

**Magnetised**

An item which you would not normally associate with the amateur workshop, but once used soon becomes an invaluable "tool" is the magnetiser/demagnetiser.


Ideal for demagnetising those screwdrivers and drills which have a habit of becoming magnetised, without reason and picking up any metal debris, including nuts and bolts, often found on the workbench and depositing them in the workpiece before you can take any action. Then there's the opposite case where you wish you had a magnet to reclaim an item which had accidentally dropped into the "works" and caused untold time wasting and curses trying to devise other methods of retrieval.

A suitable magnetiser/demagnetiser, at a fairly low budget price of £9.95, is available from Magnadyne Products and may prove to be a worthwhile investment for those "butterfinger" types like myself.

Claimed to be capable of producing a bar magnet up to 9mm diameter and any length, the magnetiser/demagnetiser is available from Magnadyne Products, Dept EE, 6 Lulworth Road, Welling, Kent, DA16 3LQ.



Magnadyne magnetiser/demagnetiser

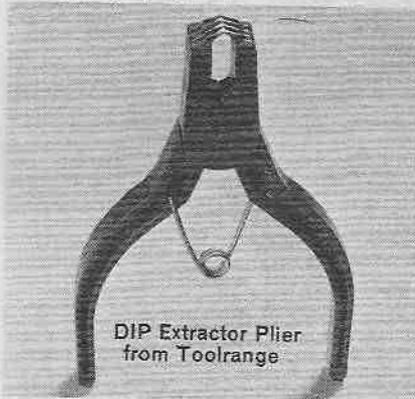

DIP Extractor Plier from Toolrange

**Extractor Plier**

Another unusual item, available from Toolrange, which may appeal to the constructor who has tried to remove i.c.s from circuit boards is the DIP Extractor Plier, price £6.50 plus VAT.

It is claimed that this new hand tool will remove 8 to 40 pin dual-in-line devices from sockets and desoldered circuit boards in seconds. The teeth of the pliers grip devices as close as 0.25in in densely packed boards. The pliers are insulated for live board work and the metal teeth also act as a heat sink and shorting bar.

**PLEASE NOTE**

All prices quoted in this issue are **Pre-Budget**

**Soldering Irons**

A new range of soldering irons from S & R Brewster Ltd., may be worth further investigation.

These irons are the Ceco Vari-Stat range, for which they have acquired the manufacturing and sales rights, used extensively by the trade.

Amongst the range is the S.R.B. "Mighty Midget" which is an excellent 18 watt iron with interchangeable bits suited for our type of work. The more robust of their range, primarily designed for industrial use, are temperature controlled and rated from 50W to 500W. For more details readers should contact S & R Brewster Ltd, Dept EE, 86-88 Union Street, Plymouth, PL1 3HG.

Another company we must not overlook when we are talking about soldering iron requirements is Light Soldering Developments Ltd.

They cover such an extensive range that you can practically hand pick one to meet your own personal needs, including a "carry-it-anywhere" cordless type with built-in recharger.

For more details and leaflets readers should write to Light Soldering Developments Ltd., Dept EE, 97/99 Gloucester Road, Croydon, CRO 2DN.

**CONSTRUCTIONAL PROJECTS**

Availability of components for this month's constructional articles should not cause too much difficulty and should only be a matter of looking through advertisers catalogues.

**Dual Line Game**

In view of the large quantities of transistors and diodes called for in the *Dual Line Game* it would seem to be a good idea to approach advertisers regarding a special "bulk purchase" price for these items. A discount price may also be available for the 3-5mm jack plugs and sockets. The rest of the components for this project should be readily available items.

Most advertisers will probably supply the BC108 in the metal TO-18 can. This also applies to the Lights Warning.

**Battery Voltage Monitor**

The multiturn preset potentiometer VR1 listed in the *Battery Voltage Monitor* project is available from Watford Electronics and Maplin Electronic Supplies. However, there is no reason why a standard miniature preset potentiometer should not be used with a slight loss in fine adjustment.

**Lights Warning System**

The CD4011 used in the *Lights Warning System* is a standard CMOS i.c. and is usually generally available from most advertisers. Transistor type BC307B is listed by Watford Electronics. The suffix B denotes the gain of the device.

**Pretuned 4-Station Radio**

The ferrite coil needed in the *Pretuned 4-Station Radio* is the Denco type MW/LWFR5 and is stocked by Watford, Maplin and Ambit International. Suitable trimmer capacitors for C1 to C4 are available from Home Radio as types VC29LC and VC29L.

We cannot foresee any buying problems for the *Uniboard—Audio Tone Generator* and the *Auto Fade* projects.

# Part 8

By S. R. Lewis,  
B.Sc.



# TEACH-IN 80

**F**OLLOWING last month's description of the basic principles of transistors, we will now go on to look at one of the most important uses of transistors—as simple **two-state devices**, with a clearly defined ON state and OFF state.

In isolation such circuits can be used to drive simple devices such as indicator lamps or relays but together with other similar circuits they can form part of a logic circuit such as may be found in a digital computer.

## ANALOGUE AND DIGITAL

Over the past twenty years or so electronics has divided into two main fields: **analogue** and **digital**. They have almost become two separate disciplines since the techniques used in each appear to be completely different.

Analogue electronics is concerned with the generation and manipulation of continuously changing signals. The term "analogue" is used since the electrical signals are often an analogue of some physical quantity. For instance, an amplifier has voltages inside it which are analogies of the sounds which we want to hear—voltage is used to represent air pressure.

In digital circuits only two states are normally to be found for any particular section. These two

states are used to represent the two logical alternatives **true** and **false**. By coding information in terms of complicated patterns of true and false, complex and manipulations can be carried out on the data at incredible speeds.

Analogue electronics is the older field, probably since continuously variable signals occur more often in nature than discrete signals. A wave in water or sound travelling through the air can be simulated using electronic voltage to represent height of the wave or sound pressure. Fig. 8.1 shows an analogue and a digital signal compared.

Fig. 8.1. The analogue signal shown at (a) varies continuously between its limits whilst the digital signal at (b) only takes two distinct values, the change from one to the other being very rapid.


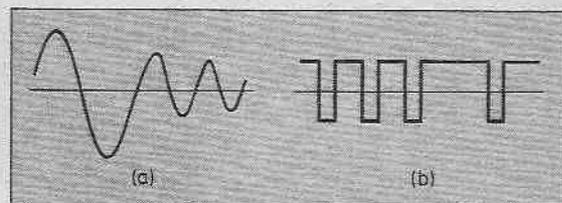


Fig. 8.2. A switch which is part of a system must be able to switch other similar circuits and must be capable of being switched by a circuit similar to itself.

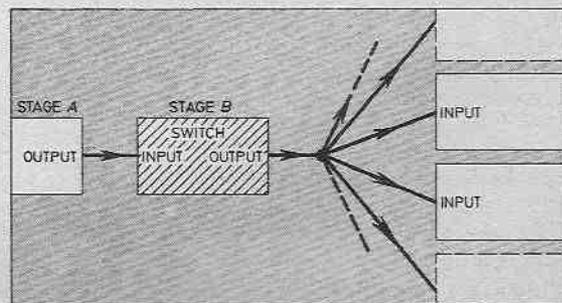

Digital circuitry implies a more abstract conception of real situations but the power of this approach can be judged by the proliferation of digital machines in more and more aspects of modern life.

The purpose of this month's part is not to look at "logic" in the abstract but to look at how transistors can be used as two-state devices and how they can be combined to do useful tasks.

## THE TWO STATES

The basis of the digital approach is that the transistor is used simply as an on/off switch, the two states representing "true" and "false."

It does not matter which state we use to represent true provided all the circuits are designed with the same convention. Also it does not matter what the absolute voltages are which are used to indicate true and false; provided there is no possible way in which they can be confused we are quite safe.

The two states which we are trying to achieve must therefore be stable, repeatable and independent of variations in the transistors themselves.

Of course, there must be a time when the transistor is in neither the ON state or the OFF state, that is when it is changing from one state to the other, but we must make sure that the time the transistor spends in this intermediate state is as small as possible and that it cannot get stuck in this undesirable position.

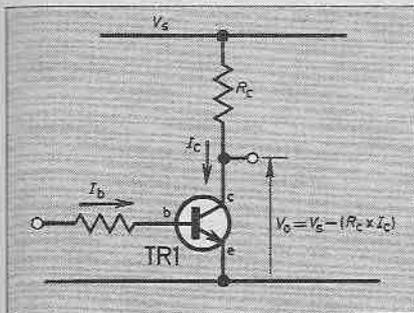


Fig. 8.3. A simple transistor switch using the common emitter configuration. The base current must be greater than that just needed to saturate the transistor.

Let us look at how the circuitry around a transistor can be designed so as to achieve the conditions we require.

If the switch that we are designing is to be used along with other similar switches in a system, then it must both be capable of being switched by another stage and of switching other similar stages.

Fig. 8.2 shows how the switch might fit into a system. Note that we do not allow outputs of different switches to be connected together as we could get into a situation where one switch is trying to switch on and the other off—which one wins will be a matter dependent on the circuitry rather than the inputs to the two switches.

However more than one input can be connected together since a switch will often be required to drive many other switches.

### THE OFF STATE

If we define the transistor as being off when no current flows in its collector then we can achieve this quite simply with a common emitter circuit by either leaving the base open circuit or by making sure that the voltage on the base is not high enough to forward bias the base-emitter junction.

Now, since we have said that the switch must be able to be driven by another similar switch, the option of open-circuiting the base is not possible. We must therefore make sure that the voltage on the output of our switch is well below the voltage needed to forward bias base-emitter, that is about 0.7V for a silicon transistor.

As we saw last month, the current through the collector will never be exactly zero as some

leakage current will flow even when the base is not forward biased. However, this current is so small that it can be ignored in this context.

When the transistor is in this state we say that it is "cut-off".

### THE ON STATE

Looking at the circuit of Fig. 8.3, if the base current is gradually increased from zero the current in the collector resistor  $R_c$  will gradually increase and the voltage at the collector will fall steadily because of the increasing voltage across the resistor.

Now the voltage at the collector cannot fall to zero but reaches a minimum of about 0.2V for a silicon transistor. In order that this voltage is reached no matter what the gain of the transistor, we can use a safety factor of ten by making the base current ten times that which is needed to just saturate the transistor, assuming minimum gain.

For a BC108 the minimum gain is 110 so providing the base resistor is ten times the value of the collector resistor we can be certain that even at worst case the output voltage will be around 0.2V when the input is taken to the positive supply.

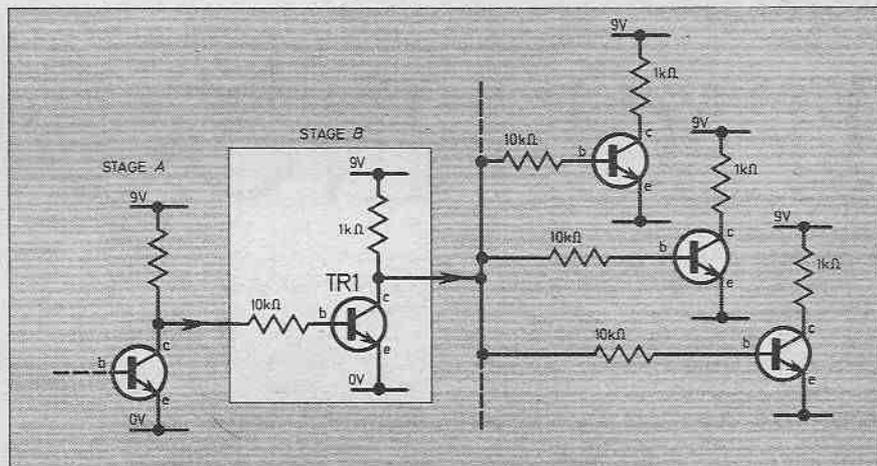


Fig. 8.4. The transistor switch (Fig. 8.3) as it looks when in a system. Note that only one output feeds it whilst it feeds many inputs.

Increasing the base current still further produces a lower voltage at the collector until a point is reached when increasing the base current any further produces virtually no change in the collector voltage.

What has happened is that the base current has produced a current in the collector which produces a voltage across the collector resistor which is almost equal to the supply voltage. Obviously this resistor cannot drop more than the supply voltage so the extra base current has very little effect.

We call this state **saturation** for obvious reasons. To define saturation more rigorously we say that saturation will be reached when the base current exceeds the maximum collector current (the power supply voltage divided by the collector resistor) divided by the  $h_{FE}$  of the transistor.

$$\text{Saturation: } I_b > \frac{V_s}{R_c} + h_{FE}$$

### RESISTOR VALUES

To put in some resistor values then let us use a 1 kilohm collector resistor and a 10 kilohm base resistor. Does the circuit thus produced fulfil our needs? To find this out we have to slot the circuit we have produced back into our original system of Fig. 8.2 (see Fig. 8.4).

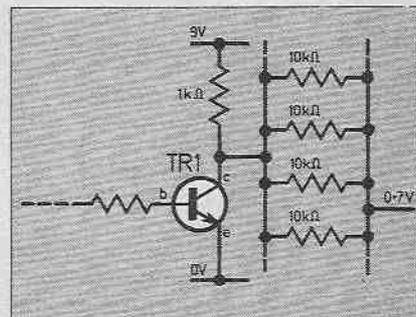


Fig. 8.5. The loading on the switch in Fig. 8.4 can be redrawn thus. The load appears as a number of 10kΩ resistors in parallel all to 0.7V.

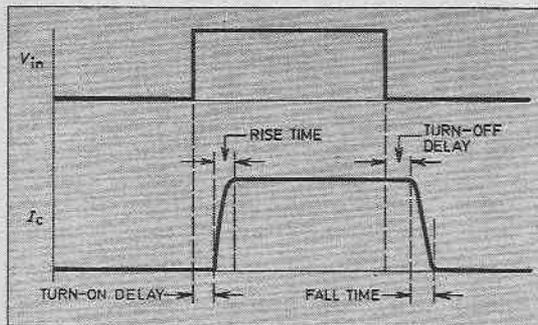


Fig. 8.6. When a pulse is applied to the input of our switch the output does not change instantly but with the delays as shown here.

Assume the first stage (A) is on so that the output voltage is 0.2V. The base emitter junction of the second stage (B) cannot be forward biased as the voltage to do this is 0.7V. Thus stage B will be off (no current in its collector resistor). Now the collector resistor of stage B has to supply the base current to all the other stages to which it is connected.

Each stage has a 10 kilohm input resistor, all of which have 0.7V on their lower ends if their respective transistors are conducting. We can thus draw the loading on stage B output as in Fig. 8.5.

Note that if ten stages are connected to output B then the voltage drop across its collector resistor will be 4.15 volts and the current through each of the base resistors will be only half of that stipulated in the first design.

If we now say that this current is our absolute minimum then we are merely stating that one of these circuits can drive no more than ten similar circuits.

This figure is called the **fan-out** of the circuit since it defines how many other circuits we can fan out our output to.

Apart from this restriction our circuit seems to meet the criteria of two distinct states, independent of the transistor variations. But how long does it take to switch from one state to the other?

## SWITCHING SPEED

To predict how long a switching circuit takes to go from one state to the other requires a much deeper investigation of the workings of a transistor that it is possible to present in this series.

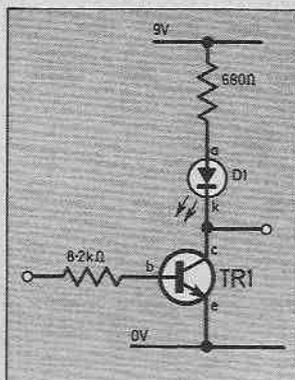


Fig. 8.7. If it is desired to drive a light emitting diode from one of our switches then the circuit shown can be used.

However, we can look at the actual behaviour of the circuit and make some remarks about the speed of switching circuits in general.

Assuming we are driving the switch with a voltage that changes from high to low and back again in zero time, what will the output of the circuit under consideration look like? Fig. 8.6 shows the input and output waveforms that we are likely to see.

We see that the output does not follow the input immediately but both at "switch on" and "switch off" it goes through two stages.

There is a delay when nothing appears to be happening followed by a gradual change from one state to the other. The delay before the transistor switches on is due to the time taken for the base voltage to build up to a value sufficient to forward bias the base-emitter junction. After this the collector current increases steadily to its final value. We call these two times the **turn-on delay** and the **rise time**.

Now, we are putting much more base current into the transistor than is needed to produce the collector current that we have. When the input voltage is taken to zero this extra current is "remembered" in the form of a charge within the transistor which tends to keep the transistor on for a short time. This is called the **turn-off delay**. After this the collector current falls steadily to the off state. This is called the "fall time".

You may have got the impression that we have a very slow circuit but it must be realised that the times we are talking about are measured in millionths of a second

(microseconds or  $\mu s$ ) or less so that even this very crude switch is extremely fast by everyday standards.

## HIGH CURRENT LOADS

Quite often the requirement will arise to be able to drive some sort of output device such as a lamp or a relay using a simple switch such as the one we have described. We used light emitting diodes in an earlier section of this series to indicate the flow or absence of current, so how would one of these be driven by a transistor?

First ascertain the current needed through the load; for an l.e.d. this would be about 10mA. Now the l.e.d. will drop about 1.6V when it is conducting. The transistor if fully on will drop about 0.2V so that we must use a series resistor to drop the remaining voltage which will be the power supply minus (1.6+0.2)V. For a 9V supply the resistor must drop 7.2V at 10mA. This works out as 720 ohms, the nearest preferred value being 680 ohms.

Assuming the transistor has a minimum gain of 100 then a base current of 0.1mA will just saturate the transistor. Allow a safety factor of ten, giving a required base current of 1mA. If we are driving this switch from a similar one then we must be rather careful in selecting our base resistor since our base current has to flow through the l.e.d. of the previous stage.

A base resistor of 8.3 kilohm is needed if connected to the power supply, so dropping this to 6.8 kilohm should give some allowance for the voltage drop across the l.e.d. and its resistor.

But note: if we try to feed two similar stages then the current through the output l.e.d. will be 1.5mA, enough to illuminate it! Therefore this circuit has a much lower fan-out than the transistor switch described previously. In fact it has a fan-out of only 1. Fig. 8.7 shows the circuit.

## A TWO-STAGE CIRCUIT

As an alternative to a l.e.d. we might want to drive a relay which needs say 100mA. Our first problem is that 100mA is the maximum current for a BC108 transistor so right away we must look for a transistor with a greater current capability than this.

The next problem is that using our "ten times" criterion means that we need 10mA to switch on the driving transistor and if we want to drive it from the output of one of our simple transistor switches, this value of current is just not available.

The answer to the problem is that we will have to use a two-stage circuit of some kind: the first one to "buffer" the output of the driving switch from the high current demand of the relay driver.

A simple circuit is shown in Fig. 8.8. The first transistor (TR1) needs only 1mA to switch it on. When it is on there is only 0.2V on the base of the driver (TR2) so the latter is off. When the first transistor is off then 10mA base current flows into the driver through the collector resistor of the first transistor which now be-

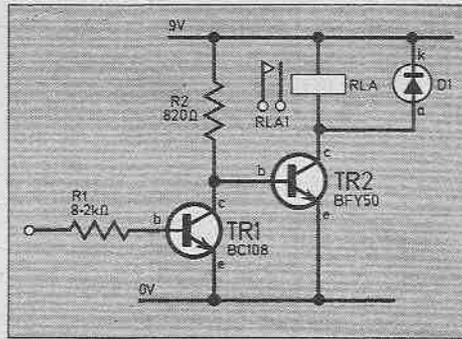


Fig. 8.8. A relay with its higher current requirement and back e.m.f., requires a slightly more complicated circuit. This circuit also produces an inversion of the logic input.

comes the base resistor of the second.

### DIODE PROTECTION

Note the diode across the coil of the relay. This is to protect the transistor from the large back e.m.f. which is produced when the

transistor switches off.

The current which flows when the transistor is on cannot disappear instantaneously as the inductance of the relay coil acts as a store of current. If the diode is not there the voltage at the collector would rise to many tens of volts and could destroy the transistor.

The diode clamps the voltage at the collector to the supply voltage plus one diode forward voltage drop (0.7V). This does mean that the energy in the relay takes longer to be dissipated but we are not interested in this time for our particular application.

One further point to note about this circuit is that it inverts the sense of the input. When the input is high (near the positive supply) the relay is off and when the input is low (near the 0V supply) the relay is on.

### EXPERIMENT 8.1: LED DRIVER

**Components needed:** 680Ω 1/4W resistor (2 off), 10kΩ 1/4W resistor (2 off), BC108 transistor (2 off).

In this simple experiment we use a switch to provide the input signals for a light emitting diode driver which then drives another similar stage. The circuit is shown in Fig. 8.11a and the layout on the Tutor Deck in Fig. 8.11b.

With the switch in one position, i.e. D1 is on and i.e.d. D2 is off. The situation is reversed when the position of the switch is changed, showing the inverting action.

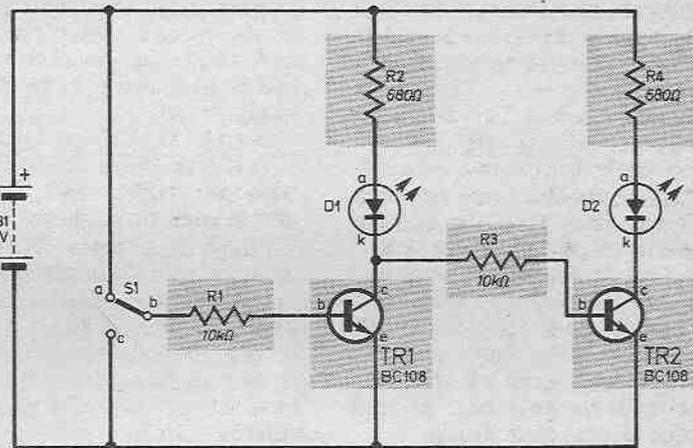


Fig. 8.11a

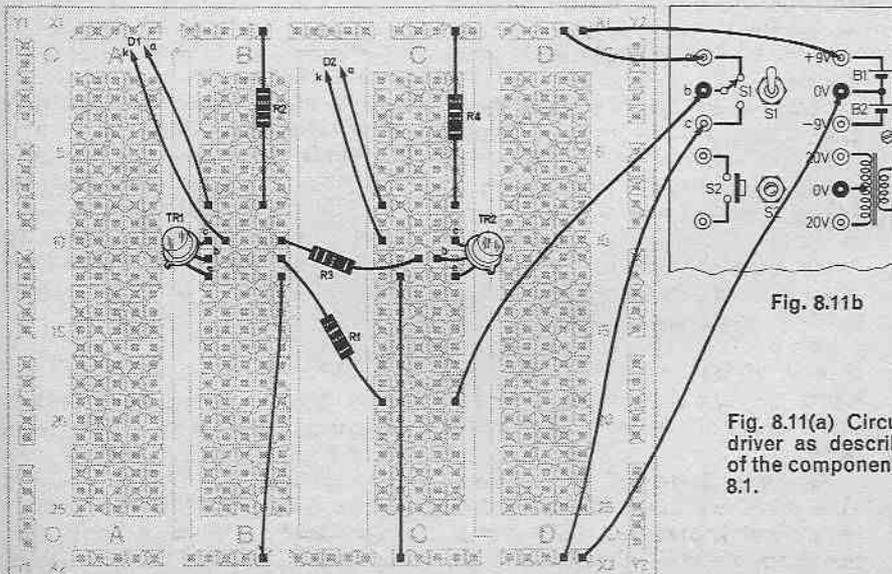


Fig. 8.11b

Fig. 8.11(a) Circuit diagram of the two stage i.e.d. driver as described in Experiment 8.1. (b) Layout of the components on the Tutor Deck for Experiment 8.1.

## EXPERIMENT 8.2: SWITCH WITH DELAY

**Components needed:** 680Ω ¼W resistor, 100kΩ ¼W resistor, 470μF 16V capacitor, BC108 transistor.

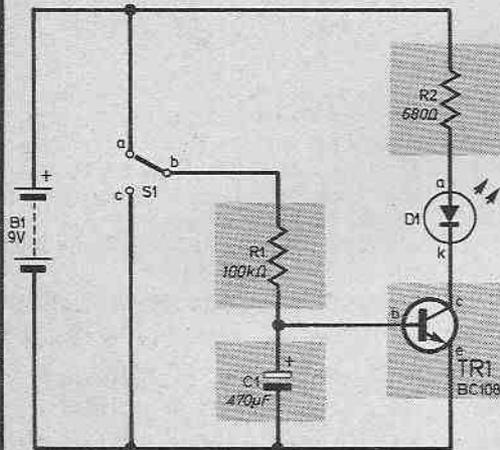


Fig. 8.12(a) Circuit diagram of Experiment 8.2. (b) Layout of the components on the Tutor Deck for Experiment 8.2.

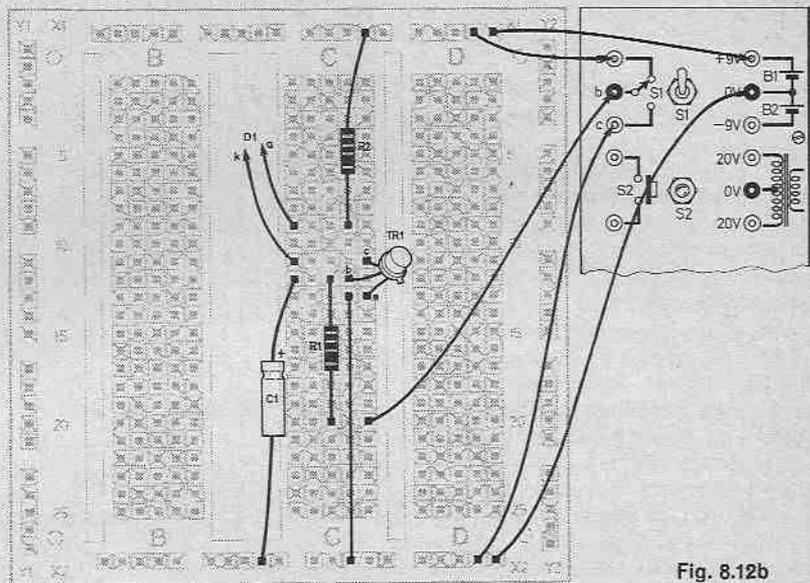


Fig. 8.12b

This experiment shows how the charging time of a capacitor can be used to produce a delayed switching circuit. The circuit is shown in Fig. 8.12a and the layout in Fig. 8.12b.

The switch is used to switch the i.e.d. on and off but the change in the state of the i.e.d. occurs some time after the change in the state of the switch. The

capacitor has to charge (or discharge) through the base resistor before the base becomes forward biased and the transistor switches on (or off).

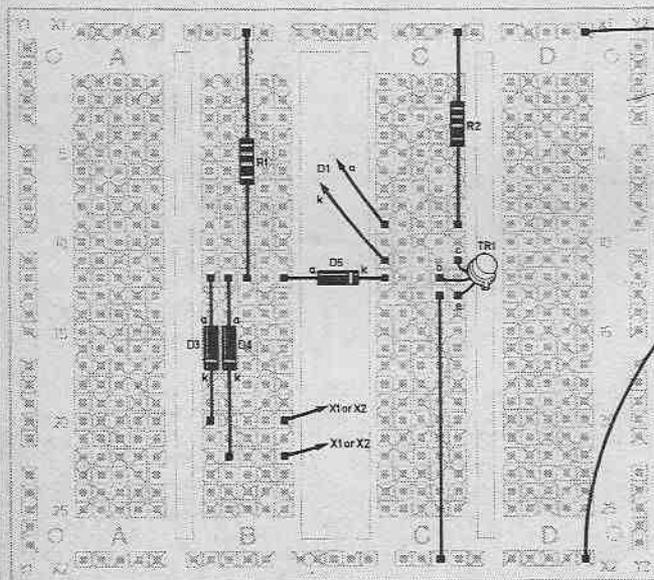


Fig. 8.13b

In this experiment the simple AND gate using two diodes (see Fig. 4.11) is improved by adding a transistor switch. Note, however, that the diode AND gate is now a diode-transistor NAND gate because the transistor switch produces an inversion of the logic levels.

The circuit is shown in Fig. 8.13a and the Tutor Deck layout in Fig. 8.13b.

Fig. 8.13a


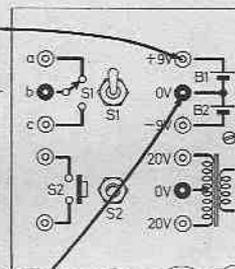


Fig. 8.13(a) Circuit diagram of the two input NAND gate as described in Experiment 8.3. (b) Layout of the components on the Tutor Deck for Experiment 8.3.
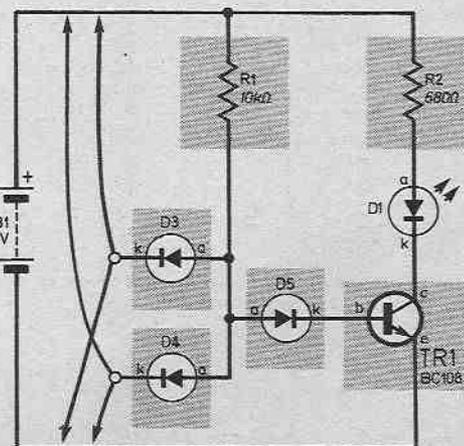
## EXPERIMENT 8.3: TRANSISTOR-DIODE NAND GATE

**Components needed:** 680Ω ¼W resistor, 10kΩ ¼W resistor, IN4148 diodes (3 off), BC108 transistor.



## LOGIC GATES

When we looked at diodes (Part 4) we saw how a simple logic "gate" could be formed which gave a "true" output only when both inputs were "true". The problem with the gate shown there (Fig. 4.8, Fig. 4.9) was that it could not easily be connected to other circuits of the same type.

Combining the diode gate with a transistor switch produces a gate circuit which can be connected to many other circuits.

Note the extra diode D3 that is needed in the base circuit of the transistor (Fig. 8.9). This is necessary because even with both diodes (D1, D2) fed with a low voltage (0.2V) from previous stages, the voltage at the base of the transistor without the extra diode would be 0.2+0.7V. This is more than enough to forward bias the base-emitter junction and switch the transistor on when it should be off. The extra diode reduces the voltage at the base to 0.2V so that it is well and truly off.

## DIGITAL INTEGRATED CIRCUITS

Because of the importance of digital techniques, a lot of work has gone into producing switching circuits which act at extremely high speeds yet consume as little power as is possible. The huge number of switches needed in a large digital computer led to the development of integrated circuits which are packages in which a large number of transistors and resistors and diodes are fabricated on a single piece of silicon (a "chip").

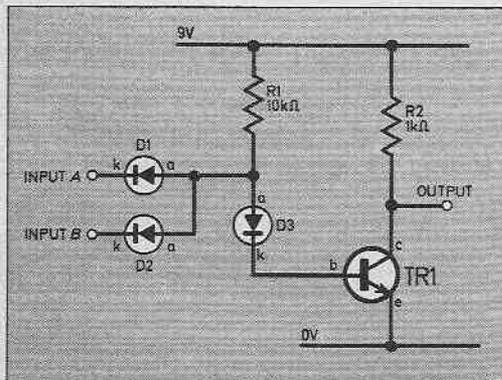


Fig. 8.9. The circuit shown is a logical NAND gate. Only when both inputs are high does the output go low.  
Fig. 8.10.(right) The circuit of a TTL two-input NAND gate which performs exactly the same logical function as the circuit of Fig. 8.9 but a great deal more effectively.

## PART 8 QUESTIONS

8.1. The collector to emitter voltage of a saturated transistor is:

- a) 2V
- b) 0.2V
- c) 5V
- d) 0.7V

8.2. What current into the base is needed to saturate a transistor with  $h_{FE} = 50$  and collector current of 100mA:

- a) 100mA
- b) 1mA
- c) 2mA
- d) 10mA

8.3. To increase the fan-out of our switch we could use a transistor with different characteristics. Which of the following is most useful, all other parameters being the same:

- a) higher gain
- b) higher power

- c) higher collector current capability
- d) higher speed

8.4. Switching time of a transistor switch depends on which of the following:

- a) type of transistor
- b) the circuit used
- c) both of these
- d) neither of these

8.5. What does TTL stand for:

- a) Two transistor levels
- b) Transistor timing logic
- c) Transistor transistor logic

## PART 7 ANSWERS

7.1. a) 7.2. c) 7.3. b) 7.4. a) 7.5. b)

The most dominant technology in digital integrated circuits over the last ten years has been Transistor Transistor Logic or TTL for short.

TTL circuits have now become extremely cheap because of the vast quantities in which they are made. They are very fast, switching speeds being measured in thousandths of millionths of a second (nano seconds or ns) rather than microseconds. They are reliable and can drive many other similar circuits. Nowadays improved versions of these circuits have been produced which are even faster and consume far less power.


A typical TTL circuit is shown in Fig. 8.10. Some special features worth noting are the input transistor TR1 with its multiple emitters which act just like the

diodes in our simple gate, and the fact that the collector resistor of the output transistor TR3 has been replaced by another transistor TR4. This gives the circuit the capability of driving other circuits at higher speeds than would be possible with just a simple resistor.

Other technologies that are popular are CMOS which has the advantage of working with a wide range of supply voltages whilst consuming only minuscule amounts of power and PMOS which is used for cramming vast numbers of circuits onto a single piece of silicon since each transistor can be made very small.

In a later part of this series we will look at CMOS logic and go a little further into its capabilities.

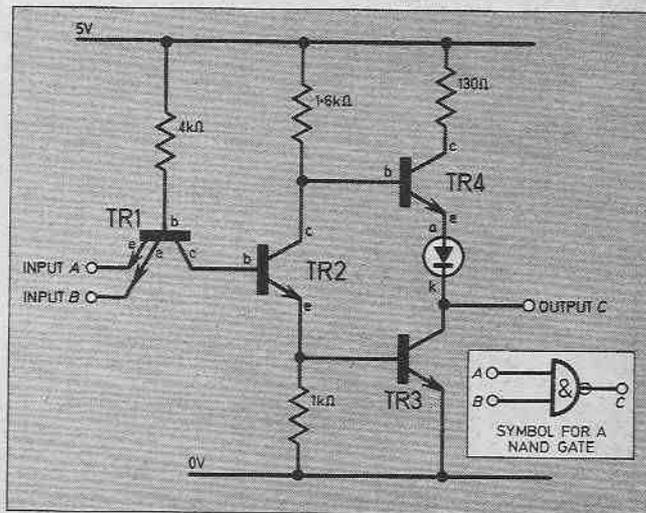Next month we will consider the transistor as a linear amplifier.





# ELECTRONIC WARFARE

BY G. A. G. BROOKE

**A** TELEVISION feature described some of the secret cat and mouse activities in World War II that are now called Electronic Warfare. And from time to time this intriguing term appears in the press, as for instance the announcement by Decca Radar of the order for £2 million worth of "EW equipment" to be installed in new Danish warships. Little else was said and in fact intimate details are never published by the manufacturers or armed forces concerned.

This is generally in line with military necessity; but new aircraft, for instance, are often itemised minutely, particularly in American specialist magazines, so why this secrecy about Electronic Warfare equipment and what is it anyway?

A major chess game is in continuous operation between NATO and Iron Curtain electronic design engineers, each side trying to get a step ahead of the other. As made clear in the TV programme, there is nothing new about this, the first instance of the use of EW having been by the Royal Air Force in April 1942.

As soon as a radar is switched on, either by an aircraft, ship or ground station, two things follow. First, a suitable receiver can

supply its operator with several of the radar parameters (from which can be obtained considerable information about their source) and second, after an internal delay for assessment, a jamming device can be set in operation which will confuse the radar's operator.

Bearing in mind that radar first came about for warlike purposes, it was natural that these two activities should follow its introduction almost immediately.

## EARLY JAMMING DEVICES

It was a jamming device that first appeared, RAF bombers using it against the German "Freya" early warning radars, and within months an improved version was in use along a 200 mile front. The next year US bombers used "Chaff", thousands of small strips of aluminium foil that were released to provide an effect somewhat similar to dense sea clutter, in order to obscure their own echoes.

Chaff is still in use (a Squadron Leader was recently on record describing an amusingly Heath-Robinson method he thought up for dispensing it from the Jaguar aircraft) but enormous strides have since been made in both monitor-

ing and jamming. Nor is that all: anti-jamming measures on behalf of the radar have been developed and the scene soundly set for our international chess game.

Here it is necessary to introduce the accepted EW jargon. The passive side—monitoring—is ESM (Electronic Support Measures); the active side—jamming—is ECM (Electronic Counter Measures); the defence against jamming is ECCM (Electronic Counter Counter Measures); and there is also Elint (Electronic intelligence, of a future tactical rather than immediately useful nature).

The early jammers (ECM) were simply radio transmitters that radiated a continuous amplitude noise-like signal across the enemy radar's frequency band, already deduced by special aircraft with sensitive receivers (ESM). Generally speaking the radar would receive a strong signal that obliterated that of the inevitably weak echo-return.

In the case of Plan Position Indicator displays, the jamming signal served to illuminate a wedge-shaped sector whose angular width corresponded to the beamwidth of the radar aerial. Because the early radars had relatively wide beamwidths an air-

borne jammer could nullify a large portion of the display. The early aerials also had significant sidelobes and this further assisted the jammer by expanding the width of the "whited-out" section.

## COUNTER COUNTER MEASURES

With the Cold War, followed by conflict in Korea and Vietnam, EW continued to develop, particularly ECCM. The airborne jammer had weaknesses that the ground radar could exploit, one being limited power due to limited size and weight. Not so restricted, the ground radar designer had recourse to greater power, defying jamming, and larger aerials with reduced beamwidth and sidelobes.

Another ploy was the use of radar magnetrons which could be rapidly retuned to a different frequency, forcing the jammer either to carry a special operator with radio receiver for monitoring, or to resort to "barrage jamming" across an active band which reduced available jamming power.

Yet another technique was to have two or three different transmitters, so that perhaps three successive radar pulses would all go out on different frequencies. This necessitated a separate jammer for each frequency and the jammer was further embarrassed by the introduction of new types of high power valves which could be retuned more quickly and over a broader band. The advent of the digital computer provided new

techniques for processing radar signals that made it easier to detect weak target echoes among jamming.

It might be thought that ECM was now well on top of ECCM but developments in microwave valves were also helping the designers of jammers. For example, valves such as the backward-wave oscillator and voltage-tuned magnetron enabled the jammer to retune more rapidly or to sweep the jamming signal across the known band. The chess game was gathering momentum!

## TRAVELLING WAVE TUBE

The travelling wave tube (TWT) amplifier, a broadband linear device was the next ally of the jammer, offering an entirely different approach in that in company with the frequency memory loop it could be used to deceive a radar rather than overwhelm it.

This combination made it possible to receive and transmit back to a ground radar a copy of its own pulses, however varied these might be by ECCM techniques. They stored the received pulse in a memory device and then retransmitted it, so that the radar first received the weak echo return and then an identical but stronger one. The result was a series of spurious targets, each at a different range. This type of jammer was of particular use against radars used for fire control, in particular the many types of missiles which depend on radar for guidance.

## MISSILES

The sinking of the Israeli destroyer Eilat by a single (Russian) missile from an Egyptian gunboat one tenth its size in the Six Days War awoke the armed forces of the entire world to the efficiency of missiles. Their cost-effectiveness was such that here was a long range, powerful, accurate weapon that could be carried in a fast patrol boat as easily as in a cruiser.

Almost from that moment there was a rush to arm with missiles, and also of course to arm with the anti-missile capabilities of Electronic Warfare. From then on, activity has been immense and as varied as there now are radar systems to be assisted or combated with specialised departments of major electronics firms doing nothing else.

Fire control radars normally track the target automatically once the human operator has designated it. He does this by assigning it a range tracking gate. The radar locks on and, in effect, turns off its receiver until an echo can be expected at the approximate range of the chosen target, taking its speed into account. This procedure is open to deception jamming by "range gate stealing".

At the outset, the jammer immediately repeats back the received pulse, which allows the radar's

A typical small ship ESM for gleaning information about enemy radars and their sources.

Our heading picture (artist's impression) shows a Vesper Type 21 frigate in an "EW environment". The anti-missiles are intercepting a sea skimming missile and a high flying aircraft, while the ship engages enemy ships with Exocet missiles.

A Decca hand-held lightweight ESM system for use in helicopters and small vehicles.



automatic gain control to adjust to this stronger signal (because it assumes it to be the chosen target). The deception jammer then gradually introduces increasing delays before transmitting back. The radars range-gate circuiting begins to track the stronger jammer signal and gradually wanders off from the correct target range.

## BEAM SPLITTING

In order to measure target position within the beam more accurately, modern surveillance radars use a signal processing technique called beam-splitting. This boils down to measuring the point of strongest return because it corresponds to the centre of the beam. A deception-repeater can upset such a technique by using a procedure called inverse-gain. This effects the direct reversal of the normal method of retransmission of the received radar pulse using power proportional to the strength of the received signal.

When the leading edge of the radar beam first (weakly) strikes the jamming aircraft, this retransmits the pulse with *higher* power; and when struck by the strong signal from the centre of the radar beam, the jammer replies weakly. Thus the beam-splitting process is turned on its head.

## CONICAL SCAN

Some fire control radars, both ground and airborne, employ a conical-scan technique to track their targets. The aerial points in


the last-known direction of the target and its narrow beam is made to scan across a small arc around the aiming point to ensure that the beam will catch the target occasionally, despite the latter's movements.

This small volume scan is usually effected by a high speed, off-centred rotation of the aerial or its feed. The return will be strongest when the beam is directly on target, it will be weak to zero when the target is only partially or not illuminated at all. The radar continuously compares echo strength with aerial position to determine target position (and to redirect the aerial centre in the right direction).

A deception-jammer can disrupt this type of radar every effectively by retransmitting pulses that are modulated with spurious amplitudes at the conical-scan frequency, i.e. displaced in time-phase. This will cause the radar to sense that the target is, for instance, below and to the left of its aerial position when in fact it is above and to the right. The jammer can gradually introduce errors by increasing the spurious time-phase shift.

An alternative radar design which is not vulnerable to this jamming technique is to use a non-scanning transmit aerial and a separate receive only aerial the beam of which does the scanning. This means that the jammer cannot tell the frequency of the radar's receive aerial, forcing the former to sweep its modulation across a band.

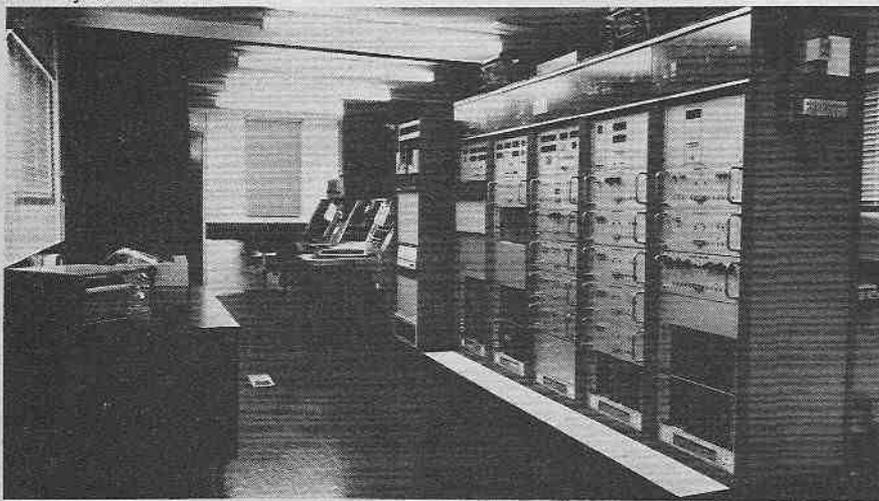The Electronic Warfare Engagement Simulator built by Plessey. Under development for four years, it can simulate, in real time, many different combat conditions including intensive use of ECM techniques by the supposed enemy. Its purpose is to aid development of new ECM techniques that can be used to protect aircraft flying against fire control radar systems.



Spy in the sky. A German Dornier "Kiebitz" tethered rotor platform goes aloft from its support truck. Unmanned, it takes electronic equipment up to 1,000ft greatly increasing its operation range.

Monopulse radar is another method of frustrating angle-deception jammers. This employs the interferometer principle to measure target angle, using two or more separated receiving aerials for training and two others for elevation (the displaced aerials measuring the relative phase, or amplitude, of the echoes to determine angle).

## DOPPLER SYSTEMS

When continuous wave and pulse Doppler type radars were introduced to detect low flying aircraft in ground clutter (see *Rapier Missile System*, EVERYDAY ELECTRONICS, April, 1977) special deception procedure had to be developed. The basic principle of these radars concerns the Doppler shift of echoes due to target velocity.

For the first mentioned (continuous wave) the method of deception is to retransmit the signal with a spurious Doppler shift, gradually increasing its magnitude to cause break-up of velocity tracking. Apart from introducing errors into the system's computation of lead angle, velocity gate wander can result in loss of target tracking when the jammer stops its retransmission.

Against the pulse Doppler type, a TWT is used, the jammer introducing a spurious Doppler shift when it retransmits the received pulses.

## AT SEA

Though the foregoing has concentrated on land and air, navies are equally dependent on Electronic Warfare. Ships are loath to use their radars for fear of giving

their presence away to an ESM equipped enemy. When they do, ECCM is employed to the full to confuse the ESM operator.

Chaff is fired from rockets or guns, ships sometimes putting up a modern version of the old smoke screen, behind which they manoeuvre to outwit the detected missiles.

Missiles do not always fly straight, some rise to a great height and plunge down on their target, though the mechanism to ensure accuracy to the necessary few yards beggars the imagination and is of course hideously expensive.


Many types of missiles can be launched from over the horizon, directed by near real-time targeting data provided by reconnaissance aircraft or air/ship-based Elint receivers and data linked to the launching platforms. These can be small fast patrol boats, as mentioned or submarines below the surface. It is also thought that the integration of data obtained by satellite is possible. Probably the best defence is a mixture of weapons (such as guns and anti-

missile missiles), the EW techniques touched on above, and suitable tactics.
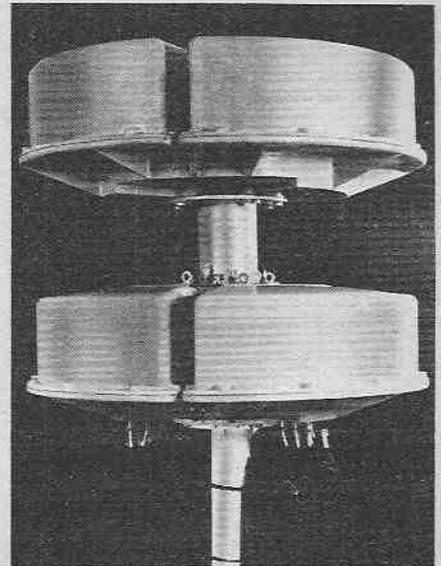
## SUPERIORITY BATTLE

Further examples of move and counter move are endless, sometimes one side gaining the ascendancy, sometimes the other. It is obvious why secrecy is vital. Historically, the Soviet invasion of Czechoslovakia was a big plus to them, since their ECM technique was successful in blinding NATO's early warning devices on the frontier. Later the Americans can be said to have won the EW battle against the Russian supplied N. Vietnamese air defence system.


Lastly, in the Israeli-Egyptian "October" war, Electronic Warfare was a key element all round, both at sea and in the air. The Israelis used a pilotless decoy plane that on one occasion was attacked by a total of 32 missiles but returned safely and in a naval engagement the Eilat defeat was reversed by four Israeli fast patrol boats who hit eleven Egyptian ones, all concerned armed with missiles.



Double cake shaped aerial of Decca's EW equipment. Being designed to fit around a mast, it does not compete for the sought after masthead position.

It is a fair conclusion that all radiating electronics can be jammed and any jamming technique can be countered eventually. So an end to Electronic Warfare is not in sight, nor ever seems likely to be. ☐

## USING YOUR FREE GIFT

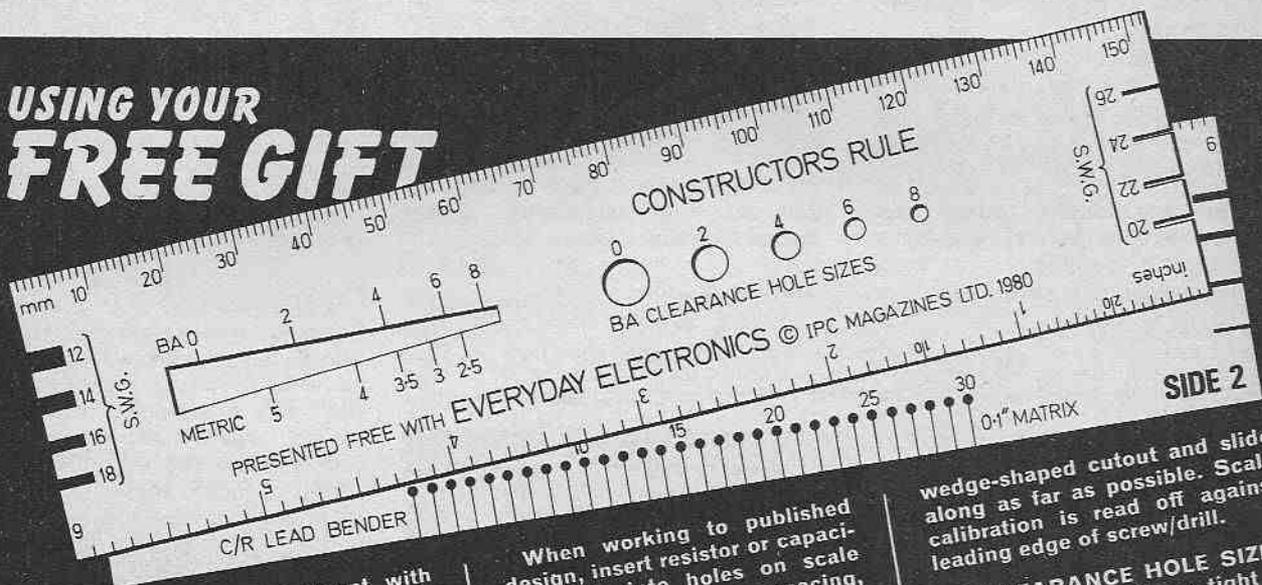

Pocket size instrument with Imperial and metric scales 0-6 inches (0-153mm), plus four gauges of particular usefulness to electronics conductors.

**CAPACITOR/RESISTOR LEAD BENDER.** The holes correspond to holes in 0.1 in matrix strip-board or perforated plain s.r.b.p. In general, component leads should be bent not less than 0.1 in. from the body of the component.

When working to published design, insert resistor or capacitor leads into holes on scale giving the required spacing, as denoted on component layout diagrams.

Push component body close to Rule surface, straighten and parallel the leads. Finally trim off both leads about 1mm from Rule and remove.

**BA AND METRIC GAUGE** Insert screw or drill into wide end of

wedge-shaped cutout and slide along as far as possible. Scale calibration is read off against leading edge of screw/drill.

**BA CLEARANCE HOLE SIZES** Correct drill will be a tight fit in appropriate hole.

**S.W.G. GAUGE** for Sheet metal and connecting wires in the most common sizes from 12 to 26 s.w.g. Especially useful for matching drills and wires.

# BATTERY VOLTAGE MONITOR

A.P. DONLEAVY

**T**HIS article describes a simple car voltmeter using l.e.d.s to give a continuous indication of battery voltage. The instrument can be calibrated over a range of about 11 to 15 volts and is easily constructed and installed in any car whether positive or negative earth.

## CIRCUIT

The circuit is shown in Fig. 1. The LM324 integrated circuit contains four operational amplifiers (op-amps). The inverting terminal of each op-amp is connected via R13 to the junction of R14 and D5 (D5 is a Zener

diode, providing a fixed reference voltage of about 6V).

## REFERENCE VOLTAGE

Resistors R1, R3, R6, R9 and VR1 form a potential divider chain. The values of these resistors are chosen to give voltages of between 5 and 7 volts at the non-inverting terminals of the op-amp.

The actual values will vary with the supply voltage, that is the battery voltage. Each op-amp will amplify the difference in voltage between its inverting and non-inverting inputs several thousand times.

If the voltage at pin 10 of IC1 is higher than that at pin 9 (which is the reference voltage), then the output at pin 8 will be high (12V approximately) and the l.e.d. D1 will be on.

As the supply voltage increases, more of the non-inverting inputs will be at a higher potential than the reference voltage, hence more l.e.d.s will be turned on. VR1 is adjusted to give the range of voltage measurement required.

The diode D6 is used to prevent damage to IC1 if the instrument is wrongly connected to the supply. It could be omitted but this is not advised.

## COMPONENTS

Many components used in this design are not critical and there is a wide range of tolerances in the published values and types.


The variable resistor VR1 is a multi-turn preset, although the more usual skeleton type could be used instead.

D6 is any diode which has a reverse voltage greater than 20V and D5 is any Zener diode with a value between 5 and 6V.

Resistor R1 may need to be a slightly different value to compensate for the actual Zener value used.

The l.e.d.s D1 to D4 may be of any type or colour. A different colour may also be used for the last l.e.d. D4 giving a warning of too high a battery voltage, indicating a faulty voltage regulator.

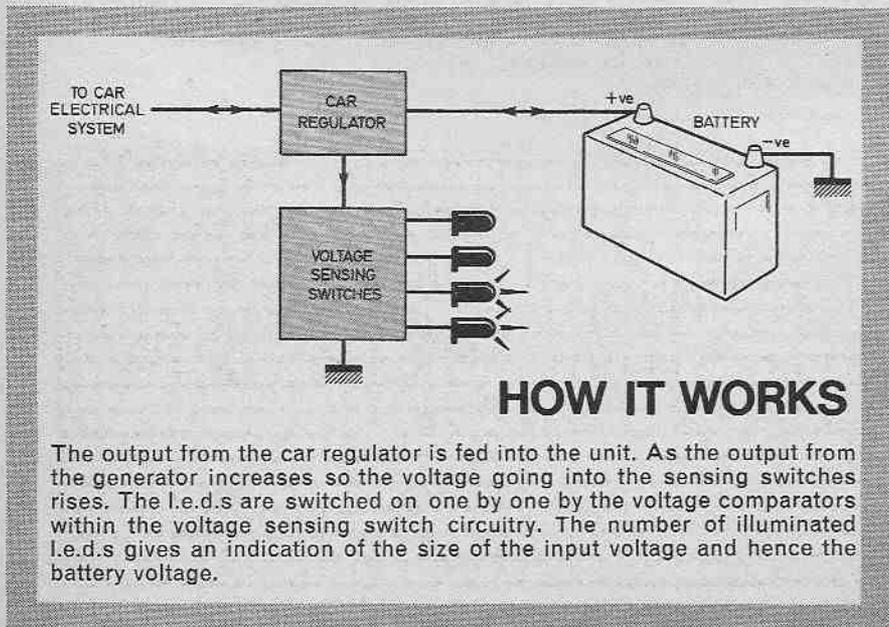The brightness of the l.e.d.s may be altered by changing the values of R4, R7, R10 and R12.



The output from the car regulator is fed into the unit. As the output from the generator increases so the voltage going into the sensing switches rises. The l.e.d.s are switched on one by one by the voltage comparators within the voltage sensing switch circuitry. The number of illuminated l.e.d.s gives an indication of the size of the input voltage and hence the battery voltage.

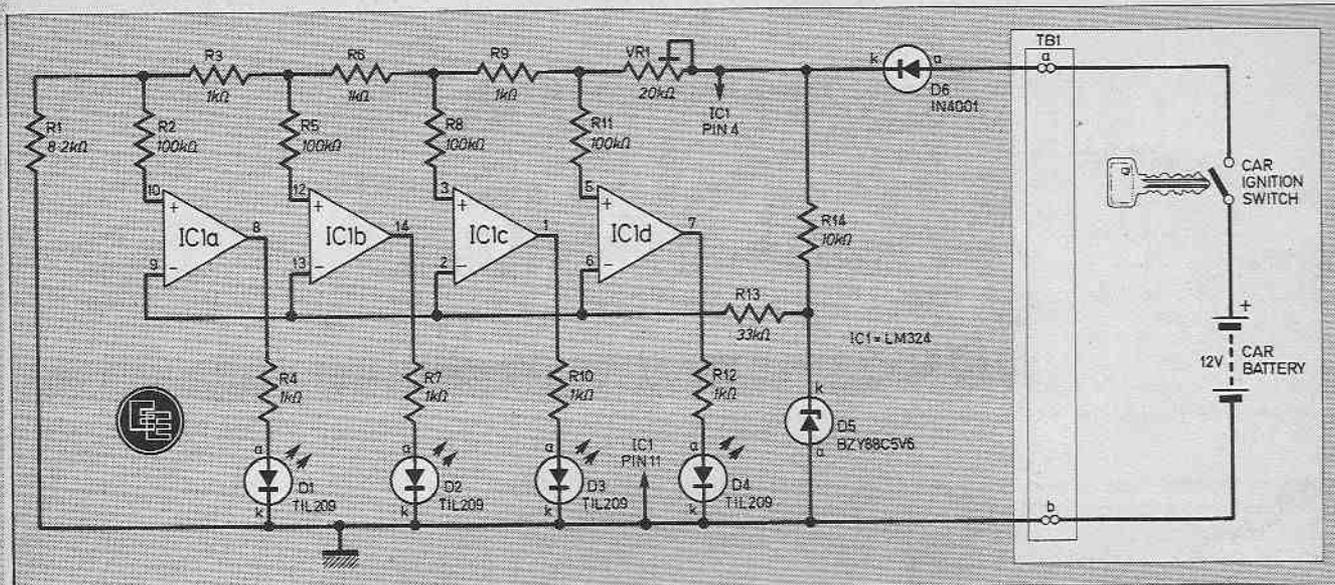


Fig.1. Complete circuit diagram for the Battery Voltage Monitor.

## COMPONENTS

### Resistors

R1	8.2k $\Omega$	R11	100k $\Omega$
R2	100k $\Omega$	R12	1k $\Omega$
R3	1k $\Omega$	R13	33k $\Omega$
R4	1k $\Omega$	R14	10k $\Omega$
R5	100k $\Omega$		
R6	1k $\Omega$		
R7	1k $\Omega$		
R8	100k $\Omega$		
R9	1k $\Omega$		
R10	1k $\Omega$		

All  $\frac{1}{4}$ W carbon  $\pm 5\%$

See  
**Shop  
Talk**  
page 323

### Semiconductors

IC1	LM324 quad op-amp i.c.
D1-D4	TIL209 l.e.d. (4 off)
D5	BZY88C5V6 5.6 volt 400mW Zener diode
D6	1N4001 rectifier diode

### Miscellaneous

VR1	20k $\Omega$ multi-turn preset potentiometer
TB1	2-way screw connector block

Stripboard, 0.1 inch matrix, 17 strips  $\times$  32 holes; case, 100  $\times$  50  $\times$  25mm (optional); connecting wire; screws for fixing unit to vehicle; d.i.l. socket for IC1.

**COMPONENTS**  
approximate  
cost **£3**


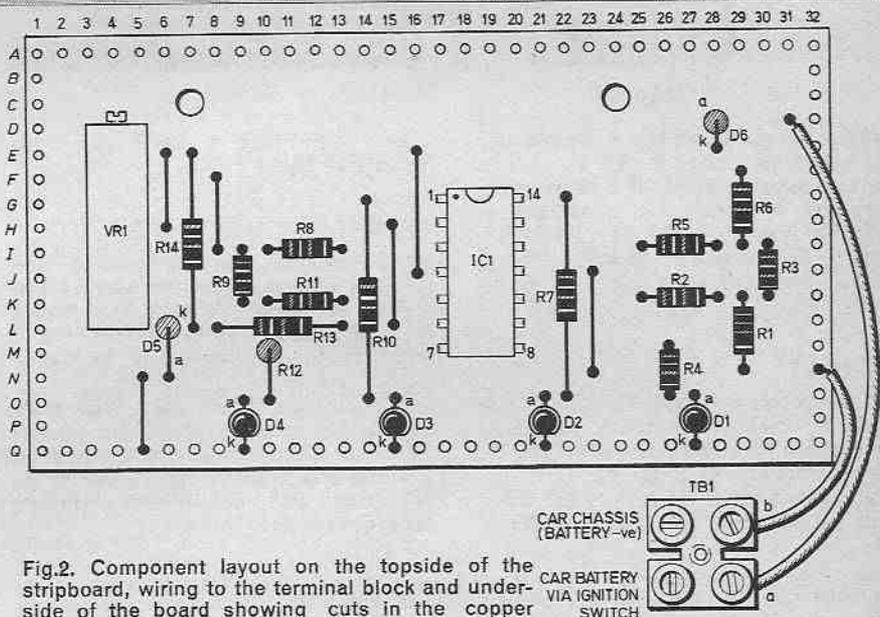


Fig.2. Component layout on the topside of the stripboard, wiring to the terminal block and underside of the board showing cuts in the copper track. The l.e.d.s may be mounted separately from the board, see text.

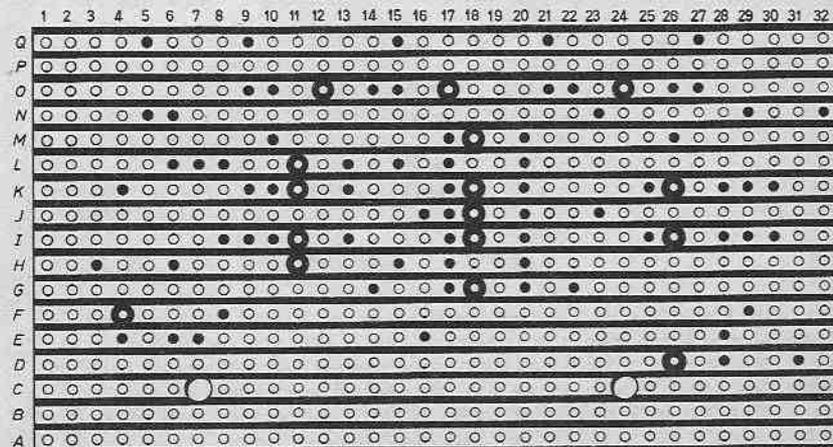

# CONSTRUCTION starts here

## ASSEMBLY

All the components, including the l.e.d.s, are mounted on a piece of 0.1 inch matrix stripboard, 17 strips by 32 holes. The layout is shown in Fig. 2.

The unit is housed in a small box, 50 x 100 x 25mm. Drill the lid of the box in such a way that the l.e.d.s protrude through the surface and fit tightly into these mounting holes.

The constructor may like to alter these mounting arrangements. One

possibility is to mount the l.e.d.s separately in the case. Another is to drill the dashboard and mount them where they can clearly be seen, fitting the stripboard somewhere behind the dashboard.

The input from the battery is made via a double screw connector block TB1 glued on the outside of the case.

## CALIBRATION

Calibration is best done before installation. Connect a voltmeter across the input terminals and adjust VR1 so that the fourth l.e.d. D1 turns on at about 15V.

Check that all the l.e.d.s are extinguished at somewhere between 10.5 and 11V. The value of resistor R1 may need to be altered to achieve this, either 6.8 or 10 kilohms may be necessary depending on the value of D5.

An 18V supply to feed the current through a 1 kilohm variable resistor will suffice for a power supply to calibrate the instrument. The current consumed will be about 18mA with all four l.e.d.s. alight.

## INSTALLATION

When installing the unit in the car use an auxiliary lead from the ignition switch to provide power. In normal operation D3 and D4 should light when the ignition is switched on. D2 may also light when the engine is running.

If D4 lights up on its own, this indicates that the battery voltage is low and so the battery needs recharging or replacing. If all the l.e.d.s come on, the voltage regulator may be suspect (assuming the instrument has been properly calibrated). □

## COUNTER INTELLIGENCE BY PAUL YOUNG

### First Exhibition

In December I visited the "Breadboard Exhibition" and splendid it was too. I do wish that they would rename it. Several people thought it was a Bakery Exhibition.

I must say it bought back memories. It was held in the Horticultural Hall at Westminster and I remember years ago that one of the first of these exhibitions was held there. It was called the "Radio Hobbies Exhibition".

We had a stand there, and three incidents stick in my mind. My brother had pre-fabricated our display on hardboard. We arrived at the hall and started to erect it. Blunder number one; up rushes a Union Official and told us we had to employ a Union man to do it.

We had no alternative but to agree. As it turned out our chap was quite useful and didn't object to our helping him.

The next calamity was even more worrying. Thirty minutes before the show was officially opened, along comes

an Inspector. He takes one look at our hardboard and says, "That's not fire proof, I can't allow the show to open".

Fortunately in the end he compromised, and said that if we painted the backs of the display boards with fire proof paint he would lift the ban. I remember us slapping on black paint as hard as we could go, and the day was saved. Between you and me, the paint we put on would have made it burn better than ever, but as they say, what the eye doesn't see the heart doesn't grieve about.

Finally, when we were packing up to go, I carried out a beautiful display case made of quarter inch plate glass. It was raining and I stood it on the bonnet of our van. Slowly, it slid to the edge while I stood and watched hypnotised, then it plunged into the road and shattered into a thousand fragments.

My brother came along a few seconds later, while I was still gazing at the mess in sheer disbelief. His only cryptic comment was, "Oh! dear, what a pity, I would like to have seen it!"

## Component problems

Over two years ago, I forecast that the range of components might be reduced, and I pointed out that it was not likely to inconvenience the constructor. This has now happened. Toggle switches for example are reduced to two types, single-pole on/off and double-pole double-throw, but since this covers the whole of our needs it is of no great consequence.

Sometimes we run out of a particular value of quarter-watt resistor so we send a half-watt. This upsets no one and only worries the un-enlightened.

I had a case recently, of a customer returning a small transformer and complaining it was open circuit. I remembered that I had had a similar experience myself, but I refused to believe that both the primary and secondary windings were faulty, so I rubbed the connecting wires with "emery" and re-tested it. It was perfect.

These transformers are obviously dipped in a clear varnish which invisibly coats the connecting wires and prevents contact. I mention this in case you come across a similar problem.


## JACK PLUG & FAMILY...

BY DOUG BAKER

YOU KNOW, APART FROM EVERYTHING ELSE, THE REVOLUTIONARY CHIP WILL PROVE TO BE A TIME-SAVING AND—



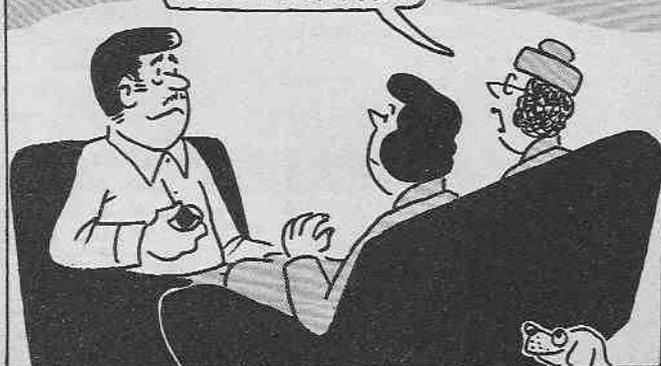IT'S OBVIOUS. YOU SIMPLY WARM UP THE NEW PRE-COOKED CHIPS AND SERVE, SO YOU SAVE TIME BY NOT HAVING TO PEEL POTATOES.



# Next Month

## AUTOPHASE

One of the most popular effects units with pop bands. A four-stage phasing unit that has continuously variable symmetrical automatic sweep. The sweep rate is adjustable by externally mounted control. Suitable for all musical instruments and vocals.

## COURTESY LIGHT DELAY

Allows for a delay—adjustable 0 to 30 seconds—in the operation of the car interior light so that driver and passenger may settle down with doors closed and to start the engine before the light goes out automatically. A boon for every motorist. Easy to build and install.

## A.F. SIGNAL GENERATOR

A valuable item of test gear covering the entire audio frequency spectrum in three ranges. Sine and square waves. Continuously variable attenuator. High level of performance. Low noise and distortion.

## AUTOWAA

An add-on effects unit for the pop guitarist and organist. This produces the usual waa-waa sound without the use of a foot-operated pedal. This has been simulated electronically and has variable speed and adjustable sweep contour.


SOUND EFFECTS

# Everyday ELECTRONICS

JUNE 1980  
ISSUE ON SALE  
FRIDAY, MAY 16  
Price 50p

# Dual Line Game

By A. Russell

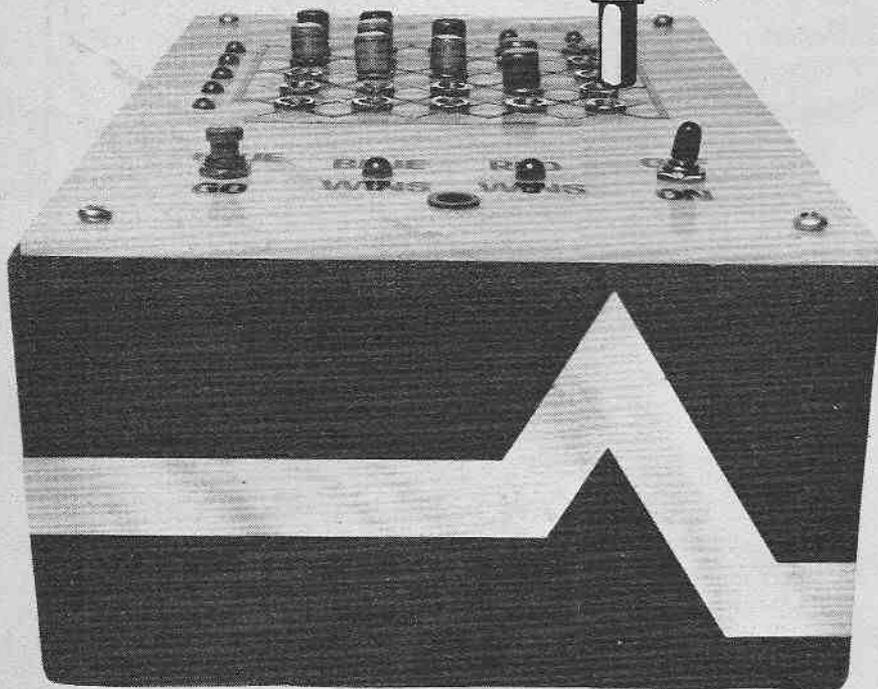

strategy of the machine consists of choosing the resistor across which the maximum voltage occurs. If two or more resistors show the same maximum voltage, one is selected at random.

The move is indicated to the human contestant by lighting two l.e.d.s which point to the row and column co-ordinates of the socket where the machine would like its move made. Of course this requires a measure of integrity on the part of the human contestant because the machine cannot tell when it is being cheated.

A simple machine may be made by using light bulbs, instead of resistors, in the network of Fig.1. The machine moves can then be determined by observing which bulb glows the brightest. It is often difficult to decide which of several bulbs is brightest and so a more sophisticated circuit was developed to automate this decision.

The difficulty here is how to detect the network resistor with the highest voltage across it, bearing in mind that there is no common point in the circuit to measure the voltage with respect to.

## RULES OF THE GAME

THE GAME of Dual Line is played by two contestants on a board marked out with a lattice of interwoven red and blue lines. One contestant (for example BLUE) has a supply of blue plugs, the other (RED) has red plugs. Each player takes turns to insert a plug into an unoccupied socket on the board (there are sockets at each point on the board where red and blue lines cross).

The object of the game, for the RED player, is to create an unbroken red line from top to bottom of the board. When a red plug is inserted into a socket, the red line through that point is assumed to be completed, and the blue line broken. A winning line may zigzag about all over the board so long as it connects the two opposite sides of the board with an unbroken line.

Similarly the BLUE player is trying to complete a blue line stretching between the left and right hand sides of the board. Unlike the game of noughts and crosses the game can never end in a draw because one player can only prevent his opponent from winning by winning himself.

## RESISTOR ANALOGUE

The unit decides the moves for one of the players (in this case BLUE). It operates on the following principle. A resistor network (Fig.1) corresponds

to the lines of play open to the BLUE player (lines of play for the RED player are shown on the same diagram as dotted lines). All resistors have the same value.

When BLUE inserts a plug into a jack socket, the resistor corresponding to that socket is short-circuited. When RED inserts a plug into a jack socket, the resistor corresponding to that socket is open-circuited. Thus when BLUE completes his line from left to right hand side of the board and wins, the entire network is short-circuited.

Similarly when RED completes a line from top to bottom of the board the network is open-circuited. These two conditions are detected by the win detecting circuit (Fig.3) and cause the RED WINS or BLUE WINS l.e.d.s to light.

## MAKING A MOVE

When the circuit is called upon to decide its next move, a voltage source is applied across the network. The

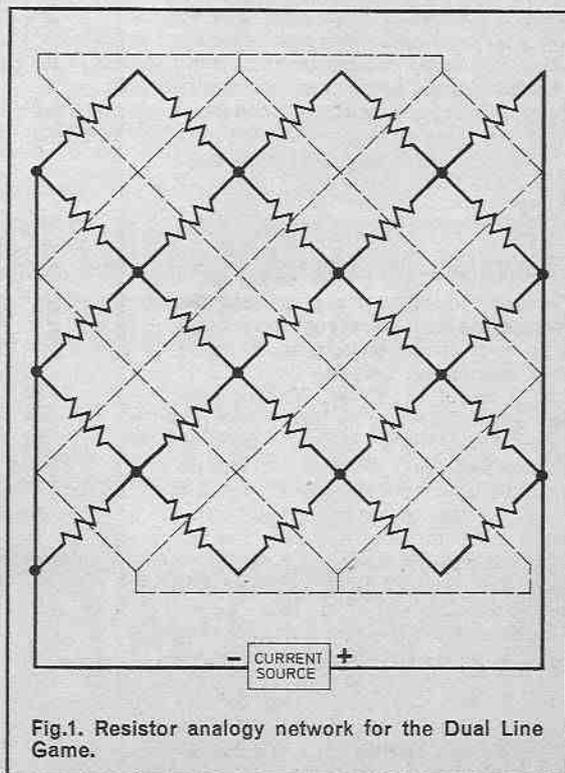


Fig.1. Resistor analogy network for the Dual Line Game.

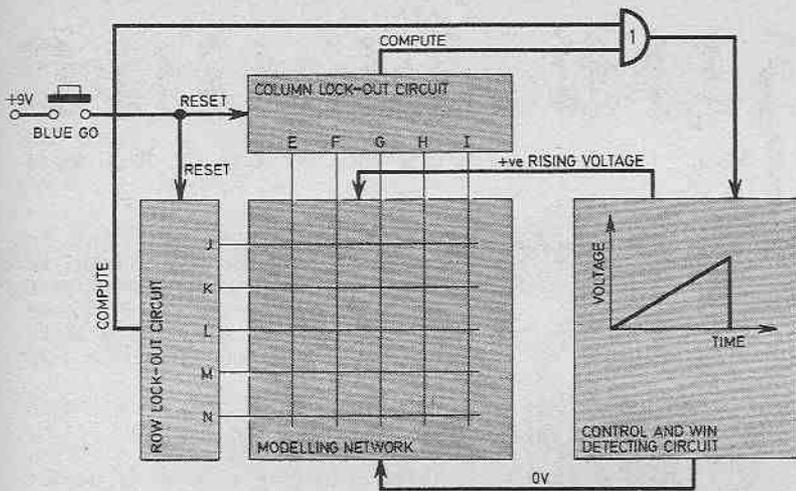


Fig.2. Block diagram showing all sections of the game.

In this circuit the emitter-base voltage of a silicon transistor (which is the same between transistors at the same temperature) is used as a reference. Each resistor in the modelling network has a transistor emitter-base junction across it. Those resistors where current could flow in either direction depending on the state of play have two transistors connected in opposite senses.

### BLOCK DIAGRAM

The sequence of events, which takes place when the machine decides its next move, is best visualised by referring to the block diagram (Fig.2). When the BLUE GO button is pressed, row and column lock-out circuits (Fig.4) are reset which in turn send compute signals to the control circuit (Fig.3). Compute signals cause a variable voltage generator in the control circuit to apply an increasing voltage to the modelling network (Fig.5).

### POTENTIAL DIFFERENCE

Voltage continues to rise until the potential difference across one resistor is enough to switch on its associated transistor. Sensing lines (E, F, G, H, I and J, K, L, M, N) from the row and column lock-out circuits (Fig.4) detect row and column coordinates of the switched on transistor, light the appropriate l.e.d.s and take away the compute signals which causes the output of the voltage generator to return to zero.

Lock-out circuits hold the row and column l.e.d.s on until BLUE GO is pressed again. If either BLUE or RED has won, no voltages will be developed across any resistor in the modelling network. The output of the control circuit will rise until the win detecting circuit comes into play and identifies the winner.



The completed Dual Line Game.

## COMPONENTS

### Resistors

R1	10kΩ	R18	10kΩ	R35	10kΩ
R2	47kΩ	R19	100kΩ	R36	100kΩ
R3	1kΩ	R20	2.2kΩ	R37	2.2kΩ
R4	220Ω	R21	2.2kΩ	R38	10kΩ
R5	10kΩ	R22	100kΩ	R39	100kΩ
R6	2.7kΩ	R23	2.2kΩ	R40	2.2kΩ
R7	27kΩ	R24	100kΩ	R41	100kΩ
R8	10kΩ	R25	2.2kΩ	R42	2.2kΩ
R9	10kΩ	R26	10kΩ	R43-67	2.2kΩ (25 off)
R10	100kΩ	R27	100kΩ		
R11	2.2kΩ	R28	2.2kΩ		
R12	10kΩ	R29	10kΩ		
R13	100kΩ	R30	100kΩ		
R14	2.2kΩ	R31	2.2kΩ		
R15	10kΩ	R32	10kΩ		
R16	100kΩ	R33	100kΩ		
R17	2.2kΩ	R34	2.2kΩ		

All 1/4W carbon ±5%

### Capacitors

C1	50μF 15V elect.
C2	50μF 15V elect.

### Semiconductors

TR1, 2, 3	BC108 npn silicon (3 off)	D6-8	} TIL 220 red light emitting diode (12 off)
TR4-TR15	BC557 pnp silicon (12 off)	D15	
TR16-TR49	BC108 npn silicon (34 off)	D22	
D1-D4	} IN 4148 or similar small signal silicon diode (126 off)	D29	
D9-D14		D36	
D16-D21		D49	
D23-D28		D56	
D30-D35		D63	
D37-D48		D70	
D50-D55		D77	
D57-D62			
D64-D69			
D71-D76			
D78-D139			
D5	BZX85 5.1V Zener diode		

### Miscellaneous

SK1-SK25	3.5mm jack sockets with one normally closed switch (25 off)
S1	single-pole on/off toggle
S2	miniature push-to-make single-pole switch
B1	9V type PP3
Stripboard: 0.1 inch matrix, 36 strips × 51 holes (3 off); 6 metres of ten-way ribbon cable; PP3 battery connector; size 10 knitting needles, one set plastic one set metal, for pegs; 7mm diameter wood dowelling and red and blue enamel paint for pegs; materials for cabinet; three 4BA nuts and bolts with spacers for mounting circuit boards.	

COMPONENTS  
approximate  
cost £20

See  
**Shop  
Talk**  
Page 323

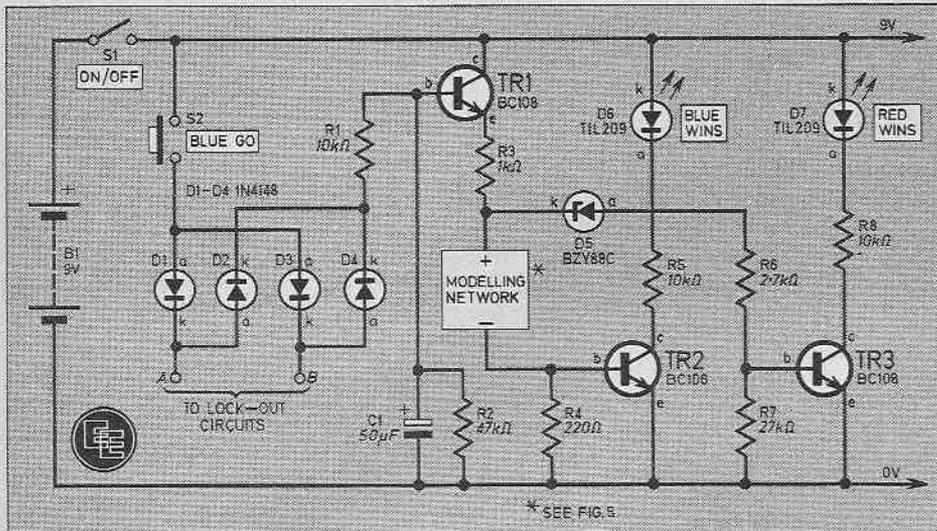


Fig. 3. Complete diagram of the control and win detecting circuit. This is built on board A.

### CONTROL CIRCUIT

The complete circuit of the control and win detecting circuit is shown in Fig. 3.

When the BLUE GO button is pressed 9V is applied via diodes D1 and D2 to lines A and B of the row and column lock-out circuits. This resets the system and in turn applies 9V back to the control and win detecting circuit via the diode or gate D3 and D4.

Because of the C-R network (made up of R1 and C1), the voltage at the base of TR1 rises exponentially to-

wards 9V. This rising waveform is buffered by the emitter follower stage formed by TR1 and fed into the modelling network (Fig. 5).

If nobody has won yet, the voltage across the modelling network continues to rise until the voltage across one of the resistors in the network is sufficient to cause the associated BC108 transistor (TR16 to TR49) to conduct. Current is then fed from this transistor, through two isolating diodes, onto two sensing lines from the lock-out circuits.

### WIN OR LOSE

If RED has won, the modelling network is open circuit and the emitter voltage of TR1 is free to rise toward 9V. When this voltage reaches 5.8V, D5 starts to conduct and feeds current into the base of TR3 which switches on and lights the RED WINS l.e.d. D7.

Similarly, if BLUE has won, the modelling network is short circuit and the current through TR1 rises until about 3mA is flowing at which time the voltage drop across R4 is about 0.7V; TR2 switches on and the BLUE WINS l.e.d. D6 is lit.

### LOCK-OUT CIRCUITS

The modelling network is flanked by two lock-out circuits, one for the rows, one for the columns, and their function is to record and display the network element with the highest voltage across its terminals.

When the BLUE GO button is pressed, line A or B (depending on whether we are considering row or column lock-out circuits) is taken to +9V (see Fig. 4). This energises TR9 (or TR15) which switches off TR4, 5, 6, 7 and 8 (or TR10, 11, 12, 13 and 14). At the same time compute signals are applied to the control and win detect circuit which in turn applies a rising voltage to the modelling network.

Assuming neither player has won, one of the elements in the modelling network switches on causing a volt-


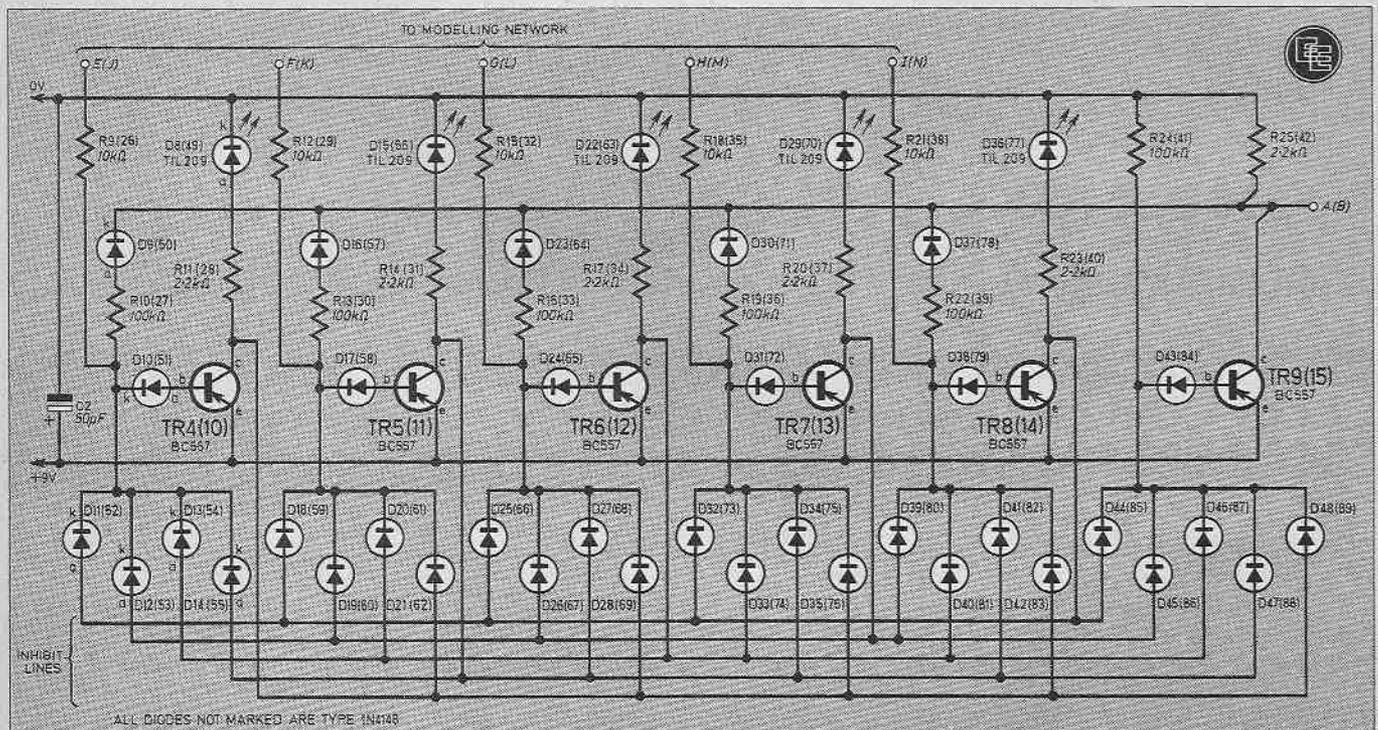


Fig. 4. Complete diagram of the lockout circuits. Note that two of these are required, one for the rows and one for the columns. Bracketted component references are for the column lockout circuit and unbracketed ones for the row lockout circuit. These are both built on board B.

# HOW IT WORKS

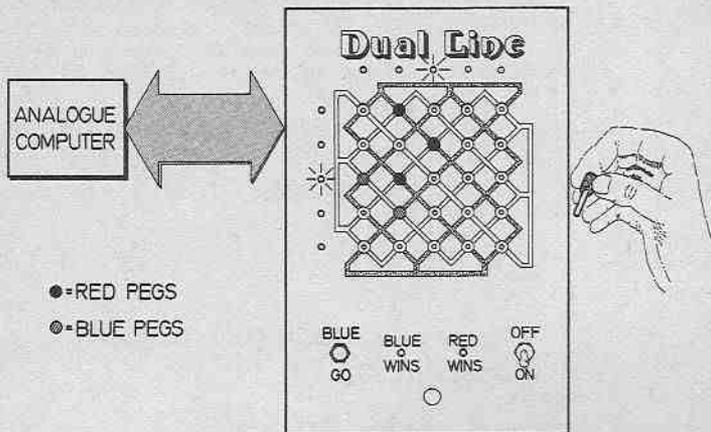

In this electronic game of Dual Line, the machine always uses blue pegs and the human contestant red pegs.

Assuming red moves first, the appropriate colour peg is taken and placed in the selected position. The BLUE GO button is then pressed. This causes the analogue computer within the unit to work out the best counter-move and indicate its position by lighting up two l.e.d.s on the front panel.


The player then inserts a blue peg in the position given and the whole process is repeated again and again until there is a complete line of pegs—either blue or red.

When this happens, the machine works out who has won the game and lights up the correct WIN l.e.d.
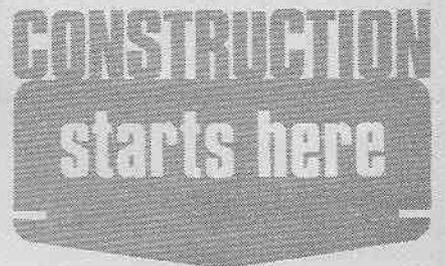
## MODELLING NETWORK

The complete circuit of the modelling network is shown in Fig.5. You will notice that there are two types of circuit elements. However, both essentially consist of a resistor connected across a semiconductor junction, the ends of which are connected into the matrix. There are also two sensing outputs X and Y each connected to the sensing lines from the lock-out circuits.

When the applied voltage across the network is sufficient to turn the transistor on in a particular element, these outputs go high energising their respective sensing lines. This causes the lock-out circuits to register this condition and indicate the next move.



## CIRCUIT BOARDS

Most of the components in the Dual Line Game are mounted on three circuit boards. These are all identical pieces of 0.1 inch matrix stripboard 36 strips by 51 holes and full details of component mounting and drilling are given in Figs. 6, 7 and 8.

Construction should start with the control and win detecting circuit board (Fig.6). It will be noticed

age to appear on its respective sensing line. When this happens, the associated transistor in the lock-out circuit switches on illuminating the l.e.d. in its collector line.

To stop other transistors being activated at the same time, a set of

inhibit lines are provided. These are initially all at 0V. When one transistor turns on it immediately clamps its associated inhibit line to +9V which turns off TR9 and prevents any of the other lock-out transistors from turning on.

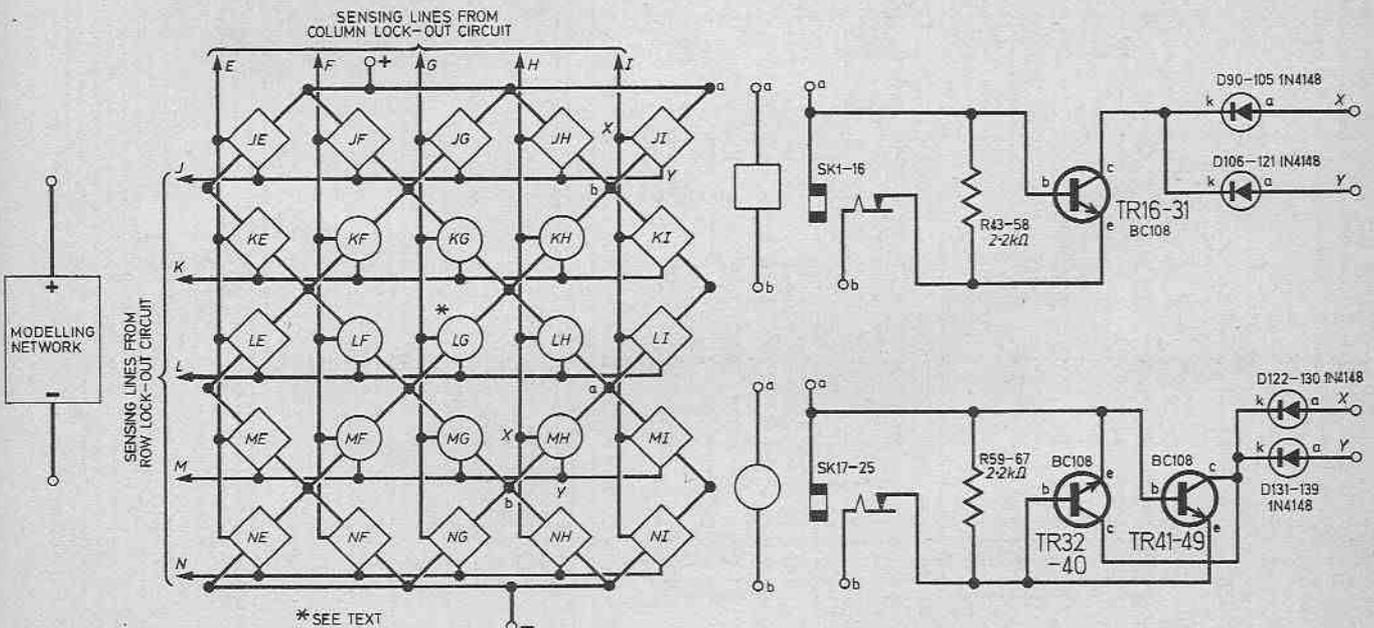


Fig.5. Circuit diagram of the modelling network. Note that this is made up of identical network elements, the circuit diagrams of which are shown on the right. This is built up on board C.

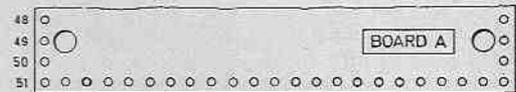
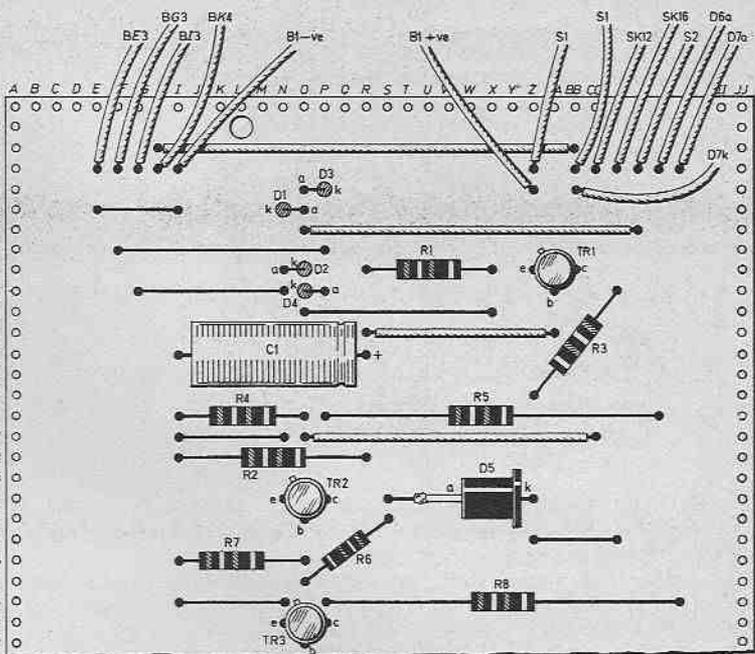
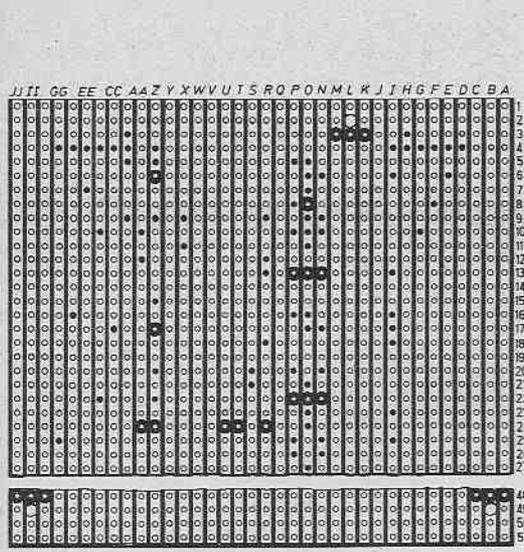


Fig.6. (above and left). Circuit board layout of the control and win detect circuit (Board A).


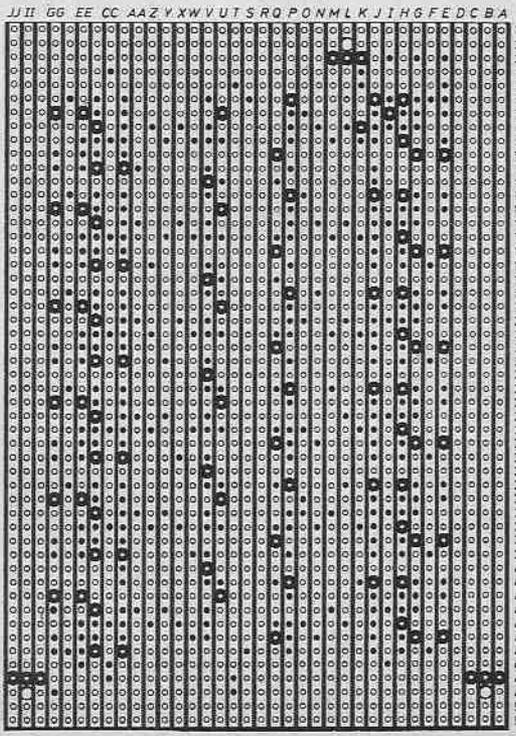


Fig.7. (below and left). Circuit board layout of the lockout board (Board B). See text for an explanation of the inter-board wiring references.

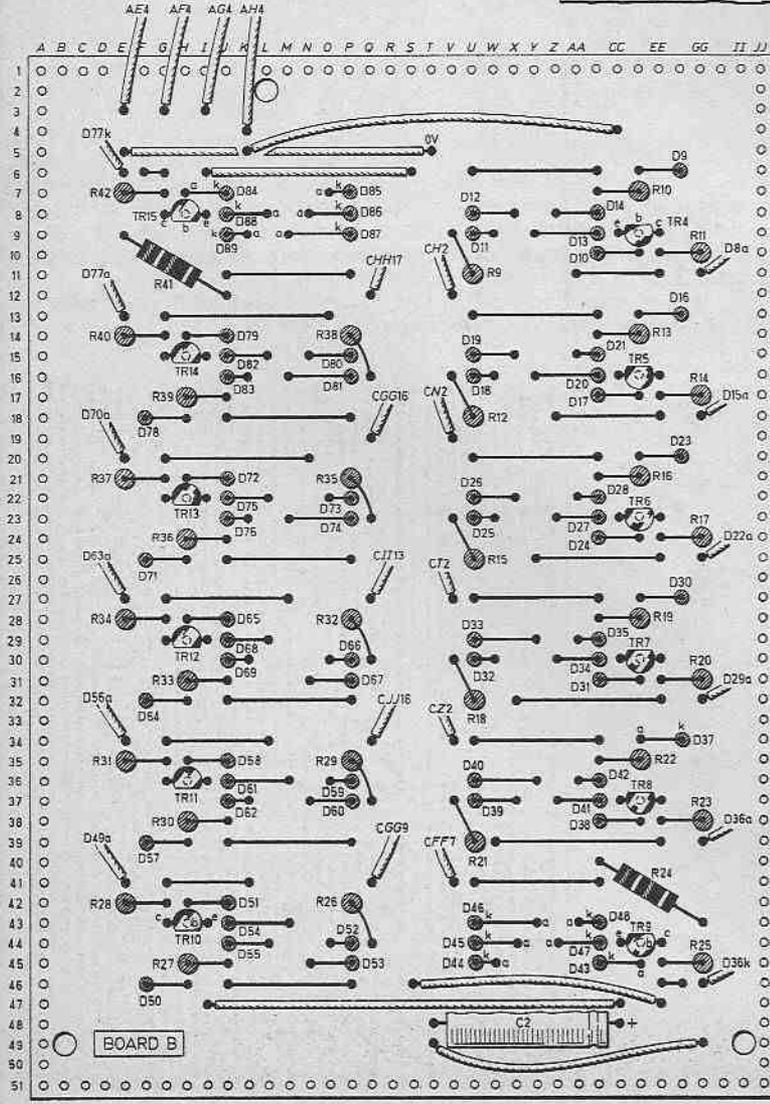

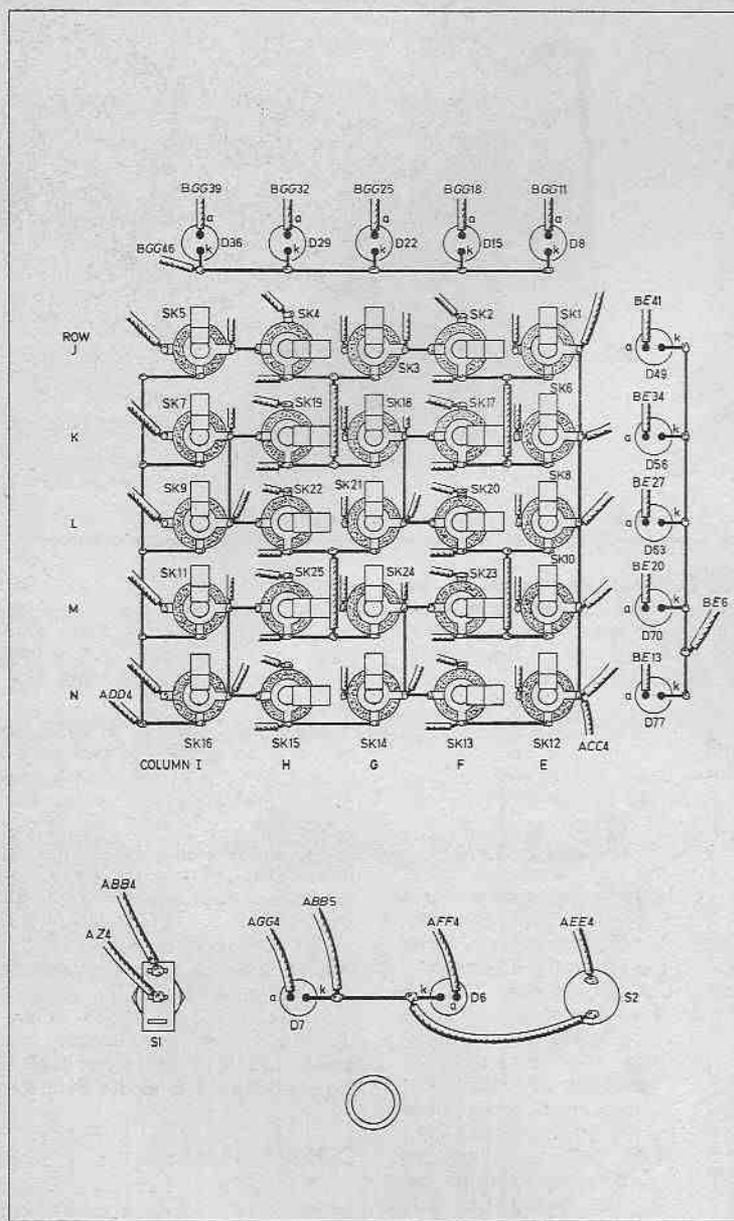


Fig. 9. Wiring of the rear of the front panel.

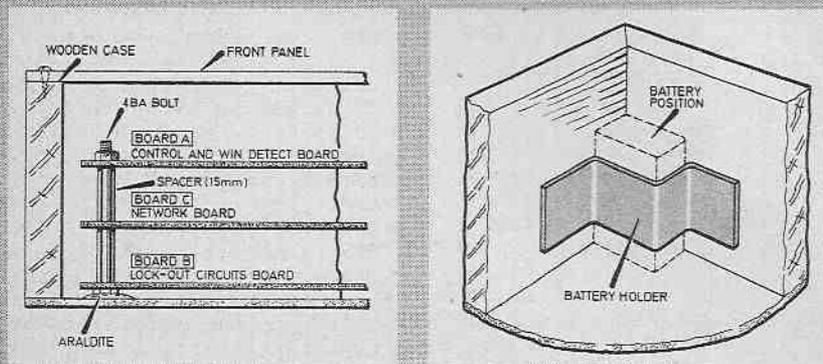


Fig. 10. Interior views of the cabinet. The diagram left, shows the circuit board mounting arrangement and the one on the right shows the battery mounting clip.

immediately that only half the board area is used. However making all circuit boards the same size, means that mounting them in the cabinet is a lot simpler and this is what has happened here.

Multi-way ribbon cable is used for front panel connections both on this board and the others as this makes lead identification much easier and keeps the wiring reasonably neat.

To make it easier to keep track of interboard wiring, a simple system of board location identification has been adopted. The first letter refers to the board itself, and the rest of the letters and numbers refer to the strip/hole co-ordinates of a particular location in the usual way.

For example location CAA17 refers to location AA17 on board C (the modelling network board).

The lock-out circuit board (Fig. 7) can be tackled next. Both row and column lock-out circuits are accommodated on the same piece of strip-board and apart from C2 are identical.

### NETWORK BOARD

Finally the network board can be assembled. A quick glance at Fig. 8 will confirm that this consists of a large number of separate small circuits each with two wires going to a socket on the front panel and one each to the appropriate row and column lock-out circuit.

Bus wires made up of thick gauge copper wire are mounted about 7mm clear of the board from one side to the other to provide common returns for the lock-out circuit board input lines. This can be seen clearly in the layout diagram.

You will see that plastic encapsulated BC108 transistors have been used in the prototype. The more familiar TO-18 types can be used instead but take care that their cans do not short circuit to other parts of the circuit.

Component identification is made very simple by the fact that all transistors, all resistors and all diodes are of the same type and value. On the other hand, lead out wires from each section should be made easily identifiable so that they can be connected to the correct socket on the front panel. Care must also be taken to get the polarities of circuits round the edge of the board correct.

### CABINET AND FRONT PANEL

In the prototype the cabinet (dimensions 200x130x70mm) was made up from 75x15mm (3x1/2 inch) softwood with a hardboard bottom.

The front panel is made up from a piece of 3mm coloured Perspex. Great care is needed in drilling this material and a hand powered drill is best. Red and blue lines are made

with coloured drafting tape and captions with rub on lettering protected by clear sticky tape.

The interior layout can be seen both in Fig. 9 and in the accompanying photographs. It is sensible to mark out and drill all the holes in the Perspex panel before mounting any components and it is also a good idea to check each jack socket. Some may need their contacts adjusting and this is easier to do before they are attached to the front panel.

A battery holder can also be made from a suitably shaped piece of plastic (or metal) and glued into position in one corner of the box (see Fig.10).

The completed circuit boards are mounted one above the other on three 4BA bolts which have been fixed with Araldite to the floor of the case. Spacers can be made up from old ball point pen cases.



Once interwiring between the boards is complete, they can be fixed in position using 4BA nuts, and wiring to the front panel completed. The unit is now ready for testing.

## BLUE AND RED

To complete and test the Dual Line Game a set of plugs (or pegs) is required, 12 for RED and 12 for BLUE.

The red pegs are made up from size 10 plastic knitting needles. A 25mm section of needle is cut and Araldited to a 7mm long section of 7mm diameter wooden dowel. The pegs are finished off by giving the top a couple of coats of red enamel.

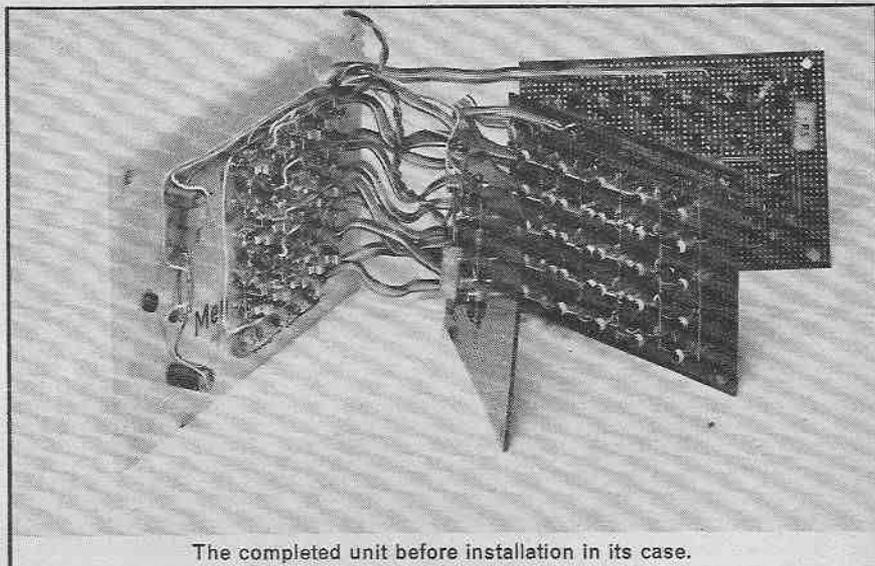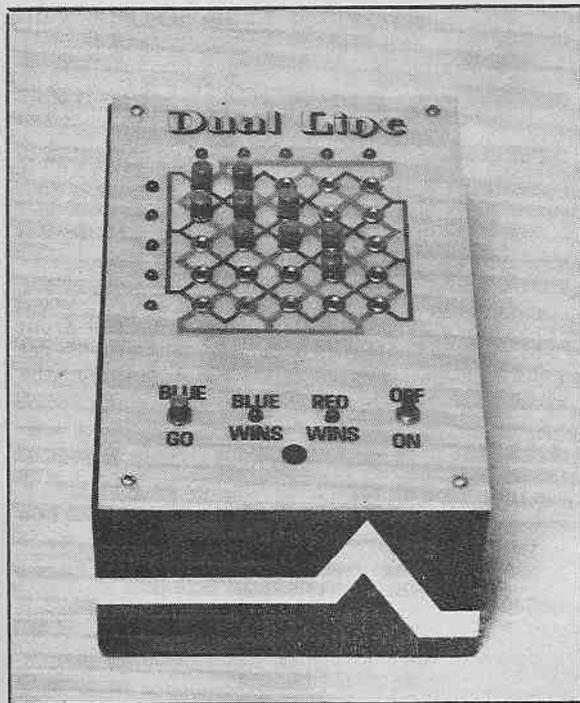The blue pegs are made up in a similar way, the only difference being



The completed unit before installation in its case.

that metal knitting needles should be used, sanded down to ensure a good contact in the sockets.

Testing and setting-up the equipment can now proceed.

## TESTING

When the circuit is first switched on it should draw about 10mA from a 9V battery and two l.e.d.s should be lit, one row and one column indicator. Pressing BLUE GO will cause the l.e.d.s to flash briefly, during which time current consumption will rise to about 25mA. A row and column l.e.d. will again be lit, probably different.

The 2.2 kilohm resistor on the modelling network board, board C, in circuit LG (R63) should now be increased in value (to about 3.3 kilohms) until every time BLUE GO is pressed D22 and D63 come on (no jack plugs should be in the board for this adjustment). This ensures that when the circuit is given the first go in a game it will choose the centre position which is the best first move.

Each position on the board can then be tested by forcing the machine to choose every position in turn. This is done by making a line of red pegs from top to bottom of the board, broken only at the point you wish the machine to choose.

Obviously, if the circuit is working correctly, it must choose to place its plug in the gap this being the only

move which can prevent immediate defeat. Any fault shown by this test must be traced back from the front panel to modelling network board to lock-out circuit board until the error is found.

After passing this test the machine is ready to challenge you to a game. If you give it the first move you can expect to lose the game on most occasions. (Only one line of play has been found that can defeat it when it has first move.) When you take first move it has less chance of winning, but will if you make a bad mistake.


The advantage of the first player can be reduced if it is agreed that the first move may not be in the centre position. Under these rules the machine cannot calculate its first move, but it plays rather well if it is give position MG as its first move.

## COMPONENTS

This circuit uses quite a large quantity of rather a small range of common components. For this reason it pays to shop around to find the best value. The advertisements in this magazine are a good place to start.

The semiconductors used in this circuit are not critical, any small signal silicon npn transistor will do instead of BC108 and any silicon pnp instead of BC557. The TIL220 and 1N4148 diodes may be replaced by any reasonable equivalent. It is not recommended that manufacturers "fall outs" be used in this circuit.

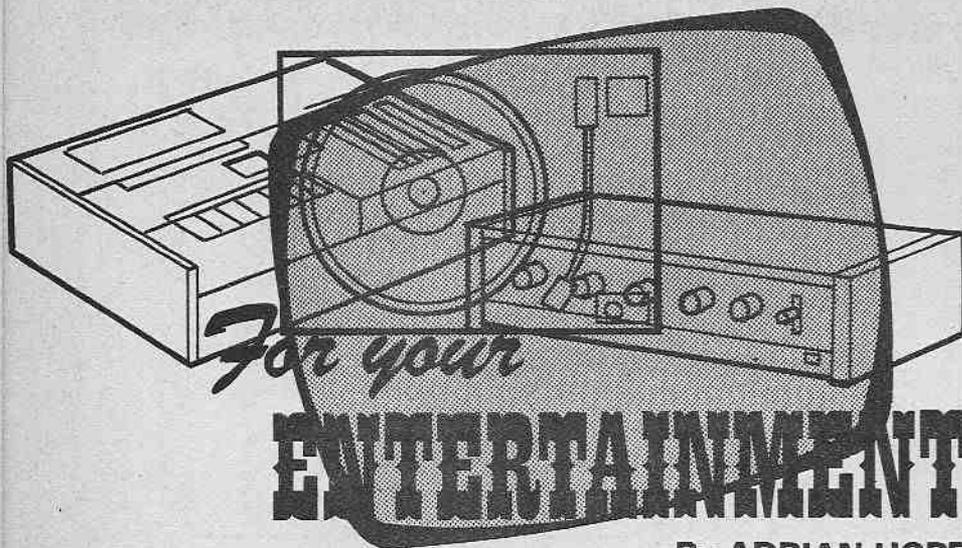This article has described an analogue electrical resistance network which calculates moves for a simple game. There are similar resistance analogues for some other games. The processing power of these and more complex networks containing inductors, capacitors and other elements are overlooked in these days of digital computers. □



By ADRIAN HOPE

### Protective Words

Specialists in any area tend to talk their own particular language. This is partly because it is all too easy for an "expert" in electronics, hi fi, video or computers to forget that others are less expert in that field. But it is also a defence mechanism: a protective moat of words to ward off critics.

It isn't just electronics specialists who talk in jargon. Professionals, such as doctors, solicitors and accountants are past masters at the art of staying "one up" by using long words understandable only to other professionals in the same field. (An animal vet once told me that a cat which licked off its fur had "chronic lick-titis"). Some shop assistants, especially in the electronics area, play exactly the same game, assuming that no one will want to risk losing face by admitting that they don't understand a technical term.

*Don't fall for it.* If you are being sold something, whether it's advice from a professional, education from an instructor or equipment from a shop, *you are entitled to understand what is being said.* If you don't understand a technical term when it's thrown at you, don't try and disguise the fact. Instead own up and ask for an explanation.

As often as not you'll find that those who use the most exotic technical terms, and gabble them the fastest, don't really understand what they mean. It is they who will be embarrassed, not you, if you ask for an explanation. If you don't believe me, try it just once when you are next shot a piece of jargon by an expert . . .

### Headphone Stereo

This train of thought was triggered by the realisation that it still isn't safe to write, even in the hi fi press, about "binaural" or "dummy head" stereo without also adding a brief explanation of what this technique involves. The idea of binaural stereo reproduction, which provides a very wide spread of sound from a two channel recording heard over headphones, dates back to the early part of the century and long before anyone succeeded in reproducing a stereo spread of sound from a pair of loudspeakers.

When you think about it, binaural recording is the obvious way to reproduce a

realistic all-round image of sound. In real life we hear sound from all around, and identify the direction of individual sounds, by listening with our two ears. The brain is able to decode subtle directional clues in the sound arriving at each ear because the size and shape of a human head introduces phase, time and level differences into similar sounds arriving at both ears.

In theory, if you put a microphone in each ear of a human stereo head and record sound picked up at each ear on a two channel stereo recording system you will capture an accurate replica of the original sound field. You can achieve a similar effect by building a dummy head of the same shape, size and mass as a human head.

For reproduction you simply feed sound from the left recorded channel into the left side of a pair of stereo headphones, and feed the sound from the right channel into the right headphone. This gives each ear the artificial equivalent of what the ears of the recording head heard. The brain then decodes the phase, time and level difference to produce a mental illusion of the original sound field.

You'll notice that I used the phrase "in theory". A binaural (two-eared) or dummy head stereo recording system can work remarkably well but it isn't quite as straightforward in practice as it sounds on paper.

A microphone, which is an electromechanical transducer and not flesh and bone, obviously can't accurately imitate the audio characteristic of the human inner ear, especially when it's fixed outside in the ear lobes. Likewise a headphone unit, which is another electromechanical transducer and is clamped over the outside of the ear lobe can't completely accurately mirror the sound of nature.

In practice the main audible short-coming of binaural sound reproduction is what has become known as "front back ambiguity". A sound recorded from the centre in front of the recording head may sound on replay as if it is coming from behind, and *vice versa*.

This is why many binaural recordings cheat a little by giving the listener an artificial fix on the sound field. For instance someone on the recording conveniently announces that they are "standing in front". It also has to be said that some binaural recordings are technically

much better than others in this respect and recordings that produce a good illusion of the sound field for one listener may not sound so realistic to another.

### Bad Image

Why hasn't binaural sound recording ever been a commercial success? In short it's anti-social and inconvenient to listen on headphones. So engineers soon lost interest in headphone stereo after they had devised a system of producing a stereo spread of sound from a pair of loudspeakers in a room.

Unfortunately a binaural stereo recording will not produce good stereo from loudspeakers. Moreover, a conventional stereo recording intended for loudspeaker reproduction (which in effect means virtually every commercially available recording) will not produce a true surround of sound when heard on headphones. In fact an ordinary stereo recording usually sounds as if it is coming from inside the listener's head when heard on headphones.

When a binaural recording is played over loudspeakers the stereo image is muzzy and diffuse unless the listener sits in just the right position so that only sound from the left speaker reaches the left ear and only sound from the right speaker reaches the right ear. In fact this neatly sums up the basic difference between the two types of stereo.

With binaural stereo the sound for each ear is at all times kept separate: for loudspeaker stereo the sound from the left and right channels mixes and blends in the room after it leaves the loudspeakers. This mix or blend is heard slightly differently by each ear of the listener and the slight differences produce an illusion of natural sound.

### Binaural Sounds

For anyone whose appetite has been whetted by this brief introduction to binaural sound, the BBC occasionally broadcasts a binaural programme and there are several binaural records on the market. But because many record shopkeepers haven't a clue what binaural is all about (another good example of disguised specialist ignorance) they will often file binaural under "quadraphonic" and recommend that the records need to be played on "special" reproduction equipment. In fact *all* you need is a stereo gramophone system and a pair of stereo headphones.

So where to buy binaural records? A good starting point is Quadramail, the Huntingdon based mail-order company which specialises in specialist discs and usually has a sales stand at major hi fi exhibitions. Also, part-time audio journalist Mick Skeet has produced a range of binaural EP discs which are available at £1.50 each (including postage) from Whitetower Music, 2, Roche Gardens, Bletchley, Milton Keynes MK3 6HR.

Some discs are far more worthwhile than others but if you like rock music I'd suggest AMC 705 (which features a semi-pro rock band called "Sinner") and if your musical tastes are more conservative I'd suggest AMC 704 (which on one side features some delightfully original organ and trumpet music recorded in a church).


# STEVENSON

## Electronic Components

### OPTO

LED's	0.125in.	0.2in.	each
Red	TIL209	TIL220	10p
Green	TIL211	TIL221	15p
Yellow	TIL213	TIL223	15p
Clips	3p	3p	
<b>DISPLAYS</b>			
DL704	0.3 in CC		130p
DL707	0.3 in CA		130p
FND500	0.5 in CC		100p

### SKTS

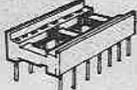

Low profile by Texas

8 pin	10p	18 pin	16p	24 pin	22p
14 pin	12p	20 pin	18p	28 pin	26p
16 pin	13p	22 pin	20p	40 pin	38p

3 lead T018 or T05 skt. 12p each.  
Soldercon pins: 100 for 60p.

### PCBS

#### VEROBOARD

Size in.	0.1in.	0.15in.	Vero Cutter 110p.
2.5 x 1	16p		
2.5 x 3.75	52p	45p	
2.5 x 5	60p	55p	Pin insertion tool 150p.
3.75 x 5	70p	70p	
3.75 x 17	250p	210p	

SS pins/100 45p 45p  
Fibreglass board: 80p each.  
Alfac - 33p per sheet.

### RESISTORS

Carbon film resistors. High Stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix: each 100+ 1000+

0.25W 1p 0.9p 0.85p  
0.5W 2p 1.5p 1.3p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £8.50. 0.25W £5.30.

**METAL FILM RESISTORS**  
very high stability, low noise rated at 1/4W 1%. Available from 51 ohms to 330k in E24 series. Any mix:

each 100+ 1000+  
0.25W 4p 3.7p 3.5p

**POTENTIOMETERS**  
Preset vertical or horizontal 100 ohms - 1M 6p  
Rotary 5K-2M2 Log or Lin single 30p  
Rotary 5K-2M2 Log or Lin double 90p  
Slide 60mm travel 5k-500k Log or Lin, single 60p  
Suitable knobs for above with coloured caps in red, blue, green, grey, yellow and black. Rotary controls 16p each. Slide type 12p each.

### MISC.

Murata Ultrasonic Transducers	350p pair
64mm 8 ohm speakers	100p each
64mm 64 ohm speakers	100p each
SRB 17W soldering iron	430p each
Reel of 22SWG solder (39.6m)	320p each
Desoldering tool	510p each
Precision screwdriver set	170p each
Titan Electric drill	1095p each
Miniature 606 and 909 at 100mA transformers	110p each

### SWITCHES

<b>TOGGLE</b>		
Standard	SPST 36p	DPDT 50p
Miniature	SPDT 75p	DPDT 85p
Subminiature	SPST 58p	DPDT 78p
<b>SLIDE</b>		
Standard		DPDT 17p
Miniature		DPDT 16p
<b>ROCKER (10A rating)</b>		
SPST 34p each.	SPST	46p each.
<b>ROTARY</b>		
1P12W, 2P6W, 4P3W or 3P4W		51p each
Key operated DPDT (Yale key)		395p each
<b>PUSH</b>		
Non locking - push to make		16p each
- push to break		22p each
Locking - SPST		75p each
- DPDT		100p each

### REGULATORS

100mA +ve	1A +ve	1A -ve
LM309K 140p	LM317T 220p	LM323K 480p
78L05 30p	7805 70p	7905 85p
78L12 30p	7812 70p	7912 85p
78L15 30p	7815 70p	7915 85p

### TRANSISTORS

AC127 22p	BC548 11p	TIP32C 60p
AC128 22p	BCY71 16p	TIP2955 66p
AC176 22p	BCY72 16p	TIP3055 53p
AD161 40p	BD131 40p	ZTX107 12p
AD162 40p	BD132 40p	ZTX108 12p
BC107 12p	BD139 33p	ZTX300 14p
BC108 10p	BD140 33p	ZTX500 15p
BC108C 12p	BFY50 23p	2N3053 25p
BC109 12p	BFY51 23p	2N3054 56p
BC109C 12p	BFY52 23p	2N3055 50p
BC147 9p	MJ2955 100p	2N3702 9p
BC148 9p	MPSA06 16p	2N3704 9p
BC177 16p	MPSA66 16p	2N3819 20p
BC178 16p	TIP29C 60p	2N3906 10p
BC182 10p	TIP30C 48p	2N3906 10p
BC182L 10p	TIP31C 50p	2N5459 33p
BC184 10p		2N5777 50p
BC184L 10p	1N914 4p	1N4006 7p
BC212 10p	1N4148 3p	1N5401 14p
BC212L 10p	1N4002 5p	BZY88ser. 8p
BC214L 10p	1N4148	£1.50 per 100.

### CAPACITORS

**POLYSTYRENE**  
High quality foil type. 63V working, 5% tol.  
22pf to 100pf 7p each  
1500pf to 0.01uF 9p each

**TANTALUM BEAD**  
0.1, 0.15, 0.22, 0.33, 0.47, 0.68  
1 & 2.2uF @ 35V 10p each  
4.7, 6.8, 10uF @ 25V 18p each  
22 @ 16V, 47 @ 6V, 100 @ 3V 22p each

**MYLAR**  
0.001, 0.01, 0.022, 0.033, 0.047 4p each  
0.068, 0.1 5p each

**POLYESTER**  
Mullard C280 series  
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1 6p ea.  
0.15, 0.22 8p each  
0.33, 0.47 12p each  
0.68 17p each  
1.0uF 22p each

**CERAMIC**  
Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p each

**MINIATURE TRIMMERS**  
Miniature film type, in 1.4pF - 5pF, 2pF - 22pF, 2pF - 22pF, 2pF - 10pF, 5.5pF - 65pF. 22p each

**RADIAL LEAD ELECTROLYTICS**


63V	0.47	1.0	2.2	4.7	10	6p each
						8p each
						16p each
						20p each
25V	10	22	33	47		6p each
						8p each
						12p each
						18p each
						28p each

### PACKS

Specially developed packs intended for development work.

1/4W CF resistor, 10 each value E12 series 4.7 ohm to 1 Megohm (650 total) 530p each  
1/4W CF resistor, 10 each value E12 series 4.7 ohm to 1 Megohm (650 total) 850p each  
1/4W MF 1% resistor, 10 each value E24 series 51 ohms to 330k (930) 2950p each  
Preset potentiometers 5 each value from 100 ohms to 1 Megohm (65) 390p each  
Polyester capacitors 5 each value 0.01 to 2.2uF (70) 690p each  
Ceramic plate capacitors 10 each value 22pF to 0.01uF (310) 575p each

### CONNECTORS

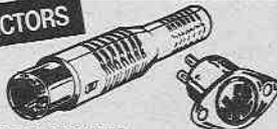

**DIN PLUGS AND SOCKETS**

plug	chassis socket	line socket
2 pin	8p	12p
3 pin	12p	12p
5 pin 180°	12p	17p
5 pin 240°	14p	22p

**JACK PLUGS AND SOCKETS**

	unscreened	screened	socket
2.5mm	10p	15p	8p
3.5mm	10p	16p	9p
Standard	16p	30p	19p
Stereo	23p	39p	22p

**1mm PLUGS AND SOCKETS**  
Suitable for low voltage circuits, Red & Black. Plugs: 7p each. Sockets: 8p each.

**4mm PLUGS AND SOCKETS**  
Available in blue, black, green, brown, red, white and yellow. Plugs: 12p each. Sockets: 13p each.

### CMOS

4000 20p	4023 20p	4054 120p	4502 120p
4001 20p	4024 50p	4060 120p	4507 60p
4002 20p	4025 20p	4063 120p	4508 330p
4006 90p	4026 160p	4066 60p	4510 80p
4007 20p	4027 45p	4068 20p	4511 90p
4008 95p	4028 85p	4069 20p	4512 80p
4011 30p	4029 85p	4070 20p	4516 80p
4012 20p	4031 220p	4071 20p	4518 80p
4013 35p	4033 150p	4072 20p	4520 80p
4014 80p	4036 350p	4073 20p	4527 90p
4015 80p	4039 300p	4075 20p	4528 90p
4016 30p	4040 110p	4076 90p	4529 150p
4017 65p	4041 85p	4077 20p	4531 150p
4018 90p	4042 80p	4078 20p	4532 130p
4020 100p	4043 95p	4081 20p	4538 160p
4022 100p	4046 110p	4082 20p	4543 110p
	4048 60p	4086 75p	4566 170p
	4049 45p	4093 60p	4558 120p
	4050 45p	4095 110p	4589 420p
	4051 70p	4098 120p	4591 330p
	4053 80p	4501 20p	4585 110p

### LSTTL

74LS00 16p	74LS47 80p	74LS126 45p	74LS175 90p
74LS01 22p	74LS48 90p	74LS132 80p	74LS190 90p
74LS02 16p	74LS54 22p	74LS136 50p	74LS191 90p
74LS03 22p	74LS73 35p	74LS138 75p	74LS192 90p
74LS04 16p	74LS74 35p	74LS139 75p	74LS193 90p
74LS08 22p	74LS75 40p	74LS151 60p	74LS195 90p
74LS10 22p	74LS76 40p	74LS155 65p	74LS196 90p
74LS13 38p	74LS78 45p	74LS156 80p	74LS197 85p
74LS14 65p	74LS83 68p	74LS157 70p	74LS221 100p
74LS16 22p	74LS85 85p	74LS158 65p	74LS251 70p
74LS17 22p	74LS86 40p	74LS160 75p	74LS266 35p
74LS21 22p	74LS90 40p	74LS161 60p	74LS290 80p
74LS22 28p	74LS93 55p	74LS162 80p	74LS365 55p
74LS27 28p	74LS95 65p	74LS163 80p	74LS366 55p
74LS30 22p	74LS107 45p	74LS164 80p	74LS367 55p
74LS32 30p	74LS114 40p	74LS165 80p	74LS368 55p
74LS37 40p	74LS123 80p	74LS173 135p	74LS369 50p
74LS42 60p	74LS125 45p	74LS174 95p	74LS670 200p

### TTL

7400 12p	7442 40p	7493 30p	74157 40p
7402 12p	7445 50p	7496 38p	74164 55p
7404 14p	7447 50p	74121 28p	74165 55p
7408 16p	7448 48p	74123 40p	74174 55p
7410 14p	7473 23p	74125 38p	74177 50p
7413 24p	7474 23p	74126 38p	74190 50p
7414 39p	7475 28p	74132 48p	74191 50p
7420 14p	7476 28p	74141 48p	74192 50p
7427 22p	7485 55p	74145 48p	74193 50p
7432 18p	7486 18p	74148 90p	74194 50p
	7490 30p	74150 55p	74196 50p
	7492 30p	74154 68p	74197 50p

### LINEAR

709 40p	LM10 400p	LM3909 72p	TBA800 80p
741 18p	LM301A 30p	LM3914 280p	TBA810S 110p
747 50p	LM308 70p	LM3915 280p	TA1008 350p
748 35p	LM318 85p	LM3911 160p	TD A1022 630p
7106 850p	LM324 52p	LM3911 120p	TD A1024 120p
AY-10212 660p	LM330 80p	MM57160 650p	TD A2020 360p
CA3046 70p	LM330 80p	LM1458 40p	TL071 75p
CA3080 75p	LM332 140p	LM1830 180p	TL072 135p
CA3130 90p	LM338 120p	MC3340P 135p	TL074 200p
CA3140 50p	LM338 200p	MC3360P 135p	TL081 45p
CA3209 820p	LM338 90p	MM57160 650p	TL082 125p
ICM7555 100p	LM338 90p	NE555 23p	TL170 60p
ICM7556 POA	LM338 120p	NE556 60p	XR2206 390p
LF347 135p	LM339 100p	NE568 120p	XR2207 450p
LF351 45p	LM339 100p	NE567 120p	ZN414 80p
LF353 85p	LM391 170p	NE570 420p	ZN419 POA
LF355 92p	LM1310 140p	NE571 460p	ZN424 150p
LF356 95p	LM2917 280p	NEB37 POA	ZN425E 420p
LF357 92p	LM2924 160p	RC4136 100p	ZN460 360p
	SAD1024 1310p	SN76477 230p	ZN1034 230p

### MICRO

2112 220p	CPU's 6800 650p	SUPPORT 6810 350p
2114LP 420p	8080A 610p	6821 600p
4116 620p	Z80 1090p	6850 550p
2708 680p		AY5-1013 370p
2716 1980p		

We now offer one of the widest range of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Road, Bromley, from Mon - Sat, 9am - 6pm (8pm on Wed and Fridays). Special offers always available. We also provide an express telephone order service. Telephone orders received before 5pm are shipped same day.

**TELEPHONE ORDERS: 01-464 2951/5770.**

Details of our entire range of components are contained in our new 1980/81 catalogue containing over 100 illustrated pages. Price 50p includes postage (& 50p voucher). Prices VAT inclusive.



Please add 50p carriage on orders under £15. Official orders welcome.

Mail orders to: STEVENSON (Dept EE)

# 76 College Road, Bromley, Kent BR1 1DE.



# Everyday News

"Contrariwise," continued Tweedle-dee, "if it was so, it might be; if it were so, it would be; but as it isn't it aint. That's logic!"

Try asking the man in the street what he knows about the silicon chip and you may end up feeling like Alice. Indeed the very mention of the "mighty-micro" will probably cause his eyes to glaze over and conjure up visions of Star Trek and a certain Italian car commercial.

## In the Home

In fact the microprocessor is more commonly used than we think although you wouldn't really know unless you looked closely. The Daily Mail Ideal Home Exhibition held last month at Earls Court gave ample opportunity to seek out examples of the "new technology" applied around the home—and we do mean seek out, despite what you may have been led to believe by pre-show publicity.

It is clearly evident from the exhibition that domestic appliance manufacturers seem notoriously slow in adopting new ideas. It's true that the odd one or two washing machines, cookers and sewing machines use microprocessor control, but we are still a long way off complete electronic control—strange, when it is cheaper and more reliable than equivalent electromechanical systems. Perhaps it's not a strong selling point.


Quartz watches are now being produced in China for the growing world market. They use a Japanese electronic assembly but the cases are made locally.

## GOLD RUSH


Electronic component manufacturers have been rushing ahead with gold surcharges following the huge lift in world gold prices. First in the field was RCA with a gold surcharge, quickly followed by TI, Fairchild and National.

Gold is used extensively in semiconductors, thick and thin film microcircuits, and edge connectors. Surcharges can be as little as 0.3p for a simple low-cost plastic packaged device but as much as 50p for a complex ceramic assembly.


## AN IDEAL HOME FOR CHIPS

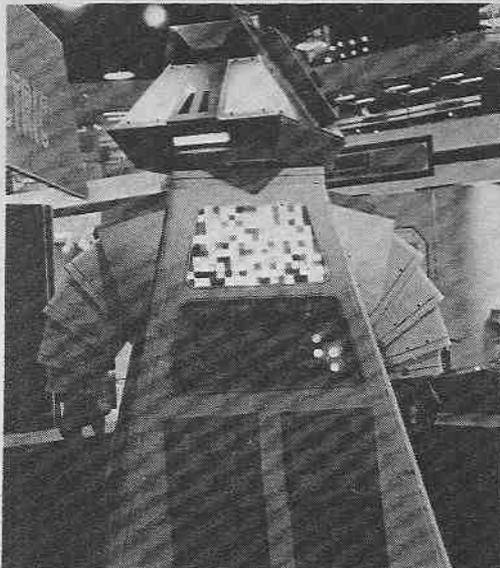

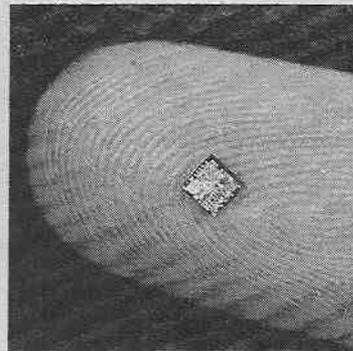Choose Electric says Fred the talking robot on the Electric Council Stand



This is a silicon "chip"

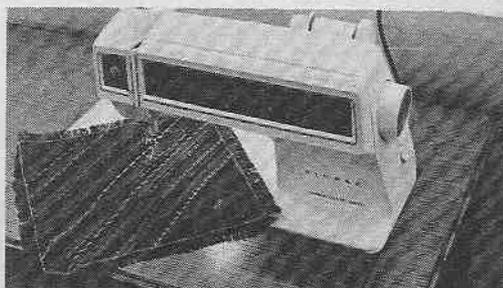

Singer Futura 2001 touch sensitive machine



Creda Carefree Electronic Cooker

The one exception to this was Plessey Ltd. Their whole stand was devoted to silicon chip technology and many devices one would expect in the Ideal Home of the '80s were on display. These included a new infra-red remote controlled slide projector, a heat sensitive

hair dryer and a special set-up designed to illustrate silicon chip manufacturing techniques.

So perhaps next year we can look forward to a true Ideal Home of the future.

## Fly Electric

A new concept in aviation is the all-electric plane proposed by research engineers in Lockheed. It would still use aviation fuel for propulsion but would substitute very efficient electric generators and motors for the present hydraulic systems.

This, says Lockheed, would use less overall power and reduce fire risk because an all-electric system would be lighter and hydraulic fluid is prone to ignition.

Reduction in fuel consumption, first costs and maintenance costs over the lifetime of a medium-sized transport aircraft could be as much as £50 million. Electronic solid state control would be an essential feature in any new design.

## Colour Blind

Advice for the component manufacturer for selecting suitable colours for marking resistors and capacitors is the subject of the new British Standard BS5890 "Guide for the Choice of Colours to be used for the Marking of Capacitors and Resistors." Price £1.20.

The object of the new standard is to reduce errors or misunderstandings which may result from improper selection or interpretation of colours.



## Exhibition

"Hands on Experience" is the title of a series of new exhibitions currently being planned by Eurofairs to appear throughout the country, commencing in Bristol on 27 to 29 June.

The exhibitions aim to introduce the latest home computers, electronic games and remote control equipment/models to potential buyers. For further details write to Eurofairs, 9 Park Place, Clifton, Bristol BS8 1JP.

## Inta-Stella Encounters

Scientists working on high energy physics are sending each other scientific data through the European OTS communications satellite.

The new scientific data network is called Stella and it enables participating laboratories to exchange data with high accuracy at a rate of a million bits of information a second. This is roughly the same speed as a scientific computer and will obviate the long delays of sending magnetic tapes by post.

Stella will link the Rutherford Laboratory in the UK with other laboratories in Germany, France, Italy, Austria and Ireland.

## CB FINES

In 1979 there were 78 prosecutions for illegal use of CB Radio with another 56

cases pending. This compares with only three prosecutions in 1978 and four in 1977.

The Irish Republic, reversing an earlier decision, is now to legalise CB but the waveband to be used is still in question.

## COMPSTAT '80

The fourth Symposium on Computational Statistics, COMPSTAT '80, is being held at University of Edinburgh from 18 to 22 August.

Papers will include reviews of current methodology as well as descriptions of recent research on new techniques and software. An exhibition featuring the main statistical packages, computational aids and microprocessors is also planned, including "hands on" demonstrations.

Since Compstat '80 coincides with the first week of the Edinburgh Festival accommodation is obviously going to be limited and anyone interested in attending is advised to register early.

Further information and registration forms can be obtained from Compstat 80, Program Library Unit (Dept EE), University of Edinburgh, 18 Buccleuch Place, Edinburgh EH8 9LN.

## Video Pirating

Illegal recording which has cost the audio industry millions of pounds is now worrying the video com-

## On-Line Computers

A computer-controlled voice and data radio link is to be introduced on the St. Pancras-Bedford line of British Rail. It is being supplied under a £750,000 contract by Ultra Electronics and the German company AEG-Telefunken.

London Transport has invested in two extra Honeywell computers for control of times, routes and frequencies of trains to Cockfosters.

## Carfax

Some 450 cars fitted with radios adapted for the BBC's Carfax motoring information service should be on the road by the end of June. The service is only in its trials stages but if proved successful later this year the go-ahead will be given for car radio manufacturers to produce equipment.

Motorists can stay tuned to Carfax or listen to other programmes with Carfax automatically overriding the programme whenever there is a motoring announcement. Additional cost to the motorist for a Carfax radio is expected to be in the region of £5 to £20.

## Credit Card Petrol

A pilot experimental scheme in the Norwich area allows motorists to pay for their petrol at the pump by direct debit using their Barclay cards. The service is available at a number of Esso garages.

Automatic funds transfer is the basis of the cashless society which reduces "mugging" and the risk of robbery where there are large concentrations of cash.

panies who are now researching encoding systems which will make it difficult or impossible to copy a video recording successfully on a home recorder.

## Cheap Video

Japanese researchers are reported to be active in developing techniques to enable digital video signals to be recorded on a standard audio cassette although the tape may need to be of special type.

## ANALYSIS

### HOT STUFF

We know now that the electromagnetic spectrum is enormous extending from wavelengths of 100km at the low frequency end up to mere fractions of a micrometre (10<sup>-6</sup> metre). Visible light is only a small part of the spectrum with wavelengths between 0.4 and 0.8 micrometres (i.e. 750-375GHz in frequency).

During this century, scientists and inventors have managed to exploit the whole of the spectrum in various applications. At the low frequency end for terrestrial communications, long wave, medium wave, short wave radio in the first quarter of the century, gradually extending up to v.h.f., u.h.f. and microwaves which gave us more communication channels including television, plus radar and a number of navigational aids as well as satellite communications. At the frequencies higher than the visible spectrum, X-rays and gamma rays are used extensively in medicine and industry.

Either side of the visible spectrum are the infra red and ultra-violet which also have medical, industrial and military applications.

It is the infra red region which has attracted so much research in the past twenty years. Most people don't realise that any and all objects emit radiation in the infra red region, the amount depending on temperature. Even as you are reading these words you are unconsciously radiating infra red rays, as indeed are all the objects around you.

Such emissions can be detected with an infra red sensor and by scanning a scene it is possible to build up, point-by-point an infra red "picture" and, by electronics, convert it to a visible picture. The process is known as thermal imaging.

Who would want to use infra red imaging? More than at first appears. In medicine an infra red picture will show up incipient breast cancer because a tumour has a higher temperature than the surrounding tissue. Point an infra red camera at high voltage power lines and you can pick out instantly the hot spots that could lead to breakdown, and without climbing the pylon.

An infra red sensor is a good intruder alarm, sensing the heat of a body against a less hot background. In air-sea rescue the body in the water shows up plainly against the cooler background of the sea. An overflight of a housing estate will show which houses have roof insulation and which haven't. Fire brigades can locate the seat of a fire in a building even though inaccessible and obscured by smoke.

Obscured by smoke! This is the clue that leads up to the reason why infra red imaging is a top military priority. Infra red operates through cloud, smoke, camouflage and in dark shadow. Ordinary TV can't do this.

Brian G. Peck

..... AND NOW AN ELECTRIFYING NUMBER FROM EE  
BY STEVE BEECHING



**T**HE UNIT to be described here was originally designed with a factory background music system in mind to provide voice-operated paging which overrides the music, when calling the required personnel.

This Auto Fade Unit can also be used by a DJ with a disco system to provide voice announcements over the music. The unit has provisions for stereo music and a mono microphone, where the speech can be switched into both channels at once. There is no problem in using a mono system, one input being left unconnected.

The unit cannot really be used as a simple voice-operated switch, for example in transmitter applications, as there is no relay in the circuit to switch external power

circuitry. Nevertheless the unit can be considered versatile and no doubt be used for other applications to those originally intended.

### CIRCUIT DESCRIPTION

The full circuit of the Auto Fade Unit is shown in Fig. 1. The actual switching between music and speech is provided by IC4a to IC4d, a CD4016 quad bilateral switch CMOS i.c. Normally, in the off condition there is a very high resistance between input and output of each switch for example IC4a. Here, between input, pin 1 and output, pin 2 there is a resistance of approximately 10M $\Omega$ . The control terminal for this gate is pin 13, which is normally low when the switch is considered to be off.

The remaining three switches operate in a similar manner. When the control input is taken high the switch is turned on and a low resistance appears between input and output, this being about 300 ohms.

In the normal rest state the control inputs to gates IC4a and IC4b are high, thus the switches are on and the music is able to pass straight through to the output.

The remaining two gates, IC4c and IC4d have their respective inputs connected together to which the speech signal is applied. Their outputs, pins 9 and 10 are connected to the LEFT and RIGHT channels respectively. Thus when these gates are turned on speech is applied to both channels at the same time. In the normal rest state the control inputs are low.

### AMPLIFIER

An LM382 dual amplifier is used in two stages as a microphone amplifier with a gain of about 20dB. The first stage consisting of IC2a amplifies the low level signal from the microphone to a sufficient level so that it can pass through the remaining stages with little attenuation. A proportion of this signal is tapped off by the TRIGGER LEVEL control, VR1 and applied to the second stage, IC2b.

The second stage provides a high gain limiting action, amplifying the signal to a more than sufficient level for applying to the d.c. rectifying circuit. The rectifying circuit comprising R4, D1, D2 and C8 provides a d.c. switching level which is used to change the states of IC3a and IC3b.

Normally pin 3 is high, and pin 4 low. We thus have the required conditions applied to the switches to enable them to assume the states mentioned earlier.

When speech is applied through the various stages, the d.c. level causes the high condition at pin 3 of IC3a to go low, thus turning off the music, and the low condition at pin of IC3b to go high thus turning on the speech enabling the speech to be connected through to the output.

When there is no further speech, there is a delay of about half a second before the circuit reverts back to its original state and the music is once more able to pass through.

Power for the unit is provided by two batteries giving 18V. A 15V regulator i.c., IC1 is then used to provide a stable 15V supply to the circuit.




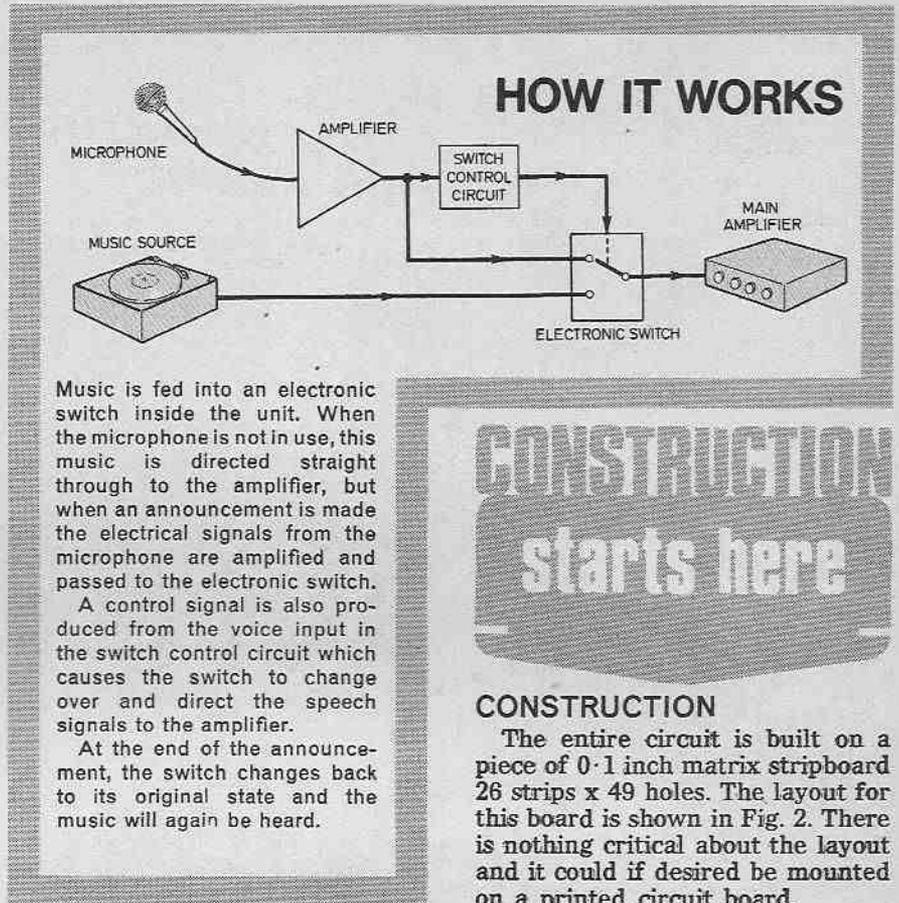
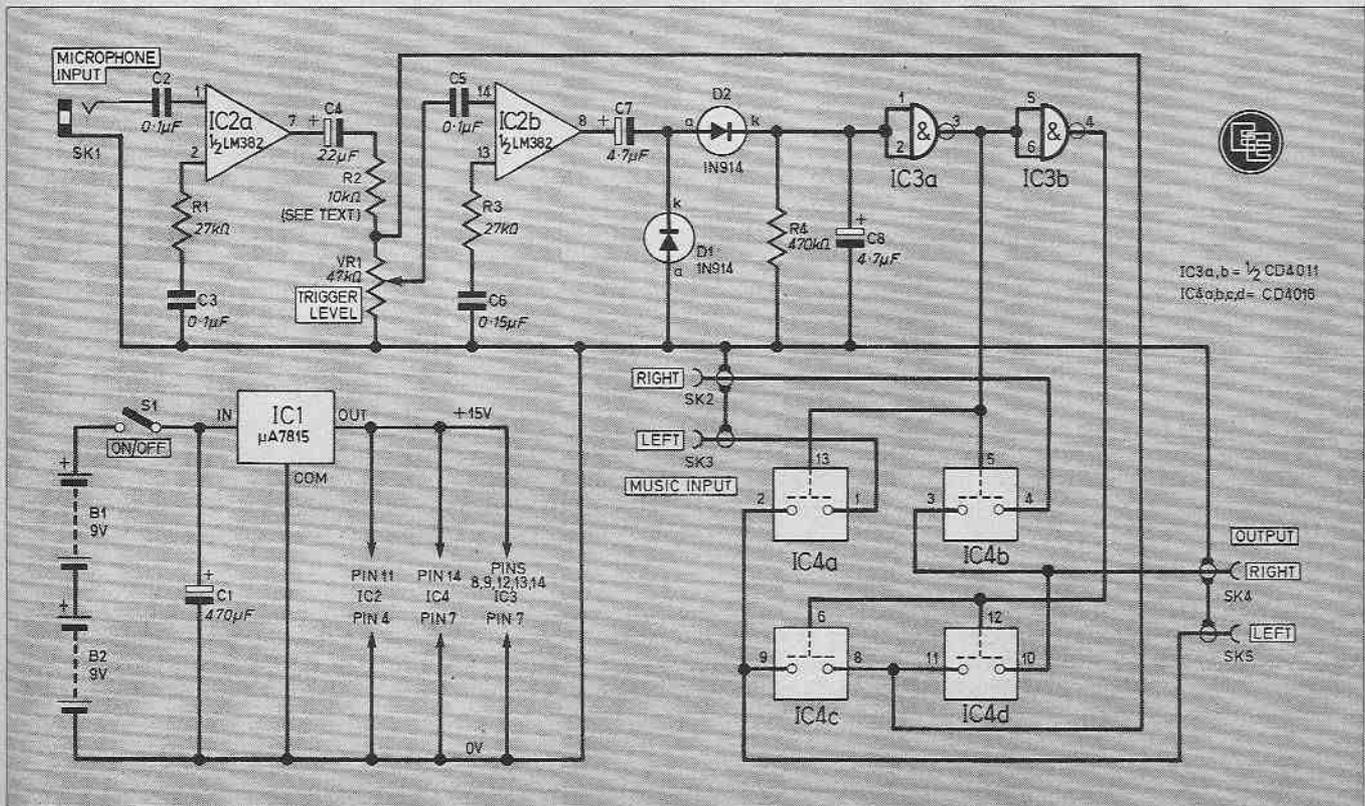


Fig. 1. Complete circuit diagram of the Auto Fade Unit.

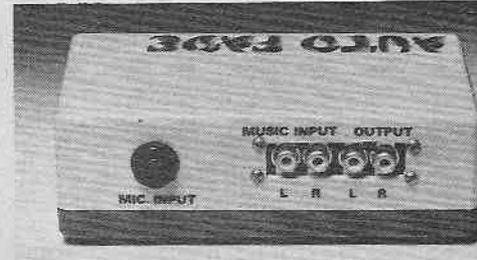

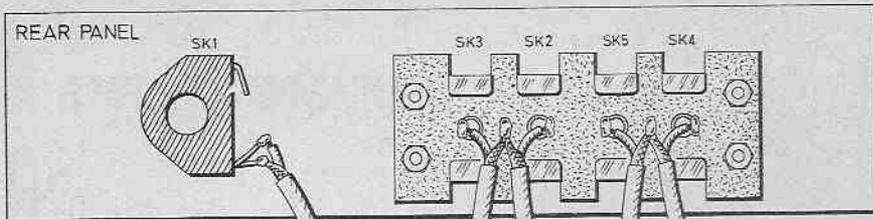

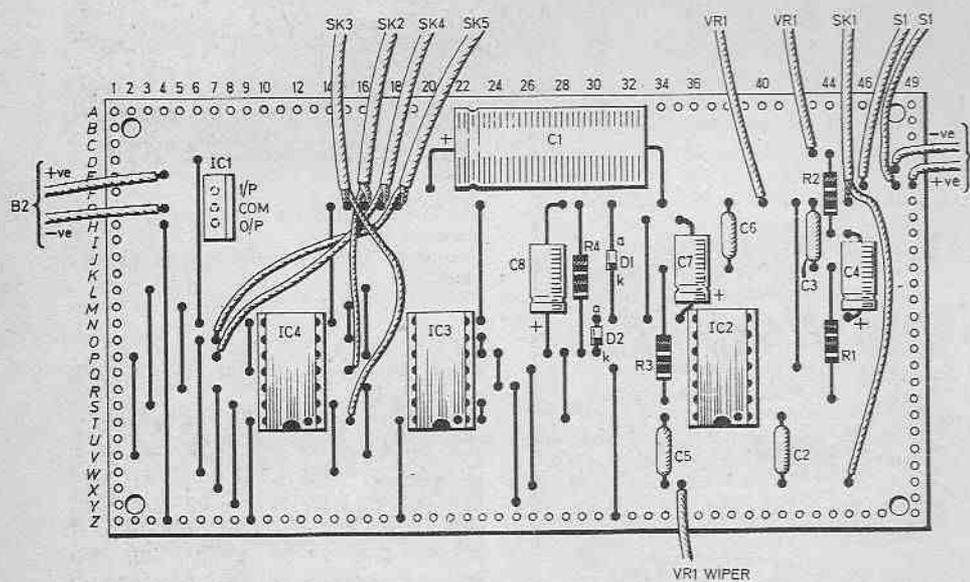
Rear view of the unit showing the phono socket strip and mic. input jack socket.



Also shown in this diagram is the front and rear panel wiring details. The case used was a small Verobox type 65-2520J, with dimensions of 150 x 80 x 50mm, although any similar size case can be used. It does not have to be metal to provide screening for the circuit.

Remember to observe the usual precautions when handling the CMOS i.c.s. Sockets were used in the prototype, but providing you are fairly swift with a soldering iron, they could be dispensed with.

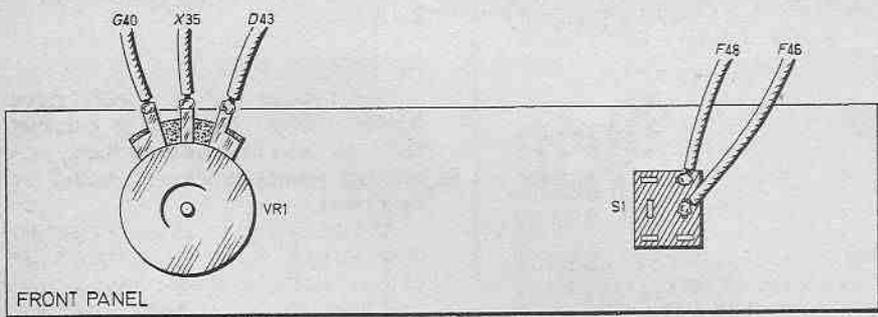Screened lead is used for the input and output sockets. It is not advisable to use ordinary connecting wire as there is a possibility of hum appearing. This is especially true of the input.



### TESTING

After assembly is complete, it is a good idea to check over for errors, particularly because of the large number of link wires. It is easy to miss one or two. If all seems well the batteries may be connected and the unit switched on. If possible check with a voltmeter that 15V appears across the supply.

Connect a mono audio source to one channel of the music inputs and connect the corresponding output to an amplifier. If the circuit is functioning correctly the audio will pass through with little or no attenuation. Do the same with the other channel.

Now connect a microphone to the SPEECH input, start with the trigger level control fully anti-clockwise and slowly rotate it clockwise until a point is reached where the circuit switches, and the speech appears across the output. You may find that after speech is removed the circuit tends to oscillate very slowly, not switching off cleanly. If this happens, it is probable that VR1 is



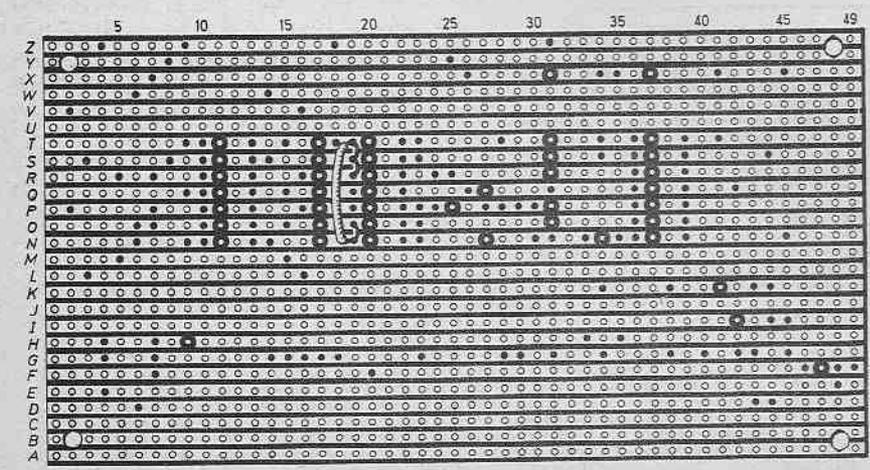


Fig. 2. Complete wiring details for the Auto Fade Unit. Be extra careful when wiring the links, as a mistake will be difficult to trace later on. Note the four links on underside.

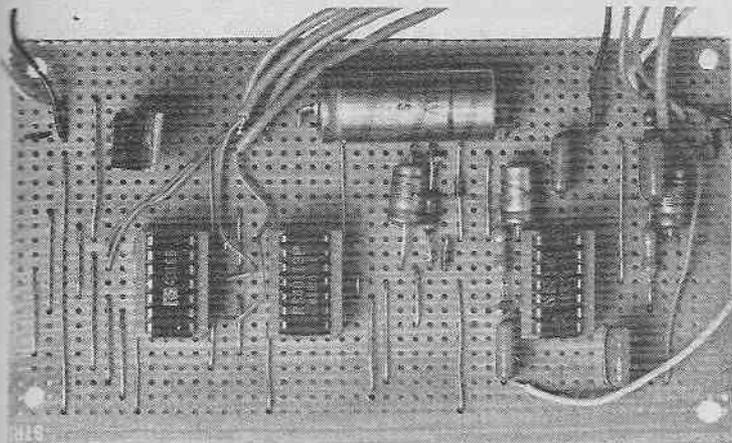

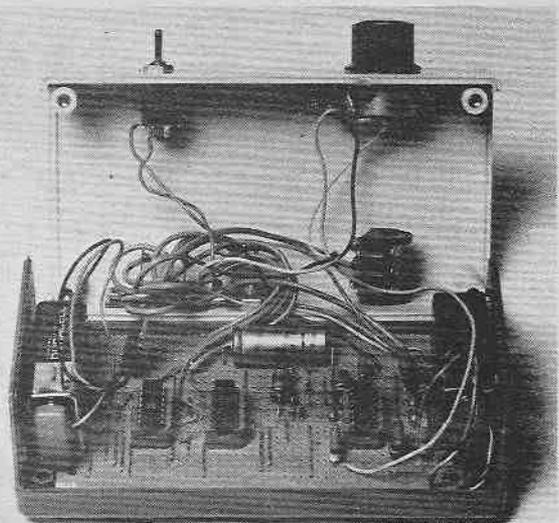Layout of components on the completed circuit board for the Auto Fade. We strongly recommend the use of i.c. sockets as the i.c.s can easily be damaged during soldering.



The completed Auto Fade with top cover removed.

Note the careful positioning of the two batteries.

## COMPONENTS



### Resistors

- R1 27k $\Omega$
- R2 10k $\Omega$
- R3 27k $\Omega$
- R4 470k $\Omega$
- All  $\frac{1}{4}$ W carbon  $\pm 5\%$

### Capacitors

- C1 470 $\mu$ F 18V elect.
- C2 0.1 $\mu$ F polyester
- C3 0.1 $\mu$ F polyester
- C4 22 $\mu$ F 18V elect.
- C5 0.1 $\mu$ F polyester
- C6 0.15 $\mu$ F polyester
- C7 4.7 $\mu$ F 18V elect.
- C8 4.7 $\mu$ F 18V elect.

### Potentiometer

- VR1 47k $\Omega$  lin. carbon

### Semiconductors

- IC1  $\mu$ A7815 15V voltage regulator
- IC2 LM382 dual preamplifier
- IC3 CD4011 quad 2-input NAND gate
- IC4 CD4016 CMOS quad bilateral switch
- D1,2 1N914 silicon diode (2 off)

### Miscellaneous

- S1 miniature single-pole toggle
- B1,2 9V PP3 battery (2 off)
- SK1 standard jack socket
- SK2-SK5 phono sockets (4 off)
- Stripboard 0.1 inch matrix 26 strips  $\times$  49 holes; Verobox type 65-2520J 150  $\times$  80  $\times$  50mm or similar size case; 14 pin i.c. sockets (3 off); small knob; miniature screened cable; stranded connecting wire.

COMPONENTS  
approximate  
cost **£7**  
excluding case

See  
**Shop  
Talk**  
page 323

set too high or that the value of R4 is too high. Rotate VR1 until the circuit switches off. This must be done slowly. Then recheck that, with speech applied, the circuit switches.

At this stage you may notice that the microphone signal is somewhat larger than the music signal. If this is the case then the value of R2 should be increased

until the two signal levels are roughly the same.

If the tests are satisfactory the unit is then ready for use. Remember though that the level control is only adjusted for that one particular microphone, if others are to be used then the control needs to be readjusted each time.


### IN USE

The reader will probably have his own ideas on how to connect the unit into an audio system, one or two points however should be observed.

As the unit is in effect a change-over switch, both the microphone output and the music source output should be suitable for the same amplifier input. This means that if for example a magnetic cartridge is used, it will need some form of pre-amp and equalisation before being fed into the auto-fade unit.

The diagram of Fig. 3 shows one suggested arrangement.  $\square$

Fig. 3. Example of how to connect the unit into an audio system. This is for guidance only—there will probably be variations with the equipment used.

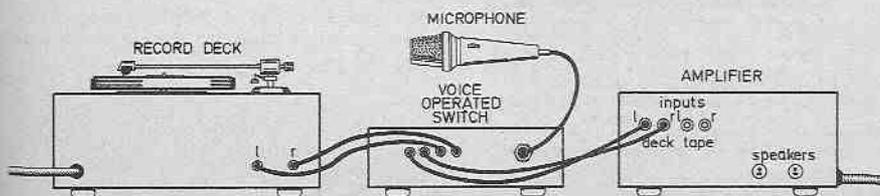

The completed Auto Fade ready for use.



**B**OTH the *Burglar Alarm Module* and *Opto Alarm* projects earlier in this series have utilised a miniature audible warning device as the alarm tone generators. Being solid state, these units have the advantage of low current consumption (about 15mA) as well as small size when compared with electromechanical buzzers.

The project described here is a two-transistor circuit which produces an alarm tone via a miniature 8 ohm loudspeaker. It can be used in place of the audible warning device mentioned above.

The Audible Tone Generator is easily constructed from readily available parts and is ideal for beginners. This device incorporates a preset control enabling the frequency of the tone to be varied to a certain extent.

It can be used in any project which operates from a 9 volt rail; 12 volts must be considered the absolute maximum supply voltage for the unit. Being a direct replacement for the audible warning device described earlier, this unit also draws in the region of 15 to 20mA.

## CIRCUIT DESCRIPTION

The circuit diagram of the Audible Tone Generator is shown in Fig. 1. Regular readers will recognise this as a unijunction transistor oscillator, TR1, followed by a single-transistor amplifier, TR2.

TR1 has three terminals which, unlike a "normal" transistor, are designated emitter, base 1 and base 2. The transistor is connected to form a relaxation oscillator operating at audio frequencies. When power is applied to the circuit, the capacitor C1 will charge up through the resistors R1 and VR1. Eventually a point is reached when the transistor will switch over, and C1 will discharge itself into the emitter of TR1 and R4 to 0V.

TR1 will then switch back over to its high impedance state, and so C1 starts to charge up again. The whole cycle repeats itself, a constant stream of pulses being present at base 1.

By adjusting the timing components (R1, VR1 and C1), the frequency of the pulses can be altered. In fact by varying VR1 this particular unit was measured as operating between 100 and 350 Hertz.

The output pulses are coupled to TR2 by R3. This second transistor amplifies the audio tone generated by TR1 and associated components, and directly drives the loudspeaker LS1. The speaker used in the prototype was a 45mm diameter type, although a larger size (e.g. 65mm) could be used.

Capacitor C2 decouples the power supply and enables the peak current requirements to be met.

# UNIBOARDS

**SIMPLE  
TRANSISTOR  
DESIGNS**

**By A.R. Winstanley**

**5**

## AUDIO TONE GENERATOR

**CONSTRUCTION  
starts here**

### CIRCUIT BOARD

The circuit can be built onto a standard-sized piece of 0.1 inch matrix stripboard measuring 10 strips x 24 holes, Fig. 2. This particular size is available from suppliers, but it can if necessary be cut out from a larger piece.

Commence by drilling two 6BA clearance holes in the positions B3 and I3 as shown. These will enable the completed board to be fixed down with 6BA hardware and spacers.

There are six breaks to be made in the copper strips, in order to prevent the mounting hardware from shorting together adjacent copper strips. After doing this, the components may be soldered in.

The transistors being semiconductors of course are sensitive to heat, so it is wise to use a heatshunt on the transistor leads being soldered.

Transistor TR2 was fitted with a push-on TO-18 heatsink purely as a precaution, as the transistor temperature did rise slightly after prolonged use with a 12V supply rail. The heatsink can be omitted if it is not available, but if one is used, it must be

fitted to the transistor *before* the device is soldered into position. Otherwise the possibility exists of the leads of the transistor being accidentally bent or deformed, because of the pressure required to push on the tight-fitting heatsink.

The only points to watch are correct orientation of the transistor leads, plus proper polarisation of the electrolytic capacitor C2. Four flying leads connect up the loudspeaker switch and the power supply; these can be made up from standard multi-purpose hook-up wire (preferably stranded) and can either be soldered to terminal pins or straight to the circuit board.

### INSTALLATION

The completed unit can either be installed in a separate box (together with the loudspeaker) or it can be fitted into the same case (if there is any room) as the equipment from which it is to be powered.

The miniature loudspeaker is carefully glued to the inside of the case: a smear of Uhu or similar adhesive around the rim of the speaker should be enough to fix down the loudspeaker, but do not apply any glue to the actual cone of the speaker. A series of holes should be made in the case where the speaker is to be positioned, so that the sound of course can get out.

Testing the generator comprises applying 9 volts (from a battery) and setting VR1 until a tone of the desired frequency is obtained.

**Next Month: Voltage Converter**


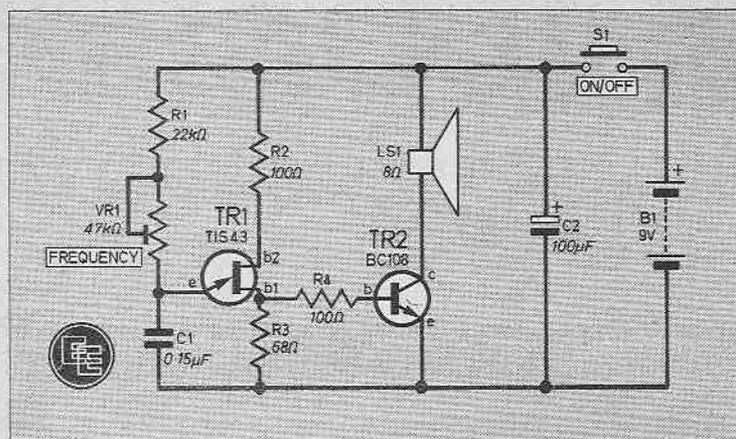


Fig. 1. Circuit diagram for the Audio Tone Generator.

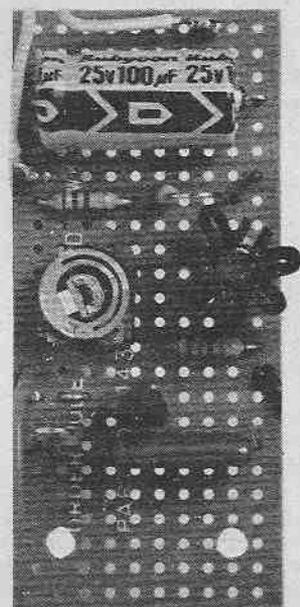

(above) The completed circuit board. The use of a heatsink for TR2 is optional.

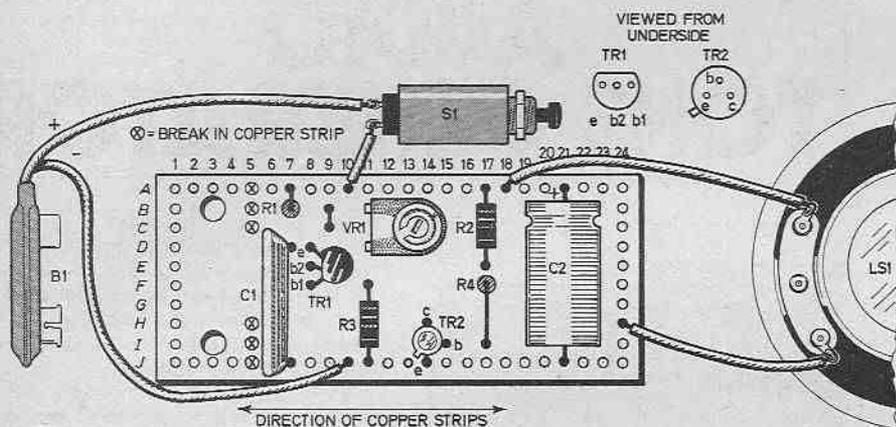


Fig. 2. Layout of components on the topside of the circuit board together with interwiring to loudspeaker, on/off switch and battery connector. Note that there are six breaks to be made in the copper strips on the underside.

## COMPONENTS

### Resistors

R1	22kΩ	} All ¼W carbon ± 5%
R2	100Ω	
R3	100Ω	
R4	68Ω	

### Capacitors

C1	0.15μF polyester type C280
C2	100μF 10V elect.

### Semiconductors


TR1	TIS43 <i>n</i> -channel unijunction transistor
TR2	BC108 <i>n</i> p <i>n</i> silicon

### Miscellaneous

VR1	47kΩ miniature horizontal preset
LS1	miniature 8-ohm moving coil loudspeaker
S1	push-to make pushbutton switch
B1	9V type PP3 or in-built supply—see text

Stripboard 0.1 inch matrix size 10 strips × 24 holes; push-on TO-18 heatsink (optional, see text); 6BA mounting hardware; case to suit; PP3 battery clip.

Approx. cost **£2.20**  
Guidance only

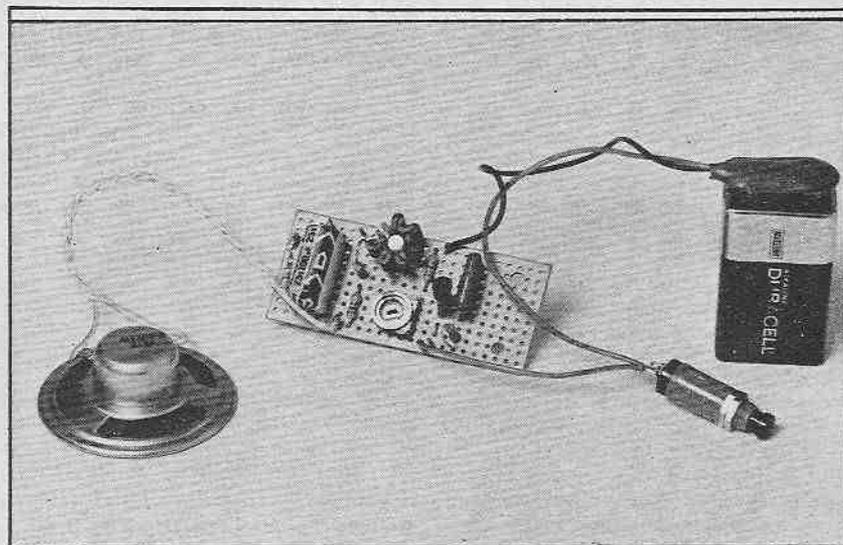

The completed Audio Tone Generator. The method of housing the finished unit is left to individual choice.

# RADIO WORLD

By Pat Hawker, G3VA

## Power for Radio

When most of us think of radio, telecommunications and broadcasting, we think in terms of electronics rather than electric power. Yet, in practice, as soon as one moves equipment away from the electric supply mains, the basic problem of providing electricity looms very large indeed.

A simple radio receiver can be run from dry batteries, although the cost, in terms of power delivered, is several hundred times as much as from supply mains.

Rechargeable cells, particularly the convenient nickel-cadmium (nicad) units, are the most popular and practical means of powering small amateur-radio transceivers, but this assumes moderate loads and regular access to the mains. What about equipment that needs to run, day-in day-out, often unattended, in remote locations?

Many exotic, high-density power sources are regularly announced yet relatively few of these prove in the end to be as cost-effective as the traditional methods. Remember when in the sixties "fuel cells" were so confidently predicted as being about to sweep normal large capacity storage batteries off the market? Somehow Leclanche dry batteries and lead-acid car batteries seem to have survived!

Some ingenious power sources were exploited during World War II for clandestine and infiltration radio links: stationary bicycle generators (an energetic "rider" can develop over 100 watts for a limited period of time); the more sophisticated form of this approach was a "beach chair" version that could be folded up and carried as a back-pack; wind-generators of course; thermo-couple chargers using the Seebeck effect of dissimilar junctions (in the 1930s this was used to permit radio receivers to be "run from the gas mains"); there was even a small steam-driven generator with a boiler that could be suspended in a charcoal-burning brazier, coupled to a twin-cylinder engine which, with a steam pressure of 30 to 35lb, could charge a 6V battery at about 4A.

More recently the solar generator has found increasing application, not only for space satellites, but also for many purposes in remote, sunny areas. Even the early form of zinc-air batteries (once used to operate door bells in many houses) has been very successfully revived and used in South Africa to run remote radio repeaters; the trick is to use the disposable but very large zinc-air battery to keep large nicad cells (better able to supply intermittent loads) fully charged.

Many systems have been used for rural telecommunications in Australia. For example Telecom Australia has over 50 solar power systems in use and these are proving cost-effective for loads of up to about 200 watts.

This organisation has also used thermoelectric generators, mostly for powers of under 60W. Originally these were heated from propane gas but suffered from high costs and poor reliability; however a new range of improved units, delivering up to 120W, with hermetically-sealed thermopiles and all-stainless-steel construction, are now being developed for locations where there are adequate supplies of propane, butane or natural gas.

## Wind Generators

Wind generators have been found to need careful design since their performance in low wind conditions is usually much more important than their ability to deliver considerable power in strong winds. Current work is on a 5kW design that is expected to "cut-in" and deliver useful power whenever the wind exceeds a modest 10km/hour; these are expected to support (with the aid of storage batteries) ten times the load of earlier 2kW units.

The Americans are thinking of very large wind-generators to feed power into the electric grid; some of these may be in the form of tall, elegant windmills. Some people, however, are concerned lest the large revolving blades upset television reception over large areas, in much the same way as reflections from aircraft can do, or as happens in areas where there are large moving cranes producing a changing pattern of multipath ("ghostly") pictures.

Late last year, an experimental American medium-wave broadcasting station, WBNO at Bryan, Ohio, began using a large solar array of 33,600 photovoltaic cells that can generate 15kW from sunlight; they are used in conjunction with four large unitized diesel tubular batteries.

The rising costs of electric power, even from the mains, is already worrying American broadcasters; a couple of years ago an engineer at one of the very high power u.h.f. stations told me that his station had given up late night TV as it was too expensive: not the cost of programming but the power bill!

## Lines on TV

The Science Museum in London is currently staging a special exhibition (open until September) called "The Great Optical Illusion" and marking 50 years of television broadcasting. The anniversary is based a little tenuously on one of the many events surrounding the early Baird 30-line mechanical system which helped pave the way for good TV pictures but which was never itself of real home-entertainment value.

The poor performance was due to poor synchronisation as well as the poor resolution of the pictures; though mechanical systems of television subsequently

proved capable of providing very acceptable pictures on 180 lines, 240 lines and even (with the Scophony large screen system) on 405 lines. The limit of 30 lines was due to the restricted bandwidth available on medium waves; it was only when television moved up to v.h.f. that real progress became possible.

In the UK we all recognise the extremely valuable work done by the Marconi-EMI research team leading to the 405-line system that opened (alongside the Baird 240-line sequential system) in November 1936 at Alexandra Palace. But I do feel that we tend, a little chauvinistically, to overlook the important work during the thirties in France and Germany.

A 180-line service was officially opened in Berlin in 1935 and soon included the use of electronic cameras; at the same time many firms in Germany were working on 375-lines and a public service opened in 1938 using 441 lines.

The Germans televised the 1936 Olympic Games using both mechanical and electronic cameras and, at the Berlin Radio Exhibition that year, receivers for 180 and 375 lines were exhibited by Fernseh, Telefunken, Loewe, Lorenz, Philips and Te-Ka-De (a firm that specialised in mechanical systems); the German Post Office (which had opened a video telephone link between Berlin and Leipzig using a co-axial cable and a 180-line system) showed iconoscope-type cameras as well as an intermediate film system similar to that used by Baird at Alexandra Palace. With this technique the film was processed in just about a minute (the main drawback curiously enough was the poor sound of the film recording).

Although the BBC television service closed down on September 1, 1939, the sound transmitter later being used to "bend" German navigational beams, the Germans kept their Berlin service going until November 1943 when the transmitter was destroyed by Allied bombing; they also ran a service for Wehrmacht occupation troops from the Eiffel Tower that actually stayed on the air until ten days before the Liberation of Paris in August 1944. Pictures from this service were monitored on the Kent coast and it has been claimed that useful information was obtained from this Intelligence operation.

## Our three-colour eyes

The truly remarkable colour-fidelity that can be achieved with modern television based on the transmission of three colour signals (red, green and blue) becomes more understandable now that it is firmly accepted that human colour vision similarly depends on just three classes or retinal receptors and that these, also like colour TV, have overlapping spectral sensitivities.

Apparently these human colour sensitivities are centred on violet, green and yellow, though spectrally these are not far away from TV's red, green and blue.

If one could only find a way of stimulating the brain directly from video signals, it might be possible to transmit a colour picture without the need for a picture tube or having to keep our eyes open! But of course if we could do that, and similarly with sound, we would be well on our way to enabling the deaf to hear and the blind to see.

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

**ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 3p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE.**

**VAT** Export orders no V.A.T. Applicable to U.K. Customers only. Unless stated otherwise all prices are exclusive of V.A.T. Please add 15% to total cost including P & P.

**We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday 9.00 am-5.00 pm. Ampie Free Car Parking space available.**

**POLYESTER CAPACITORS:** Axial Lead type (Values are in  $\mu F$ )  
50V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n, 330n, 470n 47p; 680n 52p; 1k 64p; 2k 82p.  
160V: 39 $\mu F$ , 10n, 15n, 22n 41p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n, 470n 11p; 680n 14p; 1k 17p; 2k 22p; 3k 27p; 4k 33p; 5k 39p; 6k 47p; 8k 56p; 10k 68p; 15k 82p; 20k 100p; 30k 120p; 40k 150p; 50k 180p; 60k 220p; 80k 270p; 100k 330p; 150k 420p; 200k 510p; 300k 630p; 400k 790p; 500k 990p; 600k 1200p; 800k 1500p; 1000k 1900p.

**POLYESTER RADIAL LEAD CAPACITORS (250V)**  
10nF, 15n, 22n, 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n, 470n 11p; 680n 14p; 1k 17p; 2k 22p; 3k 27p; 4k 33p; 5k 39p; 6k 47p; 8k 56p; 10k 68p; 15k 82p; 20k 100p; 30k 120p; 40k 150p; 50k 180p; 60k 220p; 80k 270p; 100k 330p; 150k 420p; 200k 510p; 300k 630p; 400k 790p; 500k 990p; 600k 1200p; 800k 1500p; 1000k 1900p.

**ELECTROLYTIC CAPACITORS:** (Values are in  $\mu F$ ) 500V, 10 40p; 47 68p; 250V: 100 65p; 33V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8p; 10, 15, 22, 33p; 47, 50, 100 21p; 150 27p; 200 33p; 300 47p; 400 68p; 500 100p; 600 150p; 800 220p; 1000 330p; 1500 470p; 2000 680p; 3000 1000p; 4000 1500p; 5000 2200p; 6000 3300p; 8000 4700p; 10000 6800p; 15000 10000p; 20000 15000p; 30000 22000p; 40000 33000p; 50000 47000p; 60000 68000p; 80000 100000p; 100000 150000p; 150000 220000p; 200000 330000p; 300000 470000p; 400000 680000p; 500000 1000000p; 600000 1500000p; 800000 2200000p; 1000000 3300000p; 1500000 4700000p; 2000000 6800000p; 3000000 10000000p; 4000000 15000000p; 5000000 22000000p; 6000000 33000000p; 8000000 47000000p; 10000000 68000000p; 15000000 100000000p; 20000000 150000000p; 30000000 220000000p; 40000000 330000000p; 50000000 470000000p; 60000000 680000000p; 80000000 1000000000p; 100000000 1500000000p; 150000000 2200000000p; 200000000 3300000000p; 300000000 4700000000p; 400000000 6800000000p; 500000000 10000000000p; 600000000 15000000000p; 800000000 22000000000p; 1000000000 33000000000p; 1500000000 47000000000p; 2000000000 68000000000p; 3000000000 100000000000p; 4000000000 150000000000p; 5000000000 220000000000p; 6000000000 330000000000p; 8000000000 470000000000p; 10000000000 680000000000p; 15000000000 1000000000000p; 20000000000 1500000000000p; 30000000000 2200000000000p; 40000000000 3300000000000p; 50000000000 4700000000000p; 60000000000 6800000000000p; 80000000000 10000000000000p; 100000000000 15000000000000p; 150000000000 22000000000000p; 200000000000 33000000000000p; 300000000000 47000000000000p; 400000000000 68000000000000p; 500000000000 100000000000000p; 600000000000 150000000000000p; 800000000000 220000000000000p; 1000000000000 330000000000000p; 1500000000000 470000000000000p; 2000000000000 680000000000000p; 3000000000000 1000000000000000p; 4000000000000 1500000000000000p; 5000000000000 2200000000000000p; 6000000000000 3300000000000000p; 8000000000000 4700000000000000p; 10000000000000 6800000000000000p; 15000000000000 10000000000000000p; 20000000000000 15000000000000000p; 30000000000000 22000000000000000p; 40000000000000 33000000000000000p; 50000000000000 47000000000000000p; 60000000000000 68000000000000000p; 80000000000000 100000000000000000p; 100000000000000 150000000000000000p; 150000000000000 220000000000000000p; 200000000000000 330000000000000000p; 300000000000000 470000000000000000p; 400000000000000 680000000000000000p; 500000000000000 1000000000000000000p; 600000000000000 1500000000000000000p; 800000000000000 2200000000000000000p; 1000000000000000 3300000000000000000p; 1500000000000000 4700000000000000000p; 2000000000000000 6800000000000000000p; 3000000000000000 10000000000000000000p; 4000000000000000 15000000000000000000p; 5000000000000000 22000000000000000000p; 6000000000000000 33000000000000000000p; 8000000000000000 47000000000000000000p; 10000000000000000 68000000000000000000p; 15000000000000000 100000000000000000000p; 20000000000000000 150000000000000000000p; 30000000000000000 220000000000000000000p; 40000000000000000 330000000000000000000p; 50000000000000000 470000000000000000000p; 60000000000000000 680000000000000000000p; 80000000000000000 1000000000000000000000p; 100000000000000000 1500000000000000000000p; 150000000000000000 2200000000000000000000p; 200000000000000000 3300000000000000000000p; 300000000000000000 4700000000000000000000p; 400000000000000000 6800000000000000000000p; 500000000000000000 10000000000000000000000p; 600000000000000000 15000000000000000000000p; 800000000000000000 22000000000000000000000p; 1000000000000000000 33000000000000000000000p; 1500000000000000000 47000000000000000000000p; 2000000000000000000 68000000000000000000000p; 3000000000000000000 100000000000000000000000p; 4000000000000000000 150000000000000000000000p; 5000000000000000000 220000000000000000000000p; 6000000000000000000 330000000000000000000000p; 8000000000000000000 470000000000000000000000p; 10000000000000000000 680000000000000000000000p; 15000000000000000000 1000000000000000000000000p; 20000000000000000000 1500000000000000000000000p; 30000000000000000000 2200000000000000000000000p; 40000000000000000000 3300000000000000000000000p; 50000000000000000000 4700000000000000000000000p; 60000000000000000000 6800000000000000000000000p; 80000000000000000000 10000000000000000000000000p; 100000000000000000000 15000000000000000000000000p; 150000000000000000000 22000000000000000000000000p; 200000000000000000000 33000000000000000000000000p; 300000000000000000000 47000000000000000000000000p; 400000000000000000000 68000000000000000000000000p; 500000000000000000000 100000000000000000000000000p; 600000000000000000000 150000000000000000000000000p; 800000000000000000000 220000000000000000000000000p; 1000000000000000000000 330000000000000000000000000p; 1500000000000000000000 470000000000000000000000000p; 2000000000000000000000 680000000000000000000000000p; 3000000000000000000000 1000000000000000000000000000p; 4000000000000000000000 1500000000000000000000000000p; 5000000000000000000000 2200000000000000000000000000p; 6000000000000000000000 3300000000000000000000000000p; 8000000000000000000000 4700000000000000000000000000p; 10000000000000000000000 6800000000000000000000000000p; 15000000000000000000000 10000000000000000000000000000p; 20000000000000000000000 15000000000000000000000000000p; 30000000000000000000000 22000000000000000000000000000p; 40000000000000000000000 33000000000000000000000000000p; 50000000000000000000000 47000000000000000000000000000p; 60000000000000000000000 68000000000000000000000000000p; 80000000000000000000000 100000000000000000000000000000p; 100000000000000000000000 150000000000000000000000000000p; 150000000000000000000000 220000000000000000000000000000p; 200000000000000000000000 330000000000000000000000000000p; 300000000000000000000000 470000000000000000000000000000p; 400000000000000000000000 680000000000000000000000000000p; 500000000000000000000000 1000000000000000000000000000000p; 600000000000000000000000 1500000000000000000000000000000p; 800000000000000000000000 2200000000000000000000000000000p; 1000000000000000000000000 3300000000000000000000000000000p; 1500000000000000000000000 4700000000000000000000000000000p; 2000000000000000000000000 6800000000000000000000000000000p; 3000000000000000000000000 10000000000000000000000000000000p; 4000000000000000000000000 15000000000000000000000000000000p; 5000000000000000000000000 22000000000000000000000000000000p; 6000000000000000000000000 33000000000000000000000000000000p; 8000000000000000000000000 47000000000000000000000000000000p; 10000000000000000000000000 68000000000000000000000000000000p; 15000000000000000000000000 100000000000000000000000000000000p; 20000000000000000000000000 150000000000000000000000000000000p; 30000000000000000000000000 220000000000000000000000000000000p; 40000000000000000000000000 330000000000000000000000000000000p; 50000000000000000000000000 470000000000000000000000000000000p; 60000000000000000000000000 680000000000000000000000000000000p; 80000000000000000000000000 1000000000000000000000000000000000p; 100000000000000000000000000 1500000000000000000000000000000000p; 150000000000000000000000000 2200000000000000000000000000000000p; 200000000000000000000000000 3300000000000000000000000000000000p; 300000000000000000000000000 4700000000000000000000000000000000p; 400000000000000000000000000 6800000000000000000000000000000000p; 500000000000000000000000000 10000000000000000000000000000000000p; 600000000000000000000000000 15000000000000000000000000000000000p; 800000000000000000000000000 22000000000000000000000000000000000p; 1000000000000000000000000000 33000000000000000000000000000000000p; 1500000000000000000000000000 47000000000000000000000000000000000p; 2000000000000000000000000000 68000000000000000000000000000000000p; 3000000000000000000000000000 100000000000000000000000000000000000p; 4000000000000000000000000000 150000000000000000000000000000000000p; 5000000000000000000000000000 220000000000000000000000000000000000p; 6000000000000000000000000000 330000000000000000000000000000000000p; 8000000000000000000000000000 470000000000000000000000000000000000p; 10000000000000000000000000000 680000000000000000000000000000000000p; 15000000000000000000000000000 1000000000000000000000000000000000000p; 20000000000000000000000000000 1500000000000000000000000000000000000p; 30000000000000000000000000000 2200000000000000000000000000000000000p; 40000000000000000000000000000 3300000000000000000000000000000000000p; 50000000000000000000000000000 4700000000000000000000000000000000000p; 60000000000000000000000000000 6800000000000000000000000000000000000p; 80000000000000000000000000000 10000000000000000000000000000000000000p; 100000000000000000000000000000 15000000000000000000000000000000000000p; 150000000000000000000000000000 22000000000000000000000000000000000000p; 200000000000000000000000000000 33000000000000000000000000000000000000p; 300000000000000000000000000000 47000000000000000000000000000000000000p; 400000000000000000000000000000 68000000000000000000000000000000000000p; 500000000000000000000000000000 100000000000000000000000000000000000000p; 600000000000000000000000000000 150000000000000000000000000000000000000p; 800000000000000000000000000000 220000000000000000000000000000000000000p; 1000000000000000000000000000000 330000000000000000000000000000000000000p; 1500000000000000000000000000000 470000000000000000000000000000000000000p; 2000000000000000000000000000000 680000000000000000000000000000000000000p; 3000000000000000000000000000000 1000000000000000000000000000000000000000p; 4000000000000000000000000000000 1500000000000000000000000000000000000000p; 5000000000000000000000000000000 2200000000000000000000000000000000000000p; 6000000000000000000000000000000 3300000000000000000000000000000000000000p; 8000000000000000000000000000000 4700000000000000000000000000000000000000p; 10000000000000000000000000000000 6800000000000000000000000000000000000000p; 15000000000000000000000000000000 100p; 20000000000000000000000000000000 15000000000000000000000000000000000000000p; 30000000000000000000000000000000 22000000000000000000000000000000000000000p; 40000000000000000000000000000000 33000000000000000000000000000000000000000p; 50000000000000000000000000000000 47000000000000000000000000000000000000000p; 60000000000000000000000000000000 68000000000000000000000000000000000000000p; 80000000000000000000000000000000 1000p; 100000000000000000000000000000000 1500p; 150000000000000000000000000000000 2200p; 200000000000000000000000000000000 3300p; 300000000000000000000000000000000 4700p; 400000000000000000000000000000000 6800p; 500000000000000000000000000000000 100p; 600000

# SQUARE one

## FOR BEGINNERS

### STOCKING UP

**T**HIS month we suggest a range of capacitors for the new constructor to purchase as part of an initial stock of components.

Capacitors are not used to the same extent as resistors, but they do come in a variety of forms, shapes and sizes, to say nothing of the capacitance values.

Therefore the holding stock will be numerically much smaller than in the case of resistors. On the other hand the choice of actual types and values is more difficult. In the tables below we have set out our recommendations concerning type and value. This selection of capacitors should meet most general requirements.

### NON-POLARISED CAPACITORS

Capacitors are classified according to the material used to form the dielectric (the insulating surface between the two "plates" of the capacitor).

Table 1 lists the more frequently used values and the types of capacitor in which they are available.

Recommended minimum quantities are in italics. If resources permit, it would be wise to multiply all these quantities by a factor of two or even five.

**TABLE 1**  
NON-POLARISED CAPACITORS

Value	Polystyrene	Ceramic	Polyester
10pF	2		
47	2		
100	2	2	
220	2	2	
470	2	1	
0.001 $\mu$ F	2	2	
0.0022	2	2	
0.0047		3	
0.01		3	3
0.022		2	2
0.047		3	3
0.1		3	5
0.22		2	2
0.47		2	2
1.0		1	1

**POLYESTER CAPACITORS:** These are widely used and cover the middle range of capacitances: typically from 0.01 $\mu$ F to 2.0 $\mu$ F. Tubular, tablet and block forms are common. Tolerance 10 and 20 per cent.

**CERAMIC:** These include the smallest capacitors and range from 1.8pF to (0.1 $\mu$ F) typically. Close tolerance, low loss, and high stability are their important characteristics. They are small, thin disc- and plate-shape components.

**POLYSTYRENE:** These capacitors are available in the range 10pF to 0.1 $\mu$ F. Thus they cover very nearly the same range as ceramics. They have a better electrical performance than the ceramics, and are available with close tolerances such as 5, 2 $\frac{1}{2}$  and 1 per cent. However polystyrene capacitors are rather more expensive and are

only used where their special characteristics are essential.

Polystyrene capacitors are tubular in shape and rather more bulky than ceramics.

### ELECTROLYTIC CAPACITORS


Electrolytic or polarised capacitors are a special case. They provide quite a large value of capacitance, but must be connected right way round in circuit. They are made with specific working voltages, which must not be exceeded in practice. It is however permissible to use them at a lower voltage than the stated working voltage (WV).

Generally, always follow the recommendations given in Component Lists for projects and use the specified type of electrolytic.

Table 2 gives a selection of electrolytics that should cover many needs. A working voltage of 25V is adequate for most battery operated projects. The higher rating of 63V has been given for the three smallest capacitors, since this is the lowest WV in which they are available.

Electrolytics are available as "double-ended" types with the connecting leads emerging from either end; also as "single-ended" types with both leads at same end of component. Double-ended types are recommended for the present purpose, see illustration in Fig. 1.

Some typical capacitors drawn to scale and showing their characteristic physical forms. The electrolytic is a double-ended type with axial leads.

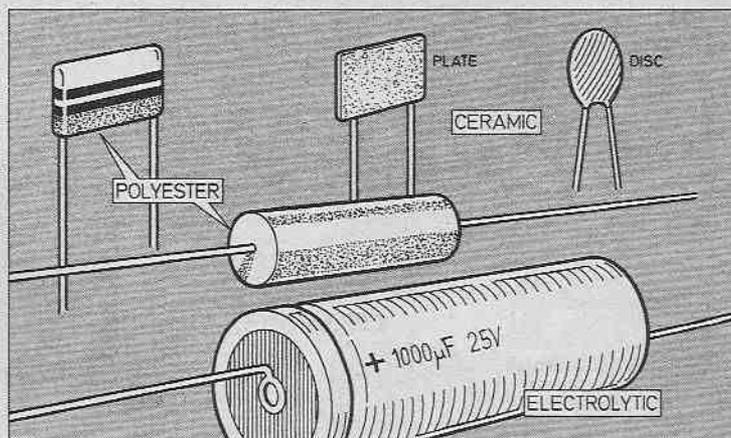

**TABLE 2**  
ELECTROLYTIC CAPACITORS

Value	WV	Qty	Value	WV	Qty
1 $\mu$ F	63	1	47 $\mu$ F	25	1
2.2	63	1	100	25	2
4.7	63	1	220	25	1
10	25	2	470	25	1
22	25	1	1,000	25	1

# Casio's new SUPERCALC!

You always wanted a calculator that does everything except make tea-

HERE IT IS!

## CASIO FX-8100



46 scientific functions, clock calendar, alarm, countdown alarm, interval alarm timer, hourly chimes, 1/100 sec stopwatch

ONE YEAR BATTERY LIFE (approx. used continuously). LC Display; 8 digit mantissa plus 2 digit exponent, 5 level parenthesis, full access memory. Trigs, logs, hyperbolics, standard deviations, co-ordinate conversions, sexagesimal to decimal conversions, fractions, percentage, cube roots, sign change, register exchange, Pi entry etc. CLOCK displays hours, minutes, seconds, am/pm and day. CALENDAR pre-programmed to 1999; day, date, month and year. 24 hour ALARM, hourly chimes. Countdown ALARM TIMER, interval (repeater) ALARM TIMER or 1/100 second STOPWATCH measuring net, lap and first and second place times to 10 hours. 6.6 x 70 x 129mm (2 1/2 x 5 1/4 inches) Leatherette wallet. RRP £27.95

Only £24.95

## Be the first with THE MIGHTY CHIP

The "in" pendant for 1980

Winner of the 1980 GIFT AWARD



(Fashion and personal accessories) Features a genuine metal oxide silicon EPROM (Erasable Programmable Read Only Memory) chip, set in a 9ct. gold, or a sterling silver, case. Approx. 1 1/2 x 3/16 inch, 11gm. Supplied with a leather thong.

Sterling Silver £30  
9ct. Gold £69

SEIKO

Latest 1980 models  
Around 30% off!

## SEIKO'S STAR BUY

### TS2 Alarm Chronograph

Comprehensive display of hours, minutes, seconds, day, date and month. 24 hour alarm and hourly chimes. Stopwatch from 1/100 second to 20 minutes, then seconds to 20 hours. Upper display-lap times. Lower display-total time. S/Steel encased—8mm thick plus front buttons.



ONLY £47.50



### TS1 Alarm Chronograph with Countdown Alarm

Hours, minutes, seconds. Alpha day and date on upper display; And day, date, month. Alarm and hourly chimes. Countdown alarm (upper display). Stopwatch from 1/100 sec to 12 hours; net, lap and 1st & 2nd place times.

Only £57.50

### TS5 World Time/Alarm

TWO alarms, local and world time. Hourly chimes. Hours, minutes, seconds, day; or hours, minutes, day, date, month. World time mode displays an atlas. Each of the 19 time zones flashes when selected.



Stainless £79.95  
Gold pl. £99.95



### H127 Digi/Ana

Independent analogue display. Digital hours, minutes, seconds, day; And day, date, month. 1/100 second stopwatch to 20 minutes, then seconds to 12 hours. Net, lap and 1st & 2nd place. Single or dual counters.

Only £69.95 (£95)

## STAR BUYS FROM CASIO

### 81QS-35B Alarm Chronograph

Stainless steel. Mineral glass. Water resistant 5 YEAR BATTERY Hours, minutes, seconds, day; And day, date, month and year. 12 or 24 hour display. 24 hour hour alarm, hourly chimes. Stopwatch from 1/100 second to 7 hours; net, lap and 1st and 2nd place times.

(£34.95) £29.95



### 95QS-36B Chronograph

Similar to above but with dual time (12 or 24 hour) facility in lieu of alarm and chimes



### 83QS-41B Alarm Chronograph.

S/S encased. Mineral glass. Water resistant. 3 YEAR BATTERY Hours, minutes, seconds, date, am/pm; or hours, minutes, alpha day, date am/pm. 24 hour alarm, hourly chimes. Stopwatch from 1-10 second to 12 12 hours; net lap and 1st and 2nd place. Nightlight.

ONLY £24.95

F-80 As above but with black resin case/strap with S/S back and front trim

£19.95

### C-80 Calculator Watch

(Finger-touch keyboard) Hours, minutes, seconds, am/pm, day, Date, date, month auto calendar pre-programmed to 2009. Professional 24 hour stopwatch; net, lap, 1st & 2nd place to 1/100 sec. Dual time. 8 digit calculator. Nightlight. Water resistant. Glass. Black resin case/strap. 44.9 x 35.8 x 10.2mm

ONLY £24.95



New lower prices. F8C now only £9.95

F-200 now only £12.95. 95 QS 328 £16.95

LADIES CASIO WATCHES from £12.95

## Mini SUPERCALC!

### FX-7100

1 YEAR BATTERIES 30 scientific functions. As FX-8100 but 8 digits, without hyperbolics, fractions and calendar. Only 1 countdown alarm timer (repeat) or stopwatch function. Alarm and hourly chimes. 1 1/2 x 2 1/4 x 3 1/4". Leatherette wallet (£27.95)

£24.95



## NEW SCIENTIFICS



### Casio FX-100

LCD, 10 digits, 44 scientific functions as FX-8100 above but with 6 levels ( ), FIX, SCI, NORM, ENG, RND and RAN in lieu of hyperbolics, %, 7,500 hours battery 1 1/2 x 3 x 5 1/2 inches.

£15.95 (£17.95)

FX-81 £12.95. FX-330 £15.95. FX-310 £17.95. FX-510 £19.95. FX-2600 £19.95. FX-3200 £21.95. FX-501P £54.95. FX-502P £74.95. FA-1 £19.95.

### Melody 81.11 note melody maker

(£24.95) £22.95

Musical alarms (two), countdown timer, hourly chimes, Stopwatch from 1/10 second to 12 hours; net, lap, 1st & 2nd pl. Calculator with full memory. 5/16 x 4 1/2 x 2 1/4" 1 year batteries



### NEW! Casio PW-81

Card size clock, calculator, alarm, hourly chimes. Full memory, %, 3/16 x 3 1/4 x 2 1/4 inches.

£14.95

## BARGAIN BASEMENT

Clearance offers while stocks last.

95QS-32B Chronograph. Chrome Pl. £16.95

CQ-82 Desk clock/calc. 4 alarms £13.95

HQ-21 Clock/calculator £8.95

UFO Master Blaster (£24.95) £16.95

Grandstand Adam Simon +3 £16.95

Grandstand 4-in-1 (£24.95) £16.95

Send 25p for our illustrated catalogue of Casio and Seiko products  
OUR RETAIL SHOP IS MOVING! PERSONAL CALLERS PLEASE TELEPHONE FIRST

Prices include VAT, P & P. Send your cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:-

# TEMPUS

Dept. EE, Beaumont Centre, 164-167 East Rd.,  
Cambridge CB1 1DB. Tel. 0223 312866

# vero


# vero

# vero

VERO ELECTRONICS LTD RETAIL DEPT.  
Industrial Estate, Chandler's Ford,  
Hampshire SO5 3ZR  
Tel: (04215) 62829



## Wiring Accessories

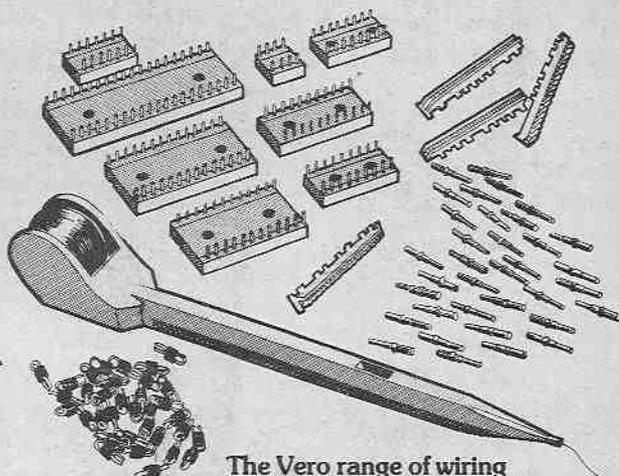

The Vero range of wiring accessories are all highest quality 'professional' products, carefully selected to ease your interconnection problems. There's a full range of pins and DIP sockets (including low-profile) for solder or wire wrapping techniques and the popular Verowire prototype wiring system. Add these to our established range of boards, boxes, frames and cases and you've got all you need for your project. It's all in our catalogue — just send 40p. and it's yours by return.

## The NEW Marshall's 79/80 catalogue is just full of components

*and that's not all . . .*

... our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.C.s, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100s of prices cut on our popular lines including I.C.s, Transistors, Resistors and many more.


If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426501/2.
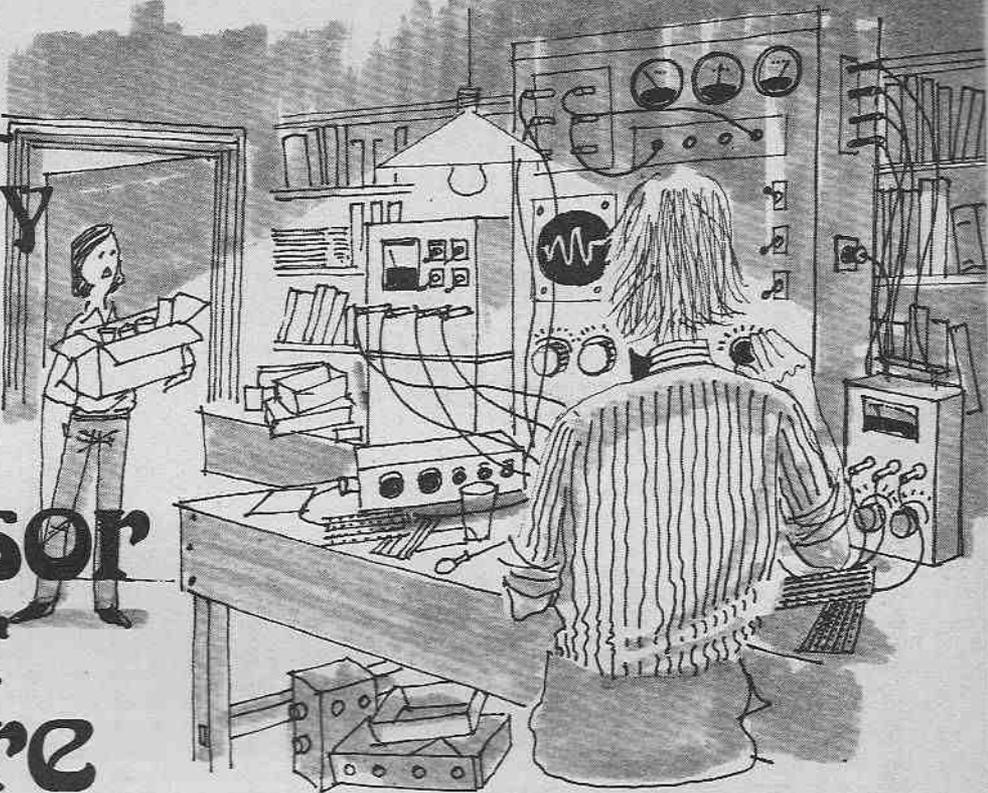
# The Extraordinary Experiments of Professor Ernest Eversure



by Anthony John Bassett

As Bob arrived once again at the Laboratory to be greeted by the Prof., his mind was full of thoughts of the Simulated Space Environment which the Prof. had produced with the aid of a giant vacuum chamber equipped with a wide range of electronic equipment; computers and lasers, electron-guns and other beam-producing equipment for experiments on energy beams, and many other applications of vacuum electronics.

The Prof's experimental robots could enter the vacuum chamber through the air-lock and Bob could see through the large windows that they and the Prof. had been at work installing more equipment.

## FLYING SAUCERS

"Your Space Environment Simulator looks more like real space exploration equipment every time I see it, Prof! I dream that we might even take a real space-trip in it!"

"Then you'll be interested in my latest experimental device, Bob."

"Wow, Prof. are you going to turn the experimental gravity control down past zero, and actually take-off and fly in the vacuum-chamber?"

"No, Bob, last time I tried that it caused yet another flying saucer scare around here, and also a UFO defence alert. I had quite a difficult job dodging the modern radar trackers and the latest batch of highly sensitive UFO detectors which have been built by investigators of such phenomena.

## RADAR JAMMER

I had to rig-up an emergency radar jammer to produce pictures of hundreds of flying saucers all over the radar screens for a short time whilst I gave them the slip and got back here safely! It must have caused quite a flap!"

"How does a radar jammer work, Prof?"

"When a craft is being scanned by radar, receiving instruments on board can detect the radar beam. To jam the radar, the craft may then transmit a series of pulses of energy at the frequency of the radar beam. This results in a number of false images on the radar screen to confuse the radar observer.

"Just as with TV games, electronic circuits operating in synchronism with the scan frequencies of the TV set can produce a great variety of images on the TV screen. So, by detecting the scan frequencies of the radars and transmitting a variety of synchronous pulses, a whole range of interesting 'objects' can be made to appear on the radar screen to divert the operator whilst the craft escapes!

"The radar jamming beam or broadcasting can produce an almost endless series of replicas of the image of the craft to appear all over the radar screen. It is amazing what can be carried on a beam of energy and your interest in the study of various energy beams and their widely differing properties can lead you to some fantastic discoveries!

## ABOLITION OF SPACE

"Some investigators consider that force fields can cause matter to become organised into objects whose structure and function are direct results of the 'originating' force fields, which are in some cases considered to precede and 'mould' the objects, which may include living creatures!"

"But Prof., if that is so, won't it result in the abolition of space itself? Because magnetic, electrical and gravitation fields can extend for infinite distances in space, if they were really responsible for the formation of objects and living creatures, surely space would soon become so filled-up there would be no gaps left in it!"

## COMPLICATIONS

"If that were so, Bob, we could all retire relatively smartly at a speed of  $c-\Delta c$  into our brand new individually pre-packed black holes, but fortunately things are more complicated than that. In most known instances, for example, force fields merely act in readily understood ways to guide the formation of objects, and the growth of crystals, for instance, is an example of this which is taught in many science classes. Here an object is formed under the influence of electrostatic field forces with no danger from black holes or other apocalyptic phenomena—the force fields merely acting to guide the atoms and molecules into places in the crystal lattice structures.

## REPLICATION BEAM

"With other objects less regular than crystals the picture is more complex and my latest experiment uses energy beams to influence the force-fields in space to induce the formation of replicas of objects, in regions where interfering energy-beams have produced congruent antinodal and nodal structures in the fields which exist in space."

"Prof., the ways in which force-fields and energy beams can influence one another, and in turn influence material objects are fascinating areas for advanced study—but how can antinodes and nodes be congruent with one another?"

## SCIENCE FAIR PROJECT

"An apparatus for demonstration of the existence of congruent nodes and antinodes would make a good practical construction project for your School Science Society, Bob, and could make a good, entertaining and educational School Fair exhibit. Think about it; such a project could demonstrate simultaneously a number of scientific principles and there is plenty of scope in it for the use of electronics!"

"It would be quite easy, for instance, to arrange that the nodes and antinodes of a microwave low power field, for example, should be congruent with those of, say, an acoustic field of the same, or different wave length, and with the different forms of energy travelling in transverse directions or at various angles. Then, of course, there are quite a variety of mechanical shear or transverse waves, compression waves, surface-displacement waves and so on, to experiment with, which could make spectacular mystifying and educational displays where luminescent, reflective or refractive media can be used."

"I understand now, Prof! The nodes and antinodes of different fields of standing-waves or interfering waves,

whose energy may be travelling in differing directions or in the same direction, may quite readily be congruent with one another and produce interesting and sometimes complicated combined effects!"

"That's right, Bob. Now watch this!"

## TELE-PORT

The Prof. placed a small metal object upon a low pedestal which was surrounded by strange electronic sensors connected to an energy beam projector apparatus.

When he operated the apparatus, Bob saw that, just for a moment, the metal statue seemed to be surrounded by a phosphorescent halo of light, and also to glow with a light which seemed to come from within the very core of the solid metal.

But the statue seemed to come to no harm.

"This is because," explained the Prof., "what I am doing is merely making a record of the structure of the object—it does no more harm than taking an ordinary photograph. Now, the beam-projectors are set to focus and converge on that table. Watch, and also observe carefully what happens to the small heap of grey crystals on the pan of the nearby laboratory weighing balance."

The balance tilted sharply as the crystals turned from the grey of lead sulphide to the yellow of sulphur, and thus rapidly lost weight. Bob saw that one of the Prof's experimental robots had to remove quite a lot of weights from the opposite pan before the scales would balance again. At the same time a shimmering replica of the small lead statue formed on the table. The Prof. picked it up and handed it to Bob.

"It is identical to the original," Bob explained, "down to the last tiny scratch—and I'll bet it weighs exactly the same."

"Yes—the Robot has just confirmed that." The Prof. switched the machine into reverse, and with a shimmering

sparkle and a sudden loss of weight, the statue faded from Bob's hand, and at the same time the crystals on the scale returned rapidly to their customary weight and grey colour.

"Will this work with living creatures too, Prof?"

"Yes, Bob, try it!" Bob himself stood on the pedestal and as the Prof. once again operated the device, this time with the assistance of a couple of his robots, Bob seemed to find his whole body and consciousness filled for just a moment with a flash of shimmering light. Then a perfect replica appeared on the table a few metres away, together with another replica of the Prof's lead statue which was still on the pedestal of the Replication Machine.

As Bob picked up the statue and examined it once again, his replica on the table picked up the replica of the statue and examined that.

After a short time the Prof. switched the machine into reverse and once again the replicas disappeared. Bob stepped down from the pedestal.

"That was amazing!" he reported to the Prof.

"As I was examining one side of the statue, the replica was examining the other side, and so I could see both sides of the statue simultaneously. Also I could see you in close-up with my own eyes, and from a distance through those of the replica. I could see the whole lab from two viewpoints, like being in two places at once! Really great! Want to try it again—but tell me, can this machine produce more than one—several replicas simultaneously?"

"That is possible Bob, but the mental and psychological problems would be multiplied, and could easily reach dangerous proportions even with one replica of an unbalanced person. So my next Extraordinary Experiment will be aimed not at increasing the number of the replicas, but the distance to which they can be projected!"

To be continued

## The Adventures of Tanty Bead

By Matthew Reed



**NEW**

# CONSTRUCTORS PACK 7

## ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

- \* EASY TO BUILD \* 5 PUSH BUTTON TUNING \* MODERN STYLING DESIGN \* ALL NEW UNUSED COMPONENTS
- \* 6 WATT OUTPUT \* READY ETCHED & PUNCHED P.C.B.
- \* INCORPORATES SUPPRESSION CIRCUITS



**£10.50** p&p £1.75

The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

**CONSTRUCTORS PACK 7A**  
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.  
**£1.95** Per Pack, p & p £1.00.  
Pack 7A may only be purchased at the same time as Pack 7.  
**NOTE:** Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.


**A FEATURED PROJECT IN PRACTICAL ELECTRONICS**



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.  
21A HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm  
Closed Thursday

### NEW 12+12 AMPLIFIER KIT

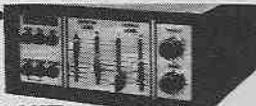


An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you still supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/2" x 8 1/2" x 4" approx. p&p £2.55

**£13.95**

**TWO WAY SPEAKER KIT** To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.85.

Available only to first time purchasers of the 12 + 12 kit.

### 50WATT MONO DISCO AMP

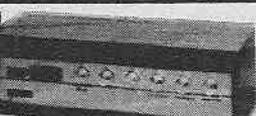

Size approx 13 1/2" x 5 1/2" x 6 1/2"  
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infogrip push-pull switches. Independent bass and treble controls and master volume.

**£30.60** p&p £3.20

**NOW AVAILABLE**

### 30 + 30 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 3" x 10" approx. **£32.90** p&p £3.30

**BUILT AND READY TO PLAY**

### Mullard AUDIO MODULES IN BARGAIN PACKS

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHOSE BUYING OUR BARGAIN PACKS.

CURRENT CATALOGUE PRICE AT OVER

**£25 PER PACK**

SEE OUR PRICES

**1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE p&p £1.10 **£5.00**

**2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. illus. OUR PRICE **£7.65** p&p £1.15

**ACCESSORIES** Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.80

**Two Way Speaker Kit** Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p **£4.05**

### £76.00 p&p £4.00 100 WATT MONO DISCO AMP



Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10 1/2". Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

### EMI SPEAKER BARGAIN

Stereo pair 350 lit. System consists of 13" x 8" approx. woofer with rolled surround, 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance.

**£18.25**

Per stereo pair p&p £4.20

### BSR P200

**£25.50**

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00  
Shure M75 8 Magnetic Cartridge to suit. **£7.95**



**BSR** Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m spindle adaptor ideally suited for home or disco use. OUR PRICE **£12.25** £2.75

### PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY.



### BARGAIN OFFER

Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over **£30.00**. **OUR £11.95** PRICE p&p £2.50




323 EDGWARE ROAD, LONDON W2  
21A HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 15%  
All items subject to availability. Price correct at 22.2.80 and subject to change without notice.  
All enquires Stamped Addressed Envelope.  
NOTE: Persons under 16 years not served without parent's authorisation.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

# TUNE IN!

## Build the World Famous CHROMA-CHIME

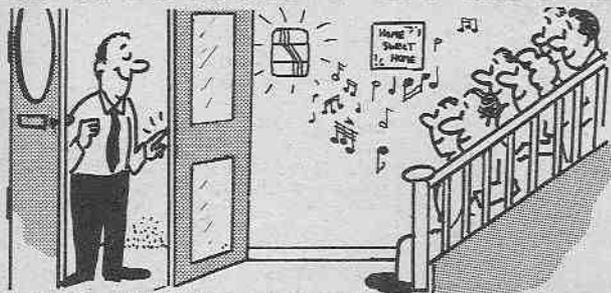

Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

\* Save pounds on normal retail price by building yourself.

**ONLY  
£9.95  
+ 75p p&p  
UK ONLY**

**TMS 1000N** - MP0027A Micro-computer chip available separately if required. Full 24 tune spec device supplied with data sheet and fully guaranteed.




New low price only **£4.95 inc. p&p**

## R/C MODELLERS - LISTEN FOR THE C.B. MENACE GET A 27MHZ MONITOR

- \* Audibly confirm your channel's clear.
- \* Tunes over whole 27mhz model band. (CB)
- \* Receives normal broadcast AM/FM bands as well.
- \* Sensitive with telescopic aerial.
- \* Totally portable.
- \* Runs on standard batteries.

This neat three band Superhet receiver not only provides an invaluable service, checking your channel and TX, but gives normal broadcast reception when you need it as well. Costing less than a decent Servo, you'll find it cheap and reassuring insurance!

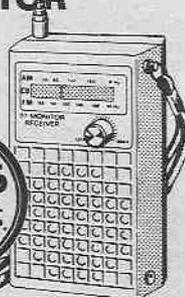**ONLY  
£17.95  
INC. V.A.T.  
AND P. & P.**



ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE  
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Chromatronics, Riverway, Harlow, Essex.

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/PO value £ \_\_\_\_\_

or debit my ACCESS/BARCLAYCARD account no. \_\_\_\_\_

Signature \_\_\_\_\_

# CHROMATRONICS

## GIVE US SPACE

YES WE'VE DONE IT AGAIN—ANOTHER HUGE PURCHASE OF COMPONENTS HAS ARRIVED AND OUR STORES ARE OVERFLOWING WITH BARGAINS. SO HERE'S YOUR CHOICE:—

**CUT OUT WHOLE COUPON—ADD MONEY, MARK NUMBER OF PACKS REQUIRED IN BOX**

1. **MINIATURE FM TRANSMITTER KIT.** (No case). Transmits up to 500 yds to any FM Radio. Building instructions—all components. This item is not licensable for use in UK. **£6.00**
2. **RESISTORS**—our giant pack, minimum quarter kilo, of assorted resistors—all types. **£1.00**
3. **TELEVISION GAMES CHIP** (colour) AY3-8600 by General Instruments—ball & paddle, tennis, hockey, soccer, squash practice, grid ball, basket ball. Includes data. **£1.00**
4. **TELEVISION GAMES CHIP** (colour) AY3-8550 ball & paddle, tennis, soccer, squash. Includes data. **£1.00**
5. **ZENER DIODE PACK**—15 assorted high & low wattage zeners—mixed voltages. **£1.00**
6. **20 ASSORTED TRANSISTORS**—no junk—all working branded—plastic and metal cans. **£1.00**
7. **TERRIFIC VALUE**—our capacitor packs (100 approx.) may include discs, mylars, electrolytics, polyester. **£1.00**
8. **DIODES**—20 assorted. May include signal, planar germanium rectifiers. **£1.00**
9. **ASSORTED POTENTIOMETERS AND PRESETS**—carbon, wire-wound, rectilinear, etc. **£1.00**
10. **MULTIMETER BARGAIN**—Essential to every experimenter. 20,000 Ω/V, .5–1000V AC/DC, 50 μA5–500mA, 10 Ω–10K. Plus unique built in 465kHz 1F alignment oscillator and 1kHz Signal Tracer—robust protective case, leads. **£9.95**
11. **25 WIREWOUND RESISTORS** 2-10 watt, many useful values. **£1.00**

**FREE**—All orders over £10 get a free junk box filler pack. Lots of useful bits. (My order is over £10). **FREE**

**Arrow Electronics Ltd., Leader House, Coptfold Rd., Brentwood, Essex CM14 4BN**

**ONLY PACKS 1-5 INCLUSIVE AVAILABLE FOR EXPORT.**

Prices include V.A.T., POSTAGE 40p but free if you order £5 or over to: (your name and address)

Please print clearly and give your postcode and post with cheque, postal order or cash to:

**ARROW ELECTRONICS LTD.**  
LEADER HOUSE, COPTFOLD ROAD,  
ESSEX CM14 4BN.

OR you may collect at our shop (open 9-5 Mon.-Sat. Closed PM Thursday).

# WORKSHOP MATTERS

By Harry T. Kitchen

## Signal Sources

In an earlier article I covered the choice of a multimeter, and in the next article or so I want to cover signal sources. These can be very broadly defined as a signal that is injected into equipment in order to ascertain whether it is working within its parameters, or if it is not working, to ascertain where it has failed. Such sources cover a vast range: from the "tickle" induced into sensitive stages by an educated finger, to the more sophisticated sources. It is these that I want to discuss.

Let us start by drawing a division between the source that is very closely controlled for frequency and voltage accuracy, and that which is less closely controlled if at all. The former is defined as a generator, the latter as an oscillator.

## A.F. Sources

If you are an a.f. or hi fi type then you will almost certainly be interested in such sources as a means of checking your equipment, or if you are into design work, of checking your designs. What should such a source offer? Opinions differ, but my order of priorities, in descending order, would be:

- 1 Very low distortion.
- 2 High frequency accuracy
- 3 High voltage output accuracy
- 4 High resetting accuracy of frequency and voltage
- 5 Wide frequency range
- 6 Square wave output

Having detailed my order of priorities, let me now justify them! Most modern audio equipment has distortion figures that are extremely low, and if we are to measure these, or design amplifiers that are similarly rated, then our signal source must have an output that has distortion figures that are very much lower; a factor of  $\times 10$  is not unrealistic for work of the highest calibre.

Faced with equipment with a distortion figure of 0.01 per cent we must use a source that has, at the most, 0.001 per cent distortion. It is possible to reduce this distortion figure, but then our results will be less reliable.

## Frequency Response

For the plotting of frequency response curves, a high degree of frequency scale calibration is necessary, and this also helps when "spot" frequencies must be set. Greater accuracy is possible if the frequency varying element—almost always resistance or capacitance with modern designs—has some form of slow motion tuning incorporated. This has the additional advantage of permitting frequency sweeping to be effected.

Another important factor is freedom from frequency voltage bounce, an effect where the output voltage literally bounces up and down when the frequency is altered. It is very difficult to make any source completely free from bounce, but it should be closely controlled, and should settle down very rapidly.

The output voltage should be closely controlled so that it is possible to accurately set any required voltage. This can be effected by calibrated attenuators, sometimes complimented by an output meter that monitors the voltage applied to the attenuators. There should be at least two attenuators, one for the coarse adjustment of output voltage, the other for fine adjustment.

Both frequency and output voltage should be capable of being reset to any previously set figure, and should be adequately buffered so that neither is affected by any external loads. This is not always the case with simple designs where the output is extracted directly from the oscillator, and it is quite possible to alter both frequency and output voltage by an appreciable amount by varying the load applied to the output terminals. This can invalidate any results obtained; as such, simple designs must be used only for non-critical work.

Although it is accepted, by tradition, that the audible frequency range is from around 20Hz to 20kHz, the source must possess a much wider frequency range, ideally 10Hz to 100kHz. Such a wide frequency range is essential to check reproducing equipment for vagaries that, though they may well be outside the audible bandwidth, may yet affect the reproduction.

Subsonic instability may be inaudible, yet it can modulate the reproduced signal and cause audible distortion. Similarly, supersonic instability may be well above 20kHz, yet it can degrade the signal and in extreme cases it is not unknown for multi-unit 'speakers to have the tweeters ruined through overheating of the voice coil due to an amplifier oscillating vigorously and applying an almost perfect square wave to the 'speaker. With a wide frequency source, the amplifier can be checked for misbehaviour at both ends of the frequency spectrum.

## Square Wave

If you own an oscilloscope you will find a square wave output invaluable. This is, in comparison to the sinewave output we have so far considered, a signal having perfectly vertical sides, and perfectly parallel tops and bottoms.

The square wave is usually derived from the sinewave oscillator and thus has the same frequency. The two outputs sometimes share the same output terminal and attenuators, though separate attenuators and output terminals increase

the versatility of the instrument since both waveforms can be used simultaneously if desired.

The great attraction of a square wave is the ease, and speed, with which it can tell the practised user the characteristics of the equipment through which it has passed. If the verticals slope and the originally sharp corners are rounded off, it indicates a poor high frequency capability.

Sloping tops and bottoms indicate a poor low frequency capability. The greater the sloping and rounding-off, the worse the h.f. or l.f. response.

## Supplies

Last, but not least, the power supply used for the source, and the case in which it is placed. Batteries are expensive, and if the equipment is much used, have a limited life. A mains supply thus seems to be attractive.

For certain work the mains power supply is no disadvantage, but at low levels the mains frequency of 50Hz, and some of its harmonics can cause problems. For critical low level work I believe that there is no alternative to battery power, expensive though it may be.

For screening, a metal case is essential, but this should be well insulated on the outside, by the liberal use of paint or Vinyl covering, so that if two cases touch there is no unintentional earth path between them that may cause problems with earth-loops.

## Bind it

It's so easy and tidy with the Easibind to file your copies away. Each binder is designed to hold approximately 12 issues and is bound and blocked with the Everyday Electronics logo. Gold letraset supplied for self blocking of volume numbers and years.

Price £4.10 including postage, packing and V.A.T.. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd, Post Sales Dept, Lavington House, 25 Lavington St, London SE1 0PF

It's easy with **EASIBIND**

## Order Form

**Everyday ELECTRONICS**

I enclose p.o./cheque value ..... for ..... binders. Years required .....


(BLOCK LETTERS PLEASE)

Name .....

Address .....

Date .....
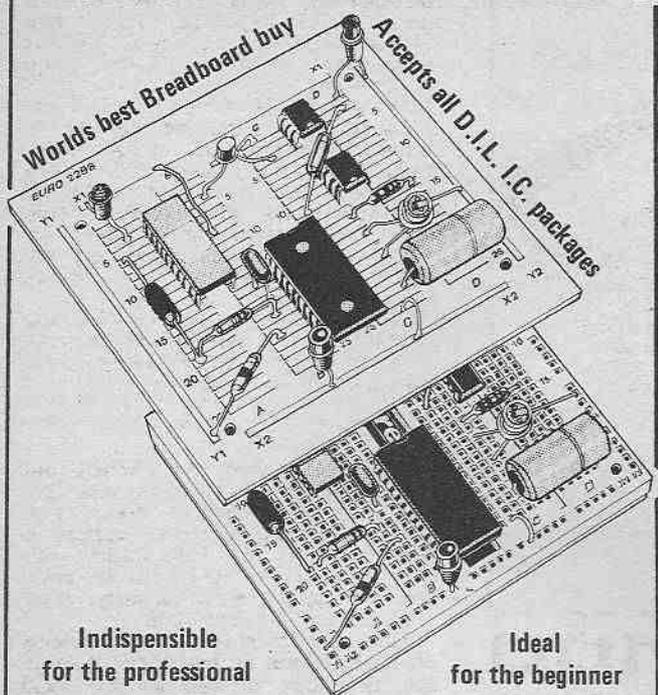
## First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

### First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects). Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

### Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's or

### And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales, EE 5.  
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.

Please send me:—

- |                       |          |                       |        |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard      | @ £ 6.20 | <input type="radio"/> |        |
| or 2 EuroBreadBoards  | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick   |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> |        |

All prices are applicable from Jan. 1st 1980 and include VAT and PP but add 15% for overseas orders.

Name .....

Company .....

Address .....

Tel. No .....

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

# MITRAD

(MIDLAND TRADING COMPANY)

## ZETRON!

TAKE YOU INTO THE  
EIGHTIES WITH TWO REALLY SUPERB  
PIECES OF MODERN TECHNOLOGY

### GENTS ALARM CHRONO (12/24 CYCLE)

A really superb watch and module with numerous facilities available. It can be set as a 12 or 24 hour watch with Hours, Minutes, Seconds, AM/PM and Weekday indication always on display. A unique calendar is built into the watch. You can have month followed by date or date followed by month, it's entirely up to you. A 24-hour alarm can be set to anytime within a 24-hour period whether in the 12 or 24-hour cycle.

The Chronograph has a twelve hour capacity and runs at 1/10 s. split and lap mode facilities are available.

Battery Hatch. Mineral Glass. Long life battery and a closely woven adjustable Stainless Steel strap finish the watch off with impeccable looks.



**ONLY  
£16.50!**

### GENTS QUARTZ ANALOGUE

A truly superb timepiece with extreme accuracy.

A choice of two colours on this outstanding watch are available, Blue or White.

The calendar in the watch can be set to give a readout in either French or English, with date indication being automatic.

An infinite adjustable Stainless Steel strap is built in as part of the watch.

The watch is fitted with a Long Life battery and comes with luminous markings to aid night-time vision.



**ONLY  
£19.95**

**ZETRON! WHERE RELIABILITY, STYLE,  
AND ELEGANCE REALLY COUNT**

Just look at the following points.

- |  |  |
|--|--|
| (i) 48-hour despatch.                          | (iii) 10 day money back guarantee.           |
| (ii) Full instructions and 12 month guarantee. | (iv) Free presentation case with each watch. |

For further information turn to page 000.


P/P per item 85p which includes insurance.

Cheques or PD's made payable to MITRAD and sent to (Dept.

58, Windmill Ave, Kettering, Northants NN16 8PA

Telephone: (0536) 522024

## EE SPECIAL REPORT

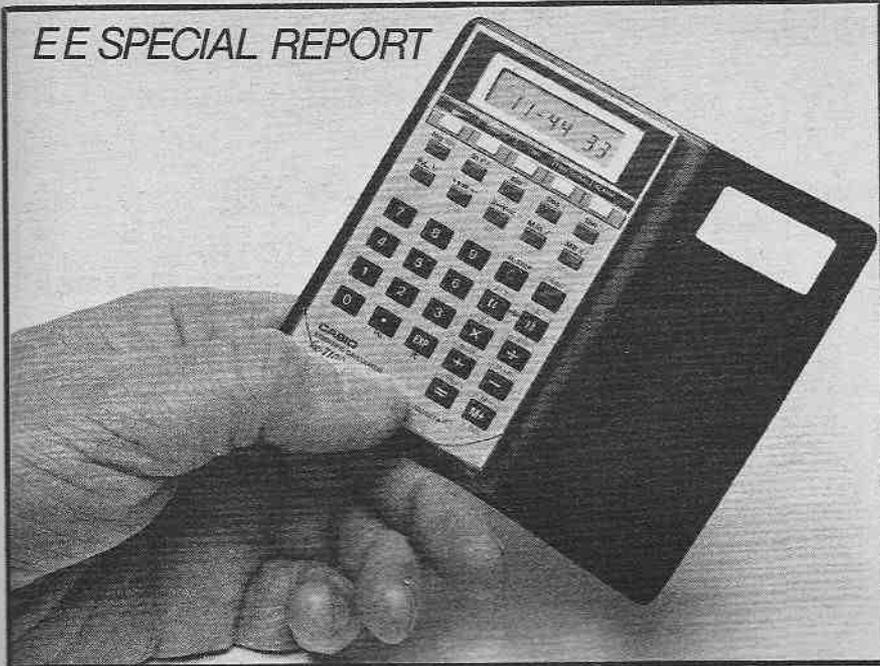

# THE CASIO fx-7100 SCIENTIFIC CALCULATOR

**E**LECTRONIC pocket calculators have been with us for almost ten years now and electronic digital watches and clocks for a little less. It was only a matter of time before the two were combined. This time has come, and it is no surprise to find that it is from a Japanese company. Casio, the world's leading calculator manufacturer have just released some calculating timepieces, one of which is the fx-7100. Strangely though, this is only called a "scientific calculator".

The fx-7100 is truly a pocket (or handbag) sized instrument, measuring only 98 x 65 x 10mm in its leather-look wallet having a window over the display. It is similar in size to a season ticket/bankers card wallet and can thus be carried with comfort in the breast pocket for example.

The display is the more economical and popular liquid crystal type (5mm high digits). Current consumption is therefore very low giving long life to the two silver oxide batteries fitted. Depending on the battery types obtained, continuous use over 9 to 12 months can be expected.

There are thirty-seven actual keys on the unit, most of them having dual functions and some having three. At first, this multilayer key arrangement caused problems, with wrong functions being keyed in, but in a short time one becomes accustomed to the key shift modes. Also the small size of the keys and the closeness in relation to the human digit takes a little getting used to.

### CLOCK

The clock has a 12-hour format with a PM flag to indicate the same.

The readout is in hours, minutes and seconds and is accurate to within  $\pm 3$  seconds per day. The clock is also equipped with an alarm.

The decimal keyboard is used for setting the alarm time which is entered in hours and minutes. This is much more convenient than the step setting on most digital watches. The new alarm time overwrites the existing alarm time. Once activated a piercing modulated tone sounds for 20 seconds. The alarm facility can be "switched" out. Alarm ready state is shown on the displays by a "sound" flag.

### STOPWATCH

Another useful facility is the stopwatch. This counts in 1/100ths of a second up to 0.01 secs short of 10 hours. This stopwatch once started can be stopped in either of two modes and these modes may be alternated throughout the timing sequence.

In one mode, the "watch" can be stopped and when restarted will continue to count from the displayed time. In the other mode, the counting sequence carries on counting internally displaying the halted time. When operated a second time, the display leaps to the counting time. Very useful for sports events where lap times can be recorded. The stopwatch would also be very useful in the electronic workshop where time delay circuitry is being tested and time constants observed.

### COUNTDOWN

The housewife is also catered for. In the kitchen, the device may be

used as a cooking timer when put in its countdown mode. Here the cooking time may be entered by means of the decimal keyboard, and when initiated will count down to zero at which time the alarm sounds, again for 20 seconds.

Countdown is from a maximum 9 hours 59 minutes or may be in minutes only from 99 minutes maximum. This is a repeat timer i.e. when it reaches zero, it reverts to the set countdown time. This facility should prove very useful once again for sport events such as when competitors set off at pre-arranged intervals, e.g. car rallying.

During both countdown and count-up (stopwatch), the display may be returned to regular time display without affecting the counting.

### CALCULATOR

Calculations may be carried out without affecting any clock functions that may be running. A break from calculation back to clock function is possible, but any information you have accumulated and wish to retain must be transferred to memory. Other registers will be cancelled.

This tiny machine has enormous ability handling no less than 39 scientific functions as well as the usual basic calculations including constants for  $+/-/\times/\div/x^2/x^1/y$ .

Positive and negative numbers may be entered up to 8-digits in length (with or without decimal point) or in exponent form, 6-digits with 2-digit exponent up to  $10^{99}$ . The accuracy of the scientific functions is  $\pm 1$  in the 8th digit.

We were pleased to see the inclusion of "brackets" on this machine which allows quite complex formulae to be "worked out" without recourse to the memory and inverse keys as with many other calculators. A five-deep nest of brackets is available.

A statistical mode package is included which calculates all the common statistical functions.

As would be expected, a memory is included. This can be added to, subtracted from, recalled and overwritten. Memory contents may also be exchanged with display register. Whenever there is a number in memory this calls yet another flag, M, to appear on the display.

A useful feature included in the design is to exchange the contents of the display register with the working register. This enables the last but one entered number to be recalled.

These and the rest of the functions, including the versatile percentage key, are contained in a comprehensive 70-page manual that comes with the calculator.

The recommended retail price of the fx-7100 is £27.95, but can be obtained from Tempus (Dept. EE), Talk of the Town, 19-21 Fitzroy Street, Cambridge CB1 1EH, at a discount price of £24.95 including postage and packing.

A larger version (135 x 75 x 12mm, with 6mm high display digits) the fx-8100 Scientific Calculator/Chronograph has all the facilities of the fx-7100 and more and costs the same.

### LIGHTING CONTROL KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

Directly replace conventional light switch and control up to 300W of lighting. No mains rewiring. Insulated touchplates. Easy to follow instructions.

**TD300K TOUCHDIMMER.** Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamps. Neon lamp helps find the switch in the dark. **£6.50**

**TDE/K Extension kit for TD300K for 2-way switching etc.** **£1.50**

**TSD300K—TOUCH SWITCH& DIMMER.** Single touchplate, small knob controls brightness. **£5.50**

**TSA300K—AUTOMATIC.** Single touchplate. Time delay variable 2 secs. to 3/2 mins. **£4.30**

**LD300K—LIGHTDIMMER KIT** **£2.90**

### INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	19p
AY-5-1224 Clock	£2.80
AY-5-1230/2 Clock/Timer	£4.20
AY-3-1270 Thermometer	£8.20
ICL7106 DVM (LCD drive)	£7.80
LM377 Dual 2W Amp	£1.85
LM379S Dual 8W Amp	£3.50
LM380 2W Audio Amp	80p
LM382 Dual low noise preamp	£1.00
LM386 250mW low voltage amp	75p
LM1830 Fluid Level Detector	£1.50
LM2907 1v Converter	£1.40
LM3909 LED Flasher/Oscillator	55p
LM3911 Thermometer	£1.20
LM3914 Dot/Bar Driver	£1.30
MM57160 (stack) Timer	£5.90
MM74CS11 4-digit display controller	£3.50
MM74CS15 7-segment BCD converter	85p
MM74CS26 4-digit counter with 7-seg outputs	£4.50
S568B Touchdimmer	£2.50
SS263 Touchswitch 16-way	£4.85
TB800 5W Audio Amp	55p
TB8104S 7W Audio Amp	85p
TDA1024 Zero Voltage Switch	£1.00
TDA2020 20W Audio Amp	£2.85
TN1034E Timer	£1.88

All ICs supplied with data & circuits. Data sheets only 5p

### DIGITAL VOLTMETER/ THERMOMETER KIT



Based on the ICL7106. This Kit contains a PCB, resistors, capacitors, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply. (PP3 battery) **£20.75**

#### LEDs



0.1" Red	9p
0.1" Green	12p
0.1" Yellow	12p
0.2" Red	9p
0.2" Green	12p
0.2" Yellow	12p
0.2" clips	20p
Rectangular Red	25p
Rectangular Green	25p

#### DISPLAYS



DL304 Red 0.3" c.c. pin compatible with DL704	70p
DL307 Red 0.3" c.c. pin comp.	70p
DL707	70p
DL847 Red 0.8" (pin comp. DL747) c.a.	£1.80
DL950 Red 0.8" c.c. (pin comp. DL750)	£1.80
DL727 Dual 0.5" c.a. Red	£1.50

### MINI TRANSFORMERS



Standard mains primaries 240V a.c. 100mA secondaries  
6-0-6V **80p**  
9-0-9V **85p**  
12-0-12V **90p**

### D.I.L. IC SOCKETS

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	36p

Soldercon Pins 50p/100

### 24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1KW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac. PCBs & full instructions. **£14.90**

**CT1000K Basic Kit** **£17.40**  
**CT1000KB with white box (56/131 x 71mm)** **£22.50**

### CAPACITORS

<b>Polyester 250V</b>			
0.01	6p	0.22	12p
0.022	6p	0.33	12p
0.033	7p	0.47	15p
0.047	7p	0.68	18p
0.068	7p	1.0	24p
0.1	7p	1.5	27p
0.15	11p	2.2	31p

<b>Electrolytic A=Axial R=Radial</b>			
63V	1.0 R	16V	10 R 3p
	2.2 R		22 R 3p
	4.7 R		33 R 3p
	10 R		47 R 4p
	47 R		100 R 5p
25V	22 R		220 R 6p
	47 A		470 R 9p
	100 A		1000 R 15p
	220 A	10V	47 A 6p
	470 A		100 A 6p
	1000 A		220 A 6p

<b>Tantalum (bead)</b>			
35V	0.1	7p	10V 22 12p
	0.22	7p	6.3V 33 12p
	0.47	7p	47 14p
	1.0	7p	3V 100 14p
25V	2.2	8p	
	4.7	9p	
	10	12p	

### VOLTAGE REGULATORS

Available in 5V, 12V & 15V versions.  
78L series 100mA pos. **26p**  
78L series 100mA neg. **80p**  
78 series 1A pos. **52p**

**LM317T adjustable 1.2V-37V 1.5A** **£1.80**

### MINI KITS

These KITS form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB short instructions and all components.

#### TEMPERATURE CONTROLLER/THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. PCB (4 cm sq.) potentiometer, plus all other components included with instructions. **500W £3.20 1KW £3.50**

#### SOLID STATE RELAY

Ideal for switching motors, lights, heaters etc. from logic. Opto isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

#### BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

#### BURST FIRE/PROPORTIONAL TEMPERATURE CONTROLLER

Based on the TDA1024 Zero Voltage Switch this kit contains all the components required to make a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. **1.5KW £5.25 3KW £5.55**

### BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black or white.  
**PB2 95x71x35mm** **65p**  
**PB3 115x95x37mm** **78p**

### RESISTORS

<b>ZENER DIODES</b>		1W 22ohm-10M Pack of 10 (one value) 10p
400mW 3.3V-30V	8p	10 packs (10 values) 80p
1.3W 7.5-30V	15p	

### TRIACS

400V Plastic Case (Texas)		
3A	48p	18A 90p
8A	58p	20A 165p
12A	88p	25A 190p
6A with trigger	80p	
8A isolated tab	55p	
Diac	18p	

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 35p P&P. MAIL ORDER—CALLERS WELCOME BY APPOINTMENT.



**TK Electronics (EE)**

106 STUDLEY GRANGE ROAD  
LONDON W7 2LX. TEL. 01-5799794



# NEW FM/AM Receiver from Eddystone Radio



- From the professional stable for the radio enthusiast
- Digital readout
- Long, medium, 3 short-waves plus FM
- 'S' meter
- AFC AM and FM
- BFO/Product Detector for CW and SSB reception
- Tape recorder output
- Fitted telescopic aerials
- Mains or 12V D.C. operated

Write or phone for details TODAY

## Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England  
Telephone: 021-475 2231 Telex: 337081

A GEC-Marconi Electronics Company.



*It's faster and more thorough than classroom learning: you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.*

**Understand Digital Electronics**

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

**DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.50**

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:  
**Book 1** Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.  
**Book 2** AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.  
**Book 3** Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.  
**Book 4** Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.



**DESIGN OF DIGITAL SYSTEMS £11.50**

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.

**Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.  
**Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.  
**Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.  
**Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).  
**Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.  
**Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.



**Flow Charts and Algorithms**


are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.

**THE ALGORITHM WRITER'S GUIDE £3.75**

explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.

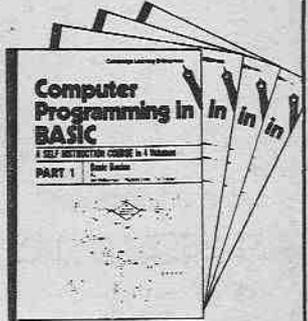**Microcomputers are coming - ride the wave! Learn to program.**

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.



**COMPUTER PROGRAMMING IN BASIC £7.50**

**Book 1** Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.  
**Book 2** High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.  
**Book 3** Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.  
**Book 4** Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

**THE BASIC HANDBOOK £11.50**

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

**FORTRAN COLORING BOOK £5.40**

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

**A.N.S. COBOL £4.40**

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

**GUARANTEE - No risk to you**

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Please send me:-

- ....Digital Computer Logic & Electronics @ £7.00
- ....Design of Digital Systems @ £11.50
- ....Algorithm Writer's Guide @ £3.75
- ....Computer Programming in BASIC @ £7.50
- ....BASIC Handbook @ £11.50
- ....Fortran Coloring Book @ £5.40
- ....A.N.S. Cobol @ £4.40

All prices include worldwide surface mailing costs (airmail extra) - IF YOUR ORDER COMES TO OVER £18, DEDUCT £2

Cheques/PO's payable to Cambridge Learning Enterprises or charge to Access/Barclaycard/Diners Club/etc  
 account no. ....

Telephone orders from credit card holders accepted on 0480-67446. Overseas customers (inc Eire) use credit card, or bank draft in sterling drawn on a London bank, or International Money Order (add £1 handling charge.)

Name .....  
 Address .....

.....  
 Cambridge Learning Enterprises, Unit 60 Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England.

# Britain's first comp

**A complete personal computer for a third of the price of a bare board.**

**Also available ready assembled for £99<sup>95</sup>**

## The Sinclair ZX80.

Until now, building your own computer could easily cost around £300 – and still leave you with only a bare board for your trouble.

The Sinclair ZX80 changes all that. For just £79.95 you get *everything* you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to your own cassette recorder and black and white or colour television; everything!

And yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers on the market at several times the price. The ZX80 is programmed in BASIC, and you could use it to do quite literally anything from playing chess to running a power station.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. Once assembled, it immediately proves what a good job you've done. Connect it to your TV set... link it to an appropriate power source\*... and you're ready to go.


### Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs – all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVED and LOADED on to any portable cassette recorder.)
- FREE course in BASIC programming and user manual.
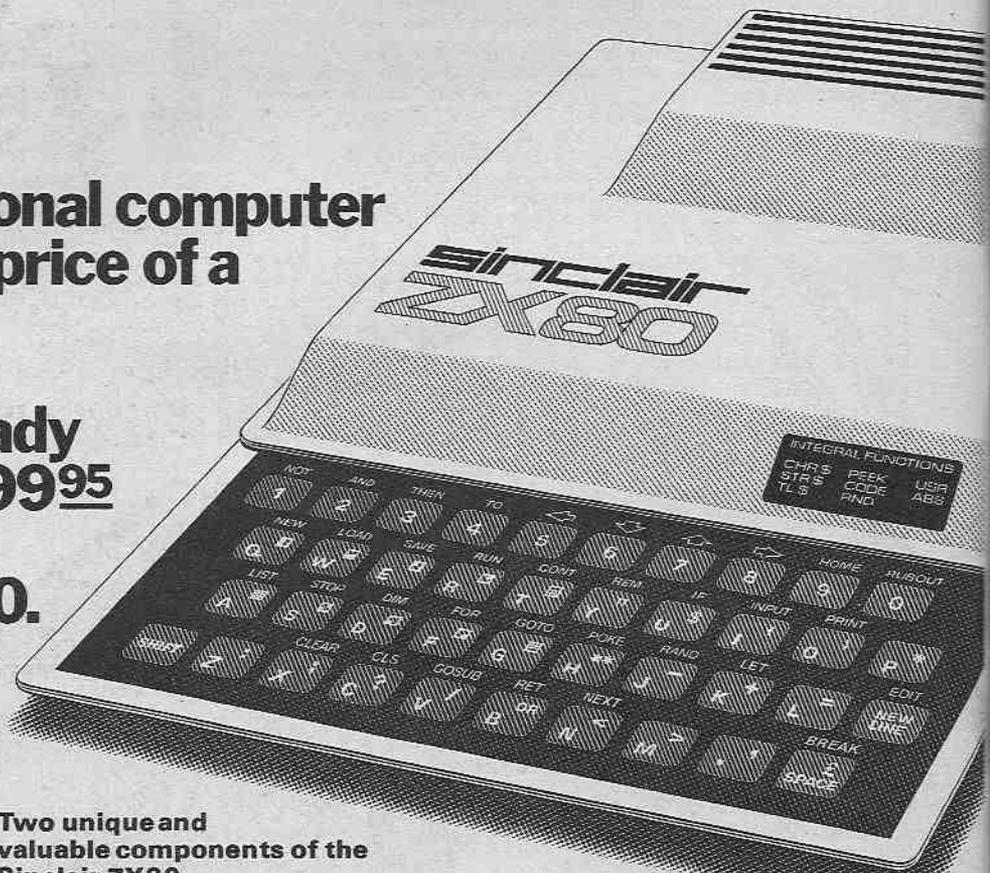
### Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately – see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available – see coupon.)

\*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).



### Two unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.


### The unique Sinclair BASIC interpreter... offers remarkable programming advantages:

- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability – takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input-to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.

- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.


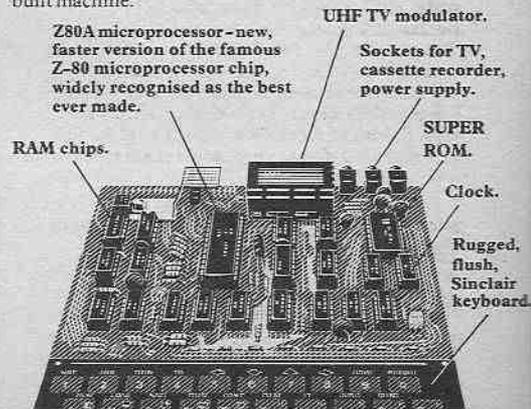
### ... and the Sinclair teach-yourself BASIC manual.

If the features of the Sinclair interpreter listed alongside mean little to you – don't worry. They're all explained in the specially-written 128-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit or built machine.



Everyday Electronics, May 1980

# Complete computer kit.

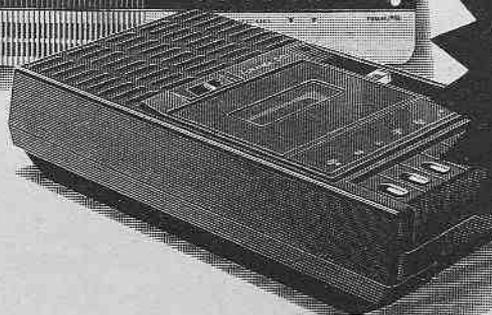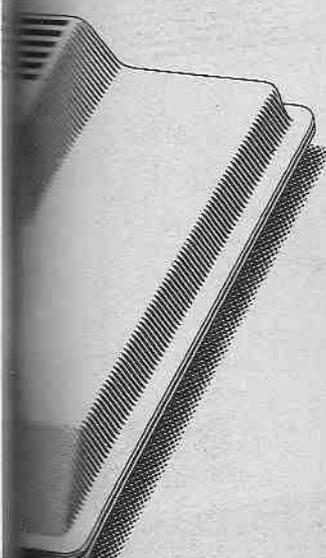

**£79<sup>95</sup>**  
 Including VAT.  
 Including post and packing.  
 Including all leads and components

**Fewer chips, compact design, volume production – more power per pound!**

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer – typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines.

And Benchmark tests show that the ZX80 is faster than all other personal computers.

No other personal computer offers this unique combination of high capability and low price.

**The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!**

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Whether you choose the kit or the ready-made, you can be sure of world-famous Sinclair technology – and years of satisfying use. (Science of Cambridge Ltd is one of the Sinclair companies owned and run by Clive Sinclair.)

To order, complete the coupon, and post to Science of Cambridge for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied.

**sinclair  
ZX80**

**Science of Cambridge Ltd**

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
 Tel: 0223 311488.

Everyday Electronics, May 1980

## Order Form

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
 Remember: all prices shown include VAT, postage and packing. No hidden extras.

Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	
		<b>TOTAL</b>	£

NB. Your Sinclair ZX80 may qualify as a business expense.

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ \_\_\_\_\_  
 Please print  
 Name: Mr/Mrs/Miss \_\_\_\_\_  
 Address \_\_\_\_\_

# KITS FOR SOUND EFFECTS AND OTHER PROJECTS

## PHONOSONICS

DEPT EE83, 22 HIGH STREET,  
SIDCUP, KENT DA14 6EH



### P.E. GUITAR EFFECTS PEDAL

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls. Basic parts with foot switches KIT 42-1 £8-45  
Basic parts with panel switches KIT 42-2 £5-55  
PCB & layout chart PCB 42A £1-57  
Text photocopy £28

### P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit including variable controls affecting the fuzz quality whilst retaining the attack and decay, and also providing filtering. Can be used with other electronic instruments. Set of basic components KIT 56-1 £7-57  
PCB & layout chart PCB 56A £1-78  
Text photocopy £68

### GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit. Set of basic components, PCB & chart KIT 74-1 £4-97  
Text photocopy £39

### P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration. Basic compo, foot switches, PCB & chart KIT 75-1 £5-64  
Basic compo, panel switches, PCB & chart KIT 75-2 £4-08  
Text photocopy £38

### P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control. Set of basic components, PCB & chart KIT 51-1 £3-99

### P.E. AUTO-WAH UNIT

Automatically Wah or Swell sounds with each note played. Basic compo, foot switches, PCB & chart KIT 58-1 £8-43  
Basic compo, panel switches, PCB & chart KIT 58-2 £5-31  
Text photocopy £58

### P.E. THREE CHANNEL SOUND-TO-LIGHT

A simple sound-to-light control. Set of basic components, PCB & chart KIT 52-1 £14-16  
Text photocopy £24

### MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET.

### P.E. PHASER

An automatic 6-stage phasing unit with integral oscillator. Set of basic compo, PCB & chart KIT 88-1 £10-14  
Text photocopy £68

### ELEKTOR PHASING & VIBRATO UNIT

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage. Set of basic components KIT 70-1 £19-11  
PCB & layout chart KIT 70A £2-56  
Text photocopy £67

### P.E. PHASING UNIT

A simple but effective manually controlled phasing unit. Set of basic compo PCB & chart KIT 25-1 £3-52  
Text photocopy £28

### P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses. Set of basic components, PCB & chart KIT 89-1 £3-82  
Text photocopy £78

### P.E. SMOOTH FUZZ

Set of basic components, PCB & chart KIT 91-1 £5-01

### TREMOLO UNIT

A slightly modified version of the simple P.E. unit. Set of basic components, PCB & chart KIT 54-1 £3-23

### WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit. Set of basic components, PCB & chart KIT 28-1 £4-68  
Text photocopy £28

### P.E. MICROPHONE PRE-AMP

Includes preset gain-control to match most microphones, bass roll-off, treble lift, master gain control. Set of basic components, PCB & chart KIT 61-1 £4-20

### P.E. TUNING FORK

Produces 84 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments. Set of basic compo, PCB & chart KIT 46-1 £16-42  
Power Supply compo, PCB & chart KIT 46-2 £6-90  
Text photocopy £97

### P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of KIT 46 is not required. Basic compo, PCB & chart, but excl sw. KIT 69-1 £8-19  
Text photocopy £58

### P.E. DYNAMIC RANGE LIMITER

Presets to automatically control sound output levels. Set of basic components, PCB & chart KIT 62-1 £5-03

### P.E. CONSTANT DISPLAY FREQUENCY COUNTER

An improved version of the project published in P.E. Readout does not count visibly or flicker due to blanking. Set of basic components & PCB KIT 79-2 £32-28  
Text photocopy £78

### TAPE NOISE LIMITER

Effectively reduces tape-recording hiss. Set of basic components, PCB & chart KIT 6-3 £4-13  
Power Supply compo, PCB & chart KIT 6-2 £5-15  
Text photocopy £19

### P.E. DISCOSTROBE

4-channel sound-to-light controller also giving sequential, random or strobe modes of control. Set of basic components KIT 57-1 £20-00  
PCB & layout chart PCB 57A £3-78  
Text photocopy £78

### MANY MORE KITS

for synthesizers, Rhythm Generators, Electronic Pianos and other projects, big, small, simple or complex, are available, plus a range of keyboards, separate components and accessories. Details in our lists.

**COMPONENT SETS** incl all necessary res, caps, s/cs, pots, t/formers. Hardware such as cases, skts, knobs, kbds, etc, are not incl, but most can be bought separately. Fuller details in lists.

### ADD: POST & HANDLING

U.K. orders; under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurances against postal mishaps: add

50p for cover up to £50, £1 for £100 cover, etc., pro-rata, must be added to credit card orders. N.B. Eire, C.L., B.F.P.O. and other countries are subject to higher rates.

### ADD 15% VAT

(or current rate if changed). Must be added to full total of goods, post & handling on all U.K. orders. Does not apply to exports, or to photocopies.

**LIST:** Send stamped addressed envelope with all U.K. requests for free list giving fuller details of our goods. Europe send 25p, other countries send 50p, or equivalent in international reply coupons

**TERMS: C.W.O., MAIL ORDER OR COLLECTION BY APPOINTMENT**  
(TEL: 01-302 6184)



**DIRECT DRIVE VARIABLE CAPACITORS** 5pf @ 75p, 10pf @ 75p, 50 + 50pf @ £1, 125 + 125pf @ 60p, 100 + 200pf @ 60p, 25 + 25 + 25pf @ 75p, WITH S.M. DRIVE. 250 + 250 + 20 + 20 + 20pf @ 75p, 500 + 500 + 25 + 25pf @ 60p, 25 + 25 + 25pf @ £1, 500 + 500pf. With 3/16" Spindle @ 60p.

**CERAMIC TRIMMERS** 2.5 to 6pf, 3 to 10pf, 4.7 to 20pf, 7 to 35pf, 10 to 40pf, all at 15p each.

**EDDYSTONE TRANSMITTING VARIABLE** Type 831. 30 + 30pf (60pf) @ £2.20. 3/16" COIL FORMERS with core at 6 for 25p.

**SUB-MINIATURE 10p AIR SPACED TRIMMER** at 20p each.

**50. BC 107-8-9 TRANSISTOR** untested @ 60p.

**50. PLASTIC BC 107-8-9 TRANSISTORS** untested @ 60p.

**50. PLASTIC PNP TRANSISTORS** untested @ 60p.

**50. OC 71 TRANSISTORS** untested @ 75p.

**25. 5 AMP STUD MOUNTING S.C.R.'s** untested @ 75p.

**50. 1 AMP S.C.R.'s T05** case untested @ £1.

**10. 20 AMP STUD MOUNTING SILICON DIODES** untested @ 60p.

**50. 2 WATT ZENERS** untested assorted @ 80p.

**50. AC 12V TRANSISTORS** branded but untested @ 60p.

**20. PHOTO TRANSISTOR AND DARLINGTONS** assorted untested @ £1.

**10. ASSORTED SLIDE POTENTIOMETERS** for £1.

**10. PUSH BUTTON BANKS** assorted less knobs for £1.30.

**50. DISC CERAMICS** assorted for 50p.

**50. TUBULAR CERAMICS** assorted for 60p.

**20. 10 AMP STUD MOUNTING SILICON DIODES** untested for 60p.

**DISC CERAMICS** 22pf, 33pf, 270pf, 330pf, 2200pf, all 20p doz., -1uf 25v.w., -1uf 63v.w., -22uf 6v.w., all at 5p each.

**MAINS TRANSFORMERS** 240 Volt Input. Type 1. 24 volt Tapped at 14 volt 1 amp @ £1.30 (P&P 25p). Type 2. 30-0-30 volt 500 mA @ £1.30 (P&P 25p). Type 3. 45 volt 8 amp at £4.50 (P&P 95p). Type 4. 20 volt 1 amp Twice, 10 volt 1 amp Twice @ £4.50 (P&P 95p). Type 5. 45 volt 2 amp, 45 volt 500mA @ £3.50 (P&P 85p). Type 6. 16 volt 2 amp @ £1.60 (P&P 25p). Type 8. 30 volt 1-75 amp @ £1.60 (P&P 25p). Type 9. 13 volt 1 amp @ £1.60 (P&P 25p).

**SMALL ELECTROLYTIC CAPACITORS** Wire ended 5000uf, 15v.w., @ 20p each, 1000uf 10v.w., @ 3 for 20p, 100uf 25v.w. @ 16p each.

**200 RESISTORS** 1/2 WATT. Assorted values for 75p.

**MINIATURE TRANSISTOR TRANSFORMERS** input Types, impedance ratio 100K to 1K @ 35p, Ratio 150K to 1K @ 35p, Ratio 20K to 1K @ 35p. Driver Types, 10K to 2K @ 35p. Output Transformers 250mW 1-2K to 8 ohm @ 35p, 250mW 500 ohm to 8 ohm @ 35p, 500mW 500 ohm to 8 ohm @ 35p.

**PLASTIC POWER TRANSISTORS** BD 135, BD 136, BD 175, BD 187. All 25p. TIP 33 @ 20p, BD 207 @ 50p.

**WIRE WOUND POTENTIOMETERS** 2 Watts 2K, 5K, 10K, 4 Watt 100K. All at 30p each.

**VHF WIRE ENDED MINIATURE R.F. CHOKES** 10uH, 30uH, 330uH. All at 7p each.

**THYRISTORS (S.C.R.'s)** 10 amp Type 100 PIV @ 28p, 400 PIV @ 55p, 800 PIV @ 85p, 5 amp 700 PIV @ 50p, 200 PIV 300mA TIC 47 @ 18p.

**VHF FETS** BF 256C @ 4 for 75p, E304 @ 30p, 4 for £1.

**DUAL GATE MOS FETS** LIKE 40673 @ 33p, 4 for £1.10.

**ERIE MINIATURE RED CAP 100 v.w., DISCS** .01uf at 5p each.

**MINIATURE POLYESTER CAPACITORS** 1uf 63v.w., @ 5p, 4-7uf 63 v.w., @ 10p, 10uf 63 v.w., @ 15p.

Please add 20p for post and packing on U.K. orders under £2. Overseas postage charged at cost.

## J. BIRKETT RADIO COMPONENT SUPPLIERS

25 The Strait, Lincoln LN2 1JF Tel. 20767

**OHIO SCIENTIFIC Superboard** 2. Assembled 50Hz model £150 + 15% vat, post free.

\*\*\*\*\*  
\* Special offer:- If bought with \*  
\* superboard these items are at \*  
\* the reduced price shown first. \*  
\* Also sold separately at the \*  
\* bracketed prices. Add 15% vat. \*  
\* Modulator and power supply \*  
\* kit £4-95 (£7-95). 4K extra ram \*  
\* £18-40 (£24). Case £19 (£21). \*  
\* Cassette recorder £12-13 (£14-74) \*  
\*\*\*\*\*

**SINCLAIR PRODUCTS** New 10MHz scope £145. Ptm200 £51-95, case £2-07, adaptor £4-03, connector kit £13-95. Microvision tv £91, adaptor £6-88, Pdm35 £34-23, adaptor £4-03, case £2-07. dm350 £76-70, dm450 £102-17, dm235 £55-58, rechargeable batts. £7-99, adaptor £4-63, case £3. Enterprise prog. calculator + accessories £19-95.

**COMPUTER GAMES** chess champion 6 £49-95. Chess challenger 7 £24. Phillips G7000 home computer £149. Videopaks £12-95. Atari videocomputer £147. Cart-rides £14-85.

**TV GAMES** AY-3-8500 + kit £7-26. AY-3-8600 + kit £17-26. Stunt cycle chip kit £18-86. AY-3-8603 chip £13-63.

**BI-PAK AUDIO MODULES** s450 £25-06. AL60 £25-06. Pa100 £17-33. Spm80 £4-74. Bm180 £6-08. Stereo 30 JC21 5W.


**IC AUDIO AMPS** with pcb. JCI2 6W £2-06. JC20 10W £3-14.

**BATTERY ELIMINATORS** 3-way type 6/7/9/300ma £2-84. 100ma radio type with press-studs 9v £3-57. 9-9v £4-79. Car Converter 12v input, output 4.5/6/7/9/300ma £2-66.

**BATTERY ELIMINATOR KITS** 100ma radio types with press-studs 4.5v £1-49, 6v £1-49, 9v £1-49, 11-4.5v £1-92, 6-1-9v £1-92, 9-9v £1-92. Stabilised 8-way types 3/4/5/6/7/9/12/15/18v 100ma £2-60, 1 Amp £5-50, stabilised power kits 2-18v 100ma £2-98, 1-30v 1A £6-75, 1-30v 2A £12-10, 12v car converter 6/7/9v 1A £1-35.

**T-DEC AND CSC BREAKBOARDS** s-dec £3-79, t-dec £4-58, u-dec £4-69, u-dec £7-16, exp4b £2-64, exp300 £6-61, exp350 £3-62, exp325 £1-84.

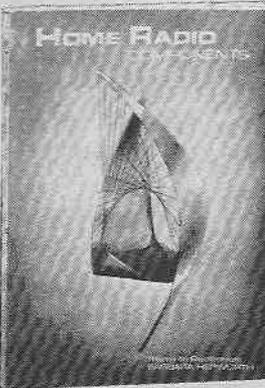**SWANLEY ELECTRONICS** Dept. EE, 32 Goldsei Rd., Swanley, Kent Post 35p extra. Prices include VAT unless stated. Official and overseas orders welcome. Lists 27p post free. Mail order only.



## Top Priority for every constructor- HOME RADIO COMPONENTS CATALOGUE

- Over 2,000 items clearly listed.
- Profusely illustrated throughout.
- Over 100 A-4 size pages.
- Bargain list included free.

Send cheque or P.O. for £1-30.


**HOME RADIO Components LTD.** Dept. EE, P.O. Box 92, 215 London Rd. Mitcham, Surrey. 01-648 8422

# Conquer the chip.


Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

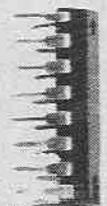Learn the technology of the future today in your own home.



## ELECTRONICS

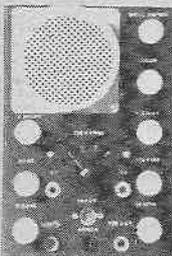

Build your own oscilloscope.

Learn to draw and understand circuits.

Carry out over 40 experiments.

## DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



## COMPUTER TECHNOLOGY


Learn to operate and programme your own home computer.


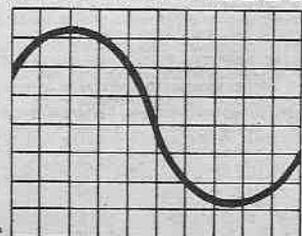
# FREE BROCHURES



No previous knowledge is necessary.  
— Just clip the coupon for a brochure



## TUTORCOURSE ELECTRONICS

Please rush me details of your  
ELECTRONICS COURSE

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_ **EER5**  
Block Caps. Please

Post now, without obligation to:

**British National Radio  
& Electronics School.**

P.O.Box 156, Jersey, Channel Isles

**ELECTRONIC BOOKS**

Ref.	Title	Price
126	BOYS BOOK OF CRYSTAL SETS	25p
200	HAND BOOK OF PRACTICAL ELECTRONIC MUSICAL NOVELTIES	50p
202	HANDBOOK OF IC EQUIVALENTS AND SUBSTITUTES	100p
207	PRACTICAL ELECTRONIC SCIENCE PROJECTS	75p
208	PRACTICAL STEREO AND QUADROPHONY HANDBOOK	75p
218	BUILD YOUR OWN ELECTRONIC EXPERIMENTERS LABORATORY	85p
221	28 TESTED TRANSISTOR PROJECTS	85p
222	SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS	95p
224	50 CMOS IC PROJECTS	95p
225	A PRACTICAL INTRODUCTION TO DIGITAL ICs	95p
226	HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS	120p
227	BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS	125p
RCC	RESISTOR COLOUR CODE DISC CALCULATOR	20p
BP1	FIRST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES	60p
BP7	RADIO AND ELECTRONIC COLOUR CODES AND DATA CHARTS	25p
BP14	SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES	110p
BP32	HOW TO BUILD YOUR METAL AND TREASURE LOCATORS	95p
BP43	HOW TO MAKE WALKIE-TALKIES	125p
BP48	ELECTRONIC PROJECTS FOR BEGINNERS	135p
BP56	ELECTRONIC SECURITY DEVICES	150p
BP57	HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE	150p
BP58	50 CIRCUITS USING 7400 SERIES ICs	135p
BP59	SECOND BOOK OF CMOS ICs PROJECTS	150p
BP61	BEGINNERS GUIDE TO DIGITAL TECHNIQUES	85p

Please add 20p p & p per book. No VAT on books. Send SAE for full list of Babani Books

DIL SOCKETS		ANTEX SOLDERING IRONS		VERO-BOARDS	
8 pin	16p	C-15W	400p	2 1/2 x 5	55p
14 pin	11p	CCN-15W	415p	3 1/2 x 5	48p
18 pin	12p	CX-17W	420p	3 1/2 x 3 1/2	58p
18 pin	24p	X25	420p	3 1/2 x 17	222p
IC INSERTION/EXTRACTION TOOL		C-15W Kit	570p	No track cutting	185p
		Spare Bits	50p	Pkt. of 100 pins	35p
		Stand	160p	Insertion Tool	100p
				S.F. Cutter	85p

TRANSISTORS		LINEAR ICs		TTL/CMOS		VOLTAGE REGULATORS	
AC126/7	25p	CA3046	70p	7400	15p	4017	80p
AC126	25p	CA3080E	75p	7401	15p	4018	80p
AC176	25p	CA3089E	225p	7402	15p	4019	45p
AD149	70p	CA3090	375p	7403	15p	4022	100p
AD161/2	45p	CA3140E	50p	7404	17p	4023	22p
BC107/8	11p	ICL8038	340p	7408	19p	4024	50p
BC109	12p	LF356P	95p	7410	15p	4027	50p
BC177/8	17p	LM301A	75p	7413	30p	4030	35p
BC178	18p	LM309K	135p	7414	60p	4046	110p
BC182/3	10p	LM311	120p	7416	27p	4050	49p
AC184	11p	LM324	70p	7420	17p	4049	45p
BC212/3	11p	LM339	75p	7427	34p	4051	80p
BC214	12p	LM348	95p	7430	17p	4058	600p
BC548	18p	LM377	175p	7432	30p	4069	20p
BCY71/2	22p	LM380	90p	7440	17p	4070	20p
BC131/2	50p	LM381AN	180p	7447A	60p	4081	20p
MPSA12	50p	LM710	50p	7448	80p	4093	120p
TIP31A	58p	LM741	20p	7450	17p	4411	£11
TIP32A	68p	LM748	35p	7470	36p	4502	120p
TIP33A	80p	LM3900	70p	7473	30p	4503	70p
TIP34A	115p	LM3909	100p	7474	24p	4511	150p
TIP41A	65p	LM3911	130p	7475	36p	4516	110p
TIP42A	70p	LM4136	120p	7476	35p	4520	90p
ZTX108	12p	MC1310P	150p	7483	90p	4528	120p
2N2219A	25p	MC1458	55p	7486	34p	4584	90p
2N2222A	25p	MC3340P	120p	7490	35p		
2N2369A	20p	MC3360P	120p	7489	175p		
2N2546	50p	NE531	140p	7492A	46p		
2N2926	8p	NE555	22p	7493	33p		
2N3053	30p	NE560	70p	74107	34p		
2N3055	25p	NE567	175p	74121	28p		
2N3442	140p	SN76003N	175p	74123	55p		
2N3773	300p	SN76013N	140p	74141	70p		
2N3819	25p	SN76013ND	120p	74154	100p		
2N3702/2	12p	SN76023ND	120p	74157	70p		
2N4123	27p	SN76033N	175p	74180	100p		
2N4401	27p	TBA641B1T	225p	74181	100p		
2N5191	83p	TBA800	100p	74184	120p		
2N5194	90p	TBA810S	110p	74198	150p		
2N5245	40p	TCA940E	175p				
2N5401	50p	TDA1022	600p				
2N5457/8	40p	TL072	90p				
2N5459	40p	TL074	150p				
2N6107	40p	TL081	48p				
2N6254	130p	TL084	130p				
2N6247	190p	TL082	90p				
2N6290	85p	ZN414	100p				
40873	75p	ZN425E	400p				
40871/2	90p	ZN1034E	200p				

OPTO-ELECTRONICS		MULTIMETERS	
Red LEDs	Displays	Pocket Multimeter	5 00
0.125" 13p	DL707 130p	LT22 (20K/V)	12 00
0.2" 14p	DL747 240p	Microtest 60R	16 00 P & P 0-75
Green	FND500 110p	Supertester 680R	33 50 P & P 1-00
0.125" 16p	FND507 110p		
0.2" 20p	ORP12 90p		
Clips	3p		

EXPERIMENTER BREADBOARDS		STABILISED POWER SUPPLY	
No soldering suitable for DIL ICs		400mA	3V 6V 7.5V 9V
EXP325 (1 IC up to 22 pin)	170p		5-10
EXP 300 (up to 5 x 14 pin)	575p		
EXP600 (up to 1 x 40 pin)	830p		
EXP350 (up to 2 x 14 pin)	3-15		

PROTO BOARDS SOLDERLESS		ULTRASONIC TRANSDUCERS	
Socket Strips/Bus Strips/Blinding Posts mounted on sturdy base plate		Rx & Tx	3-45 pr.
PB 6	6 x 14 pin DIL ICs		
PB 100	10 x 14 pin DIL ICs		
PB 102	12 x 14 pin DIL ICs		
PB 103	24 x 14 pin DIL ICs		
PB 104	32 x 14 pin DIL ICs		
(The above boards are suitable for all DIL ICs)			

VAT Rate. Please add 15% to your total. Please send SAE for full list. Add 30p p & p (75p p & p for official orders) CALLERS WELCOME MON-FRI 9.30-5.30 SAT 10.30-4.30

**TECHNOMATIC LTD**  
17 BURNLEY ROAD, LONDON NW10  
(2 minutes from Dollis Hill Tube)  
Tel. 01-452 1500 Tlx. 922800



# Wilmslow Audio

**THE firm for speakers!**

**SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST**

- AUDAX ● AUDIOMASTER ● BAKER BOWERS & WILKINS ● CASTLE CELESTION ● CHARTWELL ● COLES DALESFORD ● DECCA ● EAGLE ● ELAC EMI ● FANE ● GAUSS ● GOODMAN'S HARBETH ● ISOPHON ● I.M.F. ● JORDAN JORDAN WATTS ● KEF ● LOWTHER MCKENZIE ● MISSION ● MONITOR AUDIO MOTOROLA ● PEERLESS ● RADFORD RAM ● ROGERS ● RICHARD ALLAN SEAS ● SHACKMAN ● STAG ● TANNAY VIDEOTONE ● WHARFEDALE



## WILMSLOW AUDIO (Dept. EE)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF  
Tel: 0625-529599 FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.  
Tel: 0625-526213 (SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

## Random Electronic
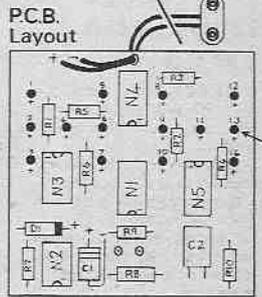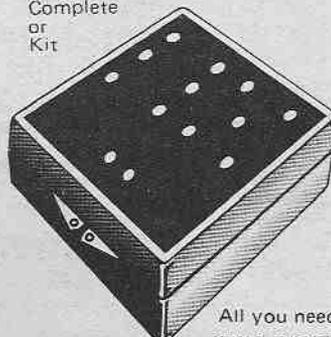
# EASY DICE

Build your own 'EASY DICE' from the 5 intergrated circuits and full components supplied, including box and descriptive instructions.



Complete or Kit

All you need is a soldering iron  
TWO DICE FACES TOUCH CONTROL...

- a \*Self Assemble Dice £4.50 + P&P 25p
- b \*Ready built Dice £5.45 + P&P 25p

Order now from: **Fringewood Electronics Ltd**  
1 Hatton Court Ipswich Suffolk 0473-210151

Amount enclosed £ \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_

please state amount required in appropriate box  a  b

# MITRAD

(MIDLAND TRADING COMPANY)

## ZETRON

### BRITAINS FINEST SELLING RANGE

## ZETRON

#### GENTS 4 BUTTON CHRONO

A NEW STYLE chronograph with the added advantage of 4 buttons plus date flag. Hours, mins, secs, weekday, am/pm indication on constant display.

Date flag indication with month and date.

1/100th sec chrono, with a 12 hour capacity.

Split and lap mode facilities.

Back-light. Adjustable stainless steel strap.

Special **£8.95**



#### GENTS FRONT BUTTON CHRONO ALARM

LATEST 1980 STYLE. Super slim and attractive. Basic working modes of (i) Chronograph (ii) 24 hr. alarm (iii) Dual time zone, hours, minutes, seconds.

Weekday indication, with am/pm T2 and A1 flags month and date indication.

Running horse style chrono to 1/10 sec.

60 sec activation time on the alarm system. 6 digits 5 flags.

Backlight, adjustable stainless steel strap.

**£15.50**

Also available in black resined case and strap.

Only **£12.50**



#### GENTS MELODY ALARM CHRONO

BRAND NEW melody alarm chrono which we believe will be the watch of 1980.

Hours, mins, secs, weekday, am/pm and mode square flag indication.

Chrono to 1/10th sec, with split and lap mode facilities.

Dual timing facilities.

The alarm system is unique in the fact that it plays the tune "Yellow Rose of Texas", for 20 seconds.

The tune can be activated at any instance by the press of a button.

Backlight, infinite adjustable built in stainless steel strap.

Only **£17.75**



#### GENTS FRONT BUTTON ALARM

LATEST 1980 STYLE. Constant display of hours, mins, secs, am/pm, weekday and alarm indication.

Two further display modes are available.

7 digits, 12 function. Programmed to the year 2009, 24 hour alarm operating for 30 seconds.

Backlight and a closely woven adjustable stainless steel strap finish the watch off with a really superb look.

Only 8mm thick.

**£13.25**



#### GENTS MEMORY CALENDAR ALARM CHRONO

LATEST TECHNOLOGY. Hours, mins, secs, weekday and snooze alarm indication.

Two further optional display modes are available.

The calendar and month can be increased or decreased to give the appropriate month of the year.

1/100th sec chronograph, with split and lap mode facilities. 12 hour capacity.

24 hour alarm with a 10 minute snooze. Backlight, adjustable stainless steel strap.

Outstanding value **£19.95**



#### LADIES COCKTAIL

ELEGANCE AND STYLE for the lady with a discerning taste.

In gold or silver finish with matching adjustable bracelet.

Constant display of hours and mins, with month, date, secs.

Auto calendar, backlight.

**£10.50**



#### LADIES SUGAR COATED

ANOTHER SUPERB LADIES WATCH, with that extremely popular sugar frosted finish. (Gold or silver).

Links can easily be removed from the strap and the clasp has a spring mechanism built in to give a comfortable fitting.

Constant display of hours and mins, with month, date, secs, auto-calendar, backlight.

**£10.50**



#### GENTS CHRONOGRAPH

PROBABLY THE BEST looking chrono on the market.

Constant display of hours, mins, secs, with am/pm indication.

Also month, date and week-day indication.

1/100th and 1/10th sec with split and lap mode facilities, backlight, closely woven adjustable stainless steel strap.

Special **£8.95**



#### GENTS MELODY CHIME ALARM CHRONO

LATEST TECHNOLOGY. Hours, mins, secs, date, weekday, month, with mode and chime indication.

A musical alarm is built in and can be set to any time within 24 hours, playing the tune "Oh Suzanna".

Two further alarm systems: (i) 24 hour alarm (ii) Count down alarm (1 sec accuracy).

The watch can be set to chime on every full hour. 1/100th sec chrono, can be switched off, mineral glass.

Backlight and infinite adjustable stainless steel strap.

Very special **£19.95**



## ZETRON

### WHERE RELIABILITY, STYLE AND ELEGANCE REALLY COUNT

## ZETRON

WE ARE ABLE YET AGAIN to offer you the above watches, plus the complete ZETRON range. All at unrivalled prices. Just look at the following points.

- (i) 48 hour despatch guaranteed on both retail and trade orders.
- (ii) Full instructions and 12 month manufacturers guarantee.
- (iii) Our own free back up service.
- (iv) 10 day full money refund if not completely satisfied.
- (v) Free felt presentation case with each watch.

# ZETRON

PHONE OR WRITE for free full comprehensive catalogue on the complete range of watches we offer. Large discounts available for bulk buyers. Trade lists on application. Agents wanted everywhere. P/P per item 85p which includes insurance.

Cheques or PO's made payable to MITRAD and sent to (Dept ), 58 Windmill Ave, Kettering, Northants, NN16 8PA.

(0536) 522024.

**U.K. RETURN OF POST MAIL ORDER SERVICE also WORLDWIDE EXPORT SERVICE**

**BAKER LOUDSPEAKERS "SPECIAL PRICES"**

Model	Ohms	Size inch	Power Watts	Type	Our Price
Major	4, 8, 16	12	30	Hi-Fi	£12
Deluxe Mk II 4	8, 16	12	15	Hi-Fi	£14
Superb	8, 16	12	30	Hi-Fi	£22
Auditorium	8, 16	12	45	Hi-Fi	£20
Auditorium	8, 16	15	60	Hi-Fi	£30
Group 35	8, 16	12	40	PA	£12
Group 45	4, 8, 16	12	45	PA	£15
Group 50	4, 8, 16	12	60	PA	£20
Group 50	8, 16	15	75	PA	£30
Group 75	4, 8, 16	12	75	PA	£24
Group 100	8, 16	12	100	PA	£29
Group 100	8, 16	15	100	PA	£35
Disco 100	8, 16	12	100	Disco	£29
Disco 100	8, 16	15	100	Disco	£35

**4 CHANNEL MIXERS £3.00**

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated with switch for four channel mono or two channel stereo working.

**MINI MODULE BAFFLE KIT Post £1**

EMI 15 x 8 1/2 in. 3-way Loudspeaker System, 5in. Bass, 5in. Middle, 3in. Tweeter; 3-way Crossover & Ready Cut Baffle. Full assembly instructions supplied. Response 60 to 20,000 c.p.s. 12 watt RMS 8 ohms £10.95 per kit. Two kits £20. Suitable Bookshelf Cabinet £29.50 each. Post £2.



**SINGLE RECORD PLAYER**

Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable size 7in. diameter, a.c. mains 240V 3 speeds plays all size records. £9.95 Two for £18. Post £1 on each.

**NEW BSR SINGLE PLAYER £24.50**

Model P182 3-speeds flared aluminium turntable. "S" shaped arm, cueing device, stereo ceramic cartridge. B.S.R. De-Luxe Autochanger with stereo cartridge, plays all size records. Post £2. THE "INSTANT" BULK TAPE ERASER Suitable for cassettes and all sizes of tape reels, a.c. mains 200/240V £7.50 Post £1.

**BAKER 150 WATT ALL PURPOSE MIXER AMPLIFIER**



Ideal for Groups, Disco, P.A. and Musical Instruments. 4 inputs speech and music 4 way mixing. Output 4/8/16 ohm, a.c. Mains 240V. Separate treble and bass controls. 100 volt line model £14 extra. £85 Post £2

**BAKER 50 WATT AMPLIFIER**



**IDEAL FOR DISCOS, GROUPS, PUBLIC ADDRESS**

Two inputs with volume controls. Master treble bass and volume controls Suitable for all loudspeakers. £65. Post £2.

**R.C.S. SOUND TO LIGHT KIT**

Complete kit of parts with R.S.C. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. KIT £18.00 Post 75p.

**R.C.S. 10 WATT AMPLIFIER KIT**

This kit is suitable for record players, tape play back, guitars, electronic instruments or small PA systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms 7W into 15 ohms. Response 20c.s. to 30Kc.s. Size 9 1/2 x 3 x 2 in. A/C mains operated. Mono kit £12.50 Stereo kit £20 Post £1 Easy to build. Full instructions supplied.

**LOW VOLTAGE ELECTROLYTICS**

1. 2. 4. 5. 8. 16. 25. 30. 50. 100. 200mF 15V 15p. 25V 20p. 50V 30p. 100mF 12V 17p. 25V 35p. 50V 47p. 100V 70p. 200mF 40V 60p. 25V 42p. 250mF 50V 62p. 300mF 25V 47p. 50V 65p. 2700mF 76V £1 4700mF 63V £1.20; 25V 75p; 35V 85p. 5600mF 76V £1.75. 1200mF 76V 80p.

**HIGH VOLTAGE ELECTROLYTICS**

|               |                |                  |
|---------------|----------------|------------------|
| 3/350V 22p    | 8+8/450V 50p   | 80+ 50/300V 50p  |
| 16/350V 30p   | 8+16/450V 50p  | 32+ 32/450V 75p  |
| 32/500V 75p   | 16+16/450V 50p | 100+100/275V 65p |
| 50/500V £1.20 | 32+32/350V 50p | 150+200/275V 70p |
| 8/800V £1.20  | 16/500V 65p    | 220/450V 95p     |

**WOOD PLINTH CUT FOR B.S.R. £1.**  
Size: 16 x 14 1/2 x 3 1/2 in. Teak Veneered.  
**METAL PLINTH CUT FOR B.S.R. OR GARRARD**  
Size: 16 x 14 x 3 in. £4. Silver or Black finish. Post £2.  
**TINTED PLASTIC COVERS ALL POST £2**  
Sizes: 14 1/2 x 12 1/2 x 3 in. £3.50. 16 x 14 x 3 1/2 in. £6. 15 1/2 x 13 1/2 x 4 in. £4. 17 1/2 x 9 1/2 x 3 1/2 in. £3. 18 x 13 1/2 x 3 in. £6. 18 x 12 1/2 x 3 in. £6. 18 x 13 1/2 x 3 1/2 in. with stand-up hinges £7.

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS Post 45p £2.95**  
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240V a.c. Output voltages available 6 or 7, 5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required.

**MAINS TRANSFORMERS ALL POST 99p each**  
950-0-950V 80mA 6-3V 2A £3.45  
250-0-250 80mA 6-3V, 3-5A, 6-3V 1A £4.60  
350-0-350V 250mA 6-3V 5 amp, 5V 2A £12.50  
300-0-300 120mA 2 x 6-3V 2A C.T.; 6-3V 2A £8.50  
220V 45mA, 6-3V 2A £2.50  
**HEATER TRANS 6-3V 3A £2.20 1/2 amp**  
**GENERAL PURPOSE LOW VOLTAGE Tapped outputs at**  
2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £6.00  
1A, 5, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 45, 60 £6.00  
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £9.50  
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50  
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £18.00  
5, 8, 10, 16V 1A 22-50 12V 100mA £1.30 12V 300mA £1.50  
12V 750mA £1.75. 40V 2A tapped 10V or 30V £3.50  
10-0-10V 2A £3.40V 2A £3.50. 30V 5A + 34V 2A CT £4.2 x 18V 6A £11. 12-0-12V 2amp £3.50.  
25-0-25V 2A £4.50. 20-0-20V 1A £3.50. 30V 1 1/2A £3.30. 20V 1A £3.9V 3amp £3.50. 60V 40V 20V 1A £4.  
15/0/15V 2A £3.75. 32-0-32V 1 1/2A £11. 9V 250mA £1.50. 30V 2A £3.50.  
**AUTO TRANSFORMERS 115V to 230V or 230V to 115V 150W £7; 250W £9; 400W £9; 500W £10.**  
**CHARGER TRANSFORMERS Input 200/250V for 6 or 12V 1 1/2A £4.25. 3 amp £4.4A £7.25.**  
**FULL WAVE BRIDGE CHARGER RECTIFIERS 6 or 12V outputs 1 1/2A 85p; 4A £1.60. HALF WAVE 12V 1 1/2A 35p.**

**BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in sides, 6 x 4 in 95p, 8 x 6 in £1.40; 10 x 7 in. £1.55; 14 x 9 in. £1.90; 16 x 8 in. £1.85; 12 x 3 in £1.20; 16 x 10 in. £2.20; 12 x 3 in. £1.70.**

**ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in. 24p; 8 x 6 in. 38p; 10 x 7 in. 54p; 12 x 5 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1.16; 16 x 10 in. £1.16.**  
**ALUMINIUM ANGLE BRACKET, 6 x 3 x 3 in. 25p.**  
**ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK 4 x 2 x 2 in. 80p; 3 x 2 x 1 in. 65p; 6 x 4 x 2 in. 95p; 8 x 6 x 3 in. £1.50; 9 x 4 x 4 in. £1.70; 10 x 7 x 3 in. £2.20; 12 x 8 x 3 £2.50.**

**RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K.**

Minimum post 50p. Phone orders with Access and Barclaycard. Same day despatch. Components Lists 20p. Open 9-6 Sat. 9-5 (Closed Wednesday all day). Tel. 01-584 1665

**DO YOU EVER WISH YOU HAD A FEW MORE HANDS?**

YOU KNOW WHAT IT'S LIKE WHEN YOU'RE ABOUT TO START THAT NEW PROJECT — ARMED WITH A NICELY HOT SOLDERING IRON IN ONE HAND, THE SOLDER IN THE OTHER, YOU SUDDENLY FIND YOU'VE NO HANDS LEFT TO HOLD THE CIRCUIT BOARD AND COMPONENT, LET ALONE THE HEAT SINK.




Experience a new freedom with . . . .

A twist of the clamping control nut and the Board is held securely. The jaws can then be flipped across so that either side of the board is accessible at will. Flexible arms terminating in crocodile clips hold components and in addition an arm can be provided to hold a magnifying lens to reduce the strain on those valuable eyes of yours.

Provision is made for the fitting of up to four flexible arms if required.

**POST COUPON TODAY TO—**  
**Messrs. ABSONGLEN LIMITED, THE FORGE,**  
**STAPLOW COTTAGE, STAPLOW,**  
**LEDBURY, HEREFORDSHIRE HR8 1NP.**

**THE MINIBENCH\***

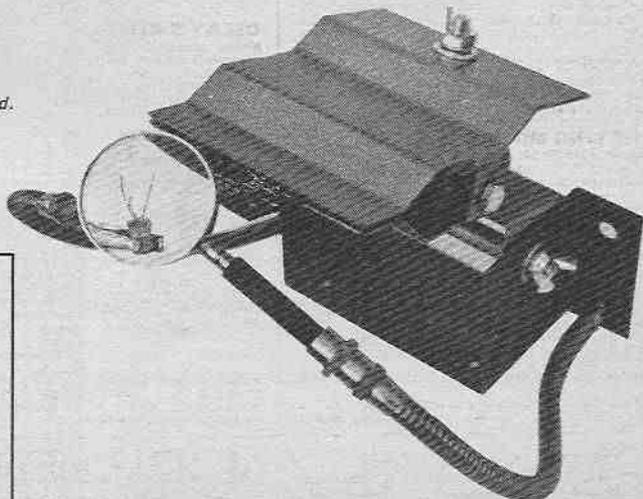

Please supply ..... Minibench @ £13.95 each  
Flexible Arms with Clips..... @ £4.25 each  
Flexible Arms with Lens ..... @ £5.25 each  
Postage and Packing £1.50  
Cheque/Postal Order enclosed for £.....

Name .....  
Address .....  
Postal Code.....

\* Trade Mark


Patent Applied For

# You will not be too late

For most of the bargains listed in the newsletter reprinted below, even though it is our JAN/FEB issue, because the part of the newsletter with the items in short supply is not reprinted. However, you will receive the whole of our MARCH/APRIL newsletter if you send us an order this month and as an extra inducement we will send you our MAY/JUNE newsletter directly if it is printed, which is usually about two months before it can appear in this magazine.
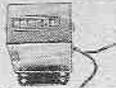
## SIX DIGIT COUNTERS

One pulse moves one digit—Type 1 for 230V AC or 100V DC not resettable. Price £8.00—Type 2 for 48V DC or 115V AC and resettable £1.85.



## COMPONENTS BARGAIN

Ref. W0998. Modern fibre glass board, contains a multitude of very useful parts, some of which are:—SCR ref. 2N 5050/2, 35 assorted resistors including four 3 amp 400V types (made up in a bridge) 8 transistors type BC 107 and 2 type BFY 51 electrolytic capacitors. 250uF 100V DC and 100uF 25V DC and over 100 parts including variable, fixed and wire wound resistors, electrolytics etc. Don't miss this snip at £1.15.

## SIREN OR BLEEPER

American Delta mechanical type, works on 6 to 12V to DC or 12 to 24V AC. Price 75p or £60 per 100. Electronic Bleeper THS emits high pitched wailing note of varying pitch. In red plastic case with fixing bracket. £5.00.



## CASSETTE PLAYER/RECORDERS

With record and playback heads, all electronics, switches and speaker. Price £9.95 (surely this must be the bargain of the year). Music centre replacement stereo with heads but not electronics. £14.95.

## DESOLDERING PUMP

Ideal for removing components from computer boards as well as for service work generally. Price £8.35.



## ENGRAVER

Very useful tool will engrave on metal or plastic. Kit comprises mains solenoid, micro-switch and instructions. A few other parts are included but you will probably have these in your junk box. Price £3.00.

## HEADPHONE AMPLIFIER (STEREO)

With volume, tone and balance control/9 operation. All made up ready to go. Price £4.50.



## MAINS SOLENOIDS

All have powerful pull. TT2 size 1 1/2" x 2 1/2" x 2". Price £3.95 TT6 size 2 1/2" x 1 1/2" x 2". Price £3.50 TT10 size 3" x 2 1/2" x 2". Price £4.95

## ELECTRONIC JIGSAW PUZZLE

One of the many things you can make with this miniature uni-selector. We give the circuit free when you order. Price £3.45.



## MAINS OPERATED VALVES

Made by Asco. Two models available both suitable for water and non-corrosive liquids, both for normal mains operation. Ref. V1 for 3/4" pipes and low pressure operation. V2 is for 1" pipe and high pressure operation. Only £4.60 either type.

## VERSADRILL

A 12 volt battery operated power drill, not just suitable for printed circuit boards but will do all the jobs and is powerful enough to perform all the functions and operations normally expected of Black & Decker and other mains drills. Its chuck accepts up to 1/4" drills. Size approx. 150mm x 50mm. Price £16.75.



## DOOR SWITCH

Neat tubular pattern for letting into door frame. This is a changeover switch so can be used in opening or closing circuits. Price 57p. D.I.Y. burglar alarm parts available, request diagram and price list of our mains operated system.

## V3 MICROSWITCHES


Over 50,000 in stock, all 250 AC working, all with 3 silver contacts for c/o circuits. 10 amp 25p each or £20 per 100, 15 amp 35p each or £30 per 100.

## DOOR MOVING MOTOR

Francis reversible single phase 140W AC motor with gear box giving final speed 56 rpm very powerful motor, weight approx. 13lb. Price £15 carriage £3 mainland only.
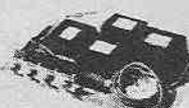
## MULLARD UNILEX

A mains operated 4+4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy-to-assemble modular form this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16 including VAT and postage.



FREE GIFT—Buy this month and you will receive a pair of Goodman's elliptical 8" x 5" speakers to match this amplifier.

PLEASE NOTE: The "4+" sign after the amount shows the amount V.A.T. The postage, if quoted, is based upon the amount the article costs to send if it forms part of a larger parcel. Should your order be less than £10.00 however, please send an additional 50p. BARCLAYCARD & ACCESS WELCOMED. Phone 01-888 1833.

## MINIATURE MAGNETIC CIRCUIT BREAKERS

Operate faster than fuses. 1 amp, 2 amp, 5 amp, 10 amp, 15 amp and 25 amp types. All £2.30 each.

## NEW KIT

6 WAVE BAND SHORT WAVE KIT Bandspread covering 13.5 to 52 metres. Complete kit includes case, materials, six transistors and diodes, condensers, resistors, inductors, switches etc. Nothing else to buy, if you have an amplifier to connect it to or a pair of high resistance headphones. Special price is £11.95 inc.




## DRILL CONTROLLER

Electronically changes speed from approximately 10 revs to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £3.45

Made up model £2.00 extra

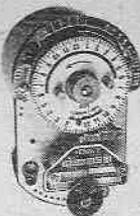
## VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs, repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are new but without case, but we can supply plastic cases (base and cover) £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.


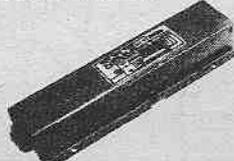
## FLUORESCENT TUBE INVERTER

For camping—car repairing—emergency lighting from a 12V battery you can't beat fluorescent lighting, it will offer plenty of well distributed light and is economical. We offer Phillips inverter for 12" 8 watt miniature tube for only £2.75 with tube and tube holders as well.



## THIS MONTH'S SNIPS

3 CHANNEL SOUND TO LIGHT KIT Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for Disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special snip price is £13.50 in kit form or £16.50 assembled and tested.

REMOTE CONTROL for Sound to Light (ours or any other circuit) saves connecting to speaker or amp—kit consists of 1 watt amplifier, crystal mike, case, sundries and diagram. Price £3.95.

LIGHT EXPANDER AND LATCH for Sound to Light, enables 3000 watts of lighting to be controlled by single channel or each channel and enables lights to be latched on. Kit consists of latching relay, control switch, case, sundries and diagram. Price £4.25.

SINGLE CHANNEL KIT still available. Price £5.18.

## DELAY SWITCH

Mains operated—delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens a few minutes after 1st contact. 95p.



## MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings—2000 o.p.v. mirrored scale.

Instant ranges measure:—DC volts 10, 50, 250, 1000, AC volts 10, 50, 250, 1000, DC amps 0-100 mA.

Continuity and resistance 0-1 meg ohms in two ranges.

Complete with Test Prods and instruction book showing how to measure capacity and inductance as well.

Unbelievable value only £6.75 + 30p post and insurance.

FREE Amps ranges kit to enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one, send £2.50.

## J. BULL (ELECTRICAL) LTD

(Dept. E.E.), 103 TAMWORTH RD., WEST CROYDON, SURREY  
Tel: 01-688 1833

IT'S FREE... so you will only have yourself to blame if you miss the 150 or so bargains listed in each issue of our Advance Advertising News. Produced bi-monthly the newsletter also includes topical tips, special snips and "too few to advertise" items. You will get this current copy whenever you buy us, or if you send us some long, stamped addressed envelopes we will send them as they are printed.

## 12V SUBMERSIBLE PUMP

Just join it to your car battery, drop it into the liquid to be moved and up it comes, no messing about, no priming etc. Suitable for water, paraffin and any non-corrosive non-explosive liquid. One use if you are a camper, make yourself a shower. Price £8 + 90p. A free gift, first 100 purchasers will get tap built in switch and length of plastic tubing.

## THIS MONTH'S ELECTRICAL SNIP

Parcel of M.E.M. White flush 13 amp sockets, switches etc. Total retail value over £56 + VAT. For only £28 + £4.20 you get 10 double 13 amp sockets and 6 single 13 amp S. Sockets with neons, 14 power 20 amp dpt switches and spurs some with neons) 20 single ganged one way, two way and intermediate switches and superfree gift worth £3. If not collecting please add £2.00.

## DELAY SWITCH

Mains operated, delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps—second contact opens few minutes after 1st contact £1.50.

## 6 DIGIT COUNTER—RESETTABLE

Coil voltage 48DC or 115V AC current 100mA approx. Price £1.95 + 30p.

## DRY FILM LUBRICANT

In aerosol can for easy application and for putting lubricant into places where the normal oil cannot reach. Offered at about half the original list price 50p + 7p per can (8 oz.) or 12 cans for £4.60 post £1.50. The lubricant is I.C.I. Fluon L169.

## ASSORTED MICROSWITCHES

10 different small, medium and large sizes to suit most projects and repair jobs. Price £1.50 + 22p. If this pack does not contain the one you want give us a ring and we may have it.

## TELEPHONE PICK UP

Coil attached by suction to phone body, enabling conversation to be recorded, put through amp or headphones. Price £1 + 15p.

## MAINS TRANSISTOR POWER PACK

To operate transistor radio, cassettes, amplifiers etc. take the place of any of the following batteries, PP1, PP3, PP4, PP6, PP9 and others. You can make voltage output anything from 3V to 9V at up to 300 mA. Complete kit but no case £1.75 + 25p. Case 75p + 13p.

## INTERRUPTED BEAM KIT

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components—relay, photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2 + 30p.

## FM TUNER

Nicely boxed in wooden case and has a smart dial with cord drive and pointer, it covers the range 88-108 mhz, has an input sensitivity of 10uV, uses 6 transistors and 3 diodes. It is an excellent performer and when tested here we have had results quite equal to a tuner costing over £40. Price only £7.50 + £1.12 or with stereo decoder £11.50 + £1.72 + post £1.00.

## INTERCOM OUTFIT

Brand new intercoms with 50' inter-connecting lead. Master and sub, in neat plastic cases suitable for office or home or as a baby alarm etc. These are new stock but please expect a little fault. Offered at less than the price of the 2 speakers, switches and cases. Only £3.74 the pair.

WANT A CHEAP ELECTRIC FAN? We offer a quiet running induction motor and a 5" five-bladed fan for only £2.95. Mount this on a stiff wire frame or a piece of handy angle and you will be able to keep yourself cool this summer.

## EXTRACTOR FANS

By Woods still available 5" £6.00, 6" £7.00.

## HEATING PAD

11" x 8 1/2" water tight 250 watt. Price £1.16.

## PAPST MOTORS

Sometimes described as the motor with the built-in flywheel. Used in high quality tape recorders and in other equipment where wow and flutter has been reduced to a minimum. We have five different motors in stock, these are all physically about the same size (about 3" dia. x 2 1/2" deep). We quote their type numbers but we have no other technical information.

Price includes the capacitor required. HSZ 20.50-4 540D dual voltage 120/220 50Hz £8.50. SSZ 20.50-4 255D 110V 50/60Hz £8.50. KLZ 20.50-4 540D 220V 50Hz £9.50. KLZ 20.50-4 425D 115V 60Hz £8.50. KLZ 20.50-4 468D 110V 50Hz £8.50.

## TWO TRACK RECORD/PLAYBACK HEADS

For transistor circuits, separate erase head. Special offer this month £1 or mounted on tape guide plate £1.75.

## EX GPO TELEPHONES

Normal desk instrument with dial and internal bell, latest type £6 each, preceding type £5.00 each.

## TANGENTIAL BLOWER

Metal bladed Smiths made super silent with dozens of applications, cooker hoods, fume extractor—blower heater fresh air impeller etc. Air outlet is rectangular size approx. 10 1/2" x 2 1/2" £4.95. Post £1.50.

## 8 BATTERY MOTORS

For model makers, smallest is about as big as a thimble and the biggest is powerful enough for a drill. £2 the 8.

## 12V MOTOR BY CROUZET

A powerful motor virtually impossible to stop by hand, size approx. 2 1/2" long and 2 1/2" dia. permanent magnet so reversible simply by changing polarity and has a relatively constant speed with or without load. Fitted with a splined shaft which could directly engage a toothed wheel or to which a pulley could be attached. Ideal for large models, or small machines etc. Priced £4.25.

## MAINS OPERATED LOW SPEED MOTORS

Programmer type as used in time switches etc. The following final speeds in stock:—1r 24 hrs — 1r 8 hrs — 1r 4h — 1r h — 2r h — 4r h — 12r h — 20r h — 30r h — 1r min — 2m — 4m — 8m — 15m — 25m — 30m — 200m — all at £3.50 each.

## SPIT MOTORS

These are powerful mains operated induction motors with gear box attached with easy to fix to, squared shaft, final speed is approx. 5 revs. per min., price £2.25—similar motor but with final speed 110 rpm, 80 rpm £2.15.

## SUB MINI MICROPHONE

Size only 3/8" x 3/16" so small enough for a bugging device, ex-hearing aids but guaranteed. Price £1.50.

## TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversations to be picked up with FM radio. Can be made in a matchbox—all electronic parts and circuit £2.00.

## RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.50.

## DP-DT TOGGLE SWITCH

Normal size, normal fixing bright plated toggle and fixing nuts—by NSF. 3 amp 250V price 40p each. £35 per 100.

# Simply ahead . . .

## I.L.P.'s PROVEN RANGE OF HIGH

*Chosen in more countries throughout the world than any other U.K. make*



- FIVE POWER AMPLIFIERS EACH ENCAPSULATED WITHIN LARGE HEATSINK.
- PRE-AMP/ACTIVE TONE CONTROL MODULE COMPATIBLE WITH ALL I.L.P. AMPS AND POWER SUPPLIES.
- SEVEN MATCHING POWER SUPPLY UNITS (FOUR WITH TOROIDAL TRANSFORMERS).
- EASY ASSEMBLY DESIGNS WITH WELL PRESENTED INSTRUCTIONS.

I.L.P. constructional modules are different. Whereas most others come with components neatly arranged on open P.C.Bs with little else, I.L.P. modules are encapsulated within totally adequate heatsinks and need no extra components to complete them. As a result, I.L.P. power amplifiers, pre-amp and matching power supply units are infinitely more rugged, impervious to working in extremes of temperature and can be easily positioned to requirement. No additional metal work is needed to take away heat, connections are minimal and utterly simple. Circuitry, workmanship and performance are of the highest standards, equal to the demands of loudspeakers, pick-ups, tuners, digital signals etc. even more exacting than those of today, making amplifier systems less than the best completely inadequate. Now study the tested and guaranteed specs. for I.L.P. That is why more people in more countries prefer these British designed and made modules.

### Why toroidal?

Toroidally wound transformers are more compact than their conventionally laminated equivalents, being only half as high and heavy. Their circular profile ensures greater operating efficiency and as such are particularly valuable in heavy duty applications. We have our own production section for winding and making toroidal transformers enabling us to offer this much sought-after type at competitive prices. Four of the larger models in our range of power supply units are now supplied with this type.

**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS  
IN ELECTRONIC MODULAR DESIGN**

AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS


# and staying there

## PERFORMANCE MODULAR UNITS

### HY5 PRE-AMPLIFIER



With easy to use connector.


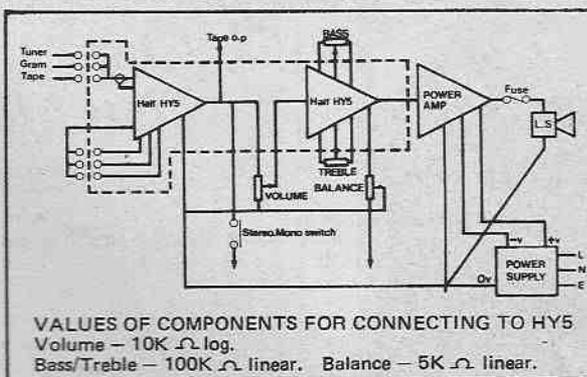


VALUES OF COMPONENTS FOR CONNECTING TO HY5  
Volume - 10K  $\Omega$  log.  
Bass/Treble - 100K  $\Omega$  linear. Balance - 5K  $\Omega$  linear.

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz-0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


### THE POWER AMPLIFIERS

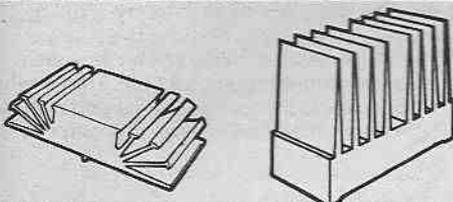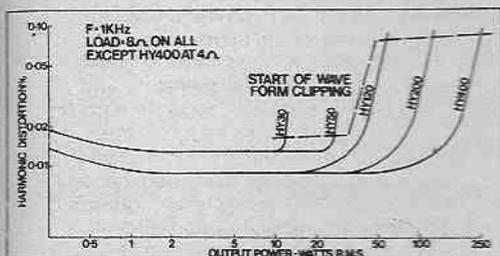

| Model | Output Power R.M.S.   | Distortion Typical at 1KHz | Minimum Signal/Noise Ratio | Power Supply Voltage | Size in mm | Weight in gms | Price + V.A.T. |
|-------|-----------------------|----------------------------|----------------------------|----------------------|------------|---------------|----------------|
| HY30  | 15 W into 8 $\Omega$  | 0.02%                      | 80dB                       | -20 -0 +20           | 105x50x25  | 155           | £6.34 + 95p    |
| HY50  | 30 W into 8 $\Omega$  | 0.02%                      | 90dB                       | -25 -0 +25           | 105x50x25  | 155           | £7.24 + £1.09  |
| HY120 | 60 W into 8 $\Omega$  | 0.01%                      | 100dB                      | -35 -0 +35           | 114x50x85  | 575           | £15.20 + £2.28 |
| HY200 | 120 W into 8 $\Omega$ | 0.01%                      | 100dB                      | -45 -0 +45           | 114x50x85  | 575           | £18.44 + £2.77 |
| HY400 | 240 W into 4 $\Omega$ | 0.01%                      | 100dB                      | -45 -0 +45           | 114x100x85 | 1.15Kg        | £27.68 + £4.15 |

Load impedance - all models 4 - 16  $\Omega$   
Input sensitivity - all models 500 mV  
Input impedance - all models 100K  $\Omega$   
Frequency response - all models 10Hz-45KHz -3dB
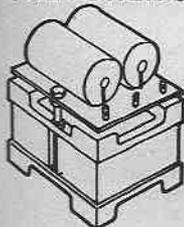
### THE POWER SUPPLY UNITS (Laminated and Toroidal)



I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

|        |   |                    |
|--------|---|--------------------|
| PSU 30 | $\pm 15V$ at 100ma to drive up to five HY5 pre-amps | £4.50 + £0.68 VAT  |
| PSU 36 | for 1 or 2 HY30's                                   | £8.10 + £1.22 VAT  |
| PSU 50 | for 1 or 2 HY50's                                   | £8.10 + £1.22 VAT  |
| PSU 60 | (Toroidal) for one HY120                            | £9.75 + £1.46 VAT  |
| PSU 70 | with toroidal transformer for 1 or 2 HY120's        | £13.61 + £2.04 VAT |
| PSU 90 | with toroidal transformer for 1 HY200               | £13.61 + £2.04 VAT |
| PSU180 | with toroidal transformer for 1 HY400 or 2 x HY200  | £23.02 + £3.45 VAT |

NO QUIBBLE  
5 YEAR GUARANTEE

7-DAY DESPATCH ON ALL ORDERS

INTEGRAL HEATSINKS

BRITISH DESIGN AND MANUFACTURE

FREEPOST SERVICE - see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

#### HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.



**I.L.P.**

**ELECTRONICS LTD.**

FREEPOST 1 Graham Bell House, Roper Close,  
Canterbury, Kent CT2 7EP.  
Telephone (0227) 54778 Telex 965780

Please supply .....

..... Total purchase price £ .....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Account/Barclaycard Account No. ....

NAME .....


ADDRESS .....

Signature .....

# ELECTROVALUE

## SUPPLIERS OF

### COMPONENTS THAT COUNT

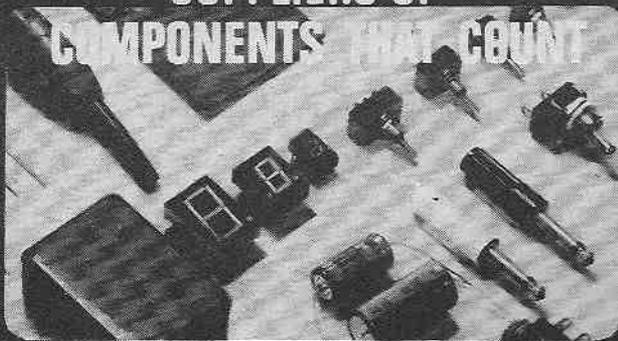

|  |  |   |
|--|--|---|
| <b>SIEMENS</b><br>SEMI-CONDUCTOR<br>CAPACITORS<br>FERRITES | <b>NASCOM</b><br>MICRO COMPUTERS<br>AND<br>ANCILLARIES | <b>VERO</b><br>BOARDS<br>CASES &<br>KITS  |
| <b>ISKRA</b><br>RESISTORS                                  | <b>RADIOHM</b><br>POTENTIOMETERS                       | <b>BREADBOARDS</b><br><b>SOLDER TOOLS</b> |
|  | <b>OPTO-ELECTRONICS</b>                                | <b>SWITCHES</b> <b>CATALOGUE 10</b>       |

### OUR MINI-SELECTION POINTS THE WAY!

#### EXAMPLE ONE - SOLDERING IRONS

|         |            |                    |           |
|---------|------------|--------------------|-----------|
| Aryx 50 | £12.08 net | Antex x 25         | £4.83 net |
| Isotip  | £25.90 net | Desolder tool SR3A | £7.48 net |
| Antex C | £4.83 net  | 500 gm reel solder | £6.61 net |

#### EXAMPLE TWO - PRINTED CIRCUIT MATERIALS

|                       |           |                  |           |
|-----------------------|-----------|------------------|-----------|
| PCB's 300 x 150 mm    |           | Etch Resist Pen  | £1.14     |
| SRBP S/S £1.38        | D/S £1.73 | Breadboards      |           |
| F/Glass S/S £1.96     | D/S £2.13 | Bimboard 12F9.23 |           |
| Positive resist 75cc  | £1.67     | Euroboardboard   | £6.56 net |
| Ferric Chloride 500 g | £3.45     | T-DeC            | £5.18     |

#### EXAMPLE THREE - SWITCHES

|               |          |  |            |
|---------------|----------|--|------------|
| Chrome toggle |          | 13A time switch adaptors                     |            |
| Std. SPDT 85p | DPDT 89p | Smiths TS100                                 | £14.43 net |
| Min. SPDT 66p | DPDT 92p | Wavechange - Lorlin, 1P12W, 2P6W, 3P4W, 4P3W | 46p each   |

#### EXAMPLE FOUR - CAPACITORS BY SIEMENS

**Polyester 7.5mm PCM**  
1, 1.5, 2.2, 3.3, 4.7µF, 10, 15, 22, 33, 42µF 8p each, .1µ 12p, .15µ 15p, .22µ 18p, .33µ 21p, .47µ 27p, .68µ 34p, 10mm PCM 1µ 37p.

**Electrolytic, axial, (µ F/V)**  
1/40 24p, 1/100 15p, 2.2/25 24p, 2.2/63 15p, 4.7/16 24p, 4.7/40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 19p, 47/10 15p, 47/25 18p, 47/40 15p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 65p.

Also full supporting ranges of other ceramic, plastic and electrolytic caps.

#### EXAMPLE FIVE - POTENTIOMETERS BY RADIOHM

|                        |      |                             |          |
|------------------------|------|-----------------------------|----------|
| Single gang lin or log | 34p  | (Twin types stereo matched) |          |
| Twin gang lin or log   | 83p  | Slider knobs                | 10p each |
| Mono slider lin or log | 83p  | Presets lin, horiz, or vert | 10p      |
| Twin slider lin or log | 136p |                             |          |

#### EXAMPLE SIX - RESISTORS

1/4W 2.3p 1W 6p  
Wirewound from 21p

#### AND AS FOR SEMI CONDUCTORS ...

|           |       |        |       |         |       |          |     |
|-----------|-------|--------|-------|---------|-------|----------|-----|
| 1N914     | 6p    | 40673  | 99p   | MU481   | £1.70 | T1P41A   | 69p |
| 1N4007    | 9p    | AC128  | 36p   | MJ481   | £1.88 | T1P41C   | 74p |
| 1N4148    | 5p    | AC176  | 67p   | MJ2955  | 97p   | T1P42A   | 69p |
| 1N5402    | 19p   | AD136  | £4.25 | MJE2955 | £1.13 | T1P42C   | 74p |
| 2N1599    | £1.01 | AD149  | £1.01 | MJE3055 | £1.00 | T1P2855  | 69p |
| 2N2369A   | 24p   | AD151  | 40p   | MPSA12  | 42p   | T1P3055  | 69p |
| 2N3055    | 81p   | AD162  | 52p   | MPSA63  | 44p   | T1S43    | 40p |
| 2N3702-11 | 11p   | AF127  | 43p   | OA47    | 12p   | WQ2      | 35p |
| 2N4443    | £1.78 | AL102  | £1.94 | OA90    | 8p    | 2Tx107.9 | 14p |
| 2N4444    | £2.28 | BA379  | 29p   | OA91    | 8p    | 2Tx300   | 14p |
| 2N4931    | 98p   | BB103  | 43p   | OA202   | 16p   | 62Tx500  | 16p |
| 2N5457-9  | 45p   | BB104  | 70p   | OC29    | £1.23 |          |     |
| 40HF40    | £2.25 | BB105  | 37p   | OC36    | £1.18 |          |     |
| 40361     | 49p   | C106D1 | 52p   | T2800D  | £1.20 |          |     |
| 40362     | 49p   | E1110  | 92p   | T1P31A  | 52p   |          |     |
| 40636     | £1.69 | E1210  | 97p   | T1P32A  | 52p   |          |     |

**INFORMATION** - To show everything we supply would take about seven pages of closely packed type in this journal - the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 - OUR 120 PAGE CATALOGUE FREE FOR THE ASKING.

**PRICES AND V.A.T.** - All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

**POSTAGE** - For orders up to £5.75 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

**DISCOUNTS** - 5% allowed on non-net items if order value exceeds £11.50. 10% if order value exceeds £29. Quantity discount prices on most components.



**ELECTROVALUE LTD.** Dept. 28 St. Judea Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 284475.

Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.



Designed originally for logic wiring applications, it is now accepted and used extensively throughout industry, education and research. ROADRUNNER is used by hobbyists, students, technicians, designers and engineers to carry out:-

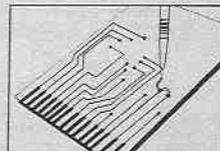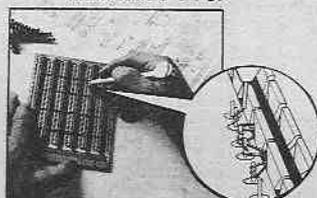- ★ PCB REPAIRS ★ ANALOGUE BREADBOARDING
- ★ SIMPLE LOGIC WIRING-PROJECTS
- ★ COMPLEX INTERCONNECTING OF MICROPROCESSORS, MEMORIES ETC.




PCB REPAIR

WIRING OF LOGIC, MICROS AND MEMORIES
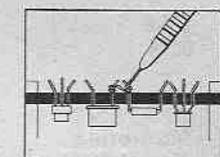
#### ROADRUNNER PRODUCTS

Euro Introkitt £15.73. Project Introkitt £8.80. Pencil loaded with Bobbin £2.44. Wire Distribution Strips. Glue fix 20 pkt. 8" long £2.80. Press fix 20 pkt. 2" long £2.82. Single Eurocard. High Density 3 Plane 36 x 16 pin DILS £4.50. Double Eurocard. High Density 3 Plane 84 x 16 pin DILS £7.25. Project Card. High Density S. Sided 20 x 14 pin DILS £2.65. Bobbins - Blue, 4/pkt £2.12. Green 4/pkt. £2.12. Pink 4/pkt. Gold 4/pkt. £2.12. 1 of each col. in pkt. £2.20. Tinned Copper Wire 4/pkt. £2.12. Adhesive £0.36/tube.



ANALOGUE BREADBOARDING

ACCESS & BARCLAY CARDS ACCEPTED  
DEALER ENQUIRIES WELCOME

Send large SAE for further details on ROADRUNNER products

To T. J. BRINE ASSOCIATES  
56b HIGH STREET, HASLEMERE, SURREY GU27 2LA  
PLEASE ADD 40p P & P PLUS VAT AT 15% TO ALL ORDERS

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City and Guilds Certificates:  
Telecommunications Technicians  
Radio, TV, Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
MPT Radio Communications Certificate

Diploma Courses:  
Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

**ICS** To: International Correspondence  
Schools

Dept U268 Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....  
Name .....  
Address .....  
Tel: ..... Age: .....



# New Bear Components



## Microcomputing IC's

|                |        |
|----------------|--------|
| MC6800         | £6.75  |
| MC6802         | £8.50  |
| MC6809         | £20.60 |
| MC6821         | £4.63  |
| MC6850         | £4.99  |
| MC6810AP       | £3.61  |
| MC6840         | £9.42  |
| Z80 CPU 2.5Mhz | £8.99  |
| Z80 PIO 2.5Mhz | £7.99  |
| Z80CTC 2.5Mhz  | £7.99  |
| Z80A P10 4Mhz  | £10.00 |
| Z80A CPU 4Mhz  | £13.99 |
| Z80A CTC 4Mhz  | £10.00 |
| SC/MP II       | £8.88  |
| INS8154N       | £8.18  |
| 8080A          | £6.00  |
| 6502           | £9.90  |
| 6522           | £7.90  |
| 6532           | £12.56 |
| 6551           | £10.79 |

## Memories

|                    |       |
|--------------------|-------|
| 4116 (16K Dynamic) | £6.99 |
| 2102-1*            | £0.85 |
| 2102L-1*           | £0.99 |

|            |        |
|------------|--------|
| 2112       | £2.25  |
| 2114       | £6.99  |
| 2708       | £6.99  |
| 2716 INTEL | £21.50 |

## SHARP

MZ80K ..... from £520.00

## ACORN

|                      |        |
|----------------------|--------|
| 6502 Based Micro Kit | £65.00 |
| PSU                  | £5.00  |
| V.D.U. Kit           | £88.00 |
| 8K RAM Kit           | £95.00 |

## ZEN

Editor/Assembler for Z80

Formats available:-

|          |        |
|----------|--------|
| standard |        |
| Nascom.1 |        |
| TRS.80   | £14.50 |

77-68 The low cost 6800 Micro now upgradable to 6809

|   |        |
|---|--------|
| 77-68 CPU Board Kit                       | £35.00 |
| 77-68 4K RAM Board Kit                    | £55.00 |
| 77-68 MON.1. Board Kit                    | £37.50 |
| 77-68 V.D.U. Board Kit                    | £42.50 |
| 77-68 MON.2 Board Kit                     | £47.50 |
| 77-68 EPROM Board Kit                     | £21.50 |
| 77-68 PIO Board Kit                       | £40.00 |
| 77-68 32K Dynaram Kit (with 16K Supplied) | £75.50 |

Disc Interface & 6809 boards available send for free system description.

## TERMS:

50p Postage and packing. Official orders (Min. £10). Access and Barclaycard welcome. Please add 15% VAT to all prices.

Send for catalogue and booklist.

Mail order & Callers:-40, Bartholomew Street, Newbury, Berkshire. Tel: (0635) 30505

Callers only:-220-222, Stockport Road, Cheadle Heath, Stockport. Tel. 061 491 2290

Newbear Components is a division of Newbear Computing Store Limited.

## VARI WIPE

### WIPER DELAY CONTROL

The Vari Wipe provides intermittent operation of the windscreen wipers with adjustable control to delay each wipe between 3 and 60 seconds. Set the control to suit the conditions to clear light drizzle, fog, snow, sleet or spray. Easily fitted to British, Continental & Japanese cars with 12 volt self park wipers. Complete kit contains all components, including timer chip, PCB, case, mounting panel, wire, etc., with full instructions.

VARI WIPE KIT £6.75 inc. P & P  
ASSEMBLED £9.25 inc. P & P

or send large s.a.e. for details



DEVELOPMENTS

Dept EE 2

Card Holders Phone 0253 27244

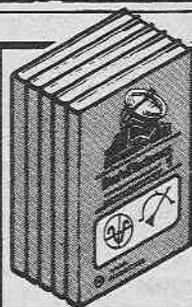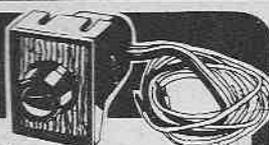**Spimin**

FREEPOST Thornton Cleveleys, Blackpool FY5 2BR



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages. Bound in stiff linen. Cover size 8 1/2" x 5 1/2". Price £8.50 per set (we pay the postage).

- Book 1. Introducing Electronics  
Book 2. Resistors/Capacitors  
Book 3. Inductors/Diodes  
Book 4. Meters/Voltage-dividers  
Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order now:  
Selray Book Company  
60 Hayes Hill  
Bromley  
BR2 7HP

### OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £

Name: \_\_\_\_\_

Address: \_\_\_\_\_

EE 21



## TOPS THE PACK!

**COMPONENTS** - Now over 1,000 types in stock.  
**MODULES** - New ready-built functions.  
**SERVICE** - 1st Class same day despatch.  
**QUALITY** - All guaranteed products.  
**PRICES** - Many reductions!  
**MAGAZINE PROJECTS** - Trouble-free!


"LET US QUOTE FOR YOUR HARD TO GET COMPONENTS - SHOP TALK ITEMS A SPECIALITY"

I enclose 30p\*, please send catalogue.

Name \_\_\_\_\_

Address \_\_\_\_\_

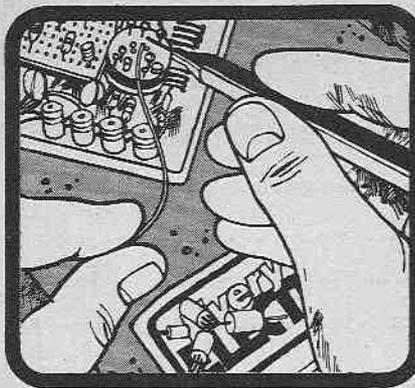\*Refundable with future orders over £5.00.



# CLASSIFIED

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £5.00 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury

notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## Receivers and Components

### NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state Transmitter-Receiver Kit. Only £10-95 plus 25p P. & P.

'Brain-Freeze' 'em with a MINI-STROBE Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere £4-75 plus 25p P. & P. Experiment with a psychedelic DREAM LAB, or pick up faint speech/sounds with the BIG EAR sound-catcher; ready-made multi-function modules. £5-45 each plus 25p P. & P.

LOTS MORE! Send 30p for lists. Prices include VAT.

### BOFFIN PROJECTS

4 CUNLIFFE ROAD, STONELEIGH  
EWELL, SURREY. (E.E.)

**DIGITAL WATCH BATTERIES**, any sort 75p each. Send SAE or 15p with number or old battery to Disclec, 511 Fulbridge Road, Werrington, Peterborough PE4 6SB.

**DISCOVER ELECTRONICS**. Build forty easy projects including: Metal Detector; Breathalyser; Radios; Stethoscope; Lie Detector; Touch time-switches; Burglar Alarms, etc. Circuits, plans all for £1-50 including FREE circuit board. Mail only. RIDLEY PHOTO/ELECTRONICS, Box 62, 111 Rockspark Road, Uckfield, Sussex.

100 DIODES 85p, 50 Transistors 95p, 10 switches 90p, 10 Leds £1-15. All mixed. Lists 15p. SOLE ELECTRONICS, E/E, 37 Stanley Street, Ormskirk, Lancs L39 2DH.

**TURN YOUR SURPLUS** capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs, 0945 4188. Immediate settlement.

## Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Rd, Harrogate, N. Yorkshire. Tel: 0423 55885.

SERVICE SHEETS from 50p and SAE. Catalogue 25p and SAE. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

## For Sale

**NEW BACK ISSUES** of "EVERYDAY ELECTRONICS". Available 75p each Post Free, open PO/Cheque returned if not in stock. BELL'S TELEVISION SERVICES 190 Kings Road, Harrogate, Yorkshire. Tel: (0423) 55885.

## Record Accessories

STYL, CARTRIDGES FOR MUSIC CENTRES &c. FREE List No. 29. For S.A.E. includes Leads, Mikes, Phones, etc. FELSTEAD ELECTRONICS (EE), LONGLEY LANE, GATLEY, CHEADLE, CHES SK8 4EE.

## Books and Publications

### WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS

A genuine opportunity to success. LARGE PROFITS. You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated Manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. NO PREVIOUS KNOWLEDGE IS REQUIRED, as the Manual covers in 13 Chapters, where to obtain all the work you need, materials required, all instructions re wind charts and how to take data, etc. A goldmine of information. How to set up your home workshop and how to coat each job to your customer. £4-50 inclusive of P. & P. U.K. CWO to:

### INDUSTRIAL SUPPLIES

102 Parrswood Road, Withington,  
Manchester 20, Dept. EE

## Wanted

**WANTED: ELECTRONIC COMPONENTS**, Redundant Stock, Test Equipment, Tools, Machines, Hardware; Factories cleared. Immediate cash decision. Contact: Mr. Quirk, "Q" Services Electronic (Camberley) Ltd, 29 Lawford Crescent, Yateley 871048, Camberley, Surrey.

## Miscellaneous

**TUNBRIDGE WELLS COMPONENTS**, BALLARD'S, 108 Camden Road, Tunbridge Wells, Phone 31803. No lists, enquiries S.A.E.

### AERIAL BOOSTERS

Improves weak VHF Radio and Television reception. B45-UHF TV, B11-VHF Radio, B11A-2 metres. For next to the set fitting. Price £6.

### SIGNAL INJECTOR

A complete range of A.F. and R.F. Frequencies up to the UHF Band, (variable AF). Price £5-00.

S.A.E. for leaflets—Access.

**ELECTRONIC MAILORDER LTD**,  
62 Bridge Street,  
Ramsbottom, Bury, Lancs. BL0 9AG.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E4.  
Reg. Office, 22 Coningsby Gardens.

### ENAMELLED COPPER WIRE

| SWG      | 1 lb  | 8 oz | 4 oz | 2 oz |
|----------|-------|------|------|------|
| 10 to 24 | 3-10  | 1-86 | 1-10 | ·80  |
| 30 to 34 | 3-50  | 2-00 | 1-15 | ·80  |
| 35 to 39 | 3-95  | 2-36 | 1-34 | ·98  |
| 40 to 42 | 5-10  | 2-97 | 2-28 | 1-42 |
| 44 to 46 | 6-00  | 3-60 | 2-50 | 1-91 |
| 47       | 8-87  | 5-32 | 3-19 | 2-50 |
| 48 to 49 | 15-95 | 9-58 | 6-38 | 3-88 |

### SILVER PLATED COPPER WIRE

|          | 5-30 | 3-03 | 1-85 | 1-20 |
|----------|------|------|------|------|
| 14 to 22 | 6-50 | 3-75 | 2-20 | 1-40 |

Prices include P&P and VAT. Orders under £2 please add 20p SAE for list. Dealer enquiries welcome. Reg office 22 Coningsby Gardens.

FREE 1980 AMTRON CATALOGUE with new range of kits and equipment cabinets. Send SAE. Amtron UK Ltd., 7 Hughenden Road, Hastings, Sussex TN34 3TG. Tel: Hastings 436004.

## DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener, full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send £7-50 for complete kit and get into a fast growing business. Prompt despatch.

WATCH BATTERY REPLACEMENT CO. (EE 14)  
11 Percy Avenue, Ashford, Middx., TW15 2PB

PLEASE  
MENTION

EVERYDAY  
ELECTRONICS

WHEN  
REPLYING  
TO

ADVERTISEMENTS



# TRANSFORMERS Continuous Ratings + VAT 15%

**30 VOLT RANGE**  
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

| Ref | Amps | Price | P & P |
|-----|------|-------|-------|
| 112 | 0.5  | 2.99  | 0.90  |
| 78  | 1.0  | 3.33  | 1.10  |
| 3   | 2.0  | 6.35  | 1.10  |
| 20  | 3.0  | 6.82  | 1.31  |
| 21  | 4.0  | 8.79  | 1.31  |
| 51  | 5.0  | 10.86 | 1.52  |
| 117 | 6.0  | 12.93 | 1.67  |
| 88  | 8.0  | 16.45 | 1.89  |
| 89  | 10.0 | 18.98 | 1.89  |
| 90  | 12.0 | 21.99 | 2.24  |
| 91  | 15.0 | 24.18 | 2.39  |
| 92  | 2.0  | 32.40 | O.A.  |

**50 VOLT RANGE**  
Sec Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

| Ref | Amps | Price | P & P |
|-----|------|-------|-------|
| 102 | 0.5  | 2.75  | 0.90  |
| 103 | 1.0  | 3.57  | 1.10  |
| 104 | 2.0  | 7.88  | 1.31  |
| 105 | 3.0  | 9.42  | 1.57  |
| 106 | 4.0  | 12.82 | 1.75  |
| 107 | 6.0  | 16.37 | 1.99  |
| 118 | 8.0  | 22.29 | 2.39  |
| 119 | 10.0 | 27.48 | O.A.  |
| 109 | 12.0 | 32.89 | O.A.  |

**MAINS ISOLATORS (Screened)**  
Sec 120/240 Sec 120/240V CT

| Ref | VA   | Price | P & P |
|-----|------|-------|-------|
| *07 | 20   | 4.84  | 0.91  |
| 149 | 60   | 7.37  | 1.10  |
| 150 | 100  | 8.38  | 1.31  |
| 151 | 200  | 12.28 | 1.31  |
| 152 | 250  | 14.61 | 1.73  |
| 153 | 350  | 18.07 | 2.12  |
| 154 | 500  | 22.52 | 2.47  |
| 155 | 750  | 32.03 | O.A.  |
| 156 | 1000 | 40.92 | O.A.  |
| 157 | 1500 | 56.52 | O.A.  |
| 158 | 2000 | 67.99 | O.A.  |
| 159 | 3000 | 95.33 | O.A.  |

\*Pri 0-220-240V Sec 115 or 240V.

**CASED AUTO TRANSFORMERS**  
115V USA earthed flat pin socket outlets.

| VA   | Price | P & P | Ref |
|------|-------|-------|-----|
| 20   | 6.55  | 1.04  | 56W |
| 75   | 8.59  | 1.31  | 64W |
| 150  | 11.06 | 1.31  | 4W  |
| 250  | 12.55 | 1.67  | 69W |
| 500  | 20.13 | 1.89  | 67W |
| 1000 | 38.67 | 2.65  | 84W |
| 1500 | 42.82 | O.A.  | 93W |
| 2000 | 54.97 | O.A.  | 95W |

**EDUCATIONAL METERS**  
(Moving Coil)  
0-10A (0-1A)  
0-15V  
0-30V. Free standing large scale easily read meters with top screw terminals for quick connections. The 10A current meter can be shunted to give 0-1 amp. £4.50 PP 66p + VAT.

**12 OR 24V OR 12-0-12V**  
Pri 220-240 volts

| Ref | Amps | 12V  | 24V   | Price | P & P |
|-----|------|------|-------|-------|-------|
| 111 | 0.5  | 0.25 | 2.42  | 0.52  |       |
| 213 | 1.0  | 0.5  | 2.90  | 0.90  |       |
| 71  | 2    | 1    | 3.88  | 0.90  |       |
| 18  | 4    | 2    | 4.46  | 1.10  |       |
| 85  | 5    | 2.5  | 6.16  | 1.10  |       |
| 70  | 6    | 3    | 6.99  | 1.10  |       |
| 108 | 8    | 4    | 8.16  | 1.31  |       |
| 72  | 10   | 5    | 8.93  | 1.31  |       |
| 116 | 12   | 6    | 9.89  | 1.52  |       |
| 117 | 16   | 8    | 11.79 | 1.37  |       |
| 115 | 20   | 10   | 15.38 | 2.39  |       |
| 187 | 30   | 15   | 19.72 | 2.39  |       |
| 226 | 60   | 30   | 40.41 | O.A.  |       |

**TEST METERS P & P £1.15 15% VAT**

|               |       |
|---------------|-------|
| AVO 8 MK5     | 91.50 |
| AVO 71        | 38.60 |
| AVO 73        | 50.70 |
| AVO MMS minor | 35.85 |
| Wee Megger    | 78.25 |

**Special Offer—Multimeter (20KΩ with combined audio/IF test oscillator at 1KHz and 465 KHz. AC/DC to 1000 volts. DC current to 500 mA. resistance to 1KΩ. Size 160 x 97 x 40mm. £28.50 P & P. £1.00. VAT 15%.**

**SCREENED MINIATURES Primary 240V**

| Ref | mA       | Volts        | £    | P&P |
|-----|----------|--------------|------|-----|
| 238 | 200      | 3-0-3        | 2.83 | 63  |
| 212 | 1A, 1A   | 0-5, 0-6     | 3.14 | 90  |
| 13  | 100      | 0-0-8        | 2.35 | 44  |
| 235 | 330, 330 | 0-9, 0-9     | 2.19 | 44  |
| 207 | 300, 500 | 0-8-8, 0-8-9 | 3.05 | 85  |
| 208 | 1A, 1A   | 0-8-8, 0-8-9 | 3.88 | 90  |
| 236 | 200, 200 | 0-15, 0-15   | 2.19 | 44  |
| 239 | 50       | 12-0-12      | 2.83 | 37  |
| 214 | 300, 300 | 0-20, 2-20   | 3.08 | 90  |

**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-498 3316/7/8  
Nearest Tube Stations: Aldgate & Liverpool St.

# KITS FOR E.E. PROJECTS

|                                 |        |          |        |
|---------------------------------|--------|----------|--------|
| SLIDE TAPE SYNCHRONISER         | (ZB42) | Feb 80   | £11.50 |
| VARICAP RADIO                   | (ZB1)  | Sept 79  | £8.50  |
| TRANSISTOR TESTER               | (ZB2)  | Sept 79  | £5.00  |
| ONE ARMED BANDIT                | (ZB33) | Oct 79   | £21.00 |
| MORSE PRACTICE OSCILLATOR       | (ZB43) | Feb 80   | £6.00  |
| WARBLING TIMER                  | (ZB5)  | Aug 79   | £5.80  |
| MODULATED TONE GENERATOR        | (ZB50) | Dec 79   | £3.50  |
| ELECTRONIC TUNING FORK          | (ZB7)  | Aug 79   | £8.90  |
| MICRO MUSIC BOX                 | (ZB45) | Feb 80   | £17.00 |
| DARK ROOM TIMER                 | (ZB17) | July 79  | £2.50  |
| UNIBORAD BURGLAR ALARM          | (ZB51) | Dec 79   | £5.00  |
| SIGNAL LEVEL INDICATOR (stereo) | (ZB36) | Oct 79   | £4.50  |
| UNIBORAD 9V POWER SUPPLY        | (ZB47) | Jan 80   | £4.50  |
| TREMULO UNIT                    | (ZB18) | June 79  | £10.00 |
| ELECTRONIC CANARY               | (ZB19) | June 79  | £4.50  |
| SIMPLE S.W. RECEIVER            | (ZB44) | Feb 80   | £18.00 |
| INTRUDER ALARM                  | (ZB23) | May 79   | £23.00 |
| ELECTRONIC DICE                 | (ZB24) | May 79   | £13.50 |
| MAINS ON/OFF TIMER              | (ZB48) | Jan 80   | £30.00 |
| BABY ALARM                      | (ZB40) | Nov 79   | £8.50  |
| LOFT ALERT                      | (ZB46) | Jan 80   | £33.00 |
| CHASER LIGHT                    | (ZB4)  | Sept 79  | £17.50 |
| SHORT WAVE CONVERTER            | (ZB25) | May 79   | £13.75 |
| TOUCH BLEEPER                   | (ZB27) | April 79 | £3.25  |
| FUNCTION GENERATOR              | (ZB52) | Nov 79   | £25.00 |
| OPTO ALARM                      | (ZB41) | Nov 79   | £5.00  |
| POWER SUPPLY 9V                 | (ZB6)  | Aug 79   | £8.25  |
| SWANEY WHISTLER                 | (ZB8)  | Aug 79   | £3.50  |
| REVERB UNIT                     | (ZB49) | Jan 80   | £29.00 |

All above kits include parts as described in articles i.e. veroboard, i.c. sockets connecting wire and cases where applicable.

## TEACH-IN '80

New to electronics? Then start at the beginning. All electronic components for construction of Tutor Deck and Teach-In experiments during the first six parts of the series.

Lists A and B £20.00

List C £2.50

**ALL PRICES INCLUDE V.A.T.**  
**BARCLAY/VISA/ACCESS CARDS ACCEPTED.**  
**MINIMUM TELEPHONE ORDER £5.00.**

## T. POWELL

306, ST. PAUL'S ROAD, LONDON N.1.

TELE: 01-226 1489.

SHOP HOURS: MON.—FRI. 9AM—5.30PM. SATURDAY 9AM—4.30PM

## INDEX TO ADVERTISERS

|                                     |           |
|-------------------------------------|-----------|
| Ace Mailtronix                      | 381       |
| A.J.D.                              | 310       |
| Absongen Ltd.                       | 376       |
| Ambit                               | 305       |
| Arrow Electronics                   | 364       |
| Barrie Electronics                  | 384       |
| Bi-Pak                              | 312 & 313 |
| Birkett J.                          | 372       |
| B.N.R.E.S.                          | 373       |
| Brine Assoc.                        | 380       |
| Bull J.                             | 377       |
| Cambridge Learning                  | 369       |
| Chromatronics                       | 364       |
| Continental Specialties Corporation | Cover 2   |
| Eddystone                           | 368       |
| Electronic Design Associates        | 306       |
| Electrovalue                        | 380       |
| George Sales, David                 | 366       |
| Greenweld                           | 310       |
| Home Radio                          | 372       |
| I.L.P. Electronics                  | 378 & 379 |
| Intertext (ICS)                     | 380       |

|                                 |               |
|---------------------------------|---------------|
| Magenta Electronics             | 307           |
| Maplin Electronic Supplies Ltd. | 311 & Cover 4 |
| Marshall A.                     | 360           |
| Meca                            | 383           |
| Menocrest                       | 374           |
| Metac                           | 308 & 309     |
| Midland Trading                 | 366 & 375     |
| Newbear                         | 381           |
| Phononics                       | 372           |
| Powell T.                       | 384           |
| R & T.V. Components             | 363           |
| Radio Component Specialties     | 376           |
| Science of Cambridge            | 370 & 371     |
| Selray Book Co.                 | 381           |
| Spimin                          | 381           |
| Stevenson C. N.                 | 347           |
| Swanley Electronics             | 372           |
| Tandy                           | Cover 3       |
| Technomatic                     | 374           |
| Tempus                          | 359           |
| T.K. Electronics                | 368           |
| Vero Electronics                | 360           |
| Watford Electronics             | 357           |
| West London Direct Supplies     | 384           |
| Wilmslow Audio                  | 374           |

## MAINS INTERCOM



**NO BATTERIES NO WIRES ONLY**  
**£36.99**  
PER PAIR  
+ VAT £5.55

The modern way of instant 2-way communications. Just plug into power socket. Ready to use. Crystal clear communications from room to room. Range 1-mile on the same mains phase. On/off switch. Volume control, with 'buzzer' call and light indicator. Useful as inter-office intercom, between office and warehouse, in surgery and in homes. P. & P. £1.80.

**4-STATION INTERCOM £31.95**  
+ VAT £4.80

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs) in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. A battery and other accessories. P. & P. £1.60.

## TELEPHONE AMPLIFIER



**£18.95**  
+ VAT £2.85  
+ P & P £1.15

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase calls; leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume control, conversation recording model at £20.95 + VAT = £3.15. P. & P. £1.15p.

## DOOR ENTRY SYSTEM

No house/business/surgery should be without a DOOR ENTRY SYSTEM in this day and age. The modern way to answer the door in safety to unwanted callers. Talk to the caller and admit him only if satisfied by pressing a remote control button which will open the door electronically. A boom for the invalid, the aged and busy housewife. Supplied complete d.i.y. kit with one Internal Telephone, outside Speaker panel, electric door lock release (for Yale type surface latch lock), mains power unit, cable (8-way) 50 ft and wiring diagram. Price £49.95 + VAT £7.50 + P. & P. £1.85. Kit with two Telephones £59.95 + VAT £9.00 + P. & P. £1.95.

10-day price refund guarantee on all items.

WEST LONDON DIRECT SUPPLIES (E.E.4)  
169 KENSINGTON HIGH STREET, LONDON, W8

# The Logic Probes

## Spend Less

## Test More



### LP-1 Logic Probe

The LP-1 has a minimum detachable pulse width of 50 nanoseconds and maximum input frequency of 10MHz. This 100 K ohm probe is an inexpensive workhorse for any shop, lab or field service tool kit. It detects high-speed pulse trains or one-shot events and stores pulse or level transitions, replacing separate level detectors, pulse detectors, pulse stretchers and pulse memory devices.

All for less than the price of a DVM

**£31.00\***



### LP-2 Logic Probe

The LP-2 performs the same basic functions as the LP-1, but, for slower-speed circuits and without pulse memory capability. Handling a minimum pulse width of 300 nanoseconds, this 300 K ohm probe is the economical way to test circuits up to 1.5 MHz. It detects pulse trains or single-shot events in TTL, DTL, HTL and CMOS circuits,


replacing separate pulse detectors, pulse stretchers and mode state analysers.

(Available in kit form LPK-1 £11.92)

**£18.00\***

The logic probes shown are all suitable for TTL, DTL, HTL and CMOS circuits.

\*price excluding P.&P. and 15% VAT

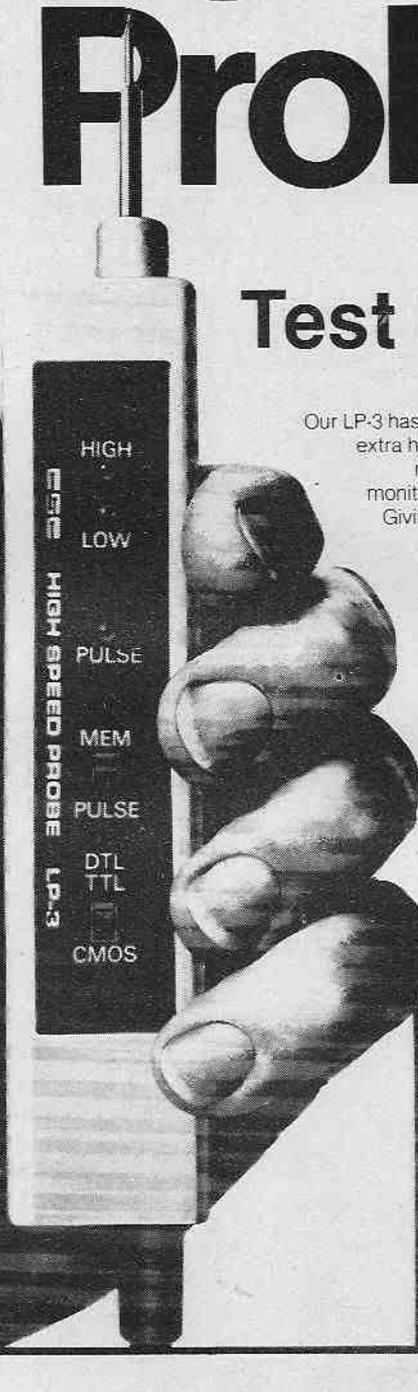

### LP-3 Logic Probe

Our LP-3 has all the features of the LP-1 plus extra high speed. It captures pulses as narrow as 10 nanoseconds, and monitors pulse trains to over 50 MHz. Giving you the essential capabilities of a high-quality memory scope at 1/1000th the cost.

LP-3 captures one shot or low-rep-events all-but-impossible to detect any other way.

All without the weight, bulk, inconvenience and power consumption of conventional methods.

**£49.00\***




### The New Pulser DP-1

The Digital Pulser: another new idea from C.S.C. The DP-1 registers the polarity of any pin, pad or component and then, when you touch the 'PULSE' button, delivers a single no-bounce pulse to swing the logic state the other way. Or if you hold the button down for more than a second, the DP-1 shoots out pulse after pulse at 1000 Hz.

The single LED blinks for each single pulse, or glows during a pulse train. If your circuit is a very fast one, you can open the clock line and take it through its function step by step, at single pulse rate or at 100 per second. Clever! And at a very reasonable price.

**£51.00\***

CONTINENTAL SPECIALTIES CORPORATION

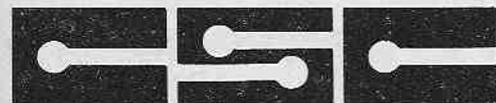

C.S.C. (UK) Limited,  
Dept.411, Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477

C.S.C. (UK) Ltd., Dept.411, Unit 1, Shire Hill Industrial Estate, Saffron Walden Essex CB11 3AQ  
Prices include P.&P. and 15% VAT

|      |        |      |      |        |      |      |        |      |      |        |      |       |        |      |
|------|--------|------|------|--------|------|------|--------|------|------|--------|------|-------|--------|------|
| LP-1 | £37.38 | Qty. | LP-2 | £22.14 | Qty. | LP-3 | £58.08 | Qty. | DP-1 | £60.38 | Qty. | LPK-1 | £14.86 | Qty. |
|------|--------|------|------|--------|------|------|--------|------|------|--------|------|-------|--------|------|

Name \_\_\_\_\_ Address \_\_\_\_\_

I enclose Cheque/P.O. for £ \_\_\_\_\_ or debit my Barclaycard/Access/  
American Express card no \_\_\_\_\_ exp date \_\_\_\_\_

**FOR IMMEDIATE ACTION** — The C.S.C. 24 hour, 5 day a week service  
Telephone (0799) 21682 and give us your Barclaycard, Access, American Express  
number and your order will be in the post immediately

for FREE  
catalogue  
tick box

# STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy  
and **STEP UP TO  
MAPLIN SERVICE  
NOW**




Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

EE 5/80

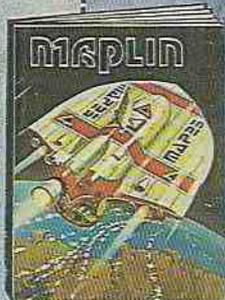

## **MAPLIN**

**ELECTRONIC SUPPLIES LTD**

All mail to:

**P.O. Box 3, Rayleigh, Essex SS6 8LR.**

**Telephone: Southend (0702) 554155.**

**Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).**

**Telephone: Southend (0702) 554000.**